

JANUARY 1985

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50


£1.00

BEER N' AGENCY  
6 \$1.80  
BARELY ST., F'CRAY

# TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

## Simple Pattern Generator

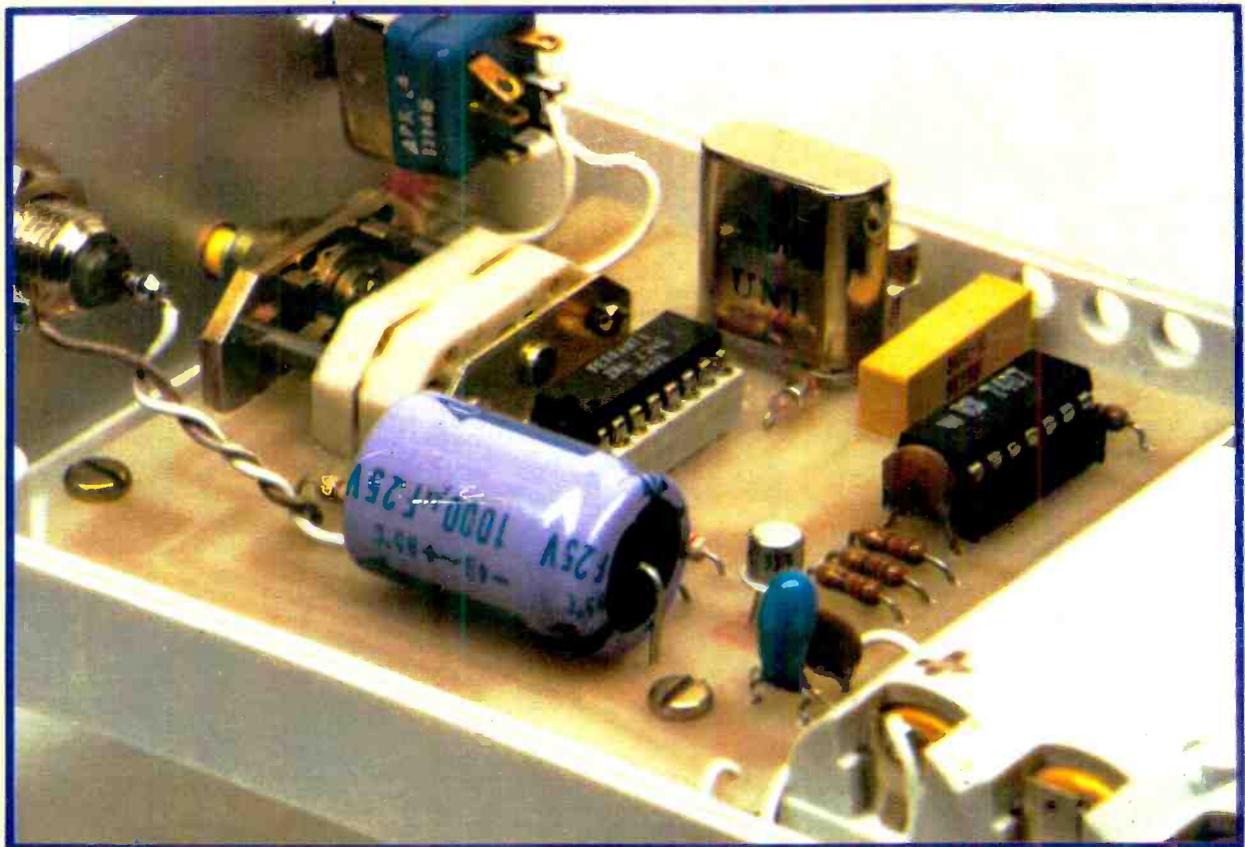


**The VHS Hi-Fi Sound System**  
**Servicing the s-s Indesit T24**  
**Test Report • Christmas Lights**  
**Goodbye to 405 • DX-TV**  
**VCR Clinic • TV Fault Finding**
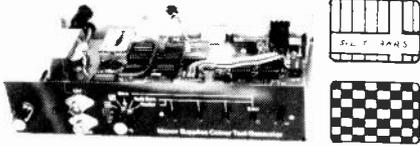
# MANOR SUPPLIES

NEW MKV PAL COLOUR  
TEST GENERATOR FOR TV & VCR.

TEST  
DEMONSTRATIONS  
AT 172  
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**  
De Luxe Case (10"×6"×2¼") **£7.40**  
Optional Sound Module (6MHz or 5.5MHz) **£3.90**  
Built & Tested in De Luxe Case including Sound Module **£105.00**

SPECIAL TEST  
REPORT  
'TELEVISION'  
DEC. 1982

Post/Packing £2.50  
Add VAT 15% TO ALL PRICES

## PAL COLOUR BAR GENERATOR (Mk4)

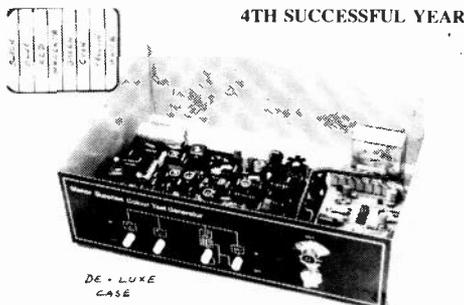

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£30.00**. DELUXE CASE **£7.40**. BATT HOLDERS **£2.80**. MAINS SUPPLY KIT **£4.20** (Combined P&P **£2.20**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£58.00** + **£2.20** P & P.  
MK 4 DE LUXE (MAINS) BUILT & TESTED **£68.00** + **£2.20** P & P.  
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75**.  
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.  
(ADD VAT 15% TO ALL PRICES)

TELETEXT EXTERNAL ADAPTOR KIT (Less case)  
with cable remote control **£120.00**

THORN TX10, PHILIPS G11  
Mullard Teletext Decoder + Interface panels suitable for either the above **£50.00**

Additional Prestel units including line coupler **£50.00** p.p **£2.50**

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

## TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

LOPTS, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

### SPECIAL OFFER NEW VALVES

- Branded makes, PCF80, PY88, PFL200, PCL84 FOUR for **£2.00** p.p. 80p.
- THORN TX10 Facia Control Panel incl. Infra Red Remote Control receiver **£7.50** p.p. £1.50.
- THORN TX10 type Remote & Tuning Control Panel **£9.40** p.p. £1.50.
- THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£5.00** p.p. £1.50.
- PHILIPS UHF Modulator (Audio & Video Input) **£15.00** p.p. £1.00.
- SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50** p.p. £1.20.
- THORN TX9, TX10 Saw Filter IF Panel. **£7.50** p.p. 80p.
- PAL DECODER KIT for RGB Monitors **£27.00** p.p. £1.00.
- SPECIAL OFFER TEXAS XM11 Teletext Decoder New & Tested at reduced price. **£40.00** p.p. £1.60.
- TELETEXT 23 Button De-Luxe Handset with 5 yds Cable. **£6.80** p.p. £1.20.
- XM11 Stab. Power Supply. **£3.80** p.p. £1.20.
- CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. 80p. (Alum. Case **£2.55**, De Luxe Case **£6.80** p.p. £1.40). ADDITIONAL GREY SCALE Kit **£2.90** p.p. 45p.
- UHF SIGNAL STRENGTH METER KIT **£20.00** (VHF version **£22.00**). Alum. Case **£2.55**, De Luxe Case **£7.40** p.p. £1.80.
- CRT TESTER & REACTIVATOR PROJECT KIT For Colour & Mono **£28.00** p.p. £2.80.
- BUSH Z718 BC6100 series IF Panel **£5.00** p.p. 90p.
- BUSH A816 IF Panel (Surplus) **£1.65** p.p. 90p.
- DECCA 80 Series IF. Frame, T.B. **£5.00** p.p. £1.40.
- GEC 2040 Convergence Panels, Decoder Panels. **£2.50** p.p. £1.80.
- GEC 2040 IF Panels **£2.80** p.p. £1.60.
- GEC 2110 PANELS Frame **£8.50**, Preset (Touch Tune) Control **£5.00**, Convergence **£5.00**, p.p. £1.80.
- GEC "20AX" Series Switch Mode Power Supply **£5.00** p.p. £1.80.
- PYE 691-7 CDA Panels. Makers tested stock. **£6.00** p.p. £1.45.
- THORN TX9 Panels ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.00** p.p. £2.00.
- THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00** p.p. £2.80.
- THORN TX9 Panels ex factory salvaged complete cond. **£20.00** p.p. £2.80.
- THORN TX10 T.B. Panels salvaged ex factory. **£15.00** p.p. £3.00.
- THORN TX10 IF/Decoder Panels salvaged ex factory. **£15.00** p.p. £2.00.
- THORN 3000/3500 Power supply P.C.B. **£3.50** p.p. £1.00.
- THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. £1.80.
- THORN 8000/8500 Frame T.B. Panels salvaged/spares **£2.50** p.p. £1.40.
- THORN 9000 IF/Decoder Panels Salvaged. **£5.00** p.p. £1.60.
- THORN 9000 Series. Long panel facia unit incl. 6 Position Channel Selector & Loudspeaker **£6.00** p.p. £2.00.
- PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50** p.p. £1.60.
- G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00** p.p. £2.50.
- G11 PANELS, Power, Frame, IF, Decoder. **£18.00** each. p.p. £2.00.
- GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. £1.00.
- VARICAP. U321, U322, ELC1043/5 **£7.80** p.p. 80p. Makers Varicap Controls PYE CT200 4PSN **£7.50**, BUSH 4PSN **£4.80**, DECCA 4PSN **£5.80**, 6PSN **£6.80** p.p. 80p. etc.
- SPECIAL OFFER ELEVEN POSITION Varicap Control Unit UHF/VHF **£1.80** p.p. £1.00.
- BUSH "TOUCH TUNE" Varicap Control Z179, Z718 types **£3.80** p.p. 95p.
- VARICAP UHF-VHF ELC2000S **£9.80**, BUSH **£7.80** p.p. 90p.
- VARICAP VHF PHILIPS. **£6.90** p.p. 80p.
- UHF/625 TUNERS, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. £1.80.
- TV SOUND IF Panels **£6.80** p.p. £1.00.
- LOPT TESTER, Service Dept approved **£15.90** p.p. £1.20.
- LOPTS New and guar. P/P Mono **£1.35**, Colour **£1.50**, Bobbins 80p.

BUSH 161 to 186 (twin panel) .....	£5.90	R.B.M. A823 .....	£4.90
BUSH, MURPHY 774 series .....	£8.50	R.B.M. Z179 .....	£9.80
BUSH, MURPHY A816 series .....	£8.50	R.B.M. T20, T22 .....	£9.80
FERG., HMV, MARCONI, ULTRA		R.B.M. 120, T22 Bobbin .....	£5.60
1400, 1500, 1590, 1591 .....	£5.90	DECCA Bradford (state Mod No.) .....	£8.80
THORN 1600, 1615, 1690, 1691 .....	£9.15	DECCA 80, 100 .....	£8.80
GEC 2000 to 2038 series .....	£6.80	GEC 2028, 2040, 2100 .....	£5.80
GEC series 1 & 2 .....	£8.00	GEC 2110 series .....	£10.60
INDESIT 2024/EGB .....	£7.65	ITT CVC 5 to 9, CVC20 .....	£9.80
ITT/KB VC200, 300 .....	£7.65	ITT CVC25, CVC30 series .....	£8.80
MURPHY 1910 to 2414 (twin panel) .....	£5.90	PYE 691-697 (state model no.) .....	£10.00
PHILIPS 170, 210, 300 series .....	£7.65	PYE 713, 715 .....	£6.80
PYE, INVICTA, EKCO, FERR.		PYE 725 (907) 731 to 741 .....	£9.20
368, 169, 569, 769 series .....	£7.65	PHILIPS G8 .....	£8.80
		PHILIPS G9 .....	£10.80
SPECIAL OFFER		PHILIPS 570, 571 .....	£6.80
DECCA 2024, 1700, 2000, 2401 .....	£3.80	PHILIPS K13 .....	£12.50
GEC 2114/Junior FineLine .....	£2.80	THORN 3000/3500 SCAN, EHT .....	£6.90
PYE 40, 67 .....	£1.75	THORN 8000/8500/8800 .....	£12.90
KB VC ELEVEN (003) .....	£1.75	THORN 9000 to 9600 .....	£12.90
KB VC1 .....	£2.80		

### OTHERS AVAILABLE. PRICES ON REQUEST. ALSO LOPTS.

TRIPLERS Full range available. Mono & Colour.  
Special Offer: Thorn 8000 (2 lead) EHT Tray **£2.80** p.p. 80p.  
TRANSFORMERS suitable for G8, A823, Bradford etc. **£1.50** p.p. 60p.  
6.3V CRT Boost Transformers for Colour & Mono **£5.40** p.p. £1.20.  
THORN TX10 focus control **£8.80** p.p. 80p.  
THORN 8000 mains input choke **£6.80** p.p. £1.40.  
CALLERS WELCOME AT SHOP PREMISES  
THOUSANDS OF ADDITIONAL ITEMS. ENQUIRIES INVITED  
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS  
TELEVISION MAGAZINE PROJECT PARTS & REPLACEMENTS  
STILL AVAILABLE

Telephone 01-794 8751, 794 7346

## MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)  
W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD VAT 15% TO ALL PRICES



# TELEVISION

## SUBSCRIPTION SERVICE

A TV licence enables a householder to enjoy viewing without fear of interruption by callers from the BBC detector van. In the same way a subscription to Television enables you to update yourself on the latest developments without fear of interruption because copies have been sold out.

A regular subscription overcomes this problem. You know how annoying it can be when you have a gap in an important series of monthly articles. Why not avoid sell-out disappointment by arranging for Television to be delivered to you direct from the publisher? Just fill in the the order form overleaf and post in the addressed envelope attached. Then leave us to do the rest.

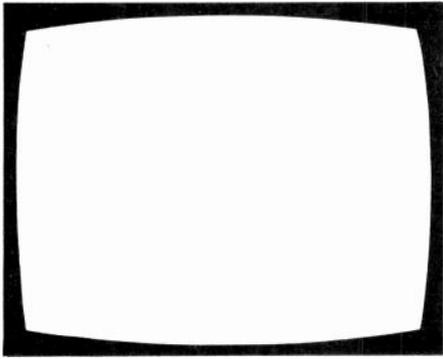
### GIFT SUBSCRIPTIONS

A subscription to Television makes an ideal gift for someone in the same line as yourself. All you have to do is complete the appropriate section of the order form and post in the same way. When we receive it, then we take over. We'll even send a card announcing your gift with your own personal message on it.

**TELEVISION**  
**Subscription Service**  
**...we'll keep you posted.**







# TELEVISION

January  
1985

Vol. 35, No. 3  
Issue 411

## COPYRIGHT

© IPC Magazines Limited, 1985, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

## SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

## BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

## BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 129 Leader**
- 130 Teletopics**
- 135 Christmas Lights** *William Harrison*  
How to get the travelling light effect with a sequencer and strings of LEDs.
- 136 VCR Clinic**  
Reports on VCR faults and servicing from Derek Snelling, Steve Beeching, T. Eng., Dewi James, Philip Blundell, Eng. Tech., Keith Hamer and Garry Smith.
- 138 My friend Jim** *Les Lawry-Johns*  
Jim's more interested in building than TV servicing, so what does he do with sets he doesn't like the look of?
- 139 Letters**
- 141 Next Month in Television**
- 142 Long-distance Television** *Roger Bunney*  
Reports on DX conditions and reception plus news and an investigation into wideband inductive combiners/splitters.
- 145 Test Report: Tele-Part Pattern Generators** *Eugene Trundle*
- 146 TV Fault Finding**  
Notes on TV faults from Malcolm Burrell, Philip Blundell, Eng. Tech., Chris Avis, Paul Hardy, Keith Hamer and Garry Smith.
- 150 Simple Pattern Generator** *Barry J. Thurlow*  
An inexpensive video/TV pattern generator based on the Ferranti ZNA234E chip. Fits into a small Verobox and provides grey-scale, peak white, crosshatch, dot, vertical line and horizontal line displays.
- 151 Suspect Transistors** *George Wilding*  
You may think that the transistor in a faulty stage is the obvious suspect but may well be wrong.
- 152 Goodbye to 405 lines** *Pat Hawker*  
This month sees the end of the system that's served the UK since 1936. A fond farewell.
- 153 Postscript on 405** *Nick Lyons*
- 154 Video Servicing** *Mike Phelan*  
A look at camera electronics.
- 156 Servicing the solid-state Indesit T24EGB** *Mike Phelan*  
A set with some unusual circuitry but fairly predictable faults.
- 158 Colour Bar Program** *G. J. Phillips, B.Sc., C.Eng.*  
How to get colour bars from the BBC Model B microcomputer.
- 158 MISFITS** *Richard Roscoe*  
Multiple independently sited faults in TV sets!
- 159 Book Notice**
- 160 VHS Hi-Fi Sound** *Derek Snelling*  
How the new VCR hi-fi sound systems work, with particular reference to the Panasonic NV830/NV850.
- 162 Service Bureau**
- 163 Test Case 265**

OUR NEXT ISSUE DATED FEBRUARY WILL  
BE PUBLISHED ON JANUARY 16

# P. V. TUBES

## HAVE MOVED

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.

Buy with

Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521  
Accrington (0254) 32611  
Telex: 635562 Griffin G (For P.V.)

SUPPLIERS OF TELEVISION COMPONENTS

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

VARICAP TUNERS	SWITCHES & ACCESS.	OIO YOU KNOW WE'VE GOT LOTS OF NEW THINGS!	PHILIPS KT3 SPECIFICS	SPECIFIC COMPONENTS
ELC1043-05 8.40 ELC1043-06 8.40 ELC2003 16.50 Philips G8/G9 10.50 Philips G11 (U321) 8.50 U322 7.20 U341 9.50 Rank T20 13.00	On/off gen. purpose 4A 75 G8 on/off 1.38 G11 on/off 1.58 G11 on/off remote 1.58 Gen. purpose rotary 66 Thom Tx 9/10 1.06 GEC 2040 98 Thom 1591 push on/off 2.90 Rank tuner buttons 1 1/2" x 1/2", 2" x 1/2", 2" x 3/8" Rank drive cams 35 GEC 2110 tuner neons 15 Thom 3500 A1 beam 14 GEC 2110 A1 cont. R/B/G 70 ITT CVCS on/off 58 ITT CVCS on/off 1.24 ITT mains switch + solenoid 4.50 Rank mains switch + solenoid 4.50	Decca speaker 16R 4.50 8R 3.75 B+K tube bases Dynascan No. 3 9.50 No. 13 11.11 No. 6 11.08 No. 14 16.78 No. 8 10.08 No. 23 13.86 L5 7" x 3 3/8" speaker 4.25 C12 computer cass. 30 C18 computer cass. 33 5 1/4" floppy disc s/s s/d 1.61 15R fused res. G9 55 G11 line lin coil 2.95 G11 pot G2 R.G.B. 5.30 G11 line scan panel 54.00 G11 power panel 37.50 G11 timebase panel 37.50 G11 bridge trans. 97 G11 EW correc. coil 1.95 G11 final anode lead 1.50 G11 focus unit 5.80 G11 39R 3W resistor 60 G11 RGB 10G diodes 50 Labgear CM7091 UHF/VHF colour bar gen. 116.00 Televerta up converta 37.20	KT3 posistor 1.50 Mains electrolytic 225/25 380V 2.50 Selector unit Mod. 933 13.42 On/off switch Mod. 933 3.20 Tripler 10.65 Luminance chroma panel 24.00 2003 IF module 14.95 U321 IF module 13.50 R.G.B. panel 10.30 Sound panel 8.50 Power panel 10.60 Mains input panel 14.30 Line sync panel 10.20 Mark II chroma panel 16.50 15R fused res. G9 55 LOFT 9.70 Focus unit 3.50	Philips G8 knobs sm/g 50 90° transductor 2.60 Thom 1591 speakers sm lg 4.50 Thom 1500 controls 59 390K frame 470K line contrast 1k5 each 1.83 Focus control Thom/GEC 5.95 Thom 9000 focus unit 4.75 Thom 8500 focus unit 9.00 Decca bridge trans. 1.97 Decca 30 width cont. 50 Decca 2M2 HT cont. 25 Rank T20 focus cont. 2.20 Pye 731 HF choke 6.50 Delay lines DL20, DL60, DL70, DL50 2.20 CRT tube base 70 EHT final anode cap 53 6.3V CRT boost trans. 5.80 Focus rod 1.25 Focus holder 2.00 AFC unit G8 8.82 IF gain module 9.00 C.D.A. panel 20.00 G8 rear conv. panel 23.00
<b>PUSH BUTTON ASS.</b> Decca 4 way 6.88 6 way 7.50 GEC 2110 6 way 7.98 GEC Slim 6 way 6.50 GEC/ITT/PYE 7 way 14.50 Pye 4 way (713/15) 9.00 Pye 6 way (207/715) 16.00 Pye 697 repair kit 9.00 Pye 725-735 11.00 Pye 725-735 with tuning head 14.60 Philips G8 (early) 15.50 Philips G8 (late) 13.90 Rank A823 10.75 Rank T20A 9.75 Hitachi 4 way 10.75 Philips G11 unit 23.00 Philips KT3 14.50 Philips KT30 10.30 ITT CVC 8/9 (mod) 12.00 ITT 6 way with VCR 8.90 Thom 9000 unit 10.60 Thom 9000 switchback 5.30	<b>EAGLE MULTIMETERS</b> KEW 7N 6.75 KEW 14 9.00 KEW 20 14.50 EM5 11.95 EM20A 15.95 EM10 13.95 MM150 31.25 Bench Meters MM100 44.50 MMT20 21.50 MM150 75.00 T1206 intercom 8.50 MMC100 21.95 Case TS350 21.95	<b>K30 SPECIFICS</b> K30 LOFT 17.50 K30 focus unit 2.90 K30 EHT lead 5.90 Selector unit 1002 (early) 11.20 TMS 10B0 panel 1234 13.00 Euro decoder panel 1234 46.00 Power supply 1234 23.50 A1 gun switches 70 On/off switch 2.60 Selector unit 1002 (late) 9.90 Hand set 1201 14.50 Hand set 1234 14.50 Diode ZTX 33B 90 DL 20 delay line 2.20	<b>SPARK GAPS</b> Decca 100 52 0.75 pf 1.50 0.01 pf 32 Specific Video Leads (please state models) 4.25 Universal Video Lead Kit 6.00 EHT Cable per mtr 25 BNC to BNC Lead 1.75 BNC Plugs 1.16	
<b>SERVICE AIDS</b> SERVISOL Freeze-It 1.02 SUPER SERVISOL 92 SERVISOL Foam Cleanser 89 SERVISOL Plastics Seal 1.00 SERVISOL Silicone Grease 1.08 SERVISOL Tubes Silicone Grease 1.64 SERVISOL Aero Kiene 84 SERVISOL Aero Duster 1.10 SERVISOL Excel Polish 88 SERVISOL Video Head Cleanser 82 Super 40 1.50 Fire Extinguisher 640G 2.50 Heat Sink Compound 25G 1.08 Silicone Rubber Tube 110G 2.98 Solda Mop standard red 74	<b>ANTEX SOLOERING EQUIPMENT</b> C15W Iron 240V 4.41 C240 Element 1.80 Bits 102 90 106 90 820 90 821 90 CS17W Iron 240V 4.41 CS240 Element 2.25 Bits 1100 90 1101 90 1106 90 XS25W Iron 240V 4.59 XS240 Element 2.25 Bits 50 90 51 90 Temp. Controlled 10.50 30W Iron CSTC 10.50 40W Iron XSTC 10.50 Unit for above TCSU1 32.64 Stand 2.00 MLXS Auto Repair Kit 6.30	<b>SUNORY EQUIPMENT</b> Test Lead Set 4.20 Degaussing Coil Stick 17.00 Signal Injector 4.00 Elect. Circuit Tester 1.50 5A Choc Bloc (12) 40 Fuse Wire 5A, 15A, 30A 05 4-way 13A Mains Conn. 5.00 Safe Block (mains) 7.00 13A Plug Top (box 10) 4.80 Portable Oscilloscope 155.00 Probes (x10) 10.90 Probes (x1) 10.90 CRT Tester/Rejuv. 172.00 KHP30 Meas. Probe 30kV 32.00 Bell Wire (100m) 5.00 Mains Cable (circular 100m) (2 core) 10.75 (3 core) 13.25 Factory recon. Avo meters 119.00 Avo Batteries 2.20 Vero Board 2.59 Isolating trans. 500vA 240V 40.00 Solder 500g 7.00 D.I.Y. Solder 45 Solder Sucker 6.50 Nozzles 81 Dynascan CRT Res. 455.00	Solda Mbp Stnd. 74 Sidecutters sm. 1.20 Long Ncse Pliers 1.20 SM Torch 4.20 Quick Set Adhesive 75 Sm. Neen Screwdriver 40 Lg. Neen Screwdriver 65 Min. Screwdrivers 15 Antistatic Foam (12" sheet) 75 I.C. Inserters 1.18	<b>PLUGS</b> Phono Plugs 12 DIN Plugs 3 pin 22 4 pin 22p 5 pin 20p stnd 20 Car Aerial Plug 18 2.5mm Jack Plug 14 3.5mm Jack Plug 14 Stand Jack Plug 20 Stereo Jack Plug 36 Coax Plugs each 18 ten 1.80 PL259 40 Reducers for PL259 16 Line Connectors 16
<b>ELECTROLUBE PRODUCTS</b> Electrolube Adhesive 62 Electro-Mech lubricant 1.49 Elect. cleaning solvent 1.62 Freezer 1.49 Foam cleanser 1.12 Heat transfer compound 1.14 Silicone compound 1.94 Special contact fluid (Snorkell) 3.20 Permagard 1.52 Elec. mech. lubricant pen 74	<b>WELLER</b> Heat gun 12.00 Heat gun tips (pair) 57 3/16" Iron tips 25W (MT5) 57	<b>DATA BOOKS (Zero VAT)</b> TVT 80 A-Z only 3.75 TVT 80 2N-2S only 4.00 LVT 80/80 A-Z/2N-2S (pair) 7.50 LIN IC Books (data only not equiv.) 1.00 LIN1 5.95 LIN2 5.95 2M Fly Lead 70 4M Fly Lead 1.20 10M Fly Lead 1.90 Figure 8 Mains Lead 62 Computer to TV 97 7 pin din to 5 pin din 98 5 pin din to 5 pin din 98	<b>OATA BOOKS (Zero VAT)</b> TVT 80 A-Z only 3.75 TVT 80 2N-2S only 4.00 LVT 80/80 A-Z/2N-2S (pair) 7.50 LIN IC Books (data only not equiv.) 1.00 LIN1 5.95 LIN2 5.95 2M Fly Lead 70 4M Fly Lead 1.20 10M Fly Lead 1.90 Figure 8 Mains Lead 62 Computer to TV 97 7 pin din to 5 pin din 98 5 pin din to 5 pin din 98	<b>CASSETTE DRIVE BELTS</b> 35m 35 46mm 37 57m 37 66m 39 71m 43 76m 43 90m 43 110m 59
<b>VIDEO</b> Video care kits 3.50 VHS E30 video tape 3.06 VHS E60 video tape 4.00 Scotch E120 video tape 5.00 E180 video tape 4.50 Beta L500 video tape 4.90 Beta L750 video tape 5.80 Philips VCC 240 6.20 Philips VCC 360 8.30 Philips VCC 480 10.21 Philips LVC 1700 15.10	<b>LABGEAR</b> CM7261 Power Unit 10.70 CM7262 Reg. Power Unit 12V 11.67 CM7060 MHA 10db 12V W/B 9.39 CM7065 VHF/UHF MHA W/B 12V 13.66 CM7067 UHF 12V MHA (Specify A-B or C/D) 10.21 CM7068 UHF 12V MHA High Gain (Specify A-B or C/D) 15.19 CM7053 Behind Set UHF Amp. (Mains) 12.13 CM7054 Behind Set UHF Amp. (Battery e.g. Caravans) 9.92 CM7043 Second Set Amp. UHF 11.54 CM7093 Behind Set UHF Amp. 3 Sets 14.54 CM7063 Dist. Amp. VHF/UHF 17db/output 12V 20.10 CM7108 VHF/UHF 8+1 Dist. Amp. 41.20 CM7900 27mhz CB Suppress. 3.86 CM6011 Outdoor Splitter (2 way) W/B 7.46 CM9003 Flush Single Outlet 1.40 CM9010 Flush Twin Outlet 1.86 CM9034 UHF Group Filters with DC Through Pass (state A/B/CD) 6.97 CM6006 6 Way Passive Splitter 10.97 CM7042 TV Games Combin. 2.68 CM9009 Flush TV/FM Outlet 2.90 CM7091 Col. Bar Gen. 116.00	<b>OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC.</b> <b>WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER</b> <b>AERIAL EQUIPMENT</b> Outdoor Splitter 5.50 Plastic Tape 50 F.M. Plugs 25 Set Top Aerial 2.30 Loop Aerial 1.00 Mast Amp/Power Unit WB 18.00 Aerial Isolator Kit 2.08 Attenuator 6dB, 12dB, 18dB 1.80 27MHz Filter 50dB 2.10 Cable Clips 7mm per 100 1.18 Single Outlets 80 Surface Splitter 70 A Splitter 1.70 100M Coax 15.00 Coax Plugs per 10 1.80 1" U Bolts 30 J Bolts 25	<b>P.V. MICROCOMPUTER CENTRE</b> Why not pay us a visit and see our range of Micros, Software Books and Peripherals. Please ring for prices. Spectrum 48K Vic 20 Oric Commodore 64 We are also authorised dealers for the BBC Micro and accessories.	<b>SHEILA'S SURPRISES</b> £55 <b>SHARP VIDEO HEADS</b> VC2300 VC6300 VC7300/7700/7750 VC8300 VC220/381/383/388/9100/9300/9500 VC3300/9700 <b>SANYO VIDEO HEADS</b> £45 VTC 9300/9500 VTC 5300/5000 VTC 5350 VTC 5500 VTC 9350 <b>REMOTE CONTROL HAND UNITS</b> Grundig Telepilot 200/300 18.87 Philips G11 Teletext 23.80 Grundig Telepilot 12/16 13.87 Philips G11 non-Teletext 22.00 Philips KT2/KT3 13.87 Decca 100 23.80 JVC/Ferguson TX 10 16.87
<b>AUDIO HEADS AND MOTORS</b> Mono record/playback 4.32 Stereo playback 4.79 Stereo record/playback 4.99 Stereo record/playback (Dolby) 6.90 Mono/stereo erase 2.25 <b>Electronic/rotation clockwise motors</b> 6V MD6515 4.95 9V MD9516 4.95 12V MD12517 4.95	<b>STATIONERY (Zero VAT)</b> Service Call Pad (100) 1.20 Repair Ticket (100) 3.90 Job Card (100) 2.50 Rental Payment Card (50) 3.50 Rental Agreements (100) 3.50 H.P. Agreements (100) 3.50 Maintenance Agreement (100) 3.50	<b>ANTIFERRECE</b> SB11 Splitter 1.91 COB11 Outlet 80 CS200 Combiner/Splitter 3.03 CS1000 Combiner/Splitter 6.15 PU1240 Power Unit 11.00 UP1300 MHA 8.25 XS2U Xtraboost 11.63 4 way VHF/UHF Amp 33.75 6 way VHF/UHF Amp 42.00 XG8 High Gain Aerial A-B-CD-WB 16.00	<b>TELEPHONE JACK SOCKETS</b> 5.00 Complete with details connecting diagram. We also have a full range of telephone fixing accessories. Please ring for prices. <b>PLEASE ORDER FROM LATEST COPY OF MAG. TO AVOID PRICE INCREASES</b>	

T.T.L. 74LS SERIES				
74LS00	58	74LS37	35	74LS92
74LS02	58	74LS38	35	74LS93
74LS03	58	74LS40	35	74LS94
74LS04	58	74LS42	80	74LS109
74LS05	58	74LS47	85	74LS112
74LS08	58	74LS48	83	74LS113
74LS09	58	74LS49	33	74LS114
74LS10	58	74LS51	33	74LS123
74LS11	58	74LS54	43	74LS125
74LS13	37	74LS55	60	74LS126
74LS14	46	74LS73	60	74LS132
74LS15	33	74LS74	65	74LS138
74LS20	35	74LS75	65	74LS139
74LS21	35	74LS76	65	74LS151
74LS22	35	74LS78	65	74LS153
74LS26	44	74LS83A	89	74LS155
74LS27	35	74LS86	39	74LS156
74LS30	35	74LS85	98	74LS157
74LS32	90	74LS90	1.22	74LS158
65	74LS160	90	74LS245	2.30
60	74LS161	85	74LS251	65
80	74LS162	4.04	74LS253	95
58	74LS163	85	74LS257	1.20
50	74LS164	85	74LS258	95
44	74LS165	1.50	74LS259	1.70
70	74LS173	1.32	74LS273	1.90
85	74LS174	85	74LS283	1.30
75	74LS175	85	74LS293	1.20
1.02	74LS191	1.02	74LS352	1.40
1.30	74LS192	1.30	74LS353	1.40
1.30	74LS193	1.30	74LS365	75
75	74LS194A	75	74LS366	82
95	74LS197	95	74LS367	1.65
95	74LS240	2.20	74LS368	65
2.20	74LS241	2.20	74LS373	1.40
2.20	74LS242	2.20	74LS374	1.55
2.20	74LS243	2.20	74LS393	1.20
2.20	74LS244	2.20	74LS670	1.78

# P. V. TUBES

104 ABBEY STREET, ACCRINGTON

TEL: 0254  
36521/32611

'4000 B' SERIES CMOS				
4001B	21	4032B	1.04	4072B
4002B	21	4035B	80	4073B
4008B	72	4038B	99	4075B
4011B	21	4040B	72	4076B
4012B	21	4042B	58	4077B
4013B	30	4043B	71	4078B
4014B	74	4044B	71	4081B
4015B	76	4046B	96	4093B
4016B	31	4047B	70	4094B
4017B	66	4049UB	32	4099B
4018B	72	4050B	32	4160B
4020B	76	4051B	72	4161B
4021B	70	4052B	72	4162B
4022B	70	4053B	72	4163B
4023B	21	4060B	96	4502B
4024B	50	4066B	43	4505B
4025B	21	4068B	22	4510B

MAINS DROPPERS		NEW VALVES		THER-MISTORS	
DECCA 20	2.48	30FL2	1.70	EF183	99
DECCA 27R/47R	1.40	DY802	98	EF184	1.09
DECCA 56R/68R	1.40	DY867	66	EH90	1.02
R.B.M. A823 56R/68R	94	ECC81	1.08	EL34	3.50
R.B.M. 161	82	ECC82	98	EL84	1.05
GEC 2000/2018	70	ECC83	1.07	EY867	68
GEC 27840	64	ECC84	80	EY500A	1.50
PYE 713/15 3R5/15/45R	1.80	ECC85	98	EZ80/1	56
PYE 725/31 3R0/56R/27R	1.84	ECC88	1.35	GY501	1.45
PYE 725 56R/27R	1.04	ECF80	80	GZ34	3.50
PHILIPS 210/5050 30R/125R/2K85	1.75	ECF81	88	KT66	8.50
PHILIPS 210/5051 -/118R/148R	93	ECF82	1.60	KT88	12.00
PHILIPS G8/5081 47R Section	50	ECL80	84	PC92	3.00
PHILIPS G8/5083 2R2/68R	1.90	ECL82	1.30	PC885	85
THORN 1500	1.22	ECL86	1.99	PCC805	1.40
THORN 1600	1.38	EF80	95	PCF80	1.00
THORN 3500	1.77	EF86	1.96	PCF20D	1.35
THORN 8000	1.94				
THORN 8500	1.36				
THORN 9800	1.30				
DECCA 3R9 Modulohm	60				

LINE OUTPUT TRANS.		RECTIFIER TRAYS		REPLACEMENT ELECTROLYTICS	
R.B.M. T20A	13.95	THORN 950 Mk II	4.25	PYE 169 (200/200/100/32)	3.40
R.B.M. A774 Mono	11.74	THORN 1400 3 Stick	5.20	PHILIPS 320 (400/400/200V)	2.70
R.B.M. 2179	15.00	THORN 1500 3 Stick	5.20	DECCA 30 (400/400/350V)	3.40
R.B.M. 2718 22"	19.50	THORN 1500 5 Stick	5.29	DECCA 80 (400/350V)	3.97
PHILIPS 320	8.70	THORN 1600	4.95	OECCA 100 (800/250V)	4.83
PHILIPS 210/300 Mono	10.00	THORN 3000/3500	7.98	OECCA 1700 (200/200/400/350V)	2.30
PHILIPS G8	8.75	THORN 8000	5.28	PHILIPS G8 (600/300V)	2.21
PHILIPS G9	7.75	THORN 8500/8800	7.15	PHILIPS G9 (600/300V)	2.90
PHILIPS G11	13.50	THORN 9000	7.93	PHILIPS G11 (470/250V)	2.70
PYE 697 (Printed)	14.50	OECCA 1730/1830	4.48	PYE 691/7 (200/300/350V)	2.31
PYE 713/731	10.00	DECCA 30	6.76	PYE 731 (600/300V)	1.66
PYE 725 90°	10.50	DECCA 80	6.60	RBM A823 (2500/2500/30V)	2.83
PYE 169	10.00	DECCA 100	7.50	RBM A823 (600/300V)	3.55
OECCA 80/100	8.58	UNIVERSAL ITT or REMO	6.00	RBM Z146 (300/300/350V)	2.00
OECCA 1700	9.00	GEC 2100	7.40	RR1 T20A (220/400V)	2.98
OECCA 1730	8.58	GEC 2200 (20AX)	6.50	ITT CVC5/9 (200/200/75/25)	2.00
OECCA 2230	8.58	GEC 2040/2028	6.60	ITT CVC 20 (220/400V)	1.94
GEC 2110	16.75	GEC 2110 Pre Jan '77	7.00	GEC 2110 (600/250V)	1.19
GEC 2040	9.50	PHILIPS G8 Short Focus Lead	6.75	GEC 2040 (1000/2000/35V)	4.10
ITT CVC 1-9	10.85	PHILIPS G8 Long Focus 550	6.75	GEC 2040 (300/300/150/100/50)	3.0
ITT CVC 25/30/32	8.65	PHILIPS G9	6.37	THORN 3500 (400/40V)	1.83
ITT CVC 20	8.60	Pye/Philips K3 Tripler	10.65	THORN 950 (100/300/100/16/275V)	2.79
THORN 3000 EHT	9.95	PYE 691/3	6.58	THORN 1500 (150/150/100/300V)	2.20
THORN 3000 SCAN	7.95	PYE 713/4 Lead	8.79	THORN 1500 (12/300V)	31
THORN 8000	11.33	PYE 713 Doubler 5 Lead	8.79	THORN 3500 (175/100/100/400/350V)	2.78
THORN 8500	11.33	PYE 731/725	7.60	THORN 3500 (1000.63V)	86
THORN 9000	10.65	R.B.M. A823 (plug in) AV	7.60	THORN 3500 (1000.70V)	86
THORN 3000/3500		KORTING (similar to Siemens TVK1)	7.32	THORN 8000/8500 (2500/2500/63V)	3.38
Mains	10.00	ITT KB CVC5/9	6.90	THORN 8000/8500 (700/250V)	2.31
THORN 1591	8.68	ITT KB CVC20/25/30 (Mullard)	5.95	THORN 8000/8500 (400/350V)	2.56
THORN 1691	9.68	RR1 T20	6.80	THORN 9000 (400/400V)	3.28
THORN TX10	12.50			GEC (200/200/150/50)	2.64
THORN 1615	9.75			PHILIPS 69 2200/63V	1.25
PHILIPS KT3	9.70			THORN 4700 P/C 25V	1.20
RANK BUSHRANGER	£10.00			THORN 1591/1691 4700/25V	1.20
PYE 741	8.20				
B+O (2000, 3000)	12.70				
B+O (3000 EHT)	18.90				

CRYSTALS & FILTERS		MULTITURN POTS		THERMAL CUT OUT	
6Mhz	74	100K	55	THORN 3000 2A Metal	1.60
5.5Mhz	74	GEC TCE	55	GEC 2040 Metal	2.50
4.3Mhz	1.30	PHILIPS G8	55	THORN 8000 Plastic	2.35
8.8Mhz	1.30	DECCA, RANK	55		
9.94Mhz	6.00				
10.692Mhz	6.00				

DISC CERAMIC CAPS		POLYESTER CAPS	
8kV (12kV)	40p	250V 0.01mF	12p
39pF, 2000F		0.1mF	
150pF, 220pF		0.22mF	
180pF, 250pF		400V 0.01mF	12p
		0.1mF	
		0.22mF	

TANTALUM CAPACITORS		CONVERGENCE POTS	
6.3V	47mF	3W/5R-6R8-10R-15R-20R	60
	100mF	50R-100R-200R-500R	
16V	10mF		
	22mF		
	47mF		
25V	22mF		
35V	0.1mF		
	0.22mF		
	0.47mF		
	1mF		
	2.2mF		
	4.7mF		
	10mF		

MIXED DIELECTRIC CAPS		SLIDER POTENTIAL	
250V 0.91mF	1.15	1250V 0.1mF	59
400V 0.22mF	29	1500V 0.0047mF	32
800V 0.1mF	38	0.022mF	30
1000V 0.01mF	24	0.033mF	62
	0.047mF	0.05mF	65
	0.033mF	33 2000V 0.0052mF	1.20
	0.1mF	35 2500V 0.0022mF	50
	0.22mF		
	0.47mF		

FUSES		NEW MONO TUBES	
1 1/4" QUICK BLOW		MULL. A31/510 110" 12"	18.50
100ma	73	MULL. A34/510 110" 14"	20.00
250ma-500ma-750ma-1A	60	A51/120WR 110" 20"	15.00
1.5A-2A-2.5A-3A-5A	60	A61/120WR 110" 24"	17.50
		VEGA 12" 90° (Jap Types)	15.00
1 1/4" ANTISURGE			
250ma, 500ma, 600ma, 630ma, 750ma, 850ma,			
1A, 1.25A, 1.5A, 2A	1.70		
2.5A, 3A, 5A	2.70		
20mm ANTISURGE			
80ma	4.80		
100ma	2.50		
160ma, 200ma	2.20		
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A,			
2A	1.30		
2.5A, 3.15A, 4A, 400ma, 5A	1.90		
20mm QUICK BLOW			
100ma, 250ma, 500ma, 630ma, 800ma	90		
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	60		
1" MAINS			
2A, 3A, 5A, 10A, 13A	1.00		

REBUILD COLOUR TUBES		SLIDER POTENTIAL	
ALL AVAILABLE EX-STOCK ON GLASS FOR GLASS EXCHANGE FROM TRADE COUNTER. SOME TYPES AVAILABLE WITHOUT EXCHANGE FOR SMALL GLASS CHARGE		Lin or Log	
17" A44/271X	32.00	470R-1K-2K2-4K7	65
18" A47/342X (Low Focus)	32.00	10K-47K-470K	
18" A47/343X (Std Focus)	32.00		
20" A51/110X	30.00		
19" A49/120X	30.00		
22" A56/120X	30.00		
22" A55/14X	30.00		
25" A63/200X	34.00		
26" A66/120X	34.00		
26" A67/120X	34.00		
22" A56/140X (410X) 110"	36.00		
26" A66/140X (410X) 110"	36.00		
20" A51/161X	60.00		
22" A56/510X	50.00		
A56 540X	89.00		
A66 540X	75.00		
A66 500X	64.00		
P.I.L. TUBES - we can rebuild your own glass - please ring for quotes.			

SKELETON PRE-SET POTS		MIDGET CONTROLS	
Standard or miniature		Insulated Spindle Length 44mm	
Horizontal or Vertical		Log or Lin Without Switch	
100R-2M2	16p	5K-10K-25K-50K-100K-200K-500K-1M	39p
		With D.P.S.T. Switch	
		Log: 5K-10K-25K-50K-100K	81p
		250K 500K, 1M, 2M	
		Dual gang Controls	1.25
		16mm Rotary Controls 10K, 22K, 100K, 1M, 10K	39p

WIREWOUND RESISTORS*		THICK FILM RESISTOR NETWORK	
4W 1R-10K	24p	THORN 3500 (5 pin connection)	1.98
7W 1R-22K	29p	PYE 731 (6 pin connection)	2.20
11W 1R-22K	26p	THORN 9000 (Circuit Ref. R704/7)	1.98
17W 1R22K	32p		
(Preferred values)*			

CARBON RESISTORS*		EVER READY BATTERIES	
1/4W 3R3-8M2	20	HP2	26
1/2W 3R3-8M2	20	HP7	12
1W 10R-10M	36	HP11	24
2W 10R-10M	62	HP16	13
Sold in packs of 10 per type i.e. per value		PP3	42
		PP3-C	53
		1289	45

STOP PRESS Special Prices 5 1/2" Floppy Disc		SERVICE MANUALS (Zero VAT)	
SS/SD	1.10	THORN 1590/1	4.00
SS/DD	1.61	1615	2.95
SS/DD	1.70		

# P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US  
 104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.  
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

**HOW TO ORDER**  
 ADD 75p per order P+P  
 (U.K.). Heavier parcels e.g. cable, service aids, degausers, coils please allow £1.30 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.  
 Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

## SEMICONDUCTORS

AC107	35	BC558	9	BF355	56
AC126	30	BCY72	13	BF362	68
AC127	32	BD115	45	BF363	72
AC128	32	BD116A	65	BF371	30
AC128K	40	BD124P	79	BF392	35
AC141K	39	BD131	50	BF422	34
AC142K	38	BD132	49	BF423	46
AC176	35	BD133	60	BF435	35
AC176K	35	BD135	38	BF457	35
AC186	41	BD136	38	BF458	43
AC187	38	BD137	38	BF459	43
AC187K	38	BD138	35	BF460	86
AC188	35	BD139	35	BF462	86
AC188K	39	BD140	44	BF469	46
AD143	82	BD144	1.70	BF470	66
AD161	54	BD150	60	BF597	10
AD162	54	BD159	65	BF757	54
AD161/62 MP	1.15	BD166	52	BF758	54
AF106	49	BD179	70	BRF39	27
AF114	89	BD182	1.20	BRF40	85
AF124	1.20	BD183	75	BRF79	30
AF125	75	BD201	85	BRF90	1.74
AF126	48	BD202	91	BT42	39
AF125	46	BD203	80	BT43	39
AF126	46	BD204	99	BFW10	60
AF127	38	BD222	46	BFX29	40
AF139	48	BD223	56	BFX84	42
AF178	1.54	BD225	47	BFX85	30
AF239	60	BD232	68	BFX86	30
AL102	2.00	BD233	60	BFX88	46
AU106	2.50	BD234	63	BFY50	30
AU113	2.00	BD235	60	BFY51	30
BC107	20	BD236	65	BFY52	24
BC108	20	BD237	57	BFY90	95
BC109	20	BD238	65	BR100	34
BC114	12	BD243	85	BR101	45
BC115	17	BD244	85	BR103	63
BC116A	16	BD410	79	BR303	83
BC117	30	BD434	74	BRC4443	1.46
BC118	24	BD437	86	BRC4444	98
BC119	36	BD438	94	BRX46	40
BC139	28	BD507	52	BRY39	56
BC140	32	BD508	55	BRY55	45
BC141	26	BD509	56	BRY56	57
BC142	30	BD510	60	BSR59	1.80
BC143	31	BD278A	61	BSV57B	89
BC147	13	BD517	80	BSW67	68
BC148	9	BD520	75	BT100	1.65
BC149	12	BD535	82	BT101	1.20
BC157	16	BD536	91	BT102/500	1.20
BC158	16	BD696A	1.49	BT106	1.60
BC159	15	BD697	1.24	BT108	1.69
BC160	25	BD698	1.39	BT109	99
BC161	28	BD698	1.50	BT116	1.21
BC170B	15	BD707	95	BT119	3.56
BC171	15	BDX32	2.10	BT120	3.66
BC172	15	BF115	38	BT151/800	1.20
BC173	12	BF117	36	BU104	1.50
BC174	10	BF125	25	BU105	2.08
BC177	27	BF127	47	BU108	1.80
BC178	26	BF154	23	BU124	1.90
BC182L	9	BF158	18	BU126	1.75
BC183L	12	BF160	27	BU204	1.50
BC184L	14	BF167	24	BU205	1.42
BC186	18	BF173	22	BU206	1.80
BC187	25	BF177	52	BU208	3.00
BC204	10	BF178	46	BU208A	1.65
BC208	13	BF179	28	BU208D	2.20
BC209	10	BF180	39	=BU800	
BC212	9	BF181	39	BU208A2	2.10
BC212L	13	BF182	36	BU326A	1.75
BC213	13	BF183	29	BU407	1.70
BC214	10	BF184	36	BU426	3.07
BC237	14	BF185	36	BU500	2.30
BC238	14	BF194/394	16	BU526	2.46
BC251A	18	BF195	16	BU508	3.20
BC252	12	BF196	16	BU806	1.40
BC261	18	BF197	16	BU807	2.94
BC262	18	BF198	18	BUW84	1.45
BC300	50	BF199	21	BUW91A	3.84
BC301	53	BF200	35	BUX84	1.50
BC303	33	BF224	25	E1222	
BC307	20	BF225	20	MCR101	45
BC308	25	BF241	25	MCR220	1.50
BC323	99	BF256	55	ME0411	20
BC327	18	BF257	28	MJE340	68
BC328	18	BF258	25	MJE520	50
BC337	18	BF259	35	MJ3000	1.98
BC338	18	BF262	84	MPSA92	35
BC461	30	BF263	75	MR814	45
BC547	13	BF271	24	MR854	55
BC548	13	BF273	24	MR475	2.46
BCX32	30	BF274	24	MR479	2.60
BC549	8	BF336	36	ON447	99
BC550	7	BF337	41	DN448	99
BC557	8	BF338	41	OT112	1.91

## INTEGRATED CIRCUITS

AN2140	3.91	SN76023N	2.00	OT121	1.91
AN240	3.84	SN76110N	1.15	R2008B	1.90
AN318	3.98	SN76115N	2.27	R2010B	1.92
AN262	2.45	SN76131N	2.00	R2265	1.50
AN301	5.15	SN76226DN	2.00	R2322	62
AN7150	3.97	SN76227N	1.18	R2323	67
AN630	7.85	SN76533N	1.70	R2461	1.50
AN6341N	5.10	SN76033N	2.49	R2540	2.20
AN6344	7.85	SN76544N	2.35	RC4558	2.20
BA521	2.80	SN76650N	1.05	RCA16334	99
BA536	3.00	SN76660N	80	RCA16029	99
CA555	46	SN76666N	80	RCA16039	99
CA556	84	SN76530A	1.47	RCA16091	2.95
CA741	25	STK015	5.25	RCA16092	99
CA748	45	STK032	13.25	RCA16040	96
CA3065	1.80	STK043	11.05	RCA16041	84
HA1151	3.89	STK435	5.65	RCA16334	90
HA1322	2.65	STK436	9.06	RCA16335	99
HA1342	2.49	STK437	5.50	RCA16799	99
HA1306N	2.60	STK439	6.62	RCA16957	2.88
HA1366WR	2.80	STK459	8.20	TIC45	90
HA1392	3.95	STK441	8.10	TIC46	60
HA11219	2.49	STK461=465	9.60	TIL32	65
LA01224	1.98	TA7050P	14.30	TIL78	48
LA4031P	3.21	TA7051P	2.74	TIP29C	43
LA4032P	2.90	TA7063P	95	TIP30A	47
LA4250	3.57	TA7074P	95	TIP30C	43
LA4500	3.05	TA7108P	1.00	TIP31C	55
LA4422	3.28	TA7120P	3.43	TIP34B	42
LC7130	5.93	TA7129AP	2.43	TIP41C	47
LC7120	5.87	TA7130P	3.76	TIP42C	50
LM1377	5.50	TA7141P	1.93	TIP47	70
LM1011	3.25	TA7146P	4.67	TIP120	65
LM1340T	75	TA7172P	4.67	TIP2955	90
MB3712	1.95	TA7173P	5.67	TIP3055	63
MC1307	1.99	TA7176P	2.50	TIS91	21
MC1310P	1.60	TA7202P	4.27	TU106/02	1.80
MC1327	1.70	TA7204P	4.72	2N696	21
MC1351P	2.93	TA7205AP	3.72	2N918	82
MC1349	1.99	TA7208P	3.40	2N2904	51
MC1350	1.50	TA7210P	3.40	2N2905	28
MC1352	1.75	TA7222	2.42	2N3054	60
MC1358P	1.50	TA7223P	3.74	2N3055	60
MC1495L	3.00	TA7227P	5.98	2N3702	11
MC13002	3.90	TA7228P	5.98	2N3703	10
MC14011BCP	66	TA7310P	2.78	2N3706	10
MC14049UB	43	TA7609P	4.39	2N3708	17
MC7742	1.35	TA7611AP	2.92	2N5294	48
ML231	1.35	TAA300	58	2N5296	48
ETTR6016	2.20	TAA310	58	2N5298	69
ML232	2.20	TAA320	2.00	2SB337	1.86
ML236	5.35	TAA550	55	2N5496	53
ML237	2.50	TAA630	3.90	2N6107	75
ML238	6.00	TAA8400S1	1.96	2S715	81
ML239	2.50	TAA661B	1.20	2SA715	1.98
ML920	4.12	TBA120A	1.20	2SC495	1.10
ML922	3.29	(A), (S), (AS), (SA),		2SC496	1.31
TBA120B	1.30	TBA120B	1.37	2SC643A	1.50
TBA120S	1.37	TBA120T	95	2SC1096	1.72
TBA395	1.10	TBA120U	6.65	2SC1172Y	2.20
TBA396	1.10	TBA396	1.10	2SC1173Y	1.69
TBA440N	2.75	TBA440N	1.20	2SC1306	2.73
(TBA1441)		TBA440N	80	2SC1307	3.00
TBA440P	2.50	TBA440P	2.50	2SC1449	1.87
TBA480Q	1.50	TBA480Q	1.50	2SC1520	68
TBA510	3.00	TBA510	3.00	2SC1678	2.87
TBA520(Q)	1.68	TBA520(Q)	1.68	2SC1909	2.90
TBA530(Q)	1.38	TBA530(Q)	1.38	2SC1953	1.44
TBA540	1.68	TBA540	1.68	2SC2028	1.82
TBA550(Q)	1.58	TBA550(Q)	1.58	2SC2029	2.60
TBA560Q	1.59	TBA560Q	1.59	2SC2078	2.90
TBA673	2.45	TBA673	2.45	2SC2091	1.34
TBA700	2.12	TBA700	2.12	2SC2166	2.73
TBA750	2.64	TBA750	2.64	DEC1	2.20
TBA800	1.62	TBA800	1.62	DEC2	2.20
TBA810AS	1.10	TBA810AS	1.10	THY15/80	2.20
TBA820	1.70	TBA820	1.70	THY15/85	2.20
TBA820M	1.25	TBA820M	1.25	BU208B	2.20
TBA890	3.94	TBA890	3.94	BUW81A	3.84
TBA920(Q)	1.20	TBA920(Q)	1.20		
TBA950(2X)	3.05	TBA950(2X)	3.05		
TBA970	4.09	TBA970	4.09		
TBA990	1.90	TBA990	1.90		
TBA1440E	2.44	TBA1440E	2.44		
TCA160	2.30	TCA160	2.30		
TCA760	2.30	TCA760	2.30		

## DIODES

AA119	9	UPC1180C	1.84	AA119	9
BA102	17	UPC1181H	1.62	BA102	17
BA115	13	UPC1182H	2.95	BA115	13
BA145	17	UPC1183H	1.38	BA145	17
BA148	17	UPC1185H	3.66	BA148	17
BA154	6	UPC1188H	2.20	BA154	6
BA155	14	UPC1190H	1.20	BA155	14
BA156	15	UPC1197C	1.06	BA156	15
BA317	26	UPC1198C	84	BA317	26
BAX13	4	UPC1200V	1.18	BAX13	4
BAX16	8	UPC1211V	2.70	BAX16	8
BB105G	30	UPC1212V	1.34	BB105G	30
BY126	12	UPC1215V	1.66	BY126	12
BY127	11	UPC1216V	1.20	BY127	11
BY133	15	UPC1217G	1.13	BY133	15
BY164	45	UPC1218H	1.80	BY164	45
BY176	85	UPC1223C	2.20	BY176	85
BY179	63	UPC1225H	1.50	BY179	63
BY182	87	UPC1227V	1.56	BY182	87
BY184	55	UPC1228H	1.68	BY184	55
BY199	28	UPC1229H	54	BY199	28
BY206	14	UPC1230H	3.95	BY206	14
BY210/600	28	UPC1238V	1.16	BY210/600	28
BY210/800	33	UPC			

**WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US**

**G.G.L. COMPONENTS**  
 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY  
 PHONE (0228) 20358/39693

**BUY WITH**



E.H.T. TRAYS	
RBM T20/22A	7.35
RBM A823	7.85
PHILIPS G8-550	7.90
PHILIPS G9	6.45
PHILIPS KT3	10.00
THORN1500-3S	5.05
THORN1500-5S	5.40
THORN3500	8.25
THORN8000	5.20
THORN8500/8800	7.80
THORN9000	8.70
PYE 731	7.30
DECCA 2230	7.20
DECCA 80	7.20
DECCA 100	7.35
ITT CVC 20/30	6.85
Universal	5.90

INTEGRATED CIRCUITS	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TRAN-SISTORS	TYPE PRICE	TYPE PRICE	TYPE PRICE	TYPE PRICE	LINE O/P TR.	
LA4031	1.66	STK036	12.67	TBA800	0.90	UPC1176C	2.15	BC548	10	BR100	18
LA4031P	2.45	STK043	11.33	TBA810AS	1.15	UPC1177H	2.30	BC557	10	BR101	32
AN103	1.95	LA4032	2.34	STK050	20.75	TBA820	1.40	AC127	22	BC558	10
AN214	2.25	LA4051	2.79	STK070	21.95	TBA890	2.95	AC128	22	BD124P	70
AN240	2.20	LA4101	1.88	STK077	8.58	TBA9200	1.50	UPC1181H	2.20	AC128K	30
AN253	1.93	LA4102	1.87	STK078	8.45	TBA950/2X	2.85	UPC1180C	3.05	AC187K	30
AN315	1.66	LA4121	2.97	STK082	9.75	TBA990	1.55	UPC1181H	2.20	AC188K	33
AN318	6.95	LA4201	2.95	STK086	12.89	TCA270S	1.30	UPC1185H2	3.30	AD149	70
AN337	4.41	LA4400	2.80	STK415	9.66	TCA800	4.10	UPC1188H	3.30	AD161	42
AN360	1.45	LA4420	1.94	STK433	7.25	TCA940	1.55	UPC1190C	2.10	AD162	42
AN6332	6.97	LA4422	2.75	STK435	7.75	TDA1002A	1.50	UPC1198H	1.30	AF127	36
AN7110	1.93	LA4430	1.93	STK437	7.77	TDA1003A	2.80	UPC1200V	1.90	AU110	3.10
AN7114	2.33	LA4460	2.95	STK439	7.86	TDA1004A	2.70	UPC1208C	1.85	AU113	4.60
AN7115	2.37	LA4461	2.95	STK441	9.52	TDA1035	3.20	UPC1211C	4.05	BC107	14
AN7120	2.43	MB3712	2.30	STK443	11.33	TDA1044	3.10	UPC1215V	2.50	BC108	14
AN7140	2.10	MB3713	2.25	STK459	9.55	TDA1170	1.80	UPC1216V	2.00	BC109	14
AN7145	3.25	MB8719	5.20	STK461	9.95	TDA1412	90	UPC1217G	3.35	BC141	26
AN7150	2.89	MC1327A	1.60	STK463	10.88	TDA2004A	4.35	UPC1218H	2.75	BC142	23
AN7151	2.89	MC1358P	1.00	STK501	8.98	TDA2020	2.95	UPC1222	2.05	BC143	25
HA1137	2.30	MC1330P	90	TA7072P	2.75	TDA2522	1.80	UPC1223	3.40	BC147	39
HA1144	2.39	ML2318	1.95	TA7108P	2.10	TDA2523	2.25	UPC1225	3.10	BC148	39
HA1151	1.97	ML2328	1.70	TA7120P	2.05	TDA2530	2.10	UPC1226	2.55	BC157	10
HA1156	1.97	ML237	2.50	TA7129	3.00	TDA2532	2.20	UPC1227	2.10	BC158	11
HA1166	2.65	ML238	4.22	TA7130P	1.20	TDA2540	1.95	UPC1230H	3.45	BC159	11
HA1197	2.30	SA11024	2.55	TA7139P	2.80	TDA2560	1.80	UPC1245	1.99	BC160	22
HA1199	2.30	SA11125	4.70	TA7157P	3.00	TDA2581	1.70	UPC1250V	2.45	BC170	13
HA1202	1.75	SA11250	3.85	TA7171P	3.40	TDA2590	2.25	UPC1350C	4.50	BC172	22
HA1211	1.87	SA11251	5.20	TA7172P	3.40	TDA2591	2.70	UPC1353C	2.60	BC177	22
HA1306	2.97	SA15010	5.10	TA7176AP	2.90	TDA2593	2.30	UPC1356C2	3.05	BC182	10
HA1319	2.99	SA15012	5.70	TA7193P	4.20	TDA2600	5.50	UPC1358H	3.05	BC182L	11
HA1322	2.10	SAS560S	1.83	TA7202P	3.00	TDA2611A	1.50	UPC1363C	3.20	BC183L	11
HA1325	2.30	SAS570S	1.90	TA7203P	3.00	TDA2640	2.30	UPC1365C	5.05	BC184L	11
HA1338	2.78	SAS580	2.40	TA7204P	1.80	TDA3560	5.10	UPC1366C	2.85	BC208	12
HA1339	2.80	SAS590	2.40	TA7205AP	1.80	JPC41C	2.95	UPC1367C	2.85	BC212L	10
HA1342A	2.33	SL901B	5.65	TA7208P	2.20	UPC554C	1.30	UPC1368C	3.76	BC213L	10
W/WR	2.30	SN76003N	2.90	TA7210P	5.60	UPC555H	0.70	UPC1370C2	3.80	BC214L	10
HA1368	2.20	SN76013N	2.30	TA7222P	1.70	UPC566H3	2.10	UPC13737H	1.20	BC237B	11
HA1371	2.97	SN76023N	2.30	TA7223P	3.15	UPC577H	3.00	UPC1377C	4.60	BC337	11
HA1374	2.56	SN76110N	90	TA7227	4.65	UPC585C	1.40	UPC1378H	3.80	BC338	11
HA1377	3.80	SN76226DN	1.45	TA7310P	1.70	UPC1009H	2.15	UPC1384C	5.50	BF990	1.60
HA1388	4.20	SN76227N	1.00	TA7313P	2.10	UPC1017G	2.55	UPC2002H	2.20	BFY51	22
HA1397	4.15	SN76660N	65	TAA550	28	UPC1018C	1.15	DECCA 30(400/400)350V	2.55	DECCA/ITT 4W	6.45
HA11211	2.43	STK0039	6.45	TBA120AS	70	UPC1025H	3.30	DECCA 80/100(400)350V	2.90	DECCA/ITT 6W	7.95
KIA7217	2.75	STK0040	5.95	TBA120SB	90	UPC1026C	1.45	(800)250V	2.00	PYE201 6W	15.80
HA11221	2.77	STK0050	7.50	TBA120U	1.00	UPC1028H	2.15	PHILIPS G8(600)30V	2.00	PHILIPS G8S/L	14.90
LA1201	1.88	STK011	7.35	TBA395	1.25	UPC1031H	2.85	PHILIPS G9(2200)30V	1.15	PHILIPS G8S/Q	12.00
LA1230	2.30	STK014	7.65	TBA396	85	UPC1032H	0.85	PHILIPS G11(470)250V	1.95	HITACHI 4W	8.95
LA1365	2.25	STK015	7.15	TBA520	1.30	UPC1035C	2.50	PYE 691/7(200-300)350V	2.10	ITT CVC5 7W	10.40
LA2200	2.25	STK016	7.45	TBA530	1.00	UPC1042C	2.40	RBM A823(2500/2500)30V	1.10	ITT CVC8/9	12.80
LA3122	2.10	STK020	9.05	TBA540	1.27	UPC1043C	2.45	THORN3500(175/100/100/400)350V	2.25	PHILIPS G11 (TIP SW.)	26.90
LA3301	1.97	STK032	11.32	TBA550	1.40	UPC1052H	2.45	THORN3500(1000)70V	85	1043/05TFK	8.30
LA3350	1.93	STK035	12.67	TBA7500	2.45	UPC1169C	2.70	THORN9000(400)400V	2.75	U321 TFK	7.95
						UPC1170C	1.55			U322 TFK	7.40

DIODES	
TYPE	PRICE
DECCA 2230	8.30
BY127	10
BY133	15
DECCA 100	8.50
DECCA 80	8.50
R2010B	1.45
ITT CVC 20	7.75
ITT CVC 25/30/32	8.00
ANTI-SURGE FUSES	
BY210/800	30
BY223	36
BY227M	23
BYX10	20
YX55/600	26
OA90	07
1N4001-7	07
1N5401-8	12
BZ451-range	18
BZ98-range	11

MOTORS	
6-9-12-13.2V Motors	5.00

SUNDRIES	
PYE IF GAIN MOD	7.85
E/W COIL G11	1.65
VA110A	70
PY500A	1.90
PH8	69
PL509/519	69
PL508	69
PL504	1.50
PFL200	1.35
PCL86	81
PCL84	81
2SC2029	2.00
2SC2078	2.20
2SC1969	2.45
2SC1172Y	1.85
BF198	14
BF241	11
BF256LC	25
BF258	26
BF259	26
BF337	28
BF338	30
BF458	30
BF459	36
BF990	1.60
BFY51	22

**NEW**

Sony  
SG613/  
6533 8.50

TV ELECTROLYTICS	
DECCA 30(400/400)350V	2.55
DECCA 80/100(400)350V	2.90
(800)250V	2.00
PHILIPS G8(600)30V	2.00
PHILIPS G9(2200)30V	1.15
PHILIPS G11(470)250V	1.95
PYE 691/7(200-300)350V	2.10
RBM A823(2500/2500)30V	1.10
THORN3500(175/100/100/400)350V	2.25
THORN3500(1000)70V	85
THORN9000(400)400V	2.75

PUSH BUTTONS/TUNERS	
DECCA/ITT 4W	6.45
DECCA/ITT 6W	7.95
PYE201 6W	15.80
PHILIPS G8S/L	14.90
PHILIPS G8S/Q	12.00
HITACHI 4W	8.95
ITT CVC5 7W	10.40
ITT CVC8/9	12.80
PHILIPS G11 (TIP SW.)	26.90
1043/05TFK	8.30
U321 TFK	7.95
U322 TFK	7.40

Available also a range of 2SA/B/C/D Transistors. Phone or write for lists.

**ORDERING**  
 Please Add 50p For P/P U.K.  
 Add 15% VAT to This Total.  
 Export Orders - Cost.  
 DELIVERY BY RETURN ON ALL STOCK ITEMS.

**TV LINE OUTPUT TRANSFORMERS**  
 PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

<b>RANK BUSH MURPHY</b>	ITT: VC200, VC205, VC207	9.20
A774 with stick rectifier	VC300, 301, 302, 400, 401, 402	9.20
A816, T16, T18, Z712, Z715	CVC1, CVC2 (FORGESTONE)	11.50
T20, T22, T26, Z179, A823	CVC5, CVC7, CVC8, CVC9 series	9.20
Z718 Basic unit	CVC20, CVC30, CVC32, CVC45	9.20
T24e, T24h split diode	FT110, FT111. P/no AT2063/02	11.50
<b>DECCA</b> : 1210, 1211, 1511	PYE: 169, 173, 569, 368 series	9.20
1700, 2001, 2020, 2401, 2404	CT200, CT200/1, CT213 series	10.35
CS1730, 1733, 1830, 1835	725-731, 735, 737, 741 Series	9.78
30, 70, 80, 90, 100, 110, 130 Series	<b>PHILIPS</b> : 170, 210, 300 series	9.20
<b>FERGUSON, THORN</b> : 1590, 1591	320 series	9.78
1690, 1691, built in rect.	TX, T8 mono series	P.O.A.
1600, 1615, 1700 series	KT2, KT3 series colour	9.20
1790 mono portable	G11 series split diode	P.O.A.
3000, 3500, 8000, 8500, 8800	G8 and G9 Series	£9.20
9000, 9200, 9300 series	K30	£P.O.A.
9500, 9600, 9650 series	<b>BINATONE</b> : 9909 mono	13.04
9800, TX9, TX10 series	FINLUX 9560, 9670	13.91
<b>MOVIESTAR</b> 3781, 3787	<b>GRUNDIG</b> : most models in stock	
<b>FIDELITY</b> : FTU12 mono	<b>NORDMENDE</b> : FC125, Z206, Z306	11.50
CTV14R, CTV14S colour	<b>SANYO</b> : CTP5101, 5103, TJ series	11.50
<b>G.E.C.</b> 2047 to 3135 mono	<b>SHARP</b> : C1851H, C2051H	12.32
1201H, 1501H, 2114, 3133, 3135	<b>TELETON</b> : TH14 mono	13.68
DUAL & SINGLE hybrid col.	<b>TOSHIBA</b> : C800, C800B	19.45
SINGLE STD solid state	<b>TANDBURG</b> : 190, CTV2-2, CTV3-3 P.O.A.	
SINGLE STD split diode	<b>TELEFUNKEN</b> : most models in stock	
<b>INDESIT</b> : 24EGB hybrid	<b>LINE OUTPUT TESTER</b>	16.79
12LGB, 12SGB mono portables		
<b>WINDINGS</b>		
TYNE: main winding		
RBM: T20, T22, T26, Z179		
WALTHAM: W125 eht winding		
WALTHAM: W190, W191 eht coil		
KORTING: hybrid winding		

**Tidman Mail Order Ltd.,**  
 236 Sandycombe Road,  
 Richmond, Surrey.  
 Approx. 1 mile from Kew Bridge.  
 Phone: 01-948 3702  
 Mon-Fri 9 am to 12.30 pm &  
 1.30-4.30 pm  
 Sat 10 am to 12 noon.

**FREE CAREER BOOKLET**

Train for success, for a better job, better pay  
 Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.  
 Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!  
 Look at the wide range of opportunities awaiting you.  
 Whatever your interest or skill, there's an ICS Diploma Course there for you to use.  
 Send for your FREE CAREER BOOKLET today—at no cost or obligation at all.

Over 40 'O' and 'A' Level subjects from which to choose. Your vital passport to career success.


COMPUTER PROGRAMMING	<input type="checkbox"/>	RADIO AMATEUR'S LICENCE	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
COMMERCIAL ART	<input type="checkbox"/>	WRITING FOR PROFIT	<input type="checkbox"/>
TV, RADIO & AUDIO SERVICING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>		

Please

# EAST CORNWALL COMPONENTS

1985 CATALOGUE AVAILABLE - Many prices reduced - range increased - 123 pages fully illustrated. Price 65p, per copy (free upon request with orders over £5) - includes 30p Credit Note, special offer sheets, order form and pre-paid envelope. SEND NOW YOUR COPY.

VALVES		TRANSISTORS + DIODES		Type		Price (£)		Type		Price (£)		Type		Price (£)		Type		Price (£)	
DY802	0.88	AC127	0.30	BC108	0.10	BC302	0.32	BD244A	0.65	BF258	0.30	BT101/300	1.15	BYX36/150	0.22	TC106A	0.70	2AC1449	0.63
DY86/87	0.75	AC128	0.30	AB or C	0.12	BC303	0.32	BD375	0.32	BF259	0.32	BT101/500	1.25	BYX36/600	0.22	TP30A	0.46	2SC1507	0.63
ECC81	0.95	AC128K	0.34	BC113	0.14	BC307	0.10	BD410	0.10	BF262	0.30	BT102/300	1.35	BYX48/300	0.72	TP13C	0.54	2SC1678	1.06
ECC82	0.65	AC132	0.55	BC115	0.12	BC308A	0.10	BD434	0.68	BF263	0.30	BT102/500	1.65	BYX49/300	0.47	TP32	0.40	2SC1758	0.68
ECC83	0.75	AC141	0.26	BC116	0.15	BC327	0.14	BD437	0.76	BF271	0.26	BT108	1.30	BYX55/300	0.29	TP32C	0.60	2SC1909	1.20
ECC84	0.65	AC142	0.48	BC117	0.22	BC328	0.14	BD438	0.75	BF273	0.18	BT109	1.18	BYX71/600	1.18	TP34A	0.72	2SC1945	2.88
ECC85	0.95	AC142K	0.26	BC118	0.17	BC337	0.12	BD439	0.68	BF274	0.32	BT116	1.25	BYZ12	0.42	TP41C	0.46	2SC1953	0.74
ECC88	0.95	AC151	0.48	BC119	0.30	BC338	0.12	BD507	0.48	BF273	0.92	BT119	3.62	CI06D	0.80	TP42A	0.52	2SC1957	0.76
ECC89	0.75	AC152	0.45	BC125	0.12	BC350	0.12	BD508	0.53	BF336	0.26	BT120	3.60	ET1222	0.40	TP47	0.60	2SC1969	2.88
ECC84	0.75	AC176	0.28	BC141	0.42	BC441	0.32	BD510	0.48	BF338	0.26	BT138/600	1.30	ET1972	0.48	TP110	0.88	2SC2028	0.73
ECL82	0.95	AC176K	0.46	BC142	0.30	BC461	0.32	BD517	0.56	BF355	0.42	BT151/560R	0.90	ITT44	0.04	TP305S	0.60	2SC2029	2.10
ECL86	0.78	AC187	0.42	BC143	0.30	BC457	0.32	BD520	0.66	BF363	0.82	BT151/300R	1.15	ITT2002	0.11	TP305S	0.60	2SC2078	1.05
EF80	0.65	AC187K	0.48	BC147	0.08	BC548	0.12	BD699	1.25	BF367	0.24	BTY79/400R	2.80	ME0402	0.20	TP305S	0.60	2SC2091	0.73
EF86	1.60	AC188	0.44	A or B	0.10	BC549	0.12	BD699	0.88	BF371	0.27	BU100A	2.30	ME040/2	0.24	TP305S	0.60	2SC2098	2.90
EF86	1.60	AC188	0.44	A or B	0.10	BC549	0.12	BD699	0.88	BF371	0.27	BU100A	2.30	ME040/2	0.24	TP305S	0.60	2SC2122A	3.20
EF183	0.75	AC188K	0.48	BC148	0.08	BC550	0.12	BDX18	2.35	BF422	0.38	BU104	2.00	MEU21	0.60	TP110	0.88	2SC2166	1.20
EF184	0.75	AC188K	0.48	BC148	0.08	BC550	0.12	BDX18	2.35	BF422	0.38	BU104	2.00	MEU21	0.60	TP110	0.88	2SC2166	1.20
EH90	0.94	AD143	1.10	BC157	0.10	BC558	0.12	BF117	0.54	BF458	0.36	BU108	1.80	MJ2000	1.98	TXZ122	0.28	2SC2371	0.90
EL34	3.25	AD149	0.96	BC158	0.10	BCX34	0.27	BF119	0.82	BF459	0.44	BU124	1.75	MJ2000	1.98	TXZ122	0.28	2SC2749	2.70
EL84	0.69	AD161	0.42	BC159	0.10	BCY70	0.15	BF120	0.38	BF459	0.44	BU124	1.75	MJ2000	1.98	TXZ122	0.28	2SC2749	2.70
EL84	0.69	AD161	0.42	BC159	0.10	BCY70	0.15	BF120	0.38	BF459	0.44	BU124	1.75	MJ2000	1.98	TXZ122	0.28	2SC2749	2.70
EM57	2.55	AD161/AD162	0.42	BC160	0.30	BCY71	0.17	BF123	0.40	BF460	0.22	BU133	1.25	MJE370	0.88	IN4003	0.06	2SD234	0.64
EV86/87	0.67	AF106	0.48	BC168B	0.12	BCZ10	1.45	BF127	0.38	BF461	0.22	BU204	1.35	MJE520	0.48	IN4006	0.07	2SD348	3.30
EV500A	1.65	AF114	2.10	BC169C	0.10	BCZ11	1.45	BF151	0.16	BF461	0.32	BU206	1.70	MJE3055	0.70	IN4148	0.07	2SD398	0.62
PCCB4	0.50	AF115	2.10	BC170	0.12	BD124P	0.80	BF154	0.23	BF462	0.28	BU208	1.55	MPSL01	0.28	IN5400	0.12	2SK134	3.60
PCCB5	0.65	AF116	2.10	BC170B	0.14	BD130	0.68	BF157	0.40	BF462	0.28	BU208A	1.63	MRF475	2.50	IN5402	0.15	2SK135	4.80
PCCB8	0.74	AF117	2.10	BC171	0.10	BD131	0.34	BF158	0.22	BF462	0.28	BU208A/2	2.05	MRF477	10.00	IN5405	0.16	2SK136	1.90
PCCB9	0.95	AF118	0.85	BC171	0.10	BD132	0.34	BF159	0.24	BF462	0.28	BU208A/2	2.05	MRF477	10.00	IN5405	0.16	2SK136	1.90
PCFB0	0.75	AF12	0.62	A or B	0.08	BD131/BD132	0.95	BF162	0.23	BF463	0.30	BU407	1.65	OA47	0.10	IN5406	0.20	3SK45	0.76
PCFB6	1.25	AF124	0.48	BC172	0.08	BD135	0.32	BF167	0.30	BF464	0.79	BU407D	0.90	OA90	0.08	IN5408	0.08	3SK48	0.66
PCF200	0.95	AF125	0.48	A or B	0.12	BD136	0.36	BF173	0.25	BF464	0.79	BUX80	3.00	OA91	0.09	2N697	0.55	3SK135	5.20
PCF801	1.45	AF126	0.48	BC177	0.20	BD137	0.36	BF177	0.42	BF464	0.79	BUY20	1.75	OA95	0.18	2N706A	0.33	PVC Insulating	1000
PCF802	1.45	AF127	0.48	BC178A	0.22	BD138	0.38	BF178	0.30	BF464	0.79	BUY69A	2.60	OA200	0.06	2N706A	0.33	FPC Insulating	1000
PCF806	1.20	AF139	0.68	BC182	0.09	BD139	0.38	BF179	0.32	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PCLB2	0.90	AF140	0.68	BC182	0.09	BD140	0.38	BF180	0.32	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PCLB3	2.50	AF239	0.68	BC182L	0.09	BD144	1.60	BF181	0.30	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PCLB4	0.90	AF279S	0.75	A or B or C	0.09	BD145	1.82	BF182	0.32	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PCLB6	1.15	AL100	2.50	BC183	0.09	BD150A	0.85	BF183	0.32	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PCLB5/85	1.35	AL102	5.90	A or B or C	0.10	BD159	0.65	BF184	0.32	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PD500	3.75	AL113	2.20	BC183L	0.08	BD160	1.65	BF185	0.32	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PFL200	1.35	ASV80	0.65	A or B or C	0.12	BD165	0.45	BF184	0.08	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL30	1.50	AU110	1.40	BC184	0.10	BD175	0.40	BF195	0.10	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL36	1.45	AY102	4.42	A or B or C	0.10	BD182	1.00	BF196	0.10	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL81	0.85	BA102	0.34	BC207	0.15	BD183	1.10	BF197	0.10	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL82	0.75	BA110	0.67	BC208	0.16	BD184	1.20	BF198	0.14	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL83	0.65	BA121	0.40	BC212	0.09	BD201	0.77	BF199	0.16	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL84	0.75	BA129	0.38	A or B or C	0.10	BD202	0.82	BF200	0.26	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL95	2.00	BA148	0.16	BC212	0.08	BD204	0.80	BF222	0.48	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL104	1.20	BA154	0.08	A or B or C	0.10	BD222	0.80	BF222	0.48	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL108	2.40	BA155	0.10	BC213	0.09	BD225	0.86	BF224	0.16	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PL109/519	5.95	BA156	0.08	A or B	0.10	BD232	0.45	BF240	0.20	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PV88	2.40	BA157	0.28	BC131	0.10	BD233	0.60	BF241	0.20	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
PV500A	1.90	BA164	0.14	A or B	0.10	BD234	0.62	BF244	0.26	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
U26	1.90	BB14B	0.16	BC235	0.10	BD235	0.62	BF244A	0.28	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
UCB81	0.90	BB105B	0.30	BC238	0.12	BD236	0.62	BF244C	0.24	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
UCJ82	1.70	BB105G	0.48	BC239C	0.14	BD237	0.65	BF245A	0.28	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
6J5CT	1.75	BB110B	0.42	BC251	0.12	BD238	0.66	BF254	0.15	BF464	0.79	BUY69B	1.98	OA202	0.15	2N706A	0.33	TPC Insulating	1000
6S7J	2.20	BC107	0.10	A or B or C															

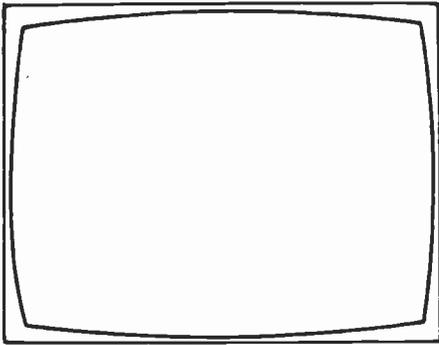

# TELEVISION

## The Video Boom is Over

That remarkable phenomenon the video boom seems to have blown itself out the world over. In the UK the boom peaked in the second quarter of 1983, when deliveries of VCRs to retail and rental outlets totalled 680,000. The figure for the second quarter of 1984 was 268,000 – in fact deliveries for the first half of 1984 were less than for the second quarter of 1983, and the year on year first half comparison shows a decline of 53 per cent. At the peak of the boom, VCR shipments to the UK were exceeding those to the USA and there were more VCRs per household in the UK than in Japan! The rental chains played a great part in getting the VCR established as a household item in the UK but came close to panic earlier last year (1984) when VCR returns rose to the same level as new rental contracts. It seems that the end of the summer produced some increase in consumer demand for VCRs, but rental companies could still be holding very large stocks of returned machines.

The rapid reversal in UK demand was of little consequence to Japanese manufacturers so long as demand in other markets, particularly the USA, continued to increase. But the peaks of the boom appear to have been passed everywhere. Japanese VCR exports rose to a record of just under two million last August. Since then there's been a weakening US demand, accompanying a general economic slow down there, while exports to Europe have continued to decline and sales in Japan itself fell in September. As a result, the Electrical Industry Association of Japan revised its estimate of VCR production for 1984 from 27 million down to 25.7 million. Not a great percentage drop perhaps, but something that hasn't happened before. This levelling off or reduced production is already beginning to affect other parts of the Japanese electronics industry, in particular the semiconductor manufacturers and suppliers of parts to the VCR makers.

The consumer should certainly benefit from this, as price cutting goes hand-in-hand with the introduction of machines offering more features and thus better value. Hi-fi sound and longer playing times are not things that have been easily achieved: they require considerable advances in the basic technology used in VCRs. The Japanese Ministry of International Trade and Industry has been trying to co-ordinate VCR production levels in an attempt to avoid excessive price cutting, but this may have only a limited impact at the retail end of the distribution chain. It's also of significance that South Korean VCR manufacturers are about to start exporting machines – to date they've been limited to domestic production under the terms of the technology transfer agreements entered into with Japanese manufacturers. The next few months may well turn out to be a good time to buy a VCR.

The problem of an over-supplied market does not apply to VCRs alone. Cassette production capacity world wide rose sharply in 1984. Whilst capacity in 1983 has been estimated at being able to supply only 70 per cent of demand, during 1984 it's reckoned to have increased to the point where twice the current demand can be supplied. This again is leading to increased price competition on the one hand and improved quality on the other – 3M for example have been advertising a "lifetime guarantee" for their tapes. 3M's approach has involved considerable investment in tape research and improved production technology. Greater precision has been achieved in specifying parameters for the oxide coating, film and solvents and in monitoring the dispersal of material on the film – specially designed laser scanners are now used for this purpose. Slitting the sheets of coated tape to the width required for spooling has always presented problems. It's claimed that the percentage of satisfactory quality tape coming from the slitters at 3M's Swansea plant has increased from between 60-70 per cent in 1983 to over 95 per cent. The plant is at present in the middle of an investment programme aimed at tripling production. This is against the background of reduced demand – a "serious decline" is the way in which Jarvis Astaire, chairman of Intervision Video (Holdings), has put it. It's evident that the profitability of the distribution side of the tape industry has been badly hit.

One can't help wondering what the Japanese consumer electronics industry will come up with next. There's always been something to offer once a particular market has reached saturation level. Transistor radios, audio equipment, television sets, personal portable audio, then the VCR: the obvious follow-ups would be electronic photography/movie equipment and personal computers. Much work has gone into both fields – 8mm video and camcorders on the one hand, the MSX system on the other. Active video has never been a major market however. People tend to treat video as they do other domestic electronic equipment – as something you switch on and let it do its stuff. Movie making is a world apart and something that by its nature has a much more limited market. With electronic still photography the problem remains that quality is inferior to traditional chemical photography while being a lot more expensive. With the personal computer it could be that the Japanese onslaught on the market has for once come too late. Microcomputer demand has weakened in the main markets – the US, UK and Japan – and MSX hasn't met with the instant success that's usual with Japanese offerings.

Is this the end of the boom for the Japanese consumer electronics industry? That's hardly likely. Customers will start to buy again before long, and what's then bought will depend on the continuing efforts of manufacturers. One thing Japanese manufacturers have always done is to maintain their R and D work whatever the market conditions, something that pays off in the long run.

### EDITOR

John A. Reddihough

### ADVERTISEMENT MANAGER

Roy Smith  
01-261 6671

### CLASSIFIED ADVERTISEMENTS

Barbara Blake  
01-261 5897

### PRICE INCREASE

The price of *Television* will be £1.10 from our next issue dated February. We regret the need for this increase which is due to the continued rise in our production costs. The next issue will have extra pages however and further bumper issues will be published during the coming year.

### INDEXES

The index to volume 33 of *Television*, available from our Post Sales Department (see page 121), sold out rapidly. A reprint has been ordered and the index will soon be available again. The index to volume 34 has been compiled and is now being printed.

# Teletopics

## TRADE SCENE

Trade figures (from BREMA) for the first six months of 1984 compared to 1983 show a dramatic fall in deliveries of VCRs, a small fall in large-screen CTV deliveries and a continued rise in small-screen CTV deliveries. Though the totals are relatively small, an increase of 95 per cent in teletext receiver imports, to 39,000, is worrying. Basic figures are as follows:

Product	Jan-June 1983 (000s)	Jan-June 1984 (000s)	Change (%)
VCRs	1,230	572	-53
CTVs, large	995	899	-10
CTVs, small	504	699	+38*
Mono TVs	449	326	-27

\* UK produced +27%, imports +46%.

Stocks are at present large. The latest survey, Media Leisure, from Leisure Consultants (Lint Growis, Foxearth, Sudbury, Suffolk, price £210) suggests that sales and rentals of VCRs and TV sets, also home computers, will drop in 1985/6, with consumer spending in the domestic electronics field remaining static. TV rentals may be given a fillip by the advent of more sophisticated sets with FS tubes, stereo sound and digital circuitry. An even sharper fall in VCR deliveries is forecast.

At mid-1984 there were 47,000 terminals linked to the Prestel network and 2.16 million teletext sets were in use, a household penetration of ten per cent.

## SATELLITE SCENE

The setting up of a privately owned, Luxembourg based TV satellite system called Coronet was mentioned in this column last July. Since then the project's sponsors have been seeking financial backing. The Swedish industrial holding company Investment AB Beijer has now taken a ten per cent stake in the scheme and it appears that the US Home Box Office cable film channel service has taken a further five per cent interest. It thus seems that the scheme, which has the backing of the Luxembourg government, is on the move. The cost of putting up the two satellites (one as a reserve) is expected to be around \$180 million and a launch date in early 1987 is planned with a service start in about June of that year. Coronet will be responsible for launching and operating the satellites: a consortium is to be set up to provide the actual programme material. The medium-power satellites will have a footprint covering most of western Europe - the EIRP for the primary service area will be 51dBW, and most of the UK will be within this area. The satellites are being designed to provide a sixteen channel service in the 12.5-12.75GHz band, i.e. just above the 12GHz broadcast DBS band. While the primary purpose of the project is to distribute programme material to cable TV networks there's no hiding the fact that direct broadcasting to domestic viewers is envisaged. Beijer's investment will give it an interest in two Nordic language channels.

As a result of recent changes to the plans for a UK DBS service the design of the satellites is under review.

When the BBC originally arranged for the design and construction to be undertaken by United Satellites a two TV channel service with extra transponders for telecommunications use was envisaged. Present plans for a three-channel service could lead to the elimination of the satellites' telecommunications channels. In addition cost reductions are being sought to improve the economics of DBS.

The first chairman of the Satellite Broadcasting Board, which is being set up to regulate the UK's DBS services, will be the IBA's chairman Lord Thomson of Monifieth. The board will have six members, half from the BBC and half from the IBA, with the chairmanship alternating annually between the chairmen of the BBC and the IBA. The board has not been formally set up since agreement between the participants in the DBS scheme has yet to be reached. Lord Thomson recently commented that "the challenge the Board will face is to find imaginative new ways of providing the public with services which the present four TV channels cannot fully meet and for which the public will be prepared to pay extra".

The Nordic Council of Ministers has given the go ahead to the establishment of a Scandinavian DBS service (Nordsat) with four TV channels, using the C-MAC/Packet transmission standard. The service is expected to come into operation in 1990.

## CABLE DEVELOPMENTS

The government has now announced the names of the majority of the members of the Cable Authority, which is being set up to regulate the provision of cable TV services in the UK. Professor James Ring has been appointed deputy chairman to Richard H. Burton, whose appointment as chairman was announced last August. Other members are Paul Johnson, Elizabeth MacDonald-Brown and Peter Paine. Two further appointments remain to be made. At present the authority doesn't have very much to regulate, but it hopes to start awarding new franchises at the rate of five every four months: Mr. Burton, who feels that the gloom over cable prospects has been overdone, says the "first and paramount priority of the authority will be to get the franchising process moving as fast as possible".

The Cable Television Association's chairman Peter Gosling has appealed to the government for greater help for a "cash hungry business in its formative years". Minister for Information Technology Geoffrey Pattie has ruled out any of the financial concessions proposed by the Association however. He's reported to have commented "I may wish them well but that's all I'm going to do", though he added that "if there's something so fundamentally amiss that there's a danger of them (the cable companies) being wiped out then obviously we would look at it again very carefully indeed".

Plessey Scientific-Atlanta, the Anglo-US joint venture that was set up to develop and sell cable TV equipment in Europe, has ceased operations. Plessey's director of technology Dr. Keith Warren, who was chairman of the joint venture, reported that the parent companies were not prepared to continue to spend money when there was little prospect of any orders materialising. A similar joint venture, GEC-Jerrold, was terminated last March. Plessey Scientific-Atlanta had developed a prototype two-way cable switch which had been specified by three of the original eleven cable

TV franchisees, Clyde, Croydon and Ealing, but no orders have been placed.

Thorn EMI, with British Telecom and local newspaper group Courier Press (Holdings) as minority shareholders, has announced that the Coventry Cable service is expected to begin operations this spring. Meanwhile Thorn EMI's cable activities in Swindon seem to have aroused local opposition – a pressure group called CACTUS (Concern About Cable Television Under Swindon) has been formed. Complaints include the fact that cable ducts are being laid to every house in the area whether the householder wants it or not, the disruption caused by the cable laying operations and the unacceptable condition in which the pavements have been left.

### **WHICH? ON VCR RELIABILITY**

The latest issue of the Consumers' Association monthly *Which?* reports that VCRs are unreliable generally while some models are a lot less reliable than others. The report is based on a survey of 6,340 users in the UK, W. Germany, Holland, Belgium and Denmark. It was found that there's "at least" a one in three chance that a VCR will need repair before it's two years old. The least reliable brands failed four times as often as the most reliable. Panasonic did best with 18 repairs per 100 machines. With all machines the most common faults were streaky pictures and fast wind/rewind problems. A quarter of the repairs to Akai machines related to poor sound, while Sanyo machines tended to go "completely wrong". In the first two years only seven per cent of machines needed new heads: the figure rose to seventeen per cent in the fourth year. The average time taken to repair an owner's VCR in the UK was 8.3 days while rented machines were dealt with in 3.2 days.

### **MATSUSHITA UK'S TEN YEARS**

Celebrations attended by Prince Phillip as guest of honour were held at the Panasonic factory in Cardiff on November 2nd to mark the tenth anniversary of Matsushita Electric UK's establishment. The Cardiff factory now employs over 600 people. Production is expected to reach 220,000 sets this year (1984) of which 45 per cent will be exported. The factory is being extended to increase the production capacity to 300,000 sets a year – there are also plans to start VCR production. Approximately 70 per cent of the components used come from UK or continental sources and productivity is the same as in Matsushita's Japanese plants.

Amongst the interesting items on show at a technology exhibition held at the factory was a record/playback colour video disc system using semiconductor laser technology. The 8in. disc has a playing time of just over thirteen minutes. At present the system is intended for commercial/industrial use.

### **MITSUBISHI'S COLOUR VIDEO PRINTER**

Mitsubishi, who introduced the world's first printer for the instantaneous printout of TV pictures in 1983, has developed a colour version. This consists of five main sections. In the first, composite NTSC video signals are demodulated to provide RGB outputs. These are then converted into digital form and stored in a memory which holds a frame of picture. The signals read from the memory next have to be converted to yellow, magenta and cyan since a subtractive colour printing process is



*Mitsubishi's colour video printer.*

used. The final section produces a full colour print with sixteen gradations by means of a thermal transfer system.

When the print button is pressed a TV frame in digital signal form is stored in the memory, which consists of twelve 64kbit DRAM i.c.s. The memory's output is then processed and the print made on plain paper. The whole process takes about a minute. The ink sheets are easy to change since they're in cassettes that hold enough sheets to produce 100 pictures.

### **SERVICING HOME COMPUTERS**

The problem of servicing the hundreds of thousands of home computers sold recently once their warranties have expired has been taken up by Computer-fix, which has set up a national network of five hundred dealers (initially) offering cheap, guaranteed repairs in only 48 hours plus the time required for delivery to and from the firm's headquarters at Camberley, Surrey. Faults are diagnosed by a computer called ACUMEN (Advanced Computer Memory Tester) which can detect a fault in any of the top brands of home microcomputers in just seconds – it doesn't even need to be told the make or model it's testing. Prices seem very reasonable, ranging from £15.50 for the ZX80/ZX81 to £40.25 for the BBC model, inclusive of labour, spares, postage, insurance and VAT. All repairs are covered by a three-months parts and labour guarantee. Further details can be obtained from Computer-fix, Albany Park Estate, Frimley Road, Camberley GU15 2PL.

### **THE TV LICENCE FEE**

Every three years the BBC has to apply to the Home Office for a review of the TV licence fee. And every three years the same old rows seem to resurface. This time the BBC has asked for an increase of roughly forty per cent in the colour licence fee, from £46 to £65, which would provide the BBC with an extra £1 billion a year. The haggling has started, but a decision is not expected until after January, when the accountancy firm Peat, Marwick Mitchell's "value for money" inquiry into the BBC will be completed. The BBC's case is based on the cost of maintaining the present services, with a modest amount for growth, taking inflation into account. As usual when this triennial business arises there have been calls from the advertising industry for the BBC to cover some of its costs by carrying advertising – the Institute of Practitioners in Advertising has called on the Home Secretary to allow advertising on all UK

radio and television networks. Well it would, wouldn't it? The government appears to be paying little attention to this lobbying. The ITV companies don't seem too happy with the idea either, since it would most likely spread much the same amount of advertising more thinly. The levy on the profits of the ITV companies is also under review. What with all this and the problem of financing a future DBS service the broadcasting organisations seem to be rather on edge at present.

### **VIDEO MATTERS**

TDK have introduced a range of new formulation (Super Avilyn) cassettes for use with Beta and VHS hi-fi VCRs.

Fuji has announced that it will shortly be introducing in Japan an 8mm camcorder, the Fujix-8. It seems that the photographic rather than the traditional video companies are pushing this format at present. There's also the Fujix TV-Photo system which enables you to view colour photographs via a television set: the system involves making a magnetic recording of the photographs on a 47mm floppy disc which can be played back. You buy the player unit - at around £200 - but the recording is done as a service at between £3 and £7 per disc. The Fujix-8 and TV-Photo system both operate on the NTSC standard only at present.

The recently opened National Interactive Video Centre in London is being funded by Thorn EMI, Philips and the government. Its purpose is to promote the use of interactive video systems in industry, commerce, education and the professions.

Japanese components manufacturer Alps Electric is setting up a £5 million factory at Milton Keynes to produce tuners and u.h.f. modulators for use in VCRs. It's expected that the factory will employ some 230 people by the end of the year.

### **ITT SAFETY NOTE**

Reference was made in this column last October to a safety recommendation issued by ITT concerning certain of their TV sets. ITT have now advertised the problem in the national press and will reimburse dealers according to a fixed fee for carrying out the work required. Models affected are as follows: CB502, CB602, CB702, CS512, CS712, CS522, CS622, CS722, CB9504, CB9602, CB9604 and CB0506.

### **TV AND NECK ACHE**

It's perhaps not too widely appreciated that the neck is quite a sensitive part of the body and that stress/strain here can give rise to many problems. Most large-screen colour sets have for many years been supplied with a stand that sites the set below the normal seated adult's eye level. This means that much viewing is done with the head lowered excessively, which doesn't seem to be a particularly healthy situation. Maybe some of our readers with medical knowledge would like to comment?

### **1985 TRADE SHOWS**

The agreed date for the annual London hotel trade shows this year is May 19th-22nd. In addition it's proposed to hold a trade/public exhibition, Vidtel 85, at the National Exhibition Centre, Birmingham, from August 29th to September 1st. This event, called the International Home Video and Television Show, would have two trade-only days followed by two days open to

the public. For the present it doesn't seem to be eliciting much enthusiasm from the industry.

### **SOLID-STATE IMAGERS FROM MULLARD**

Two imaging devices for use in solid-state cameras have been announced by Mullard. The new arrivals are charge-coupled, frame transfer devices which produce two interlaced 289-line fields with a 4:3 aspect ratio. Both provide a 604 × 575 pixel display giving a horizontal resolution of 420 TV lines, meeting CCIR standards. The NXA1010 (monochrome) and NXA1020 (colour) sensors have a 7.5mm image diagonal that matches the half-inch camera tube format so that they can be used with low-cost, commercially available lenses. They are suitable for all types of 625-line/50Hz PAL/SECAM cameras (525-line, NTSC compatible devices are expected to be announced shortly). The NXA1020 has an on-chip colour-stripe filter to provide RGB outputs. Complementary i.c.s have been developed to provide the necessary timing and drive signals.

### **THE EUROMAX AERIAL**

With the needs of those touring in caravans in mind Maxview Aerials (Maxview Works, Setch, King's Lynn, Norfolk PE33 0AT) have introduced the Euromax Universal aerial. This is in effect two aerials in one, covering both the v.h.f. and u.h.f. bands. The fixing kit supplied with the aerial includes strong suction pads and a bracket and mast. Price is £23.75 including VAT and the aerial comes in a box which gives fitting instructions in eight European languages plus Arabic.

### **NEW VCRs**

Three new VCRs have been added to the Ferguson range. The 3V43 is a full-specification machine with hi-fi stereo sound, two-speed operation and a suggested price of around £679. The 3V42 replaces the 3V36 as a mid-range model with a suggested price of around £549 while the 3V39 is intended as a budget model selling for around £399.

Sanyo have introduced a Beta hi-fi VCR, Model M40, at around £600. The new Mitsubishi HS306 is intended as a budget machine, carrying a suggested price of £440. Grundig's second VHS machine, Model VS220, features stereo sound. Suggested price is £489. Both machines now have infra-red remote control as standard. The first Philips all European VHS machine, Model VR6560, has been released with a suggested price of £459. There are also three new Philips V2000 format machines, Models VR2334, VR2350 and VR2840.

### **AERIAL CATALOGUE**

South West Aerials (11 Kent Road, Parkstone, Poole, Dorset BH12 2EH) have published their 1985 catalogue which is available at 60p per copy. An extensive range of aerials and associated equipment, including a 6in. v.h.f./u.h.f. TV set of particular interest for DX reception, is available from the firm.

### **SONY PROJECTION SYSTEM**

A new Sony projection TV system being sold in the USA for around \$3,000 is of interest in employing a 5.25in. beam indexing tube. This type of colour tube has a single beam to which the R, G and B signals are applied in sequence, in synchronism with the phosphor

**POST A PART ELECTRONICS**  
**6 CHAPMAN COURT, CHARFLETS ROAD,**  
**CANVEY ISLAND, ESSEX SS8 0PQ.**

Telephone 0268 690868  
 Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY  
 ADD 60p P&P, THEN 15% VAT.  
 ADD POSTAGE FOR OVERSEAS ORDERS.  
 ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 100 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 7001	1.00
Pye 713 Complete Tube Base Panel	
with Focus Slider & Leads	2.75
Pye 713 Control Knobs	4 for 45p
Tube Base Socket ITT CVC32	50p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Insertor 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	40p
Anode Cap	97p
Sanyo Anode Cap Assy + Lead, 12TCD-CT-16	65p
Degauss Thermistors, PT37P, ITT/GE	35p
Degauss VDR E2990/HP230 3000/8000	25p
Casters Set of 4	1.90
Double Fuse Holder on Small Pax Board	
20mm type	10p
Single Fuse Holder on Small Pax Board	
20mm type	5p
Direct Panel Mounting 20mm Fuse	
Clips (pair)	15p
Single Fuse Holder on Small Pax Board	
As per early 3000 mains input	6p
EHT Cable	25p
13A Plugs	12 for 4.00
BF259 with Heatsink	14p
TIP110 with Heatsink	40p
L129/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
8K5/9K Lum Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
1500 Metal Chassis Supports Pair	40p
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn 180 9W (3K5) R752	30p

**SERVICE AIDS**

Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amertube	6oz 1.89
Ambersil Ambertron	16oz 1.95
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Ambersilans Foaming Cleaner	13oz 1.26
Ambersil Circuit Lacquer	14oz 2.15

**THICK FILM RESISTOR UNITS**

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

**FUSES**

50MA	10 for 70p	250MA	10 for 65p
315MA A/S	10 for 50p	750MA	10 for 65p
500MA	10 for 50p	7A	10 for 50p
1A	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9600	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1590/91	7.25
Thorn LOPT 1690/91	7.25
Thorn LOPT 8000	9.00
Thorn LOPT 8500	9.00
Thorn LOPT TX9	9.85
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.00
Sanyo LOPT (CW21) 4-2751-44700	5.00
ITT LOPT CVC5-9	8.60
ITT LOPT CVC30	9.75
ITT LOPT CVC45	9.75
Beird 8750	10.25
Beird 8752	10.25
Korting AZ9100	10.25
Korting B92-170	10.25
Korting AZ2101	10.25
Korting AZ2103	10.25
Korting ZTR1001	10.25
Siemens V1155	11.75
Siemens V1823	11.75
Zanussi BS2222	10.25
Zanussi BS2223	10.25
Salora FR0057	10.25
Salora FR0029	10.25

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
20 Mixed Ferrite Cores	50p
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC172	9	BC559	8	BF179	29	BFR81	29	NKT453	1.65
AC131	40	BC174B	23	BC595	8	BF180	33	BFR87	25	DT112	1.92
AC138	40	BC177	24	BCX33	22	BF181	30	BFR90	1.74	DT121	2.00
AC141K	39	BC182B	12	BCX34	11	BF184	30	BFR91	2.08	R1038	80
AC142K	38	BC183	12	BD115	49	BF185	30	BFT43	30	R1039	80
AC153	39	BC184L	13	BD131	30	BF194	16	BFX38	40	R2008B	1.40
AC176	33	BC187	24	BD132	46	BF195	16	BFY30	30	R2030	1.10
AC176K	15	BC294	15	BD133	59	BF196	16	BFY51	34	R2265	1.30
AC128K	93	BC238	9	BD139	36	BF197	15	BFY52	34	R2305	80
AC188	38	BC212L	9	BD140	38	BF198	19	BRC116	1.50	R2322	50
AD142	1.18	BC213L	12	BD144	1.70	BF199	15	BRC1693	1.43	R2443	25
AD143	1.08	BC237	12	BD150	50	BF223	18	BU105	1.00	RCA1644E	30
AD149	98	BC238B	8	BD163	98	BF224	19	BU126	1.10	RCA16599	1.25
AD161	32	BC238L	8	BD201	74	BF238	20	BU207	1.05	RCA16600	1.40
AD162	32	BC250A	15	BD203	78	BF240	9	BU208	1.15	RCA16798	1.13
AD263	1.05	BC251	8	BD204	99	BF241	21	BU208A	1.15	RCA16800	1.42
AF127	45	BC252A	20	BD222	48	BF256	10	BU326A	1.30	RCA16802	1.28
AF139	38	BC294	37	BD225	52	BF256S	20	BU407	1.70	S1299	2.35
AF239	41	BC301	31	BD232	50	BF257	28	BU408	2.76	S28000	1.25
BC107	15	BC303	32	BD233	60	BF259	28	BU500	2.30	S8080A/B	3.50
BC108	15	BC307	10	BD234	60	BF271	25	BU526	2.46	S8080V	1.30
BC109	15	BC308	8	BD237	55	BF274	11	BU807	2.94	T8052V	1.30
BC115	16	BC309	14	BD238	85	BF287	85	BU829	9	T8057	1.25
BC117	21	BC327	18	BD241	59	BF338	34	C1172B	9	T9010V	1.45
BC125	26	BC328	18	BD244	40	BF355	40	E5386	54	T9053V	1.30
BC126	23	BC337	17	BD278A	81	BF362	50	E9003	28	T9054V	1.10
BC139	27	BC338	17	BD386	68	BF391	21	E9005	25	T9059V	1.00
BC141	34	BC347	8	BD433	71	BF394	16	ME0404	10	TIC45X	50
BC142	30	BC394	8	BD437	83	BF422	47	ME0412	10	TIC46	48
BC143	31	BC454	8	BD592	1.20	BF423	53	ME6002	10	TIC106C	40
BC147	12	BC455	8	BD589	1.20	BF450	43	MJ2501	2.36	TIP29	42
BC148	12	BC456	10	BD676	1.35	BF453	53	MJ3001	2.21	TIP30	42
BC149	12	BC460	40	BD707	95	BF458	37	MJE182	47	TIP31	35
BC153	16	BC463	22	BD708	95	BF459	40	MJE340	50	TIP32	43
BC1540R	16	BC546	8	BDX10	30	BF461	59	MJE520	50	TIP33	61
BC154YL	16	BC547	12	BDY20	1.09	BF556B	35	MJE2955	1.40	TIP41	42
BC157	12	BC548	12	BDY22	1.09	BF556	29	MC3055	1.50	TIP42	42
BC158	12	BC549	8	BF137	20	BF694	16	NKT241W	8	TIP110	61
BC159	15	BC557	10	BF153	20	BF757	62	NKT241G	8	TIS91	25
BC171	9	BC558	10	BF154	25	BFR52	31	NKT241Y	8	ZTX550	30

**INTEGRATED CIRCUITS**

BRC1330	1.40	SN76033ND	1.80	TBA530	1.26	TDA2002	2.80
BRC3064	1.00	SN76023N	1.80	TBA540	1.00	TDA2030	2.10
BRC/M/200	1.00	SN76033N	2.00	TBA550Q	1.82	TDA2522	2.10
BRC/M/300	1.00	SN76115	2.00	TBA560C	1.50	TDA2530	2.61
CA3060	1.58	SN76131N	1.50	TBA641	2.05	TDA2540	3.50
LM1303P	1.48	SN76226N	1.25	TBA651	2.50	TDA2581	3.50
ML231B	2.20	SN76227N	1.00	TBA720A	2.49	TDA2591	1.90
ML237B	2.00	SN76530P	1.30	TBA750	2.20	TDA2611A	1.95
ML239B	2.86	SN76622N	1.00	TBA800	1.82	TDA2640	2.90
ML327AP	1.25	SN76680N	80p	TBA810S	1.00	TDA2630A	6.00
MCI358P	1.30	SN76666N	90p	TBA810AS	1.00	TDA3580	1.50
Thorn LOPT 9600	12.00	SN76744	1.92	TBA920	2.08	TDA9503	2.90
Thorn LOPT 1615	7.25	SN76744	1.92	TBA950	1.95	TCEP100	3.48
Thorn LOPT 1590/91	7.25	TA7109AP	1.00	TBA1440	1.32	TEA1008	1.95
Thorn LOPT 1690/91	7.25	SAA1025	7.20	TCA270SA	1.05	MC14426P	4.50
Thorn LOPT 8000	9.00	SAA1124	4.50	TCA270C	1.05	MC14429P	4.50
Thorn LOPT 8500	9.00	SAA5010	6.00	TCA270CQ	1.05	MC14514	5.00
Thorn LOPT TX9	9.85	SL432A	1.80	TDA120C	4.00	UA758PC	2.50
Pye LOPT 713	10.00	SL1430	2.50	TDA1004A	4.00	UA1008A	2.66
Pye LOPT 725	9.85	SN15846N	60p	TDA1035T	3.50	ULN2185	1.30
Pye LOPT 731	10.18	SN15846N	60p	TDA1037	7.00	ULN2216A	1.25
Philips LOPT G9	8.80	SN74123N	65p	TDA11705	1.00	UPC1385C	5.75
Philips LOPT G11	13.75	SN74154N	1.40	TDA1200	2.42	SC9488P	1.40
GEC LOPT 3113	7.40	SN78001N	1.40	TDA1270	2.76	SC9511P	1.40
Diode Split LOPT AT2076/35	14.75	SN78001N	1.40	TDA1470	2.76	SC9511P	1.40
Sanyo LOPT AM-WM-21	6.75	SN76110N	1.14	TBA510	1.90	SW153	2.50
Sanyo LOPT AM-WM-4	7.30	Thorn 8/8K5 ex equip panels		Thorn 3/3K5 ex equip panels		Thorn 4000 PSU panel ex-factory	2.50
Philips LOPT G8	7.00	PSU	2.88	PSU	3.75	Thorn 3K5 beam limiter board	1.75
Sanyo LOPT (CW21) 4-2751-44700	5.00	FTB	3.75	LTB	3.75	new	1.75
ITT LOPT CVC5-9	8.60	Decoder	4.00	Video	2.50	Thorn 3K5 PSU bottom board	2.75
ITT LOPT CVC30	9.75	Thorn 9K ex equip panels		Chroma	2.00	PC206 new	2.75
ITT LOPT CVC45	9.75	PSU	12.00	IF	2.75	Thorn 3K5 IF panel new	3.00
Beird 8750	10.25	Decoder	5.00	Conv. 3K	1.75	Thorn 3/3K5 EHT & scan TX + R2008B on alum chassis ex-factory	1.00
Beird 8752	10.25	Thorn 9K6 ex equip panel		Conv. 3K5	3.00	Thorn 8/8K5 damaged FTB for spares	1.25
Korting AZ9100	10.25	untested		Autovox Decoder FG/01 new boxed	5.00	Thorn 8/8K5 damaged decoder for spares	2.25
Korting B92-170	10.25	Decoder	5.75	Thorn 4000 Convergence panel ex-factory	3.75		
Korting AZ2101	10.25	UHF TV Aerial for portable		50p Coax Plugs	10 for 1.65		
Korting AZ2103	10.25	Indoor Aerial Parabolic Type Reflector to Help Combat Ghosting Problems		2.50	Bend Change Switch Assy, Pye 725	40p	
Korting ZTR1001	10.25	Line Connectors		38p	Switched Rush Fitting Aerial Outlet	1.00	
Siemens V1155	11.75						
Siemens V1823	11.75						
Zanussi BS2222	10.25						
Zanussi BS2223	10.25						
Salora FR0057	10.25						
Salora FR0029	10.25						

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
30 Mixed Neons & Bulbs	1.00

BF167	24	BFR62	28	NKT276	20
BF173	29	BFR81	29	NKT453	1.65
BF179	32	BFR87	25	DT112	1.92
BF180	33	BFR90	1.74	DT121	2.00
BF181	30	BFR91	2.08	R1038	80
BF184	30	BFT42	30	R1039	80



**CHROMOVAC**

**QUALITY  
REBUILDS**

**SPECIAL  
OFFERS!**  
ON  
INLINE



**Get on the hot-line today!**

SUPERIOR QUALITY TUBES

051

**DELTA RE-BUILDS**

**428 8777**

most types of **Inline Re-builds** or  
**new ex-stock**

★ 2 YEAR WARRANTY  
★ 4 YEAR OPTIONAL

**Delta Rebuilds**

Up to 19" ..... £28  
Up to 22" ..... £30  
Up to 26" ..... £34  
110° up to 22" .... £34  
110° up to 26" .... £38  
Low focus ..... +£2  
A47 342 New .... £34

Delta only. Less 7½% 5+  
Less 10% 10+ and over

**Inline Rebuilds**

Up to 22" ..... £40  
Up to 26" ..... £45  
A56 - 540x ..... £56  
A66 - 540x ..... £58  
Bonded Coil .... +£5

ALL SIZES OF  
NEW MONO TUBES  
AT COMPETITIVE PRICES

**IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS**

370 HFB ..... £45  
370 HUB ..... £45  
420 CSB ..... £45  
420 EDB ..... £45  
420 EZB ..... £45  
420 ERB ..... £45  
510 UFB/A51-590 ..... £55  
A51-570 ..... £55  
A51-210 ..... £55  
510 VSB ..... £60  
AXT 51-001 ..... £60  
560 DYB ..... £62  
560 EGB ..... £62  
560 CGB ..... £62

560 DMB ..... £62  
AXT 56-001 ..... £62  
660 AB ..... £65  
A67-701 ..... £65  
670 CZB ..... £65  
H6817 ..... £65  
370 KRB ..... £55

CARRIAGE  
£5 Singles. 2-3 £10. 4 £12  
10 £15. 10+ Carriage paid  
EXCLUSIVE OF VAT  
TERMS  
Cash with order

QUANTITY  
DISCOUNT  
AVAILABLE  
Ask for details

★ OUR TECHNICAL DEPT WILL ADVISE YOU ON  
PROBLEMS YOU MAY ENCOUNTER ON FITTING  
INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order.  
Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

**CHROMOVAC**

CHROMOVAC LTD. UNIT 7, BEAR BRAND COMPLEX,  
ALLERTON ROAD, WOOLTON, LIVERPOOL 25

Ask for Mr Butterworth or Betty Ford ON: 051-428 8777

**Ex-Rental  
Colour TVs**

**PHILIPS**

26" — 520 from £4 22" — 520 from £8  
26" — 550 from £8 22" — 550 from £12

All makes and models many working!  
Inc. Thorn 8800/9000, Pye 222, GEC 2147  
Van loads direct from source  
For price list & DETAILS:  
**TEL KLW Ltd.**

**SOUTH**

Francis  
0582 24177  
17 West Side Centre  
LUTON

**YORKS**

Pauline  
0274 665670  
1043 Leeds Road  
Thornbury  
BRADFORD

**LANCS**

Frank  
0925 826387  
Priestwood Court  
Risley Ind. Estate  
Junction 11 M62  
WARRINGTON

**SCOTLAND**

Matt  
0698 282141  
Peacock Cross  
Ind. Estate  
Burnbank Road  
Hamilton

**NORTH WALES  
TELEVISION  
SUPPLIES**

**FLINT 5878**



Working sets from **£25**  
Untested sets from **£15**  
Mono **£4**  
Portable **£15**



Unit 32,  
**Manor Industrial Estate,  
Bagillt, Clwyd.**

stripes – indexing stripes laid on the screen tell the control circuitry which colour stripe is being scanned. The advantage is the increased brightness obtained by avoiding the need for a shadowmask – Sony say the brightness level is about seven times more than that obtained with a good shadowmask tube, an important point with a projection system. An ethylene glycol-water cooling system is required.

### PICTURES VIA THE TELEPHONE

The Philips slow-rate transmission system for sending video pictures via the telephone system has been given BT approval for connection to the network. Further details can be obtained from Philips Business Systems, Cromwell Road, Cambridge.

### TV SETS AND MONITORS

Akai's first TV set on the UK market is a 14in. colour model with infra-red remote control and facilities for RGB and composite video inputs. Suggested retail price is £279. Both ITT and Grundig have announced colour sets fitted with 20in. FS tubes. The Grundig FST range also includes two 14in. models. Samsung Electronics UK Ltd. (Hook Rise, Business and Industrial Centre, 225 Hook Rise South, Surbiton, Surrey KT6 7LD) have released a couple of monochrome portables, the 12in.

Model BT309K at around £50 and the 14in. Model BT351K at around £60.

Philips' BM7502 monitor has a 12in. green phosphor tube that gives a full screen display of 25 lines with up to 80 characters per line. The circuitry has been designed for minimum distortion and is suitable for graphic displays. There's a built-in speaker for sound and the suggested price is £79.95. It's intended for home computer users and is compatible with most home/personal computers, e.g. the Apple II series, Commodore Vic 20 and BBC.

### TV HEADPHONES

Ross Electronics (49-53 Pancras Road, London NW1 2QB) have introduced a headphone set, type RE2280, designed specifically for use with TV sets and VCRs. The frequency response is given as 20Hz-20kHz. The price, which includes a 6.4mm stereo jack plug, an adaptor for 6.4 and 3.5mm monosound sockets and 16½ft of cable, is £8.95.

### NEW MULLARD LINE OUTPUT TRANSISTOR

Mullard's new BU508D line output transistor is an updated version of the BU508A incorporating a parallel efficiency diode. Like its predecessor, the BU508D is encapsulated in the easy to mount SOT93A pack.

# Christmas Lights

William Harrison

The mains-driven light chain is a perennial Christmas hazard. A safe alternative is a low-voltage chain using 5mm LEDs of the type available from Sendz. Wire them in colour sequence to get the "travelling" effect. These LEDs require 2V and should be operated at around 20mA for a long life. The red type has a slightly lower voltage drop. To correct for this, I used six LEDs in the green and yellow chains and seven LEDs in the red chain. If the voltage is above 12V it may be necessary to add a series resistor – adjust the value for 20mA drive current.

Fig. 1 shows the basic circuit which uses a 4001B CMOS i.c. as the sequencer. Only three of the four gates in the i.c. are used – the other gate could be used to get four outputs, but I found that start-up was then erratic. The three outputs from the i.c. drive 2N2905 transistors which supply the strings of LEDs.

Fig. 2 suggests some alternative output arrangements to drive longer strings of LEDs. The ULN2003 incorporates seven Darlington amplifiers which can supply 0.5A each. For a still larger output, the ULN2003 can be used to drive TIP2955 power transistors, which will require heatsinks. Note that while the 4001B will work at a lower voltage than 12V the ULN2003 requires a minimum of 12V.

The LEDs are wire-ended, the longer wire being the positive connection. Don't shorten the wires: bend at right-angles, in opposite directions. They can then be soldered in series, in colour sequence along a four-wire cable, to obtain the moving-light effect.

If 2mm LEDs are used the current required is 10mA.

The unit was housed in a Verobox type 303 (120 × 80 × 35mm), with the components on a piece of stripboard.

A five-way DIN socket with a mating plug on the light chain completed the job. The LEDs can be obtained from Sendz or from Cricklewood Electronics Ltd., 40 Cricklewood Broadway, London NW2 (who can also supply the box and i.c.s).

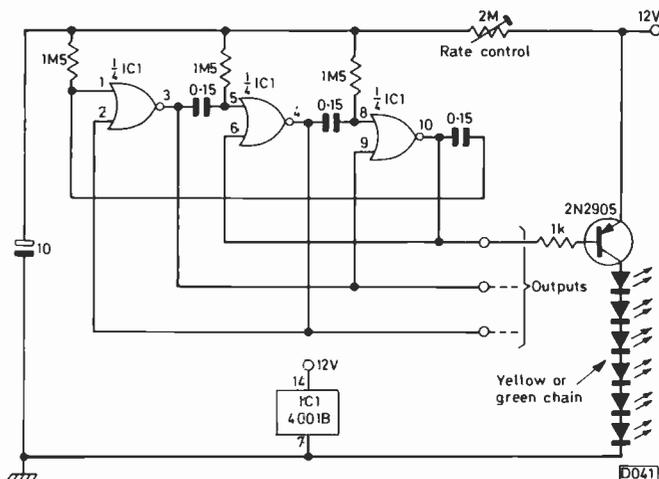


Fig. 1: Basic circuit, with sequencer to drive three chains of LEDs alternately to give the travelling light effect. If miniature electrolytics are used, connect the positive sides to pins 1, 5 and 8 of the 4001B i.c.

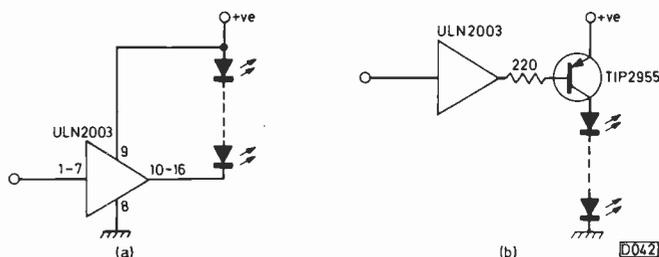


Fig. 2: Alternative arrangements for driving longer strings of LEDs.

# VCR Clinic

*Reports from Derek Snelling, Dewi James, Philip Blundell, Eng. Tech., Keith Hamer, Garry Smith and Steve Beeching, T.Eng.*

## Hitachi VT9700

Intermittent no operation was the complaint with an Hitachi VT9700. At switch on all was well for five minutes after which the counter and operate light began to flash on and off though the clock remained steady. We've had problems with the voltage regulator i.c.s used in this machine. They are on the rear panel, bolted to the heatsink. In this case the 9V regulator's output was intermittent, a replacement curing the problem.

D.S.

## Panasonic NV333

A Panasonic NV333 came in with the symptoms playback o.k., no record. In fact no stations could be tuned in with the machine in the E-E mode. The tuner proved to be faulty – only the second faulty tuner I've had in a VCR in three years.

D.S.

## Hitachi VT8000/VT8500

There are two 1.5k $\Omega$  resistors in the Hitachi VT8000/8500 power supply circuit (syscon panel), R054 and R069. I've had both fail on several occasions, but not together. R069 has been mentioned before and gives the no record symptom as there's no not-playback 12V line when it goes open-circuit – this line supplies the tuner and the i.f. strip. When R054 goes open-circuit there's no operation, with no operation light, as the regulated 15V supply is no longer present. If you get no operation but the operation light comes on, check the 5V supply to the microcomputer IC901: I've had zener diode D055 (RD5-1EB) go short-circuit on a couple of occasions.

D.S.

## Ferguson 3V35

The complaint with a Ferguson 3V35 was that there was no TV picture on three channels with the machine connected. Sure enough when I got there a quick check showed that with the aerial connected directly to the TV set (an old GEC model) everything was o.k. (ignoring a flat tube and half a dozen minor faults) but when the VCR was connected only BBC-2 worked, the other three channels producing a blank screen. All four channels were present in the E-E mode however. Luckily I had a Philips colour portable in the car. A quick check with this showed that all was well with the VCR – or did it? Closer examination showed that the picture was slightly noisy. In fact the VCR's aerial amplifier turned out to have marginally low gain as far as the TV set was concerned, a replacement curing the problem. Obviously something was faulty or out of adjustment in the TV set to produce a blank screen when the signal was only marginally down – in fact if it hadn't been for this the customer would probably never have noticed the slight loss of gain.

D.S.

## Sharp VC9700

One of these popular VCRs came in with the complaint "chews tapes". On trying the machine we found that it had very little take-up torque but too much supply reel

torque. The take-up torque is adjustable but the supply reel torque isn't. To measure the take-up torque you monitor the voltage across R7783, which is in series with the reel motor. This resistor is driven by transistor Q708 which turned out to be short-circuit.

P.B.


## Hitachi VT8500

Little did I know when my friend Geoff sent me an Hitachi VT8500 that wouldn't eject what trouble and expense it would cause. The machine wouldn't unlace and it was found that Q902 in the loading motor drive circuit (see Fig. 1) was open-circuit. The curious thing was that it turned out to be a BD131. Other transistors had been removed and replaced as well – legs were sticking out at all angles. I hate to see this sort of thing. Why can't some people be bothered to tidy up? Three i.c.s had also been soldered and may or may not have been removed. The 9V supply for this part of the circuit comes from the series regulator transistor Q060: R081 (2.2 $\Omega$ ) which is in series with this transistor was open-circuit. I replaced it with a resistor, a standard modification, but this didn't have any bearing on the main fault.


When Q902 was changed to a sturdier TIP31 the threading problem was cured. So the machine went back to Geoff with the comment that it had already received attention. Geoff phoned the following day to complain that it wouldn't wind fast forward and enquired whether I'd checked this? Well yes, play, record, rewind – but perhaps not fast forward. He also said his customer was adamant that apart from head cleaning the machine had received no servicing attention during the three years he'd had it. This time one of the transistors in IC906 (TA4193) was open-circuit. So the i.c. was replaced and Geoff took the machine back to check it for himself as a final quality control. The remote control unit didn't work due to corroded batteries and he had some difficulty in setting it for timer recordings, but apparently the customer wasn't too concerned about the timer.

A week later Geoff called with a "guess what?" comment to tell me that the Hitachi had again blown up. This time we had more accurate information. The customer had left the machine in fast forward and had subsequently returned to find it stopped and smoking. Back on the bench we found Q902 once more open-circuit and R081 burnt up. This was getting serious: it was obvious that the problem was of a somewhat unusual nature.

After replacing the defective components I left the machine in fast forward. After a while Q902 got very hot. So did IC906. This was strange as Q902 should be off for fast forward. I left the machine to cool down then put it into fast forward in order to make a few measurements. Result: there was 600mV that shouldn't be there at the base of Q902. It took some time to find the source of this voltage. Tracing back I found that it came via pins 6 and 7 of IC905 from pin 6 of IC906. Within IC906 the current was flowing via Tr4, a 265 $\Omega$  resistor, a diode and a 220 $\Omega$  resistor. Q901 and Tr1 are

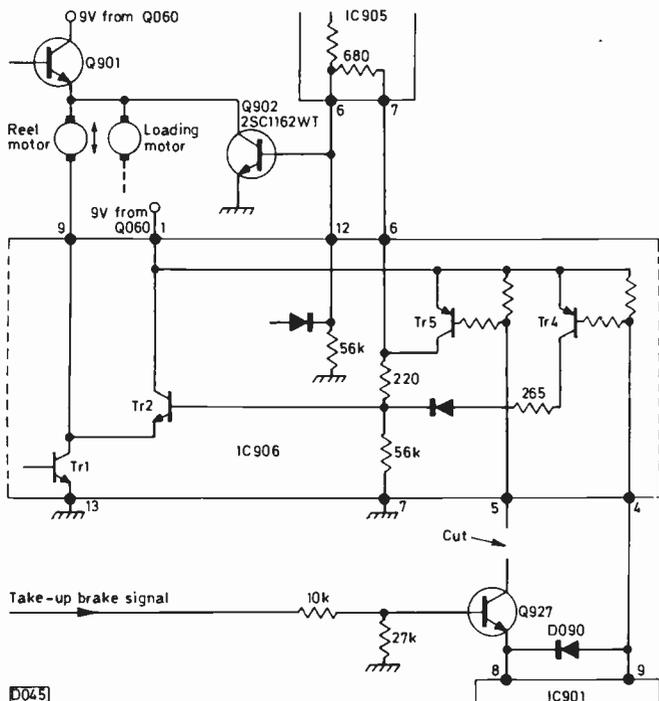

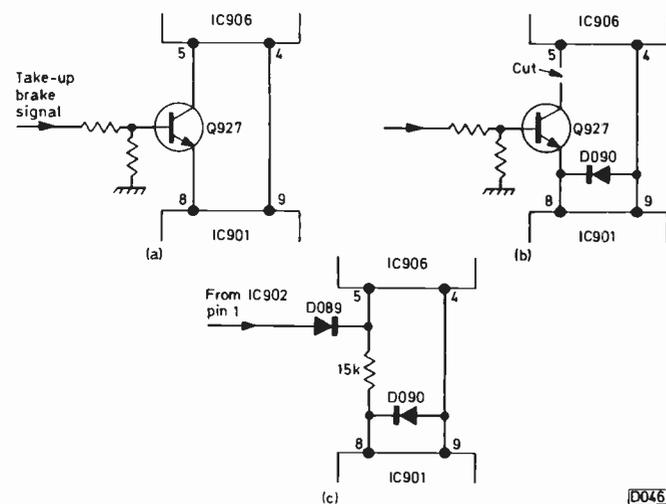**D045**  
**Fig 1: Reel motor drive circuit, Hitachi VT8500. Q901/Tr1 drive the motor for fast forward; Tr2/Q902 drive the motor for rewind. Q901 and Q902 are also part of the loading motor drive circuit.**



**D046**  
**Fig 2: Modifications to the control circuit: (a) original version; (b) version in the faulty machine; (c) the later version.**

on for fast forward: as Tr1 heated so Tr4 turned on more until eventually Q902 turned on. At this time the only circuit I had for the machine was one that didn't show Q927: telephone calls to Hitachi confirmed that there had been modifications to this part of the control circuit.

I suggested to Hitachi that the transistor that should be used in the Q902 position, type 2SC1162WT, might have some special characteristics. It transpired that the Vbe of a 2SC1162WT is 800mV, so some were sent for. On fitting one things were a little better, but as IC906 got hot 800mV was reached at the base of Q902 and it switched on. Cooling IC906 with freezer reduced Q902's base voltage and it switched off.

A new reel motor was tried to see if it ran without heating up IC906 too much. The temperature stability

was much improved, but not to my satisfaction as there was some 650mV at the base of Q902. Not enough margin with respect to 800mV for safety. The new reel motor was accused of consuming too much current and thus causing IC906's temperature to rise. Another new motor produced quite good results: I could run fast forward through an E180 cassette without overheating, but that 650mV was still there!

Whilst making further checks it was discovered – by accident – that if the recorder was put into the timer record mode while hot the reel motor turned in a slow rewind. This was due to Tr4 turning both Tr2 and Q902 on. As Tr2 was not fully on it got very hot.

At this point attention was directed at the circuitry around Q927, since a modification had been carried out here. The connection to the collector of Q927 had been cut, leaving pin 5 of IC906 open-circuit, and a diode (D090) had been added between pins 8 and 9 of IC901.

IC906 was replaced but the rogue 650mV persisted. Pin 4 of IC906 was disconnected and it went away. The microcomputer system-control i.c. (IC901) was next suspected and changed but we were still no nearer a solution. It was then realised that the modification had left the base-emitter junction of Q927 in circuit. Now the reverse breakdown voltage of such a junction is only 2-3V, so a leakage current path was present via D090, Q927 and the base circuit resistance. It was enough to turn Tr4 on.

Fig. 2 shows the circuit changes in this area – (a) the original version of the circuit, (b) the version in the machine in question and (c) the final version.

Whoever was responsible for the defective (b) version will probably never be known. What I do know is that the repair was carried out over a number of weeks and cost me a fortune. It cost the customer very little. I wonder who put the BD131 in?

S.B.

### Ferguson 3V35

A one month old machine came in with the complaint "no clock display". The various supply voltages were in order but on disturbing the filament power generator subpanel, which is mounted on the reverse side of the tuner/presetter board, the display returned. Further disturbance extinguished the display but there was no visual evidence of dry-joints around the oscillator. We resoldered all the connections in this area but the intermittent fault remained. The connections inside the oscillator coil screening can were the only ones untouched: to gain access we had to remove the complete coil assembly from the board. We then spotted the cause of the trouble – a loose lump of solder on pin 6 at the base of the oscillator coil (T1) was intermittently shorting to the can. At least it made a difference from having too little solder on the connections. K.H.-G.S.

### Panasonic NV333

We've had several problems with this machine, as follows.

**Intermittent audio erase:** Remove R4049 (4.7Ω) in the bias oscillator circuit and replace it with a shorting link.

**Intermittent chroma on record:** Connect a fast-acting diode (MA161 or MA162) between pins 11 and 12 of IC6003 on the syscon board, cathode to pin 11.

**Clock not lighting, capstan motor not turning:** No 18V regulated line due to Q1002 (2SD973) being open-circuit.

D.J.

# My friend Jim

Les Lawry-Johns

I've known Jim for a good few years now. He's in the trade and often pops in to buy some bits and pieces he needs and hasn't got in stock. Usually my last G8 line output transformer or 9000 tripler – you know, the kinds of things you're going to need during the next minute or so. He's not all that interested in servicing however. His main interest seems to be in building. The upshot is that whenever he gets a set he doesn't like the look of he'll bring it along with a comment like "have a look at this for me old chap, only I've got a floor up and really must fix it before the wife comes home". And off he goes leaving me with a bitch of a job.

## The Thorn 9600

He carted this Ferguson 9600 in and left it with me. The 2.5AT mains fuse had blown in a nasty way so I went straight for the filter capacitor, which was innocent. Next the bridge rectifier, which was short-circuit. So I whistled a happy tune as I replaced it, stuck a new fuse in and switched on. There was the usual pause, then it started up normally. A white line appeared across the screen so I checked the supply to the field timebase and then the output transistors. These were all o.k. It wasn't until I turned to the line/field oscillator subpanel on the right-hand side that I found a BC147 transistor (VT402) open-circuit.

With this replaced we had full scan, quite a nice picture and loud, clear sound. I then remembered something else Jim had said. Apparently the set often worked all right for some ten minutes or so and then tripped out. I left it on for some time and sure enough it suddenly gave a few gulps and went into a strike situation. I noticed that just before it did this the sound went down. So with enormous presence of mind I removed the 500mA fuse (F513) in the supply to the audio panel. The set then came on when asked to and apparently stayed on.

I removed the left-hand side audio panel and checked each transistor separately. They all proclaimed their innocence of course. The output pair were on heatsinks but the driver wasn't, so bearing in mind the loss of volume before the set tripped I reasoned (wrongly of course) that the driver could well be at fault. This is a BD386, which I didn't have in stock. I put in a BD204 instead, confident that it wouldn't give in easily. Quite right, it didn't. The set behaved happily for an hour or so then Jim came in to collect it.

## Jim's Return

Within the hour Jim was back with it. "Tripped after ten minutes" he said. So I removed the audio panel and left the set on without it. After half an hour it tripped. Back went the audio panel and the set played away happily enough for quite some time. Then the sound decreased and off it went into sullen silence. Everything shut down except the supply to the chopper circuit. I checked everything in sight and out of sight. Then I started to think.

The sound went down before the set tripped, and the

fault wasn't in the audio panel. So I removed the 500mA fuse F511 in the feed to the 24V regulator. This upset the field timebase but the set didn't trip. To cut a long story short, it wasn't until I removed the supply to IC2 (MC1358P) on the signals panel that the tripping stopped. When this i.c. was replaced our troubles were over. The intercarrier sound and audio preamplifier chip for heaven's sake. What next? Jim then came to collect the set.

## The GEC-Hitachi

An hour later he was back again. This time however he didn't lug in the Thorn. Oh no! That was just a forgotten incident now. This time he had a GEC set we didn't recognise. It was a C2265 (Hitachi NP81CQ chassis) and it took me some time to realise that what I took to be a chopper transistor was in fact a chopper i.c. (IC901, STR441). So I studied the notes in the manual, hoping to get a clue as to how to start the thing up. They did provide a lead, and when I put the meter on R605/6 in the chopper feedback line the set sprang to life. It frightened the life out of me because the sound had been left turned fully up. I turned it down and switched off. When I switched on again the set remained dead until I prodded around the feedback network – the chopper is a sort of blocking oscillator arrangement. The set then came to life. Until the meter probe slipped. There was a nasty flash and the 2.5AT mains fuse disintegrated. "Oh dear" I said.

Like a fool, I put another fuse in and tried again. FLASH! I checked the strange STR441 and found it short-circuit. So I ordered one and got it (along with some other things) next day. I fitted the three-legged device and bravely switched on. The fault was still there. I checked each item in the feedback network and they all read right. I then took them out to make sure. They were all right, so I put them back again and after that the set performed perfectly. Just another dry-joint? Must have been, but it certainly didn't show.

## Thanks Frank

On the subject of GEC I must pass on a message of thanks from several of my trade friends who have had cause to be grateful to Frank Pretty of the GEC technical advice department. He's been most helpful to all who have phoned asking for advice and have received more than they hoped for. I haven't had the pleasure of talking to Frank yet, but I very nearly did over the C2265.

## The Passing of Ben

You no doubt remember me chattering about our dog and cat (and bird). Well Ben isn't with us any more and we do miss him. Spock seems to complain all day long, loudly. Ben lost the use of his back legs and was unable to digest his food. He passed away peacefully but still seems to be around. Thanks Ben. I do wish that cat would shut up.

# Letters

## STREAMLINING THE TRADE

I'd like to discuss a couple of improvements that I feel would greatly improve the TV business. Most of the work of engineers, and most of the content of *Television*, are concerned with the repair of TV sets and VCRs that are a few years old. It strikes me that this whole area could be streamlined, leading to greater efficiency and profit for each individual engineer and company. The following ideas could also provide profitable business opportunities for anyone putting them into operation.

More often than not, repairing an old piece of equipment involves a long and laborious process of testing this, that and the other, working one's way around the equipment often without a circuit diagram. Once the faulty items have been located there starts an equally laborious hunt around for replacement parts. For many sets these are no longer available from the original manufacturer. Even when they are, the prices are often ridiculous in relation to the value of the set - so wherever possible it makes sense to fit second-hand parts in second-hand sets.

Here's how we could improve on all this.

- (1) Compile an exhaustive list of every model sold in this country. List first by brand/manufacturer, then chassis, then individual model. On this list should go the manufacturer's address and phone number.
- (2) List the common faults on each chassis. List by symptom, and opposite this put the action and parts required, with suitable equivalents. Such information is not supplied in service manuals since common faults show up only after thousands of sets have been in use for some time. Most of the information could be obtained by going through *Television* from around 1970 onwards. The result would be a complete list of models sold in the UK, with the common faults found over a 14 year period and how to deal with them. Surely this would be welcomed by all, especially employers who would prefer to pay for such information rather than continue to pay for their engineers to do their own trial and error research!

All this information could eventually be transferred to computer storage. This would enable a subscriber to get access to information on a particular set within seconds.

- (3) List inexpensive sources of further information, i.e. circuit diagram or service manual.

- (4) Approach suppliers of second-hand parts from stripped sets for details of what they can supply at what price. This information could be used to expand the list.

When repairing an older set, the action would be (a) to check that the symptoms are as described by the customer, (b) refer to the list, (c) check whether you have a stock fault, (d) look across for the action required, (e) look further for names of suppliers of second-hand parts.

I think this would help us rapidly clear our repair backlogs, don't you?

The converse of this is the business opportunities.

- (1) Companies could set themselves up as specialists in new and second-hand parts for particular makes of chassis.

- (2) They could advertise, offering to buy abandoned sets cheaply. This would provide a source of parts.

- (3) The fault compendium previously described would provide a guide as to the stock levels required for particular parts.

Wouldn't this be better than the present hunt for a line output transformer here, an i.c. there and a speaker somewhere else?

I hope this sets some minds at thinking. These suggestions could make a lot of dollars for some people and provide a lot of relief for the rest of us!

Colin Guy,  
Telly-Centre,  
Tunbridge Wells, Kent.

## DISCO-LIGHT EFFECT

Les Lawry-Johns mentions a strange disco-light effect with a Decca Bradford chassis (November issue). I had something similar with a Thorn 3500 and feel sure that it was due to the shadowmask kinking. The mask would kink back and forth, upsetting all purity adjustments. There was also a very slight pinging sound.

Philip J. Lomas,  
Television, Audio and Video Repairs,  
Coal Aston, Sheffield.

## MAINS FUSE PROBLEM

Over the past few weeks I've been plagued by a mains fuse blowing problem with three early GEC C2110 series sets. In the first case I replaced the fuse in the customer's home and could find no other fault. The

## BILLINGTON VALVES

23, Irwin Drive, Horsham, W. Sussex RH12 1NL  
Mail Orders Only; No Callers  
NEW, BOXED, GUARANTEED VALVES

3AT2B	£4.60	ECH82	£0.85	EL509	£6.90	PCF801.Mul	£2.00	PL504+	£0.95
6J5	£2.50	ECH81.Mul	£3.00	ELL80	£20.50	PCF802+	£0.57	PL504.Maz	£1.50
12BY7A	£3.15	ECH83.Maz	£1.80	EM87	£2.00	PCF806.Mul	£1.75	PL508	£1.80
12HG7	£4.20	ECH84	£0.50	EY86/7	£0.65	PCF808.Maz	£1.65	PL509 Philips	£2.80
17DW4A	£3.75	ECH84.Maz	£1.60	EY500A	£1.50	PCH200.Maz	£1.45	PL509+	£5.25
21LUB	£5.10	ECL80+	£0.60	EZ80	£1.00	PCL82	£0.63	PL519+	£4.45
30FL1/2	£1.50	ECL82+	£0.58	EZ81	£1.00	PCL82.Maz	£1.15	PL802T	£4.00
30FL12	£1.60	ECL84	£0.90	GY501	£1.45	PCL83.Mul	£2.50	PL802 Philips	£5.95
31JS6A	£9.00	ECL85	£1.00	GZ34.Mul	£3.45	PCL84.Mul	£2.00	PY81	£0.69
40KD6	£8.50	ECL86.Maz	£1.75	KT66.(USA)	£8.50	PCL84+	£0.80	PY88	£0.50
6SJ7GT	£2.00	EF80.Mul	£1.20	KT88.(USA)	£12.00	PCL85+	£0.90	PY500A+	£1.60
DY86/7.Mul	£1.50	EF80+	£0.30	PC92	£3.00	PCL86+	£0.80	PY800	£0.69
DY87+	£0.53	EF85.Mul	£1.75	PC97	£1.00	PCL805/85.	Mul	PY801	£0.69
DY802	£0.85	EF85+	£0.35	PCC84.Mul	£1.35	Mul	£1.05	U26.Maz	£1.70
ECC81	£0.95	EF86.Mul	£4.00	PCC85.Mul	£1.35	PD500	£2.90	UCH81+	£0.65
ECC82	£0.95	EF89.Mul	£2.10	PCC89	£0.70	PFL200.Maz	£1.30	UCH81.	
Philips	£0.90	EF183.Maz	£1.00	PCC189	£0.70	PFL200+	£0.85	Mul	£2.50
ECC83	£0.76	EF184	£0.50	PCC805	£1.30	PL36	£0.80	UCL82.Mul	£1.70
ECC84.Mul	£1.60	EH90	£0.90	PCF80	£2.00	PL81.Mul	£1.50	UCL83	£1.75
ECC85.Mul	£1.65	EL34.Mul	£4.00	PCF80+	£2.00	PL82	£1.35	UY85+	£0.70
ECC88	£0.95	EL84+	£0.75	PCF86	£1.20	PL83	£1.40	UY85.Mul+	£2.00
ECP80	£0.74	EL84.Mul	£3.45	PCF200	£1.80	PL84	£0.75		

Please add 70p post + packing, and VAT @ 15%.

All valves listed above are new, boxed and guaranteed 90 days. All types listed are in stock today, and prices are correct on 6/11/84.  
+ Denotes foreign brand of valve. Mul denotes Mullard brand in original blue box. Maz = Mazda

### SUBSTANTIAL DISCOUNTS FOR QUANTITY

We stock a huge range and can obtain valves for Japanese audio + T.V. equipment. Also valve sockets.

Send a large, stamped S.A.E. for our latest catalogue.

CATHODE RAY TUBES (Brand New + Boxed). We stock a wide range, S.A.E. quotation on your requirements.

USED VALVES Tested working. Clean. Boxed. 28 days guarantee.

Reduced to 20p: DY37, EF80, EF183/4, PFL200, PY33, 6F23. At 25p: GY501, PCF808, PCL82, PCL84, PL36, PY81/800/801, U191. At 100p: PY500A, PCL83, PD500, PCF200, PZ30.

\* PL504 35p - KT88 £3.00.

Most orders are despatched 1st class post, same day as receiving order. Please allow for Christmas postal delays.

WE WISH TO PURCHASE VALVES E.G.: PX4, PX25, PP3/250, PP5/400, DA30, DA60, DA100, 807.

same with the second set. After going through this procedure on several more occasions with both sets a third came into the workshop. I replaced the blown fuse, switched on and all was well. The set was left working while attention was turned to another one, then suddenly the fuse blew again. After a quick check I replaced the fuse and discovered that the holder was very hot. It was an old rectangular type with a poor grip on the fuse, so I replaced it with a standard screw-in type in a hole just below the original holder. Result: no more problems! The same action was then taken with the two sets in the field. I hope this word of warning will be of help to others: in future I shall always change the holder just in case.

*Kenneth D. Bunting,  
Huntingdon, Cambs.*

### PLUGTOP MYSTERY -1

The subject of loosening terminals has been with us for many a year. I remember first reading about it in the sixties, when a contributor to another journal complained of having to keep retightening immersion heater terminals. I've often come across the problem and have discussed it with colleagues. Two main points have always been made: (1) that the effect is generally evident only with higher current equipment; (2) that as far as anyone can remember it never occurred with d.c. mains supplies.

Two theories have been put forward. First, that with high currents the terminal contact pins heat up. This continual heating on load and cooling off load and consequent expansion/contraction loosens the terminals. This however doesn't explain why the effect is not present with a d.c. supply. Secondly, around any current carrying conductor there's a magnetic field, therefore between any two conductors there's a force generated by that field. With an a.c. mains supply this field/force will be absent a hundred times a second (at the waveform zero crossover points) and will then rise to a peak. This alternate presence and absence of force will result in vibration – it's the same sort of force that makes transformers hum, LOPTs whistle and electric fires sing. Could it be this vibration that loosens the terminals?

On a totally different matter, I take Mr. Bird's point (letters November) about the return visits to the PCL86 fault. In mitigation I'd like to say that many a "valve" fault turns out to be due to an intermittent passive component fault – how many good valves have been slung away because a new one apparently cured the fault, only for it to return a few days later? In this case it just happened to be what it should have been! Also I don't charge the customer for popping my head around the door – it takes only a few minutes when you're in the area anyway!

*Nick Lyons,  
Normanton, W. Yorks.*

### PLUGTOP MYSTERY -2

I've been following the correspondence on loosened connections in 13A plugtops with interest. It seems that some of your correspondents, in talking of electron flow from "negative" to "positive", assume the use of a half-wave rectifier in the equipment supplied. With an a.c. mains supply however the neutral pin remains at earth

potential while the live side alternates positively and negatively with respect to neutral. Consequently the electron current is alternating too and so far as the load is concerned the crossing over of the brown and blue leads makes no difference – though safety demands that we should follow the code correctly at all times.

I've heard people suggest that "a.c. shakes screws loose" but have no evidence to support this. What I have observed is that both neutral and earth connections can get loose while live generally remains tight. The live connection is usually of a different mechanical type from the simple hole and screw used in the neutral and earth pins. As G.C.C. Wride pointed out, the fuse provides some mechanical isolation for the live termination while neutral and earth can wag about. The cheaper and nastier the plug, the more the likelihood of looseness and burning.

Lastly, a method I've used for years when fitting these plugs. It's never let me down. Strip off enough insulation to provide a length of bared strands twice as long as you need. Twist them first, then double back the end, giving you double thickness. With a heavy cable you'll only just be able to get this into the hole in the terminal, with the screw nearly falling out. Then do up the screw with a good, solid screwdriver (not a grub-screwdriver) as tightly as you can without splitting the screw head. Also use a respectable make of plug. These measures will substantially reduce your troubles. Note also that the quite expensive MK plugs with rigid "bending-post" terminals have never caused me any trouble, even with hefty loads.

*Keith Cummins,  
Southampton.*

**Editorial comment:** Our thanks to several correspondents who have written on the subject of the a.c. mains supply and the importance of fitting good quality plugs. David McIntyre points out that some cheap imported plugtops bear a marking stating that they are manufactured to BS1363, but if they don't display the BS kite mark they don't need to be tested by the standards authority and are still suspect. The consensus of opinion is that the different mechanical arrangements at the neutral and live terminations are the cause of burning/looseness at the neutral pin.

### THE THORN 1400 CHASSIS

The Thorn 1400 was probably the last dual-standard monochrome chassis to remain in production. I've been using a couple of these sets, with 23in. tubes, for over two years for domestic and DX-TV purposes. They've given trouble-free service following renovation and provide pictures that are far superior to those produced by sets of more modern manufacture, despite the fact that both sets are fitted with the original tubes which must be getting on for seventeen years old. I've always found that the 19 and 23in. types of tube lasted much longer and gave much better picture quality than the later 20 and 24in. types.

The 1400 can be recommended for DX-TV use because of its excellent gain and the ease with which it can be modified to receive 625-line v.h.f. transmissions. All that's necessary is to move the lead from tag 43 to tag 44 (marked 625-VHF) and to cut the middle (grey) lead from the microswitch on the v.h.f. tuner, leaving the systems switch inoperative. The v.h.f. coils, accessible

at the front after pulling off the tuning knob, now need to be reset for the European channels. There's also a demand for sets modified in this way in areas where RTE can be received at v.h.f.

I hope other readers will find the following notes on renovating these sets of use.

First, whether you're a DX enthusiast or not, it's worth carrying out the systems switch modification described above. We all know the trouble that systems switches give, and there would be nothing worse than getting a phone call from a customer to say that the set switched to 405 but wouldn't switch back to 625! Both contrast controls continue to operate when the modification is done as described.

Secondly, the manual suggests that a PCF808 is a suitable alternative to the 30FL14 sync separator/flywheel sync amplifier valve. This is definitely not the case. I've seen the PCF808 advertised at somewhat cheaper prices than the 30FL14, but using one in the V4 position produces a picture miles out of tolerance with severely loaded-down e.h.t.

If you get the no-results symptom with the 1.5A mains fuse blown the cause is almost certainly the mains filter capacitor C101. It's rated at 600V d.c. but a 1.5kV d.c. rated type should be fitted. As in all sets these filter capacitors can go short-circuit at any time – at switch on or after anything up to several hours' use. Another possibility for fuse blowing at switch on is the BY127 h.t. rectifier diode to the right of the fuse.

No results with the heaters alight usually means that there's a broken mains dropper section. It's better to replace the dropper complete – exact replacements are not expensive. The fusible resistor R145 (100Ω, 5W) on the dropper will give similar symptoms when open. Note that dropper section R135 was changed to 1.7kΩ in later production to eliminate field cramping.

If you have the six-inch grid pattern an inch from the right-hand side of an otherwise perfect picture, replace the line output valve's screen grid decoupling capacitor C115. This is usually 1μF but was changed to 0.1μF, 350V for greater reliability in later production.

Loss of signals on u.h.f. only with background noise is normally due to a faulty u.h.f. tuner. These are available very cheaply. You may well find that the preset channel selector knobs need replacing since modern Thorn tuners use quarter-inch spindle shafts rather than the eighth-inch type previously used.

The 1MΩ width control and its 330kΩ series resistor can fall in value resulting in lack of width – a low-emission PL504 can produce the same symptom.

The most difficult fault I've had to deal with on one of these sets was an intermittent sound spluttering problem (sound intermittently blocked by crackles and spluttering). This was particularly bad while viewing RTE in Band III (I could receive this at times when I lived in Devon). The cause of the fault was eventually traced to one of the ratio detector diodes, W8, which is in the sound detector can. Access to the components in this can is not easy – care is needed while removing the aluminium can itself since the coils can easily break.

As with the later 1500 chassis, the line output transformer is so reliable that it can virtually be forgotten about, which is probably why so many of these sets are still in use. The tripler can give trouble, though I've not personally had this one.

Spares are readily available from advertisers in this magazine – triplers from Manor Supplies, tuners from

# next month in

# TELEVISION

## EXTRA PAGES!

Features in next month's bumper issue include:

### ● SERVICING THE PANASONIC TC2205

Features of this set (U2 chassis) include a self-oscillating chopper circuit that provides mains isolation, magic-line tuning, infra-red remote control and 10W audio output. The design lends itself to systematic fault finding. David Botto tells how.

### ● LNC FOR 11GHz RECEPTION

Many TV signals are available at relatively high levels from the ECS-1 satellite, while components for use at these frequencies are becoming readily available: Hugh Cocks describes a low-noise converter using the latest devices – details of a companion low-noise amplifier will be given in a later article.

### ● WORKSHOP DECODER ALIGNMENT

Denis Mott describes a simple method of aligning PAL decoders where R-Y and B-Y outputs are available. Using the technique, engineers are able to test, align and repair up to 70 decoder panels a day.

### ● HIGH-POWER UHF TRANSMITTERS

High-power u.h.f. transmitters are a world on their own, with output powers ranging from about 1kW up to 55kW peak sync. To achieve such powers at u.h.f. requires special techniques. Nigel Cawthorne describes what's involved.

### ● HINTS ON THE CVC5-9 SERIES

The ITT CVC5-9 series hybrid chassis seems to be the great survivor of the breed – large numbers of these sets continue to give good service. Chris Avis provides hints and tips based on his experience of renovating these sets.

**PLUS ALL THE REGULAR FEATURES**

**ORDER YOUR COPY ON THE FORM BELOW:**

TO .....

(Name of Newsagent)

*Please reserve/deliver the February issue of TELEVISION (£1.10), on sale January 16th, and continue every month until further notice.*

NAME .....

ADDRESS .....

.....

.....

Senz Components, the main electrolytic and dropper from PV Tubes, to name just a few items. PM components (Selectron House, Wrotham Road, Meopham Green, Meopham, Kent DA13 0QX) can supply all the valves at decent prices – their Selectronic brand valves are very reliable.

Finally, don't forget to reconnect any earthing strips/leads to the chassis after servicing one of these sets.

Failure to do so can lead to static problems which can be difficult to solve if you don't realise that a lead or strip has been disconnected somewhere! For a more detailed coverage of the 1400 chassis (with circuit and component layout diagrams) refer to Les Lawry-Johns' articles in the August/September 1976 issues of *Television*.

Brian Renforth,  
Wallsend, Tyne and Wear.

# Long-distance Television

Roger Bunney

October proved to be more active than usual, with relatively plentiful Sporadic E reception and two tropospheric openings. Meteor scatter signals also provided some excitement, with several enthusiasts reporting reception in the lower Band III channels. First the SpE log:

- 9/11/84 CST (Czechoslovakia) ch. R1.
- 11/11/84 Unidentified signals in chs. E2/R1.
- 12/11/84 TVE (Spain) E2-4; TVP (Poland) E3.
- 13/11/84 RAI (Italy) IA, B; JRT (Yugoslavia) E3; TVE E2-4; RTP (Portugal) E3.
- 14/11/84 RAI IA, B; TVE E3, 4; RTP E3; MTV-1 (Hungary) R1; EPT (Greece) E3.
- 16/11/84 RAI IA.
- 17/11/84 TVE E2-4.
- 21/11/84 TVE E2, 4; RAI IA; CST R1; NRK (Norway) E2-4; RUV (Iceland) E3, 4; also unidentified ch. R1, 2 signals.
- 22/11/84 TVE E2, 3; RAI IA; RTP E2, 3; SR-1 (Sweden) E2, 3.
- 24/11/84 TVE E2-3.
- 25/11/84 TSS (USSR) R1.
- 26/11/84 TSS R1; TVP R1.
- 27/11/84 TSS R1; TVE E2; plus unidentified ch. E2/R1 signals.
- 28/11/84 SR-1 E2; TSS R1.
- 29/11/84 RAI IA; TVE E3.
- 30/11/84 CST R1.
- 31/11/84 TVE E3, 4.

Our auroral reporter Iain Menzies observed several occurrences. The 11th produced identifiable NRK signals on chs. E2-4 and SR-1 ch. E2 between 21-2300 BST; auroral activity returned on the 18th and 19th, and on the 20th there were identifiable SR-1 signals on chs. E2 and 3. Apart from auroras, which result from storms on the sun, solar activity is at a very low level – we're entering the depth of the present solar cycle.

The two main tropospheric openings could hardly be termed "wide open" unfortunately. During the 12-16th there were widespread signals from the Benelux countries, W. Germany and (unusually) RTE (Eire) in Band III and at u.h.f. RTE Mullaghanish ch. D vertical caused some confusion for most of us, using horizontal Band III arrays. Canal Plus in Band III was widely seen throughout the UK, as far north as Scotland, as were the usual French u.h.f. stations. Conditions tended to favour a more north-south path by the 15-16th, bringing Tyne-Tees ch. 29 to the south coast and NRK (Norway) on all Band III channels to the central/southern UK for example – with

Denmark ch. E10 as a bonus. French ATV signals, notably F1EDM and F3LP, were seen over a wide area in south/SE UK. One interesting signal was the new ARD (W. Germany) logo – a figure one with various regional identifications inserted. The second tropospheric opening over the 30/31st produced signals from the Benelux countries, France and W. Germany, in Band III and at u.h.f., also DFF (E. Germany) ch. E11 and RTL (Luxembourg) ch. E7 at quite startling levels.

Canal Plus started operations in early November, with scrambling during the evening transmissions – we had been given to understand that scrambling would not start until January.

My thanks to Iain Menzies (Aberdeen), Tim Anderson (Bexhill), Dave Shirley (Hastings), Cyril Willis (Ely), Tony Privett (Basingstoke) and Gareth Foster (Twickenham) for sending in details of their reception.

## From our Correspondents . . .

Remember June 22nd, 1984, when an afternoon SpE opening gave UK reception of multi-hop signals with CBHT, Halifax, Nova Scotia ch. A3 and a mysterious "NTV" caption at 1600BST on ch. A2? Frank Lumen (Denver) has now identified Don Bassnett's reception of the NTV caption in Glasgow as Newfoundland Television. NTV is the new logo of the Newfoundland Broadcasting Company Ltd. The ch. A2 outlet operates at 3kW e.r.p. from Grand Bank. It's part of the CTV Network (Canadian TV), with the NTV main office/studios at St. Johns, Newfoundland. Congratulations to Don and thanks to Frank!

During a recent holiday in Bombay Bindu Padaki received Oman TV chs. E5, 7, 10 and u.h.f., Abu Dhabi ch. E9 and Yemen ch. E5. Bindu reports that the Indian government is establishing a network of 180 Band III transmitters, with typically 1kW e.r.p., to relay the INSAT-B programmes from New Delhi.

Marios Colocassides (Nicosia) has sent us a couple of photos showing "Middle East Television", ch. E12. The station operates from a site in the Lebanese mountains and was established by the "High Adventure Ministries" of California, then sold to another broadcasting concern. The signals are well received in the Lebanon, Syria and Israel as well as Cyprus.

Wenlock Burton (Victoria, Australia) recently sent several photocopies of old DX-TV articles from the magazine *Radio, Television and Hobbies*, the earliest dated January 1949. An item in this issue reports on the conversion at the Moscow TV Centre from 343- to 625-line operation, while the Leningrad TV centre was changing from 240 lines before the war (with regular programmes twice weekly) to 440 lines with programmes four times weekly "soon"! Interesting that such regional variations in transmission standards should have existed concurrently. The March 1957 issue contained reports on London/Sydney ch. B1 reception using a Hallicrafters

SX28 which produced the 41.5MHz sound and a 45MHz vision buzz "several times". The 41.25MHz French TV sound was also heard.

### News Items

**UK:** The RSGB, Alma House, Cranborne Road, Potters Bar, Herts EN6 3JW would welcome reports on reception of the new 50.1MHz beacon. Send to the General Manager.

The "Channel 36" pirate transmitter mentioned last month, operating on ch. E21, was closed down by the DTI on October 18th. It was working from Church Road, Crystal Palace, London. Thameside TV, operating on ch. E28, has continued however, using an accommodation address - 1 Grosvenor Parade, London W5. Incidentally Rotterdam is at present free from TV pirates: the cable companies now monitor the system output following main transmitter closedown - if a pirate signal appears it's removed and a "cable test card" is inserted.

**Belgium:** The Law Courts, Brussels ch. E48 transmitter has been closed following improved coverage from the Botanic Gardens ch. E25 outlet (BRT-2). TV-5, the French programme distributed by the ECS satellite, has been seen on ch. E64: the source is not known.

**Australia:** New channel allocations have been announced (see below). The new system allows for the introduction of two-channel sound.

Ch.	Frequency (MHz)	Ch.	Frequency (MHz)	Ch.	Frequency (MHz)
0	45-52	33	561-568	53	701-708
1	56-63	34	568-575	54	708-715
2	63-70	35	575-582	55	715-722
3	85-92	39	603-610	56	722-729
4	94-101	40	610-617	57	729-736
5	101-108	41	617-624	58	736-743
5A	137-144	42	624-631	59	743-750
6	174-181	43	631-638	60	750-757
7	181-188	44	638-645	61	757-764
8	188-195	45	645-652	62	764-771
9	195-202	46	652-659	63	771-778
10	208-215	47	659-666	64	778-785
11	215-222	48	666-673	65	785-792
28	526-533	49	673-680	66	792-799
29	533-540	50	680-687	67	799-806
30	540-547	51	687-694	68	806-813
31	547-554	52	694-701	69	813-820
32	554-561				

### New Products

Antiference have added a twin-input (v.h.f./u.h.f.) diplexing amplifier, Model UP3301, to their Uniplus range. The amplifier draws 37mA at 12V and is housed in a CS1000 type case. Performance figures are as follows. V.H.F.: passband 40-230MHz with gain 27dB  $\pm$  1.5dB, a noise figure of 2.8dB and typical maximum signal handling capability 35.5dBmV. U.H.F.: passband 470-860MHz with gain 23.5dB  $\pm$  2dB, a noise figure of better than 3.5dB and typical maximum signal handling capability of 36dBmV.

Another interesting unit is the UP1300/V wideband v.h.f. amplifier. Coverage is 40-230MHz with gain 19dB  $\pm$  2dB, noise 2.5dB and maximum handling capability 26.5dBmV.

Handling relates to a four-channel throughput at 46dB

## SOUTH WEST AERIALS

Our **NEW 1985 CATALOGUE** features many new products, it is an essential reference for the aerial user/enthusiast with its extensive listings of aerials, amplifiers, filters, rotators and multi-standard VHF/UHF televisions etc covering domestic, fringe and DXing installations. Send for your copy today - only 60p.



### EQUIPMENT & PROFESSIONAL ADVICE

South West Aerials offer a unique blend of the best equipment and impartial professional advice.

Examples from our range:

JAYBEAM NEW DY20 High Gain (16.5dB) UHF Aerial, available in Groups A, B, C/D and Wideband (chs. 21-68)	£46.85
LABGEAR CM7068 High Gain UHF three stage Masthead Amplifier, average gain 28dB; available in Groups A, B & C/D	£16.75
LABGEAR CM7066 High Gain (26dB) low noise, less than 2dB; Wideband (chs. 21-68) UHF Masthead Amplifier	£18.25
LABGEAR CM7061 Matching Power Supply for use with above amplifiers	£13.50
JVC CX610 6" Colour Television/Monitor, Multi-Standard PAL/SECAM System B/G/I/D/K VHF-UHF; 5.5/6.5MHz sound switching; 12/240 volt operation	£281.45
WALTHAM 416 6" screen VHF/UHF mono Television, System B/G operation (5.5MHz sound); covers Bands 1, 3 & UHF 12 volt and mains operation	£73.70

Above set can be adjusted to 6MHz sound for an additional cost of £2.50.

We are THE DXing Specialists, advice given on ALL reception problems (SAE please) All prices inclusive of VAT & Carriage. Delivery 7-10 days. Access & Visa welcome.



**SOUTH WEST AERIALS**  
11, Kent Road, Parkstone,  
Poole Dorset, BH12 2EH. Tel: 0202 738232.



r.m.s. peak and noise to the complete unit - not the devices.

The W. German Hirschmann company has introduced a new type of Yagi aerial. It has a rather higher gain than previous types as a result of using a double director chain. There's a conventional multi-element director assembly chain with a chain of standard half-wave elements interspaced between the full-wave director assemblies. The result is an increase in gain of some 1-1.5dB. An array with fifteen full-wave director assemblies and the additional complement of half-wave directors spaced along the boom has, in the wideband version, a gain of 12.5dB at ch. 21 rising to 16dB at ch. 40 and 18dB at channel 60, with reference to a half-wave dipole. The front-back ratio is between 27 and 30dB. Ryn Muntjewerff has been testing one recently at his Beemster, Holland location and has found that the system bettered two stacked Fuba XC391 aerials at the group E end of the spectrum though the Fuba aerials had the edge in group A.

### Wideband Inductive Combiners/Splitters

Wideband inductive combiners/splitters are available from most UK aerial manufacturers and aerial retail/rigging firms. There are two main versions: external for mast mounting, usually provided with some form of clamp, and indoor types of either wired or integral plug/socket construction. I recently had a need for such a unit with a specific performance requirement and as a result obtained six units from different manufacturers and carried out tests on them.

The performance figures quoted by manufacturers usu-

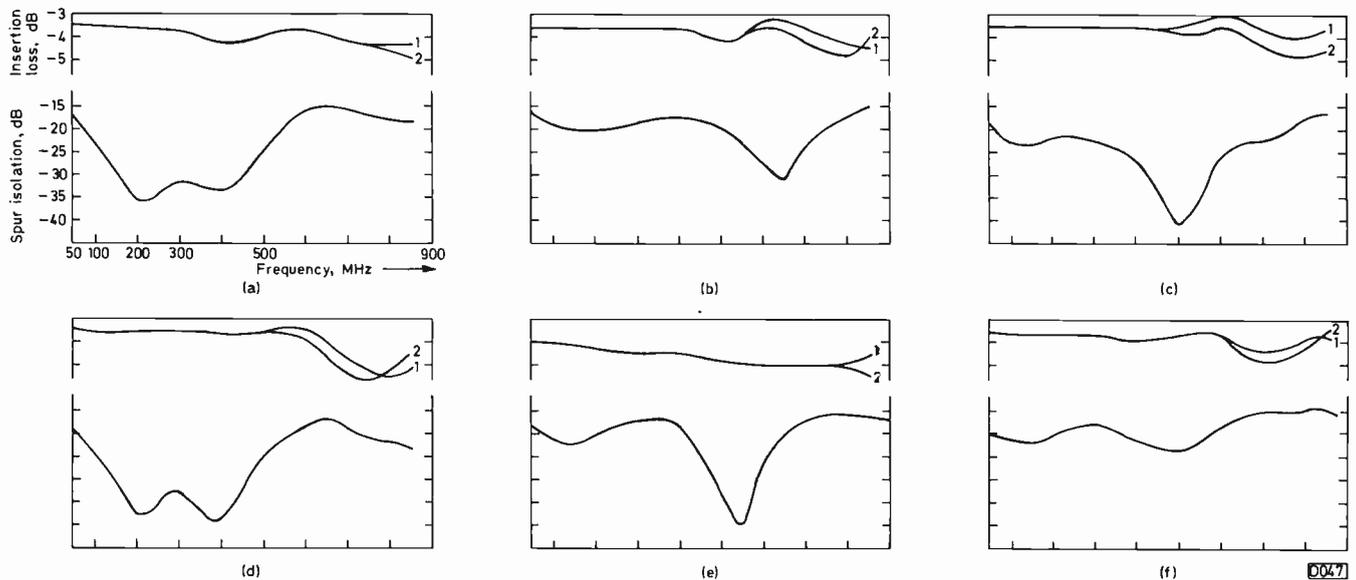


Fig. 1: Results of inductive splitter/combiner tests carried out by Fringe Electronics. (a) Antiference CS1000 unit. (b) Fringe unit. (c) Labgear CM6011. (d) ACL M1S/Maxview ST3. (e) Triax 7200. (f) Wolsey CS1/4.

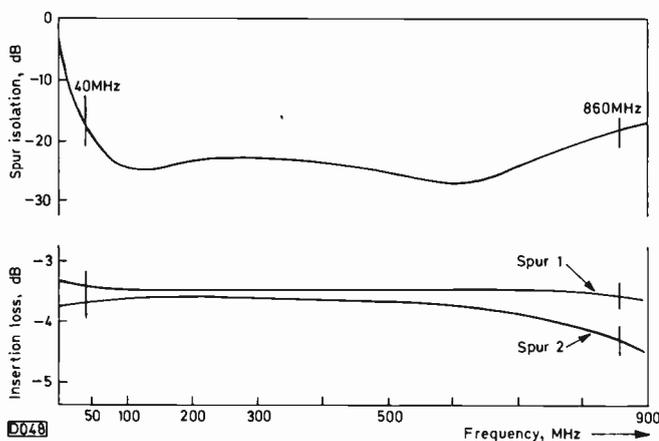


Fig. 2: Results of tests on the CM6011 carried out by Wolsey using different equipment.

ally show an insertion loss of around  $-3.5\text{dB}$  at v.h.f. and  $-4\text{dB}$  at u.h.f., with a spur isolation figure of about  $-20\text{dB}$ . My tests showed quite severe variations from manufacturers' specifications, so much so that fluctuations of several dB were occurring within a 10MHz spectrum at v.h.f. Clearly something was wrong and consultations were held with the various manufacturers. The upshot was that for accurate testing of even such a simple device as an inductive combiner/splitter expensive test equipment is necessary. Fringe Electronics tested all six filters for me, for both insertion loss and spur isolation. The results are shown in Fig. 1. Labgear tested their own unit, with the results shown in Fig. 2. These graphs show the performance of the better known splitter/combiner units at present available in the UK (the Maxview unit is made by ACL) and will enable enthusiasts to decide for themselves which unit best matches their particular needs.

The units are all housed in PVC/polythene boxes. The Antiference CS1000 is perhaps the most attractive, in black with a reusable ratchet type cable strap for mast mounting. The Fringe unit also has a reusable strap, the housing being a distinctive bright red. Triax's 7200 was the largest, housed in a standard "continental" plastic amplifier case with plated bracket/wing nut for mast mount-

ing. Labgear's CM6011/OS fits inside the standard dark green circular plastic box while the Maxview M1S is housed in a square, chocolate-brown PVC box. These two have once-only use ratchet straps for mast mounting. The most compact filter, again with once-only use strap, is Wolsey's cream coloured PVC CS1/4. All these units incorporate a PCB with various discrete components and a large ferrite toroid (or several smaller toroids). Constructional standards are good, with generally minimal lead lengths and boards designed for the purpose - the exception here is Triax which seems to use a general-purpose board.

All the units tested have d.c. throughput on one spur and the d.c. block on the other can generally be shorted to give a d.c. pass on both spurs - the blocking capacitor is usually of about  $0.001\mu\text{F}$ , mounted adjacent to the d.c. blocked spur connection.

In use as a splitter the insertion loss is less than with a resistive unit though an inductive splitter is more expensive.

An inductive combiner is useful where severe ghosting is present and two identical arrays are stacked (using equal feeder lengths!) to obtain a suitable polar response with reduced horizontal beam width.

Don't use a wideband inductive combiner on its own to link the outputs from two different channel group aerials, e.g. where an extra ITV station is required. Since the bandwidth of this type of combiner is over 40-860MHz, pickup of the local signals on the distant aerial and vice versa will produce a confusion of signals at the output. This is likely to be destructive for teletext reception and, depending on the relative phasing of the signals, ghost pickup etc., degraded pictures are likely to be obtained. For this application an appropriate frequency-selective diplexing arrangement with sufficient out-of-group rejection should be used.

Labgear have recently introduced a u.h.f. combiner/splitter, type CM9035, for the 470-860MHz band. It's housed in the usual round case and features stripline techniques. The insertion loss is less than  $-4\text{dB}$ , typically  $-3.5\text{dB}$ , with spur isolation  $-15\text{dB}$ . D.C. passage on both spurs is available. For combining the outputs from different channel group aerials, use 9034 group bandpass filters.

# Test Report: Tele-Part Pattern Generators

Eugene Trundle

In the seventeen years (ye gods, is it really that long?) that we in the UK have been in the colour television business, the evolution of the pattern generators we use for test purposes has largely mirrored the development of the sets themselves – in terms of price, circuit integration, current consumption and simplicity. The need for a pattern generator is diminishing with the latest colour sets. Gone are the days when a new set had to be completely set up at the time of installation, and even for routine servicing thereafter the pattern generator tends to stay in the van. Converging a TV set, once a source of satisfaction (or frustration?), is rapidly becoming a lost art, while modern decoders are virtually go/no go devices whose rare failures usually show up in the form of complete loss of colour or an absence or surfeit of one primary colour.

The need for specialised test patterns still exists however, and to meet it two generator “modules” have been introduced by Tele-Part of Wolverhampton. The simpler one, Telegen-1, is a pocket-size (10 × 7.5 × 4cm) instrument powered by an internal PP3 battery or an external power source via a 3.5mm jack socket. It provides five monochrome patterns – crosshatch, dots, white raster, horizontal lines and vertical lines. Its output is at around channel 32, via a flying lead with a standard u.h.f. plug.

On test I found that the twelve vertical and eight horizontal lines are sharp and well defined. The plain white raster is free from hash and patterning, and a scope test showed that the vision/sync ratio is correct at 7:3 on all patterns. The field sync pulse is of the “simple” type (a single broad pulse), but this is quite adequate for the job in hand. The u.h.f. output measured about 4mV, with virtually no spurious radiation on “ghost” channels and a complete absence of frequency drift. Current consumption came out at just over 10mA at 9V: I found that the unit will operate satisfactorily down to 6.3V, still without modulator drift. Good!

I next dismantled the unit and found a little fibreglass PCB mounted to the case by the pattern selector switch, which is a good quality, fully-enclosed type. Three i.c.s, three transistors and 57 other bits complete the ensemble, which I've no doubt will be very reliable.

Turning attention to its big brother Telegen-2, not very big actually at 12 × 10 × 4.5cm, I found a similar design and construction. This is the colour “module”, offering standard colour bars and plain rasters in red, green and blue, selected by a four-position switch. Telegen-2 works from an external 14-18V supply via a 3.5mm jack socket and provides a similar u.h.f. output to Telegen-1. It contains five chips, an 8.86MHz crystal, a 5V stabiliser i.c. and an on-board u.h.f. generator, all on a similar PCB to that used in Telegen-1. The switch and mounting method are also similar.

I was happy with the colour bars, which scope checks proved to be correct in every sense, particularly with regard to the chroma/burst/sync ratios and the burst timing (the latter is a weak point with some inexpensive colour generating equipment). The plain coloured rasters, particularly blue, were somewhat marred by a spurious patterning due to a form of internal signal breakthrough –

the effect disappeared when the instrument was dismantled, but returned when it was reassembled! This didn't distract much from the usefulness of the patterns however. The review model suffered from intermittent colour, due I believe to an internal dry-joint, and a tendency for the u.h.f. oscillator to drift with time and temperature, but this was probably pure bad luck and I wouldn't expect it to happen with other samples.


With some types of TV set it's not always possible to lose the colour completely – the colour control sometimes won't turn it down fully, and an efficient a.f.c. system with no cancelling switch may prevent you from mistuning to try for a monochrome display. For this reason, and since Telegen-1 has no grey-scale pattern, I'd have liked a colour/mono switch on Telegen-2 to facilitate easier grey-scale tracking adjustment with these “difficult” sets.

A mains power pack in the form of a “block” mounted directly on to the pin configuration of a 13A plug was supplied with the review pattern generator modules. At £4.55 one cannot complain on grounds of cost, but cheap and cheerful is the only way to describe it! It has six un stabilised output voltages (3V to 12V) which are selected by a slide switch. When modestly loaded by one of the Telegen modules it gave an output voltage between 42 and 90 per cent higher than specified, depending on range. This overvoltage caused no damage to either Telegen model during sustained tests, neither did incorrect polarisation of the (reversible!) plug on the d.c. output lead.
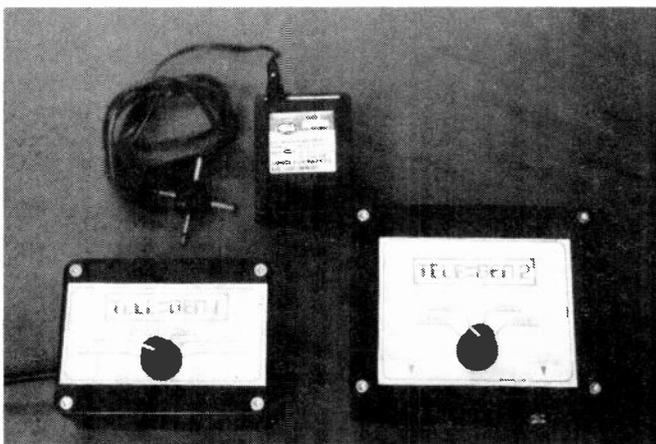
## Verdict

The odd negative comments in the above review must be considered in the light of the very reasonable price of the units – £17.20 for Telegen-1, £34.45 for Telegen-2 and £4.55 for the power supply, to which must be added £1.44 post and packing. I found them portable, convenient and useful, and would regard them as good value for money.

The units are available from Tele-Part, 13 Worcester Street, Wolverhampton, WV2 4LJ (telephone 0902-773 122).



The modules under review. Left the monochrome Telegen-1, right the colour Telegen-2, top the mains adaptor.

# TV Fault Finding

Reports from Philip Blundell, Eng. Tech., Paul Hardy, Keith Hamer, Garry Smith, Malcolm Burrell and Chris Avis

## ITT CMC301 Module

I've had a number of faults on the CMC301 remote control/frequency synthesis tuning module. Here's a typical one. The set wasn't tuning a station in – there was just snow on the screen. The scope was used to check the tuning voltage at connector TC12. For our transmitter (Sutton Coldfield) this is normally around 10V, but in this case a ramp voltage varying between 20V and 30V was present.

Checks were made on the counted-down local oscillator signal coming back from the tuner/i.f. module (plug FD1) but the waveform was correct – a 4V p-p sinewave. The frequency divider switching signal at plug FD3 was also correct – a 5V p-p squarewave. As the ramp on the tuning line wasn't going below 20V, the transistors in the D-A converter circuit were checked out of circuit. T1414 turned out to be leaky.

Other faults we've had in this area are as follows:

One inch wide bars across the picture due to C1425 (2.2 $\mu$ F) in the tuning voltage smoothing network going open-circuit.

Intermittent switching to standby due to C1419 (2.7pF) in the crystal clock oscillator circuit being leaky.

Stuck on standby due to the standby power supply mains transformer Tr1401 being open-circuit.

No tuning voltage due to C1072 (0.47 $\mu$ F blue tantalum) on the main panel being short-circuit. **P.B.**

## ITT CVC1100 Chassis

Here's an impossible one for you! The reported fault was no sound on VCR operation, and sure enough there was no sound on any signal tuned in via the VCR button. The interstation mute was operating: this is sensed by the TDA1940F sync separator/line oscillator i.c. but a replacement chip made no difference. The VCR button modifies the phase detector time-constant of course, so something in the line generator circuit just had to be out of tolerance. We checked the black electrolytics in the area (usual practice with IIT sets) to no avail. The digital voltmeter was next brought into play so that the voltages around the i.c. could be more carefully checked. The VCR select pin (pin 5) went high as it should have done, but went 1V too high (to 8.5V instead of 7.5V). The pin is fed via a potential divider (R601/R631) and R631, which is connected to chassis, was found to be open-circuit. **P.B.**

## Grundig GSC100 Chassis

This was a real pig! The field engineer said that every three weeks he had to resolder R607. Now this resistor normally runs very cool, because it's part of the start-up circuit, and goes open only when the line output stage fails. After a lot of soak testing and probing I found that on certain fairly cold days the set would trip in this way when first switched on. Much time elapsed before I concentrated on the e.h.t. control module, which controls the supply to the line output stage. It contains a 74-series monostable multivibrator chip. Now these digital chips like a supply of exactly 5V: go much higher or lower and

they won't work. This one is supplied by a rail that's stabilised by a 4.7V zener diode, Di2502. At times the voltage across this diode was as low as 3V. Replacing Di2502 cured the problem. **M.B.**

## Philips K30 Chassis

One of these sets had cross-modulation lines on the picture, as if the r.f. amplifier was being overloaded. A lot of time had been spent trying to locate the exact cause of the fault, which was cleared by replacing the tuner unit.

The fault on another of these sets was field collapse. A quick check revealed that there was no 32V rail, due to R1590 (1.2 $\Omega$ ) being open-circuit. When this was replaced it started to cook while the raster disappeared towards the bottom of the screen. The field scan coupling capacitor C1521 (1,500 $\mu$ F) was short-circuit. **M.B.**

## Thorn TX9 Chassis

Lack of width was the customer's complaint with this set. On test card the verticals were seen to be bowed while the width and pincushion controls had no effect. Obviously something to do with the EW correction circuit. A check at the emitter of the EW modulator driver transistor TR72 (TIP110) produced a slightly high voltage reading (not much higher than I'd have expected though – the normal reading is quoted as 0.15V). I decided to check the emitter resistor R251 (2.7 $\Omega$ ) which turned out to be high in value. The transistor seemed to be o.k., and replacing the resistor restored normal operation. **M.B.**

## Philips K30 Chassis

The set was brought in because it was tripping. All the usual things around the line output stage, even the deflection coils, had been checked by the field engineer. It was difficult to find the cause of the problem until I decided to try disconnecting pin 6 (excess current protection) of IC7322 (TDA2581Q) – not something to do lightly. A picture then appeared, modulated with 100Hz hum. The fault clearly lay in the power supply and was soon traced to the 285V supply reservoir capacitor C1460b. **M.B.**

## Philips K30 Chassis

A sudden drop in contrast with the control itself having no effect led us to suspect a fault in the contrast control network. The fault corrected itself before we could take any further action however and the set remained all right during a prolonged soak test. All we could do was to return it to the customer. Six weeks later it was back with the same fault. Beam limiting is also carried out via the contrast control network, so attention was paid to this. The sample point for the beam limiting is C1565 (0.068 $\mu$ F) which is connected to the earthy side of the e.h.t. circuit. This capacitor, which is close to the smoother at the bottom of the hinged panel, turned out

to be open-circuit. We've since had the same fault on two other K30s – in both cases it was intermittent.

**K.H.-G.S.**

### **Thorn TX10 Chassis**

We were called out to a six-month old Ferguson colour receiver fitted with the TX10 chassis. The customer had complained that the set was dead, but on arrival we found that it was tripping. Disconnecting the e.h.t. lead made no difference so we humped the set back to the workshop for a more detailed examination. Further checks revealed that the h.t. rail was higher than the specified 150V – the supply was building up and shutting down as soon as the overvoltage protection system came into action. Reducing the setting of the set-h.t. control stopped the tripping and restored normal operation but the control was at one end of its travel. Further checks showed that the feedback resistor R813, connected between the control and the 150V rail, was high in value at 160k $\Omega$  instead of 121k $\Omega$ .

**K.H.-G.S.**

### **Philips K30 Chassis**

“Dead” said the job card. Good we said, thinking we'd be in and out of the house in five minutes. The cause of this fault is usually the mains bridge rectifier's surge limiting resistor R6291 (4.7 $\Omega$ ) going open-circuit. Not this time however. The set worked for several minutes before the gain suddenly fell to zero, producing a blank raster. Lowering the chassis disturbed the fault and the picture and sound returned – but not for long. The tuner is unpluggable so we carried out a quick substitution. This made no difference. Back in the workshop we soon found the culprit. No, it wasn't the TDA2540 i.f. amplifier/detector i.c. A can of freezer (not a whole can incidentally) and a hairdryer led us to the a.g.c. reservoir capacitor C2147 (0.022 $\mu$ F) which is connected to pin 14 of the i.c. It was going leaky.

**K.H.-G.S.**

### **Thorn TX9 Chassis**

This set was fitted with the U725 remote control panel. The complaint was line drift. The line generator i.c. had already been changed so I put the set on soak and set up the line oscillator. Nothing happened till I switched off and on again. The line timebase was then *slightly* off frequency. Checks were made on the components around the chip but the only clue was obtained by changing channels. When the line was unlocked, pressing button eight (AV) restored lock until the set was switched off. Disconnecting R207 in the AV line resulted in immediate picture lock, as did disconnecting the AV connection on the remote control panel. Moving over to the remote control panel itself brought me to D916 (F425) which turned out to be leaky.

**M.B.**

### **Grundig 6100**

We've dealt with the basic models in the Grundig range for the past two-three years and have found them very predictable with regard to faults. Callouts usually concern tuning troubles, especially on earlier models. With the 6100 we would find that ITV and sometimes Channel 4 had to be retuned every few weeks. If the trouble persisted we would change the tuning voltage supply stabiliser – after removing the fiddly front panel and

button unit from inside the cabinet. This wasn't the right diagnosis however as the stations didn't drift to the same extent. We eventually found the true cause of the trouble. What happens is that the cabinet can warp and distort the press-button unit mechanics as the room temperature alters. This distortion affects mainly the middle positions of the assembly. The only cure we know is to remove the assembly, twist it round a little and put it back! In stubborn cases, try telling the customer to get the central heating thermostat checked.

Later models aren't affected in this way because the button unit is directly mounted on to a vertical side chassis assembly. We still get problems however. Customers somehow manage to engage all the buttons. They follow the instructions on delatching given in the Grundig booklet, then we're called out to a broken button unit damaged by hairpins, screwdrivers and, by the look of some of them, garden spades!

**K.H.-G.S.**

### **Thorn 3000/3500 Chassis**

Many of these BC (Before Ceefax) vintage sets are still in use. They're prone to displaying teletext “morse code” over the top couple of inches of the picture. I've tried a couple of suggestions relating to the field oscillator circuit without success but a recent consultation with the oracle at the Ferguson service department produced a simple and effective cure: increase the value of R441 in the flyback pulse limiting network across the field output transformer from 2.2k $\Omega$  to 5.6k $\Omega$ .

**C.A.**

### **Thorn 1500 Chassis**

The complaint was intermittent loss of picture, which turned out to be due to a faulty ring trap – the plastic had cracked with the result that the c.r.t. heater was shorting out. Whenever a tube is scrapped I always keep the ring trap if it's any good, so a spare was soon fitted and the set sent on its way. It was back a few days later however, the symptoms being no picture or sound with a visible raster. This time the ring on the replacement trap was grounding pin 1 of the tube so that the set's l.t. supplies, which are derived from the end of the heater chain, were removed. It turned out that the tube's evacuation pip was malformed, as a result of which the plastic base couldn't be pushed firmly home against the end of the tube – it sprang out. All that was necessary was to file the plastic base till it fitted the tube, then apply some adhesive to ensure that it stayed there.

**P.H.**

### **Philips G8 Chassis**

Every six months or so the 250mA fuse on the power supply panel would blow. No shorts could ever be found on any of the panels or in the wiring loom, a replacement fuse working for a time until it blew for the same inexplicable reason. This went on for a couple of years! There was obviously a fault somewhere however. Close inspection of the panels revealed a very slight burn mark on the component side of the combined i.f./decoder panel, adjacent to R212. R414, which is beside R212, was mounted horizontally instead of vertically, with the result that the earthed side of R414 was very close to the end of R212 that carries 205V. The 205V was intermittently flashing over from the end cap of R212 to the earthed leg of R414. Repositioning these resistors has provided a cure – to date!

**P.H.**

# ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

16029	1.58	25C1061	0.54	25D8988	2.67	AN320	4.97	BC171	0.10	BD186	0.38	BF137	0.11	BLY49	2.00	BY203/20	0.18
16181	1.13	25C1096	1.05	40408	0.45	AN322	4.38	BC172	0.09	BD188	0.66	BF152	0.28	BR100	0.20	BY206	0.17
16182	1.13	25C1104	2.00	40594	1.39	AN331	2.99	BC172B	0.24	BD175	0.39	BF153	0.52	BR101	0.37	BY207	0.22
16334	0.86	25C1106	4.12	40595	1.39	AN337	3.99	BC173	0.15	BD177	0.39	BF154	0.23	BR103	0.45	BY210-400	0.24
16335	0.72	25C1114	5.61	40636	0.86	AN340P	1.06	BC174B	0.24	BD179	0.44	BF157	0.23	BR888B	0.58	BY210-800	0.27
16446	0.89	25C1124	1.10	40871	1.39	AN355	3.36	BC177	0.18	BD181	0.40	BF158	0.16	BRC-M-300	1.58	BY210-800	0.30
16600	1.25	25C1151A	4.29	40872	1.39	AN362	1.47	BC178	0.23	BD182	0.90	BF159	0.16	BR116	0.80	BY223	0.85
16799	2.16	25C1152	4.25	60857	1.10	AN5111	2.34	BC179	0.23	BD183	0.90	BF180	0.28	BRC1330	1.80	BY224-400	0.90
16801	0.86	25C1157	4.12	74LS132	0.72	AN5132	3.99	BC182	0.08	BD184	1.10	BF167	0.34	BR300	1.82	BY225-100	0.79
16802	1.03	25C1162	0.95	74LS138	0.85	AN5250	3.33	BC182B	0.23	BD187	0.40	BF173	0.30	BRC4443	1.12	BY226	0.28
16803	4.81	25C1172	1.92	74LS157	0.79	AN5435	2.80	BC182L	0.09	BD189	0.35	BF177	0.56	BRC4444	1.12	BY227	0.44
16805	1.95	25C1195	2.83	74LS161AM	1.18	AN5610	6.75	BC182LB	0.12	BD190	0.29	BF178	0.26	BRC5236	0.70	BY228	0.54
17074	6.00	25C1213	0.75	74LS196	1.25	AN5613	3.72	BC183	0.09	BD201	0.54	BF179	0.32	BRC6109	0.75	BY255	0.97
17127	3.91	25C1226	1.32	74LS20	0.25	AN5620X	4.63	BC183L	0.09	BD202	0.54	BF180	0.32	BRC82	0.70	BY256	0.25
17376	1.43	25C1306	0.85	74LS244	1.65	AN6320N	3.89	BC183LB	0.23	BD203	0.54	BF181	0.25	BRC83	0.58	BY259	0.25
1N4001	0.05	25C1307	1.35	74LS30	0.29	AN6342	1.36	BC184	0.09	BD204	0.54	BF182	0.30	BRC84	0.58	BY476A	0.76
1N4002	0.05	25C1316	3.40	74LS367	1.05	AN6344	4.68	BC184L	0.09	BD207	1.00	BF183	0.35	BRC85	0.45	BYX10	0.26
1N4003	0.05	25C1364	0.49	74LS373	1.55	AN6363	10.20	BC184LB	0.23	BD208	1.00	BF184	0.30	BRC89	0.45	BYX10-350	0.48
1N4004	0.06	25C1383	1.39	74LS47	1.05	AN6551	0.56	BC186	0.24	BD222	0.44	BF185	0.35	BRY39	0.50	BYX55-350	0.25
1N4005	0.07	25C1398	0.51	74LS73	0.39	AN6552	0.52	BC187	0.18	BD225	0.44	BF194	0.15	BRY55	0.80	BYX71-350	0.67
1N4006	0.07	25C1410	2.17	74LS74	0.39	AN7145	2.04	BC204	0.14	BD228	0.57	BF195	0.12	BRY56	0.38	BYX71-600	0.85
1N4007	0.07	25C1413	3.80	74LS75	0.52	AN7150	2.22	BC207	0.12	BD229	0.63	BF196	0.15	BRS59	1.17	BYX94	0.18
1N4148	0.03	25C1505	0.58	74LS86	0.49	AN7151	2.05	BC212	0.10	BD231	0.45	BF197	0.15	BSS38	0.15	BYX94	0.18
1N4448	0.12	25C1578	6.67	74LS90	0.75	AN7156	2.05	BC212B	0.23	BD232	0.44	BF198	0.15	BSTBD1409	2.48	BYX94	1.09
1N5401	0.12	25C1617	3.35	74LS92	0.75	AN7158	2.34	BC212L	0.09	BD234	0.38	BF199	0.15	BSTBD1405	4.37	BZV15-C12	0.72
1N5402	0.13	25C1670	2.84	74LS93	1.49	AN7218	1.49	BC212LB	0.23	BD235	0.43	BF200	0.33	BSTCD146	2.25	BZV15-C12R	0.72
1N5403	0.14	25C1678	1.25	74LS95B	0.85	AP58078	4.25	BC213	0.09	BD236	0.45	BF216	0.32	BSTC0233	2.25	BZV15-C24	0.72
1N5404	0.15	25C1810	1.40	7805 TO-220	0.63	AS5805	1.43	BC213L	0.09	BD237	0.38	BF218	0.32	BSTC0246	4.51	BZV15-C24R	0.72
1N5408	0.18	25C1815	0.41	7805 TO-3	1.85	AU106	1.98	BC213LB	0.23	BD238	0.29	BF222	0.50	BSTC1233	3.91	BZV15-C30R	0.72
1N914	0.05	25C1829	2.01	7806	0.66	AU110	1.95	BC214	0.09	BD239	0.44	BF224	0.15	BSTC3146	0.71	BZV15-Range	0.16
1S44	0.06	25C1875	4.77	7808	0.54	AU113	2.16	BC214L	0.12	BD240	0.36	BF227	0.59	BSTCC0143	2.79	BZV15-C11	0.54
1S5012A	0.73	25C1891	3.35	7812 TO-3	1.05	AY102	2.62	BC214LB	0.23	BD240M	0.47	BF240	0.15	BSTC0843	3.06	BZV15-C15	0.54
1S521	0.09	25C1929	2.25	7812 TO-220	1.54	AY106K	1.89	BC225	0.24	BD241	0.45	BF241	0.15	BSTC0843	2.86	BZV15-C15	0.54
2S82	1.94	25C1942	5.70	7815	0.55	AY108	1.98	BC237	0.09	BD242	0.45	BF244	0.23	BSW68	0.38	BZV15-C30	0.54
2N1302	0.24	25C1945	4.11	7818	0.55	BA102	0.30	BC238	0.09	BD243	0.44	BF245A	0.33	BSX19	0.30	BZV15-C47	0.54
2N1303	0.34	25C1953	1.75	7824	0.55	BA1310 (IC)	1.72	BC238A	0.11	BD243A	0.50	BF255	0.18	BSX20	0.30	BZV15-Range	0.09
2N2218	0.38	25C1957	0.86	AC107	0.86	BA1320 (IC)	1.22	BC239B	0.08	BD244	0.44	BF256	0.25	BSX21	0.45	BZV15-Range	0.09
2N2219A	0.29	25C1959	0.36	AC117	0.39	BA1330 (IC)	1.82	BC251A	0.15	BD244A	0.77	BF256LC	0.38	BSY52	0.45	BZV15-C12	0.99
2N2222	0.34	25C1962	1.75	AC123K	0.39	BA145	0.07	BC252	0.12	BD245C	0.80	BF257	0.30	BSY79	0.46	BZV15-C18	0.99
2N2646	0.75	25C1969	2.92	AC128	0.28	BA154	0.08	BC258	0.22	BD246C	0.74	BF258	0.29	BT100A	1.46	BZV15-C24	0.99
2N2904	0.32	25C2027	2.67	AC138	0.08	BA155-01	0.12	BC261A	0.20	BD253	0.95	BF259	0.51	BT105	1.20	BZV15-C30	0.99
2N2905	0.39	25C2028	1.91	AC141	0.26	BA156	0.17	BC262	0.20	BD278A	0.80	BF262	0.51	BT108	1.31	BZV15-C30	0.99
2N2906	0.34	25C2029	1.49	AC142K	0.39	BA157	0.12	BC267	0.45	BD317	1.96	BF263	0.51	BT109	1.31	BZV15-C47	0.99
2N3053	0.24	25C2057	1.07	AC151	0.25	BA159	0.12	BC294	0.45	BD318	2.08	BF264	0.33	BT112	2.25	BZV15-C68	0.99
2N3054	0.90	25C2073	1.40	AC153	0.30	BA182	0.17	BC301	0.36	BD375	2.06	BF271	0.30	BT113	2.25	BZV15-C7V5	0.99
2N3055	0.55	25C2078	1.25	AC153K	0.36	BA222 (IC)	1.26	BC302	0.30	BD377	0.23	BF273	0.18	BT116	1.52	ZTK3X	0.39
2N3055H	0.77	25C2091	0.59	AC176	0.17	BA284/2	0.15	BC303	0.34	BD379	0.89	BF274	0.18	BT119	1.00	ZX18	2.47
2N3442	1.85	25C2122A	4.85	AC176K	0.40	BA301 (IC)	0.92	BC307	0.09	BD380	0.89	BF274	0.18	BT120	1.00	C1060	0.46
2N3702	0.12	25C2141	1.09	AC179	0.25	BA302	0.50	BC307A	0.14	BD410	0.44	BF336	0.27	BT121	2.25	C1129	0.52
2N3703	0.12	25C2166	1.35	AC183	0.85	BA311 (IC)	1.06	BC308	0.12	BD412	5.70	BF337	0.36	BT122	2.25	CA3110E	2.45
2N3704	0.12	25C2216	0.82	AC186	0.30	BA312 (IC)	0.98	BC308A	0.09	BD418	0.76	BF338	0.36	BT123	1.00	CA304A	3.18
2N3705	0.12	25C2233	2.20	AC186K	0.15	BA313 (IC)	1.28	BC309	0.15	BD433	0.33	BF355	0.36	BT125	2.25	CA3046	2.23
2N3706	0.12	25C2271	3.84	AC187	0.50	BA316	0.07	BC317A	0.11	BD434	0.39	BF362	0.54	BT126	2.25	CA3060	1.50
2N3707	0.14	25C2278	1.03	AC187-01	0.40	BA317	0.07	BC323	0.32	BD435	0.42	BF363	0.54	BT128	2.25	CA3065	1.37
2N3711	1.85	25C2335-KIT	7.61	AC187K	0.39	BA318	0.08	BC327	0.15	BD436	0.42	BF371	0.45	BT128P	2.79	CA3069	3.15
2N3772	1.55	25C2526	1.70	AC188	0.33	BA328 (IC)	1.00	BC328	0.10	BD437	0.41	BF391	0.36	BT129	2.25	CA3089E	1.20
2N3773	1.85	25C2551	0.95	AC188-01	0.40	BA333 (IC)	1.24	BC337	0.08	BD438	0.44	BF393	0.90	BT151-800R	1.47	CA3080	1.35
2N3819	0.28	25C2570	1.80	AC188K	0.39	BA401 (IC)	1.58	BC338	0.10	BD441	1.29	BF417	1.20	BT151-500R	1.20	CA3094	2.80
2N3823	1.06	25C2570A	0.95	AC193K	0.59	BA511 (IC)	1.98	BC360	0.30	BD442	0.56	BF418	1.70	BT18018	2.25	CA3131EN	2.03
2N3904	0.56	25C264A	4.38	AC194K	0.59	BA521 (IC)	1.98	BC368	0.23	BD443	0.54	BF422	0.26	BT180218	2.20	CA3132EN	2.80
2N3908	0.58	25C2671	1.99	AD140	0.56	BA532 (IC)	1.80	BC380	0.23	BD444	0.54	BF423	0.26	BT18024	4.02	CAH78023N	6.03
2N4101	1.10	25C2728	0.95	AD142	0.56	BA536 (IC)	2.72	BC441	0.40	BD509	1.29	BF435	0.49	BT18124	4.44	CBF16848N-07	1.41
2N4240	3.00	25C2772	1.27	AD143	0.56	BA630A (IC)	2.85	BC454	0.32	BD510	0.45	BF450	0.43	BT18214	5.44	CD1001	0.24
2N4443	1.25	25C283	1.28	AD146	1.45	BA643 (IC)	3.80	BC455	0.32	BD518	1.36	BF451	0.26	BT18224	2.70	CD4002	0.26
2N4444	1.12	25C288	0.81	AD149	0.10	BAV10	0.10	BC480	0.38	BD519	1.36	BF457	0.37	BU105	1.86	CD4008	0.94
2N4914	0.85	25C301	0.99	AD182	0.30	BAV18	0.10	BC481	0.42	BD529	0.38	BF458	0.35	BU106	2.25	CD4011	0.23
2N5054	0.64	25C458	0.55	AD282	0.95	BAV20	0.10	BC482	0.27	BD530	0.80	BF459	0.35	BU108	1.90	CD4012	0.24
2N5293	0.45	25C485	0.83	AF114	3.26	BAV21	0.17	BC483	0.58	BD533	0.80	BF465	0.54	BU109S	1.90	CD4013	0.37
2N5294	0.45	25C508	3.36	AF115	0.79	BAV12	0.10	BC485	0.58	BD534	0.44	BF466	0.27	BU110	2.52	CD4016	0.37
2N5296	0.40	25C515A	1.28	AF116	0.79	BAV13	0.10	BC485	0								

# ECONOMIC DEVICES,

REGISTERED OFFICE: 14, BEE LANE,  
FORD HOUSE, WOLVERHAMPTON WV10 6LF.

All goods should be delivered  
within 4 working days.

ESM532C	4.18	LM1302P/N	1.50	MPSU105	0.78	SAA5010	4.90	SN74190	1.81	T8029V	4.41	TBA395	1.35	TDA1230	2.93	TDAS903	2.80
ESM632C	4.18	LM1310P/N	1.25	MPSU110	0.78	SAA5012	6.50	SN7420N	0.30	T8032V	4.41	TBA395Q	1.35	TDA1235	3.52	TDAS913	2.40
ESM732C	4.18	LM3055N	0.77	MPSU155	0.90	SAA5020	5.25	SN7430	0.28	T8033V	0.73	TBA396	1.80	TDA1270	2.04	TE527	1.25
ETT6016	2.85	LM317CKC	1.30	MPSU166	0.30	SAA5030	7.50	SN7440N	0.24	T8035V	0.86	TBA400	2.17	TDA1320	1.05	TE538	1.35
FND500	5.25	LM3407	1.23	MPSU180	1.20	SAA5040A	14.75	SN7473	0.56	T8036	0.94	TBA440P	1.55	TDA1330	1.05	TE626	1.35
FT3055	1.85	LM3407S	0.75	MPS110	0.30	SAA5050	0.50	SN7474N	0.72	T8037	1.41	TBA480	1.92	TDA1370	1.90	TEA1002	3.15
GF756	0.82	LM3407T2	0.75	MR812	0.46	SAA661B	1.80	SN7490AN	0.93	T8041V	0.86	TBA480Q	1.67	TDA1365	6.35	TDIA009	0.96
GF759	1.82	LM3407S	0.75	MR914	0.85	SAA700	3.00	SN75110N	0.75	T8044V	0.86	TBA500PD	4.95	TDA1412	0.95	TEA1020SP	5.34
GF761	0.78	LM342N	0.56	MVS24002	0.52	SAB1009B	4.53	SN78001ANQ	2.25	T8045	1.80	TBA510	1.55	TDA1420	1.40	TEA1067	0.46
GH3F	1.85	LM384AN01	1.84	MVS480	0.50	SAB1046P	3.66	SN78003N	2.81	T8049	1.10	TBA510S	6.39	TDA1470	2.63	TC106C	0.55
HA11211	2.30	LM387CN	1.30	MVS480-02	0.55	SAB3011	7.34	SN78013N	3.63	T8052V	0.76	TBA520	1.67	TDA1512	2.20	TC106M	0.55
HA11215	4.80	LM748	1.85	ME545B	2.95	SAB3012	5.34	SN78013ND	2.85	T8058	0.46	TBA520Q	1.35	TDA1570	3.65	TC116D	0.80
HA11225	3.90	LM8360	2.78	ME545B	3.00	SAB3013	3.28	SN78013NDG	8.07	T8059	1.05	TBA530	0.86	TDA1700	5.56	TC144	0.85
HA11228	7.56	LM8361	2.78	ME545B	1.95	SAB3021	7.18	SN78023N	2.35	T8061V	1.89	TBA530Q	0.85	TDA1705	1.25	TC145	0.70
HA11229	2.51	MI024	2.55	ME5534N	1.48	SAB3022B	12.34	SN78023ND	1.84	T8063V	0.86	TBA540	0.98	TDA1908	2.95	TC147	0.70
HA11235	3.00	MI025	4.76	ME555	0.34	SAB3022B	11.18	SN78033N	2.33	T8065V	2.16	TBA540Q	1.18	TDA1910	2.30	TP120	0.56
HA1124	4.70	MI124	2.54	ME555	0.75	SAB3024	4.77	SN78105N	2.36	T8069V	0.87	TBA550	1.95	TDA1940	2.54	TP110	0.48
HA11244	4.32	MI130	4.80	ME555B0N	3.16	SAB3029	4.75	SN78110N	1.13	T8071V	1.27	TBA550Q	2.25	TDA1950	2.54	TP112	0.80
HA1125	3.90	MI191	5.74	ME555N	1.28	SAB3210	2.45	SN78115AN	1.46	T8073V	5.81	TBA560C	0.86	TDA2002	1.20	TP117	0.86
HA11251	3.90	MI193	10.55	ME645BN	3.00	SAB4309	12.75	SN78131	1.74	T8074V	1.52	TBA560Q	1.15	TDA2003	1.05	TP120	0.70
HA1137W	2.57	M51102L	4.82	ME648N	3.00	SAF1001	2.30	SN78226D	1.20	T8076	0.92	TBA570	1.55	TDA2004	2.52	TP121	1.00
HA1138	1.56	M5115P	4.34	ME650N	3.94	SAF1002	5.82	SN78227N	0.80	T8078	0.39	TBA570A	1.56	TDA2006	1.25	TP125	0.56
HA11414	2.50	M51231P	2.75	ME645BN	3.00	SAF1003	11.85	SN78228N	2.97	T8079V	1.25	TBA570Q	1.95	TDA2010	2.79	TP127	1.30
HA1144	6.38	M5124P	4.30	MPI1106	0.10	SAS5010	1.80	SN78229N	2.31	T8085V	1.26	TBA625A	1.37	TDA2020	2.75	TP2955	0.70
HA1156	1.23	M5134-9341	3.75	QA200	0.10	SAS5010	1.80	SN78242	4.75	T8089V	6.15	TBA625B	1.97	TDA2030	1.64	TP29A	0.51
HA11580	7.80	M51394P	6.25	QA47	0.10	SAS5010	2.97	SN78243	4.75	T8091	2.55	TBA625C	1.97	TDA2040	1.85	TP29B	0.47
HA1160	3.45	M5142P	4.30	QA90	0.07	SAS5010	2.97	SN78243	2.51	T8093V	1.03	TBA641A12	3.75	TDA2150	5.63	TP29C	0.40
HA1166	3.00	M5143P	6.80	QA91	0.80	SAS5010	2.97	SN78243	1.61	T8095V	1.82	TBA641B1	2.07	TDA2151	1.75	TP3055	0.85
HA1167	5.13	M5144P	3.42	QA95	0.08	SAS5010	2.97	SN78243	2.80	T8097V	0.93	TBA651	2.60	TDA2160	3.64	TP30A	0.41
HA11711	16.13	M51513L	2.06	OC28	0.98	SAS5010	2.97	SN78243	2.80	T8098V	2.80	TBA673	1.35	TDA2161	1.80	TP30B	0.63
HA11713	6.70	M51515BL	3.10	OC29	1.95	SAS5010	2.97	SN78243	1.90	T8099V	1.35	TBA700Q	2.19	TDA2190	3.11	TP31B	0.35
HA11714	7.05	M51516L	3.40	OC35	0.98	SAS5010	2.97	SN78243	1.80	T8102P	4.36	TBA720	2.85	TDA2190	1.82	TP31C	0.65
HA11715	7.05	M51517L	2.90	OC36	1.16	SAS5010	2.97	SN78243	1.58	T8107	1.46	TBA730	1.75	TDA2520	2.15	TP32B	0.35
HA11718	6.79	M5152L	1.00	OC44	0.40	SAS5010	2.97	SN78243	1.80	T8107A	1.58	TBA780	3.00	TDA2522	2.81	TP33C	1.25
HA11724	15.80	M5152Z	4.90	OC45	0.40	SAS5010	2.97	SN78243	1.60	T8108AP	0.80	TBA780	1.55	TDA2523	2.75	TP34	1.07
HA11725	16.80	M5191P	4.49	OC75	0.40	SAS5010	2.97	SN78243	4.55	T8108AP	0.78	TBA800	0.00	TDA2524	4.50	TP41A	0.39
HA1180	4.80	M5192	2.00	ON188	1.70	SAS5010	2.97	SN78243	3.15	T8108B	2.84	TBA810AS	1.46	TDA2525	2.96	TP41B	0.28
HA1203	1.56	M53273P	0.92	ON236	1.90	SAS5010	2.97	SN78243	3.15	T8107P	1.52	TBA810S	1.46	TDA2530	2.19	TP41C	0.44
HA1306	1.74	M53274P	1.29	OT112	0.98	SAS5010	2.97	SN78243	2.35	T8107P	1.35	TBA810T	1.46	TDA2532	2.51	TP42A	0.39
HA1322	1.74	MA06	0.97	OT121	0.70	SAS5010	2.97	SN78243	0.30	T8107P	1.35	TBA820	0.63	TDA2533	2.09	TP42B	0.71
HA1339	1.76	MA8001	0.74	PD144	2.83	SAS5010	2.97	SN78243	1.35	T8107P	1.95	TBA820M	1.85	TDA2540	1.95	TP42C	0.44
HA1342	1.90	MB3705	1.82	PT1017	2.43	SAS5010	2.97	SN78243	2.80	T8107P	1.95	TBA890	1.25	TDA2541	1.95	TP47	0.85
HA1350	2.97	MB3712	2.85	PT2014	2.76	SAS5010	2.97	SN78243	1.30	T8107P	1.95	TBA900	2.85	TDA2545Q	3.16	TP48	0.63
HA1365	3.85	MB3713	1.30	PT6042	1.82	SBA550B	1.95	SN78600	2.15	T8108N	1.41	TBA920	1.50	TDA2560	1.97	TP49	3.20
HA1366WR	1.82	MB3730	2.94	R1038	1.99	SBA550B	1.46	SN78600	1.35	T8108P	3.25	TBA920Q	2.10	TDA2571A	2.81	TS43	1.28
HA1367	3.20	MC13002	4.86	R1039	1.99	SBA550B	1.99	SN78622	1.50	T8108P	1.86	TBA940	1.75	TDA2575A	2.95	TS90	0.22
HA1368	1.89	MC1303P	1.96	R2008B	1.29	SC9488P	1.99	SN78622	0.62	T8109SP	1.54	TBA950	1.50	TDA2576A	2.95	TS91	0.26
HA1368R	1.86	MC1307P	1.90	R2009	1.29	SC9488P	1.46	SN78623	2.31	T8109SP	1.84	TBA970	2.00	TDA2577	5.31	TL07CP	2.02
HA1370	2.97	MC1310P	1.25	R2001B	1.29	SC9504P	1.50	SN78640	1.25	T8108P	1.40	TBA970Q	2.98	TDA2581	1.95	TM51000NL	10.78
HA1377	2.80	MC1327P	1.20	R2023	1.29	SC9504P	1.46	SN78640	3.84	T8108P	3.37	TBA990	1.65	TDA2582	1.98	TM53748NS	11.66
HA1389	1.82	MC1330P	1.23	R2030	1.29	SC9504P	4.38	SN78651	1.35	T8108P	1.35	TBA990Q	1.95	TDA2582	2.80	TM54116	1.87
HA1389R	1.74	MC1349P	1.20	R2057	2.16	SC613	7.80	SN78651N	2.25	T8122B/P	0.58	TBAZ31	2.33	TDA2591	2.80	TV106	1.20
HA1392	2.80	MC1350P	1.10	R2265	1.95	SG629	6.38	SN78651N	1.35	T8122P	2.00	TC4001	1.29	TDA2591Q	2.80	TV610B	2.70
HA1397	2.97	MC1351P	0.75	R2305	1.07	SG633	9.37	SN78651N	0.98	T8130P	1.15	TC4033BP	1.95	TDA2593	2.24	U05G	1.03
HA1398	2.80	MC1352P	1.01	R2306	1.23	SH-1020N	10.70	SN78705	3.38	T8136AP	0.95	TC150	1.62	TDA2594	2.80	U143M	2.80
HA1406	2.80	MC1357P	1.95	R2322	1.26	SH-1125HD	4.76	SN78705S	3.99	T8137P	1.15	TC160B	0.65	TDA2600	5.00	U3700	0.55
HA14723	5.40	MC1358P	1.55	R2323	1.23	SH-1130N	3.99	SN78709N	3.99	T8137P	0.81	TC2700	1.55	TDA2610	2.53	U3700C	0.44
HBFA00DAF	2.25	MC14001	7.15	R2348	1.82	SKE2/08	0.79	SN78709N	4.85	T8146P	3.54	TC2705	1.95	TDA2611A	1.25	UA723CA	3.02
HD4480	15.80	MC14011	0.23	R2354A	1.82	SKE2F/1/04	1.28	SN78709N	4.23	T8146P	2.10	TC2705Q	1.65	TDA2611AQ	2.55	UA758PC	5.06
HD44801A05	15.90	MC14013	0.37	R2354B	1.82	SKE2G/2/04	0.95	SN78730	4.23	T8146P	1.51	TC2820A	2.06	TDA2612	4.25	UA783PC	3.02
HM6231	8.50	MC14016CP	0.37	R2441	1.23	SKE2G/3/04	0.95	SN78810N	0.82	T8153P	4.53	TCA420A	1.96	TDA2620	1.56	UA170	2.14
HM6232	7.71	MC14025	0.54	R2443	0.80	SKE4F/1/02	1.28	SN78920N	2.83	T8161P	5.08	TC440A	1.65	TDA2630	2.34	UA180	1.35
HM9102	2.92	MC14049UBC	0.52	R2461	2.10	SKE4F/1/06	0.86	SN94041	3.45	T8162P	4.25	TCA4500A	1.95	TDA2631	2.48	ULN1265	2.14
HM9104	2.94	MC1438R	0.95	R2477	0.92	SKE4F/2/06	2.10	SN94042	3.95	T8162P	4.25	TCA500A	1.90	TDA2640	2.25	ULN2204	7.00
HT4207	15.80	MC14493P	2.56	R2501	1.16	SKE4F/2/08	0.80	SP6385	5.90	T8171P	2.58	TC640	2.63	TDA2643	6.33	ULN2216F	1.95
IS689	1.87	MC14510BAL	3.15	R2540	1.80	SKE4G/2/02	0.87	STAA411	0.27	T8172P	1.23	TC660	1.85	TDA2643	2.95	UPC1001H	5.70
IS751	1.87	MC14565BCP	3.15	R2540X	3.80	SKE5F/3/10	1.45	STK0029	3.42	T8178P	2.25	TC660B	2.84	TDA2652	7.85	UPC1009C	2.50
ITV2003	0.20	MC1712	3.52	R2615	0.80	SL1310	2.85	STK0039	4.80	T8193P	4.44	TC730	3.63	TDA2652	2.95	UPC1020H	2.12
K174YP	2.95	MC7724CP	3.17														

# Simple Pattern Generator

Barry J. Thurlow

This pattern generator was originally devised for monitor alignment and for the go/no-go testing of video switches and cables. For this purpose it provides a standard 1V peak-to-peak composite video signal (0.3V sync pulses) when terminated externally with a 75Ω load resistor. An Astec modulator can be incorporated however to obtain a u.h.f. output. The circuit is based around a Ferranti ZNA234E TV pattern generator i.c., with additional circuitry for mixing and providing a reasonable 75Ω output. The whole lot fits into a 705 Verobox which has a compartment for the four 1.25V Nicad batteries used for

the supply. The small PCB that holds the circuit has been designed to fit into this box.

Fig. 1 shows the circuit. The ZNA234E generates the patterns by counting down etc. from a 2.5MHz crystal oscillator. Vertical line width is set by an RC combination at pin 10 – in practice R8 and the stray capacitance of the pin. These together give a line width of about 100nsec.

The base of output transistor Tr1 is biased at 2.7V by R3 and zener diode D1. This holds the voltage across R4 at a fairly constant 2V. The junction of Tr1 and R4 is used as a current summing point for the video and sync signals.


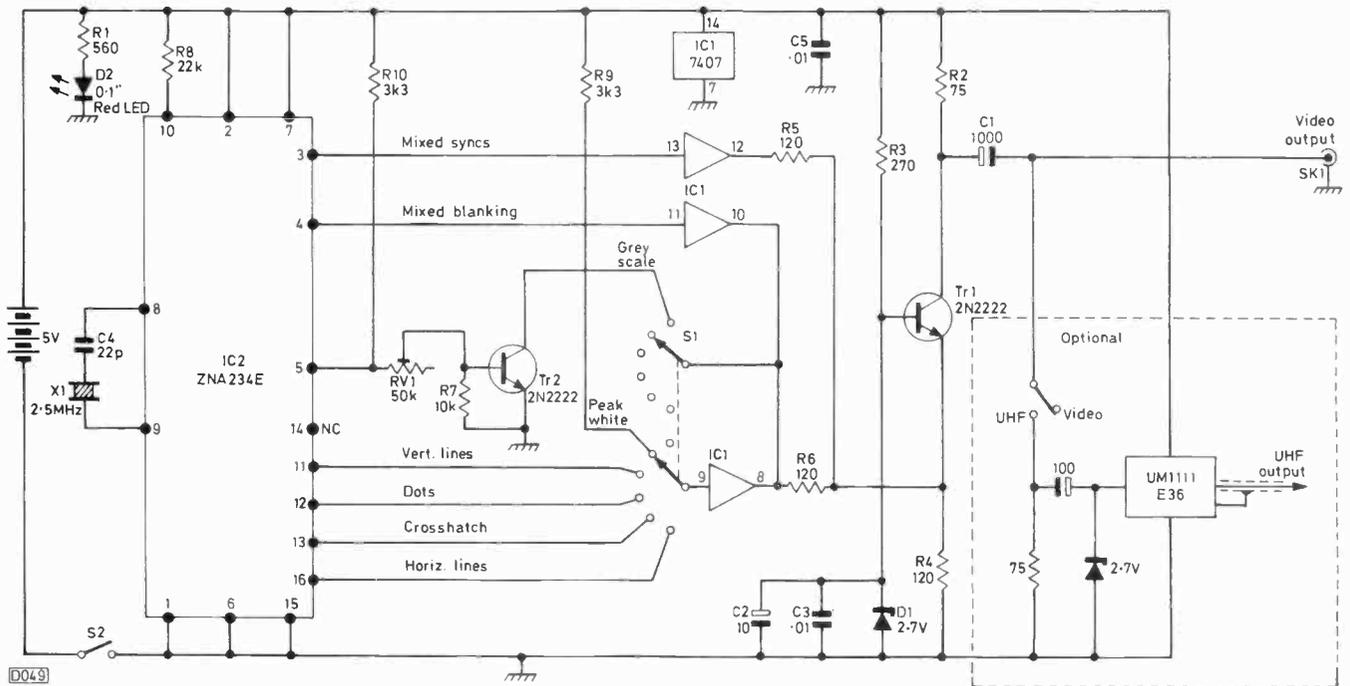
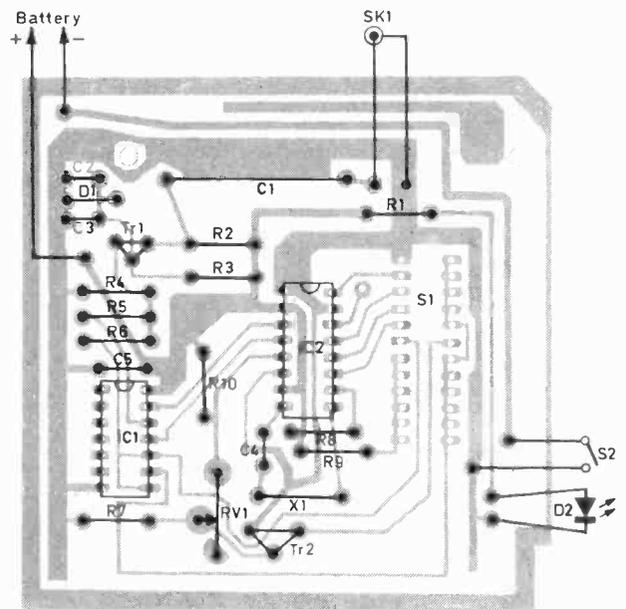


Fig. 1: Circuit diagram.

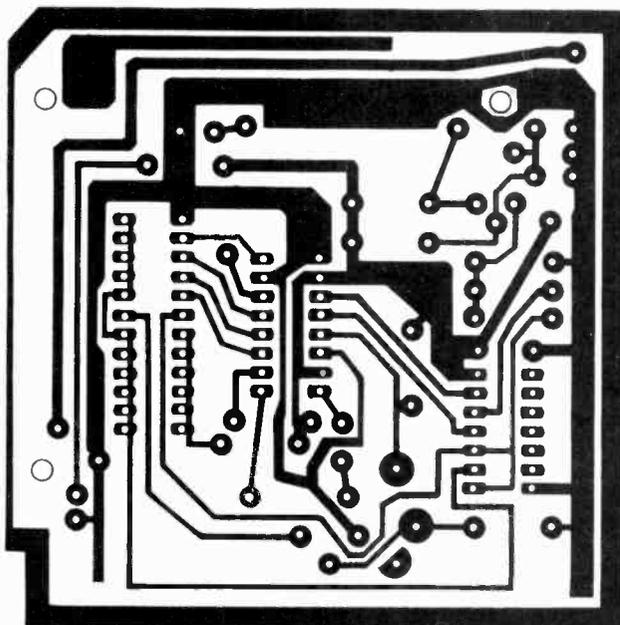


○ Mounting holes (3)

Fig. 2: PCB print pattern, actual size, left; component layout right. C1 25V axial, C2 6.3V tantalum, C3 and C5 disc ceramic, C4 polystyrene or plate ceramic.

By virtue of the transistor's gain, a composite signal of about 2V peak-to-peak is developed across R2. The various outputs from IC2 are buffered by IC1 (Tr2 in the case of the grey-scale pattern).

If the u.h.f. version is used, the output from the modulator can be connected to the front panel BNC socket. Alternatively a second socket and selector switch could be used. Although the UM1111 modulator should be operated with a 7.5V supply it seems quite happy operating at 5V and quite reasonable results were obtained with the capacitive coupling arrangement shown. There's room in the case for the modulator – it can be conveniently mounted inside the top section above the battery compartment. The modulator's bandwidth is limited, so I wouldn't recommend using its output for signal adjustments. The picture provided is quite suitable for adjusting picture geometry however.

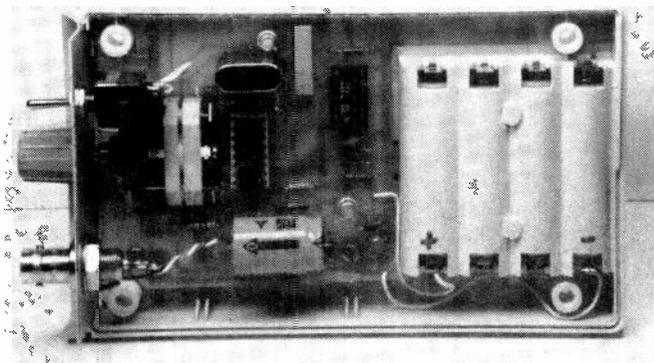The board was originally designed for use with an ITT single-pole, twelve-way switch (see photos). This however is not a stock item. We suggest the use of an RS 327-951 two-pole, six-way rotary switch mounted on the front panel with wired links to the board. The seventh position originally provided, blank raster, is no longer available. To obtain this feature, pin 9 of IC1 was connected to chassis



View of the unit with top cover removed.

with the other switch positions left open.

The case was obtained from Maplin and the ZNA234E from Technomatic Ltd., 17 Burnley Road, London NW10 1ED. An alternative source for the i.c. is Celdis Ltd., 37-39 Loverlock Road, Berks RG3 1ED (0734 585 171). It sells for around £10.

## Suspect Transistors

George Wilding

As a general rule, the presence of normal working voltages at the collector, base and emitter of a transistor will indicate that it's operational. Where the connection is to the supply line or chassis via a low value resistor or the connection is made to a potential divider however the voltage change with a defective transistor may be small. Fortunately the condition of a transistor can usually be checked in situ with near certainty by making forward and reverse resistance checks across the junctions and a collector-emitter check for possible punch-through. On occasion however you get symptoms suggesting that a transistor is faulty even though these resistance checks indicate otherwise. Here are a couple of examples.

The first was an ITT hybrid colour set (CVC8 chassis) with total lack of line and field lock. The sync separator transistor was naturally suspect but resistance checks at the junctions proved it to be in order. As Fig. 1(a) shows, the collector is connected to a potential divider. It should normally record 65V but in this case the reading was nearer 100V. Considering the proportions of the values of the two resistors in the potential divider network, this suggested that the transistor was cut off all the time. Now this wouldn't be caused by lack of signal at its base, since the input to a sync separator is used to develop the cut-off bias (except during the sync pulse periods). The only possibility therefore was that the 3.3MΩ base bias resistor R330 was open-circuit – a high-value base bias resistor is generally used with a transistor acting as a sync separator to ensure that it saturates each time a sync pulse arrives. What usually happens is that the resistor goes high in value, giving weak field lock. Since the 3.3MΩ resistor couldn't be checked in situ a replacement was fitted, restoring perfect timebase locking.

The second case concerned a Thorn monochrome set fitted with the 1500 chassis, the fault this time being no

sound and an unmodulated raster. This could have been due to a tuner, i.f. amplifier or a.g.c. fault. Transistors used as a.g.c. amplifiers seem to be more prone to breakdown than those used in i.f. amplifier stages, so the a.g.c. amplifier transistor VT3 – see Fig. 1(b) – was checked. As is usual in a transistor i.f. strip, forward a.g.c. is used, i.e. the controlled transistors are driven on harder as the signal strength increases. Under no-signal conditions the voltage at the collector of VT3 should be about 0.4V. In fact the collector was at almost the supply line voltage. As a result the controlled transistor would be saturated and thus unable to provide any significant degree of signal amplification.

It seemed likely that VT3 was defective, with one of the junctions open-circuit or the base-emitter junction short-circuit. Resistance checks on the transistor proved that it was perfectly all right however. Further, placing a short from its collector to chassis or to its emitter restored the sound and vision signals. So the cause of the fault was inadequate forward base bias.

The possibilities were an open-circuit or incorrect value resistor in the base circuit, one of the associated electrolytics being leaky or short-circuit, or maybe the a.g.c. rectifier diode W1 leaky (it normally conducts on the tips of the sync pulses only). In fact the diode had a very low reverse resistance, thus placing R34/5 in parallel with R2.

Suspect transistors are often completely innocent!

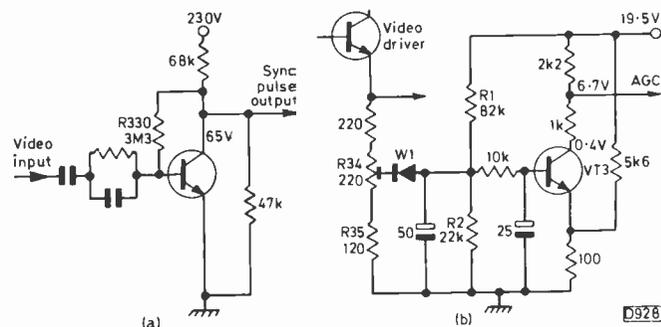


Fig. 1: Sync separator (a) and a.g.c. (b) circuits.

# Goodbye to 405 lines

Pat Hawker

The first week of January 1985 sees the end of the TV system that established television in Britain ahead of the rest of the world. All remaining BBC and IBA 405-line v.h.f. transmitters will be switched off. Band I (41-68MHz) and Band III (174-214MHz) will be lost to Britain for TV use, though v.h.f. will continue to provide the main TV channels in virtually every other country. The UK alone is firmly committing its TV future to u.h.f. and to direct broadcasting from satellite in the 12GHz (and later possibly 40GHz) band.

It's the end of the black-and-white system with which the BBC launched the world's first public high-definition service in 1936. Its death has been lingering, entering the terminal phase as long ago as November 1969 when the three-channel colour 625-line u.h.f. service came into being. Broadcasters and the trade have had a decade when few used the 405-line transmissions, but those few who did presented problems with spares and the need for cannibalisation to keep ageing sets going.

## Performance

Yet surely 405 deserves a respectful and affectionate wake before the final burial. It served us well. It was not the system's fault that low-cost line output transformers subjected many viewers to a penetrating 10,125Hz line whistle, nor that the pictures viewed were too often off-

grey rather than with correct gradations from black to white due to the use in TV sets of a.c. coupling without d.c. restoration.

At its best, on studio or transmitter control room monitors, 405-line pictures were far from negligible. The positive vision modulation may have been all too susceptible to ignition interference but could give a fine peak white. The 4½in. image orthicon cameras of the 1960s gave superbly crisp studio and OB pictures. Admittedly the 377 active lines did show the line structure, though the public seemed to have little inclination to eliminate this by making use of the spot wobble circuit that was a feature of some sets.

The 405-line transmissions could be comfortably accommodated in 5MHz of precious r.f. spectrum. The IBA could have provided two nationwide channels in Band III, as originally intended, had not the BBC and the radioastronomers intervened! Even 405-line colour was pretty good, though in the end the IBA (then the ITA) and ITV hopes of putting out colour on v.h.f. were defeated when the BBC convinced the Television Advisory Committee that Sporadic E interference would make colour in Band I a non-starter!

The present 625-line system gives us marginally better pictures of course, but the time to have dropped 405 without tears would have been in 1946, when EMI proposed a 605-line system for post-war television.


## History

The 405-line system has served us for almost fifty years, with a six and a half year interruption due to the 1939-45 war. It was "invented" one Sunday morning in 1934 in a private house in the London borough of Ealing, the home of that brilliant electronics engineer Alan Dower Blumlein, a member of the EMI and later the Marconi-EMI research team led by Sir Isaac Shoenberg. Alan Blumlein, a perfectionist, had come to EMI as part of the takeover of Columbia records.

The EMI team started to develop television in the mechanical, low-definition era, but soon turned to the concept of all-electronic TV originally proposed by A.A. Campbell Swinton in 1912. The key element was the development of the Emitron electronic camera – initially started as an independent project but in its later stages gaining significantly from the work in the USA of Vladimir Zworykin at RCA, a firm with which EMI had patent and financial links.

Following months of bickering between Baird and EMI, with the BBC anxious to end its agreement with Baird to operate an "experimental" 30-line service in the medium waveband, the government in 1934 set up a Television Committee, chaired by Lord Selsdon, to consider what should be done, after investigating the work going on in Germany and the USA. In 1935 the committee recommended an early start to a UK v.h.f. service with a minimum of 240 lines, 25 frames. Both Baird and Marconi-EMI were invited to supply the transmission equipment. A Television Advisory Committee would make final decisions.

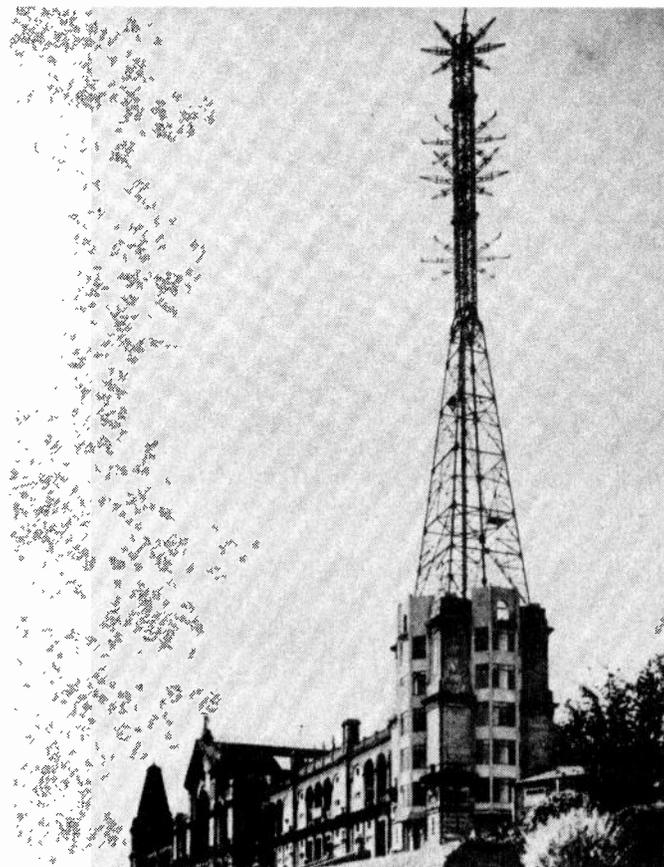It was intended that there should be a single standard,



Back at the beginning: Alexandra Palace in August 1936. The cantilever arms on the mast supported the wire transmitting aerials which were stretched vertically between pairs of arms. Photo courtesy BBC.

possibly 240 lines as advocated by Baird or possibly 243 lines interlaced as initially proposed by Marconi-EMI. Electronic interlacing to reduce flicker had been patented by RCA, although an earlier form of mechanical interlace had been used by Baird and others. But the war between Baird and Marconi-EMI could not be resolved. To compound the problem the EMI team next proposed not 243 but 405 lines.

Back to the house in Ealing where, one Sunday morning in 1934, Blumlein, Cork and Eric White had met to discuss how to breadboard a suitable waveform generator to test a system that would put EMI significantly ahead of the Baird company. Baird's 240-line system was developed partly by Captain West and drew on techniques developed by Fernseh in Germany, a company which was loosely linked with Baird. The easiest way of up-grading the 243-line interlaced system proposed by EMI, while retaining this system as a basis for comparison, was simply to change one divide-by-three circuit into a divide-by-five one. Since  $243 \times 5/3 = 405$ , this was the system developed and later confirmed by Shoenberg and put into the specification offered to the BBC.

The TAC urged Baird and Marconi-EMI to agree on a single standard, but eventually agreed that both the 240-line, 25-frame sequential and the 405-line, 50-field interlaced systems should be used alternately. It was to be a fight to the bitter end. Baird lost largely because of the inflexibility of his "live" system using the intermediate, fast-processed film technique that had been developed in Germany. He also hoped to use a Farnsworth 240-line image dissector electronic camera, but this

proved to be a disaster. Baird's 240-line mechanical film scanner (telecine) on the other hand provided better pictures (though with more flicker) than the original Marconi-EMI telecine.

The 240-line Baird system was dropped in February 1937, leaving the way open for the progressive improvement of the 405-line pictures, continuing right up to the 1960s. But it took time for the pre-war public to accept television as an entertainment medium capable of challenging the then dominant cinema. With screens only 12in. or smaller, apart from a few early projection models, and the cost of a set approaching that of the £100 Ford motor car, it was almost three years before the number of domestic sets in use increased from the initial 300 to 20,000. The BBC was committed to radio rather than television, and the service narrowly avoided extinction. It finally ground to a halt on September 1st, 1939, starting again with the Victory Parade in June 1946.

Sadly, few of the major pioneers of British TV lived to see its post-war success. Baird died in 1946, with his major wartime work on colour largely overlooked. His associate Captain West met with a mountaineering accident at about the same time. Blumlein was killed flight testing airborne radar in 1942. Campbell Swinton died before television was even born. Schoenberg lived on till 1963, Zworykin till 1982. Professor McGee who pioneered the Emitron camera, and Lubszynski of CPS Emitron fame, have happily survived. As also has Dr. Eric White, who was actually present at that meeting in Ealing fifty years ago when the 405-line system was born.

---

## Postscript

*Nick Lyons*

As I write this the 405-line system is almost at the end of its career. Few people in large urban areas like mine stayed with it to the end, though the odd set has survived – the subject of some sentimental attachment maybe, or as a second or third set in the kids' bedroom, or possibly propped up in the local chippy. It's in circumstances such as these, often with the most pokey bit of knitting needle or coat-hanger to serve as an aerial, that the ability of this v.h.f. system to provide a passable picture come what may proves itself.

As no new sets capable of receiving this standard only have been made for some fifteen or more years, most of the survivors of this breed inevitably now look tired. The same seems to be true of the equipment at the transmitting end. The standards converters used seem to be prone to a variety of problems, with vertical lines of missing picture elements, vision level changes, hum and so on. It's nothing like the quality achieved when origination was on 405 lines.

It's rather sad that the system should end like this. Younger engineers who looked at a surviving set must have wondered how on earth we ever put up with that sort of picture quality. But at its height, from the mid-fifties to the time of its supersession in the late sixties, the system provided very fine pictures indeed. The fifties saw Mullard and Mazda perfecting the display tubes, with a high standard of both picture quality and reliability, while the English Electric Valve Co. brought

about a revolution in the camera field with their 4½in. image orthicon tube. This was to become the workhorse of monochrome (or black-and-white as we called it then) television world wide. It was developed by EEV at the BBC's behest for the 405-line system.

Commercial TV also first came to us in 405-line form. This competition stimulated the BBC to produce some very fine programmes indeed. ITV brought some dross but also introduced us to much that was new and innovative, and gave us a taste for the output of that prolific industry across the Atlantic.

But the 405-line system rendered us a TV island. Being so different from any other system, no one else abroad in electronics meant Europe or the USA: the Japanese industry was just beginning to dabble with transistor radios. UK setmakers had a captive market, and though there was much innovation it was almost a cottage-type industry. Who was to step in and upset this comfy situation? It was the Pilkington committee's report that led to the changing face of the British television industry.

Pilkington signalled the end of 405 lines, though even then it had given us a quarter of a century of service. It brought information and entertainment to millions, whatever your taste, from Quatermass to Perry Mason, Dick Powell theatre to What's my Line, be it Kennedy in Berlin or being shot in Dallas, the excitement of the Tokyo Olympics and pictures via Telstar, the nation rejoicing at a Coronation or the nation in mourning as a barge solemnly carried Sir Winston down the Thames for the last time. All this was brought into our homes by the system that was developed in the early thirties by that brilliant team at EMI.

# Video Servicing

Mike Phelan

Last month we looked at a few minor bits of camera electronics – items that have nothing to do with actual signal generation. This month we'll consider first the overall camera system – see Fig. 1.

## Overall Camera System

We might as well start at the 12V input line. This input is usually stepped down to 9V via a simple series regulator – one or two transistors, an operational amplifier and a zener diode. The unregulated 12V supply is used for the zoom and iris motors. The various high voltage supplies required for the vidicon tube are often generated by an inverter driven by one of the signals from the SSG – sync and subcarrier signal generator. We'll move over to this section next, but in passing should mention that the electronic viewfinder consists of a conventional though small self-contained monochrome receiver whose high-voltage requirements are generated in the line output stage in the usual manner.

## Sync and Subcarrier Generator

Most video cameras of the type we're discussing use a dedicated chip, type HD44007A, in the SSG department (see Fig. 2). Few extra components are required. The output from the free-running crystal oscillator linked to pins 24 and 25 is divided by four within the chip to produce the 4.43MHz chroma subcarrier which emerges at pins 26 and 27 with the correct phase for V (R – Y) and U (B – Y), the V subcarrier being switched through 180° on alternate lines as required for PAL signal processing.

The LC oscillator – pins 3 and 4 – runs at 282 times the line frequency and is locked to the 16MHz crystal oscillator by a phase detector within the i.c. and an external varicap diode – the filter components are connected to pin 6.

Most of the other i.c. pins provide various outputs at

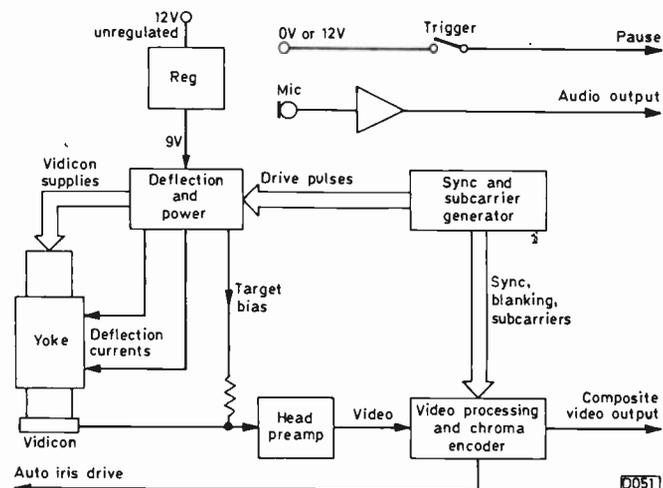


Fig. 1: Block diagram of the electronics of a typical video camera.

line and field rate. It may be stating the obvious, but the deflection signals that drive the tube's yoke must be in synchronism with the composite sync added to the camera's outgoing video signal. Line and field drive emerge at pins 8 and 7 respectively and go to their respective output stages. The 7.8kHz output at pin 20, if used, drives an inverter for the high-voltage supplies – otherwise these supplies are obtained from the line output stage as in a TV receiver. The various outputs can be buffered or inverted by CMOS logic gates – if this isn't done it's necessary to fit small-value capacitors, typically 27pF, from each pin to chassis to remove spurious clock pulses.

## Deflection Arrangements

The deflection arrangements used vary from one model to another. Very little power is required and of course the signals are already locked to the master crystal oscillator. A simplified circuit of the arrangements used in the 3V17 is shown in Fig. 3 – this camera uses a driven inverter to provide the tube's high-voltage supplies.

The field output stage is contained in IC2, an operational amplifier. Part of IC5 acts as an integrator whose sawtooth output is fed via the height control to the non-inverting input of IC2. Negative feedback from the output to the inverting input enables the linearity to be adjusted – this is more important than in a TV set, for reasons that will become apparent when we come to the chroma encoding. There's a conventional shift control and C11 with R19 provide a path to chassis for the scanning a.c. The parabola generated across R19 is fed back to provide additional linearity correction.

The line output circuit is in two halves. Transistors X1 and X2 are driven by the line drive pulses from the SSG and in turn drive the line output transistor X3. When X3 conducts, the current in the output transformer T1 rises exponentially. X3's collector is coupled to the scan coil via C4. The rate of change of the current flowing in T1 is governed by the conduction of X4 and X5, this in turn being dependent on the setting of the width control. The other end of the scan coil is driven by a linearising

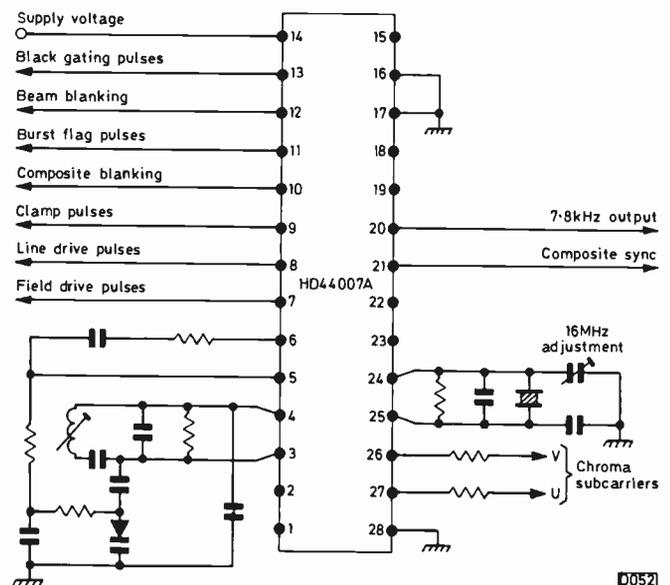


Fig. 2: Outputs from the HD44007A sync and subcarrier signal generator i.c., and the external oscillator components.

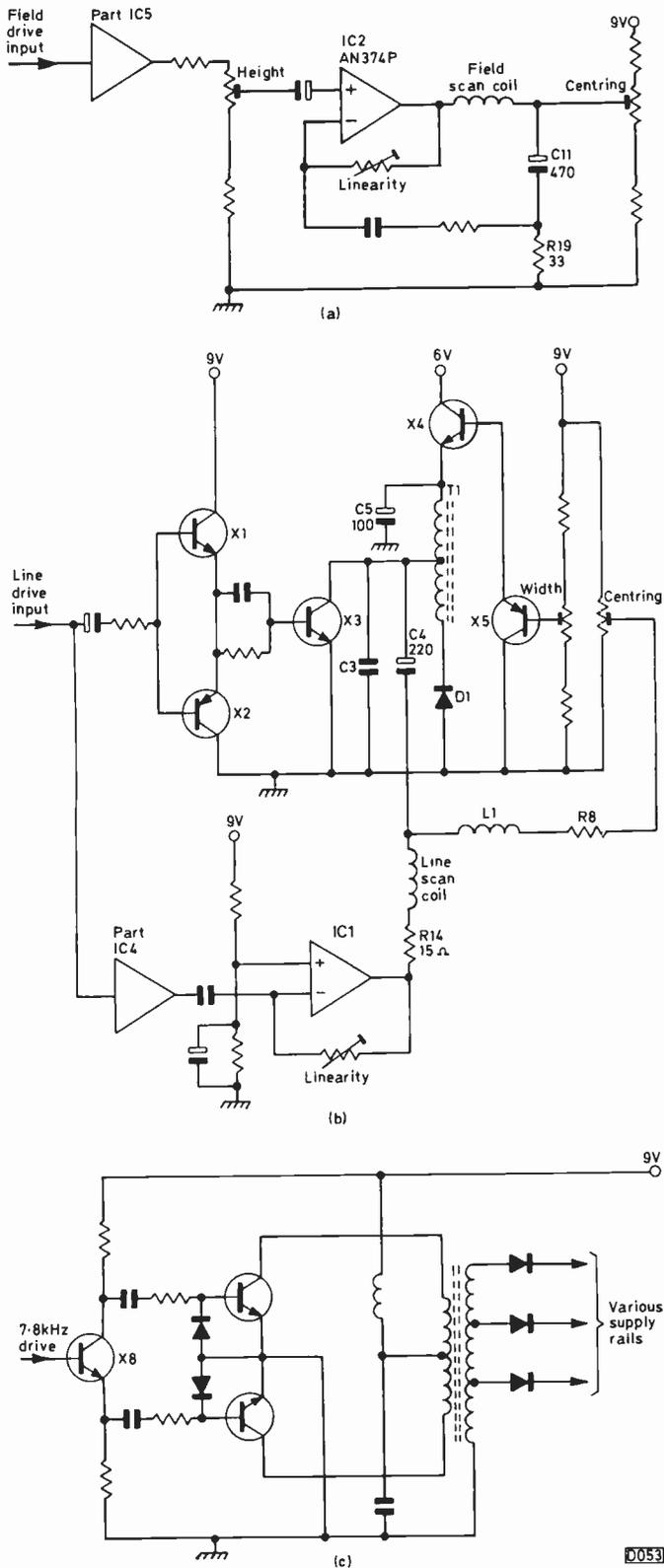


Fig. 3: The deflection and high-voltage supply arrangements used in the Ferguson 3V17 camera – simplified circuits. (a) The field timebase. (b) The line timebase. (c) Inverter used to provide the high-voltage supplies.

sawtooth current produced by IC4 and IC1, the latter having a feedback linearity control. At the start of the flyback X3 is turned off and the scan coils resonate with C3. The efficiency diode D1 conducts to damp the overswing in the usual manner. L1 and R8 isolate the a.c. component from the shift control.

What happens if one or other of the timebases fails? No, you don't get a display of line or field collapse on

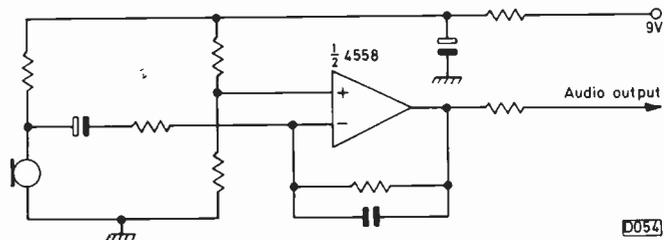


Fig. 4: Simple audio amplifier used in the 3V17.

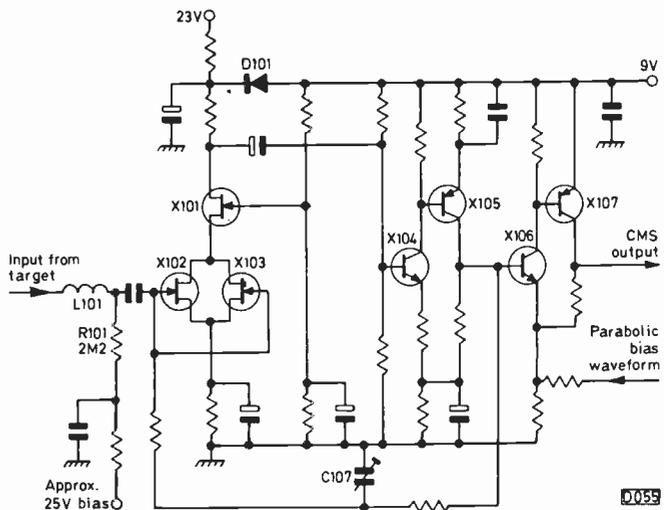


Fig. 5: Video preamplifier circuit used in the 3V20.

the monitor! Consider failure of the field scan. You might think that the vidicon will produce a single line which will be repeated on every line of the monitor's screen – such a display would consist of vague vertical lines. Since the vidicon's target would be ruined in a matter of seconds, protection circuits that monitor the scanning and shut off or reduce the beam current in the event of scan failure are generally incorporated – just one thing to look for when servicing. Only field scan failure protection is required in cameras where the vidicon's supplies are derived from the line output stage.

### Audio Channel

The audio circuit is self-contained and independent of the rest of the electronics – all it has to do is to amplify the signal from the microphone to a suitable level. A typical circuit is shown in Fig. 4.

### Video Preamplifier

Now to the video circuitry, starting at the front – the head preamplifier, see Fig. 5. This has to take the minute signal from the vidicon's target and amplify it while adding as little noise as possible. In this example the first stage consists of a cascode f.e.t. arrangement – X101-3. It has the advantage of very high gain with low noise and excellent linearity. The gates of X102/3 are a.c. coupled to the target as the latter requires a d.c. bias of about 25V, supplied via R101. The reason for using two f.e.t.s in parallel is to reduce noise: as the noise is random, some of it must cancel out – this applies only to noise produced by the f.e.t.s of course. X103 was omitted in later production. X104-7 comprise a direct-coupled amplifier from which feedback is taken to the gate of X102, adjustable by C107. L101 is

toroidally wound on a ferrite core and is included to compensate for the capacitive signal source (the target). X106's emitter is not decoupled so that the gain of this stage can be modulated by a waveform derived from the deflection circuits. This waveform is also used for dynamic focusing – it consists of field- and line-rate parabolas. The reason for applying it to the preamplifier is to increase the gain at the edges of the picture to compensate for the slight darkening that would otherwise

occur. This feature is not used in many cameras.

The entire preamplifier is enclosed in a heavily screened box which is attached to the vidicon's shield – the connection to the target is less than half an inch long. Note that the output is labelled "CMS": this stands for colour multiple signal – next month we'll discuss how the colour information comes to be there and how it's encoded to provide a conventional PAL signal.

## Servicing the solid-state Indesit T24EGB

Mike Phelan

The 24in. solid-state monochrome Indesit Model T24EGB (chassis C) looks similar to its hybrid predecessor (Model T24EGB, chassis B) both inside and outside, but there are a great many differences. Gone are the mechanical tuner and rotary controls, but there's still a row of wirewound resistors along the top edge of the chassis, and as before they do their best to burn holes in the panel. Still present is the aerial socket that backs away from you when it's approached with a plug, due to the mountings bending.

### Chassis Arrangement

The chassis consists of a long, narrow vertically mounted PCB that hinges down to a horizontal position. It looks like the PCB used in the ITT VC200 or GEC Series 1 chassis. The i.f. strip, which consists mainly of a TBA440C i.c., resides in the larger of the two cans along the edge of the panel. The small can houses the TBA120 intercarrier sound i.c. Although most of these Italian made sets should have been converted, one or two slipped through with 5.5MHz filters fitted – a coil and capacitor conversion was available from the manufacturers, or 6MHz filters. Sibilance can be reduced by changing the value of C1314 in the intercarrier sound can from 0.022 $\mu$ F to 0.047 $\mu$ F. There are separate modules, each with a TBA800 i.c., for the audio and field output stages. These modules are interchangeable – quite often a TBA800 that gives slight sound distortion works o.k. in the field output position. All cases of sound distortion can't be blamed on the chip however – the speaker can give problems. Another module contains the TBA950 sync/line oscillator i.c. and its associated components.

### Circuit Features

Before going farther, a brief description of the circuit, which has some unusual features. The power supply is shown in Fig. 1. Mains rectifier D901 is followed by a series of dropper resistors that supply 170V to the collector of TR901. This transistor, in conjunction with R906, R928, TR902 and the 6.2V zener diode D904, reduces the h.t. to a reasonably stable 120V. This is the supply to the line output stage – the set's other supplies are derived from the line output transformer. The 120V rail is set by R911 which acts as the width control (set for 120V at TP20).

D905 produces 30V across its reservoir capacitor C913. R921/C912 drop this to 25V for the field output TBA800 while R923/C916/D907 (12V zener diode) produce a stabilised 12V supply for most of the rest of the circuitry. R924/C919/D909 (12V zener diode) produce a stabilised

supply for the timebase oscillators. D906 produces 26.5V across C917: R922/C908 and the shunt stabiliser consisting of TR903/D902 and associated components produce a regulated 13V supply for the audio output TBA800 – this helps to stabilise the current demand from the line output transformer, as the current drawn by the audio output TBA800 is a function of the volume.

Note that the negative side of C901/2/3/4 (common can) is connected to chassis via C921. The 2.6V present across C921 is used as the start-up supply.

Apart from the TBA800, the field timebase consists of a unijunction transistor oscillator (TR401, type 2N4871) and the flyback switch transistor TR501 (BC327). If the BC327 goes short-circuit the result will be severe top foldover. The unijunction transistor can cause field jitter – so can the sync separator bias resistor R1406 (1.8M $\Omega$ ) on the TBA950 module.

The line driver and output stages (see Fig. 2) look very strange – there's no driver transformer for a start. The output from the TBA950 switches TR402 on and off. When it's on, TR403 and TR404 are off. When TR402 is switched off, TR403 and TR404 can conduct. The key to this is D401, which produces some 4.6V across C406 during normal operation. In addition, C404 is charged by TR404's emitter current. When TR403 switches on C404 is discharged and the emitter of TR404 is at almost chassis potential. The arrangement is self-stabilising up to a point, as the voltage produced by D401 to forward bias the bases of TR403 and TR404 is dependent on the line output transformer's load.

### Common Faults

So much for the theory, now for the problems. The usual one is a dead set. In this event check all the wirewounds in the power supply for being open-circuit or having dry-joints – they sometimes burn holes in the PCB. If all is in order there should be 120V at TP20 – check here or at one end of R907 – and a similar voltage at the collector of TR404. Next check pin 8 of the line oscillator module for a burst of line frequency squarewave at switch on – if this is absent, a 9V battery connected across C919 will supply a start-up voltage for the oscillator. If everything sounds strained, switch off. A feature of this system is that if anything stops the line output stage working the 12V l.t. rail will disappear and stay that way until the set is switched off, R925 discharges C903/C921, and the set is then switched on again.

A short-circuit BU205 will open the fusible resistor R902. Other line output stage faults give the h.t. present but otherwise dead set symptom. The most common fault

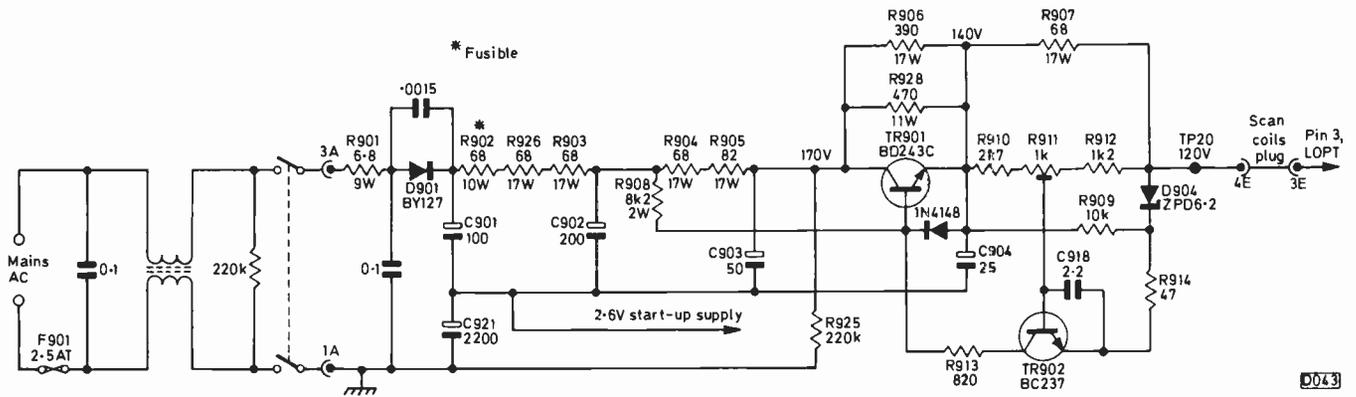


Fig. 1: The mains input and h.t. supply circuitry. The mains filtering components may not be fitted in UK sets.

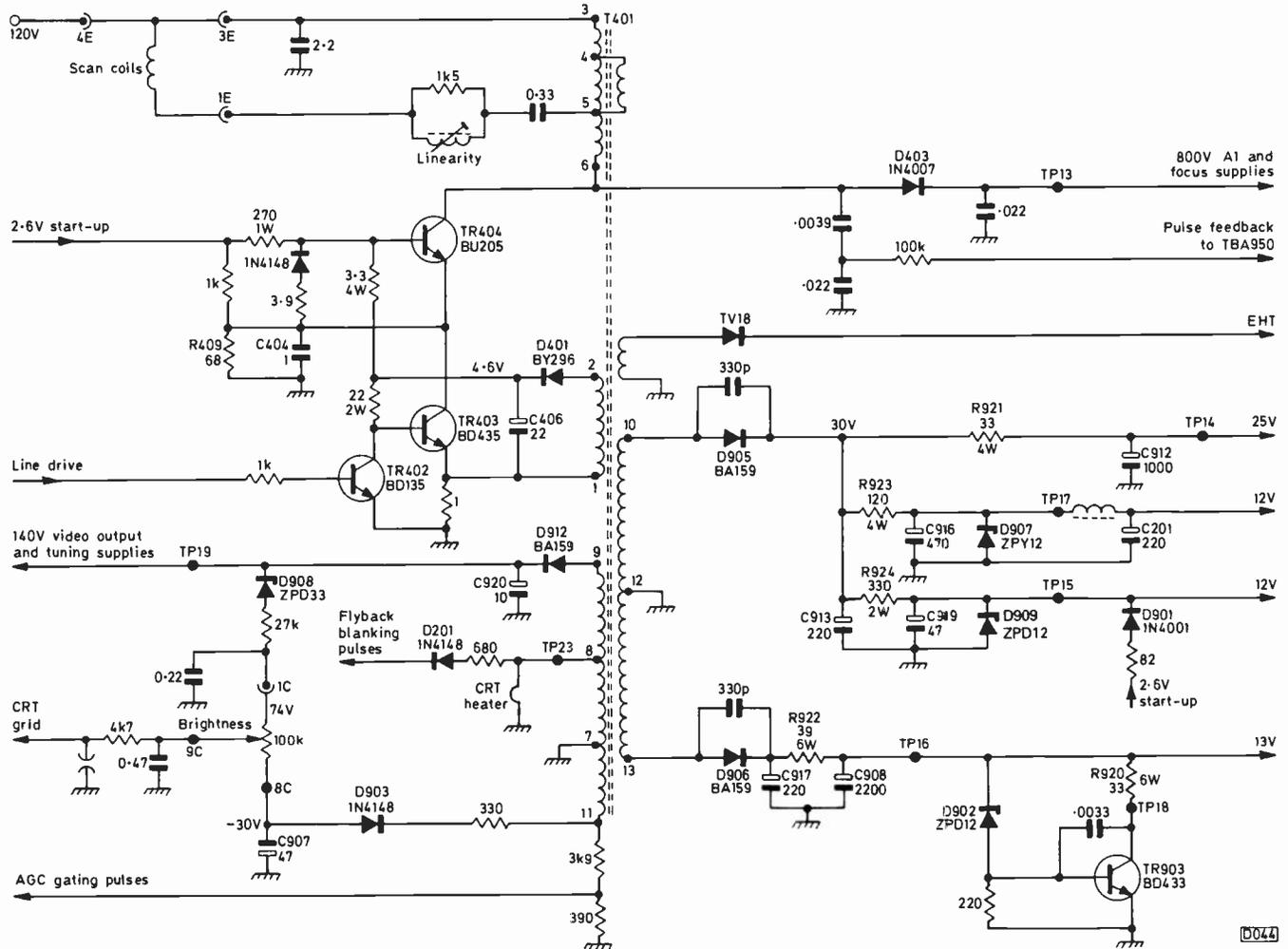


Fig. 2: The line output stage, showing the various supplies derived from the transformer. R922 may be 27Ω, 6W with R930 12Ω, 4W in series.

of this type is a defective e.h.t. stick – unfortunately it's in the line output transformer. All the large resistors in the line can be worth checking for dry-joints or being open-circuit, as are TR402 and TR403. If the line oscillator isn't working, check C1407 (0.01μF) and the TBA950.

Nothing will happen if the 2.6V supply is not generated across C921.

If there's no supply to the audio output stage, check D902 (ZPD12) and TR903 (BD433) in the shunt stabiliser circuit. Repeated failure is due to R920 (33Ω) going open-circuit. The line/field oscillator supply regulator D909 (ZPD12) is prone to going leaky.

The signal sections are fairly reliable. The tuner occasionally fails, as also do the video driver transistor TR201

(BC238B) and the video output transistor TR202 (BF257), failure of TR201 giving a negative picture.

The on/off switch sometimes falls to bits – or the contacts burn out. It's a special type unfortunately.

### Spares

Spares, including the line output transformer, for the T24EGB chassis C can be obtained from RTC International Ltd., Victoria Parade, Urmston, Manchester (telephone 061 748 1129). Certain spares for other Indesit TV sets can also be supplied (excluding the mains lead and aerial plug for the T12). Spares can be supplied only as long as present stocks last.

# Colour Bar Program

G. J. Phillips, B.Sc., C.Eng.

The standard BBC Model B microcomputer can be easily programmed to generate the colour bar test pattern (see below). This may seem like using a sledgehammer to crack a nut, but many establishments now possess a microcomputer that may stand idle for a lot of the time. The program consists of only eleven lines of basic and can be typed in a few minutes.

Line five clears the screen and line six calls up mode two of the microcomputer to facilitate colour graphics. The Move and Plot commands are used to generate a series of triangles which are joined together to form vertical rectangles. Line fifty is an algorithm to convert the rectangle or bar number to the correct colour number recognised by the computer. This number is called up at line sixty. Line 100 is merely a dummy statement which is

jumped to at line 110: this is done to avoid the computer's prompt appearing – it would contaminate the graphics.

The u.h.f. modulated output can be plugged into the set's aerial socket just as for normal operation. In addition, the BBC microcomputer has a composite video output which can be connected to the video input socket of a VCR to enable the pattern to be recorded for future fault finding use.

## Program

```
1 REM TV COLOUR BAR GENERATOR. G.J. PHILLIPS
5 CLS
6 MODE 2
10 MOVE 0,1000
30 PLOT 85,0,0
40 FOR bar=1 TO 8
50 IF INT(bar/2)=bar/2 THEN colour=(8-bar)/2 ELSE
   colour=(8-bar)+INT(bar/2)
60 GCOL 0,colour
70 PLOT 85,(bar*160),1023
80 PLOT 85,(bar*160),0
90 NEXT bar
100 REM
110 GOTO 100
```

## MISFITS

Richard Roscoe

Well over half the sets that come my way turn out to have more than one fault. In line with the modern mania for giving everything a fancy name I call them MISFITS (Multiple Independently Situated Faults in Television Sets). You know the type of thing I mean. The set finally packs up and after you've been called in to replace the tripler or whatever and got it going you find that the tuning drifts, the volume control crackles, or there's a bad hum bar. When you tackle the owner about it you get something like: "Well it's been like that for a while but I didn't think it was worth bothering about, not at today's prices anyway. Mind you, now you're here . . ."

In many cases these secondary faults are the work of moments to put right. On the other hand some can take much longer to fix than the fault you were actually called to see – and woe betide you if you try to charge for this extra work. "How much?? – the whole set's not worth that!" I recently had a concentrated burst of these MISFITS. They made a complete mess of an otherwise perfect summer's day.

### The Thorn 3500

It started first thing in the morning. Everything was bright and clear – except in the back of a Thorn 3500 where things were decidedly wintry. According to the owner the set had gone off without any warning the previous night. The thermal cutout hadn't tripped and none of the fuses had blown, so I switched on. Meter checks showed that power was getting to the chopper transistor and that the 30V line was working. Further checks soon revealed that the chopper driver transistor was without collector voltage due to R607 being open-circuit – it's part of the "dropper". Well, it's nice to start the day with an easy one. Switching on after replacing the dropper produced sound and a good picture – but no colour. I turned to the owner who was hovering behind.

"Ah" he said, "it does that. If you twiddle the tuner it'll come back."

I could see the set was on tune so I ignored that. Instead I concentrated on the decoder board. Tap, tap on the top of the board and R312, one of the small presets in the burst detector circuit, fell apart. I prodded the rest of the presets but they remained intact. So far so good, out with the remains of R312 and in with a new 47kΩ preset. Colour was now present but was unsteady: the hue was correct but the saturation was going up and down like a yo-yo. I was beginning to wish I'd not started on the set.

I took a deep breath and tried to think. If the hue was correct, most of the decoder circuitry would be in order (burst channel, reference oscillator, etc.). Obviously the gain of the chroma amplifier was varying, which could have been due to a fault in the colour-killer department. The colour-killer action depends on the operation of the ident amplifier (no ident, no turn-on bias, no colour). Voltage checks took me back to the ident amplifier but the d.c. conditions here were correct. So, lacking a scope, I tried bridging the decoupling capacitors. First time lucky: the transistor's emitter decoupling capacitor C321 (0.22μF) was faulty. A replacement restored good, steady colour: so much for the easy ones.

### The GEC C2110

I headed for the next patient on the list, a GEC C2110 (plastic) series, with high hopes. It's one of my favourite designs though getting a little long in the tooth now and the fault on the card, picture rolling, is a stock one – C452 (4.7μF) in the field sync circuit. I always go equipped with replacements for the other electrolytics on the field timebase panel, C455 47μF, C457 47μF, C458 22μF and C462 220μF. These usually cure the sagging height and bottom cramping the customer didn't bother to mention. My foresight was well rewarded – they were all well past their best in this particular set.

"Super" said the customer as I set up the picture. "I don't suppose you can stop the hum while you're here?"

"Hum?"

"Yes, in the quiet bits you get this hum. It's not too bad but I thought, you know, while you're here . . ."

Turning down the volume control (noisy, so out with the trusty Servisol) I found that there was indeed a definite background hum. Another electrolytic showing its age? Bridging C195 (100 $\mu$ F) which smooths the 24V supply to the audio output chip made no difference, but bridging C121 (150 $\mu$ F) which smooths the 12V supply to the intercarrier chip did. In went a spare 220 $\mu$ F, the nearest value I had.

Amidst smiles all round – i.e. the customer smiled, having got two repairs for the price of one; I had more of a fixed, glassy grin – I set off for a Sanyo CTP3101 colour portable. By now I was feeling that this was not my day, and though the reported fault was uncontrollable volume I feared the worst. I was not disappointed.

### **The Sanyo Colour Portable**

As I approached the house I could hear Play School, accompanied by a chorus of blood-curdling screams. The door was opened by a haggard mother who greeted me with obvious relief. Apparently the opportunity to watch tele with the volume at full blast without getting whacked for it was too good for her offspring to miss – and they'd asked all their friends around to join in the fun.

Like most modern sets this one uses a variable d.c. voltage for volume control, acting on a voltage-controlled amplifier within a chip, in this case IC161 (AN340). The voltage at pin 4, from the volume control, was o.k., so in went a new chip. The sound was now under control and the lady of the house cheered up enormously, which is more than I did when I caught sight of the picture. All the faces were green.

"The ident's wrong" I squawked.

"Pardon? Oh you mean the tuning." She twisted the rotary tuner and brought it back with perfect colours. "It sometimes comes on with funny colours but I can always get it right. I shouldn't bother about it. Now how much do I owe you for the new volume control?"

It was an emotional moment. Was I to leave this long-suffering paragon of virtue with a faulty set? Of course not! It seemed likely that the flip-flop controlling the R – Y switching was not being synchronised by the ident signal. The relevant circuitry is contained in IC252 (TA7161P), and since Sanyo kindly fit holders for their chips it was easy to verify that this was indeed the culprit.

### **The GEC Series 1**

I managed to get back to the van before the kids could let my tyres down. Things were looking up, or so I thought. The next call was to another GEC set, this time a 20in. monochrome one (Series 1 chassis). The fault on the card was the opposite to that with the Sanyo – almost non-existent, very distorted sound. I realised that I was in for my fourth consecutive MISFIT when the picture came on – rolling badly. The owner cleared his throat, but I got in first.

"Rolls, does it?"

"For a bit, then it stops. I thought, while you're here . . ."

I wearily opened the valve case. Into the set went a new PCL805 and a PCL86. This stopped the rolling but the sound was as bad as ever. Voltage checks then revealed that the audio output pentode's screen grid was without voltage, due to R152 (6.8k $\Omega$ ) being open-circuit. Replacing this brought the sound up to the normal level with no distortion. Finished, I thought. Not a bit of it. Now the

picture wasn't rolling I could see that the bottom was cramped.

The usual causes of bottom cramping with a valve field timebase are the components in the output pentode's cathode circuit. The resistor can change value and the decoupling capacitor can dry up. In so doing they put more strain on each other and the valve, so that the process is cumulative. The cramping in this case wasn't too bad and the owner hadn't noticed it. Nevertheless the resistor (R208) had fallen in value from 390 $\Omega$  to 200 $\Omega$  and the capacitor (C207, 250 $\mu$ F) appeared to be on its last legs. So both were replaced.

### **The Rank Z718**

The final MISFIT was a 26in. Bush Model BC6438 with the Z718 chassis, touch tuning and remote channel change. There'd been a loud crack (damp in the e.h.t. section) after which the set had stuck on Ch. 1 with only snow and noise. This one couldn't be dealt with in the field, so I whipped it back to the workshop where I could dismantle the difficult-to-get-at Z916B touch tuning unit in safety.

The heart of the unit is an ETT6016 i.c. which performs the channel-switching action. There are two associated transistors, 9VT1 (BC157) which acts as a shunt stabiliser for the i.c.'s supply and 9VT2 (BC147B) which is used to ensure that Ch. 1 is selected when the set is first switched on. In view of the fact that the set was stuck on Ch. 1, 9VT2 seemed a likely culprit. A replacement restored channel selection but a couple of channels were faulty. So in went a new chip. Finally 9VT1 was leaky, pulling down the tuning line but not the supply to the i.c.

After all that plus drying out and cleaning the e.h.t. stick and its holder I set about tuning in a picture. Up it came – with very bowed sides! No one had mentioned this of course. So over to the EW modulator circuit.

None of the controls had any effect, while the modulator diodes 5D5/6 and the driver transistor 4VT19 all read o.k. on the meter. Voltage checks took me right back to the first transistor in the control circuit, 4VT15, which was off due to lack of base bias because 4R58 (82k $\Omega$ ) was open-circuit. This resistor is used to provide the basic width/e.h.t. stabilisation in the set, being fed from the 260V line.

All I had to do after this was to resolder the deteriorating joints on the line timebase plugs and set up the field linearity – about par for the course – then return the set to its owner.

What a day!

---

## **Book Notice**

A new edition (the third) of **Beginner's Guide to Colour Television** has been published by Newnes Technical Books at £4.50. The first edition of this book was published as long ago as 1964. This latest edition, revised by Eugene Trundle, is thoroughly 1984 however. Much of the material in earlier editions has been condensed and a great deal of new material has been added. Thus we get for example single-chip decoders, the latest types of colour tubes, teletext developments (CCIR levels 1–5), MAC, high-definition TV and worthwhile sections on satellite and cable TV. A good introduction to current TV technology.

# VHS Hi-Fi Sound

Derek Snelling

Both VHS and Betamax machines with hi-fi sound, based on the use of f.m. and recording with rotary heads, are now available in the UK. This article deals with the system used in VHS machines, with particular reference to the Panasonic Model NV850B.

## Principles

First the principles involved. The stereo hi-fi sound is recorded on the tape as f.m. by two heads mounted on the video drum assembly. The signals are recorded beneath the normal video signal – or to be more accurate the video signal is recorded on top of the sound signals. The left and right carriers are at 1.4MHz and 1.8MHz. The arrangement of the head drum is shown in Fig. 1: the audio heads are mounted 60° round from the video heads and have an azimuth of ±30° (this compares with ±6° for the video heads). In addition, the sound head track with +30° azimuth is laid down beneath the video head track with -6° azimuth, thus giving a 36° difference to minimise crosstalk.

The sequence in which the tracks are laid down is shown in Fig. 2, starting with audio head 1 which lays down a 26μ wide track. The next head around is video head 2 which lays down a 70μ track on top of the audio one. The audio track is more strongly laid down however, using a higher record current and lower frequency. The f.m. video signal erases the upper part of the audio track but the audio is still present at a deeper level in the tape, as shown in Fig. 3. Audio head 2 next lays down a track, erasing the edge of video track 2. Finally video head 1 records its track, further erasing the edge of video track 2 and the upper part of audio track 2. We end up with 49μ wide video tracks that have 26μ wide "buried" audio tracks at their centres. Note that audio tracks 1 and 2 are not left and right: both audio signals are recorded by each head. The audio tracks are laid down at the centre of the video tracks to avoid crosstalk – if the audio track was to stray on to the adjacent video track the azimuth difference would be reduced from 36° to 24°.

The audio f.m. level on playback is lower than the video f.m. level, because of the lower frequency and the fact that the video is recorded on top. As a result, there's a danger that drop-outs may occur. To overcome this problem the f.m. detector is followed by a hold circuit which keeps the signal at the same level until the drop-out has passed. By passing the output from the hold circuit through a low-pass filter to smooth out the "kink" effective drop-out compensation is achieved – see Fig. 4.

A problem with having two rotating heads is that you must be able to switch from one to the other. For video switching the PG pulses are used. The same pulses are

used for audio head switching after being shifted by 60° to allow for the different positions of the heads. A further problem arises however because the switching point introduces noise. For video, the switching is arranged to occur off screen during the field blanking period. You can't do this for audio, so the hold circuit is used to maintain the audio during head switching, the head switching pulse being applied directly to the circuit.

## Practical Aspects

So much for the theory. Now for a few details of the Panasonic NV830/NV850. The sound is also recorded on the standard linear track for compatibility with other VHS machines/tapes but the linear track is mono only. The f.m.

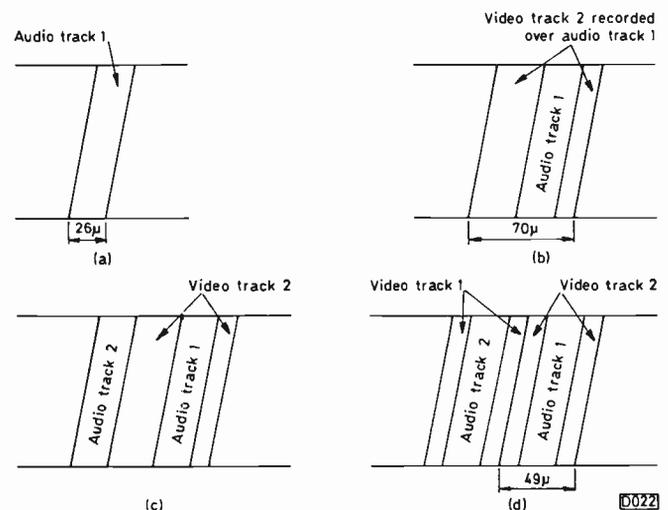


Fig. 2: Sequence in which the tracks are recorded on the tape, starting with audio head one.



Fig. 3: The audio signals are recorded at a deeper level in the tape's oxide coating than the video signals.

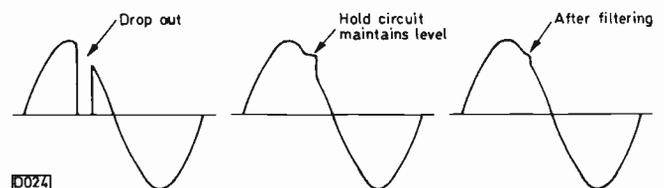


Fig. 4: Overcoming the effect of an audio drop-out.

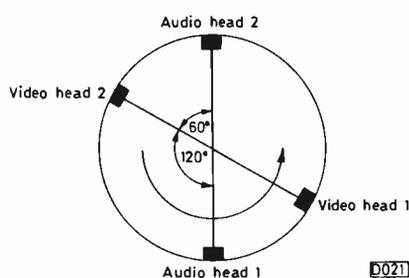


Fig. 1 (left): Positions of the video and audio heads in the drum.

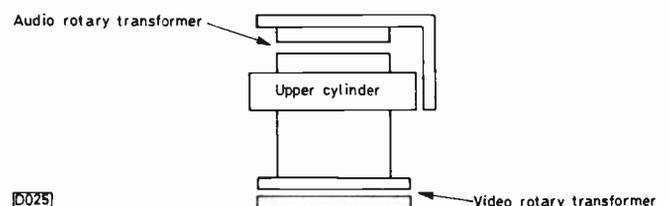


Fig. 5: Drum assembly, Panasonic Model NV850.

sound signals are passed through record level circuits that have a ganged level control with a "click" normal position: left and right record-level meters are provided. The linear audio circuit is the same as with ordinary machines. Recording can be done from the off-air TV or an external source - straight audio, a camera or a simulcast transmission (simultaneous TV and radio broadcast).

It follows from this that the machines can be used as high-quality sound only recorders. This raises a problem in that without video there's no field sync pulse to which the heads can be locked, so in this mode the field sync input to the servo is earthed and a 50Hz signal counted down from the 4.43MHz oscillator is used instead.

During record the TV set can be used to monitor either the f.m. or linear sound track - when monitoring the f.m., the E-E sound level varies with the setting of the record controls. A noise reduction system is used during both record and playback to achieve a dynamic range of 80dB. Audio dub is available but operates with the linear track only: this means that you can have a tape with a stereo track and a separate commentary on the linear track or three separate mono signals - useful perhaps for multilingual recordings. Ch. 1, 2 or linear can be separately selected during playback, which can be either via the TV set or an external sound system.

If a non hi-fi tape is played on the machine or the f.m. output from the heads drops below 50 per cent an f.m. mute circuit switches the machine to linear sound.

The f.m. sound will be affected by the tracking control of course: as the track width is narrower than that for the picture the setting is more critical - because of this one of the record-level meters doubles as a tracking meter during

**Table 1: Performance comparison.**

Characteristic	Linear operation	Hi-fi operation
Relative speed	23.99mm/sec	4,850mm/sec
Dynamic range	50dB	more than 80dB
Frequency response	80Hz-8kHz	20Hz-20kHz*
Wow and flutter	0.2%	less than 0.005%

\* The hi-fi frequency response is deliberately limited to 20kHz by bandpass filters.

the playback of f.m. sound (the f.m. output is fed to the meter via an a.c. to dB converter). As the audio track is in the centre of the video track, optimum audio tracking should correspond with optimum video tracking.

One of the differences between the NV830 and the NV850 is that the latter has an extra video head for super fine stills etc. Because of this the mechanical arrangement of the video/audio head assemblies used in the two machines differs. The NV850 has a separate rotating transformer mounted above the video heads for sound pick-up - see Fig. 5: the NV830 has them all combined beneath the video heads. This is probably because with five heads (NV850) crosstalk could be a problem with a combined transformer whereas with four heads (NV830) the windings can be "spaced out" more so that the problem does not arise.

**Performance Characteristics**

Table 1 compares the performance figures for conventional linear and hi-fi sound operation.

<p><b>CAPACITORS</b></p> <p>91 5 x .0047/1500 AB23 Chassis 1.50 92 10 x 220MFD 16V Elect 0.50 93 10 x .047MFD 400V Mtl Pol 0.50 94 5 x 4.7/100V CS14 T3500 1.25 95 5 x .47/1000 Dublier 3.00 97 10 x 0.1/2000V W/E 2.00 98 5 x 1/250 Supp ITT etc. 1.50</p> <p><b>EHT TRAYS</b></p> <p>50 ITT CVC 5/9 3.00 51 Decca 1730/1830 5.00 52 Decca 80 Series 4.50 53 GEC 2040 Hybrid 3.80 54 T1500 5 Stick 3.50 55 Thorn 9000 7.00 56 Thorn 1400 2.00 57 Philips G9 3.50 58 Universal ITT Type 4.50 59 5 x TV11 EHT Rec for PTV's 1.80 60 3 x TV46 EHT Rec Z718 1.80 61 ITT CVC 46 4.00 63 RRI Z179 3.00 64 Pye 691/697 3.50 65 Pye CT200 4 Lead 3.50 66 Pye CT200 5 Lead 4.50 67 Korting 90 OGR Hyb 5.00</p>	<p>68 Grundig 3010/1500 3.00 69 Thorn 3500 7.50 70 Thorn 8500 5.40 71 Philips G8 6.30 72 Pye 731 4.50 89 10 x Anti Track EHT Cap 2.00</p> <p><b>INTEGRATED CIRCUITS</b></p> <p>140 5 x TDA440 3.00 141 5 x TBA120AS 1.80 142 5 x TBA540 4.00 143 5 x TBA5400 4.00 145 5 x TBA560 3.50 146 5 x TBA810S 3.00 147 5 x TBA9200 4.50 148 5 x TBA990 3.25 149 5 x TBA5200 4.00 150 5 x TBA530 4.25 151 5 x TBA950 4.50 154 10 x TCA2705Q 4.00 155 5 x MC1327Q 2.50 180 TDA1170 1.35 181 TDA1190 1.90 182 TDA1006A 1.45 184 TDA1035 1.83 186 TDA1044 2.23 186 TDA1190 1.90 187 TDA1412 0.90 187 TDA2002 1.80 187 TDA2020 2.50 187 TDA2030 2.15 187 TDA2523 2.35</p>	<p>179 TDA2532 2.40 180 TDA2540 1.85 181 TDA2541 2.67 182 TDA2560 3.28 183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2593 2.23 190 TDA2600 4.00 191 TDA2611 1.24 192 TDA2640 2.35 210 ETR8016 2.28 211 ETR8018 2.28 212 ETR8018 2.28 220 SL9018 Int Circuit 5.00</p> <p><b>LINE OUTPUT TX</b></p> <p>001 Philips G8 7.50 002 Decca 30 Series 7.80 003 Decca 100 Series 6.50 004 ITT CVC 25/30/32 7.80 005 Philips G9 7.50 006 RRI T20 9.32 007 RRI A823 7.80 008 RRI Z718 18" 18.95 009 RRI Z718 20/22/26" 18.95 010 RRI A774 Mono 10.87 011 Thorn 1890/91 7.80 012 Thorn 1615 6.50 013 ITT CVC 46 6.50 014 Phil TX Chass. 5.00 015 RRI Ranger 1/2 5.00 016 ITT CVC 5/9 8.50 017 Philips E2 Chass. 5.00 018 Thorn 9000 12.00 019 Thorn 9500/9800 8.50 020 Poliak 161 Mono 6.80 021 Thorn 3500 Scant 4.50 022 Thorn 8500 11.80 023 Thorn 1590/91 8.50 024 Thorn 1500 15KV 4.00 025 GEC 2040/2100 Hybrid CTV 4.00 026 Bush 161 Mono 5.00 027 GEC Single Std Mono 5.00 028 Pye 691 (wired) 5.00</p>	<p>030 GEC 2100 Hybrid 4.00 032 Thorn T x 9 Chass. 14.50 033 Philips KT3 8.00 034 RRI T24 Chass. 14.00 035 Sanyo CTP5101 9.50 037 Split Diode EHT Lead 1.35</p> <p><b>PUSH BUTTON UNITS</b></p> <p>110 Pye 713 4 Way 7.87 111 Pye 715 6 Way 11.95 112 Phil G8 Square 12.75 113 Phil G8 Sloping 14.98 114 Thorn 9000 2.50 115 Thorn 1615 4 Way 7.87 116 Decca 6 Way 6.95 117 Decca 4 Way 6.50 118 GEC 2110 6 Way 7.95 119 GEC 2136/7 Tapered 7.95 120 ITT CVC5 9.25 121 ITT CVC8 11.45 122 ITT 6 Way with V.C.R. 7.95 123 RRI A823 etc. 7.95 124 Hitachi 4 Way 7.95 125 RRI T20 6 Way 8.95</p>	<p><b>SPECIFIC COMPONENTS</b></p> <p>351 Thorn 1591 Speaker 2.00 352 Thorn 1600 Dropper 0.50 353 T x 10 Preset Drawer 3.00 354 T x 10 CRT Base Assy 4.00 355 3" Round BR Speaker 1.00 358 5 x Tho/3500 200 Conv. Pot. 1.00 359 5 x Tho/3500 50R Conv. Pot. 1.00 360 5 x TCE3500 A1 Rectifier 0.75 362 T9000 Rem. Receive Assy 5.00 363 T3500 Meins TX 5.00 364 T8500 Meins TX 7.50 365 T8500 (Plastic) Cut Out 1.50 370 Pye 731 Thick Film Resis. 1.50 371 Pye 713/731 Vis. Gain Med. 6.50 372 Pye 731 3R3 50W Metal cld. 1.25 373 100K x3 Drawer P'set Aht Pye 731 2.00 378 Grundig 5010/6010 Vid Mod. 4.80 384 5 x 10R Phil. G8 Conv. Pot. 2.40 385 5 x 15R Phil. G8 Conv. Pot. 2.40 386 5 x Phil. G8 2k x2 Lin. Bright. 2.50 387 5 x Phil. G8 10k Log. Colour 2.50 388 5 x Phil. G8 47k Log. Vol. 2.50 389 G8 Plastic Meins Switch 0.75</p>	<p>390 G8 Metal Meins Switch 1.23 391 G8 Line Stor/Eq. 2.00 Coil 2.25 392 G8 R/G Symetry Coil 3.33 397 20 x 3.15A A/S 20mm Fuse 1.50 398 20 x 800MA A/S 20mm Fuse 1.50 399 20 x 2.5A A/S 20mm Fuse 1.40 400 20 x 2A A/S 20mm Fuse 1.40 401 20 x 1A A/S 20mm Fuse 1.40 402 20 x 1.25A A/S 20mm Fuse 1.40 403 5 x RRI T20 Tube Base 4.35 410 Phil. G11 E/W Load/ Coil 1.50 411 Phil. G11 Bridge TX 1.50 412 Philips G11 Speaker 1.00 413 10 x TDA2600 IC Holder 1.90 415 PALKT3 Speaker 1.50 435 10 x Decca 30 10R Fusible 0.50 436 5 x Decca 30 3R9 Modulohm 1.75 437 Decca 30 47k Vol.-Switch 1.25 463 5 x 5R Universal Conv. Pot. 1.00 464 5 x 20R Universal Conv. Pot. 1.00 465 5 x 100R Universal Conv. Pot. 1.00 466 5 x 470R Universal Conv. Pot. 1.00 467 10 x 100k Tun/Pres TCE etc. 3.00 468 10 x 100k Tuner Preset G8 3.00 468 ELC1043/05 Tuner 6.00</p>	<p>460 ELC1043/06 Tuner 6.00 461 U321 New Tuner 7.95 462 U322 New Tuner 7.95 463 98003 Posister 0.99 464 98009 Posister 0.99 465 Mull.0L50 Delay Line 0.95 466 5 x VA1104 2.70 469 Cut Out Metal GEC 2100 1.00 470 5 x GEC2100 3 Leg Thermist. 1.00 479 5 x Gen. Purp. Roc- tary Switch. 3.00 480 5 x Gen. Purp.Push/ Switch 3.75 481 20 x Neons GEC etc. 2.25 482 5 x Univ. Aerial Skt. Kit 5.50 483 10 x Metal Coax Plug 1.70 484 Focus Unit T20 Type 1.25 485 Foc/Unit Thorn 8500 Type 1.25 486 4.43MHz Ring 0.40 488 10 x Crystal Type Spk/ Gap 1.50 496 TX10 Chass. Focus Unit 7.00 497 De-Soldering Pump 3.50 498 1 x 10 Trimming Tool 1.00</p>
<p>All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days. Please add 15% VAT and 90p P &amp; P</p>						
<p><b>TRANSISTOR/DIODES</b></p> <p>230 10 x AC128 1.50 235 50 x BC213L 2.50 250 10 x BD124 2.50 251 10 x BD131 1.50 270 10 x BU208A 8.80 271 10 x BU208 7.50 272 10 x BU326 10.00 273 5 x BU205 3.75 280 25 x 2N3055 (Texas) 7.50 281 10 x 2N2905 (Equiv. BC161/303) 0.50 290 10 x BT106 Thyristor 9.00 292 5 x BT119 4.50 293 5 x BT120 4.50 335 50 x BY127 Diodes 3.00 340 25 x TIP41A 6.50 341 25 x TIP41C 7.00</p>						

**QUICK SAVE T.V. SPARES**

MUXTON HOUSE, MUXTON, TELFORD, SALOP.  
REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £1.50 postal order (made out to IPC Magazines Ltd.), the query coupon from page 163 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## **JVC HR3300**

I cannot resolve a locked picture in the E-E mode and when a known good tape (made on another machine) is played back there's a negative colour picture with heavy hum on sound – the TV set has to be retuned to get a little sound with the negative picture.

The overloading on playback and E-E points to either the circuitry on the luminance/chrominance board common to both or the r.f. converter (modulator). Try another converter if possible. Should the converter turn out to be o.k., reduce the playback luminance level (R37 on Y/C board). If the converter is at fault, try adjusting it – remove its cover, plug it back into the machine, then adjust the preset farthest from the small coil can.

## **PHILIPS G11 CHASSIS**

There's intermittent cramping at the bottom of the picture – the lower lines of the frame rise by one-two inches though the rest of the picture remains fairly stable.

The trouble could be due to poor regulation of the 33V or 37V lines – greatest current consumption occurs at the end of the field scan. Try scoping the LT3 rail and pin 15 of the field timebase i.c. If any significant 50Hz ripple is present, check C3144 or C2097/8 respectively. If all is well here, look for dry-joints on the convergence panel and the output filter coil L2092 then suspect the field scan coupling capacitors C2099/2100, also C2083.

## **PANASONIC NV8600B**

This machine plays prerecorded tapes faultlessly. In the E-E mode and when recording however there's persistent flashing on the screen while the brightness fluctuates between very high and very low.

First check the record/playback switches on the thin hinge-open board beneath the machine. Clean or preferably replace them. If the switches are o.k., there's almost certainly a dry-joint in the r.f./i.f. stages. You can check by feeding a video signal in at the video input socket or by scoping TP301 on the luminance panel to see if the waveform here varies with the fault.

## **SONY KV1810UB Mk II**

When the set is first switched on a grainy picture appears. The set keeps trying to produce a normal picture and eventually does so, but may alternate between grainy and normal several times. The problem is not present once the set has warmed up. Also the height occasionally fluctuates when the set is cold.

First check the tuner a.g.c. action by applying an external source of 3V d.c. to the tuner's a.g.c. pin, i.e.

across C133. If this restores normal operation from cold, check the tuner a.g.c. transistors Q211/212 and the associated components as necessary. If not, replace the tuner. Height fluctuations are generally caused by thermistor Th501 in the field output stage. Also check that the field timebase presets are not noisy.

## **FERGUSON 3V22**

The picture has a horizontal wobble, as if there's a tape speed variation. The capstan and other parts in contact with the tape have been cleaned but this has made no difference.

Almost certainly the pinch wheel requires replacement. Be careful not to bend the arm on which it's mounted. Less likely causes are defective ball races in the lower drum or the relay pulley – usually audible – or a defective drum motor (the ripple on the positive side should be less than 0.2V in pause).

## **PHILIPS N1700**

The fault on this machine occurs only when playing back one of the longer tapes. The picture momentarily goes to monochrome, with vertical white lines equally spaced but tending to zig-zag superimposed. Horizontal bands of colour flash can also be seen at times in this condition. The time between the "drop-outs" can vary between a few seconds and several minutes.

As the fault appears only with longer tapes, i.e. when there is a greater weight of tape on the reels, it would seem that there's either a lack of capstan drive torque (clean the capstan and pinch wheel and check the latter for wear) or more likely the back-tension brake is defective. To gain access to this, remove the reel disc assembly, noting the positions of all shims. Examine the two neoprene brake pads attached to the chassis under the lower reel disc and the felt friction clutch. Clean with alcohol.

## **NATIONAL PANASONIC TC86G**

When the set is first switched on the sound is normal but the picture is very snowy. A clean picture can be obtained by turning the a.g.c. delay control fully anticlockwise then fully clockwise. The set will then operate normally until switched off. In the fault condition the voltage at the tuner's a.g.c. input pin is 1.5V but when the gain is restored the voltage rises to 5.5V. There's a corresponding change at pin 4 of the AN331 jungle i.c. The latter has been changed along with the various electrolytics in this area.

We suspect that the trouble is in the tuner's gain-controlled stage where there's some sort of leak to chassis. A new tuner would cure this but you might be able to overcome the problem by permanently biasing pin 1 at 5.5V. Try connecting a 5.6kΩ resistor between pins 7 and 1 and a 4.7kΩ resistor from pin 1 to chassis, disconnecting the a.g.c. line.

## **JVC HR3300**

This machine plays back its own recordings correctly, and they are all right on other machines, but when a prerecorded tape or a tape recorded on another machine is played back there's no colour.

It seems that the colour a.f.c. loop is slightly out of adjustment. Try slight adjustment of R249 on playback – return it to its original position if this has no effect. In the absence of a scope and frequency counter, suspect IC204 (AN236) and IC202 (AN305) in that order.

## SANYO CTP5101

The fault is tuning drift, with low sound and caption buzz. The voltages around the tuner seem to be o.k. and the a.f.c. and i.f. i.c.s have been replaced.

If the fault can be cleared by retuning it's likely that the tuner itself is defective – we've had trouble with this type of tuner on several occasions. If the trouble is confined to the sound, the picture remaining in colour during the fault condition, concentrate on the intercarrier sound circuit – use of heat and freezer should help pinpoint the culprit.

# TEST CASE

## 265

*Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

The Decca 30 was one of the better hybrid chassis, though most of these old sets must by now have been consigned to the scrapheap – after long and honourable service. As with all equipment that's approaching the end of its useful life, the decision whether to repair or scrap is a difficult one. So often it happens that a repair is carried out only to have the set fail, due to quite another cause, within a short time.

Such were the circumstances that attended our dealings with a Model CS2230 recently. On its first visit to the workshop we found that the BY127 h.t. rectifier D600 was short-circuit, taking with it the 3-9Ω surge limiting resistor R603. After replacing these items we returned the set to the customer – the picture was reasonable in view of the age and condition of the set. All went well for a couple of weeks, then the set reappeared in our out-patients' department, with a cryptic "same again, recent repair, no charge" label. The symptoms were the same – dead set. The cause was quite different of course, and the "no charge" bit became something of a bone of contention!

This time the h.t. fuse F1 (500mA) had blown. When we replaced it the anode of the PY500A boost diode glowed cherry red within a few seconds of switching on. The PL519 line output valve remained quite cool. New valves produced similar results. Lack of line drive was discounted because the result of that is generally overheating in the PL519, which remained cool beside its throbbing neighbour. It appeared that there was a short from the cathode of the PY500A to chassis, and an ohmmeter check produced a reading of just a few ohms. The short remained with both top caps removed (measuring from the PY500A's top cap to deck), so the valves were o.k.

The fifth-harmonic tuning capacitor C435 is connected directly from the PY500A's top cap to chassis – it sits on the line output transformer's pins. Disconnecting this item

proved its innocence, so a less direct short-circuit path was sought. The boost capacitor C436 lives down on the timebase panel – it links the transformer's primary winding to chassis via a secondary winding. We confidently snipped it out, but the short-circuit still remained! C431 (feedback to the width control circuit) had no leakage, and disconnecting plug PT/B (timebase panel) made no difference to the short-circuit reading. Continuing along these lines, we disconnected the plugs associated with the scan yoke and the convergence coils, again with no effect on the reading. The tripler connection was next removed, and a careful inspection of the connections and leads to the transformer was carried out. No burn or arc marks were visible, and still the short was there.

At this point the tube was tested to see whether the case was worth pursuing. The emission was reasonable, so after a telephone conversation with the owner the decision to carry on was taken. The culprit was found soon after. What was it? – see next month.

## ANSWER TO TEST CASE 264 – page 105 last month –

We were embroiled in the vision detector/video driver/sync separator/a.g.c. section of a Thorn 1590 monochrome portable last month – no wonder this part of the circuitry was called the jungle when it was put into i.c. form. In the jungle and up the creek without a paddle we were – until we got that scope trace at the collector of the video driver transistor VT6.

When we looked at the waveform at VT6's emitter we were confronted with huge negative-going line pulses. They were larger still at the other end of R1, which links the video signal to the preset contrast control in the a.g.c. detector/amplifier circuit. They were coming through the a.g.c. detector/amplifier transistor VT1, whose emitter was open-circuit and whose collector-base junction was leaky. The a.g.c. gating diode W1 was also leaky, so that there was a clear path from pin 7 of the line output transformer via W1, VT1, the preset contrast control and R1 to the emitter of VT6, where the flyback pulses used to gate the a.g.c. circuit were playing havoc with VT6's operating conditions.

We stuck to our estimate of £16 (supply and fit two transistors and one diode!) though the true cost of the time spent on this one would have bought a handsome new monochrome portable! It's fortunate that this is not too common an occurrence . . .

## QUERY COUPON

Available until 16th January 1985.  
One coupon, plus a £1-50 (inc. VAT)  
postal order, must accompany EACH  
PROBLEM sent in accordance with the  
notice printed on page 162.

TELEVISION JANUARY 1985

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

# MANTEL

**Manchester's No. 1 in Ex-Rental TVs**  
**VHS Video now in stock**

## Working sets ready for re-sale

Philips G8 550s	22/26	£45
Philips 18"		£40
Philips G8 520s	22/26	£35
GEC S/State	from	£35
Thorn 17" 8000		£30
Decca 30	18/20/22/26	£30
Japanese	from	£30

**Many other makes available**  
**from £25**

Discount on quantity

## Some Examples of UNTESTED TVs available

Thorn	10 for	£125
Philips	6 for	£90
Bush	6 for	£80
GEC	6 for	£60
Decca	6 for	£60
Mono TVs avail. s/s		£4 each
New TV trolley stands		
All sizes		£4.95
All Prices subject to V.A.T.		

**Ex Equipment Panels & Tubes Available**

**Over 2,000 TVs in stock**

Ring for quote. Callers welcome.

**419 Barlowmoor Road, Chorlton, Manchester M21 2ER.**  
**Tel: 061-861 8501**

## CentreVision

TEL: 0222-44754

SLOPER ROAD

LECKWITH

CARDIFF CF1 8AB

OPPOSITE CITY FOOTBALL GROUND

5 MINS FROM M4

TELEVISION/VIDEO

(VHS + BETA)

FROM £165

★ ITT CD752 REMOTE	£115
★ PHILIPS G11	£50
★ GEC STARLINE 22-20 (Remote)	£35
★ PYE CHELSEA	£25
★ THORN 9000 20"	£39
★ DECCA 22" BLACK FRONT VERICAP	£25
★ RANK T20 REMOTE	£50
★ PHILIPS 550	£25

**PRICES SUBJECT TO VAT**

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30

SATURDAY 9.00 - 1.00

## COLOURTRADE

MANY YEARS OF SUPPLYING TRADE

### WORKING COLOUR TVs

PHILIPS 550	£35.00
BUSH	£25.00
BUSH 2718	£45.00
THORN 22" V-CAP	£35.00
THORN 8-800	£45.00
JVC 20"	£35.00
GEC ... ITT ... DECCA ... etc!	

### DISCOUNT FOR QUANTITY

WIDE RANGE OF MAKES AND MODELS  
 ARRIVING DAILY — ALL WITH GOOD  
 CABINETS — MANY TO CLEAR FROM  
 'ONLY' £5.00. MIXED LORRY LOAD OF  
 SETS DELIVERED TO YOUR DOOR  
 DIRECTLY FROM SOURCE!

TELEPHONE NOW

021-359 0449

COLOURTRADE

221 Bridge Street West,  
 Hockley,  
 Birmingham B19 2YU

AA117	9p	BC328	6p	BFX85	20p	TIP112	54p	2N3773	100p	BYX70/500	31p	DY802	45p	4042	58p	7482	78p	74LS367	52p	HA-1368	190p	TCA270	40p
AA119	9p	BC557	6p	BFX87	15p	TIP115	45p	2N3819	29p	BYX70/800	36p	EC32	40p	7403	57p	7485	85p	74LS369	52p	HA-1369	190p	TCA800	80p
AA32	9p	BCY32	15p	BFX88	15p	TIP120	56p	2N3866	68p	BYX71/600	80p	EC33	43p	4044	56p	7486	28p	74LS670	130p	LA-1365	170p	TCA940	85p
AC107	28p	BCY33	15p	BFY50	14p	TIP120	47p	2N4031	25p	OA47	6p	EC34	40p	4047	65p	7489	100p	LA-1301	180p	LA-1301	180p	TDA1170	90p
AC126	17p	BCY34	15p	BFY51	14p	TIP121	46p	2N4036	25p	OA90	4p	EC35	40p	4048	49p	7490	35p	LA-3350	150p	LA-3350	150p	TDA1412	160p
AC127	15p	BCY42	20p	BFY52	14p	TIP122	47p	2N4037	25p	OA91	4p	EC36	40p	4049	49p	7492	58p	LA-4031	140p	LA-4031	140p	TDA2002	80p
AC128	15p	BCY56	16p	BFY56	25p	TIP125	47p	2N4443	76p	OA280	7p	EC38	52p	4050	40p	7493	35p	LA-4032	190p	LA-4032	190p	TDA2103	150p
AC128K	23p	BCY70	16p	BFY57	25p	TIP126	56p	2N4444	76p	OA282	7p	EC39	57p	4051	62p	7495	48p	LA-4051	250p	LA-4051	250p	TDA2020	140p
AC141K	23p	BCY71	16p	BFY64	25p	TIP127	56p	2N5061	20p	IN314	2p	EC38	57p	4052	61p	7497	80p	LA-4101	140p	LA-4101	140p	TDA2030	140p
AC142K	22p	BCY72	16p	BFY67	20p	TIP147	100p	2N5294	30p	IN401	4p	EC38	57p	4053	61p	7497	80p	LA-4102	140p	LA-4102	140p	TDA2032	140p
AC153K	23p	BD111	20p	BFY100	18p	TIP2955	114p	2N5296	30p	IN4002	4p	EC38	57p	4054	85p	74111	52p	LM723	32p	LA-4420	150p	TDA2530	90p
AC176	18p	BD124P	50p	BSX20	15p	TIP3054	38p	2N6106	40p	IN4003	4p	EC38	57p	4055	90p	74116	85p	LM741DI	15p	LA-4430	150p	TDA2532	90p
AC176K	20p	BD124	11p	BT106	90p	TIP3055	34p	2N6107	40p	IN4004	4p	EC38	57p	4056	95p	74119	85p	LM741 Met	15p	M83712	150p	TDA2540	75p
AC187	15p	BD128	35p	BT107	90p	TIP3056	34p	2N6108	40p	IN4005	4p	EC38	57p	4057	95p	74122	85p	LM741 Met	15p	M83712	150p	TDA2540	75p
AC187K	15p	BD131	35p	BT116	80p	TIP3056	34p	2N6109	40p	IN4006	4p	EC38	57p	4058	95p	74123	20p	LM741 Met	15p	M83712	150p	TDA2540	75p
AC188	17p	BD132	25p	BT119	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4059	25p	74125	40p	NE556	40p	SAS570	110p	TDA2590	100p
AC188K	23p	BD135	20p	BT120	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4060	25p	74126	45p	NE556	40p	SAS570	110p	TDA2590	100p
AC198	48p	BD136	20p	BU104	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4061	25p	74127	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AC198K	48p	BD137	20p	BU105	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4062	25p	74128	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AD142	48p	BD137	20p	BU105	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4063	25p	74129	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AD142K	48p	BD137	20p	BU105	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4064	25p	74130	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AD149	45p	BD138	20p	BU110	110p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4065	25p	74131	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AD151	22p	BD139	20p	BU126	140p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4066	25p	74132	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AD162	22p	BD140	20p	BU204	75p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4067	25p	74133	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AF124	25p	BD140	20p	BU204	75p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4068	25p	74134	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AF125	25p	BD150	30p	BU205	70p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4069	25p	74135	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AF127	25p	BD150	30p	BU200	75p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4070	25p	74136	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AF139	24p	BD157	38p	BU208A	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4071	25p	74137	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AF239	22p	BD158	38p	BU208D	120p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4072	25p	74138	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AL112	70p	BD166	30p	BU326	85p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4073	25p	74139	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AL113	80p	BD177	30p	BU406	85p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4074	25p	74140	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AL113K	80p	BD177	30p	BU406	85p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4075	25p	74141	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AS217	100p	BD179	32p	BU408	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4076	25p	74142	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AU110	100p	BD181	45p	BU500	110p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4077	25p	74143	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AV102	180p	BD182	60p	BU526	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4078	25p	74144	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
AV102K	180p	BD182	60p	BU526	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4079	25p	74145	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BA145	18p	BD201	33p	MJ2500	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4080	25p	74146	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BA145K	18p	BD202	33p	MJ2501	110p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4081	25p	74147	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BA148	10p	BD203	42p	MJ2955	55p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4082	25p	74148	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BA154	10p	BD204	42p	MJ3000	115p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4083	25p	74149	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BA157	12p	BD222	31p	MJ3001	115p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4084	25p	74150	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BB101	13p	BD225	31p	MJ29A	30p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4085	25p	74151	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BB103	16p	BD232	31p	MJE340	23p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4086	25p	74152	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BB105	16p	BD234	32p	MJE30A	30p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4087	25p	74153	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BB205B	24p	BD237	21p	MJE350	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4088	25p	74154	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC107	7p	BD238	24p	MJE520	30p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4089	25p	74155	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC108	7p	BD433	25p	MJE2955K	90p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4090	25p	74156	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC109	7p	BD437	28p			TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4091	25p	74157	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC115	10p	BD535	38p	OC28	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4092	25p	74158	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC118	11p	BD536	38p	OC29	80p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4093	25p	74159	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC140	10p	BD537	40p	OC35	100p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4094	25p	74160	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC141	10p	BD538	40p	OC36	120p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4095	25p	74161	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC142	19p	BDX32	100p	OC45	50p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4096	25p	74162	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC143	19p	BDX65	80p	OC71	30p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4097	25p	74163	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC148	6p	BF181	18p	OC72	50p	TIP3056	34p	3N1433	65p	IN4007	5p	EC38	57p	4098	25p	74164	42p	AN-214P	200p	SN7603N	140p	UPC-556H	80p
BC148K	6p	BF181	18p	OC200	180p	TIP3056	34p	3N143															

# CENTRAL T.V.

## LATE MODEL T.V. NOW IN STOCK

**G.11 REMOTE + TEXT, ITT REMOTE, THORN 9600, 9800,  
BUSH T20/T22/T26, DECCA 80/100, G.E.C. IN LINE**

### SPECIAL OFFERS ON WORKING SETS

10 550 G8 22" .....	£220
10 520 G8 22" .....	£180
10 ITT CVC 5-8-9 .....	£180
10 DECCA HYBRID .....	£180
10 BUSH MIXED .....	£140
10 THORN 8500 .....	£250

### SPECIAL OFFERS ON OFF THE PILE SETS

10 550 G8 22" .....	£130
10 520 G8 22" .....	£90
10 ITT CVC 5-8-9 .....	£120
10 DECCA HYBRID .....	£120
10 BUSH MIXED .....	£90
10 THORN 8500 .....	£170
10 THORN 3000, 3500 .....	£100

## VHS VIDEOS – 100's IN STOCK

### BRAND NEW 14" AND 16" PORTABLES

### BRAND NEW PYE 20", 22", 26" WITH STEREO – TEXT – REMOTES

MANY MORE BARGAINS IN STOCK – PHONE AND HAVE *YOUR* ORDER READY FOR COLLECTION  
LORRY LOADS DIRECT FROM SOURCES DELIVERED TO YOUR DOOR

### HOT LINE BIRMINGHAM

**021-622 1023**

**021-622 1517**

48/52 PERSHORE STREET  
BIRMINGHAM B5 4RR

### HOT LINE LONDON

**01-807 4090**

**01-884 1314**

CEDAR HOUSE, NOBEL ROAD,  
ELEY ESTATE, EDMONTON, LONDON

## MAIL ORDER ADVERTISING

#### British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

#### Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."

## TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

**TELEPART**

32 Temple Street,  
Wolverhampton, WV2 4LJ.  
Phone: (0902) 773122.

## IRISH TV NOTICE (EX RENTAL T.V. SALE)

We can supply in good working order Bush, Pye and Ferguson from £60, Philips G.8. From £80, Decca from £90, B/White £25, Re-Gunned C.R.T.s from £40 (We have our own Re-Gunning plant). 500 sets to choose from. Fresh stocks weekly. Phone now for full price list to Ireland's largest distributor of used TVs to the trade.

ALL PRICES INCLUDE V.A.T.  
We can deliver to any part of Ireland.

### TELE SPARES LTD.

Unit 113, Elm Road,  
Western Industrial Estate,  
Dublin 12, Ireland.  
Telephone: Dublin 521211/521756.



# KEEP SNUG!

## THIS WINTER

Find out about the wide choice of portable heaters in Practical Householder's January issue.

**BEAT THE POWER CUTS!**  
D.I.Y. Emergency Heating & Lighting

**plus** \* Traditional Hand Tools  
\* Fitted Bathroom Units  
\* Tile Face-lift

**not forgetting**  
**HOME PLUS**

the BONUS colour magazine.

in

January issue



# Practical Householder

## TELETRADERS

Forde Road, Brunel Industrial Estate,  
Newton Abbot, Devon  
Telephone: (0626) 60154

The Best Quality Sets Available  
Anywhere

All First Class working order and excellent  
cabinets.

Philips G8 550	£40
Philips G11	£85
GEC Solid State	£35
Thorn 3500 Electronic 22"	£35
Thorn 9000	£60
Thorn 8800	£45
Thorn 9800	£55
Thorn 1500 Mono 20" very clean	£6

Full spares back-up of tubes and panels—  
Bulk terms to other wholesalers



**THE NO. 1 WHOLESALER IN THE SOUTH**

## T.V. DISTRIBUTORS NORTHERN (LEEDS)

Large stock of good quality ex rental/part  
exchange colour TV's.

THORN, ITT, PHILIPS, GEC, PYE,  
DECCA, BUSH, JVC

★ ★ ★  
**KORTINGS TO CLEAR FROM ONLY £10.00**  
★ ★ ★

TEL: LEEDS (0532) 624996

TV DISTRIBUTORS NORTHERN,  
UNIT 10, Ashley Trading Estate,  
Buslingthorpe Green, Leeds LS7 2HG.

2 YR. GUARANTEE **APOLLO** 20/30 AX

**TRADE AND QUANTITY DISCOUNTS**

FREE LOCAL DELIVERY — SAME DAY ● FITTING SERVICE £20.  
FAST MAIL ORDER GB 2-3 DAYS — OVERSEAS ON REQUEST.

A47 32/343X 470 BCB22	£37
470 ESB22/EFB22/ERB22	£45
A51-161X	£45
A51-220X/192X	£37
510 JKB22/JEB22/JDB22/ALB22	£45
A56-120X/123/140/410	£38
560 DZB22/HB22/AKB22	£45
A63-120X	£39
A66-120X A67-120X/140/150/200X	£39
20AX A56-500X/510X A66-500X/510X	£48
30AX A56-540X/A66-540X	£48

If your tube type is not in stock we can arrange collection — rebuilding + redeliver


PLEASE PHONE BEFORE CALLING

**061-799 0854.** 24 hour answering service  
43 Clarke Crescent, Little Hulton, Worsley, Nr Manchester M28 6XL

The World of . . . .
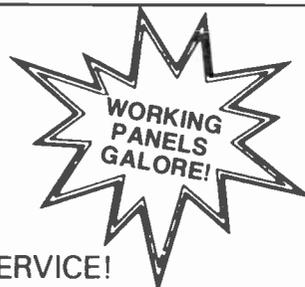
# “TELE PANELS”

52 Mount Pleasant Road, Chigwell, Essex.  
Telephone 01-729 0506.



COMPARE OUR PRICES!

COMPARE OUR SERVICE!

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731	8.00		10.00		18.00	10.00	7.00	8.00		4.50
PUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00				5.00	14.00		
DECCA BRADFORD	3.00		7.00			4.00		FRAME TIME BASE £4		
DECCA 80	12.00	P.O.A.	14.00		12.00	10.00		14.00		P.O.A.

Other makes of panels — telephone for prices!

TRIPLERS FOR ALL MODELS £3.00    SPEAKERS £1.50

P+P 1 PANEL £1.50    2 PANELS OR MORE £3.00

CASH WITH ORDER — PLEASE

**POST OFF YOUR CHEQUE NOW! & YOUR PANELS SENT BY RETURN OF POST!!!**

## HOCKLEY DISCOUNT TELEVISIONS

94 Soho Hill, Hockley,  
Birmingham B19 1AE.

Telephone: 021-551-2233

PRICES START FROM £6  
WORKING SETS FROM £18  
FROM OUR SHOWROOM

**DISCOUNT ON QUANTITY**  
BEST QUALITY SETS AVAILABLE  
AT UNBEATABLE PRICES

PHILIPS G8 550 FITTED WITH  
REGUNNED TUBES £38

Philips G8, G11, Bush T22, GEC, Starline, Japs.,  
Decca 1800, Pye 222s, BRC 9000, 9600, 9800,  
Sony, latest Hitachi, ITT, CVC30, CVC45, plus  
remote control models.

## NORTHERN T.V. DISTRIBUTORS

Unit 2, Perth Court,  
Team Valley Ind. Estate,  
Gateshead, Tyne & Wear  
Telephone: 091-487 5389

Opening hours 9 - 7 Monday - Saturday  
Sundays by appointment.

## TEL-X BLACKBURN

FOR THE VERY BEST IN  
TELEVISION DISPOSALS

Decca      Thorn      Pye      Bush  
Philips      ITT      GEC      + Remotes

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

HUNDREDS TO CHOOSE FROM  
WORKERS FROM      **£25.00**  
Off the Pile from      **£ 8.00**

☆ ☆ ☆ ☆ ☆ ☆ ☆ ☆

DELIVERIES ARRANGED ON QUANTITY

## TEL-X BLACKBURN

Unit P3, Roe Lee Industrial Estate,  
Whalley New Road,  
Blackburn, Lancs.

**Tel: 0254 679984**

## SETS & COMPONENTS

BRAND NEW MONOCHROME 20" 110 degrees CRT's £10. Each. 10% off tens. 01-897 2602.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

JAPANESE COLOUR TVs. Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished. Trade only. J.M. Pearson Television. 0484 863489.

### TRADE COLOUR TVs ALWAYS 200 IN STOCK

Colour from £5.00 Mono £2.00  
Tested colour tubes from £5.00 plus p+p

BRAND NEW VIDEOS  
V2022 and V2023  
VHS and BETA

Just in  
20" + 22" GEC  
Boxed with stand £85.00

ALL STOCK CHANGES WEEKLY  
(0934) 514047/512792/27560  
P&R SUPPLIES, Unit 5,  
Worle Industrial Estate,  
Weston-Super-Mare. Exit 21 M5.

### WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output  
Z718 (T703A, T706A) £20.50  
New (Complete)  
Less Focus Module and  
Rectifier £10.50  
T20, T22 (T705A) £11.00  
T26 (T705B) £11.00  
Switch Mode  
T114A/B £8.00

Genuine RBM Units.

#### AERIALS

UHF Aerials P & C Wideband 4 Bay  
Bowtie (12.5 dB) £20.00  
Above with built-in Broadband amp.  
(27dB) plus stabilised power  
supply £45.00

Prompt Postal Service P&P Paid.  
Add 15% VAT to all prices.  
DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,  
Pinner, Middlesex. HA5-2QT.  
Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

## TELEVISION

GOOD QUALITY TRADE  
TVs COLOUR OR MONO  
SUITABLE FOR SALE OR  
RE-RENT, WIDE CHOICE  
OF MAKES AND  
MODELS

**GENERAL FACTORS** UNION STREET  
DONCASTER  
DN1 3AE

TEL (0302)  
68416

GOOD MOTORWAY ACCESS

# TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.30 per single column centimetre (minimum 2.5 cms). Classified advertisements 37p per word.

## SCREENPLAY

Your Friend in the  
TV Business

Guaranteed - Complete Sets  
Trade Workers  
Panels by Post  
Mono's  
Stands Aerials Accessories Etc.

from £5.00  
from £25.00  
from £3.00  
from £1.00

### TO CLEAR

BUSH SINGLE/DOUBLE CHIP 5 for £25.00

BRADFORD DECCA 5 for £45.00


PHONE US FIRST FOR WORKING SETS IN  
QUANTITY, WE'LL GIVE AN UNBEATABLE  
PRICE.

OPEN 6 DAYS 10-6.30pm/10-5.00pm SAT.

Phone:

Baldock 894905

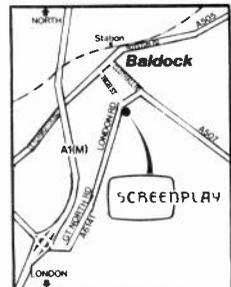SECTION THREE, UNIT FOUR, SERL COMPLEX,  
LONDON ROAD, BALDOCK, HERTS.



### A.B.D. TELEVISIONS

Suppliers of colour and  
mono televisions to the  
trade.

Workers and  
non-workers:

*Pye Chelsea, Philips, Pye,  
GEC, Thorn 8500, 8800,  
9000 and 9600, Bush T20  
and TT22, ITT 600 series,  
Japanese, Hitachi, Nat.  
Pan J.V.C.*

Many other modern sets  
by popular  
manufacturers.

For quotation and  
prompt service:

Ring Notts (0602) 864627

UNIT 3+3A,

Meadow Trading Est.  
Meadow Lane,  
Nottingham NG3 3HQ.

### The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

Part 1.  
The Colour Signal  
Part 2.  
The Receiver Decoder  
Part 3.  
Receiver Installation

VHS★★★V2000★★★  
BETAMAX★★★UMATIC

For full details telephone  
0253 725499 (Day)  
0253 712769 (Night)

Or send for precise details  
FLINTDOWN CHANNEL 5  
339 CLIFTON DRIVE SOUTH,  
LYTHAM ST ANNES FY8 1LP  
(enclosing this advert)

NAME .....  
ADDRESS .....  
..... TEL:.....

**T.V. SPARES, PANELS  
AND MANUALS**  
PHILIPS · GRUNDIG

TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.

Thorn 3000/3500  
Thorn 9000  
**UNIVERSAL**  
1 year guarantee

**TRIPLERS**  
**£4.95** inc.  
p&p

The UNIVERSAL TRIPLER can be used in most  
G.E.C., I.T.T., Pye, Rank, Decca & Continental  
sets.

**WING ELECTRONICS**

15 Waylands, off Tudor Rd, Hayes End, Middlesex

# SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

## IRISH TV TRADE

CAN WE BE OF SERVICE TO YOU?

Regular supplies of Quality Colour TVs

**LOWEST PRICES**

Working Sets from £18

Non-working Sets from £8

FREE DELIVERY ANYWHERE

contact:

# J. M. G. Electronics

Omagh, Co. Tyrone,  
Northern Ireland.  
Omagh (0662) 46032 night  
Omagh (0662) 47911 day



## COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-
DECCA 13/30	3.00	-	7.00	5.00	-	4.00
BUSH A823	4.00*	-	10.00*	5.00*	2.50	4.00
THORN 8/8½	-	-	10.00	5.00	-	5.00
PYE 205	3.00	3.50	5.00	10.00	-	-
THORN 3/3½	5.00	5.00	5.00	8.00	-	10.00
G8	6.00	-	8.00	7.00	15.00	5.00

\*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.  
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

### GOLCAR T.V. SERVICES (formerly LAVITE LTD.),

Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.

## EAST ANGLIA SUPPLIES

Fully working colour TVs from £25.00 plus VAT straight from our retail shelves. Most makes are available and small regular orders are welcome. Personal services guaranteed and if we can help you boost your rental or retail trade we would be delighted.

Free delivery available  
(only petrol charged).

Contact John, Dave or Steve at

**Barry T.V. Services**

on Cambridge 69215  
or Ely 61462

## STARLITE ELECTRONICS

NOW MOVED TO:  
WILLOWS FARM,  
A13 RAINHAM, ESSEX.  
Rainham 23225 also  
Hornchurch 50238.

- TV TUBES -

2 year guarantee

Most types available

Japanese including Sony

Ex-Rental TVs from .....£15.00

Untested Panels.....£4.00

## CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.

Tel: Canvey Island (0268) 690577

### CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50

INLINE TUBE TYPE FROM £35.00

MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed  
to Original Manufacturers Specifications.

MULTISTANDARD Colour Television. LUXOR VHF/UHF TV/Monitors to most standards, including PAL/L/SECAM/L (UK/French) option. 20", 22" & 26" from £280. ex VAT. PORTATEL CONVERSIONS LTD., 25 Sunbury Cross Centre, Sunbury, Middlesex. Tel. 09327 88972.



\* Britain's most reliable source of quality TVs.

\* Hundreds of working polished TVs.

\* GEC Starline

\* Decca 80

\* Decca 88

\* Decca 100

\* Pye G11

\* Thorn 8800

\* Pye 222 Series

All working and polished.

These are not from major companies. A lot are from hotels and have had very little use.

Excellent reliable sets for rental.

Krystal Marketing Ltd,  
Breedon Cross  
Storage,  
Dale Road, Selly Oak,  
Birmingham B29 6AQ.

Phone 021-471 3023  
Telex 335540-G  
Ask for Les

## Trent Tubes

31 RADCLIFFE ROAD,  
WEST BRIDGFORD, NOTTINGHAM

THE QUALITY REBUILDER

PHONE: (0602) 813329

ALL TUBES CARRY A TWO YEAR GUARANTEE

EXTENDABLE TO FOUR YEARS

All Sizes of Standard Deftas  
ONLY £27.50 (A56-120 - A66-120 etc.)

A51-161 - A51-163 £39.00

A55-66 500/510 (20 AX) £42.00

560 DZB 22 £43.00 - 560 EGB 22-510 VLB 22 £45.00

1000's more available. VDUs, MONOs, Industrial etc.

WE NOW REBUILD SONY TUBES

Phone for details

STOCKISTS

Peterborough: H. DONNOR 0733 71809 Derby: VTA WORKSHOPS 0332 369132

TECHNICAL ADVICE SERVICE

All prices + VAT & Exchange

Suppliers to Broadcasting Authorities

Quantity Discounts

### COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Crosshatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. £75.90

### OUTPUTS PROVIDED

UHF OUTPUT  
VIDEO OUTPUT  
SOUND OUTPUT  
LINE PULSE  
FIELD PLLSE



Line Output Transformer Tester £11.50  
BW Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale £18.50  
In Circuit Transistor Tester £14.25  
Capacitance Meter measures 10pF to 1µF complete with moving coil meter £14.75  
Car Alarms £12.50

S.A.E. for details. - Prices include P&P & VAT.

**C.M.J. ELECTRONICS**

Unit 8, 16 Union Mill Street, Horseley Fields,  
Wolverhampton WV1 3DW.  
Tel: (0902) 871563


# N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

## Bonanza Clearance!!! New Year Prices...

100's of good class HP Repos and  
Ex Rental Colour TV's reduced to  
**ROCK BOTTOM PRICES!**

Bush T20 (Excellent Cabs)	was £60	.....	NOW £40
Bush 718 P.I.L. Tube	was £30	.....	NOW £25
Bush 2 Chip Decoders	was £15	.....	NOW £8
Philips G8	was £28	.....	NOW £23
Philips G11	was £70	.....	NOW £55
GEC 2010	was £25	.....	NOW £20
Thorn 3500	was £12	.....	NOW £8

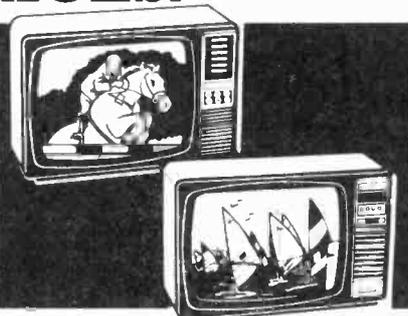

Hybrids £5 all makes!



Many more inc Pye KT30, Ferguson TX etc.

### Video

VHS – Sharp 7300, 8300, 9300. Ferguson 3V28, 3V22.  
Sony Beta.

**Mono TV's £1 each (lots of 25)**

Thorn 1500 £4, 1600 £12. Discount for Quantity (like new).  
**No cheques.**

### White goods

Hoover Twins from £6. Hotpoint 1460 from £10.  
Autos all makes from £10.

### SPARES! SPARES! TV PANELS

	I.F.	DECODER	LINE O/P	POWER	CONVERG.	VIDEO	FRAME T3
BUSH 2 CHIP	3.00	8.00	6.00	3.00	3.00	—	5.00
3000/3500	2.00	4.00	8.00	8.00	5.00	5.00	6.00
G8	5.00	7.00	14.00	8.00	5.00	—	5.00
	with sound panel						
GEC 2110	10.00	5.00	12.00	6.00	5.00	5.00	5.00
BUSH 718	8.00	15.00	25.00	3.00	5.00	—	15.00
BUSH T20	8.00	15.00	20.00	20.00	5.00	—	15.00

P&P 1 panel £1.50, 2 panels £2.00, 3 panels £2.50 etc. Quick Despatch – C.W.O. please.

**All prices plus VAT**

**CASH ONLY – NO CHEQUES**

**DELIVERY CAN BE**

**ARRANGED TRADE ONLY**

**(0274) 688458 OPEN 6 DAYS A WEEK**

Unit 12, Wharfedale Road  
M606 Euroway Estate  
Bradford

OPEN MON-SAT 9-5.30  
Don't forget! We are open  
all day Saturday!

### 11GHz Satellite TV Receiver

Receives 'Music Box' Pop music TV Channel on ECS satellite. Can be supplied with or without dish (1.5M minimum in most of UK). Stereo sound decoders available shortly for this channel. *Phone or write for more details.*

**HUGH COCKS TV SERVICES,**  
Cripps Corner, Robertsbridge,  
Sussex TN32 5RY.  
Tel: 058083 317.

### T.V PANELS

REPAIR EXCHANGE SALES SERVICE  
PRICES FOR REP. EXC. AS FOLLOWS

Chassis	IF	Decoder	Line Scan	Power Supply	Frame
Philips G11	18	16	20	18	16
Bush T20	X	12	16	15	12
Bush T26	X	16	18	15	X
Bush 718	X	12	18	X	12

All panels are repaired and aligned according to rank std.

Ring for prices to buy panels. Prices shown inclusive of postage, etc.

All panels guaranteed for 3 months.

**T. K. PANELS SERVICE**

31 Bronte Paths, Stevenage (0438) 61567

### WIZARD DISTRIBUTORS TV & VIDEO SPARES

Visit our trade counter and see the huge range of components inc. tubes and video heads. Only minutes from the town centre and motorway routes.

Fast friendly service and technical assistance available.

Come in and see our trade counter special offers.

Open Monday to Friday 9 am to 4.45 pm  
Trade Only

**EMPRESS STREET WORKS**

Empress Street  
Manchester M16 9EN

Tel: 061-872-5438, 061-848-0060

### WORKING CTV's

*The Best & Cheapest in Lancashire*

I.E. Decca 18" to 26"	£24.00
GEC 20" to 26"	£30.00
Philips G8 22" to 26"	£25.00
Bush 20" to 26" 2 chip	£18.50

*All sets are tested & working*

Many more makes & types available. Working mono's only £3.50. Non workers available.

Phone: John Powney  
at Kirkham, near Preston  
(0772) 683392.

## FOR SALE

**CRT Regunning Plant:**  
Comprising of:-

- 2 x Ovens,
  - 2 x Vacuum Pumps and Diff's,
  - 1 x Spot Knocker,
  - 1 x Getter Fireer,
  - 1 x Welding Machine,
  - 1 x Annealing Oven,
  - 1 x Precision Emission Tester,
  - 1 x Let Down Station,
  - 1 x Custom Built Extraction System,
- All gun and glass stock, plus goodwill. Plus many other items.

To be sold as a complete lot,  
£6,500.

Contact: Mr Adolpho on  
0622 872400

## REBUILT COLOUR TUBES

EXAMPLE PRICES DELTA

All sizes up to 22" — £28.00  
26" From — £32.00

*All In Line P.I.L. Mono Gaming Machine*  
*C.R.T.s 560EGB22 56-611-510JKB22*

20 AX £40.00

30 AX £48.00

Fast U.K. Delivery

Call or Phone:

**RE-LIFE T.V. TUBES**

PLANE STREET,  
OLDHAM, LANC'S.

061-665 2668

*Wholesalers REG in North & South Wales*  
*Competitive Prices*

### TELEVISION TUNER REPAIRS

BRITISH, EUROPEAN  
JAPANESE ETC.

ELC 1043/05 TUNERS  
AS NEW £4.60 inc.

**MEN-TU ELECTRONICS LTD.**

SALTERS LANE,  
FAREHAM, HANTS.

Tel: 0329-235116

#### GUARANTEED 90% WORKING

100's of GEC 2110/2111 stripped to spares

Decoder	Line Output	Power	Convergence	Tram-Time Base	Tripler
13.00 single	£4.00	£2.50	£2.50	£3.00	£2.50
combined					

Other types e.g. Bush, G8, Thorn 8500, Fye, GEC Hybrid all non-working/complete.

Decoder	Line	Power	Convergence	Frame	IF	Tripler
Bush	£5.00	£5.00	£3.00	£3.00	£2.00	£2.50
G8	£3.00	£5.00	£4.00	£3.00	£5.00	£2.50
3500 Thorn	£3.00	£4.00	£4.00	£3.00	£2.00	£2.50
GEC	£3.00	£5.00	£4.00	£2.00	£2.00	£2.50
Fye	£3.00	£5.00	£5.00	£2.00	£2.00	£2.50

**SABACO, Elastic Yarns Building,**  
Derby Road, Sandiacre, Notts.  
Tel: (0602) 397555

PHILIPS G11 and Bush T20. Regular supplies. For prices phone 01-845 2036.

**PL519 £4.45. PL508 £1.80**

**PY500A £1.60**

New - Boxed - Guaranteed

**BILLINGTON VALVES**  
IRWIN DRIVE, HORSHAM

### WORKING COLOUR T.V.'s

TO THE TRADE FROM

**£15**

LARGE SELECTION OF  
COLOUR T.V.'s INCLUDING  
GOOD DISPLAY OF WORKING  
SETS, MANY LATE MODELS, IN  
OUR SHOWROOM

DELIVERY CAN BE ARRANGED

'PHONE MARK WOODWARD 0299-250161

TRADE, UNIT 40,  
HARTLEBURY TRADING ESTATE,  
NR. KIDDERMINSTER, WORCS.

### EX-RENTALS TELEVISIONS IN BULK

Most makes including late models.

MONITEC 0299 400233.

Always hundreds in stock

**COUNTY DURHAMS ONLY**  
**WHOLESALE**

All markets catered for

	UNTESTED	WORKING
G8 520	From £12.00	From £20.00
G8 550	From £12.00	From £30.00
GEC S/S	From £15.00	From £25.00
All Hybrids	From £12.00	From £20.00
Jap	From £20.00	From £30.00

All sets sold as working are fully prepared to the highest standards and are ready for retail or rental.

### REGUNNED TUBES

Up to 22" Delta	£27.00	2 yr guarantee
Up to 26" Delta	£30.00	"
Pil & Inline	£45.00	"

All tubes are regunned to the highest specifications. We are the best because we want our customers to come back.

### INTERTEL

Unit 27 Whesoe Road,  
Darlington (0325) 486896  
Co. Durham.

#### Order form

Please insert the enclosed advertisement in the next available issue of Television

Heading .....

Signature .....

Date .....

No. of ins..... Chq/PO .....

**TELEVISION**  
Classified Advertisement  
Department,  
Room 2612,  
King's Reach Tower,  
Stamford Street,  
SE1 9LS.

NAME AND ADDRESS

**! YOU HAVE TRIED THE REST  
NOW TRY THE BEST !**

## Quality 6 Button TVs on Offer

Ultra 6725 22"	GEC S/S
Furg. 3738 22" T/T	ITT CK505
Furg. 3749 22"	Philips 550 22"
Furg. 3722 22"	Bush T20

Also 17" 8000 various models + many more to choose from.

**SCARBOROUGH TV TRADERS CO LTD**  
85 Columbus Ravine, Scarborough,  
N. Yorks. 0723 368087.  
1 hour from A64/A1 junction

## TELEVISION

Trade & Retail supplies of  
s/h colour & mono TVs.  
Most makes available,  
workers or non-workers

## SOUTH PARK DISTRIBUTORS

Unit 4 Rubastic Road,  
Brentpark Industrial Estate,  
Southall, Middx. UB2 5LL.  
01-574 4631, Ext 28

## SITUATIONS VACANT

**WANTED:** Exp TV engineer to work in Northern Ireland starting Feb 85 to service ex-rental televisions. Must have good exp on most sets including British and Japanese. Good wages and accommodation. Write to TV Box No. 190.

## AERIALS

**SPECIALIST VHF AERIALS,** 28-170 MHz, OIRT/TV-DX, Amateur, AB/MB/Cordless. Folder SAE, AERIALTECH, 33 Cherville Street, Romsey, Hants SO5 8FB.

**EVERYTHING NECESSARY** for multi-outlet systems. Filters, diplexers, amplifiers, etc. Use trade gear and save pounds. Catalogue 50p (refundable). Professional system planning/advice £5.00 (refundable). Quick queries free. Wrights Aerials, 43 Greavesike Lane, Micklebring, Rotherham.

## CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and comprehensive range of signal amplification equipment. For example: low noise electronically remote controlled masthead pre-amp 1.6db noise. CH. 17-69. Set side amplifiers, distribution amplifiers, notch filters 4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db gain or 4 6db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

**CLEARVIEW AERIALS,**  
173 Kings Road,  
Kingston Upon Thames, Surrey.

## AERIAL BOOSTERS

**B45H/G-UHF TV** next to the set fitting, gain about 20db, PP3 battery or 8V to 14V/working. Price £8.70. P&P 30p.

**UHF TV BOOSTER MODULE.** PCB ready made up to cover the complete UHF TV band. Gain 10db, noise 1.9db. 8V to 14V/W. Price £2.50. P&P 30p.

**AMPLIFIED SET TOP AERIALS.** Trebles the gain, fully portable, price includes batteries. Price £9.70. P&P 50p.

**B11 VHF/FM RADIO** next to the radio fitting, gain 14db. Price £7.70. P&P 30p.

**ELECTRONIC MAILORDER,**  
62 Bridge Street, Ramsbottom,  
Lancashire, BL0 9AG.  
Tel: Ramsbottom (070 682) 3036.

S.A.E. for leaflets. Access/Visa Welcome.

## BUSINESS OPPORTUNITIES

### BUSINESS OPPORTUNITY LUMINANCE DELAY LINES FOR COLOUR T.V.

We are looking for stocking distributors in all the countries for Luminance Delay Lines manufactured by our unit INDIAN TELEVISION INDUSTRIES as per Standard Specifications, and tested and passed by Department of Electronics Govt. of India. Business Houses and individuals interested in this offer are requested to write to us for terms, giving details of their contacts with colour T.V. manufacturers and other consumers of LDL with technical data and quantity of LDL required by them and market potential they command in their area, within 15 days.

**DIPLOMAT PRIVATE LIMITED**  
49/2, Gurjaipal Nagar, JALANDHAR-144 001 INDIA

## SERVICE SHEETS

### TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

**Colour £2.00 Mono £1.50**

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and enquiries.

**SANDHURST TV SERVICES (MAIL ORDER)**  
49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

### 30,000 SERVICE SHEETS IN STOCK ALL AT £3.00 ALSO COLOUR MANUALS AVAILABLE AT £6.00 EACH

TV Sheets, Black and White, also Radiograms, Record Players, Music Centres. Japanese models in stock. Circuit diagrams only. Also Tape Recorders etc., etc. Please forward s.a.e. Send cheque or P.O.

**C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.**

**BELL'S TELEVISION SERVICES** for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

## EQUIPMENT FOR SALE

**COMPLETE TUBE** re-gunning plant in good working order. Electric ovens for regunning. Re guns 15 colour (Sony Trinitron, Pil, in line, tubes, etc). Tubes in 24 hour cycles. Only £4,000 plus VAT. Free training provided. Tel. 0582 410787.

## VIDEO

**ARE YOU A TV ENGINEER WHO WANTS  
TO KNOW ABOUT VIDEO RECORDERS?**

THEN YOU NEED

**"DOMESTIC VIDEO CASSETTE  
RECORDERS A SERVICING GUIDE"**  
by S. R. BEECHING

Available for only **£15.50** inc. p&p

From: **NEWARK VIDEO CENTRE,**  
108 London Rd., Balderton, Newark, Notts.  
Tel: 0636 71475 **ACCESS OR VISA**

## FOR SALE



# Sabaco

For a  
great deal!

### VAN LOAD DIRECT FROM SOURCES

Remember all sets cleaned and soak tested. Most makes available, any quantity e.g. GEC, Bush, Decca, ITT, Pye G11, T22, 9000, 9800 etc. Mixed sizes.

**WORKING SETS FROM £20 upwards.** e.g. GEC 2110 £25 min of 6 and etc.

**COMPLETE NON-WORKERS from £10** in quantities.

Black/White in batches of 10 at £1.50.

### SPECIAL OFFER!

26" G8/3500/HYBRIDS


QUANTITIES OF 10 @ £5 each

SPARE PARTS AVAILABLE AT COMPETITIVE PRICES.

PLEASE SEE SEPT/OCT ISSUES.

N.B. Add 30p extra per panel.

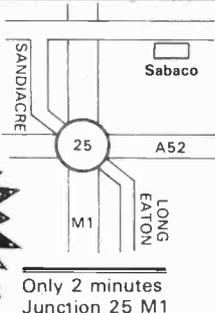**ALL PRICES SUBJECT TO VAT & AVAILABILITY.**



Only 2 minutes  
Junction 25 M1

**Sabaco**  
Elastic Yarns Building,  
Derby Road, Sandiacre,  
Nottingham.

Open 6 days a week  
9.30 a.m. — 6.00 p.m.

Telephone: (0602) 397555

## FOR SALE

173 TELEVISION COPIES 1962 to 65. 1974 to 83. Complete less five copies. Enquiries Chorley 73081.

100 TELEVISION RENTAL accounts for sale in North London/Herts area, turnover 10,000 pa. TV Box No. 191.

## TRADE ONLY

Closing down warehouse. All stocks to be cleared.

TV Components, Audio, Wire, Electrical, Racking. Etc.

Offers are invited for bulk purchase of stocks listed above.

No reasonable offer refused.

Send for catalogue to:

## ELECTRONIC SUPPLIES

18 Leucha Road, Walthamstow E17 7LG or Telephone: 01-521 3912, after 6.30 evening.

## BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

FULL SIZE TOP QUALITY service sheets £2.50 + I.s.a.e. CTV/Music Centres £3.50 + I.s.a.e. Repair data almost any named TV/Video £10.50 inc. circuits. L.s.a.e. brings any quite free magazine/pricelists. TIST, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

RADIO AND TELEVISION SERVICING BOOKS. New 74/75 £15. 76/77, 77/78, 78/79, 79/80, 80/81, 81/82, 82/83, 83/84 £22.50 each. Free delivery. U-VIEW, 29, Warmsworth Road, Doncaster. 0302 855017. Callers ring first.

## WANTED

SERVICEABLE TRINITRON TUBE. Type 520KB22 for Sony KV2000UB. Telephone Reading 0734 475869.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

WANTED: Quantity Pye Philips G11. Televisions also Ferguson videos. Telephone 04024 58513.

## MISCELLANEOUS

DON'T RELY ON the testcard. Labgear colour bar generators £55 post paid. Also GEC minitest multimeters (requires Altai leads) £6 post paid. Both working order. Beacon TV, 335a Cotmanhay Road, Ilkeston, Derbys 0602 303613.

2 LABGEAR CM6022/RA Tele-Verta. £18 each. G M LO-VEL, Orchard House, Boscastle. N. Cornwall PL35 0AT.

MANOR SUPPLIES MkV test generator tube restorer books etc. Phone Southampton (0703) 899062.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

If an  
advertisement  
is wrong  
we're here to  
put it right.

If you see an advertisement in the press, in print, on posters or in the cinema which you find unacceptable, write to us at the address below.

The Advertising  
Standards Authority. ✓

ASA Ltd. Dept 3  
Brook House, Torrington Place,  
London WC1E 7HN

## IRISH T.V. DEALERS

Large selection of fully reconditioned precision in-line UHF-VHF colour T.V.s at keen prices

Also in stock: Dual Standard Beta & VHS Video Recorders

Quantity discount. Delivery arranged.

*(Limited amount of spare panels, components, button units, etc.)*

**SPECIALISTS IN  
OVERSEAS ORDERS**

**T.V. TRADE SALES**  
EDI House, Kylemore Park West,  
Ballyfermot, Dublin 10.  
Tel: 264139 ext. 11.

*(Open 10 a.m.-5.30 p.m.)*

## COLOUR TELEVISIONS

THORN 9000, 9200, 9600 Remote Control

PYE 420/450, G11

MANY OTHER TYPES

Working panels and tubes available.

REBUILT TUBES

Delta - In Line - PIL.

SOUTHBRIDGE TV CENTRE

120, Selhurst Rd., London, S.E.25.

Tel: 01-771 3535.

EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

**IMMEDIATE CREDIT AVAILABLE — TRADE ONLY**

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN  
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

*Applies to U.K. only.*

**TELEPART (W'TON)**

32 TEMPLE STREET,  
WOLVERHAMPTON (0902) 773122

20AX Line lin coil 50p	G11 470M/250V SP £1 each	BD 517 30p
GEC switch mode trans 20AX	Min 12 volt Relays 75p	BD 519 30p
ITT CVC20 etc mains switch 60p	Y 933 5p	BD 544 30p
ITT 2,800 mains remote switch 50p	Y 969 50p	BD 595 30p
2110 GEC Power Panel £8.00	Y 977 30p	BD 610 30p
Line o/p frame panels GEC 20AX £10.00	R 1038 40p	BD 646 30p
GEC 20 AX Transductor £1.00	R 1039 40p	BD 676 30p
All diodes at 10p or less in this list 20 of one type £1.00	R 2009 80p	BD 678 30p
OA 47 8p	R 2010b £1	BD 681 30p
OA 90 8p	R 2029 50p	
IN 60 5p	R 2210 60p	
IN 541 5p	R 2257 60p	
IN 914 3p	R 2265 50p	
IN 2069a 10p	R 2305 50p	
IN 2070 10p	R 2306 50p	
IN 4001 3p	R 2322/2323 pair 80p	
IN 4002 3p	R 2323 15p	
IN 4003 4p	R 2396 50p	
IN 4004 4p	R 2461 80p	
IN 4005 4p	R 2030 50p	
IN 4006 4p	R 2443=BD124 40p	
IN 4007 5p	R 2737 40p	
IN 4148x40 £1	R 2738=TIP41 30p	
IN 4448x40 £1	R 2775=TIP41c 40p	
IN 4722 10p	R 3129=TIP47 40p	
IN 4751 10p	S 2008b 80p	
IN 5235 10p	BU 105/04 80p	
IN 5254 10p	BU 108 £1	
IN 5349 10p	BU 124 50p	
IN 5392 10p	BU 126 80p	
IN 5928B 10p	BU 180a 65p	
I.A.V. 30 10p	BU 204 70p	
IM 72Z55 10p	BU 205 £1	
IR 106a 20p	BU 206 £1	
IR 3051 10p	BU 207 £1	
IS 164 10p	BU 208 80p	
IS 921 10p	BU 208 on heat sink £1.10	
IS 3011a 10p	BU 208A 90p	
IS 3072a 10p	BU 208D 90p	
IS 5024a 10p	BU 226 £1	
IS 5030 50p	BU 326 £1	
ITT 921 10p	BU 407 60p	
ITT 923 10p	BU 426V 60p	
ITT 1075 10p	BU 500 £1.10	
ITT 2001 10p	BU 508A £1.20	
ITT 2002 10p	BU 526 75p	
ITT 4150 10p	BU 807 £1	
Rank Panels	BUX 84 50p	
Z904 Line £10	BUY 84 30p	
Z905B Decoder £10	BUY 71 £1	
Z736 Tuner I.F. £10	TIC 106a 30p	
A805 Conv. £2	TIC 116m 40p	
TL36A Scan Drive £10	TIC 116mY 1003 35p	
Z780 Line O/P £10	TIC 126N 40p	
Z968 £10	TIC 206m 30p	
AA 113 10p	TIC 225S 40p	
AA 119 8p	TIC 226E 40p	
AA 144 10p	TIC 226m 30p	
BA 102c 10p	TIC 236m 30p	
BA 157 8p	TICV 106D (TOP case 2A/400V) 10p	
BA 159 8p	TTP 29 20p	
BA 173 8p	TTP 30 35p	
BA 182 8p	TTP 30A 35p	
BA 201 8p	TTP 30B 40p	
BA 202 8p	TTP 30C 45p	
BA 243 8p	TTP 31 30p	
BA 248 8p	TTP 32 25p	
BA 316 5p	TTP 33B 70p	
BA 318 5p	TTP 33C 70p	
BAV 10 10p	TTP 34A 50p	
BAV 21 10p	TTP 34B 60p	
BAW 21 10p	TTP 34C 70p	
BB 103 10p	TTP 35B 50p	
BB 105A x 12 £1	TTP 35C 70p	
BB 105B x 12 £1	TTP 35D 80p	
BB 105G x 12 £1	TTP 36 50p	
BB 121a 10p	TTP 36C 70p	
BRB 83c13 10p	TTP 41B 40p	
BZX 46c22 15p	TTP 41D 40p	
BZX 61 9-1 6p	TTP 42/BRC 6109 30p	
BZX 61c110 6p	TTP 48 40p	
BZX 61c20 10p	TTP 49 30p	
BZX 61c30 10p	TTP 57 30p	
BZX 61c220 10p	TTP 100 30p	
BZX 70c6v2 8p	TTP 102 30p	
BZX 70c12 20p	TTP 112 30p	
BZX 70c33 8p	TTP 115 50p	
BZX 79c3v9, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 11, 12, 30, 47 10p each	TTP 117 50p	
BZX 83c4v3, 5v6, 8v2, 12, 13, 24, 27, 33 10p each	TTP 120 35p	
BZX 84c6v8 x 10 30p	TTP 125 35p	
BZX 85c8v2 10p	TTP 130 30p	
BZX 88c8v7, 3v9, 4v3, 6v2, 8v2, 12 10p each	TTP 131 25p	
1A/1600V 10p	TTP 136 30p	
2 amp bridge rec. wire end 15p	TTP 140 50p	
CV 8617 10p	TTP 147 50p	
Y 716 10p	TTP 640 50p	
Y 729 30p	TTT 2955 35p	
Y 730 10p	T 6032 30p	
Y 827: 6A/1KV 20p	T 6036 40p	
Y 860 30p	T 6040 40p	
	T 6042 40p	
	T 6049 40p	
	T 6051 40p	
	T 6052 40p	
	T 9004 40p	
	T 9005 40p	
	ZTX 102c 10p	
	ZTX 107 10p	
	ZTX 108c 10p	
	ZTX 109k 5p	
	ZTX 213 5p	
	ZTX 341 10p	
	ZTX 342 10p	
	ZTX 384 10p	
	ZTX 451 10p	
	ZTX 550 10p	
	MJ 2253 60p	
	MJE 3040 60p	
	MJE 2209 10p	
	SP 8385 50p	
	SAB 3205 £1.00	
	SAB 4209 £1.00	
	SPECIAL OFFER CVC 21 Chassis complete £35	
	Computer Transformer 20v/2.25A; 20v/1.5A; 17v.5A; 19v.5A; 28v.05A £3	

**PHILIPS DIY HOME SECURITY ALARMS KITS**  
Send for details. Prices £54 to £112.

10 Mixed TV & radio speakers £4	<b>VIEW DATA PANELS</b> NEW 19 I.C. £5	8 SEG LED Display with driver I.C. LM1017 50p
2x Hi-Fi Philips car tune up tweeter EN8320 £10	Philips GP422.4CH (£40 cost) £6	20AX GEC Split Diode lead £1.00
ITT CVC45 8 way resistor unit for v/cap £3	Stereo Dynamic Cartridge	GEC Dynamic 20AX Convergence C2233H-R223GH £2.00
4700/10v x 10 50p	12 Volt Aerial Changer over Relays 144 Mc/s 45 watts 50p	Mullard 12.5V/170 Mc/s 45 watt BLW60 £5.00
68/16 x 10 50p		BLW60C £5.00
150/16 x 10 50p		Mullard Broadband R.F. power modules VHF. BGY33 £15
4725 x 10 50p		UHF. BGY22E £5
22025 x 10 50p		PT4236C £5
1/250 x 10 50p		PT9783 £5
G8 Speaker £1	<b>GEC Hitachi</b> V/Cap tuner, after 1979 Series £8	
8000/30v 50p	6 Push Button Unit for GEC 2100 Series Replacement for Touch Button Unit £12	
470/40v x 10 £1		
22/100v x 10 £1		
100/350v 70p		
400/350v 70p		
.47/500v 25p		
1/600v 25p		
.022/1kv 10p		
<b>Various Tools and Accessories</b>		
Philips Philips Neon Lamps for TV sets £1.00		
Freeze 5p		
Foam Cleaner £1.20		
Contact Cleaner £1.20		
Push Button Mains 75p		
Lorlin Full Remote Relay Switch fit most TV sets, mains 4 tag, 2 tag 12 volt Mains timer. 13 amp — up to 2 hours: easy to use, plugs into socket £3.00		
Sellotape PVC Electric Insulation 25mm x 20M 50p	50mm x 20M 70p	
ITT CVC £8.25	Chassis £40.00	
Screen locking agent, large can £1.50		
20 GEC Service Manuals & Rank £5.00		
Red E.H.T. LAED and Anode Cap £1.00		
10 x G11 Cap 470/250 £15.00		
Soldering iron 6v/23w £2.50		
TX 10 Focus Units £6.00		
Weller solder iron 15 watt/25 watt £5.00		
2 way baby alarm/intercom with long leads £5		
Philips universal battery tester/charger, fuse/bulb tester £2		
Eisenmann NICAD CHARGER 5.5V/150 ma £2.50		
12V Nicad pack. "AA" £6.00		
Hitachi 7.2v/1.8A Nicad pack £7		
Hitachi TP 007 Battery pack 7.2v/1.6A 60p		
Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V £1		
70ML Silicone Sealer (clear) £10.00		
100 Coax Plugs £5.20		
De-solder pump + 2 nozzles 75p		
Plastic box for i.c.s with anti-static pad 6" x 3" x 1/2" 40p		
Can of handy oil "mobil" 12p		
Flat Red LED £7		
500gm 60/40 solder reel £1		
Clearweld glue pack £1		
Dual v/u meter -20 - +10db 70p		
3 x C90 Cassettes £3.00		
K30 thermistor 232266298009 £3.00		
GEC Mains Power Supply R.E.G. 1Kg reel of solder £8.00		
75R/25 Watt 25p		
18R/11 Watt 25p		
120R/17 Watt 20p		
Front End Music Center. VHF/MW/LW 13" x 3 1/2" £3		
Output Stage for music center £5		
SONY 1400KV Chroma Panel £6		
SONY 1400KV Tuner unit £3.50		
SONY 1400KV Touch button unit £3.50		
12 Volt Mains Trans 500M/A £1.00		
18v or 12 Volt Mains Trans 500M/A 75p		
Texas Viewdata Decoder VDP 12/80 Issue 3 with all IC's £10.00		
<b>Quantity Reductions</b>		
BY204/4 25 for £1.00		
BY206 25 for £1.00		
W005 bridge 20 for £2		
KT3 touch button black 6 for £1		
G11 touch button red 6 for £1		
K30 full remote Dawer Ass with 3 I.C. £7.00		
K30 VHF. UHF Dawer Ass £6.00		
BY298 3 amp/fast/R 20 for £1.50		
BD239 25 for £1.50		
BU126 10 for £6.00		
BU205 10 for £8.00		
BU105 10 for £6.00		
25C2122A 10 for £8.00		
BF458 10 for £1.00		
BD136 10 for £1.25		
BF224 20 for £1.40		
OA90 40 for £1.00		
BYX10 100 for £4.00		
KT3 multips 10 for £7.50		
50 Ceramic Condensers £1.50		
Mixed Mounting Kit for Power Transistors 50p		
300 Condensers £1.50		
300 Resistors £1.50		
150 Electrolytics £2.00		
15 Bulbs 40p		
Antistatic Discloth 5 for £1		
100 Diodes £1.50		
Plastic Boxes 50p		
100 Fuses £2.00		
100 W/W Res. £1.50		
BF 199 20 for £1		
10 x 20 Turn 100k pots. Rank £2		
Thorn 9 volt power supply regulated £3.00		
BF 470 20 for £2		
20 Slider Knobs 70p		
6 Mixed UHF Aerid Isolating Sockets, some with long leads. Fit ITT, GEC, Philips, Pye £1.00		
<b>Mixed Packs</b>		
TO66 12 Power Trans RCA 16182 NPN Replacement for BD124 and Mounting Kits £1.00		
50 Mixed AC series Transistor £4.50		
15 Panel mount rocker switch 250V/10A £1.50		
25 Panel Mount Bulbs & Neons £1.50		
10A £1.50		
Mixed ribbon cables £1.00		
25 LED red/yellow/green £1.50		
20/C Holders £1.20		
20 Large LED Red £1.00		
20 Small LED Red £1.00		
10x20 Turn 100K Pots £1.00		
100 Transistor £2.50		
20 Convergence Pots 80p		
100 Sticks £1.00		
10 Thermistors 50p		
20 Slider Pots £1.00		
30 Presets 50p		
15 VDR + thermistors, degaussing, HT, etc. £1.00		
40 glass reed switch £1		
10 press to make switch 70p		
40 Pots £1.50		
10 Gun Switches 50p		
5 Tube Bases £1.00		
1,000 Diodes, Condensers, Resistors on Bandolier £2.00		
Lucky Dip 600 gram £1.00		
Jungle Bag 5Kg £3.00		
20 Knobs £1.00		
40 Pots, 1/4" + 6mm spindles for audio/TV £3		
20mm Fuse Holders £1		
Chassis Mount 20 for £1		
1N4001/6 100 mixed £2.50		
EHT Diodes, small 20 for £1		
20 Mixed Switches £1		

**SENDZ COMPONENTS**  
TO ORDER SEE BACK PAGE

# SENDZ COMPONENTS

## TO ORDER SEE BACK PAGE

DETACH HERE MOISTEN HERE AND FOLD DOWN

<b>Thorn Spares</b>		BY 602	10p
9000 Frame panel	£8	F 247	10p
9000 Cyclops panel	£1.50	XX 3102	50p
8000/8500 timebase panel	£8	XX 3123	50p
8800 convergence panel	£6	Hitachi 2A/1500V metal case wire	20p
8500 convergence panel	£6		
4000 Chroma	£20		
4000 Power supply	£3		
1600 Mains lead, switch			
3500 6 push button + cable form	£1.50		
T605 1vNPN T066 80v/6A	10p		
9000 Sound output panel	£1		
3500 Focus unit	£1.50		
3500 Mains Trans	£4		
3500 2amp thermal cutout	75p		
3500 IF panel	£2		
3500 Frame panel	£2		
3500 Line panel	£3		
3500 A1 Diode	20p		
Export 3500 IF panel	£2		
IC board with set of SN74LS	£1		
4000 Tube base	£4		
3500 A1 pots	50p		
Beam limiter panel	£1.50		
3500 Power panel with Y969	£1		
3 Way regulated adaptor 240V	£3.50		
6V/7.5V/9V/300mA			
Rank/Toshiba preh unit			
0354	£9.50		
2 banks of 3 PB unit, Pye 731	£2		
4 Push button unit preh	£1.00		
5 Push button VHF/UHF for vcap, GEC-Deca type	£7.00		
7 Push button for CVC5 IIT	£8.00		
KT3 12 Push button unit	£2.00		
KT3 (Export) 12 P.B.U.	£2		
5 Push button Unit Thorn	£1.00		
6 Push button Unit fits GEC & Decca etc.	£6.00		
6 Push button unit for GEC 2040 and ELC 1043/05	£6.00		
Hearing aid unit	£3		
6 Push button unit PYE 713	£7.00		
7 Button Unit GEC with Lamps	£7		
<b>Mains Droppers</b>			
G8 2R2 + 68R	£1.25		
G8 47R 15 watt	75p		
Pye 731 3+56+27R	50p		
Pye 3R5/15R/45R	50p		
Thorn 50/17/1K5	£1.00		
120/20/20/48/117	£1.00		
270/10/6 for Thorn 4000	50p		
18/320/70/39	£1.10		
Thorn 50-40R-1K5	50p		
Ae Socket & Lead			
GEC, IIT, Philips, Pye	25p		
7x3 Thorn	£1		
Rank Toshiba Tube Bases	30p		
<b>Speakers</b>			
5x4 G11	25 ohm	70p	
5x4 24	3 ohm	£1.00	
8x3	80 ohm	70p	
8x3	50 ohm	50p	
8x3	35 ohm	70p	
8x4	15 ohm	£1.00	
7x3	70 ohm	£1.00	
8x3	8 ohm	70p	
7x3	16 ohm	£1.00	
5" dia	8 ohm	£1.50	
4" dia	4 ohm	£1.50	
4" dia	3 ohm	£1.50	
4" dia	8 ohm	75p	
4" dia	8 ohm	75p	
4" sq.	15 ohm	75p	
KT3 speaker	K30	75p	
3" dia	15 ohm	60p	
<b>K30</b>			
OF-550	E.W.	10p	
OF-513	correction	10p	
<b>Diodes</b>			
BY 127		10p	
BY 133		10p	
BY 134		10p	
BY 164		50p	
BY 176		25p	
BY 179		40p	
BY 184		25p	
BY 187		10p	
BY 190		40p	
BY 196		30p	
BY 198		10p	
BY 204/4		8p	
BY 206		8p	
BY 208/800		8p	
BY 210/400		5p	
BY 210/800		10p	
BY 223		60p	
BY 224/600: 4.8A/600v bridge	50p		
BY 226		15p	
BY 227		15p	
BY 228		20p	
BY 229/400		30p	
BY 237		5p	
BY 254		10p	
BY 255		30p	
BY 298		10p	
BY 299		10p	
BY 406		8p	
BY 527		20p	
BY 407a		10p	
International Rectifier EHT Diodes	G770/HV34 6KV	3 for 8p	
6A/600V Stud Diodes	BTW 92/800R	£3	
6A/1000V Stud Diodes	25A473 PNP C/P	10p	

NEW PYE 725 line O/P panel with L.O.P.T. & Tripler	£10.00	210/12KV	10p
Thorn Mains Isolator unit for 70-80I. Ex-speaker	£2	1000/12KV	10p
NEW GEC 20AX Power Supply Switch Mode	£12.00	1200/12KV	10p
Complete new GEC portable chassis M120H/M150IH with P.B.U., v.cap/LOPTI			
Field + Jungle panel for GEC 3133/3135	£1.50		
GEC 2110 line panel with transformer	£7.00		
GEC 2110 tuner unit + IF Panel	£12.00		
Pye/Chelsea Line op panel	£12.00		
Pye 713 IF panel and tuner	£7.00		
Pye 713 Chroma	£10.00		
Pye/Chelsea Timebase panel with LOPTI	£10.00		
Pye 731 Frame Panel	£5.00		
Pye 731 Convergence Panel	£5.00		
Pye 731 line O/P panel with transformer + tripler	£12.00		
Pye 731 Chroma	£10.00		
Pye 731 IF panel + tuner	£10.00		
Pye 607/205 Line panel with transformer	£10.00		
Pye CDA/205 panel	£6.00		
GEC portable chassis + LOPTI 2114 New	£4.00		
Thorn 1613/1713 chassis	9.75		
Hills 520 multimeter + case. 20,000Ω/volt, fuse diode protected + logic test facility. 10meg/1200 volt	£19.50		
<b>NEW MULLARD TELETEXT</b>			
250/64	10p		
Decoder Panel (VM6230)	£15.00		
Panel 6101	£15.00		
Panel 6330	£15.00		
G8 Tuner Unit + Panel	£6.00		
G8 Convergence Panel (late type)	£12.00		
G8 Power Supply	£6.00		
G8 6 Sloping PBU	£8.00		
G8 IF & Chroma	£12.00		
G8 Chroma	£6.00		
G11 IF Detector	£3.00		
G11 Selector gain module	£3		
Complete CVC 825 Chassis (both panels)	£40.00		
AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670	£3.00		
Z714 RANK IF Panels 6MHz 1 I.C. SL437F	£3.00		
Z909B RANK IF Panels			
Export 5.5MHz 2 I.C.'s TBA1205B TCA2705Q	£2.50		
Z743 RANK IF Panel			
Export 5.5MHz 3 I.C.'s TBA750+SC9504P+SC9503P	£1.50		
Pye G11 Front panel transducer, pots, tuner pots, 6 pb switch + lead	£5.00		
GEC V/cap VHF/UHF tuner and IF + sound O/P PC 706B3 (Export)	£12.00		
GEC Line O/P PC 659B3	£6.00		
2110 GEC Power Panel	£8.00		
GEC Power Supply (Export)	£10.00		
G11 dynamic correction panel	£6		
CVC 32 Front panel with sliders + mains input panel	£4		
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots	£14		
CVC 5 Mains on/off + 5 pots	£2		
Universal Focus. Fits Pye, Thorn and Decca Units.			
Large Type	75p		
Decca Small	75p		
KT3 Focus Unit	75p		
K30 Focus Pot	75p		
TX10 Focus Units	£6.00		
CVC 32 Focus Unit			
Focus Rod	25p		
G11 focus	£2.00		
IIT Small for use with Split Diode	50p		
TV11	50p		
Remo TV12SP	50p		
TV13	50p		
TV14	50p		
TV18	60p		
TV20	£1.00		
IV45	50p		
Thorn 14/1500 rec stick	5p		
16 Button Key Pad 1 to 0 + * + #			
4 blank (Cherry)	£3.00		
<b>G7000 Philips Video Games Packs</b>			
11 types	£8.75 each		
G11 drawer ASS 3 pots Mains switch and lead	£2.00		
Line O/P panel GEC 2217/2218/2213/2214/2226/2227/2228	£10		
3500 thick film	£2.00		
4000 thick film	£2.00		
PYE 731 thick film	£2.00		
<b>DISPLAYS</b>			
4040 Clock	£1.00		
7seg Red LED	50p		
2 digit LED 8.8	50p		
2 digit LED ÷1.8 with panel + MCI4511	£1.00		
4700/63	£1.50		
Infra Red and Ultrasonic G11 Teletext Decoder Panel	£30		
RANK & IIT Mains Remote On-Off Switch (720R)	£1.50		
RANK & IIT Mains Remote Switch 2865 ohm	£1.50		
RANK & IIT Remote Switch 2800 ohm	£1.50		
G11 Mains Switch	50p		
4 amp Mains Switch	25p		
GEC Mains Switch 4 amp	30p		
KT3 Mainswitch	£1.00		
THORN Rotary Mains Switch	50p		
G8 Mains Switch	75p		
Thyristor 600/4 amp C106/2	24p		
G11 Preh Red LED P/Buffer for C.H. Change	20p		
RANK TOSHIBA Transducers TPC-2011	50p		
CVC 5 Mains on/off	£2.00		
+250K + 100K + 500K + 50K + 500K Pot on Panel	£2.00		
Thorn 12 or 24 volt battery convertor for portable colour T/V	£12.00		
Tape Heads R/Play/Back Mono/Stereo	£1.00		
Post £1			

<b>Multi-Caps</b>		10 for £15
470/250 G11		
Thorn 3500		
175/100/100/350v	£1.75	
KT3/200/25/25/385v	£1.00	
300+300+150+100+50MFD		
350V	£2	
47/220/350v	60p	
150/150/100/100/320v	£2.00	
2500/2500/63v	50p	
470/470/250v	50p	
150/200/200/300v	70p	
400/400/200v	£1.70	
300/100/100/16/275v	£1.50	
100/200/325v	40p	
150/150/100/375v	£1.50	
300/300/100/32/32/300v	2.00	
1500/2000/30v	50p	
Jelly pot Thorn 00D4/013	£3	
150/150/100/100/320v	£2.00	
100/350 + 300/200/100/16/275v	£2.00	
300+300/300	£1.00	
225+25/380	70p	
200/100/100/350v	£1.50	
500/500/25v	50p	
150/150/100/300v	75p	
200/150/150/300v	1.00	
<b>IIT Panels</b>		
CVC 40/2 Chassis, new £30, complete with intrfase panel		
CVC 820 Line O/P Panel		
CVC20 Mains Panel	£3.00	
IIT 8 & 6 Push Button Unit	£1.00	
CMA 10	£2.00	
CMA 11	£2.00	
CMA 30	£2.00	
CMA 40	£1.50	
CMA 10/2	£5.00	
CMA 38	£8.00	
CMA 45	£1.50	
CMA 47	£1.00	
CMA 52	£1.50	
CMA 57	£6.00	
CMA 58	£8.00	
CMA 59	£8.00	
CMA 67	£3.75	
CMA 67/2	£4.00	
CMA 68	£4.00	
CMA 12	£10	
CMA 32	£5.00	
CMA 33	£5.00	
CMA 40	£5.00	
CMA 41	£5.00	
CMA 42	£2.00	
CMA 43	£2.00	
CMA 44	£2.00	
CMA 45	£2.00	
CMA 46	£2.00	
CMA 47	£2.00	
CMA 48	£2.00	
CMA 49	£2.00	
CMA 50	£2.00	
CMA 51	£2.00	
CMA 52	£2.00	
CMA 53	£2.00	
CMA 54	£2.00	
CMA 55	£2.00	
CMA 56	£2.00	
CMA 57	£2.00	
CMA 58	£2.00	
CMA 59	£2.00	
CMA 60	£2.00	
CMA 61	£2.00	
CMA 62	£2.00	
CMA 63	£2.00	
CMA 64	£2.00	
CMA 65	£2.00	
CMA 66	£2.00	
CMA 67	£2.00	
CMA 68	£2.00	
CMA 69	£2.00	
CMA 70	£2.00	
CMA 71	£2.00	
CMA 72	£2.00	
CMA 73	£2.00	
CMA 74	£2.00	
CMA 75	£2.00	
CMA 76	£2.00	
CMA 77	£2.00	
CMA 78	£2.00	
CMA 79	£2.00	
CMA 80	£2.00	
CMA 81	£2.00	
CMA 82	£2.00	
CMA 83	£2.00	
C		

# SENDZ COMPONENTS

63 Bishopsteignton,  
Shoeburyness, ESSEX SS3 8AF  
SAME DAY SERVICE

All items subject to availability.  
No Accounts - No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then £1 Postage  
Add Postage for overseas  
Callers: To shop at 212 London Rd.,  
Southend. Tel. 0702-332992

Open 9-1/2.30-6. G.V.M.T + school orders accepted on official  
headings add 10% handling charge.

THORN 1400 4P.B. Mech. Tuner	20p
IHORN 1500 4P.B. Mech. Tuner	40p
THORN 1590 4P.B. Mech. Tuner	40p
IHORN 3500 4P.B. Mech. Tuner	75p
EHORN 8000 4P.B. Mech. Tuner	£1.00
THORN 8500 Mech. Tuner	£1.00
All new & boxed.	£4.00 each

Delay Lines		
DL20A 80p	DL600	£1.00
G8 (Old Type)		£1
DL600		£1.00
DL700		£1.00
DL710		£1.00
UDL11		30p
K F3 Luminescence		75p
Luminescence Delay Line (CVC 45)		
10x630ma fuse		25p
10x2A fuse		50p
10x3.15 fuse		50p
10x500mA		80p
10x1 amp		80p
10x1.6 amp		80p
20 3 15 AS Fuses		£1.70
Co-Ax Joint		DM742
Co-Ax Belling Lee Plug		12p
Co-Ax Splitter		£1.00
UHF Modulator CCIR		£3.00
Intra Red Emitting Diode		20p
NE286H Small Neon Lamps GEC & Philips		5p
Mullard 5 Watt Amps. LP1162		75p

I.V. Tubes		
12" A31/300 Hitachi		£10
15" A38/170W Hitachi		£8
18" Hitachi PH tube with scan coils 470 KCB22-FC03		£25

Integrated Circuits		
AC76003		£1.50
AM25LS23PC		10p
BAV40		40p

BC414	10p	BC414	10p
BC416	10p	BC416	10p
BC440	30p	BC440	30p
BC454	10p	BC454	10p
BC455	10p	BC455	10p
BC456	10p	BC456	10p
BC460	25p	BC460	25p
BC462	10p	BC462	10p
BC463	10p	BC463	10p
BC478	10p	BC478	10p
BC527	10p	BC527	10p
BC532	10p	BC532	10p
BC546	10p	BC546	10p
BC547	10p	BC547	10p
BC548	10p	BC548	10p
BC556	10p	BC556	10p
BC557	10p	BC557	10p
BC558	10p	BC558	10p
BC559	10p	BC559	10p
BC635	10p	BC635	10p
BCX31	25p	BCX31	25p
BCX32/36 Pair	75p	BCX32/36 Pair	75p
BCX32	25p	BCX32	25p
BD116	25p	BD116	25p
BD124	50p	BD124	50p
BD124 (metal)	60p	BD124 (metal)	60p
BD130	25p	BD130	25p
BD131	30p	BD131	30p
BD132/238	30p	BD132/238	30p
BD135	25p	BD135	25p
BD136	25p	BD136	25p
BD138	30p	BD138	30p
BD176	25p	BD176	25p
BD182	£1.00	BD182	£1.00
BD183	70p	BD183	70p
BD202	60p	BD202	60p
BD204	60p	BD204	60p
BD221	20p	BD221	20p
BD222	30p	BD222	30p
BD228	30p	BD228	30p
BD226	20p	BD226	20p
BD233	30p	BD233	30p
BD235	30p	BD235	30p
BD239	15p	BD239	15p
BD243c	30p	BD243c	30p
BD244	50p	BD244	50p
BD250a	30p	BD250a	30p
BD252	20p	BD252	20p
BD253B	50p	BD253B	50p
BD331	20p	BD331	20p
BD332	20p	BD332	20p
BD373b	20p	BD373b	20p
BD416	25p	BD416	25p
BD433	25p	BD433	25p
BD437	25p	BD437	25p
BD439	50p	BD439	50p
BD501	30p	BD501	30p
BF761	30p	BF761	30p
BF858	30p	BF858	30p
BF871	30p	BF871	30p
BF879	15p	BF879	15p
BF882	7p	BF882	7p
BF889	15p	BF889	15p
BF881	15p	BF881	15p
BF887	10p	BF887	10p
BF890	10p	BF890	10p
BF894	10p	BF894	10p
BF897	10p	BF897	10p
BF898	10p	BF898	10p
BF899	10p	BF899	10p
BF1000	10p	BF1000	10p

SAA5000A	£1.50	SN76110N	£1	MJE2801	30p
SAA5012A	£5.00	SN76115AN	50p	MJE2955	50p
SAA5020	£3.50	SN76131	50p	MJE13005	30p
SAA5030	£5.00	SN76141N	£1.00	Sanikron Diode	
SAA5040	£3.50	SN76226	£1.00	SKE2G2/04	30p
SAA5040A	£4.40	SN76227N	60p	Transistors	
SAA5050	£3.50	SN76228N	£1.00	A1222	15p
SAF1032p	£2.50	SN76270	£1.00	A1223	15p
SAF1039	£2.00	SN76532N	50p	AC106	15p
SAS560	£2.00	SN76544N	£2.00	AC121	15p
SAS560	£1.00	SN76545	£3.50	AC124	15p
SAS670	£1.00	SN76550	£1.00	AC128	15p
SL901B	£5.00	SN76552	30p	AC137	15p
SL918	£6.20	SN76570	£1.00	AC151	15p
TA7122	£1.15	SN76620	50p	AC138	15p
TAA320A	50p	SN76650	50p	AC144	15p
TAA470	£1.50	SN76660N	40p	AC152	15p
TAA570	75p	SN76620AN	50p	AC153K	15p
TA611B	£1.50	SN76666	£1.00	AC142K	15p
TA621	£2.00	SN76705N	£1	AC169	15p
TA661	£1.75	SN76707N	75p	AC176	15p
TA6611	£1.50	SN76708AN	75p	AC176K	15p
TA7117	50p	SN76720	£1.00	AC178K	15p
TA7120P	50p	UA783P3C	40p	AC179	15p
TA7315AP	50p	BT100A/02	40p	AC186	15p
TA7607AP	40p	BT138/10A	70p	AC187K	15p
TA7609P	50p	BT146	30p	AC188	15p
TBA120A	40p	TBA540Q	£1.50	AC188K	15p
TBA120AS	50p	TCA270	£1.00	ACY21	25p
TBA120SA	40p	TCA270Q	£1.00	AD143	50p
TBA120SB	40p	TCA640	£1.00	AD149	50p
TBA120SQ	£1.00	TCA660	£1.00	AD161/162	pair 40p
TBA120S	40p	TCA270S	£1.00	AF139	25p
TBA120Q	£1.00	TCA270SQ	£1.00	AF181	£1.00
TBA120C	40p	TCA740	£1.00	AF239	25p
TBA120A	40p	TCA800	£2.00	AF367	25p
TBA1441	£1.00	TCA830	£1.00	AL102	£1.75
TBA231	75p	TCEP100	£2.25	BC161	30p
TBA395Q	50p	TCE120CQ	£1.00	BD507	30p
TBA396Q	£1.00	TDA440Q	£1.00	BD509	30p
TBA396	75p				