


**JULY 1987**

Australia \$2.20, New Zealand \$2.95 (inc. GST), Malaysia \$5.95

**£1.30**

# TELEVISION

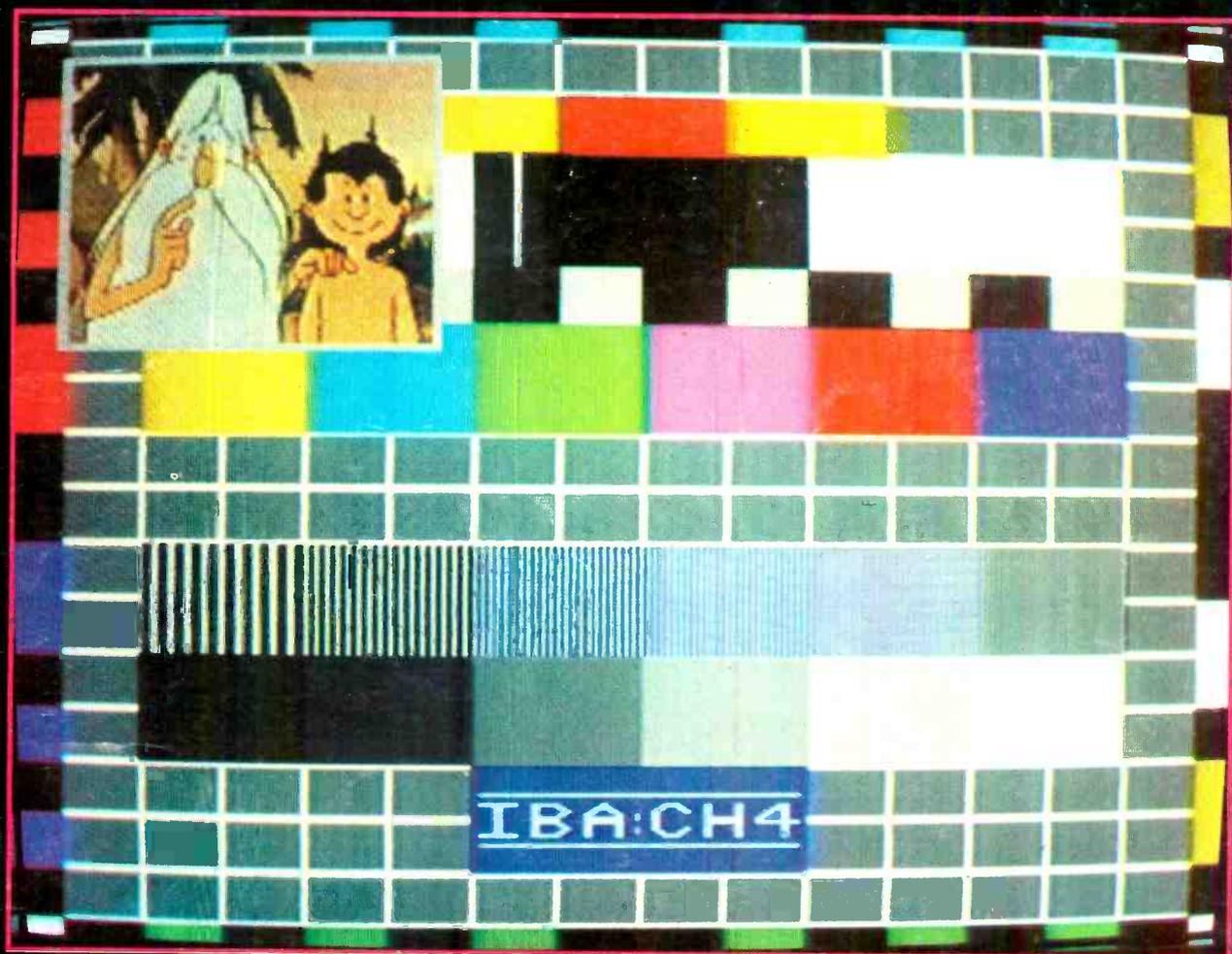**SERVICING·PROJECTS·VIDEO·DEVELOPMENTS**



**The S-VHS Specification  
TX9 Thyristor PSU Servicing  
Series and Shunt Networks  
Video-8 Audio Techniques  
A Vintage TV Restoration  
VCR Clinic • The Glue Gun  
TV Fault Finding • DX-TV**

# MANOR SUPPLIES

MKV PAL COLOUR  
TEST GENERATOR FOR TV & VCR.

TEST  
DEMONSTRATIONS  
AT 172  
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**  
Case (10"×6"×2¼") app. **£8.60**  
Optional Sound Module (6MHz or 5.5MHz) **£3.90**  
Built & Tested in Case including Sound Module **£108.00**

SPECIAL TEST  
REPORT  
'TELEVISION'  
DEC. 1982

Post/Packing £2.80  
Add VAT 15% TO ALL PRICES

## PAL COLOUR BAR GENERATOR (Mk4)

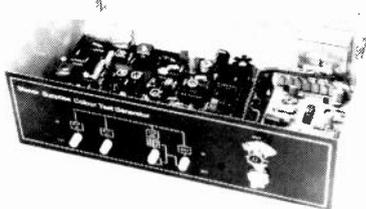

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT  
**£30.00. CASE £8.60. BATT HOLDERS £4.20. MAINS  
SUPPLY KIT £4.20 (Combined P&P £2.80).**

MK 4 (BATTERY) BUILT & TESTED **£58.00 + £2.80 P & P.**  
MK 4 (MAINS) BUILT & TESTED **£68.00 + £2.80 P & P.**  
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75.**  
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD  
VAT  
15%

### TELETEXT DECODER PANELS (TESTED)

Mullard VM6101 **£30.00**, Philips KT3, K30 **£30.00**, Texas XMII (TIFAX) **£28.00** (untested **£5.00**) p.p. **£1.80**

THORN TX9 MK2/3, TX10, teletext  
Mullard Decoder panel + Interface **£35.00** p.p. **£1.80**  
THORN TX10, PHILIPS G11 PRESTEL, TELETEXT  
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£38.00**  
p.p. **£2.50**

## TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF  
TECHNICAL EXPERTS

LOPTS, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

SPECIAL OFFER Mullard/Philips quality UHF modulator (audio & video input) ex new equipment **£5.00** p.p. **£1.00**.  
PHILIPS G11 6 position touch tune channel selector units **£16.00** p.p. **£1.80** (can replace earlier mechanical selector unit).  
PHILIPS G11 PANELS (tested).  
Frame, IF, decoder **£18.00** each p.p. **£2.00**, Scan **£28.00** p.p. **£2.80**.  
PHILIPS G11 PANELS ex rental (untested).  
Scan **£10.00**, Frame, Decoder **£5.00** p.p. **£2.00**.  
PHILIPS HANDSETS (New Replacements) p.p. **£1.50**.  
G11 Ultrasonic Nontext **£22.50**, Infra red Text **£22.50**.  
KT3 Non text (RC4001) **£20.00**, KT3, K30 etc. Text **£26.50**.  
PHILIPS HANDSETS Ex rental, text, Untested, KT3, K30, **£3.50** p.p. **£1.00**.  
COLOUR MANUALS p.p. **50p**.  
PHILIPS G11 **£3.50**, KT3 **£3.50**, CTX-E **£1.50**, CTX-S **£1.50**.  
THORN REMOTE CONTROL HANDSETS  
TX9 ULTRASONIC (3-button) **£15.00**; TX9, TX10 Infra red (type 725) **£18.00**; TX9, TX10 Infra red Teletext **£20.00**, p.p. **£1.20**.  
TX9 Ultrasonic remote handset transducer **£2.00**, switches 3 for **£1.50** p.p. **50p**.  
TX9/TX10 Teletext interface panel **£5.00** p.p. **80p**.

THORN TX9 Ultrasonic Remote/Control Receiver panels, **£8.50** p.p. **£1.50**.  
TX9, TX10 Facia control panel incl. infra-red remote receiver **£8.50** p.p. **£1.80**.  
THORN TX9, TX10 Saw Filter IF Panel, **£5.00** p.p. **80p**.  
TX9, TX10 Remote & tuning control panel (1515) **£10.50** p.p. **£1.80**.  
SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision, **£28.50** p.p. **£1.20**.  
PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. **£1.00**.  
PAL ENCODER KIT (RGB to Video) **£18.50** p.p. **£1.30**.  
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00** p.p. **80p**, (Alum. Case **£2.90** p.p. **£1.40**.) ADDITIONAL GREY SCALE Kit **£2.90** p.p. **45p**.  
UHF SIGNAL STRENGTH METER KIT **£22.00** Alum. Case **£2.90**, De Luxe Case **£8.60** (Built & Tested **£48.00**) p.p. **£2.30**.  
CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with Case, Panel Meter Indicator - can be adapted for latest CRTs **£29.50** p.p. **£2.80**.  
BUSH A823 Convergence, Time Base Panels **£5.00** each p.p. **£1.80**.  
GEC 20AX Line Time Base **£18.00** p.p. **£2.00**.  
ITT CVC30 SERIES: Convergence & Purity Control Panels, **£5.00** p.p. **£1.50**.  
ITT CVC30 SERIES PANELS SURPLUS (untested) **£5.00** each, CMP31, CM131, CMA30, CM532, p.p. **80p**; CMD33, p.p. **£1.80**.  
THORN TX9 Panels ex factory for small spares. Includes ICs & Semiconductors etc. **£3.00** p.p. **£1.80**.  
THORN TX9 Panels salvaged ex factory for spares incl. Electrolytic & Mains Transformers **£8.50** p.p. **£3.00**.  
THORN 8000, 8500, 8800 IF Decoder Panels Tested **£10.00** p.p. **£2.30**.  
THORN 8000/8500 IF/Decoder Panels salvaged **£3.20** p.p. **£1.80**.  
THORN 9000 IF Decoder Panel **£6.00** p.p. **£2.30**.  
THORN 9000 IF Decoder Panels Salvaged, For spares **£2.50** p.p. **£1.80**.  
PHILIPS G8/G9 IF Decoder Panels for small spares incl. ICs **£2.50** p.p. **£1.60**.  
PHILIPS G8 Line Driver Panel incl. Equalizing Coil, **£1.00** p.p. **60p**.  
GRUNDIG 8630 Series Varicap Tuners **£5.00** p.p. **£1.00**.  
VARICAP TUNERS U321, U322/204, ELC1043/05 **£7.80** p.p. **£1.00**.  
VHF Philips, NS - **£6.80** p.p. **£1.00**.  
BUSH "TOUCH TUNE" T2022 Series Fascia Unit **£7.50** p.p. **£1.50**.  
VARICAP UHF-VHF ELC 2000S **£9.80** p.p. **£1.00**.  
UHF/625 TUNERS, many different types in stock, DECCA Bradford 5 position, MULLARD 4 position **£2.50**, JAP Rotary **£4.80** p.p. **£1.80**.  
TV SOUND IF Panels **£6.80** p.p. **£1.00**.  
LOPTS New and guar. P/P **£1.50**, Bobbins **80p**.

FERG., HAY, MARCONI, ULTRA			
1590, 1591, 1612, 1613, 1712	£4.80	R.B.M. 120, 122	£9.80
FERGUSON 3787 (Normide)	£9.80	R.B.M. 120, 122 Bobbin	£5.60
THORN 1600, 1615, 1690, 1691, 1790	£9.00	DECCA Bradford (estate Mod No)	£8.80
THORN 3000, 3500SC, AN 1111	£6.90	DECCA 80, 100	£8.80
THORN 8000, 8500, 8800	£12.80	FIDELITY ZX2000, 3000	£14.00
THORN 9000 to 9600	£9.80	GEC 2110 series	£10.60
THORN TX9	£12.50	ITT CVC 5 to 9, CVC20	£9.80
THORN TX10	£16.50	ITT CVC 25, CVC30 series	£8.80
		ITT CVC 45	£9.80
		PYE 725 (90) 731 to 741	£9.20
DECCA 1700, 2001, 2020, 2101, 2120	£3.80	PHILIPS G8	£8.80
ITT VC 300	£4.80	PHILIPS G9	£10.80
GEC 2110 Junior Endline	£2.80	PHILIPS G11	£18.80
PHILIPS 820	£2.80	PHILIPS K13	£9.80
RBM AS23	£4.80	PHILIPS K30, K35	£18.50
GEC 2028, 2040, 2100	£4.80	PHILIPS CTX-E	£21.00
PYE 691-7 chassis type only	£5.00	PHILIPS CTX-S	£21.00
PHILIPS 89	£6.80		

OTHERS AVAILABLE. PRICES ON REQUEST.

TRIPLERS Full range available Mono & Colour  
SPECIAL OFFER TRIPLERS  
THORN 3000 3500 **£2.50**, PYE 725 731 (4 lead) **£1.50** p.p. **£1.20**  
THORN 1500 5 Stick **£1.50**, 1500 3 Stick **£1.50** p.p. **80p**.  
6-3V CRT Boost Transformers for Colour & Mono **£5.90** p.p. **£1.40**.  
THORN TX10 focus control **£7.50** p.p. **£1.00**.  
CALLERS WELCOME AT SHOP PREMISES  
THOUSANDS OF ADDITIONAL ITEMS. ENQUIRIES INVITED  
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS


Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order) ADD VAT 15%.

Telephone 01-794 8751, 794 7346

**MANOR SUPPLIES**  
172 WEST END LANE, LONDON, NW6 1SD

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)  
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)  
Access from all over Greater London.

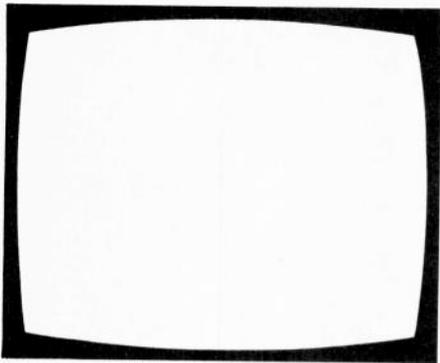Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT  
PLEASE ADD VAT 15% TO ALL PRICES INCL. P+P



# TELEVISION

July  
1987

Vol. 37, No. 9  
Issue 441

On sale June 17th

## COPYRIGHT

© IPC Magazines Limited, 1987. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

## SUBSCRIPTIONS

An annual subscription costs £16 in the UK, £19 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

## BACK NUMBERS

Some back issues published during the last six months are available from the Editorial Office at £1.40 inclusive of postage and packing. Address requests to *Television*, Editorial Office, IPC Magazines Ltd., King's Reach Tower, Stamford Street, London, SE1 9LS.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. Correspondents should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 597 Leader**
- 598 TX9 Thyristor PSU Servicing** *Gordon Haigh*  
One of the problems with the earlier versions of the Ferguson TX9 chassis is the tendency for the mains fuse to blow for various obscure reasons. How to deal with this and other common problems.
- 600 Letters**
- 604 The Super-VHS Specification** *Steve Beeching, T. Eng.*  
Improvements in video tape recording technology have made it possible to upgrade the VHS system to give greatly enhanced performance. Details of the new specification.
- 605 Next Month in Television**
- 606 Now Read This** *Les Lawry-Johns*  
Details of some new fuses that could fool you and accounts of some of the odd things that come into the shop, including a certain radio set . . .
- 607 Product Report: Glue Guns** *Harold B. Berkley*  
The glue gun can be a very helpful addition to the tool kit, enabling various repairs you might otherwise be unable to handle in the field to be dealt with.
- 608 The 8mm Video System, Part 4** *Eugene Trundle*  
This time the audio side of the Videc-8 system, covering the f.m. and PCM audio techniques.
- 614 Teletopics**  
News, comment and developments.
- 616 TV Fault Finding**  
Reports from J.K. Potts, Guy W.E. Mundy, T. Eng., Hugh MacMullen, Mick Dutton, Steve Leatherbarrow, Lawrence Ingram and G.C. De Fraine.
- 618 Getting Started with Satellite TV** *John Hopkins*  
A light-hearted account of some of the problems you face when first getting a satellite TV receiver system going.
- 619 Test Pattern Program for the Vic 20** *Bill Brown*  
A simple program to enable the Vic 20 computer to be used as a test pattern generator.
- 622 Series and Shunt Networks** *S.W. Amos, B.Sc., C. Eng., M.I.E.E.*  
The characteristics of series and shunt networks, their relationships and how they can be used.
- 625 Micro Clinic**  
Reports from Roger Burchett and Nick Beer.
- 626 A Vintage TV Restoration** *Steve Rowley*  
How a fifty-year old Ekco TA201 vision adaptor was restored to working order.
- 628 VCR Clinic**  
Reports from Steve Beeching, T. Eng., Eugene Trundle, Philip Blundell, Eng. Tech. and Patrick Rafferty.
- 630 Long-distance Television** *Roger Bunney*  
Reports on DX conditions and reception and news from abroad. Details of a compact v.h.f. aerial of Russian design.
- 633 Service Bureau**
- 634 Test Case 295**

OUR NEXT ISSUE DATED AUGUST WILL  
BE PUBLISHED ON JULY 15

# P. V. TUBES

104 ABBEY STREET, ACCRINGTON, LANCS  
 Tel: 0254 36521/32611/390936 BB5 1EE.  
 Telex: 635562 Griffin G (For P.V.)

TRADE  
 COUNTER  
 OPEN  
 MON-SAT  
 9am-5pm  
 (not Wed pm)



**HOW TO ORDER**  
 ADD 87p per order P+P (U.K.).  
 Heavier parcels e.g. cable, service  
 aids, degassing coils please allow  
 £1.50 P+P (U.K.). Export orders  
 charged at cost. First Class Mail is  
 used whenever possible. Add 15%  
 VAT to total except where it states  
 zero rate. Bulkier items will be  
 sent by carrier £7.00 + VAT up to  
 25K (except tubes).

**THERE IS VAT ON P+P.**

BOOKS AND MANUALS ARE ZERO V.A.T.  
 Goods are despatched on the day we receive your order.  
 If for any reason we are out of stock we will try to inform  
 you as quickly as possible. We try our best to give a  
 speedy, fair and efficient service. V.A.T. invoice on  
 request. Give us a ring - we'll give you service. Please  
 ask if what you need is not listed - we will try to help.  
 Prices are subject to change without notice. In some  
 cases we may have to supply an equivalent.

## INTEGRATED CIRCUITS

AN214Q	3.91	SL1430	1.58
AN240	3.84	SL1432	3.36
AN318	6.37	SL76544	2.05
AN262	4.10	SL490	1.89
AN301	5.15	SN76709	8.00
AN715Q	3.97	SN76115N	2.27
AN6341N	8.97	SN76131N	2.00
AN6344	7.85	SN76226DN	1.78
AN6360	6.81	SN76227N	2.12
BA521	2.80	SN76533N	1.70
BA536	3.00	SN76033N	2.49
CA555	46	SN76544N	2.35
CA556	84	SN76660N	80
CA741	25	SN76666N	1.52
CA748	45	SN76530A	1.47
CA1532	4.20	STK015	7.36
CA3065	1.80	STK433	5.65
DC1411WF	30	STK435	9.06
CV12E	3.07	STK436	6.50
GH3F	1.82	STK437	7.85
HA1151	3.89	STK439	8.40
HA1342	3.58	STK459	9.50
HA1306N	2.60	STK441	11.57
HA1366WR	2.80	STK461=465	12.50
HA1377	3.20	STK463	14.30
HA11219	4.21	STK2129	17.27
HA11244	4.04	STR441	6.50
HA1741	23.22	STR454	4.73
IS1555	43	STR451	6.50
LA3350	1.59	STR6020	8.50
LA4031P	3.21	SW153	3.90
LA4032P	3.15	TA7050P	95
LA4012	3.37	TA7051P	95
LA4112	3.25	TA7063P	2.20
LA4422	3.28	TA7074P	3.46
LA7801	2.20	TA7108P	3.43
LC7130	5.93	TA7120P	2.43
LC7120	5.87	TA7129AP	3.76
LC7137	5.50	TA7130P	1.93
LM1011	3.25	TA7146P	4.63
LM1340T	75	TA7193P	5.67
LM8361=		TA7171P	8.90
MM5387ANN	4.15	TA7172P	8.90
M293	7.10	TA7173P	8.90
M30790SP	6.90	TA7176P	2.50
M54544L	3.80	TA7202P	4.27
MC13002	4.98	TA7204P	3.72
MC14493	8.97	TA7205AP	3.72
MN1219	11.43	TA7208P	3.40
MB3712	2.60	TA7210P	6.60
MC1307	1.99	TA7222	2.42
MC1310P	1.84	TA7223P	3.74
MC1327	1.70	TA7227P	5.98
MC1330P	1.84	TA7228P	5.98
MC1351P	2.93	TA7310P	2.78
MC1349	1.99	TA7609P	4.39
MC1350	1.99	TA7611AP	2.92
MC1352	1.75	TAA570	3.98
MC1495L	3.00	TAA310	2.83
ML231	2.20	TAA320	2.00
ETTR6016	2.20	TAA550	55
ML232	2.20	TAA630	3.90
ML237	2.50	TBA120SA	1.49
ML238	6.00	TBA120B	1.30
ML239	2.90	TBA120SB	1.37
ML922	3.29	TBA120T	1.47
ML923	2.90	TBA120U	1.49
ML928	2.18	TBA1440G	2.20
NSM5807	7.87	TBA395	1.75
MS1513L	2.80	TBA396	1.75
MS1515L	3.28	TBA440N	
SA11025	8.50	(TBA1441)	2.75
SA11124	5.34	TBA440P	
SA11250	4.99	(TBA1440G)	2.50
SA45000	6.15	TBA480Q	1.82
SA45010	6.30	TBA510	3.00
SA45012	6.50	TBA520(Q)	1.68
SA45020	5.90	TBA530(Q)	1.38
SA45030	8.25	TBA540	1.76
SA45050	8.50	TBA560(Q)	1.93
SAF1032	6.30	TBA570	1.59
SAF1039	7.77	TBA690	1.70
SAS560S	2.07	TBA700	2.12
SAS570S	2.07	TBA720	2.64
SAS660	3.25	TBA750	2.98
SAS670	3.25	TBA800	1.62
SAS580	2.90	TBA810AS	1.38
SAS590	2.90	TBA820	1.70
SG-264A	5.12	TBA820M	1.25
SG629	8.05	TBA890	3.94
SG-6533	13.20	TBA920(Q)	3.00
SL901B	7.00	TBA950(2X)	3.25
SL917B	9.25	TBA970	4.09
SL1310	1.80	TBA990	2.75
SL1327Q	1.20	TCA760	2.30

TCA270SQ	2.50
TCA800	5.95
TCA830	3.44
TCA900	2.20
TCA910	2.20
TCA940	1.95
TCP4621AF6	13.87
TDA440	2.20
TDA1002	1.95
TDA1003A	5.50
TDA1006A	2.50
TDA1005	3.60
TDA1010	3.30
TDA1011	4.00
TDA1035	4.70
TDA1037	2.95
TDA1044	4.37
TDA1060A	4.44
TDA1083	1.68
TDA1170S	3.00
TDA1190	3.50
TDA1190P	3.50
TDA1180	2.91
TDA1236	3.44
TDA1270	3.95
TDA1327	1.70
TDA1352B	1.60
TDA1412	1.50
TDA1415	1.40
TDA1470	4.67
TDA1770	5.60
TDA1908A	1.95
TDA2002	2.80
TDA2003	1.20
TDA2004	2.52
TDA2006	1.78
TDA2010	2.40
TDA2140	5.95
TDA2151	3.25
TDA2020	4.66
TDA2030	2.80
TDA2270	1.65
TDA1870	6.46
TDA2522	2.66
TDA2523	3.40
TDA2524	2.25
TDA2525	4.00
TDA2530	2.70
TDA2532	2.90
TDA2540	3.84
TDA2541	3.84
TDA2560	3.50
TDA2576A	3.75
TDA2577	4.73
TDA2578A	5.12
TDA2581	3.95
TDA2582	2.60
TDA2593	2.95
TDA2600	6.90
TDA2610	3.20
TDA2611A	2.35
TDA2640	2.90
TDA2653	5.90
TDA2680	3.40
TDA2690	2.72
TDA3190	2.00
TDA3330	2.21
TDA3500	6.90
TDA3560	6.00
TDA3561	6.66
TDA3562	8.60
TDA3571	3.75
TDA3651A	4.50
TDA3652	6.00
TDA3810	3.86
TDA3950	4.37
TDA4420	5.55
TDA4500	5.84
TDA4503	5.98
TDA4600	2.95
TDA4600-2D	2.95
TDA8180	4.00
TDA9503	4.21
TEA1009	1.86
TL494CN	6.57
UPC554	2.63
UPC566H	2.95
UPC575C2	3.40
UPC576H	2.60
UPC585	3.06
UPC587C2	2.34
UPC1025H	2.95
UPC1026H	1.24
UPC1028H	2.52
UPC1032H	94
UPC1042C	1.56
UPC1156H	4.26
UPC1158H	3.50
UPC1163H	2.48

UPC1167C2	2.70
UPC1168C	3.20
UPC1176C	2.53
UPC1177H	3.15
UPC1178C	4.21
UPC1180C	1.84
UPC1181H	1.62
UPC1182H	2.95
UPC1183H	2.48
UPC1185H	3.66
UPC1186H	1.60
UPC1188H	4.99
UPC1190G	4.20
UPC1198C	1.00
UPC1200V	1.18
UPC1211V	2.70
UPC1212V	1.34
UPC1215V	1.66
UPC1216V	1.20
UPC1217V	2.24
UPC1218H	1.80
UPC1223H	2.20
UPC1225H	1.50
UPC1226C	2.00
UPC1227V	5.4
UPC1228V	5.4
UPC1230H	4.39
UPC1238	2.50
UPC1245V	1.35
UPC1277	4.01
UPC1350C	4.15
UPC1353C	4.76
UPC1365C	6.38
UPC1366C2	2.08
UPC1367	2.08
UPC1358H	1.88
UPC1360C	2.20
UPC1363C	2.15
UPC1368H2	2.16
UPC1370C2	2.58
UPC1382C	1.08
UPC1384	3.79
UPC1394C	3.07
UPC1447H	5.8
UPC414C	2.80
UPC575C	2.46
UPC585C	1.28
UPC1167C2	2.20
UPD5535C1	20.76
UPD7519G	17.13
UPD7538G	11.06
UPD546C107	22.28
UPD547C049	11.18
U05G	1.27
V11N	1.27
10E2	4.43
10 Volt TUS	8.74

<b>COMPUTER ICs</b>	
74LS260	55
2732	3.30
2764	1.87
27128	3.13
27256	4.15
4116	1.70
4532/20NL	3.00
4164	1.60
6264	2.75
6522	4.09
Z80A CPU	1.70
8271	60.00
ZTX213	17
ZTX313	27
ZTX650/1	35
LM1889	2.00
74LS260	0.55

<b>COMMODORE ICs</b>	
6510 CPU	5.66
6526 CIA Keyboard	Int.
6561	5.11
6569 Col. Vid.	7.74
6581 Cont.	20.77
6582 Sound	3.37
6583 Gen.	7.79
901225 Char.	3.37
ROM	3.37
901226 Basic	6.45
RDM	6.45
901227 Kernel	3.52
ROM	3.52
906114 PLA	4.51
4164 RAM	1.60
Timer	84
8701 Clock Chip	5.46

<b>THYRISTORS</b>	
DEC1	2.20
DEC2	2.20
THY15/80	2.40
THY15/85	2.40
Transistor mounting kit TO66, TD3, TO220AB	
	30

<b>SEMICONDUCTORS</b>	
AC107	35
AC126	34
AC127	34
AC128	34
AC128K	40
AC141	62
AC141K	39
AC176	35
AC187	41
AC187K	38
AC188	46
AC188K	46
AD143=OC28	82
AD145	85
AD161	54
AD162	54
AD161/62 MP	1.15
AF106	49
AF114	89
AF121	75
AF124	48
AF125	53
AF126	53
AF127	53
AF139	63
AF178	1.54
AF239	60
AF279	1.56
AL102	4.90
AU110	3.01
BC107	20
BC108	20
BC109	20
BC114	12
BC115	17
BC116A	35
BC117	30
BC118	24
BC119	36
BC139	32
BC140	32
BC141	30
BC142	30
BC143	31
BC147	13
BC148	13
BC149	12
BC157	16
BC158=BC558	16
BC159	15
BC160	52
BC161	32
BC170B	15
BC171	15
BC172	15
BC173	16
BC174	10
BC177	27
BC178	26
BC182L	15
BC183L	15
BC184L	15
BC186	35
BC187	25
BC204	10
BC208	13
BC209	10
BC212	15
BC212L	15
BC213	15
BC214	15
BC237	14
BC238	14
BC251A	12
BC252	18
BC261	33
BC262	30
BC300	50
BC301	51
BC303	33
BC307	20
BC323	99
BC327	22
BC328	18
BC337	18
BC338	18
BC461	42
BC527	35
BC547	13
BC548	13
BCX32 = BC637	39
BC549	10
BC550	10
BC557	10

BC558	9
BC635	19
BC637	39
BC638	33
BC639	30
BC640	32
BC772	13
BC372	55
BD115	48
BD116A	90
BD124P	84
BD131	50
BD132	49
BD133	

# P.V. TUBES

TEL: 0254  
36521  
32611  
390936

## CALLERS ALWAYS WELCOME

TELEX: 635562  
GRIFFIN G  
FOR P.V.

### VIDEO PINCH ROLLERS

PANASONIC	NV7000	4.35
SANYO	VTC9300/VBS7000	4.35
SONY	C7J7/SL17	4.35
JVC	TCE3V00/01/06/16/23/24	4.35
JVC	HR2200/3320/3330/3660/1100/7700	4.35
AKAI	VS9700	4.35
HITACHI	VT5000	4.35
SHARP	VCS300/6500	4.35
SONY	TCS GEN	4.35

### VIDEO BELT KITS

VEKIT 1 AKAI	VS9300/VS9500/VS9800	
JVC	VS9300/VS9500/VS9800	
HR3300/HR3320/HR3330/HR3360		
TCE	8903/3V00/3V16/3V22	3.50
VEKIT 2 PANASONIC	NV7000B/NV7200B	3.00
VEKIT 3 SONY	SLC57	3.75
VEKIT 4 SONY	SL8000/8500/8600	4.50
VEKIT 5 SONY	SL3000UB	4.00
VEKIT 6 PANASONIC	NV3000B	3.00
VEKIT 7 SANYO	9300P	4.25
VEKIT 8 PANASONIC	NV2000B	3.75
VEKIT 9 PANASONIC	NV8600B/8610/V011	4.42
VEKIT 10 TOSHIBA	V8500	3.00
VEKIT 11 SHARP	VC7300	3.50
VEKIT 12 SHARP	VC6300/6660	4.00
VEKIT 13 SANYO	VTC5000	1.95
VEKIT 14 SANYO	VTC5300	2.50
VEKIT 15 JVC	HR7650	2.50
VEKIT 17 SHARP	9300	1.75
VEKIT 18 SHARP	9300	1.75
VEKIT 19 HITACHI	VT8000	1.12
VEKIT 20 HITACHI	VT11/33	2.15
VEKIT 21 HITACHI	9500	1.12
VEKIT 22 SONY	SLC6	7.95

### VIDEO IDLER TYRES

SONY	O.Dia	I.Dia	Width	50p
SONY	23.7	17.4	4.9	50p
SONY	24.2	18	5.1	50p
HITACHI	31.8	25	4.9	50p
PANASONIC	37	27	3.9	52p
AKAI	26	20	3.9	50p
JVC	32.8	3.4	3.9	56p
JVC	23.9	4.8	4	56p
NATPAN	31.2		56p	

### VIDEO HEADS

Thom New Life (Nat Pan)*	25.95
Thom New Life Heads (exchange)*	22.95
3HSSV	24.93
4HSS (3HSSN)	24.93
PS3B Sony/Beta	28.12
Philips V2000 and V2023	64.00
Philips 1700	64.00
Sanyo 9300/9455/9500	53.00
Sanyo 5000/5300/5400	53.00
Toshiba 9600 Upper Ass.	12.50
Toshiba 9600 (Rep. type only) PS3BT	37.50
Sony 8000 UB	49.39
Sony SLC9	49.39
Sony SLC5, 6, 7	49.39
Sharp 8300	58.00
Sharp 3300/3700	56.00
Sharp 3HSS (S.P.)	40.62
Hitachi H1V1/VT8000E	35.62
Hitachi VT33E/GEC 4004	35.62
Hitachi VT11/GEC 4100	35.62
Sharp 7300	49.39
Hitachi 9300/4001 3HSSH	32.12

\* Thom New Life heads are refurbished heads and we have types to cover most VHS types on an exchange basis

### VIDEO TAPE

SKC E60	2.50	Scotch E30	3.86
E120	2.88	E60	4.00
E180	2.80	E120	3.24
E240	3.78	E180	3.86
L500	2.90	L750	5.22
L750	3.40	VCC360	6.33
Philips LVC 1700	17.50	VCC480	7.23

### VIDEO SUNDRIES

VHS Drum Motor	25.50
VHS Capstan Motor	25.50
Sanyo 5000 Reel Motor	12.95
Sharp Reel Motor	19.50
Take up Idler Ass./Clutch Ass.	
VHS (general purpose)	5.95
Thom/JVC etc.	
Sharp 381/383/386/9100 9300/9500	2.97
Sanyo	6.95
Hitachi F.F. Idler VT11E/VT39E	2.90
Video Lamps	
Nat. Pan. Bulb VHS	1.30
General Purpose VHS 3V23 with plug VHS	1.41
Video Cars	1.95
Care Kit Deluxe	5.00
Universal Copy Kit	5.50
Head Cleaner	90
Beta Eccentricity Gauge	56.00

### VARICAP TUNERS

ELC1043-05	8.40
ELC104305 Mullard	12.50
ELC1043-06	8.40
ELC2003	18.50
Philips G8/G9	10.50
Philips G11 (U321)	9.90
U322	7.30
U341	9.50
U342	8.50

### PUSH BUTTON ASS.

Hitachi 4 way	12.36
Philips G8 (early)	17.82
Philips G8 (late)	18.97
Philips G11 Tip Switch unit	26.50
Philips KT3	16.67
Philips KT30	13.22
Thom 9000 6 way	20.70
Pye 697 repair kit	10.35
Pye 725-735 (also Red Mk.1)	12.60
Pye 725-735 tuning head with PCB	12.50
Decca 4 way	7.93
Decca 6 way	9.17
Decca 4/6 way conversion kit	17.50
Decca 7 way piano key rep. kit	15.62
GEC 2110 6 way	10.92
GEC 6 way slim	10.29
GEC/ITT/PYE 7 way	16.67
GEC Conversion kit	16.67
Rank A823	12.36
Rank T20A	11.21
ITT CVC 8/9 (mod)	13.80
ITT 6 way with VCR	8.90
Thom 8500	6.50
GEC 7 B/P c neons	10.50

### LINE OUTPUT TRANS.

Philips 210/300 Mono	10.00
Philips G8	8.75
Philips G9	9.50
Philips KT3	15.95
Philips K30	17.94
Philips TX2	13.39
Philips TX3	14.41
Philips G11	15.58
Pye 713/715	10.00
Pye 725 90°	10.50
Pye 169	10.00
Pye 741	9.90
Bang & Olufsen (2000,3000)	14.69
DECCA 80	8.58
Decca 100	8.58
Decca 1700	9.00
Decca 1730	8.58
Decca 2230	8.58
GEC 2110	16.75
GEC 2040	9.50
ITT CVC 1/9	10.85
ITT CVC 25/30/32	8.65
ITT CVC 20	8.60
ITT CVC 45	8.60
R.B.M. T20	13.95
R.B.M. BUSHRANGER T16A	10.00
R.B.M. BUSHRANGER T18A	10.00
Thom 3000 EHT	9.95
Thom 3000 SCAN	7.95
Thom 8500	17.50
Thom 3000/3500 Mains	10.00
Thom 1615	12.50
Thom 1691	9.68
Thom TX9	23.85
Thom 9600 (Gen Thom)	21.79
Thom 9000	25.53

### RECTIFIER TRAYS

Thom 1500 3 Stick	5.20
Thom 1500 5 Stick	5.99
Thom 3500	7.98
Thom 8000	6.95
Thom 8500/8800	7.15
Thom 9000	8.70
Decca 1730/1830	5.48
Decca 30	6.76
Decca 80	7.12
Decca 100	7.50
Decca/Tatung 120/130	6.50
GEC 2100	7.40
GEC 2200 (20AX)	6.50
GEC 2040/2028	6.60
GEC 2110 (pre or post Jan '77)	7.00
Philips G8 Short Focus Lead	7.12
Philips G8 Long Focus 550	7.12
Philips G9	6.37
Pye/Philips KT3	12.50
Pye 691/3	7.58
Pye 713 4 Lead	8.79
Pye 713 5 Lead	8.79
Pye 731/25	8.75
R.B.M. A823 plug in	8.75
Rank T20/22	7.12
ITT CVC5/9	7.50
ITT CVC20/25/30 (Mullard)	7.12
ITT CVC45	8.65
Universal	6.00
TV 11 Stick	90
TV 13	1.26
TV 14	1.29
TV 18	1.10
TV 20	1.43

## SECURITY DIST. FOR EQUIPMENT SHORROCKS

B1 Shorrock Acorn	
075 panel	32.50
B2 Eurobell Comp.	21.00
B5 "C" Polyprop. box with back plate	4.55
B6 "C" Polycarb. box with back plate	7.80
B7 Freidland Bell	12.47
CA15 4 core cable	5.55
CA16 6 core cable	7.94
CA17 8 core cable	10.31
817S Shorrock P.I.R.	22.50
815S Shorrock P.I.R.	41.50
010 Orion I.R.	24.00
SL8 Infrascan	62.94
137 Shorrock SAB	8.76
BA9 1.9A battery	7.77
S3 712 Siren	5.75

### FULL LIST ON REQUEST

### GEN. EQUIPMENT/TOOLS

Testlead Set (AVO Type)	2.20
Degaussing Coil Stick	19.00
Signal Injector	4.00
Electric Circuit Tester	1.50
Probes (x10) or (x1)	10.90
Philips Switchable Probes	13.25
Automatic Wire Strippers	6.95
I.C. Inserters	1.18
Micro Pliers	4.20
Micro Cutters	5.00
Trim Tools Metal Ended	30
Side Cutters sm.	1.20
Long Nose Pliers	1.20
Sm. Neon Screwdriver	40
Quick Set Adhesive (Superglue)	75
Dynascan Tube Reju./testers	
467 model inc. bases *	399.00
470 model inc. bases *	299.00
available without bases for 50.00 less	

(see "SPRING OFFER")

### Tube Bases For Dynascan

No. 1	9.09	No. 14	16.63
No. 3	9.50	No. 15	16.44
No. 5	9.09	No. 18	10.63
No. 6	11.08	No. 19	10.83
No. 7	9.09	No. 21	14.40
No. 8	10.08	No. 23	13.86
No. 9	9.09	No. 24	27.07
No. 13	11.11	No. 25	12.57

### Avo Meters Factory Recon.

Avo Battery	2.09
Solder Sucker Antistat min.	4.50
Solder Sucker Antistat std.	5.40
Solder Sucker Antistat lge.	6.20
Solder 500g	7.00
D.I.Y. Solder Small Pack	45
Solder Sucker Nozzles	81
Solda Mop Std.	77

For sold. irons see Antex/Weller Under Specific Spares

Choc Bloc 5A	20
Fuse Wire 5A, 15A, 30A	05
Fluorescent Starter 4-80W)	15
Battery Press Studs min.	11
Battery Press Studs std.	15
Vero Board	2.59
Double Sided Adhesive Tape	5.75
Tinned Copper Wire	
185 WG 45 Amp	1.86
14SWG 100 Amp	1.86
17SWG 60 Amp	1.86
19SWG 45 Amp	1.86
20SWG	2.75
22SWG	1.86
Insulated Copper Wire	9.11
Cable Ties ALT1 per 100 (small)	84
Cable Ties ALT21 per 100 (large)	1.69
Power Adapter (12v)	5.95
Reg. 88 Power Adap.	5.50
Reg. 650 Power Adap.	6.50

### TURBO RECHARGEABLE

Screwdriver Kit	22.71
Drill Kit	25.99
Sold. Iron Kit	16.99
Rep. Tips	2.00
Rep. Bulbs	6.20

## FOR ALL YOUR SPECIFIC COMPONENTS

### THORN/FERGUSON

SONY	
AMSTRAD	
FIDELITY	
HITACHI/GEC	
PHILIPS	
DECCA	
SINCLAIR	
COMMODORE	
ANTEX	
ANTIFERRENCE	
EVER READY	
LABGEAR	
NEWLIFE	
AMPROBE	
SERVISOL	
UNISEF	
ARROW	
SCOTCH	
SKC	
SPARKOMATIC	

### JUST ASK!!

We cannot advertise our complete range of products. Please ask if you require something which is not listed, ie: Stationery, Stylis, Axial/Radial Electrolytics, Mixed Dielectric Caps., Polyester Caps., Carbon Resistors, Wirewound Resistors, Filament Lamps, Thermistors, LEDs, IC Sockets, Floppy Discs, Computer Cassettes, Thom New Life Tubes (collection only), New Mono Tubes, Crystals, Cables (post chgs extra), Aerial Equipment, Electrical Plugs/Sockets, Components for Sinclair, Amstrad and Acorn. Unisef Audio Range.

### SEND FOR CATALOGUE!

SEND FOR OUR FULL CATALOGUE



THORN NEW LIFE \*  
VIDEO HEADS FOR  
NAT. PANASONIC  
VEH0103  
VEH0121 £25.95  
VEH0218 exchange

Full equivalent list on request

SERVISOL  
COLDKLENE 110  
DEGREASE SOLVENT  
87p

F.M. AERIAL (round)  
OMNI-DIRECTIONAL  
£7.95

SURGE PROTECTION PLUG 13A

£12.50

### REMOTE HANDSETS

PHILIPS	
IR8331 KT3/K30 Non Text IR	15.85
IR8420 KT3/K30 Text IR	16.70
IR8435 G11 8 Way Text IR	20.85
OS8263 G11 Non Text US	19.50
US8518 G11 2 Function US	18.75
691, 17181 G11 31 Button US	27.80
218, 20578 KT3 K30 K35 KT4 KT40 (Non Text or Text)	25.00

### J.V.C.

RTPB43 Text IR (Also G11)	13.50
---------------------------	-------

### GRUNDIG

RTP20 Teleplot 12	13.50
RTP05 Teleplot 8	13.50
RTP06 Teleplot 160	13.50
RTP07 Teleplot 300	13.50
RTP 400/01	13.50

### DECCA

US8513 101 Non Text US	20.85
US8511 80/100 3 Func. US	19.50

### THORN

IR8442 T723	19.50
IR8688 T725 TX9/10	23.00
IR8864 T736 TX9/10/100 Text	23.85
IR8689 T731 TX9	23.85

### FIDELITY

FD09193 Txt. 32 butt	15.90
FD09820 15500	13.81
FD09156 F14R	13.81
FD0911 AVS	13.75
FD09141 CTU 20R/140R (IR8876)	13.75

### SONY

C5 RM75T	29.04
C6	22.82
C7 RMT200	42.00
C9 RH2/3	42.00

### HITACHI/GEC

9300/V4001	9.93
Remote Control Tester	29.94

### DIY AERIAL PACK



TELEVISIONS  
AND VIDEOS  
FROM HOTELS  
AND PRIVATELY  
OWNED RENTAL  
COMPANIES

# Are you having problems finding the right stock at the right price?

— Are you looking for a supplier who offers:

- \* A PERSONAL SERVICE TO BOTH INDIVIDUAL AND VOLUME CUSTOMERS
- \* A VAST SELECTION OF WORKING STOCK IN SHOWROOM CONDITION
- \* VALUE FOR MONEY \* CONTINUITY OF SUPPLY \* TECHNICAL SUPPORT
- \* MODERN WAREHOUSE FACILITIES \* WARM FRIENDLY ATMOSPHERE?



HITACHI, GRUNDIG, GEC, JTT, JVC,  
MITSUBISHI, PHILIPS, FERGUSON  
DECCA/TATUNG — PLUS MANY MORE

THEN STOP WORRYING —  
COME AND SEE US —  
WE'VE BEEN HERE ALL THE TIME!

— OPEN —  
MONDAY TO FRIDAY 10AM - 5.30PM  
ALL OTHER TIMES BY APPOINTMENT

# PRO-VISION

BREEDON CROSS STORAGE  
DALE ROAD  
SELLY OAK  
BIRMINGHAM  
B29 6AQ

THE PROFESSIONALS  
THE PROFESSIONALS  
STAN STAN

**WE ARE HERE**

**FROM M5 Junc 4**

**FROM M6 Junc 6**

TELEPHONE  
021 471 5116  
NOW  
AND ASK FOR  
OUR NEW  
CATALOGUE




HOW TO INCREASE YOUR PROFITS, IMPROVE YOUR SERVICE, WITH COST EFFECTIVE TEST EQUIPMENT.

### HAMEG OSCILLOSCOPES

HAMEG are Europe's top selling DUAL TRACE OSCILLOSCOPES. Select from four superb models. All incorporate a useful COMPONENT TESTER. Size - all models - 285mm x 145mm x 380mm. Clear display 8 x 10cm. Mains supply 110/125/220/240V AC 50/60Hz. **2 YEAR WARRANTY**

#### HM203-6 20MHz Standard

FREE Securicor Delivery

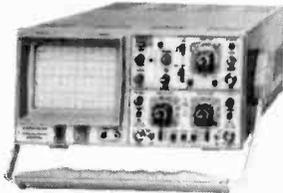

- SPECIFICATION**
- Bandwidth DC-20MHz
  - Sens. Ch1, Ch2, 2mV/cm
  - Time Base 0.25s/cm - 20ns/cm
  - Trigger DC-40MHz AC, DC, HF, LF, (TV Frame)
  - Active TV Sinc. Sep.
  - Invert both channels
  - Variable hold-off 10:1
  - Calibrator
  - Plus many more features

Price £314.00 + £47.10 V.A.T.

Including two probes


FREE Securicor Delivery

#### HM204-2 20MHz Multi-function

**SPECIFICATION**


- Bandwidth DC-20MHz
- Sens. Ch1, Ch2, 1mV/cm
- Delay Line
- Time Base 1-25s/cm - 10ns/cm
- Delayed Sweep 100ns - 0.1s
- Trigger DC-50MHz AC, DC, HF, LF, (TV Frame)
- Variable hold-off 10:1
- Overscan LED indicators
- Calibrator
- Plus many more features

Price £418.00 + £62.70 V.A.T.

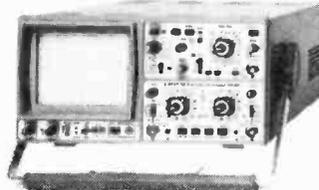

#### HM205 20MHz Digital Storage

FREE Securicor Delivery

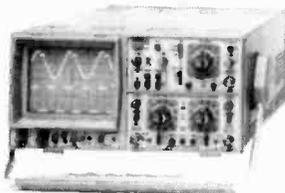

- SPECIFICATION**
- Digital Storage
  - Analogue Real Time (Same as 203-6)
  - Bandwidth DC-20MHz
  - Sens. Ch1, Ch2, 2mV/cm
  - Trigger DC-40MHz AC, DC, HF, LF, (TV Frame)
  - Active TV Sinc. Sep.
  - 100KHz Sample Rate
  - 2 x 1K Storage
  - Storage Range, 1ms-5s/cm
  - Variable hold-off 10:1
  - Calibrator
  - Plus many more features

Price £498.00 + £74.70 V.A.T.

Including two probes


FREE Securicor Delivery

#### HM605 60MHz Multi-function

**SPECIFICATION**

- Bandwidth DC-60MHz
- Sens. Ch1, Ch2, 1mV/cm
- Delay Line
- Delayed Sweep 100ns - 0.1s
- Trigger DC-80MHz AC, DC, HF, LF, (TV Frame)
- Variable hold-off 10:1
- Switchable Calibrator
- Overscan LED indicators
- Plus many more features

Price £583.00 + £87.45 V.A.T.

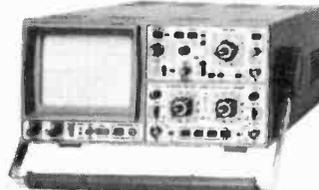

#### B.K.'s CRT TESTER-REJUVENATOR



Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

Price £32.00 + £4.80 V.A.T.

#### B.K.'s REVOLUTIONARY DYNAMIC 'LOPT' TESTER

Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC

Price £25.99 + £3.90 V.A.T.



#### THANDAR SC110A PORTABLE OSCILLOSCOPE



Price £195.00 + £29.25 V.A.T.

- Only 2 1/4" thick
- Fits in a brief case
- Sens. 10mV
- Bandwidth 10MHz
- Full trig. fac. inc. TV frame etc.
- Battery or mains adaptor
- Size 255mm x 148mm x 50mm

**ACCESSORIES**

- Carry Case £6.25 + £0.93 V.A.T.
- Probe £7.50 + £1.30 V.A.T.
- Mains Adaptor £7.30 + £1.09 V.A.T.

#### DIGITAL LCR METER

- LCD Display
- 18 Ranges
- Inductance 1µH - 2H
- Capacitance 1pf - 200µf
- Resistance 1ohm - 20Mohm
- High accuracy

Price £85.00 + £12.75 V.A.T.



#### INSULATION TESTER 500V



- Electronic battery operated
- Measuring Voltage 500V DC
- Measuring Range 0-100Mohm
- Centre scale 2Mohm

Price £65.00 + £9.75 V.A.T.

### LEADER LCT910-A CRT TESTER REJUVENATOR



Price £317.00 + £47.55 V.A.T.

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W CRT's.

- Tests for shorts and leakage between electrodes.
- Tests cathode emission characteristics.
- Separately checks condition of guns.
- Removal of shorts and leakage between electrodes.
- Checks heater warm-up characteristics.
- Rejuvenation of low emission cathodes with automatic timing.
- Super rejuvenation with manual control.
- Complete with tube base adaptors.
- Size H230mm W330mm D120mm.

### SADELTA FIELD STRENGTH METER TC-402

THE SADELTA FIELD STRENGTH METER TC-402 has been designed to measure the signal levels delivered by the antenna to a TV or FM receiver, in order to test the performance of the antenna and evaluate the best conditions during installation, etc. To facilitate measurements, the tuning frequency readout is shown on a digital display.

#### FEATURES

- Covering FM and all TV bands (UHF/VHF) including CATV freq.
- Digital tuning display (3 digits) for direct frequency readout.
- Accurate 10 turn tuning potentiometer.
- Built-in loudspeaker enables monitoring of sound in AM/FM.
- Meter measurement in voltage and dB from 20µV (26dB/µV).
- Continuity tester 0-500 ohms.
- Fully portable (battery).
- Sturdy carry case.



Price £249.00 + £37.35 V.A.T.

### SADELTA COLOUR PATTERN GENERATORS

THE SADELTA RANGE OF HAND HELD COLOUR PATTERN GENERATORS is intended for use in production, installation and service of both colour and monochrome TV sets, video and computer monitors. In order to control and adjust the various parameters eight switchable patterns are provided. The technician has ready access to Laboratory, workshop and field use as the Generator has been designed using the latest micro-technology to achieve truly pocket size instruments. Internal re-chargeable Ni-Cd's. Supplied with 9V power supply charger. Size 131mm x 81mm x 23mm.

#### T.V. PATTERN GENERATOR PAL MC11B UK

- Band IV (21-34)
- O/Put 10mV into 75ohms
- Band III (5-12)
- Sound output
- PAL I.

Price £124.95 + £18.74 V.A.T.

#### PAL VIDEO COMPOSITE GENERATOR

- PAL B.G.I.
- Audio O/Put 10mV
- O/Put 1V p.p. @ 75ohms
- Switching 12V @ 4K7ohms

Price £124.95 + £18.74 V.A.T.

#### SECAM VIDEO COMPOSITE GENERATOR


- SECAM B.G.D.K.L.
- Audio O/Put 10mV
- O/Put 1V p.p. @ 75ohms
- Switching 12V @ 4K7ohms

Price £124.95 + £18.74 V.A.T.

#### R.G.B. PATTERN GENERATOR

- O/Put sigs. Pos.RGB
- Neg. Composite
- O/Put TTL 5V P-P
- Blank Pulse etc. CCR

Price £111.95 + £16.79 V.A.T.

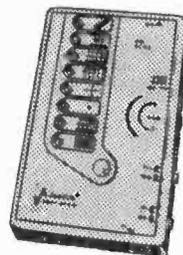

#### DIGITAL THERMOMETER



- Pocket Size
- -50°C to +750°C
- 1°C Resolution
- 0.5" LCD
- Supplied with thermocouple

Price £59.50 + £8.92 V.A.T.

#### 200MHz DIG. FREQ. METER




- Pocket Size
- 8 Dig. LED Display
- Freq. Range 20Hz to 200MHz
- Resolution 0.1Hz
- Sensitivity 10mV

Price £75.50 + £11.32 V.A.T.

#### LEADER HIGH VOLTAGE METERED EHT PROBE

LEADER High Voltage Metered EHT PROBE. Measures up to 40KV DC with safety. Built in meter. Accuracy ±3%

Price £45.00 + £6.75 V.A.T.

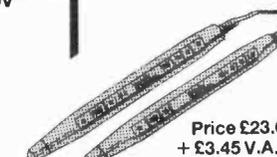

Price £23.00 + £3.45 V.A.T. each

The THANDAR TP1 LOGIC PROBE and TP2 LOGIC PULSER are effective and economical tools for checking both TTL and CMOS circuits. TP1 can show 14 different circuit conditions and can detect pulses down to typically 10ns. TP2 can inject a signal directly into a circuit without damaging sensitive components. Together they can stimulate and monitor responses of components 'in circuit', greatly aiding fault finding.




U.K. POST PAID, export enquiries welcome. Visa/Access or cheque with order, payable B.K. Electronics. Official Orders welcome from Govt. Depts., Colleges, P.L.C.'s etc. Large S.A.E. for technical leaflets of complete range. Delivery normally within seven days.



**B. K. ELECTRONICS DEPT. T**  
UNIT 5, COMET WAY, SOUTHEND-ON-SEA,  
ESSEX. SS2 6TR TEL: 0702-527572

**JULY SPECIALS**

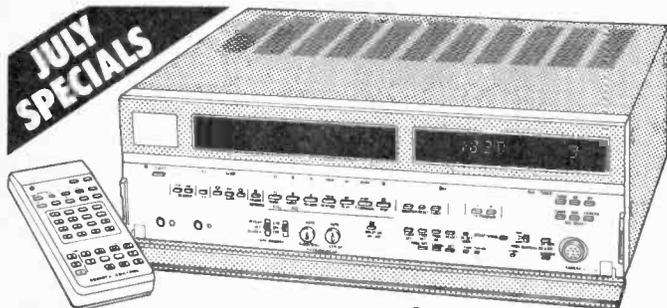

**3V23 JVC/THORN**  
FULL REMOTE INC. HANDSET

MIN ORDER 5

**ONLY £115**  
FULL WORKING ORDER

MECHANICAL 3V16/22 **FROM £65**  
MIN ORDER 5

**CELTEL**

2 BREACH ROAD, WEST THURROCK, ESSEX. Tel: (0708) 861404

Phone: **0800-289239 (Toll Free)**

TELEX: 295141 TX LINK G - MBX 708861404  
EXPORT ENQUIRIES WELCOME



**Now Arriving...**

**MICROWAVES  
COMPACT DISC  
AUDIO**

**CALL NOW FOR DETAILS**

REPLACEMENT  
JVC/THORN  
CLOCK TRIM - 3V22 etc.



**ONLY £1.50**

NEW COLOUR PORTABLES  
IN SELF-ASSEMBLY FORM (SKD)  
AVAILABLE SHORTLY...  
TAKING ORDERS NOW

**TEST BENCH FACILITIES**  
*You check it!*

**New Branch Opening Soon**  
Watch this space for details.

**SOUTHSIDE TV**

**NOW OPEN**

AT UNIT 8, APPLE IND. EST.,  
WHITTLE AVE.,  
SEGENSWORTH WEST,  
FAREHAM. J9/M27.

**FOR SALE  
OF TOP QUALITY  
EX-RENTAL TELEVISIONS  
AND VCR'S**



**LOCKSHEATH  
(04895)  
77251**

**FOR FURTHER INFORMATION**

**MAKE YOUR INTERESTS PAY!!**

Train at home for one of these Career Opportunities

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio & TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Elec. Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
<b>GCE over 40 'O' &amp; 'A' level subjects</b> <input type="checkbox"/>	

Name: \_\_\_\_\_

Address: \_\_\_\_\_

P. Code \_\_\_\_\_

**ICS** International Correspondence Schools,  
Dept. EGS77, 312/314 High St., Sutton, Surrey  
SM1 1PR. Tel: 01-643 9568 or 041-221 2926  
(both 24 hours).



**INTERNATIONAL LTD.**

**WHOLESALE OF  
QUALITY EX. RENTAL EQUIPMENT  
TO UK & EUROPE**

It seems customary for many wholesalers to advertise the largest range in the UK, at the lowest prices. However when you arrive at some of these places the equipment looks as though it has come out of a war zone and has been delivered by tipper.

At TVS, we purchase our sets from one of the countries principal rental companies, who deal with virtually every major manufacturer thus giving us a range of products that we genuinely feel are unbeatable. Don't take our word for this though. If you care to give us a ring we will send you free of charge, by return a comprehensive price list of all our products. You will also find the prices we advertise are the prices you pay, (a refreshing change we feel these days).

**As well as a large range of TVs we have many VCRs on special offer this month including:**

<b>FERGUSON 3V29</b>	<b>£100.00</b>
<b>FERGUSON 3V30</b>	<b>£105.00</b>
<b>FERGUSON 8940 stereo</b>	<b>£115.00</b>

*These are not just workers but fully refurbished, wrapped and include instruction books.*

*These must be the best prices in the country for the most popular electronic VCR ever made.*

*We also have a limited number of other refurbished machines from only £60.00.*

To reserve your order phone while stocks last.

**EXPORT INQUIRIES WELCOME**

Phone Head Office, Bromsgrove

**FOR FURTHER DETAILS AND A COMPREHENSIVE PRICE LIST CONTACT:**

**COLIN BROOMFIELD  
TVS INTERNATIONAL LTD.**

Head Office, Unit 7, Station St.,  
Bromsgrove, Worcs. B60 2BS.

**(0527) 71186 or 37037**

or call our latest franchise dealers:

Pitchford & Evans,  
Unit 2, Station Hill,  
Oakengates,  
Telford TF2 9AA.  
0952 616771

Videoscope Europe Ltd.,  
190 Graig Rd.,  
Godrergrraig,  
Swansea SA9 2NY  
0639 843839

*Prices quoted for cash payment and subject to VAT*

**Comprehensive spares back up available  
Delivery service available to UK & Europe**



# SWITCH ON TO PROFIT!

3,000 TV's and Video's in stock—  
Teletext from £50

Thorn 9-6 from £25 working

Working Mechanical Videos  
from £65.

Working Electronic Videos  
from £90.

**SUPERB  
RANGE OF  
WORKING  
VIDEOS**

Non-working Videos  
from £25.

T.V. Stands, Spares  
& Remotes.

Also New & Graded White Goods.  
Small Appliances with  
Manufacturer's guarantee.  
Delivery arranged.

**LEADING  
BRANDS**

**ELECTRIC**

Incorporating MONITEC NEW 16,000 sq.ft  
WAREHOUSE

UNIT 22, GREEN ST INDUSTRIAL ESTATE  
GREEN ST, KIDDERMINSTER DY10 1HN  
Telephone (0562) 755526 or 741666

Main distributors for Skyscan Satellite Products

**City**

## VHS VIDEOS

### FERGUSON 3V22

WORKING £80  
NON-WORKING £35 (EASY FAULTS)

ALL MACHINES ARE COMPLETE  
NO MISSING TRIM  
GOOD CABINETS

### ELECTRONIC VIDEOS

MANY MODELS – SOME REMOTES

WORKERS £100  
NON-WORKERS £70

## V.C.R. ELECTRONICS

(THE VIDEO PEOPLE!)

UNIT 5, PRESTWOOD COURT,  
LEACROFT ROAD,  
BIRCHWOOD, WARRINGTON, CHESHIRE  
TELEPHONE: 0925 819081

## FIRST IN TUBE REBUILDING TECHNOLOGY 30AX; 540 SERIES!

**REDUCED SERVICING COST,  
FIT A DIRECT REPLACEMENT**

**AVAILABLE ONLY FROM CHROMAVAC.  
PRE CONVERGED AS ORIGINAL.  
EXTERNAL MULTIPOLE UNIT NOT REQUIRED.**

**QUALITY  
REBUILDS**

**SPECIAL  
OFFERS  
ON  
INLINE**



Get on the hot-line today!

LOOK! AT NO EXTRA COST  
30AX PRE CONVERGED

061  
**681 2959**

most types of Inline Re-builds or  
new ex-stock

PRICES SUBJECT TO  
GLASS EXCHANGE

### Delta Rebuilds

Up to 19" ..... £28  
Up to 22" ..... £30  
Up to 26" ..... £34  
110° up to 22" ..... £34  
110° up to 26" ..... £38  
Low focus ..... +£2  
A47 342 New ..... £28  
17FHP New ..... £30  
470EHB New ..... £30  
Delta only. Less 5% 5+

### Inline Rebuilds

Up to 22" .. From £40  
Up to 26" .. From £45  
A56 - 540x ..... £56  
A66 - 540x ..... £58  
Bonded Coil ..... +£5

ALL SIZES OF NEW AND  
REBUILT MONO TUBES  
AT COMPETITIVE PRICES

### IN LINE TYPES (NOT REBUILDS) PHONE RE STOCK POS.

Please enquire types not listed

370 HFB-A37-590 ..... £50	AXT 56-001 ..... £67
370 HUB ..... £50	670 CZB ..... £80
AXT 37-001 ..... £50	A66-540 ..... £110
420 CSB ..... £50	420FSB ..... £60
420 EDB-A42-590 ..... £50	
420 EZB ..... £50	
420 ERB ..... £50	
470 KUB ..... £50	
510 UFB/A51-590 ..... £67	
510 VSB ..... £67	
AXT51-001 ..... £67	
560 DYB-560 DTB ..... £67	
560 EGB ..... £67	
560 CGB ..... £67	
560 DMB ..... £67	

MIN. CARRIAGE £5  
£10 if glass collected.  
TERMS  
Cash with order  
ALL PRICES  
EXCLUSIVE OF VAT

NOTE  
Surcharge  
without  
exch. glass.

★ WE PURCHASE SURPLUS STOCKS  
OF INLINE TUBES: ALSO A56/  
66 – 510/540 ETC. OLD GLASS.  
DELIVERY: By return on all stock items.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

**CHROMAVAC**

CHROMAVAC LTD., PUMP STREET,  
HOLLINWOOD, OLDHAM OL9 7LR

Ask for Mr Butterworth ON: 061-681 2959

AA117	9p	B0370	30p	BR100	14p	TIP54	140p	3N.128	55p	PCF200	135p	BA-6135	250p	LA-4505	260p	STK-435	510p	TD-2004	170p	25C-461	30p	TIC44	22p
AA119	9p	B0371	30p	BR101	43p	TIP105	65p	3N.143	65p	PCF801	110p	BA-6208	250p	LA-4507	260p	STK-436	500p	TD-2005	170p	25C-462	30p	TIC45	22p
AA323	9p	B0433	28p	BR103	37p	TIP106	65p			PCF802	100p	BA-6304	190p	LA-4510	160p	STK-437	670p	TD-2006	150p	25C-536	30p	TIC47	32p
AC107	40p	B0434	30p	BR139	55p	TIP110	47p			PCF805	100p	CA-3011	110p	LA-5112	120p	STK-441	740p	TD-2007	200p	25C-733	30p	OPTO	
AC126	21p	B0435	31p	BR149	30p	TIP111	50p	AA119	9p	PCF806	100p	CA-3012	110p	LA-5113	120p	STK-442	740p	TD-2008	140p	25C-828	25p	ELECTRONICS	
AC128	21p	B0437	28p	BR154	33p	TIP112	40p	BY100	100p	PCF807	100p	CA-3013	110p	LA-5114	120p	STK-443	740p	TD-2009	100p	25C-940	40p	OR121	100p
AC128K	26p	B0438	36p	BR155	33p	TIP113	40p	BY101	100p	PCF808	100p	CA-3014	110p	LA-5115	120p	STK-444	740p	TD-2010	100p	25C-1060	90p	OR122	100p
AC141K	26p	B0439	36p	BR156	33p	TIP114	40p	BY102	100p	PCF809	100p	CA-3015	110p	LA-5116	120p	STK-445	740p	TD-2011	100p	25C-1172	150p	OR123	100p
AC142K	26p	B0440	36p	BR157	33p	TIP115	40p	BY103	100p	PCF810	100p	CA-3016	110p	LA-5117	120p	STK-446	740p	TD-2012	100p	25C-1060	90p	OR124	100p
AC153K	23p	B0440	40p	BT100A	40p	TIP120	43p	BY164	40p	PCF811	100p	CA-3017	110p	LA-5118	120p	STK-447	740p	TD-2013	100p	25C-1060	90p	OR125	100p
AC176	23p	B0441	40p	BT106	70p	TIP121	46p	BY176	85p	PCF812	100p	CA-3018	110p	LA-5119	120p	STK-448	740p	TD-2014	100p	25C-1060	90p	OR126	100p
AC176K	23p	B0442	40p	BT108	90p	TIP122	47p	BY179	36p	PCF813	100p	CA-3019	110p	LA-5120	120p	STK-449	740p	TD-2015	100p	25C-1060	90p	OR127	100p
AC187K	28p	B0444	40p	BT116	80p	TIP125	47p	BY182	32p	PCF814	100p	CA-3020	110p	LA-5121	120p	STK-450	740p	TD-2016	100p	25C-1060	90p	OR128	100p
AC188	21p	B0534	38p	BT119	100p	TIP126	56p	BY184	32p	PCF815	100p	CA-3021	110p	LA-5122	120p	STK-451	740p	TD-2017	100p	25C-1060	90p	OR129	100p
AC198K	21p	B0535	38p	BT120	100p	TIP127	56p	BY187	32p	PCF816	100p	CA-3022	110p	LA-5123	120p	STK-452	740p	TD-2018	100p	25C-1060	90p	OR130	100p
AC198	21p	B0536	38p	BT138	60p	TIP131	50p	BY196	20p	PCF817	100p	CA-3023	110p	LA-5124	120p	STK-453	740p	TD-2019	100p	25C-1060	90p	OR131	100p
AC198	21p	B0536	38p	BT146	99p	TIP142	90p	BY206	110p	PCF818	100p	CA-3024	110p	LA-5125	120p	STK-454	740p	TD-2020	100p	25C-1060	90p	OR132	100p
AD142	100p	B0537	40p	BT151	58p	TIP145	65p	BY207	110p	PCF819	100p	CA-3025	110p	LA-5126	120p	STK-455	740p	TD-2021	100p	25C-1060	90p	OR133	100p
AD149	35p	B0538	40p	BT146	90p	TIP146	90p	BY208	18p	PCF820	100p	CA-3026	110p	LA-5127	120p	STK-456	740p	TD-2022	100p	25C-1060	90p	OR134	100p
AD161	60p	B0675	40p	BU104	100p	TIP295	42p	BY210	22p	PCF821	100p	CA-3027	110p	LA-5128	120p	STK-457	740p	TD-2023	100p	25C-1060	90p	OR135	100p
AD164	200p	B0676	40p	BU105	100p	TIP304	45p	BY225	120p	PCF822	100p	CA-3028	110p	LA-5129	120p	STK-458	740p	TD-2024	100p	25C-1060	90p	OR136	100p
AF124	30p	B0677	38p	BU108	100p	TIP305	42p	BY226	18p	PCF823	100p	CA-3029	110p	LA-5130	120p	STK-459	740p	TD-2025	100p	25C-1060	90p	OR137	100p
AF125	30p	B0678	38p	BU110	100p	TIP306	42p	BY227	18p	PCF824	100p	CA-3030	110p	LA-5131	120p	STK-460	740p	TD-2026	100p	25C-1060	90p	OR138	100p
AF126	30p	B0679	38p	BU111	100p	TIP307	42p	BY228	18p	PCF825	100p	CA-3031	110p	LA-5132	120p	STK-461	740p	TD-2027	100p	25C-1060	90p	OR139	100p
AF127	30p	B0680	40p	BU112	100p	TIP308	42p	BY229	18p	PCF826	100p	CA-3032	110p	LA-5133	120p	STK-462	740p	TD-2028	100p	25C-1060	90p	OR140	100p
AF139	30p	B0681	45p	BU126	70p	TIP309	42p	BY230	20p	PCF827	100p	CA-3033	110p	LA-5134	120p	STK-463	740p	TD-2029	100p	25C-1060	90p	OR141	100p
AF139	30p	B0682	45p	BU205	70p	TIP310	42p	BY231	20p	PCF828	100p	CA-3034	110p	LA-5135	120p	STK-464	740p	TD-2030	100p	25C-1060	90p	OR142	100p
AF201	30p	B0683	45p	BU206	100p	TIP311	42p	BY232	20p	PCF829	100p	CA-3035	110p	LA-5136	120p	STK-465	740p	TD-2031	100p	25C-1060	90p	OR143	100p
AL100	450p	B0684	45p	BU206	100p	TIP312	42p	BY233	20p	PCF830	100p	CA-3036	110p	LA-5137	120p	STK-466	740p	TD-2032	100p	25C-1060	90p	OR144	100p
AL112	300p	B0685	45p	BU206	100p	TIP313	42p	BY234	20p	PCF831	100p	CA-3037	110p	LA-5138	120p	STK-467	740p	TD-2033	100p	25C-1060	90p	OR145	100p
AM150	30p	B0686	45p	BU206	100p	TIP314	42p	BY235	20p	PCF832	100p	CA-3038	110p	LA-5139	120p	STK-468	740p	TD-2034	100p	25C-1060	90p	OR146	100p
AM151	30p	B0687	45p	BU206	100p	TIP315	42p	BY236	20p	PCF833	100p	CA-3039	110p	LA-5140	120p	STK-469	740p	TD-2035	100p	25C-1060	90p	OR147	100p
AM154	35p	B0688	45p	BU206	100p	TIP316	42p	BY237	20p	PCF834	100p	CA-3040	110p	LA-5141	120p	STK-470	740p	TD-2036	100p	25C-1060	90p	OR148	100p
AM156	35p	B0689	45p	BU206	100p	TIP317	42p	BY238	20p	PCF835	100p	CA-3041	110p	LA-5142	120p	STK-471	740p	TD-2037	100p	25C-1060	90p	OR149	100p
AM156	35p	B0690	45p	BU206	100p	TIP318	42p	BY239	20p	PCF836	100p	CA-3042	110p	LA-5143	120p	STK-472	740p	TD-2038	100p	25C-1060	90p	OR150	100p
AS215	100p	B0691	45p	BU206	100p	TIP319	42p	BY240	20p	PCF837	100p	CA-3043	110p	LA-5144	120p	STK-473	740p	TD-2039	100p	25C-1060	90p	OR151	100p
AS217	100p	B0692	45p	BU206	100p	TIP320	42p	BY241	20p	PCF838	100p	CA-3044	110p	LA-5145	120p	STK-474	740p	TD-2040	100p	25C-1060	90p	OR152	100p
AU113	600p	B0693	45p	BU206	100p	TIP321	42p	BY242	20p	PCF839	100p	CA-3045	110p	LA-5146	120p	STK-475	740p	TD-2041	100p	25C-1060	90p	OR153	100p
BA148	10p	B0694	45p	BU206	100p	TIP322	42p	BY243	20p	PCF840	100p	CA-3046	110p	LA-5147	120p	STK-476	740p	TD-2042	100p	25C-1060	90p	OR154	100p
BA154	6p	B0695	45p	BU206	100p	TIP323	42p	BY244	20p	PCF841	100p	CA-3047	110p	LA-5148	120p	STK-477	740p	TD-2043	100p	25C-1060	90p	OR155	100p
BA157	12p	B0696	45p	BU206	100p	TIP324	42p	BY245	20p	PCF842	100p	CA-3048	110p	LA-5149	120p	STK-478	740p	TD-2044	100p	25C-1060	90p	OR156	100p
BA158	7p	B0697	45p	BU206	100p	TIP325	42p	BY246	20p	PCF843	100p	CA-3049	110p	LA-5150	120p	STK-479	740p	TD-2045	100p	25C-1060	90p	OR157	100p
BA159	7p	B0698	45p	BU206	100p	TIP326	42p	BY247	20p	PCF844	100p	CA-3050	110p	LA-5151	120p	STK-480	740p	TD-2046	100p	25C-1060	90p	OR158	100p
BB101	13p	B0699	45p	BU206	100p	TIP327	42p	BY248	20p	PCF845	100p	CA-3051	110p	LA-5152	120p	STK-481	740p	TD-2047	100p	25C-1060	90p	OR159	100p
BB103	13p	B0700	45p	BU206	100p	TIP328	42p	BY249	20p	PCF846	100p	CA-3052	110p	LA-5153	120p	STK-482	740p	TD-2048	100p	25C-1060	90p	OR160	100p
BB158	24p	B0701	45p	BU206	100p	TIP329	42p	BY250	20p	PCF847	100p	CA-3053	110p	LA-5154	120p	STK-483	740p	TD-2049	100p	25C-1060	90p	OR161	100p
BB205B	24p	B0702	45p	BU206	100p	TIP330	42p	BY251	20p	PCF848	100p	CA-3054	110p	LA-5155	120p	STK-484	740p	TD-2050	100p	25C-1060	90p	OR162	100p
BC107	8p	B0703	45p	BU206	100p	TIP331	42p	BY252	20p	PCF849	100p	CA-3055	110p	LA-5156	120p	STK-485	740p	TD-2051	100p	25C-1060	90p	OR163	100p
BC108	8p	B0704	45p	BU206	100p	TIP332	42p	BY253	20p	PCF850	100p	CA-3056	110p	LA-5157	120p	STK-486	740p	TD-2052	100p	25C-1060	90p	OR164	100p
BC109	8p	B0705	45p	BU206	100p	TIP333	42p	BY254	20p	PCF851	100p	CA-3057	110p	LA-5158	120p	STK-487	740p	TD-2053	100p	25C-1060	90p	OR165	100p
BC109C	8p	B0706	45p	BU206	100p	TIP334	42p	BY255	20p	PCF852	100p	CA-3058	110p	LA-5159	120p	STK-488	740p	TD-2054	100p	25C-1060	90p	OR166	100p
BC115	10p	B0707	45p	BU206	100p	TIP335	42p	BY256	20p	PCF853	100p	CA-3059	110p	LA-5160	120p	STK-489	740p	TD-2055	100p	25C-1060	90p	OR167	100p
BC118	11p	B0708	45p	BU206	100p	TIP336	42p	BY257	20p	PCF854	100p	CA-3060	110p	LA-5161	120p	STK-490	740p	TD-2056	100p	25C-1060	90p	OR168	100p
BC140	20p	B0709	45p	BU206	100p	TIP337	42p	BY258	20p	PCF855													



## £1 BAKERS DOZEN PACKS

Price per pack is £1.00.\* Order 12 you may choose another free. Items marked (sh) are not new but guaranteed ok.

1. 5 - 13 amp ring main junction boxes
2. 5 - 13 amp ring main spur boxes
3. 5 - surface mounting light switches
4. 4 - in flex line switches with neons
9. 2 - mains transformers with 6V 1A secondaries
10. 2 - mains transformers with 12V 1/2A secondaries
11. 1 - extension speaker cabinet for 6 1/2" speaker
12. - glass reed switches
17. 1 - ultrasonic transmitter and 1 receiver with circuit
19. 2 - light dependent resistors
25. 4 - water switches - 6p 2 way, 4p 3 way, 2p 6 way, 2p 5 way, small one hole fitting and good length 1/4 spindle your choice
28. 1 - 6 digit counter mains voltage
30. 2 - Nicad battery chargers
31. 1 - key switch with key
32. 2 - aerosol cans of ICI Dry Lubricant
34. 48 - 2 metre lengths colour-coded connecting wire
39. 1 - long and medium wave tuner kit
41. 8 - rocker switch 10 amp mains SPST
45. 1 - 24 hour time switch mains operated (sh)
49. 10 - neon valves - make good night lights
50. 2 - 12V DC or 24V AC, 3 CO relays
51. 1 - 12V 2 CO miniature relay very sensitive
52. 1 - 12V 4 CO miniature relay
55. 1 - locking mechanism with 2 keys
56. 1 - miniature selector with circuit for electric jigsaw puzzle
60. 5 - ferrite rods 4" x 5/16" diameter aerials
61. 1 - Mullard thyristor trigger module
66. 1 - magnetic brake - stops rotation instantly
67. 1 - low pressure 3 - level switch can be mouth operated
69. 2 - 25 watt pots 8 ohm
70. 2 - 25 watt pots 1000 ohm
71. 4 - wire wound pots - 18, 33, 50 and 100 ohm your choice
77. 1 - time reminder adjustable 1-60 mins clockwork
85. 1 - mains shaped pole motor 3/4" stack - 1/4 shaft
89. 1 - mains motor with gear box 1 rev per 24 hours
91. 2 - mains motors with gear box 16 rpm
96. 1 - thermostat for fridge
98. 1 - motorised stud switch (s.h.)
101. 1 - 2 1/2 hours delay switch
102. mains PSU 9V
103. 1 - mains power supply unit - 6V DC
104. 1 - mains power supply unit - 4 1/2V DC
107. 1 - 5" speaker size radio cabinet with handle
112. 1 - heating pad 200 watts mains
114. 1 - 1W amplifier Mullard 1172
115. 1 - wall mounting thermostat 24V
118. 1 - leak effect extension 5" speaker cabinet
120. 2 - p.c. boards with 2 amp full wave and 17 other recs
121. 4 - push push switches for table lamps etc.
122. 10 - mtrs twin screened flex white p.v.c. outer
125. 25 - clear plastic lenses 1 1/4 diameter
127. 4 - pilot bulb lamp holders metal clip on type
128. 10 - very fine drills for pcbs etc.
129. 4 - extra thin screw drivers for instruments
132. 2 - plastic boxes with windows, ideal for interrupted beam switch
134. 10 - model aircraft motor - require no on/off switch, just spin to start
142. 10 - 4BA spanners 1 end open, other end closed
145. 2 - 4 reed relay kits 3V coil normally open or c/o if magnets added
146. 20 - pilot bulbs 6.5V 3A Philips
154. 1 - 12V drip proof relay - ideal for car jobs
155. 3 - varicap push button tuners with knobs
169. 4 - short wave air spaced trimmers 2-30f
172. 10 - 12V 6W bulbs Philips m.e.s.
178. 3 - oblong amber indicators with lipnuts 12V
180. 6 - round amber indicators with neons 240V
181. 100 - p.v.c. grommets 3/8 hole size
182. 1 - short wave tuning condenser 50 pf with 1/4" spindle
184. 1 - three gang tuning condenser each section 500 pf with trimmers and good length 1/4" spindle
188. 1 - plastic box sloping metal front, 16 x 95mm average depth 45mm
193. 6 - 5 amp 3 pin flush sockets brown
195. 5 - B.C. lampholders brown bakelite threaded entry
196. 1 - In flex simmerstat for electric blanket soldering iron etc.
197. 2 - thermostats, spindle setting - adjustable range for ovens etc.
199. 1 - mains operated solenoid with plunger 1" travel
200. 1 - 10 digit switch pad for telephones etc.
201. 8 - computer keyboard switches with knobs, pcb or vero mounting
211. 1 - electric clock mains driven, always right time - not cased
216. 1 - stereo pre-amp Mullard EP9001
232. 12 - 12V solenoids, small with plunger
236. 1 - mains transformer 9V 1 amp secondary C core construction
241. 1 - car door speaker (very flat) 6 1/2" 15 ohm made for Radiomobile
242. 2 - speakers 6" x 4" 4 ohm 5 watt made for Radiomobile
243. 2 - speakers 6" x 4" 16 ohm 5 watt made for Radiomobile
244. 1 - mains motor with gear-box very small, toothed output 1 rpm
245. 4 - standard size pots, 1/2 meg with do switch
249. 1 - 13A switched socket on double plate with fused spur for water heater etc.
266. 2 - mains transformers 9V 1/2A secondary split primary so ok also for 115V
267. 1 - mains transformers 15V 1A secondary p.c.b. mounting
291. 1 - ten turns 3 watt pot 1/4 spindle 100 ohm
296. 3 - car cigar lighter socket plugs
298. 2 - 15 amp round pin plugs brown bakelite
300. 1 - mains solenoid with plunger compact type
301. 10 - ceramic magnets Mullard 1" x 3/8 x 5/16
303. 1 - 12 pole 3 way ceramic wave charge switch
304. 1 - stereo amp 2W per channel
305. 1 - tubular dynamic microphone with desk rest
308. 1 - T.V. turret tone (black & white T.V.)
310. 2 - oven thermostats
313. 5 - sub miniature micro switches
316. 1 - round pin kettle plug with moulded on lead
453. 2 - 2 1/2in. 60ohm loudspeakers
454. 2 - 2 1/2in. 8ohm loudspeakers
463. 1 - mains operated relay with 2 sets c/o contacts
464. 2 - gaskets resin filler/sealer with cures
465. 3 - 5A round 3 pin plugs will fit item 193
466. 4 - 7 segment l.e.d. displays
470. 4 - pc boards for stripping, lots of valuable parts
473. 1 - 5" 4ohm speaker with built in tweeter Radio mobil
480. 1 - 3A double pole magnetic lift, saves repairing fuses
498. 4 - 1000uf 25V axial electrolytic capacitors

## MULLARD UNILEX AMPLIFIERS

We are probably the only firm in the country with these now in stock. Although only four watts per channel, these give superb reproduction. We now offer the 4 Mullard modules - i.e. Mains power unit (EP9002) Pre amp module (EP9001) and two amplifier modules (EP9000) all for £6.00 plus £2 postage. For prices of modules bought separately see TWO POUNDERS.

## CAR STARTER/CHARGER KIT

Flat Battery! Don't worry you will start your car in a few minutes with this unit - 250 watt transformer 20 amp rectifiers, all parts with data £15 case £4 p&p £2.



## VENNER TIME SWITCH

Mains operated with 20 amp switch. One on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95 without case, metal case - £2.95, adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

Ex-Electricity Board. Guaranteed 12 months.

## SOUND TO LIGHT UNIT



Complete kit of parts of a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form.

## 12 volt MOTOR BY SMITHS

Made for use in cats, etc. these are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle. 1/10 hp £3.45 1/8 hp £5.75. 1/6 hp £7.50

## 25A ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. A beautiful unit at £2.50

## THIS MONTH'S SNIP

3" floppy disc drive unit plug in and with all electronics. Japanese made, brand new. We are told that this is a standard replacement in many Amstrad and other popular computers, and we supply with technical information. Special snip price £27.50 including post and VAT.

## MAKING SUNBEDS?

CHOKE AND STARTER for 6" 100uVa tube £2, post £1 for 1 or 50p each in quantity. TUBE HOLDERS Canopy type spring loaded, 4 pairs for £1, 100 pairs £20, 1,000 pairs £150, post paid.

400 Watt Mains Isolation Transformer 230 volts in 230 volts out. Supplementary 10 volt winding for voltage adjustments. Toroidal construction makes it most compact. Regular price £40. Our price only £10.00 + £2 post.

## FANS & BLOWERS

Woods extractors 5" £5 + £1.25 post. 6" £6 + £1.50 post 4" x 4" Muffin equipment cooling fan 115V £2.00 4" x 4" Muffin equipment cooling fan 230/240V £5 5" Planair extractor £5.50 9" Extractor or blower 115V supplied with 230 to 115V adaptor £9.50 + £2 post. All above are ex computers but guaranteed 12 months. 10" x 3" Tangential Blower. New. Very quiet - supplied with 230 to 115V adaptor on use two in series to give long blow £2.00 + £1.50 post or £4.00 + £2.00 post for two.

## IONISER KIT

Refresh your home, office, shop, work room etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included. £9.50 plus £2.00 post.

## TELEPHONE BITS

Master sockets (has surge arrestor - ringing condenser etc) and takes B.T. plug ..... £3.95 Extension socket ..... £2.95 Dual adaptors (2 from one socket) ..... £3.95 Cord terminating with B.T. plug 3 metres ..... £2.95 Kit for converting old entry terminal box to new B.T. master socket, complete with 4 core cable, cable clips and 2 BT extension sockets ..... £11.50

## MINI MONO AMP

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.50 each, or 13 for £12.00



## J & N BULL ELECTRICAL (T)

250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QT

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £20 add £1 service charge. Monthly account orders (min £20) accepted from schools and public companies. Access & Bcard orders accepted. Brighton 0273 734648. Bulk orders: write for quote

## OVER 400 GIFTS YOU CAN CHOOSE FROM

There is a total of over 400 packs in our Baker's dozen range and you become entitled to a large free gift with each dozen pounds you spend on these packs. A classified list of these packs and our latest 'News Letter' will be enclosed with your goods, and you will automatically receive our next news letter.

## £2 POUNDERS\*

- 2P2 - Wall mounting thermostat, high precision with mercury switch and thermometer
- 2P3 - Variable and reversible 8-12V PSU for model control
- 2P4 - 24 volt psu with separate channels for stereo made for Mullard UNILEX
- 2P6 - 100W mains to 115V auto-transformer with voltage tappings
- 2P8 - Mains motor with gear box and variable speed selector. Series wound so suitable for further speed control
- 2P9 - Time and set switch. Boxed, glass fronted and with knobs. Controls up to 15 amps. Ideal to program electrical heaters
- 2P10 - 12 volt 5 amp mains transformer - low volt winding on separate bobbin and easy to remove to convert to lower voltages for higher currents
- 2P12 - Disc or Tape precision motor - has balanced rotor and is reversible 230V mains operated 1500 rpm
- 2P14 - Mug Stop kit - when thrown emits piercing swawk
- 2P15 - Interrupted Beam kit for burglar alarms, counters, etc.
- 2P17 - 2 rev pr minute mains driven motor with gear box, ideal to operate mirror ball
- 2P18 - Liquigas shut off valve mains solenoid operated
- 2P19 - Disco switch-motor drives 6 or more 10 amp change over micro switches supplied ready for mains operation
- 2P20 - 20 metres extension lead, 2 core - ideal most Black and Decker garden tools etc.
- 2P21 - 10 watt amplifier, Mullard module reference 1173
- 2P22 - Motor driven switch 20 secs on or off after push
- 2P24 - Clockwork operated 12 hour switch 15A 250V with clutch
- 2P26 - Counter resettable mains operated 3 digit
- 2P27 - Goodmans Speaker 6 inch round 8 ohm 12 watt
- 2P28 - Drill Pump - always useful couples to any make portable drill
- 2P31 - 4 metres 98 way interconnecting wire easy to strip
- 2P32 - Hot Wire amp meter - 4 1/2 round surface mounting 0-10A - old but working and definitely a bit of history
- 2P34 - Solenoid Air Valve mains operated
- 2P38 - 280 R.P.M. Gearing Mains Motor 1" stack quite powerful, definitely large enough to drive a rotating aerial or a tumbler for polishing stones etc.
- 2P43 - Small type blower or extractor fan, motor inset so very compact, 230V
- 2P46 - Our famous drill control kit complete and with prepared case
- 2P47 - Telephone ringing unit reduces mains to 50 volts and changes frequency from 50 hz to 25 hz to give night ringing tone
- 2P49 - Fire Alarm break glass switch in heavy cast case
- 2P51 - Stereo Headphone amplifier, with pre-amp
- 2P55 - Mains motor, extra powerful has 1 1/2" stack and good length of spindle
- 2P62 - 1 pair Goodmans 15 ohm speakers for Unilox
- 2P64 - 1 five bladed fan 6 1/2" with mains motor
- 2P66 - 1 2kw tangential heater 115v easily convertible for 230V
- 2P67 - 1 12v-0-12v 2 amp mains transformer
- 2P68 - 1 15v-0-15v 2 amp mains transformer
- 2P69 - 1 250v-0-250v 60 mA & 6.3v 5A mains transformer + £1 post
- 2P70 - 1 E.M.I. tape motor 20 amp speed and reversible
- 2P72 - 1 115v Muffin fan 4" x 4" approx. ex computer
- 2P75 - 1 2 hour timer, plugs into 13A socket
- 2P82 - 9v-0-9v 2 amp mains transformer
- 2P84 - Wooden board with press keys for telephone redialer
- 2P85 - 20v-0-20v 1/2A Mains transformer
- 2P88 - Sangamo 24 hr time switch 20 amp S.H.
- 2P89 - 120 min. time switch with knob
- 2P90 - 90 min. time switch with edgebore engraved controller
- 2P95 - 13A socket on satin chrome plate very superior G.E.C.
- 2P97 - mains transformer 24V 2A uplight mounting
- 2P98 - 20m 4 core telephone cable, white outer
- 2P99 - 500 hardened pin type staples for telephone cable
- 2P101 - mains transformer 15v 4A uplight mounting
- 2P105 - capillary type thermostat adjustable for air temperatures with 10A c/o switch
- 2P107 - membrane keyboard, telephone type superior plug in type
- 2P108 - mains motor with gear box giving 110rpm
- 2P109 - 5" wide black adhesive pvc tape 33m, add £1 post if not collecting
- 2P111 - ITT line output unit
- 2P112 - 6 volt 200MA Voltage regulated PSU for 13 amp socket
- 2P113 - 9 volt 200MA Voltage regulated PSU for 13 amp socket
- 2P114 - 12 volt 200MA Voltage regulated PSU for 13 amp socket
- 2P116 - FM front end with tuning capacitor and F.M. circuitry
- 2P118 - 30rpm mains motor with gearbox
- 2P119 - Under carpet switch mat for burglar alarm etc.

## LIGHT CHASER KIT

Motor driven switch bank with connection diagram, used in connection with 4 sets of X-mas lights makes a very eye catching display for home, shop or disco, only £5 rel 5P56.

## £5 POUNDERS\*


- 5P1 - 12 volt submersible pump complete with a tap which brought over the basin switches on the pump and when pushed back switches off, an ideal caravan unit.
- 5P2 - Sound to light kit complete in case suitable for up to 750 watts.
- 5P3 - Silent control ultra sonic transmitter and receiver kit, complete
- 5P6 - 12V alarm bell with heavy 6" gong, suitable for outside if protected from direct rainfall. Ex GPO but in perfect order and guaranteed.
- 5P15 - Uniselecter 5 pole 25 way 50 volt coil
- 5P18 - motor driven water pump as fitted to many washing machines
- 5P20 - 2 kits, matchbox size, surveillance transmitter and FM receiver
- 5P23 - miniature (appr. 2 1/2" wide) tangential blow heater, 1.2kw
- 5P24 - 1/4hp motor, ex computer, 230v, mains operation 1450rpm. If not collect add £3 post
- 5P25 - special effects lighting switch. Up to 6 channels of lamps can be on or off for varying time periods
- 5P27 - cartridge player 12v, has high quality stereo amplifier
- 5P28 - gear pump, mains motor driven with iniel and output pipe connectors
- 5P32 - large mains operated push or pull solenoid. Heavy so add £1.50 post
- 5P34 - 24v 5A toroidal mains transformer
- 5P35 - mcdia board from telephone auto dialler, complete with keypad and all IC's
- 5P41 - 5" extractor fan, very quiet runner sh, gntd 12 mths.
- 5P45 - pack of 6 cooker clock switches
- 5P48 - telephone extension bell in black case, ex-GPO
- 5P50 - box of 20 Infra red quartz glass enclosed 360w heating elements
- 5P51 - 20w auto transformer 230v to 115v toroidal
- 5P52 - mains transformer 26v 10A uplight mounting, add £2 post
- 5P54 - mains motor with gear box, final speed 5rpm
- 5P58 - Amstrad stereo tuner FM and LM and S. AM
- 5P60 - DC Muffin type fan 18w to 27v, only 3w
- 5P61 - drill pump mounted on frame, coupled to mains motor
- 5P62 - 2 1/2kw tangential blow heater, add £1.50 post if not collecting
- 5P69 - Fluorescent light box for viewing PCB's or can be used for shop window sign

ADD £1 POST
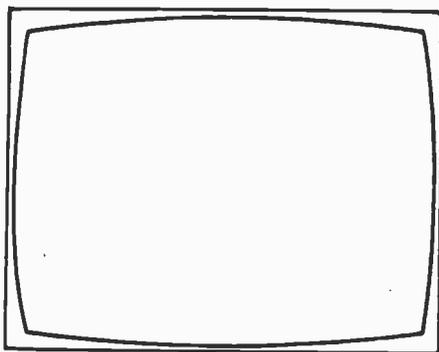
## TRANSFORMER IN WATERPROOF METAL CASE

24V 5A output. Ideal for garden lighting or to operate pond pump etc. Case has cable glands for mains in and low voltage output leads. Price £5 plus £1 post, rel 5P88.





# TELEVISION

## Trade Wars, Phoney Wars

There are growing signs of trade wars, particularly in the consumer electronics field, though one can't help but feel that they will turn out to be phoney wars. The start of the present skirmishes was the dispute between the USA and Japan over semiconductor production, pricing and sales. Dissatisfied with the Japanese response to claims of chip dumping, in part through intermediate markets, the US government slapped a 100 per cent duty increase on a range of Japanese goods including colour TV sets and computers. Concerned about the growing trade deficit between the European Community and Japan, and the possibility of a switch of Japanese exports from the USA to Europe as a result of the US government's duty increases, the EC has threatened to do much the same (no suggested figure this time, the phrase is "punitive tariffs"). The problem here is that the EC's trade deficit with Japan is now running at an annual figure of \$21 billion and shows no sign of any decrease.

One can appreciate the concern of Western governments and industrialists over these trade imbalance problems. It's less easy to see what can or indeed should be done about them. Let's first consider the Japanese situation. The country after all has its own problems, stemming in particular from its geographical constraints. Some 70 per cent of Japanese land is usable neither for industry nor for agriculture, consisting largely of mountains. The country's large population is squeezed into a small land area with little by way of natural resources. To export something or other is the only way of survival given this situation. In short, the country can support itself only by the export of saleable goods. There have been complaints that this is too much of a one way affair, that the Japanese don't buy foreign products and that their markets are not open to foreign manufacturers. But since they do so well themselves it seems a bit pointless to expect them to import manufactured goods on any scale.

In theory it shouldn't matter if Japan has a whopping surplus in the trade of manufactured goods since there are deficits elsewhere - in the need to import fuel and raw materials, and in a traditional though growingly less important reliance on the use of bought in services (banking, insurance, etc.). But of course Japan's income has steadily advanced because of the value added nature of its exports. The result has been growing monetary imbalances in favour of Japan. But what's to be done with this income? You can invest only so much of it in research and development, and the Japanese have a great deal left over. In recent years it's been going into funding the USA's government and trading deficits. Investing in dollar assets that depreciate is a mug's game however, and the Japanese have already lost a fortune in this way. They do it for want of an alternative but are aware of the nature of the problem. Hence the growing tendency of Japanese manufacturers to establish overseas production, not only in low-cost countries around the Pacific basin but in the Americas and Europe. This isn't done out of any particular altruism but because, to quote a phrase, there is no alternative. So far as the consumer is concerned, instead of getting his nice Japanese goods from Japan they come from local plants. And this means, amongst other things, that some local employment is generated.

The growing Japanese predominance in certain spheres of production is naturally of concern to industrialists elsewhere. But you can't really blame the Japanese for it nor expect them to do very much about it. The idea that they should "open up their markets" etc. is really rather futile. Since they can make most of what they want as well or better than others, exactly what is to be sold to them? The answer to this usually seems to be scotch, rollers, smoked salmon and suchlike. That's hardly a solution to the problem.

The Japanese have got where they are by working out their production plans on a global basis, assisted by a benign domestic economic climate (ready finance at low rates of interest and little by way of industrial problems). Others could have done much the same. But traditionally entrepreneurialship in the west has consisted of seizing opportunities as they arise and making the most of them. And you can hardly develop a long-term strategy when, as for so many years in the UK, you have to operate in the context of a roller-coaster, stop-go approach to economic management.

There is, when you consider it, nothing particularly special about the Japanese approach to industry other than the fact that they get their act together rather well. Where does this leave the rest of us right now? We can't undo Japanese success nor wish their industries away - and the consumer would soon feel the deprivation of not having ready access to the fruits of Japanese production. All we can do is to learn the lessons that are clearly there and try to do a bit better ourselves. The long overdue dollar depreciation against the yen, starting in late 1985, has had severe effects on the profitability of Japanese industry. You can't indefinitely maintain unrealistic exchange rates, though the markets don't operate with the efficiency one would wish. From the longer term view it already looks as though the trade imbalance problem is no longer the insoluble one it once seemed. Meanwhile the calls for Japan to import more and expand its economy, and the threats of sanctions and tariffs, are beginning to look like so much posturing.

The problem of Japan's ability to run value-added industries and benefit from substantial research and development work remains. This is not the sort of thing that can be changed overnight. In the short term the only practical solution lies in greater collaboration and more joint-venture projects.

### EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 585.

### ADVERTISEMENT MANAGER

David W.B. Tilleard  
01-261 6671

### SECRETARY

Janet Reeve  
01-261 6671

### CLASSIFIED ADVERTISEMENTS

Pat Bunce  
01-261 5942

### ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey  
01-261 6035

### SUBSCRIPTION ENQUIRIES

0444 459 188

### COVER PHOTO

Our cover photo this month shows a picture-in-picture display on a Sanyo Model CBP2146. An article on PIP circuitry will appear in a later issue.

# TX9 Thyristor PSU Servicing

Gordon Haigh

Later versions of the Ferguson TX9 chassis (PC1044 main panel) use a chopper power supply, with all the advantages this brings, such as lower component count, reduced weight and simplified operation. The circuitry will also in general provide automatic protection in the event of an overload or other malfunction without necessarily blowing the mains fuse. With the earlier thyristor type of power supply (sets with main panel types PC1001 or PC1040) this is not so – any distressful situation in the power supply is likely to blow mains fuse FS1. This article deals with the earlier type of power supply circuit since this is the one that's more likely to give you problems. The complete circuit of the earliest version (PC1001 panel) is shown in Fig. 1: there were several minor modifications in the PC1040 version and in this the diodes have D instead of W reference numbers, the transistors have TR instead of VT reference numbers, while the thyristors have CSR instead of SCR reference numbers.

## Quick Checks

The block diagram in Fig. 2 shows how the various voltage supplies are distributed through the set. All these voltages as well as the 22-26kV e.h.t. depend on the power supply producing the correct stabilised h.t. of 115V at the output side of R197. A 120V tuning supply is tapped from the other side of R197. It's a relatively easy task to do some quick spot checks on these voltages – all readings shown are taken with respect to chassis. Chart 1 gives a quick guide to supply line faults.

Chart 2 shows a more detailed approach to adopt when the symptoms are a dead set with FS1 intact. Note that the line oscillator will not receive its start-up supply if the line driver transistor VT67 has failed – this is a weak link. If R223 is burnt the replacement should be a 470Ω, 5%,

0.5W fusible type and with this value fitted R216 must be 1kΩ, 5% 0.5W.

## Mains Fuse Blown

We come next to the bit we all like best – wondering whether there will be enough 1.6AT fuses in stock. It's important to appreciate that the circuit incorporates a crowbar thyristor (SCR2) which fires when the h.t. exceeds 130V or the current demand is excessive. As a starter, follow the procedure given in Chart 3.

A severely blackened fuse suggests that the crowbar trip has operated. A replacement fuse may restore normal operation, but for only say a couple of days – this prompted one contributor (see *Television* July 1984) to design an electronic circuit breaker. Fortunately Ferguson have compiled another fault-finding procedure – see Chart 4 – using a 2A thermal cutout. This second approach should be used when the first has been exhausted or proves to be inconclusive. A 100μF capacitor and 3A fuse are also required when doing battle in this way with the more sticky or subtle faults.

Intermittent fuse blowing should direct attention to zener diodes W85 and W83, transistor VT66 and the crowbar thyristor SCR2. The regulating thyristor SCR1 can blow the fuse without measuring short-circuit, so as with any suspects it's best to fit a new replacement part, if only for elimination purposes to save time. R184 (220kΩ) in the set-115V control network can go high in value to cause fuse blowing.

Ferguson state that if EW modulator diode W96 goes short-circuit the crowbar thyristor will fire, blowing FS1, and that this fault can damage VT72/3/4 and R251 in the EW modulator drive circuit.

The degaussing thermistor must be replaced with the

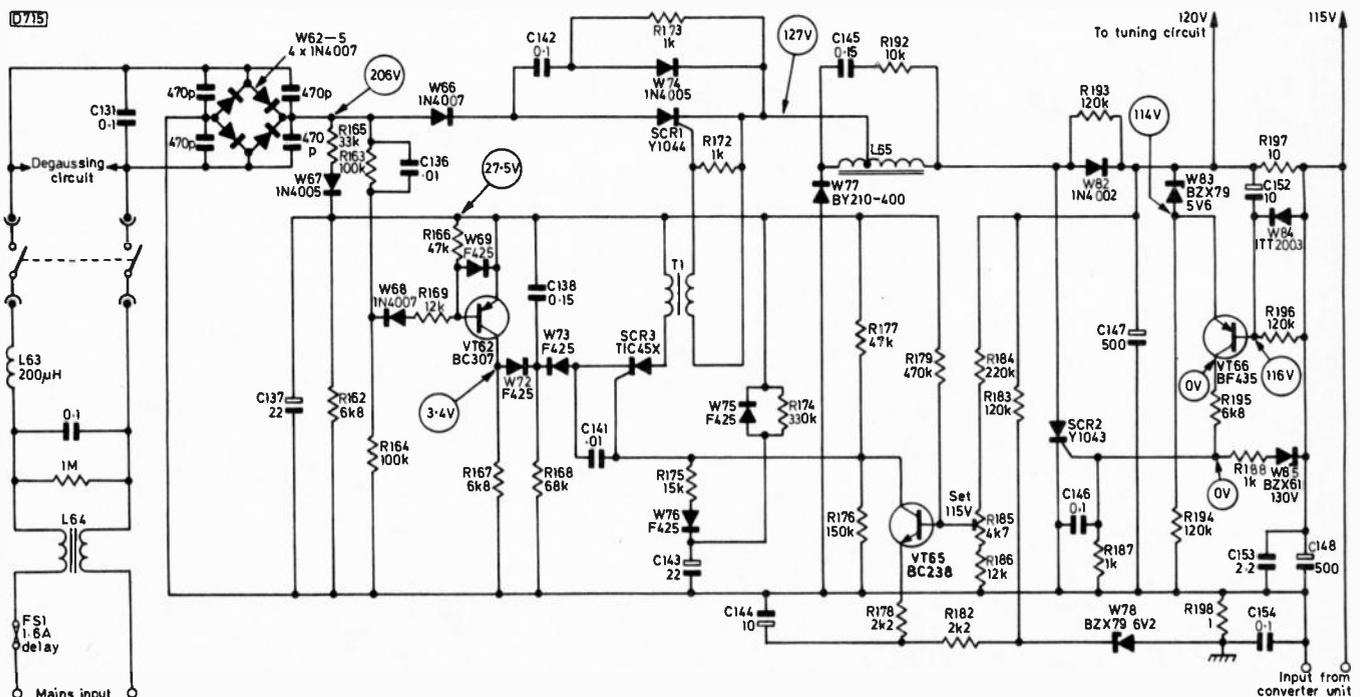


Fig. 1: Thyristor power supply circuit used in the initial version of the Ferguson TX9 chassis (main panel PC1001).

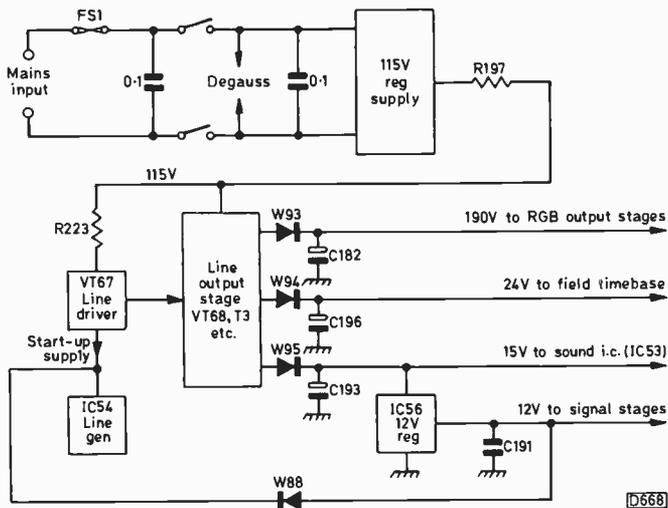


Fig. 2: Block diagram showing the origin of the various supply lines in the TX9 chassis.

correct type – the wrong type can go up in smoke, with perhaps fuse failure.

If SCR1 goes short-circuit the momentary rise in h.t. before FS1 blows can damage the following components: the line output transistor VT68, the 24V rectifier W94, W103 and the TDA1170S chip in the field timebase, the 15V supply reservoir capacitor C193 and the 12V regulator chip IC56.

There are several official modifications for dealing with the problem of random mains fuse blowing. These are as follows. PC1001 panel: (1) change C146 to 22 $\mu$ F, 16V; (2) change R223 to 470 $\Omega$  and R216 to 1k $\Omega$  – these two changes must be implemented simultaneously (see above); (3) change the line driver transistor VT67 to the correct Ferguson approved type (part no. 00TR-029-701-1TG). PC1001/1040 panels: (4) change L65 to the later type; (5) change W85 to the correct Ferguson approved type (part no. 02V4-718); (6) change C134/5 to 0.001 $\mu$ F, 1kV.

### Displaced Picture

A problem that sometimes arises with these sets is horizontal displacement of the picture to the left. The cause is either R212 or R217 (both 220k $\Omega$ ) in the line generator feedback loop going high in value or open-circuit. Originally carbon-film resistors were used in these positions. They were changed to metal glaze resistors in later production.

### Set's Label

Finally, don't forget the label pasted in the set. It carries enough information to locate and carry out quite a few preset adjustments, which is helpful in the field.

### Chart 1: Supply line checks.

In the event of a dead set, can you hear the line start up? If not check for 115V at R197 then refer to Charts 2-4. If the line start up is audible, is there a slight buzz from the speaker? If there is, check for 12V at C191 – if this supply is absent suspect IC56.

For no sound check whether 15V is present at the cathode of W95. If o.k. check R156 and IC53.

For field collapse with normal sound check for 24V at the cathode of W94. If o.k. suspect IC55 stage.

If there's a bright raster with flyback lines and normal sound check for 190V at C182. If o.k., suspect IC52.

### Chart 2: Set dead, FS1 intact.

Check the voltage at the cathode of SCR1.

If 120V, check whether R223 is burnt. If so check IC54 and VT67. If not check W82, R197, VT67 and VT68 (could be open-circuit).

If the voltage at the cathode of SCR1 is approximately 12.5V check W78.

If there's 0.2V at the cathode of SCR1, check for about 210V at its anode. If there's zero voltage here check the mains bridge rectifier, W66 (if in series with SCR1) and the mains input. If the 210V supply is present check the a.c. voltage at the anode of SCR3, via an 0.1 $\mu$ F capacitor. If the reading is 0.2V a.c. check SCR1 and T1. If the reading is 0V check for 30V at the emitter of VT62. If the reading here is approximately 20V VT62 is short-circuit. If the reading is 0V check W67 for being open-circuit and C137 for being short-circuit. If the 30V is present, check VT65, C138, C143, C144, W73 and SCR3.

### Chart 3: Dead set, FS1 blown, Method 1.

Switch off at the mains. Replace FS1. Turn R185 fully anti-clockwise (minimum h.t.) and the volume control to the half-way point. Switch on.

If the sound comes up then the fuse blows check VT62 and VT65.

If there's sound but no raster, check the 115V line at R197: adjust R185 to increase the h.t. slowly to exactly 115V. If FS1 blows go to Method 2.

If FS1 blows, disconnect the mains lead and fit a replacement fuse. Disconnect the degaussing coil. Then check the resistance across the mains lead both ways, using the middle ohms range.

If the reading is 1k $\Omega$  one way, check for shorted bridge rectifier diodes.

If the reading is 100k $\Omega$  both ways, check SCR1 for being short-circuit. If its resistance is greater than 1M $\Omega$  anode to cathode, check the resistance of SCR2 from anode to chassis (red lead to chassis, black to SCR2 anode).

Check SCR2 and W77 if the reading is a short-circuit.

If there's an initial short-circuit, rising to 20k $\Omega$  as C147/8 charge, check W93, W94 and W95 for being short-circuit and for shorts across the 15V and 24V lines.

If the reading is 3-4k $\Omega$ , check VT67 for being short-circuit or for a short across the 190V line.

If the reading is 1k $\Omega$ , disconnect VT68's collector and re-measure. If the reading is still 1k $\Omega$  there's a short-circuit across the 115V supply. If the reading rises to greater than 20k $\Omega$ , check VT68.

### Chart 4: Dead set, FS1 blown, Method 2.

Switch off at the mains. Connect a 2A thermal cutout (as used in Thorn 3000/8000 series chassis) in series with the live side of the mains supply. Replace FS1 with a 3A fuse. Solder a 100 $\mu$ F capacitor across C143 to increase the slow-start action. Switch on.

If FS1 blows immediately, check W62-5, SCR1, C130, C131 and W72 for shorts.

If FS1 blows after a few seconds, switch off and reset the cutout. Monitor the voltage at the cathode of W82. Switch on. Note the voltage indicated by the meter before the cutout operates.

If above 115V, check VT65, VT62, W66, W69, W68, W72 and W78. The h.t. could be set too high.

If the reading is 50-100V, check W77, W83, W94 and W95 and for shorts across the 24V and 15V lines.

If the voltage is below 2V check W85, SCR2 and C147, and for a short across the 115V line.

If the reading is 5-15V, switch off and disconnect the collector of VT68. Reset the cutout and switch on. If the cutout holds, check VT68 and W96. If it operates, check C148, VT66 and for a short across the 190V line.

# Letters

## SERVICING CHARGES

I've been a regular reader of your magazine for some years now and find it a great help, — being self-employed, I have little time available to go on up-dating courses or anything of that sort. One thing bothers me however. There never seems to be any discussion on the subject of pricing repairs. Prices are often given in your test reports and other items relating to pieces of equipment, but when it comes to repair prices — nothing! Anyway, I'd like to start the ball rolling on this topic.

It's a fact that our trade has been adversely affected by retail discounting. Many small businesses have had to cut down on retail sales to such an extent that their main turnover now comes from servicing. Conversely, the discount merchants have their problems when it comes to servicing. They've got themselves a very poor reputation as a result of the poor wages they pay (how can they pay more when they make so little on sales?). Poor wages mean that they end up with substandard engineers. I'm not saying that all their engineers can be so described, but when I worked for two large discount houses some years ago I was disgusted with the quality of many of their engineers. It seems that the best engineers at such organisations have to be confined to benchwork — a good man is seldom sent out on housecalls. These discount firms tend to have a discount service. They are poorly organised and costs run high. It's not uncommon for them to charge over £25 for a call out.

Let's consider the possibilities this opens up for the smaller firm. I'm not suggesting that we enter into a price war with respect to call-out charges — it would be counter-productive to do so — but I feel that by being more efficient we can charge similar rates while making a better profit. We have two big advantages. First, we are local and know most of our customers on sight. Secondly we can be available more quickly and for more hours than the large groups.

I used to send customers packing when they came in carrying their Hinsho, hi-mo or Flymo come to that, but I then came to my senses. These people deserve all that comes their way. So I'll repair their equipment, but at a price: they are charged at a higher rate than I charge my faithful customers. I can hear you saying "what a rip-off merchant this man must be". Not so. Just think how often you have taken on unfamiliar equipment and found yourself losing money on the job. Now ask yourself what these customers have done for you. Don't think you will get them to buy from you as a result of your efforts — if you're lucky one in a hundred may come back to purchase something, and that's not good odds.

So down to charges. I feel that one must have a standard call-out charge, but with flexibility to allow for regular customers. Say £20 to £25. This should cover the first half hour spent in the customer's house. If the repair cannot be completed in that time it's probably better done in the workshop anyway. Charges for workshop repairs should again be in the region of £25 an hour. It makes no difference to costs whether a transistor radio or a VCR is being worked on — the overheads, wages and costs are all the same, so the charges should also be the same.

I find it advantageous to swap service information with

other small local businesses: we all help each other in this respect. Also, we don't criticise each other and we don't discount each other. In this way we find that there's a good living to be made for all of us. As a general rule in my town we all cooperate with each other and there's no backbiting to worry about.

When I suggested to a friend of mine in the next town that he should increase his prices he said he'd lose all his customers. Two years later he's doubled his prices and trebled his number of customers! In fact he's expanding in the service field and closing down his retail shop.

Let's face facts. We are keeping what must seem like the eighth wonder of the world in good condition and deserve payment to suit. I spend a lot of money on equipment, and pay my staff well. We have to be qualified to a high standard not only in being able to diagnose and repair faults in electronic equipment but also in rally driving, plumbing, joinery, building, bottany and coffee sampling! We are expected to listen to the customer's family history and smile whilst attending to a set next to a bloody great fire while the kids empty the tool kit, the dog gets in the way and the customer wants to make you a cuppa. All you want to do is to get out as fast as you can! As engineers, we must surely be worth more than an electrician or a plumber, a motor mechanic or even a refuse disposal man.

In conclusion, if we are to pay ourselves a respectable wage for a respectable trade, we must charge respectable prices.

D. Tasker,  
Harrogate, Yorkshire.

## CHECKING CRT HEATER SUPPLIES

J. LeJeune's novel approach to the problem of assessing c.r.t. heater voltage when the supply is non-sinusoidal (c.r.t. heater voltage checker, January 1987 issue) interested me for a couple of reasons.

First, I had occasion in the past to tackle this problem and found a simple solution: I used a car dashboard type voltmeter. This type of movement — in common with others used on the instrument panel — has as its basis a bimetal strip which is heated by a coil of resistance wire (see Fig. 1). The strip is coupled to the pointer in such a way that its small displacement is amplified. This displacement is a function of the true r.m.s. value of the current flowing in the coil, irrespective of its waveform. The bimetal strip is U shaped, with the winding on one leg only. The direction of displacement in each leg due to the ambient temperature is such that these displacements cancel at the pointer coupling. Thus the meter registers

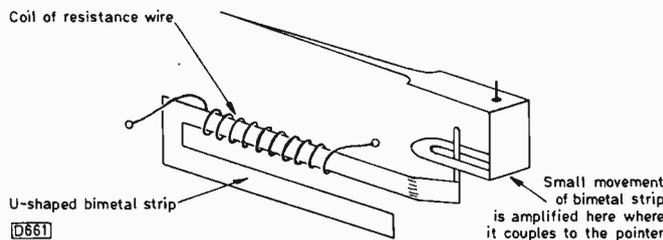


Fig. 1: Basic mechanism of a car instrument panel meter.

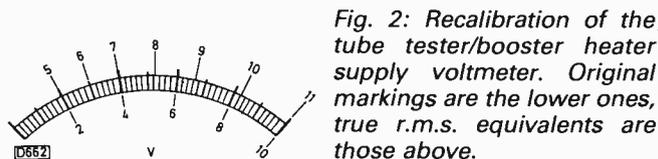


Fig. 2: Recalibration of the tube tester/booster heater supply voltmeter. Original markings are the lower ones, true r.m.s. equivalents are those above.

# Supertel

## BUY DIRECT

### TOP QUALITY EX-RENTAL TV'S & VIDEOS

#### ALL THE BIG NAME BRANDS!

 **Panasonic** 

**HITACHI SONY  
TOSHIBA PHILIPS**

**SUPERB  
CHOICE  
OF  
ELECTRONIC  
VHS**


**AVAILABLE NOW!**

### DIRECT TO TRADE PRICES

### NATIONAL TRADE NETWORK


- 478-486 OLD KENT ROAD, LONDON SE1 TEL: (01) 232 0547
- 247-249 HIGH ROAD, TOTTENHAM N15 TEL: (01) 809 4866
- 221-225 WALTON ROAD, LIVERPOOL L4 4AJ TEL: (051) 207 1138
- 426A HELEN STREET, GOVAN, GLASGOW TEL: (041) 445 6566
- 618 GREAT HORTON ROAD, BRADFORD TEL: (0274) 502881

# Supertel

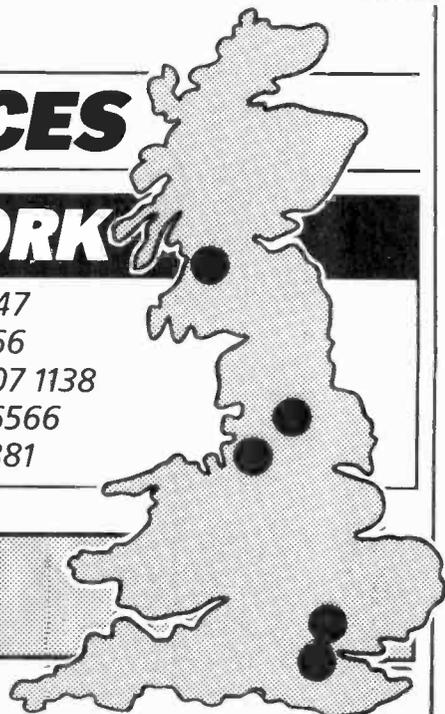
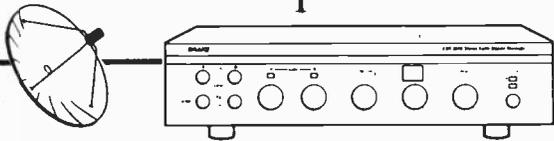
# DRAKE

The answer to your satellite TV questions.



Drake brings satellite TV down to earth. An exciting variety of television entertainment exists and the Drake line of satellite equipment will bring it into your home — EASILY and AFFORDABLY. Get on the road to expanding your entertainment horizon by seeing the Drake line TODAY!

Become a DRAKE SATELLITE DEALER and take advantage of our special dealer prices. We are the main importers and distributors for R.L. Drake, one of the largest USA manufacturers. Don't be misled by inferior products when you can sell the best. From only £495 + VAT (inc 10mts cable). Contact

## ALSTON-BARRY SATELLITE SERVICES

36 MILTON ROAD  
CAMBRIDGE. (0223) 69215

ALSO AT

32 BROAD STREET  
ELY (0353) 61462

TELEVISION AND VIDEOS AT REALISTIC PRICES FROM THE SPECIALISTS. LATE MODELS ALWAYS AVAILABLE WITH 100% CABINETS AND TUBES. ALL SETS READY FOR INSTANT INSTALLATION AND VIDEOS FULLY SERVICED.

**QUALITY AND RELIABILITY IS OUR AIM AT ALL TIMES.**

KT3 ..... from only £60  
K30 ..... from only £75  
CTX ..... from only £125  
K35 ..... from only £135

LATER MODELS ALSO AVAILABLE.

ELECTRONIC VIDEOS FROM ONLY £135 + VAT. MOST MAKES IN STOCK. FREE DELIVERY FOR SENSIBLE SIZED ORDERS

### UPDATING COURSES

HIGH PERCENTAGE OF PRACTICAL WORK INTENDED FOR QUALIFIED SERVICE ENGINEERS.

### VCR SERVICING

(3 WEEKS FULL TIME)

NEXT COURSES START ON

OCTOBER 12th & NOVEMBER 30th 1987 -

TUITION FEE £575

### MICROCOMPUTER SERVICING

(ONE WEEK FULL TIME)

NEXT COURSES START ON

JULY 20th, JULY 27th & AUGUST 3rd -

TUITION FEE £250

*Unemployed may be eligible for new JTS grant support.*

Further details from:

**LONDON ELECTRONICS COLLEGE**  
(VC Dept.), 20 Penywern Road, Earls Court,  
London SW5 9SU  
Tel: 01-373 8721

## CRICKLEWOOD ELECTRONICS LTD



**It's no secret...**

that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

### CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161

Telex: 91 4977



TV

only the difference in temperature between the legs due to the coil current.

The particular voltmeter I used had a coil resistance of around 400Ω and drew only 15mA at 6.3V. The original scale was marked from 6-17V. When this was carefully recalibrated at 1V intervals, using the bench power supply, it was found to start indicating at 5V. The one snag with this type of meter is that it's very slow to respond and has to be left connected for several seconds until the pointer finally settles.

It's possible to boost the heater of an ageing tube by introducing a turn of wire around the core of the line output transformer in series with the existing heater supply. By using a true r.m.s. meter you can then tailor the value of the series resistor in the supply to give a heater voltage in the region of 7.5V, a figure which shouldn't really be exceeded. If the extra turn is in the wrong direction the heater voltage will of course be reduced.

All this has made me aware of an oversight on my part – in my c.r.t. tester/booster article (February 1987). The heater voltmeter in this tester/booster measures the average voltage of a rectangular waveform. Now this is different from the r.m.s. value, which is what really counts. The difference is greatest when the voltage is low and comes closer to the r.m.s. value as it increases. The relationship between the two in this particular case is  $V_{rms} = \sqrt{V_{ave} \times 12}$ . Fig. 2 shows how the meter dial should look. With the unit as it stands tubes are tested and boosted at a higher voltage than that shown.

*Alan Willcox,  
Cardiff, South Glamorgan.*

### PORTABLE PUZZLE

A great number of traded-in monochrome portables fitted with the Thorn 1590 have come my way over the years. I find that the worst trouble is inability of the 11.6V regulator to stabilise. In some cases I've changed every component in the power supply and have even changed the line output transformer on the assumption that it might have been loading the supply, but all to no avail.

Have other readers experienced this difficulty? And would it, with hindsight, have been better to arrange for all the circuits to run off the 11.6V rail rather than having some of them run off the 25V boost rail?

*K.J. Treeby,  
Plymouth, Devon.*

### CUSTOMERS' DIAGNOSES

Although I've not been in the trade for as long as Colin Goodman (Letters, April) I've heard all those diagnoses from customers – and several others as well. In the event of an intermittent fault that clears as you arrive, it's "you've got the magic touch" or "it's like when you visit the dentist and your toothache goes" – if I'd had a quid for every time I've heard that one I'd be able to retire. Other customer clichés include "we didn't touch it, it just went like that" – what they mean is that the transmitter went off the air for ten seconds, in which time they twisted all the tuning knobs from ch. 21 to ch. 68.

Then there are the "famous names", rental customers who call in about ghosting whenever a tanker is anchored in the Solent, or for co-channel interference, and it's always the same – "it's never done it before", "our old set didn't do it", and "we don't get you out for nothing you

know". But the records show that engineers have spent enough time at these addresses to be almost able to set up residence there. Do such customers really expect engineers to believe them, especially when the same engineer calls each time, or do they think TV engineers have just swung down from the trees? "Famous names" can progress to become "really famous names": with these people you can be 90 per cent certain of what you'll find wrong (usually nothing) and what they'll say to you.

*Alfred Damp,  
Ryde, Isle of Wight.*

### HIGH-VOLTAGE FILAMENT VALVES

Your recent article on vintage mains supplies makes me wonder how many readers remember the OSDA-GANZ valves of the early thirties? If I recall correctly these valves ran their high-voltage filaments directly off d.c. mains supplies: you could read a book by the light they emitted.

*R.E.D. Mathews,  
Christchurch, Dorset.*

### PANASONIC U2 CHASSIS

Recently another Panasonic TC2205 (U2 chassis) came my way with a low-emission c.r.t. and an EW fault. The tube was changed, after removing the boost transformer from the circuit, and I then set about checking the electrolytics, four of which came away in my hand. I finally tackled the EW fault. The usual trouble-makers here are the BD237 EW modulator driver transistor Q753 and the 4.7Ω resistor R770 in its collector circuit. The resistor turned out to be faulty, but after replacing both these items the fault persisted. Further investigation revealed that there was only a slight negative voltage at the junction of the modulator diodes instead of the usual 12-15V. This led me to check the resistance across the lower diode, which gave a correct reading of 4.8kΩ – replacing both diodes made no improvement. In desperation I resorted to swapping all the components in the circuit, using those from an identical set. The faulty item turned out to be the last one changed – the loading coil L752. I hope this note will be useful to other readers.

*John L. Howard,  
Barnstaple, N. Devon.*

### NO MORE FUN?

Mr. Kendall's letter (March) took me back a few years further. I first became interested in electronics about sixty years ago, at the age of eight, when I built my first crystal set. I remember saving for weeks to buy a valve, and building a set which eventually had a loudspeaker made from an earphone with a paper cone attached to the diaphragm!

In 1948 I started on TV with a set much like Mr. Kendall's, only I had built a simple oscilloscope with a 3in. tube which provided the display. I remember watching the trade programmes in the mornings – Petula Clark was on one piece of film that appeared regularly, and an extract from William Walton's *Facade* also comes back.

When the *Wireless World* design appeared I set to work to build it. Lots of EF50s and wind not only your own r.f. coils but the scan coils and the line output transformer as well. A visit to Lisle Street, in those days a feast of radio junk shops and not, as now, Chinese food stores, produced a pre-war 9in. Mazda tube, new, for about £10 and

I was in business. The set was in advance of its time in some ways – flyback e.h.t. for example (though only about 5kV if I remember) – and with modifications gave yeoman service for about ten years, when the tube gave up. By then it had had a Haynes line output transformer and scan coils fitted and incorporated a regulated power supply of about 300mA at some 300V, black-level clamping, flywheel sync and lots of other things which were luxuries in those days. I still have the original hand-wound scan coils.

The set and its immediate successor gave me a lot of fun and entertainment, but I feel that the fun is no longer

there in the hobby. So much of what we do is now contained in little black chips. When you build something it's a matter of putting the right chips into the right places on the PCB, and unless there's a defective chip it works. Designing is now much more difficult for the amateur without a lot of reference books. I'm not against chips: I built the *Wireless World* teletext adaptor (around 100 chips!) and I also have a computer which I pull to pieces at intervals, but again it's mostly a matter of just plugging in chips!

*M.C. Matthews,  
Dorchester, Dorset.*

## The Super-VHS Specification

**Steve Beeching, T.Eng.**

It's almost ten years now since I saw the first VHS video cassette recorders – the JVC Model HR3300. Some of these early machines are still in service, having stood the test of time.

### Comparisons

In all VCR systems the luminance signal to be recorded is first frequency modulated on to an h.f. carrier. It's recorded on tape as the lower sideband of the spectrum produced by this f.m. process. Fig. 1 shows the signal spectra for various VCR systems, (a) standard VHS, (b) Beta super hi-band and (c) the new Super VHS (S-VHS). As you can see, the luminance signal bandwidth, and hence the picture resolution, depend on the extent of the lower sideband frequency spectrum that can be recorded on the tape.

The advent of the 8mm video system has led to claims that this will become the new domestic VCR standard. I don't agree with this, nor do I agree that Video-8 is significantly better than the standard VHS system. The Video-8 system has been able to take advantage of developments in video tape recording technology. What if the VHS system was to take advantage of these same developments? This is where the S-VHS system comes in.

In the past, certain Betamax machines gave rather better performance than their VHS contemporaries. This was basically because the Beta system's luminance carrier deviation is slightly wider at 3.8-5.2MHz than the standard VHS carrier deviation of 3.8-4.8MHz. Whilst this higher specification didn't increase the resolution much it did significantly reduce the video noise content. As a result, greater enhancement could be used for the same signal-noise ratio than with VHS. So Beta machines could provide an apparently better bandwidth and resolution.

With the Video-8 system the luminance f.m. deviation is 4.2-5.4MHz. Since the carrier is at a higher frequency than with standard VHS or Beta, the result will be a wider lower sideband f.m. bandwidth and thus improved resolution. The wider deviation of 1.2MHz compared to standard VHS will give an improvement in signal-noise performance, but this is offset by higher density recording on the narrower 8mm tape. Further improvement is allowed for however by the use of higher grades of metal tape.

Thus to achieve improved performance with a video recording system, three factors require attention. First a higher luminance carrier frequency to enable the bandwidth and thus the resolution to be improved. Sec-

only a wider frequency deviation to improve the signal-noise performance. And thirdly an improved type of tape is required to enable the first two factors to be implemented.

The Super Beta standard is shown in Fig. 1(b) for comparison. The luminance carrier frequency of 4.8-6MHz gives increased resolution (370 lines) compared with standard Beta while the 1.2MHz deviation provides a good signal-noise ratio. Overall the performance is much better than with standard Beta.

### Super-VHS

The new Super VHS specification pushes the luminance bandwidth even farther up the scale, the carrier deviation being 5.4-7MHz. This results in a massive resolution increase from 250 to 400 TV lines while the wider 1.6MHz deviation improves the signal-noise ratio. The bandwidth of the down-converted chroma signal is increased to over 500kHz, centred on 627kHz, giving enhanced colour. The luminance white and dark clip levels have been increased to 250 per cent and 70 per cent respectively.


The new specification also reduces cross-colour effects. If you compare Fig. 1 (a) and (c) you will see that the upper sideband of the chroma signal and the lower sideband of the luminance signal no longer overlap – in fact there's a gap of some 200-300kHz.

JVC intend the new S-VHS machines to have separate luminance and chrominance inputs and outputs so that the improved cross-colour performance and bandwidth are maintained. JVC also intend to market a high-grade colour TV set with separate luminance and chroma facilities. It will take advantage of the improved S-VHS specification, though standard r.f. and composite facilities will no doubt be provided. All this is likely to upset the Euro camp with its SCART connector.
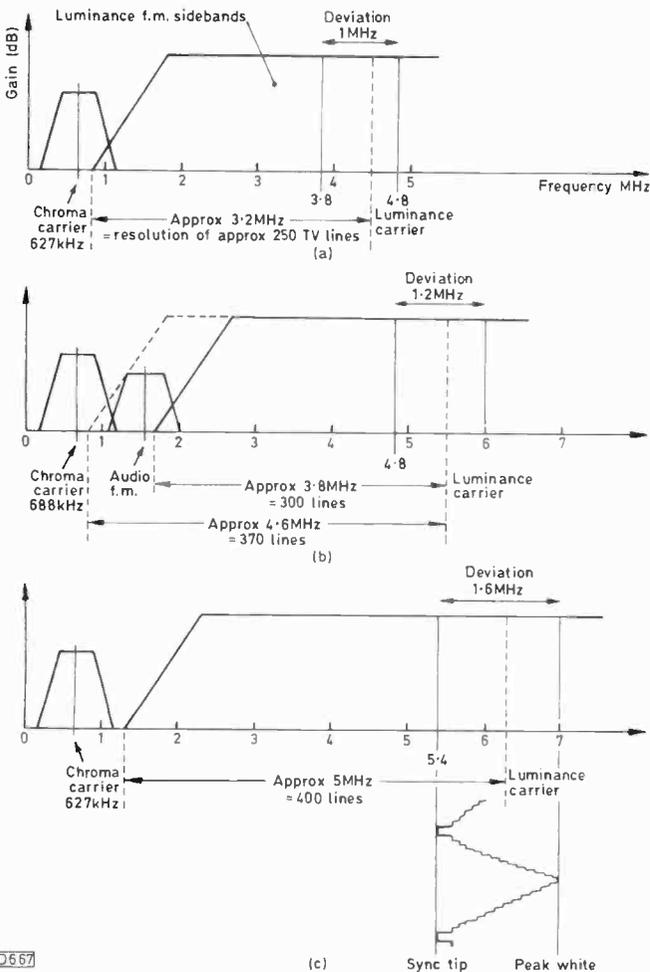
### Tape

The whole system depends on the availability of a tape capable of handling the wider bandwidth. A new tape, intended exclusively for S-VHS use, has been developed. It uses a highly efficient cobalt iron oxide material and has the high coercivity of 800-900 Oersteds (the high grade and super high grade tapes currently available have the relatively high coercivity of 720-750 Oersteds). The cassette has an identification hole so that the VCR can identify the type of tape.

There would be no point in using the new tape with



D657

Fig. 1: Comparison between the signal spectra for various VCR systems. (a) Existing VHS. (b) Beta super hi-band. (c) The New Super-VHS specification.

current VCRs. They would not be able to erase it let alone record on it, though it may be suitable for use with some updated models to be produced later this year. The new tape will be manufactured by Fuji, Maxell, TDK and Scotch in addition to JVC.

### Recorders

The new S-VHS VCRs will have dual VHS standard capability, being able to record and playback to either specification. Current models are not able to handle S-VHS tapes.

S-VHS machines will be released this summer by JVC, Panasonic, Mitsubishi, Hitachi and Sharp - in Japan. There's no PAL version as yet, though I expect some S-VHS models to be released in Europe by the end of the year or early next year. The price is likely to be in the region of £1,000. In due course Sony will no doubt announce a new super duper Beta format to handle extended definition TV signals (EDTV), with a resolution of 500 lines. When you come across references to ED Beta some time in 1988, remember that you read about it first in *Television!*

As an aside, whilst we in the UK are still stuck with standard terrestrial TV transmissions it would nevertheless seem that the designers of C-MAC satellite TV decoders should be thinking of providing a separate chroma output. I've no doubt that it would be easy enough to modify TV sets to buffer out the chrominance. Any ideas as to which SCART pin we could hijack?

next month in

# TELEVISION

### ● DIGITAL SERVICING WITH A LOGIC PULSER

Tackling the complex digital circuitry used in many VCRs is perhaps the biggest problem that service engineers face today. Hours can be spent in trying to pinpoint faults in system control circuitry, and many expensive chips may be replaced without clearing the fault. Use of equipment specifically designed for fault-finding in digital circuitry greatly helps. Two such items are now readily available at a reasonable price, the logic probe and logic pulser. The former is similar to the traditional signal tracer while the latter acts as a logic signal generator.

In an earlier article (November 1985) David Botto described the use of a logic probe. This time he takes digital servicing a step further in describing the use of a probe and pulser combination. Until recently several types of pulser would have been required to cope with the various logic families: it's now possible to obtain for less than £17 a logic pulser that operates effectively with all types of logic circuitry.

### ● BUDGET VARIABLE PSU

A recent bench power supply test report stressed its many uses in the workshop. For the impecunious or those with less exacting requirements William Harrison presents a simple, low-cost variable regulated power supply.

### ● TELEVISION ON TAP

J. LeJeune takes a close look at cable television, starting with a survey of the various types of systems that have been used over the years.

### ● MORE ON VIDEO-8

The concluding instalment of Eugene Trundle's Video-8 series deals with further aspects of PCM audio and servicing procedures for Video-8 equipment.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....  
(Name of Newsagent)

Please reserve/deliver the August issue of TELEVISION (£1.30), on sale July 15th, and continue every month until further notice.

NAME .....

ADDRESS .....

# Now Read This

Les Lawry-Johns

I'm told that some of you who repair Ferguson videos don't recognise a fuse when you see one. Now I don't care to get involved with VCRs myself but when I was given this information I thought it would be prudent to pass it on, although the majority of you probably know what it's all about already. The point is that the fuses concerned don't look like fuses, they look more like a small diode or a transistor with two legs. They're called Wickman fuses and are rated at 150V. Close scrutiny of the list given in Table 1 reveals that the current rating is obtained by multiplying the type number by 40, for example type ICP-F10 has a rating of 400mA ( $10 \times 40 = 400$ ). Cries of never . . . Table 2 lists the range of Wickman fuses available from Philips Service, and their code numbers for ordering purposes. I hope you find this of interest. Take a note of it, just in case.

## The Big Roberts

This large set was brought in the other day by two big fellows who puffed a bit. It turned out to be fitted with the Philips G9 chassis, which was bad news for uncle Les. There was about four inches of field scan on the 26in. tube, almost full width, no control of brightness and very little sound. Now as you know the first thing to do with this chassis is to check the condition of C138 (2,200 $\mu$ F) which decouples the emitter of the BU208 line output transistor, serving as the reservoir capacitor for the 42.8V supply. I didn't suspect it of being the cause of the fault conditions but checked it just the same. It was on the way out, emitting thick black fluid. I changed it and tried the set again. Still the same. The BU208's emitter voltage was low at about 20V, thus explaining the poor field scan, low sound, etc. I removed the plug connected to the timebase panel (line oscillator, field timebase, EW correction circuit etc.) and the BU208's emitter voltage rose to 40V.

Like a fool I fitted another timebase panel. The symptoms remained the same. So I concentrated on the line

output panel and found a leaky diode (D176) in the beam limiter circuit. Replacing this didn't alter things one jot and I was getting fed up. After further checks I found that the "lower" diode in the diode modulator circuit, D156 (BYX55-600), was open-circuit. Heaving a sigh, I replaced this and put the panel back in. It worked. Full voltage at the BU208's emitter, a lovely field scan, full control of brightness and good sound. I would have thought that an open-circuit diode in this position would have had a more drastic effect on the width, but it didn't. Something else to remember.

## The Pye 196

This set gave me a bit of a headache. It's a small monochrome portable fitted with the Philips TX chassis. The complaint was that the picture would go off at irregular intervals, leaving a blank raster with slight radio music or talking sounds in the background. To me this meant trouble in the i.f. strip. My problem was that the fault just wouldn't put in an appearance. The picture stayed on for days. Eventually, one morning, the picture did go off, leaving a blank raster.

I leapt at it and found that the voltages at the base and emitter of the first i.f. amplifier transistor were higher than they should have been – about the same as at the collector. If I switched off to check the transistor however the fault would be gone and we would be back to normal. So I followed the base bias back to the a.g.c. amplifier transistor TS351 and found that this had no base bias. Its collector voltage was thus high and the i.f. amplifier transistor TS217 was being turned on excessively. The base of TS351 is biased by R353 (820k $\Omega$ ) which was open-circuit. After replacing this the set behaved itself for several days and the owner was glad to collect it.

The set was used in a caravan and had always behaved for the husband but always gave his wife trouble. She blamed him and he was glad to be out of the doghouse. It's all right for him. I live in one all the time. Tessa and Zeb are good really: it's the cat that leads me a dog's life.

## The Radio Set

This was a killer. A shop (I won't say who it was, Peter) had told this chap that the only place where he would get his radio set repaired would be here. I said I would have a look at it if he brought it in. Shortly after this he appeared with his wife, carrying a small wooden box. His wife explained the trouble.

"When we turn up the volume it screams at us."

I took the back off and looked inside. On the right-hand side there was a tall object which I took to be the dropper. Next to this there was a valve which seemed to be a 6Q7. It was obviously a double diode triode anyway. There were two further valves to the left, both with top caps connected to the tuning gang (two sections). I looked for an output valve and rectifier but they weren't there.

"Did you say this set goes?"

"Yes, but it howls at you."

I plugged it in and switched on. Something flashed and went bang underneath. I unplugged it and removed the chassis screws and the knobs at the front. The whole thing came out, including the speaker. When I turned it over I saw that the mains filter capacitor had disintegrated. So I clipped it out. "We'll fit another if a strong station has a hum behind it" I explained.

I switched it on again and was aware of an obnoxious smell.

Table 1: Wickman fuses used in Ferguson video equipment.

Type	Rating	Part no.	Used on
ICP-F10	0.4A	01X0-042-112	3V33/38/39/42/43/45/47/48/49/54/56
ICP-F15	0.6A	01X0-040-407	3V29/30/35/36/38/39/49/50
ICP-F20	0.8A	01X0-086-061	3V46/50
ICP-F38	1.5A	01X0-057-320	3V38
ICP-N10	0.4A	01X0-058-395	3C01, 3V44/45/48/50
ICP-N25	1A	01X0-085-007	3V44/45

Table 2: Wickman fuses from Philips Service.

Rating	Code no.	Rating	Code no.
63mAT	253 10058	1.25AT	253 10075
160mAT	253 10054	1.6AT	253 10046
250mAT	253 10071	2A	253 10051
315mAT	253 10074	2AT	253 10039
400mAT	253 10064	2.5A	253 10082
500mAT	253 10041	2.5AT	253 30089
630mAT	253 20089	3.15AT	253 10048
800mAT	253 30104	4AT	253 10047
1AT	253 10052	5AT	253 10065

Note: T after A indicates time-lag type.

"It's the smell that's getting us down" he said.

I sniffed around and it seemed to come from the dropper. I looked at it closely. It wasn't a dropper, though it looked like one. It was an old selenium rectifier. I disconnected one end and fitted a BY127. "It won't smell any more" I said.

"That little thing in place of that big one?" he queried. "The march of time" I explained.

I examined the set in more detail and came to the conclusion that the double diode triode drove the speaker, that what I had assumed was the i.f. amplifier was in fact the second r.f. amplifier, and that what I had assumed was the frequency changer was the first r.f. amplifier. It wasn't a superhet at all, it was a t.r.f. receiver. This meant that the "volume control" was in fact a reactance control, hence the oscillation when it was turned up. I connected the short aerial lead to the braiding of a TV aerial and the set started to perform. With the set tuned to the h.f. end of the medium wave band I tuned the trimmers on top of

the gang. The stations now came through loud and clear. I turned up the "volume control" and the set howled, so I turned it down for comfortable listening.

"How long an aerial lead do you use?" I enquired.

"About four feet, connected to a water pipe" he replied.

"Well don't connect the aerial lead to a water pipe unless you use it as an earth. Use a bloody great length of single lead and don't connect it to anything."

"Why?"

"Because the ideal length for an aerial is half a wavelength. Radio four on the long wave is 1,500 metres. The aerial length for this is therefore 750 metres. Get the drift?"

"Yes. Thanks very much."

So they went off leaving me feeling full of nostalgia for the old days. I thought I'd forgotten it all but back it came. I still wonder about that double diode triode driving the speaker.

## Product Report: Glue Guns

Harold B. Berkley

For some time now I've been using a glue gun for both field and bench work. It's proved to be so useful that I never venture into the field without one. Traditionally we seem to carry in our kit everything for repairing the set, but seem to overlook damage to the cabinet, knobs and other bits and pieces. Very often a second, wasteful call is needed. With a glue gun in your hand you can eliminate many of these problems.

### The Weapon

Glue guns use hot-melt adhesive sticks – many types of glue sticks are available for bonding different materials. I prefer the clear, general-purpose sticks usually provided with the gun. These will deal with most plastics, wood, fabric, paper, etc.

There's no shrinkage of the glue and the bond is ready when cool. The material is a good insulator and can be used as a sort of potting compound.

For around £10 you can pick up an electric glue gun, with glue sticks, and get started. There are two types of sticks: short, manual fed ones and longer, trigger fed sticks. Both types are o.k.

Camping Gaz have introduced a cordless glue gun. One of these (type P500) has been supplied to me for evaluation and I'll be reporting on it at a later date. It's powered by a Camping Gaz CV360 butane gas cartridge which should give around four hours' continuous use. Ignition is electronic, using one small battery. Two of the longer glue sticks (11mm x 210mm) are provided. The catalytic heating system means that there's no naked flame. The gun is good but not cheap at around £35.

### Applications

You will doubtless find many uses for your glue gun. Here are some of mine.

Cabinet repair is where the glue gun really shines – in the field instead of having to cart a set in for repair or even cabinet replacement. Repairs that are possible in the field include: cracked cabinets and fascias; internal damage to plastic mouldings; switch and push-button

mountings.

The gun can be of great help with older and obsolete sets for which parts are no longer available. Have you ever been to an older set which has push-buttons that go flying across the room when you change channels? No problem with the glue gun!

The above remarks also apply to bench work and refurbishing of course.

Here are some specific uses. With whistling line coils, for example in the Thorn 9600 chassis, a quick squirt of glue will usually provide a cure. This is worth a try on other noisy chokes and transformers. Where an on/off switch has been pushed into the set, breaking the plastic moulding, a new switch can be glued in – allow to cool before testing. When the aerial socket comes away from the cabinet, for example in Korting sets, a glue gun will come to the rescue. In fact the list is endless.

### In Conclusion

In conclusion, this must be one of the few gadgets that will earn its keep very quickly. With the new cordless type giving greater convenience ever more uses will be found. If anyone finds some good ones, let us know!



The Bostik thumb-operated hot-glue gun in blister pack.

# The 8mm Video System

## Part 4

Eugene Trundle

As Fig. 1 showed, the very thin tapes used in Video-8 cassettes have a much shallower magnetic layer than that of conventional video tape. This means that the depth-multiplex audio recording technique, as used for VHS hi-fi, is not possible. Various ways of recording the sound are used in the Video-8 system. These are as follows: (1) A mono audio signal can be recorded on the tape via the video heads, using a frequency-modulated 1.5MHz carrier. (2) The audio signal (digital, stereo) can be recorded via the video heads in the form of pulse-code modulation (PCM) that occupies its own section of the recorded video track (see Figs. 5-7). (3) Provision is made for recording a mono audio signal as a longitudinal track via a stationary head – this is referred to as “auxiliary audio”. All Video-8 machines are equipped with an f.m. audio system. The more sophisticated models also incorporate PCM audio. So far as I am aware no production machines to date have made use of the third (lo-fi!) technique. We’ll consider the f.m. audio system first.

### FM AUDIO

As Fig. 8 showed, f.m. audio has its own part of the Video-8 frequency spectrum. It offers a performance comparable with that of VHS and Beta hi-fi, albeit in mono only, with the frequency response limited to 15kHz.

### Comping

The secret of the excellent performance of the f.m. audio system used with Video-8 equipment is the companding (compression-expansion) technique employed (this technique is also used with VHS and Beta equipment of course). While it calls for great precision in the record and playback electronics – easily implemented by using purpose-designed i.c.s – it’s capable of better frequency response, dynamic range and signal-to-noise ratio than any attempt to record the audio without such processing.

The principle of companding is shown in Fig. 27. Starting with 0dB input (top right-hand corner), for each 20dB input signal decrease a gain of 10dB is applied. So a -20dB input signal level emerges as -10dB, a -40dB

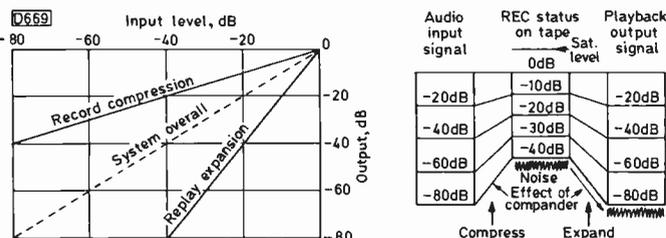


Fig. 27 (left): Companding characteristic. The dB scale is logarithmic, so the compression and expansion effects are fiercer than this diagram suggests.

Fig. 28 (right): How companding reduces playback noise and keeps the “magnetic swing” in the tape small. This technique would not be practical with a “direct” tape recording system – the slightest non-linearity in the transfer characteristic would cause large-amplitude distortion effects – but can be used with a precision f.m. system.

input signal level emerges as -20dB and so on. The result (upper line in Fig. 27) is to compress an input signal dynamic range of 80dB (10,000:1) into a recorded span of 40dB (100:1). Hence the expression 2:1 (logarithmic) compression ratio. This total range of 40dB is very easily accommodated by the tape system.

To restore correct signal conditions during playback 2:1 expansion is applied – see the lower line in Fig. 27. The broken line shows the overall result: the original audio input and the system output levels have been equated. In the process there’s a tremendous reduction in noise level, as Fig. 28 shows. Here the tape noise is shown as being at a level of about -45dB. After the playback expansion process it will be at some 85dB below the peak sound level.

### FM Record System

Because the sound signal is going to be used to frequency modulate a carrier, various conditioning processes are required in preparation for this – these are in addition to the amplitude compression. Fig. 29 shows the basics of the audio f.m. record system.

After passing through a sharp 15kHz cut-off filter (to avoid TV line frequency breakthrough and to ensure correct operation of the noise-reduction circuit), and in the case of a camcorder a sharp (12dB/octave) 200Hz high-pass filter (to lose wind, handling and lens-motor noise), the signal is applied to the non-inverting input of the main operational amplifier (MOA). Compression is applied by adjusting the feedback to the MOA’s inverting input. As you can see, the MOA’s output passes via the weighting filter to an r.m.s. detector. This is a very precise measurer of the effective signal level. The output from the r.m.s. detector is used to control the gain of a voltage-controlled amplifier (VCA) which regulates the level of the feedback applied to the MOA. The VCA’s characteristic is that shown in Fig. 27: the stronger the input signal the greater the feedback and vice versa. The 2:1 compression is thus put into effect.

Weighting and pre-emphasis are also carried out via the feedback circuit. The pre-emphasis-1 block consists of a filter with a falling response of around 1.5dB/octave between 2kHz and 14kHz: by reducing the h.f. negative feedback a boost is given to the higher frequencies. Pre-emphasis-2 is carried out by a filter in the signal path to the VCA. This has a falling response at around 1kHz, and since it is again in the negative feedback path the effect is to boost the higher audio frequencies. The weighting filter in the path to the r.m.s. detector increases the VCA’s gain, largely cancelling the effect of pre-emphasis-2, when the predominant audio signal components are of high frequency. This improves the linearity and ensures that with large h.f. signals the f.m. deviation limits aren’t exceeded.

The result of all this is a carefully tailored, shaped and 2:1 compressed audio signal which is passed to a limiter circuit. This is included to clip any signal excursions that may cause over-deviation in the f.m. modulator. The latter consists of an astable voltage-controlled oscillator (VCO) whose output is the record f.m. signal, with a

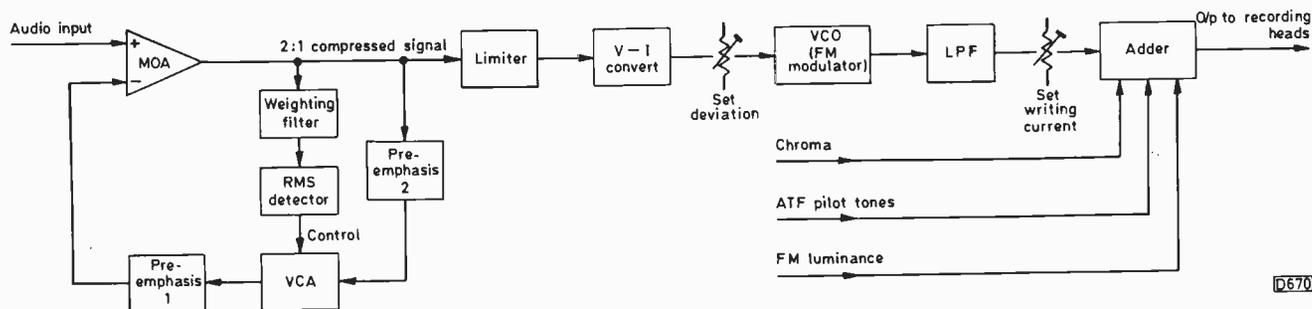


Fig. 29: Block diagram of the audio f.m. recording system.

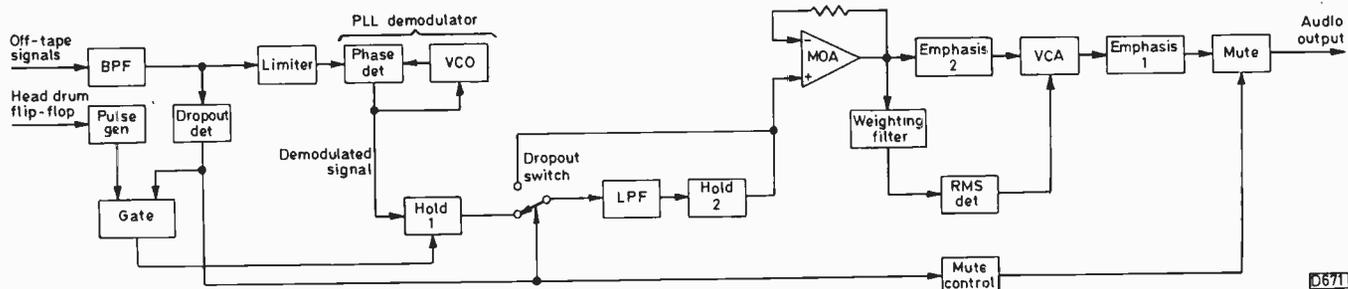


Fig. 30: Block diagram of the audio f.m. playback electronics.

centre frequency of 1.5MHz. This frequency is set by a "carrier" potentiometer while the deviation (nominal 60kHz, maximum 100kHz) is set by the "set deviation" potentiometer. The f.m. modulator's output is fed to a low-pass filter with a crossover frequency of around 1.7MHz, then a carrier-level preset which adjusts the audio f.m. writing current to a level about 13dB below the chroma writing current level. The f.m. audio is finally added to the chroma, luminance and ATF signals, the lot then passing to the rotary video heads for recording.

### FM Playback

The playback system shares much of the record circuitry. Fig. 30 shows the arrangement in block diagram form. The audio f.m. is filtered from the other off-tape signals by a bandpass filter that's sharply tuned to 1.5MHz, having a bandwidth of about 250kHz. The main playback path is via the limiter (to remove a.m. components) then to a phase detector whose other input is a 1.5MHz signal from the same VCO that was used as the f.m. modulator in the record mode. The VCO and phase detector form a phase-locked loop (PLL) which demodulates the f.m. audio.

The demodulated audio next passes through some dropout compensation circuitry. It goes first to the block labelled hold-1 which is primarily concerned with masking the signal discontinuity at the head change-over points. The output from this block is normally routed through a low-pass filter thence via the hold-2 block to the expander circuit. In the event of a dropout however the dropout detector will sense the shortfall in carrier level and produce an output that activates the dropout switch. The hold-2 circuit then provides dropout compensation to maintain the instantaneous audio signal level until the dropout has passed. The low-pass filter has a slight delay effect on the signal with respect to the hold operation. A prolonged dropout (or lack of f.m. signal for any cause) will bring the mute control circuit into action, shutting down the audio output altogether.

The main feature of the audio playback electronics is the expander, which again uses the MOA and associated

circuitry. This time the MOA has a fixed resistive feedback path and acts simply as a buffer. Its output passes through the record pre-emphasis-2 network whose falling h.f. response now provides de-emphasis. Next comes the VCA which is still controlled by the r.m.s. detector. Since the VCA is now in the main signal path rather than in a negative-feedback path, its effect is to reduce the gain as the off-tape signal decreases, giving the expansion characteristic shown on the right-hand sides of Figs. 27 and 28. Pre-emphasis filter-1, still depressing the higher frequencies, now provides de-emphasis-1. On emergence from this filter the audio signal has been fully restored and is ready to be buffered out.

### PCM AUDIO

Whereas the audio f.m. system and its main feature of companding are used for hi-fi sound in other VCR systems, the use of a domestic digital audio record/playback system (PCM) is unique to the Video-8 format - though the imminent introduction of DAT (digital audio tape) will change that. Before launching into the workings of the PCM circuitry we need to know a bit about digitising analogue signals.

Sampling and quantisation are the two processes required to convert an analogue signal into an equivalent digital bit stream. The procedure is shown in elementary form in Fig. 31. First comes sampling: a gate is momentar-

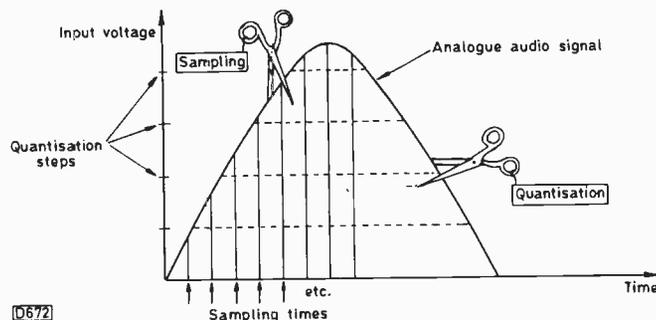


Fig. 31: Principle of digitising an analogue signal.

ily opened at short, regular intervals to take a "snapshot" of the signal level at each instant. With the Video-8 format the sampling frequency (for PAL machines) is 31.25kHz, twice the line rate. Now Nyquist's law states that the sampling frequency must be at least twice the highest signal frequency, so a sampling frequency of 31.25kHz implies that the highest signal frequency the system will handle is 15kHz. To avoid aliasing effects, the signal must first pass through a low-pass filter with a very steep roll-off above this frequency.

The second step is to quantise each sample in turn: its amplitude is measured and converted to the appropriate binary number. The final quality - in terms of fidelity and signal-to-noise ratio - of a signal that's processed in this way depends almost entirely on how many digits we use for this binary number, i.e. the greater the number of bits the greater the number of signal level differences we can accommodate. This quantisation is something of a compromise since (assuming real-time operation) the entire digital word has to be generated and conveyed in the short, fixed period between samples. So the more bits we use the greater the bandwidth required in the transmission circuits and the greater the storage capacity of the disc or tape. Various bit rates are used for entertainment audio: 16 bits for studio applications and the compact disc; 14 bits for the EIAJ standard as used for example in the PCM-F1 format; and 8 bits for Video-8 PCM. With Video-8 the initial sampling is done at 10 bits however: this gives some advantages, as we shall see. Ten bits offers us a total of 1024 quantisation levels. So at the output of the analogue-to-digital converter used in our PCM system we have a rapid-fire string of binary words forming a signal that has only two amplitude levels, one and zero.

### Basic PCM System

We've already seen (Figs. 5-7) that the PCM signal is recorded on a "forward extension" of the video track, and since only 30° of head rotation is available for it the sound signal has to be time compressed by about 6:1. Fig. 32 shows in broad outline the audio signal processing in the PCM mode. In the record mode the analogue audio signal first passes through the same compander/emphasis circuitry we've already described for noise reduction in the audio f.m. mode - all that technology is too good to waste! The first step after this is analogue-to-digital (A-D) conversion - to 10-bit words. This is followed by non-linear reduction to 8 bits. Error-correction words are then added to the data before it's stored in a pair of 16K RAMs, to be tone modulated and passed in turn to each

of the video heads as they traverse the first 30° of the helical tracks. A slight audio signal delay is inherent in this process: the audio that accompanies field  $n$  is recorded on the tape during the PCM segment preceding field  $n + 2$ . During playback the need for processing and time expansion means that the segment of sound is reproduced during field  $n + 3$ . This 60msec delay is not perceptible to the viewer however.

The signal processing arrangements so far described are used again for playback. The modulator becomes a PLL demodulator, and the memories are loaded with off-tape digital sound data during the 2.9msec or so when each video head is connected to the PCM circuit by the switching shown. During the next 20msec or so the memory in use is read out via error correction and concealment circuits. The digital sound data is then D-A converted to amplitude-compressed audio. Noise reduction is applied in the expansion process and the audio is finally passed out of the machine.

### A-D Conversion

The A-D conversion process is based on the action of a single integrating capacitor. Fig. 33(a) shows the principle. During the first (discharge) period a gate opens momentarily to discharge the capacitor to a level proportional to the analogue input voltage at that instant: this is the sampling time. The capacitor is then recharged by a constant-current source until the voltage across it reaches reference level REF H. With a constant charging slope, the time taken for this is proportional to the initial charge on the capacitor. This period is measured in terms of clock pulses to give a rough count of the value of the analogue sample voltage. In this way the five most significant bits (MSB) of the 10-bit word are formed.

Unless the master clock rate is very high (which is expensive in terms of hardware) there's a degree of uncertainty in this process: the accumulated count depends on the chance timing of the ramp termination relative to the incidence of a clock pulse. Correction for this is carried out during the "fine integration" period, when the capacitor is charged from level REF H to a further fixed voltage REF L by a much smaller constant current - in fact 31 times smaller than that which produces the initial, steep ramp. Once more clock pulses are accumulated in a counter during this period, and the contents of the counter when the voltage across the capacitor reaches level REF L make up the five least significant bits (LSB) of the 10-bit digital word. The five LSB (maximum count 32) can influence the value of the

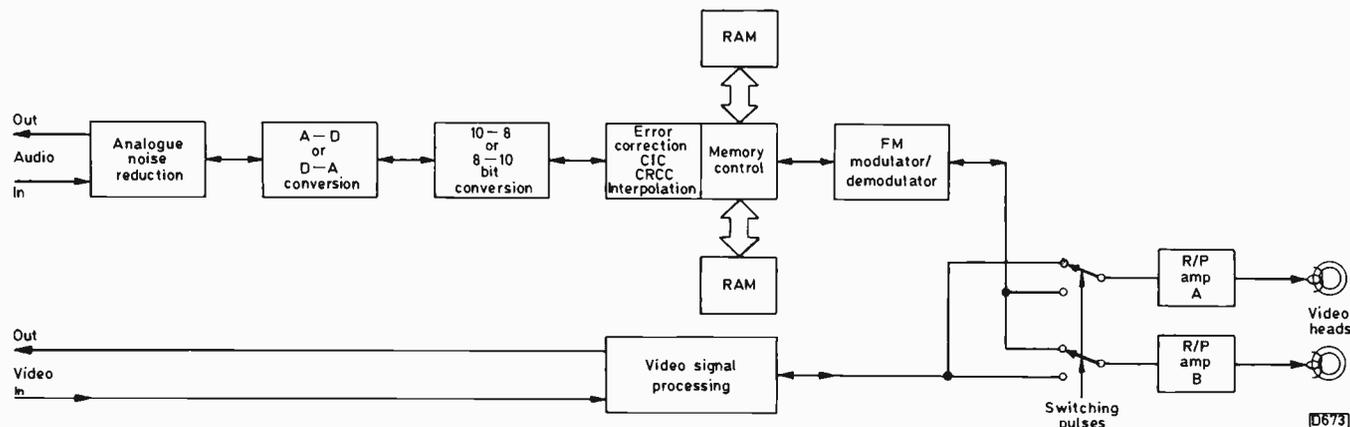


Fig. 32: Block diagram of the PCM processing arrangement.

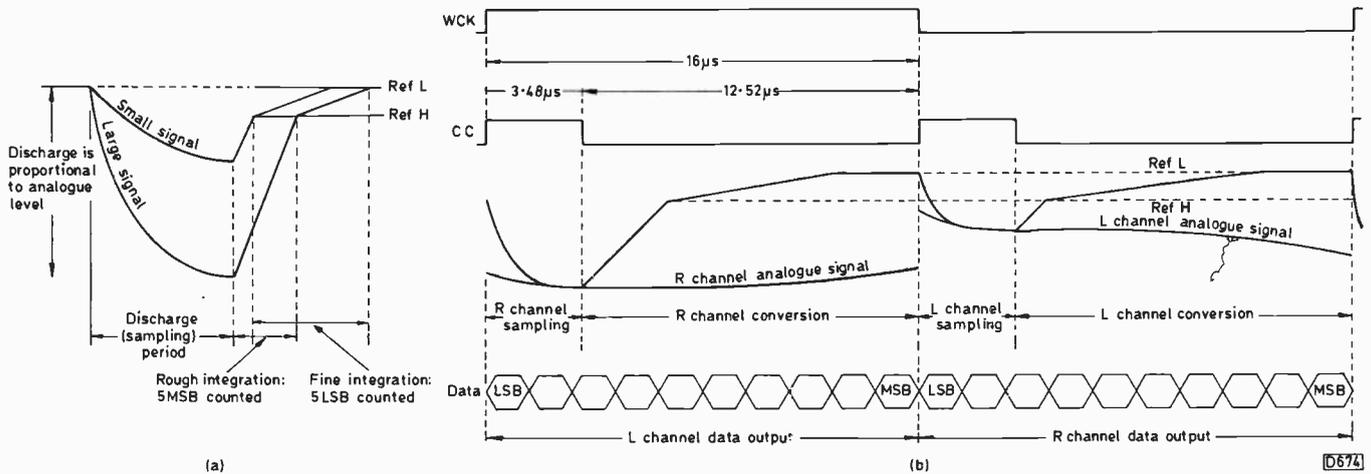


Fig. 33: A-D conversion: (a) working principle; (b) timing diagram.

word (maximum count 1024) by only about three per cent, so the action of the second ramp-up can be considered as a "trimming" or "vernier" process. The two 5-bit sections are assembled end-on to form the 10-bit word.

Fig. 33(b) shows a timing chart for the A-D process. Right and left audio channels are digitised in turn, each at 32µsec intervals. The top waveform is that of the word clock WCK, whose positive section lasts for 16µsec. For the first 3.48µsec of this period a gate (controlled by CC, convert command) is opened to give the R-channel audio access to the sampling capacitor. When the gate closes another one opens to pass a constant-charge current into the capacitor. A path is simultaneously opened to allow clock pulses into the 5-MSB counter. A comparator, sitting on the REF H level, detects the finishing point of the first ramp, whereupon it shuts down the 5-MSB counter, simultaneously switching over to the "low" constant-charging current and diverting clock pulses into the 5-LSB counter. A second comparator, whose reference is REF L, shuts down both these processes at the end of the second ramp.

At this point the sampling capacitor is fully charged and the A-D converter is ready to do the same job on the L-channel signal during the WCK's 16µsec "low" period. In our drawing the L-channel audio level is quite different from the previous R-channel sample, and this is reflected in the much shorter primary ramp period. The secondary ramp is of nominally the same length in both cases of course. Note that the R-channel data (bottom of diagram) is clocked out during the period of L-channel digitisation.

This "dual-slope, single-integration" method of A-D conversion is one of several that could be used. Choice of method is always a compromise between cost, accuracy and speed of performance. The choice is an excellent one in this case, giving very good results. The A-D converter chip is also capable of running "backwards" to carry out D-A conversion. We'll return to this shortly.

### 10 to 8 Bit Conversion

The performance of a linear 8-bit audio data system is not good enough for high-fidelity reproduction. Its main drawback is "quantising noise", the "dither" experienced by signals that fall between the quantising levels. This can be overcome by non-linear conversion from ten to eight bits (see Fig. 34), in which 10-bit quantisation is used for small signals, decreasing to 9 bits for moderate signals, 8 bits for average signal levels and 7 bits for the largest signals. Thus the 512 levels initially available on each side

of zero signal level are reduced to 128 levels in the 8-bit output word. The data is in two complement form, which means that the most significant bit (MSB) indicates the polarity of the analogue signal – one for a negative sample, zero for a positive sample. 10-bit to 8-bit conversion as shown in Fig. 34 is carried out by referring to a look-up table held in a ROM in IC101 (see Fig. 36).

The effect on the audio signal of non-linear quantisation is shown in Fig. 35. As you can see, quantising noise is small at low-signal levels due to the "high definition" 10-bit conversion: it becomes progressively greater as the quantising steps get larger on signal peaks. The resultant noise is lost in the loud signal however, and the effective dynamic range of the system is an impressive 90dB. This is one example of the many bit-reduction techniques that are used in data storage and transmission systems.

### Data Storage and Protection

The data is stored in a pair of 16K RAMs into which it's clocked in the form of parallel 8-bit words during the

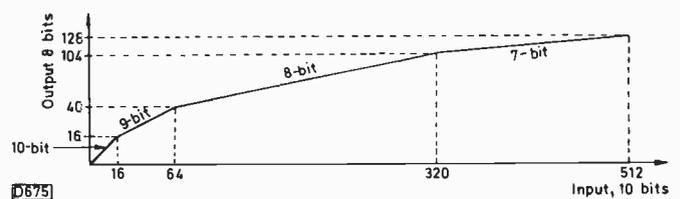


Fig. 34: 10-bit to 8-bit conversion chart. As the graph shows, the 8-bit output signal is non-linear.

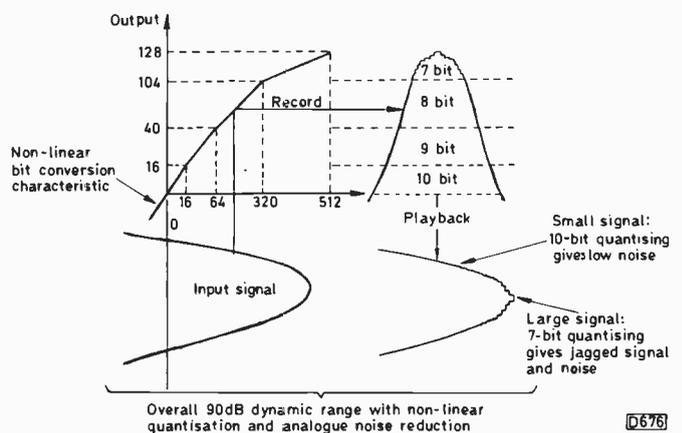


Fig. 35: The effect of non-linear quantisation on the playback signal: quantising noise is present only with large (loud) signals.

storage period. When the PCM write period comes round the data is rapidly clocked out – with several alterations and additions. It has ID data added to indicate the nature of the data, i.e. stereo/bilingual, reverse record, multi-PCM etc. It has P and Q parity words added to facilitate error correction. The data is “scattered” throughout the PCM record period in accordance with a cross-interleave code (CIC) which is part of the Video-8 format: this is a general precaution against the effect of a dropout, which instead of blowing a big hole in the data stream merely damages odd bits here and there, hopefully not beyond the repair capability of the parity-check system and the second protection arrangement, a 16-bit CRCC (cyclic redundancy check code). This latter is added en route between the RAMs and the PCM f.m. modulator. The bit redundancy of the PCM format used in the Video-8 system is 38.5 per cent, which is not as wasteful as it seems when the recording system is the unpredictable one consisting of magnetic tape and a tiny read/write head.

### **Recorded Data**

The data is finally passed to the PCM record modulator which operates in the FSK (frequency shift keying) mode: the recorded frequencies are 2.9MHz for a zero and 5.8MHz for a one. The maximum bit transmission rate of 5.8Mbit/sec may be compared with that of 2.03Mbit/sec for the CD system. The difference of course is that with CD the data transfer is in real-time whereas for Video-8 PCM data the transfer is time-compressed to about 6:1 to fit it into the tape and time slots available.

### **Practical Arrangement**

The foregoing explanation was of necessity a bit theoretical, and will do little to clear the waters when you examine the circuit diagram – the relevant part (pages 142-4 of the EVS700 manual) looks something of a jungle! To assist with this, Fig. 36 shows how the functions and processes are divided up between the main i.c.s used and the routing of the signals, data and control lines between them. It also gives an idea of the remarkable dual-function operation of most of the chips, which reverse their function during playback to undo, as it were, what they did in the record mode. This applies to the A-D converter chip as well, which is switchable to D-A operation using many of the same internal components.

We'll look at the record path first. The 10-bit serial data enters IC101 at pin 16 for conversion to the non-linear 8-bit format – the ROM instructions for doing this are incorporated in the chip. From pin 9 the serial data passes to pin 46 of IC102, in synchronism with the transfer clock between pins 4 and 3 respectively of the two chips. The data is passed via the serial-to-parallel and multiplex block to the RAM port control section, which is basically a manipulator of addresses. The cross-interleave code and the ID data from IC154 are also inserted at this point, the latter via a 4-bit parallel bus linked to pins 34-37. IC154 takes its instructions from the “feature CPU” chip IC001 which governs the entire PCM processing. The data storage RAMs IC105 and IC106 are read, written and addressed via parallel 8-bit buses which are linked to pins 9-33 of IC102. Also within IC102 is the ROM-based CRCC and the means of inserting it into the serial data stream. Finally, IC102 incorporates the f.m. modulator, an astable VCO which acts as a PLL f.m. demodulator during playback. The FSK f.m. data leaves IC102 at pin 8 for buffering between pins 10 and 12 of IC103 on its way

to the recording heads.

The lower blocks in Fig. 36 are concerned with pulse generation and housekeeping. The master clock generator (MCK, 11.5MHz) is in IC104, the output at pin 8 being phase-locked to the 50Hz “off-air” field sync pulses via the S REF signal coming through IC153. The phase detector for this purpose is in IC101, between pins 14 and 1 with its output appearing at pin 20. IC152 delays the head flip-flop pulses for the multi-PCM mode (see later). IC151 generates timing pulses for activation of the flying erase head, particularly during the PCM-dub and multi-PCM modes. IC111 is concerned only with generating video masking signals during the PCM-dub process – the need for these will be explained later.

During playback the off-tape PCM signal is routed via the PLL section of IC103, the f.m. modulator section of IC102 forming part of the loop. After demodulation the data takes the same path (in reverse) through IC102. De-interleaving takes place at the RAM port control section, by address manipulation. Error checking and parity correction of the 8-bit word also take place in IC102: if it can't cope, an error flag is passed to pin 5 of IC101 to invoke an error-masking process. The 8-bit data is converted back to 10-bit linear form between pins 9 and 16 of IC101, again in accordance with the ROM look-up table. When it emerges from pin 16 the reconstituted data is ready for D-A conversion.

### **Data Format on Tape**

In all, 157 blocks of data are recorded on the tape, along with a preamble and post-amble (both at 5.8MHz), during the 2.9msec occupied by the heads' first 30° of tape scan. The preamble is there to synchronise the playback detector PLL. The post-amble's main job is to ensure that all “old” data is eliminated and all new data recorded in the PCM-mode: it accommodates any slight timing errors.

Fig. 37 shows progressive expansions of sections of the PCM data period – one of the 157 blocks is shown in detail. The first three data bits indicate the start of a block. The next eight contain an address to indicate to the RAM control section the CIC and ID status. Next comes an 8-bit Q parity word for error checking. This is followed by the first four 8-bit words of actual data, W0-W3, then an 8-bit P parity check. W4-W7 are the remaining four data samples, after which comes a 16-bit CRC error-detection code word.

One of the data words is further expanded below. No change during a bit period indicates 0; a change during a bit period indicates 1. This particular word is thus 00111010. The successive data words W0-W7 don't follow the sequence left-1, right-1, left-2, right-2 etc. because of the cross-interleave code. Typically the scattering may be as follows: Q = Q366; W0 = L0; W1 = R48; W2 = L95; W3 = R143; P = P288 etc. This would be impossible to sort out without the standard CIC held in ROM in the PCM processing chip IC102. As with CD, all Video-8 machines work to the same code book of course!

### **PCM Playback**

During playback the output from each head is in turn gated to the PCM processing department for the appropriate 2.9msec/30°. The f.m. data is demodulated by a PLL and stored in the same pair of 16K RAMs that are used in the record mode. The RAM controller section ensures that the data clocked out of the RAMs is realigned in accordance with the playback CIC. The

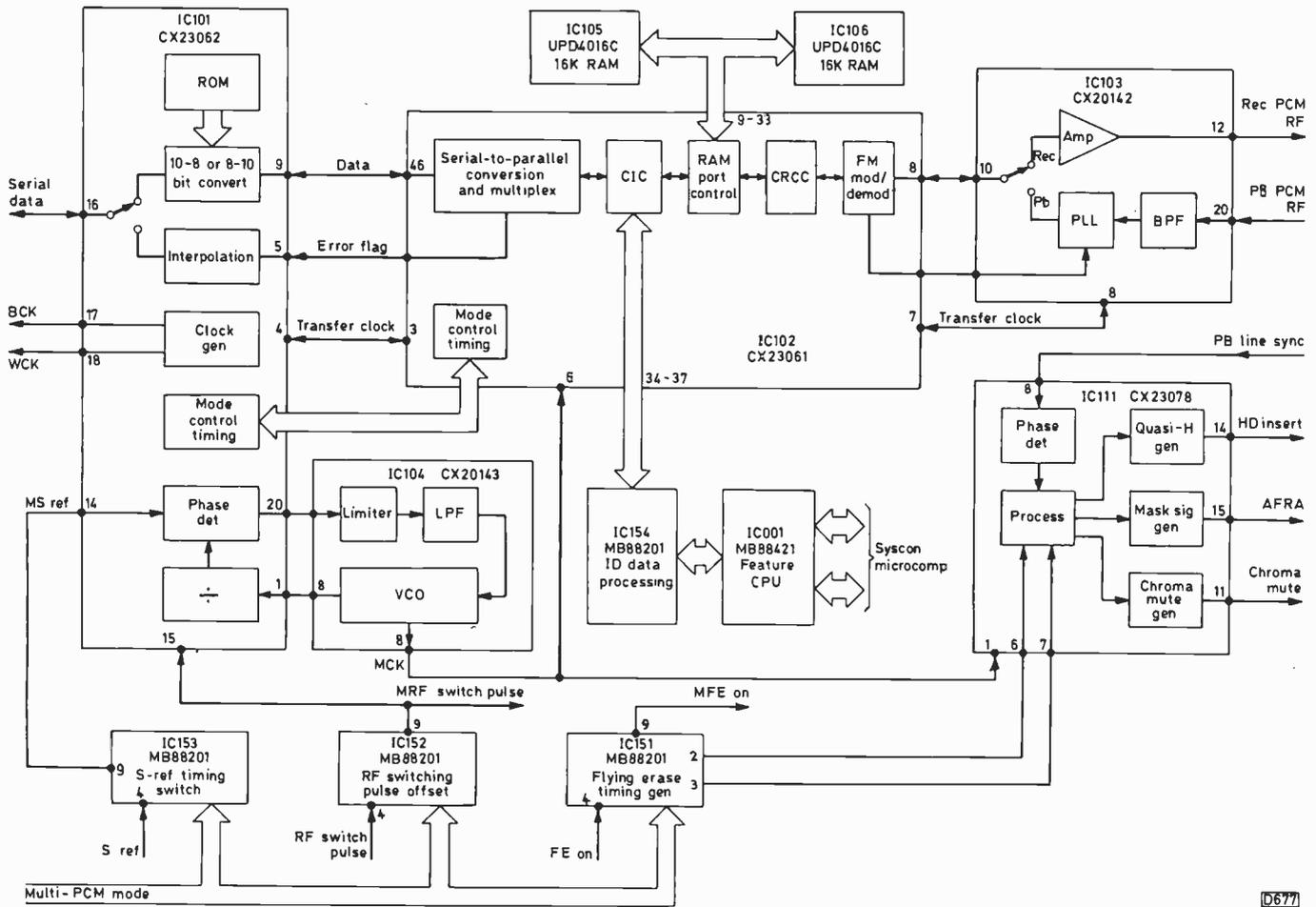


Fig. 36: PCM processing is carried out by several i.c.s, as shown here with their relationships and interconnections. IC111/152/153 are mainly concerned with multi-PCM operation: IC151 additionally deals with PCM dub processing.

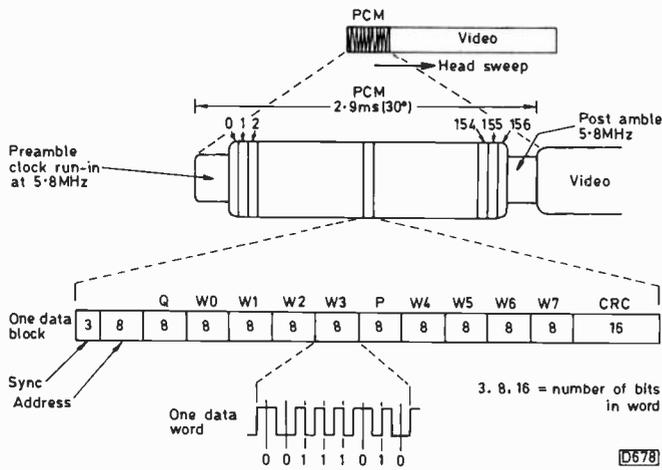


Fig. 37: Analysis of the PCM segment of a recorded tape track. The characteristics are explained in the text.

CRCC section indicates the presence of any data errors in each block: these will normally be corrected by the P and Q parity check words. If the error is too great for this correction an error flag appears, invoking the interpolation section.

Most data errors are caused by dropouts and can generally be corrected by the combined effects of the 16-bit CRCC word and the two 8-bit P and Q parity check words. If the dropout is so severe that all these measures fail, interpolation is carried out. With this process a badly corrupted sample is discarded and replaced with a synthesised one derived from preceding and succeeding

samples.

The way in which this is done is illustrated in Fig. 38. In (a) one data word, D2, is missing. Primary interpolation takes place: D2 is reconstituted as a word carrying data consisting of the average of the words on both sides, D1 and D3. Secondary interpolation is used where, as in (b), two consecutive words (D2 and D3) are damaged. D2 is simulated by taking an average of the data in words D1 and D4: a new D3 is formed from the average of the new D2 and the existing D4.

What happens if three or more consecutive words are so corrupt that they have to be discarded? It becomes impossible for the electronics to speculate on what they might have been during the short time available, so the chip goes into a "pre-hold" mode, as shown at (c), in which the value of the last good word is held until the reappearance of valid data.

The data leaves the de-interleave and error correction section still in non-linear 8-bit form. It must next be expanded back to 10-bit form. The process is similar to

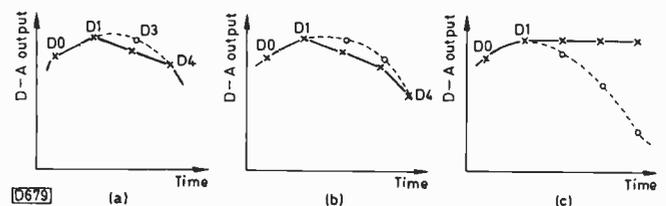


Fig. 38: Interpolation processes: (a) primary operation in the absence of one sample; (b) secondary operation where two samples are missing; (c) "pre-holding" where three or more samples have been lost.

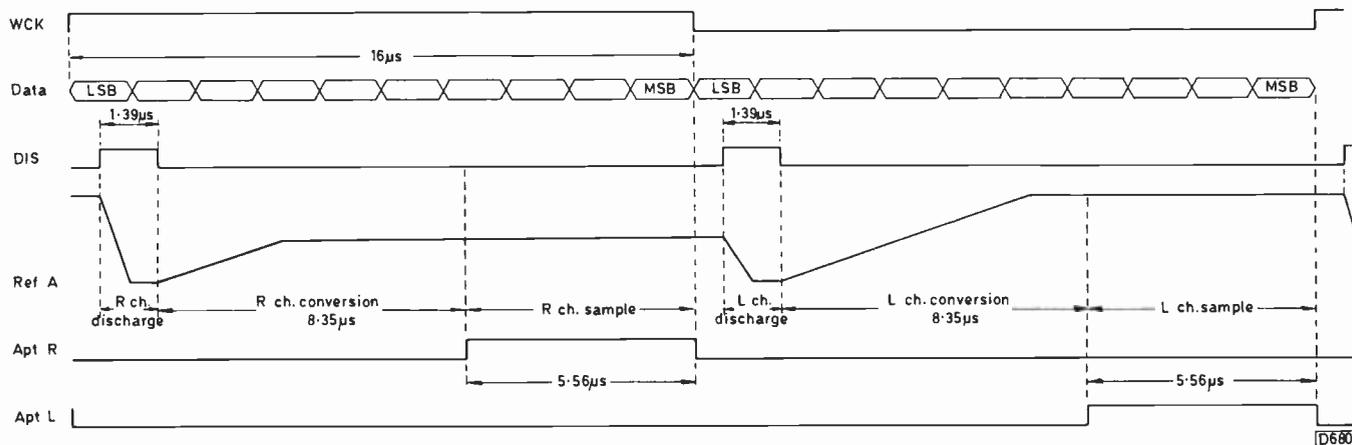


Fig. 39: D-A conversion during PCM replay. In this example the R-channel output is much lower than the L-channel output.

that used for 10- to 8-bit conversion during record, again using a look-up table in ROM. The error concealment process just described in fact takes place at the linear 10-bit stage.

D-A conversion makes use of the same integrator stage and storage capacitor as before. Fig. 39 shows a timing chart for the D-A conversion process. The capacitor is first rapidly discharged (during the DIS pulse) to a fixed (2.5V) reference voltage, REF A. At the end of the DIS-pulse period the capacitor is charged by a constant current for a period depending on the contents of the data word being converted. The maximum charging period (corresponding to peak sound) will not exceed  $8.35\mu\text{sec}$  and the final charge level (at constant current, remember) is proportional to the charging period. This level is sampled (APT pulse period) during the final  $5.56\mu\text{sec}$  of the

conversion process: a succession of these samples is integrated to form the analogue output signal. As shown in Fig. 39, left- and right-channel signals are dealt with alternately, in a  $32\mu\text{sec}$  cycle. Again there's a timing delay – the L-channel sampling/integration takes place as the succeeding R-channel data is being clocked into the conversion registers.

The analogue signal thus reconstituted is still in amplitude-compressed form of course, and next undergoes expansion in the compander circuit previously described in connection with the audio f.m. section. It's then ready to be passed out of the machine. It's amazing, when listening to the crystal-clear and noise-free audio reproduction from a PCM tape, to think of all the aliases, disguises and transformations the signal undergoes during its passage through the entire system.

## Teletopics

### AT THE SHOWS

There were several interesting innovations and hints of things to come at this year's brown goods' trade shows. Large screen CTV sets for a start. Both Grundig and Mitsubishi showed sets using a 36in. FS tube – the same tube in fact, made by Mitsubishi. Grundig's "Super Large Screen" set retails at just under £3,500 and is intended primarily for commercial use. Fidelity have developed a digital TV chassis using ITT chips: it will be used in a range of models with different screen sizes, from 14in. upwards. Hinari's Sunrise Model TVA1, a 14in. colour set, is designed specifically for use in the bedroom: it incorporates a digital clock timer to wake you up to morning TV and a fall-asleep function which automatically puts the set into the standby mode until the morning if you drop off at night. With full function remote control it comes at a suggested price of £199.95. Colour LCD TV sets are likely to be available from several manufacturers before long, including Philips who have just announced a £45m investment in a new plant at Heerlen specifically for the manufacture of LCD panels and TV sets. Philips expect to introduce a 3in. model later this year, featuring an "active LCD" which is claimed to give higher resolution and better colour than passive types.

Digital was the buzzword in the VCR field, with several new models incorporating digital video processing circuitry to provide features such as picture-in-picture and

freeze frame. Sharp, in a special "take a look at the future" show, revealed work on a 3D VCR using standard VHS cassettes. Sansui showed a digital video processor, Model VX99, to provide various special effects in conjunction with a camera that can be genlocked. Effects include eight background colours, oil-painting effects, wipes/mixing/fading and picture-in-picture – all for an anticipated price of around £400. Entryvision CCTV systems are being introduced by various companies including Sharp and Toshiba (see also note last month on the Sony Watchcam). The Toshiba system has a camera the size of a fountain pen and a colour LCD monitor. Sharp's system uses an interphone line to provide multiplexed transmission of sound, video and phone signals plus power.

### NEW JOINT VIDEO VENTURE

Hinari Consumer Electronics has formed a 50:50 joint venture company with Japanese manufacturer Shintom to establish a new VCR plant at Cumbernauld near Glasgow. An investment of over £4m is envisaged and the plant is expected to be in operation within a few months. There will be four models initially and about half the output will be exported to other EEC countries.

### TOUGH EEC ACTION

The European Community has adopted a tough stance in efforts to counteract the EC trade imbalance with Japan and avoid possible diversion of Japanese goods to Europe following the recent imposition of tariffs by the USA. The proposed EC measures are aimed particularly at con-

sumer electronics goods, including components for use in VCR manufacture. "Punitive" tariffs could be imposed on colour TV sets in the event of evidence of trade diversion from the US market.

### **THE VCR RABBIT**

A new system, called the VCR Rabbit, which enables a VCR to drive up to five TV sets around the house, with remote control from another room, has been introduced by EGH (UK) Ltd., Cross Green Industrial Estate, Leeds LS9 0SG. It involves the use of two types of module. The transmitter module is connected to the VCR's output and to the main TV receiver via a standard coaxial cable. A second wire only 0.7mm thick links the transmitter module to a remote Rabbit receiver module up to 50m distant. This thin wire carries the VCR's video signal to the receiver module which converts it to r.f. for feeding into a second set – up to three more sets can be linked to the system via receiver modules. The link wire also carries remote control signals back to the transmitter. Each receiver module is able to receive infra-red remote control commands, while the transmitter module can provide an infra-red output to control the VCR. Thus a handset used with any of the receivers will control the VCR. A simple pack consisting of a transmitter and a receiver unit with link wire costs £99. Extra receivers cost £49 each (with wiring).

### **BRANDS AND THE SPARES GUIDE**

Teleton Electro (UK) Co. Ltd.'s parent company The General Corporation has adopted the new corporate name Fujitsu General Limited. Fujitsu General will replace the General brand name. Both Fujitsu General and Teleton branded goods will be sold in the UK.


Our TV/VCR Spares Guide, published with the April issue, should have given Technical and Optical Equipment (London) Ltd. as the source of spares for Rigonda sets, not Zenith International. The address and telephone number given were correct.

Information and spares for the Lincoln 35C, about which several readers have asked, are available from Nikkai Imports Ltd., Regents Park House, 45 Byron Street, Leeds LS2 7Q5 (0532 441 640). Spares for Harwood TV sets, which were distributed by Harman Isherwood of Leeds, are available from Jackson Products Ltd., 18th Floor, Station House, Harrow Road, Stonebridge Park, Wembley, Middx HA9 6DE (01-900 0433). This firm can supply only to bona fide trade customers. Spares for Cihan (pronounced GeeHan) and Aro sets are available from Key Electronic Services, 10 Hey Street, Bradford, W. Yorks BD7 1HS (0274 370 348). The Cihan brand was used by Greens and the Aro brand by Makro.

We have been asked by Willow Vale Electronics to point out that they are the sole UK distributors appointed by Sharp (UK) Ltd. Wizard Distributors should not have been listed as an official Sharp spares distributor.
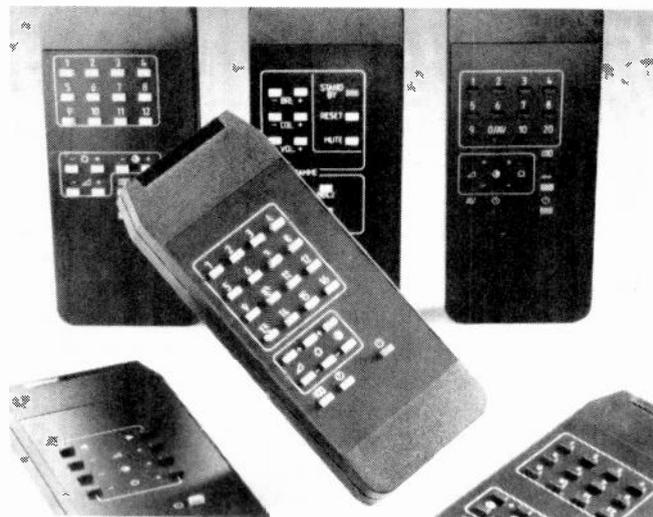
### **AMPMACE REMOTE CONTROL UNITS**

Ampmace (Beechwood House, Falkland Close, Coventry CV4 8HQ) have introduced a range of remote control units which can be used for replacement purposes with TV sets and VCRs from various manufacturers. Ampmace point out that the demand for remote control units is increasing as more and more remote control TV sets appear in the second-hand market and as original



*Some of the range of Ampmace remote control units.*

handsets are damaged or lost. Units currently in stock are suitable for use with Decca, Ferguson, JVC, Philips and Grundig TV sets. The range is to be expanded to cover ITT and Sony sets, Ferguson VCRs and various continental models. Trade prices are £14 plus VAT for ultrasonic units and £14.50 plus VAT for infra-red units.

### **NEW MASTHEAD AMPLIFIER**

The UP3302 is the latest addition to the Antiference range of masthead amplifiers. It provides high gain at u.h.f. with a v.h.f. bypass that doesn't require termination if not used. The two-stage amplifier provides a gain of 27dB at u.h.f.,  $\pm 2$ dB, with a noise figure of 2.5dB and "exceptionally good" VSWR characteristics. Remote power can be taken from a base power unit or a distribution amplifier with 12V line output, e.g. the Antiference XS6/32. Provision is incorporated to line power a masthead v.h.f. amplifier via the U3302. The retail price is £18.50 plus VAT.

### **SONY MIC FOR VIDEO-8 USE**

Sony has introduced an electret condenser microphone for use with its complete range of Video-8 camcorders. The ECM-K120 has variable directivity – the response can be supercardioid, unidirectional or omnidirectional – and is powered either by battery or from the camcorder. A special suspension for the pickup capsules and receptacle damper reduce the effect of contact noise or vibration from the camcorder. The plugs are gold-plated to provide quality connections.

### **IN BRIEF**

Amstrad has withdrawn from participation in British Satellite Broadcasting, the UK DBS venture. BSB has been awarded a separate fifteen-year franchise to provide advanced teletext on three DBS channels . . . Mullard is investing some £15m at its Durham TV tube plant to extend production to include high-resolution data graphic display tubes. Production will initially concentrate on 90° 14in. DGD tubes and is expected to reach an annual level of a quarter of a million tubes by the end of 1988 . . . Kodak has announced the availability in the UK of its Megaplug camera. This is an advanced solid-state monochrome camera with the high resolution of 1.4 million pixels. It's intended for industrial and scientific applications.

# TV Fault Finding

Reports from J.K. Potts, Guy W.E. Mundy, T. Eng., Hugh MacMullen, Mick Dutton, Steve Leatherbarrow, Lawrence Ingram and G.C. De Fraine.

## Decca 110 Series Chassis

These sets have proved to be quite reliable apart from occasional failure of the e.h.t. tray which can be replaced with a standard type. This is usually all that's required. Recently however one came in with the usual faulty tray but damage to the chopper power supply had occurred. On inspection we found that the d.c. fuse F601 has blown, the fusible resistor R627 in the start-up circuit was open, and both the chopper transistor Tr605 and transistor Tr604 in the driver stage were short-circuit. Tr604 is type BSR59 and it turned out to be very difficult to get a replacement. It's a special device with a fast-switching junction and seems to have been discontinued. We eventually had to go to Tatung who supplied a Ferranti FST164K5. On fitting this the set was back to normal, but a lot of delay and telephone enquiries had been involved.

J.K.P.

## Grundig 6632GB

We've had several of these older remote control models with the same symptoms: set on permanent standby, won't switch on but the channel numbers change. In each case the problem has been due to Tr1341 (BC548B) on the self-seeking module being leaky.

G.W.E.M.

## Fidelity ZX3000 Chassis

The problem with this set was predominantly green/pink pictures with occasional surges of green saturation. A scope check on the colour bars at the base of the green output transistor revealed "squashed" green chroma. R224 (100k $\Omega$ ) which biases the base of the green driver transistor TR14 had risen in value to 203k $\Omega$ .

G.W.E.M.

## Zanussi 22Z616

This modern stereo TV set would start to display a white hum bar and a slightly reduced picture size, with the power supply "chirping", after about four hours' use. It would then switch to standby and would subsequently restart and run again. Obviously the fault was a thermal one. Use of the hairdryer/freezer technique established that the TDA4600 switch-mode power supply control chip IC301 was faulty.

G.W.E.M.

## Sony KV1810UB

This set suffered from severe field cramp when the back was on. It was a difficult fault to find. The culprit eventually turned out to be the coupling electrolytic C522 (22 $\mu$ F, 16V) which became leaky at a certain critical temperature.

H.MacM.

## Rank-Toshiba T24 Chassis

This has proved to be an extremely reliable chassis. One problem is the lack of a field shift control. If there's slight field cramp and the picture is a bit low, increasing the value of C317 in the feedback circuit from 2.2 $\mu$ F to 4.7 $\mu$ F will put matters right.

No chroma is usually caused by R229 (3.6k $\Omega$ ) going open-circuit.

An occasionally snowy picture can be caused by plug

501 from the tuner to the i.f. strip being dirty – you can't see this, it looks so clean from the outside.

H.MacM.

## Sharp 12P41

Lack of height with cramping at the top and bottom can be caused by a dry-joint on the deflection coils subpanel where there's a centre-tap connection.

H.MacM.

## Philips G11 Chassis

This set had no chroma – whenever I left the customer's house. I eventually discovered that connection 17 on chroma/luminance module U6200 had never been soldered.

H.MacM.

## Ferguson TX90 Chassis

The height on this portable was a trifle enthusiastic – we estimated about 18ft. On one shot we were trying to work out what the silvery object that covered a third of the screen was – it turned out to be a man's belt buckle! A BZV85 68V zener diode in the field output stage read normal in the forward direction and 18k $\Omega$  in reverse. Replacing it cured the fault. Before finding this one I had tried changing the field output transistors – note that the zener diode is not present in earlier production models.

Another of these sets went into shutdown periodically, needing to cool for ten minutes or so before it would work again. Due to the nature of the fault it was some time before we discovered that the regulator was the culprit. Freezer and heat had little effect.

S.L.

## Philips KT3 Chassis

A variety of highly intermittent and unpredictable faults on these sets with the tuner preset draws have been encountered – all sorts of colour variation and tuning change etc. on one or more channels. None of the usual methods of fault provocation seem to work and the only cure is to plod through all the plug pins and sockets on the selector and tuner panels, soldering and adjusting every one of them.

L.I.

## Grundig CUC220 Chassis

The complaint with this set was white lines at the top when hot – it would show up only in a warm room with the back cover on. A puff of freezer on the TDA2655B field timebase chip revealed the culprit.

L.I.

## Blaupunkt FM120

A common fault with this model is sound and h.t. present but no e.h.t. You will probably find the 18 $\Omega$  wire-wound resistor in the feed to the BU208D line output transistor open-circuit. Check the line output transistor before replacing the resistor, and remember the c-c reading due to the diode in the BU208D.

In one of these sets the 18 $\Omega$  resistor was open-circuit and the BU208D was leaky. After a check on the line drive we switched on. Enormous sparks came from the focus tag on the line output transformer and the internal

resistors were found to be very low in value. A new transformer had to be fitted. **L.I.**

### Philips KT3 Chassis

There was no h.t. and no output from the TDA2581 chopper control chip. The U470 chopper module was removed and the 12V supply to the chip was checked – it comes from the junction of R300, C300 and zener diode D300 on the U450 mains rectifier panel. The zener diode (12V) was found to be open-circuit and further investigation showed that the print from R298 runs between the tags of C300. A minute amount of carbon was found here. The print was cut out and bridged and D300 and C300 were replaced. The chip failed almost immediately after switching on so this also had to be replaced. **L.I.**

### Sony KV1320 Mk. 1

I get quite a number of sets that are brought down from London by owners of weekend cottages etc., also a number of Sonys which have been turned away elsewhere. This set fell into both categories. It had not been used for some while and was partly dismantled. Someone had broken the e.h.t. rectifier – a 3AT2 valve in the Mk.I version – and had given up. With this replaced and the set reassembled it seemed to work very well. After a long test it went back to London – to reappear a few weeks later. “Gradually goes dark” was the complaint this time, and after three days it did indeed go dark. Touching board P restored the brightness and it took ages to go wrong again. Careful probing then led us to the tube’s screen voltage control VR602. To be on the safe side a new one was fitted. **R.B.**

### Plustron Palladium C14ENS

Twice the e.h.t. stick arced over to the screening can, killing the TA7146P intercarrier sound chip. I removed the can and cut up an old Pye hybrid chassis focus control to enclose the stick fully and stop any further fireworks. **R.B.**

### Fidelity ZX3000 Chassis

The problem with this colour portable was that if it was left for more than a day or two it would start up with screams of protest from the line output stage, eventually settling down and working normally from then on. A raster with a foldover could sometimes be seen. After trying a new line output transformer we found that replacing the BU508A line output transistor cured the problem. I must say that I’ve not come across this sort of behaviour due to a line output device before. Incidentally the set was very badly affected by nicotine: when I washed the back half of the cabinet shell in soapy water I found that it was silver, not a jaundiced yellowy-grey.

The ZX3000 is also used as the basis of some computer monitors (Prism for one). The owner of one of these had been fiddling with the first anode control and had split the slot with an unsuitable screwdriver. I just managed to reset it correctly with a pair of pliers. **R.B.**

### Philips K40 Chassis

The problem with this set was a predominance of blue. Faint blue flyback lines were also visible. Checks on the tube base panel showed that the fault lay in the blue

output stage, since the output transistor’s collector voltage was low at 100V instead of 160V. The base voltage was correct and the emitter voltage was slightly out. We checked the values of the resistors in the blue channel in comparison to the other two channels but could find no differences. After disconnecting everything in turn we discovered that the h.f. compensation capacitor C2216 was leaky (about 400 $\Omega$ ). This didn’t show up in circuit because there’s a series resistor. Replacing C2216 provided a cure. **M.Du.**

### Panasonic TC2201

The complaint was no picture with a funny noise on the sound. When we switched the set on there was indeed no picture and the funny noise was loud motorboating. Use of a can of freezer proved very helpful: when the AN331 a.g.c./sync chip IC301 was squirted the picture and sound returned to normal. A replacement chip put matters right. **M.Du.**

### Thorn 1590 Chassis

The complaint with this set was that the picture shrank from the bottom when it warmed up. We tried just about everything in the field driver and output stages without success. The cause turned out to be the field oscillator isolating diode W3. It measured perfect out of circuit but a replacement cured the fault. **M.Du.**

### Toshiba C2290B (Rank T24 Chassis)

This set suffered from very grainy pictures. We at first suspected the tuner as we’ve had many similar repairs due to lightning damage. In this case however the tuner was blameless: the cause of the fault was a dry-joint on the tuner coupling coil 1L31. **M.Du.**

### NordMende T4231/Ferguson 3787

The complaint with this set was that it died after about fifteen minutes. This was indeed the case and we found that regulation thyristor DU11 (type 17058) was the culprit. It was going open-circuit when warm. **M.Du.**

### Panasonic TC2203 (U1 Chassis)

There was no output from the power supply. The chopper transistor Q801 was found to have 325V at its collector but nothing at its emitter. There was no voltage at its base either as R832 (150 $\Omega$ ) had gone open-circuit. **M.Du.**

### Ferguson TX90 Chassis

The set came in with the complaint of intermittent loss of picture and sound. It ran for two days before the fault put in an appearance, then the slightest touch on the board restored normal operation. No tapping or movement would make the set go off again. When the next failure occurred the tube’s heaters went out, there was no focus voltage and the readings at the collectors of the RGB output transistors were low at 95V. Eventually the set failed completely – just as well or I’d still be looking! It turned out that the winding between pins 9 and 6 of the line output transformer was open-circuit, but to add to the confusion pin 9 was internally shorting to pins 5, 7 etc. Hence a 95V h.t. rail. What had happened inside that transformer I shall never know. **G.C.DeF.**

# Getting Started with Satellite TV

John Hopkins


Having made the decision to become the first stockist of satellite TV receiving equipment in Felixstowe I sent off an order, with cheque, to a supplier. That was on November 7th. Exactly twenty days later a small white delivery van drew up outside to deliver the goods for my latest venture.

We unloaded the four parcels and carried them into the shop in the fond hope that we might find everything labelled with full instructions enclosed. But alas we should have realised: Murphy's Law still governs all new ventures!
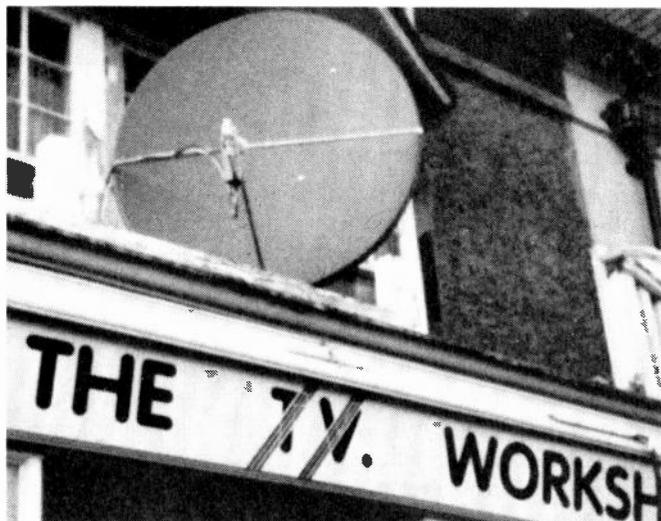
## Aerial Assembly

The aerial assembly comes in three parts, the dish itself which we instantly recognised, the stand assembly which had clear instructions, and the polar mount which is where the supplier started to lose interest. We followed the instructions up to the point where we had a perfect stand assembly. The next step was to attach the dish to the polar mount by means of four long bolts. This was where Murphy's Law started to apply. Unfortunately the top two bolts have to be longer than the bottom two because the top rib is longer and has a bracing strut to fit on to it. This item is referred to as part reference E, with no further explanation. Also supplied is part reference F, which is shown as a short length of flat strip steel rounded off at one end, with two holes at the square end and one hole at the round end. This turned out to have two holes, both of which were square, at each end.

We decided to assemble the dish in the shop for two reasons. First to see how it went together. Secondly customers might come into the shop to see what we were up to – and might actually buy something. After a quick trip to the local builders' merchants for the correct length bolts we followed all the instructions and found that we had a bit left over. It was a long bar of black steel, 22.5 × 1in., with a large hole at one end and a small hole at the other. It acts as a bracing strut between parts E and F, but we first had to make a further trip to the builders'



Success – the dish assembly on the balcony above the shop.

merchants for a bolt to secure the small hole to part E.

Now we had only to secure the feedhorn to the dish, using the three steel rods provided. So we unpacked the final parcel and there it was – gone! We had ordered an inclinometer so that we would have everything ready for installation by the date we had advertised but this and the feedhorn had not been delivered. They came two days later, via the postman. The feedhorn had three wires hanging from it, coloured red, white and black. These obviously went to the earth, pulse and +5V connections on the receiver, but which way round? A phone call to the supplier gave us a hint. "If you look at the back of the receiver you'll see that there are three connections, red, white and blue." "But mine are red, white and black." "Yes but we remember it easier as red, white and blue." So I asked him which colour went to +5V and he said he didn't know but they connected as red, white and blue in that order. Nice to find that we all know what we're talking about even if we haven't the faintest idea what we're doing.

## Switch on

The dish was reassembled in the back yard and everything was connected up. So I decided to take the plunge. Using a long stick I poked at the on-off switch. Well not quite, but I did feel that I might be about to destroy something I was not sure about. Just to be on the safe side I had left the feedhorn wires off when I switched on. Then I switched off, connected the wires, and switched on again. Sure enough the signal strength indicator light dimmed. I quickly switched off and connected the wires as follows: red to +5V, white to pulse, black to ground. The light came up to full brightness again and I prayed to forgotten gods that I hadn't destroyed anything.

## Finding a Satellite

Now we come to the bit that counts. As I write this I've finished my first installation and can afford to say it's not too bad, or you just do this and then that. Don't you believe it! Imagine a piece of paper about four inches square with a pin hole somewhere in it and that you have to find the hole using a pin while blindfolded. If you start tracking at the top left-hand corner and move to the right then back again you'll eventually find it, but if your satellite is the hole and the dish is the pin you also have to have your receiver correctly tuned to the satellite TV signal and correct polarity alignment. Get either of these wrong and you can go right past the satellite without noticing it.

We set the stand on level ground and checked that it was not only level but that the centre pole was straight on all sides, using a spirit level, then mounted the dish and pointed it due south. Right at the building next door! I decided to give up for the day and went in for my tea.

## Next Day

Next day I set the receiver to number five and by using a small, short-range walky-talky managed to get a very

poor patch of light in the centre of the screen. At this point a small warning: don't fit an aerial to the u.h.f. input of the satellite receiver or you may find you're trying to tune in the BBC or ITV. We tried tuning in the satellite receiver and at about three we got RAI. This is an Italian station on the lines of ITV and comes through quite sharply, though the sound is a bit paper-and-combish. By slight adjustments to everything on the dish we were able to get the best we were going to unless we pulled down our neighbour's shop, so we decided to move the dish.

For the rest of the day we moved the dish all over the yard and the shop next door moved with us. Fortunately we have a small balcony over the top at the front of the shop, and a quick trip with the compass confirmed that we would have a clear view to the south if we pulled down part of the balcony rail.

Another day dawned on this Herculean task and saw us repeating the whole exercise on the balcony. This had the advantage of shorter cables, and we were really beginning to feel confident. It seemed that we had RAI in no time at all, and this time it was better than the local station.

### Polarity

Then we hit the next snag! We had RAI, Europa (it was still on then) and TV5, also a very poor (scrambled) Sky. But where were all the other stations? There's a polarity button on the front of the receiver, but pushing this didn't seem to do anything. Time for another call to

our suppliers. The chap there told me that when I'd connected my red, white etc. leads I'd jammed the polarotor motor. He told me to take it apart and, using a pair of needle pliers, turn the motor manually to free it. I didn't like the idea of doing this but tried it anyway and was rewarded by a motor noise when the polarity switch was pressed. Lo and behold we'd a lot more stations to look at, including Music Box – a 24-hour pop music program in English.

### In Conclusion

I won't bother you with the number of days that passed by. We had snow, rain, Christmas and the New Year. Somewhere along the line we found another satellite, about 40° to the right. This gave us Premier with movies, the Children's Channel, CNN news, Screen Sport and Lifestyle. One final note: the bracing strut between E and F has to be drilled in several places, and there's a certain amount of play in all the joints – this has to be allowed for in the final adjustments. All in all it turned out to be a very worthwhile project, and having done it once I now know that I can save time by tuning in the customer's TV set and receiver to the dish in a matter of minutes and that the dish will be easier to align because I know where to point it.

Hopefully this account of my comedy of errors will encourage others to have a try at this product, because it really is here to stay.

## Test Pattern Program for the Vic 20

Bill Brown

Various computer test pattern programs have appeared in *Television* in the past, but I've yet to spot one for the Commodore Vic 20 – until now!

Like the Commodore 64, the Vic 20 has a screen border which can't be used for display. This can be overcome by using double-height, user-defined graphics and altering the number of rows and columns, then recentring the display. A total of ten screen displays is instantly available after running the following program. This is made possible by redefining the characters used rather than by redefining the entire screen. In lines 90-120 press keys f1, f3, f5 and f7 as indicated between the quotes: do not type f1 etc. Further improvements could be incorporated, e.g. sound, colour bars, etc., but a grey scale is not available with the Vic 20.

The patterns are called up as follows:

Key pressed	Effect
1	Changes display to black characters on white screen
2	Changes display to white characters on black screen
f1	Displays horizontal lines
f3	Displays vertical lines
f5	Displays crosshatch
f7	Displays dot matrix
Any other	Displays combined crosshatch with dot matrix

I've found this program to be very useful when setting up the convergence in the absence of an off-air test

pattern display and hope that others will also find it a useful servicing aid. I would expect that the idea could be adapted to suit other computers, but if so the locations would have to be changed.

### Program

```

10 POKE 36879,25:POKE 36869,255:POKE 52,28:POKE
56,28: CLR
20 X=7680:Y=8185:Z=30720:H=36864:V=H+1:C=V+1:
R=C+1:MS=7168:ME=7183
30 FOR A=X TO Y:B=A+Z
40 POKE A,0:POKE B,0: NEXT
50 GOTO 240
60 GET I$:IF I$="" THEN 60
70 IF I$="1" THEN POKE 36879,25: GOTO 60
80 IF I$="2" THEN POKE 36879,17: GOTO 60
90 IF I$="f1" THEN 200
100 IF I$="f3" THEN 210
110 IF I$="f5" THEN 220
120 IF I$="f7" THEN 230
130 GOTO 240
200 FOR L=MS TO ME: POKE L,0: NEXT: POKE 7175,255:
POKE ME,255: GOTO 60
210 FOR L=MS TO ME: POKE L,16: NEXT: GOTO 60
220 FOR L=MS TO ME: POKE L,1: NEXT: POKE 7175,255:
POKE ME,255: GOTO 60
230 FOR L=MS TO ME: POKE L,0: NEXT: POKE 7171,16:
POKE 7179,16: GOTO 60
240 RESTORE
250 FOR J=0 TO 15: READ E: POKE MS+J,E: NEXT
260 POKE V,13: POKE H,7: POKE R,37: POKE C,156:
GOTO 60
1000 DATA 1,1,1,17,1,1,1,255
1010 DATA 1,1,1,17,1,1,1,255

```

# ECONOMIC DEVICES & QUICK SAVE T.V. SPARES

1580H	3.71	2SA940	0.58	2SC535	0.79	AF180	0.55	BA656	5.46	BC560C	0.14	BDX63A	1.96	BFY52	0.27	BYX71-350	1.40
1585R	3.30	2SA940-2	2.14	2SC536	0.33	AF181	0.53	BA7100	11.35	BC635	0.36	BDY20	1.21	BFY79	0.49	BYX94	0.16
16039	0.79	2SA950	0.72	2SC537	1.16	AF186	0.53	BA841A	28.98	BC636	0.42	BDY81	1.18	BFY90	0.60	BYX96	1.20
16181	1.04	2SA951	1.26	2SC605L	1.16	AF279	0.43	BA843	3.96	BC637	0.24	BF115	0.20	BLY49	2.21	BZ93C30	1.86
16182	1.04	2SA966-Y	1.16	2SC620	1.46	AF279	0.43	BA854	5.76	BC639	0.20	BF117	0.66	BR100	0.22	BZ98 RANGE	0.10
16334	0.98	2SA999	1.36	2SC643A	1.56	AF279	0.43	BA854	5.76	BC640	0.24	BF118	0.67	BR101	0.65	BZ61 RANGE	0.18
16335	0.94	2SB774	1.15	2SC668	0.67	AN113	1.36	BAV19	0.11	BC879	0.39	BF121	0.25	BR103	0.75	BZ79 RANGE	0.10
16446	0.98	2SB785	1.13	2SC681	4.40	AN115	3.98	BAV20	0.31	BC880	0.31	BF123	0.21	BR303	1.23	CI06D	0.46
16600	1.38	2SB785	3.87	2SC682	1.89	AN155	1.89	BAV21	0.34	BCX34	0.40	BF127	0.13	BR303	1.23	CI06M	0.76
16802	1.27	2SB800	0.40	2SC684	1.65	AN206	2.58	BAW62	0.19	BCY70	0.30	BF137	0.29	BR300	2.01	CI129	0.58
17052	5.61	2SB405	1.03	2SC693	0.63	AN208	3.55	BAX12	0.44	BCY71	0.21	BF153	0.58	BR300	2.01	CI206	2.55
17053	5.61	2SB449B	6.98	2SC710	0.69	AN210	2.28	BAX13	0.11	BCY72	0.20	BF154	0.26	BR300	0.77	CA3089	0.83
17074	9.30	2SB511	2.50	2SC711A	0.50	AN211	3.25	BAX16	0.11	BD115	0.46	BF157	0.33	BR302	1.08	CA3090AQ	3.25
17089	3.45	2SB54	1.39	2SC717	1.28	AN214Q	2.75	BC107	0.13	BD116	0.70	BF158	0.18	BR303	2.19	CA3094	2.20
17127	3.51	2SB546	3.75	2SC734	1.43	AN234	5.52	BC107A	0.11	BD124	1.31	BF159	0.18	BR304	2.08	CA3131EM	3.12
17376	1.58	2SB56	2.90	2SC761-Y	0.95	AN236	3.52	BC107B	0.18	BD124P	0.69	BF160	0.31	BR304	2.08	CBF16848N-071	1.56
17524	1.32	2SB618A	2.22	2SC783	3.98	AN239	6.95	BC108	0.15	BD131	0.57	BF167	0.38	BR304	0.67	CD4001	0.34
1N4001	0.06	2SB631	0.61	2SC790Y	1.73	AN240P	1.52	BC108B	0.15	BD132	0.42	BF173	0.34	BR309	0.69	CD4002	0.27
1N4002	0.06	2SB669	3.67	2SC828	1.28	AN241	1.71	BC109	0.12	BD133	0.53	BF177	0.35	BR309	0.69	CD4008	1.35
1N4003	0.06	2SB681	3.95	2SC867A	3.84	AN245	4.49	BC109B	0.15	BD135	0.36	BF178	0.40	BSB38	5.87	CD4011	0.29
1N4004	0.06	2SB695	1.98	2SC876	0.96	AN253	2.97	BC109C	0.12	BD136	0.26	BF179	0.36	BSTC024E	6.99	CD4012	0.24
1N4005	0.08	2SB75	1.04	2SC930	0.54	AN260	3.85	BC113	0.14	BD137	0.36	BF180	0.36	BSTC0233	7.25	CD4013	0.33
1N4006	0.08	2SB774	0.61	2SC935	4.13	AN262	1.98	BC119	0.26	BD138	0.46	BF181	0.32	BSTC0143	3.07	CD4016	0.46
1N4007	0.07	2SB819	0.89	2SC936	8.66	AN272	7.92	BC126	0.23	BD139	0.34	BF182	0.34	BSTD1043	2.85	CD4017	0.82
1N4148	0.03	2SC1034	6.75	2SC940	4.98	AN281	6.65	BC132	0.14	BD140	0.29	BF183	0.43	BSV57B	3.69	CD4020	1.23
1N4448	0.05	2SC1050	5.06	ZSD1128	2.30	AN285	5.52	BC135	0.14	BD144	1.20	BF184	0.39	BSW68	0.80	CD4021	0.39
1N5401	0.14	2SC1096	1.16	ZSD1138	0.84	AN301	3.60	BC137	0.18	BD150	1.25	BF185	0.39	BSX19	1.29	CD4023	0.28
1N5402	0.15	2SC1104	3.98	ZSD1273	1.36	AN302	3.99	BC138	0.34	BD157	0.67	BF194	0.14	BSX20	0.34	CD4025	0.64
1N5403	0.16	2SC1106	4.54	ZSD1453	5.39	AN303	4.29	BC139	0.28	BD160	1.60	BF195	0.14	BSY52	0.50	CD4028	0.84
1N5404	0.15	2SC1114	3.25	ZSD152K	2.64	AN305	8.95	BC140	0.45	BD163	0.71	BF196	0.17	BSY79	1.51	CD4040B	0.85
1N5408	0.35	2SC1116	4.35	ZSD198	3.87	AN315	2.46	BC141	0.34	BD165	0.62	BF197	0.18	BT100A	0.61	CD4047	1.06
1N914	0.04	2SC1124	1.28	ZSD234	0.49	AN316	5.53	BC142	0.34	BD166	0.42	BF198	0.17	BT106	1.55	CD4049	0.46
1R3403	5.00	2SC1129	0.34	ZSD235	0.60	AN318	5.44	BC143	0.19	BD168	0.73	BF199	0.17	BT108	1.45	CD4052	0.75
1S1555	0.31	2SC1131	0.64	ZSD254	2.29	AN320	5.47	BC147	0.08	BD175	0.60	BF200	0.37	BT119	1.76	CD4066	0.30
1S44	0.10	2SC1158	3.33	ZSD257	2.94	AN321	2.25	BC148A	0.10	BD179	0.49	BF218	0.36	BT120	2.17	CD4069	0.29
1S5012A	0.81	2SC1162	1.05	ZSD292	2.59	AN322	5.85	BC148B	0.13	BD181	0.99	BF224	0.17	BT121	2.48	CD4070	0.66
1S921	0.10	2SC1172	2.22	ZSD313	2.59	AN331	4.59	BC148C	0.11	BD182	0.99	BF237	0.65	BT123	1.98	CD4081	0.35
2N1303	0.38	2SC1195	5.80	ZSD325D	2.26	AN337	3.81	BC149	0.11	BD183	0.99	BF240	0.17	TBA970	3.06	CD4093	0.72
2N2219A	0.33	2SC1212A	1.97	ZSD348	16.13	AN340P	1.17	BC149B	0.13	BD184	1.21	BF241	0.17	BT151-800R	0.89	CD4511	1.10
2N2222	0.38	2SC1213	0.89	ZSD350	5.20	AN355	5.98	BC153	0.14	BD187	0.53	BF245	0.50	BT16018	4.42	CD4528	2.04
2N2646	0.80	2SC1226	1.46	ZSD350A	2.80	AN362	1.75	BC154	0.14	BD189	0.69	BF245A	0.52	BT18124	2.89	CD4556	1.47
2N2904	0.36	2SC1293	0.90	ZSD353	8.38	AN370	3.95	BC159	0.36	BD190	0.69	BF245B	0.49	BU106	2.48	CRV2AM-8	1.55
2N2905	0.43	2SC1306	1.38	ZSD389	2.41	AN5010	5.70	BC160	0.40	BD201	0.98	BF246A	2.52	BU108	1.50	CR12E	4.09
2N2906	0.38	2SC1316	10.25	ZSD401	1.55	AN5111	2.92	BC161	0.28	BD202	0.60	BF255	0.20	BU109	2.65	CX095D	3.14
2N2926	0.15	2SC1317	0.87	ZSD414	1.98	AN5120N	4.50	BC168	0.36	BD203	0.50	BF256	0.38	BU110	5.89	CX104	9.64
2N3053	0.27	2SC1364	0.49	ZSD471	2.13	AN5132	4.39	BC169C	0.16	BD204	0.61	BF256LB	0.42	BU111Y	4.16	CX108	10.50
2N3054	0.99	2SC1383	1.20	ZSD588A	2.95	AN5250	3.98	BC170	0.16	BD207	1.79	BF256LC	0.42	BU125	2.48	CX109	7.86
2N3055	0.61	2SC1391	2.45	ZSD600	2.36	AN5435	3.08	BC171	0.11	BD208	0.34	BF257	0.34	BU126	1.25	CX130	8.76
2N3442	1.56	2SC1398	0.94	ZSD601R	3.25	AN5610	2.85	BC172	0.13	BD222	0.49	BF258	0.36	BU137	6.53	CX134	12.32
2N3702	0.14	2SC1413A	3.05	ZSD613	0.65	AN5612	4.68	BC172B	0.27	BD225	0.49	BF259	0.34	BU205	1.08	CX136	11.49
2N3703	0.18	2SC1446	1.25	ZSD613	1.03	AN5613	4.63	BC173	0.17	BD228	0.63	BF262	0.57	BU206	1.27	CX139	11.83
2N3705	0.16	2SC1447	2.07	ZSD621	12.85	AN5630	3.95	BC174B	0.27	BD229	1.05	BF263	0.57	BU207	1.65	CX157	4.84
2N3706	0.14	2SC1475	0.37	ZSD636	0.55	AN5701N	1.66	BC177	0.35	BD232	0.50	BF271	0.34	BU208	1.46	CX158	5.52
2N3707	0.16	2SC1505	1.00	ZSD639-R	0.77	AN6250	2.95	BC178	0.26	BD234	0.42	BF273	0.20	BU208/02	1.97	CX177	6.46
2N3711	0.11	2SC1514	1.69	ZSD655	0.98	AN6300	4.40	BC179	0.26	BD237	0.47	BF274	0.20	BU208A	1.12	CX187	6.84
2N3717	1.71	2SC1578	8.74	ZSD657	3.50	AN6310	8.74	BC182	0.08	BD238	0.39	BF324	0.35	BU208D	1.95	CX755	12.95
2N3773	2.29	2SC1583	1.17	ZSD661A	0.80	AN6320N	4.28	BC182L	0.10	BD239	0.48	BF336	0.33	BU209	1.36	CX85A	6.85
2N3819	0.42	2SC1617	3.89	ZSD731	2.45	AN6340	11.00	BC182LB	0.14	BD240	0.37	BF337	0.40	BU226	2.95	DEC1	2.20
2N3823	1.17	2SC1675	1.41	ZSD773	0.33	AN6341	5.98	BC183L	0.11	BD241	0.39	BF338	0.33	BU326	2.00	DE2	2.20
2N3904	0.62	2SC1678	1.98	ZSD811	7.65	AN6342	1.61	BC183LB	0.26	BD242	0.39	BF355	0.29	BU326A	2.20	DS3486N	4.33
2N3908	0.62	2SC1741	1.25	ZSD823	1.98	AN6363	16.00	BC184	0.13	BD243A	0.33	BF362	0.66	BU326S	2.20	DS3487N	4.33
2N4101	1.73	2SC1810	1.70	ZSD837	1.98	AN6371	9.24	BC184L	0.14	BD243C	0.29	BF363	0.60	BU406	1.49	E1222	0.40
2N4240	3.30	2SC1815	0.66	ZSD841	3.65	AN6387	10.65	BC184LB	0.26	BD244	0.51	BF371	0.50	BU406D	1.79	E5024	0.28
2N4444	1.73	2SC1826	0.65	ZSD856	1.45	AN6531	1.95	BC186	0.27	BD244C	0.79	BF391	0.25	BU407	1.82	E5386	0.25
2N5293	0.50	2SC1829	3.34	ZSD857Q	1.84	AN6551	1.35	BC187	0.28	BD245C	0.99	BF417	0.84	BU407D	0.09	E9003	0.46
2N5294	0.50	2SC1875	5.85	ZSD882	1.50	AN6552	0.68	BC204	0.16	BD246C	1.25	BF418	1.87	BU412	1.15	ES005	0.50
2N5296	0.49	2SC1881K	2.98	ZSD894	1.63	AN6610	2.40	BC207	0.14	BD246	1.05	BF422	0.29	BU426A	9.13	ESM310BP	4.15
2N5297	0.50	2SC1893	3.02	ZSD898	3.45	AN6677	8.95	BC212	0.11	BD278A	0.80	BF423	0.52	BU500	1.95	FND500	5.78
2N5298	0.61	2SC1906	0.98	ZSK105H	2.15	AN7111	1.45	BC212B	0.26	BD317	2.60	BF450	0.35	BU508A	1.75	GC374	1.65
2N5771	1.18	2SC1921	1.37	ZSK152	2.95	AN7111E	8.54	BC213L	0.10	BD318	2.85	BF451	0.29	BU536	5.80	GD243	4.95
2N6109	1.58	2SC1923	1.07	ZSK34	0.76	AN7115	3.38	BC213LB	0.15	BD319	0.76	BF452	0.41	BU608	2.65	GF75	

# PO BOX 228, TELFORD TF2 8QP

# TEL 0902 712083

HA1374	4.80	LR3419	9.37	NE565N	1.33	SKE4F2/08	1.24	STK3042	10.25	TA7312P	2.45	TD62105P	2.50	TD3560	5.25	TJA2000	8.98
HA1377	4.98	LR3471	9.37	NE645BN	3.35	SKE4F2/06	3.35	STK3044	5.75	TA7313AP	1.36	TD62104P	1.36	TD3571Q	2.97	TV106	1.86
HA1389P	2.05	LU1141	7.27	NP1106	8.60	SKE4F2/10	0.85	STK4019	4.50	TA7314	5.94	TD62706P	4.50	TD3576	7.09	TV6010B	2.97
HA1392	2.39	LU52012	5.95	DA020	0.11	SKE4G2/02	0.96	STK430	11.75	TA7322P	1.15	TD10011P	2.35	TD3590	5.79	U055	1.14
HA1394	1.65	LU52011	14.95	OA47	0.16	SKE5F3/10	1.60	STK433	6.25	TA7325P	3.15	TD1003A	2.21	TD3591	6.45	ULN2204	11.45
HA1397	3.76	LU03112	12.37	OA95	0.09	SKS1/10	2.15	STK4332	8.25	TA7339P	1.75	TD1005A	5.06	TD3650	7.95	UPA53C	4.94
HA1398	3.98	M193	12.75	OC28	0.12	SL1310	3.14	STK435	5.94	TA7340P	1.06	TD1006A	2.22	TD3652	2.95	UPC1003	5.95
HA1406	2.97	M21C	1.13	OC29	2.95	SL1430T	2.95	STK4352	12.25	TA7607AP	3.10	TD1010AF	4.25	TD3651AQ	2.95	UPC1009C	8.95
HA1452	0.85	M23C	2.83	OC36	1.28	SL414	3.69	STK436	4.70	TA7609	3.20	TD1011	2.98	TD3651	1.95	UPC1025H	3.00
HBF4030AF	2.48	M293	6.95	OC44	0.35	SL432A	3.44	STK437	9.65	TA7611AP	4.80	TD1011A	2.98	TD3651A	2.75	UPC1026C	1.24
HD14538	2.07	M51102L	6.35	OC45	0.18	SL439	2.48	STK4372	3.85	TA7616P	5.25	TD1012	1.25	TD3650	2.95	UPC1028H	2.00
HD38702-A2	8.95	M5115P	5.24	OC72	0.44	SL471	4.78	STK439	7.25	TA7622AP	8.94	TD1011A	3.25	TD4050B	3.95	UPC1020H	2.77
HD38750A53	7.25	M51203L	3.15	OC75	0.44	SL480	3.98	STK441	10.25	TA7628P	5.06	TD1028	2.45	TD40280	7.20	UPC1032H	0.62
HD38750A-7	8.95	M51231P	0.95	DN236	1.06	SL490	2.44	STK443	10.25	TA7629P	7.50	TD10348	2.42	TD44290	4.47	UPC1042C	8.95
HD38800A50	14.09	M5134-9341	4.13	DN782	1.98	SL901B	6.95	STK457	13.45	TA7630P	2.98	TD1035T	1.85	TD44400	2.27	UPC1156H	2.96
HD44801A05	18.25	M51353P	5.25	OT121	1.45	SL918A	6.95	STK460	6.95	TA7672P	2.40	TD10375	1.78	TD44420	4.02	UPC1158	5.84
HEF4001BP	0.67	M51381P	5.09	PT6042	2.45	SN16861AN0	4.95	STK461	9.68	TA7676P	2.81	TD10370	2.05	TD44422	3.65	UPC1161C	4.50
HISH1010	8.59	M51393AP	9.35	PT8504	4.95	SN16862AN	2.98	STK463	11.53	TA7726P	10.25	TD1044	2.62	TD44427S	9.00	UPC1182H	1.22
HISH1004	6.00	M51394P	11.97	R1038	2.19	SN16966N	10.25	STK466	11.77	TA7726P	11.77	TD1044	2.05	TD44431	2.27	UPC1186H	1.00
HISH1002	9.50	M5142P	6.85	R1039	2.19	SN29717N	7.19	STK483	16.95	TA7726P	16.95	TD1047	4.10	TD44440	3.26	UPC1181H	1.25
HM6231	9.81	M5144P	4.25	R2008B	1.33	SN29716N	3.66	STK501	6.32	TA7726P	6.32	TD10598	0.98	TD44442	4.75	UPC1185H	1.95
HM6232	10.65	M51512L	2.55	R2009	1.98	SN29715N	3.66	STK502	5.74	TA7726P	5.74	TD1054M	1.35	TD44450	4.55	UPC1188	7.40
HM6251	6.25	M51515BL	3.23	R2010B	1.33	SN29722	11.55	STK531A	12.32	TA7726P	12.32	TD1060	2.60	TD44460	4.80	UPC1225H	3.25
HM7103	4.85	M51517L	3.71	R2029	1.33	SN29723AN	7.65	STK5730	3.95	TA7726P	3.95	TD1082	3.25	TD44620	4.78	UPC1230	5.24
HM9032	3.22	M5192	2.20	R2030	1.33	SN29764AN	1.38	STK7216	14.50	TA7726P	14.50	TD1151	1.22	TD45500	6.03	UPC1238	4.09
HM9012	3.22	M5194AP	5.74	R2257	3.71	SN29767	4.95	STK772	6.95	TA7726P	6.95	TD1170S	3.75	TD45700	2.75	UPC1239	4.09
HM9015	3.24	M5231L	1.95	R2265	1.49	SN29770B	3.84	STR1096	5.45	TA7726P	5.45	TD119E	4.87	TD47270S	2.25	UPC1277H	5.85
HT4207	17.16	M53274A	1.33	R2305	1.18	SN29772B	4.91	STR4090	11.98	TA7726P	11.98	TD119E	3.96	TD48190	2.47	UPC1278H	5.80
HT4208	18.25	M54532P	2.15	R2322	0.59	SN29771B	1.48	STR440	7.85	TA7726P	7.85	TD120C	2.52	TD49403	2.35	UPC1351C	1.80
IN5401	0.11	M54544P	4.75	R2323	0.76	SN29791	2.90	STR441	6.95	TA7726P	6.95	TA6232-600	0.79	TD49503	2.92	UPC1350C	1.41
IR2403	4.25	M58478P	8.77	R2354A	2.01	SN29798N	5.56	STR451	5.14	TA7726P	5.14	TA6262-600	1.20	TD49513	5.44	UPC1353	7.85
IR2C05	4.25	M58485P	13.65	R2354B	2.01	SN29799	0.44	STR453	8.56	TA7726P	8.56	TBA120AS	1.24	TD49513	2.68	UPC1355C	2.13
IR3P06	2.25	MA06	1.07	R2443	0.88	SN7400N	0.34	STR454	7.50	TA7726P	7.50	TBA120SB	1.05	TD49513	1.33	UPC1363	4.20
IR3P08	4.95	MA8001	0.82	R2461	1.50	SN7401N	0.36	STR6020	8.31	TA7726P	8.31	TBA120T	0.95	TD49513	1.05	UPC1362	2.98
IR94558	2.25	MA8003	1.16	R2540	1.95	SN7402N	0.65	TG029V	5.75	TA7726P	5.75	TBA120U	2.50	TD49513	2.55	UPC1365C	6.98
IS751	6.85	MB3705	1.98	R2540X	3.30	SN7404N	0.24	TG035V	0.73	TA7726P	0.73	TBA120V	1.05	TD49513	1.86	UPC1366	8.38
ITT425	0.18	MB3712	1.85	R2615	0.67	SN7408N	0.27	TG036	0.67	TA7726P	0.67	TBA1440	2.03	TD49513	3.30	UPC1360C	4.51
I20003GE	5.37	MB3713	1.69	RCA16029	2.01	SN7410N	0.22	TG037	2.11	TA7726P	2.11	TD1470P	1.62	TEA1020SP	8.21	UPC1378H	4.25
I20020GE	5.93	MB3730	2.94	RCA16600	1.38	SN74121	1.60	TG044V	0.97	TA7726P	0.97	TD1506	5.20	TIC106E	0.61	UPC141C	3.75
K174YP	4.36	MC13002	3.69	RCA16802	1.08	SN7413N	0.37	TG045	1.20	TA7726P	1.20	TD151H	2.80	TIC106M	0.57	UPC1458	2.86
KA2101	2.92	MC1310P	2.25	RCA17074	6.60	SN74141N	2.65	TG049	1.45	TA7726P	1.45	TD151E	3.99	TIC116Y100	2.07	UPC151C	2.95
KC581C	6.32	MC1327P	1.33	RCA17376	1.58	SN74151AN	1.51	TG052V	0.87	TA7726P	0.87	TD151E	1.10	TIC14	0.72	UPC2002	1.48
KC582C	3.97	MC1330P	2.88	RCA17524	0.83	SN74154N	1.27	TG058	3.08	TA7726P	3.08	TD155H	1.10	TIC45	0.77	UPC30C	2.51
KC583C	6.63	MC1350P	1.61	RCA17523	0.83	SN74190	1.35	TG059	2.77	TA7726P	2.77	TD155H	2.90	TIC47	0.35	UPC324C	4.17
L200CV	1.69	MC1351P	3.96	RCA2060	2.00	SN7420N	0.34	TG033V	1.25	TA7726P	1.25	TD157H	2.39	TD177H	3.85	UPC339C	4.90
LA1201	1.02	MC1352P	2.50	RGP01-15	1.65	SN7430	0.49	TG005V	2.38	TA7726P	2.38	TD1905	1.55	TD1910	1.76	UPC339C	4.90
LA1210	1.56	MC1357P	2.15	RGP10	0.30	SN7440N	0.27	TG011V	0.49	TA7726P	0.49	TD1908	1.30	TD1911E	0.85	UPC41C	4.10
LA1230	2.87	MC1358P	1.55	RGP30M	0.48	SN7472	1.54	TG013V	7.96	TA7726P	7.96	TD1940	1.95	TD1912	0.88	UPC458C	4.90
LA1352	2.87	MC14001	2.40	RT402	1.58	SN7474N	0.44	TG014V	2.60	TA7726P	2.60	TD1950	2.11	TD1917	0.95	UPC474	2.15
LA1357N	11.07	MC14013	0.41	RT905A	2.38	SN7490AN	0.93	TG016	1.92	TA7726P	1.92	TD2005	1.84	TD1921	0.87	UPC554C	1.85
LA1363	1.05	MC14493P	11.95	SI299	7.98	SN74LS26N	0.53	TG019V	1.58	TA7726P	1.58	TD2006	1.55	TD1926	0.73	UPC566H	2.95
LA1364	3.16	MC14494P	2.15	S175	31.48	SN76001N	1.65	TG034V	1.45	TA7726P	1.45	TD2007	1.30	TD1932	1.40	UPC574	3.25
LA1365J	1.44	MC14510BAL	3.75	S2062D	2.07	SN76013ND	1.50	TG035V	2.33	TA7726P	2.33	TD2008	0.27	TD1937	1.50	UPC575C2	2.40
LA1385	3.94	MC14511BCP	1.10	S2802	3.47	SN76023ND	5.15	TG051	1.95	TA7726P	1.95	TD2009	1.15	TD1939	0.75	UPC578H	2.58
LA1387	8.10	MC14528BCP	2.70	S2818	4.05	SN76033N	3.65	TG057V	0.70	TA7726P	0.70	TD2010	1.68	TD1940	0.46	UPC578C	8.70
LA1355	1.25	MC1712	3.88	S3702S	6.15	SN76110N	0.90	TG062V	0.49	TA7726P	0.49	TD2013	1.40	TD1943	0.63	UPC580C	4.13
LA3301	1.65	MC5192	19.50	S40V	16.68	SN76115AN	1.61	TG064	1.03	TA7726P	1.03	TD2140	1.60	TD1944	1.68	UPC587C	2.14
LA3350	3.89	MC7724CP	3.49	S6808B	8.80	SN76131	1.92	TG0602	4.35	TA7726P	4.35	TD2150	1.71	TD1945	0.75	UPC592H	1.35
LA3361	3.89	MC7818C	2.18	SAA063	5.17	SN76227N	1.33	TG0727	1.98	TA7726P	1.98	TD2151	2.07	TD1946	0.75	UPC595	2.95
LA3365	3.95	MCR1007	1.65	SAA1006	1.75	SN76226DN	1.90	TG0750	1.74	TA7726P	1.74	TD2160	4.13	TD1947	0.41	UPC596	1.98
LA3390	4.25	MCR106-5/6	0.95	SAA1020	4.76	SN76228N	3.27	TG0751	1.74	TA7726P	1.74	TD2161	0.87	TD1948	0.16	UPD1514C	8.95
LA4030P	2.20	MCR2707	2.28	SAA1025	4.40	SN76242	8.95	TG0754	2.55	TA7726P	2.55	TD2170	3.85	TD1949	0.34	UPD2819C	4.95
LA4031P	3.20	ME0402	0.17	SAA1024	2.81	SN76243	2.80	TG0760AP	0.71	TA7726P	0.71	TD2220	4.65	TD1951B	0.38	UPD4013B	4.95
LA4032P	2.35	ME0404/2	0.47	SAA1075	6.25	SN76396	9.50	TG0761AP	1.27	TA7726P	1.27	TD2250	2.65	TD1951C	0.50	UPD4066B	4.95
LA4100	1.25	ME0411	0.28	SAA1121	7.44	SN76532N	2.47	TG0765	3.13	TA7726P	3.13	TD2250	3.36	TD1952A	0.53	UPD553-164	19.25
LA4101	1.30	ME6002	0.26	SAA1124	3.25	SN76532N	2.95	TG0769	1.83	TA7726P	1.83	TD2252	2.47	TD1952B	0.69	UPD8049C-1	11.50
LA4102	0.81	ME6102	0.28	SAA1130	4.99	SN76545	3.87	TG0772P	5.87	TA7726P	5.87	TD2254	1.71	TD1953C	0.40	X0007TA	4.68
LA4112	2.56	ME8001	0.34	SAA1174	7.77	SN76546N	3.47	T									

# Series and Shunt Networks

S.W. Amos, B.Sc., C.Eng., M.I.E.E.

The star and delta networks shown in Fig. 1 are familiar to power engineers. They can be equivalent: in other words, provided the component values for one network are related to those of the other in a particular way the two networks have identical electrical characteristics. Thus for equivalent networks it's impossible to determine, from measurements made at the terminals, whether the components are star- or delta-connected.

These networks are also well known to electronic engineers of course, but usually appear differently in circuit diagrams. The star network is generally shown as in Fig. 2(a) and is known as a T network: the delta network is drawn in the form shown in Fig. 2(b), the pi network. Again the T and pi networks can be equivalent so that, given the component values used in one network, it's possible to calculate the component values needed in the other network to give identical characteristics. One of the two alternatives may be more suitable than the other for a particular application however. In this article we'll give some examples and show how to calculate the component values required.

Our first example consists of a two-stage amplifier with the transistors connected in cascade, see Fig. 3(a) – the circuit is shown in simplified form. The idea here is to apply negative feedback to improve the linearity but more particularly to make the amplifier's performance less dependent on the characteristics of the particular transistors used.

One way of applying negative feedback is to use a series-connected resistor, R3, between the collectors of the two transistors as shown. It's immediately apparent that R1, R2 and R3 form a pi network. An alternative approach is to use the shunt-connected resistor R4 to feed the two collector load resistors, as shown in Fig. 3(b). The three resistors now form a T network. In both circuits the

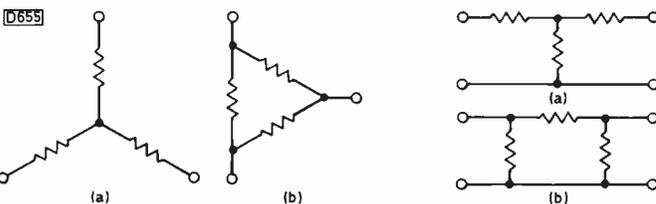


Fig. 1 (left): Star (a) and delta (b) networks.

Fig. 2 (right): The star network is better known to electronic engineers as the T network (a) while the delta network is better known as the pi network (b).

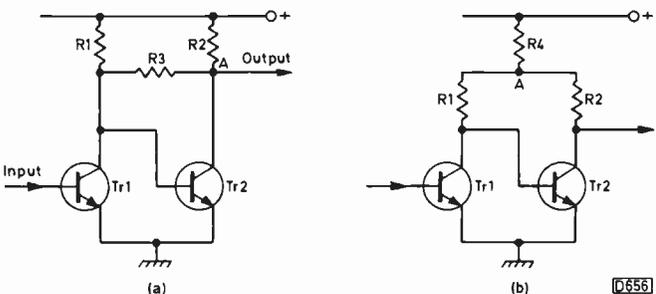


Fig. 3: Two ways of applying negative feedback to a two-stage amplifier, (a) by means of a pi network and (b) by means of a T network.

feedback affects Tr2 only – Tr1 is outside the feedback loop and serves only to introduce the input signal to Tr2.

In examining the behaviour of the two circuits shown in Fig. 3 we must remember that bipolar transistors are current-operated devices, even though they are often used as voltage amplifiers – an example of such an amplifier will be given later. We will consider the circuit therefore in terms of Tr2's input and output currents. We can calculate the effect of the feedback applied in circuit (a) in the following way. Tr2's effective collector load consists of R2 and R3 in parallel, but if the value of R3 is large compared to that of R2 its shunting effect can be neglected. Thus Tr2's collector current ( $I_{out}$ ) sets up a voltage  $I_{out}R2$  across R2: this voltage drives a current  $(I_{out}R2)/R3$  through R3. This is the feedback current  $I_{fb}$  that's applied to Tr2's base. Thus we have  $I_{fb} = (I_{out}R2)/R3$ , giving  $I_{out}/I_{fb} = R3/R2$ .

We'll assume that R3 applies a considerable amount of feedback. Thus the feedback current  $I_{fb}$  is many times the base current, and Tr2's input current  $I_{in}$  (which must be equal to the sum of the feedback and base currents) is very nearly equal to  $I_{fb}$ . We can thus say with little error that Tr2's current gain is:

$$I_{out}/I_{in} = R3/R2 = \text{feedback resistance/load resistance.} \quad (1)$$

The gain is therefore independent of Tr2's characteristics and is determined by the component values used in the negative feedback circuit.

Now consider the alternative circuit shown in Fig. 3(b). Tr2's output current  $I_{out}$  flows through R4, generating a voltage  $I_{out}R4$  which in turn drives a current  $I_{fb}$  of  $(I_{out}R4)/R1$  into Tr2. On the same basis as before we can

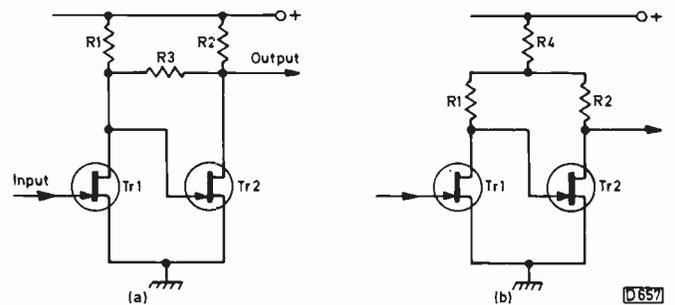


Fig. 4: Feedback arrangements as in Fig. 3 but this time with field effect transistors.

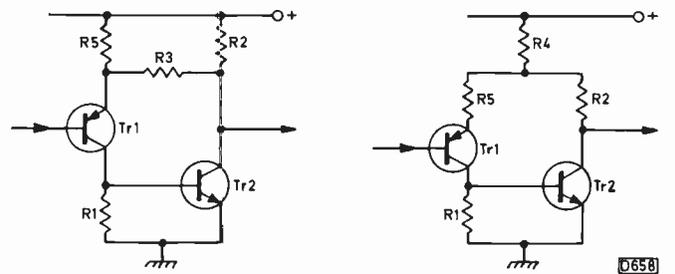


Fig. 5 (left): The arrangement shown in Fig. 4(a), but this time with complementary transistors.

Fig. 6 (right): Complementary bipolar transistor circuit with T network negative feedback.

say that Tr2's current gain is given by:

$$I_{out}/I_{in} = R1/R4 = \text{load resistance/feedback resistance.} \quad (2)$$

The current gain is once more independent of transistor characteristics provided the feedback is considerable.

Notice that in both circuits the current gain is equal to the ratio in which Tr2's output current is split at point A. This is a useful feature of this type of circuit, enabling the current gain to be deduced by simply checking the component values used in the current divider.

If the two amplifier circuits shown in Fig. 3 are to provide the same current gain we get, equating expressions (1) and (2),  $R3/R2 = R1/R4$ , i.e.  $R3R4 = R1R2$ . Thus the product of the feedback resistors is equal to the product of the collector load resistors.

The values of R1 and R2 are normally chosen to suit the required operating conditions for the transistors and the supply voltage. Thus for a given amplifier circuit their product is fixed and there's a reciprocal relationship between the equivalent values of R3 and R4 – the higher R3 is made, the smaller must be R4 to provide the same degree of feedback.

As an example, suppose R1 is 4.7k $\Omega$  and R2 3.3k $\Omega$ . The product is  $15.5 \times 10^6$ . We can now choose a value for R3 (or R4) to give the required gain. Let's choose to have a current gain of 5. Thus from expression (1) we would give R3 a value of  $5 \times 3.3k\Omega =$  approximately 16k $\Omega$ . If instead we chose the T network feedback circuit R4 would be  $(15.5 \times 10^6)/16k\Omega =$  approximately 1k $\Omega$ , a result which can be obtained just as easily from expression (2).

What happens if Tr1 and Tr2 are field-effect transistors or valves, i.e. voltage-operated devices? We can't in this case analyse the circuit behaviour in terms of currents because these devices respond only to the voltage applied to the gate or grid. Fig. 4 is a repeat of Fig. 3 with junction-gate field-effect transistors replacing the bipolar transistors.

In Fig. 4(a) R1 and R3 comprise a voltage divider across Tr2's load resistor R2, applying a fraction –  $R1/(R1 + R3)$  – of the output voltage  $V_{out}$  to Tr2's gate. If the value of R3 is large compared to that of R2, as is usual, the division ratio becomes approximately  $R1/R3$  and the feedback voltage is  $(V_{out}R1)/R2$ . Provided the feedback employed is considerable, this is almost equal to the input voltage  $V_{in}$  provided by Tr1. Thus  $V_{in} = (V_{out}R1)/R3$ , so that Tr2's voltage gain is given by:

$$V_{out}/V_{in} = R3/R1 = \text{feedback resistance/load resistance.} \quad (3)$$

In Fig. 4(b) the voltage divider across Tr2's output is formed by R2 and R4. The feedback voltage generated across R4 is applied to Tr2's gate via R1. Thus Tr2's voltage gain is given by:

$$V_{out}/V_{in} = R2/R4 = \text{load resistance/feedback resistance.} \quad (4)$$

In both circuits the voltage gain is given by the ratio of the two resistors that form the negative feedback voltage divider across the amplifier's output. Thus once more the feedback amplifier's voltage gain can be deduced from the values of these two resistors.

For equal voltage gain with the two circuits shown in Fig. 4 we have from expressions (3) and (4)  $R3/R1 = R2/R4$ , giving  $R3R4 = R1R2$ , which is precisely the same result we had with the bipolar transistor circuits. This general result is therefore applicable to all forms of active

device.

As an example, consider the circuit previously suggested, with R1 4.7k $\Omega$  and R2 3.3k $\Omega$ , giving a product of  $15.5 \times 10^6$ . This time we want the feedback to give us a voltage gain of 5 from Tr2. If we use a pi feedback circuit then from expression (3) R3 must be  $5 \times 4.7k\Omega = 23.5k\Omega$ . If we use a T network instead, R4 should be  $(15.5 \times 10^6)/23.5k\Omega = 660\Omega$ , a result which can also be obtained from expression (4). These values for R3 and R4 are not the same as those that were required to give a current gain of 5 – in fact use of expressions (1) and (2) would show that these particular values for R3 and R4 would give a current gain of 7.1. Thus for a particular circuit the voltage gain is not equivalent to the current gain. The disparity can in fact be enormous, as shown later.

### Choice of Circuit

Thus we have two possible ways of applying negative feedback in an amplifier circuit – by means of a pi-section or a T-section network – and by suitable choice of value for R3 or R4 both can be arranged to provide the same gain. Does one network have an advantage over the other?

If, in addition to establishing the gain and improving the linearity, the negative feedback is used to shape the frequency response, there may be a good reason for choosing one type of circuit rather than the other. For example, R3 in Fig. 3 and Fig. 4 could be shunted by a capacitor to increase the h.f. negative feedback, providing a response that falls as the frequency rises. To achieve the same result with a T-section network it would be necessary to add an inductor in series with R4. Connecting a capacitor in series with R3 would reduce the feedback as the frequency falls, giving a response that rises with decreased frequency. To obtain the same response with a T-section network an inductor would be required in parallel with R4. If a capacitor is connected in parallel with R4 the response rises as the frequency is increased. To obtain this result with a pi-section network an inductor would be required in series with R3. Since no one likes to use an inductor where a capacitor can be used to achieve the same effect, pi or T networks can be used depending on the shape of the required frequency response. It's significant that in each of these three examples a capacitor included in one network requires an inductor in the other to give the same frequency response shape.

### Two-stage Feedback

So far we've treated Tr1 as a source of signal for Tr2. It would clearly improve the linearity of the whole amplifier if Tr1 was included within the feedback loop. Doing this is simplified if Tr1 is of complementary type to Tr2, permitting direct connection between the collector of Tr1 and the base of Tr2. One possible arrangement is shown in Fig. 5. Tr1's collector load resistor R1 is now connected to the negative side of the supply. Its position in the pi-section feedback circuit is taken by R5, Tr1's emitter resistor. One might think that the analysis previously given for the circuit shown in Fig. 3(a) doesn't apply to this arrangement, but in fact it does. So long as the analysis is confined to the signal currents the inclusion of Tr1 within the feedback loop makes no difference. The feedback current flowing through R3 is applied to the emitter of Tr1. It thus passes through Tr1, emerging virtually unchanged in amplitude or phase at Tr1's collec-

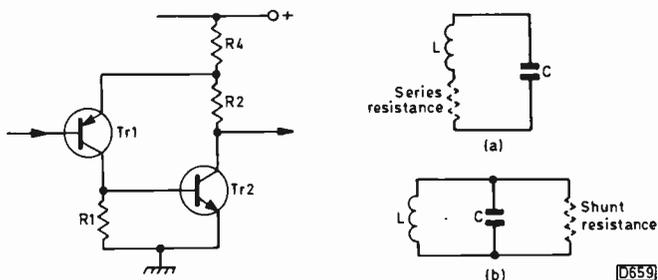


Fig. 7 (left): The arrangement shown in Fig. 6, but with  $R_5$  omitted.

Fig. 8 (right): The losses in an  $LC$  circuit can be represented as a series (a) or a shunt (b) resistance.

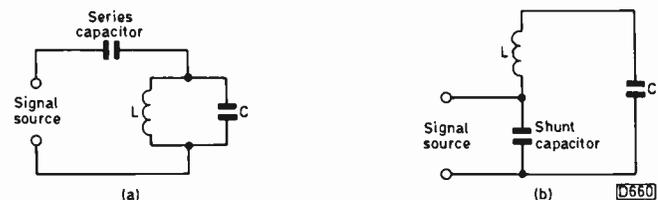


Fig. 9: Two methods of capacitive coupling to an  $LC$  tuned circuit, (a) by means of a series capacitor and (b) by means of a shunt capacitor.

tor. As before, it's then applied to  $Tr_2$ 's base. It's assumed that  $R_5$  is large compared with  $Tr_1$ 's emitter a.c. resistance and that  $R_1$  is large compared with  $Tr_2$ 's base input impedance – both reasonable assumptions in a practical circuit. So the feedback current enters  $Tr_2$ 's base as in Fig. 3(a) and  $Tr_2$ 's current gain is given by  $R_3/R_2$ .  $Tr_1$  acts as a common-base amplifier for the feedback current – such an amplifier has unity current gain of course.  $Tr_1$  is still a common-emitter amplifier of the current fed to its base, with considerable current gain which is unaffected by the feedback current.

How does this circuit react to voltage signals? This is a quite different story, because  $R_3$  and  $R_5$  now act as a voltage divider across  $Tr_2$ 's output and the feedback voltage generated across  $R_5$  behaves as an input voltage for  $Tr_1$ , a voltage which is amplified by  $Tr_1$  to appear of increased amplitude but non-inverted at its collector and thus at  $Tr_2$ 's base. So  $Tr_1$  is now well and truly within the feedback loop and its gain is reduced, along with that of  $Tr_2$ , to give an overall voltage gain of  $R_3/R_5$ . Thus in this circuit there's a great disparity between the voltage and the current gain.

Applying the series/shunt transformation to Fig. 5 gives us the circuit shown in Fig. 6. Here the ratio of  $R_2$  to  $R_4$  determines the overall voltage gain and  $R_5$ , which in Fig. 5 determines the degree of feedback, no longer serves any useful purpose. In fact it attenuates the feedback voltage applied to  $Tr_1$ 's emitter and can be eliminated, giving the circuit shown in Fig. 7. This is often used as a linear voltage amplifier – see for example  $Tr_1/2$  in Fig. 4 on page 113 of the December 1986 issue of *Television*.

### LC Circuits

In discussing feedback networks we have seen that the product of the equivalent series and shunt resistors is equal to a product characteristic of the amplifier – in fact the product is that of the two resistors. This reciprocal relationship between equivalent values of series and shunt components crops up in a number of different areas in electronics. It occurs for example in  $LC$  circuits, where the series resistance in the circuit is related to the shunt

resistance according to the expression:

$$\text{series} \times \text{shunt resistance} = (L \text{ or } C \text{ reactance})^2.$$

In an  $LC$  circuit however the series resistance is unlikely to be that of a component deliberately included in the circuit. It's more likely to be resistance that's inherent in the inductor, representing the losses due to ohmic resistance, skin effect and proximity effect. This resistance is not often directly encountered in electronics: it's more likely to be known indirectly because it determines the inductor's  $Q$  value according to the relationship:

$$Q = \text{reactance/series resistance.} \quad (5)$$

For example, the coil in a TV i.f. tuned circuit might have an inductance of  $1\mu\text{H}$ , which represents a reactance of approximately  $230\Omega$  at an i.f. of  $36.5\text{MHz}$ . The undamped  $Q$  value might be 100, and expression (5) tells us that the series resistance is  $2.3\Omega$ .

The loss in an i.f. winding can alternatively be represented as a resistance in parallel with the  $LC$  circuit, as shown in Fig. 8(b). This is often known as the parallel resistance, or dynamic resistance, of the tuned circuit. It's related to the  $Q$  value and the reactance as follows:

$$Q = \text{shunt resistance/reactance.} \quad (6)$$

Using the same figures as above, this is equal to  $23\text{k}\Omega$ .

Such a shunt resistance is not a physical component but a fictitious one effectively connected across the  $LC$  circuit: it's nevertheless real in its damping effect on the circuit, and limits the  $Q$  value to 100.

The  $Q$  value determines the bandwidth of the tuned circuit (being equal to bandwidth/centre frequency). We would probably decide that a value of 100 is too high for a TV i.f. amplifier, giving a bandwidth of only  $365\text{kHz}$  at a centre frequency of  $36.5\text{MHz}$ . To obtain a  $6\text{MHz}$  bandwidth, as required for a 625-line TV signal, a  $Q$  value of about 6 is more suitable. From expression (6) this corresponds to a shunt resistance of  $1,400\Omega$ . To obtain this result we could connect a resistor of say  $1.5\text{k}\Omega$  across the  $LC$  circuit or, more practically, we could arrange for the input resistance of the following transistor to provide the required damping.

We have so far confined our attention to series and shunt resistors, but star/delta transformations are possible with other components. Suppose for example that we wish to inject a signal into a tuned circuit. Mutual inductance is frequently used of course to provide the coupling between the signal source and a tuned circuit – very convenient because this doesn't require any additional components. Sometimes however mutual inductance isn't convenient (an example is given later) and a capacitor is used instead. The coupling capacitor can be used as a series component, as in Fig. 9(a), or as a shunt component, as in Fig. 9(b). The magnitude of the signal injected into the  $LC$  circuit is determined by the coupling coefficient which, for series and shunt capacitors respectively, is given by the following relationships:

$$\text{coupling coefficient} = \text{series } C / \text{tuning } C \quad (7)$$

$$\text{coupling coefficient} = \text{tuning } C / \text{shunt } C \quad (8)$$

Combining these expressions, we can see that the values of the series and shunt capacitances required to give the same degree of coupling are related by the expression:

$$\text{series } C \times \text{shunt } C = \text{tuning } C^2.$$

Let's take a practical example. A  $465\text{kHz}$  i.f. transformer commonly employs two similar tuned circuits which are loosely coupled to provide a bandpass effect.

The coupling coefficient needs to be about 0.015 to give a bandwidth of 7.5kHz, suitable for use in an a.m. radio receiver. A common tuning capacitor value for such an i.f. transformer is 250pF. If series-capacitance coupling is used, expression (7) shows that the coupling coefficient calls for a series capacitor of 3.75pF. If, on the other hand, shunt-capacitance coupling is used, expression (8) shows that the value of the coupling capacitor should be 0.017 $\mu$ F.

Shunt-capacitance coupling is useful when the two tuned circuits forming a bandpass pair are physically separated – as for example in a TV receiver where one section of a bandpass tuned circuit is mounted in the tuner and the other at the input to the i.f. strip. Nowadays the tuner is mounted on the same PCB as the i.f. strip, but in earlier designs it was common to couple the two circuits together via a length of coaxial cable whose capacitance formed part of the coupling capacitance.

# Micro Clinic

*Reports from Roger Burchett  
and Nick Beer*

## Sinclair Spectrum

It's been said before that the first check with these machines should be on Tr4 and the -5V line. The machine can initialise and appear to be o.k. (until the keyboard is used) with the -5V line missing, so to save time and heartache remember to make voltage checks first.

Colour problems with later Spectrums and Spectrum Pluses are generally due to the SN94459N chip – replace it with an LM1889. **R.B.**

## Acorn Electron

My colleague found the d.c. power socket dry-jointed and the output lead broken at the power pack end. Too late though: on this machine the ULA (type 12C021) appears to succumb first. It's expensive at over £20. The moral of course is always to look after your power supplies. **R.B.**

## Printers

We've started to take on printer repairs – more by default than design. A Micro Peripherals MP165 (an NEC clone) is owned by a local printer who kept on using it with a very dodgy head. On fitting a new one we found that the descenders and the underlining were missing. One of the pins was not firing, due to the relevant driver transistor (type 2SD1308) being short-circuit collector-to-emitter.

Next came an Epson FX80 which would work with an Amstrad but not with a BBC computer. On setting up a test we found that the BBC computer knew the printer was connected and kept on trying to fill the printer's buffers without success. While checking around the parallel interface we found that pin 29 was permanently low. This is a return for the "busy" line. The pull-up resistor (3.3k $\Omega$ ) is part of a multiple thick-film package which appeared to have a bad connection on one leg. To be sure we changed it. Why the printer worked with an Amstrad computer is not too clear. Perhaps someone with knowledge of IBM and compatibles can explain this? **R.B.**

## Sinclair Spectrum Plus

We sold a batch of "new" Spectrum Pluses to a local school and congratulated ourselves on beating Dixons etc. for the order. That was a mistake! We've had a few back with odd problems which we've had to repair ourselves under guarantee. The common link is that they've all received attention before.

One machine had had reset problems since we'd supplied it. The reset had been slow and not always completed. Also the logo had occasionally been accompanied

by the flashing cursor. On investigation the machine turned out to be a Spectrum issue 3B that had been converted to a Spectrum Plus. The reset arrangement was novel – instead of taking the CPU reset pin to chassis it took the 5V line to chassis! No apparent damage had been caused by this brutal treatment and the machine now works normally.

Following this we've had a number of other Spectrum Pluses with old boards inside. One was a real heartache. It came in with Tr4 short-circuit and a number of chips damaged. We did a memory check before boxing it up and found that it worked only as a 16K machine. To shorten a long story, it would appear that Sinclair sold a number of 48K machines that were working only with 16K – labelling them as 16K of course. The extra 32K of RAM was soldered in (no holders), ready to spring any poor unsuspecting soul about to upgrade them a surprise. This particular board had been recycled in a Spectrum Plus case and had been sold again (in a large Liverpool store), still only as a 16K machine. No one appears to have checked it at any stage during this procedure. Just to add a little spice to the fun, the membrane was very intermittent on extend mode, delete and symbol shift. As we're a long way from Liverpool we repaired all this and levied a nominal charge, hoping to get the loss covered by future business.

Way back in BC (before computers) we made it our policy always to check TV sets before delivering them. We continued this policy AD (after digital?) and it has paid dividends over and over again. We refuse to sell an item still boxed unless the customer is adamant. Even so we recently missed an Amstrad printer whose ribbon was twisted. **R.B.**

## Atari 1010 Cassette Decks

We've had a number of these with the plastic function selector buttons broken. Replacement requires quite a bit of dismantling but is fairly straightforward. **N.B.**

## Commodore 64

This machine wouldn't stop at the end when loading a program from a cassette or wouldn't load after acknowledging finding the program. The cause was a faulty 6510 chip. **N.B.**

## Sinclair Spectrum

In this Spectrum both Tr4 and the 5.1V zener diode had gone short-circuit, thus preventing operation of the power supply. **N.B.**

# A Vintage TV Restoration

Steve Rowley

Following the start of regular TV broadcasting in November 1936, and the subsequent decision in February 1937 to adopt the Marconi-EMI 405-line system and drop alternate transmissions using the Baird 240-line system, it has to be said that the sale of TV receivers was, to put it mildly, disappointing. Television was surrounded by an air of mystique. Indeed one of the rumours that abounded at the time was that "they" could see into your home in the same way that the viewer could watch an outside broadcast. It was almost certainly not for this reason however, but simply because of the cost, that so few sets were sold.

Jobs were scarce in the depressed thirties, and money to spend on luxuries was scarcer still. To add to the problem many families would have recently bought a wireless set and would probably not be able to buy a new TV set whilst still paying for the wireless. At sixty to a hundred pounds or more TV didn't come cheap. The radio and TV manufacturers responded by bringing out smaller sets with five, seven and nine inch screens. The smallest of these, the five inch HMV 904/Marconiphone 706, cost 29 guineas – the seven inch versions sold at 39 guineas. These sets were bought in reasonable numbers, but the price was still beyond the reach of most people.

By 1939 a number of manufacturers, notably Ekco, Pye and GEC, had brought out "television adaptors". These were vision only receivers that produced pictures in the normal manner on their small screens: the accompanying sound was obtained by connecting the "adaptor" to one's wireless set. By omitting the loudspeaker and audio output stage the size of the cabinet could be reduced and the price could be kept down to a level within reach of a wider section of the public. The Ekco Model TA201 was one such set: it sold for 22 guineas.

## The Ekco TA201

By the standards of the day the TA201 was a small set. It measured 19½ × 17 × 16in. yet weighed a hefty 70lbs. The 7in. tube produced a 6½ × 5½in. picture – note that the pre-war aspect ratio was 5:4. The cabinet was of polished, fine-grained walnut, and a matching stand was available for an extra two guineas. Also available was a sister model, the TS701, which was similar in appearance but had sound and cost 26 guineas.

Judging by the amount of promotional material produced, Ekco obviously expected great things of the TA201. Original leaflets and brochures for pre-war sets are nowadays very scarce, so it's perhaps an indication of how much material was produced that I've three different brochures on this model.

## Condition

As a collector and restorer of vintage TV sets I acquired a TA201 from a fellow collector some six years ago. It was in a sad state, with a rusty chassis and a control knob and the fibre back missing. Worst of all the tube was broken. Despite several advertisements and much searching I couldn't find a replacement tube, either new or used. Everything comes to those who wait however, and during the next couple of years two more TA201s plus a spare

tube came into my possession. One of these sets I've passed on: the other, though minus its cabinet, provided all the missing parts, including the tube and fibre back cover.

## Restoration

The methods and techniques used in restoring vintage sets couldn't be farther removed from those employed in the modern repair shop. The thought of switching on then, if the set survives, finding upwards of 25-30 faults would be unthinkable for a commercial servicing organisation.

My own approach is first to remove the chassis from its cabinet and then, using a stiffish paint brush together with a fine-nozzled vacuum cleaner, to clean the chassis thoroughly, sucking away all the accumulated dust and rubbish. The next step is to clean around the tube's e.h.t. connection, also the connecting cable.

The chassis of the TA201 is well laid out from a maintenance point of view. There are three units, one mounted horizontally at the bottom and one at each side, with the valves facing inwards. This layout gives easy access to the undersides of two of the three units. The bottom unit is the power supply which doesn't need much attention to its underside whilst the set is running.

With the set in a clean condition my next task was to replace all the waxed paper and electrolytic capacitors – the majority of the latter are underneath the power supply chassis, for h.t. smoothing. Without exception all the waxed paper capacitors were leaky, so around ten faults were probably removed in one go. The leads of the new capacitors were coiled to form small "tubes" which could be soldered in place over the severed leads of the original components. This gives a neat appearance, and the joints and layout remain in the original condition. Once the capacitors were sorted out I gave the resistors a quick look over for signs of over heating and where necessary checked the value with an ohmmeter. None of the resistors appeared to be seriously adrift, so it was time to switch on.

## The Big Moment!

The big moment had arrived! Would the Ekco work after forty-five years out of service? Perhaps predictably, the results were somewhat less than exciting. For my efforts so far I was rewarded with nothing more than a ghostly white blob which didn't appear to respond to any amount of knob twiddling. Clearly the timebases weren't working.

Both timebases have T41 thyratrons as the generators. The line output stage uses an AC6 while the field output stage uses a Pen45. All four valves were changed, but there was no improvement in the results obtained. Unfortunately E.K. Cole didn't permit publication of the circuit diagram, so my fault finding was seriously hampered. The service information at my disposal consisted of three pages from the July 1939 issue of the "Radio Marketing" *Service Man's Manual*. This included just about everything other than the vital circuit diagram.

Not to be outdone, I worked my way around the circuit and eventually found a very leaky capacitor hidden away behind a potentiometer mounting panel on top of the chassis. This capacitor is part of the line form circuit, and on replacing it I soon heard the familiar 10kHz whistle telling me that the line timebase was now working. Replacement of the two 0.1µF Visconol 4kV e.h.t. reservoir/smoothing capacitors cured the massive hum bar that moved slowly down the screen, and I now had a blank raster that could be controlled in height, width and focus.

My success was unfortunately short-lived. The screen slowly turned dark and smoke began to issue from the power unit. A check with the ohmmeter confirmed the worst – the e.h.t. transformer had developed shorted turns. Anyone who restores vintage TV sets lives in fear of this happening – finding a replacement is virtually impossible, and rewinding the original is costly, always assuming that you can find someone prepared to do it.

In the present case I'd the spare chassis, so the e.h.t. transformer was quickly removed from this. Not surprisingly, the "new" transformer was itself a replacement type, so it would appear that the original transformer was prone to failure. Fortunately the replacement worked, so I was back with my blank raster.

#### 405-line Material

There's one major stumbling block when restoring 405-line sets – there are no longer any transmissions! But we have our ways. If, like myself, you're not lucky enough to possess a standards converter, there are basically two choices. The first is to use a simple 405-line pattern generator. This is adequate for restoration purposes, but provides little of entertainment value for subsequent viewing! A much better solution is to use video recordings of 405-line material. Normal 625-line recordings cannot be used unless processed through a standards converter. Connect the VCR's video and audio output sockets to a v.h.f. modulator operating at the correct frequency for the TV set – the construction of a suitable modulator was described in the October 1984 issue of *Television*. I'm fortunate in possessing both pre- and post-war v.h.f. material, including "Television Comes to London", a short film about the construction of the Alexandra Palace studios and transmitter.

#### Getting the Picture

The v.h.f. modulator's output was connected via a length of standard coaxial cable to the TA201's aerial input socket. Being a born optimist, I drew the curtains and switched off the lights in readiness for some viewing. As anyone in the trade will confirm, such rashness always invokes a variety of faults – and this was no exception. Sod's Law again prevailing, there remained a blank raster and no amount of contrast increase (gain) or focusing adjustment would resolve a picture.

The SP41 vision r.f. amplifier valves were replaced, as were the SP42 sync separator and the SP41 video amplifier valves. All to no effect. The fault was eventually traced to the vision demodulator valve which wasn't lighting up. This was difficult to find as the valve, a D1 subminiature type, was concealed in what looked like another r.f. tuning coil can. The D1 is a strange little valve, with three pins in a row at one end and a further pin at the other end. Replacing it had the desired effect, and after carrying out adjustments to the hold controls and the contrast and focus controls the familiar figure of

## BILLINGTON VALVES

### NEW, GUARANTEED VALVES + COMPONENT BARGAINS

#### NEW VALVES — BOXED, 90 DAY GUARANTEE

DY87 .....	45p	KT66 USA ..	1000p	PL504 .....	90p	PY88 .....	48p
DY802 .....	43p	KT66 GEC...	1300p	PL508 .....	165p	PY800/801 .....	68p
ECC81 .....	80p	KT88 USA ..	1100p	PL509 .....	400p	PY500A .....	150p
ECC82 .....	65p	PCF802 .....	60p	PL519 .....	440p	30FL2 .....	135p
ECC83 .....	65p	PCL82 .....	63p	PL802 .....	550p	3AT2B .....	295p
EL34 .....	190p	PCL805/85 .....	80p	PL802T .....	390p		

#### USED VALVES clean & tested working — 28 DAY GUARANTEE

ECC81 Mullard Mfg (CV 4024) 80p

ECC82 Mullard Mfg (CV 4003) 70p PL509 £2.00

#### PHONE FOR IMMEDIATE QUOTATION ON ANY VALVE

Almost any type available from stock. Rarities our speciality. Competitive prices.

#### NEW, GOOD QUALITY TRANSISTORS

BU126 70p, BU208A 80p, BU326A 65p,

BU508A Sanyo 130p, BU508D 130p

**E.H.T. MULTIPLIER.** Good quality universal triplers £4.40 + VAT + post. Suitable for nearly all sets — B+O, Decca, GEC, Grundig, ITT, Philips, Pye, Rank + continental.

1000 resistors or 1000 capacitors £3.50 post paid.

**INCREDIBLE BARGAIN PACKS.** Parcels of mixed I.C.s, transistors, relays, capacitors, resistors, potentiometers, switches, etc., etc. 2.5kgs £5 + VAT delivered 10kgs £10 + VAT delivered.

**TO ORDER: Please add 50p post/packaging per order and VAT @ 15%. Same day despatch now guaranteed. Govt + export orders welcome. We accept Barclaycard. Possible delays during staff holidays June 8-21 [on unusual items only].**

**WE WILL BUY VALVES!** We are short of audio types PX4, PX25, KT66, KT88 etc. (plus PP3/250, PP5/400, DA30 etc.).

### BILLINGTON VALVES

39 Highlands Road, Horsham, West Sussex RH13 5LS  
Phone 0403 210729 Fax 0403 210108 Telex 87271 PRODSS G

If visiting in person, please phone first to check that office is attended

Mickey Mouse came into view. This cartoon was the very last programme to appear on TV prior to the wartime close down. It was perhaps ironic that it should appear on the screen after I'd devoted so many hours to the restoration.

#### Results

The sound output socket (complete with its original plugs) was connected to the gramophone sockets of a contemporary Cossor wireless set, Model 375. This time I was lucky, and after a couple of minutes of warming-up time "The Lambeth Walk" was echoing round the room. Both the picture and sound were of good quality, the latter being considerably better than the sound obtained from many modern-day sets. The geometry and contrast were good but the brightness was such that viewing was best either in an unlit room or with the light source behind the set. Advancing the setting of the brightness control too far produced flaring, which was only to be expected with a set of this age. Judicious adjustment of the r.f. cores produced a further improvement, as did adjustment of the sound rejector capacitor, which improved the line hold.

The set is now used on a fairly regular basis, mainly for the entertainment of those who are either too young to remember or who simply couldn't afford pre-war television. Watching the Ekco TA201 is not at all like watching a modern TV set. For me it invokes a feeling of excitement, as though I was one of the pioneers who produced the first television pictures. Last year saw the fiftieth anniversary of the start of high-definition TV broadcasting in the UK. I wonder whether the little Ekco will be producing pictures in another fifty years' time?

# VCR Clinic

Reports from Steve Beeching, T. Eng., Eugene Trundle, Philip Blundell, Eng. Tech. and Patrick Rafferty

## Saisho VR9055

There was no cassette tray operation, no eject and a tape was stuck in the machine. As the motor was without power the main drive i.c., type RA6209, was suspected. After replacing this the operation was sluggish and hesitant, with intermittent eject. The motor had been checked with an external power supply (yes, the RS one E.T. reviewed in the May issue – he got his after seeing mine!), so we were back to the chip. As luck would have it however I checked the wiring to the motor. This is wrapped around the cassette compartment metal chassis, was tight and had cut through, shorting the motor's output to chassis. **S.B.**

## Sharp VC8381

There were no playback pictures and the E-E pictures showed signs of white clipping. The supply lines were correct. Rather than getting bogged down with the clipped whites attention was turned to the absence of playback pictures. IC402 had no sync pulses at pin 1 and no video signal at pin 20, though there was a video signal at pin 18. In the E-E mode there were signals at both pins 18 and 20, but the signal at pin 20 was clipped. After changing the i.c., for no good reason whatsoever, the voltages were checked. Pin 18 read 5.1V instead of 4.3V. C439 was found to be leaky. **S.B.**

## JVC HRD725

There was a background sizzle on the sound from the right-hand stereo hi-fi channel. The left-hand channel was fine. Various checks were made, including increasing the level of the right-hand 1.8MHz carrier. All to no avail. Only replacing the video heads (ouch!) provided a cure. Although the left and right audio channels are recorded by the audio heads as a mixed carrier, head wear seems to affect the right-hand channel first – presumably because of the higher frequency.

Another problem that can occur with these machines is failure of the power supply regulator transistor Q2. This can create unforeseen problems – the symptoms range from full to no display, with the capstan motor running. If Q2 has failed, change both Q1 and Q2 and check D2. As the rail voltage can increase to 20V or so a regulator circuit on the tuner panel is likely to be destroyed, so replace the following as a precaution: Q3, D13, D17, D18, D19, D20, C13, C14, L1 and IC1. **S.B.**

## Grundig VS380

Intermittent sound erasure is generally due to cracks in the solder joints on the coils around the erase oscillator. These are mounted horizontally and are subject to mechanical shock.

Low audio from the left-hand channel with an AV input was traced to failure of the input select i.c. Customers should be told not to connect plugs and sockets while the machine is powered. **S.B.**

## Grundig VS300 Series

You may sometimes find that the head drum goes around backwards. The drum motor is bidirectional and is told which way to rotate by the microcomputer chip, via a

series/parallel shift register and a four-way buffer driver. If the micro gets incorrect data from any source it tends to rotate the drum the wrong way. In one case the cause of the trouble was found to be the input data interface while in another the cause was a seized capstan motor. Drum motor winding failure will create the same problem. So remember: backwards drum rotation is only a symptom and the cause could well be something apparently not related to the drum. You must check the power rails, resets, FGs, CTL and optocoupler input to the syscon before ripping out expensive i.c.s. Ask Grundig Pete! **S.B.**

## Grundig VS380

Intermittent operation of the f.m. audio record level display was traced to a poor joint on T2049. This removed the 22V supply. **S.B.**

## Ferguson 3V44/JVC HRD140

There were no functions and no "operate" power up. After checking all the circuit protectors attention was turned to the syscon microcomputer chip which was replaced. Note that the M50730-607SP has been replaced by the M50730-610SP – I don't know why. **S.B.**

## JVC HRD180

One of these machines lost time. Replacing the clock crystal X101 and resetting C102 as per the manual cured the trouble.

With another one there were no functions and circuit protector CP4 was open-circuit. This was bridged with a piece of wire as a check but there was no 12V at pin 9 of the 12V regulator. With a new regulator fitted there were still no functions and CP4 was again open-circuit. The cause of the fault was traced to the motor drive chip IC602 which was short-circuit – a 12V, 3A power supply helped sort this out.

There was inconsistent channel selection with another of these machines – when changing channels the u.h.f. numbers would alter and the machine would be off tune. For example, if programme 9 was tuned to ch. 58, selecting 9 would result in ch. 21 or 57 appearing, though reselecting would produce ch. 58. Changing the tuning memory chip, the tuning PLL chip, then the timer/display microcomputer chip had no effect. The resets, power rails and clocks were all checked – even the timer was changed. The cause? C7 on the power panel had a dry-joint at one end. This put a ripple on the 30V line, confusing the memory chip. **S.B.**

## Panasonic Oil Clutch Motors

Heard about the new Panasonic oil clutch motors? What will we tell customers – it leaked? **S.B.**

## JVC GRC1

One of these camcorders wouldn't record. The cause was a faulty record inhibit switch.

Intermittent audio recording and no playback tracking was traced to a wire to the erase head shorting to the

servo panel – the sharp component pins penetrate the screened cable. This is a problem with portable equipment which is subject to mechanical shock.

On another of these machines intermittent audio recording was traced to a dry-joint in the oscillator circuit: all suspect joints were touched up. **S.B.**

### **NEC PVC744E**

There's a good chance that the reel motor is faulty if any of the reel drive transistors have failed (Tr11 and Tr12 usually go).

When refitting the cassette housing make sure that it doesn't catch on the back-tension band – or you'll find that the machine won't thread up. **P.B.**

### **Sony SLC6 Mk. 2**

The metal cassette flap had come off and was loose inside the machine. When it was refitted the machine would thread up but the loading ring wasn't being held in position. A quick read through the manual was needed to discover that the brake/select solenoid wasn't being pulsed. Q613 was short-circuit. **P.B.**

### **Sharp VC387**

The problem with this machine was tracking noise on playback – the noise was stationary and the tracking control had no effect. As the drum lock (TP701) and capstan lock (TP708) voltages were normal attention was turned to the tracking control which was found to be open-circuit.

For no power on but the clock working check that IC801 on the mechacon board has 9V at pin 64. If not, follow the track back and you'll probably find an open-circuit semiconductor fuse (this isn't shown on the circuit diagram!). **P.B.**

### **ITT VR3916**

We've had two more cases of no clock display. In one case R423 on the timer board was open-circuit, in the other R2 in the power supply was responsible. **P.B.**

### **JVC GXN70**

The reported problem was no colour, though a scope check showed that the CVBS output had chroma information. Investigation on the SSG/deflection panel showed that the subcarrier frequency was incorrect at about 4.42716MHz. The problem was solved by replacing crystal X701, which enabled the subcarrier frequency to be correctly set with the trimmer.

In this camera the screening cans that surround the crystal and SSG chip are extremely tricky to remove: there's a great risk of damage to the board and nearby components. **E.T.**

### **Toshiba V8600**

The accusation against this old battleship of a VCR was that it lost five minutes in each hour. Set to run in the workshop it kept better time than my wristwatch for two days on the trot. It was then returned to the customer's home, where it continued to keep exemplary time. The likelihood is that a spike or transient on the mains supply had triggered the microcomputer chip into 60Hz operation of the clock counter. In future we'll advise customers with

this sort of problem to unplug from the mains, count to ten and try again before bringing the machine to the workshop. **E.T.**

### **Sony SLC6**

The customer had no sooner taken this machine home after a workshop overhaul than he was on the phone to complain that it wouldn't thread up. This sort of problem has cropped up in the workshop too, on various makes and models. The solution lies in getting a correct microcomputer reset. The customer had switched on at the mains with the VCR operate switch already on: it's sometimes essential to apply mains power before you switch on at the front panel. **E.T.**

### **JVC HRD180**

This machine, one of the latest, came back to the workshop with a no vision recording fault. It was intermittent, like all the best ones. The effect was complete loss of picture to a screenful of snow while the sound continued. The problem lay at CN2/7 (/REC) on the video board, where a stiff ribbon cable enters from J2 on the mechacon board. The solder connection had probably broken when the 03 video board was hinged down during assembly. **E.T.**

### **JVC GZS3/S5**

The picture produced by this camera was very dark, with a pink and purple chroma overlay. Turning the colour fully down at the monitor gave us a very dark picture with only the brightest highlights (workshop lamps and windows) emerging from the blackness. The luminance signal was o.k. up to Q2 on the 01 video processing board: it then virtually disappeared. The trouble was in the black-level clamp circuit, where the /CP2 pulse ties the luminance signal to a fixed 1.7V potential during the line blanking period. This clamp reference voltage is held by a 10µF tantalum capacitor, C5, which was open-circuit. **E.T.**

### **Grundig VS180**

On most occasions a known good tape would play back perfectly but now and again the picture would begin to jump for a few seconds at intervals of 40-45secs. When playback returned to normal the fault wouldn't occur until the machine had been stopped and restarted. The time interval between the jumping sessions suggested that the problem was due to the rotation of the spools in the cassette rather than electronic trouble.

We found that when the fault occurred the back-tension tape control arm was firmly locked to the optosensor instead of being free to swing back and forth to level out tape pay-out irregularities. When the fault was not present the arm was free to trigger the sensor as it should. There's a small plastic sleeve on the control arm's stop peg. It's retained by a "hooked" end on the peg, presumably a buffer. This sleeve must have flattened a little, since now and again the hooked end would latch over the back plate of the optosensor at start up. As the owner came from afar and wanted to leave at once I slipped a small length of RS red plastic sleeving tightly over the peg-and-sleeve so that the red sleeving stopped the hook engaging. Results were first class. Note that the diagram on page 74 of the manual doesn't show either the plastic sleeve or the hooked end to the stop peg. **P.R.**

# Long-distance Television

Roger Bunney

As hoped, April proved to be a rewarding month for Sporadic E reception. This is always a pointer to a good season starting in mid-May. There were several periods of SpE activity, including an excellent opening on Easter Monday afternoon – it's most unusual for an opening to occur during a public holiday! The settled weather conditions proved helpful for tropospheric propagation, and as an additional bonus the April Lyrids meteor shower (April 19-25th) produced substantial signal pings at frequencies rising as high as Band III. The SpE log, collated from various UK reports, is as follows:

- 5/4/87 NRK (Norway) ch. E2; SR (Sweden) E2; DR (Denmark) E3.
- 14/4/87 DFF (E. Germany) E4; NRK E4; CST (Czechoslovakia) R1.
- 16/4/87 TVE-1 (Spain) E2-4; TVE-2 E2; RTP (Portugal) E2; ARD (W. Germany) E2.
- 19/4/87 RAI (Italy) IA, B; ORF (Austria) E2a; TVE-1 E2-4; TVE-2 E2.
- 20/4/87 TVE-1 E2-4; TVE-2 E2; RTP E2, 3.
- 26/4/87 TVE-2 E2; RTP E3.

The 21st provided CB SpE at 27MHz, with various southern European stations being heard at high levels. Band I was not affected.

Tropospheric propagation improved from the 12th. Band I, III and u.h.f. signals from RTE (Ireland) were received in central/western UK by the 15th. W. German Band III/u.h.f. signals were also improving, with reception in central/southern UK. But the most active period was from the 23rd to the 29th. Throughout this period W. German/Benelux/French Band III/u.h.f. signals were received at good strengths as far west as Wales. Perhaps the most active day was the 28th, with Swedish v.h.f./u.h.f. and Danish Band III signals being added. Interesting that on the 29th Iain Menzies (Aberdeen) received very strong E. German u.h.f. signals during the morning – conditions died down later that day.

The new Dutch third programme (NOS-3) transmitter at Smilde (ch. E44, 1,000kW e.r.p.) was on test during April – so keep a careful watch on this channel.

During the April Lyrids meteor shower Mark Baldwin (Rugby) logged ORF (Austria) ch. E5 and CST (Czechoslovakia) ch. R6. This reception occurred on the peak day – the 22nd. MS propagation was fairly active during the period, with medium/short pings in Band I. Band III MS is not usual but, as Mark as shown, can occur.

## News Items

**Spain:** A new TVE-1 transmitter is in operation on ch. E2 at Casares, a small mountain town some 22 miles NNE of Gibraltar. The output power is at present unknown but is expected to be low.

**UK:** John Butcher, under secretary of state at the DTI, has indicated that the department is giving sympathetic consideration to the use of the 50MHz band (50-52MHz) by class B amateur radio operators – the band is at present

used only by class A operators. Power level limitations could be eased.

The DTI has also indicated that the UK Citizens' Band is to be increased to 80 channels, using the new European standard (CEPT). Use of the original 40 channels will be reviewed in 1990.

**W. Germany:** A network is being commissioned to transmit the SAT-1 satellite TV service to main areas. Most of the transmitters operate at under 1kW e.r.p. The main ones of interest are as follows:

Augsburg ch. E38/40, 6kW. Bremen ch. E45, 1kW. Kaiserslautern ch. E50, 1kW. Munchen ch. E29, 1kW. Saarbrucken ch. E56, 1kW. Bamberg ch. E45, 1kW.


**Denmark:** Rumours suggest that from 1990 onwards all v.h.f. transmitters will gradually be closed, starting with the ch. E3/4 outlets which are soon to have u.h.f. counterparts. The new transmitter tower in West Copenhagen, due to open on April 1st 1988, will transmit DR-1 on ch. 31 and TV-2 on ch. E53 – the old ch. E4 outlet will continue in use for some years.

**W. Germany:** The following private/local TV transmitters will operate in Schleswig-Holstein: Kiel ch. E24 400W e.r.p. TV-1; Flensburg ch. E24 100W e.r.p. TV-1; Flensburg ch. E28 200W e.r.p. TV-2.

New identifications have been announced for the Bremen ZDF and Radio Bremen 3 test patterns – "2. Programm K34" and "3. Programm K42" respectively, with "Bremen" above in both cases.

Channels E61 and E69 are to be released for TV broadcasting. The BDXC report that for NDR/RB/SFB programme linking there's a high-power tropospheric link between Gartow/Hohbeck in W. Germany and W. Berlin. The link uses ch. S13 (245-25MHz vision) and operates at 500kW e.r.p.

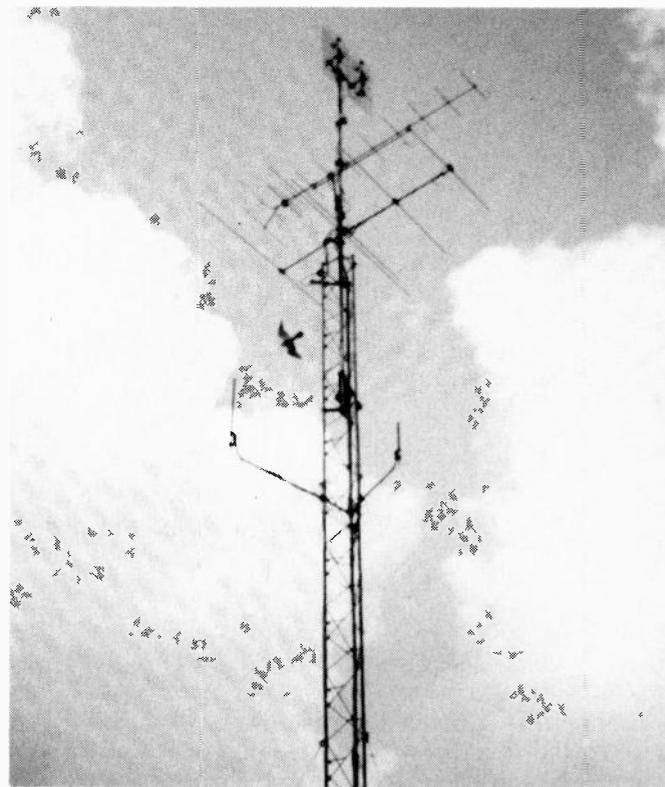**USSR:** The Moscow first programme now starts an hour earlier, at 0400 GMT. The first news programme, Vremja, is at 0430-0500.



Roger's DX aerial mast complete with Les Wallen 27 and 49MHz aeriels and full-size plastic decoy falcon to the rear of the Band I array.

**France:** Two new TV6 (now called M-6/Metropole 6) transmitters are in operation - Lille/Lambersart ch. E53 and Dunkerque-Ville ch. E62. The power is 1kW e.r.p. in both cases.

**USA:** Of interest though not exactly DX-TV news - US military officials have activated a communications satellite that had been "in storage" for at least seven and a half years. The Ford satellite was the third in a series of four and was held stored due to the excellent performance and life of the second satellite in the series, NATO-IIIB.

### Spectrum Deregulation and Pricing

The DTI has just published a substantial document entitled "Deregulation of the Radio Spectrum in the UK". This considers potential changes in the spectrum to accommodate new services, new frequency planning, and "the possible benefits from introducing market forces and the price mechanism into spectrum management". It requires closer study than we have so far been able to give it, but several points are clear.

There is to be no development of ground radar in the TV band 582-606MHz and existing installations are to be phased out in the interests of reducing TVI. These installations currently operate at 60kW peak power. The subdivision of Band III has been reviewed - details were given in an earlier column. It's suggested that Band I could be split into two allotments approximately 8MHz wide, though the possibility of interference from foreign broadcasters and "some computer and other electronic equipment" is recognised. Some of the suggested users are cordless PABX (operators may need a bandwidth of 8MHz to allow high packing density), diversity paging (using several frequencies at specified time intervals), and that old favourite PMR. The document recommends early release of the Band I spectrum to allow rapid, cost-effective development of the equipment that would be required. Implementation would be helped by increased revenue from licence fees. An indication of the future!

### DX-TV Tuner Unit

HS Publications of 7 Epping Close, Mackworth Estate, Derby DE3 4HR have announced a new converter unit, the Special D100; that covers Band I, II (TV), III and u.h.f. It costs a little more than the Standard D100 which omits Band II. It's based on the NSF 47807 tuner and includes switched selectivity. For further information send an s.a.e. to HS Publications.

### Far East Report

Our correspondent in South Korea, Jean-Louis Dubler, has been on his travels again. He reports that there are four TV networks in Thailand, though their coverage is limited. Bangkok has four TV channels, three of which have affiliated Band II f.m. transmitters for relaying dual-language sound. Two of the networks are operated by the army, the others being private. Singapore has three channels, one with 100 per cent English language transmissions and the other with various Malay dialects. There's a single TV channel in Bali - but Malaya ch. E3 is available via transequatorial tropospheric propagation at a distance of some 700 miles, reception varying from fair to poor!

### Aerials and Other Things

As mentioned last month, I've been looking into the possibilities of using small active and passive aerials for

## FERNSEH-ANTENNA Combined Band 1/3 Aerial for TV-DXing



The 1987 Sporadic-E season is now with us! Time to take advantage of a special offer from **Aerial Techniques** to re-equip your system. The Fernseh-Antenna DR1712 is an efficient low cost Wideband VHF aerial covering both Bands 1 & 3, it has a gain of 3.5dB in Band 1 and 9.5dB in Band 3. Folded dipoles for peak efficiency are used in both Band 1 & 3 sections. Front to back ratio is 11dB - Band 1; 25dB - Band 3. The aerial has been gold lacquered for high resistance against weather corrosion. This array has close spaced elements, making it a very compact length of 72", ideal for the enthusiast with restricted space, or those unable to erect separate aerials. This aerial only requires a single coaxial downlead.

In certain areas the use of a wideband VHF amplifier can be advantageous, the Antiference UP1300 fits the bill. This preamplifier covers 40-230MHz (Bands 1 to 3) with a gain of 19dB and a low noise figure of 2.5dB. The amplifiers matching power supply unit provides 12v DC via the coaxial downlead.

**FERNSEH-ANTENNA** Combined Band 1/3 Aerial - Special offer - carriage free! ..... **£43.75**  
**ANTIFERENCE** UP1300 Band 1 & 3 Amplifier ..... **£17.30**  
**ANTIFERENCE** PU1240 12v DC Power Supply (mains operated) ..... **£14.25**  
**KINGROTOR** Automatic 'offset' Antenna Rotator and Control Console (uses 3 core cable) ..... **£39.95**  
**SUPPORT BEARING** for heavier load applications ..... **£13.95**

Aerial Techniques, the company that knows the TV-DXing hobby carry a large and comprehensive range of aerial equipment for every type of installation - and with a huge range of filters, amplifiers, cables, rotators, masts and supporting hardware. Send for our illustrated **Catalogue at 65p**, if it doesn't list what you want, then we can obtain it quickly.

**STOP PRESS** - New Triax style Notch Filter, covers whole of the UHF Band; 470-860MHz completely tuneable. Notch depth up to 26dB ..... **£6.95** (includes postage).

All prices inclusive of VAT & Carriage Delivery normally 7-10 days.

**ACCESS & VISA** Mail and Telephone Orders welcome.



### AERIAL TECHNIQUES (T)

11, Kent Road, Parkstone,  
Poole, Dorset, BH12 2EH. Tel: 0202 738232.



## TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

TRANSISTORS, IC's, ALSO STOCKED.

<b>BAIRD:</b> 8290, 8752, 8773, 8180	12.00	<b>ITT:</b> VC200 to VC402	9.20
<b>RANK BUSH MURPHY</b>		CVC1, CVC2 (FORGESTONE)	11.50
A774 with stick rectifier	9.78	CVC5, CVC7, CVC8, CVC9, CVC20	10.35
A816, T16, T18, Z712, Z715	10.35	CVC25, CVC30, CVC32, CVC45	9.20
T20, T22, T26, Z179, A823	11.50	CVC800, 1100, 1150, CVC40	P.O.A.
Z718 Basic unit	13.50	CVC1200, 1204, 1210, 1215, 2600	P.O.A.
<b>DECCA:</b> 1210, 1211, 1511	11.50	<b>PYE:</b> 169, 173, 569, 368	9.20
A816, 2001, 2020, 2401, 2404	9.20	CT200, CT200/1, CT213	10.35
CS1730, 1733, 1830, 1835	9.20	725-731, 735, 737, 741	9.78
30, 70, 80, 90, 100	9.20	<b>PHILIPS:</b> 170, 210, 300	9.20
120, 130, 140, 160	P.O.A.	320 series	9.78
<b>FERGUSON, THORN:</b> 1590, 1591	9.20	TX, T8, TX2, TX3 mono	P.O.A.
1690, 1691, built in rect.	9.78	G8 and G9 Series	£9.20
1600, 1615, 1700, 1790	P.O.A.	KT2, KT3 series	9.20
3000, 3500, 8000, 8500, 8800	P.O.A.	CTX G11, K30, K4, K40, split diode	P.O.A.
9000, 9200, 9300 series	12.00	<b>BINATONE:</b> 9909, 9860, 9488	P.O.A.
9500, 9600, 9650 series	10.99	<b>DORIC</b> Mk3, Mk1	11.50
9800, TX9, TX10, TX90, TX100	P.O.A.	<b>SONY</b> KV 1400, 1612, 2000	P.O.A.
<b>MOVIESTAR</b> 3781, 3787, 8180	12.00	<b>GRUNDIG:</b> most models in stock	
TX10 focus unit	10.87	<b>NORDMENDE:</b> 8290, Z206, Z306	P.O.A.
<b>FIDELITY:</b> FTV12 mono	10.35	<b>SANYO:</b> 5101, 5103, 7118, 7130	P.O.A.
ZX2000 ZX3000	16.43	<b>SHARP:</b> C1851H, C2051H, 1405	P.O.A.
<b>G.E.C.</b> 2047 to 3135 mono	9.20	<b>TOSHIBA:</b> C800, C800B	P.O.A.
1201H, 1501H, 2114, 3133, 3135	9.20	<b>TANBURG:</b> 190, CTV2, CTV3	P.O.A.
DUAL & SINGLE hybrid col.	10.00	<b>TELEFUNKEN:</b> most models in stock	
SINGLE STD solid state	12.00	<b>HITACHI:</b> 1471, CPB260, 2501	P.O.A.
SINGLE STD split diode	P.O.A.	<b>AMSTRAD:</b> CTV2200, CTV2210	P.O.A.
<b>INDESIT:</b> 24EGB, 12LGB, 12SGB	10.35		
<b>WINDINGS</b>			
<b>TYNE:</b> main winding	6.80		
<b>RBM:</b> T20, T22, T26, Z179	6.33		
<b>WALTHAM:</b> W125 eht winding	2.37		
<b>WALTHAM:</b> W190, W191 eht coil	6.00		
<b>KORTING:</b> hybrid winding	6.90		
<b>THORN:</b> 8000, 8500, 8800 eht	6.70		

Delivery by return of post.  
Shop callers welcome.

**Tidman Mail Order Ltd.,**  
236 Sandycombe Road,  
Richmond, Surrey TW9 2EQ.  
Approx. 1 mile from Kew Bridge.

Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm &  
1.30-4.30 pm  
Sat 10 am to 12 noon.

DX-TVing. The Les Wallen 49MHz UK paging service aerial has now been mounted on my mast at the 40ft level: the equivalent 27MHz base aerial is mounted on an adjacent stub mast (see accompanying photo). The 27MHz base aerial is 40in. overall and again has an integral SO329 socket (for use with PL259 plug). Both aerials consist of a helical element within a waterproof PVC tube, with an efficient built in vertical mast clamping bracket arrangement. Initial tests suggest that at 49.83MHz the gain of the 27MHz aerial is some 8-10dB up on that of the 49MHz aerial – it will be interesting to check on the results obtained when the SpE season starts. I'm told that Revco now have an in-line "tube-like" preamplifier that covers the whole radio spectrum to 1GHz with a gain of around 13dB, a noise figure of 3-5dB and excellent linearity/overload performance – a sample is awaited. Initial assessment of the 27MHz aerial showed that it worked well from 6MHz upwards through to the 450MHz u.h.f. band, with a scanner.

If you look at the photograph you'll see that there appears to be a bird flying close to the lattice mast. As

DXers and radio amateurs will know, various birds love to perch on aerial elements. This leads to the build up of excrement on the alloy tubing, which then tends to corrode. This is in addition to the droppings to ground from such birds. I noted the suggestion in a recent magazine of using a decoy bird of prey to frighten other birds off and eventually found at a local garden centre a replica plastic hawk modelled in flight. This was suspended from the rear of the Band I array using fishing line nylon. Initial results suggest that starlings are wary, though a local pigeon is quite happy to sit nearby.

One of the nylon supports snapped after just one day, so stainless steel fishing line was then fitted. Three days later the hawk crashed to earth due to excessive spin on the two stainless steel support wires used. Shorter wires have now been fitted to prevent this spin. The plastic bird of prey certainly looks realistic, seeming to hover in a gentle breeze. One concerned neighbour reported a large bird caught up in the mast – could I climb up and release it! So if you are suffering from aerial damage caused by birds, a plastic hovering bird of prey could be the answer.

Details of a "small-dimension TV aerial for the v.h.f. band" have been received from a contact in Poland. Unfortunately the text is largely in Russian, making it extremely difficult to establish the theory of the aerial and the claimed performance. Constructional details are shown in Figs 1-4 and Table 1. It should be possible to make up this aerial, using helical elements within plastic tubing (rainwater/drain piping). The original articles include gain figures which indicate wideband performance, ranging from 9dB at 50MHz to around 10-25dB peak – these figures are based on an array with five directors, a single dipole and a sheet reflector.

The main feature of the aerial is the helical director and dipole elements which have eight turns in each half element, with ten close-spaced turns at the centre (directors – the dipole has a matching arrangement), using 1mm diameter enamelled wire located in a slot. Metal cones are fixed at each end of the elements and are connected to the far ends of the spiral element wire. There's no boom connection at the centre of the elements – the plastic boom is some 90cm long with a diameter of 30mm. Each element varies in turn detail (see Table 1).

Hopefully the information given will be sufficient to enable an aerial of this type to be tried. If the aerial does indeed provide the performance claimed it could well be the answer to the problem of minimising the visual impact of a v.h.f. DX-TV aerial in a modern housing estate. The detailed metal cone diagrams suggest that the profile is important in obtaining the claimed performance. I wonder whether a tube of copper (water pipe) would suffice, the coil being wound on a given plastic/PVC pipe complete with end copper tube and the assembly then slid inside a slightly larger PVC tube to provide weatherproofing.

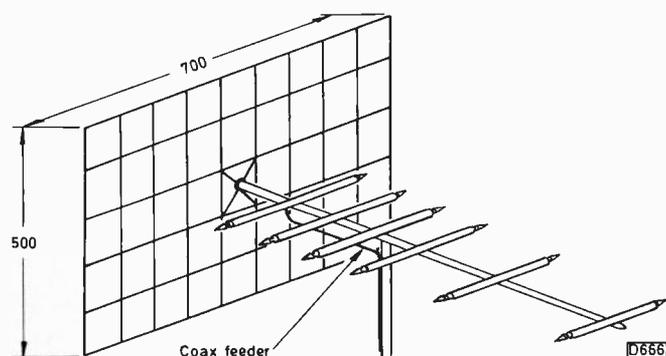


Fig. 1: Overall view of the Russian wideband v.h.f. array.

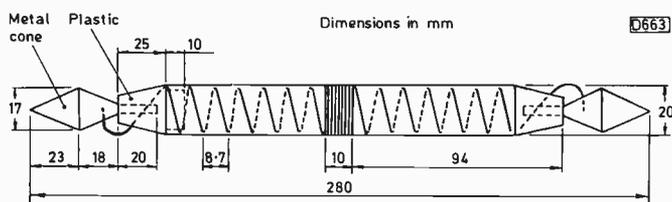


Fig. 2: Constructional details of the first director.

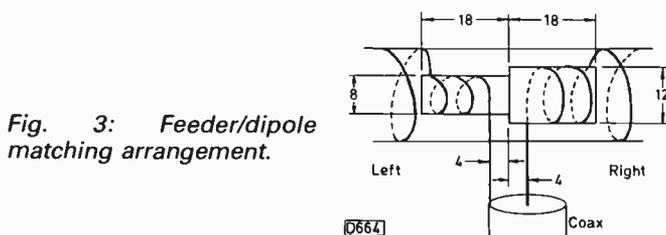


Fig. 3: Feeder/dipole matching arrangement.

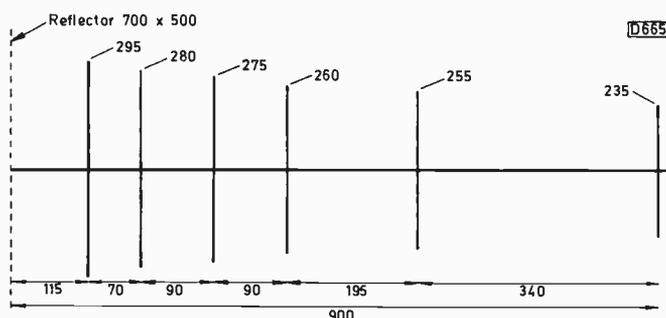


Fig. 4: Element dimensions and spacing.

Table 1: Element coil details.

Element	Spacing between turns (mm)	Overall length of coils in each half element (mm)	Overall length of 1mm enamelled wire per half element (mm)
Dipole	8.8	90	720
Director-1	8.7	84	672
Director-2	8.6	78	624
Director-3	6.8	70	560
Director-4	6.4	64	504
Director-5	6.3	62.8	502.4

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £1.50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## **GRUNDIG CUC70 CHASSIS**

The problem with this set is colour patterning during monochrome reception. It works perfectly with colour programmes. The patterning is intermittent and can occur with the set at any temperature from cold to fully warmed up. Tapping the decoder board makes no difference and there don't seem to be any dry-joints. The only way in which the interference can be cleared is to turn the colour right down.

The problem is not with the set but with the broadcasting authorities who nowadays seldom seem to switch off the burst signal during monochrome transmissions. As a result the Grundig set's colour-killer doesn't switch off, leading to colour confetti if the signal is anything less than impeccable. The only solution, it seems, is to turn down the colour control during the rare periods of monochrome pictures.

## **SANYO VTC5000**

The problem with this four year old machine is continual mains fuse blowing. The 315mA fuse may blow after a day or it may last a month. The machine works perfectly once the fuse has been replaced. About six fuses have been fitted so far, and adding a transient suppressor in the mains plug has not improved matters. The fuse always blows when the machine is in the standby mode.

The fault is quite common on these machines. It should clear after replacing the mains filter capacitor C5201 with an 0.0047 $\mu$ F, 350V a.c. type. RS Components stock a suitable capacitor.

## **FERGUSON TX90 CHASSIS**

The bottom two inches of the field scan are very unstable when the set is first switched on, and a white line is present about two inches from the bottom. A very light tap on the cabinet will cure the fault temporarily. The field scan occasionally collapses for a second or so. After half an hour the field scan is usually normal.

This problem is quite common and is almost always caused by dry-joints on the legs of the field output transistors TR104 and TR105. Resolder these carefully, along with any other suspect looking joints in the same area of the board.

## **SONY SL8000UB**

This machine will run for only five-fifteen minutes in the record or play modes. After this the keys return to the stop position – as if end-of-tape is activated. Subsequent attempts at restarting produce no results as the keys spring back up: only the rewind function is available. If the machine is left for a considerable time you can get another

five-fifteen minutes of record or playback. The heads and threading ring have been cleaned and a new belt has been fitted.

The machine plainly thinks it has reached tape end, due to cessation of oscillation in the left-hand side end-sensor coil. While a faulty coil or intermittent plug/socket connections can be responsible, the fault is more often due to failure of the forward sensor preset RV701. Replace it, along with RV702, then set up both of them as specified in the manual.

## **ITT CVC32/3 CHASSIS**

The programme suddenly changed to channel 1 while we were watching channel 3. Now this is the only programme that can be obtained whichever button is pressed. The SAA1024 chip in the remote control transmitter has been changed but this had no effect.

The most likely cause of the problem is the SAA1025 remote control decoder chip IC1 in the CMC60 remote control assembly in the set. Before condemning it check for 18V at pin 16 of IC4 and 8.2V at pin 8 of IC2. If either of these supply lines is incorrect, suspect zener diodes D2 and D4.

## **PANASONIC NV333**

The problem with this machine is that the lid won't stay down. It seems to be permanently in the eject mode. If the loading mechanism is wound manually the lid shuts, but as soon as power is reapplied the loading motor comes on and lifts the lid up again.

We suggest that you check the operation of the cassette-down and loading-end switches before suspecting trouble in the syscon department. Make sure that the eject button is not stuck, leaky or corroded. If all these things are in order and the contacts on the remote control jack socket are making properly the most likely culprit is the mode select switch.

## **FERGUSON TX10 CHASSIS**

There's quite severe darkening of the picture when white captions are displayed and, depending on the white content of the picture, there's a constant variation of the background brightness-level – particularly on video playback. The VCR is not at fault since it works correctly with another set. The picture seems rather flat generally despite the fact that a new tube has been fitted recently.

It seems very much as though something is amiss in the beam current limiter circuit. Prove it by disconnecting R622, when normal contrast should be restored. If not, the TDA3560 decoder chip IC601 is suspect. If normal contrast does return, check C609 (10 $\mu$ F) then the components between R622 and the tube's outer conductive coating.

### QUERY COUPON

Available until 15th July 1987.  
One coupon, plus a £1.50 (inc. VAT) cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice printed above.

TELEVISION JULY 1987

## ITT CVC1200 SERIES CHASSIS

The problem with this set is that the BU508A chopper transistor goes short-circuit at switch-on. Trying to check on the cause is getting rather expensive!

A very common cause of this symptom is that R716 (150k $\Omega$ ) is faulty. Replace it anyway. If the old one checks o.k., test the following items before restoring power: line output transistor T501, EW modulator diode D501 and the rectifier diodes D732 and D733. If the problem lies with any of these four, leakage or a short-circuit will be indicated.

# TEST CASE

## 295

*Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

VCR repairs are eagerly undertaken by those of our technicians who are following the practical VCR servicing course of the City and Guilds Institute at the local college. They represent good practice for this summer's "hands-on" examination.

Useful experience was promised by a Ferguson 3V42 in the awaiting repair queue. Its problem was noted down as no colour, and the man who picked it up was anxious to deal with it "by the book", as he would have to on the day. Having connected it up and tuned the monitoring TV set to its output channel, he replayed a good test tape of colour bars. Despite the fact that the VCR's rear-mounted switch was set to colour the monitor displayed a crisp black-and-white step wedge.

His next move was to make a recording of the colourful bars reproduced in the E-E mode from a pattern generator and to replay the tape via a working machine. This proved that the fault was also present in the record mode – playback of the tape was in monochrome, with occasional breakthrough of vertical bars of incorrect colour. So it was back in with the colour-bar test tape and settle down to trace the fault with the 3V42 in the playback mode and the scope as the main diagnostic tool.

This machine's video circuit board is mounted print side up in an ideal position for access and diagnosis – above the deck. All the components and test points are clearly marked and the service manual is a helpful one. In short, the working conditions were ideal. Our technician's first check was for an off-tape 625kHz colour-bar signal at TP404, the input to the main up-converter on the board. It was present and at the correct 300mV peak-to-peak level. An output from the converter was present at pin 23 of IC401 and the signal was also present at TP401, proving that the 4-43MHz bandpass filter BPF402 was intact and also that the converter was receiving an input from the sub-converter stage via BPF401.

Continuing along the helpful green dotted line on the circuit diagram, our technician traced a 4-43MHz signal which looked like good colour bars through the crosstalk cancelling circuit then back into IC401 at pin 1. Within the chip, the signal passes from pin 1 to pin 21 via the playback colour-killer, which plainly took some objection to the signal it was seeing: for most of the time the chroma at TP405 was muted. At odd moments the colour-bar signal would appear at TP405, but the monitor's display remained firmly in monochrome! It was correctly deduced that this was due to the action of the auto colour-killer in the TV set – further evidence that the chroma signal was in some way sub-standard, though it looked quite acceptable on the oscilloscope's screen.

The VCR's chroma signal channel was clearly intact, so our technician decided to check the frequency of the voltage-controlled 4-43MHz crystal oscillator. The counter showed that it was correct to within 20Hz: its amplitude at TP403 was also correct. The a.f.c. setting (for 625kHz at TP422) was also found to be correct. Enquiry amongst colleagues on the subject of strange no-colour faults produced horror stories about incorrectly wired video heads, but the drum and the wiring to it had not been disturbed. What next? D.C. voltage checks at the i.c. pins perhaps. These were not very fruitful, and in terms of the practical examination period time was ebbing away. Which essential test had been omitted? See next month's test case page.

### ANSWER TO TEST CASE 294

— page 560 last month —

Our patient last month was a Decca TV set fitted with the 100 series chassis. It appeared to have an evil and obscure a.g.c. fault that put a heavy horizontal shading bar across the picture and thoroughly upset the line and field sync. We had proved that the cause of the trouble was on the i.f. panel – by fitting a known good one. After refitting the set's own panel we'd then encountered some rather puzzling conditions in the a.g.c. department.

The root of the trouble lay at pin 6 of the TCA270S vision demodulator/a.g.c./a.f.c. chip. One generally finds a single capacitor connected between this pin and chassis, the 47nF a.g.c. reservoir capacitor – in this case C126. The Decca designers however had decided to add an extra network consisting of D103 (1N4148) followed by the parallel combination of C125 (4-7 $\mu$ F) and R110 (120k $\Omega$ ) connected to the 12V line, which of course is grounded signalwise. D103 had gone short-circuit, effectively placing C125 in parallel with C126. This hundred-fold increase in the value of the reservoir capacitor was clearly not to the chip's liking.

The network D103/C125/R110 does not normally take any part in the a.g.c. circuit's action – it's there as a clipper to prevent noise spikes and similar disturbances producing spurious a.g.c. effects.

Not a nice fault, though we should perhaps not have taken so long to find a dead short in the only standard diode (as opposed to the various zeners) on the entire i.f. panel.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £16, overseas (surface mail) £19 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

# SPECIAL OFFER THIS MONTH

## PHILIPS YEARS AHEAD THE CREDIT CARD CALCULATOR SOLAR POWERED £4.75

NEW PHILIPS SBC 1833 Solar & Battery Powered Calculator

£8.00

RECEIVER K3 Tex Front Panels with I.C.s (SAA3027P/SAB3013/HO448328)	£5.00	HI-FI MICROPHONE N8501 Philip	£8.00
GEC 1060 Series Automatic Telephone Answering Machine, Ex Demo	£15	G8 TUNER V/CAP on Panel	£3.50
G8 100K Pots on Panel & Lead for 6 Push Button Unit	£2.00	G8 SPEAKER	75p
K30 Mains Switch remote	£1.00	9,000 SPEAKER	£1.00
K35 Mains Switch remote	75p	THORN 9000 Sound OP Panel	£30p
K35 Aerial Socket and Plug in Lead to Tuner	£1.50	ONE I.C. K35 Decoder	£7.00
KT3-K30 Slider Pots 4.7ku 47ku	20p each	THICK FILM, Hitachi RB-32 4A	£2.00
LARGE Foams Pots, Fits Pye, GEC, ITI, Decca	75p	K30 IF/K35 IF	£2.00
G8 Power Supply Panel	£4.00	THICK FILM, Hitachi Frame	£5.00
EX DECCA 80-100 Decoder	£5.00	THORN Lopt 8500-8800	£4.00
EX DECCA 80-100 Frame	£5.00	TX9 THORN Tuner Panel with ICS Pots	£3.00
THORN 8000-8500-8800 Decoder	£6.00	N.E.C. Light Emitting Diodes	20p
GLASS BEADS Diodes 200n/1.2A	25 for £1.00	BY223 Replacement	30p
G11 IF Panel	£8.00	THORN CHASSIS 1600-1700 Series Mono	£10.00
G11 Decoder Panel	£8.00	THORN 1600 Rec. & Anode Cap	50p
SHARP Idler Motor VC180	£7.00	KT3-K30 Slider Pots 4.7k	£1.00 for 10
VIDEO HEADS JVC JHSS	£25	KT-614 UHF V/CAP Tuner	£2.00
NEW and Model PS3B Betamax Equivalent to Sony BSR 08R and 010R-011R and RSV3B	£33.00	K35 20 Turn Pots	6p each
G11 611 Condenser 470/250V ITI	£2.00	HITACHI & GEC 20k Pots	20 for £1.00
G9 Power Panel	£3.50	KT3 K30 Speaker	30p
G8 Line Panel	£12.00	K35 Sound O/P Panel Plug in	£3.00
G8 6 Push Button	£9.00	K35 12 way Push Button Unit	£1.50
KT4-KT3-K30 Handset Replacement	£12.00	K35 L.O.P.T. Split Diode	£6.00
HT520 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90	RANK T20 Front Panel	£6.00
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00	G8 6 Button Unit, New Type	£9.00
LATEST VIDEO For Latest Philips, GEC, Pye and Hitachi Front panel with memory chip and push button and pots and LED's.	£6.00 NEW	6 off LED DISPLAYS, Mixed	£1.00
30AX GEC LOPT Panel with Split Diode	£4.00	HAND SET TESTER, Infra Red	£8.00
LOPT Split Diode 2432871	£7.00	PHILIPS SBC 471 2 Way Stereo Headphone with Volume Controls	£17.00
RANK T20 Focus Pot	75p	AERIAL SPLITTER with filter	£1.00
RANK 718 Focus Pot	£1.00	DYNAMIC STEREO HEADPHONE EM 6146	£10.00
26" LOPT Split Diode 2432301	£8.00	PHILIPS UNI DIRECTIONAL Dynamic Microphone	£10.00
16" LOPT Split Diode 2433481	£6.00	20 TURN POTS with Band Switch	10p
Ex Panel Split Diodes 2432871/2432981	£5	PUSH BUTTON Mains Switch with Screw Holes Fixing	4 for £1
Split Diode 2433752	£6	PYE 713 Line Trans	£4.50
HITACHI Mains Switch	50p	PYE 731 Line Trans	£3.50
HITACHI AE Socket	30p	890v DIODES at 3 amps. Glass Beads	6p each, 20 for £1.00
1 CONDENSER Axial Leads 450 A/C 1200 D/C	15p	G11 6 Touch Unit with Cable Forms (Drawer Unit) Replacement	£12.00
MAINS TRANSFORMER 240v in/20v/8v	£1.00	KT3 Line Output Transformer	£5.00
GREEN FLAT, NEC, LED's	3p each 100 for £2	9000 THORN Front Panel with POTS & Push Buttons	£4.00
15V015V 1 Amp Print Type	£1	THORN 8500 Time Base	£3.00
12+12V 2.8VA Print 1"x1"	75p	7 SEG DISPLAYS 4 Bank Displays Z-042T	50p
8+8V 1 Amp Print	75p	SPLIT DIODE FB51245AR	£5.00
HITACHI 6 x 4 - 8Ω Speaker	50p	PHILIPS KT3 4R7 W.W. Resistor	15 for £1.00
ET596 UHF V/CAP Tuner, small	£2.50	BU508D	for £1.00 each
FIDELITY Panels with I.C	£1.00		
FIDELITY LOPT Split Diode AT2076/80	£3.00		
AT 2076/80	£5.00		
ITT CVC20 to 45 PANELS Send for list	£5.00 each		
PHILIPS KT3-KT35 PANELS Send for list	£5.00 each		

2432211  
2432301  
2432461  
2432491  
2432871  
2432981  
2433212  
2433581  
2433751

**£5  
EACH  
HITACHI  
L.O.P.T.**

33651  
36072  
36362  
36383  
36482  
36761  
36841  
36832  
36833

**L.O.P.T.  
SPLIT DIODE  
PHILIPS  
£5 EACH**

AT2036/00  
AT2048/11  
AT205  
AT2076/35  
AT2076/38  
AT2076/51  
AT2076/55  
AT2076/71  
AT2088/15  
RCO ST CT3325  
OT2041

**£10  
EACH**

# SENDZ COMPONENTS

63 BISHOPSTEIGNTON, SHOEBOURNESS, ESSEX SS3 8AF.

SAME DAY SERVICE

All items subject to availability. No Accounts: No Credit Cards. Postal Order/Cheque with order.  
Add 15% VAT, then £1 Postage. Add Postage for Overseas.

Callers: To shop at

**212 LONDON ROAD, SOUTHEND. Tel. 0702-332992**

Open 9-1/2.30-6. GVMT + school orders accepted on official headings.

Add 10% handling charge.

## HITACHI VHS COLOUR CAMERAS

Mains Only Tested/  
Working – £125

## VHS VIDEOS FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29,  
3V30, 3V31, 3V32, 3V35

## HITACHI

5000, 8000

## NATIONAL PANASONIC

NV8600, 8610, 2000, 7000,  
370, 333, 2010

## SHARP

620, 630, 640, 2300 H T/P  
Untested from £70

## BETAMAX VIDEOS

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9

Untested from £30

HITACHI VHS TUNER/TIMER £10,  
HITACHI VHS BATTERY CHARGER  
£10, ROBERTS VHF RADIOS £5

VHS/Beta tapes used –  
from 40p each

## PLUS

17" 18" 20" 22" 26" Hybrid/  
Solid State from £8. Also available  
CTVs Remote Control & Teletext  
All prices subject to 15% VAT

Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER  
(Electrical) LTD  
FURNACE ROAD,  
GALLOWES INN,  
ILKESTON**

**Phone: 0602 303124**

**W. TREE'S TVs**  
are moving to larger premises.

# SPECIAL CLEARANCE SALE

## OF VIDEO RECORDERS AND TELEVISIONS

Large Selection of Colour TVs  
including portables, remotes  
and Teletext.

Good selection of VHS Videos,  
National Panasonic, Model NV333

**£115 plus VAT.**

National Panasonic, Model 2000

**£115 plus VAT.**

JVC Front loader, Model D120EK

**£145 plus VAT.**

## SPECIAL OFFER

of ex hotel video recorders,  
Philips VHS Model No 6560  
Infra red remote

**£165 + VAT.**

**Present Address:**

**Unit 9, Stonebridge Mills,  
Stonebridge Lane,  
Armley, Leeds 12.**

**New Address:**

**Sunshine Mills, Wortley Road,  
off Whingate Road, Leeds 12.**

By the time this issue is published we hope to be  
installed in our new premises, five minutes drive  
away. If, due to unforeseen circumstances, our move  
is delayed please contact us at our old address.

**Telephone:**

**Leeds (0532) 638804**

# HUSSAIN CENTRAL TV LTD

**BRAND NEW VHS VIDEO  
BEST PRICE IN THE UK  
ONLY £180 – YES £180**

Full Remote – Front Loader – 14 day – 4 event – O.T.R.

**BEST DEAL IN UK FOR NEW VIDEO  
ALSO NOW STOCKING A FULL RANGE OF THORN  
EX RENTAL VIDEO AND TV**

**HOT NEWS. 5,000 LATE MODEL TV'S AVAILABLE**  
27" SONY TEXT – TX STEREO TEXT – PHILIPS' STEREO TEXT  
HITACHI AND TOSHIBA MONITOR STYLE TEXT – 16" STEREO TEXT  
14" and 16" R/C PORTABLES – 14" and 16" PORTABLES  
Plus many more models in stock. All Handsets supplied with working  
TV's, and all Cabinets in excellent condition.

## VIDEO

**CHEAPEST EVER ELECTRONIC WORKING VHS VIDEO**

**From £85**

**CHEAPEST EVER ELECTRONIC WORKING BETA VIDEO**

**From £20**

*Many models and types in stock*

*All stock is the highest quality in the UK  
If you are looking for the best stock you must visit  
one of our branches now*

*All prices are subject to 15% VAT and based on quantity*

<b>BIRMINGHAM</b> 021-622 1023 021-622 1517	<b>LONDON</b> 01-961 5005	<b>PRESTON</b> 0772-312101	<b>SOUTHAMPTON</b> 0703-777254	<b>CHEPSTOW</b> 0291-271000
---	------------------------------	-------------------------------	-----------------------------------	--------------------------------

# MONTANA MAIL ORDER

## SPECIAL OFFER

FREE

T.V. LOOP AERIAL  
WITH ALL ORDERS  
OVER £5.00

### TRANSISTORS

AC127	£0.34	BF258	£0.40
AC128	£0.34	BF259	£0.35
AC176	£0.34	BF336	£0.30
AC187	£0.38	BF337	£0.40
AC188	£0.38	BF338	£0.40
AD149	£1.00	BF355	£0.52
AD161	£0.54	BF362	£0.78
AD162	£0.54	BF422	£0.30
AF124	£0.48	BF423	£0.48
AF125	£0.48	BF458	£0.32
AF126	£0.48	BF459	£0.54
AF127	£0.50	BF462	£1.48
AF239	£0.60	BF597	£0.16
AU113	£5.20	BRF39	£0.35
BC107	£0.19	BRF79	£0.35
BC108	£0.19	BFY50	£0.35
BC109	£0.19	BFY51	£0.48
BC141	£0.40	BR100	£0.28
BC142	£0.40	BR103	£0.84
BC143	£0.40	BR303	£1.40
BC147A	£0.10	BSS101	£0.08
BC148	£0.12	BT116	£1.86
BC149	£0.14	BT151-800	£1.60
BC157	£0.12	BU126	£1.68
BC158	£0.16	BU128	£1.48
BC159	£0.12	BU208A	£1.40
BC171	£0.15	BU208D	£1.90
BC172C	£0.28	BU326A	£1.80
BC177B	£0.28	BU406	£1.00
BC182B	£0.11	BU407	£1.20
BC182C	£0.12	BU426A	£1.54
BC183	£0.10	BU500	£2.30
BC183L	£0.13	BU508A	£2.00
BC184	£0.13	BU526A	£2.20
BC184L	£0.13	BU596	£1.60
BC186	£0.34	BU807	£1.60
BC212	£0.10	BUX84	£0.50
BC218	£0.14	BYW56	£1.34
BC213	£0.14	BYW96E	£0.80
BC213L	£0.14	BY127GP	£0.18
BC214	£0.14	BY164	£0.56
BC214L	£0.14	BY179	£0.86
BC237	£0.14	BY206	£0.16
BC238	£0.14	BY210-800	£0.32
BC239	£0.18	BY227	£0.38
BC258	£0.10	BY228	£0.80
BC300	£0.48	BY229-800	£1.00
BC307	£0.13	BY298	£0.24
BC308	£0.14	BY299	£0.26
BC309	£0.16	BY310	£0.38
BC309B	£0.12	BY355-600	£0.30
BC327	£0.16	C106D	£0.46
BC328	£0.14	ME6002	£0.08
BC337	£0.16	MJE340	£0.56
BC337L	£0.16	0891	£0.06
BC339	£0.16	SK44F	£0.06
BC413C	£0.15	SK55F	£1.60
BC547	£0.12	STR441	£0.08
BC548	£0.12	STR451	£0.08
BC549	£0.10	STR6020	£0.20
BC557B	£0.12	TIC44	£0.68
BC558	£0.12	TIP30C	£0.54
BC639	£0.17	TIP31A	£0.54
BC640	£0.20	TIP32A	£0.48
BC727	£0.22	TIP32C	£0.46
BC771	£0.29	TIP33	£1.00
BCX30	£0.15	TIP41A	£0.45
BCX36	£0.15	TIP41C	£0.45
BD124P	£0.76	TIP42A	£0.45
BD131	£0.46	TIP42C	£0.45
BD132	£0.50	TIP47	£0.82
BD136	£0.34	TIP112	£0.72
BD137	£0.13	TIP117	£0.72
BD138	£0.32	TIP132	£1.10
BD139	£0.20	TIP137	£1.10
BD179	£0.72	TIP2955	£0.98
BD203	£0.62	TIP3055	£0.98
BD222	£0.66	VA1104	£0.90
BD225	£0.68	VA8650	£0.56
BD233	£0.68	7805	£0.82
BD234	£0.44	7812	£0.82
BD237	£0.48	IN971	£0.06
BD238	£0.48	IN4001	£0.06
BD239	£0.42	IN4002	£0.06
BD278A	£0.72	IN4003	£0.06
BD410	£1.00	IN4004	£0.06
BD437	£0.50	IN4005	£0.06
BD438	£0.50	IN4007	£0.09
BD441	£0.68	IN4148	£0.04
BD442	£0.68	IN4446	£0.04
BD589	£0.84	IN5410	£0.13
BD707	£0.84	IN5402	£0.17
BD708	£0.84	IN5404	£0.15
BD709	£0.84	IN5406	£0.17
BDX32	£1.88	IN5407	£0.18
BF180	£0.36	IN5408	£0.18
BF178	£0.10	2N3055	£0.80
BF194	£0.20	2N4444	£2.00
BF195	£0.12	2N5246	£0.80
BF196	£0.16	2N5496	£0.80
BF197	£0.22	2N3702	£0.10
BF198	£0.15	2N3703	£0.10
BF199	£0.17	2N3704	£0.10
BF200	£0.60	2N3706	£0.10
BF257	£0.36	2N3904	£0.10

### INTEGRATED CIRCUITS

BRC-M-300	£6.00	STK436	£8.00
BA301	£1.20	STK439	£9.00
BA311	£1.20	STK441	£13.95
BA313	£1.60	STK443	£13.50
BA511A	£2.50	STK459	£10.00
BA521	£2.30	STK460	£12.95
BA536	£3.80	STK461	£12.95
BA843	£4.00	TA7060AP	£1.00
BA1330	£1.90	TA7072P	£1.00
HA1306W	£2.60	TA7152P	£4.00
HA1322	£3.00	TA7176	£2.46
HA1366W	£1.96	TA7193P	£6.95
HA1369WR	£2.80	TA7201P	£3.00
HA1367	£7.20	TA7203P	£2.60
HA1368	£1.90	TA7204P	£1.90
HA1368R	£2.40	TA7205AP	£2.40
HA1377	£6.00	TA7208P	£2.70
HA1385	£3.36	TA7210P	£4.50
HA1389R	£2.54	TA7241P	£3.00
HA1392	£3.04	TA7215P	£2.95
HA1393	£5.00	TA7222AP	£2.20
HA1398	£4.00	TA7227	£3.40
LA1352	£2.00	TA7229P	£5.40
LA3160	£2.30	TA7313AP	£1.66
LA3350	£1.46	TA8100	£3.60
LA3361	£1.64	TA7608	£3.95
LA4031P	£3.00	TA7611	£4.40
LA4032P	£2.00	TA8550	£0.40
LA4051P	£2.80	TA8621	£2.50
LA4100	£1.28	TBA120SB	£1.10
LA4102	£1.46	TBA120U	£1.10
LA4125	£2.82	TBA395	£1.40
LA4420	£1.80	TBA396	£1.34
LA4430	£1.50	TBA5300	£1.60
LA4480	£3.00	TBA540	£1.50
LA4481	£3.00	TBA560	£1.80
LM1011	£2.24	TBA720A	£1.56
M5152L	£1.06	TBA7500	£3.00
M51515BL	£1.82	TBA800	£1.12
M5327AP	£1.40	TBA810S	£1.46
MC1352	£1.10	TBA920	£1.90
ME3705 2X	£2.80	TBA950 2X	£1.80
MB3712	£1.80	TBA990	£1.56
MB3713	£1.80	TBA1441	£2.00
ML231B	£2.60	TCA2700	£2.20
ML237	£2.60	TCA800	£7.00
NE555	£0.40	TCA940	£2.00
SA1025	£6.00	TD4440	£3.00
SA1124	£4.80	TD1002	£1.60
SAAS100	£8.00	TD1003	£3.70
SA1251	£4.00	TD1006	£2.40
SAS560	£2.10	TD1035T	£3.50
SAS570	£2.52	TD1044	£3.10
SAS580	£3.00	TD1074	£1.70
SAS90	£3.00	TD1170	£1.83
SL901	£7.50	TD1180P	£2.94
SL917	£7.50	TD1190P	£4.00
STA401	£6.00	TD1236	£4.30
STK0059	£8.00	TD1327	£1.80
STK013	£4.00	TD1412	£1.52
STK014	£1.00	TD1512Q	£4.40
STK016	£1.00	TD1770	£5.95
STK016	£1.00	TD1908	£2.80
STK077	£8.00	TD2003	£1.90
STK080	£16.00	TD2004	£1.80
STK433	£6.00	TD2006	£1.80
STK435	£6.50	TD2010	£2.80

### ENQUIRIES WELCOME FOR PARTS NOT LISTED

### FUSES

A/S 20mm 63-80	£2.80	OB 20mm 250-5	£0.70
100-315	£1.95	OB 1 1/4 500-5	£1.00
400-6-3	£1.30	1" Mains 2, 3, 5, 13	£1.00
A/S 1 1/4 250-5	£2.40		

### CAPACITORS - AXIAL

220mfd 63v	£0.42	1000mfd 25v	£0.40
47mfd 63v	£0.68	2200mfd 25v	£0.68
1000mfd 63v	£1.20	1mfd 63v	£0.06
10mfd 25v	£0.10	2200mfd 63v	£1.38
22mfd 25v	£0.11	1mfd 450v	£0.24
47mfd 25v	£0.12	2.2mfd 450v	£0.30
100mfd 25v	£0.14	3.3mfd 450v	£0.38
220mfd 25v	£0.20	4.7mfd 450v	£0.48
470mfd 25v	£0.32	10mfd 450v	£0.60
1000mfd 25v	£0.52	22mfd 450v	£0.70
2200mfd 25v	£0.84	33mfd 450v	£0.72
4700mfd 25v	£1.20		
1mfd 63v	£0.10		
2.2mfd 63v	£0.11		
4.7mfd 63v	£0.11		
10mfd 63v	£0.13		
22mfd 63v	£0.13		
47mfd 63v	£0.18		
100mfd 63v	£0.26		

### CAPACITORS - RADIAL

1-22mfd 25v	£0.06	100mfd 16v	£0.08
4.7mfd 25v	£0.08	220mfd 16v	£0.10
10mfd 25v	£0.10	470mfd 16v	£0.16
22mfd 25v	£0.14	1000mfd 16v	£0.22
47mfd 25v	£0.22		

### E.H.T TRAYS

Univers KT3	£5.50	Anode Cap	£0.60
Philips 68 550	£7.95	Coax Coupler	£0.17
Thorn 9000	£8.20	Coax Plug	£0.17
ITT CVC 30	£8.75	TX10 Focus Unit	£9.95
ITT CVC 45	£7.80	General Purpose on/off switch	£17.95
Decca 80	£7.05	Mains front mounting	£8.75
	£7.00	Tuners and other trays available on request	

### SUNDRIES

Anode Cap	£0.60
Coax Coupler	£0.17
Coax Plug	£0.17
TX10 Focus Unit	£9.95
General Purpose on/off switch	£17.95
Mains front mounting	£8.75
Tuners and other trays available on request	

### OSCILLOSCOPES

TELEQUIPMENT D83. Dual Trace 50MHz Delay Sweep. Large Tube.	£375
TELEQUIPMENT D75. Dual Trace 50MHz. Delay Sweep.	£325
TELEQUIPMENT D61A. Dual Trace 10MHz With Manual.	£150
S.E. LABS SM111. Dual Trace 18MHz Solid State Portable AC or External DC operation 8 x 10cm display with Manual.	£165
TELEQUIPMENT D43. Dual Trace 15MHz. With Manual.	£100
TELEQUIPMENT S54A. Single Trace 10MHz. Solid State. With Manual.	£110

### MULTIMETERS

AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently) Complete with Batteries & Leads	£55
AVO 8 Mk2 Complete with Batteries & Leads	£45
Above Items in GOOD WORKING ORDER - appearance not A1 hence the price.	
AVO TEST SET NO 1 (Military version of AVO 8) Complete with batteries, leads & Carrying Case	£85
TEST LEADS suitable for AVOMETERS. Red & Black with 2 Croc-Clips & 2 Prods. (p&p £2)	£5

### ANALOGUE POCKET MULTIMETERS

Philips/Taylor/AVO etc. Complete with Batteries & Leads	from £10
---	----------

### AVO TRANSISTOR TESTER TT169

Handled. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12

B+K Precision CRT Restorer/Analyser Model 467. Supplied with 2 Bases and Manual. (P&P £7)	ONLY £125 each
Labgear Colour Bar Generator KG1 8 Test Patterns. (P&P £4).	ONLY £40 each
LABGEAR COLOURMATCH PATTERN GENERATOR Type CM6038-DB Crosshatch/Grey Scale/Blank Raster. Mains or Battery. (ONLY £12 each P&P £2)	
MARCONI TF2604 (Later version of TF 1041 VTVM) 20Hz-1500MHz; AC/DC/Ohms AC 300mV-300V FSD	£50
MARCONI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V FSD	£40
PHILIPS COLOURBAR GENERATOR type 5501 (P&P £5)	£100
PHILIPS COLOURBAR GENERATOR type 5508. Video out. Many Functions	£125

### USED EQUIPMENT - WITH 30 DAYS GUARANTEE. MANUALS SUPPLIED IF AVAILABLE. This is a VERY SMALL SAMPLE OF STOCK. SAEL or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.

## STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: 0734 68041

Callers welcome 9 am-5.30 pm Mon.-Fri. (until 8 pm Thurs.)

# BOLTEN LTD.

63, JEDDO ROAD, LONDON W12 9EE.  
Tel: 01-749 0915 (2 lines)  
Telex: 262421 BOLTEN G

### VIDEO HEADS

Sony Universal Eq. DSR 36	£29.95
Sony Universal Eq. DSR 43	£29.95
Sony C-9	£47.95
Ferguson/JVC Universal	£28.50
National Panasonic Universal	£28.50
National Panasonic (370/380/430/460)	£32.95
National Panasonic (777/330)	£46.95
Hitachi 5000 (Not Genuine)	£29.95
Hitachi VT11/HIVI/VT33 (Genuine)	£29.95
Toshiba 9600	£39.00
Sanyo (Genuine)	£44.95
Fisher Universal Eq. FVH D720	£37.00
Akai Universal	£28.50
Sharp	£39.95
Amstrad 7000/9000/4600	£32.95
Saisho 605/705/805/905/100	£32.95
Triumph	

AN127Q	£2.20	AN7146M	£2.20	HA1199	£1.85	LA1111P	£0.95	M5106P	£2.75	STK451	£6.75	TA7628P	£2.95	2SA101	£0.60
AN203	£2.20	AN7154	£2.20	HA1306W	£1.85	LA1140	£2.20	M5134P	£2.25	STK570	£6.80	TA7640AP	£1.75	2SA103	£0.60
AN210	£1.75	AN7156N	£2.50	HA1319	£1.50	LA1201	£0.85	M5155P	£1.85	STK570	£4.25	TA7641BP	£1.95	2SA329	£0.60
AN211A	£2.30	AN7158N	£2.25	HA1339A	£2.50	LA1230	£1.00	M51102L	£3.95	STK7308	£5.95	TA7658P	£1.75	2SA350	£0.60
AN214Q	£1.80	AN7160	£3.75	HA1366W	£1.80	LA1231	£2.35	M51513L	£1.80	STK7400	£5.80	TA7668BP	£1.98	2SA445	£0.40
AN217B	£2.20	AN7168	£2.75	HA1366WR	£1.85	LA1240	£1.95	M51514AL	£1.95	STK7441	£5.80	TA7688P	£2.95	2SA539	£0.40
AN228W	£2.90	AN7168	£2.75	HA1368	£1.85	LA1240	£1.95	M51515BL	£2.70	STK7441	£5.80	TA7688P	£2.95	2SA562	£0.40
AN234	£2.95	AN7178	£2.75	HA1368B	£1.85	LA1240	£1.95	M51516BL	£2.70	STK7441	£5.80	TA7688P	£2.95	2SA643	£0.30
AN236	£2.50	AN7213	£2.20	HA1368R	£1.85	LA1240	£1.95	M51517BL	£2.70	STK7441	£5.80	TA7688P	£2.95	2SA733	£0.30
AN239Q	£4.20	AN7223	£3.95	HA1372	£3.50	LA1460	£2.50	M51518BL	£2.20	STK7441	£5.80	TA7688P	£2.95	2SA768	£0.95
AN240P	£1.50	AN7273	£3.95	HA1374	£2.50	LA2100	£2.95	M51521AL	£1.90	TA7051P	£1.80	UPC41C	£2.30	2SA952	£0.40
AN241P	£1.50	AN7310	£1.20	HA1377	£2.20	LA3160	£1.50	MB3705	£1.80	TA7054P	£2.20	UPC56H	£0.75	2SA1015	£0.35
AN247P	£2.50	AN7311	£1.20	HA1388	£3.50	LA3161	£2.50	MB3712	£1.50	TA7066P	£1.50	UPC573C	£2.50	2SA1102	£0.20
AN259	£2.75	BA301	£0.80	HA1389	£2.20	LA3201	£0.95	MB3713	£1.60	TA7070P	£1.95	UPC574J	£0.65	2SA1103	£0.20
AN260P	£2.20	BA311	£0.95	HA1389R	£2.20	LA3210	£0.75	MB3722	£3.50	TA7074P	£1.95	UPC575C	£1.00	2SA1104	£0.20
AN262	£1.50	BA313	£0.80	HA1392	£2.20	LA3300	£1.30	MB3730	£2.50	TA7106P	£1.50	UPC576H	£2.20	2SA1106	£0.20
AN271A	£2.50	BA318	£1.50	HA1394	£2.95	LA3350	£1.30	MB3731	£3.50	TA7108P	£2.50	UPC578C	£1.30	2SB54	£0.70
AN274	£2.75	BA401	£0.80	HA1397	£2.75	LA3361	£1.20	MB3756	£2.60	TA7120P	£0.75	UPC592H	£0.95	2SB75	£0.70
AN295	£3.60	BA402	£0.80	HA1398	£2.75	LA3370P	£2.00	MB8719	£3.85	TA7122AP	£0.90	UPC595C	£2.20	2SB831V	£0.75
AN301	£3.50	BA403	£1.95	HA1457W	£3.75	LA4030P	£2.00	SI-1125H	£10.50	TA7136P	£1.00	UPC1001H	£2.20	2SB8405	£0.75
AN302	£3.30	BA511A	£1.80	HA1123W	£3.75	LA4031P	£1.95	SI-1125H	£10.50	TA7136P	£1.00	UPC1001H	£2.20	2SB8426	£0.75
AN303	£2.75	BA514	£1.90	HA11211	£2.30	LA4032P	£1.90	STK011	£9.95	TA7137P	£1.00	UPC1018C	£1.95	2SB8471	£0.75
AN305	£3.50	BA521	£1.80	HA11215A	£4.35	LA4051P	£2.20	STK013	£7.25	TA7139P	£2.50	UPC1025H	£3.30	2SB8492	£0.75
AN313U	£2.95	BA526	£3.50	HA11219	£3.25	LA4100	£1.20	STK014	£7.25	TA7140P	£1.75	UPC1026C	£1.00	2SB85090	£1.95
AN315	£2.30	BA527	£1.60	HA11221	£3.75	LA4101	£1.00	STK015	£5.20	TA7142P	£2.95	UPC1028H	£0.90	2SB8536	£0.35
AN316	£3.75	BA532	£1.60	HA11223W	£3.80	LA4102	£1.40	STK020	£5.75	TA7145P	£2.50	UPC1031H	£1.95	2SB8546	£0.50
AN318	£4.95	BA536	£2.40	HA11225	£1.95	LA4110	£1.75	STK022	£3.50	TA7150P	£2.75	UPC1032H	£0.60	2SB8561	£0.35
AN331	£2.95	BA547	£2.50	HA11227	£2.40	LA4120	£2.95	STK025	£7.50	TA7152P	£2.50	UPC1035C	£1.95	2SB8588	£0.30
AN340P	£1.50	BA612	£1.80	HA11235	£2.30	LA4125	£2.20	STK043	£10.50	TA7167P	£2.75	UPC1156H	£2.95	2SC372	£0.35
AN360	£1.30	BA631	£3.75	HA11244	£2.60	LA4126	£2.60	STK077	£6.50	TA7193P	£4.00	UPC1158H	£0.95	2SC380	£0.35
AN362L	£1.60	BA656	£4.50	HA11401	£2.80	LA4140	£0.80	STK078	£6.75	TA7202P	£4.50	UPC1165C	£1.30	2SC458	£0.35
AN366P	£2.20	BA843	£4.50	HA11423	£2.75	LA4150	£0.80	STK080	£7.50	TA7204P	£1.90	UPC1168C	£1.30	2SC460	£0.35
AN374P	£2.00	BA847	£7.75	HA11440A	£3.50	LA4152	£2.50	STK082G	£7.75	TA7204P	£1.75	UPC1170H	£1.95	2SC461	£0.35
AN377	£2.00	BA853	£7.50	HA11701	£3.50	LA4182	£2.10	STK086	£9.50	TA7205AP	£1.00	UPC1171C	£1.50	2SC5039	£0.70
AN610P	£1.80	BA1310F	£1.75	HA11703	£4.50	LA4192	£1.95	STK430	£3.50	TA7207P	£1.75	UPC1176C	£1.75	2SC536	£0.35
AN612	£1.80	BA1320	£1.25	HA11704	£5.20	LA4200	£1.50	STK431	£3.95	TA7208P	£1.75	UPC1177H	£1.60	2SC537	£0.35
AN5033	£5.25	BA1330	£1.75	HA11705	£6.95	LA4201	£1.60	STK433	£5.25	TA7210P	£2.50	UPC1181H	£1.10	2SC5710	£0.35
AN5265	£3.50	BA1360	£1.80	HA11706	£4.75	LA4220	£1.50	STK435	£5.50	TA7214P	£2.60	UPC1182H	£1.10	2SC5732	£0.35
AN5510	£2.75	BA1610	£1.80	HA11710	£3.75	LA4230	£2.25	STK436	£5.25	TA7215P	£2.60	UPC1183H	£2.20	2SC5783	£0.35
AN5620X	£3.50	BA1502A	£2.75	HA11711	£9.50	LA4250	£2.75	STK437	£5.50	TA7217AP	£1.60	UPC1185H	£2.50	2SC5828	£0.35
AN5701	£1.80	BA5406	£3.20	HA11713	£6.50	LA4420	£1.60	STK439	£9.95	TA7220P	£2.50	UPC1186H	£0.90	2SC640	£0.35
AN5722	£1.60	BA6137	£2.75	HA11714	£5.95	LA4422	£1.40	STK441	£7.95	TA7222AP	£1.30	UPC1187V	£1.75	2SC690	£0.35
AN5730	£1.85	BA6209	£3.20	HA11715	£6.25	LA4430	£1.40	STK443	£7.95	TA7223P	£2.30	UPC1215V	£1.35	2SC9290	£0.35
AN5732	£1.85	BA6304	£3.75	HA11716	£6.75	LA4440	£2.50	STK457	£6.50	TA7225P	£3.25	UPC1223C	£2.20	2SC9300	£0.35
AN5753	£2.95	CK0642	£3.50	HA11717	£5.75	LA4445	£2.75	STK459	£6.75	TA7226P	£2.20	UPC1225H	£2.00	2SC1034	£0.75
AN6250	£2.30	CK0642	£3.50	HA11718	£4.75	LA4460	£1.80	STK461	£7.50	TA7227P	£2.20	UPC1230H	£2.50	2SC1061	£0.20
AN6310	£2.25	CK0658	£2.95	HA11727	£9.50	LA4461	£1.80	STK463	£8.40	TA7229P	£3.25	UPC1263C	£2.50	2SC1096	£0.70
AN6341N	£4.00	CK095C	£2.85	HA11745	£9.00	LA4500	£2.60	STK465	£9.50	TA7230P	£1.95	UPC1277H	£2.75	2SC1364	£0.35
AN6344	£4.75	CK100D	£2.85	HA11747	£9.50	LA4505	£2.80	STK501	£6.25	TA7232P	£2.95	UPC1278H	£2.75	2SC1815V	£0.40
AN6350	£7.50	CK101G	£7.75	HA11747A1	£9.50	LA4507	£4.25	STK6025	£4.95	TA7240AP	£2.95	UPC1350C	£1.20	2SC1875	£2.95
AN6366N	£4.50	CK130	£4.75	HA11749	£4.75	LA4520	£2.50	STK6029	£4.75	TA7241AP	£2.95	UPC1353C	£1.95	2SC1842	£0.35
AN6360	£4.50	CK130	£4.75	HA11750	£5.00	LA5112	£1.85	STK6039	£4.75	TA7270P	£2.75	UPC1356C	£2.00	2SC1957	£0.80
AN6362	£5.50	CK136A	£7.50	HA11751NT	£8.50	LA6580	£1.20	STK6040	£6.25	TA7310P	£1.85	UPC1363C	£2.20	2SC1969	£0.75
AN6363	£7.50	CK143A	£7.50	HA11753NT	£8.50	LA7016	£1.75	STK6049	£6.50	TA7312P	£1.50	UPC1378H	£2.40	2SC2078	£1.95
AN6387	£5.95	CK157	£4.25	HA11758NT	£8.50	LA7215	£1.75	STK6059	£7.00	TA7313AP	£1.50	UPC1382C	£1.20	2SC2166	£1.95
AN6610	£1.80	CK158	£3.75	HA11768	£4.50	LA7751	£4.75	STK6080	£6.75	TA7314P	£2.50	UPC1384C	£2.85	2SC2335	£1.50
AN6677	£3.50	CK160	£3.50	HA11788	£3.50	LA8105	£2.20	STK2028	£7.50	TA7315AP	£2.35	UPC1387C	£2.50	2SC2577	£1.95
AN6811	£1.60	CK161A	£3.50	HA11816NT	£6.50	LA7800	£2.95	STK2029	£3.95	TA7319P	£2.95	UPC1395C	£2.95	2SC2784	£2.25
AN6873	£4.50	CK162	£3.95	HA11828NT	£6.50	LA7801	£2.95	STK2129	£6.75	TA7324P	£2.50	UPC1403CA	£5.75	2SC2579	£2.95
AN6884	£2.30	CK170	£6.75	HA12001W	£6.50	LA7806	£2.75	STK2230	£6.50	TA7325P	£1.00	UPC1408CA	£6.50	2SC2580	£2.50
AN7105	£2.30	CK181	£6.75	HA12002	£2.95	LA7808	£2.95	STK3042	£6.50	TA7328AP	£2.20	UPC1458C	£1.95	2SC2580	£2.50
AN7110	£1.50	HA1124A	£2.75	HA12017	£2.75	LB1287	£7.75	STK4060	£6.50	TA7331P	£2.20	UPC1503HA	£1.75	2DA0202	£0.80
AN7111	£1.75	HA1137W	£2.75	HA12035	£3.50	LA8105	£2.20	STK4141H	£7.50	TA7343P	£2.95	UPC4557C	£1.50	2DA0203	£0.80
AN7114E	£1.75	HA1137W	£2.75	HA12038	£2.95	LC4066B	£2.95	STK4191H	£3.95	TA7347P	£2.95	UPC4588C	£2.95	2DA0204	£0.80
AN7115E	£1.60	HA1144	£4.25	HA12413	£3.50	LC7120	£3.50	STK4332	£5.75	TA7608CP	£3.95	UPD1514C	£3.75	2DA0205	£2.75
AN7116	£1.50	HA1151	£2.50	HA13001	£2.95	LC7130	£3.50	STK4392	£7.50	TA7609P	£2.70	UPD1548C	£3.50	2DA0206	£1.50
AN7120	£1.50	HA1156W	£1.20	HA13402	£4.95	LC7131	£3.75	STK5211	£6.75	TA7611AP	£2.30	X0042CE	£2.20	2DA0207	£1.40
AN7130	£1.30	HA1167	£1.75	HA13403	£7.50	LC7136	£2.75	STK5421	£6.75	TA7614AP	£2.75	X0077EE	£9.95	2DA0230	£1.40
AN7145M	£1.95	HA1136	£1.75	HA13404	£4.50	LC7137	£2.75	STK5422	£6.75	TA7617AP	£2.50	X0092CE	£5.60	2DA3562A	£5.50

# T. POWELL

16 PADDINGTON GREEN,  
LONDON W2 1LG

Tel: 01-723 9246 (Answerphone)

<b>VIDEO BELT KITS</b>	<b>LATE EXTRA</b>		
AKAI VS-2EG/5EG (5)	£2.00	AN5430	£2.95
AKAI VS 9700G (6)	£2.25	AN7140	£2.20
FISHER VBS 7000 (6)	£2.70	UPC1365C	£3.60
FISHER VBS 9000 (3)	£1.50	UPC1394C	£1.95
HITACHI VT5000 (7)	£2.20	SA11	

# FAST VIDEO SPARES FAST

## VIDEO HEADS

<b>Panasonic</b>	
NV2000, 2010, 7000, 7200, 8600, 8610, 333, 370 genuine	£44.00
NV366, 688, 777, 788 genuine	£64.50
Panasonic 4HSS Equivalent heads (Not NV366)	£31.95
<b>Ferguson</b>	
3292, 3V00, 3V16, 3V22, 3V23, 3V24, 3V29, 3V30, 3V35, 3V36, 3V38 genuine	£49.50
Ferguson 3HSS Equivalent heads	£31.95
<b>Sharp</b>	
VC9300, 9500, 9700, 381, 386, 387, 388, 482, 581 genuine	£67.20
Sharp VC7300, 7700, 8300 genuine	£73.00
Sharp VC9300 etc Equivalent	£39.90
<b>Sony</b>	
C5, C6, C7 genuine	£49.50
Sony SL8000, 8080 genuine	£54.50
Sony C9, C20, C30 genuine	£54.50
Sony C9	£46.50
Sony C5, C6, C7 Equivalent	£31.95
Sony C20, C30 Equivalent	£36.50
<b>Sanyo</b>	
VTC9300, 5000, 5150, 5300, 5400 genuine	£49.90
<b>Toshiba</b>	
V9600, V31, V33 Equivalent	£42.50
Toshiba V9600, V31, V33 genuine	£54.60
Toshiba V8600 genuine	£67.50
<b>Hitachi</b>	
VT5000, 8000, 8300, 9300, 9500, 9700, VT11, VT14E genuine	£39.95
Amstrad 7000 Equivalent	£39.90
<b>Fisher</b>	
615/620 Equivalent	£46.00
<b>PINCH ROLLERS</b>	
<b>Panasonic</b>	
NV2000, 7000, 7200	£5.95
NV333, 366, 688, 370	£7.95
NV430, 730	£7.95
<b>Sharp</b>	
VC6300	£7.90
VC7300, 7700, 8300	£8.70
VC9300, 381, 386 etc	£5.40
<b>Hitachi</b>	
VT5000, 8000, 9000	£6.95
VT11E, 14E, 17E, 19E	£6.95
<b>Sony</b>	
C5, C6, C7	£5.95
SL-C20, C30, C40	£5.95
SL8000, 8080	£5.95
<b>Ferguson/JVC</b>	
3V00, 3V16, 3V22	£5.95
3V23, 3V24, 3V29, 30	£7.95
3V35, 36, 38, 39	£8.90
<b>Sanyo</b>	
VTC9300, 5000, 5300	£7.95
VTC5400, 5150, 6500	£7.95

ALL STOCK ITEMS ARE DESPATCHED BY RETURN OF POST

**WE CARRY HUNDREDS OF VIDEO SPARES INC. PLAY IDLERS, CLUTCHES, MOTORS, SERVICE MANUALS, TENSION BANDS, BELTS AUDIO/CONTROL HEADS, ALIGNMENT TOOLS AND TAPES ETC. \*\*SPECIAL ORDER FACILITIES\*\* \*\*FOR NON-STOCK ITEMS\*\***

**CREDIT CARD ORDERS BY TELEPHONE RECEIVED BY 4 PM. ARE DESPATCHED SAME DAY**

ALL SPARES LISTED ARE GENUINE PARTS. WE ALSO STOCK THE FULL RANGE OF CHEAPER REPLACEMENT PARTS E.G. BELT KITS, PINCH ROLLERS, HEADS, ETC. P.O.A.

## IDLERS (GENUINE)

<b>Panasonic</b>	
NV2000, 7000, 7200	£3.45
NV333, 366, 688, 788	£3.45
NV777, 370, 430	£4.50
NV730	£6.50
<b>Sharp</b>	
VC9300, 9500, 9700	£3.90
381, 386, 387, 388	£3.90
482, 483, 486, 581 etc	£3.90
<b>Amstrad</b>	
7000	£3.90
<b>Sony</b>	
C5/C7 Idler kit	£4.95
C6 Idler kit	£4.95
C5/6/7 Idler only	£1.65
<b>Sanyo</b>	
Reel drive pulley	£8.88
VTC5000, 5150, 6500	£8.88
<b>Hitachi</b>	
VT8000, 8300, 8500	£4.72
VT9300, 9500, 9700	£4.75
VT11E, 14E, 17E, 19E	£6.50
<b>Ferguson</b>	
Clutch assy large	£6.95
3292, 3V00, 3V16, 3V22	£6.95
Clutch assy small	£6.95
Idler assy 3V29, 30	£3.45
3V35, 3V36, 3V38, 3V39	£4.50
<b>Fisher</b>	
FVHP615 etc	£6.90

## SENSOR LAMPS

All Panasonic	£1.80
All Ferg/JVC	£2.90
Sharp VC9300 etc	£2.90
Sharp VC7300 etc	£2.90
All Hitachi	£1.80

## SENSOR L.E.D.'s

All Panasonic	£2.90
All Ferg/JVC	£2.90
All Hitachi	£5.75

**HUNDREDS OF SPARES FOR PANASONIC, HITACHI, SANYO, SONY, FERGUSON, ETC. AVAILABLE**

## BELT KITS (GENUINE)

<b>Panasonic</b>	
NV2000, 2010	£6.50
NV7000, 7200	£6.50
NV333, 366	£6.50
NV688, 788	£4.70
NV8600, 8610	£6.50
<b>Sharp</b>	
VC6300	£6.50
VC7300, 7700	£6.50
VC9300	£6.50
VC9300, 381 etc	£6.50
<b>Sanyo</b>	
VTC9300	£6.50
VTC5000	£1.99
VTC5300, 5400	£6.50
<b>Sony</b>	
SLC5, C7	£6.50
SLC6	£7.50
SL8000, 8080	£6.50
<b>Hitachi</b>	
VT5000	£6.50
VT8000, 8500	£2.90
VT9300, 9300	£3.30
VT11E, 14E, 17E	£6.50
<b>Ferguson/JVC</b>	
3V00, 3V16, 3V22	£6.50
3V23	£4.50
3V29, 3V30	£6.50
3V35, 36, 38, 39	£3.90
<b>Toshiba</b>	
V9600	£6.50
V8600	£6.50
<b>MOTORS</b>	
<b>Reel Motors</b>	
Sharp 9300 etc	£18.20
Amstrad 7000	£18.20
Sanyo 5000 etc	£14.20
Panasonic NV333	£16.80
<b>Drum Motors</b>	
Ferg/JVC, 3V22 etc	£29.90
Sharp 9300 etc	£29.30
Hitachi VT5000	£24.75
Sharp VC7300, V08300	£26.40
<b>Capstan Motors</b>	
Sharp 9300, 9500	£29.30
VC8300	£39.90
VC7300, 7700, 7750	£29.30
Ferg/JVC, 3V22 etc	£29.90
3V29, 3V30	£29.60
3V35, 36, 38, 39	£29.90
Hitachi VT5000	£24.75
VT8000, 8300, 8500	£37.70
VT9300, 9500	£37.70
VT11E, 14E, 17E	£27.30
Sony C5, C7	£34.50

MOST OTHERS AVAILABLE

## TELEVIDEO SERVICES

**145 STATION RD, BEESTON, NOTTINGHAM NG9 2AZ, TEL: 0602-226070**



Send 2 x 18p stamps for full catalogue.

Please add 50p post & packing and then add 15% VAT to total

OVERSEAS ORDERS WELCOME ON CREDIT CARDS, POSTAGE AT COST OFFICIAL ORDERS WELCOME FROM COLLEGES ETC.

## NEW VIDEO HEADS

from  
**£24.95 each plus V.A.T. & carriage**

Our selected range of NEW VIDEO HEADS have been manufactured to the Highest specification and are fully covered by our 1 Year Guarantee.

We supply HEADS of Most Types for  
AKAI - FERGUSON - JVC - SANYO - SONY  
- NAT. PANASONIC - Etc - Etc.

Please contact us for details of Our Full Range of Video Spares including Motors, Pulleys, Belts, Idlers, Etc.

Our Full List will be sent on request.

**ELECTROVISIA LIMITED**

P.O. Box 55  
Stratford-upon-Avon  
Warks. CV37 0UB  
0789-298510

## TELEVISIONS

Limited number of Colour and Mono Televisions are now available Mixed Models sizes and types available singly or in tens. They are catalogue returns and may be faulty or have marked cabinets, but the tube is warranted good. All are suitable for refurbishment or rental and show a substantial saving on price.

For Further Details:

## COLOURTRADE

221 Bridge Street West, Hockley, Birmingham B19 2YU.  
Tel: 021 359 7020

## CUSTOMER CAN'T PAY?



**DONT LOSE HIM FIT A TV METER**

COINAGE AVAILABLE: 10p - 50p - £1  
COMPLETELY VARIABLE TIMINGS

**Alberice METERS LIMITED**

MANUFACTURERS OF TV COIN OPERATED METERS

Contact: (0202) 674272  
87-89 Sterte Avenue, Poole, Dorset BH15 2AW  
Telex: 418253 PORTLX G.



# ENGINEERS

Looking for a brighter future?  
Join the fast moving and lucrative  
computer servicing industry.

Vacancies are now available on our

## MICROPROCESSOR SYSTEMS TECHNICIANS COURSE

A 16 week full time course designed for TV Engineers  
wishing to retrain in:

### MICROPROCESSOR TECHNOLOGY


The course concentrates on realistic hands on  
practical work.

Start dates: **JUNE 22nd 1987**  
**JULY 14th 1987**  
**OCTOBER 12th 1987**

Apply with full CV to:

**MILTON KEYNES SKILLCENTRE**  
Chesney Wold, Bleak Hall, Milton Keynes  
Or ring Bryan Hall on (0908) 670001  
for further details.

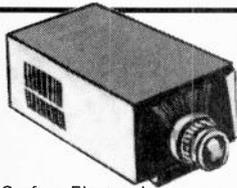NO TUITION FEES. A training allowance  
and lodging/travel allowance will be paid.  
(M.S.C. - J.T.S. funded course)



## CCTV CAMERAS FROM ONLY £69.50 EACH! PLUS CARRIAGE & VAT

Crofton Electronics are now able to offer C.C.T.V. cameras from as little as £69.50 + VAT & carriage. These cameras have been refurbished to a high standard. The output is 1volt p-p and will work with most video equipment. These cameras are powered from 240volt mains, and have a vidicon rack giving a focusing range from an inch or two to infinity. A standard 16mm lens is also supplied. The sensitivity is in the order of 10 lux which allows their use in the domestic environment. Pictures can be produced with only 2.5 lux but with a worse signal to noise ratio. Low light versions are available having sensitivities of 0.1 lux (half moonlight) at £350 + VAT and carriage. Many other lens are available from stock. A mounting bush is standard. Many other cameras are available from stock both reconditioned and new, ie brand new mini 12volt camera at only £80 plus VAT and carriage, lens extra. Many other items of C.C.T.V. equipment such as monitors (both new and refurbished) switchers, panning units, housings, time and date generators are available from stock. We also supply camera and monitor tubes, as well as scanning yokes for a wide range of equipment.

### SPECIAL SPECIAL SPECIAL SPECIAL

Currently on offer is a professional drive board and tube to make a superb 12" professional green panelled tube monitor at £23.50 inclusive. Would normally cost well over £200+. Buy 10 off and they will only cost you £180.00 inclusive. Be sure to ask us to quote for any of your camera/monitor requirements, we will never be beaten on price.

### HURRY HURRY HURRY

(Not many left. First come first served)

Brand New Time Date generators at a fraction of their original price. Only £132 inclusive. Normal price £477. These generators are mains driven and accept normal composite video in. They produce video out with time/date/day/month/year added to the signal in normal or reverse video. Adjustable positioning anywhere on the screen. Switchable character size also provided. A REAL MUST FOR SECURITY APPLICATIONS WHEN RECORDING.

We also have a host of used items such as cooling fans power supplies at give away prices, so why not ask for a list?

Send a 40p SAE for our complete range of catalogues.

**MOST MAJOR CREDIT CARDS ACCEPTED**

**CROFTON ELECTRONICS** ☎ 05448 557

'KINGSHILL', NEXTEND, LYONSHALL, HEREFORDSHIRE HR5 3HZ

# "BRITAIN'S NEWEST" SUPPLIERS

OF EX-RENTAL TVs  
and VIDEOS  
WE ARE BASED IN THE  
MIDLANDS

# "SPECIAL OPENING OFFERS"

ALL SETS ARE  
UNTESTED  
AND COMPLETE

COLOUR TVs  
from £6.00

VIDEOS from £25.00

MONOS from £2.00

DIRECT LOAD FROM  
SOURCE AT  
VERY KEEN PRICES.  
EXPORT ENQUIRIES  
WELCOMED

ALL PRICES ARE SUBJECT TO 15% VAT  
AND BASED ON QUANTITY

STRICTLY TRADE ONLY

**EURO A.M. LTD**  
**(0827) 61515**

# BRITAIN'S LARGEST SUPPLIERS

## OF EX-RENTAL TV AND VIDEO SPECIAL OFFER

BETA  
SANYO C5, C6, C7, C9  
FROM

# £20

VHS

HITACHI 5000      FERGUSON 3V22

# £60

Makes inc. PHILIPS, GEC,  
HITACHI, ITT, BUSH,  
PANASONIC, SONY, DECCA,  
FERGUSON, GRUNDIG etc.  
COLOUR TV from £5

CALL & SEE OUR SELECTION  
DELIVERY ARRANGED FOR  
BULK PURCHASES  
LOAD DIRECT FROM SOURCE  
AT VERY KEEN PRICES

## FRANK FORD

(TV TRADE DISPOSALS)


SCHOOL LANE

GUIDE

BLACKBURN, LANCS

TEL: 0254 64489

## UNIVERSAL NICAD CHARGER

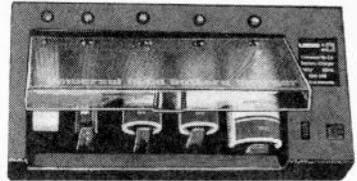

A brand new universal charger (charges any combination of PP3, AA, C & D CELLS), for only £5.95 plus £1 post and packing.

### ONLY £5.95

NEW AA/HP7 NICADS  
90p each when ordered with charger.

FERGUSON

9.6 volt standard rechargeable battery type VA282. Use with Videostar C camera/recorder, model no. 3V41, also suits JVC camcorder models JR1 and 2 £18 each + £1 p&p.

## E. CROYDON DISCOUNT ELECTRONICS

40 LOWER ADDISCOMBE ROAD,  
CROYDON, SURREY

☎ 01-688 2950

SHOP HOURS Mon-Sat 10-5.30  
(Closed Weds)

## ATTENTION DEALERS IN THIS AREA

SAVE  
TIME!  
SAVE  
MONEY!

SEMPLER SERVICE



YOUR

LOCAL

EX RENTAL WAREHOUSE

59 HALL ROAD, CLENCH WARTON, KINGS LYNN

0553 766766

## APOLLO LANCASHIRE

### NATIONWIDE MAIL ORDER

#### LOCAL DELIVERY - 2 YR GUARANTEE

A47 342/343X - 470 BC822/CTB22/BGB22/	£39
470-ESB22/EFB22/ERB22/FTB22	£53
A51-220X/192X	£39
A51-161X/162/163/168	£53
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£53
510-VLB22(E56) DTB22/001/RFB22/RGB22/SFB22	£53
A51-590 New	£56
A51-570X/590/001/210/241	£53
A56-120X/123/140/410	£39
560-DZB22(E56)/HB22/AKB22/TB22/AWB22	£55
560-ETB22/DTB22/CSB22/DMB22/DNB22	£53
A56-611X/615X	£53
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£53
30AX - A56-540X - A66-540X	£56

### PHONE FOR QUOTE

#### SONY TYPES £69

470DLB22/FWB/KHB/KTB  
KLB-520SB22/NB/RB/XB  
A49JHT00X-570DB22/EB/HB  
GB/JB-A53JBW01X/JCG00X  
JB00X-680CB22/DB/EB

#### 14" PORTABLES £59

3708UB-AXT3001-  
37-550/2/3/4-A37-570  
580/590

PLEASE PHONE BEFORE CALLING  
LOCAL DELIVERY FROM ACCRINGTON, LANCS.


Phone enquiries and letters to:

**Apollo, The Potters Wheel,**  
Mullion Cove, Mullion, Nr. Helston, TR12 7ET.  
0326 240781


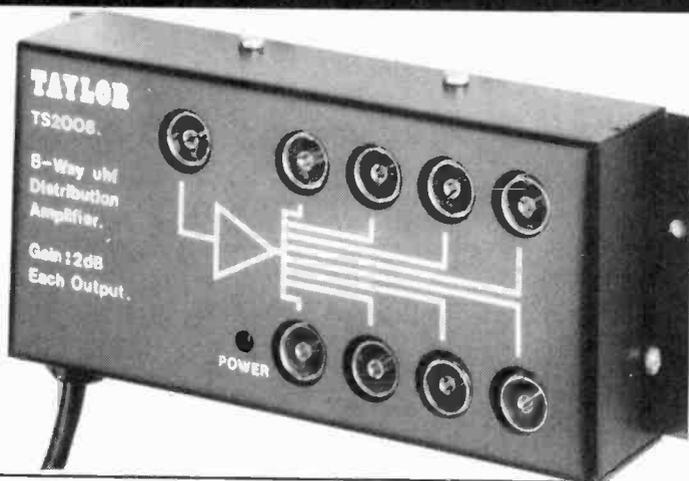
# TAYLOR

**T.S. 2008 8 WAY U.H.F. T.V.  
DISTRIBUTION AMPLIFIER**



## PRICE

1- 3 .....	£19.95 each
4-19 .....	£15.62 each
20-99 .....	£13.86 each
100 + .....	£13.48 each

Prices exc. V.A.T. & Carriage.

## SPECIFICATION

Frequency	- 470-860 MHz
Gain per Outlet	- 2dB minimum
Power Requirement	- 240V A.C. 4.8 Watts


**RUGGED SCREENED CASE**

**TAYLOR BROS (OLDHAM) LTD**  
**BISLEY STREET WORKS, LEE STREET,**  
**OLDHAM, ENGLAND.**  
**TELEPHONE: 061 652 3221 TELEX: 669911**
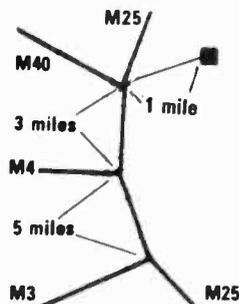
## DISPLAY ELECTRONICS LTD.

- ★ Do you use cathode ray tubes?
- ★ Can't find a replacement or shocked by the cost?
- ★ It may well be that a rebuilt tube will solve your problem.

Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



## WE ARE LOCATED IN UXBRIDGE

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40.

Why not telephone Terry Smith on Uxbridge (0895) 55800, to discuss your requirements?

## DISPLAY ELECTRONICS LTD.

UNIT 4, SWAN WHARF,  
 WATERLOO ROAD,  
 UXBRIDGE, MIDDLESEX.

## JUNCTION 11 TV TRADE DISPOSALS LTD

Unit 11, Prestwood Court, Leacroft Road,  
 Birchwood, Warrington. Phone: 0925 826387

## FULL RANGE OF THORN TV'S AND VHS VIDEOS

8800 N/R .....	£20	9900/9200 N/R	£40
8800 R .....	£25	9900/9200 R ....	£45
9000 N/R .....	£25	9600 .....	£40
9000 R .....	£30	TX9/10 .....	£65

Text **£70**

All prices subject to VAT. Discounts for quantity.

## CentreVision

TEL: 0222-44754  
 SLOPER ROAD, LECKWITH, CARDIFF  
 EXIT 33 OFF M4

## 3V22 VHS VCR - WORKING

ONE OFF **£85**      10 OFF **£75**  
 20 OFF **£68**      30+ **£65**

MANY ELECTRONIC VIDEOS IN STOCK  
 MANY TOP QUALITY REMOTE CONTROL WORKING TVs  
 PHONE FOR LATEST PRICES  
**PRICES SUBJECT TO VAT**

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30; SATURDAY 9.00 - 1.00

# THE WORLD OF . . . "TELEPANELS"

8-10 Rhoda Street, London E2 7EF. Tel: 01-729 0506.

P+P 1 PANEL £1.50. 2 PANELS OR MORE £3.00



WORKING  
PANELS  
GALORE!

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	6.00	5.50	8.00	16.00	15.00	9.00	6.00	9.00		4.50
THORN 3000/3500	3.00	6.75	5.00		9.00	9.00	6.00	7.00	6.00	2.75
GEC 2110	11.00		6.00		13.00	7.00	6.00	6.00	6.00	6.00
PYE 731			11.00		19.00	11.00	8.00	9.00		5.50
BUSH Z/718	8.50	7.50	15.00		25.00	4.00	6.00	15.00		
BUSH T/20	8.50	7.50	15.00		20.00	20.00	6.00	15.00		
PHILIPS G11	15.50 <small>WITH COMBINED SOUND MODULE</small>		13.00		20.00	20.00	6.00	15.50		
DECCA 80	13.00	POA	15.00		13.00	11.00		15.00		POA

POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!

## MODERN COLOUR TVs AND ELECTRONIC VHS VIDEOS

**Fantastic Bargain**  
10 Working Electronic  
VHS Videos £1000  
Modern Working Colour  
TVs. Large selection  
**Ring for Prices**

## TELETRADERS

Forde Road, Brunel Industrial Estate,  
Newton Abbot, Devon  
Telephone: (0626) 60154  
**THE NO. 1 WHOLESALE IN THE SOUTH**

## REPLACEMENT VIDEO HEADS AT COMPETITIVE PRICES from Luton only.

FOR AKAI, AMSTRAD, BAIRD, DECCA, FERGUSON, FISHER,  
GEC, HITACHI, ITT, JVC, MITSUBISHI, NEC, NORDMENDE,  
ORION, SABA, SAISHO, SANSUI, SHARP, SIEMENS, SONY,  
TATUNG, TELEFUNKEN, TENSUI, TOSHIBA, TRIUMPH  
TROPHY.

D.I.Y. TV TUBE POLISHING KIT

Kit Price £57 inc P&P and VAT. Available from Luton only.

### Quality, High Temperature Reprocessing

TUBE SIZE UP TO & INCLUDING	IN LINE & PIL i.e.	MININECK (22.5mm colour)	SONY TRINITRON
	AXT37-001 AXT51-001 560BYB22		330AB22
	A51-421X 510VAB22 560DYB22		400EFB22
	A51-426X 510VLB22 560DZB22	370HGB22	470DLB22
	A51-570X 510VSB22 560EGB22	370KRB22	470FWB22
	A51-580X A56-510X A66-510X	370KSB22	520KB22
	A51-590X A56-540X A66-540X	370KXB22	520NB22
	A51-701X A56-701X A67-701X	420FTB22	520SB22
	AXT56-001	470NUB22	570HB22
		510YXB22	680DB22
			680EB22
20"	£44	£50	£58
22"	£46	—	£64
26"	£48	—	£85

All tubes exchange glass required.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

## WELL VIEW

114-134 Midland Rd,  
Luton, Beds.

Open Mon-Fri 9am-6pm. Late opening Tuesday & Thursday till 8 pm.  
Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

Phone between 2-5pm.

West One Distributors Ltd., Chesham, Buckinghamshire.  
Tel. 0494 778197

Best price paid for A66-540X, old glass

## SPECIAL PURCHASE

R.G.B. Interface units for Spectrum and Sinclair computers normally an optional extra greatly enhances display and a massive saving on the normal price

**Mono T.V. Chassis  
Teletext Decoder  
Remote Control Board**

Both adaptable to other models!

Price £3.99 each, or any 3 for £10.00 inc. P&P

For Further Details:

**COLOURTRADE**  
221 Bridge Street West,  
Hockley, Birmingham B19 2YU.  
Tel: 021 359 5970

## N.G.T. COLOUR TUBES

First Independent Rebuilder with  
B.S.I. CERTIFICATION

**DELTA - IN-LINE - PIL - BONDED YOKE**  
including  
AXT Series, DZB series 20AX - 30AX  
A56 610/67 610 series, A51 570/580/590X  
A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

**N.G.T. ELECTRONICS LTD.,**  
120 SELHURST ROAD, LONDON SE25  
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

**SETS & COMPONENTS**

Thorn 3000/3500  
Thorn 9000  
**UNIVERSAL**  
1 year guarantee

**TRIPLERS**  
**£5.95** inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

**WING ELECTRONICS**

15 Waylands, off Tudor Rd., Hayes End, Middlesex

# TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £7.20 per single column centimetre (minimum 2.5 cms). Classified advertisements 45p per word (minimum 12 words), box number 75p extra.

## INDEPENDENT TELEVISION & VIDEO COMPANY

### OFFERS **TOP QUALITY TELEVISIONS & VIDEO'S** **AT LOW-LOW PRICES**

**WORKING, (SWITCH ON TO PROFITS WITH US) TO RETAIL AND TO INCREASE YOUR PROFITS.**

E.G. V.H.S. VIDEO WORKING FROM..... **£60.00**

E.G. TELEVISION – THORN TX9, TX10, PYE PHILIPS KT3, KT30 – SONY 2020-2204UB –NAT. PAN. – TC.2205 – HITACHI – AND MANY MANY MORE TO CHOOSE FROM..... **£55.00**

PHILIPS G11. PYE G11. TANBERG. ITT ETC..... **FROM £40.00**

THORN 9000 ETC **£25.00** PLUS MANY MORE TESTED, WORKING PORTABLE TELEVISIONS & ELECTRONIC VIDEO'S ON SALE


F.O.B. PRICE

**WE ARE EXPERIENCED IN EXPORT MARKET**  
**REFURBISH TELEVISIONS – VIDEOS – ELECTRICAL GOODS**  
**& OTHER COMMODITIES. ENQUIRIES WELCOME**  
**TELEX: 378414 BL BIRD-G**      **FAX: 602 588505**

C.I.F. PRICE

OR UNTESTED TELEVISIONS & VIDEOS. DIFFERENT MODEL OFF PILE TO CHOOSE FROM – MIXED LOADS WELCOME DIRECT FROM SOURCE AT **ROCK BOTTOM PRICES**. TRY US, GUARANTEE NO DISAPPOINTMENT. ALL PRICES SUBJECT TO 15% VAT.

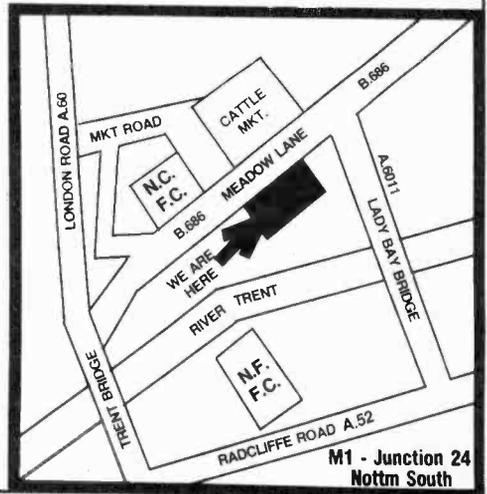**UNIT 3-8, MEADOW TRADING ESTATE,**  
**MEADOW LANE, Opp. CATTLE MARKET**  
**in National Tyre Yard, NOTTINGHAM NG2 3HQ**  
**Tel: 0602 864627**



M1 - Junction 24  
Nottm South

### NORTHAMPTON TRADE TV'S

**CLEAN WORKING**  
**COLOUR TV'S**  
FROM **£20.00** (plus VAT)  
**OFF THE PILE SETS**  
FROM **£12.00** (plus VAT)  
in lots of 10

**Telephone (0604) 37425**

### Trent Tubes

*For Professionally Rebuilt Tubes*  
35A RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM  
NG2 5FF TEL: (0602) 813329

TWO year guarantee extendable to FOUR years

A56-A66-510 **£44.00**      A56-A66-540 **£49.00**

560DZB ● AXT types ● A51-570/580/590 370LDB ●  
370NJB etc available. All one price **£48.00**

560DZB ● AXT AXT TYPES ● A51-570/580  
One price **£48.00**

**FST ● 45AX ● SONYs ● AVAILABLE**  
Please phone for Prices.

**1000's** more available.

**VDU & MONITOR types a speciality.**

**INSURED DELIVERY SERVICE AVAILABLE**

**ALL PRICES EX WORKS + VAT & EXCHANGE**

TV's HITACHI, MITSUBISHI, Panasonic, Sony, Toshiba, JVC, Sharp, fully refurbished. PEARSON TELEVISION, 0484 863489. Delivery arranged.

## DHOUPER VISION

Ex-Rental wholesale in T.V.s & Videos, unbeatable prices, good quality sets at trade prices

**(Sets from £7.00)**

(Working or non-working sets)

674 Coventry Road, Small Heath, Birmingham B10 0TJ

Tel: 021-772-2743

Lorries direct from rental source

### TURN YOUR SURPLUS

ICS transistors etc. into cash, immediate settlement. We also welcome the opportunity to quote for complete factory clearance.

Contact:

**COLES-HARDING & CO**  
103 South Brink, Wisbech, Cambs.

Tel. 0945 584188

★ ESTABLISHED 15 YEARS ★

### B.G. COMPONENTS

T.V. & VIDEO SPARES

We supply spares for most makes including Sony and Fidelity all at competitive prices.

We also stock a comprehensive range of rebuilt C.R.T.'s including Hitachi and Sony.

Open Monday-Saturday

Hill Street, Oldham OL4 2AG

061-624 1753

# SERVICE PAGES

Prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, Ltd. crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 204B (H.H.), IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

GRUNDIG, TELEFUNKEN, PHILIPS, SONY, SANYO, MITSUBISHI, FIDELITY, ROBERTS DYNATRON, BUSH/MURPHY

## T.V. BREAKERS

Ex-equipment or/and new spares for most makes/models, parts supplied on pro-forma basis only. Send order with S.A.E. to:

T.V. Breakers,

16 North Street, Oscornby, Lincs NG34 0DR

**IF IT IS AVAILABLE  
WE CAN SUPPLY IT**

NO CALLERS

## GIANT SCREEN TV'S VIDEO PROJECTORS

All leading makes available. Large quantities of some lines. New and second hand equipment bought and sold.

J. H. Roche & Co. Ltd.,

36 Station Road, Wyld Green,  
Sutton Coldfield, West Midlands B73 5JY.

Tel: 021 354 2393 (24 hrs).

## HALTON TV TRADE DISPOSAL

The Wholesaler you won't find competing with you on the High St.

TV and Videos

GEC, Philips, Decca, Doric, Thorn

★ Remember, we have NO retail outlet ★

St Michaels Industrial Estate, Widnes

Tel. 051 423 1577

## 2000 TV TUNERS

UHF PUSH BUTTON TV TUNERS IN SLIM-LINE CABINET WITH COMPOSITE VIDEO OUTPUT. CHEAP TO CLEAR. MINIMUM ORDER 10. CONTACT:

SCREENS MICRO COMPUTERS & ELECTRONICS LTD.  
MAIN AVENUE, MOOR PARK, NORTHWOOD, MIDD.

TEL: 09274 20664

TELEX: 929224 SCREEN G

## VIDEO SPARES

Stock items despatched by return Access & Visa welcome

### VIDEO HEADS

Universal VHS heads most models	£29.50
Hitachi, Ferguson, Panasonic etc. (most models) (genuine)	£35.00
Sharp VC9300, VC9500 etc. (equivalent)	£39.50
Sony SLC5, C6, C7 (genuine)	£42.00
Sony SLC5, C6, C7 (equivalent)	£39.50
Sony SLF1, C20, etc. (equivalent)	£35.00
Toshiba V9600, V31, V33 (equivalent)	£39.60

### Reprocessed Heads

(Send old head with order. The drum should be free of scratches and marks)

Most VHS models	£29.00
Sharp (most models)	£37.50
Most VHS 4 head types	£47.50

### VIDEO MOTORS

#### Drum Motors

Ferguson/JVC (mechanical models)	£29.00
Sharp VC9300, VC9500, VC9100 etc.	£26.60

#### Reel Motors

Sanyo VTC5000, 5150, 5300, 5400, 6500	£9.90
Sharp VTC9300 etc. (most models)	£18.30

#### Capstan Motors

Ferguson/JVC (mechanical models)	£29.00
Ferguson 3V35	£29.95
Hitachi VT11, VT33, VT14, VT17	£25.00
Hitachi VT8000, VT8300, VT8500, VT9300	£35.00
Sony SLC5 SLC7 (BHF 1100d)	£29.95
Sharp VC9300, VC9500 etc.	£27.60

### BELT KITS

Most Models	£3.50
Sanyo VTC5000	£1.00
Sanyo VTC9300	£3.75
Ferguson 3V31, 3V35, 3V36	£1.95
Fisher VBS 7000	£4.50

### PINCH ROLLERS

Most Models	£4.95
Ferguson 3V31	£7.90

### IDLER ASSEMBLIES

Sharp (most models)	£2.95
Hitachi VT11, VT14, VT17, VT19, VT33 etc.	£4.50
Hitachi VT9300, VT9500, VT8000	£6.50
Ferguson/JVC Take up clutch (mechanical model)	£6.50
Sanyo VTC5150, VTC5000, VTC6500 complete reel drive pulley unit	£8.90
Sony SLC5, SLC7 rewind kit	£5.95
Ferguson 3V29/30 Take up idler	£2.20
Ferguson 3V29/30 Take up clutch	£3.50
Ferguson 3V29/30 Reel idler	£3.95
Ferguson 3V35 Reel idler	£3.95
Ferguson 3V35/36/38/39 Take up clutch	£3.50

### IDLER TYRES

(Please state size in mm and make a model of video)

Panasonic NV370 etc. (VXP0521)	£3.95
--------------------------------	-------

### MISCELLANEOUS

IC STR6020 Modification kit for Hitachi CPT1471/1473 (intermittent power supply fault)	£5.95
BU208A	£1.00
Exchange Modulator, Aerial Booster	£14.95
Universal Video Copying kit	£4.45
Universal Video Copying kit (scart)	£5.85
Universal Video Cassette Lamp	£0.50

Please add 75p per order for p&p and then add 15% VAT



## A.Z. ELECTRICS

174 Kettering Road, Northampton NN1 4BE  
Telephone (0604) 24380



## TUBES

NEW OR REGUNS

### ONE YEAR GUARANTEE

14" 370 - KR8 - LHB - HGB - HFB - HUB - BRB - EGB - EFB - MEB - GUB - AXT 37 - 001 - AXM 37 - 001 - 37 - 565 - 570 - 552 - 554 - 590 - A34 EAC 90X.  
Broken Tube We Can Help.

16" 420 EDB - EFB - CZB, 42 - 001, 42 - 556.  
20" 51 - 161, 51 - 500 - 554 - 570 - 575 - 580 - 590 - 51 - 001 AXT - 510 JKB - VB - UFB - RJB - UDB - HWB - 510 ABUB from £45.

22" 56 - 500 £45, 56 - 540 - 610 - 611 - 615 - 700 - 712 - 560 EGB - DAB - DMB - BYB - EGB - TB - GAB - AXB - ETB - HB - DYB - ATB - BMB - HW 56 - 001 AXT.

26" 66 - 500 - 510 - 540 - 611 - 615 £55.  
HITACHI 510 HWB - VLB - VSB - 560 DZB - HWB - 490 DKB22 FROM £34.

SONY £65 Cash & Carry only.  
DELTA £29.00 Reguns.

£14.50 Slightly used. 6 month guarantee.  
A56-120 A56-140 A51-110 A49-191 A47-342 or 343  
A44-270-1 A66-120 A66-140 (410) A67-120  
All prices are inclusive

### U-VIEW

29, Warmworth Road, Doncaster,  
Yorkshire DN4 0RP. Tel: 0302 855017.  
Callers ring first, open every day including Sunday  
1/2 a mile from A1

## WE BUY SURPLUS

ICs, Transistors, Tuners & Transformers, etc for cash settlement.  
Factory redundant stocks purchased.

Contact

D&S SPARES,  
183 WATLING STREET, RADLETT  
Phone: (09276) 4252



## PROMOTE & PROTECT with

## PERSONALISED PROTECTIVE COVERS

Eliminates scratching and damage to screens and cabinets, etc. "a good investment in my opinion" Eugene Trundle, Television March 87

For Televisions, Video Recorders, Audio Visual Equipment, White Goods, etc.

### PERSONALISED T.V. TRANSIT COVERS

These are tea-cosy style and come in three sizes:  
Standard (to fit up to 22" comfortably - they will even fit some of the 26" models)

Extra Large (for the "brutes")

Portable (to fit up to 16")

### PERSONALISED VCR PROTECTIVE COVERS

Designed to give all-round protection, they fit all modern models (but may not fit some of the older, larger models). The recorders fit snugly inside the covers, which then fasten with Velcro fasteners, thus avoiding dangling mains flexes during transit, and allowing discreet removal to and fro.

### PERSONALISED JUMBO COVERS

A universal cover for fridges, freezers, washing machines, etc.

Tea-cosy style (36" x 24" x 24")

### PERSONALISED TIDY WRAP

Keep the floor of your vehicle free from clutter with this handy little wrap with Velcro fasteners (18" x 12")

### PERSONALISED SPECIAL DISCOUNT PACKAGE (A)

(2 x Std TV, 2 x VCR and 1 x X/Large TV)

### PERSONALISED SPECIAL DISCOUNT PACKAGE (B)

(4 x Std TV, 4 x VCR and 2 x X/Large TV)

COMPANY LOGOS - These look absolutely super - Please phone for details.

OTHER EQUIPMENT - We can make protective covers for any equipment to specification - Please ring!

ALL COVERS ARE MANUFACTURED IN HIGH QUALITY 135g. POLYESTER-FILLED NYLON QUILTING FOR MAXIMUM PROTECTION AND DURABILITY.

**AND DON'T FORGET! - ALL COVERS SUPPLIED WILL BE CUSTOMISED WITH YOUR TRADING OR DEPARTMENT NAME IN A VIVID EYE-CATCHING PRINT AT NO EXTRA COST!!**

DON'T DELAY - ORDER TODAY - YOU'LL WONDER WHAT YOU DID WITHOUT THEM!!

If you have any queries, please ring for friendly service.

HOW TO ORDER: 1. Indicate your trading name with order  
2. Add Postage and Packing as follows:  
Orders up to £50 - add £3. Orders up to £100 - add £5.  
Orders over £100 - free P&P.

3. Add 15% V.A.T.  
Please make cheques payable to N.F.P.C. and forward to:  
N.F.P.C., 'Bywell House', 3 Fenham Hall Drive,  
Newcastle upon Tyne NE4 9UT.

TEL: (091) 272 4646

Please allow 28 days for delivery

Mail Order Terms: Cheque with order.

Monthly account orders accepted from Education Depts., Local Authorities, Hospitals, Public Companies.



# BESCO LTD T/A NORTH WEST ELECTRONICS NEW STOCKS ARRIVING DAILY

## SPRING BARGAINS

DISCOUNT FOR QUANTITY  
WORKING TVS AND VIDEOS  
ON SHOW

## H.P. REPOS AND EX. RENTALS COLOUR TV'S AND VIDEOS

### Refurbished TV's

BUSH T20/T26	£45
G11	£50
PYE KT3	£65
Ferguson TX	£70

### WORKING EX-EQUIPMENT PANELS

IF	Con- verger	De- coder	Line scan	Power	Frame
T20/22 X	5	14	18	17	14
T26 X	5	16	20	17	X
718	7.50	5	14	20	3 14.00
Philips					
G11	14.50	5	12	20	20 11.50

ALL PRICES INCLUSIVE OF  
POSTAGE BUT PLUS VAT  
CHEQUE WITH ORDER PLEASE

### Annual Clearance Rock Bottom Prices

PYE G11 EXC		PYE KT3	£50
CAB.	£40	GEC 2213	£20
BUSH T20/26 CH	£35	THORN 3000	£7
HITACHI 191	£15	GRUNDIG G415/ 4206	£25
FERGUSON TX	£55		

GEC 2010	£15	Best Stock in Country over 2000 in stock (90% of our TV's Switch on)
PYE 222	£15	
PHILIPS 550	£10	Special Price Quoted For Bulk Purchases From Source. DISCOUNT FOR QUANTITY
BUSH 718	£15	
BUSH 2 CHIP	£8	
GRUNDIG 5010	£10	

### Video

WORKING  
SHARPS 7300, 8300,  
9300  
HITACHI, VT11,  
FERGUSON 3V29

Due to our excess video  
stock and limited time  
we have electronic VHS  
videos with  
slight fault £60

SPECIAL  
PRICE FOR  
LARGE ORDER


SANYO, SONY,  
BETA

LAUREL STREET, LEEDS ROAD,  
BRADFORD, W. YORKSHIRE BD3 9TP.

5 MINS FROM MOTORWAY

100's PX  
HOOVER JUNIOR  
VACS  
All models in stock

Tel (0274)  
660995

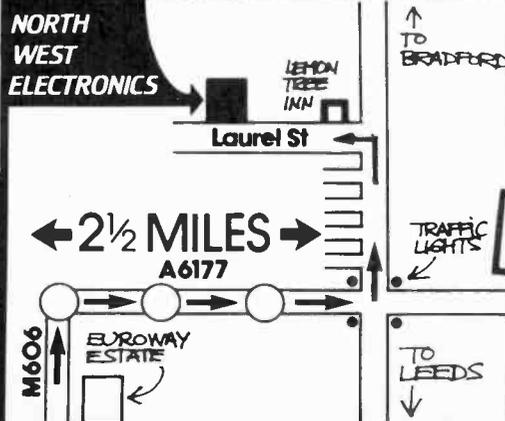

P.X. WASHERS  
COOKERS  
ETC

CASH ONLY

OPEN 6 DAYS  
SAT 9-5.30

# 'BOBS'

TELEVISION WAREHOUSE  
A NEW CONCEPT IN EX-RENTAL T.V. & VIDEO

## WORKING TV & VIDEO

ENGINEERED TO THE HIGHEST SPECIFICATION READY FOR YOUR SHOWROOM

## NON WORKING

GUARANTEED COMPLETE AND UNCANNIBALISED GOOD CABINETS AT LOW LOW PRICES

ELECTRONIC, REMOTE, FRONT LOADER VIDEOS

**NAT PAN, JVC, HITACHI, TOSHIBA, SANYO, SONY, ETC., ETC.**

K30, KT3, G11, TEXT, REMOTE AND BASICS


**ITT, GEC, BUSH, JAPS., DECCA, ETC.**

PHONE BOB BEAN ON:

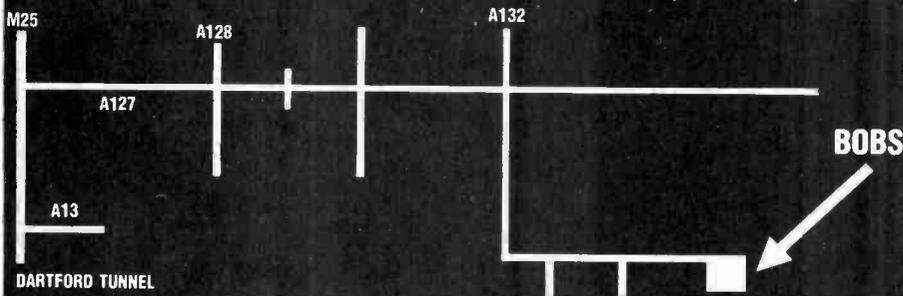**0268 728966**

AND DISCUSS YOUR REQUIREMENTS

BOBS T.V. WAREHOUSE, 1 Swinbourne Ct, Burnt Mills, Basildon, Essex



# 'BOBS'

TELEVISION WAREHOUSE

**NEW  
PHILIPS  
NEW  
PHILIPS  
NEW  
PHILIPS**

**NEW PHILIPS EX  
CATALOGUE RETURNS**

**LARGE STOCK NOW  
HELD. ALL SIZES AND  
CURRENT MODELS**

**ALL WORKING AND  
SHOWROOM READY**

**GUARANTEED**

**PHONE**

**BOB BEAN 0268 728966  
TO RESERVE YOUR SUPPLY NOW**

## DEALERS IN THE SOUTH WEST PLEASE NOTE

We are a new Trade Warehouse in the Newton Abbot area.

Regular direct supplies of clean, working VHS videos and TVs available at fair prices.

**Discounts on Quantity**

**Phone or Call**

3V22 WORKING £60 IN TENS	<b>ACORN TV WAREHOUSE IPPLEPEN (0803) 813281</b>	3V23 WITH HANDSETS WORKING £115 IN TENS
You'll find us opposite Two Mile Oak Inn, on Totnes/Newton Abbot Road		

## BOURNEMOUTH

WORKING PRICES — 500+ IN STOCK

10 DECCA £250, 10 9600 R/C £450

10 G11 £300, 10 TX 9/10 £650

10 9000 R/C £350, 10 TEXT £1000

ALL + VAT

**LARGE STOCKS OF BETA + VHS — PHONE FOR PRICES**

**TRADE ONLY — CASH ONLY**

WE HAVE NO RETAIL OUTLET

Warehouse Open Mon-Fri 9-1, 2-5

**HILLIER'S, UNIT 2A,  
11-15 FRANCIS AVENUE,  
WALLISDOWN. TEL: 0202 581932**

## DEALERS

We have vast quantities of working Thorn 9000 CTVs with excellent tubes from £30. Also working VHS videos from £80

**TEL: 01-729 3356**

PLEASE  
MENTION  
TELEVISION  
WHEN  
REPLYING  
TO  
ADVERTISEMENTS

**T.V. SPARES, PANELS  
AND MANUALS  
PHILIPS · GRUNDIG**

**TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.**

# TVs GREAT BUYS

G11s from £20

REMOTES I/R AND SONIC from £35

TEXT MANY MAKES from £55

**200+** FULLY WORKING SETS AVAILABLE. ALL SEEN IN OUR COMFORTABLE TRADE ONLY SHOWROOM. EXCELLENT CABINETS, READY FOR SALE OR RENT, BASIC TO TEXT. NO JUNK.

**VHS** VIDEOS ALL ELECTRONIC, GOOD CLEAN MACHINES NOT KICKED ABOUT, BASIC TO FULL I/R WITH DOLBY. MAKES BY PANASONIC, HITACHI, JVC, MITSUBISHI, FISHER ETC. AND OTHERS AS THEY ARRIVE.


**2000** SYSTEM VIDEOS FROM ONLY £20 LOAD ON STOCK, GOOD CLEAN MACHINES AT BARGAIN PRICES, ALL HAND PICKED. 2020-2021-2022. PHILIPS, GRUNDIG 4x4 and 2x4 SUPER AS AVAILABLE.

**TVs** ALL OF THE FOLLOWING MAKES AND TYPES IN STOCK ON PREPARATION OF THIS ADVERT: **DECCA** 80-88 100. **FERGUSON** TX 9 + 10, 9000. **GEC** 2642-2242, 2642 TEXT. **GRUNDIG** 7200-7400-6012-6610-6245-2200. **SONY** 1810-2040-2022. **ITT** CVC 8-9-20-23-25-30-32. **TELEFUNKEN** 8256. **MITSUBISHI** CT200-2606. **TANDBERG**. **KORTING**. **PANASONIC**. GOOD CLEAN CABINETS ON MOST SETS. WE LOOK AFTER THEM FOR YOU.

**GENERAL FACTORS** 0302-  
UNION STREET, DONCASTER  
SOUTH YORKS 349583

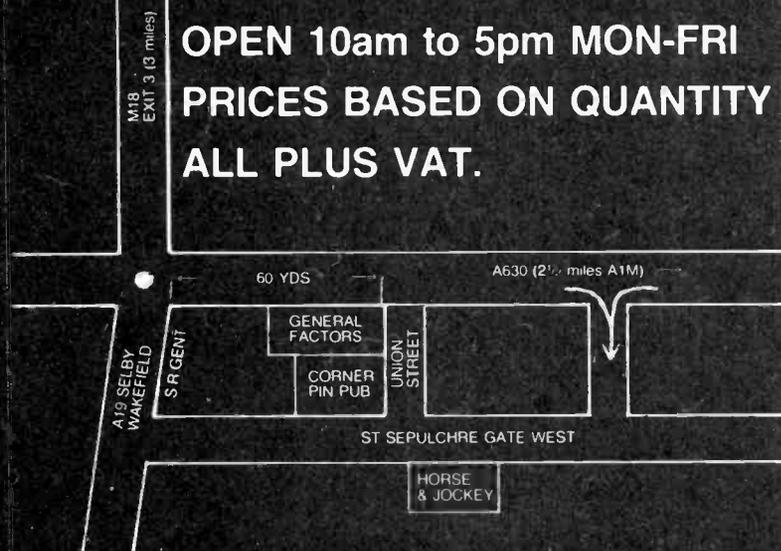**CASH ONLY**

**OPEN 10am to 5pm MON-FRI**  
**PRICES BASED ON QUANTITY**  
**ALL PLUS VAT.**



## TV SALES & SERVICE CENTRE

We are component part stockists for:

**SANYO, SONY, SHARP,  
NATIONAL PANASONIC,  
HITACHI, TOSHIBA &  
FERGUSON.**

Ask for details about our  
**TV, VIDEO & AUDIO  
TECHNICAL PROBLEMS  
ADVICE BUREAU**

Phone (09276) 4252  
185 Watling Street, Radlett,  
Herts WD7 7NQ.

## WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS,  
PYE, RANK, GEC, SHARP, SONY,  
HITACHI, DECCA + ITT.

**FIDELITY SPARES MAIN DISTRIBUTOR.**

Did you know we also stock

FUSES	I.Cs
TUBES	TOOLS
AERIALS	VIDEO LEADS
RESISTORS	AUDIO LEADS
CAPACITORS	SEMICONDUCTORS
VALVES	SERVICE MANUALS
HANDSETS	TEST EQUIPMENT
VIDEO HEADS	TV/VIDEO TROLLEYS
	TELEPHONE ACCESSORIES
	AND MUCH MORE

Counter open Monday-Friday 9am-4.45pm

**TRADE ONLY**

**EMPRESS STREET WORKS,  
EMPRESS STREET,  
MANCHESTER M16 9EN.**

Tel: 061-872 5438; 061-848 0060.

## COURSES

### TV & Radio Aerial Rigging? Intensive "Foundation" Training Courses for the Technician Engineer

Start off on the right course... be fully informed! One week intensive instructional courses, run by an ex-broadcasting engineer. Residential, marvellous accommodation with **excellent food**. Theoretical and practical "Hands on" instruction. Training covers all aspects of television and radio reception. Become an aerial erector who can provide the best, because he's learnt the best way!

Courses held throughout the year, amidst the beautiful Highland scenery. Non-participating partners welcome at minimum extra cost. Transport from Inverness provided if necessary.

Further details by SAE to:  
**R.B. Mannion** (Assoc. Member of  
Confederation of Aerial Industries),  
Badcaul House, Badcaul,  
Dundonnell, By Garve,  
Ross-Shire IV23 2QY.  
Tel: 085-483-213.



# Sabaco

FOR A GREAT DEAL

FOR A GREAT DEAL

TOP QUALITY TV & VIDEO AT ROCKBOTTOM PRICES

LARGEST SELECTION OF  
8800, 9000, 9200, 9600,  
TX9, TX10, STEREO TEXT  
COLOUR PORTABLES

4000 NW  
THIS MONTH'S  
OFFER  
10s PRICE  
**£5 EACH**

VHS VIDEOS  
GOOD WORKING ORDER  
3V22, 3V23, 3V29  
PORTABLE VIDEOS etc. etc.

ALL SETS & VIDEOS OFF THE PILE


PYE KT30, G11, T20, T26  
JAPANESE & MANY  
MANY MORE

9600 NW  
THIS MONTH'S  
OFFER  
26"-10s PRICE  
ONLY  
**£15 EACH**

OPEN MON-SAT 9.00-5.30  
SUNDAY BY APPOINTMENT  
CASH ONLY - ALL GOODS  
SUBJECT TO VAT & AVAILABILITY  
Send SAE for full price list  
& Special Offers

EXPORT  
ENQUIRIES  
WELCOME

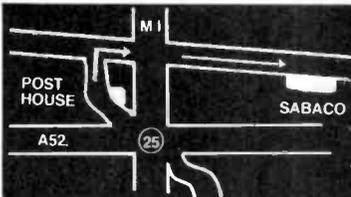PHONE NOW FOR UP TO THE MINUTE COMPUTERISED PRICE & DELIVERY DAYS  
MAKE YOUR DAY — RING NOW



ENGLAND (HEAD OFFICE)  
SABA HOUSE  
46a DERBY ROAD  
SANDIACRE  
NOTTINGHAM 0602 397555

SCOTLAND  
75 ROBERTSON STREET  
GLASGOW  
041-221-2146



**SERVICE and SELL WITH CONFIDENCE**

## SHARP & GRUNDIG

**PARTS ARE FAST FROM WILLOW VALE**

*The manufacturers who care about Service*

**30,000 + different stock parts**

**24 hour despatch**

**Over 95% 'first pick' supply ratio from stock**

Willow Vale's comprehensive parts listings for Sharp and Grundig products make ordering and identification easy.

Contact the Sole UK Parts Distributors and find out what SERVICE is really about.

**Willow Vale Electronics Ltd**

11, Arkwright Road, Reading, Berks. RG2 0LU.

Telephones: 0734-876444 (24 hours) 8 lines  
Telex: 848953 Willow G  
Faxline: 0734-867188

also at:  
Enterprise Park, Reliance Street,  
Newton Heath, Manchester 10  
Telephones: 061-682-1415  
Faxline: 061-682-9031

Please send me your comprehensive Sharp, Grundig spares catalogues together with wallcharts of the other spares you stock:  
(TRADE ONLY) I enclose 50p stamp for postage.

Dealer/Engineer: \_\_\_\_\_

Address: \_\_\_\_\_

2

Postcode: \_\_\_\_\_

**PHILIPS COLOUR TVs  
AT NEAR TRADE PRICES**

A large purchase of surplus warehouse returns enables us to offer the public some magnificent bargains. Choose from a wide range of features including 14" to 26" screens, remote control, teletext, text printer, flatter squarer screens, etc. Stands and video bars supplied with appropriate models. Every set tested before sale with 3 month guarantee.

**VISION PROMOTIONS**

Branches at 3A Commerce Estate,  
Kingston Road, Leatherhead  
Hours 9am to 5pm.

Phone 370066 for stock availability  
321 Old London Road, Hastings  
Hours noon to 8pm, Sats 9am to 5pm, closed Mondays  
Phone 444415

240 ISOLATING TRANSFORMERS. 250 watt continuous, 500 intermittent. £8.00. 2 for £15.00. SHANE HILL ELECTRONICS, 5 St Josephs, Ballycruttle, Downpatrick BT30 7BN.

**3V22/16's** FULLY ENGINEERED WITH REMOTES LEADS & INSTRUCTIONS. VERY GOOD CONDITION, FOR IMMEDIATE RENTAL. **£75.00**

NEW LIFE A56-120 CRT's 2 Year Guarantee.

TO CLEAR AT **£25.00** Ditto A44-27IX **£15.00**

SELF CONTAINED TV TUNER UNIT O/P's - Sound 3W, Vision 1V, ideal for Teletext Converter or Sound Source.

BRAND NEW **£15.00**

ALL PRICES PLUS VAT & P/P


**UNDERWOOD ELECTRONICS  
0902 756140**

FOR SALE

# EURO-SAT

SUPPLIERS TO H.M. FORCES AND M.O.D.  
MANUFACTURERS OF FIBREGLASS DISH ANTENNAS  
ANNOUNCING: TWO NEW DISH ANTENNAS TO OUR RANGE

1-2M OFFSET INC. POLAR MOUNT	1-0M DIA 1-2M DIA 1-6M DIA 1-8M (PETAL) 2-0M DIA 2-3M (PETAL) 3-0M DIA	£58 £78 £88 £157 £180 £248 £737	1-6M PRIME FOCUS INC. POLAR MOUNT
	1-2M OFF SET POLAR MOUNT FEED SUPPORT ASSEMBLY	£78 £102 £21	

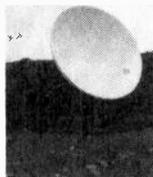

£178

EURO-SAT, 107 CROSS ST., SALE, CHESHIRE, ENGLAND  
TEL: 061-437 2631 = 061-881 4249

£188

PLEASE NOTE: WE ARE DISH  
MANUFACTURERS ONLY AND DO NOT  
SUPPLY SYSTEMS. PLEASE ENCLOSE S.A.E.

MISCELLANEOUS

## PICTURE TUBE REPAIR EQUIPMENT BMR 90

Versatile and reliable. Although many things have become cheaper, picture tubes are still expensive. So utilize tubes fully by using our new generation machine.



Regenerates picture tubes even better - Also IN-LINE - Removes short-circuits, even between cathode and filament - Measures beam current, emission current, life expectancy, etc.

can pay for itself in 4 weeks, if you are not using BMR 90 - you are making less profit than you could.

Sole Agents BLENDOWN LIMITED, 34 Glan-y-Mor Road, Penrhyn Bay, Llandudno, Gwynedd, Wales. Tel. (0492) 49246

GOULD OSCILLOSCOPES OS260 15 mhz dual beam £110. OS3000 40 mhz dual trace dual timebase £195. (02774 54096.

RETAILERS SURPLUS TUBES 14 x Delta 20"-26", offers. 0229 23187.

LARGE MURPHY, 30 year old console television with doors, offers. Diss (0379) 51345.

### BOOKS AND PUBLICATIONS

MACDONALDS RADIO & TV SERVICING BOOKS, NEW 74-75, 75-76, 76-77, 77-78, 79-80, 80-81, 82-83, 83-84, 84-85, 85-86, 78-79 and 81-82 OUT OF PRINT

Macdonalds Price	85-86	£24.55
OUR PRICE	NOW AVAILABLE	£23.00
Two or more		£22.00 each
Full set of 10		£199.00

Prices include delivery

U-VIEW, 29 Warmsworth Road, Doncaster, Yorkshire DN4 0RP. Tel. 0302-855017. Callers ring first

## THE DOMESTIC VIDEO RECORDER SERVICING BOOK

THE ENGINEERS BIBLE

WITH CHAPTERS ON HI FI, DIGITAL SERVICES, LUMINANCE AND CHROMINANCE SIGNAL CIRCUITS, FAULT GUIDES AND CONNECTION DATA.

A MUST FOR ALL VIDEO REPAIRERS AND STUDENTS. THE COMPLETE REFERENCE TO VIDEO RECORDER CIRCUITS

ORDER YOUR COPY NOW

FOR ONLY **£16.95** inc. P&P

OTHER TITLES AVAILABLE

SEND S.A.E. FOR LIST DIRECT FROM: GROVE FARM, LONG LANE, BARNBY IN THE WILLOWS, NEWARK, NOTTS.

CHEQUES AND PO'S PAYABLE TO D. BEECHING.

### VIDEO

## ELECTRONIC VIDEOS/TV's CLEAN MODERN WORKING

VID's/JVC/Hitachi/Panasonic etc. TV's/Sony/Philips/Panasonic etc.

Long term relationship required with a few reliable dealers able to take 5's - 20's of TV's or Videos or mix on a regular basis.

Based in the North West

Prices reasonable and stable  
Box 234

WHY NOT LET TELEVISION SELL YOUR PRODUCT FOR YOU  
**RING NOW ON 01-261-5942**

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc s/sheet - or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

PHILIPS 1502 Video £50. 100,1500/1700 tapes £100. o.n.o. 0782 623464 (daytime).

### SERVICE SHEETS

## TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European, and Japanese TV Sheets in stock

Colour £3.00, Mono £2.00 (POST FREE)

NEW - MACDONALDS RADIO + TV SERVICING BOOKS £22 EACH

1985-86, 84-85, 83-84, 82-83, 80-81, 79-80, 77-78, 76-77, 75-76, 74-75  
Two or more £21 each Full set of 10 £195

NEWNES BOOKS - Colour television servicing by Gordon J. King .....	£12.95
Television and video engineers pocket book by Eugene Trundle .....	£9.95
Domestic video cassette recorders (servicing guide) by Steve Beeching .....	£15.95
Servicing monochrome portable television by George Wilding .....	£14.95
Beginners guide to colour television by Gordon J. King .....	£4.95
Communications satellites (the technology of space communications) .....	£12.95

\*Send stamped addressed envelope for free lists of books and sheets.  
\*No extra charge for postage or VAT on sheets and books.

**SANDHURST TV SERVICES (Mail Order)**  
57 High Street, Sandhurst, Camberley, Surrey GU17 8HB.

## TECHNICAL INFO SERVICES (T) - 76 Church St., Larkhall, Lanarkshire ML9 1HE.

World's Sole Publishers of Comprehensive TV/Video Repair Manuals & Largest Known Stockists of Service Manuals and Service Sheets for all kinds of equipment both British and Foreign from 1935 to latest issues.

MAIN STOCKIST OF ALL HEINEMANN-NEWNES TECHNICAL BOOKS  
DELIVERY BY RETURN FULL LIST ON REQUEST

Big Catalogues of thousands of Service Sheets & Manuals + Chassis Guide + £4 Vouchers - saves time and expense £3.

Any published single service sheet for £2.50 + Isae except ctv/mus-c/combis from £3.50 + Isae. A selection from our stocks of thousands of Service Manuals ready for despatch by return post. Any Sony: Hitachi ctv from £9.50. Thom 3000/3500 £9.50. Thom 8000/8004/8500/8600 £9.50. Philips G8 complete £9.50. Decca 30/31 £8.50. Ferguson/JVC 1st video £19.50 or 3V00 types basic manual £19.50. Any Finlandia: Tyne CTV £9.50 each. Rank A823 complete £9.50.

COMPREHENSIVE PRACTICAL TV REPAIR MANUAL £9.50 PRACTICAL RADIO SERVICING & REPAIR COURSE £9.50  
THE 12 TUNBRIDGE TV REPAIR MANUALS ONLY £99 THE 5 McCOURT TV REPAIR MANUALS ONLY £35  
ANY SET OF 5 INDIVIDUAL TV VIDEO REPAIR MANUALS FOR £12.50 OR ALL 3 SETS (15 MANUALS) FOR £36.

## UNIQUE COLLECTIONS OF CIRCUITS, LAYOUTS, ETC. . . . FANTASTIC VALUE

British ctv from hybrids to modern (3 binders) £60 (2off) Videos, all types (3 binders) £58 . . . any 1 for £22  
Mono TV (2) £40 Foreign ctv (2) £38 Domestic Eqpt (2) £38 Portable British ctv (1) £22 plus VAT.

## COMPLETE REPAIR SYSTEMS . . . huge savings from published prices

British ctv 4 binders of Circuits plus 7 Repair Manuals plus ref books, etc. for only £140  
Foreign ctv 2 binders of Circuits plus 4 Repair Manuals, etc. for only £70  
Videos 3 binders plus 15 individual Repair Manuals cover all the commonest models for only £90  
Complete Integrated T.V. Repair System only £275 or in 12 sections at £27 per section.  
Contents: 8 binders of circuits/17 Repair Manuals/dozens of other manuals . . . Any new publications from us within 1 year of ordering 1st section will be added at no extra charge. No VAT on Systems

NEW 1987 British CTV Repair Manuals for £8.95 NEW. NEW Repair Manuals for Spectrum with circuits only £5.00 NEW. NEW Collection of 20 Hoover's W/Mc circuits £8.95 NEW. NEW Domestic Equipment Repairs & Servicing £14.95 NEW.

Repair data/Circuits/Service data almost any individual mono tv £12.50 basic ctv £12.95 video £10.50

LSAE BRINGS ANY REQUESTED QUOTATION - FULLER DETAILS - FREE MAGAZINE - PRICE LISTS ETC.  
PHONE 0698 884585 Mon-Fri before 5pm or 0698 883334 any other time - FOR FAST QUOTES

## GERMAN SERVICE SHEET SPECIALISTS

Our connections are world-wide. We furnish any kind of German, European and Japanese service sheet or manual. Thousands of different sheets and manuals in stock. For any enquiries:

**DÖNBERG ELECTRONICS**  
Schoolmasters House, Rannafast,  
Co. Donegal, Republic of Ireland.  
Phone: 075 48275

## SERVICE DATA-UK VCR & CTV

Circuits + layouts or complete manuals  
Comprehensive lists inc. £1.00 Voucher  
redeemable on first purchase. Send 50p  
Cheque or P.O. (No SAE required)

**DATA-GO, 112 Ameyford Road,  
Ferndown, Dorset BH22 9QE**

\*\*\*\*\*  
★ **WORKSHOP SERVICE MANUALS** ★  
★ **Thousands stocked** ★  
★ **Most Makes, Models, Types** ★  
★ Audio, TV, Video, Test, Amateur etc. LSAE ★  
★ enquiries/quotation and FREE Review/ ★  
★ price lists with details of our Unique Repair ★  
★ and Data Guides, from Valves to Video's. ★  
★ **MAURITRON (TV),** ★  
★ 8 Cherry Tree Road, Chinnor, Oxon OX9 4QY. ★  
\*\*\*\*\*

## AERIALS

**MULTI-OUTLET/MULTI-CHANNEL** Installations.  
Large or small distribution systems. Equipment and/or  
consultancy by post or on site. Catalogue (full or trade  
know-how and trade equipment) £1 (refundable).  
**WRIGHTS AERIALS, 43 Greaves Sike Lane,  
Micklebring, Rotherham. (0709) 813419.**

## SATELLITE TV RECEPTION EQUIPMENT



LNB's, Receivers, Dishes, polar mounts and accessories

Japanese LNBs from £95.00  
Japanese RX from £169.00  
Ku Band feedhorns from £5.99  
'F' Connectors only 0.20  
'N' - 'F' Adaptors only £1.40  
10db line amps only £12.00  
Prices excl. VAT. SAE for leaflets.



**KESH ELECTRICS LTD.**  
Main St., Kesh, Co. Fermanagh, N.I.  
Tel: 03656 31449 Tlx: 747412

## METERS

### GEM METERS

We buy and sell TV slot meters.  
Why not try our repair service?

Contact Mr Wolstenholme on:  
**0942 826126**

**METERS.** Reconditioned 10p/50p available from  
stock. Contact **THE METER CO. (Poole) LTD.**  
(0202) 683498.

### AVON METERS

**50p or £1 TV meters  
from £5.95 each plus V.A.T.**  
(Discount for Quantity)  
We also repair and buy unwanted meters.  
Phone now:  
48 Mead Road,  
Stoke Gifford, Bristol BS12 6PT  
Tel. 0454 776413

## REPAIR SERVICE

**AVO'S OSCILLOSCOPES & TEST EQUIPMENT**  
repaired. Manuals available. J.R. COAD ELEC-  
TRONIC SERVICES. Phone 01-340 0230.

## WANTED

### SURPLUS/REDUNDANT ELECTRONIC COMPONENTS WANTED

I/Cs - Tuners - Transistors - Valves -  
Diodes etc, any quantity considered -  
immediate payment.

**ADM Electronic Supplies**  
Tel. 0827 873311.

**WANTED.** Crown portable TV/Radio Model 5TV-  
65R. With rechargeable battery and in good working  
order. Non-working for spares considered. Any in-  
formation on spares for this monochrome 5 inch  
screen Jap receiver appreciated. Tel. 085-483-213  
(Scotland).

**RADIO & TV SERVICING** Volumes pre 1966 and  
past 1972. Oxford 735821.

**WANTED.** Ex rental colour TV, any quantity, quick  
collection. Discretion assured. Cash paid. Sheffield  
312832.

**WANTED VIDEO** TVs, portables. Cash paid, any  
quantity, fast collection. Television Direct, Manchester  
061-788 8997.

## SPECIAL OFFERS

**FREE MEMBERSHIP** to a new national electronics  
club. For details and a free pack of components worth  
over £10, send only £1 P&P to Dept Tel, Woodside,  
Dowsett Lane, Ramsden Heath, Billericay, Essex  
CM11 1JL.

**FOR FURTHER  
INFORMATION RING  
PAT  
01-261-5942**

# NEW CONTRACT

# 1000

**ELECTRONIC VCR's**  
**DELIVERED EACH WEEK**  
**ALL MAKES**  
**AND PRICES**



## Kent Ledgerwood Wholesale Ltd

**BRADFORD**  
TRITEL TV  
1043 Leeds  
Road  
Thornbury  
Roundabout  
BRADFORD  
Tel: 0274 665670

**LEEDS**  
TRITEL  
DISCOUNT  
STORES  
Long Row  
Horsforth  
LEEDS  
Tel: 0532 590252

**SCOTLAND**  
TRITEL TV  
Unit 4  
Peacock Cross  
Industrial  
Estate  
Burnbank Rd  
HAMILTON  
Tel: 0698 282141

**LONDON**  
UNIT E1,  
Waterloo Road,  
Staples Corner,  
London NW2.  
Tel: 01 208 2063

## SPANISH CUSTOMERS

- **1000 RECONDITIONED VIDEOS NOW IN STOCK**
- **CONNEXION SATELLITE COMPLETE SYSTEMS IN STOCK**
- **COLOUR TELEVISIONS ARRIVING SOON**

**AGENTS REQUIRED  
IN ALL REGIONS**

Contact Antonio Grande at:  
**KENT LEDGERWOOD  
MAYORISTAS S.A.**

**KELESA, CAP BLANC 38, LOCAL 9,  
CARRETERA,  
ALICANTE/VALENCIA 332**  
TEL: FROM SPAIN 965 843654  
TEL: FROM ENGLAND  
010 3465 843654  
TELEX: ENGLAND 517739  
KLWLTDG





# SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Matsushita PY34220 Tuner	E7	K35 Decoder	£8.00	Rank T20 Z136 Panel	£6.00	Tube Thempath 167	£1.00
Toshiba VHF-UHF LC4411	E6	K38 Sound OP	£4.00	NEW 167 THORN Chassis with IC's & AU113	£5.00	Rank Secam Decoder Panel UHF & VHF	£1.00
Toshiba VHF-UHF LC65221	E6	K38 Split Diode 3122-438-35930	£10.00	NEW GEC 20AX Power Supply Switch Model 200	£12.00	TT15A	£13.00
Mitsumi MI-C1-F51	E5	1/4" Thick Film Daughter KIT 3122-127-43891	£3	Complete new GEC portable chassis M120H/M150H with P.B.U./v.cap/LOPTI	£10.00	10 off .91 CAP G11	£2
<b>Thorn Spares</b>				Field + Jungle panel for GEC 3133/3135	£1.50	Philips K4 CAP 150M/385V	50p
New 9000 Decoder	£8.50	12 C.H. K30 Tex Rec Front Panel with IC	£5	GEC 2110 line panel with transformer	£7.00	<b>Multi-Caps</b>	
9000 Frame panel	£8	K35 HF	£5.00	GEC 2110 tuner unit + IF Panel	£10.00	150V 400M + 300M	50p
9000 Cxlops panel	£1.50			Pvc/Chelsea Line op panel	£12.00	400V 400M	60p
8000/8500 Imtbase panel	£8			Pvc 205 Tuner	£3.90	350V 400M	60p
8800 convergence panel	£6			Pvc 205 Line op panel	£7.50	Thorn 3500	£1.00
8500 convergence panel	£6			Pvc 713 H. panel and tuner	£7.00	175/100/100/350v	60p
4000 Power supply	£3	Fidelity Tube Base with transistor & focus pot	£1.50	Pvc/Chelsea Timebase panel with LOPTI	£10.00	K13/200/25/25/385v	£1.00
1600 Mains lead, switch				Pvc 731 Frame Panel	£5.00	200+200+75+25M 325V	£1.00
3500 6 push button + cable form	£1.50			Pvc 731 Convergence Panel	£5.00	300+300+150+100+50MFD	£1.00
1605 1.5N7P 1066 80V 6A	10p			Pvc 731 Chroma	£10.00	350V	£2
9000 Sound output panel	£1			Pvc 731 HF panel + tuner	£6.00	G11 CAP 470 250	£2
3500 Focus unit	£1.50			Pvc CDA205 panel	£10.00	47/220/350k	60p
3500 Mains Trans	£4			G19 portable chassis + LOPTI 2114 New	£4.00	150/150/100/100/320k	£2.00
3500 cut outs	10 for £4			Thorn 1613/1713 chassis	£9.75	250/250/400k	50p
3500 HF panel	£2			G9 Power Panel	£3.00	300/100/100/16/275v	70p
3500 Frame panel	£3			Mono RANK Chassis 127A NI-W	£10.00	100/200/325v	40p
3500 Line panel	£3			NI-W G9 Frame Panel	£4.00	150/150/100/375v	£1.50
3500 AI Diode	20p			NEW G11 HF Panel	£10.00	200/200/75/25M 325V	£1
Export 3500 HF panel	£2					Thorn TX9 Caps 500+500M 175v	£1.75
IF board with set of SN741 S	£1					300/300/100/32/32/300k	2.00
4000 Tube base	£4					1500/2000/30k	50p
3500 AI pots	50p					150/150/100/100/320k	£2.00
Beam limiter panel	£1.50					1400 x 10	30p
3500 Power panel with Y969	£1					225+25/380 G1-C	70p
3 Way regulated adaptor 240V 7.5VA 300mA	£3.50					200/100/100/350k	£1.50
Rank Toshiba preh unit 0354	£9.50					150/150/100/300k	75p
4 Push button unit preh	£1.00					200/150/150/300k	1.00
6 Push button VHF UHF for v.cap. GEC-Decca type	£7.00						
7 Push button for CVCS IFT	£8.00						
KS Push Button Unit	£10.00						
K13 12 Push button unit	£2.00						
K13 (Export) 12 P.B.U.	£2						
6 Push button Unit Thorn	£1.00						
6 Push button GRC	£6.00						
6 Push button PVE 731	£6.00						
Hearing aid unit	£3						
Rank Z718 4 P.B.U. Unit MI-CTI	£4						
7 Button Unit G1-C with 1 amp	£7						
697 Push Button Unit	£6.00						
Z91nB Panel	£5.00						
1513AP Panel	£5.00						
<b>Mains Droppers</b>							
G8 2R2 + 68F	£1.25						
G8 47R 15 watt	£1.00						
Pvc 731 3 x 50 27R	£1						
Thorn 50 17 1K5	£1.00						
120/20/20 48/117	£1.00						
270/10/6 for Thorn 4000	50p						
18.320 70 39	£1.10						
Thorn 50 40R 1K5	50p						
Ac Socket & Lead							
G1-C IFT 1, Philips, Pvc	25p						
78 35 4 Thorn	£1.50						
Thorn 1604/1700	£1.50						
Rank Toshiba Tube Bases	30p						
<b>Speakers</b>							
6 x 4 G11 25 ohm	£1.00						
5 1/2 x 2 1/2 15 ohm	£1.00						
5 x 3 80 ohm	70p						
5 x 3 50 ohm	50p						
5 x 3 35 ohm	70p						
6 x 4 15 ohm	£1.00						
6 x 4 speaker 16 ohm	£1.00						
7 x 3 70 ohm	£1.00						
8 x 5 8 ohm 15 watt	£2						
8 x 5 8 ohm	£1						
8 x 5 8 ohm	70p						
8 x 5 16 ohm	£1.00						
8 x 5 8 ohm	£1.00						
8 x 5 8 ohm	£1.00						
6 1/2 dia 4 ohm	£1.50						
6 1/2 dia 3 ohm	£1.50						
5 7/8 dia 8 ohm	75p						
5 7/8 dia 8 ohm	75p						
4 1/2 sq 15 ohm	£1.00						
K13 speaker 8 ohm	75p						
7 dia 15 ohm	60p						
1600 x 3 12 ohm	£1						
K45 Philip 15 ohm	75p						
K40 15 watt	£1						
<b>KT3-K30</b>							
CI 425	10p						
CI 550	10p						
CI 513	10p						
CI 557	50p						
<b>DIODES</b>							
BY 126	10p						
BY 127	10p						
BY 133	10p						
BY 134	10p						
BY 164	50p						
BY 176	25p						
BY 179	40p						
BY 184	25p						
BY 187	10p						
BY 190	40p						
BY 196	30p						
BY 198	30p						
BY 201 4	8p						
BY 206	8p						
BY 208 500k	8p						
BY 210 800k	8p						
BY 223	60p						
BY 224 600 1.5A 600k bridge	50p						
BY 226	15p						
BY 227	10p						
BY 228 150k	20p						
1A BY 229 black	15p						
BY 209 Red	30p						
BY 229 40p	30p						
BY 209 60p Fig	30p						
BY 237	5p						
BY 251	10p						
BY 255	30p						
BY 268	10p						
BY 269	10p						
BY 306	8p						
BY 327	8p						
BY 407a	10p						
BY 527	10p						
BY 602	10p						
E 247	5p						
CP200	5p						
NK 3102	20p						
BYA 28 200	20p						
800x 2.75 amps	20p						
International Rectifier FET Diodes	3 for 8p						
6A 600V Stud Diodes	20p						
6A 1000V Stud Diodes	20p						
K35 Decoder	£8.00						
K38 Sound OP	£4.00						
K38 Split Diode 3122-438-35930	£10.00						
1/4" Thick Film Daughter KIT 3122-127-43891	£3						
12 C.H. K30 Tex Rec Front Panel with IC	£5						
K35 HF	£5.00						
Fidelity Tube Base with transistor & focus pot	£1.50						
Bush Tube Base on panel	£1.00						
Line Transformers							
120V O.P. Trans Mono 1X 12" 14"							
Philips							
2752	£10						
4822	£10						
10273	£10						
Thorn 1600 LOPTI	£6.50						
2 J Pos 3.800 1 off each type	£3.00						
G8 Trans. Philips	£7.00						
G11 Split Diode	£12.00						
CVC 820 Split Diode IFT	£10.00						
Thorn B.W. ADS 80RF + Suk + Lead	£1.50						
1600 Thorn IFT over-wind with diode lead & anode cap	£2.50						
G1-C 2040	£3.00						
G1-C 2110	£7.00						
Mullard A1 2036	£1.50						
Pvc 169 1 me Trans	£3.00						
Pvc mono	£3.00						
Rank mono 1704A	£3.50						
Split Diode Trans	£7.00						
G1-C 20 V.A. Rank Z522	£3.00						
Rank I O.P.T. Z970	£5.00						
CVC 20 IFT	£7.00						
A12080 15	£5.00						
CVC 30 IFT	£5.00						
CVC 32 Line Tran	£7.00						
CVC 800 Line Trans	£6.00						
CVC 40 Split Diode	£12.00						
CVC 45	£5.00						
G1-C Portable G1012041	£3.00						
G1-C Portable G1012046	£3.00						
IHT Split Diode Leads IFT	£1.00						
8801 O.P.T. & IFT Trans	each £2.00						
I O.P.T. Rank Z763	£5.00						
K35 Split Diode 3122 13835930	£10.00						
<b>Black Triplers</b>							
S.T.C. Universal Tripler	£5.00						
CI 111	£2.50						
CI 110 V	£2.00						
IFT CVC 5 8 9	£3.50						
Rank 12511 Tripler	£2.00						
Rank IHT CV 823							

# SENDZ COMPONENTS

63 Bishopsteignton,  
Shoeburyness, ESSEX SS3 8AF  
SAME DAY SERVICE

All items subject to availability.  
No Accounts - No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then £1 Postage  
Add Postage for overseas

Callers: To shop at 212 London Rd.,  
Southend. Tel. 0702-332992

Open 9-1/2.30.6. GVMT + school orders accepted on official  
headings add 10% handling charge.

Tuner Units	
VHF-UHF with Data Tuner MEC1-F51	£3
Thorn TX10 Export V-Cap UHF VHF	£6
G8 Tuner V/Cap New	£2
G8 6 Button Unit	£9
V/Cap Rank UHF 2776 Unit	£6
V/Cap Rank VHF 2773 Unit	£5
NEW G8 Tuner V/Cap	£3.50
L20 6 Push Button Unit	£7
FLC 2000 on Panel	£2.50
GEC 6 Push Button Unit	£6
FLC 6 Push Button Unit	£6
DFCCA 6 Push Button Unit	£6
GEC or Hitachi 6 push button unit 2110 Conversion	£8
GEC 2110 V/Cap	£5
FLC043 (V-Cap)	£3.75
FLC042	NEW £5.50
FLC2000	NEW £4.00
FLC2004	NEW £8.00
FLC2006	NEW £4.00
GEC Tuner V/Cap Hitachi After 1979 F-ES48, E1547, F-1541B	£8.00
AS1E-C UM1183	£10.00
V314 (VHF)	£5.00
V317 (VHF)	£7.00
V334 (VHF)	£5.00
U321	£6.00
U341 (UHF)	£7.00
U342 (UHF)	£5.00
U411 (UHF)	£7.00
U.V. 411 Tuner	£10.00
U.V. 415	£7.00
U.V. 417	£7.00
Fidelity and Anstrad 2000 V/Cap Tuner	£5.00
Small V-Cap Mitsumi	£4.00
UHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF-VHF-Vancap (old type)	£8.00
Moskit UHF-VHF (new type)	£8.00
UHF-2-B3 Fidelity V-Cap Tuner	£6
UHF-VHF V/Caps on panel	£3.00
HITACHI 20 Turn Pot	£6.00
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Video Mini UHF	£2.50
Toshiba VHF-UHF E-G5221	£5.00
Multiband Video Modulator	
Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.T.V. system Data supplied	£10.00
UHF Tuner GTR Sylvania	
F4714A	£2
VHF Tuner GTR Sylvania E3720B	£2

Sylvania UHF F-4720B	£6.00	BD1610	40p
Sylvania VHF 900	£6.00	BD1646	50p
Small Tuner DX 175 220MHz		BD707A	40p
Auto Changerover	£5.00	BD807	20p
9000 Hour Tuner on Panel	£7.00	BD826	50p
Hitachi 1400 4P B Mech Tuner		BD948	20p
Hitachi 1500 4P B Mech Tuner		BD1075	20p
Hitachi 1590 4P B Mech Tuner		BD104B	50p
Hitachi 3500 4P B Mech Tuner		BDU66	50p
All new & boxed	£4.00 each	BF761	30p
TDK 19000A	50p	BF769	30p
Delay Lines		BF788	30p
DI 20A 80p	DI 600 £1.00	BF819A	30p
G8 (Old Type)	£1	BF888	30p
DI 600	£1.00	BF871	30p
DI 700	£1.00	BF839	15p
K1.31 omnidirectional	75p	BF852	7p
Luminance Delay Line (C.C. 45)		BF879	15p
Co Ax Joint	15p	BF881	15p
Co Ax Belling Lee Plug	12p	BF887	10p
Co Ax Splitter	£1.00	BF887	10p
UHF Modulator C.O.R	£3.00	BF887	10p
Intra Red Emitting Diode	20p	BF887	10p
NI 2861 Small Neon Lamps GEC & Philips	5p	BF887	10p
Mullard 5 Watt Amps (P116) New	75p	BF887	10p
I.V. Tubes		BF887	10p
L2 110 310 with coils	Post £2.50 £5	BF887	10p
12 A31 300 Hitachi	£10	BF887	10p
N.W. Filters	S.W. Filters		
1AW2013	50p	SW183	£1
SW453	50p	SW183	50p
SW180	£1	SW184	50p

NE555P	60p	TMS4014	70p
NE555S	60p	TX-012	£1.00
HD3898K	£3.00	TMS9902	£1.20
HL1	20p	ULN2216	75p
OPT160	20p	UIC3661	£1.00
OPT161	20p	UIC3662	£1.00
SAA611	£1.00	UIC3663	£1.00
SAA661	£1.75	UIC3664	£1.00
SAA1020	£4.00	UIC3665	£1.00
SAA1134	£2.50	UIC3666	£1.00
SAA1024	£2.50	UIC3667	£1.00
SAA1025	£2.50	UIC3668	£1.00
SAA1073	£3.00	UIC3669	£1.00
SAA1074	£3.00	UIC3670	£1.00
SAA1075	£3.00	UIC3671	£1.00
SAA1124	£2.50	UIC3672	£1.00
SAA1174	£3.00	UIC3673	£1.00
SAA1176	£2.00	UIC3674	£1.00
SAA1251	£3.00	UIC3675	£1.00
SAA1272	£3.00	UIC3676	£1.00
SAA1274	£3.00	UIC3677	£1.00
SAA1276	£3.00	UIC3678	£1.00
SAA3027P	£4.00	UIC3679	£1.00
SAA5000A	£1.50	UIC3680	£1.00
SAB3013	£2.00	UIC3681	£1.00
SAB3210	£2.00	UIC3682	£1.00
SAB3209	£2.00	UIC3683	£1.00
TBC00124	£1.00	UIC3684	£1.00
SAA5001A	£1.50	UIC3685	£1.00
SAA5010	£2.20	UIC3686	£1.00
SAA5012A	£5.00	UIC3687	£1.00
SAA5020	£3.50	UIC3688	£1.00
SAA5030	£4.50	UIC3689	£1.00
SAA5040	£3.50	UIC3690	£1.00
SAA5040A	£3.00	UIC3691	£1.00
SAA5051	£4.50	UIC3692	£1.00
SAA5052	£2.50	UIC3693	£1.00
SAA5053	£2.00	UIC3694	£1.00
SAA5054	£2.00	UIC3695	£1.00
SAA5055	£2.00	UIC3696	£1.00
SAA5184	£2.00	UIC3825	£1.00
SAA5185	£2.00		