


OCTOBER 1991

£1.80
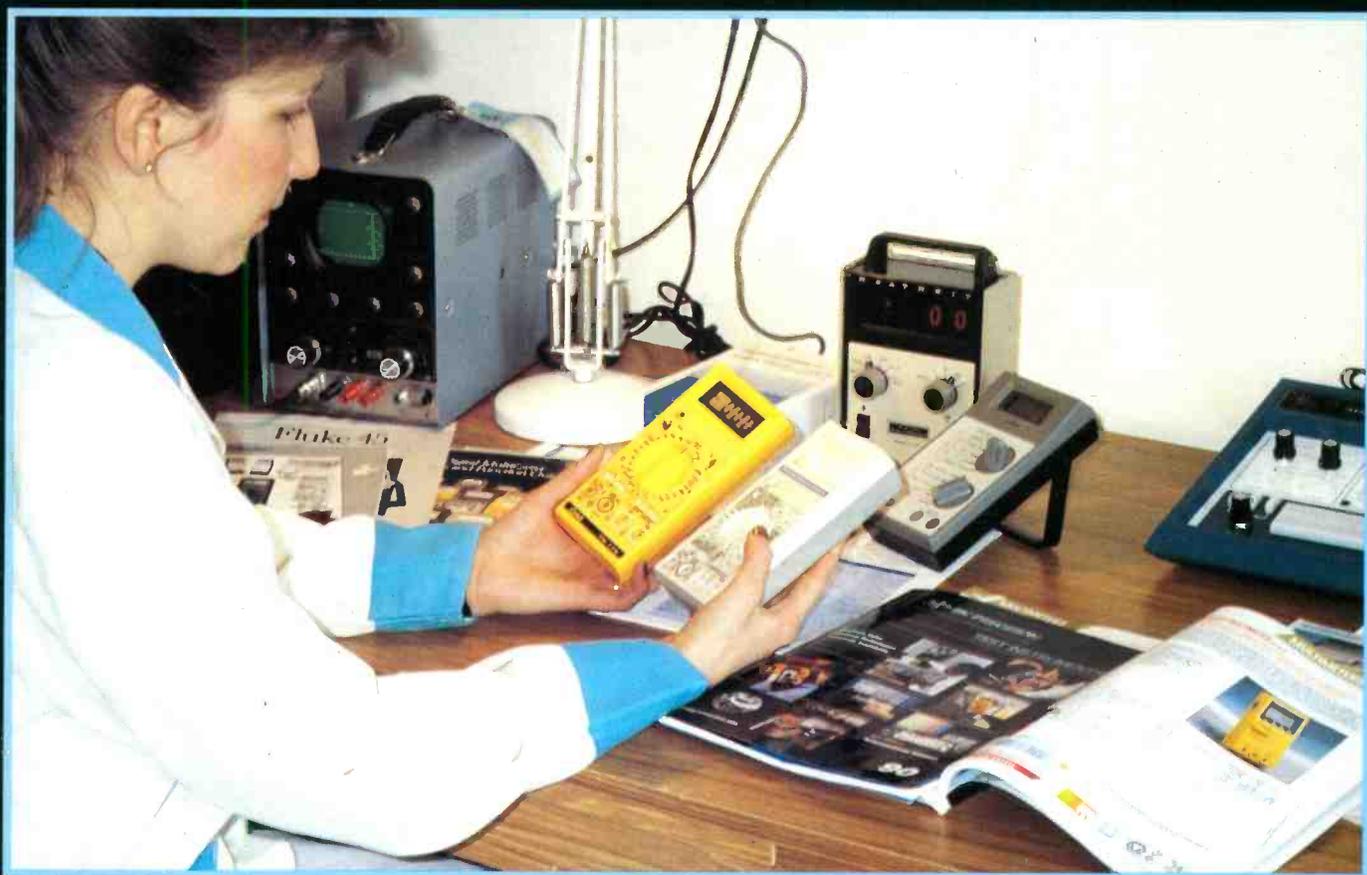
# TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

**FREE MAGNIFYING LENS  
PLUS COMPONENTS CATALOGUE**



**Choosing a Digital Multimeter  
Adding a Scart Connector • DX-TV  
Servicing the Saisho VR1200 VCR  
The Photo CD Format • Camcorner  
VCR Clinic • TV Fault Finding**



**FLUKE®**



**PHILIPS**

# NICAM testing? Get the multistandard solution!



Colour TV pattern generators that give you both NICAM and analog sound channels.

If you need NICAM testing facilities in a single, versatile instrument, Philips has a cost-effective solution. Three multi-standard generators, PM 5515 TN, PM 5518 TN and PM 5518 TNI, that give you every video and audio test signal you need – including both NICAM and analog sound channels. The PM 5518 TNI is remote controllable via IEEE interface. On-board audio test functions include mono, stereo and dual signals for digital

and analog sound, with over 55 selectable digital test signals, plus high-stability (2 p.p.m.) subcarrier and sound carrier signals.

You also get versatile video test functions – like full RF coverage with synthesized frequency control, over 70 instantly selectable test patterns and combinations, Teletext, storage for up to 10 multi-program test sequences and external video modulation facilities.

So for NICAM testing, choose the generators that give you a one-stop test solution.


**Philips Test & Measurement**  
Colonial Way, Watford WD2 4TT  
Tel: 0923 240511 Telex: 934583 PHITMD G  
Fax: 0923 225067

*A division of Philips Scientific*

Available for hire from  
**LIVINGSTON HIRE**  
Call 0800 886000



**PHILIPS**

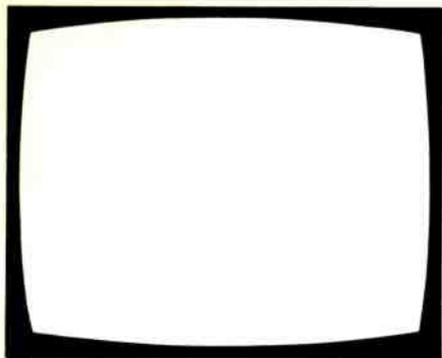

# TELEVISION

October  
1991

Vol. 41, No. 12  
Issue 492

On sale September 18th

## COPYRIGHT

© Reed Business Publishing Ltd., 1991. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Editorial correspondence should be addressed to "Television", Editorial Dept., Reed Business Publishing Group, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

## INDEXES AND BINDERS

Indexes to Vols. 37 and 38 are available at £1 each from the Editorial office (address above). Photostats of the indexes to Vols. 31-36 can be supplied at £1 each.

Binders that hold twelve issues of *Television* are available for £4.50 from Television Binders, 78 Whalley Road, Wilpshire, Blackburn BB1 9LF. Make cheques out to "Television Binders".

## SUBSCRIPTIONS

An annual subscription costs £21.60 in the UK, £25.50 overseas (by surface mail – ask for airmail quote if required). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

## BACK NUMBERS

Subject to availability, copies of issues published during the last 12 months are available at £1.80 each from Television, John Denton Services, Unit 13, Thornham Grove, Stratford, London E15 1DN. Please make cheques/postal orders payable to Reed Business Publishing Ltd.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them.

## this month

- 861 Leader**
- 862 VCR Plus** *George Cole*  
A VCR timer setting system, based on published codes and a handset with its own timer, that's about to be introduced in the UK.
- 864 Teletopics**  
News, comment and developments.
- 865 CD Player Casebook**  
Reports from Mike Leach and Philip Blundell, AMIEIE.
- 866 Adding a Scart Connector** *K. Wevill, B.Sc.*  
An interface circuit that enables a scart connector to be added to sets employing common i.f., sound and PAL decoder chips.
- 870 In Baird's Footsteps** *J. LeJeune*  
Reinventing the 30-line mechanical TV system to discover the problems that Baird had to deal with in the Twenties and early Thirties.
- 873 The Photo CD Format** *George Cole*  
Specification of the Photo CD system, which stores photographic images in data form on a compact disc, and the way in which the system works.
- 876 VCR Clinic**  
Reports from Philip Blundell, AMIEIE, Ed Rowland, Roger Burchett, Brian Storm, Nick Beer, Chris Avis, J. Edwards and Mick Dutton.
- 878 What a Life!** *Donald Bullock*  
The fault-finding process can go awry when prejudice intervenes.
- 879 Choosing a Digital Multimeter, Part 1** *David Botto*  
Features and types of DMM and their mode of operation.
- 882 The Ferguson Singapore Briefing** *Graham Exeter*  
During a visit to Ferguson's new joint venture video plant in Singapore an outline of the firm's video marketing strategy was given.
- 883 Next Month in Television**
- 884 Letters**
- 886 Steve's Camcorder** *Steve Beeching, T.Eng.*  
Camcorder servicing notes.
- 890 Servicing the Saisho VR1200/Matsui VX820** *Ed Rowland*  
A run-down on common faults with these popular VCRs.
- 892 A Video Nasty** *Nick Beer*  
The problem with this Panasonic NV-FS1B was particularly difficult to sort out.
- 893 Long-distance Television** *Roger Bunney*  
DX conditions and reception and news from abroad. Also a MOSFET Band 1 preamplifier circuit.
- 895 Service Briefs – Pioneer**  
Official notes on Pioneer Laservision and CD players.
- 896 TV Fault Finding**  
Reports from Brian Storm, Paul Hardy, Stephen Leatherbarrow, Michael Dranfield, J. Edwards, J.K. Potts and John C. Priest.
- 898 Test Case 346**

OUR NEXT ISSUE DATED NOVEMBER WILL  
BE PUBLISHED ON OCTOBER 16

AA932	9p	BD332	40p	BT779	140p	TI117	50p	OA47	10p	PCF801	110p	AN7145	195p	ICL7166	650p	LM3909	80p	STK436	490p	STK7226	800p	TA7310	100p
AC107	30p	BD361	60p	BU100A	110p	TI210	37p	OA90	10p	PCF802	80p	AN7146	210p	ICL7167	240p	LM3911	80p	STK437	500p	STK7308	410p	TA7312	120p
AC125	30p	BD362	60p	BU104	80p	TI211	49p	OA91	10p	PCF803	115p	AN7154	180p	ICL7168	240p	LM3914	80p	STK438	500p	STK7309	410p	TA7313	110p
AC126	30p	BD363	60p	BU108	80p	TI212	47p	OA92	10p	PCF804	100p	AN7155	180p	ICL7169	240p	LM3915	80p	STK439	500p	STK7310	410p	TA7314	110p
AC127	30p	BD371	60p	BU109	80p	TI215	47p	QA202	10p	PCF811	65p	AN7168	200p	ICM75566	80p	LM3916	270p	STK443	740p	STK7345	410p	TA7315	200p
AC128	35p	BD410	80p	BU109	80p	TI216	56p	IN.914	2p	PCL82	80p	AN7178	270p					STK457	600p	STK7356	600p	TA7317P	240p
AC128K	40p	BD433	28p	BU110	110p	TI217	56p	IN.4001	3p	PCL84	80p	AN7222	270p	KA2101	100p	M50115F	320p	STK458	600p	STK7358	600p	TA7324	240p
AC141K	40p	BD434	28p	BU111	110p	TI218	56p	IN.4002	3p	PCL85	80p	AN7223	270p	KA2102	100p	M50117P	320p	STK459	600p	STK7360	600p	TA7325	90p
AC142K	45p	BD435	31p	BU124	66p	TI219	30p	IN.4003	3p	PCL86	80p	AN7256	260p	KA2103	150p	M50119F	525p	STK461	720p	STK7402	600p	TA7326	80p
AC176	22p	BD436	28p	BU126	66p	TI221	30p	IN.4004	3p	PCL805	80p	AN7310	90p	KA2206	150p	M50120P	650p	STK463	780p	STK7406	800p	TA7328	200p
AC167K	28p	BD437	28p	BU180	100p	TI241	90p	IN.4005	3p	PFL200	110p	AN7311	90p	KA2209	128p	M50130P	650p	STK465	720p	STK7408	800p	TA7329	250p
AC187	28p	BD438	28p	BU184	100p	TI242	90p	IN.4006	3p	PL82	65p	AN7410	260p	KA2212	80p	M50178	600p	STK467	800p	STK7410	1200p	TA7341	280p
AC187K	40p	BD439	30p	BU216	80p	TI246	90p	IN.4007	3p	PL82	65p			KA2212	80p	M50178	600p	STK469	800p	STK7412	1200p	TA7343	280p
AC188	25p	BD440	30p	BU205	70p	TI246	90p	IN.4148	2p	PL83	60p	AY-1015	290p	KA2213	130p	M50190	600p	STK475	800p	STK7561	700p	TA7357	400p
AC188K	40p	BD441	30p	BU206	100p	TI247	100p	IN.5400	9p	PL84	80p	AY-1270	290p	KA2214	160p	M51161	300p	STK483	800p	STK7563	900p	TA7358	200p
AC1918	48p	BD442	30p	BU208	70p	TI250	90p	IN.5401	9p	PL85	180p	AY-1350	450p	KA2215	160p	M51355P	300p	STK7348	810p	STK8050	1800p	TA7401	400p
AD149	60p	BD453	38p	BU208A	90p	TI255	42p	IN.5402	8p	PL86	100p	AY-8910	360p	KA2216	100p	M51381P	200p	STK745	500p	STK8280	1800p	TA7658	270p
AF125	50p	BD536	38p	BU208D	80p	TI255A	45p	IN.5404	45p	PL808	200p	AY-8912	400p	KA2264	100p	M51387P	200p	STK760	600p	STK8280	1800p	TA7608	360p
AF127	50p	BD537	38p	BU209	140p	TI255B	42p	IN.5405	11p	PL819	430p			BA301	85p	M51392	660p	STK770	760p	STK8280	1800p	TA7609	270p
AF133	30p	BD538	38p	BU210	140p	TI256	42p	IN.5406	12p	PL820	400p			BA311	85p	M51397	660p	STK772	780p	STK73410	1860p	TA7611	280p
AF239	30p	BD543	60p	BU226	190p	TI256A	15p	IN.5407	12p	PL821	400p			BA313	85p	M51544	150p	STK1039	850p	STR70	680p	TA7612	360p
		BD545	60p	BU312	120p	TI256B	15p	IN.5408	12p	PL822	400p			BA333	100p	M51724	300p	STK1040	700p	STR70	680p	TA7616	400p
		BD545	60p	BU325	85p	TI256C	15p	IN.5409	12p	PL823	400p			BA401	80p	M51848	150p	STK1049	800p	STR70	680p	TA7621	520p
		BD545	60p	BU326	75p	TI256D	15p	IN.5410	12p	PL824	400p			BA402	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7622	420p
		BD545	60p	BU406	70p	TI256E	15p	IN.5411	12p	PL825	400p			BA403	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7623	420p
		BD545	60p	BU406D	80p	TI256F	15p	IN.5412	12p	PL826	400p			BA404	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7624	420p
		BD545	60p	BU406E	80p	TI256G	15p	IN.5413	12p	PL827	400p			BA405	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7625	420p
		BD545	60p	BU406F	80p	TI256H	15p	IN.5414	12p	PL828	400p			BA406	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7626	420p
		BD545	60p	BU406G	80p	TI256I	15p	IN.5415	12p	PL829	400p			BA407	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7627	420p
		BD545	60p	BU406H	80p	TI256J	15p	IN.5416	12p	PL830	400p			BA408	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7628	420p
		BD545	60p	BU406I	80p	TI256K	15p	IN.5417	12p	PL831	400p			BA409	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7629	420p
		BD545	60p	BU406J	80p	TI256L	15p	IN.5418	12p	PL832	400p			BA410	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7630	420p
		BD545	60p	BU406K	80p	TI256M	15p	IN.5419	12p	PL833	400p			BA411	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7631	420p
		BD545	60p	BU406L	80p	TI256N	15p	IN.5420	12p	PL834	400p			BA412	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7632	420p
		BD545	60p	BU406M	80p	TI256O	15p	IN.5421	12p	PL835	400p			BA413	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7633	420p
		BD545	60p	BU406N	80p	TI256P	15p	IN.5422	12p	PL836	400p			BA414	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7634	420p
		BD545	60p	BU406O	80p	TI256Q	15p	IN.5423	12p	PL837	400p			BA415	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7635	420p
		BD545	60p	BU406P	80p	TI256R	15p	IN.5424	12p	PL838	400p			BA416	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7636	420p
		BD545	60p	BU406Q	80p	TI256S	15p	IN.5425	12p	PL839	400p			BA417	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7637	420p
		BD545	60p	BU406R	80p	TI256T	15p	IN.5426	12p	PL840	400p			BA418	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7638	420p
		BD545	60p	BU406S	80p	TI256U	15p	IN.5427	12p	PL841	400p			BA419	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7639	420p
		BD545	60p	BU406T	80p	TI256V	15p	IN.5428	12p	PL842	400p			BA420	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7640	420p
		BD545	60p	BU406U	80p	TI256W	15p	IN.5429	12p	PL843	400p			BA421	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7641	420p
		BD545	60p	BU406V	80p	TI256X	15p	IN.5430	12p	PL844	400p			BA422	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7642	420p
		BD545	60p	BU406W	80p	TI256Y	15p	IN.5431	12p	PL845	400p			BA423	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7643	420p
		BD545	60p	BU406X	80p	TI256Z	15p	IN.5432	12p	PL846	400p			BA424	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7644	420p
		BD545	60p	BU406Y	80p	TI2570	15p	IN.5433	12p	PL847	400p			BA425	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7645	420p
		BD545	60p	BU406Z	80p	TI2571	15p	IN.5434	12p	PL848	400p			BA426	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7646	420p
		BD545	60p	BU4070	80p	TI2572	15p	IN.5435	12p	PL849	400p			BA427	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7647	420p
		BD545	60p	BU4080	80p	TI2573	15p	IN.5436	12p	PL850	400p			BA428	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7648	420p
		BD545	60p	BU4090	80p	TI2574	15p	IN.5437	12p	PL851	400p			BA429	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7649	420p
		BD545	60p	BU4100	80p	TI2575	15p	IN.5438	12p	PL852	400p			BA430	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7650	420p
		BD545	60p	BU4110	80p	TI2576	15p	IN.5439	12p	PL853	400p			BA431	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7651	420p
		BD545	60p	BU4120	80p	TI2577	15p	IN.5440	12p	PL854	400p			BA432	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7652	420p
		BD545	60p	BU4130	80p	TI2578	15p	IN.5441	12p	PL855	400p			BA433	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7653	420p
		BD545	60p	BU4140	80p	TI2579	15p	IN.5442	12p	PL856	400p			BA434	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7654	420p
		BD545	60p	BU4150	80p	TI2580	15p	IN.5443	12p	PL857	400p			BA435	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7655	420p
		BD545	60p	BU4160	80p	TI2581	15p	IN.5444	12p	PL858	400p			BA436	80p	M5200P	100p	STK1050	760p	STR70	680p	TA7656	420p
		BD545																					

LINEAR IC's		CONT.		JAPANESE TRANSISTORS		VIDEO HEADS																	
TD4120	200p	TD4503	300p	2N4325	340p	2SA1315	100p	2SC945	20p	2SC1855	85p	2SC2502	200p	2SC3104	1650p	2SC3787	100p	2SD-921	320p	2SD-1273	100p	2SD-1455	320p
TD4140	140p	TD4505	300p	2N4438	510p	2SA1316	100p	2SC950	20p	2SC1856	50p	2SC2509	200p	2SC3105	3600p	2SC3789	75p	2SD-923	320p	2SD-1275	100p	2SD-1457	320p
TD4150	380p	TD4510	600p	2N4519	190p	2SA1317	30p	2SC959	225p	2SC1861	400p	2SC2516	125p	2SC3112	35p	2SC3790	120p	2SD-946	120p	2SD-1276	200p	2SD-1459	120p
TD4151	200p	TD4515	600p	2N4556	640p	2SA1318	30p	2SC980	250p	2SC1865	700p	2SC2519	80p	2SC3114	50p	2SC3795	200p	2SD-947	120p	2SD-1277	190p	2SD-1468	60p
TD4152	300p	TD4520	600p	2N4557	640p	2SA1319	30p	2SC981	250p	2SC1866	800p	2SC2520	100p	2SC3115	50p	2SC3796	200p	2SD-948	120p	2SD-1278	190p	2SD-1469	60p
TD4153	300p	TD4525	600p	2N4558	640p	2SA1320	30p	2SC982	250p	2SC1867	600p	2SC2521	100p	2SC3116	50p	2SC3797	200p	2SD-949	120p	2SD-1279	190p	2SD-1470	60p
TD4154	450p	TD4530	380p	2N4559	1200p	2SA1321	30p	2SC983	120p	2SC1868	200p	2SC2522	200p	2SC3117	120p	2SC3798	120p	2SD-950	350p	2SD-1280	300p	2SD-1471	450p
TD4155	200p	TD4535	380p	2N4560	160p	2SA1322	30p	2SC984	600p	2SC1869	600p	2SC2523	150p	2SC3118	50p	2SC3799	120p	2SD-951	350p	2SD-1281	400p	2SD-1472	450p
TD4156	200p	TD4540	200p	2N4561	200p	2SA1323	30p	2SC985	600p	2SC1870	200p	2SC2524	150p	2SC3119	50p	2SC3800	120p	2SD-952	350p	2SD-1282	400p	2SD-1473	450p
TD4157	200p	TD4545	200p	2N4562	200p	2SA1324	30p	2SC986	600p	2SC1871	200p	2SC2525	150p	2SC3120	50p	2SC3801	120p	2SD-953	350p	2SD-1283	400p	2SD-1474	450p
TD4158	200p	TD4550	200p	2N4563	200p	2SA1325	30p	2SC987	600p	2SC1872	200p	2SC2526	150p	2SC3121	50p	2SC3802	120p	2SD-954	350p	2SD-1284	400p	2SD-1475	450p
TD4159	200p	TD4555	200p	2N4564	200p	2SA1326	30p	2SC988	600p	2SC1873	200p	2SC2527	150p	2SC3122	50p	2SC3803	120p	2SD-955	350p	2SD-1285	400p	2SD-1476	450p
TD4160	200p	TD4560	200p	2N4565	200p	2SA1327	30p	2SC989	600p	2SC1874	200p	2SC2528	150p	2SC3123	50p	2SC3804	120p	2SD-956	350p	2SD-1286	400p	2SD-1477	450p
TD4161	200p	TD4565	200p	2N4566	200p	2SA1328	30p	2SC990	600p	2SC1875	200p	2SC2529	150p	2SC3124	50p	2SC3805	120p	2SD-957	350p	2SD-1287	400p	2SD-1478	450p
TD4162	200p	TD4570	200p	2N4567	200p	2SA1329	30p	2SC991	600p	2SC1876	200p	2SC2530	150p	2SC3125	50p	2SC3806	120p	2SD-958	350p	2SD-1288	400p	2SD-1479	450p
TD4163	200p	TD4575	200p	2N4568	200p	2SA1330	30p	2SC992	600p	2SC1877	200p	2SC2531	150p	2SC3126	50p	2SC3807	120p	2SD-959	350p	2SD-1289	400p	2SD-1480	450p
TD4164	200p	TD4580	200p	2N4569	200p	2SA1331	30p	2SC993	600p	2SC1878	200p	2SC2532	150p	2SC3127	50p	2SC3808	120p	2SD-960	350p	2SD-1290	400p	2SD-1481	450p
TD4165	200p	TD4585	200p	2N4570	200p	2SA1332	30p	2SC994	600p	2SC1879	200p	2SC2533	150p	2SC3128	50p	2SC3809	120p	2SD-961	350p	2SD-1291	400p	2SD-1482	450p
TD4166	200p	TD4590	200p	2N4571	200p	2SA1333	30p	2SC995	600p	2SC1880	200p	2SC2534	150p	2SC3129	50p	2SC3810	120p	2SD-962	350p	2SD-1292	400p	2SD-1483	450p
TD4167	200p	TD4595	200p	2N4572	200p	2SA1334	30p	2SC996	600p	2SC1881	200p	2SC2535	150p	2SC3130	50p	2SC3811	120p	2SD-963	350p	2SD-1293	400p	2SD-1484	450p
TD4168	200p	TD4600	200p	2N4573	200p	2SA1335	30p	2SC997	600p	2SC1882	200p	2SC2536	150p	2SC3131	50p	2SC3812	120p	2SD-964	350p	2SD-1294	400p	2SD-1485	450p
TD4169	200p	TD4605	200p	2N4574	200p	2SA1336	30p	2SC998	600p	2SC1883	200p	2SC2537	150p	2SC3132	50p	2SC3813	120p	2SD-965	350p	2SD-1295	400p	2SD-1486	450p
TD4170	200p	TD4610	200p	2N4575	200p	2SA1337	30p	2SC999	600p	2SC1884	200p	2SC2538	150p	2SC3133	50p	2SC3814	120p	2SD-966	350p	2SD-1296	400p	2SD-1487	450p
TD4171	200p	TD4615	200p	2N4576	200p	2SA1338	30p	2SC1000	600p	2SC1885	200p	2SC2539	150p	2SC3134	50p	2SC3815	120p	2SD-967	350p	2SD-1297	400p	2SD-1488	450p
TD4172	200p	TD4620	200p	2N4577	200p	2SA1339	30p	2SC1001	600p	2SC1886	200p	2SC2540	150p	2SC3135	50p	2SC3816	120p	2SD-968	350p	2SD-1298	400p	2SD-1489	450p
TD4173	200p	TD4625	200p	2N4578	200p	2SA1340	30p	2SC1002	600p	2SC1887	200p	2SC2541	150p	2SC3136	50p	2SC3817	120p	2SD-969	350p	2SD-1299	400p	2SD-1490	450p
TD4174	200p	TD4630	200p	2N4579	200p	2SA1341	30p	2SC1003	600p	2SC1888	200p	2SC2542	150p	2SC3137	50p	2SC3818	120p	2SD-970	350p	2SD-1300	400p	2SD-1491	450p
TD4175	200p	TD4635	200p	2N4580	200p	2SA1342	30p	2SC1004	600p	2SC1889	200p	2SC2543	150p	2SC3138	50p	2SC3819	120p	2SD-971	350p	2SD-1301	400p	2SD-1492	450p
TD4176	200p	TD4640	200p	2N4581	200p	2SA1343	30p	2SC1005	600p	2SC1890	200p	2SC2544	150p	2SC3139	50p	2SC3820	120p	2SD-972	350p	2SD-1302	400p	2SD-1493	450p
TD4177	200p	TD4645	200p	2N4582	200p	2SA1344	30p	2SC1006	600p	2SC1891	200p	2SC2545	150p	2SC3140	50p	2SC3821	120p	2SD-973	350p	2SD-1303	400p	2SD-1494	450p
TD4178	200p	TD4650	200p	2N4583	200p	2SA1345	30p	2SC1007	600p	2SC1892	200p	2SC2546	150p	2SC3141	50p	2SC3822	120p	2SD-974	350p	2SD-1304	400p	2SD-1495	450p
TD4179	200p	TD4655	200p	2N4584	200p	2SA1346	30p	2SC1008	600p	2SC1893	200p	2SC2547	150p	2SC3142	50p	2SC3823	120p	2SD-975	350p	2SD-1305	400p	2SD-1496	450p
TD4180	200p	TD4660	200p	2N4585	200p	2SA1347	30p	2SC1009	600p	2SC1894	200p	2SC2548	150p	2SC3143	50p	2SC3824	120p	2SD-976	350p	2SD-1306	400p	2SD-1497	450p
TD4181	200p	TD4665	200p	2N4586	200p	2SA1348	30p	2SC1010	600p	2SC1895	200p	2SC2549	150p	2SC3144	50p	2SC3825	120p	2SD-977	350p	2SD-1307	400p	2SD-1498	450p
TD4182	200p	TD4670	200p	2N4587	200p	2SA1349	30p	2SC1011	600p	2SC1896	200p	2SC2550	150p	2SC3145	50p	2SC3826	120p	2SD-978	350p	2SD-1308	400p	2SD-1499	450p
TD4183	200p	TD4675	200p	2N4588	200p	2SA1350	30p	2SC1012	600p	2SC1897	200p	2SC2551	150p	2SC3146	50p	2SC3827	120p	2SD-979	350p	2SD-1309	400p	2SD-1500	450p
TD4184	200p	TD4680	200p	2N4589	200p	2SA1351	30p	2SC1013	600p	2SC1898	200p	2SC2552	150p	2SC3147	50p	2SC3828	120p	2SD-980	350p	2SD-1310	400p	2SD-1501	450p
TD4185	200p	TD4685	200p	2N4590	200p	2SA1352	30p	2SC1014	600p	2SC1899	200p	2SC2553	150p	2SC3148	50p	2SC3829	120p	2SD-981	350p	2SD-1311	400p	2SD-1502	450p
TD4186	200p	TD4690	200p	2N4591	200p	2SA1353	30p	2SC1015	600p	2SC1900	200p	2SC2554	150p	2SC3149	50p	2SC3830	120p	2SD-982	350p	2SD-1312	400p	2SD-1503	450p
TD4187	200p	TD4695	200p	2N4592	200p	2SA1354	30p	2SC1016	600p	2SC1901	200p	2SC2555	150p	2SC3150	50p	2SC3831	120p	2SD-983	350p	2SD-1313	400p	2SD-1504	450p
TD4188	200p	TD4700	200p	2N4593	200p	2SA1355	30p	2SC1017	600p	2SC1902	200p	2SC2556	150p	2SC3151	50p	2SC3832	120p	2SD-984	350p	2SD-1314	400p	2SD-1505	450p
TD4189	200p	TD4705	200p	2N4594	200p	2SA1356	30p	2SC1018	600p	2SC1903	200p	2SC2557	150p	2SC3152	50p	2SC3833	120p	2SD-985	350p	2SD-1315	400p	2SD-1506	450p
TD4190	200p	TD4710	200p	2N4595	200p	2SA1357	30p	2SC1019	600p	2SC1904	200p	2SC2558	150p	2SC3153	50p	2SC3834	120p	2SD-986	350p	2SD-1316	400p	2SD-1507	450p
TD4191	200p	TD4715	200p	2N4596	200p	2SA1358	30p	2SC1020	600p	2SC1905	200p	2SC2559	150p	2SC3154	50p	2SC3835	120p	2SD-987	350p	2SD-1317	400p	2SD-1508	450p
TD4192	200p	TD4720	200p	2N4597	200p	2SA1359	30p	2SC1021	600p	2SC1906	200p	2SC2560	150p	2SC3155	50p	2SC3836	120p	2SD-988	350p	2SD-1318	400p	2SD-1509	450p
TD4193	200p	TD4725	200p	2N4598	200p	2SA1360	30p	2SC1022	600p	2SC1907	200p	2SC2561	150p	2SC3156	50p	2SC3837	120p	2SD-989	350p	2SD-1319	400p	2SD-1510	450p
TD4194	200p	TD4730	200p	2N4599	200p	2SA1361	30p	2SC1023	600p	2SC1908	200p	2SC2562	150p	2SC3157	50p	2SC3838	120p	2SD-990	350p	2SD-1320	400p	2SD-1511	450p
TD4195	200p	TD4735	200p	2N4600	200p	2SA1362	30p	2SC1024	600p	2SC1909	200p	2SC2563	150p	2SC3158	50p	2SC3839	120p	2SD-991	350p	2SD-1321	400		








# PARTS PROBLEM?

For  
**Sharp**  
Sansui

Phone David Allen  
0734-876444

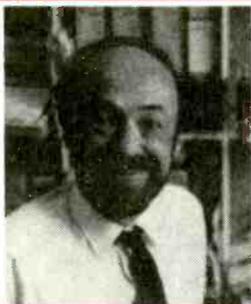

**Grundig**

Phone Stan Perkins  
0734-876444



**Philips/Pye**  
Whirlpool

Phone Frank Pratt  
0734-876444



**Ferguson**  
**GEC**  
**Fidelity**

Phone Philip Pratt  
0734-876444




**Amstrad, Akai, Fisher,  
Mitsubishi, Moulinex, Goldstar,  
JVC, Nat Panasonic, Pioneer,  
Matsui, Saisho, Samsung,  
Salora, Sanyo, Sony, Toshiba,  
Yamaha and many others.**

Phone Mike Curtis  
0602-870789



**COPS CATCHES  
THE PARTS  
THE OTHERS  
CANNOT REACH  
AT PRICES  
THE OTHERS  
CANNOT MATCH**

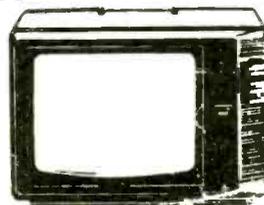VIEWDATA  
PRESTEL  
PHILIPS  
MOVIES  
*Willow Vale*  
COPS



14in SCREEN  
FULL KEYBOARD  
BUILT IN MODEM  
PRINTER PORT  
RS232 PORT  
FLOPPY DISC  
PORT  
TAPE RECORDER  
PLAYPORT  
SECURITY KEY  
SWITCH  
BRITISH MADE  
BSI APPROVED  
BT APPROVED

**RECONDITIONED  
TERMINAL**  
**£238**  
+ VAT

INTEREST FREE CREDIT  
SUBJECT TO %APR

This business terminal is a unique concept, it exploits the latest technology within a television receiver.

A microprocessor is used to guide you through a wide choice of features simply and quickly. Options are presented on the screen in the form of menus which invite you to select Teletext, Prestel or any computerised order processing facility for which you have access to, i.e. *Willow Vale COPS*, Philips MOVIES, Sharp VIEWDATA, National Panasonic, Hitachi, etc.

The system is open ended in that future facilities can be catered for in the programming of the micro-processor, such as cable TV, video disc and in house data systems.

A typewriter style keyboard is supplied and allows you full composition and editing facilities in LOCAL EDIT mode and pages of text can be transferred from the internal memory to cassette tape, to a printer, or downline at will. Clock display and timer, time out, stand by mode, security key with locking key, telephone number memory bank are all standard.

ACCESS 24 HOURS A DAY - 7 DAYS A WEEK

# NO PROBLEM




The Parts Distributor  
who says YES

HOW TO INCREASE YOUR PROFITS, IMPROVE YOUR SERVICE, WITH COST EFFECTIVE TEST EQUIPMENT.

## HAMEG OSCILLOSCOPES

HAMEG are Europe's top selling DUAL TRACE OSCILLOSCOPES. Select from four superb models. All, with the exception of the HM 1005, incorporate a useful COMPONENT TESTER. Size - all models - 285mm x 145mm x 380mm. Clear display 8cm x 10cm. Mains supply: 110/220.240V AC 50/60Hz. All supplied with 2 PROBES, a COMPREHENSIVE MANUAL and a 2 YEAR WARRANTY.

### HM203-7 20MHz STANDARD

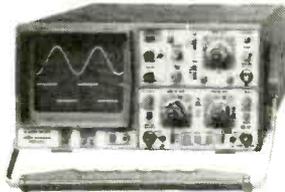


- SPECIFICATION**
- \* 2 Channels
  - \* Bandwidth: DC - 20MHz
  - \* Sens: Ch.1, Ch.2, 1mV/cm
  - \* Timebase: 0.1s - 20ns/cm
  - \* Triggering: DC - 40MHz
  - \* Active TV - Sync - Separator
  - \* Variable hold-off
  - \* Trigger LED Indicator
  - \* Calibrator: 1KHz Square wave
  - \* Component tester
  - \* Plus many features

Price £338.00 + £59.15 V.A.T. FREE Specialist Carrier Delivery

### SPECIFICATIONS


- \* 2 Channels
- \* Bandwidth: DC - 60 MHz
- \* Sens: Ch.1, Ch.2, 1mV/cm
- \* Timebase: 2.5s - 5ns/cm
- \* Triggering: DC - 80MHz
- \* Active TV - Sync - Separator
- \* After delay trigger
- \* Sweep delay
- \* Delay line
- \* Trigger LED Indicator
- \* Calibrator: 1KHz & 1MHz Sq. Wave
- \* Component tester

### HM604 60MHz UNIVERSAL

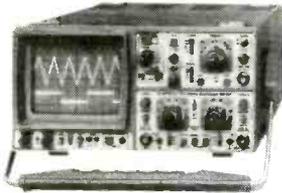

Price £610.00 + £106.75 V.A.T. FREE Specialist Carrier Delivery
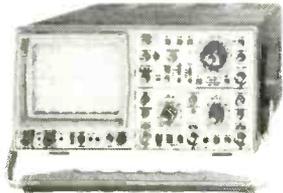
### HM1005 100MHz UNIVERSAL 3 CHANNELS - UP TO 6 TRACES




- SPECIFICATION**
- \* 3 Channels
  - \* Bandwidth: DC - 100MHz
  - \* Sens: Ch.1, Ch.2, Ch.3, 1mV/cm
  - \* Timebase A: 2.5s - 5ns/cm
  - \* Timebase B: 0.2s - 5ns/cm
  - \* Triggering DC - 130MHz
  - \* After delay trigger
  - \* Delay line
  - \* Trigger LED Indicator
  - \* Overscan LED indicator
  - \* Active TV - Sync - Separator
  - \* Calibrator: 1KHz & 1MHz Sq. Wave

Price £792.00 + £138.60 V.A.T. FREE Specialist Carrier Delivery

### HM205-3 20MHz DIGITAL STORAGE

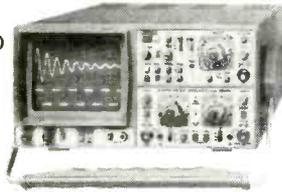
#### SPECIFICATION

- \* Digital Storage
- \* Analogue real time (Same as 203-7)
- \* Bandwidth: DC - 20MHz
- \* Sens: Ch.1, Ch.2, 1mV/cm
- \* Timebase Digital: 5s-1µs/cm
- \* Triggering DC - 40MHz
- \* Active TV - Sync - Sampling
- \* Max sampling rate: 2 x 20MHz
- \* Memory: 2 x 2048 x 8 Bit
- \* Dot joiner
- \* Printer/plotter output



Price £610.00 + £106.75 V.A.T. FREE Specialist Carrier Delivery

### B.K.'s CRT TESTER REJUVENATOR

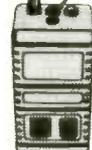

Tests and rejuvenates blue, green and red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120 x 65 x 60mm. Supply 240V AC

Price £32.00 + £5.60 V.A.T.

### DIGITAL CAPACITANCE METER

- \* High accuracy.
- \* 0.1pF-2,000µF.
- \* LCD display.
- \* 8 ranges.
- \* Accuracy +/- 0.5%.
- \* Full scale +/- 1 digit.
- \* Inc. protective case.



Price £38.00 + £6.65 V.A.T.

### LEADER FM STEREO SIGNAL GENERATOR

At last! A generator specifically designed for testing and fault finding on FM stereo and monaural VHF receivers including stereo multiplex circuits.

#### FEATURES

- \* Carrier frequency 100 +/- 1MHz (adjustable).
- \* Output level 0.1mV - 10mV.
- \* Pilot signal 19KHz +/- 2Hz.
- \* L & R separation over 50dB.
- \* External Modulation 50Hz - 15KHz.
- \* Pre-emphasis 50µs, 75µs & off.
- \* Comprehensive test lead set included.
- \* Mains powered.
- \* Size: 80 x 200 x 250mm.



Price £299.00 + £52.33 V.A.T.

### LEADER HIGH VOLTAGE METERED EHT PROBE




Light weight, easy-to-grip high-impact plastic handle with arc-over protection and no need of extra equipment. An indispensable item in your TV service kit. Measures up to 40kV DC with safety and the greatest of ease. Entirely self-contained. Connect the lead clip to chassis and probe tip to the check point, read the meter for voltage.

A must for the Health and Safety at Work Acts. Price £66.00 + £11.55 V.A.T.
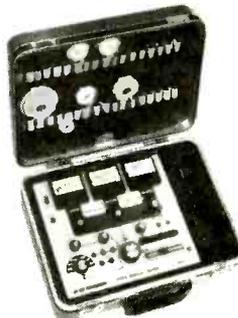
## B & K PRECISION CRT ANALYSER-RESTORER

The number one CRT Test Instrument. Over 5000 U.K. Television engineers wouldn't be without it.



\* All CRT's checked identically, including all in-line and one gun types \* Tests all three guns of colour CRT's simultaneously under actual operating conditions (model 490) \* Exclusive multiplex technique (model 490) \* Measure true dynamic beam current that actually passes through G1 aperture to screen \* Measures all shorts and leaks - preserving more CRT's \* Tests focus electrodes lead continuity finding faults that other testers miss \* Uses most powerful restoration method known with minimum danger to CRT \* Rejuvenated CRT's guaranteed as new for two years \* Obsolescence proof - perpetual set up chart updated and new adaptors developed \* Tests and rejuvenates VDU's and oscilloscope tubes \* A range of over 40 CRT base adaptors available \* Increase profit \* Pays for itself in months.

#### Prices

- Model 490 Tri-dynamic three meter instrument inc. 6 common adaptors..... £446.00 + £78.05 V.A.T. Without adaptors..... £393.00 + £68.77 V.A.T.
- Model 480 Single meter instrument inc. 6 common adaptors..... £334.00 + £58.45 V.A.T. Without adaptors..... £281.00 + £49.18 V.A.T.

## SADELTA SIGNAL STRENGTH METERS

The Sadelta Field Strength Meters have been designed to facilitate the dish alignment of satellite TV systems and aerial alignment of VHF/UHF television and radio systems. Signal levels can be accurately measured on the TC402-C and the TC90, allowing the evaluation of signal conditions for satisfactory operation. Both models have a clear LCD direct frequency readout, coupled to a multiturn tuning control enabling precise channel identification.

### TC402-C VHF & UHF

#### FEATURES

- \* Three bands:
  - Low VHF: 45-110MHz
  - High VHF: 110-300MHz
  - UHF : 470-862MHz
- \* Digital display for direct frequency readout.
- \* Built-in monitor loudspeaker AM/FM.
- \* Signal measurement from 20µV to 100mV.
- \* Powered by eight 1.5 AA batteries.
- \* Fully portable with sturdy carrying case.



Price £259.00 + £45.33 V.A.T.

### TC90 VHF-UHF- SAT.

#### FEATURES

- \* Five bands:
  - Low VHF : 45-110MHz
  - High VHF : 110-300MHz
  - Hyper VHF : 300-470MHz
  - VHF : 470-862MHz
  - Satellite : 950-1750MHz.
- \* Digital display for direct frequency readout.
- \* Signal measurement VHF/UHF 20µV to 3V.
- \* Signal measurement satellite -70dBm to -10dBm.
- \* Audible indication of satellite signal level.
- \* Built-in monitor loudspeaker AM/FM (not satellite).
- \* Powered by rechargeable battery (complete with charger 220/240V AC).
- \* Fully portable with sturdy carry case.



Price £470.00 + £82.25 V.A.T.

## BLACK STAR COLOUR PATTERN GENERATOR

### THE 'ORION' THREE-IN-ONE PAL VHF/UHF - PAL VIDEO COMPOSITE - R.G.B.

The Orion is a compact, bench instrument offering a wide range of patterns and facilities at a truly low cost.

In addition to a switchable sound carrier facility which allows use with the majority of PAL TV systems, the Orion provides highly flexible RGB outputs, ensuring compatibility with most video monitors.


More than 50 pattern combinations can be selected, including those for testing static and dynamic divergence, video amplifier linearity, colour purity, general colour performance, focus etc.

A separate video input to modulate camera signals; fully variable RF and video output levels facilitating AGC testing; trigger output allowing easy triggering of difficult oscilloscope waveforms; external sound modulation Input via DIN connector for frequency response testing of TV sound systems; adjustable wide frequency coverage of VHF and UHF TV bands.

Just some of the features making the Orion Pattern Generator an indispensable tool in the manufacture, test, and servicing of televisions, and computer and video monitors.
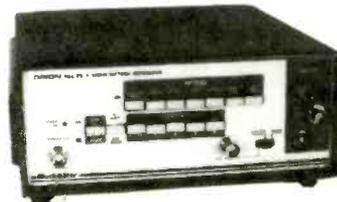
#### FEATURES

- \* Colour bars, purity, greyscale, crooshatch, dots, focus, etc.
- \* VHF/UHF Channels.
- \* 5.5MHz, 6.0MHz, 6.5MHz Sound Carriers.
- \* Internal/External Sound.
- \* External Video Output.
- \* Trigger Output.
- \* PAL B,D,G,H,I,K.
- \* Separate R, G, B and sync. O/P's.
- \* RGB @ TTL & 1V.
- \* Green + 0.3V Syncs.
- \* Composite Video Output.
- \* Variable RF/Video Output.
- \* Switchable Video Polarity.
- \* Mains powered 220/240V AC 50/60Hz.
- \* Size: 98 x 219 x 240mm.



Price £209.00 + £36.58 V.A.T.



U.K. POST PAID, export enquiries welcome. Visa/Access or cheque with order, payable B. K. Electronics. Official Orders welcome from Govt. Depts., colleges, P.L.C.s etc. Large (A5) S.A.E. for technical leaflets of complete range. Credit card orders are accepted by 'phone, fax or post. Delivery normally within seven days.



**B. K. ELECTRONICS**  
UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA  
ESSEX SS2 6TR  
Tel: 0702 - 527572 Fax: 0702 - 420243

# EURAS Information SYSTEM

The Largest Database of  
CD, TV and Video Repair  
Tips Information In Europe  
Available On-Line or in  
Books and NOW.....

## NEW Stand Alone PC Version

Purchase the Whole System or just one Manufacturer

It's Fast and Easy to use

There are no Hidden Costs

Updates available

Suitable for any IBM compatible PC

You can even enter all your own Repair tips

“No more Bits of paper”

**STILL AVAILABLE:**

**13 Major manufacturers**

**The Books**

**73,000 Repair Tips**

*Or*

**5,300 Models**

**The On-Line System**

**180 Manufacturers**

**Tel: 0272-724475**

**Fax: 0272-723374**

Euras International Limited  
Heston House  
79 Emery Road  
Brislington  
Bristol BS4 5PF  
England



# P.V. TUBES

**104 ABBEY STREET  
ACCRINGTON, LANC  
BB5 1EE**  
☎ 0254 236521/232611  
FAX 0254 395361  
**24 Hr Answering Service**  
Partners: S & B CUCKNELL

## COMPLETE SECURITY

We have a complete range of security products and sell them individually or can tailor make a package to your own requirements. E.G. this package is basic and low cost and would fit a 3 bed. house.

**COST £117.00 PACK INCLUDES**  
(Typical 3 bed house)

- ★ Two zone keyswitched panel Logic 4
  - ★ Polyprop. bell boxback platesticker
  - ★ Battery tamper switch
  - ★ External sounder
  - ★ Two passive infra red detectors
  - ★ Five pairs windowdoor contacts
  - ★ 100m 4 core cable and clips
  - ★ Internal sounder
  - ★ Buzzer for edEntry timer
  - ★ Panic button.
- TELL US YOUR NEEDS — WE DELIVER FAST

## REMOTE CONTROLS

SPECIAL OFFER PRICE — ANY ONE £12.00 — FOR THE FOLLOWING RCs:

- (a) PACE 3000/FERGUSON SRA1
- (b) PACE 6000 STEREO/FERGUSON SRA1-5/HINARU NETWORK/ALLSAT/DANSAT/INTERSAT/SEEMANS/SATEC
- (c) FERGUSON T789 FASTEXT
- (d) FERGUSON T785 FASTEXT

## ALSO NEW PRODUCT

**PROGRAMMABLE REMOTE CONTROL**  
Use for Hi-Fi, TV, Satellite, Video, in fact anything which is infra red controlled.

ONLY £27.89

## COMPUTER SPARES

We have a full range of both mechanical and electronic spares for Amiga 500 and Commodore 64 as well as most parts for Sinclair Spectrum/Spectrum Plus.

MEMBRANE 48K SPECTRUM .....	£4.50	EXTENSIVE RANGE OF ROM SPECTRUM .....	£3.50	74LS 280A CPU .....	£1.70	RAMS etc	£3.50
906114 .....	£3.50	PLEASE ASK.	6526 .....	£8.50	WE WILL TRY	901227 .....	£10.44
POWER SUPPLY UNIT .....	£28.00	COMM 64 SERVICE MANUALS .....	£15.00				

## 21" FST MULTISYSTEM TELEVISION

Will work on eleven different overseas systems. PAL/SECAM/NTSC etc. Has audio out & in and video out & in. Suitable for use as a TV outside UK as a computer monitor, with security cameras, with laser karaoke systems . . . superb value £204.00 + VAT. Service Manuals available.

## SATELLITE SYSTEMS

We can supply DISHES, RECEIVERS, LNB, FIXING BRACKETS, F CONNECTORS, CABLE, SAT FINDER METERS, CRIMPING TOOLS, TAPE, LEADS, MASTS ETC. FULL RANGE AVAILABLE AS LISTED IN CATALOGUE. PLEASE SEND LARGE SAE

## NEW VALVES

Over 2000 types available and now an exciting NEW RANGE of specialist HI-FI, PRE-AMP, and POWER VALVES.

## DEGAUSSING COILS

External Stick Type Degaussing Coil for Demagnetising £27.50

## VIDEO RABBIT

SEND VIDEO/AUDIO SIGNAL TO ANY OF THE TV SETS IN YOUR HOUSE. LIKE HAVING A VIDEO IN EVERY ROOM. TRANSMITTER AND WIRE SO THIN IT CAN HARDLY BE SEEN. ALSO WORKS FOR SATELLITE. £47.00

## TRIPLERS/LOPTX

FULL LIST IN CATALOGUE. SEND LARGE SAE PLEASE.

## BEAT THE BURGLARS

**Phantom 240 MTS and Phantom MTS Adaptor**

The Phantom 240 MTS is a passive infra red external switching device and can transmit a signal along your mains wiring hence the term 'mains transmission signalling' (MTS), without any internal wiring. The MTS Adaptor looks similar in appearance to an ordinary domestic electrical adaptor and simply plugs into any 13 amp socket in the house or premises. The unit is then able to detect the signal from the Phantom 240 MTS transmitted along the mains wiring. On receipt of the signal the MTS Adaptor will automatically switch on any appliance with a load of up to 650 Watts. This will activate 5-10 seconds after your external floodlight has come on and will go out 10 minutes later. The MTS Adaptor also has a piezo buzzer which operates day and night if an intruder enters the detection zone. The overall effect of the two units working together is to make potential burglars think you are in when you are out!!  
Beat 'em!!!

PHANTOM MTS £45.00

ADAPTOR £29.00

# BRAND NEW TVs AND VIDEOS

**BRANDED MAKE — 12 MONTHS PARTS WARRANTY — FULL SPARES BACK UP — SERVICE INFORMATION AVAILABLE — FULL BROCHURE ON REQUEST**

4.5" MONO TV WITH RADIO/CLOCK COMBINATION .....	£52.00
10" REMOTE CONTROL TV MAINS/BATTERY COLOUR TV .....	£140.00
14" REMOTE CONTROL COLOUR TV .....	£125.00
14" REMOTE CONTROL, TEXT, COLOUR TV .....	£155.00
14" MULTISYSTEM REMOTE CONTROL TV NTSC/SECAM ETC .....	£137.00
28" FST REMOTE CONTROL TEXT TWIN SPEAKERS .....	£359.00
AVAILABLE SOON 21" NICAM STEREO AND 25" NICAM STEREO AVAILABLE SOON 21" REMOTE CONTROL AND 21" TEXT REMOTE VHS VIDEO RECORDER, TWIN SPEED, REMOTE CONTROL 6 EVENT, 14 DAY TIMER, UP TO 8 HOURS .....	£169.00
VHS VIDEO PLAYER, PLAY ONLY, MAINS/BATTERY .....	£125.00

AVAILABLE AT TRADE COUNTER OPEN 6 DAYS A WEEK OR BY CARRIER NEXT DAY. DELIVERY CHARGED AT COST INCL. INSURANCE.

## TV AND FM AERIALS

SPECIAL OFFER 50 x 10 ELE AERIALS .....	£125.00
State which group	
Next day delivery	£8.50 carriage
ANTIFERRENE XG10 HIGH GAIN JHF .....	£25.00
ALSO LOW LOSS COAX FOR 5 rolls 100m .....	£35.00
METAL COAX PLUGS 100 FOR .....	£15.00
FULL RANGE OF AERIALS, MASTS, BRACKETS	
F.M. AERIALS	
5 ELE MUSHKILLERS ANTIFERRENE .....	£20.11
ALL ROUNDER OMNI DIRECTIONAL .....	£9.60
RADIO ROD (Vertical) .....	£7.99

## FILMNET DECODERS

BECAUSE OF THE DIGITISING OF SOUND ON FILMNET MANY DECODERS HAVE BEEN RENDERED USELESS. HOWEVER DO NOT THROW YOURS AWAY FOR IN APPROX. 12 WEEKS TIME WE WILL HAVE AVAILABLE DIGITAL AUDIO FOR ANY FILMNET DECODER. WATCH THIS SPACE!!  
AVAILABLE NOW FOR THE ALFASAT 1 DECODER — AN UPGRADE FOR RTL/ALSO A STAND ALONE SEPARATE RTL/ DECODER.  
END OF LINE STOCK . . . VIDEOCRYPT DECODERS AVAILABLE.  
COMPATIBLE WITH ANY SATELLITE RECEIVER £65.00 + VAT

**SPECIAL OFFER WHILE STOCKS LAST**  
AMSTRAD SRD 400  
Satellite System  
60cm Black Mesh Disc, Receiver and LNB  
**£175 + VAT**

## NEW PRODUCT

EXCITING NEW SATELLITE ACCESSORIES

DUAL OUTPUT LNB AND MULTISYSTEM AT LAST THE DUAL OUTPUT LNB IS AVAILABLE YOU CAN NOW WATCH DIFFERENT PROGRAMMES ON RECEIVERS ALL OVER THE HOUSE. EACH RECEIVER WILL THINK THAT IT HAS ITS OWN DISH.  
DUAL OUTPUT LNB £87.00  
FOUR-WAY MULTISWITCH £27.00  
1.2ohm LNB — THIS BRAND NEW LNB HAS BEEN DESIGNED AS A DIRECT REPLACEMENT FOR THE BLUE CAP LNB £45.00  
ALSO AVAILABLE 60cm AMSTRAD BLACK MESH DISH WITH LNB (i.e. NO RECEIVER) £75.00

FULL RANGE OF COMPLETE VIDEO SERVICE KITS — PLEASE RING FOR CROSS REFERENCE ON MANY MAKES AND FOR PRICES. BOTH GENUINE TYPES AND ECONOMY VERSIONS AVAILABLE.

WE CAN'T LIST EVERYTHING THAT WE STOCK. OUR RANGE IS EXTENSIVE. WE HAVE A TRADE CATALOGUE ON REQUEST. WE ARE ALSO ON LINE WITH "MOVIES" TO ORDER ANY PHILIPS

PART QUICKLY. JUST SOME OF THE THINGS WE SELL:  
AERIALS, BRACKETS, BATTERIES, CABLE CONNECTORS, CMOS CAPACITORS, COMPUTER ACCESSORIES, DISCS, DIODES, ELECTRICAL ACCESS FUSES, ICS, LOPTX, LEADS, MANUALS, PUSH BUTTON UNITS, PHONES, PHONE ACCESS, POTENTIOMETERS, RELAYS, SEMICONDUCTORS, STRIPBOARD, STYLE SMOKE DETECTORS, SWITCHES, TUNERS, TV BATTERY LEADS, TV WALL BRACKETS, TOOLS, TEST EQUIPMENT, VALVES AND EVERYTHING YOU NEED FOR VIDEO REPAIRS — HEADS, IDLERS, TYRES, PINCH ROLLERS, CLEANERS, TEST CASSETTES, VIDEO TAPE (inc. BETA and V2000) etc.

## SPECIAL OFFERS

EUROBELL SECURITY BELLS	9.50
LEADS 3.5mm JACK TO 2 PHONES	0.40
METAL CROCODILE CLIPS RS N0423 021 Pk20	2.00
3HS5 VIDEO HEAD HITACHI VT4000/2005000/5500	13.50
4 WAY EXTENSION BR LEAD WITH PLUG (13A)	4.00
4 WAY TRAILING SOCKET WITH NEON (13A)	2.50

## NEW — LOUSPEAKER BRACKETS

MINOR 50 UP TO 5KG	6.33 per pair
BEK 100 UP TO 25KG	12.30 per pair
QUO 220 CLAMPING BRACKET	18.05 per pair



HOW TO ORDER: Up to 1K ADD £1.00 per order P+P (U.K.)  
Heavier parcels e.g. cable, service aids, degaussing coils please allow £3.25 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 17.5% VAT to total except where it states zero rate. Over 3K will be sent by carrier £10.00 + VAT up to 25K (except tubes). We do not despatch on Saturdays



**TRADE COUNTER OPEN**  
MON-FRI 9am-5pm  
SAT 9am-4pm

## THERE IS VAT ON P+P.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. VAT invoice on request. Give us a ring — we'll give you service. Please ask if what you need is not listed — we'll try to help. Prices are subject to change without notice. In some cases we may have to supply an equivalent. We need expiry dates for credit card orders. MIN ORDER £5.

## BOOKS & MANUALS ARE ZERO VAT

# LRC SPARES

**TEL 071-323 2107  
FAX 071-323 2191**  
3-5 WHITFIELD STREET  
LONDON W1P 5RA

## OCTOBER SPECIAL OFFERS

CLE825 & CLE 826 ORIGINAL HITACHI REMOTE CONTROL (SEE PHOTOS IN JUNE ISSUE) £10.00  
FV21R ORIGINAL FERGUSON LCD REMOTE CONTROL SUITABLE FOR MANY FERGUSON AND JVC VCR'S £20.00  
IR100R PROGRAMMABLE REMOTE CONTROL 124 COMMANDS POSSIBLE £17.40  
NP77 ORIGINAL SONY CAMCORDER BATTERY PACK £33.15  
5458282 ORIGINAL HITACHI VIDEO HEAD VT4000/4200/5000/5030/5500 £10.00  
UNIVERSAL CASS MOTORS 6V & 9V CLOCKWISE, 12V CLOCKWISE & 12V ANTI-CLOCKWISE £3.70

**WE CARRY A FULL RANGE OF ORIGINAL AND REPLACEMENT VIDEO SPARES FOR MOST BRANDS AT VERY COMPETITIVE PRICES**

DEALING WITH LRC IS EASY AND VERY PLEASANT. FILL IN AND SEND THE FORM BELOW FOR AN INSTANT CREDIT ACCOUNT

## PLEASE ANSWER ALL QUESTIONS IN BLOCK CAPITALS

1) DATE .....

2) COMPANY NAME .....

TYPE OF COMPANY (EG. LTD, PARTNERSHIP, SOLE TRADER) .....

3) FULL ADDRESS (INC POST CODE) .....

4) TELEPHONE (INC STD CODE) .....

5) COMPANY HAS BEEN TRADING SINCE .....

6) YOUR FULL NAME .....

POSITION .....

7) FULL NAMES ANY OTHER DIRECTORS, PARTNERS, ETC

1 .....

2 .....

3 .....

8) NAME AND ADDRESS OF COMPANY'S BANKERS (INC. POST CODE) .....

BRANCH SORT CODE .....

ACCOUNT NUMBER .....

**PLEASE ATTACH SPECIMEN OF LETTERHEAD OR ORDER FORM.**



**ORDERS BEFORE 4.009 PM — SAME DAY DESPATCH**  
**ALL LIST PRICES ARE EX-VAT**

Orders Under £10.00 (Ex VAT) Please Add £2.50 Handling then VAT  
Orders Under £25.00 (Ex VAT) Please Add £1.50 Handling then VAT  
Orders Over £25.00 Free Despatch





# EAST CORNWALL COMPONENTS



SEND FOR OUR 1991/92 CATALOGUE — 132 FULL PAGES £2.00

119 HIGH STREET DEPT.TV9 WEM SHROPSHIRE SY4 5TT TEL: 0939 32689 FAX: 0939 33800

FULL RANGE OF ECONOMY ELECTRONIC KITS — ALSO VELLERMAN KITS — SEE OUR CATALOGUE

## OCTOBER — SPECIAL OFFER

YUASA Sealed Lead Acid Battery



**SUPER PRICE!**  
6V, 10AH for £10.50  
Two for £19.00  
  
12V 24AH for £35.00  
Two for £60.00

Max Initial Charge Current	CHARGE VOLTAGE		Number Of Cells
	Cyclic	Standby	
2.5A	2.5V/cell	2.3V/cell	6
6.0A	7.5	6.9	3
	15	13.8	6

YUASA CODE	DIMENSIONS		
	H	W	D
NP 10-6	101	x	151
NP 24-12B	125	x	166

### QUARTZ-HALOGEN SPOTLIGHT

THIS UNIT SUBJECT TO DESIGN CHANGE Hand held or hanging. Heat resistant polycarbonate housing; highly polished reflector. Protective lens cover doubles as base stand. With On/Off switch and 12ft curly cable terminating in cigar lighter plug. Produces 250,000 candle power — 5 times the intensity of average car headlamps. Power 12Vdc. 4.5A 55W Dims: 160 x 88 x 110mm



Price £5.75

### "CLOSED CIRCUIT TELEVISION SYSTEM

1 x CAMERA BRACKET £120  
1 x CAMERA £75  
USED 1 x MONITOR TOGETHER (Plus £10.00 carriage) £7.75  
**PRICE: £185**

BT APPROVED	
Master Socket (Flush)	£3.30
Master Socket (Surface)	£3.25
Secondary Socket (Flush)	£2.25
Secondary Socket (Surface)	£2.15
B.T. Cable (per metre)	15p
15 199M 4 CORE	£12.00
15 199M 6 CORE	£17.00
Line Jack Cord with Plug	£2.20
Extn. Lead 5 metres	£2.75

**HOME ALARM PACKAGE**  
Includes:  
\* Optima Alarm Control Panel  
\* External Feed Bell Box  
\* 2 x 1 Internal Passive I/R  
\* 2 x Door Contacts  
\* Siren for Bell Box  
\* 100 mtrs cable and clips  
\* Full fitting instructions  
**ONLY £130.00**  
\* BACK UP LEAD ACID BATTERY 12V 1.9 £14.00

FULL RANGE OF BABANI BOOKS IN OUR CATALOGUE

**FM KIT** For those of you who enjoy building kits — we now offer the above transmitter in kit form ideal for the beginner — supplied complete with full, easy to follow instructions. Box NOT INCLUDED — See our BOXES Section for suitable housing.  
**PRICE: £7.50**

**FM TRANSMITTER** Made in U.K. Very high quality Mini-Bug — ideal for baby alarm etc! A very good range, is obtainable — we have obtained over 1/2 mile, but it does depend on conditions. Simply remove cover — insert battery — and you're ready to go. Reception can be obtained on any FM radio Frequency: 87.5-109MHz FM.  
**PRICE: £9.99**

**SOLDER 18 & 22 SWG -500gm REEL**

18swg	1+	£4.95	10+	£47.70
22	1+	£4.99	10+	£47.75

Remember. Our prices INC. VAT

**COMPUTER GRADE CAPACITORS** 4700uF 100V  
Max Ripple 8.4 at 100Hz + 85 C  
DIMS: 115 x 50mm  
List price is over £14 each!!  
Reliability, not for fun.

1+	£3.50
10+	£3.00

ORDER CODE: SOICOMG

**C.D. PLAYER G060 (CDP 10)**  
\* 3-beam semi-conductor laser  
\* 6 track programmable memory  
\* Repeat one — repeat all facility  
\* Built-in 3" disc adaptor  
\* Track search and index

System Compact disc digital audio system  
Optical pick-up 3-beam semi-conductor laser  
Error correction CIRC  
Sampling frequency 41.1KHz  
D/A conversion 16-bit linear  
Filter Digital filter + active filter  
Frequency response 20-20000Hz  
Harmonic distortion < 0.09%  
S/N ratio > 80dB  
Channel separation > 70dB  
Max. output voltage 2Vrms  
Dims 350 x 90 x 290mm

**£99**

**B.S.R. TURNABLES**  
We have just taken delivery of another large quantity of B.S.R. Turnables, which this time are mounted on a plinth, finished in black. They really look good. Plinth is 1/2" chipboard for easy drilling etc. Supplied complete with cartridge & stylus, and drive belt.  
Motor Rating 12V 0.6EA  
Plastic arm, speed selector, 33/45 rpm.  
Complete with arm lift lever.



**COMPONENT SPEAKER SYSTEM B020 (TC6500) PRICE £25.75**  
2 x 3-way component speaker system comprising two 6.5 woofers, two 4 mid-range, two 2.25 tweeters and all leads, filters and fixing screws.  
Finished in black with black mesh grilles.  
Maximum power 60W/side  
Frequency response 60-20000Hz  
Speaker sizes 6.5 woofer, 4 mid-range, 2.25 tweeter  
Impedance 4Ω

**RESISTOR KITS — each value individually packed**

1/4W pack 10 each value E12 — 10R to 1M 610 pieces	5.10
1/4W pack 5 each value E12 — 10R to 1M 305 pieces	3.75
1/4W pack Popular — 10R to 10M 1000 pieces	6.99
1/2W pack 10 each value E12 — 2R2 to 2M2 730 pieces	8.75
1/2W pack 5 each value E12 — 2R2 to 2M2 365 pieces	5.40
1/2W pack Popular — 2R2 to 10M 1000 pieces	10.75
1W pack 5 each value E12 — 2R2 to 1M 365 pieces	15.25
2W pack 5 each value E12 — 10R to 2M2 317 pieces	25.00

**ADDITIONAL KITS**

DISC CERAMIC 50V	125 pieces	£3.99
ZENER DIODES Sea	55 pieces	£3.99
ELECTROLYTIC CAPS: RADIAL	100 pieces	£8.50
FUSES 0.5 BLOW 20mm	60 pieces	£4.75
FUSES 1 DELAY 20mm	80 pieces	£8.50
PRE-SET POTIS Hor	120 pieces	£7.75
PRE-SET POTIS Vert	120 pieces	£7.75
POLYESTER 100V	110 pieces	£5.00
NUT & BOLT	800 pieces	£5.99

P.O.A.

**NI-CAD RECHARGEABLE BATTERIES** PRICE EACH  
1+ 10+  
AAA £0.95 £1.30  
AA £0.95 £0.85  
C £1.95 £1.80  
D £2.00 £1.85  
PP3 £3.90 £3.75

**NI-CAD CHARGER** Charges AAA, AA, C, D & PP3 Ni-Cads  
**£4.99**

**ORDER 100 AA NI-CADS AND PAY £6.70 EACH incl. VAT**

**20mm Quick Blow FUSES**  
QUICK BLOW - 80mA, 100, 125, 160, 200, 250, 315, 400, 500, 630, 800, 1A, 1.25, 1.5, 1.6, 2, 2.25, 3, 3.15, 4, 5, 6, 3 A  
TIME DELAY - 50mA, 80, 100, 125, 160, 200, 250, 315, 400, 500, 630, 800, 1A, 1.25, 1.5, 1.6, 2, 2.25, 3, 3.15, 4, 5, 6, 3 A

**14" QUICK BLOW FUSES**  
500Ma, 1A, 1.25A, 2A, 12A

**AUTOMATIC LIGHT SWITCH** Plug-in light switch which turns on (table lamps, radios, etc.) up to 500W (max.) when the ambient light level falls below a pre-set level, switching off again when the light level rises.  
Power 220/240V ac  
50Hz  
Dims: 145 x 65 x 42mm  
**£11.50**

**CINE/VIDEO CONVERTER** Cine/video converter designed to transfer cine film or projector slides to video tape. The image from the projector is transferred to a high contrast screen where it can then be picked up by video camera with micro capability. Sound is added later. Adjustable height.  
Dims: 205 x 145 x 153mm  
**£15.75**

### FULL RANGE OF VIDEO BELT KITS — See our Catalogue

FULL RANGE OF CASSETTE PLAYER DRIVE BELTS  
19-57mm 25p, 60-94mm 29p

TURNABLE DRIVE BELTS: 121-710 Dmm £1.99  
CASSETTE DRIVE BELTS: 68-70mm £4.5p  
81-95mm 50p  
CASSETTE DRIVE BELTS (Walkman type) 30p

**TRIPLERS**  
Universal Philips - KT3 VID/TIC1 £6.65  
VID/TXT38 £8.35

**CASSETTE LAPPE SERVICE MANUALS**  
UNIVERSAL SONY SL-C5 6 7  
High quality 12 Volt FERGUSON VHSTJ1  
Universal Video Cassette 3V00 HR3330EK  
Recorder Lamp and Head. Lead length: FERGUSON VHSTJ1  
Approx. 30cm 3V22 HR3320EK  
ORDER CODE: VID LAMP ALL £8.00 EACH

**MOTORS**

Description	Order	Price
AUDIO 12V CW 5mm Shaft	VID 2107	5.90
12V CW 5mm Shaft	VID 2103	6.25
12V CW 7mm Shaft	VID 2105	6.85
12V CW 7mm Shaft	VID 2106	6.85
12V CW 10mm Shaft	VID 2114	4.00
9V CW 10mm Shaft	VID 2115	4.90
9V CW 10mm Shaft	VID 2107	5.45
SHARP Reel VC300 9100	VID 2122	22.00
Reel VC483H	VID 2122	22.00
Loading S3 93 8700	VID 2142	21.60
Capstan VC3100 9300	VID 2155	45.45
Drum VC200 9300 9500	VID 2154	7.00
Reel VIC-510	VID 2123	7.15
Reel Beta M10-50	VID 2192	36.00
Reel HR1200 1300	VID 2191	36.00
Capstan SL-261 ES	VID 2163	10.00
Drum BH 1100D	VID 2184	65.00
Capstan PU45979	VID 2194	35.00
Drum HR3300 3330	VID 2120	18.00
Reel HR7700	VID 2108	10.00
Capstan HR7700	VID 2163	95.00
Reel HR220 2650	VID 2175	78.00
Capstan HR2650	VID 2176	50.00
Reel SV23	VID 2168	10.00
Capstan SV23	VID 2163	95.00
Capstan 3V35 36 38 39	VID 2163	95.00
Load 3V42-48 54 55	VID 2167	75.00
Capstan 2V4 4.45 46 54	VID 2186	75.00
Capstan VT-5000	VID 2143	10.00
Capstan VT-5000	VID 2149	75.00
Capstan VT-8000 8500	VID 2157	65.00
Capstan VT-3300 8500	VID 2158	30.00
Drum VT-5000 5500	VID 2154	75.00
Reel NV333 366	VID 2152	70.00
Reel NV7000E	VID 2153	10.00

NAT PAN CW Clockwise CCW Anticlockwise

**TWIN FLUORESCENT LAMP — 12V**  
A very attractive twin tube lamp holder with two 12V 9W fluorescent tubes. White plastic case with plastic ribbed diffuser and ON/OFF switch. Supplied with 90cms of twin flex for connection to 12V battery. (Red stripe to positive) Ideal for caravans, boats, vans etc.  
Overall dimensions: 370 x 65 x 41mm  
ORDER CODE: Dpto/TFL12

**PORTABLE FLUORESCENT LAMP — 12V**  
Free-standing or hanging with 1.1m cable terminating in cigar lighter plug. For use in car, boat, van or home emergency. 370 x 65 x 41mm  
ORDER CODE: Dpto/FL12

**SPARE TUBES 8W**  
Replacement tube for above Twin and Single fluorescent lamps. Fits most 12V fluorescent lamps. Philips etc. Tube length: approx 300mm (inc pins).  
ORDER CODE: Dpto Tube £1.50 ea 10 for £12

**8 WAY SPLITTER**  
8 way splitter amplifier to supply 8 TV's from one antenna. White plastic box with aluminium panel. On/Off switch with neon indicator.  
Gain: 20dB  
Band width: 30dB per channel. 200-810MHz  
Impedance: 75Ω  
Max output (signal/noise modulation): 6dB  
Noise: 40dB min.  
Isolation between outputs: 40dB min.  
Power: 240Vac 50Hz  
Dims: 250 x 100 x 60mm  
**£29.99**

**AERIAL ROTATOR**  
Automatic antenna rotator controlled remotely to give rise, easy, rapid and economical aerial redirection. Ideal for TV or FM radio aerials where best signals come from different sources. Comprises two major components, the control unit and the rotator. Provides excellent performance with optimum signal achieved by dialling the exact antenna direction. Black controller and gold coloured cast metal rotator. Full instructions and mounting hardware supplied.  
Rotation time: 365 with mechanical stop  
Rotation time: 65 seconds  
Torque: 220kg-cm  
Max. load: 45kg (100 lbs)  
Motor voltage: 240Vac 50Hz  
Input power: 240Vac 40VA  
Dims: Controller 180 x 150 x 80mm  
Rotator 290 x 150 x 120mm  
**£46.50 £40.00**

### FULL RANGE OF VIDEO REPAIR KITS

REMOTE CONTROLS	P.O.A.	DAF
AKAI VP-77 88 7100 V51 2 3 5 10	VID 2511	15.85
VS77 9300 9100 9700 9800	VID 2511	15.85
FERGUSON 3V00 3V21 3V29	VID 2511	15.85
3V18 3V22 3V23 3V24 3V30 3V31	VID 2511	15.85
3V35 3V36 3V38 3V39 8903	VID 2647	15.85
HITACHI VT11 VT14 VT33	VID 2504	28.20
VT3000	VID 2511	15.85
VT4000 4200 5000	VID 2503	29.15
VT6500 7000 8090 V&8000 8500	VID 2509	28.20
9000 9300 9500 9700 9900	VID 2509	28.20
JVC HRD 110E 110E 111 120 121 225	VID 2647	15.85
2200 3680 7600 7610 7650 7700 7647	VID 2511	15.85
HR3300 4100 7200	VID 2511	15.85
N.E.C. N830 831 833	VID 2647	15.85
PC9 2300 2400	VID 2543	23.00
NATIONAL PANASONIC NV100 370 380	VID 2526	18.50
NV121 333	VID 2520	15.85
VEH124 NV366	VID 2521	46.75
NV740	VID 2528	47.85
SANYO VTCS000	VID 2530	34.00
SHARP VC200 300 330	VID 2536	28.65
VC381 481	VID 2537	29.75
VC581 583	VID 2539	29.95
VC83 485	VID 2541	49.00
SONY SL C5 C6 C7	VID 2546	21.60
SL C9	VID 2544	44.15
SL C20 C24 C30	VID 2545	27.75
SL R8000	VID 2543	23.00
TOSHIBA VS470 5480	VID 2547	32.75
VR660	VID 2548	29.50
VT381 8385	VID 2597	24.95

**PINIC ROLLERS**

AKAI 1EG 2E4G 5EG 5EG 6EG 9EG SC15EG	£3.45
VS7700	£4.85
FERGUSON 3V00 3V24	£3.45
3V29 3V32	£4.45
HITACHI ALH	£3.45
JVC HR2000 3000 3300 3660 4100 7700	£3.45
N.E.C. N830 N833	£3.30
ORION VHS 1 2	£2.45
PANASONIC NV100 180 332 333 366	£3.45
600K 777 778	£3.45
2000 2300 3000 370 430	£3.45
460 465 7000 7200 730	£3.45
780 810 8200 830 8400	£3.45
850 8600 8610 870 890	£3.45
PHILIPS VR 6460	£3.45
VR 6560	£3.95
SANYO VTCS000	£3.45
VTCS000 510 530 530 5350 5400 5500 6000	£3.45
6500 9100 9300 m10 11 20 21 30 31	£3.45
SHARP 200 282 384 385 386 388	£3.45
390 3300 2300 6000 6200	£3.45
6300 7300 7700 7750 9000	£3.45
8300 9300 9500 9700	£3.45
SONY SL-C5 6 7	£6.00
TOSHIBA VL5	£3.30

**VIDEO HEAD TESTER**  
A VHS video head tester for determining whether a video head is in good condition by detecting the wear state and displaying it on a meter. Complete with carrying case and leads.  
**PRICE £40.35**


**SATELLITE CABLE BRITISH MADE WHITE**  
A REEL 100 metre roll  
**£15.00**

**SCART ADAPTOR (T113Z (2XSC))**  
Start plug to two Scart sockets. For coupling together three pieces of audio/video equipment with Scart sockets.  
**£9.99**

ORDERING: All components are brand new and to full specification. Please add £2.00 postage/packing (unless otherwise specified) to all orders. Minimum order £5.00. Either send cheque/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges etc most welcome. (Do not forget to send for our catalogue - only £1.50 per copy). Delivery by return on ex-stock items. All prices subject to change without notice. WEM RETAIL shop open Mon-Thur 9.00-5.30. Friday 9.00-5.00. REMEMBER ALL PRICES INCLUDE VAT.

VISIT VISIT VISIT  
MARCO TRADING THE MALTINGS HIGH ST WEM SY4 5ET Tel: 0939 32763  
SUPERTRONICS 86 HIGH STREET BIRMINGHAM B5 4TE Tel: 01 666 6504  
WALTONS 55A WORCESTER ST WOLVERHAMPTON WV2 4LL Tel: 0902 22039

**p&p NOW £2.25**

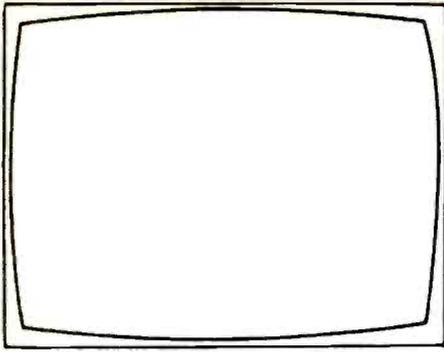

# TELEVISION

## Over at Last?

The recession of 1990/1 has turned out to be one of the most exasperating on record. First we were told that it wasn't going to be. Then that it would be a comparatively mild affair. Then, through the period from late last year to the middle of this year, it took a real hold and turned out to be one of the deepest recessions since the war. It has been devastating for many small firms – and many not so small ones. In the second quarter of this year the number of business failures was 82 per cent higher than a year ago: some 1,970 firms are on record as having failed. We've now reached the point however where commentators are beginning to suggest that it's at last at an end. The Bank of England has talked of "bumping along the bottom"; the Organisation for Economic Co-operation and Development suggests that the "worst of the recession may be over"; the National Institute of Economic and Social Research speaks of a "slow and hesitant" recovery; while the Confederation of British Industry reports "widespread if modest optimism throughout British Industry". The Treasury and, of course, the government have been making optimistic noises, and commentators are now beginning to concern themselves with assessing exactly when the upturn will be, how strong it will be, and how lasting.

We're not wanting for advice and comment! Yet those who monitor events and issue forecasts have a very poor record. You'd think, with all the effort that's gone into the subject in recent years, that forecasters, including the Treasury and the Bank of England, would by now be rather better at it. Yet they keep getting caught out. Badly. It's of course difficult if you are using old figures and economic models, with only the past to act as a guide to an uncertain future. Maybe we should all ignore the economic forecasters. Yet it's their views and assessments that lead to interest rates hikes and, subsequently, all those business failures. One could make out an excuse for the forecasters by saying that economic activity in the UK since the mid-Eighties has been exceptionally volatile. It's relatively easy in hindsight to see what happened and what went wrong. Harder to suggest how things could have been managed better.

The history of recent economic events in the UK starts with deregulation of the banking system in the early Eighties. It was felt that the banks were a sort of cosy cartel and were not making their full contribution to the economy. Deregulate them, let others – the building societies, Continental banks and associated newcomers – compete with the major banks and all should be better. Well, at least we get some interest on our current accounts now. And yes the banks did respond and in consequence lent money hand over fist to all and sundry with few questions asked. Bank managers were ordered to increase their lending since if they didn't the business would go elsewhere. There was another mechanism that came into operation in the late Eighties and helped matters to get out of hand. Excessive lending led to excessively rising asset values – in particular rocketing house prices. This then provided the collateral for further lending. The whole thing began to bubble over and threatened to lead to collapse. Eventually the government, which had been slow to cotton on to what was happening, largely because of all those misleading forecasters, was forced to act. But following deregulation it had virtually no means of doing so save a savage hoist in interest rates. This works – eventually. Lowering interest rates takes a long time to have any appreciable effect and, as we saw late last year and earlier this year, raising them does too. There's an analogy about pulling a brick across a tabletop using a piece of elastic. Nothing happens for a long time, then wham!

We've now had our period of repressive interest rates and the recession they eventually created. We've heard all about the light at the end of the tunnel – it's been a rather long tunnel though. But at last there have been some genuine signs of reviving confidence. And confidence is the basis of economic activity in a market economy. Without it people stop buying and ordering. Businesses start to run down their stocks rather than replace them. Banks get edgy as bad debts mount and then start to curtail new lending and call in old. There was talk a few months ago of the possibility of economic collapse because of banks' unwillingness to make new loans. At the time that seemed to be a rather excessively pessimistic view. It may have been a major contributor to the depression in the early Thirties, but some lessons at least have been learnt since then. However that may be there comes a time when borrowing falls or is stabilised, savings rise and people start to think about new ventures and new purchases. It's this that gets things started again.

If the CBI is right about reviving confidence we should be grateful. It's a good sign: the CBI has been rather more accurate in its assessments and forecasts than more academically based organisations. It seems unlikely that we shall experience another full-bodied boom of the type we had in the late Eighties: too many people burnt their fingers. The question that is now being asked is whether the excesses that followed deregulation were a once-off adjustment to a new situation?

The effect of the recession on the radio and TV trade has been a curious one. As a result of market saturation, conditions in the consumer electronics field were already soft before the recession started. What the latter has done is to delay any uplift, despite the advent of new products like satellite TV. There are a lot of new products in the pipeline: if they come along at a time of renewed consumer confidence there will be good business to be done.

### EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 849 or faxed to 081-661 8965.

### EDITORIAL ASSISTANT

Tessa Winford

### ADVERTISEMENT MANAGER

Jan Thorpe  
081-661 8114

### DISPLAY SALES MANAGER

Shona Finnie  
081-661 8115

### CLASSIFIED ADVERTISEMENTS

Pat Bunce  
081-661 8339  
Fax 081-661 8956

### ADVERTISING ADMINISTRATION

Kathy Lambart  
081-661 8116

### ADVERTISING PRODUCTION

Brian Chapman  
081-661 8681  
Fax 081-661 8917

### SUBSCRIPTION ENQUIRIES

0444 440 421

### PUBLISHER

Robert Marcus  
081-661 3930



**REED BUSINESS  
PUBLISHING  
GROUP**

# VCR Plus

George Cole

Many people have problems with VCR timers. Users complain that programming systems are over complex, with the result that the wrong programme at the wrong time is recorded – or the VCR fails to record anything at all. Some users simply ignore the timer, or leave programming to the resident “timer expert” (often the youngest member of the household). A fair number of service calls for “faults” are simply the result of incorrect programming.

It's fair to say that many timers seem to be more suitable for use by computer programmers than ordinary members of the public. In recent years however various companies have developed new, simpler systems. Examples are Panasonic's bar-code programming, Akai's on-screen displays, Hitachi's LCD remote programming and the teletext-based systems. There are even talking handsets (Sharp) that guide the user through the programming sequence. Despite these innovations, research carried out by Ferguson revealed that a third of adults have problems with setting the timer: some in the trade feel that the figure is much higher.

A new system called VCR Plus could make programming as simple as making a phone call. It was developed by a US company, Gemstar, and was launched in the USA last November. Since then it has sold remarkably well.

VCR Plus consists of a handset that looks like a basic VCR remote control unit and Plus codes. The latter are four- or five-digit numbers that are printed next to the TV programme details in newspapers and TV guides. The VCR Plus handset contains its own timer. To set this the user simply punches in the Plus code number. The handset is then left in sight of the VCR. At the relevant time it sends an IR command to the VCR to tell it to switch on. The Plus Codes contain details of the programme's date and time, the channel number and also the stop time. Thus the handset is able to switch the VCR off once the recording has been made. An alternative arrangement, adopted by Thomson for its US models, is to incorporate the VCR Plus system in the VCR and use a simplified handset to control it.

The Plus codes are now included in over a hundred newspapers and magazines in the USA. A VCR Plus handset costs around £37 there.

The system is to be launched in the UK this autumn or early next year. *TV Times* has already signed up with Gemstar to publish Plus codes. Meanwhile Gemstar is developing the handset to suit UK and European requirements – for example American date displays show the month first, then the day, while the US system has a heavy emphasis on cable channels.

The VCR Plus handsets are powered by four AA batteries, with in addition a lithium battery that acts as a backup. Layout of the handset (see the accompanying photograph) is clear and neat, with large keys and an LC display panel. Current handsets can store up to 14 events, which is more than most VCRs offer. It seems that the handsets store a number of IR command codes, enabling them to be used with the majority of remote-control VCRs.

Installation will be very straightforward if the instructions for the US handsets are anything to go by. A pull-up

flap at the top conceals eight buttons. To set up the unit a table of two-digit installation codes printed at the back of the instruction book is first consulted. One of these should match the VCR make – for example Panasonic is 03, Sony 13. The VCR is set to channel three or four and is then switched off. Pointing the VCR Plus handset at the VCR and pressing the enter button transmits a test code to it. If the VCR switches on and turns to channel nine the save button is pressed and the system is installed. If nothing happens you try other codes. The next procedure is to set the clock.

The LC display tells you the date and time and provides programming details. It uses time bars – a series of dashes – to tell the user how much tape is required to record a particular programme. Each dash represents an hour or less. There's also a low-battery indication. Another indication is a warning of programme clash – when programmes overlap. In this event the user can opt to cancel one of the programmes or instruct the VCR Plus to tell the VCR to record the first programme to the end then switch over to the second one. The system will record a programme once, daily or weekly.

Other handy features include a review button that lets you check your programming and a cancel button. The recording time can be extended by pressing a button that continues the recording after the preset stop time: it works in increments of a quarter of an hour and is useful for programmes that tend to overrun, such as sports events.


Once the user has entered the Plus codes he requires, the handset is placed in its caddy pointing at the VCR – the system will work at a range of up to fifteen feet. As the system in its usual form is independent of the clock in the VCR, mains failure doesn't affect its operation.

When recording is about to start, a small red light at the end of the handset flashes to provide a reminder to load a blank tape.

United Media is acting as Gemstar's European agent. Price of the handsets in the UK is expected to be around £50. The system's simplicity could make it a winner. Though it doesn't have the advantage of the teletext-based PDC (programme delivery control) system, which identifies the programmes rather than their scheduled times, it's easier to use. The only problem is that the public is likely to be confused by the multiplicity of systems on offer, especially now that PDC has been given yet another name, Startex – which is all right so long as you realise that it's start-tex and not star-tex . . .



The VCR Plus handset in its caddy.

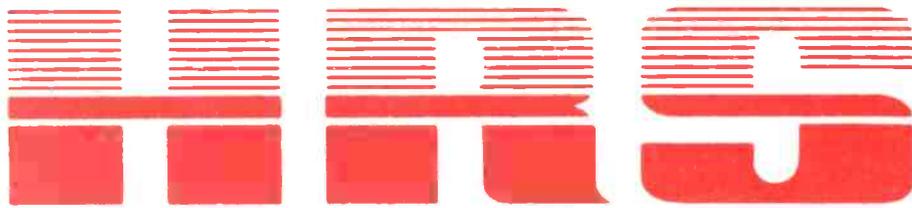

. . . *servicing the future*

**IT'S HERE!!**

**THE NEW  
1991/92  
HRS CATALOGUE**

**IT'S HERE!!**



- \* OVER 600 PAGES CRAM PACKED WITH EVERYTHING FOR THE SERVICE, RETAIL AND COMMUNICATIONS TRADE
- \* OVER 220 PAGES IN FULL COLOUR
- \* SECTION INDEX FOR QUICK AND EASY REFERENCE
- \* HUNDREDS OF NEW PRODUCTS
- \* THOUSANDS OF ILLUSTRATIONS TO HELP YOU IDENTIFY THE PRODUCT MORE EASILY

**TO ARRANGE YOUR COPY AND A VISIT  
FROM YOUR LOCAL REPRESENTATIVE**

**PHONE 021-789-7575**

*freefax 0800 212 179*



**HRS ELECTRONICS PLC  
GARRETT'S GREEN LANE, BIRMINGHAM B33 0UE  
PHONE: 021-789 7575 TELEX: 339992 FAX: 021-789 8040**

# Teletopics

## PHILIPS' LINKS

A joint venture, D2B Systems, set up by Philips and Matsushita to pool electronics standardisation know-how has been given provisional approval by the EC Commission. The two companies had asked the Commission a year ago for exemption from EC competition rules. In its initial finding the Commission states that though the venture limits competition it will yield technological advances and benefit consumers. It has taken a "favourable position" but asks for comments from others. The venture is 75 per cent owned by Philips, 25 per cent by Matsushita.

Meanwhile Philips and Sony have been holding talks on cross-licensing their new audio recording systems – the Philips DCC and Sony Mini Disc. Both are due to be launched next year.

## TV SETS

Ferguson has decided to postpone the launch of its 16:9 wide-screen TV set that was demonstrated at the trade shows earlier this year. It was expected to be launched this autumn at a price of around £3,500. Launch will now be early next year. Ferguson puts the blame for the delay on the continuing recession.

Grundig launched two 16:9 sets at the Berlin Funkaustellung. The 36in. model is fitted with a conventional tube while the 46in. model uses a projection system. Both models are due for launch in the UK this month, the smaller-screen one at a price of around £3,000 and the projection set at around £5,000.

Ferguson has added a 10in. colour portable, Model A10R, to its range. It's fitted with the new TX80 chassis (see Teletopics August). Features include 40-programme direct access tuning, on-screen graphics, child lock and a menu control system that provides simple operation via the remote control handset. A sleep timer puts the set into standby half an hour after pressing a button and provides auto switch-off that's variable between a quarter of an hour and two hours. A 12V battery adaptor and an optional swivel bracket for mounting the set under shelves or cupboards are available.

The latest addition to the JVC range, Model AV25FX11, features a 25in. Blackline Invar-mask tube, colour transient improvement and video noise reduction circuitry, simulated surround and Nicam sound, comprehensive on-screen menus, Fastext, an S-video socket, 100 station presets and the ability to detect 16:9 MAC/D-MAC signals and display them letterbox style. Suggested price is £729.

## SATELLITE TV

The latest satellite TV receiver packages from Amstrad feature a dual-output LNB than enables the user to run two receivers from a single dish.

Electronic Mailorder, 62 Bridge Street, Ramsbottom, Bury, Lancs has introduced a tunable satellite audio module that enables more radio stations, including the ITN news channel and many pop stations, to be received. It can be fixed to the front, back or side of a satellite TV receiver with only three connections being required. Price is £18 in kit form, £24 assembled, plus £1 post and packing.

BSkyB is actively monitoring the promotion of pirate Filmnet decoders and will withdraw Authorised Sky Agent

status from any dealers who continue to sell, advertise or display these decoders. BSB is at present losing £1.6m a week, a dramatic reduction on the losses being made at the time of the Sky/BSB merger.

A booklet entitled *A Householder's Planning Guide for the Installation of Satellite Television Dishes* is available from the Department of the Environment, PO Box 135, Bradford, West Yorkshire BD9 4HU.

## TRADE NEWS

Pace Micro Technology Ltd. has appointed CPC plc, 180-200 North Road, Preston PR1 1YP (0772 555 034) official spares distributor for Pace satellite receivers. Pace is the largest satellite receiver manufacturer in Europe – total production has now passed the half million mark.

Spares for ITT products continue to be available from Hoopwell Ltd., Unit B9, Larkfield Trading Estate, Larkfield, Maidstone, Kent ME20 6SW (0622 882 285) – but not for current in-guarantee ITT Nokia products. A new, expanded catalogue is in preparation.

Two firms are in talks with Loewe Opta on the distribution of spares in the UK.

Pioneer is moving production of stereo radio tuners from Belgium to its new plant in Wakefield, West Yorkshire. The plant will also make CD players.

## DEVELOPMENTS

The BBC held the first UK demonstration of its Digital Audio Broadcasting (DAB) system in Birmingham at the end of July. DAB offers CD quality reception from simple push-button radios at home or on the move and is highly efficient in frequency use – up to twelve stereo radio channels occupy the space normally taken by just two. A coach was used to demonstrate the ruggedness of the system in a city-centre environment. The BBC has been carrying out research on DAB for several years.

A method of transmitting full-colour pictures from one PC to another via the cellular radio network has been developed by software company Origin Technology in Business, Redhill, Surrey. Transmission takes less than half a minute. The technique is based on a fractal transform process – the transmitting PC scans the picture looking for parts that are the same as images held in memory. When identification is made the system transmits the formula representing the pattern, not the pattern itself. The formula is compressed for transmission. Special software is required for decoding at the receiver end. Since this requires little memory space it can be sent along with the picture.

Panasonic has opened an R and D centre at Langen, Germany. Its main activities will be to gather information on the standardisation of TV specifications and to undertake research into European HD-TV systems.

## VIDEO NEWS

Sony has launched three new Video 8 camcorders. Model CCD-F455 has a ×8 zoom and costs £800; Model CCD-F555 at £900 has a ×10 zoom and hi-fi stereo sound; Model CCD-V600 at £1,000 has Hi-8 picture quality, hi-fi stereo sound and a ×8 zoom.

Philips has introduced a low-price, three-head VHS VCR at £299, Model VR312. Features include remote control, a one month/six event timer, still frame and slow motion. Also from Philips comes a portable TV/VHS recorder, Model PVR200, at £1,000. Features include a PAL I and B/G tuner, a 24-hour timer and a 4in. LCD screen. Weight is 3.9kg including batteries.

Ferguson's new budget-priced VCR, Model FV50B at

around £279, features remote control, a one year/eight event timer, four-speed variable picture search, assemble edit control and a full digital servo system.

### NEW PUBLICATIONS

Various new publications from Mauritron Technical Services, 8 Cherry Tree Road, Chinnor, Oxfordshire OX9 4QY (0844 51694) should make life easier in the service department. They include books containing VCR equivalents listings, TV models/chassis listings and trade addresses. The latter includes TV, video, test equipment and computer firms and is revised and reprinted approximately every three months.

Infotech, 76 Church Street, Larkhall, Lanarkshire ML9 1HE (0698 883 334) has available a wide range of practical VCR fault-finding guides. The latest, by John Coombes, covers the Panasonic 700 series. The company also publishes TV/Audio/Radio repair and servicing yearbooks that contain numerous adjustment details and fault lists for particular models/chassis. They are intended for use with the company's large-scale circuit diagram collections.

Tandy's 1991/2 electronics catalogue is now available

free of charge from over 500 Tandy stores and authorised dealers throughout the UK. There are 135 full-colour pages featuring 2,400 products of which 380 are new.

### PHILIPS' LATEST PATTERN GENERATOR

Philips Test and Measurement, Colonial Way, Watford, Herts WD2 4TT (0923 240 511) has introduced a new top-of-the-range TV pattern generator that offers just about every feature likely to be required for testing the latest TV sets, monitors and VCRs, including those with Nicam and teletext facilities. The PM5518TNI even has an optional built-in IEEE interface to allow its outputs to be selected remotely with IEEE-based automated test systems. There are over seventy patterns, including special test patterns for VCRs, teletext and video programming. Up to 55 different sound test signals are available for Nicam stereo, standard f.m. stereo and dual/mono sound channels. An RGB option is available. The 5518 is a multi-standard generator for use with PAL, SECAM and NTSC systems.

All PM5515/5518 teletext versions now offer extended test facilities with a selection of teletext pages including standard, FLOF, TOP, VPT and VPS.

## CD Player Casebook

Reports from Mike Leach and Philip Blundell, AMIEE

### Philips CD104

This player wouldn't read discs. When a disc was loaded it immediately span very fast and wouldn't stop. The laser whistled a bit and the error light on the front panel came on. I started by checking the earth-through connections on the servo and decoder panels, but for once they were all in order. My next checks were on the supplies, but again everything was o.k.

I then noticed that the turntable span fiercely with no disc inserted. This was a good indication that the fault lay somewhere in the turntable motor servo or its associated circuits. Voltage checks were made around the MC1458 chip IC6209 on the servo board: this chip, along with transistors 6233 and 6234, provide the turntable motor drive. Apart from the supplies most of the voltages were incorrect. When I moved back to the LM339 chip IC6205 I found that the voltages were again wrong. With a working machine pin 13 should be at 0V in the stop mode and at 4V when play is selected. It was high at 4.6V in the stop mode and fell to 2.1V when play was selected. As a result the turntable servo became unstable, causing the reported fault. A new LM339 chip cured the problem. The machine then performed quite well – all that was now needed was a quick laser lens clean and a soak test for possible intermittencies with regard to those earth-through connections. **M.I.**

### Goodmans GCD550 Multiplay

This player first came in about a year ago. The trouble seemed to be quite straightforward. When the disc magazine was inserted and the play button was pressed a very loud rattling noise could be heard as the disc tried to load. Fortunately the disc wasn't damaged, but it sounded as if the mechanism was suffering. I found that the magazine would load all right if pressure was applied to the top of the mechanism. After much stripping down, with modifications and grease everywhere, I gave up and used a complete mechanism from a scrap machine (cheat!). The customer was happy however and so was I. The machine

worked correctly for many months then a few weeks ago came back again. The note on the job ticket suggested that the fault symptom was the same as before. Sure enough the player rattled fiercely while trying to load a disc.

My first thought was that the cause of the trouble was to do with the magazine itself, but the same thing happened with a different one. So that ruled the magazine out. When the disc loading motor, on the left-hand side, has been removed you can turn the feeding gear by hand. At the point where the disc is loaded into the mechanism the gear became very tight and started to slip against the feeding rack. I lifted the feeding gear from the chassis at this point, exposing the rack. The teeth on both were badly worn and it was this that caused failure of the disc to load and the rattling. The part numbers are as follows: feeding rack 21W8135, feeding gear 21W8141. **M.L.**

### Denon DCD800

This machine read the TOC all right and played the first few tracks normally. Occasionally however it would skip and jump at the outer edge of the disc. With many players this fault is often caused by a worn or faulty laser unit. Turntable motor problems or mechanical failure are other causes. Not this time though. As with all cases of tracking problems I went through the setting-up procedure. The PLL adjustment was slightly off: correcting this cured the tracking problem with all discs. This is a fault condition I've not come across before. **M.L.**

### Philips CD350

This machine wouldn't read the TOC. Focus was obtained and the h.f. signal was present, but the disc rotated much too fast. The motor control signal (MCES) should be present even in standby. In this case it was missing. Checks around the SAA7020 chip showed that the chassis pin (38) was at 5V. The earth return is via C2362's negative lead, which is soldered on both sides of the board. Not in this case however – there was a dry-joint on the underside. **P.B.**

# Adding a Scart Connector

K. Wevill, B.Sc.

The scart connector is nowadays a standard fitting in most current TV sets, satellite TV receivers and VCRs, enabling video and audio signals to be fed in and taken out directly instead of having to go through a u.h.f. modulation/demodulation process. This results in improved quality and permits RGB inputs and stereo sound, both inputs and outputs, to be used. RGB inputs enable a TV set to be employed as a computer monitor or, with a MAC decoder, to obtain better resolution than is possible with a composite PAL signal, with no cross-colour effects. The stereo audio outputs can be used with an external stereo amplifier or hi-fi system.

The interface described in this article enables many older TV chassis, without video and audio input or output facilities, to be fitted with a scart connector. It was designed primarily for chassis that use a TDA2540 i.f. chip, a TDA1035 intercarrier sound/audio chip and a TDA3560 PAL decoder chip. It could however be adapted for use with chassis that employ similar i.c.s. The chassis with which it was developed was an ITT CVC800. Examples of other chassis that use the same chips are the Ferguson TX9 and TX10: these are equally suitable for the modifications described here.

Fig. 2 shows the scart connector, which is also known as a Peritel connector or Euroconnector. The signal levels and impedances expected at each pin are listed in Table 1. The function switching, blanking and RGB signals are inputs with a TV set and outputs with a VCR, computer or satellite receiver. As yet the communication lines are undefined.

## Safety

The most important aspect of the modification process is to ensure that the TV chassis used is isolated from the mains. Many chassis that are suitable for the modification have a non-isolated switch-mode power supply and a bridge rectifier that's fed straight from the mains supply. This means that the chassis will be live at all times, irrespective of which way the mains plug is wired. To overcome the problem, an isolating transformer must be used. It must be a toroidal type, as this has a negligible external magnetic field and thus avoids magnetic interference to the c.r.t. The transformer should be rated to cope with the TV set's power requirements: 120VA is adequate for the TX9 and CVC800 chassis and should be suitable for most, but it's as well to check the set's power consumption before obtaining the transformer. Transformers rated at 80VA and 120VA are available from Jaytee Electronic Services, 143 Reculver Road, Herne Bay, Kent CT6 6PL. Many modern TV chassis are designed with mains isolation in mind and thus don't call for the use of an isolation transformer. Examples are the Ferguson TX10 and TX100.

## Mode of Operation

Fig. 1 shows a block diagram of the interface, which consists of a video input amplifier, a video output buffer, a stereo audio switch, audio output buffers, RGB interfacing and switching circuits.

The external TV composite video (CVBS) signal is fed to

the video input amplifier which has a gain of 2.5 times. Its output is similar to that produced by a TDA2540 i.f. chip. The video output (CVBS) is taken from the same point, making loop-through of the video signal possible.

The audio circuit is a little more complex, as the inputs and outputs are stereo while the set's internal audio amplifier is mono. In the internal off-air mode audio from the intercarrier sound i.f. section is fed via the input buffer and two of the switches in IC1 (4053) to the left and right output buffers. When the external mode is selected, the left and right input buffers are fed with left and right inputs via the switching. The left and right inputs are also summed and fed to the TV set's internal audio amplifier as a mono signal. Thus if a stereo signal from for example a stereo VCR is fed into the interface the TV set's output will be in mono but the stereo signals will also be available to feed to an external hi-fi system. There's provision to adjust the signal levels to and from the TV audio amplifier to maintain the same volume control settings for both internal and external use.

The RGB inputs go straight through to the TDA3560 PAL decoder chip along with the fast blanking input. Note that when RGB inputs are used a sync signal must be provided and fed into the external video (CVBS) input, otherwise the picture will be unlocked.

Switching between internal and external signal sources is achieved by using one or more of three methods: (1) control by pin 8 of the scart socket; (2) control by external switching; (3) control from the channel selector.

When the internal mode is selected, the video amplifier is turned off and the external input to the TV audio

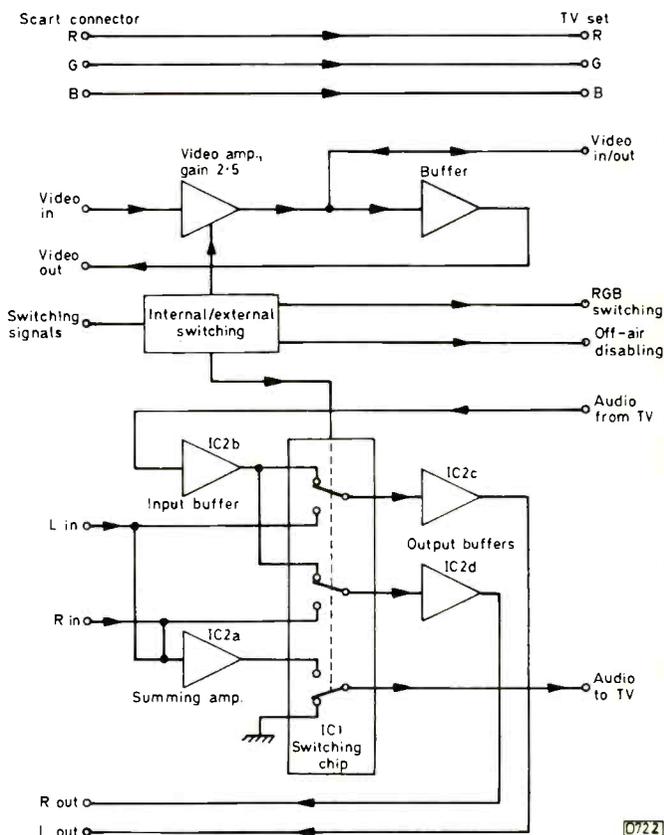


Fig. 1: Block diagram of the Scart interface system.

# MANOR SUPPLIES

MKV PAL COLOUR TEST GENERATOR  
FOR DOMESTIC TV & VCR.

TEST  
DEMONSTRATIONS  
AT 172  
WEST END LANE



- ★ 40 different patterns and variations.
- ★ Fully interlaced sync pulses with correct picture blanking
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black
- ★ Chequerboard
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£75.00**  
Case (10" x 6" x 2 1/4") app **£15.00**  
Optional Sound Module (6MHz or 5.5MHz) **£3.90**  
Built & Tested in Case including Sound Module **£122.00**  
Post/Packing **£3.50**  
Add VAT 17.5% TO ALL PRICES

## PAL COLOUR BAR GENERATOR (Mk4)

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.
- ★ Backup service available.

PRICE OF MK4 COLOUR BAR GENERATOR KIT **£35.00. CASE £5.80. BATT HOLDERS £4.20**

**MAINS SUPPLY KIT £5.80**  
(Combined P&P £3.50)

VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£6.80.**  
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD  
VAT  
17.5%

## LINE OUTPUT TRANSFORMER TESTER

- ★ Saves time and money.
- ★ Checks short turns.
- ★ Simple to use
- ★ Reliable.
- ★ Battery operated.
- ★ Pocket size.

ADD  
VAT  
17.5%

**PRICE £20.00**  
POST/PACKING **£2.50**

## KITS AND PROJECTS

SAW IF AND TUNER UNIT complete and tested for video & audio outputs **£28.50** p.p. **£1.80.**

PAL DECODER KIT (Video to RGB) for Monitors **£27.00** p.p. **£1.80.**

PAL ENCODER KIT (RGB to Video) **£18.50** p.p. **£1.80.**

CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator. Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£15.00** p.p. **80p.** (Alum. Case **£6.00** p.p. **£1.40.**) **ADDITIONAL GREY SCALE Kit £3.50** p.p. **£1.80.**

UHF SIGNAL STRENGTH METER KIT **£30.00** Alum. Case **£6.00.** De Luxe Case **£12.00** (Built & Tested **£58.00**) p.p. **£3.50.**

CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with Case, Panel Meter Indicator - can be adapted for latest CRTs **£40.00** p.p. **£3.00.**

# TV & VIDEO SPARES

## TELETEXT PANELS

GEC/HITACHI — PC174A-4 **£10.00**  
GFC — C2285, C2287, Text Conversion Kit **£15.00**  
ITT — Compact B, D & Mono Print 13, 14" 20" Text Conversion Kit **£15.00**  
MULLARD VM6103 **£10.00**  
POST PACKING FOR ABOVE **£2.50**

## PHILIPS SPARES

GII 6 POS touch tune channel selector (replaces old type) **£14.00** p.p. **£1.80**  
MANUALS 2B, C1\*0 **£3.50.** CTX-E, CTX-S, CF1 **£2.50.** KT4,  
K40, 3A **£4.50** 2A **£10.50.** p.p. MANUALS **£1.80**  
BACK UP BATTI. 2.4V **£3.80.** 1.2V **£2.60** p.p. **80p.**  
K30, KT4, CTX-EHT Lead **£3.20** p.p. **£1.00.**

## THORN/FERGUSON SPARES

9000 Series IF/Decoder tested **£10.00** p.p. **£2.80.**  
TX10 Focus control **£8.50** p.p. **£1.00.**  
TX9/TX10 Saw filter IF panel **£5.00** p.p. **80p.**  
TX9/TX10 Remote & tuning 1515N **£5.00** p.p. **£1.80.**  
TX9/TX10 Remote & tuning 1508A (incl. SAA5012) **£2.50** p.p. **£1.80.**  
TX9/TX10 Remote & tuning 1536 (incl. SAA5012, SL471) **£3.50** p.p. **£1.80.**  
TX10 Stereo Audio Board **£3.50** p.p. **£1.80.**  
TX90 Mains TX **£23.00** p.p. **£2.80.**  
TX100 Chopper TX **£22.80** p.p. **£2.50.**

## IC SELECTION

AN5521	£3.80	SAA5030	£6.80	STR6020	£5.80	TD2579	£3.80	TD2654	£3.20
AN5901	£2.20	SAA5040	£6.80	TA7680AP	£5.80	TD2581	£2.20	TD2658	£2.80
BA6238A	£4.80	SAA5050	£11.80	TA7681P	£5.80	TD2582	£2.80	TD2660	£3.80
CN602	£4.80	SAA5231	£5.80	TA7688P	£6.80	TD2593	£1.50	TD2661A	£1.50
HA11211	£2.80	SAB3035	£6.80	TBA120	£1.20	TD2594	£3.80	TD2662A	£13.50
HA11423	£2.10	SAB3037	£15.80	TBA750	£2.20	TD2595	£4.80	TD2663	£5.80
HA51338SP	£11.80	SAE1032	£4.50	TBA920	£2.20	TD2600	£6.80	TD2664	£6.80
LA4445	£3.00	SAF1039	£2.20	TBA950	£2.20	TD2611A	£1.90	TD2665	£3.80
LA7801	£1.80	SL470471	£4.00	TCA270	£1.80	TD2640	£3.20	TD2666	£2.80
LA7520	£7.20	SL486	£6.80	TCA800	£6.80	TD2653A	£3.20	TD2667	£6.80
LA7801	£3.50	SL490	£3.80	TD103ST	£2.40	TD2654	£5.70	TD2668	£5.80
LA7830	£2.80	SL1430	£1.80	TD1037	£1.90	TD2655B	£8.60	TD2669	£2.80
M293B1	£7.80	SL1432	£1.40	TD1044	£2.90	TD2670	£3.20	TD2670	£7.80
M3901B1	£14.80	SN76226DN	£1.80	TD1082	£4.80	TD2680	£3.80	TD2680	£6.80
M4910B1	£9.80	SN76705	£9.80	TD1170	£2.20	TD2690	£3.80	TD2681	£6.80
N494	£9.80	STR5325	£6.80	TD1180	£2.20	TD2780	£6.80	TD2682	£3.80
MC1302P	£5.80	STR5332	£6.80	TD1190Z	£2.20	TD2790	£4.20	TD2683	£3.80
MDA2061	£4.40	STR5338	£6.80	TD1432P	£5.70	TD2830	£6.80	TD2684	£4.80
MDA2062	£3.80	STR5339	£6.80	TD1470	£2.80	TD2830	£6.80	TD2685	£2.20
ML237	£3.80	STR5421	£6.80	TD1670A	£3.20	TD2830	£6.80	TD2686	£3.80
ML238	£6.80	STR5422	£8.50	TD1701	£3.80	TD2830	£6.80	TD2687	£3.80
ML926	£4.80	STR5471	£6.80	TD1770	£3.20	TD2830	£6.80	TD2688	£2.20
NIN15425	£14.50	STR5481	£7.80	TD1870	£6.80	TD2830	£6.80	TD2689	£3.80
SAA1024	£5.80	STR5482	£6.80	TD1908	£2.80	TD2830	£6.80	TD2690	£3.80
SAA1025	£5.80	STR7308	£6.80	TD1940	£3.20	TD2830	£6.80	TD2691	£3.80
SAA1124	£3.50	STR7348	£10.80	TD1950	£3.50	TD2830	£6.80	TD2692	£3.80
SAA1250	£3.80	STR441	£7.80	TD2040	£7.80	TD2830	£6.80	TD2693	£3.80
SAA1251	£8.40	STR450	£6.80	TD2150	£3.20	TD2830	£6.80	TD2694	£3.80
SAA1292	£13.20	STR451	£5.80	TD2270	£2.80	TD2830	£6.80	TD2695	£1.80
SAA1293.02	£8.80	STR454	£5.80	TD2510	£6.80	TD2830	£6.80	TD2696	£3.80
SAA3027	£5.80	STR4211	£6.80	TD2548	£5.80	TD2830	£6.80	TD2697	£1.80
SAA5000	£2.80	STR5412	£5.80	TD2576A	£3.80	TD2830	£6.80	TD2698	£6.80
SAA5010	£5.80	STR50103	£4.50	TD2577	£4.80	TD2830	£6.80	TD2699	£4.95
SAA5012	£5.80	STR54041	£10.80	TD2577A	£4.80	TD2830	£6.80	TD2700	£1.90
SAA5020	£5.80	STR58041	£8.50	TD2578	£3.80	TD2830	£6.80	TD2701	£3.80

IC p.p. 90p

VARICAP TUNERS: Grundig 860 series **£5.50** p.p. **£1.00.** U321, U322/U341N, ELC1043 (equiv), SC4, VHF NSF203 **£7.80** p.p. **£1.80.** UHF/VHF UV411 **£10.80.** U343 **£10.80** p.p. **£1.00.**

## LINE OUTPUT TRANSFORMERS

BUSH T20, T22	£9.80	LOEWE Classic M124, M27	£33.00
DECCA 80, 100	£8.80	LOEWE Contur M27	£33.00
FIDELITY ZX2000, CTV140	£15.50	LOEWE Other (Quote model No.)	£21.80
FIDELITY ZX3000	£14.50	PHILIPS 321	£2.80
HINARI C14, C15	£24.80	PHILIPS G8	£8.80
HITACHI CPT1455, 1456, 1476, 1491	£28.80	PHILIPS G9	£12.80
HITACHI CPT174, 767, 778	£28.80	PHILIPS K73	£13.80
HITACHI P/N2433752	£29.80	PHILIPS K80	£31.80
ITT Compact B, 110	£19.80	PHILIPS TXE-E S	£24.80
ITT Compact 80, 110	£17.80	PHILIPS K74, 40	£22.40
ITT Compact 80, 90P	£22.80	PHILIPS 2A	£23.80
ITT Compact 80, 110P EST	£19.80	PHILIPS 3A, 2B	£23.80
ITT CVC 201	£9.80	PHILIPS C11	£32.80
ITT CVC 25, 30, 32	£10.80	PYE T31, 741	£9.20
ITT CVC 45	£9.80	SAISHOMATSU 3714002	£32.80
ITT CVC 800, 801, 803	£24.00	SANYO T1732, 80P Chassis	£39.80
ITT CVC 1100, 1200, Picos	£18.50	SONY KV1882	£34.50
ITT CVC 1150, 1175	£22.80	SONY KV2026	£34.50
ITT CVC 1201, 1201, Mini 2	£18.50	SONY KV2704	£60.00
ITT CVC 1314	£11.50	THORN 1590, 91, 1612, 13, 1712	£4.80
ITT CVC 1210/1215/17	£17.80	THORN 1690, 1691	£9.80
ITT Digi 3, 110P	£19.80	THORN 3757 (NORIMENDE)	£9.80
ITT Core 110P, 90P	£19.80	THORN 9000, 9600	£9.80
ITT Core 110P EST	£19.95	THORN TX10 (Chopper)	£16.50
ITT TX3267	£22.80	THORN TX85	£19.80
ITT TX446	£22.80	THORN TX90 14"	£19.80
ITT Monomont A	£21.80	THORN TX90 20"	£21.80
LOPTS p.p. £1.80		THORN TX100, 110P Green Spot	£19.80
ITT Core 110P EST	£19.95	THORN TX100 90P EST Yellow Spot	£21.80
		POST PACKING LOPTS	£1.80

TRIPLEX: THORN 9000 **£9.80** p.p. **£1.50.**  
UNIVERSAL (best quality) **£7.80** p.p. **£1.50.**  
CONTINENTAL TVK & BG RANGE (quote exact no.) replacements **£13.80**  
DECCA/TATUNG **£7.80** p.p. **£1.50.**  
6.3V CRT Boost Transformers for Colour & Mono **£6.80** p.p. **£1.40.**  
455 CRYSTALS for Remote Control Handsets. 4 for **£1.00** p.p. **50p.**  
AERIAL DISTRIBUTION AMP. 6 way **£35.00** p.p. **£2.80.**  
VHF to UHF Converters **£35.00** p.p. **£2.50.**  
DEGAUSSING ROD **£33.75** p.p. **£2.80.**  
TRANSPARENT SERVICE CASSETTE **£6.80** p.p. **£1.80.**

HOW TO ORDER: ADD p&p TO ORDER + VAT 17.5% TO THE TOTAL  
PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

Telephone 071-794 8751, 794 7346  
Fax 071-431 5778



**MANOR SUPPLIES**

172 WEST END LANE, LONDON NW6 1SD



amplifier is earthed to avoid interference problems.

In the external mode the i.f. amplifier and intercarrier sound i.f. are disabled to avoid interference problems. The time-constant for the line sync is also changed. The audio and video output buffers remain active in both modes. RGB switching is normally done by the fast blanking input at pin 16 of the scart connector, but a switch is provided to override this if no such signal is available.

## Circuit Description

Fig. 3 shows the full circuit of the scart interface. The video input amplifier consists of TR3/4, with TR5 forming the output buffer. The amplifier is switched on and off by TR2 which either connects or disconnects the bias to TR3.

Audio switching is done by IC1, which is a triple, two-way CMOS switch. IC2c/d are the output buffers, IC2a is the summing amplifier/buffer that generates the mono signal for the set's internal audio amplifier while IC2b acts as a buffer for the internal audio signal from the intercarrier sound circuit. Use of these two input buffers enables the signal levels to be altered easily to match the internal and external signal levels. To alter the output level, increase the value of R30 to raise the level or decrease its value to reduce the level. Alter the value of R29 similarly to increase or decrease the volume from the TV set's loudspeaker. The levels should be such that the volume is the same in both the internal and external modes.

Switching between the internal and external mode is achieved by TR1/2. When the external input is required,

either pin 8 of the scart socket is taken to 12V or switch SW1 is set to the Ext position (12V). This switches TR1 and in turn TR2 on, enabling the video input amplifier. The i.f. amplifier is turned off by taking pin 14 of the TDA2540 chip low via D6, while the TDA1035's intercarrier section is turned off by taking pin 2 high via D7 and R21. The line generator chip's time-constant is changed by applying 12V to the selector pin via D8.

The RGB inputs are much easier to implement, as the TDA3560 PAL decoder chip is designed to accept analogue RGB video signals – these inputs are normally used for teletext. RGB selection is done by setting the blanking signal input to 5V. The RGB inputs must be a.c. coupled: C1/2/3 and the terminating resistors R1/2/3 are included for this purpose. Some TV chassis may already have these components fitted, or there may be provision to incorporate them. In this case they need not be fitted on the interface PCB.

## Construction

Construction is not unduly critical – the circuit can be built on Veroboard. The leads to the video amplifier should be kept short however. It's best to use a socket for IC1 as this is a CMOS device. Fit it after all the other components. Layout depends on the space available for the interface and which of the facilities are required. For example it's not necessary to include the RGB interface if this is not required or the set's colour decoder chip has no provision for RGB inputs.

## Interfacing with the Set

The interface circuit requires a 12V supply, which can usually be obtained from the PAL decoder supply or some other convenient point in the set. The video input/output must be connected to the TDA2540 chip's output (pin 12) after the intercarrier sound take-off point. In many sets this is contained within an i.f. module, so connection can be made at the module's video output pin.

With the Ferguson TX9 and TX10 chassis the relevant point is pin 8 of the i.f. module, at PL4: in the ITT CVC800 it's at pin 23 of the tuner/i.f. module.

The i.f. disable output is connected to pin 14 of the TDA2540 chip, via the a.g.c. time-constant circuit. With the TX9/10, make the connection at pin 9 of PL4; with the CVC800, make it at pin 22 of the i.f. module.

If there's no module, make the connections to the TDA2540's video output (pin 12) after the intercarrier sound take-off and to pin 14 (i.f. disable) via a 100Ω resistor.

Audio input and output connections to the TDA1035 chip are made at pins 7 and 3 respectively. In some versions of the TX9 pin 3 is available at PL21. In others and in the CVC800 pin 3 is connected to chassis. In this case the PCB track will have to be cut and a 4.7kΩ resistor and 10nF capacitor in parallel will have to be added between pin 3 and chassis.

The a.f. disable can be connected directly to pin 2 of the TDA1035 or, if the chip is in a module, as in the CVC800, the connection can be made to the relevant module pin (29 with the CVC800).

With other chassis check the circuit diagram for suitable points to connect the interface.

Connect the AV time-constant line to the line generator chip's VCR select input. The pin to use depends on the chip. With the CVC800 it's available at TC6. In the TX9 it's at PL23. An alternative point is the set's VCR time-

Table 1: Scart pin connections.

Pin Function	Level/impedance
1 R audio out	0.5V/<1kΩ
2 R audio in	0.5V/>10kΩ
3 L audio out	0.5V/<1kΩ
4 Audio earth	–
5 B video earth	–
6 L audio in	0.5V/>10kΩ
7 B video in	0.7V/75Ω
8 Source switching	Internal mode 0-2V, external mode 9.5-12V/ >10kΩ
9 G video earth	–
10 Communication data 2	–
11 G video in	0.7V/75Ω
12 Communication data 1	–
13 R video earth	–
14 Communication data earth	–
15 R video in	0.7V/75Ω
16 Blanking	Composite video source 0V-0.4V; ext. RGB 1-3V/75Ω
17 Composite video earth	–
18 Blanking earth	–
19 Composite video (CVBS) out	1V/75Ω
20 Composite video (CVBS) in	1V/75Ω
21 Common earth (shell)	–


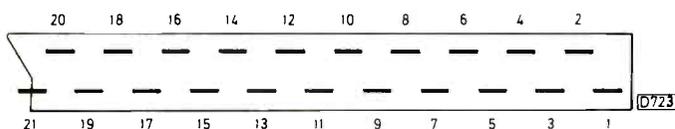


Fig. 2: Scart connector pin layout.

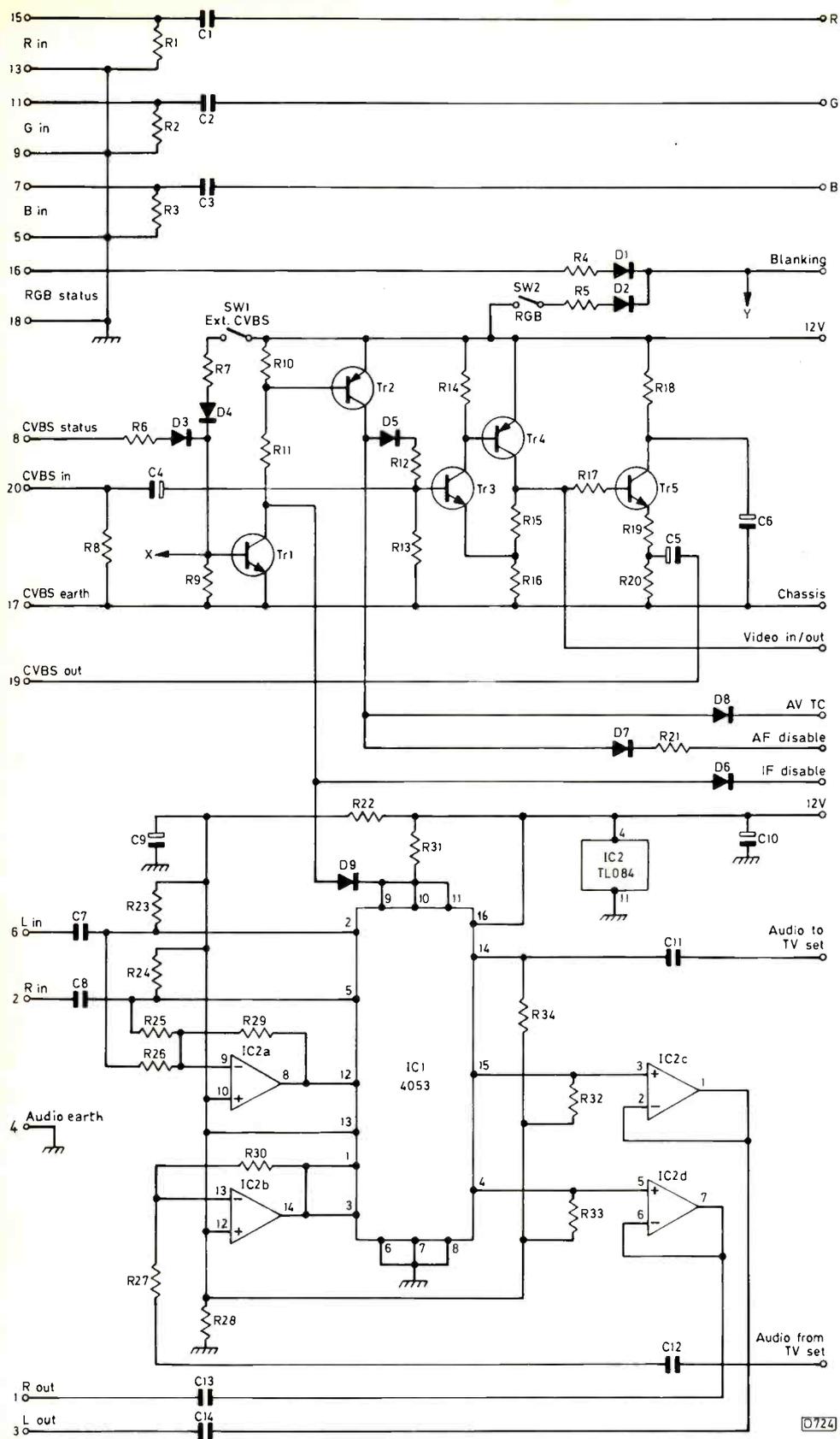

## Components list

<b>Resistors:</b>	R18	100Ω	
R1	82Ω	R19	68Ω
R2	82Ω	R20	220Ω
R3	82Ω	R21	18k
R4	100Ω	R22	4.7k
R5	680Ω	R23	100k
R6	12k	R24	100k
R7	12k	R25	100k
R8	75Ω	R26	100k
R9	10k	R27	100k
R10	15k	R28	4.7k
R11	47k	R29	100k
R12	8.2k	R30	100k
R13	2.7k	R31	47k
R14	5.6k	R32	1M
R15	1.5k	R33	1M
R16	1k	R34	1M
R17	100Ω		All 0-25W

<b>Capacitors:</b>	C1	100n	
C2	100n	C3	100n
C4	47μF 16V	C5	220μF 16V
C6	22μF 16V	C7	220n
C8	220n	C9	22μF 16V
C10	47μF 16V	C11	220n
C12	220n	C13	470n
C14	470n		

<b>Semiconductor devices:</b>	D1-9	All 1N4148	
IC1	4053	IC2	TL084
Tr1	BC548	Tr2	BC558
Tr3	BC548	Tr4	BC558

<b>Remote control interface:</b>	R35	100	
R36	10k	R37	10k
D10-12	1N4148	IC3	4028
Tr6	BC548		
	Resistors	0-25W	

**Miscellaneous:**  
Scart connector, i.c. socket, Veroboard. Toroidal isolating transformer.

Fig. 3: Circuit diagram of the Scart interface system.

constant control line, usually found on the channel selector or the remote control receiver/decoder.

## Installation

The first step in carrying out the installation is to fit the isolation transformer (where required). Space can be found in most sets. Keep it as far as possible from the c.r.t. Some experimentation to find the best compromise

position will usually be necessary, and a bracket may have to be made to fix it in place. In most sets it can be wired up immediately after the mains on/off switch, but in chassis with a remote control system that uses a relay to switch the set on and off the transformer should be wired after the relay contacts. The TX9 is an example of the former arrangement, the CVC800 an example of the latter. Ensure that the position chosen doesn't cause any magnetic interference to the c.r.t.

Once the position of the transformer has been decided, find a suitable place to fit the scart connector and the interface board. It will be necessary to make up a bracket to support the connector, the switches and the board and to cut a hole in the case. The board and connector should be mounted close together, with the connections to the TV circuitry kept as short as possible. Use screened cable for the audio leads.

### Remote Control

It's possible to control the interface switching from the TV set's remote control system, where fitted. This can be done without affecting the normal off-air channel selection as many systems are actually capable of 16-channel operation but use only eight. If this is the case, connect the four channel select outputs A, B, C and D to a 4028 decoder chip as shown in Fig. 4. Also connect the D output to the D input of the channel number display decoder. This input is usually earthed, so the track may have to be cut. Output 8 of the 4028 is connected to the base of TR1 via

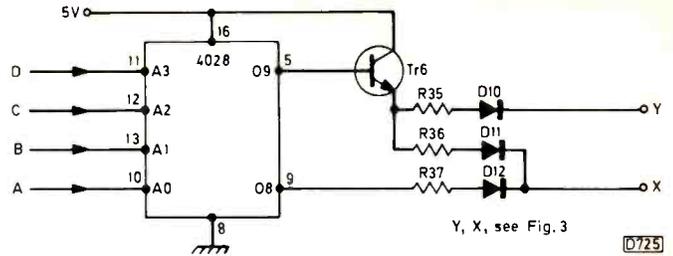


Fig. 4: Remote control interface system.

R37 and D12. Then, when channel 9 is pressed on the remote control unit, the scart interface is selected and 9 is displayed by the channel indicator.

Fig. 4 also shows how RGB selection can be made via the remote control so that when input ten is selected the RGB input is enabled and zero is displayed by the channel selector. Note that the interface is switched to the external mode so a sync signal must be fed into the video (CVBS) input to provide sync pulses.

# In Baird's Footsteps

J. LeJeune

It's easy to be blasé about the achievements of those who first developed television. Not so long since I began to wonder what went on in the mind of J.L. Baird in those early days of mechanical television in the early Thirties. Just what problems did he face? There seemed to be only one way to find out: to recreate the situation by reinventing the 30-line system. Much of my effort was done on paper only, as a sort of mental exercise, saving a lot of time that would otherwise have had to be spent on trial-and-error experiments.

### Basic Decisions

I'll begin by saying that the exercise was not as easy as you might think. Basic decisions had to be taken then subsequently altered, mainly about the size of major items like the scanning disc. This affects the picture size and curvature. Following logically, the next decision concerned the size of the scanned aperture. This affects the amount of light needed at the transmitter and the brightness of the received image. All this had to be considered before a sketch of a workable system could be made.

There's probably nothing simpler than the idea of a spinning disc with holes around the perimeter, arranged so that they scan a subject with a spot-beam of light. The main problem was to get enough light through the holes then reflected with sufficient intensity from the subject to the pick-up photocells. Compromise was necessary right at the start. I'd neither the room nor the spare cash to make a sizeable disc so that largish holes that would allow significant light through them could be used, and eventually settled on a 23.6cm diameter disc.

Baird must have considered scanning photographic negatives at some stage, but live television was his real goal and this was more difficult. I chose a 24 x 30mm aperture, behind which a 24 x 36mm (35mm) transparency could be placed. This would cut about 3mm from the top and bottom of the transparency, not enough seriously to impair the picture obtained from the scanned slide. The light source was to be a 300W slide projector, focused on the

aperture, with the scanned slide on the far side of the disc, away from the intense heat of the focused light. The idea of scanning an object and picking up the reflected light was abandoned. Fig. 1 shows the arrangement adopted.

I decided to use interlacing, which is easy enough to arrange with a mechanical system. A subsidiary lamp and photocell would be used to generate field sync pulses via another hole in the disc placed in a convenient position. Why didn't Baird think of interlacing? It would have made even the 30-line system more acceptable! Synchronisation was another of his troubles – it was more a matter of luck than lock!

On the receiver side I decided to use a modern servo system, unashamedly copied from VCR technology, to synchronise the disc. In fact the motors used to drive the rotating discs were rescued from the scrap bin, having been pronounced too noisy for a couple of Ferguson 3V35s. A drop of 3-in-1 oil at the base of the shaft quietened things down a bit – don't try this on your VCR, as the motor operates shaft-down and the oil will thus run out on to the pulley and belt.

The remainder of the video system looked simple enough and was left till last. How different that would have been in Baird's day! Servo techniques were in their infancy

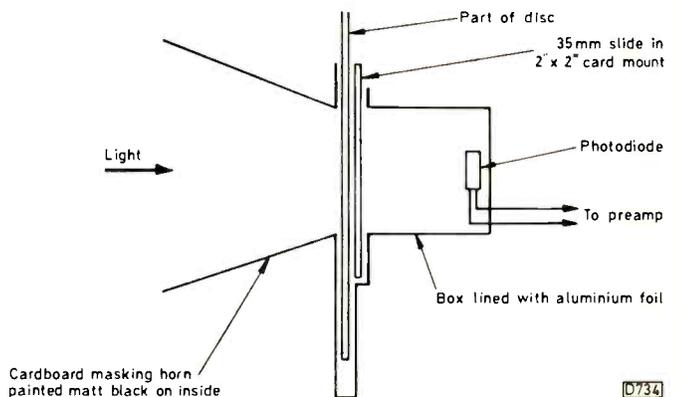


Fig. 1: Transmitter arrangement.

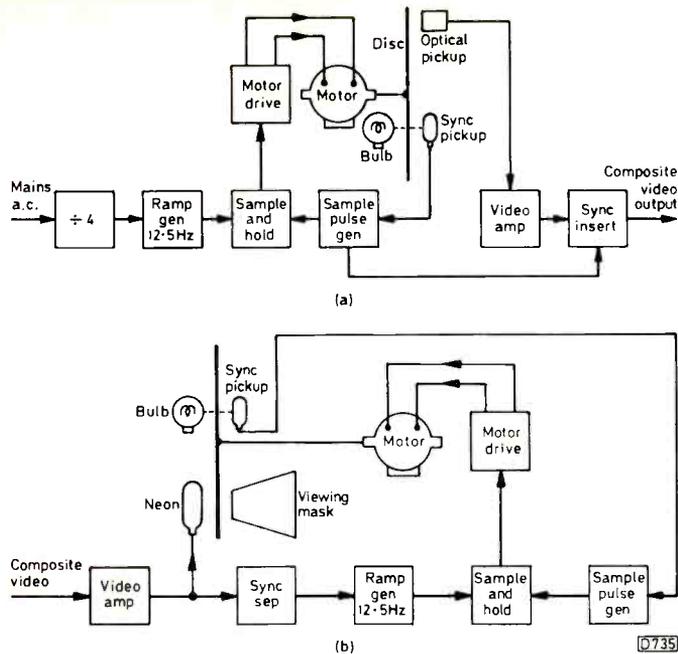


Fig. 2: Block diagrams of the transmitter (a) and the receiver (b).

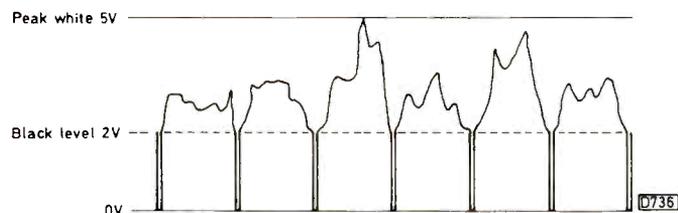


Fig. 3: The composite video waveform.

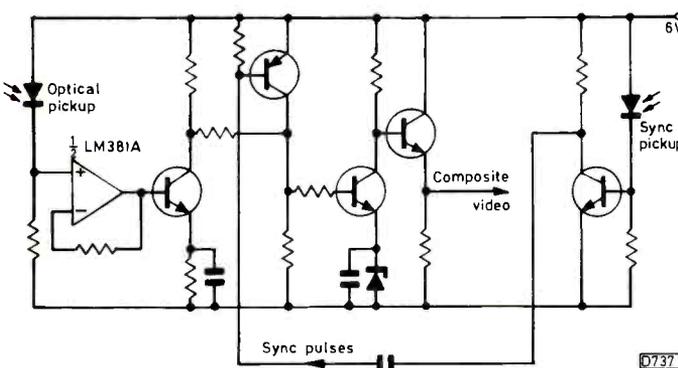


Fig. 4: The transmitter video amplifier circuit.

in the late Twenties and early Thirties. Valves were crude, noisy devices until the mid-Thirties, with a limited high-frequency performance.

The discs rotate at 750 r.p.m. to give a 30-line, 12.5 frames per second scanning rate. Line frequency is therefore  $12.5 \times 30 = 375\text{Hz}$ . With the 4:5 format of the picture, the highest video frequency to be handled would be around 100kHz for a good squarewave response. Thus a good, low-noise video amplifier could be devised with very little trouble. I decided to use semiconductor devices wherever possible. Although trouble was anticipated with the receiver light source it was not experienced. At the start I thought that a solid-state light source could be used, but this had to be abandoned because of inadequate size and intensity. So it was back to the neon lamp. Unfortunately a neon lamp's response is somewhat slower than that of a solid-state light emitter, but it was the most practical and cheapest light source available. Photodiodes

were used at the transmitter to convert the light from the scanner into a video signal.

### Mechanical Parts

In due course the scanning disc was made. You can get the rigidity required by using a thick duralumin disc, but the light has to travel through a tunnel-like hole. The diameter of the latter was 1mm – and the disc was 1mm deep! To get round this problem the holes were countersunk on the illumination source side of the disc. This worked extremely well.

With a  $24 \times 30\text{mm}$  aperture there's considerable curvature of the scanning lines. Horizontal scanning is used, with the narrower side of the picture uppermost. The disc rotates clockwise viewed from the light source/viewing side. Overall diameter of the disc is 235mm and the radius of the outermost scanning hole is 114mm. Line one is scanned by the innermost hole.

Disc drilling must be done very precisely and shouldn't be undertaken lightly. A friend with a good sheet-metal working facility is a valuable asset! Both discs were made simultaneously by employing the simple expedient of bolting them together. Countersinking of the holes was done with a stand drill set up to permit only 0.8mm penetration of the bit.

### Disc Drive

Making the disc is the hardest part, but as this is a mechanical operation it's straightforward for an experienced sheet-metal worker. Fig. 2 shows a block diagram of the transmitter and the receiver. I decided to lock the transmitter to the mains frequency: the servo used was pinched directly from modern VCR technology. The incoming 50Hz is divided by four to obtain a 12.5Hz reference. Locking to the mains was decided upon because of the use of an a.c.-powered lamp, though the 300W mains-voltage projector lamp didn't produce any noticeable flicker-beat when free-running.

The disc shouldn't be eccentric, though this gives rise to some quite comic effects. Disc mass is sufficient to give some flywheel action to the servo systems: phase locking was necessary only to keep the synchronism steady. Because of their mass, the discs take a time to run up to speed. They are steady and reliable when the servo is in full operation. 750 r.p.m.

### The Electronics

The 30-line system electronics are simple, and one is left wondering what sort of system Baird would have developed had transistors been available in the early Thirties.

Phase-controlled servos are used to synchronise the discs, mains locking is used at the transmitter, and a sync pulse is generated by a subsidiary hole in the transmitter disc. This pulse is used to synchronise the disc servo at the receiver directly. There are no line sync pulses. The disc sync pulse is inserted at the end of each frame and is negative-going. The video signal is positive-going, the transmitter producing 3V of it. Sync pulse amplitude is 2V, so the composite video waveform is as shown in Fig. 3, with a peak-to-peak amplitude of 5V.

The transmitter amplifier (see Fig. 4) uses conventional a.f. techniques and commonly available low-noise devices. D.C. stabilisation is incorporated. The black level is 2V: this is the d.c. pedestal on which the video waveform sits.

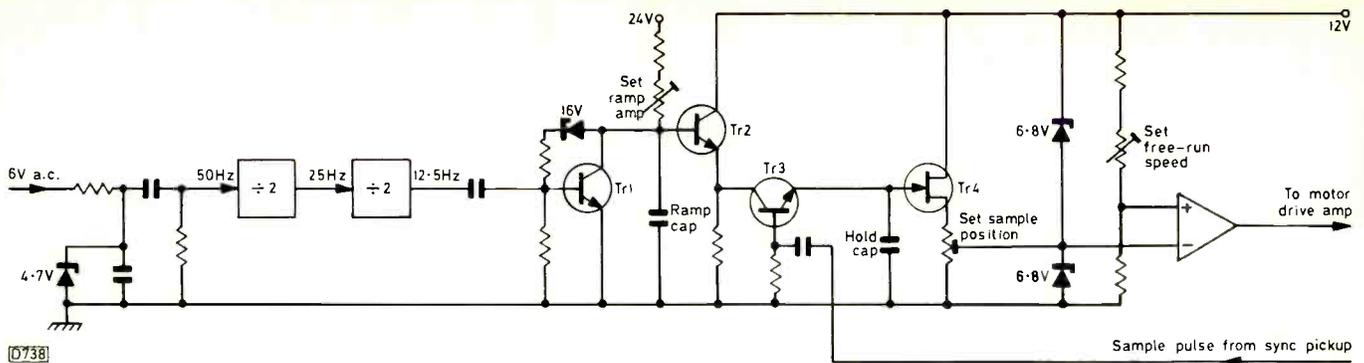


Fig. 5: The transmitter servo circuit.

The disc sync pulse is inserted into this 2V pedestal by taking it to chassis potential. When you consider the simple circuit shown, one's thoughts must again be with Baird, working as he did with selenium cells and thermionic devices for amplification. Think of triodes with the Miller effect crunching the h.f. response and pentodes with their noise contributing snowflakes to the hot shade of pink provided by the neon discharge.

At the receiver the incoming video signal is amplified to a level of approximately 85V peak-to-peak to modulate the neon lamp. Although I had a kind offer from Thorn Lighting in the form of a specially-made neon, I decided to forgo this in favour of a lamp that could be purchased at an electrical retailer anywhere and could be easily modified for the purpose. The modification is necessary to remove the series resistor incorporated in the lamp cap for 240V operation. You can remove the cap by desoldering the contacts, with the help of a pump and wick, then sawing off the end of the cap using a junior hacksaw judiciously either on the insulator or on the cap itself very close to the insulator. Any attempt to remove the cap in its entirety will end with breakage of the bulb.

I must emphasise that neon lamps don't give out a lot of light. So the resultant image at the receiver is very dim. Darkness is necessary to view the "picture".

Baird would have loved the LED. When I read about his demonstrations of large-screen TV using arrays of incandescent bulbs I'm tempted to think "if only the poor man could have had some LEDs"!

### Mirror-drum Alternative

On the face of it the mirror-drum system appears to be a better way of getting adequate light, but a word of warning is necessary here for the amateur experimenter. If anything, the allowable error in the construction of a mirror-drum scanner is even less than that with a disc, while a remarkably good adhesive is required to fix the individual mirror sections to the drum. The adhesive must be very strong and mustn't attack the mirror backing. Attaining even a passable assembly of this type is not easy for the amateur working on the kitchen table. Remember that a fragment of mirror flung from a drum rotating at 750 r.p.m. can hurt. This is a hazard even with today's modern adhesives: when Baird was attempting such things in the Thirties danger money should have been paid to people operating the equipment!.

### Servo Systems

A servo system is used to maintain the correct disc speed and position (phase). As previously mentioned, mains-frequency locking is used to keep the rotational (angular)

velocity of the transmitter disc constant. Fig. 5 shows the servo circuit. A.c. from a secondary winding on the mains transformer is clipped and differentiated. Division by four is then performed by two bistables within a chip. The output from the second bistable, at 12.5Hz, is again differentiated. The negative-going pulse is discarded while the positive-going pulse is used to trigger the discharge transistor (Tr1) in a ramp generator stage. This ramp forms the reference signal. The sample signal is derived directly from the frame sync hole in the disc, via a lamp and photodiode that are on opposite sides of the disc and 180° away from the scanning aperture. The photocell sees the lamp as line thirty's hole is leaving the aperture and line one's hole is about to scan it. As a result, the sample pulse occurs roughly half way up the ramp. It closes a switch (Tr3) momentarily, charging the hold capacitor via a current amplifier (Tr2) to the voltage attained by the ramp at that instant – this is the famous sample-and-hold circuit used in the early second-generation VCRs like the Ferguson 3V00. The voltage produced by this arrangement is used to control the disc motor's speed via its drive system.

Simple circuitry is used throughout: the "televisor" is sufficiently lacking in sophistication to allow it. A similar servo arrangement holds the receiver disc in sync. The reference signal is generated by the frame sync pulse which triggers a ramp generator, the sample pulse being provided by a lamp, a photodiode and a hole in the disc. A similar sample-and-hold circuit is used, but the sample pulse is arranged to occur between lines fifteen and two – half way through one frame scan and half way through one complete revolution of the receiving disc.

### In Conclusion

There are better ways of displaying the received picture – a small c.r.t., an array of LEDs, and so on – but superior displays call for the insertion of line sync pulses in the video waveform. If anyone is tempted to try such improvements, line sync is the first requirement. It's easy enough to generate and insert, but is unnecessary with the original disc system. Incidentally you'll need over 1,100 LEDs to obtain a display with equal vertical and horizontal resolution.

The results obtained with this Baird-type system were of barely entertainment quality. Its achievement sixty years ago would have been considerable, but today it's of curiosity interest only. Once I'd got it working I discarded the equipment: it had served its purpose. What it showed was that Baird, working in an entirely new sphere with only the efforts of Campbell-Swinton and Paul Nipkow before him to act as starting points, must have had a terrible time trying to get his crude apparatus to work.

# The Photo CD Format

George Cole

The Photo CD format has been jointly developed by Philips and photographic giant Kodak. It enables up to a hundred photographic images to be stored on a compact disc, with playback via a TV set acting as a monitor. The system employs a mixture of film, video, compact disc and computer technologies and is aimed at both the consumer and business markets.

This is not the first time that photography and video have converged as a single system. In 1985 Fuji offered Japanese consumers a TV-Photo system that enabled the user to view his shots in video form and select the best ones for development on film. There's also still video, which records video images on a floppy disc or SRAM card for TV viewing. Neither of these formats has proved to be popular with consumers. Kodak is nevertheless confident that Photo CD will be a success. It points out that systems like still video suffer from poor image quality, and that users want hard copy prints as well as TV images. Photo CD can provide high-quality pictures with a resolution sixteen times better than current TV systems and four times better than any proposed HD-TV system. Users can get the usual prints and negatives from their film, and high-quality prints can be produced from a Photo CD disc.

According to Kodak some 300 million 35mm cameras are in use worldwide: around sixty billion photographs are taken each year. Thus the potential market is enormous. Photo CD discs will be available anywhere in the world, though the players will have to be produced to suit the

NTSC/PAL/SECAM markets. An advantage is that as the images are stored in digital form it's possible to perform effects such as cropping, panning and zooming, also colour correction.

## Basic Principles

The basic idea is that camera users will be able to take their film to a photofinishing retail outlet that will supply them with a recorded Photo CD disc and/or film negatives/prints. Disc playback can be via a Photo CD, a CD-I or a CD-ROM-XA player. The former two use a standard TV set as a monitor while the later can be connected to a desk-top computer with a monitor. The Photo CD format is also suitable for use as an image store for computers. While the format was originally designed for use with 35mm film, it can now be used with other types of film such as 120 rolls.

Photofinishers will use a £60,000 Photo CD (PCD) processing system produced by Kodak. The disc production system is as follows. First a human operator checks the film orientation. The Kodak PCD scanner then scans the slides or negatives using 2,048 lines with 3,072 pixels each and twelve bits for each of the primary-colour (red, green and blue) components. A PCD Data Manager 100, which contains a Sun SPARCstation computer, then performs colour correction. After this a PCD writer stores the processed data on the disc. Index prints for a Photo CD

## ProPoint E THE COMPLETE INSTALLATION ANALYZER

ANTENNA ALIGNMENT - CABLE AND SMATV HEADENDS - EMI ANALYZER

### ● SPECTRUM ANALYZER

45 - 160 MHz  
160 - 465 MHz  
465 - 860 MHz  
0.9 - 2.0 GHz

- BASEBAND SWEEP
- TV RECEIVER WITH TUNABLE AUDIO
- AUDIO TONE FOR ANTENNA ALIGNMENT
- AUDIO/VIDEO MONITOR (WITH OUTPUTS)
- INTERNAL BATTERY (4HRS USE), MAINS POWER SUPPLY AND CHARGER



SPECIAL LAUNCH  
PRICE £1185 EX VAT

MADE IN THE UK BY:  
Oxford Applied Technology Ltd  
Gainfield, Faringdon, Oxon, SN7 8QH  
Tel: 036 787 413 Fax: 036 787 392

AMONG OUR OTHER PRODUCTS  
Synthesised and Multi-channel Satellite Receivers,  
Data/Addressing Equipment, Filters, UHF Bypass Units (for Cable Set-tops)  
Power Supplies and Custom Designed Specials

“jewel case” and standard prints and enlargements can then be produced by a Kodak Index Printer. A CD-ROM-XA reader will be used for producing image copies, prints and enlargements.

### Photo CD Images

The colour encoding system used by Photo CD is known as Photo YCC: each colour pixel is represented by an eight-bit luminance (Y) component and two eight-bit chrominance (C) components. YCC is converted back to RGB form for display purposes.

Each Photo CD image is stored on the disc as a hierarchy of components: this enables various options from a relatively low-resolution image with 128 lines by 192 pixels to a high-resolution image with 2,048 lines by 3,072 pixels to be obtained. The low-resolution images are used for index prints and PIP effects, and are uncompressed. A Base image, also uncompressed, is used for TV and computer displays. The high-resolution images are used for HD-TV displays and hard copy enlargements.

The image hierarchy is arranged as an Image Pac which has an average size of 4.5Mbytes – Image Pacs can consist of anything from three to six Mbytes. Since a compact disc has a storage capacity of around 600Mbytes, it follows that a hundred or so Photo CD images can be stored on a single disc.

Each Image Pac is stored on the disc as a standard CD-ROM file known as ISO 9660. It can therefore be read by a computer. Additional data such as Microcontroller Readable Sectors (MRS) are included so that the Image Pacs can be read by consumer (Photo CD and CD-I) players as well.

### Encoding Process

The first step in Photo YCC encoding is to scan the slide or negative. An initial problem is that the light and colour vary from scene to scene and film to film. In addition, the image quality with a hard copy print is quite different to that obtained from a video display system. For these reasons the Photo YCC system assumes that the light level in the original scene conforms to an international standard for luminance. The scanner is also calibrated to meet CCIR recommendations for colour phosphor displays. Photo YCC also includes colours outside the CCIR's recommendations however.

The RGB signal components obtained by image scanning are converted into YCC form in three stages. First, a non-linear transformation is applied to maintain compatibility with the most popular display systems. After this the non-linear values are converted into one Y and two C components. The final step is to convert the three YCC components into 8-bit data for storage on the disc.

### Image Structure

To improve access time and increase the storage capacity, the Photo CD images are stored on the disc in a compressed form. The need for this is apparent when you consider that a full-resolution  $2,048 \times 3,072 \times 24$ -bit colour image uses 18Mbytes of data: since the transfer rate of a CD player is 150kbytes/sec, it would take two minutes to call up such a high-resolution image while the disc would be able to store only some thirty images. Compression takes the following form. High-resolution components are removed from a standard base image, compressed and stored as data in residual files. Table 1 shows the various

**Table 1: Forms of Photo CD image.**

Image	Lines	Pixels/line
Base/16	128	192
Base/4	256	384
Base	512	768
Base 4	1,024	1,536
Base 16	2,048	3,072

forms of image in the hierarchy: base, base/4 and base/16 are not compressed while base 4 and base 16 employ compression. In addition the chrominance data is subsampled twice in the horizontal and vertical directions.

These processes reduce the image to around 9Mbytes. Further reduction is achieved by compressing the highest-resolution elements. This is done by using a data compression algorithm known as Huffman encoding.

### Forming a High-resolution Image

So how is a high-resolution image produced? Let's take conversion of a  $512 \times 768$  lines/pixels base image into a  $1,024 \times 1,536$  base 4 image. Interpolation is used to convert the base image to  $1,024 \times 1,536$  form. The residual base 4 data is then decoded, decompressed and added to the pixels to increase the resolution. The same process is used to convert from a base 4 to a base 16 image, except that this time the process is also applied to the chrominance data. Figs. 1 and 2 show the processing steps.

### Image Pacs

Fig. 3 shows the structure of an Image Pac. The first section, the Image Pac Attribute (IPA), stores information such as where and when it was produced. The various base sections are shown to the right, with increasing resolution: between each there's a Microcontroller Readable Sector (MRS). The final section, Image Pac Extension (IPE), is currently undefined – it could be used for features such as audio recording or obtaining even higher resolution.

Fig. 4 shows the arrangement used for base, base/4 and base/16. The ICA sector, which is microcontroller readable, contains attribute information on the image, such as its rotation (in  $90^\circ$  increments), highest resolution and whether there's an IPE. ICD stands for the image data.

The base 4 and base 16 data structure is different, see Fig. 5. Line pointers (LPT) in player and computer-

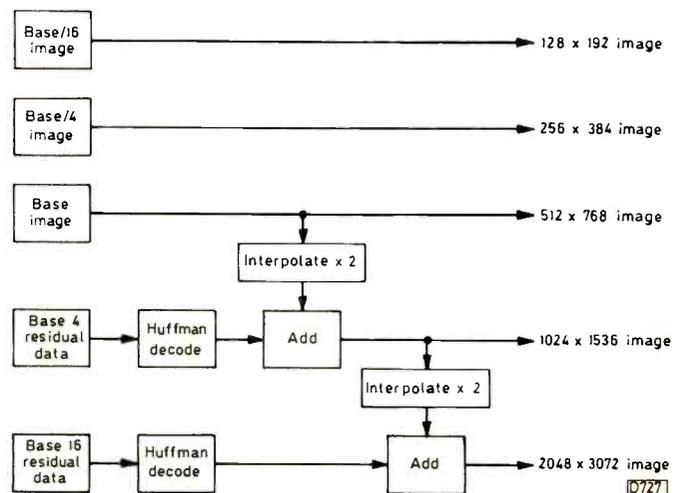


Fig. 1: Reconstituting luminance images.

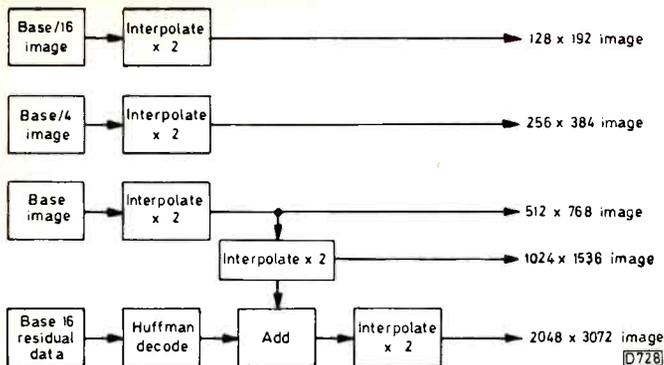


Fig. 2: Reconstituting the chrominance information.

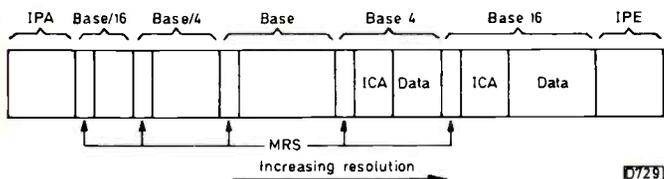


Fig. 3: Image Pac structure.

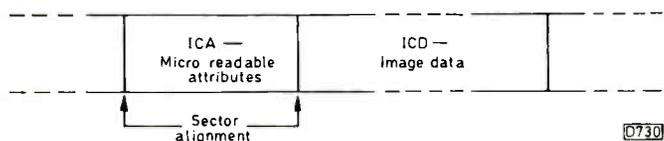


Fig. 4: Base, base/4 and base/16 data structure. The length of the ICD sector depends on the image type.

readable formats are included to give the location of the last lead-out track. The Huffman Quantiser Table (HQT) is used for residual file decoding.

The base/16 images are all stored as an Overview Pac (see Fig. 6), forming a central information store. There are two OPAs (Overview Pac Attributes), one for computer reading and the other (MRS) for consumer player reading.

### File System

Photo CD uses a hierarchical directory system for computer search to find the relevant data and instructions. On each disc there's a directory (list of files) that contains in turn an image directory, overview file and other files. The image directory contains a file for each image. The other files are Photo CD Information, which is used for computer applications, and CD-I for CD-I players.

### Disc Format

The Photo CD disc format is an extension of the CD-ROM-XA (XA = extended architecture) format known as the Mode 2, Form 1 sector structure. It enables the discs to be used with CD-ROM-XA drives and CD-I players. Fig. 7 shows the layout of a sector. First comes sector sync, with twelve bytes, for synchronisation. The header part contains the file name and additional file information. At present the subheader part is unused. After the user data part there are the error detection code (EDC) and the error correction code (ECC) sections. The latter has 172 bytes for P parity and 104 bytes for Q parity.

Photo CD uses a "hybrid disc", the standard being laid down in the Sony/Philips Orange Book for recordable compact discs. The discs are referred to as hybrid because they contain elements of the audio CD, CD-I, CD-ROM and CD-R systems.

The discs contain multiple program areas called



Fig. 5: Base 4 and base 16 data structure.

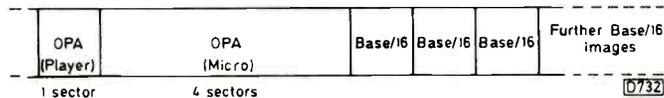


Fig. 6: Base/16 images stored as an Overview Pac.

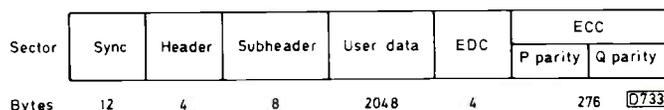


Fig. 7: Layout of a Mode 2, Form 1 sector.

"sessions" that allow additional recordings to be made on a disc (there's normally only a write-once facility with recordable discs). These enable the user to take a partly-filled disc to a photofinisher for additional images to be recorded. When this feature was first announced there was some puzzlement as to how it could be done. Audio discs have a table of contents (TOC) that stores details of the tracks and timings on the disc. Since this is written only once, any additional recordings wouldn't be listed in the TOC and would, as far as the player is concerned, not be there. Likewise anything beyond the lead-out track would normally be ignored by a CD-ROM drive. The answer is to incorporate additional software that instructs the player/drive to look beyond the last lead-out track to see whether any additional tracks are present.

### Future Developments

Photo CD can offer two extensions to image resolution, currently unused. The format can also incorporate audio recording to add words to pictures.

### Marketing

Finalisation of the CD Photo standard is expected by the end of this month (October). The European launch is due later next year, with Photo CD players costing around £300 – they will also play conventional audio compact discs. Upon finalisation of the standard by Philips and Kodak the specifications will be released to manufacturers worldwide, the hope being that they will start to include Photo CD in some of their models. The Photo CD facility adds around £100 to the price of a CD player. CD-I decks will play Photo CD discs and when the price of CD-I hardware falls it seems likely that dedicated Photo CD players will cease to be produced.

According to Kodak the Photo CD service should cost the user around £12-£13 for a Photo CD disc plus prints and negatives (the price is for 24 exposures). Additional Photo CD recordings will cost around 45 pence per exposure.

As we go to press there are conflicting claims as to whether Photo CD will be available with Commodore's CD-TV format, which is a rival to the CD-I system.

### Acknowledgement

Acknowledgement is due to Scott Brownstein, manager of advanced development at the Eastman Kodak company, for his help in the preparation of this article.

# VCR Clinic

*Reports from Philip Blundell, AMIEE, Ed Rowland, Roger Burchett, Brian Storm, Nick Beer, Chris Avis, J. Edwards and Mick Dutton*

## Philips VR6463

This machine was dead with no 5V output from the power supply because of a short to chassis. If plug P12 was removed the short disappeared, so the search continued on the P603 module. There are quite a lot of decoupling capacitors here. Fortunately the second one I tried was the cause of the short – C2919 (47 $\mu$ F, 16V). **P.B.**

## JVC HRD520

For mechanical malfunctions such as the tape being ejected while still laced up try changing the control cam, part no. PQ32413. The latest type is made of grey plastic instead of white. **P.B.**

## Philips VR2022

For a dead machine with a rattling deck solenoid check for dry-joints on bridge rectifier 6005 in the power supply. **P.B.**

## Grundig VS200/220

If the machine is completely dead check whether D410 (ZD16) is short-circuit. While you have the panel out look at the centre pin of C407. When this electrolytic capacitor begins to swell it pushes the positive pin through the board, cracking the solder. **P.B.**

## Osaki VCR31

There were no E-E signals with this machine as the 12V supply to the tuner/i.f. section was absent. The cause of the trouble was failure of the 2SA966A transistor Q410 which is on the bottom PCB. As we didn't have this type of transistor in stock we fitted a TIP32. This restored normal operation. **E.R.**

## Ferguson 3V23/JVC HR7700

Destruction of F3 (1.6AT) at switch on proved to be the result of a faulty d.c.-d.c. converter on the display control PCB. **E.R.**

## Alba VCR4000X

As reported by others in these pages, the Nikkai chassis used in this and similar models can cause confusion when the reset fails to work. In this one the machine appeared to be in the timer record mode, with the operate and record LEDs on and no display. When a cassette was inserted the machine set itself to record. To stop it the plug had to be pulled out. When this was refitted the cassette was ejected. All very confusing! **R.B.**

## Panasonic NV-L25B

This unit was inoperative with just the timer flashing zeros. There was no power up. When offered a tape the machine loaded it and kept it. The dealer who had brought this one in had changed the systems and servo control chip IC2001 and the operation and timer chip IC7501.

I started by carefully checking all the supply lines.

Everything here was fine. Something was inhibiting IC2001 and IC7501 however, but what? I decided to scope the serial clock and data lines between these two chips – this can sometimes show up problems. To my surprise there was 5V on both lines. I disconnected the serial clock and data feeds to the front panel. The 5V remained on the main PCB. Where else do the clock and data lines go? Well on this model there's an additional subsystems circuit for control of the audio dub and insert edit operations. It's undertaken by the MN15522VMS chip IC6801. A quick check showed that it was short-circuit between the 5V line and the data and clock lines. When these lines were disconnected the machine powered up and returned my test tape. Replacing IC6801 restored normal operation. **B.S.**

## Ferguson FV41R

This new machine was pretty inactive. The clock display showed "3:7" but otherwise it wouldn't do anything. Checks on the power supply showed that everything was all right here. Next step was over to the system microcomputer chip on the front panel. The supplies were o.k., as were the reset line and the main oscillator. SCL wasn't being generated however. As there was no excessive loading on this line it seemed that the micro chip was at fault, which proved to be the case. The circuit for these machines isn't very good – there are few voltages, the connection notation is confusing and a high or low chip reset both have the simple label "reset". **N.B.**

## Panasonic NV7200

There was a very loud knock from the mechanism when lacing or entering the cue mode – but not review. It suggested noisy loading motor bearings, but in fact the cause was a very worn capstan bearing. **N.B.**

## Philips VR6180/6185/6285, Pye DV186

No fluorescent display was the complaint. I found that there was no –28V supply to the operation panel though it was present at the power supply output plug. The supply goes via the P90 panel, where it's fused by ICP1001 (80mA). This fuse was open-circuit, but no cause for its failure could be found. **N.B.**

## Luxor 9272

The problem with this machine was tape path distortion: as the tape went around the entry guide it buckled cyclically. The frequency of the effect was the same as the rotational frequency of the guide pole sleeve, which provided a clue. When the pole was removed we saw that the sleeve had a very slight dig in it. This dig seemed quite disproportionate to the effect it created, but was the cause of the trouble. **N.B.**

## Ferguson 3V53/5/7, JVC HRD755

The red LED was lit but there were no functions and no clock display. Integrated circuit protector CP3 in the power supply had failed, causing loss of the unswitched 12V

supply. Failure of one or other of the four ICPs in the power supply circuit for no apparent reason is not uncommon. The engineer can be responsible however when the screening can is removed from the mechanism with the unit powered – switch off first. **N.B.**

### **Ferguson FV31R**

The card said that this machine was dead. When checked on the bench the power supply was pumping and whistled at me. With the covers removed I switched back on at the mains to find that the machine started up all right. Now for a bit of highly technical fault-finding: I tapped the tuner/i.f./signals PCB that sits across the top of the machine. Doing this would stop and start the machine. In my experience this is very often the area in which the fault lies, however strange the symptoms. After looking at thousands of perfectly good joints I found an intermittent short in the tuner/r.f. amplifier. **N.B.**

### **Telefunken 1930i/Ferguson 3V35**

No playback colour was quickly traced to the usual XB401 oscillator block. One was ordered and fitted, whereupon the machine refused to turn on! A gremlin in the waiting room had struck at the SW9V rail on the video board, shorting it out. As we expected, the cause was a short-circuit in the 4.7 $\mu$ F decoupling capacitor C419, which is of the dreaded blue tant variety. In the Ferguson version it's a 100 $\mu$ F, 10V type. **C.A.**

### **Saisho VR1200/Matsui VX820**

"Recording problems" said the ticket. "Worn head" said the pictures on the monitor. So a replacement was ordered and fitted. This seemed to put matters right, and the machine was duly collected and paid for. Next day it was back again. "It's just the same" protested the owner, "it records for only five minutes, then nothing." As I'd given the machine a full three hour record/playback test this seemed unlikely, but I checked it again. After five minutes the f.m. luminance record signal disappeared in a snow storm.

I found that the signal could be restored or killed by flexing the luminance subpanel on the YC board. As the print side of the panel is inaccessible when in situ I solderwicked all 29 pins, removed the sub-panel then wired it temporarily to the print side of the YC board for detailed inspection. There are printed pads along the edges of several subassemblies on the luminance panel. These assemblies are inserted into the panel at right angles, then soldered. It's rather like a microscopic version of the old ITT CVC5 i.f. module. The assemblies suffer from the same problem too – hairline cracks across the thinly soldered junctions. When I'd resoldered actual and suspect cracks, using a fine tip, I found that the panel could be flexed without any faults arising. So it was refitted in the normal manner. This wire-looping technique may sound lengthy and laborious, but it's a useful aid to diagnosis with an inaccessible board. This particular job took less than an hour to complete. **C.A.**

### **Ferguson FV31R**

It seemed that this machine had damaged heads, but a new drum produced no improvement. A look at the circuit showed that the outputs from the heads enter the TA7772P preamplifier chip IQ80 at pins 2 and 6, the output

appearing at pin 10 where there should be an 0.3V peak-to-peak f.m. waveform. In fact the output from only one head was present, a straight line being displayed where the other head's output should have appeared. So we had a head switching problem or a lower drum fault.

The head drum flip-flop signal from the servo panel is connected to the signals panel at pin 8 of connector BW04. There's a test point, BW11, and the amplitude should be 3.6V peak-to-peak. The waveform was missing however. So it was back to the servo panel, where the drum FF squarewave is generated by the microcomputer chip IT01. The output, at pin 14, depends on pin 8 receiving a pulse from the drum optocoupler via IM01. As there was a signal at pin 8 but not at pin 14 we replaced IT01. To our relief this cured the trouble. Unfortunately the manual provides no details of the voltages or waveforms around this chip. Note also that two types have been fitted in these machines. If, as in this one, there are two small subpanels mounted vertically on the servo/power supply panel, use type ZC93168P. The other type is EF6801U4DTD243.

Conclusion: if a badly damaged head is suspected, check the drum FF signal. **J.E.**

### **Hinari VLX5**

The E-E and playback pictures were unstable with very poor contrast. There was hardly any vertical or horizontal lock and no colour. A scope check at the video input pin on the r.f. in/out converter module showed that whilst the luminance signal was normal there were no field or line sync pulses. Tracing back from this point – we'd no manual – we came to a 47 $\mu$ F, 16V electrolytic capacitor (C354) which is connected to the collector of a transistor. At this transistor's base the video signal was correct. It was also correct at the collector once C354 had been disconnected. The capacitor checked out all right with our scope tester but we decided to fit a replacement. This restored normal operation. **J.E.**

### **Akai VS1**

This machine would lace up but not run. The head drum rotated but the capstan motor didn't start. It's driven by the BA6209 chip IC7 which contains a logic circuit, preamplifier and the motor drive stage. Checks on the driver stage, after finding that the logic inputs were o.k., showed that the servo input was high at 24V instead of 1.4V. This input comes via an operational amplifier in IC11 which seemed to be o.k. when checked. We concluded that there was a short-circuit in IC7 and a replacement provided the cure. **M.D.**

### **Logik VR950/Samsung VI611**

The complaint was of tape chewing. I thought I had an easy idler job, but when I ran the machine up it laced all right and started to play. Then the tape looped around the pinch wheel and stopped. In wind and rewind the tape moved, but very slowly. Further investigation showed that the operation of the reel motor was sluggish. Checks around the BA6209 driver chip IC0212 revealed that the supply at pin 8 was low at 9.2V instead of 12V. Also the chip was running warm. The 13V supply was correct and regulator Q0221 was o.k., but there was nearly 3V across R0282. The circuit gives the value of this resistor as 3.3 $\Omega$ , but it read 12.6 $\Omega$  when checked. A replacement of the correct value cured the problem. Incidentally this machine is of Samsung manufacture. **M.D.**

# What a Life!

**Donald Bullock**

Comes on then dies said the report with Mrs Laird's Fidelity CTV140 colour portable. And so it did. At switch on there was sound, accompanied by the rustle of e.h.t., then the set expired. I figured that either the h.t. was decaying or a short was dragging it down. So I reached for my new Cirkit TM175 meter – and found that I'd left it switched on over the weekend. A little word looked up at me from the display: "Bat".

Expensive things these PP9s, as I've come to learn in the short time I've had the meter. I've had to buy several of them. They used to be ten pence – ten old pennies, four pence in today's joke money. Now they are a couple of quid. I'd had enough, so I set to work and knocked up a little 9V power pack. The meter is now mains driven.

I soon found that the trouble with the Fidelity CTV was that the h.t. faded away, which is not unusual in these little sets. So I disconnected the set from the mains supply, dived in and checked the bits and pieces that I suspected in the power supply. An hour later I was no further forward. It was then that Greeneyes breezed in.

"I bought an Elvis Presley CD record at the village hall sale" she announced. "Can't wait to hear it, but every time I put it in the Sony player and press the drawer in it comes back out. It's been doing this for quite a while."

"Perhaps the machine's got it's pride!" I said. "It's been used to proper singers like Bing and Ella."

"What's wrong with the player though" she persisted.

"Can't imagine" I said, "at first it did it only occasionally but now it refuses to accept a disc at all – not even if I hold the drawer shut."

"Shall I take it to Snoddies then?"

I made a mental note to swot up on the machine as I switched the Fidelity set on again. It surged into power then died. Greeneyes gave it a look. "That set needs a new switch" she said before leaving.

I left it plugged in and checked a few voltages in the power supply. Only there weren't any. Then I moved over to the switch. There was a.c. at the input, nothing at the output. Why hadn't I tried the switch first? Prejudice of course.

## **McTurdey's TX100**

Just as I'd finished it a builder's labourer bowled into the drive with a set in a wheelbarrow.

"Me name's McTurdey and it's driving me mad" he said. "In the first place there's a big bite outa each side of the picture, and even the bit I got left keeps cutin' out for an hour. Then it's o.k. for the evenin', only I'm not, it gets me all wound up."

The set was a Ferguson one fitted with the TX100 chassis, 110° version. As I put it on the bench McTurdey scooped up his wheelbarrow and waltzed off in a cloud of dust.

Sure enough there was no EW correction then, after a few minutes, the set reverted to standby with the channel indicator displaying only a dash. When the back was taken off the set started to work again and stayed on. So I refitted the back and got a repeat performance. After several minutes of this I took the chassis out and scanned the

power supply and line output sections, hoping to see a dry-joint or two. As every joint looked perfect I plugged the set in again, connected the meter across the mains bridge rectifier's reservoir capacitor and discovered that the cause of the trouble was in the power supply. I then tried to locate it by using freezer and the workshop hairdryer. As this didn't do me any good I started to trace through the voltages, starting with the a.c. input. Now and again the set sprang to life, giving me moments to reflect upon the possibility of a different job ... Then suddenly it died again. I'd got as far as R134, a 1.2k $\Omega$ , 5W resistor that's part of the snubber circuit. There was lots of voltage at one end but nothing at the other. Wagging it not only produced the intermittent fault but allowed me to lift it clean out of the panel, leaving the joints underneath looking good and solid.

Cleaning off the resistor and resoldering it cleared the intermittent power failure fault. I then looked into the lack of EW correction and discovered that the little correction panel by the line output transformer was bathed in a pool of tacky brown liquid. A clean up put that right.

## **The Philips Saga**

The next set, a Philips 21CE1250/05B (CP90 chassis), would provide only a snowy raster. It's owner, Mr Dropins, explained that it had been all right before his fortnight's holiday. This news filled me with pleasure. I smiled in anticipation of a fast buck and told him it would be ready in a couple of hours' time.

I found the orange battery or, since it's a condenser, I'd better call it a capacitor! It was at the front of the set. I then embarked on the problem of extracting the chassis board from its inscrutable plastic grip-runners. I couldn't find the bits to lift or depress, push or pull or squeeze and, try as I might, it wouldn't budge. As time went by my brain kept telling me to remain scientific and rational but my instinct was to yank it out by force. Eventually the panel was freed. I changed the battery and switched on. This time the set was dead. What had I done? Why hadn't I been gentler, and how was I going to get out of the mess I'd got myself into in the time I'd allowed?

I reached for my giant magnifier and scanned the panel at length for wicked breaks or disturbed joints, but found none. There was plenty of h.t., so I checked the line output transistor and several other items in this area. No good. Perhaps Philips Service could help?

I phoned through and a wonderfully relaxed and detached expert advised me to change diode D6665 (1N4148) and resistor R3665 (4.7 $\Omega$ ) then, if still no luck, to replace the CNX63 optocoupler. I had no CNX63 but the other items tested o.k. with both my meter and component tester. As the set remained as dead a doornail I wrote out an order for an optocoupler and wondered how I was going to tell the customer that the live set he'd brought in was now dead.

## **Handsets Galore**

Then Mr. Dropins showed up, reached into his pocket and pulled out a remote control unit which he thrust into my hand. "Forgot to leave this with the set" he said, "see you later." He smiled and left.

I stood at the bench reflecting on how slowly the sets come off it these days compared to twenty-five years ago. Then I noticed the Magic Mirror IR detection card that had recently arrived. I stood it against the mirror at the back of the bench, picked up the remote control unit and

fired it at the Magic Mirror. The set burst into life and frightened me no end. Recovering, I hurriedly plugged in the aerial and, since the set had no proper channel selector knobs, danced my fingers around the dreaded search-tune buttons. Up came a perfect picture with sound. My relief was enormous. Then I noticed that something else was wrong. There was no colour – on any channel.

The set had no colour control, nor much else, and no matter how I pummelled the remote control unit I couldn't get a trace of colour. So it was into the chroma circuitry. Checks here did no good. Time passed, and I was feeling weary. Then Mr. Dropins turned up again.

"I don't know what's the matter with me" he said. "I meant to leave this instruction booklet with you – oh, and you might as well have the right remote control unit. The one I brought in was for my father's old set. We use it

because it's smaller and handier.

After he'd gone I read through the instruction book, hoping to find something under the heading "how to restore colour after giving the chassis a mauling"... No hints of course, so I returned to the house for tea and sympathy. Anyway, there was tea.

Back in the workshop I picked up the set's proper remote control unit, pointed it at the black-and-white picture and pressed colour control. Up came the colour.

Mr. Dropins was soon back on the scene. I tuned his set in, fitted the back, accepted his cheque and waved him and his set towards his car.

"I'm glad it didn't give you any trouble Mr. Bullock" he said. Then he was gone. I returned to my stool drained. How can all these things happen to just one person? And why does it have to be me?

---

# Choosing a Digital Multimeter

## Part 1

David Botto

Whether we like it or not, the old analogue multimeter is gradually disappearing from the workshop. This is simply because recent advances have made the digital multimeter today's most effective measuring instrument for TV/video work. In fact it used to take a whole stack of instruments and a lot of bench space to provide the range of tests that can be carried out with a modern DMM. The latest models use microcontroller technology to provide more features and functions than ever before. In addition to the traditional voltage, current and resistance ranges, many of today's DMMs can measure capacitance, frequency, duty cycles, min/max voltages, temperature and digital logic levels, make good/bad checks on diodes and transistors and measure transistor gain. With such a meter you've a portable test bench in your hand. This is especially helpful for the field service engineer.

Before buying a DMM it makes sense to study carefully what's available then decide on which instrument is best suited to your needs. A massive range of DMMs is on offer today, ranging from economy waistcoat pocket models to large bench instruments. The aim of this article is to help you cut your way through the DMM jungle in order to choose an instrument that best fits your particular requirements. Most readers will be familiar with DMM terminology, but Table 1 is included as a handy reference. We'll also be taking a brief look at the basic working principle of a simple DMM.

## Why Digital?

Until quite recently there were certain things that an analogue meter could do but a digital meter couldn't. For example, many older DMMs couldn't check diode and semiconductor junctions.

The heart of an analogue multimeter is its delicate moving-coil meter movement. This is easily damaged by an overload. Connect one on one of its resistance ranges to the mains supply or to the 350V h.t. line in a TV set and you'll be rewarded with a cloud of smoke and a wrecked instrument. This is especially so with cheaper meters that don't have a cutout or fuse protection. The moving needle of an analogue meter did have one definite advantage however. This was when making null or peak adjustments with a TV set or VCR. With early DMMs, especially those

that used a neon tube display, it was impossible to make such adjustments – if you tried, you were rewarded with a display resembling that of a fruit machine. Many DMMs now have electronic analogue pointers, known as bar graphs, to overcome this problem. A DMM of this type has the advantages of DMM accuracy and analogue convenience.

Since the circuitry in a DMM is more complex than that in an analogue multimeter there is in theory more to go wrong. In practice however a good-quality DMM is extremely reliable, failure being rare. One reason for this is the fact that the internal circuitry operates at low voltage levels.

An analogue voltmeter's input resistance is stated in ohms per volt – this is the meter's resistance multiplied by the full-scale voltage measurement. Thus a 20k $\Omega$ /V analogue meter set to its 1kV d.c. range presents a circuit load of 20M $\Omega$  (1,000  $\times$  20,000). When the meter is switched to its 5V range however the circuit is loaded by only 100k $\Omega$  (5  $\times$  20,000). This is much too heavy a load for much modern CTV and video work. In contrast a DMM normally has a minimum input impedance of 10M $\Omega$  on all its voltage ranges. Some special-purpose DMMs have an input impedance of 25M $\Omega$ .

If an analogue meter is accidentally dropped, or falls over the edge of the bench, its moving-coil meter may well be permanently put out of business. At best it will cost a lot of money to repair. In contrast a quality DMM is not only tough enough mechanically to stand up to rough treatment, it's also not easily damaged by overloads. It's not good policy to abuse your DMM however – good instruments deserve good treatment.

Perhaps the most popular analogue multimeter of all time was the finely engineered Avometer Model 8, which is protected by a safety cutout. Its price today is around £240 plus VAT. Not so long ago nearly every radio/TV workshop possessed one or more of these meters. Their accuracy on the d.c. ranges is  $\pm 1$  per cent at full-scale deflection, which is pretty good for an analogue meter. The a.c. tolerance is 2 per cent of f.s.d., with the resistance ranges  $\pm 5$  per cent at centre scale. To obtain this level of accuracy you have to peer carefully at the meter needle, making use of the mirror scale. Good as this accuracy is, a top-quality DMM has an accuracy of  $\pm 0.05$  per cent or

## Table 1: DMM terminology.

**Accuracy:** Measured as a percentage error ( $\pm$  per cent)

**Annunciators:** Display symbols that indicate range or function.

**Autorangeing:** Automatic selection of the correct range to match the input being measured.

**Bar graph:** LCD analogue scale pointer.

**Continuity test:** Uses a piezo-electric beeper that sounds with resistance values below  $100\Omega$ .

**Crest factor:** The ratio of peak to r.m.s. a.c. waveform value.

**Data hold:** Function that freezes the measured value on the display.

**Digits:** DMM display numbers.

**Display count:** Maximum count readable on a DMM.

**Frequency response:** Band of a.c. frequencies the DMM will measure.

**Functions:** The kinds of measurement that can be made.

**High ohms:** A resistance range where the test voltage is high enough to forward bias diodes and transistor junctions.

**Low ohms:** A resistance range where the test voltage is too low for diodes and semiconductor junctions to become conductive.

**Input impedance:** A DMM's combined a.c. and d.c. input resistance.

**LCD:** Liquid-crystal display.

**Min-max:** Function that stores the highest and lowest readings.

**Peak hold:** Function that holds the highest value reached when changing voltages or currents are being measured.

**Range hold:** Locks an autoranging DMM to one range.

**Resolution:** The smallest change a DMM can measure.

**Sensitivity:** The lowest value a DMM will indicate.

**Touch hold:** Similar to data hold.

better over its entire d.c. ranges. Those intended for servicing work are usually accurate to  $\pm 0.5$  per cent or better.

## How a DMM Works

The basic elements of a DMM are shown in Fig. 1. It consists of an analogue-to-digital converter (ADC) followed by a decoder and display. AD conversion is carried out by an integrator followed by a counter. The input, on whichever range, must first be converted to a form suitable for integration, i.e. a chopped d.c. waveform that's proportional to the input being measured. Integration produces a ramp which is fed to a counter along with a clock pulse input. The number of clock pulses that occur during the ramp represents the AD converted signal, since ramp duration is proportional to signal input. The AD converted measurement is of no use on its own of course: it has to be decoded so that an appropriate voltage/current/resistance reading is displayed.

Older DMMs such as the Heathkit 2.5-digit Model IM1202 (an excellent instrument whose neon digits could be read at the other end of the workshop!) used a single-slope integration technique – see the waveform in Fig. 2. Today virtually all DMMs use dual-slope integration, in which the waveform is of the shape shown in Fig. 3.

## A Basic DMM

A more detailed account of DMM operation will be given in a separate article at a later date. Meanwhile Fig. 4 provides an outline of a basic DMM that measures a.c. and d.c. voltage and current and resistance. Integration is carried out by the operational amplifier IC1, which produces a dual-slope output. This is fed to a quartz-crystal controlled counter/decoder where the duration of the ramp is checked. A 3.5-digit LC display provides the readout. When the user selects different ranges the decimal point in the display is automatically moved to its correct place.

The lowest voltage range with this design is  $199.9\text{mV}$  ( $200\text{mV}$  range). Calibration control VR1 adjusts the reference voltage and is set so that the reading is  $199.9\text{mV}$  when the input is the same.

SW1A/B/C is a ganged range selection switch; SW2A/B/C/D is a ganged function selection switch. When SW2 is set to read d.c. voltages, SW1A selects the appropriate range –  $200\text{mV}$ ,  $20\text{V}$ ,  $200\text{V}$ , and  $1\text{kV}$ . It also selects the a.c. voltage ranges, which are the same. In the a.c. positions an a.c.-d.c. converter is switched into circuit.

In the current measuring positions current is converted to voltage by passing the current through a series of precision resistors arranged in decade steps. When the resistance ranges are selected resistance is converted to d.c. voltage by using a constant-current source. For example in the  $200\Omega$  range the constant-current generator feeds a constant  $1\text{mA}$  through the  $1\text{k}\Omega$  resistor and  $R_x$ . The resistance ranges of a DMM are much nicer to use than the ohms scales of an analogue meter. Unlike the majority of analogue meters, the resistance scales are

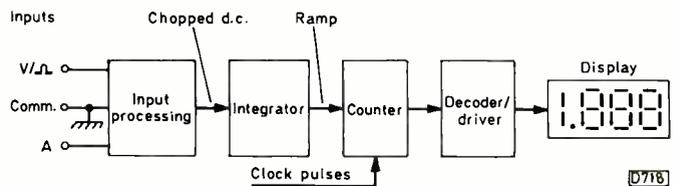


Fig. 1: Block diagram showing the elements of a digital multimeter.

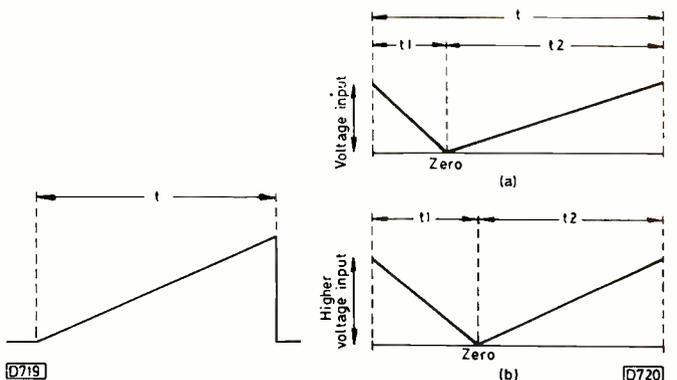


Fig. 2 (left): Single-slope integration waveform. Duration and slope of the ramp vary with the input voltage.

Fig. 3 (right): Waveforms with dual-slope integration; (a) and (b) show how different input voltages affect the slope timing.

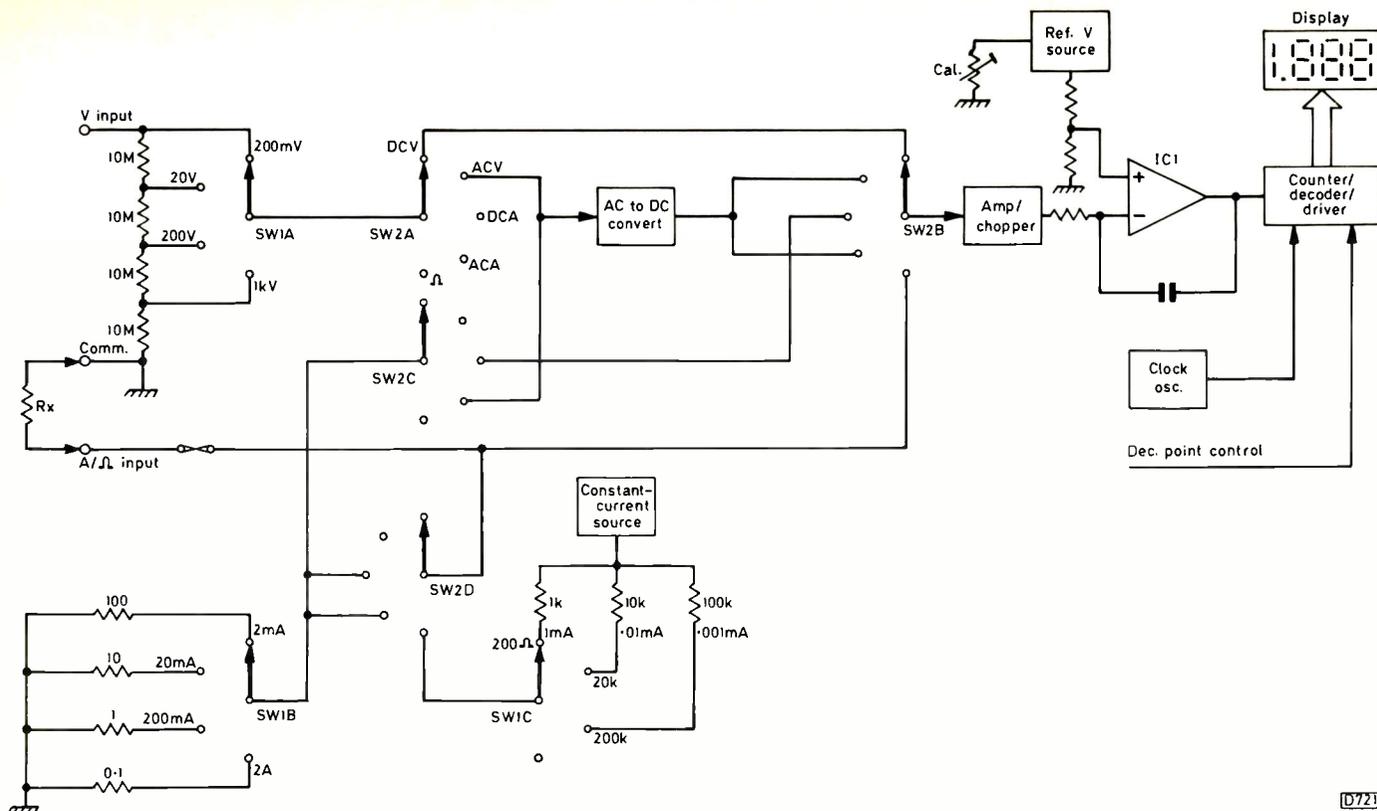


Fig. 4: Showing in simplified form the operation of a basic DMM.

linear. Thus 0.1Ω is just as easy to read accurately as 199.1Ω.

### Points to Note

Many DMMs now have capacitance ranges. They use an internal constant-current source, as with the resistance ranges, but the integrating arrangement may not be employed as the counter can simply measure the time taken for the capacitor under test to charge to a given voltage level.

The counter/decoder system is sometimes used, together with input gates, to measure signal frequency.

While many DMMs continue to use manual range switching an increasing number of today's models use microcontroller technology to provide autoranging: the user selects the function then the microcontroller senses the input, decides on the correct range and switches in the appropriate circuitry.

Be warned however. DMMs are not all the same. Don't be tempted to buy the cheapest model. Especially for workshop use it pays to invest in a good-quality instrument. After all, you'll be using it for a good many years.

### Types of DMM

Most of today's DMMs come in one of four forms – pocket type, probe type, hand-held or bench models. A brief note on each.

The pocket type is of much the same size and weight as a pocket calculator. Such meters generally have provision for making only a limited range of resistance and a.c. or d.c. voltage measurements. Accuracy on the lowest d.c. voltage range is typically about ±2 per cent. These meters are handy when installing equipment but are of little use for servicing work.

Probe-type instruments have everything, including

function/range selection and the readout, in a single probe. Ranges and accuracy are similar to the pocket type.

The hand-held type is the most useful for TV/video/computer servicing work. A good-quality instrument will provide a wide range of measurements with a high degree of accuracy. These meters take up very little bench space, which is a big advantage, and are also handy for the outside engineer.

Bench models may be mains or battery operated or both. They are useful where a high degree of accuracy and stability are required – greater than are needed for most TV/video servicing work – but generally don't provide the wide range of functions available with hand-held models.

### Switch Quality

Pay careful attention to switch construction when choosing a DMM. Many high-performance DMMs use good-quality push-button switches. It's often claimed that these are more reliable and have lower contact resistance than the rotary switches used in many less expensive models. A rotary switch is perfectly o.k. however provided it's of robust construction. With some cheaper models an economy is made by combining the switch with the meter's PCB, using printed tracks as part of the switch. This arrangement can give rise to trouble in time, especially should high contact resistance develop. You can usually tell a good-quality rotary switch by its nice, positive click feeling.

It's also vital that the DMM has a good-quality case that will stand up to workshop use. Many hand-held meters now have tough ABS plastic cases and protective holsters.

### Next Month

In Part 2 next month we'll consider some other aspects of DMM technology and present a table to help in the selection of a suitable model.

# The Ferguson Singapore Briefing

Graham Exeter

In late July Ferguson took a party of UK journalists to Singapore to hear about its new video strategy and to see the Thomson video operations in the country – Thomson recently established a joint venture with Toshiba, called International Video Products. Thomson bought Ferguson from Thorn EMI in 1987 and owns a number of other brands including RCA, GE, Telefunken, Saba and NordMende. It claims to be number two internationally in the video field, after Matsushita (Panasonic).

A brief overview of the world video market in 1990 revealed that some 40 million VCRs and eight million camcorders were sold that year. Japanese companies manufactured 63 per cent of the VCRs and 98 per cent of the camcorders (the other two per cent were produced by Korean companies). It's felt that Europe can close the gap, though the Japanese have a strong grip on the supply and manufacture of i.c.s for video products. A series of major research and development projects have been started in Europe devoted to chip design and production.

## UK Strategy

An initial seminar on Ferguson's UK strategy was given by Jay Chinnadorai, director of marketing, and Andrew Duncan, video and camcorder marketing manager. It began with a discussion on the BBC's decision to call Nicam "BBC Stereo", a move that has angered and dismayed manufacturers and retailers alike, since it's likely to add to consumer confusion. It seems that the BBC might now be having second thoughts about this. Incidentally Nicam services have recently started in Singapore, Spain, Hong Kong and the Scandinavian countries.

Except in Japan S-VHS is selling slowly. Ferguson plans to launch wide-screen (16:9) S-VHS software, which will make the wide-screen TV sets more attractive. The company has decided to delay the UK launch of its wide-screen TV sets until early 1992 however.

The company also plans to launch a laser disc player, as a joint venture with Pioneer. Unlike Pioneer's I450 player it won't have NTSC playback capability. This is because of complaints by film companies about possible piracy. It's a shame as there are hundreds of NTSC titles but very few PAL laser discs. The general feeling amongst those who attended the seminar was that a PAL-only laser disc player stood little chance of being a success in the UK.

According to Ferguson, UK VCR penetration is now around 73 per cent. Sales for the current year are forecast at 2.15 million, giving the market a retail value of around £689 million. About 71 per cent of the VCRs sold in the UK cost less than £350, and 87 per cent are remote-control programmable. Ferguson has decided to concentrate on making its VCRs easy to use and programme. The company is not at present interested in picture enhancement systems like Akai's I-HQ and Nokia's ASO.

## Timer Problems

A survey carried out for Ferguson found that 28 per cent of all adults admitted to having problems in setting the VCR timer: 35 per cent of women had problems and 50

per cent of adults over 45. Ferguson made the point that the 45-59 age group in the UK will rise from 6.5 million to 7.5 million by the year 2000. By that year 44 per cent of VCR buyers will be over 45, compared with 36 per cent in 1989. Hence the increasing need for user-friendly VCRs.

Two new Ferguson models, the FV51R and FV52L, feature Instant Help Programming (IHP) which gives on-screen help with timer programming. Both models come with two remote control handsets, a full-function unit and a basic one. The latter controls the VCR's major functions and has just nine large buttons. Sony has an ingenious reversible handset, with all the controls on one side and just the basic ones on the other. Ferguson claims that people still have problems with this complex-looking handset. The basic Ferguson unit can of course be used as a back-up handset, and the company plans to offer it separately for use with other models. The two new VCRs feature a one year/eight event timer, a 40-channel tuner and on-screen tape remaining indication. Model FV52L also features VISS, long play and trick features.

Around 80 per cent of large-screen sets at present on the market in the UK feature teletext, household penetration for teletext now standing at 34 per cent. Ferguson sees teletext becoming a major VCR feature for two reasons. First, there are around 7.5 million people with poor hearing in the UK. Many would like to be able to record subtitled programmes, preferably in colour. Around ten per cent of UK TV programmes are at present subtitled, and there's pressure for an increase – in the USA legislation may force all programmes to be made with subtitles. The second reason is that teletext can be used for timer programming. As mentioned in Teletopics last month, Channel 4 is to launch Programme Delivery Control (PDC) later this year.

## Teletext Timing – PDC

Teletext timing isn't new. A system called VPS (video programming system) has been in use in Germany for some years. It works by assigning to each programme a unique identification that's transmitted as a data signal on a spare teletext line. This enables a teletext-equipped VCR to identify programmes and their start and end times. Thus a recording can be started when the relevant identification is received and the user doesn't lose the end of a programme that starts late. PDC works on the same principle, but instead of using a whole teletext line for identification a hidden packet (26) is included in the advance listing pages. This reduces access time and doesn't waste teletext space.

In use the VCR's timer system stores the PDC codes of wanted programmes. PDC data is transmitted continuously and is constantly scanned by the VCR, which looks for matching codes. The start code occurs thirty seconds before the beginning of a programme. Likewise an end code occurs thirty seconds before the programme ends.

Ferguson has issued a guide that provides answers to some possible problems, such as what happens should a PDC-marked programme end after the start of the next timer event? The answer to this one is that the PDC programme would override the next event, even if this was also PDC marked. If there's a break in transmission whilst

a PDC programme is being recorded the timer will continue. Should PDC signals fail to appear for some reason the VCR will automatically revert to the programmed start and stop times. PDC is robust, using a powerful Hamming Code error correction system. Ferguson pointed out that if the PDC data was so badly corrupted that it couldn't be read the picture quality would be extremely poor as well. Incidentally PDC has no effect on subtitling.

PDC has its weaknesses however. Users have to call up the teletext service, then dial the TV listing pages. Couldn't a user go to these directly? Apparently Ferguson is looking into this. Another question was whether the system could be combined with the VCR Plus system (see elsewhere in this issue)? This appears to be unlikely. Another problem is that teletext programming can be used only with TV programmes to be broadcast several days ahead, though timers are usually set several hours ahead. At present the PDC system can't follow programmes that move to another channel, for example when a sports programme is transferred from BBC-1 to BBC-2: later versions will have this capability however. In theory PDC could be used to record programmes of a particular type, e.g. sport or soap operas. It could even be used to eliminate the advertisements from a recording, though it's doubtful whether the public would ever be offered this feature.

### Development of PDC

The basic PDC system was set out by BREMA and the UK broadcasters last February. Channel 4 began test transmissions in April. In the same month the European Broadcasting Union (EBU) finalised the PDC standard, which is known as 8/30 Format 2. Ferguson will be launching its first PDC VCR, Model FV54LX, this autumn. Features will include colour subtitle recording, VISS, long play and a one year/eight event timer. It will sell for about £400. The company points out that the original VPS concept was first patented by Telefunken in 1976. Thomson, which subsequently took over Telefunken, retains this patent in Germany and other countries.

BREMA has decided that PDC should be marketed under the name Startex, which it feels will be more meaningful to the public. According to Ferguson PDC will add around £50 to the price of a VCR. The company adds that although PDC has been standardised the operating software hasn't, so that various makes of PDC VCRs may operate differently.

### The IVP Venture

The International Video Products venture is 51 per cent owned by Thomson, 49 per cent by Toshiba. It's Thomson's largest VCR operation and is involved in manufacturing, engineering and R and D work. The plant is massive, covering some 33,000 square metres, with the mechanical deck operation adding a further 6,000 square metres. By the end of the year the workforce is expected to have risen to 3,000. The plant seemed to be more labour-intensive than some Japanese factories I've visited, but there's little doubt that Japanese production standards can be met. Thomson expects IVP to account for 45 per cent of its VCR production by 1992. This year's VCR production figure is targeted at around 1.4 million. The plant produces VCRs, video players and video kits for the European, Far Eastern, US and Canadian markets.

# next month in

# TELEVISION

## FREE CATALOGUE

Greenweld Electronics' new 1992 catalogue, worth £2, comes free with the November issue of *Television*. Includes components, test equipment, accessories, security items, audio and disco equipment, kits, power supplies, etc.

### ● CHOPPER POWER SUPPLIES

J. LeJeune looks at TV receiver switch-mode power supplies, in particular the type based on the TDA4600 series control chip. Circuit and regulation action are explained and advice given on fault finding.

### ● SATELLITE SOUND IF ADAPTOR

S. Pearson found that the sound panel used in the GEC C2110 series chassis can be put into service to obtain satellite TV sound where this has a different sound-vision spacing from the standard for which the main receiver is designed.

### ● EW SCAN CORRECTION

Design of the deflection yoke in a TV set has traditionally involved compromise between spot quality and raster geometry. Since the geometry can be corrected by external means, spot quality has been the main aim in yoke design. For many years large-screen, 110° sets have used a modulator circuit to provide EW correction, modulating the line scanning at field frequency. The operation of this type of circuit has been rather an obscure matter in the past. Next month Joe Cieszynski gives a clear explanation of the operation of the commonly used circuits, lists common problems and outlines fault diagnosis techniques.

### ● WHICH DMM?

In Part 2 of his article David Botto explains DMM characteristics and their relevance to servicing and provides details of the models available from the major manufacturers.

PLUS ALL THE REGULAR FEATURES

## ORDER YOUR COPY ON THE FORM BELOW

TO .....  
(Name of Newsagent)

**Please reserve/deliver the November issue of TELEVISION (£1.80), on sale October 16th, and continue every month until further notice.**

NAME .....

ADDRESS .....

.....

.....

# Letters

## REPLACING MAINS PLUGS

I've been reading the letters in recent months on whether or not to fit new shielded-pin, three-point plugs to equipment when the old-type plug is still in good condition. While I'm not in the TV trade, my business being portable industrial heaters, your readers may be interested in my experience.

The heaters that come into my workshop for service or repair can be anything from six months to twenty-five or more years old. I find that the plugs on the heaters brought in during the winter season fall into the following three groups. Out of say every hundred about fifty will be of the new type, in various states. If they are good, they stay on. If not, a new one is fitted. Of the remaining fifty, forty will be older-type plugs, again in various states. These I change for the new type regardless of condition, and the owner is charged for the replacement. The way I see it is that if the owner goes back and electrocutes himself on the old-type, unshielded plug the first thing that will be said is "you serviced the heater, why didn't you fit the new-type plug?" It's a situation I don't want to find myself in.

What about the remaining ten plugs? Well, this is the horror department – cracked tops, naked wires, live and negative wired the wrong way round, earth wire disconnected or even cut off.

Needless to say, the plug is the first thing I check before I even think of plugging in.

*O. W. Rogers,  
Bodmin, Cornwall.*

## GEC/GRANADA EQUIVALENTS

A correction is required to the equivalents information in my letter last month. The GEC equivalents of the Granada C20AA4 and C22AA4 are Models C2089H and C2289H respectively (Hitachi NP83CQ text chassis). The GEC C2087H and C2287H were fitted with the Hitachi NP81 series chassis.

*S. McManus, Technical Dept. (GEC Radio & TV),  
Hotpoint Ltd., Celta Road, Peterborough PE2 9JB.*

With reference to the letter from S. McManus (GEC) last month, the GEC C1657/1658/2295 were sold by Granada as retail sets, quite simply that: they were not modified or customised, just manufacturer's models retailed by Granada. The codes listed are put on by Granada for its own purposes and are sometimes the only identification on the set. The C2295, although based on the Tatung 160/161 chassis, was still a GEC retailed set. The other models Mr. McManus lists are identifiable from the code charts provided.

*Roy Baines,  
Peterborough.*

## SATELLITE RECEIVER PROBLEM

Keith Cummins' letter (September) confirms my opinion on the Amstrad satellite TV receiver problem and raises the new point of capture effect. This is certainly an interesting thought. With the re-reflected signal delayed by forty feet of cable compared to the original forward signal, a delay of probably 60nsec is introduced. Because of the lag, the forward and re-reflected instantaneous f.m.

spectra will not be identical, but for the spectra to be so different to appear to be two distinct signals (and therefore for the capture effect to apply) seems unlikely.

Mr. Glenton's letters refer to the quality of installations and indicate that the cable may not be a good fit, and therefore not a good match at the LNB. This adds weight to my theory. Perhaps Mr. Baker would like to check his cable at the LNB while the summer weather is with us? It seems that a good installation is essential before all the blame can be put on the receiver, even if it obviously isn't perfect. An important point to note at LNB output frequencies is that the wavelength in the cable is about one foot, which means that the distance between standing wave maxima and minima is about three inches. Discontinuities must be much less than one quarter wavelength in order not to cause impedance changes. Thus a cable flattened for half an inch of its length is possibly useless.

Another way of attempting to increase the Amstrad receiver's input impedance might be to place a small ferrite ring over the cable at the receiver end and slide it along the cable to obtain optimum results.

*Ray Porter, M.Sc., C.Eng., M.I.E.E.,  
Stourbridge, W. Midlands.*

## FILMNET RECEPTION

Most of your readers will probably be aware that Filmnet, the movie channel transmitted via the Astra satellite, has recently adopted digitised encoded sound. This is obviously a disadvantage to users of unauthorised Filmnet decoders. It's difficult to obtain any accurate information on Filmnet's sound encoding method. According to Astra technical information Filmnet is using Nicam sound. Would the use of a Nicam decoder such as the Maplin one, with the correct input filter for Filmnet's primary sound carrier, be successful? Perhaps one of your readers could supply information on this.

*Brian Webb,  
Havant, Hants.*

## TESTING IR HANDSETS

Until fairly recently I used to test IR handsets by hanging a scope across the handset's LEDs. There are physical difficulties in doing this however and I discovered that it's not reliable – one handset I tested in this way appeared to have pulses across the LED but still didn't work.

Having recently stripped down an old Rediffusion set I thought it would be a good idea to use the IR detector, which is neatly packaged in a tin box with a built-in preamplifier. So I set to work to add a few components – transistor, resistors and LED – to indicate the presence of IR pulses. Depending on the polarity of the pulse output from the preamplifier, one of the circuits shown in Fig. 1 should work. The additional components were built into the detector box and a 9V PP3 battery was strapped to the side. The results obtained are excellent. At normal handset to TV set distances the LED flashes at the repetition rate of the IR pulses. I now always carry this with me when I suspect a faulty remote control handset.

The other week I was called to check out an IR handset. Four of the channel buttons had stopped working. Guess which? Right, one to four, the most used ones. It was either a new handset (not easy to obtain with this particular make, and expensive too) or try to carry out a repair. The problem was with the carbon impregnated pads beneath the buttons. They seem to "dry up" and become non-conductive. What could be done? I couldn't put new pads

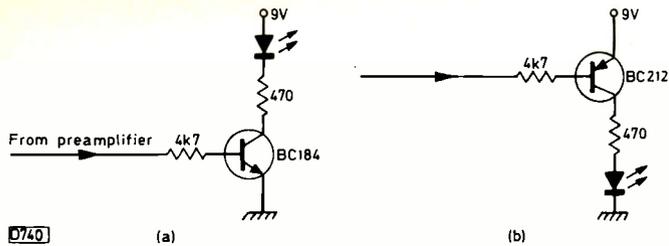


Fig. 1: LED driver circuits, (a) for positive-going pulses, (b) for negative-going pulses.

in as all the buttons are on the same mat.

A few minutes thought and to the kitchen I went to pinch a bit of the wife's cooking foil. Armed with a pair of scissors and a tube of super glue I stuck a button of foil to the underside of the faulty pads and, presto, repaired the unit. I'm not suggesting that all remote control faults are caused by dried-up pads, but armed with an IR tester, foil and super glue a great many handsets can be repaired!

Mel Davies,  
Skelmersdale, Lancs.

As the manufacturer of the infra-red detector mirrors referred to in a letter in the August issue (page 712) we would like to comment on the suggestion that they are expensive. Electronic workshops today are full of expensive, high-tech test equipment – oscilloscopes, digital meters, frequency counters, the list is long. Our IR detector mirror on the other hand is a low-cost, reliable and extremely useful piece of equipment, costing only £9 including VAT with no post and packing charges. Component suppliers such as SEME Ltd., Willow Vale Electronics and Chas. Hyde and Son Ltd. stock the mirrors. One further point is that the mirrors last a long time and don't use batteries, making them environmentally friendly.

C. R. Dempster, *Electronic Consultant Services*,  
6 Nethersole St., Polesworth, Warcs B78 1EE.

## HELP WANTED

Can anyone supply a line output transformer and the four slider knobs used in the Grundig 1500GB/3010GB/717GB hybrid colour sets? New or used, name your price!

B. Lawler, 6 Chindit Close,  
Formby, Lancs L37 2JH.  
0704 832 625.

Can anyone supply a wire-type remote control or a front panel for the Tatung VRH8300TK VCR, also a front panel for the Ferguson 3V22?

Stephen Davies, *Cwrt-y-Gorffwys, Golden Grove*,  
Carmarthen, Dyfed SA32 8NN.

I'm seeking a TV sound only tuner similar to the one that used to be marketed by Radio and TV Components Ltd. of Acton. Can anyone oblige?

A. L. Wragg,  
29 Eastern Road, Sutton Coldfield, W. Midlands B73 5PA.  
021 354 4265.

Would the two gentlemen from Antrim, N. Ireland who phoned in reply to my earlier letter (July) concerning a Condor Model VHS 8120 VCR please get in touch again – I didn't get your names etc. The manufacturer is Daewoo incidentally, in Co. Antrim. Many thanks for their help.

Can anyone supply a TDA1104 chip, or suggest a modification, for the Panasonic TC2205? Neither SEME nor Panasonic can help.

M. B. Wilson, 1 Playwell Court,  
Glanton, Alnwick NE66 4BL.  
0665 78 437.

**Editorial note:** There have been a number of calls for help with the TDA1104 chip used in the Panasonic U2 chassis. We understand that the NP1106, available from Panasonic or SEME, is a direct replacement. Our thanks to Nick Beer for this information.

Can anyone supply an M193CB1 chip for the Network Model NWC1402? Also I have a Universum FRC27915 TV/Radio/tape combo made by Quelle International. Trouble is that the sound is a.m. Does anyone have a circuit or manual or can suggest a way of converting the TV sound to f.m.?

C. E. Toms,  
212 Teignmouth Road, Torquay, Devon TQ1 4RX.  
0803 325 177.

Can anyone supply a line output transformer assembly for the Network Model 1402R, new or secondhand?

Sight and Sound, 1 Stonewall Cottage, Hill Top Farm,  
Caythorpe Heath, Caythorpe, Lincs. NG32 3EU.  
0400 73448.

Can anyone supply a Woodsdale Components plug-in module to replace the TDA2190, or information on it?

Fred Garland, Fernhill, St. Ives Road,  
Carbis Bay, St. Ives, Cornwall TR26 2JT.  
0736 795 620.

Can anyone suggest a source of a service sheet for the NordMende 1201M green-screen computer monitor? I assume that it's about 8-10 years old.

F. B. Greenhall,  
24 Trelissick Road, Hayle, Cornwall TR27 4HY.

Can anyone supply a circuit diagram and c.r.t. base adaptor for the Video Circuits type V33 tube tester?

E. J. Edwards, 8 Anderson Court,  
Plymyard Ave., Bromborough, Wirral,  
Merseyside L62 6EF.  
051 334 8733.

## FOR DISPOSAL

I have for disposal a prototype dual-standard colour receiver chassis fitted with a round tube. It's free but would have to be collected.

H. H. Journeaux,  
7 Blair Avenue, Poole, Dorset BH14 0DA.  
0202 748 072.

## IR RADIATION/COMMENTARY-FREE SOUND

Kevin Davies (Letters, August) asks how I discovered that a CCD camcorder sees IR radiation? The answer is simplicity itself: the Sony camcorder comes with a remote control unit that was pressed while it was in the camcorder's shot. I've recently been told that the ability of CCD camcorders to convert IR radiation to the visible spectrum is now being exploited in the security and photographic fields.

While on the subject of IR radiation, the universal, programmable remote control handsets currently being advertised are almost but not quite universal. One I tested copied all available remotes – including Peugeot and Renault car keys! – but failed with a Salora satellite TV receiver.

Back to commentary-free sound. My reason for raising the subject is that it's something about which most people, if they would care to admit it, have at some time or other

had cause to complain then dismissed the thought on the grounds that it's just a part of life and can't be changed. But it can be! The technology is there, and while I accept Kevin Davies' findings on motor racing (they must apply to most speed/distance sports) I still feel that a selectable commentary/no commentary option is a very desirable feature that should be made available to viewers.

*Gus Cusick,  
Preston, Lancs.*

## Steve's Camcorner

**Steve Beeching, T.Eng.**

I'm becoming more reluctant to tackle intermittent faults on camcorders that are still under guarantee. Possibly it's because I'm being sent too many. Anyway, to the point.

### Panasonic NV-M7

A Panasonic NV-M7 that came along recently wasn't actually under guarantee, but an estimate was requested. The fault symptom was a vertical blue area on the left-hand side of the picture, merging to red/orange on the right-hand side. This red/orange area covered about two-thirds of the picture. The fault was intermittent but was usually apparent. You can hear the dealer's subcontractor saying "sod that one – send it to Steve". Well thanks fellas!

It's not very easy to explain how I tracked down the cause, starting at the chroma output and working back through the encoder and CCD delay lines to the luminance/chrominance signal processor IC304. I eventually found that the outputs from the B – Y and R – Y matrix had a large triangular waveform superimposed on them – this was the cause of the discolouration.

The main input at pin 41 of IC304 was o.k. So was the Y output at TP2. But pin 17 had this incorrect waveform. It didn't enter the chip with any d.c. supply or the white balance levels. I eventually discovered that its source was at pin 9. C323 which decouples this pin was cracked and was thus intermittently open-circuit.

### JVC GRC7

Darren was struggling with a JVC GRC7 the other day. He came to the conclusion that the drum was running slow. I asked him why? His reply was to the effect that if you placed your finger on the drum then slowed it a bit more and let it go you got a momentary picture as the speed increased. The tracking control didn't work either.

When I checked the blank LC display I was able to tell him about changing C6 on the operation panel. That's the third time we've had the fault.

### Mystery Cures

So many faults clear up for no apparent good reason while you're carrying out checks. One did on a Panasonic NV-MS1. The symptom was no capstan servo lock on playback.

There were no CTL pulses at IC2002. Nor did any noise come through when pin 11 of IC2001 was touched. C2025 had an effect when it was wiggled – the CTL pulses returned. I changed C2025 without much conviction and

noted that if QR2005 unexpectedly turned on it would shut the CTL amplifier down. So D2013 was checked. But as the fault had now gone away there was not much else I could do.

A similar mystery cure occurred with a Panasonic NV-MC20. The owner complained that the dew light came on intermittently. Darren checked, agreed and sent me off at a tangent. In fact both the dew and the operate indicators flashed under the fault condition when, after a short forward wind in the play mode, the loading system failed to operate and lace up the tape.

No one at Panasonic seems sure what this emergency indication means. The fault had cleared however once the deck and connectors had been dismantled and checked.

A further note should perhaps be added. If the dew sensor is active the camcorder won't work at all and just the dew indicator flashes. It seems that if the dew sensor is activated after play has been selected the operate light also flashes, as an emergency indication. This may indicate a connector problem, or it may yet turn out to be a different software message. Who knows?

### Ferguson 3C01

The Ferguson 3C01 strikes me as being a hybrid design consisting of a JVC camera head with a Panasonic deck and VTR circuitry, though the construction suggests NEC manufacture. Be that as it may, the fault report was no viewfinder image. In fact the camera section wasn't producing any signals and investigation showed that the camera tube's high-voltage supplies were absent.

They are produced by what is almost a mini version of a line output stage. A 2SD975 transistor, Q48, drives the high-voltage transformer. It was damaged, leaky in fact, and the thermal fuse TF1 in its collector circuit was open. Destruction of this transistor is usually caused by failure of the transformer. It's small and produces around 3kV, so it works hard. I replaced the transformer, the transistor and the fuse, ran the thing on the bench for a test recording, then sent it on its way.

To my surprise it came back a few weeks later with no 8V camera section supply. This time IC1, which controls and regulates the 5V and 8V camera supplies, was open-circuit at its 8V output. It's this supply that feeds the previously mentioned transistor Q48.

A new chip was fitted and the unit was left on soak test in the record mode – you can't leave it on in the monitor mode as the battery save circuit switches it to standby. I noticed occasional severe picture break up, and eventually it went off, blowing IC1 again.

An 8V supply link, across IC1, gives operation whilst the drive pulses and power lines are being checked. When the picture broke up there was disruption to the H sync pulses. So attention was turned to the sync generator chip IC31, which was checked for dry-joints. Then the oscillator crystal was replaced. This seemed to restore stability and as no further problems were seen during a soak test IC1 was

replaced once more. The subcarrier control was checked and reset and after that the unit was returned to the dealer. So far so good.

Life being what it is however the camera bounced back almost immediately. A chat with the dealer revealed that, though he'd soaked tested it and found it to be stable, when the owner tried it in the shop there was a loud clicking noise from the camera and it went off.

Back on the bench I found that the thermal fuse TF1 was once more open-circuit. When it was replaced the camera worked very well. Then a little light bulb glowed above me. What was the common factor previously overlooked? The battery! When this was connected the camera played up as its power supply fizzled on and off. When it was connected to the charger the battery fizzled for a short period then settled down to charge. It seems, though I don't have proof, that the battery had a poor internal connection that resulted in mistrigging of the camera tube's power supply and overheating of Q48. All this was in addition to the sync generator problem.

### Panasonic NV-MS1

This fault was a real pig. A Panasonic NV-MS1 had no record or playback servo operation. Could we provide an estimate? The audio/control head was loose and the guide to the right of it was misadjusted. Not nice, but a fair enough job. The estimate was accepted, so a new head was fitted and aligned along with the guide. Super playback, into its case and away. Except for one small problem. When a record/playback soak test was carried out the original fault, no recording of the control track, became apparent. What's more, once the camcorder was in the record mode it could be stopped only by removing the power. This was the start of a very exasperating experience.

There was no record control pulse output at pin 11 of IC2001. All the other signals were correct except for the CTL duty signal at pin 36, and at that stage I wasn't sure whether this was an input or an output. There was no choice but to change IC2001, which is not an easy job – and proved to be fruitless. Super Gerald at Panasonic said that the main microcomputer chip IC6001 is often the cause of this fault, so it was changed. There were still no control pulses. Attention was then turned to IC2007, a micro chip

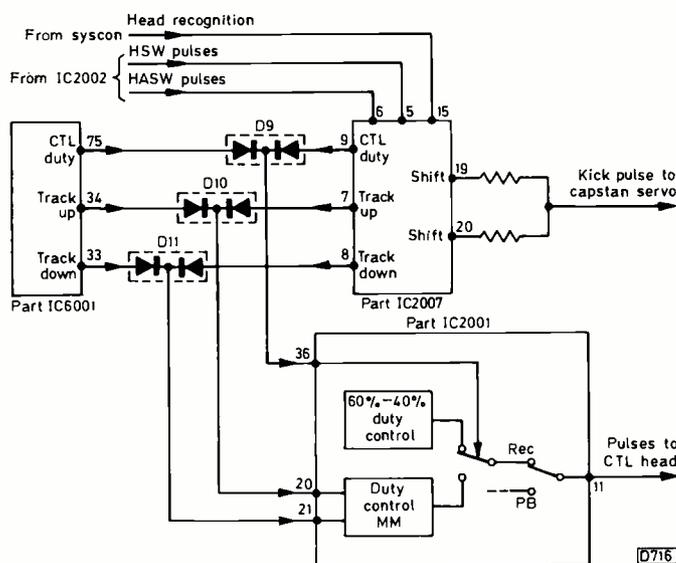


Fig. 1: Block diagram of the CTL pulse generation/head identification arrangement used in various Panasonic models.

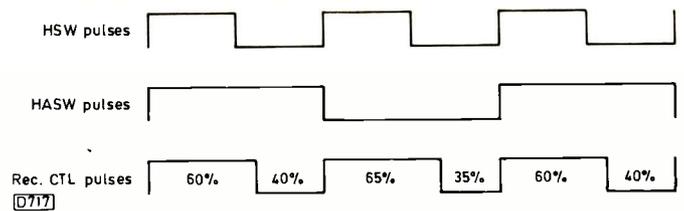


Fig. 2: Waveforms associated with Fig. 1.

with a reset pin and a clock crystal. But what did it do?

Perusal of various Panasonic technical guides brought me to one that provided the answer. It was for the NV-M7 and contained the block diagram shown in Fig. 1. The idea is to vary the duty cycle of the control track signal on alternate frames so that the machine can identify which head recorded a track. This is done to ensure that the head that records a track also plays it back. Thus an error called reverse tracking, when the head drum locks 180° out-of-phase during playback with respect to record, is prevented. Otherwise you can get differential picture wobble – the top and bottom sections wobble in different directions (S distortion).

The NV-M7 is a four-head machine with a small drum. Its video heads are designated A1, B1, A2, B2. Heads A1 and A2 are 180° apart, as are heads B1 and B2. Without a control system the drum could lock 180° out of phase, with head A1 playing back head A2's tracks and vice versa, and similarly with the B heads.

Head/track identification in the NV-M7 is effected by altering the mark/space ratio of the control track signal whilst recording, the sequence being 60/40, 65/35, 60/40, 65/35 etc. (see Fig. 2). During playback the control track pulses are compared with the 40msec head switching signal and the 80msec head amplifier signal. When reverse tracking is identified, the capstan servo is kicked back by 40msec so that correct tracking is restored.

So much for the theory, now back to the fault. With this new information I deduced that what was missing was the output at pin 9 of IC2007. Due to some peculiarity within IC2001 the result was no output at pin 11.

The input timing signals HSW and HASW at pins 5 and 6 of IC2007 were present, the clock was running, the supplies were present and correct and the reset was high. Obviously IC2007 was fault. Wrong again.

At this point desperation set in. I costed a new PCB, drank some more coffee, then phoned Gerald. Anything!! Anyway Gerald and I discussed the pros and cons of the situation and he philosophically mentioned that he didn't trust those little diodes with the boxes around them (D9, 10, 11, see Fig. 1). They are in pairs with a common encapsulation.

First I replaced D9. I then tested it with the Avo, after first mounting it on Blu-Tac to stop it running away. D9 tested o.k., so both D10 and D11 were removed and tested. As they were o.k. they were put back. Dejected and feeling suicidal I switched on to record. Lo and behold, to my surprise I now had control track pulses. My conclusion was that although D9 wasn't itself faulty there must have been leakage or a short between its pins, and that the low at pin 75 of IC6001 was holding pin 9 of IC2007 at chassis potential.

Some questions remain. First, why did the fault condition affect both the record start/stop, normal stop and inhibit power off? Secondly, why did a low at pin 9 of IC2007 completely remove the record control pulse output at pin 11 of IC2001? We may never know, unless some kind Japanese gentleman hears our plea.

# ECONOMIC DEVICES PO BOX 15, WOLVERHAMPTON, WV2 4AZ

1560H	3.72	2SC1583	0.34	AN2140	2.40	BC2207	0.33	HU1196	1.43	MC1330P	1.98	SAS650T	5.42	STR1096	4.78	TB970	3.86	TD4444	1.95
1565R	3.72	2SC1617	3.89	AN235	4.65	BC2126	0.29	BU204	1.50	HA13001	7.63	SAS570T	5.42	STR4090	12.65	TB990	3.86	TD4440	3.18
1565S	4.90	2SC1618	1.98	AN236	3.33	BC2134	0.30	BU205	1.15	HA13006	2.26	MC1351P	1.25	STR4450	6.18	TC2705	3.47	TD4500	2.75
17052	5.61	2SC1741	0.11	AN200P	0.10	BC214	0.10	BU206	1.25	HA13022	7.06	MC1352P	1.49	SAS580	2.85	TR451	5.77	TD4600-2	1.92
17074	9.30	2SC1810	2.06	AN241	1.71	BC225	0.10	BU207	1.61	HA13043	11.35	SAS6000	1.33	TR454	4.96	TC290A	2.26	TD4610	5.99
17089	3.45	2SC1815	0.20	AN245	5.48	BC237	0.10	BU208	1.12	HA13424	8.89	MC1358P	4.48	SAS660	2.97	STR50103A	4.12	TC440	7.75
17127	2.50	2SC1826	0.69	AN253	1.80	BC238	0.08	BU209	0.66	BU208	2.35	HA1345A	12.25	MC1493P	3.99	SAS6700	1.63	TC440	1.89
17376	1.58	2SC1829	3.35	AN260	3.85	BC239B	0.25	BU210	0.67	BU208A	1.12	HA1367	2.75	MC1497	7.10	SAS670	3.96	TC460	2.75
1N4001	0.04	2SC1875	4.50	AN272	7.92	BC251A	0.31	BU211	0.25	BU208A	2.06	HA1368R	2.45	MC1497	1.10	SAS6710	2.21	TC620V	0.40
1N4002	0.06	2SC1893	3.85	AN295	8.28	BC264	0.30	BU212	0.13	BU226	1.07	HA1374A	2.86	MC1712	3.88	SC94203	19.35	TC637	0.97
1N4003	0.06	2SC1921	1.37	AN300	5.26	BC300	0.48	BU213	0.13	BU226	1.07	HA1374A	1.59	MC3340	1.40	SDA2306	17.10	TC644V	1.80
1N4004	0.05	2SC1923	3.30	AN302	3.99	BC304	0.50	BU214	0.29	BU356A	1.79	HA13177	0.95	MC7724CP	3.50	SDA21122	12.96	TC645	1.20
1N4005	0.05	2SC1929	2.35	AN305	8.88	BC302	0.53	BU215	0.58	BU406	1.49	HA1388	1.87	MC5192	1.90	SDA2100	2.50	TC646	1.09
1N4006	0.08	2SC1942	2.17	AN315	2.46	BC303	0.48	BU216	0.54	BU406	1.24	HA1389R	2.05	MC7724CP	3.50	SDA21122	12.96	TC646	1.20
1N4007	0.06	2SC1959	0.20	AN316	4.16	BC308A	0.11	BU217	0.33	BU407	0.54	HA1389	2.69	MC106556	1.56	SG264A	9.26	TC652V	4.87
1N4148	0.03	2SC1957	0.95	AN318	7.16	BC309	0.17	BU218	0.18	BU412	5.29	HA1392	4.28	MC29207	1.25	SG613	12.37	TC658	0.95
1N4448	0.03	2SC1953	1.93	AN320	5.47	BC317A	0.13	BU219	0.16	HA256A	1.67	HA1394	2.65	ME0411	0.75	SG629	2.27	TC659	4.22
1N5401	0.11	2SC1962	1.93	AN321	2.25	BC327	0.09	BU220	0.31	BU500	6.31	BU500	6.31	ME0302	0.26	SG633	14.28	TC693V	1.25
1N5402	0.13	2SC1969	1.79	AN322	1.73	BC328	0.13	BU221	0.38	BU508A	1.50	BU1398	2.55	ME102	0.28	SI1830HD	20.62	TC9013V	1.74
1N5403	0.18	2SC1983	1.32	AN337	0.37	BC337	0.09	BU222	0.34	BU536	1.53	HA1406	2.07	ME9002	0.45	SKE2F104	1.25	TC9014V	2.42
1N5404	0.10	2SC1985	0.60	AN340P	1.53	BC338	0.12	BU223	0.55	BU608	1.54	HA1452	0.85	ME9201	0.26	SKE2G304	1.25	TC9016V	1.02
1N5405	0.16	2SC2009	0.34	AN355	1.65	BC356	0.17	BU224	0.40	BU705	2.67	HA1457V	2.23	MM4965	2.50	SKE4F06	1.00	TC9017V	1.25
1N614	0.04	2SC2029	1.15	AN362	3.50	BC441	0.69	BU225	0.36	BU806	0.98	HD30870-A23	7.46	MJ2501	3.30	SKE4F208	0.37	TC9019V	1.00
1S1555	0.18	2SC2028	2.11	AN370	0.45	BC450	0.36	BU226	0.36	BU807	0.98	HD30870-A23	7.46	MJ2501	3.30	SKE4F208	0.37	TC9019V	1.00
1S44	0.10	2SC2063	0.99	AN5111	3.43	BC454	0.42	BU227	0.32	BU825A	1.95	HD38750-A	8.13	MC2855	0.84	SKE4F208	0.37	TC9019V	1.00
1S521	0.10	2SC2078	1.10	AN5120N	4.50	BC461	0.46	BU228	0.34	BU848A	0.68	HD38800A50	14.52	MC3055	1.15	SKE4F208	0.37	TC9019V	1.00
2N2219A	0.29	2SC2073	2.73	AN5132	5.08	BC462	0.51	BU229	0.39	BU848	0.50	HD44801A05	10.47	MJ340	0.49	SKE4G104	0.54	TC9054V	3.99
2N3033	0.35	2SC2085	1.65	AN5250	5.04	BC463	0.30	BU230	0.43	BU845	0.74	HSH1010	14.60	MJ520	0.49	KS1510	2.15	TC9057V	0.44
2N3054	0.99	2SC2091	1.80	AN5256	1.86	BC478	0.32	BU231	0.39	BY126	0.13	HSH1002	9.50	MJ231	0.99	SL1310	3.14	TC9064	2.40
2N3055	0.10	2SC2111	0.87	AN5612	5.47	BC479	0.28	BU232	0.14	BY127	0.09	HM6211	14.55	MJ232	3.01	SL1430T	2.31	TC9065V	3.86
2N3042	1.16	2SC2166	0.80	AN5613	1.00	BC532	0.38	BU233	0.36	BY128	0.16	HA1393	1.20	MJ300	1.95	SL1430T	2.31	TC9065V	3.86
2N3072	0.10	2SC2216	0.60	AN5630	3.95	BC546	0.08	BU234	0.14	BY164	0.04	HM6232	2.20	Z38	5.65	SL432A	3.18	TC9072	4.80
2N3073	0.18	2SC2233	1.29	AN5701N	1.66	BC547	0.10	BU235	0.24	BY176	0.93	HM6251	5.69	SL309	3.49	SL432A	3.18	TC9072	4.80
2N3075	0.15	2SC2236	0.89	AN6250	1.75	BC549	0.10	BU236	0.17	BY179	0.85	HM703	2.97	ML926	3.45	SL471	4.45	TC9075A	2.55
2N3076	0.14	2SC2278	1.14	AN6300	2.73	BC550	0.19	BU237	0.17	BY182	1.05	HM9032	4.00	MM5314N	8.99	SL480	7.24	TC9076AP	0.71
2N3077	0.16	2SC2314	0.60	AN6310	4.54	BC556	0.13	BU238	0.37	BY187	0.79	HM9032	3.22	MM5316N	3.50	SL490	8.32	TC9076AP	1.27
2N3171	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3171	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3172	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3172	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3173	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3174	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3175	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3176	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3177	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3178	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3179	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3180	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3181	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3182	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3183	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3184	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3185	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3186	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3187	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3188	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3189	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3190	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3191	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3192	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3193	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13
2N3194	1.15	2SC2335+Knt	7.00	AN6320	0.86	BC558	0.07	BU239	0.16	BY188	1.76	HT4207	11.99	MM5318N	3.11	SL501B	2.37	TC9076AP	3.13</

USE YOUR ACCESSOR VISA

TEL 0902 72083

DECLARATION OF QUALITY

AS DISTRIBUTORS OF QUALITY VIDEO SPARES FOR THE LAST TEN YEARS, WE FULLY UNDERSTAND THE REQUIREMENTS OF THE REPAIR TRADE. THERE IS A CERTAIN QUALITY WHICH MUST BE MAINTAINED IN ORDER TO EXECUTE HONEST, RELIABLE REPAIRS. THEREFORE, WE GUARANTEE THAT ALL VIDEO SPARES SUPPLIED BY US ARE OF THE FINEST QUALITY AND WE CAN ASSURE YOU THAT ALL STOCKED ITEMS WILL BE DISPATCHED THE SAME DAY.

Table with multiple columns listing various video spares (e.g., Video Head, Pinch Roller, Belt Kit) and their corresponding part numbers and prices. The table is organized into several vertical sections, each starting with a brand or model name like 'AIWA', 'AV-66', 'AV-77', etc.

NEW IN STOCK, A LARGE RANGE OF SLIMLINE REMOTES. JUST SUPPLY MAKE, MODEL & PART No. IF POSSIBLE FOR AN IMMEDIATE QUOTE. AVERAGE PRICE £18.00

NEW FAX NUMBER 0902-29052

10,000 Line Catalogue available with order, or at operation without notice. Stock queries by post only. By request, SAE please (9" x 4"). Telephone 0902-712083 (24hr. answering machines for Access & Barclaycard users.) Orders from Govt. Institutions, Schools, Nationalists, accepted with official order. All goods should be delivered within 4 working days.

REGISTERED OFFICE: THE COACH HOUSE, MUXTON LANE, TELFORD \* MAIL ORDER - CALLERS STRICTLY BY APPOINTMENT

# Servicing the Saisho VR1200/Matsui VX820

Ed Rowland

The Saisho VR1200 and its Matsui equivalent, Model VX820, were released during the latter part of 1986. The Saisho VCR was sold through Dixons outlets and the Matsui version through Currys stores. They are identical units and the following notes therefore apply to both.

Although these machines were manufactured down to a price they have proved to be reasonably reliable apart from a few problems that can by now be classified as stock faults and some others that, though not as common, will no doubt be encountered by engineers who deal with these VCRs fairly regularly.

The power supply, see Fig. 1, is straightforward and in general doesn't give much trouble. There are a couple of fairly common faults however, not least of which is failure of the 2SD1207 12V regulator transistor Q2502. It lives

directly in front of the STK5332 regulator chip. Note that this transistor is a safety component: although other types will work in this position, it's important that the correct replacement is used in order to comply with safety requirements. When Q2502 fails the result is no functions, often with the red "operate" LED lighting momentarily when the function button is pressed. A new transistor is usually all that's required to restore normal operation.

Another cause of no functions is failure of the STK5332 chip IC2501, in which case the display will usually be o.k. and the machine will accept a cassette, though no other functions are possible.

Failure of the machine to power up, with the display strobing, should lead to a check on diodes D501 and D502. Replace them both.

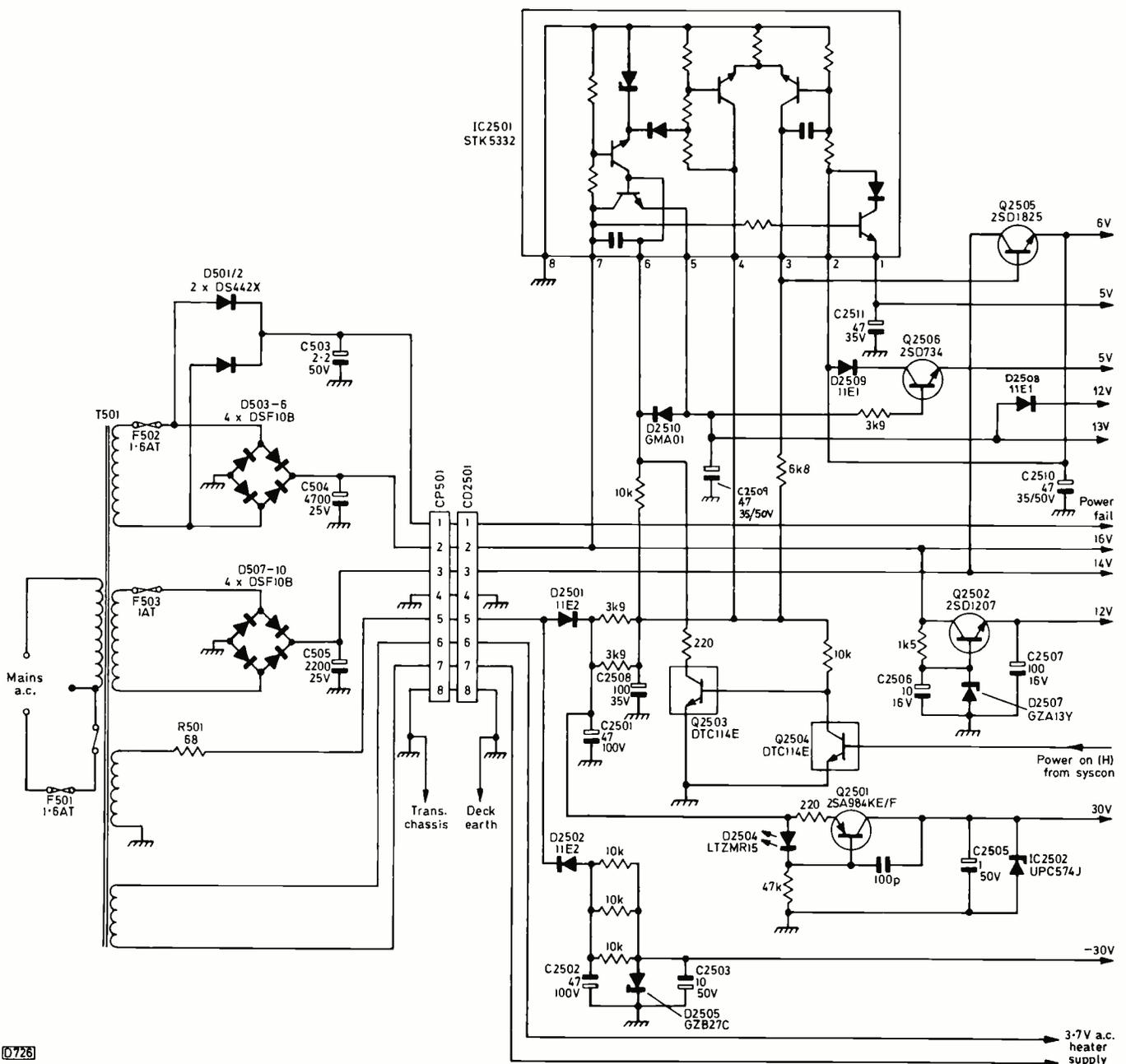


Fig. 1: Power supply circuit used in the Saisho VR1200/Matsui VX820.

We've never known the 6V regulator transistor Q2505 to fail. In general, as previously mentioned, we've found that the power supply is pretty reliable.

### Fault Round-up

No functions can be the result of things other than the power supply going wrong. We've had trouble with the mode switch for example. It's located beneath the right-side of the carriage and can give rise to several symptoms, some of which are quite perplexing. They include switching off after the machine has ejected a cassette, intermittent stopping in the record or play mode, and no functions after accepting a cassette. The only sure way of providing a cure is to replace the switch - cleaning it usually doesn't produce any improvement.

Loss of functions can also occur when the BU2176S chip IC2001 fails. It's located on the main PCB and is fairly easy to replace. We've had this fault only once however, though we have had drum speed problems due to this i.e. on a few occasions.

We've had a number of these machine come into the workshop with a cracked front operations PCB, though goodness knows how users manage to do it! Depending on the severity of the damage the job can be a more or a less arduous undertaking, as there are literally dozens of fine tracks. These require very delicate microsurgery to effect a repair. In situations like this we find that the fibre pencils sold by SEME can be extremely useful for removing the etch-resist from the damaged print in order to expose the copper track.

One of the faults most frequently encountered is loss of the steel activating pin from the limiter post lever assembly, which is situated next to the pinch roller. What

happens is that the nylon bush that holds the pin splits, with the result that it falls into the machine. The outcome is that when play is selected the machine laces up and then, after displaying for a few seconds a picture that looks as though the machine is in the pause mode, it unlaces. The pin can be refitted using Superglue, but a replacement lever is a better option.

To remove the old lever assembly simply ease back the nylon clip that holds it in place and, using long-nosed pliers, raise it above the clip. Then rotate the lever assembly anticlockwise and the limiter post arm clockwise until the pin on the arm disengages from the slot in the lever assembly, which can now be lifted clear. Don't forget to recover the old pin from within the machine: it could cause problems, though it quite often drops out through the ventilation holes when the machine is being transported.

Other faults that you could meet are as follows: failure to accept a cassette due to faulty end sensors or alternatively the BA6329A chip IC1003; no drum rotation because circuit protector CP209 is open-circuit; no E-E signals because C6017 (1.000pF) between pin 5 of IC6001 and chassis is leaky; and varying capstan speed accompanied by wide noise bars on the screen because of failure of the BA6305 chip IC2004.

In the event of there being no clock display, with everything else o.k., remove the back-up battery BT601 from the main PCB and refit it after 20-30 seconds.

Tape edge damage is usually caused by a faulty clutch and/or pinch roller. If in doubt replace them both.

If you find that it's necessary to replace the loading belt it is advisable to obtain the service manual before undertaking the operation. Its replacement involves dismantling the loading gear mechanism, a rather complex

AN236	£2.30	SIK2025	£7.00	STR2013	£4.60	TD3651	£2.10	BU407	£0.55	2SC253	£0.35	BELT KITS	£1.89	SL8000 8080	£1.89
ANS1010	£2.95	SIK2028	£5.60	STR3125	£5.80	TD3651A	£2.40	BU407D	£0.80	2SC268	£1.30	V51 V52 V55	£0.90	LOADING BELTS	£0.30
ANS256	£2.95	SIK2029	£5.00	STR4090	£5.80	TD3652	£2.20	BU408	£0.80	2SC269	£1.15	VCR4600	£1.45	JVC FFR3V29	£0.30
ANS5101	£2.85	SIK2038	£4.50	STR5412	£4.50	TD3654	£1.85	BU408D	£0.88	2SC271	£0.70	VCR7000	£1.45	JVC FFR3V35	£0.35
ANS521	£2.85	SIK2129	£6.10	STR6620	£4.50	TD3653	£1.50	BU426	£0.70	2SC273	£0.70	VCR7000	£1.45	HITACHI VT11	£0.30
ANS135	£2.40	SIK2145	£9.00	STR11906	£6.00	TD4100	£3.95	BU500	£1.05	2SC2828	£0.20	3V22 3V30	£0.20	HITACHI VT1900	£0.38
AN6248	£2.00	SIK2155	£10.00	STR4090A	£3.65	TD4150	£3.05	BU500A	£0.75	2SC2941	£3.15	3V29 3V30	£0.50	VS8300 9800	£2.50
AN1720	£1.25	SIK2230	£10.00	STR5412	£4.85	TD4505	£3.10	BU526	£0.78	2SC2998	£3.05	3V42 43	£0.60	VS1 2/3 5.0	£2.50
AN1743	£2.00	SIK2240	£8.50	STR6113	£4.85	TD4510	£3.10	BU526	£0.78	2SC3000	£1.60	3V48 5V10 14	£1.35	VS105 244 516	£2.50
AN168	£2.50	SIK2250	£7.60	STR50213	£6.50	TD4600	£1.90	BU536	£1.05	2SC3030	£1.75	HIMAR VCR 6.9	£2.50	VS125 240 512	£2.50
BA308	£1.30	SIK3041	£4.71	STR4090	£5.00	TD4600-2	£1.75	BU536BDF	£1.25	2SC3106	£2.60	VT1117 33	£1.80	VCR4500 4600	£2.50
BA3506	£2.00	SIK3042	£4.71	STR4090A	£5.00	TD4600-3	£1.75	BU536BDF	£1.25	2SC3115	£2.45	VT15000	£3.10	VCR7000	£3.00
BA5102	£2.50	SIK3044	£5.75	TA7070	£1.15	TD4610	£1.95	BU1114	£0.70	2SC3170	£2.45	VR1800	£0.50	3V22	£2.50
BA5402	£2.50	SIK4024-2	£9.50	TA7081	£0.70	TD4650	£2.25	BU112	£0.85	2SC3185	£1.08	VR3300	£0.45	3V29 3V32	£2.50
BA6109	£1.75	SIK4026	£6.00	TA7205	£0.89	TD4650A	£4.00	IP30	£0.25	2SC3342	£1.20	VR6465 86	£1.50	3V48 5V10 14	£2.50
HA1124	£1.15	SIK4029-2	£6.80	TA7684	£2.35	TD4721	£1.15	IP31A	£0.22	2SC3429	£1.35	HR3300 HR3660	£1.40	FVHP15 830	£3.00
HA1377	£1.15	SIK4060	£5.80	TA8120S	£0.40	TD4720	£2.90	IP33	£0.50	2SC3445	£1.06	HR7200	£0.80	VR13 33	£2.50
HA1235	£1.85	SIK4121	£6.50	TA8120P	£0.40	TD48145	£1.05	IP32B	£0.25	2SC3507	£1.30	HR7200	£0.80	VR13 33	£2.50
HA11423	£2.00	SIK4121-2	£7.00	TA8120U	£0.40	TD4815	£1.05	IP32B	£0.25	2SC3517	£1.05	HRD110 225	£1.00	VT8000 9800	£2.50
HA11423	£2.00	SIK4141-2	£4.40	TA8600	£0.45	TD48170	£3.00	IP41	£0.20	2SC3678	£1.12	NV333	£1.20	HR3300 3660	£2.50
HA11714	£2.00	SIK4141-2	£7.00	TA8520	£1.00	TD48185	£4.80	IP41A	£0.20	2SC3682	£1.45	NV339	£1.45	HR7200 7665	£2.50
HA12017	£2.10	SIK4152-2	£10.00	TA8540	£0.85	TD48190	£2.10	IP41C	£0.22	2SC3760	£1.50	NV390	£1.40	HS200 304 700	£2.50
HA13001	£1.85	SIK4161-2	£8.50	TA8650	£2.85	TD48196	£3.10	IP42C	£0.23	2SC3818	£1.20	NV390	£1.40	HS300 400 710	£2.50
HA13002	£2.10	SIK4171-2	£9.10	TA8680	£3.70	TD49045	£3.10	IP42C	£0.23	2SC3818	£1.20	NV7000	£0.90	NV100 340 788	£2.50
LA1460	£2.05	SIK4172-2	£10.50	TA9000	£1.00	TD49503	£2.21	IP110	£0.45	2SC3913	£1.85	NV7010	£0.90	NV100 340 788	£2.50
LA1462	£1.15	SIK4181-2	£8.50	TA9540	£1.85	UPC100	£1.50	IP110	£0.45	2SC3913	£1.85	NV7010	£0.90	NV100 340 788	£2.50
LA4445	£2.00	SIK4182-2	£10.00	TA9540	£1.85	UPC1023	£0.80	MEJ340	£0.25	2SC2021	£1.15	VT1000	£0.70	NV12 18	£2.50
LA4460	£2.00	SIK4191-2	£11.00	TA9540	£1.85	UPC1032	£0.80	MEJ340	£0.25	2SC2021	£1.15	VT1000	£0.70	NV12 18	£2.50
LA4505	£2.50	SIK4191-2	£11.00	TA9540	£1.85	UPC1032	£0.80	MEJ340	£0.25	2SC2021	£1.15	VT1000	£0.70	NV12 18	£2.50
LA4510	£1.50	SIK4231-2	£16.00	TA1010A	£1.00	UPC1377	£1.00	MEJ521	£0.35	2SC2258	£1.15	VCR3000 6300	£1.25	VHS5000 8300	£2.50
LA4555	£2.50	SIK4311	£15.00	TA1015	£1.00	UPC1382	£0.80	MEJ521	£0.35	2SC2258	£1.15	VCR3000 6300	£1.25	VHS5000 8300	£2.50
LM1011N	£1.50	SIK4332	£16.00	TA1028	£2.08	UPC1394	£1.20	2N3653	£0.25	2SC2591	£1.20	VCR3000 9500	£1.20	VCR481 8300	£3.00
LM1111	£1.15	SIK4362	£6.25	TA1029	£2.40	UPC1031	£1.05	NW473	£0.10	2SC2751	£1.80	SLC5 6 7	£1.30	VCR51 793	£3.00
LM318	£1.15	SIK4372	£6.25	TA1035	£1.20	UPC1458	£0.50	AC141	£0.35	2SC2751	£1.80	SLC5 6 7	£1.30	VCR51 793	£3.00
LS1405	£1.50	SIK4383	£6.50	TA1044	£2.20	UPC1458	£0.50	AC141	£0.35	2SC2751	£1.80	SLC5 6 7	£1.30	VCR51 793	£3.00
MS106P	£1.50	SIK4423	£9.00	TA1044	£2.20	UPC1458	£0.50	AC141	£0.35	2SC2751	£1.80	SLC5 6 7	£1.30	VCR51 793	£3.00
MS152L	£1.50	SIK4473	£9.00	TA1047	£3.60	AC720	£3.30	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3 PIN	£0.05
MS218L	£2.50	SIK4803	£7.50	TA1054M	£1.82	AC720	£3.30	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	4 PIN	£0.06
MS218L	£2.50	SIK4833	£6.50	TA1054M	£1.82	AC720	£3.30	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	2 PIN	£0.07
MS5434L	£1.85	SIK4843	£7.50	TA1060	£1.75	BC141	£0.20	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	18 PIN	£0.15
ST401	£1.85	SIK4853	£9.00	TA1072	£2.10	BC107	£0.10	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	20 PIN	£0.12
ST441	£2.25	SIK4873	£10.00	TA1082	£1.85	BC107	£0.10	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	IC SOCKETS	£0.05
ST8011	£2.70	SIK4913	£12.20	TA1170	£0.80	BC107	£0.10	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	SEEG 5MH-40 SR-110-7MH	£0.45
ST8015	£1.90	SIK5314	£5.80	TA1190	£0.95	BC181	£0.07	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	STR5013 + Mod Kit	£6.00
STK035	£4.75	SIK5315	£6.50	TA1270	£1.85	BC181	£0.07	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	TV AND VIDEO SPARES	£2.00
STK043	£2.30	SIK5324	£3.50	TA1410	£2.00	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V29 TAKE UP IDLER	£1.07
STK056	£3.20	SIK5329	£3.80	TA1518A	£2.35	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V29 TAKE UP CLUTCH	£2.05
SIK050	£19.00	SIK5331	£5.00	TA1908	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP IDLER	£1.07
SIK077G	£6.50	SIK5332	£2.50	TA2012	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK078	£6.50	SIK5333	£2.50	TA2012	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK080	£6.50	SIK5338	£5.00	TA2014	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK082	£6.50	SIK5339	£7.00	TA2025	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK084	£6.50	SIK5361	£4.60	TA2029	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK086	£6.50	SIK5362	£4.60	TA2030	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK092	£6.50	SIK5451	£5.00	TA2030	£0.90	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK093S	£9.50	SIK5461	£8.50	TA2161	£5.00	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK093S	£9.50	SIK5471	£4.20	TA2270	£2.65	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK094	£4.50	SIK5481	£4.50	TA2320	£2.65	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK094S	£4.50	SIK5482	£4.00	TA2340	£2.00	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK095-2	£4.40	SIK5730	£6.00	TA2377	£1.75	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK095-2	£4.40	SIK5730	£6.00	TA2377	£1.75	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK096	£2.20	SIK5731	£5.80	TA2377	£1.75	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK096	£2.20	SIK5731	£5.80	TA2377	£1.75	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK096	£2.20	SIK5731	£5.80	TA2377	£1.75	BC211	£0.06	2SC2817	£1.95	2SC3128	£3.30	JVC FERG 3HSV	£6.40	3V35 TAKE UP CLUTCH	£1.65
SIK096	£2.20	SIK5731	£5.80	TA2377											

undertaking that's not too easy even with the manufacturer's instructions to hand. Fortunately very little trouble is experienced in this section of the machine.

Two tuners have been used in these machines, types TEEB1X032A and UE30-B03. They are interchangeable.

Spares for the Matsui/Saisho range are available from CPC, Chas. Hyde, HRS Electronics and Mastercare.

---

# A Video Nasty

**Nick Beer**

A VCR fault I had recently could contend with some of Steve Beeching's and no doubt many others' for the video fault of the year title. The machine involved was a Panasonic NV-FS1B. It's a first-generation S-VHS VCR that uses the G mechanism, not that the mechanism had anything to do with the fault.     3

## Symptoms

As the customer was an AV technician at a local school he had enough technical background to be able to give a fairly accurate description of the symptoms. The main symptom was a vertical bar about a inch wide at each side of the playback picture, approximately one and a quarter inches in from the side of the screen. When the playback picture had dark areas, falling to black level, at the edge the bars took the form of a blue cast. As the video level in these areas increased, the colour of the bars changed, becoming orange/yellow at white level. In addition, at or near black level a third bar could be seen about an inch from the left-hand one. This bar had no chroma content – it looked more like a parasitic oscillation. The fault was present on playback only: recordings made on the machine and played back via another one were perfect.

But this was only one of the symptoms! When a tape with high chroma content was played chroma phase inversion occurred, e.g. highly saturated reds/oranges became green. The saturation had to be high for this to happen: when the colour-bar section of the Panasonic test tape was played only slight errors were present – the chroma was smeary, shifted and weak but no inversion occurred. I used a known good machine to record the colour bars, with a high level of chroma, from our colour-bar generator. When these were played back there was chroma inversion.

The symptoms were worse when the machine was in the LP mode and worse still in S-VHS.

## Fault Tracing

The cause of the fault was likely to lie in a common playback area, so large chunks of the circuitry could be ruled out as being unlikely to be involved. This done, there was still a large area for investigation. I decided that the symptoms probably had a common cause, and also that I would find it much more easily by concentrating on the first symptom. The luminance/chrominance signal processing circuitry in this model is extremely complex in block diagram form, let alone by reference to the circuit diagram. As a start, I played back a blank raster and scoped the chroma output from the head amplifier. The output was as expected: pretty inert and, most significantly, flat across the line period. The signal is

buffered on the main PCB and is then fed to pin 32 of the YC module, where it goes to pin 13 of the hybrid chip IC801. Scope checks showed that the signal was o.k. up to this point.

The chroma signal output from the hybrid chip is at pin 11. At this point spikes could be seen on the line-frequency chroma display, corresponding with the bars on the picture. The circuit here becomes common to the record and playback signals – the record chroma passes through a 1kΩ resistor on the hybrid chip, leaving at pin 9. I disconnected pin 9 to eliminate any possible problems here. Now an optimist would check for such things as a noisy supply to the chip, then try a new chip. Being one I did just this, and of course it didn't make the slightest difference.

Checks around the hybrid chip failed to reveal anything new, so I came to the conclusion that a fault upstream was introducing an incorrect impedance in the chroma signal's path. One interesting factor I discovered, purely by chance, was that very slight pressure just behind the exit guide, effectively increasing the tape wrap length, removed the symptoms from the screen. This was presumably due to altered chroma signal level.

I was left pondering theoretical possibilities, and was also considering the second symptom – the phase problem. Before I wasted too many more hours I decided that consultation with Panasonic was a sensible step. The local branch hadn't experienced such a problem, but the engineer I spoke to was intrigued by the symptoms and offered to take the machine off my hands. That would have meant that I couldn't write about the fault when I did find its cause, so I declined the offer, at least temporarily!

Further thought led me to suspect delay line trouble, or a capacitor or inductor fault. Bridging or checking suspects proved only that they weren't at fault. A call was then made to Bracknell to enquire whether this fault had been experienced. The answer was no, but the engineer went away for ten minutes to consult with his colleagues. When he got back he confirmed my first suspicion, that the 2H delay line DL802 could be responsible.

Panasonic viewdata said that there was no such part number (EFDHR124A13S). Our storeman consulted Panasonic spares who consulted Japan. A delivery time in weeks was being talked about. While all this was going on I discovered that the same device is used in the Panasonic NV-G25. One was swiftly removed from a stock machine and fitted in the faulty one. Lo and behold, a complete cure! When the cover was removed from the faulty delay line a quarter inch crack could be seen in the glass. Very strange, as the device is mounted in a fairly central position and there was no suggestion that any shock had been applied.

## Panasonic Comment

Shortly after this incident I attended a Panasonic seminar on camcorders. A point made was that one of two nasty problems with video equipment had been traced to damaged delay lines . . .

## Salora J Chassis

On a different subject, Steve Cannon in his article "Gremlins and Gurus" in the July issue mentioned DB712 in the Salora J series chassis' power supply. In a previous article I mentioned that it can go short-circuit, which is the usual thing that happens. But like Steve I too have had it go open-circuit on occasion.

# Long-distance Television

Roger Bunney

The 1991 Sporadic E season has turned out to be rather quiet. There have been numerous openings for those able to monitor Band I during the day, but for those of us whose time is limited reception has been infrequent. Tropospheric activity has been present but reception has been limited mainly to the south and east coast areas. The following SpE log looks respectable enough, but remember that it's a collated log based on a number of reports.

- 5/7/91 TSS (USSR) chs. R1, 2; SVT (Sweden) E2; NRK (Norway) E4; TVP (Poland) R1; RAI (Italy) IA; TVE (Spain) E2, 3, 4.
- 6/7/91 RAI IA; TVE E2, 3; NRK E2; TVP R1; DR (Denmark) E3; CST (Czechoslovakia) R2.
- 7/7/91 RAI IA; TVE E2, 3; TVE-2 E2; DR E3; C+ (France) L2.
- 8/7/91 SVT E2; RAI IA.
- 9/7/91 TVE E4.
- 11/7/91 SVT E2.
- 12/7/91 RAI IA, B; TVA (Italy) IA; TVE E2, 3, 4; TVE-2 E2; MTV (Hungary) R1; NRK E3; JRT/RTV (Yugoslavia) E3, 4.
- 14/7/91 TSS R1, 2; RAI IA; TVE E2, 3, 4; MTV R1, CST R1.
- 15/7/91 RAI IA, B; RTP (Portugal) E3; TVE E2, 3, 4; TVE-2 E2.
- 16/7/91 RAI IA, B; TVE E3; YLE (Finland) E3, 4; NRK E3; SVT E2, 3, 4; RUV (Iceland) E4; TSS R1, 2.
- 17/7/91 TVE E2.
- 18/7/91 RAI IA, B; EPT (Greece) E3; C+ L3.
- 19/7/91 RAI IA, B; TVE E2; MTV R1; JRT/HTV E3.
- 20/7/91 TVP R1; TSS R1, 2; TVE E3, 4; RAI IA.
- 21/7/91 TVP R1; TSS R1, 2, 3; SVT E2; NRK E2; CST R1; RAI IA; TVE E2, 3, 4; ORF (Austria) E2a.
- 22/7/91 ORF E2a; JRT/HTV E4; TSS R1; TVE E2, 3, 4; +PTT (Switzerland) E3; ARD (W. Germany) E2, 3.
- 23/7/91 RAI IA; TVE E2, 3, 4; C+ L3; TSS R1, 2, 3; CST R1.
- 25/7/91 TVE E2, 3, 4; +PTT E2; SVT E2.
- 26/7/91 TSS R1-5; YLE E3, 4; SVT E2; NRK E2, 3, 4; RUV E3; +PTT E2; TVP R1, 2, 3; MTV R1, 2; ORF E2a; RTSH (Albania) IC; TVE E2, 3, 4; ARD E2, 3; JRT E4.
- 27/7/91 RAI IA, B; +PTT E2; C+ L2, 4; TVE E2, 3, 4; ARD E2; CST R1; MTV R1; SVT E2; DR E4; RTP E3; TVE E2, 4; TSS R2.
- 28/7/91 RAI IA, B; TVE E2, 3, 4; C+ L2; TSS R1, 2; NRK E2, 3; SVT E2.
- 29/7/91 TVE E3; JRT/HTV E3.
- 30/7/91 RAI IA.
- 1/8/91 JRT/HTV E3, 4; TVE E2; RAI IA; CST R1.

Tropospheric lifts occurred on July 4/5th, with reception from Norway, Denmark and W. Germany; on July 10/11th with reception from W. Germany in the north east; on July 13-16th with reception from Denmark, Sweden, Norway and Germany along the east and south east coasts; on July 23rd with reception from the Benelux countries; and on the 28/29th with reception from Denmark, Germany the Benelux countries in the east and south east.

Thanks to Simon Hamer (Powys), Peter Schubert (Rainham), Roger Fussell (Torpoint), David Glenday (Arbroath) and Brian Williams (Penarth) for sending in reports to supplement my own log.

Veteran TV-DXer Nick Brown (Rugby) recently moved and has installed a new aerial system. At u.h.f. he is using two stacked Wolsey Colour King aerials with the outputs combined and fed to a Labgear CM7271 head amplifier. For Band III a wideband, eight-element Jaybeam ABM8 feeds a Fringe Electronics v.h.f. 1220-3 head amplifier with a gain of 20dB and a 1.8dB noise figure. Beneath this there's a combined Band I/II aerial for SpE reception. Indoors an HS Publications D100 unit converts the v.h.f. signals to u.h.f., feeding a Toshiba colour receiver. The aerials are four metres above the roof. Initial results indicate that the system is working well: with just a slight tropospheric lift low-level Band III/u.h.f. signals are received from Germany, France, Ireland and the Benelux countries.

The mystery 525-line ch. R1 signal that's been received several times in the UK during periods of intense F2 propagation and is thought to originate in the Far East has, it seems, now been received by Robert Copeman in Australia. He recorded a 525-line ch. R1 signal on May 5th and reports that its strength was such that it overrode other, simultaneous Chinese transmissions on ch. C1. Unfortunately only pictures were seen, with some writing in the lower right-hand corner. Clearly the signal is coming from somewhere in S.E. Asia. Does anyone have any suggestions as to its source?

## News Items

**Ireland:** The 1990 Broadcast Act may be amended shortly. It was intended to redistribute advertising by imposing restrictions but simply seems to have led to losses by RTE and could affect the viability of the proposed TV3 commercial network. RTE is considering the possibility of distributing a programme consisting of RTE1/2 material to

## AERIAL TECHNIQUES


### SPECIAL PRODUCTS FOR TV-DXING

**5" Screen B&W TV with AM/FM Radio**



Ideal for TV-DXing, covers Band 1, 3 & UHF. 3-way power source; Mains; 12v DC (lead included) or dry batteries, completely portable. **£89.95** inclusive of Vat. Carriage & Insurance £6.50

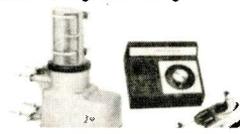**AR300XL Aerial Rotor, Control Unit & additional Alignment Bearing.**



Vertical load carrying 45kg, takes 2" main mast, 1 1/2" stub mast. **£44.95** inclusive of Vat. Additional Alignment Bearing **£18.60** inclusive of Vat. P. & P. on Rotor £3.50.

**NEW Compact Combined B1/3 Array for TV-DXing.**  
Total Length only 4ft 10in.



Complete with folded dipoles for both Band 1 and Band 3 for optimum performance. Covers Band 1 (47-70MHz) at 3.5dB gain. Band 3 (175-230MHz) at 8dB gain. **£44.50** inclusive of VAT. Carriage & Insurance £6.50

**VHF to UHF Upconverter, Model 3638**



Converts input band of 40-230MHz to equivalent bandwidth at UHF. Ideal for TV-DXing with a domestic TV. **£49.95** inclusive of Vat, post & pack ng

Aerial Techniques, the company that knows the TV-DXing hobby. We stock a large range of equipment for all types of aerial installation, all detailed in our 29 page **Catalogue at 75p**, why not send for your copy today. We also have available Multi-standard TV's and Video recorders for all systems. **PAL, SECAM & NTSC**. Most makes of Satellite equipment carried, together with decoders for **Canal Plus, RAI UNO, RAI DUE, PAL/D2-MAC** Satellite receivers now in stock, also **SECAM to Pal** Transcoders (SAE details).




**SPECIAL PRICE!!! UNIDEN UST-92 D2-MAC to PAL Decoder** ..... £399.00 + VAT, free delivery (SAE for details)

ACCESS

ACCESS, VISA & AMERICAN EXPRESS  
Mail & Telephone orders welcome (24hr service)

BANGLAYCARD  
VISA

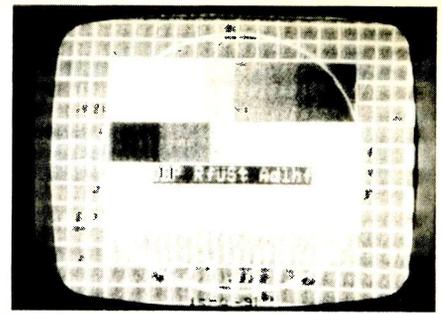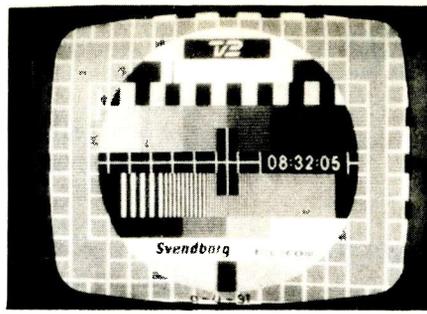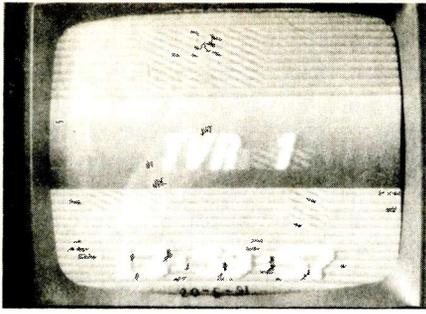**11, KENT ROAD, PARKSTONE, POOLE, DORSET BH12 2EH**  
Tel: 0202 738232 Fax: 0202 716951



Left: SpE reception of TVR 1 (Rumania) in Holland. Centre: New Danish TV2 network test pattern identification, received on ch. E32. Right: German test pattern, generally used by ex-DDR1 transmitters. Photos courtesy Ryn Muntjewerff.

cable systems in the UK via satellite. There could also be a dedicated Irish sports channel.

**Denmark:** The TV2 network has run into financial difficulties and might be forced to close this December. The government has refused to provide more funds.

**Lithuania:** A new independent TV service is called Nepriklausomas Lietuvos Televizija (NLTV), which translates as Independent Lithuanian Television. Satellite derived material from SAT-1, Tele 5, Childrens' Channel etc. plus a one-hour (1700-1800) CNN news programme is used. Currently the Vilnius service is on ch. R10. The USSR-based service continues on ch. R2 from 1800. Technical problems are common: the test card is type UT0167, rarely with any identification.

**Ukraine:** The CT-2 network transmitters are now broadcasting locally produced programmes with CT-2 infilling.

**Czechoslovakia:** A new high-power transmitter is in operation at Chomutov, on ch. R52, near the German border. The Slovakian region now receives a service called TA3 via the former OK3 transmitters. Programme content is part satellite, part local with a CNN programme at night. The unlicensed independent NTV service has closed down but has applied for a licence to restart.

**Hungary:** The NAP-TV breakfast show (0600-0900) has moved to MTV-2.

**Korea:** An expansion of the TV services over the next nine years is planned. Another three channels are to be made available via satellite by 1994 while the US Forces' AFKN-2 service is to be taken over in 1993. By the end of the year six nation-wide TV networks will be in operation, including Seoul TV which opens this autumn.

**New EBU Listing:** Berlin Schaeferberg ch. E56, 100kW horizontal, carrying ARD-4 with directional aerial aimed at 70° into the eastern part of Germany.

### 50MHz Amateur Band

The following reports come by courtesy of *Six News*. At 1536GMT on April 29th, during an intense auroral event, Scottish amateur GM3WOJ contacted Jorge DeCastro, CX8BE, in Uruguay using s.s.b. The distance of 7,063 miles is a new world record for auroral operation. Actual frequency was 50-14MHz. It's possible that propagation was partially by TE/F2 into the auroral curtain, but anyway it was a very fine achievement.

Solar cycle 22 continues, but with the peak now passed and a slow decline. F2 and auroral activity should remain high during the rest of the year however. The sunspot minimum with this cycle will occur in 1996: the peak count was a smoothed 158.1 in July 1989.

Yugoslavia now allows amateur operation in the 50-50.9MHz band on a secondary user basis. Maximum

output levels are 10dBW urban, 20dBW rural. Turkey also allows limited operation within the area 40°E to 40°N. Limited operation is to be allowed in Poland from next year, in areas where there are no Band I TV transmissions.

### Satellite TV

New regulations for satellite TV aeriels have been issued by the Department of the Environment (see Teletopics last month, page 799). The larger size of dish (90cm) can be used to the west and north of a line that runs approximately from Devon through West Glamorgan and Manchester to Humberside. If you are on the east/south side of this line planning permission will be required for a tracking dish of say 1m diameter mounted on a house. Provided a garden sited dish is not too obtrusive and isn't of over 2m height it should fall within permitted development under the terms of the Town and Country Planning Act, since sheds and fencing are permitted provided they don't exceed 2m.

The French company Clinvest has provided Super Channel with financial assistance worth over £20m to enable the services and presentation to be revamped.

Satellite Japan Corporation intends to launch two satellites by 1994 and offer carriage of domestic communications and TV services. It will be the third Japanese telecommunications company to enter this field. Each satellite will have 24 transponders operating at up to 50W output. The Japanese BS3a satellite has lost power due to solar panel faults. As a result only two of its three transponders, carrying NHK and JSB TV, are in operation - there will be no back-up until BS3b comes into operation.

A press statement has been issued by SES following rumours about possible solar panel problems with the Astra 1B satellite. It states that 1B has not lost a solar array and that no transponders have been switched off to save power - neither has Astra 1A lost the use of any of its back-up transponders.

Russia is to place a fourteen tonne space platform in orbit next year, carrying telecommunications equipment for TV relay. Another two platforms, each weighing eighteen tonnes, are to be placed in orbit by 1997, giving a total downlink capacity of thirty TV channels.

Telecom Eireann has opened an earth station at Elfordstown near Cork. More earth stations are coming into operation to work with the Eutelsat system, the latest being at Lario near Milan. Stations in Yugoslavia and Rumania are due to open during the coming year.

The Eutelsat II F5 craft will be launched in October 1992. The 13°E II series craft has been carrying HD-TV test transmissions between Thomson's Paris plant, Philips at Eindhoven and ITT Nokia in Finland.

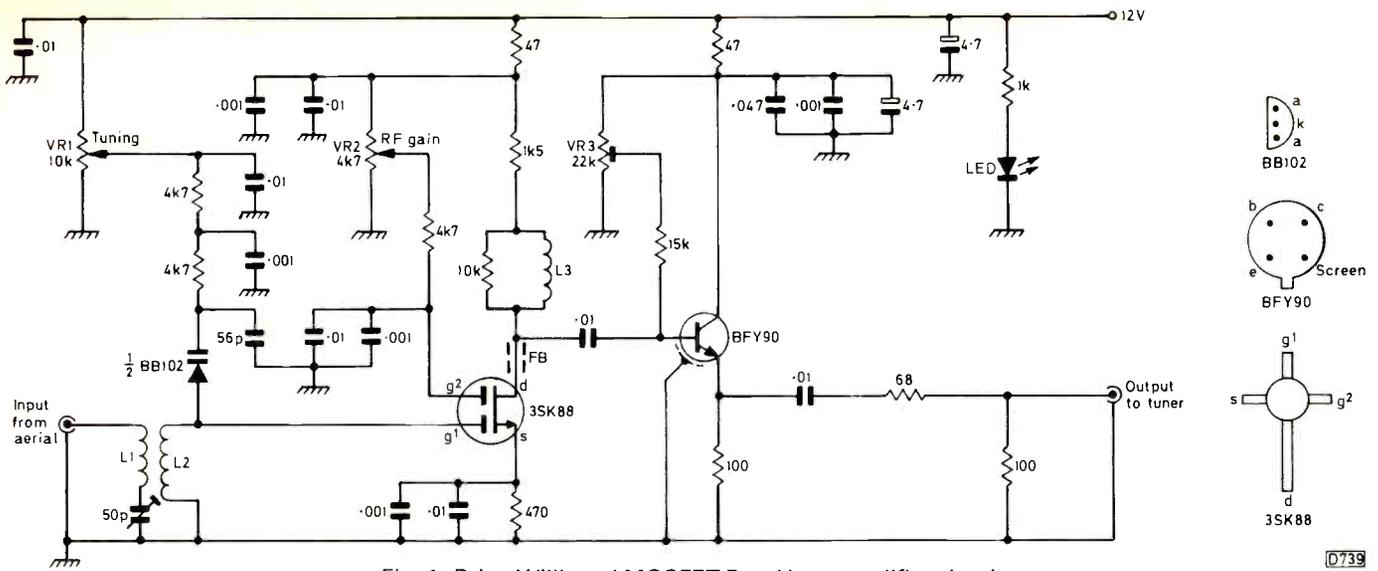


Fig. 1: Brian Williams' MOSFET Band I preamplifier circuit.

The European Commission is backing the Euronews project which will provide a centralised TV news service for the EBU region.

It's hoped that the Telecom 2A satellite, to replace the seven-year old 1A craft, will be launched by the end of the year in time for the winter Olympics. Funding is shared between France Telecom (60 per cent) and the French Defence Ministry (40 per cent).

### Band I Preamplifier

Brian Williams has come up with the interesting Band I preamplifier circuit shown in Fig. 1, based on a tuned input MOSFET with a gain control. The advantage of having a tuned input is virtual elimination of cross-modulation (overload) problems from nearby transmissions. I've no performance figures but Brian comments that it's excellent in terms of optimum gain with minimum noise. He says that the absence of noise on the screen when the amplifier is tuned to resonance with the aerial removed is striking,

and that the stability over the band is excellent – with the coil as specified, the coverage is 40-78MHz. The BFY90 transistor provides buffering and improved matching into the 75Ω output. The varicap diode used is one of a matched pair in a common encapsulation. Take the usual care over construction. The prototype was built inside a tobacco tin with an earthed screening strip across the MOSFET to maintain stability – the subminiature ceramic plate capacitors are soldered directly to this strip.

Coil L2 consists of eight and a half turns of 16 s.w.g. copper, air cored with a diameter of half an inch. The coupling coil L1 consists of one and a half turns of thin flex at the end of L2 (not over it). Two 25pF trimmers are used at the input where the circuit shows a single 50pF trimmer. L3 is an r.f. choke consisting of ten turns wound on the associated 10kΩ, 0.25W resistor. VR3 should be adjusted for the best signal/noise performance with a stable, weak signal. When correctly set the voltage at the emitter of the BFY90 transistor should be approximately 0.8V.

## Service Briefs – Pioneer

The following repair tips and modification notes have been compiled from recent Pioneer service communications.

### CDV/Laservision

**Model CLD1450:** To overcome analogue audio dropouts add a 1μF, 50V electrolytic capacitor between the 5V rail and the end of R828 nearest to connector CN10. Do this on the component side of panel ASCB, which is the lowest of the three PCBs. A wire link marked +5V will be seen just above and to the right of connector CN10. This is the supply connection point for the capacitor.

### CD Players

**Models PD4500/4550/5500:** If the swing lever (item 105, page 11 in the service manual) is bent or has jumped out of the rack (item 7) the tray won't open. This tends to happen as a result of rough handling while being transported. If the

lever can be reshaped or refitted this can be done, but there's an improved version (part no. PNB1225). When the repair has been completed, disconnect the mains supply with the tray open. Then gently push the tray shut. This leaves the swing lever in its lowest position where it's less liable to damage in transit.

**Models PDX303/707/909, PD5010/6010/7010, M6:** To cure intermittent skipping add a magnet (part no. PMF1001) adjacent to the shaft of the spindle motor. Glue the magnet in position as close as possible to the shaft without fouling it. If this problem is experienced with discs that last over an hour, add rubber sheets to the clasper holder arm – part nos. PEB336 (large) and PNM054 (small). If the problem is experienced in conjunction with mechanical sensitivity to vibration, fit modified floating mechanism cushions: replace the four existing PEB293 cushions with part no. PEB321 (grey colour) in the rear right-hand corner and part no. PEB320 (black) in the other three corners.

**All models:** When removing the operating bar or front panel it's important to take care of the mains switch. To remove the bar from the switch shaft, always have the switch in the off position, then lever the bar off gently using a flat bladed screwdriver – otherwise the switch latch will be damaged. Always remove the bar before removing the front of the machine.

# TV Fault Finding

Reports from Brian Storm, Paul Hardy, Stephen Leatherbarrow, Michael Dranfield, J. Edwards, J.K. Potts and John C. Priest

## Panasonic TC1485 (Z3 Chassis)

"Dead set" the job card said. Well not quite: the main h.t. rail was up and running, but there was not much else. The l.t. supply from the chopper transformer T801 was quite low. This usually indicates that the power supply is running at the wrong speed because of no line drive. A check at pin 15 (X-ray protection) of the M51407SP i.f./colour decoder/timebase generator chip IC101 confirmed that the protection circuit was in operation, as there was a voltage there. After disconnecting various feeds to the sensing circuit transistor Q502 was pronounced guilty. But why? After much voltage checking in the associated circuitry R560 (270k $\Omega$ ) was found to be open-circuit. **B.S.**

## Panasonic TX28A2 (Alpha 3 Chassis)

The complaint with this set was that it would go off after about three and a half hours. So I left it to run. Just as Graham Gooch came out to bat two and a half hours later the picture went black, the bottom third went white, the top third broke into white lines, the bottom half went green then the whole raster went bright white. The power supply next shut itself down with a scream of agony. I went across and switched the set back on as Graham Gooch watched the first ball of the day sail harmlessly over his head. Atherton went back to the pavillion, closely followed by Graeme Hick and Allan Lamb, then just as Robin Smith walked out to bat the set performed its pyrotechnics again and shut down.

I removed the back and gazed in awe at the congested inside of this monitor-style set. Where to start? The vertical circuit boards were all securely plugged into the main boards. Fortunately my eye was drawn to a large silver heatsink at the bottom of the set. The clip that should have been holding IC891 to its heatsink hung loosely across it. I gratefully refitted the clip, put the back on and left the set to run. It was still working perfectly later that afternoon as Robin Smith completed his century. **B.S.**

## Panasonic TX21T1 (Alpha 2 Chassis)

There was no sound from this set. The voltages around IC253 seemed to be within reason but there was no life and the situation didn't feel like a faulty chip. As the voltage at pin 2 seemed to be slightly low I disconnected C269. Up came the sound. C269 (10nF, 50V) read about 3k $\Omega$  when checked with my meter. **B.S.**

## Grundig C2402 (CUC51KT Chassis)

This set was dead – in fact the 124V line was low. No obvious shorts or leaks could be found. Eventually I discovered that D656 (BYW76) was going high forward resistance under load, though it read o.k. when tested with a meter. **P.H.**

## NordMende SC7732

Bright flyback/teletext lines were present over the first couple of inches of the field scan. Much time was wasted making checks in the first anode and blanking circuits on the tube's base board, which proved to be blameless. The

cause of the fault was eventually traced to C57 (1 $\mu$ F, 50V) in the field timebase module. It had gone low in value. Note that this capacitor is present with only certain modules – several different types were used in these sets. **P.H.**

## Philips K35 Chassis

The complaint was that the set wouldn't lock to channels in the search tuning mode. What struck me immediately was that with no signal present the line oscillator sounded way off frequency. Changing the TDA3571BQ oscillator chip provided a cure. **P.H.**

## Philips K40 Chassis

This set arrived with a blank raster. Advancing the setting of the first anode control showed that the cause was field collapse. The field output chip was short-circuit while its l.t. feed resistor R3186 was open-circuit. When these items were replaced we still had problems however. For the first ten minutes the lines at the top of the screen were expanded. Thereafter normal service was resumed. Freezer and a hairdryer brought us to C2107 (100 $\mu$ F, 50V) which was partially open-circuit. **S.L.**

## Grundig CUC120 Chassis

Very severe patterning that varied with the brightness was soon traced to ripple on the 19V rail. C662 (470 $\mu$ F, 25V) was completely open-circuit. **S.L.**

## Doric CU36502D

This set seemed to be fitted with a Sharp chassis of a type we've not seen before. The fault was field collapse. Checks showed that the voltages around the field output transistors were incorrect, with little bias applied to Q502. R513 (1.2k $\Omega$ , 1W) was found to be open-circuit. As a precaution we also replaced both output transistors (Q501/2). **S.L.**

## Hitachi CPT2176 (G6P Chassis)

This set was dead with just a low-frequency whine from the power supply. We found that the voltage at the collector of the line output transistor Q781 was low. The cause was C909 (220 $\mu$ F, 160V) which smooths the output from the chopper power supply. **J.E.**

## Hitachi CPT1474

This set greeted me with a very bright raster and no sound when I switched it on. Within three seconds the power supply tripped and screamed. When I next switched the set on I turned down the first anode control. This time the set remained on but still had an over-bright raster and no sound. A check at the collectors of the RGB output transistors showed that the voltages were only 40V, though there was 200V at the line output transformer. It seemed that the RGB output transistors were conducting heavily, so the drives from the TDA3565 colour decoder chip IC501 were disconnected. Up came the collector voltages

and out boomed the sound. A new TDA3565 cured the problem. **J.E.**

### Saisho CT141X/Matsui 1420A

This set was dead but the usual faulty bits were o.k. This time C508 (4.7 $\mu$ F, 50V) in the STR50103A's start circuit was found to be low in value. Replacing it restored normal operation. The fault can also be caused by R502 (100k $\Omega$ ) or R503 (82k $\Omega$ ) in the start supply. **M.Dr.**

### Hitachi CPT1474/1646

No picture, no sound and no field scan is a simple fault. Not so when you don't have the manual! With a CPT1646 that came in the 12V supply was found to be missing in places. The cause was an open-circuit 0.47 $\Omega$  safety resistor, R228. We've had the same problem with Model CPT1474, where the culprit was R222 (same value). **M.Dr.**

### Ferguson ICC5 Chassis

The complaint was of random flashing lines on the screen, but we found that a signal fed in via the scart socket produced a perfect picture. As we've had similar faults caused by the tuner this was our first suspect. We hooked up a rotary tuner from an old monochrome set as a check. This cured the fault, so a new tuner was obtained and fitted – only to find that the fault remained as before. A check on the 11.5V supply to the tuner showed that it was stable and ripple-free. The voltage at the tuning pin was also stable but the scope showed that there was a low-frequency noise component at some 10-20mV peak-to-peak. My first thought was that this was audio noise, but decoupling various points in the audio output circuit made no difference. The surface-mounted capacitors CT01, C103, C105 and C109 in the tuning voltage supply were changed but this had no effect on the fault. What next? In desperation I cooled the U6316 PLL chip IT20. This provided a cure. When IT20 was then heated the fault was back again. A new PLL chip restored correct operation. **M.Dr.**

### Saisho CT141X/Matsui 1420A

For no luminance with these sets check and replace as necessary D602, D603 and D613. Type 1N4148 diodes will do. Also check and/or replace the 2SA733 transistor Q601.

If you have to replace the 5.6 $\Omega$ , 5W surge limiter resistor R501, as you will have to do if the chopper chip IC501 and the over-voltage zener diode D508 have gone short-circuit, use the Amstrad type AM1422138 from CPC of Preston. It's the same but cheaper. **M.Dr.**

### Philips CTX Chassis

There was a very odd fault with this set, bad patterning on the screen. It was like CB radio interference. It went away when the colour was turned down, so something was affecting the chroma circuits. There was no ripple on the 12V supply to the TDA3560 colour decoder chip, and a replacement chip made no difference. While studying the fault over a cup of tea I noticed that the patterning seemed to change in sympathy as people in the picture talked. Something was amiss with the sound rejector trap. Shorting it out made no difference, proving that 6MHz sound was entering the colour decoder chip. A replacement obtained from a scrap set provided a complete

cure. When the old one was examined the coil's continuity was found to be o.k. so I came to the conclusion that the internal series tuning capacitor was open-circuit. **M.Dr.**

### Ferguson TX100 Chassis with Teletext

The problem was loss of memory: the set had to be retuned every time it was switched on. Visual inspection of the panel didn't reveal anything amiss and the i.c. voltages all appeared to be correct. The next logical thing to do seemed to be to replace the M293B1 tuning memory and control chip IC7. A new one provided a complete cure. **J.K.P.**

### Some Quickies

**Ferguson TX90 chassis:** No field output was caused by dry-joints on TR105 (TIP112H) at the rear of the central heatsink.

**Philips CTX-E chassis:** No sound was caused by absence of the l.t. supply to the audio output chip. R3170 (3.3 $\Omega$ ) was open-circuit for no apparent reason.

**Ferguson TX9 chassis:** Intermittent operation was due to dry-joints at the collector of the line output transistor TR68, where the struts enter the PCB. **J.K.P.**

### Bush 2114/2020

For fizzing or squealing from the chopper transformer at switch-on, possibly dying away after a few minutes or alternatively continuing for much longer, accompanied by fine tearing of verticals in the picture, replace C818 (1 $\mu$ F, 50V). It decouples the set-h.t. potentiometer.

If the set seems to be dead but the fuses are o.k. check R422 (1 $\Omega$ , 1W safety type) in the line output stage. It feeds the 16V rectifier and in turn the LM7812 12V regulator, which supplies the TDA2579 chip where the line oscillator resides. TH801 and R817 (5.6k $\Omega$ , 0.5W) in the power supply start-up circuit are other possibilities. **J.C.P.**

### NEC 3022E

Apart from a few cases of dry-joints where the 15-pin decoder input/output socket is soldered to the main PWB(B) these satellite TV receivers have proved to be pretty reliable. This is the first actual fault I've had. The complaint was of "flashing on the picture", and sure enough soon after the set was switched on from standby there was a white flash across the screen – a band about 1mm high, the full width of the screen. At the same instant there was a "tick" from the sound. The symptoms recurred at about two to three second intervals and were present on all channels, the effect being similar to that when an unsuppressed fridge or central heating thermostat switches off. The repetition rate ruled out this possibility of course.

The LNB supply was steady, so a spare receiver was used to check the LNB/dish/cable part of the installation. As expected, the results were perfect with no trace of flashing. We left the spare receiver and took the one that was clearly faulty back to the workshop. When it was connected to our own dish the fault was immediately visible, so after a quick check on the five main outputs from the power supply attention was turned to the tuner unit. We then noticed that on some channels there was a noticeable falling off in picture quality and an increase in picture noise during the half second or so before each flash, when the signal sprang back to normal before

restarting its slow decline.

The tuner's supply voltages were stable and although there was a slight variation at the two a.g.c. terminals it was not until the a.f.c. was monitored that I struck gold: the voltage at this pin was swinging in time with the ticks and flashes. Tracing back from the a.f.c. pin took me via pin 7 of socket VC to the microcomputer chip IC1001 on Main PWB(A). The a.f.c. voltage at pin 39 of this chip should be a steady 2.7V. In this case however it was swinging between zero and 3V in time with the flashes. Since the connection between the tuner and IC6001 is a direct path, pin 39 was isolated by disconnecting the link between the two boards (pin 7 of connector VC). The voltage at pin 39 continued to vary so a replacement  $\mu$ PD1700CU-520 chip was ordered from SEME. Fitting it provided a complete cure.

J.C.P.

# TEST CASE

## 346

*Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

Most of the equipment that's featured in these Test Case items is middle-aged, simply because that's what we mainly see on the bench. This month's tale relates to a brand new machine however, though the point it illustrates is relevant to most makes and vintages of VCR. To solve this puzzle it's not necessary to have the service manual: the main thing is to know where to look!

The machine involved was a Sony SLV777, which is a VHS home deck with two speeds, hi-fi and editing facilities. It had been delivered to a customer new but had to be retrieved the very next day because of a colour problem. As there wasn't another of these machines in stock the repair had to be done pronto. The symptom showed up with the Eastenders recording that was still in the machine: the colour was very poor and grainy and was strewn with confetti. The underlying black-and-white picture was clean and noise-free however.

As the tape was the machine's own recording a known good tape was played back. The results were the same: luminance fine, colour saturation about correct, but grain and noise speckled the coloured areas of the picture. Head cleaning didn't improve the results obtained. The next step we took was to narrow down the field of search by checking as many modes of operation as possible.

A recording of colour bars was made in the SP and LP modes. The tape was rewound and then played back using another dual-speed machine. At both speeds the colour was bright and clear. Playback via the faulty machine gave noisy chroma in both modes. So the trouble was confined

to playback and was present with both standard and long-play operation. Having established the exact symptom, it was time for diagnosis. It then emerged that almost everyone in the workshop had virtually no knowledge of VHS (or any other for that matter) colour signal processing. They all claimed that they'd never had a real colour fault before, which says much about the reliability of this part of a VCR but not much for the lads... The repair became a joint effort, a sort of community project.

Someone suggested that the heads might be responsible, but that was overruled on the grounds that recordings were o.k. and that separate heads were used for the SP and LP modes. Next it was decided that the quality of the output signal at the scart AV socket should be checked. When this was linked to a Sony set's scart port the results were no better. It was thus concluded that the fault lay in the chrominance processing circuitry. An oscilloscope was brought into use, along with a three-hour tape recorded throughout with a colour-bar signal. If the fault wasn't found in three hours we would get a five-minute break while the tape was rewound!

Investigation began on board YC-65, which is where the colour signal processing takes place. IC801 does most of the work here. The chroma signal goes into it and comes out several times, finally emerging at pin 21 after which it goes to the YC adder department. The waveform at pin 21 of IC801 was of correct amplitude but was ragged and noisy.

In which part of the processing circuitry was the fault most likely to lie, considering the symptom? Should we have gone upstream or downstream from IC801? See next month for the answer and another test case item.

### ANSWER TO TEST CASE 345

— page 822 last month —

A surprising amount of fault diagnosis can be carried out successfully in TV sets and VCRs without detailed knowledge of circuit operation and theory. A bit of it would have helped with last month's bench session though! The symptom with the JVC HR-D140 was drum speed runaway, smartly followed by deck shutdown.

The drum servo has two loops, one digital and one analogue — the phase and speed control loops respectively. The relevant one here was the speed control loop, which maintains the motor speed at 1,500 r.p.m. using feedback from the FG (frequency generator) built into the motor. A frequency-to-voltage converter inside the servo chip maintains its input frequency at 1,500Hz, which corresponds with 1,500 r.p.m. If the converter sees no FG signal it drives the motor harder to try to find some.

This was what was happening, but no feedback ever appeared because the FG printed coil leadout had a badly soldered joint. A check with the scope at TP414 or at pin 6 of IC404 would have shown this, and a d.c. continuity check would have provided confirmation. Fortunately with this motor it's easy to remove and repair the FG PCB, which is bolted to the underside of the motor.

The loading mechanism service job would have had to be done sooner or later anyway!

**ELC EAST LONDON COMPONENTS**  
**AUDIO TELEVISION VIDEO**  
**COMPONENTS AT VERY KEEN PRICES**  
**TEL: 081-472 4871 FAX: 081-503 5926**

**REMOTE CONTROLS FROM £12.99**

VIDEO HEADS		VIDEO BELT KITS	
JVC FERUGSON 3H55	£8.50	HITACHI	£1.25
JVC FERUGSON 3H55VA	£19.99	VT-5000	85p
AKAI VS201/301	£18.99	VT-9000	85p
PANASONIC 3H55N	£8.50	VT-9300	85p
PANASONIC NV370	£24.99	VT-52/63/65	£1.75
PANASONIC NV366	£29.99		
PANASONIC NV730	£29.99		
HITACHI VT11/33	£15.99		
HITACHI VT17/35/39	£29.99		
HITACHI VT120/220	£17.99		
FISHER FMPS10910	£16.99		
AMSTRAD PSE11P/PS2	£15.99		
ALBA SENTRA GOLDSTAR	£20.99		
SAISHO HINARI	£18.99		
SHARP VC651	£17.99		
SAMSUNG	£20.99		

**VIDEO IDLERS**

3V29 TAKE UP IDLER	£1.45p	PANASONIC	£1.35p
VT 9000 PLAY IDLER	£2.95p	NV-333	£1.50p
VT 11/14/17	£1.95p	NV-370	£1.50p
VC 0005EZZ	£1.95p	NV-720	£1.50p
VC 0006EZZ	£1.95p	NV-777	£1.50p
VC 651 IDLER ASSEMBLY	£8.99p	NV-2000	£1.25p
NV 370 IDLER	£2.95p	NV-7000	£1.00p
FISHER 615/625 IDLER	£3.50p	NV-G10	£1.10p
AKAI VS105/250	£11.99p	FISHER	£1.10p
FISHER GEAR ASSEMBLY	£5.99p	FVH-905/910	£1.10p
VT 11 CLUTCH ASSEMBLY	£7.99p	FVH-710/725	£1.10p
IDLER TYRES FOR MOST MODELS	50p	AKAI	£1.37p
SHARP REEL MOTOR	£14.99p	VS-2EG/5EG	£1.00p
PINCH ROLLERS FOR MOST MODELS	£2.95p	VS105/250	£8.99p
AMSTRAD MOD. KIT	£8.99p	L.O.P.T.	£21.99p
UNIVERSAL CASSETTE LAMP	50p	TX 90	£10.99p
SHARP CASSETTE LAMP	50p	TX 100	£10.99p
SHARP REEL MOTOR	£14.99p	CT 45	£10.99p
HITACHI MOULDE HM6251	£5.00p	CPT 1474	£11.99p
3V29 TENSION BAND	£1.99p	2174	£11.99p
UNIVERSAL TRIPPLERS	£5.00p	ITT 80R	£10.99p
CIRCUIT PROTECTORS ICP	80p	PHILIPS KT3	£16.99p
TX 10 FOCUS UNIT	£7.99p	40	£16.99p
PHILIPS BACKUP BATTERY	£2.50p	SONY KV2705	£11.23p
ALBA BATTERY .1F 5.5V	£2.99p	HA11423	£22.99p

**ELC EAST LONDON COMPONENTS**  
**63 PLASHET GROVE, EAST HAM,**  
**LONDON E6 1AD. TEL: 081-472 4871**  
**FAX: 081-503 5926 OPEN 9AM TO 7PM.**  
**two minutes walk from Upton Park Tube Station**  
**PLEASE PHONE US IF WHAT YOU NEED**  
**IS NOT LISTED AS WE HOLD THOUSANDS**  
**OF ITEMS IN STOCK**  
**ADD £1 P/P ADD 17.5% VAT**  
**ALL GOODS DESPATCHED SAME DAY**  
**PRICE SUBJECT TO CHANGE WITHOUT NOTICE**  
**VISA ACCESS ACCEPTED. MIN ORDER £5.00**

VIDEO SERVICE KITS FROM		TRANSISTORS	
3V35/3V45 CASSETTE HOUSING	£4.99p	TA7270	250p
VT33/VT65 CASSETTE HOUSING	£24.99p	TA7271	275p
VR46/67 CASSETTE HOUSING	£17.99p	TA7272	260p
3V35 CAPSTAN MOTOR	£22.99p	TA7273	350p
VT11/VT33 CAPSTAN MOTOR	£24.99p	TA7274	260p
		TA7275	400p
		TA7281	330p
		TA7282	260p
		TA7289	480p
		TA7680	480p
		TA8000	200p
		TA820M	310p
		TA950	200p
		TA1515	120p
		TA1670	300p
		TA1908A	100p
		TA1908B	100p
		TA2003	100p
		TA2005	130p
		TA2575	200p
		TA2577	250p
		TA2581	200p
		TA2593	150p
		TA263A	150p
		TA3560	200p
		TA3562	260p
		TA3565	300p
		TA3651	250p
		TA3652	290p
		TA4500	360p
		TA4503	300p
		TA4600	300p
		TA4740	300p
		TA8180	500p
		TA9503	240p
		UPC1031	180p
		UPC1181	110p
		UPC1182	110p
		UPC1183	230p
		UPC1189	275p
		UPC1225P	210p
		UPC1230	210p
		UPC1232	230p
		UPC1277	240p
		UPC1278	240p
		UPC1318	240p
		UPC1318	240p
		UPC1363	210p
		UPC1370	200p
		UPC1378	200p
		UPC1480	200p
		UPC1482	200p
		UPC1484	200p
		UPC1486	200p
		UPC1488	200p
		UPC1490	200p
		UPC1492	200p
		UPC1494	200p
		UPC1496	200p
		UPC1498	200p
		UPC1500	200p
		UPC1502	200p
		UPC1504	200p
		UPC1506	200p
		UPC1508	200p
		UPC1510	200p
		UPC1512	200p
		UPC1514	200p
		UPC1516	200p
		UPC1518	200p
		UPC1520	200p
		UPC1522	200p
		UPC1524	200p
		UPC1526	200p
		UPC1528	200p
		UPC1530	200p
		UPC1532	200p
		UPC1534	200p
		UPC1536	200p
		UPC1538	200p
		UPC1540	200p
		UPC1542	200p
		UPC1544	200p
		UPC1546	200p
		UPC1548	200p
		UPC1550	200p

250p	25A-726	25p	25B-548	40p	25C-1345	30p	25C-2238	60p	25D-523	150p
275p	25A-733	20p	25B-554	350p	25C-1359	20p	25C-2240	25p	25D-525	70p
260p	25A-748	20p	25B-557	300p	25C-1368	40p	25C-2274	30p	25D-526	70p
350p	25A-755	300p	25B-558	300p	25C-1382	40p	25C-2275	50p	25D-560	50p
260p	25A-769	130p	25B-560	35p	25C-1383	35p	25C-2278	75p	25D-570	40p
400p	25A-771	130p	25B-561	20p	25C-1384	35p	25C-2320	25p	25D-571	30p
330p	25A-777	50p	25B-562	35p	25C-1383	30p	25C-2335	120p	25D-592	20p
270p	25A-794	60p	25B-564	70p	25C-1398	70p	25C-2371	45p	25D-600	80p
260p	25A-798	50p	25B-566	110p	25C-1399	60p	25C-2427	80p	25D-611	20p
480p	25A-817	25p	25B-568	40p	25C-1403	25p	25C-2440	70p	25D-612	40p
480p	25A-841	60p	25B-569	240p	25C-1413	240p	25C-2458	30p	25D-613	450p
50p	25A-844	15p	25B-569	75p	25C-1447	20p	25C-2482	40p	25D-636	25p
50p	25A-861	50p	25B-568	325p	25C-1445	250p	25C-2500	30p	25D-637	25p
120p	25A-872	20p	25B-568	40p	25C-1446	60p	25C-2501	85p	25D-639	25p
250p	25A-893	15p	25B-562	40p	25C-1447	75p	25C-2502	90p	25D-641	310p
300p	25A-896	35p	25B-563	50p	25C-1454	320p	25C-2537	450p	25D-666	25p
100p	25A-899	60p	25B-561	20p	25C-1473	30p	25C-2546	70p	25D-669	25p
130p	25A-905	20p	25B-564	25p	25C-1475	45p	25C-2555	150p	25D-687	60p
200p	25A-915	30p	25B-567	30p	25C-1490	25p	25C-2564	230p	25D-716	120p
250p	25A-916	30p	25B-568	55p	25C-1509	45p	25C-2565	260p	25D-718	130p
200p	25A-917	35p	25B-569	40p	25C-1514	40p	25C-2570	50p	25D-721	150p
150p	25A-921	10p	25B-573	80p	25C-1520	60p	25C-2575	25p	25D-725	350p
150p	25A-940	50p	25B-581	250p	25C-1550	60p	25C-2577	125p	25D-745	250p
200p	25A-950	25p	25B-586	250p	25C-1567	60p	25C-2579	120p	25D-748	150p
300p	25A-958	70p	25B-588	130p	25C-1568	60p	25C-2580	175p	25D-761	30p
260p	25A-962	60p	25B-595	325p	25C-1573	40p	25C-2581	200p	25D-773	50p
300p	25A-964	65p	25B-705	200p	25C-1627	80p	25C-2582	40p	25D-781	30p
250p	25A-965	30p	25B-716	30p	25C-1665	60p	25C-2603	20p	25D-788	30p
290p	25A-966	25p	25B-717	70p	25C-1677	30p	25C-2611	40p	25D-789	25p
360p	25A-970	70p	25B-718	70p	25C-1677	150p	25C-2631	40p	25D-792	340p
400p	25A-984	15p	25B-738	25p	25C-1669	85p	25C-2634	40p	25D-794	60p
300p	25A-985	65p	25B-744	60p	25C-1670	85p	25C-2660	85p	25D-822	400p
200p	25A-992	30p	25B-755	310p	25C-1675	20p	25C-2668	50p	25D-837	400p
300p	25A-999	20p	25B-757	350p	25C-1677	85p	25C-2668	50p	25D-837	400p
500p	25A-1016	20p	25B-784	25p	25C-1702	20p	25C-2781	50p	25D-838	475p
240p	25A-1016	20p	25B-772	45p	25C-1722	60p	25C-2785	50p	25D-845	250p
180p	25A-1020	30p	25B-792	45p	25C-1756	30p	25C-2791	325p	25D-850	260p
110p	25A-1048	20p	25B-793	35p	25C-1758	30p	25C-2792	275p	25D-859	100p
110p	25A-1062	125p	25B-817	200p	25C-1770	85p	25C-2844	175p	25D-869	320p
230p	25A-1094	180p	25B-826	60p	25C-1815	15p	25C-3078	40p	25D-869	320p
250p	25A-1095	275p	25B-836	60p	25C-1815	15p	25C-3156	325p	25D-870	320p
210p	25A-1108	200p	25B-857	60p	25C-1819	50p	25C-3179	200p	25D-871	320p
230p	25A-1110	200p	25B-861	60p	25C-1845	20p	25C-3182	250p	25D-880	40p
240p	25A-1110	60p	25B-866	85p	25C-1846	45p	25C-3284	175p	25D-882	70p
240p	25A-1110	60p	25B-789	50p	25C-1848	45p	25C-3298	120p	25D-898	250p
240p	25A-1111	40p	25B-790	80p	25C-1875	20p	25C-3298	120p	25D-917	180p
240p	25A-1141	200p	25C-815	15p	25C					

AN3215K	£4.50	AN7172K	£2.95	HA11713	£3.50	LA4178	£2.75	PLL02A	£5.00	STK5325	£6.75	TA7628P	£1.95	BP491	£1.20
AN3312	£2.95	AN7173K	£3.50	HA11714	£3.50	LA4180	£1.95			STK5337	£7.25	TA7640AP	£1.30	BY99	£0.50
AN3320K	£4.95	AN7178	£2.50	HA11715	£3.50	LA4182	£1.95	SAA1124	£2.50	STK5338	£4.50			BY96	£0.20
AN3792	£2.95	BA1420	£1.95	HA11716	£4.75	LA4193	£2.20	SAA5030	£3.50	STK5421	£6.50	TC91066P	£4.95		
AN3821K	£5.95	AN7470	£2.20	HA11717	£4.75	LA4199	£1.75	SAA5042	£3.00	STK5422	£6.50	TA01010A	£1.40	BU208A	£1.30
AN3822K	£6.95	BA1335	£2.50	HA11718	£4.75	LA4201	£1.75			STK5425	£5.30	TA01015	£1.50	BU326A	£1.20
AN5010	£3.95	BA1356	£2.20	HA11724	£8.00	LA4201	£1.60	TA3A01A	£3.95	STK5451	£5.50	TA01170N	£1.50	BU406	£0.95
AN5011	£3.95	BA5102A	£2.50	HA11727	£8.00	LA4260	£2.30	TA4A01A	£4.50	STK5471	£5.50	TA01170S	£1.50	BU407	£0.70
AN5030	£4.50	BA5115	£2.50	HA11736	£6.50	LA4261	£2.30	TA4A11C	£2.75	STK5481	£5.95	TA01170S	£1.50	BU408	£0.95
AN5033	£5.25	BA5124	£2.50	HA11744	£5.95	LA4270	£2.75			STK5482	£5.95	TA01170S	£1.50	BU408	£0.95
AN5071	£1.20	BA5402A	£2.50	HA11745	£5.95	LA4290	£2.50	STK0029	£4.75	STK5740	£4.25	TA011510	£1.95	BU426A	£0.80
AN5135K	£3.95	BA5406	£1.50	HA11745N	£7.50	LA4420	£1.50	STK0039	£4.75	STK5725	£4.25	TA01150S1	£3.95	BU426C	£0.70
AN5150	£3.50	BA5408	£2.20	HAHA11747A	£7.50	LA4422	£1.50	STK0040	£6.25	STK5730	£4.25	TA011515A	£2.50	BU500	£1.00
AN5151N	£6.50	BA6104	£2.20	HA11747AN	£7.50	LA4440	£2.50	STK0049	£6.50	STK6732	£11.75	TA01522	£2.95	BU508A	£1.00
AN5256	£2.20	BA6109	£1.80	HA11749	£4.25	LA4445	£2.20	STK433	£5.25	STK7308	£5.95	TA01770A	£2.95	BU508D	£1.00
AN5265	£1.75	BA6122	£2.20	HA11750	£5.00	LA4446	£2.20	STK435	£5.50	STK7309	£5.95	TA02002	£0.80		
AN5410	£3.95	BA6124	£2.20	HA11751	£5.00	LA4508	£1.80	STK437	£7.50	STK7340	£4.95	TA02003	£1.95	2N3055	£0.50
AN5435	£2.20	BA6208	£1.95	HA12003	£2.20	LA4461	£1.80	STK443	£8.95	STK7404	£6.95	TA02004	£1.95	2N3773	£1.50
AN5436	£2.20	BA6209	£1.95	HA12045	£3.25	LA4465	£2.30	STK457	£7.50	STK8050	£8.95	TA02005	£1.50		
AN5510	£2.75	BA6218	£1.95	HA12016	£3.75	LA4466	£2.30	STK459	£7.50	STK8250	£8.95	TA02006	£1.50	2SA1106	£2.75
AN5512	£2.95	BA6219	£2.20	HA13001	£1.90	LA4500	£2.50	STK463	£6.50	STK8260i	£12.50	TA02020	£1.50	2SA1106	£3.95
AN5515	£2.20	BA6229	£2.20	HA13007	£4.50	LA4505	£2.80	STK465	£9.95			TA02030	£1.50	2SA1164	£1.95
AN5521	£2.20	BA6238A	£1.95	HA13119	£2.50	LA4508	£1.80	STK1050	£7.25			TA02030	£1.50	2SA1186	£2.95
AN5610N	£4.50	BA6239A	£2.20	HA13118	£2.75	LA4510	£1.75	STK1060	£7.95	STR370	£5.20	TA02030	£1.50	2SA1489	£2.95
AN5615	£2.95	BA6302A	£1.80	HA13403V	£5.50	LA4520	£1.50	STK1070i	£9.75	STR371	£5.20	TA02030	£1.50	2SA1516	£2.50
AN5620X	£3.50	BA6304	£1.75			LA4570	£2.75	STK2028	£7.50	STR380	£5.20	TA02633A	£3.50		
AN5622	£3.20	BA6305	£1.95	KA2101	£1.95	LA6358D	£1.20	STK2029	£6.50	STR440	£5.20	TA03300	£5.50	2SB528	£0.60
AN5635N	£3.75	BA6328	£2.20	KA2206	£1.75	LA7031	£2.60	STK2038i	£9.50	STR441	£5.20	TA03301	£5.50	2SB531	£0.60
AN5701	£1.75	BA6411	£2.20	KA2212	£1.20	LA7032	£2.60	STK2048i	£9.50	STR442	£5.20	TA03305	£4.20	2SB581	£1.75
AN5701	£1.75	BA7005	£2.20	KA2261	£1.20	LA7042	£2.60	STK2125	£6.95	STR450	£5.20	TA03310	£5.50	2SB863	£2.95
AN5750	£3.75	BA7023L	£2.50	KA2284	£1.20	LA7520	£3.25	STK2129	£6.95	STR451	£5.20	TA03360	£3.90		
AN5753	£1.95	BA7751AL	£1.95			LA7800	£1.50	STK2139	£8.00	STR453	£5.20	TA03561A	£3.95	2SC1403A	£4.50
AN5900	£2.20	EX8341	£4.50	LA1130	£2.50	LA7801	£1.50	STK2155	£9.50	STR454	£5.20	TA03562A	£4.50	2SC1413A	£2.60
AN6130N	£2.50			LA1135	£2.50	LA7806	£2.50	STK2230	£6.50	STR457	£5.20	TA04500	£3.95	2SC1815	£0.10
AN6136	£1.95			LA1140	£2.20	LA7808	£2.75	STK2240	£6.50	STR1096	£4.95	TA04501	£4.50	2SC1913	£1.20
AN6247	£1.75	HA1196	£1.75	LA1150	£1.75	LA7820	£2.20	STK2250	£6.50	STR2005	£6.20	TA04503	£3.50	2SC1969	£1.75
AN6250	£1.50	HA1197	£1.80	LA1170	£1.75	LA7830	£2.20	STK3041	£6.50	STR2010	£6.20	TA04505	£3.95	2SC2166	£1.00
AN6310	£3.50	HA1199	£1.90	LA1185	£1.60	LA7831	£2.50	STK3042	£6.50	STR2011	£6.20	TA04510	£3.95	2SC2325	£0.40
AN6326N	£5.50	HA1338	£2.95	LA1230	£1.50			STK3044	£5.75	STR2012	£6.20	TA04510	£3.95	2SC2335	£1.20
AN6327	£3.50	HA1339A	£3.50	LA1231N	£2.00	LB1403	£1.50	STK3062	£6.75	STR2013	£6.20	TA04600-2	£2.50	2SC2570	£0.50
AN6328	£3.50	HA1367	£2.50	LA1363	£1.20	LB1405	£1.50	STK3062i	£6.95	STR2014	£6.20	TA04600-20	£2.50	2SC2580	£2.75
AN6330	£2.95	HA1372	£3.50	LA1365	£1.50	LB1416	£1.50	STK3102ii	£6.95	STR2015	£6.20	TA04600-20	£2.50	2SC2580	£2.75
AN6332	£4.75	HA1377	£2.20	LA1385	£1.95	LB1416	£1.50	STK3152ii	£6.95	STR2016	£6.20	TA04750	£4.95	2SC2681	£2.80
AN6340	£3.75	HA1388	£2.95	LA1460	£2.75	LB1640	£2.20	STK4017	£7.50	STR2017	£6.20	UPC575C	£1.00	2SC3153	£3.20
AN6342N	£2.50	HA1392	£2.20	LA2000	£1.75	LB1649	£2.50	STK4025	£6.50	STR2018	£6.20	UPC1025H	£2.30	2SC3281	£2.95
AN6344	£4.75	HA1394	£2.50	LA2100	£2.95	LC1737	£4.50	STK4121ii	£6.95	STR2019	£6.20	UPC1025H	£2.30	2SC3281	£2.95
AN6346N	£3.75	HA1396	£2.50	LA2200	£1.50	LC1763	£3.75	STK4122ii	£6.95	STR2020	£6.20	UPC1191V	£1.20	2SC3409	£2.75
AN6356N	£3.85	HA1397	£2.50	LA2400	£1.50	LC7800	£3.75	STK4131ii	£6.95	STR2021	£6.20	UPC1191V	£1.20	2SC3409	£2.75
AN6357N	£4.50	HA1398	£2.50	LA3101	£1.75	LC7815	£2.95	STK4132ii	£6.95	STR2022	£6.20	UPC1230H	£2.50	2SC3466	£2.95
AN6359N	£5.50	HA1122W	£2.95	LA3160	£0.95	LM1303N	£1.50	STK4141ii	£7.50	STR2023	£6.20	UPC1230H	£2.50	2SC3466	£2.95
AN6360	£2.50	HA11211	£2.30	LA3161	£1.20	LM13914N	£2.75	STK4141iv	£7.50	STR2024	£6.20	UPC1241H	£1.95	2SD358	£0.60
AN6362	£4.50	HA11215A	£2.20	LA3201	£0.95	LM1393N	£1.50	STK4142ii	£7.30	STR2025	£6.20	UPC1263C	£2.30	2SD371	£2.50
AN6371	£3.25	HA11219	£1.75	LA3210	£0.85	LM13944N	£2.75	STK4151ii	£7.50	TA7217AP	£1.80	UPC1277H	£2.50	2SD424	£3.95
AN6387	£1.50	HA11221	£2.20	LA3220	£1.50	LM3915N	£2.75	STK4152ii	£7.85	TA7222AP	£1.80	UPC1287H	£2.50	2SD476	£0.90
AN6562	£1.50	HA11223W	£2.50	LA3300	£1.65	LM3915N	£2.75	STK4161ii	£7.95	TA7229P	£1.80	UPC1288V	£2.75	2SD525	£0.90
AN6610	£1.80	HA11225	£1.95	LA3301	£1.30			STK4162ii	£7.95	TA7230P	£1.80	UPC1318AV	£2.75	2SD600	£1.00
AN6671K	£4.95	HA11226	£4.50	LA3310	£2.75	M5218L	£1.95	STK4171ii	£8.95	TA7232P	£1.80	UPC1335V	£2.75	2SD768	£1.20
AN6676	£5.50	HA11227	£2.20	LA3350	£1.30	M5218P	£0.95	STK4172ii	£8.95	TA7233P	£1.80	UPC1363C	£2.75	2SD811	£2.95
AN6677	£4.95	HA11235	£1.95	LA3361	£1.20	M51102L	£2.95	STK4181ii	£8.95	TA7240AP	£1.80	UPC1364C	£4.20	2SD845	£2.95
AN6678	£1.50	HA11244	£2.95	LA3370	£2.20	M51104L	£3.20	STK4181ii	£8.95	TA7241AP	£1.80	UPC1365C	£2.95	2SD898	£2.95
AN7062	£2.75	HA11251	£2.50	LA3376	£2.20	M51398P	£4.50	STK4192ii	£9.50	TA7243P	£1.80	UPC1373H	£4.20	2SD1207	£0.60
AN7106K	£2.50	HA11401	£2.80	LA3600	£1.50	M51398P	£4.50	STK4332	£4.50	TA7250BP	£1.80	UPC1387C	£1.95	2SD1275	£1.00
AN7143	£2.50	HA11423	£2.20	LA4030	£2.50	M51398P	£4.50	STK4352	£5.90	TA7251BP	£1.80	UPC1391H	£1.50	2SD1276	£1.20
AN7147	£2.50	HA11440	£2.95	LA4031P	£1.95	M51398P	£4.50	STK4793IV	£9.50	TA7270P	£1.80	UPC1403CA	£6.75	2SD1397	£2.00
AN7148	£2.30	HA11580	£3.50	LA4032P	£1.90	M51512L	£1.50	STK4803	£8.50	TA7271P	£1.80	UPC1420CA	£6.20	2SD1398	£1.50
AN7149N	£2.50	HA11701	£3.50	LA4108	£2.20	M51522P	£1.50	STK4833	£9.50	TA7280P	£1.80	UPC15016	£1.60	2SD1411	£1.50
AN7156N	£2.50	HA11703	£4.50	LA4101	£1.00	MS4544L	£1.75	STK4843	£8.95	TA7281P	£1.80	BC517	£0.25	2SD1407	£1.95
AN7161	£3.50	HA11704	£5.20	LA4102	£1.00	MS4544L	£2.75	STK4853	£9.50	TA7299P	£1.80	BC639	£0.22	2SD1426	£2.95
AN7166	£3.70	HA11705	£5.95	LA4110	£1.75	MB3712	£1.50	STK5211	£6.75	TA7317P	£1.80	BC640	£0.22	2SD1427	£3.30
AN7168	£2.75	HA11706	£3.75	LA4145	£1.70	MB3730	£2.20	STK5314	£6.75	TA7807AP	£2.20	B0243C	£0.50	2SD1439	£2.20
AN7169	£2.95	HA11710	£3.75	LA4160	£1.75	MB3731	£2.20	STK5315	£6.75	TA7809P	£2.20	B0244C	£0.50	2SD1453	£1.95
AN7171K	£3.50	HA11711	£6.50	LA4170	£1.75	MB8641	£5.75	STK5324	£5.75	TA7611AP	£2.20	BRF90	£0.70	2SD1453	£1.95

**T. POWELL**  
**16 PADDINGTON GREEN,**  
**LONDON W2 1LG**  
**Tel: 071-723 9246**


# TELEPRICE

LIMITED

In just 4 years, Teleprice has grown to be the largest supplier of ex-rental TVs and videos in the United Kingdom;

and we have built ourselves a reputation for quality and dependability that is second to none.

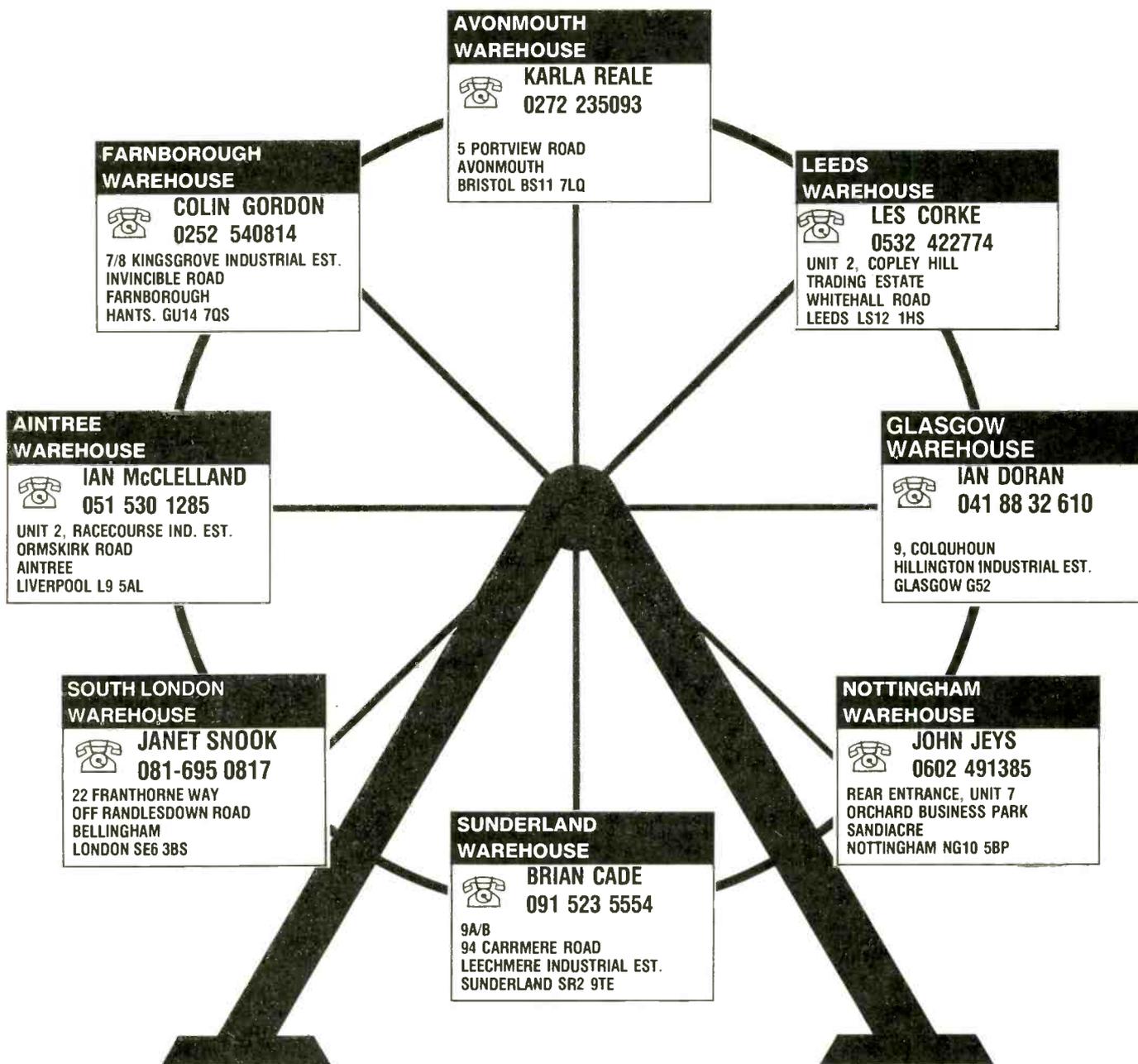Why go round in circles? Come straight to the source!



Whether you're a direct retailer or not, we can probably meet all your supply requirements. From the earliest top loading videos to the very latest Nicam stereo – from 9,000 series to stereo FSTs – working or non working – one single unit or one hundred, our

national network of warehouses and distribution centres provides us with a continuous supply of top quality equipment to help meet all your demands. Phone your local warehouse for this month's special deals.

INTEGRATED CIRCUITS	BA3704 £2.75	L7808 £1.80	LMLM6417 £1.80	MMS458N £2.50	STK435 £8.00	TA7241 £2.50	TD41022P £4.50	TD42593 £1.50	U4108 £1.60	2SC2631 £0.30
BA4210 £2.50	L7812 £1.80	LMT486N 6 PIN £1.80	MMS5108 £2.50	STK4352 £8.00	TA7241AP £2.50	TD41035 £4.50	TD42594 £3.00	U416B £1.60	2SC2632 £0.30	
AN103 £1.60	BA4220 £2.00	L7815 £1.80	MM7317 £3.75	STK437 £10.00	TA7243 £3.30	TD41035T £1.90	TD42600 £6.80	UA767PC £1.20	2SC2655 £0.60	
AN2140 £2.50	BA4236 £2.75	L7818 £1.80	MM74C901 £1.10	STK4392 £7.00	TA7245 £4.50	TD41037 £2.90	TD42611A £1.00	UA7810 £2.00	2SC2958 £2.50	
AN240P £1.90	BA4402 £1.90	L7824 £0.95	M104 £1.00	STK441 £10.50	TA7267P £2.80	TD41044 £2.50	TD42640 £3.50	UA78M15 £2.00	2SC2979 £3.00	
AN253P £1.80	BA4403 £2.75	L7905 £0.80	M29381 £11.00	STK459 £11.00	TA7270P £2.50	TD41044U £1.50	TD42653A £2.75	UA81080DP £2.00	2SC3153 £3.40	
AN3821K £6.75	BA5102 £2.45	L7912 £0.80	M4908B1 £1.10	STK461 £10.50	TA7271P £3.25	TD41057 £2.00	TD42822 £2.00	UPC1185H £2.50	2SC3429 £0.40	
AN3822 £7.50	BA5204 £2.75	L7915 £0.80	M4918B1 £1.50	STK463 £14.50	TA7274 £2.60	TD41082 £3.50	TD43190 £0.95	UPC1225H £2.50	2SC3519 £4.60	
AN5015 £3.30	BA524 £3.00	L7918 £0.80	M50127AP £6.00	STK465 £12.00	TA7280 £3.00	TD41083 £1.70	TD43303 £15.00	UPC1252H £2.75	2SC3678 £1.25	
AN5033 £3.00	BA5202 £2.40	L7924 £0.80	M50431-1015P £2.00	STK5315 £6.50	TA7280P £3.75	TD41151 £1.50	TD43330 £4.50	UPC1230 £3.00	2SC3715 £4.80	
AN5132 £3.95	BA5406 £2.50	LA1180 £2.60	M5045-3012P £2.20	STK5322 £6.50	TA7281P £2.75	TD41170S £2.10	TD43340 £5.00	UPC1238V £3.10	2SC438 £0.20	
AN5965 £1.35	BA6104 £2.50	LA1185 £2.60	M5056-010P £2.70	STK5325 £5.50	TA7291P £2.75	TD41180 £1.80	TD43354 £1.25	UPC1263 £2.20	2SC479 £2.50	
AN5510 £4.50	BA6109 £1.80	LA1201 £0.95	M51014L £1.95	STK5331 £6.00	TA7299P £3.00	TD41180P £3.00	TD43560 £3.00	UPC1378H £2.20	2SD1047 £2.75	
AN5512 £1.95	BA6124 £2.75	LA1235 £2.50	M51164 £1.40	STK5332 £3.50	TA7302 £1.30	TD41180P £3.00	TD43561 £2.50	UPC1381C £3.00	2SD1051 £0.85	
AN5521 £3.50	BA6154 £2.50	LA1260 £1.75	M51356P £3.00	STK5333 £12.00	TA7303 £1.10	TD41190 £1.90	TD43562A £3.00	UPC1382C £4.50	2SD1128 £1.50	
AN5730 £2.50	BA6208 £2.75	LA1403 £3.75	M51381P £1.50	STK5338 £6.00	TA7310 £1.75	TD41270M £1.10	TD43565 £3.00	UPC1363 £1.50	2SD1138 £0.85	
AN5760 £2.00	BA6209 £1.95	LA1482 £2.10	M51383 £1.50	STK5361 £6.25	TA7312 £1.75	TD41365 £4.90	TD43571BQ £3.50	UPC1365 £3.50	2SD1159 £0.75	
AN5900 £1.50	BA6222 £3.10	LA3210 £1.90	M51513 £10.00	STK5421 £5.50	TA7313 £1.90	TD41412 £1.00	TD43580 £3.00	UPC1377C £2.50	2SD1207 £0.75	
AN6326 £4.00	BA6229 £1.85	LA3350 £1.50	M51515L £3.10	STK5422 £5.00	TA7313AP £1.40	TD41470 £5.00	TD43651 £3.00	UPC1379H £2.20	2SD1273 £1.00	
AN6332 £4.40	BA6238A £1.95	LA3361 £1.50	M51516 £4.00	STK5451 £5.00	TA7323 £2.25	TD41501A £3.20	TD43651AQ £6.50	UPC1382 £1.50	2SD1275 £1.30	
AN6341 £2.75	BA6239 £3.75	LA3600 £3.50	M51903L £3.50	STK5451 £5.25	TA7325 £2.50	TD41510 £3.20	TD43652 £1.50	UPC1382 £1.50	2SD1288 £1.70	
AN6344 £4.50	BA6259 £3.00	LA3700 £2.50	M5213L £3.10	STK5471 £5.25	TA7325P £1.50	TD41510A £3.20	TD43653 £2.80	UPC1394 £1.70	2SD1328 £0.85	
AN6346 £4.50	BA6301 £2.00	LA4100 £1.00	M52184 £1.00	STK5476 £6.00	TA7329 £2.00	TD41510A £3.20	TD43654 £2.80	UPC1420A £7.00	2SD1391 £4.20	
AN6346 £4.50	BA6302A £1.80	LA4102 £1.20	M52314 £1.10	STK5481 £5.00	TA7335 £2.00	TD41515A £2.50	TD43655 £3.00	UPC1458 £1.95	2SD1398 £1.75	
AN6359 £3.50	BA6304 £1.70	LA4125 £2.00	M54543 £1.75	STK5482 £5.20	TA7335P £1.50	TD41515A £2.50	TD43656 £3.00	UPC1513HA £2.00	2SD1426 £4.50	
AN6360 £3.75	BA6305 £1.75	LA4140 £0.70	M54543L £1.85	STK5482 £5.20	TA7342 £2.10	TD41670A £2.60	TD4440 £2.00	UPC1539C £3.00	2SD1453 £1.60	
AN6362 £4.25	BA681 £0.90	LA4160 £1.25	M54544L £1.85	STK5482 £5.20	TA7343 £1.75	TD41701 £3.00	TD44422 £3.25	UPD4011 £1.75	2SD1455 2SD130 £1.00	
AN6387 £3.50	BA7001 £1.90	LA4182 £2.10	M54549L £4.50	STK5482 £5.20	TA7350 £2.10	TD41770A £3.00	TD44503 £3.80	UPD4066 £1.95	2SD1496 £4.00	
AN6612 £2.20	BA718 £1.80	LA4183 £2.75	M58478P £4.75	STK5482 £5.20	TA7358 £1.50	TD41905 £1.40	TD44501 £4.80	TRANSISTORS	2SD1497 £2.60	
AN6651 £0.60	BA728 £1.10	LA4192 £2.10	M58655P £5.50	STK5482 £5.20	TA7358 £1.50	TD41905 £1.40	TD44503 £3.80	2SA1065 £5.50	2SD1497-02 £3.95	
AN6671K £3.50	BA7677S £5.00	LA4422 £1.30	M58839 £8.00	STK5482 £5.20	TA7607AP £2.70	TD41908A £1.75	TD44505 £3.95	2SA1092 £5.90	2SD1497-06 £5.95	
AN6677 £5.25	BT76018 £3.50	LA4440 £2.70	M708 £5.50	STK5482 £5.20	TA7609P £2.40	TD41940 £1.80	TD44510 £4.40	2SA1105 £5.50	2SD1497-06 £5.95	
AN6684 £2.75	HA11215A £3.50	LA4445 £2.50	M709 £4.75	STK5482 £5.20	TA7614 £2.50	TD41950 £2.50	TD44600 £2.60	2SA1112 £0.95	2SD1650 £3.50	
AN6912 £2.00	HA11223 £3.75	LA4460 £1.70	MA150E £2.20	STK5482 £5.20	TA7628P £2.40	TD42002 £1.40	TD44600-2 £2.60	2SA1112 £0.95	2SD1877 £2.30	
AN7111 £1.50	HA11225 £2.10	LA4461 £1.80	MB3106 £1.00	STK5482 £5.20	TA7629 £4.00	TD42030 £1.00	TD44601 £2.10	2SA1120 £1.10	2SD639 £0.35	
AN7112 £3.00	HA11226 £3.75	LA4500 £2.70	MB3730 £2.75	STK5482 £5.20	TA7629P £2.75	TD42004 £1.70	TD44610 £4.50	2SA1396 £4.70	2SD667 £1.00	
AN7116 £1.20	HA11235 £3.10	LA4507 £2.70	MB3731 £3.25	STK5482 £5.20	TA7630P £2.75	TD42005 £1.70	TD44610 £4.50	2SA1396 £4.70	2SD725 £3.70	
AN7143 £1.65	HA1124A £1.75	LA4570 £2.20	MC13002P £5.00	STK5482 £5.20	TA7640 £2.00	TD42005S £2.95	TD44610 £4.50	2SA1396 £4.70	2SD787E £0.30	
AN7148 £1.70	HA11414 £2.50	LA5522 £2.20	MC1310 £1.25	STK5482 £5.20	TA7658 £2.00	TD42006V £1.95	TD44720 £5.50	2SA1412 £0.95	2SD811 £2.95	
AN7158 £4.00	HA11701 £3.10	LA5527 £1.95	MC1330P £2.95	STK5482 £5.20	TA7668 £2.00	TD42020 £3.50	TD44720 £5.50	2SA1412 £0.95	2SD836 £1.10	
AN7160 £5.00	HA11713 £3.90	LA4658 £3.80	MC140018CP £1.10	STK5482 £5.20	TA7680 £4.90	TD42030 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD837 £0.80	
AN7169 £3.50	HA11714 £3.50	LA7016 £2.50	MC14093B £1.50	STK5482 £5.20	TA7681AP £5.75	TD42030H £2.50	TD44720 £5.50	2SA1412 £0.95	2SD845 £2.70	
AN7171K £8.00	HA11715 £3.20	LA7096 £4.00	MC14426P £2.20	STK5482 £5.20	TA7687 £2.00	TD42030V £1.75	TD44720 £5.50	2SA1412 £0.95	2SD868 £3.50	
AN7205 £1.95	HA11747A £12.75	LA7210 £3.10	MC14429P £2.20	STK5482 £5.20	TA7688A £6.85	TD42040 £2.00	TD44720 £5.50	2SA1412 £0.95	2SD869 £3.00	
AN7213 £1.10	HA11749 £7.00	LA7305 £6.90	MC14497P £3.50	STK5482 £5.20	TA7698AP £1.50	TD42151 £3.00	TD44720 £5.50	2SA1412 £0.95	2SD870 £3.50	
AN7218 £1.20	HA11750 £5.10	LA7309 £3.75	MC14518CP £2.00	STK5482 £5.20	TA7759 £2.50	TD42161 £1.75	TD44720 £5.50	2SA1412 £0.95	2SD871 £4.50	
AN7220 £1.50	HA12005 £3.80	LA7507 £4.00	MC14518CP £2.00	STK5482 £5.20	TA7759 £2.50	TD42170 £3.00	TD44720 £5.50	2SA1412 £0.95	2SD885 £2.00	
AN7222 £2.10	HA12017 £2.00	LA7520 £3.25	MC1458UPC145 £1.95	STK5482 £5.20	TA7759 £2.50	TD42190 £10.00	TD44720 £5.50	2SA1412 £0.95	2SD888 £2.75	
AN7223 £7.60	HA12026 £2.00	LA7800 £1.50	MC1458UPC145 £1.95	STK5482 £5.20	TA7759 £2.50	TD42270 £2.00	TD44720 £5.50	2SA1412 £0.95	2SD888 £2.75	
AN7224 £1.40	HA2413 £1.20	LA7801 £1.25	MC3359 £1.10	STK5482 £5.20	TA7759 £2.50	TD42320 £0.90	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7225 £1.90	HA13001 £1.80	LA7820 £1.90	MC32632 £1.90	STK5482 £5.20	TA7759 £2.50	TD42510 £4.30	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7273 £2.00	HA13402 £3.20	LA7830 £2.50	MDA2061 £7.00	STK5482 £5.20	TA7759 £2.50	TD42521 £3.75	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7310 £1.10	HA13403 £4.80	LA7913 £3.80	MDA2062 £5.50	STK5482 £5.20	TA7759 £2.50	TD42522 £10.75	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7311 £1.75	HA1350 £9.00	LA7937 £4.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7315 £1.75	HA1368P £2.55	LA8100 £1.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7324 £4.50	HA1374 £5.00	LA8101 £1.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7410 £2.10	HA1377 £2.00	LA8102 £1.25	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7415 £1.40	HA1388 £4.90	LA8103 £3.70	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7420 £3.20	HA1392 £3.00	LA8104 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
AN7818F £1.50	HA1394 £4.00	LA8105 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
B1403 £1.00	HA1397 £5.40	LA8106 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA1320 £1.50	HA1398 £3.50	LA8107 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA1332 £1.00	HA1406 £2.00	LA8108 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA301B £1.50	HA1457 £2.10	LA8109 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA318 £2.50	HA1459 £2.70	LA8110 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA328 £1.10	HD14081 £0.25	LA8111 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA3306 £2.10	HD4539 £2.70	LA8112 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA333 £1.40	KAZ210 £0.30	LA8113 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA3416L £2.75	L7805 £0.80	LA8114 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA3417 £1.20	L7806 £0.80	LA8115 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	
BA3505F £2.75	L7806 £0.80	LA8116 £3.00	ME42050 £4.50	STK5482 £5.20	TA7759 £2.50	TD42530 £1.00	TD44720 £5.50	2SA1412 £0.95	2SD908 £4.00	

# A.Z. ELECTRICS

Stock items despatched by return

Access & Visa Accepted

<b>TDA8180 ORIGINAL</b>		<b>£9.50</b>
TRANSISTORS	BD244 £0.30	BU406 £0.90
BC184 £0.09	BD244C £0.30	BU406D £1.50
BC212 £0.09	BD278A £0.80	BU407 £0.50
BC213 £0.09	BD434 £0.80	BU426A £1.00
BC214A £0.07	BD508 £0.90	BU500 £1.00
BC214B £0.07	BF195 £0.07	BU508A £1.00
BC214L £0.09	BF196 £0.15	BU508AF £1.70
BC237 £0.07	BF197 £0.15	BU508D £1.70
BC238 £0.07	BF198 £0.07	BU806 £0.75
BC307 £0.12	BF199 £0.14	BU807 £0.75
BC308B £0.07	BF244 £0.40	BU111 £0.95
BC327-25 £0.07	BF259 £0.22	BU111AF £1.96
BC328-40 £0.05	BF422 £0.15	BUW64 £1.00
BC337 £0.07	BF458 £0.22	BUX84 £0.60
BC372 £0.95	BF459 £0.22	SD12659 £0.75
BC392 £1.50	BF469/BF471	T9064V £2.28
BC441 £0.25	BF471 £0.25	TP110 £0.45
BC461 £0.25	BF472 £0.25	TP112 £0.45
BC547 £0.07	BF870/BF472	TP29 £0.30
BC549 £0.07	BF870/BF472	TP29 £0.30
BC557 £0.07	BU108 £0.25	TP31 £0.30
BC559B £0.07	BU126 £0.70	TP32 £0.30
BC639 £0.18	BU208 £1.00	TP42C £0.40
BC640 £0.30	BU208A £1.00	TP47 £0.98
BD131 £0.50	BU209 £1.00	TP191A £1.20
BD132 £0.40	BU208T £1.00	ZTR604 £0.55
BD137 £0.35	BU208T	ZTK650 £0.70
BD237 £0.22	(TOSHIBA)	
BD238 £0.22		
BD243B £0.30	BU326A £1.00	
BD243C £0.40		

<b>BELT KITS</b>		VS310/315 320/380/385 £2.40
Belt Kits for most models are stocked. Some examples are:		
<b>AKAI</b>		
VS1,2,5 £1.20		
VS4,6,9,15 £1.10		
Ask for models not listed.		
<b>AMSTRAD</b>		
TVR1,2,3, VCR4600, 4700,5200 £1.90		
Ask for models not listed.		
<b>FERGUSON/JVC</b>		
3V00/3V16/3V22 etc. £1.60		
3V29/3V30 £1.20		
3V35/36/38/39 £1.10		
3V42/43/44/45/48/53/54/55/57 £1.00		
Ask for models not listed.		
Loading belts on certain models also available.		
<b>FISHER</b>		
FVHP520 530 £1.00		
FVHP615 620/622/710/711/715/716/720/721/725/830 £0.65		
840 £1.00		
VHR1100/1300/1500 £1.00		
Ask for models not listed.		
<b>SHARP</b>		
VCF3/V4C02/500/511/581/582/583/584/585 £1.10		
460 £0.65		
VS180/200/220/262 £0.95		
265/267 £2.20		
Ask for models not listed.		

Hitachi VT33 Original £32.00	
Hitachi VT64 Original £19.75	
Hitachi VT8000 series Original £34.50	
Hitachi VT9000 series Original £34.50	
Sharp VC7000 series Original £30.50	
<b>MODE CONTROL MOTORS</b>	
Ferguson 3V42, 43, 44, 45, 48, 49, 52, 53 £6.00	
Ferguson 3V58, 59, 65, FV10, 11, 12, 13, 14, 20, 21, 22, 26 £4.50	
<b>Sharp Reel Motor Pulley only £1.20</b>	
Replacement of plastic pulley on a number of Sharp Reel Motors with the above metal pulley gives better rewind/FF performance.	
<b>IDLER ASSEMBLIES</b>	
<b>FERGUSON</b>	
Take up Clutch (Mechanical models) £5.00	
3V29/30 Take up Idler £2.80	
3V29/30 Take up Clutch £2.85	
3V29/30 Reel Idler £3.00	
3V35 Reel Idler £3.00	
3V35, 36, 38, 39 Take up Clutch £2.85	
3V58, 59, 64, 65, FV10, 11, 12, 13, 14 Idler Arm £1.80	
Clutch Assembly 3V44, 45, 48, 49, 52, 53, 54, 55 £14.00	
Clutch Assembly 3V42, 43 £14.00	
<b>FISHER</b>	
FVHP615, 905, 910, Idler Assembly Original £5.00	
FVHP615 Gear Idler Assembly £4.35	
FVHP905, 910 Gear Idler Assembly £5.00	
FVHP520, 530 Idler £3.00	
FVHP520, 530 Pulley £0.70	

<b>REMOTE CONTROLS</b>	
Ferguson, Grundig, ITT, Philips, Pye, Sony, Hitachi, Matsui, Logik, Panasonic, Saisho, Salora, Samsung, Tashiko, Tatung, Toshiba. Various models TV & Video. From £14.50	
<b>MANY HITACHI TV REMOTE CONTROLS NOW IN STOCK.</b>	
<b>SONY REMOTE CONTROL RUBBER PADS. STATE MODEL FOR PRICE.</b>	
<b>New Additions</b>	
Universal Remote Control £25.00	
Sony type RC670, RM670, RM673 £15.50	
Sony type RC661, RM652, RM654, RM657 £15.50	
RM663, RM664, RM651 £15.50	
Panasonic Models TC2110, 2255, 2655, 2680, TX1752, 2251, 2656, 5500 £14.50	
Panasonic Models TC1632, 1642, 2232, TX2034, 2044, 2200, 2234, 2244, 2636, 3300 £14.50	
<b>TV ON/OFF SWITCHES</b>	
ITT, Philips, Decca, Thorn, Fidelity, Grundig, Sony and Hitachi. State model for price.	
<b>PINCH ROLLERS</b>	
A range of Pinch Rollers is in stock, most of them @ £2.80. Makes include Akai, Amstrad, Ferguson, Fisher, Funai, GEC, Goldstar, Grundig, Hinari, Hitachi, ITT, JVC, Marantz, Mitsubishi, NEC, Nordmende, Orion, Panasonic, Philips, Samsung, Sanyo, Schneider, Sharp, Sony, Tensai, Thomson, Toshiba etc. Please state model and make.	
Philips Pinch Roller for models VR6180, H185, 6285, 6362, 6367, 6467, 6468, 6470, 6561, 6670, 6760, 6761, £6.90	
<b>OTHER SPARES</b>	
Universal Video Copying Kit £4.25	
Universal Copying Kit (Scart) £5.20	
Universal Camcorder Kit £6.90	
Video Cassette Lamps from £0.50	
CRT Anode Caps £0.60	
Video Tape Splicing Kit £2.95	
Hitachi TV Frame Module HM6251 £5.50	
Hitachi TV Frame Module HM6232 £5.50	
Cassette Housing Assembly Ferguson 3V35, 36, 38, 42, 43, 44 £25.25	
Cassette Loading Roller Assembly 3V23, 3V31, 3V32 £3.50	
Philips 1.2V Back up Battery £1.75	
Philips 2.4V Back up Battery £2.80	
5.5V Back up Cap £1.85	
Degaussing Positor Blue £1.55	
Degaussing Positor White £1.30	
Cassette Housing Assembly Hitachi VT11 £19.50	
End Sensor for Hitachi VT63, 64, 65 (Pair) £2.75	
Cassette LED Sensor for Panasonic etc. £1.60	
I.C. Circuit Protectors £0.60	
Clear Service Cassette £5.90	
Push Button Unit Thorn TX90 £12.75	
Matsui/Saisho Limiter Post £1.75	
Cassette Housing Modification Kit for Sharp VCA113HM Series. Includes cassette switch and star sensor PCB. Fault symptom No eject & intermittent load/unload £6.50	
Cassette Housing assemblies for Philips available.	

<b>DIODES AND THYRISTORS</b>	
BA157 £0.07	BY206 (BY96R) £0.20
BR100 £0.20	DT112 £2.20
BR101 £1.40	BY210/800 (BY96) £0.55
BR103 £0.75	RG15K £0.55
BR303 £1.50	BY227 £0.20
BR556 £0.75	BY228 £0.15
BT116 £2.50	BY229 £1.50
BT128P £4.50	BY259 £0.50
BT129P £4.50	BY96D £0.30
BT151 800R £1.75	BY96G £0.55
BY126 £0.20	BYW56 £0.50
BY127 £0.08	BYW96 £0.50
BY133 £0.20	BYX10 £0.50
BY164 £0.90	BYX55 600 £0.55
BY164/SKB2/02 £0.90	FZ506 £1.50
BY179 £1.10	IN4001 £0.06
BY184 £0.65	IN4002 £0.06
BY189 £2.00	IN4003 £0.10
BY223 £2.00	IN4004 £0.10
	IN4005 £0.10
	IN4006 £0.08
	IN4007 £0.08
	IN4148 £0.10
	IN5408 £0.25
	KBL08 £1.95
	SK1102 £1.20
	SK1115 £0.65
	SK1115/02 £0.75
	SK2G2/02 £0.75
	SK2G3/04 £1.30
	SK4F1/04 £0.45
	SK4F1/06 £0.45
	SK5F3/10 £2.20
	SR2M £0.75
	T9053V £1.40
	T9064V £2.28

<b>NEW LINES</b>	
Universal Video Head Puler £16.00	
Video Idler Spring Kit £5.95	
Video Washer and E Clip Kit £5.00	
<b>LINE OUTPUT TRANSFORMERS</b>	
Decca 100 £9.50	
ITT CVC20 £12.50	
ITT CVC25/30/32 £9.50	
ITT Compact 80 Series 110 £16.75	
ITT Compact 80 Series 90 £19.75	
ITT CVC45 £18.00	
ITT I109F £14.00	
ITT CVC1204 £11.50	
ITT CVC800/1/3 £21.50	
ITT CVC1100 £16.50	
ITT CVC1150/1175 £20.00	
ITT 6325 £18.50	
ITT 3546 £18.50	
ITT 1200-1 £20.00	
<b>Other ITT transformers available</b>	
Fidelity all models up to 20" ZX3000 £10.50	
Fidelity Panel for ZX2000 £1.00	
Fidelity 22" ZX3000 £24.50	
Hinari CT4/5 & TVA1 £14.75	
Philips KT3 £12.95	
Rank Bush T20A £11.50	
Thorn TX100 Green Spot 110 £16.75	
Thorn TX90 Mains Trans £18.85	
Ferguson TX90 LOPT £17.75	
Ferguson 3V35/36 Mains Transformer £23.00	
Ferguson 3V44/44/45 Mains Transformer £18.85	
Sony - Please state model for price	
Universal Tripler £4.75	
Universal Tripler with focus unit £9.50	
Decca 120/130 series tripler £8.50	
Thorn TX10 Focus Unit Kit £9.00	

<b>ASK FOR SEMICONDUCTORS NOT LISTED</b>	
<b>VIDEO HEADS</b>	
<b>AMSTRAD</b>	
3HSSR-VCR7000 (Saisho/Orion) £18.00	
PSF1-VCR4500, 5200, 9000 £15.00	
PSF2-VCR4600, 4700 £15.00	
PSF3-VCR6000 £21.50	
<b>FERGUSON</b>	
3HSSV-2 Head universal £7.50	
3HSSVA-3V42, 44, 45, 46 etc £20.00	
3HSS4VB-3V32/HR7655 £25.00	
3HSS4VC-3V48/HRD565 £26.00	
3V48, 58, 59, 65, FV10, 11, 12, 13, 14, 20, 21, 26	
And most other Fergusons	POA
<b>HITACHI</b>	
3HSSHA-VT8000, 9000 series £17.00	
3HSSHB-VT11, 33 etc £17.00	
10082-VT120, 220 £29.00	
10081-VT130, 135 £30.50	
<b>PANASONIC</b>	
3HSSN-2 Head universal £7.50	
3HSSU1N-NV100, 370, 380/Philips VR6460 £11.00	
3HSSU2N-NV230, 470, 480, G9, 10, 11, 15PX £21.00	
3HSSU3N-NV430, 460 £16.00	
3HSS3N-NV77, 330 £18.50	
3HSS4NB-NV730 £26.00	
3HSS4NA-NV366 £24.00	
NVG30, 33, 40, 45, 46, 130, & most other Panasonics	POA
<b>SANYO</b>	
3HSSSY-VHR1100, 1110, 1300 £20.00	
3HSS3SY-VHR1500 £34.00	
<b>SHARP</b>	
3HSSSP-VC9300, 9500, 9700, 381, 481, 482, 483, 486 etc £17.00	
3HSSSPB-VC581, 583, 651, 670 etc £17.00	
VC7000, 8000 series (Brass) £42.00	
<b>OTHER MAKES</b>	
Alba 4000, Goldstar 8000, Sentra 8000, 1000 Solavox £22.50	
Fisher FVHP510, 520, 530, 615, 710 etc £18.00	
Fisher VBS7000, 9000 etc £25.00	
Hinari VXL2, 4, 3, 20, 25 £18.00	
Hinari VXL5, 6, 20H £15.00	
Mitsubishi HS306, 710 £38.00	
Orion VC150, 180, VHI, 2, 3 etc £18.00	
Saisho VR100, 605, 705, 805, 905 £18.00	
Samsung Universal 2 Head £24.25	
T o s h i b a	
V71, 73, 74, 75, 81, 82, 83, 84, 85, 87 £20.00	
Toshiba V93 £21.00	

<b>ASK FOR VIDEO HEADS NOT LISTED</b>	
The above heads are new and replacements.	
<b>VIDEO MOTORS</b>	
<b>REEL MOTORS</b>	
Ferguson 3V29/30 £20.00	
Ferguson 3V58, 59, 65, FV10, 11, 12, 13, 14, 20, 21, 22 £17.25	
Ferguson FV260 £14.50	
Hitachi 8000, 8300, 8500 £8.50	
Sanyo VTC5000, 5150, 5400, 5300, 6500 £7.50	
Sharp VC9300, 9500 etc, Original £15.00	
Panasonic NV333, 366 Original £13.20	
All other Panasonics	POA
<b>DRUM MOTORS</b>	
Ferguson/JVC (Mechanical models) £23.00	
Sharp 7000 series Original £24.63	
All Panasonic Original	POA
<b>CAPSTAN MOTORS</b>	
Ferguson 3V35, 36 Original £22.50	
Ferguson/JVC (Mechanical models) £20.00	
Hitachi VT11 Original £30.00	

<b>ASK FOR SEMICONDUCTORS NOT LISTED</b>	
<b>VIDEO HEADS</b>	
<b>AMSTRAD</b>	
3HSSR-VCR7000 (Saisho/Orion) £18.00	
PSF1-VCR4500, 5200, 9000 £15.00	
PSF2-VCR4600, 4700 £15.00	
PSF3-VCR6000 £21.50	
<b>FERGUSON</b>	
3HSSV-2 Head universal £7.50	
3HSSVA-3V42, 44, 45, 46 etc £20.00	
3HSS4VB-3V32/HR7655 £25.00	
3HSS4VC-3V48/HRD565 £26.00	
3V48, 58, 59, 65, FV10, 11, 12, 13, 14, 20, 21, 26	
And most other Fergusons	POA
<b>HITACHI</b>	
3HSSHA-VT8000, 9000 series £17.00	
3HSSHB-VT11, 33 etc £17.00	
10082-VT120, 220 £29.00	
10081-VT130, 135 £30.50	
<b>PANASONIC</b>	
3HSSN-2 Head universal £7.50	
3HSSU1N-NV100, 370, 380/Philips VR6460 £11.00	
3HSSU2N-NV230, 470, 480, G9, 10, 11, 15PX £21.00	
3HSSU3N-NV430, 460 £16.00	
3HSS3N-NV77, 330 £18.50	
3HSS4NB-NV730 £26.00	
3HSS4NA-NV366 £24.00	
NVG30, 33, 40, 45, 46, 130, & most other Panasonics	POA
<b>SANYO</b>	
3HSSSY-VHR1100, 1110, 1300 £20.00	
3HSS3SY-VHR1500 £34.00	
<b>SHARP</b>	
3HSSSP-VC9300, 9500, 9700, 381, 481, 482, 483, 486 etc £17.00	
3HSSSPB-VC581, 583, 651, 670 etc £17.00	
VC7000, 8000 series (Brass) £42.00	
<b>OTHER MAKES</b>	
Alba 4000, Goldstar 8000, Sentra 8000, 1000 Solavox £22.50	
Fisher FVHP510, 520, 530, 615, 710 etc £18.00	
Fisher VBS7000, 9000 etc £25.00	
Hinari VXL2, 4, 3, 20, 25 £18.00	
Hinari VXL5, 6, 20H £15.00	
Mitsubishi HS306, 710 £38.00	
Orion VC150, 180, VHI, 2, 3 etc £18.00	



## PHONE TODAY

**RENTAL FINANCE**  
TVs, VCRs, Satellite

**0903  
821020**

**STOCKING FINANCE**  
TVs, VCRs, Satellite

**0903  
821020**

**BLOCK DISCOUNTING**  
Rental & HP Agreements

**0903  
820968**

*Written Quotations Available  
On Request*



**Broughfame Limited**  
Colonnade House  
High Street  
WORTHING  
West Sussex BN11 1NZ

User Friendly

## SOFTWARE

FOR IBM COMPATIBLE PC'S RUNNING ON MSDOS  
A FAMILY OF PROGRAMS FOR TV/VCR BUSINESSES

1. Receipt/Repair/Invoice
2. Rental
3. Service/Maintenance Contract and Sales

*Phone or write for details:*

**TBR Software**  
369 Chepstow Road  
Newport, Gwent. NP9 8HJ  
Tel. 0633 282556

TRADE ONLY

## MICROWAVE OVEN PARTS

MAGNETRONS · DIODES · TRANSFORMERS  
LAMPS · FUSES · MICROSWITCHES

PHONE NOW FOR PRICE LIST

**A.W.I. MICROWAVE OVEN COMPONENTS**

Samuel Whites Estate, Medina Road,  
Cowes, Isle of Wight PO31 7LP  
Telephone: 0983 296121  
Fax: 0983 296122

# TUBES

- ★ 14" and 16" portable tubes ..... from £39
- ★ 20" TX9 51-580 ..... £44
- ★ 20" KT3 51-570 ..... £49
- ★ 20" 51-590 ..... £39
- ★ 22" 30AX 56-540 ..... £49
- ★ Various FST tubes ..... from £60

Comprehensive range of new  
and rebuilt tubes always  
available.

## RING FOR QUOTE

We pay cash or give credit for  
certain types of 45AX and FST  
old glass.

## GOLDEN OLDIES

- ★ 20" Thorn 9K 51-161 ..... £19
- ★ 20" G11 51-500 ..... £19
- ★ 22" G11 56-500 ..... £29
- ★ 22" Thorn 9.6K 56-610 ..... £19



Add carriage and  
VAT to all prices



## EXPRESS TV

The Mill, Mill Lane,  
RUGELEY, Staffs WS15 2JW

**Tel: 0889-577600**  
**Fax: 0889-575600**

BRISTOL (AGENT) 0545-316285	SOUTH-WEST A.J.C. 0395-266210	LONDON (ANSWERPHONE) 081-863 9371
-----------------------------------	-------------------------------------	---

# The Black Book is back . . .

How and why scrambling systems are hacked.  
How are Smartcards hacked? How secure is VideoCrypt?  
What is the future for hackers?

## . . . with the answers!

The original **European Scrambling Systems** quickly became the industry handbook on the black arts of signal security. Now in **European Scrambling Systems 2**, John McCormac analyses all aspects of scrambling systems from the very basic facilities to the crypto-systems.

Considered by many to be one of the leading European authorities on scrambling and piracy, John McCormac reveals the secrets of hacking supposedly 'secure' systems, again written with his characteristic cynical and humorous slant.

### **Inside European Scrambling Systems 2:**

- **Introduction to Scrambling**  
covering the basics of scrambling systems
- **Principles of Security**  
including a database of most European scrambling systems in use
- **Descrambler Building Blocks**  
with hacker decoder circuits for various systems, including Filmnet, RTL 4V and SAVE
- **Analogue & Digital Audio Scrambling**  
covering FM'd, spectrum inversion, NICAM, Delta, and duobinary encoding
- **Dirty Tricks**  
used in piracy, counter-piracy and reverse-engineering
- **Basic Cryptology**  
covering the DES and RSA systems
- **Video Manipulative Systems**  
including VideoCrypt, MAC and EuroCypher
- **Cable and Microwave Distribution**
- **Descrambler Hookups**  
for common systems

**European Scrambling Systems 2** is available now from Swift Television Publications for only £29 (P&P FREE in UK). Complete the order form below or telephone us today and find out just how quick our service is.

### **Swift Television Publications**

17 Pittsfield, Cricklade, Swindon SN6 6AN Tel or Fax 0793 750620



**WARNING**  
The information contained in this book is for educational use only. Swift Television Publications, the publishers and the author do not assume any liability for the use or misuse of the information provided. In some countries, the unauthorised use of certain circuits and techniques may be prohibited by law.

Please send me \_\_\_\_\_ copies of **European Scrambling Systems 2** at £29 each.  
Post and packing is **FREE** (within UK). Europe add £4.  
I enclose cheque/PO for £\_\_\_\_\_ made payable to Swift Television Publications or please debit my Access/Visa card:

Number: \_\_\_\_\_ Exp: \_\_\_\_\_  
Name: \_\_\_\_\_ Signature: \_\_\_\_\_  
Address: \_\_\_\_\_  
Postcode: \_\_\_\_\_

# ELECTRONICS WORLD

+ WIRELESS WORLD

SIX PAGES  
OF ELECTRONIC  
CIRCUIT DESIGN  
EVERY MONTH

Subscribe today and save £10

Simply phone our credit card  
hotline on 0789 200 255 for a  
special subscription price of £20  
for 12 issues\*.

\*Normal price £30/12 Issues

TELEPHONE  
(0742)  
739622

# IRWIN ELECTRONICS

TRADE COUNTER OPEN 10AM-1PM, 2PM-6PM  
ORDERING: ORDERS ARE ACCEPTED FROM TRADE SERVICE ONLY  
FOR ORDERS UNDER £15.00 PLEASE ADD £0.60 POST & PACKING. ALL ORDERS ADD V.A.T.  
PAYMENT — CHEQUE, C.W.O. OR  

UNIT 200  
ALBYN COMPLEX  
BURTON ROAD  
SHEFFIELD S3 8BX

## Why Compromise??

WHEN YOU CAN BUY ORIGINAL MANUFACTURERS COMPONENTS AT THESE PRICES!!

IDLERS			IDLERS			VIDEO HEADS		
<b>JVC</b> HR7200			<b>SHARP</b> VC473 to VC581			<b>JVC</b> HR7650		
<b>FERGUSON</b> 3V2930			Part No. Function Each			<b>FERGUSON</b> 3V29 to 3V39		
Part No. Function Each			NIDL0006GEZZ Rewind 2.75			Part No. 12.95 Each		
PU51402 Take up 1.15			Manufacturer...SHARP			PU31332L 12.95 Each		
PU53462 Take up Clutch 2.10			N.B. 0005 and 0006 Idlers may also be used in many Matsui and Saisho videos.			Manufacturer...JVC		
PU48967B Reel 1.95								
Manufacturer...JVC			MOTORS			<b>PANASONIC</b> NV300NV333 NV2000NV7000		
<b>GEC</b> V4004 to V4100			Part No. Function Each			Part No. 8.95 Each		
<b>HITACHI</b> VT11 to VT64			<b>GEC</b> V4100			VEH0103 8.95 Each		
Part No. Function Each			<b>HITACHI</b> VT64			NV366		
6886971 FF Rewind 1.85			Part No. Function Each			Part No. 19.95 Each		
Manufacturer...HITACHI			5577355 Capstan 15.95			VEH0174 19.95 Each		
<b>SHARP</b> VC381 to 386 VC9300 to 9700			These also are a suitable replacement for VT11 and VT33, but not for Hi-Fi or Extended Play versions, e.g. VT14 and VT17.			Manufacturer...PANASONIC		
Part No. Function Each			Manufacturer...HITACHI					
NIDL005GEZZ Rewind 2.75								
Manufacturer...SHARP								
						<b>LIMITED OFFER WHILE STOCKS LAST</b>		

Service

Maintenance

Warranty

## Control Yourself!

### MACHINE TRACK the Program to Efficiency

Machine Track is a remarkable new aide to the service and maintenance sector. This simple program, enhanced by powerful graphic displays, allows total control of your workflow in the most effective way possible. One days training will make you an expert.

From the tracing of individual units by serial number tracking that guarantees accuracy, through to daily scheduling, production of reminder slips, final accounting and invoicing, Machine Track is a complete tool that every Service Manager needs.

Whether your business is computers, televisions, videos, washing machines or other appliances, Machine Track is the most cost effective and comprehensive package on the market.



If quality service is your business - Machine Track is your route to profit!

Field and In-house service  
Maintenance Contracts  
Warranties  
Preventative Maintenance  
Scheduling  
Repair and Error reports

Warranty, M/C and service sales  
Item Tracking  
Reminder Slips  
Vehicle routing and Scheduling  
Invoicing

Pennine Software can introduce you to the benefits of Machine Track at the level you require, whether you're buying computers for the first time or updating with the best program available. We are also an authorised IBM dealer who provide a full range of hardware and software packages, full training and superb back up at really competitive prices.

Get in touch now for an informal chat, a brochure or demo disk.

**IBM**

AUTHORISED  
DEALER

**pennine**

SOFTWARE PUBLISHING

Bywell Home Farm, Bywell, Stocksfield, NE43 7AQ. Tel: 0661 842 784



**UNIDEN SATELLITE RECEIVER** Brand new units (model 8008) £60.00 ref 60P4R (no remote controls)

**SPECTRUM +2 COMPUTER** Built in data recorder, 128K, psu and manuals £59.00 ref 59P4R

**SPECTRUM +3 COMPUTER** Built in disc drive, 128K, psu and manuals £79.00 ref 79P4R

**AMSTRAD CPC464 COMPUTER** No manuals but only £79.00 ref 79P5R (including monitor)

**AMSTRAD CPC6128 COMPUTER** Again no manuals but only £149.00 ref 149P4R

**AMSTRAD GT65** Green screen monitor £49.00 ref 49P4R

**HIGH POWER CAR SPEAKERS.** Stereo pair output 100w each. 40m impedance and consisting of 6 1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7R

**2KV 500 WATT TRANSFORMERS** Suitable for high voltage experiments or as a spare for a microwave oven etc. 250v AC input. £10.00 ref 10P93R

**MICROWAVE CONTROL PANEL.** Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. £6.00 ref 6P18R

**FIBRE OPTIC CABLE.** Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R

**12V SOLAR CELL.** 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42R

**PASSIVE INFRA-RED MOTION SENSOR.** Complete with daylight sensor, adjustable lights on timer (8 secs - 15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. £25.00 ref 25P24R

Pack of two PAR38 bulbs for above unit £12.00 ref 12P42R

**VIDEO SENDER UNIT** Transmit both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range (tune TV to a spare channel). 12V DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P191R

**FM TRANSMITTER** housed in a standard working 13A adaptor (bug is mains driven). £26.00 ref 26P2R

**MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases. £30.00 ref 30P12R

**FM CORDLESS MICROPHONE.** Small hand held unit with a 500' range! 2 transmit power levels req PP3 battery. Tunable to any FM receiver. Our price £15 ref 15P42AR

**CAR STEREO AND FM RADIO.** Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db, wow and flutter less than 35%. Neg earth. £25.00 ref 25P21R

**LOW COST WALKIE TALKIES.** Pair of battery operated units with a range of about 150'. Our price £8.00 a pair ref 8P50R


**7 CHANNEL GRAPHIC EQUALIZER** plus a 60 watt power amp! 20-21KHZ 4-8R 12-14v DC negative earth. Cased. £25 ref 25P14R

**NICAD BATTERIES.** Brand new top quality. 4 x AA's £4.00 ref 4P44R. 2 x C's £4.00 ref 4P73R. 4 x D's £9.00 ref 9P12R. 1 x PP3 £6.00 ref 6P35R

**TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE.** The ultimate equivalents book. Latest edition £20.00 ref 20P32R

**CABLE TIES.** 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104R. Bumper pack of 1,000 ties £14.00R

## VIDEO AND AUDIO MONITORING SYSTEM

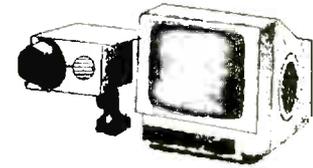

**£99.00**

Brand new units consisting of a camera, 14cm monitor, 70 metres of cable, AC adapter, mounting bracket and owners manual. 240v AC or 12V DC operation complete with built in 2 way intercom. £99.00 ref 99P2R

**1991 CATALOGUE AVAILABLE NOW IF YOU DO NOT HAVE A COPY PLEASE REQUEST ONE WHEN ORDERING OR SEND US A 6"X9" SAE FOR A FREE COPY.**

**GEIGER COUNTER KIT.** Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R

**FM BUG KIT.** New design with PCB embedded coil. Transmits to any FM radio. 9v battery req. £5.00 ref 5P156R

**FM BUG** Built and tested superior 9v operation £14.00 ref 14P3R

**COMPOSITE VIDEO KITS.** These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R

**SINCLAIR C5 MOTORS** 12v 29A (full load) 3300 rpm 6"x4" 1/4" O/P shaft. New. £20.00 ref 20P22R

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P8R

**SINCLAIR C5 WHEELS** 13" or 16" dia including treaded tyre and inner tube. Wheels are black, spoked one piece poly carbonate 13" wheel £6.00 ref 6P20R. 16" wheel £6.00 ref 6P21R

**ELECTRONIC SPEED CONTROLLER** Kit for c5 motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3R

**SOLAR POWERED NICAD CHARGER.** Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3R

**MOSFETS FOR POWER AMPLIFIERS ETC.** 100 watt mosfet pair 2S799 and 2SK343 £4.00 a pair with pin out info ref 4P51R. Also available is a 2SK413 and a 2S7118 at £4.00 ref 4P42R

**12 VOLT BRUSHLESS FAN.** 1/2" square brand new ideal for

boat, car, caravan etc. £5.00 ref 5P206R

**ACORN DATA RECORDER ALF503** Made for BBC computer but suitable for others. Includes mains adapter, leads and book. £15.00 ref 15P43R

**VIDEO TAPES.** Three hour superior quality tapes made under licence from the famous JVC company. Pack of 10 tapes £20.00 ref 20P20R

**PHILIPS LASER. 2MW HELIUM NEON LASER TUBE.** BRAND NEW FULL SPEC £40.00 REF 40P10R. MAINS POWER SUPPLY KIT £20.00 REF 20P33R READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R. SOLDER 22SWG resin cored solder on a 1/2kg reel. Top quality. £4.00 a reel ref 4P70R

**600 WATT HEATERS** ideal for air or liquid, will not corrode, lasts for years. coil type construction 3"x2" mounted on a 4" dia metal plate for easy fixing. £3.00 ea ref 3P78R or 4 for £10.00 ref 10P76R

**TIME AND TEMPERATURE MODULE** A clock, digital thermometer (Celsius and Fahrenheit (0-160 deg F) programmable too hot and too cold alarms. Runs for at least a year on one AA battery. £9.00 ref 9P5R

Remote temperature probe for above unit £3.00 ref 3P60R

**GEARBOX KITS** Ideal for models etc. Contains 18 gears (2 of each size) 4x50mm axles and a powerful 9-12v motor. All the gears etc are push fit. £3.00 for complete kit ref 3P93R

**ELECTRONIC TICKET MACHINES** These units contain a magnetic card reader, two matrix printers, motors, sensors and loads of electronic components etc. (12"x12"x7") Good value at £12.00 ref 12P28R

**JOYSTICKS** Brand new with 2 fire buttons and suction feet these units can be modified for most computers by changing the connector etc. Price is 2 for £5.00 ref 5P174R

**GAS POWERED SOLDERING IRON AND BLOW TORCH** Top quality tool with interchangeable heads and metal body. Fully adjustable, runs on lighter gas. £10.00 ref 10P130R

**CAR IONIZER KIT** Improve the air in your car! clears smoke and helps to reduce fatigue. Case required. £12.00 ref 12P28R

**6V 10AH LEAD ACID** battery by yuasha eq equipment but in excellent condition now only 2 for £10.00 ref 10P95R

**12 TO 220V INVERTER KITS** As supplied it will handle up to about 15 wat 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R

**VERO EASI WIRE PROTOTYPING SYSTEM** ideal for designing projects on etc. Complete with tools, wire and reusable board. Our price £6.00 ref 6P33R

**MICROWAVE TURNTABLE MOTORS.** Ideal for window displays etc. £5.00 ref 5P165R

**STC SWITCHED MODE POWER SUPPLY** 220v or 110v input giving 5v at 2A, +24v at 0.3A, +12v at 0.15A and +90v at 0.4A £6.00 ref 6P59R

**HIGH RESOLUTION 12" AMBER MONITOR.** 2v 1.5A Hercules compatible (TTL input) new and cased £22.00 ref 22P2R

**VGA PAPER WHITE MONO** monitors new and cased 240v AC. £59.00 ref 59P4R

**25 WATT STEREO AMPLIFIER** c. STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P69R (Circuit dia included)

**MAINS FANS.** Small type construction, Approx 4"x5" mounted on a metal plate for easy fixing. New £5.00 5P166R

**POWERFUL IONIZER KIT.** Generates 10 times more ions than commercial units! Complete kit including case £18.00 ref 18P2R

**MINI RADIO MODULE** Only 2" square with ferrite aerial and tuner. Superhet. Req's PP3 battery. £1.00 ref BD716R

**HIGH RESOLUTION MONITOR.** 9" black and white Philips tube in chassis made for OPD computer but may be suitable for others. £20.00 ref 20P26R

**BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10** £4.00 REF 4P92R, PACK OF 100 £30.00 REF 30P16R

**CB CONVERTORS.** Converts a car radio into an AM CB receiver. Cased with circuit diagram. £4.00 ref 4P48R

**FLOPPY DISCS.** Pack of 15 3 1/2" DSDD £10.00 ref 10P88. Pack of 10 5 1/4" DSDD £5.00 ref 5P168R

**SONIC CONTROLLED MOTOR** One click to start, two click to reverse direction, 3 click to stop! £3.00 each ref 3P137R

**FRESNEL MAGNIFYING LENS** 83 x 52mm £1.00 ref BD827R

**LCD DISPLAY.** 4 1/2 digits supplied with connection data £3.00 ref 3P77R or 5 for £10.00 ref 10P78R

**ALARM TRANSMITTERS.** No data available but nicely made complex transmitters 9v operation. £4.00 each ref 4P81

**TRANSMITTER RECEIVER SYSTEM** Originally made for nurse call systems they consist of a pendant style transmitter and a receiver with telescopic aerial 12v. 80 different channels. £12.00 ref 12P26R

**CLAP LIGHT.** This device turns on a lamp at a finger 'snap' etc. nicely cased with built in battery operated light. Ideal bedside light etc. £4.00 each ref 4P82R

**ELECTRONIC DIPSTICK KIT.** Contains all you need to build an electronic device to give a 10 level liquid indicator. £5.00 (ex case) ref 5P194R

**UNIVERSAL BATTERY CHARGER.** Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R

**ONE THOUSAND CABLE TIES** 175mm x 2.4mm white nylon cables only £5.00 ref 5P181R

**PC MODEMS** 1200/75 baud modems designed to plug into a PC complete with manual but no software £18.00 ref 18P12R

**ASTEC SWITCHED MODE POWER SUPPLY** 80mm x 165mm (PCB size) gives +5 at 3.75A, +12 at 1.5A, -12 at 0.4A. Brand new £12.00 ref 12P39R

**BULL ELECTRICAL**  
 250 PORTLAND ROAD HOVE SUSSEX  
 BN3 5QT TELEPHONE 0273 203500  
**MAIL ORDER TERMS: CASH OR CHEQUE WITH ORDER PLUS £2.50 POST PLUS VAT.**  
 PLEASE ALLOW 10-14 DAYS FOR DELIVERY  
 NEXT DAY DELIVERY £8.00  
 FAX 0273 23077

**VENTILATED CASE FOR ABOVE PSU** with IEC filtered socket and power switch. £5.00 ref 5P190R

**IN CAR POWER SUPPLY.** Plugs into cigar socket and gives 3.4, 5.6, 7.5, 9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R

**CUSTOMER RETURNED** switched mode power supplies. Mixed type, good for spares or repair. £2.00 each ref 2P292R

**DRILL OPERATED PUMP.** Fits any drill and is self priming. £3.00 ref 3P140R.

**PERSONAL ATTACK ALARM.** Complete with built in torch and vanity mirror. Pocket sized, req's 3 AA batteries. £3.00 ref 3P135R

**POWERFUL SOLAR CELL 1AMP .45 VOLT** only £5.00 ref 5P192R (other sizes available in catalogue)

**SOLAR PROJECT KIT.** Consists of a solar cell, special DC motor, plastic fan and turntables etc plus a 20 page book on solar energy! Price is £8.00 ref 8P51R

**RESISTOR PACK.** 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R

**CAPACITOR PACK 1.** 1100 assorted non electrolytic capacitors £2.00 ref 2P286R

**CAPACITOR PACK 2.** 40 assorted electrolytic capacitors £2.00 ref 2P287R

**QUICK CUPPA?** 12v immersion heater with lead and cigar lighter plug £3.00 ref 3P292V

**LED PACK.** 50 red leds, 50 green leds and 50 yellow leds all 5mm £8.00 ref 8P52R

**WASHING MACHINE PUMP.** Mains operated new pump. Not self priming. £5.00 ref 5P18R

**IBM PRINTER LEAD.** (D25 to centronics plug) 2 metre parallel. £5.00 ref 5P186R

**COPPER CLAD STRIP BOARD** 17" x 4" of 1" pitch 'vero' board £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R

**STRIP BOARD CUTTING TOOL** £2.00 ref 2P352R

**TV LOUDSPEAKERS.** 5 watt magnetically screened 4 ohm 55 x 125mm. £3.00 a pair ref 3P109R

**SPEAKER GRILLS** set of 3 matching grills of different diameters. 2 packs for £2.00 (6 grills) ref 2P364R

**50 METRES OF MAINS CABLE** £3.00. 2 core black precut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91R

**4 CORE SCREENED AUDIO CABLE 24 METRES** £2.00. Precut into convenient 1.2 m lengths. Ref 2P365R

**TWEETERS 2 1/4" DIA** 8 ohm mounted on a smart metal plate for easy fixing £2.00 ref 2P366R

**COMPUTER MICE** Originally made for Future PC's but can be adapted for other machines. Swiss made £8.00 ref 8P57R. Atari ST conversion kit £2.00 ref 2P362R

**6 1/2" 20 WATT SPEAKER** Built in tweeter 4 ohm £5.00 ref 5P205R

**5" X 3 1/2" 16 OHM SPEAKER** 3 for £1.00! ref CD213R

**ADJUSTABLE SPEAKER BRACKETS** Ideal for mounting speakers on internal or external corners, uneven surfaces etc. 2 for £5.00 ref 5P207R

**PIR LIGHT SWITCH** Replaces a standard light switch in seconds light operates when anybody comes within detection range (4m) and stays on for an adjustable time (15 secs to 15 mins). Complete with daylight sensor. Unit also functions as a dimmer switch! 200 watt max. Not suitable for fluorescents. £14.00 ref 14P10R

**WINDUP SOLAR POWERED RADIO!** FM/AM radio takes NICAD batteries complete with hand charger and solar panel 14P200R

**240 WATT RMS AMP KIT** Stereo 30-0-30 psu required £40.00 ref 40P200R

**300 WATT RMS MONO AMP KIT** £55.00 Psu required ref 55P200R

**ALARM PIR SENSORS** Standard 12v alarm type sensor will interface to most alarm panels. £16.00 ref 16P200R

**ALARM PANELS** 2 zone cased keypad entry, entry exit time delay etc. £18.00 ref 18P200R

**35MM CAMERAS** Customer returned units with built in flash and 28mm lens. 2 for £9.00 ref 8P200R

**STEAM ENGINE** Standard Mamod 1332 engine complete with boiler piston etc £30 ref 30P200R

**TALKING ALARM CLOCK** What more can we say?? £14.00 ref 14P200R

**12V & 6V 2A CASED BENCH SUPPLY** Also includes a lead acid charger pcb plus space inside for a 6v 10AH battery. £7.00 ref 7P31R

**IEC MAINS CABLE WITH 13A PLUG** Standard 2 metre lead 2 for £3.00 ref 3P141R

**OZONE FRIENDLY LATEX** Ideal for holding wires PCB's etc in place easy to peel off when set. 250ML tube. £2.00 ref 2P370R

**TELEPHONE HANDSETS** Brand new units with subminiature 'bug' style microphone. 2 sets for £3.00 ref 3P142R

**SOUND OPERATED LIGHTS** Ideal for beside the phone at night etc battery operated and cased. Inbuilt time delay. £3.00 ref 3P143R

**AC STEPDOWN CONVERTER** 240v ac to 110v ac 1000 watts, cased. Suitable for resistive loads only! £2.00 ref 2P371

**CURLY CABLE** 6 core extends from 8" to 6 feet. Fitted with 9 way D type at one end. £3.00 for 4 ref 3P144R

**PROJECT BOX** Black plastic 5 1/2" x 3 1/2" x 1" screw on lid. 2 for £2.00 ref 2P372R

**HEX KEYBOARD** Same size as above box 2 for £2.00 ref 2P373R

**CHOC BLOCK PACK** 100 2way connectors ideal for spares box £2.00 ref 2P374R

**SHAVERS SOCKETS** Unswelled pirs but only £2 for 10! ref 2P375R

**MINI MONO AMP** 3 watt 12 volt dc amplifier built on a 2"x3" PCB £1.00 ref BD495R

**TELEPHONE EXTENSION LEAD** 5 metres long with new style plug one end socket the other. White £2.00 ref 2P375R

**PLUG IN POWER SUPPLY** Designed to plug into shaver socket, cased complete with lead and 3 5mm plug. Our price is 6 for £2.00 ref 2P376R

**3 WAY 13A MAINS ADAPTER** Standard domestic units with unswelled pins 4 for £2.00 ref 2P377R (ideal for workshop etc)

**SOLAR CELL** Amorphous silicon 100mm x 60mm 1.87v 153mA £4.00 ref 4P93R

**SOLAR CELL** 3 feet by 1 foot! 12v Amorphous silicon £40 callers only please!

**35MM CAMERAS** Customer returns so may need slight attention. Built in flash and motor drive £6.00 each ref 6P60R

**CAMERA FLASH UNITS** Ideal for multi flash photography etc 3 units for £10.00 ref 10P101R

**DISC DRIVES** 5 1/4" 720K Mitsubishi £35.00 ref 35P6R

**WE ARE ALWAYS LOOKING FOR NEW ITEMS TO SELL SO PLEASE FAX ANY DETAILS ON SUITABLE ITEMS. MINIMUM QUANTITY 50- ANY ONE ITEM.**

# HOCKLEY DISCOUNT TELEVISIONS

(WEST MIDLANDS)  
140 HOCKLEY HILL, HOCKLEY  
BIRMINGHAM B18 5AN

TEL: 021-515 2003

FAX: 021-515 2004


★ ★ **HDT NEWS** ★ ★ **STOP PRESS** ★ ★

**AMAZING OPENING OFFERS**

## LOOK



REMOTE CONTROLS  
From £4.95

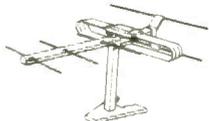

SET TOP AERIALS  
From £1.25

3 HR. VHS  
VIDEO  
TAPES  
Only 90p



FLY LEADS (MALE TO FEMALE)  
Only 28p



AM/FM CLOCK  
RADIO ALARM  
£5.99



VIDEO HEADS  
From £4.99



PERSONAL STEREO'S  
AM/FM RADIO CASSETTE  
PLAYER £5.95

CAR PARKING ON SITE  
FOR FRIENDLY SERVICE - TRY US - YOU'LL LIKE US  
**FOR MORE OFFERS RING 021-515 2003**

(OFFERS APPLY WHILE STOCKS LAST - ALL PRICES SUBJECT TO VAT)

If you're  
looking for . . .

# EX-RENTAL TV'S OR EX-RENTAL VCR'S

Stock currently includes THORN TX Basic, TX Text, stereo Text  
and numerous NON THORN including PHILIPS, GRUNDIG,  
and TOSHIBA, THORN VCR's 3V29/30/31/32, 3V35/6,  
3V43/4/5 plus SHARP, AKAI, SAMSUNG,  
TOSHIBA and SANYO.

PORTABLE CTV AVAILABLE  
. . . you should call  
us NOW.

## West Midlands T.V. & Video Wholesale

2 mins from Junction 9 - M6. Warehouse in Passage off,  
Little London, Caldmore, Walsall. Tel: 0922-724542/722208.  
Open: Mon.-Fri. 9am-6pm. Sat. 9am-2pm.





Sonic House  
Abberley Street Smethwick  
Birmingham B66  
Tel: 021-565 1727  
Fax: 021-555 5367



**Sonic TV Distributors Ltd**

Preston Branch:  
34 Roman Way, Longridge Road  
Ribbleson, Preston PR2 5BB, Lancashire  
Tel: 0772 655011

**NEW STOCK ARRIVING EVERY DAY  
AND  
THE PRICE IS RIGHT**

**Mk IV TEXT**  
**£45** **BARGAIN PRICE**

**SIMPLY PHONE US**

**BIRMINGHAM**  
**021-565 1727**  
**ASK FOR INDY**

**PRESTON**  
**0772-655011**  
**ASK FOR PAUL**

**EXPORT ENQUIRIES WELCOME** ALL PRICES ARE SUBJECT TO 17½% VAT

**W. TREE ★ TRADE ★ WAREHOUSE**

**GREAT REDUCTIONS**

**REGUNNED TUBES**  
WITH 2 YEAR WARRANTY  
INDIVIDUALLY PROCESSED  
Now Only £47

**END OF SEASON SALE REDUCED BY 17½%**  
**SAMSUNG B GRADE**

**AMSTRAD SATELLITE SYSTEMS**  
UNTESTED  
**Now £75**  
Saving 17½% TESTED £10 EXTRA

Standard Play £139  
Twin Speed £155  
20" RC 30 Channel TV  
Digital Tuning £155

Ex-Hotel 54cm FST  
Remote Control Colour TVs  
REDUCED NOW

**ALL TESTED & WORKING**

**£139**  
**TX9 PORTABLES**  
Mint Tubes  
Now **£59**

**MICROWAVE OVENS**  
**Tested & Working from £65**  
**B GRADE**

**Daisy Wheel Printers**  
(serial interface)  
**£24**

Also many business computers and monitors available.

**MANY MODELS AVAILABLE**

**UNIT ONE, SUNSHINE MILLS,  
WORTLEY ROAD, LEEDS 12.**  
Telephone: 0532 638804  
Fax: 0532 310275

**ALL PRICES ARE INCLUSIVE OF VALUE ADDED TAX**

**NEW STOCK ALWAYS ARRIVING — TELEPHONE FOR DETAILS**

**CAMCORDERS & SATELLITE SYSTEMS NOW IN STOCK  
ALSO BRAND NEW BOXED TV/VIDEO STANDS FROM £3**

<b>COLOUR PORTABLES</b> FROM £35.00	<b>FRONT LOAD</b> VHS VIDEOS FROM £60.00	<b>F.S.T. REMOTE</b> TEXT TV's FROM £50.00	<b>RADIO CASSETTE</b> RECORDERS FROM £15.00
<b>MIDI HI-FI's</b> FROM £20.00	<b>C.D. MIDI's</b> FROM £50.00	<b>C.D. PLAYERS</b> FROM £33.00	<b>L.P. VHS £125 + VAT</b> WITH L.C.D. £135 + VAT
<b>FERGUSON</b> 21" FASTEXT BOXED WITH STAND £200.00 + VAT	<b>FERGUSON 21"</b> NICAM F/TEXT BOXED WITH STAND £230 + VAT	<b>PLEASE NOTE</b>	<b>THIS STOCK IS ALL B-GRADE</b> RETURNS OR NEW, NOT EX- RENTAL. ALL PRICES INCLUDE VAT UNLESS STATED.
<b>AMSTRAD 464</b> (HOME COMPUTER) WITH MONITOR £50.00	<b>AMSTRAD 6128</b> (HOME COMPUTER) WITH COLOUR MONITOR £80		

**NOW IN STOCK** 14" REMOTE PORTABLES £100 INC VAT (BOXED)  
10" MAINS/BATT PORTABLES £100 + VAT (BOXED)

**GOGGLEBOX**  
DISCOUNT ELECTRICAL WAREHOUSE

**TEL: LEEDS**  
**0532-310359**  
ASK FOR ROBERT



T V Video Audio Satellite

Unit 17, Leeway Court, Leeway Industrial Estate, Newport, Gwent  
Tel 0633 271772

**NEW WHOLESALERS OPEN NOW IN SOUTH WALES**

**SUPERB RANGE OF TV'S & VCR'S AUDIO & SATELLITE  
DIRECT LOADS AVAILABLE**

**STOCK ARRIVING DAILY FROM SOURCE  
EXPORT ENQUIRIES WELCOME**

**WHY TRAVEL THE COUNTRY FOR STOCK! WHEN WE HAVE  
THE BEST DEALS FOR ALL YOU LOCAL DEALERS**

**OPEN 6 DAYS A WEEK - SO FOR THE BEST IN NEW AND EX-  
RENTAL PRODUCTS CONTACT DRAGON VISION ON**

**0633 - 271772**

ALL PRICES ARE SUBJECT TO V.A.T.



**CENTRAL TV**

**EX-RENTAL**

- SUPERB RANGE OF TV'S & VCR'S
- THORN & GRANADA
- DIRECT LOADS AVAILABLE FROM SOURCE
- EXPORT ENQUIRIES WELCOME

**B' GRADE**

TV'S • VIDEOS • AUDIO  
 MICROWAVES • HIFI  
 PORTABLES • FSTS • NICAM • FASTEXT  
 ☆ ☆ ☆ **STOP PRESS** ☆ ☆ ☆ **STOP PRESS** ☆ ☆ ☆ **STOP PRESS** ☆ ☆ ☆  
 NOW IN STOCK QUANTITY OF BRANDED  
 TWIN SPEED VHS VIDEO'S

**SATELLITE**

**AMSTRAD & TRISTAR**  
 FULL SYSTEMS AVAILABLE PLUS ALL USUAL ACCESSORIES

**CENTRAL TV WHOLESALE  
 DISTRIBUTION LTD**  
 369 Stratford Road, Sparkhill  
 Birmingham B11  
 TEL 021-772 1591  
 FAX 021-766 6383  
**CTV LONDON**  
 Eley Estate, Nobel Road  
 Edmonton N18  
 TEL 081-807 4090  
 FAX 081-884 1314

**REBUILT  
 COLOUR TUBES**

*First Independent Rebuilder with B.S.I. Certification*  
**PIL - In Line - FST**  
**N.G.T. ELECTRONICS LTD.**  
 120, Selhurst Road, London SE25 6LL  
**PHONE: 081-771 3535**  
*Britain's Oldest Established TV Tube Rebuilder*

**RELAY**

OMAGH LTD COMPUTER SOFTWARE

**DO YOU RENT TELEVISIONS?  
 DO YOU STILL USE A CARD SYSTEM?  
 DO YOU FIND IT DIFFICULT TO KNOW YOUR ARREARS TOTAL AT ANY GIVEN TIME?**  
 If you do then we recommend our computer TV and Video Rental package. This package includes  
 ★ automatic updating of each customer's record  
 ★ alphabetical print-out of each customer's arrears and payments missed  
 ★ total arrears immediately available  
 ★ easy to use and operate.

**NEW HIRE PURCHASE PROGRAMME NOW AVAILABLE AS WELL.**  
 These programmes operate on all IBM compatibles running under MS-DOS. Free demonstration discs available.

**CONTACT** **WILLIAM J THOMPSON**  
 Donaghianie Post Office  
 Beragh Co. Tyrone  
 Telephone Beragh 58214 (0662 7)

**SEMPLER SERVICE**  
 THE ONLY APPROVED THORN TELEPRICE DISTRIBUTOR FOR E. ENGLAND

**SIMPLY  
 THE BEST**

BEST PRICES BEST QUALITY

**IN EX-RENTAL TV & VIDEO EQUIPMENT**

**RING LUKE ON**  
**Tel: 0945 476319**  
 FOR YOUR BEST DEAL YET!

**SEMPLER SERVICE**  
 15 REGAL ROAD  
 WEASENHAM LANE  
 WISBECH  
 PE30 2RQ





**THE BOSS HAS  
GONE MAD  
AGAIN**

**PRICES SLASHED**

**AMSTRAD SATELLITE SYSTEMS**

*(The Best Seller in the U.K.)*

**SRD400 RECEIVER (with built-in Videocrypt Decoder)**

**60cm BLACK MESH DISH with LNB**

**80cm BLACK MESH DISH with LNB**

(in lots of 12 +)

6-11

3-5

1-2

**£132.66**

**£136.06**

**£141.16**

**£144.57**

**£151.81**

**£155.72**

**£161.57**

**£165.50**

ONLY LIMITED STOCKS AVAILABLE. BUY **NOW** AT THESE FANTASTIC **LOW PRICES**

**SUPERVISION**

*Group*

LTD.



LEEDS

**0532**

**444195**

LEICESTER

**0533**

**626468**

NOW OPEN

WARRINGTON

**0925**

**445588**

SCOTLAND

**041**

**445 6606**

**THE BOSS HAS  
GONE MAD  
AGAIN**

**DALBANI (UK) LTD.**

**JAPANESE COMPONENTS SPECIALISTS  
ELECTRONIC COMP. DISTRIBUTORS (Imp. Exp.)  
EX-STOCK DELIVERY 6,000 DIFFERENT PARTS**

1991  
CATALOGUE  
NOW  
AVAILABLE  
£2.00 CHEQUE  
OR P.O.

TRANSISTORS			INTEGRATED CIRCUITS			
2SA	BD	BUY	AN	LM	SAB	TC
2SB	BDW	DTA	BA	M	SI	TCA
2SC	BDX	DTC	CX	MB	SLA	TD
2SD	BF	MJ	HA	MC	STA	TDA
2SJ	BT	MJE	KA	MDA	STK	TEA
2SK	BU	1N	KIA	MEA	STR	TTL
3SK	BUT	2N	LA	MN	STRD	UPC
AD	BUW	1S	LB	NE	TA	UPD
BC	BUX	TIP	LC	SAA	TBA	CMOS

STOCKISTS OF IC's & TRANSISTORS, AUDIO AND VIDEO HEADS, MOTORS, IDLERS, PULLEYS, ROLLERS, BELTS AND TYRES FOR RADIO CASSETTE, VIDEO AND TV'S. (ORIGINAL AND COPY REPLACEMENT PARTS AVAILABLE)

**DALBANI (UK) LTD**

**587A KINGSTON ROAD, RAYNES PARK, LONDON SW20 8SA, ENGLAND**

**Tel: 081-543 1971 • Fax: 081 542 2082 • TIX 914040**

# VISIONS • LONDON

Suppliers of **THORN** ex-rental TVs and Videos  
Working or Off-the-pile

Unit 4, Rainstar Ind. Estate,  
Eley Estate, Nobel Rd,  
Edmonton N18 0AA  
(just off the A406)

**OPEN**  
9 - 5.30 MON to FRI  
9 - 1 SATURDAY



ELECTRONICS



Main Distributor in London

**APPROVED**  
**THORN TELEPRICE**  
**DISTRIBUTOR**


**Phone now!! 081-807 7476/7579**

**EXPORT ENQUIRIES: Fax 081-345 6597**

OPEN SUNDAYS BY  
APPOINTMENT ONLY
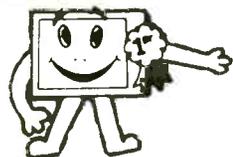
## UNBEATABLE PRICE OFFERS ON VIDEO & TV SPARES

REMOTE CONTROLS • TRANSFORMERS • VIDEO HEADS  
SERVICE KITS • SERVICE AIDS • REFURB MATERIALS



# CentreVision


Suppliers of Surplus TVs to the Trade  
CENTREVISION HOUSE • SLOPER ROAD • LECKWITH • CARDIFF • CF1 8AB  
Telephone 0222 344754

## SUMMER BARGAINS

FST SETS IN STOCK FROM £60.00 VIDEO LESS THAN 3 YEARS OLD FROM £85.00

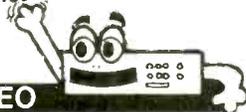**PHONE 0222 344754**

ALL THE BEST TVs AND VIDEOS ARE GOING THERE — WHY DON'T YOU?




### WORKING TELEVISION

TX9-10 Basic	£27.00
TX9-10 R/C	£30.00
TX10 Text	£48.00
KT3/30 Text	£45.00
Philips G11 Text	£35.00
Philips G11 Basic	£18.00
GEC Starline	£25.00
Hitachi Text	£57.00
Doric MK4 Text	£49.00
Doric MK4 Basic	£30.00
Doric MK3 22"	£17.00
ITT Text	£48.00
ITT Basic	£26.00
ITT R/C	£33.00

### WORKING VIDEO

Hitachi 9000	£48.00
Hitachi 8000	£48.00
Panasonic NV333	£48.00
Panasonic NV7200	£48.00
Panasonic NV2000	£45.00
Thorn 3V29	£50.00
Thorn 3V30	£56.00
Thorn 3V31	£65.00
Thorn 3V32 LP/SP	£65.00
Thorn 3V35	£75.00
Thorn 3V40	£56.00
Rediffusion 9300	£60.00
Sharp 8300	£45.00
Sharp 9300	£65.00

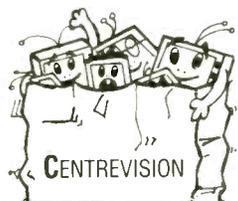10% OFF 10 TV's  
15% OFF 50 TV's OR MORE  
ON SELECTED LINES



EXPORT ENQUIRIES WELCOME — ALL PRICES + VAT

GEC  
STARLINE  
**£18**

K30  
TEXT  
**£45**

TX  
TEXT  
**£55**

MK III  
**£15**

PANASONIC  
TEXT  
**£40**

**TEL: 021-505 2619**

# NATIONAL TV DISTRIBUTORS

10 Minutes from  
M5 – Junction 1

**19 LOWER HIGH STREET,  
WEDNESBURY, WEST MIDLANDS**

HITACHI  
T/LOADER  
**£45**

SHARP  
F/LOADERS  
**£65**

3V29  
**£45**

3V35  
**£75**

SLIMLINE  
**£85**

**ALL PRICES ARE SUBJECT TO 17½% VAT**

**NEW 'B' GRADE STOCK NOW AVAILABLE**

**HUGE SAVINGS ON  
LEADING BRANDS**

**NATIONWIDE  
DELIVERY 24hrs**

**COMPLETE, TESTED, BOXED**  
COLOUR TV'S: FST, F/TEXT, NICAM,  
14", 17", 21", 25", 28"

VIDEOS: LCD, EX-PLAY, T/TEXT, NICAM STEREO  
AUDIOS: MIDI CD, SEPARATES, PORTABLE CD, RAD/CASS,  
MICROWAVES: Manual, Digital, 650-700W, COMBIOVENS



KEVIN GARDNER  
1043 Leeds Road  
Bradford BD3 7DB  
Tel: (0274) 665670/660196  
Fax: (0274) 665246

FRED BEAN  
Unit 7, Lloyds Court,  
Manor Royal, Crawley  
Tel: (0293) 615363  
Fax: (0293) 615359

**CAMPION  
WHOLESALE LTD.**

**QUALITY USED T.V.  
& VIDEO**

**COMPLETE RANGE OF  
T.V's AND VIDEOS  
MOST MAKES AND  
MODELS AVAILABLE**

**STOCK ARRIVING DAILY  
T.V's from £3.00  
Videos from £30.00  
Prices Ex-VAT**

**Free Delivery Service  
to most areas of the U.K.**

**UNIT 80, BARRACKS ROAD,  
SANDY LANE INDUSTRIAL ESTATE,  
STOURPORT-ON-SEVERN,  
WORCESTERSHIRE DY13 9QB**

Just 10 Mins from  
M5 Junct. 6 Worc's North

**02993-79642 or 79643  
FAX: 0299 827984**

## CREWE WHOLESALE TV LTD.

**OFFER OF TWO OPTIONS**

### OPTION 1

A GOOD RANGE OF MIXED TV'S AND VIDEOS  
UNTESTED BY OURSELVES  
TELEPHONE FOR DELIVERY DAYS  
AND BUY STRAIGHT OFF THE WAGON

**TEL: 0254 64489**

**SCHOOL LANE GUIDE, LANCS**

### OPTION 2

A GOOD RANGE OF GENUINE MIXED WORKING  
TV'S AND VIDEOS AT COMPETATIVE PRICES  
ALSO A RANGE OF TESTED NON WORKING  
TV'S AND VIDEOS

PLUS A GOOD SELECTION OF  
UNTESTED TV'S & VIDEOS  
RING FOR CURRENT STOCK & PRICES

**TEL: 0270 582924**

**WILLIAM STREET CREWE,  
CHESHIRE**

**FAX: 0274  
722229**

**BESCO LTD  
EX-RENTAL TV's  
& VIDEOS**

Huge selections. Complete range.  
All makes and models available.

★ New Stocks Every Day ★

VHS Video from £30

Television from £3

Washers, Fridges, Vax, Microwaves  
Now Available

Working Ex-Equipment Panels

IF	Converger	Decoder	Line Scan	Power	Frame
T20/22X	5	14	18	17	14
T26 X	5	16	20	17	X
Philips G11 14.505		12	20	20	11.50

All prices include Postage & Packing. But + VAT

★ IF THE PANEL YOU REQUIRE IS NOT LISTED PLEASE ASK ★

**BRADFORD**

Springmill St  
Manchester Rd, BD5 7RL  
Ring Tony (0274) 308186

**MANCHESTER**

Unit 3, Mersey Rd.  
North Ind Est., Failsworth  
Ring David (061) 683 4612

Visa/Access welcome  
Prices are Plus VAT & Based on Quantity  
OPEN 6 DAYS 9-5

**NEW (B) GRADED FERGUSON STOCK**

i.e. 51/59cm FAST TEXT

**£260.00** inc. VAT

i.e. or 51cm FAST TEXT WITH NICAM

**£311.00** inc. VAT

**BRAND NEW NIKKAI STOCK**

IN STOCK NOW - MULTISYSTEM TVs

i.e. 20", 21, 28/10" COLOUR PORTABLES AC/DC +  
NIKKAI LP VIDEOS FROM £169.00 BOXED

**CROWN 14" PORTABLES**

BRAND NEW

- Full remote control ● Digital Display on Screen ● UHF/VHF Tuner
- 32 Function Remote ●

**only £115.00**

**SAMSUNG 14" PORTABLES**

Full remote control ● Digital Display on Screen ●  
from £130

**EX-RENTAL TVs**

9.0	£12
9.6	£16
TX26" Full Remote	£35
TX9 Text 20"	£50
TX10 Text 22"	£55
TX10 Text 26"	£50

**WORKING STOCK**

Brand New Handsets for  
TVs & Videos  
from only £7.50

NON-THORN TVs (OFF PILE) FROM  
**£3.00**

3V29, 3V30...£55      QUANTITY...£50  
8941 Remote...£75      8942 Remote L.P....£85

NON-THORN VCRs FROM £35.00

FRESH STOCK ARRIVING DAILY - RING FOR UPDATE ON STOCK

★ SPECIAL OFFER ★  
STEREO TEXT...£55.00

TX9/TX10 BASICS...From £25.00

**NEW  
PHILEX UNIVERSAL  
REMOTE CONTROL**  
In quantities of 10 £19.95

Now you can use just  
ONE remote for all your  
Infra-Red Equipment.

★ ALL PRICES ARE SUBJECT TO VAT ★ (OFFERS APPLY WHILE STOCKS LAST) ★  
OPEN MON.-FRI. 9 a.m. - 5.30 p.m. SAT. 9 a.m. - 1.00 p.m.

WHY TRAVEL THE WHOLE COUNTRY?

RING SID NOW ON DIRECT LINE TO TV WAREHOUSE

LEEDS (0532) 444200 FAX: (0532) 425777

EXPORT ENQUIRIES WELCOME

**SUPERVISION**

UNIT 16, TOWER WORKS, 2 GLOBE ROAD, LEEDS LS11 5QG  
OFF WATER LANE, NEAR HILTON HOTEL. EASY ACCESS FROM M1 & M62 (2 Mins)

**COLOUR TRADE**

ESTABLISHED 1973 - WHOLESALE ONLY

**NEW 'B'  
GRADE**

**ONLY**

LATEST  
NICAM  
FASTEXT  
F.S.T.

MAJOR BRANDS  
TV - VIDEO - HIFI  
SATELLITE

COMPLETE BOXED - WITH STAND  
- HANDSET - BOOK - ETC - MINT

Phone 021-359 7020/021-359 5970

FAX 021-359 6344

221-222 BRIDGE ST WEST, HOCKLEY,  
BIRMINGHAM B19 2HU

# VISION LAND

TV & VIDEOS  
WHOLESALE'S

— NEW WAREHOUSE OPEN NOW —  
**THE WORKING SET  
WHOLESALE YOU CAN  
RELY ON**


We specialize in supplying trade customers with top quality working ex-rental TVs & videos.  
We offer good products, friendly service & keen prices.

<b>TVs</b>	Thorn 9000/9200/9600/ 9800/9900 from .....	£15
	Thorn TX9/10 Basic .....	£30
	Thorn TX9/10 Remote .....	£40
	Thorn TX9/10 Text .....	£55
	Thorn TX100 Text .....	£65
	Thorn Stereo Text .....	£65
	FST's from .....	£85
	Philips KT3/30 .....	£25
	Philips KT3/30 Text .....	£50
	Philips KT35/40 Text .....	£55
	Bush T20/22/26 .....	£15
	Portable TV from .....	£50
	Portable Text from .....	£70

<b>VIDEOS</b>	Thorn 3V23 .....	£60
	Thorn 3V29/30 .....	£55
	Thorn 3V31/35 .....	£80
	Thorn 3V32 Long Play .....	£90
	Thorn 3V43/44/48/55/59 from .....	£110
	Hitachi 8500/9300 .....	£55
	Hitachi VT11 .....	£60
	Hitachi VT33 .....	£70
	Sharp 9300/381 .....	£60
	Amstrad 7000 .....	£50
	Pan NV333/7200 .....	£55
	Pan NV777 .....	£70

**BRAND NEW HANDSETS  
TV STANDS, TV/VCR STANDS  
and Video Heads for sale**

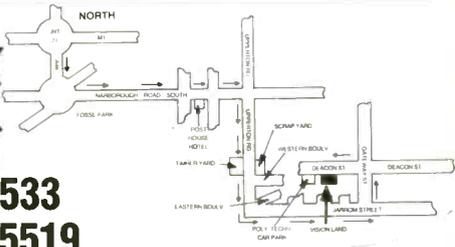**USED SPARES  
VARIOUS ITEMS  
TELEPHONE  
FOR LATEST  
STOCK DETAILS**



**0533  
555519**

**Open Mon-Sat 9 - 5**  
Numerous other manufacturers names stocked:  
Sony, Sanyo, Toshiba, Hitachi and Panasonic

**NEW STOCK ARRIVING EVERY WEEK. SPECIAL  
DISCOUNTS & DELIVERY ON LARGE QUANTITIES**

Prices: All prices subject to VAT  
but include handsets (where appropriate).

**SANDWICHES AND COFFEE FOR  
ALL OUR LONG-DISTANCE CUSTOMERS**

**VISION LAND** 34 Deacon Street,  
Leicester LE2 7EF

Approx. 5 mins from Jnct 21 M1. Opposite Polytechnic car park.

**TEST  
FACILITIES  
AVAILABLE**

# Chromavision

TVs, VCR WHOLESALE

**ONE AND ONLY THORN APPROVED  
WHOLESALE IN MANCHESTER &  
BOLTON FOR THE NORTH WEST**

1,000s of VCRs WORKING and UNTESTED      1,000s of TVs WORKING and UNTESTED

## THORN & GRANADA STOCK AVAILABLE

- ★ TOP LOADERS ..... From £45
- ★ FRONT LOADERS ..... From £60
- ★ NEW VIDEOS IN STOCK P.O.A.
- ★ BASIC TVs ..... From £10
- ★ TELETEXT TVs ..... From £45
- ★ STEREO TEXT ..... From £60

ALL PRICES SUBJECT TO VAT AND QUANTITY


**TRAILER LOADS ARRIVING  
EVERY WEEK DIRECT FROM SOURCE**  
★ GRADED STOCK NOW IN !!! ★  
VIDEOS, PORTABLES, AUDIO - FASTEXT - NICAM ETC.

**EXPORT ORDERS - WELCOME!!**

## NOW OPEN in BOLTON

DUNCAN STREET, BOLTON BL1 2SF

Tel: 0204 363728  
0860 732580

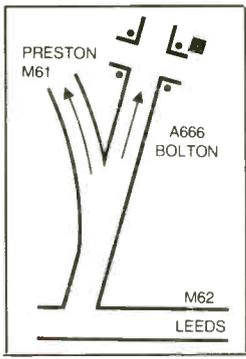

**SPECIAL OPENING OFFERS**  
**TELETEXT PORTABLE**  
BLACK MONITOR STYLE - B GRADE - BOXED -  
WORKING WITH REMOTE - ONLY

**£105** IN QUANTITY

WORKING B GRADED VCR TWIN  
SPEED - BOXED - with REMOTE  
ONLY £130

— PARTS SECTION OPEN —  
Video Heads, Carriages, Range of Handsets, Idlers,  
Belts, Transformers, etc etc.

# MANCHESTER

95 LANGWORTHY ROAD, SALFORD M6 5PH

FAX/TEL: 061 736 6333

MOBILE: 0860 732 580

**FRIENDLY SERVICE - GUARANTEED  
DELIVERY SERVICE AVAILABLE**



# C.T.V.

UNIT 5, THE PHOENIX BUILDING, RUSHOCK TRADING ESTATE,  
DROITWICH ROAD, NEAR KIDDERMINSTER

TELEPHONE: 0299-251522 0836-585829/0860-809673 (24 HR)

**SUPPLIERS OF HIGH QUALITY EX-RENTAL  
TELEVISIONS AND VIDEOS**

**LARGE STOCKS ALWAYS AVAILABLE**

**ALL AT COMPETITIVE PRICES**

**Also available: 'B' Grade Products Ferguson 15" Remote, 21" Remote, 25" Remote. All FST Fاستext**

**OPEN: MON-FRI - 9.30-5.30**

**TEL: 0299-251522**  
**0836-585829/0860-809673 (24 HR)**

**Fax: 0299-251543**

**EXPORT ENQUIRIES WELCOME**

## INDEX TO ADVERTISERS

A-Z Electronics	902, 903
Aerial Techniques	893
A.M. Components	904
ASJ	919
Audio Electronics	902
AWI Ltd	905
B.K. Electronics	856
Beechwood Electronics	905
Besco	917
Broughfame Ltd	905
Bull Electrical	908
Campton Wholesale Ltd	916
Central TV Wholesale	912
Centrevision	915
Chromavac Ltd	904
Chromavision	918
Colour Trade	917
CPC	—
C.T.V.	919
Crewe Wholesale TV	916
Dragon Vision Audio	911
East Cornwall Components	860
East London Components	899
Economic Devices	889-889
Electro Smart	916
Euras International	857
Express TV Supplies	905
GGL Components	858
Gogglebox	911
Grandata Ltd	850-854
Helmrose Electronics	893
Hockley Discount TV	909
HRS Electronics PLC	863
Hussain Central TV	913
ICS Intertex Group	902
Inwin Electronics	907
JJ Components	891
KSA Wholesale Components	900
LRC (Spares)	859
Manor Supplies	867
NGT Electronics	912
Nikko Electronics	914
Oxford Applied Techno	873
Pennine Group	907
Philips T&M	Cover II
PV Tubes	859
Relay Omagh Ltd	912
Simple Service	912
Senz Components	928, Covers III, IV
Sonic TV Distributors	910, 916
Stewart of Reading	899
Supervision Group	914, 917
Swiftpark Components	899
Swift T.V.	906
T Powell	900
Teleprice Ltd	901
Tridman Mail Order Ltd	899
Tree, W. Trade TV	910
Visionland	918
Visions (GB) Ltd	915
Vista Electronics	900
Willow Vale Electronics	855
W. Midlands TV & Video	909

## ALBA BUSH

### HINARI

**SALVAGED SPARE PARTS  
AND PCBs FOR:**

**HINARI CT18/TVA1**

**BUSH 2020/2020T/2114/2114T/2321/2321T**

**ALBA SAT 200/300**

**MARCONI BLUE CAP LNB ONLY**


**PLUS TV/VIDEO MIDI STANDS, HEADPHONES,  
MICROPHONES, STYLII, CARTRIDGES,  
VARIOUS SIZE GLASS DOOR  
AND PERSPEX DOORS AND LIDS**

**roadstar SENTRA**  
**EXCLUSIVE SERVICE & SPARES**

**asj Electrotechnik**

**Mandale Mill, Beacon Road, Wibsey,  
Bradford, West Yorkshire BD6 3DQ**  
Telephone: 0274 690241  
Fax: 0274 602701
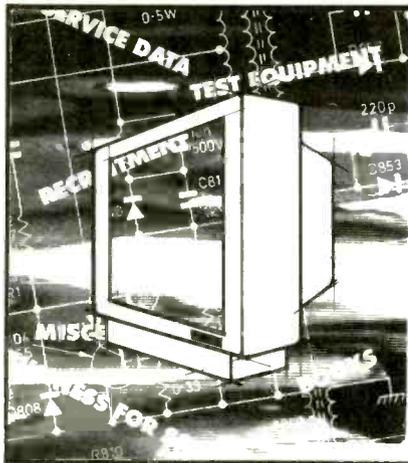
# CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED



## TELEVISION CLASSIFIED

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting is £10.35 per single column centimetre (minimum 3 cm). Classified advertisements 70p per word (minimum £12), box number £4.00 extra. All prices plus 17½% VAT. All cheques, postal orders etc., to be made payable to Reed Business Publishing Group. Advertisements, together with remittance, should be sent to the Television Classified Room L327, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.



**PHONE 081-661 8339 FAX 081-661 8931**



### LINEAGE

**FOR SALE.** Sony Video 8 cassette recorders, model EVO-1000B PAL. £125 + VAT. Sony PCM stereo processors for use with EVO-1000B. £100 + VAT pair £150 + VAT. ex-demo. Contact G.V.C. SERVICES, Unit 9, Woodcock Hill Ind Estate, Harefield Road, Rickmansworth, Hertfordshire. Tel. 0293 896293.

**WANTED VALVES** EL37, KT66, KT77, KT88, PX4, PX25. Complete collections, shop clearance. Also transistors and IC's. Send written list, we reply within 24 hours. **BILLINGTON VALVES**, Oakdene Industrial Estate, Bolney Road, Cowfold, Near Horsham, Sussex RH13 8AZ. Phone 0403 865105, Fax 0403 865106, Telex 87271.

**BROADCAST REDUNDANT EQUIPMENT** Vectorscope, Waveform Monitors, TBC's, min price £20.00 - max £80.00. Sold as seen. Tel: 0923-896293.

**AVO MULTIMETER** Model 8 £40.00, 500 volt Megers £30.00 prices plus VAT. Send S.A.E. for lists of surplus instruments & scopes etc. **A.C. ELECTRONICS**, 17 Apleton Grove, Leeds LS9 9EN. Tel 0532 496048.

**STANDARDS CONVERSIONS**, VHS, NTSC, SECAM-PAL N&M to VHS, PAL I, 'U' MATIC LB, NTSC-PAL to VHS, PAL I - £18.50 ph inc. Tel. 0923-896293.

**WANTED REGULAR SUPPLIES** of large & small quantities television & VHS videos, best prices paid. Tel. (0934) 641742 (daytime), 516483 (evening).

**FOR SALE TELEVISION MAGAZINES**, all copies April 1975-1991. Mint condition. Offers please. 0274 564893.

**SURPLUS COMPONENTS/PANELS**, valves, tuners, I.C.'s. Best offer will obtain. Wanted: Television Magazines. Nick (Ilford) 081-503 9136.

**OCHRE MILL TECHNICAL SERVICES**. Grundig TV spares for most models to 1985, fast, friendly, helpful, sensible prices. Gr Lype Farm, Charlton, Nr. Malmesbury, Wilts SN16 9DR. Tel. 0666 823228.

**PRIVATE RETAILER** has excellent part-exchange colour televisions to clear. 0494 814317.

**TRY BEFORE YOU BUY.** TV, Video, HiFi sales, service business, south side of Glasgow. Cheap rented shop. Box No. 260.

**WANTED OLD VALVE RADIOS** and black and white television, any condition, any area. Telephone 0283 35639 evenings.

**AMSTRAD SATELLITE OWNERS.** Convert to tuneable audio, more stations, free leaflets. EMO Ramsbottom, Lancashire BL0 9AG. Tel. 0706 823036.

**METERS RECONDITIONED** £1.00, slot meters for TV Rental £5.95, 50p slot £2.95. Tel. AUDIOTECH 07903 245.

**METERS** Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) Ltd. (0202) 683498.

**WANTED EX RENTAL** colour TV's. Cash on collection. Quick service. 0742 312832.

**BUSINESS FOR SALE**, TV/video sales/repairs with video library. Leasehold, lockup shop. Further details on application. Tel. 071-274 8669.

**WANTED HANDSETS** for Amstrad teletext CTY 2210. Tel. 051-639 7235.

### SPARES & COMPONENTS

**TOP CLASS PANASONIC WORKING TV & VIDEO**

+ **GOOD CHEAP STOCK "OFF THE VAN"**

Good Selection of Makes

**Tom Poole or Brian Ricketts**

**061-273 2854/274 3409**

**REPO**

**DAISY WORKS,**

**345 STOCKPORT ROAD,**

**LONGSIGHT, MANCHESTER**

(A6 Between Stockport & Manchester)

### SPARES

A massive purchase of spares (ex Serviscope) enables us to offer very competitive prices on all T.V., Video, C.D. and Audio Spares.

All the common transistors and I.C.s available ex stock. We also have remotes, heads, test equipment etc.

**TRY US FOR THAT ELUSIVE PART!!**

**STOCKS AND SPARES**

Electronic Component Distributors, Unit 2, Victoria Mill Estate, Manchester Road, Droylsden,

Manchester M35 6EQ

TEL: 061-370 7959

FAX: 061-371 8398

ACCESS MAIL ORDER VISA

P.S. HAVE YOU JOINED "THE LIBRARY" YET - SEE OUR OTHER AD!

### West Wales Wholesale TV

Working TVs from £18.

Videos from £60.

Discount for quantity.

**8 CILLEFWR IND. EST.  
JOHNSTOWN CARMARTHEN  
(0267) 222047**

## TELEVISION CLASSIFIED LINEAGE

advertisements can be submitted on this coupon with a cheque made payable to Reed Business Publishing Group. Television Classified Room L327, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. The charge per word is 70p plus 17½% (minimum £12.00 + VAT.)


For Issue Dated ..... or next available. Total insertions ..... Total of Cheque £.....  
Name ..... Address .....  
Post Code ..... Tel Num ..... Signature .....



**Debit my Access/ Visa Card (delete)**



Expiry Date ..... VAT Reg. No. 238 8937 10

# CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

## ELECTRONIC COMPONENTS

ADD 17.5% VAT and £1.18 POSTAGE TO TOTAL

TV & VIDEO I.C.s		
AN262	95	LA7033 2.80
AN304	2.52	LA7210 1.25
AN5015K	2.50	LA7505 1.75
AN5612	1.54	LA7910 1.05
AN5620X	2.65	LU11417A 3.60
AN6306	5.50	LU52511A 3.60
AN6320N	2.10	LVA508 1.40
AN6326N	2.45	LM1889N 2.80
AN6328	2.45	M51393AP 2.50
AN6346N	2.62	MC1408PB 1.00
AN6347	2.10	MN15823FVG 10.80
AN6350	4.27	OEC0001B 4.45
AN6360	1.82	OEC0005 4.45
AN6362	2.95	OEC2001 2.85
AN6881	2.30	SONY CX134A 4.25
BA618	1.15	TD62105P 1.00
BA6301	1.40	ULAIH035E2 1.55
BA7001	1.05	UPA53C 3.45
BA7004	1.40	UPC1382C .77
BA8500	9.95	UPC1397C 3.15
HA17458PS	70	14DN156 4.50
LA7031	1.75	14DN157 4.50
LA7032	2.06	14DN244C 4.85

All Satellite equipment prices include VAT; Post and Packing Extra.

**LNB's**  
10.95 - 11.7GHz

2.3dB max.	£30.65
1.4dB max.	£79.39
1.2dB max.	£89.50
1.1dB max.	£110.15

**Prime-Focus Feeds**

Ku-Band Feed Horn	£26.50
C Band Feed Horn	£42.25
Racal Magnetic Polariser	£42.75

**Global Accessories**

Line Amplifier	£23.19
2 way Splitter	£19.21
4 way Splitter	£36.58
V/H Switch	£49.45

## AMSTRAD

4600 Video and Audio PCB	£17.63
4600 Systems Control/Servo PCB, Display and Control PCBs	£29.38
4600 MkII Video and Audio/Timer/Control PCB Assy.	£40.82
4700 Video and Audio/Timer/Control PCB Assy.	£40.82
VCR100 Video and Audio/Timer/Control PCB Assy.	£40.82
5200 Timer and Channel Display PCB Assy.	£17.63
5200 Audio Tuner PCB	£15.28
5200 Video PCB	£14.10
5200 Syscon. Servo Power PCB	£23.50
5200 Varicap Tuner Type 1810829	£7.05
4600 Video Cassette complete mechanism (no drum or video heads)	£29.38
4600 Video Cassette complete mechanism (with drum no video heads)	£35.25
4600 Mk II/4700 Power Supply	£4.70
4600/4700 Capstan Motor	£11.75
7000 Loading Motor MCB2B01	£3.53
9000 Loading Motor MCB9B02	£3.53
9000 Cassette Housing Assy.	£15.28

**HANDSETS**

VCR4600/4600MkII	£11.75
VCR4700	£17.63
VCR5200	£11.75
VCR6000 Easy Programme	£25.85
VCR6100 Barcode	£29.38
TS90/99 Tower System	£11.75
VCR9000 Handset	£11.75

CTV2000 Line Output Transformer FB171	£9.40
CTV2200 PCB No:3 (Part 270087)	£3.53
CTV2200 PCB No:4 (Part 270088)	£4.70
TVR1 Control Panel/Preset PCB	£7.05

AMSTRAD SPARES: PRICES INCLUDE VAT, POST AND PACKING EXTRA.

ALL ITEMS ARE BRAND NEW AND GUARANTEED  
\* \* SAME DAY DESPATCH \* \*  
Write or Phone for FULL catalogue.

## Harrison Electronics

CENTURY WAY, MARCH, CAMBS PE15 8QW. FAX: (0354) 51416. TEL: (0354) 51289

## THRIFTY SPARES (WALES)

C/O CENTREVISION, SLOPER ROAD, LECKWITH, CARDIFF CF1 8AB  
INCREASE YOUR PROFITS WITH USED SPARES

MANY MAKES OF USED VIDEO AND TV PANELS - GUARANTEED WORKING HUNDREDS NOT LISTED - PHONE OUR HOTLINE

# 0222 344218

VIDEO THORN, HITACHI, TOSHIBA, I.TT, SHARP, AMSTRAD, PANASONIC ETC.

USED WORKING VIDEO SPARES	From	
MIXED BOOSTER	£12.80	WORKING DORIC MK3, MK4, MK4A BOARDS
SERVO PANEL	£15.50	MK3A LINE SCAN (STATE TUBE) £10.00
LOADING MOTOR ASS	£10.50	MK3A POWER PANEL £10.00
BOTTOM BOARD	£20.50	MK3A IF VIDEO ETC. £8.00
MODULATOR	£15.50	MK4 LINE SCAN £22.50
MECH 'A' COM	£15.50	MK4 POWER PANEL 90 OR 110 £15.50
DRUM ASS	£12.80	MK4 IF PANEL £12.50
CAPSTAN MOTOR	£15.50	MK4 VIDEO £7.50
POWER PANEL	£15.50	MK4 MANUAL TUNER HEAD ASS £5.00
TUNING BOARD	£18.00	MK4 REMOTE BOARD £12.50
		MK4 TEXT BOARDS £10.00
		MK4 FRONT ASSEMBLY £10.00
		MK4 TRIPLERS £5.50
		MK4 CRT TUBE CALLERS ONLY £23.00
		MK4 TEXT HANDSET £14.50
		MK4A TEXT HANDSET £14.50

ALL ABOVE PRICES VAT INC. MANY MAKES OF TV USED - SPARES ALSO IN STOCK  
OPENING HOURS 9am-1pm - 2pm-5pm  
POSTAGE & PACKING £2.50 ORDERS OVER £50 P&P FREE  
DON'T DELAY PHONE 0222 344218 TODAY 24 HOUR ANSWER PHONE

## CATHODE RAY TUBES

For scopes, radar, professional - regret no domestic television types

ICP1	£29.50	D13 611GH	£59.00	F16 101GM	£75.00	M31 182GV	£45.00
12CP4	£35.00	D13 603GH	£39.00	21 130GR	£75.00	M31 184W	£55.00
1074H	£45.00	D14 200GH	£75.00	F31 12LD	£75.00	M31 190GR	£45.00
30780	£95.00	D16 100GH97	£65.00	L708	£75.00	M31 191W	£58.00
8931 (W.H.)	POA	DG7 5	£45.00	H7 120W	£19.50	M31 325GH	£35.00
CME 822W	£7.00	DG7 6	£45.00	H14 100GH	£35.00	M38 100W	£59.00
CME 1523W	£9.50	DG7 32	£55.00	M17 151GVR	£175.00	M40 120W	£59.00
CRE 1400	£29.50	DG7 36	£55.00	M21 11W	£55.00	MV6-5 (MM1)	£30.00
D9 110GH	£45.00	DH3-91	£50.00	M23 112GV	£45.00	S65FF31	£45.00
O10 220GH	£45.00	E723 (EEV)	POA	M24 121GH	£55.00	19750	£75.00
O10 230GH	£45.00	ECR3-5	£39.50	M24 122WA	£55.00	VL3429A5	POA

Phone or fax for any type not listed - 5000 types in stock.

IMPORT/EXPORT/AGENCIES, VALVE/CRT DEALERS ETC.  
PLEASE FAX FOR COPY OF WHOLESALE CATALOGUE.

Also 1,000,000 valves in stock for television, audio etc.  
Minimum order £50.00 + VAT. PLEASE FAX FOR QUOTES.

## BILLINGTON EXPORT

F2 Oakdene Industrial Estate, Near Horsham, West Sussex RU13 8AZ

UK callers by appointment only, 9am to 5pm, Monday to Friday

TELEPHONE: 0403 865105

FAX: 0403 865106

## ALLPARTS DISTRIBUTORS

### SATELLITE SPARES

TV & VIDEO SPARES FOR THE TRADE AND PUBLIC  
BELT KITS, TRANSISTORS, ICs, REMOTES,  
FERGUSON, PANASONIC, SHARP, GRUNDIG, SONY,  
KONIG, PHILEX, AMSTRAD

### ALLPARTS DISTRIBUTORS

101 ROCKY LANE, TUEBROOK, LIVERPOOL L6 4BB

051-260 4825

## VIDEO STANDARDS CONVERSION

American NTSC to PAL

Vice Versa to and from any video format

£19.50 fully inclusive.

**GTV** 850 Manchester Road,  
Bury BL9 8DU.  
Tel: 061-767 9067

## SURPLUS/REDUNDANT ELECTRONIC COMPONENTS WANTED

I/Cs - Tuners - Transistors - Valves - Diodes etc, any quantity considered - immediate payment.

ADM Electronic Supplies

Tel. 0827 873311. Fax 0827 874835

## LOST COST REPLACEMENT L.O.P.T.

Fidelity 3000 chassis 14 and 20 inch  
£8.50 each + £1 P&P + VAT  
Send large SAE for list of bargain priced spares.

**A.G.S. ELECTRONICS**

Unit 2, Haxter Close, Belliver Ind Est,  
Plymouth, PL6 7DD. Tel: 0752 767738

## ADMIN TELEVISION

KT3 BASIC	£15.00
GEC 26 CHASSIS	£20.00
ITT	£15.00
K30	£15.00
MK 4 DORICS	£15.00
ALL TEXT	£35.00
PORTABLES	£40.00
G11 TEXT	£20.00
TX9s/10s	£15.00
PHILIPS G11 BASIC	£12.00
JAPS	FROM £10.00

VIDEOS FROM  
£20.00

ALL REMOTES  
£25.00  
ALL PRICES PLUS VAT

PHONE

051-548 4414

UNIT J, ADMIN BUILDINGS,  
KIRKBY, LIVERPOOL L33 7JX

## RCS VARIABLE VOTAGE D.C. BENCH POWER SUPPLY

1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps D.C. Fully stabilised. Twin panel meters for instant voltage and current reading. Overload protection.

Fully variable. Operates from 240V A.C.  
Compact Unit: size 9x5 1/2 x 3ins. £45 inc. VAT + Post & Ins. £4  
NEW MODEL. Up to 38 volts DC at 6 amp. 10 amps peak. Fully variable. Twin panel meters. Size 14 1/2 x 11 x 4 1/2. £96 inc. VAT. Carr £6.

## RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON  
SURREY, U.K. Tel: 081 684 1665

ACCESS VISA

List, Large S.A.E. Delivery 7 days Callers Welcome Closed Wednesday

## ASJAA INTERNATIONAL LTD

Japanese Components Specialists  
Electronic Comp. Distributors  
(IMP/EXP)

2SA 2SB 2SC 2SD AD BC BD BF  
BU BUW BUX BUY MJE 1N TIP  
AN BA CX HA KA LA LB LM M MB  
NE STK STR TA TBA TDA UPC

WE ARE PRESENTLY UPDATING OUR  
STOCK SO YOUR ORDERS WILL HAVE  
NO DELAYS.

OUR CATALOGUE WILL BE OUT IN  
OCTOBER 91

Stockist of:

IC's & TRANSISTORS, AUDIO/VIDEO  
HEADS, MOTORS, IDLERS, PULLEYS,  
RX ROLLERS, BELTS AND TYRES FOR  
RADIO CASSETTE, VIDEO & TV

36 Gloucester Road, North Harrow,  
Middx HA1 4PW England (UK)

Tel: 081-427 8213 Fax: 081-861 1282

Telex: 933986 G ATT: ASJAA

# CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

## WIZARD DISTRIBUTORS MANCHESTER

### TV, VIDEO & SATELLITE SPARES

FERGUSON, HITACHI, I.T.T., LOWE OPTA, PHILIPS, SAKURA, SHARP, TATUNG, & MANY OTHERS

**MAIN DISTRIBUTOR FOR SCHNEIDER NON ACCOUNT CUSTOMERS**

Fidelity Spares Main Distributor

**Always in stock—**  
Video Heads for over 500 models  
Service Manuals for over 200 models  
Handsets for over 200 models  
Spares for over 20 manufacturers

Plus huge range of IC's, Semiconductor and Service Aids, etc. etc.

**SATELLITE SPARES NOW AVAILABLE ASK FOR CATALOGUE SUPPLEMENT**

**WIZARD OFFER A GREAT DEAL**  
Counter open Monday-Friday 9am-4.45pm  
Mail Order-Access/Visa

**TRADE ONLY**

**EMPRESS STREET WORKS, EMPRESS STREET, MANCHESTER M16 9EN.**  
Tel: 061-872 5438; 061-848 0060.

## HITACHI VT8000 and VT8500's

Top Loaders  
VHS Models

### MANY REMOTE MODELS

Complete Untested  
**£20 + VAT**  
Working Units  
**£40 + VAT**


## BENTRONICS LTD.

500 Thornton Road, Thornton, Bradford, West Yorks.  
Tel: 0274 832195  
Fax: 0274 830339

Callers by appointment only. Nationwide Delivery
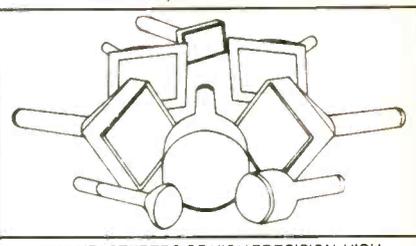
## NEW CENTURY ELECTRONICS LTD.

UNIT 3, SWAN WHARF, WATERLOO ROAD, UXBRIDGE, MIDDLESEX UB8 2RA.



MANUFACTURERS OF HIGH PRECISION, HIGH RESOLUTION PHOTOQUALITY CATHODE RAY TUBES

Applications:—

- Scanning Electron Microscopes
- Medical Imaging
- Telecine
- Camera Viewfinders etc

Remanufacture Service also available

Why not telephone Dave Dyson on (0895) 255800 to discuss your requirements?  
Fax No.: 0895 255619

## SATELLITE

# J.W. HARDY

## COMPARE THE VALUE

### NEW FROM PROMAX



**MC-312 - INSTANT STREAMLINED ACTION FOR THE PROFESSIONAL AERIAL INSTALLER & SYSTEMS ENGINEER**

Optimizes tuning process with digital frequency meter, 30 programmable tuning memory, 60 dB attenuator. **£545 + £8.00 pp.**

**MC-160 - FOR THE DISCRIMINATING TV/AERIAL INSTALLER**

Remarkable performance - capable of systems work. Built-in frequency meter. Easy to carry. Low cost. **£344 + £8.00 pp.**

**MC-477B - TOP OF THE RANGE FOR THE PROGRESSIVE SYSTEMS ENGINEER**

Spectrum analyser. Built-in monitor. Viewable dB frequency. 39 programmes can be pre-tuned. **£1200 + £8.00 pp.**

**SAT SIGNAL DETECTOR**

MS-150 Permits a TV-Sat antenna to be optimally directed to required satellite. Built-in sound indicator. **MS 150 + £2.50 pp.**

**SAT SIGNAL LEVEL METERS**

**MS-450** Measures signal levels from -60 to -10 dBm. Accoustic signal level indication. Frequency digital display. **£378 + £8.00 pp.**

**MS-850B** Same features as MS-450 plus additional channel selector and video output. **£938 + £8.00 pp.**

All models (except MS-150) are complete with superb padded carrying case in highly resilient black nylon.

## CONSULTANT IN SATELLITE TV & TV DISTRIBUTION NETWORK SYSTEMS.

### PALCOM SATELLITE RECEIVERS


SL500 **£179.00**  
SL4000RP **£335.00**

Antenna Mounts, Stands, Universal Remotes, Polarscans, OMT's, LNB's. P.O.A.
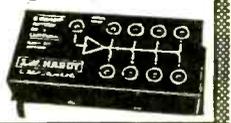
### J.W. HARDY 8-WAY UHF AMPLIFIER

FOR TV DISTRIBUTION

High quality - top value. Frequency 470-860MHz. Gain: 20dB per outlet. Power: 20W AC 4.5 Watts. Rugged, screened case. **£18.95**



### NEW REMOTE LEARNS UP TO 124 COMMANDS!

Universal Remote Control. Macro function - 4 commands in 1 button. Easy to use. Outmodes ordinary remotes. **£21.00**

### MAXIMISE YOUR AERIAL PROFITS!

10 Element TV Aerials (indoor/outdoor) with pole mounting bracket. Box of 24. **ONLY £54.00** (ie £2.25 each). 1-off sample **£6.00**

### ANNOUNCING Pace 9200 IRD

90 channels, enhanced frequency scan mode. Plus access to all receiver features as well as favourite channels. P.O.A.

## Can we help you?

All the items below are provided with full technical assistance and service back-up. We shall be pleased to offer advice on suitability and fitting of any of our products. Let us know how we can help you.

**TRADE ONLY** PHICES CORRECT AT TIME OF GOING TO PRESS

**MINIMUM TRADE ORDER £60.00**

All prices quoted are plus carriage, plus VAT

**021-784 8478**

J.W. HARDY, 231 Station Road, Stechford, Birmingham B33 8BB.

## U.H.F. Aerials

Groups A, B, C, D & W

### THE DIAMOND RANGE

Diamond DC 10 Housed **6.95**  
Diamond DC 18 Housed **9.95**  
Diamond Colour Grid **16.95**  
Diamond Quad 8 **16.60**

### THE TRIAX RANGE

Units 24 **20.17**  
Units 24 **25.10**  
Units 32 **42.13**  
BB Grid **16.95**  
Yagi 10 **8.38**  
Yagi 20 **21.63**

## Chimney Lashing

Standard Repair Kit **1.28**  
5 Metre Wire Coil **0.80**  
Corner Plates **0.06**  
1.4" J Bolt & Nut **0.14**  
1.4" V Bolt & Nut MS **0.12**  
2.1/2" V Bolt & Nut **0.22**

### Chimney Brackets

6" x 6" Pressed **0.68**  
6" x 6" Welded **0.98**  
6" x 9" Welded **1.48**  
7 1/2" x 7 1/2" Welded **2.15**  
1 1/2" Cradle Welded **2.85**  
Double Lashing Pair **2.85**

### Clamps

Aerial to Mast Clamps  
15mm to 2 1/2" **0.30**  
Cross Clamp **0.65**  
V Bolt & Nut M6 **0.12**  
Armsat Stud to Mast **2.73**

Mast to Mast Clamps  
1 1/2" to 2" Cross Clamp **0.75**  
1 1/2" to 2" Universal **1.60**

## Wall & Floor Brackets

6" x 6" Painted **1.97**  
6" x 6" Galv. or Polyester **1.48**  
6" x 9" Painted **2.26**  
9" x 9" All Angled, Painted **3.75**  
12" T & K Painted **5.27**  
18" T & K Black Polyester **4.75**  
18" T & K Black Polyester **6.27**  
24" T & K Painted **5.35**  
24" T & K Black Polyester **7.85**

### Spigot Sat Brackets

Ratio Mount 1 1/2" Black Poly **9.95**  
Ratio Mount 1 1/2" '90' Bend **10.95**  
Saddle Bracket Pair Wall **4.50**  
Armsat etc. Sat to Mast **2.75**  
24" H Duty Wall Black Poly **POA**  
28" H Duty Wall Black Poly **POA**  
36" H Duty Wall Black Poly **POA**  
2" Crossed Wall Stand Poly **POA**  
3" Ground Wall Stand Poly **POA**

### Fixings

Hilti HRD-11 10/10S & Bolt **0.32**  
Alungo 10 x 50A Bolt each **0.19**  
Alungo 10 x 50A Bolt each **per 100 14.00**

### Cable Clips

5, 6 & 7mm Uni Clip **per 100 0.78**  
9mm Uni Clip **per 100 0.95**  
11mm Uni Clip **per 100 1.05**  
13 x 7mm Uni Clip **per 100 1.25**  
6 x mm Tower Clip **per 100 0.78**

### Adhesive Tapes

20M 3/4" PVA **3.70**  
10M x 19mm PHS Self Amalg. **3.70**  
10M x 25mm PHS Self Amalg. **3.70**

## Attenuators

1/2, 1, 2, 3, 6, 12, 18, 24 dB **1.25**  
1/2, 3, 6, 12, 18 dB **1.40**

## Sat. Antenna

Dish with Polar Mount & Feed with Wall or Floor Stand, Spigot Aerials

90cm 2" **105.00**  
90cm 3" **133.00**  
100cm 2" **143.00**  
125cm 2" **183.00**  
160cm 2" **273.00**  
180cm 3/2" **383.00**  
200cm 3/2" **410.00**

Dish Spigot Aerials on Ratio Ring  
90cm "1" Boss **75.00**  
90cm Feet Horn & Scaler **87.00**

Dish Sidel & Azel Mount  
60cm Mesh Concentric **25.00**  
90cm Mesh Concentric **45.00**  
60cm Mesh Marconi **35.00**  
180cm Gray Lensom Floor **50.00**  
120cm "1" Boss, Floor Stand **75.00**

## Amplifiers

Telesat Mast Head

Multi 4 and power **7274 19.95**  
Multi 3 and power **7273 19.95**  
UHF 15dB **7271 8.55**  
UHF 20dB **7076 8.55**  
UHF 20dB Cascode **7080 19.0A**  
UHF 20dB **7265 12.55**  
UHF 20dB Cascode **7268 12.55**  
Power Supply 20mA **7261 7.50**  
Power Supply 80mA **7262 12.50**

Telesat Multi Outlets

Two Set 7dB **7291 12.95**  
Two Set **7292 13.95**  
Three Set **7293 16.95**  
Four Set **7294 23.95**  
6 + 1 **7296 38.95**  
8 + 1 **7298 42.95**

Wobley Multi Outlets

Set Back 12dB **9.99**  
Two Set 7dB **9.99**  
Three Set 12 & 9dB **12.95**  
Four Set 12, 9 & 6dB **16.95**

J.W. Hardy Multi Outlets

4 Way 20B **12.95**  
8 Way 20B **18.95**

## Global Sat. I.F.

Spitters to 2 Tubs

2 Way 1004-2GHz **6.45**  
3 Way 9-2GHz **6.76**  
4 Way 9-2GHz Active **15.11**  
8 Way 9-2GHz Active **27.32**  
8 Way 9-2GHz **21.94**

Taps to 2GHz

1-Tap 12dB 1004-2GHz **5.45**  
1-Tap 10dB 1004-2GHz **5.45**

Spitters to 2GHz

2 to 1 V112 Pol/DK **20.45**  
2 to 1 V112 Pol **20.45**  
2 to 1 V113 13/17V Line **14.90**  
2 to 1 V114 Vse 1 Adj **14.90**  
2 to 4 Magic 13/17V Line **18.18**  
2 to 4 Magic 13/17V Line **29.05**  
4 to 4 Magic Pol/DK **172.50**

Interface to 2GHz

INT 11 13/17V Line to 1Psi **19.32**  
INT 21 1Psi to 13-17V Line **24.15**

Frequency Converter

TE 11 Pulse Control **69.00**  
TE 2F V Control **69.00**

Power Supply

DC Back & Power Insert **19.04**  
DC Back & Power Insert **8.21**

Line Amplifiers

13at 9-2GHz **10.35**  
Slop 1004-2GHz **15.87**  
Slop 9-2GHz **21.39**

## Masts

12" x 1" Left Stand **1.00**  
24" x 1" with 90° Bend **1.35**  
5" x 1" 18g **1.63**  
6" x 1" 18g **1.93**  
13" x 1 1/2" 18g **9.05**  
16" x 2" 14g **9.18**  
20" x 2" 14g **26.00**  
20" x 2" 10g **26.00**  
20" x 2" 7g **P.O.A.**

Need

10" x 1" **1.95**  
13" x 1 1/2" **3.00**  
16" x 2" **8.00**  
18" x 2" **9.00**  
20" x 2" **10.00**  
4" x 1" x 1 1/2" dia 90° Bend Sat. **4.08**  
6" x 1" x 1 1/2" dia 90° Bend Sat. **7.50**  
"S" Bend for Sat. **2.80**

## Coaxial Cable

Priced in 100 metre lengths all Cables can be supplied in 100 or 250 Metre Lengths. Attenuation figures are approx at 900 MHz/100m

Voley Ranges

C55B 21dB Brown **11.95**  
C55W 21dB White **11.95**  
C56H 17dB Black Sat **11.95**  
C56W 17dB White Sat **11.95**  
CT101 19dB D.S. Sat **20.00**  
CT125 PVC 15dB D.S. White **22.90**  
CT125 PVC 15dB D.S. Black **26.00**  
CT125 PE 15dB D.S. **22.90**  
CT16725 PE 11dB D.S. **68.00**  
CT167 RBH 11dB D.S. **92.00**

J.W. Hardy

DS75 20dB D.S. **21.90**  
DS100 19dB D.S. **19.00**  
DS165 PVC 11dB D.S. **58.00**  
DS165 PE 11dB D.S. **58.00**  
DS1002 19dB Coax & Twin Sat. **35.00**

Alum

RC6 **13.90**

## Coax Connectors

Coax Plug Alloy Screwon each **0.30**  
Coax Plug Alloy Screwon per 50 **12.95**  
Coax Plug Alloy each **0.20**  
Coax Plug Alloy per 100 **12.95**  
Coax Coupler per 50 **5.95**  
Coax Coupler each **0.20**  
1" Screw per 100 **13.00**  
1" Screw each **0.20**  
1" Crimp Banded Ring per 100 **12.00**  
1" Loose Ring per 100 **9.00**  
1" Crimp Loose Ring per 100 **60.00**

## LNB, Feed, Polarota

LNB

Marconi Blue Cap **1.80B 40.00**  
Marconi Compact **1.6dB 45.00**  
M.T.L. **1.5dB 50.00**  
1.5dB **56.50**  
Sharp **1.1dB 60.00**  
Sharp Triple Band **1.5dB 149.95**

Feed

Marconi Horn **15.00**  
O.M.T. V-11 **45.00**

Polarota

Royal **29.95**  
IRTE **29.95**

Polarota/Feed

Agm 100 Pinc **29.95**  
Agm 101 CBSE **29.95**  
Marconi Bulhet **25.95**

Polarota Interface

IRTE **19.95**  
Rical **19.95**  
Chapal **24.95**

## Sat. System

Amethyst U 64dBmV **148.50**  
Amethyst W 64dBmV **181.50**

Telesat Sat I.F. 950-1750 MHz

4dB-14dBmV **5100 176.00**  
11dB-Line amp **5110 176.00**  
4 Way 7dB **5104 25.19**  
8 Way 7dB **5108 38.50**

## Filters, All Types POA

## Decoders

Video Crypt SVAC2 Reconditioned **43.00**  
Video Crypt SVAC2 New **65.00**  
Falcon MK II incl. lead **68.00**  
Falcon MK III incl. lead **78.00**  
Falcon Inter Face **18.95**  
Falcon MK II **52.00**  
Falcon Digital Sound **POA**  
Decoder Leads **4.50**

## Sat. Receivers

1000 9000 **120.00**  
Pace 9200 IRD **POA**  
Pace 9000 IRD **145.00**  
Armsat SRD400 **POA**  
Palcorn SL500 **179.00**  
Palcorn SL4000 **335.00**  
Pace 9000 Post-tune **73.00**

# CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED


**EURO-SAT**  
SUPPLIERS TO H.M.F. — M.O.D.  
MANUFACTURERS OF G.R.P. DISH ANTENNAS

1.0M DIA	£63.00	80cm DIA	£61.00
1.2M DIA	£65.00	2.0M DIA	£187.00
1.2m off set	£93.00	2.3m (PETAL)	£259.00
1.5M OFF SET	£119.00	3.0M DIA	P.O.A.
1.6M DIA	£119.00	FEED SUPPORT	
1.8M (PETAL)	£197.00	ASSEMBLY	£23.00

PLEASE NOTE: We are dish manufacturers only and do not supply systems.  
Please enclose S.A.E.  
EURO-SAT, 107 CROSS ST., SALE,  
CHESHIRE M33 1JM, ENGLAND  
TEL: 061-962 0542 — 061-881 4249

## VIDEO AND HANDBOOK TRAINING IN SATELLITE TELEVISION

*It's very very good!*

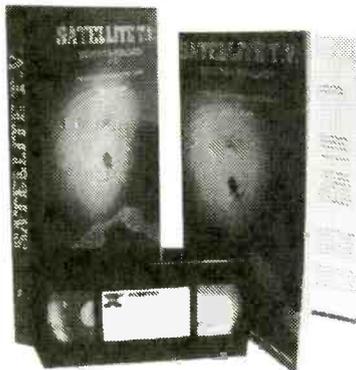

A 55 minute video with a lavishly illustrated supporting 46 page A4 handbook aimed at the practical sales person and installer. All you need to know to become conversant with the subject. A brand new course written and produced by experts in the industry. Send for full details.

Microforge Ltd., 339 Clifton Drive South,  
St. Annes, Lancashire FY8 1LP.  
Tel: 0253 725499

Please send me further information on  
"SATELLITE TELEVISION SERVICING  
AND INSTALLATION"

Name.....

Address.....

Post Code.....

## BOOKS & PUBLICATIONS

### SATELLITE BOOKS

#### WORLD SATELLITE TV & SCRAMBLING METHODS — NEW 2nd EDITION

£29

F Baylin, R Maddox and J McCormac. Large format 340 pages providing in-depth study of many scrambling methods.

#### EUROPEAN SCRAMBLING SYSTEMS 2 New!

£29

J McCormac. Circuits, Tactics and Techniques. How are smartcards hacked? How secure is VideoCrypt? Decoder circuits for Filmnet, RTL 4V and SAVE. Includes video manipulative systems.

#### KU-BAND SATELLITE TV — NEW 4th EDITION

£23

F Baylin & B Gale. Comprehensive introduction to satellite TV. Includes many footprints, dish theory. Completely revised edition.

#### SATELLITE TELEVISION INSTALLATION GUIDE — 2nd EDITION

£12

J Breeds. Europe's most popular satellite book. Includes all practical aspects of dish installation. Used in City & Guilds satellite courses.

#### VIDEO SCRAMBLING & DESCRAMBLING

£25

R Graf & W Sheets. Advanced theory. How to build encoders/decoders. Contains details of many cyphering patents and circuits.

#### SATELLITE, OFF-AIR & SMATV

£25

F Baylin, S Berkoff & T Meints. Aspects of private cable and multi-unit dwellings. SMATV systems in hotels, condominiums, apartments etc.

#### 1991 WORLD SATELLITE ANNUAL

£36

M Long. More than 600 pages. Includes over 100 footprints and other satellite details. Colour coded sections.

#### THE SATELLITE BOOK — A Complete Guide to Satellite TV Theory & Practice

£28

J Breeds. The definitive guide! Covers every possible technical and practical related subject. Invaluable tips and tricks of the trade. Well illustrated throughout. Easily the best value satellite book today!

#### NAUGHTY WINDOW STICKERS!

£1

Good quality — poor taste! Fun PVC window stickers. 'Satellite Installers Do It with their Parabolics!' Produced in two colours against a white background. Very popular with satellite traders.

ORDERING. Postage per book: Add £2.50 in UK. Add £5 for Europe. Add £15 for Rest of World.

Please send me the book(s) as indicated. I enclose cheque/PO for £ made payable to **Swift Television Publications**, or please debit my Access/Visa card;

Number  
Name  
Address

Expiry  
Signature  
Postcode



**Swift Television Publications**

17 Pittsfield, Cricklade, Wilts, SN6 6AN Tel or Fax 0793 750620

### MANUALS

1. WHY TURN WORK AWAY BECAUSE YOU HAVEN'T GOT THE MANUAL?
2. WHY BUY A MANUAL YOU MAY NEVER USE AGAIN?

JOIN "THE LIBRARY!"

A one off annual fee of £30.00 + VAT (£25.00 till end of September) gives you access to our vast library of manuals covering the full range of brown and white goods. Up to two manuals at any one time for up to two weeks. Have as many as you like during the year!! The best idea to hit the servicing trade in years!

Don't be the one that turns work away — be the one that counts the money!!  
LOTS OF SPARES AVAILABLE — SEE OUR OTHER AD!

**STOCKS AND SPARES**

Electronic Component Distributors, Unit 2, Victoria Mill Estate,  
Manchester Road, Droylsden, Manchester M35 6EQ.

TEL: 061-370 7959 FAX: 061-371 8398  
ACCESS MAIL ORDER VISA

### A GUIDE TO SERVICING DOMESTIC VIDEO CASSETTE RECORDERS

A fully comprehensive series consisting of 7 separate videos, with additional illustrated teaching booklets.

This set of teaching programmes is a must to anyone concerned with the understanding and repair of video cassette machines.

Programmes also available  
separately.

Microforge Limited, 339 Clifton Drive South  
St. Annes, Lancashire FY8 1LP  
Tel: 0253 725499

Please send me further information on  
'SERVICING DOMESTIC VIDEO CASSETTE RECORDERS'

Name.....

Address.....

Post Code.....

# VIDEO SERVICING 1989-90

Covers the following 227 models  
(plus cross references to 26 other models)

**AIWA**  
HVG-55

**AKAI**  
VS-422  
VS-425  
VS-427  
VS-467  
VS-485  
VS-765  
VS-767

**ALBA**  
VCR-4000 XI  
VCR-7000  
VCR-8000

**AMSTRAD**  
VCR8600  
VCR8700

**BAIRD**  
VC141L

**BUSH**  
VCR3401  
VCR3451

**DE-GRAF**  
WHS-FS4

**FERGUSON**  
FV20B  
FV21R  
FV22L  
FV26D  
FV30B  
FV31R  
FV32L  
FV33H  
FV37H  
VC141L

**FIDELITY**  
VR900

**FINLUX**  
VR3300  
VR3400

**GOLDSTAR**  
GHV1290i  
GHV1296i  
GSE1296i  
VCP4300i

**GOODMANS**  
VTV300  
VCP500  
VCP550  
TX1101  
PX1101  
PX2200  
PX2201  
VCR2500  
DX3300

**PANASONIC**  
NV-L20  
NV-L28  
NV-J30  
NV-J35

**PHILIPS**  
VR-6180  
VR-6182  
VR-6185  
VR-6285  
VR-6470  
VR-6490  
VR-6548  
VR-6648  
VR-6670  
VR-6870

**PIONEER**  
VR-525  
VR-727

**PYE**  
DV186  
DV190  
DV286  
DV571

**SABA**  
VR-6420  
VR-6640

**SAISHO**  
VXL12  
VXL12X  
VP3000  
VRS3200  
VR3300X  
VR3400  
VR3500

**GRANADA**  
VHS-FY1  
VHS-GY2  
VHS-GY4  
VHS-FS 4

**GRUNDIG**  
VS-500  
VS-520  
VS-540  
VS-550  
TVR-4500  
TVR-4510  
TVR-5510

**HINARI**  
VXL-8,9,11,19  
VXL-10  
VXL-12  
VCR-34H  
VXL-90  
VTV-100,200  
VTV-300

**HITACHI**  
F70  
VT-580E  
VT-520  
VT-522E  
VT-530E  
VT-580  
VT-M622  
VT-M630  
VT-M640E

**INGERSOL**  
VR965  
VR995

**ITT**  
VR-3619  
VR-3719  
VR-3749  
VR-3769  
VR-3908  
VR-3929  
VR-5720  
VR-5730  
VR-5740  
VR-5760

**JVC**  
HR-D320  
HR-D700EK  
HR-D750  
HR-D830

**LOGIK**  
VR945  
VR950  
VR955  
VR960  
VR960A

**SAISHO**  
VR3650  
VR3700  
VR3800  
VRS4000  
VRS4200  
VRS4400  
VRS5000  
VRS5000X  
VRS5500

**SALORA**  
SV-6800  
SV-6900  
SV-6910  
SV-9900

**SAMSUNG**  
VI-710  
VI-711  
VI-730  
VI-750  
VI-770  
VI-790  
VI-970

**SANYO**  
VHR-4150  
VHR-4350  
VHR-D4410  
VHR-D4610  
VHR-5200  
VHR-5240  
VHR-5350  
VHR-D5450

**SENTRA**  
VX8500LP  
VX8600LP

**MATSUI**  
VCP100  
VX730  
VX735  
VX735A  
VX750  
VX755  
VX765  
VX770  
VX850  
VX866  
VX877  
VX888  
VX3000  
VX6000  
VX6000A  
VX6600

**MITSUBUSHI**  
HS-B11  
HS-B21

**MURPHY**  
VCR-7101

**NEC**  
PX-1200K  
DX-1800K

**NIKKAI**  
J1

**NORDMENDE**  
V1005M  
V1005M1  
V1405U  
V1805K  
V1805U  
V1905K  
V4000 UNIC

**ORION**  
VCR-LA1  
VCR-L1  
VR-MDTT1  
VCR-X1  
VCR-M2  
VCR-L2  
VR-MDTT2S2  
VCR-LAD2S2  
VR-LD2S2  
VR-LD2  
VR-LD3  
VCR-M3  
VCR-LD3  
VCR-MD3  
VXL12  
VTV300  
D1200

**OSAKI**  
VCR-34H

**SHARP**  
VC-A100  
VC-A105  
VC-A111  
VC-A131  
VC-A140  
VC-A170  
VC-T310  
VC-A501  
VC-A502  
VC-T510  
VC-793  
VC-D801  
D805  
VC-A5011

**SONY**  
SLV-201  
SLV-301  
SLV-401

**TATUNG**  
TVP-1311

**TELEFUNKEN**  
VR-4935  
VR-4945

**THOMPSON**  
V-610  
V-630

**TOSHIBA**  
V-109B  
V-209B  
V-300B  
V-309B  
V-500B  
V-509B  
V-700B  
V-700H

# SPECIAL OFFER

WHILE STOCKS LAST

# VIDEO SERVICING 1987-88

ISBN 0 9513897 3 4  
MODELS COVERED

Model	Model	Model	Model
AKAI VS22	I.T.T. VR 3918	QUESTAR 100	200
AKAI VS23	VR 3919	SALORA SV6700	SV8700
AKAI VS25	VR 3938	SV8710	SV8800
AKAI VS35	J.V.C. HRD 170	SAMSUNG VI611	VI616
AKAI VS53	HRD 180	VI621	VI626
AKAI VS55	HRD 210	VB900	VB910
AKAI VS240	HRD 230	VRH 500	VRH 910
AKAI VS245	HRD 370	VRH 520	VRH 3100
ALBA VCR4000	HRD 430	VRH 3300	
ALBA VCR5000	HRD 530	SENTRA VX 5000	VX 8000
ALBA VCR6000	HRD 565	VX 8400	
AMSTRAD VCR6000	HRD 755	SHARP VCT 72H	VCT 781 HM
AMSTRAD VCR6100	MITSUBISHI HSB 10	SOLAVOX NCVR 1000	NCVR 5000
DECCA 8495 DK	HSB 20	TASHIKO VVE 922	VVE 931
FERGUSON 8951	HSB 30	TATUNG TVR 6111	VRH 8350
FERGUSON 3V64	N.E.C. DX 1000 K	VRH 8490	VRH 8495
FERGUSON 3V65	N 9053	VRH 8550	
FERGUSON FV10B	N 9055	TELEFUNKEN VR 2920	VR 2925
FERGUSON FV11R	N 9210	VR 2930	VR 2931
FERGUSON FV12L	NORMENDE V 1001	VR 2935	VR 2941
FERGUSON FV13H	V 1005	VR 2971	VR 3935
FERGUSON FV14T	V 1015	VR 3945	VR 3975
FIDELITY VCR 100	V 1025	TOSHIBA V77B	V80B
FIDELITY VCR6000	V 1035	V81B	V83B
FIDELITY VCR6100	V 1041	V85B	V90B
FISHER FVH-P 5000	V 1205	V93B	
FISHER FVH-P 5100	V 1235		
FINLUX VR 1010	V 1245		
FINLUX VR 1020	V 1305		
FINLUX VR 1025	V 1403		
FINLUX VR 1030	V 2405		
FINLUX VR 2005 SW	V 3005		
FINLUX VR 2010	V 3105		
FINLUX VR 2020 G	V 3405		
FINLUX VR 2020 W	V 4405		
FINLUX VR 2025 G	V 5005		
FINLUX VR 2025 W	NIKKAI NVR 100		
FINLUX VR 2040	NVR 500		
GOLDSTAR GHV 12401	PANASONIC NVG 25		
GOLDSTAR GHV 12441	NVG 40		
GOLDSTAR GHV 12461	NVG 45		
GOLDSTAR GHV 12481	NVG 48		
GOLDSTAR VCP 41301	PHILIPS VR 6462		
GOODMANS VCR 2000	VR 6465		
GRANADA VHS EH2	VR 6467		
GRANADA VHS EH3	VR 6468		
GRANADA VHS ES2	VR 6561		
GRANADA VHS EY1	VR 6760		
GRANADA VHS EY2	VR 6761		
GRANADA VHS F 63	VR 6843		
GRUNDIG VS 400	PIONEER VR 505		
GRUNDIG VS 440	VR 515		
GRUNDIG VS 450	VR 707		
HITACHI VT 410 E	PROLINE 5000		
HITACHI VT 420 E	7000		
HITACHI VT 430 E	9000		
HITACHI VT 450 E	9100		
	PYE DV 464		
	DV 468		
	OV 552		
	OV 761		

Radio & Television Servicing  
1985-1986 £10.00 each  
including delivery.

**£55.00**  
+ delivery.

For Special Offer please quote OCTOBER TELEVISION

## Interest Free Credit

On Video Servicing 1989/90. Send £50 with a £50 Post Dated Cheque for the following month and a £45 Post Dated Cheque for the month after that. Books despatched on receipt of order. If ordering a FULL set of books, please ring for credit details.

Post, Packing and Insurance

1 Book £4  
2 or more Books £7



NOTE:



Video Servicing 1989-90 is a TWO volume purchase and is therefore £7 delivery.

For Airmail delivery to Europe add £5 per book. For Australia, New Zealand & the rest of the world add £10 per book.

No VAT on books.

TELEVISION SERVICING 1989-90 £65.00

ISBN 0 9513897 1 8 Covers 749 models

Only 90 volumes now left

VIDEO SERVICING 1989-90 £138.00  
ISBN 0 9513897 2 6 TWO 336 page volumes covering 227 models.

Satellite Servicing  
over 80 models covered  
OUT SOON

Libraries and County Councils only supplied on Invoice. 28 days net.

U-VIEW 29 Warmsworth Road, Doncaster, South Yorks. England. DN4 0RP.

Tel: 0302 855017 Fax: 0302 855267

**CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED**

# Technical Information Services

76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE  
Tel. (0698) 884585 Mon-Fri 8.30am-5.00pm or (0698) 883334 Outwith business hours  
FAX facility available all day on both lines



Write now with an SAE for your **FREE QUOTE FREE VOUCHERS & FREE CATALOGUE**  
**!!NOW!! ALL TRADE ADDRESSES GIVEN !FREE!**  
**JUST PHONE TO FIND THE NUMBER OR ADDRESS YOU NEED**



## COMPREHENSIVE ELECTRONIC DATA REFERENCE MANUAL

*Incorporates:*

### ★ TELEVISION CHASSIS GUIDE ★

*This lists thousands of both colour & mono TV's, and all chassis are cross-referenced. This enables you to identify ANY chassis for ANY television from any equivalent model number.*

### ★ VIDEO RECORDER & CAMERA EQUIVALENTS ★

*This has the LARGEST number of models and all their equivalents ever compiled in one publication.*

### ★ AUDIO EQUIP', TEST EQUIP' DOMESTIC EQUIP' and LOTS MORE ★

*More information, again fully cross-referenced, on almost every piece of electronic equipment you could think of.*

COMES WITH: FREE UPDATING & £4 OF VOUCHERS. ALL CROSS-REFERENCES ARE QUICK & EASY TO FOLLOW.

**ONLY £5.95 FOR ALL THIS INFORMATION.**

Don't waste money on expensive imitations of this, THE ORIGINAL "TRADE REFERENCE GUIDE"

*Remember, not only do we have EVERY service sheet ever produced, but we also have*  
**THE WORLDS LARGEST COLLECTION OF**

# SERVICE MANUALS

**& WE ARE SOLE SUPPLIERS OF VARIOUS FAULT-FINDING GUIDES, REPAIR MANUALS & TECHNICAL MANUALS**

### INTEGRATED SYSTEMS FROM TIS

10 GIANT BINDERS of CTV CIRCUITS, LAYOUTS, WAVEFORMS plus OVER 20 CTV REPAIR MANUALS & Thorn's PAL System plus MUCH MORE for £399

ALL the ABOVE PLUS over £300 of TV Service Manuals PLUS other TV Books (enough to start a business) for £599  
6 GIANT BINDERS of VCR CIRCUITS, LAYOUTS, WAVEFORMS plus 30 matching FAULT-FINDING GUIDES for only £230  
**REMEMBER! WE HAVE HUNDREDS OF OTHER GUIDES & BOOKS, SO SEND AN S.A.E.**  
**NOW FOR OUR FREE CATALOGUE**

## NEW PRODUCT!!

*How many wasted hours have you spent on servicing?*

**E.C.S.** offers you complete index of approx. 5,000 TV and video faults listed in 10 years of TV mag.

Index's are alphabetically listed by make, model, fault and are now available for just:

**£7.50** for Television Faults

**£7.50** for Video Faults

or **£15.00** for both sets complete with protective ring binder. Regular updates are also available. But one of the above index's must be purchased in order to qualify for this service. To secure your order please make Cheques/Postal Orders payable to:

**E.C.S.**

**31 Prenton Road West,  
Prenton, Birkenhead,  
Merseyside L42 9PY.**

*Please add £1.50 per order for P&P*

## TV & VIDEO

### TRADE REFERENCE MANUALS

UNIQUE REFERENCE DATA FOR THE TV AND VIDEO SERVICING TRADE

#### ● TELEVISION CHASSIS GUIDE

Listing thousands of Models (Colour & Mono) and their Chassis Designations. Enables you to identify any chassis for any TV from the model number.

#### ● VIDEO RECORDER EQUIVALENTS

Lists all known models and their alternatives. Fully cross referenced for fast and easy use.

#### ● TRADE ADDRESSES

Hundreds listed including TV, Video, Test and Computers. Includes all the obscure and hard to find suppliers of the unusual brand names.

*These 3 books contain the most comprehensive reference data available anywhere for the TV and Video Trade.*

ONLY £5 EACH PLUS £2 POST/PACKING PER ORDER  
Phone your order with Access or Visa for immediate dispatch.

Hundreds of other Repair and Data Guides available from our Catalogue available FREE upon receipt of a stamped envelope.

### MAURITRON TECHNICAL SERVICES



8 CHERRY TREE ROAD  
CHINNOR, OXFORDSHIRE  
OX9 4QY



Tel:— (0844) 51694. Fax:— (0844) 52554

*Service manuals available — See our other advert elsewhere in the magazine.*

# CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

Ever wondered what happened to McDonalds TV & Radio Yearbook?

Now a superior yearbook is available! **MORE DATA, MORE PAGES  
LARGER CIRCUITS (A2) & NEW MODELS**

-----○○○-----

## TV-AUDIO-RADIO Complete Service & Repair Data Volume 2

-----○○○-----

### CTV

Our CTV section features the complete FERGUSON range TX-85/86/89/90/98/99/100 with EVERY modification & amendment known, PLUS all versions of the ICC5 chassis used in FERGUSON, NORDMENDE & TELEFUNKEN. PLUS PHILIPS 2A & 3A and SHARP chassis.

### SATELLITE

We have pages of general data as well as full coverage of the AMSTRAD/FIDELITY SRX-100/200, SRD-400 and the FERGUSON SRX-1/1S, SRB-1, SRD-2, SRV-1 and ALL OF PACE.

### VCR

For the first time anywhere, we have compiled general repair/servicing data for VHS camera recorders and VHS-C camcorders, featuring full data for the PHILIPS VKR-6800, AMSTRAD VMC-100 and FERGUSON FC-06.

PLUS - Special feature on the Atari ST-520/1040 all versions

Vol.2a - This book is packed with almost 150 large pages giving all required data, plus circuit and operational descriptions together with full FAULT-FINDING DATA including all the known STOCK FAULTS as well as the standard and possible faults with their cures.

Vol.2b - This is a HUGE binder packed with every CIRCUIT, LAY-OUT & WAVEFORM for every modification ever published. All pages are A2 or A3 in size! Diagrams can be up to 24" x 16.5" in size, which is the largest diagrams ever produced as standard in ANY yearbook.

**VOLUME 2A on its own is £16.95 VOLUME 2B on its own is £36.95**

**VOLUME 2 (COMPLETE) is only £49.95**

**VOLUME 1 is only £39.50 when you buy VOLUME 2**

-----○○○-----



## INFOTECH



76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML8 1HE

Tel. (0698) 884585 Mon-Fri 8.30am - 5.00pm

Tel. (0698) 883334 Outwith business hours

FAX facility available all day, Mon-Sat, on either line

Send a large SAE for your FREE catalogue of our other publications

### SONY TUBES REPROCESSED WITH ORIGINAL SONY GUNS

HIGH TEMPERATURE RE-PROCESSING of Sony, Mullard 45AX, 30AX, In-line, PiL, Mini (22.5mm) Neck and FST Tubes.

370KR822	£48.00	A51-231X	£46.00	A34JBU10X	£74.00
370LHB22	£48.00	A51-570X	£46.00	A49JHT00X	£64.00
400EFB22	£58.00	A51-580X	£46.00	A51EAL00X	£58.00
510YXB22	£58.00	A51-590X	£46.00	A51EB500X	£58.00
520SB22	£64.00	A56-540X	£48.00	A51JAR00X	£64.00
560GB22	£54.00	A56-701X	£48.00	A53JBW00X	£64.00
560DYB22	£54.00	A66-540X	£56.00	A59AK00X	£64.00
570HB22	£64.00	A67-701X	£56.00	AXM37-001	£48.00
680DB22	£85.00			AXT37-001	£44.00
680EB22	£85.00			AXT51-001	£46.00
				AXT56-001	£52.00

For tube types not listed please enquire.

All prices quoted are excluding VAT. Exchange CRT is required.

Callers welcome. Please phone first.

Your local stockists are:

**WELL VIEW,**  
114/134 Midland Road,  
Luton, Beds. LU2 0BL  
Tel. 0582-402499.

**WELL VIEW,**  
Southampton, Hants.  
Tel. 0703-449783.

**WEST ONE**  
Distributors Ltd.  
Chesham, Bucks.  
Tel. 0494-778197.

### TEST EQUIPMENT

## MÜTER · AT2 · BMR95 · BMR700

**AT 2, Audi-Multi-Tester,** 16 test-circuits for loudspeakers, tuners, amplifiers, headphones, tape recorders, mikes, boosters.



car radios, CD-players; measurement of millivolt, drift, watt, performance; with generator, radio, signal tracer/injector, 13 volt supply etc.



**BMR 95**

**BMR 700**



**Regenerating Computers & Measurers for CRT's** with cathode protection, gas clean-up aid, short repair; exhausted CRT's becomes bright and sharp again even if all other machines do not succeed.

United Kingdom: P & E Services, Llandudno, Tel. (0492) 549246, Fax 547880.

Ireland: Dönberg Electronics, Ranafast, Co. Donegal, Tel./Fax (0 75) 4 82 75.

New Zealand: TDON Ltd., Onehunga, Auckland, Tel. 6 68-9 07, Fax 6 68-4 99.

Germany: Ulrich Müter, Oer-Erkenschwick, Fax (0 23 68) 5 70 17.

# REBUILT TV TUBES

DIRECT FROM THE FACTORY  
WHERE THE BEST COSTS LESS

## FINEST QUALITY LOWEST PRICES

### SPECIAL DISCOUNTS FOR BULK BUYERS

2 YEAR GUARANTEE, 4 YEAR OPTIONAL

ALL MAKES INC. SONY

NATIONWIDE DELIVERY

**SHERWOOD TUBES LTD**  
60A PEVERIL STREET, NOTTINGHAM NG7 4AH.  
Tel. 0602 786896

## INFOTECH

76 CHURCH STREET, LARKHALL,  
LANARKSHIRE ML9 1HE

Tel. (0698) 884585 Mon-Fri 8.30am-5.00pm

Tel. (0698) 883334 Outwith business hours

FAX facility available all day, Mon-Sat, on either line



## PRACTICAL TV REPAIRS

by FC TUNBRIDGE BSc  
2nd Edition



At last! The BEST SELLING TV book  
has been updated.

The 1st Edition became a trade standard for general fault-finding in all types of TV, and is used by 1,000's of independent firms, engineers, universities, colleges, etc.

The 2nd Edition updates & improves the information covered in the first edition, PLUS, new fault causes and cures tables. Now includes modern digital chassis, NICAM sound and control systems.

All repair data in this publication is complete with all known possible standard faults. Not just the few random, useless tips as found in any other 'competitors' manuals.

What are people saying about it?

"... Mr. Tunbridge is a Genius ..." J. McDonagh F.S.T.R.E.E.

**BUY NOW, AND YOU TOO WILL DISCOVER WHY.**

We think it is the most comprehensive  
and easily understood book of its kind

For a limited time only price held at



# CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED



## SERVICE MANUALS



Available for most Video Recorders, Colour & Mono Televisions, Cameras, Test Equipment, Amateur Radio, Vintage Valve Wireless, Any Audio, Music Systems, Computers, Kitchen Appliances etc.

Equipment from the 1930's to the present and beyond.

Over 100,000 models stocked, originals and photostats.

FREE catalogue Repair & Data Guides with all orders.

**MAURITRON TECHNICAL SERVICES (TV),**  
8 Cherry Tree Road, Chinnor, Oxfordshire OX9 4QY.  
Tel: (0844) 51694. Fax: (0844) 52554

### SERVICE MANUALS

THOUSANDS OF DIFFERENT MODELS HELD IN STOCK.  
PRICES: VCR from 10,000, CTV from 5.50, MTV from 3.50.  
ALL UK ORDERS SUBJECT TO 1.00 P&P. NO VAT.  
AUDIO, SATELLITE, MICROWAVE ALSO AVAILABLE.  
WRITE FOR EXACT QUOTE TO—  
**D-TEC, PO BOX 1171, FERNDOWN,**  
**DORSET, BH22 9YG.**  
'phone 0202 870656.

### GERMAN SERVICE SHEET SPECIALISTS

Our connections are world-wide. We furnish any kind of German, European and Japanese service sheet or manual. Thousands of different sheets and manuals in stock. For any enquiries:

**DÖNBERG ELECTRONICS**  
Schoolmasters House, Rannafast,  
Co. Donegal, Republic of Ireland.  
Phone: 075 48275

### FAST FIX

It's quick, compact, easily updated.

It's fault finding made easy.

THIS CARD INDEX SYSTEM CONTAINS COUNTLESS TV, VIDEO & CD FAULT SYMPTOMS AS PUBLISHED IN TELEVISION FROM 1981-1990 INCLUSIVE. FAST FIX TV £20.00. FAST FIX VIDEO £20.00.

For further details ring  
**A.G. HUMPHREYS ON 0244 532961**

### THE VINTAGE WIRELESS AND TELEVISION BOOK LISTING.

Published regularly containing 100s of out of print, old and collectable wireless and TV books, magazines etc. Send four first class stamps for next copy or £2.25 for next four.

**WANTED** Pre 1975 Wireless and Television books and magazines, manuals or any printed material relating to wireless and television.

**BRITISH TELEVISION. THE FORMATIVE YEARS.** R Burns. Special purchase of an out of print book on early television. Organised by J.E.E. History of Technology in association with the Science Museum. Covers the period 1922-1939. 488pp. Well illustrated. A highly collectable item based on written primary source material. Published at £52. Our price £45 incl post. Access & Barclaycard phone orders accepted.

Dept T, **CHEVET BOOKS**  
157 Dickson Road, Blackpool FY1 2EU.  
Tel. 0253 751858

### MISC

#### VIDEO TRANSCRIPTION AND STANDARDS CONVERSION SERVICE

#### TO OR FROM VHS, BETA, U-MATIC, ETC

Tetris offers highly competitive terms for copying any video format - VHS, Beta - or any other type - converting to or from UK Continental, Middle East, Far East, American or any other standards.

#### ALL STANDARDS AND TAPE TYPES COPIED

We offer a rapid turn-round service.

#### TETRIS VIDEO TRANSCRIPTIONS

23 Fairmile, Henley-on-Thames, Oxon RG9 2JR  
Tel. 0491-574548 Fax. 0491-576270

### TEXSCAN CATV DECODER

Tuner FX range 54MHz-450MHz. Features: full 60 channel capability. High performance. 611 MHz IF. Built-in prescaler. Uses advanced ECL. Integrated circuits and dual gate MOSFETS. Output on channel 48 UHF-PAL synthesiser controlled. Brand new, boxed, with circuits and information. Not tested.

**TELFORD ELECTRONICS**  
Tel: 0952 605451. Fax: 0952 677978

### REPAIRS

#### LOEWE OPTA TV REPAIRS FAST EFFICIENT SERVICE

Factory Trained Engineers  
Competitive Rates

**MARWETECH,**  
Unit A7B, Aladdin Workspace,  
426 Longdrive, Greenford,  
Middlesex UB6 8UH.

Tel: 081-575 0434 Fax: 081-575 0468

### BUSINESS FOR SALE

#### FREEHOLD BUSINESS PREMISES

2 3 bedroom living accommodation, beautiful, decorated throughout, with large fenced rear garden. Ideal for living & running TV and Video. Sale & Repair that goes with asking price of £71,000 o.n.o. There is also a block of rented videos and TVs to be sold for £35,000 which the buyer of the property has first refusal.

Phone 0642 485337

### TRAINING

#### BASIC ELECTRONICS TRAINING

Are you an employer seeking to provide your newest staff member(s) with a first class professionally structured and administered distance learning package, to the standards of the City and Guilds of London Institute 224 Electronics Servicing Course?

Yes! Then write or 'phone now:-

K. Sparrow etc... 11 Claydon Green  
Whitchurch BRISTOL BS14 0NG  
Telephone: Bristol (0272) 835669  
for a PART-PACK brochure.

#### Start training now for the following courses.

- Telecomms Tech C&G 271
- Radio Amateur Licence C&G
- Microprocessor
- Introduction to Television

Send for our brochure - without obligation or telephone us on 06267 79398 (Ref: TV10/91)

Name.....

Radio & Telecommunications  
Correspondence School,  
12 Moor View Drive, Teignmouth,  
Devon TQ14 9UN

### FOR SALE

#### MICRO-LAB

Save TIME and MONEY

by speeding up fault diagnosis.

Our MICRO-LAB instruments will help you find faults faster.

The improvements can be dramatic.

**We know! We use them!**

Write or phone for a free brochure.

#### COLEBOURN ELECTRONICS

Dept TV, 20 Folly Lane, Telephone  
St Albans, AL3 5JT 0727 44785

### TUBES

#### RENVUE CRT LTD.

All Types of Tubes, including

Sony, Monitors, V.D.U.,

FST & Glass Polished

New Tubes also supplied

Re-Gunned Mono Monitors

20" .....£25 + VAT

24" .....£30 + VAT

25a MONTROSE AVENUE

HILLINGTON

GLASGOW. G52 4LA

**041-883/8272**

**TX90 REMOTE PANEL IC TMS1000 AND M293 £12**  
**LNB's WITH FEED HORN AND POLARIZER 10GHz TO**  
**12.75GHz 1.5 db s.n. £35. SEND FOR DATA.**

**SATELLITE RECEIVERS**  
**19 C.H. with Hand Set £40**  
**32 C.H. £50**

**THORN FRAME IC**  
 TX100 etc  
 IC TDA 3652  
 IS OBSOLETE  
 REPLACEMENT  
 TDA 3654 £2.00

**JUST SPRAY AND IT IS CLEAN. PHILIPS' NEW**  
**VIDEO HEAD SPRAY CLEANER:**  
**£2.10 OR 10 FOR £1.50 EACH**

**60cm SATELLITE**  
**DISH £35**

Philips Video  
 RTV Handset AV5661  
 with LCD AV5659  
 display £6

PB500 Panic and Button  
 Transmitter 180MHz £1.00  
 G11 CAP 250V, 470M £1.35

**6 TOUCH**  
**G11**  
**Replacement**  
**Draw Unit**  
**£10**

**TOSHIBA**  
**MAGNETRON**  
**2M172 AH**  
**£20**

**PHILIPS**  
**STEREO**  
**HEADPHONE**  
**£4.00**

**PHILIPS C.D.**  
**MECH. 691-30212**  
**£19.00**

VHF/UHF S.BAND TUNER £3.00  
 NEW PLASTIC CASE 32 C.H. SAT. RECV. POWER (no hand set) £35 (Post £5)  
 NEW METAL CASE SAT. RECV. £35 (Post £5)  
 DAM MAINS CHASSIS AMSTRAD MONITOR C £10  
 UNIVERSAL TRIPLER NEW TYPE £4.00  
 VIDEO LEADS 80p  
 AMSTRAD Line O.P. Transistors with Diode 2SD453 £1.00  
 BT 208A Lamps Long Life £1.00  
 VIDEO LAMPS Long Life £1.00  
 HITACHI & GEC FRAME Thick Film £6.00  
 FIDELITY SPLIT DIODE FCC2215AE £20 FCC2015BE £10 FCC2215BH £10  
 K30 FRONT PANEL TEL. TEXT TYPE £5.00  
 NEW G11 LINE-UP PANEL £8.00

**CAMCORDER**  
**SANYO**  
**NP22**  
 6v 1300mah  
 Rechargeable  
 Battery Pack  
**£6.00**

NEW PROFESSIONAL SATELLITE  
 RECEIVER WITH HAND SET.  
 METAL CASE WITH METAL  
 DOLBY CHANNEL C WITH  
 POLARIZER SUPPLY  
**£75.00**  
 SEND FOR DATA AND PHOTOS

PHILIPS YEARS AHEAD  
 THE CREDIT CARD CALCULATOR Solar Powered £3.75  
 NEW PHILIPS SBC 135 Solar & Battery Powered Calculator £8.00  
 THORN PANEL TX9 REC & REMOTE PANELS with Mains Trans £5.00  
 TX10 REC & REMOTE PANELS with Mains Trans £5.00  
 TX100 FRONT PANEL £5.00  
 TX10 TUBE BASE ON PANEL £3.00  
 TX91 £2.00  
 THORN TX STEREO SOUND O.P. PANEL (I.C. TA7227P) £5.00  
 THORN TX STEREO SOUND O.P. PANEL (I.C. TA7227P) £1.00  
 THORN VIDEO AERIAL AMP. OH. M4-597401 £6.00  
 ULTRASONIC TRANSDUCER £15p  
 IN LINE 12-35 VOLT SUPPRESSOR 4.000MRD £20p

**ELECTRICAL**  
**TEST METER £4**  
 Cost £50  
**COMPUTER £12**  
 4 13 Amp Sockets on  
 Distribution Box  
 with filters, plug and box lead  
 (3 amp per socket)

Gas Soldering Irons Special Price £8.00  
 Variety Nickel Cadmium Batteries from Telephone Type to  
 Sub-C 50p per cell. Mainly in packs of 6 to 12  
**AUTO RANGE**  
 DC and AC and Resistance Pocket 3000 Philips £12.00  
 G11 8 Touch Button with Lamps, Non-remote £18.00  
 Philips New Hand Set Digital RC5991 fit all  
 Text Sets after G11 £12.50

**NEW**  
**PANELS**  
**FIDELITY**  
 3000 Main  
 Chassis,  
 non-Remote  
 & Remote  
**£15.00**  
 and 4000  
 CHASSIS  
**£15.00**

K75-K30-K4-K40 CTC ETC Mains Switch 75p each  
 G8 LOPTS PHILIPS £6.00  
 G11 LOPTS £3.00  
 PHILIPS DESK TYPE Dual Power Calculator SBC1704 £7.00  
 K40 FOCUS POT £1.00  
 L7p K13 W/W 10 for £1.00  
 FOCUS POT HDK TP4000 £2.00  
 K75 Triplers £5.00  
 K3 Text Front Panels with L.C.S (SAA 9027) SBA3013  
 (H0448326) £5.00  
 G8 100k Flats on Panel & Lead for 6 Push Button Unit £2.00  
 K30 Mains Switch remote £1.00  
 K35 Mains Switch remote 75p  
 K35 Aerial Socket and Plug in Lead to Tuner £1.50  
 K13-K30 Slider Pots 4.7k 20p each

Philips Stereo Headphones No. SBC 3140 £4.00  
 Stereo Headphones cost £7.50  
 Philips SBC3040 Mono Uni Directional Condenser Microphone £9.00  
 Microphone Philip Dynamic £6.00  
 10mm THICKNESS SOLAR POWER RADIO WITH EARPHONES £2.00  
**TX9-TX100 FRONT PANEL £5**  
**WITH REMOTE £10**  
**NON REMOTE**  
**8 push button £10**

PHILIPS Desk Calculator £7.00  
 PHILIPS UNIVERSAL BATTERY TESTER SBC 1695 £5.00  
 GEC 20AX POWER SUPPLY Mark 1 and 2 £10.00  
 ONE I.C. K35 Decoder £10.00  
 REGULATED PWR. SUP. 300MA 1.5V-12V DC switched & + £5.00  
 ITT Tuner & HF. Car HF-module 2 UK £20.00  
 K13-K30 HF £5.00  
 PROBE £4.00  
 WIRE PIPE stud detector £4.00  
 MICROWAVE leak detector £4.00  
 WIRE & PIPE detector £4.00

**STEREO HEADPHONES** £1.00  
**THORN RECEIVER**  
**PANEL TX100** £6.00  
**STEREO K30**  
**SOFT O.P. PANELS** £2.50  
**NEW**  
**PHILIPS DUAL TRACE**  
**OSCILLOSCOPE SBC30** £165  
**G11 470 MFD 250V**  
**£1.35**  
**CAR ADAPTOR**  
 fused 3Amp  
 Long Lead with plug  
 for TV etc  
 25p 500 ohm, 15p Each  
**TELEPHONE LEADS**  
 With Plug, 4 Wire & 6 Wire  
 Plug and Socket 15p  
**TELEPHONE EXT. LEAD**  
 3 Metre 30p  
**SCART TO SCART LEAD**  
 All Pin Long £2.50  
**BRIDGES RECTIFIER**  
 Mixed BR-31 to 34  
 2 Amp to 5 Amp 8 for £1.00  
**TX90 MOD 37 4B**  
 The Sweep Tuning System  
 TX9139/001 £8.00  
**T6070V TX9 Transistor** £1.00  
**TX9 90D4-106-034** £1.00  
**TX9 90D4-109-001** £1.00  
 Chopper Transformer £1.00  
**TX9 063-025-011 Choke** £1.00  
**TX9 90D4-093-011 CRTG** £1.00  
**VIDEO SCART TO SCART**  
**ALL PIN. LONG LEAD**  
**£3.00**  
**TX90 TX95 TX100**  
 Mains Switch with Stand-by  
 and Lead 3 for £1 or 50p each  
**UNIVERSAL VIDEO-RECORD**  
**KIT STEREO**  
 This kit may also be used to  
 connect a mono to stereo. £10.

LARGE Focus Pots, Flats, Pvc, GEC, ITT, Decca  
**L.C.D DISPLAY LANGUAGE**  
**TRANSLATOR — ENGLISH, FRANÇAIS,**  
**DEUTSCH, ESPANOL, ITALIANO — £15**

**PHILIPS NEW TYPE**  
**U/V HAND SET £10**

GLASS BEAMS Diodes 200/1, 2A  
 G11 Tip Switch £20.00  
 G11 HF Panel £8.00  
 G11 POWER PWR. £3.50  
 G9 Power Panel £3.50  
 G8 Push Button Unit £2.00  
 G8 Cam Panel New Back Type £4.00  
**50% OFF ALL G11 PANELS**

**MIXED**  
**TOSHIBA**  
**HAND SETS**  
**FIVE FOR £12**

**SECURITY FLASHING**  
**LIGHT WITH RED &**  
**AMBER LENSES &**  
**MAGNETIC FACILITIES**  
**£1.00 EACH**

**C-CAM INCODER**  
**PHILIP MADE FOR K40 CHASSIS**  
**IC No. TDA 3590**  
**£10.00**

**TELEPHONE EXT. LEAD**  
 3 Metre 30p  
**SCART TO SCART LEAD**  
 All Pin Long £2.50

Have you got Acid Rain in your garden? PH METER  
 Video Power Supply for Amstrad, Last year mod. £5.00  
 Mains Transformer for Amstrad Video £1.50  
 25p (£1 post)

**LA TEST VIDEO**  
 For Latest Philips, GEC, Pvc and Hitachi. Front panel with memory chip and bush button and pots and  
 LEDs £6.00 NEW

**FIDELITY NON TEXT HAND SET**  
 for 3000 chassis, 8 button  
**£5.00**

**TX90 MOD 37 4B**  
 The Sweep Tuning System  
 TX9139/001 £8.00

20AX GEC LOPT Panel with Split Diode £4.00  
 RANK 130 Focus Pot 75p  
 RANK 718 Focus Pot £1.00  
 16" LOPT Split Diode 2433481 £6.00  
 16" Panel Split Diodes 243287/243288 £5.00  
 Split Diode 2433752 £6.00  
 770A LOPT Transformer Rank with Focus Pots and  
 Diodes £2.00

**TX100 FRONT**  
**PANEL £5**  
**8 Button**

56420A 20A/600V THYRISTOR £1.75  
**HILL METER 6000**  
 Cost £35  
**£25**

**VIDEO SCART TO SCART**  
**ALL PIN. LONG LEAD**  
**£3.00**  
**TX90 TX95 TX100**  
 Mains Switch with Stand-by  
 and Lead 3 for £1 or 50p each

MAINS TRANSFORMER 240v to 230/230v £1.00  
**GREEN FLAT, NEC, LEDs** 3p each 100 for 12

100 OHM 20p Each  
 1 OHM 50p Each

**A M S T R A D**  
**VIDEO MAIN PANEL MODULATOR**  
**HF TUNER and ICs**  
**Damaged Panels £5.00**  
**Model A1 to A33**

**VIDEO SCART TO SCART**  
**ALL PIN. LONG LEAD**  
**£3.00**  
**TX90 TX95 TX100**  
 Mains Switch with Stand-by  
 and Lead 3 for £1 or 50p each

15W15V 1 Amp Print Type £1.00  
 12x12x2 8VA Print 17x7 75p  
 8x8 5V 1 Amp Print 75p  
 ET596 UHF V.C.P. Tuner, small £2.50  
 FIDELITY Panels with L.C. £5.00  
 FIDELITY LOPT Split Diode A1207680  
 A12076281 £5.00

SW 153 75p  
 SW 154 75p  
 SW 514 75p  
 SW 504 £1.00  
 SY 153 75p  
 SY 154 75p  
 SW 270 75p  
 SW 303 75p  
 SW 305 75p  
 SW 303 75p  
 SW 185A 75p  
 SW 505 75p  
 SW 146 75p  
 SW 453 75p  
 SW 174A 75p

**SALORA & LUXOR**  
**32 CH SATELLITE RECEIVERS**  
 No hand set  
**£30.00 post £5**

**BRIDGE RECTIFIERS**  
 10 FOR £1.00  
 4 Amp for Video Power Supply

MILLARD TEL. TEXT DECODER Type VM6113 £7.00  
**WE HAVE OVER 1,000 6 DIODE TRIPLER AT £1 EACH**  
 TX10 Sway button unit £8.00  
 THORN TX90 Remote chassis 14" Complete £12.00  
 PHILIPS VHS Tape 180 £2.25

TX90 TO TX100  
 8 BUTTON UNIT £4.00

**BRIDGE RECTIFIERS**  
 10 FOR £1.00  
 4 Amp for Video Power Supply

**BRIDGE RECTIFIERS**  
 10 FOR £1.00  
 4 Amp for Video Power Supply

2432984  
 2432971  
 2432901  
 2435016  
 2434952  
 2434993  
 2432311  
 19048A  
 1878R243  
 17830610  
 K41 O.P.T.  
 K35 L.O.P.T.  
 K40  
 TX9 L.O.P.T.  
 2432101-2

**SPLIT-DIODE**  
 2434752 £20  
 TX100 Green Spot £15.00  
 TX100 Blue Spot £15.00  
 TX100 Yellow Spot £15.00  
 1 O.P.T. £10.00  
 TX90 White Spot £10.00  
 1 O.P.T. £20.00  
 Split Diode 110 £12.50  
 Orion 65-3M  
 G11 C 85-9793-6

CTK, Lopt  
 S.W. Filters  
**L.O.P.T.**  
**SPLIT-DIODE**  
**PHILIPS**  
**£10 EACH**  
 TOSHIBA  
 DST 186N243 £10  
 TFB 4025AD £10  
 CP90 Philips Split  
 Diode £10.00

**TRANSFORMERS**  
 A1206601 £1.00  
 A12048/11 £1.00  
 A12085 £1.00  
 AT2076/35 £1.00  
 A12076/38 £1.00  
 A12076/51 £1.00  
 A12076/51 £1.00  
 CVC 300 £1.00  
 CVC 300 £1.00  
 AT2076/55 £1.00  
 A12076/71 £1.00  
 AT2089/5 £1.00  
 RC4351 CT3325 £1.00  
 OT2041 £1.00  
 FB105KA Orion £1.00  
 CVC 300 £1.00  
 CVC 300 £1.00  
 A1206601 £1.00  
 A12048/11 £1.00  
 A12085 £1.00  
 AT2076/35 £1.00  
 A12076/38 £1.00  
 A12076/51 £1.00  
 A12076/51 £1.00  
 CVC 300 £1.00  
 CVC 300 £1.00  
 AT2076/55 £1.00  
 A12076/71 £1.00  
 AT2089/5 £1.00  
 RC4351 CT3325 £1.00  
 OT2041 £1.00  
 FB105KA Orion £1.00  
 CVC 300 £1.00  
 CVC 300 £1.00

**SHARP**  
**MSH11C119**  
**£10**  
**EACH**

**BRIDGE RECTIFIERS**  
 10 FOR £1.00  
 4 Amp for Video Power Supply

**ITT TUNER CAN**  
 CNR 800/3 £20.00  
 Decca 1001 OPT Panel  
 and Frame £5.00

**BURGLAR**  
**ALARM**  
**£2.00**  
 with siren  
**9 VOLT**

SEND FOR LIST BRITISH MADE V.H.S. VIDEO HEADS from £8.20 to £60. SEND FOR PRICE LIST. V3HSS V, V3HSSV-L £8.20.

SEND FOR LIST OF VIDEO SPARES, VIDEO LEAD AND BELTS

12V/1 AMP POWER SUPPLY WITH MAINS PLUG £4

PHILIPS HALOGEN LIGHT. NEW. NO ON/OFF SWITCH. NO HANDLE WITH CORD. BLACK IN COLOUR £5

**ITT PANEL**  
 CMC 301 CMC 113 CMC 302  
 CMC 115 CMC 303 CMC 994  
 £5.00

**RELAYS 35p**  
**5V-12V-24V-48V**  
**Large and Small**

**PHILIPS HAND SET**  
**G11 TEXT ULTRASONIC £10**

**G11 TEXT IN RED**  
**HAND SET £12.50**

**G11 HAND SET**  
**ULTRASONIC £10**

**PHILIPS RC5**  
**EASY CONTROL £10**

**CMR 800**  
 Power Supply Switch Mode  
 £5.00

**BUZZER**  
**6 VOLT, Small**  
**10P EACH**

TRV3 Amstrad Cassette Mechanisms. New with 2 motors and sound head. £15.  
 TRV3 Power Supply. £5. Amstrad Television Tuner UHF. Small. Fits most Amstrads. £6.

**SENDZ COMPONENTS, 63 BISHOPSTEIGNTON, SHOEBURYNNESS, ESSEX SS3 8AF.**

**SAME DAY SERVICE**  
 All items subject to availability. No accounts. No Credit Cards. Postal Order/Cheque with order.  
 Add 17 1/2% VAT and VAT on Post.

Callers: To GEC at 212 LONDON ROAD, SOUTHEND. Tel. 0702-332992. Fax 0702 338805  
 Open 9-12/23-6. GVM1 + school orders accepted on official headings. Add 10% handling charge.

# SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

LA11440	£1.00	K35 Decoder	£8.00	Voltage Regulators	30p	CV 8617	10p	Philips Handset IC	£3.00
TA A7751	50p	K35 Sound OP	£4.00	+5V/7805	£3.00	Y 716	10p	SA A3010P	£3.00
HA 411485	£1.00	Thick Film Daughter KT3 3122-127-43891	£3.00	+6V/7806	£3.00	Y 729	30p	MAH8461/W063	£3.00
UIC 1373	50p	12 C.H. K30 Tex Rec Front Panel with I.C.	£5.00	LM 317T	30p	Y 730	10p		
MS5657P	£1.00	K35 IF	£5.00	LM 337	30p	Y 827 6A/1KV	10p	MAB 8420P-CY13	£3.00
N401BB1	£3.00	Plug In		LM 347/8	30p	Y 840	50p	MAB 8400B-6	£3.00
MS0441/50	£1.00	K4 Focus Pot	£1.00	LM 347/10	50p	Y 933	30p	MAB 8400P-D070	£3.00
MS5658P	£1.00	Fidelity Tube Base with transistor & focus pot	£1.50	+12V/1A 340T12	50p	Y 969	50p	MAB 8400P-D056	£3.00
Receiver TX100 Panel I.C. No. SA B035	£6.00	Bush Tube Base on panel	£1.00	+18V/1A 78M18	20p	Y 997	50p	MAB 8441P-1001	£3.00
—SA A1041		TX10 Tube Base on Panel	£3.00	+24V/78M24	£3.00	Min 12 volt Relays	75p	MAB 8441P-1132	£2.00
—IC8571P		1100 L.O.P.T. Green Spot		MC 7724p	40p	R 1038	40p		
New Model Philips Meter	£20.00	TX100 Thrm		MC 7824	40p	R 1039	40p	M58484P	£2.00
700 Hills Meter	£12.00	Line Transformers		Power Supply for Sincolor Spectrum +2	£5.00	R 2009	80p	Hand Sets — Fidelity	£15.00 to £35.00
4 Types Fidelity front panels with I.C. & pots	£2.00 each	G8 Lopt	£5.00	U 19885	40p	R 20106	£1.00	ITT 3 and 6 Push Button	£1.00
BB 103	10p	G9 Lopt	£4.00	U 3845	15p	R 2210	60p	1pc 731 LOPTs	£6.00
BB 105A x12	£1.00	6 Diode Tripler, Millard	75p	MR 508	10p	R 2257	60p	Thorn R500-R800 LOPTs	£5.00
BB 105B x12	£1.00	Line O.P. Trans. Mono T.A. 12" 14" Philips G8	£10.00	MR 501	10p	R 2265	50p	CNC 301 front panel	£5.00
BB 105C x12	£1.00	2745 Split Diode Leads IFT	£10.00	MR 502	10p	R 2306	30p	CNC 303 front panel	£5.00
BB 121a	10p	4822	£10.00	BCV 718	40p	R 2323	15p	CNC 302 Panel with TC minis switch etc	£5.00
47	10p each	10273	£10.00	BYE 1202	10p	R 2396	80p	CMD 800 Decoder	£8.00
1A1600V	10p	Thorn 1600 LOPT	£7.50	BYE 1204	10p	R 2433=BD124	30p	C7 Hand Set	£6.00
DG3P EQV-BY 228	10 for £1.00	2 J Pos 3.500 1 off each type	£3.00	BYF 3126	40p	R 2541	£2.00	A.C. Power Supply G11 Full Remote Receiver Panel	£3.00
2 amp bridge rec. wire end SK1-4G202	15p	G8 Trans. Philips	£7.00	BYF 3214	40p	R 2737	30p	Meters 11Bis 520	£17.00
Exp. BYX71/600 500ms.	15p	G11 Split Diode	£12.00	BYX 10	10p	R 2738=TI141	40p	Meters 11Bis 420	£20.00
9000 Frame panel	£8.00	CVC20 Split Diode IFT	£10.00	BYX 30600	35p	R 2775=TI141e	40p	11Bis 11D5000 Digital Meter 1000V DC	£20.00
9000 Cyclops panel	£1.50	Thorn B.W AD5308F + 50k + Lead	£1.50	BYX 49600R	75p	R 3129=TI147	50p	750AC 10 Amp 20 MRG Rungts	£28.00
3 Way regulated adaptor 240V/6V/7.5V/300mA	£3.50	GEC Portable G10T2041	£3.00	BYX 55350 (Head)	10p	T 688V	£1.00	11T100 Multimeter	£6.75
Rank/Toshiba prech unit 1034	£9.50	GEC Portable G10T2046	£3.00	BYX 71350	20p	S 2008b	80p	11T300 Multimeter	£7.75
4 Push button unit prech	£1.00	Rank 1, O.P.T. 2970	£1.50	BYX 71600	20p	2S1898B	£1.00	11T500 Multimeter	£9.00
6 Push button VHF/UHF for v.c.p. GEC-Decca type	£7.00	Pyc 169 Line Trans	£3.00	BYX 72300	20p	2S1942	£1.00	11T700	£15.00
7 Push button for CVC5 IFT	£8.00	Pyc mono	£3.00	BYW 2950	15p	Hitachi sets etc.	£2.00	11D400 Digital	£13.00
K13 12 Push button unit	£2.00	Rank mono T704A	£3.50	BYW 2950	15p	STR454	£2.00	11D2500	£18.00
K13 7 (1 sport) 12 P.B.U	£2.00	Split Diode Trans	£7.00	BZV 93675	54p	STR620	£1.00	11D3000 Digital	£25.00
6 Push button Unit-Thorn	£1.00	GEC 20 A.X. Rank Z522	£3.00	BZV 9518	30p	S 2000A/1 line o.p.	£1.00	11D5500 Digital	£29.00
6 Push button GRC	£6.00	Rank 1, O.P.T. 2970	£1.50	BZV 1530	30p	2S2940	£1.00	11D6000 Digital	£32.00
6 Push button PYE 731	£6.00	CVC600 Line Trans	£6.00	BZV 162w2	10p	BU 1105/44	80p	11D8000 Digital	£35.00
1 hearing aid unit	£3.00	CVC825 Split Diode	£10.00	BZV 79.3v	10p	BU 108	£1.00	11D9500 Digital with capacity Temp Trans Volt/Ohms and Amps ranges	£60.00
Rank Z7184 P/B Unit MEC11	£4.00	CVC 45	£5.00	BRIDGES	30p	BU 124	50p	Infra Red Handset Tester	£8.00
7 Push Button Unit	£6.00	GEC Portable G10T2046	£3.00	KBL005	30p	BU 136	80p	Works at 24 feet — Sound repeater. Works off 9 volt battery. Fits in top pocket.	£8.00
Z916B panel	£5.00	Rank 1, O.P.T. 2970	£1.50	KBL02	30p	BU 150a	80p	Handset Tester with LED	£4.50
Z913AD panel	£5.00	ITT CVC 5-8-9	£3.00	KBP04	30p	BU 180a	80p	Repaired Handsets	
TT14 GEC TEX-DECODER 13IC Panel with cable form	£9.50	Rank T25L1 Tripler	£2.50	W02	15p	BU 204	80p	Philips K4-K35, RC5350-RC5300, RC5370, RC5375, repaired same day	£10.00
PHILIPS Decoder SA4 IC S120-S130 S40B-S105	£8.00	Rank 11TCPC AR23	£3.50	W04	15p	BU 216	80p	RC4001 Full Remote KT3 K30 Teletext Handsets exchanged	£15.00
K40 Text Panel	£8.00	TU 25 30K Rank	£3.00	W04	15p	BU 206	£1.00	GEC Full Remote Infra-red, 1983 models	£15.00
OF-425	50p	G9 Phinix	£3.00	800V Bridges 2/2 Amp	20p	BU 207	£1.00	TOSHIBA HAND SETS	
OF-555	50p	G11 Phinix	£4.00	G11 Drawer ASS 3 pots Mains Switch and Lead	£2.00	BU 208	80p	CT9185 CT9176 CT9133 CT9188	£4.00 each
OF-513	50p	GEC 2110	£4.00	K30 Drawer Ass with pots cable form	£1.00	BU 208A	75p	CT9195 CT9144 CT9185 CT9193	£4.00 each
OF-557	50p	3500 Thorn	£3.00	TX10 Drawer with 8 way pots. ass	£2.50	BU 208D	90p	Rediffusion MK3	£5.00
KT3-K30	50p	8500 Thorn	£4.00	Hills 9 piece tool kit in case	£5.00	BU 222	£1.00	TOSHIBA HAND SETS	
DIODES	40p	9000 Thorn	£4.00	Philips Coaxial Cable Stripper SHC325	£7.50	BU 326	80p	24 Button CT928C Infra-remote	£5.00
BY 126	10p	9500 Thorn	£4.50	Self adjusting cutter-stripper	£5.00	BU 407	80p	32 Button CT983 Videotext	£6.00
BY 127	10p	9640 Thorn	£4.50	10 mixed tube bars	£4.00	BU 426A	80p	VCR Front Display Panel	£7.00
BY 133	10p	2040 GEC	£3.50	5000 Diodes-Resistors	£3.00 pack	BU 455	80p	Large type ITT TV and V.C.R. Handset	£15.00
BY 134	10p	GEC TVM25 Tripler	£2.00	10P push minis switch	20p each	BU 455	80p	GEC Ultrasonic RC11 Full Remote	£10.00
BY 170	25p	Universal Tripler	£5.00	Mains lead & Iax pin socket for radio cassette	35p	BU 455	80p	G11 Full Remote Ultrasonic	£10.00
BY 176	25p	OR Tripler	£5.00	T.V. loop aerial	75p	BU 455	80p	G11 Ultrasonic Teletext Handset	£10.00
BY 184	25p	CVC 3E-32	£5.00	Radio Telescope Aerial	£1.00	BU 455	80p	G11 Ultrasonic GEC Full Remote	£15.00
BY 187	10p	Decca 80 100	£4.50	Philips Silicon Grease	£1.50 each	BU 455	80p	New Replacement for G11 Ultrasonic Full Remote	£12.00
BY 190	10p	Ground 1VK 52	£3.00	Freeze Philips	£1.50 each	BU 455	80p	Thorn 4000 insert with 7 buttons	£5.00
BY 196	10p	111BQ Pyc 731	£3.00	Foam Cleaner Philips	£1.50 each	BU 455	80p	Decca RC 11	£14.00
BY 179	25p	11T1V	£4.00	Contact Cleaner Philips	£1.50 each	BU 455	80p	Decca RC 12	£14.00
BY 184	25p	D22 for Pyc IC colour portable	£4.00	100 Coax Plugs	£ACT11 14p	BU 455	80p	ITT Infra-red full teletext	£20.00
BY 190	10p	I.P. 119363	£4.00	Desolder pump + 2 nozzles Philips	£4.00	BU 455	80p	Dynatron-Full remote CT11 62, 63, 64	£19.00
BY 196	10p	RG 10051	£3.25	Flat Red LED and Green	5p	BU 455	80p	Hitachi infra red handset	£18.00
BY 204/4	8p	ERG Tripler print type with focus POT	£5.00	500gm 60/40 Solder reel	£6.00	BU 455	80p	Philips full remote K73, 160 9280/934, 7228/7324, K12 26C 797/157/66K, 1826	£12.00
BY 206 — BY 407 Eqp.	8p	12-14V. 200 for £5.00 200 for £25.00	£14.00	Dual v/u meter — 20 — 10kV	£1.00	BU 455	80p	GEC infra red full remote 8 channel (I.C.S.AA1250)	£14.00
BY 208/801	8p	GEC 8 touch unit assy complete with all I.C.'s + pots	£4.00	K30 Thermistor 232266298019	75p	BU 455	80p	Philips infra red full remote 9 channel for 60 CT2605	£6.00
BY 210/401	5p	G11 E.W. Transformer	50p	Desolder Pump	£2.50	BU 455	80p	Philips infra red full remote 12 channel for 60 CT2605	£12.00
BY 210/801	5p	G11 E.W. coils	£1.00	Portasol Flameless Gas Soldering Iron	£C16.00	BU 455	80p	RC5 35	£12.00
BY 214/4	8p	G11 Transient Suppressors 245V	20p	Green and Red LED pack mixed	100 for £1.00	BU 455	80p	No RC5150-RC5176-RC5171-RC5177	£13.00
BY 216	10p	G11 Scan Coils	£5.00	Hill Meter Leads, S/Rubber and Probes	£4.00	BU 455	80p	Special Price	£13.00
BY 216	10p	G11 100K tuner pots	12 for £1.00	International Rectifier UHT Diodes G77/HHV34 6KV	3 for 8p	BU 455	80p	RC4001, K73 and Teletex	£14.00
BY 219	10p	KT3 line OSC transformer	£1.90	6A/1000V Stud Diodes	20p	BU 455	80p	ITT CVC 32 handset repaired	£15.00
BY 220/401	8p	K13 K30 infra-red receiver head	£1.00	25A/473 PNP C/P	10p	BU 455	80p	CVC 32 Hand Set	£15.00
BY 220/801	5p	K30 drawer unit with IC's (home)	£10.00			BU 455	80p	CVC 45 3 and 2 Pin	£12.50
BY 220/801	5p	K30 drawer unit with IC's (portable)	£10.00			BU 455	80p	TX10 Hand Set Text	£12.50
BY 226	15p	KT3 AE Sockets	50p			BU 455	80p	TX9 & TX10 button print	£2.00
BY 227	15p	KT3 receiver panel	£8.00			BU 455	80p	TX10 Focus Pots	£5.50
BY 228 1500V	15p	KT3 line driver transformer	50p			BU 455	80p	ITT	
Flat BY 229 black	20p	Pyc. K30, GEC, etc. Pre-mains stand-by switch	£1.00			BU 455	80p	TV & Video Processor, 1200 Type	£10.00
BY 229 Red	20p	Decca 80/101 II panel	£5.00			BU 455	80p	PHILIPS UNIVERSAL HAND SET £12.00 RC5 KT3 — K45	
BY 229/401	30p	NPN PNP 81V 6 Amp TO66 O.P.	pair 25p			BU 455	80p	We have all parts for Philips Handsets	
BY 229/601 Tag	30p	Trans. pair 25p				BU 455	80p	RC5353	£15.00
BY 237	5p	700ms touch tuner BBC1/2 ITV/1/2 video with 500k 500k 500k	£7.00			BU 455	80p	RC5800	£12.00
BY 254	10p	Control panel 5 sliders + mains lead 4.5	£1.50			BU 455	80p	Philips RC5	£15.00
BY 296	10p	G11 8 touch button unit replaces old 6 P.B.U.	£24.00			BU 455	80p	TEXT-TYPE Replace Hand Set for Philips KT3-K30, K4 etc	£12.30
BY 299	8p	Tube base + base unit for R20 Euro chassis	£4.00			BU 455	80p	THORN HAND SETS 9000, 9600, TX9 — TX10 — TX100 Text and Non-Text	£10.00
BY 306	8p	GEC Line O/P Trans. & Rec Stick for Portable	£3.00			BU 455	80p	PHILIPS RC5171	£12.00
BY 307	8p	CVC 20/25 30/35/40 decoder panel	£10.00			BU 455	80p	K35-K4 HAND SET Repaired for £5.00	
BY 308	8p	CVC 20/25 30/35/40 decoder panel (untested)	£5.00			BU 455	80p		
BY 309	8p	CVC 40/45 IF panel	£5.00			BU 455	80p		
BY 327	10p	40K Transducer	50p			BU 455	80p		
BY 602	10p	PHILIPS NE511N	£1.20			BU 455	80p		
BYV 26C	10p	LM337M Reg.	30p			BU 455	80p		
G247	10p	20 GEC Black Spark Gaps	£1.00			BU 455	80p		
GP20G	5p	KT3 Front Panel Control Assy.	£2.50			BU 455	80p		
GR180G (TX10)	5p	BTW 2050	50p			BU 455	80p		
NK 3102	20p					BU 455	80p		
BYV 26/200	20p					BU 455	80p		
Bridge TX10 800/3 amps	30p					BU 455	80p		
KBFC35-02 Bridge	£1.50					BU 455	80p		
Bridge Rec. D35B11	40p					BU 455	80p		

# SENDZ COMPONENTS

63 Bishopstelgton,  
Shoeburyness, ESSEX SS3 8AF.  
S.A.M.E DAY SERVICE

All items subject to availability. Technical information by telephone only. No accounts: No Credit Cards  
Postal Order/Cheque with order  
Add 17% VAT, VAT on post  
Add Postage for overseas.  
Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992. Fax 0702 338805  
Open 9-12.30.6. GVMT - school orders accepted on official headings. Add 10% handling charge.

TUNER UNITS	
TX90/TX100 Tuners with AE socket	£5.00
Thorn TX Tuner V/Cap cap. to ELC1043	£4.50
Min. UHF Tuner 40dB gain	£1.50
AMSTRAD Tuner	£1.50
Thorn TX10 Export V/Cap UHF	£3.00
VHF	£3.00
V Cap Rank UHF Z7767/Unit	£6.00
V Cap Rank VHF Z7731/Unit	£5.00
NF-W G8 Tuner V Cap	£5.50
E306 Fish Boat Unit	£7.00
E.C.2000 Panel	£2.50
GLC 2100 V Cap	£3.00
ELC1043 (Ex Panel)	£3.75
ELC2000	NEW £4.00
ELC2003	£4.00
GLC Tuner V/Cap Hitachi After	£8.00
1979 ET588, ET537, ET541B	£6.00
E1546	£6.00
Moulton Astec UM1233	50p
UL33-101 Amstrad UHF Tuner	£5.00
VHF/UHF EG522F	£6.00
ASTEC UM183	£10.00
V314 (VHF)	£5.00
V334	£4.00
U321	£6.00
U322	£8.00
U341 UHF	£6.00
U342 (UHF)	£5.00
U343 (Phone)	£5.00
U344C	£6.00
U344C	£10.00
U411 UHF	£4.00
UVE10	£8.00
U.V. 411 Tuner	£8.00
U.V. 412	£8.00
U.V. 417	£8.00
U.V. 617	£6.00
UHF/VHF Tuner 1301DK0	£5.00
U743 Tuner	£7.00
Ficklen/Amstrad 2000 V/Cap Tuner	£5.00
Small V/Cap Mitsumi	£4.00
UHF	£3.00
VHF	£3.00
VHF & UHF ET588P Tuner	£6.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
Mosin UHF/VHF (new type)	£8.00
UL33-101 Ficklen V/Cap Panel	£6.00
UHF-VHF V-Cap on panel	£3.00
HFAACH 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videon	£2.50
MFS 900	£2.50
Multiband Video Modulator. Application: video tapes, recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied	£10.00
4 Rotation Rank Z18 Tuner	£4.00
TSS 250. AC means filter (L1=0.02µF) inductor & earth clip	25p
NEW U321 Multiband	£4.50

Astec UM1623 VHF	£2.00
Astec UM1286	£4.00
VHF/UHF Tuner S Band	£3.00
UHF/VHF Tuner EGG13F	£6.00
ENV-5765G2 VHF/UHF	£5.00

Change over switch co-ax type box with lead 50p

TX90MOD 37141B	£8.00
The Sweep Tuning System	
TX9 139/101	

Delay Lines	
DI 700	£1.00
KT 3 Luminance	75p
Luminance Delay Line (CVC45)	
Co-Ax Joint	15p
Co-Ax Belling Lee Plug	14p
Co-Ax Splitter	£1.00
Infra Red Emitting Diode	20p
NE28611 Small Neon Lamps	
Geac & Philips	5p
Mullard 5 Watt Amps. LPI162	
New	75p

S.W. Filters		S.W. Filters	
HW2011	50p	SW1R5	£1.00
HW2013	50p	SW153A	50p
SW453	50p	SW154	50p
SW151	£1.00	SW173	50p
HW2013	50p	SW173	50p
RW303	50p	F1035B	50p
SY2153	50p	F1045A	50p

BD646	50p
BD676A	40p
BD817	20p
BD826	50p
BD933	40p
BD939	40p
BD948	40p
BD131A	50p
BD175	20p
BDV64B	50p
BDU65	50p
BF761	40p
BF769	40p
BF788	20p
BF819A	30p
BF858	30p
BF869	30p
BF871	30p
BF852	7p
BF851	15p
BF860	10p
BF142	20p
BF157	40p
BFW11	40p
BFXNS 100V. Lamp	30p
BS1215	50p
BS136	£4.00
AN6350	£2.00
BRC-M-200	40p
BRC-M-300	50p
NE28611 Small Neon Lamps	£1.00
BRC 3064	£1.00
BTT822	£1.00
BTT8016	£1.20
BTT9018/ML237B	£1.50
BTT9218	£1.50
BTT9124	£1.00
BTT9224	£1.00
BTT922A	£1.00
CA2701A	50p
CA2702W	50p
CA2702C	50p
CA2801A	£1.00
CA1310	50p
CA3046	50p
CA3065D	50p
CA3084AE	50p
CA3123	50p
CA3146	£1.00
CA3189	40p
CF6648	30p
CD4510	30p
CD4510B	30p
CD4555BE	30p
DM1792	50p
HA1112A	50p
HA1196	40p
HA1377	£2.00
HA11223	£1.00
HA1320	£1.00
HA11440	50p
HA11484	£3.00
HA11485 Ant	£1.00
HA17458	50p
HEF4001	50p
HEF4519H	25p
HEF4011A F	50p
HEF4053B	50p
HEF4063P	20p
HEF4527	£1.00
HEF4528	£1.00
HEF4590C	£3.00
K5731D 1001012	£1.00
LA3220	50p
LA4102	£1.00
LA4261	£1.00
LA7830	£2.00
LA7831	£2.00
LM1111N	£1.00
LM1017N	£1.00
LM8361	£3.00
PCF8571P	£5.00
6913	£2.00
M1024-SAA	£2.00
M1025-SAA	£2.00
M5841A-84RS	£3.00
MC1748	80p
MC1347	75p
MC1312	25p
MC1331 GN76530	£1.00
MC1332	£1.00
MC1338	£1.00
MC1496	25p
MC14002	15p
MC1401	25p
MC14016	25p
MC14066	30p
MC14514	50p
MC1748	80p
NEM4956	£1.00
ML231	£2.50
ET16016	£2.00
ML232	£1.00
ML236E	£1.00
ML237B	£1.00
ML238A	£4.00
ML239	£2.00

MA18400B-C	£1.00
MA18400C	£2.00
MA18441 P/DH0	£2.00
MA18441 PTH0	£3.00
MA18420PCU35	£2.00
MA18422P-C0015	£2.00
MA18440P	£2.00
MA18400X	£3.00
M08181	£2.00
MMS587	£1.00
MMS611	£1.00
MMS840	£3.00
PCD8571P	£3.00
K35 Philips Receiver IC	£3.00
MA1250BJC	£3.00
MA18181	£3.00
M58401-84RS	£5.00
MMS200N-4	75p
MMS3188N	£4.00
MN650	£1.00
MN1250BJC	£2.00
MN1366	25p
N6110	£1.00
NI 555P	60p
NI 555	60p
NE555C	60p
NE646	50p
HDW8981C	£3.00
HE4011	20p
OPT601	20p
PI2369	10p
PCD8571P	£2.00
PCD8572P	£2.00
SAA661	£1.00
SAA1021	£4.00
SAA1073	£2.50
SAA1074	£3.00
SAA1075	£3.00
UPD48491C	£2.00
SN2848	£2.50
SN297018N	£2.00
SN297118N	£2.00
SN297218N	£2.00
SN74011	£1.00
SN740318D	£1.00
SN74118N	£1.00
SN7615AN	£1.00
SN76131	50p
SN76141N	£1.00
SN76151	£1.00
SAB3037	£2.00
SAB3038	£2.00
SAB3205	£2.00
SAB3206	£2.00
SAB3207	£2.00
TBO0124	£1.00
SAA3008P	£3.00
SAA3010	£2.00
SAA3012A	£5.00
SAA3016	£3.00
SAA3021D	£3.00
SAA3040	£2.00
SAA3041A	£3.00
SAA3043	£3.00
SAA3045	£2.50
SAA3046	£2.50
SAA3047	£2.50
SAA3200	£2.50

Thyristors	
Philips Kns OT21	50p
IR180A	50p
IR15180	50p
BT106 Plastic	1.20
BT106 Metal	1.20
BT119	75p
BRC3443	75p
RC1 Thyristor	60p
Deco 40-100	£1.00
3N444	£1.00
MC827-6	25p
BT112	£1.00
TF33M	£1.00
HC441	£2.00
7852	£2.00
78581	£2.00
78582	£2.00
78583	£2.00
92PM	£2.00
RCA Line Thyristor	£2.00
CC2001	£2.00
CC2002	£2.00

Thermistors	
PT18BGNIM	75p
CS Degausing	15p
Philips Type V1114	30p
ITT236312	2