

Practical Wireless, January 6th, 1934.

THE LUCERNE WAVE PLAN EXPLAINED!

Practical Wireless

3^d

Published every Wednesday by


**GEORGE
NEWNES
LTD.**

Vol. 3.—No. 68.
JANUARY 6th, 1934.

Registered at the G.P.O. as a Newspaper

EDITED BY F.J. CAMM.

Making the **PORTOMISOR**

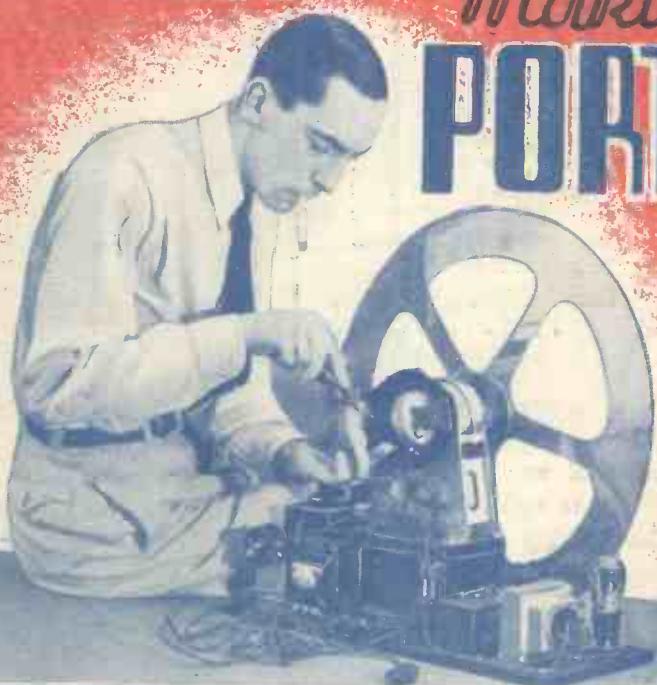

The First PORTABLE
TELEVISION RECEIVER

SEE OUR ADVERTISEMENT ON PAGES III AND V
OF TELEVISION SUPPLEMENT

Peto-Scott FOR ALL Television

PETO-SCOTT CO. LTD. 77 City Road, London, E.C.1

ADVT


"I was amazed... station after station rolled in..."

The original of this letter may
be inspected at our Head
Office, Cossor House,
Highbury Grove, London, N.5.

Dear Sirs,

I am using a well-known Set which is noted for the way it brings in stations. I recently borrowed a Cossor Metallised Screened Grid Valve to try. I first tried three other makes of S.G. Valves and there was not much difference between them. Then I tried the Cossor. I was amazed—station after station rolled in. I set the dials to a certain station, took out the Cossor and tried the other S.G. Valves, result—flat nothing—only a whisper. I put back the Cossor and without touching the dials the Set was roaring the place down. You cannot give a better test than this.

Yours faithfully,
Signed

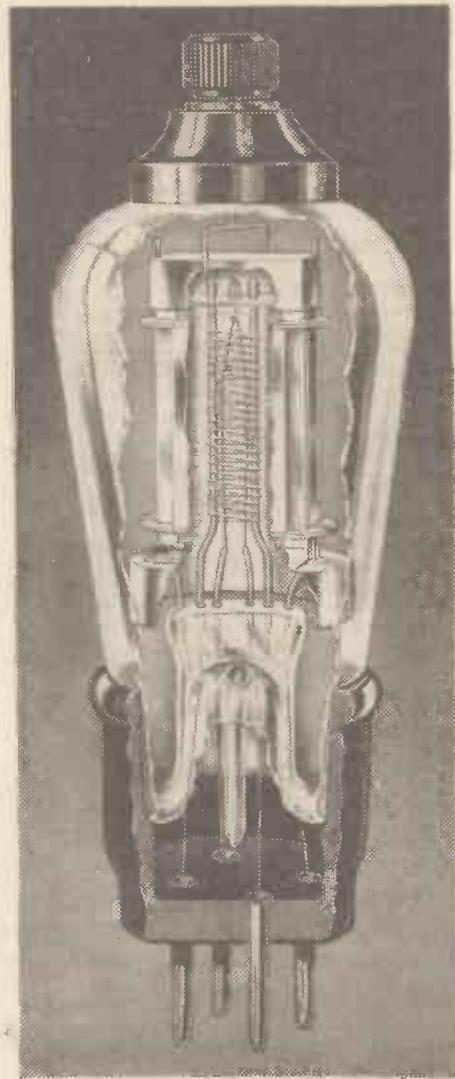

THE simplest and most economical way to increase the efficiency of your Receiver is to replace your old Screened Grid Valves with Cossor. The right type of Cossor Screened Valve will make your Set like new again—restore its vigour. Thousands of Wireless Users are rejuvenating their Sets with Cossor—Britain's most efficient Screened Grid Valves. You should too.



To A. C. COSSOR, LTD., Melody Department, Highbury Grove, London, N.5.

Please send me, free of charge, a copy of the Cossor 72-page Wireless Book B.V. 33.

Name.....

Address.....

PRAC. 61 94.

COSSOR SCREENED GRID VALVES

A. C. COSSOR LTD., Highbury Grove, London,
N.S. Depots at Birmingham, Bristol, Glasgow,
Leeds, Liverpool, Manchester, Newcastle, Sheffield,
Belfast, Cardiff and Dublin.

4300

INSIDE ! BUILDING THE NUCLEON CLASS B FOUR

Practical Wireless

EDITOR:
Vol. III. No. 68 || F. J. CAMM || Jan. 6th, 1934.
Technical Staff:
W. J. Delaney,
H. J. Barton Chapple, Wh.Sch., B.Sc. (Mons.), A.M.I.E.E.,
Frank Preston, F.R.A., W. B. Richardson.



ROUND the WORLD of WIRELESS

The Lucerne Plan

IT has previously been announced in these columns that the new "Lucerne Plan" would come into operation on January 18th, and many readers have written to ask in what way this would affect them. Briefly, it can be stated that the wavelength changes will have only a very slight effect upon the listening public, and that reception will be no more difficult than before. As a matter of fact, the modified wavelengths will, in nearly every case, simplify the selectivity problem, but so that every reader may have a thorough understanding of the new position which will be created we have had prepared a special article on this subject. The article appears on page 781 of this issue, and, since it has been written at the last moment, it is right up-to-the-minute, including even those wavelength adjustments which have been called for at the very last moment. This article gives further proof of our policy of keeping all readers well abreast of the latest developments.

Television is Hero

THERE are still a few sceptics who claim that television is not popular, and even that it cannot be so until vast changes have taken place in regard to the method of transmission and reception of light. These sceptics are generally of the "Micawber" type who are "always waiting for something to turn up" instead of helping in the development of new sciences. Whilst such people are dreaming, PRACTICAL WIRELESS is acting, and all readers will welcome the essentially-practical constructional article in this issue which tells you how to make a really efficient portable television receiver. This new piece of apparatus is easy to make, and by no means costly, so that there is no reason why every PRACTICAL WIRELESS reader should not proceed at once to enjoy to the full the many television broadcasts which are now made by the B.B.C. It is a true fact that the present television broadcasts are of distinct entertainment value, and any intelligent person who has lately "looked-in" with an efficient receiver such as the "Portovisor" will not dispute this fact.

The "Portovisor" is the *very first portable television receiver to be offered to the home constructor* and it marks a really definite forward step in modern television technique — yet another proof that "PRACTICAL WIRELESS" ALWAYS LEADS !

New KDKA Broadcast Feature

IN addition to the special transmissions made for the benefit of trappers, police, and other inhabitants of the Polar circle, the KDKA and W8XK stations of East Pittsburgh broadcast on every fourth Sunday of the month a brief sacred service and special messages to foreign missions

the same districts. When reference is made to them they are to be known as follows: Toulouse-Muret, Lyon-Tramoyes, Nice-La Brague, Paris-Villejuiste, Lille-Camphin, Marseille-Realtor, and Rennes-Thouries. Their power varies between 60 and 100 kilowatts.

Germany Nearing Five Million Listeners

IN the course of November, 202,000 new registered licences were taken out in Germany, thus bringing up the total to 4,837,539. It is hoped that the five million mark may be reached by the New Year. To beat England's figures Germany still has a long way to go, as we are over one million ahead.

Wireless in Taxis

IN the United States, whence the idea originated, some two thousand taxi-cabs which were equipped with wireless sets for the entertainment of both driver and passengers were ordered by the police to remove the apparatus or to have their licences revoked. The decision was taken following an accident in which a man was knocked down and seriously injured. The New York authorities, in taking their decision, stated that in addition to distracting the attention of the drivers, radio broadcasts in such vehicles would increase street noises to the extent of making the taxicabs a public nuisance. Although they had become popular with the general public, the disadvantages of the innovation far outweighed its benefits.

More Powerful Broadcasts from U.S.A.

A RECENT decision taken by the American Radio Commission permits three of the most important U.S.A. stations to increase their power to 50 kilowatts. In these circumstances it is expected that the range of WGN, Chicago (416.7 m.), WBZ, Boston (303 m.) and WHAM, Rochester, New York (260.9 m.), will be greatly extended, and their broadcasts should be picked up more easily in the British Isles. It is anticipated that a similar licence may be given to them. They are: WMAQ, Chicago (447.8 m.); WHAS, Louisville (365.9 m.); KNX, Hollywood (285.7 m.); and WBT, Charlotte (277.8 m.).

INSIDE ! No. 2 OF "PRACTICAL TELEVISION"

MAKING A PORTABLE TELEVISION RECEIVER

AMATEUR TELEVISION IS HERE !

throughout the world. This is carried out on the lines adopted by the Vatican station at Rome, except for the fact that the transmissions in this instance are destined to Baptist, Methodist, and Presbyterian denominations. The broadcasts may be picked up in the British Isles at G.M.T. 04.30 (Mondays) on 308 metres (KDKA) and 48.86 metres (W8XK).

France's High-Power Stations

THE seven high-power transmitters which the French State System is erecting have now been given official names in order to distinguish them from other private stations which are operating in

ROUND the WORLD of WIRELESS (Continued)

Eko Bakelite Factory

AT the bakelite plant at the Eko works, fourteen hydraulic presses are in operation at the present time, including one 1,500-ton and two 1,100-ton machines. Each of these presses weighs over 100 tons, and stands 35ft. high from its base. This base is situated in vaults below the main floor of the plant. Nearly 2,000 tons of concrete were used in preparing the foundations, which are sunk 13½ ft. into the ground. The hinged dies used for moulding cabinets weigh over 5 tons each, except on the 1,500-ton press, where the die weighs 15 tons. Two cabinets are produced simultaneously by this machine. The electricity consumed by the power plant amounts to nearly 10,000 units a day, or three and a half millions a year. Movement of an electrically worked lever plunges the upper die into the mould. A specially prepared sand-glass is used for timing, in preference to a clock or other mechanical device.

When the die is released, the cabinet is lifted out of the mould. Mortised screw sockets and metal inserts are firmly moulded in place, and the only operation needed to complete the cabinet is to break off a thin "flesh" of bakelite, and to give the edges a slight polish.

Concerts of British Music

IN addition to the seven new works to be introduced at the Six Concerts of British Music to be held in Queen's Hall, under the auspices of the B.B.C., some fifteen or so major works already well-known to the public are included in the programmes. On January 1st Delius's *A Song of the High Hills*, for chorus and orchestra, will be given, as well as Constant Lambert's *The Rio Grande*, for solo piano, chorus, and orchestra. The former is one of Delius's most beautiful works, and "is full of a sense of spacious solitudes and far horizons." Few contemporary works have won such wide popular approval as Lambert's *The Rio Grande*, which is undoubtedly one of the most successful attempts yet made to apply the rhythmic idiom of modern dance music to a serious symphonic work.

January 5th brings Arthur Bliss's *A Colour Symphony*, a work of outstanding merit deriving "its name from the fanciful attachment of a colour to each of the four movements." Another important work is Eric Fogg's Bassoon Concerto which is dedicated to Archie Camden, the renowned principal bassoon of the B.B.C. Orchestra, who is to be the soloist on this occasion.


Revue Fare from Birmingham

ON January 12th, listeners will hear on the Midland wavelength both a play and a revue. The play is Philip Johnson's one-act comedy, *To-day's the Day*, and it will be given by the Birmingham Repertory Theatre Company from the specially equipped studio at this theatre. The revue, a Martyn Webster production, is entitled *Hold That*, and represents an hour in a film studio. The book and lyrics are by Michael Barringer, author of many scenarios, and the music by Reginald

INTERESTING and TOPICAL PARAGRAPHS

Bristoe, who has also written many compositions for the films. Alma Vane and Hugh Morton will be in the cast.

THE POWER OF THE PRESS!

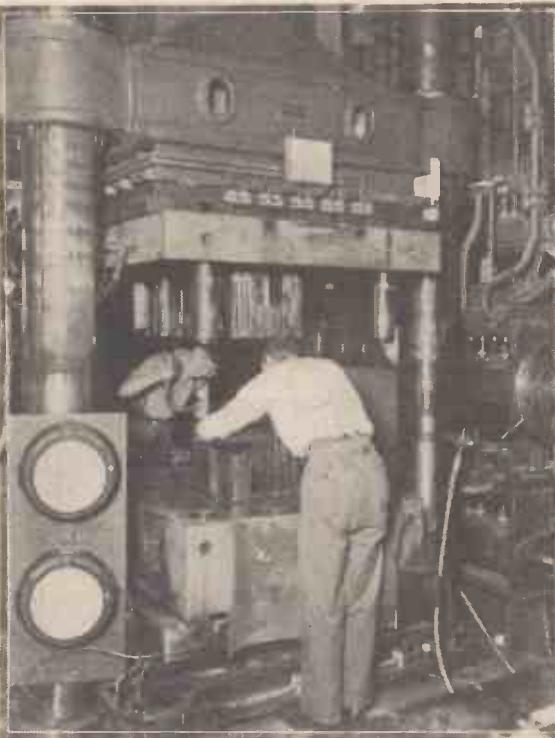

How bakelite is moulded at the Eko Factory. (See the paragraph on this page.) This press produces two Model 74 Cabinets at one stroke.

SOLVE THIS!

Problem No. 68

Jenkinson made up a mains receiver employing an S.G. H.F. stage, detector and L.F. stages. When tested results were very poor, and he accordingly connected a milliammeter in the anode circuit of each valve in turn. The detector and output stages were quite in order, but the H.F. valve showed no anode current at all. The H.F. choke was tested and found continuous, and an H.T. reading could be obtained between the anode and the earth line. All connections to the valve-holder were found to be soundly made and the valve was tested and found up to standard. What was wrong? Three books will be awarded for the first three correct solutions opened. Address your attempts to The Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., 4-11, Southampton Street, Strand, London, W.C.2. Envelopes should be marked Problem No. 68, and posted to reach here not later than January 8th.

SOLUTION TO PROBLEM No. 67

In joining the grid leak to the first valve, Jones overlooked the fact that a condenser was also needed in order to avoid short-circuiting the grid-bias control. It should have been joined between the grid and the top end of the coil.

The following three readers successfully solved Problem No. 66, and books have accordingly been forwarded to them:

K. Goldsmith, 47, Sycamore Grove, Southend, Essex. J. J. Keegan, 7, Hilton Street, Salford 5, Lancs. H. Jones, 67, Treborne Road, Caerau, Bridgend, Glam.

Musical Comedy Excerpts

THE name of David Wilson (baritone) has become synonymous with the Belfast station's programmes of musical comedy excerpts. He will make another appearance before the microphone on January 8th, in a programme of this type.

It includes excerpts from *The Desert Song*, *The Maid of the Mountains*, and *The Lady of the Rose*.

Aladdin

THE first relay from the Opera House, Belfast, comes into the programmes on January 9th, when an excerpt from the pantomime *Aladdin* will be heard by Belfast listeners. This is the thirty-ninth annual pantomime which has been performed in this theatre, and a long list of "stars" has been assembled for it.

Missing Links

A COMEDY in three scenes by Charles K. Ayre, *Missing Links*, will be heard by Northern Ireland listeners on January 12th. Charles K. Ayre is one of the most popular of the Ulster playwrights, and a number of his plays have been broadcast, including *Loaves and Fishes* and *The Wee Moiley Cow*. *Missing Links* is a witty story of golf and science intermingled.

Military Band Concerts

THERE are two band programmes from the Midland Regional studio during the week—one by the Creswell Colliery Band, conducted by David Aspinall, on January 9th, and the other by the Birmingham Military Band, conducted by Wf. Arthur Clarke, on the 11th. Interludes in the two programmes are occupied respectively by Patricia Rossborough (syncopated pianisms) and Harold Pollard (entertainer).


Interesting Talks from Midland Regional

TWO talks of special interest to the Midland coalfields will be given in the week's Midland Regional programmes. On January 8th, Robert Tredinnick interviews a Midland miner for the Boyhood in Industry series, and on January 10th Professor K. Neville Moss, of the University of Birmingham, gives a talk on the development of mining in the region during the past century. Professor Moss had several years of practical experience in Staffordshire coalfields before coming to Birmingham University.

Television in Italy

ENGINEERS of the E.I.A.R., the Corporation responsible for the broadcasting system, have installed the first Italian television transmitting and receiving station at the Palace of Electricity at Turin. Broadcasts will be made on short waves, namely, between 5 and 8 metres, and will consist of relays of topical events, public performances from theatres, and scenes from streets. A regular service will not be started until a similar station has been completed at Rome; it is being built for the transmission of sound films on 180 lines and 25 images.

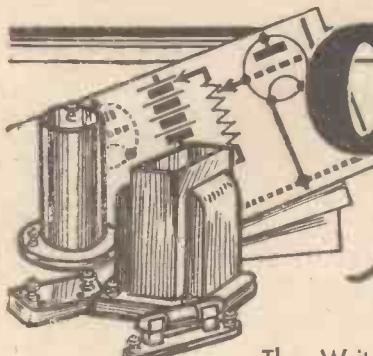**CLAIM YOUR TOOL KIT
WITHOUT FURTHER DELAY!**



Old Components in New Circuits

The Writer Explains in this Article How Many of the Newer Circuit Arrangements Can Be Tested by Using Old Components in Various Ways.

By BERNARD DUNN

ANY enthusiast who does a fair amount of experimenting collects so much surplus gear that there is some difficulty in knowing how best to dispose of it. Many of the parts could be used to make up an obsolete set, but that would not interest the keen experimenter in the least. The difficulty is that most of the newer circuit arrangements entail the use of new components of special design and

which tuning is carried out by means of a more up-to-date dual-range tuner. It will be seen that the wire which previously joined the aerial terminal to the aerial tuning coil has been removed and another wire taken from the aerial terminal to one end of a second coil, across which is connected another .0005 mfd. tuning condenser. A connection is taken from the "top" end of each coil to the "fixed plate" terminals of a differential condenser, which may be of any capacity between .0001 and .0003 mfd.; the centre terminal of the condenser (moving plates) is not used. The arrangement shown and de-

scribes is that of "top-capacity" band-pass tuning, the differential condenser providing the small capacity coupling. This condenser behaves like two small variable condensers connected in series, with a result that the actual capacity in circuit is only a few microfarads. Capacity is at a maximum when the moving plates are half in mesh with the two sets of fixed ones, and can be reduced almost to zero by fully meshing the moving plates with either set of fixed ones. This method of tuning not only

increases selectivity, but makes the degree of selectivity easily variable. Thus the circuits tune most sharply when the capacity is at a minimum, and vice versa. In trying the band-pass system described the new and old coils (or tuners, as the case may be) should be arranged with their axes at right angles, or else they should be screened from each other. If the two coils are identical the settings of the variable condensers will be practically the same for any particular wavelength, but in any case both condensers should be tuned accurately and with care. The simplest way to tune to any station is first of all to set the capacity of the differential to its maximum and find the rough tuning positions; after that the capacity can gradually be reduced and the condensers finely adjusted at the same time.

A.V.C. with a Spare Valve

Every experimenter wants to try automatic volume control, but it is not everyone who feels prepared to buy special apparatus until the efficacy of the scheme has been verified. Provided that a spare valve (of practically any type) as well as two high-tension batteries (which need not be in new condition) and a few odd resistances and condensers are on hand, an excellent form of A.V.C. can be tried out by using the connections given in Fig. 2. The drawing shows that a lead is taken from the "top" end of the detector H.F. choke to the positive socket of the 60-volt G.B. battery, whilst a 50,000 ohm potentiometer is connected between two tappings on the same battery, its slider being joined to the grid of the A.V.C. valve. Low tension for the A.V.C. valve is taken from the common source, but high tension and grid bias are obtained from the new batteries already mentioned. It will be seen that the negative lead from the H.T. battery is taken to the filament of the A.V.C. valve through a .25 megohm resistance, and it is across this that the

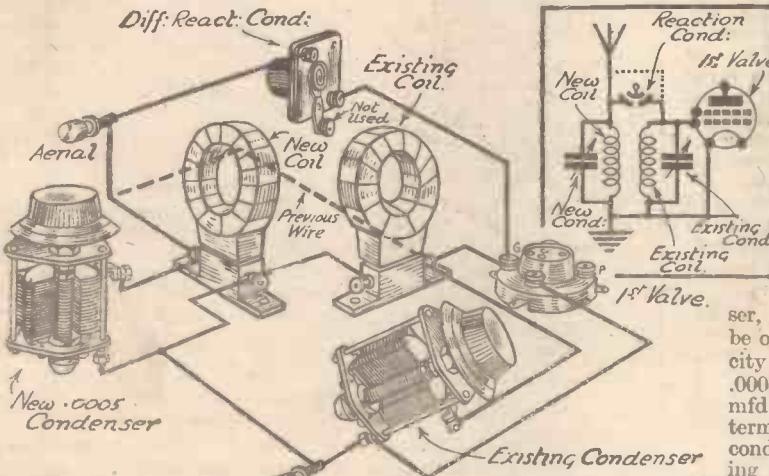


Fig. 1.—This sketch shows a simple means of converting the aerial tuning condenser of a receiver to a simple band-pass arrangement.

having characteristics in keeping with the modern circuit, and there are undoubtedly many possessors of old parts who are not prepared to go to the expense of buying new ones and scrapping those which are already on hand. In this article it is hoped to show how old parts, perhaps taken from the junk box, can be employed with fair success in the latest types of receivers. It is not going to be suggested that the old parts will give results equal to those to be obtained by using modern ones of special design, but they will, at least, enable the experimenter to try out some of the newest circuit ideas at a minimum of expense.

A Simple Band-Pass Scheme

Nearly every set built more than a couple of years ago suffers from comparatively flat tuning, so that anything which will give increased selectivity is to be appreciated. A very simple, and yet reliable, method of obtaining really sharp tuning with practically any type of set is shown in diagrammatic form at Fig. 1. In that drawing it is assumed that plug-in coils are employed in the existing set, but it should be mentioned that the very same idea is equally applicable to a receiver in

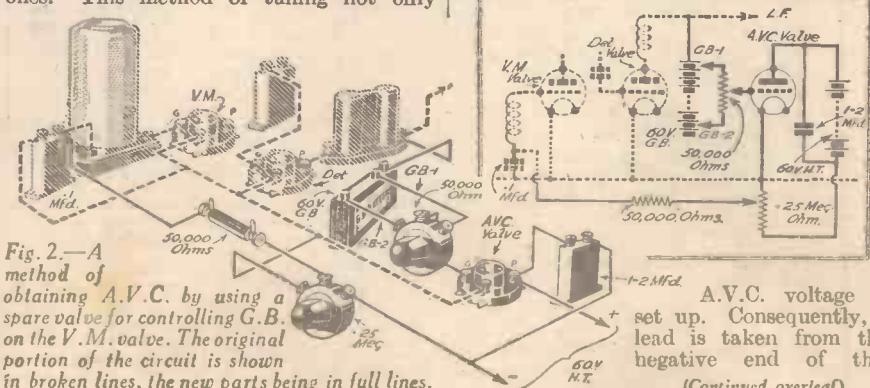


Fig. 2.—A method of obtaining A.V.C. by using a spare valve for controlling G.B. on the V.M. valve. The original portion of the circuit is shown in broken lines, the new parts being in full lines.

A.V.C. voltage is set up. Consequently, a lead is taken from the negative end of this (Continued overleaf)

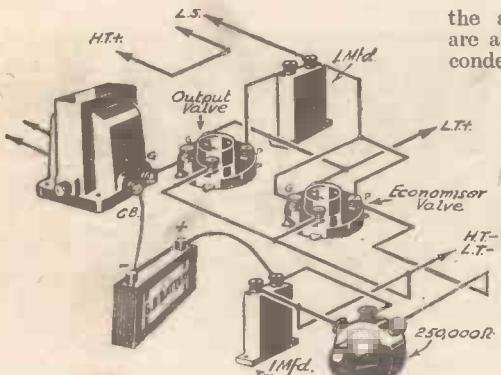


Fig. 3.—A good method of reducing the H.T. current consumption of the output valve by using an additional valve as an "economizer."

(Continued from previous page)

to the grid circuit of the V.M. valve, through a 50,000 ohm decoupling resistance. In order that the arrangement can be followed more easily, the new parts and wiring are shown in full lines, the normal portion of the receiver being represented by broken lines. The method of adjusting this A.V.C. arrangement is as follows. First remove both G.B. wander plugs and tune in a weak station in the usual way; next insert the plug marked "G.B.-1" and find a position for it at which signal strength is unaffected; finally insert the second G.B. plug into a socket giving about 9 volts less than that occupied by the first plug. If signal strength then becomes less, adjust the potentiometer until it is brought back to the previous level. Should it be decided to retain the A.V.C. as a standard, fitting a switch should be included in the lead from the potentiometer to the G.B. battery to prevent the latter from being run down whilst the set is out of use.

H.T. Current Economizer

Another interesting use for a spare valve is represented by the arrangement shown in Fig. 3. In this case the valve acts as an H.T. economy device by reducing the current consumption of the output valve, which may be either a triode or a pentode. The valve now acts as a half-wave rectifier and therefore the grid and anode may be joined together. The two are then connected to the anode of the output valve through a 1 or 2 mfd. condenser, a 250,000 ohm potentiometer being joined between the anode and filament of the valve. If two L.F. valves are employed in the set it will be necessary to use a second G.B. battery, but if there is only one the original battery may be used, and the connections to it altered as shown. The principle upon which the scheme works is fairly simple and is that some of the signal currents appearing in

"economizer" where they are rectified, so setting up a difference of potential across the ends of the potentiometer. As the positive side of the G.B. battery is connected to the potentiometer, it thus becomes more positive in respect to the filament. This is the same as making the grid bias voltage applied to the output valve less negative. It will be understood that the voltage developed across the potentiometer varies in proportion to the signal voltages being handled by the output valve, and thus the negative bias actually applied becomes less as the signal voltages increase. Because of this it is possible to apply a nominal G.B. voltage much greater than that required by the valve when it is fully loaded, without running the risk of introducing distortion. The connections are self-explanatory, and it need only be added that the negative grid-bias wander plug should be inserted in about twice the voltage previously employed, after which the potentiometer should be adjusted to a position at which there is no distortion on either weak or loud signals. A certain amount of initial experiment might be called for in order to find the most suitable voltage, but once that has been done the "economy" device is perfectly self-compensating. Try it!

Q.P.P. with Old Transformers. Quiescent push-pull amplification is not used very widely now, due to the fact that Class B is cheaper and equally effective, but it gives a much greater output than can be obtained from

an ordinary power or pentode valve. This system of amplification can be tried fairly easily and in a form that will prove reasonably effective by following the connections shown in Fig. 4. Two ordinary L.F. transformers are used, the primary windings of these being connected in parallel and the secondaries in series in order to obtain a high step-up ratio. "Stopper" resistances of 50,000 ohms each are included in the grid leads to the push-pull valves, but these will not be essential if the valves have similar characteristics and if the transformers are alike. In any case, however, it is desirable that the valves should be of the same types and that both transformers should have the same ratio. The valves represented are pentodes, although triodes can be used instead, merely by omitting the two leads marked "H.T.+2" and "H.T.+3." For preference, the output choke should be a special Q.P.P. one, but it is sometimes possible to obtain good results by using an ordinary centre-tapped choke, provided that it has a low D.C. resistance and a high inductance. As an alternative, a pair of plain chokes may be joined in series, the H.T. positive lead being taken from their junction. Of course

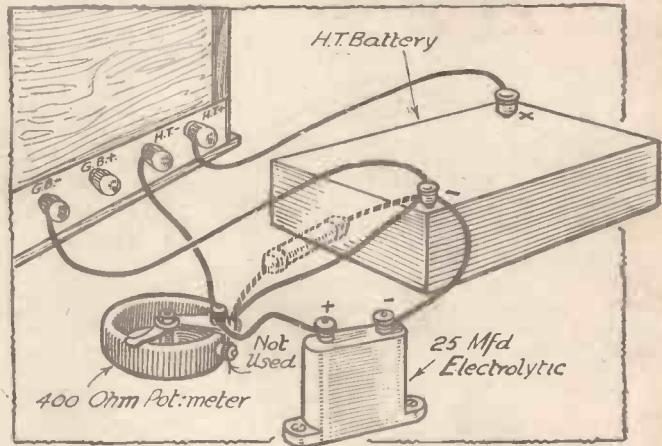


Fig. 5—Automatic grid bias can be provided in the manner shown above by making use of an old potentiometer.

any form of output choke would be unnecessary if a loud-speaker of the special Q.P.P. type were to be used with the set.

In using the improvised Q.P.P. amplifier the G.B. voltage to the last two valves should be increased to about twice the value normally required by the valves. It is also desirable that the preceding (detector) valve should be of comparatively low impedance; one of the "detector" or "L.F." type will fill the bill.

(Continued on page 803)


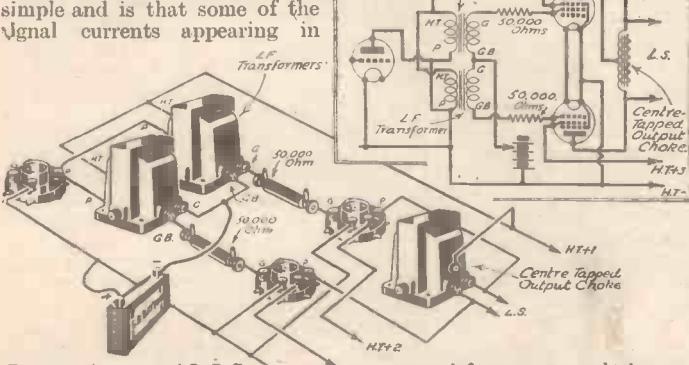


Fig. 4.—A system of Q.P.P. with Old Transformers.

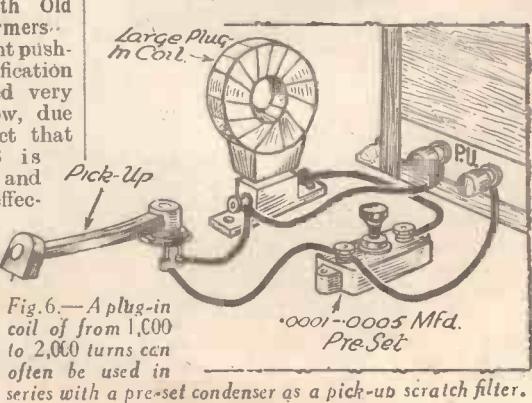amplification in which two are used in the input circuit.





The LUCERNE WAVE PLAN and its CONSEQUENCES

In this Article, Mr. J. Godchaux Abrahams Discusses the New Wavelengths and Their Effect Upon Your Particular Receiver.

THE alleged revolutionary upheaval of the broadcasting world due to the coming into force of the new Lucerne Wave Plan on January 15th appears to have aroused some anxiety in the minds of many listeners. From the letters we have received on the subject it would seem that many readers are labouring under the impression that the game of "general post," played by the European transmitters on that date, is likely to cause considerable inconvenience, inasmuch as such a change in channels will necessitate a complete re-dialling and will render the present condenser scales obsolete.

Let it here be said that however drastic the re-allocation of wavelengths appears at first sight, the practical result of the allotment of new channels to the individual stations will not affect listeners to any appreciable degree. As will be explained later, the actual adoption of the new wave plan will only restrict the number of broadcasts available to the energetic knob-twiddler; it means that such advertised features as "logs of eighty and one hundred stations" may become a thing of the past. The number of transmissions receivable may be curtailed, it is true, but on the other hand the placing of the transmitters in the wave-band having been carried out in a more judicious manner, the relatively fewer programmes tuned in will be less marred by interference and thus a greater proportion of worth-while broadcasts should be available to the ordinary listener.

How the Stations are Divided Up

To understand the reason for which a lesser number of stations will be captureable, it is necessary that some explanation should be given of the new Lucerne Plan. It must be borne in mind that at present wavelengths have had to be found for over two hundred and thirty different European stations, and this number is still likely to grow. Do not forget that in addition to providing a "place in the sun" for the broadcasting studios, clear channels must exist for wireless transmitters connected with such vital services as shipping, commerce, meteorology (weather forecasts, storm warnings, etc.), fog beacons, and for the police, military and naval authorities of the various States. For this reason the band which can be allocated for the use of wireless education and entertainment is strictly limited, and its boundaries are well defined. To place, therefore, over two hundred and thirty stations, it has been necessary to create one hundred and thirty separate channels comprised in three different bands, namely, (a) 1,000–2,000 metres (300–150 kilocycles), (b) 600–1,000 metres (500–300 kilocycles), and

(c) 200–600 metres (1,500–500 kilocycles). Of these (a) and (c) may be said to be mainly reserved to broadcasting stations, but (b) is merely "lent" for the purpose on the understanding that the use of it may be withdrawn if it is found that any interference is caused to other services.

The reason for which exclusive channels for all stations has not been found possible is attributable to the fact that if mutual interference between two neighbouring stations is to be avoided, a definite separation of at least nine kilocycles must exist between their respective transmissions. It is, consequently, this necessary separation which has restricted the number of available wavelengths throughout the three wave-bands and which, for the same reason, has compelled the authorities to create four different classes of channels. These are (1) exclusive, (2) shared, (3) national common and (4) international common. Let me make this clear. In the first case we have, without doubt, a channel coveted by all, namely, an exclusive one to the station to which it has been allocated; in the second we find a wavelength which must be shared with some other transmitter. In this instance the geographical position plays an important part; where such a split channel has been allocated the choice has fallen on two stations at the greatest distance possible from each other. The disadvantage of this arrangement as against the exclusive wavelength will be seen later. The national and international common waves are self explanatory; the former are channels reserved to one country for a number of stations, and on which a programme may be simultaneously broadcast—it will be mainly used for relays—the latter represents a channel allotted to a number of different countries and, as may be realised, can only be used for low power stations in view of the fact that they may be operating at the same time, and will be broadcasting individual entertainments.

How the Listener is Affected

Now, before going into the question of power, let us see in what way this new plan can affect the listener. If we consider the exclusive channels nothing much has happened as, whether we tune in Rome on 420.8 metres as against its present position on 441 metres, we are not affected in any way. We may change the exclusive channels all round with the sole result that in the case where dial readings are in degrees we shall have to make a fresh list of the stations. Where the dials of manufacturers' receivers have been made out in station sequence, most of them have taken steps to provide their clients with new readings to conform with the wave plan.

If your neighbour, Mr. Brown, moves from No. 78 in your street to No. 20 in the

next, there is nothing to prevent your telephoning to him; all that has happened is that his calling number has changed and you will require a new telephone list by your instrument.


But what about shared waves? Well, here we are not so well off because, to use the same illustration, Mr. Brown and Mr. Smith may be living in the same house and now possess the same telephone number. In reality, in the case of shared channels, although a clean transmission may be secured locally, it is unlikely that a listener at a distance will be able to receive the transmission without interference.

If you happen to be living at a point situated half-way between the two stations and your receiver is capable of capturing signals from both, it is evident that the jumble of sounds originating from different programmes will be an unpleasant one. Such a contingency, however, so far as is possible, is warded off, as already stated, by allocating the channel to two transmitters at a great distance from each other. As an example let me cite Limoges (France) and Dniepropetrovsk (U.S.S.R.), both ordered to work on 328.6 metres. As there is little chance of your hearing the latter in the British Isles, there is a good possibility that the French concerts through the former will still be picked up fairly free from interference. Most of the trouble which might have arisen through the sharing of channels has also been obviated by limiting, in either or both cases, the power of the transmissions.

Allocating the Power

The new wave plan, however, had many snags to contend with, one of the most troublesome lying in the power to be used by transmitters already under construction. The limitation of energy permissible in the different wave-bands in respect of the various classes of waves could not be enforced without exceptions, a matter which increased the difficulty of compiling the plan. Roughly speaking, the power allowed to the stations is as follows: For those working on wavelengths between 1,000 and 1,980 metres, up to 150 kilowatts, with a special dispensation granted to Moscow, already in operation, to use 500 kilowatts; transmitters located on channels between 272.7 and 545 metres, 100 kilowatts (Budapest, Vienna, Prague, Leipzig, Paris PTT, Toulouse PTT and Rennes-Thouries were exempt from this restriction); 60 kilowatts maximum if working between 240 and 272.7 metres and 30 kilowatts for waves between 200 and 240 metres. For the common waves allotted to stations in one specified country, not more than 5 and 2 kilowatts, and for international waves in the last class 200 watts is not to be exceeded.

(Continued on page 784)

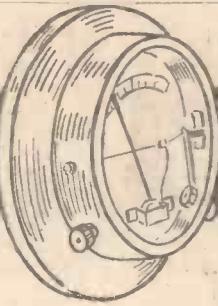

MAKING A HOT-WIRE AMMETER

An Ammeter has Many Applications in Wireless, and This Article Describes How a Simple and Efficient Instrument can be Made at Home.

THE construction of a meter for measuring current is not a task that is generally undertaken by the amateur, principally because it is considered to be outside his scope. This might be true so far as instruments of the moving-coil or moving-iron type are concerned, but a hot-wire instrument can easily be made by anyone who is accustomed to using simple tools, especially if he has some knowledge of electricity. A hot-wire ammeter of the kind to be described is illustrated in Fig. 1, and it can be seen from this that there are very few parts required, whilst none of these are of an intricate or complicated nature.

How It Works

Before dealing with the actual constructional work it will be better to describe briefly the principle upon which the type of meter under discussion operates, so that later remarks will more easily be understood. As the name implies, a hot-wire ammeter reads the intensity of a current due to the heating of a length of wire. The wire used has a (comparatively) high resistance, being made of german silver, nichrome or some similar alloy, and thus as current is passed through it the wire becomes hot, just in the same way as does the element of an electric fire or the filament of an electric lamp. It is well known that when a metal is heated it expands, and it is this property which is made use of in the hot-wire type of meter. The length of resistance wire in the meter is so arranged that when it expands it is caused to sag, due to the tension exerted upon it by a thread attached to a spring. In passing from the wire to the tension spring the thread passes over a small pulley or roller to which is attached a pointer. Thus, as the resistance wire expands (and sags), the thread moves, rotates the pulley, and so drives the pointer over a scale, which may be calibrated in amps or volts as required.

Parts Required

Rather than give a specific design entailing the use of exact parts, which might in some case make it necessary to employ a lathe in their construction, more general information will be given so that it may be applied in utilizing small parts, as well as odds and ends, that might be on hand. The principal parts are shown in Fig. 2, and in that illustration it is assumed that the reader will have facilities for turning up in a lathe the wooden case. Failing such facilities, it will be found quite possible to employ a rigid cardboard or paxolin tube mounted on a wooden baseboard. Yet another alternative is to use a short length of metal cylinder attached to a baseboard, but in that case insulating washers must be provided for all the

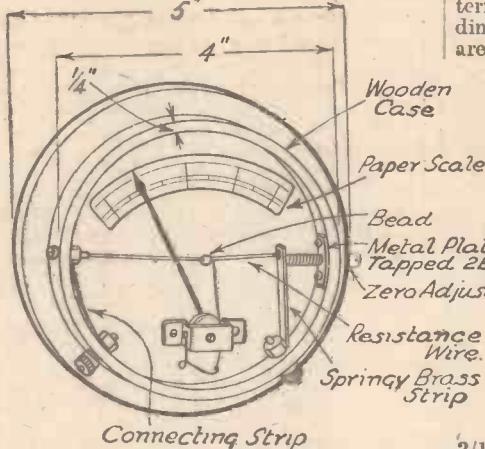


Fig. 1.—Sketch of the finished hot-wire meter described: dimensions are only approximate.

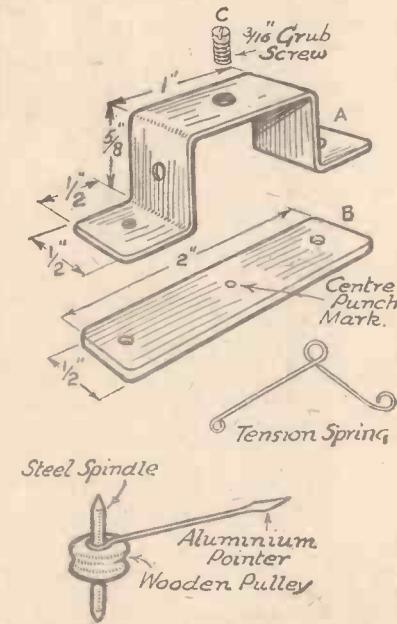


Fig. 2.—The above sketches give all constructional details for the more important parts of the meter described.

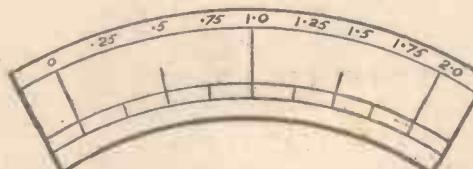


Fig. 4.—This sketch shows how the paper scale is calibrated in fractions of an ampere.

terminals and screws. The casework is dimensioned, although the figures given are really arbitrary ones, which may be modified in accordance with the actual component parts which are made use of. Assuming the use of a wooden case, the first thing to make is the "bridge" that serves as a mounting for a steel spindle, on which are mounted the pulley and pointer. All dimensions are given, and the most convenient metal is mild steel hoop, but those who prefer to make a rather better-looking job will prefer to use a stout gauge of brass sheet.

First make the piece marked "A" by cutting off the metal to length and bending it in a vice. Next drill the necessary holes; three of these are about $\frac{1}{8}$ in. diameter, the third being drilled $5/32$ in. and tapped out with a $3/16$ in. Whitworth tap. After that the piece marked "B" can be cut to length and suitably drilled, using a $\frac{1}{8}$ in. bit. It is essential that the holes in "A" should register exactly with those of "B," and this can be ensured by using the former part as a template. The final task in connection with the spindle-mounting "bridge" consists of making a small indentation with a centre punch in the centre of the piece marked "B" and also in the centre of the $3/16$ in. grub screw marked "C." Here again accuracy is an important feature, so great care should be taken that the two punch marks are directly opposite to each other. This can be ensured by first making a pointed screw to fit in place of "C," mounting "A" and "B" on a flat piece of wood and tightening down the screw until its point makes a mark on "B"; this mark will then indicate exactly where the point of the centre punch should be placed. Another way is to use the ordinary screw, turn this down until its end touches plate "B," and then carefully scribe round it, afterwards finding the centre of the small circle.


The Spindle and Pointer

The small spindle can next be made from a short length of steel wire. Both ends are pointed, and the points can be formed most satisfactorily in a lathe, but failing that, they can be made with a file, or on a small grindstone or emery wheel. The points should be really hard, and, therefore, if the wire has been filed or ground, it will be best to harden them by heating the wire to redness, allowing it to cool to the point at which it is just changing from yellow to blue and then plunging it in water. A small pulley must next be made to fit tightly on to the spindle, and this can be done most easily in a lathe. On the other hand, a suitable pulley might be found in the junk box, whilst failing that, it can be

(Continued on page 784)

TABLE-TOP CINEMATOGRAPHY

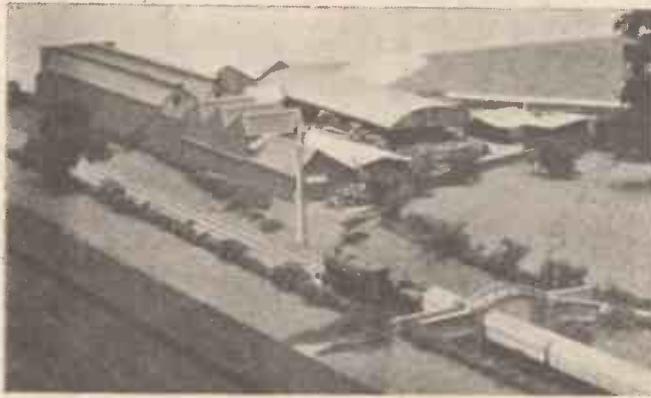How interesting Movies can be Taken with Models.



This model looks like "the real thing" in a home cine film.

Studio pictures, whether "stills" or "movies," go on through winter, undeterred by the short days and poor natural light. But you do not need to be a professional to take good indoor shots. It is quite sufficient to use the ordinary lights of the room, together with an inexpensive lamp in a good reflector. One of the simplest forms of indoor photography is the "table-top" picture. Model railway engines and accessories in these days are built with careful regard to detail, therefore a good imitation of the real thing can quite easily be made up and an interesting movie table-top film can then be taken. Amateur photographers are given still more scope for ingenuity in movie table-top pictures which have an increasingly popular future.

Other Features

A HOME-MADE TALKIE APPARATUS FOR TWELVE SHILLINGS AND EIGHTPENCE

How a reader solved the cost problem.

SECRETS OF TITLING

By the Editor.

THE JANUARY

HOME MOVIES AND HOME TALKIES

NOW ON SALE




EVERYWHERE

Obtainable at all Newsagents, Bookstalls and Dealers, or post free 7d. (Subscription rates: Inland and Abroad, 7/- per annum. Canada, 7/- per annum, from G. Newnes, Ltd., 8-11, Southampton Street, Strand, London, W.C.2.)

Geo. Newnes, Ltd.

POLAR FOR SOUND DESIGN

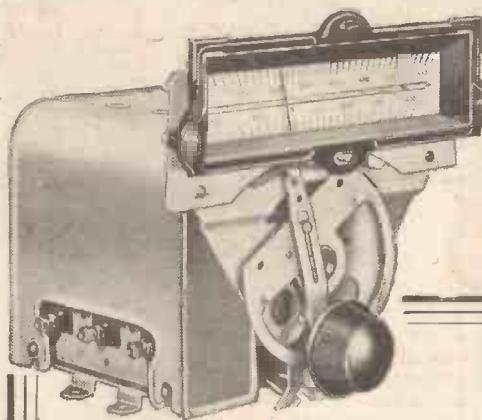

This

POLAR

STAR MINOR 3 GANG CONDENSER WITH HORIZONTAL DRIVE

SPECIFIED for the

NUCLEON

CLASS B FOUR

As illustrated above, with frame made of cadmium plated steel. Trimmers operated from top. Sections matched within $\frac{1}{2}$ per cent. or 1 mmfd. (whichever is the greater).

Supplied with moulded escutcheon. Calibrated in wavelengths and 0-100°.

COMPLETE AS SHOWN

3 x .0005

Condenser only - 18/9

24/6

... Also Specified

POLAR "PRESET"

A reliable and efficient condenser, built in brown moulded case, fitted with nickel plated terminals.

.0003

1/6

WINGROVE & ROGERS, LTD.

188/189, STRAND, LONDON, W.C.2.
Works: OLD SWAN, LIVERPOOL.
'Phone: Temple Bar 2244.



SEND FOR THE
NEW POLAR
CATALOGUE

4335

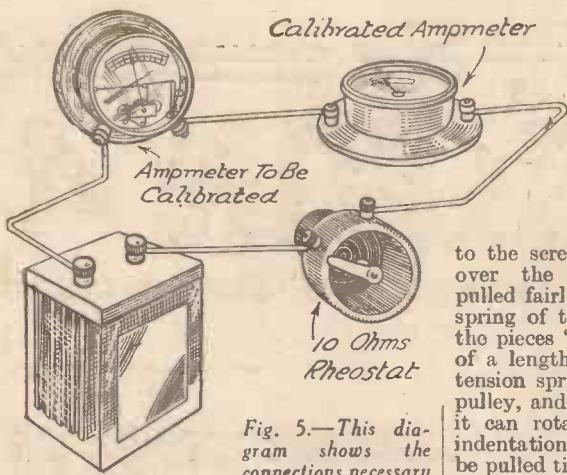


Fig. 5.—This diagram shows the connections necessary when calibrating the hot-wire ammeter.

(Continued from page 782.)

built up by winding a narrow strip of thin paper round and round the spindle, applying thin glue while winding.

The tension spring is called for next. A suitable shape is indicated in Fig. 2, although the exact form is by no means important provided that it maintains a (rather weak) steady tension on the thread. A short length of 24-gauge spring-steel wire is most suitable, and if this is not on hand it can be obtained from practically any ironmonger. At first it will be quite hard and springy, so that it is impossible to bend it to shape without first annealing it by holding it in a gas flame until it becomes red hot. Allow the wire to cool slowly, and then bend to shape with a pair of small round-nose pliers. The wire must then be tempered again by heating it and plunging in water when it cools to the temperature indicated by a blue coloration. The spring is attached to the piece we have called "A" by means of a short 4 B.A. bolt and nut.

When that has been done the spindle can be fitted with a pointer made from a length of 22-gauge wire. Copper wire of this gauge can be used, and it should first be straightened and then looped round the spindle and secured with a spot of solder. Later it can be cut to the correct length, after which the end should be flattened out to enable more accurate readings to be taken.

The Zero Adjustment

The final step in regard to the constructional work is to fit the terminals (either 4 B.A. or 2 B.A. can be used) to the case, mount the length of resistance wire, and fit the "zero adjuster." The latter name might not be quite understood, so it should be explained that after prolonged use the resistance wire will become permanently elongated, and therefore some provision must be made for tightening it and setting the needle to read zero when no current is being passed through the meter. The method of complying with these requirements is straightforward enough, since it is only necessary to attach one end of the resistance wire to a strip of springy brass, which is held under the head of one terminal and arranged so that it can be moved by means of an adjusting screw. The latter is merely a 2 B.A. brass bolt passed through a strip of brass or steel tapped out and screwed to the inside of the case. If the latter were made of metal, the tapped plate would, of course, be sweated on instead of being held by screws.

Assembling the Parts

In assembling the meter the terminals and zero adjuster should first be fitted. After that, a screw should be attached to the inside of the case diametrically opposite to the adjusting screw. One end of a length of resistance wire should then be soldered to the screw, a small glass bead slipped over the end, and the wire then pulled fairly tight and soldered to the flat spring of the zero adjuster. Now mount the pieces "A" and "B," attach the end of a length of thin thread or silk to the tension spring, wind this once round the pulley, and fit the spindle in place so that it can rotate easily in the centre-punch indentations. Finally, the thread should be pulled tight and tied to the bead. Now set the pointer to a zero (left-hand) position, when the meter will be ready for calibration. Before this can be carried out a scale, consisting of a strip of paper glued on to a thin strip of wood, must be made as shown in Fig. 3. This should be fitted inside the case by means of two screws which can easily be removed again later on.

Calibration

For calibration purposes the meter should be connected up in series with an ammeter (any type) of known accuracy, a filament rheostat of between 10 and 20 ohms, and an accumulator (see Fig. 4). By turning the knob of the rheostat into various positions a number of current readings can be taken, and the positions of the pointer corresponding to, say, .25, .5, 1, 1.5, and 2 amps. can be marked off in pencil on the blank scale. After that the scale can be removed and neatly divided up into suitable parts as shown at Fig. 4. It will be found that the divisions are not proportional to the current passing, but that they are more "crowded" toward the bottom of the scale; this is due to the fact that the sag of the wire is not proportional to the expansion, nor is the expansion proportional to the current.

So far no mention has been made of the gauge of resistance wire needed. As a matter of fact, this depends upon the maximum current reading required, the particular kind of wire employed, and the size of the meter (more correctly, the length of the wire). When using Eureka wire and making the case to the approximate dimensions shown, the wire should be about 32 s.w.g., when a maximum reading of 1 amp is required, or 26 s.w.g. when the instrument is to read up to 2 amps. If a still lower maximum reading is called for, such as when measuring the aerial input current from a transmitter, 36 or 38 s.w.g. wire will prove more suitable. It might

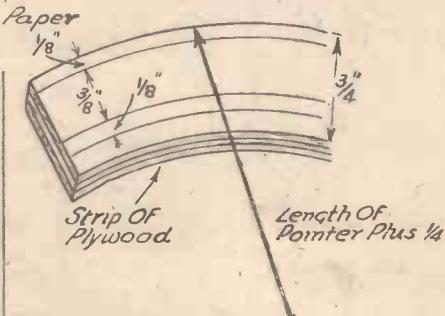


Fig. 3.—Showing how the paper scale is drawn and mounted on a strip of wood.

be mentioned that it is always best to make the meter so that the full-scale deflection is only slightly greater than the value of current to be measured most frequently. By following this rule the most accurate results will be obtained, since it is obvious that more correct readings are to be obtained on the "open" part of the scale.

The instrument described can be used as a voltmeter for reading up to 10 volts or so, if the resistance wire is of about 32 gauge. In that case it can be calibrated with fair accuracy by connecting it in parallel with a high-resistance voltmeter which is known to give true readings.

THE LUCERNE WAVE PLAN

(Continued from page 781)

In addition, stipulations were made as regards direction of aerials and also in some instances transmitters must reduce their power after sunset. As you will see, many points have been considered and much has been done with a view to making the plan the best possible in the circumstances; it would be a great pity if in practice its results fell far short of its theoretical possibilities.

The British listener who is content to limit his wireless entertainments to those provided by the B.B.C. stations has no cause for complaint; the B.B.C. authorities have successfully fought out his case and, as will be seen by the channels secured, the majority of wavelengths are exceedingly favourable. There is, in general, very little change from those used to date.


When, however, the 150-kilowatt station at Droitwich is ready to take over its duties as a National transmitter in lieu of Daventry, some further alterations will be made. The power of the London, North, West and Scottish Regionals will be raised to 70 kilowatts and the London, North and West National on the medium-waves will close down. This will permit a slight change over in channels which will prove to our advantage.

Re-shuffling May Be Necessary

It is to be remembered that of the thirty-six European States interested in the Lucerne discussions, delegates of only twenty-seven countries agreed to the decisions on the day the Convention was signed. As Finland, Luxembourg, Sweden, Poland, Lithuania, Hungary, Holland and Greece refused to recognise the wave plan—at least in some of its findings—a certain amount of re-shuffling may still take place.

As far as can be foreseen the failure of the dissenting States will not affect the medium broadcasting band, but there is every likelihood that much alteration must be made in the allotment of channels between 1,000 and 2,000 metres before these countries will declare themselves satisfied. In these circumstances, it would appear that stations working on the "high" waves may not change over on January 15, but until further notice will continue in their present positions.

It is evident that the Lucerne Plan was only compiled as a *modus vivendi*, and that if it is to satisfy all interested parties, some concessions may be needed. As it is, it is supposed to stand good for two years, but revisions are not barred, and it forms an excellent basis for negotiations. It will be given a thorough trial when stations take up their allotted channels in January, and as may be seen from the list published, it should go far to alleviate the present congested state of the ether.

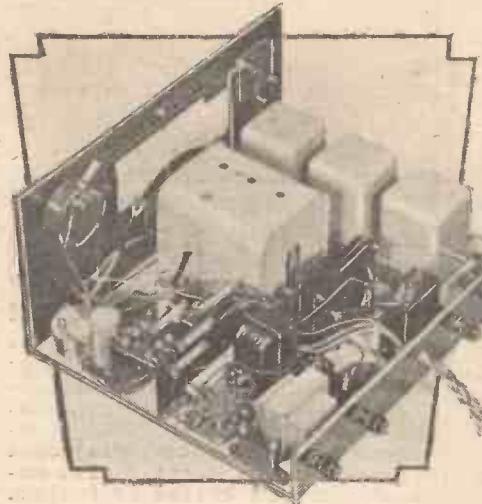

Building the NUCLEON 4

A Simply-Constructed and Highly-Efficient Four-Valve Receiver Which Employs Iron-Core Tuning Coils and a Class B Output Stage

ALARGE number of readers have asked for a receiver which embodies the two most recent improvements in battery-receiver design, and also has a wavelength calibrated dial. The great difficulty with this type of tuning device is that it is not always possible to obtain an accurate indication of the exact wavelength to which the receiver is tuned owing to the use of coils and condensers of different makes, or which are not adapted

scales having an accurately calibrated wavelength scale, and these are designed for coils having a certain inductance value which must agree on both wave-bands. Thus, in this particular case we find that the scale is suitable for coils which on the medium wave-band have an inductance of $157\mu\text{H}$ and on the long wave-band an inductance of $2000\mu\text{H}$. The Nucleon coils manu-



Fig 1.—Neat panel layout of the Nucleon Class B Four.

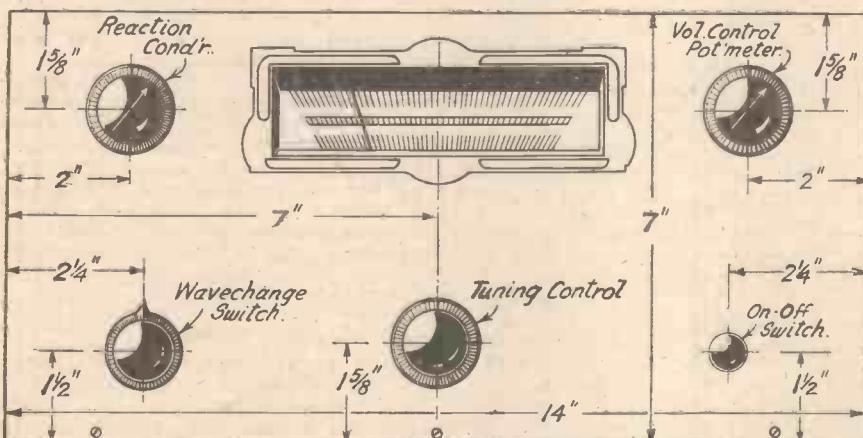


Fig. 2.—Front of panel layout.

to one another. The condensers which are supplied by Messrs. Wingrove and Rogers are designed to be fitted with full-vision

factured by Messrs. Wright and Weaire are found to have these precise figures, and thus it should

be possible to combine the two components to provide an accurately tuned receiver. Our experiments have confirmed this point, and we are thus able to introduce to the reader an easily constructed receiver which does not employ an expensive combined tuning pack, but which does, at the same time, enable him to obtain one of the great advantages of the commercial receiver,

namely, a calibrated receiver. Station searching is greatly facilitated when this type of receiver is employed, as all that is necessary is to look up the wavelength of the desired station and to set the pointer to that portion of the dial. If the station is within range it will be heard, and there will be no loss of time due to searching for a station which is probably out of range of the receiver.

The Circuit

Having described the principal feature of this circuit, and the reason for its adoption, we may examine the remainder of the receiver, and see in what manner it differs from other sets which we have described in the past. Firstly, it will be seen from the theoretical circuit, Fig. 5, that the tuning of the aerial circuit is carried out by means of one coil, and this is coupled to a second coil in the grid circuit of the variable-mu H.F. valve,

(Continued overleaf)

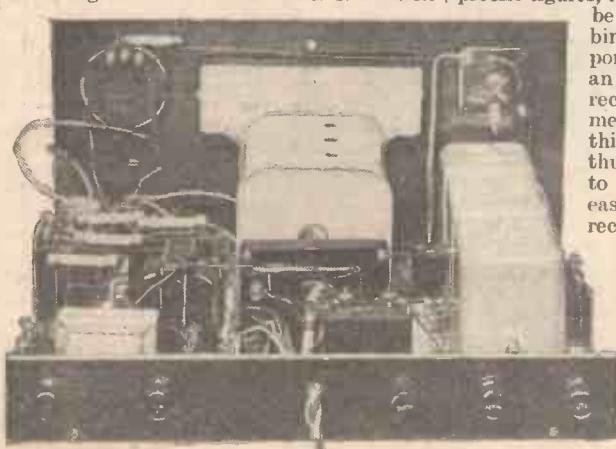


Fig. 3.—Rear view of the Nucleon Class B Four.


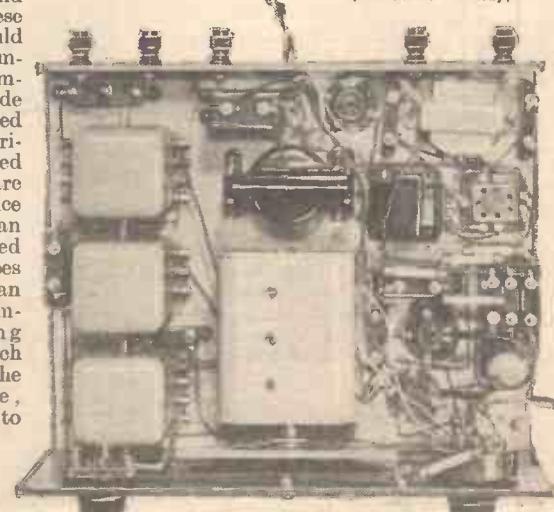


Fig. 4.—Top view of the Nucleon Class B Four.

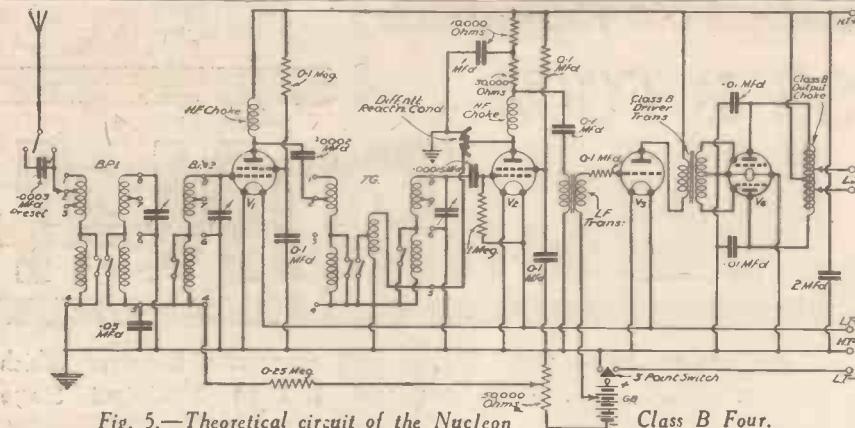

(Continued from previous page)

the complete arrangement forming a highly-efficient band-pass tuner, giving a high degree of selectivity with good signal strength. The combination of this type of tuner with a variable-mu valve thus gives one of the most efficient types of H.F. amplifier which can be built for battery operation at the present day. The H.F. valve is coupled to the detector valve by means of a similar coil, which is provided with a winding for reaction purposes. This may be used to augment signal strength and also to assist in selectivity where this is found necessary. The three tuned circuits are tuned by the separate sections of a ganged condenser as already mentioned, and trimmers are provided on this condenser in order to balance out stray capacities when the receiver is first put

into commission. The detector valve is transformer-coupled to a valve of the small L.F. type, and this in turn is transformer-coupled to an output valve of the Class B type. A tone modifier is fitted in the output circuit, and this supplies a moving-coil

loud-speaker. It will be seen, therefore, that the circuit is perfectly straightforward and possesses no "frills" or other stunts which might render it freakish in operation. It may thus be built up in the certain knowledge that it will function straight away, and no time will have to be spent in carrying out intricate circuit balancing.

The Layout

From the photographs it will be seen that in this instance we have departed from the usual chassis construction. Quite a number of readers have asked for a receiver of this design, as they apparently object to the wiring of a receiver on two sides of a baseboard. They find that they get confused when passing wires from one side to another, and, although we do not think that the majority of readers experience this difficulty, we have arranged this receiver on the older method of construction in order to cater for everyone. It will be seen that this unfortunately results in a rather crowded layout, many

(Continued on page 804)

LIST OF COMPONENTS FOR THE NUCLEON CLASS B FOUR

- One set Wearite Iron-Core Coils (Types BP. 1, BP. 2 and T.G.). (Wright and Wearite.)
- One Polar Star Minor Three Gang Condenser with Horizontal Drive. (Wingrove and Rogers.)
- One Polar Pre-Set Condenser (.0003 mfd.) (Wingrove and Rogers.)
- One 50,000 ohm Megrite Potentiometer. (Graham Farish.)
- One .00015 Differential Reaction condenser. (Graham Farish.)
- Three 4-pin valveholders and one 7-pin. (Graham Farish.)
- One .03 mfd. Non-inductive condenser
- Three .1 mfd. Type 81 ditto
- One .0002 mfd. Type 34 ditto
- One .00015 mfd. Type 34 ditto
- One 1 mfd. Type 50 ditto
- Two .01 mfd. Type 34 ditto
- One 2 mfd. Type 50 ditto
- One 250,000 ohm 1 watt resistance
- Three 100,000 ohm. ditto
- One 30,000 ohm. ditto
- One 10,000 ohm. ditto
- One 1 megohm ditto
- One 3-point On/Off Switch Type S.39. (Bulgin.)
- One Type H.F.P.A. Screened H.F. Choke. (Wearite.)
- One Midget Screened H.F. Choke. (Bulgin.)
- One A.F.3 L.F. Transformer. (Ferranti.)
- One Hypernik Class B Driver Transformer. (Lissen.)
- One Metaplex Baseboard (14in. by 11 in.). (Peto-Scott.)
- One Panel (14in. by 7in.). (Peto-Scott.)
- One Terminal Strip (14in. by 1½ in.). (Peto-Scott.)
- One 7-way Battery Cord. (Bellings and Lee.)
- Five Type B Terminals (Aerial, Aerial, Earth, L.S.— and L.S.+). (Bellings and Lee.)
- Two Coils Connecting Wire, Length of Screening Braid, Screws, etc. (Peto-Scott.)
- One 220 VSG valve
- One 210 DET valve
- One P.215 valve ..
- One 240B valve ..
- One 120-volt Lion Battery
- One 16-volt Lion Grid Bias } Vinces Battery
- One 2-volt 40 amp. Accumulator. (Lissen.)
- One Rola P.M.F4 Loud-speaker. (Rola.)

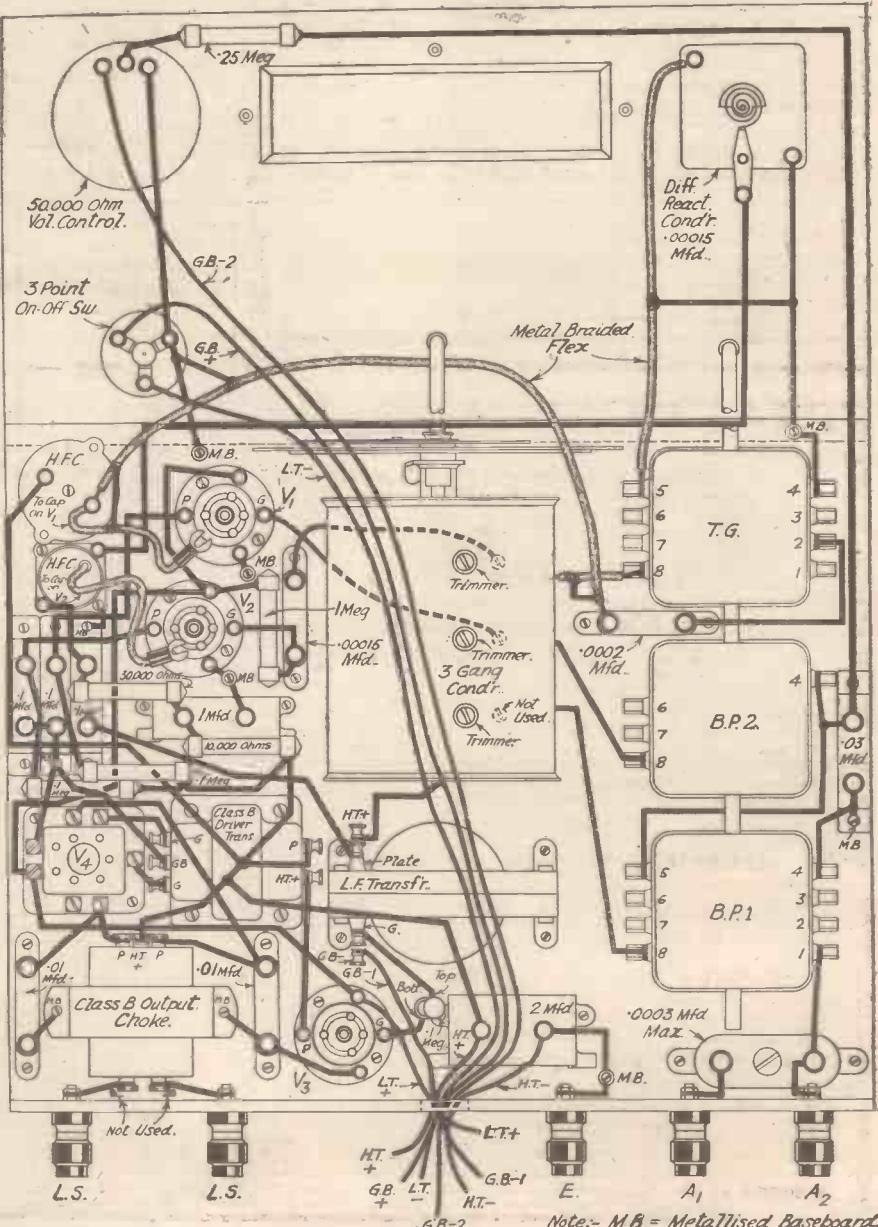



Fig. 6.—Complete wiring plan for the Nucleon Class B Four.

The

NUCLEON CLASS B FOUR

is built around

Reg. Trade Mark

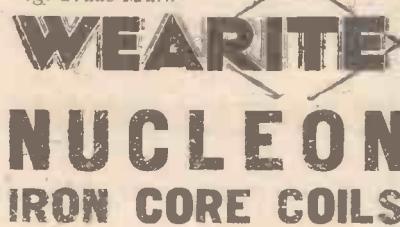

The very heart of this most modern receiver is its coils—Wearite Nucleon Coils. Their amazing characteristics, giving such a high degree of selectivity—permitting the valves to make the most of the initial signals, has prompted the very design of this set. Your coils must be WEARITE NUCLEON.

COUPON To Messrs. WRIGHT & WEARIE Ltd.,
740, High Road, Tottenham, London, N.1.
Please send me a copy of your new booklet, No. GN2, giving full details
of your components, together with technical data, and also Full-size
Blue Print with constructional details for building the "WEARITE
TEAMSTER." I enclose 3d. in stamps to cover cost and postage.

NAME _____

ADDRESS _____

Please write in block letters


The SPECIFIED
Wearite Components . . .

One Set Nucleon Iron-Core Coils
consisting of

BP1 12/6 BP2 12/6
TG 12/6

One Wearite H.F.
Screened Choke
with Pigtail
H.F.P.A. 4/-

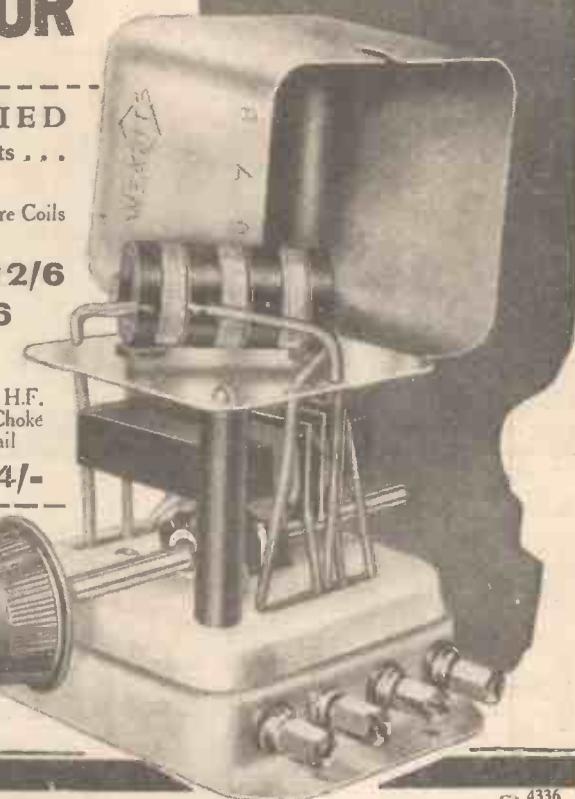Patents
pending
31367/32,
31377/32,
15746/33,
15747/33.
Pending Registration
Trade
Mark 542011.



4336

NEWNES'

PRACTICAL AND HELPFUL WIRELESS BOOKS

Will prove of the utmost value to everybody who wants to understand wireless from A to Z.

Latest Titles

THE WIRELESS CONSTRUCTOR'S ENCYCLOPAEDIA

By F. J. CAMM (*Editor of "Practical Wireless"*), 2nd Edition.

Written in plain language by one of the most accomplished designers and writers on wireless construction. The whole subject is fully covered, and the volume is remarkable for the number of practical illustrations it contains, there are hundreds of circuits, wiring diagrams and layouts. Wireless terms and definitions are clearly explained. No matter in which branch of radio you are interested, you will find everything adequately dealt with here.

5/-; By Post 5/6

THE ELEMENTS OF WIRELESS

By RALPH STRANGER.

The Author starts with elementary principles, covers the whole field of wireless reception, both from the theoretical and practical points of view, and finishes with a complete survey of a four-valve wireless receiver, explaining its working from the aerial terminal to the loud-speaker.

FIFTY TESTED WIRELESS CIRCUITS

By F. J. CAMM (*Editor "Practical Wireless"*)

This handbook contains every modern circuit, complete with instructions for assembling, component values, and notes on operation.

DICTIONARY OF WIRELESS TERMS

By RALPH STRANGER.

The author, who is master of lucidity, has produced in his "Wireless Dictionary" a valuable and fully-explained synopsis of technical terms that everybody can understand. An indispensable boon to every wireless enthusiast who reads technical books and journals.

Other Titles

THE OUTLINE OF WIRELESS

By RALPH STRANGER. (*Omnibus size*)

8/6
By post, 9/-

A comprehensive work on wireless that everybody can understand. Specially written for the "man in the street," and covers the whole subject of wireless reception from A to Z. Fourth Edition. 816 pages.

THE MATHEMATICS OF WIRELESS

By RALPH STRANGER.

5/-
By post, 5/4

This book is essential for the wireless amateur who desires to gain a fuller knowledge of his subject. Written by one who has the gift of explaining abstruse subjects in a simple fashion. Fully illustrated.

WIRELESS, THE MODERN MAGIC CARPET

By RALPH STRANGER. (*Fifth Edition*)

3/6
By post, 3/10

Wireless simply explained at the beginning and seriously treated at the end.

FINDING FOREIGN STATIONS

By R. W. HALLOWS. (*Long Distance Wireless Secrets*)

3/6
By post, 3/10

A book which will be eagerly welcomed by all wireless enthusiasts. It will solve your difficulties and enable you to obtain the best possible results of which your set is capable.

WIRELESS STEP BY STEP

By "DICTRON." (*Tenth Edition*)

2/6
By post, 2/10

A book which shows the wireless enthusiast how to obtain the maximum enjoyment from his wireless set.

RADIO PLAYS

By L. DU GARDE PEACH

2/6
By post, 2/10

Millions of wireless listeners who have been thrilled by such plays as "The Path of Glory," and "The Mary Celeste" can now read them in book form. Mr. du Garde Peach has written some of the most successful plays ever broadcast.



COLVERN SPECIALISE IN COILS

Made under licence from the patentee, Hays Voigt.

accuracy

If you could see the consummate care with which Colvern Coils are made, if you knew the amount of scientific re-

search that has gone—and is going—into the making of them, you would realise why Colvern are the most accurate coils ever made... why practically every expert chooses them. Every coil is thoroughly tested and guaranteed.

Write to-day for Radio List No. 12, telling you all about Ferrocarr.

COLVERN 'Ferrocarr'

COLVERN LTD., ROMFORD, ESSEX.

London Wholesale Dept.: 150, King's Cross Road, W.C.1.

CONVERT YOUR SET TO "CLASS B" AT LOW COST

THE 362 KIT

comprises everything for making a properly matched "Class B" Adaptor, i.e., "Class B" Valve, 7-pin Valveholder, Input and Output Transformers, with full instructions.

28·6

POST FREE



Complete with
"Class B" valve.
50·-
POST FREE

Cash with order. Cheques and P.O.'s must be crossed and made payable to:—
THE 362 RADIO VALVE CO., LTD. (Dept. W.), STONEHAM ROAD, LONDON, E.5.



Read this
QUALITY
Produces
EFFICIENCY

TESTED BEFORE DESPATCH

The original BECOL ebonite low loss formers are thoroughly reliable. They are used in all parts of the world. Look for the BECOL trade mark. Ask your dealer. If unable to supply write direct. SEND NOW, enclosing 6d. (post free) for third edition up-to-date handbook of tuning coils for DUAL RANGE, BAND-PASS, and SUPER-HET. circuits. Fully illustrated with data. A very interesting handbook.

RODS, SHEET, TUBES, PANELS

The BRITISH EBONITE Co., Ltd.,
Hanwell, London, W.7.

NEWNES' FILMCRAFT SERIES

TWO IMPORTANT NEW BOOKS

These textbooks will prove of the greatest service not only to all home-movie makers but to every student of the cine art. It is not necessary to be a practical cinematographer to read and enjoy them—they are brilliantly written and should find a place on the bookshelf of every man and woman who desires to keep up to date in matters pertaining to this great modern art.

FILMCRAFT

By ADRIAN BRUNEL

An outline of the technique of film production intended primarily as a guide for amateur film enthusiasts. Every step from the choice of a subject to the final cutting and editing of the film is clearly explained, while the value of the book is enhanced by a series of appendices written by other well-known experts.

The "Daily Mail" says: "I am happy to be able to recommend 'Filmcraft'.... This is an admirable text-book, written with sound common sense and a grand sense of humour."

FILM TECHNIQUE

By PUDOVKIN

Pudovkin ranks with the greatest Directors of the Cinema and the influence of his pioneer work is found in every modern film. This new edition of his classic work on Film technique is of immense value not only to amateur and professional cinematographers but also to students of the cinema as an art.

The "Evening Standard" says: "...his theories are stimulating to anyone who takes an interest in the artistic future of the talkies."

3/6 each; by post 3/10 each

GEORGE NEWNES, LIMITED


8-11 Southampton Street, Strand, London, W.C.2.

Geo. Newnes, Ltd.

READERS' WRINKLES

THE
HALF-GUINEA
PAGE


Using Bell System for Speaker Connections
IN these days of "a Speaker in Every Room" the following is an easy way of leading the set's output through the house for those who possess the usual house bell system. The latter is usually fairly well insulated, has a low resistance, and is not earthed. Transformer or choke output is necessary in the set, the usual speaker connection being shown at "A." The positive lead is taken to any convenient point on the bell system. If connected at a "push" it is worth trying the

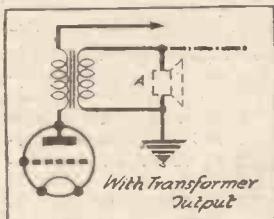

Wiring diagrams showing how a bell system may be used for speaker extensions.

effect of connecting to alternative sides of the contacts. If one lead from the speaker is now connected to any other point in the system, and the other lead connected to earth (usually a convenient gas pipe) reproduction will be obtained with very little loss of signal strength. Alternative connections should also be tried when tapping off at a "push." This latter point is more important when using a bell system run from a mains transformer, as in some cases slight "mains hum" is picked up on one side of the wiring. For convenience two pin plugs can be arranged alongside the bell pushes, one wire connected to wiring, the other being earthed. A fine wire led down the wall and covered by a narrow strip of paper to match has been used in my case, and is almost invisible. Connection may also be taken from the

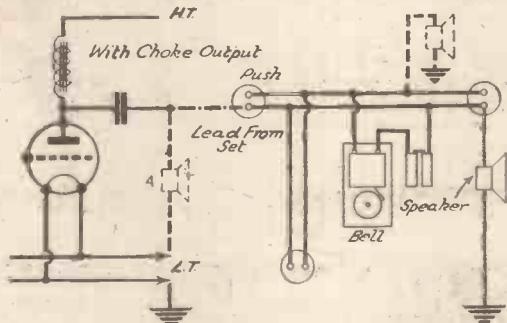
door bells for outside use if required. A useful point is found in the fact that when the bell rings a loud buzz is heard on the speaker.—S. R. RUSHBROOK (Glasgow).



Safe H.T. Connections

THOSE amateurs who use accumulators for H.T. (and some battery users) usually keep them in a cupboard, bringing the wires through a hole in the top, and taking them either direct to the set, or to a terminal board. Both methods have objections, the former owing to the fact that the leads may short when disconnected, and the latter that in the event of any metallic object falling on the terminals, either the front or the back, the results will again not be advantageous to the battery.

The terminal board illustrated will be found to be absolutely fool-proof in spite of its simplicity. The terminals should be of the completely insulated type, and they are mounted on a strip of ebonite or wood, the edges of which are chamfered at 45 degs. This fits into the corner formed between the top of the cupboard and the wall, and is held in place by two screws driven diagonally into the corner. The leads are taken through a hole drilled as near as possible to the corner, thus the connections at the back of the terminals are totally enclosed, and the lettering on the terminal tops is easily read. For quick connections insulated plugs and sockets could be used, but whichever method is adopted the result is a neat and fool-proof terminal board.—E. L. PARKER (London, S.E.15).

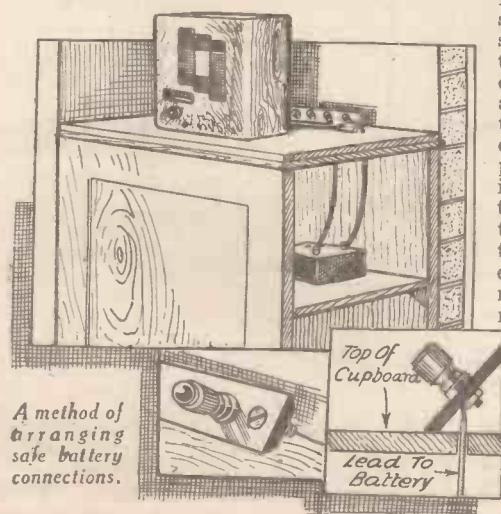

A method of arranging safe battery connections.


A Cheap Anti-Breakthrough Choke
AN excellent anti-breakthrough choke, which will effectively prevent medium-wave interference

when listening on long waves, can be made from an H.F. transformer of the old-fashioned plug-in type. The transformer must be one intended for medium-wave reception and only one of its windings (either the primary or secondary) is actually made use of. The method of connecting the "choke"


is shown in an accompanying sketch, from which it can be seen that it is inserted between the aerial terminal and the corresponding terminal on the first tuning coil. In order to put the "choke" out of circuit when reception is being carried out on the lower waveband, an ordinary two-point on-off switch is connected in parallel with it. For those who do not happen to have a suitable transformer on hand it might be mentioned that these components can often be picked up for a penny or so from "junk" stores dealing in obsolete wireless apparatus.

The pins on the base are arranged in the same order as those on a valve, the "filament" pins being connected to the primary winding, and the "grid" and "anode" pins taking the secondary connections. In using the transformer for the purpose mentioned above wires may be soldered to the pins or a neater job can be made by fitting the component into an ordinary valve holder. There should be no necessity to screen the choke, although it may be found worth while to vary its position in relation to other unscreened coils, etc.

(Continued overleaf)

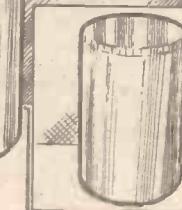

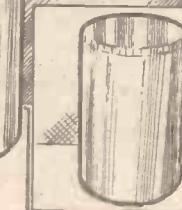Details for making emergency coil screens



READERS' WRINKLES

(Continued from previous page)



Emergency Coil Screens

WHEN experimenting with a set the constructor often wishes to try the effect of screening the coils (providing they are not "canned"), the H.F. choke, or similar components. A coil screen can easily be made from copper foil, and thin cardboard or stiff paper.

A rectangular piece of cardboard should be cut, the width being equal to the height of the required screen, and the other dimension being sufficient to go round the coil. If the required diameter is known, the length will be about three and a half times this dimension. A piece of foil of similar size is cut, and is wrapped with the cardboard to make a tube. It is fastened by means of paper clips.

A circular piece of cardboard is cut with four lugs. A piece of foil with a slightly larger diameter is also prepared. Cuts are made about $\frac{1}{8}$ in. deep towards the centre, and it is then placed on the circle of cardboard, the edge of the foil being wrapped underneath. The lugs are bent down, and the whole is inserted in the top of the tube. A little adhesive will secure it in position, and a short wire joining the foil top to the side will complete the screen.—E. L. PARKER (London, S.E.15).

Inlaying

MODERN cabinet design has certainly kept pace with set design during recent months. A survey of the present models, both for home constructors and those incorporating sets, possibly make one's own set appear quite meagre.


It is not a difficult job, however, to build a modern cabinet, and the part which seems the most difficult is, in reality, the simplest. I refer, of course, to inlaying. If veneered plywood is used in the construction, it is an easy matter to cut the top ply with a sharp knife, guided by a straight steel edge (a twelve-inch steel rule will answer the purpose). The veneer can then be "prised" off, leaving a recess not quite 1-32 in. deep.

Any black material can then be cut to fit the design required, thin ebonite or bakelite can be used, or a black "celluloid" material known as xylonite, and obtainable commercially, will be found very suitable. Any of the well-known adhesives can be used, but if the black material is polished on both sides, the side that is to be stuck should be roughened with sand-paper. The edges of the fret should be sand-papered quite smooth, and then given a coat of black. Failing any alternative, two coats of India ink will be found very suitable. The drawing shows a presentable cabinet with a fret made on these lines.

A Simple Microphone Made from a Telephone Earpiece

A SIMPLE and fairly effective microphone for experimental use can be built into the case of an old telephone earpiece in the manner shown in the accompanying sketch. First of all the magnets and all connections must be removed from the old earpiece and then a wooden ring should be made to fit into the case. The ring should be made a tight fit, and should have a hole about 1 in. in its centre. A small circular tin (one of the kind used for samples of pills or manicure powder is quite suitable) which is a tight fit in the hole should then be obtained, and a wire soldered

HEADPHONE CASE

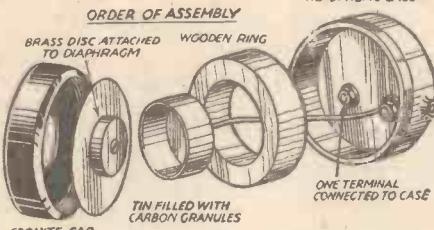

A simple microphone made from a telephone earpiece.

to it and connected to one of the terminals. All insulation must then be removed from the second terminal so that it makes good contact with the metal case. The metal diaphragm is used to take the second connection, and, therefore, if it is enamelled it should first be scraped bright. In the centre of the diaphragm is attached a brass disc about $\frac{1}{8}$ in. diameter by $\frac{1}{16}$ in. thick, the purpose of this being to make contact with carbon granules with which the tin should be lightly packed. It will be obvious that the small tin must be sunk very slightly below the surface of the wooden ring to prevent its making contact with the diaphragm. Connections are taken from the terminals in the normal way.

Some readers might find difficulty in obtaining the ring and might not have facilities for turning it up in a lathe; in such cases an equally effective one can be built up by winding a strip of paper round a wooden rod, applying glue whilst winding, so as to make the finished ring reasonably solid.

50 TESTED WIRELESS CIRCUITS

Edited by F. J. CAMM

Obtainable at all Booksellers, or by post
2/6 from Geo. Newnes, Ltd., 8-11, Southam-
pton Street, Strand, London, W.C.2.

2/6


A Useful Indicator Light.

THOSE amateurs who used drum-drive for tuning, and who have fairly deep escutcheons, will probably find that the latter project some little way through the panel. If a narrow slot is cut in the top part and a bulb fitted, as shown in the sketch, the light will shine through the slot on to the dial, serving the double purpose of illuminating the dial and indicating that the set is switched on. The slot can be made by drilling a few small holes in a line and then filing them into the slot. If a bulb of the .06 amp. rating is used the increased current consumption is practically negligible, being much less than that of a single valve.—E. PARKER (London, S.E.15).

A Simple Wavetrap

A N efficient wavetrap which gives excellent results is shown in the accompanying sketch.

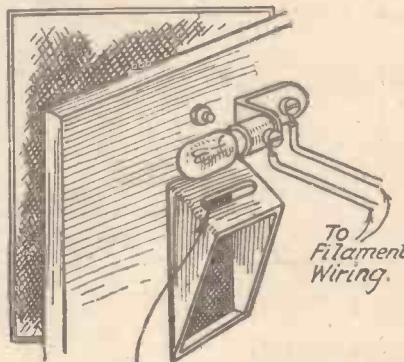The selectivity is splendid and there is no loss of volume; in fact, the volume is greater using the unit than without it. All that is needed are two .0003 variable condensers, one .01 fixed condenser, and a 60-turn centre-tapped coil. These components are connected up as shown in the sketch.



Slot Cut In Escutcheon.


A useful indicator light.

to it and connected to one of the terminals. All insulation must then be removed from the second terminal so that it makes good contact with the metal case. The metal diaphragm is used to take the second connection, and, therefore, if it is enamelled it should first be scraped bright. In the centre of the diaphragm is attached a brass disc about $\frac{1}{8}$ in. diameter by $\frac{1}{16}$ in. thick, the purpose of this being to make contact with carbon granules with which the tin should be lightly packed. It will be obvious that the small tin must be sunk very slightly below the surface of the wooden ring to prevent its making contact with the diaphragm. Connections are taken from the terminals in the normal way.

not moving about as it does when using some wavetraps.—W.M. TUCKER (Swansea).

Easing Screws

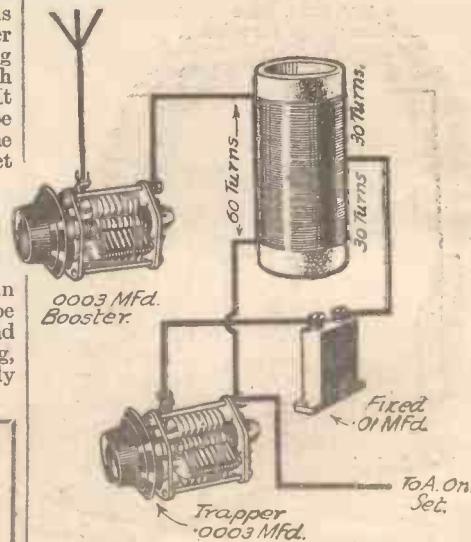A POINT worth remembering when driving screws into hard woods and plywood is that risk of turning off the heads of small or brass screws is avoided if the screw is first rubbed on a piece of grease or soap. A clearance hole should, of course, be drilled before the screw is driven home.



An efficient type of wavetrap.

Practical Television

JANUARY, 1934. Vol. 1. No. 2.

THE "Portovisor" provides a satisfactory reply to those critics who say that television is expensive, and will, I hope, encourage all "waverers" to make a start straight away.

First of all, as will be gathered from the accompanying illustrations, the machine is transportable, quite unobtrusive in appearance, and is entirely self-contained. The reader, if he so desires, can build up the design in stages, and the results obtained from the "Portovisor" will undoubtedly come as a revelation to those who have not looked in before. The cost involved is only

THE "PORTOVISOR"

By H. J. BARTON CHAPPLER,
Wh.Sch., B.Sc., A.M.I.E.E.

gramme in comfort, then a lens frame complete with lenses can be removed from the cabinet, where it is housed for convenience, and placed in front of the aperture.

As far as the complete design is concerned it is suitable only for those readers with A.C. mains, and after being plugged into

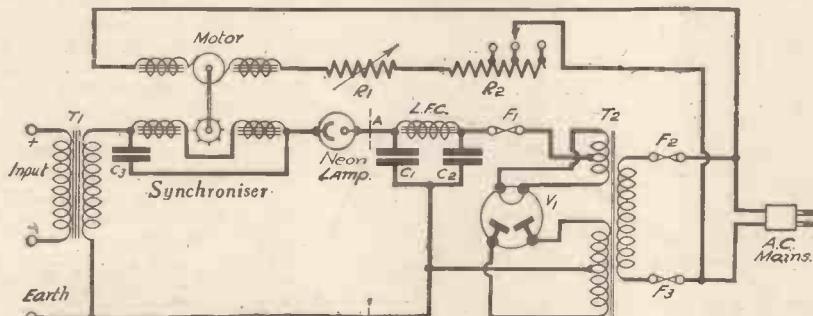


Fig. 1.—The theoretical circuit employed in the "Portovisor."

a few pounds, and, provided the complete instructions are followed carefully, nothing can go wrong or in any way upset anticipated performance.

The image as built up at the cabinet aperture is true disc size, as is the case with all machines of this type. From experience I find this small image suited best to the carrying out of any individual experiments by the constructor as far as his radio receiving set is concerned. He can watch the effects of any changes with greater ease, but when it is desired to "magnify" the image so that three or four people can watch the television pro-

gramme in comfort, then a lens frame complete with lenses can be removed from the cabinet, where it is housed for convenience, and placed in front of the aperture.

As far as the complete design is concerned it is suitable only for those readers with A.C. mains, and after being plugged into

the house electricity supply is joined to the radio receiver by three wires only. Surely that is reducing "trouble" to a minimum,

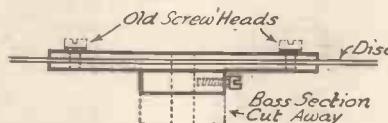


Fig. 2.—How depth is saved by cutting away a portion of the boss.

and a reference to the theoretical diagram of Fig. 1 will show how it is done.

Dissecting the Circuit

First of all the A.C. mains supply passes

COMPONENTS FOR "PORTOVISOR."

- 1 Output Transformer, Type OPM1C (Ferranti).
- 1 L.F. Choke, List No. 751 (Heayberd).
- 1 Television Disc (Peto-Scott).
- 1 Mains Transformer, for 506 B.U. Rectifying Valve (British Radiogram).
- 3 Type B Terminals, Input +, Input -, and Earth.
- 2 Terminal Mounts (Belling-Lee).
- 2 4-mfd. T.C.C. Condensers, Type 87 (T.C.C.).
- 1 1-mfd. Condenser, Type 65 (T.C.C.).
- 1 Universal Motor complete with mounting bracket and synchronising gear (Peto-Scott).
- 1 150-mA. Fuse and F12 Holder (Bulgin).
- 1 Twin Fuse Holder, Type F11 (1 amp. fuses) (Bulgin).
- 1 Baseboard Valve-holder (W.B.).
- 2 Mervyn Lenses.
- 1 506 B.U. Rectifying Valve (Cossor).
- 1 Fixed Resistance, Type MR12 (Bulgin).
- 1 Special Neon Lamp and Bakelite Holder (Peto-Scott).
- 1 150-ohm Variable Resistance (50-watt rating) (Peto-Scott).
- 1 6in. Extension Rod (Bulgin).
- 1 Portable Cabinet (Peto-Scott).
- 1 Baseboard with Motor Platform (Peto-Scott).

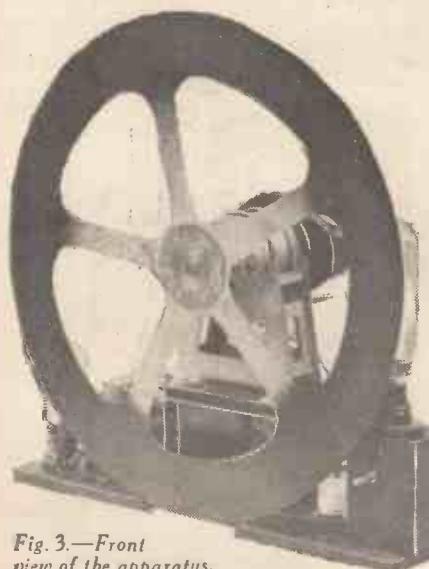


Fig. 3.—Front view of the apparatus.

to one side of the motor, which has to drive the disc at its speed of 750 revolutions per minute, a tapped fixed resistance R_2 and a variable resistance R_1 being included for the dual purpose of cutting down the volts to the value required for driving the motor and also to control the speed.

The lower part of the diagram illustrates a mains eliminator whose function is to supply the polarizing current required to render the neon lamp incandescent, and also to pass through the synchronizing coils. As a measure of protection to the eliminator a pair of one amp. fuses F_2 and F_3 are included, it being noted that these are not in the motor circuit. A dual wound secondary winding on the mains transformer T_2 feeds the rectifying valve V_1 , and, after passing another protective fuse F_1 (150 mA), the usual smoothing equipment consisting of a low-frequency choke (L.F.C.) and reservoir condensers C_1 and C_2 complete the eliminator section.

Across A and B, therefore, we have our H.T. supply, and to this is joined the neon lamp (flat plate type), pair of synchronizing coils (this being part of the motor equipment as supplied, having the thirty-toothed cogwheel mounted on the motor shaft as shown diagrammatically), and the secondary winding of the transformer T_1 . This transformer is of the one-to-one ratio type, and serves the purpose of passing on the television signals from the radio receiver so that the intensity of glow of the neon lamp will respond to the fluctuations, and so produce the television image when scanned by the disc. The two input terminals join to the nominal loud-speaker output terminals of the set, the extra terminal being linked to the earth point of the receiver.

Flexible Design

The description just furnished covers the complete design but actually the instrument is quite flexible in character. The motor is of the universal type, and in consequence runs equally well on both A.C. and D.C. supplies. The reader who has a direct current supply, therefore, has merely to omit the eliminator section and join his mains across the points A and B (positive to A and negative to B), a variable resistance being joined in series with the

(Continued overleaf)

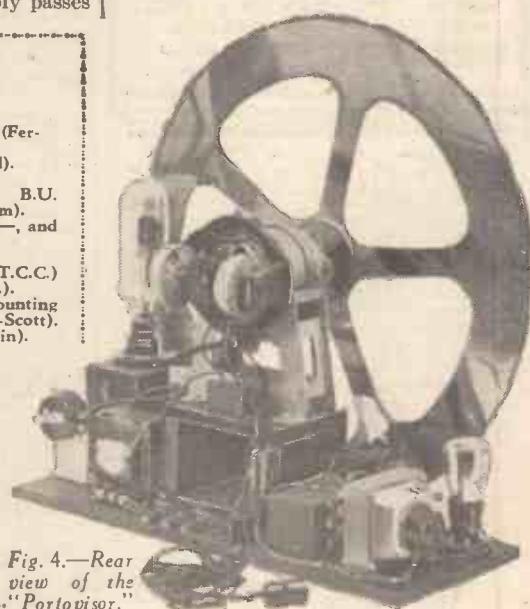


Fig. 4.—Rear view of the "Portovisor."



Heayberd Choke chosen for "Porto- visor"

Practical Wireless Technicians have started the New Year well—by specifying the Heayberd 751 Choke for Mr. Barton Chapple's "Portovisor." The reason why Heayberd Mains Apparatus is chosen is because it is the most reliable on the market.

MODEL 751 - - Price 12/6

Heayberd also have, in their wide range, a Transformer ideally suitable for television work. This is the

MODEL 803 MAINS TRANSFORMER
Output : 250+250v. 75 ma. 2+2v. 1 amp., and 2+2v. 5 amps.

Price 32/6

— — — POST COUPON NOW — — —

I enclose 3d. in stamps for 36 p. booklet showing how I can build my own Mains Unit or Battery Charger, and containing full details of Transformers, Chokes and Class "B" units.

Mr.

Address

PRA

**F. C.
HEAYBERD
& CO.,**

10, Finsbury St.,
LONDON, E.C.2.
MONARCH OF THE MAINS.

GRIPSO
PATENT
NAMED PLUGS
& SPADES
LISTS FROM MAKERS
THE
GRIPSO COY.
28 VICTORIA ST. LONDON S.W.1.


LT.—
PLAIN OR
NAMED
GRID
12 EACH

Engineer's Guide
CONTAINING THE WIDEST CHOICE OF
ENGINEERING COURSES IN THE WORLD
Outlines The T.I.G.B.'s up-to-date, home-study Courses in Wireless, Electrical and
Mechanical Engineering, etc. Shows how
to become A.M.I.E.E., A.M.I.Mech.E.,
A.Rad.A., etc., and how to qualify for a
well-paid post. Training until Successful
Guaranteed.

WRITE NOW for Free Guide.
**THE TECHNOLOGICAL
INSTITUTE OF GREAT
BRITAIN**, 42, Temple Bar
House, London, E.C.4.
(Founded 1917. 10,000 Successes)



To Success

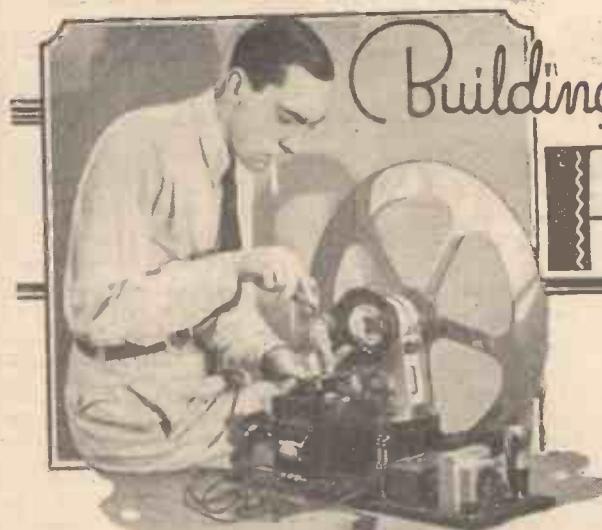

(Continued from previous page)

positive main and A so as to regulate the current passing to the neon lamp.

Finally, if the reader does not want to feed the points A and B from mains at all, he can connect a 200-volt battery across,

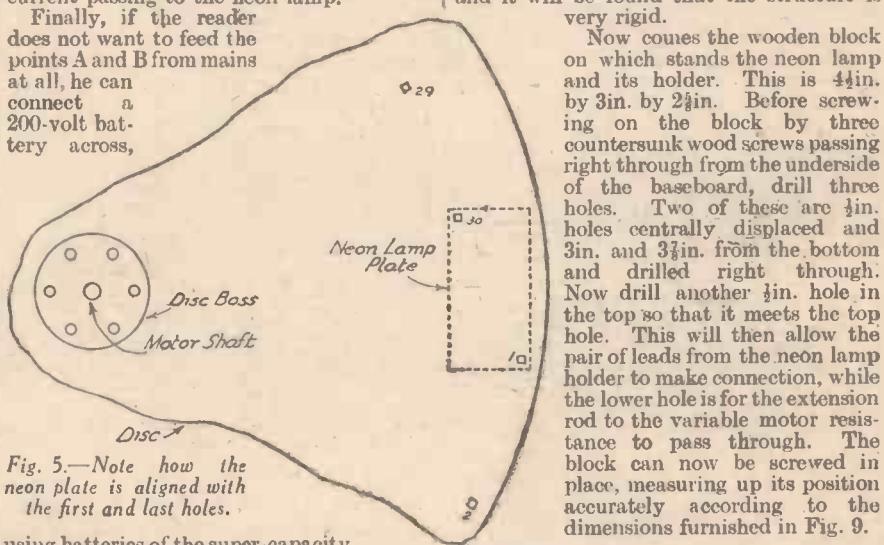


Fig. 5.—Note how the neon plate is aligned with the first and last holes.

using batteries of the super-capacity type. This last-named course must also be followed by those who have no mains available at all, while the motor instead of being a mains-driven type is replaced by a six-volt machine and fed from accumulators.

The First Step

We can now turn to the practical side and see how easy it is to duplicate the design featured in the illustrations. A complete list of the components is included elsewhere, every one of the items being quite standard, and hence readily obtainable from the makers mentioned.

If the combined wooden baseboard with motor platform is not obtained complete, then it must be built up to conform exactly to the dimensions given in Fig. 9. First of all there is the main baseboard 20½ in. by 8in. by ½ in. A piece 5in. by 1in. must be cut out from the front edge in the centre as shown to enable the disc to run freely. Then make up the motor platform which, of course, has to be built

AN EFFICIENT TELEVISION PORTOVISOR

very solidly. A piece of wood 4½ in. square and ¼ in. thick has two side pieces 4in. by 4½ in. by ½ in. screwed to it, with three long screws on each side as indicated. Before adding the top platform screw the base to the baseboard after having accurately marked off its position from the

dimensions given in Fig. 9. Finally, add the top platform 6ins. by 4½ in. by ½ in. and it will be found that the structure is very rigid.

Now comes the wooden block on which stands the neon lamp and its holder. This is 4½ in. by 3in. by 2½ in. Before screwing on the block by three countersunk wood screws passing right through from the underside of the baseboard, drill three holes. Two of these are ½ in. holes centrally displaced and 3in. and 3½ in. from the bottom and drilled right through. Now drill another ½ in. hole in the top so that it meets the top hole. This will then allow the pair of leads from the neon lamp holder to make connection, while the lower hole is for the extension rod to the variable motor resistance to pass through. The block can now be screwed in place, measuring up its position accurately according to the dimensions furnished in Fig. 9.

Changing the Motor Direction

In nearly every disc television receiver described so far, the synchronizing

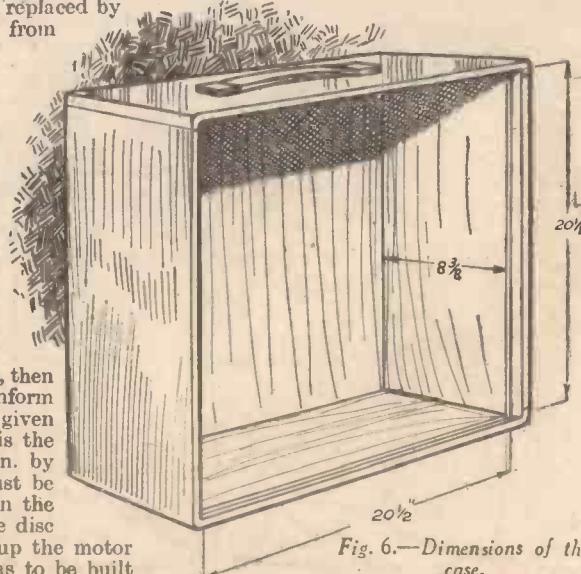


Fig. 6.—Dimensions of the case.

January 6th, 1934

PRACTICAL TELEVISION

AND SIMPLE
RECEIVER

VISOR

mechanism is at the front of the motor, the disc at the back and, of course, the neon lamp on the right. With the "Portovisor," however, I decided to have the disc at the front, and in order to maintain the disc rotation correct, and give the normal scanning of bottom to top and right to left, it became necessary to reverse the motor direction. This is a very simple process and is carried out in the following way:

Remove the synchronizing gear complete by withdrawing the two screws holding the springs against the movable framework. Take off the cogwheel, and then pull out the brushes, after unscrewing the two caps. The aluminium end casing of the motor at the synchronizing gear end may then be pulled off gently, and the motor armature withdrawn at the same time. To reverse the motor direction we must reverse the field winding. At the brush end of the motor casing will be noticed two leads, one at each brush point, which are just sprung into place. Ease off each lead and interchange their positions, then replace the armature, brushes and end plate, screw back the synchronizing mechanism in place and fit the cogwheel once more to the motor shaft. The motor now runs counter-clockwise when viewed from the end remote from the synchronizing equipment.

A Question of Space

Being anxious to reduce the cabinet width as much as possible, and to allow the disc to be as close as possible to the front aperture, the following steps have to be taken. First of all, saw off a piece of the motor shaft at the disc end so that only $\frac{1}{4}$ in. remains. Then take the disc which is supplied with a fairly long boss, and has cheese-headed screws holding the disc between the two flanges, and cut off a piece of the cylindrical boss so that the length remaining is $11\frac{1}{32}$ in. This will necessitate drilling and tapping a new grub screw hole, but that is quite an easy matter. Now remove the cheese-headed screws one at a time and replace with countersunk head screws, and quite a substantial saving in depth will be effected, as indicated by the sketch Fig. 2.

Complete Assembly

The constructor can now make a start on the assembly of the apparatus. The pictorial diagram, Fig. 8, the wiring plan,

(Continued on page IV)

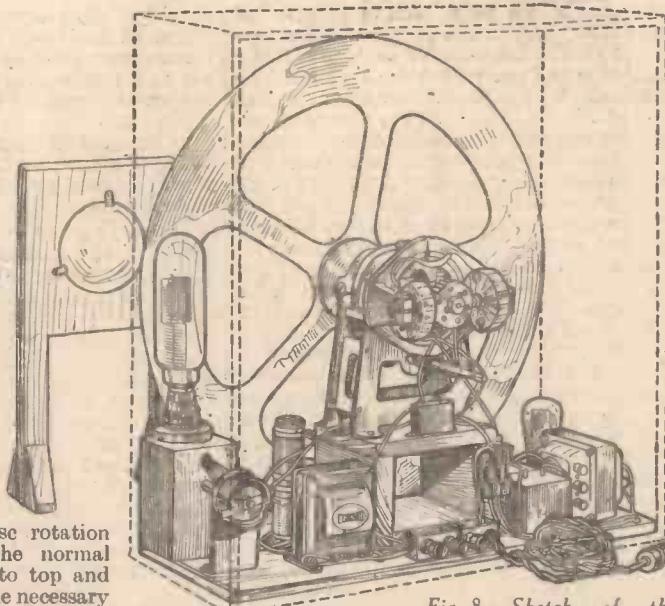


Fig. 8.—Sketch of the finished apparatus.

Fig. 11, and the accompanying photographic illustrations will assist in this connection, and should be studied carefully for there is little room

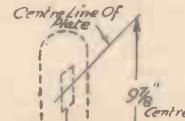


Fig. 9.—The wooden base and motor support.

board edge. Fixing dimensions for the feet are given in Fig. 12, and these must be adhered to. Next comes the neon lamp holder, and

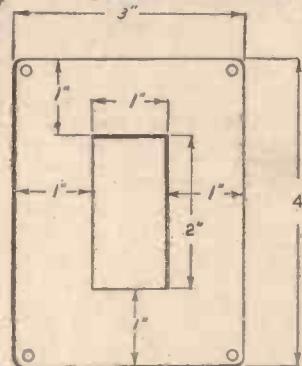


Fig. 7.—The aluminium mask should be cut to these dimensions.

PILOT
TELEVISION KITS

Television for the Home Constructor is now a definitely established fact, and is creating enormous interest among all sections of the public. Once again, as in the past, PETO-SCOTT are first in this new field, readily prepared to supply the needs of Television enthusiasts in all parts of the world. PETO-SCOTT are pioneers in Television and Radio and founders of PILOT AUTHOR KITS. Our service to the British Public was introduced in 1919. Customers in all parts of the globe come to us for all their Radio and Television requirements—Sets, Kits of all descriptions, Part Kits, Miscellaneous Components and Television Equipment. Purchases can be made for Cash, C.O.D., or on Easy Payments. Peto-Scott's Easy-Way System with its strict privacy and no THIRD PARTY COLLECTIONS—We Deal with You Direct Policy—will bring Radio and Television to your home by convenient monthly payments. Readers of this paper should know that Peto-Scott were first with Television Equipment by Mail. During 14 years of solid service and satisfaction we have established a reputation that defies competition.

EVERYTHING FOR
TELEVISION
—SPECIALISTS IN ALL
TELEVISION
COMPONENTS

MOTORS

SYNCHRONISING GEAR

SCANNING DISCS

NEONS

LENSES

PHONIC WHEELS

MIRROR DRUMS

KERR CELLS

MIRROR SCREWS

OSGLIM LAMPS

OUTPUT TRANSFORMERS

MAINS TRANSFORMERS

CABINETS

ETC., ETC.

All prices of components and cabinets on application. SEND FOR DETAILED LISTS.

PETO-SCOTT CO. LTD.
77, CITY ROAD, LONDON, E.C.1.

West End Showrooms:
62, High Holborn, London, W.C.1

NUMEROUS Bulgin Products

are ideal for use in Television apparatus, particularly these switches.

Choose from this comprehensive range.

List No.	Type	Price
S. 102	On-Off	1/3
S. 103	S.P.C.O.	1/6
S. 104	D. Pole	2/-
S. 80	On-Off	1/6
S. 81	S.P.C.O.	1/9
S. 87	3-Point	1/9
S. 88	D. Pole	2/6
S. 89	D.P.C.O.	3/-
S. 98	D.P.D.T.	2/3
S. 91	Rotary	1/9

For further details
SEND FOR 80 PAGE CATALOGUE AND MANUAL
Enclose 2d. Postage.
A. F. BULGIN & CO. LTD.,
Dept. "N.",
Abbey Road, Barking, Essex

BULGIN

In a Class alone.

THE HOME BROADCASTER

A New Practical Home Mike for Wireless Broadcasting at Home. A solo mike for hand or stand in fine bakelite case with back terminals, front metal grille. New and **5/6** finely finished.

THE DIX-ONEMETER. The idea of multi-range moving coil meters. Built to first-grade British Engineering Standard. 50 ranges on one meter. Measures Microamps to 20 amps., millivolts to 1,000 volts, 50 ohms to megohms. Six terminals. Two clear scales, mirror, and knife-edge pointer for accurate reading. Complete in case. **60/-**.

THE DIX-MIPANTA VEST POCKET TESTER. A wonderfully versatile moving-iron multi-range meter for service on A.C. jobs. No projecting terminals. THREE ranges of volts: 0-7.5, 0-150, 0-300. Used for MILLIAMPS reads: 0-12.5 mA., and 0-75 mA. In black bakelite case. Measures only 2½ in. by 2½ in. Complete in case with pair of test leads and plugs. Leaflet "N" gives full information. **19/6.**

S. G. BROWN'S BATTERY SUPERSEDER makes H.T. from your L.T. 2-volt battery, rectified and smoothed. 3 tappings. A boon to those who are not on the mains. Reduced from £4 15s. New and Guaranteed, **37/6.**

LESDIX CHARGERS. We have 25 models to offer and build special types to special requirements. Three popular sizes are the AC109A for 36 cells at £10 9s.; the AC106 for 108 cells at £12 10s.; and the Lesdix Super Six for 200 cells at £32 7s. 6d. Ask for Charger Leaflet "N."

ENGINEERING. Morse Silent Chains, new, 29 ins. long, with large and small sprockets and Chain Cases, 1 H.P. rating, for motor drive, 35/-, quarter price. 10 Skew drive Gear Boxes for Cinema, 1 to 1 H.P., 10/-; Rubber Diaphragms, 18 ins. dia., 1/16 in. thick, new, 2/6. Thermofasters, 2/6. 220 Thermofasters, 2/6.

METERS. We carry large stocks of Meters from 3/6 upwards. Switchboard Ammeters of 3 in. to 8 in. dial of from 0 to 10 amps. to 0 to 1,000 amps., both A.C. and D.C.

Why not send for our Bargain Sale List, "N," post free, and you will save money?

ELECTRADIX RADIOS,
218, UPPER THAMES ST., LONDON, E.C.4
'Phone: City 0191.

here again we must remove superfluous material. With a hacksaw cut off a segment of the lamp-holder base, so that the flat edge is flush with the circular holder portion. This is shown very clearly on the left of Fig. 12. See that the centre of the holder, and hence the centre of the flat plate of the neon lamp, is 8½ in. from the centre of the motor shaft. Another important point to note is that when cutting off the segment of the bakelite neon lamp-holder, position the cut so that the neon lamp when in its holder has its flat plate parallel with the baseboard edge. Two new screw holes must be drilled before the holder can be held down on its wooden mount.

Next make up a small right-angled bracket to hold the 150-ohm variable resistance R_1 . The position of this bracket on the baseboard is fixed automatically if the extension shaft is added, and the bracket moved forward until the shaft flange is 1 in. away from the front of the wooden neon lamp-holder mount.

Next screw down in position both the vertical tapped tubular resistance R_2 and the 0.1 mfd. fixed condenser C_3 .

I have detailed the work up to this point, for this completes the task of assembly for those who desire the simple television receiver alone without the eliminator and transformer feed. In addition, those constructors using a six-volt motor to be driven from accumulators will omit the vertical tubular resistance, and replace the 150-ohm variable resistance with a 6-ohm one. Only one or two leads need be added now by these constructors, and the apparatus is complete.

Completing the Work

Naturally, the best course for those with A.C. mains is to carry out the complete design, and then the remainder of the components can be screwed to the baseboard as indicated in the wiring diagram, Fig. 12. When this is done complete the wiring. For convenience this has all been carried out in single rubber-covered flex. The runs of each wire are shown in Fig. 12, and care should be taken to trace out each lead so as not to go wrong. As far as the output transformer is concerned, although this is a push-pull type, the centre tap points of each winding are ignored. The lead connecting one terminal of the variable resistance R_1 to the tapped resistance R_2 terminates in a crocodile clip to enable the correct tapping to be ascertained. Also be sure that the mains transformer primary winding is joined to the proper voltage tapping to correspond with the house mains electricity rating.

A Preliminary Trial

At this juncture it is as well to give the "Portovisor" a preliminary trial to ensure that both the wiring and assembly are free from errors. Place the neon lamp in its holder and the disc on the motor shaft, holding the latter in place by its grub screw. Turn the disc gently by hand to see that it does not foul any of the components. Owing to its flimsy nature it tends to flap somewhat, but this is not harmful and when you run up to its isochronous speed it will whip out flat.

Clip in the pair of one amp. fuses and the single 150 milliamp. one, and insert the rectifying valve in its holder. Tap off the maximum resistance on R_2 , insert the A.C. mains plug into a convenient socket and switch on. The first thing to notice is whether the neon lamp lights up correctly. The flat plate should glow uniformly with

a fairly bright orange red colour, but if the short horizontal bar behind the plate glows instead, switch off the mains, reverse the two connections in the bakelite lamp holder, and matters will be rectified.

Next note that the motor is rotating the disc in an anti-clockwise direction when facing the disc, and, of course, see that the blackened side of the disc faces the observer.

It now becomes necessary to see that the motor, disc and neon lamp are in the correct relative positions, so as to scan the whole of the glowing neon lamp plate. Disconnect the mains and temporarily remove the crocodile clip from the tubular resistance. This will break the motor circuit and prevent it from running. Switch on the mains once more, so that the neon lamp glows, and turn round the disc by hand until the first and last of the scanning holes are positioned as in Fig. 5. The dotted rectangle represents the glowing plate, and the first and last holes (Nos. 1 and 30) of the disc should be just accommodated within the bottom right-hand and top left-hand corners respectively. If this is so, then every hole will scan a strip of the neon plate. If the lamp is a trifle too far to the left or the right, then ease the screws gripping the lamp holder to its wooden base, and adjust the lamp position until the condition shown in Fig. 5 is obtained. Switch off the mains, replace the crocodile clip and prepare to accommodate the apparatus in its cabinet.

Cabinet Details

The appearance of the cabinet can be gathered from the accompanying photographic illustrations. It has internal dimensions of 20½ in. by 20½ in. by 8½ in., being made of ½ in. wood and having a detachable back. Fig. 6 gives all the details, and if the constructor prefers he can have it made up in any wood desired by Messrs. Peto-Scott, Ltd., who regularly advertise in this journal. The back is detachable, having one hole drilled to allow the synchronizing framing shaft to pass through, and also a rectangular section cut away at the bottom to allow access to the three terminals and give the mains lead free passage.

At the front, on the right, an aperture (midway between top and bottom) is cut out 2½ in. wide by 3 in. deep, so that its centre coincides with the centre of the neon lamp plate. Below this is a hole to take the bush of the extension rod, and to enable an easy control of the variable resistance to be effected from outside. When the aperture and hole have been made, slide the whole apparatus into the cabinet from the back. See that the disc boss does not touch the back of the cabinet front, and then once more connect the plug to the mains socket and switch on. The disc as it gathers speed will flap a little and knock against the cabinet frame slightly, but this is quite normal and as soon as it is revolving fast it will run quite flat, and not in any way foul anything. The strips of light area of the neon lamp will now be observed through the disc holes, and it becomes necessary to mask off the cabinet aperture with a blackened aluminium plate ½ in. thick cut to the dimensions shown in Fig. 7. Position this over the aperture while the apparatus is running, so that the hole in the mask just exposes the glowing light area, and then attach it to the cabinet front by four small wood screws.

(Continued on page VI)

PETO-SCOTT

Peto-Scott are pioneers in Radio and Television. Our service to the British public was introduced in 1919, and during fourteen years of solid Service and Satisfaction we have established a reputation for fair dealing that defies competition. Customers in all parts of the globe come to us regularly for all their radio requirements—Sets, Kits of all descriptions, Part Kits, Miscellaneous Components, Speakers,

EVERYTHING RADIO—CASH C.O.D. or EASY TERMS

Eliminators, and Accessories. Purchases can be made for cash, C.O.D., or on Easy Payments. WE DEAL WITH YOU DIRECT. Peto-Scott's Easy Way System, with its strict privacy and no third-party collections, will bring radio to your home by convenient monthly payments. Send list for quotation: no obligation. Easy Terms on miscellaneous components over £2.

PILOT AUTHOR KITS

BRITISH RADIOPHONE MATCHED PERFECTION SEVEN

KIT "A" Author's Kit of first specified parts including METAPLEX baseboard, less Valves, Westectors, Cabinet and Speaker. Cash or C.O.D. Carriage Paid, £8/5/0. Balance in 11 monthly payments of 15/-.

Send for FREE BLUE PRINT of the MATCHED PERFECTION SEVEN, together with detailed list of parts.

ALL THE RAGE PILOT CLASS 'B' SPEAKER - AMPLIFIER KIT

Assemble this amazing Unit yourself in less than half an hour. Gives seven times the volume with mains quality from your existing battery set. Complete Kit comprises B.V.A. Class "B" Valve, Peto-Scott Permanent Magnet Moving Coil Speaker, B.R.G. Driver Transformer and Input Choke, seven-pin Valveholder, Peto-Scott Baffle and B's aboard Assembly, all necessary Wires, Screws and plug-in Valve Adapter, with full-size Diagrams and Assembly instructions.



Complete with Speaker
Cash or C.O.D.
Carriage Paid 55/-
Or Send only 6/-
Balance in 11 monthly
payments of 5/-.

SUITABLE FOR ANY BATTERY SET

W.B. EQUILODE EXTENSION SPEAKER with adjustable Switch, Chassis and Equilode Unit for perfect matching.

Cash or C.O.D. Carriage Paid, £1/13/6.

Balance in 7 monthly payments of 4/-.

R. & A. MULTEX EXTENSION SPEAKER for Commercial or Home-Built Receivers, past or present, no matter what the circuit. Chassis Model.

Cash or C.O.D. Carriage Paid £1/10/0.

Balance in 7 monthly payments of 4/-.

EPOCH CLASS "B" COMBINATION SPEAKER, a complete Class "B" Adapter, carefully balanced to give superb quality with colossal volume. Complete with Class "B" Valve.

Cash or C.O.D. Carriage Paid, £2/3/6.

Balance in 11 monthly payments of 5/9.

B.T.H. MINOR PICK-UP AND TONE ARM Cash or C.O.D. Carriage Paid, £1/1/0.

Balance in 4 monthly payments of 4/6.

ATLAS G.A.25, for Mains, "Class B" and Q.P.P. Four tappings: 60/80, 50/90, 120, 150, 25 m/A. Cash or C.O.D. Carriage Paid, £2/19/6.

Balance in 10 monthly payments of 6/-.

PETO-SCOTT P.M. MOVING-COIL SPEAKER, Input Transformer. For Power or Pentode, complete with Transformer.

Cash or C.O.D. Carriage Paid, 19/6.

Balance in 5 monthly payments of 4/-.

PILOT "Class B" CONVERSION KIT

Converts your present Valve Set to "Class B" Amplification.

Complete with all necessary components, including driver transformer, "Class B" output choke, W.R. 7-pin valve-holder, B.V.A. 240B valve, wire and screws, etc.

Full-size Blueprint, assembly instructions and diagrams. Cash or C.O.D., 37/8. Balance in 7 monthly payments of 5/6.



YOURS FOR
5/-

37/8

Exact to Specification

NUCLEON CLASS "B" FOUR

KIT "A" Author's Kit of first specified parts including Peto-Scott Ready-drilled Panel and METAPLEX Baseboard less Valves and Cabinet. Cash or C.O.D. Carriage Paid, £8/8/0. Balance in 11 monthly Payments of 15/3.

KIT "B" As for Kit "A" but with set of Specified Valves only. CASH OR C.O.D. and Peto-Scott Nucleon Four Cabinet. Cash or C.O.D. Carriage Paid, £10/13/8. Balance in 11 monthly Payments of 19/6.

KIT "C" As for Kit "A" but with set of Specified Valves only. CASH OR C.O.D. and Peto-Scott Nucleon Four Cabinet. Cash or C.O.D. Carriage Paid, £11/14/8. Balance in 11 monthly Payments of 21/6.

KIT-BITS You pay the Postman. We pay post charges on all orders over 10/- GREAT BRITAIN ONLY.

1. Peto-Scott Metaplex Cabinet 14" x 7" 1 9

2. Peto-Scott Panel 14" x 7" Ready Drilled 4 8

3. Peto-Scott "Nucleon" Class "B" Four Cabinet 1 0

4. Wairite set of Nucleon Iron Core Coils 1 7

5. Polar Star Minor 3-gang condenser with drive 1 4

6. Ferranti A.P.3 L.V. Transformer 1 5

7. Set of Specified Valves 1 0

8. Set of Specified Valves 1 0

9. Set of Specified Valves 1 0

182. Set of Specified Valves 1 0

(Continued from page IV)

Enlarging the Image

The television image observed through the rectangular hole in this mask will be the true size as traced out by the disc holes, that is approximately 2in. by 1in. For certain experimental purposes this is sufficient, but on many other occasions when it is desired to sit down and watch the programme provided by the B.B.C. transmissions, lens magnification must be resorted to.

Details of a simple outfit for this purpose are shown in Fig. 10. First of all obtain two lenses, one a 4in.-diameter double convex of 11.5in. focal length, and a second of 6in. diameter, single convex, having a 17in. focal length. Now make up the wooden structure indicated in Fig. 10. When the hole centre has been marked off, scribe off with dividers or compasses two holes on one side of $3\frac{3}{4}$ in. and 4in. diameter respectively. On the other side two similar concentric circles of $5\frac{1}{2}$ in. and 6in. diameters respectively. Cut out the inner circle of $3\frac{3}{4}$ in. with a fretsaw, and then with a spokeshave chamfer off sufficient wood so that there is a bevel between the 4in. diameter hole at the back and the 5in. diameter circle at the front.

Place the large lens central with the 6in. diameter circle so that its flat face touches the wood, and hold it firmly in position with three small brass clips as shown in Fig. 10. Turn the structure over and mount the smaller lens in place, that is central with the hole, and fix it securely with three small clips. This can now be painted black, and in use just stands in front of the cabinet mask, and in this way magnifies the image considerably. As the cabinet has rubber feet at the bottom, the height of the lens centres just corresponds with that of the aperture centre.

To house the assembly when not in use make two U-shaped clips and fix these to the inside of one cabinet side, on the right facing back preferably, to accommodate the feet of the lens stand. Then screw a short length of 1in. thick wood

to the inside top of the cabinet, nearly flush with the top end of the lens frame, and add two clips to hold it in place with the feet resting in the U clips.

The "Portovisor" is joined to the receiver through the pair of input terminals and earth terminal. Join the former direct to the normal loud-speaker terminal if there is not a step down output transformer already included in the set. If there is, join the pair of terminals to the plate of the output valve and H.T.+ after having first disconnected the set's output transformer primary.

Having connected the earth terminal to an earth point on the set, switch on the "Portovisor" five or ten minutes before the television transmission is due to start to allow the motor to warm up and run steadily. Assuming the London National station which broadcasts the television programme has been previously tuned in on the set, then as soon as the transmission begins, some form of image, very probably distorted to start with, will be seen in the right-hand cabinet aperture.

A series of black lines will be noticed sweeping upwards or downwards, depending on whether the motor is running too fast or too slow, the correct speed being 750 revolutions per minute. The variable motor resistance must be adjusted carefully until the lines lie horizontal, it being

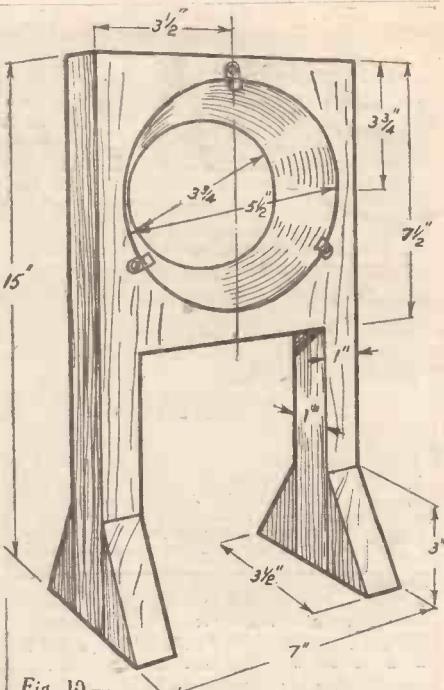


Fig. 10.—
The lens mount. Note the bevelled hole.

noted that if this does not happen, then another tap on the tubular fixed resistance must be tried.

When this state of affairs is reached, the synchronizing equipment will come into action, and maintain the image steady. If, however, the condition of synchronism is brought about with two sections of the image lying side by side, then increase the motor speed slightly until the images move slowly upwards and drift to the left. Let this go on until the double picture resolves itself into a single one, and then quickly bring back the speed of the motor to normal again. This is called phasing the image.

Again, it may happen that two portions of an image appear one vertically above the other. To rectify this, turn slightly the knob at the back and so "frame" the image centrally.


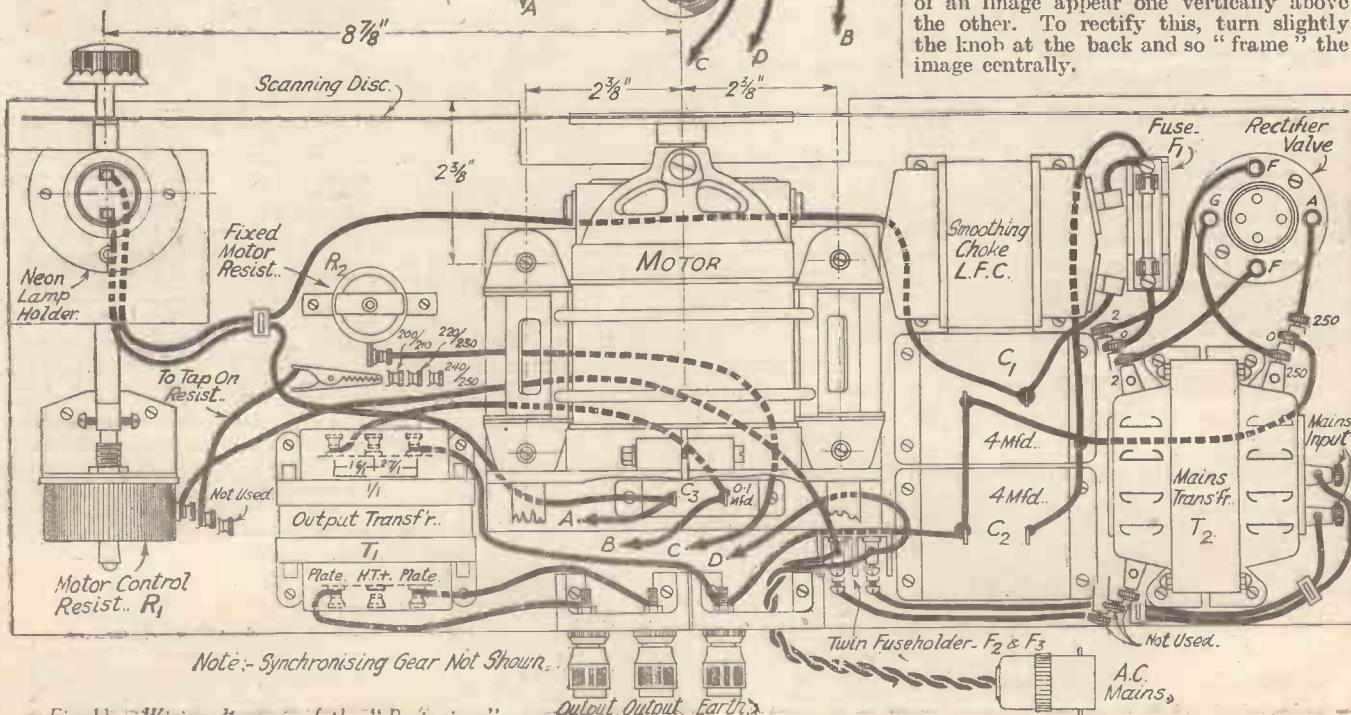


Fig. 11.—Wiring diagram of the "Portovisor."

The Beginner's Supplement

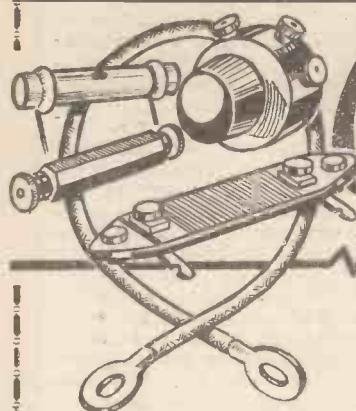

Choosing and Using **RESISTANCES**

In this Article the Author Simply Explains How the Correct Type and Value of a Resistance for any Purpose can be Decided Upon.

WITH the evolution of new and up-to-date circuits it appears that resistances (or more correctly resistors) are being required in rapidly increasing numbers. A few years ago the only resistance that one was likely to find in a standard type of receiver was the grid leak, but nowadays quite an ordinary three-valve battery set might have as many as a dozen, whilst more complicated circuits (especially those for mains working) frequently contain a score of resistances of various patterns. There is no doubt that, although many of the resistances are not absolutely essential, they do improve the performance of the set, in addition to simplifying the operation to a considerable extent. That is all very well for the advanced experimenter who understands the function of each component, but the beginner is very apt to find himself quite "at sea" in trying to decide upon the correct type and pattern for any particular purpose. It is hoped to remove any such difficulty by explaining the applications of each pattern, and showing how the resistance value can most easily be determined.

Types of Resistances

In the first place let us consider the principal varieties of resistances. First, there is the wire-wound one which is generally employed in positions where a good deal of current has to be carried, and where a certain amount of self-inductance is of no consequence. Then there is the so-called metallized resistance, which usually consists of a thin "lead" of metallized material running through the centre of a porcelain rod which has metal connecting caps or wires at each end. Another type of resistance is the "composition" one in which the resistance element consists of a composition made principally of finely-divided carbon, this being enclosed in a bakelite, glass or porcelain tube. Lastly there is the so-called spaghetti resistance in which the element is very thin wire wound in helical fashion on a core of asbestos string. This kind of component is very convenient, since it can generally be connected directly to the terminals of other components; but it is somewhat fragile, due to the very thin resistance wire which must be used in making it. Consequently, it cannot carry heavy currents, and it is liable to be fractured if it is "kinked" or bent to a sharp angle.

Neglecting the spaghetti resistance for a moment, it can be broadly stated that

the wire-wound component is most suitable for carrying heavy currents, partly because the wire has a higher current-carrying capacity than have carbon compositions, and partly because the heat developed can more readily be dissipated. Moreover, this kind of resistance is "permanent" and cannot cause crackling sounds due to its resistance value fluctuating frequently. The carbon composition type, on the other hand, is more liable to introduce crackling sounds, due to the variable contact between the particles of conducting material. In making this statement it should be pointed out that there are a few composition resistances on the market which are practically as reliable as wire-wound ones, especially when they have to deal with comparatively low currents. Metalized resistances are rather similar in their properties to composition ones, but on the whole they are probably more reliable. The last kind of resistances, those in which a conductive film is deposited on a porcelain or similar rod, can be classed along with metalized ones, since their properties are found to be very similar indeed. It would appear that they would better be able to dissipate any heat developed, but this does not seem to be the case in practice.

Variable Resistances

All the above remarks have actually been applied to fixed resistances, but most of them are equally applicable to variable resistances and potentiometers, the only difference being that there are but two general types of variable resistances. One type is wire-wound,

and should be used when there is any appreciable current (more than 1 milliamp. or so) to be carried, and the other is the carbon composition type, where a layer or film of carbon is traversed by a rotating arm. For illustrations of the various types of resistances mentioned see Fig. 2.

Finding the Correct Value

The first thing that the beginner requires to know about resistances is how the correct value for any particular requirement can easily be determined. This brings us to the old favourite, Ohm's Law, which states that the current flowing in a circuit is equal to the applied voltage divided by the circuit's resistance; the three factors must be in amperes, volts, and ohms. As, however, it is generally milliamps. which are dealt with in a wireless set, it is better to modify the law by saying that the current (in milliamps.) is equal to the applied voltage multiplied by a thousand, and divided by the resistance in ohms. By re-arranging the expressions in the formula we can get the equation that the voltage dropped by a resistance is equal to the current (in milliamps.) multiplied by the resistance in ohms and divided by a thousand. Similarly we

(Continued overleaf)

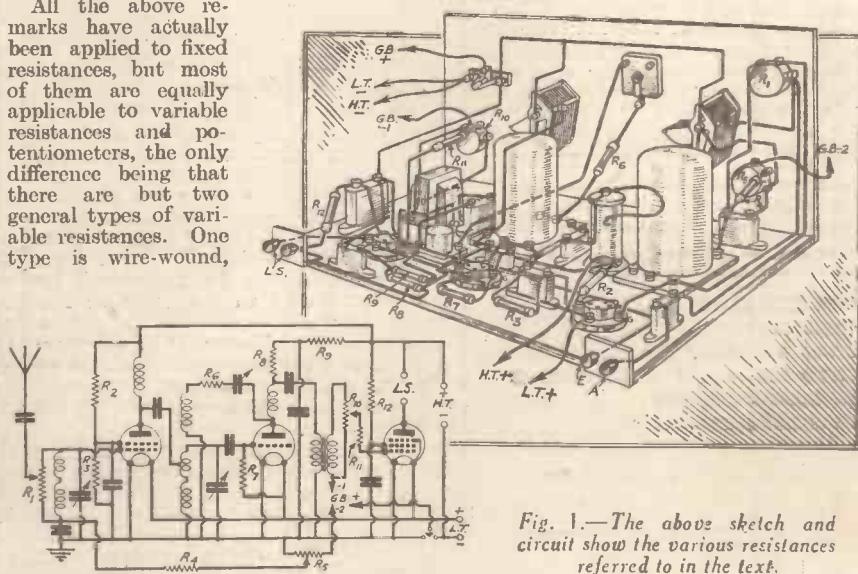


Fig. 1.—The above sketch and circuit show the various resistances referred to in the text.

ANNOUNCEMENT

to men who want careers in RADIO

In the sign language of the Broadcasting Room this symbol means "Announcement."

The I.C.S. Radio Courses cover every phase of radio work, from the requirements of the youth who wishes to make wireless engineering his career to the man who wants to construct and maintain a broadcasting set for his home. The Radio industry is progressing with amazing rapidity. Only by knowing thoroughly the basic principles can pace be kept with it. Our instruction includes American broadcasting as well as British wireless practice. It is a modern education, covering every department of the industry.

OUR COURSES

Included in the I.C.S. range are Courses dealing with the Installing of radio sets and, in particular, with their Servicing, which to-day intimately concerns every wireless dealer and his employees. The Operating Course is vital to mastery of operating and transmitting.

There is also a Course for the Wireless Salesman. This, in addition to inculcating the art of salesmanship, provides that knowledge which enables the salesman to hold his own with the most technical of his customers.

We will be pleased to send you details of any or all of these subjects. Just fill in, and post the coupon, or write in any other way, stating which branch of Wireless interests you—the information you require will be forwarded at once.

International Correspondence Schools, Ltd.,
Dept. 94, International Buildings,
Kingsway, London, W.C.2.

Without cost, or obligation, please send me full information about the Courses I have marked X

- COMPLETE RADIO
- RADIO SERVICING
- RADIO EQUIPMENT
- RADIO SERVICING AND SALESMANSHIP
- WIRELESS ENGINEERING
- WIRELESS OPERATORS

Name..... Age.....

Address

(Continued from page 797)
can obtain the equation that the resistance required for any circuit (in thousands of ohms) is equal to the voltage to be dropped divided by the current in milliamps.

The Wattage Rating

Another factor which must be decided before a resistance is bought is its required wattage rating. Every reader will have noticed that resistances are stated as being of 1, 2, 3, 4 watts, etc., and will perhaps have wondered what is the meaning of this. Power, in watts, is determined by multiplying voltage by current (in amps.): thus a valve filament which takes .1 amp. at 2 volts consumes .1 multiplied by 2, or .2 watt. On the other hand, a resistance which, when passing 20 milliamps., "drops" 100 volts will consume .02 (20 milliamps. expressed in amps.) multiplied by 100, or 2 watts. Another way of finding the power consumption of a resistance is by squaring the current which it passes (in milliamps.),

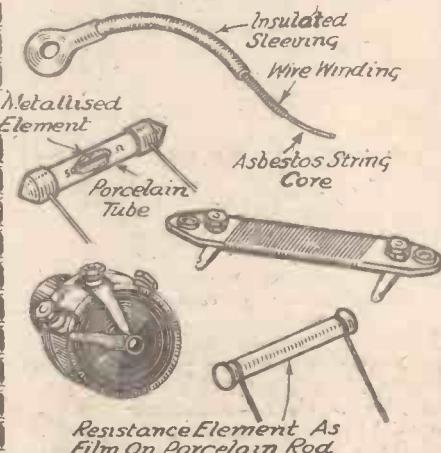


Fig. 2.—Various types of resistances are shown in the above sketch; some of these are sectionalized to indicate the form of construction.

and multiplying that by the ohmic value of the resistance. For example, a resistance of 5,000 ohms which carries a current of 20 milliamps. must have a power rating of .02-squared multiplied by 5,000, or .0004 times 5,000 which is just 2 watts.

Resistances in H.T. Circuits

The simple calculations which have been explained are applicable to most resistances required in the high and low-tension supply circuits of a wireless set, but are of little value when deciding upon the resistances called for in high-frequency circuits. These latter require rather special consideration, and their functions will best be understood by making reference to the more or less standard circuit arrangement for a three-valve variable-mu H.F. detector-pentode receiver such as that shown at Fig. 1. All the resistances, both fixed and variable, have been numbered for easy reference. The purpose of R.1 is to act as a volume control by varying the amount of signal energy passed on to the first tuned circuit from the aerial. Its total resistance must be much higher than the (high-frequency) impedance of the tuning coil, and a value of from 100,000 to 250,000 ohms is generally correct. The resistance element must be

entirely non-inductive or else it will create various "resonance peaks" which will affect tuning; it has not to carry any D.C. current, and therefore a component of the composition type is to be preferred on every count.

R.2 and R.3 act together as a fixed potentiometer, their purpose being to apply the correct potential to the screening grid of the first valve. Assuming that they had to carry no D.C. current at all their resistances would be in the same ratio as that of the S.G. potential to the total voltage of the H.T. battery. For example, if the screening grid required 50 volts and the battery gave 100 volts, the two components should be of equal value; if the screening grid required 40 volts, and the battery gave 120 volts, R.2 should be half the resistance of R.3, or one-third of the sum of the resistances of R.2 and R.3. Actually, R.2 does carry a small D.C. current, and this fact modifies the calculation slightly, although for most purposes this can safely be ignored. It is generally best to choose R.2 and R.3 so that their combined resistance is approximately 100,000 ohms.

R.4 and R.11 are for the purpose of preventing the passage of H.F. currents, although they must offer little impedance to L.F.; values from 25,000 ohms upwards would serve the purpose. Both resistances should be non-inductive, but, as they have to deal with alternating current only, this is not any disadvantage.


R.6 is to prevent the passage of L.F. into the reaction circuit, and may have a value of between 100 and 500 ohms.

R.5 is a potentiometer, the purpose of which is to apply a variable potential to the grid of the first valve. Theoretically it could have any value from about 5 to 100,000 ohms, but if the value were so low as the first figure the G.B. battery would rapidly be exhausted, whilst if it were so high as the latter it would not provide the "neatness" of control that is desirable. Thus the value generally chosen is either 25,000 or 50,000 ohms, and it does not matter very much whether the component is wire-wound or of the composition type, although the former is likely to be somewhat more reliable. It is also desirable that R.5 should be "graded" in order that its resistance value should change by a lesser amount for any given movement of the knob when the latter approaches the "positive" position.

R.8 is used to couple the detector valve to the L.F. transformer, and it should have a resistance equal to from two to two-and-a-half times the impedance of the valve. In most cases it will have to carry but a small D.C. current, and therefore any type of half or 1-watt component will serve. Where the valve operates on the power-grid principle, the current will be considerably higher, so that in some cases a 2-watt resistance will be called for, that can be decided by making the calculation previously described.

R.9 decouples the anode circuit of the detector, and at the same time reduces the total H.T. voltage to a figure suitable for the anode of the detector. Generally its value will require to be between 10,000 and 50,000 ohms, but this can be determined by calculation, as also can the necessary voltage rating.

(Continued on page 800)

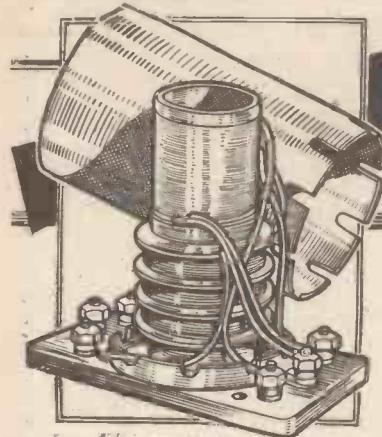

MAKING YOUR OWN Screened Coils

This is the Fifth and Concluding Article of the Series, and in it the Author Describes Some Simple Methods of Ganging Sets of the Coils Previously Described, Besides Giving Some Useful Circuits and Other Information.

By FRANK PRESTON.

In previous articles of this series I have described in fair detail the construction of practically every type of screened tuning coil normally required, so that some further information in regard to the use of the coils described will prove useful. Different types of single coils have been dealt with and circuits have been given to show how two or more of these could be employed together. The principal difficulty in using a number of the coils, however, has been that a separate wave-change switch has been required for each, thus complicating matters to a certain extent. Fortunately, a new switch has lately been placed on the market by Messrs. Wilkins and Wright (of "Utility" fame) which is an excellent adjunct to the coils under discussion. The switch is a flat one, occupying a minimum of space and having an entirely negligible self-capacity, and it can thus be mounted alongside the coils without adding greatly to the space they occupy. This flat switch can be obtained in two or three different types, but the one which will be most useful in connection with our home-made coils is the three-pole shorting switch. The latter can be used for wavechanging on three ganged coils of the type normally requiring a push-pull switch for each, but

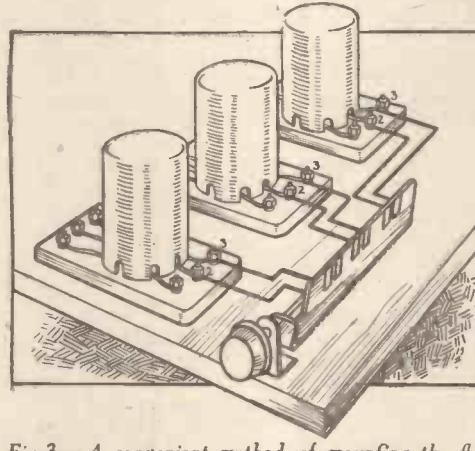


Fig. 3.—A convenient method of mounting the flat wave-change switch beside a set of coils.



Fig. 1.—A flat switch of the type referred to. The particular component illustrated is a 3-pole change-over switch.

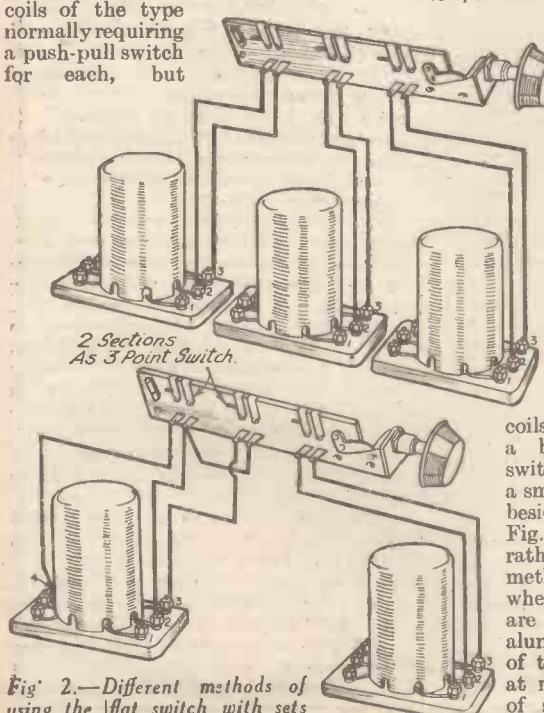


Fig. 2.—Different methods of using the flat switch with sets of the coils described in this series.

when one of the coils is of the kind requiring a three-point switch for wavechanging, a four-pole switch can be used to operate on three coils. A photograph of a switch of the kind referred to is given at Fig. 1, whilst various methods of connection for different coil combinations are clearly shown in Fig. 2.

Ganged Coils and Switching

A practical detail we have not yet considered is in connection with the method of mounting the flat switch. If all the coils are screwed directly on to a baseboard or chassis, the switch can easily be attached to a small component bracket fixed beside the coils, as shown in Fig. 3. Another and perhaps rather more "professional" method is illustrated in Fig. 4, where the coils and the switch are together mounted on an aluminium baseplate; the edges of the baseplate are bent over at right-angles to form a kind of shallow chassis on the underside of which the switch can

be mounted very neatly by means of a small aluminium bracket. The sketch will be self-explanatory, and it need only be added that the switch should always be mounted so that the connections to it from terminals on the coils are as short and direct as possible.

All-Wave Tuning

Coils for short waves, as well as for the broadcast bands, have been fully dealt with, but no information has yet been given in regard to employing a combination of broadcast and short-wave coils in an all-wave receiver. This is certainly a combination that is rapidly becoming more popular, and which has been proved (by the "All-Wave Two" and the "All-Wave Unipen," both described in PRACTICAL WIRELESS) to be thoroughly satisfactory and efficient. The circuit of a two-valve detector and low-frequency receiver is given in Fig. 5, where the two coils employed are the second to be described (illustrated on page 684, in Fig. 3) and the short-wave coil described on page 731. A flat switch of the type above referred to is used for shorting out a section of each coil, a separate three-point push-pull switch being employed for cutting out the broadcast coil entirely. This is a very convenient system of wavechanging, since the lower and higher band on either the short or broadcast ranges can be obtained by means of the ganged flat switch, whilst to change from broadcasting to short waves it is only necessary to pull out the knob of the three-point switch.

The circuit is so arranged that the

(Continued on page 800)

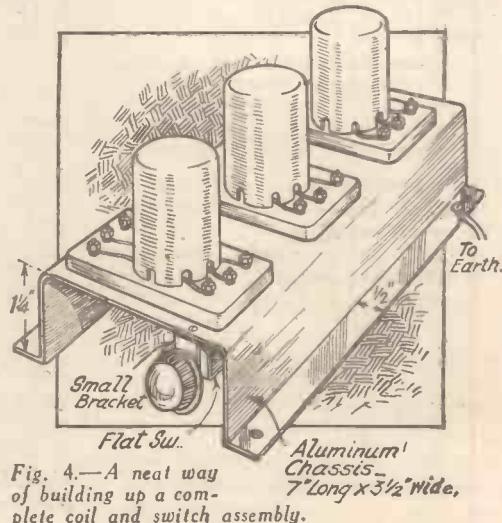


Fig. 4.—A neat way of building up a complete coil and switch assembly.

MAKING YOUR OWN SCREENED COILS

(Continued from previous page)

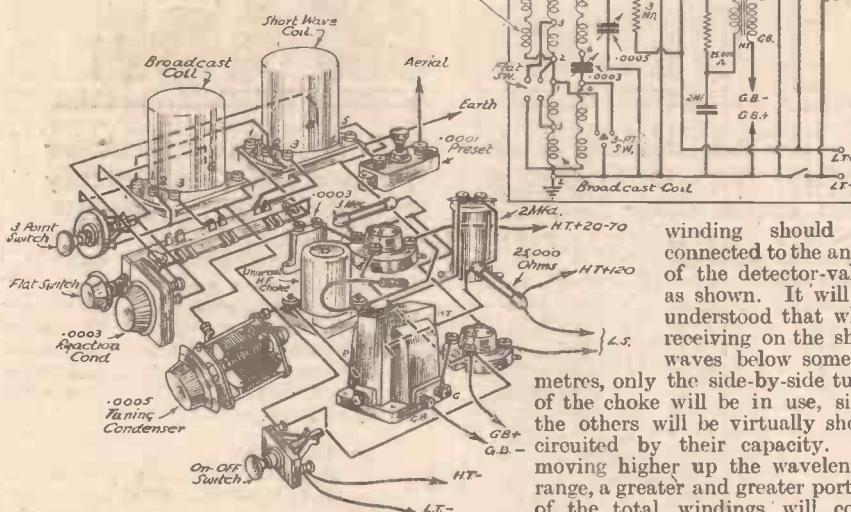


Fig. 5.—A useful all-wave two-valve circuit using two of the coils described.

reaction condenser comes between the two reaction windings, and because of this the moving vanes (which are connected to the spindle, of course) are at earth potential; in consequence, hand-capacity effects are not likely to be troublesome. A .0005 mfd. variable condenser is shown for tuning purposes, and this capacity is admittedly rather high for short-wave reception, although it is essential for covering the full band of wavelengths on the broadcasting ranges. So that tuning shall not be too critical a process, it is practically essential that the condenser should be provided with a reliable slow-motion drive. The reaction condenser is .0003 mfd., and although this is on the high side it is not likely that any great difficulty will be experienced in operating it; if it should seem rather "fierce," a smaller capacity can be tried. As a matter of fact, even a .0002 mfd. condenser will give reaction over the full range of wavelengths when a screen-grid valve is used for detection, as shown, but with medium-impedance triodes, such a capacity will be found rather too low to produce oscillation at the higher condenser readings.

A "Universal" Choke

A "universal," or all-wave high-frequency choke is shown, and most of the components sold under one or other of these names can successfully be used in this position. As an alternative, a short-wave and broadcast choke can be wired in series, connecting the short-wave component to the anode of the detector valve. Yet another method, and one which will be favoured by keen constructors, is to make the choke from similar materials to those employed for the coils. Constructional details of such a choke are given at Fig. 6, and it will be seen from this sketch that a small portion of the windings are arranged as side-by-side turns (for short-waves), the other portion being placed in slots formed by means of the dividing washers supplied with the coil former. There are 900 turns in all of 34-gauge d.c.c. or enamelled wire, and of these 25 are wound side by side, 50 are placed in the first slot, 105 in the second, and 180 in each of the remaining four. The "top" end of the

winding should be connected to the anode of the detector-valve, as shown. It will be understood that when receiving on the short waves below some 30 metres, only the side-by-side turns of the choke will be in use, since the others will be virtually short-circuited by their capacity. On moving higher up the wavelength range, a greater and greater portion of the total windings will come into use until, on long waves, the whole choke will be in action.

Points of Interest.

There are a few other practical points which should be dealt with before concluding this series. A reader wrote some days ago from Aberystwyth asking if it would not be better to use silk-covered wire in place of the d.c.c. specified in the previous articles. As reason for this question the reader said that he had been informed that cotton

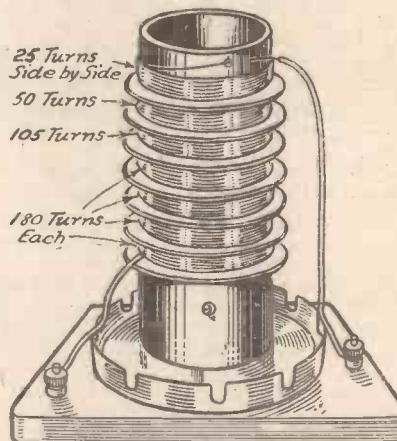


Fig. 6.—Details of an excellent all-wave or universal H.F. choke.

possesses some property which makes it unsuitable for coil winding. This is not quite true, although the reader had probably seen it stated at some time that cotton absorbs moisture rather easily, and when it becomes damp it is liable to act as a kind of high resistance short between adjacent turns. In practice, however, it is scarcely likely that the finished coil will be situated in a damp place where the moisture could produce an effect such as that mentioned. Should there be any danger of the coil being attacked by damp, it would be best to apply a thin coat of shellac varnish or melted paraffin wax to the windings. Here again we come up against a question that is often disputed—whether or not shellac and cotton produce a compound which attacks and corrodes the copper wire. There might be

something in the suggestion that copper is attacked in this way, but I have never found any proof of it. In any case, whether using shellac or wax, make quite sure that only the thinnest possible layer is applied, because it will increase the self-capacity of the finished coil and thereby reduce its efficiency to some extent.

The difficulty just referred to would, of course, be non-existent if enamelled or silk-covered wire were used for the windings. Enamelled wire was given as an alternative in the specifications in respect to all the coils described, and this is eminently suitable provided that care is taken in winding it to prevent adjacent turns rubbing each other and scraping away the enamel. If enamelled wire is used, the number of turns should, theoretically, be modified slightly, due to the fact that the inductance and self-capacity are changed. In practice, however, the difference is generally so slight that the correction factor need not be taken into consideration. The only point that should be considered is that the distance between the ends of windings should be the same as those mentioned and shown in the various drawings. And as enamelled and silk-covered wires are thinner than those with cotton covering, the medium-wave turns occupy a shorter space on the former. The same remarks apply to silk-covered wire as to enamelled, except that in this case there is no danger of the insulation being scratched.

There is a little point in regard to soldered connections that ought to be dealt with. Under no circumstances should acid or chloride be used as a flux in soldering fine wires, since if it is, the joints are almost sure to corrode sooner or later, when trouble will naturally be experienced. Perhaps the best flux of all is resin, because this is not only non-corrosive, but it leaves a protective layer over the joint and is not "messy" in use. Additionally, it is an insulator, so that if any should "splutter" when the hot soldering iron is applied, no harm can be done.

CHOOSING & USING RESISTANCES

(Continued from page 798)

R.10 is an L.F. volume control, and varies the amount of L.F. signal current passed from the transformer secondary to the grid of the output pentode. Its function is comparable to that of R.1, although low-frequency, instead of high-frequency, current is being handled. The maximum resistance should be considerably higher than the impedance of the transformer, or else there will be some loss in the way of high-note response. A good value for general use is 250,000 ohms, and the component may be either wire-wound or otherwise; the former type is liable to be a bit "noisy" when the control is in use, but the latter might—if not of very sound construction—be productive of crackling noises. As in the case of R.5, it is an advantage to have this resistance of the "graded" type so that the resistance variation near the "full-volume" (grid) end of the element is less than at the other end.

R.12 is for decoupling the priming grid of the pentode, and it also cuts down the voltage to a suitable figure; the method of deciding upon its value is similar to that employed for R.9. It should be added, however, that an average value is about 2,000 ohms, which serves to prevent the passage of low-frequency alternating currents without "dropping" the voltage.

FROM THE FLASH LAMP

"MICRO-MICRO-FARADS"

By "Photon"

THE capacity of a conducting sphere in infinite space is, in electrostatic units, defined as equal to its radius in centimetres. To avoid the use of the term "infinite" it is easy to interpret this by saying that *well in the open* the capacity of a conducting sphere is somewhat greater than its radius expressed in cm. This enables us in many cases to assess the capacity of a component or part of a component by mere inspection with sufficient accuracy to decide whether it is important, and to compute what its effect will be on the

Fig. 1.—A sphere whose capacity is 1 micro-micro-farad.

Fig. 2.—The capacity of a metal fitting can be estimated from the size of a sphere which will contain it.

circuit of which it forms a part, but the result being in centimetres means nothing to the ordinary man used to dealing with microfarads. The conversion factor fortunately is simple and easy to remember thus:—

One micro-micro-farad = 0.9 of an electrostatic unit, that is to say 0.9 of a centimetre. For ordinary purposes, especially if the equivalent sphere has to be guessed, it is sufficient to say that a capacity

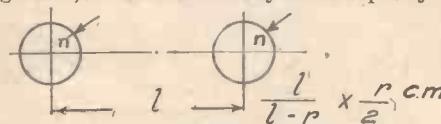


Fig. 3.—Two equal spheres at a distance l apart.

of 1 cm. is equal to 1 m.m.f. As an amusing example of this it may be remarked that the radius of the earth is a matter of 640 by 10^6 centimetres, and therefore on this approximate basis its electrostatic capacity is 640 microfarads only! What a paltry thing is our earth! More accurately the figure is 700 microfarads. As a practical application of this rule, the following examples are interesting. We can always make an *outside estimate* of the capacity of any metal fitting such as a grid-leak clip, or cap, or a terminal by describing around it the smallest sphere that will contain it, then the radius of that sphere in centimetres gives the capacity in m.m.f. Again, if we have to deal with an H.F. choke, we can approximate the end portions by imaginary spheres, and so assess the capacity. There is, however, one thing to guard against, capacities assessed in this manner are capacities between the part, or its equivalent sphere, and the surrounding earthed metal work, as for example, the screening or other metal panel. This means that the capacity may be greater than given by the estimate, but unless the space is exceptionally cramped the error will not be substantial. The method is capable of refinement without much complication. For example, if there are two equal spheres at opposite

potential widely separated the capacity between them (one + and the other —) is half that of a single sphere, or if separated by a distance l (centres) the capacity of one

$$\text{to the other is } \frac{1}{l-r} \times \frac{r}{2} \text{ cm.}$$

Some Examples

In conclusion a few examples are given in Figs. 1, 2, 3, 4 and 5. Fig. 1 represents a sphere whose capacity in the open = 1 m.m.f. Fig. 2 is the simple case of a metal fitting supposed to be far removed from earthed surroundings, a limiting figure being given by the radius of the containing sphere, as drawn. Fig. 3 is the case of two equal spheres distance l apart, Fig. 4 is the case of a single sphere at a distance = $l/2$ from an earthed boundary wall. Fig. 5 shows the manner in which it is possible to estimate the capacity of a choke coil; here, however, if the dielectric is in part solid, such as ebonite, the capacity will be greater than for a naked winding. This may be assessed knowing the value of the specific inductive capacity K . For ebonite $K=2.8$ to 2.9; there appears to be no suitable material available with a lower value.

It often happens that in putting up or remodelling a set one or more condensers of small capacity are found to be required, it is far easier to make such condensers than to buy them, and it costs less. If C_{11} stand for the capacity in m.m.f.


$$KA = \frac{C_{11}}{11.3} \text{ b}$$

where A is area in cm.^2 ; b is thickness of dielectric in cm. and K is the specific inductive capacity. In air $K=1$.

Two examples will suffice. If the dielectric is air, and the thickness $b = \frac{1}{2}$ mm. = .05 cm. Then one m.m.f. will require an area:—

$$A = 11.3 \times .05 = .565 \text{ cm.}^2$$

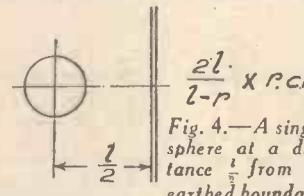It should be noted that $\frac{1}{2}$ mm. is about the usual air gap in a variable tuning condenser, hence for a condenser of .0005 m.f. (=500 m.m.f.) about 280 cm. 2 is required. A sample measured was found to have vanes of 14 cm. 2 area and 20 dielectric



spaces which is in perfect agreement.

If the dielectric be mica the value of K may be taken = 5. A usual thickness of mica is $2\frac{1}{1000}$ inch or .008 cm. Hence area required for one m.m.f.

$$A = \frac{11.3 \times .008}{5} = 0.18 \text{ cm.}^2$$

In building up small mica condensers it is convenient to use copper foil rather than tin foil. The copper foil should be as thin as procurable.

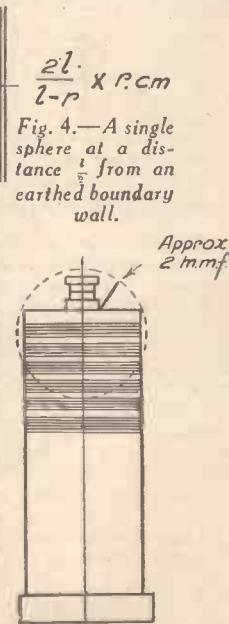


Fig. 5.—Illustrating the method of estimating the capacity of a choke.



... again the SOLE Specification

ROLA

FR6 - PM - 22 - Class B
(39/6)

is solely specified for the
NUCLEON CLASS B FOUR

Whenever the highest quality and the most impressive volume are required, makers and "constructor set" designers alike turn instantly to Rola to satisfy their requirements. And Rola has never let them down. For realistic reproduction Rola speakers are in fact as well as name "the World's Finest Reproducers."

ROLA

the World's Finest Reproducers



ROLA CLASS B SPEAKER AMPLIFIER UNIT

Fitted in 5 seconds to any battery receiver, this remarkable unit will increase its volume and sensitivity at least 5 times. Ask your dealer to demonstrate. PRICE 57/-.


THE BRITISH ROLA CO. LTD.,
Minerva Road, PARK ROYAL, N.W.10.

'Phone: Willesden 4322-3-4-5-6.

ROLA
SPEAKERS

for better
Radio Reception



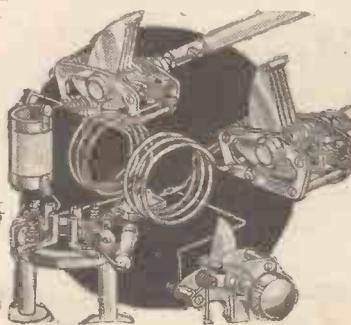

Short Wave Section

THE LESSER LOGGED SHORT

WAVERS

By E. THURWAY

CONDITIONS are now proving very favourable for the capture of distant transmissions on short waves, and daily reports are being received of the logging of stations of which signals had not been tuned-in for several months. Generally speaking, most of the short-wave transmitters can be classed under two separate headings in our lists, namely, those we can pick up at almost any period of the year, and those for which only a useful search can be made during certain months. As a rule, amongst the former may be found most Europeans, a number of North Americans and, to a certain extent, Australians, such as Sydney VK2ME; in addition, we can also look forward to hearing such stations at Nairobi, Bandoeng, and a few others from the East. In January especially the following guide will be found useful, as it gives the various times at which we may expect to hear broadcasts from the different quarters of the globe.

From midnight onwards to roughly 6 a.m. is the favourable period for East Coast and mid-west North Americans, and for stations situated in the Argentine, Brazil, Mexico, and so on, in the 30-50 metre band; from 6 to 9 a.m. you may expect to log Australian calls, as well as broadcasts from the American Pacific coast. Starting again towards midday, the 16 to 25-metre band should be searched, such broadcasters as W3XAL, Bound Brook, and the Dutch stations at Bandoeng usually coming in at that time; also Europeans working on channels between 19 and 32 metres. Again, from 5 to 8 p.m. we can try for India, South Africa, Kenya Colony (all included in 30-50 metres), or in the immediate lower band for North America, then until midnight in the wave-lengths ranging from, say, 35-70 metres and above.

If, as I assume, this is not your first attempt at listening to short-wave transmissions, you will have already secured the dial readings of some of the more better known or more powerful broadcasters, possibly in different sections of the wave band; if such is the case, it will help you greatly to narrow down your search for other wanted transmitters, as the loggings will give you a landmark for the various dial degrees at which to start. Casual twirling of the condensers is usually very disappointing, as tuning on the short waves must be very accurate, and consequently it is an easy matter to pass over a number of signals which very careful and slow moving of the dial would have caught.

European Wavelength Alterations
Before giving you details of a number of new stations, now being heard, let me mention a few alterations in some of the regular Europeans. Poznan (Poland), which had closed down temporarily when my last notes were published, is again on the air on Tuesdays and Thursdays at G.M.T. 17.30. The wavelength at present is slightly higher than hitherto, namely,

31.63 metres (9,485 kc/s). Jeløy, which relays the Oslo broadcasts, is now working on 42.92 metres (6,990 kc/s), on which channel it is providing both excellent quality and exceedingly loud signals. You will hear on this wavelength the usual musical-box signal usually associated with the Oslo entertainments in the higher broadcasting wave-band. Vienna (UOR2) on 49.41 metres (6,075 kc/s) has also resumed its tests on Tuesdays and Thursdays, and may be picked up at odd hours between G.M.T. 13.30 and 21.00. There is no change to report in the time schedules or frequencies of the British, French, and German transmitters.

The station used by the Technical College of the University of Bucarest, which had not been logged for some months, has been overhauled and now operates on 45.5 metres (6,593 kc/s) at slightly increased power. The best time to make the search is on Sundays from G.M.T. 15.00. It may be identified by the fact that the studio possesses a woman announcer and that the call frequently given out is *Radio Romania*.

OXY, Skamblebaek, after trying out a few channels around 49 metres, seems to have settled down again on 49.4 metres (6,075 kc/s); through this station you may get an excellent reception of the Copenhagen programmes.

In the 49-metre Band

Now for the lesser logged foreigners. In the 49-metre band we find several, but it will repay you to devote some time to the capture of La Paz (CP5), Bolivia, on 49.3 metres (6,085 kc/s), which is a daily transmitter between G.M.T. 00.30 and 04.30; the station also uses an alternative channel for its daylight broadcasts, namely, 19.61 metres (15,295 kc/s), which should be picked up between G.M.T. 16.30 and 17.30.

Barely two or three kilocycles above the former wavelength between midnight and 01.30, you may come across a Canadian call: VE9BJ, St. John, New Brunswick, a privately owned station which does not fail to mention its owners (C. and A. Munro); gramophone records are broadcast as well as a news bulletin.

Working up higher, if you hear Spanish and English announcements, you should stand by to secure identification, as CMCI, Marianao (Cuba) is on the ether daily from about 22.00; it is a powerful station on 49.5 metres (6,060 kc/s), of which the signals have already been logged in the British Isles. W4XB, on 49.67 metres (6,040 kc/s), the short-wave relay of WIOD, Miami Beach (Fla.) is also a possible and equally deserves a careful search.

Exploration of the 50-75 metre band, beginning with the powerful Moscow station, on most nights will bring good results; it is a mistake to believe that all the broadcasters work on the lower channels. A few evenings spent in this direction will amply repay your trouble. HJ4ABE,

Medellin (Colombia) on 52.17 metres (5,750 kc/s) works from 00.30-04.00 on Tuesdays, and from 23.30-01.00 on Thursdays and Saturdays; also on other days from 16.00-05.00. Another South American, HCJB, Quito (Ecuador), I am informed, has changed his wavelength to 73 metres (4,110 kc/s) and operates every night from 01.15-02.45; the calls are in Spanish and English and the interval signal a two-tone chime.

Transatlantic and Other Distant Stations

A few metres above this channel you will find a welter of Dutch, French, and other amateur transmitters (75-85.7 metres), which at times provide items of interest. Working down, you will pass through the channels used by the International Service of Criminal Police, e.g., HAP2, Budapest, on 72.09 metres, and by the transatlantic and other liners (71.82 metres). There are many degrees of the condenser dials on which you will wish to spend a little time, as most of them represent busy commercial or other channels.

Landmarks, as already stated, in the form of detailed logged condenser readings, are indispensable to the short-wave enthusiast. In every instance they will provide a quick jumping-off point and save considerable delay and worry. They also permit, by comparison, if a wavelength is not available, a fairly good estimate of the wavelength on which a transmission has been tuned in. Should you have found W8XK, East Pittsburgh, one of the KDKA pioneers, on 48.86 metres—it is on the air nightly—work up very slowly, degree by degree—when you will probably capture YV3BC, Caracas, on 48.92 metres (6,132 kc/s), the relay of the medium-wave broadcasting station in that city. From G.M.T. 21.00-02.00 on week-days is the most favourable period; on Sundays at that time the transmissions are carried out on 31.56 metres (9,510 kc/s). In the call you will hear a reference made to the *Radio-difusora Venezolana*. A further Venezuelan station, namely, YV11BMO, situated at Maracay, operates on 48.95 metres (6,127 kc/s). You may distinguish it from the previous one by the fact that it announces itself as the *Broadcasting Company of Caracas*; a man presides at the microphone.

Finally, reports have been received respecting two new Russian 500-watt transmitters, RNZ and RTL, respectively, on 62 metres (4,839 kc/s) and 54.74 metres (5,480 kc/s). They are situated in Kamtschatka.

Exploring the ether with a good short-wave receiver to-day provides a fresh interest in radio; moreover, it permits its owner to hear transmissions which are not vouchsafed to him in the ordinary broadcast band.

THE WIRELESS CONSTRUCTOR'S ENCYCLOPÆDIA

(2nd Edition)

By F. J. CAMM
(Editor of "Practical Wireless")

THIS invaluable encyclopædia is written in plain language by one of the most accomplished designers and writers on wireless construction. The whole subject is fully covered, and the volume is remarkable for the number of practical illustrations it contains.

No matter in what branch of radio you are interested, you will find everything adequately dealt with here.

Obtainable at all Booksellers, or by post 5/- from Geo. Newnes, Ltd., 8/11, Southampton Street, Strand, London, W.C.2.

5/-

RADIO RAMBLINGS

By JACE

Gottings from my Notebook

Loosely-Fitting Coil Covers

THERE is a point regarding tuning coils which is worth mentioning. I refer to the fitting of the covers of the "canned" type. Sometimes these do not fit at all tightly. This may not at first appear to be a very serious fault until we remember that the position of the cover affects the tuning range. This means that, in the case of ganged circuits, any movement of one of the coil covers is liable to upset the ganging. Of course, some coils have the covers held firmly in place by means of a nut on top. A simple safeguard of this nature is really all that is necessary.

Sometimes the covers fit fairly well, but tend to move when operating the wave-change switch incorporated in the base of the coils. I came across an example of this in a set of three coils mounted on one base with the switches linked by a rod in the popular manner. Every time the switch knob was turned the three covers wobbled from side to side!

"Intermittent" Rating of Accumulators

I SHOULD also like to give two suggestions concerning accessories. The first concerns the rating of accumulators. Could not the out-of-date and misleading "intermittent" rating be discontinued? It was based on the purely arbitrary assumption that an accumulator used to work a trembler coil, as for motor ignition or similar purposes, would last twice as long as when on continuous discharge. Under this system an accumulator capable of delivering 10 ampère-hours of electricity would be marked "20 amp.hrs.int." or "20 a.h.i." Often, however, the "int." is omitted and the purchaser is led to believe that he has a 20 amp.hrs. battery whereas, in reality, it is only of 10 amp.hrs. capacity. Of course, if it is stamped "20 amp.hrs. actual" there can be no mistake, but, as it is, a rating of 20 ampère-hours without any other qualification may mean either of two figures. If the intermittent system were abolished there would be no possibility of ambiguity.

Battery Cords

THE other suggestion I should like to make is that portable and such like receivers could be considerably cleaned up and at the same time made more fool-proof by eliminating most of the battery cords. Instead of using wander plugs, the H.T. and G.B. batteries would be fitted with brass contacts or clips somewhat similar to pocket-lamp batteries. All that would be needed when renewing a battery would be to slide the old one out and slip a new one in. The brass contacts would automatically connect with corresponding ones inside the case. This arrangement would make battery changing easier besides eliminating the possibility of plugging-in to the wrong sockets.

The batteries would have to be standardized as regards shape and size and would be fitted with a number of brass clips in place

of the sockets used at present. The contacts inside the set would be in the form of spring-loaded plungers and placed so as to register with the clips on the battery which gave the appropriate voltages. Of course, each battery clip would be provided with a socket as well so that the battery could still be used in the orthodox manner with sets employing wander plugs.

Whistling in the Dark

I WAS privileged recently to witness a performance of *Whistling in the Dark*, a gangster play on American lines produced at the Comedy Theatre. The plot in brief is this: A dope and bootlegger gang are anxious to "bump off" an undesirable official who is in their way. An unsuspecting novelist, looking out for quiet retreat, happens upon them and asks to be allowed to look over the house. Amusing incidents result in his being held prisoner by the gang until he has produced a plan, on thriller lines, of the perfect crime which said gangsters can apply to aforesaid official. As a writer of crime stories the novelist here applies his imagination and produces a workable scheme. The play continues through amusing efforts on his part to warn the victims of his plot. Eventually he converts the radio set into a two-way system of communication with the telephone exchange, the gang having disconnected and removed the telephone. This part of the play was well done, and it is the first time, so far as I am aware, that radio has been used as a theatrical property in this way. The play is well acted, and I particularly liked Miss Billie Riccardo's acting as the eloping bride-to-be of the novelist. I had seen this actress only once before in the revival of *The Belle of New York*, in which she daintily played the part of Fifi with grace and distinction.

Siemen's Full o' Power Batteries

IT is always interesting to learn something about the construction of the apparatus or accessories which we use in conjunction with our radio sets and generally accept as a matter of course.

I have just been given some very interesting information concerning the Full o' Power Radio Battery which is claimed to be entirely distinct in construction to other types of dry batteries. Most of us visualize a dry battery as consisting of the type with a "dolly" wrapped with fabric surrounded with a moist paste or jelly electrolyte in an outer zinc container with soldered seams. In the Full o' Power Battery, however, the made-up "dolly" is dispensed with, a special manganese mix being compressed directly into the zinc container which, in this case, consists of a one-piece seamless cup pressed out from zinc sheet of heavy gauge. The zinc cup is thus perfectly leak-proof. It is most important to observe, however, that the manganese mix is not permitted to come into direct contact

with the zinc, an insulated lining of very thin but tough paper being inserted into the zinc cup before the manganese mix is compressed into it. By this method it is possible to compress approximately 20 per cent. more active materials into the Full o' Power cell with a consequent increase in its life.

OLD COMPONENTS IN NEW CIRCUITS

(Continued from page 780)

Many amateurs whose experiments were commenced several years ago will have a 400-ohm potentiometer lying about. This was probably used to vary the potential applied to the detector grid through the grid-leak, but it can now be employed as an automatic grid-bias resistance in the L.F. circuit. The method of connection is perfectly simple, as can be seen from the sketch given at Fig. 5. The lead which was previously connected to the negative H.T. wander plug is now joined to one side of the potentiometer, whilst the other side is taken to the G.B. negative terminal and to the negative wander plug on the high-tension battery. In order to prevent instability a fixed condenser is connected in parallel with the potentiometer. The condenser shown is a 25 mfd. electrolytic one, this being most suitable, but if such a condenser is not readily available, an ordinary 1 or 2 mfd. one will make a good substitute. A correct value of bias for some types of valves can be obtained by varying the slider of the potentiometer, but the maximum resistance available will be too low for valves of other types, and in such cases it will be necessary to include a fixed resistance in the lead between the potentiometer and H.T. negative; this is shown by broken lines in Fig. 5. In any case the actual resistance value required can be found by dividing the grid-bias voltage required by the valve at maximum anode voltage by the anode current taken under the same conditions, and multiplying by a thousand. All the figures required for the calculation can be obtained from the makers' instruction sheet. An example will remove any difficulty in following the above statement; for the moment consider the Cossor 220 P.T., which requires 9 volts G.B. and takes 23 milliamps high-tension current. The bias resistance required is 9 divided by 23 and multiplied by 1,000, or 391 ohms. Suppose the valve in use had been a Cossor 215P, which requires a G.B. voltage of 7.5 and consumes 10 millamps anode current, the bias resistance necessary would be 750 ohms, and therefore a fixed resistance of about 500 ohms could be wired in series with the potentiometer and the optimum setting of the potentiometer slider found under working conditions.

Scratch Filters

It frequently happens when using a pick-up that needle scratch is troublesome and some kind of filter is desirable in order to eliminate it. Scratch filters can be bought, but those who are still in possession of a set of plug-in coils will be pleased to know that one of these—having between 1,000 and 2,000 turns—may be used in conjunction with a small pre-set condenser as an excellent filter. The connections are shown in Fig. 6, and these are self-explanatory. It need only be pointed out that the pre-set condenser should be adjusted until needle scratch becomes inaudible or is reduced to its lowest volume level.

FACTS & FIGURES

Components tested in our Laboratories

BY THE PRACTICAL WIRELESS TECHNICAL STAFF.

BRITISH RADIOPHONE PERFECTION SEVEN

BRITISH RADIOPHONE, LIMITED, announce that they are shortly releasing a free blue print of an ingenious seven valve superhet receiver in which their well-known Radiopak is employed. The circuit arrangement employed is of the single H.F. separate, oscillator type, and a metal rectifier (or cold valve) is employed for second detection and a separate similar rectifier for delayed automatic volume control purposes. An output stage of the pentode type is used to deliver an output of slightly over 1 watt. The blue print gives full constructional details and a list of recommended accessories, and we hope to have an opportunity of testing a complete receiver built to the specification in the near future. A point of interest for the more technical-minded reader is the choice of a frequency of 117.5 kc/s as an intermediate frequency in place of the more orthodox 110 or 126 kc/s. The chart may be obtained free from British Radiophone, Ltd., Aldwych House, Aldwych, London, W.C.2, or from your local dealer.

TESTING MULTI-PIN VALVES

USERS of the Six-Sixty valve and set testers will have probably found that it is a rather difficult matter to test the new multi-pin valves in these testers. The same point applies to all users of testers in which the standard type of holder for a valve is fitted. The Six-Sixty Valve Company have now issued an interesting pamphlet which gives the following useful information for using the testers with the latest type of valve. They advocate the mounting of 7-pin valveholder of standard type on a suitable small baseboard and suggest that a flexible lead should be joined to each of the terminals. A plug should terminate the leads, and this should be of a type suitable for plugging into the existing valve sockets on the tester. The valve to be tested is then inserted in the 7-pin holder and the appropriate leads are plugged into the socket of the valveholders on the test panel as indicated below.

Battery H.F. pentodes are tested as normal S.G. valves. Battery Class B (each half tested separately): B to 7; C to 9; D to 8; and E to 10.


Mains H.F. pentodes: B to 12; C to 11; D to 13; E to 15; F to 16; G to 15; and top cap to 17.

Mains duo diode triode: D to 8; E to 10; F to 11; G to 9; and top cap to 7. This test is for triode section only. The diodes will fail when cathode emission fails, a fact which will be revealed by the triodetest above.

Mains single diode tetrode: B to 12; C to 14; D to 13; E to 15; F to 16; and top cap to 17.

Mains duo diode pentode: B to 12; D to 13; E to 15; F to 16; and top cap to 17.

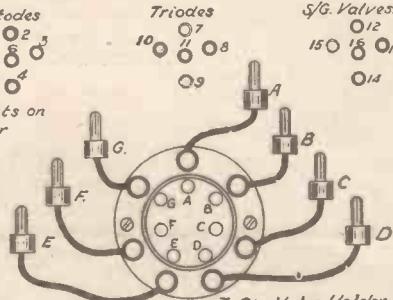Mains output pentode: B to 2; C to 1; D to 3; E to 5; F to 6; and G to 4.



The connection for an additional valve-holder for testing Multi-pin valves on the Six-Sixty and similar test sets.

tone, and the upper notes coming out in a crisp manner without squeakiness. At 10s. 6d., complete with dustbag, this is a line which no reader should pass by. A Class B model is available at 22s. 6d.

MAGNUM COMPONENTS

A MONG recent new Magnum components are the H.F. choke and the two-gang condenser. The former is wound with high-grade copper wire on a slotted ebonite former. A high inductance with a low self-capacity is obtained, and the choke is suitable for use in the anode circuit of a S.G. valve, or for simple reaction purposes. The component is designed for one-hole fixing, and terminals are provided for ease of connection. The price is 2s. 6d. The two-gang condenser incorporates two of the .0005 mfd. magnadensers, together with a Magnum slow-motion drive, and an independent drive is provided for trimming purposes. Both drives are positive and non-slipping, and the dial is calibrated 0 to 100, or, if desired, in wavelengths for use with Magnum coils. The price of this unit is 10s. 6d., and, if desired, a grey cellulose cover may be obtained for an additional 1s.

BUILDING THE NUCLEON 4

(Continued from page 786)

of the small fixed condensers having to be accommodated near to their respective associated components instead of being disposed below the surface. However, it is not possible to have things both ways, and, therefore, the difficulty of wiring and other drawbacks of the "one-side layout" must be contended with.

Construction

Before commencing construction the various components should be placed on the baseboard exactly as shown in the Wiring Diagram, Fig. 6, and not until every part has been found to be exactly in place should the fixing screws be driven home. It will be found most convenient to leave the tuning condenser until last, and to fit only the valveholders and the fixed condensers at the outset, the various interconnecting wires being put in as the assembly progresses. If the whole of the components are mounted first, it may be found by some constructors that the wires to the filament terminals of the valveholders, for instance, are impossible to connect. When the valveholders have been wired the transformers may be mounted and then the terminal strip at the rear. The leads to the terminals should be fitted, and then the three coils mounted in the space provided. Care must be exercised to get these in the correct positions, as it will be noticed that two of these are for the band-pass tuner and the third has entirely different connections. If they are reversed on the baseboard the receiver will not function. Coil TG is nearest the panel, and coil BP2 is the centre one.

The Panel

Now drill the panel, using the dimensions in Fig. 2 as a guide, and marking out the window from the template supplied with the drive. To cut this out a fretsaw may be used, or a number of small holes may be drilled all round the edge of the opening and the central piece of ebonite then broken out. It will not be necessary to file the opening smooth if the hole is made slightly larger than that recommended on the template. Mount the escutcheon and the other panel components, and then attach the leads to the reaction condenser, potentiometer, and switch. Place the panel in position and fix the retaining screws, after which the remaining wires may be fitted into position. It will be seen that in many cases soldering has been resorted to in order to make quite certain of good connection, but there is no reason why the task of building should be shirked on this account, as soldering is a really simple job, and, as has already been mentioned many times in these pages, the principal point to bear in mind is cleanliness. If the iron is used when it is really hot and the work is clean the solder will run quite freely, and a really sound connection will result.

PRACTICAL LETTERS FROM READERS

The Editor does not necessarily agree with opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

A Very Useful Little Set

SIR,—I received the PRACTICAL WIRELESS Kit of Tools safely, with which I am delighted. They are a very useful little set, and are well worth the money. I am a regular reader of your valuable paper, so I also have the set of spanners and drill gauge. Every success to PRACTICAL WIRELESS.—F. HANDS (Burton-on-Trent).

"Time Constant"

SIR,—In the December 2nd issue the term "time factor" is mentioned in Photon's article, "The Subdivision of Copper." I would be grateful if you would tell me in plain words:

1. Where the question of time comes in?
2. The importance of the "time factor."
3. And physical explanation of the term.

In reading an article on electric instruments I came across "Maximum time factor." What does this mean?—M. NEIDLE (London, S.E.).

[Firstly it would appear that when you mention "time factor" you are misquoting from the article in which the term used is "time constant." The time constant is a term used in electrical engineering to denote the relation between L the inductance, and R the ohmic resistance of a circuit, but it is also applied to circuits having a capacity and resistance in which the time constant is:

C X R

More generally it applies to any physical change, whether electrical or otherwise, which follows the logarithmic law. For example, when an E.M.F. is applied to a circuit that comprises a resistance only the current rises immediately to a value = V/R. If there is an inductance also in circuit the current rises logarithmically, ultimately reaching the same value V/R, but the initial rate of rise is determined by the inductance only and the time constant is the time which would elapse if this initial rate of rise were to continue till the value V/R is reached. The actual current flowing after that period of time is approximately two-thirds of the full value V/R.]—ED.]

A Wonderful Kit.

SIR,—I wish to take this opportunity of thanking you for your wonderful Pocket Tool Kit. One look at these tools is enough to convince anyone that they are made to stand the test of time. PRACTICAL WIRELESS will also stand this test, because it is always kept up to a high standard.—G. BAILEY (London, N.).

"Proud To Own Such a Set"

SIR,—Thanks very much for the Tool Kit just received. Such a kit was, you may be sure, scrutinized severely, and as a practical man I have not the slightest hesitation in stating it is (in my opinion) a kit of the essential tools every amateur constructor should possess. I am proud to own such a kit, and urgently urge others to write you for one.—F. O'C. COOPER (Dover).

"Remarkable Value for the Money"

SIR,—I beg to acknowledge receipt of my Tool Kit, and I must say that it exceeded

all of my expectations. The gift is like PRACTICAL WIRELESS, remarkable value for the money.—R. TAYLOR (Churt).

"A Wonderful Volume"

SIR,—I have been a regular reader of PRACTICAL WIRELESS since the first edition, and I think it is a very good wireless magazine for beginners and experts alike. I also wish to thank you for your "Popular Mechanics Encyclopaedia," which I have just received. It is a wonderful volume, and will be most useful to me.—G. ALLAN (Forest Gate).

"Exactly What Is Required"

SIR,—I should like to take this opportunity in wishing your paper every success. I consider that it is about the best weekly wireless periodical that I have read since about 1922. No, I have not been a reader since No. 1 issue, but that I regret. However, I consider that your gift Tool Kit is exactly what is required by a person who spends nearly all his time at the experimental bench.—G. BARTHOLOMEW (Bulford).

"The Ideal Tool Kit"

SIR,—I must write and thank you for the really first-class Tool Kit which arrived O.K. It is the ideal kit for the wireless enthusiast.—J. E. BISHOP (London, W.C.).

CUT THIS OUT EACH WEEK

DO YOU KNOW?

—THAT whilst indirectly-heated valves are warming up, the primary of an L.F. transformer is unloaded.

—THAT the above point explains the cause of hum when first switching on a mains receiver.

—THAT it is not possible to convert an inductive condenser into a non-inductive condenser by external means.

—THAT, generally speaking, it is not possible to use A.V.G. in a D.C. mains receiver unless a simple inefficient circuit is employed.

—THAT a whistle which accompanies loud-speaker reproduction, and which stops when the grid of the output valve is touched, denotes L.F. instability.

—THAT the simplest cure for the above is to reverse the connections to one of the L.F. transformer windings.

—THAT instability can be caused by the vibration of the vanes of a tuning condenser.


—THAT an H.F. choke may be wound on a tapered former to improve its characteristics.

—THAT a sectional-wound choke, with small sections at either end, acts in a similar manner to the above type.

NOTICE.

The Editor will be pleased to consider articles of a practical nature suitable for publication in PRACTICAL WIRELESS. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, W.C.2.

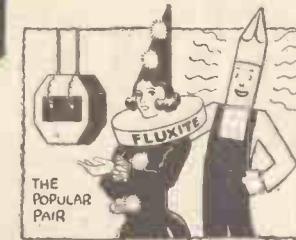Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.



"We're Fluxite and Solder—For Wireless RECEPTION
the reliable pair! we've done our share
Famous for Soldering—So NOW we're announced as
known everywhere! THE POPULAR PAIR!"
See that Fluxite and Solder are always by you
—in the house—garage—workshop—anywhere
where simple, speedy soldering is needed.


ALL MECHANICS WILL HAVE FLUXITE

IT SIMPLIFIES ALL SOLDERING

All Ironmongers sell Fluxite in tins : 4d., 8d., 1s., 4d., and 1s. 8d. Ask to see the FLUXITE POCKET SOLDERING SET—complete with full instructions—7s. 6d. Ask also for our leaflet on HARDENING STEEL with Fluxite.

FLUXITE, LTD.
(Dept. W.P.), ROTHERHITHE, S.E.16.

FOR ALL REPAIRS!

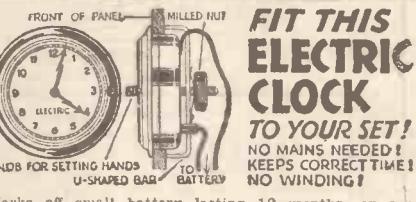

FIT THIS ELECTRIC CLOCK

TO YOUR SET!
NO MAINS NEEDED!
KEEPS CORRECT TIME!
NO WINDING!

Works off small battery lasting 12 months, or can be plugged into G.B. battery without affecting reception. Uses practically no current. Fits into hole 3½ in. dia. in any panel up to ½ in. thick. Easy to fix—no screws required. Only ½ in. from front of panel to back of case. Swiss movement. Hands set from front. Nickel-plated bezel. Useful addition to any set.

RIVERSIDE MFG. CO., LTD.,
Dept. 21, Crisp Road,
Hammersmith, W.6.
Telephone: Riverside 6392.

12/6
COMPLETE WITH BATTERY
POSTAGE 6D

PLASTAPE

The "Modern Aerial"
for the
Modern Set

AMPLION (1932) LTD.

AERIALS, EARTHS
EXTENSION
WIRES

END H.T. WORRIES ONCE AND FOR ALL

Thousands of listeners have proved the Standard Leclanche Battery a paying proposition. Gives abundant pure current year in year out, at half cost of dry batteries. Does away with constant replacements and poor results. Always up to voltage, regardless power when not in use. Annual replenishment all that is necessary. J. M. of Edinboro' writes: "Have used this battery for last five years and found it good and superior to dry batteries." 120V, 12,500 m.a., £2 complete, car. paid. Write for details.

ALL STANDARD BATTERY SPARES SUPPLIED.
THE WET H.T. BATTERY CO. (Pr.),
26, LISLE STREET, LONDON, W.C.2. Gerard 6121

EASY PAYMENTS

"There's no place like HOLMES."

The first firm to supply Wireless parts on easy payments. Nine years advertiser in Wireless Press. Thousands of satisfied customers.

EPOCH SPEAKERS

Monthly Pay-

	Deposit.	ments,
SUPER DWARF	23/6	4/4
20th Century	35/-	4/10
11in. SUPER	45/-	4/11
B5.P.M.	84/-	7/8
		11 of 10/8

Lissen Skyscraper	4	112/6	10/-	11 of 10/3
TELSSEN 325 Star Kit	39/6	5/5	7 of 5/5	
EXIDE H.T. Accum.				
120v.	60/-	6/-	9 of 6/8	
BLUE SPOT 29PM.	32/6	4/5	7 of 4/5	
ATLAS ELIMINATOR.				
No. G245	59/6	5/-	11 of 5/6	
B.T.H. Pick-up	21/-	3/10	5 of 3/10	
Parts for any Kit Set.				
All make of Speaker.				

New Goods Obtained for Every Order. Send us a list of the parts you require and the payments that will suit your convenience, and we will send you a definite quotation. Anything Wireless.

H. W. HOLMES, 29, FOLEY STREET,
Great Portland Street, London, W.1.

Phone: Museum 1414.

EPOCH CLASS 'B' ADAPTOR

If you already have a moving-coil speaker and wish to incorporate Class "B" amplification, the EPOCH Class "B" Adaptor is ideal for your purpose. It converts your set to Class "B" without any alteration whatever.

SEND ONLY 5/-; if satisfied pay further 5/- at once, then 8 monthly payments of 5/- (Cash in 7 days, 45/-). Supplied complete with Class "B" Valve.



E. J. HERAUD, Ltd. (Dept. P.40),
NUMBER ONE, EDMONTON, LONDON, N.18
Satisfaction or Money Back Guaranteed.

EASY TERMS PROMPT DELIVERY

Any Amplion, Blue Spot, Baker, Celestion, Epoch, R. & A. Rola, Sonochord, Grampian, Igranic, Lamplugh, Magnavox, Ormond, W.B. or Ferranti Moving Coil Speaker Supplied.

Send 5/- only

and pay the balance by monthly instalments. No references. Entirely private and confidential.

KITS, PARTS, SETS, ELECTRIC CLOCKS ON EASY TERMS.

Write for Catalogue and state requirements.

TURNADGE AND PARTNERS, LTD.
Ludgate House, Fleet St., London, E.C.4.

Telephone: Central 1903.

OSBORN RADIO CABINETS CHEAPER & BETTER

CHAS. A. OSBORN

SOLE MANUFACTURERS OF OSBORN RADIO CABINETS

1933

CATALOGUES RECEIVED

To save readers trouble, we undertake to send on catalogues of any of our advertisers. Merely state, on a postcard, the names of the firms from whom you require catalogues, and address it to "Catalogues," PRACTICAL WIRELESS, Geo. Neuner Ltd., 8/11, Southampton St., Strand, London, W.C.2. Where advertisers make a charge, or require postage, this should be enclosed with applications for catalogues. No other correspondence whatsoever should be enclosed.

MULLARD H.F. PENTODES

CONSTRUCTORS contemplating the use of screened (H.F.) pentodes in their next receiver should obtain a copy of a new Mullard leaflet on these valves which has just been issued. The special properties of the screened pentode are fully described, and are followed by full operating data and characteristics, with curves of the two Mullard types—V.P.A. and S.P.A.—and practical operating hints for using these valves in modern circuits.

EELEX SHORT-WAVE CONVERTERS

THE problem of getting a short-wave superhet type converter to work with superhet receivers has been effectively solved by J. J. Eastick and Sons who have produced a range of compact converters of single and two-valve types, the two-valve models having an extra stage of amplification. The converters are suitable for all types of broadcast receivers which are designed for reception above 1,000 metres. The wavelength range of the converter with the standard coil supplied is 15-60 metres, although this range can be increased to 120 metres by means of an additional coil. Booklets containing full particulars can be obtained from the above-mentioned firm at 118, Bunhill Row, London, E.C.1.

THE ALL-METAL WAY, 1934.

THIS is the title of an attractive handbook dealing with the construction of H.T. battery eliminators and battery chargers embodying Westinghouse metal rectifiers. The book, which is primarily of interest to home constructors who prefer to build their own apparatus, deals fully with rectification, battery eliminator problems, mains conversion, and battery charging. There is also a section devoted to Westectors and their uses in various circuits. The book is well illustrated with diagrams which should be very useful to the home constructor. Copies of the handbook can be obtained for 3d. each, post free, from The Westinghouse Brake and Sash Signal Company, 82, York Road, King's Cross, N.1.

RADIO CLUBS AND SOCIETIES

Club Reports should not exceed 200 words in length and should be received First Post each Monday morning for publication in the following week's issue.

THE CROYDON RADIO SOCIETY

A popular comparison of members' gramophone pick-ups took place on December 12th at St. Peter's Hall, S. Croydon. A motor was fixed to a special test board, around which was screwed each pick-up on arrival. Switching enabled any two to be compared at a time, and all of them fed into a high-class receiver, using an A.C. H.L. and an L.S.6a at 350 volts for output. A discussion revealing some inherent difficulties in records and their reproduction first took place. Correct tracking was vital, and the needle must remain at right angles to the radius. There was also the difficulty of side pull on the groove, methods of minimizing this being indicated. In any case needle scratch limited top response at 3,500 cycles, while impracticability of a wide groove limited the bass. Tests were performed on a special musical frequency test record, and various needles were tried in turn. The Society is preparing for its New Year campaign for members, and PRACTICAL WIRELESS readers can gain ready admittance on application to the hon. secretary, E. L. Cumbers, Maycourt, Campden Road, S. Croydon.

SLADE RADIO

It was a "Members' Night" at a meeting held recently, and the opportunity was taken to deal with the following:

1. Questions on subjects relating to lectures during the past quarter.
2. General questions.
3. Interference, mains, etc.

A large number of questions were raised and dealt with in a very satisfactory manner by Messrs. A. Freeman and G. T. Peck, the joint technical advisers. During the evening an oscillator of the latest type was exhibited and inspected by the members with great interest — Hon. Sec., 110, Hillaries Road, Gravelly Hill, Birmingham.

BATTERSEA AND DISTRICT RADIO SOCIETY

On Friday evening, December 15th, the Battersea and District Radio Society held its last meeting for 1933, when Mr. D. Ashby, of the Westinghouse Brake and Sash Signal Co., Ltd., gave a lantern lecture on the "Westector and its Associated Circuits." Various circuits for detection, automatic volume control, and H.T. current economizing by means of the Westector were shown by means of slides, and ably explained by

the lecturer. The next meeting will be on January 9th, when it is hoped that the finishing touches will be given to the new D.C. mains receiver which the members have been building.—L. W. Smith, Hon. Sec., 8, Emu Road, Battersea, S.W.8.

INTERNATIONAL SHORT-WAVE CLUB (LONDON CHAPTER)

At the meeting of the London Chapter held at R.A.C.S. Hall, Wandsworth Road, S.W.8, on Friday, December 15th, Mr. P. J. L. Macfarlane, G.S.M.E., gave an illustrated talk on the layout and construction of short-wave receivers. He also gave some details of a new method he has discovered of obtaining reaction. A discussion then followed, dealing with the propagation of ultra-short waves. Various theories being put forward by the members, who showed great interest in this subject. Our new series of meetings commenced on January 5th at 8 p.m.—A. E. Bear, Sec., 10, St. Mary's Place, Rotherhithe, London, S.E.16.

INTERNATIONAL SHORT-WAVE CLUB (MANCHESTER CHAPTER)

A large number of short-wave listeners attended the inauguration of the Manchester Chapter of the International Short Wave Club, held on Tuesday, December 12th, at 75, Long Street, Middleton, nr. Manchester. Mr. F. Fielding, of Allied Newspapers, Ltd., and Mr. F. Sharpe were present. Mr. H. Wild, chairman, in opening the meeting spoke of the many advantages of being a member of this world-wide organization. Mr. Fielding then gave a talk on short-wave receivers, and mentioned the thrills to be obtained by hearing Australia for the first time. Mr. H. B. Shields, technical adviser, then described and demonstrated several short-wave receivers. All present agreed that they had enjoyed a most interesting evening. Many exclusive features have been arranged for future meetings, and all PRACTICAL WIRELESS readers in the district who are interested in short-wave work are invited to attend. The next meeting will be held at 75, Long Street, Middleton, nr. Manchester, at 8.0 p.m. on Tuesday, January 9.—R. Lawton, Secretary, 10, Dalton Avenue, Thatch Leach Lane, Withcester, Nr. Manchester.

REPLIES TO BROADCAST QUERIES

MAC (London, N.10): We can trace the following call signs: (2) G6VK, A. R. Dellbridge, "Normanhurst," High Road, Laindon, Essex; (4) G2WS, W. A. Scarf, B.A., 4, Ridge Mount, Cliff Road, Hyde Park, Leeds, Yorkshire; (5) G5VT, A. E. J. Cooper, "Halfacres," Blisshops Stortford, Hertfordshire; (6) G5VL, R. W. Leader and H. J. Powditch, Porth House, Porth, St. Columb Minor, Cornwall; (9) G5CV, P. D. Walters, 45, Fairfax Road, Bedford Park, W.4; (11) G2SK, K. G. Styles, 19, Southampton Buildings, Chancery Lane, W.C.2; (12) G5UK, M. B. Buckwell, 114, Tankerville Drive, Leigh-on-Sea, Southend, Essex; (13) G6VI, W. MacCallum, 21, Park Place, Stirling, Scotland; (16) G5VB, A. F. Elton Bott, "Francisca," Barlow Road, Hampton, Middlesex; (17) G5SB, S. Berry, 143, Cheltenham Road, Bristol, G.6; (18) G5RB, A. R. V. Garrett, Swinley House, South Ascot, Berkshire; (20) HAF4A, Denes Bibo, 50, Marvany Utca, Budapest, I., Hungary; (21) PAOAG, R. H. Brouwer, 14, Groote strasse, Rijssen, Holland; (23) PAOHB, W. M. F. J. Otten, Haarvermarkt, Breda, Holland; (25) PAORO, J. R. Lettre, 111, Scheveningensestraat, The Hague, Holland; (27) PAORP, M. E. A. Bevelmans, 24, Bezuidenhout, The Hague, Holland; (28) PAOMF, J. H. Van Dijk, 381, Hoofdweg, Amsterdam, Holland; (30) F8VG, Georges, Rue de l'Eglise, St.-Laurent près Epinal (Vosges), France; (31) F3BL, Marc Tonna, 134, Boulevard Dauphinot, Rheims, France; (33) F3CP, Louis Regnier, 9, Rue de Mazenay, Le Creuzot, France; (34) F8PU, Bassus, 2, Rue Sainte-Vincent-de-Paul, Bordeaux (Gironde), France; (36) F8QS, Eugène Darteville, 21, Rue des Douze, Sous-le-Bois, Maubeuge, Nord, France; (37) F3AM, P. Munch, 1, Rue du Hugsteln, Guebwiller (Haut Rhin), France; (38) F8KI (K?), M. Yvonnet, 8, Rue Desnoettes, Paris 15, France; (39) F8VV, Marcel Doudouet, Chalet D.9, Colombelles (Calvados), France; (40) F8AC-Lagien, 12, Rue Edmond Rostand, Marseilles, Bouches-du-Rhône, France; (41) F8CL, De Commissie de Marsilly, Villa Saint Georges, Saint-Lô (Manche), France; (42) F8JE, Leon Coizic, 8, Rue Victor Hugo, Brest (Finistère), France; (43) F3BN, Marcel Mathias, 36, Rue Marchais, Orléans (Loiret), France; (44) F8ZB, Bouchard, Les Erables, Route de Corcelles, Dijon (Côte d'Or), France; (45) F8VL, Caradeac, 177, Rue Croix-Nivert, Paris 15, France; (46) F8YR, Beaujeau, 85, Rue Sadi-Carnot, Armentières (Nord), France; (47) EAR155, Ignacio Guittinan, 44, General Lacy, Madrid, Spain; (49) HB9K, Philip Recordon, Grand Champ, Lausanne, Switzerland; (50) HB9AA, Hans Buechler, 77, Scheucherstrasse, Zurich, Switzerland; (51) ON4BL (A?), H. de Thier, 115, Avenue du Chêne, Heusy, Verviers, Belgium; (52) F8MI (L?), Lieutenant Paqueron, Chef de Transmissions du Territoire, 22, Rue du Commandant Mellier, Fez (Morocco); (53) CTIFU, Mario de Vasconcelos, 461, Rua das Valas, Oporto, Portugal. AUSSI (Kent); SILVANUS HAYWOOD (Tipton): VK2ME, Sydney (Australia) received direct on 31.28 m. The interval signal is the call of the Kookaburra (Laughing Jackass). The address is: Amalgamated Wireless, Ltd., 17, York Street, Sydney, N.S.W., Australia.

REPLIES TO

**LET OUR TECHNICAL STAFF SOLVE
YOUR PROBLEMS**



QUERIES and ENQUIRIES

by Our Technical Staff

The coupon on this page must be attached to every query.

If a postal reply is desired, a stamped addressed envelope must be enclosed. Every query and drawing which is sent must bear the name and address of the sender. Send your queries to the Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton St., Strand, London, W.C.2.

SPECIAL NOTE.

We wish to draw the reader's attention to the fact that the Queries Service is intended only for the solution of problems or difficulties arising from the construction of receivers described in our pages, from articles appearing in our pages, or on general wireless matters. We regret that we cannot, for obvious reasons—

- (1) Supply circuit diagrams of complete multi-valve receivers.
- (2) Suggest alterations or modifications of receivers described in our contemporaries.
- (3) Suggest alterations or modifications to commercial receivers.
- (4) Answer queries over the telephone.

Please note also that all sketches and drawings which are sent to us should bear the name and address of the sender.

THERMAL DELAY SWITCH

"As a new reader of your interesting periodical I have just seen reference to what is called a thermal delay switch. I realize from the name that this operates on a temperature basis, but regret that I cannot see its application in a normal receiver. Please could you let me know just what it is, and its general application?"—G. H. (Kettering).

The switch is employed on the mains side of a receiver, which uses a rectifying valve of the indirectly-heated type. The heater of such a valve is fed from a secondary winding on the mains transformer, and the centre tap of this winding is employed as the H.T. positive lead. Obviously, therefore, when the mains are switched on the H.T. positive connection is completed to the receiver, but the heater takes thirty seconds or so to obtain maximum emission, and thus there is a risk of condensers and other components breaking down due to the excessive load caused by the fact that no anode current can flow until the valve is giving emission. Where the valves in the receiver are of similar type the danger is increased. The delay switch is wired in series in the H.T. lead, and it is fed from the same heater winding. Thus, whilst the heater is attaining maximum temperature the switch is also warming up and only closes when a certain temperature is obtained. This is designed to take approximately the same time as the normal I.H. valve. The switch may, of course, be employed in a D.C. mains receiver for the same reason.

WAVE-CHANGE SWITCH FAULTY

"My receiver has been working for quite a long time without any trouble, but find I cannot now get Daventry or other long-wave stations. When I switch over to the long waves there is a sort of rustling noise, but there are no signals and reaction also seems dead. Can you give me any idea what is wrong?"—R. B. (Pimlico).

It is most probable that the wave-change switch has become faulty, due either to corrosion or a bad contact caused by a weakened spring. There is, however, the remote possibility that one of the long-wave windings (if more than one coil is used) has broken, although with the majority of commercial coils this should not happen. Examine the switch carefully and we think you will find that this is the real cause of the trouble. Whenever a set works well on one wave-band and fails on another it may be taken that the fault can only arise in the part of the circuit which is changed, and with the majority of broadcast receivers one part of the coil is simply shorted out for medium waves, thus localising the fault as being in the switch or that portion of the coil which is brought into circuit.

FUSE SHORTING TO CHASSIS

"I have finished the Orbit but am rather puzzled by a peculiar fault which is occurring on it. When I finished and screwed the fuse bulb in it glowed fairly

brightly. The switch was 'off,' and so I pulled it into the 'on' position, and was surprised to see the fuse go out and the valves then lit up and the set worked. Results are really splendid, and I could not wish for a better set, but I cannot understand whether I have made a mistake in the wiring, or whether the fuse should work as it does. It is definitely alright when the switch is off and goes out when the set is on. Is this normal?"—W. D. G. (Bromsgrove).

The fault is due to the fact that you have screwed the fuse bulb too hard into its holder, and this has forced the lower contact down on to the metallized chassis. If you give the bulb one or two turns upward you will find that it will go out and will then function in the ordinary way. A number of readers seem to have experienced this peculiarity, and it would, therefore, appear to be a good plan to fit a disc of paper or thin card below the fuse holder when mounting this in order to avoid the risk.

DATA SHEET No. 68.

Cut this out each week and paste it in a notebook.

SHUNT RESISTANCES FOR CONVERTING A 100-OHM METER.

Required Shunt (Ohms)	Multiply-ing factor	Required Shunt (Ohms)	Multiply-ing Factor
0.100	1,000	2.04	50
0.125	800	2.56	40
0.200	500	3.45	30
0.251	400	5.26	20
0.334	300	11.11	10
0.503	200	14.29	8
1.010	100	20	6
1.266	80	25	5
1.695	60	33.33	4
		50	3
		100	2

From the above table it will be seen that if a meter having a resistance of 100 ohms and reading 5 milliamperes is required to read 50 milliamperes (that is 10 times) a shunt of 11.11 ohms will be required. Knowing the resistance of the meter, any resistance can be ascertained from the above table.

FURY FOUR PROBLEM

"I have finished the Fury Four and can only get very weak signals. I have tried everything to bring up the strength but without avail. I finally borrowed a meter and find that the total H.T. across the terminals are only 30 volts. I have checked all the resistances by replacing them with others and can still get no results. Can you give any clue to the trouble?"—T. Y. D. (Gloucester).

There is undoubtedly a short-circuit across your H.T. supply in some part of the receiver, and the only way to find it is to connect a meter across H.T. positive and negative and then to go right through the circuit disconnecting various components one at a time until you find that the voltage rises to normal. This may seem tedious, but it is infallible, and it will most likely be found that there is a short-circuit on to the chassis.

MEASURING OUTPUT VOLUME

"I am getting really interested in the performance of my set since I have taken up 'Practical Wireless,' and I have a problem to put to you. I know nothing of mathematics, or the technical side of wireless, but I am immensely keen to be able to measure the actual volume given off by my set as I wish to carry out experiments with various ideas and to compare them with what I get now. I can, of course, judge the quality by my ear, but I cannot judge actual power and I should like to measure this, as I read that an increase

of 50 per cent. is not detectable by the ear alone."—F. L. P. A. (Holloway).

If a circuit is made up by you and you cannot detect an increase in volume, there is hardly any necessity to measure it. However, from an interest point of view you probably wish to carry out some experiments, and therefore the easiest arrangement is to fix up the following apparatus. Obtain a small disc of polished aluminium, say, about as large as a penny. Have a really high polish on one side, similar to a mirror. Stick this, mirror side outwards, on a length of very thin silk, and stretch the silk between two firmly fixed arms. The entire structure should be really rigid, and the length of silk should be adjusted so that the mirror can rotate, or at least vibrate freely. This piece of apparatus should be stood directly in front of your loudspeaker (the actual optimum distance being found by experiment), and a small lamp focused on the mirror with no signals coming through. When the set is switched on it will be found that the sound waves will cause the mirror to move about, and you can then arrange the lamp and mirror so that the spot light cast by the latter is directed on to the wall. The maximum movement will be obtained by the loudest signal, and you should be able to arrange matters so that you get only a small movement with the present set and thus be able easily to see the circuit which produces maximum volume. Of course, the lamp and mirror must always be placed exactly in the same position.

ADDITIONAL LOUD-SPEAKER

"I was very interested in the recent article on connecting an extra loud-speaker, but I find that although that article the author did not deal with the push-pull circuit. As I am at present using this arrangement, and should like to use an extra speaker, I should be glad of directions for connecting it to my circuit."—H. A. S. (Gainsborough).

The conditions of a push-pull circuit are generally similar to a triode employing an output choke. That is, the two anodes of the push-pull valves are joined together through a choke or the primary of an output transformer. The centre tap of this winding is joined to H.T. positive. Therefore, an extra speaker may be joined to the two anodes, either direct, or through a fixed condenser of 2 mfd. There is no D.C. flowing in the normal push-pull stage so that the condensers are not essential, and they need only be used when the extra speaker is supplied at some distance from the apparatus. If the present speaker is joined to the anodes, then it will be preferable (as in the other cases mentioned in the article) to obtain a speaker with an output transformer, or a separate transformer, and to use this for supplying one speaker and the primary, to be used as a choke.

STATICS

"I am rather puzzled by the phenomenon which I receive regularly on my set. If I set the tuning dials to a spot slightly below London there is practically dead quiet. As I turn the dials towards London, however, there comes in a lot of cracklings and noises which are strongest when I am tuned to London, and if there is no music on there is a most horrible noise."—G. T. (Edgware).

The fault is quite beyond your control, and is due to the high efficiency of your H.F. stage, or stages. The carrier-wave of the local station acts as a conveyor for all kinds of static and other noises and these are in themselves untuned but accompany the carrier wave. Thus, when tuned to a point where there is no broadcast station the noises are not so clearly audible as when you tune in a powerful carrier with its accompanying "mush." Obviously the noises (as well as the general signal) will be reduced if you lower the amount of H.F. amplification.

**FREE ADVICE BUREAU
COUPON**

This coupon is available until January 13, 1934, and must be attached to all letters containing queries.

PRACTICAL WIRELESS, 6/1/34.

PRACTICAL WIRELESS MISCELLANEOUS ADVERTISEMENTS

Advertisements are accepted for these columns at the rate of 3d. per word. Minimum charge 3d. All advertisements must be prepaid.

PREMIER Supply Stores, 20, High Street, Clapham, S.W.4. See our advt. on Page 748 of December 23rd issue.

SOUTHERN RADIO'S Wireless Bargains.—See manufacturers' guaranteed surplus.

VARIABLE Condensers.—Lotus 2-gang 0.0005 complete with dial, knob, escutcheon, 8/6; Lotus Dublock Single Variable 0.0005 Condensers with dial, knob escutcheon, 4/8, (list 9/6); Hydra block condensers, new, 16 mfd., 2+2+2+2+1+1, 1,000 volt test, 7/ each; 4 mfd., 2/6; 2 mfd., 1/9; 1 mfd., 1/6. Block condensers 1,500 volt, with terminals 20 mfd. (2+2+2+2+2+2+2+1+1) 12/9; 10 mfd. (2+2+2+2+1+1) 8/3.

RAUDIOPHONE Volume Controls and Switch. 50,000 and 10,000 ohms, 3/3 each (list 10/6).

HELLESEN 8 mfd., Electrolytic Condensers, 3/6 each, 4 mfd., 3/ each.

SPEAKERS.—Permanent magnet, 28/- (listed 49/6); D.C. mains energised, 2,500 to 6,500 ohms, complete with humbucking coils and transformers. 16/0 (list 39/6); Magnavox D.C. speakers, M.C. latest type "154" all voltages, 17/0 each. G.E.C. Stork speakers, complete in magnificent cabinet, 19/6 (listed 23/15); Ormond speakers, complete in cabinets, 10/- (listed 25/15); Blue Spot, 100 U, 13/6 (list 37/6).

READY Radio "303" A Kits, complete with cabinet, M.C. speaker, less valves, £2/5; with 3 Mullard valves (P.M.I.L.F., P.M.2.D.X., P.M.2.). £3/5 (list £2/17/6).

READY Radio Meteor "A" 3-Valve Screen Grid Kit, complete with cabinet, M.C. speaker, less valves, £3/7/6; with 3 Mullard valves (P.M.12.A., P.M.2.D.X., P.M.2.A.), £4/10 (list 8/7/6).

READY RADIO ST.400 Kits, as specified by R. Scott Taggart, £2/19/6 each (list £4/17/6), all kits brand new in original sealed cartons.

B.T.H. Senior Pick-ups, 1934, complete with volume control, 28/6 each (list 37/6). Blue Spot Pick-ups, with volume control, Model "88," 26/- each (listed 63/1); Ferranti Chokes, C.T., 20 Hys., 50 m.a., 6/0 each (list 35/1); H.M.V. volume controls, 1/6 each (list 12/6). Dubblier 4 mfd. condensers (2+1+1), 1,000 volt, 2/0 each. 4.5 mfd. (2.25+2.25), 1,000 volt, 3/- each. Luminophor D.C. Moving Coil Speakers with terminals, 11/6 each (list 39/6). Main Switches, 3 amp., 250 volt, 8d. each, 7/6 doz. Edison Bell Centre Tapped Inductance Coils, all values from 20 upwards, 9d. each, 7/6 doz. assorted. Amplion Loudspeaker Units, 2/3 each (list 12/6). Every article perfectly new.

All Goods guaranteed New and Perfect and carriage paid.

ALL Goods guaranteed New and Perfect and carriage paid.

PLEASE Note.—We have opened branches at 271-275, High Rd., Willesden Green, N.W.10, and at 46, Lisle Street, W.C.2, where callers are cordially invited to inspect our large stocks of wireless bargains. Please send all post orders to 323, Euston Rd., N.W.1. **S**OUTHERN RADIO, 323, Euston Rd., London, N.W.1 (near Warren St. Tube). Phone: Museum 324.

THE following valves are guaranteed unused and perfect, and any valve differing from the makers' characteristics will be exchanged; and all latest types. A.C./Pens, P.T.4s, A.C.S.G/V.M.s, Pen, 4V.s, M.V.S.G.s, A.C.S.2/Pens, M.M.4V.s, P.T.625s, V.M.S.4s, D.C.2/Pens, D.P.T.s, P.M.24M.s, M.P.T.4s, V.M.4V.s, A.C.S.1/V.M.s, P.M.24B.s, D.C.28.G/V.M.s, 11/- M.S.4s, M.S.4B.s, A.C.S.G.s, S.4V.A.s, S.4V.B.s; M.S.G./L.A.s, D.S.B.s, A.C.S./2s, D.C.25.G.s, 9/- U.14s, 10/-; Class B : P.M.2.B, P.D.220, 220B, 8/6; M.L.4s, A.C./P.s, P.M.24s, 8/-; A.C./H.L.s, 16V.s, 354V.s, A.C.2/H.L.s, 41M.H.L.s, U.10s, U.60/250s, M.H.4s, M.H.L.4s, 7/6; V.S.2s, 215S.G.s, 220S.G.s, P.M.12s, P.M.12A.s, 0/-; 442B.U.s, D.W.3s, 8/6; 215P.s, 220P.s, L.P.2s, 4/9; P.2s, 6/6; P.T.2s, P.M.22A.s, 0/-; H.L.210s, H.210s, L.2s, 3/9. All Types of Brand New American Valves in Stock, first-class makes : 247s, 235s, 224s, 236s, 237s, 238s, 239s, 245s, 243s, 12/-; 227s, 220s, 230s, 9/6; 242s, 232s, 11/-; U.X.250s, 10/-; 231s, 14/6. Carriage Paid. Cash with Order or c.o.d. Westinghouse rectifiers unused. H.T.8, 10/-; H.T.9, H.T.10, 11/3. Dubblier or T.C.C. electrolytic condensers 8 M.F.D., 3/0. Magnavox D.C. 152 (2,500 ohms) or 6,500 ohms, 9in. cone, 25/- Ward, 45, Farringdon St., E.C.1.

MELFOR-RAD "Guaranteed Kit" Specialists. Nucleon CL/B.4, described within. First specified Kit, £5/8/0. ST.500, 78/-; Century Super, £5/0/0. D.C. Mains Kit, £5/5/0. Universal A.C. D.C. Mains, £5. "Melforad," 5, Queens Place, Hove.

RADIO SUPPLIES

Send your list of Radio needs for our quotation. Kits, Parts, Sets, etc. Everything in Radio stocked, prompt delivery, 7 days' approval. Catalogue free. Taylex & Standard Wet H.T. replacements stocked.

N. TAYLOR, 9, GROVE RD., BALHAM, S.W.12

Easy Terms

Strict Privacy Guaranteed
—we deal with you direct

N.T.S. PICK-UP

SEND FOR IT ON 7 DAYS' TRIAL.

Frequency response 80-5,000 cycles. Bakelite head. Florentine bronze finish. Complete with lead and arm support.

2/6
DOWN

Send only 2/6 for 7 days' trial. If approved, balance in 4 monthly payments of 4/3. Cash or C.O.D. Carriage Paid, 17/6.

BLUE SPOT 29 P.M. MOVING - COIL SPEAKER

SEND FOR IT ON 7 DAYS' TRIAL.

A very popular P.M. Moving-coil Speaker for operation from Power or Pentode.

2/6
DOWN

Send only 2/6 for 7 days' trial. If approved, balance in 6 monthly payments of 5/6. Cash or C.O.D. Carriage Paid, £1/12/6.

TELSEN ELIMINATOR

SEND ON 7 DAYS' TRIAL.

Model W.346, 150 volts at 28 m.a. S.G. and Detector tappings.

Send only 2/6 for 7 days' trial. If approved, send further 2/6. Balance in 7 monthly payments of 6/-.

Cash or C.O.D. Carriage Paid, 24/17/6.

NEW BLUE SPOT CLASS 'B' OUTPUT STAGE

SEND FOR IT ON
7 DAYS' TRIAL.

With Class "B" Output Valve (less speaker). Send only 2/6 for 7 days' trial. If approved, send further 1/6.

Balance in 12 monthly payments of 4/-.

Cash or C.O.D. Carriage Paid, 22/3/8.

N.T.S. CLASS 'B' SPEAKER

SEND FOR IT ON 7 DAYS' TRIAL.

Gives perfect reproduction. With input power or pentode.

2/6
DOWN

Send 2/6 for 7 days' trial. If approved, pay balance in 5 monthly payments of 4/6. Cash or C.O.D. Carriage Paid, 22/6.

Also model for Power or Pentode. Same Price and Terms.

New Times Sales Co.

56, LUDGATE HILL, LONDON, E.C.4.

Dear Sirs:

(a) Please send me.....

(b) I enclose Cash/Deposit.....

NAME.....

ADDRESS.....

Pr.W.6-1-34.

ERICSSON 3/1 L.F. Transformers, List price, 17s. 6d. New and guaranteed. Our price, 2s. 3d. post free U.K.—Pioneer Radio, Coptic St., London, W.C.1.

REPAIRS TO ANY MAKE RADIO APPARATUS. 24 Hours service, guaranteed laboratory tested. Transformers, loud-speakers from 4/-, Eliminators, Mains Transformers, etc. New cones fitted to Moving Coil speakers. Estimates free. Wates Volt/Amp meters a specialty, 3/6, other makes quoted for Repair Dept. C. WEEDON POWER LINK RADIO CO., 185, Earlham Grove, London E.7. Maryland 4344.

CHAL Electric offers Brand New Set Manufacturers' surplus Moving Coil Speakers. Magnavox Type D.C.144, 9-in. cones 100/190 D.C. (2500 ohms) (20/76 M.A.) and 190/280 D.C. (6500 ohms) (29/43 M.A.) at 26/- each. 152 Type, 9-in. cones same voltages at 26/- each. ROLAS F.6 (voltages as in Magnavox), 7-in. cones at 18/-; F.7 9-in. cones same voltages at 25/-; Permanent Magnets, F.6 P.M., list 49/6, at 28/-; F.7 P.M., list £3, at 33/- State if Power or Pentode Transformer. All fitted Humbuckers. Also number of Class "B". State requirements. All goods Carr. Paid. Cash with order or C.O.D. Chal Electric, No. 6, Conduit Street, London, W.1. Regent 6240.

WANTED good Modern Wireless Parts, Sets, Eliminators, Meters, Valves, Speakers, etc. Spot Cash Waiting. Send or bring. We pay more than any other Dealer. Open 9-8.—University Radio, 142, Drummond St., Hampstead Rd., N.W.1.

TELEVISION APPARATUS. We specialise in all components for Portovision described in this journal. Send for illustrated list.—H. E. Sanders, 4, Grays Inn Rd., London, W.C.1.

£50 CASH PRIZES FOR POEMS; particulars free. Fiction also invited. Current Catalogue on application. Stockwell, Ltd., 29, Ludgate Hill, London.

PATENTS & TRADE MARKS

KING'S PATENT AGENCY, LTD., 146b, Qn. Victoria Street, F.C.4, offer "Advice Handbook" and Consultations free. 47 years' references. Write, call, or phone (Central 0682). Director, B. T. King, C.I.E., Reg. Patent Agent, G.B., U.S.A., and Canada.

MAKES LIFE WORTH WHILE



French Maid (who has just been given the sack): "Ah, perfidious Albion, you burn Joan of Arc, you send the great Napoleon to exile, and now you dismiss me!"

The HUMORIST
EVERY FRIDAY. TWO PENCE.
At all Newsagents and Bookstalls.

ADVERTISEMENT INDEX

Amplion (1932) Ltd.	805
British Ebrite Co., Ltd.	788
British Rola Co., Ltd.	801
Bulgin, A. F., & Co., Ltd.	IV Supp.
Colver, Ltd.	798
Cossor, A. C., Ltd.	Inside Front Cover
Electradit Radios	IV Supp.
Fuxlite, Ltd.	805
Gripco Co.	II Supp.
Heayberd, F. C., & Co.	II Supp.
Heraud, E. J., Ltd.	806
Holmes, H. W.	806
International Correspondence Schools	798
King's Patent Agency, Ltd.	808
Newnes, Home Library	Back Cover
Newnes, Home Mechanic	Third Cover
Newnes, Home Movies	783
Newnes' Tit-Bits	Third Cover
Newnes' Wireless Books	787
New Times Sales Co.	803
Osborn, Chas. A.	806
Peto-Scott, Ltd.	Front Cover Strip, III and V Supp.
Riverside Mfg. Co., Ltd.	805
Taylor, N.	808
The 362 Radio Valve Co., Ltd.	788
Technological Institute of Gt. Britain	II Supp.
Turnadge & Partners	806
Wet H.T. Battery Co.	805
Wingrove & Rogers, Ltd.	783
Wright & Weaire	787

'LISTENERS IN' !

IS YOUR WIRELESS LICENCE
NUMBER IN THIS LIST ?

**IT MAY BE WORTH
£50**

 Compare your number
and claim your reward

£50

will be paid to holder of Licence
No. AO 802918

£25

will be paid to holders of Licences :
Nos. AR 785505 AS 080957

£10

will be paid to holders of Licences :
Nos. AP 054882 AQ 548196

£5

will be paid to holders of Licences :
AS 373545 AP 128899 AQ 797088 AR 787019 AQ 562226

£2

will be paid to holders of Licences :

AL 728832	AO 849536	AP 425963	AQ 170467	AQ 260084	AR 145810	AR 115239
AL 978818	AO 944774	AP 822997	AQ 208645	AQ 823651	AR 479299	AR 926405
AL 765324	AP 692736	AP 128891	AQ 308456	AQ 166702	AR 896464	AR 832394
AL 894655	AP 027949	AQ 001730	AQ 129841	AQ 014289	AR 247583	AS 006012
AO 374688	AP 991119	AQ 373643	AQ 800846	AR 359002	AR 076426	AS 373520

£1

will be paid to holders of Licences :

AL 883309	AO 944902	AP 054761	AQ 547922	AQ 171538	AR 816707	AR 145795
AL 589716	AO 802930	AP 330979	AQ 040893	AQ 840752	AR 618620	AR 235566
AL 395874	AP 843999	AQ 098775	AQ 688746	AQ 014983	AR 406112	AR 832194
AL 862309	AP 246433	AQ 837930	AQ 413299	AR 201908	AR 897000	AR 568362
AL 884812	AP 993161	AQ 479766	AQ 426317	AR 365802	AR 911000	AR 747123
AN 637925	AP 128864	AQ 170604	AQ 863448	AR 987011	AR 782894	AS 371169
AO 418601	AP 027894	AQ 217707	AQ 320893	AR 373304	AR 358240	AS 346094
AO 850000	AP 296415	AQ 562198	AQ 166941	AR 69105	AR 604975	AS 080955

 This offer applies to licences which are actually in force on Saturday, January 6, 1934.

Before the awards are paid, claimants will be asked to undertake a simple publicity service in distributing leaflets to encourage the sale of licences amongst those who at present do not fulfil their obligations by taking out a Post Office Licence before receiving broadcast programmes. Claims cannot be considered in connection with any Licence the date of issue of which is after Jan. 4, 1934.

For full particulars for
claiming awards and a com-
plete list of numbers see

TIT-BITS

ON SALE EVERYWHERE SATURDAY, January 6

PRACTICAL HANDBOOKS

Clearly written and fully illustrated.

This series covers a wide field and will prove of the greatest value to everyone interested in models and how to make them; woodwork and other crafts.

ACCUMULATORS

An up-to-date handbook dealing with every type of accumulator, methods of charging them at home, care and maintenance, also explains how to erect a charging station.

MOTOR CAR UPKEEP AND

OVERTHAUL

Information covering the engine, decarbonising, valve grinding, the lighting system, the carburettor, cooling system, lubrication, springs and shock absorbers, steering gear, brakes, wheels, axles, tracing noises, etc., etc.

TOY MAKING FOR AMATEURS

How to make clockwork toys, model aeroplanes, model locomotives, model boats, ingenious toys operated by sand, wooden models and toys, electrical toys, steam toys, guns, kaleidoscopes, acrobats, etc.

TWENTY-FIVE TESTED WIRELESS CIRCUITS

All the sets described have been designed to meet modern needs. They range from simple crystal receivers to a seven-valve super-heterodyne, and all the sets have been made and tested before inclusion.

SIMPLE ELECTRICAL APPARATUS

An excellent little book for those who wish to make simple and useful electrical appliances, such as galvanometers, electric motors, dynamos and Leyden jars.

MODEL BOAT BUILDING

Contains designs for battleship, speed boat, paddle steamer and yachts. Excellent models can be built with the simple directions and diagrams given.

THE HOME WOODWORKER

Clear instructions on how to make a large variety of articles in wood, together with many useful hints on wood-working.

MODEL AEROPLANES AND

AIRSHIPS

Contains full descriptions of easy-to-make models of every description that will fly.

THE HANDYMAN'S ENQUIRIES

WITHIN

Hundreds of practical ideas and hints of value to the man who is clever with his hands.

25 SIMPLE WORKING MODELS

Ingenious and practical designs for electric, steam and clock-work models.

NEWNES'

HOME MECHANIC BOOKS

Obtainable at all Newsagents and Bookstalls, or by post 1½ each from George Newnes, Ltd., 8-11, Southampton St., Strand, W.C.2.

1/-
each

Geo. Newnes, Ltd.

A Sensible INVESTMENT for everyone in the Wireless business.

One of the many valuable action illustrations in this work.



Lifting out the Diaphragm and Coil of a Magnavox Speaker.
This enables the speech coil to be examined if short circuited or broken windings are suspected.

A MODERN REFERENCE WORK

THE progress in wireless practice during the past few years has been enormous. The Screened Grid, the Pentode, the Bigrid, and the Variable-Mu Valves have made their appearance in rapid succession. Band Pass Tuning, Push-Pull Amplification, the Stenode, the Autotone, the Dual Speaker, are other items which were unknown to the wireless industry a few years ago.

This fully illustrated work is designed to bring every reader of "P. W." right up-to-date on the theory, design, and construction.

To feel at home amongst such a variety of electrical appliances the modern wireless man must have a thorough grounding in electrical theory. This point has been kept well in mind in the compilation of the present work. No effort has been spared to make the theoretical treatment complete.

Included in this work are many proved circuits and designs, together with full details of the methods of construction and wiring, and many articles devoted to the servicing of high-class receivers and radiograms.

We are convinced that the wealth of information which has been brought together in this work will be of real use to the enthusiastic wireless amateur and absolutely essential to the man to whom "wireless" is bread and butter.

FREE Newnes' Complete Wireless is bound in 4 serviceable volumes. If you are interested send post card to-day for free illustrated descriptive folder and details of a convenient easy purchase scheme to:



THE HOME LIBRARY BOOK CO.

(Dept. "Practical Wireless" 6134),

23-24, TAVISTOCK STREET,
COVENT GARDEN, LONDON, W.C.2.

NEWNES' COMPLETE WIRELESS

This fully illustrated new work deals with the whole theory of wireless from the very simplest principles up to the most advanced stage. It shows you the most up-to-date practice as exemplified in the fine commercial sets which have been placed on the market recently. It shows you the possibilities of short-wave work, and contains numerous useful designs.



Another splendid illustration showing the fitting of a New Cord to the Drum of the Marconiphone 42 Receiver.



Testing the Insulation Resistance between Mains Input Terminals and Earth.

Geo. Newnes, Ltd.

P.W. Gift Stamp No. 1

Printed by NEWNES & PEARSON PRINTING CO., LTD., Exmoor Street, Ladbrooke Grove, W.10, and published by GEORGE NEWNES, LTD., 8-11, Southampton Street, Strand, W.C.2. Sole Agents for Australia and New Zealand : GORDON & GOTCH, LTD., South Africa : CENTRAL NEWS AGENCY, LTD. "Practical Wireless" can be sent to any part of the world, post free, for 17/4 per annum ; six months, 8/8. Registered at the General Post Office for Transmission by Canadian Magazine Post.