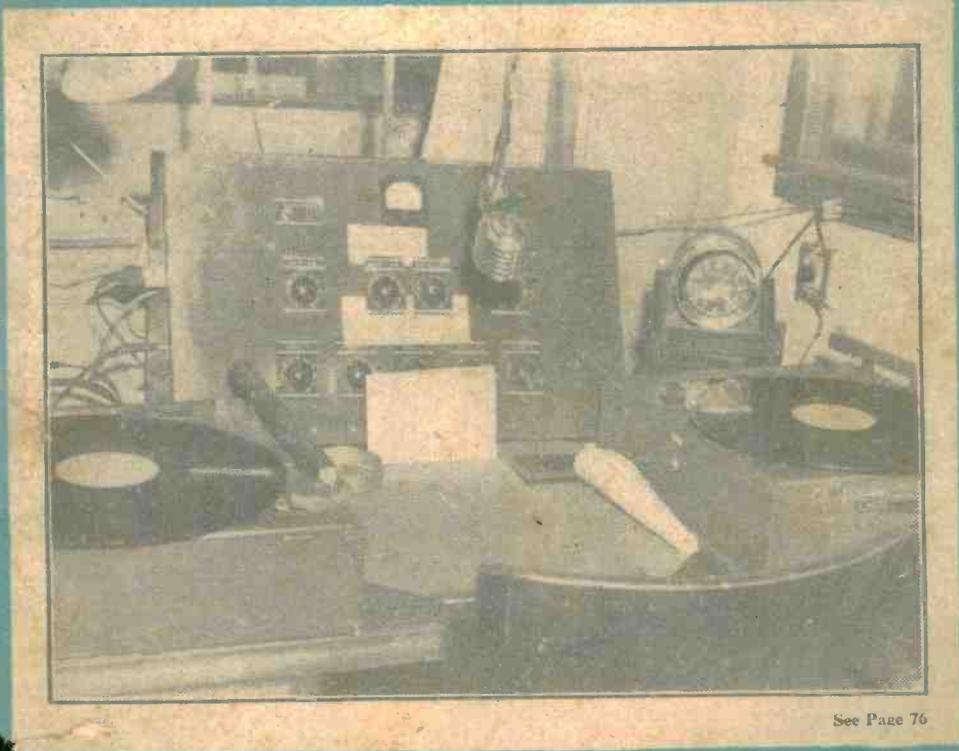


*Graphman*

PUSH-PULL PHASE SPLITTING

# Practical Wireless

Vol. 24 - No. 499 || Editor: F. J. CAMM || FEBRUARY, 1948



See Page 76

## PRINCIPAL CONTENTS

Novel Battery Circuits  
 Cathode-ray Tube Data  
 Static Aerials  
 Relay Stations

Bandspread Receiver  
 The Quantum Box  
 Radio Amateurs' Examinations  
 Test Instrument Design

Post your **DENCO** orders to

# VALLANCE'S

For a sure pick-up using a 1.5 lb. weight of pressure. All in a portable case.

## COILS

500 p.p.m. 1.31. 500 p.p.m. 1.31. 500 p.p.m. 1.31.

## COIL FORMERS

Horizontal 1.00 Polystyrene 2.3.  
Vertical 1.00 Polystyrene 2.3. 100 p.p.m.

## COIL HOLDERS

Horizontal 500 p.p.m. 1.31.

## COILS

The following table identifies the coils:  
**Blue**—R.F. Grid Coil, with Variable Inductance.  
**Yellow**—Detector or Mixer Coil, C.T. 1.00 p.p.m. 1.31.

**Green**—Detector or Mixer Coil, with 100 p.p.m. 1.31.  
**Red**—Speaker Oscillator, 1.00 p.p.m. 1.31.  
Large 1.00 p.p.m. 1.31. 500 p.p.m. 1.31.

2. 1.65. 7. 5. 70. 40.  
3. 1.65. 7. 5. 70. 40.  
4. 1.65. 7. 5. 70. 40.

Range 1.5 (100 p.p.m. variable)  
Range 3.0 (100 p.p.m. variable)  
Range 4.5 (100 p.p.m. variable)

Plug in (variable range) 3.4/2 inch, except green, 4.8 inch  
Chassis type to match 3.10 inch, except green, 4.8 inch  
Range 6 to 3.37 inch, except green 4.5 inch

## DENCO VARIATOR

10z. 11. 30z. 25.

## STAND-OFF TYPES

SO1 2. 11d., 2m.  
SO1 1 1 0 d., 3m.  
SO1 1 1 3. 1m.

## INSULATORS, POLYSTYRENE

1. 1. 1. 1. 1. 1.  
2. 1. 1. 1. 1. 1.

## LOW LOSS VARIABLE CONDENSERS

Type V.C.R. Polystyrene in oil on V.C.R. 15 6 11. 15 p.p.m.  
V.C.R. 15 6 11. 15 p.p.m.  
V.C.R. 15 6 11. 15 p.p.m.  
V.C.R. 15 6 11. 15 p.p.m.

## COIL TURRET, TYPE C.T.1

4 wavebands, 1 F., 1.6 m. s. 7.0-11.75 m. s.  
15-17 m. s. 11.7-27.0 m. s.

Position 500 Coil Turret around Mixer or Signal Grid when recording is used for gramophone reproduction.  
A twin range 300pf variable is mounted on the turret, the whole makes a very efficient R.F. Tuner Unit. Price, 60/6.  
Blue prints of circuit are available. Price, 1/6 each.

## COIL TURRET, TYPE C.T.2

This turret is identical in appearance and dimensions to the C.T.1, but has an I.F. of 95 kc/s.  
Actual bands covered are—  
1. 150-350 kc/s.  
2. 520-1,700 kc/s.  
3. 5-12.5 m. s.  
1. 12.5-30 m. s. Price, 60/- Circuit, 1/6.

## COIL TURRET, C.T.3

6 band R.F. Unit, with a 3-gang mounted on the Turret, 300 pf, each section. Gang is locked to provide band spread.  
Bands covered are—  
1. 15-7 m. s., 2,000-420 metres.  
2. 5.5-1.5 m. s., 545-200 metres.  
3. 1.75-5.1 m. s., 171-58 metres.  
4. 5.1-11.5 m. s., 58-26 metres.  
5. 11.5-24.5 m. s., 26-12 metres.  
6. 24-42 m. s., 12.7 metres.

Complete with calibrated dial. Band switch colour coded to correspond with dial markings. Knobs, drive assembly, etc. Price, £8 10/0.

## OTHER LINES AVAILABLE FROM STOCK

**SILVER MICA CONDENSERS**—4 per cent  
5-10 150p., 11d. 100-200-350pf., 1/3.  
20-25-30pf., 1/2. 300-350-500pf., 1/5.  
40-100pf., 1/2.

**SILVER MICA CONDENSERS**—5 per cent.  
5-10 150-30-50-100pf. 1/10.

**MOVING COIL METERS**  
0-50 ma. round, 2 1/2" dia. flush mounting, 3 1/2" dia. Resistance 1,200 ohms., 60/-  
0-100 ma. 2 1/2" dia. flush mounting, 45/-  
0-50 ma., 2 1/2" dia. flush mounting, 18/-  
0-50 v.c.t., 2 1/2" dia. flush mounting, 18/-  
0-10 amp., 2 1/2" square, bar scale with white pointer and capillary oil. Same as No. 14, 14/-  
0-20 amp., 2 1/2" dia., 0 v.c., with external shunt, 18/0.

**SPECIAL OFFER**—Essex-Bedcombe moving coil meter. 6in. scale, calibrated 0-150 v.c.t., full scale deflection 0-1ma., in black bakelite case, size 7 1/2" x 3 1/2". This meter has a magnifying movement and is 2 1/2" dia. Price, 1/6. Provides an ideal case for a portable meter 100 ohms per volt. Price, 6/6.  
Wellen Cracked Carbon Pressure Resistor.  
1. Resistor 1 watt, 15 ohms.  
500, 1,000, 2,000, 3,000, 50, 100, 100,000, 200,000, 400,000.

We despatch goods wherever possible the day we receive your order. These are 2 1/2" dia. packed against damage, and delivered C.W.O. or C.O.D., whichever suits you better. When sending C.W.O. please include sufficient for packing and postage.

## VALLANCE & DAVISON, LTD.

144, BRIDGE VLE, FEEDS, L. Phone 29428 & 29429.  
S7P Call Signs—G2HHV—G2PSX—G3ABD—G3AHV—G3BID

# The Connoisseur



The "CONNOISSEUR" high fidelity pick-up is now in production and limited supplies are available.

Faithful reproduction of all recordings from 12,000 C.P.S. to 30 C.P.S.

- New type damping material working in gap direct on to armature does not affect bass resonance point.
- The required downward pressure is 1 1/2 ozs. which has been achieved without counter-balancing or springs.
- Being a constant velocity device. Bass compensation is required in the amplifier and alternation of high frequencies to suit individual recordings.
- Output direct from pick-up ... .1 volt With transformer coupled ... .5 volt


Apply to:—Albion Electric Stores, 125, Albion Street, Leeds, 1. or to Lawton Brothers (Sales), Ltd., Henry Square, Ashton-under-Lyne.

Made by:  
**A. R. SUGDEN & CO. (ENGINEERS) LTD.**  
BRIGHOUSE, YORKS.

# Ex M.O.S. Radio BARGAIN IDEAL FOR CONVERSION INTO A TELEVISION

# RECEIVER

OR 90 MEGS F.M. RECEIVER

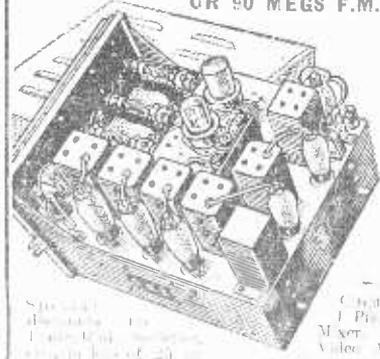

# 7 GNS

Carriage Paid  
Cash with Order  
10 VALVE  
1 1/2 METRE  
SUPERMET

complete with schematic circuit diagram

Special Offer—Essex-Bedcombe moving coil meter. 6in. scale, calibrated 0-150 v.c.t., full scale deflection 0-1ma., in black bakelite case, size 7 1/2" x 3 1/2". This meter has a magnifying movement and is 2 1/2" dia. Price, 1/6. Provides an ideal case for a portable meter 100 ohms per volt. Price, 6/6.  
Wellen Cracked Carbon Pressure Resistor.  
1. Resistor 1 watt, 15 ohms.  
500, 1,000, 2,000, 3,000, 50, 100, 100,000, 200,000, 400,000.  
We despatch goods wherever possible the day we receive your order. These are 2 1/2" dia. packed against damage, and delivered C.W.O. or C.O.D., whichever suits you better. When sending C.W.O. please include sufficient for packing and postage.

**WIRELESS INSTRUMENTS**  
54-56, The Headrow, Leeds, T.

*Manufacturers*  
SPECIFY IT BECAUSE IT IS  
THE FINEST CORED SOLDER  
IN THE WORLD

SPECIAL  
HANDY CARTON

ENOUGH FOR  
100 AVERAGE  
JOINTS

MULTICORE SOLDERS LTD., MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1

# PREMIER RADIO Co.

MORRIS & CO. (RADIO) LTD.

**MIDGET RADIO KIT.** Build your own midget radio. A complete set of parts, including valves, loudspeaker, and instructions. In fact, everything except cabinet necessary to build 4-valve medium and long wave C.R.F. radio operating on 200/250 v. mains, A.C. or D.C. Valve line-up 6K7, 6J7, 25A6, 25Y5. Wavelengths covered 200-557 and 700-2,000. Size 10in. x 6in. x 6in. Completely drilled chassis. Price, including tax, 28/0/11.

**SUPERHET MIDGET RADIO KIT.** A complete kit of parts for a 5-valve superhet. Covers 19-50 and 200-557 metres. A.C./D.C. 200-250 v. 6K8, 6K7, 6Q7, 25A6, 25Y5. Size 10in. x 6in. x 6in. Completely drilled chassis. Price, including tax, 29. An attractive brown bakelite cabinet can be supplied for other kit at a cost of 21/7/3.

**ALUMINIUM CHASSIS.** Substantially made of bright aluminium with four sides, 10in. x 8in. x 2 1/2in., 7-7/8" 15in. x 9in. x 2 1/2in., 7/8" 10in. x 8in. x 2 1/2in., 8/6" 20in. x 8in. x 2 1/2in., 10/8" 22in. x 10in. x 2 1/2in., 13/8". METERS. All meters are by the best makers and are contained in bakelite cases. Prices are about one-quarter of original cost.

Range	Ext. Dia.	Res.	Fitting	Type	Price
300v.	3 1/4in.	10K	Flush	M.I.A.C.	7/6
500ma.	3in.	—	Proj.	M.C.D.C.	12/6
40v.	2in.	8K	Flush	M.C.D.C.	7/6
25 a.	2in.	—	Flush	Thermo. H.F.	7/6
10 a.	2in.	—	Proj.	H.W. H.F.	3/6
20 a.	2in.	—	Flush	M.C. D.C.	7/6
40 a.	2in.	—	Flush	M.C. D.C.	7/6
25 a.	3 1/4in.	—	Flush	"I.C. D.C.	7/6
25 a.	3 1/4in.	—	Proj.	M.C. D.C.	7/6
25 a.	3 1/4in.	—	Flush	M.I. D.C.	7/6

**TEST UNIT TYPE 73,** consists of a special purpose Oscilloscope that requires only covering and the addition of a few Condensers and Resistors to convert into a standard Oscilloscope, input 230v. 50c. A 3in. C.K. Tube and 1 SU220A, 1 8E84, 1 5Z4, 3 8P41, 2 EA80, are included. Controls are "Brightnes," "Velocity," "X Shift," "Y shift," "Focus Amplifier" "in/out" "Calibrate," "on/off/TX." Price 28/8/0, carriage and packing, 20/-.

**ROTARY TRANSFORMERS,** input 12 v., output 180 v., 30 m.a., 4 v., 2-3 a., with 19 volts input, output is 50 per cent. higher. May be used on D.C. mains as L.T. charger. With small conversion could operate as D.C. Motor. Original cost over 25. Supply powerful ring magnet. Price 10/- each.

**OSCILLOGRAPH POWER UNITS.** Consist of a complete kit of parts for a 1,000 v. power unit with a 6.3 v. L.T. winding. Includes transformer, voltage doubling metal rectifiers and smoothing condensers. Price 20/-.

**TWO-VALVE SHORT-WAVE BATTERY KIT.** A complete Kit of Parts for a 2-valve receiver, covering 15-600 metres, including valves, coils, drilled chassis, H.T. and L.T. dry batteries to last approximately 6 to 12 months; a pair of double headphones and full instructions. Price 28/16/4. An extra coil can be supplied, covering 600-1,900 metres, at 4/-.

**EF. 50 VALVES.** Brand new Government surplus, 8/-; EA50 diodes, 5/-.

**FIRST GRADE OIL-FILLED PAPER CONDENSERS.** With miniature stand-off insulators and fixing clips, 2 mfd., 1,000 v.w., 2/6 or 20/- per dozen; 2 mfd., 600 v.w., 1/9 each or 14/- per dozen.

**SPECIAL OFFER.** Moving-coil Meters, Bush 0-500 m.a., dial marked 0-15 and 0-600 v., 2in. Just the meter for a multi-range test set. Price 7/6.

**TEST SET No. 87.** A specialised Signal Generator for 150-300 mc/s operation. Incorporates UHF Oscillator Valve Type RL18, 8 VR65, 1 5Z4, a completely smoothed Cover Pack, output 250 v., 120 m.a., 6.3 v., 4-6 a. Contained in a superb steel cabinet (Standard Sig. Gen. Type). Price 24/5/0, Carriage and packing, 5/-.

**TEST UNIT AP5874,** consists of a Test Unit for a U.H.F. T.X., incorporates a 250 v. 50 c. Power Pack, with a smoothed output of 240 v. up to 50 m.a. and 6.3 v. 2 a., 2 EF50, 1 EC32, 1 EA80, 1 5Z40, 1 163 Magic Eye, and a large quantity of Condensers, Resistors and Tuning Gear. Contained in an attractive steel case. Size 10 1/2in. x 9in. x 9 1/2in. Price 45/- Carriage and packing, 5/-.

**RELAY UNIT TYPE 9.** Consists of a 24 v. operated relay unit incorporating 3 KT300 Valves, a Telephone Line (Unispector) Switch with 6 poles, 26 contacts, 5 P.O. type relays, 2 high speed relays and a quantity of other material. Contained in an attractive relay rack type metal case 18in. x 9 in. x 9 1/2in. deep. Price 24/5/0, or without Valves, 30/- Carriage and packing, 5/-.

**SIGNAL GENERATOR TYPE 33,** consists of a battery driven Generator, with two separate units for approx. 1-metre and 5-metre operation. Includes two CV9 (VR125) Horned Triodes and 1 Diode. A large quantity of U.H.F. Tuning Gear. Contained in a tank case size 13in. x 8in. x 8in. Price 30/-.

**OUTPUT TESTER TYPE 9,** consists of a unit incorporating 3 separate Diode Detectors and a 2-valve Amplifier, each diode with its separate U.H.F. Tuning System. A retractable 18in. aerial is fitted and three VR136 (EL23) Valves, 3 H.I. Diodes and a large quantity of U.H.F. Tuning Gear is included. Contained in a tank case size 18in. x 8in. x 8in. Price 30/-, or minus three HL23 Valves 15/-.

**ALL POST ORDERS TO 167, LOWER CLAPTON ROAD, LONDON, E.5. 'Phone : Amherst 4723**

**ALL CALLERS TO 169, FLEET STREET, LONDON, E.C.4 'Phone : Central 2833.**

Send 2d. stamp for our list. Terms of business: cash with order, or C.O.D. over £1.

## CLYDESDALE

The Radioman's Shop

for Bargains in ex-Services Electronic Equipment

**R1481. VHF R/T RECEIVER**  
For 65.86 mc s., 10 Valves, 2 8P41s, 4 4EF39s, EF34, EK32, 6J5, P41, plus 7475 Voltage Stabiliser, Screened R.F. unit, S.M. Tuning Dial, 1 Tuned R.F. Circuits, "S" Meter, B.F.O. Attenuator 250, 60, 15 mw. 600 ohms phone output. Circuit, Power Input required, 210v, 35ma. H.T. 6.3 v. L.T. Suitable for 10in. x 11in. Tested and guaranteed working before despatch.  
**OUR PRICE £8/19/6** each Carriage and Packing ONLY 15/- extra.

**R1224 BATTERY SHET RECEIVER**  
3 wavebands, 1.0, 2.1 mc/s, 2.1, 4.3 mc/s, 4.3/9 mc/s, 5 Valves, 2 VP23s, FC2A, HL2, KT2, Multihead dials, R.F. S-are, 470 kΩ's I.F. 600 ohm 'phoneline, complete in grey finish wood case size 14in. x 9in. x 9in. Requires 120v. H.T., 9v. GB and 2V. L.T.  
**OUR PRICE £4/19/6** each Carriage and Packing ONLY 10/- extra.

**BRAND NEW**  
Half-wave **DIPOLE AERIAL** with reflector, for approx. 6 metres, size 9ft. 8in. x 4ft. 11in. x 9ft. 7in., with 39ft. of co-axial feeder and co-axial plug.  
**OUR PRICE 21/-** Carriage Paid.


**STILL AVAILABLE AND BRAND NEW**  
**WHEATSTONE BRIDGE.** Resistance and Continuity Test Set at 42/- plus 8/- Carriage and Packing.  
**EX-U.S. NAVY. AN/APA-1** Cathode Ray Indicator and Repeater Amplifier Unit at 90/-, plus 7/8 Carriage and Packing. Plus 1,000's of items. Condensers, Resistors, etc.

**CIRCUITS** now available. T1154Tx, 2/3, R1116Rx, 2/3, R1155Rx 1/3, R1155 Power Unit, 6/-, MCR1Rx, 2/9, F1124Rx, R1125Rx and Power Unit, 1/2, R122Rx, 1/3, American I.P.F. ABK Rx Tx, 1/9, A1134 Amp, 1/3, All Post Free.

STAFF "HAMS" GMBASM, GMBBL

Send now for new illustrated lists: please print name and address

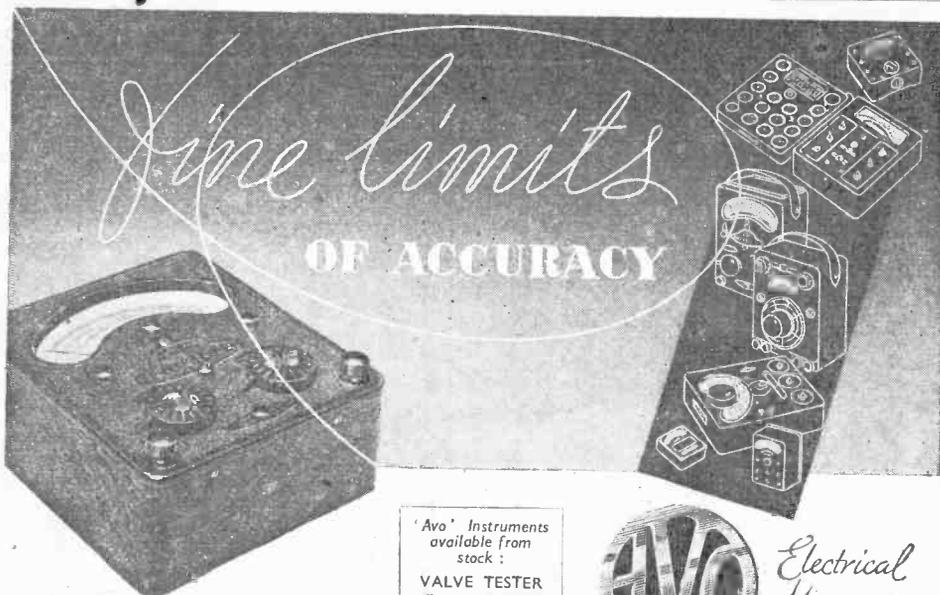**CLYDESDALE SUPPLY CO., LTD.**  
2, Bridge Street, Glasgow, C.5 'Phone South 270619  
Visit our branches in Scotland, England and Northern Ireland



The Model 7 Universal AvoMeter is the world's most widely used combination electrical testing instrument. Fully descriptive literature available from the Sole Proprietors and Manufacturers:—

'Avo' Instruments  
available from  
stock:


VALVE TESTER  
TEST BRIDGE  
D.C. AVOMINOR



*Electrical  
Measuring  
Instruments*

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT Co., Ltd.,  
Winder House, Douglas Street, London, S.W.1.

Phone: VICTORIA 3404-9.

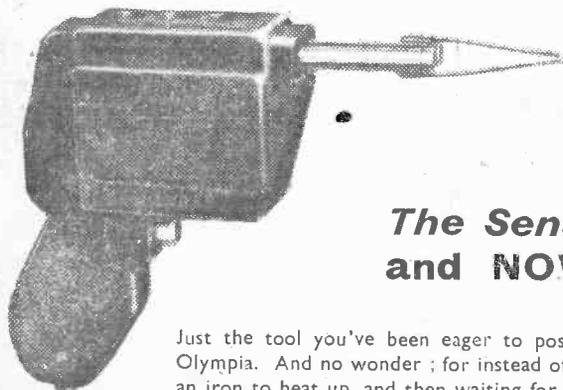

## THE BURGOYNE 'SEVEN-SECOND' SOLDER GUN

*The Sensation of Radiolympia  
and NOW Available to YOU!*

Just the tool you've been eager to possess ever since you saw it demonstrated at Olympia. And no wonder; for instead of waiting best part of a quarter of an hour for an iron to heat up, and then waiting for it to cool off before putting it away, you

**JUST PLUG INTO A.C. MAINS,  
COUNT SEVEN—AND SOLDER!**

All the time you press the button the bit remains at soldering heat. When you release your pressure it **COOLS OFF INSTANTLY**. Thus there's no risk of burning anything while you put the iron down for a minute. No risk of shock—no element to burn out—saves time, *fuel* and money. But supplies for the home market are limited, so **MAKE SURE OF YOURS BY ORDERING NOW!**

**£4** Carr.  
Paid

**M.O.S.**

MAIL ORDER SUPPLY CO. (Dept. PW), 24, New Road, London, E.1. Stepney Green, 2760-3906

# Practical Wireless

16th YEAR  
OF ISSUE

EVERY MONTH  
VOL. XXIV, No. 499, FEBRUARY, 1948-

and PRACTICAL TELEVISION

Editor F. J. CANN

BY THE EDITOR

COMMENTS OF THE MONTH

## A Recording Development

**I**N a paper on the Development of Sound Recording and Production Sir Ernest Fisk dealt with transient pulses for the attainment of the highest standard of fidelity. He explained how the frequency distribution of these irregular non-repeating wave-forms determines the tonal character of a particular sound.

These transient pulses are known to extend well up to the top limit of human hearing and even into the supersonic range. He stated that for the first time in the history of sound science frequencies of up to 20,000 cycles per second were now being recorded on gramophone records. This development will have an important bearing on the future of television recording.

This important development in the science of sound recording and reproduction means that every note and every tonal characteristic detectable by the human ear in an original performance can now be heard with equal fidelity off a gramophone record.

The upper frequency response limit of the human ear is a factor which varies enormously with the individual and according to age. Few people can detect frequencies above 15,000 cycles per second.

He made an important statement concerning the accusations sometimes made that the gramophone industry is holding back development of sound recording methods on film and tape, etc., in order

to protect their investment in the disc manufacturing business. He revealed that the biggest companies here and in America are spending large sums in research and development in connection with these new systems, and although he thought that for certain purposes they would become universally employed he did not think they would ever take the place of the disc record, having regard to the ease with which the latter could be mass-produced. On this point we disagree with him.

A gramophone using a photo-electric cell and a strip of celluloid containing a sound track was shown at one of the exhibitions some years ago. It was very successful scientifically speaking, and a few of them were sold to the public. The company was, however, bought out, and the invention "killed."

There were no needles or wind-

ing of motors. Several hours performance could be recorded on a coil of celluloid occupying no more space than a 12in. record. Excellent though the disc method is and although we agree that it will not entirely vanish, we feel that it is going too far to say that nothing will ever replace it.

### Poor Inspection

**A** COLLEAGUE of ours who owns a commercial portable receiver recently found it necessary to replace the mains transformer, which had burnt out. He sent to the manufacturers for a replacement, correctly quoting the type number. With commendable celerity the new transformer arrived. Although it was marked "passed and checked" it had been wrongly connected, and had our friend not possessed technical knowledge its installation in the receiver would have caused considerable damage.

Many factories adopt what is known as "batch inspection"—that is to say, only one component out of a hundred is submitted for test. This may be good enough in the case of certain components, such as mechanical parts, but certainly is not good enough for valves, transformers or condensers. The standard of inspection in the radio industry could usefully be raised. There are many complaints.

### Broadcasting in Schools

**I**N a letter sent to local Education Authorities in England by the School Broadcasting Council for the United Kingdom it is stated that the biggest weakness in the school broadcasting service is the quality of the reception in the schools.

The object of the letter is to improve the quality of the reception, for the use of school broadcasting can be fully justified only when its reception is natural and undistorted and can be heard by the whole class without strain. Good reception in schools depends on awareness of the special problems of school reception, the choice of suitable apparatus, the method of installing the apparatus and efficient maintenance.

The method of installing apparatus is as important as its selection. The Council have, therefore, arranged to give demonstrations.—F. J. C.

Editorial and Advertisement Offices:  
"Practical Wireless," George Newnes, Ltd.,  
Tower House, Southampton Street, Strand,  
W.C.2. Phone: Temple Bar 4963.  
Telegrams: Newnes, Rand, London.  
Registered at the G.P.O. for transmission by  
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

# ROUND THE WORLD OF WIRELESS

## Blood Donors

**A**N appeal for blood donors after the Southern Railway accident at South Croydon recently met with an immediate response from the Mullard Radio Valve Co., Ltd., of Mitcham, Surrey. It occasioned a letter of thanks from Dr. Murphy himself, the director of the National Blood Transfusion Service.

In it he said: "I should be very grateful if you would convey to each donor who came forward on Saturday my thanks for their donation of blood and, in the case of some, for bringing new potential donors along with them."

## Radio Telephones Move

**T**HE radio telephone services, which used to be operated from the International Exchange at Faraday Building, were recently transferred to the Wood Street Building, E.C.1.

Since the end of the war the traffic from this country to the Continent of Europe has increased to such an extent that it has become necessary to transfer out of Faraday Building, Queen Victoria Street, the radio telephone service to the Empire, the United States of America and South America.

## Radio for Fishermen

**A**NGLERS fishing off Long Island, New York, report their catches to each other across the bays and inlets.

If there are any *hungry* fish in the place their location is reported on the new two-way communication units and everybody catches more. All this takes place on the 2,100 to 2,738 kc band.

## Radio Taxi Service

**L**ONDON'S first radio-taxi system, providing two-way communication between driver and a booking office recently came into operation. It is estimated that by being able to call and re-direct a cab 50 per cent. "dead mileage" petrol will be saved. There are 12 cabs belong to Cosyears, of Streatham, and preliminary reports show that the scheme works very well up to a range of 15 miles.

## Radiced Royal Wedding Pictures

**T**HE largest volume of traffic in the 21 years' history of phototelegraphy was stimulated by world interest in the Royal Wedding on November 20th. During the 32 hours between 4 p.m. on November 19th and midnight, November 20th-21st, Cable & Wireless, Ltd., who trebled the staff of their facsimile room at Electra House for the occasion, received 271 photographs from overseas press correspondents in London. Fifteen of these were cancelled after transmission—49 before transmission—to make way for better pictures filed later. In all, Cable & Wireless transmitted 222 pictures to 15 countries: 77 went to New York, 73 to Australasia, 33 to Capetown, 12 to Stockholm, eight to Buenos Aires, and smaller numbers to Bombay, Bermuda (the latter inaugurating the new London-Bermuda service), Cairo, Colombo, Malta, Montreal, Rome and Vienna. Wedding pictures received via Colombo were the first phototelegrams ever received in Wellington, New Zealand.

## Lecture on "Industrial Radiology"

**R**ECENTLY, Mr. R. H. Cooke, M.S.R., of the Industrial X-Ray Dept., Philips Electrical, Ltd., gave a lecture to members of the Institute of Electronics on "Industrial Radiology." The lecture, held in the rooms of the Royal Society of Arts, was illustrated by slides and surveyed the uses of X-rays in industry and their various applications.

Mr. Cooke began his address by discussing the historical aspect of the discovery of X-rays. He then proceeded to trace the origin and propagation of these rays and the consequent development of the X-ray tube. Next, he dealt with the various types of industrial X-ray apparatus in use at the moment, at the same time giving a full description of the many factors involved in industrial radiology, such as the processing of the X-ray film.

In conclusion, Mr. Cooke gave some interesting examples of how X-rays are being utilised by an ever-increasing number of industries.



Col. Sir Stanley Angwin, K.B.E., making the opening speech at the Amateur Radio Exhibition. Also in the picture are S. K. Lester, President of the R.S.G.B., John Claricoats, and H. Freeman, Exhibition Organiser.

## The Radio Industries Club

FOLLOWING the success of the Radio Industries Ball, held at the Royal Albert Hall on October 3rd, the committee of the Radio Industries Club at their last meeting decided that a Radio



At the radio-taxi booking office, in Streatham, London. Cars can be called and re-routed without returning to their H.Q.

Industries Ball should be made an annual event to be held under the auspices of the club, the date and place to be varied according to circumstances.

## 20 Years on Radio

DONALD PEERS, well known to radio listeners and theatre audiences in London and the provinces as the cavalier of songs, celebrated 20 years of broadcasting when he sang in Music Hall on December 20th. His rich baritone voice was first heard by cat's whisker fiddlers in 1927, when he broadcast from 2LO on December 17th of that year. Since then his signature tune, "By a shady nook, by a babbling brook," has become a national ballad.

For the future, Donald Peers, whose name sold over half a million gramophone records in 12 months, has made it his policy to sing "particularly pleasing" songs. By that he means songs to suit family audiences and numbers easily understood. It is for this type of singing that he has already earned a well-deserved reputation.

## Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ended October 31st, 1947.

Region	Number
London Postal .. ..	2,062,000
Home Counties .. ..	1,443,000
Midland .. ..	1,563,000
North Eastern .. ..	1,696,000
North Western .. ..	1,444,000
South Western .. ..	948,000
Welsh and Border .. ..	624,000
<i>Total England and Wales</i> .. ..	<i>9,780,000</i>
Scotland .. ..	1,048,000
Northern Ireland .. ..	170,000
<i>Grand Total</i> .. ..	<i>10,998,000</i>


The above total includes 27,850 television licences—an increase of 2,800 over the previous month.

In spite of the steady increase in the number of licences, the Post Office is constantly detecting unlicensed sets, and during October, 1947, there were 626 prosecutions.

The requirement that each separate family or household using wireless apparatus in a house, part of a house or flat should have a licence applies not only to those who have bought their own sets, but also to those using sets which are rented or hired.
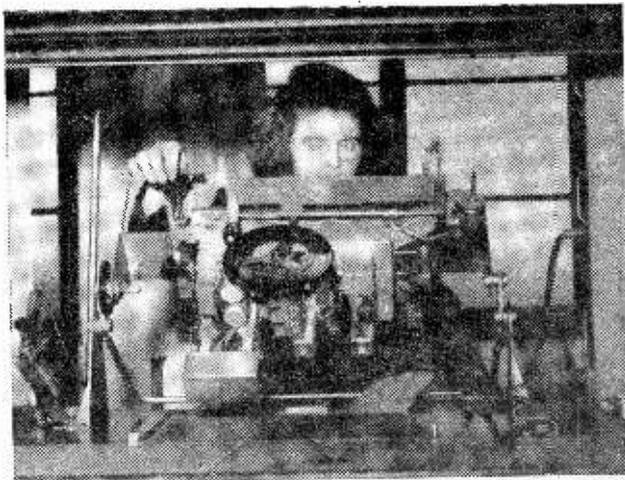
## Australian Amateur F.M.

AMATEURS in Australia have been granted permission to employ frequency modulation for transmissions between 27.185 and 27.453 Mc/s, on 50 Mc/s and above. Pulse transmission is permitted on, and above, 166 Mc/s.



"Kongress" Radio receivers are now being mass produced in Czechoslovakia. Note the chassis cradle for easy handling.

# Novel Battery Circuits-1

How Economies May be Effected Without Sacrificing Efficiency. By C. SUMMERFORD

THE experimenter who, because of location or for other reasons, has to derive the power supply for his receivers from batteries is at a great disadvantage as compared with the more fortunate mains user, and because of this is always ready to consider using circuits which could be called battery savers, provided this latter is not achieved at the expense of efficiency.

An unfortunate use of the word "freak" in describing circuits which are somewhat out of the ordinary tends to give the impression that such circuits are tricky, unstable or generally inefficient, and, although there may have been some justification for this belief with the older types of circuit, nowadays, with modern valves and components, these uncommon circuits can be made to give excellent results. In this article, therefore, it is hoped to show just how efficient these "freak" circuits can be with proper design and, although the four circuits shown are "paper" designs only and are intended as a basis for further experiments, there is little likelihood of trouble being experienced by constructors who build receivers around any of these circuits.

The increasing popularity of all-dry receivers has led valve manufacturers to devote considerable time and energy to the design of efficient and economic 1.4-volt valves. One such valve, the American 1D8GT, is a good example of what has so far been accomplished. This particular valve is one of the three-in-one type having the functions of diode, triode and output pentode and takes a filament current of 100 milliamps, with a total H.T. consumption of about 6.5 milliamps at 90 volts.

## One-valve Reflex

By disregarding the diode section and using the triode and pentode sections only we can design a most efficient one-valve reflex receiver, as shown in Fig. 1. Apart from the use of a single valve instead of the more usual two, the circuit follows normal reflex practice. However, for the sake of those who are not conversant with

this type of circuit we will briefly trace the signal through the whole receiver.

R.F. signals are applied to the grid of the pentode section (which acts as an R.F. amplifier of slightly lower efficiency than would be the case were a normal R.F. valve used) and after amplification are taken from the pentode anode circuit and transferred by choke-capacity coupling to the grid circuit of the triode section, which is used as a grid-leak detector.

So far the circuit has followed normal practice, but now comes the more unusual part. Instead of using a further valve for amplifying the rectified signals appearing at the detector anode, use is made of the pentode section again for carrying out

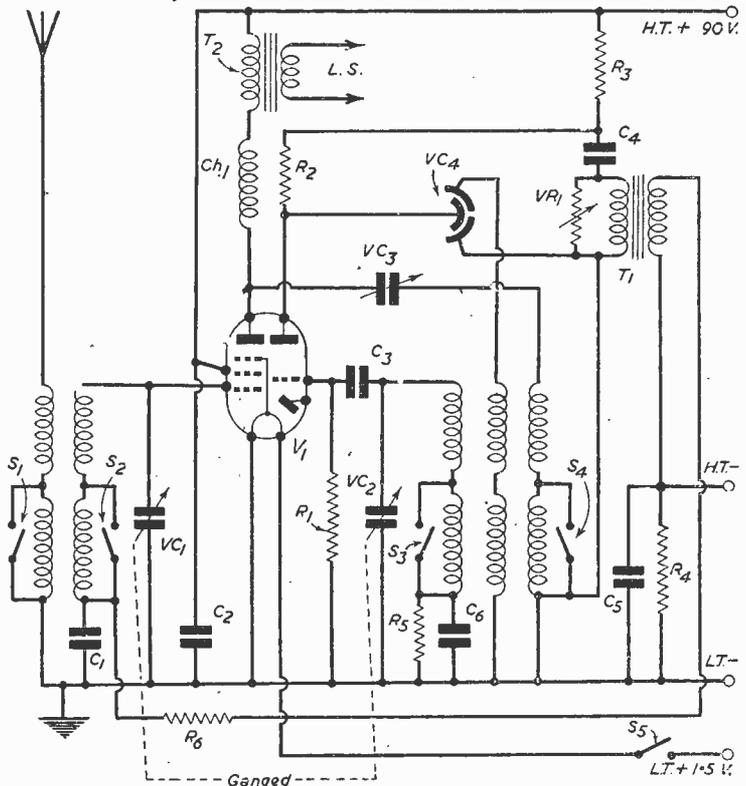


Fig. 1.—An efficient one-valve reflex receiver.

## SUGGESTED COMPONENTS Fig. 1.

- |                          |   |
|--------------------------|---|
| VI—American 1D8GT.       | R1—1 meg., $\frac{1}{2}$ watt.          |
| C1, C6—.003 $\mu$ F.     | R2—20,000 ohms, $\frac{1}{2}$ watt.     |
| C2, C4—.1 $\mu$ F.       | R3, R6—50,000 ohms, $\frac{1}{2}$ watt. |
| C3—.0002 $\mu$ F.        | R4—850 ohms, $\frac{1}{2}$ watt.        |
| C5—10 $\mu$ F. elec.     | R5—5,000 ohms, $\frac{1}{2}$ watt.      |
| VC1, VC2—.0005 two-gang. | VR1—50,000 ohms. potentiometer.         |
| VC3—.0005 preset.        | T1—1 : 4 parafeed transformer.          |
| VC4—.0003 diff.          | T2—To suit speaker.                     |

this function. Thus we have the pentode section of the valve being used as R.F. amplifier and output valve, with the triode section as detector. Coupling between detector and output stage is by parafeed transformer, the normal grid connection of the transformer being taken to the junction of the aerial tuning coil and isolating condenser. As this condenser is virtually in shunt with the secondary of T1 it should not be larger than about .003  $\mu$ F. or reproduction will be rather lacking in top response.

However, the actual capacity is rather dependent on personal taste—and on the type of loudspeaker used—and if different values are tried until the desired response is obtained no filter will be needed across the primary of the output transformer. Actually, the figure given above is about the right capacity in most cases. C6, which is used in conjunction with R5, is inserted to maintain reasonably accurate ganging and should be of the same capacity as C1.

Working under maximum conditions, i.e., with 90 volts H.T. on anode and screen, the pentode

A.F. amplifier gives an output of approximately 200 milliwatts.

By inserting a resistor (R4) in the E.T. negative circuit automatic bias is provided for the pentode section. R4 should be shunted with an electrolytic of not less than 10  $\mu$ F. in order to prevent negative feedback taking place at audio frequencies.

**Additional L.F. Stage**

A similar circuit is shown in the diagram of Fig. 2, but with the addition of a triode A.F. amplifier between detector and output.

Suitable valves for this extra stage are the American 1E4G or 1E4. As, however, neither of these valves is very easily acquired at the moment, it is suggested that a 1H5G is used instead. This valve is really a diode triode, the triode portion of which is of much higher impedance than the above-mentioned types. Notwithstanding this, no trouble should be experienced, provided the anode circuit is adequately decoupled.

The stage may discriminate somewhat in favour of the higher audio frequencies, due partly to the

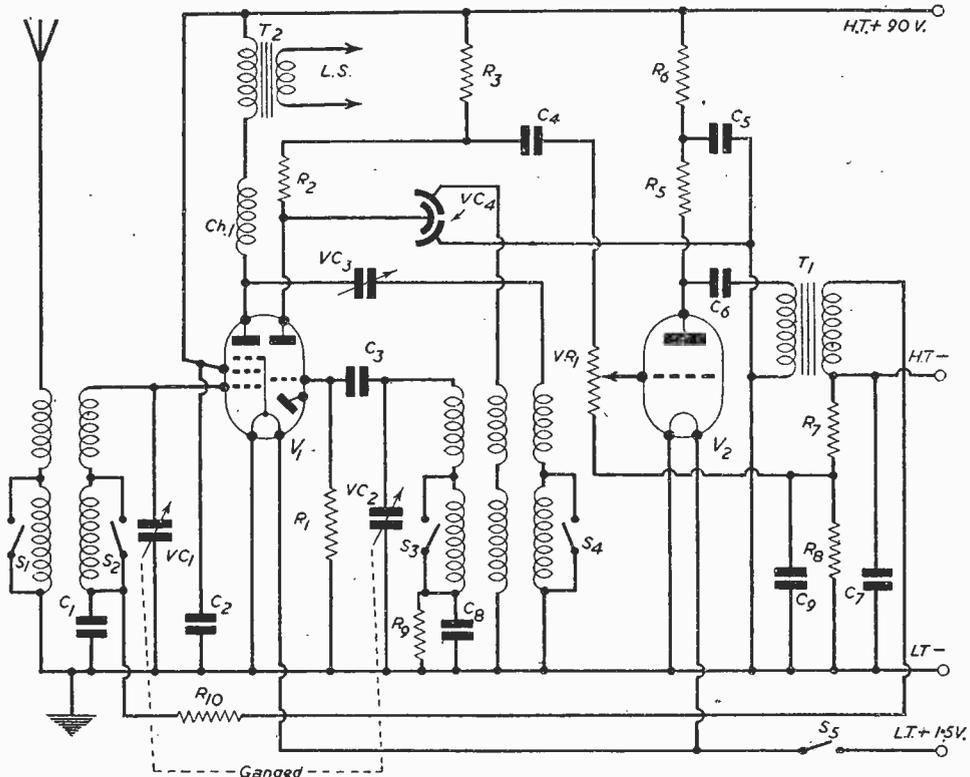


Fig. 2.—The arrangement of Fig. 1 with an additional stage and auto-bias.

**ADDITIONAL COMPONENTS REQUIRED Fig. 2**

- |                          |                    |                              |
|--------------------------|--------------------|------------------------------|
| V1—5 mcg. potentiometer. | V2 1H5G {          | R5—100,000 ohms, ½ watt.     |
| R5—50,000 ohms, ½ watt.  |                    | R6—50,000 ohms, ½ watt.      |
| V2 1E4 {                 |                    | R7 plus R8—800 ohms, ½ watt. |
| R6—20,000 ohms, ½ watt.  |                    |                              |
| R7—350 ohms, ½ watt.     | C4—.01 $\mu$ F.    |                              |
| R8—400 ohms, ½ watt.     | C5—2 $\mu$ F.      |                              |
|                          | C—10 $\mu$ F elec. |                              |

high valve impedance and partly to the high value anode load resistor used. Correct balance can, however, be restored by increasing the capacity of C1. It should be borne in mind that an increase in the capacity of C1 also entails a similar increase in the capacity of C8, otherwise accurate ganging will not be obtained. The remainder of the circuit is self explanatory.

### Three-valve Superhet

Use is made yet again of the 1D8GT in the circuit shown in Fig. 3, but this time in a more normal manner, i.e., as detector, A.V.C. and output valve. The one other valve used in this circuit is a Cossor 1A7VG frequency changer.

In a recent article it was shown how the normal I.F. valve in a superhet receiver could be dispensed with by using a regenerative leaky grid detector in place of the more usual diode. As the saving both in initial expense and in H.T. and L.T. consumption is fairly considerable, use has again been made of this system here.

Taking the circuit in more detail: From the aerial to the anode of the frequency changer normal superhet practice is followed, but in place of the usual two winding I.F. transformer coupling the frequency changer to the following stage is a three winding type such as the Bulgin C51. By using the third winding as an ordinary reaction coil and controlling regeneration with a variable condenser of .0005  $\mu\text{F}$ , an enormous increase in I.F. gain may be obtained—so much so that the absence of the normal I.F. amplifier is not noticed.

A condenser of .0003  $\mu\text{F}$  is connected between the detector anode and diode to provide an I.F. signal at the diode anode for A.V.C. purposes. A.V.C. is of the simple undelayed variety and is applied to the input grid of the frequency changer via the tuned circuit. The controlling of one valve only by A.V.C. is hardly adequate, however, but by returning the earthy end of the detector grid leak to the A.V.C. line we can obtain not only excellent A.V.C. but automatic selectivity also.

(To be continued.)

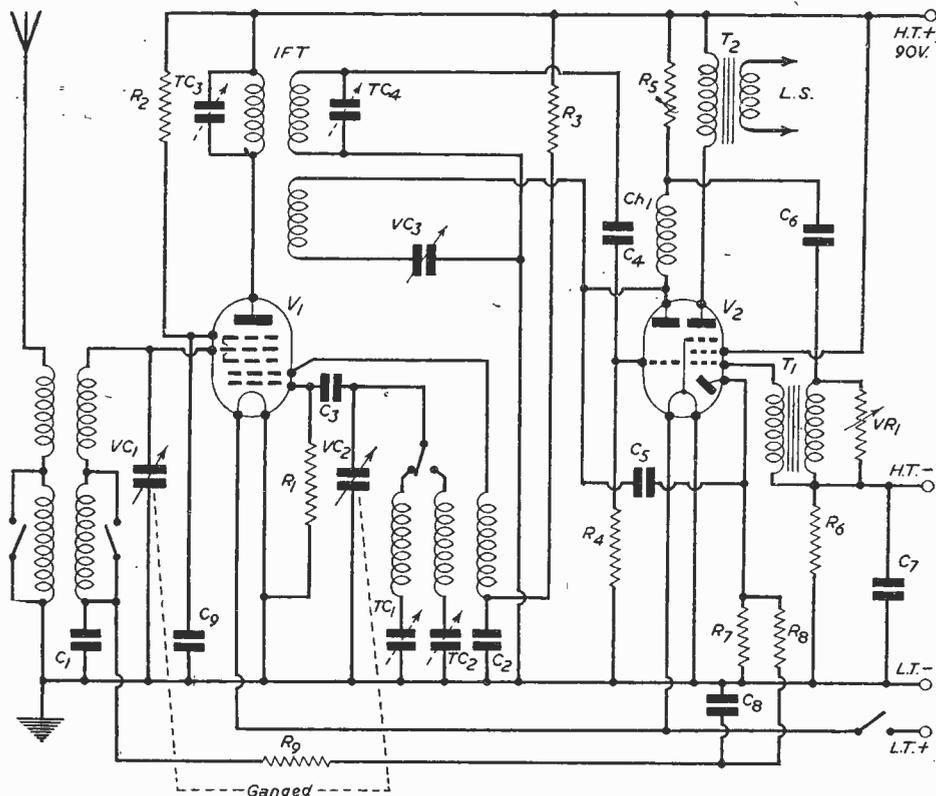


Fig. 3.—A superhet circuit with only two valves.

### COMPONENTS REQUIRED

V1—Cossor 1A7VG.  
 V2—American 1D8GT.  
 VC1, VC2—.0005 two-gang.  
 VC3—.0005 mica diel. variable.  
 TC1, TC2—M. and L.W. padders.  
 C1, C8—.05  $\mu\text{F}$ .  
 C2, C3, C6—1  $\mu\text{F}$ .  
 C4, C5—.0002  $\mu\text{F}$ .

C7—10  $\mu\text{F}$  electrolytic.  
 IFT—Bulgín C51.  
 T1—1 : 4 parafeed transformer  
 T2—To suit speaker.  
 R1—100,000 ohms.  
 R2—40,000 ohms.  
 R3—5,000 ohms.

R4— $\frac{1}{2}$  meg.  
 R5—75,000 ohms.  
 R6—550 ohms.  
 R7—1 meg.  
 R8— $\frac{1}{2}$  meg.  
 R9—1 meg.  
 All resistors  $\frac{1}{2}$  watt type.

# Practical Television Construction—2

Planning the Layout, and Designing the Power Pack are Dealt With This Month

By W. J. DELANEY (G2FMY)

**L**AST month we dealt with the main features of a modern television receiver, and we now come to the most important part, namely, the question of layout and construction. The modern broadcast receiver is generally built on a single chassis, but quite a number of manufacturers adopt a scheme much favoured by home constructors, namely, the separate construction of receiver and amplifier. In many cases, it is found that it is even worth while also to separate the mains unit, as not only does this facilitate modifications in design from time to time, but also enables one to carry out servicing tests much more easily. It has been shown that the television receiver is a complicated piece of apparatus, and therefore when we come to the question of design, we must bear in mind the facts already covered. There are two time bases to be lined up, a receiver to be adjusted for the satisfactory reception of the vision signal, and one for the sound, as well as the power supplies. There is thus every incentive for the complete receiver to be built as a series of separate units and, in fact, this is the principle which is adopted in many of the better class of commercial receivers. The only drawback from the amateur point of view is that the actual constructional work seems more tedious and there is some risk of trouble when it comes to connecting up the separate units.

## Five Units

Experiment has shown that the most satisfactory scheme for the home constructor is a five unit combination, the two receivers being made up as one unit, the two time bases separated and the remaining two units consisting of the actual tube assembly and the power pack. It might be argued that if the two receivers are combined, why could not the two time bases be similarly combined. The answer to this is that to economise on valves, and also to simplify operation it is desirable to build the receiver so that the early valves operate both on sound and vision frequencies. Thus, to avoid long leads carrying H.F., it is desirable to have the sound receiver input close to the H.F. stage(s) which is carrying both frequencies, and the screening of two radio units is not a difficult matter. On the other hand, any leakage of energy in the time bases may result in difficulty in obtaining a steady picture, as nothing is worse than line frequencies leaking into the frame scanner. The sync. stage or stages can be combined in one of the time bases, or may follow on the vision radio chassis, and this is not difficult to arrange.

## H.T. Supply

On the power pack side there are one or two points to receive attention. The E.H.T. winding may be carried on the main transformer, but this will necessitate the purchase of a specially wound component. On the other hand, a single E.H.T.

transformer is not a very expensive item, and then standard mains transformers may be used for the rest of the unit. If hard valve time bases are employed some difficulty may be experienced in feeding the heaters, but simple chokes may be included in the heater circuit after tests if found desirable.

The amplifier associated with the time bases may include a large type of power valve requiring up to 450 volts H.T., and in view of the heavy H.T. current drain it may be found necessary to use two rectifying valves in parallel. It is the writer's opinion after tests that if one has to purchase two rectifiers it is better to make the H.T. unit in two sections, one delivering, say, 300 or 350 volts for the circuits calling for a working voltage of 250 volts (allowing for the voltage drop through decoupling circuits), and one delivering a higher voltage for the P.A.s. In this way the current called for may be split up amongst the two valves, and better voltage regulation is obtained and certain risks of interaction are avoided. If the separate mains transformers also carry low-voltage heater windings then the L.T. supplies may also be split up and this will be found an advantage in some circuits.

## Final Layout

Having decided that the final receiver will consist of five units, the only question that arises is how they should be disposed in the final design. Certain panel controls must be provided, and the C.R. tube assembly must be arranged more or less as a centre piece. There are controls on the time bases and also on the radio receivers. But some of these may be treated as "pre-set" controls and may quite conveniently be tucked away as they will not be needed once the receiver has been set up. Opinion differs as to just what should be called a "panel control." If a good strong signal is received (and the receiver and aerial system may be so chosen and designed that a suitable signal is received), then there should be no need to want to touch any of the time base controls after the initial setting up. Picture width and height, and the "hold" controls should stay put if the design is good, and that leaves only radio controls to consider, plus the necessary tube control. To safeguard the tube, and to get the best picture result, the control of bias on the tube must be a panel control. This is generally labelled "Brilliance" and should be combined with the on/off switch so that when switching off the picture is blacked out first. Similarly, when switching on the control should be turned up only after a picture has been allowed for all valves to attain their working temperature. Again, control of focus should be fitted for the vision and sound frames. In practice it is usually found that once the receiver is

set up in a certain position there is very little variation in strength except on the edges of the reception area, and thus a vision or "volume control" is not a necessity. On the sound side it is desirable to turn down the volume on certain items and turn it up on others, so that a sound control is also desirable on the panel. One other control is found desirable on the panel and that is a focus control. Rising temperatures in the equipment do vary the focus and it is found that during a programme it may be necessary to adjust this, so that leaves three panel controls, or four on the fringes of the reception area.

#### Suitable Sockets

Each unit should be terminated in a multi-socket or with flexes fitted with a plug, and the unit which

follows it should be so wired that the two may be joined easily, without the risk of connecting the wrong units together. The Belling-Lee multiple plugs are ideal for the purpose. The sizes of the units should be such that they fit round one another, and as the output from the V.F. amplifier to the tube must be short, the "end" of the vision receiver should obviously be near the C.R. tube base. This means that the input or aerial connector must be at the opposite end, and this calls for the unit (in view of its overall size) to run the depth of the complete receiver, lying by the side of the tube. The sound receiver can lie along the front of the C.R. tube chassis, tucked behind the tube front, and the time bases can then run along the other side of the complete assembly, with a multiple connector at the rear, joined to the tube holder.

## Flying Relay Stations

**I**NTERNATIONAL air liners have formed their own chain of flying radio relay stations across the North Atlantic for an experimental period of six months, under plans drafted by a technical working group of the International Air Transport Association (I.A.T.A.).

The relay system operates on a V.H.F. radio band during periods when normal H.F. transmission is interrupted by magnetic disturbances. It is expected to help increase regularity of service over one of the most important world air routes.

Plans for the V.H.F. relay were completed by the North Atlantic Communications Working Group of the I.A.T.A. Technical Committee, made up of airline experts, which has been studying improvement in the high standard of communications service on the North Atlantic in the light of the last year's experience.

Under normal conditions, the range of H.F. transmission is great enough to enable planes to transmit their regular hourly weather and position reports and other operational messages directly to ground stations on either side of the Atlantic. The range of V.H.F. transmission is much shorter, but the relay plan will enable aircraft to pass messages on from one to another until they come within range of a ground station.

Beginning at one minute after midnight on December 15th, crew members of scheduled air liners over the North Atlantic started to maintain a constant watch on V.H.F. bands to intercept messages and pass them on during periods of H.F. blackout, to notify each other of any changes in the service.

The world airline organisation has normally enough I.A.T.A. air over the ocean at any complete relay chain. If ships stationed on the North Atlantic fill in.

International Civil Aviation provisions for serving the North Atlantic, the

I.A.T.A. group suggested the following alterations to arrangements drafted at the I.C.A.O. Dublin conference in April, 1946:

Rearrangement of frequencies so that ground stations need not handle more than eight communications channels at one time.

Transfer of weather reports to other than route frequencies in order to reduce the load on present circuits.

Broadcast of weather reports by major terminals to include reports of alternate airports as well, in order to keep to a minimum the number of stations on the air at any one time.

In order to relieve an overload on channels now used for the so-called "middle route" from North America to Europe via Shannon, Eire, the I.A.T.A. airlines have informally agreed among themselves to a distribution of the groups of frequencies each will use for normal operational messages.

#### Consol Beacons

I.C.A.O. was strongly urged to expedite the building of Consol radar beacons in Norway, Northern Ireland, Iceland, the Azores, Newfoundland and Bermuda, particularly because the existing North Eastern chain of Loran beacons, an alternative radio device, may have to close in 1949 when radio channels may no longer be available to them. Use of Consol was agreed upon by governments taking part in the Dublin meeting.

The I.A.T.A. group's arrangements will affect North Atlantic operations of the following I.A.T.A. member airlines: Aerline Eireann (Eire), Air France, American Overseas Airlines, British Overseas Airways, K.L.M. Royal Dutch Airlines, Pan-American World Airways, Sabena (Belgium), Scandinavian Airlines System, Swisair, Trans-Canada Air Lines, and Trans-World Airline (U.S.).

The working group is headed by W. A. Schrader, of A.O.A., while its secretary is Stanislav Krojcek, assistant secretary of the I.A.T.A. Technical Committee. Its meetings here were attended by several observers for I.C.A.O.



# ON YOUR WAVELENGTH

By THERMION

## F. J. C. at I.P.R.E. Annual Dinner

THE first annual dinner of the Institute of Practical Radio Engineers was held at the Connaught Rooms in October. But for pressure of space and early press days I would have recorded this notable event before, because I feel that this Institute is a live body of great value to the industry and a forum for those of kindred radio interests having the necessary qualifications to meet and to disseminate their knowledge and experience. It is a radio parliament and a pool of knowledge.

In his opening remarks, the then president-elect, Mr. J. F. Tomlin, stated that one of the primary aims of the Institute was to raise the standard and status of service engineers. Their efforts have met with considerable success.

Mr. F. J. Camm, in proposing the toast of the Institute, said that a body with 800 members and 900 students was already a force with which to reckon. He expressed the hope that the high standards already set would be maintained, and that membership of the Institute would continue to be recognised as a hall-mark of knowledge and integrity.

The question of apprenticeships was a matter to which the Institute might give consideration. The guests included: Dr. J. E. C. Hughes, A.C.G.I., D.I.C., B.Sc., Ph.D., A.M.I.E.E., and Mr. H. A. Curtis, F.C.I.S., Secretary of the R.T.R.A. Mr. Curtis said that the I.P.R.E. was fulfilling a function the importance and value of which was fully recognised by his Association.

Mrs. B. A. Smye-Rumsby, A.I.P.R.E., at present the only lady member of the Institute, made a plea for more women service engineers, quoting the wartime activities of women in the Services as justification.

The occasion was marked by the election of Mr. F. J. Camm to an honorary fellowship of the Institute in recognition of his long and valuable services to the industry.

I can certainly recommend all readers with the necessary qualifications to join this Institute which daily gains in prestige and membership.

## A Note for the Malady Maker

THE *Musical Express* has for a long time been criticising another musical journal whose policy I facetiously labelled as Malady Making. In these days of paper shortage I should have thought the malady maker could have devoted some of its space to answering these well-directed criticisms. Instead, they devoted a leading article to yours truly, criticising and, of course, disagreeing with my criticisms of clap-trap drummers, jazz, and crooning generally. You will remember that I replied to this criticism, since when the malady-maker has remained as silent as it did over the *Musical Express*. The managing editor of this latter journal wrote to thank me for my comments.

## A Ballad Singer

I was interested to see that Josef Locke, since his debut with Columbia in August, has become one of the most popular singers in the lists. There is something in the way he puts a song over that has caught the imagination of listeners: the secret is indefinable, but certainly two cardinal ingredients must be a really fine voice plus a lively microphone personality. Ballad is Locke's speciality, though he has had experience in other branches, notably opera. His public will find him this month among the Victorians. The combination "Weatherly-Adams" means fine examples of those songs, some sacred, which delighted the drawing-rooms of the end of the last century. F. E. Weatherly, Oxford tutor, Bristol lawyer, and highly popular author of many lyrics, and Stephen Adams, prolific composer of ballads, have produced two very charming songs for Josef Locke in "Star of Bethlehem" and "The Holy City."

## The Tele-record

MANY "viewers" were interested when the B.B.C. gave a repeat programme of the morning's Remembrance Day ceremony at the Cenotaph; technicians at Alexandra Palace filmed the service from the television screen. The method is, of course, temporary and has its limitations. We do not agree with a morning newspaper which claimed that the method made television "history."

## Guild of Radio Service Engineers

THE Guild of Radio Service Engineers (G.R.S.E.) in the current issue of their journal, which now enters its second year, deals with the methods adopted by some of its members during the power cut last winter. The arrangements made varies from the staggering of hours to the use of gas-heated soldering-irons, battery-operated rotary converters, and the use of battery-operated oscillators to give a signal when the B.B.C. was off the air.

## B.B.C. WEATHER FORECASTS

"Weather will be fine in all parts of the British Isles, except where it is dull and cloudy, with patches of rain turning to drizzle or drizzle turning to rain. Rain in north spreading south, and rain in south spreading north. Visibility will be good except in areas of fog which are probable between Iceland, Shetlands and Biscay. Temperatures will be higher or lower than of late. A ridge of low pressure is stationary over mid-Atlantic and rapidly approaching our western seaboard, with ridges of high pressure following in its train."

It's that, or something like it,

Four times every day,

And these oft-repeated forecasts

Steal our programme time away.

We prefer more entertainment,

It is that for which we pay.

Weather forecast's deadly boring

When broadcast four times each day.

"TORCH"

# Cathode-ray Tube Data

**I**N response to our request in the December issue for data relative to Service cathode-ray tubes, we have received many interesting lists and details from our readers.

General Notes on Service Cathode-ray Tubes which are Now on the Market, and Some Circuits in which They May be Used

varied in different models and we therefore do not give the actual contacts for all of the types of base. It is, however, not a difficult matter to trace out the leads if the tube is purchased already fitted in some piece of apparatus. In general, the 12-pin

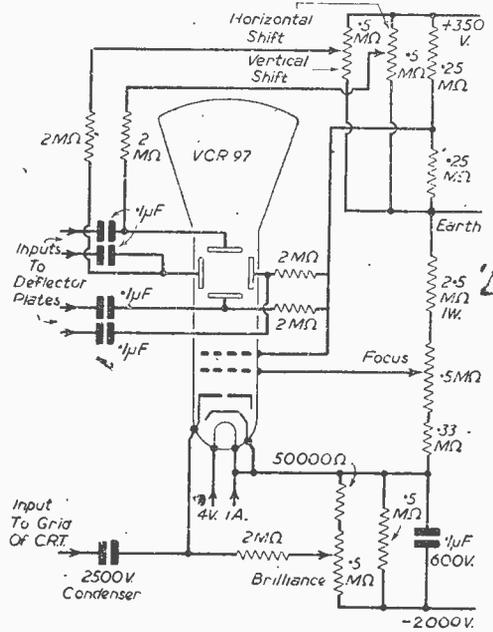


Fig. 1.—Typical circuit for the VCR97 and its equivalents.


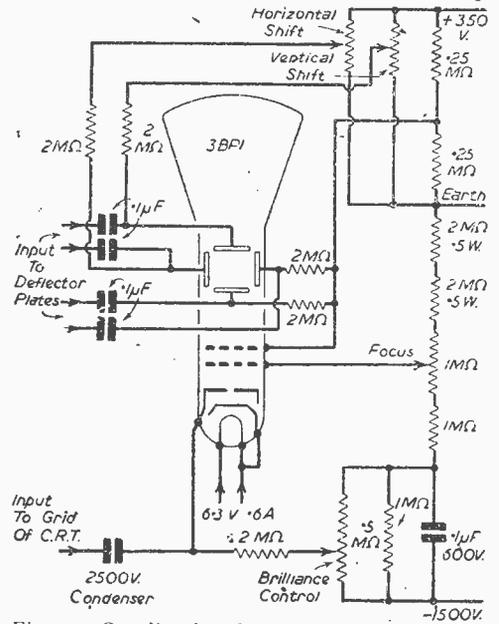


Fig. 2.—Supplies for the 3BP1 are shown here.

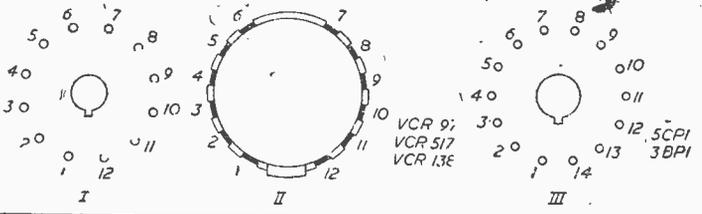These have been analysed and the important material collated so as to form a useful list for the experimenter, and this will be found on page 58. It should be pointed out, however, that some of the base connections are



Tube Type	Voltage A1	A2	A3	Grid V. Normal	Cut off	Base Connections														Side cap	Dia.					
						1	2	3	4	5	6	7	8	9	10	11	12	13	14							
VCR97	2,000 max.	250-450	—	-30	-100	G	C	H	H	—	A <sub>2</sub>	—	Y <sub>2</sub>	X <sub>2</sub>	A <sub>1</sub>	X <sub>1</sub>	Y <sub>1</sub>	—	—	—	—	—	—	—	6in.	
VCR517	2,000 max.	250-450	—	-30	-100	G	C	H	H	—	A <sub>2</sub>	—	Y <sub>2</sub>	X <sub>2</sub>	A <sub>1</sub>	X <sub>1</sub>	Y <sub>1</sub>	—	—	—	—	—	—	—	—	6in.
VCR138	1,500 max.	300 approx.	—	-20	-60	G	C	H	H	—	A <sub>2</sub>	—	Y <sub>2</sub>	X <sub>2</sub>	A <sub>1</sub>	X <sub>1</sub>	Y <sub>1</sub>	—	—	—	—	—	—	—	—	3½in.
VCR139, ACR10	800 normal	120-130	—	-6	-12	C	G	H	H	A <sub>2</sub>	—	Y <sub>2</sub>	X <sub>2</sub>	A <sub>1</sub>	X <sub>1</sub>	Y <sub>1</sub>	—	—	—	—	—	—	—	—	—	2¾in.
3BP1	1,500	430 approx.	—	-30	-45	H	C	G	—	A <sub>2</sub>	—	Y <sub>1</sub>	Y <sub>2</sub>	A <sub>1</sub>	X <sub>1</sub>	X <sub>2</sub>	—	—	—	—	—	—	H	—	—	3in.
5CP1	1,500	430 approx.	3,000	-30	-45	H	C	G	—	A <sub>2</sub>	—	Y <sub>1</sub>	Y <sub>2</sub>	A <sub>1</sub>	X <sub>1</sub>	X <sub>2</sub>	—	—	—	—	—	—	H	A <sub>3</sub>	—	5in.

The first four tubes are of the 4v filament type and the last two are rated at 6.3v 0.6a.

side-contact base has the modulator taken to pin 1 and the heaters to pins 3 and 4. A1 is pin 5, A2 pin 6 and A3 pin 10. The coating is generally found on pin 7, whilst X and Y plates may be found at various points on the remainder of the connections or "top cups."

This +1,500 can easily be obtained by the use of a doubler circuit with the junction of the doubler condensers taken to earth.  
A method of obtaining E.H.T. of about -900 volts, which is ample for such tubes as the VCR139, is shown in Fig. 3. Here a 250-0-250 transformer,

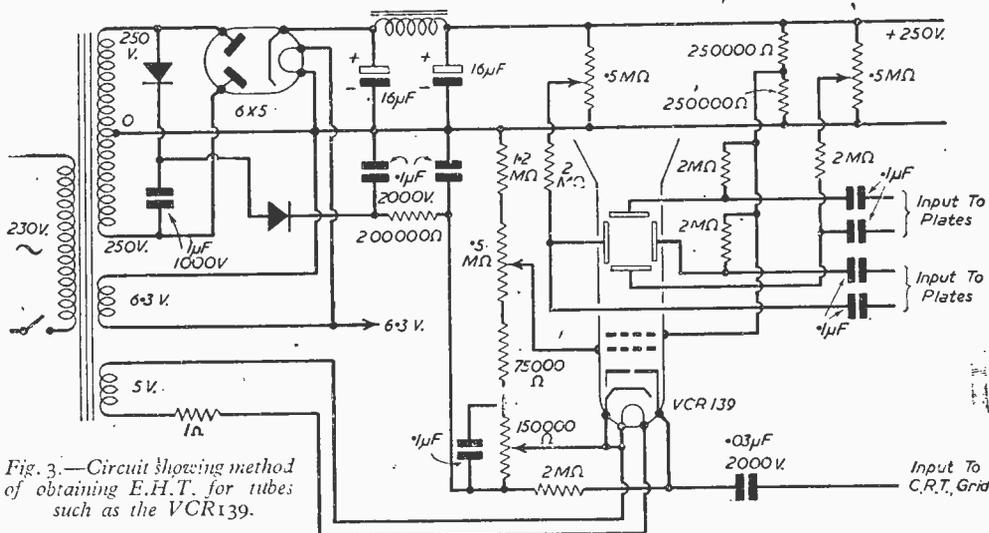


Fig. 3.—Circuit showing method of obtaining E.H.T. for tubes such as the VCR139.

It may be stated as a more or less general rule that all tubes except the VCR97 have short or medium afterglow, the 97 having a long afterglow.

**Circuits**

In the illustrations, circuits for the supplies to the electrodes of the VCR97, 139 and 3BP1 are given. The 5CP1 can be used in a similar circuit to the 3BP1, except that it requires a voltage of 3,000 volts (+1,500 to earth) on its third anode, which is brought out to a clip on the side of the bulb.

with 6.3 volt and 5 volt low-tension heater windings, is used to supply all the voltages for the tube and oscilloscope. A voltage multiplying circuit using metal rectifiers is used for the -900 volts and a 6X5 rectifier is used to supply the normal 250 volts H.T. The 6X5 has a high heater to cathode insulation (350 volt. max.) and is heated by the same supply as is used to heat the rest of the valves. The 5 volt winding is used to heat the cathode-ray tube heater, and is taken to it via a 1 ohm resistor, which will drop 1 volt and give 4 volts on the heater. The metal rectifiers in this circuit may be either of the special type for scope power supplies or else may be of the ordinary receiver type connected in series. They must each be able to withstand the peak inverse voltage across the 500 volt (250 + 250) winding of the transformer. Of course, the E.H.T. smoothing condensers must be of ample rating.

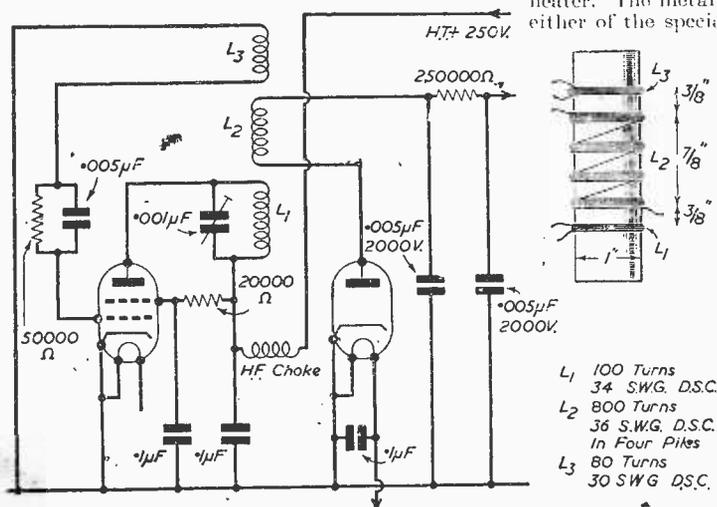


Fig. 4.—Another scheme for obtaining E.H.T. by means of an oscillator.

**E.H.T. Supplies**

A method of obtaining high-voltage, low-current supplies is shown in Fig. 4. This method, very popular in America, utilises a high-frequency alternating current generated by the oscillator valve, a 6V6 or other power valve, to induce a high voltage across a secondary coil wound

(Concluded on page 76)

## Ex-Service Cathode-ray Tube Data

NAVAL Type	Base	Size (m.m.)		Cathode		Focus and deflect	A <sub>3</sub> max. Kv.	Sensitivity m.m./v.v.		Screen	
		L	D	V <sub>h</sub> (V.)	I <sub>h</sub> (A.)			X	Y	Colour	Diam. in.
NC1 (W.306)	Br. 9-pin	160	40	4.0	1.1	E.E.	0.5	60	80	Green	1.5
NC2 (W.307)	8 pin bayonet	414	136	0.6	1.2	GAS/E	1.5	450	450	Green	5
NC3 (W.308)	Br. 9-pin	205	71	4.0	1.1	E.E.	.8	120	150	Green	2.5
NC4 (W.1070)	As NC2 except	for fluorescent screen.								Blue/Grn.	5
NC5 (W.1071)	6-clip base	495	136	4.0	1.1	E.E.	3	600	675	White	4.5
NC6 (W.1307)	12-pin spigot	354	79	4.0	1.1	E.E.	3.4	350	250	Green	3
NC7 (W.1308)	12-pin spigot	638	295	4.0	1.0	E.E.	6	1,425	1,270	White/Grn	12
NC8 (W.1920)	As NC2 except	for fluorescent screen.								Red	5
NC9 (W.1921)	12-pin spigot	380	114	4.0	1.1	GAS/E.E.	2.0	350	390	Blue	4.5
NC10 (W.1851)	As NC5 to wider	specification test limits.									
NC12 (W.3128)	12 contact	431	160	4.0	1.0	E.E.	5.0	625	1,175	Green	5
<b>ARMY</b>	<b>Voc. No.</b>										Diam. m.m.
ACR1	ZC.0123	495	136	4.0	0.9	E.E.	4.0	600	675	White	110
ACR2	ZC.0697	495	136	4.0	0.9	E.E.	4.0	600	675	White	110
ACR8	ZC.3081	—	—	4.0	1.2	E.E.	3.0	870	500	White/Grn	110
ACR10	ZC.3141 (Equivalent R.A.F. VCR 139A.)	205	70	4.0	1.1	E.E.	1.0	170	170	Green	.55
ACR12	ZC.1955	620	295	4.0	1.0	E.E.	5.0	650	650	Green	220
ACR13	ZC.3596	431	160	4.0	1.0	E.E.	5.0	620	1,160	Green	120
3BP1	—	—	—	6.3	0.6						3in.
5CP1	—	—	—	6.3	0.6		3				5in.
<b>R.A.F.</b>											Diam. in.
V.C.R.84 (10E/10)	12-pin spigot	677	295	4.0	1.1	E.E./M	4	800	500	—	12
V.C.R.85 (10E/11)	12-pin spigot	660	295	4.0	1.0	E.E./M	6	1,345	1,250	—	12
V.C.R.86 (10E/12)	As V.C.R.84	520	160	4.0	1.0	E.E.	5	900	700	—	6
V.C.R.87 (10E/13)	12-pin contact base	512	160	4.0	1.1	E.E./M	3.5	900	750	—	6
V.C.R.97 (10E/222)	12-pin contact	431	160	4.0	1.0	E.E.	2.5	600	1,140	Green	6
V.C.R.112 (10E/171)	7-clip base	495	135	4.0	1.0	E.E.	3	870	500	Grn/White	5
V.C.R.131	As V.C.R.87	585	300	4.0	1.1	E.E.	4	950	950	Green	12
V.C.R.138 (10E/407)	As V.C.R.97	340	90	4.0	1.1	E.E.	2	360	780	Green	3½
V.C.R.139A (10E/466)	10-pin spigot	205	70	4.0	1.1	E.E.	1	170	170	Green	2½
V.C.R.140 (10E/420)	—	587	306	4.0	1.2	M.M.	5	—	—	—	12
V.C.R.511 (10E/586)	As V.C.R.87	585	300	4.0	1.1	E.E.	6	1,000	1,000	—	12
V.C.R.514 (10E/658)	12-pin contact	370	90	4.0	1.1	E.E.	2	380	580	Green	3½
V.C.R.515 (10E/13026)	EMI 8-pin	384	90	4.0	1.05	E.E.	1.2	480	400	Green or Blue	3½

# Anti-static Aerials

Some New Ideas in Interference Elimination.

By G. R. WILDING

**F**REQUENTLY the view is expressed that the present high technical development of radio design affords little scope for serious experiment and research by the amateur radio technician unequipped with elaborate apparatus. This view is, I maintain, quite wrong, for investigation into methods of combating radio interference at least, requires no special apparatus or laboratory standard equipment.

If any projected anti-static device will in any way



Fig. 1.—Diagram to explain the reception of a signal on two aerials.

materially reduce radio interference without sensibly affecting signal strength, the simplest of tests will prove it. Furthermore, in no field of radio experiment will any degree of success be more valuable, so it is the aim of this short article to indicate fresh fields of experiment for the amateur radio enthusiast.

### Principles

First, a word about contemporary anti-static aerials. These almost universally comprise a mast or aerial proper, mounted as high as possible, and in as interference-free an area as possible, connected to the receiver by a screened down-lead to prevent static being picked-up from adjacent electric wiring, etc.

But in the types of aerial to be described, an entirely different principle is employed, and to make their functioning quite clear I must revert to basic radio theory.

Consider a transmitting aerial A, and a receiving aerial B, as in Fig. 1. Now, according to the electrical height of the aerial A, and the field strength of the transmitter, a voltage will be induced in it, which we will assume to be 50 mV.

Assume now that an identical receiving aerial C is erected by the side of aerial B at an equal distance from the transmitter. Obviously this aerial C will have a voltage induced in it, equal to, and in phase with, that of aerial B. But consider what happens when this second aerial is placed behind the first aerial.

As it would be slightly farther away from the transmitter, it will have a correspondingly smaller E.M.F. induced in it, but this would be unmeasurable and in any case doesn't concern us. What does concern us, however, is the phase difference between

the voltage induced in aerial B and the voltage induced in aerial C, now that they are at different distances from the transmitter, provided that this distance is not a wavelength or multiple of the wavelength radiated by the transmitting aerial.

Instead of their individual E.M.F.s rising and falling together, the voltages induced in aerial C would lag behind the voltages induced in aerial B. However, if a second transmitter D is now placed equidistant between the two receiving aerials on a

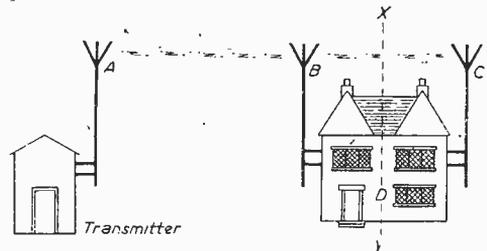


Fig. 2.—This diagram shows the two aerials on one building.

line XY, the E.M.F.s induced in them by this transmitter will be equal and in phase.

### Phase Differences

Therein lies the germ of the idea, for if we feed the two receiving aerials to a centre-tapped coil as in Fig. 2 the equal voltages induced by transmitter D will cancel out and leave only the voltage difference between the E.M.F. induced in the two receiving aerials by the transmitter A.

This means that our aerial system will receive signals from A or any other transmitter not equi-

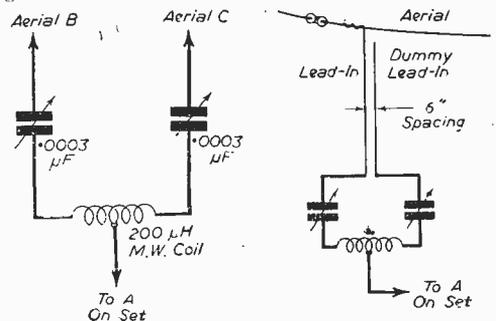


Fig. 3.—Coupling arrangement for the two aerials.

Fig. 4.—Another anti-static aerial idea.

distant from it, but will not receive D or any other transmitter situated on the line XY.

If we now draw Fig. 1 in practical fashion, transmitter A becomes any broadcasting station, aerials B and C comprise the listener's anti-static

aerial array, and transmitter *D* becomes the strong zone of static emanating from the household mains wiring and local electrical machinery.

It will be obvious that this aerial system functions as, and is in every way identical to, a giant one-turn loop or frame aerial, with the advantage that its extreme dimensions enable it to be immune from man-made static radiated from the entire domestic electric wiring.

In order that complete electrical balance can be obtained between the two aeriels, it is essential to use some form of variable coupling between each half of the aerial coil or alternatively arrange that the central tapping point can be adjusted.

Ideally, a fixed tapping point with an adjustable powdered iron core would enable optimum results to be obtained most easily, but here experiment alone would be the best guide.

The aerial leads *should* be screened, but in many cases it will be found that this is not absolutely necessary, but an electrostatic screen between the two halves of the coil will be found an advantage. This screen should, of course, be earthed, and it

might be advisable in some cases to enclose the coil completely in an earthed can.

The disposition of the two aeriels is the most important feature of the idea, and gives great scope for experiment. The simplest way of testing the effectiveness of the aerial system when erected, and when the coil tapping or coupling has been adjusted for minimum static, is to disconnect either of the two aeriels and note if this produces an increase in static.

If it does, of course the aerial system is functioning correctly.

A coil unit I have found very effective, and which has the advantage of being easily constructed, is shown in Fig. 3, where the coil utilised can be an old two-pin plug-in coil fitted with centre-tap.

Another aerial designed for minimum static pick-up is shown in Fig. 4, where a dual down lead is employed, fed to a coil unit similar to the type required for the first mentioned aerial. With this scheme the static picked up by each down lead is cancelled out by the coil leaving only the E.M.F.s induced in the aerial itself.

# A Bandsread Receiver

A Simple Set with an Efficient Tuning Device.

By R. M. S. HALL

**M**ANY of the new broadcast receivers use bandsread tuning on several short-wave bands. The normal electrical bandsread uses a small variable condenser or condensers in parallel with the main tuning condenser(s), thus enabling any part of the band to be spread. It is not proposed to discuss this further as many articles have been written on this particular type of bandsread. In my case I was faced with the problem of providing easy short-wave tuning on a BC receiver just being constructed.


There were several methods open:

1. To have a high ratio SM drive.
2. To spread the whole band.
3. To employ several spread bands.

It was decided to use a combination of the first and third, thus avoiding calibration troubles.
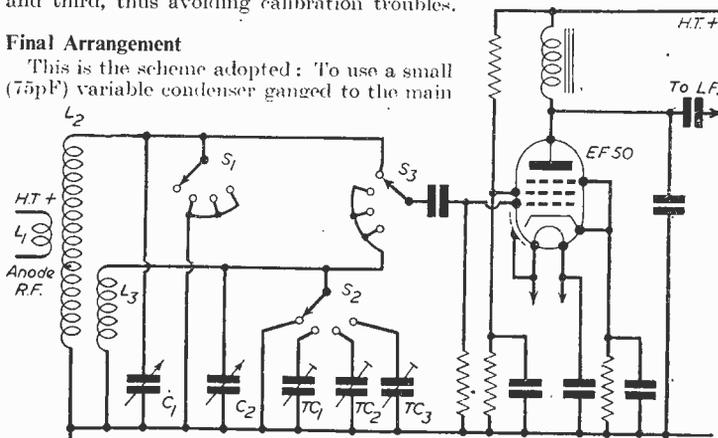
## Final Arrangement

This is the scheme adopted: To use a small (75pF) variable condenser ganged to the main



Circuit of the Bandsread Receiver described above.

(500pF) tuning condenser. With a normal (16-50 m., 200-550m.) S.W. and M.W. coil this scheme works quite well.

The size of the band-determining trimmers (TC1/2/3) varies with the band to be spread, but the approximate size can be easily found from the fact that the ratio of the wavelengths is equal to the ratio of the square roots of the tuning capacitances, remembering that a normal coil tunes to 51.2 m. with 500 pF (0.0005μF) in circuit.

Example: 16-metre band, 47pF, so use a 50pF trimmer.

The selectivity of the set was found to be quite good, using high-μ coils and a regenerative detector. The line-up was:

RF buffer-stage, EF50, Mullard.

Regenerative det., EF50, Mullard.

Output pentode (3W), EL32, Mullard.

In the diagram, S1, S2 and S3 are ganged.


In position 1 of these switches, M.W. coil is used, tuning by C1. S.W. coil shorted.

In position 2, S.W. coil is used, tuning by C2, M.W. coil shorted.

In position 3, S.W. coil is used, tuning by C2, M.W. coil shorted.

In position 4, S.W. coil is used, tuning by C2, M.W. coil shorted.

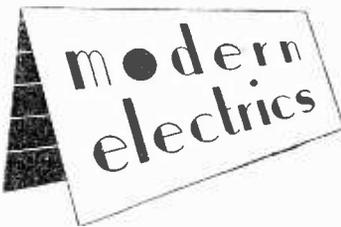Thus any number of bands may be spread to cover the frequencies of most interest to you.



**ALL GOODS GUARANTEED NEW AND UNUSED.**

**TEST INSTRUMENTS.**—The entire range of Taylor instruments now available on Hire Purchase. S.A.E. for Catalogue and Terms.

**VALVES.**—Huge stocks of English and American types, including 2Q5, 18, 24, 25AG, 42, 43, 80, etc.

**SPEAKERS.**—For "Hi-Fi" enthusiasts. Goodman 12in. double cone, £8 8s. Wharfedale 12in., £6 15s. All makes in stock from 2in. to 15in.

**PICKUPS.**—The famous Connoisseur Lightweight, complete with transformer, £4 5s. Rothermel crystal Metal arm, £2 12s. 6d. Moulded, £2 18s. 3d.

**SAPPHIRE NEEDLES.**—Rothermel Straight, 12s. Traller, 16s. Ministyle, 16s. Sapphox Straight, Traller, and Ministyle, 14s.

**COILS.**—R.F. iron cored, "Hi-Q." L.M.S., Ac. H.F., and Osc. 3- each. Wearite "P" coils, 3/- each. Matched pairs T.R.F., 8/9 pair.

**STROBOSCOPES.**—Single speed, 78 r.p.m., 50 cycle., 6d. each, 84d. post n.e. Under 30/- C.O.D. or C.W.O. over 20/-. When ordering C.W.O. please allow sufficient for packing and postage.

**MODERN ELECTRICS LTD.**

164, Charing Cross Road, London, W.C.2  
Tel: TEMple Bar 7587



**MODERN PICK-UPS**

**Moving Coil Types:—**

for the highest fidelity. Both the following give approximately .03 volts output and, therefore, pre-amplification is normally needed.

**WILKINS & WRIGHT "N" MOVING COIL**

For use with standard miniature needles, miniature thorns or sapphires. Adjustable needle pressure. Complete with equalizing transformer ... .. £7 13 4

**LEXINGTON "SENIOR" MOVING-COIL PICK-UP**

Incorporating ingenious semi-automatic insertion and rejection of Lexington sapphire needles ... .. price £7 6 9  
Lexington input Transformer (shielded), £1 13 2

**Lightweight**

**Armature Type:—**

giving extremely good reproduction with a reasonable output. Can normally be used with most existing amplifiers and radio receivers; output approximately .5 volts from transformer secondary. In common with most modern pick-ups, the Connoisseur has "constant velocity" characteristics and therefore bass-compensation is needed.

**CONNOISSEUR LIGHTWEIGHT ARMATURE TYPE**

Response substantially level from 200 to 8,500 c.p.s. Uses standard miniature needles. Complete with input transformer, price £4 4 7

**Pick-up Accessories:—**

**SAPPHOX SAPPHIRES**

For use with Wilkins & Wright type "N," Connoisseur and other Pick-ups using miniature needles ... .. 14/-

**CONNOISSEUR STEEL NEEDLES**

Modern miniature needles in packets of ten ... .. price 2/9

**WILKINS & WRIGHT "SCRATCH-FILTER"**

Useful low-pass filter cutting above 8.5 Kc/s. £2 0 0

**WEBB'S RADIO, 14, SOHO ST., OXFORD ST., LONDON, W.1.**

Note our SHOP HOURS: 9 a.m. to 5.15 p.m.  
Sats. 9 a.m. to 1 p.m.  
Telephone: GERrard 2089



**FOR QUALITY RADIO COILS.**—Permeability tuned superhet coils wound on high-quality formers. Wave-range coverage 700-2,000 m., 200-550 m., 16-50 m., with iron-dust cores and fixing nuts, 3/- each.

**COIL PACKS.**—Type B covering 13-35 m., 34-100 m., 200-550 m. Type J covering 16-50 m., 200-550 m., 700-2,000 m. Permeability tuned. Angle or flat plate mounting. Complete with suggested circuits. Really efficient packs, 36/- each.

For complete range of Products, including:—HiQ Superhet Coils. Air core covering 12-2,000 m. I.F. Transformers, 465 kc/s. TRF Coils. Complete Tuning Hearts and other components. Price list on application.

224, Hornsey Road, Holloway, London, N.7.

**LASKY'S RADIO**

Everything for the Home Constructor, Amateur Radio Enthusiast, Experimenter and Serviceman. We have your requirements in our huge stock.

**RADIO VALVES.** British, American and Continental, A.C., A.C., D.C., Battery, Glass, Bantam, Miniature, Octal, Loctal, UX. Send us your enquiries. Order C.O.D. Our technical department will be pleased to advise you on substitutes for unobtainable or obsolete types.

**TRANSFORMERS.** Mains 4v. and 6v. output, heavy duty, push-pull, multi-ratio, 0v., midget output, miniature intervalve, I.F.T., iron-cored, air-cored, etc., etc.

**COILS.** Aerial, H.F., Osc., "P" type, Wearite, L. and M., T.R.F., S., M. and L. Superhet, H.F. chokes, etc., etc.

**CONDENSERS.** Electrolytics of all types, wet and dry, high and low voltage, bias, paper, mica, aluminium, cardboard, block oil-filled, cathode-ray, tuning 2- and 3-gangs, etc., etc.

**PICK-UPS.** Rothermel, B.T.H., Acos, Marconi, Lexington, Goldring, Moving-coil, Magnetic and Crystal. Playing Desks, Collaro Micro-grams. Electric turntables with pick-up in carrying case.

**TEST GEAR.** All types: Avo, Pullin, Taylor, etc., etc. Moving-coil amp. meters, Micro amp. meters, Voltmeters, Milliamperometers.

All goods offered are new and unused unless otherwise stated, and carry our usual guarantee. Satisfaction or your money refunded.

We have a very large and varied selection of ex-Government radio equipment. TRANSMITTERS, RECEIVERS, TEST SETS, METERS, etc., etc.

IT WILL PAY YOU TO PAY US A VISIT. Get your name on our mailing list to-day. Send id. for our current list and bulletin.

**LASKY'S RADIO**  
370, HARROW ROAD, PADDINGTON, LONDON, W.9.

(Opposite Paddington Hospital)  
Tel.: Cunningham 1979. Hours: Monday to Saturday, 9 a.m. to 6 p.m. Thursday Half-day.

**YOU can become a first-class RADIO ENGINEER**

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

**T. & C. RADIO COLLEGE**  
NORTH ROAD, PARKSTONE, DORSET.

Post in unsealed envelope 1d. postage.  
Please send me free details of your Home-Study Mathematics and Radio Courses.  
NAME .....  
ADDRESS.....  
P. 87




# The Quantum Box.

A Useful Addition to the Service Workshop or Experimenter's Workbench

By JAMES LAIRD

**I**N these days of supply difficulties, here is a most useful piece of apparatus, which I have named the Quantum Box. It contains, always to hand, 36 different condensers and resistances. As is well known, routine testing reveals a large number of condenser and resistance faults. When these are suspected, the Quantum Box almost invariably picks out the faulty one. It is invaluable as a substitution in condenser or resistance open circuits and, by moving one prod only, correct values can be ascertained. With a unit such as this speedy service is assured, and in the majority of cases better performance is obtained. Of course, the more accurate the components, the better the unit. Condensers and resistances with a tolerance of one or even the half of one per cent. cost money, and the serious experimenter would doubtless require them, but for ordinary use my choice is quite adequate.

on six screws bolted to the panel, and soldered to the screw ends. To go into details of construction is quite unnecessary as the diagrams explain everything. A unit of this description, or one of even greater accuracy, will become a necessity to the workshop and to the serious electronic worker in the near future, as the modern trend seems to be for greater accuracy and precision. The beauty of this instrument lies in its absence of complicated switching, and also in having only one prod to change.


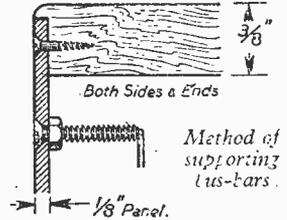


### Construction

The construction is quite simple and straightforward, and should not present any great difficulties even to a beginner. Heavy wire should be used (18 s.w.g.), and all joints well and truly soldered. A heavy wire is run round, near the edges of the underside of the panel, and all negatives and one prod are soldered to it. It is supported
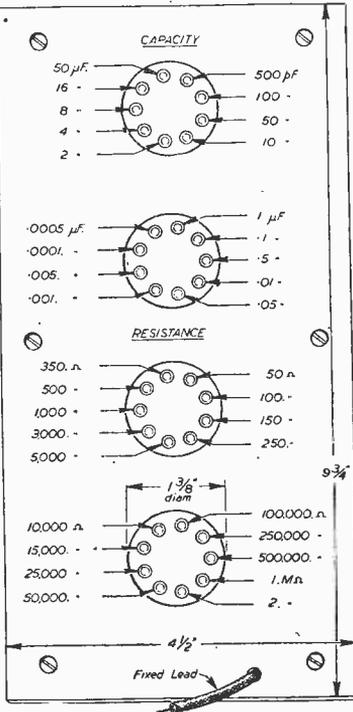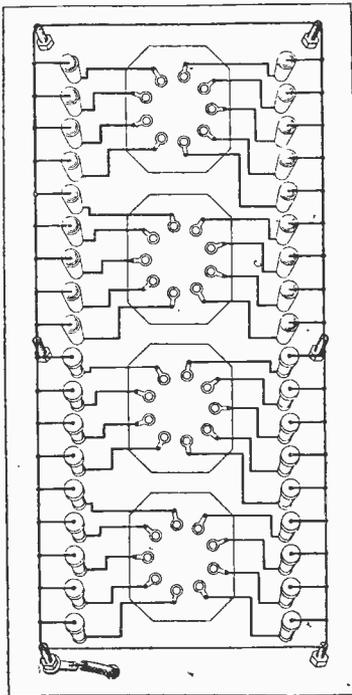
### Using the Box

In use, especially when searching for the cause of hum in a set, always short the prods of the Quantum Box before and after each test in order to discharge internal condensers. Failure to do this will result in fireworks or even a nasty shock. If it is decided to fix a crocodile clip on the negative prod, which is very handy, and clip it to the chassis of set, then shorting the other prod to the chassis will suffice. The 50, 16, 8 and 4  $\mu\text{F}$  condensers in the box are electrolytics, therefore their proper polarity must always be observed. The nine-pin valve-holders used have a ring on the underside of each socket, which holds the tips of the sockets together, and thereby ensures good contact, even with the thinnest of prod plugs.



### LIST OF PARTS

- 1 Panel, 9 3/8 in. x 4 1/2 in. x 1/8 in.
- 4 Valve holders, 9 pin (British).

	Condensers	Resistances
50	$\mu\text{F}$ 50 v.v.	50 ohms.
16	" 500 "	100 "
8	" " "	250 "
4	" " "	500 "
2	" " "	1,000 "
1	" " "	5,000 "
.1	" " "	10,000 "
.5	" " "	25,000 "
.01	" " "	50,000 "
.05	" " "	100,000 "
.001	" " "	500,000 "
.005	" " "	1 megohm.
.0001	" " "	2 megohms.
.0005	" " "	150 ohms.
10 pF.	" " "	350 "
50 pF.	" " "	3,000 "
100 pF.	" " "	15,000 "
500 pF.	" " "	250,000 "

The diagram shows the layout and method of wiring the Quantum Box, whilst a list of the parts required is given above.

# Radio Amateurs' Examinations

The 1947 Test Paper and a Report on the Results which were Obtained

**I**N order that prospective transmitting amateurs may gain some idea of the standard required by the G.P.O. examinations, we again give the full Test Paper which was set last year. The City and Guilds of London Institute have reported on this examination and their report follows the Paper.

## 1947 Radio Amateurs' Examination:

*Candidates should attempt as many questions as possible. Use should be made of diagrams where applicable. The maximum possible marks obtainable is affixed to each question.*

1. An alternating voltage of 10 volts at a frequency of  $\frac{100}{2\pi}$  Mc/s is applied to a circuit consisting of the following elements connected in series:

- (i) an inductance of 10 micro-Henrys,
- (ii) a capacitance of 10 pico-farads,
- (iii) a resistance of 10 ohms.

- (a) What current flows through the circuit? (5 marks.)
- (b) What voltage appears across the inductance? (5 marks.)

2. What is meant by the "selectivity" of a tuned circuit? On what circuit constants does it depend?

Why is this quality necessary in a receiver? (10 marks.)

3. What is understood by the term "C.W.," and what special method is needed to detect C.W. signals? Describe a circuit arrangement which could be used for this purpose, illustrating your answer by a diagram. (10 marks.)

4. What is meant by modulation? Describe a method of modulating a typical low-power R.F. amplifier. (10 marks.)

5. What are the relative advantages and disadvantages of a variable-frequency master oscillator over a crystal-controlled oscillator for use in an amateur transmitter? Describe a variable-frequency oscillator of good frequency-stability. (15 marks.)

6. Describe, with the aid of a diagram, the circuit arrangement of a low-power crystal-controlled transmitter for the 58.5 to 60 Mc/s frequency band. (15 marks.)

7. Describe FOUR types of aerial commonly used for amateur transmission and how they may be coupled to the transmitter. What are their relative advantages and disadvantages? (10 marks.)

8. Condition 8 of the Postmaster-General's licence to establish an amateur wireless station stipulates:

"Where the sending apparatus is not crystal-controlled there should be kept at the station . . . a reliable frequency meter of the piezo-electric crystal type or other type approved by the Postmaster-General, for measuring the frequency to an accuracy of not less than  $\pm 0.1$  per cent."

Describe an apparatus to meet the foregoing

requirement. Illustrate your answer by a diagram and explain how the apparatus is used. (20 marks.)

## Report on the Papers

The following general report is given on the papers as a whole and is not necessarily applicable to the work from individual schools.

Year	No. of Cands.	No. of Passes	No. of Failures	Percentage of Failures
1947	320	120	206	63
1946 (Nov.)	216	150	66	30.5
1946 (May)	182	145	37	22.2

The report on the last examination commented on the falling-off in the percentage of entrants obtaining a pass and suggested that a number of persons had sat for the examination without adequate preparation. The tendency then noted has become accentuated in the 1947 examination, the percentage of passes having fallen to 37, and the majority of the entries were of an extremely low standard. From the phraseology and vocabulary used, and the general way in which the answers were given, it is apparent that a large number of entrants, unused to sitting for examinations, had received little or no coaching for the Radio Amateurs' Examination. The use of abbreviated and corrupt English, such as is commonly used by amateur radio operators, is to be deprecated for examination purposes. Some of the answers were of a flippant nature, and on the whole there appeared to be a tendency to treat the examination as a not very serious matter. Confidential notes to the Examiner, regretting ignorance, do not give a good impression. A report on the questions follows:

**Question 1 (calculation):** Comparatively few candidates attempted this question; of those who did, less than half did so correctly.

**Question 2 (selectivity)**  
**Question 3 ("C.W.")**  
**Question 4 (modulation)** } Fairly well done by the better candidates.

**Question 5 (master oscillators):** The essential points in the design of a variable frequency oscillator of good frequency-stability were not at all well understood.

**Question 6 (the transmitter):** Many incorrect answers were given concerning the required frequency of the crystal and the methods of multiplication suggested to obtain the required final frequency showed little regard to efficient operation.

**Question 7 (aerials):** Not well done, in particular the methods of coupling to the transmitter were dismissed very briefly.

**Question 8 (frequency meter):** Very poorly done by the comparatively few entrants who attempted the question. They seemed to have a hazy idea of what a frequency meter of the piezo-electric type really is, and of how to use it.


# Practical Hints

## Handy Connector

HAVING made several midget portable sets, I have found that the handiest little gadget to use in these confined spaces is the metal contact fitted to American octal holders.

I always remove any spare tags from my holders and have, at various times, used them as follows:

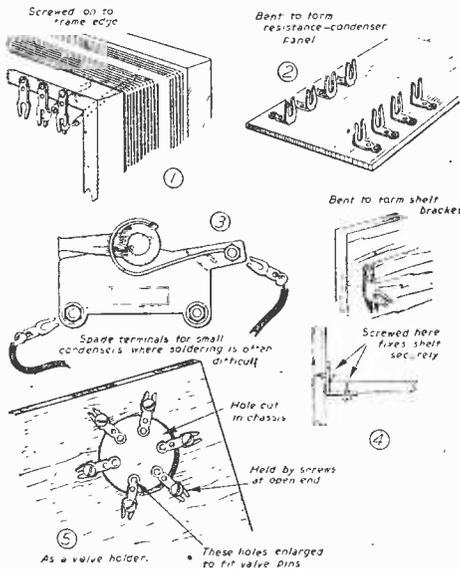1. For anchoring ends of frame aerial.
2. For making small resistance-condenser panels.
3. For spade terminals for small variable condensers—where soldering is sometimes very difficult.



Useful aids made from valveholder tags.

4. For an angle bracket for shelves—or anything else that requires holding.
5. For a valveholder.

Other readers who make their own sets may be able to think out still further uses for these handy little pieces of metal.—J. Brown (Heaton, Bradford).

## Short-wave Coil-making Hint

WHEN it is desired to wind 4- or 6-pin short-wave coils with fairly heavy gauge wire for, say, the grid windings, certain snags arise. It is all right fixing the start of the winding through a hole to one of the pins. When the end of the winding is arrived at, however, it is next to impossible to pass this end through a similar hole, without all the turns loosening.

The author has made many coils with quite thick gauge tinned wire, in the following manner: A light gauge wire is first wound round to get the

### THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay half-a-guinea for every hint published on this page. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newner, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints."


### SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page 61 of cover.

approximate length required. The stouter gauge wire is then cut to this length plus about 12in. extra.

A hole is then drilled in the coil former for the top end of the winding, and a slot cut in one of the ribs at the approximate end of the winding. This distance is calculated from wire gauge tables, giving spacing for various numbers of turns at spacing of one diameter of wire. The slot is cut right down to the bottom of the rib. The stout wire is then passed through the top hole and out through the usual bottom hole of the former,

and is soldered to the appropriate pin. Then the other end is fixed in a vice and the wire pulled taut. The coil former is then rotated in the two hands, the person moving slowly towards the vice as the winding proceeds. When the turns are completed, and this should bring the wire to the slot, the wire is allowed to enter this slot, and keeping the wire taut all the time the coil former is twisted to bend the wire. This takes the wire parallel with the rib, but at the bottom. Still keeping a tension on the wire, this is turned once round the appropriate pin for the end of this winding. Only then is the

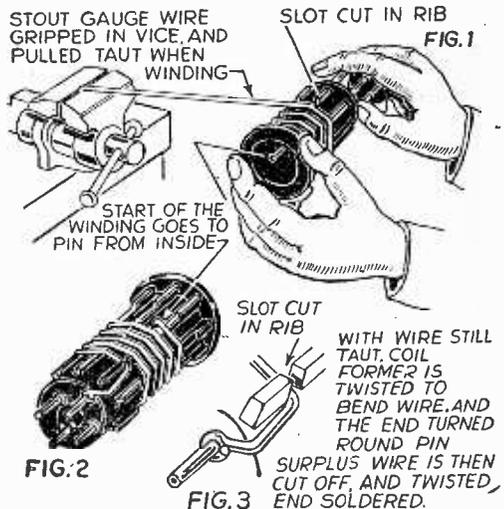

Effective coil-winding hint.

tension on the wire relaxed, and after soldering to the pin the surplus wire is cut off carefully, using a small metal saw.

This procedure gives a very rigid coil on plain ribbed formers. Where a reaction or other winding carrying H.T. is wound on the remaining length of ribbing, at this end, a strip of mica should be inserted just over the thicker wire where it runs parallel with the rib. If the slot is to be full depth of the rib, however, there should be ample clearance without it.—R. L. G. (Chelmsford, Essex).

MANY alternative circuits can be utilised to provide the opposite voltage phases necessary for push-pull output stages. Most of them are adaptable for battery or mains valves. The circuits included in Figs. 1 to 8 are a basis to the majority of modern push-pull amplifiers. Whatever his range of components, the experimenter or constructor should readily find one circuit suitable to his requirements and available "spares."

The push-pull transformer coupling shown in Fig. 1 is probably best known. The circuit uses battery valves, although mains types only require the addition of suitable bias resistors and condensers. The transformer has a centre-tapped secondary, its ratio being determined by the operating conditions of the output valves. The anode circuit of V1 is shown decoupled, the H.T. current of the valve passing through the transformer primary. When a midget transformer is used it should be parallel fed to prevent core saturation. The essential modification is given in Fig. 2.

Typical transformer ratios under different output conditions are: Class B, 1.5 : 1; Class A, 1 : 2; Q.P.P., 1 : 8; and about 1 : 4 for Class AB2. Parallel feed is usually preferable for "quality" amplifiers where the two output valves are operating under Class A conditions.

**Using Standard Transformer**

Fig. 3 provides an alternative to Fig. 1. A normal intervalve transformer replaces the centre-tapped push-pull component. The circuit offers a useful standby if a suitable centre-tapped push-pull transformer is not to hand. The only additions are the resistors R2 and R3. Each must be of similar value, not exceeding 500,000 ohms and preferably in the region of 250,000 ohms. Class A operation is usual with this arrangement. However, with a 1 : 5 transformer, there is no objection to a

# Push-pull Ph

A Further Explanation of

By R. V

Q.P.P. output stage if the equipment is battery operated. Again, parallel feed may be employed for the transformer primary, provided the valve

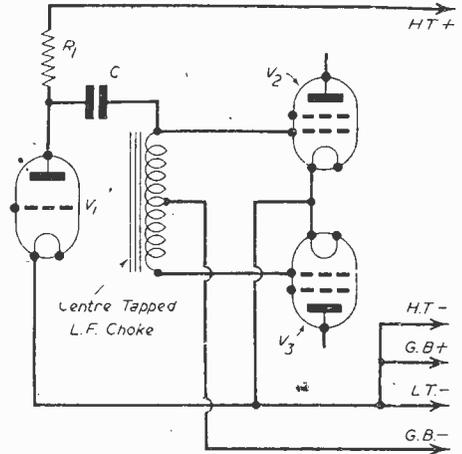


Fig. 4.—Basic circuit for inclusion of a centre-tapped L.F. choke.

V1 is not overloaded due to the volts drop across the inserted anode load resistor.

The centre-tapped choke shown in Fig. 4 is of practical value, although less adaptable than the transformer when connected as an intervalve unit. It is most suitable for Class A, but can be used for

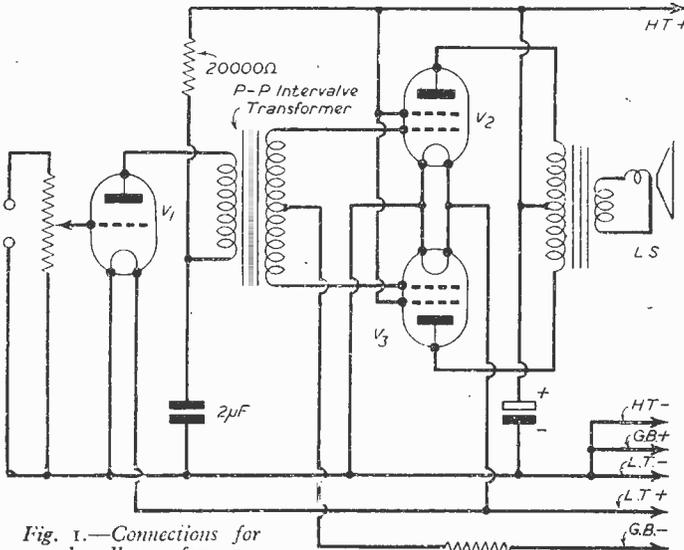


Fig. 1.—Connections for push-pull transformer.

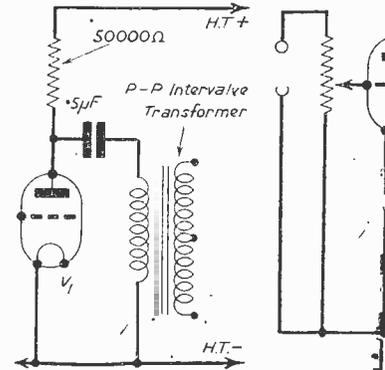


Fig. 2.—Connections for valve and transformer, using parallel feed.

Fig. 3.—

# Phase Splitting

Modern Amplifier Design  
LUMBARDA

Q.P.P. if adequate L.F. drive is available without overloading V1. Unlike a transformer, a centre-tapped choke does not provide any voltage


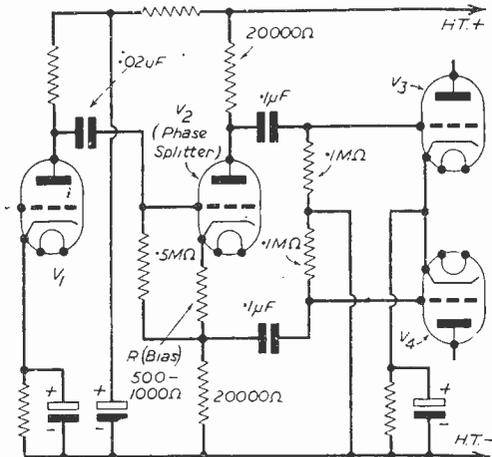


Fig. 5.—Phase-splitting valve with principal component values.

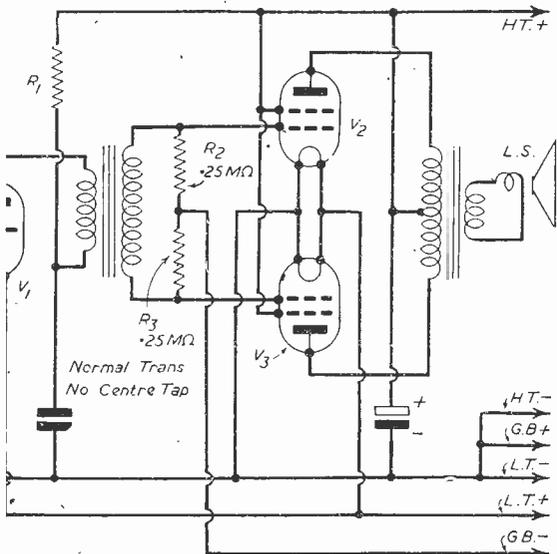step-up to the individual output valves. The value of the resistor R1 is between two and three times the anode impedance of V1. Starting at,



Alternative circuit, using normal inter-valve transformer.

say, .5 μF, several alternatives might be tried for C. A smaller capacity will usually reduce the bass response of the circuit, while a critical value, depending on the inductance of the choke, will even produce a restricted bass boost. A high-inductance choke should be used for maximum stage gain, otherwise there will be a noticeable bass attenuation, especially if the value of R1 exceeds 50,000 ohms.

### Phase-splitting Valve

The use of a valve for phase splitting, as in Fig. 5, is applicable to mains receivers or amplifiers utilising indirectly-heated valves. A triode is usual, although a pentode connected as a triode, with suppressor and screen grids strapped to anode, can be substituted. The valve performs its duty purely as a phase-splitter, there being no gain as in a normal amplifier stage. It must be able to handle a signal at L.F. sufficient to drive the grids of the output valves at full swing during maximum volume. Standard component values have been introduced in Fig. 5 for guidance. Push-pull Class A output is used. This, with the phase-splitter, provides an ideal combination for a mains "quality" amplifier.

The method illustrated in Fig. 6 can be used without variation on either mains or battery equipment. The circuit relies on the upper output valve V2 to provide the opposite phase necessary to drive V3. Component values are given. In most instances they will be the same for mains valves, with the addition of the necessary bias components. Reasonable volume and quality may be expected with mains valves, and a pair of triodes in the output stage. But for battery operation the circuit has its limitations. Economy of H.T. current necessitates Q.P.P. operation. Only under favourable conditions of H.T. can sufficient L.F. drive be obtained to load the output stage without

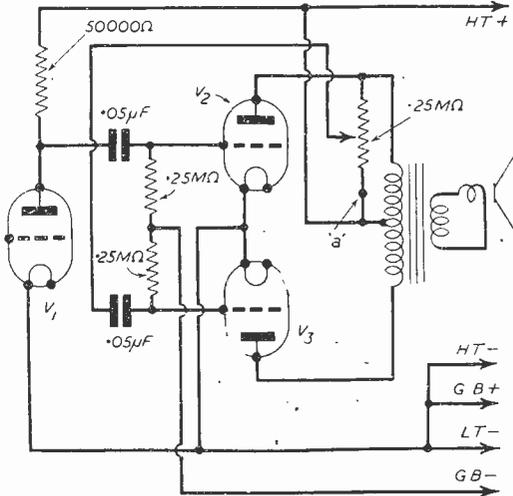


Fig. 6.—"Phase splitting" for push-pull, when the required input for V3 is taken from the output of V2.

overloading V1. Besides, although economical in components, the circuit suffers from the fact that distortion in the anode circuit of valve V2 is fed back to the grid circuit of V3, and so to the output and loudspeaker.

**Paraphase Circuit**

A more satisfactory version of the "paraphase" circuit is given in Fig. 7. A separate triode valve V2 is employed to feed the grid of the output valve V4. The potential divider also comprises the

cient, there is no reason why the circuit should not be used with battery valves and Q.P.P. output.

A word about the potential divider in Figs. 6 and 7. Once set, this should not need readjustment. A graded volume control is ideal for the purpose.

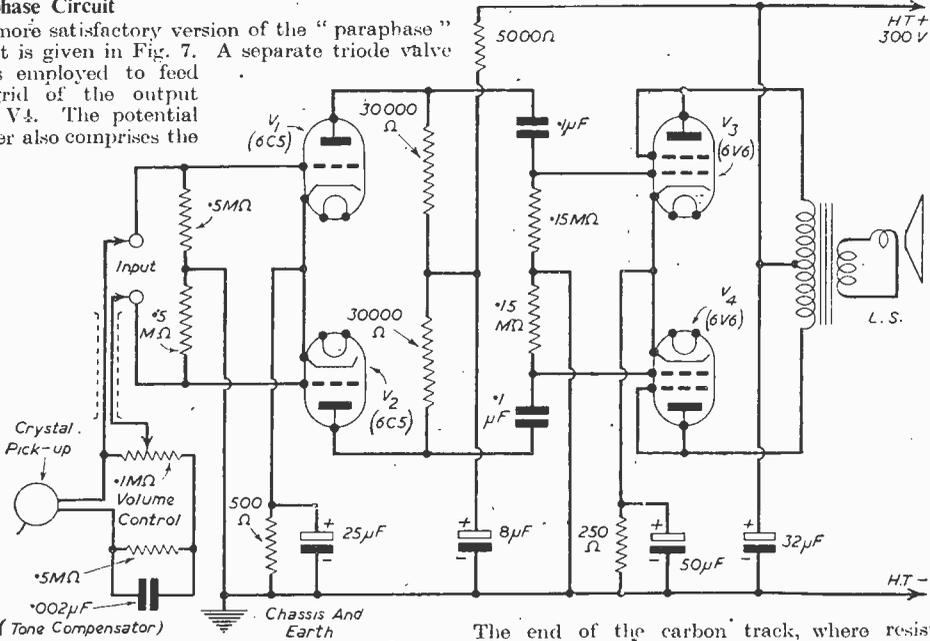


Fig. 8.—Twin-channel amplifier circuit, using "strapped" tetrodes as output triodes. Typical circuit for crystal pick-up is also shown.

anode load of V1. Principal component values are indicated. It may be more convenient in practice to substitute V1 and V2 by a single double-triode valve. Provided the L.F. signal from V1 is suffi-

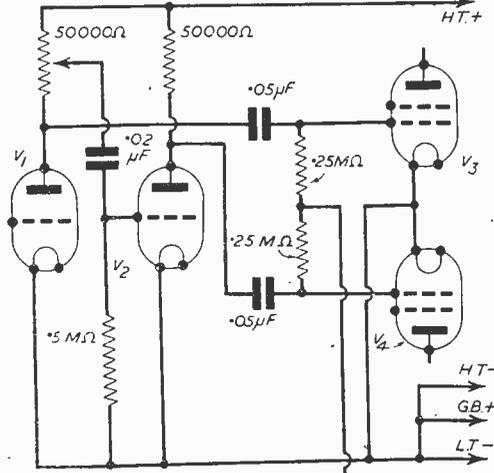


Fig. 7.—The "paraphase" circuit.

The end of the carbon track, where resistance variation is least, is best connected to "a." The position for the slider of the control will be found at a setting near the end corresponding to point "a." Correct setting will ensure that the grid of

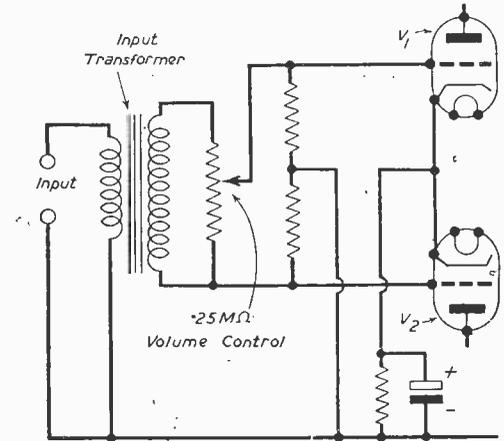


Fig. 9.—Connections for input transformer and volume control.

each output valve is being equally fed, the signal to each valve having the same peak L.F. volts.

The circuit shown in Fig. 8 has two input channels with separate valves, or a double-triode, to feed the matched output pair V3 and V4.

# Test Instrument Design-2

This Month Signal Generators and Beat Frequency Oscillators are Dealt With

By P. E. TOOKE

**T**HE oscillator is the heart of a Signal Generator. On this depends whether it has any useful purpose or is just another "maybe." In an article such as this, to attempt to describe an instrument suitable for all tastes is impossible, so it is intended to run stage by stage through an average circuit.

Fig. 1 shows the completed circuit, excluding minor modifications which are explained in the text. The oscillator comes first. This was dealt with last month. Nevertheless a few points are worth noting. An E.C.O. circuit is shown with a modulated buffer stage. The triode circuit hardly needs any explanation. The range should be kept within 100 kc/s to 5 Mc/s, for an all-range job. This should be broken up into about five ranges. Coils on the

incorporated, a variable gain control can be put on the screen to adjust modulation. It is very useful to bring out the modulation frequency to the front panel for checking L.F. stages of sets, etc., H.T. on the Colpitts valve should be switched to allow pure C.W. output when desired. The modulated output from the buffer can now go straight to the attenuator, or if it is to be measured, an R.F. meter stage will have to be put in.

### R.F. Meter

Fig. 2 shows an R.F. meter, using a diode rectifier feeding a D.C. voltmeter. Of course, if one has a thermo-couple meter available, this is ideal. However, not everyone is lucky enough to possess one; and if they do, it is generally too versatile an instrument to "tie up" on a piece of gear. On most commercial instruments the diode circuit is used, however, and it serves very well. The diode rectifies the output from the buffer, and feeds the resultant D.C. voltage into the meter. The meter should be calibrated at 1 volt with the modulation off. This should be done with a reliable valve voltmeter, then the modulation checked at 40 per cent., and this noted on the scale. Then all that is necessary is to adjust to the R.F. level with the "mod." off; and then with the "mod." on, adjust the audio gain control, till the meter reads

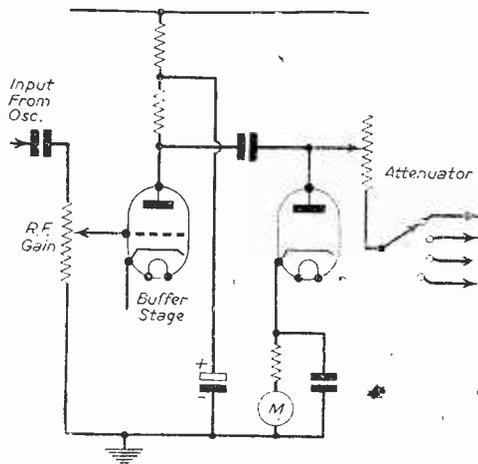


Fig. 2.—An R.F. meter and rectifier circuit showing modification of buffer stage for R.F. gain control.

L.F. side should, if possible, be Litz wound. To give a good "Q," further inductance can be given by means of iron dust cores, but these should be sealed when set. Notice the decoupling on the plate circuit. The buffer is loosely coupled through about .0001  $\mu$ F capacity; the output from the buffer should be about 1 volt, so the coupling may have to be increased for the L.F. ranges.

Modulation is injected on the screen of the buffer. The modulation oscillator is a Colpitts circuit, using a small choke, and has a frequency of approximately 400 c/s., modulation is at a depth of 40 per cent. If no means of checking is

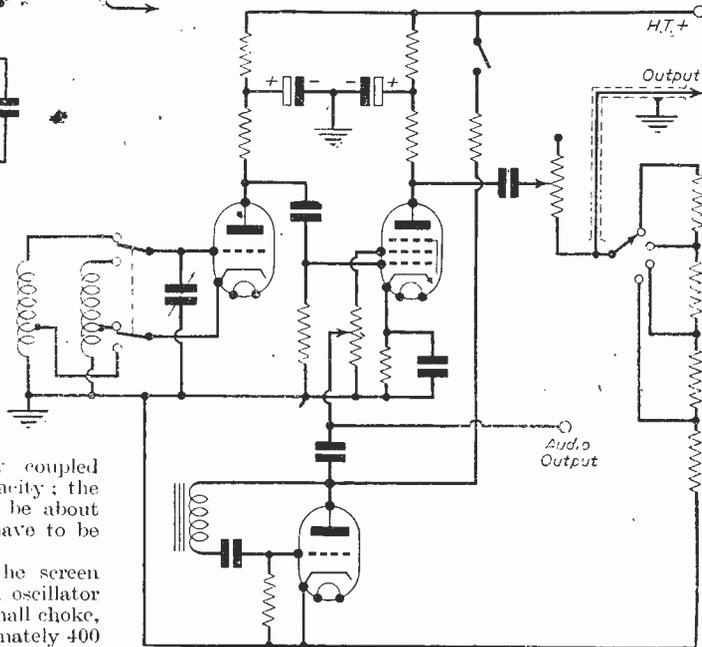


Fig. 1.—A signal generator using an E.C. oscillator.

to the modulation calibration. Most servicemen will put these calibrations in for a few shillings if a valve voltmeter is not available.

The attenuator is not very elaborate. A potentiometer slider, feeding a fixed, switch-tapped "bleeder" network. The slide wire should be equal to one resistance of the bleeder; and each tap of the bleeder should be a one tenth of the last. The resistance used should be wire wound, non-inductive if possible, and the whole circuit screened to prevent any stray pick up. The output lead should be coaxial; and matched, if possible, to the attenuator impedance.

### Construction

A few tips on construction. The buffer and oscillator stages should be screened, preferably completely canned with coils, switching, etc. If one is anything of a mechanic a coil turret should be attempted. This is by far the best method of coil switching as the coils are right on the contacts with a minimum length of lead.

A good dial is an investment. This is really worth while, as the accuracy of the calibration staying constant relies only on the dial and oscillation. If the dial has back-lash, or it slips, all the good work put into the oscillator to ensure stability is of no avail.

Calibration of all gear is probably the amateur's number one bugbear. Failing the possession of a

multi-vibrator or sub standard, a good reliable signal generator should be begged or borrowed. After setting mod. and R.F. gain controls (if you have incorporated these refinements), the standard generator should be used to beat against yours, using a radio for mixing and demodulation. The beat note should be zeroed, or as near as possible, and the dial marked. Checks should be made at about three or four positions on each range. Be very careful that you beat the fundamentals and not a harmonic. Otherwise, it will take a few hours to unscramble it.

After all trimmers are set they should be sealed and the instrument put in a case. If a wooden one is used, line it with foil and earth it to chassis.

### Beat Frequency Oscillator

So much for the Signal Generators. Now for the next most used test instrument, the Beat Frequency Oscillator; or B.F.O. This very useful piece of apparatus is, as its name implies, two oscillators, one with a fixed frequency and the other slightly variable, the outputs of which are fed into a mixer stage and the resultant beat note demodulated. This is then fed as an audio note into the output.

This piece of apparatus is very useful for checking receiver audio stages and amplifiers. Super frequency checks in conjunction with a frequency sub standard can also be made. With it curves can be drawn for transformers, etc., and to anybody interested in audio work of any sort it is essential.

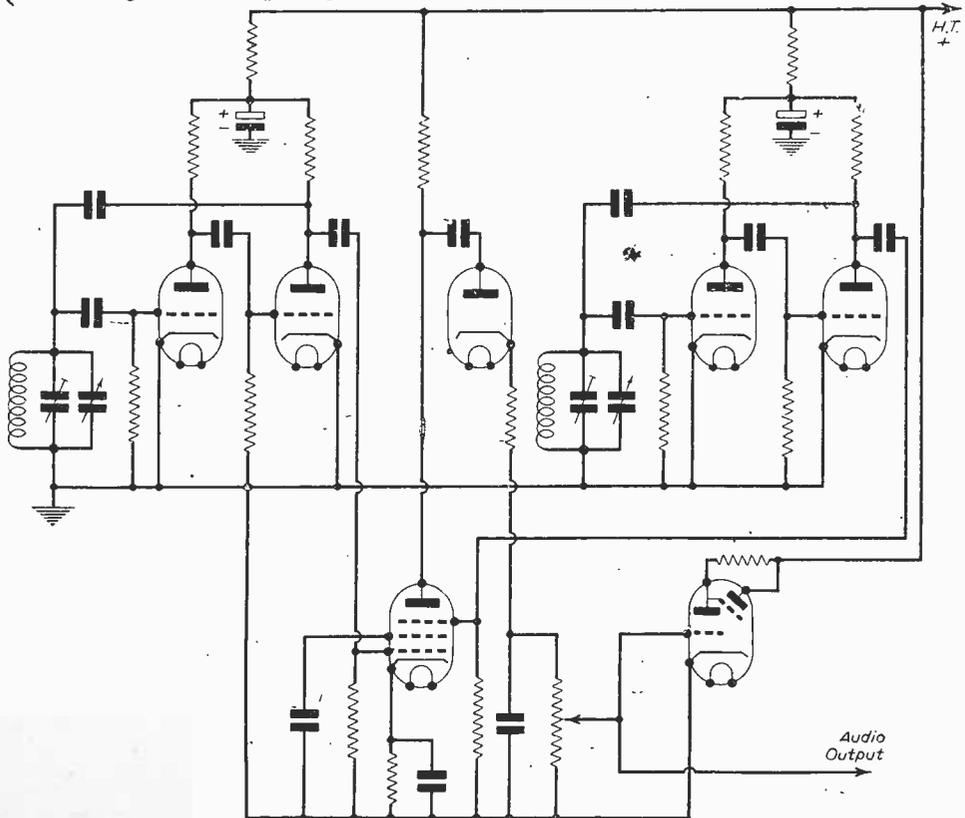


Fig. 3.—This circuit shows a Beat Frequency Oscillator with Franklin oscillators, and a cathode-ray zero indicator.



tends to block the receiver, and check that oscillation is obtained over all the frequencies covered. Maximum gain is obtained just below the point of oscillation and tuning should be found to be sharp

blocking and not by a fierce howl. The oscillation is, of course, amplified by the receiver in the same way as an incoming signal. The reaction setting should hold pretty well over the width of an amateur

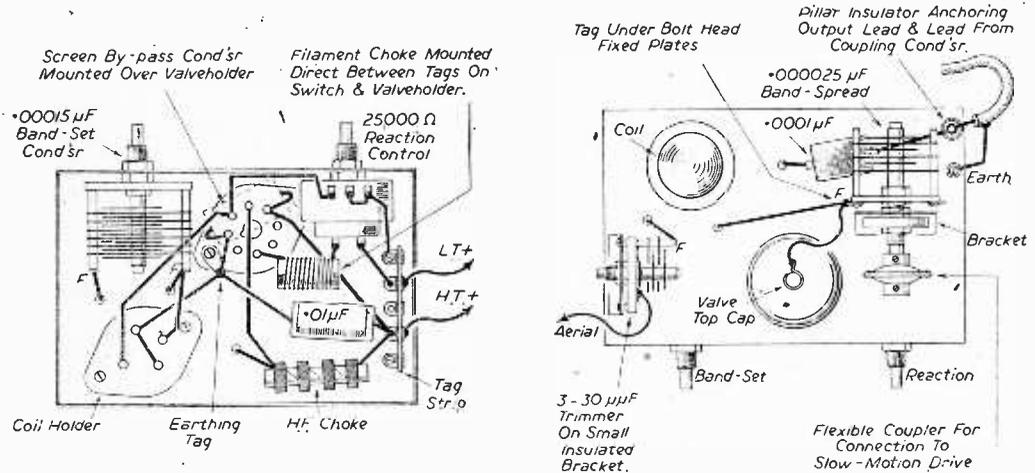


Fig. 2.—Top and below chassis wiring diagrams for the pre-selector.

and sensitivity considerably increased. The reaction control should be quite smooth in operation, and it may be necessary to experiment with the reaction winding so that oscillation is shown by a decrease in signal strength due to the receiver

band so that it is only necessary to keep the tuning in step.

While a 1.4 volt valve is shown, a low consumption 2-volt R.F. pentode could be substituted for use with a receiver using 2-volt valves.

## B.F.O. for the R.116

I HAVE operated one of these receivers for eight months on the amateur bands and have been very much impressed by its fine performance when properly handled. I am, however, a Morse enthusiast and have felt myself handicapped to some extent by the fixed frequency B.F.O.

Recently I determined to remedy the situation by fitting a variable pitch control and, after considerable experiment, finally solved the problem to my complete satisfaction.

### Components Required

The extra control needs only a 100 mmfd. variable condenser with a mounting bracket and extension spindle while the addition involves no alteration to the original wiring.

It is necessary to remove the right-hand aerial socket. This will leave a panel hole of the right size to accommodate the extension spindle bush. The variable condenser can then be mounted on the right-hand side of the metal cabinet so that it lines up with the bushed hole but is some 4ins. behind it. An Eddystone, or similar, extension spindle can be fitted and the job finished off with a small instrument knob and scale on the panel.

The only connection necessary for the condenser may be made with an 8in. length of single-core rubber-covered flex. One end is connected to the fixed vanes of the condenser and the other is taken

through a small hole in the screening can of V8 to be pushed in alongside the anode pin of that valve in the appropriate socket. (The moving vanes of the condenser are automatically earthed via the mounting bracket and chassis.)

### Avoid Short-circuits

Care should be taken, before switching on, to make sure that the new lead is not shorted to earth since it is connected to the high tension positive line! If it is found that the whole swing of the condenser does not give a satisfactory pitch variation, the existing B.F.O. trimmer—C35—may have to be readjusted. This is quite simply achieved, the correct trimmer being found beneath the "inspection cover" of L23 underneath the chassis.

The whole of the work involved in this modification may be achieved in a couple of hours without using a soldering iron or (except for the removal of the spare aerial socket and its connection to the left-hand socket) in any way disturbing the original wiring.—(W. T. J.)

## REFRESHER COURSE IN MATHEMATICS

By F. J. CAMM

8/6, by post 9/-

# Beginner's Guide to Radar-3

In This Concluding Article Transmitter-receiver Switching and P.P.I. Presentation are Dealt With

**L**AST month we saw how it was made possible to distinguish between enemy and friendly aircraft and proceeded to a discussion of some of the more usual types of aerial. One of the most popular was the stacked half wave with wire-mesh reflector, and this is illustrated below in Fig. 7. Amateurs who are familiar with the Sterba and 8 JK systems will be well acquainted

one quarter-wave away from the transmitter feeders. When the pulse is applied to the aerial, arcing takes place and the gap is effectively closed. This means that there is a quarter-wave stub across the aerial feeders. And it is known that such a stub offers infinite impedance; it is, in fact, often known as a "metallic insulator."

While the gap is closed the receiver is completely isolated from the transmitter aerial feeders. Immediately the pulse is completed and there is no output from the transmitter, the gap automatically opens. At the same time, the impedance of the transmitter output circuit rises to a value which is very high in relation to the input impedance of the receiver: the aerial therefore feeds straight into the receiver.

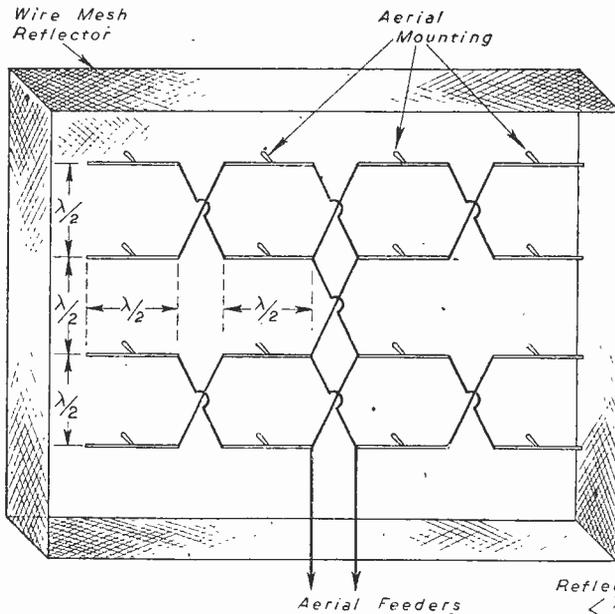


Fig. 7.—A representative form of stacked dipole aerial array, with wire mesh back reflector. The whole array is arranged to rotate for direction-finding.

with this particular form of assembly. The Yagi aerial is illustrated in Fig. 8 and is somewhat less efficient, but this is offset by the fact that it is more compact. The arrangement of Fig. 7 was used mainly for coast-watching stations (amongst other things) and the Yagi is used principally with the G.L. and S.L.C.

### Transmitter-receiver Switching

It has been stated already that the same aerial array is often used for both transmission and reception. Obviously, it is essential that the receiver should be disconnected each time the transmitter pulses, for otherwise the receiver would be damaged. This requirement can be met more easily than may at first appear. The method is shown in simplified form at Fig. 9, where it will be seen that a spark gap is connected across the feed lines to the receiver at a point which is exactly

### Peak and Mean Power

The question of power output from a radar transmitter is an interesting one. Instead of being given in terms of power input to the aerial it may be stated in terms of either the peak power in the pulse or the mean power. The two are vastly different due to the fact that the time during which the transmitter is actually transmitting is only a very small fraction of the total time. For example, if two micro-second pulses are being generated at a p.r.f. (pulse recurrence frequency) of 500 per second, the quiescent period

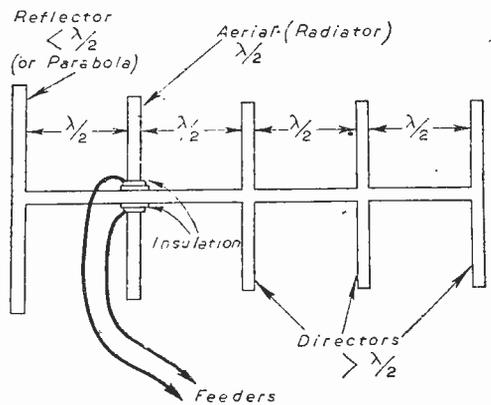


Fig. 8.—The Yagi type of directional aerial has a reflector, which is slightly longer than the aerial itself, or which consists of a parabola and any number of directors, which are slightly shorter than the aerial. The narrowness of the beam angle is governed by the number of directors. All elements are spaced by one-half wavelength.

between the pulses is 2,000 micro-seconds; the ratio between the "working" and "resting" times is therefore 1:1,000. This means that if the peak power were 200 kW.—by no means an unusual figure—the average power would be only 200 watts.

An advantage accruing from this is that relatively

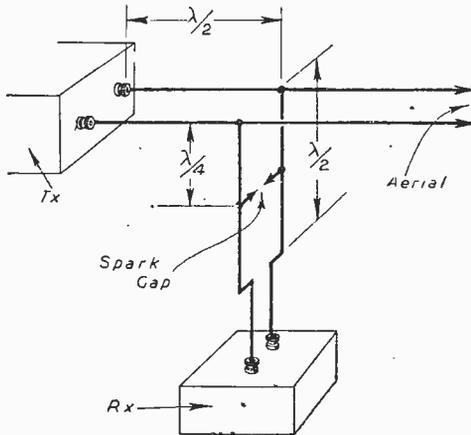


Fig. 9.—The method of connecting both transmitter and receiver to the same aerial is shown here. The spark gap (normally of the vapour-tube type) arcs over when the transmitter emits a pulse and so completes the quarter-wave "metallic insulator."

small valves can be used for the generation of very high peak powers, because of the long rest periods between pulses.

### P.P.I. Presentation

It has been mentioned that a G.C.I. (ground control of interception) system may be used for plotting enemy aircraft after they have crossed the coast inland, and for vectoring our night fighters on to the hostile craft. The G.C.I. equipment introduces another form of C.R. tube presentation, although it should be mentioned that a corresponding system is employed with some coast-watching radars. This particular presentation is known as P.P.I.: or plan position indicating. The P.P.I. tube shows the aircraft on a grid scale corresponding to a map of the country for a radius of 100 miles or so of the G.C.I. station.

This is done by using a special form of C.R. tube using magnetic instead of electrostatic deflection; coils mounted outside the neck of the tube replace the deflection plates. Bias is applied in the "X" direction so that the range trace is in the form of a radius on the screen. In addition, the "Y" coils are mounted on bearings and arranged to rotate around the neck of the C.R. tube at the same speed as the aerial array; in this case the aerial rotates through a complete revolution. By this means the radial trace is caused to rotate, or pivot, about the centre of the tube. The output from the receiver is applied to the grid of the C.R. tube to produce brightness modulation. The tube is normally biased so that the radial trace is only

just visible. But when the aerial picks up an echo the detected output from the receiver causes a bright spot to appear on the trace at a distance from the centre of the tube to correspond with the distance of the aircraft from the aerials. As the aerial array is constantly rotating, the bright spot would appear for only a very short time. To ensure that the spot remains visible for a sufficient length of time for plotting to take place, however, the tube has a fluorescent coating which produces an "after-glow" of about 25 seconds. As the aerial rotates once in 20 seconds, it will be seen that the bright spot, which actually resembles a small sausage,

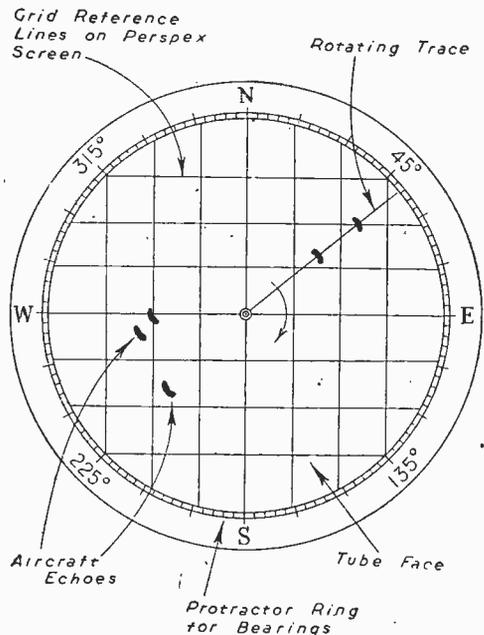


Fig. 10.—This illustration gives a good impression of the type of presentation obtained on a P.P.I. (plan position indicator) tube.

remains visible on the screen as long as the aircraft is within range.

The general appearance of the screen on a P.P.I. tube is shown in Fig. 10. The plan position indicator is used in conjunction with a normal range tube, similar to that already briefly described. In the case of a G.C.I. station two sets of stacked dipole aerials are used, one being mounted above the other. When receiving, however, the receiver can be switched from one aerial to the other at high speed, by using an electronic switch, so that two blips are obtained for each echo. This is done when height finding, as already explained. By comparing the size of the two blips an accurate estimation of height can be obtained from the calibration chart.

**NEWNES SUPERHET MANUAL**

6/-, or 6/6 by post from

**GEORGE NEWNES, LTD. :: Tower House, Southampton Street, London, W.C.2**

# Underneath the Dipole

Television Pick-ups and Reflections. By "THE SCANNER"

TELEVISION can no longer be said to be in its infancy. This oft-repeated bromide might have been true in 1937 or 1938, but it is now a cliché rarely uttered by regular viewers. Television has made much technical progress, of course, but I have come to the conclusion that the most rapid progress has actually been made not by the research engineers, but by the men behind the Emitron cameras—the producers, the editors, the technicians manipulating the equipment and also the performers who regularly disport themselves in front of the cameras. Every week the miracle of the entertainment world is performed by the boys at the Alexandra Palace, and it is time they had a hearty pat on the back.

## Shopping For Entertainment

In spite of very strict limitations, both of budget and studio space, the B.B.C. manage to put on about 30 hours of varied entertainment, most of which has to be specially adapted for the requirements of television. Not all the entertainment is of universal appeal, of course, and to attempt to satisfy all tastes all the time would be quite impossible. In any case, nobody can afford the time to allocate more than about five or six hours a week to viewing, and this allows fairly reasonable selective "shopping" to be done. Choose the programmes you think you will like, after referring to *The Radio Times*, and deliberately refrain from looking at others. That's a safe piece of advice for new viewers. There is little risk of television becoming the drug that ordinary broadcasting now is in many homes, where the loudspeakers bray all day long and nobody listens to the braying. Music while-you-work is all very well as a superficial background to this mechanical age, but its message is of necessity hackneyed and trivial. Television will never drop to this level; its strength and its weakness lie in the concentration upon which it insists.

## New Art Forms

Talk of "new art" probably conjures up in the minds of my readers the kindergarten varieties of drawings and paintings associated with long hair, dirty finger-nails and corduroy trousers in the vicinity of Chelsea or Bloomsbury. But no one will deny that the cinema is a new art form, with its own special way of story telling, in which both picture and sound are now separately and distinctly used in punctuative effect. The "talkie" has travelled a long way since the early silent films and ever since *The Singing Fool* introduced the use of sound films. Sound is no longer a mere accompaniment of the words spoken; music, effect noises and commentary each make their contribution to the final design.

The cinema had progressed a long way before the advent of sound, and many great silent pictures achieved a distinction which put them in a class entirely separate from the ordinary weekly "flick."

Sound seemed to stop progress in this respect for a few years, and now, especially in English-made films, we observe a competent handling of this composite craft which again places it in the "art" category. Television has made similar strides, and though its form may derive from a combination of sound radio and the motion picture, the most successful producers are those who ignore the concepts of either medium.

## Television Producers' Problems

The small screens of the home receivers, particularly those smaller than the 10in. by 8in. size, present the television producer with a special set of problems. Long shots cannot be seen in great detail, and, therefore, he must arrange his television cameras to make the greatest possible use of mid-shots and close-ups. Most of the devices of the cinema are available to him; cuts or dissolves from shot to shot, travelling ("tracking") or panning ("panning") cameras, sound effect backgrounds and so forth. But it has become obvious that they must be handled in a very different manner. On television, quick cutting from shot to shot, rapid panoramic movements of camera, or multiple dissolves are to be avoided. In short, the editing technique has to be modified to a much slower tempo, with emphasis on close-ups.

This rule applies not only to studio performances but also to outside television broadcasts, though in this case long shots are more tolerable. Consider the dignified presentation of the television broadcast of the Cenotaph ceremony, in which the many television camera angles were utilised with great discretion; changes of viewpoint being made at precisely the correct moments, and not too often. The prime object of the producer manipulating the controls is to make the "cut" from shot to shot as unnoticeable as possible. He can best do this by closely relating these changes to the associated sound, speech or music. Thus, on the Cenotaph ceremony transmission, cuts were made at the ends of the verses of hymns, on precise music beats. Another notable fact about this excellent outside broadcast was the remarkable transmission of the atmosphere of crowd emotion and reaction, which had a most moving effect upon viewers. The same could not be said of the remarkable film record, photographed from the end of a cathode-ray tube and televised the same night, nor of the newsreels' version of the event.

## Physical Limitations

Television plays and studio performances present the producer with a new set of problems. Limitations of studio space, lack of time for making wardrobe or make-up changes between scenes, apart from budget considerations, place restrictions upon the imaginations of the television script writers. On television, once a play is started, it has to play right through: there is no second chance

and very rarely an interval. A film-shot lasting, perhaps, 20 seconds on the screen occupies possibly an hour in its making, and many "takes" frequently have to be made before the film director is satisfied. With television, everything is "Take One," and that take may last an hour! The film studio which succeeds in completing the shooting of more than ten minutes' screen time on a picture in a week is doing very well; the B.B.C. have to produce 30 hours of television entertainment! What a contrast, and what a triumph for the boys at the A.P.! Their professional handling of a complicated technique must be the envy of the television engineers and producers of other nations. It is the intuitive use of the television equivalent of the old-established Dramatic Control Panel, together with the most careful pre-planning, that gives the modern television play its smooth continuity and polish.

### Independent Frame

Conscious of the acute rise in the costs of production, the film people have also become "pre-planning" conscious, and have evolved their own special system under the title "Independent

Frame." By exploring the smallest detail of every proposed camera set-up when a production is in the script stage, they are able to figure out ways and means of using various technical tricks to reduce the size and number of the settings which have to be constructed. For instance, a scene in which a principal artiste is seen in a railway station giving up his ticket at the platform barrier may, in fact, merely comprise a small piece of barrier erected in front of a ground-glass screen upon which is projected (from behind) a view of the railway station with engines and huge crowds well in evidence. Back-projection of moving backgrounds, such as the passing scenery viewed from a train or a car, has been a device used most effectively in films for many years. Static backgrounds with moving figures are far more difficult, and the wholesale substitution of projected backgrounds for expensively-built settings has required the improvement of many pieces of equipment. Perhaps some of these devices will be available for the television producers in due course. In the meantime, they will carry out, no doubt, quite happily in their own independent frame!

## Cathode-ray Tube Data

(Concluded from page 57)

on the same former as the oscillator coil. A half-wave valve rectifier is used. The smoothing condensers need be only of small capacity because of the high-frequency, but they must be able to withstand the voltage across them. A trimmer may be connected across the anode coil to adjust the output voltage and regulation of voltage. The output of the circuit shown should be about 1,500 volts, although by suitable modification much higher output voltage can be obtained. This circuit is much safer than the normal circuit because the condensers have a low capacity and any heavy loading of the circuit will cause the voltage to fall sharply. R.C.A. suggest this method for some of their cathode-ray tubes.

### A.C./D.C. Television Set

It is rather interesting to note that this high-frequency oscillator method of obtaining the high voltage for the cathode-ray tube indicates that it would be possible to make an A.C./D.C. television set or oscilloscope.

## Our Cover Subject

OUR cover illustration this month shows the control room of an Army radio station in Canada. Many ex-Servicemen will remember the various Army and Service radio stations which operated in all parts of the world, and that depicted is at station CFWH, situated at Whitehorse, Y.T., and is operated by Canadian Army personnel. All operations, including announcing, putting programmes on the air, etc., is carried out on a voluntary basis, and the station is on the air from 7 to 11 o'clock each night, especially for the benefit of the troops at Whitehorse.

## Club Notes

### THE BIRMINGHAM AND DISTRICT SHORT WAVE SOCIETY

Hon. Sec.: N. Shirley.

THE annual meeting of the above society was held on Monday, December 1st, when the following officers were elected: Chairman, Mr. T. Burton, G2BON; treasurer, Mr. L. Hawkesford, G2HKT; secretary, Mr. X. Shirley; librarian, Mr. R. Moreton; sale and exchange section, Mr. C. Wallis, G3CWV.

As from January 5th, 1948, meetings are held on alternate Mondays at 220, Moseley Road, Birmingham 12. Items planned for future meetings include a demonstration of an all-dry portable G—1, a five metre TX built from ex-Government equipment, talks on the principles of oscilloscopes and tips for the newly licensed amateurs.

### BURNHAM AND HIGHBRIDGE AMATEUR RADIO SOCIETY

Hon. Sec.: A. D. Taylor, G8PG, c/o P.O. Radio Station, Highbridge, Somerset.

THE above society is now in course of formation and it is hoped to hold a first meeting shortly. Interested amateurs in the Burnham area of Somerset are requested to communicate with the acting hon. secretary.

### RADIO SOCIETY OF HARROW

Hon. Sec.: J. Lavender, G2KA, 29, Crofts Road, Harrow, Middlesex.

ON Tuesday, November 4th, an interesting lecture on magnetic recording was given by Mr. Amos, B.Sc., A.M.I.R.E. of the B.B.C. A practical demonstration of a wire recorder, kindly loaned for the occasion by Mr. Greasley, G8VQ, then followed. Future programmes include a series of "Around the Shacks" talks by licensed members, starting off with a description of his gear by the secretary, Mr. Lavender, G2KA. Club membership now exceeds 70 and meetings are very well attended. Refreshments are available. Meetings alternate Tuesdays.

### LONDON SHORT WAVE CLUB

Hon. Sec.: R. Lisney, 4, Ongar Road, Fulham, London, S.W.6.

THE past month has been spent mainly in the renovation and building of the club transmitter at H.Q. at the "Crown", Battersea Park Road. The transmitter is now in the final stages of testing and a club licence is being applied for in the near future. Features at the meetings include Morse instruction and general discussion. Recently a discussion was held on centimetre oscillators with a number of members putting forward some interesting observations.

Now Available.

### Metric & Decimal Tables

By F. J. CAMM.

3/6, or 4/- by post from

GEORGE NEWNES, LTD., Tower House,  
Southampton Street, Strand, London, W.C.2




**"Beautiful!"**  
**"Satisfying!"**  
**"Unconventional!"**  
 —they say

NO wonder people are talking about the new Extension Speaker that gives nothing but the truth. No "box" resonance, because this isn't a "box." It's the

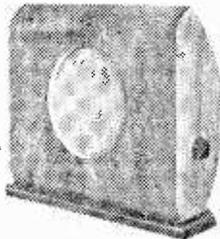**"Bafflette"**

by  
**Richard Allan**  
 Regd. Design No. 851509



Unique design is the secret of its fidelity. Technically perfect, lovely to look at in walnut veneer, 4 GNS.

(Mahogany, £4 10s.)

Reputable Retailers have it

**RICHARD ALLAN RADIO LTD.,**  
 CALEDONIA ROAD, BATLEY, YORKS.  
 Tel.: Batley 1123 'Grams: "Acoustics Batley."

**PITMAN'S ★**  
**Radio Books**

**The Cathode Ray Tube Handbook**

By S. K. Lewer, B.Sc. A guide to the basic principles of design, construction and operation. **ELECTRONIC ENGINEERING** says: "An excellent survey of the basic principles of the tube leading to the complete oscillograph, with a surprising amount of interesting allied information." Second Edition, 6s. net.

**Modern Radio Communication 2 Vols.**

By J. H. Reyner, B.Sc.(Hons.), A.C.G.I., D.I.C., M.I.E.E., M.Inst.R.E. A model of clear exposition, this work throws light on all branches of modern radio theory. The two volumes together provide a complete groundwork for the student of radio engineering. Vol. I, Ninth Edition, 8s. 6d. net. Vol. II, Fourth Edition, 7s. 6d. net.

**Thermionic Valves in Modern Radio Receivers**

By Alfred T. Wits, A.M.I.E.E. A comprehensive handbook covering every aspect of modern theory and practice in the application of thermionic valves to radio receivers. It is a first-class book for all engaged in commercial radio work, as well as for students and keen amateurs. Second Edition, 10s. 6d. net.

**PITMAN**, Parker St., Kingsway, London, W.C.2

**CRYSTAL SETS**

A charming new model of the Lesdix Boudoir Crystal Set in bakelite, with semi-perm. detector mounted on top; condenser tuning: 1716. Headphones 12/6 a pair. Spare crystals, 1/6 per pair.



**MOTORS.**

Electradix Micro Motors for Instrument work and models 2in. x 1 1/4in., weight only 10 ozs., 12/24 volts;

work from dry cells or A.C. Mains through transformer, laminated fields, ball bearings, totally enclosed, small vee pulley, centrifugal relay speed governor on shaft removable for second shaft drive. Precision made ex W.D. stock. Worth 45/- . Price 21/- each. Limited stocks.

**TERMINALS.** Mk. III solid brass double terminals with nuts and washers, 7/6 dozen. Belling Lee plated or brass 5/- dozen. Heavy insulated Belling, 10/- dozen.

**LAMPS.** Neon lamps miniature, 1/2 watt 230 volts, 2/6 each; letter plate Neons E.S. fitting standard size, 2/6, postage 9d. Osglin Beehive Neons, 230 volts, 3/1, postage 9d.

**MAGNETS.** D.C. Electric magnets, weight 10 oz., lift on 2 volts 11lb., 4 volts 31b., 6 volts 41b., new, surplus, 7/6 each. Permanent powerful flat bar magnets, 2in. x 1in. x 1/8in., drilled 2 holes each end, for any pole pieces, 2/- pair. The wonder Midget magnets. Alni perm. steel disc: 5/8in. diam., 3/8in. thick, with 3/16in. centre hole, 3/6 each. Large stock of Horseshoe magnets. Send for special Magnet Leaflet, "P.W."

Please include postage for mail orders.

**ELECTRADIX RADIOS**

214, Queenstown Road, London, S.W.8

Telephone: MACaulay, 2159

**FIRST-CLASS RADIO COURSES . .**

**GET A CERTIFICATE!**

**QUALIFY AT HOME—IN SPARE TIME**

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

**FREE GUIDE**

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Brit.I.R.E., A.M.I.E.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams, Matric., London B.Sc. (Eng.), A.M.I.P.E.E., A.M.I.Mech.E., Draughtsmanship** (all branches), etc., together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSES**

**NATIONAL INSTITUTE OF ENGINEERING**  
 (Dept. 461), 143, HOLBORN LONDON, E.C.1.

Have you Heard—

**THE CONCERTO**

For your Pick-up and Speaker ?

This is the finest record reproducer available because—

1. Distortion is only 1 1/2 per cent. at 6 watts, 2 per cent. at 12 watts. (Independently certified figures.)
2. Hum level is negligible.
3. It will take any type of pick-up—moving coil—moving iron—crystal.
4. Separate Base and Treble controls with a double bass boost circuit.
5. 12 months unconditional guarantee.
6. 9 valve circuit—8 triodes plus Rectifier.

PRICE **£27 : 10 : 0**

The "Concerto"—the amplifier that is making itself heard.

**CHARLES AMPLIFIERS LIMITED**

1e, Palace Gate, Kensington, W.8.  
 Telephone: Western 3350

## H.B.L. FOR THE HOME CONSTRUCTOR

We specialise in supplying complete kits and individual component parts for all circuits described in this journal.

**SPECIAL OFFER.** Sin. P.M. Speakers, 2/3 ohm., 17/6.

**SHORT WAVE COILS.** 4-pin, set of 3, covers 12 to 80 metres. Complete with circuit, 9/9.

**MATCHED PAIR DUAL WAVE COILS** with circuit diagram, 9/- . Single coil with circuit, 4/6.

**LEE COIL PACK.** 3-waveband, complete with wavechange switch, trimmers and full instructions.—How to employ in a Superhet receiver, £11/15/0.

**WEARITE 605B COIL PACK.** £2/2/0.

**WEARITE CERAMIC SWITCHES.** We supply individual parts or kits of parts to make 1 pole 12-way, 2 pole 6-way, 4 pole 3-way, from 1 to 6 bank.

Send 2d. stamp for our Brochure of Kits, Peto-Scott Receivers, Components, etc. Also details of our Practical How-to-Build-it Books, complete instructions and designs for Amateur Constructors.

**HENBEST BROS., LTD.,**  
26, Green Lanes, London, N.13.

Telephone: - BOWES PARK 6289.

### ALEC DAVIS (Supplies) LTD.

18 Tottenham Court Road, W.1

offer for sale the following from stock:—

**METERS.** 2in. 20 amp charging meters with non-calibrated scale, 6/-; 2in. 12 amp R.F., 8/6; 2in. square flame flush mounting, 0.5 m/a and 0.1 m/a, 12/6 and 17/6, respectively; 2in. plug-in 0.500 Mm, 25/-; 1in. 0-500 Mm/a, with luminous scale and pointer on black dial and locking ring for fixing, 17/6. 6d. carriage on all.

**RECTIFIERS.** 12 volt 1 amp. by Westinghouse, 4/-, plus 6d. carriage.

**IMPULSE COUNTERS.** operating on 24 volts. Made with circular scale, plain or three-quarters of circumference and red for fourth quarter. "Clicks" 120 times for one complete revolution and completes external circuit over red quarter of scale, 5/-, plus 6d. carriage.

**VIBRATOR PACKS.** 12 volts D.C. input. 210 volts/70-m.a. D.C. output, 38/6, plus 1/6 carriage.

**DIAGRAMS** for U.S. receiver CC-46145 of BC-946, 5/-.

**HEADPHONES & HAND MICROPHONES.** complete with moving coil insets for "mikes" and "phones." 12/6 plus 1/- carriage.

**MIDLAND INSTRUMENT CO. RECEIVERS.** No. 19 SET, complete with four valves, (3)-A.R.P.12, and A.R.B. operates from 2-v. L.T. and 120-v. H.T. Range 6 to 9 mcs., superhet, calibrated S.M. drive with other controls, suitable for phones or small speaker, front panel size 9 1/2 in. x 6 in. An attractive receiver offered at a fraction of original cost, 35/- post paid.

**VIBRATOR PACKS.** input 6-v., output 90-v. 20-m/a., contacts require cleaning, otherwise in perfect condition, 10/- . No. 81-B RECEIVERS, complete with 8 valves 2.4 to 6.7 mcs. 6.3 and 250-v., 60/- . **ELIMINATORS.** 200-250-v. A.C. output 120-v. 20-m/a., D.C. fitted neon stabiliser, brand new, 40/- . **ATTENUATOR** units type 17, fitted control knob with pointer scale marked 0-100, brand new, boxed, 3/6, 36/- doz.

Hundreds of other interesting radio and electronic items, send for our current lists. Orders over 30/- post paid. No C.O.D. under 20/-.

**MOORPOOL CIRCLE**  
**BIRMINGHAM, 17.**  
Tel.: HARBORNE 1308 or 2844.



We are all familiar with shortages—material shortages—but there is one shortage that nothing on this earth can put right—and that is TIME. On every hand, one hears such remarks as "I haven't had the time."

Radio amateurs are no exception—in fact, it is true to say that radio amateurs lack time more than most—to build or modify equipment—erect new aerials—actually work "on the air"—and the host of other complications which attend a radio amateur's life.

In "the good old days," there was little option but to build one's own equipment. Today, we say good luck to the man who still prefers to build his own gear—there is nothing like some practical experience. Many "hams" will have learnt that whilst "straight" sets are not difficult to make, even then many snags crop up and it is not easy to obtain a good performance over the wide range of high frequencies allotted to amateurs.

Few will question the necessity of using a highly selective superheterodyne receiver in this days of congested bands. Those who have actually attempted to build one will know that a lot of time is taken up in the actual construction and usually even more in making adjustments, getting rid of the "bugs", and obtaining adequate performance on all the usual bands.


Some amateurs (usually those with a professional background) have the knowledge, and test equipment, to build an excellent receiver. To others we say buy an Eddystone "640" Receiver. Commercial interests aside, we can assure you in all sincerity that you will be well satisfied with its performance—many receivers are now in use and by every post we receive testimonials to the excellent results obtained. You will get excellent value for your money—the receiver is a solid engineering job, entirely British made, and costs £42 0 0. (Plus P.T.) which, judged by modern standards, is anything but dear.

Space does not permit the discussion of the finer points of the "640" and of their relative importance but we hope to do so in future advertisements. If you are not already familiar with the receiver, you are invited to get in touch with one of our agents, or with us direct for information.

With a first-class communications receiver sitting on your operating table, your problems on the receiving side will be at an end, and you will have more of that infinitely precious, if abstract, commodity—TIME—to devote to your many other interests.

# EDDYSTONE

## CRYSTAL PICK-UP

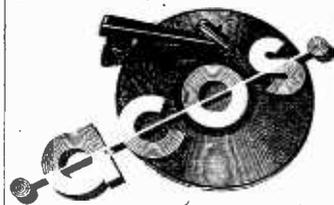

WITH *Unbreakable* CRYSTAL

The ACOS G.P.10 combines purity of reproduction with extreme reliability. A unique flexible assembly renders the crystal virtually unbreakable, while a needle-pressure adjustment is incorporated in the base. Resonance-free response from 50-8,000 cps. Output 1.5 v. at 1,000 cps. Needle pressure 1 1/2 ozs. (adjustable). Vibration-free arm movement. Screened lead. Flexible coupling A protects crystal B against breakage. Price in Great Britain 49/- (including P.T.). Licensed by Brush Crystal Co. Ltd.



Obtainable only from Radio Dealers

**COSMOCORD LTD**  
ENFIELD; MIDDLESEX

## A FREE BOOK on Morse Code Training



There are Candler Morse Code Courses for Beginners and Operators.

Send for this Free "BOOK OF FACTS" It gives full details concerning all Courses.

**THE CANDLER SYSTEM CO. (S.L.O.)**  
121, Kingsway, London, W.C.2.

Candler System Co., Denver, Colorado, U.S.A.

## "DORSET" SUPERHET CIRCUITS

2/6

**A.C. FIVE.** Three wave.

**A.C./D.C. FIVE.** Three wave.

**BATTERY FOUR.** 1.4v. Three wave.

**BATTERY PORTABLE.**

Four Valve medium and long.

Six Valve A.C./D.C. AMPLIFIER

**BUILD A "SUPER" SET**


Theoretical circuit, under chassis layout, above chassis layout, heater wiring, group board assembly and point to point wiring instructions, also parts list. Can be made without previous radio experience. (Chassis, coil packs, group boards, I.F.'s, 5m. Speakers, in stock.

Theoretical circuit and price list only 2 1/4.  
**WELDONA RADIO ACCESSORIES, LTD.**  
38, GLOUCESTER ROAD, BRIGHTON

# Trade Notes
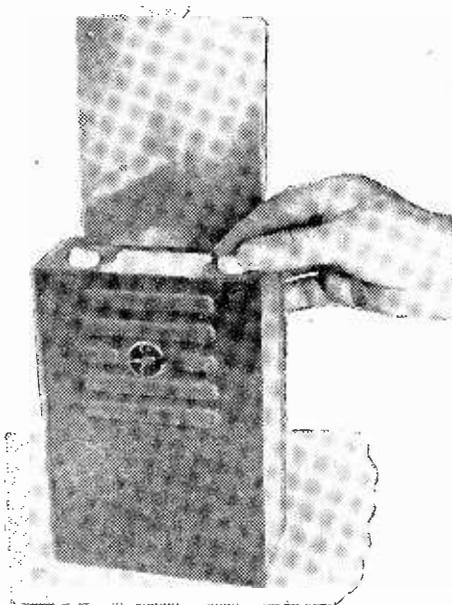
## Hermes Radio Tourist

A NEW type of "personal" receiver has been produced by Hermes, Brooke & Co., a British firm, and is made under the Enham Industries scheme by disabled ex-Servicemen. As may be seen from the accompanying illustration the receiver is finished off to resemble a book, and has a fabric finished metal case available in powder blue, cream, green, rose, black-and-gold, brown, etc. The aerial is enclosed in a slide at the rear and is withdrawn to the position shown in the illustration when it is desired to listen. There are two controls, tuning and combined volume and on/off switch. The




The Hermes "Radio Tourist."

central plate carries tuning points for various stations. In spite of its miniature overall dimensions (8½ in. high, 6 in. wide and 2½ in. deep), it incorporates a 3½ in. moving-coil loudspeaker and operates from two U2 cells and a 67½ volt H.T. battery. The circuit is of the superhet type, utilising four valves of the 1.4 volt type, and provision is made for the connection of an external aerial if this is called for. A sling carrying case may be obtained in water-proof leather and canvas. The quality of reproduction is quite pleasing, and the receiver is, of course, directional, due to the frame aerial. The price is £13 13s., plus P.T.
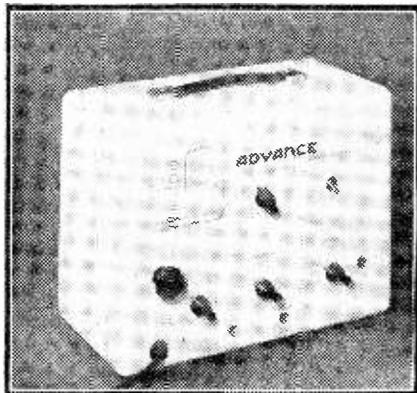
## Advance Signal Generator

WITH the increasing use of television equipment, Servicemen find a need for a signal generator, which includes the television frequencies as a

fundamental of the range. In the majority of signal generators the range does not include these frequencies and thus one has to make use of harmonics, and it is not always a simple matter to select the right ones. In addition, of course, the accuracy may suffer. In the "Type E" Generator,



The "Advance" Type E Signal Generator.

produced by Advance Components, Ltd., the actual fundamental range goes up to 60 Mc/s, whilst the harmonic range runs from 60 to 120 Mc/s. Described by the makers as a laboratory instrument at a popular price we have found the generator fully up to the maker's claims. There are six tuning ranges, 100-300 kc/s, 300-1,000 kc/s, 1-3 Mc/s, 3-10 Mc/s, 10-30 Mc/s and 30-6 Mc/s. These are selected by the top central control, and the three lower controls adjust the A.F. output—in steps from 0 to 5 volts, the voltage output from 0 to 10 and a multiplier of five steps from 1/10 V to 100 mV. There are also three jacks providing the A.F. output, full R.F. and attenuated R.F. Supplied with the equipment is a shielded A.F. lead provided with crocodile clips, and an R.F. coaxial lead, with a dummy aerial padder, giving three separate outputs. The entire instrument, measuring 13 in. by 10½ in. by 7½ in., is finished in cream enamel and weighs 15½ lbs.

On test the instrument performed very well indeed, and was, in fact, used for lining up a home-built television receiver. The sound and vision frequencies are separately marked on the appropriate range and it was found that the shielding and general design was of a very high order so that settings were most accurately obtained. The only point to be observed at the U.H.F. is to keep the leads from the padding unit very short—not more than three inches, to avoid standing waves and similar troubles. At 19gns. this provides a really first-class servicing instrument which may be highly recommended.

## REFRESHER COURSE IN MATHEMATICS

8/6 by post 9/-

From: GEORGE NEWNES LTD.  
Tower House, Southampton Street, Strand, W.C.2

# Programme Pointers

The Music of To-morrow is Discussed by MAURICE REEVE

CONCERTS are arranged, artists booked and programmes drawn up with far greater prescience and foreknowledge than coal is laid up for the winter or the level of income tax decided. When we hear a symphony concert to-morrow it is the result of plans drawn up anything from six to twelve months ago. It is no exaggeration to say that the musical life of the country for 1949, rather than for 1948, has, for better or worse, been largely decided; that for the year just beginning was hatched long, long ago.

What are those plans? And what can one's summing up be on the year now past? Neither are rosy and both can be delivered in the same phrase, the mixture as before. Masses and masses of symphony concerts and solo recitals—mostly piano—with, for the most part, the same hackneyed programmes. Beethoven, Chopin and Tschaiikowsky *ad nauseam*, with perhaps a little less Tschaiik than in the immediate past. This welcome retrocession is doubtless due to the even more welcome resurrection of Wagner.

With the return of some of the famous pre-war virtuosos, the indiscriminate and unthinking filling of concert halls is largely a thing of the past. The quality of the performance is again beginning to take its rightful place in the concert-goer's mind. "They are doing Beethoven's Fifth," and off they rushed. Now, "Who is doing it?" is often asked before money and time are spent on totally inadequate performances. And, if only "So-and-So" is doing it, and not So-and-So, more and more are exercising discrimination.

## Modern Music

More programme space is given, and will continue to be given, to modern music than was allotted to it after the 1914-18 war, which is very proper and necessary, though it does act as a great deterrent to the box office. The innate conservatism of the British people is no more prevalent and undying anywhere than in music, and the first part of a programme has to be of the very highest, appeal if the "innovations" and "originalities" introduced into part two are not to act as a dead weight on the attractions of the concert as a paying concern. No recognised British master, living or dead, can "draw an audience" on his own, nor is he seldom asked to, for that matter, whilst the younger school, especially the continental flowerings, have to rely for their support on their own especial sympathisers and imitators, as with all freak growths everywhere.

Although this music must be performed (one recalls Malvolio's "I have a reasonable good ear for music, let us have the tongs and the bones"), one cannot help feeling that most of it will share the same fate that was meted out to the "masters of the future" in the days above referred to. These latter, to-day, are little more than museum pieces. But they had to be tried; they formed the trial XIs from which Debussy and Strauss, Sibelius and Elgar, to go no farther back, were picked for international honours.

## More Wagner?

The coming year would seem as if it will be run on the same lines as was 1947, with, perhaps, more Wagner and more opera, though German opera is most unlikely for some time to come. That glorious form of musical self-expression, chamber music, will be prevalent, and the unforgettable Schnabel - Fournier - Szigeti - Prinnrose combination will be emulated by the collaboration of other famous soloists. We shall continue to look to the B.B.C. and it will not be in vain, as our chief provider, the Covent Garden of music, distributing the world's produce in all its manifold variety to all corners of the land. Through its magnificent series of symphony and other concerts, at which financial loss, if any, does not carry the same shattering and catastrophic results as in the adventures launched under private enterprise, we shall continue to hear the rightly beloved classics together with the best, and not so good, of the modern world. To continue in our horticultural metaphor, the pineapples and the peaches, together with the medlars and the gooseberries, will be served up to us, all ripe and unrationed. Raspberries we shall have to continue to grow ourselves.

## Private Enterprise


For private enterprise, the position may well seem intolerable and the problem unsolvable. On the one hand it is told it must not give so many performances of the hackneyed masterpieces, which are the only concerts that really pay (and, in parenthesis, are the only concerts at which the great virtuosos can be heard because they simply will not appear in new and untried works); whilst on the other, it is bidden to perform more "originally designed" programmes, even if only for art's sake, but which do not pay to anything like the same extent, if at all. The B.B.C. seems the only complete answer.

A word about the totally needless repetition of programme items, artists' names and other data. Recently, I turned on a symphony concert at *half time*, and from then to the end I had to listen to the fact that the concert was coming from the Royal Opera House, Covent Garden, the works performed, the orchestra's name, together with its leader and conductor, chorus and chorus master, no fewer than six times! Heaven knows how many times in all it must have been repeated. The whole thing was, or is, perfectly ridiculous, and the more so when we remember that it is all in *The Radio Times*, which we are told sells three million copies per week, and is therefore obviously being referred to by the vast majority of listeners. In sporting commentaries the disease is much more virulent, and the repetition of runs scored at cricket, goals at football and, worst of all, that the inside left of such and such a team is "that tall, sturdy Scot," or that "Blankshire opening batsman who, you will remember, scored a century in his first Test," is not less, than nauseating. The whole question urgently requires the most serious attention.

# HENRY'S

**RADIO  
RUCO  
TUNING  
ASSEMBLY**

**£5  
ONLY**

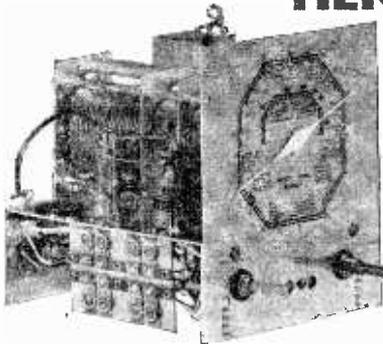

Send stamp for Latest Component List. Cash with order or C.O.D. (over £1).

Unit includes : 3-Wave Coil Pack, I.F. Trans., Wave-change, Valve-holders, Dial with drum drive, .0005 three way, with wide-scope Osc. Section for band-spread tuning on S.W. Padders, Trimmers and all small components necessary to complete circuit of a 6K8 Freq. Changer, and 6K7 Amplifier. Wired, tested and aligned, complete with circuit.

**THE FIRST MIDGET COIL PACK—**

“Q” COIL PACK.—8 High, “Q” ultra midget coils, wound on plastic low-loss formers, adjustable iron cores. Complete switching and trimmers. Ready for use. Size 3 1/2 in. x 2 in. x 2 1/2 in. 15.5-52m., 200-590m., 800-2,000m. Price, 33/- only. Weymouth and Atkins Coil Packs can also be supplied from stock.

**MIDGET VALVES.** We can supply from stock, by return, 185 at 15/10, 1R5 at 15/10, 1T4 at 14/-, 3S4 at 14/-. Ceramic Valve-holders for above 1/- each.

**MIDGET VALVE CANS.** Complete can, with retaining spring, mounted on ceramic base, for above, 2/6 each.

**MIDGET I.F.T.s.** 465 Kcs., iron-cored, 2/6 each.

**WEARITE,” 21/- pair. “WEYMOUTH,” 18/9 pair.**

All your component requirements.

**HENRY'S, 5, Harrow Road, W.2.**  
Paddington 1008 9.



Now that Stentorian Extension Speakers are coming back to the shops the pleasure of listening again becomes complete. Just plug in one of these superb permanent magnet speakers to your set and you can enjoy its clean, pure tone anywhere in the house: sitting-room, kitchen, bedroom, wherever you happen to be. Ask your local dealer about them.

**PRICES**

<b>SENIOR MODEL</b>	£ s. d.
Type SC with Universal Transformer	5 15 6
8X minus	5 2 8
<b>JUNIOR MODEL</b>	
Type JC with Universal Transformer	5 0 0
JX minus	4 19 6
<b>CADET MODEL</b>	
Type CC with Universal Transformer	4 10 0
UX minus	4 0 0
<b>BABY MODEL</b>	
Type BC with Universal Transformer	2 19 6
BX minus	2 13 6
<b>MINOR MODEL</b>	
Type MC with Universal Transformer	2 5 6
MX minus	1 19 6



# Stentorian

THE PERFECT EXTRA SPEAKER FOR ANY SET  
WHITELEY ELECTRICAL RADIO CO. LTD., MANSFIELD, NOTTS

**O. GREENLICK, LTD.**

**RESISTANCES.** Heavy duty twin resistance with variable slider, 300 ohms, 1 amp., a compact job, 25/-. Mains droppers, 800 ohms, 0.3 amp., 5/6; 1,000 ohms, 0.2 amp., 4/6; 600 ohms, 0.3 amp., 4/-. Potentiometers, wire wound, 1,000, 2,000, and 50,000 ohms, 2/6 each.

**TUNING UNITS, COILS.** The “Ruco” tuning assembly, completely wired all wave, for use with a 6K8G and 6K7G valves, complete with dial, I.F.s., etc., factory aligned and tested, 45/-. The “WEYMOUTH,” all wave coil pack, comprising chassis with all coil padders, etc., 36/6. M.L. wave T.R.F. coils with reaction, High Gain, pair, 7/6. “Weymouth” midget iron cored I.F. trans., 18/9. Standard iron cored I.F.s., 15/- pair, 2 Meg. I.F.s., 2/- each.

**CONDENSERS.** 8 mfd, 500 v., 4/-; 32 mfd, 350 v., 5/-; 8+16 mfd, 350 v., 7/6; 20 x 20 mfd, 150 v., 7/6; 8 mfd, 75 v., 1/-; 4 mfd, 12 v., 9d.; 0.1 mfd., 8/- doz.; 0.01 mfd., 8/- doz.; 2-gang, .0005 mfd., 11/-; 6/-; Split Stator, .00017 mfd., 6/-; 3-gang, .0001 mfd., 7/6.

**TEST BRIDGE.** The “AVO” test bridge, A.C. operation, checks all values of condensers and resistances, valve voltmeter indicator, 21/.

**MAINS NOISE SUPPRESSOR.** for the suppression of all noise from Fluorescent Motors, Friges, Cleaners, etc., each, 16/6.

**SPEAKERS.** P.M. Minus trans., 5in., 17/6. Goodmans, 12in., T21235/15, 48/10. **CABINETS,** table model, Walnut veneered, inner dimensions, 21 1/2 in. x 10 1/2 in. x 7 1/2 in., 35/-; midget, sprayed cream and green, 13in. x 7in. x 6in., 35/-.

**CHOKES.** Ultra midget 40 ma., 5/-; midget 40 ma., 5/6; Standard, 100 ma., 8/6; Heavy Duty, 1,500 ma., 12/6.

**PICK UPS.** “Rothermel” Model S.3 or S.12, at pre-budget price, 52/6. **CHASSIS.** The W5V for the 5 v. superhet, fully drilled for valveholders, I.F.s., etc., 11 1/2 in. x 5 1/2 in. x 2 1/2 in., 7/-; the W4V chassis for the 4 v. receiver, 11in. x 4 1/2 in. x 2 1/2 in., 6/0. **SWITCHES.** Yaxley type, 3 Pole 2 way, 2/-; 4 pole, 3 way, 3/-; 4 pole, 4 way, 3/6. Our list at 24d. contains a host of other interesting lines.

34, Bancroft Road, Cambridge Heath Road, London, E.1. STE 1334.

# “K” COILS

High efficiency coils with adjustable iron dust cores, in screening cans, size 2 x 1 x 1 in.

Five wave bands available in aerial, H.F. and oscillator types. 4/9 each, all types.

**I.F. TRANSFORMERS**

465 Kc/s permeability trimmed. Size 2 x 1 x 1 in. Type P2. 17/6 pr.

**WEYMOUTH RADIO MANUFACTURING CO., LTD., CRESCENT WORKS, WEYMOUTH.**

**1948 OFFERS**

**5 VALVE SUPERHET. RECEIVER CHASSIS,** 200-250v. A.C./D.C. Outstanding performance on all three wavebands. Size 11-51-61 ins. Valves 6K9, 6K7, 6Q7, 25A6, 25Y5. A really first-class job, with attractive square plane dial. Price including tax, £13.5.0 only. Satisfaction guaranteed. Delivery from stock.

**T.R.F. RECEIVER KIT,** Long and Medium Waves, 200-250v. A.C./D.C. Complete in every detail, only cabinet required. Includes valves 6K7, 6J7, 25A6, Rectifier, 5in. P.M. Speaker. Drilled aluminium chassis, 10-51-2 ins., slow motion drive. Attractive coloured station-named illuminated ivorine dial, wire, sleeving, screws, solder, etc. All components of first-class quality and guaranteed. Circuit and detailed wiring diagrams supplied. Price including tax, £7.6.9.

**DIAL & DRIVES.** Complete with S.M. Drive, Pointer, Glass and Escutcheon. Square plane 41-34 ins., Airplane 31 ins. diam. with I. & M. Wave. Station-named ivorine dial, 10.6 each. Full Vision 8-51 ins., with 3 waveband fully station-named ivorine dial in three colours (exceptionally attractive dial and escutcheon), 11.6 each.

**CABINETS,** Highly polished wood (walnut) attractive design, 121-7-61 ins., 25/6. Suitable L. & M. Wave ivorine Dial, I.E. Aluminium chassis 10-51-2 ins., 3.9. sin. P.M. Speaker, 15/6. .0005 mfd. 2-gang tuning condenser with S.M. Drive, 10/6.

**SOL. CONTROLS,** 5,000, 10,000, 50,000 ohms, 5 meg., 1 meg. less switch, 2/9 ea., 10,000 ohms, .25 meg., .5 meg., 1 meg. with switch, 5/6 ea.

**LINE CORD,** 3-way, .3 amp., 60 ohms per ft., 7d. per ft.; .2 amp., 90,100 ohms per ft., 8d. per ft.

**MISC.** Metway shrouded mains droppers, .3 amp, 750 ohms, for external mounting, 4/9 ea. T.R.F. coils, combined medium and long wave, with reaction, boxed with circuit, 7/6 pr., 25 mfd, 40 v. Electrolytics, 14/- doz.

**TERMS.** C.W.C. or C.O.D. under £1. Orders over £2 post free. Special terms for Trade. Lists 21d.

**E. POWELL, LIDGET HILL, PUSEY, LEEDS.**

## LONDON CENTRAL RADIO STORES

"WESTECTORS." Type W.X. 6. Brand new. 1/6 each.

**EX-RADAR VIEWING UNITS.** Consisting of 6in. diameter electrostatic C.R. Tube. 7 valves, including 4 EF50, potentiometers, resistances and other components. In metal cabinet, 18 x 8 x 7 1/2in. Bargain price. **£3/7 6**, carr. and pkg. **17/6** extra, **10/-** allowed for return of case.

**MULLARD** Logal, 9-pin valve holders, 6/- per doz.

**MOVING COIL HEADPHONE OR MIKE INSERTS.** Voice coil resistance 30 ohm. Owing to large purchase now reduced to 3/- each.

**FRACTIONAL H.P. A.C. MOTORS.** Brush type, 220-250 v., 50 cycles, approx. 5,000 r.p.m. Overall diam. 10 x 4in. In. spindle extends 1in. both ends. **37/6**. Post 2 6 extra.

Telephone line or misclecto switches, 3 or 4 bank, 26 contacts. Have various applications, including automatic tuning, circuit selection, etc. Operates on 25-50 volts, 3 bank, **25/-**; 4 bank, **28 6**; 6 bank, **30/-**.

**EX-G.P.O. ELECTRO MAGNET COUNTERS.** 500 ohm D.C. coil, count up to 9,999, operate from 25-50 v. D.C., numerous applications, 5/6 each.

**EX-R.A.F.** Camera Motors, dimensions 3in. x 2in. x 1 1/2in., 12v. and 24v., **8 6**.

**TYPE N1147A.** 7-valve U.H.F. receiver, range approx. 200 megacycles (with 4 Acorn valves). A real opportunity. Beautifully constructed and fitted with micro-condenser drive. Valve types: two EF36 and EBC33, three 954, one 955. In black metal case, 8in. x 7in. x 6in. Set complete with valves. Carr. paid, **£2 7s. 6d.**

**TWIN ELEMENT HEAVY DUTY** sliding resistances, in the following sizes: 5.4 ohm at 20 amps., **47/6**; 12 ohm at 10 amps., **39/6**; 70 ohm at 5 amps., **35/-**. Single Element 14 ohm at 5 amp., **13 6**. **SELF ENERGISING HANDSETS, 15/-**.

**TELESONIC 4 valve portable**, new, fixed range, suitable for conversion to nidget set. **37 6**, plus 2/6 postage and packing. Brand new Class B output Amplifier, ready for use, **15/-**.

The famous R.A.F. 1155 all-wave set, complete with separate Power Unit and Speaker. **£20**. Carr. and pkg. **17/6** extra, **10/-** allowed for return of case. New 2-Valve Battery, Class B, output amplifier, **25/-**.

**VISUAL UNITS.** With 4in. Cathode Ray Tube, two EF50 and two YR 5F valves, potentiometers, etc. Complete on chassis 15 x 5 1/2 x 5in., **42/6**. Carr. and pkg. **17/6** extra, **10/-** allowed for return of case. I.F.F. set 9 valve rotary transformer 18 volts 3.13 amps. to 450 volt, **34/6** carriage paid.


We still have stocks of Ex-R.A.F. Valves as advertised in previous issues.

We have a large stock of Ex-Govt. Radar U.H.F. and Radio Receivers. It will pay you to give us a call. Nearest tube: Leicester Square.
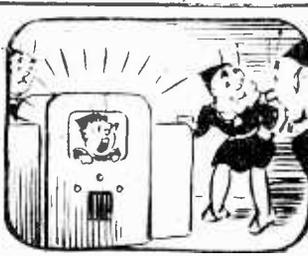
## LONDON CENTRAL RADIO STORES

23 Lisle Street, London, W.C.2  
(GERRARD 2969)

Closed Thursday 1 p.m. Open all day  
Saturday.



The "Fluxite Quins" at Work

"Look who's there! Televising to-night!  
Why, it's Ol demonstrating FLUXITE!"

From within came a cry:  
"Televising! My eye!  
I've soldered myself in here tight!"

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in government works and by the leading engineers and manufacturers. Of all ironmongers—in tins, 10d., 1/6 and 3/-.

To CYCLISTS: For stronger wheels that will remain round and true, there's a time tested tip. Tie the spokes where they cross with fine wire and SOLDER. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 1/6, or filled, 2/6.



ALL MECHANICS WILL HAVE

# FLUXITE

IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE, also on "WIPE JOINTS." Price 1d. EACH.

FLUXITE LTD. (DEPT. W.P.),  
BERMONDSEY ST., S.E.1

Headline seen in recent papers:

## "LIFE LONG VALVES"

"RESEARCH SUPPRESSED"

We at BULL'S wonder how much Truth there is in it—what we know is—our VALVES are certainly LONG-LIFE Products.

**BIRMINGHAM**—1D5, 1D6, 5B, 250A, 6B6, 6K6, 6K7, 6S37, 6SN7, 6T7, 6V6, 7B5, 7B7, 7B8, 7C6, 7Y4, 8D2, 9D2, 10D1, 11D3, 11D5, 12SR7, 25Z4, 15D2.

**CONSOR.**—4TPB, 4TSP, 13SPA, 13VPA, 40SUA, 41MHL, 41MP, 41MPT, 41MRC, 41STH, 42-OT, 42OT-DD, 42PTB, 202VP, 202VPB, 203THA, 210DDT, 210LF, 210LF-2, 215SG, 220HPT, 220OT, 220P, 220PA, DDLA, MP/PEN, MS/PEN, MS/PENB, MVS/PEN, OM4, OM6, OM9, OM10, PT10, H1VAC—XD, 4H, XL, XP, XSG, XY, XW.

**MARCONIOSRAM.**—CRT-E4102/B7, D41, D42, D63, DA30, DG2, DL63, DL74M, GTC, GU50, H30, H63, H62, HD24, H12, HL2K, KT2, KT4, KT41, KT61, KT63, KT763, KT71, KT74, KT751, KTW63, KTZ41, KTZ63, KTZ73M, L2B, L63, L72, L55B, MH41 MKT4, MLA, MS4B, MSP4, MX40, N14, P2, P125H, PX25, QP21, S23, U10, U14, U16, U17, U18 20, U31, U50, U52, U74, VM4G, VMS4B, W31, X61M, X65, X71M, Y33, Z22, Z33, 301, 302, 303, 304.

**VAZDA.**—AC6PEN, AC6PEN, AC.P, AC.Pen, ACP4, ACTH1, D1, DCP, DCSG, DD41, DD101, DD207, DD206, H210, HL21DD, HL23, HL23DD, HL41, HL41DD, HL42DD, HL133DD, HLDD133D, P41, Pen25, Pen45DD, Pen45DD, PenDD4020, QP25, QP220, SG215, SP41, SP42, 2P2220, TH2321, TP22, TP25, TP28, UUT, V914, VP23, VP41, VP133, VP132, UY5300.

**AMERICAN.**—OZ4, 1A4, 1A5, 1B4, 1D7, 1E5, 1E7, 1F4, 1F5, 1F6, 1F7, 1G6, 1H6, 1L6C, 1LN5, 1S5, 1T4, 1T5, 1-V, 2A6, 2A7, 2B6, 2B7, 2X2, 3A8, 3B7, 1291, 3Q6, 5U4, 5VA, 5Y3, 5Z3, 5Z4, 6A3, 6A4, 6A6, 6AB7, 6B3, 6AC7, 6B2, 6AE5, 6AE6, 6AG5, 6AG6, 6A67, 6AK5, 6B4, 6B7, 6B8, 6C4, 6C5, 6C6, 6C8, 6D5, 6D6, 6D8, 6E5, 6E6, 6E7, 6F6, 6F7, 6F8, 6G6, 6H6, 6J5, 6J7, 6J8, 6K6, 6K7, 6K8, 6L5, 6L6, 6L7, 6N7, 6V7, 6F6, 6R7, 6SA7, 6SC7, 6SF7, 6SG7, 6SH7, 6SL7, 6SK7, 6SL7, 6SK7, 6SR7, 6T7, 6V6, 6X5, 6Y5, 7A6, 7A7, 7B5, 7B6, 7B7, 7B8, 7C5, 7C6, 7C7, 7H7, 7S7, 7Q7, 7Y4, 10, 12A, 12A5, 12A6, 12B7, 12C8, 12S5, 12K7, 12K9, 12Q7, 12SG7, 12GS7, 12SK7, 12SQ7, 12SF5, 12S7, 12T5, 14A7, 14B5, 14G7, 15, 17, 2, 23, 25, 26, 27, 25Z4, 26, 27, 28D7, 29, 31, 32, 33, 34, 35A5, 36, 37, 38, 41, 42, 43, 46, 48, 49, 50, 53, 55, 59, 77, 79, 80, 81, 83, 84, 89, 807, 832, 866A, 854, 955, 956, 11Z26, 1299A, 1620, 7193, 9001, 9002, 9003, 9004, 9005, 9006, and 101 more types.

Order C.O.D. above listed numbers' or equivalents (subject to stock). Please enquire for any valve you require, even if not listed. We may have it. Old and new types are arriving daily.

**THIS MONTH'S SPECIALS:**  
Radio Servicing and Maintenance, 8/6. Trimmer Tool Kits (old price), 30-. Taylor Meters on easy terms. Electric Motor, to work off 31 to 8v. battery, 12/6. Radio Craft Library, 10 complete books (unrepeatable), 38/-. Batteries, ex-A.M. units, inert, 120v., 10 9. Morse Tappers, 1/11. Wall Telephones, complete installation, 2 instruments, etc., £3 15s. 0 5 mA. Luminous 1 1/4" x 3 1/4" Meters, 12/275, 14/47. Vidor Portable Elec. Cooker, with oven (no tax), £2 2s. 6d. Mouse-traps, electric, hygienic (no wattage), 12 6. Sunray Lamp "Collaro," complete with goggles, £5 18s. 10d. Waffle Machine, electric, tax free, £5 5s. Trouser Pressers, electric, 23 6. Pen Torch, chromium plated, complete, 12 9. Tie Pressers, electric, 27/- Mechanical Finers, American tool for difficult jobs, 9/- STOP PRESS. "Hermes" Personal Miniature Receiver, 4 valve superhet, portable in book form, £18 0s. 7d.

Write at once, please, to BULLS (PW)  
246, High Street, Harlesden, N.W.10  
Bulls wish you a Happy New Year

# Impressions on the Wax

## Review of the Latest Gramophone Records

IT has been perfectly obvious during Gigli's recent tour that the magnetism of his singing remains immensely strong; huge audiences have been drawn to his recitals and to Covent Garden. A giant in opera, Gigli is just at home in songs of the carol type, and in selecting the always appreciated "Adest Fideles" and the grand old Austrian hymn "Silent Night, Holy Night" for his latest recording on *H.M.V. D.41874*, he gives us a record which will be eagerly sought after by his admirers.

There are few interpreters of romantic music to beat Artur Schnabel. This explains why his help was enlisted for the production of the film, "Song of Love," a picture above the average of its kind, dealing with the life and melancholy death of Robert Schumann. Important figures in contemporary German music are represented; among them Brahms, whose life-long devotion to Robert and, after his death, to his widow Clara is a matter of history. The music of the two great composers is very different: Schumann frankly romantic, Brahms restrainedly lyrical over a stout classical basis. I have mentioned "Song of Love" because the latest recording by Schnabel and the melodies he plays in the film. They are "Traumerei" and "Liebeslied" recorded on *H.M.V. DB6532*.

### Record Token Service

A number of readers have written in asking for details of the Record Token Service run by His Master's Voice. The Service was introduced in 1939, but owing to the shortage of record supplies was temporarily suspended in 1942. During its short existence many thousands of pounds worth of tokens were sold. It had been readily accepted as an ideal form of making gifts, and the reasons for its favour with music-lovers are not far to seek. Gramophone records, even more than books (that other class of gifts closely associated with tokens), are fragile things, difficult of transport. Moreover, it is a chancy proceeding to give records unless the taste of the recipient is intimately known. The tokens enable you to get round these obstacles in record-giving. The receipt of a record token enables a man to call at his music shop and order precisely what he most wants up to the face value of the token. Details of the service, and specimens of the attractively decorated tokens, can be had from your nearest "His Master's Voice" dealer.

### A Novel Challenge

When Peter Dawson arrived in London in September, he remarked to reporters that the popularity of crooners among Australian "bobby-soxers" disgusted him. Very naturally, a howl of rage arose from the admirers of the American style, and Dawson has been challenged to a radio singing duel, he to sing two numbers and then two recordings in crooner style to be played. Listeners will judge. The duel will be on when the veteran ballad-singer returns to Australia after his English tour. During this recent tour Dawson has started to make records again, after an interval of some

years. The great recording artist—he has made over 3,000 immensely popular records for "His Master's Voice"—is incontestably in as fine voice as he ever was, and this new addition to his long and steady output will be heartily welcomed. "Fret-foot" is a song of his own composition; he composes under the pen-name of "J. P. McCall." whilst on the reverse side of *H.M.V. B9592* is "Walk Down the Road."

### "Peter Grimes"

Benjamin Britten's opera "Peter Grimes" is derived from the poem "The Borough," by George Crabbe. Crabbe was born at Aldeburgh, on the Suffolk coast, and his poem deals with the life of a small fishing and shipbuilding town. Britten is also an East Anglian (he was born at Lowestoft, within sound of the sea). "My life as a child," he relates "was coloured by the fierce storms that sometimes drove ships on to our coast and ate away whole stretches of the neighbouring cliffs. In writing 'Peter Grimes' I wanted to express my awareness of the perpetual struggle of men and women whose livelihood depends on the sea." The orchestral interludes are fully understood only when heard in their context, but at the same time their inclusion in concert programmes does give a taste of the magnificent score Britten prepared for this opera. He has identified himself completely with Crabbe's poem, and the sound of the windy sea is always behind the drama of the little fishing town. The orchestration is superb; there are effects so telling and yet so simple technically that Britten's work must be considered one of the most important operas ever to come from a British composer. The opera has been recorded on *Columbia DX1441-2* by the London Symphony Orchestra under the able baton of Sir Malcolm Sargent.

### Dance Music

All the latest up-to-the-minute tunes have been recorded in the recent releases, including "I wish I Didn't Love You" and "Peg o' My Heart," played by Geraldo and his Orchestra on *Parlophone F2255*; "An Apple Blossom Wedding" and "Sleepy San Benito," played by Jimmy Leach and his New Organolians on *Columbia, FB3358*, and "South America Take it Away" and "That's My Desire," played by Joe Loss and his Orchestra on *H.M.V. BD5990*.

Following their interpretation of Tchaikovsky's "Nutcracker Suite" (*BD1182-4*), Spike and the City Slickers are back again this month with two recordings in the comedy vein.

The "Puppy Love Song," sung by tail-waggers, Dr. Horatio Q. Birdbath, George Rock and Sir Frederick Gas, is a saga of a romantic interlude between a Pekinese and another dog, appropriately—if somewhat boisterously—interrupted by Spike's three vocal confederates.

"Pop Corn Sack" is a delicious satire on those filmgoers who insist on crunching popcorns, and paper, during a dramatic movie scene. The record is *H.M.V. BD1188*.

**SAMSONS SURPLUS STORES**

169-171, EDGWARE ROAD  
LONDON, W.2 Pad. 7851

**METERS.** Brand new and boxed by all famous makers: 0-500 ma. m.c. 2 1/2 in.; 0-300 ma. m.c. 2 1/2 in.; 0-150 ma. m.c. 2 in.; 0-100 ma. m.c. 2 1/2 in.; 0-50 ma. m.c. 2 1/2 in.; 0-20 amps. m.c. 2 1/2 in.; 150-300 volts m.c. 2 1/2 in. with external resistance; 0-4 amp. R.F. built in rectangular bakelite case. All one price, 17/8. post 6d.

**HOWARD BUTLER M.C. motor.** 6in. scale, calibrated 0-150 volts D.C. Built in bakelite carrying case 7in. x 7in. These meters have an accuracy test of 1%. Price 57/6. postage 8d.

**MASTER A.C. VOLTMETERS** 0-20 v. 5in. scale built in circular metal case. Price 27/6. postage 8d.

**EX-A.M. RADAR RECEIVERS TYPE 3170.** Complete with the following valves: 30 EF50, 1 VU134, 1 V370, 1 VR137. Smoothing chokes, resistors, condensers, etc. Wonderful component value. Supplied brand new in packing case as from makers. Price £4 10s., carriage 6/- No C.O.D.

**M.C.R.I. MINIATURE RECEIVERS** still available. To operate on battery or mains. Complete with power unit to work on from 107v. to 250v. A.C. or D.C. 2 H.T. batteries, earphones, aerial, earth, etc. Frequency range 20-3,000 metres. Brand new packed and sealed in makers' tins. Price £11 10s., carriage 2/6. No C.O.D.

**C.R. TUBE INDICATORS TYPE 182C.** Complete with 2 tubes types VCR 517 and VCR 39. Fine selection of components including valves, 3 VR65, 1 6J5G, 4 diodes; resistors, condensers, etc. Suitable for oscilloscope and television construction. Brand new. Dispatched in wooden packing case as from makers. Price £4 10s., carriage 5/- No C.O.D.

**2-BATTERY BATTERY AMPLIFIERS TYPE A1134.** L.T. 2v., H.T. 120v. Valves 6P210 and 6LMF. Brand new in neat metal cases. Price 25/-, postage 1/8. No C.O.D. under £2.

**GALPINS**

ELECTRICAL STORES  
408, HIGH STREET, LEWISHAM,  
LONDON, S.E.13

Tel.: Lee Green 0309. Near Lewisham Hospital.

**TERMS: CASH WITH ORDER.  
NO C.O.D.**

**EX-R.A.F. CALIBRATOR UNITS TYPE 18.** These units consist of 1-100 k/c. Xstl 2-EF 50 valves and numerous other components (new boxed), 35/- each, PIF.

**EX R.A.F. ROTARY CONVERTERS** (D.C. to A.C.) 12 volts D.C. Input 220 volts A.C. 50 cycle 1 phase at 100 watts output. Price 90/- each fully guaranteed.

**AUTO WOUND TRANSFORMERS** (Mains Boosters), tapped 0, 6, 10, 19, 175, 200, 220, 225, 240 and 250 volts at 1,500 watts (new ex-Govt.); 25/10/-, post 5/-.

**AUTO WOUND TRANSFORMERS** (Voltage Changer), tapped 0, 10, 20, 25, 90, 130, 150, 190, 210 and 230 volts at 1,000 watts. (It will be seen that almost any voltage can be obtained from this Transformer.) Price 25/10/-, post 5/-.

**METERS. ALL BY WELL-KNOWN MAKERS.** Ex-Govt., new boxed 1st Grade Moving Coil. 0 to 1 ma., 21/-; 0 to 40 volts, 15/-; 0 to 10 amps., 15/-; 0 to 5 ma., 17/6; 0 to 20 ma., 17/6; 0 to 50 ma., 20/-; all 2in. fsd. 0 to 3 ma., 22/6; 0 to 50 ma., 22/6; 0 to 200 ma., 22/6; 0 to 4 amp. Thermo Coupled, 30/-; 0 to 20 volts A.C. calibrated 50 cys., 25/-; 0 to 3,500 volts Electrostatic, 35/- All 2 1/2 in. fsd.

**L.T. RECTIFIERS** (new), 6 volts, 1 1/2 amp. 7/6 each; 12 v. 1 1/2 amp., 10/6 each, 9d. post. Instrument Rectifiers, 5.H., 10 or 20 ma. types, 4/6 each.

**MAINS CHOKES,** 9 hy., 100 ma., 61/6; 20 hy., 120 ma., 10/6 each; 30 hy., 150 ma., 22/6 each.

**MAINS TRANSFORMERS,** 230 volts, 50 cys. 1 ph. input. Output, 500/0/500 volts at 250 ma., 5 v. 3 a., 47/6 each. Another with two windings of 6 1/2 volts 5 amps., 30/- each; another with 3500/0/350 v., 180 ma., twice three 6.3 volt windings and two 5-volt windings, 42/6 each; another 50 volts at approx. 50 amps., also a 5-volt winding, 23/15/-, each C/F. All the above Transformers are very large type so please allow 3/6 for carriage.

**EX-NAVAL CATHODE RAY RECTIFIER UNITS.** New and unused, sold for components which consist of: 2 x 5 mf. 2,500 v., 1 x 1 mf. 5,000 v., 6 x 2 mf. 800 v., 2 x 8 mf. 800 v. 15 volume controls, various valves, approx. 100 small condensers and resistance, smoothing choke and 9 v. holders, including 3 EF50 and 1 tube base. All components wired and with the addition of mains transformer would make a good oscilloscope. Price 45/-, carriage paid.

**EX-GOVT. VARIOMETER** for No. 19 sets; these contain C.T. Westector, .001, 5,000 v., condenser, etc., price 7/6 each. Complete in metal case with graduated dial.

**SHUNT WOUND D.C.** 110 volt motors, 1,500 r.p.m. approx. 1/2 h.p., condition as new, 17/6 each, post 2/-.

**EX-GOVT. NEW MAINS TRANSFORMERS.** Input, 200/250 volts. Output, 525/0/525 v. 150 ma., 5 v. 3 a., 6.3 v. 5 a., 35/- each, post 2/6. Special price for lots of half dozen or more.

**T.C.C. CONDENSERS** (new), 4 mf. 1,000-volt working, 3/6 each. PIF Mains Smoothing Chokes (new), 10 hy. 150 ma./180 ohm., 8/6 each. Ditto 10 hy. 80 ma./200 ohm., 6/6 each.

**U.S.A. AIR FORCE RECEIVERS**

**BC 348R**

The finest offer yet made to the Radio Amateur. We have been fortunate enough to secure a quantity of the U.S. Army Air Forces Communications Receiver No. BC 348R. Unlike other ex-Servic Radio Receivers that have been offered, these are **BRAND NEW and UNUSED.**

Don't delay, order yours NOW.

Specification: 8 valve superhet with crystal filter. Sensitivity less than 1 microvolt; 6 bands, covering following ranges:—

500-200 Kc/s.	9.5- 6 mc/s.
3.5-1.5 mc/s.	13.5- 9.5 mc/s.
6 -3.5 mc/s.	18 -13.5 mc/s.

Complete with built-in 28 volt Dynamotor, which is easily removed for replacement if required by power pack operating from normal mains voltages. **BRAND NEW and UNUSED and COMPLETE WITH INSTRUCTION BOOK.**

ONLY £32/10 0 (carriage 10/-)  
C.W.O. Please. S.A.E. for lists.

**U.E.I. CORP.,  
THE RADIO CORNER,**

138, Gray's Inn Road, London, W.C.1  
(Terminus 7837)

We are 2 mins. from High Holborn,  
5 mins. from King's (Cross.)

**CALLING AMATEURS  
with BUCCLEUCH**

Precision Built Equipment  
STEEL CHASSIS SMOOTH  
BLACK 17" x 10 1/2" x 2 1/2" 8/9.  
17" x 10" x 2" 8/9.



PANELS-CRACKLE  
19" x 31" 4/-, 19" x  
17" 6/9, 19" x 8 1/2"  
7/9, 19" x 10 1/2" 8/9.



ANGLE BRACKETS 12 1/2" long, pr. 7/6.  
(Bright Aluminium, same cost.)  
COMPLETE RACK ASSEMBLY  
(Rigid 4-Column) 31" £2.5s.  
63" £3.5s.

CHASSIS, etc., To Order, 1d. sq. inch.

(Include slides when costing.)  
PUNCHING CHARGES to 4" 2d.  
VALVE HOLES 1", 1 1/2" or 1 3/4" 6d.  
METER HOLES, etc., 1/6.

SQUARE HOLES 2/-  
**BUCCLEUCH RADIO MANUFACTURERS**  
1 & 2 Melville Terrace, Edinburgh, 9

**BULGIN**

*A Name  
famous  
in Radio*



A. F. BULGIN & CO., LTD.  
Bye Pass Road, Barking, Essex  
Tel: RIPpleway 3474 (5 lines).

**L.R.S. IN STOCK!**

(Immediate dispatch)

**AVOMETERS**

Avominer D.C. ...	£ 4 4 0
Avominer A.C./D.C. ...	£ 8 10 0
Model 7 ...	£19 10 0
Oscillator, Mains ...	£13 0 0
Valve Tester, complete ...	£16 10 0

Postage 1/6 extra

(These meters are available on Easy Terms)

Forthy Richards Cydon Door Chimes  
Far more pleasant than the ordinary doorbell or buzzer.

Leaflet of any item on request.

**The LONDON RADIO SUPPLY Co.**  
BALCOMBE (Est. 1925) SUSSEX

**IRON DUST  
CORED COILS**

of Exceptional Efficiency and Stability  
**AERIAL AND OSCILLATOR**, short, medium, or long wave, size 1in. x 1in. 7/6 pair.  
**AERIAL AND OSCILLATOR**, medium or long wave, size 1in. x 1in. 8/9 pair.  
**DUAL WAVE COILS**, medium and long wave aerial and h.f. 9/8 pair.  
**I.F. TRANSFORMERS**, Standard Frequency 465 Kc/s. Size, 1in. diam. x 1 1/2 in. high. 9/6 each.

**MINIATURE ROTARY SWITCH**, 4 pole, 3 way, 3/9 each.

**CONDENSERS**, Silvered Mica, .0001 mfd., 4/- doz.

**AVOMETER**, Model 7, 19/10/-.

All coils fitted with adjustable iron cores, and supplied with circuit diagram.

**TERMS:** Cash with order or C.O.D. on orders over £1.

**MONOCHORD RADIO**  
(Established 1929)  
17, Streatham Hill, London, S.W.2  
Phone: Tulse Hill 1051/2

# Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## All-wave Three

SIR,—Having just returned from overseas I had, as you can guess, quite a pile of PRACTICAL WIRELESSES to sort through, and being very keen on S.W. listening I decided on building the All-wave Three of December, 1944, and on behalf of your magazine would like to thank the designer for marvellous results obtained. Herewith a few results:

20 metres, 'phone: HK3BF, HK3BJ, FA8BG, HKIDZ, XACP, FF8FP.

40 metres, 'phone: ZS6DN, W7GRL, VP4TS, CM2LT.

I am using Cossor VSG220 for H.F., Marconi LP2 triode detector and Marconi KT2 pentode output, with Premier 4-pin coils. May I also take this opportunity of thanking you for a splendid mag. Keep up the good work!—A. BLAIR (Farnham).

## Ex-R.A.F. Equipment

SIR,—I have seen many letters expressing gratitude for the fine bargains obtained in ex-Government radio and radar equipment, but, although these may seem to be bargains to the average man in the street, I wonder what many satisfied buyers would say if they knew the huge profits made by the trade on this stuff. Here are some examples:

Cost to Trade	Sold to public	Profit
Valves, all sorts, 2s. . . . .	6s.	100 per cent.
V.H.F. receivers, with rotary converter, complete with valves and ready for use, 12s. 6d. . . . .	£5 12s. 0d.	300 per cent.
C.R. tubes, complete with all valves and power unit, £1 5s. . . . .	£1 15s.	100 per cent.
R1116 receivers, £3 10s. . . . .	£12	400 per cent.
L. M. and S. wave 8-valve C.M. receiver, with power pack, £5: Receiver . . . . .	£11	
Separate power pack . . . . .	£3 10s.	300 per cent.

These are just a few items and I know of people who bought this stuff and I have seen it being sold at the prices as stated. If one considers that a trader usually gets a profit of 33½ per cent., I call this real black-marketing, and I would suggest that the public gets a chance to buy direct, instead of allowing traders only to attend the sales.—K. A. ROOSENBERG (Liverpool).

SIR,—Regarding Mr. J. A. Brockie's letter in the January issue, the power plug on the front of the receiver of the set, No. 18, Mark III, to which he is referring, couples the receiver to the transmitter, and the connections to this plug are: Pin No. 1, aerial; pin No. 2, G.B.—; Pin No. 3, L.T.+; Pin No. 4, H.T.+; pin No. 5 (centre pin) (L.T.—, H.T.—).

Please note that this set is not operated on 120 volts H.T., but from a 162-volt battery, tapped at 12 volts for grid bias.

The L.T. supply also is normally contained in this battery, but a 2-volt accumulator is quite adequate for this purpose.

I have a limited number of circuit diagrams, lists of component values and other information regarding this receiver, which I shall be pleased to pass on to any enthusiast.—B. E. HARRIS (12, Hillside Road, Harpenden, Herts).

## Receiver R1147A

SIR,—Could any reader come to my rescue? I have recently purchased an ex-R.A.F. receiver, type 1147A, but have been able to obtain no information whatever concerning it. The R.A.F. are unable to supply me with their handbook relating to the receiver and thus I am at a complete loss regarding the information necessary to put it into operation. If any reader has the relevant Air Ministry (or other) publication relating to the set, or its associated control unit, which he is prepared to sell, or to lend me for a few days, I should be extremely grateful to him.

May I take this opportunity of congratulating PRACTICAL WIRELESS upon the fine job it is doing in spite of the paper shortage.—W. F. JACOBS ("Trehaven," Stapler's Road, Newport, I.W.).

## Information Wanted

SIR,—I have an ex-R.A.F. 4-valve short-wave (communications type) receiving set. It is a Model 3 Mark II. I believe it was used in the "resistance movement."

Could any reader please give me any information regarding it? What sort of aerial should I use? It is used for L.R. 'phones; can I use a speaker with it? Are any alterations necessary for speaker use?

It is very good indeed on an ordinary horizontal aerial. I get Radio Australia, Canada and many U.S.A. stations on it. I also receive Manila (Voice of Philippines) and dozens and dozens of others. I would welcome any letters about it from readers who have one. Specification, I think, is 4-valve communications receiver, covering 3-16 Mc/s. in 3 bands, using 2 7R7 and 2 7Q7 local valves, mains 9-100 at 8-10 mA., 6.3 v. L.T., 4½ v. G.B. At least, that's what someone told me.—PETER P. B. SKIVINGTON (16, Banood Road, Enfield, Middlesex).

SIR,—I have a German radio which I cannot get working. It is a Telefunken 612 GW. This is an A.C. and D.C. set, with the usual valve heaters wired in series with barrotter. It also has a transformer inside; this I take it is for A.C. operation. The trouble started when the correct barrotter got broken.

EU VI 220/240 v. }  
EU VII 110/130 v. }

This I take it is for working on 220-240 v. A.C. The correct barrotter for D.C. working is EU VII 110/130 v.; both of these are marked on the back of the set.

The barrotter which was supplied in place of the broken one is a Valvo C10 IP20 Wehrmacht.

When this was placed in the set the filament of the rectifier valve burnt out, which to me proves that it must have been an incorrect replacement. However, if anyone can help me with the valve data, I might be able to fix it up.

Valves for set as per diagram on set:  
 EU VI 220/240 v. (A.C. barretter) }  
 EU VII 110/130 v. (D.C. barretter) }  
 Telefunken AZI, 4 volt {  
     Bie Gleichstrom.  
     Widerstand.  
     Bie Wechselstrom.  
     AZI.  
 Telefunken Valvo CL4  
 Telefunken CF7  
 Replacement barretter, Valvo C10, 1P20.  
 The set is to be used on A.C. 230-250 v.—F. L. MEDHURST (88, Marsglas Crescent, Newport, Mon).

SIR.—Can any reader please give me the answer to my valve puzzle? I have no particulars as to types or wiring of base; a friend tells me that they are American base valves, but they will fit an English base (octal) if the centre is filed out.

Valve one is marked ZA7023, ARP12; has six pins and a top cap and lights up with 2 volts applied (metallised). Valve two: only marks are on electrode support, viz., T 350 PR1; has 8 pins and top cap; has two plates inside which are connected to the top cap and lights up with 2 volts applied. On both valves the locating spigot measures 11/32in. I would be very grateful for details of the types of these valves and the valveholder connections.—H. A. STAINSBY (27, Dipton Avenue, Newcastle-on-Tyne 4).

SIR.—Could any reader supply me with information about an Austrian valve, S.D.2?—R. E. TURNER (179, Branstone Road, Burton-on-Trent, Staffs).

#### Ex-Service Cathode-ray Tubes

SIR.—Thanks for publishing my letter in the December issue, and thanks very much to S./Sgt. L. J. Avery for the information he gives, and also to H. G. Weatherhead for calling my attention to the article in the April issue. But the ACR 10 lights with a green, not a blue, glow. The General Electric Co., Osram Valve Dept., Kingsway, inform me that the ACR 10 is not exactly the same as their 2½in. tube, but the contacts are the same. They also informed me that the Army 6in. tube, VCR97, is the equivalent of their E4504-B-16 6in. tube.

Readers who have purchased ex-service indicator cathode ray units are well advised to examine the set-up presented by the Admiralty to the Science Museum, South Kensington (first floor), and they might perhaps recognise some pieces of equipment that they have bought, all assembled and explained, and also visit the Electronic Exhibition on the ground floor.

One of the Admiralty sets includes a VCR97 indicator unit with time base. This set in turn is only one piece of a set of equipment so complex, and with so many units in it, that anyone can see at once that it is out of the question thinking of using any one of the units for their original purpose, either the receiver unit—which also includes the indicator unit power pack—or any other. But each

one must be dismantled and rebuilt to a less cumbersome and involved design. In other words, ex-service equipment for the main part is only useful for the valves and parts one can get out of them.—Wm. J. LAW (Ealing).

#### Speaker Networks

SIR.—Thanks are due to yourself and to Mr. Kemsey-Bourne for further information of speaker filter networks in January issue.

Could I add a little further useful information? I see no objection to making the chokes iron cored, thus reducing the number of turns needed and also the resistance of the choke winding.

I use a mains transformer core of about 2in. square and 50 to 80 turns tapped every 5 turns for fine balancing.

Mr. Bourne's method of matching unlike units should interest many readers—as I myself have had many letters asking a similar query.—S. I. HOLT (St. Annes).

#### Assistance Required

SIR.—I wonder if any of your readers can assist me to identify the loads of the Canadian "58" "walkie-talkie," as I have only the instrument but no accessories. I have succeeded only in finding those of Rx section up to now.

Also, particulars required of the ex-army TX/RX No. "19" and where circuit diagram may be obtained!—THOMAS WILLS (43, Tideswell Road, Firth Park, Sheffield, 5).

#### Cathode Follower Amplifier

SIR.—Some time ago my attention was drawn to a new type of amplifier in which the output (loudspeaker) was taken from the cathode circuit of the push-pull valves. As it was claimed that this gave quality superior to any form of amplifier then in use, I decided to try it out, with equipment which I had by me. I connected everything up and was greeted by the most appalling distortion, which soon ceased when the mains transformer broke down. I spoke to one or two friends about this, and then was told that a special mains transformer is required. I have not seen any circuits on this scheme, and wondered if any readers had experimented with such a circuit and what results have been obtained. It seems to me that if it is possible to obtain by this means quality superior to any other arrangement, then surely it should be popularised.—J. PORTER (Colindale).

#### Remote Control System

SIR.—Many thanks for the idea in your September issue on distant control. I built up this, with a little modification to suit a special type of ex-government switch in my box, and it really works fine. I appreciate radio programmes much more now, as it is not necessary to run from room to room to switch on and off. It is these little ideas and gadgets which make radio so interesting. Thank you again.—W. A. CONQUEST (Harrow).

#### NEWNES SHORT-WAVE MANUAL

6/-, or 6/6 by post from

GEORGE NEWNES, LTD. :: Tower House, Southampton St., London, W.C.2

**CLASSIFIED ADVERTISEMENTS**

**RATES:** 3- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

**RADIO SOCIETY OF GREAT BRITAIN** offers the following publications of interest to all transmitting amateurs and short-wave experimenters—

**R.S.G.B. BULLETIN**, the Society's journal, 16 monthly.

**THE TRANSMITTING LICENCE** (32 pages), for the newcomer to Amateur Radio, 1/-

**SERVICE VALVE EQUIVALENTS** (28 pages), gives Commercial Equivalents of numerous Service valves, including CV types, 1/-

All prices include postage and packing. Watch for further publications in the R.S.G.B. "Amateur Radio" series.

28-30, Little Russell Street, London, W.C.1.

**THESE YOU CAN HEAR**—36pp. art paper, lavishly illustrated, containing descriptions and schedules of popular S.W. Stations, plus useful data; 2/- from local booksellers, or direct from Short Wave News, 57, Maida Vale, London, W.9.

**RECEIVERS & COMPONENTS**

**KITS** of Radio Receivers from £7.80, 4 and 5 valve. All new materials, Table Models, Semi-Midget. Our latest Kit—Wylwyn Star 1948—has connections for Gramophone Pick-up and extensions to Loudspeakers. 17/6. Hours average time for constructing. Full details and diagrams with each kit. C.W.O. or C.O.D.—Isherwoods, Reme House, 81, Plungington Road, Preston, Lancs. Tel.: 3348. Estd. 1936.

**OSMOR A.C./D.C.** 3-wave 5v. superhet receivers, excellent reproduction and sensitivity adjustable cabinet, early delivery, shipping wave-band if required. Write for literature. Trade inquiries invited.—Morgan, Osborne and Co., Ltd., Southview Road, Warringham, Surrey.

**NATIONAL RADIO SUPPLIES**

Bournemouth's new style radio components shop. Everything for the constructor, amateur and experimenter. New components and ex-Govt. lines always in stock with something new each week. A large selection of chassis, cabinets and components to choose from. Denon & Raymex stockists. Send for 10-page catalogue, 21d. post free from National Radio Supplies, 63, Holdenhurst Road, Bournemouth 5232.

**OSCILATOR KITS**, 4 wave bands, modulated, BTX model, 75/-, A.C./D.C. model, 98/6 complete, including metal chassis, panel, components, valves, all new.

Coils and Switches Ready Wired. "cr" unit, wiring diagram. Details of both models 2/-.—Lee, 49, Booth Farm Road, Birmingham, 22.

**R155 WESTERN ELECTRIC RECEIVERS**, 34-38 mcs, 12 valve midget using 6AK5, 9001, 12A6 and EB3C3 valves. Brand new and complete with valves and remote control stand and connecting leads, 65 ea. carriage paid. Receivers only, complete less valves, 50/- ea., or partly stripped chassis containing 4-g. tuning, unit 7, and complete wiring to 4 RF stages, 10 button 4 VHS and screens, etc., 17/6. P.A. type speaker units, P.M. 3 ohms; for horn speakers, approx. 20 watts. Brand new, 25/- ea. CR tubes, brand new, 6in. elec. VC97, 45. 5in. mag. 5P7, 45/- F and D coils to suit, 15/- 3in. elec. 3P7, 30/- Bank of 12 MV dust tuned coils, 18/- Bulgin panel lights, red or amber, 1/9. Other types, green, blue or clear, 1/3. 12 assorted vols and vcs, long and short shafts, 500 to 1 mek., brand new, 11/6. 12 assorted output transformers, standard and 100 ohm, 10/- H and L ratio, intervalve, etc., all brand new and fitted tags and panels, including 3 midget types and 9 standard or larger, worth 46, our price 24/- lot. 6 assorted LF chokes up to 120 mA., 12/- 6 assorted HF and UHF chokes, 3/- Assorted Res. and cons., brand new onpax panels, mica, silver mica and tubular and 1 to 5 resistors, 72 for 12/- Coloured knobs, 2/- doz. Inter-communication telephone sets, 19/6 ea. S.A.E. for lists of numerous other bargains. H. English, The Maltings, Rayleigh Rd., Hutton, Essex.

**PRATTS RADIO**

1070 Harrow Road, London, N.W.10 (Nr. Scrubs Lane) Phone: LADbroke 1734

**AMPLIFIERS**. College 10 watt A.C. 4-valve, mike stage, twin inputs and faders; output matches 4, 8, 15 ohm speakers, £8 18/6. A.C./D.C. 10 watt 6-valve P.P. output, with case, £12 12/0.

**ACE 550 Receiver**. We can supply this popular set as a chassis and speaker for use in existing radiograms, etc. 3-waveband A.C. pamphlet available, 5/- valve, price £18 5/9 inc. tax.

**TRANSFORMERS**. Mains 350-0-350, 4v., 4v. or 6v., 5v., 26 6; shrouded, 28 6; 150 mA. 35/- Output Transformers, midget universal, 5 6; Pentode, 5/9; 5 watt multi-ratio, 7 6; 30 watt, 28 6; intervalve midget, 3-1, 6 3; 5-1, 6 6; class B Driver, 7 6.

**LINE OUTPUT**, 3 amp. (60 ohms ft.); 2-way, 2 1/2 ft.; 3-way, 8d. ft. Voltage Droppers, 3 amp., 800 ohm or 2 amp., 1,000 ohm, 5 6 ea.

**COILS, ETC.** 3 Wave Superhet Coil Units, 25/-; Wearite, similar, 42/-; L. and M.W. coils with reaction, 7/9 pair; Superhet coils, 3-waveband, A. and Osc., 8/6 pair; dual range coil with reaction, 4/11; Wearite P coil, 3/- ea.; 465 kc/s 1 1/2 p.f. 2 p.f.; Weymouth midget, 18/9; Wearite standard, £1; ultra midget, 21/- pair.

**CIRCUIT DIAGRAMS**. A1 4-valve, A.C./D.C. 2-wave T.R.F. set; A2 8 watt P.P. A.C. Amplifier, with mike stage; B1, 3 valve, 2 wave T.R.F. Set battery, 20/9.

**CONDENSERS**, 8 mfd., 4-; 4 mfd., 3 6; 16 mfd., 4 6 (450v.); 25 mfd., 25/-; 2 3 50 mfd., 50/-; 3/6. Paper 50 p.f. to 1 mfd., 9d. each; 5 mfd., 500v., 1/10.

**SPEAKERS**, P.M. L/Trans., 2in., 26 6; 3in., 29 6; 5in., 16/6; 6in., 21 6; 8in., 21; 16in., 32/-; 5in., with transformer, 20/9.

**PRESSETS**, 30 p.f., 7d.; 50 p.f., 10d.; 100 p.f., 1 3; 00025, 2; 0005, 2 3. Dielectric variable condensers, .0003 and .0005, 3 9; standard, 2 gang, .0005 V.Con., L.Tr., 12/-; W.Tr., 12/9.

**VALVES**, 25A6G, U31, 25Y5G, DAF91, 6F7, etc., etc., 21d. stamp for List. Orders over £1 post free. C.O.D. or C.W.O. Open 10-6. Buses 662, 664, or 18b pass door. New unused goods. Immediate despatch.

**CHARLES BRITAIN (RADIO) LTD.**

46, LISLE STREET, LONDON, W.C.2. GERard 6653.

**VIBRATOR PACK**, Size 7 1/2 x 3in. x 2 1/2in. Black crackle case valves only. Employs a "Stratosil" vibrator and gives 250v. at 80 m a. The output is not rectified, but the outfit contains all the necessary filters, etc. Price, 27/6, plus 1/6 carriage and packing.

**COMPONENTS**. We offer the following selection from our large and comprehensive stock:

**LOUDSPEAKERS**, Rola 10in. P.M., less trans., £1. Rola 8in. P.M., less trans., £1. Para 5in., P.M. less trans., 14 6. Goodman's 12in. Hi-Fi twin cone (Axion Twelve), £7 10s. od., plus 5/- carriage and packing. Goodman's 12in. 15-ohm speech coil, 45 17s. 6d., plus 5/- carriage and packing.

**SMOOTHING CONDENSERS**, and Phillips 8in. and Wet can, 450v. wkg., 4/-; T.M.C., 8-24, 250v. wkg., 7/6; 16-24 mid., 350v. wkg., 7 6; 20-20 mid., 450v. wkg., 7 6; 32-32 mid., 250v. wkg., 7/6; 16-16 mid., 450v. wkg., 7/6; 50 mid., 12v., 1 6. All the above are Can type.

**SPECIAL OFFERS**, 35 Assorted Tubular Condensers; .001 mid. to 1. 10 6; 72 Assorted Resistors, 1 and 1 watt, all new, 100 ohms to 6 meg., 12 6; 72 Assorted Metal-cased Condensers containing .01 1 .15 and including 2 .01 2,500v. wkg., all new, 27 6; 35 Mica Condensers, .001 to .01 all new, 12 6; 12 volume-controls, less switch, 5,000 ohms to 3 meg., 17 6; 24 Valveholders (Loctal, Octal), 5- and 7-pin, etc., all new, 10/-.

Send for List "P.W." of other bargains available.

**Charles Britain (Radio), Ltd., Radio House, 2, Wilson Street, London, E.C.2. Tel.: Bis. 2868.**

**MORTONS**. Now have full range of the famous test-ear resistors. Type A, 1 1/2in. x 2 1/2in., in three ratings, 1,000 1/2a., 600 1/2a., 4 9 ohm, 1,500 1/2a. 5/- Type B, 1 1/2in. x 3 1/2in., in four ratings, 1,000 1/2a., 600 1/2a., 750 1/2a., 5/- each, 1,500 1/2a. 5 3. 5 watt wirewound, RMA colour coded, 34 ratings, 50 1/2 to 2,500 1/2, 1 6 each, 10 watt, 2 1/2 each, 5 watt wirewound adjustable, 2 1/2in. x 1 1/2in., or slider 50 10 15 20 25 30 1 9 each. All above items space wound, with nickel chrome wire.

Crystal detectors semi-permanent, 2 6 each (+3d. post). Crystal and catwhisker, 8d. each (+2 1/2d. post). Moulded bakelite cabinets, with T.R.F. or S.H. chassis. Ideal for many of the "Practical Wireless" sets. Get yourself a blueprint and build a grand total set, complete. Diagrams and grid condenser. Spindly 5in. loudspeaker. Mo. tot. s. 13. Camden Road, Walthamstow, London, E.17 (Trade Supplied)

**MAT RADIO SERVICE**  
Kingston 8353.

29, Castle Street, Kingston-on-Thames, Surrey

**DUAL TESTOSCOPES**



This new dual model indicates 2 to 30 volts and 100 to 750 volts.

Send for leaflet (A. 24) on "Testing"

**RUNBAKEN-MANCHESTER**

**SOUTHERN RADIOS' WIRELESS**

Latest Radio Publications:

**RADIO VALVE MANUAL**, British and American equivalents, 3/6. Post 3d. All publications previously advertised still available. COMPLETE LIST OF PUBLICATIONS 9d.

**REAR-THROAT MIKES**, Brand new, with 3ft. lead and jack plug, 4 6 each, post 6d. **LUFIRA ADJUSTABLE HOLE CUTTERS**, For use on wood, metal or plastic, 5/-, post 6d.

**RELAYNS**, Brand new. Post Office Type, 30 ohm, 400 ohm plus 200 ohm, 150 ohm and 500 ohm, 2 9 each, post 6d.

**TANNOY CARBON MICROPHONE INSERTS**, 2 6 each, post 6d.

**A.C. MOTORS**, Input 230/250 volts A.C. Revs. 2,000 r.p.m., constant speed, Power 1 h.p. consumption, under 4 amp. Weight, 20lbs. approx. £2 15s. each, carriage 5/-.

**MIDGET TWIN GANGED CONDENSERS**, 2in. x 1 1/2in., 5/- each, postage 6d.

**MIDGET SINGLE GANG CONDENSERS**, 1 1/2in. x 1in., 2 6 each, postage 6d.

**R.A.E. MORSE KEYS**, 2/6 each, post 4d. **INSTRUCTORS' PATTERN MORSE KEYS**, with bakelite case, 7/6 each, post 6d.

**POWER PACKS, M.C.R.I. PATTERNS**, Input 30 250 A.C. or D.C. Output 90 volts and 71 volts i.t. D.C. £2 each, post 1/-.

**CONDENSERS**, 1 plus 1 plus 1, 2 6 each. **EX-ARMY HEADSETS**, Carbon mikes and cushioned moving coil earphones, guaranteed perfect, 12 6, post free.

**EX-GOV'T. INFANT SPEAKERS**, Ratio 1:49.9 mu metal core, 4 6, post 1/-; Ratio 1:7 mu metal core, 4/6, post 1/-; **NYSTOFLIX**, Assorted sizes and colours, 2/6 per dozen lengths.

**FORMABAD**, 3 in.m. cotton-covered plastic sleeving, 8 6 per 144 yards (minimum quantity).

**SOUTHERN RADIO SUPPLY, LTD.**, 46, LISLE STREET, LONDON, W.C.2. GERard 6653.

**CHARLES BRITAIN (RADIO) LTD.**  
**VIBRATOR PACK**, Size 7 1/2 x 3in. x 2 1/2in. Black crackle case valves only. Employs a "Stratosil" vibrator and gives 250v. at 80 m a. The output is not rectified, but the outfit contains all the necessary filters, etc. Price, 27/6, plus 1/6 carriage and packing.

**COMPONENTS**. We offer the following selection from our large and comprehensive stock:

**LOUDSPEAKERS**, Rola 10in. P.M., less trans., £1. Rola 8in. P.M., less trans., £1. Para 5in., P.M. less trans., 14 6. Goodman's 12in. Hi-Fi twin cone (Axion Twelve), £7 10s. od., plus 5/- carriage and packing. Goodman's 12in. 15-ohm speech coil, 45 17s. 6d., plus 5/- carriage and packing.

**SMOOTHING CONDENSERS**, and Phillips 8in. and Wet can, 450v. wkg., 4/-; T.M.C., 8-24, 250v. wkg., 7/6; 16-24 mid., 350v. wkg., 7 6; 20-20 mid., 450v. wkg., 7 6; 32-32 mid., 250v. wkg., 7/6; 16-16 mid., 450v. wkg., 7/6; 50 mid., 12v., 1 6. All the above are Can type.

**SPECIAL OFFERS**, 35 Assorted Tubular Condensers; .001 mid. to 1. 10 6; 72 Assorted Resistors, 1 and 1 watt, all new, 100 ohms to 6 meg., 12 6; 72 Assorted Metal-cased Condensers containing .01 1 .15 and including 2 .01 2,500v. wkg., all new, 27 6; 35 Mica Condensers, .001 to .01 all new, 12 6; 12 volume-controls, less switch, 5,000 ohms to 3 meg., 17 6; 24 Valveholders (Loctal, Octal), 5- and 7-pin, etc., all new, 10/-.

Send for List "P.W." of other bargains available.

**Charles Britain (Radio), Ltd., Radio House, 2, Wilson Street, London, E.C.2. Tel.: Bis. 2868.**

**MORTONS**. Now have full range of the famous test-ear resistors. Type A, 1 1/2in. x 2 1/2in., in three ratings, 1,000 1/2a., 600 1/2a., 4 9 ohm, 1,500 1/2a. 5/- Type B, 1 1/2in. x 3 1/2in., in four ratings, 1,000 1/2a., 600 1/2a., 750 1/2a., 5/- each, 1,500 1/2a. 5 3. 5 watt wirewound, RMA colour coded, 34 ratings, 50 1/2 to 2,500 1/2, 1 6 each, 10 watt, 2 1/2 each, 5 watt wirewound adjustable, 2 1/2in. x 1 1/2in., or slider 50 10 15 20 25 30 1 9 each. All above items space wound, with nickel chrome wire.

Crystal detectors semi-permanent, 2 6 each (+3d. post). Crystal and catwhisker, 8d. each (+2 1/2d. post). Moulded bakelite cabinets, with T.R.F. or S.H. chassis. Ideal for many of the "Practical Wireless" sets. Get yourself a blueprint and build a grand total set, complete. Diagrams and grid condenser. Spindly 5in. loudspeaker. Mo. tot. s. 13. Camden Road, Walthamstow, London, E.17 (Trade Supplied)

**SANGAMO SYNCHRONOUS MOTORS.** Self-starting, 200-250 V. A. 50 c.p.s. consumption 21 watt, size 2 1/2 in. x 2 in., geared 1 in. 60 mins., can be reset to zero by friction drive from front or back shaft. 1 in. x 1/10 in. to run clockwise, ideal movements for making electric clocks, time switches, etc. Nickel-plated finish, price 22/6 each; 1 1/2 to 1 dial trains to fit above spindle; 2/6 per set extra.

F/3.5 lenses, 2 inch focus, by well-known makers, ex-Govt. stock, as new, fitted in oxidised mount, flange, etc. ideal for 35 mm. enlargers, cameras, etc.; price, 27/6 each, postage 6d.

**TO CALLERS ONLY.** A.C. main-driven oscillators, type 37, 22 to 70 m.c.s., complete with 6 valves, 807 valve in output stage and milliammeter in output circuit; receiving units, type 89; C.R. power units, type 526; performance meters, type 53874; A.C. mains wavemeters, type W1252; battery wavemeters, type W1056; receivers, type 1147; A.C. mains power packs for 1487; receivers 310; radio L.O. sets, 210; signal transformers; receivers, type 76A; battery driven amplifiers, large assortments of volt. amp. and milliammeters, neutralising units with R.F. meters, metal rectifiers, relays, vibrator coils, inter-com sets, signal generators D.C. and A.C. converters; Brown's A type headphones; E.M.I. cathode-ray tubes; 6-valve receivers incorporating Clouston unit; A.C. power units suitable for 1155 receiver; a quantity of Lorenz transmitting gear, etc.

**H. FRANKS, 58, New Oxford St., W.C.1.**  
Tel.: MUS. 9594.

**LOUD SPEAKER Repairs.** New cones fitted, transformers, clock coils, chokes and mics., rewound. Prices quoted. E. Mason, 5, Balham Grove, S.W.12, Balham 6063.

**REPAIRS TO loud-speakers.** Cones, coils fitted, fields altered, rewind, output transformers, clock coils. No mains trans. accepted. Prices quoted. Satisfaction guaranteed.—L. S. Repair Service, 49, Trinity Rd., West, Rooking, S.W.17, Closed Saturdays. Phone: 1848 2559.

**KIT SETS WIRED.**—Apparatus constructed to your design. Any receiver serviced. Send diagram or set for quotation, to F. A. Sharp & Sons, 53, Weedington Road, Kentish Town, N.W.5. Phone: GUL 1759.

**RADIOGRAPHIC LTD.**—3-Piece Valve Screens, 1/6; T154 Oscillator Panels, new, 19/6; Rack-mounted Mains Power Units, £3 19/6; Amplifier Mixer Units, £2 19/6; Ex. V. Ind. Valve, 1/6; 100k.c. Crystals, two types, 15/6 and 19/6; Igranite Jack Sockets, 1/6 each. S.A.E. for Latest List, Transmitting and Special Purpose Valves from Stock.—Radio-graphic, Ltd., Mail Order Specialists, 66, Osborne Street, Glasgow, C.1. Tel.: Bell 3776.

**FRED'S RADIO CABIN.**—463 kc/s Iron Core I.P. Coils, 12/6 pr.; Osmer High Q All-wave Coil Pack. Plastic iron core coils with switch and trimmers. With circuit, 33-; 5 Watt, 50 to 2,500 ohms. wire wound, 1/6 each; Multi-core solder, 6d. packet. Weymouth MW/LW with reaction, T.F. coils, 9/6 pr. Coll formers, Paxolin, 1in. x 4in., 7/8in. x 4in., 4d. 2in. x 2d. Flexible insulated couplers, 1,000 volts, 4in. dia., 1/6. 1in. brass couplers, 9d. 2 and 3 amp. droppers, Low heat type, 4/9. Bakelite .005 mfd. tuning conds., 4/6 each. 5-valve chassis, 10 x 5 x 3in., 4/6. Aerial and earth strips, 3d. Sator 25K midget pots, 6d. each. 3-waveband superhet. coils, 10/6 pr. S.H. Speaker Transformer, 2/6. Code only 4/6. KB taper tone controls, 2/6. 4-in. chassis mount valveholders, 3d. each. 2/6 doz. Many other bargains for callers. South London's Leading Radio Depot, Fred's Radio Cabin, 77, Newington Butts, Elephant and Castle, London, S.E.1. Note new address. Phone: Rodney 2180.

**L.P. DISMORE** (formerly Morton and Dismore) for Test Equipment. This month's special offers: Avo Valve Tester, latest type, complete with selector panel, absolutely new condition, used once. My price, £14/0/0. Mullard C.R. Tube Unit complete with power unit, Focus and Brilliance Controls, and 2 1/2n. Tube. For use with external Time Base, £9/0/0. Cassor 3339 D.B. Scope, completely overhauled and in perfect condition. Price, £30/0/0. Write and let us know your testgear requirements. We buy, sell and exchange Test Equipment of all types. We can overhaul and recalibrate all testgear.—L.P. Dismore, 52c, Oldchurch Road, Chingford, E.4.

**SPARKS' DATA SHEETS** are prepared and published by L. Ormond Sparks, a name synonymous since 1923 with **TRUSTWORTHY DESIGNS.** Every design is built, tested and guaranteed, and components are available.

**COMPLETE DETAILS.** Every Sparks' Data Sheet has a full-size wiring diagram, Drilling, Assembly and Wiring Plans, plus detailed descriptive matter.

**THE CHALLENGER PORTABLE.** This is my latest design. It is an exceptional A.C./D.C. Portable (3 valve T.R.F. plus rectifier) covering M.L. waves, 2.6 to 11. Drilling, Assembly and Wiring Plans, plus detailed descriptive matter.

**MIDGET PORTABLES.** All-dry batteries. Four-valve T.R.F. med. waves only, 5in. speaker. No. LO/16, 2/6. Three-valve M.L. waves. The famous little LO/S, 2/6. Two-valve med. wave only, for local station. No. LO/14, 2/6. One-valve M.L. waves for 'phones. No. MP/1, 2/6. All the above are self-contained.

**SETS (Batt.).** Two-valve M/L waves. No. LO/12, 2/6. Three-valve "Straight" med. wave only, No. 2VA, 2/6. Three-valve T.R.F. M.L. waves. No. LO/4, 2/6. Four-valve ditto, with P/P output. No. LO/8, 2/6.

**MAIN SETS.** A.C. Two-valve M/L waves. No. LO/5A, 2/6. Three-valve T.R.F. (A.C.). No. LO/9, 2/6. Three-valve ditto for A.C./S.A.E. No. 114, 2/6. All-ways superhet, A.C. 3/6, plus rect. No. LO/11, 2/6.

**AMPLIFIERS.** A.C. 3/6 watt. No. ACA/10, 2/6. A.C. 8 watt, P/P output. No. LOQA.8, 2/6. A.C./D.C. ditto. No. LOQA.4, 3/6. Two-valve bat. No. 2VA, 2/6. Three-valve ditto P/P output. No. 2VA.11, 2/6. **MANY other Tested Designs Available.** Stamp for Full List and with Order.

**L. ORMOND SPARKS (P.)**  
9, Phoenix Road, Brockley, S.E.4.  
Phone: LEON 0393.

**FIRTH RADIOGRAPH LTD.** The Leicester Specialists, offer from their comprehensive stocks:—20, 40 and 80 m. Eddystone 4-pin Coils, 5/- set of 3. **TUNING CONDENSERS,** standard 3-gang, .0005 ceramic insulation, 4in. spindle with both ends, or clockwork, or anti-clockwise operation, 7/6; Standard single ended 3-gang, .000160, 7.6; **3-WAVE BAND S.M. drive** with glass and 7in. x 4in. escutcheon, 12/6; **EPIC/CLIC** drives 5, 1, 1/6.

84/2 m. A., 11 vds. 2/6; 144 vds., 10-; **METERS,** 3in. **FLUSH TYPE** 0-20 v. A.C., 10-0-10 m.A. D.C., 1-0-1 m.A. D.C., 0-12 A. R.F. thermo. D.C., all at 12/6; 0-12 A. D.C., 0-20A. D.C., 0-5-20 milliro. D.C., all at 15/-; 500 microamp Ferranti, 25/-; 2in. Square flush, 0-1 m.A., 25/-; Everitt Edgrecum 0-5000 v. M Coil, 3/4n. 25/-; **MAINS TRANSFORMERS,** 250-0-250 v. 80 mA., 6/-; 2 A., 5/-; 2 A., 19/6. **STANCO** soldering iron 200 or 110 v. list 21/-; plate, 12 G. G.E.C. 5/750 v. block condensers, 6/- doz. Owing to the impossibility of listing many separate items, we offer a special Bargain Parcel of Ex-Govt. components having a retail value of over £5, for only 21/- Over 50 useful items, our selection, but satisfaction guaranteed or money refunded. Latest lists of many other items free on request. Trade supplied.—**FIRTH RADIOGRAPH LTD.,** 68-71 Church Gate, Leicester. Phone: 58927.

**THE LAST WORD IN RADIO KIT AND COMPONENT BARGAINS:** Really detailed Instructional Manuscript how to build best type 3-valve plus rectifier A.C. or Universal receiver, 2/6. Absolute complete Kit incl. valves and super cabinet, £8 carr. paid. Also 5-valve high-gain 3-wave Superhet Assembly, Universal, £5; A.C. £6/17/6, carr. paid. Postage for full specifications, 2/1n. 0-1 mA. 1st grade m.c. meters by Ferranti etc., 27/6; 5 mA. meter rectifiers, 7/6; selenium rectifiers, 250v., 45 mA., 5/-; Midret mains transformers, giving output 6.3 volts, 1.5 amps., 12/6. Standard Mains Transformers, £3.0/0/0, £3.0/0/0, £3.0/0/0, £3.0/0/0. Quality I.F.'s, 465 kc/s, iron-cored, 12/6 pair. Very best P.M. speakers, 5in., 17/6; 6in. Rola, 19/-; 8in. R. and A., 21/-; Transformers, 5/6; Ex-Govt. valves: EF50, EBC33, 6/5; 6L3, 5/6; EF30, EF35, 2/6; 9A, 1/10 per cent. Revolutionary new "Q" iron-cored 3-wave Coil Pack, 33/-; Immediate dispatch, all AVO Instruments. Pullin Series, 100 Multirange meters, 10,000 ohms per volt, A.C./D.C. voltm. amps, and ohms, large dial, 10 kc/s, carr. paid. Send postage now for Special P.V. List. Terms: C.W.O. or any item. C.O.D.—N.R.S., 66, Parkhill Road, London, N.W.3.

**SALE.** Eddyst. A.W.2. completely stripped and rebuilt as new. Special valves and three new coils. C. Mar. Manufactures' Supplies. Maker's chassis and cab. real fine dx-er. With phones. Carr. paid, £7 or near.—R. A. Fitzjohn, Smeeth Road, Nr. Wisbech, Cambs.

**SEVEN SHEETS** purchased and cash paid, state quantity to **BULLS, 246, Fish St. Harlescott, W.10.**

**ELIC REPEATER MOTORS.**—Govt. Surplus Bargain. For mod. A.C./D.C. 6.50 volt or remote control, including mod. instructions. 5/-, post 8d.—Lucas, 22, Hengrove Road, Bristol, 4.

**RADIO CONSTRUCTORS** have unrepeatable bargains in all types of Radio Equipment, ex-Govt., Manufacturers' Surpluses, etc., all brand-new. Stocks change too rapidly to list accurately here. Send S.A.E. for current lists at once to Radio Constructors, 26, Spital Hill, Sheffield, 4. Trade supplied.

**QUALITY AMPLIFIERS,** built of first grade parts (Partridge Transformers), special Partridge output transformer, to Mr. Williamson's spec. A first-class amplifier for the quality enthusiast. Price £25. Assembled and tested. Pre-amplifier, 12in. speakers and Gram. motors extra if required. 8in. speakers from 17/6.—R. T. S. (Ealing), Ltd., 141, Little Ealing Lane, W.5. Ealing 6902.

**HIGH FIDELITY AMPLIFIERS.**—Kits supplied for High Fidelity Amplifiers, any output as specified. Input, Microphone or any type of Pick-up, as required, extra if required. 8in. speakers from 17/6.—R. T. S. (Ealing), Ltd., 141, Little Ealing Lane, W.5. Ealing 6902.

**EX.W.D.—SP111, 68H7s, 4-** each. Most new.—"Carfrol," Elm Road, Hereford.

**VALVES and components, C.O.D. or C.W.O.** (postage extra). **WROTEBEYS (PW), 20, Brishton Rd., London, N.16.**

## SITUATIONS VACANT

**THE AIR MINISTRY** has vacancies in the Meteorological Office organisation for a number of civilian Radio (Meteorological) Mechanics to maintain radio and radar equipment. Applicants must possess a knowledge of the fundamental principles of radio and radar and have had practical experience in the use of tools, filing, drilling, sand and soft soldering, wiring and in the maintenance and use of electronic and radar instruments, including cathode ray oscilloscopes. Preference will be given to former R.A.F. personnel and any other ex-servicemen possessing the requisite qualifications. Staff selected will be required to serve at any station at home or abroad, and in the case of appointments at home units will generally be expected to make their own arrangements for accommodation. Successful applicants will be engaged on a temporary non-responsible basis only, at commencing weekly wages (in the United Kingdom) of £6/5/- per week (inclusive) for appointees aged 21 and over. Applications should be addressed to Air Ministry (S.5.h), Bush House, North West Wing, Aldwych, London, W.C.2.

## TUITION

**RADAR, WIRELESS, TELEVISION, etc.** Be prepared for tremendous peace-time developments. Students of both sexes trained for appointments in all branches of radio. Boarders accepted. Low fees, 2d. stamp for prospectus.—Wireless College, Colwyn Bay.

**THE INSTITUTE OF Practical Radio Engineers** have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E. Service entry and professional exams. A tuition fee at pre-war rates—moderate. The Syllabus of Instructional Text may be obtained, post free, from the Secretary, 20, Fairhead Road, Crouch End, Colwyn Bay.

**FOUR CIGARETTES** per day or Associate Membership of the I.E.E. Which would you rather have? Expert and successful tutors of the British National Radio School will coach you for I.E.E., Brit.I.R.E., and a whole series of G.C. examinations for 80 per cent. day I write, send for our free booklet and unequalled guarantee. Studies Director B.Sc., A.M.I.E.E., M.Brit.I.R.E., 66, Addiscombe Rd., Croydon, Surrey.

# Practical Wireless BLUEPRINT SERVICE

## SPECIAL NOTICE

THESE blueprints are drawn by the same firm as the original designs. The descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the initials in which the description appears. Thus "P.W." refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamp) and be obligingly to PRACTICAL WIRELESS, Blueprint Dept. George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

### SUPERHETS

**Battery Sets: Blueprints, 3s. each.**  
 Variety Four .. .. . WM365\*  
 The Request All-Wave .. .. . WM367\*  
**Mains Sets: Blueprints, 2s. each.**  
 Home-Trade Super Three A1 .. .. . WM369\*

### PORTABLES

**Four-valve: Blueprints, 3s. each.**  
 Holiday Portable (SG, D, LF, Class B) .. .. . AW395\*  
 Handy Portable (HF, D, RC, Trans) .. .. . AW397\*  
 Toys Portable (SG, D, 2 Trans) .. .. . WM397\*

### SHORT-WAVE SETS. Battery Operated

**One-valve: Blueprints, 2s. each.**  
 S.W. Short-wave for America .. .. . AW429\*  
 Bonus Short-wave .. .. . AW432\*  
**Two-valve: Blueprints, 2s. each.**  
 Ultra-short Battery Two (SG, det Pen) .. .. . WM402\*  
 Home-Trade Coll Two (D, Pen) .. .. . AW410  
**Three-valve: Blueprints, 2s. each.**  
 Experimental 3-metre Set (D, Trans, Super-conc) .. .. . AW438  
 The Carrier Short-wave (SG, D) .. .. . WM399\*

**Four-valve: Blueprints, 3s. each.**  
 A.W. Short-wave Wide-band (HF Pen, D, RC, Trans) .. .. . AW426\*  
 Standard Four-valve Short-wave (SG, D, LF, P) .. .. . WM388\*

**Superhet: Blueprint, 3s.**  
 Simplified Short-wave Super .. .. . WM397\*

**Mains Operated**  
**Two-valve: Blueprints, 2s. each.**  
 Two-valve Mains Short-wave (D, Pen, A.C.) .. .. . AW433

**Four-valve: Blueprints, 3s.**  
 Standard Four-valve A.C. Short-wave (SG, D, RC, Trans) .. .. . WM391

### MISCELLANEOUS

S.W. 1-valve Converter (Price 1s.) .. .. . AW329  
 Enthusiast's Power Amplifier (10 Watts) (2-2) .. .. . WM387\*  
 Listener's 5-watt A.C. Amplifier (3-2) .. .. . WM392\*  
 Radio Unit (2-2) for WM392 (2-2) .. .. . WM398\*  
 Harris Electrogram battery amplifier (2-2) .. .. . WM399\*  
 The Lyaxe Concert A.C. Electro-gram (2-2) .. .. . WM405\*  
 New Style Short-wave Adapter (2-2) .. .. . WM388  
 E.L.D.L.C. Short wave Converter (2-2) .. .. . WM405\*  
 Wilson Tone Master (2-2) .. .. . WM406\*  
 The W.M. A.C. Short-wave Converter (2-2) .. .. . WM408\*

## HINTS COUPON

This coupon is available until February 2nd, 1948, and must accompany all Practical Wireless, FEB. 1948.

### PRACTICAL WIRELESS

No. of E. J. Cannon's A.C. Superhet 4 .. .. . PW59  
 Blueprints. P. J. Cannon's Universal 44 Superhet 1 .. .. . PW60  
 "Quadrone" (Five-valve) Four .. .. . PW73

### CRYSTAL SETS

**Blueprints, 1s. each.**  
 1927 Crystal Receiver .. .. . PW71\*  
 The "Junior" Crystal Set .. .. . PW91\*

### STRAIGHT SETS. Battery Operated

**One-valve: Blueprints, 2s. each.**  
 All-Wave (Hifon) (Pentode) .. .. . PW31A\*  
 Beginners' One-valve .. .. . PW57\*  
 The "Pyramid" One-valve (HF Pen) .. .. . PW96\*  
**Two-valve: Blueprints, 2s.**  
 The Signal Two (D & LF) .. .. . PW76\*  
**Three-valve: Blueprints, 2s. each.**  
 Selection Battery Three (D, 2 LF (Trans)) .. .. . PW10  
 Summit Three (HF Pen, D, Pen) .. .. . PW37\*  
 Half-Mark Coll 4 (D, LF, Pen) (HF Pen, D, Pen) .. .. . PW48\*  
 E. J. Cannon's Silver Souvenir (HF Pen, D, Pen, Pen) (All-Wave Three) .. .. . PW49\*  
 Congo Midge, Three (D, 2 LF (Trans)) .. .. . PW51\*  
 D.L.S. Sintonone Three-Four (HF Pen, HF Pen, Westcopter, Pen) .. .. . PW52\*  
 Battery All-Wave Three (D, 2 LF (RC)) .. .. . PW55\*  
 The Monitor (HF Pen, D, Pen) .. .. . PW51\*

The "Coll." All-Wave Three (D, 3 LF (RC & Trans)) .. .. . PW72\*  
 The "Ronald" Standard 3 (D, 2 LF (RC & Trans)) .. .. . PW82  
 E. J. Cannon's Oracle All-Wave Three (HF, Det, Pen) .. .. . PW75  
 1928 "Wobair" All-Wave Three (HF Pen, D, Pen) .. .. . PW78\*  
 E. J. Cannon's "Sprite" Three (HF, Pen, D, Det) .. .. . PW87\*  
 The "Hurricane" All-Wave Three (SGH, Pen, Pen) .. .. . PW89\*  
 E. J. Cannon's "Push-Button" Three (HF Pen, D (Pen), Det) .. .. . PW92\*  
**Four-valve: Blueprints, 2s. each.**  
 Beta Universal Four (SG, D, LF (C, B)) .. .. . PW17\*  
 Nicholson Class B Four (SG, D (SG, LF, 2L, B)) .. .. . PW31B\*  
 Fury Four 8s per (SG, SG, D, Pen) .. .. . PW31C\*  
 Battery Half-Mark 4 (HF, Pen, D, Push-Button) .. .. . PW46\*  
 "Aunt" All-Wave 4 (HF Pen, D (Pen), LF, 2L, B) .. .. . PW53\*  
 The "Abdual" Four (HF Pen, HF Pen, D, Pen (RC)) .. .. . PW80\*

### Mains Operated

**Two-valve: Blueprints, 2s. each.**  
 Selectone A.C. Radiogram Two (D, Pen) .. .. . PW16\*  
**Three-valve: Blueprints, 2s. each.**  
 Double-Diode Three (HF Pen, DD, Pen) .. .. . PW22\*  
 D.C. Ace (SG, D, Pen) .. .. . PW25\*  
 A.C. Three (SG, D, Pen) .. .. . PW33\*  
 A.C. Leader (HF Pen, D, Pen) .. .. . PW34\*  
 H.C. Premier (HF Pen, D, Pen) .. .. . PW35\*  
 L'Esque (HF Pen, D (Pen), Pen) .. .. . PW36A\*  
 E. J. Cannon's A.C. All-Wave Silver Souvenir Three (HF Pen, D, Pen) .. .. . PW50\*  
 "All-Wave" A.C. Three (D, 2 LF (RC)) .. .. . PW54\*  
 A.C. 1630 Sintonone (HF Pen, HF Pen, Westcopter, Pen) .. .. . PW55\*  
 Mains Record All-Wave 3 (HF Pen, D, Pen) .. .. . PW70\*  
**Four-valve: Blueprints, 2s. each.**  
 A.C. Fury Four (SG, SG, D, Pen) .. .. . PW29\*  
 A.C. Fury Four Super (SG, SG, D, Pen) .. .. . PW31D  
 A.C. Half-Mark (HF Pen, D, Push-Button) .. .. . PW45\*  
 Universal Half-Mark (HF Pen, D, Push-Button) .. .. . PW47\*

### SUPERHETS

**Battery Sets: Blueprints, 2s. each.**  
 41 Superhet (Three-valve) .. .. . PW10  
 42 Superhet (Two-valve) .. .. . PW32\*  
**Mains Sets: Blueprints, 2s. each.**  
 A.C. 45 Superhet (Three-valve) .. .. . PW43  
 D.C. 45 Superhet (Three-valve) .. .. . PW42\*

### SHORT-WAVE SETS. Battery Operated

**One-valve: Blueprint, 2s.**  
 Single S.W. One-valve .. .. . PW88  
**Two-valve: Blueprints, 2s. each.**  
 Midget Short-wave Two (D, Pen) .. .. . PW85\*  
 The "Fleet" Short-wave Two (1 (HF Pen), Pen) .. .. . PW91\*  
**Three-valve: Blueprints, 2s. each.**  
 Experimental Short-wave Three (SG, D, Pen) .. .. . PW36\*  
 The Perfect 3 (D, 2 LF (HF and Pen)) .. .. . PW63\*  
 The Handspread S.W. Three (HF Pen, D (Pen), Pen) .. .. . PW69

### PORTABLES

**Three-valve: Blueprints, 2s. each.**  
 E. J. Cannon's FLIP Three-valve Portable (HF Pen, D, Pen) .. .. . PW65\*  
 Parvo Flightweight Midget Portable (SG, D, Pen) .. .. . PW77  
**Four-valve: Blueprint, 2s.**  
 "Imp" Portable 4 (D, LF, LF, Pen) .. .. . PW86

### MISCELLANEOUS

**Blueprint, 2s.**  
 S.W. Converter-Adapter (1 valve) .. .. . PW48A\*

### AMATEUR WIRELESS AND WIRELESS MAGAZINE CRYSTAL SETS

**Blueprints, 1s. each.**  
 Four-station Crystal Set .. .. . AW427  
 Lovers' Talking Collar AW427 .. .. . Ia  
 HCA Crystal Set .. .. . AW 114  
 Modern Crystal Set .. .. . AW 70

### STRAIGHT SETS. Battery Operated.

**One-valve: Blueprint, 2s.**  
 B.B.C. Special One-valve .. .. . AW387  
**Two-valve: Blueprints, 2s. each.**  
 Full-wave Two (S.H. det, Pen) .. .. . AW392\*  
 A modern One-valve .. .. . WM409  
**Three-valve: Blueprints, 2s. each.**  
 45 5s. S.G. 3 (SG, D, Trans) .. .. . AW412  
 Laeone Ranger (SG, D, Trans) .. .. . AW422  
 45 5s. Three De Luxe Version (S, D, Trans) .. .. . AW435  
 Transportable Three (SG, D, Pen) .. .. . WM271  
**Four-valve: Blueprints, 2s. each.**  
 Economy Pentode Three (SG, D, Pen) .. .. . WM357  
 "W.M." 1934 Standard Three (SG, D, Pen) .. .. . WM351\*  
 23 1s. Three (SG, D, Trans) .. .. . WM351\*  
 1935 26 6s. Battery Three (SG, D, Pen) .. .. . WM354  
 B.T. Time (Pen, D, Pen) .. .. . WM389  
 Certainty Three (SG, D, Pen) .. .. . WM393  
 All-wave Winding Three (SG, D, Pen) .. .. . WM400  
**Four-valve: Blueprints, 3s. each.**  
 65c. Four (SG, D, B, Trans) .. .. . AW379  
 Self-contained Four (SG, D, LF, C, B) .. .. . WM331  
 Laeone Straight Four (SG, D, LF, Trans) .. .. . WM350  
 65c. 5s. Battery Four (HF, D, 2LF) .. .. . WM378\*  
 The H.K. Four (SG, D, Trans) .. .. . WM384\*  
 The Auto Straight Pen (HF Pen, HF Pen, DD, Pen) .. .. . WM404\*  
**Five-valve: Blueprints, 2s. each.**  
 Super-quality Five (2 HF, D, RC, Trans) .. .. . WM520  
 Class B Quadradyne (2 SG, D, LF, Class B) .. .. . WM444  
 New Class B Five (2 SG, D, LF, Class B) .. .. . WM340

### Mains Operated

**Two-valve: Blueprints, 2s. each.**  
 Cosmopolitan Two (D, Pen, Pen) .. .. . AW402\*  
 Cosmopolitan A.C. Two (D, Pen, A.C.) .. .. . WM286\*  
**Three-valve: Blueprints, 2s. each.**  
 Mantova A.C. Three (HF, Pen, D, Pen) .. .. . WM374\*  
 415 15s. 1936 A.C. Radiogram (HF, D, Pen) .. .. . WM401\*  
**Four-valve: Blueprints, 2s. each.**  
 All-Metal Four (2 SG, D, Pen) .. .. . WM329  
 Harel Jubilee Radiogram (HF, Pen, D, LF, P) .. .. . WM356\*

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEAIGHT & SONS, LTD., Exmouth Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (Asia), LTD. South Africa: CENTRAL NEWS AGENCY, LTD. Subscription rates including postage: London 10s. 6d. per annum. Abroad 10s. per annum. (Orders should be sent to the General Post Office for the Canadian Magazine Post. CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers, first, be lent, re-sold, hired out or otherwise disposed of by way of Trade except at the full retail price of 9d., and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade; or affixed to or as part of any publication or advertising, literary or pictorial matter, whatsoever.

# The TAYLOR Junior UNIVERSAL METER

MODEL 120A

21 RANGES

Sensitivity 1,000 ohms  
per Volt A/C and D/C

IMMEDIATE  
DELIVERY



POCKET SIZE

HIRE PURCHASE TERMS  
14/10 DEPOSIT  
ELEVEN MONTHLY  
PAYMENTS OF 14/4

PRICE  
**£7-10-0**

D.C. VOLTS:-  
5mV to 5000V  
D.C. CURRENT:-  
20μA to 500mA  
A.C. VOLTS:-  
2V to 5000V

Write for Descriptive Leaflet

## TAYLOR

ELECTRICAL INSTRUMENTS LTD.

419-424 MONTROSE AVENUE, Slough, Bucks.

Telephone: SLOUGH 21381 (4 lines)

RESISTANCES:-  
0.5 to 200,000 ohms  
(and 20 megohms  
with external battery)

## AMBITIOUS ENGINEERS

### HAVE-YOU HAD YOUR COPY OF "ENGINEERING OPPORTUNITIES"?

Whatever your age or experience—whether you are one of the "old school" or a newcomer to Engineering anxious to hold your position under post-war conditions—you must read this highly informative guide to the best paid Engineering posts.

The Handbook contains among other intensely interesting matters, particulars of B.Sc., A.M.I.C.E., A.M.I. Mech.E., A.M.I.E.E., A.M.I.M.I., A.M.L.P.E., A.M. Brit.I.R.E., CITY & GUILDS, CIVIL SERVICE, and other important Engineering Examinations, outlines home-study courses in all branches of CIVIL, MECHANICAL, ELECTRICAL, AUTOMOBILE, RADIO, TELEVISION, AERONAUTICAL and PRODUCTION ENGINEERING, DRAUGHTSMANSHIP, GOVERNMENT EMPLOYMENT, BUILDING and PLASTICS (the great peacetime careers), MATRICULATION, etc., and explains the unique advantages of our Employment Department.

### WE DEFINITELY GUARANTEE 'NO PASS—NO FEE'

If you are earning less than £10 a week you cannot afford to miss reading "ENGINEERING OPPORTUNITIES"; it tells you everything you want to know to make your future secure and describes many chances you are now missing. In your own interest we advise you to write for your copy of this enlightening guide to well-paid posts NOW—FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

409, SHAKESPEARE HOUSE, 17, 18 & 19, STRATFORD PLACE, LONDON, W.1.

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD