

6K7 POCKET RECEIVER


Practical Wireless

9^D
EVERY
MONTH

Vol. 24. No. 504. ||

Editor: F. J. CAMM ||

JULY, 1948

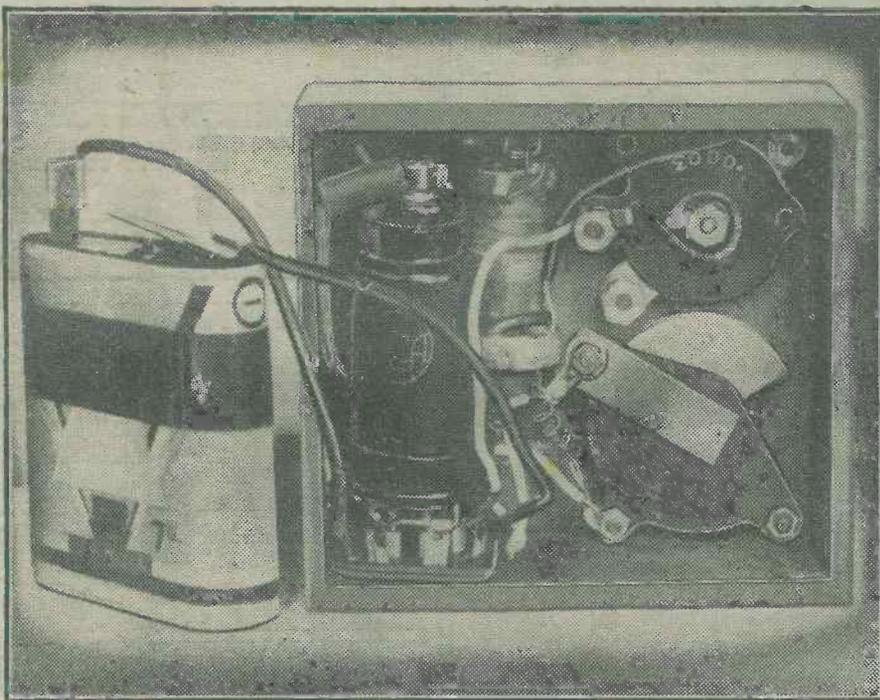

See Page 270

PRINCIPAL CONTENTS

High-Fidelity Radiogram
Practical P.A. Working
F.M. Oscillator
Recording Technique

A.C./D.C. Circuits
Technical Notes
Test Instrument Design
A V.H.F. Adapter

MAGNETRONS - T.V. UNITS - 'Q' UNITS etc.

MAGNETRONS.—U.S. made. Mounted in unit, complete with magnet-spark gap and other electrical and mechanical details. Price £12.10.0. Plus £1 carriage and packing-case.

TELEVISION UNITS. We are able to offer, for less than the value of the valves alone, an ideal 8-valve unit which has a response curve virtually flat from 12-18 Mc/s. By fitting an oscillator valve, quite a simple job (we will give details where requested), the unit can become the perfect picture receiver. Signals with a field strength as low as 20 micro-volts can be received quite well.

We are pleased to be able to offer these units complete with valves and in perfect order at 55/- each, plus 2/6 postage and packing.

RADIO UNIT "Q". Here is your opportunity to purchase for 12/6 equipment which must have cost at least £25. This is not quite a complete receiver, so we call it RADIO Unit "Q".

It contains amongst other things a strong chassis, 18in. x 6in. x 3 1/2in., fitted with 13 Amphenol type Valve Holders. Among the parts mounted on the chassis are relays, 1 mfd. and 2 mfd. can type condensers. Ceramic variable condensers, small transformers and chokes, grid caps and Flye plugs, etc. Three banks of Mica condensers (approximately 30). Also eight Paxolin panels, 6in. x 2 1/2 in., with feet containing approximately 60 assorted resistors and 25 assorted tubular condensers. The special bargain price of this unit is only 12/6 plus 3/6 carriage. The supply is limited, so time is precious, don't delay, order immediately.

AC-348. We have converted a number of BC 348 (2100 class communications receivers). Fitting an A.G. power pack in place of the dyna-motor and carrying out necessary wiring alterations. The price of these "ready to work" receivers is £22/10/- plus 1/6 for wooden packing-case, insurance and carriage.

RECEIVER TRANSMITTER No. 18. This is a combined Receiver/Transmitter of the Walkie-Talkie type. Frequency coverage 6-9 Mc/s, complete with six valves, and in case which is fitted up for batteries (not included). PRICE £21/0/-, carriage 10/- extra.

DATA BOOKS.—Copied from official publications, giving circuit diagrams, component values and useful notes: BC.342—BC.348—BC.312—BC.221—R.208—R.103a—R.107—M.C.R.1—R.1155—W.S.22—RT.18—W.S.19—R.1116A—all at 2/3 each, also Walkie-Talkie 58, 3/6.—"Demobbed" valves, 2/6. List free on application.


NFRA RED IMAGE CONVERTER TUBE

This is a highly sensitive Photocell, which in addition to ordinary ray control operations, can be used for direct conversion of infra-red into visible light. Price 14/6. post and insurance. 1/6 extra. Send S.A.E. for leaflet.

W.D. SALES, 7 Electron House, 42-46, Windmill Hill, Ruislip Manor, Middlesex.

Connoisseur Products

NOW
available

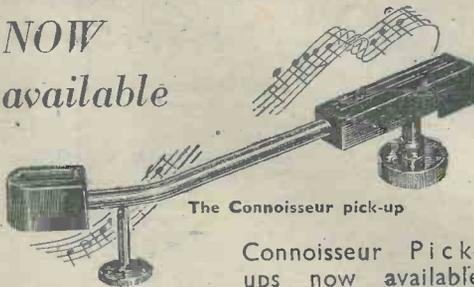

The Connoisseur pick-up

Connoisseur Pick-ups now available with transcription arms for playing 17in. discs. All models are available with low impedance coils of 25 ohms.

Connoisseur miniature steel needles, also sapphires mounted in duralumin shanks.

One valve pre-amplifier for 4 or 6 volt. heater operation. Full compensation for recording characteristics by means of variable bass and treble controls.

Apply to:—Albion Electric Stores, 125, Albion Street, Leeds, 1, or to Lawton Brothers (Sales), Ltd., Henry Square, Ashton-under-Lyne.

A. R. SUGDEN & CO. (ENGINEERS) LTD. BRIGHOUSE, YORKS.

Varley
REGD. TRADE MARK

Products of
Quality & Reliability

MAINS TRANSFORMERS
A. F. TRANSFORMERS
SMOOTHING CHOKES
THERMAL
DELAY SWITCHES
POWER RESISTANCES

Made by

OLIVER PELL CONTROL LTD

Telephone - WOOLWICH 1422
CAMBRIDGE ROW · WOOLWICH'S E 18

HENRY'S

Will our customers please note that we are now approved stockists of "DENCO" products. General catalogue of these well-known coils, etc., can be supplied at 9d.

"DENCO" COIL, TURRET TYPE.—CT5V. Improved version. Five wavebands: 150-400 kc/s., 530-1,500, 1.5-4 mc/s., 4-12 mc/s., 10-30 mc/s. Foolproof construction, eliminating wafer switches. Extra position for "Gram." Iron-cored coils. Polystyrene formers and insulation throughout. Silver-plated contacts. Supplied complete with tuning condenser, drive assembly, and large vertical reading black glass dial. Also provision for magic eye. The dial is illuminated from the rear, and two M.B.S. bulb holders are provided for the purpose. Cabinet opening for dial should measure 6 1/2in. x 6 1/2in. The whole, complete, with full wiring diagram and instructions, £4.19.6.

CATHODE RAY TUBE.—6in. VCR97, equivalent to Mullard ECR60. Electrostatic, non-persistent, each brand new, and individually boxed, ready for transit. Complete with printed data sheet giving full necessary details. 55/- only. Registered postage and packing, 7/8 extra.

"OSMOR" ULTRA MIDGET "Q" COILS.—By the manufacturers of the now famous midget coil pack. Size only 1in. x 1 1/2in. Iron-cored, polystyrene formers. At present available in normal 3-wave bands. Aerial or Oscillator Coils only. Circuit supplied. 3/- ea. coil.

Other Coils and Coil Packs in stock, include "Wearite," "Denco," "Atkins," "Weymouth," etc. etc. We can meet your every requirement.

VARLEY PRODUCTS.—EP47 Mains Transformer, 350-0-350v., 230 ma., 6.3v. 5a., 5v. 3a., 2-0-2v. 4a., 52/8 only. EP56 Mains Transformer, 500-0-500v. 200 ma., 6.3v. 3a., 5v. 2.5a., 2-0v. 4a., 72/6.

Also in stock, EP50, EP51 and chokes DP51. We also have many other types of Mains Transformers and Chokes in stock, for all purposes.

VALVES.—We have over 10,000 new and boxed Valves in stock, including ID6GT, 75, DK32, DAC32, DF38, DL33, GA7, etc. etc., all at current B.O.T. prices.

A stamp will bring our latest comprehensive list. C.W.O. or C.O.D. (over £1).

HENRY'S 5, HARROW RD., W.2
Paddington 1008/9

VALLANCE'S OFFER

A LIMITED QUANTITY OF AVO ALL-WAVE OSCILLATORS for operation on 200 to 250 v. A.C. are available for immediate delivery—now discontinued and will not be offered again after stocks are exhausted. This is an inexpensive modulated oscillator, suitable for test room or general laboratory use. It covers a continuous fundamental frequency band from 95 mc. to 40 mc. by means of six separate coils mounted on a rotary turret selector. Each band is directly calibrated in kc. on a large, clearly marked dial, calibration errors being not greater than 1 per cent. at any frequency.

RANGE III	30 mc.-30 mc.	4	700 kc.-2,200 kc.
1	14 mc.-40 mc.	5	250 kc.-800 kc.
2	5 mc.-15 mc.	6	95 kc.-300 kc.
3	1,800 kc.-6,000 kc.		

PRICE—£13. Railing Charge, 3s. 6d.

We can supply from stock the following—

TEST EQUIPMENT.—D.C. Avo Minor, £4 4s. Universal Avo Minor, 22 ranges, £8 10s. Taylor 120A Junior, A.C./D.C. ranges, £7 10s. Taylor 90A, 1,000 ohms/volt, A.C./D.C. 40 ranges, £15 15s. Mullard Resistance and Capacity Bridge, 10 ohms to 10 megohms, and 10 PF. to 10 mid., £15 15s.

PICKUPS.—Connoisseur, with transformer, 847, S.E.1 moving coil with transformer, 79/9. Rothermel crystal, senior model, 82/-, S.12, 52/6. Amplion crystal, 51/7. Goldring super magnetic, 30/7. Pickup head, fits all tone arms, 28/- Prices include tax. Delivery immediately.

MICROPHONES.—Crystal type, Rothermel, 12 gns.; Carbon type, Mico, 70/-; Hand mike, 30/-. Moving coil type, Reslo, 110/-. Ribbon type, Shaftesbury, 12 gns.

SOLDERING IRONS.—Pyrobit, 200/220 v., 45 watts, Instrument type, 22/-. Wireless type, 22/-. Model 6GB, 200/220 v., 65 watts, 22/-. Solon, 200/220 v. or 230/250 v., 65 watts, Pencil Bit, 21/-. Straight Bit, 19/6. Elco, 220/250 v., 60 watts, 18/4. L.L.P., 230/250 v., 60 watts, 18/9.

PYROBIT SPARES. Elements, Instrument, 230 v., 45 w., 3/6. Wireless, 230 v., 45 watt, 4/6. Universal, Fits either 200/220 or 230/250 v., 50 watt, 4/6.

BITS. Large Instrument, 4/-. Small pencil, 6d. Solon straight bits, 3/6. Pencil bits, 10/4d. Elements, 20 or 220 v., 4/6. And all other lines you are ever likely to need in radio.

Prompt C.O.D. or C.W.O. Service. Please include extra for packing and postage.

VALLANCE & DAVISON, LTD.,

144, Brigade, Leeds, 1. Phone: 29428/9.
Staff call signs:—G2HHV, G8SX, G3ABD, G3AHV.

R.K.C. KIT No. RG/30



This attractive 5 Valve 3 Wave A.C. Model can be built from R.K.C. Kit No. RG/30.

Retail price 20 Gns. Plus P/T.

For further details of this and other kits send for R.K.C. list.

RADIO KITS CO. LTD. HOLLINGBURY PLACE BRIGHTON.



LOCTAL VALVEHOLDERS

FOR LOCK-IN TYPE VALVES E8L2I, ECH2I, 7A7E, 7B8, etc.



TYPE VH 540/8

A double-plate laminated valveholder designed with 8 special sockets and centre spigot socket meeting the requirements of the B8G and B8B range of Loctal Valves.

THE GENERAL ACCESSORIES CO. LTD.

21 Bruton Street, London, W.1 Tel. MAYfair 5543

FOREMOST IN VALVEHOLDER DESIGN

MCR 1 POWER PACKS. The midget power packs that were made for the famous "Spy" set. A.C. or D.C. mains input 107-235v., output 90v. H.T. and 7.5 L.T. Metal rectification and efficient smoothing incorporated. Complete in grey metal case, size 8 1/2 in. x 3 1/2 in. x 2 1/2 in. Only 39/6 (carriage 1/6). Brand New.

EX-R.A.F. BATTERY AMPLIFIERS. These very fine little amplifiers are still in great demand for use with a gramophone, pickup, home intercom, unit, etc. etc. Operating voltages 2v. L.T. and 120v. H.T. Complete with valves types QP 21 and 210 L.F. [Brand New in Transit cases. Only 25/- (carriage, etc., 2/6).

INDICATOR UNITS TYPE 6. Contains 6 1/2 in. tube V.C.R. 97, EF 50s, EB 34s, etc. etc. Readily convertible into an oscilloscope. Only 67/8 (carriage, etc., 15/-). Send for complete list of the numerous types of ex-Services C.R. tube units we have in stock.

SHORT WAVE CONVERTERS. Eminently suitable for use on the "Ham" bands. Normal voltage inputs. Operate on 5 pre-set frequencies, but easily convertible to tuneable units by replacing ceramic switch with 3 ganging type 15 pf condensers. Contains 3-6v. SP 41s, 7 mcs. I.F. Output. Type 24 for 15-30 mcs. Type 25 for 30-45 mcs. Only 16/6 each (carriage 1/6). Type 27 is a tuneable converter covering 60-80 mcs., and contains 2 valves EF 54 and 1 type EC 52.7 mcs. I.F. Output. Fitted with 3 in. slow motion dial. Only 27/6 (carriage 1/6).

C.W.O. Please.

S.A.E. for lists.

U. E. I. CORP.,

The Radio Corner,
138, Gray's Inn Road, London, W.C.1
(TERminus 7937)

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn, 5 mins from Kings X.

'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark



The UNIVERSAL AVOMINOR Electrical Measuring Instrument

A small but highly accurate instrument for measuring A.C. and D.C. voltage, D.C. current, and also resistance. It provides 22 ranges of readings on a 3-inch scale, the required range being selected by plugging the leads supplied into appropriately marked sockets. An accurate moving-coil movement is employed, and the total resistance of the meter is 200,000 ohms.


The instrument is self-contained for resistance measurements up to 20,000 ohms, and, by using an external source of voltage, the resistance ranges can be extended up to 10 megohms. The ohms compensator for incorrect voltage works on all ranges. The instrument is suitable for use as an output meter when the A.C. voltage ranges are being used. Supplied complete with leads, testing prods, crocodile clips, and instruction booklet.

If any difficulty in obtaining locally, please send us the name and address of your nearest Radio Dealer.

Sole Proprietors and Manufacturers:—
AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1
Phone, VICTORIA 3404-9

D.C. Voltage	A.C. Voltage
0-75 millivolts	0-25 volts
0-5 volts	0-100 "
0-25 "	0-250 "
0-100 "	0-500 "
0-250 "	
0-500 "	
D.C. Current	Resistance
0-2.5 milliamps	0-20,000 ohms
0-5 "	0-100,000 "
0-25 "	0-500,000 "
0-100 "	0-2 megohms
0-500 "	0-5 "
	0-10 "


Size: 4 3/8" x 3 3/8" x 1 3/8"

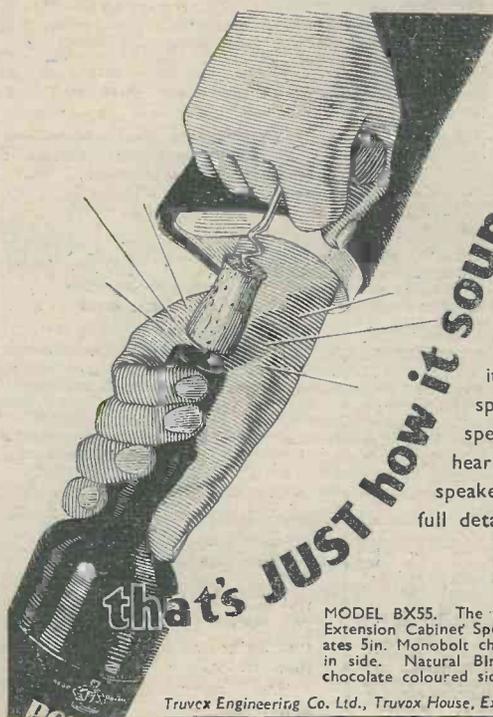

TRUVOX

The cork is drawn, the party's on and you are there, there with all the gaiety that perfect reproduction can bring you. Truvox owners are getting extra realism that makes all the difference in listening to a favourite programme—Home, Light or Third. It has taken us 18 years to achieve it... it's yours today. A range of three extension cabinet speakers is in the dealers' shops already, "Monobolt" speaker chassis in four sizes are there too, you can hear them now. High fidelity pickups and "Wafer" speakers are well on the way. A postcard will bring full details.

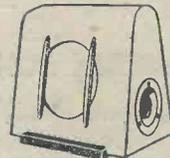MODEL BX55. The first of a new range of Truvox Extension Cabinet Speakers. This model incorporates 5in. Monobolt chassis, volume control recessed in side. Natural Birch cabinet, with contrasting chocolate coloured sides. List Price 65/-.
Truvox Engineering Co. Ltd., Truvox House, Exhibition Grounds, Wembley, Middx.



Practical Wireless

16th YEAR
OF ISSUE

and PRACTICAL TELEVISION

EVERY MONTH

VOL. XXIV. No. 504

JULY, 1948

Editor, F. J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

The Tax and Unemployment

LAST month we dealt with the effects of the increase in the purchase tax on radio and television receiver sales, and expressed the view that it would cause unemployment. That, indeed, unhappily has proved to be the case. On the shelves of radio dealers all over the country are 500,000 radio and television receivers for which retailers are unable to find buyers. Our investigations show that manufacturers and retailers place the blame entirely upon the purchase tax for this ruthless destruction of the market.

Worse than this, during the past two months over 6,000 people have been discharged by manufacturers, and at the moment of going to press many more are under notice as factories close and production is cut.

There seems to be a senselessness about the Government's policy. It invited manufacturers to increase production and to export a high percentage of that production. In order to cut down home sales a purchase tax of 33-1/3rd per cent. was imposed, thus forcing manufacturers to export receivers they could not sell in the home market.

The manufacturers loyally responded and many millions of pounds worth of radio receivers, components and valves have been exported under that policy. The Government thought that there was no limit to the pressure it could bring to bear on manufacturers, and no burdens too heavy for the British citizen, and so at the last Budget the purchase tax was doubled. The inevitable result was, as everyone but the Government pundits knew, that sales dropped overnight. Worse than that. The Government has been cutting down its purchases from overseas in the insane belief that we can sell everything to foreign countries and buy nothing from them. Little wonder, therefore, that overseas countries have ceased to buy from us or, alternatively, have imposed restrictive import tariffs which make the export of goods a virtual impossibility unless manufacturers are prepared to allow the Government to raise its dollar credits at the expense of British shareholders.

This quite rightly they are not prepared to do. The overseas market having been considerably diminished due to an unimagina-

tive Government export policy, the trade now finds itself without a home market either, because of the crippling purchase tax. Can the Government wonder, therefore, that manufacturers have cut production and in some cases closed down altogether?

It is true to some extent that the spending boom is ended, and that the incursion of new firms is cutting up the trade. It is also true to some extent that British receivers are so well made that a listener does not buy a new one until the old one has given at least five years' good service.

The fact is that there is no demand to-day for commercial wireless receivers. The only way to save the industry from complete disaster is for the purchase tax to be removed and at once.

Evidently Sir Stafford Cripps is worried about the situation because he has asked the Radio Industry Council to draw up an analysis of the crisis. Shop stewards of one of the largest manufacturers have sent a detailed report to the Ministers of Labour and Supply, the President of the Board of Trade, the Chancellor of the Exchequer, local M.P.s and union officials pointing out that it is time the Government realised that radio is a necessity and asking for an immediate decrease in the purchase tax. The matter has been raised in Parliament.

Those interested in Stock Exchange statistics may like to know that the crisis has meant a loss of £7,000,000 in 12 months to investors holding shares in seven of the largest wireless manufacturing companies.

What is happening in the wireless trade is happening in many others, and the time has come when the Government must realise that the public will not continue to countenance taxation on a wartime basis, three years after the victory bells have pealed. The Government has nationalised many industries and denationalised many others. These wrecking tactics cannot be allowed to continue.

The high costs resulting from nationalisation do not encourage the belief that the Government has sufficient experience of business to plan it.

The radio industry is too important to be regarded as a pigeon to be plucked.

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd.,
Tower House, Southampton Street, Strand,
W.C.2. Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

ROUND THE WORLD OF WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ending March 31st, 1948:

Region	Number
London Postal	2,096,000
Home Counties	1,465,000
Midland	1,590,000
North Eastern	1,727,000
North Western	1,464,000
South Western	964,000
Welsh and Border	645,000
Total England and Wales	9,951,000
Scotland	1,057,000
Northern Ireland	182,000
GRAND TOTAL	11,190,000

This number includes 45,550 television licences, an increase of 2,050 over the previous month.

Prosecutions in March for operating wireless receiving apparatus without a licence reached the record figure of 637.

Radio Export Record

ACCORDING to latest figures issued by the Radio Industry Council, the value of exports of British radio equipment of all kinds in January last was £1,151,954. The previous highest monthly total was £1,018,000 in December, 1946.

Radio receivers alone accounted for an export value of £457,266. Other export values for the month were:

Components and sound reproducing equipment	£303,182
Transmitters, navigational aids and industrial electronic equipment	£231,128
Valves	£160,378

Twenty-one Years' Service

ANOTHER stage in the history of The Whiteley Electrical Radio Co., Ltd., was recently reached when over 40 employees with 10 years or more service gathered together in the works canteen to pay tribute to Mr. D. James (assistant works manager), who is the first employee to complete 21 years' continuous service. The occasion was marked by a presentation from the directors of a gold watch and chain, which was suitably inscribed. A cheque was also handed to Mrs. James.

Mr. A. H. Whiteley (managing director), in congratulating Mr. James and thanking him for his loyal service, recalled that Mr. James had at various times been associated with practically every department in the works and was held in great regard by every member of the organisation. In expressing his appreciation, Mr. James said that he had been privileged to grow up with the company from the days when it occupied an area of 2,000 square feet and employed just a few people, until to-day, when the factory area was over 100,000 square feet and employs nearly 1,000.

B.I.R.E. Meeting

A LONDON Section meeting was held on May 13th, last, at the London School of Hygiene and Tropical Medicine, at which Mr. I. A. Harris (Associate), read a paper on "The Calculation of Electrode Temperatures in the Radio Valve."

Television Set for Old Folk

AMONG the many gifts at the inauguration of the first of the homes to be opened by Ealing Eventide Homes, Ltd., was a Philco A.1707 television receiver.

This had been presented by Philco and Airmec employees out of surplus funds in the sports and social club.

The home is at "Downhurst," Castlebar Road, Ealing, and is to accommodate 24 elderly ladies who have been chosen out of 250 applicants; it is, incidentally, the first home of its kind in this country to have a television receiver.

R.C.M.F. Council, 1948/49

THE following member firms will serve on the R.C.M.F. Council for the coming year:

Automatic Coil Winder and Elec. Equip. Co., Ltd., W. F. Newell; British Insulated Callender's Cables, Ltd., W. C. Handley; British Moulded Plastics, Ltd. (A), M. J. Nash; British N.S.F. Co., Ltd., S. Wilding Cole; Garrard Engineering and Mfg. Co., Ltd., Hector V. Slade; Hellermann Electric, Ltd. (A), J. Bowthorpe; Morgan Crucible Co., Ltd., E. T. Tregenza; Plessey Co., Ltd., J. A. Smith; Reliance Electrical Wire Co., Ltd., C. H. Davis; Telegraph Condenser Co., Ltd., P. A. Sporing; Telegraph Construction and Mtncce. Co., Ltd., W. F. Randall; Telephone Manufacturing Co., Ltd., W. A. Jackson.

(A) Associate Member.

The following officers have been elected for 1948/49.

Chairman, J. A. Smith; vice-chairman, C. H. Davis; treasurer, Hector V. Slade.



The scene at the presentation to Mr. James at the Whiteley Electrical Radio Company.

Television City

THE U.S.A. radio industry is considering the erection of a "Television City" in New York. It is claimed that the idea would economise in announcers, and the companies would be able to pool resources. It is hoped to include in the "City" a large arena and swimming pool for spectacular sports-shows.

P.A. for Turf Club

ONE of the largest installations of public address and paging equipment in the Far East has recently been completed by The General Electric Co., Ltd., at the Turf Club Stadium, in Singapore.

Comprising a three-unit amplifier, single-bay, rack assembly with gramophone player, a three-position control box and a series of microphones and loudspeakers, the installation provides music relay and paging facilities through the grandstand and principal buildings. In addition, a separate amplifier, with its associated microphone and loudspeaker, is provided for paging purposes in the car park. The microphone for this subsidiary installation is located on the pavement outside the main entrance, and is also used by the police for traffic control.

The main control box is normally operated from the assistant secretary's office, as he is the person mainly responsible for the upkeep and general running of the course and buildings, but, if desired, it can also be plugged into a socket adjacent to the main rack assembly or into a similar socket in the secretary's office. Two rows of push buttons, together with their associated pilot lamps and switches control the input and output circuits; this very simple method of control being achieved by means of groups of telephone-type relays.

Suppression of Radio Interference

CONTINUING its campaign for the voluntary suppression of interference with television and short-wave communications the Radio Industry Council held the third of its demonstrations on the fringe of the London television area at Penn, Buckinghamshire. The guests included representatives of the motor-car and sparking plug manufacturers invited by the R.I.C. through the Society of Motor Manufacturers and Traders. Austin, Delco-Remy and Hyatt, Ford, Humber, Jaguar, Rolls-Royce, Scammell, Singer and Vauxhall were represented as well as Lucas, A.-C. Sphinx, Champion, KLG and Lodge. Transport owners were represented by Mr. S. H. Jardine, secretary of the Road Haulage Association, the Hays Wharf Cartage Co. group, which includes Pickfords and Carter Paterson, Thomas Allen, Ltd., and George Neal, Ltd.

The Hays Wharf group of companies had already agreed in principle to the suppression of its vehicles. The United Dairies Company, which was also represented, is proposing to start suppression. The GPO, which was represented at the demonstration by Colonel A. G. Macdonald, recently announced its intention of suppressing the whole of its 25,000 vehicles throughout the country.

A Piece of Cake!

ONE of the highlights of the television ball held recently by Kennard's, of Croydon, in their restaurant, was an exact replica of a Philips 563A television receiver—made of cake!

Baked by Kennard's chef, Mr. H. C. Axford, to a pre-war recipe the cake was hardly distinguishable from the real thing, so skilful was the decoration. It weighed 140lbs. and was built up in five layers. The loudspeaker fret was carried out in icing, and the walnut effect simulating the polished finish of a real Philips television set was achieved by painting with vegetable dyes. The only items that were not made of cake were the glass tuning dial that projects from the top of the set, the escutcheon on the front, and the photograph placed on the "screen" to represent the television picture.

The item was televised by the B.B.C. Mr. MacDonald Hobley, television compere interviewing the chef on the spot and interrogating him on his labours in the baking of the cake.



The television cake and its maker at the Croydon Television Ball.

The television ball was held in aid of three local hospitals, the funds going towards the cost of equipping them with television receivers. Television sets were on display around the dance floor, and dancing was to Geraldo and his band.

Morning Television

IN response to requests from many viewers, the composite film of television newsreels (this comprises the previous fortnight's newsreels) is now being televised on Saturday mornings instead of Monday mornings. This replaces the demonstration film, which continues to be shown each morning from Monday to Friday inclusive for the benefit of the radio trade.


The change took effect from May 1st.

Political P.A.

THE West Bengal Government has prohibited the use of vehicles fitted with loudspeakers except with the written permission of the Commissioner of Police. The order is in force for an indefinite period.

6K7 Pocket Receiver

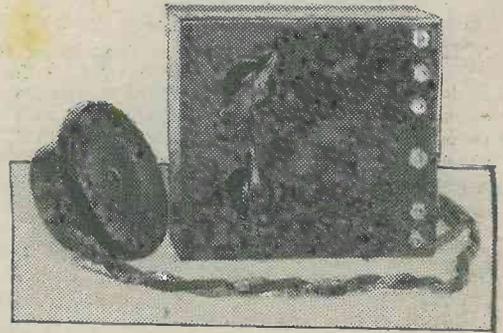Details of a Novelty Using Only a 4.5 Volt Battery.
By F. G. RAYER



MANY constructors are interested in the construction of novel types of working receivers, and the very small pocket type of set, although providing only headphone reception, has a wide field of practical use. The receiver to be described, and which is illustrated on our cover this month, utilises a 6K7, which is a pentode of small size which maintains good efficiency with a very low anode voltage. It is easy to obtain and lends itself to the construction of a small pocket set, because a single 4.5 volt dry battery will provide both heater and high-tension currents. The current consumption is about .3 amp., which is about the same as an average 2-valve battery set and not in any way excessive.

Battery replacement is cheap and easy, and the complete receiver, including battery, is only 4in. by 3½in. by 2in. A single earpiece or pair of headphones may be used in conjunction with it. A few feet of thin flex are used as a throw-out aerial, giving ample headphone volume on the more powerful stations. With a longer aerial some foreign stations can be received.

Constructional Details

From the circuit shown in Fig. 1 the few necessary parts can be seen. For tuning and reaction solid dielectric condensers are necessary. The reaction condenser may be either an ordinary type or a differential condenser; a capacity of .0005 µF. is also suitable.

A valveholder with open sockets simplifies construction as it can be mounted in the same way as a baseboard holder. Other types of holder will have to be supported on short stand-off sleeves. There is room for a tuning coil ¾in. in diameter

and several of the small coils available are suitable. Before building the case to the dimensions given check that the condensers and coil can be accommodated and that the valve can be inserted. The battery (a standard 4.5 volt pocket-lamp battery) fits beside the valve, flat against the variable condensers.

In addition to the two control knobs, the positions of which will be seen from Fig. 2, six small terminals are fixed along the front near one edge.

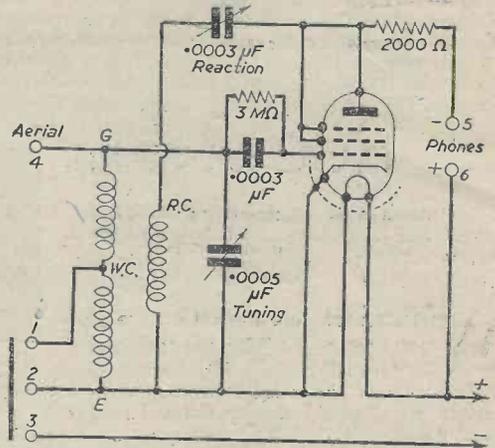


Fig. 1.—Circuit of the pocket receiver.

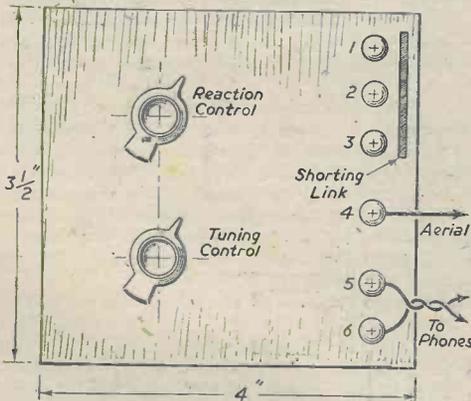


Fig. 2.—Layout of the panel.

Wiring Details

The three upper terminals serve as an on-off and wavechange switch in the simple manner as follows. When it is desired to listen, a connecting link, in the form of a 1in. length of copper wire or anything similar, is placed across the terminals. The set is then switched on for medium-wave operation. If long-wave reception is required, terminals 2 and 3 only are shorted.

It must be noted the valve is indirectly heated. Hence 15 or 20 seconds will elapse before it begins to function after switching on.

Using Phones

All connections are shown in Fig. 3. With phones with low internal capacity the 2,000-ohm resistor can be omitted without affecting results. Note that the valveholder connections shown are for the top of the holder itself, not for the

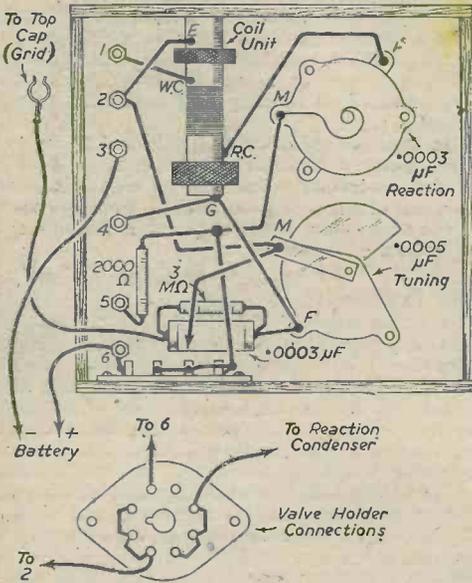


Fig. 3.—Internal arrangement of parts and wiring.

valve pins as viewed from the bottom of the valve.

Flexible leads about 4in. long, ending in clips, are used for battery connections. A piece of cardboard 3¼in. by 2¼in. placed against the condensers prevents any shorting to the battery tags.

With some coils it is possible that insufficient reaction may be obtained, particularly on long waves. If so, the number of turns on the reaction winding may be increased. Local stations will be received without reaction.

If the receiver is required for use in a locality where all that is desired may be received on the medium-wave band, construction may be simplified by using the Wearite "P" type coil, (PA2 or PA7). A fixed condenser could be included in the aerial lead and the primary used for reaction, the tapping and Terminal 1 being then omitted.

It should be unnecessary to point out that the receiver is intended mainly as a novelty, but that even so it is capable of surprising results under certain conditions. If a large outside aerial is employed, some difficulty is bound to be experienced on the grounds of selectivity, and therefore to sharpen up the tuning it may be found desirable to include a small variable condenser (one of the pre-set types will do) between the aerial lead and the aerial socket (No. 4) on the panel.

Recording Technique-2

This Article Outlines the Requirements of a Volume-indicating Device, and Describes in Particular the Use of Copper-oxide Rectifier Meters

By R. KEMSEY-BOURNE

WHEREVER possible the monitor speaker should be fed from its own power output stage, and the input to the monitor amplifier is bridged across the input to the main recording amplifier at a high-impedance point, or suitably transformer-coupled. Obviously the later in the main circuit that the monitor feed-point comes the better; it must be following the tone control or equaliser stages so that any changes to the frequency characteristic obtained by adjustments which are made will appear on the monitor.

The monitor amplifier must be as similar in design and performance to the main recording amplifier as possible, although it is not required to give as much power output. For example, if the main power output stage consists of PX25s in Class A push-pull with transformer phase-splitting, then the monitor might well be PX4s similarly aligned, giving less power but comparable quality. Such a system is shown in Fig. 2. The more nearly similar the main and monitor amplifiers are made, the closer to reality is the impression given by the monitor.

If it is not practicable to build a complete push-pull monitor amplifier, then use a single triode or pentode, always assuming that at the point of bridging there is sufficient voltage swing to give

satisfactory monitoring volume. The pentode has the advantage of greater sensitivity, although it will be necessary to fit a tone filter to correct as

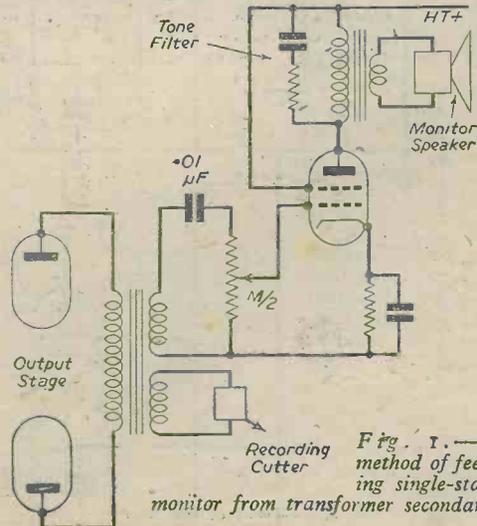


Fig. 1.—A method of feeding single-stage monitor from transformer secondary.

far as possible for the differences between single-ended pentode and push-pull triode (or pentode) outputs; filters as shown in Figs. 2 and 3 will help.

If more convenient, a single-stage monitor may be fed from a secondary winding on the output transformer, particularly a high-impedance secondary (500-2,000 ohms). Like the circuits of Figs. 2 and 3, the line-up of Fig. 1, operating in Class A, draws no grid current, no power, and thus cannot upset the main output stage or the impedance match between the primary and the secondary feeding the recorder. The monitor as shown may be shunted directly across secondaries having impedances of 500 ohms or greater, and will not affect the recording.

In general practice, audio monitoring of the recorded matter by means of headphones or loud-speaker will be used in conjunction with some form of volume indicator or power-level meter. The recordist thus has both qualitative and quantitative checks on what is fed to the cutter-head. The monitor speaker presents the necessary picture of balance, tone and subject matter at any time, and the volume indicator shows whether too little or too much audio power is being supplied, although it gives no idea of its range and quality.

Types of Indicator

The volume indicator (V.I.) may be one of two general types. It may be a pointer instrument, such as a milliammeter suitably connected, in which case the swing of a needle is followed as showing changes in power level, and this is the

most generally used type. Alternatively, it may be a visual device, such as a cathode-ray tube, a "magic eye," or a neon lamp, in which changes in level produce variations in the ordinate of a cathode-ray trace or in the shadow-angle of the "eye," and cause flashing and extinction of the neon tube.

Both types of indicator really show A.C. voltage across a particular load, and, of course, for a given load the power dissipation will be proportional to the square of the voltage across it. Strictly speaking, the square-law holds only for a load that is independent of frequency.

Pointer Instruments

The meter type of V.I. is the most generally applicable, especially for amateur and general professional uses. Any meter must draw a small amount of power from the circuit to which it is coupled, but if the meter is carefully chosen and properly connected this power can be made so small that it may safely be neglected. As we said above, our V.I. is to show A.C. voltage, so that what is required is an A.C. voltmeter sufficiently sensitive to draw virtually no power and with a rapid and even response over as wide an audio-frequency range as possible.

The moving-iron class of meter, although satisfactory for relatively large currents at low frequencies such as 50 cycles, is not sufficiently sensitive for reading small currents at higher frequencies. It usually draws too much current to act as a good voltmeter and has too high a

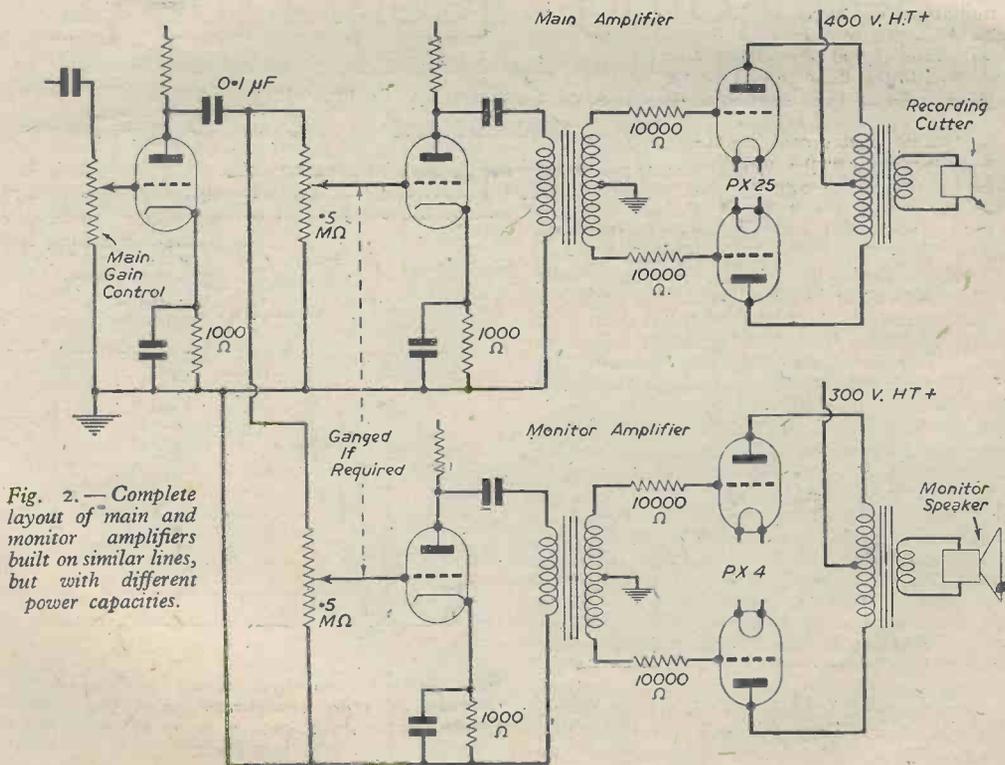


Fig. 2.— Complete layout of main and monitor amplifiers built on similar lines, but with different power capacities.

moment of inertia, so that it is not suitable for direct use as a V.I.

Thermocouple meters have excellent frequency characteristics but are in general insufficiently sensitive, since they also require relatively high currents for operation.

The simplest effective V.I. consists of a low-current moving-coil meter fed through a rectifier of some sort, and connected to the voltage source through an appropriate large resistance. The lower the full-scale D.C. current taken by the meter the better.

Instrument Rectifiers

Fig. 4 shows how a microammeter or milli-ammeter M is wired to a bridge-connected copper-oxide rectifier B. This type of rectifier is a minute version of the Westinghouse variety used for H.T. and L.T. supplies, and is designed for use with particular meters—500 microamps., 1 milli-amp., 5 milliamps., etc. The value of resistance R depends on the voltage range to be covered and the D.C. current taken by the meter for full-scale deflection. The meter itself must draw as little current as possible, down to 100 microamps., and preferably not more than 1 milliamp.; between these limits the value of R will lie between 10,000 and 1,000 ohms for each volt of the full-scale deflection.

There will be some voltage drop in the rectifier bridge itself, so that for a given A.C. voltage range resistance R will have a smaller value than the dropping-resistance would have for the same range of D.C. voltage. For example, to make a 0.1 milliammeter have a full-scale reading of 5 volts A.C., we require a total series resistance of 5,000 ohms (1,000 ohms/volt), but because the bridge contributes some resistance the value of R (Fig. 4) will be of the order of 4,000-4,500 ohms only.

Copper-oxide instrument rectifiers are cheap, and so at present are 0.1 milliammeters and even microammeters. This type of V.I. is recommended, since it is efficient and economic. The Universal Avominer, used on the 5 volt A.C. range, makes an effective indicator across low-impedances such as 15 ohm cutter-heads in spite of the fact that its resistance on this range is only 2,000 ohms; it would be still better if it drew less current. Use the most sensitive meter you can afford.

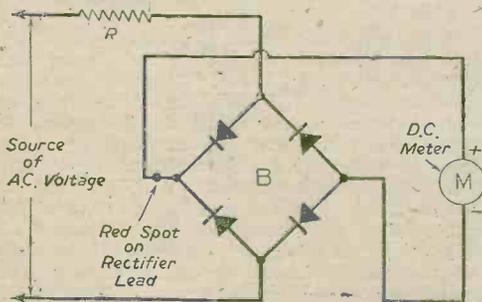


Fig. 4.—Copper-oxide rectifier enables D.C. milli-ammeter or microammeter to be used as a volume indicator.

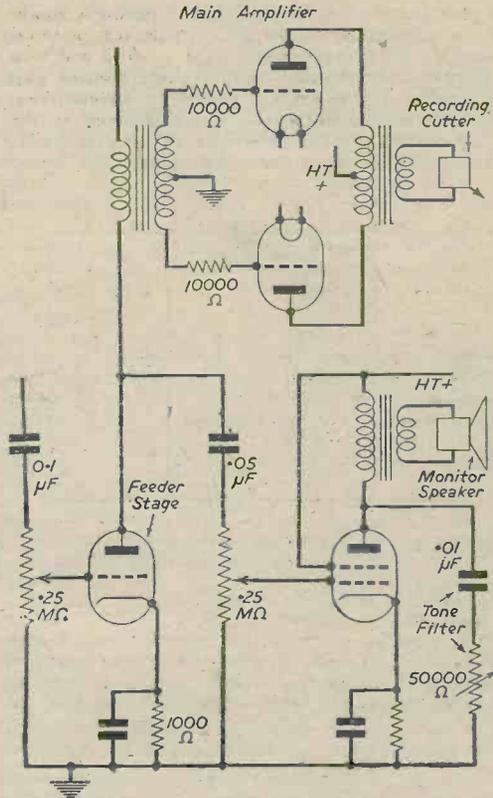


Fig. 3.—Pentode monitor stage fed from main recording amplifier, giving adequate sensitivity for speaker operation.

Properties of Rectifier Meters

Meters with copper-oxide rectification read the average amplitude of the A.C. wave. Overloads will be caused by the peak voltage exceeding the maximum permissible, so that the recordist works

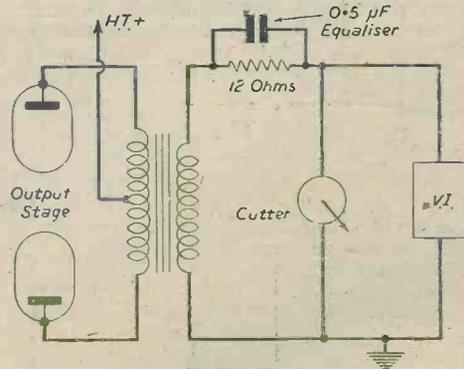


Fig. 5.—V.I. connected across low-impedance recorder, or other transformer-fed device. For 15-ohm cutter, bass equaliser is as shown; range of V.I. is 5 volts.

on past experience, knowing the handling capacity of his apparatus and making allowances as he controls the transmission.

Copper-oxide meters read slightly low at high frequencies. The reading drops by about 1 per cent. for each 1,000 cycles rise in frequency, due to by-passing by the electrostatic capacity of the rectifier. This effect, and the slight variation of

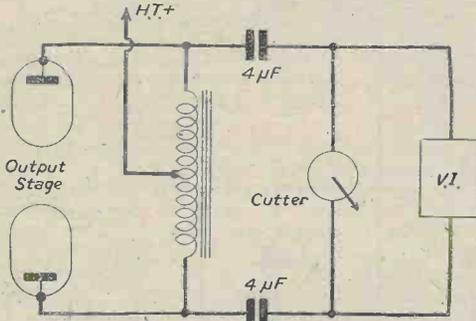


Fig. 6.—V.I. connected across high-impedance recorder, choke-fed via high-voltage paper condensers.

the rectifier's characteristics with temperature, are negligible in everyday practice.

Again, when a meter has been calibrated with sinusoidal A.C., the readings will not hold if harmonics are present. Such considerations as these are neglected, since the V.I. is used rather like a speedometer—to prevent the safe limit being exceeded and warn us when we are cutting it rather fine.

Other Types of Rectifier

Silicon and germanium crystal rectifiers are available for use in meter circuits, but are more used in R.F. than in A.F. circuits, since their frequency response is excellent. They may be used in bridge connection for full-wave rectification, but cost more than the normal instrument type.

Valve rectification will be referred to later; it has the advantage of practically infinite input impedance.

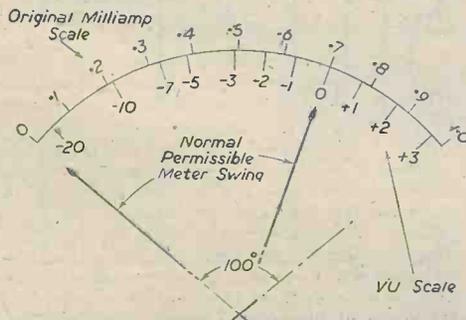


Fig. 8.—Typical appearance of VU-scale, showing angle of swing for the meter needle. Needle should overshoot only rarely.

Connecting the Indicator

The obvious place to wire the V.I. is directly across the cutter-head leads, where it will give most information. The effect on recording performance of a high-resistance meter is not noticeable. Putting an A.C. meter across the primary of the output stage would involve either blocking the flow of D.C. from the H.T. supply or balancing it out.

Figs. 5 and 6 show volume indicators of the type of Fig. 1 connected across low and high

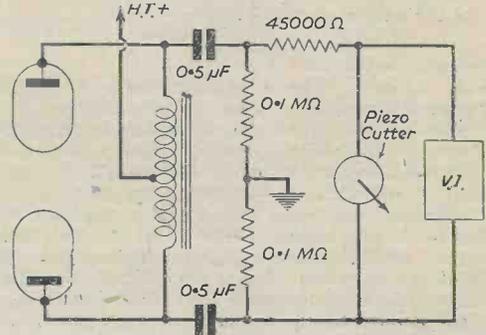


Fig. 7.—Circuit for piezo-electric recorder cutting constant-velocity characteristic, with turnover at 500 cycles. Overall range of V.I. is 150 volts; average peaks should be recorded at about 100 volts level.

impedance recording heads, and Fig. 7 illustrates the method for a piezo-electric cutter. Fig. 5 gives A.C. voltage ranges for cutters of different

Recorder-head impedance (ohms)	4	7.5	15	500	2,000	5,000
A.C. Voltage range of V.I.	3	4	5	35	65	100
Total resistance for 0.1 mA. meter (ohms)	3,000	4,000	5,000	35,000	65,000	100,000
Total resistance for 500 μA meter (ohms)	6,000	8,000	10,000	70,000	130,000	200,000

A.C. voltage ranges for recording heads of different impedances.

impedances from 4 to 5,000 ohms, and the total resistance values for each range. The total resistances tabled include the rectifier.

Using the V.I.

Arrange your meter so that a normal peak voltage for the cutter-head corresponds to 70 per cent. of the full-scale deflection. Then on sustained high-volume levels and on normal peaks keep the meter needle at or just below this deflection. It may, of course, flick past on transients.

Commercial indicators have standard ballistic characteristics, with an input impedance of the order of 7,500 ohms for shunting on 500 or 600 ohm lines. They are basically copper-oxide voltmeters of suitable range. Since a V.I. indicates a mean level over a short period rather than an actual instantaneous power level, it is calibrated not in decibels but in "volume units" (VU), although VU readings correspond with decibel levels above one milliwatt in the case of steady sinusoidal voltages.



ON YOUR WAVELENGTH

By THERMION

The Radio Critic and the Brains Trust

I WAS interested in listening to the Radio Critic recently and to hear his views on the Brains Trust, which coincides with those which I have expressed so often. He thinks, as I do, that each session needs a different group of people, or alternatively that there should be an expert available on almost every subject. I see that Joad has been replaced by Bertrand Russell. I know him to be a clever mathematician, but I do not think that he has the necessary knowledge and experience to deal with the type of questions submitted to the Brains Trust. I write in the presumption that, unlike myself, many people like the Brains Trust. I am all in favour of a properly constituted Brains Trust. I do not like an item foisted on to listeners as a Brains Trust which turns out to be a third-rate music hall act which would get the "bird" even in the remotest districts of this country.

This programme has received undue publicity in view of its very poor show, and I do not accord it any marks, as an examiner, for the replies given to what I consider to be examination questions.

It does not concern me that Joad is no longer in the Brains Trust, nor would it worry me if the remainder of them were changed. If there is a need for a Brains Trust let it be a real Brains Trust and not an exhibition of tergiversatory circumlocution interlarded with an exuberance of verbosity which some of them may find effective in disarming too shrewd a criticism, or in cloaking a lack of knowledge of the subject.

I had a letter from one of my readers Mr. P. J. Rust, of Bournemouth, who thoroughly agrees with my views. He says that in the old days though mistakes were made, the discussions were interesting and informative. Now we are asked to listen to a discussion on the inane question, which produced the expected inane answers, of "What is love at first sight?" Of course, no one could ever be right or wrong on such a question. I wonder if any member of the Brains Trust could give a succinct answer to the question: "What is the square root of minus one?"

I wonder whether the Brains Trust could give a clear answer to the question: "What are the principles of atomic energy?" or "What are the principles of jet propulsion?" or "Why is the sky blue?" or "Why is water wet?" I doubt it very much.

As one who can lay claim to reasonable scientific knowledge, who is an engineer by education and training and a journalist by accident, I have been amazed at the deplorable display of ignorance evinced by the Brains Trust. I can only conclude that those responsible for the programme select questions of the type "What is Love?" so that the Brains Trust can never be right or never

wrong. I do not believe that all of the questions which are submitted are of this type. On the face of it it would seem that there is some element of selection about these questions.

As the B.B.C.'s own Radio Critic is so critical of the Brains Trust, I ask the B.B.C. to remodel this programme, or drop it in its present form altogether. I would ask members of the Brains Trust to remember that they are not actors:

Empty shells from 8 till 10,
Filled with the wit of other men.

Twenty Questions

Mr. Rust does not agree with me on the subject of "Twenty Questions." He finds it entertaining, and he does not think that the listening public would prefer a different set of "experts," each time. I have put that word "experts" in quotation marks deliberately because I do not think that Anona Winn, Jack Train, Richard Dimbleby or any other member of this music hall turn would claim to be experts. It all depends what you mean by "experts" I suppose.

But as the same group of people are expected to be able to divine the answer on a wide variety of topics they would need to have an encyclopaedic knowledge and to be omnifarious readers. I do not think any of them would claim to be either. In any case my main objection was that some of them should be asked to "pipe" down a bit and not to regard it as *their own* programme.

Here is another letter, this time from C. Boswell, of Smethwick. He thinks that my article was written to get readers busy with pen and paper! "I do not think the B.B.C. programmes are by any means good, but surely to criticise them in the way you do this month is without reason. 'It gets more than a little boring at the commencement of most objects to hear Anona bobbing up with the first question. I suppose this programme is amusing to children, but I do not think in general that parlour games are suitable for radio. If I am wrong about that, I certainly am right in stating that the listening public would prefer to hear a different set of experts each time.'"

My correspondent does not think that I could be wrong about one thing and right about another! This indicates that his logic is at fault. I know from readers' letters that the majority of them would prefer to hear a different set of voices each time. The "experts" get used to the questionmaster. They do not come strange to the studio. They are able to discern from the twinkle in his eye or the inflection of his voice a point which should count as a question. In any case I reassert that no four people, whether it be Brains Trust or "experts," are qualified week in and week out to give sensible and accurate answers to a wide variety of topics.

Practical P.A. Working-1

In This Introductory Article R. SELBY Discusses the Main Requirements of Public Address Equipment

THE uses of public address equipment up to 1939 were already very wide, but the impetus given by war conditions, when almost every factory was fitted with an installation to provide "Music While You Work," announcements, warnings, etc., and the extensive use of loudspeaker vans for many purposes, has caused the general acceptance of P.A. in some form or another as a *sine qua non* for almost any occasion where people are gathered together even in comparatively small numbers.

The term "Public Address" is not altogether a happy one, embracing as it does anything from a small gramophone amplifier suitable for private parties up to a speech and music installation with an A.F. output of a kilowatt or more, but is now generally accepted, at any rate by technicians.

A large volume could be written on the many technical and practical aspects, but in this series of articles, based on a good many years' experience, the writer hopes to touch upon some of the more important points for the benefit of readers who are interested in the subject.

At the outset it should be made clear to those who are contemplating P.A. from the business angle that it involves a fairly heavy capital expenditure on equipment. It is, as the writer has performed found by hard experience, possible to effect many economies by means of ingenuity and hard work, but the standard of performance required to-day, now that mere novelty has worn off, is so high that it is useless to attempt it with insufficient loudspeakers, poor quality microphones, or amplifiers having too low an output. Moreover, every P.A. job varies in some way or another, and experience counts for a good deal in obtaining the best results.

There are many ways in which types of P.A. work could be classified, but probably the broad division between indoor and outdoor jobs will suffice. In both cases, of course, the aim is to obtain as faithful reproduction as possible, whether it be speech, live music, or gramophone records, and to make that reproduction clearly audible to every person present, but there are considerable differences in the technique and equipment required. These may be summarised as follows:

Indoor Work

Amplifiers, particularly if for speech only, need not be very large, but must be as distortionless as possible, and may almost invariably be mains operated.

The highest quality microphones obtainable are necessary.

Generally, cabinet or baffle speakers will be required.

Outdoor Work

(With which may also be grouped many factory installations.)

Amplifiers must be of much higher power, often

capable of operation from car batteries, but complete freedom from frequency and harmonic distortion is not quite so vital, although naturally desirable.

Microphones. Here again the highest quality is not quite so essential.

Loudspeakers will invariably be of the horn or directional baffle type.

Various accessories such as loudspeaker stands, extra cable, ladders, remote control units, etc., may be required.

It is now proposed to deal with some of these points in some detail.

For the majority of indoor jobs in halls a 15-watt amplifier is sufficient, but it is essential that it have as nearly as possible a straight-line frequency characteristic and that its apparent output impedance be as low as possible. The obvious reason for these requirements is to obtain good quality reproduction. But there is an even more important point. The bugbear of P.A. work, particularly indoors, is acoustic feedback, also known as howling and singing. As the reader probably knows, this is due to the fact that when the amplifier gain exceeds a certain critical point the sound coming from the loudspeakers reaches the microphone with sufficient strength to be picked up and re-amplified, thus quickly building up into a sustained ear-splitting howl. The volume of reproduced sound is thus limited to something below the howling point. This effect is inevitable, but obviously one minimises it by careful positioning of microphone and speakers. If, however, the amplifier, loudspeakers or microphone have any resonances or peaks in their frequency response characteristics, it is clear that the overall amplification of the whole chain is greater at that frequency. Consequently the gain of the amplifier must be reduced sufficiently to prevent howling at this peak frequency, with a consequent unwanted reduction in amplification over the remainder of the audible band. If the peaks can be eliminated by good design, a much greater overall amplification can be obtained before the howling point is reached. It might perhaps be thought that this is rather an academic point, but in the writer's experience it is of vital importance—much more so than the disposition of microphone and speakers. The reason for specifying a low apparent output impedance in the amplifier (obtainable by the use of heavy negative feedback) is to assist in damping loudspeaker resonances, with the same object in view:

A Fallacy

This seems an appropriate point at which to expose a fallacy often put forward by the layman, viz., that a large amplifier will give better results than a small one. As far as indoor situations are concerned, if the microphone is within earshot of the loudspeakers, the volume of sound attainable is always limited by the acoustic feedback factor. Consequently, if, in some given situations, the

limit of sound obtained before howling commences is equivalent to, say, 8 watts delivered to the speakers, there is no point in using a 30 watt amplifier. A 10- or 15-watt outfit will do the job equally well with a margin of safety, and will be lighter to handle. As mentioned previously, 15 watts output is sufficient for the majority of indoor work even if gramophone record amplification is required. Naturally, this remark does not apply to installations for factories or Olympia exhibitions.

Continuing to deal with amplifiers, it is hardly necessary to add that reliability is of paramount importance. It is principally a matter of taste (and cash available) whether one builds the amplifiers or buys them ready made. If they are purchased, it is advisable to stick to a reputable make, and to make sure that they are designed to operate with the particular type and make of microphone and pickup which one intends to use. Ex-Government surplus amplifiers need particularly careful investigation on this point. Other points to watch are the degree of convenience (or otherwise) provided for

making speaker, microphone, pickup, mains, etc., connections, and convenience of controls, switching and voltage adjustment, also portability, range of output tappings provided, and availability of spare valves.

The same points must also be considered when building one's own equipment, and in addition it must be borne in mind that not only is a good circuit design called for but also the highest quality components and workmanship. Resistors, condensers, etc., must have an ample margin of safety in their ratings, wiring must be sound and well insulated, and components should not be suspended in the wiring. Adequate ventilation is essential. It must be remembered always that P.A. equipment receives much rougher handling during transport and installation than a domestic outfit, and that the consequences of a breakdown are infinitely more serious.

In the next article some practical points in P.A. amplifier design will be dealt with.

Technical Notes-2

Our Contributor "DYNATRON," Discusses Feedback and Transmitter Problems

FOR the following experiment you should procure two coils and condensers which will tune over approximately the same frequency-range, and connect-up to a triode of moderately high amplification factor as in Fig. 4a.

At first, leave everything unscreened. You will have an excellent oscillator over most of the tuning range. If the coils are coupled fairly closely, this oscillation can be of a complicated kind, arising from magnetic feedback from anode to grid circuits, together with electrostatic feedback via the valve inter-electrode capacity C_{ag} . Different considerations apply to the phase of these two types of feedback, so it is possible you will observe shrieks or whistles suggestive of an audio beat between two different high frequencies.

All right, let us eliminate one form of coupling. Let us keep the coils well apart and enclose them in earthed screening-cans, as indicated by the dotted outlines in 4a. There will now be little or no magnetic feedback.

But oscillation persists almost as well as before? It will have altered in character; probably the shrill whistle will have disappeared, giving a more pure single oscillation which occurs over only part of the tuning-range. Still, there is an unmistakable self-oscillation, as may be observed, for example, by varying the tuning near to a fairly sensitive receiver.

Of course, the cause of self-oscillation is "reaction" between anode and grid circuits—here, via the minute internal capacitance of $5\mu\mu\text{F}$. or so existing between the anode and grid

electrodes, exactly as if a small condenser of this value "tied" anode to grid.

As it is an "internal" capacitance, no ordinary measures outside the valve can accomplish much in the way of remedy. To demonstrate what was once done, you might try shunting the anode-and/or grid-tuned circuits with resistances to "damp" them, starting, say, with 250,000 ohms and working downwards until oscillation ceases. You will then have a measure of "stability" all right, but what an H.F. amplifier! It was by no means uncommon to find overall gain improved by dispensing with the "H.F. stage."

Balancing-out the Feedback

Then came a real remedy, even though very

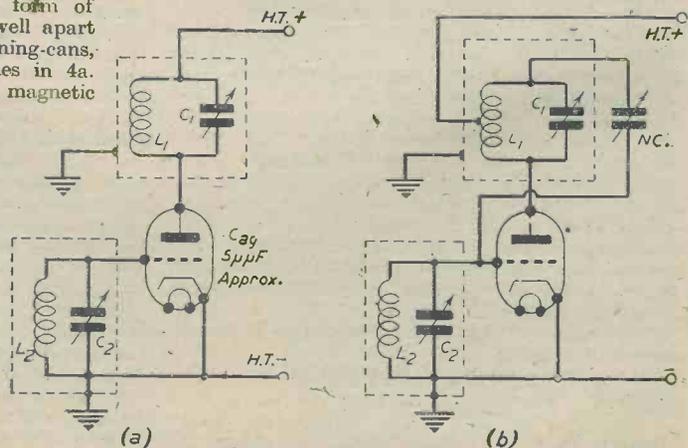


Fig. 4. The "H.F. amplifier," Fig. 3, will make a good T.A.T.G. oscillator, as in (a); (b) shows a simple method of neutralising.

difficult to set over a wide range of frequencies.

Since the advent of the screening-grid which reduced C_{ag} to something like $.002 \mu\text{F}$ or less, it seems amazing that it took so long to develop what now look like the obvious remedies. Indeed, if it took many years to realise fully that the valve inter-electrode capacitance was the culprit, and it was left for Miller, with his complicated equations, to develop the complete generalised theory of the triode network—and, believe me, it is not "simple"!

A capacitance of $5 \mu\text{F}$ does seem exceedingly small, but if you work out its A.C. reactance at

tion of the coupling via C_{ag} can be observed in H.F. ammeters, etc.

In a modulated Class C stage it is most important to ensure that no feedback occurs, which, if at 90 deg. to the existing drive, will result in *phase-modulation* on top of the amplitude modulation. There are other complications if a power stage is not properly balanced, such as difficulties in tuning the anode circuit correctly owing to a combination of H.F. output from the valve and "forward feed" via the inter-electrode capacitance.

Short-wave experimenters will be familiar with several methods of "neuting."

In general, we may say that with the H.T. supply switched-off, Fig. 5a, any adjustments made to the anode tuning will affect grid-circuit conditions via the coupling provided by C_{ag} , if the stage is not properly neutralised. The two tuned circuits $L1C1$ and $L2C2$ form a capacitively-coupled network as shown in 5b. The usual indication used is a change in the reading of a grid-current meter, mA., as the anode tuning is varied through resonance.

If correctly balanced, any adjustments in the anode circuit (with H.T. off) should have no effect whatever on the grid-current.

Another interesting method which involves switching-off the H.T. is shown in 5a. Even though there may be little or no extraneous couplings between $L1$ and $L2$, a small reading can be observed in the closed-circuit H.F. ammeter A, due to energy being coupled from the driving source at the grid via C_{ag} , i.e., "forward feed" through the inter-electrode capacitance.

Often, the closed-circuit ammeter is too insensitive to give any readable indication at the small amount of coupling which exists, and either a more sensitive thermo-ammeter may be inserted, or—what is generally sufficient—a flash-lamp bulb may be connected across two or three turns of the anode coil.

When the anode tuned circuit is adjusted to resonance, the lamp will light to maximum brilliance, then the neutralising condenser is adjusted until the bulb is extinguished. If NC is turned beyond this point, the bulb will come up again, the correct setting being about midway. For more exact balancing, a sensitive thermo-ammeter should be employed.

A "hot" method of neutralising, i.e., with all power supplies, including the H.T., "on," makes use of the fact that if, in addition to the normal output of the valve, energy is being supplied via C_{ag} , peculiar results will be observed in the anode tuning.

Normally, an H.F. power stage is tuned for *minimum* H.T. feed, and this will coincide with *maximum* current registered by the closed-circuit thermo-ammeter. But if there should be any forward feed to complicate matters, "minimum" and "maximum" indications on these two meters will not coincide—minimum D.C. will occur at a slightly different condenser setting from maximum closed-circuit amperes.

Hence by closely observing the meters in a

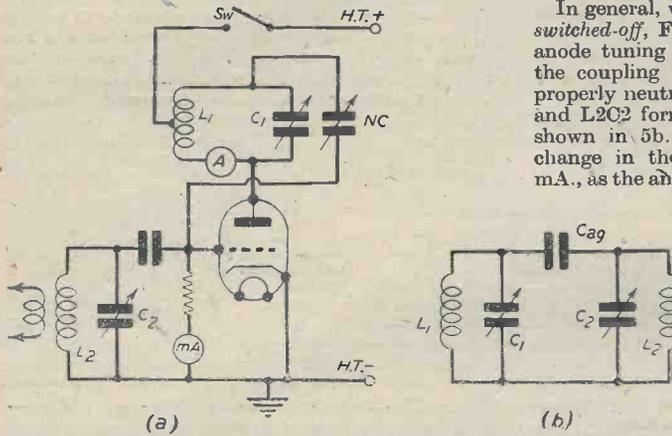


Fig. 5. Discussing methods of neutralising a triode transmitting stage: (b) shows the capacitive coupling between anode- and grid-tuned circuits.

1,000 kc/s., you will find it comes to about 32,000 ohms. That is quite a large degree of reactive coupling from anode to grid. At 30 metres (10 Mc/s.), it drops to 3,200 ohms!

Anyway, if you can get hold of a small single-vane neutralising condenser of about the same order of capacitance as C_{ag} ($5 \mu\text{F}$), perhaps you will derive a little amusement trying out the balancing method shown in 4b.

Adjust NC until oscillation ceases at, say, one fixed setting of the condensers. It will probably start again at other settings. It is not difficult to neutralise a transmitting valve working at one fixed frequency; but receivers were a rather different story with a waveband covering M.W. and L.W.

No doubt you have read of the "see-saw" principle used to explain balancing. H.F. voltage gets back to the grid via C_{ag} . Because the centre-point of the anode coil is made "earthy," by tapping-down + H.T., the H.F. voltage feed back from the top end of the coil via NC will be diametrically opposite to that fed back from the anode end via C_{ag} . The two voltages will also be exactly equal when the neutralising condenser is adjusted to the right value, hence the resultant feedback will be nil.

"Ancient history," perhaps, but studying important radio principles is always of value.

Interesting Facts About Transmitter Neutralising

Where sufficient power is available in the grid circuit, as in transmitter drives, a direct demonstra-

driven stage, whilst carefully varying the anode tuning over a few degrees, it is easy to test under actual working conditions whether the stage is properly neutralised or not.

Tuning Class C Stages

Reference to what was said above about anode tuning having no effect upon the *grid-current* of a properly neutralised stage, observe carefully that this will be far from true in normal conditions with the H.T. "on."

Even if perfectly neutralised, any change in the anode tuning will immediately affect the grid-current. In fact, one good way of tuning a Class C stage is to adjust the anode circuit for *maximum grid-current*—note carefully, not minimum, as for the anode meter.

At a transmitter with which I have been associated, I have had a merry old-argument about this, or, rather, whether the grid-current does change if the

anode volts are swinging at modulation frequencies—not necessarily implying any observable change in the *mean grid-current* registered by a meter.

We will not go into that now. But why should any alteration in the tuning of the *anode* circuit cause the *grid-current* to change at all, if a stage is properly neutralised? Neutralising implies there is no "coupling" whatever between the two circuits.

No, there is no coupling—magnetic or electrostatic. But the total space current divides between anode and grid, the amounts depending upon the relative + potentials of these electrodes. The grid is driven a certain amount positive, whilst the anode has a certain *minimum voltage* at the instant when peak voltage occurs across the tank load.

The latter will be at a maximum when the tank has maximum impedance, at resonance, hence the volts on the anode will become an absolute minimum, whilst the positive grid potential will cause a few more electrons to be diverted in that direction. Hence "I_g" increases.

Test Instrument Design-6

In Concluding the Series, P. E. TOOKE This Month Discusses Photographic Work With an Oscillograph

ALTHOUGH not in strict keeping with the rest of these articles, it is very useful to have some knowledge of using a camera to record permanently the oscillograms seen on a "scope."

For some work, examining transients, etc., where the speed of the trace is very high a photographic record is the only means of checking it at leisure.


Assuming that you have a 'scope at your disposal, the rest of the apparatus need not be expensive. There are two ways of recording. The first and cheapest is by using the time-base of the 'scope to form the picture and then photographing the tube face. Or, by using the spot alone, to produce the trace vertically and recording by means of a moving film.

Of course, the latter is more expensive, and not all work can be done by either method. Some entail one way, and no other way will do.

For the amateur who just wants to experiment with photographing traces of wave form using the time-base, the least expensive is, of course, the best, so we will start off with this method.

A simple set-up can use the ordinary box camera. If it has a "portrait" lens so much the better; if not you will have to fix it in this way. Purchase a spectacle lens with about a 12in. focal length. The lenses you can buy at the cheap stores are just the thing; you will find that they are marked with a number. This number is their focal length in inches. Mount it over the lens—adhesive tape is ideal, only be sure it does not obstruct the lens in any way. When this is mounted fix the camera firmly in some way in front of the 'scope, with the distance from the screen to the lens equal to the focal length. This should be measured and not left to chance. Also line the camera up so that it is pointing fully at the screen. Do not rely on the viewfinder, as it is not accurate at this short range.

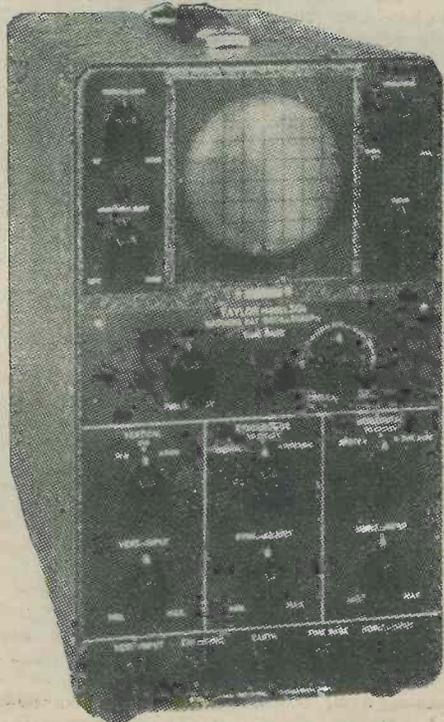If the 'scope has a blue trace so much the better. A green one will do, however, although it will need a slightly longer exposure.



A typical commercial oscilloscope for high-class work. The Taylor model 30A.

Load the camera in the normal manner with, preferably, orthochromatic film, not panchromatic. Then produce the trace you want to photograph and steady it as much as possible. Focus it as fine as it will go, with the brilliancy a little higher than you would normally have it for visual work. When everything is set and steady just give it a time exposure as quickly as possible; this is about a second's exposure. If your camera has shutter speeds fitted so much the better; if not, you must flick the shutter control up and down with the time knob out. After a few attempts you will be able to get results quite easily and need not worry about not catching a particular trace.

It is much more interesting and better to develop your own film, as then you can control the process to give the contrast you require. Developing is quite cheap and easy. Just a couple of dishes and a packet of developer and fixing salts. Use a "contact" developer and follow instructions on the bottle. There is hardly anything that can go wrong, as you only have an exposed trace in one tone, with no semi-tones to worry about as in a snapshot.

With the method just described results can be obtained which are comparable with the results or output of a commercial camera, and permanent records are invaluable for keeping for future reference.

Now we come to the recording of transients, etc., with a moving film. Unfortunately there are very few short cuts for cheapness in this way of recording. A reliable camera and a motor to turn it are needed. If a commercial one is bought it runs out quite expensive, and unless you are exceptionally handy with tools there is not much hope of constructing one.

If one is not worried too much about expense,

a good commercial type of camera should be obtained, such as the Cossor model 427. It is specially designed for use with the Cossor Single or Double Beam Oscilloscope and will take single shots of the screen or continuous moving film records.

For moving film work a motor is needed to turn the shaft which operates the film. The makers state 1/40 h.p. is sufficient, but I have found that a 1/10 h.p. is really needed to cover all speeds. A series of pulleys can be made so that different speeds for different traces are obtainable. With this particular type of camera speeds of up to 20ft. per second are possible. The average speed for normal recording is, however, about 2ft. per second. A paper film or normal 35 mm. negative fits the camera. The paper is cheapest and best, although if more than one copy of the record is wanted, film will have to be used. This runs out very expensive as 25ft. of film costs approximately £2.

Operation is quite simple. The 'scope is focused and the brilliancy set, then the camera mounted and loaded, making sure that the shutter is open, the signal to be recorded is fed into the 'scope, and the camera motor started up. When the desired length of film has run through, the shutter is closed and the motor stopped. The cassette containing the film can be taken out and processed right away if wanted.

The processing of lengths of film is rather too much except for anyone with a proper darkroom. A frame is needed on which to wind the film, and large tanks to take the frame. Processing by a photographic dealer is the best way and the cost is not very high. In the long run it is really the cheapest except for a large firm using the camera all day.

Self-priming Battery

THE Exide self-priming battery was developed during the war, for working with wireless transmitters and receivers for emergency use on ships' lifeboats. Batteries for such duties may be called upon at a moment's notice and they must, therefore, be available for service at all times. Exide self-priming batteries require no maintenance or attention while they are in storage and yet they are capable of supplying current immediately on priming without the necessity for an initial charge.

Each battery consists of a number of individual cells, either cemented together or assembled in a wooden crate, depending on the type of battery. The cells are made up with dry charged plates assembled in a hermetically sealed compartment, with the electrolyte in a separate compartment, and, as the electrolyte is not in contact with the plates, the battery may be stored for long periods without losing its charge.

When the battery is required for use, it is necessary to punch through the seals of the acid compartments, thus giving the electrolyte access to the plates. The battery may then be discharged within a few minutes without any previous initial charge being necessary. Subsequent cycles of discharge and charge may be obtained as required by recharging the battery in the normal manner.

A. F. Measurement Service

A SERVICE has been developed for the purpose of giving comprehensive performance data, in a standardised form, on specimen amplifiers submitted for the duration of the test. At present the service can supply performance data on complete amplifiers as listed, or on the audio-frequency section of radios or radiograms. It is hoped later to extend the service to cover a wider field of A.F. apparatus, including microphones, loudspeakers, pick-ups, and to perform other electro-acoustical measurements.

Form of Results

The data is supplied in a form most suited to its nature, normally in one of three ways, graphically, numerically or photographically, that is, a photograph of an oscillogram.


A short note on the interpretation of the test accompanies each result, also a block diagram of the apparatus used, any formulae, an accuracy estimation based on all possible determinate and indeterminate errors in accordance with standard laboratory practice, and other information concerning conditions of test. Full details of the service, which, at the moment, is for manufacturers only, may be obtained from A. E. Cawkell, 7, Victory Arcade, The Broadway, Southall.



Whatever your soldering job, in your home or workshop, you will prefer to use Ersin Multicore Solder. No extra flux is required. Multicore is the simple and precision method of making sound soldered joints for all household purposes. Just apply it simultaneously with the soldering iron; the three cores automatically provide correct proportions of flux to solder.

6^{d.}
CARTON
Shown above

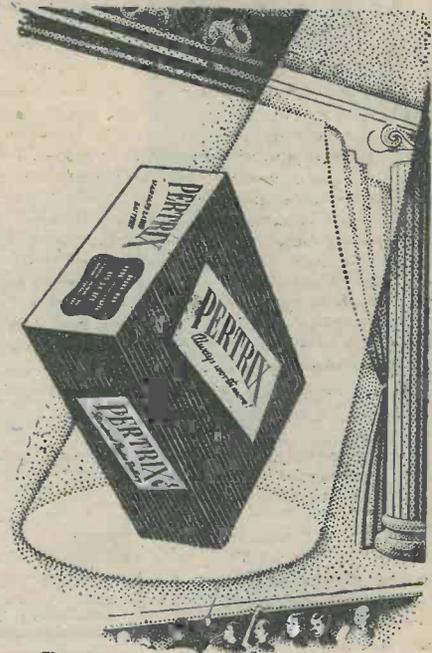WORKSHOP SIZES, 4/10 - 6/9 each.
MULTICORE SOLDERS LTD.
Mellier House, Albemarle Street, LONDON, W.1
Tel.: REGent 1411



No 'Noises off'


PERTRIX RADIO BATTERIES, in the red and yellow pack, are now firmly established in the post-war market. One reason — a Pertrix battery supplies power and nothing else. No mush or crackle to interfere with good listening — the result of a battery doing its work quietly, efficiently and unobtrusively. What's more it goes on doing it for a long time. Stick to Pertrix.

HOLSUN BATTERIES LIMITED
157 Victoria Street, London, S.W.1.

CELESTION

The quality of reproduction secured from Celestion Speakers greatly increases the pleasure of radio in the home.

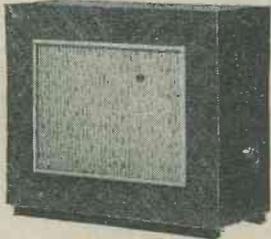The model illustrated has an attractively designed Cabinet with a special mahogany finish; it employs an 8in. speaker of high sensitivity and excellent response. It is fitted with a volume control and is one of the finest 8in. extension speakers available.



STANDARD 8 CABINET MODEL

Mahogany finish.

Size: Height 10" Width 12" Depth 5" **PRICE £3: 18: 0**

Price with Universal Transformer £4: 4: 0

Chassis Model CT107 (as used in above Cabinet Model), peak power capacity 4 watts. Price less transformer £1: 17: 6

(Suitable for outputs 1-5 ohms)
Price with Universal transformer... £2: 3: 6
(Suitable for all Receivers)

ALL CELESTION CABINET AND CHASSIS MODELS CAN BE SUPPLIED THROUGH YOUR LOCAL DEALER.

CELESTION LIMITED
KINGSTON-ON-THAMES, SURREY.



Interesting New Components

AVAILABLE AT WEBB'S

B.T.H. "SILICON" CRYSTAL DETECTORS

Type CS7A, the most satisfactory permanent Crystal Detector yet devised, especially recommended for broadcast crystal receivers. Type CS7A, price 7/6. Type CS2C—similar to the CS7A, but will operate at broadcast and V.H.F. frequencies. Type CS2C, price 9/6.

B.T.H. "GERMANIUM" CRYSTAL RECTIFIER

Type CGIC, similar, but improved pattern of U.S.A. type IN34. Has many uses for field-strength meters and radio detection in general. Recommended as broadcast detector, with preliminary R.F. amplification. Price, 11/3.

Postage and Packing 6d. each on all above Crystals.

BEAM AERIAL LUBRICANT

We are U.K. distributors for famous Victor Rowe Graphite Cup Grease, especially adapted for slow-running mechanisms such as beam aerial bearings. Per 1lb. tin, 4/-.

BURGOYNE INDUCTION SOLDERING GUN

The Soldering Iron of the future! Takes only 7 seconds to reach operating temperature. Why waste time waiting 10 minutes for your iron to get hot? A scientific instrument of proven design, operates from A.C. mains only, consumption 90 watts. Price, 14/-.

PRECISION FIXED CONDENSER

A useful component, with an accuracy of ± 1 per cent. Silver mica. .01 mfd. Working voltage 350 volts. Price 2/6

WEBB'S RADIO, 14, SOHO STREET, OXFORD STREET, LONDON, W.1

Note our SHOP HOURS:

9 a.m. to 5.30 p.m. Sats. 9 a.m. to 1 p.m. Telephone: GERRARD 2089

NEW! PRESS-BUTTON COIL PACK!


GRAM. L.M.S.

Something exciting! Something new! The famous 30 Coil Pack now designed for press-button switching. Used to modernise existing receivers. Smart in appearance, simple and convenient in use, and just as efficient as ever.

THE P.B.30 COIL PACK

4 Buttons select 3 wavebands plus Gram. High Q coils in Superhet circuit, 465 kc/s. I.F. Fully aligned and gain tested. Pick-up can be permanently connected. Size 4 1/2 in. x 4 1/2 in. x 2 in. deep. NO PURCHASE TAX. Trade enquiries invited. Price 58/3

Send stamp for latest list P.1

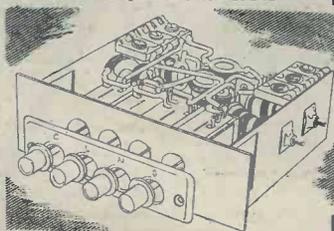


LONDON TELEVISION CO. LTD., 694, LEA BRIDGE ROAD, LONDON, E.10. Phone: LEY 4380.

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE
KING EDWARD AVE., AYLESBURY.

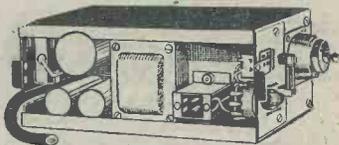Post in unsealed envelope 1d. postage. Please send me free details of your Home-Study Mathematics and Radio Courses.
NAME
ADDRESS
P. 91.



Electronic Laboratories U. S. A. 2-VOLT VIBRATOR PACKS

Complete with 2 Willard 2 v. 20 amp. accumulators in container for attachment to unit. The whole in transit case at the low figure of 87/6 (carr. and packing 5/-). OR VIBRATOR PACK ONLY, 52/6 (carr. and packing, 2/6). SPARES AVAILABLE: 2 2v. 20 amp. accumulators, 15/- per pair. Vibrators, 2 v. synch., 9/6. Fuses, 6d. Charging cables, 2/6. Instruction books, 3/6. These fine units were designed for the famous Canadian 50 Transceiver "Walkie-Talkie." Specification: Output, 90 v. or 180 v. 35 mA. H.T. 1.5 v. L.T. Provision for 21 v. G.B. Battery in pack. Size of vibrator unit 9 x 5 x 3 1/2 in. Provision for battery charging.



HEADLAMP SETS

This is one of those items that has universal appeal. It will fit around your forehead, enabling you to keep both hands free for any job required. The ideal prerequisite for car or cycle owner, serviceman, and for your den. Keep one with you always. Only 9/11. complete with battery box, leads, bulb and clips. (Takes standard 4.5 v. battery.)

M.O.S. SPECIAL!

A specially assembled kit for the benefit of all radio enthusiasts:—

- The kit comprises the following brand new equipment:—
- 1 Morse key.
- 1 pr. S.G. Brown or Multitone high resistance phones.
- 1 pr. S.G. Brown low resistance phones.
- 1 carbon hand microphone.
- 1 A.C./D.C. power pack to operate on any mains supply. Will give sufficient output for superhet receiver. As designed for the MCRL. The KIT FOR 35/- includes carriage and packing, 3/6.
- 80-WATT ROTARY CONVERTERS**
- A unit designed to operate from a 24 v. battery supply and to provide 230 v. 50 c/s single phase A.C. The input is coupled to unit via leads and plugs supplied. The output connections are taken to a 3-pin socket, and a control switch is included in the circuit. Brand new and unused. Only 60/- (carriage and packing, 5/-).
- SPRAGUE CONDENSERS**
- The finest tubular aluminium condenser money can buy! .01 mfd. 1,000 v. D.C. working. 4/- dozen. .1 mfd 350 v. D.C. working. 5/- dozen. 10 per cent. discount for gross lots.

Have you had your current issue of the M.O.S. Newsletter? Send 6d. for copy.

M.O.S. MAIL ORDER SUPPLY CO., Dept. PW 3 ROBERT ST. HAMSTEAD ROAD LONDON, N.W.1 Callers to 24, New Road, E.1 STEpney Green 2760 - 3906

A.C./D.C. Circuits-2

Dial Light Arrangements, and "Battery-mains" Working are Described This Month

By W. J. DELANEY (G2FMY)

LAST month we discussed the main features of the A.C./D.C. type of receiver and ended by emphasising the necessity for remembering that the chassis and everything connected to it are "live." A point sometimes overlooked in this connection is that although a fixed condenser may be inserted between the chassis and the actual earth connection the aerial tuning coil is connected to

lead with a shunt to control the voltage across them. It will be obvious that with the first arrangement interruption caused by a broken filament in either valve or dial lamps will break the circuit and the receiver will cease to function. In the other arrangement if either of the lamps blows the valves will still remain alight and the H.T. current will flow through the lamp shunt resistance, permitting the receiver to continue functioning. In the two circuits illustrated two lamps have been shown. In some receivers only one is used, whereas in others there may be up to four lamps, each one illuminating a separate part of the tuning scale. It is obvious that switches may be provided so that any desired lamp may be included in either of these circuits, and the switch may be operated with the wave-change control.

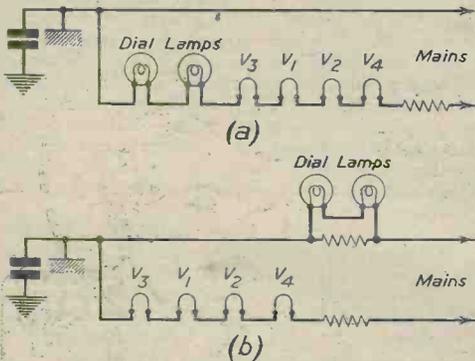


Fig. 5.—Skeleton circuit diagrams showing two main methods of wiring dial lamps in A.C./D.C. receivers.

the chassis line, and therefore its other end is "live." Consequently, unless a small fixed condenser is included in the aerial lead (between the aerial terminal (or socket) and the tuning circuit) it will be possible to get a shock when plugging in the aerial lead if a metal plug is used.

On the mains side we have already touched upon the mains filters which may be fitted, and small mica condensers are also often fitted to by-pass H.F., but these arrangements are normal filtering schemes and will not be dealt with here.

Dial Lamps

The next point to receive attention is the dial lamp circuit. In many A.C./D.C. sets it will be found that a dial lamp blows the set refuses to function, whereas in other receivers of a similar type the dial lamps can fail and signals still be received. The reason is quite simple and is illustrated in Fig. 5. Here are the two normal methods of wiring, in the first the lamps being in series with the valve filaments, and in the second they are wired in the other mains

Battery-mains Working

Just before the war some receivers were imported into this country from America which had the then new low-consumption valves for all-dry battery working, but in which provision was made for all-mains working also. This meant that there was no accumulator to worry about, a self-contained L.T.-H.T. dry battery of only about 90 volts being enclosed in the cabinet, and in addition a length of mains lead was also fitted so that the receiver could be plugged into any type of mains socket and the set would operate without disconnecting the batteries. British models were also manufactured on similar lines, and in one well-known British receiver it was unnecessary to operate

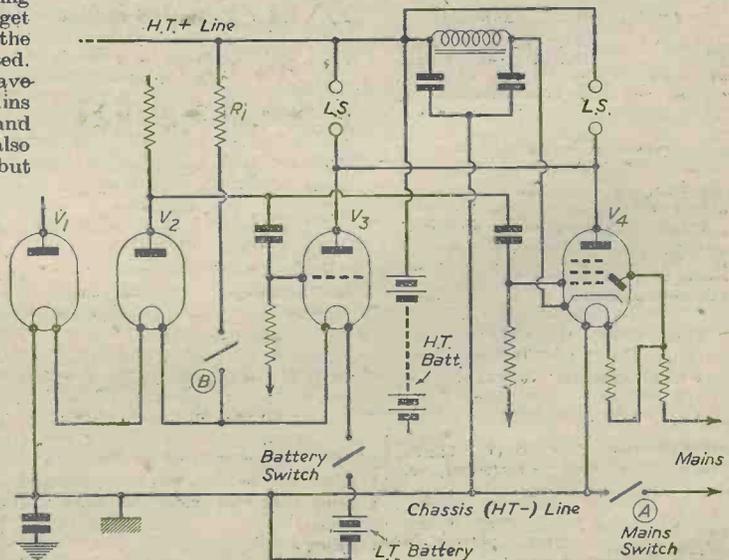


Fig. 6.—One scheme for providing battery or mains working. The filaments of V₁, V₂ and V₃ are not in circuit order.

a switch, the receiver merely being plugged into the mains and automatically switching over to the mains supply when the mains were switched on at the power point. In the event of a mains failure the receiver automatically changed back to the battery supply.

Although these arrangements sound complicated they are really fairly simple and the basic idea is shown in Fig. 6. Here, for simplicity, only a 3-valve receiver has been indicated, and the circuit is in skeleton form. V1, V2 and V3 are the low-consumption all-dry battery valves, whilst V4 is a mains type combined half-wave rectifier and output pentode valve.

It will be seen that the battery valves have their filaments wired in series and in series with the L.T. supply, just as in the case of A.C./D.C. valves. (This means, of course, that instead of a 1.5 volt battery, a 4.5 volt battery would be required for three valves, and so on.) The mains valve is provided with the usual series resistance to control the voltage across the filament and, if required by the particular make of valve used, a series resistance on the H.T. side. The anodes of both V3 and V4 are joined to the loudspeaker and the anode of V2 is joined through the customary coupling condenser to both V3 and V4 control grids. A series resistance is joined between the normal H.T. positive line and a tapping point in the battery-filament line—between V2 and V3. A switch is sometimes included in series with the resistance as shown at (B) and this can be one pole of a normal D.P.D.T. mains switch.

If the mains switch is in the "off" position and the battery switch set to "on," the L.T. supply will be completed through the battery,

the valves will light up and the loudspeaker will be operated through V3. V4 in this condition has no effect on the working of the receiver. If, now, the mains switch is set to "on" (and at the same time, of course, the battery switch must be set to "off") the valve V4 will heat up, but the filament circuit for V1, V2 and V3 will be open until V4 has attained its full emission. At this stage normal H.T. will be fed to the H.T. positive line, and as the resistance R1 is in series with the filaments of V1 and V2 across the H.T. supply, current will flow and the filaments of V1 and V2 will pass current. V3, however, has no filament supply and so remains inoperative. When V2 is at working temperature the signals at its anode are fed to V4 which, being now operative, delivers its output to the speaker, and so the receiver is working with the mains supply. The mains and battery switches are generally ganged or form a multi-pole unit, and in the Pilot automatic receiver previously referred to the battery switches are operated by a standard type of relay which closes when the output-rectifier valve attains maximum emission. Failure of the mains supply or mains valve removes the current from the relay which springs back to its original position and thus switches in the battery supplies once more.

The above are the basic details, and there are, of course, as with most receivers, individual refinements introduced to provide smoother supply, easier manufacturing or servicing facilities, etc., but enough has been written to show that the "All-mains" type of receiver is, after all, only a simple modification of standard schemes and well within the capabilities of the average home-constructor.

The Desert Air-mail

RADIO OFFICER WOOD, who holds the P.M.G. Radio Operators Licence No. 5, tells the story of the pioneer days of the earliest British overseas air route—the route between Cairo and Baghdad.

Now B.O.A.C. Regional Signals Officer at Johannesburg, Mr. Wood has been concerned with air radio since he joined the R.A.F. as a boy apprentice in 1918.

Mixed Duties

Radio Officer Wood writes: The Cairo-Basra weekly air-mail service was opened in December, 1926, by Imperial Airways. It was the first British overseas air route and I was proud to be assigned to it so soon after joining the company.

The aircraft, the old three-engined De Havilland *Hercules*, were very reliable and did a grand job, but their biplane construction still had something of the "sticks and string" era about it, while the cruising speed was under 100 m.p.h. Any strong head wind reduced our speed to that of a motor-car, and often we saw the Nairn Transport long distance buses overtaking us, churning up clouds of dust below as they went on their journeys between Baghdad and Damascus.

The aircraft of those days could not fly very high compared with modern standards and were therefore affected by the hot air currents rising from the desert, resulting often in bumpy journeys.

Those were the days of open cockpits and the pilot and myself were exposed to the intense heat, the rain and the fumes from the hot engines. However, our Marconi radio receiver and transmitter, although providing for few of the facilities known nowadays, were reliable for the type of use to which they were put, mainly the passage of weather and routine messages to and from the small number of stations in that part of the world.

But besides our wireless operating duties, there was much else to be done, since we wireless operators were the only crew carried in addition to the Captain.

We were up at the crack of dawn or before, to superintend the freight loading. Then we had to help to start the engines. Our only uniforms were white coats, and if the engine back-fired the coat changed its colour for the trip.

In the air, we had to take petrol, oil temperature and engine revolution readings and switch-over petrol cocks as ordered by the Captain. We were also responsible for working a "Heath Robinson" contraption which indicated to the passengers our position, e.g., "Passing Suez," "Jerusalem," "Dead Sea."

A further duty was to hand round tea or coffee and sandwiches during the flight.

On completion of a round-trip, the Radio Officers had one day stand-off and reported at the airfield the next day to service the radio, while the remainder of the time before the next flight was spent in assisting the engineers to make engine changes or in cleaning plugs. Incidentally, our basic salary was £3 ls. 1d. per week plus 5s. an hour flying pay!


Practical Hints

A Soldering Iron Repair

BITS of soldering irons should last a considerable time providing normal care is taken to avoid overheating and to seeing that they are always properly tinned.

However, after some years of continual use the craftsman may be confronted with a very badly pitted tip, as shown in sketch 1. This is more likely to occur with the ordinary iron than with the electric or gas iron, the heating of which can be more easily controlled.

Separate replacement bits can sometimes be purchased, but a temporary repair can be undertaken quite easily, as shown in the sketch. An extension bit is cut out of sheet copper and riveted to the old bit, the latter being cut down to receive it. A flat is cut out of the old bit as shown at 2, and a hole drilled through both this and the new extension. A small copper pan-headed rivet is used to secure the two meeting faces.

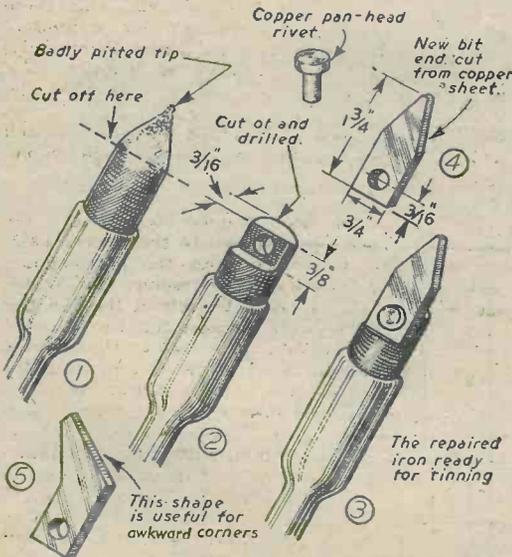

New bits for soldering irons are easily made up as described in the accompanying paragraph.

The finished repair is shown at 3, whilst the extension piece and rivet are shown at 4. The copper sheet should be as thick as possible, up to $\frac{3}{16}$ in. thick, if available, so as to conduct the heat well. The extension bit should be nicely filed and tinned in the normal manner.

If extra copper sheet is available the shape shown at 5 is very suitable for awkward corners, and particularly suitable for radio wiring work.

Such a conversion or repair will not, of course, tackle heavy work, as the heat reaching the tip will be less.

THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay half-a-sovereign for every hint published on this page. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints."


SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page iii of cover.

The sizes given will in most cases need modifying according to the particular iron it is required to repair.—R. L. G. (Chelmsford).

Handy Trimming Tool

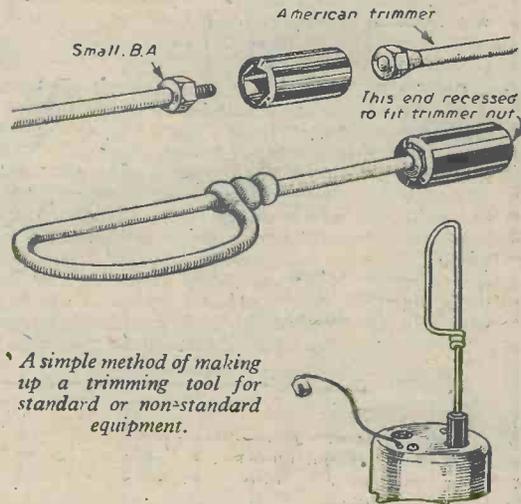I FOUND it necessary the other day to adjust the trimmers of an American set. Instead of the usual screw the trimmers had an odd shape of nut, so I devised the following tool: From the junk box I got a few large-size banana plugs and removed the metal part. Next, I took one of the nuts from the trimmer and fixed it in a long,



A simple method of making up a trimming tool for standard or non-standard equipment.

threaded rod, and heated it on the fire and burnt an impression on one end of the tube from the plug. I then removed the nut and replaced it with a small B.A. nut which had the same thread. Next, on the other end I burnt another impression, then bent the rod to form a handle. I repeated this on various sizes of nuts from trimmers and other plug tubes and now have a very useful adaptable servicing aid.—E. G. MATHEWS (Llandilo).

WORKSHOP CALCULATIONS TABLES AND FORMULÆ

Eighth Edition

by F. J. CAMM

A handbook dealing with methods of calculation, solutions to workshop problems, and the rules and formulae necessary in various workshop processes. It contains all the information a mechanic normally requires.

From all booksellers, 6/- net, by post 6/6 from the publisher.

GEORGE NEWNES, LTD. (Book Dept.), Tower House, Southampton Street, W.C.2.

at point of band where maximum gain is secured.

Theoretical gain with 5,000 ohms load should be $5 \times 6.5 = 32.5$ times (gm of EF50 is 6.3 mA per volt, neglecting stray capacities). The effect of even small stray capacities is seen when it is found that the impedance of even $10\mu\text{F}$ is 30,000 ohms at 550 kc/s, 15,900 ohms at 1,000 kc/s and only 10,600 ohms at 1.5 Mc/s. Including average stray capacities, an average of 10-15 times stage gain should be obtained from this stage.

Screen voltage in first, second and third stages is obtained via dropping resistances and not from potential divider, as this has been found to give better stability and smoother A.V.C. action. The third stage is straight, i.e., not vari mu, and its cathode resistance is fixed at 200 ohms. The first and second stages have fixed cathode resistances of 250 ohms, and a variable 3,000 ohms controlling both first and second stages and used as manual gain and selectivity control. First and second cathodes are separately decoupled with $0.5\mu\text{F}$ condensers. To reduce chance of modulation hum the coupling condensers are kept low ($50\mu\text{F}$) and leak of third stage is 250,000 ohms.

Power Pack

To keep stability at a high level and keep hum as low as possible, a small power pack is used to supply R.F. and demodulator section and cathode follower aerial unit only. This consists of an old Philco mains transformer giving about 325-0-325 volts and uses a type 80 rectifier. Smoothing is heavy, three chokes in series, two 25H and one 32H, being used with two $8\mu\text{F}$ and one $32\mu\text{F}$ electrolytic condensers, an additional $8\mu\text{F}$ electrolytic by-pass being used in tuner unit, the voltage available at set end being 250 volts at 70mA. A 250mA fuse bulb is used direct from rectifier valve to first electrolytic and saves possible need to replace rectifier and maybe mains transformer in event of a short or electrolytic condenser failure.

Demodulation and A.V.C.

As large a signal as possible having now been obtained it is applied to the grid of the double-diode-triode valve, which has its load in the cathode circuit. This load consists of a good M. and L.W. choke (an old Lewcos is used, although an R.I. Varley has been used and works O.K.): The valve used is a MHLDB, available as a VR101. This valve needs a total cathode resistance of 680 ohms to give

it correct bias, so that if D.C. resistance of R.F.C. is not sufficient it must be made up to this value by means of a resistance by-passed by a $.1\mu\text{F}$ condenser.

If no VR101 is available a Mullard EBC33 can be

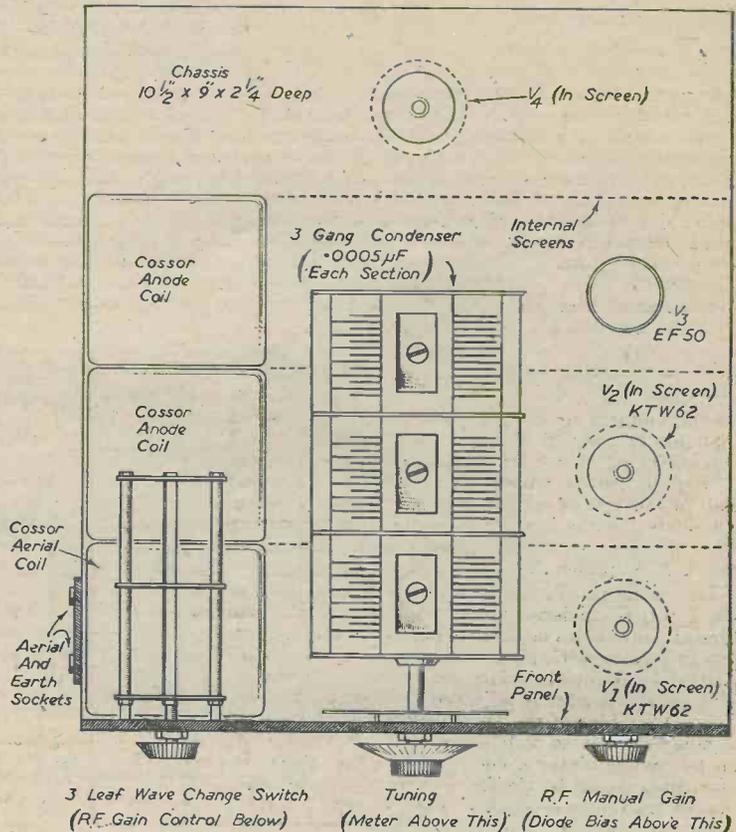


Fig. 3.—Chassis layout.

used but needs total cathode resistance of 1,150 ohms. It has however a lower mutual conductance than the VR101. It will be seen that the triode section is used solely as a cathode follower "feeder" for the two diodes, which share the same cathode return circuit and are thus fed with the R.F. voltages appearing there. As the working impedance of cathode follower across its output is given by $\frac{1,000}{\text{gm}}$ ohms approximately; if mutual conductance is 3mA per volt, then it will be seen that the output impedance is only 330 ohms. As this is so low compared with the normal impedance of a tuned circuit (which might be 100,000 to 500,000 ohms) it will be obvious that much smaller values of diode load can be used than normally employed (actually 20,000 ohms) and thus greatly reduce high-note attenuation due to R.F. by-pass condensers and stray capacities. It will also be found that 10-15 volts peak A.F. output can be easily obtained from the demodulator section—more than sufficient for

a normal A.F. amplifier and allowing a large margin for losses in tone control networks. Judged aurally, distortion even with large output appears to be far less than normal diode circuits and about on a par with that obtained from the infinite impedance demodulator without the latter's disadvantage of not giving A.V.C.

The A.V.C. diode (left section in diagram) uses a by-pass of $.02 \mu\text{F}$, and D.C. voltage is taken to A.V.C. line via 1 megohm resistance and $0.25 \mu\text{F}$ condenser, giving a time constant of .25 sec. This does not give response to quick fading (which is rarely heard on M.W.), but also does not cause much attenuation of the very low notes modulating the carrier. A change-over switch is used to connect A.V.C. line to (1) A.V.C., (2) earth (for manual control). This is useful for highest possible quality on strong steady signals and also for "lining up" the tuned circuits.

Demodulation Diode

This is also fed from the cathode circuit and has the same load as A.V.C. diode, i.e., 20,000 ohms. Its R.F. by-pass is reduced to $500 \mu\mu\text{F}$ only. Although this may seem large compared to the normal value of $100\text{--}250 \mu\mu\text{F}$ it must be remembered that due to the use of a low diode load of 20,000 ohms, $500 \mu\mu\text{F}$ will have the same by-passing effect to high notes as would $20 \mu\mu\text{F}$ with the normal load of 500,000 ohms. It is thus possible, by using low diode loading, greatly to increase R.F. filtering efficiency, thereby reducing risk of R.F. leaking into the A.F. amplifier.

The diode return to earth for R.F. and A.F. is via a $0.1 \mu\text{F}$ condenser and to D.C. via a special type of meter to an adjustable point on a 3,000 ohms potentiometer with about 15 volts D.C. across (as part of a potential divider from H.T. + to earth). This potentiometer is adjusted to the point where the cathode bias of the triode section of the D.D.T. is balanced out so that there is no delay voltage on the demodulator diode. (The A.V.C. diode is, of course, biased to the full extent of the cathode, bias of the triode section, giving 2-8 volts "delay" according to the type of D.D.T. used.) The tapping point of the potentiometer is decoupled to earth by a $50 \mu\text{F}$, 50 volt electrolytic condenser, which also prevents any trace of hum voltage leaking through. The special meter used is a Marconi "left right" D.F. indicator from the R1155 equipment, and are available (in several different makes all equally as good) as ex-government stock at 7s. 6d. to 10s. each. They are beautifully made and consist of two $100 \mu\text{A}$ meters, one zero on left and the other zero on the right and mounted with needles crossed. The movements were used individually in the R1155, but for our purpose are connected as shown in diagram, when D.C. current of the demodulator diode—which is zero biased, and therefore affected by signals of every strength—flows through both sections of the meter and causes both needles to "dip" together, giving a very effective tuning meter. For our purpose it is necessary to remove the case, but the outer metal one may be found a very tight fit. It can usually be gently pushed off, when three small screws will be found holding on the glass front. Remove these carefully and take off front. Now disconnect the internal shunt and series resistances found inside, but

leave the movements connected to the same terminals on the back. Paint out the L. and R. yellow letters on the black dial with a little black enamel or, better still, photographer's "dead black." Then replace front and see if both needles "zero" satisfactorily from the adjusters on the front. When O.K. replace screws. I have not found it necessary to replace the outer metal case (intended,

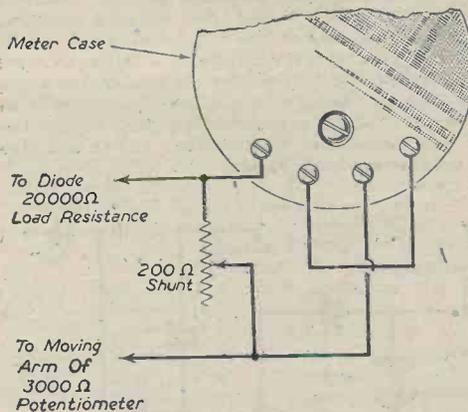


Fig. 4.—Connections to the tuning meter.

I believe, as a magnetic screen). The meter is mounted upside down compared with its usual position. Increase of current from nil causes both needles to swing down, giving a dip when the set is tuned over a station. It will be noted that the use of this tuning meter, while very effective, does not in any way affect the process of demodulation, and there is no alteration in the A.C./D.C. load ratio, causing heavy distortion on deep modulation such as occurs when a "magic eye" is connected to the demodulation diode. The meter is still affected by weak signals, which does not occur with the "magic eye" when (in an effort to avoid the distortion mentioned above) it is connected to the delayed A.V.C. diode.

It will be seen that a variable shunt of 100-200 ohms is connected across the meter and is used to adjust the meter readings to a good value.

The A.F. output from the demodulator diode is taken to A.F. amplifier via a 50,000 ohm resistance and another $500 \mu\text{F}$ condenser, forming an R.F. filter, and then through a $0.5 \mu\text{F}$ condenser through screened flexible low-capacity coaxial microphone cable via a coaxial plug and socket.

(To be continued.)

REFRESHER COURSE IN MATHEMATICS

By F. J. CAMM

8/6, by post 9/-

FROM

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2

A New I.F. Transformer

Preliminary Details of an Indian Invention

MR. S. K. DANDEKAR, of Standard Radio Service, Poona, has, according to a report in the *Radio Times of India*, developed a new type of I.F. transformer and no doubt readers will welcome a brief description of this, and the lines on which it works.

The main feature of these I.F. transformers is to increase the gain considerably, so much so as to eliminate the need of an I.F. amplifying valve, and—this is more important and perhaps difficult to understand—to accomplish detection (usually done by the diode section of a double diode triode valve) without rectification.

It may also be taken for granted that the difference between detection (reference here is to detection effected by the diode section of the double diode triode valve) and rectification is fully understood by readers, though quite often one does come across these two words being used rather loosely, and so inseparable as almost to convey the idea that rectification is indispensable for detection, which, however, is not the case.

These transformers are hereafter mentioned as two-stage first I.F. transformer and two-stage detector I.F. transformer. The gain of the two units and the detecting action of the second unit together completely eliminate the need for an I.F. amplifier valve and also the second detector. When a 50 L6-GT output valve is used, properly matched to an efficient speaker (a normally good—at present available—efficient moving coil type permanent magnet speaker is good enough) the gain of these I.F. transformers also eliminates the need for a low-frequency amplifier stage which is usually provided by the triode portion of the double diode triode valve.

Main Details

Details are given hereunder for the more technically inclined of the readers. Both the I.F. transformers are housed as usual in one metal shield, each cylindrical in shape, the minimum dimensions being 2½ in. diameter and 5 in. height. Both the I.F. transformers have three windings,

one of which is tapped, thus making seven leads. The first I.F. transformer is an all air core type and one section of the second I.F. transformer is iron core type—pulverised iron—but the number of turns being many more than usual to make it almost a low-frequency choke. Detection is thereby obtained without rectification, so naturally doing away with the conventional diode, crystal or oxide rectifier. Although these are referred to as two I.F. transformers, electrically they constitute one I.F. coil system, since there is no I.F. amplifying valve between the two—the two being coupled by a network of mica condensers and two H.F. chokes; it will be more proper, though, to refer to these as intermediate frequency chokes. The performance of the set incorporating these I.F. transformers is equal to any good make on the market embodying 12A8-GT, 12SK7, 12SQ7, 50L6-GT and 35Z5-GT or similar other types of valves.

3-valve Superhets

It will at once be noticed that this opens a possibility of making three valves all-wave superhets using 12A8-GT, 50L6-GT and 35Z5-GT; or 6A8-GT, 6V6-GT and 5Y3-GT; or similar other selection of valves. Apart from certain radical departures in the I.F. transformer construction and connections, the circuit requires no additional components. The rest of the circuit is about as conventional as that of any five-valve set. The reduction in the number of valves (I.F. amplifier valve and double diode triode valve), components associated with them, circuit simplicity and saving in components cost and assembling cost will be quite considerable.

The author has already wired up an actual model of this three-valve set embodying these I.F. transformers, and the performance has been checked side by side with a standard five-valve set and is not found wanting.

The author shortly hopes to be in a position to publish without prejudice to interests involved, the complete diagram with mechanical details, connections and values of circuit constants.

(Courtesy *Radio Times of India*.)

Safer Flying

AN inexpensive radio communication system for light aircraft was recently seen at the British Industries Fair, Olympia, and demonstrated by the manufacturers, E. K. Cole, Ltd., at Southend Municipal Aerodrome, to the Press representatives of the Ministry of Civil Aviation, key men from flying-clubs, and charter companies and aerodrome operators. For under £100 an owner-pilot can equip his aircraft with a light-weight twin-channel receiver-transmitter with which, at distances up to sixty miles, he can obtain an accurate bearing to his base in cloud, or for night flying.

A V.H.F ADAPTER

(Cont. from page 291)

For lower wavelengths less turns can be used, or the diameter of the coil may be reduced. Three turns of slightly larger diameter may be used for reception below 5 metres. The circuit will oscillate with one single turn, tapped half way round, but the limitations of reception upon such frequencies must be kept in mind as there may be no stations operating close enough to be received.

An examination of Fig. 2 will show what components are required.

Frequency Modulated Oscillator

A Unit for Use in Conjunction with the Home-made Oscillograph Described in Our December, 1947 Issue.
By E. D. WARD

WHEN the oscillograph, described in the December, 1947, issue, was designed, it was with the prime object of using it in conjunction with a frequency modulated oscillator for lining up superhets.

This oscillator has been working for some time, and it is very instructive to be able to "see" the I.F. response curves of various receivers.

a band width of the fundamental frequency of the oscillator valve V2.

Constructional Details

Commence by making the coils L1, L2, L3 and L4 and wire up V1 and V2. When V2 is oscillating V1 must also be in circuit with a bias on the grid equal to half that of the maximum sweep voltage obtained from the oscillograph. Set the frequency of V2 at 4 Mc/s so that when the sweep voltage is applied to the Miller valve V2 will be swept equally either side of 4 Mc/s.

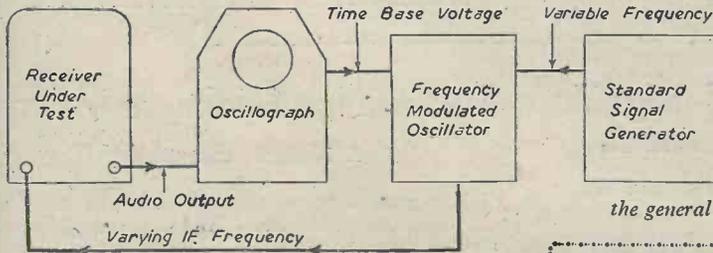


Fig. 1.—Block diagram showing the general layout of the complete assembly.

The Circuit

The oscillator valve V2 is tuned partly by a variable pre-set condenser C6 and partly by the inter-electrode capacity of V1, which utilises the Miller effect. (The input capacity varying with the gain of the valve.) The gain depends on the voltage applied to the grid, and by varying this the total tuning capacity is varied, so we apply the varying voltage from the sweep of the time base to the grid of the Miller valve via a 1 megohm variable resistance. Therefore, V1 sweeps the oscillator valve V2 through a range of frequencies:

The output of the oscillator is fed to the triode portion of a mixer valve (the original model used a 6P8G, but almost any 6 volt triode hexode will do). The hexode portion of the valve is fed from the attenuator network of a standard signal generator (carrier-wave only).

Now suppose you want to line up a receiver with 465 kc/s I.F.'s; the standard signal generator is set to the fundamental frequency of the oscillator valve (V2), plus 465 kc/s, and at the anode of the mixer valve will be found 465 kc/s varying over

NOTES ON COILS USED IN F.M. OSCILLATOR

- All coils are wound on one 3in. former, starting at the top with:
- L2—26 turns of 22 S.W.G. D.C.C. ; allow a small space and wind:
- L1—16 turns of 22 S.W.G. D.C.C. ; allow a further small space and wind:
- L3 and 4—26 turns of 22 S.W.G. D.C.C.

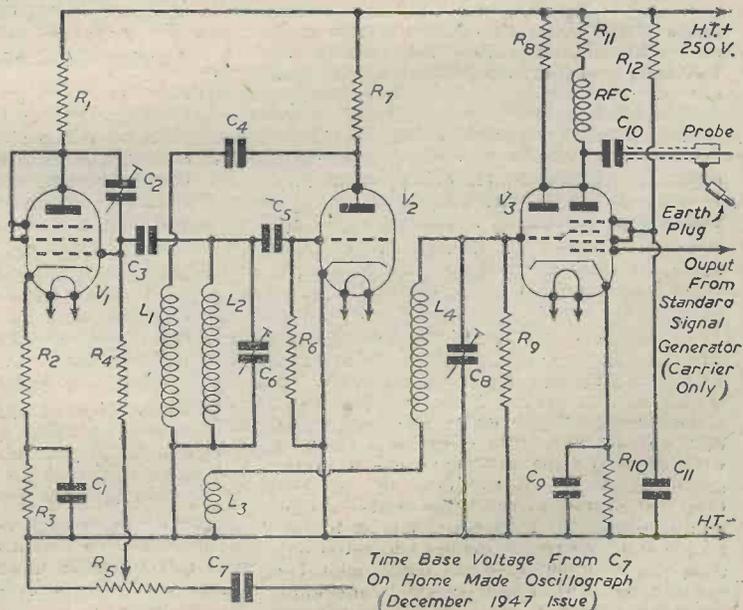


Fig. 2.—Theoretical circuit of the oscillator.

Valve Mounting ^c

The valves may be mounted on an open chassis 9in. by 5in. by 2½in., and this may then be mounted on the side of the signal generator, taking heater and H.T. voltages from a modification therein. The output from the receiver under test is taken from any convenient spot (usually the top end of the volume control) and fed to the amplifier on the oscillograph, and it will be necessary to cut out the internal speaker of the set, first loading the output transformer with a 50 ohm resistance to prevent damage to the output valve.

The internal speaker should be cut out because of the noise this combination makes.

Lining up procedure is exactly the same as for audibility or output meter, only the I.F. response curve can be seen on the screen of the C.R.O.

LIST OF COMPONENTS

R1 2,500 ohms.	R7 .1 megohm.
R2 150 ohms.	R8 30 K ohms.
R3 450 ohms.	R9 25 K ohms.
R4 ½ megohm.	R10 300 ohms.
R5 1 megohm. var.	R11 25 K ohms.
R6 1 megohm.	R12 40 K ohms.
C1 25 μF.	C7 .25 μF.
C2 50 pF.	C8 150 pF.
C3 .0005 μF.	C9 .1 μF.
C4 .0005 μF.	C10 .0025 μF.
C5 25 pF.	C11 .1 μF.
C6 150 pF.	
V1 6K7C.	
V2 6C5G.	
V3 6P8G.	
L1, 2, 3, 4. See Notes on p. 293.	

Suppressors for Car Ignition Two Million Miniature Valves

Some Hints as to their Efficient Use

A Mullard Achievement

THE news that the G.P.O. is fitting suppressors to the ignition systems of its 25,000 vehicles in the London area, in order to prevent interference with television sets, is of considerable interest to motorists, many of whom have fitted them already to prevent interference to their own car radio sets. It is one thing, however, to go to the trouble and expense of fitting suppressors to obtain improved reception on one's own car—it is quite another to do so purely for the benefit of a relatively small number of television viewers.

It may be, indeed, that some motorists will not follow the G.P.O.'s example, and will argue that cars came first and that the manufacturers of television sets must design their sets so that they are not affected by cars! There are about a million cars, goods vehicles and motor cycles in London and the adjacent counties—quite apart from visiting vehicles—and to equip all these with suppressors for the benefit of the few would appear a big task. Television will, of course, spread to the rest of the country eventually.

Those motorists, however, who wish to eliminate the crackle set up in their own car radio sets by their own ignition systems may well be advised to fit suppressors, and for these the following hints, offered by the Lodge plugs company, will be useful. The suppressors should be fitted as near as possible to the actual points where sparking occurs—i.e., at the distributor end of the lead from the coil to distributor, and at the sparking plug end of the plug leads. The suppressors should have a value of from 5,000 to 15,000 ohms, but when they are fitted in both distributor and plug leads the total value of the distributor suppressor and any one plug suppressor should be kept below about 20,000 ohms. If they are of much higher resistance than this, the actual power of the spark may be reduced, with resultant oiling of the plugs, but suppressors of the correct type should have no adverse effect on easy starting or general engine performance.

THE production of the two-millionth valve at the Mullard factory at Gillingham, Kent, recently, was the subject of a small ceremony which took place when Mr. Kempson-Jones, head of the valve-making department, visited the factory.

He brought with him the actual "two-millionth" valve, which, he said, "has been mounted and brought to Gillingham where it will remain in recognition of the efforts made by everyone, and as a reminder to all in future of the large output obtained from this small but efficient factory."

American Standards

When presenting the valve to Mr. S. Bagust, manager of the factory, Mr. Kempson-Jones said:

"One of the aims when the Gillingham factory started was to reach production speeds from assembly groups comparable to those obtained in the United States on similar types, and I am now pleased to tell you that this has almost been achieved. . . .

"You may think, 'Why must we attempt to obtain U.S.A. speeds?' The reason is that we must export these valves overseas and we have to compete with valves of American manufacture, and therefore we must make our valves as cheap as the Americans. . . .

"As far as Gillingham is concerned, this means, firstly, we must meet the programme so that we can make economical use of the factory and also the equipment and labour at Mitcham. Secondly, it is necessary to maintain the present high level of production per group. Thirdly, to maintain and improve the quality of the assemblies.

"I hope that all of you will be here when the five-millionth assembly is completed."

The Gillingham factory is one of two (the other is at Hove, Sussex) given over to the manufacture of miniature and sub-miniature Mullard valve assemblies.

Underneath the Dipole

Television Pick-ups and Reflections. By "THE SCANNER"

SHOULD television have a signature tune, with appropriate accompanying picture? The short introductory film has been chopped and changed about as a result of the opinions expressed in "Viewers' Viewpoint" and "Viewers' Vote," and, at the time of writing, seems as if it is going to disappear altogether. I hope it isn't. I agree that the original signature tune film was inclined to be flickery and variable in quality of both picture and sound. Nevertheless, I preferred to carry out final little adjustments of volume and contrast on this, rather than upon the somewhat harsh lettering of the tuning frame which precedes the transmissions. The fault of the B.B.C.'s television signature film lies not in the shots of the aeriels, nor in the aerial shots, but in the quality of film transmissions, which still lags behind live television. When tele-cine has been improved a little more, the signature film should be restored, though not necessarily in its original form.

Stage Play Relays

The relaying of plays from theatres, such as has been done from the Intimate Theatre, Palmer's Green, suffers from obvious disadvantages. Apart from the difficulties presented to the technique of both producers and engineers, the laughs, coughs and rustles from the audience tend to distract television viewers. However, regular viewers make allowances for these distractions and derive considerable enjoyment from such relays. One of the most successful transmissions from Palmer's Green was "The Shop at Sly Corner," which kept my family and some friends, at any rate, enthralled for an hour or so, though I can understand new or "stray" viewers getting the wrong idea about television if it happened to be their first viewing. However, I hope that we shall continue to have the privilege of joining the audience of the very small Intimate Theatre, which grows in size from a few hundred on ordinary nights up to a comfortable 100,000 on television nights!

Unesco

I don't think many viewers kept their receivers on for "Unesco," the item which followed "The Shop at Sly Corner." My own home audience melted away before the conclusion of the somewhat pompous introductory speech and I have yet to discover a viewer who survived the latest excursion into documentary television. From the same stable as "Searchlight," it carried with it the same political implications. As an "entertainment" it proved that cinema exhibitors are right in their contention that audiences will not tolerate this kind of stuff unless forced to view it at the point of the machine gun! Fortunately, viewers were able to switch their sets off and escape from "Unesco," which developed into a session of long drawn-out documentary films of the very type the

cinemas reject. This is the kind of material which "un-sells" television to prospective viewers.

It is a strange and important thing, the first impact of a television programme upon the would-be purchaser of a television set. The atmosphere of the radio store or a great exhibition is certainly not favourable for an initial viewing, but a radio dealer told me that a trial of a set in the actual home of a prospective customer almost invariably led to a sale. Much depended upon the type of programme viewed during the period the set was "on approval," and he told me that if there was a high proportion of film being televised, or the "A.P." boys were trying out any arty-crafty experiments, then a sale did not result. Comedy programmes hold the greatest appeal for new viewers and the Saturday night revues have roped in more television licence holders than anything else. Everyone—the new viewer and the old one, too, is starving for laughs, and the television producers would do well to increase our comedy ration. Who will be the Tommy Handley of television? There are now many comedians (and comediennes), who are thoroughly at home on television, and we simply can't see too much of them. Leslie Henson, Jimmy Edwards, Richard Hearne, Sonnie and Binnie Hale, Hermione Gingold and Claude Hulbert are just a few of the names that occur to me.

Long Distance Viewing

The sign of the dipole is no longer an exceptional sight at distances over fifty miles from the Alexandra Palace. I am surprised at the large number of television aeriels which are to be seen above the houses in towns on the south coast, even in situations where hilly ground lies in the direct line between the receivers and the Alexandra Palace. At first, one noted such aeriels with great interest; they were conspicuous on account of their elaboration and the height of their masts. In the course of time, these pioneer outposts of television seemed to have gathered around them a brood of new viewers, not quite so ambitious with their aerial arrays, but who seem, none the less, to be obtaining highly satisfactory results with the latest sets. One comes across a perfect little colony of dipoles within a small area, and then may travel many miles before discovering another similar crop. Obviously, the strenuous efforts of the man with the highest aerial has proved the possibilities of television at great distances, but it is strange that subsequent aeriels in the same neighbourhoods should be so very much lower and frequently in positions which are obviously exposed to motor car ignition and other forms of interference. Some of the latest sets have their own special circuit arrangements for reducing the effect of such interference, but it must still be there, all the same. You really cannot take too much trouble with your aerial unless you're practically on the doorstep of the "A. P."

Television Tax

Once more the Chancellor of the Exchequer has piled penalties upon the radio trade in general and the prospective television viewer in particular. The vicious increases in purchase tax now makes the cost of television receivers in Britain considerably higher than they are in the United States, where the television craze is just "catching on." Will Britain maintain her lead in television? I think not. The purchase tax will play its part in retarding development and progress here, while in America the competitive efforts of hundreds of television stations and programme sponsors will accelerate the pace. Enterprise and initiative in Britain are discouraged by the practical restrictions imposed

in each succeeding budget, and the rhetorical exhortations of the politicians are now exposed in all their hollowness. Perhaps some day we shall cease to be guinea pigs for past students of the London School of Economics and other seats of learning, and gain once more the respect of the world for our commercial and scientific predominance. But, for the time being, things gradually come to a standstill in the radio trade and every other so-called "luxury" industry, with axes, taxes, controls, snoopers, quotas, licences, levies and red tape. It is impossible to comment upon the present trend of the trade without getting hot under the collar! The radio trade in England, in the beginning, was built up by amateurs. Now it is being ruined by another kind of amateur!

Trade Notes

CLIX PRODUCTS

THE sales of Clix radio and television components manufactured and hitherto marketed by British Mechanical Productions, Ltd., are now handled by the General Accessories Co., Ltd., of 21, Bruton Street, London, W.1. The General Accessories Co., Ltd., are the wholly owned subsidiary of British Mechanical Productions, Ltd., and are their selling organisation through whom all Clix products, in future, will be marketed.


BRIMAR VALVE MANUAL

THE new Brimar Valve Manual is now available in sufficient quantities to meet all demands. The manual includes details of nearly two hundred types of valves listed in numerical order throughout, and covering 139 pages.

Characteristic curves and operating data for the modern types are given, including details of the loctal and miniature "all glass" ranges.

The circuit section contains diagrams of several amplifiers with outputs of 5-75 watts, whilst the manual concludes with a selection of formulae used in radio engineering, together with some useful abacs and a valve equivalent list.

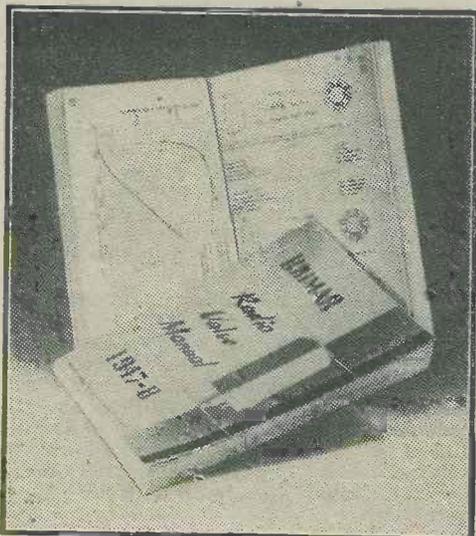Owing to production costs to-day, a charge of 2s. 6d. is made.



The new Brimar Valve Manual and a specimen page.



This illustration gives an idea of the new lines of the latest G.E.C. portable.

NEW G.E.C. PORTABLE

THE new G.E.C. portable will appeal to all those who are looking for an elegant and really portable set with long battery life and exceptional performance. Its dimensions are, height, 12½ in.; width, 13½ in.; depth, 7 in.; and its weight is 18 lb.

The revolutionary design of handle and cabinet, which are streamlined in mottled green plastic, makes the set pleasing in appearance and easy to carry. A large tuning dial lies below the handle, and three milled-edge controls for tuning, volume and waveband selection are conveniently recessed above the loudspeaker louvres.

All-glass miniature valves are used in the four-valve superhet circuit, and waveband ranges of 200-550 metres and 1,000-2,000 metres are provided. The separate H.T. and L.T. batteries have a working life of over 250 hours, the 90-volt H.T. battery being the new compact G.E.C. "layer" type, and the L.T. battery of exceptionally high capacity. The performance of the set with its internal frame aerial is equal to that of the average table receiver using an outside aerial.

MULLARD ELECTRONIC PRODUCTS, LTD.

THE Mullard Wireless Service Co., Ltd., have changed their name, and are now known as Mullard Electronic Products Ltd.

This change of name has been made necessary by the expansion of the company's activities from that of the purely "wireless" field into other branches of electronics—particularly those with applications in industry, science and communications.

CLYDESDALE

The Radioman's Shop

For Bargains in ex-Services Electronic Equipment

BRAND NEW, in maker's sealed wrapper.
EX-U.S.A.A.F. JEFFERSON-TRAVIS.
SYNCHRONOUS VIBRAPACK U.F.I.
 Complete and self-contained vibrator. Power unit for 12 volts input, outputs 150-120 volts 30-50 mA. choke/capacity smoothed, L.T. and Bias, plus 4 feet screened input lead fitted with crocodile clips, with circuit in metal case 7in. x 4 1/2in. x 6 1/2in. finish black.

CLYDESDALE'S PRICE ONLY 19/6 each. Post Paid.

BRAND NEW, in maker's sealed cartons.
EX-U.S.A.A.F. MALLORY SYNCHRONOUS VIBRAPACK
 Input 12 volts. Outputs 150-120 v., 30-50 mA. Complete unit totally enclosed and fully screened. Dimensions 5 1/2in. x 2 1/2in. x 5in.

CLYDESDALE'S PRICE ONLY 12/6 each. Post Paid.

BRAND NEW, in maker's cartons.
R.F. UNIT, TYPE 26.
 for 50-65 mc/s, condenser tuning. Makes an ideal 5- and 6-metre converter. Act now, only a few available.

CLYDESDALE'S PRICE ONLY 35/- each. Post Paid.

R.F. UNIT, TYPE 27.
 for 65-85 mc/s, condenser tuning. With mods. makes a 5- and 6-metre converter. Used, good condition.

CLYDESDALE'S PRICE ONLY 25/- each. Post Paid.

R.F. UNIT, Type 24. 26-30 mc/s. with switched position tuning.

BRAND NEW, in maker's cartons.
CLYDESDALE'S PRICE ONLY 19/6 each. Post Paid.

Used, good condition.

CLYDESDALE'S PRICE ONLY 12/6 each. Post Paid.

Send now for new illustrated lists; please print name and address

CLYDESDALE SUPPLY CO., LTD.

2, BRIDGE STREET, GLASGOW, CS. Phone: South 2708/9
 Visit our branches in Scotland, England and Northern Ireland



You won't miss
 your next

'APPOINTMENT
 WITH FEAR'
 if you rely on



FOR THE
 RADIO SERVICE
 MAN, DEALER
 AND OWNER

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

Write to the I.C.S. Advisory Dept., stating your requirements. It places you under no obligation

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94, International Buildings,
 Kingsway, London, W.C.2


Please send me your free booklet describing I.C.S. instruction in the subject marked X.
Complete Radio Engineering Elementary Electronics
Radio Service Engineers Elementary Radar
Radio Service and Sales Advanced Short-wave
Elementary Radio Radio

If you wish to pass a Radio examination, indicate it below.
 British Institute of Radio Engineers
 P.M.G. Certificate for Wireless Operators
 City and Guilds Telecommunications
 R.A.F. Wireless Operator and Mechanic

Examination students are coached until successful!

Name..... Age.....
 (USE BLOCK LETTERS)

Address.....

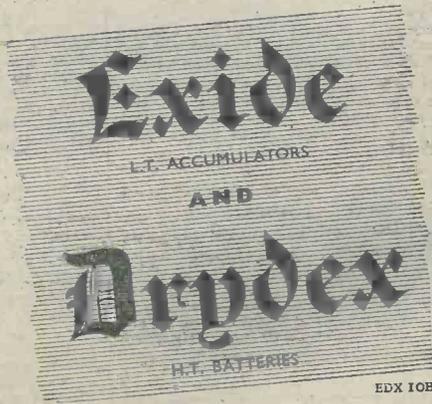

ISSUED BY
 THE CHLORIDE ELECTRICAL STORAGE CO. LTD

O. GREENLICK, LTD.

TUNING UNITS, COILS. The "Ruco" tuning assembly, complete wired all wave, for use with 6K8G and 6K7G valves, complete with dial, I.F.s, etc., factory aligned and tested, 85. The "WEYMOUTH" all-wave pack, comprising chassis with all coils, padders, etc. 36/6. M.L. wave T.R.P. coils with reaction, pair 7/6. Ditto coils, with adjustable iron cores, for highest gain, no reaction, pair 10/6. "Weymouth" midget iron-cored I.F. trans. 18/9. Standard iron-cored I.F.s, 15/- pair, 2 mer. I.F.s, 2/- each. **TEST PRODS.** A pair of polished ebonite prods, metal tipped, 5in. long, on flexible leads, 15in. fitted plugs, pair, 4/-. **AMPLIFIER CASES.** Undrilled chassis, 17in. x 11in. x 2 1/2in., with perforated detachable covers, 30/-. **CONDENSERS.** 8 mid., 500 v., 4/-; 20 x 20 mid., 150 v., 5/-; 8 mid., 75 v., 1/-; 4 mid., 12 v., 9d.; 25 mid., 25 v., 2/-; 2 mid., 1,000 v., 8/-; 4 mid., 100 v., 8d.; 0.1 mid., 5/- doz.; 0.01 mid., 5/- doz.; 2-rang. 0.005 mid., 11/-; 0.001 mid., 6/-; split stator, 0.0017 mid., 6/-. **DIALS-DRIVES.** Full vision drive assembly, S.M.L. complete with glass and esutocheon, 7in. x 4in., 12/6. Square plane M.L. ditto, 5in. x 4in., 11/6. Dials, S.M.L., in colours, 5in. x 3 1/2in., 2/6; 4in. x 3 1/2in., 2/-. Glass dials S.M.L., coloured, 8in. x 6in., 5/-. Epicyclole reduction drives, 3/3. String drum drives, with pulley and spring, 3/-. Horizontal drive assembly, S.M.L. dial, 12in. x 4 1/2in., 25/-. **SLEEVEING.** In reels of 3540 yds., 1 mill., 1/6 reel, various colours. **SWITCHES.** Trolley-type, 3 pole, 2 way, 9/-; 4 pole, 3 way, 3/-; 4 pole 4 way, 9/6. Midget rotary switches, 4 pole 3 way, 3/-; 4 pole 2 way, 3/-. **CABINETS.** Table model. Walnut veneered, inner dimensions 21 1/2in. x 10 1/2in. x 7 1/2in., 85/-; midget, sprayed cream and green, 13 1/2in. x 7in. x 6in., 35/-. **CHOKES.** Ultra midget, 40 ma., 5/-; midget, 40 ma., 5/6; standard, 100 ma., 8/6. **TRIMMER KITS.** In case, 45/-. Our list at 2/6. contains a host of other interesting lines.

Near Whitechapel Station,
265, Whitechapel Road, London, E.1.
Tel.: Bishopsgate 5079.



NEW G.P.12 CRYSTAL PICK-UP

with permanent sapphire stylus

—was fully described in *The Wireless World's* recent article "Crystal Pick-ups"—Basis of Design for Fidelity Reproduction.

This remarkable pick-up, which represents the ultimate in high-fidelity reproduction, is now available in limited quantities through your radio dealer, price 104/- incl. P.T.

FREE ILLUSTRATED FOLDER describing this new pick-up may be obtained by returning the coupon below.

TO COSMOCORD LTD.
ENFIELD, MIDD.X

Please send folder of ACOS Pick-ups.

NAME _____

ADDRESS _____

P.W.

GALPIN'S

ELECTRICAL STORES,

408, HIGH STREET, LEWISHAM,
LONDON, S.E.13.

Telephone: LEE GREEN 0309.

TERMS: CASH WITH ORDER. NO C.O.D.

EX-GOVT. (AS NEW) ALTERNATORS, 230/250 volts D.C. input 230 volts 50 cys. 1-phase at 65 amps. Output, separately excited 24 volts at 4 amps 85 each, carriage 7/6.

EX-NAVAL (SELF-ENERGISED) TELEPHONE HANDSETS, 10/6 each, or complete Telephones Magneto Ringing with Neon Light, 35/- each, post 2/6.

VARIAC TRANSFORMERS, 2,000 watts 230 volts input tapped 115 volts 0 to 230 volts output, 25/10/- each, post 5/-.

CONTROLLER ELECTRIC PUSH-BUTTON UNITS, 5 press switches and master Dewar switch (complete, brand new), useful for all model work telephone and remote control, 5/- each, post 1/-.

MAINS TRANSFORMER EX-GOVT. All 50 cycles input, 230 volts input, 500/0/500 volts, at 250 M/amps. L.T. 5 v. 3 a., 37/6 each, carriage 3/6. Another 50 volts at 30 amps., output, 75/- each, carriage 6/-.

Another two L.T. windings, 6 1/2 volts, at 10 amps., 27/6 each. Another 230 volts, input 700 volts at 150 M/amps., 4 v. 2 a., 4 v. 1 a., output, 27/6 each, carriage 3/6. Another 700/0/700 volts, 80 m/a., 12 v. 1 a., 4 v. 2 a. output, 30/- each.

MAINS TRANSFORMERS (new), input 200/250 volts, 50 cycles, 1-phase, output 350/0/350 volts at 180 M/amps., 4 v. 4 a. C.T. 6.3 v. 4 a., C.T. 5 v. 3 a., 37/6 each, post 1/6. Ditto 500/0/500 volts, 150 M/amps., 4 v. 4 a., C.T. 5 v. 3 a., 47/6 each, post 1/6. Another tapped 6, 12 and 24 volts at 10/12 amps., 45/- each, post 1/6. Auto wound Voltage Changer Transformers, tapped 0, 110, 200, 220 and 240 volts, 250 watts, 45/-; 350 watts, 55/-; 500 watts, 70/- each, carriage 1/6. (Please note these transformers can be delivered ten days from receipt of order.)

EX-GOVT. (G.E.C.) ELECTRIC FANS, 12 volts, ACIDC laminated field, complete with 5in. impeller. New, boxed, 20/- each, post 1/-; Transformer to suit, 230 volts, input 12/16 volts at 4 amps. output, 32/6 each.

MAINS VARIABLE RESISTANCES, ex-Government (new) slider type, 450 ohms to carry 0.7 amps., 30/- each; 4,000 ohms, 25 amps., 35/- each. Worm Wheel Control, slider type, 60 ohms to carry 1 1/2 amps., 22/6 each; 5.7 ohms, 8 amps., 32/6 each. Dimmer Resistances Stud Switch Arm Type, 2,700 ohms to carry 2.7 amps., 30/- each.

MAINS VARIABLE RESISTANCES (slider type), new, ex-Govt., 14 ohms, carry 1 to 4 amps., graduated; useful as dimmers, etc., 25/- each; another, 0.4 ohms, carry 25 amps., 25/- each, post 1/6. Ex-Govt. Moving-coil Cell Testers, 3-0-3 volts (new), 25/- each.

EX-GOVT. (NEW) MAINS TRANSFORMERS, 200/250 volts, 50 cycles, 1-phase input, 525/0/525 volts, 150 M/amps., 6.3 volts, 5 amps. 5 volts 3 amps. output standard rating, 35/- each, post 2/-. Mains Smoothing Chokes, 10 Hy, 150 M/amps., 180 ohms D.C. Res. 8/6, ditto, 100 M/amps., 5/6 each, post 9d. All the above can be offered in large quantities. Please write for special quotation.

EX-R.A.F. MICROPHONE TESTERS (new). These consist of a Ferranti 0 to 450 M/amp. 2 1/2in. scale meter shunted to 1 m/a., incorporated Westinghouse Rectifier; the whole encased in polished teak case, calibrated at present 0 to 10 volts, 32/6 each.

MAINS TRANSFORMERS, as new, input 230 volts, 50 cycles output, 12 volts, at 8 1/2 amps., A.R.P. shelter transformers, 25/- each, post 2/-.

H.B.L.

FOR THE HOME
CONSTRUCTOR

We specialise in supplying complete kits and individual component parts for all circuits described in this journal.

PETO SCOTT. All Dry Portable 4-valve 2-waveband superhet in neat wooden cabinet finished in leatherette. Overall size 10in. x 12 1/2in. x 4 1/2in. Weight of receiver complete with batteries 14 1/2lb. £20.16.3, or on H.P. TERMS Deposit £4.3.3 and 12 monthly payments of £11.1.3.

POCKET VOLTMETER, moving coil, ranges 0/15 and 0/250 volts, D.C. (ex Service), 18/6.

SPECIAL OFFER. 2 1/2in. dia. SPEAKERS, Speech Coil Impedance, 3 ohm. Brand New, 17/6. Also 5in., same price.

H.B.L. 2-VALVE S.W. KIT.—A simple to build and efficient battery short-wave receiver, covering 12 to 30 metres. Complete kit of components, chassis, valves and full instructions, 43.14.6.

Circuit wiring diagram and component list for the H.B.L. 1-valve, S.G.3, or S/W2 kits, price 1/-.

Send 2/- stamp for our Brochure of Kits, Peto-Scott Receivers, Components, etc. Also details of our Practical How-to-Build-It Books, complete instructions and designs for the HOME CONSTRUCTOR.

HENBEST BROS., LTD.,

26, Green Lanes, London, N.13

Telephone: BOWES PARK 6289.

LYONS RADIO

3, Goldhawk Road,
Shepherd's Bush, W. 12

Telephone: Shepherds Bush 1729.

CRYSTALS. Brand new American, plug-in 'Siz' 4 1/2in. x 1 1/2in. x 1/2in. with 4in. pin spacing. 24 crystals, complete instructions, 4,035 kc/s. and 5,955 kc/s.

11/6 each, or 3 for 33/- (post free). **MORSE TRAINING SETS (W.T. Mark III).** The ideal morse practise set. Comprises 2 valve oscillators with 9-way tone control and switchable atmospheric simulator. Battery operated. Valves, key and connectors included. In wooden case with lid.

22/6 each (carriage 3/6). Additional morse keys with connector, 2/9 each. Suitable phones, 4/6 pair.

INDICATOR UNIT BC-1151-A. A piece of brand new American equipment fitted with 2 electro-magnetically deflected cathode ray tubes, type 5F77 (4 1/2in. flat screens). Includes 2 200v. metal valves, relays and other components. Approx. 14in. x 11in. x 7in.

30/- each (carriage 2/6). **DUAL PURPOSE PANEL CONTROL (G.P.E.C. Type 7).** A heavily-built unit in metal case size 18in. x 8in. x 2 1/2in., deep fitted with 0/100v. rectifier type A.C. moving coil meter (2 1/2in. dia.), 0/40v. moving coil voltmeter (2in. dia.), 80v. A.C. carbon pile regulator, 24v. carbon pile reg. (20/40 amps.), accumulator cut-out, B.F. suppressor 5 mfd. block condenser, 8 Slydock fuses, etc. New and unused, in special transit cases.

35/- each (carriage 6/-). **WAVEMETERS.** Type W1239 (EX-R.A.F.) Frequency range 39-51 mc/s. For A.C. mains (250-250v.) Rectifier type, employing 4 valves (VR92, 6J5, VT103, 6X5). Built to lab. standards. In copper-lined boxes, 15in. x 10in. x 9in. As new. Complete ready to switch on. Supplied in special transit cases.

43-19-6 (carriage 5/6). **POWER UNITS.** Type 228. Dual outputs of 350v. (stabilised) and 400v. Input 80v., 1,000 cps. Fitted with valves, type 5U4C, VU120 and 6V6G. Other components include 3 Slydock fuses, chokes, 2 0.26/0.000v. condensers. New, Supplied in special transit cases. 35/- each (carriage 5/-).

Programme Pointers

This Month, Our Correspondent, MAURICE REEVE, Discusses the Question of
a National Concert Hall

ONE of the saddest, most evocative and most bewildering sights to be seen in war-scarred London to-day is that of poor, blitzed, burnt out Queen's Hall. I passed by it the other day, and I couldn't help but wander up and down Riding House Street into Great Portland Street and back into Regent Street, meditating, reminiscing, and casting my mind and heart back over years of unforgettable memories. Door No. 8 in Riding House Street, Orchestra entrance in Gt. Portland Street; how many times had thousands of us stood outside there to hear the greatness of "London music's golden era"—Padrewski, Bosini, Rosenthal, Chaliapin, Kreisler, Nikisch. Did it not give us riches such as no other London concert hall could match? (Wigmore, originally Bechstein, perfect and also redolent, but too small for the epicurean feasts of Langham Place.) Could the vast spaces and echoes of good Prince Albert's memorial ever hope to vie with it in that intangible quality of atmosphere and mystique which were so part and parcel of Queen's? Wasn't it, also, the birthplace and cradle, nursery, school and realisation of the "Proms," when Proms were Proms, banquets but not orgies, where enough was as good as a feast, and where student and pedagogue rubbed shoulders with, I venture to say, greater camaraderie than they do to-day? In brief, wasn't Queen's Hall perfect of its kind? Acoustics, size, situation. And there it is to-day, six years after its rape, still an empty, burnt-out shell, whilst London music screams out for its replacement.

I do not pretend to know the whys and the wherefores of this tragic cum comic situation. I believe it is Crown property, and I have heard that ten times the rent is now required for the site. Why, I don't know, when the rental of the Oval, Duchy of Cornwall land, remains much as it ever was. Meanwhile, a few bricks are bought and a few programmes are sold annually for the "Henry Wood Memorial Hall Fund," a scheme which, on present lines, cannot hope to bear fruit except in the lives of the youngest of us, and whose projected site in Marylebone Road is likely to be as detrimental to its welfare as the original site in South Kensington would unquestionably have been to the National Theatre.

The lamentable sight of this beautiful ruin which has, for six years, been so melancholy to music lovers, together with the Chancellor of the Exchequer's recent statement on behalf of the Government regarding a National Theatre, raises the question of the practicability, possibility and desirability of a National Concert Hall. The problem is a big one, and, in many ways, bigger than that of the theatre.

Mixed Reception

The announcement concerning the National Theatre was received by the London Press with

quite a remarkable degree of disapproving unanimity, at least as far as the financing of it was concerned. The concensus of opinion was very much against the Exchequer—in other words, the taxpayer anywhere and everywhere between John o' Groats and Land's End—standing the racket for something the patrons of which would overwhelmingly consist of Londoners. With no little justice was it also pointed out that, in common fairness, similar theatres should be provided, as well, in the larger provincial centres, Scotland and Wales. And again, by way of a third cold douche on the proposals, it was argued that national funds should not be used for something that only interests a very very small percentage of the taxpayers.

Now, I seem to remember no less a person than Mr. Ernest Newman emphasising the latter point when he opposed similar proposals some years ago regarding opera. If there is any weight in the arguments concerning a National Theatre, they would probably carry still heavier guns if directed against the concert hall project, as probably an even smaller percentage of the population would be concerned.

In using the term "concert hall," I obviously infer a centre of music wherein everything from an opera to a piano solo could be adequately presented.

Opera Only?

What is there in the whole realm of music, other than opera, that could be profitably performed in such a metropolis of the art that cannot be heard every week of the year in existing halls as run under private enterprise? Certainly no such "alibi" as Shakespeare exists for bringing the idea to fruition. Whilst knowing little of what would comprise the repertoire at the National Theatre, other than Shakespeare, the mind certainly reels at the very idea of finding the Tchaikowsky or Rachmaninov concertos popping their heads up for performance at the national music centre! Perhaps it could become the home of the Promenade Concerts, an insitution if ever there was one.

Regarding the arguments against making the majority pay for what only the minority is interested in, I am not so sure this is as fool proof as it may seem at first hearing. I suppose we all belong to a minority of one sort or another. Some of us don't believe in battleships or bombers, whilst others wouldn't give a snap of the finger for all the food subsidies in the land. Many think all art a result of a wasted youth just as much as accomplishments at bridge or cricket are. But the nation as a whole might be not unsuitably defined as an amalgam of minorities, each for all and all for each. A nation without its artistic blood coursing through its veins, freely and unfettered, would be a poor one indeed. Thank heaven England has never been such a one.

It is not enough to spend vast sums on a palace of music for the mere performance of what already exists. The schools and academies are an even greater priority, and the homes of the people and their cultural and artistic environment yet more still. We shall be judged by our ability to continue producing great creative and executive artists, and both the National Theatre and the National Concert Hall should it ever materialise, will probably stand or fall on its stimulating effect, or otherwise, on our artistic impulses as a nation rather than on their ability to produce works of drama and music better than neighbouring theatres and concert halls can. Were we to look down on either from above after a hundred years of functioning, only to see them producing what exists to-day, then I would indeed say they had failed in their chief purpose.

A Practical Proposition

Music is so tremendously, so unalterably cosmopolitan. Its writing and its performance are alike

inspired by people from all the corners of the earth. Inasmuch as native drama, even the classics on their own, is more than sufficient to keep a national theatre fully occupied the whole year round, native music is as a mouse to a lion by comparison. I'm afraid the concert hall doesn't seem a practical proposition, short of a school of native opera, though it does seem little short of grotesque that a million pounds of public money can be offered to add one more of a thing of which we already have thirty or forty in London alone, whereas it is seemingly impracticable where there are but two of their kind, neither of which are in any way suitable for the main problem. But, regret it as we may, the very nature of music compared to the drama, other than opera, which makes its multiple and simultaneous presentation in excellent quality so easy and successful, does make the question entirely different from that of the national theatre.

The extinction of the aristocratic millionaire class was certainly the worst possible thing for music.

News from the Clubs

READING AND DISTRICT AMATEUR RADIO SOCIETY

President : Dr. Lemon (G2GL).

Hon. Sec. : Mr. L. Watts (G6WO), 817 Oxford Road, Reading, Berks.

THE first annual general meeting of the above society, under the new rules formulated last autumn, was held on April 3rd. The annual election of officers took place, the only changes being for the position of secretary and treasurer, who did not stand for re-election.

After the elections, Dr. Lemon gave his presidential address on the subject of "The Amateur Licence," with emphasis on the observance or otherwise of the conditions of licence.

Meetings are held at Palmer Hall, West Street, Reading, at 6.30 p.m. on the second and last Saturday of each month.

WIRRAL AMATEUR RADIO SOCIETY

Hon. Sec. : B. O'Brien, G2AMV, 26, Coombe Rd., Irby, Heswall, Cheshire.

THIS society continues its usual activities as reported last month. Prospective members will be welcome and may obtain full particulars from our hon. secretary, address above.

PETERBOROUGH AND DISTRICT RADIO AND SCIENTIFIC SOCIETY

Hon. Sec. : Mr. S. Woodward, 72, Priory Road, Peterborough.

THE society has a membership of 40 and since Christmas has run weekly lectures which have been very well attended. The society now have their own Club House.

At the General Meeting held in April the following officers were elected:

President, D. Crisp; vice-president, Mr. Barber; chairman, R. H. Whitley, vice-chairman, Mr. Smith; secretary, S. Woodward; treasurer, Mr. Frisby; assistant secretary, Mr. Moss; assistant treasurer, Mr. Bennett; technical adviser, C. J. Berridge, M.I.E.E.; communications adviser, F. Wood. All future meetings will be held in the Club House, 61, Padholme Rd.

THE RADIO SOCIETY OF HARROW

Hon. Sec. : J. R. Pickett, 93, Whitmore Road, Harrow, Middlesex.

FORTHCOMING Meetings are: June 15th: Transmitter problems by G4GB, G2TA and G2DD; July 13th: Loudspeaker quality reproduction, by a representative of Messrs. Goodmans (Demonstration).

Mr. Pickett is now Hon. Secretary of the society, Mr. N. J. Hanscomb having moved out of London for business reasons.

BURTON ON TRENT AND DISTRICT RADIO SOCIETY

Hon. Sec. : E. B. Harty (G3-BSL), Hill Cottage, Dunstall, Nr. Burton on Trent.

MEETINGS are held monthly, usually in the evening on the third Wednesday in the month, at the local Education buildings, Guild Street, Burton. These meetings are advertised in the local press.

The Secretary will be pleased to receive offers of lectures from firms interested, for next winter session.

The society is always on the look-out for new members, and a hearty welcome is always there. Further details can be obtained from the Secretary. The subscription is 6s. a year; 2s. 6d. for Junior members.

THE WEST MIDDLESEX AMATEUR RADIO CLUB

Hon. Sec. : C. Alabaster, 34, Loftham Avenue, Hayes, Middlesex.

THE Annual General Meeting of the above club was held on April 14th, 1948, and new officers and committee were appointed. The address of the new Hon. Secretary appears above.

Enthusiasts interested in any aspect of radio and electronics are cordially invited to join—the club caters for all tastes.

Regular meetings continue to be held from 7.30 to 10.30 p.m. on the second and fourth Wednesdays of every month at the Labour Club Rooms, Uxbridge Road, Southall, Middlesex.

THE TELEVISION SOCIETY (MIDLAND CENTRE)

AS television broadcasting will be extended to the Midlands in the near future, it is essential for all interested in this new science to have a common platform for study, discussion and practical construction. The Television Society, which was founded in 1927, have, therefore, formed a Midland Centre with headquarters in Birmingham. The inaugural meeting was held in April at the University in Birmingham, and the next meetings will take place on every first Wednesday in the month at 7 p.m., and after the summer recess during July and August the new session will begin with a meeting on September 15th at 7 p.m., the others following on every first Wednesday of each month.

Engineers, electrical contractors, and radio dealers alike will find it an advantage to become members of the Television Society, the programme of which caters for the scientist, and engineer, and also for the television salesman and service man. It is also intended to arrange a series of introductory lectures on the subject, and all interested are invited to write to the Lecture Secretary, Dr. W. Sumner, F.T.S., M.Inst.E., 169, Maryvale Road, Bournville, Birmingham, 30.

LEEK AND DISTRICT RADIO SOCIETY

A RADIO SOCIETY was recently formed at Leek, and will be known as the "Leek and District Radio Society." The secretary is Mr. W. L. Woodcroft, of 35, The Crescent, Leek, Staffs.

It was formed on April 9th at a meeting called by the new Secretary, and was attended by about 12, after a roll-call of absent would-be members, it was announced that 35 will be on the list for the next meeting.

The members of the nearby S.O.T. Radio Society welcomes this new Radio Club, and as soon as it is ready for lectures, etc., it will co-operate in the exchange of lecturers and ideas, also hopes that field days can be organised between the two clubs.

TELERADIO.

Adopt
"Peter Pan"



The latest addition to our range of first-class KITS.

Attractive A.C./D.C. 3 valve plus rect. med./long wave T.R.F. receiver with excellent performance and quality. All components available from stock. 3 full-scale blueprints and full list of parts required. 3/6.

Complete kit, 10 gns., plus P.T. £4/10/-.

Full illustrated lists (2½d. stamp) from

THE TELERADIO CO.
157, Fore Street, London, N.18.

LASKY'S RADIO

EX. A.M. RECEIVER TYPE R.3547. Containing in all 23 valves, ceramic bases valve holders. 9 EF50, 1 VR55, 1 VR56, 3 VR54, 2 VR116. Also including I.F. strip (Receiver unit 153), containing 6 EF50 and 1 EA50. Hundreds of resistances and condensers. 2 large pot/meters; 10,000 and 100,000 ohms. 11 other pot/meters, relays and other components. Size: length, 18ins.; width, 13ins.; depth, 8ins. Weight: 45 lbs. approximately.

Totally enclosed in a metal case.

IDEAL FOR TELEVISION CONSTRUCTION

LASKY'S PRICE: 79/6, carriage 5/- extra.

EX. A.M. MODULATOR UNIT TYPE 169. Containing 4 valves: 1 EF50, 1 5U4G, 1 CUB5 (special type) and 1 10 cm. klystron CV87. 3 neon stabilizers and holders, high voltage oil filled condensers, modulation transformers chokes, metal rectifiers. Size: length, 18ins.; width, 8ins.; depth, 7ins. Weight: 35 lbs. approximately.

Totally enclosed in a metal cabinet.

LASKY'S PRICE: 35/-, carriage 5/- extra.

EX. A.M. MODULATOR UNIT TYPE 155A. Containing 9 valves: 1 5U4G, 2 VU113, 5 CV73, 1 MH41. Relays, chokes, metal-rectifiers. Inductor condenser unit type 32 with modulation transformer. Size: length, 18ins.; width, 8ins.; depth, 7½ ins. Weight: 35 lbs. approximately.

Totally enclosed in a metal cabinet.

LASKY'S PRICE: 85/-, carriage 5/- extra.

SEND A 10/- STAMP TODAY FOR A COPY OF OUR NEW STOCK LIST AND BULLETIN OF OTHER EX. SERVICE BARGAINS.

LASKY'S RADIO,

370, HARROW ROAD, PADDINGTON,

LONDON, W.9. (Opposite Paddington Hospital).

Phone: Cunningsham 1979.

Hours: Mon. to Sat., 9.30 a.m. to 6 p.m.

Thurs., 1 p.m.

Full Value for Money!

CRYSTAL SETS. The New Lesdix Boudoir Crystal Set in charming Bakelite case, wound coil, condenser tuning, crystal detector and terminals, 17/6.



HEADPHONES. High resistance headphones for crystal reception, bakelite caps and case, metal headband and cord, light weight, 12/6.

SPIRAL AERIAL. For indoor use. Single, 30ft., 1/9; twin, 30ft., 2/9. Copper aerial for outdoor use, 50ft., stranded, 7/22, 3/6; 100ft., 5/-.

DYNAMOS. Special stocktaking bargains, 12 volts 10 amps., 1,400 r.p.m., new condition, 45/-; 30 volts 5 amps., 1,500 r.p.m., £5; 24 volts 30 amps., £4; 50-70 volts 10 amps., £15.

TELEPHONE, ex P.O. Hand combination telephone, bakelite body, switch in handle, and cord, 15/- each, 25/- pair. G.P.O. moulded bakelite hand-com. sound power type, with cord and plug, as new, 21/- each, 40/- pair.

TELEPHONES. Wall type constructors' parts, ex-G.P.O., comprising cabinet 8in. x 6in. x 3in., bracket, mike, transformer and condenser, mag. bell, switch-hook and contacts, hand mag. ringer, P.O. type receiver terminals and connection diagram, 35/- per pair.

HAND MAGNETO GENERATORS, 4 and 5 Magnet type, 75 volts A.C., 25 m.a., perm. steel magnets, wound armature, gearing in handle, 12/6.

TERMINAL BOXES. Highly polished black bakelite, 3½in. x 2½in. x 2½in., with ½in. centre filler and screwed cover, 2-pole, 5/16 connection studs and nuts, 10/50 amps., wall or ceiling fixing, 2/6 each, 20/- dozen, new.

BOURDON BOOST GAUGES. Plus 8 lbs. per sq. inch to minus 7 lbs., for testing blowers, vacuums, etc., bakelite case, luminous dial, new and boxed, 7/6. Low-pressure Bourdon gauge, movements complete and new, 5/-.



DIMMERS. Panel dimmer resistances, 100 ohms, ¼ amp., 50 ohms, ½ amp., totally enclosed for small light controls or safety switches on test circuit, 2/6.

SWITCHES. Dewar key panel type, 8-pole C/O. flush fitting, 5/-; Yaxley 3-pole 3-way, 3/6; 8-pole 1-way, 3/6. D.P.C.O. toggle switch, 250 v. 1 amp., flush panel, 3/-; S.P.C.O., 7/1-. 8-way Lucas switchbox, 3/6; 6-way, 3/-.

SEWING MACHINE MOTORS. 1/25 h.p., new, 230 v. A.C./D.C., square construction, totally enclosed with pulley belt and bracket, 24/10/-.

LIQUID LEVEL INDICATORS. Electrical type, less meter, geared float, watertight case, for reading on distant dial, 3/6.

PARCELS. 7 lb. useful oddments for the junk box. All clean, dismantled from Government and other surplus apparatus, 7/6 post free. (Not for Overseas buyers.)

Please include postage for mail orders.

ELECTRADIX RADIOS

214, Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

TWO AMPLIFIERS

covering all normal requirements for the highest quality record reproduction.

THE CONCERTO—12 watts—8 triodes plus rectifier. Separate treble and bass controls with two steps of bass boost. £27.10s.

THE KI—5 watts—7 valves. Compare this specification with any other 5-watt amplifier in this price region. Push-pull with negative feedback, distortion less than 1 per cent. Separate treble and bass controls. 17 gns. Available as a kit, 13 gns. Blueprint separately, 2/6.

Both Amplifiers are designed to take any type of Pick-up, Moving-Coil, Moving Iron, or Crystal, without additional pre-Amplifiers or Tone corrections. Radio input sockets are provided and tapped output transformer provides 15, 7 and 3 ohm impedances.

Send stamps for fully illustrated catalogue of Amplifiers, Pick-ups and Speakers.

CHARLES AMPLIFIERS LTD.

1e, Palace Gate

Kensington, W.8

(WEStern 3350)

VARLEY TRANSFORMERS, 250-0-250 v. 90 m.a., 6.3 v., 5 v., ideal 1155 power pack, 3/1/6; 350-0-350 v., 80 m.a., 4 v. or 6.3 v., 25/6; 120 m.a., 6.3 v., 32/6; 120 m.a., 4-4 v. windings, 42/6; 425-0-425 v., 120 m.a., 4 v.—4.4, 6 v.—4.4, 5 v.—3.4, 42/6; Condensers, T.C.C. Drillic, 500 v., 16x16.8/; 16x8, 7/6; 8x8, 5/9. Clips with cans, 8 mf., 3/9; 25 mf., 25 v., 2/-.

F.M. SPEAKERS, 6in., 16/6; 6in., 18/6; 8in., 20/-; T.F. TRANS., 485 kc/s, 12/- pair.

MULTI TEST METERS, B.P.L.: 1,000 o.p.v., £7/17/6; Pullin series 100, £9/10/0; Labgear ranger, res. and cap., £4/12/6.

ELECTROSTATIC meter, 0-2,000 v., 1/5/6; Pocket meter, 0-15v., 0-250 v., 18/9.

New boxed valves, 6H6, 5/6; EF50, EF54, 6/5, 6X5, 7/6; 6SH7 and 6AC7, metal, 9/6; 6V6, 10/6; 6 v. vibrator, Masteradio type, 15/-; Switches, small Yaxley 4 p., 3 w., 2/9; 3 p., 2 w., 2/3; 2 p., 2 w., 1/9; Rockman soldering guns, 12/6; 2 bit type, 18/-.

New goods, unrepeatable. Satisfaction guaranteed. C.W.O., C.O.D. Under £2 post extra.

RELIANCE RADIO SERVICE.

137, Lockhurst Lane, COVENTRY.

Phone: 85553.

MIDLAND INSTRUMENT Co.

BURGESS MICRO SWITCHES, 2/-; ALTI-METERS, sensitive K type, 20/-; MAINS MOTORS, 200/250 v. A.C./D.C., 5,000 r.p.m., ball bearings (converted motor generators), 30/-; BOND TESTERS, ohm-meters 0 to 1 ohms, less battery, 20/-; R.F. Meters, 0-350 m/a, 5/-; TRANSFORMERS, 230 v. output 50 v. 11 amp., 25/-; carriage 7/6. U.S.A. gunsight telescopes, contain 8 high-grade lenses, 15/-; RELAYS, 1,000 ohm, s.m., 1/-; CLAW movements, complete, for 16 m.m. cameras or projectors, 2/6. OXYGEN flow indicators, 6/-; PLUGS with jacks, 4-way, 2/6. ENGINE DRIVEN GENERATORS (D.C. dynamos), output 12 v. 750 watt, 30/-; carriage 5/-; ELIMINATORS, 200/250 v. A.C. output 120 v. 30 m/a. D.C., fitted neon stabilizer, etc., 40/-, post paid.

Also hundreds of other Radio, Electronic and Mechanical items, send 2d. with s.a.e. for current lists.

Orders over 30/- post paid. Our C.O.D. service is cancelled for the time being.

Moorpool Circle, Birmingham, 17

Tel.: HARborne 1308 or 2664.

SPARKS' DATA SHEETS

Provide detailed Instructions with Easy-to-follow Full-size Constructional Prints of Tested and Guaranteed Designs.

THE "CRUISER"

An All-dry High Efficiency 3-valve T.R.F. Circuit.

Three Pentodes. Fine range, power and quality. Low cost. Wide selection of stations on M.L. waves with short aerial. Specially designed for those wanting a compact, all-dry, trouble free design for the home, caravan, camping, yachting, etc. Data Sheet. ... 2/6

THE "OLD FOLK'S TWO"

An A.C./D.C. 2-Valve Plus-Rect. for those who cannot be bothered with tuning. 3 Station Selection by Switch. L/M Waves. 2/9

THE "CUB." A Fine Little A.C./D.C. 2-Valve. Plus Rect. M.L. Wave receiver. Powerful, Inexpensive and Simple to Build ... 2/6

THE "CADET" A.C./D.C. AMPLIFIER. A full 3! Watts Output. Vol. and Tone Controls. Good Quality. Ideal for P.U. ... 2/6

THE "CHALLENGER" PORTABLE. An amazing A.C./D.C. Portable. 3-Valve plus Rect. M.L. Waves. Power and Quality ... 2/9

MANY OTHER DESIGNS for Sets and Amplifiers available. Send S.A.F. for latest List and please include stamp with order. Prompt Service. Components supplied.

L. ORMOND SPARKS (P),
9, PHOEBETH ROAD,
BROCKLEY, S.E.4.

(Nearest Station : Ladywell, S.R.)
Telephone : Lee Green 0220

"DORSET" SUPERHET 2/6 CIRCUITS

A.C. FIVE. Three wave.
A.C./D.C. FIVE. Three wave.
BATTERY FOUR. 1.4v. Three wave.
BATTERY PORTABLE.
Four Valve medium and long.
Six Valve A.C./D.C. AMPLIFIER

BUILD A "SUPER" SET

Theoretical circuit, under chassis layout, above chassis layout, heater wiring, group board assembly and point to point wiring instructions, also parts list. Can be made without previous radio experience. Chassis, coil packs, group boards, I.F.s, 5in. Speakers, in stock.

Theoretical circuit and price list only 2/6d.

WELDONA RADIO ACCESSORIES, LTD.
38, GLOUCESTER ROAD, BRIGHTON

HIGH "Q" IRON CORED COILS

of Unsurpassed Quality for Discerning Amateurs

AERIAL, H.F. OR OSCILLATOR, short, medium or long wave, size of former 1in. x 1in. 3/9 each.
INPUT FILTERS, 465 kc/s., parallel or series tuned, 3/9 each.
I.F. TRANSFORMERS, 465 Kc/s., midgeet, permeability tuned, size 1in. diam. x 1 1/2 in. 9/6 each.
I.F. TRANSFORMERS, standard, 465 Kc/s., permeability tuned, size 1 1/2 in. square x 3 1/2 in. high, 8/6 each.
All coils fitted with adjustable iron cores; and supplied with circuit diagram.


TERMS : Cash with order or C.O.D. on orders over £1.

TRADE INQUIRIES INVITED

MONOCHORD RADIO
(Established 1929)
17, Streatham Hill, London, S.W.2
Phone : Tulse Hill 1051.

H. P. RADIO SERVICES LTD.

OFFER

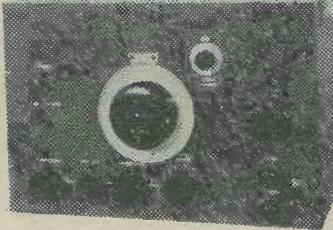

Brand New Ex-R.A.F. R1224a Battery Reception Receiver.

5 Valve Superhet of the Highest Class. 3 Wavebands x 33-70 metres, 70-150 metres, 150-300 metres. Valves 2VP2's, FC2A, HL2, PM2A, all included. Has R.F. stage. Muir-head dials, two Output Jacks. Air Ministry grey cabinet, 15ins. long, 10ins. high, 9ins. deep. Requires Aerial, 120v. H.T., 2v. L.T., 9v. C.B., and Loudspeaker or phones to put into immediate operation. All leads clearly marked.

Designed specially for long distance high quality reception.

We have such a high opinion of these receivers that we unhesitatingly GUARANTEE Satisfaction or Money Returned within 7 days. Price 25/10s. Carefully packed. Carriage Paid per Pass. Train. Instant Delivery.

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House
55 County Rd., Walton, Liverpool, 4
Tel: Aintree 1445 Etab. 1935

COULPHONE RADIO

"THE RETURN OF POST MAIL ORDER SERVICE"

58, Derby Street Ormskirk, Lancs.

New Goods Only-C.O.D. or cash with order. All orders over 5/- post free. A few of our lines are listed below, send 2/6 stamp for latest 24-page catalogue and valve list.

Valves.—All B.V.A. and Tungram, including American. Eddystone short wave gear. S.W. Manual, 2/6. Bernards Radio Books. Mains Transformers.—Interleaved and Impregnated. For 200/250 v. mains, with 4 v. or 6.3 v. and 5 v. L.T.s. 250 v. 100 mA. 25/-; 300 v. 100 mA. 27/6; 350 v. 100 mA. 28/6; 450 v. 200 mA. 45/-.

Smoothing Chokes.—40 mA., 5/-; 60 mA., 6/6; 90 mA., 7/-; 100 mA., 7/6; 200 mA., 22/6.
Speaker Transformers.—Midgeet Power/Per. 40 mA., 5/6. Std. size Push-Pull Universal, 60 mA., 7/6; Heavy Duty P.-P., 22/6. Extra H.D. 100 mA., 37/6.

Mains Dropper Resistors, with feet and two sliders, 2 amp., 4/6; 3 amp., 5/-; Resistors 1w., 6d.; 1w., 9d.

Loud Speakers P.M., 21in., 27/-; 31in., 29/6; 5in. 20/6; 8in. 23/6; 10in. 35/6. With Trans. 5in., 24/6; 10in., 42/6.

Weymouth Tuning Coil Pack.—Completely wired. Short, Medium and Long Wave Superhet type for 465 kc/s. I.F. 36/6. Midgeet I.F.T.s. 18/9.

Line Cord, 60/70 ohms per foot. 3amp. 2-way, 2/3; 3-way, 2/6; 14/35 flex. 6d.; 23/36, 9d. Slewing, 3d. yd.

Tuning Condensers.—Midgeet 2-gang .0005 with 2-speed drive, 16/6. L/Dr. 11/6. Undrilled Polished Aluminium Chassis, 3in. deep, 10in. x 6in., 10in. x 8in., 8/6; 12in. x 9in., 10/6; 14in. x 9in. and 16in. x 8in., 11/6; 20in. x 8in., 12/6.

EXCLUSIVELY MAIL ORDER.

SOUTHERN RADIO'S WIRELESS BARGAINS

RADIO PUBLICATIONS : RADIO VALVE MANUAL. British and American Alternatives and Equivalents. 3/6. FREQUENCY MODULATION MANUAL. 3/6. SOUND EQUIPMENT MANUAL. 2/6. Publications previously advertised still available. Full list, 2/6. Postage on books, 3d. **A.C. MOTORS,** 200/250 volts, one-eighth h.p. 2.00 p.p.m. Consumption one-half amp. Ideal for light work. Brand new, 55/-, plus 5/- carriage. **R.A.F. BOMBSIGHT COMPUTERS.** Brand new with Sperry gyroscope. 2-23 volt motors. Gearing, counters and hundreds of other components. £3. carriage paid. **R.A.F. RT TESTERS.** 2.500/6, 700 kc/s. 45/120 metres. two valves. In metal carrying case with leather handles, 16in. x 10in. x 6in., 20/-, carriage paid.

TANNOY CARBON MIKE INSERTS, 2/6 each, post 3d. **INSPECTION LAMPS,** with cord and Lucas plug, 3/6.

INPUT TRANSFORMERS. 50 : 1 or 7 : 1 mu metal 5/6. **DIPOLE AERIALS** (folding), H.V.F., 4/6.

LUBRA HOLE CUTTERS. For use on wood, metal or plastic, 5/6. **75 PF. MIDGET CONDENSERS.** Twin gang, 5/-; single gang, 2/6, post 6d.

THROAT MICROPHONES. New with 3ft. lead and plug, 5/-.

THROAT MIKE INSERTS, 1/6 each. **PERMANENT CRYSTAL DETECTORS** 2/6 each, post 4d.

H.T. BATTERIES. 7 1/2 v. l.t. and 90 v. h.t. For M.C.R.I. receivers, 6/6, post 9d.

WESTECTORS. W.X.6 and W.112. 1/- each, post 2/6. 9/- per doz., post 6d. **oil-FILLED CONDENSERS.** .1 mfd 7,500 v.d.c. and .5 mfd 7,000 v.d.c., 7/6 each, post 9d.

GEARED DIAL DRIVES. 4 : 1 ratio, 3/6.

SOUTHERN RADIO SUPPLY LTD., 46, Lisle Street, London, W.C.2. GERard 6653.

HIGH FIDELITY

We welcome all enthusiasts to our new premises. We carry stocks of Partridge and Varley Transformers and Chokes, matched output valves, matched resistors, high quality loudspeakers, P.U.s., gramophone motors, baffles, Bass Reflex cabinets, and all components for High Fidelity Receivers and Amplifiers. Complete equipments are also available. Our price list is available and we will be glad to send you a copy on receipt of your address and 2/6d. stamp.

ROGERS DEVELOPMENT CO, 106, HEATH STREET, HAMPSTEAD, LONDON, N.W.3.

Telephone : HAMpstead 6901.

JEFFERSON-TRAVIS VIBRATOR POWER PACKS

New ex-A.M. smart black crackle case, 4in. x 7in. x 6in., weight 10lb. Input : 12 volts D.C. (heavy sheathed cable with crocodile clips for attachment to accumulator). Output : Fully smoothed H.T. 150 volts at 30 mA. or 120 volts at 50 mA. Also L.T. and grid bias. A bargain at 19/6 each, post and packing 1/6 extra.

FIVE PIN PLUGS AND SOCKETS (Bellini-Lee type). Ex-A.M., 2/4 each complete. Seven pin do., 2/10 each, post free.

FIVE CORE CABLE

71d. per yard, seven core do., 9d. per yard

PANEL LIGHTS

M.E.S. fitting. Green, blue or clear, 9d. each, 7/6 per dozen, all post free.

Send stamp for bargain lists.

A. McMILLAN,

5, Oakfield Road, Bristol 8.

Impressions on the Wax

Review of the Latest Gramophone Records

AMONG organists the name of Goss-Custard is a household word. As organist of Liverpool Cathedral he has command of the largest cathedral organ in the world. America has what is the biggest organ in existence, but as it is in the Convention Hall at Atlantic City, N.Y., Liverpool still has the largest instrument in a building of cathedral status. On this magnificent instrument, then, Harry Goss-Custard comes back to records after an interval of some years, with Walford Davies' well-known tune "Solemn Melody" coupled with the equally famous "Trumpet Voluntary."—*Columbia DX1477*.

Sir Malcolm Sargent conducting, the Liverpool Philharmonic Orchestra give a fine rendering of "Valse Triste" which with "Finlandia" was for many years almost the only example of Sibelius' music known well in Britain. It is, of course, a minor work compared to the massive things that are the composer's real masterpieces, but it is extremely picturesque and its long popularity is fully deserved. On the reverse side is the tune known as "Air on the G String," which comes from the third orchestral suite of the four Bach wrote, whether at Leipzig or at Cothen seems uncertain. Both of these pieces are beautifully handled by Sir Malcolm Sargent on *Columbia DX1479*.

Another record which will receive a ready welcome by music lovers is "The Bartered Bride, Overture," played by the Sadler's Wells Orchestra conducted by Lawrence Collingwood on *Columbia DX1478*. Sadler's Wells has often given us colourful performances of this opera in the course of its admirable productions of famous musical stage works in English, and the Sadler's Wells Orchestra gives a sparkling performance.

Vocal

Like most of the songs of Modeste Moussorgsky, the "Song of the Flea" is strikingly direct and realistic, with a sardonic twist admirably brought out by Osear Natzka on *Columbia DB2363*. This New Zealand bass has lately distinguished himself at Covent Garden in the part of Sarastro. Natzka has Russian blood in him, and is the first singer from New Zealand to take a principal role at Covent Garden. On the reverse side of this record he sings "Oh, Could I But Express in Song." Natzka is accompanied on the piano in each case by Herbert Greenslade.

Listeners to the B.B.C.'s Third Programme and to "Music in Miniature" know Margaret Ritchie well, and discerning critics have praised her renderings of Schubert especially. The beautiful clarinet obligato to "The Shepherd on the Rock," which she sings in German on *H.M.V. C3688*, is in the expert hands of Reginald Kell, and Gerald Moore accompanies on the piano.

Isobel Baillie's singing of "The Kingdom—The Sun Goeth Down, Op. 51," on *Columbia DX1443* once more gives us an instance of the flawless tone and style which have brought her to the highest peak of excellence in oratorio. Musically, Elgar's

"The Kingdom" is the equal of the two preceding oratorios, "Gerontius" and "The Apostles." With them it forms a perfect trinity.

Light Music

The Queen's Hall Light Orchestra conducted by Sidney Torch have chosen two pieces from the Maurice Ostrer picture of "Idol of Paris" for their latest recording. The two pieces "Illusion" and "Dedication" are both by that talented composer Mischa Spoliansky, who composed the music for such films as "Sanders of the River," "Wanted for Murder" and "King Solomon's Mines." They are both attractively treated and the composer is at the piano.—*Columbia DX1458*.

"Malaguena"—a piano piece from the suite "Espagnole"—was composed by Ernest Lecuona, one of America's foremost writers of Latin-American music. It is a lively Spanish dance similar in nature to the fandango, and on *H.M.V. B9637* the melodic and harmonic peculiarities of the traditional music have been successfully captured by George Melachrino conducting the Melachrino Orchestra. On the reverse is "Lady of Spain," which has been presented in a variety of musical settings, and it is admirably played by the Melachrino Strings.

Ever since Donald Phillips' "Concerto in Jazz" was first broadcast and recorded by Charles Shadwell's orchestra in 1946, the work has steadily grown in public favour. One of the primary distinctions of "Concerto in Jazz" is that the young composer has evolved a symphonic style embodying some of the main characteristics of jazz music. It has now been recorded by the famous Skyrockets Orchestra specially augmented by a large string section. A particular point of commendation is that the piano passages feature the virtuosity of Pat Dod—*H.M.V. C3722*.

Variety

In "Grandfather's Clock" and "Three Little Fishes" the musical and comedy talents of the highly original Radio Revellers are showpiece with considerable effect on *Columbia FB3394*.

From jazz rhythms to Latin-American themes, every kind of music is skilfully executed by Reginald Dixon, versatile organist of Blackpool's Tower Ballroom. Following his delightful samba version of "Tico Tico," *Columbia FB3362*, Reginald returns to Spanish-American strains with a selection of well-known tangos which should satisfy the most exacting lover of this graceful dance—*Columbia FB3392*.

The combined talents of vocalist Carole Carr and arranger Denny Vaughan are displayed in the latest recording by the Geraldo Orchestra. "Where Flamingos Fly," with lyrics added by Jimmy Kennedy, is given the polished vocal and orchestral treatment that is the hallmark of a Geraldo performance. Ann Carbutt's "Sometimes I Think of Spring," already a favourite over the air, is orchestrated by Denny Vaughan and sung by Carole Carr—*Parlophone F2290*.

THESE ARE IN STOCK

RADIO RECEIVER DESIGN, Volumes 1 and 2
by K. R. Sturley. 28s. each. Postage 8d.

RADIO MAINS SUPPLY EQUIPMENT
by E. M. Squire. 12s. 6d. Postage 4d.

KLYSTRONS AND MICROWAVE TRIODES
Edit. by Hamilton, Knipp and Kuyper. 45s. Postage 9d.

MICROWAVE RECEIVERS
Edit. by Van Voorhis. 48s. Postage 9d.

WIRELESS SERVICING MANUAL
by W. T. Cocking. 10s. 6d. Postage 4d.

CATHODE RAY OSCILLOGRAPH IN INDUSTRY
by W. Wilson. 18s. Postage 6d.

TELEVISION SIMPLY EXPLAINED
by R. W. Hallows. 9s. 6d. Postage 4d.

THE MATHEMATICS OF WIRELESS
by Ralph Stranger. 7s. 6d. Postage 4d.

NEWNES ELECTRICAL POCKET BOOK
7s. 6d. Postage 4d.

RADIO RECEIVER CIRCUITS HANDBOOK
by E. M. Squire. 6s. Postage 4d.

ELECTRICAL ENGINEER REFERENCE BOOK, 1948
By Molloy, Say, Walker. 42s. Postage 9d.

THEORY AND APPLICATION OF MICROWAVES
by Bronwell and Beam. 36s. Postage 9d.

RADIO ENGINEERING, Volume I
by E. K. Sandeman. 45s. Postage 9d.

THE CATHODE-RAY TUBE HANDBOOK
by S. K. Lewer. 6s. Postage 4d.

THE WIRELESS WORLD VALVE DATA
2s. Postage 2d.

We have the finest stock of British and American radio books. Complete list on application.

THE MODERN BOOK CO.,
(Dept. P.5), 19-23, Prad Street, London, W.2.

VALUE! MATT has it

Order with confidence.
Full satisfaction assured.

SPECIAL OFFERS

HEADPHONES.—W/Lead and Jack Plug, 5/- pair (boxed 2 pairs), 54/- doz. pairs.

LINE CORD.—3 amp. 60 ohms per ft., 2-way, 1/6 yd.; 3-way, 2/- yd.

TUNING CONDENSERS.—0005 POLAR MIDGET, 11/6. 0005 Standard, 5/6.

CONDENSERS.—002, 2/6 doz., .006, 3/- doz., .1, .01, 9/- doz., 16 mfd/500v. canned, 8/6. 8 mfd/350v. midgets, 3/-, 8 mfd/450v., 4/-, 4 + 4 block, 3/-.

SPEAKERS.—P.M. (less trans.), 5in., 14/-; 6in., 24/-; 8in., 27/6. Trans. to match, 5/6. Multi Ratio Do., 7/6.

VOL. CONTROLS.—All values (Centralab), L.S. 3/6; W.S. 4/9. Postage Extra.

LARGEST ASSORTMENT OF VALVES ALWAYS IN STOCK. U.S. HAVE YOUR ENQUIRIES. 29, Castle Street, Kingston-on-Thames, Surrey.

MATT RADIO SERVICE
Kingston 8353

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925.

"NAPP" mains transformers, primaries. All 0-200, 220, 240 volt 50 c/s.

T.710. 350-0-350 volt, 80 m/a; 6.3v. 3a.; 5v. 2a. 26/6

T.718. Ditto but 100 m/a. 30/-

T.719. 350-0-350 volt 100 m/a, 4v. 4a.; 4v. 3a. 30/-

All above are fully shrouded and screened.

T.720. 350-0-350 volt 150 m/a; 6.3v. 4a. tapped at 4 volt; 5v. 3a. tapped at 4 volt 39/6

T.717. 275-0-275 volt 90 m/a; 6.3v. 3a.; 5v. 2a. Drop through chassis type half shrouded. 30/-

PROMPT SERVICE. PHONE LUTON 2677.

COVENTRY RADIO
191, DUNSTABLE ROAD, LUTON, BEDS.

WE OFFER

A large range of used and new Test Equipment, Converters, Recorders, Amplifiers, Motors, Transformers, etc. All guaranteed and at very attractive prices.

We buy good modern used equipment of all types for spot cash.

UNIVERSITY RADIO LTD.

22 LISLE STREET, LONDON, W.C.2.
Tel.: GER 4447 and GER 8582.

In addition to the usual comprehensive selection of Radiogram and Amplifier equipment, including Motors, Pickups, Cabinets, Amplifiers, Speakers, etc., are the following outstanding bargains in ex-Govt. equipment. Brand new headphones, 3/3 pair, post free. Mic or Speaker unit, 3/6, post free. S.a.e. brings full detailed list.

Radio Unlimited.

16, Carnarvon Road, Leyton. Caller clients. 272, Romford Road, Forest Gate, E.7. Opp. Princess Alice.

SAMSONS SURPLUS STORES

MASTER OSCILLATOR BY R.C.A. Frequency range 1-10 mc/s. Output sufficient to drive any P.A. Uses 807 valve in extremely stable circuit. Very accurate dial calibrations with unique dial mechanism. Metering of doubler or buffer stages grid current included. Housed in solid cast case with shock absorber mountings. Supplied brand new with accessories and operating manual. As from makers: 25 10s. 6d., carriage, 5/- No C.O.D.

169-171, Edgware Road, London, W.2. Telephone: PAD 7851.

BULGIN

A Name famous in Radio

A. F. BULGIN & CO., LTD.
Bye Pass Road, Barking, Essex
Tel.: RIPpleway 3474 (5 lines).

"TESTGEAR" RESISTORS

Wound on ceramic formers with nickel chrome wire

5 WATT WIREWOUND.—50 to 2,500 ohms, 1/6 each. 3,000 to 50,000 ohms now available at 2/3 each.

10 WATT WIREWOUND.—50 to 2,500 ohms, 2/- each. (All resistors are colour coded).

TESTGEAR MAINS DROPPERS.—Type A. 3in. high, 1 1/2in. dia., 1,000 ohms 2 a., 600 ohms 3 a., 4/9 each. 1,500 ohms 15 a., 5/-; Type B. 3 1/2in. high, 1 1/2in. dia., with 2 adjustable clips. 1,000 ohms 2 a., 600 ohms 3 a., 7/6 ohms 3 a., 5/- each. 1,500 ohms 15 a., 5/6.

ADJUSTABLE 5 WATT WIREWOUND.—Size, 2 1/2in. x 1in., 50, 100, 150, 200, 250 ohms only. 1/9 each.

TESTGEAR I.F. TRANSFORMERS.—An entirely new design developed from successful type used in Service equipment. Iron cored coils, ceramic trimmers. Accurately adjusted to 465 kc/s. Per matched pair, 17/6.

MORTONS, 13, CAMDEN ROAD, WALTHAMSTOW, LONDON, E.17.

DUNK & HEALEY "WESTALITE" METAL RECTIFIERS


Westinghouse's latest development in Semi-midget Rectifiers. 60 m/A, 250 v. Type 47. (List 18/6). Our Price 7/6 each. 120 m/A, 250 v. Type 48, 12/6 each. Our 40 v. 2 amp. 230 v. 50c vs. Primary Transformer. Heavy cast shrouds, fitted terminal block, high voltage insulation. Perfect for charging, etc., room on bobbin enables it to be easily rewound to any secondary voltage. (up to 120 watts). Brand new, 16/- each.

EF50. Brand new in original manufacturer's cartons. 7/6 each.

S. C. BROWN, high impedance lightweight headphones, brand new, boxed, 12/6 a pair. Please add 8d. for post. 2/d. stamp for latest list. Mail Order only.

67, Osnaburgh St., London N.W.1.

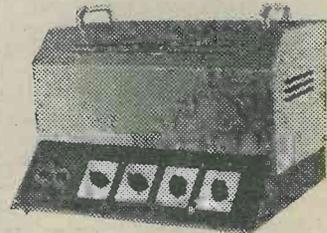ATTENTION, PLEASE!
— A really SOUND Amplifier Case



Two Colour Crackle finish 15" x 10 1/2" x 9 1/2"
£3-15-0. Trade enquiries invited. Detailed leaflet from
BUCLEUCH RADIO Manufacturers,
Meville Terrace, Edinburgh, 9

Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

German Valve Details

SIR,—I am very pleased to say that my letter in your May issue has already had a large response and that I can be of help to so many who in return are very kind to me. Contrary to public opinion a Scotsman has even offered to send me valve data without asking for something in return. But, of course, I am also willing to help without return offers.

Just a little favour I ask from you: Please draw attention to the fact that ordinary postage to Germany is 3d., and that books, papers, etc., can be sent by book post at the rate of a few pence (I do not know the exact charges).

With the best thanks for your kind attention.—
WERNER MAASS (Hamburg).

Anti-static Aerial

SIR,—The article on an anti-static aerial unit in the May issue of PRACTICAL WIRELESS makes me want to mention my own arrangement.

My particular district is a hot-bed of interference on all wavelengths, and after several experiments to get rid of noise I finally used a 6ft. length of aluminium tube as the aerial with a length of television 80 ohm co-ax. as downlead. The curious part of the system is this—the aerial is vertical and the cable inner is connected to the bottom of its length; but the cable outer screen is left floating at both ends, only the inner going to the set aerial terminal. This completely suppresses all noise, which it doesn't do if the outer screen is earthed.

Perhaps some reader can supply the reason why.—
S. A. KNIGHT (Wellingborough).

Correspondents Wanted

SIR,—May I take this opportunity of congratulating you on the high standard of your magazine.

I should like to correspond with another amateur of about my age (I'm almost 17) interested in short waves and receiver construction, preferably not too far from my home.—
P. M. TALL (132, Wilmslow Rd., Withington, Manchester, 20).

SIR,—I would be pleased to correspond with any reader interested in wireless, who is between 15 and 16 years old. I would prefer a boy living in Lancashire. I am not very keen on short-wave.—
J. CLEMENTS (29, Rickhayes, Wincanton, Somerset).

Reader's Thanks


SIR,—Please allow me to tender my sincere thanks to all your readers who readily responded to my letter of December, 1947, in PRACTICAL WIRELESS, by giving me information, circuit diagrams, etc., re connections for set Mk. II B19.

Grateful to friends in Germany and Middle East.—
RUFUS ALLEN (Lagos, Nigeria).

Reducing Phase Shift

SIR,—I was very interested in the article on the above subject in your November issue last year and have been trying out the scheme. I used an old transformer I had by me and rewound it, but am doubtful about one point. It was not clear to me from the article just how the separate windings (particularly the feed-back winding) should be arranged on the core, and I should be glad if you could give me any information on this point.—
R. STEBBINGS (Harrow).

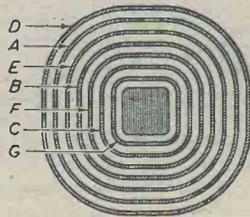[The accompanying illustration will no doubt help to solve the difficulty if studied in conjunction with Fig. 1 in the article in question. Windings A, B and C are the primary, D, E, F and G the secondary windings. In Fig. 2 in the article winding F was used as the feed-back section, the speaker being connected across D, E and G in series.—ED.]



Amateur Results

SIR,—I am 14 years of age and have been a reader of your excellent magazine for 2½ years now and am very interested in ham radio. My RX is a 1-v-2 battery set using a 35ft. indoor aerial. Here are a few 'phone stations I have logged recently on 14 Mc/s.
C7TY, UA1GB, VO2BP, CN8BV, UA3KAB, VO4Q, LO2JC, UL2CK, VO6X, CO7VP, VE1AX, VS7PS, FA362, VE1BH, ZB2A, FT4AI, VE4IF, ZB1AI, OX3BD, VO2BH, ZC6JL, ZS6JC and nearly 40 Ws.—
G. R. KELMAN (Leicester).

Cutting Wanted

SIR,—I have been a regular reader of PRACTICAL WIRELESS for some years now, and I find that I have some pages missing from the January, 1943, issue, owing to the fact that I built the wartime midget A.C.-D.C. receiver which appeared in that particular issue. I removed the pages for reference purposes, and now I am demobilised from the Army I wish to carry out one or two repairs to my receiver and I need the circuit for reference. As all back numbers are out of print, I wonder if any reader can help me with this back number?—
D. M. SMITH (69, Painswick Road, Cheltenham, Glos.).

Modified R1116

SIR,—I have been following "Open to Discussion" in PRACTICAL WIRELESS for the past 12 months for any help in converting the R1116 receiver to L.S. output. I have the circuit and full details of components and have converted the set to loudspeaker output, but get serious distortion

at normal L.S. volume. I have quite a long experience as an amateur, but simply cannot find where the trouble is, after trying literally everything. Can any reader give me details of successful conversion?—N. V. FORTNAM (29, Abbotsford Road, Goodmayes, Essex).

Car Radio Problem

SIR,—On two occasions having fitted a dropper resistance in series to enable a 6 v. car radio to be used from a 12 v. battery, I find that I get twice the amount of vibrator noise than if used on a 6 v. battery, and even worse when tuned to a signal. Having tried chokes and condensers in all positions on the feed line, I am still unable to cure the trouble. I might add that if I tap the 12 v. battery at 6 v., and couple it to the output side of the dropper resistance, the noise reverts to normal. I would be glad if anyone can suggest the cause of the trouble, as I do not like the practice of tapping the battery at 6 v. and so put all the load on one half.—J. PERRY (Woking, Surrey).

Television Interference

SIR,—I wonder if any data is forthcoming regarding the various forms of interference on television. I am near an aerodrome and get a fluctuating picture when aircraft fly overhead. I have tried to collect data showing the form the distortion, etc., takes when the plane is in various positions, but unfortunately cannot see the picture and be out in the garden at the same time. The lightning recently also affected the picture, but synchronism was entirely unaffected. Is this due to my circuit, or is it usual? I should be glad to know whether anyone has yet succeeded in collecting data on the distortion of the received signal under special conditions, and whether the fading caused by aircraft can be overcome.—W. J. COX (Colindale, N.W.9).

Hi-Fi Radiogram

SIR,—I have been experimenting for some time to try to build a high-fidelity radiogram. I have tried various circuits published in your magazine as well as those in other periodicals. Each has had some merit, but has failed to give exactly the results I required. I wonder if you could give a design for a set which would meet my needs—not too dear, although I am prepared to spend a fair amount on it, and if possible, using much of the surplus gear, valves, etc., which are now available.—G. REECE (N.W.5).

[It is difficult to design a receiver which will meet every need of every individual reader. One will like more top note response than another, and so on. It is just the same with the programmes which are broadcast—it is not possible to please everyone all the time. However, we think the Hi-Fi Radiogram, the construction of which is commenced in this issue, will interest you, as it has a number of separate adjustments for tone, etc., which should enable you to obtain the response curve you require, and it is flexible, using a large quantity of ex-service equipment.—ED.]

The Amateur Spirit

SIR,—I must write and thank you for your courtesy in publishing my letter, and also to thank the many readers who came to my assistance. I had no idea the amateur fraternity was so wide-spread and of such friendship. I am unable to devote the time necessary to replying to everyone individually, but take this opportunity of thanking everyone who wrote to me and especially to those who sent cuttings, photos, etc. They have been of the greatest help. I have replied direct to those who enclosed stamped envelopes.—G. BEST (Breckon).

For Dublin Readers

SIR,—May I take up some of your valuable space to make an appeal to Dublin S.W.L.s? Will any of those living in the South City area interested in forming a club—with the object of pooling information and ideas and the ultimate object of establishing a club S.W. station—get in touch with me at the following address by letter?—KEVIN MOLAN, (63, W. Mount Street, Dublin, Eire).

Ex-Service Equipment

THE co-operation of readers is sought in helping others out of difficulties regarding items of surplus gear as follows:

M. B. Henville, of Chapin Road, Wembley, Middx, requires details of the 12- and 6-pin connectors on the front panel of a Power Supply and L.F. Amplifier Unit No. 1, ZA.21331 M.R. Ser. No. 16994, and the possible output of the vibrator section.

W. Marshall, of "Avalon," Finglesham Road, Sholden, nr. Deal, Kent, requires details of receiver and power pack No. 111 Mk. II (3.1-15.5 Mc/s).

B. Blincoe, 11, Adams Road, Compton, Wolverhampton, has a B.50 receiver and is unable to trace what type of valves it uses.

J. F. Paine, of 48, Worton Way, Isleworth, Middx, has a "V.I. 108," of which he requires data.

B. Taylor, 10, High Street, Quarry Bank, Brierley Hill, Staffs, would like help regarding the 3-pin socket on a TR/9H R.A.F. receiver, and would like to hear from any reader who has succeeded in modifying the tuning arrangements.

S. Limning, Hall Cottage, Wainfleet, Lincs, has receiver type 3170A, and would like data which is now no longer available from Air Ministry.

E. McMillan, 8, Waldershaw Road, Forest Hill, S.E.23, wishes to convert radar unit AC/APA-1 into an oscilloscope, but cannot trace out the circuit. Has anyone a copy of this?

G. E. Cousins, of 3, New Monks Cottages, Upper Brighton Road, Lancing, Sussex, would be grateful to any reader who could supply information concerning receiver type R.1355.

G. Fooks, 31, Percy Road, Yeovil, Somerset, has an 81-B receiver, and requires details of the circuit and plug connections.

L. N. McCord, of 49, Kangaroo Street, Manly, N.S.W., Australia, is unable to obtain in that country details of receiver R.1116 and amplifier A.1134A. He would like to hear from any readers who possess the receiver, with a view to exchanging performance data, aerials, power pack, etc.

A. Milkam, 18, Giffels Terrace, St. Leonards-on-Sea, Sussex, has receiver 18 Mk. III, but cannot obtain circuit details of battery connections.

K. Evans, 17, Cambridge Street, Hawthorn East, E.3. Victoria, Australia, requires the original circuit of the MCR.1, together with power pack.

G. Ford, of 2, Norris Road, Stanfields, Tunstall, 8-O-T, would like to get into touch with any amateur who has had any experience with ex-Service GAK3, 9001, 9002 and 9003 valves.

G. Richardson, 36, Renwick Road, Antree, L'pool, 9, requires information on receiver BC.455.B.

J. Baldwin, The Dingle, Habberley Road, Bewdley, Wores, would like to contact any readers who are interested in ex-radar equipment and have a circuit of an indicator unit No. 96, Ref. 100B/198, and oscillator unit type 221, Ref. 10VB/8034.

E. Northcott, 60, Harwell Street, Plymouth, Devon, wishes to add an "R" meter to a receiver, R.107, and would like to contact any reader who may have carried out this modification.

I. H. Stevens, 29, Fron Terrace, Rhyl Road, Denbigh, N. Wales, would be grateful for any information concerning the U.S. Army receiver, BC.455.B.

CLASSIFIED ADVERTISEMENTS

RATES: 3/- per line or part thereof, average five words to line, minimum 2 lines, Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

8th SALE.



By Order of the Minister of Supply. WITHOUT RESERVE. **ASHCHURCH, GLOS.** Within 2 miles of Tewkesbury and 7 of Cheltenham. Sale by Auction

A large Quantity of GENERAL STORES, including:—
RADIO AND ELECTRICAL equipment, Wireless Receivers, Cables, etc.
SURVEYING EQUIPMENT. Theodolites, Planimeters, Dumpy Levels, Drawing Boards, Stationery, etc.
PHOTOGRAPHIC MATERIALS, Chemicals, Glazing Presses, Printing Paper, etc.
PAINT, VARNISH AND ENAMEL.
VEHICLES, comprising 13 Jeeps, 2 Cars, 3 Trucks, Trailers and Tyres.
HAND TOOLS, etc.

Auctioneers: **BRUTON, KNOWLES & CO.,** in conjunction with **GEORGE HONE**
SALE DAYS: TUESDAY, WEDNESDAY, THURSDAY AND FRIDAY, JUNE 15th, 16th, 17th, 18th and JUNE 22nd, 23rd, 24th and 25th, 1948 at 11 o'clock punctually each day.

VIEW DAYS: THURSDAY AND FRIDAY, JUNE 10th and 11th, and MONDAYS, JUNE 14th and 21st. From 10 a.m. to 4 p.m., and on Sale Days from 9 a.m. to 10.45 a.m.

CATALOGUE: Covering complete sale, price 6d. (Postal Orders ONLY) may be had of the Auctioneers, Bruton, Knowles & Co., Albion Chambers, Gloucester (Tel. Gloucester 2257), or of George Hone, Tewkesbury (Tel. Tewkesbury 2110).

NOTE: Applications for catalogues to be sent in envelopes marked ASH top left-hand corner.

ADMISSION WILL BE BY CATALOGUE ONLY.

R.S.G.B. TECHNICAL PUBLICATIONS The following are of special interest to transmitting amateurs and short-wave enthusiasts:

MICROWAVE TECHNIQUE An up-to-date treatise on a subject of vital interest: 68 pages, 2/3, post free.
SERVICE VALVE EQUIVALENTS Essential component parts of many hundreds of Service and CV types: 23 pages, 1/- post free.

THE TRANSMITTING LICENCE How to obtain an amateur licence. 32 pages, 1/- post free.

RADIO HANDBOOK SUPPLEMENT, 4th Edition. Radio Mathematics, D/F, C.R. Tubes, etc. 188 pages, 2/9, post free.

R.S.G.B. BULLETIN Monthly publication of the R.S.G.B.: 1/6 post free. (Free to Members).

RADIO SOCIETY OF GREAT BRITAIN, 28, Little Russell Street, London, W.C.1

BUILD a really efficient all-dry 3-valve portable, 10in. x 5 1/2in. x 4 1/2in. Thoroughly tested and will give outstanding speaker performance anywhere in the country. M/L waves. Cheap and easy to construct. Comprehensive constructional details, 2/6.—Singland Radio, 36, Church St., Blackpool.

AMPLIFIER MEASUREMENTS.—We can put your Amplifier through a series of rigid laboratory tests, including square-wave testing, frequency range down to 1 c/s. All types of amplifiers for Special application, laboratory demonstration, etc. A. E. Cawkell, Electro-Acoustic Engineer, 7, Victory Arcade, The Broadway, Southall, Middx.

A FREE BOOK on Morse Code Training



These are Candler Morse Code Courses for Beginners and Operators.

Send for this Free "BOOK OF FACTS" It gives full details concerning all Courses.

THE CANDLER SYSTEM CO. (S.L.O.) 121, Kingsway, London, W.C.2.

Candler System Co., Denver, Colorado, U.S.A.

RECEIVERS & COMPONENTS

KITS of Radio Receivers from £78/0, 4 and 5 valve. All new materials. Table Models, Semi-Midget. Our latest Kit—Wylwyn Star 1948—has connections for Gramophone Pick-up and extensions to Loudspeaker. A.V.C. 8 hours average time for constructing. Full details and diagrams with each kit. C.W.O. or C.O.D.—Isherwoods, Remo House, 81, Plumington Road, Preston, Lancs. Tel.: 3348. Estd. 1938.

BARNES Rad-Elec & Wholesale Co., 2 Elmwood Rd. (Mount Rd.), Penn. Wolverhampton. Forget restrictions and worries and tour the world with the famous 8-worries R1116 "Double Superhet" all-wave battery receiver: "Air tested" by specialists. new valves, perfect order: 15-2,500 m. continuous in 7 wavebands: A.V.C. BFO (2 v. L.T., 120 v. H.P. works speaker). £10 C.W.O. free delivery plus 30/- returnable case. Send for Leaflet R.1 and Catalogue S.5. of service gear and components. T115 transmitter coils (12 in special case, 30/-).

MINIATURE and Personal radios. If you are contemplating building one of these, consult Meteor Electronics, who have a complete range of coils and kits of components for constructing these items. Permeability tuning coming very shortly, send your name in for details when available.—Meteor Electronics, Gloucester Row, Weymouth, Dorset.

MORE RADIO Constructors Bargains.—1.224 Battery Communications Receivers, £5 10s. Eliminators of super quality—200-250 V.A.C. in 120 v. at 50 m/A. Stabilised output, 35-1, 134 Battery Amplifiers at 17/8. TU-5B Transmitter Unit at 24/-. Type 73 Medium Wave Car Radio Type Receivers at 90/-. 38 Set Walkie Talkies, with all spares, Vibrator Pack, L.F. Amplifier and all Connectors at 90/-. Famous ABK Receivers at Final Reduction to Clear—GIFT at 39/6. All Brand New Condition and Post Free. Hundreds of other snips. 21d. stamp for Bumper May Clearance Lists to: Radio Constructors, 28, Spital Hill, Sheffield, 4.

SPECIAL FREE GIFT OFFER (see below)

18-valve Receivers for valves and salvage parts, 7 x SP61, 4 x RA50, 2 x RL7, 2 x P41, 2 x VU39, PEN.46, £2 each, carriage 10/- extra, or less the VU39 and PEN.46, 30/- each, plus carriage.
Canadian 52 Communication Receivers, 13 Valves, S. meter, crystal, etc., £12 10s., as new.
H.R.O. Communication Receivers, prices from £12 10s. each, with valves, switches and crystal, less coils.

Indicator Units with VC97 tubes and time base. Various types available from £3, carriage 10/- extra.
Telescopic Aerial Masts, 34ft., £2 5s.; 22ft., 30/-; 9ft. Dinghy masts, 10/-, carriage extra.
Valves of all types available, new or used. Sent C.O.D. or quote. For this month only, pair of Balanced Armature-type Headphones free with every order for £1 or over. Owing to restricted advertising space, we can only advertise a small percentage of the goods we have to offer. It will pay you to send S.A.E. for our lists. We guarantee a fair deal or your money back.—H. English, The Maltings, Rayleigh Road, Hutton, Brentwood, Essex.

OLDCHURCH LABORATORIES—New Ultra-compact D.C. Testmeter, 2,000 o.p., ruggedly built in bakelite case only 24 by 4 1/2. Volts, 10, 100, 1000. Mills, 1, 10, 100. Ohms, 5,000. Price, 55/-. Never before a real Radiomans Pocket Multimeter at such a figure! An entirely new product. Our T.S.73 Conversion Data a great success at £1, post free. Kit of components to complete conversion, £2/10/-. T.S.74 Conversion Data ready shortly. Another New Product. Linear Time-base Units, for providing "X" Sweep on any Tube. Complete in cabinet, £9. We can undertake all work connected with C.R. Tube Gear, of which we have a long experience. We buy, sell, exchange and repair all types of Test Equipment. Remember we are instrument specialists. L. F. Dismore, 52c, Oldchurch Rd., Chingford, E.4. Phone: Sil 4887.

RADIOGRAPHIC LTD.—3-Piece Valve Socket, 1/6; T1154 Oscillator Panels, new, 19/6; Rack-mounted Mains Power Unit, £3/19/6; Amplifier Mixer Units, £2/19/6. Ex-Govt. Valves, from 4/- each; 100K's Crystals, two types, 15/8 and 19/6. Isratic Grid Sockets, 1/6 each. S.A.E. for Latest List of Specializing in Special Purpose Valves from stock.—Radio-graphic Ltd., Mail Order Specialists, 66, Osborne St., Glasgow, C.1. Tel.: Bell, 3776.

J. V. NEWSON, G3G 23, Market Place, North Walsham, Norfolk, everything for drop in price, receiver and test gear. Stockists of equipment by Eddys, a Hamrad, Raymat, Labgear, Wooden, Denco, Wearite and other well-known makers, Rapid postal service. C.W.O. or C.O.D.

SPECIAL THIS MONTH—"Europa" Superhet radio chassis, A.C./D.C. M & S. Wave, fully wired, aligned and tested, brand new, £6/5/- incl. speaker.
THE BEST IN KITS—The "Victory 4" 3-valve plus rect. complete kit, incl. valves, Loudspeaker and standard cabinet. A.C./D.C. £8/4/-; A.C. only £8/9/- or with deluxe model cabinet, 15/- extra. Or our "Overseas 5" 3-wave Superhet Assembly, A.C./D.C. £6; A.C. £6/17/6, incl. valves. Speakers and cabinets available. Send postage now for full specifications and P.W. Bargain List. Selenium rectifiers, 4in. x 1in., 250 v. 45 m/A, 5/-; 350 v. 70 m/A, 8/6. Filament transformers, 6.3 v. 1.5 amp, 12/8. Mains transformers, shrouded, drop in price type, 110-250 m. 275-0-275 70 m/A, 6/3 and 5 v. out, 25/-. Permeability-tuned I.F. transformers, best quality, 12/6 pair, midget ditto, 12/6 pair.

SPEAKERS—Best makes only: 5in., 16/-; 8in., 19/-; 9in., 21/-; 10in., 30/-; 12in. Hi-Fi 12in. models. Standard output transformers, 6/6, multi-ratio, 9/6.

GOV. SURPLUS VALVES.—All guaranteed: 6J5, 16L, EP50, EBC33, 5/6; EF39, EF38, EL33, EC33, EK32, 9/-; 6X8, 6K7, 6C6, 6V6, 6F6, 6J7, 6X5, 5/6. Multi-10; 5U4, 6L6, KT66, 11/6. matched pairs supplied. Morgan Osborne "Q" Coil Packs, L. M and S. Superhet, 33/- with circuit of complete receiver. "Wearite" 3-wave Coil Packs, L. M and S. or M. and 2 S., gramophone position, 42/-.

GRAMOPHONE EQUIPMENT—Pick-ups: B.T.H. Magnetic with v/c, 39/6; New Roethermel Crystal Pickup, U48, 37/6; S.H.E.F.L. Moving-coil Pickup with trans., 53/9. A.C. 200-250 v. Gram. Motors, British made, £4/19/6, inc. £4/19/6. Specialised **INSTRUMENTS** by Mail Order; Immediate, safe despatch: AVO minor, £4/4/-; Universal Minor, £8/10/-; Model 7, £19/10/-; Mains Oscillator, £13; Valve-tester, £6/10/-; Pull-in 10,000 o.p.v. Multi-meter, A.C./D.C. and ohms, £10/10/-; Terms: C.W.O. or C.O.D., postage extra under £5.—Northern Radio Services, 66 & 102, Parkhill Road, London, N.W.3. Gulliver 1458.

BUILD IT YOURSELF—Black Prince Superhet 5-valve, 3 waveband, A.C. model, £10 10s., A.C./D.C. £9 10s. 8in. Speaker and Trans., £1 2s. 6d. extra, or Radio Heart supplied only, consisting of complete plans. Aiy. Chassis, Valve Holders, 2 waveband control pack, W/C Switch, Drum, Point-to-Point Scale, etc., 2-gang, 0005, 465 kc/s, I.F. coils; all mounted in position, 75/- lot.—Fred's Radio Cabin, 77, Newington Butts, S.E.11. Rodney 2120.

R.A.F. Type 1124 Receivers, with 6 valves, 31.F. Stages, ideal to convert for Television base. Sound assured. Components worth £10, bargain, 35/-, carriage paid. S.A.E. for lists. J. Rae, 39, Penn Road, Wolverhampton.

FRITH RADIOCRAFT, LTD. offer: sub-standard harmonic generators DRS 1A. Gives spot frequencies every 100 kc/s from 200 kc/s to 50 mc. mains operated complete with 6V6, 6K7, 5Z4, 100 and 1,000 kc/s xtals. Brand new with maker's instructions, £6/6. carriage paid. BC221AF frequency meters 125 kc/s to 20 mc. amazing accuracy, with xtal. spare set valves, calibrated charts and 50 p. manual, in original packing, £15/0. carriage paid. Bendix Radio Compass RX. MN 26C, 3 bands 150-325, 325-655, 655-1,500 kc/s. 2 R.F. stages, valves 5 v 6K7, 2 v 6J5, 2 v 6N7, 6B9, 6F6, 6L7 (metal) 24 v. operation. Full instructions for converting to A.C. £10. carriage paid. Bendix UHF RX BCR39A. 100-156 mc. Valves 9,002, 3 x 9,003, 4 x 6SG7, 6S7Q, 6K6. R.F. stage, BFO, 13" meter, 4-in. rack mounting. A magnificent example of American radio engineering, £14. carriage paid. Blind landing indicators comprising twin 0-115 micro-amp. movements, 5/-, do with 0-1 mA and 1-0-1 mA movements, 5/-, 10 H. 120 500 Hz. (wks. wt. 7lbs.), 10/-, do 10 H. 60 mA, 5/-.

Tuning condensers 3-gang, .0016 or .0005, 7/6. Valves, new and guaranteed 1R5, 1T4, 1S5, 3S4, 50/- set. V191EF50; V192EA50; VR65A/SP41; VR65B/SP41; VR65B/EB34; CV6, 6AC7; 6H6; 6SH7, 12H6, all at 5/-. 6S7, 6B4C, 6K7G, 6S47, 6S7J, 6SK7, 6SL7, 6SNT, 12S7, all at 12/6.

Bargain Parcels: over 50 new components and sub-assemblies, 21 x 50 asstd. resistors and condensers all different, 10/-, 72 yds. asstd. sleeving, 5/-. Latest lists free, trade supplied. Satisfaction guaranteed or money refunded without question.

Frith Radiocraft, Ltd., 69-71, Church Gate, Leicester. Phone: 5827.

HARRY JAMES PRODUCTIONS. 270, Leith Walk, Edinburgh, G. Mail Order Specialist in Cash. Wholesale Order. Electrolytics, new, not W.D. surplus B.I. Hints etc. 8 mids., 3/2; 16 mids., 5/3; 16+8 mids., 6/3; 8+8 mids., 6/-; 4 mds., 2/9; 25 mds., 25 v., 2/-; 50 mds., 50 v., 2/9. T.R.F. Chassis, 6 v. T.R.F. coils, M.E.L., 3 pairs, CV73, 3/0. 0.01, 0.05, 500 p.f. 5d. each. Variable 2-gang, 0.0005, 12/-, with Trimmers, 13/6. Loudspeakers, 5in. P.M., 19/6; 6in. energised 1,000 ohms, 29/6. 8in. P.M., 25/-. Volume Controls, Long Spindle, W.S. 5/6; 15, 3/6. Mains Transformers, 350-0-350 6.3 v. and 5 v. or 4 v. Heaters, 30/- Output Multi Ratio, 9/-, Valve Holders 5 pin, 7 and octal, 7d. each. Amphenol type, 9d. each. Voltage Droppers, 0.2 amp. 1,000 ohms, 3/9; 0.3 amp. 800 ohms, 4/9. Line cord, 4 pin, 12 v. 3 cores, 3d. 9d. per ft. Special Offer, 0-1 milliamm. metres, suitable for multi meters, etc., price 12/6. Valves C.O.D. Large stocks of British and American types. Enquire for anything in Radio. S.A.E. for lists.

COMPLETE Amplifying Unit, consisting of Four-valve Amplifier, 12 v. or 24 v. Gaius microphone, two turntables and pickups, built-in cabinet and equal to new. Best offer over £50.—Edwards, Hadleys, Alveley, Bridgnorth.

97/6. CHARGING SWITCHBOARDS. 12v./32v., 500 and 1,200 watts, volts, amps., cut-outs, fuses, resistances, etc. 4 take-offs superb unit, in case; or send £5 carriage paid.

75/- DYNAMOS. 24 volts, 1 or 200 watts, 9in. by 7in., 3in. spindle, or send 80/- carriage paid.

75/-, 230v./150, 15 v. p. ELECTRIC MOTORS. incorporating 125 cycle converter, or send 80/- carriage paid.

58/- MAINS TRANSFORMER SWITCHBOARDS. 230v. A.C. to 12v., 5 separate take-offs, complete distribution panel, all switches, fuses, amps., etc., brand new, or send 60/- carriage paid.

55/- ELECTRIC MOTORS. 12v. and 24v., 14 h.p., 4in. by 4in., with 3in. spindle for drive, beautiful job, or send 60/- carriage paid.

45/- DYNAMOTOR UNITS, containing 12v., 24v., 130v., and 300v. D.C. dynamo, or suitable as 6v., 12v., or 24v. motor, approx. 1 h.p., 11in. by 5in., with spindle to take small grindstone, mop, etc., also contain adjustable 24v. cut-out, 12v. automatic voltage control, smoothing condenser, resistances, and many other extremely useful fittings, beautifully made, or send 50/- carriage paid.

38/- RADIO WAVEMETERS, adjustment dial, 350-370 Mc/s. beautiful instrument in case, or send 40/- carriage paid. Host other valuable equipment. Lists free. Benmots, Summerley Street, Earsfield, S.W.18. WIM 3833. (10 yds. S. Rly. Electric Line; 10 minutes Waterloo.)

CHARLES BRITAIN (RADIO), LTD. R.F. Units, Type 24 and 25, contains 3 SP61, 5-way 3-bank ceramic switch, etc., easily adapted for use as short-wave converter. Tuning ranges are as follows: Type 24, 20 to 30 Mc/s. Type 25, 40 to 50 Mc/s. Price 16/6. Post Free.

BLACKOUT UNITS, contains 10 EF50, 2 EB34, 1 relay and over 100 condensers and resistors, complete in case and a real bargain at 39/6. carriage and packing 5/-.

INDICATOR UNIT, Type 182a. Containing tube No. VCR 517C and 8 valves, 15U4G, 4 SP61, 3 EF50, 11 volume controls, and numerous small components. The CR tube used in this unit is the persistent type, but has the same base connections as the VCR 97. It can be used for a scope or television if the EHT is kept fairly low, in any case we think you will agree this is an amazing "buy" for 39/6 for callers only, we will demonstrate each tube (6ins.).

AMERICAN AIRCRAFT receiver, Type RC966A (ABF), complete with 13 valves; 3 V191EF (R.F. pentodes), 6S7Q, 7B9, 12D1 and motor generator which can be easily converted to a useful motor for use on A.C. or D.C. mains, 230 volts. This item is brand new and in makers' crates. Price 39/6. 7/6 carr. and packing.

WISH LIST—Very similar to the above and contains 10 valves, rotary generator and etc. Price 25/-, 7/6 carr. and packing.

VIBRATOR PACK—Size 11in. x 6in. x 3in., complete with 12v. vibrator, Neon Valve, 12V. rectifier, smoothing capacitors, condensers, chokes, etc. Circuit Diag. is supplied with each one, 12/6 post free.

CHARLES BRITAIN (RADIO), LTD. Radio House, 2 Wilson St., London, E.C.2. Tel. B15 2966.

BARGAINS—Midget Motors, 4in. diam. 24 v. with pulley and wheel, useful for sewing machine, models etc., 9/11.

Speakers, moving coil, new, 5in., 14 1/2 6in., 15 1/2; 8in., 16 1/2; 10in., 26/-.

Valves, Ex-W.D. H.L. 12, SP61, DFD2, P.T. Tuning Pack with 4 coil Unit and 2 gang condenser, covers about 10-250 metres, useful for Sig. Gen., 6/9.

Amplifier M.58. Ex-Adm. VHF Unit, with grounded grid triode CV53, complete with power valve (2 H.T. and 2 rect.), in sealed case, 19/6, packing 5/- extra.

19 Set Phone Kit, contains pair Moving Coil phones, M.C. hand-mic., w/w, Junction Remote Control Units, Nos. 1 and 2 (with useful components) and haversack. All in original sealed cartons, 15/- (post 13/-).

Midget Ex-W.D. Buzzer, 1/3.

Mains Transformers, 6.3 v. 3 a., 5 v. 2 a. 300-0-300, 80 mA., 200 250 v. Prim., 19/11.

Over 5,000 valves in stock, including T41, 1H5, 1A7, EK32, EBC3, FX1, MVS/PEN. B. etc.

Terms C.W.O. or callers. Add 6d. extra for postage.

TINY FOR RADIO, 36a. Dalston Lane, London, E.3.

SHOP BY POST direct from the actual buyers from the Ministry of Supply. You pay no fancy prices. All is carriage free to you and free to C.B. Britain. Send 2d. stamp (no envelope) to-day for our latest lists. This month's Special Bargain!! Control panel, type Mk. IV, contains 2 meters, 1, 0-500 micro-amps., 1 0-150 micro-amps., 3 useful Transformers, 2 Yaakim, 2 Yaakim switches, instrument rectifier panel light, several volume controls, octal valveholders, and several pounds' worth of condensers, resistances, etc., contained in a steel case, approx. 18in. x 6in. x 6in. Limited number, only 35/-.

Transmitter etc. racks, very well made, steel racks, 4ft. x 20in. x 14in. Detachable side panels, weight approx. 112lbs., to take standard panel. As we urgently require the room these racks occupy we are clearing at a ridiculously low price of 32/6 each. Packets of 3/16in. Perspex contain approx. 200 sq. ins., 6/6 pack. Two valve amplifier, with valves and power pack 70/-.

Air thermometer, -30° to +30° cent., 10/6. S.V.N. electric motor, 20 v. 1/2 hp., 5/10. 12/6. B.B. battery communication receiver, with valves, £6/10/0. 1154 transmitter, with valves and meters, £7/10/0 etc., etc. C.W.O. only.—Walton's Wireless Stores, 205, Staveley Road, Wolverhampton, Estab. 1923.

REPAIRS to loud-speakers. Cones, coils fitted. Fields altered, rewound. Output transformers, clock coils. No mains trans accepted. Prices quoted. Satisfaction guaranteed.—L. S. Repair Service, 49, Trinity Rd., Upper Tooting, S.W.17. Closed Saturdays. Phone: Balham 2359.

WINDS—Re-winds and individual transformers constructed. Send your problem for quotation.—Slingland Radio, 58, Church St., Blackpool.

REWIND SERVICE—Armatures, Gram. Motors, Vacuum Cleaners, Drill and all small motor Transformers—Fields Pick-ups, Speakers—New Cones and Speech Coils fitted—New Vac. Cleaners supplied. All work guaranteed and promptly executed. Special Terms to the Trade. Send S.A.E. for Price List and Radio Spares.—A. D. S. Co., 291-3-5, Lichfield Road, Aston, Birmingham, 6.

LAMP SHADES—All materials and fitting for the homecraftsman. Frames, Parchment, etc. Send 4d. for instruction sheet and price list.—Technicrafts (D.), 182, Malmesbury Park Road, Bourne-mouth, Hants.

BATTERY Components Cheap. R. W. Edgoose, Walton Highway, Wisbech.

EVERYTHING for the wireless constructor. Send stamp or price list. H. Tabner 118, Nightingale Road, Hitchin, Herts.

WANTED—Electrolytic Condensers, Midget Communications Receiver Mk1, Harwood, 51, Trevor Road, West Bridgford, Nottingham.

FOR SALE—Avometer Model 7. Avometer Oscillator, Avometer Test Bridge, Avometer Tester, Service Manuals, Valves and assorted spares. Offers, 104, Dudley Road, Wolverhampton, Staffs.

KIT SETS, wired, tested, 15/-. All types receiver serviced. Rewinds of all descriptions. Large stocks of ex-Government and new components at keen prices. S.A.E. for lists. H. Dowler, 1, Little Priest Lane, Pershore, Worcs.

COPPER Wires, enamelled, tinned, 12/6, cotton, silk covered. All gauges. B.A. screws, nuts, washers, soldering tags, eyelets. Ebonite and laminated bakelite panels, tubes, coil formers, Tuning rod, fuses, crystals, permanent detectors, headphones, etc. List S.A.E. Trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4.

TUITION

RADIO AND RADAR—Training for a career in Air or Marine Service as Operator, Operator Mechanic, or Engineer. Residential and non-residential Courses at the Radio and Radar School of Britain's Air University. Enquiries to the Commandant, Air Service Training, Hamble, Southampton.

"ENGINEERING OPPORTUNITIES" Have you had your copy of this free guide to A.M.I.Mech.E., A.M.I.E.E., and all branches of Engineering, Building and Plastics? Become technically trained on "No Pass—No Fee" terms for higher pay and security. For free copy write B.I.E.T. (Dept. 242B), 17, Stratford Place, London, W.1.

FOUR CIGARETTES per day or Associate Membership of the I.E.E.!! Which would you rather have? Expert and successful tutors of the British National Radio School will coach you for I.E.E. Brit.I.R.E. and a whole series of C. & G. examinations for 8d. per day!! Write to-day for our free booklet and unequalled guarantee. Studies Director, B.Sc., A.M.I.E.E., M.Brit.I.R.E., 66, Adiscombe Road, Croydun, Surrey.

WIRELESS (sea and air) TELEVISION. Broadcasting, Radar, etc. offer tremendous opportunities. Students, both sexes, age 14 upwards, trained for appointments in all branches of Radio. Low fees, boarders accepted, 2d. stamp for pros.—Wireless College, Colwyn Bay.

THE INSTITUTE of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E. Service entry and progressive exams; tuitionary fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the Secretary, Fairfield Road, Crouch End, N.6.

Practical Wireless BLUEPRINT SERVICE

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the blueprint number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

PRACTICAL WIRELESS		No. of Blueprint	F. J. Cunniff's A.C. Superhet 4	PW59
			F. J. Cunniff's Universal 44 Superhet	PW60
			"Qualitone" Universal Four	PW73
CRYSTAL SETS				
Blueprints, 1s. each.				
1927 Crystal Receiver		PW71*		
The "Junior" Crystal Set		PW94*		
STRAIGHT SETS. Battery Operated				
One-Valve: Blueprints, 2s. each.				
All-Wave Unipen (Fentode)		PW31A		
Beginner's One-valver		PW85		
The "Pyramid" One-valver (HF Pen)		PW93*		
Two-valve: Blueprints, 2s.				
The Signet Two (D & I F)		PW76*		
Three-valve: Blueprints, 2s. each.				
Selectone Battery Three (I, 2 LF (Trans))		PW10		
Summit Three (HF Pen, D, Pen)		PW37*		
Hall-Mark Cadet (D, LF, Pen (RC))		PW48*		
F. J. Cunniff's Silver Souvenir (HF Pen, D (Pen), Pen) (All-Wave Three)		PW49*		
Cameo Midget Three (D, 2 LF (Trans))		PW51*		
1936 Sonotone Three-Four (HF Pen, HF Pen, Wector, Pen)		PW53*		
Battery All-Wave Three (D, 2 LF (RC))		PW55*		
The Monitor (HF Pen, D, Pen)		PW61*		
The "Colt" All-Wave Three (D, 2 LF (RC & Trans))		PW72*		
The "Rapid" Straight (3, 2 LF (RC & Trans))		PW82*		
F. J. Cunniff's Oracle All-Wave Three (HF, Det., Pen)		PW78		
1935 "Triband" All-Wave Three (HF Pen, D, Pen)		PW84*		
F. J. Cunniff's "Sprite" Three (HF, Pen, D, Tet)		PW87*		
The "Hurricane" All-Wave Three (SG, D, Pen, Pen)		PW89*		
F. J. Cunniff's "Push-Button" Three (HF Pen, D (Pen), Tet)		PW92*		
Four-valve: Blueprints, 2s. each.				
Beta Universal Four (SG, D, LF (C, B))		PW17*		
Nucleon Class B Four (SG, D (SG), LF, C, B)		PW34B		
Fury Four Super (SG, SG, D, Pen)		PW34C*		
Battery Hall-Mark 4 (HF, Pen, D, Push-Pull)		PW46*		
"Acme" All-Wave 4 (HF Pen, D (Pen), LF, C, B)		PW53*		
The "Admiral" Four (HF Pen, HF Pen, D, Pen (RC))		PW59*		
Mains Operated				
Two-valve: Blueprints, 2s. each.				
Selectone A.C. Radiogram Two (D, Pow)		PW19*		
Three-valve: Blueprints, 2s. each.				
Double Diode-Triode Three (HF Pen, DDT, Pen)		PW23*		
D.C. Ace (SG, D, Pen)		PW25*		
A.C. Three (SG, D, Pen)		PW29*		
A.G. Leader (HF Pen, D, Pow)		PW35C*		
D.C. Premier (HF Pen, D, Pen)		PW35B*		
Ubique (HF Pen, D (Pen), Pen)		PW36A*		
F. J. Cunniff's A.C. All-Wave Silver Souvenir Three (HF Pen, D, Pen)		PW50		
"All-Wave" A.C. Three (D, 2 LF (RC))		PW54*		
A.C. 1936 Sonotone (HF Pen, HF Pen, Wector, Pen)		PW56*		
Mains Record All-Wave 3 (HF Pen, D, Pen)		PW70*		
Four-valve: Blueprints, 2s. each.				
A.C. Fury Four (SG, SG, D, Pen)		PW20*		
A.C. Fury Four Super (SG, SG, D, Pen)		PW34D		
A.C. Hall-Mark (HF Pen, D, Push-Pull)		PW45*		
Universal Hall-Mark (HF Pen, D, Push-Pull)		PW47		
SUPERHETS				
Battery Sets: Blueprints, 2s. each.				
E5 Superhet (Three-valve)		PW40		
F. J. Cunniff's 2-Pipe Superhet.		PW52*		
Mains Sets: Blueprints, 2s. each.				
A.C. E5 Superhet (Three-valve)		PW43		
D.C. E5 Superhet (Three-valve)		PW42*		
SHORT-WAVE SETS. Battery Operated				
One-valve: Blueprint, 2s.				
Simple S.W. One-valver		PW88*		
Two-valve: Blueprints, 2s. each.				
Midget Short-wave Two (D, Pen)		PW38A*		
The "Fleet" Short-wave Two (D (HF Pen), Pen)		PW61*		
Three-valve: Blueprints, 2s. each.				
Expendable Three Short-wave Three (SG, D, Pow)		PW30A*		
The Precect 3 (D, 2 LF (RC and Trans))		PW63*		
The Band-spread S.W. Three (HF Pen, D (Pen), Pen)		PW68*		
PORTABLES				
Three-valve: Blueprints, 2s. each.				
F. J. Cunniff's ELF Three-valve Portable (HF Pen, D, Pen)		PW65		
Parvo Flycatcher Midget Portable (SG, D, Pen)		PW77		
Four-valve: Blueprint, 2s.				
"Imp" Portable 4 (D, LF, LF, Pen)		PW86*		
MISCELLANEOUS				
Blueprint, 2s.				
S.W. Converter-Adapter (1 valve)		PW48A*		
AMATEUR WIRELESS AND MAGAZINE CRYSTAL SETS				
Blueprints, 1s. each.				
Four-station Crystal Set		AW427		
Lucerne Tuning Coil for AW427		1s.		
1934 Crystal Set		AW444		
150-mmc Crystal Set		AW460		
STRAIGHT SETS. Battery Operated.				
One-valve: Blueprint, 2s.				
B.B.C. Special One-valver		AW387*		
Two-valve: Blueprints, 2s. each.				
Full-volume Two (SG det, Pen)		AW392		
A modern Two-valver		WM409*		
Three-valve: Blueprints, 2s. each.				
E5 5s. S.G. 3 (SG, D, Trans)		AW432*		
Lucerne Ranger (SG, D, Trans)		AW422*		
E5 3s. Three De Luxe Version (SG, D, Trans)		AW435		
Transportable Three (SG, D, Pen)		WM271		
Economy Pentode Three (SG, D, Pen)		WM337		
"W.W." 1934 Standard Three (SG, D, Pen)		WM351		
E3 3s. Three (SG, D, Trans)		WM354		
1935 E6 6s. Battery Three (SG, D, Pen)		WM371		
PTF Three (Pen, D, Pen)		WM389		
Certainly Three (SG, D, Pen)		WM393		
All-wave Winning Three (SG, D, Pen)		WM400		
Four-valve: Blueprints, 3s. each.				
6s. Four (SG, D, RC, Trans)		AW370		
Self-contained Four (SG, D, LF, C, B)		WM331		
Lucerne Straight Four (SG, D, LF, Trans)		WM350		
E5 5s. Battery Four (HF, D, 2LF)		WM381*		
The H.K. Four (SG, SG, D, Pen)		WM384		
The Auto Straight Four (HF Pen, HF Pen, DDT, Pen)		WM404*		
Five-valve: Blueprints, 3s. each.				
Super-quality Five (2 HF, D, RC, Trans)		WM320		
Class B Quadradyne (2 SG, D, LF, Class B)		WM344		
New Class B Five (2 SG, D, LF, Class B)		WM340		
Mains Operated				
Two-valve: Blueprints, 2s. each.				
Conoelectric Two (D, Pen), A.C.		AW403*		
Economy A.C. Two (D, Trans), A.C.		WM286		
Three-valve: Blueprints, 2s. each.				
Mantovani A.C. Three (HF, Pen, D, Pen)		WM374*		
E15 15s. 1936 A.C. Radiogram (HF, D, Pen)		WM491*		
Four-valve: Blueprint, 3s. each.				
All-Metal Four (2 SG, D, Pen)		WM329		
Harris Jubilee Radiogram (HF, Pen, D, LF, F)		WM386		
SUPERHETS				
Battery Sets: Blueprints, 3s. each.				
Variety Four		WM395*		
The Request All-Waver		WM407		
Mains Sets: Blueprints, 2s. each.				
Heptode Super Three A.C.		WM350*		
PORTABLES				
Four-valve: Blueprints, 3s. each.				
Holiday Portable (SG, D, LF, Class B)		AW393*		
Family Portable (HF, D, RC, Trans)		AW447*		
Tyers Portable (SG, D, 2 Trans)		WM367*		
SHORT-WAVE SETS. Battery Operated				
One-valve: Blueprints, 2s. each.				
S.W. One-valver for America		AW426*		
Roma Short-waver		AW452*		
Two-valve: Blueprints, 2s. each.				
Ultra-short Battery Two (SG, det Pen)		WM402*		
Home-trade Coil Two (D, Pen)		AW440		
Three-valve: Blueprints, 2s. each.				
Experimenter's 6-metre Set (D, Trans, Super-regen)		AW438		
The Carrier Short-waver (SG, D, B)		WM390		
Four-valve: Blueprints, 3s. each.				
A.W. Short-wave World-beater (HF Pen, D, RC, Trans)		AW436*		
Standard Four-valver Short-waver (SG, D, LF, P)		WM383*		
Superhet: Blueprint, 3s.				
Simplified Short-wave Super		WM397*		
Mains Operated				
Two-valve: Blueprints, 2s. each.				
Two-valve Mains Short-waver (D, Pen), A.C.		AW453		
Four-valve: Blueprints, 3s.				
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans)		WM391*		
MISCELLANEOUS				
S.W. 1-valve Converter (Price 1s.)		AW329		
Enthusiast's Power Amplifier (10 Watts) (2-1)		WM337*		
Listener's 8-watt A.C. Amplifier (2-1)		WM392*		
Radio Unit (2v.) for WM392 (2-1)		WM398*		
Harris Electrogram battery amplifier (2-1)		WM399*		
De Luxe Concert A.C. Electrogram (2-1)		WM403*		
New Style Short-wave Adapter (2-1)		WM388		
E.L.D.L.C. Short-wave Converter (2-1)		WM405*		
Wilson Tone Master (2-1)		WM406		
The W.M. A.C. Short-wave Converter (2-1)		WM408*		

HINTS COUPON

This coupon is available until July 5th, 1948, and must accompany all Practical Hints.

PRACTICAL WIRELESS, JULY, 1948

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEIGHT & SONS, LTD., Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (Aasia), LTD., South Africa CENTRAL NEWS AGENCY, LTD. Subscription rates including postage: Inland 10s. 6d. per annum; Abroad 10s. per annum. Registered at the General Post Office for the Canadian Magazine Post. CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of by way of Trade except at the full retail price of 9d.; and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade; or affixed to or as part of any publication or advertising, literary or pictorial matter, whatsoever.

PREMIER RADIO CO.

MORRIS & CO. (RADIO) LTD.

COLLARO ELECTRIC GRAMOPHONE MOTORS with 12in. turntable. A.C. only. 100-250 v. £5 18/4.

COLLARO ELECTRIC UNIT with Magnetic Pick-up and Auto Stop. A.C. only. 100-250 v. £9 13/6.

DIPTO UNIT with Crystal Pick-up. A.C. only. 100-250 v. £11/2/2.

COLLARO AUTO CHANGERS with Magnetic Pick-up. A.C. only. 100-250 v. £22 4/4.

CONRAD RIM DRIVEN ELECTRIC GRAMOPHONE MOTORS with 9in. Turntable. Fixed Speed (78 r.p.m.) for 200-250 v. A.C. only. £4 19/8.

C.R. TUBES: VCR37. 6in. diameter, green screen, 4 v. 1 a. Heater, 2,500 v. max. H.T. Complete with socket, in makers original cartons. 55/-

MULLARD M.V. 18-2 TELEVISION TUBES. 7in. diameter. 2 v. Heater. 5KV max. H.T. Mazda Octal Base. £5 19/6. In makers cartons.

C.R. TUBES. We have available a large quantity of E.M.I.41 Cathode Ray Tubes. 3 1/2in. diameter, Green Screen, short persistence, 4 v. 1.3 a. Heater. 800 v. H.T. Complete with socket. 17/6 each.

C.R. TUBES V.C.R.133 (equivalent to E.C.R. 35). 3 1/2in. diameter, Green Screen, 4 v. 1 a. Heater. 1,200 v. H.T. Complete with socket and Muntzel Screen. 49/6 each.

SPECIAL VALVE OFFER

	1A7, 1H5, 1N5, 3Q5, 9 6 each	36 - Set.		
6F6	10 6	VU131 (HVR2)	10/-	
6V6	8 6	VU39 (R3)	9/-	
CV6	5/-	VR137 (EC32)	5/-	
VR65	(SP41, 6.3 v.)	VR136 (EF34)	7/6	
VR82	(E.A50)	V570 (1475)	7/6	
VR55	(EF38)	VT60A (307 Ceramic)	10/-	
VR78	(D1)	717A	7/6	
VR55	(EBC33)	123H7	7/6	
VR78	(6K7 met)	123L7	10/-	
VR503	(KT33C)	123A6	7/6	
VR53	(EF39)	VR91 (EF50)	6/6	
VR57	(EF32)	RI13	12/6	
951	—	5Z4	7/6	
6B8	—	6K8	6/6	
6B7	—	1S3	5/-	

MIDGET RADIO KIT. Build your own midget radio. A complete set of parts, including valves, loudspeaker and instructions. In fact, everything except cabinet necessary to build 4-valve Medium and Long Wave T.R.F. radio operating on 200-250 v. mains. A.C. or D.C. Wavelengths covered 200-537 and 700-2,000. Size 10 x 6 x 6in. Completely drilled chassis. Price, including tax, £8 0/11.

SUPERBET MIDGET-RADIO KIT. A complete kit of parts for a 5-valve superbet. Covers 16-50 and 200-557 metres. A.C. D.C. 200-250 v. Size, 10 x 6 x 6in. Completely drilled chassis. Price, including tax, £9. An attractive brown bakelite cabinet can be supplied for either kit at a cost of 27/3.

PRE-BUDGET PRICES WHILE STOCK LASTS.

PREMIER MAINS TRANSFORMERS. All primaries are tapped for 200-230-250 v. mains, 40-100 cycles. All primaries are screened. All L.T.s are centre tapped.

List No.	Output	Price
SP.175A.	175-0-175 v. 50 m/a. 6.3 v. 2-3 a., 5 v. 2 a.	25/-
SP.175B.	175-0-175 v. 50 m/a. 4 v. 1 a., 4 v. 2-3 a.	25/-
SP.250A.	250-0-250 v. 60 m/a. 6.3 v. 2-3 a., 5 v. 2 a.	25/-
SP.250B.	250-0-250 v. 60 m/a. 4 v. 1-2 a., 4 v. 3-5 a.	25/-
SP.300A.	300-0-300 v. 60 m/a. 6.3 v. 2-3 a., 4 v. 2 a.	25/-
SP.300B.	300-0-300 v. 60 m/a. 4 v. 2-3 a., 4 v. 3-5 a., 4 v. 1-2 a.	25/-
SP.301A.	300-0-300 v. 120 m/a. 5 v. 2-3 a., 6.3 v. 3-4 a.	28/-
SP.301B.	300-0-300 v. 120 m/a. 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 3-5 a.	28/-
SP.350A.	350-0-350 v. 100 m/a. 5 v. 2-3 a., 6.3 v. 2-3 a.	29/-
SP.350B.	350-0-350 v. 100 m/a. 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 3-5 a.	29/-
SP.352.	350-0-350 v. 150 m/a. 4 v. 2-3 a., 6.3 v. 2-3 a., 6.3 v. 2-3 a.	36/-
SP.501A.	500-0-500 v. 150 m/a. 5 v. 2-3 a., 6.3 v. 2-3 a., 6.3 v. 2-3 a.	50/-

NEW 2-VALVE SHORT WAVE KIT. 16 to 2,000 metres. Switched Coil Pack ready wired and tested. 2 Mazda HL23 Valves, Phones, H.T. and L.T. Batteries, Condensers, resistors, diagrams and steel case, all ready to assemble. £8/19/6.

Send 21d. stamp for our list.
Terms of business: cash with order, or C.O.D. over £1.

ALL POST ORDERS TO 167, LOWER CLAPTON ROAD, LONDON, E.5.

Phone: Amherst 4723

ALL CALLERS TO 169, FLEET STREET, LONDON, E.C.4. Phone: Central 2833.


THERE ARE MORE

Stentorian

SPEAKERS IN USE BY RELAY COMPANIES THAN THOSE OF ALL OTHER MAKERS COMBINED

From the earliest days of relay radio, Whiteleys have enjoyed a close, friendly relationship with these companies. Now, after 20 years intimate association, Whiteley loudspeakers are in use by the great majority of relay subscribers, a majority which grows each week. Experience teaches—and our experience is at the disposal of any relay organisation not already served.

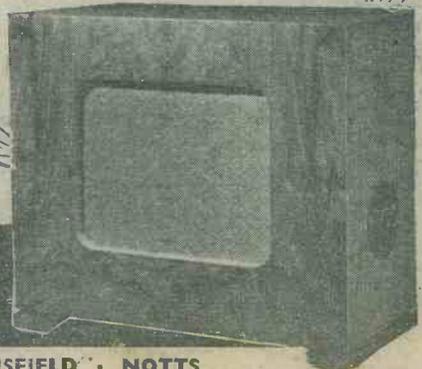Illustrated is the Stentorian "Cadet" Walnut cabinet, 7" Unit. £4.0.0 (with transformer £4.10.0) Other models from £1.19.6.



RELAY SPEAKERS & COMPONENTS

WHITELEY ELECTRICAL RADIO CO. LTD. • MANSFIELD • NOTTS