

# Practical Wireless


9<sup>D</sup>  
EVERY  
MONTH

AND PRACTICAL TELEVISION

Vol. 25, No. 513

|| Editor: F. J. CAMM ||

APRIL, 1949

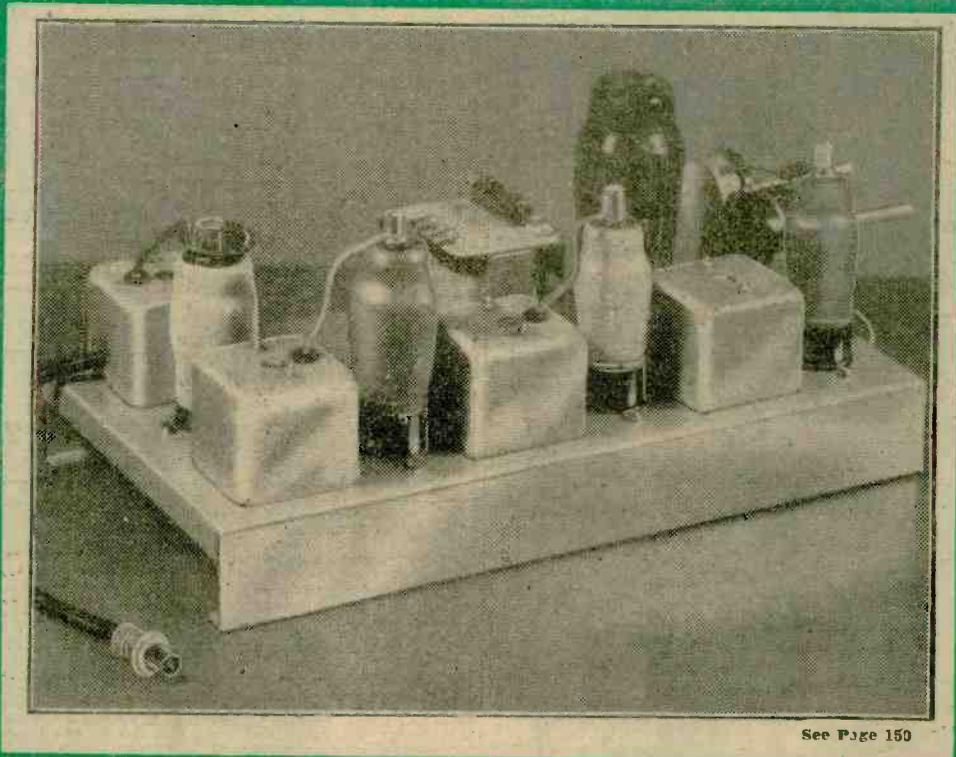

See Page 150

## PRINCIPAL CONTENTS

Building a Television Receiver  
 Remote Control  
 Using the Oscilloscope  
 G.P. P/A Amplifier



A 5-metre Converter  
 A Personal Portable  
 Occasional 6-volt Quality 3  
 A New Sync. Separator

FDX-146.

**The best—**  
**HIGH and LOW**



**Exide**  
L.T. ACCUMULATORS  
and  
**Drydex**  
H.T. BATTERIES

*for better*  
**battery radio reception**

ISSUED BY THE CHLORIDE  
ELECTRICAL STORAGE COMPANY LIMITED

**AT LAST!**

**A Remote Control Pre-Amplifier**

that can be mounted in a position best suited to the user, up to 15 feet from the power amplifier. Will operate from any moving-coil, moving iron or crystal P.-U. ; from any moving-coil microphone ; from any radio unit.

**Controls :** Input Selector ; Bass Gain and Loss ; Treble Gain and Loss ; Volume.

**Distortion :** 0.05%. **Price** £6 15 0.

The above has been designed for use with the

**New "Point One" 12 watt Triple Loop Feedback Power Amplifier**

**Distortion :** at 1,000 c/s. and 10W, output 0.1%.

**Frequency Response :**  $\pm 0.1$ db., 20 c/s.-20 kc/s.

**Damping Factor :** 20 (Regulation : 0.2db.)

**Phase Margin :**  $20^\circ \pm 10^\circ$ .

**Gain Margin :** 10db.  $\pm 3$ db.

**Sensitivity :** 160 mV. **Price** £25 15 0.

If you would like to know more about amplifiers in general and the above amplifier in particular, write for

**Booklet P**

**H. J. LEAK & CO. LTD.,** Brunel Road,  
Westway Factory Estate, London, W.3.  
Telephone : SHEpherd's Bush 5626

**DENCO** "THE DESIGNERS AND MAKERS OF QUALITY PRODUCTS."

(CLACTON), LTD.

**DENCO MAXI-Q COILS** have the following features : High Q-Lite Windings on Polystyrene Formers Adjustable Iron Dust Cores. Two types available : Chassis Mounting has Single 0 B.A. fixing, or Plug-in type fits Standard Octal Valveholder. Seven ranges available, in Aerial, H.F. and Oscillator coils covering :

3.6-6 metres, 6-10 metres, 9-30 metres.  
20-60 metres, 56-180 metres, 190-570 metres.  
560-1,800 metres.

Wiring instructions supplied with each coil. Price : Chassis Mounting type, 3/9 (with Reaction, 4/9 each). Plug-in type, 4/- (with Reaction, 5/- each).

**TELEVISION COMPONENTS**—Efficiently Screened Line Output Transist., 27/- . Scanning Coil Assembly for 9in. and 12in. Tubes, 33/- . Focus Coils, Thumbscrew Adjustment, suit Electronic circuit, 25/- . Line Time Base Blocking Oscillator Unit, 27/- .

**COMPLETE KIT OF PARTS**.—Comprising 5 valves plus Metal Rectifier to build Five W/band A.C./D.C. SUPERHET. Uses C.T.6 Coil Turret, covering 10-30, 25-75, 75-200, 200-560, 750-2,000 metres (and GRAM position), the stages being Mixer (C.C.H.35), I.F. Amplifier (CF39), Det. A.V.C., and 1st A.F. (EBC33), Tuning Indicator (EM34), Output (C.L.33). Building is made easy, the tuning and I.F. units being assembled and aligned at Denco factory, thus ensuring a high performance. Has four controls : Tuning, Tone, Volume and W/Band Switch (with Gram. position), and gives 4/5 watts output. Convenient size of 12in. x 8in. x 11in. high. Wiring diagram and comprehensive building instructions included.

Price £11/11 - (plus £2/9/5 P.T.)

Other available Denco Products are listed in a most comprehensive Catalogue. Price 9d.

EXPORT and TRADE ENQUIRIES INVITED.

**DENCO DISTRIBUTORS LTD.,**

115, FLEET STREET, E.C.4.

(Telephone : CENTral 5614 and 2280)

**HENRY'S**

We are pleased to announce that a demonstration model of the "Inexpensive Television" can be seen working at these premises. The booklet "Inexpensive Television" is available at 1/6. Total cost of necessary Ex-Govt. items should not exceed £20. All are available.

**EX-GOVT. VALVES.** All brand new and guaranteed. 6V6, 6C6, EF36, EF39, EBC33, EK32, EL32, 6X50GT, 2X2, 5Z4, EF50, EF54, EF55, RL37, 6KT7, 6KT8, 6K8CT, 12S17, 12S17, 12S17K7, 6SL7, 6SC7, 6SN7, 12X7, 12Y5, 12Y6, 12Y7, 3D2, 3D2, 15D2, at 7/6 each only. U18, 5T4, 5R4, 6F7, 6A65, RL18, all at 10/- each. 6L6, at 12/6; 3S4 and IS4 at 9/- each. 15S, 1T4, at 5/- each. EA50, SP61, EB34, at 3/6 each. DI at 2/6 each only. Most of these valves are boxed. In addition we have over 1000 new boxed E.V.A. Valves in stock, at current B.O.T. prices.

**SUPERHET RECEIVERS TYPE 25 and 173.** Ex-Govt.—The receiver portion of the TR1188. Containing 1 pr. 450 k/c.s. I.F.T.'s plus 2 valves EF36, 2—EF39, one EK32, and one EBC33. Easily converted to home use. Outstanding value, only 25/- each. Plus carriage, 1/6.

**L.F. TRANSFORMERS.** Input 200-250 v.v. Output 6v. and 12v. at 3a. 15/-.  
Input 200-250 v.v. Output 6.3 v. at 12 a. 37/6.  
Input 200-250 v.v. Output 12 v. and 24 v. at 6 a. 42/-.

N.B. Above voltages are when "on load."

**MILLIAMETERS.** 0-1 m/a. 2in. scale. square, moving coil, panel mounting, only 10/- each. 0-1 m.a. 2 1/2 in. scale, moving coil, panel mounting, 15/-, 0-5 m.a. 2 1/2 in. scale, moving coil, two mounted on panel. New and unused. 12/6 pr.

**POCKET VOLTMETER.** Ex-Govt. Two range. 0-15 v. 0-250 v. D.C. Brand new and complete in web carrying case. Only 10/6.

**E. H. T. TRANSFORMERS.** 2500 v., 4 v. 1.5 a., 2-0-2 v. 2 a., only 37/6. 3250 v., 6.3 v. 1 a., 2-0-2 v. 2 a., only 39/6. 4000 v., 2-0-2 v. 2 a. 59/6. 5000 v., 2-0-2 v. 2 a., 65/- . All are for 200/250 v. Input. 50 cycles, and fully guaranteed.

A stamp will bring our latest Component List. Probably the most up-to-date in the trade.

**HENRY'S, 5, Harrow Road, W.2**  
Paddington 1008 9.

**BUILD YOUR OWN TELEVISION FROM EX-GOVT. GEAR**

At the cost of only a few pounds it is possible to build a Television Receiver, utilising ex-Govt. Radar Units. The FULL CONSTRUCTIONAL DETAILS, containing 26 large pages of data, photographs and wiring diagrams, can be purchased for only 7s. 6d., but if the undermentioned Radar Units are ordered the data is supplied gratis. Alternatively, the cost will be allowed if the units are purchased within 14 days.

UNIT 1 is a Vision Receiver IF Strip at 55/-.

UNIT 2 is a Radar Indicator containing CR Tube, etc., at 75/-

**THE COMBINED H.T. & E.H.T. MAINS TRANSFORMER** is specially made and costs 110/-, but if this is ordered with the above units the total cost is ONLY £11 10s., showing a saving of 10/- . Customers ordering by post are requested to add 12/6 carriage, plus 10/- deposit on a returnable packing case.

The receiver is, of course, designed for reception from Alexandra Palace, but for use in the Birmingham Area when transmissions start. It will only be necessary to utilise coils having slightly less turns, as the Birmingham Station is of a higher frequency. Midland Constructors are advised to purchase now, even if they do not intend to build immediately. Supplies of the Radar Units at the moment are ample, but the demand is very great. Please bear with us if there is a few days' delay in delivery, as all orders are dealt with in strict rotation.

Optional items which are available are an Aerial, designed for indoor use, at only 15/-, and a Magnifying Lens which adds to the entertainment value by increasing the picture size, at 29/6 (postage on each 1/6).

For the convenience of callers, we are two mins. from High Holborn (Chancery Lane Station), and 5 mins. from King's Cross (Buses 18b, 613, etc.). We are open from 9-6, Saturdays 9-1. C.W.O., please. S.A.E. for lists.

**U.E.I. CORP.**

**THE RADIO CORNER**  
138, GRAY'S INN ROAD, LONDON, W.C.1

(Phone TERminus 7937.)

**PREMIER RADIO CO.**

MORRIS & CO. (RADIO) LTD.

GOVERNMENT SURPLUS MAINS TRANSFORMERS. All are for use on 230 volt 50 cycle Mains.

Type 33	38 v. 2 a. Tapped at 32, 24, 30 v.	15/-
42	500-0-500 v. 170 mA 4 v. 4 a.	25/-
44	10 v. 5 a., 10 v. 5 a., 10 v. 5 a.	35/-
51	350-0-350 v. 60 mA, 6.3 v. 1 a., 6.3 a. 2.5 a.	12/6
53	250-0-250 v. 60 mA, 5 v. 2 a., 6.3 v. 2-3 a.	15/-
54	275-0-275 v. 60 mA, 5 v. 2 a., 6.3 v. 2-3 a.	15/-
55	250-0-250 v. 100 mA, 5 v. 2 a., 6.3 v. 3-5 a.	17/6
56	330-0-330 v. 70 mA, 5 v. 2 a., 6.3 v. 2-3 a.	17/6
57	300-0-300 v. 70 mA, 4 v. 2 a., 4 v. 3-5 a.	17/6

**LOUDSPEAKERS BY FAMOUS MAKER**

5in. P.M. 2-3 ohms	10/11	10in. P.M. 2-3 ohms	23/6
6in. " 2-3 "	16/5	12in. " 15 "	85/-
8in. " 2-3 "	17/6		

**TANK AERIALS.** Seven 2ft. lengths of tube which fit into each other, making a very efficient aerial. 3/6 each. Rubber Bases to fit 2/8 each.

**NEW 2-VALVE ALL WAVE KIT.** 16 to 2,000 metres. Switched Coil Pack ready wired and tested. 2 Mazda HL23 Valves, Phones, H.T. and L.T. Batteries, Condensers, resistors, diaphragms and steel case. All ready to assemble. £3/19/-, including Purchase Tax.

**NEW 1948 MIDGET SUPERHET RADIO KIT,** with Illuminated Glass I Dial, All parts, including Valves, M/C Speaker and instructions, 4 valves plus Metal Rectifier. 16-50 metres and 200-57 metres. 200 to 250 v. A.C. or A.C./D.C. mains. State which is required. Size. 10in. x 6in. x 6in. £8/5/-, including Purchase Tax.

**MIDGET RADIO CABINETS** in Brown Bakelite. Can be supplied for the above Midget at 25/-, including P.T.

**NEW MIDGET T.R.F. RECEIVER.** Special offer of completely built and tested T.R.F. Receivers in bakelite cases. Medium and Long Wavebands. Size, 12in. x 6in. x 6in. Two models are available, an A.C. and an A.C./D.C. Both for 200-250 v. mains. These are offered at the pre-war price of £7/19/6, including Purchase Tax.

**COLLARO ELECTRIC GRAMPHONE MOTOR** with 12in. turntable. A.C. 100/230 v., £5/18/4.

**CONRAD ELECTRIC GRAMPHONE MOTOR,** 9in. turntable, 200/250 v. A.C., £7/8. All above motors include Purchase Tax.

**COLLARO AUTO CHANGERS.** Mixer/Changer Rim Drive. High fidelity crystal pick-up. Repeat reject mechanism. £14/8/8.

**COLLARO A.C./D.C. GRAMPHONE MOTORS,** with turntable but without pick-up or auto stop, £8/5/6.

**H.T. ELIMINATOR AND TRICKLE CHARGER KIT.** Consists of a complete kit of parts to construct an H.T. Eliminator with an output of 120 v. at 20 mA and provision for Trickle Charging a 2 v. Accumulator. Two Metal Rectifiers are employed. With circuit, 35/-.

**SPECIAL OFFER OF ELECTROLYTIC CONDENSERS.**

16+16 mf. 500 v. working, Cardboard	4/11
8+8 mf. 500 v. " "	4/11
32+32 mf. 350 v. " All Cans	5/11
32 mf. 350 v. " "	2/6
16 mf. 350 v. " "	2/6
16 mf. 450 v. " Cardboard	3/9
8 mf. 450 v. " "	3/-
4 mf. 500 v. " "	2/-
16+8 mf. 450 v. " All cans	4/11

**2 VOLT 18 AMP ACCUMULATORS, 7/8.** Type 1355 Units, used. 30/-, plus 10/- packing and carriage, new, 45/- . R.F. Units Type 24 or 25 for same, used, 12/6. R.F. Unit Type 26, new, 27/6. Supersensitive Balanced Armature Double Headphones, low resistance, 3/8.

**AERIALS,** aluminium 7-section, total length 5ft. 6in., make excellent dipole, 3/11. Resistors, high stability, plus minus 2 per cent., 1s. 10/- 100K, 1 meg., 1/- each, either type. Morse Code Training Sets, consist of a good quality key and high-note buzzer, mounted on a base. 3/6. D.C. Generators for engine drive, 12 v. 500 w., 30/- . Germanium Crystal Diodes, type CV102. A super biased detector for crystal sets. 3/8. Balanced Armature Single Ear Pieces supersensitive 70 ohms, 1/9. Meter Kils, moving coil meters, 2 1/2 in. diam., flush mounting, scaled 15 v. and 600 v., complete with multipliers to read 1.5 v., 15 v., 60 v., 150 v. and 600 v., 10/- . 2 Volt Vibrators synchronous type, complete with transformer, output 135 v. 30 mA., 12/6 the pair.

**POST ORDERS TO 167, LOWER CLAPTON RD., E.5.**

Phone : Amherst 4723.


**CALLERS TO 152/3, FLEET ST., E.C.4.** Central 2833.

**NEW BRANCH : 207, EDGWARE RD., W.C.2.** Ambassador 4033.

This branch is open until 6 p.m. on Saturdays.

Our 1949 List is available. Please send 2d. stamp for copy.

# RM Extension SPEAKER TYPE 3815

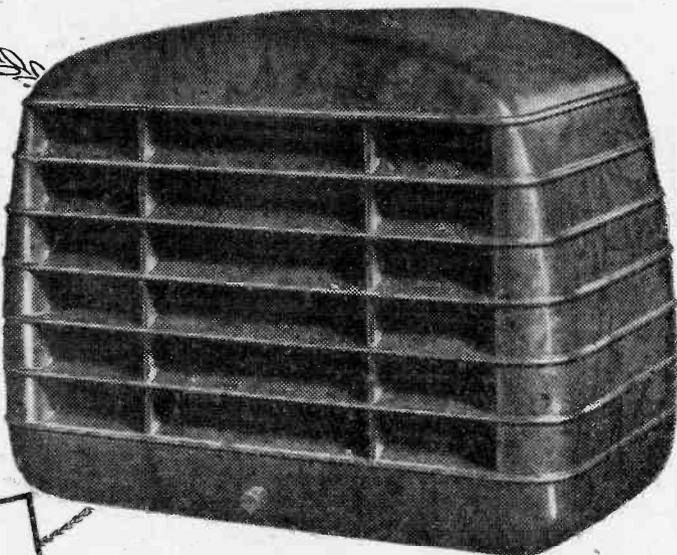

**LIST PRICE**  
**£2 14. 6.**

Here is an attractively styled Extension Speaker designed to provide entertainment in any room. It incorporates a highly efficient permanent magnet chassis, 6 $\frac{1}{2}$ in. diameter, having an impedance of 2-3 ohms. 9 $\frac{1}{2}$ in. x 7 $\frac{1}{2}$ in. x 5 $\frac{1}{2}$ in. Plastic Cabinet, Walnut Finish. The volume control is continuously variable.

R.M. ELECTRIC LTD., TEAM VALLEY, GATESHEAD 11,



# 'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set. Stocks are now available of these two famous "Avo" Instruments. If you have any difficulty in obtaining one locally, please send us the name and address of your nearest Radio Dealer.

## The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.

Size: 4 $\frac{1}{2}$ ins. x 3 $\frac{1}{2}$ ins. x 1 $\frac{1}{2}$ ins.  
Nett weight: 18 ozs.

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price: £8 : 10 : 0

## The D.C. AVOMINOR

is a 2 $\frac{1}{2}$ -inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4 $\frac{1}{2}$ ins. x 3 $\frac{1}{2}$ ins. x 1 $\frac{1}{2}$ ins.  
Nett weight: 12 ozs.

Complete as above.

Price: £4 : 4 : 0

D.C. Voltage	A.C. Voltage
0-75 millivolts	0-5 volts
0-5 volts	0-25 "
0-25 "	0-100 "
0-100 "	0-250 "
0-250 "	0-500 "
0-500 "	
D.C. Current	Resistance
0-2.5 milliamps	0-20,000 ohms
0-5 "	0-100,000 "
0-25 "	0-500,000 "
0-100 "	0-2 megohms
0-500 "	0-5 "
	0-10 "

**GUARANTEE:** The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new Avominor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

Sole Proprietors and Manufacturers—  
**AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.**  
Winder House, Douglas Street, London, S.W.1.  
Phone: VICTORIA 3404-9

# Practical Wireless

17th YEAR  
OF ISSUE

EVERY MONTH  
VOL. XXV. No. 513 APRIL, 1949

and PRACTICAL TELEVISION

Editor F. J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

## Television Servicing

**T**HE City and Guilds of London Institute, in conjunction with the Radio Trades Examination Boards, has, as reported elsewhere, drawn up a syllabus for a television servicing certificate examination. The City and Guilds of London Institute certificates are a hall mark of technical qualifications in a wide number of industries. Had they, in the early days of radio, produced a similar scheme the public would have been safeguarded against swindlers, quacks and incompetent service engineers, and we should not have, even to-day, so many complaints regarding exorbitant charges for inferior work.

The C.G.I. is to be congratulated upon being so early in the television field. Television is developing, and if, as is confidently hoped, the purchase tax is removed after the budget in April there will be many more viewers and a corresponding increase in the demand for competent service engineers.

The servicing of a television receiver is a more complicated task than servicing an ordinary sound receiver, and it requires a more specialised knowledge as well as a greater range of test equipment.

Moreover, the average householder will not be able to undertake even the simpler adjustments of a television receiver, adjustments which he is able with confidence to effect in sound receivers, not only because he will not have the necessary equipment, but because of the high voltages employed and the corresponding danger if repairs are attempted by unskilled hands. The examination will comprise two written papers, each of three hours' duration, and a practical test of three hours' duration, and candidates must satisfy the examiners in all sections of the examinations. The written papers, set by the City and Guilds of London Institute, may contain questions selected from any part of sections A and B of the following syllabus:

Section A: Light and Vision; Production of the Picture Signal; Reproduction of Picture from Signal; Complete Simple Television System; B.B.C. Standard Transmission; Reception of Standard Transmission.

Section B: T.R.F. Receiver; Superheterodyne Receiver; Demodulation; Video-Frequency Amplification; The Cathode Ray

Tube; Time Bases; Synchronising Pulse Separation; Sound Receivers; Power Supply Circuits; Aerial and Feeder Systems; Interference; Picture Defects, their Cause and Correction; Servicing Requirements.

Practical tests will be conducted under arrangements made by the Radio Trades Examination Board, and will include a soldering test of half an hour's duration. The written examination may be taken at centres throughout the country, at which other City and Guilds examinations are taken. The practical tests will be held at a smaller number of centres, each within the range of a television transmitter, and candidates will be asked to attend at the most convenient centre. Successful candidates will receive the television servicing certificate.

Entries must be made on a special form, obtainable from the Secretary, Radio Trades Examination Board, 9, Bedford Square, London, W.C.1. The examination fee is three guineas.

### Car Radio Licences

**I**T is not generally realised that when a radio set is fitted to a car, a separate licence is required. The impression seems to be abroad that if a licence is taken out in respect of the home radio set this also covers the use of another wireless receiver in the car. The police, we understand, are instituting an extensive drive to detect unlicensed car radios. This drive, which will continue throughout the year, will be extended to all parts of the country.

### More Copies of P.W.

**A**S a result of the increasing paper allocation many readers who have hitherto been unable to obtain this journal will be able to do so. The extra allocation does not, unfortunately, enable us to enlarge the journal, nor to revert to weekly publication. The whole of the allocation is being used to print extra copies, and so to reduce our lengthy waiting lists of would-be subscribers. The latter should go to their newsagent forthwith, and place an order for the regular delivery of this journal. It is still not possible for supplies to be made available to newsagents for casual purchasers.

Editorial and Advertisement Offices:  
"Practical Wireless," George Newnes, Ltd.,  
Tower House, Southampton Street, Strand,  
W.C.2. 'Phone: Temple Bar 4363.  
Teletrans: Newnes, Rand, London.  
Registered at the G.P.O. for transmission by  
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.  
Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

# ROUND THE WORLD OF WIRELESS


## Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ended December 31st, 1948.

Region	Number
London Postal .. .. .	2,134,000
Home Counties .. .. .	1,512,000
Midland .. .. .	1,617,000
North Eastern .. .. .	1,784,000
North Western .. .. .	1,482,000
South Western .. .. .	1,001,000
Welsh and Border Counties ..	662,000
<b>Total England and Wales ..</b>	<b>10,192,000</b>
Scotland .. .. .	1,078,000
Northern Ireland .. .. .	187,000
<b>Grand Total .. .. .</b>	<b>11,457,000</b>

The above total includes 92,800 television licences—an increase of 10,400.

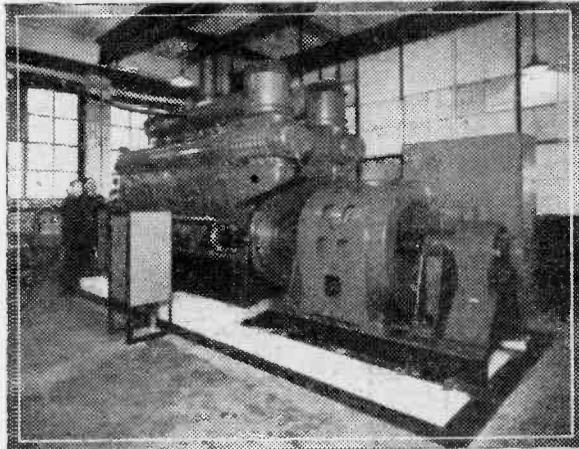During December 658 prosecutions were authorised for operating wireless receiving sets without a licence. This number includes several cases of motorists who did not have separate receiving licences for the wireless sets fitted in their cars.



The newly installed 600 kW generator at Philips' Mitcham Works.

## Radiolympia Organiser

THE Radio Industry Council's exhibition organising committee has appointed Dudley Stretton as organiser of Radiolympia (September 28th to October 8th) in succession to the late Alex. Moody. His appointment dates from February 1st.

Mr. Stretton is 45 years of age, and whilst with the Ministry of Information was responsible for the Exhibitions Division, "Greater London Plan" exhibition and the tours of "Back to Work" and "Mulberry."

## E.M.I. Technical Papers

REPRINTS of Technical Papers read by members of the staff of Electric and Musical Industries, Ltd., before learned societies are now available at 2s. 6d. per copy. These Papers are printed on art paper with a semi-stiff cover, and are well illustrated. The titles at present available are:

Commercial Disc Recording and Processing: B. E. G. Mittell.

The Development of Sound Recording and Reproduction: Sir Ernest Fisk.

Sound Recording and Reproduction: G. F. Dutton.

High Quality Disc Recording: W. S. Barrell.

Others will be produced in due course.

Applications for copies of the above should be addressed to Advertising Division, E.M.I. Sales and Service Ltd., Hayes, Middlesex.

## National Ekco Radio in India

FOLLOWING the recent agreement with the Tata Organisation for the manufacture of Ekco radio in India, E. K. Cole, Ltd., now announce the name of the newly formed company. It will be known as The National Ekco Radio and Engineering Company Ltd., with offices at Bombay House, Bruce Street, Bombay. Products, on which manufacture is starting immediately, will be distributed by General Radio & Appliances, Ltd. (previously Fazalbhoy Ltd.). Big developments in the V.H.F. and electronic fields as well as domestic radio are planned.

## B.B.C. Helps Police at Cup-tie

AT the thrilling Yeovil v. Sunderland Cup-tie recently, F. N. S. Creek, the B.B.C. commentator, was probably more exhausted than the players.

Creek, who is an ex-amateur international, was briefed by the West of England sports editor, Nicholas Crocker, to record the high-lights of the game—five or six minutes of commentary for "Sport in the West" the same evening. But between two and three thousand people gathered in the narrow street outside the packed Huish Football Ground unable to obtain admission, so Police Superintendent G. S. Hamham asked the B.B.C. to help them to keep control of the situation. B.B.C. engineers Pyke and Fraser ran a line out to two police wireless cars and the locked-out spectators were then able to hear the commentary.

Norman Creek found he had to give 110 minutes of commentary as extra time had to be played instead of the 20 or 25 minutes of high-lights that he had intended to give. Then he rushed back to Bristol by car through the fog to introduce his own recordings in "Sport in the West," walking into the studio just as the red light went on.

### The British Institution of Radio Engineers

THE London Section held a meeting at the London School of Hygiene and Tropical Medicine recently, when a Paper on "Radio Frequency Welding," was read by Mr. L. Grinstead (Member) and Dr. H. P. Zade.

The Paper considered the influence of frequency, voltage, variation in physical constants and thermal conductivity in the welding of thermo-plastic materials at radio frequencies.

Suitable R.F. generator circuits were specified and analysed in detail, and a review of present and future trends in R.F. welding technique was included.

### Stand-by Generator

A NINE-HUNDRED horse-power diesel engine driving a 600 kW. generator has been installed at the Mitcham Works of Philips Electrical Ltd. in a specially built power house.

Night workers will be relieved for day duty by the provision of this equipment, as its output is about one-quarter of daytime consumption.

The 900 horse-power diesel component was designed and used as one of a pair of propulsion units in a tank landing craft. It weighs well over 15 tons and was purchased in the U.S.A., no suitable equipment being obtainable quickly in this country.

The Philips Plant Department at Mitcham constructed all accessory equipment, such as switch-board, control panels, cables and connectors and piping. For the storage of fuel a tank with a capacity of 28,000 gallons has been provided.

Further stand-by power arrangements have been made at other factories of the Philips Group.

At Philips, Balham, 100 kW. are provided, at Brixton, 60 kW.

Mr. L. H. Kendrick, senior plant engineer, said, in an interview:

"Two main purposes are served by the installation of these generators. We are complying with the Ministry of Fuel and Power's request to provide as much of our own power as we can to relieve the load on the public supply and, further, we feel a good deal less at the mercy of the weather this winter."

Mr. A. H. Whiteley, M.B.E.

READERS and many friends in the trade will be pleased to learn that Mr. A. H. Whiteley, of the well-known firm of Whiteley Electrical (makers of the W.B. speakers), has been awarded the M.B.E. in the New Year Honours List in recognition of his services to the A.T.C.

### V.H.F. in Fact and Fiction

V.H.F. two-way radio telephony is rapidly breaking into many commercial fields.

Recently it has appeared in two quite unexpected places—one in fact and the other in fiction.

First, it was announced that a team of three Hillman Minx cars competing in the Monte Carlo Rally were equipped with Pye two-way V.H.F. mobile R/T for intercommunication between the three cars during the three and a half days' journey.

Second, two-way R/T appeared in its first strip cartoon, for Buck Ryan, hero of a hundred thrilling exploits in the *Daily Mirror*, adopted this latest V.H.F. development to aid him in chasing lorry bandits on the Great North Road.

In both cases, however, while showing ingenuity, this use of car-to-car communication must be regarded as exceptional, for in the ordinary way such equipment is permitted to be used only in conjunction with a fixed station.

The coincidence of the use of Pye equipment at this time for two such dissimilar purposes is perhaps not so extraordinary as it would seem. Mr. J. H.

Kemsley, of Petts Wood, Kent, is an enthusiastic user of their R/T apparatus in his hire car service.


In the case of Buck Ryan, cartoonist Jack Monk, approached Pye Telecommunications London Publicity Office to obtain photographs of Pye R/T equipment, on which his drawings are based.

### GOOD NEWS

We are now permitted by Paper Control to print more copies, although not sufficient to meet all demands. If you have not succeeded in obtaining PRACTICAL WIRELESS regularly, we would advise you to ask your newsagent at once to reserve a copy of every issue for the future. We hope you will be successful, but do not blame your newsagent if his supplies have already been exhausted.
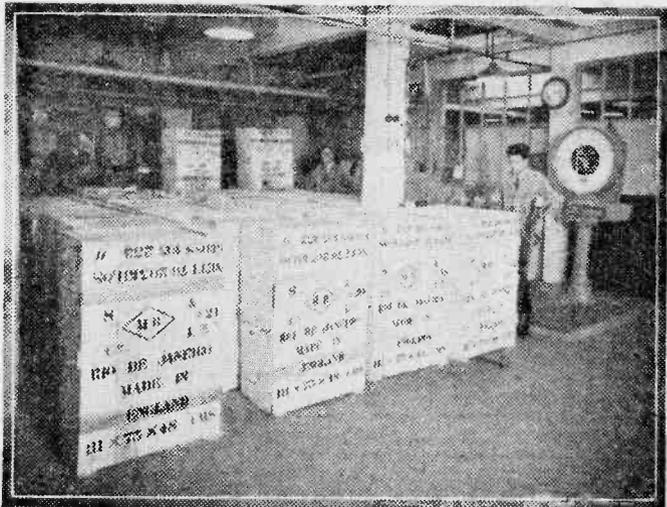
### Eddystone Brazilian Order

IN face of strong competition from U.S.A. and neighbouring countries, Messrs. Stratton & Co. secured an order for 100 of their "640" communication receivers for Brazil.



Some of the 100 Eddystone "640" receivers ready for despatch to Brazil.

# Remote Control of Your Receiver—2

This Month J. R. DAVIES Discusses Some More Schemes

**T**HE usual form of tone control which uses a variable resistor, and is shown in Fig. 5(d), is not of great use in the speaker circuit. This is because the relatively large power that may be developed in the A.F. circuit across the variable resistor is liable to cause arcing between the slider and the track, particularly when the slider is very nearly at the minimum resistance position.

## Switching the Set On and Off

When we leave the province of volume and tone controls for that of switching the set on and off remotely, we leave the field where control may

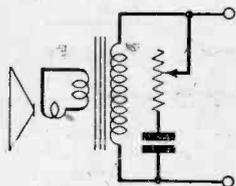


Fig. 5(d).—A method of tone control which is NOT recommended for connection at the speaker.

be effected by purely electrical means and enter that where use must be made of electro-mechanical devices. In other words, we have to start thinking of relays!

Fig. 6 shows the simplest possible circuit in which a relay may be used for switching a receiver from a distant point. It has the great disadvantage that, whilst energised, the battery is continually draining through the coil. For the home-constructor this method is therefore uneconomic and wasteful.

A home-constructed trip-operated relay as shown in Fig. 7 will afford a very useful substitute, however. It is very simple to construct and its operation is as follows: On pressing the remote

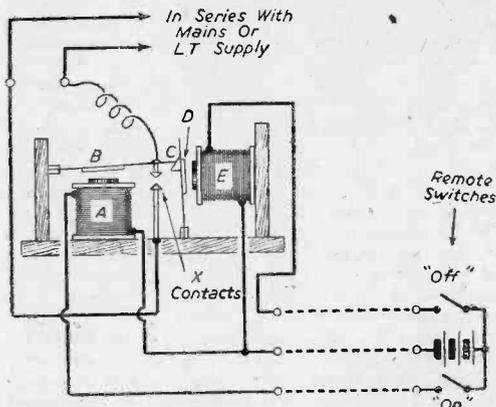


Fig. 7.—A trip mechanism for switching a receiver which takes current only momentarily from the energising battery.

“On” button the coil A energises, pulling the armature B towards it thereby making the contacts X. The button is then released and the armature B is held in position by the catch C on the second armature D. When the “Off” button is depressed the coil E is energised; this attracts the armature D, thus releasing the armature B, which springs back to its original position, breaking the contacts X and switching the set off again. The “Off”

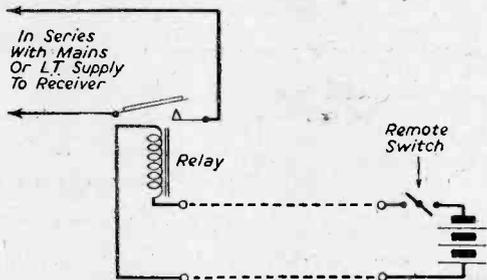


Fig. 6.—Simplest method of remotely switching a receiver on and off.

button may then be released, whereupon the whole cycle of operations can be started again.

Another system which uses only two wires between the two points makes use of a polarised relay, which may also be home-made, and which is shown in its essentials in Fig. 8. An armature A is pivoted at B and is free to move between the poles of a permanent horseshoe magnet C, as shown by the arrows. When the remote “On” button is pressed the armature is so energised by the coil C that the end adjacent to the magnet poles is magnetised as a south pole. This causes it to be repelled by the south pole of the permanent magnet and attracted to the north pole. It therefore swings over to the latter pole. This causes the contacts X to be made, thereby switching on the set. The “On” button is then released but, despite the lack of energising current, the attraction between the armature and the magnet pole still holds the armature in position. When the “Off” button is pressed, due to the method of connection of the remote batteries the current now flows through the coil C in the opposite direction and the end of the armature becomes a north pole. This causes the reverse of the previous operation and the armature swings over to the south pole of the permanent magnet, breaking the contacts X and switching the set off. Two brass slugs, D and E, are fitted to the magnet poles to prevent the armature actually touching them, as otherwise sticking might occur.

A third and very effective method of switching the remote receiver on and off, and which again only uses two interconnecting wires, is shown in Fig. 9. For this circuit one relay only is required. This relay is a high-resistance model having a resistance

of some 2,000 ohms or so and requiring 5 milliamps energising current to close. This circuit is only practicable with mains receivers, mainly because the relay is energised from the H.T. supply, and it would be very wasteful (and expensive!) to use an H.T. battery for this purpose.

The sequence of operations is as follows: When the remote switch A is depressed the batteries B energise the relay, which closes, switching on the receiver. After some seconds, the rectifier in the receiver will have warmed up sufficiently to pass H.T. current. The remote switch may then be released, and the relay will remain closed by the H.T. supply of the receiver, via the limiting resistor. When it is desired to switch off the receiver, the

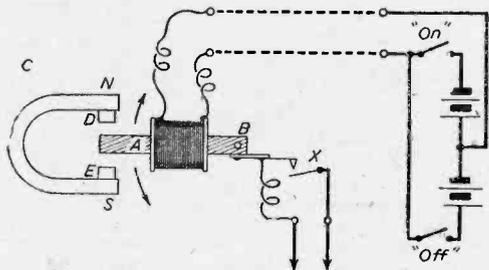


Fig. 8.—A polarised relay which takes current only momentarily from the energising battery and which only requires two leads for interconnection.

button C is depressed. This shorts out the relay winding, which then opens. The limiting resistor ensures that no excessive H.T. current is passed. The only disadvantage with this circuit is that the remote battery B needs to have a relatively higher voltage for the initial switching on. However, 25 volts is a more than sufficient value and can easily be supplied by means of three 9-volt grid bias batteries in series. It is also important to see that the battery is connected as shown in Fig. 9, as otherwise its voltage, when switched on, will be in opposition to that from the H.T. supply.

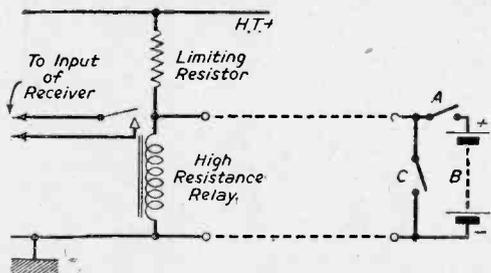


Fig. 9.—A relay circuit which may be used with a mains type receiver where there is no necessity to economise with H.T. current. The limiting resistor should have a value of approximately 40 KΩ and a rating of 5 watts.

**Tuning the Receiver Remotely**

To obtain complete control of the receiver, the only additional circuit that we now require is one that will tune the receiver remotely. This is a

more difficult task than those previously discussed, and the complication of the circuit required is governed entirely by the number of alternative programmes that are desired.

Taking the simplest instance first, let us assume that only two stations, both on the same wave-band, are required. Fig. 10 shows how switching may be applied to a receiver with two tuned circuits, these being either the R.F. and detector circuits of a T.R.F. receiver, or the aerial and oscillator circuits of a superhet. (If a T.R.F. receiver is used it may be necessary to screen the two "live" relay contacts from each other to prevent instability.) The receiver is tuned by the

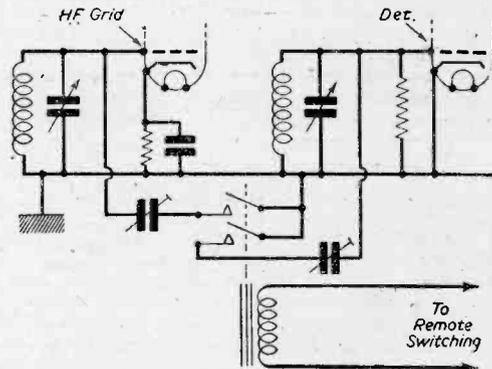


Fig. 10.—A simple method of changing stations using one relay.

normal tuning condenser to that one of the two stations which requires the least capacity in the tuned circuit for resonance (i.e., the station having the higher frequency). When the relay is closed the two preset condensers are then adjusted to bring in the second station. When it is desired to listen to the receiver from a remote position the set is tuned primarily to the first of the two required stations. Should the second station be required the relay is then energised, the required programme being switched on instantaneously. The trouble with this system is that it may be necessary to energise the relay for long periods of time. For the purposes of economy the energising voltage may be obtained from the accumulator in the case of a battery set, or from the H.T. supply (as in Fig. 9) in the case of a mains receiver. In the latter case, incidentally, it is better to employ the "shorting" method of switching the relay on or off as is done by the pushbutton C in Fig. 9, as this will ensure that the full H.T. voltage does not find its way into the remote control lines, with possible risk of shock or breakdown.

This method of changing stations may be extended, of course, by the simple process of using more relays if a greater choice of programmes is required. A further relay may also be added for wave-change purposes. The whole idea is quite practicable, the only snag being that of battery consumption mentioned above; and it might be well worth while, if the construction of a new receiver is being contemplated, to incorporate a sufficient number of relays into the H.F. and detector (or frequency-changer) tuned circuits in the original design.

An entirely different method of tuning the receiver remotely is offered by using a version of the uni-selector. This possesses the advantage that

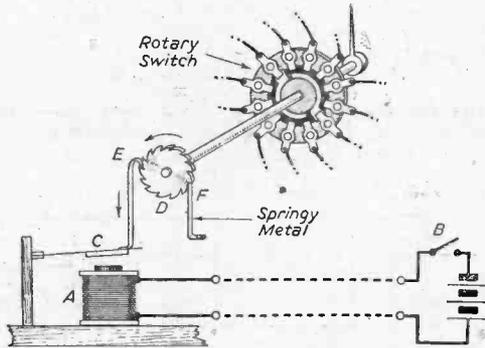


Fig. 11.—A solenoid operated rotary switch which may be used for station selection.

only momentary current is required for station selection and that only two interconnecting wires are needed. Given sufficient ingenuity a rotary switch may be constructed following the design of that shown in Fig. 11. The coil A, when energised by depressing the remote button B, pulls down the armature C. This, in turn, pulls round the ratchet wheel D by means of the hook E. When the button is raised, the coil A is de-energised and the hook springs back to the next tooth of the ratchet wheel, ready to bring it round when required. To prevent the wheel from turning backwards on the release of the hook, a pawl F is fitted, being so adjusted that it just falls from one tooth to the next when the coil is energised. The ratchet wheel is fitted to a spindle, this latter rotating a switch arm designed to make a different contact at each position of the wheel. (If the ratchet teeth are close together, these contacts may be made at spacings of two or three teeth.) When it is desired to set the switch to a

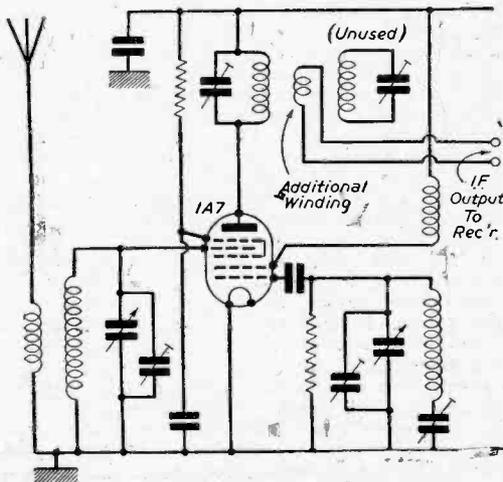


Fig. 12.—A remote tuner unit.

different position, the remote button B is pressed the requisite number of times. This, incidentally, is a very simplified version of what occurs when a telephone number is dialled, the button B being replaced by the dial which, among other things, makes and breaks a contact a pre-arranged number of times, that number being proportional to the one dialled.

**Using a Separate Frequency-changer**

Yet another method of tuning a receiver, and one which enables as many stations as are required to

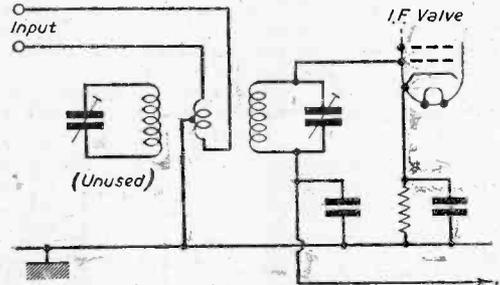


Fig. 13.—Connecting the receiver to the tuner unit.

be received, can be provided by using a separate tuning unit consisting of a frequency-changer with its associated tuned circuits, the intermediate frequency being led to the receiver by means of lines, where it is subsequently amplified and detected.

Fig. 12 shows a typical example. A 1A7 type valve is used, in common with a small, or midsize, two-gang condenser. The coils may also be of small dimensions; Wearite "P" coils, for instance, being excellent for the purpose. The intermediate frequency is fed from the anode of the 1A7 to the I.F. transformer, one coil of which is unused, although it should be tuned to give maximum results if a tightly coupled transformer is chosen. To obtain a low impedance outlet to the receiver about 15 turns of thin d.e.p. or d.s.c. wire are wound on the transformer, these being connected to the lines to the receiver. Fig. 13 shows the method of coupling used at the receiver. Again, about 15 turns are added to an I.F. transformer, but this time care must be taken to see that they are accurately centre-tapped and are physically symmetrical on either side of this centre connection. This is to minimise radiation as far as is possible and ensure that no interference with neighbouring receivers results. For this purpose it is also advisable to use screened wire for the interconnecting link. Alternatively, lighting flex, or similar wire, could be used, provided that it runs for all its distance alongside a well-earthed pipe, such as a mains conduit, and is actually touching the pipe all the way. This would ensure considerable attenuation of any radiation.

(To be continued)

**DUSTBIN MENACE**

Waste Paper thrown out as rubbish means  
dollars lost to Britain, so save every scrap.

# Using the Oscilloscope-5

Further Investigations Using Oscillograph Technique and an Interesting Time Base

By H. R. McDERMOTT

OF the many interesting tests and experiments that can be performed with the aid of the oscillograph there are few that require such a small number of auxiliary items as the simple time base to be described. Apart from the oscillograph, the only extra components required are one condenser and a variable resistor—not a very imposing list! The name "Time Base" does, to me at least, conjure up a vision of a horizontal line produced by the rapid motion of the spot from

far and that such a simple arrangement could not possibly do these things; however, a little further thought on the matter will help.

### Time-controlled Mains

As previously mentioned in this series of articles, most of us have available in our homes a most accurate time-piece, (No! not that alarm clock) in the form of the time-controlled A.C. mains. Let us consider the method by which the circle is formed. It is evident that the spot revolves in a circular orbit, but what we require to know is the time taken by the spot to complete one revolution. If a very low frequency alternating E.M.F., say one cycle per second, were applied across a suitable R and C in series, then it would be observed that the spot performed one revolution each second; it follows that if the applied frequency were 50 cycles/sec., then the spot takes 1/50th sec. to complete one revolution and if 1,000 cycles/sec., 1/1,000th of a second. We are now in the happy position of knowing that when using 50 cycle mains the spot revolves once in 1/50th, i.e., 0.02 sec., and due to the combination of the tube afterglow and persistence of vision, we see a stationary circle, the problem remaining being the practical one of how to make use of this unique time-piece.

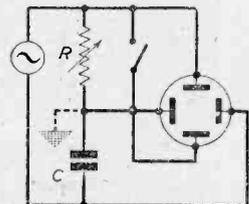


Fig. 1.—Circuit of a simple form of circular time base.

left to right, but this time base is rather different in that a circular trace is normally produced on the screen of the instrument.

The circuit of this circular time base is nothing more than that of a simple R.C. phase splitter as shown in Fig. 1. If the sensitivity of both X and Y plates is equal and the voltages applied to them are equal too, and 90 or 270 degrees out of phase, a perfect circle will be produced on the screen. It is obvious that if we use a perfect condenser C, and a resistor R, then the voltage across C will lag, by 90 degrees, that present across R, and if these E.M.F.'s are equal then a perfect circle will be produced. To ensure that the voltage across the condenser and that across the resistor are equal, it is necessary that their impedances should be equal at the frequency under consideration. The required condition is that  $R=1/\omega C$ , and for a frequency of 50 cycles, C may be 0.1  $\mu F$ , and R, a 50,000 ohm variable resistance. The voltage required to produce an adequate circular trace on the screen depends on the sensitivity of the deflecting system of the tube, but generally 80 to 100 volts will be sufficient and may be obtained from a transformer or auto-transformer. The object of the variable resistor is to help compensate for any differences in the deflection sensitivities of the X and Y plates, and also in the measured value of the condenser C, apart from its value as stated on the label.

With this simple arrangement we can do some quite remarkable feats. For instance, we can measure very small periods of time, such as the opening and closing of a camera shutter or the speed with which various switches and relays operate, quite easily to an accuracy better than one tenth of a milli-second. Your first thought may be to suggest that this is stretching things just a little too

Probably the simplest method of utilising our knowledge is in the testing of a camera shutter, but before going any further, let us set up the equipment ready to perform the experiments. The top end of resistor R (Fig. 1), is connected to the Y or vertical plate and the bottom end of condenser C attached to the X or horizontal plate, the junction of R and C going to the common X and Y plate, usually earthed. The combination of R and C in series is fed from a 100-volt 50-cycle source.

The procedure for making the test is extremely simple and consists of taking a photograph of the tube screen. The camera is, of course, placed at a suitable distance from the oscillograph screen, depending on the type of lens used in the camera, so as to obtain good focus on the film. The more

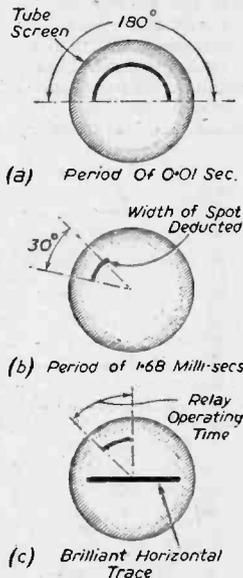


Fig. 2.—Oscillograph traces from the circular time base.

expensive cameras have high-speed shutters, usual times for operation are 1/100th and 1/250th of a second. You can imagine the difficulty in making sure, by ordinary methods, that the speeds are as specified. The speed at which the shutter opens and closes makes it impossible to judge at all accurately whether all is well.

Let us think for a moment of the revolving spot with the camera facing the screen ready for checking at 1/100th sec. When the camera shutter opens and closes in this position, the film should have been exposed for exactly 1/100th of a second; we know that with a 50-cycle voltage applied the spot takes 1/50th of a second to travel 360 degrees, so that in 1/100th of a second it will have covered half this distance, Fig. 2(a), i.e., 180 degrees, a semi-circle, and so we view the picture on the developed film. If the picture obtained is not a semi-circle, then it is obvious that the camera shutter did not stay open for 1/100th of a second. If the resulting

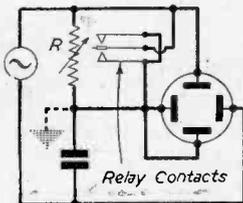


Fig. 3.—Modification of Fig. 1 for relay testing. The input to this and to Fig. 1 is a 50-cycle 80-100 volt A.C. supply.

arc was greater than 180 degrees, then the shutter was open for longer than 1/100th sec., and, if the arc was less than 180 degrees then the shutter-operating time was less than 1/100th-second.

#### Method of Calculation

By means of a simple calculation we can reckon the time period indicated by say, one degree.

If the spot revolves 360 degrees in 1/50th sec., i.e., 0.02 sec., one degree is covered in:

0.02

—sec. = 0.0000556 sec. = 0.0556 milli-sec.

360

= 55.6 micro-sec.

From this we can calculate the time period represented by any arc by measuring the angle, in degrees, subtended by it at the centre of the circle, and multiplying this by 0.0556 to obtain the time in milli-seconds, i.e., thousandths of a second. Few precautions are necessary, the main points being that a short persistence cathode ray tube is needed in order to avoid errors due to the afterglow of the screen and that, for accurate results, the width of the spot should be subtracted from the measured angle of the arc as in Fig. 2(b).

Often, it is necessary to know the speed, or otherwise, of operation of various relays and switches in some particular signalling circuit, which may be remote controlled. Again we are able to use this phase-splitting circuit to measure with good accuracy the lag in the opening and closing of the switches under consideration. Most normal relays take from three to 20 milli-seconds to operate and the measurement of this is easily within the scope of the device.

The method employed uses the same resistor and condenser as the previous circuit, but in parallel with R are the contacts of the relay to be tested.

The circuit is arranged so that when the relay is at rest, R is shorted out and when the relay has closed R is also shorted out. It is only during the transient period of the relay, i.e., the period when it is actually operating, that R is again present in the circuit. The effect of this is that whilst R is shorted, the alternating voltage applied to the vertical plates is shorted too, resulting in the circle collapsing into a horizontal straight line. Whilst the relay is operating, R is no longer shorted and the spot, instead of travelling back and forward in a horizontal direction, leaps out from the line and starts to travel in a circular path. When the transient period is completed and the relay contacts closed, the spot falls back into its horizontal path again, resulting in an arc being produced on the screen corresponding to the time taken to operate the relay contacts. This time period is calculated exactly as in the previous method, a typical screen pattern for this type of test is shown in Fig. 2(c).

The requirements of the tube in this test, without resorting to photography, are exactly the opposite of the method previously described, in that a long persistence tube is a great advantage because of the fact that the spot is not constantly travelling in a circular path and the start and finish of the arc to be measured can be judged with accuracy. If a tube with a long persistence screen is available then the arc can be measured quite easily without having to photograph the image. Certain ex-Government cathode ray tubes have screens that remain bright for as much as twenty seconds after the electron beam has caused it to fluoresce, this type is admirable for the purpose. However, any other type of tube can produce good results if the image is photographed, so at this point we will turn to some matters that are easily overlooked.

As previously mentioned, the camera is placed at a suitable distance from the tube screen and the image is photographed. The shutter must be opened just before the relay opens and immediately after it has closed, just enough to photograph the full cycle of operations. If this is not done, there is great risk of the film fogging due to the brilliance of the horizontal base line which is present on the screen all the time except during the period that the relay is actually operating. The 50 cycle mains supply, as previously noted, may be used to supply the alternating voltage required, but if other than an isolating transformer is used then great care must be exercised otherwise a few hearty shocks may be acquired. In this latter connection it is well to note that in many oscillographs one X and one Y plate are tied down to earth, and in that case a hundred or so volts may be present from the case of the instrument to a true earth. It is much better to play safe and use an isolating transformer.

When you first try out the simple phase-splitter circuit, you will, in all probability, encounter a snag in the form of difficulty in obtaining an accurate circle. The first thing to do is to try changing the value of R by means of the variable element. The effect of this is to change the E.M.F. applied to one pair of deflector plates and so alter the screen image from an ellipse to a true circle. If, even now, a true circle cannot be obtained then the fault is quite certainly due to the condenser used in position C. If this latter component has a poor power factor, the circle will become an ellipse. The remedy is obvious—replace the condenser.



# ON YOUR WAVELENGTH

By THERMION

## Earthing to Water Pipes

**A** BOROUGH water engineer recently drew attention to the danger of earthing electrical installations to water pipes, and I understand that the British Water Works Association are considering making such connections illegal. It is, of course, a common practice to connect the earth lead of a wireless set to a water pipe in flats and other domiciles where a buried earthplate would necessitate a long earth lead which, as all readers know, is accompanied by serious disadvantages from the point of view of reception. The earth lead should be kept as short as possible. This water engineer was referring to a particular case at Machen, when a "short" in the electric cooker resulted in the water supply system becoming alive, and therefore dangerous. With the frequent use of asbestos-cement pipes by water undertakings, earthing to water mains does not become effective, and a water supply system would remain alive if a "short" took place. In my view the electric supply authorities should provide their own earthing arrangements as part of the installation. There have, of course, been a number of cases, some fatal, due to the earthing of radio and other electrical apparatus to water pipes. The danger is not confined to the householder. It spreads to the Water Board employees repairing services and supply mains.

## A Tricky Point

**A**CCORDING to a new clause in the Wireless Telegraphy Bill, the Postmaster General has powers to prohibit a person who manufactures apparatus which does not comply with the regulations as to the radiation of electromagnetic energy from selling it or hiring it out. Many Northern listeners must have experienced the annoying whistle on the North Regional transmitter, due to a nearby receiver with a 465 kc/s I.F. being tuned to the Light Programme on 200 kc/s. In view of this, are manufacturers to be forbidden to use 465 kc/s., or will they be compelled to suppress the radiation in other ways? And what about the receivers already in use? Are listeners to be compelled to change their intermediate frequencies?

If this does not come under the new Bill there is nothing to prevent any enterprising youth from connecting and disconnecting his aerial at long and short intervals in order to contact his friend across the way.

No doubt the above trouble will take care of itself when the new wavelength reshuffle takes place, but meanwhile, does the hypothetical young gentleman require a transmitting licence?

## Interaction

**I**F one compares the average home-built receiver with a comparable commercial receiver, several differences will be noticed. The chief difference is that commercial receivers are more compact, whilst the home-built receiver is much more

"spread out." When the latter is tidied up and compressed a little it seldom works so well and this is undoubtedly due to poor screening and resulting interaction. It is in order to avoid this that certain conventional lay-outs have been adopted for the home constructor. The main thing to be avoided is interaction between two tuned circuits. When a set uses a stage of H.F. amplification, the grid circuit of the H.F. valve and the grid circuit of the detector (or the anode circuit of the H.F. valve—really the same thing) will be tuned to the same wavelength.

Since a tuned circuit consists of a coil and a condenser, it is obviously of little avail to screen the coils from one another while the condensers lie side by side on the front panel. This is one good reason for using a screen of the same depth as the base board, and partitioning off the H.F. stage altogether. A metal or metal-backed panel and a base board covered on the underside with copper foil help to avoid interaction.

The screen-grid valve was invented to remove the anomaly that whilst it is possible to screen the grid and anode circuits from each other, the grid and anode were still fairly closely coupled inside the valve. A meshed screen was therefore introduced between them, and the anode lead brought out at the end of the valve opposite to the others. To make the most of the screen-grid valve it is necessary to ensure that the grid and anode really are screened from one another.

## The Advance of Television

**T**HE introduction of a television supplement to this journal is a nostalgic reminder to me that the Editor of this paper in the very early days of television started a magazine entitled *Practical Television*, which suspended publication in 1939 when the television transmissions closed down. The rapid advance of television, an advance which will gather momentum within the next few years, gives me feelings akin to those I held in the early days of radio when Writtle, call sign 2MT, radiated its weekly programme of half an hour with P. P. Eckersley acting as chief announcer, chief engineer, and general factotum. I want to build a television receiver and am carefully studying all the literature on the subject and accumulating all the parts. One third of Britain's population will be within range of television this autumn when the Midlands station at Sutton Coldfield opens.

Television cost us about £700,000 in 1947-8, but only produced £91,000 revenue in that time. But £700,000 is a comparatively small sum of money to spend on the development of a science which will affect the lives of all of us, when we consider the cost of production of the Brabazon, which approaches £10,000,000. In fact, at least £10,000,000 will need to be spent on television if we are to retain the scientific lead achieved as the result of private enterprise.

# General Purpose P.A. Amplifier

An Easy-to-build Three-stage Unit with 15-watt Push-pull Output

By K. KEMSEY-BOURNE

**T**HIS unit is very economical in cost and space, since it uses for two of its stages small double triodes which each do the work of two normal triodes, and it has output valves just over 3in. high that are yet capable of giving 15 watts of audio power.

The specification of components is not critical; as long as the parts used satisfy the electrical requirements given in the list good results will be obtained. Only one resistor that is not a half-watt type is needed. All the valves are Octal based, and most of the parts will be readily available in the experimenter's workshop. No building instructions will be given here, since this circuit can be fitted on to almost any chassis in the 12in. x 8in. field, including the power-pack.

The power output is sufficient for dances, parties, and record recitals, or for providing music at dramatic shows in theatres holding up to 300 people. It could be used for recording or modulating a transmitter, and, although this is not claimed to be a high quality unit, its performance is more than adequate for most normal purposes.

## The Input Circuits

V1 provides amplification and completely independent mixing of the two inputs fed into controls R1 and R2. A high-impedance source, such as a moving-iron pickup or a radio feeder, can be connected direct to R1. Low-impedance sources, such as moving-coil microphones or pickups, are connected to R2 via a suitable matching transformer T3, which serves also to raise the signal level. T3 may be built permanently on to the

amplifier chassis or not, at the discretion of the constructor, but if it is built-in then it should be shielded in a mu-metal case and mounted as far as possible from the mains transformer; otherwise a high hum level will result whenever this channel is brought in. The inputs fed through R1 and R2 are separately amplified in the two halves of V1 and the resulting signals are mixed in the anode circuit.

These input circuits are easily modified for special requirements. To mix two high-impedance pickups, for instance, omit T3 and feed the second pickup direct into R2, and replace C2 by a resistor and capacitor in series like R6 and C3.

## Tone Control

V1 is resistance-capacity coupled to the phase-splitter stage of V2. Shunted across the output of V1 is the tone control, consisting of C4 and R7. As the setting of R7 is decreased in value the amount of tone cut is increased.

## Phase Splitter

This is a simple but effective design in which the first half of V2 amplifies the input from V1 and passes its output direct to V3 via C6. At the same time the second half of V2 receives via its cathode circuit a signal 180 deg. out of phase with the original, and this is equally amplified and fed to V4 via C7. Thus the grids of V3 and V4 are fed with equal and opposite voltages, since the two halves of V2 provide the same amount of gain. Unlike the cathode-follower this circuit serves to boost the signal level as well as feed the push-pull stage.

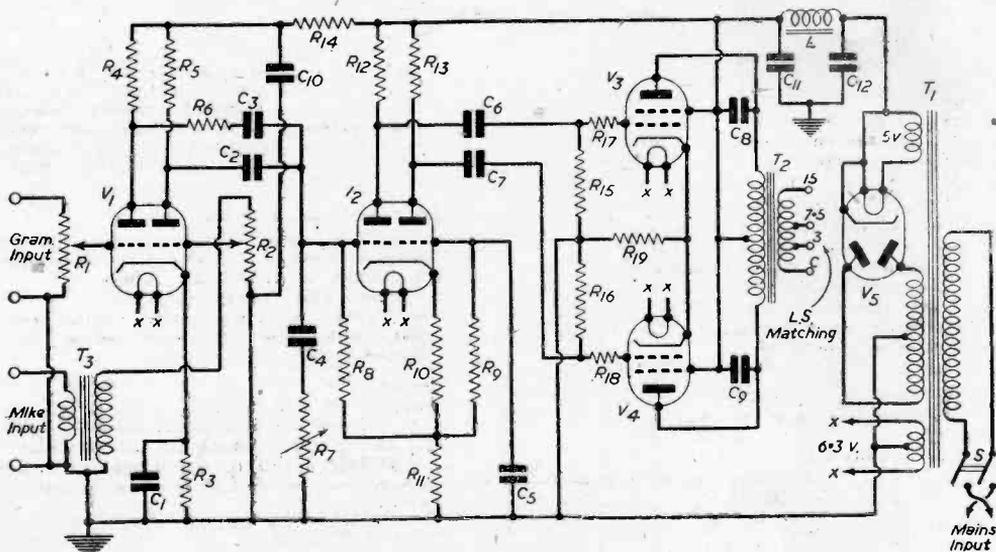


Fig. 1.—Complete circuit diagram of the amplifier described in this article.

**Output Stage**

Two beam-power valves are driven in class AB1, and will give 15 watts output with an input grid-to-grid swing of about 40 volts. The common cathode-bias resistor is not by-passed. R17 and R18 are grid-blocking resistors to suppress parasitic oscillation. C8 and C9 are shunted across the two

to 3, 7.5 or 15 ohms secondary load, or whatever value may be needed for transmitter or recorder.

**Power Pack**

This is conventional enough, using a full-wave indirectly heated rectifier and condenser-input smoothing filter.

The amplifier requires approximately 100 milliamps at 300 volts, which is easily handled by a 5Z4. Like all the other tubes listed in the specification the 5Z4 is small and may be mounted in any position that is convenient, vertically or horizontally; ventilation must, of course, be adequate.

The H.T. positive line is 300 volts, and it must not be any greater than 320 volts. If you wish to use a 350-0-350 mains transformer then you must insert a dropping resistor in series with the choke L to bring down the potential to the correct figure. With a 350-0-350 volts transformer L may be replaced directly by a speaker field of 1,000-1,250 ohms.

Output Connector

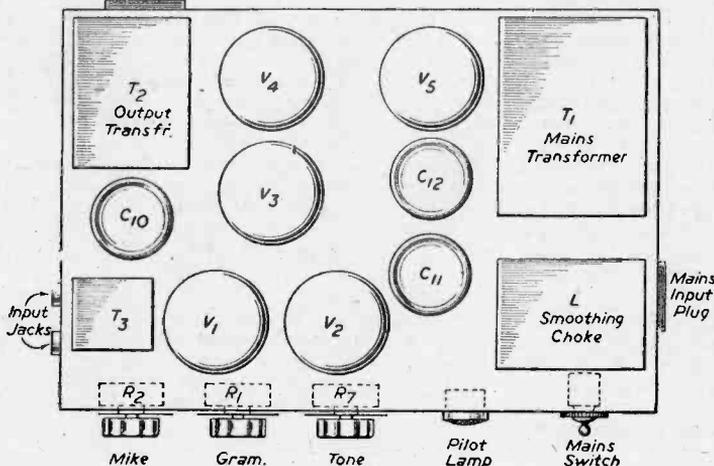


Fig. 2.—Typical component layout. Plan view, looking down on chassis.

halves of the primary of the output transformer to act as a corrective filter. The output transformer must be capable of carrying 50 milliamps in the primary windings and of handling the full 15 watts of output without saturation. The anode-to-anode load is 8,000 ohms, and this needs to be matched

principles of layout should be observed, such as keeping all wiring as short as possible, twisting the heater leads together and screening the input leads to the grids of V1. A 12in. x 8in. x 2½in. chassis should be more than adequate. As regards layout, no doubt individual experimenters will use the time-honoured

**Construction**

There are no special precautions to be taken, other than the one mentioned with microphone transformers. The normal prin-

**LIST OF COMPONENTS**

**RESISTORS**

(All are normal ½ watt rating except R19)

- R1, R2—0.5 MΩ potentiometer.
- R3—2kΩ.
- R4, R5, R6—100kΩ.
- R7—0.25 MΩ potentiometer.
- R8, R9—0.75 MΩ.
- R10—1kΩ.
- R11—10kΩ.
- R12, R13—68kΩ.
- R14, R17, R18—47kΩ.
- R15, R16—220kΩ.
- R19—250 ohms, 2 watt, wirewound.

**CAPACITORS**

- C1—50μF, 12 volts working.
- C2—0.05μF, 400 volts working.
- C3, C6, C7—0.1μF, 400 volts working.
- C4, C5—0.01μF, 400 volts working.
- C8, C9—0.02μF, 400 volts working.
- C10, C11, C12—8μF, 450 volts working.

**TRANSFORMERS**

- T1—Primary for mains input. Secondaries, 300-0-300 volts (R.M.S.) at 120 milliamps, 5 volts at 2 amps (rectifier), and 6.3 volts at 3 amps (heaters).

- T2—Output transformer. Primary load, 8,000 ohms, matching to secondaries 15, 7.5 and 3 ohms. Required ratios are 22.5, 32.5 and 52.5 to 1, respectively. Primary winding centre-tapped, to carry 50 mA each half.
- T3—To match microphone to grid. Ratio, 100 : 1 or as required for particular microphones. Mu-metal screened.

**OTHER COMPONENTS**

- L—Smoothing choke. 10-20 henries, to carry 120 milliamps, 500 ohms resistance. Replaceable by suitable speaker—field winding.
- S—Mains toggle switch, D.P.S.T. Also chassis, valveholders, pilot lamp, knobs, dial plates, input and output jacks, wire, flex, sleeving, etc.

**VALVES**

- (Alternatives are listed in order of performance. Service code numbers follow in brackets)
- V1, V2—6SC7 (CV1969), or 6N7 (CV1957), or 6SN7GT (CV1988). Equivalent glass types, normal size, are ECC32 or 6N7G (CV181 or CV1285).
- V3, V4—6V6 (CV510), or 6V6GT (CV511).
- V5—5Z4 (CV1864).

method of shuffling valve holders, etc., about on the surface of the chassis to find a satisfactory layout before drilling a single hole.

### Performance

The average pickup gives plenty of gain, and it may be necessary to attenuate the input from a crystal pickup to prevent crowding of the controls.

On the microphone channel adequate boost is easily obtainable with medium-priced moving-coil microphones, and if the speaking distance is more than a few inches it will be necessary to apply plenty of top-cut to prevent the tendency to feedback when the microphone and speakers are in the same hall or room. Government surplus "hand microphone No. 7" gives plenty of good, clear speech at close talking distances. Throat microphones, which are invaluable for eliminating unwanted noise on P.A. occasions, give good results at reasonable quality.

### Alternative Valves

Alternatives are given in the parts list. Whereas a 6SC7 has a stage gain of the order of 35 times, a 6N7 provides only 24 times and a 6SN7-GT has a voltage step-up of only 14 times. Obviously, with a high signal input two 6SN7-GT valves would give satisfactory results, but low input levels will need 6SC7 valves as V1 and V2 if the output stage is to be fully loaded.

The 6V6 and 6V6-GT have identical performances, and only differ in appearance and size.

The preferred valves are miniature metal types, so that the amplifier can be made very compact. If the equivalent glass-bulb types are used the

performance will be the same, but more space must be allowed in construction, since the G types are longer and wider.

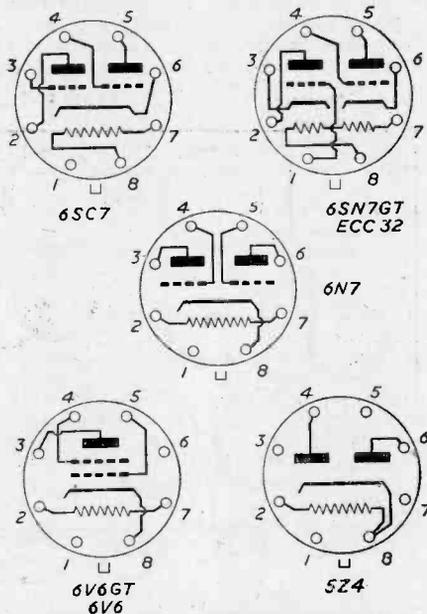


Fig. 3.—Diagrams showing base connections of all valves referred to in the parts list. All have International Octal bases.

# Five-metre Converter

Instructions for Modifying Ex-Service RF Unit Type 26

By I. S. ROBERTSON and W. J. WHEELER

**R**F unit type 26, frequently seen advertised in the columns of this magazine, is ideal for conversion to the 5-metre band. As it stands, however, it is felt that one or two modifications are required.

Due to the noisy character of the local oscillator, and also the tendency towards frequency creep, the oscillator has been completely redesigned. Also, the damping of the mixer anode circuit is no longer required, as the original 4 Mc/s bandwidth is obviously not needed. Provision has also been made for stabilisation of the H.T. supply to the oscillator. All components removed are used in the modified circuit, and the only extra items needed are:

1. Eddystone VHF choke.
2. 10 k $\Omega$  5 w. wire-wound resistor.
3. One voltage stabiliser, type VR 105-30, and
4. International Octal valveholder with fixing pillars.

The voltage stabiliser is of a type easily obtainable from surplus stores. The oscillator is of a design

by Mr. Clapp, of the General Electric Co. of America, and described fully in the May 1948 issue of "QST." One of its advantages is its exceptional stability at high frequencies.

### Dismantling

Fig. 1 shows the unmodified circuit diagram. First, locate R14 beneath the chassis, as shown in Fig. 2, and remove. Retaining the oscillator coil L4 in position, remove all other components from the oscillator compartment, excepting C26 and C27 (shown in Fig. 2). Also disconnect the wire joining end of "pipe" to L4. The trimmer C30 is carefully removed and is then replaced, but without earthing either tag. Do not remove the coaxial cable from the Jones plug or interfere with the heater wiring. With reference to Fig. 3, remove C31 and R13. The remaining connections in the oscillator should now appear as in Fig. 2. The wires joining the fixed vanes of the rear section of the two-gang variable condenser to the lower tag of L4 and to pin 8 of the oscillator valveholder should be removed.

**Rebuilding**

To the oscillator grid pin (pin 2) attach one end of the 100 kΩ resistor (formerly R13), the other end being earthed; also attach to pin 2 one lead of the 100pF. condenser (formerly C28), the other end of the condenser being attached to the upper tag of L4. To the cathode (pin 3) solder one end of the 500pF. condenser (formerly C25), the other end also going to the upper end of L4. One end of C30 is joined to the lower tag of L4, whilst the other tag of C30 is taken through the chassis via the small hole near the base of L4 to the lower tag on the stator of the 2-gang variable condenser. The frame of the condenser is already earthed. The V.H.F. choke is now connected between cathode and earth. A lead from the cathode is now joined to the "pipe," thus providing the injection voltage for the mixer.

On the rear panel above the valves is fixed an International Octal valveholder, mounted on two stand-off insulators, so that the tags are clear of the metal, having previously fixed two wires to pins 2 and 5. The wire on pin 2 is attached to one of the valveholder fixing bolts by means of a suitable tag. Mounted vertically, also on the rear panel, is a paxolin tag-board,

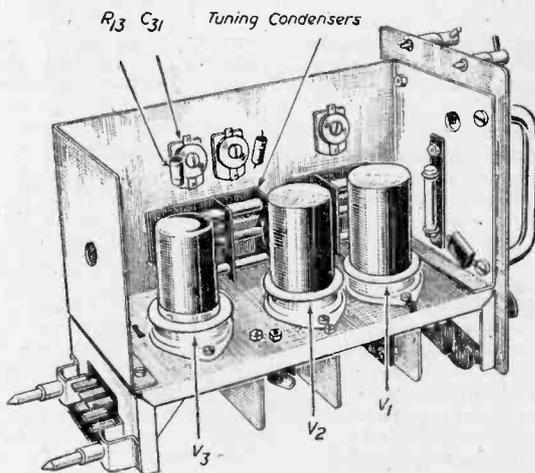


Fig. 3.—Pictorial diagram of the Unit with essential markings. Condenser C31 and resistor R13 are removed. Other modification details are shown in Fig. 2 on the next page.

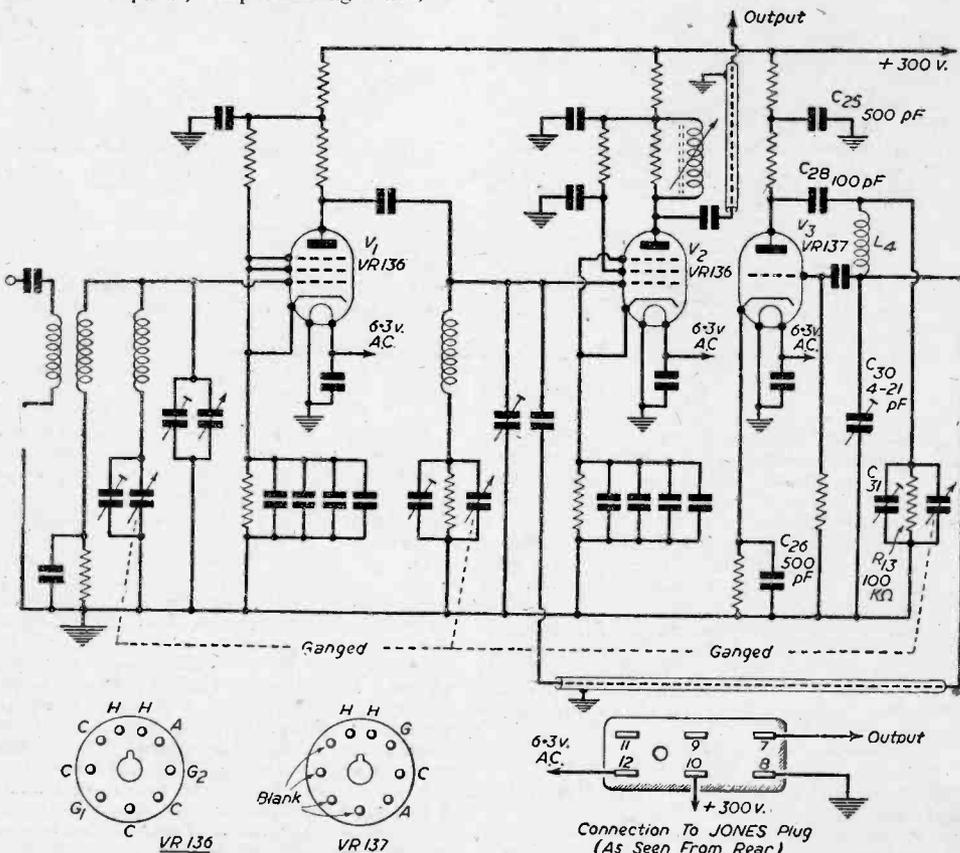


Fig. 1.—Unmodified circuit of the RF Unit Type 26, valve base and Jones plug connections.

similar to the one already fitted behind the front panel (this, incidentally, is used for holding the dropping resistor for the supply to the dial light above the vernier drive). If this light is missing this panel may be utilised, as the required bulbs are not easy to obtain. On this panel is fitted the  $10k\Omega$

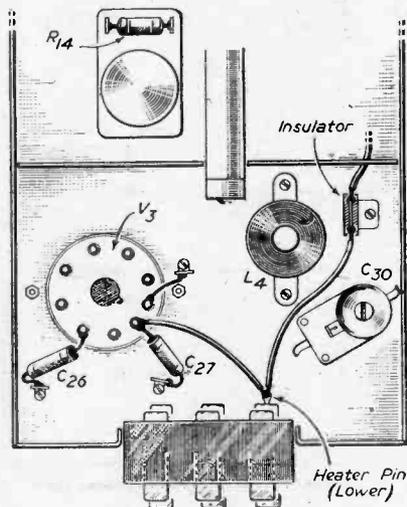


Fig. 2.—How the oscillator connections should finally appear.

5w. resistor, being placed above the chassis in order to prevent over-heating of the Clapp oscillator. To one end of the resistor is attached the lead from pin 5 of the International Octal base. This lead is then joined to the anode (pin 4) of the oscillator valve base. The opposite end of this resistor is joined to pin 10 of the Jones plug.

The local oscillator is now as shown in Fig. 4, thus completing the construction.

#### Operation

The next step is to get the converter lined up. H.T. and L.T. are connected via the Jones plug, and the output is fed to the aerial socket of a normal

short-wave receiver tuned to 7.5 Mc/s, and at maximum gain provided that stability is maintained. The aerial is connected to the plug on the front of the converter and the aerial trimmer is

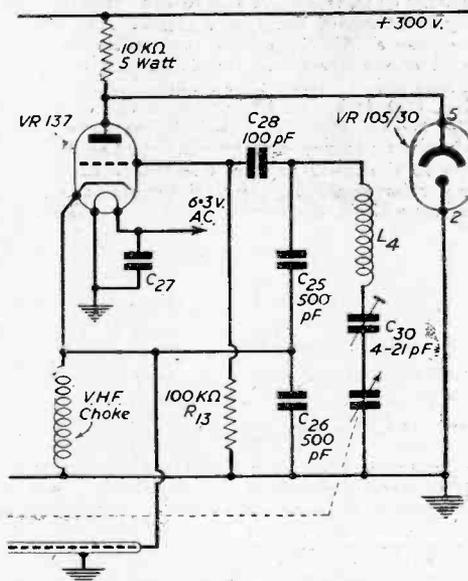


Fig. 4.—The redesigned oscillator circuit.

set for maximum noise. The main tuning dial is set to 170 and the oscillator trimmer C30 is also adjusted for maximum noise. The other trimmers beneath the chassis are then also adjusted to increase the noise.

The main dial is next set to 20 and the aerial trimmer readjusted. To increase the noise the two trimmers above the chassis are adjusted. This latter adjustment will slightly upset the previous adjustment at 170, which is therefore repeated as previously.

The converter is now ready for operation. The 5-metre band should appear between 30 and 50 on the dial.

## British Radio Telephones For Netherlands

ANOTHER triumph for British radio technique abroad has been achieved by one of the leading British radio manufacturing firms, who have obtained and are carrying out a £10,000 order for VHF mobile radio telephone equipment for the Netherlands Government.

The firm concerned is Pye Telecommunications, of Cambridge, who have done much of the pioneer work in this country on the type of radio telephone apparatus now so widely used by police, ambulance and fire services, as well as many industrial organisations.


#### Police Radio

Already a considerable part of the contract has been fulfilled, and the familiar whip aerial, such as

is seen on police and other vehicles equipped with mobile 2-way VHF radio telephones, is to be observed in the streets of Amsterdam, where, in the two cities, some sixty vehicles are already using their British radio telephone sets. These are in communication with a number of official fixed base stations.

Reports from the Netherlands already indicate the success of these first radio phone installations, and it is stated that they are giving extremely satisfactory service. What adds particular interest to the contract, however, is that it was obtained by the British company in face of keen competition both from the Dutch home market and from the United States of America.

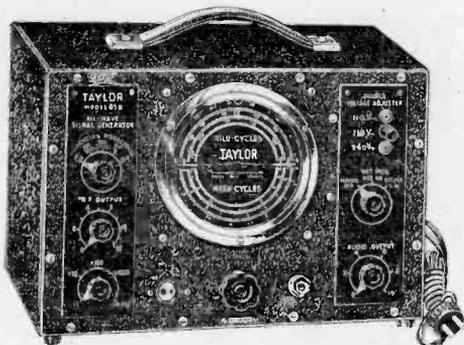**MINISTRY APPEALS TO HOUSEWIVES**  
Keep Waste Paper separate, dry and clean  
for salvage.



## THIS NEW SIGNAL GENERATOR COVERS 100 Kc/s TO 160 Mc/s

### MODEL 65c

The latest addition to the Taylor range, specially designed to cover all Television frequencies. Mains operated, compact and reliable with an accuracy of better than 2% on all ranges. **LIST PRICE £17.15.0** or on H.P. TERMS

- 7 ranges, 6 covering 100 Kc/s to 80 Mc/s on fundamentals, and the 7th 46 Mc/s to 160 Mc/s on 2nd harmonic.
- Scales directly calibrated in Kc/s and Mc/s.
- Internal or external modulation.
- Coarse and fine R.F. attenuation.
- 400 c/s Audio signal output.

TAYLOR PRODUCTS INCLUDE: MULTIRANGE A.C. D.C. TEST METERS • SIGNAL GENERATORS • VALVE TESTERS • A.C. BRIDGES • CIRCUIT ANALYSERS • CATHODE RAY OSCILLOGRAPHS • HIGH AND LOW RANGE OHMMETERS • OUTPUT METERS • INSULATION TESTERS • MOVING COIL INSTRUMENTS

**TAYLOR ELECTRICAL INSTRUMENTS LTD**  
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND



Telephone: SLOUGH 21384 (4 lines)  
Grams & Cables: 'TAYLINS' SLOUGH



## FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

Write to the I.C.S. Advisory Dept., stating your requirements. It places you under no obligation

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94, International Buildings, Kingsway, London W.C.2

Please send me your free booklet describing I.C.S. instruction in the subject marked X.

Complete Radio Engineering	Elementary Electronics
Radio Service Engineers	Elementary Radar
Radio Service and Sales	Advanced Short-wave
Elementary Radio	Radio

If you wish to pass a Radio examination, indicate it below  
British Institute of Radio Engineers  
P.M.G. Certificate for Wireless Operators  
City and Guilds Telecommunications  
R.A.F. Wireless Operator and Mechanic

Examination students are coached until successful

Name ..... AGE .....

(USE BLOCK LETTERS)

Address .....



## Special Offer of MAINS TRANSFORMERS !!

All 200/230/250 volts 50 c.p.s. with screened primaries. Type "A" — Half-shroud drop-through. "B" — Upright un-shrouded.

MT/E. 350-0-350v. 100 m.a. A or B. 4v. 3a., 4v. 5a. C.T. 37/6.  
MT/A. 350-0-350v. 100 m.a. A or B. 5v. 3a., 6.3v. 4a. C.T. 37/6.  
MT/EA. 350-0-350v. 100 m.a. A or B. 4v. 3a., 6.3v. 4a. C.T. 37/6.  
MT/1. 250-0-250v. 100 m.a. A or B. 4v. 3a., 4v. 5a. C.T. 37/6.  
MT/2. 300-0-300v. 100 m.a. A or B. 4v. 3a., 4v. 5a. C.T. 37/6.  
MT/3. 325-0-325v. 100 m.a. A or B. 5v. 2a., 6.3v. 3a. C.T. 37/6.

We are still able to offer the **MT/M. MIDGET MAINS TRANSFORMER**. Compact—Efficient—Versatile in Application. Upright Mounting. Dimensions, 3in. high x 2 1/2in. x 3 1/2in.

Primary : 200/230/250 volts. 50-100 c.p.s. (screened).  
Secondary : 250-0-250 volts, 50 m.a.

tapped 5 volts 2 amps. } Rectifier.  
4 volts 2 amps. }  
6.3 volts 1.5 amps. 24/- post free.

**24 VOLT DIMMER SWITCH BOX.** Comprising one 200 ohm + 200 ohm wire wound potentiometer, one 400 ohm potentiometer, with switch (isolating slider from track), one SPDT bakelite toggle switch and two connector sockets. Mounted on bakelite base. Size 6in. x 4in. Nev. 2/6 post free.

**DOUGLAS MIDGET COIL PACK.** Medium and Long Waves. Oscillator Coil mounted on wavechange switch with separate aerial coil. I.F. 465 kc/s. Complete, with all trimmers, padders and circuit. Boxed. 23/6 post free.

**METERS.** Taylor Junior 120A. £8/8-; D.C. Avomitor. £4/4-; Universal Avomitor. £8/10/-; Pflco Radiometer. 25/- plus 9d. (minimum) post and packing.

**SPEEDY POSTAL SERVICE C.W.O. or C.O.D.**

When sending C.W.O. please include sufficient extra for post and packing.

**VALLANCE & DAVISON, LTD.,**  
P.W. Dept.,  
144, Briggate, Leeds 1. Phone 29428/9  
Staff call signs :-G2HHV, G3ABD.

# EVERY MAN HAS HIS OPPORTUNITY

—this is yours!

Qualify for that key position quickly! The foremost and most famous of all Correspondence Colleges will give you the friendly personal training you must have to take you to the top. Let us advise you. Take the first step to an assured future and send for free particulars NOW.

## BUILD UP A CAREER—VIA THE BENNETT COLLEGE

Blue Prints.  
Book-keeping.  
Building.  
Cambridge Senior School Certificate.  
Carpentry and Joinery.  
Civil Engineering.  
All Commercial subjects.  
Television.  
Shorthand (Pitman's).  
Telecommunications. (City and Guilds).

Draughtsmanship, all Branches.  
Heating and Ventilating.  
Radio Service Engineering.  
Mathematics.  
Matriculation.  
Plastics.  
Wireless Telegraphy and Telephony.  
Structural Engineering.  
Quantity Surveying.  
Teachers of Handicrafts.

If you do not see your own requirements above, write to us on any subject. Full particulars free.

Direct Mail to Dept. 104

The **Bennett College**  
SHEFFIELD (LTD)

# COVENTRY RADIO

Component specialists since 1925

## STOCKTAKING CLEARANCE SALE

Send now for FREE LIST of special offers, components below cost prices, cannot be repeated when stock is cleared. You can save pounds. Send name and address only on 1d. postcard. 1949 full component Catalogue available, 6d. post paid.

DUNSTABLE RD., LUTON, BEDS.

## ALLEN AND GOULD

The following goods are new and guaranteed.  
**NEW BOXED VALVES.**—7193, 3/6; EF36, 7/6; 6Q7G, 8/-; 6K7G, 8/6; 5Z4, 8/6; 638C, 4/9.  
**TELEVISION VALVES.**—6SH7, high slope amplifier for use in sound and vision receivers, time base circuits, and also as high gain audio amplifier, 4/6. 6H6, double diode as detector, noise limiter, etc., 2/6. EF50, 6/6; EA50, 3/6; T41, 12/10; pen 45, 12/10; pen 46, 18/3; U8, 18/3.  
**TELEVISION BOOKS.**—A Modern Home-built Televisor, 2/6. Television Constructor's Manual, 3/6.  
Miniature tubular condensers, .1 mf. 150 volt, .01 mf. 250 volt, 2/6 doz. or 24/- gross.  
Electrolytic condensers, 32+16 mf. 350 volt, 4/-; 45/- doz.  
Moving coil microphone, 3/6. Moving coil headphones and mike, 6/6. Mike transformer, 1/9. 60 mva choke, 5/-. 485 k/c pre-tuned I.F. filters, 1/3; 12/- doz. 8,000 ohm wire wound pots, 1/-; 10/- doz. P.M. SPEAKERS.—6in., 13/11; 8in., 14/11; 10in., 22/6. Please include postage.

ALLEN AND GOULD

5, OBELISK PARADE, LEWISHAM, S.E.13  
Opposite Gaumont Cinema. Telephone: Lee Green 4038.

# MATT Special Offers ALL NEW AND GUARANTEED

**TRUVOX P.M. SPEAKERS.** 8in. w/Trans., 18/6; 8in. less Trans., 14/6; 5in. L/Trans., 12/6; Trans. to match, 3/3 each.  
**LINE CORD,** 2-way, 1/6 per yd., 3-way, 2/- per yd., 60 ohms per ft.

**TUNING CONDENSERS,** Midg., .0005 w/Trims and S/motion drive, 11/- each.

**TUNING CONDENSERS,** Ultra Midg., .0005, 2-gang, 10/6 each.

**VOL. CONTROLS CENTRALAB.**—All values w/s., 4/9 each; L/s., 3/6 each.

**CONDENSERS, CANNED TYPES,** 8 mfd. 450 v., 3/- each; 16 mfd. 350 v., 2/9 each; 25 mfd. 25 v., 1/9 each; 16 mfd. (T.C.C.), 7/9 each; 32 mfd. 275 v., 3/9 each; 16+8, etc., etc.

**MULTI RATIO TRANS.,** 12 ratio, 7/6 each.

**MAINS TRANS.,** 6 v. and 4 v., 26/6 each (Shrouded).

**VIBRATORS,** Mallory, 4-pin, 6 v., 4/11 each.

**HEADPHONES,** ex-Govt., W/Jack Plug, 3/11 per pair.

**WEARTE "P" COILS,** all types, 3/- each.

**RESISTANCES, "ERIE,"** Types 1 w., 4d. each; 1 w., 8d. each.

**SILVER MICA CONDENSERS,** all values, 12/- per gross, assorted.

**PICK-UPS,** B.T.H. Magnetic type, 40/- each. "DE LUXE" Rothermal Crystal, 65/- each, including purchase tax.

**COLLARO, A.C. Gram. Motors,** w/pick-up complete, £5 13s. 4d. each.

**COLLARO, A.C./D.C. Gram Motors,** w/turn-table, only £9 3s. 6d. each.

**PLESSEY A.C. Gram. Motors,** auto changers complete, £18 7s. 6d. each.

All Orders under £1 postage extra.

Let us have all your Radio requirements.

Largest Stock of B.V.A. and American Valves in Surrey.

# MATT RADIO SERVICE KINGSTON 8353

29 Castle St., Kingston-on-Thames, Surrey.

## M. & J. PEARSON

373, EGLINTON STREET, GLASGOW, C.5

Special Bankrupt Stocks, Ex-Govt. offers, Allander, Mahogany Console type, 5 valve, 3 Wave-band, A.C. Superbet Radio with Osram 8.3 volt valves and 10in. P.M. Speaker. Original Cost £38, our price for limited quantity only, £19 each, inc. Tax. New and in original wrappings.

Speakers: 6in. Plessey P.M. type, 12/6 ea.

8in. ditto 14/6 ea., boxed.

Valves: EF50, VU120, VU111, all at 5/- each. 1LA6, 1LN5, 1LD5 and 3D6, all at 6/6 each. Y63, 7/6 each.

Condensers: Midget Two-Gang, .0005, 6/6 each.

Standard size ditto 5/6 each.

32 mfd. 350 Volt Electrolytics, large size, 3/- each. 50 mfd. 25 Volt, 7/6 doz. .001 and .01 Sprague, 6/- doz. 1,000 Volt, 5/- doz. 1 mfd. 350 Volt Tubular, 5/- doz. 2,000 mfd. 12 Volt, 2/6 ea.

.001 and .01 mica, 5/- doz. Special Clearance offer of 230/250 Volt A.C. Gram Motors; internal rim drive type with motor board and turntable, only £2/15/- ea. incl. Tax. Ferranti 0-500 microammeters, 2/11. Flush Mounting Type. Boxed, 16/6 each. Terms: We pay all carriage. Gt. Britain only, and cash with order, please. No lists supplied.

## H.A.C.

### Short-Wave Equipment

Noted for over 15 years for

Short-Wave Receivers and Kits of quality

One Valve Kit, Model "C" .. Price 20/-  
Two " " " " "E" .. " 43/-

These kits are complete with all components, accessories, and full instructions.

Before ordering send stamped, addressed envelope for descriptive catalogue.

Note new sole address:—

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH) 66 New Bond Street, London, W.1

# A Personal Portable

A Midget 3-valve Receiver Using 1.4 Volt Valves and a 2in. Loudspeaker

By PHILIP H. BEARMAN

**T**HIS easily constructed radio was designed to give maximum results with a minimum of expenditure, running costs have also been kept in view by the use of low consumption valves and also an unorthodox output valve which proves very satisfactory. The actual size of the completed receiver is 4½in. x 4½in. x 2½in.

It is recommended that the case be built at the same time as the set as no chassis is employed and components are fixed directly to the case. Firstly, the base should be constructed of seven-ply wood, and then the front to the specification given. Any cloth or speaker fret may be employed for the grille. The frame aerial is semi-pile wound around four small nails insulated with sleeving. The front of the receiver may then be nailed to the base and the loudspeaker and output transformer fitted in their respective positions.

### Controls

The side containing the controls should then be fitted and fixed to the base board. The tuning condensers, which may be purchased from Premier Radio, should have the spindle and screw thread cut down to a minimum to reduce the projection. When this has been completed, the wiring may be commenced. The author did not use a push-pull type switch as specified but a narrow two-way type which was stripped from an ex-Government unit. A small piece of ebonite or wood should then be cut to contain the two Hivac valveholders, and this should be arranged so that it may be tilted away from the set in order that the valves may be inserted; a similar arrangement is recommended for the output valve.

After completion of the wiring, the remainder of the woodwork can be completed and various types of attachment may be used to secure the back of the receiver. The author's set is con-

structed from three-ply with the exception of the base, which is of seven-ply; it may then be stained, although to give a professional finish, rexine or American cloth may be used; the addition of a handle would no doubt be beneficial and a leather

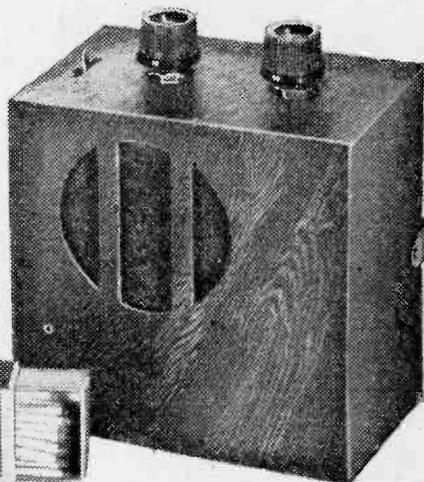


Fig. 1.—The finished receiver, photographed with a matchbox to give an idea of its size.

strap would doubtless be extremely useful in this respect. The set operates in a similar way to any receiver employing a reacting detector and no difficulty should be experienced here. If the frame aerial is connected as per diagram one is certain of obtaining reaction, otherwise it may be very difficult to reverse one of the windings after the completion of the set. In the author's set, there

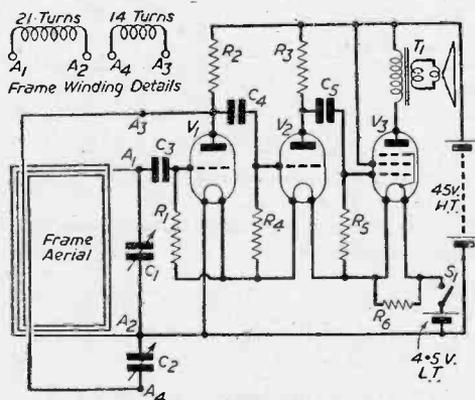


Fig. 2.—Theoretical circuit of the Portable.

### LIST OF COMPONENTS

- V1, V2 Hivac type XH.
- V3 Type 1T4.
- T1 90 : 1 Midget o/trans.
- C1, C2 .0005µF v/mica condensers.
- C3 .0001µF.
- C4, C5 .01µF., 150 v. working.
- R1 2MΩ.
- R2 100kΩ.
- R3 150kΩ.
- R4, R5 1MΩ.
- R6 80Ω.
- S1 Push-pull switch (see text).
- 45 v. Siemax H.T.
- 4.5 v. flashlight battery.
- 2½ in. Celestion L.S.
- Two Hivac valveholders.
- One button base valveholder.
- Two midget knobs.
- Miscellaneous wire, sleeving, wood, etc.

was a slight tendency to microphony due to a defective valve, and this was easily cured with cotton wool as will be seen from the photograph.

It may be found necessary to use some bias on

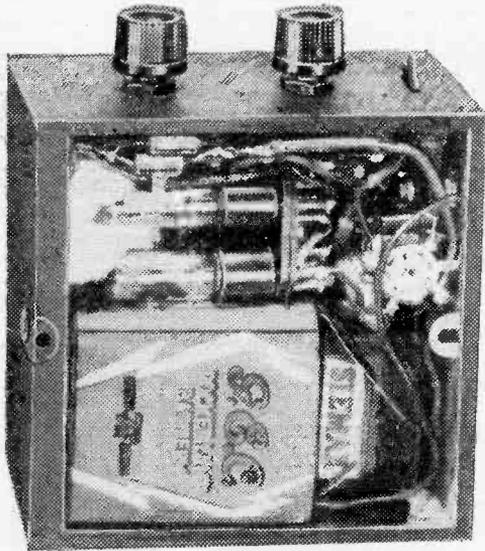


Fig. 3.—An interior view of the receiver showing the batteries.

the output valve and this may be obtained by running a potentiometer from the filament of the output valve to the earth to obtain the desired voltage.

## Radio Aids

THE Automobile Association recently announced a new scheme whereby radio-controlled vans with modern equipment for roadside repairs are directed to the immediate assistance of motorists whose cars break down at night anywhere within the London Postal Area. The only cases which the scheme excludes are breakdowns caused by accidents and those which occur when the car is at the owner's home or at a garage. The committee of the Association has agreed to extend this service not only to all A.A. members but also to any unaccompanied woman driver who experiences mechanical trouble with her car between 6 p.m. and 6 a.m.

Throughout the night each breakdown team will be in continuous contact by radio telephone with the A.A. Headquarters at Fanum House, and it will thus be possible to locate and assist any motorist who is in difficulties and who telephones for help, with little or no delay.

This new London night service—believed to be the first of its kind in operation—is an extension of the A.A. Breakdown Scheme whereby members may have emergency repairs carried out by garages in any part of the country, the charges within certain limits being defrayed by the Association. It has been introduced owing to the inability of motorists to obtain mechanical first aid from garages in many parts of London after normal

The author's set is very satisfactory and has proved an invaluable lightweight, weighing, as it does, only two pounds.

### The Frame Aerial

The aerial in the original model was wound with 34 s.w.g. enamelled wire. Double-cotton or silk-

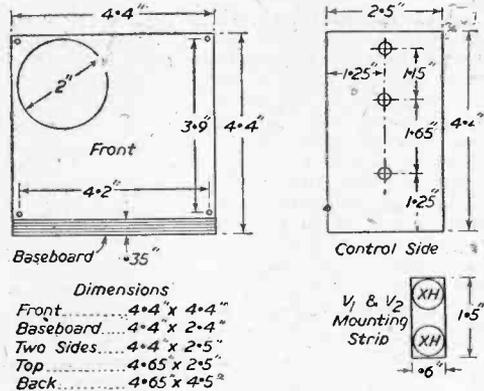


Fig. 4.—Details of cabinet construction.

covered wire could, of course, be used if desired. In cases where insufficient volume is obtained, an external (outside) aerial could be coupled to the receiver by winding a few turns of wire round the outside of the case and connecting one end to the aerial and the other end to a nearby earth. This will, of course, give a considerable reduction in selectivity, and in some areas it may be found impossible then to separate the local transmitters.

working hours, particularly at week-ends. It is emphasised that in providing this emergency assistance the Association is in no way competing with the motor trade, which often finds it uneconomical in certain districts to keep mechanics on duty throughout the night.

At present the A.A. Night Breakdown Service will apply only to the London area, but its extension to the big provincial cities will be considered should there be evidence of a sufficient demand for it.

### Electric Ear to Defeat Burglars

AN interesting device produced by The General Electric Co., Ltd., is believed to provide an excellent solution to the problem of protecting warehouses, shops, stores and houses, etc., against burglars, without exposing the watchman to any risk of attack or causing the burglars' suspicions to be aroused.


In each of the areas likely to be broken into a special type of microphone is installed. They are wired to an amplifier and loudspeaker in the watchman's post. Should an unusual sound be heard, the watchman operates a simple switch arrangement and listens-in to each area in turn, an illuminated panel showing quite clearly the locality.

Once he is satisfied that there are suspicious sounds, he can telephone for the police without leaving his post.

# Practical Hints
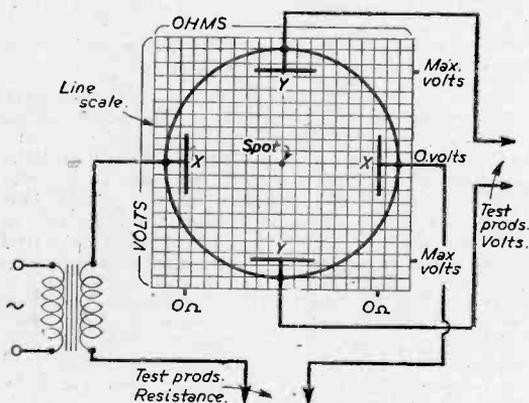
## C.R. Tube Meter

**T**HIS device consists simply of a small C.R. tube working from a conventional power supply. To measure resistance, any pair of deflector plates are connected to the secondary of a low-voltage mains transformer, the circuit being broken by a pair of test prods. The effect of shorting the prods is to cause the spot to trace a line on the screen, and minimum resistance is indicated by maximum line-length. It is a simple matter to place over the tube screen a line scale and to calibrate in ohms from known resistors. Various ranges can be used by putting a multi-way switch in the circuit, which switches in resistors, the values of which are found by experiment.



Using a C.R. tube as a testmeter.

To measure volts the remaining pair of plates are connected to test prods, and calibration carried out from known sources of potential. Maximum volts are indicated by maximum line length. Also, a great variety of ranges are available by placing a multi-way resistance switch in the circuit. A.C. volts are shown as a line length, D.C. is indicated by spot movement, the direction of which depends on the plate potential.

A word about the resistance values for the range switch. Ohm's Law does not apply, since only a potential is required on the plates to deflect the beam.—A. E. BOOTH (Coventry).

## Line Cord Replacement

**M**ANY American midgets are fitted with a ballast tube such as a 185.R8, etc., to bring the line voltage to 117 for American mains supply, and for British mains working a line cord is, usually fitted. The drawbacks of the line cord are too widely known to need comment here. Therefore, when recently I had the common

### THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay half-a-guinea for every hint published on this page. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notice sent in must be original. Mark envelopes "Practical Hints."

### SPECIAL NOTICE


All hints must be accompanied by the coupon cut from page iii of cover.

problem of a broken line cord, I used this method of dispensing with the line cord in a neat, unobtrusive manner.

The ballast tube (185.R8 with U.X. base) was removed and an old valve-base rescued from the "junk box." The total resistance required to replace the line cord and the ballast tube was calculated to be 425 Ω at 40 watts (for 200 v. working). The next step was to obtain a wire-wound vitreous resistor of this rating. This problem was solved by the purchase of two ex-W.D.

resistors of 850 Ω, 20 watts, at sixpence each, from a "surplus" store. (These are obtainable at many such shops.) These were connected in parallel and mounted as shown on the valve-base, being secured by stiff lead wires to appropriate pins after the metal end clips were removed from the resistors. Next, the "junk box" supplied an aluminium can which was a press fit over the valve-base. A ¼ in. hole was made in the top and several ¼ in. holes drilled in the

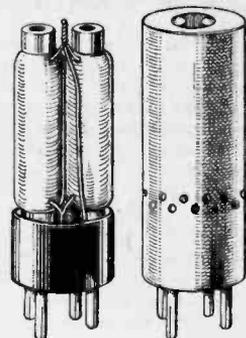A line cord may be replaced by fixed resistors as shown in this hint by Mr. Watson.



sides just above the valve-base to assist in cooling by causing convection currents of air to flow through the can from bottom to top.

Now, with the case fitted and the lower edge turned under (making sure not to short the pins), the finished article is rigid, efficient and has quite a commercial appearance. Plug in, in place of the ballast tube; use ordinary flex to connect the set to the mains and the set is ready for use. Total cost, one shilling, and you have the ballast tube left over for some other purpose.—F. H. J. WATSON (Plumstead).

## NEWNES TELEVISION MANUAL (7th Edition)

Price 7/6, or 8/- by post.

From GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, London, W.C.2.

# Building a Telev

The Sound Unit is the Su

By S. A

**T**HE theoretical circuit diagram of the sound receiver is shown in Fig. 1. It consists of a five-valve chassis, wired as a superhet, and comprises R.F. amplifier, frequency-changer, I.F. amplifier, second detector, A.V.C. and first audio-amplifier, and output pentode. The circuit itself is quite conventional, but it might be worth while to discuss briefly the function of each stage.

V17 is a pentode type SP61 (VR 65) working as a wide-band R.F. amplifier. Its input is derived from the vision chassis described in Part I of this series, and the first valve stage of the latter chassis is common to both vision and sound signals. The sound signal is taken from the second coil on the vision receiver by a single turn coupling loop and fed through a short length (1ft. to 2ft. or less as convenient) of coaxial cable to L1 of the sound receiver, where it is correctly matched by being tapped one turn up from the earthy end of the coil. The anode load of V17 is R2, a resistance of 7,500  $\Omega$ , which permits an appreciable gain to be obtained from the stage while retaining adequate bandwidth to do justice to the quality of the television sound signal. R3 and R4 in conjunction with C1 and C2 decouple the stage from the rest of the receiver.

V18 is the frequency-changer (ECH35) and is very similarly wired to the equivalent stage in the vision receiver. A.V.C. is applied to the control grid through R5, and C5 serves to prevent it being shorted through L2 to earth. The oscillator section is a Hartley circuit with V1 as trimmer-tuner, L0, the oscillator coil, being a Wearite type PA 4 with the coupling winding stripped off exactly as was described for the vision frequency-changer. C13 is included to make up the tuning capacity and so make the adjustment of V1 less critical. The remainder of this part of the circuit is perfectly conventional and no more need be said about it.

In the choice of intermediate frequency there are conflicting factors to consider. From the point of view of high gain a low I.F. is indicated, but the difficulty here is one of oscillator drift. If an I.F. such as 465 kc/s is chosen, then the oscillator and signal circuits are only separated by this small frequency difference, and a drift in the oscillator (which must be working at about 41 Mc/s, sound being radiated on 41.5 Mc/s) of only a few hundred kc/s will completely throw out the I.F. tuning. At the same time there is little object in having an I.F. of 13 Mc/s or more as was the case in the vision receiver. There, a bandwidth of at least 2.5 Mc/s was aimed at; in the sound receiver a bandwidth of 20 to 50 kc/s is perfectly adequate. On these accounts the writer decided on an I.F. of somewhere between 2 and 4 Mc/s, and in practice a frequency of 3 Mc/s was found very suitable.

The I.F. transformers are hand wound

and are perfectly simple to make. Details are given later. For the present L3 and L4 form the first I.F. transformer, tightly coupled in the anode circuit of V18, tuned by iron plungers and fixed condensers C10 and C11. The tuning is quite flat and there is no difficulty in setting up the I.F. coils during alignment, complete details of which are to be given in a later section of this series.

V19 is the I.F. amplifier EF39 (VR53) and is quite conventional. Its output is tuned by the second I.F. transformer L5-L6, and passed on to the detector, one diode of V20, which is valve type EBC33 (VR55). R13, C19 and C20 form an I.F. filter, and R14 is the diode load across which the rectified signal appears. This is applied via C21 and the volume control VR1 to the grid of V20, where A.F. amplification takes place. A.V.C. voltage is derived from the detector anode through C22, rectified by the second diode, and so applied

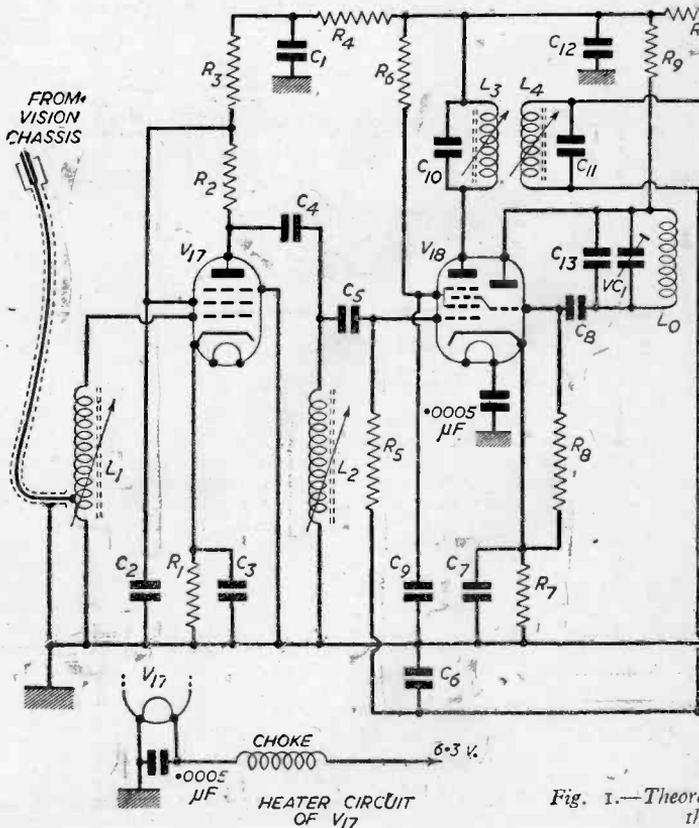


Fig. 1.—Theoretical

# ion Receiver—3


of This Month's Article,  
IGHT

to V18 and V19 through the filter R18 and C25. Note that C6 and C25 are actually in parallel; C6, however, is wired close to the mixer end of the A.V.C. line to give decoupling at this point, C25 providing decoupling at the detector end. Note also that V19 and V20 have a common bias resistance R15, and this is decoupled by a midget 0.5  $\mu$ F. condenser.

After V20 there is a tone control VR2, and the output valve is an EL33 conventionally wired. The output transformer should suit the valve, and its primary is shunted by C27. A 6F6 may be used as output valve provided R21 is increased to 400  $\Omega$ . No other change is necessary.
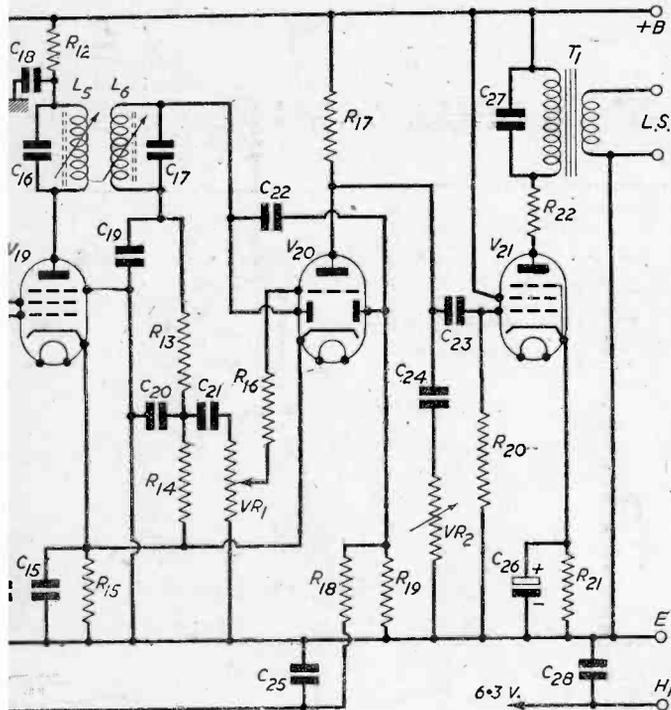
### Construction Details

The photograph on the cover shows the general upper chassis layout and this arrangement should be followed as closely as possible. Fig. 2 shows



circuit diagram of the sound receiver. It is a 5-valve superhet, and  $f_s$  is 3 Mc/s. Coil details will be found on page 153.

the under-chassis layout, and this too should be closely followed, particularly in those parts associated with V17 and V18.

Aluminium is a suitable chassis material, and the size is 12in. by 6in. by 2in, although slight variations are permissible. Two aluminium screens divide V17 and V18 from each other and the rest of the circuit, and R4 and R11 pass through these screens as shown. This kind of construction is essential if stability is to be maintained. Notice also the heater choke in the heater feed to V17. This consists of 12 turns of 22 s.w.g. enamelled wire wound on a pencil shaft and then slightly expanded to become self-supporting.

There should be no difficulty whatsoever in wiring up the chassis, for it is much easier than the vision chassis and rather more liberties can be taken with the layout after V18.

The coils and I.F. transformers need some discussion as these are home-made components, and some little care is required in their construction. First, the tuning coils L1 and L2: these are wound on the small formers as used in the vision receiver, and are very similar. L1 consists of seven turns of 34 s.w.g. enam./s.s.c. wire tapped up rather more than one turn from the earthy end. Fig. 3 shows the dimensions to be followed. L2 consists of an untapped coil of six turns wound as shown in Fig. 3, the wire used being as for L1.

Now all coils, including the I.F. transformers, in this receiver are camed as the photograph shows. In the writer's receiver the cans measure 2in. all ways and were obtained from some old ex-Government gear. Any suitable screening cans may be used, though nothing less than 2in. square should be used on account of increased circuit capacity. The height is not so important. The height is not so important. L1 and L2 are bolted down to the chassis, a hole being provided in the latter so that the iron core may be adjusted from below, and the can is then fitted over them. A small tag strip may be used close to the coils so that the grid lead which emerges from the top of the can is firmly anchored within; the free end of the coil which is thin should not be brought out through the can, either above or below the chassis, but heavier leads should be attached to a tag strip conveniently fitted inside the can close to the coil former. In the can with L2 are mounted the following: C4, C5 and R5.

Fig. 4 shows the layout of the I.F. transformers inside their cans. Both are identical. The formers used are the same as those for L1 and L2, two being used in each can. The actual coils are wound, as shown in Fig. 3, four in all being required. With care it is a simple matter to get two perfectly even layers of wire, each layer consisting of 25 turns, on each former, as shown. The ends

should be fixed with a little wax, and the whole coated with a dope such as polystyrene solution and allowed to dry hard for a few hours before fitting to the chassis. (This also applies to L1 and L2.) The coils are then mounted side by side on the chassis, the latter being drilled so that the iron cores may be adjusted from below. The dimensions are given in Fig. 4 and are not critical, though they should be adhered to as closely as possible. Inside each can are mounted the fixed tuning condensers associated

with the coils, i.e., C10, 11, 16, 17. These are silver-mica components of 70 pF. capacity, tolerance  $\pm 2$  per cent. This tolerance is necessary, though in an extreme case where such accuracy could not be obtained 5 per cent. types could be used. A tag strip is used in each I.F. transformer can to provide anchorage for the coil ends and the heavier outgoing leads. The connections to the ends of the coils are immaterial. When the formers are fitted to the chassis, and the downward going leads

## LIST OF COMPONENTS

R1, R16—160 $\Omega$ .	R12—3.3k $\Omega$ .
R2—7.5k $\Omega$ .	R13—22k $\Omega$ .
R3, R11—470 $\Omega$ .	R14—270k $\Omega$ .
R4—1,500 $\Omega$ .	R15—270 $\Omega$ .
R5—200k $\Omega$ .	R17—47k $\Omega$ .
R6—40k $\Omega$ .	R18—470k $\Omega$ .
R7—250 $\Omega$ .	R19—1M $\Omega$ .
R8—68k $\Omega$ .	R20—330k $\Omega$ .
R9—30k $\Omega$ .	R21—200 $\Omega$ .
R10—100k $\Omega$ .	R22—47 $\Omega$ .

Eric Ceramic, etc.

(All resistors  $\frac{1}{2}$  watt type, but  $\frac{1}{4}$  watt could be used if desired for bias and A.F.C. circuits.)

C1, C4—.001 $\mu$ F.
C2, C7, C9, C21, C23, C24—.01 $\mu$ F.
C3, C6, C27—.005 $\mu$ F.
C5, C9, C20—60pF.
C8—30pF.
C10, C11, C16, C17—70pF. ( $\pm 2\%$ ).
C12, C28—.002 $\mu$ F.
C13, C22—20pF.
C14, C18—1 $\mu$ F.
C15—5 $\mu$ F.
C25—.05 $\mu$ F.
C26—25 $\mu$ F Electro.

Two at .0005 $\mu$ F for heater by-pass on V17 and V18, T.C.C., etc.

(Condensers in R.F., Mixer and I.F. stages should preferably be mica or silver-mica.)

VR1 (volume)—.5m $\Omega$ .

VR2 (tone)—.25M $\Omega$ .

Valves—One SP61 (VR65); one ECH35 (VR99A or ARTH2)\*; one EF39 (VR53); one EBC33 (VR55); one EL33 or 6F6.

\* The ARTH2 is a metallised valve, and is preferable to the VR99A, which is clear. This also applies to the vision mixer, where the ARTH2 may be used with advantage.

Valveholders—One Mazda Octal; four International Octal.

Coil Formers with cores (plain or ready wound)—Six (Midco Radio, Wellingborough).

Oscillator coil—Wearite, Type PA 4.

Oscillator tuning—Ceramic air-spaced 25pF. max.

Chassis and dividing screens: 12in. x 6in. x 2in.

Coil cans: Four, minimum 2ins. square.

Output transformer: To suit output valve.

Wire, sleeving, length of coaxial cable, nuts, bolts, solder tags, tag strips, etc.

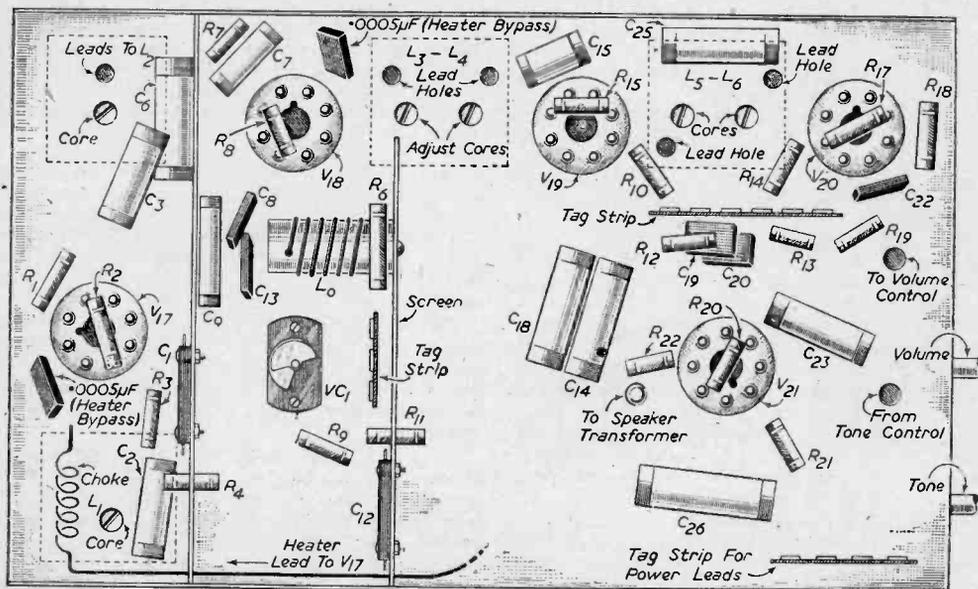


Fig. 2.—Layout for the sound receiver. R11 and R4 pass through the screens, as shown. Above the chassis are VR1, VR2, C21, R16, C24, C27 and the O/P transformer. VR1 must be completely insulated from the chassis.

have been passed through, the screening cans are fitted overall, the grid lead to V19 coming through the top of its can. Check that the can does not short anything to earth before actual wiring begins.

Turning now to the oscillator circuit the layout as shown in Fig. 2 should be closely followed. The trimmer VC1 is a small air-spaced ceramic insulation variable condenser of maximum capacity 25 pF. and it must be completely isolated from the chassis, that is, from the point of view of both fixed

series. The coil should be mounted so as to clear the chassis by at least  $\frac{1}{16}$  in. It does not matter which way round it is wired.

There are few other points of importance. Keep all wiring tidy, make good soldered joints and use good components. The condensers used in the R.F., mixer and I.F. stages should be mica or silver-mica types in preference to rolled paper; all resistances may be rated half-watt, and ceramic types used where passing through screens is necessary.

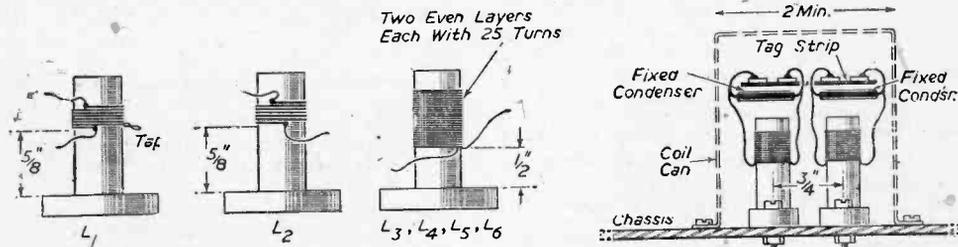


Fig. 3.—Details of the coils used. All are wound with 34 s.w.g. enamelled s.s.c. wire.

and moving vanes. The parallel capacity C13, which is a 20 pF. silver-mica component, is included to make the adjustment of VC1 less critical; the oscillator operates at a lower frequency than the signal circuit, that is, at 41.5–3 Mc/s.—38.5 Mc/s., and so the adjustment is much easier than the corresponding case in the vision receiver where the oscillator frequency is 58 Mc/s. The lower frequency is chosen instead of the higher (which would be  $41.5+3=44.5$  Mc/s) on account of the proximity of the latter to the vision signal on 45 Mc/s. The higher frequency results in the destruction of the picture on the tube due to feedback into the vision channel. The lower frequency overcomes this difficulty and there is no interaction whatever between vision and sound. The coil  $L_6$ , as already stated, is a Wearite PA 4, and the coupling winding is stripped off exactly as was described for the vision oscillator in Part I of this

series. For bias and A.V.C. resistances quarter-watt types are quite adequate. Valveholders are ordinary paxolin or Amphenol types, and wiring is carried out in 22 s.w.g. tinned copper run in insulated sleeving.

Outgoing power leads are taken from the receiver (good quality flex wire), and will later be connected to the power unit as marked. For the present they should be left of a good length, say, 2ft. or 3ft.; use a heavy lead for the heater and common earth return.

#### The Time Base

In last month's issue we described the Time Base Unit. In the circuit diagram on page 111 it will be found that condenser C6 has been omitted. It should be joined between the screen grid of V12 and resistor R20. It should also be noted that resistor R5 should have a value of  $470 \Omega$  and not  $470 k \Omega$  as given in the list of components.

The next article will describe the tube unit.

## Nations Discuss R.F. Allotment

THE continuing growth of international air travel has increased the need for communication between aircraft in flight and ground stations. This, in turn, has produced a serious scarcity of the radio frequencies used in such communication and has made it necessary to redraft the world pattern of frequency allotment.

The draft allotment plan for the international air routes of 51 nations, members of the International Civil Aviation Organisation, was carefully examined by technical experts at the third session of the I.C.A.O. Communications Division which opened in Montreal recently.

The draft plan was originally prepared at a conference of the International Telecommunications Union. The I.T.U., which is the United Nations specialised agency responsible for the allocation of all radio channels, has invited I.C.A.O.'s help in completing a system to enable civil aviation to get the greatest possible service from the available frequencies

The first steps in the allocation programme were taken at New Delhi, India, last November, when an I.C.A.O. regional meeting co-ordinated the frequency requirements for South East Asia. As for European frequencies, a meeting is being held in Montreal concurrently with the Communications Division session.

The results of these meetings will be consolidated for consideration first by the Air Navigation Commission and the Council of I.C.A.O. They will then be transmitted to the International Telecommunications Union before the end of June, 1949.

Only 149 radio channels in the high-frequency bands are available for the exclusive use of civil aviation on a world-wide basis. During daylight hours a number of transmitting stations can operate on the same frequency without interference, providing that they are sufficiently far away from each other. On the other hand, at night, when radio signals travel much farther, stations working on the same frequency are likely to interfere seriously with one another even when they are far apart.

# Occasional 6-volt Quality Three

A Low-priced Receiver for Operation from a Rotary Transformer

By R. V. LUMBARD

**T**HE receiver to be described is intended to meet the need for a "quality" receiver that is essentially "non-mains." Special features include operation from a 6-volt car-type battery; the set being primarily designed for the occasional reception of selected Home programmes.

The circuit theoretical diagram is shown in Fig. 1. To assist in battery economy, a compromise is reached in limiting the number of valves to three. V1 serves the dual purpose of R.F. amplifier and diode detector. A pentode is used as A.F. amplifier; followed by a beam-tetrode in the output stage.

Negative feedback is taken over two stages,

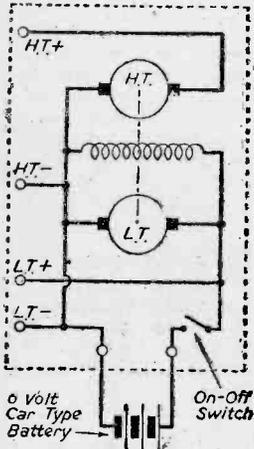


Fig. 2.—Theoretical circuit of a power unit using a rotary transformer rated at 6/200-225 volts at 50mA.

from output transformer secondary to a part of the cathode-bias resistance to V2. Reversal of the two feedback leads at "X" will be necessary if the feedback is found to be positive instead of negative.

The H.T. feed to the anode of V3 is separately smoothed by the choke L3 and 16  $\mu$ F. condenser C15. The remaining H.T. feeds go via the resistor R16, and smoothing is completed by the inclusion of C13. The addition of C7, although in parallel with C13, ensures efficient by-passing of radio-frequencies.

H.T. is supplied by a rotary transformer. Fig. 2 shows the rotary transformer theoretical diagram. The heaters of the three valves are parallel connected for operation on 6 volts. The rotary transformer unit is best kept separate from the receiver; even without power-unit screening, no radio interference should be experienced if both are 3-4ft. apart. It is, in fact, convenient to have the power-unit on the floor near the battery.

An efficient outdoor aerial is advised; also a good earth. This, and the R.F. amplification

available, ensures that sufficient signal input reaches the diode, so minimising distortion in the detector stage.

## Tone Control

Tone control is included to give a substantial amount of "bass-boost." This is provided by the resistance/condenser network R6, R7, R8 and C9; resulting in some 6 db. rise in response approaching 40 c/s. Frequencies above 500 c/s are unaffected by the tone control.

Besides compensating for any general deficiencies in the bass response of the loudspeaker, the "bass-boost" tends to mask any harshness in reproduction due to a rise in speaker response above 1,000c/s. The inclusion of "bass-boost" is considered well worth while in view of the much better balance so obtained.

An infinite baffle arrangement is recommended for the loudspeaker. This greatly assists in the reproduction of the lowest frequencies. It also scores over the popular baffle mounting, since it can be accommodated in less space. A closed cube, with speaker aperture, and made of stout  $\frac{1}{2}$ in. wood is suitable. The size of the cube outside can be 15-18in. square. The inside of the cabinet is lined with thick felt; or covered loosely with cloth and the space between the cloth and the sides of the cabinet filled with sound-absorbent material. Fig. 3 shows this in sectional diagram form. Top and bottom are also lined.

The practical layout of the receiver is best carried out on a steel chassis to the constructor's own requirements. The main essential is to keep

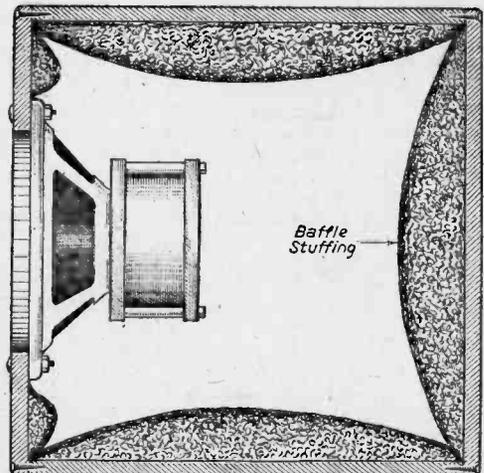


Fig. 3.—Section of infinite baffle speaker arrangement showing essentials.

the tuning coils L1 and L2 separately screened and apart; also seeing there is no undue stray coupling between the anode and grid circuits of V1. Insulation of C2 and T3 must be good to withstand the maximum H.T. voltage; and the presence of H.T. should be remembered when trimming!

**Screening**

The gain of V2 is considerable, and the grid lead will probably require screening. If V2 is close to V3, a metal screen may be necessary between the two valves to avoid instability.

If desired, the coils can be home wound on, say, a lin. paxolin former, using 90-100 turns of 32 s.w.g.

**LIST OF COMPONENTS**

**Condensers :**

- C1, C2, two-gang .0005 $\mu$ F.
- C3, .1  $\mu$ F tubular.
- C4, .0002  $\mu$ F mica.
- C5, .0001  $\mu$ F mica.
- C6, C7, .1  $\mu$ F tubular.
- C8, .02  $\mu$ F mica.
- C9, .005  $\mu$ F mica.
- C10, .1  $\mu$ F tubular.
- C11, 25  $\mu$ F electrolytic.
- C12, .02  $\mu$ F mica.
- C13, C15, C16, 16  $\mu$ F electrolytics.
- C14, 50  $\mu$ F electrolytic.
- T1, 200 pF aerial trimmer.
- T2, T3, 60 pF trimmers.

**Resistors :**

- R1, 50,000 ohms.
- R2, 300 ohms.
- R3, 30,000 ohms.
- R4, .25 megohm.
- R5, .5 megohm volume control.
- R6, 350,000 ohms.
- R7, 150,000 ohms.
- R8, 2 megohm.
- R9, 1 megohm.

- R10, .25 megohm.
- R11, 1,500 ohms.
- R12, 100 ohms.
- R13, .5 megohm.
- R15, 2,500 ohms.
- R14, 250 ohms.
- R16, 2,500 ohms. (1 watt.)

**Coils and Choke :**

- E1, L2, medium-wave coils (as described).
- L3, smoothing choke.
- Output transformer; ratio 50 : 1 (2-3 ohm speaker).

**Valves (Octal) :**

- V1, 6B8-G, D.D. Pentode.
- V2, 6J7-G, Pentode.
- V3, 6V6-G, Output Beam Tetrode.

**Loudspeaker :**

- 10-inch P.M.

**Power-Unit :**

- Rotary-transformer, 6-volt inp./200-225 volt
- 50 mA. out.
- On-off switch, 5-amp.

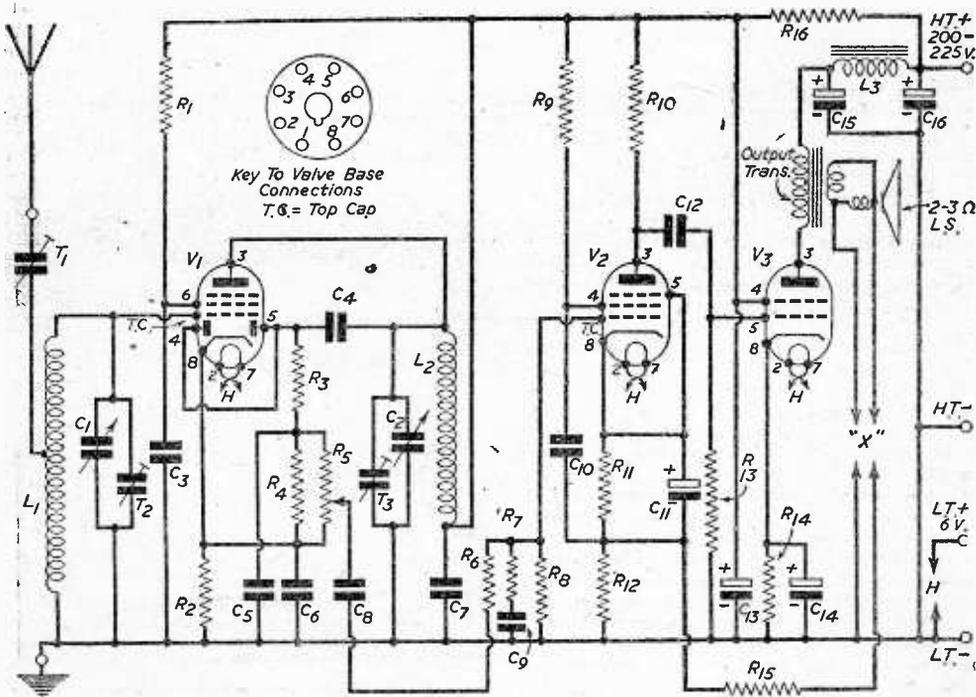


Fig. 1.—Theoretical receiver diagram—less power unit and on/off switch.

enamelled copper wire close wound in a single layer. Both the coils have the same number of turns, although L1 is tapped about 40 turns from the bottom to connect the aerial trimmer T1. Various other tappings can, in fact, be tried in order to match the tuned circuit to the particular aerial used.


An alternative to the two-gang condenser

C1 and C2 and trimmers T2 and T3 is to use switched pre-set condensers for the two nearest local stations. This will also overcome any ganging troubles. Only the medium waves are covered. If standard medium-wave coils are already to hand, the aerial trimmer will be taken to the aerial winding of the R.F. coil instead of to the centre tap. Only the tuned winding of the detector coil will be used.

## News from the Trade
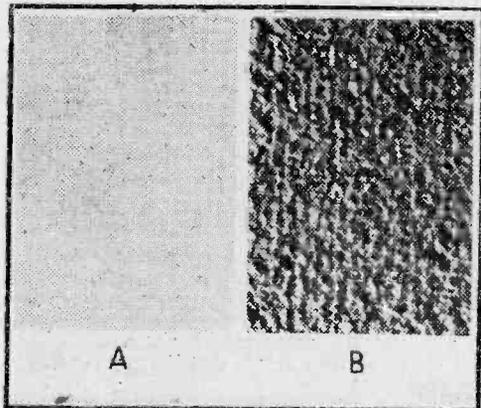
### Plessey Electrolytic Capacitors

THE present trend towards smaller and more efficient electrolytic capacitors has taken a further stride forward in a development by the Plessey Co., Ltd., Ilford, Essex, of a new type to be known as FP or fabricated plate. This is the outcome of the company's development of fabricated



Comparisons of electrode materials. Plain foil is shown at "A" and the new FP at "B."

electrode material, manufactured by applying pure aluminium to a gauze base of chemically inert material, the aluminium being deposited in a manner which leaves the metal pure and entirely free from contamination.

The plates so produced have a considerably greater effective area than either plain or chemically etched foil, this being due to the extremely irregular spongy nature of the surface and to the gauze or net-like structure of the electrode. The cathode iq effect extends through the electrolyte to all surfaces of the gauze structure and results in appreciably reduced sizes of complete units: the capacity of a given area being up to 12 times that of the plain foil type.

Extensive tests have also shown that reliability, shelf and service life, and consistency of product show an improvement over contemporary designs. Leakage current and power factor are also improved, the only limitation being that compared with plain foil, some reduction in ripple current handling capacity has been shown, but the ripple current rating at even higher temperatures

is still ample for the more usual receiver and communications applications.

The capacitors are housed in an aluminium casing which is negative and has a negative solder tag in the base.

The complete range has been covered in five diameters from  $\frac{1}{2}$  in. -  $1\frac{1}{2}$  in. and the length does not exceed 2 in.


### New E.M.I. Radio Unit

E.M.I. recently announced an electrogram—a high-quality record player with twin speakers. To go with this they have now produced a radio unit, illustrated below. It is not, however, limited to use with this equipment.

The output from the unit can be fed into almost any high-quality A.F. amplifier having a suitable input impedance, or alternatively it can be utilised to operate a sensitive high fidelity loudspeaker; when a large output is not the prime consideration.

The aerial is inductively coupled to the high efficiency tuned grid circuits of the R.F. amplifier. All coils are iron-dust core and station selection is effected by switching in suitable trimming condensers in the signal circuits and coils in the oscillator circuit by means of the station push-buttons. Image rejection on long wave is provided. A visual tuning indicator is provided to facilitate setting the push-button controls.

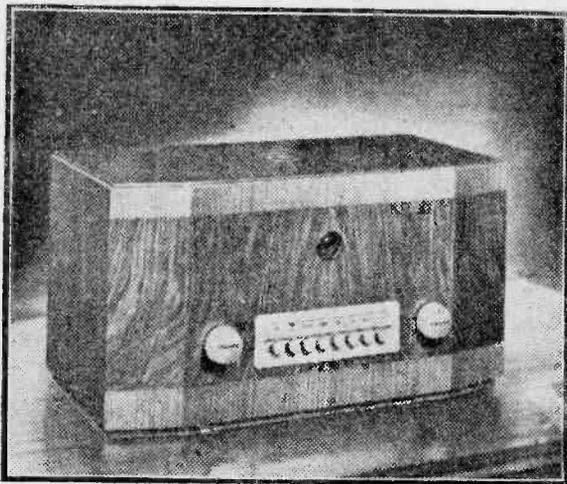The output from the detector is fed, via the volume control, to the A.F. amplifier, which is resistance-capacity coupled to the tetrode output valve. A degree of negative feedback is obtained by a connection from the secondary of the output transformer to the cathode of the A.F. amplifier.



The new E.M.I. radio unit referred to above.

# SPARKS' DATA SHEETS

Provide detailed Instructions with Clear, Full-size Assembly Plans of TESTED AND GUARANTEED DESIGNS.

## HERE IT IS The "CRITERION" A.C. RADIOGRAM

A Design for which discriminating Quality enthusiasts have been waiting. TWO T.R.F. STAGES. INFINITE IMPEDANCE DETECTOR. TONE CORRECTOR STAGE. INDIVIDUAL HIGH & LOW NOTE CONTROLS. VOLTAGE AMPLIFIER. PHASE-SPLITTER. TWO TRIODES. IN-CLASS A PUSH-PULL. MEDIUM & LONG WAVES. P.U. SWITCHING. 87 WATTS OF QUALITY REPRODUCTION. 3 Sheets of Full-size Assembly and Wiring Plans, Plus Descriptive Matter, etc., 5/6.

This is another outstanding example of the Efficiency and Reliability of the Designs produced by

L. ORMOND SPARKS.

### MANY OTHER DESIGNS.

SPARKS' DATA SHEETS cover Portable, Midgets, H/Grams, Amplifiers, etc., etc. for Mains and Battery. Stamp for List. Components Supplied.

"YOU ARE SURE OF A SQUARE DEAL FROM SPARKS"

L. ORMOND SPARKS (P), 9, Phoebeth Road, Brockley, S.E.4

(Phone: Lee Green 0220.)

## HIGHSTONE UTILITIES

Crystal Sets.—Our latest Model is a real radio receiver, fitted with a permanent crystal detector. Why not have a set in your own room—9/6, post 6d. De Luxe Receiver in polished oak cabinet, 13/6, post 1/- Spare Permanent Detectors, 2/- each. When ordered separately, 2/6. With clips and screws, 2/10, post 3d. Headphones, in good order, 4/6 and 5/6, post 6d. (Better quality, 7/6). New Headphones, 10/- a pair. Balanced armature type (very sensitive), 12/6 a pair, both post 6d. New Single Earpieces, 3/6. Bal. armature type, 4/6. ex-R.A.F. earpieces, 2/-, post 4d. All headphones listed are suitable for use with our crystal sets. Hand Microphones, with switch in handle, and lead, 4/- Similar instrument moving coil, 7/6, post 6d. Sparking Plug Neon Testers, with vest pocket clip, 3/3, and 4th gauge, 3/6, post 3d. Soldering Irons. Our streamlined Iron is supplied with two interchangeable bits, one each straight and curved. 200/250 wats, 9/- Standard iron with adjustable bit, 200/250 v., 60 wats, 9/6. Heavy Duty Iron, 150 wats, 12/6. All post 6d. S.R.C. Neon Indicator Lamps, for use on mains, showing "live" side of switches, etc., 3/6, post 4d. Telephone hand generator with handle, 7/6, post 1/6. Bell, 4/6, post 6d. EX-R.A.F. 2-Valve (2-volt) Amplifiers, can be used to make up a deaf aid outfit, intercommunication system, or with crystal set, complete with valves, 20/- post 1/6. Ditto, less valves, 10/- Wooden box to hold amplifier, 2/- extra. Meters, 0-300 m/a, 2in., m/c, 7/6. 3.5 amp., 2in., T.C., 5/-; 4 amp., 2in., thermo coupled in case with switch, 7/6; 30 m/a, 2in., m/c, 6/-; double reading 40/20 m/a, 2in., m/c, 8/-; 20 amp., 2in., m/a, 9/6; 15 volt, 2in., m/c, 9/6; 150 v., 2in., m/c, 10/-; 15 v./600 v., double reading, 2in., m/c, 8/-; 300 v., 2in., m/i, 12/6; 6,000 v., 3in., m/c, 57/6; 3,500 v., 3in., m/c, 20/- Meter movements, 2in., size with magnet (500 micro-amp.) and case, 2/6. Post Extra. Money refunded if not completely satisfied.

HIGHSTONE UTILITIES  
58, New Wanstead, London, E.11.  
Letters only. New Illustrated List sent on request with 1d stamp and s.a.e.

## VALUE FOR YOUR MONEY Monster Bargain COMPONENT KIT

We proudly present the first of a new "Britain" series! Just look at the contents of this parcel! 8 electrolytic condensers as follows: 1 16+24 mfd. 350 v. wkg., 1 8+16 mfd. 450 v. wkg., 1 8 mfd. 450 v. wkg., 1 8 mfd. 175 v. wkg., 2 50 mfd. 12 v. wkg., 2 25 mfd. 25 v. wkg., and an aluminium chassis 2in. x 6in. x 13in. already drilled to accommodate a 5 valve superhet, 2 wave-change switches, 2 toggle switches, 1.2 amp. mains dropping resistance, 1 volume control with switch, 1 volume control less switch, 36 resistors, 36 assorted tubular, mica and ceramic condensers and 12 high voltage condensers. All Components New and Unused. Offered at an "all can afford" price of

Hurry, stocks will soon be exhausted. **22/6** POST FREE METERS.—We have available a limited number only of D.C. meters stripped from equipment, but only superficially soiled. They are of the 2in. square type and are currently priced at 6 for 10/6 post free. A good investment for all and sundry. Note our price.

LOUDSPEAKERS. — Several famous makers are represented. These speakers are all new and complete with pentode transformer: 5in. 12/6, 8in. 17/6, 10in. 25/- SPECIAL OFFER THIS MONTH ONLY. A Portable TEST METER in Bakelite case ranges 0-1.5v, 0-3v, 0-60-m/a, 0-5,000 ohms. Can be rapidly modified to make a superb general purpose Test Meter. Brand New and Boxed, only 17/6 post free.

## Best Buy at Britain's CHARLES BRITAIN (RADIO) LTD.



11, Upper St. Martins Lane, London, W.C.2  
Open 9 to 6, including Saturday.

## TELEVISION

Why not make your own?

### "THE HOME BUILT TELEVISOR"

Book of instructions, wiring diagram and full list of parts 6/6 post free.

Full scale blueprints shortly available.

### UNITS SUPPLIED READY WIRED

E.H.T TRANSFORMERS.	£3.7.6
FOCUS COILS.	£1.17.6
LINE TRANS.	£2.2.0
SCANNING COILS.	£1.12.6
9" WHITE MASKS.	12.0
12" WHITE MASKS.	£1.0.0

Send now to:-

**TELERADIO**  
157, Fore St.,  
Edmonton, N.18.  
Phone: TOT 3386.  
THE LEADING KIT SUPPLIERS

## ★ Radiospares Quality Parts

The Service Engineer's First Choice

## ★ CRYSTAL SET

incorporating the latest CRYSTAL VALVE as used in radar receivers. Adjustable Iron Coré Coil RECEPTION GUARANTEED

Polished wood cabinet. 15/- post 9d. Send S.A.E. for lists of copper wires, screws, nuts, paxolin tubes, ebonite, tufnol rod and panels etc.

POST RADIO SUPPLIES  
33, Bourne Gardens, London, E.4

## INEXPENSIVE TELEVISION

The Following Specified Items Available from Stock

"Television For The Home Constructor." 1/6

R1355 Receiver, Complete with Valves. Brand New in Original Crates. 59/6 carr. paid.

RF25 Unit. Complete Ready for Use in R1355 Receiver. Brand New in Original Sealed Cartons.

19/6 post 1/-.

These units are far superior to the used patterns on offer at lower prices, but being brand new and unused can be relied on to operate.

OUR GUARANTEE: MONEY REFUNDED IF NOT SATISFIED ON RETURN OF GOODS WITHIN 7 DAYS.

### H. P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House,  
55, County Road, Walton,  
Liverpool 4.  
Estab. 1935. Tel.: Aintree 1445.  
Staff Call Signs: G3DGL, G3DLV.

**You're SURE to get it at**

# STERN'S

ESTABLISHED 25 YEARS

**Resistances—**  
Special Offer. Parcel containing 100 popular assorted values. 1 watt type, 8/6 per 100; 1 watt type, 11/6 per 100. (Price enquires invited).  
**Oil Speakers.**—Well-known manufacturer's surplus, all 2-3 ohms and P.M., 10in. 23/6; 8in. 17/- (15 ohm, 18/9); 6in., 16/6; 5in., 10/11 and 12/9 (with Transf. 18/6); 3in. 13/9; 2 1/2in. 14/9. Energised also available.  
**METRIC RECTIFIERS.**—Westinghouse. 0.5 m A., 3/11; 0-10 m A., 7/6; 0-1 m A., 10/6.  
**SELENIUM RECTIFIERS.**—H.T. h.wave. 250 v. 50 m A., 5/9; 200 v. 100 m A., 5/9; 250 v. 100 m A., 7/6; 250 v. 300 m A., 13/9; Bridge Rec. 6 v. 1 amp, 6/9; 12 v. 1 amp, 12/6; 12 v. 3 amp, 24/-; 12 v. 6 a., 37/6; 70 v. 11 a., 37/6. Also L.T. 2-12 v. 1 amp, 3/6.  
**CHARGE TRANSFORMERS.**—Each has Input 230 v. Outputs 24 v. (tapped 15, 8 and 4 v.), 3 amps., 27/6; 30 v. (tapped 15 and 9 v.), 3 amps., 25/6; 15 v. (tapped 9 v.), 3 amps., 17/6.  
**FILAMENT TRANSFORMERS.**—Input 200-250 v., output 6.3 v., 11 amps., 9/-. Also with output 4 v., 11 amps., 9/-.  
**I.X.-G.W.T. (T.M.C.)** Reed-type Headphones, 70 ohms, 1/9 each (3/6 pair with leads). Single earphones, 75 ohms, with adjustable Headband, 1/6. Midget Output Trans., 32-1, and Parafed Trf., 4-1, both 1in. x 1in. x 1in., 3- each. P/Pull Intervalve, 2.5-1 each half. Output Trf., 60-1, both 1 1/2in. x 1 1/2in., 3- each. Tannoy Transverse Carbon Mike inset, 2/3. Midget Intervalve Transf., 3-1, 5/9 or 4-1, 3/9 each. Multi-ratio Matching Transf., 4 windings (2 C.T.), over 10 ratios between 10 and 100-1. 2in. x 1 1/2in. x 1 1/2in., 3/9. 12 volt D.C. motor suitable for models, 19/6. Moving Coil Mike with S/R Switch, 2/6. M Coil Headphone, 2/-. Carbon Hand Mike, with S/R Switch, 2/11.  
**I.X.-G.W.T. (T.M.C.)** 1 mfd. 5,000 v. Mansbridge, 6/9. 25 mfd. 2,000 v. Mansbridge, 1/6. Throat Mikes, 3/6.  
**GARRARD A.C.**—100-250 v. Gram. Motor with turntable and Pick-up. Auto-stop. £5 18s. 6d.  
**PLESSEY AUTO-CHANGER.** A.C. 200-250 v., 8 records mixed. Mag. Pick-up. £12 6s. 8d.  
**COLLARO GRAM MOTOR.**—Auto-stop, Turntable. A.C. 100-250 v. £5 18s. 4d.  
★ Send 2id. stamp for very full Stock Lists. When ordering please cover packing and postage.  
**STERN RADIO, LTD., 109 & 115, FLEET ST., E.C.4**  
Telephone: CENTRAL 5814 and 2280.

## THESE ARE IN STOCK

Radio, Television and Electrical Repairs. Ed. R. C. Norris. 10s. 6d. Postage 9d.  
**Radio Tube Vade Mecum**—1946 edition, by P. H. Brans. 9s. Postage 6d.  
**Radio Laboratory Handbook**, by M. G. Scroggie. 12s. 6d. Postage 4d.  
**News' Television Manual**, by F. J. Cunn. 7s. 6d. Postage 5d.  
**Television Explained**, by W. E. Miller. 3s. 6d. Postage 2d.  
**Amateur Radio Valve Technique**, by D. N. Corfield and P. V. Cundy. 3s. 6d. Postage 2d.  
We have the finest stock of British and American radio books. Complete list on application.  
**THE MODERN BOOK CO**  
(Dept. P.4) 19-23, Praed Street, London, W.2

## PLAN YOUR CAREER

RADIO, TELEVISION AND OTHER INDUSTRIAL ELECTRONIC SUBJECTS.

WRITE NOW FOR FREE BOOKLET summarising the careers available in Electronics and giving particulars of POSTAL & ATTENDANCE COURSES in Industrial Electronics, Maths, Radio, Television, Telecommunications, and other Electronic subjects.

## E. M. I. INSTITUTES

Dept. 32, 43, Grove Park Road, Chiswick, London, W.4. Telephone CH15Wick 44178

E.M.I. Institutes—backed by the Electronic Organisation which includes "H.M.V.", Columbia, Marconi/phone, etc. E.106A

## LASKY'S RADIO TELEVISION SPECIALS

**TYPE 62 INDICATOR UNIT**  
Complete with 20 valves: 16 SP61, 2 EA50, 2 EB34, and 6in. cathode ray tube, type VCR97 (short persistence).  
**RECEIVER TYPE 1959**  
LASKY'S PRICE 59/6, carriage 7/6 extra. BRAND NEW AND UNUSED. SEALED IN MAKER'S WOOD TRANSIT CASE. Contains 11 new valves: 8 VR65, 1 5U4G, 1 VU12, 1 VU12, resistances, condensers, and many other components. LASKY'S PRICE 42/6, carriage 5/- extra. As above but used. LASKY'S PRICE 30/- plus carriage 5/- extra.


A booklet giving full data for building a television set, using the above Ex-Government units is available. Price 1/6 per copy. **MAINS TRANSFORMERS.** New and Fully Guaranteed. 200/250 volts. 50 c.p.s. Input, with screw tapping adjustment. 350-0-350 volts. 100 m A., 6/3 volts, 3 amps. 5 volts, 2 amps., output. Semi-shrouded, chassis mounting.

LASKY'S PRICE 20/-, post 1/6 extra.  
**E.H.T. TRANSFORMERS FOR THE**  
Specifications: Primary 200/250 volts 50 c.p.s. Secondary 2,500 volts at 4 m A., 4 volts at 1.1 amps., and 4 volts (centre tapped) at 1.5 amps.

LASKY'S PRICE 35/-, post 1/6 extra.  
**E.H.T. SMOOTHING CONDENSERS**  
1 mfd. 3.5 k.v.v. 1/6 each, post 4d.  
1 mfd. 7 k.v.v. 15/- each, post 6d.  
LET LASKY'S HELP YOU BUILD YOUR INEXPENSIVE TELEVISION FOR EVEN LESS MONEY.

HAVE YOU RECEIVED YOUR COPY OF THE "LASKY'S BULLETIN"? IF NOT SEND IN 2id. FOR THIS MONTH'S COPY, WHICH GIVES FULL DETAILS OF OUR EX-GOVERNMENT STOCKS. PLEASE WRITE YOUR NAME AND ADDRESS IN BLOCK LETTERS.

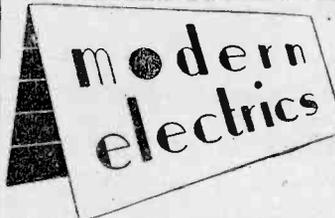**LASKY'S RADIO**  
370, Harrow Road, Paddington, London, W.9. (Opposite Paddington Hospital). Telephone: CUNNINGHAM 1979.  
Hours: Mon. to Sat., 9.30 a.m. to 6 p.m. Thursday, Half Day.



**SPECIAL OFFER.** Universal Avomitor, £7.10.0. D.C. Avomitor, £13.15.0. New. Boxed. Guaranteed. All other Avo instruments available ex. stock, including New Electronic Meter at £35 and the Latest Avo Wideband Signal Generator at £25. 0.0  
**TAYLOR TEST EQUIPMENT.** The entire range of test equipment by this famous maker is now available on hire-purchase. Send S.A.E. for catalogue and terms.  
**"KROBOS" PHONES.** Single speed, 78 r.p.m., 50 cycles. 6d. each (8/1d. post free).

**PICCO RADIOMETERS.** 0-8 volts and 0-240 volts A.C./D.C., 25/-

**SPECIAL OFFER OF ELECTROLYTICS.** Not ex-Government. T.M.C., 32 mfd., 4/6; 16 and 8 mfd., 5/-; 16 mfd., 4/-; 8 mfd., 4/-.

**GRAM MOTORS.** Collaro A.C. motor and 12in. plate less pick-up, £5 18/4.  
Collaro A.C./D.C. motor and 12in. plate less pick-up, £9.5/6.

Collaro A.C. motor and plate with pick-up and Auto-stop, £9 13/6.  
Collaro A.C./D.C. motor and 12in. plate with pick-up and Auto-stop, £12 18/10.

NEW Collaro A.C. auto-changer, 10in. or 12in. records, mixed, £14 6/8.  
Garrard A.C. "S" unit, including pick-up and Auto-stop, £5 19/3.

Auto changers by "Plessey," "Garrard," "Collaro." Let us have your requirements. Under 20/- C.W.O. only; C.O.D. or C.W.O. over 20/-. When ordering C.W.O. please allow sufficient for packing and postage.

**MODERN ELECTRICS Ltd.**  
164, CHARING CROSS ROAD, LONDON W.C.2. Telephone Bar 7687

## SAMSON'S SURPLUS STORES

**BRAND NEW A.M. TRANSFORMERS.** 500v.-500v., 250 m A., 300v. 100 m A., 12v. 15. Centre tapped 6.5v. 3.5a., 4v. 3.5a. Input 100v.-250v., 45/-, post 2/6.

**SPECIAL OFFER OF UNI-SELECTOR SWITCHES:**

6 Way, 35/- each.  
7 " 37/6 "  
8 " 40/- " Post 9d. per switch.

**HEAVY-DUTY TRANSFORMER.** 12v. 70A. Input 200/250v., £4 10/-, carriage 4/-.

**CATHODE RAY UNIT 1623.** Complete with 2 CR. Tubes VCR917 and VCR139, 3 VR65, 1 VR52, 4odes, resistors, condensers, etc. Suitable for vision construction. Brand new in maker's packing case. £3 17/6, carriage 3/6.

**RADAR RECEIVER TYPE 184.** Complete with 14 valves, including: 1 CU6G 4 VR91, 7 VR65, 1 VU11, 1 VR92. This receiver contains a 45 mc./s. I.F. strip, ideal for television construction. Brand new, £2 5/0, carriage extra.

**PARCEL OF VALVES.** Brand new ex-Government valves. One VR56, 1 VR65, 1 VR54, 3 VR135, 1 615G. Price £1.

**CO-AXIAL CABLE.** 30ft. length of cable, 30 ohm. A Pye male connector each end. Brand new. 8/6 each.

169/171 EDGWARE ROAD, LONDON, W.2. TEL: PAD 7851

125 TOTTENHAM COURT ROAD, LONDON, W.1. TEL: EU5 4982

All orders and correspondence to our Edgware Road Branch, please.

# Programme Pointers

Our Music Critic, MAURICE REEVE, Looks Back at the Christmas Programmes

IN discussing the Christmas programmes—which is the task I am allotting myself this month—two main factors will govern my conclusions, namely, about how many people do any listening during the holiday, and, secondly, what opportunities are there for good, critical listening. These two points may, at first glance, sound rather like one and the same thing. They are not, however, for the reason that a person may have every intention and desire to listen to a certain item, but finds that there is no opportunity to do so when the time comes. I feel that, if the item is wanted by a sufficient number, the B.B.C. should provide it. They cannot, naturally, be held responsible for providing the opportunities in our domestic and social arrangements for listening in.

Take the first point first—just how many people do listen-in during the Christmas vacation—which is the one that most concerns us here. My own opinion is, many fewer than normally. And those that do would do so much less critically. I wonder if I am right? It rather looks as if I am, on the second count, at any rate, judging by the types of items chosen for the Home Service, which were much "lighter" than average. I doubt whether many tuned in to the Scottish Regional's orchestral concert bang in the middle of Christmas afternoon, however; one hour long, immediately following the King, although their programme was airy and attractive. Or the Northern's concert on Boxing Day, from three until four-thirty, including the Brahms Violin Concerto and a Haydn Symphony—tough going, surely, for both players and listeners.

The inclusion of the first Reith Lecture, by Bertrand Russell, on the Sunday at 9.15, was criticised in some quarters. But I rather feel that the festive dining and wining had probably been well slept off by then, though visiting may have been taking place. Anyhow, I heard it in quite an alert frame of mind.

## Well Chosen

On the whole, I thought the programmes were well chosen and entertaining. I missed "Christmas at Dingley Dell," a reading of which might well become an annual item, perhaps alternating with other classic descriptions of the festival from English literature. It would at least serve as a chastening reminder of the days and the life that are beyond recall, though the descriptions of the festive boards may be a little too much for our gastric juices in these less spacious days.

The "Good Neighbours" programme was interesting without being anything like up to the standard of similar Christmas tours, prefacing the late King George V's talks before the war. I liked *Hansel and Gretel* on Christmas Eve evening, a charming work, and, so far as I know, the sole survivor of the output of its composer, Humperdinck. The Christmas Day Music Hall was vastly superior

to the usual stuff put out on Saturday evenings, as it was presumably meant to be, judging from the galaxy of stars that composed the bill.

The Sunday programme was an ordinary Sunday affair, with all the Sabbath features in their usual places; whilst the Boxing Day menu was even slightly lighter than Christmas Day, lacking, as it did, a symphony concert.

The Third Programme stooped and fell in line with the popular revels to the extent of including in its forbidding pages such "un-Thirdish" items as "Little People and Co.," a talk by Algernon Blackwood, "Christmas Remembered," by Lady Bonham Carter, and "The Stolen Turnips"; "The Magic Tablecloth," "The Sneezing Goat" and "The Wooden Whistle," told by Arthur Ransome. Such goings-on can never have been known before, and will doubtless not be repeated again till next Yule. Its honour was defended, however, by a full length symphony concert under Sir A. Boult, including Bartok's Concerto for Orchestra, and the Franck Sonata, by Campoli and Gritten. All the other days of the holiday, its austerity was at its usual flood level. Much as I usually like it—by temperament and nature, I am a "Thirder" rather than a "Homer," and certainly a "Lighter"—I wonder if it was listened to by more than a small handful? Still, perhaps it was better there, on tap, than that one hungry soul should be deprived of his Bartok or his Franck. In spite of my innate "Third" leanings, heaven help me, personally, from such stuff on Christmas evening, which brings us to the second point set out at the start.

## "Good" Listening

The opportunities for good listening at Christmas-time, as apart from just turning the knob and seeing what's on, must be so considerably fewer than normally that they are bound to influence programme building and to shift the centre of gravity from serious to light or lightish. For tens of thousands Christmas is a day of very hard work, at any rate, until the clock is well on its round. They can't listen to more than a catchy tune played or sung, or to pick up a joke from *Much Binding* or a similar show, as they pass to and fro on their lawful occasions. Entertaining and being entertained preoccupies many others, especially Boxing Day, not to mention the Boxing Night theatres and pantomimes. I shouldn't be surprised if listening-in was reduced to 50 or 60 per cent. of its normal, and critical listening to something even less than that.

To sum up, it was pretty good fare we were served up with. There was not too much repetition of the more commonplace Christmas adjuncts, though there were two performances of *Hely-Hutchinson's Carol Symphony*. Whether it is possible, and if possible, worth while, devising some startlingly original programmes for the next festival which would compel our attentions.

more than at present, I wouldn't like to say. Something that would bring the public to the microphone—or back to the microphone—instead of taking the mike to the public. Perhaps a little too much emphasis is laid on that latter policy, but if I am right in my belief that there is little chance of selective listening at Christmas time, then that policy is obviously the right one.

(Note. Regarding my reference to broadcasting "Christmas at Dingley Dell," or some similar excerpt, I notice that "A Christmas Carol," abridged, was included in the Woman's Hour on Christmas Eve; a programme to which I am not normally accustomed to tuning in.)

### Tommy Handley

No article on radio programmes would be possible without its author's personal tribute to the late Tommy Handley. At the time of writing, although it has been more or less decided there will be no more "Itma" programmes, the question of a

successor on similar lines is still, I believe, open. If that type of show is finally abandoned, it will be the first time, in my recollection, at any rate, that "the show has not gone on." Will it be a precedent, and a break with one of the oldest traditions? "Itma," itself, was something entirely new in radio shows; it had a personality and a quality which were not only all its own, but which I don't think I am alone in saying were above even Tommy Handley. Was "that man" just Tommy and Tommy alone, or was it the prototype of a character, almost Dickensian in the width of its appeal; one which could be played in a tradition such as the Falstaffian or the Pickwickian traditions, by another comedian of genius, were he given the chance? I admit an adequate successor to Tommy Handley would be difficult to find. But before the curtain is rung down for ever, further counsel might be taken without loss to anyone concerned.

## News from the Clubs

**STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY**  
Hon. Sec.: W. A. Higgins (G8GF), 35, John Street, Brierley Hill.

**TWENTY-EIGHT** members were present at a meeting of the above society in the Science Block, King Edward's School, Stourbridge, to listen to a talk given by Mr. Pratt, of AVO, Ltd., London, entitled "Measuring Instruments." Some of the latest AVO equipment was on show and at the end of Mr. Pratt's most excellent contribution, members were able to inspect the instruments at close range.

Morse transmissions were arranged for non-transmitting members and the president (Mr. J. Timbrell) announced a scheme for the presentation by Stourbridge Borough to the society of station QSL cards for transmitting members.

All radio enthusiasts are welcome at meetings, which take place on the first Tuesday in each month and prospective members should contact the secretary.

**THE WEST MIDDLESEX AMATEUR RADIO CLUB**  
Hon. Sec.: C. Alabaster, 34, Lothian Avenue, Hayes, Middlesex.

**THE** West Middlesex Amateur Radio Club continues to flourish and attract enthusiasts with a variety of radio and electronic interests. Recent meetings have been devoted to a lecture on valves given by Mr. S. R. Claudot, of the Radar Association, and a discussion on amplifiers by club members. Meetings in the immediate future will be given over to a junk sale and an evening's discussion on V.H.F.

Prospective members are cordially invited to attend the meetings which are held on the second and fourth Wednesdays of every month at the Labour Hall, Uxbridge Road, Southall, Middlesex, at 7.30 p.m.

**SOLIHULL AMATEUR RADIO SOCIETY**  
Hon. Sec.: G. Haring, 121, Bradbury Road, Olton, Birmingham.

**A** MEETING of the above society was held at its headquarters, "The Old Manor House," recently, when a very instructive and enjoyable lecture on radar was given by Mr. F. T. Smith (G6FK), of Wolverhampton. The next meeting of the club will be addressed by one of its own members, Mr. G. Hill (G8MZ), on his 10-metre rotary beam.

Meetings are held fortnightly at the above address, when visitors and new members will be cordially welcomed.

**THE BRIGHTON AND DISTRICT RADIO CLUB**  
Hon. Sec.: R. J. Donald (G3DJD), 2, Canfield Road, Brighton.

**A**T the A.G.M. the following officers were elected—chairman, A. C. Sofe; hon. secretary, R. J. Donald; treasurer, F. R. Jupp. The club's station, G3EVE, is now active on 1.7, 3.5 and 7 Mc/s (phone) and reports on reception will be welcome. Meetings are held every Thursday at St. Mary's Hall, Bred Street, Brighton, from 7.30 p.m. The second Thursday in each month is the occasion of a talk by a visiting speaker. New members are invited to attend.

**STAMFORD AND DISTRICT RADIO SOCIETY**  
Hon. Sec.: F. K. Parker, 122, Empingham Road, Stamford, Lincs.

**THIS** society, formed in October, 1948, has a membership of 12 at the time of writing. Full society meetings are held on the second Monday in each month at the Albert Hall, High Street, Stamford. Meetings are held for the remaining three weeks of the month at 31, St. Mary's Street, Stamford, at 8 o'clock. These meetings take the form of a general discussion on set subjects.

The annual subscription is fixed at 5s. payable to the treasurer, Mr. F. Naylor (G3CUD), on any club night.

Mr. T. Allen has been elected chairman of the society. It is hoped that at some future date to arrange morse classes for those wishing to obtain amateur transmitting licences, while all members endeavour to help any prospective amateur in the task of passing the examination for the technical side of the problem.

Out of the 12 members on the society's books three have amateur transmitting licences, all signs being G3CUD, G3DKG, G3EKV.

Anybody who wishes to join the radio society (and the need for more members is very pressing) should communicate with the secretary.

**SOUTH MANCHESTER RADIO CLUB**  
Hon. Sec.: M. I. Wilks, "Ormsby," 57, Longley Lane, Northenden, Manchester.

**THE** club is still going strong with an increase of membership at each meeting.

At a recent meeting members heard an interesting talk by Mr. King (G3EON) on the "Straight Receiver," commencing from the very simple Rx and gradually building up to the more elaborate types showing the reason for each component, its advantages and drawbacks, etc.

Plans for the club Tx are going ahead and it now all depends whether permission may be obtained for erecting a suitable antenna at the Church Schools. The rig the committee have in mind is something portable, as there is nowhere available to keep gear between meetings, and also in favour of the portable rig is the fact that during the coming summer it will be possible to have a field day, etc.

Plans for future meetings are still in the making and it is very difficult to tie down a certain lecturer to a given evening but talks, etc., are hoped to include V.H.F. technique, Practical Construction and The Part Radio Plays in Medicine.

Morse classes, which have dropped off at the last few meetings are to be restarted and two groups will be active at all future meetings, resulting in a little QRM and also an opportunity for both those only beginning and the advanced to have practice at the same time.

Regarding visits, it is hoped to have the chance to see the local police installations and also go round a newspaper office, etc. Meetings are being held fortnightly throughout the year.

# SPECIAL CLEARANCE OFFER

## 14ft. AERIAL MAST

Carr. paid 4/9 complete

Consists of two lengths of paxolin tubing 2 3/8 in. and 3 1/2 in. dia. respectively, with 3/16 in. wall. The smaller tube fits tightly into the larger, both having metal ends. When fitted, the aerial has an over-all length of 14ft. Ideal for a transmitting or receiving aerial, but has many other uses also. May be fixed to the ground or to a fixture such as a chimney, wall, etc. Very sturdy.

### ALEC DAVIS SUPPLIES LTD.

13 Tottenham Court Rd., London, W.1.  
Tel. MUS. 4539 and MUS. 2453

THE LATEST EDITION OF

### THE HOME

## CONSTRUCTOR'S HANDBOOK IS NOW AVAILABLE, AND

- \* Contains details of many circuit diagrams of radio receivers, etc.
- \* A complete range of Radio and Television components at the very lowest prices.
- \* Pages of servicing and constructional information.
- \* Complete Resistance Colour Code.
- \* A considerable amount of invaluable general radio information; and in addition
- \* Details of a magnificent new bonus profit-sharing scheme.

This booklet, which was originally priced at 2/6 is now available to you for only 1/- FROM

### SUPACOILS

98, GREENWAY AVENUE, LONDON, E.17.

## L-R'S IN STOCK

### CASH or EASY TERMS

- GOODMANS 12in. and Axiom Speakers.
- Wharfedale Speakers.
- COLLARO Gram Unit & pick-up.
- COLLARO auto record changer.
- ARMSTRONG CHASSIS All models, All available for cash or easy terms, also many other items. Please let us have your enquiries. Particulars and leaflets on request.

- AVO Model 7 Meter.
- AVO Valve Tester.
- AVOMINOR A.C./D.C. Meter.
- AVOMINOR D.C. Meter.

The London Radio Supply Co.  
(Est. 1925)  
BALCOMBE, SUSSEX

## ELECTRADIX RADIOS

For Best British Bargains



**MICRO-PHONES.** The New Lesdix Table Mike, high grade carbon inset in bakelite case and mounted on polished bakelite base with transformer, 12/6. G.P.O. mike

button, 3/6. Self-energised magnetic microphones in solid rubber case, 1 1/2 in. dia., 7/6 each. The Tannoy hand mike, dual carbon type, metal clad with neat switch in handle, 10/-.

**THE DEM. CONTINUITY TESTER.** A self-contained portable circuit tester for all electrical circuits, almost pocket size, 6 1/2 x 3 1/2 x 2 1/2 in., a beautifully made Govt. instrument, new, totally enclosed Polish wood case with carrying strap and contact switch. The experimenter's best friend. Worth 2 guineas. A limited number are offered at 12/6 post free.

**DIMMER RESISTANCES.** Totally enclosed, panel type, 100 ohms 1/2 amp. or 50 ohms 1/2 amp., 2/6 each, post 6d.

**LAMPS.** 1/2 watt Neon lamps, 230 volts, miniature type, with small bayonet cap, 3/6, postage 9d. extra; 5-watt Standard Neons, bayonet cap, 4/-, postage 9d.; letter plate Neons with E.S. cap, 2/6, postage 9d.

**BATTERY CHARGER KIT,** for home charging from 230 volts A.C. double wound transformer, metal rectifier, ballast resistance terminals and base plate, 2 volts 1/2 amp., 21/-; 6 volt 1/2 amp., 35/-, with connection diagram.

**LIGHTING PLANTS.** Stuart Turner and Pelapone, slow speed engines and dynamo set on C.I. bed plate. 500 watt single cylinder 2-stroke water-cooled self-oiled engine, mag. ign., coupled to 50/70 volts 10 ep. shunt dynamo, 1,000 r.p.m., 84s. Villiers Portable plants, 1 1/2 kW, 35 volts 35 amps., £22/10/-; Chore-Horse 300 watt 12 volt 25 amp., £14/10/-.

**INDUCTOR ALTERNATORS.** 400 watts, totally enclosed, single or 3-phase 50 cy., 230 volts 4 pole ball bearings speed 2,800 r.p.m., need 6/8 v. 6/8 amp. separate excitation, 85s. as new.

**MOTOR BLOWERS.** 24 volts D.C., Keith Blackman 5in. inlet and 5in. outlet, £3/10/-.

**TRANSFORMERS.** B.T.H. 200/230/250 volts, 50 cy., input 2 v. 20 amps., and 75 v. 6 amp., with 15 taps output G.P.O. transformer cores with lams and wire, 500 watts, 25/-.

**SWITCHBOARDS.** 500 watt, in metal case 15in. x 15in., with doors, 5 mov. coil meters, 4 variable slider resistances, 3 enclosed cutouts, switches, terminals, etc., £4, ex-Battersea Stores.

**PETROL ENGINES.** 1 h.p. single cylinder 2-stroke water-cooled with petrol tank, £10, carriage extra.

**PARCELS.** 10lb. Parcel of useful oddments for your junk box, all clean and dismantled from Government and other apparatus, 7/6, post free. Not for overseas buyers.

Please include postage for mail orders

## ELECTRADIX RADIOS

214, Queenstown Road, London, S.W.8  
Telephone: MACaulay 2159

## MIDLAND INSTRUMENT CO.

Brand New Govt. Surplus Stock.

Tools, Terrys B.A. spanner sets, 8 sizes, 1/-; Elliot Lucas 6in. flat-nosed pliers, 1/6; Apollo 9in. box spanners, one end 4 B.A. the other 6 B.A., 6d.; ditto 4 B.A. only, 4d.; one of each 3, 3, post 9d. Mu-19 Dual Coil Sets, low range L and high range N. In coil set containers, 1 1/2 in. x 4 1/2 in. x 3 1/2 in., post 1/-.

**Crystal Valve Rectifiers.** Sylvania IN21, 3/6, post 3d. Hand Generators, generates 6 v. 1 amp., complete with handle and cut-out for charging battery, 25/-, post 1/4.

**Amplifiers Type 1134,** contains two civilian-type valves, 210-LF and QP-21, four transformers, switches, etc., operates from 2 v. L.T. and 120 v. H.T., an ideal battery amplifier for gram. pick-up, microphone or as two-way loudspeaking intercom, in metal cases, also wood transit case, 15/-, post 1/4; ditto, less valves, 7/6, post 1/4.

**Headphones,** moving coil, 7/6, post 9d.; high resistance super-sensitive, 7/6, post 9d. Berkshire Motors, 12 v. 4 amp. A.C./D.C. fitted reduction gearbox, final drive 1,000 r.p.m., 15/-, post 1/4; ditto, 24 v. 1.7 amp., 10/-, post 1/4.

**Mains Transformers,** input 220 v., output 50 v. 11 amp., 25/- carriage 6/-.

**Engine Driven Generators (D.C. dynamos),** output 12 v. 750 watt, 20/-, carriage 5/-.

**Accumulator Cut-outs,** in bakelite cases, two types, 12 or 24 v., both 60 amp., 7/6, post 9d. Mains Motors, 200/250 v. A.C./D.C. approx. 1 amp. fitted in. shaft, ball-bearing, continuous rating, 20/-, post 1/-.

**Vibrator Packs,** complete with all smoothing, input 6 v. L.T. H.T. and G.B. output for 18 and 30 sets, 20/-, post 1/4.

**Waldie-Falkie Aerials,** copper collapsible, 9 sections, 7ft. long, also makes an ideal fishing rod, 2/6, post 6d.; 3 for 6/9, post 9d.

**Receivers Type 1124A,** less valves, 10/-, post 1/4.

**Voltmeters,** moving coil 0-300 v., 2 1/2 in. sq. scale, 5/-, post 4d. R.F. Meters, 0-350 m.A., 3/6, post 4d.; 0-4 amp. fitted two press buttons, 5/-, post 6d.

Also thousands of other interesting items; send for our new current lists, 2d. with s.a.c. Orders over 30/- post paid, carriage orders extra. Call C.O.D. service is cancelled for the time being.

## MOORPOOL CIRCLE, BIRMINGHAM.

17, Tel: HARborne 1308 or 2664.

## RADIOLECTRON

22, Frances Street, Scunthorpe, Lincs. New Goods Only. No W.D. Surplus.

**CONDENSERS.** Electrolytic 2 mfd. 3/3; 4/3; 8/3; 16/4; 7/8; 8-8; 4/9; 8-16; 6/1; 16-16; 6/11; 2/5 x 25 v. 2/4; 25 x 50 v. 3/4; 50 x 50 v. 3/9; Tubulars up to .0005, 7/4; up to .005, 8d.; up to 1/1. Ltd. 4 Micro up to .0005, 9d.; up to .005, 1/-; up to .01, 1/3; Tuning .0005, 1 gang, 4/3; 2 gang, 1/1; Drum or Epicur. drives, 3/-; Nylon Drive Cord, 7d. yd.

**VOLUME CONTROLS.** Lg. Spdls. 3/3; with Sw. 5/-; W.W. less Sw. 5/-.

**RESISTORS.** Carbon 1 watt, 4d.; 1 watt, 7/-; W.W. 1 watt, 1/-; 5 watt, 1/6; 20 watt, 2/1; Mains Droppers, 2A, 4/4; 3A, 4/11; 6A, 15/6; 8A, 17/-.

**LOUD SPEAKERS.** P.M., 5in., 14/-; 6in., 15/6; 8in., 17/-.

**TRANSFORMERS.** Output, Pow/Pen., 5/6; Multi-ratio, 7/3; Intervalve, Parafeed, 5/-; Dir. Feed, 3 or 6/1 ratio, 6/-; Class B Driver, 7/-; Q.P.P. Driver, 8/6.

**TRIMS:** Cash with order. Over 10/- post free, under add 4d. C.O.D. extra. 2/6 stamp will bring you copy of our latest list.

## RADIO G200 ANNOUNCES

These Special Bargains

**VIBRATOR.** Unit No. 4. 12 volts D.C. in 250-300 volts at 100 m.A. or more out, 4 metal rectifiers. These are the power unit from the famous No. 22 set, are ideal for car radio etc. Fully suppressed, a bargain at only 19/6.

**ALTIMETER.** ARNL. This American-built transmitter-receiver unit contains 4 ACORN 1 VR150/30 and 8 metal octal tubes exquisitely built, is very useful to the 400 m.p.h. enthusiast. Brand new in original packing for only 70/-.

**GENEMOTORS.** 11.5 volts D.C. in 250 volts 125 m.A. D.C. out. G200s, price 19/6. 11.5 volts D.C. in 480 volts, 65 m.A. D.C. out. (This gives about 250 volts when run from a 6 volt car supply) G200s, price only 18/6. Please note new address where callers can see hundreds of other desirable bargains.

**A. C. HOILE,**  
55, Union Street, Maidstone

# LYONS RADIO

3, Goldhawk Road,  
Shepherds Bush, W.12

Telephone : Shepherds Bush 1729.

## LIGHTWEIGHT MIDGET AMERICAN HEADPHONES

These super headphones are highly sensitive and designed so that they can be worn for long periods without discomfort. They measure only 1 1/2 in. in diameter and are the last word in headphone efficiency. Brand new. Low resistance.

Also fitted with midget transformer in lead for high resistance output.

Price only 5/9 pair, post free.

Price 7/6 complete, post free.

## MINE DETECTOR AMPLIFIERS

Brand new units fitted with 3-174 valves. These are well made resistance-capacity coupled amplifiers housed in aluminium cases.

Price 22/6, post free. Spare valves-7/6 each. Amplifier Unit, less valves, 7/6.

## MOVING COIL D.C. VOLTMETERS

3 1/2 in. dia. Projecting pattern with built-in resistance. Approx. 500 ohms per volt. Made to highest possible standards. Brand new. Special clearance line and unrepeatable at the price.

Price only 25/- (postage 1/6).

## MORSE PRACTISE BUZZER SET

Mounted on 6 1/2 in. square wooden base with adjustable buzzer. Super quality and brand new. Operates from 4 1/2 in. V. dry battery.

Price 5/9 (postage 1/2).

## MOTOR GENERATORS TYPE J

12 v. input. Outputs : 6 v. at 5 a., 150 v. at 100 m/A, 300 v. at 70 m/A. cont. and up to 240 m/A intermittent. Best British manufacture. Easily convertible to powerful mains motors. Price 18/- (carriage 2/6).

## Mains Transformers, Screened, Fully Interleaved and Impregnated

- |   |                               |
|---|-------------------------------|
| H.S. 63. Input 200/250. Output 250/10250. 60 m/A 6.3 v. at 3 amps. 5 v. at 2 amp. | <b>15/6</b><br>Half Shrouded  |
| H.S. 40. Windings as above. 4 v. at 4 amp. 4 v. at 2 amp.                         |                               |
| F.S. 2. Input 200/250. Output 250/10250 80 m/A                                    | <b>19/6</b><br>Fully Shrouded |
| F.S. 3. Input 200/250. Output 350/1350. 6.3-4.0 v. at 4 amp. 5-4.0 v. at 2 amp.   |                               |
| H.S. 2. Windings as F.S. 2. 80 m/A  | <b>17/6</b><br>Half Shrouded  |
| H.S. 3. Windings as F.S. 3. 80 m/A  |                               |
| F. 4. Filament. Transformer 200/250. Input 4 v. at 2 amp. output                  | 7/6 each                      |
| F. 6. Filament. Transformer 200/250. Input 6.3 v. at 2 amp. output                | 7/6 each                      |
| F. 44. Filament. Transformer 200/250. Input 4 v. at 4 amp. output                 | 13/6 each                     |
| F. 12. Filament. Transformer 200/250 Input 12.6 v. tapped at 6.3 v. at 3 amp.     | 15/6 each                     |
| F. 24. Filament. Transformer 200/250. Input 24 v. tapped at 12 v. at 3 amp.       | 21/6 each                     |
| Multi-ratio Output Transformer  | 5/- each                      |
| Midget Pentode. Output transformer  | 33/- per dozen                |
| C.W.O. (add 1/- in the £ for carriage. Over £2 carriage paid)                     |                               |

H. ASHWORTH, 676, Gt. Horton Road, Bradford, Yorks.



METERS. All models available. AVO, TAYLOR, etc. Easy terms on Taylor Instruments.

CATALOGUES FREE  
Q-MAX Chassis Cutters, all sizes, at 12/6. Keys 1/-.  
SOLDER Multicores, 13 SWG, 4/10; 16 SWG, 5/3.  
POTENTIOMETERS, wire wound, 5 ohms, 1,000 ohms, 5,000 ohms, 10,000 ohms, 25,000 ohms.  
14-foot (seven sections) AERIALS, very rigid. Ext. joint. Bargain. Post free 8/6.  
SERVICE SHEETS. Our best selection, 10/6 per dozen. We shall endeavour to include one sheet—your own choice—when it is available.

## G.E.C. HOME BROADCASTER

BUCO MAINS NOISE SUPPRESSORS. 16/-



You can now ENGRAVE on anything, even the hardest Metal, Plastic, Glass, Wood, Leather, Jewellery, etc. Operates on A.C. mains. Plugs straight into any light socket. Every user enthusiastic. Pleasure to work it. Profitable, too. 28 pages illustrated. Instruction Manual enclosed. Fully guaranteed, 52/6, plus 1/- postage.

Introducing the new A238 Indoor television aerial kit. Fit your own indoor television aerial in five minutes. In the greater number of television installations, an indoor television aerial is all that is required for adequate sensitivity.

We have been experimenting with this type of aerial, and we can now supply all the necessary fittings that will enable you to install a television aerial in 15 minutes. Fixed in a Jiffy, can be easily transported to the job in your coat pocket, as they are of the collapsible type. Simple yet efficient. Every item required for fitting the aerial in the loft is supplied in the kit. All you need is a hammer and five minutes time, plus 1/- postage.

VARIABLE CONDENSER. Midget two-gang fitted with trimmers and complete with perspex dust cover. These condensers made by "Plessey" are of the type used for tuning personal receivers. Price 7/2 each.

Bin. P.M. LOUDSPEAKER—Plessey, less transformer—complete with dust lid. Price 12/9.

TRANSFORMER. Bryce 100 watt 230 in. 110 volt out. Price 17/6. MAINS DROPPER. Made by "Erie." drops approximately 130 volts at 2 amps.—lapped for rectifier under. Vitreous enamel covered. An excellent replacement for line cord in midget receivers. Price 1/6. E.H.T. SMOOTHING. .02 mfd. at 5,000 volts Tropolized, 1/6 each.

MAINS TRANSFORMERS. 350-0-350 at 80 m/A. 4 v. 4 amp. and 4 v. 2 amp. Price 20/3, plus 1/- postage.

Mains Transformer, 250-0-250 at 70 m/A. 6.3 v. at 3 amp. 5 v. at 2 amp. Price 17/3, plus 1/- postage.

EX-W.D. HAND TORCH. This is quite a useful torch of very similar construction to an ordinary cycle lamp, with the exception that it is fitted with a hood and a coloured screen. Nevertheless, these items can be quickly replaced when it becomes an almost standard torch to take the type 900 twin cell battery. The switch mechanism is rather better than most torches, and it is complete with bulb. Price 2/6 each. Metal cased paper condenser. .01-1,000 v. working. Price 5/3 per dozen.

ELECTROLYTIC 10 mfd. x 350 v. Dubiler drilled. 2. 10 mfd. x 500 v. B.E.C. can type, 3/-, 8 mfd. x 450 v. B.E.C. can type, 2/3. 16 mfd. x 16 mfd. x 450 v. T.M.C. cardboard. 46. 32 mfd. x 350 v. B.E.C. can type, 2/-, 50 mfd. 12 v. American can type, 1/-, 25 mfd. x 25 mfd. x 200 v. B.I. block, 5/3. 25 mfd. 25 v. midget tag ends, 1/6. 10 mfd. 25 v. T.C.C. micro-pack, 1/3. 25 mfd. 50 v. B.E.C. cardboard wire end, 1/6.

P.M. LOUDSPEAKER, Bin., less output transformer (Plessey), 12/9. Bin., fitted output transformer (Plessey), 15/9. 6 1/2 in. fitted output trans. 17/6.

Please write immediately to Bull's (P.W.)

### RADIO BULL'S VALVES

46, HIGH ST., HARLESDEN, N.W.11

# PRATTS RADIO

1070 Harrow Road, London, N.W.10  
(Near Scrubbs Lane.) Tel. : LAD 1734

## AMPLIFIERS—College A.CIOE. 10 watt. 4-valve A.C. Neg. Fpk., £3/18/6. Model AC15E. 15 watt. 6-valve P-pull output. feedback over 2 stages. A.C. £13/18/6. Model UIOE. 10 watt. 6-valve D.C.A.C. P-pull output with feedback over 2 stages. 21/11/6. All above have separate mike stands and separate mks and gram inputs. 2 faders and tone control. Complete with case and chrome handles. Model AC4C. A.C. or Model U4C. D.C./A.C. 3-valve Record/Radio Amplifiers. complete with 3 Ohm O/Transfr. 25 9/6. Hundreds of P.W. readers have purchased College Amplifiers and testimonials prove their popularity. Can we help you or your club, etc.?

**SPEAKERS.** P.M. 3 1/2 in. 17/6. Truvox 5 in. 10/-, Goodmans 5 in. 14/6. 5 in. 14/9. 10 in. 28/6. 12 in. 130/- with Transfr. 5 in. 12/3. 6 1/2 in. Rola. 17/6. 8 in. 21/9. Condensers T.C.C. 25mfd. 25/-, 1/8. Plessey 8 x 450 v. 2/3. 8 1/2 x 8 x 450 v. 3/9. 8 x 16 450 v. 4/-, 16 x 16. 350 v. 4/6. 16 x 16 450 v. 4/9.

**TRANSFORMERS.** Portinminster 330-0-350 v. 6 v. 5 v. 80 m/A. 23/9. 100 m/A 6 v. 5 v. or 4 v. 4 v. 26/6. 120 m/A 6 v. 5 v. 35/-, 275-0-275 v. 6 v. 5 v. 23/9. Midget Power/Pen. 4.6. 5 w. Multi-Ratio, 7/6. 30 w. 23/9. I.F.S. Philco. 7.6 pr. Atkins. 9/6 pr. Wearite 21 or M400. 21/- pr. Fil. 6 1/2 v. 11 A. 7/-.

**COILS.** Dual Range with Reactor 4/6. Wearite "P" Coils, 3 each L & M.W. with reaction. 6/9 pr. Q. Coil Pack. 39/2.

**TUNING CONDENSERS.** .0003 or .0005 solid dielectric, 3/- each. 2 gang small .0005, 6/6. 3 gang .0005 small, 6/11.

**MISCELLANEOUS.** Vol. Controls 3-. W/Sw. 5/-, Octal bases, 5d. Chokes 60 m/A 20 in. 4/3. 150 m/A 10 in. 1/4. 250 m/A 5 in. 4/8. Lincore. 50 ohm 2/2. 7d. 3 w. 8d. ft. Presets 50ft., 10d. 100 ft., 1/3. .00025, 2/-, .0005, 2/3.

**VALVES.** B.V.A. or Tungram. Almost any return of post. 2d. stamp for list or query. C.O.D. or C.W.O. Post Paid Over 21. Open 10-6/0.

## NEW USED GOODS ONLY

### INSTRUMENT WIRE

Enamelled, Tinned Copper, Cotton Covered, and Silk Covered.

**ENAMELLED.** 16, 17, 18, 19, 20 swg., 1/6 per lb. reel. 21, 22 swg., 1/9 1/2 lb. 23, 24 swg., 2/- 1/2 lb. 25, 26 swg., 2/2 1/2 lb. 27, 28, 29, 30, 31, 32, 33, 34, 35, 36, 37, 38, 39, 40, 41, 42, 2/3 2 ozs. 42, 2/6 2 ozs. 2-oz. reels half above+3d.

**COTTON COVERED.** 16, 17 swg., 2/6 lb. 18, 19, 1/6 1/2 lb. 20, 1/9 1/2 lb. 21, 22, 1/10 1/2 lb. 23, 24, 2/- 1/2 lb. 25, 2/6 2/3 1/2 lb. 27, 28, 2/6 1/2 lb. 30, 2/9 1/2 lb. 32, 3/3 1/2 lb. 34, 3/6 1/2 lb. 36, 4/3 1/2 lb. (Please add 3d. towards postage).

**MANY OTHER SIZES IN STOCK.** Send S.A.E. for full range. (Trade enquiries welcomed).

**SPECIAL OFFER.** (High Resistance) HEADPHONES with adjustable headband and plated holders for earpieces. Splendid value at 12/6 per pair. Send for yours now, while stocks last.

**LATEST RADIO AND TELEVISION BOOKS.** Send S.A.E. for details.

**MORTONS, 13, CAMDEN ROAD, WALTHAMSTOW, LONDON, E.17.**

## A FREE BOOK

on Morse Code Training



There are Candler Morse Code Courses for Beginners and Operators.

Send for this Free "BOOK OF FACTS"

It gives full details concerning all Courses.

**THE CANDLER SYSTEM CO. (5.L.O.)**

121, Kingsway, London, W.C.2.

Candler System Co., Denver, Colorado, U.S.A.

# Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## "Smash and Grab"

SIR.—In these days of a never-ending stream of smash-and-grab raids, where radio shops seem to be specially favoured, the police are often the target for a charge of inefficiency.

The following facts in connection with our own recent smash-and-grab raid go to prove that the police do sometimes get their men.

On the night of December 11th we were visited by the S. and G. gentlemen; on the 14th we were informed by the flying squad that they had apprehended two men and recovered a portion of the stolen property. The focal point moved to the London Sessions on January 13th, where one of the two men detained was given a sentence of 15 months' imprisonment and the other, a mere lad of 18, was given three years' Borstal training.

If you publish this letter we trust that the facts will provide a measure of comfort to our fellow traders who are all too often the victims of these pests.—MODERN ELECTRICS, LTD. (London, W.C.2).

## "Crystal-grinding Technique"

SIR.—I was interested in the article "Crystal-grinding Technique" in the October, 1948 issue of PRACTICAL WIRELESS and would like to comment as follows:

In the list of apparatus required, Mr. Maloney itemises "a sheet of plate glass . . . (or old piece of window pane will do) . . ." It is most desirable that the working surface used for the lapping process be as flat as possible, i.e., optically flat. Any divergence from optical flatness will introduce a source of trouble when endeavouring to keep the crystal blank surface truly flat. For this reason the use of window pane is ill-advised as it is usually a long way from being flat. It is therefore most strongly recommended that any lapping carried out should be performed using nothing less true than twin-ground plate glass.

Referring to the point in the frequency spectrum at which the changeover from AT to BT cut occurs, the generally accepted frequency for changeover, in U.K., is around 3 Mc/s. My experience has been that although plates up to 4.5 Mc/s may be found in American type crystal units the position varies with British manufacturers and BT cuts may be found at frequencies as low as 2.9 Mc/s. I have not met an AT cut produced in U.K. with a frequency higher than 3.5 Mc/s. I have mentioned these points as they may save confusion to your readers when following the useful instructions laid down by Mr. Maloney.

In testing blanks prior to lapping or processing, Mr. Maloney does not mention the action which should be taken if the crystal plate is of poor or nil activity. The majority of thickness shear-mode crystal plates processed several years ago were finished to final frequency by lapping methods only. The "ageing" of a crystal plate so processed results in a loss of activity, due to deterioration of the major surfaces of the plate, and occurs in a

very large percentage of units containing plates processed in this manner. It may, therefore, be of assistance to add a few more words on the method of processing plates found to be below par.

On the assumption that the crystal plate is found to be defective as the result of ageing it will be necessary to lap both surfaces of the crystal plate to remove the "disturbed" or aged layer of quartz. The amount of quartz, in terms of increase of plate frequency in kc/s., to be removed from each major surface to ensure complete removal of the disturbed layer, is given by  $f^2/kc/s.$  where  $f$  is the frequency of the crystal plate in megacycles. It would, therefore, be good practice to remove not less than this amount of quartz from one face of the blank and proceed to bring the plate to required final frequency by the removal of quartz from the other major face as detailed by ZL3DE. The lapping of both major faces of the blank is an unavoidable procedure with a badly aged plate and although it may result in a greater tendency for these faces to lose their parallelism, this is where the skill of the operator is of importance and is measured by the results achieved. It will be appreciated how important this point is when it is realised that if parallelism of the major surfaces is outside a tolerance of the order of 1 micron the activity of the plate drops.

Incidentally, and in conclusion, the reader will have noted that in the foregoing I have at no point mentioned the term "grinding." This latter term, although commonly used, is a slack one and is, technically, an erroneous one. The process is intended to be one of "lapping" and is a process distinct from that of "grinding." The separate meanings of the two terms may be illustrated by the following definition:

"Lapping is a refined finishing process using loose abrasive grains, and is distinct from grinding involving the use of bonded grains."

As a title to the article I would have preferred the term "Crystal Processing Technique."—E. A. BARNSDALE (Risley).

## "R1355 and Television"

SIR.—Further to the letter of Mr. K. Berry, of Surbiton "R1355 and Television" (March, 1949), we should like to make the following comments:

Re the "4 Mc/s. bandwidth" we afterwards realised that this figure was incorrect, and when reprinting the articles as a booklet we altered this statement to read "has a suitable bandwidth."

Mr. Berry's statement that "the actual bandwidth is  $\pm 0.6$  Mc/s for 6 dB down, i.e., 1.2 Mc/s. bandwidth," is itself misleading. This statement was taken from Air Ministry, Publication 2557A Vol. 1, and refers to the position as the R1355 is purchased. By stagger tuning the I.F.s, and adjusting the R.F. unit trimmers to give single sideband reception, it is possible to resolve the -2 Mc/s. grating on Test Card C. Mr. Berry's statement that "the R.F. units 25, 26, 27, etc., are very suitable for

television as they stand" is obviously incorrect, as the R.F. 25 unit is the only one which covers the required frequencies without modification.

Should Mr. Berry be still unconvinced of the suitability of the R1355 receiver for television, maybe a personal demonstration would change his opinion. This we shall be pleased to arrange if he will contact us through these pages.—C. OVERLAND (G2ATV), LIONEL E. HOWES (G3AYA).

### "D.C. Oscillograph Amplifier"

SIR,—I should like to raise two points in connection with my article "D.C. Oscillograph Amplifier," which appeared in the March issue of PRACTICAL WIRELESS. Ch.1, the choke in the anode circuit of the 6J7 should be about 20 millihenries, i.e., 2,900 turns of 30 S.W.G. on a  $\frac{3}{4}$  in. diameter former filling a length of  $\frac{3}{4}$  in. along the former to a height of  $\frac{3}{4}$  in. and held between cardboard cheeks. The output from the 50 cycle neon synchroniser should be taken via a 50 pF condenser to form a differentiating circuit. Also, the Mullard ECR35 is stated to be the same as the VCR135. This should be VCR138.—BRUCE F. WALKER (Dundee).

### No. 18 Receiver

SIR,—On looking through February PRACTICAL WIRELESS, I see a further letter on the No. 18 receiver—Mk. III. I have had this excellent little set running for well over six months without any aerial tuning arrangement whatever. The aerial, incidentally, is 50ft. long, being a dipole resonating at 7 Mc/s, fed by a quite unbalanced feeder made from ordinary twin flex.

On seeing Mr. K. Berry's letter, I am hoping that this will not discourage anyone using the 1355 for a vision receiver, because the bandwidth can be brought up to about 3 Mc/s by staggering the I.F. trimming.

Now for the VCR97 or 517 question. Surely these widely differing results with the E.M.T. are due to the age of the tube. I have had no experience with either of these tubes yet but I feel this is the solution to the problem.—R. M. OLIVER (Tolworth).

SIR,—In view of the recent interest shown by the "Readers' Letters" regarding the No. 18, Mark III RX (6.9 Mc/s), here are my attempts at converting this receiver into a three waveband L.M.S. superhet for loudspeaker reception.

The results have proved so pleasing that I thought perhaps they would prove interesting to others.

On the H.F. side of the set I removed the two-gang .00017  $\mu$ F tuning condenser, coils, R.F. and mixer valveholders and replaced them by a two-gang .0005  $\mu$ F tuning condenser; an L.T.C. coil pack Model 30 and a KK32 valve was used as a frequency changer (the R.F. stage being discarded). On the L.F. side the output transformer was removed and the original chassis was extended by means of a small chassis 5in. by 2 $\frac{1}{2}$ in. to accommodate a PM22A output stage.

The set was aligned as recently described in PRACTICAL WIRELESS, and the quality is excellent on medium and long wavebands. Many DX broadcasting stations on the short waveband have been heard, including "All India Radio," "Radio

Australia" and "Radio Canada."—DENNIS E. GATES (Gt. Yarmouth).

### Ex-Service Equipment

SIR,—May I reply to J. Hall (Harrow) and M. Francies (N.W.5). To the former may I say that I am using a VCR97 with 3,000 volts through a 100 K $\Omega$  pot. and in all modesty technical friends have described the results as comparable to a commercial set-up employing magnetic deflection. Furthermore, this may be viewed in daylight.

The circuit line-up is 5 R.F.s. det., Video A, cathode follower, DCR., a two-stage Sync. Sep., Miller frame and line integrators with paraphase amplifiers.

This is no fluke, as two friends have used this line-up with similar results.

To Mr. Francies:

Try EF50 paxolin bases. These produce a perfect fit and the valves seat really beautifully and without all those wire and screw gadgets. These bases were used with confidence on Service gear for frequencies as high as 400 Mc/s, which should speak for itself.

Personally, I discarded the ceramic type a long time ago.—A. S. TORRANCE (W.1).

### Home-made Television Receiver

SIR,—I have read with interest the article concerning the construction of a home-made television receiver in the television supplement of your March issue. I find that I disagree with two statements that you make: (1) the lack of ease and simplicity with which they can be built, and (2) the need for test gear and instruments. I might also mention that I have never built a radio set, the reason for this being that I have no knowledge of radio. But on looking through your pages I saw an advertisement for a kit of parts for a television receiver. I contacted the advertiser and the result was that I purchased a kit of parts price £23 10s. Twenty-eight hours after receiving it I was viewing and hearing the transmission.

That should take care of part 1. As for part 2, the only gear I possessed was an electric soldering iron, a screwdriver, a pair of pliers.

The screwdriver was all that was needed to align the receiver.

There must be many amateurs who, like myself, thought television construction, at home, beyond their skill, but I now have proof every evening that this is not so.

The twenty-eight hours, by the way, were working hours.—J. E. JAMES (S.E.5).

### Home Recording

SIR,—I would like to thank Mr. W. Mackintosh for the letter he sent about home recording. I, too, am very interested in this hobby, but, like the others, I am unable to obtain any sort of gear. I have had some very small success with pick-up recording, but it is nothing like good enough. There are (as Mr. Mackintosh suggested) quite a few of us interested in recording who are stuck because of equipment. Therefore I also would like to see some manufacturer enterprising enough to help us.—H. WOODWARD (Llanhilleth, Mon.).

# Impressions on the Wax

## Review of the Latest Gramophone Records

THE latest addition to Columbia's Masterworks Series is Prokofiev's Symphony No. 5 in B Flat, which has been recorded for the first time in this country by the Philharmonic Symphony Orchestra of New York, conducted by Artur Rodzinski on *Columbia LX1147-51*. The Fifth Symphony is probably better known in America than it is here. It is unsensational, but perhaps it is all the more worthwhile for an absence of excessive window dressing. Though the large orchestra is used very fully, there is little padding.

All Mozart's violin concertos are early works, written at Salzburg in his youth. The Concerto in D Major K.218, which has been recorded on *H.M.V. DB6678-80* is dated 1775, in which year Mozart was 19. It is a buoyant, melodious work, the solo part being played by Jascha Heifetz, ably supported by Sir Thomas Beecham conducting the Royal Philharmonic Orchestra. The interweaving of sound between the orchestra and the purity of the soloist's tone is something that will give the keenest pleasure to every lover of music. The two great names of Heifetz and Beecham have been well served in the recording, which is clear and resonant.

In November, 1946, a new ballet, with music by Lord Berners and choreography by Frederick Ashton, was given at Covent Garden. It was the first ballet score undertaken by Lord Berners since before the war. An early Edwardian extravaganza, "Les Sirènes," transports its audience to the Riviera in 1904; the sirens are the Edwardian ladies in the height of fashion, and the music has all the wit and fantasy associated with the talented composer. "Les Sirènes" is recorded by the Philharmonia Orchestra, conducted by Ernest Irving on *Columbia DX1542*.

Another outstanding orchestral recording is Wagner's "Lohengrin," Prelude, Act I, played by the Philharmonia Orchestra, conducted by Paul Kletzki, on *Columbia LX1153*. "Lohengrin" is built entirely upon one theme, a beautiful one, expressive of the sanctity of the Grail, of which Lohengrin is one of the knights. Violins and flutes open the Prelude with long-drawn-out chords, followed by the Grail Motive in the violins. Some passages in this piece are still quoted in orchestral textbooks as superb examples of light, airy string writings. Though the one theme is used throughout the Prelude, Wagner's skill and invention prevent any feeling of monotony.

### Light Music

Music lovers have, no doubt, welcomed the return of Peter Yorke's "Sweet Serenade" broadcasts. This is the third series of these popular Sunday lunch-time broadcasts. "La Vie en Rose" is the Continental favourite which, with its English title, "Take Me to Your Heart Again," recently swept to song stardom in this country. In his

latest record, Peter Yorke treats it as an orchestral piece. On the reverse is "Heaven in Your Smile," a new British waltz, featuring the singing of Neville Williams, who was heard with Peter Yorke in his "Sweet and Lovely" broadcasts—*Columbia DB2496*.

Harry Davidson and his Orchestra conjure up warm musical memories with two fine interpretations of tunes that were all the rage just before World War I. The novelty piece, "Policeman's Holiday," has been recorded by Mr. Davidson in response to numerous requests. On the reverse is "The King's Waltz," which was written in 1913 by J. H. Greenhalgh, with steps devised by A. E. Brown—*Columbia DX1547*.

Many and varied are the works which George Melachrino selects and arranges for his famous strings. This month he chooses the enchanting "Valse Bluette," by Riccardo Drigo, the Italian composer, who died in 1930. "Valse Bluette," which is often heard as a violin solo, is here for the first time given a string-ensemble setting. It is coupled with an arrangement of "Stardust" on *H.M.V. B9723*.

### Variety

Bill Johnson, whose recordings are becoming increasingly popular, has chosen the ever-popular Irving tune "Always" for his latest recording on *Columbia DB2495*. The coupling is a slow ballad by Eddie Cassen, "I Can't Get You Out of My Mind."

"It's Magic" is a number with a gay lilt, and a slightly beguine tempo. Tony Martin completely enters into the spirit of the lyric, and puts it over in a most persuasive manner on *H.M.V. B9726*. On the reverse is "It's You or No One."

The Geraldo Orchestra, in skilful arrangements by altoist Wally Stott, and featured vocalist Denny Vafghan, give fine performances of four outstanding American tunes. The titles are "On a Slow Boat to China" and "Bouquet of Roses" on *Parlophone F2333*, and "It's Magic" and "Put 'Em in a Box" on *Parlophone F2334*.

"It's a Wonderful World" and "I'd Love to Live in Loveland" are the two titles chosen by that popular combination The Organ, the Dance Band and Me, under the leadership of Billy Thorburn, who plays the piano. The number of the record is *Parlophone F2338*.

Edmundo Ros, popular band-leader at London's exclusive Bagatelle night spot, is undoubtedly Britain's most popular practitioner of genuine Latin-American music. On *Parlophone F2336* he features "Chevere" with a samba coupling, "Manguera." Joe Loss and his Orchestra have four popular titles for their latest discs. They are "Bluebird of Happiness" and "Maybe You'll Be There" on *H.M.V. BD6032*, and "For You" and "I Never Knew an Angel Told Lies" on *H.M.V. BD6033*. His new choral group, The Loss Chords, are featured in these titles.

## CLASSIFIED ADVERTISEMENTS

**RATES:** 3/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

**RADIOS FOR 37/-** (tax paid) special design, short wave; Works off 9v. G.B. for H.T. and U.2. 1.5 v. for L.T. No earth needed, only short aerial. Complete Kit, parts, valve, dried and punched chassis, screws, instructions, etc. Brand New. Sent instantly on receipt of Cheque or P.O.—Supreme Radio, 43, Melbourn St., Stalybridge, Cheshire.

**TELEVISION KITS, Radio Kits and Complete Chassis, Amplifiers, 5-500 watts. Feeder Units. The complete range of Denco Products, including the latest CT7 Turret (with R.F. stage). Also 5 and 10 waveband Gram Chassis covering 330 mc/s. and 150-1500 kc/s. S.A.E. for leaflet of single items, or illustrated catalogue, price 9d. to Masons (PW), Wivenhoe, nr. Colchester.**

**RADIO and electrical bargains—Brand new Garrard and Collaro, etc., recordgram motors—autochangers—record players with amplifiers—radio sets—clocks—irons—radio spares, etc., at bargain prices. Send S.A.E. for list to Radio Bargains, 261, Lichfield Road, Aston, Birmingham.**

**BARGAINS. New Supercio IF Trans. 465 kc/s with vari. iron dust cores, complete easy fixing type at only 9/11 per pair. Meters, MC. 1 m.a. 3 ma., 8 v., 20 v., new and boxed at 5/11 each. RF units, No. 26. 18/11; No. 27. 16/11; post 1/4. Valves, new. 6K7. 7/7. 12A6. 1632. 80, DDT2. 6F8. 12SC7. QP21. 2v.SG. 6SN7. 6SC7. 12CB. 6SH7. 6SK7. VR130/50. 28D7. at 6/9; 12SQ7. 6A7. 25Y5G. 43. at 6/11. Equiv. to KT41. MKT4. PEN 36C. AZ31. 7/3; 25A6. 5U4. 6X5. 6V6. at 7/6; 25L6. 25SN7. KT33C. at 8/6; PEN46. 9/11. C.W.O. post. 9d. extra.—Tiny for Radio. 36A. Dalston Lane, London. E.8 (write or call—Sat. to 7.30 p.m.).**

**RECEIVER, Type 76. Frequency coverage 150-505 kc/s., 3 valves, 1 calibrated tuning dial. £12/6. Receiver, Type 78. Frequency coverage 2.4-13 mc/s. 5 valves with crystal unit, 2 calibrated tuning dials, new in case. £22/6. Signal Generator 196 I.F.F. range: 1 valve V.T. 237. £17/7/6. Modification Units, Type 64. 7 valves. £17/6. Motor Generators input 27v., 16 amp. 4,000 r.p.m., output 60v. 2.5 amp. 150 watt. £12/6. Frequency Meters No. 906. £2/12/6. Receiver No. 1066. £17/6. Receiver No. 966. £1. Radio Voltage Control Panels, 80v., A.C., 6/-. Ferranti Output Test Set, Type 2. £12/6. Indicating Unit Cathode Ray Tube, £1. Master Connector (Precision winding clock movement), 10 pins. Meters, Power Units Type PP/104/4.P75. £1. Send post card for list. C.W.O. carriage paid.—St. Mark's Garage, St. Mark's Street, Bolton, Lancs. 'Phone: 2632.**

**BARGAIN Radio Components. Write for free list.—Barmaper, 1. New Court, Carey Street, London, W.C.2.**

**SALE.—Two 10in. 3-ohm L.S., as new, in rexine-covered baffles for P.A. Or part exchange all-weather short horns.—L. J. Punt, Southminster, Essex.**

**I.F.T.'s—465 7/6 pair; 3 W.B. Coil Pack Kit. 9/6; 1 + 1 + 1 500 v., 6d. 100 PF + 100 PF, 2d.; Eylets, Tags, etc. 1/- gross; 3 amp 820 ohm Dropers. 2/3; Mains Transformers, 16/6; 50 PF Transformers, 4d.; Knobs, 4d.; B.C. Adaptors, 5d. Send for cheapest list in England. Sussex Electronics, Ltd. (P), Riley Road, Brighton, Tel.: 4446.**

**ALUMINIUM chassis and panels. Standard sizes by return, special sizes made promptly. Holes punched for valveholders, etc. Ours or your items finished in Black Crackle or Grey Cellulose. Estimates free. Precision-built coil packs. T.R.F. 12/6. Superhet. 39/6. H.F. stage superhet, £3. Stamp for lists and data sheets. Note new address.—E.A.D., 18, Broad Road, Lower Willingden, Sussex.**

**MOVING COIL Meter. 0-500 microamp. internal resistance. 500 ohms. suitable for building 2,000 ohm per volt; Voltmeter complete with explanatory booklet on multirange testmeter construction and a multi-point switch, 10/-.—Sampson, 78, Lower Addiscombe Road, East Croydon.**

**LISTS now available by return of range surplus low price goods. Oak Cabinets Exits with V.C. 27/6; 5in. IM Units, new. 40/-; Varley and RTS Transformers.—Hudson, 3b, Winner St., Paignton, Devon.**

**WANTED.—Bulgin I.F. Liner. 465 kc/s. 25B8 valve, B.T.S. S.T.800 Coil.—Box 177.**

**ELECTROLYTICS, brand new stock. Dilitic 16mf. 350v. 2/9 ea., 27/- doz.; 32mf 275 v. 2/11 ea. Can 8-16mf. 450v. 4/6 ea., 47/- doz.; 16-32mf. 350v. 5s. ea., 42/- doz. Receiver Chassis, 16 s.w.g. Aluminium 10-51-2ins. 2/3 ea., 11-8-2 1/2in. 3/11 ea., 12-9-2 1/2in. 4/6 ea., 16-8-2 1/2in. 5/6 ea., 20-8-2 1/2in. 6/6. S.T.C. Selenium Rectifiers. 600v. 40 m.a. 4/6 ea., 42/- doz.; 250v. 50m.a. 4/1 ea., 36/- doz.; 90m.a. 5/9 ea., 48/- doz.; 500v. 80m.a. 5/9 ea., 48/- doz.; 120v. Full Wave (not Bridge) 40m.a. 3/6 ea., 30/- doz.; 100m.a. 4/6 ea., 42/- doz. Manganese Vol. Controls. 5meg. with switch standard spindle. 3/9 ea., 40/- doz. Mains Transformers. Standard 220-250v. 50 c/s screened primary. Secs. 350-0-350v. 80m.a. 6.3v. 3a., 5v. 2a. P.M. Speakers, Truvox 8in. 14/9, Rola 10in. 22/9. Ex-Gov. Lines, brand new dry Batteries. 22iv. 1/9 ea., 15/- doz.; R.A.F. Test Buzzers with Morse key and battery, 3/9 ea.; Block Electrolytics, 32mf. 450v. 1/9 ea., 18/- doz.; Unused KTW1 Valves, 5/9 ea., 63/- doz.; 6J5 4/9 ea., 45/- doz.; 6H6 1/6 ea., 12/- doz. C.W.O. or C.O.D. over £1. postage extra. Send 2d. stamp for full list. Trade supplied.—Radio Supply Co., 15, Queen Square, Leeds, 2.**

**BRAND NEW.—R28/ARC5 10-valve 100-150 mc/s. with circuit, 45/-; Receiver 76, 150-505 kc/s, 27/6; BC442A Metered Aerial Relays, 6/-; Creed Highspeed Relays, 21/-; Metal Rectifiers, 600v. 30 m.a. 3/-; 280v. 100 m.a. 5/-; 12v. 4 a. 2/6; Headsets, 100 m.a. 4/6; Variable resistances, 12-ohm 5 amp., 200-ohm .5a. 7/6; Bulkhead insulators, 1/-; Bakelite pulleys, 9d.; Crystals 7010, 6090, 7/6; 5-8 mc/s, 5/-; Condensers, 30 mF. 100v. 1/3; 1 mF. 1,000v., 9d.; 001 mF. 500v., 6d.; 001 mF. 2,200v., 9d.; 25 mF. 500v., 9d.; 3-valve Modulator Units, 15/-; Yaxley's 3-pole 3-way, 3-bank 3/-; 2-pole 11-way, 3/-; 4-pole 2-way, 2/6; Indicator lampholders, 1/3 (MBC); BC433G Control boxes, 7/6; Meters, amps 0-1, 5/-, 0-2, 7/6; Flexible couplers. 1/-; Epicyclic drives, 1/3; Bulgin Twin fuseholders, 1/-; Valves: EB34, SP41, SP61, EA50, 3/-; 6SN7, 6SL7, 5R4GY, EF50, RL37, 6AC7, 5/-; 3in. knobs, 1/-; Push-pull Driver Transformers, 5/6; Transceivers, No. 38, 6-9 mc/s, 65/-; Transformers, 230 input, 20 v. 4A. output, 10/6; R.F. Unit 24, brand new, 15/-; Oil filled Condensers 4mf., 1,000v. w. 4/6, 1mf., 1,500v. w. 2/6; .01mf., 1,000v. w. 9d., Toggles 9d. Callers only: Indicators APN4, type 62, 929A etc. Bendix Receivers, 4 types, SCR523 with A.C. Power Pack, T9/APQ2, BC348, R1155. I.F.T.'s, R1355.—S.a.e. enquiries.—Benson, 308, Rathbone Road, Liverpool, 13.**

## SOUTHERN RADIO'S WIRELESS BARGAINS

Bendix Command Receivers, BC454 and BC455. Frequency 3-6 megs and 6-9.1 megs. Ideal for conversion to car radios and A.C./D.C. receivers. 6 valves, 12SK7 (3), 12SR7 (1), 12A6 (1) and 12K8 (1). Either set 35/-, post 1/6 extra. Control Boxes for BC453, 454 and 455 receivers. Comprising three slow motion dials and drives, 12/6, post 1/-. Drive Adaptors for BC453/4/5 with 1 1/2in. black or 2 1/4 per set, post 3d. Command Receiver Drive Cables, 1 1/2 feet long, 8/6 each, post 6d. Power Packs, input 12v., out 250 at 30 m.a. For car pack for BC453/4/5, 22/- each, carriage 3/-. Inert Cells, 1.5 volts. Ideal for bell batteries, 1t. on small receivers, etc. Require one filling of water for long life. Large size 2/6, small size 2/-, post 6d. Throat Microphones, magnetic, low impedance, 3ft. lead and jack, 3/6, post 6d. Fifteen-foot Copper Aerials in 7 interlocking sections, 4/6 each, post 6d. Contactor Time Switches, by Smiths and Venners, 10-hour movement giving two impulses per sec. Ideal for dark-room work. Brand new in soundproof boxes with thermostat control, 10/-, post 1/4. Lufura Hole Cutters, for use on wood, metal or plastic, adjustable to 3 1/4in. dia., 5/- each, post 6d. Westcott's W.X.6 and W.112; W.X.6—36v. at 100 micro-amps. W.112: 6 volts each side at 250 micro-amps. Either type 6/- per dozen, post 4d. Batteries, M.C.R.1 type, 90v. H.T. and 7 1/2 v. L.T., 6/6, post 9d. Marconi 60 ohm Headsets, brand new with leather headbands, 5/- each, post 6d. Morse Keys, brand new, 1/6 each, post 4d.—Southern Radio Supply, Ltd., 40, Lisie Street, London, W.C.2. GERARD 6653.

**FRITH RADIOCRAFT LTD., Leicester, offer—Super value in bargain parcels. 1. Tag strips, 2, 3 and 4 point, 40 each, total 120 for 5/- + 6d. post. 2. Sleeving 1, 1 1/2 and 2mm., 72 yards assid, colours 5/- + 6d. post. 3. Valve Holders, 8 each B9G (EF50), 4-pin UX and 5-pin Eng., total 24 for 5/- + 6d. post. 4. 1W. Resistors, 10 each 1,500, 2,700, 4,700 10K and 1meg, total 50 for 5/- + 6d. post. 5. 1W. Resistors, 12 each 4,700, 47K, 100K and 680K, total 48 for 5/- + 6d. post. 6. 1W. Resistors, 6 each 33K, 47K, 100K and 1meg, total 24 for 5/- + 6d. post. 7. 2v. Resistors, 6 each 3,300, 22K, 33K and 300K, total 24 for 5/- + 6d. post. 8. Mica Condensers, 8 each .0003, .001 and .01, total 24 for 5/- + 6d. post. 9. Ceramic Condensers, 9 each 6.8, 8, 50 and 75pf, total 36 for 5/- + 6d. post. 10. Component Boards, 12 asstd. comprising over 100 res. and cond. 5/- + 6d. post. 11. RF Chokes, 12 asstd. 5/- + 6d. post. 12. 12in. lengths screwed Brass Rod, 3 each 2, 4 and 6BA, total 9 for 5/- + 6d. post. 13. IF Transformers, 455Kc/s adjustable dust iron cores, pair 5/- + 6d. post. 14. Paper Condensers, 6 each .01/1,500v. (tub), 5/759 (block), 1.0/350 (tub), total 18 for 5/- + 6d. post. All above are brand new. Satisfaction guaranteed or cash refunded without question.—Frith Radiocraft, Ltd., 69/71, Church Gate, Leicester.**

**OLDCHURCH LABORATORIES, Aluminium Panels for the "Ham." All the following in 20 gauge half-hard aluminium—not dural. Mirror-finish both sides. 9 x 12 res., 18 x 12 3/6, 20 x 9 2/6. Also supplied in black crackle finish at 1/6 extra per sq. ft. Headphones: New ex-Govt. req. type phones at 4/9 per pair, 3 prs. 12/-, not many left. E.H.T. Transformers for V.C.R.97, etc., now supplied with two 4v. C.T. secondaries and 2 Kv. winding at 37/6. Send 2d. for our television list. L. P. Dismore, 52c, Oldchurch Road, Chingford, E.4.**

**TELEVISION! TELEVISION!** Television! Still a few Type 6 Indicator Units, complete with VCR97 Tube and all valves, brand new. £3/19/6. Please include 10/6 for strong metal-bound tool box, which is refundable if returned (optional). RX/TV includes all Valves (11) and Rotary Transformer (suitable for conversion to A.C. mains motor). 39/6. Here's a bargain! Control Panel Type IV, contains 2 meters. Yaxley switches, transformers, rectifiers, many condensers, resistances, etc., etc., and 2 6K8G and 2 6K7G valves. 29/6, plus 10/6 for metal-bound tool box. 4 point 4 way Yaxley Type Switch, 1/8 each. 18" amp. Diamond H. Double Pole 10 doz. Switch, 2/- each. 20/- doz. R.A.F. Hand Microphone, 2/- each. 21/- doz. Standard 2 point Telephone Jack Plugs, 1/- each. 8/- doz. G.P.O. 3 point Jack Plug in pairs, 1/6 per pair. 15/- doz. 1/2 Meg and 1 meg Volume Controls, 1/- each. 10/- doz. Heavy Brass 2BA Terminals. 3d. each. 2/6 doz. 3 Position Wave Change Switches. 6d. each. Microphone Transformers, 1/9 each. Miniature Output Transformers, 2/6 each. 24/- doz. Ask for special Condenser List which covers all high or low voltage, receiving, transmitting and television condensers. Con/1, J.B. Slow Motion Drive with Knobs and Dial. to fit standard 1/2 Spindle, 2/9. Do not include extra for carriage. All is free to any address in Great Britain. Send S.A.E. to-day for our latest list.—Walton's Wireless Stores, 203, Staveley Road, Wolverhampton.

**24 hr. TELEVISION (not Radar Conversion).** Uses V.C.R. 97 Tube. Send S.A.E. T.H. PRODUCTS, 92, Leathwaite Rd., S.W.11. BAT. 4889.

**COUPLHON RADIO PRODUCTS.** Standard size Mains Transformers, 250-0-250 v., 60 ma, 6.3 v., 3A, 5 v., 2A, or 4 v., 4A, 4 v. 2A, 15/6, plus 1/- post. and pkg. c.w.o. or c.o.d., from Couplhoun Radio, "The Return of Post Mail Order Service," 58, Derby St., Ormskirk, Lancs.

**3/6 VALVES 3/6**  
Send for our Lists of These and Other Bargains

**Condensers  
Transformers  
Speakers**

Magnifying Lenses Sin. from 25/-  
Magnavista Lens stocked  
(Price List on application)

**Manufacturers and Ex-Government Surpluses**

**DUKE & CO.**  
219, Ilford Lane,  
Ilford E295 Essex  
Mail Order Specialists.  
Trade Enquiries Invited.

Please send S.A.E. for Lists.

**TESTED GOODS.—S/W Tuning**  
Conds. ceramic, 100pf 1/-, 160 pf 1/6;  
Volume Controls from 1/6; Ass. Nuts,  
Bolts, etc. 2/- lb.; Meter Rectifiers 3/6;  
4v. G.B. Batteries, 6d. 3,000 ohm  
Phones, 3/6 pr.; Valves from 1/6.  
List 21d.—Carter's, 67, Bell Lane,  
Marston Green, B'ham.

**REPAIRS to loud-speakers.** Cones,  
coils fitted. Fields altered, rewound.  
Output, transformers, clock coils. No  
mains trans. accepted. Prices  
quoted. Satisfaction guaranteed.—  
L. S. Repair Service, 49, Trinity Rd.,  
Upper Tooting, S.W.17. Closed Satur-  
days. Phone: Balham 3359.

**REWIND SERVICE.**—Armatures,  
Gram. motors, Vacuum Cleaners,  
Drill and all small motor Trans-  
formers—Fields, Pickups, Speakers—  
New Cones and Speech Coils fitted—  
New Vac. Cleaners supplied. All work  
guaranteed and promptly executed.  
Special terms to the Trade. Send  
S.A.E. for Price List and Radio Spares.  
—A. D. S. Co., 261-3-5, Lichfield Road,  
Aston, Birmingham. 6.

**THE WONDERFUL NEW A.C. MIXED AUTOCHANGER** by Collaro, finished in brown and chrom. with super crystal pick-up—our special introductory offer only £14 incl. tax, carr. pd. Collaro induction type AC gram. motor with variable speed and 12in. t.t.—£5. No. 3 Collaro RP49 complete Radio-gram Unit, with autostop and latest type magnetic pick-up. £5/14/8. No. 4 ditto (but induction type, with 12in. t.t.). £9. No. 5, as No. 4, but for A.C./D.C. operation. £12/18/9. Exhaustive Constructional Manuals, enabling even beginners to build fully professional standard radio sets: No. 1, 3-valve plus rect., T.R.F. L. & M. waves for A.C. operation, 3/-; No. 2, as No. 1, but A.C./D.C. 3/-; No. 3, 5-valve All-wave Superhet of extreme power and range, A.C. 5/-; No. 4 as No. 3, but A.C./D.C. 5/-. Complete Kits of Parts (incl. valves and speaker) to build above circuits: T.R.F., complete with very attractive moulded bakelite cabinet and illuminated glass dial, A.C. or A.C./D.C., £7/17/6. Superhet. less cabinet, A.C. £9/12/6. A.C./D.C. £8/12/6, figured walnut cabinets available. The Lee Products All-dry Battery Kit, complete (except cabinet), £7. The Mighty Midget Radio—3 valve plus rect., A.C./D.C., 200-500 metres, high "Q" coils, 5in. speaker, polished walnut cabinet, built ready to switch on, 12 months' guarantee, sensational bargain at £6/19/9, incl. p.t. (carr. 2/6). money back if not delighted. The N.R.S. Audio Amplifier, 4-watts output, pick-up and 6 inputs, volume, tone and negative feedback controls. A.C. 110/250 v., special offer, £5/19/6. ex-Gov. 6J5 and L 63 valves, 3/6 each. 6 for 18/-, Osmor Coil Packs, 33/-. Send 21d. for Bargain List of Kits, Amplifiers and components. Terms: c.w.o. or c.o.d. N.R.S., 102, Parkhill Road, London, N.W.3. Tele.: Gulliver 1453.

**TELEVISION chassis and components** of the highest quality, ready for assembly to Electronic Engineering specification. S.A.E. for list.—Gomor Radio Products, Ltd., Borough Hill, Croydon, Surrey.

**12v. CHARGING SWITCHBOARDS.** 12v./32v., 500 to 1,260 watts, volts, amps, cut-outs, fuses, resistances, etc., 4 take-offs, superb unit, in case; or send £5 carr. pd. 75/-. DYNAMOS, 24 volts, 1,000 watts, 12in x 7in., 1/2in. spindle; 80/- carriage paid. 75/-. 230v./150, 1/5 h.p. ELECTRIC MOTORS, 80/- carr. pd.

**58/- MAINS TRANSFORMER SWITCHBOARDS.** 230v., A.C. to 12v., 5 separate take-offs, complete distribution panel, all switches, fuses, amps, etc., brand new; 60/- carr. pd. 55/-. ELECTRIC MOTORS, 12v. and 24v., 1/4 h.p., 4in. by 8in., with 1in. spindle for drive, beautiful job; 60/- carr. pd. 70/- Reduction-gearred ELECTRIC MOTORS, 24v., 1/10 h.p., 2-stage, enclosed 2 r.p.m., superb precision instrument.

**45/- DYNAMOTOR UNITS,** containing 14v., 28v., 130v. and 300v. D.C. dynamo or suitable as 6v., 12v. or 24v. motor, approx. 1/4 h.p., 11in. by 5in., with spindle to take small grindstone, mop, etc., also contain adjustable 24v. cut-out, 12v. automatic voltage control, smoothing condenser, resistances, etc., with 210 230 D.C. mains in the 300 D.C. makes 12v. Battery Charger, at the 14v. output, 4 amps, 50/- carriage paid.

**ROTARY CONVERTERS,** from 1-12 kW, 110v. and 220v. D.C.—230v./150. from £15. MOTOR GENERATORS, 1-6 kW., 110v. and 220v. D.C.—24v./35v. D.C. from £9. MAINS TRANS., 1-18 kva.; all types, from £5-£59. BENMOTORS POWER SUPPLIES, Summerley Street, Earlsfield, S.W.18. WIM. 3833 (100 vds. S. Ry. Electric Line; 10 minutes Waterloo).

**RAYMAX Television Sound Unit,** complete kit, uses 2, EF90, EBC33, EL33. Chassis punched and main components assembled. Price (less valves) £2 17s. 6d. Valves supplied at current prices. We specialise in supplying kits for all circuits shown in PRACTICAL WIRELESS and Techni-Gen Series, and all well known amateur booklets. Full details of the above and our Home Constructors Service are given in our general list. Push-pull intervalve Transformers, ratio 3:1 each half, 3/- ea. Collaro rind driven Gram unit, magnetic PU and autostop, £5 18s. 6d. incl. tax. Inter. Octal moulded V.H. 7/- doz. Flying Tuning Kits, 33-1, comprising flywheel, 4in. drum, ball bearing drive spindle, cord and spring, 3/9 ea. All types of components available ex stock, including cabinets for TV and table radiograms. Our Console TV Cabinet at £19 15s. 0d. is worth looking into. Good photographs of cabinets available at 6d. (returnable). Record Player Cases finished in black rexine, complete with motor board, carrying handle, etc., size 16in. x 15in. x 8in., a bargain at £3 2s. 6d., or complete with Garrard motor, PU, etc., £8 7s. 6d. Stamp for bargain and general lists. Raymax Elec. Co., Ltd., 126, Norwood Road, S.E.24.

**RF UNITS TYPE, 24,** and 24 mod. 27, 8/6 ea., plus 1/3 postage. Type 25, 12/6. Type 26 and 27 at 21/9 ea., plus postage 1/3. Indicator Units: Most types available. See our lists. IF Transformers, all in can with trimmers, 465 kc/s std., 9/- pr.; 200 kc/s midget stud. 8/- pr.; 13 mc/s std. and 14-16 mc/s std., 7/- pr. Special: 16 mc/s IF contains 6st-tuned, ideal for TV use or rewinds, 2/6 ea. or 5 for 10/-. M.C.R.I. coils, type 2, 3 and 4, 10/- ea.; 20pf ceramic variables, complete with metal bracket and ins bush, 2/6 ea. Resistor and condenser panels, 34 rs and cs, plus 3 Westectors, as new, 5/-. Phone plugs, 9d. One-hole jacks, 1/3, or with switch contacts, 2/-; R 1124 receivers, 10/6. TV sound, including 6 valves, 17/6, plus 2/6 carr. Assorted coloured knobs, 2/- doz. Panel lamps, clear 1/-; red or green, 1/6 ea. Set of 7 UHF coils, dust-tuned, 3-80 meters, 5/-. Six UHF HF and SW chokes, all different, 3/-. Uni-selector switches, 25 w 8 b, 45/- ea. H.R.O. Senior, £20. S27 AM-FM., £30. R.C.A. crystal wavemeters, 200 kc/s, 20 mc/s, £6/10/- ea. SEE OUR LIST FOR DETAILS. Phones, L.R. 3/6 pr.; Ideal Arm type, 5/- pr. Moving coil, 10/6 pr. Voltmeters, 0-40 v., 4/6; 20-0-20 a, 4/6; 50-0-50 a, 4/6. Cell testers by Turner, 3-0-3 v. and 30-0-30 v., 3in. scale, 12/6 ea. VALVES, guaranteed, 95s. 956. 6SN7, VP41, 10/- ea.; EF90, EF36, EBC33, 12A6, 6J5, 9D2, 15D2, 8D2, 4D1, all at 5/- ea. Hundreds of others. See our lists. S.A.E. please H. English, Rayleigh Rd., Hutton, Brentwood, Essex.

**MERCHANT NAVY AND AIR RADIO.** Here is an opportunity to train as Radio Officer for merchant ships and the air. The big liners are open to you, but you must first qualify for the P.M.G. Certificate. Established 30 years. We can put you through in the minimum time. Day, evening and postal instruction. Prospectus from Director, The Wireless School, 21, Manor Gardens, Holloway, London, N.7. ARC. 3694.

**RADIO OR RADAR.**—Full-time training for career in Air or Marine Services as Radio Officer (M.C.A. or P.M.G. Licences). Radio Mechanic or Radio Engineer. Residential and non-residential courses at Radio and Radar Schools, Britain's Air University. Enquiries to the Commandant, Air Service Training, Hamble, Southampton.

## For the utmost realism from records and radio

### The K.J. Amplifier




This seven valve amplifier, especially designed for the lightweight high fidelity type pick-up, is proving the real answer for the music lover who seeks a high standard of reproduction at a moderate cost. Independent bass and treble controls permit compensation for recording losses and reduce needle scratch. Tetrodes with negative feedback ensure negligible distortion and the high performance is backed by a two years' guarantee. Price complete 17 Gns., or in kit form 13 Gns. The blueprint is available separately, 2/6d. Deferred terms available.

*Charles*  
**AMPLIFIERS**  
LTD

"LIVING MUSIC"  
Our illustrated catalogue of amplifiers and tuning units will interest all music lovers. Write enclosing 5d. in stamps.

1N, PALACE GATE, KENSINGTON, LONDON, W.8  
Phone: WEstern 3350. Our equipment can also be seen and heard at  
UNIVERSITY RECORDING COMPANY  
16, Burtleigh Place, Cambridge Phone: Cambridge 54947

## Compact-Efficient

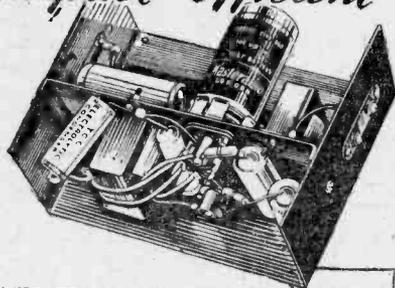

This "VIBRATOR PACK" developed by Specialists will enable users of battery sets to operate from a 6-volt car accumulator thus eliminating expensive H.T. battery replacements. Careful design has eliminated all interference. Consumption is less than  $\frac{1}{2}$  amp. Also Television and Domestic sets.

SMALLER  
than a H.T.  
Battery  
Size  
7 x 5  $\frac{1}{2}$  x 3



## Masteradio REGD. VIBRATOR PACK

MASTERADIO LTD., SALES DEPARTMENT,  
319/321, Euston Rd., London, N.W.1

**DUBOIS TRI-PLUS**  
ACTIVATED RESIN CORED SOLDER

FOR USE IN THE HOME

FOR THE SERVICE ENGINEER AND WORKSHOP

6 PER REEL

SIMPLIFIES ALL SOLDERING NO EXTRA FLUX REQUIRED

Packed in  $\frac{1}{2}$  gross display cartons. Retail price 6d. per reel. Large reels for your Service Department, etc.

## The Superior Cored Solder

Sole Manufacturers—**The DUBOIS CO. Ltd.**  
15, BRITANNIA STREET, KINGS CROSS, LONDON, W.C.1  
TELEPHONE: Terminus 6624/5. TELEGRAMS: BLEITRAP, KINCROSS, LONDON

## TELEVISION COMPONENTS

### For "A Modern Home-built Televisor"

**TELEVISOR MANUAL** (Third Edition) by Electronic Engineering, 2/9 post free. This manual contains full details of how to build a modern televisor of sound design with all circuits, layout and photographic illustrations.

**VISION PANELS.**—Brand new units to specification in above manual, containing 6 ceramic B9G valveholders, two diode valveholders, coil forms with adjustable slugs and interstage screens. Complete in aluminium box 15in. x 3 1/2in. x 1 1/2in. Ready to wire. 22/6.

**SOUND PANELS.**—As above but containing 2 ceramic B9G and one amphenol octal valveholder, interstage screens, three coil forms with adjustable slugs. Ready to wire. 18/9.

**TIME BASE PANEL.**—To specification in above manual. Aluminium chassis 15in. x 6in. x 3 1/2in., with all holes drilled and fitted with 2 ceramic B9G and 4 amphenol octal valveholders. 17/6.

**POWER UNIT PANEL.**—To specification. Aluminium chassis 15in. x 1 1/2in. x 3 1/2in., drilled and fitted with 2 amphenol octal valveholders, one high voltage 5-pin valveholder, 2 single and 2 three-way sockets. 25/6.

**GANTREYS AND STRAITS.**—Complete set, 10/-. The above units, etc., eliminate all the hard work in drilling and making the metal work for the Home-built Televisor.

**COIL FORMS WITH ADJUSTABLE SLUG.**—Alladdin, 10d. Set of 8 coils, ready wound. 15/6.

**E.I.T. TRANSFORMERS.**—Primary 210, 230 or 250 v. H.T., 4,000 v. L.T., 2 or 4 v. at 2a., 72/6.

**H.T. TRANSFORMERS.**—350-0-350 v. 250 mA., 6.3 v. 6 a., 4 v. 8 a., 0-2-6.3 v. 2 a., 4 v. 3 a., 25/5s.

**SMOOTHING CHOKES.**—5 h. 250 mA., 27/-; 10 h. 80 mA., 18/6.

**SCANNING COILS.**—Line and frame scanning coils, 32/6.

**LINE OUTPUT TRANSFORMER.**—32/6.

**FOCUS COIL.**—Focus coil assembly, 32/6.

**CONDENSERS.**—T.C.C. CE5890 0.1 mfd. 6,000 v., 15/-.

Micadisc 500 pF. 2/6. 8 mfd. 450 v. CP19. 4.6. 16 mfd. 350 v. CE26L.

4/9. 30 mfd. 350 v. CE29L. 6/6. 32 mfd. 450 v. CE37F. 10/-. Other condensers also in stock.

**POTENTIOMETERS.**—Morrantite Linear 250,000 ohms with switch. 6/6. Semi-log 250,000 without switch, 4/6. Colvern 3 watt wirewound 2,000, 2,500, 5,000 and 10,000 ohms, 5/6 each.

Colvern 3 watt wirewound 100,000 ohms, 6/7.

Postage extra on orders under £2. Television list free.

**SOUTHERN RADIO AND ELECTRICAL SUPPLIES**  
85, FISHERTON STREET, SALISBURY, WILTS.  
Telephone: Salisbury 2108.

# Practical Television

Vol. 1. No. 2

NEW SERIES

April, 1949

## Television Standards Agreement

**A** RECENT announcement by the Radio Industry Council states that four leading manufacturers in Britain and Holland have agreed on television standards for use of the Continent of Europe. The four firms are Philips of Eindhoven, G.E.C., Marconi, and Pye, who have jointly agreed to standardise equipment for the Continent on 625 line picture definition and also on positive modulation for the vision signal. The latter is already in use in Great Britain, with 405 line definition, and in France, where a system of 819 lines is projected. In the United States of America, however, negative modulation is used extensively, and the Dutch had proposed to use it before the present agreement was reached.

Other technical standards agreed upon are 25 frames per second with a 2-1 interlace, vestigial side-band operation, and a total channel width of 6 megacycles. No recommendation has been made for the method of modulating the sound signal. It was originally announced that five firms had subscribed to this agreement, but the fifth—E.M.I.—later denied that they had taken part in the joint consultations which led up to the agreement. They state they are able to supply television transmitting equipment for any and all practicable standards, including the B.B.C. standard of 405 lines, the American standard of 525 lines, the new E.M.I. standard of 605 lines, and also for 625 lines or more when such are required.

One of the leading radio industrialists, who recently returned from Holland, expressed the view that the agreement on positive modulation is of vital importance and very satisfactory from the point of view of the British manufacturer. And, of course, it is obvious that if negative modulation had been adopted on the Continent the manufacture of

sets with different forms of modulation for the home and foreign markets would have created a number of difficulties for British manufacturers, not the least of which is that, with a comparatively small demand as yet, costs would be high.

The British television industry has also been in favour of adopting its own 405 line system with positive modulation as the standard for Europe, and its view has not changed that it is still the most efficient system in relation to costs and to ether space occupied.

It has become increasingly apparent, however, that some of the European countries wished to take advantage of Britain's vast and unique experience of television in all its aspects, including studio and transmission technique, as well as receiver manufacture, whilst at the same time demanding a line definition nearer to or above the American system.

Uniformity on the Continent, especially with the British system of modulation, is of greater value than the partial acceptance of 405 lines, although the 405 line system will continue to be used and extended in Great Britain.

Sweden and Germany already favour the 625 line definition, which is higher than is used in the U.S.A. Television development work is recommencing in Sweden and Germany, and it is thought that other Scandinavian countries, as well as Belgium and Switzerland, are in favour of the 625 line system; for apart from the great advantage of being able to exchange programmes, and so sharing in the major cost of television, they would also benefit by economies in the manufacture of transmitters and receivers as a result of the standardisation now agreed.

British manufacturers state that they will at once commence production of sets suitable for export to the Continent.

### Examinations in Television Servicing

The Department of Technology of the City and Guilds of London Institute announce details of a new examination in the servicing of television receivers which has been drawn up and adopted by the City and Guilds of London Institute and the Radio Trades Examination Board. Full details are available from the Institute at 31, Brechin Place, South Kensington, London, S.W.7.

The first examination under this scheme will be held in 1950, and arrangements are similar to those for the Radio Servicing Certificate Examination, which is also jointly conducted by the City and Guilds of London Institute and the Radio Trades Examination Board.

The syllabus has been based on the assumption that, before commencing to study television, students will have a good knowledge of the basic principles of radio and be proficient in the servicing of radio equipment for sound reproduction. The course of study recommended covers a period of two years, with attendance on two evenings per week, or the equivalent if part-time or day-time classes are available. It is considered essential that at least 50 per cent. of the time should be devoted to laboratory work and practical servicing, and it is pointed out that a large amount of no-signal testing of television receivers is both practicable and desirable. Candidates must prove that they have passed the Radio Servicing Certificate Examination, the examination in radio servicing held by the Radio Trades Examination Board from 1944-1946, the C.G.I. Examination in Radio Work, the examination of the B.I.R.E., or of the Scottish Radio Relays Association, or the third year examination of the Union of Lancashire and Cheshire Institutes.

(See also leader on page 131)

# Underneath the Dipole

Television Pick-ups and Reflections. By "THE SCANNER"

**M**ORALE is high at the Alexandra Palace. In spite of the frustrations which afflict us all, and which seem to have especially retarded some aspects of the technical progress of British television, the development of the production side proceeds apace. There have been a few resignations from the television staff, true enough; but the majority carry on the good work in the magic atmosphere which is bound to surround an entirely new form of entertainment. The novelty of the medium, the pioneering and artistic experiments, the fuss about it in the Press—even the necessity for daily improvisation—build up a glamour about the job reminiscent of the earliest days of "blind radio."

From which you will gather that I have formed a very high opinion of Norman Collins and his production and engineering staffs at the Alexandra Palace. Nightly they accomplish that miracle of "independent frame," a couple of hours of entertainment produced on two small studio stages which would be considered inadequate for making a six-week "quota quickie" lasting 50 minutes on a cinema screen.

## Creative Nonsense

It is fortunate that the A.P. production boys all take a very active interest in the technical side of their craft. This is unlike their equivalents in the film studios, who tend more and more to adopt a lofty attitude to the mundane matters of the tools which fashion the job. A leading authority stated recently: "The average director, cameraman, script writer, editor, proudly claims to be an artiste, not a technician—he takes pride in his ignorance of technical matters. To him the term creative is the exact opposite of technical." It is small wonder that British films are experiencing another slump if this attitude is general in British studios. But I must admit that I myself have been to meetings of the British Kinematograph Society at which important technical developments have been disclosed—notably in connection

with lenses—and the audience has comprised a far larger number of television people than it has film personnel. At one meeting, dealing with the Taylor, Taylor Hobson lens and the new "transmission" system of calibrating (which will ultimately replace the long established "F" system) there was but one cameraman present.

## Apathy

Mind you, this apathy, laziness or call it what you will, is not confined to the technical side of the business. Meetings of technical societies and of trade unions are equally ignored, thus delivering the latter safely into the hands of the cranks, crack-pots and bobby-soxers. Fortunately the technical societies have no particular attraction for the fifth-column element in our midst. At least, not yet! Behind the iron curtain there is even a party line on every biological axiom, and no Communist will admit to you that the foal of a Derby winner will ever win a Derby! No wonder such imbeciles have become known as "Red Nazis." Let us hope that Norman Collins keeps them away from the Alexandra Palace, even if he can't do anything about that Third Programme.

## Propaganda

The television newsreel has now acquired a sure editorial touch, and has tackled this "Red" angle in a subtle way. For instance, scenes from a recent grand military parade in the Red Square at Moscow (reminiscent of Hitler's parades) were followed immediately by carnival parades and battles of flowers in Hollywood, thus effectively contrasting evil and good. Musical background and commentary forcefully drove the point home.

## Newsreel Music

Incidentally, I think that the music used on the television newsreel is pretty good, don't you? After a time, it does become rather familiar, however, and one comes to expect a certain Finkel-like intermezzo on every skiing story (of which there seem to be

many) and a specially heavy "dramatic melo" on earthquake and fire scenes. Shots of the Royal Family have their special tunes, of course, which are used impartially on the launching of battleships or laying of foundation stones. Then there's a nice little light tune which seems to be handy for bicycle races, skating or the old crooks run to Brighton, while a first-class piece of "hurry-music" does duty equally well for horse racing or car hill-climbs. Please don't think I am trying to run down the practice of using "stock" pieces of background music on the television newsreel. As a matter of fact, I am all in favour of it. Cinema newsreels, please copy!

## 16 mm. Competition

Just before the war there started a development of the 16 mm. cinema field in parts of the country not well served with normal films. Country districts which were unable to support full-sized cinemas in their small towns and villages welcomed the visits to their village halls of mobile 16mm. film shows. Both American and British film distributors became interested, and sub-standard copies of the biggest films were printed a few months after the films had finished their run on the normal 35 mm. theatres. Slowly but surely the business grew, and there are now many towns and villages which receive a weekly or even bi-weekly visit from the modern version of the itinerant showman. A few of the more successful village shows have even gone so far as to be fitted up with genuine tip-up seats! Alas! Mobile cinema exhibitors in the Home Counties fear that B.B.C. television may put them out of business. During the last few months there has been a marked drop in attendance at these 16 mm. shows in the areas near London, and it has been found that many of the regular patrons have now purchased television sets and stay at home. To make matters worse, those who haven't got sets are invited to the houses of friends who have. I must say that you can't blame

a person for wishing to stay in a comfortable arm-chair watching his home-screen in preference to going out into the night to a none-too-warm village hall to sit on a none-too-soft wooden seat looking at a none-too-new cowboy film.

**Competition**

Where will the competition of television lead? In certain towns of the U.S.A. there is

already a choice of half a dozen television stations transmitting simultaneously, and what the American programmes (for the moment) lack in quality they make up in quantity and alternative choices. It is no wonder that the American television craze has lowered the cinema takings in some cities by as much as 40 per cent. This is, of course, catastrophic.

Curiously enough, the atten-

dances at "live" shows have not suffered to anything like the same extent. My forecast is that in England the competition of television will be felt by the entertainment industry to a much less extent, particularly the music-hall and theatre. The fact is that the public will tend to become satiated with mechanised entertainment and there will be re-created a desire to patronise "live" talent.

# Trade Notes

**New Mullard Receiver**

**MULLARD ELECTRONIC PRODUCTS, LTD.**, announce the release of a table model Television Receiver.

Known as the M.T.S. 389, the new set embodies the very latest developments. It is housed in a well-designed walnut cabinet 17in. high, 25½in. wide and 13in. deep (plus a 2in. projection at the back of the cabinet to take the end of the cathode-ray tube).

The M.T.S. 389 has a 9in. tube giving a clear, well-defined black and white picture that can be viewed with ease in normal room lighting. Due to the incorporation of special limiter circuits, exceptional freedom from external interferences on sound and vision channels is experienced.

The price of the new receiver is 48 guineas, plus £11 6s. 5d. Purchase Tax. Total £61 14s. 5d.

**Magnavista Television Lenses**

**DEVELOPED** by Metro Pex, Ltd., pioneers in television lens design, the Magnavista Lens is now available for use with all types of television receiver. Magnifying the original image two and a half times, these lenses are guaranteed against discolouration. They can be supplied for fixing direct to the receiver or with a patented telescopic stand which enables the lens to be stood on the table directly in front of the receiver and adjusted instantly to the correct height whatever the distance between the screen and the base of the set.

Magnavista Lenses are stocked by all the leading dealers in sizes suitable for makers' standard 9in. tubes and 10in. tubes


respectively, at prices ranging from 6 guineas to 8½ guineas.

Enquiries should be sent to Metro Pex, Ltd., 71, Queens Road, Peckham.

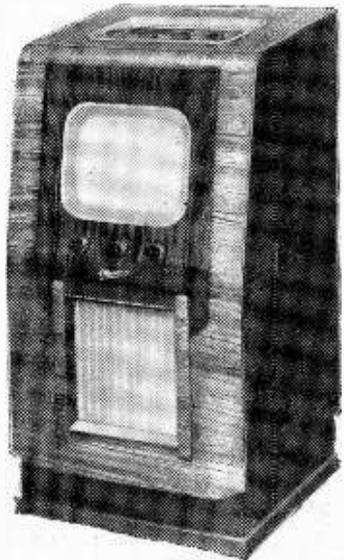
**"His Master's Voice"—Model 1805—19-Valve Television Console**

**GIVING** a picture 8½in. by 6½in. approximately, specially designed T.R.F. circuits are employed for both sound and vision channels. The former incorporates a pre-set sound sensitivity control—enabling the level of the sound signal to be adjusted to suit reception strength in a particular area—and a special envelope follower automatic inter-

ference suppressor. Interlocking of the brightness and contrast controls eliminates the necessity for re-setting the brightness



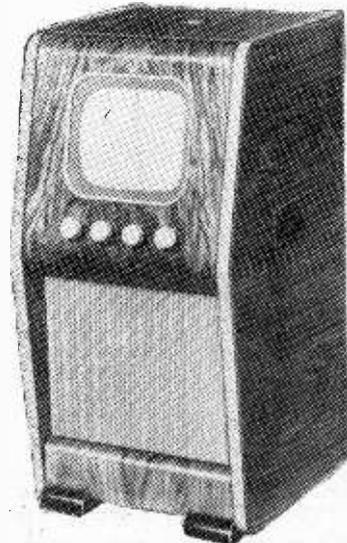*Marconiphone latest combined radio and television receiver, Model VRC52A.*



*The new H.M.V. Model 1805.*

control when the contrast is varied over normal operating amounts. The 10in. Emiscope tube is of special design and gives a degree of brightness far above that of the ordinary tube.

Total mains consumption is 200 watts, and the sound output 5 watts maximum.

**Keep Waste Paper Separate For SALVAGE**

# A New Sync. Separator

A 3-valve Circuit Which Provides Accurate Interlacing

**M**ANY experts hold that the sync separator is the most important part of the modern television receiver, and although it may be open to argument there is no doubt that unless perfect interlacing is obtained the best will not be seen of the television transmission. As most readers know the function of the synchronising circuits is to pick out the frame and line sync pulses and pass them to the respective time bases. No trace of picture impulses should be carried into these parts of the circuits, and the pulses themselves must be separated from one another. Various schemes have been recommended from time to time and claims have been made as to their efficiency. We have tried quite a number, but one of the most reliable yet tested is that shown below and which is recommended by Haynes Radio. As will be seen it employs 4 valves, two of these being diodes and contained in one envelope. The input design has one very great advantage over many devices which are in use, namely, it may be used with any type of video stage. Some sync separators must

have a positive input and others a negative, but by simply taking the signal to grid or cathode this circuit may be used with practically all modern video stages. As shown (with input to grid) it has been used by us connected to the cathode of the video stage, the tube being cathode modulated from the video anode in the usual way. The positive-going pulses at the anode of the first valve are taken to one section of the double-diode triode and the other section of this valve feeds the frame time base, being itself fed from the limiter valve. The arrangement is fairly flexible and none of the components has been found very critical, although the limiter can give erratic results if certain of the components are faulty. For instance, a leaky screen-grid decoupling condenser will give rise to erratic frame pulses, and feed-back from the line time base will be experienced if the 100 pF coupling condenser is leaky. In this connection the resistor in series with it may also prove critical. But speaking generally, it has been found to give the best results yet in our experimental equipment, giving a per-

fect interlace, perfect locking over a reasonably wide adjustment of the frequency controls, and permitting adjustment of amplitude in both directions without upsetting other controls (over the normal ranges of adjustment).

## Time Bases

The unit may be made very compact, the 6H6 being one of the very small American-type valves, and by using a KT81 for the limiter (also a small valve) the unit could be made small enough to tuck away in an existing set and probably replace the existing arrangement. The Haynes time bases which are recommended for use with this circuit are of the type designed for a total H.T. supply of less than 300 volts, frame and line output transformers having been done away with. Further details may be found in the Haynes Technical Publication No. 29. Choke feed is employed for the line and frame deflector coils. These circuits too are simple to make up and very efficient in operation.


## Technical Tips

**R**EMEMBER that the line output stage develops very high fly-back voltages and can be more dangerous than the EHT supply. Do not attempt to measure the voltage on the anode of the line amplifier.

**A**VOID laying out a home-built television receiver in such a manner that large transformers or chokes come near the picture tube. The scanning beam is easily deflected by external magnetic fields.

**P**LASTIC effects can be obtained in some cases by using a large by-pass condenser across the video cathode resistor and can give added detail to the picture. This is merely an artificial aid and must not be overdone and it is better, if possible, to improve the band-width of the vision receiver.

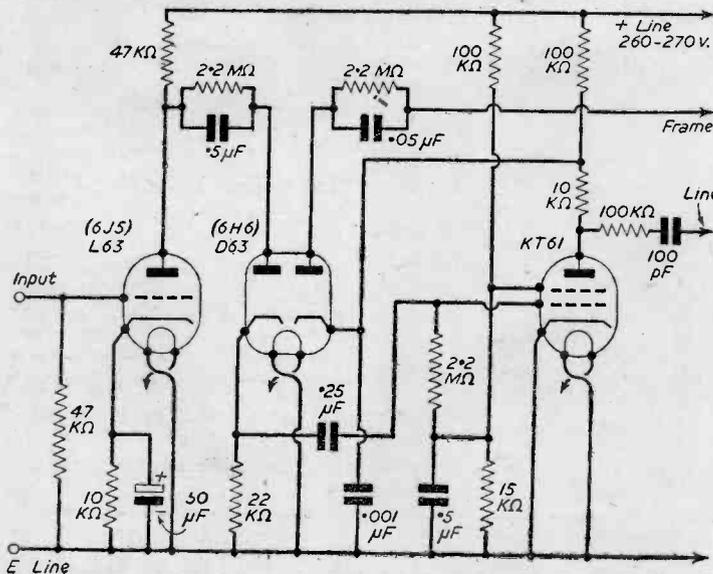**D**EFOCUSING can be caused by a focus coil getting hot during the programme time. This may be due to the presence of large power-type valves near it, or to bad ventilation. So make sure there is plenty of air circulation at this part of the equipment.



The circuit of the sync and limiter stages.

# Practical Wireless BLUEPRINT SERVICE

## SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*. Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

### PRACTICAL WIRELESS

No. of  
Blueprint

F. J. Camm's A.C. Superhet 4 .. PW59  
F. J. Camm's Universal 24 Super .. PW60  
"Qualitone" Universal Four .. PW73

### CRYSTAL SETS

Blueprints, 1s. each.  
1937 Crystal Receiver .. PW71\*  
The "Junior" Crystal Set .. PW94\*

### STRAIGHT SETS. Battery Operated

One-Valve: Blueprints, 2s. each.  
All-Wave Outpin (Pendulo) .. PW31A  
Beginners' One-valve .. PW85  
The "Pyramid" One-valve (HF Pen) .. PW93\*  
Two-valve: Blueprints, 2s.  
The Signal Two (D & I F) .. PW76\*  
Three-valve: Blueprints, 2s. each.  
Selectone Battery Three (D, 2 LF (Trans)) .. PW10  
Summit Three (HF Pen, D, Pen) .. PW37\*  
Half-Mark Carlet (D, LF, Pen (RC)) .. PW48\*  
F. J. Camm's Silver Souvenir (HF Pen, D (Pen), Pen) (All-Wave Three) .. PW49\*  
Cameo Midget Three (D, 2 LF (Trans)) .. PW51\*  
1936 Sonotone Three-Four (HF Pen, HF Pen, Westector, Pen) .. PW53\*  
Battery All-Wave Three (D, 2 LF (RC)) .. PW55\*  
The Monitor (HF Pen, D, Pen) .. PW61\*

The "Colt" All-Wave Three (D, 2 LF (RC & Trans)) .. PW72\*  
The "Raggle" Straight 3 (D, 2 LF (RC & Trans)) .. PW82\*  
F. J. Camm's Oracle All-Wave Three (HF, Det, Pen) .. PW78  
1938 "Triumph" All-Wave Three (HF Pen, D, Pen) .. PW84\*  
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) .. PW57\*  
The "Hurricane" All-Wave Three (SG, D, Pen, Pen) .. PW39\*  
F. J. Camm's "Push-Button" Three (HF Pen, D (Pen), Tet) .. PW92\*  
Four-valve: Blueprints, 2s. each.  
Beta Universal Four (SG, D, LF (C, B)) .. PW17\*  
Nucleon Class B Four (SG, D (SG), LF, C, B) .. PW34B  
Fury Four Super (SG, SG, D, Pen) .. PW34C  
Battery Half-Mark 4 (HF Pen, D, Push-Pull) .. PW46\*  
"Aqua" All-Wave 4 (HF Pen, D (Pen), LF, C, B) .. PW32\*  
The "Admiral" Four (HF Pen, HF Pen, D, Pen (RC)) .. PW96\*

### Mains Operated

Two-valve: Blueprints, 2s. each.  
Selectone A.C. Radiogram Two (D, Pen) .. PW19\*  
Three-valve: Blueprints, 2s. each.  
Double-Diode-Triode Three (HF Pen, DDT, Pen) .. PW23\*  
D.C. Ace (SG, D, Pen) .. PW29  
A.C. Three (SG, D, Pen) .. PW35C\*  
A.C. Leader (HF Pen, D, Pen) .. PW35B\*  
D.C. Premier (HF Pen, D, Pen) .. PW36A\*  
Ubuque (HF Pen, D (Pen), Pen) .. PW50  
F. J. Camm's A.C. All-Wave Silver Souvenir Three (HF Pen, D, Pen) .. PW54\*  
"All-Wave" A.C. Three (D, 2 LF (RC)) .. PW56\*  
A.C. 1936 Sonotone (HF Pen, HF Pen, Westector, Pen) .. PW70\*  
Four-valve: Blueprints, 2s. each.  
A.C. Fury Four (SG, SG, LF, Pen) .. PW20\*  
A.C. Fury Four Super (SG, SG, D, Pen) .. PW34D  
A.C. Half-Mark (HF Pen, D, Push-Pull) .. PW45\*  
Universal Half-Mark (HF Pen, D, Push-Pull) .. PW47\*

### SUPERHETS

Battery Sets: Blueprints, 2s. each.  
66 Superhet (Three-valve) .. PW40  
F. J. Camm's 2-valve Superhet .. PW52\*  
Mains Sets: Blueprints, 2s. each.  
A.C. 25 Superhet (Three-valve) .. PW43  
E.C. 23 Superhet (Three-valve) .. PW42\*

### SHORT-WAVE SETS. Battery Operated

One-valve: Blueprint, 2s.  
Simple S.W. One-valve .. PW88\*  
Two-valve: Blueprints, 2s. each.  
Midget short-wave Two (D, Pen) .. PW38A\*  
The "Kleet" Short-wave Two (D (HF Pen), Pen) .. PW91\*  
Three-valve: Blueprints, 2s. each.  
Experimenter's Short-wave Three (SG, D, Pen) .. PW30A\*  
The Perfect 3 (D, 2 LF (RC and Trans)) .. PW62\*  
The Band-spread S.W. Three (HF Pen, D (Pen), Pen) .. PW68\*

### PORTABLES

Three-valve: Blueprints, 2s. each.  
F. J. Camm's "L.P." Three-valve Portable (HF Pen, D, Pen) .. PW65  
Parvo Flyweight Midget Portable (SG, D, Pen) .. PW77  
Four-valve: Blueprint, 2s.  
"Imp" Portable 4 (D, LF, LF, Pen) .. PW86\*

### MISCELLANEOUS

Blueprint, 2s.  
S.W. Converter-Adapter (1 valve) .. PW48A\*

### AMATEUR WIRELESS AND WIRELESS MAGAZINE CRYSTAL SETS

Blueprints, 1s. each.  
Four-station Crystal Set .. AW427  
Lucerne Tuning Coil for AW427 .. AW444  
1934 Crystal Set .. AW450  
150-mile Crystal Set .. AW450

### STRAIGHT SETS. Battery Operated.

One-valve: Blueprint, 2s.  
B.E.C. Special One-valve .. AW387\*  
Two-valve: Blueprint, 2s. each.  
Full-wave Two (SG, Det, Pen) .. AW292  
A Modern Two-valve .. WM409\*  
Three-valve: Blueprints, 2s. each.  
25 5s. S.G. 3 (SG, D, Trans) .. AW413\*  
Lucerne Ranger (SG, D, Trans) .. AW422\*  
45 5s. Three De Luxe Version (SG, D, Trans) .. AW435  
Transportable Three (SG, D, Pen) .. WM271  
Economy Pentode Three (SG, D, Pen) .. WM337  
"W.M." 1934 Standard Three (SG, D, Pen) .. WM351  
23 3s. Three (SG, D, Trans) .. WM354  
1935 20 6s. Battery Three (SG, D, Pen) .. WM371  
PTT Three (Pen, D, Pen) .. WM389  
Certainty Three (SG, D, Pen) .. WM393

All-wave Winning Three (SG, D, Pen) .. WM400  
Four-valve: Blueprints, 2s. each.  
65s. Four (SG, D, RC, Trans) .. AW370  
Self-contained Four (SG, D, LF, C, B) .. WM331  
Lucerne Straight Four (SG, D, LF, Trans) .. WM350  
25 5s. Battery Four (HF, D, 2LF) .. WM381\*  
The H.K. Four (SG, SG, D, Pen) .. WM384  
The Auto Straight Four (HF Pen, HF Pen, DDT, Pen) .. WM401\*  
Five-valve: Blueprints, 2s. each.  
Super-quality Five (2 HF, D, RC, Trans) .. WM320  
Class B Quadradyne (2 SG, D, LF, Class B) .. WM344  
New Class B Five (3 SG, D, LF, Class B) .. WM340

### Mains Operated

Two-valve: Blueprints, 2s. each.  
Consoelectric Two (D, Pen), A.C. Economy A.C. Two (D, Trans), A.C. .. AW403  
Three-valve: Blueprints, 2s. each.  
Mantovani A.C. Three (HF, Pen, D, Pen) .. WM374\*  
215 15s. 1938 A.C. Radiogram (HF, D, Pen) .. WM401\*  
All-Metal Four (2 SG, D, Pen) .. WM329  
Harris Jubilee Radiogram (HF, Pen, D, LF, V) .. WM386

### SUPERHETS

Battery Sets: Blueprints, 2s. each.  
"Variety Four" .. WM385\*  
The Request All-Wave .. WM407\*  
Mains Sets: Blueprints, 2s. each.  
Heptode Superhet Three A.C. .. WM359\*

### PORTABLES

Four-valve: Blueprints, 2s. each.  
Holiday Portable (SG, D, LF, Class B) .. AW393\*  
Family Portable (HF, D, RC, Trans) .. AW412\*  
Tyers Portable (SG, D, 2 Trans) .. WM397\*

### SHORT-WAVE SETS. Battery Operated

One-valve: Blueprints, 2s. each.  
S.W. One-valve for America .. AW429\*  
Konia Short-wave .. AW452\*  
Two-valve: Blueprints, 2s. each.  
Ultra-short Battery Two (SG, Det, Pen) .. WM402\*  
Home-made Coil Two (D, Pen) .. AW440  
Three-valve: Blueprints, 2s. each.  
Experimenter's 5-metre Set (D, Trans, Super-regen) .. AW435  
The Carrier Short-wave (SG, D, P) .. WM390  
Fen-valve: Blueprints, 2s. each.  
A.W. Short-wave World-beater (HF Pen, D, RC, Trans) .. AW436\*  
Standard Four-valve Short-wave (SG, D, LF, P) .. WM383\*

Superhet: Blueprint, 3s.  
Simplified Short-wave Super .. WM397\*

### Mains Operated

Two-valve: Blueprints, 2s. each.  
Two-valve Mains Short-wave (D, Pen), A.C. .. AW453  
Four-valve: Blueprints, 2s.  
Standards Four-valve A.C. Short-wave (SG, D, RC, Trans) .. WM391\*

### MISCELLANEOUS

S.W. 1-valve Converter (Price 1s.) .. AW329  
Enthusiast's Power Amplifier (10 Watts) (2-) .. WM387\*  
Liliputer's 6-watt A.C. Amplifier (3-) .. WM392\*  
Radio Unit (2v.) for WM392 (2-) .. WM398\*  
Havlin Electrogram battery amplifier (2-) .. WM399\*  
De Luxe Concert A.C. Electrogram (2-) .. WM403\*  
New Style Short-wave Adapter (2-) .. WM388  
B.L.D.L.O. Short-wave Converter (2-) .. WM405\*  
Wilson Tone Master (2-) .. WM406\*  
The W.M. A.C. Short-wave Converter (2-) .. WM408\*

## HINTS COUPON

This coupon is available until Apr. 4th, 1949, and must accompany all Practical Hints.  
PRACTICAL WIRELESS. APR. 1949

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by SPEIGHT & SONS, LTD, Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (A/asia), LTD, South Africa: CENTRAL NEWS AGENCY, LTD. Subscription rates including postage: Inland 10s. 6d. per annum; Abroad 10s. 6d. per annum. Registered at the General Post Office for the Canadian Magazine Post. CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of by way of Trade except at the full retail price of 9d.; and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter, whatsoever.



# AMBITIOUS ENGINEERS

## HAVE YOU HAD YOUR COPY OF "ENGINEERING OPPORTUNITIES"?

Whatever your age or experience—whether you are one of the "old school" or a newcomer to Engineering anxious to hold your position under post-war conditions—you must read this highly informative guide to the best paid Engineering posts.

The Handbook contains among other intensely interesting matter, particulars of B.Sc., A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.M.I., A.M.I.P.E., A.M.Brit.I.R.E., CITY & GUILDS, CIVIL SERVICE, and other important Engineering Examinations, outlines home-study courses in all branches of CIVIL, MECHANICAL, ELECTRICAL, AUTOMOBILE, RADIO, TELEVISION, AERONAUTICAL and PRODUCTION ENGINEERING, DRAUGHTSMANSHIP, GOVERNMENT EMPLOYMENT, BUILDING and PLASTICS, MATRICULATION, etc., and explains the unique advantages of our Employment Department.

## WE DEFINITELY GUARANTEE 'NO PASS—NO FEE'

If you are earning less than £10 a week you cannot afford to miss reading "ENGINEERING OPPORTUNITIES"; it tells you everything you want to know to make your future secure and describes many chances you are now missing. In your own interest we advise you to write for your copy of this enlightening guide to well-paid posts NOW—FREE and without obligation.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

409, SHAKESPEARE HOUSE, 17, 18 & 19, STRATFORD PLACE, LONDON, W.1.

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**

Come to  
*'The Radio Centre'*


OPENING DATE, MARCH 15th

M.O.S. take pleasure in announcing the opening of one of the largest radio and electrical stores in Great Britain, where you will be able to inspect the latest in technical developments and surplus releases. You are cordially invited to call and view our huge display of radio and allied equipment at the Radio Centre.

33, Tottenham Court Road, London, W.1  
(1 minute from Oxford Street).
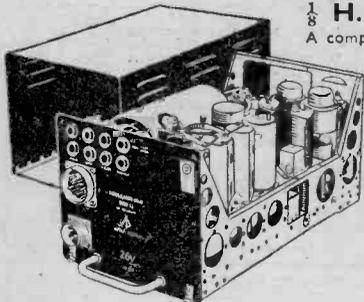
### PORTABLE TESTING INSTRUMENTS

Brand new Army general purpose, line-testing instruments. The instrument illustrated is a necessity for every electrician and radio-man, and is a reliable standby for the "ham." The instrument comprises an M.C. D.C. volt-ohm milliammeter, in an attractive carrying case with handle. The dial is calibrated for readings of 0-1.5 volts, 0-3 volts, 0-60 ma. 0-500 and 0-5,000 ohms. Additional ranges may be added. Basic f.s.d. is 6 ma, 250 ohms. Unique-unload primary cell test also incorporated. Each instrument is fully guaranteed perfect and the cost of manufacture of these was double the amount we ask. Made by famous manufacturers. The price is 21/- post free.




### $\frac{1}{8}$ H.P. A.C. MOTORS

A complete A.C. Motor ready for use without adaptation.  $\frac{1}{8}$  h.p., 2,500 r.p.m. For use on 220-250 volts A.C. mains. Spindle fitted with 2in. dia. pulley ready for use with small belt drive. Fitted with 3ft. 3-way mains lead. A far superior model to those previously offered. 37/6 post free.
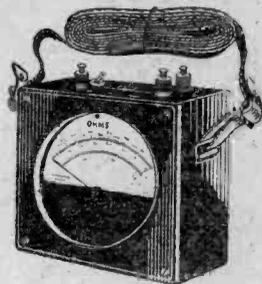
### MODULATORS TYPE 76

A 9-valve equipment comprising 2 stages, i.f. amplification (560 kc/s), Detector, A.V.C. separate B.F.O. and 1 stage audio output (phone). Also 4 valve push-pull modulation amplifier (1 valve used as A.F. oscillator on M.C.W.). Complete with valves and power unit (24v. D.C. input, with 2 outputs of 250v. D.C.). Valve line-up: 2 KT33C, 2 EF36, 3 EF39, 1 EBC33 and 1 EF50. Brand new and complete in transit case, 50/- (Carriage and Packing, 7/6). Or less valves, 30/-.

Terms: C.W.O. Remittances payable to E. & G. Distributing Corporation Limited.



**M.O.S.** MAIL ORDER SUPPLY COMPANY, Dept. PW, The Radio Centre,  
33, Tottenham Court Road, London, W.1. Telephone: MUSeum 6667-8-9.