


9d

ISSUE NO. 524

MAY 1950

EDITOR:
SAMM

PRACTICAL WIRELESS

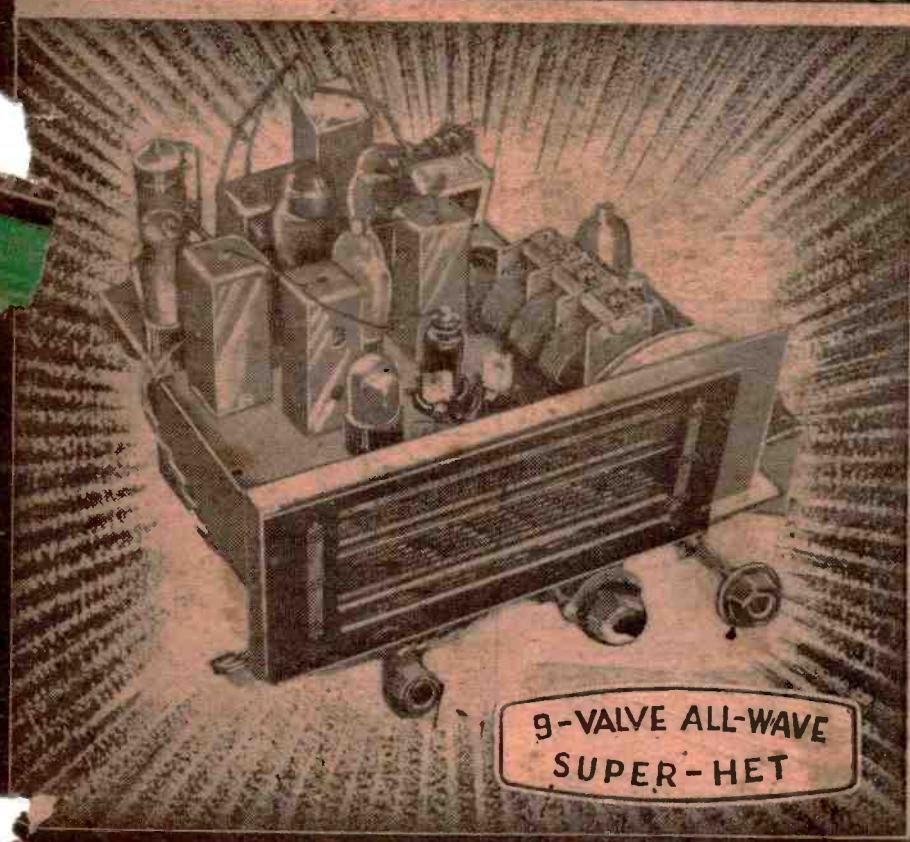

9-VALVE ALL-WAVE
SUPER-HET


CHIEF CONTENTS

P.W. Television Receiver
Valve Testers
Calling Our Friends

Stabilized Power Supplies
Designing "Personal" Receivers
The Copenhagen Pin

BAND SPREAD

by ARMSTRONG
The NEW EXP 119

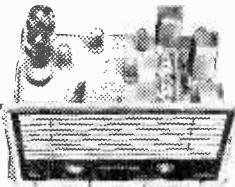**BRIEF SPECIFICATION**

1. Designed specifically for the Overseas Listener.
2. 9 wave ranges, (6 bandspread and 3 general coverage) 11-570 metres.
3. High Slope pentode R.F. stage.
4. 2 stages of I.F. amplification.
5. Variable selectivity.

Write now for fullest information.

Armstrong
THE CHASSIS PEOPLE

Armstrong Wireless & Television Co., Ltd.
Wartlers Road, Holloway, London, N.7.
Telephone : NORTH 3213

SOLE BIRMINGHAM
AGENT :

Hayes Company,
1 Alcester Rd., Moseley,
Birmingham, 13.

This model has been produced after exhaustive investigation into the requirements of Overseas Listeners. Ease of operation on the short-wave bands, high sensitivity and quality output have all been studied and incorporated in the EXP 119.

6. Automatic noise limiter.
7. 10 watts push-pull output.
8. Separate A.C. power pack to facilitate operation from a vibrator if required.
9. Hi valve circuit (including cathode-ray tuning indicator).

A few of these models are now available for the home market. Price £36 plus tax.

SOUTHERN RADIO'S WIRELESS BARGAINS

R.A.F. BOMBSIGHT COMPUTERS.—Complete with motors, gyro, blowers, gears, etc., etc. Ideal for model makers and experimenters. The best component value ever offered. 55/-, plus 5/- carriage.

SERVO UNIT ASSEMBLY for bombsight computer, including 27 volts motor, gearing, blowers, etc., 17 6/-.

CONTACTOR TIME SWITCHES. 10-hour movement with thermostatic control, 2 impulses per second. Complete in sound-proof case, 10/-, plus 1/-.

TR119 SIX VALVE SUPERHET RECEIVERS.—Complete with valves, etc., 22 6/-.

PERISCOPE. Ex-U.S.A. Type M.8, complete with removable telescope, 17 6/-.

COMMAND RECEIVERS. B.C.454 (49 100 metres), B.C.455 (84 100 metres). Complete with 6 valves. Ideal for easy conversion to mains receivers or car radio, 35/-, plus 1/-.

CAMERA CONTROL UNITS. Type 35 No. 28. Complete in wooden box, 20/-.

LUFBRY HOLE CUTTERS. Adjustable from 4in. to 31in. For use on wood, metal, plastic, etc., 5 6/-.

RADIO COMPASS INDICATORS. with Selsyn motor. 3in. dia, 360 degrees, 13 6/-.

ROTOTHERM. Temperature gauges, from 200 to 500 degrees Fahrenheit. Chromium finish, 6/-.

SECTIONAL AERIALS. 8ft. interlocking, 3 6/- base for same, 2 6/-.

WESPECTORS. Wx6 and W112 types, 7 6/- dozen.

THROAT MICROPHONES. Complete with lead and plug, 3 6/-.

CRYSTAL DIODECTORS. Semi-permanent type, 2 6/-.

RESISTANCES. 100 Assorted values from 1 watt to 3-watts. All useful values, 9/- per 100.

CONDENSERS. 100 Assorted values. All useful sizes. Mica and tubular, 15/- per 100.

INDICATOR UNITS. Type RC 920A ; 7 Valves 2X2 (1) 6X5 (1), 6H6 (2), 6G6 (1), 6SN7 (2), 3BP1 Tube, switching motor, etc., etc. Ideal for Oscillator conversion. 44/-, plus 5/- carriage.

DRIVE CABLES. for B.C.433/4/5. 14ft. long with adaptors at either end, 8/6, post U- extra.

RADIO RECEIVERS TYPE R-28/ARC-5. Complete with 10 Valves, 717 (4), 12SH7 (3), 12SL7 (2), 12a6 (1), etc., etc. 100-156 mcs., designed for Crystal Control. 55/-, plus 5/-.

Full List of Radio Publications 2/-.

RECEIVERS TYPE R1125—Brand new complete with 2 valves, 17 6/-.

-THOUSANDS OF BARGAIN LINES FOR CALLERS.

SOUTHERN RADIO SUPPLY LTD.
46, LISLE STREET, LONDON, W.C.
GERrard 6653

CLYDESDALE

Bargains in Ex-Services Radio and Electronic Equipment

Infra-Red Image Converter Cell. Brand New, in maker's carton. EX. U.S.A. S.C. Crystal Multiplier, Type MI-1946B. A frequency Multiplier to cover 2-20 mcs. with 807 and spare (2 valves), etc., external power supply required. (No xtals supplied). In metal case 13in. x 10in. x 6in. With Instruction Books. CLYDESDALE'S PRICE ONLY 39/- each.



Snooperscope. Brand New, in maker's carton. EX. U.S.A. S.C. Crystal Multiplier, Type MI-1946B. A frequency Multiplier to cover 2-20 mcs. with 807 and spare (2 valves), etc., external power supply required. (No xtals supplied). In metal case 13in. x 10in. x 6in. With Instruction Books.

CLYDESDALE'S PRICE ONLY 39/- each.

CARRIAGE PAID.

H.156. Moving Coil Mic Headphone Assy. Brand New. Comprising moving coil microphone (Hand No.7), with pair of M.C. Headphones and 3ft. lead with rubber 5-point socket. Approx. 60 ohm, per insert.

CLYDESDALE'S 12 6. POST PRICE ONLY.

PAID.

TRANSMITTER TUNING UNITS. Brand New in maker's original carton. Each having Vernier tuning dial; variable capacitors, tank coil unit etc. in metal cabinet 12 1/2 x 7 1/2 x 6in. Finish black.

TU5B, 1,500-3,000 kcs. CLYDESDALE'S 22 6/ each CARRIAGE PRICE ONLY.

PAID.

TU6B, 3,000-4,500 kcs. TU7B, 4,500-5,200 kcs. TU8B, 6,200-7,700 kcs.

CLYDESDALE'S 17 6/ each CARRIAGE PRICE ONLY.

PAID.

TU26B, 200-500 kcs. CLYDESDALE'S 10 - each CARRIAGE PRICE ONLY.

PAID.

Order direct from **CLYDESDALE SUPPLY CO., LTD.**, 2 Bridge St., Glasgow, C.5. Phone: SOUTH 2766 9. Visit our Branches in Scotland, England and N. Ireland

NO RADIO CONSTRUCTOR

can afford to miss
these bargains

CONSTRUCTOR'S PARCEL (A).

As Illustrated. Comprising heavy gauge metal chassis cut out for a 5 valve superhet, overall size 14in. x 6in. x 2in. with mains transformer (250-0-250 v. at 60 m.a. 6.3 v. at 3 amps, 5 v. at 2 amps.) and L.M. & S. scale size 5in. x 5in. and back plate complete with supporting brackets and pulleys, drive drum, pointer and 2-speed spindle, all complete with instructions showing, among other things, how the string fits round pulleys and pointer.

£1

plus 1 9 post and packing.

CONSTRUCTOR'S PARCEL (B).

As above but with 4v. type transformer, same price.

CONSTRUCTOR'S PARCEL (C).

As above but without mains transformer, same price.

post and packing.

★ THIS MONTH'S SPECIAL
This is a beautifully made 10 in. P.M. Speaker, a real precision product made by a very famous firm you will recognise immediately. It is undoubtedly a 10in. speaker with a 12in. quality reproduction, and has these special features. (A) a solid diecast frame, (B) a dustproof speech coil arrangement, and (C) a patented speech coil suspension which gives wider frequency response. Speech coil is normal 2.3 ohm impedance. The correct retail price of this speaker is 35/-, but we are able to offer them, while stocks last, for 16/6 each, plus 2 6 carriage and insurance.


MAIL ORDER ONLY.

THE INSTRUMENT CO., LTD.
11, GUNNERSBURY LANE, ACTON, W.3.

Vision in Design

The ADVANCE Signal Generator

(Type E2)

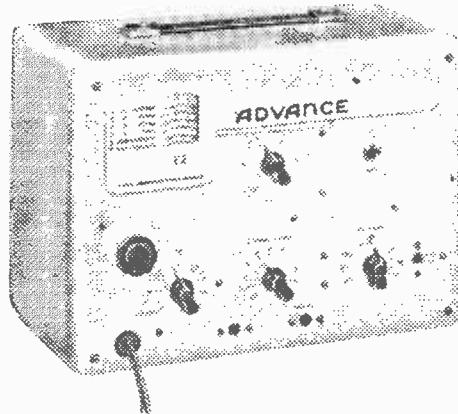

Range : 100 Kc/s-100 Mc/s in 6 bands.

Frequency : Guaranteed within ± 1 per cent.

Output : Approximately 1 volt unattenuated and variable from $1\mu V$ to 100 mV into a 75-ohm load through a matched transmission line.

Stray Field : Less than 3 μV at 100 Mc/s.

Illuminated Dial : Total scale length, 30in.

Power Supply : 110, 210, 230, 250 volts; 40-100 c/s.

Dimension : 9½in. high x 13in. wide x 8in. deep.

Weight : 15 lb.

ADVANCE COMPONENTS LTD., BACK RD., SHERNHALL ST., WALTHAMSTOW LONDON, E.17
Telephone : LARKwood 4366-7-8

The Advance Signal Generator Type E.2 has been designed with an eye to future developments in the Radio and Television fields. Its wide range of frequencies—from 100 Kc/s to 100 Mc/s on fundamentals—caters for the rising frequency requirements of modern radio and communications. It is a fine example of 'Advance' design and manufacture.

This generator offers an instrument of laboratory standard at a price within the reach of moderate purses. The remarkably high frequency accuracy of $\pm 1\%$ extends over the whole range.

SEND FOR FULLY DESCRIPTIVE LEAFLET.



"WE have heard this loudspeaker in operation and there can be little doubt that the makers' claim of a frequency range of 50 to 14,000 c/s can be substantiated."

"ON a plane baffle the Concentric Duplex gives a clean and full-bodied bass response of surprisingly good quality for a 10 in. diaphragm. The diaphragm suspension is also of a type well suited for use in conjunction with a cabinet of the 'bass-reflex' type if this is preferred."

—that's what the "Wireless World"
says about

(FEBRUARY ISSUE)

De Luxe table cabinet model
£11. - 3. 0

Corner console model, less
transformer £12. 12. 0



Leaflet
on
request.

WHITELEY ELECTRICAL RADIO CO. LTD. • MANSFIELD •



Stentorian
Concentric Duplex

HIGH FIDELITY REPRODUCER

SPECIFICATION: Series Gap magnet of Alcomax 3.
Flux in LF gap 12,000 gauss on 1" pole

" " HF, 13,000 gauss " "

Power handling capacity, 6 watts. Frequency range
50-14,000 c.p.s. Fundamental bass resonance, 65 c.p.s.

£6 - 6 - 0

Complete with matching
transformer and filter con-
denser.

NOTTS • ENGLAND

Practical Wireless

EVERY MONTH.
VOL. XXVI. NO. 526 MAY, 1950

18th YEAR
OF ISSUE

COMMENTS OF THE MONTH

Editor E.J.CAMM

BY THE EDITOR

Programme Quality Declining

A HIGH percentage of programme time is occupied by recorded programmes, especially in the case of regular feature programmes, of which there are far too many. There is also criticism of the third feature programmes, the complaint being that they are too high-brow. The recorded programme is a cheap way of filling programme time, and there are far too many feature programmes on similar lines. The gag writers are being over-worked and some of their efforts are inferior to those which may be read in a children's comic paper. The programmes, in fact, are either too high-brow or too low-brow and it is time that there was a general revision of them and an overhaul of responsible staff. Producers get tired and when they get tired they get into a rut. Criticism merely makes them turn in their grooves and, as with the theatre, there should be a general change round of jobs every year or so, so that fresh and enthusiastic people with new outlooks are able to infuse their ideas into new programmes. There is a general tendency once a feature has proved popular to overload the public not only with that particular programme but with others of a similar nature. The programme which consists chiefly of interviews with nonentities who have nothing much to say, the humour being obtained from unconsciously humorous replies prompted by questions from the interviewer, who sniggers in a self-satisfied way and seems to enjoy the programme immensely, should be abolished. Listeners do not want to know that a young lady from the cotton mills, for example, enjoys her work; that she has been engaged for a couple of years; that she has a young man but is not going to get married yet. That is the sort of undiluted drivel which is pumped out week after week. The programme consisting of some slick wisecracks, largely American in origin, is also being very much overdone. Why not appoint an independent commission to investigate the problem?

"Practical Television"

OUR new companion journal, *Practical Television*, was an instantaneous success, the first issue being sold out before publication day, notwithstanding a very heavy print.

The second issue has similarly been absorbed. In these days of production difficulties it is necessary for publishers to know well in advance how many copies to print. We suggest to every reader of this journal that, as *Practical Television* is complementary to this journal, they should place a regular order now for its delivery each month. It is similar in style, format and price, and it gives fuller details of television developments than is possible in this journal.

The New Wavelengths

THE Copenhagen Plan is now in being, the Light Programme being radiated on 1,500 metres and 247 metres, the Third Programme on 464 metres and 194 metres and the Home Service as follows: North, 434 metres and 261 metres, Scottish 371 metres, Welsh 341 metres, London 330 metres, West 285 metres and 206 metres, Midland 276 metres and Northern Ireland 261 metres. Elsewhere in this issue we show the new positions on which the stations appear on the scale. Owners of push-button receivers will, of course, have to readjust the position of the cams in accordance with manufacturer's instructions. If the tuning dial of your receiver is marked in metres it is only necessary to set the pointer to the new wavelength of the station you wish to listen to, although if station names are also marked on the dial they will not be in their correct places. Some manufacturers intend to supply new scales. With those receivers with only station names on the tuning dial each station will be found slightly to one side of its name. Receivers which have push buttons only, and not manual control, will not receive the new B.B.C. wavelengths, except the light programme on long waves, until they have been readjusted.

Nearly every station in Europe is allocated a new wavelength under the Copenhagen Plan. A list of the principal continental stations is printed elsewhere in this issue.

The new plan was, of course, rendered necessary because of the great increase in the number of broadcasting stations accommodated in the medium waveband. Moreover, the power of these stations has considerably increased during the past ten years.

F. J. C.

ROUND the WORLD of WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate number of licences issued during the year ended 31st January, 1950.

Region	Number
London Postal	2,323,000
Home Counties	1,634,000
Midland	1,713,000
North Eastern	1,874,000
North Western	1,586,000
South Western	1,045,000
Welsh and Border Counties	721,000
Total England and Wales	10,896,000
Scotland	1,113,000
Northern Ireland	200,000
Grand Total	12,209,000

National Radio Exhibition

THE National Radio Exhibition which is to be held at Castle Bromwich, Birmingham, from September 6th to 16th next, will be at Earls Court, London, in September 1951, 1952 and 1953.

The Radio Industry Council in announcing this recently, said that an earlier decision to hold the exhibition at Olympia, London, in June, instead of in the autumn had been changed, but this change came too late to secure convenient autumn dates and the necessary space at Olympia.

In view of the facilities offered at Earls Court, it was decided to go there rather than hold the exhibition at Olympia at a less convenient time.

The National Radio Exhibition, before going to Olympia in 1926, was held at the Royal Albert Hall in 1924 and 1925, the White City in 1923, and the Horticultural Hall in 1922. Sixteen National Radio Exhibitions have been held in all. The one coinciding with the Festival of Britain will be the eighteenth.

Broadcasting Committee

THE Broadcasting Committee, under the chairmanship of the Rt. Hon. the Lord Beveridge, K.C.B., F.B.A., heard oral evidence on Thursday, March 9th, 1950, from representatives of the Renters, Exhibitors and Producers Joint Committee of the Film Industry.

The Committee would like it to be known that they would still welcome representations in writing on any subject within their terms of reference. These are:

"To consider the constitution, control, finance and other general aspects of the sound and television broadcasting services of the United Kingdom (excluding those aspects of the overseas services for which the B.B.C. are not responsible) and to advise on the conditions under which these services and wire broadcast-

ing should be conducted after December 31st, 1951."


All communications should be addressed to the Secretary, Broadcasting Committee, Iron Trades House, 1, Chester Street, London, S.W.1.

V.H.F. Contest for Amateurs

THE Amateur Division of E.M.I. is organising (in conjunction with the Amalgamated Short-Wave Press) a contest amongst amateurs operating on the 144 Mc/s band. E.M.I. are donating four prizes—namely, two pairs of heavy duty rectifier valves for the transmitting section of the contest, and two sets of three receiving valves for the listener section.

A unique feature of the competition is that although each station is out to make as many contacts as possible, the "merit" of each competitor will be determined by very careful consideration of the conditions under which stations are working, thus competitors who only manage to make a small number of contacts may well be amongst the winners if they are working under difficult conditions.

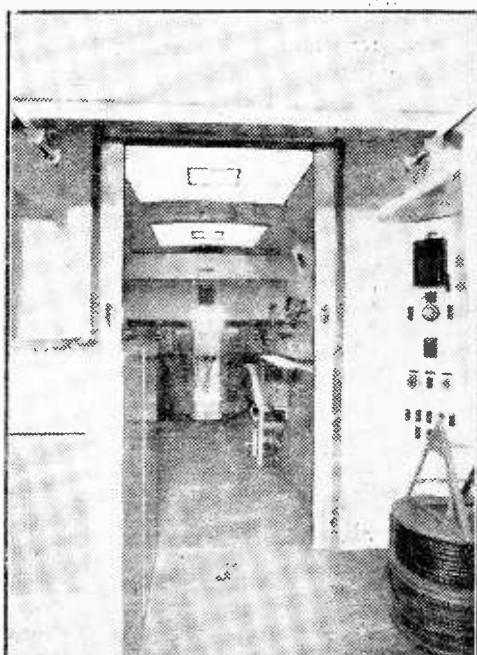The competition is to be held from 08.00 hours




Interior of a mobile broadcast recording unit supplied by E.M.I. to Radio Luxembourg.

on April 22nd until 24.00 hours on April 23rd. The closing date for receipt of completed contest logs is May 8th.

Any interested amateur who does not receive a circular letter, can obtain further information either from Mr. H. E. Smith, Amateur Division, E.M.I. Sales & Service, Ltd., Hayes, Middlesex, or

may be withdrawn, and radio-controls enthusiasts may find themselves forced to operate under the more stringent conditions imposed in other countries.

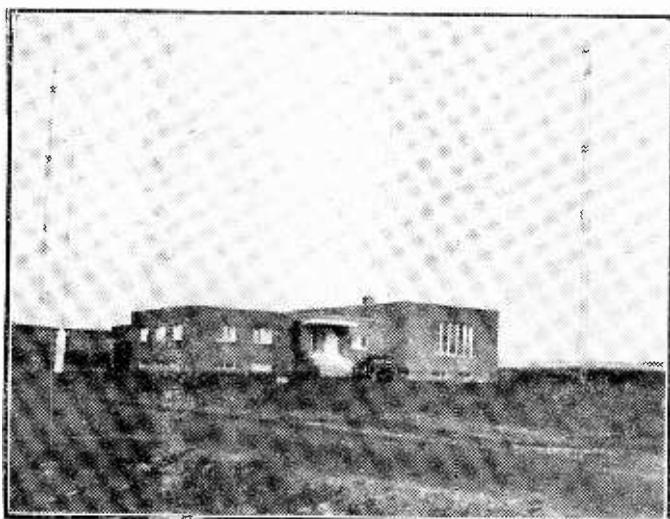Monitoring equipment of a simple type is cheap to construct and operate, and in the view of the Radio Controlled Models Society, is essential in any radio-controlled demonstration.



The most northerly broadcasting station at Vadsø, Norway.

from the Editor, *Short Wave News*, 57, Maida Vale, London, W.9.

Most Northerly Broadcasting Station

IN 1933, the most northerly broadcaster in the world was installed in Vadsø in the province of Finnmark, in Northern Norway. This 10 kW station was within the Arctic Circle, and furnished programmes to the northern half of Norway and Lapland. During the occupation of Norway in the Second World War, the station was destroyed by the Germans.

A new station has now been built, and a 20 kW broadcaster was put into service recently to cover the same area, where about 45,000 people are scattered over 19,000 square miles. By this means the Norwegian broadcasting administration has augmented its service and improved the signal strength and clarity of its radio programmes.

Both the original transmitter and the replacing transmitter were manufactured by Standard Telephones and Cables, Ltd., in England, and supplied through their associate, Standard Telefon og Kabelfabrik A/S, Oslo.

Radio-controlled Models Society

THE Radio Controlled Models Society is seriously perturbed at the number of radio-controlled models taking part in field events at which no official frequency monitoring is arranged. At these events, over which the Society has no jurisdiction, models have been observed operating outside the frequency bands allotted by the Postmaster-General for that purpose. It is of vital importance that these concessions are not abused, otherwise they

B.I.R.E.
THE following list of meetings has been arranged for April, 1950:

London Section.—London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1 (meetings commence at 6.30 p.m.) April 20th, D. W. Heightman (Member), "U.H.F. Propagation and Characteristics."

West Midlands Section.—Wolverhampton and Staffordshire Technical College, Wulfrune Street, Wolverhampton (meetings commence at 7 p.m.). April 26th, C. R. Amey, "Intermodulation Analysis."

Engineer-in-charge, Aberdeen
MR. W. BALFOUR has been appointed Engineer-in-Charge of the B.B.C. studio centre and transmitting station at Aberdeen. He replaces Mr. W. W. Inder, who has retired from the post of Engineer-in-Charge at Aberdeen, after 17 years' service.

Mr. Balfour came to the B.B.C. from the G.P.O. radio station at Portishead in 1934, and has since had wide experience in the transmitter department of the engineering division. He is a native of Gourock.

Newnes' Motorists' Touring Maps and Gazetteer
THIS book, specially produced for the motorist, has now been revised. It comprises 96 skillfully coloured maps covering the whole of the British Isles. Every road classified by the Ministry of Transport is clearly shown. Every main road is marked with its signpost number. It also shows the railways, level crossings, stations, churches, contours, etc.

The scale is 5 miles to the inch, except in the outlying parts of Scotland, where the scale is smaller.

In addition to the 96 road maps, this handy size edition contains a Gazetteer Index to Places—64 additional pages giving place-name, county, mileage from nearest big centre, population, and map reference so that the place, whether it be city, town, hamlet, or even railway station, may be found in an instant.

The book costs 17s. 6d., and is obtainable from George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

WIRELESS COILS, CHOKES AND TRANSFORMERS 8th Edition now ready.	Price 6/- by post 6/6d.
--	-------------------------

The Band-searcher Tuning Unit-4

Concluding Details of this Interesting Accessory for the Short-wave Enthusiast

By J. R. DAVIES

TH E contacts next need to be manufactured. No great accuracy is needed here, as the method of fixing allows the downward pressure as well as the sideways movement of these contacts to be adjusted. Fig. 21 (a) and (b) give details of the contacts. The material used may be springy brass (as obtained from a flash lamp battery), phosphor-bronze, or any other fairly springy metal. The contacts are self-wiping and are only needed to light a dial-lamp, so there is little need to worry about special contact surfaces. It will be seen that the contact is bent at one end to fit the semi-circular contact holder, part N. A 6 B.A. nut and bolt are fitted to the two holes drilled in Fig. 21 (a) to allow the contact to grip the holder tightly at the desired position. A small spot of solder holds the nut to the brass, making it an anchor nut. It will be seen that the screw is tightened and loosened from behind.

The part of the contact which touches the contact on the moving disc is made to present a slightly convex surface to that contact. See Fig. 21 (b) and (c). This ensures a smoother travel.

24. The moving contact just mentioned is made from brass plate, as shown in Fig. 21 (d). It is mounted as shown in the photograph, on the front side of the circular disc.

The Tuning Drum

25. The tuning drum is mounted to three 6 B.A. bolts fixed to disc B. Two of these are already holding parts B and C together (see Fig. 7). If the details in paragraph 6 were observed these screws should project forwards at least $\frac{3}{16}$ in. A third screw may now be fixed to the remaining "6 B.A. clear" hole in the disc B. This should also project forward some $\frac{3}{16}$ in. These screws hold the tuning drum as shown in Fig. 22 (a) and (b). The long screw projecting from the centre of the drum may be fitted if it is desired to use a directly-driven pointer on the dial. This point is left to the reader's own desires.

The tuning drum should have a diameter of some 2ins. Ordinary circular tin lids such as those used for boot-blacking tins, bottle tops, etc., make excellent drums, and their somewhat un-radiolike derivation may be easily camouflaged by a coat of paint! A small nut and bolt may be mounted somewhere along the periphery of the drum to give an anchoring point for the driving cord. In the case of the bandset condenser it is advisable to insert a spring in both cords going to the driver spindle, as shown in Fig. 22 (e). This is because the condenser, when being "pulled in" on going over to "bandspread," is liable to move through a few degrees of rotation. This would cause an undue strain to be placed on the cord, whose life would thus be shortened. The two springs take up

this strain, on whichever side of the drum it may appear.

The Bandspread Condenser

The bandspread two-gang condenser may be of any type, so long as its dimensions do not exceed those quoted for the bandset condenser. The author used an ordinary 500 pF condenser "cut down" by removing all the moving vanes except one on both gangs. The capacity resulting may be easily calculated by counting the spaces between the fixed and moving vanes. Before stripping, the condenser used by the author had 12 moving vanes. This gave 22 spaces between fixed and moving vanes (both outside vanes were moving vanes). When cut down there were then only two spaces between fixed and moving vanes, i.e., one on either side of the remaining moving vane (which was, incidentally, the centre vane). The remaining

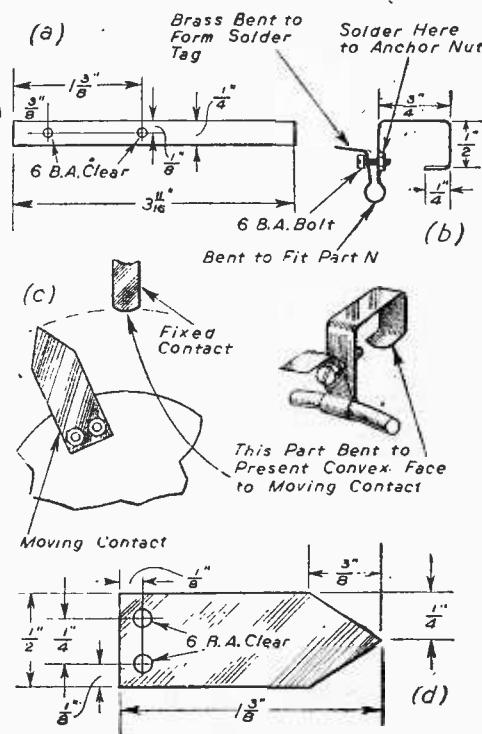


Fig. 21.—(a) and (b). Details of fixed contacts. (c) The convex contact point mentioned in the text. (d) The pointer.

capacity was therefore $2/22$ of 500 pF , which is equal to 45.5 pF . This should give just sufficient capacity to "spread" all the short-wave broadcasting bands required.

The mounting of the bandspread condenser is left entirely to the reader, as no hard-and-fast rules may be given, owing to the non-standardisation of these components.

There is plenty of room on the chassis to hold this condenser, and if its spindle is arranged to be at the same height as that of the handset condenser, two pointers may be used, giving a dial somewhat on the lines of that shown in Fig. 22 (d).

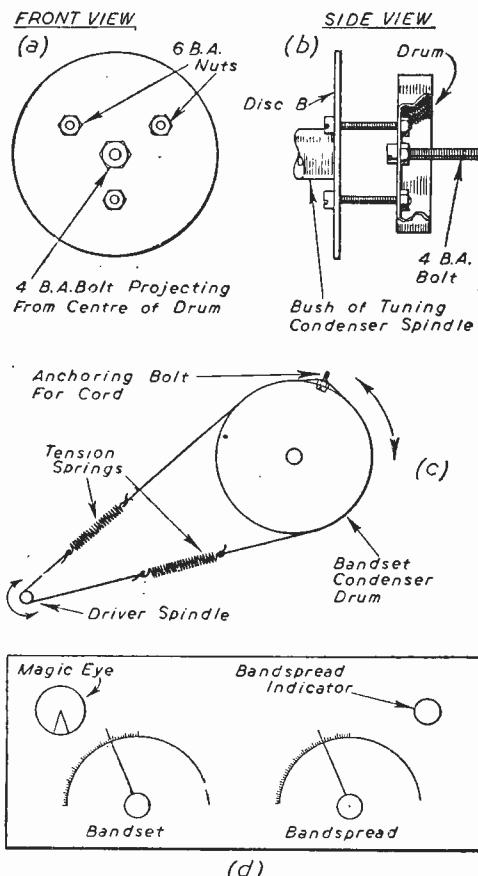


Fig. 22.—(a) and (b). How a drum for a cord drive may be fitted to the handset tuning condenser. (c) A spring is fitted to both sides of the cord drive to avoid strain (see text). (d) Suggested dial layout for the unit.

Installation in the Receiver Chassis

The installation of the unit in the receiver chassis should present few problems apart from those of obtaining symmetrical layout, etc. Three holes should be sufficient for mounting purposes, two in the front corners of chassis part J and one in the rear centre. It would give a professional touch if the chassis were mounted on soft rubber grommets at these points, thus making both tuning

condensers floating and less liable to microphonic feedback from the speaker. The driving spindles for the cord drives would need to be mounted on the receiver chassis proper.

The tuning unit may be used on more than one wave-range. The only necessity is that the bandset condenser positions for the required ranges do not clash on different ranges. Either that or that they coincide!

The warning light contacts may be used to light a particular bulb for each band, each bulb illuminating a window or section of the dial and showing

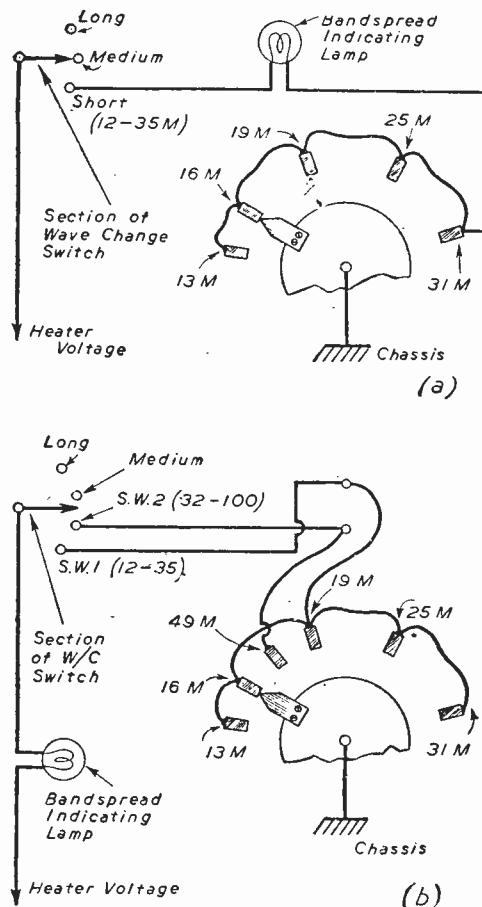


Fig. 23.—(a) and (b). Various methods of connecting the fixed contacts and bandspread indicating lamps to obtain different effects.

which band is in use. Alternatively, one bulb only may be used, the position of the bandset pointer indicating which band is being "spread." Fig. 23 shows how a single bulb or various bulbs may be connected to the wave-change switch so as to ensure that they only light when their particular range is switched on.

Fig. 23 (a) shows a simple arrangement using a

single short-wave band. Assuming that the range of the coils used is from 12 to 35 metres, we then have available the 13, 16, 19, 25 and 31 metre bands. The bandspread indicating light will only shine when the short-wave range is switched on.

Fig. 23 (b) shows a more complicated arrangement. Two short-wave ranges are now available. The S.W.1 range is the same as that of Fig. 23 (a), i.e., 12 to 35 metres. The S.W.2 range (32 to 100 metres) gives us an additional band—the 49 metre band. The contact for this band is set between two used for the S.W.1 range. It will be seen that a section of the wave-change switch is again used to ensure that the appropriate circuit is made for each wave-range. Fig. 23 (c) shows a more ambitious scheme. In this diagram a different lamp is used to indicate each band as the handset condenser approaches it. The effect of this arrangement is extremely im-

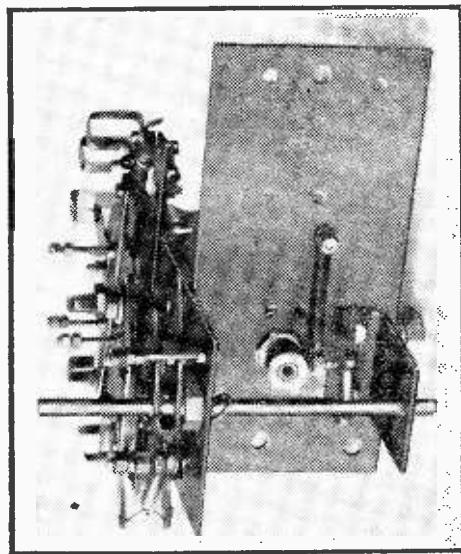


Fig. 24.—View underneath the unit. The D.P.S.T. switch mechanism is clearly visible. ("Condenser free" position, switch open.)

pressive, as may be imagined, and, combined with the ease of tuning and simplicity of accurate band-spreading, makes short-wave listening very pleasurable indeed.

RADIO SHOW PATRON

H.M. QUEEN MARY has again consented to be patron of the National Radio Exhibition which is to be held from September 6th to 16th this year at Castle Bromwich, Birmingham, instead of in London. Her Majesty was patron of the exhibitions at Olympia, London, in 1947 and 1949, but has not been able to visit the exhibition since 1947.

A prospectus and provisional plan have now been issued to prospective exhibitors with much new information about the size and scope of the exhibition.

Every possible facility is to be provided for

Pre-setting the Mechanism

When the tuner has been installed and wired, the coils, etc., should all be trimmed to their maximum performance. When the constructor is

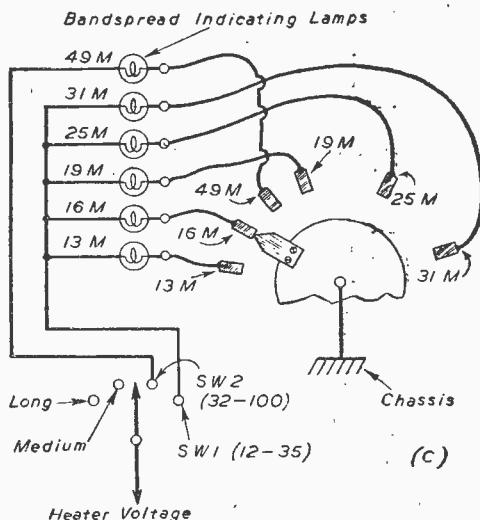


Fig. 23.—(c). Further method of connecting the contacts.

satisfied on this point he may then set up the locating mechanism.

He should first decide what bands he desires. He must then set the locating spikes E so that the handset condenser is, in each case, locked just at the high-frequency end of each band. It is better to do this whilst actually receiving stations as the calibration of some signal generators is not always sufficiently accurate for this purpose. When the locating spikes are definitely and satisfactorily fixed, the lamp contacts may be adjusted. These should be set so as to afford a contact at least a degree of rotation on either side of the locked position. The fixed contacts should perceptibly move as the moving contact passes them. On the other hand, of course, the contact must not be so tight as to impede the rotation of the handset condenser. When adjusted, the light should remain lit for some appreciable movement of the tuning knob, and the locating mechanism should "pull in" the appropriate locating spike at any point in which the light is shining.

working exhibits, subject to their prior sanction by the exhibition committee and subject to their not causing any electrical interference; with B.B.C. transmissions or with any of the exhibition services.

The three principal exhibition features, namely, the B.B.C. studio, the communal television demonstration and exhibition control-room, are all arranged at the west end of the hall opposite the main entrance.

Variety in stand designs will be permitted as in London. Space will be allotted by ballot and applications must reach the Radio Industry Council not later than April 15th.

The exhibition will be open from 11 a.m. to 10 p.m. daily, except on Sunday.

Installing Car Radio-2

The Principles and Practice of Modern Car Radio
By ERIC BALLS, A.M.I.M.I., M.A.E.T.

RADIO-frequency components in the ignition primary (low tension) circuit may be bypassed by the connection of a $0.5 \mu\text{F}$ condenser between the ignition coil SW terminal and earth. It is well to check that the leads to the coil terminals have not been crossed over, as the condenser must not be connected between earth and the lead to the distributor low tension terminal.

Ignition interference is evidenced by a regular clicking noise at tick-over speeds, increasing in periodicity as the engine is revved up. In difficult cases it may be necessary to fit an additional suppressor resistor in each plug lead. Special resistors can be obtained for this purpose and they must be positioned as close as possible to the respective plugs.

Opinions vary as to the effect on ignition efficiency of introducing resistance suppressors into high tension circuits. Nevertheless, where trouble is supposedly caused by the presence of resistors the fault is more likely to be due to some weakness or maladjustment in the ignition system itself. This opinion is confirmed by War Department experience with radio equipped vehicles during the war years and is corroborated by tests carried out by the Institution of Automobile Engineers.

Incidentally, an ignition system which is not functioning correctly will cause much more interference than one which is operating efficiently. It is important to keep sparking plugs clean and the gaps correctly set, and distributor contacts properly adjusted. Defective parts such as cracked or perished plugs, wires, or burnt-away rotor arms should be replaced.

The Dynamo

A howl or whine which rises in pitch and intensity when the engine is speeded up is probably due to interference from the dynamo circuit and will be aggravated if brushes are badly worn or commutator blackened or rough. Apart from correcting these defects adequate suppression can usually be obtained by connecting a $0.5 \mu\text{F}$ condenser between the dynamo main terminal and earth, and if the dynamo is a three-brush one, between the field terminal and earth as shown in Fig. 7. On no account must a condenser be connected to the field terminal if the charging system is a compensated voltage (two-brush dynamo) one.


On compensated voltage controlled sets trouble is sometimes experienced owing to regulator interference which makes itself heard as a buzz which comes on suddenly above a certain engine speed (i.e., when the regulator comes into operation). This can sometimes be cured by connecting a condenser between control box terminals A and E; also between terminals D and E. Messrs. Lucas are at present developing a filter for use with their control boards when persistent trouble is experienced. Delco-Remy-Hyatt have for some time been fitting specially designed filters to their heavy duty lighting sets on vehicles originally intended to be radio equipped.

Considerable noise will be heard in the loudspeaker every time the self-starter is operated but it is hardly worth while attempting to suppress this infrequent interference.

Petrol Pumps

So far as petrol pumps, wiper motors or other accessories are concerned, should any of these give trouble a $0.5 \mu\text{F}$ condenser connected between the live terminal and earth will usually be effective.

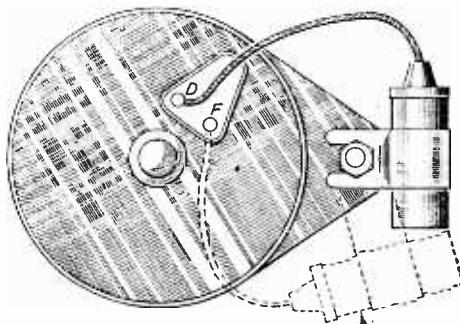Noises due to static (irregular crackly noises) may be caused by accumulations of charge between, for example, loose metal panels on the bodywork,



Additional Condenser On Three-Brush Dynamo

Fig. 7.—Suppressor condensers on a dynamo.

or an ill-fitting bonnet. The locating of the source of trouble is often difficult but, once found, a cure can be effected by bonding the parts with copper braid. In the case of static developed between wheel hubs and axle shafts the remedy is to provide a discharge path by filling the bearings with graphite grease or the provision of some form of rubbing metallic contact.

When testing a car radio installation give it a fair chance—take the vehicle on a country road where there is no screening by adjacent buildings and no possibility of interference from nearby industrial machinery or motor vehicles which may not be fitted with suppressors.

THE NEW NEWNES MONTHLY

Practical Television

Edited by F. J. Camm

No. 1. Now on Sale Price 9d.

Get Your Copy Now!

Miniature 465 K/cs Oscillator

A Simple Battery-operated Modulated Unit for the Experimenter

By A. F. STEVENS

WHEN the average home constructor has built a superhet receiver from his spares box, he usually switches on his newly-made set and nothing happens. He is then working very much in the dark when he tries to "line up." It was with this idea in mind that the oscillator was designed. It can be used to check the audio stages of a superhet or "straight" receiver and to "line up" the I.F. stages of a superhet. The complete unit can be constructed on a chassis measuring only 5in. x 2in. and the cost should not exceed 30s.

The Circuit

The three valves are 1T4 which are easily obtainable on the Government surplus market. V2 and V3 constitute the modulating oscillator which is a multi-vibrator working at about 400 c/s. Should any other modulating frequency be required the formula $f = \frac{1}{2R_4 C_4}$ gives a good approximation

(Note, C_3 must equal C_4 and $R_4 = (x+y)$; x and y have been chosen to give between 30 per cent. and 40 per cent. modulation depth. The fact that the modulating frequency is a square wave need not be detrimental in any way to the type of testing for which the unit was designed.)

The R.F. section is screen modulated and this method seems quite stable in operation. The grid coil of the R.F. valve is tuned to 465 kc/s and feed-back is obtained in the usual way by using a reaction coil. Care must be taken to connect the reaction coil the right way round; if the oscillator does not work immediately, the connections to the reaction coil should be reversed. The grid coil and its reaction coil can be constructed from an I.F. transformer (465 kc/s) the necessary modifications to which are given below. The

R.F. choke is a standard component, but should be as small as possible if size is going to be considered.

Modifying the I.F. Transformer

In the unit which the author constructed an ordinary midget I.F. can was used with the following modifications. (a) Remove the present trimmers from the unit as they are not needed. (b) Remove approximately half the turns from one of the coils (this is to be feed-back coil). Having done this, melt some wax on to the coil to prevent it unwinding further. Sufficient feed-back should take place with the coils in their original relative positions, but it is advisable to reduce the spacing of the coils to say $\frac{1}{2}$ in., and methods of doing this will, no doubt, suggest themselves to readers. It is not possible to

give them here as a lot depends on circumstances. Having modified the transformer bring the leads out to their normal terminations and replace it in its screening can.

Construction

The lay-out of components should not present any difficulty. The author's chassis measured 5in. x 3in., with $1\frac{1}{2}$ in. sides. The positioning of components does not appear to make a great deal of difference to the functioning of the unit. The leads in the R.F. section, however, should be left as short as possible and fairly rigid. The two outputs (A.F. and R.F.) should be brought out on screened leads, and in the author's case the unit was enclosed in a metal cabinet, but any other form of design could, of course, be used.


Aligning the Unit

When the unit is complete connect up power supplies and H.T., 45 v., L.T., 1.4 v. Inject the A.F. output into a pair of headphones, when the 400 c/s note should be heard in the 'phones.

Having checked the A.F. section as above, inject the R.F. output on to the grid of the first I.F. stage of a normal broadcast receiver (I.F. 465 kc/s). Turn "C" in the oscillator until maximum A.F. is heard in the loud speaker.

As the whole basis of the unit is simplicity, refinements such as attenuated output or variable frequency control have not been included but could be added by the constructor if desired.

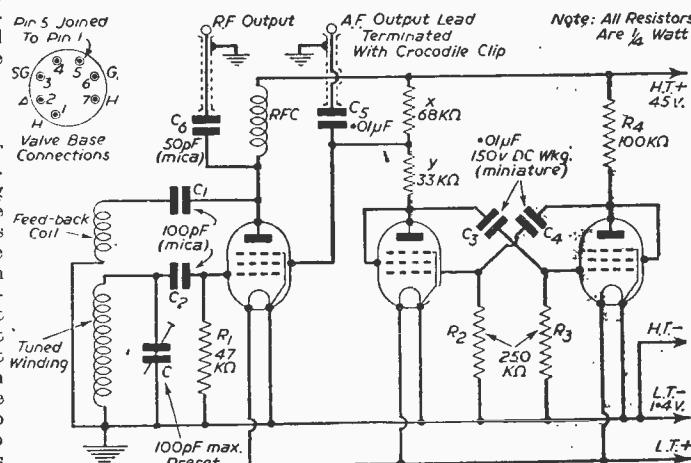It is possible to adapt the unit to frequency modulation by an additional 1T4 valve used as a reactance modulator. If such a unit were constructed it could be used in conjunction with the PRACTICAL WIRELESS miniature Oscilloscope.



Theoretical circuit of the unit.

On your Wavelength

by THERMION

On Your Frequency?

A PEDANTIC critic takes me to task for a minor lapse in grammar in our last issue. As a grammatical purist I bow the head, but in a general feature of this sort I take leave to take liberties with English and apologise in advance to the venerable Mr. Fowler and his Modern English Usage. I will split infinitives, employ terminal prepositions and tmesis where to avoid them would be to pander to pedantry. Apparently my critic will alter "what are you a-doing of," to "of what are you a-doing," a form of pedantry up with which I will not put!

My critic's letter is rendered amusing by the fact that he himself is guilty of grammatical errors! This leads me however to his postscript which was to the effect that the title of this feature should be brought up to date and changed to "On Your Frequency." This suggestion caused my mind to rove back down the decades to those hectic days when the first issue of "Amateur Wireless," one of the first journals to fall by the wayside under the onslaught of PRACTICAL WIRELESS, was being prepared. I was the founder of that journal and one of the problems which always arises when new journals are planned is the selection of titles for regular features. Members of the staff are invited to make suggestions and mine was selected for the feature to which my pseudonym has been subscribed. From that point there was a discussion as to whether the heading should be type set or drawn. Finally it was agreed that it should be in the handwriting of a member of the staff, and as the calligraphy of your present scribe resembles the hieroglyphics of a writer in Choctaw, the specimen submitted by one of my colleagues, a greater expert in pothooks and hangers, was selected. He was completely non-technical and presumably therefore had more time to form his characters neatly than your nimble Thermion. However, it is a feature which has appeared in every issue from the commencement of the now defunct paper to the present; for the first issue of this journal to absorb A. W. (remember at the time of the absorption our title was "Practical and Amateur Wireless") carried that feature over. Indeed, it was the only feature. For your present editor saw nothing in the old journal not more than adequately covered in his existing policy.

Those were indeed interesting and hectic days. A new industry had started and the public was eager to learn about it. There was scarcely a home in the country where some member of the family was not building a crystal set, or had he wished to be a little more luxurious, a one-valve set, using bright emitter valves which blue-glowed at the slightest provocation. They were, of course, of the 6-volt variety with a consumption of about half an amp each, and accumulator charging stations did a roaring trade.

Looking back on some of these old file copies

engenders a nostalgia within me. Do you remember the Skinderviken microphone transmitter button? "Amateur Wireless" published a design for a crystal set incorporating one of these buttons and which it was claimed would work a loudspeaker! Indeed, the journal sponsored the publication of a book entitled "Loudspeaker Crystal Sets," as a result of which we had plenty of queries from disappointed readers, just as I had forecast. Then the journal sponsored a receiver using full mains voltage to supply the valves by means of suitable resistances. It gave marvellous results in the office, but no reader seemed to duplicate these results. They all complained of terrific mains hum, since there were no smoothing condensers of any sort incorporated in the circuit. Investigations showed that the office supply was from a bank of accumulators! However, in the early days of any industry teething troubles such as these are inevitable.

In those days you could sell any wireless component, however bad. There were the patent aerials, patent earths, spaghetti resistances, magic condensers, hedgehog transformers, special cat whiskers and patent crystals. Fortunes were made almost overnight by racketeers. Firms sprang up from private addresses and each spoke of its laboratories which usually consisted of the corner of the kitchen table. There were the quack journalists, too, who battened themselves like barnacles on to gullible editors who could not even solder a couple of wires together. The reputation of being a wireless expert was easily made in those days by talking about cat whiskers and antennae. Of all of the advertisers supporting radio journals in those days less than a dozen remain to-day.

For a period manufacturers deserted the constructor market for the more alluring receiver market, having made up their minds that the constructor market was about to die a natural death, and it was about that time that your editor founded PRACTICAL WIRELESS. It came into the field when there were eleven competitors and, of course, it had to face the fierce onslaught of defensive attack in print and out of it by those journals which resented what they considered to be an intrusion into their special domain. But F. J. C. is a tough warrior and one by one I saw him skittle over his competitors, until to-day only one of them remains. I think it is the only occasion where the newest journal in a particular field has obliterated by merit its older-established rivals.

The specification for the constructor receiver in these early journals was a catalogue. For the various components practically every maker was specified, and it was not surprising to find that a reader who selected his components from the lists found that either the connections were different from the published designs, that the characteristics were entirely different, thus upsetting the component values, or that they could not be accommodated on the baseboard at all.

Radio Valve Review-2

This Month Voltage Amplifying Pentodes are Dealt with

FOR voltage amplification in normal radio applications pentodes are used almost exclusively, for no other type of valve is capable of giving so great a stage gain when correctly operated in conjunction with suitable coupling circuits.

The reasons for this high performance as a voltage amplifier lie in part in the inherent properties of this type of valve, namely, a high mutual conductance and high internal resistance. For R.F. applications, however, and particularly for applications involving very high frequencies, performance is enhanced by the latest constructions and manufacturing techniques whereby the inter-electrode capacitances and the lead inductances and capacitances, all of which contribute to the damping of the associated tuned circuits, are reduced to very small values.

Furthermore, the performance of a valve at very high frequencies is affected by the transit time, that is to say, the time taken by the electrons in passing from the cathode to the anode. For very high frequencies the transit time may be in the same order of magnitude as the periodic time of the R.F. signal. This may result in the phase difference between the anode current and the signal voltage being less than the normal 90 deg. The anode current can then be considered as consisting of two components—one leading the signal voltage by 90 deg. and one in phase with the signal voltage. This latter component in the region between the cathode and control grid produces the same effect as a resistance connected between those electrodes, and exercises a damping effect upon the tuned grid circuit, thereby reducing the effective signal voltage.

In the latest miniature valves, made possible by the all-glass form of construction, the electron path and therefore the transit time is considerably reduced, thus minimising this particular form of damping.

Broadly speaking, there are two main classes of voltage amplifying pentodes. The first is a short grid-base, steep slope type for use as a "straight" amplifier, that is to say, without A.G.C. The other is a long grid-base, medium slope type having an I_a/V_g curve of suitable form for operation with A.G.C. Some of these pentodes have a single diode in the same envelope, for use either as demodulator or as A.G.C. rectifier.

Pre-amplifiers

With the general adoption of the superheterodyne principle for normal radio receivers, amplification at radio frequency is not used to the same extent as it once was,

although an R.F. stage is often included in the more expensive and de luxe models. But the use of a "pre-amplifier" or R.F. stage before the frequency changer has many advantages and is well worth the extra expense. Apart from the added range and selectivity which it gives to the receiver, such a stage greatly improves the signal-to-noise ratio. It also serves as a buffer to prevent oscillation from the frequency changer stage reaching the aerial circuit.

Some R.F. pentodes can be used with advantage in a frequency changer stage, one as the oscillator and another as mixer. Fig. 1 is a practical circuit for this application for use in television receivers, the two valves being Mullard Type EF91. The oscillator circuit consists of L_3 and C_7 , and is designed to resonate at 32 Mc/s. The first I.F. circuit, which resonates at 13 Mc/s., consists of L_2 , C_2 and R_2 .

In the following tables, abridged ratings and characteristics of current British voltage amplifying pentodes are given, together with their recommended applications. The list has been compiled from manufacturers' current data, and an endeavour has been made to ensure that it is as complete as possible. New types, however, are produced from time to time so that no list of this sort can remain up to date for very long. New introductions, however, are regularly reported elsewhere in PRACTICAL WIRELESS.

In order to include the maximum amount of useful information in the space available, the column headings in the various tables employ abbreviations in accordance with the latest standard symbols. For the convenience of those who are not familiar with these symbols, the following key is given:

Heater voltage, V_h	Filament voltage, V_f
Heater current, I_h	Filament current, I_f

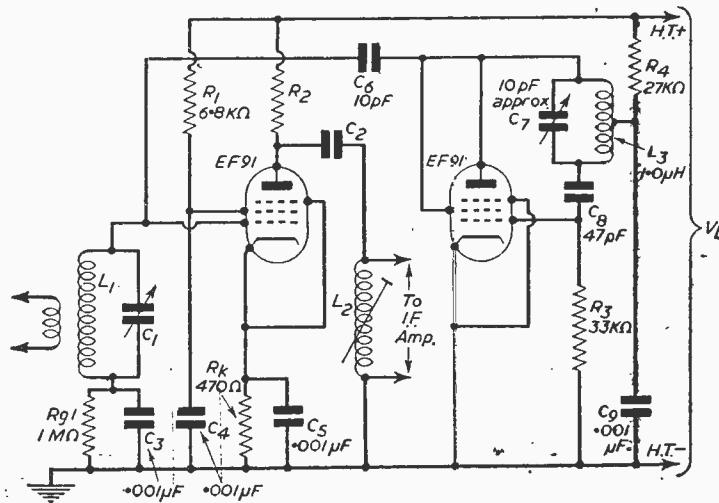


Fig. 1.—Typical television mixer circuit.

Input capacitance, i.e., the capacitance between the control grid and the cathode and any other electrodes operating at the alternating potential of the cathode C_{in}

Output capacitance, i.e., the capacitance between the anode and the cathode and any other electrode operating at the alternating potential of the cathode C_{out}

Feedback capacitance, i.e., the capacitance between the anode and control grid C_{a-g}

Anode voltage, V_a Screen voltage, V_{g2}

Control grid bias voltage, V_{g1}

Anode current, I_a Screen current, I_{g2}

Mutual conduction, G_m Anode resistance (internal), R_a

For variable-mu valves the limits of the range of grid bias adjustment and the corresponding range of mutual conductance is quoted.

It may be of interest at this point to suggest a rough guide for use when selecting or comparing voltage amplifying pentodes. Of two such valves, that with the higher mutual conductance is the more sensitive, and in this respect is the better valve. Of two valves of similar sensitivity, that with the lower values of inter-electrode capacitances is the better valve for use in high-frequency (or intermediate frequency) stages.

Type	Description or Application	Construction and Base	V_h V	I_h A	C_{in} $\mu\mu F$	C_{out} $\mu\mu F$	C_{a-g} $\mu\mu F$	V_a V	V_{g2} V	$-V_{g1}$ V	I_a mA	I_{g2} mA	G_m mA/V	R_a MΩ
MULLARD														
1—A.C. MAINS TYPES														
EQUIPMENT TYPES														
EF80	R.F. amplifier or mixer in television receivers	All-glass Naval (B9A)	6.3	0.3	7.5	3.5	0.006	170	170	2	10	2.5	7.2	0.5
EBF80	Double-diode variable-mu pentode. R.F., I.F. or A.F. amplifier	All-glass Naval (B9A)	6.3	0.3	4.0	4.6	0.002	250	85	2	5	1.75	2.2	1.6
EF91	R.F. amplifier or mixer in television receivers	All-glass B7G	6.3	0.3	7.0	2.0	0.008	250	250	2	10	2.55	7.65	1.0
EF42	R.F. amplifier or mixer in television receivers	All-glass B8A	6.3	0.33	9.5	4.5	0.005	250	250	2	10	2.3	9.5	0.44
EF41	Variable-mu pentode. R.F. or I.F. amplifier	All-glass B8A	6.3	0.2	4.7	8.0	0.002	250	100	2.5	6	1.7	2.2	1 0.022
EF40	Low noise pentode. R.C.-coupled A.F. amplifier	All-glass B8A	6.3	0.2	4.0	5.5	0.025	250	140	2	3	0.55	1.85	2.5
EAF42	Single-diode variable-mu pentode. R.F. or I.F. amplifier	All-glass B8A	6.3	0.2	4.0	5.0	0.002	250	105	2.5	6.35	1.75	2.15	0.021
EF50	R.F. amplifier	All-glass B9G	6.3	0.3	8.3	5.2	0.007	250	250	1.55	10	3	6.5	1.0
EF37	High gain, low microphony R.F., I.F. or A.F. pentode for pre-amplifier stages	Octal	6.3	0.2	5.5	8.5	0.02	250	100	2	3	0.8	1.8	2.5
EF37A	High gain, low hum, low microphony R.F., I.F. or A.F. pentode for pre-amplifier stages	Octal	6.3	0.2	5.5	8.5	0.02	250	100	2	3	0.8	1.8	2.5
EF39	Variable-mu pentode. R.F. or I.F. amplifier	Octal	6.3	0.2	5.5	7.2	0.003	250	100	2.5	6	1.7	2.2	1.25 0.0045
EF22	Variable-mu pentode. R.F. or I.F. amplifier	Octal (B8G)	6.3	0.2	5.5	6.4	0.002	250	100	2.5	6	1.7	2.2	0.022
REPLACEMENT TYPES														
EF92	Variable-mu pentode. R.F. or I.F. amplifier	All-glass B7G	6.3	0.2	4.5	7.0	0.004	250	200	2.5	8	2.1	2.5	—
EF54	High-slope pentode. R.F. amplifier	All-glass B9G	6.3	0.3	6.2	4.9	0.02	250	250	1.7	10	1.45	7.7	0.5
EF55	High slope pentode. R.F. amplifier	All-glass B9G	6.3	1.0	15.0	12.0	0.15	250	250	4.5	4.0	5.5	12.0	.055
EF36	General purpose voltage amplifier	Octal	6.3	0.2	5.5	8.5	0.02	250	100	2	3	0.8	1.8	2.5
EF9	Variable-mu pentode. R.F. or I.F. amplifier	Side Contact	6.3	0.2	5.5	7.2	0.02	250	100	2.5	6	1.7	2.2	1.25 0.0045
SP4	R.F. or I.F. amplifier or detector	5-pin	4.0	1.0				200	100	2	3			
SP4B	R.F., I.F. or A.F. amplifier or detector	7-pin	4.0	0.65	6.9	8.1	0.003	250	250	2.4	4	1.5	3.4	2.0
VP4	Variable-mu pentode. R.F. or I.F. amplifier	7-pin or 5-pin	4.0	1.0	12.4	10	0.005	200	100	2.0	4.5		2.3	10.0 0.002
VP4A	Variable-mu pentode. R.F. or I.F. amplifier	7-pin or 5-pin	4.0	1.2	12.5	16.2	0.006	200	100	2	4.25	1.8	2.5	1.4
VP4B	Variable-mu pentode. R.F. or I.F. amplifier	7-pin	4.0	0.65	5.35	8.0	0.0023	250	250	3	11.5	4.25	2.0	—
2—“D.C./A.C.” TYPES														
EQUIPMENT TYPES														
UF41	Variable-mu pentode. R.F., I.F. or A.F. amplifier	All-glass B8A	12.6	0.1	4.7	8.0	0.002	200	120	3	7.2	2.1	2.2	1.0 0.022

NOTE.—Valves with 0.1A, 0.2A and 0.3A Heaters may be operated with their Heaters in Series with the Heaters of other Valves of the same Heater rating.

May, 1950

Type	Description or Application	Construction and Base	V _h	I _h	C _{in}	C _{out}	C _{a-g}	V _a	V _{g2}	-V _{g1}	I _a	I _{g2}	G _m	R _a
			V	A	f μ F	p μ F	p μ F	V	V	V	mA	mA	mA/V	M Ω
UBF80	Double-diode variable-mu pentode. R.F., I.F. or A.F. amplifier	All-glass Naval (B9A)	17	0.1	4.0	4.6	0.002	200	85	2	5.0	1.75	2.2	1.0
UAF42	Single-diode variable-mu pentode. R.F. or I.F. amplifier	All-glass B8A	12.6	0.1	4.0	5.0	0.002	200	85	2 40.5	5.0	1.4	2.0	0.02
REPLACEMENT TYPES														
UF42	High slope pentode. R.F. amplifier in television receivers	All-glass B8A	21	0.1	9.5	4.5	0.005	170	170	2	10	23	8.5	0.2
SP13	R.F., I.F. or A.F. amplifier or detector	Side Contact	13	0.2	7.1	7.7	0.003	200	100	2	3.3	—	2.2	1.3
SP13C	R.F. or I.F. amplifier or detector	7-pin	13	0.2	6.9	8.1	0.003	200	200	2.2	2.5	0.9	2.8	2.5
VP13A	Variable-mu pentode. R.F. or I.F. amplifier	Side Contact	13	0.2	—	—	—	200	100	2.0 18.0	4.0	1.4	2.2	—
VP13C	Variable-mu pentode. R.F. or I.F. amplifier	7-pin	13	0.2	6.1	8.0	0.0023	200	200	2.0	9.0	3.6	2.2	—
3—BATTERY TYPES														
EQUIPMENT TYPES														
DF91	Variable-mu pentode. R.F. or I.F. amplifier	All-glass BTG	(V _f) 1.4	(I _f) 0.05	3.6	7.5	0.01	90	67.5	0 16	3.5	1.4	0.9 0.01	0.5
DAF91	Single-diode pentode. R.F., I.F. or A.F. amplifier	All-glass BTG	1.4	0.05	2.2	2.4	0.2	90	90	0	2.7	0.5	0.72	0.5
DF33	Variable-mu pentode. R.F. or I.F. amplifier	Octal	1.4	0.05	3.8	9.5	0.007	90	90	0 4	1.2	0.3	0.75 0.005	1.5
DF66	Sub-miniature. Voltage amplifier for Hearing Aids	Wire ends	0.625	0.015	1.7	2.4	0.2	22.5	22.5	1.05	0.05	0.015	0.1	0.2
DF70	Sub-miniature. Voltage amplifier for Hearing Aids	Wire ends	0.625	0.025	1.6	2.4	0.5	30	30	0	0.375	0.125	0.22	0.5
REPLACEMENT TYPES														
KF35	Variable-mu pentode. R.F. or I.F. amplifier	Octal	2.0	0.05	8.0	10.0	0.1	120	60	1.5 9.5	1.45	0.5	1.08 0.01	—
SP2	R.F. or I.F. amplifier or detector	7-pin	2.0	0.18	11.0	6.0	0.01	135	135	0	3.0	1.0	1.8	0.7
VP2	Variable-mu pentode. R.F. or I.F. amplifier	7-pin	2.0	0.18	10.7	6.3	0.007	135	135	0 7	3.0	1.25	1.5	0.4

NOTE.—Valves with 0.1A, 0.2A and 0.3A Heaters may be operated with their Heaters in Series with the Heaters of other Valves of the same Heater rating.

A Slow-speed Oscilloscope

A NEW instrument has been produced by A. E. Cawkell for observing and comparing slow waveforms, for which the normal oscilloscope is unsuited, and waveforms of frequency as low as .1 c/s may be easily observed on the long-persistence cathode-ray tube. Alternatively, the instrument may be used like a conventional oscilloscope, although the time base frequency normally extends upwards to 50 c/s only. Two beams are available which may be moved with respect to each other along any axis, and altered in amplitude and phase so as to be superimposed one upon the other. This enables the instrument to be used for waveform distortion comparisons at very low frequencies—a difficult procedure by any other method.

Design

Two completely separate D.C. amplifiers are incorporated with push-pull output incorporating shift controls, their outputs being electronically switched to provide two beams. Beam interaction is very small. The display is on a 6in. long-persistence cathode-ray tube with an orange filter.

A linear time base is included with automatic synchronisation of range .25 to 50 c/s. The time base (X) amplifier is also electronically switched enabling the beams to be independently shifted in the X direction by the controls. The time base

voltage and the X amplifier input are available externally.

All necessary power supplies, including 2 KV for the tube and a valve-stabilised general HT supply, are constructed in a separate matching container with multicore cable connection.

Specification

Power Requirements.— 210-250 volts A.C.

Tube.—6in. diameter, 5 secs. afterglow approx.
Orange filter fitted.

Amplifiers.—Two separate D.C. amplifiers with two electronically switched beams. Sensitivity, 100 mv for 2 cms. P.P. vertical deflection. Push-pull deflection.

Time Base.—Linear with automatic synchronisation. Frequency .25-50 c/s. Electronically switched X amplifier. Time base voltage and X amplifier input available externally.

Power Supply.—2 KV E.H.T., and valve stabilised (.5 per cent.) for general H.T. Housed in separate container.

<i>Controls.</i> —	
Y1 Gain	X Gain
Y2 Gain	Brilliance
Y1 Vertical shift	Focus
Y2 Horizontal shift	Time base & coarse

The price is £135, and the makers are A. E. Cawell, Electronic Engineers, 7, Victory Arcade, The Broadway, Southall, Middlesex.

The Practical Wireless Television Receiver-6

Aligning the Receiver, and Coil Details for Sutton Coldfield

ASSUMING that the raster has been accurately obtained as described last month, the receiver is now ready for alignment. This may be carried out in either of two ways—with or without a signal generator. The latter method is definitely to be preferred, as it eliminates all guess-work, and enables an accurate response curve of the receiver to be taken for checking purposes. As the method using the signal alone is simplest, it will be described first. All cores should be adjusted level with the top of the coil formers. Connect the aerial, and with brilliance right down and volume right up, turn up the contrast control until sound is heard from the speaker. If contrast has to be turned right up without hearing any sound, slowly turn up the brilliance control until some modulation appears on the screen. If the circuits are nearly in tune, then the contrast will have to be reduced to avoid overloading. As soon as some sort of modulation is seen endeavour

With a Signal Generator

The most satisfactory method of lining up rails for a good meter in addition to the generator. The anode circuit of the video amplifier should be opened and a meter shunted by a .001 μ F condenser inserted. A range of about 20-30 mA. is called for. An alternative is to use a meter with a full scale of 1 milliamp connected in series with cathode of the diode rectifier. Finally, the tube itself may be used, making all adjustments to obtain maximum black and white horizontal bars—keeping the input and brilliancy down to maintain the black and white bars of equal width. Peaking frequencies for the coils are as follows:

Vision	L1—45.25 Mc/s.
	L2—48 "
	L3—46 "
	L4—49 "
	L5—45 "
Sound	L6—41.5 Mc/s.
	L7—41.5 "
	L8—41.5 "

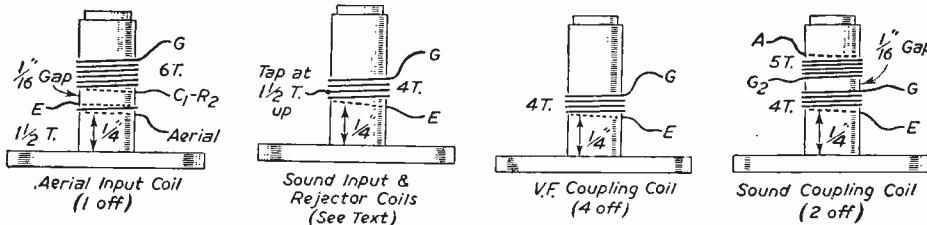


Fig. 1.—Details of the coils for Sutton Coldfield. Wire used is 28 S.W.G.

to adjust all cores to exactly 45 Mc/s or the vision frequency. This will be indicated by flaring on the tube face, but the brilliance control should be kept well down. Maximum flaring will indicate that all coils are more or less peaked at 45 Mc/s. The core of L4 should now be unscrewed $1\frac{1}{2}$ turns, and that of L2 1 turn. The core of L3 should be given about $\frac{1}{2}$ a turn out, and all sound coils (L6, L7 and L8) adjusted for maximum sound output with the coil of L1 unscrewed only a fraction. If the picture is now brightened, and contrast correspondingly reduced, it should be well detailed, although perhaps not at its best. To obtain maximum detail the test card C which is broadcast every morning (except Sunday) from 10 a.m. to 11 a.m. should be used. An endeavour should be made to obtain each of the central ruled squares clearly, without any white line following the right hand large white line. All the white ruled squares on the background should be truly square and of equal size (adjusted at the time base), and the correct setting of contrast and brilliancy will permit each of the central blocks to stand out clearly from black up to white.

Sutton Coldfield

The above frequencies are, of course, for the London transmitter, and for the Birmingham frequency alternative coils are required. In addition to the circuit as already shown one or two extra coils will be needed. Outside the "swamp" area only one extra coil is needed and this is inserted in the cathode circuit of V4 as shown in Fig. 2. Its exact position being on the side runner of the chassis as shown in Fig. 3. Note that it is inserted between the bias and feed-back resistor. At closer distances, or where sound break-through is experienced on vision a further similar coil should be inserted in the cathode circuit of V3. The 332 resistor may not be needed. The Sutton Coldfield frequencies are as follows:

Vision	L1—59 Mc/s.
	L2—61.75 "
	L3—60 "
	L4—61.75 "
	L5—59 "
Sound	L6—58.25 Mc/s.
	L7—58.25 "
	L8—58.25 "

A small point may be mentioned here in connection with L6—the sound input coil. As shown in the theoretical diagram in the January issue this has no core. In some localities this will be found quite in order, but in some cases a slight modification may be made to this particular coil. Firstly the core may be inserted and the coil peaked to provide the maximum sound output. In other localities it may be found that the sound output is not sufficient. An improvement may be effected by connecting a 47 pF silver-mica condenser across the coil—that is, from grid to chassis. This condenser is, of course, in addition to the iron-core.

Queries

There have been one or two queries raised concerning parts of the complete installation, and these have concerned only minor points which have not been clear to individual readers.

One correction should be made here. In the March issue it was stated that the separating screens in the vision unit should be soldered to pins 5 and 6 on the valve holders. As these pins are adjacent it is obviously impossible to carry out the instruction, and the diagram in the same issue shows that the pins concerned are actually 5 and 9—the latter figure unfortunately having become inverted in printing.

Another major query concerns the use of a 12in. tube. The scanning power of the receiver as designed will permit of a 12in. tube being used without any modification. An alternative mounting device will be needed, of course, and the tube is slightly longer. Brilliance should be sufficient, but if it is found that a slightly greater brilliance is needed this may be accomplished by increasing the H.T. supply to the E.H.T. unit. Resistance R44 will thus have to be modified. If it is simply reduced in

value the H.T. applied to the E.H.T. unit will rise, but unfortunately this point also feeds the EL3 output valve which is rated for a maximum of 250 volts and it will not tolerate too great an overload. Therefore, two separate resistors will have to be

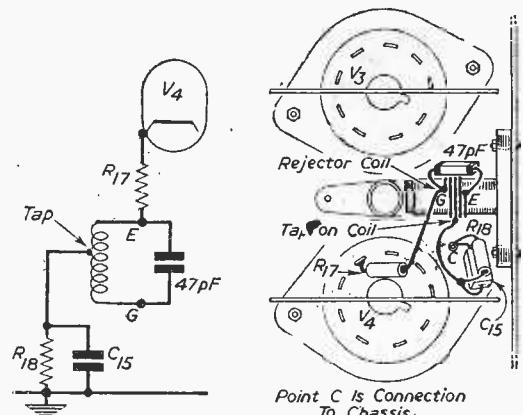


Fig. 2.—Position of the rejector coil in the cathode circuit of V4.

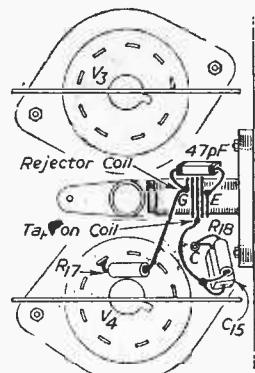


Fig. 3.—Actual position of the rejector coil on the chassis side runner.

used, one to reduce the main H.T. line to 250 for the output valve and the other to give a full 300 to the E.H.T. unit. Care must be taken not to overload this unit in view of the risk of insulation breakdown, and under all normal conditions the 7.5 Kv. provided is adequate for all but aluminised tubes.

Stereophonic Music in Cinema

AN experiment with stereophonic reproduction of music has been made in a cinema in Eindhoven by Philips. In contrast to previous demonstrations given in various places to invited guests or in private circles, this experiment was carried out as part of a normal public programme.

In this case stereophonic reproduction was applied for the music played during the interval. It is not likely to be applied for the films themselves for some time, because film producers must first decide to have the sound track recorded stereophonically, and although this is already possible technically, it seems that for the present the alterations necessary in the apparatus and the resultant cost will be considered objectionable. Moreover, the improvement to be expected in the ease of films will probably be less striking, since any faulty impression of the direction of the sound is more or less predominated and corrected by the strong visual impression of the picture. When music is played in the interval, however, direction is centred entirely upon the sound itself, particularly so when the music is reproduced mechanically, so that the audience is not distracted by the musicians.

It was therefore a promising experiment to apply stereophony for improving the reproduction under these circumstances, so as to eliminate as far as possible the mechanical nature of the music and thus afford the audience an opportunity to enjoy the music as much as if they were listening to an actual concert performance.

The music given was selected from a series of stereophonic recordings made by the Electro-Acoustic Department of Philips, by the magnetic method.

Audience Reaction

Everyone in the audience was given a questionnaire and of the 7,300-odd forms distributed more than 5,800 were returned completed and 500 only partly filled in. About 75 per cent. showed their appreciation, whilst less than 3 per cent. were definitely averse to the idea.

Although experience teaches that a statistical sounding of the public does not always lead to reliable results, and we shall therefore refrain in this case from giving any comment of our own upon the result of the inquiry, it nevertheless seemed desirable to give publicity to the experiment and its results by means of this communication. An application on a large scale can, of course only be expected when a sufficient variety of stereophonic recordings become available for this purpose.

Designing "Personal" Portables

Circuit Features of the Popular Mains-operated Bed-side and Similar Receivers

By W. J. DELANEY (G2FMY)

A TYPE of receiver which is receiving increasing attention to-day is the small mains-operated bed-side receiver. Many listeners have purchased a television receiver and have sold their broadcast receiver, and these small receivers enable odd items to be heard on "blind" radio when no television is being radiated. Some of the designs which manufacturers have produced are most interesting from a technical point of view, and, in fact, quite a number of readers have asked for details of construction for this type of receiver. It lends itself more to individuality of design than ordinary broadcast receivers, and amateurs may be forgiven for being in some doubt as to what type of circuit to adopt. An attempt will therefore be made to cover the main features of this particular type

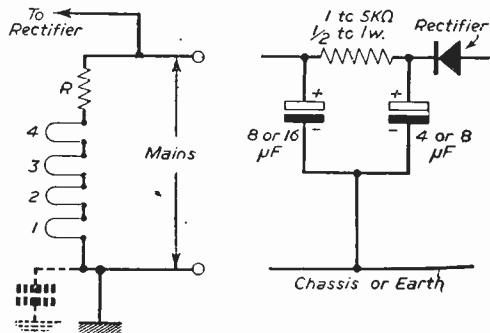


Fig. 1 (left).—Normal arrangement of heaters for A.C. or D.C. supply. Fig. 2 (right).—H.T. smoothing at its simplest.

of receiver so that those who wish may have some grounds upon which to base their constructional work.

Mains Feed

The first and most important feature is what type of mains feed to employ. This really boils itself down to the simple problem as to where excessive heat is to be placed, or whether to dispense with such heat. On the H.T. side there is nothing to worry about from a heat point of view, but on the heater or L.T. side there is quite a problem. If the receiver is to be of the A.C., D.C. type, then it is practically essential that the heaters shall be wired in series and some form of voltage dropper fitted to ensure that the heaters are operated at the correct temperature. (Fig. 1). The last heater in the chain (marked 1 on the illustration) should be the deflector in order to keep down the risk of hum. Resistance R is the problem here. It has to carry the current taken by the heaters (which obviously must all be of the same rating or otherwise adjusted by parallel resistors to ensure a constant current through the network), and must reduce the mains voltage to that required for the valves. For instance,

if the standard 6.3 volt heaters are employed, four in series would give a total of 25.2 volts, and therefore resistance R would have to dissipate a wattage equivalent to over 200 volts at .3 amps., or 60. Obviously a standard type of resistor is out of the question, and the customary method is to employ a line-cord which consists of a specially constructed flexible lead intended for connecting the receiver to the mains, and at the same time incorporating a resistance wire wound round a length of asbestos string. Naturally this gets quite warm, but to reduce the length and rating of it one uses valves with a higher heater voltage rating. Generally the early valves are of the 12 volt type, whilst the output valves (and half-wave rectifier which is needed for the H.T. supply) are usually rated at 35 or 40 volts. This arrangement gives heat outside the cabinet and enables a more compact layout to be obtained, but the line-cord may run quite hot and this is not always convenient.

Cabinet Heat

An alternative arrangement consists of using higher rated A.C./D.C. valves throughout, and then using one of the small special mains-droppers in the cabinet. But even these run fairly warm and it is generally necessary to put a sheet of asbestos inside the cabinet to prevent damage or fire risk, and obviously the cabinet cannot be made too compact.

Where the receiver is designed for A.C. mains only, however, the problem is much simplified, but again there are one or two alternatives to be considered. The series heater scheme may still be adopted, using the line-cord, but if there is no intention of using D.C. mains supplies this may be dispensed with and a simple mains transformer employed. These are available at quite a low figure, either new or ex-service, and are compact. Furthermore, they enable standard (6.3 v.) valves to be used throughout and do not call for the high-voltage heater type of valve. In addition, as there is now no need to worry about heater current the rectifier may be of the metal-oxide type.

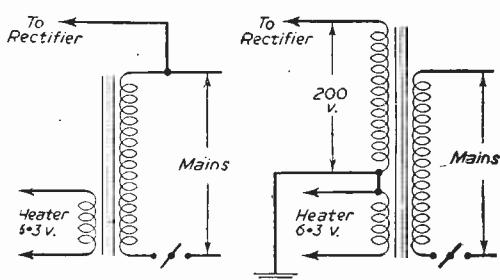


Fig. 3 (left).—Using a transformer for the heater supply. Fig. 4 (right).—Isolating the receiver from the mains by a single transformer.

These take up much less room than a rectifying valve, and generally speaking a more compact type of receiver may be constructed, in spite of the use of the transformer.

H.T. Supply

There are, however, two alternatives still available with this arrangement. The mains input may be taken direct to the rectifier, in which case the receiver is "live" to the mains, or the heater transformer may be of the type having a further secondary winding rated at 200 volts or so. In this way the receiver is isolated from the mains supply, and there is no undue increase in bulk. There is no heat to worry about and ordinary flex may be used to connect the set to the mains.

Other Design Features

The removal of heat from the cabinet enables the receiver to be designed around certain components which could not otherwise be employed. Small electrolytes may be placed where desired for efficiency without the risk of breakdown due to high temperatures; more efficient (superhet) circuits may be used without the risk of frequency drift and so on. For mains smoothing in these small

receivers it is not necessary to employ a smoothing choke. The loudspeaker generally employed does not exceed 5 in. in diameter and the bass response of these is so limited that slight residual hum passes unnoticed. Therefore a simple low-rating resistor is used for smoothing, in association with the usual canned electrolytics. Here space is saved by using the "two-in-one" type of unit.

The question as to whether to employ a straight or superhet circuit is bound up with the manner in which the receiver is to be used. If required for general listening a superhet is obviously desirable, but if only used as a stand-by for news, etc., or for the odd items not available on television, a straight two-station circuit is obviously good enough. Another point here is the type of aerial to be used. With a straight circuit there will not be much gain, and some difficulty might be experienced with the aerial. A length of throw-out wire may have to be fitted and this will limit the portability of the receiver. On the other hand, a superhet will enable the set to be used with only a small amount of wire inside the cabinet, or even a small wound frame built in, and will then provide a range of stations or at least, adequate volume from the locals, and it may be moved from room to room and plugged in as conveniently as an ordinary table lamp.

Mobile Broadcast Recording Van

E.M.I. FACTORIES, LTD., were recently commissioned by Radio-Luxembourg to supply a broadcast recording van suitably equipped for recording broadcast programmes on magnetic tape.

The interior of the van has been laid out in such a manner as to allow unhindered working by the recording engineers and is divided into two separate compartments. The forward one contains the recording equipment and operator's position, the rear compartment housing the cables, cable entries, drums, etc. therefore, no loose cabling is, necessary in the operating compartment at any time, and all input and output interconnecting cables are concealed in wall ducts.

Special translucent roof windows allow the operator to work in natural light during the daytime, and there is provision for artificial lighting from A.C. mains supplies. The interior of the van is heated by an H.M.V. Cavendish convector heater.


Tape Recorders

The main items in the equipment are two of the well-known E.M.I. magnetic tape recorders; these, working together, enable high-fidelity recordings of any duration to be made. Additionally, a disc recorder and replay desk are fitted, with provision for operation at 78 or 33½ r.p.m.

The control panel comprises a five-channel microphone pre-amplifier with individual fading, programme meter and 'phone or loudspeaker monitoring facilities. This control console is so designed as to give the operator complete flexibility

of control and interconnection of the various items of equipment, and full dubbing, mixing and cross recording facilities are available, enabling any type of studio work to be carried out. In addition, the complete console can be lifted out and carried to the recording site when the distances involved make it undesirable to run long microphone cables.

Two high-quality loudspeaker units are provided for remote replay purposes on the recording site. Communication between the van and the recording site is by a "talk-back" system and the recording signalling system consists of three coloured signal lamps, buzzers and a field telephone. Power supply is taken on site from suitable A.C. supplies, but stand-by lighting may be operated from the van's electrical system.

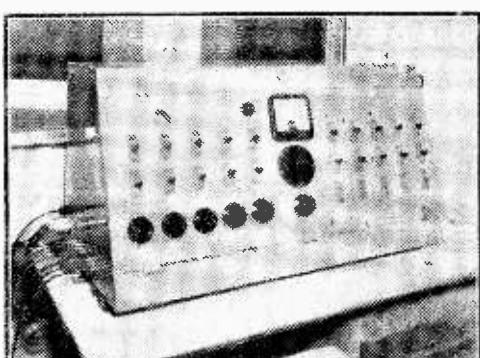

Close-up of the engineer's control panel in the recording room of the mobile recording unit. Another picture appears on page 184.

PLAN YOUR CAREER

RADIO - TELEVISION
and other INDUSTRIAL ELECTRONIC subjects

ELEMENTARY & ADVANCED COURSES

DAYTIME

- Principles and Practice of Radio — 1 year.
- Telecommunication Engineering — 2 years.
- Electronic Engineering — 3 years (including one year's practical training in E.M.I. Factories) — leading to C & G full Technological Certificate.
- Marine and Air Radio Officers' Course (for P.M.G. Licence),

also HOME STUDY

- Radio ● Television ● Industrial Electronics
- Maths ● Physics

Write for FREE BOOKLET to Dept : 32

E.M.I. INSTITUTES

10 PEMBRODGE SQUARE, NOTTING HILL GATE,
LONDON, W.2.

Telephone: BAYSWATER 5131/2

Associated with
"H.M.V."
MARCONI
PHONE
COLUMBIA
ETC.

E.166B

AN ENTIRELY NEW AUTOCHANGER UNIT



MARCONI PHONE AC 100 M

● Lightweight pick-up ensures highest quality reproduction with minimum record wear. ● For 50 cycle A.C. mains supply, 100-130 or 200-250 Volts. ● Maximum reliability. ● Handles up to ten 10" or 12" records (unmixed). £7.0.0 plus £3.0.8 Tax. Matching Transformer 10/- (no purchase tax). If desired the unit can be supplied without the transformer.

MARCONI PHONE

THE GREATEST *Marconi* NAME IN RADIO

M168A

The Marconi Phone Co. Ltd., Hayes, Middlesex.

RESISTANCES. A parcel containing 100 popular assortments values for t watt types, 8¹/₂ or 1 watt.

COILS. Denco T.R.F. Matched pair Medium and Long Waves, 6¹/₂ pair. Weymouth T.R.F. Matched pair M. and L. Waves, 9¹/₂ pair. Superhet Matched pair S. M. and L. Waves, 8¹/₂ or 11¹/₂ pair. All types Wearite "P" coils, 3¹/₂ each, in stock. Weymouth Midget 11in. x 1¹/₂ dia. Iron Core. Aerial H.F. or O.S. 3¹/₂ each, or Denco "Maxi Q".

OSMOR MIDGET COIL PACK.

Size 31in. x 21in. x 11in. covering S.M. and L. Waves. Coils wound on Polystyrene Formers with adjustable Iron Cores, ensures efficient performance. Factory wired and attested. Price including full circuits for Superhet 465 Kc. Unit, 33/-; For T.R.F. circuit covering M. and L. waves, 30/-.

THE BATTERY PORTABLE SUPERHET PACK including ready wound Frame Aerial available at 37/-.

OUTPUT TRANSFORMER. — Stern's Midget 11in. x 1in. x 1in., ratio 60:1, 4/6 (or ratio 90:1, 4/6). Elstone Multi-ratio (over 12 ratios, some C.T.), 5.6 watts, 7/6. Stern's Heavy Duty Multi-ratio, all C/Tapped, handles 13 watts and suits P.X.4, GL6s, etc., 25/6.

L.F. CHOKES. Midget 10 henry 250 ohm 40 mA. 3.6 : 15-20 henry 250 ohm 60 mA. 6.6 : 20 henry 300 ohm 100 mA. 12/9 : 5 henry 250 ohm 230 mA. 18.6 : 20 henry 250 ohm 120 mA. 18/6 : 9 henry 230 ohm 120 mA. 8.6.

ALL MINIMUM CHASSIS. Substantially made of gauge 18 S.W.G. with four sides, 7in. x 3in. x 2in., 3.3 x 9in. x 5in. x 2in., 10in. x 6in. x 21in., 4.11 : 10in. x 8in. x 21in., 5.6 : 12in. x 9in. x 21in., 6.8 : 14in. x 9in. x 21in., 6.11 : 16in. x 8in. x 21in., 7.9 : 16in. x 10in. x 31in., 8.6.

SELENIUM RECTIFIERS. 18. H.T. H. Wave, 250 v. 50 mA. 5/-; 200 v. 100 mA. 5/9/-; 230 v. 100 mA. 7.6, 12 v. 11 amp. 12/6, 12 v. 3 amp. 21/-, 12 v. 5 amp. 25/-, 24 v. 3 amp. 23.6/-.

CHARGER TRANSFORMER. Each has input of 230 volts, outputs 24 v. (tapped 15 v., 9 v. and 4 v.) x 3 amp., 21.6 : 39 v. (tapped 15 v. and 9 v.), 3 amp., 22 : 15 v. (tapped 9 v.) x 3 amp., 14.3 : 15 v. (tapped 9 v.) x 6 amp., 19.6 : 16 v. 8 amps., 37.6/-.

FILAMENT TRANSFORMER. Input 230 volts, output 6.3 v. 14 amp., 7.6 : 4 v. 11 amp., 7.6. Input 200/250 v., output

4 v. (C.T.) 11 amp., 4 v. 2 amp., 6.3 v. 2 amp., 17.6.

PRACTICAL WIRELESS "IMPROVED AUXILIARY" 3 VALVE (plus Rectifier) A.C./D.C. MAINS T.R.F. RECEIVER. We can supply all the components, including valves, drilled chassis and M'coil speaker, to build this midget set, size 7in. x 4in., as specified in the November issue, at a total cost of £4/17/6. Reprint of detailed assembly instructions (incl. practical layout) and circuit supplied separately for 9d. incl. postage.

STERN'S BATTERY PORTABLE "PERSONAL" KIT. A complete kit of parts to build a Midget 4-Valve All Dry Personal "Set".

Consists of regenerative T.R.F. Circuit, employing Flat Tuned Frequency with Denco Iron Dust Coated Coil, thereby ensuring maximum gain for Single Tuned Stage, covering Medium Waveband.

Valve Line-up : IT4 (R.F. amp.), 1T4 (Detector), 1S5 (1st A.F.), and 1S3A (Output). Includes 31in. P.M. Speaker and with chassis already drilled and shaped.

Consumption of only 7 mA ensures long battery life.

The kit is designed for a cabinet, minimum size 6in. x 4in. x 3in. Detailed Building Instr. and circuit, including Practical Layout, included with each Kit, make assembly very easy

(supplied separately for 1/6).

PRICE FOR COMPLETE KIT. £3/18/9 (plus 16/7 P.T.). Suitable Unpolished Cabinet, 12/9 : E. Ready B114 Telephone 9.7.

The MIDGET A.C. MAINS 2-VALVE RECEIVER. All the Components to build this popular Set, as specified in a technical publication, can be supplied complete for £3. Reprint of detailed building instructions, giving practical layout and circuit supplied separately for 9d. incl. postage.

A COMPLETE SET OF COMPONENTS to convert the midget A.C. mains 2-valve to a 3 valve set covering L. and M. waves 1/4

available for 35/-, reprint of assembly details available for 9d. incl. postage.


The 3-valve A.C. mains receiver circuit, as published in Wireless World. All the components to build this set covering long and medium waves can be supplied for £4/7 6. Reprint of assembly instructions (supplied separately). 9d. incl. postage.

★ Send 3d. stamp for our Comprehensive Stock List, which now shows various bits of parts and circuits available. When ordering please cover packing and postage.

STERN RADIO LTD., 109 & 115, FLEET STREET, E.C.4.

Telephone :
CENTRAL 5814 & 2289

May, 1950

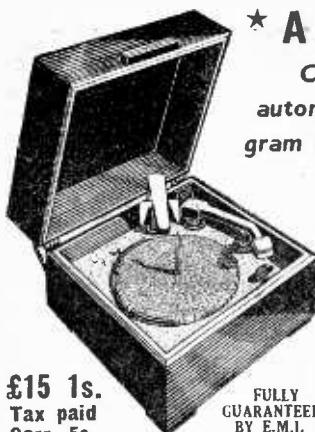

£15 1s.
Tax paid
Carr. 5s.

* A DREAM COME TRUE!

Convert your radio into an automatic radio-gram for only **£15. 1s. 0d.**

YOU can convert your radio, old or new, large or small, into a first-class Automatic Radiogram, by means of this WONDERFUL automatic record-player incorporating a unit made by E.M.I. (Electrical and Musical Industries). The player is housed in a dignified polished table cabinet. Autochange mechanism sturdily constructed for long life and reliability. Lightweight, miniature moving iron pick-up gives reproduction of highest fidelity. The tray will handle 10in. or 12in. records and can accommodate TEN discs. ALL OPERATIONS EFFECTED BY A SINGLE CONTROL KNOB.

A record can be stopped when part-way through, the next record being automatically placed on the turntable.

FULLY
GUARANTEED
BY E.M.I.

Packed and sealed by manufacturers.

£5 down & 6 monthly payments of 37/6



**DO EVERY
SOLDERING
JOB—better,
faster, cheaper
with a BURGOYNE
Instant Heat
Solder Gun**

**Maker's list
price 79/6 Our Price 52/6 post
free**

Press the button, count seven, and solder. Bit remains at soldering heat until you release pressure, when it cools instantly. No waiting to warm up or cool down—no element to burn out—no risk to crack or splinter—no risk of shock. £10,000 was spent on the design of this famous tool. For A.C. mains 200-250V. EVERY SERVICE ENGINEER MUST have one! An export order that missed the last boat to S. Africa makes this offer possible.

Special Notice

This solder gun is offered to you in the original manufacturer's carton carrying their seal. We guarantee each Burgoyne Solder Gun for TWO YEARS. We cannot service or guarantee any gun purchased elsewhere.

MODULATORS—TYPE 53

These radar Modulators represent one of the best bargains that we have offered. They contain nine valves, the types being 3 CV57; 1 VU508; 1 VU120; 2 VR63; 1 6V6; 1 807; a 24v. Blower Motor suitable for conversion for use on A.C. mains, 18 assorted condensers, including 1 KV., 10 types, 30 assorted resistors from 50 watt to 1/2 watt types, 3 high-voltage variable resistors, etc. The whole is contained in a case measuring 19in. x 12in. x 9in.

A real "GIVE AWAY" Bargain at **17/11**
(For callers only)

BRAND NEW IN ORIGINAL CARTONS

A.C. REVERSIBLE INDUCTION MOTORS

This motor is a 50v. 50 c/s. 3-phase motor rated at 1/2 h.p. and is sturdily constructed, being rated for continuous use. By means of the resistor and condenser included with the motor, it can be operated from the standard 200-250 A.C. mains supply. Full wiring instructions are given, also details of securing rotation in either direction.

Price 30/- carriage paid

Terms : Cash with order

**MAIL ORDER SUPPLY CO.,
The Radio Centre**

33, Totteham Court Rd., London, W.1
Telephone : Museum-6667-8-9

GARDNERS RADIO Ltd

will be pleased to send you a complimentary copy of their NEW 28 PAGE BROCHURE describing the
"SOMERFORD"
MAINS TRANSFORMERS
including the new types
"BURLEY" and **"HENGIST"**

POST THIS COUPON TO-DAY

To: GARDNERS RADIO LTD.,
SOMERFORD, CHRISTCHURCH, HANTS.

Please send me your New 28 Page Brochure.

Name

Address

A NEW CONVERTER for 1950

Model No. 230/110A £10. 15. 0

Incorporating many new and practical improvements to meet fluctuating mains-voltage supply.

Specification : Input, 180/270 volts D.C.; Output, 230 volts A.C., 110 watts. R.F. and L.F. Suppression. Frequency : 50 and 60 cycles.

Plug-in Vibrator, easily changed. Access to interior for tapping transformer by baseplate removal.

Developed by the specialists in Vibratory conversion. Famous since 1937.

Literature and supplies available from

VALRADIO LIMITED,
57, FORTRESS ROAD, LONDON, N.W.5
GULLIVER 5165

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925.

SPECIAL OFFER

New $\frac{1}{2}$ /1 watt Resistors, popular make, 25 standard values.

ASSORTMENT OF 100 FOR 15/-

(List Price value 50/-)

This is an opportunity not to be missed. Stock your workshop now while stocks last.

COVENTRY RADIO
189, DUNSTABLE RD., LUTON, BEDS.

Stabilised Power Supplies

An Explanation of the Series-fed Type

By E. N. C.

THE stabilised power supply unit, to a large number of radio enthusiasts, seems to have an air of mystery around it, and it is the purpose of this article to try to explain the action of the stabilised unit and point out some of its useful features. There are two main types of electronically stabilised units; these are the shunt stabiliser and the series stabiliser. The shunt stabiliser works by virtue of placing a load on the power unit which is always in opposition to the external load; for example, when the external load decreases the shunt load increases and vice versa, this tending towards a constant total load on the power unit, which therefore has a reasonably constant output voltage. The series regulator type of stabiliser is the one most commonly used and it is this type which will be discussed here. First of all, what is the stabilised power supply unit? Well, excluding batteries, it is the nearest approach to the perfect generator or power unit. Within its operating range the stabilised unit will deliver an output voltage which is independent of the input voltage, and also independent of the load current. The usefulness of this can be appreciated when one considers such things as (1) oscillators, where a drift in H.T. can cause a drift in frequency; (2) D.C. amplifiers, where a drift in H.T. can cause an error in the output; (3) modulator units, where a high power unit internal impedance will cause distortion on heavy modulation, etc.; in fact, any piece of equipment where the performance is deteriorated by having an imperfect power supply.

Principle of Operation

The series-regulator type of stabiliser is really nothing more than a cathode follower stage with an amplifier between its cathode and grid, and it is with the aid of the cathode follower that its principles of operation will be explained. The importance of the amplifier section will be realised

as the article goes on. The diagram Fig. 1, shows a set of characteristics of a heavy-duty triode having the following constants: (1) anode dissipation maximum 15 watts; (2) $g_m = 10 \text{ mA/V}$; (3) $\mu = 12.5$; (4) $R_a = 1,250 \Omega$. The curves, as can be seen, are anode current against grid volts for three values of anode volts. The circuit Fig. 2, shows a cathode-follower stage being fed with H.T. from a generator or power supply having an internal resistance of $1,000 \Omega$, and an output

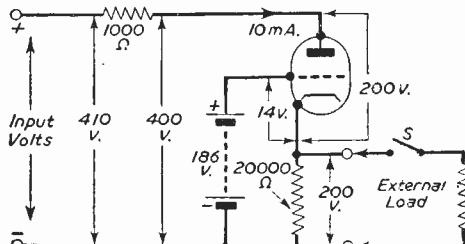


Fig. 2.—A cathode-follower stage.

voltage of 410 v. We shall see how the cathode follower reduces the effective internal resistance and maintains the output voltage reasonably constant in spite of variations of H.T. input volts and output load current. From the circuit we see that the cathode resistance is $20,000 \Omega$, the anode current 10 mA, and the output voltage consequently 200 v. The 10 mA. current causes a 10 v. drop in the $1,000 \Omega$ internal resistance of the generator, causing the terminal voltage and therefore the anode to earth voltage of the valve to be 400 v. A battery of 186 v. is connected between grid and earth and therefore the actual grid bias voltage—that is, the voltage between grid and cathode—is -14 v. We can see that these conditions agree with the valve characteristics, an anode voltage of 200 v. and a bias of -14 v. giving an anode current of 10 mA. An external load is available which is connected across the output by closing the switch S. Now let the load be of such a value as to draw a current of 50 mA, and on closing switch S let us see what happens. First of all the terminal voltage of the generator will drop from 400 v. to 350 v. because, as one can see 50 mA. through $1,000 \Omega$ produces a drop of 50 v. The output voltage of the regulator will tend to fall below its 200 v. level, but in doing so it causes the grid-cathode bias on the valve to decrease, therefore allowing the valve to pass more current. The total current through the valve is now 60 mA, and the anode voltage has dropped to 150 v. because of the terminal voltage dropping from 400 v. to 350 v. We shall now see from the valve curves what the grid-cathode bias is to suit these new conditions, and therefore arrive at what valve the output voltage comes to rest. Now from the curve of $V_a = 150$ v. and $I_a = 60$ mA. we see that the grid-

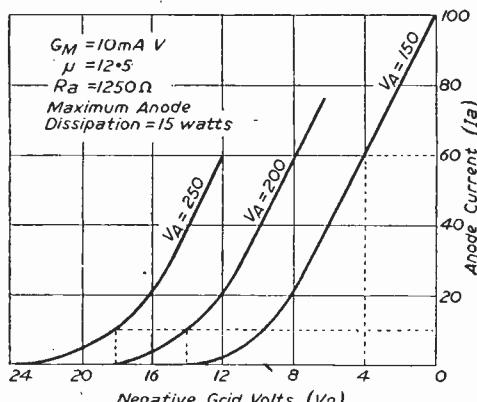


Fig. 1.—Characteristics of a heavy-duty triode valve.

cathode bias is -4 v., which means that the output voltage has fallen to 190 v., that is, a drop of 10 v. has occurred. Now the output impedance or output resistance is equal to the change in voltage divided by the change in current, which in this case is $\frac{10\text{v.}}{50\text{ mA.}}$ which equals 200Ω . We therefore

see that the regulator valve or, if you like, cathode-follower has reduced the effective output impedance from $1,000 \Omega$ to 200Ω . How the amplifier reduces it still more we shall see later. Approximate values are given so as not to confuse the argument.

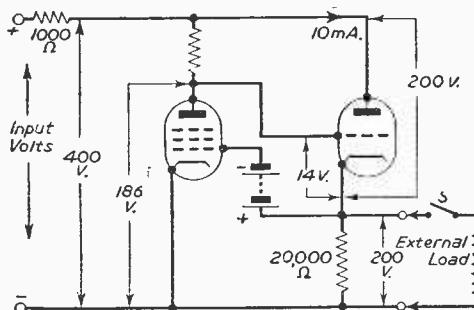


Fig. 3.—A high-gain pentode added to the circuit of Fig. 2.

Incidentally, the output impedance of a cathode-follower is given mathematically as being approximately equal to $\frac{R_a}{\mu}$ or $\frac{1}{gm}$ which in the case of

this valve should be $\frac{1}{10\text{ mA/v.}} = 100 \Omega$ and not 200Ω

but so as not to confuse those who have seen that formula it should be pointed out that it only holds good if you are always working on the straight portion of the valve curves and there is no $1,000 \Omega$ generator resistance.

Independent Voltages

This you can check for yourself. Let us now see just how independent the output voltage is upon variations of the input voltage. We will return to the position when switch S is open and the valve is passing its normal 10 mA. with an anode-cathode voltage of 200 v. Let us assume that the terminal voltage rises from 400 v. to 450 v. The anode-cathode voltage of the valve will rise to 250 v. and the extra current that flows through the $20,000 \Omega$ cathode resistor will tend to make the output voltage increase. But this increase in output voltage is causing the grid-cathode bias of the valve to be greater, this tending to restrict the rise in current. We will consult the curve of the valve for $V_a = 250$ v. and find the

value of bias required to keep the current as near as possible to 10 mA. According to the curve this value of bias is -18 v. and therefore the output has risen to 204 v. This represents a rise in the output of only 4 v. for a rise in the input of 50 v. We shall see later on how this variation is restricted even more with the aid of the amplifier. It is now becoming apparent that the cathode-follower is doing its best to deliver a constant output voltage of 200 v. regardless of variations of input volts and load current, which is indeed what the perfect power unit should do. As you will have probably realized by now, what the past explanations boil down to is that the effective resistance of the regulator valve varies to suit the input voltage and output current conditions at all times. We shall now see how with the aid of an amplifier the cathode-follower gives almost perfect stability. In the circuit Fig. 3, we see our same cathode-follower, but with the addition of a high-gain pentode amplifier between its cathode and grid. The original regulator valve grid battery voltage of 186 v. has now been replaced by the anode-cathode voltage of the amplifier valve. The battery which is connected between the cathode of the regulator valve and the grid of the amplifier valve is necessary in order to bias correctly the pentode amplifier valve; if this battery were omitted the grid-cathode bias of the valve would be $+200$ v. and the valve would obviously be saturated, and consequently would not operate. Now let us assume that the gain of the valve from grid to anode is 200; this is a gain which can easily be got as pentodes can give a gain of over 400. If we now revert to our original experiment of pressing switch S to put our 50 mA. load on the output, we saw with the original circuit that a change in bias of 10 v. was required on the regulator valve in order to give the extra current. But now look at the new circuit; the output has only to drop $\frac{19}{200}$ or 0.05 volts to give the extra current because the amplifier which has its grid connected to the output is amplifying 200 times, any change which is occurring and this amplified change is being applied to the grid of the regulator valve. Our 10 v. change in grid-cathode bias has therefore resulted

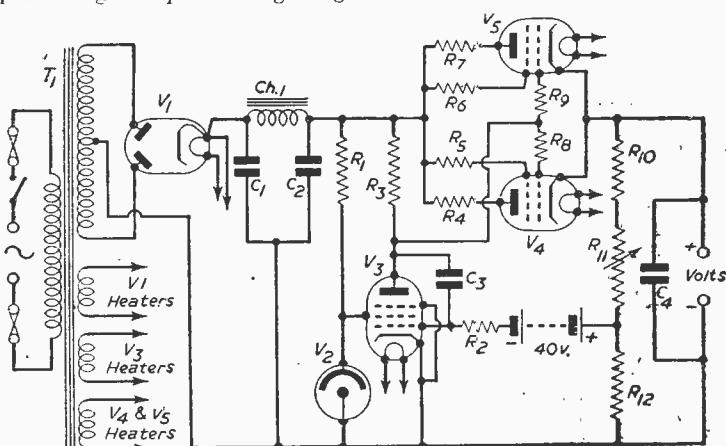


Fig. 4.—A practical circuit incorporating the features dealt with in this article.

from a drop in the output of only 0.05 volts. Let us now calculate the output impedance which is the change in voltage divided by the change in current. This is equal to $\frac{0.05 \text{ v.}}{50 \text{ mA.}} = 1\Omega$. Our unit

therefore now has an output impedance of only 1Ω instead of the original $1,000\Omega$. If we now look at the second experiment which was to see how the output was proofed against input variations, we saw that the output rose by 4 v. to nullify the

COMPONENT LIST FOR FIG. 4

T1	=Mains Transformer Primary 240 v. 50 cycles.
	Secondary 350-350 150 mA. + 4v.-2.5
	amps. (V1)+4 v. 1 amp. (V3)+4 v. 4 amps.
	(V4-5).
C1	=8 μ F. 450 v. working.
C2	=16 μ F. 450 v. working.
C3	=350 pF.
C4	=8 μ F. 450 v. working.
R1	=20,000 Ω 6 watt.
R2	=47,000 Ω $\frac{1}{2}$ watt.
R3	=150,000 Ω $\frac{1}{2}$ watt.
R4	
R5	{ 47 Ω $\frac{1}{2}$ watt.
R6	{ 47 Ω $\frac{1}{2}$ watt.
R7	
R8	{ 47,000 Ω $\frac{1}{2}$ watt.
R9	{ 47,000 Ω 1 watt.
R10	
R12	{ 4,700 Ω 1 watt.
R11	=20,000 Ω 4 watt.
V1	=UUS or any equivalent.
V2	=Cossor S130.
V3	=SP41 or VR65A or any equivalent.
V4/5	=Mazda PEN44 or any equivalent.

input change of 50 v. But, as we can see with the amplifier in circuit, the output will only have to change by $\frac{4}{200}$ or 0.02 volts to nullify the input change of 50 v. And that is really all there is in the operation of the series regulator type of stabiliser

A Practical Unit

A circuit of a practical unit and some points of interest on the design and limitations of such units are given. Fig. 4 shows a practical unit capable of giving 100 mA. over the range 100v.-250 v., the output voltage being controlled by R11.

Output Power

The maximum output power ignoring the mains transformer and rectifier is governed by the anode dissipation of the regulator valves and the maximum safe running current is determined by the lowest output voltage. This is shown as follows. The anode-cathode voltage on the regulator valves is equal to the input voltage minus the output voltage and is therefore highest when the output voltage is at its lowest. Anode dissipation is equal to anode-cathode volts times anode current, and so for a fixed maximum dissipation the anode current must come down if the anode volts go up. Therefore the maximum safe running current on the regulated unit is the current which gives the rated anode dissipation at the lowest output voltage, as this corresponds with the highest regulator valve anode voltage. It is obvious that if we could keep the anode-cathode volts at a reasonably low value we could increase the output current

before overrunning the valves. Some modern units achieve this by using grid-controlled rectifiers and using a two-gang output in control, so that when the output volts are varied the input volts are varied in sympathy, so maintaining a reasonably constant anode voltage on the regulator valve. The rear stabiliser feeding the screen of the amplifier or central valve as it is often referred to prevents long-term drift of the output volts. It can be seen that if the screen is not held stable any fluctuation of rectifier volts would communicate a signal to the output by virtue of the screen. The output fluctuation would be equal to the input fluctuation present at the screen, divided by the control grid to screen grid voltage factor. The anode and screen resistors on the regulator valves and the anode to grid condenser on the control valve are included to suppress any tendency to self oscillation.

Radio at the Wheel

ON the new Philips MotoRadio Model 574V the reception compares favourably with that obtained with domestic radio receivers, and the quality and fidelity of reproduction is fully retained under all kinds of motoring conditions. Of extremely compact design, and styled to suit every class of modern car, this new Philips MotoRadio does, indeed, bring radio at the wheel close to the perfection of radio in the comfort of the home.

The marketing of the new Philips receiver is being carried out under the guidance of Mr. Alan Knight, who is well known to all motor manufacturers and dealers as a pioneer of car radio in this country. From the year 1932 when he first introduced car radio in this country, Mr. Alan Knight has become fully conversant with all the many problems associated with car radio and its distribution, having studied this aspect of the business in the U.S.A. As the new Manager of the Philips Motor Radio Department, he thus brings with him a wealth of commercial and technical experience.

In the design of the new MotoRadio Model 574V, particular attention has been given to the ease of installation and servicing. An attempt has also been made to obtain the best possible appearance and performance so that the equipment will match and blend with the interior of even the most expensive cars, and will at the same time meet the needs of the most discriminating user of motor radio.

The equipment comprises two units, the radio unit proper, and a separate loudspeaker unit contained in a circular metal cabinet. The radio unit is designed for fitting immediately below the lip in the centre of the car's instrument panel, or in the space available in those cars where special provision has been made for the installation of radio. The controls are thus within easy reach of the driver. The loudspeaker may, if desired, be removed from its case and mounted behind the speaker grill provided in some cars. Both units have a pleasing hammered silver-grey finish, and their dimensions and weights are as follows:— Radio unit : (back), 4 $\frac{5}{8}$ ins.; height (front), 3 $\frac{3}{8}$ ins.; width, 6 $\frac{1}{4}$ ins.; depth, 10 $\frac{1}{2}$ ins.; weight, 13 $\frac{1}{2}$ lb. Loudspeaker unit : diameter, 8 ins.; depth, 3 $\frac{1}{2}$ ins.; weight, 2 $\frac{1}{2}$ lb.

THIS receiver was intended to provide entertainment from a large selection of stations, with volume and quality ample for all domestic purposes, and it fulfills these requirements well. It uses a radio-frequency amplifier before the frequency-changer and two intermediate-frequency stages, thus assuring a high degree of selectivity and sensitivity, while the push-pull output stage enables distortion in this section to be kept down and provides a satisfying reserve of power. By employing iron-cored, ready-made coils and a tuning scale to suit, difficulties in this direction are reduced and it is not difficult to align the whole receiver without any service oscillator being necessary. But this will be covered in detail later; it should meanwhile be noted that all coils and I.F. transformers throughout the circuit are iron-cored, and that the cores are adjustable. This explains why padding and I.F. transformer condensers are fixed components.

9-valve All-w

A Compact Mains-operat

By F. C.

Actually, the circuit lends itself well to construction in a simplified form. As a guide to the constructor who may be interested in this point, the original receiver was built up over a period, beginning with a five-valve circuit. If a chassis about 8in. by 12in. is used no alteration to the work already done will be required when extra stages are added to make up the complete circuit as described. The five-valve arrangement consisted of frequency-changer, I.F. amplifier, double diode, output and rectifier. (This is similar to many commercial popular superhet.) Long- and

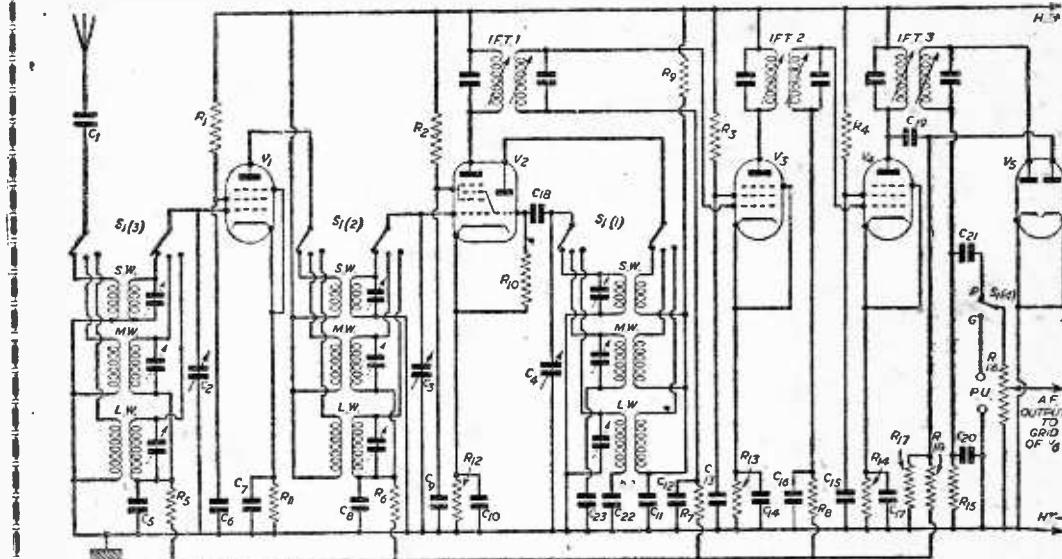


Fig. 1.—Theoretical circuit of the receiver.

LIST OF COMPONENTS

Radio Section

- R1, R2, R3 and R4 (screen resistors), 47,000 ohm $\frac{1}{2}$ watt.
- R5, R6, R7 and R8 (A.V.C. decoupling), .5 megohm $\frac{1}{2}$ watt.
- R9 (oscillator anode), 10,000 ohm $\frac{1}{2}$ watt.
- R10 (oscillator grid); 50,000 ohm $\frac{1}{2}$ watt.
- R11, R12, R13 and R14 (cathode resistors), 220 ohm $\frac{1}{2}$ watt.
- R15 (diode A.F. load), .5 megohm $\frac{1}{2}$ watt.
- R16 (volume control), .5 megohm potentiometer with switch.
- R17 and R18 (A.V.C. line), .5 megohm $\frac{1}{2}$ watt.
- C1 (aerial condenser), .0003 μ F 500 volt.

C2, C3 and C4, 3-gang .0005 μ F tuning condenser.

C5 to C17, .1 μ F each.

C18, C19 and C20, .0001 μ F each.

C21, .02 μ F.

C22 (long-wave padder), .0002 μ F (fixed).

C23 (medium-wave padder), .00045 μ F (fixed).

Aerial, H.F. and Oscillator coils for 16 to 50, 200 to 550 and 800 to 2,000 metres. (E.g., "Supacoils" types 3/1, 3/2, 3/3, 2/1, 2/2, 2/3, 1/1, 1/2 and 1/3). Nine .00005 μ F. presets.

6-pole 4-way switch. 5 octal valveholders. 3 465 kcs. I.F. transformers. Wide-vision reduction drive and dial.

ave Superhet

Receiver in Two Units

RAYER

medium-wave coils only were used, but a four-way switch was fitted so that short waves and gramophone operation would be possible later.

Subsequently, a triode was added between the double diode and output stages, and after a while the latter stage was changed to push-pull. The R.F. stage was then added, together with coils for the s.w. range. Later, the second I.F. stage was added. However, the relative simplicity of an I.F. stage may result in the constructor adding the second I.F. before the R.F. is provided, and a high standard will still be retained if the R.F. is never added.

Amplifier and rectifier sections are built on a separate chassis, thus effectively dividing the construction into two parts.

The Radio Unit

The circuit is shown in Fig. 1. Component values will be seen from the component list, but matters will be simplified if it is remembered all screen grid and cathode bypassing condensers are of $.1 \mu\text{F}$. capacity; this value is also used for A.V.C. decoupling. On the s.w. range A.V.C. is not applied to R.F. or frequency-changer valves.

An A.F. volume control is incorporated in this section, being arranged so that it is also effective when a pick-up is used. The circuit proves very satisfactory for record playing, and R.F. and frequency-changer stages are rendered inoperative to prevent possibility of radio break-through.

The chassis layout of the radio section is shown in Fig. 2. The chassis is approximately 8 in. by 12 in. When mounting the parts in the positions shown place the I.F. transformers so that the adjusting screws on the cores are easily accessible. For preference, the two left-hand transformers should have the screws to the left and the right-hand transformer should have its screws to the right.

The coils are fixed by drilling a 1 in. diameter hole for each coil, passing the narrow stem through, and pressing on the self-locking clip provided, as illustrated in Fig. 4. Place the aerial coils below the chassis (see Fig. 3), with oscillator and frequency-changer grid coils on top, as depicted in Fig. 2.

Wiring Details

The wiring plan is given in Fig. 3, but a few points should be noted. To reduce possibility of hum, keep heater wiring close against the chassis

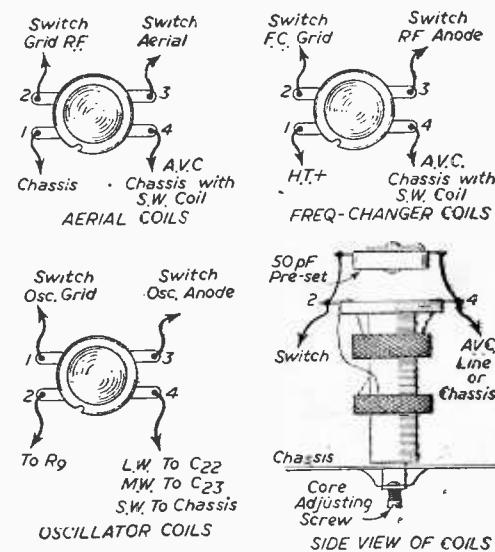


Fig. 4.—Coil connection details.

and as far as possible from grid-anode connections. All the leads shown can now be put on, leaving coil and wavechange switch connections for the moment.

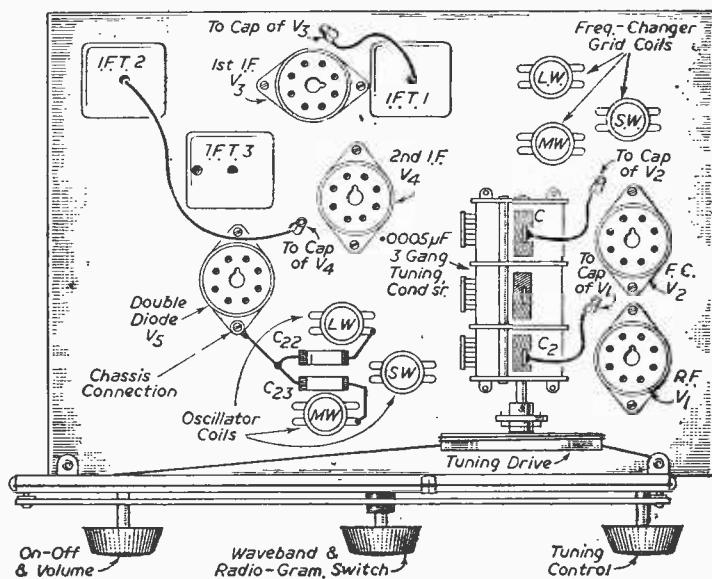


Fig. 2.—Chassis layout of the receiver section.

Some makes of I.F. transformers may have a different method of colour-coding, and this should be watched. As a rule it is quite easy to see which pairs of leads are common to the transformer windings; if not, a test for continuity will reveal this.

All connections should be insulated and joints and wire-ended resistors positioned so that no short-circuit to chassis or elsewhere is possible. Where one end of the decoupling and by-pass condensers is marked with a band or the letters "O.F.", this denotes the outside foil, and this end of the component should be taken to the chassis. (All points marked "M.C." should similarly be taken to the chassis.)

Coil Connections

Connections for the specified coils are given in detail in Fig. 4. Note that each coil has a notch, against which the relative positions of the tags can be identified. All the long- and medium-wave signal-frequency coil tags marked 4 are returned to the A.V.C. line. With the short-wave coils, these tags are connected to the chassis. Similarly, all the primary windings of the three aerial coils are returned to the chassis, and all the primary windings of the frequency-changer grid coils are taken to H.T. positive, so that wiring up is not difficult.

A .00005 μ F. preset condenser is connected in

parallel with each tuned winding, and the best method to do this is to mount the condensers immediately above each coil, as shown in Fig. 4. Connect the plate in contact with the adjusting screw of the condenser to chassis or A.V.C. line end of the coil; otherwise the presence of a metal tool used for trimming will materially affect capacity and make the final aligning of the set difficult. (These presets are not shown in Figs. 2 or 3 or in the coil diagrams in Fig. 4, for clarity.)

Wavechange Switch Wiring

All the wavechange switch connections will be shown in Fig. 5. To simplify wiring up and to avoid instability, a switch with four wafers and a long spindle is used. Referring Fig. 5 to Fig. 3, the wafers are as follows :

Wafer 1 goes at rear and is for oscillator coils. Wafer 2 is immediately before this and is for the anode circuit of the R.F. valve and grid circuit of the frequency-changer. Wafer 3 is for the aerial coils, and is near the front of the chassis. Wafer 4 is for radiogram switching and is nearest the control knob. When wiring up, note that the anode and grid circuits of the valves are not left open when the switch is in the "Gram" position, but that the control grids of the R.F. and frequency-changer valves are returned directly to the chassis.

(To be continued.)

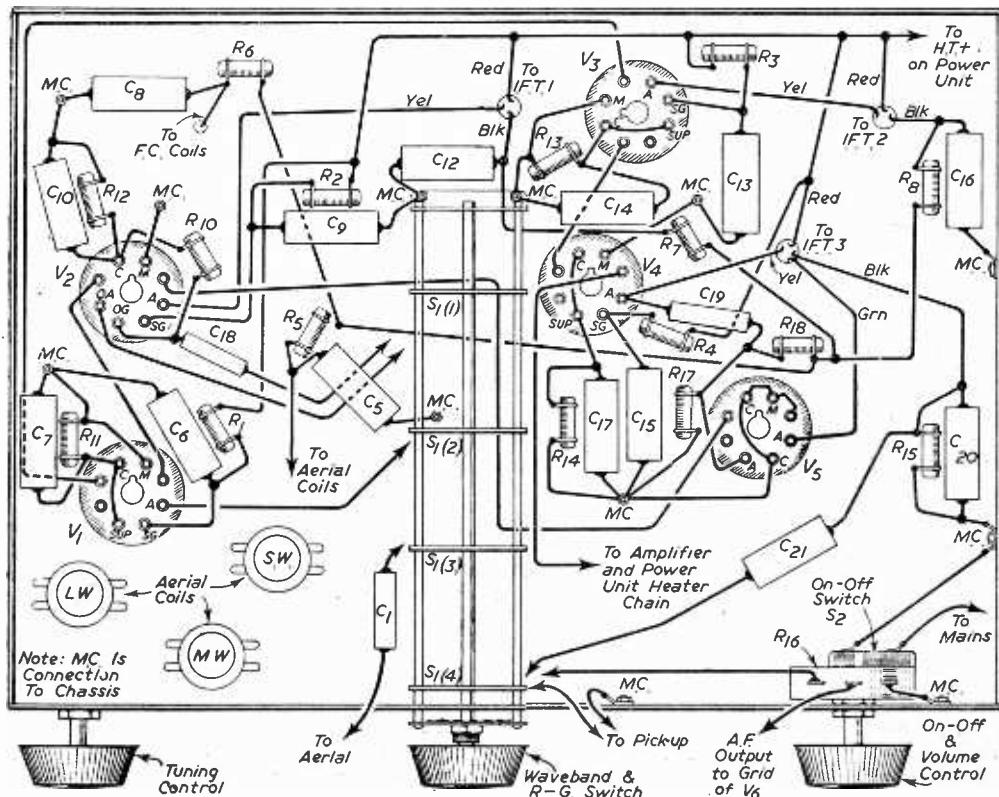


Fig. 3.—Wiring details of the receiver section. The amplifier portion will be dealt with next month.

The Copenhagen Plan

Details of the New Wavelengths

ON March 15th last, the Copenhagen wavelength plan was put into effect with mixed results. There was some confusion at first but since the introduction conditions have settled down and it would appear that the listeners will undoubtedly benefit in spite of "pirates"—stations which have so far refused to adopt the new wavelengths allocated to them.

The Need for a Wavelength Plan

It must be remembered that broadcasting is only one of many services using radio as a means of communication, all demanding clear wavelength channels which will not be subject to interference from other services. The first requirement is, therefore, to segregate the various services which is done by allocating certain blocks of wavelengths, or wave-bands, to each. This must be done on a world basis and the allocations need to be revised from time to time as the use of radio for all purposes expands. The latest revision was made at a conference of the International Telecommunication Union at Atlantic City in 1947, where the wave-bands available for broadcasting were slightly enlarged compared with those allocated at the previous Cairo Conference held in 1938. The two wave-bands allocated for broadcasting in the European area, known generally to listeners as the medium wave- and long wave-bands are as follows:

Medium Wave-band

Frequency kc/s	Wavelength metres	
525-1605	571-187	Exclusive to broadcasting.


Long Wave-band

Frequency kc/s	Wavelength metres	
150-160	2000-1875	Shared with the maritime mobile service.
160-255	1875-1176	Exclusive to broadcasting.
255-285	1176-1053	Shared with the maritime mobile service and with aeronautical radionavigation.

Broadcasting in Europe

The Atlantic City Regulations laid down that a European Regional Conference should be held to allocate individual wavelengths to broadcasting stations and this took place at Copenhagen in 1948. Thirty-three countries in the European area were represented at this conference.

The need for this detailed allocation arises because the transmissions from a broadcasting station anywhere in Europe may well be audible in neighbouring countries in the daytime and throughout the greater part of the Continent after nightfall. Something must, therefore, be done in order that the transmissions from one station shall not interfere unduly with those from another and thus prevent listeners from hearing clearly the programmes from their local stations. Ideally, every transmitter would be given a different wavelength (or more correctly a different frequency channel), but this is not possible because the number of broadcasting stations greatly exceeds the number of frequency channels available.

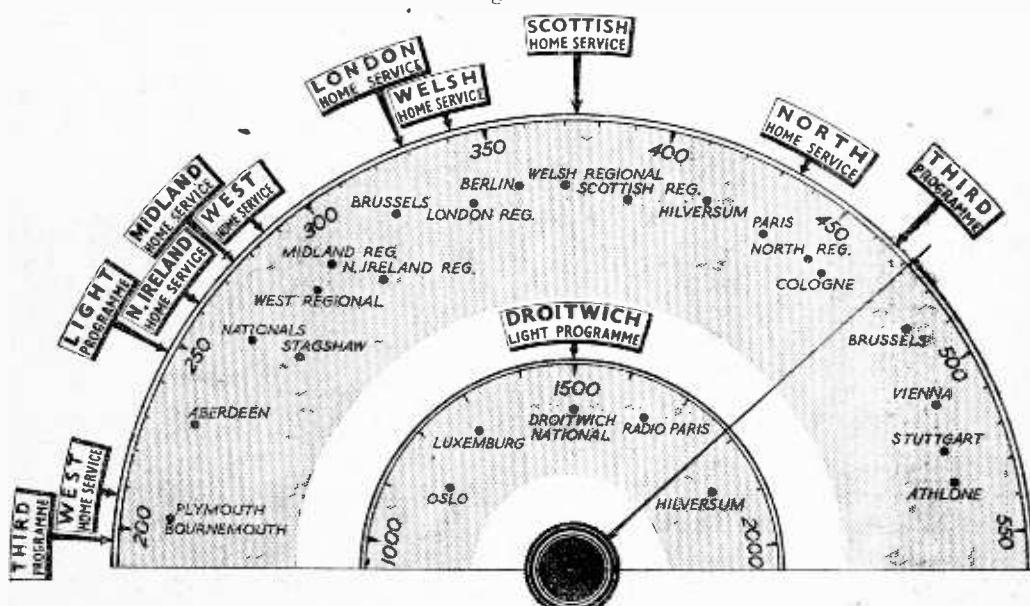

<i>Frequency kc/s</i>	<i>Approx. Wave- length metres</i>	<i>Station</i>	<i>Country</i>	<i>Power kW</i>	<i>Frequency kc/s</i>	<i>Approx. Wave- length metres</i>	<i>Station</i>	<i>Country</i>	<i>Power kW</i>
944	318	Toulouse	France	100	1205	240	Bordeaux	France	100
		Voronej	U.S.S.R.	20			Haifa	Palestine	3
953	315	Morava	Czechoslovakia	130			Lublin	Poland	10
962	312	Turku	Finland	100 (12)	1214	247	Atlantic		
		Tunis I	Tunisia	120 (13)			Reg. Azores	Portugal	2
971	309	Germany (British Zone)	Germany	70			Brookmans Park		60
		Kalinin	U.S.S.R.	20			Burghhead		20
		Smolensk		20			Lisnagarvey		10
		Izmir	Turkey	50			Londonderry		1
980	306	Algiers II	Algeria	100 (14)			Moorside Edge		58
		Göteborg	Sweden	150 (15)			Plymouth		2
989	303	Germany (American Zone)	Germany	70			Redmoss		2
		Rovaniemi	Finland	10			Redruth		2
		Beyrouth II	Lebanon	20			Stagshaw		10
998	301	Kichinev	Moldavia	100			(Newcastle)		
1007	298	Hilversum II	Holland	120			Westergren		50
		Aleppo I	Syria	20			British Troops in Germany		
1016	295	Istanbul	Turkey	130	1223	245	Kursk	U.S.S.R.	70 (18)
1025	293	Graz-Dobl	Austria	100			Stara Zagora	Bulgaria	20
		Jerusalem II	Palestine	20			Barcelona	Spain	20
1034	290	Tallinn	Estonia	100	1232	244	Fahim	Sweden	100
		Turin II	Italy	10			Budejovice	Czechoslovakia	5
		Portuguese Radio-club	Portugal	40			Cechy-Zapad		25
1043	288	Germany (U.S.S.R. Zone)	Germany	70			Moravia-Vychod		25
		Kalamata	Greece	5			Prague II	Czechoslovakia	100
		Agadir I	Morocco	20	1241	242	Vasa	Finland	50
		Marrakech I		20			Bayonne		20
		Oujda I		20			Clermont- Ferrand		20
1052	285	Tripoli	Libya	50 (16)			Corsica		10
		Jassi		10			Grenoble		20
		Focsani	Roumania	5			Le Havre		20
				10			Montbeliard		20
		Start Point	United Kingdom	150 (17)			Nice		20
1061	283	Denmark (East)	Denmark	60			Quimper		20
		Cagliari	Italy	10	1251	240	Tiraspol	Moldavia	20
		Lisbon Regional	Portugal	15			Lower Egypt:		5
1070	280	Paris II	France	100			Lower Egypt	Egypt	5
		Krasnodar	U.S.S.R.	20	1250	238	Nyiregyhaza		10
1079	278	Wroclaw	Poland	50			Zalaegerszeg		
1088	270	Korca	Albania	10	1268	237	(or Szombathely)	Hungary	20 (19)
		Shkodra		10	1277	235	Athlone II	Ireland	50
		Droitwich III	United Kingdom	150	1286	233	Stettin	Poland	100
		Norwich		20			Belgrade	Yugoslavia	135
1097	273	Bratislava	Czechoslovakia	150	1295	232	Lille	France	150
		and Synchronised network		5	1304	230	Radio Catolica	Portugal	20
1106	271	Mogilev	Belorussia	100			Kosice	Czechoslovakia	100
1115	269	Bari I	Morocco	50	1313	228	Ottringham	United Kingdom	150
		Bologna I	Italy	50	1322	227	Constantine II		20
		S. Remo		5	1331	225	Oran II	Algeria	40
		Norwegian Syn- chronised net- work	Norway	5			Danzig	Poland	50
1124	267	Brussels III	Belgium	20			Stavanger	Norway	100
		Varna	Bulgaria	5	1340	224	Onchgorod	Ukraine	100
		Viborg	U.S.S.R.	20			Genoa I		50
1133	265	Zagreb	Yugoslavia	135	1349	222	Messina		25
1142	263	Constantine I	Algeria	20			Pescara		25
		Oran I		40			Rome II		50
		Kaliningrad	U.S.S.R.	20	1358	221	Venice I		25
1151	261	Baia Mare	Roumania	5	1367	219	Alexandria	Egypt	5
		Cluj		20			Budapest		5
		Oradea		5			Magyarovár		5
		Lisnagarvey	United Kingdom	100			Miskolc		5
		Londonderry		5			Pécs		5
				100	1376	218	Crowborough	United Kingdom	150
1160	259	Strasbourg I	France	150	1385	217	Corsica		10
1169	257	Odessa	Ukraine	150			Marseilles		50
1178	255	Hörby	Sweden	100			Nantes		10
1187	253	Budapest II	Hungary	135			Toulouse		50
1196	251	Germany (French Zone)	Germany	70			Kuldiga		20
		Kerkira	Greece	15			Madona		20
		Agadir II	Morocco	20	1394	215	Tirana I	Albania	100
		Marrakech II		20			Faroe Islands		5
		Oujda II		20	1367	219	Calanissetta	Italy	25

(12) Directional aerial, protection Tunis.

(13) Directional aerial, protection Turku.

(14) Directional aerial, protection Göteborg.

(15) Directional aerial, protection Algiers.

(16) Directional aerial, protection Start Point.

(17) Directional aerial, protection Tripoli.

(18) The power shown against British troops in Germany is permitted as an exceptional addition to the normal maximum for a synchronised network.

(19) Directional aerial, protection Athlone.

Frequency kc/s	Approx. Wave- length metres	Station	Country	Power kW	Frequency kc/s	Approx. Wave- length metres	Station	Country	Power kW
1433	211	Baranovitchi	Bielorussia	20	1520	197	Coruna	Spain	20
		Bayonne		20	1529	196	Vatican City	Vatican City	100
		Lille		20			Funchal	Madera- Portugal	1
		Paris		10					
		Quimper		20					
		Montpellier		10					
		Nice		20					
		French Troops in Germany		25					
		Komotini	Greece	5					
1412	212	Banja Luka		20					
		Bijeljina		20					
		Maribor		20					
		Pristina		20					
		Rijeka		20					
		Split		60					
1421	211	Sarrebruck	Saar	20					
		Sfax	Tunisia	5					
		Tchernigov	Ukraine	5					
1430	210	Girocastro	Albania	5					
		Denmark (West)		70					
		Copenhagen	Denmark	10					
		Madrid II	Spain	50					
1439	208	Luxembourg	Luxembourg	150					
1448	207	Ancona		25					
		Florence II		3					
		Genoa II		5					
		Milan II		50					
		Naples II		5					
		Venice II		5					
		Portuguese Sync. network	Portugal	5					
		Swedish Sync. network (North)	Sweden	20					
1457	206	Craiova	Roumania	20					
		Bartley		20					
		Clevedon		60					
1466	205	Monte-Carlo	Monaco	120					
		Norwegian Sync. Network	Norway	2					
1475	203	Vienna II	Austria	30					
		Salzburg		20					
		Klagenfurt		20					
1484	202	International Common Frequency Types I and II	Albania Germany (British Zone) Austria Belgium Cyprus Vatican City Denmark Spain Finland France Gibraltar Greece United Kingdom Hungary Ireland Italy Lithuania Malta Morocco Norway Poland Portugal Roumania Rep. of S. Marino Syria Czechoslovakia Trieste Tripoli Tunisia Ukraine Yugoslavia U.S.S.R.	(20)					
1493	201	Gomel	Bielorussia	20					
		French Sync. Network	France	60					
1502	200	Zaragoza	Spain	50					
		Krakow		50					
		Warsaw II		10					
1511	199	Brussels IV	Belgium	20					
		Chania	Greece	5					
1520	197	Jihlava	Czechoslovakia	5					
		Ostrava		30					
		Pilsen		30					

(20) The Vatican City is authorised to use this wave with a power of 5 kW until receivers for 1529 kc/s are in widespread use.

(21) The methods of use of the frequency 1554 kc/s by the station of Nice, on the one hand, and by the station of the Army of Occupation of the United States of America in Germany, on the other hand, shall be the subject of a special agreement between the Governments concerned.

(Continued on page 222.)



HOME STUDY

backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an I.C.S. Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of Instruction covering radio and, if necessary, television including the following:

Complete Radio Engineering, Radio Service Engineers; Radio Service and Sales, Advanced Short-Wave Radio Elementary Electronics, Radar, Radio and Television Technology.

And the following Radio Examinations:

British Institution of Radio Engineers

P.M.G. Certificates for Wireless Operators

City and Guilds Telecommunications

Write today for our FREE "Radio" booklet, which fully describes the above ICS Courses.

International CORRESPONDENCE SCHOOLS

Dept. PW6, International Bldgs., Kingsway, London, W.C.2.

Best British Bargains!

LIGHTING SETS. 300-watt D.C. plants, 12/15 volts air-cooled 4-stroke, £16. Villiers 500-watt air-cooled 2 h.p. engine, single cylinder 4-stroke with switchboard and tank, £22/10/-, 1,260-watt Villiers 2.5 h.p. engine, 35 volt dynamo and fuel tank, £25/-, carriage extra.

A.C. LIGHTING PLANTS. 2.75 K.V.A. 3-phase 50 cycles twin cylinder-air cooled engine, exciter, mag. ignition, 130 volt Enfield generator, switchboard fitted ammeter, voltmeter, frequency meter, etc. In steel case, as new, £22/10/-, carriage extra.

MOTOR PUMPS. 230 volt A.C., for garden fountain, etc., compact unit by Stuart Turner, £5/15/- (foot valve and strainer 16/-). 12 volt for caravan or boat, lift 2ft., throw 10ft., 100 g.p.h., £5/10/-.

A.C. MOTORS, 230 volts 50 cycles S.P. $\frac{1}{2}$ h.p., 1,425 r.p.m., new, £5. Few s.h. $\frac{1}{2}$ h.p. 50 cy. S.P., 1,425 r.p.m., £3/10/-.

A.C. 3-phase motors, $\frac{1}{2}$ h.p. 440 volts, 1,400 r.p.m., £6/10/-.

TRANSFORMERS. Foster 100 watt 230 volts 50 cy. to 50 volts 2 amps., 15/-, postage 2/-, Double wound transformer, 220 volts 50 cy., input 53 volts 15 amps., 30 and 60 watts 1 amp., 6 volts 5 amps., output, £5. 900 watt Booster Transformer, 200/250 volts in 10 volt steps, £5.

RECTIFIER UNITS. Westinghouse, ex-G.P.O., 230 volts A.C. to 24 volts 6 amps in vac. metal case, £8.

DYNAMOS. D.C. 12 volt 10 amp., totally enclosed car type, 1,400 r.p.m., 40/-, 30 volt 5 amp., 1,500 r.p.m., 35/-, 24 volt 20 amp., 1,200 r.p.m., £12/10/-.

Carriage on any dynamo, 5/- extra.
Please include postage for mail orders.

ELECTRADIX RADIOS
214, Queenstown Road, London, S.W.8
Telephone : MACaulay 2159

L-R-S

FOR PROMPT & EFFICIENT SERVICE

CASH OR EASY TERMS
When you purchase on L.R.S. Convenient Terms Formalities are reduced to a minimum and you deal direct with us from beginning to end.

ARMSTRONG ALL WAVE CHASSIS
(incl. speaker and output transformer)

Model EXP/83/3, Cash price £18 17 1, or £4 12 0 with order and 12 monthly instalments of 26/-.

New Stentorian Duplex speaker with matching transformer and filter. £6 6 cash or £2 with order and 5 monthly instalments of £1.

Collaro R.C.500 Auto Record Changer £10 15 0 cash or £3 12 0 with order and eight monthly instalments of £1 0 0. Also other models.

Also available on our Easy Terms
**Goodsell-Williamson Amplifier
and Tuner Units**
Goodman's Loudspeakers
Hartley-Turner Loudspeakers
Wharfedale Loudspeakers
Leaflets available

Please let us know your Radio requirements (enclosing 2d. stamp) and we shall be pleased to quote.

Personal attention to all enquiries

**THE LONDON RADIO SUPPLY
COMPANY** Est. 1925
BALCOMBE SUSSEX



WITH only 5 connections and 1-hole fixing, the job is done in double quick time, yet efficiently and cheaply. A simple answer to all your coil and switching problems is this **Metret Coilpack**. Full circuit diagrams and instructions are supplied with each pre-aligned coilpack.

OSMOR 'Q' COILPACKS

A Portable Superhet Battery model is also available. Send stamp for FREE circuits and our new lists of coils, coilpacks and matched radio components, also latest **Bargain Bulletin**.

Trade and Export enquiries invited.

OSMOR RADIO PRODUCTS LTD. (Dept.P.4.)

Bridge View Works, Borough Hill, Croydon, Surrey

Telephone : Croydon 1220.

WE DON'T supply anything Ex-Government.
All Brand New Goods
— fully guaranteed —

All Changers recently advertised still available.

Garrard RC 65A, A.C.-A.C./D.C. & 70A, A.C. Collaro RC 500 Crystal or Hi-Fi. E.M.I. A100 M. Plessey A.C. Mixers.

VIEWMASTER. All Kits for the Birmingham and London frequencies now available.

SOLON SOLDER IRONS.—Pencil Bit, 21/-, and Straight Bit, 19/6, alt voltages. Elements—spare bits, etc., available.

TAYLOR TEST GEAR.—Entire range by this famous maker now available on HIRE PURCHASE. S.A.E. for catalogue and terms.

All AVO TEST GEAR NOW IN STOCK, including H.R. Meter. "Avo 7" Leather Cases £2.2.6.

VALVES.—Largest stock in England. Over 1,000 types.

PICK UPS and HEADS, by Decca, Connoisseur, Acos (GP20), BTH, Marconi, Shaeff, Rothermel.

SPEAKERS.—By famous makers. All boxed and guaranteed new. 3in., 14/0; 5in., 11/6 and 15/-; 8in., 17/0; 16in., 21/-.

Wharfdale Golden, 10in., £4/-; Golden, 10in., C.S., £4 10/-; Goodmans, 12in., Double Cone, £28 8/-; Single Cone, £26 15/-.

All items can be supplied C.O.D. up to 15lb. in weight. Otherwise cash with order, please.

Special attention to Overseas Orders, which are free of Purchase Tax.

MODERN ELECTRICS, LTD.,
164, Charing Cross Road, London, W.C.2
Telephone : Temple Bar 7587

HOME SERVICES

Transmitting Station	Programme	Before the introduction of the Copenhagen Plan			After the introduction of the Copenhagen Plan		
		Freq. kc/s	Approx. W/L metres	Power kW	Freq. kc/s	Approx. W/L metres	Power kW*
MOORSIDE EDGE	Northern	668	449	100	692	434	150
WESTERGLEN	Scottish	767	391	60	809	371	100
BURGHHEAD	"	767	391	60	809	371	100
REDMOSS	"	767	391	2.5	809	371	20
WASHFORD	Welsh	804	373	60	881	341	150
PENMON	"	804	373	10	881	341	20
WREXHAM	"	804	373	1	881	341	5
BROOKMANS PARK	London	877	342	100	908	330	150
START POINT	West	977	307	100	1052	285	150
DROITWICH	Midland	1013	296	60	1088	276	150
NORWICH	"	1013	296	1	1088	276	20
LISNAGARVEY	N. Ireland	1050	285	100	1151	261	100
LONDONDERRY	"	1050	285	1	1151	261	5
STAGSHAW	"	1050	285	100	1151	261	100
CLEVEDON	West	1384	217	20	1457	206	60
BARTLEY	"	1384	217	10	1457	206	60

LIGHT PROGRAMME

Transmitting Station	Before the introduction of the Copenhagen Plan			After the introduction of the Copenhagen Plan		
	Freq. kc/s	Approx. W/L metres	Power kW	Freq. kc/s	Approx. W/L metres	Power kW*
DROITWICH	200	1500	200	200	1500	400
BROOKMANS PARK	1149	261	60	1214	247	60
BURGHHEAD	1149	261	20	1214	247	20
LISNAGARVEY	1149	261	10	1214	247	10
LONDONDERRY	1149	261	1	1214	247	1
MOORSIDE EDGE	1149	261	60	1214	247	58
PLYMOUTH	1149	261	1	1214	247	2
REDMOSS	1149	261	2	1214	247	2
REDRUTH	1149	261	2	1214	247	2
STAGSHAW	1149	261	10	—	—	—
NEWCASTLE	—	—	—	1214	247	10
WESTERGLEN	1149	261	60	1214	247	50

THIRD PROGRAMME

Transmitting Station	Before the introduction of the Copenhagen Plan			After the introduction of the Copenhagen Plan		
	Freq. kc/s	Approx. W/L metres	Power kW	Freq. kc/s	Approx. W/L metres	Power kW*
DROITWICH	583	514	—	647	464	120
DAVENTRY	—	—	—	647	464	2
EDINBURGH	1474	203	2	647	464	2
GLASGOW	1474	203	2	647	464	2
NEWCASTLE	1474	203	1	647	464	2
REDMOSS	1474	203	2	647	464	2
BELFAST	1474	203	1	1546	194	5
BOURNEMOUTH	1474	203	1	1546	194	2
BRIGHTON	1474	203	1	1546	194	5
BRISTOL	1474	203	1	1546	194	—
CARDIFF	1474	203	1	1546	194	2
DUNDEE	1474	203	1	1546	194	2
EXETER	1474	203	1	1546	194	5
FAREHAM	1474	203	1	1546	194	2
HULL	1474	203	1	1546	194	5
LEEDS	1474	203	1	1546	194	5
LIVERPOOL	1474	203	1	1546	194	5
LONDON (BROOKMANS PK.)	1474	203	20	—	—	—
MANCHESTER	1474	203	1	1546	194	2
MIDDLESBROUGH (STOCKTON)	1474	203	1	1546	194	2
PLYMOUTH	1474	203	1	1546	194	5
PRESTON	1474	203	1	1546	194	2
REDRUTH	1474	203	2	1546	194	2
SHEFFIELD	1474	203	1	1546	194	2

* Maximum permitted in the Copenhagen Plan.

Fixed Resistors

Some Important Facts Regarding a Simple Component

By ERIC LOWDON

THIS resistor is, undoubtedly, the simplest and most widely used component in radio. It also gives the least trouble—when properly used. In fact, one might think that it is hardly worth while devoting an article exclusively to resistors.

Nevertheless, there are some interesting points about resistors that are not generally appreciated by the inexperienced. Sometimes even the older experimenters run into difficulties.

For instance, consider the following conundrum. When is a one-watt resistor not a one-watt resistor? At first glance this may seem to be rather silly and pointless, but the answer is of prime importance in the design of oscilloscopes, television receivers, and, in fact, any equipment where high operating potentials are used. Under high voltage conditions a one-watt resistor may be capable of dissipating only $\frac{1}{2}$ watt with safety.

The reason for this is that if the voltage impressed across a composition resistor exceeds a certain value—irrespective of its nominal wattage rating—then the ohmic value of the resistor will be reduced considerably—sometimes by as much as 50 per cent.—thus causing a corresponding drop in operating voltage in the equipment.

The writer ran into this trouble himself when a resistor which appeared to be working well within its rating kept on going down in value. It was not till a friend drew his attention to the following information that the trouble was satisfactorily cleared up.

Voltage Limits

Resistors, in common with condensers, have voltage limits placed on them by the manufacturers which are calculated to overcome this trouble. One well-known firm gives the limits for their $\frac{1}{2}$, $\frac{1}{4}$ and 1 watt resistors as 250, 350 and 500 volts respectively. These figures will no doubt vary slightly between one maker and another, but they may be taken as representative.

What effect, then, is this going to have on our choice of resistor for a particular job?

Let us consider a 1 watt, 2 megohm resistor. As already stated, the maximum voltage which can be safely developed across it is 500. That is to say the watts dissipated at this figure will be

$$W = \frac{E^2}{R} = \frac{500^2}{2 \times 10^6} = .125 \text{ watts.}$$

Thus we have the anomaly that a 1 watt 2 megohm resistor has an actual maximum rating of .125 watts. A higher dissipation than this means, of course, that a voltage higher than the specified limit is developed across the resistor, and will lead to trouble.

To take another example, suppose in some piece of equipment we have a 2,000 volt supply feeding into a resistor chain, through which is flowing .0007 amp. If now we have included in the chain a $\frac{1}{2}$ watt 1 megohm resistor, then the calculated dissipation will be

$$W = I^2 \times R = .0007^2 \times 10^6 = 0.49 \text{ watts.}$$

At first glance it would seem that our resistor is safely rated, but—what is the voltage across the resistor?

$$E = I \times R = .0007 \times 10^6 = 700 \text{ volts.}$$

Twice the maximum voltage specified for a half-watt resistor! It is even 200 volts more than that specified for a one-watt resistor. In this case, therefore, it would be necessary to use a two-watt resistor to dissipate 0.49 watt.

A few simple calculations on the above lines will show that the trouble will occur mainly with the higher resistance values and that in normal sound-receiver design the problem will not arise because the voltages involved are comparatively low.

Resistance Tolerances

Resistance tolerances, as we know, vary from 20 per cent. for general purpose resistors down to 1 per cent. for accurate special purpose resistors. In circuit diagrams the tolerance may be taken as 20 per cent. unless otherwise stated. That is to say, a resistor with a nominal value of 1,000 ohms will in actual fact have a value somewhere between 800 and 1,200 ohms.

Yet how often does one see a beginner who is assembling an experimental hook-up search despairingly through his junk box for a 1,000 ohm resistor when he has a selection of 680 ohm and 1,500 resistors, one of which may be 20 per cent. high or low to give a value as near the 1,000 ohm mark as a brand new nominal 1,000 ohm resistor.

If accuracy is important, there is no reason why the old dodge of scraping a carbon resistor should not be resorted to.

The idea is to select a resistor that is lower in value than that required and file it gradually, measuring the resistance after each stroke with the file until the desired value is obtained. But it is essential that the measuring instrument be at least as accurate as the accuracy desired in the resistor. To attempt to get 5 per cent. accuracy with an instrument that can be relied on to only 20 per cent. would, of course, be the height of folly.

Don't forget also that if very much is scraped off the resistor, then the wattage will be correspondingly reduced.

WORKSHOP CALCULATIONS TABLES AND FORMULÆ

Eighth Edition

by F. J. CAMM

A handbook dealing with methods of calculation, solutions to workshop problems, and the rules and formulæ necessary in various workshop processes. It contains all the information a mechanic normally requires.

From all booksellers, 6/- net,
by post 6/6 from the publisher.

GEORGE NEWNES, LTD. (Book Dept.),
Tower House, Southampton Street, W.C.2.

Simple Valve Tester

An Adaptable Unit for Testing Special Valves

By D. CAVE

DURING the course of building a television receiver made from ex-Government radar equipment, the writer acquired a large number of VR91 (EF50) and VR65 (SP61) valves, and it became imperative recently to test these valves, so the following simple tester unit was constructed. It was designed to test only the two types of valves indicated above; but if the principle of operation is understood it will be easy to adapt the unit for other types.

The most important factor of a valve is its mutual conductance (often called the "goodness" of a valve); and this is the extent to which the anode current changes for a change of one volt at the grid. Thus the makers quote the mutual conductance (gm.) of an EF50 as $6\frac{1}{2}$ mA. per volt and for an SP61 as $8\frac{1}{2}$ mA. per volt. This means that the anode current of the EF50 will change by $6\frac{1}{2}$ mA., whilst that of the SP61 will change by $8\frac{1}{2}$ mA., if the grid potential of either is changed by one volt over the working range.

The stage gain of a pentode with an anode load much less than the Ra of the valve is given by the product of the mutual conductance and the value of the anode load. Thus, if we use an EF50 with an anode load of 50,000 ohms the gain will be 325.

As a valve ages the mutual conductance falls; consequently the stage gain falls as well.

The Circuit

In order to test the mutual conductance it is simplest to measure the anode current at two bias voltages one volt different from one another. It is important to arrange that the one volt change covers the normal working bias of the valve. In the case of the EF50 and SP61 valves the working bias is about -2 volts. Therefore, the anode currents should be measured at $-1\frac{1}{2}$ volts and $-2\frac{1}{2}$ volts grid bias. The resulting difference in anode current will be the mutual conductance of the valve. The circuit of the tester is as in Fig. 1. The power supplies are obtained from a convenient receiver with an H.T. supply of about 250 volts, and a heater supply of 6.3 volts (one side earthed to chassis and negative H.T.).

The battery B is a twin cell dry battery with a switch S incorporated in its circuit so that battery life may be conserved when the unit is not in use. The resistances R1, R2 and R3 are chosen to give the required -1.5 volts and -2.5 volts grid bias. R3 should be 150,000 ohms, R2 100,000 ohms, and R1 depends on the exact voltage of the battery, which may be checked when purchasing. If it is 3 volts, then R1=50,000 ohms, if 3.1 volts, it is 60,000 ohms, and if 3.2 volts, then R1=70,000 ohms. All the resistances should be as close as possible to their values.

The switch T is a telephone press-button type and is chosen for its quick changeover action.


It is not wise to use a slow action switch because the grid will have no bias between the change resulting in a heavy anode current momentarily. The switch T should be so wired that in its normal position the grid is connected to X. On pressing the button, connection is made with Y and the rise of anode current is noted. The milliammeter should have a full scale deflection of 20 or 25 mA.

The tester was constructed from an A.M. control unit type 404. The cover was removed and a piece of $\frac{1}{2}$ in. paxolin sheet $4\frac{1}{2}$ in. by 10 in. was cut to fit the box. Holes were cut in the paxolin to take the meter, two valve holders (EF50 and SP61), the switch S and the press switch T (the last two were removed from the cover of the control unit). Three holes were drilled in the sides of the box to bring out the flex power supply leads which were terminated in crocodile clips. The two valveholders were wired in parallel, the grid connection for the SP61 being brought out to a clip lead through a hole drilled near the valveholder.

Other Valves

If it is desired to test valves other than those quoted, then the reader must fit the required valve-holders, choose a battery B sufficient to supply the working bias of the valves, and calculate the new values of R1, R2 and R3. To calculate these resistances allow 100,000 ohms per volt. Thus if a valve of 6 volt working bias is to be tested use a 9 volt grid bias battery and make R3 550,000 ohms (-5.5 volts), R2 100,000 ohms (1 volt) and R1 250,000 ohms (2.5 volts). On operating the switch T the bias would change from -5.5 volts to -6.5 volts. From the makers' figures check the anode current of the valve at the working bias.

It must be remembered that the battery B has not an indefinite life, so that if the unit is not used for a long period the voltage should be checked. This might be done conveniently by using the meter in the unit with the addition of a multiplier resistance R4 and a double pole two-way switch as in Fig. 2. The value of the resistance R4 would depend on the full scale deflection of the meter and the voltage range desired. Thus for a meter of 20 mA. full scale deflection, R4 might be 1,000 ohms, when the full scale deflection would become 20 volts. For a 25 mA. meter, R4 could be 500 ohms and the full scale deflection would be 12.5 volts. Smaller values than 500 ohms for R4 should be avoided.

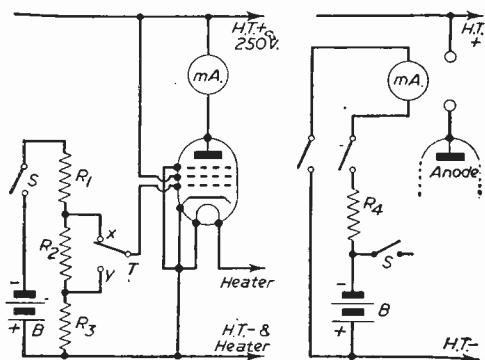

Figs. 1 and 2.—The circuit diagram and method of arranging battery check.


MIDLAND INSTRUMENT CO.**FOR GOVT. SURPLUS STOCK ETC.**

INDICATOR UNITS TYPE 162, contains two C.R. tubes, 6in. VCR-517 (suitable for television) and 2½in. VCR-138A; also 9 valves, VR-65 (3), VR-78 (2), VR-64 (2), SV-54 and VR-504. Also special CV-67 valve. 24 v. motor fitted centrifugal fan blower, panel mtc. 0-1 mA meter and other front panel controls, also stacks of other components, in metal case, size 18in. x 11in. x 8in., supplied unused, in wood crates, 70/- carriage 7/6. **INDICATOR UNITS TYPE 198**, consists of a VCR-138 3½in. C.R. tube, 8 valves, VR-65 (4), VR-92 (3) and VR-54, with a mass of other components, in metal cases, size 16in. x 12in. x 5½in., new unused, in manufacturer's sealed cartons, 40/- carriage 5/-. **AN/APA-1 INDICATOR UNITS**, contains a 3BP1 3in. C.R. tube, amplifier with 11 valves, 6SN7/GT (7) 6CG6G, 6X5, 2X2, 6H6, also control unit and other spares, operating instruction handbook, will operate from 230 v. A.C. mains or a 150-watt lamp in series, brand new, in manufacturer's sealed cartons, bargain 80/- carriage 7/6. **U.S.A. UNITS**, contains 10 valves, SH7 (6), 6H6 (2), 7193 (2) also 2 relays, chokes, coils, over 80 resistors and condensers, chassis mounted with cover, size 12½in. x 8in. x 6in., bargain, 12/6, post 1/4, ditto except has 12 valves, 1 extra 6H6 and 7193, also 1 extra relay, 15/- post 1/4. **MASER OSCILLATORS TYPE MI-19467-A**, oscillator tuning frequency 1 to 5 mc/s, multiplier tuning frequency 2 to 10 mc/s, fitted 0/10mA grid current meter, complete with two 807 valves, 1 operating, 1 spare, installation accessories, fully descriptive booklet giving all data with circuits, graphs, etc., brand new in sealed cartons, 50/- carriage 7/6.

Have you received a copy of our new lists? Contains hundreds of interesting Radio, Electronic and Mechanical items. Send S.A.E. for a copy. Our C.O.D. service is cancelled for the time being.

Moorpool Circle, Birmingham, 17.

Tel.: HARborne 1308 or 2664

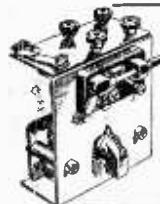

RADIO is interesting. With a 15 coil you can build this crystal set, or 1, 2, and 3 valve sets. The most comprehensive radio coil for simple circuits. With full blueprint and circuits, 5/-.
HILLFIELDS RADIO.
Dept. M, 8, Burnham Rd., Whitley, Coventry.


SUPACOILS**OFFER**

- ★ A complete range of High Q variable iron dust coated coils in wavelengths 10-30, 16-50, 30-75, 75-200, 100-550 and 800-2000 metres. Aerial, H.F. or Oscillator at the remarkable price of 1/- each, 2/- each.
- ★ **MODEL 30** famous 3 waveband superhet Coil Packs, aligned... 27/9 inc
- ★ **MODEL 40** Coil Packs—similar, with R.F. stage, aligned... 54/6 inc.
- ★ **L.F. TRANSFORMERS**, iron-cored, high stability, aligned to 465 kc/s., 12/- pair
- ★ **MODEL 30 TUNING UNIT**, consisting of 30. Coil Pack, pair of "M.M." L.F. Transformers, matched 2-gangs and attractive Dial. Components aligned together as a unit and sealed... 54.9 inc
- ★ **MODEL 40 TUNING UNIT**, similar, with R.F. stage... 86.3 inc.
- ★ **J.B. SL8** Horizontal Spin Wheel tuning assembly and dial... 25/- each
- ★ **COMPONENTS**.—Complete range of radio, television and gram components in stock at lowest prices.
- ★ **FREE**.—A copy of the enormously successful *Home Constructor's Handbook* will be forwarded **FREE** with orders of 20/- or more, or a copy can be obtained for 1/- from...

SUPACOILS, MAIL ORDER OFFICE, 88, Greenway Avenue, London, E.17.

**LONDON CENTRAL
RADIO STORES**

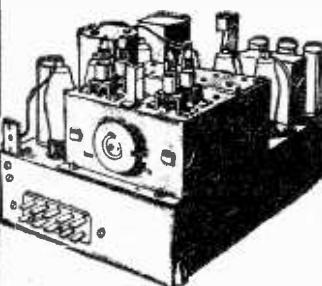6 VALVE SUPERHET RECEIVING UNIT No. 25. Easily adapted for S.W. reception for home use. Contains two EF36, two EF39, one EK32, one ECB33 valves, condensers, resistances, etc. Circuit diagram free with every set. 22/6.



BRAND NEW 2-VOLT VIBRATORS. 7-pin. Selfrectifying, 200 volts 60 mA, 7/6.

UNISELECTOR SWITCHES, 6-Bank, as new, 37/6.

BLOWER MOTORS, 12-24 and 80 volt, 12/6.

CARBON MIKE INSERTS, 2/-.

ELECTRIC MAGNETIC COUNTERS, EX-G.P.O. Every one perfect, as new. 500 ohm. coils counting to 9,000. Operates from 25-50 v. D.C. 7/6.

NEW U.S.A. HEADPHONES, 120 ohms, 4/- pair.

EX-GOV. COPPER AERIAL with Insulators, 4/3 100ft.

NEW 6-VOLT ACCUMULATORS, heavy duty 85 amps. Size 12 x 9 x 7, weight 47lbs. British made, £3 10s. 0d.

EX-R.A.F. 1155 SET, complete with Power Pack and 8 inch Moving Coil Speaker, £15 : for 200-250 volt A.C.

NEW OSRAM PROJECTOR LAMPS, 12 volt 100 watt, 9/6. Class F.

NEW CARBON TABLE MICROPHONES, 5/6 each.

12 inch V.C.R. 140 TUBES. Blue Screen Magnetic Deflection, magnetic focus. 6kv. Heater, 4-volt International Octal Standard Connections, £4 10s. 0d.

VALVES EF50, 5/6 each ; SP41, 4v. 6.3, 3/6 ; 6J5, 3/6 ; EA50 and DI, 2/6 each.

WALKIE TALKIE SETS in new condition, less ATP4 valve and Control Switch. 18/6. Wiring Diagram supplied with each set.

100yds. P.V.C. COVERED COPPER WIRE, 1/20, 5/6 coil.

TELEPHONE HAND SETS, 8/6. **NEW 1/30 h.p. MOTORS**, 220 volt A.C./D.C. double ended, 37/6.

THROAT MICROPHONES, 3/- per pair.

CAMERA MOTORS, 24 volt, 7/6.

MOVING COIL HAND MICROPHONES, 30 ohm Voice Coil, 5/6.

MIDGET BATTERY VALVES, 15S IT4 and IRS, 6/6 each ; 354, 7/6 each. All new.

23, LISLE STREET, W.C.2.
Telephone : GERrard 2969

**Everything for the
RADIO ENTHUSIAST!**

COMMAND RECEIVER for medium-wave operation. Frequency coverage 200-600 metres. Valve line-up: 3 of 12SK7, 1 of 12SR7, 1 of 12K8 and 1 of 12A6—all GT types. Will readily convert into a useful car radio or superfine domestic receiver. Unused and in excellent condition. An outstanding bargain at £41.19s. plus 2/6 carriage and packing.

COMMAND RECEIVER TYPE BC454. Frequency range 3-6 Mc/s. A 6-valve superhet, complete with valves. Line-up: 3 of 12SK7, 1 of 12SR7, 1 of 12K8 and 1 of 12A6—all GT types as for the medium-wave receiver. I.F. value 1,415 kc/s. Unused and in very good condition. Only 32/6, plus 2/6 carriage and packing.

28/ARCS VHF RECEIVER. Frequency coverage 100-156 Mc/s. Valve line-up: 4 of 717A, 2 of 12SH7, 2 of 12SL7, 1 of 12SK7 and a 12A6. **COMPLETE WITH FOUR CRYSTALS AND MOTOR TUNING.** etc. Housed in metal case size 13½ in. x 7 in. x 4½ in. Unused and in impeccable condition. 45s. plus 2/6 carriage and packing.

We hold large stocks of radio and television components and equipment, and varied items of unusual interest to every constructor. Why not visit us and inspect at your leisure? A cordial invitation extended to all.



**Best Buy at Britain's
CHARLES BRITAIN
(RADIO) LTD.**

11, Upper Saint Martin's Lane, London, W.C.2. TEM. 0545
Shop hours : 9-6 p.m. (9-1 p.m. Thursday)
OPEN ALL DAY SATURDAY

THE MODERN BOOK CO.

The Radio Amateur's Handbook—1950 Edition, by A. R. R. L., 20s. Postage 9d.

Wireless Coils, Chokes and Transformers, by F. J. Camm, 6s. Postage 6d.

Radio Servicing Equipment, by E. J. G. Lewis, 25s. Postage 9d.

Personal Portables, by E. N. Bradley, 2s. 6d. Postage 2d.

Recent Advances in Radio Receivers, by L. A. Moxon, 18s. Postage 9d.

Television Explained, by W. E. Miller, 5s. Postage 4d.

Simple Transmitting Equipment, by W. H. Allen & J. W. Mathews, 2s. Postage 2d.

Practical Wireless Circuits, by F. J. Camm, 6s. Postage 4d.

Cathode-Ray Oscillographs, by J. H. Reyner, 8s. 6d. Postage 4d.

Principles of Television Reception, by A. W. Keen, 30s. Postage 1s.

Reference Data for Radio Engineers, by W. L. McPherson, 5s. Postage 6d.

Aerials for Centimetre Wave-lengths, by D. W. Fry & F. K. Goward, 18s. Postage 6d.

"Practical Wireless" Service Manual, by F. J. Camm, 8s. 6d. Postage 5d.

Basic Mathematics for Radio Students, by F. M. Colebrook, 10s. 6d. Postage 4d.

Amateur Radio Receivers, by S. K. Lever, 3s. 6d. Postage 2d.

Radio Valve Data—Compiled by "Wireless World," 3s. 6d. Postage 3d.

We have the finest selection of British and American radio books in the Country. Complete lists on application.

10-23, PRAED STREET
(Dept. P.5) APRIL...
LONDON, W.2.
PADdington 4185.

MAINS TRANSFORMERS

(Postage extra under £2)

(As supplied by us to the ADMIRALTY, MINISTRY OF SUPPLY, B.B.C., EDUCATION AUTHORITIES etc.)

Screened primaries 200/250v. Interleaved and impregnated. Drop through type with top shroud.

(a) 250-0-250v. 60 mA., 6.3v. 3 A., 5v. 2 A. } 15.6

(b) 250-0-250v. 60 mA., 4v. 4 A., 4v. 2 A. } 15.6

Following Types have UNIVERSAL L.T. Windings. 0-4-6.3v. 4 A. C.T. 0-4-5v. 2 A.

(c) 250-0-250v. 80 mA. } 17.6

(d) 300-0-300v. 80 mA. } 17.6

(e) 350-0-350v. 80 mA. } 19.6

(f) 250-0-250v. 100 mA. } 19.6

(g) 300-0-300v. 100 mA. } 19.6

(h) 350-0-350v. 100 mA. }

Upright Types Fully Shrouded.

(i) 350-0-350v. 150 mA. 0-4-6.3v. 6 A. C.T. 0-4-5v. 3 A. ... 39/-

(j) 425-0-425v. 180 mA., 6.3v. 4 A. C.T. 6.3v. 4 A. C.T. 5v. 3 A. ... 42.6

GUARANTEED EX-GOV'T. VALVES

IC5, IN5, 524, 6AC7, 6B8, 6K7, 6J7, 6Q7, 6U7, 6V6, 6Y6, 607 at 6- ea. : IS4, JS5, IT4, 354, 6K8, 717 A at 6/6 ea. : GH6, EB34 at 2.6 ; 6L6, 9.6 : 405, 23/6 ; 813, 27.6. VCR97 in makers transit cases 32/6.

Many other types listed in catalogue.

MINE DETECTOR AMPLIFIERS

with three IT4 valves in ceramic valveholders. 22.6

T1154 TUNING PANELS with three tuning condensers 4.6

SMOOTHING CHOKES

40 mA., 5- ; 60 mA., 6.6/8; 90 mA., 7- ; 100 mA., 12/6 ; 200 mA., 21-.

VIEW MASTER TV RECEIVER.

All parts stocked.

Constructional envelopes. 5-.

E.H.T. KITS

Comprising Transformer, H.V. condensers, Resistor, Valve and circuit. Type A. 2.000v. 49/6; Type B. 2.500v.. 54/6.

COUPHONE RADIO

"The Return of Post Mail Order Service,"
53, Burrough Street, Ormskirk, Lancs.
Send 5d. Stamps for 64-page catalogue.

R.F. E.H.T.

HIGH VOLTAGE SUPPLIES FOR TELEVISION

Type SH 17/50

2.5-5 K.V. £3.15.0 retail

Type SH 8/50

5-8 K.V. £4.15.0 retail

(This is the type P.W. used in the Practical Wireless Televisor)

Coils supplied separately
Complete with full data sheets


Private and Trade enquiries welcomed

HAZLEHURST DESIGNS

LTD.

34, Pottery Lane, London,
W.II.
PARk 6955

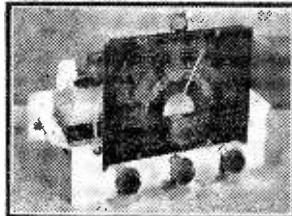YOU CAN MAKE A FINE AUTORADIOGRAM WITH THIS CHASSIS
1950 5 VALVE FOUR WAVEBAND A.C. SUPERHET. Product of a Leading Manufacturer.



Dimensions. 14in. x 8in. x 3in. Finished in cream cellulose. For A.C. operation only. 200-250 volts. 40-60 cycles. Consumption 60 watts.

FOUR WAVEBANDS 12-30 m., 30-60 m., 200-550 m., 900-2,000 m. Valve combination Mazda TH1. VP41, HL41DD, PEN45, UU6 Large illuminated glass dial, size 8in. x 5in., with coloured waveband scales and station names.

IRON-CORED COILS and I.F. Trans-formers.

HIGH SELECTIVITY AND SENSITIVITY.

PICK-UP Sockets fitted and switched in Wavechange assembly. Power output 45 watts.

Variable tone control. Extra L.S. sockets. Price includes 8in. P.M. speaker.

A MAGNIFICENT INSTRUMENT IN

EVERY RESPECT.

£10.19.6 Carriage paid.

MARCONI AUTOMATIC RECORD CHANGER with pick-up matching transformer. £10.10.8 Carriage paid.

PROMPT DELIVERY PER PASSENGER TRAIN, SATISFACTION AND SAFE DELIVERY GUARANTEED.

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House
55, County Rd., Walton, Liverpool, 4
Tel.: Aintree 1145

Established 1935

New **VALVES** 6/3
Boxed Post Free

6V6, 6K7, 6KB8, 6Q7, 6N7, 6J7, 6SN7, 6X5, 6J5, 6AG6, KTW61, H63, 6F6, L63, U50, 5Z4, SU4G, 6ACT, EL35, IS4, IT4, IR5, 3S4, 807, KT33C, 2Z5, 80, KT2.

THIS MONTH'S SPECIAL!!!

Quality 5 Valve Radiogram Chassis. 3 Waveband Superhet circuit. 6V6 Output. Large illuminated glass dial. Tone selection switching, etc. Volume and Tone controls operate on Radio and Gram. Built-in Output transformer, with provision for Extn. Speaker. Complete with 10in. High Flux P.M. Speaker.

Price £11.15.0 Carriage Paid.

New P.M. Speakers at the **RIGHT** price 5in. 10-6, 6in. 11/6, 8in. 12/6, 10in. 15.6, 12in. 35-. Last chance 10in. Elliptical 25-.

This Month's Bargain List. 1d. Stamp.

RADIO UNLIMITED
ELM ROAD, WALTHAMSTOW,
LONDON, E.17.

FIXED CRYSTAL DETECTOR THE CRYSTAL VALVE

as used in radar receivers.

Amazing Results

Size 3/8 in. x 1 in., 3/8 each. Post 2½d. Protective Tube and Fixing Brackets, 3d. extra.

CRYSTAL SET

Incorporating Crystal Valve
Adjustable Iron Cored Coil
Reception Guaranteed

Polished wood cabinet, 15/- post 9d.

Send S.A.E. for lists of copper wires, screws, nuts, paxolin tubes, ebonite, tufnol rod and panels, etc.

POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4

"YOU CAN RELY ON US"

FOR CLEAN COMPONENTS
AT COMPETITIVE PRICES

**IMMEDIATE DISPATCH
LOOK—**

**JUST A FEW OF OUR LINES
SPECIAL OFFER**

VALVES CIC, 8- ; CCH35, 8/6 ; CY31, 7.6 ; 25L6GT,

8- ; 6V6GT, 7.6 ; U50, 7.6 ; EL32, 7- ;

GZ32, 10- ; SP4 (5-pin), 8- ; 25Z6, 9- ;

EM34, 7.6 ; EL35, 9- ; Pen3520 (Pen 36c), 8.6 ; EBC33, 7.6 ; ECC32, 8- ; NONE

OF THESE ARE EX-GOVERNMENT.

BARGAIN NEW BOXED GOV. VALVES

EP36, 6- ; 5Z4G, 7.6 ; 5Z6, 7.6 ; 12J5GT, 5- ;

6H6GT, 3- . Offer for this Month only.

7.6 ; 12J5GT, 5- ; 6RGT, 5- .

BARGAIN PAIRS

Containing Paper tubular condensers.

Moulded Mica condensers. Silver Mica condensers. NO odd values. NO junk. Our

quality 10.6, post free.

STILL AVAILABLE (Midget Components)

Midget 2-pole 2-way Oak type switches 2.6

Medium Wave Coll (Iron-cored) with reaction 3.6.

Medium Long-wave T.R.F. Coils with reaction 7.6.

Super Midget Speaker Transformer to match 3S4, DL92, 184, 4.3.

Weirite 1.F.S. M400B per pair, 21½-

8 mfd. Midget Electrolytic, 450 v., 2.6.

8 mfd. plus 8 mfd., 450 v Midget Electrolytic, 4½-

1 mfd. Midget Pico-pack, 2.6.

.0005 mfd. .0003 mfd. Solid dielectric variables. 4-.

Write 'Phone, or Call for :

CATALOGUE No. 7, containing Data and Circuits. 2d. Stamp.

RADIO SERVICING CO.
444, WANDSWORTH ROAD,
CLAPHAM, LONDON, S.W.8.

Telephone : MACaulay 4155.
77, 77A Bus : 26, 28 Tram. S.R. Station, Wandsworth Road.

LYONS RADIO

3, Goldhawk Road, Dept. M.P.,
Shepherds Bush, London, W.12.

Telephone : SHEpherds Bush 1729

RECEIVER UNITS TYPE 25. The

6-valve superhet receiver of the TR 1196.

Frequency range (4.3 to 6.7 Mc/s.),

suitable for conversion to All-wave receiver.

Details in August issue of "Practical Wireless". Fitted with 2-VR56's, 2-VR53's and 1 each of VR57,

and VR55. 1 pr. of 460 Kc. I.F. trans-formers, variable condensers, etc.

PRICE, with valves, 25/-; less valves, 10.6. Post 1.6.

30ft. AERIAL MASTS. Consist of

ten sections (9 stout ashwood, 1 of metal).

Each of the 9 sections finished with metal socket and spigot so that

all fit firmly together.

A complete set of guy ropes, clamps, sandbags (filled)

etc. together with full

illustrated assembly instructions.

Absolutely nothing else needed.

In brand new condition, supplied in

maker's transit case. PRICE 45/- Carriage 4.6.

R.F. UNITS TYPE 25. We are again

able to supply these 40-50 Mc/s. con-

verters complete with valves and in

good condition. Limited stock only

so that an early order is advisable.

PRICE 32.6. Post 1.6.

ACCUMULATORS. 2 volt 20 amp-

hour. New Govt. Surplus, as new and unused.

Overall size approx. 7in. x 21in. x 31in.

PRICE 9.6. Post 1.3.

A.C. MAINS POWER UNIT TYPE

247. Input 230 v. 50 cps. Outputs :

600 v. D.C. at 200 mA., fully smoothed

and 6.3 v. A.C. at 3 A.

Really hand-somely finished with indicator light,

inspection flap and instrument handles

on front cover. Condition as brand


new and supplied in makers' transit

case. PRICE 52.6. Carriage 5.6.

NEW ILLUSTRATED CATALOGUE of

GOVT. SURPLUS BARGAINS now

ready. 3d. in stamps, please.

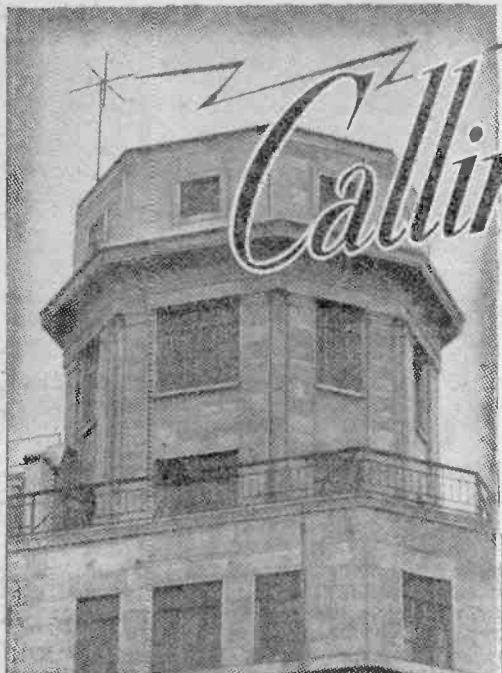

The aerial on the tower of Tower House.

ception and transmission. It is believed that Newnes & Pearson are the first publishing house to adopt this method of keeping in touch with their representatives.

Reception has proved satisfactory up to 15 miles radius, although on occasion excellent results have been

Calling Our Cars

Details of Our Publisher's Radio Link with his Travellers

A RADIO link has recently been installed at Tower House, to enable the circulation manager to keep in touch with all his Town and Home Counties representatives. Many readers may have seen the new aerial on the top of the tower of our building, and the ten cars and vans used by the circulation representatives in this area have been equipped for re-



Mr. E. D. Lush, publisher and director of G. Newnes Ltd. at the control point.



One of our representatives using the car equipment.

obtained at much greater distances. As is usual with mobile equipment, conditions vary in different localities, but so far there have been no grounds for serious complaint. Each representative has his own call sign, and the receiver is kept switched on during the day. When a call comes through he merely has to increase volume if the message is for him.

This new system will enable the publishers to give the trade a much better service in the London and Home Counties area, and in particular they are able to deal with urgent requirements with far greater rapidity than has hitherto been possible.

Programme Pointers

This Month, Our Contributor, MAURICE REEVE, Deals with
Some More Recent Programmes

STUDIO audiences have been a topic of recent discussion, so I shall be in the fashion if I add my quota of opinion to that given by others. It is a very vexing question, and would seem to concern one type of show and one only—that show in which humour, either in the dialogue spoken by the actors or in their antics and gestures, requires the response of laughter from an audience to make it seem real and alive.

Seeing that magnificent concerts, theatres, discussions, lectures, etc., are given every day without audiences, but with complete satisfaction to all concerned, tends to prove this to be the case. The symphony concert, in particular, proves the thesis right, because it is one of the very few, if not the only show we hear regularly under both conditions, i.e., in the Albert Hall with an audience (not specially assembled for the express purpose of applauding, it must be admitted) and in the studio without. Identical programmes, or types of programmes, are given in both places and, short of being present and listening to the "live" show, the consensus of opinion is that the latter are to be preferred to the former.

But, for reasons which I haven't time or space to expound here, whilst the satisfaction afforded by the most excellent performance of Shakespeare, Beethoven or Bertrand Russell is in no way impaired by the absence of rewarding applause, the comedian's jokes, gags and patter find it indispensable. Consequently, audiences have long been provided to give these shows life, substance and reality.

As we listen, however, day by day to the multitude of shows in which comedians take part, we cannot help but be struck by the way that their specially assembled audience tend more and more to defeat their object and reason for being there. Instead of, as would be the case at a "live" show; discretion being shown in the reward accorded to the good and the bad, we find the applause accorded to studio artists utterly and completely indiscriminate. Good, bad and indifferent alike, well-known or unknown, fresh or stale; all are greeted and rewarded with a volume of applause which, if recorded on a recording instrument, would not, I venture to wager, show a variation in intensity of more than five per cent. The result is an effect of complete monotony, sameness and, I fear, mediocrity.

I have never been to a studio variety show, so I cannot say how, or even if, applause is whipped up. But I do know that in studio concerts there are very often large audiences which frequently applaud vociferously, but only after the red light has changed to green.

Furthermore, studio audiences have, I regret to say, a habit that is spreading in the West End: I mean the breaking into applause over jokes, points or cracks before even the sentence has been brought to its conclusion is shocking in the last degree. So are the whistles, through the teeth—which always seem to come from the same

people, they are so precisely alike—which automatically and unthinkingly greet every "queen of song, that delightful personality," or "that bundle of humour from the North, that comedian with a smile." So is the monotony of the stereotyped announcing. So is the even more stereotyped signature tune. The whole thing wants drastic overhaul and revision. To modernise a famous motion of former days, "studio audiences are bad, are getting worse, and should be improved." I wouldn't necessarily abolish them lock, stock and barrel, but I would definitely draw them up a completely new code of conduct, or "rules governing the actions and behaviour of audiences witnessing broadcasting performances in studios."

Goethe Poems

RICHARD CAPELL'S talk on the Third, on Schubert's settings of Goethe poems, was deeply interesting. Given as part of the Goethe centenary celebrations, the speaker pointed out how, most often, the quality of the poem was the composer's chief inspiration in the writing of a song, and how the poems of Goethe, such as "Earl King," "Margaret at the Spinning Wheel," the songs of Mignon and The Harper from "Wilhelm Meister," and many others, were amongst the master's most glorious and imperishable examples. The upshot was that, not only did Schubert set more Goethe poems than anyone else but there are more masterpieces amongst them than any one else's. There must be something in it.

"The Virginians"


THE Sunday evening serial adaptation of Thackeray's "The Virginians," grievously suffers from far too much of Mr. Thackeray's narration. It clogs the works and acts as a huge brake on the sweep and action of the story, the more so as the author is made to sound so unctuous and mealy-mouthed. I have no idea whether he was actually like it in real life. The story, in any case, doesn't seem to have enough life or incident in it, in any case, to sustain it over so many weeks, delightful as it is to read.

Lord David Cecil

ANOTHER delightful talk—home service—was the fourth in "The English Novel" series, "Sir Walter Scott's Vision of Life," given by Lord David Cecil. Quoting the poet Gray as saying he would be content to pass eternity reading French romances, Lord David expressed what would be his bliss at spending it reading Scott's novels. Personally, I would like to spend mine with both those abundant and ripe harvests plus Dickens. But I suppose I should be told by the customs officials on the other side of the Styx that I had exceeded the luggage limit, especially as my "French romances" would include the last two hundred years' contributions, unknown to Gray. What would he have said!

(Continued on page 220)

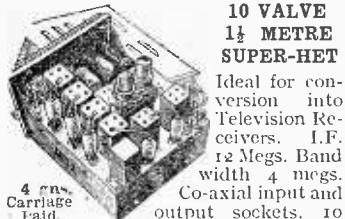Ideal for conversion into TELEVISION RECEIVERS



4 ins.
Carriage
Paid.
Coaxial input and
output sockets. 10
Mazda Mains type VR65 (SP61)
valves, 6.3 volt filaments.

10 VALVE 1½ METRE SUPER-HET

Ideal for conversion into Television Receivers. I.F. 12 Mogs. Band width 4 mugs.

Coaxial input and output sockets. 10
Mazda Mains type VR65 (SP61)
valves, 6.3 volt filaments.

ASH MASTS

30-foot Masts. 10-section best selected Ash. Stocked ends complete with guy ropes, picket posts, fixing instructions, etc. In manufacturer's sealed CASES.

£2 15/- plus 5/- carriage

Send stamped addressed envelope for Bargain Lists.

WIRELESS INSTRUMENTS (LEEDS) LTD.


54-56 The Headrow, Leeds
Telephone: 22262

AVAILABLE FROM STOCK AT GREATLY REDUCED PRICES

RK20A, 35T.....	each 25/-
60S.....	20/-
OZA, 1LNS, 1S5, IT4, 5U4 (VU7), 5Z4, 6ACT, 6CG5T, 6CR, 6F5, 6J5 6K7, 6L5, 6Q7T, GR7, 6SA7, 6SF5, 6SG7, 6SH7, 6SJ7, 6SK7, 6VG, 12A6, 12AH7, 12C8, 12D16, 12G5T, 12SK7, 25Z4, 117Z6, 2050, 9001, 9002, 9003, 9006, EBC33 (VR55).....	all at 6.6
5Y3 (U50), 6A8, 6A9G, 6C4, 6F6, 6J7, 6K8, 6N7, 6S17, 807.....	all at 7.6
3B7/1291 VHF Triode 1.4V, Fil.....	5/-
2A3 Output Valve.....	10/-
5R4C, 6BA2, 6B4, 83.....	8.6
6AB7, 6B8, 6H6, 954.....	5/-
1D1 VRP7, FA50 (VR92).....	5/-
1622 (L16), VR150 (VR151).....	12.6
929, 955.....	10/6
866A.....	17.6
Ceramic stand off ins. 1in. ribbed, 5 - doz.....	6d.
Ceramic 9in. spreaders.....	1/-
Clarostat 230-110v. .3A dropper, 445 ohm.....	2/6
Bellini & Lee 7-pin P & S.....	2/-
Voltmeter 0-300v. 2½in. scale.....	7/6
Switch 2 pole 6-way 11in. dia.....	1/-
Speaker Grills metal mesh. 6in. x 6in.....	8d.
Intervalle trans., Partridge LF/AB 600 ohm line to grid.....	15/-
Partridge L/G AB 600 ohm line to PP grid.....	10/-
" 1V25 AB 3-p. PP1. 3K, 25 Ma.	15/-
" 51H 6J7.....	7/6
" Low Mu triode—PP triodes ...	12/6
" 1 V5CT/AB Step down 1.5-1.....	15/-
" Pri 10 K, 45mils. Sec. 807, 6L6, etc.....	15/-

When ordering please include sufficient postage and packing. Phone: PAD. 6116. 5606.

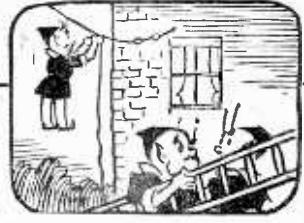TELE-RADIO (1943) LTD.,
177, Edgware Rd., London, W.2



The "FLUXITE QUINS" at Work

"We must FLUXITE our aerial," said EH.
"Let's climb without further delay."

"I say, don't look now,
There'll be a fine row,
I've taken his ladder away!"

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government work and by leading engineers and manufacturers. Of all from 1/2 ozs. in tins. 10d., 1 6d and 3/-.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 2/6, or filled 3/6.

FLUXITE

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. each.

FLUXITE Ltd., Dept. W.P., Bermondsey Street, London, S.E.1

TELEVISION

TELEVISION RECEIVERS
SCANNING AND FOCUS COILS
P.M. FOCUS UNITS
5/8 kv. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS

Technical Publications post free.

"TELEVISION CIRCUITS" a booklet
compiled for the Constructor, post free 1/6

HAYNES RADIO Ltd., Queensway, Enfield,
Middlesex.

6 VALVE, SHORT WAVE RECEIVER (TR9)

31-80 Meters. Complete with 6 Battery Operated Valves. 3 VR21's, 2 VR18's. VR22 or 118 in working order. 12/6. post 2/6. BRAND NEW VALVES. 6V6, 6K7, 6J7, 6A7, 6X5, 5Z4, 5U4, 5R4, 807, 6B8, 6/4, post 4/- for 22/6. 6B8, 6/6, 635, 4/6, post 4d. BRAND NEW 6-12 VIBRATOR UNIT. 600000 Volts at 80 Ma. 16/6. post 1/6. 80-volt BLOWER MOTOR. Enclosed centrifugal fan blower suitable for 230 v. A.C. (Intermittent Duty). 10/6. post 1/- DELCO MOTORS. A.C.-D.C. 6-27 volts (6.400 r.p.m.). 5½ x 2½ ins. spindle each end. 7/6. post 9d. 12 assorted volume controls. 6/6. post 8d. ALTIMETERS. 2/11. post 10d. SPEEDO and MILEOMETER (50 m.p.h.). 4in. dial brand new. 11/6. post 1/- REV. COUNTERS 140-0-140 f.p.m. x 10 (4in. dial). brand new. 12/6. post 1/-. NUT PLIERS, SLEEVE FIXING PLIERS. 1/2 pair. post 6d. R.A.F. COMPASS TYPE F.8 diameter 5ins. depth 3½ ins. weight 11/6. post 1/-. BROMIDE PAPER (SO. GLASS). 100 post card size. 3/6 (guaranteed). post 8d. STAN WILLETT'S. 43, SPON LANE, WEST BROMWICH, STAFFS.

THE "ADCOLA" SOLDERING INSTRUMENTS

Regd. Trade Mark



Designed to comply with the requirements of Radio Assembly, Maintenance, Instrument Makers, etc.

Working time reached 1½ mins. Consumption 25 watts. Weight, 2½ ozs. Cool Handle. Supplied in voltage ranges from 6/7 v. to 230/250 v.

1/4in. diameter copper bit Standard Model. 22/6 each.
1/4in. diameter copper bit Model. 25/- each.

Replacement Unit Bit Elements available.

British and Foreign Patents. Sole Manufacturers.

ADCOLA PRODUCTS, LTD., ALLIANCE HOUSE, CAXTON HOUSE, S.W.1.

Write or Phone: Brixton 8075.

A FREE BOOK on Morse Code Training



There are Candler Morse Code Courses for Beginners and Operators.

Send for this Free "BOOK OF FACTS"

It gives full details concerning all Courses

THE CANDLER SYSTEM CO. (5.L.O.)
121, Kingsway, London, W.C.2.

Candler System Co., Denver, Colorado, U.S.A.

RADIOGUIDE CIRCUIT MANUSCRIPTS

All Components available separately. Coil Packs, I.F. Transformers, Frame Aerials, supplied ready aligned. Chassis ready punched. MB42. First again: A combined 4 valve 2 band Portable for All-Dry batteries and Mains at the flick of a switch. 12-page manuscript. 5/-, BP42. The Popular 4-valve 2-band Battery Portable. 8 pages, manuscript. 3/-, PP42. Personal Portable 4-valve 2-band. 8in. x 5in. x 4in. 9 pages. 3/-, AC5, and AC/DC5, 3-band. 5-valve portabets. 8 pages. 5/-, AT LAST! A wealth of practical information on Magnetic Tape Recording! 13 pages. 5/3 post free. 2½d. stamp brings full details, components lists, soon! The X100 3-band Midget Coil Pack.

BURLAND RADIO ACCESSORIES

4, CARLTON TERRACE, PORTSMOUTH,
SUSSEX.

(Continued from page 218)

French Music

A MAGNIFICENT pianist in the person of Gieseck gave two marvellous programmes of French music on the Third: Debussy's first book of Preludes and Ravel's complete set of "Mirrors." Such glorious playing of this school of piano music cannot be matched to-day and has not been matched since Cortot was in his heyday. The variety of nuance, subtlety of rhythm and bringing to life of each picture the pieces portrayed, were matchless.

Solomon

THE B.B.C. Symphony Concert contained a lovely performance of a rarely heard Haydn symphony, No. 99, under Sir Adrian, and a good average one of the "Emperor," by Solomon. As with studio audiences' applause, I am sure that the variety of tone colour Mr. Solomon imparts into

cantabile passages and such pieces as concerto slow movements, cannot vary by any greater amount, if as much.

"We Beg to Differ"

SINCE I commented on "We Beg to Differ," all doubts as to whether such a type of show would "stay the course" seem to have been resolved into a very emphatic affirmative. It is now well established, though I am a little dubious as to whether its sub-title "a light-hearted discussion on topics of the moment" (I think I am right) is quite fair. It doesn't even suggest the main claim of the show to fame, the sex war. Scarcely one question is ever put to them which cannot be discussed from that angle, or which is not likely to give rise to those feelings of sex superiority, on either side, which are so delightful and entertaining. May no one ever be so foolish as to send one in.

News from the Clubs

EAST SURREY RADIO CLUB

Hon. Sec.: Leslie Knight (G5LK), Radiohme, Maderia Walk, Reigate, Surrey.

AT the A.G.M. in January it was decided to hold meetings twice a month as an experiment. Recent meetings were devoted to a sound film on "Electronics" and a 70 cm. transmitter was demonstrated. Further meetings are detailed in the Club's News Letter Service.

A Listening contest has been arranged and the winner will be presented with a silver cup given by G5LJ of Sutton Coldfield. The Club's headquarters are at the Toc H Rooms, Station Road, Redhill, Surrey.

READING RADIO SOCIETY

Hon. Sec.: Frank Hill (G2FZI), 997, Oxford Road, Tilehurst, Reading, Berks.

In February the Eko 10,000 Mc/s. Cloud and Collision Warning Radar set was described, and its uses discussed. A complete set excluding the rather cumbersome aerial system was on view to show the construction. Considerable interest was taken in the receiver frequency control system, and in particular in the construction of the very high gain 45 Mc/s. I.F. strip.

EDINBURGH AMATEUR RADIO CLUB

Hon. Sec.: David A. L. Samson (GM3EQY), 56, Elm Row, Edinburgh, 7.

After some disturbing factors which have rather upset a club routine, the Club is now back to normal and continues to meet at Unity House, 4, Hillside Crescent, Edinburgh, on Wednesdays, at 7.30 p.m. Another visit to the local headquarters of the R.N.V.(W.R.) is planned. A lecture on oscilloscopes will be given and many more lectures of interest to the hams are scheduled.

COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec.: K. G. Lines, 142, Shorncliffe Road, Coundon.

RECENT meetings of the above Society have featured a talk on "Diecasting Methods," by Mr. L. Chapman, and a demonstration of the "B.R.T. 400" by a G.E.C., Ltd., representative.

A Receiving and Transmitting contest for "Cars" members was held on February 19th. Competition is keen for the G2LGU trophy awarded to the member who can read the fastest CW.

SOUTH MANCHESTER RADIO CLUB

Hon. Sec.: M. J. Wilks (G3USW), 57, Longley Lane, Northenden, Manchester.

RECENTLY a fully-planned evening was put on, and this included a talk by the Chairman, Mr. C. M. Benny (G6DN), on the Band-switched exciter he had just completed. This was brought to the meeting and fully discussed, being of great interest, as all stages were screened to combat TVI. Following the talk, members had a "Junk Swap Sale." Originally planned as a sale, it turned into a general "Swap" towards the end.

The classes in store and in preparation for the RAE still go ahead, and the youngest member (aged about 10 years) is one

of the keenest in the CW class, copying up to about six words a minute.

New members keep coming along to the meetings, and prospective members are always welcome—no need to make enquiries beforehand. Dates of meetings in April are the 14th and 28th, and then fortnightly throughout the year at the Church Schools, Northenden, (50 or 64 bus from M/c. Piccadilly to Northenden Post Office.)

BRIGHTON AND DISTRICT RADIO CLUB

Hon. Sec.: L. Hobden, 17, Hartington Road, Brighton.

THE Club TX is being hotted up by the TX committee, and it is hoped will bring forth many QSO's on 80 metres. Recent meetings included a Quiz, a talk on AC vectors, and preparations for NFD. The Club magazine has taken on new and improved shape under the able editorship of G3DJ.D. The Hon. Sec. has promised further instalments to his interesting talk on the History of Wireless. Club nights, Tuesdays, 7.30 p.m., at Eagle Inn, Gloucester Road, Brighton.

WARRINGTON AND DISTRICT RADIO SOCIETY

Hon. Sec.: J. Speakman, Davyhulme Cottage, Dark Lane, Whitley, Nr. Warrington.

MEMBERS of the above society are now building a transmitter and if all goes well G3CKR will be on the air regularly on club nights.

Meetings are held on the first and third Monday of each month at 7.30 p.m. at the Sea Cadet H.Q., off Wilderspool Causeway, and anyone interested in membership is cordially invited.

STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: W. A. Higgins, 28, Kingsley Road, Kingswinford.

A TALK on "Matching and Feeding Systems and their Application to Antenna Systems" was given by Mr. J. F. Collett (G3BUR), of Birmingham. In addition, tuned and untuned feeders and methods of balancing, and a 48-element slacked dipole for 420 Mc/s., were described.

Another new station licensed, G3GHC, brings total to 28 licensed members out of sum total of 56 society members.

TORBAY AMATEUR RADIO SOCIETY

Hon. Sec.: K. J. Grimes, 3, Clarendon Park, Tor Vale, Torquay.

THE last meeting of the Society was opened for Questions, and many queries were asked and answered. The 1950 R.S.G.B. "Field Day" was discussed.

G2BMZ was congratulated upon obtaining the 2-metre Tropospheric Record (384 miles).

In the absence of the chairman (G2GK) the chair was taken by G3AYE.

The society's president, W. B. Sydenham, B.Sc. (G5SY), hopes to give his lecture, "Demonstration of Aerial Radiation Patterns," with the aid of the 10 cm. Klystron, at the next meeting.

Meetings are held every third Saturday in the month, at the Y.M.C.A., Castle Road, at 7.30 p.m.



The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Series Condenser Heater Circuits

SIR,—I have been using this scheme in sets for two years with 100 per cent. success. I would recommend "AEROVOX" condenser 2 μF either 600 v. or 1,200 v., obtainable ex-Government, which have porcelain insulated terminals and can be mounted inverted on a chassis so that the terminals protrude underneath. Solar condensers $\frac{1}{2} \mu\text{F}$ 600 v. are also recommended. Electrolytic condensers should be avoided at all costs.

I have built receivers similar to the one described in the March issue excepting that the valve line up was CCH 35—EF 39, EBC 33—EL 32, and having a metal rectifier for H.T. The total heater voltage is 24 volts and the condensers required are 2 μF and $\frac{1}{2} \mu\text{F}$ (total $2\frac{1}{2} \mu\text{F}$), on 240 volt mains.

The same value of condensers give satisfactory operation even if only two or three valves of the above types are used, e.g., a T.R.F. set using only an EF 39 det. and EL 32 output, or EF 39, RF-EF 39 det., and EL 32 output (metal rect. H.T. in each case), a dial lamp 6 v., .3 amp. in series does not make much difference either.

To operate two valves of the 6.3 v., .3 amp. type, 4 μF is required, whilst a single 2 μF is suitable for a 12 v., .15 amp. valve.

A good superhet can be built using a CCH 35 or EK 32 as frequency changer—EF 39 as IF amp. and EL 32 output. Detection is obtained by a Westector.

The receiver of the type I have built has three station pre-set tuning. As it was intended for local station reception only, A.V.C. was considered unnecessary, although it could easily be added if desired. The set has been designed using the minimum number of components and kept as simple as possible whilst obtaining good results.

The condenser in series with the valve heaters consists of one 2 μF and one 0.5 μF in parallel, making $2\frac{1}{2} \mu\text{F}$ in all.

A metal rectifier of the S.T.C. type is used for providing H.T. It should have a rating of 240 v. at 40 mA. Resistance capacity smoothing is quite sufficient.

The coils used are Wearite "P" coils, type PA2 and PO2. Small condensers of, say, 50 or 100 pF may be wired in parallel with the trimmers to modify the wavelength tuned.—P. E. HARVEY (Peterborough).

Pentagrid v. Triode Hexode

SIR,—With reference to J. Locke's letter on "Pentagrid v. Triode Hexode," may I submit that there is nothing extraordinary in the fact that one can change over from pentagrid to triode hexode and vice-versa.

Although when building a receiver, one would naturally use the correct circuit for the type of frequency changer valve one intended to employ—that is, tuned anode for T.H. valves and tuned grid for heptode, etc. The oscillator section of the valve is a triode to all intents and purposes, whether multigrid or T.H., and the pins are mostly identical, too.

As regards the difference in performance on the medium frequencies and high frequencies I suggest this is nothing more than inter-electrode capacity and the necessity for re-trimming when replacing a valve, even when replacing with one of the same type and make.

I recently replaced an I.F. pentode with a multi-grid F.C. valve by mistake. It worked perfectly and is still there. I suggest reader Locke examines a list of valve bases and notes in particular the American octal list, pins 4, 5 and 6, for all F.C. valves carry SG, OG, OA, and valves of the octal base type, which do not use pin 3 for anode, are either "tunerays" or double diodes.—T. BARKER (Norwich).

VCR97

SIR,—I have been a close follower of the VCR97 correspondence over the past months and perhaps my experiences and experiments based on this correspondence may be of interest and use to new entrants to the T.V. field.

E.H.T. (Final anode volts on load).—1,000 volts gives reasonable picture, using single valve T.B.s. Slight trapezium distortion and contrast rather shallow; 2,200 volts needs 2 valve T.B.s, but focus, brilliance and contrast are good enough for viewing in lighted room with screen shielded. Trapezium distortion nil.

Modulation.—2,200 volts requires approximately 40 volts signal for full modulation. This is obtained in writer's locality.

Time-Bases.—Miller integrators (paraphase amplifiers). Line linearity good, perfected by 600 pF from amplifier grid to earth. Frame linearity not perfect, but difficult to trace fault on picture, (480 volts H.T. supply).

Video.—Positive going picture requires bias

resistor lower than normal; 60 ohms approx. correct, and increases amplification of stage and power handling capacity.

Interface.—Although flyback interlaced, and half line was visible at top and bottom of picture, interlacing was not taking place. Irregular frame waveform apparently to blame. Much improved by condenser (.005 to .02) from oscillator grid to earth.

Focus.—Mr. Ward's trouble may be due to external fields as speaker and transformer fields affect beam up to about 3ft. from tube. Interlacing also appears to be faulty as lines are scarcely distinguishable on an interlaced picture 4in. high (approximately 96 lines per inch).

A shadow exists on line on my tube, but is of no consequence. A fault as yet uncurable is frequency drift on line. If locked hard on switching on drift is gradual until, after two hours, line crumples to right. No voltage change is apparent and no overheating takes place. Any information from readers who have cured this will be appreciated.—B. SHAHWELL (Oldham).

"Programme Pointers"

SIR,—In his reference to Erskine Childers in "Programme Pointers," your contributor made a bad mistake, and casts a slur on the memory of a great man. Erskine Childers was *not* shot as a traitor in the Irish Rebellion.

He was tried before the Military Court of the Pro-Treaty Party of Ireland, and he did not recognise the authority of this Court.

The charge against him was: "Being in unlawful possession of an automatic pistol."

His defence was that he was an officer of the Republican army taken in war.

The trial concluded late on the evening of November 23rd, 1922, and he was shot at dawn on the morning of November 24th, in Beggars Bush Barracks.

The Irish Rebellion took place at Easter, 1916, and Erskine Childers was shot over six-and-a-half years later.—JAMES W. GRAHAM (Perth).

(*You have your facts wrong, or, we should perhaps say, have omitted those that really matter. You will recall that the "rebellion" you mention was the Easter Rising, and was put down in a very few days. The rebellion took place in 1916-22, included the famous exploits of the Black and Tans, and culminated in the establishment of the Irish Free State, a body still acknowledging allegiance to the Crown, though with a large degree of autonomy. It was Childers's opposition to any connection with England that led him into trouble with the newly-constituted Government. Whether that Government shot him to curry favour with Westminster, we do not know. No one would dispute the actual terms of the charge proffered against Childers, as quoted by you. But we feel you have completely failed to disprove the gravamen of that charge—treason.*

Details will be found in Childers's biography in the latest edition of Messrs. Dent's "Everyman's Encyclopedia."—Ed.]

Delivery Delays

SIR,—I have read your remarks re long delivery times in the last two issues of PRACTICAL WIRELESS.

I feel that these delays are due to the wholesaler

who is handling the manufacturers' goods. This system is all right for the normal run of goods but falls down on the items less frequently called for, even if listed in the maker's catalogue.

For example, before Christmas I ordered from my dealer some close-tolerance condensers of a famous make. I still wait!

Surely the retailer should be allowed to "short-circuit" the wholesaler for special or unusual items.—J. E. ELLIS (Harrow).

(Continued from page 210)

Approx. frequency kc/s	Wav- length metres	station	Country	Power kW
1594	188	International Common frequencies Types I and II	Syria Czechoslovakia Trieste Yugoslavia	
1602	187	Germany (American Zone) Norwegian Synchronised network Portuguese Synchronised network	Germany Norway Portugal	70 2 5
(22)		Hilversum III (or synchronised network)	is authorised to use a power of 3 kW.	

NOTE: It has been agreed that, as an exception, low-power transmitters serving certain Swiss valleys may use appropriate shared frequencies, provided the protection given by the Plan to other broadcasting stations be maintained.

NOTE: The Plan states that the power of stations operating on international common frequencies must not exceed:

2 kW for stations working on international common frequencies Type I; such stations, or the countries which may use such stations are mentioned in the Plan; 0.25 kW for stations working on international common frequencies Type II; such stations are not mentioned in the Plan.

The General Effect of the Plan

The Plan evolved at Copenhagen is intended to improve listening conditions in Europe as a whole, and, of course, as part of this to improve listening conditions in the United Kingdom. The Plan calls for a change in the wavelength of almost every station in Europe. Such a change means that in every country in Europe it is necessary to make important adjustments to the transmitters.

The listener, too, must play his part if the full benefit of the Plan is to be realised. Listeners who wish to obtain the best reception will make sure that their receivers are properly installed, in the first place and that an efficient outdoor aerial is used. The receiver and aerial system should have periodic skilled attention to repair the inevitable falling-off in performance which takes place in the course of time. This point is particularly important when the listener lives at a considerable distance from the station to which he habitually listens, and if it is neglected, bad quality and interference from unwanted stations are likely.

The tables on page 212 show how the wavelengths of B.B.C. stations have been altered under the Plan.

Editorial and Advertisement Offices :
"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4383.
Telegrams : Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the writer. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed : The Editor, Practical Wireless, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and in our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

No. 1 "SYMPHONY" AMPLIFIER. Sensational new domestic amplifier by R.S.B. The most flexible on the market today. The chassis has bass, lift, treble, tilt, middle lift, treble cut, negative feed back. For A.C. 100-250 v., 5 w. output impedance to suit your speaker (please state). Input for magnetic crystal and hi-fi pickups, full provision for tuner. Price (fully guaranteed and tested). 28.19s. 6d. Immediate delivery.

No. 2 "SYMPHONY" AMPLIFIER. As above but 12/15 w. push-pull output. Price. £2.10s.

No. 1 DOMESTIC AMPLIFIER. 4 w. output with special neg. feedback circuit volume and tone controls, pickup and tuner inputs, output impedance 3 ohms or to order. Price. 5s 10s. 6d. Complete kit. 10c.

No. 2 P.A. AMPLIFIER. 12 w. push-pull 6 watts output, special neg. feedback circuit, gram., mike and tuner inputs : 3.7.5 and 15 ohms output. Price 10 guineas. Complete kit 29. Available in black crackle cabinet. 22 extra.

No. 1 HIGH QUALITY TUNER. specially recommended for above amplifiers and Leak 1. Williamson and Charles Amplifiers. L & M. wave T.R.F., infinite impedance detector. Absolutely complete, built and tested 25 10s. ditto kit £4 10s.

No. 2 L.M. & S.-WAVE SUPERHET TUNER, special quality bandwidth, beautiful full-vision dial assembly (10in. x 4in. scale), £8 10s., ditto, kit £7 10s.

LATEST GRAM UNITS : COLLARO R.C.A. mixed 8-record changer, crystal pick-up. £14 10s. 8d. MARCONI A.C.100 non-mixed 10-record changer with hi-fi lightweight pick-up and transformer. £10 10s. 7d. COLLARO A.C.504, single record player with mar. pick-up. £5 3s. 2d. COLLARO A.C.47 centre-drive motor with 12in. non-magnetic turntable. £5 18s. 4d. All our lines fully guaranteed. TELEVISION CONSTRUCTORS. All parts available for the Viewmaster and Electronic Engineering circuits. 9in. and 12in. tube (London and Birmingham models).

FULL BARGAIN CATALOGUE 2d. TERMS: c.w.o. or c.o.d. any amount. Northern Radio Services, 16, Kings College Rd., Swiss Cottage, London, N.W.3. Primrose 8314.

CUT THE CRACKLE !!! Does your Radio Crackles and Buzz, or is your Television Picture spoilt whenever a Vacuum Cleaner, Electric Motor or other appliance is in use? If so, fit an EX AIR MINISTRY HEAVY DUTY MAINS SUPPRESSOR UNIT AC/DC and enjoy uninterrupted sound and vision for only 12/6 Post Paid. Cash with order.

**DEES, Dept. P.W.,
50, ROLLS PARK AVENUE,
SOUTH CHINGFORD, LONDON, E.4.**

GLOBE KING®
"The World at your fingertips!" ★ Real Long Distance ★ Radio Reception ★
SEND FOR FREE Copy of Catalogue (1s. stamp postage) to: S. O. APPROVAL
TRADE & OVERSEAS AGENTS IN VARIOUS COUNTRIES.
JOHNSONS (Radio) SPECIALISTS LTD., CHESHIRE (ENGLAND)

RADIO G200 ANNOUNCES

Metal Rectifiers.—0.6 a 12 volt bridge, ideal for battery chargers. D.C. relays, etc. 40 each. 2 for 6s. Transformer 200-250 V.A.C. input 0.7-9.12-15.18 watts out. Suitable for use with the above rectifiers. 16/9.

Half-Wave Rectifiers. 250 v. 80 ma. 3/8 : 250 v. 100 ma. 4/8.

Build Your Own H.T. Super Capacity Battery with inert cells! The cheapest way, you just have to fill up with ordinary tap water. 60 v. 12/8, plus 2/6 carriage. 120 v. 20/-, plus 5/- carriage. Sample 1.5 v. cell. 7/1d. 5 for 2/6.

12 v. VIBRATOR Unit No. 4. (Ex. No. 22 set). Rated 12 v. 235 v. 80 ma out. Ideal car radio, sound equipment, etc. Price. 18.6. 140t. 10/- Zener-spreaders, 6in. ceramic 3/8 doz. 40 for 10/-

High Resistance Headphones. 5.6 pair. 6L6 metal. 7/9. 6SN7. 6.6. VR91. EF50. 5.6.

ARTHUR HOILE

55, Union Street, Maidstone, Kent. Phone: 3155

GREAT NEWS for Gramophone Enthusiasts

THE GOLDRING 'JUNIOR' HEADMASTER brings you the World's Finest Pick-up for only £2.40 (plus Purchase Tax, 19/-).

- Response 40-15,000 cycles without resonances.
- Interchangeable heads for all recordings.
- Negligible record-wear.
- "Floating-armature" design for perfect tracking—no distortion.
- Tonaliser : 3-point bass and treble equaliser for British and American records.

GOLDRING HEADMASTER with three heads, Tonaliser and Matching Transformer, £5.5-0 (plus 25/6 P.T.).

GOLDRING 'JUNIOR' HEADMASTER with two heads (for wide-range and pre-war recordings), £2.4-0 (plus 19/- P.T.).

Extra heads - 15/- (plus 6/6 P.T.)

Full technical information from

ERWIN SCHARF
49-51a, de Beauvoir Road,
Kingsland Road,
London, N.1

RADIOLECTRON
22, Frances Street, Scunthorpe, Lincolnshire.

New Goods Only.

CONDENSERS.—Electro. 450v. w.kg., 4md.

2.6 : 8. 3/- : 16. 4/- : 8.8. 4.8 : 8.16. 5.8 :

16. 16. 6.3 : 500v. w.kg., 4md. 2.8 : 8. 3.2 :

16. 4/3 : 8.8. 4.9 : 8.16. 6.1 : 16. 16. 6.1/1 :

25 x 25. 10/- : 25 x 50. 2.3 : 50. 12. 2/- :

50 x 50. 2.6 : Tubulars. 500v. w.kg. up to

.0005. 6d. : .005. 8d. : to 1. 10d. : Mica

up to .0003. 9d. : to .002. 1/- : .003. 1/3 :

.005. 1/6 : .01. 1/9 : Sil. Mica. up to 75Pf.

.001. 500. 9d. : to 800. 11d. : to 4,500.

14. Tuning. .00005mfd. per Sect. 1G. 5/- : 2G. 9/3.

VOLUME CONTROLS.—Lg. Spds. all

values. 2.0 : with SW. 4.6 : with DP.SW.

5.3 : Midset Type. 1. 1 & 2 mer. 4.6 : with

SW. 6.6 : with DP.SW. 7.6 : Wire Wound.

1. k to 80k. 5.3 : with SP.SW. 5k. to 50k.

7.3.

RESISTORS.—Carbon, all values. 1 watt.

BRIMSTONRS.—CZ1. 3.6 : CZ2. 2/6 :

CZ3. 1.6 : CZ4. 1.6 : CZ5. 1.6 : CZ6. 1.6 :

LOUDSPEAKERS.—PM. 5in. 10/- : 8in.

11.5/- : 8in. 12.9 : 10in. 17/- : Orders under

10/- 4d. Post. over Freq. List. 2d.

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!
QUALIFY AT HOME-IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., A.M.I.E.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Matrik., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148, HOLBORN LONDON, E.C.I.

CARLTON COILWINDING CO.

"A Name to Note and Remember."

Medium-wave Coil Units for BC443, BC454, BC455, 10-12 w. Domestic State which model required. Mains Transformers for above receivers. 31.6, for BC348 30/- BC224 26/-

Inexpensive Television Mains Transformers for RI355. 31.6. For VCR97 R.C.T. 52.8. Filament Transformer. 0.4-6.8-12.6v. 2a. 12.6. Rewinding Service. Send for catalogue. 3d.

Carco Works, Church Rd., Birkenhead. Phone 3585.



RUNBAKEN MANCHESTER !

Instrument Wire, Insulation Materials, Varnish Fibre, Mica, Leatheroid, etc.

Mains Transformers. Input 230v. 50 cy. single phase, output 50 v. 11 amp. or with series alteration 100 v. at 51 amp.; weight 45 lbs. Scrap price at 95/- carriage 8/6. Many other Radio, Electrical and Mechanical Bargains. Send S.A.E. for list.

L. C. NORTHALL,

16, Holly Road, Quinton, Birmingham, 32.

Tel. WOO 3166.

WIND YOUR OWN

I. F. Transformers, Chokes, Coils on a KAYNITE wave wound coil winder.

Standard 50/- De Luxe 84/-

Send stamp for details to

RICHARD SHEARGOLD & CO.
SUNBURY - ON - THAMES

VOLTAGE DOUBLING UNIT

Dispenses with High Voltage Transformers and Rectifier. Reliable.

For 2.5 k.v. at 54.6
For 2 k.v. at 49.6

Diagram supplied with parts. Chassis extra.

Mains Transformers, Screened, Fully Interleaved and Impregnated

I.S. 63. Input 200/250	Output 200/250	Out-	15/6
at 3 amp.	60 m/A.	6.3 v.	Half
I.S. 40. Windings as above	4 v.	at 2 amp.	Shrouded
I.S. 2. Input 200/250.	Output 250/250	80 m/A.	19/6
I.S. 3. Input 200/250.	Output 350/250	6.3-4.0 v.	Fully
I.S. 2x. Windings as F.S.2	150 m/A.	at 4 amp.	19/6
I.S. 3x. Windings as F.S.3	100 m/A.	at 4.0 v.	Half
F. 6. Filament Transformer.	Input 200/250.	Output 6.3 v.	Shrouded
Input 200/250.	Output 6.3 v.	at 2 amp.	at 7.6
F. 12. Filament Transformer.	Input 200/250	12.6 v. tapped	at 6.3 v. at 3 amp.
Input 200/250.	24 v. tapped	at 12 v. at 3 amp.	at 15.6
F. 24. Filament Transformer.	Input 200/250.	24 v. tapped	at 21.6
F. 43. Mains Transformer.	Input 200/250.	Output 425/	
C.T. 5 v. at 3 amp.	425/200	200 m/A.	6.3 v. at 4 amp.
F. 30 X. Mains Transformer.	Input 200/250.	Output 300/	
Input 200/250.	Output 300/	300 m/A.	6.3 v. at 7 amp.
5 v. at 2 amp.	300/	6.3 v. at 7 amp.	at 26.6
C.W.O. (add 1/- in the £ for carriage.			
Over £2 carriage paid.			

H. ASHWORTH, 676, Gt. Horton Road, Bradford, Yorks.

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE

Post in sealed envelope, 1d. postage.


To: R. Heath Bradley, T.C.R.C.,
50, Harland Road,
Southbourne, Bournemouth.

NAME.....

ADDRESS.....


P.106

CABINETS & COMPONENTS

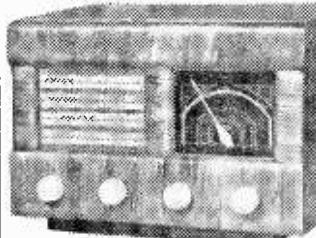

Walnut veneered cabinets approx. 12in. x 9in. x 7in. deep. 30/-.

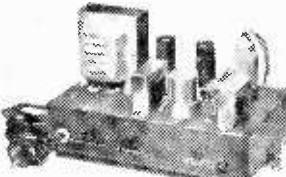Any type or quantity of cabinets made to your specification. (Send a sketch and full details.) Send 2/6 for lists and blueprints to build either a T.R.F. or Superhet Receiver in above cabinet.



4 and 4½ watt A.C. Quality Amplifiers with neg. feedback from £5 3s. Od. 5 watt Universal similar to above from £3 16s. 6d. 15 watt Universal Quality Amplifier with Push-Pull output and neg. feedback from £9 15s. Full details on request.

LEWIS RADIO CO. (Dept. K5),
322, High Road, Wood Green, London,
N.22. 'Phone: BOWES Park 5997.

Rack Panels. Crackle Finish, black or grey, other finishes to order.

19in slotted to standard Specification in 18 S.W.G. Mild Steel. Two long edges folded to provide additional strength.

11in. 3/2 ; 34in. 4/3 ; 51. 5/4 ; 7in. 6/5 ; 8in. 7.6 ; 10in. 8/7.

Chassis. 18 S.W.G. Aluminium with folded and riveted ends.

8" x 6" x 21" 4/9 : 10" x 6" x 21" 5/4
12" x 6" x 21" 5/7 : 12" x 8" x 21" 6/4
14" x 6" x 21" 7/1 : 14" x 10" x 21" 7/8

17" x 10" x 21" 8/5

Mail Order Only.

Terms - Cash with Order. Postage extra.

BURN ENGINEERING,
30, Produce Exchange Bdg.,
8, Victoria Street,
Liverpool, 2.

Post, Road, or Rail, Free of all cost.

Electrical equipment of every description from a piece of fuse wire to a generator plant, no order too small or large, a discount on all orders. No packing charges. Goods dispatched anywhere. All makes supplied. Technical information free.

GENERAL
ELECTRICAL SERVICES,
15 Hall Lane, Chingford,
London, E.4.
Telephone: SILverthorn 5251.

HIGHSTONE UTILITIES

Crystal Sets, which are fitted with a permanent crystal detector. Why not have a set in your own room—9/- post 6d. De Luxe receiver in polished oak cabinet, 16/- post 1/-, Spare Permanent Detectors, 2/- each. When ordered separately, 2/6. With clips and screws. 2/10 post 3d.

Headphones, in good order, 4/6 and 5/6. post 6d. (better quality, 7/-). New

Headphones, 10/- a pair. Balanced armature type (very sensitive), 12.6 a pair, all post 8d. New Single Earpieces, 3/-, Bal. armature type, 4/6; ex-R.A.F. earpieces, 2/-, post 4d. All headphones listed are suitable for use with our crystal sets. Hand Microphones, with switch in handle, and lead 4/-, Similar instrument moving coil, 7/-, post 6d.

Sparkling Plug Neon Testers, with vest pocket clip, 3/3, and with gauge, 3.6 post 3d.

Soldering Irons. Streamlined iron, with two interchangeable bits, one each straight and curved; 200 250w., 9/- Standard Iron with adjustable bit, 200 250v., 60 w., 9.6.

Heavy Duty Iron, 150 w., 12.6 all post 6d.

Magnets, Small ex. 2in. meters, 1/- each, post 3d. Telephone Hand Generator with handle, 7/6, post 1.6. Bell, 4/-, post 6d.

R.A.F. 2-Value (2-wire) Amplifiers, can be used to make up a deal after outfitting intercommunication system, or with crystal set, complete with valves, 20/- post 1.6. Ditto, less valves, 10/-, Wooden box to hold amplifier, 2/- extra.

Meters, 10v., 21in. Rectifier (a.c.), in wooden carrying case, 14.6 ; 15v., 21in. m.c., 9/6 ; 150v., 21in. m.c., 10/- ; 3,500v., 31in. m.c., 20/- ; 6,000v., 31in. m.c., 57.6 ; 15,000v., 21in. m.c., double reading, 8/- ; 100 m.a., 21in. m.c., 7/6 ; 3.5 amp. 21in. T.C., 5/- ; 4 amp. 21in. T.C. in case with switch, 7/6 ; Meter Movements, 21in. size with magnet and case (500 microamp), 2.6. Units containing two movements 5/-, All meters post extra. Money refunded if not completely satisfied.

HIGHSTONE UTILITIES.

58, New Wanstead, London, E.11. Letters only. New Illustrated List sent on request with 1d. stamp and s.a.e.

ANOTHER WINNER FROM WALTON'S

Once again we have been fortunate to secure another unit which represents amazing value today. These are the Transmitter portion of the Type 58 Walkie Talkie. To conform to Post Office regulations these have been partly stripped by the Ministry of Supply before release, but this only consists of removal of parts, and remaining components are in every way as new. These compact chassis are ideal for Short Wave Receivers, Battery Receivers, etc., but they are actually sold by us for the parts contained therein, which include:-

1. 200w. Air spaced variable condenser on ball bearing fitted with slow motion drive and dial.

1. 0025 ditto.

1. Midget Microphone transformer to suit carbon microphone.

1. Single pole 8-way rotary wafer switch complete with knob.

1. 2-pole 6-way ditto.

1. Double pole change-over push switch.

3. Postage Stamp trimmer condensers.

1. Westinghouse W.1 Westerotor.

1. 500 Micro-amp. Meter Rectifier.

2. Octal Valve Holders.

2. 20 ohm Volume Controls. (Ideal for speaker control.)

2. Standard Jack Sockets.

Several Tag Strips.

1. Double pole toggle switch.

About 12 1/2 watt resistors.

About 12 Mica. Silver Mica and Paper condensers.

An assortment of Rubber Bushes.

Several Hundred small screws, nuts, washers, etc.

All these parts can be easily removed without special tools and should be as new in each case, as these sets have never been in use.

OUR SPECIAL PRICE is 10/6 per unit or 2 units for 17/6.

Send S.A.E. for latest lists.

WALTON'S WIRELESS STORES
203 Staveley Road, Wolverhampton

Impressions on the Wax

Review of the Latest Gramophone Records

THE new Brahms Violin Concerto in D, Op. 77, on H.M.V. DB21000-4 (nine parts on five records, one single-sided) is a most impressive affair. Yehudi Menuhin and Wilhelm Furtwangler and the Lucerne Festival Orchestra between them contribute an intensity of feeling to this famous concerto which makes the recording very important. Many will say this is the finest reading of the work at present available. It at least deserves a hearing by those collectors who feel that their own set of the Brahms Concerto could not be improved upon.

A new addition to the "His Master's Voice" special list is a recording of Arnold Schonberg's "Verklärte Nacht," by the St. Louis Symphony Orchestra, conducted by Vladimir Golschmann, on H.M.V. DB9280-3. This most widely known of Schonberg's works is a tone poem which, unlike his later work, demands the most modest of resources: no more than a string sextet, though the volume of tone produced by six instruments is so small that the composer recommends the use of a string orchestra for concert performances. It is in this form that the work has been recorded.

"Concerto No. 3" was written by Bela Bartok in 1945 during the last months of his life. When he died he left the score unfinished by seventeen bars which were filled in by his friend and pupil, Tibor Serly. It has now been recorded by Gyorgy Sandor (piano) and the Philadelphia Orchestra, conducted by Eugene Ormandy, on Columbia LX1271-3. It is interesting to relate that Gyorgy Sandor was also a pupil of Bartok, and he, Bartok and Ormandy were all born in Hungary.

The cuckoo's note has often been sounded in music. The clavichord composers before Bach's day were specially fond of it and men like Kerl, with his "Cuckoo Capriccio" and Daquin, in "Le Coucou," have built up whole pieces on the basis of its cry. Beethoven, in the "Pastoral Symphony," gave it a place. "On Hearing the First Cuckoo in Spring," by Delius, is a masterpiece of suggestion of the bird's song and has now been recorded by the Liverpool Philharmonic Orchestra, conducted by Sir Malcolm Sargent, on Columbia DX1643. The actual cuckoo plays his part in two passages: he first sings his two notes at the interval of a minor third and then at major third, sounding again and again, each time more distant.

Vocal

The Italian film "Canzone Eterna" had its première at the Continentale Cinema in London early in January. The world-famous tenor, Beniamino Gigli, features prominently in this picture singing "Mamma" at intervals throughout the action—frequently enough, in fact, for this attractive song to be considered the theme song. "Se vuoi goder la vita" also has a place in the film, and those who have heard these pieces perhaps for the first time in the film will like to have Gigli's latest record of them on H.M.V. DA45397. The

record is a typical Gigli recording, even considered away from the picture, and no collection with a pretension to quality should be without it.

Another interesting recording has been made by Marini Del Pozo, soprano, who sings "Lucia di Lammermoor" and "Carnevale di Venezia" on H.M.V. C3967. This young, attractive soprano lives in Madrid. She visited England to make this recording, but has yet to appear in Great Britain in public. She has toured America and Scandinavia.

"The Spinning Wheel," which has now been reissued by public demand, is a traditional air sung in the Irish dialect for which it was written. It is sung by the singer who made it famous—Delia Murphy. On the reverse side is another traditional air, "Three Lovely Lasses"—H.M.V. BD1256. The guitar accompanist on both sides, Arthur Darley, has also made the arrangements.

Variety

Donald Peers, who is one of Britain's leading male exponents of popular songs, has this month recorded "Dear Hearts and Gentle People," coupled with an old favourite, "I'll String Along with You," on H.M.V. B9877.

That versatile artist, Ronnie Ronalde, presents an Italian and an Irish song in his latest recordings. "Song of the Mountains" achieved popularity in the film "The Glass Mountain" and the number features singing, yodelling and whistling. "If I Were a Blackbird" on the reverse is based on an Irish folk-song.

On her latest recording Dorothy Squires gives her own treatment to two popular favourites. "On the Sunny Side of the Street" is sung in tempo and "Do I Worry" is taken very slowly. She is accompanied in both tunes by Billy Reid and his Orchestra.

Dance Music

Eve Boswell, who made her recorded debut with the Geraldo Orchestra last summer, comes up with another winner, "Dear Hearts and Gentle People," which is enhanced by an immaculate orchestral accompaniment on Parlophone F2402. On the reverse side Geraldo gives us a beautifully-scored orchestral performance in waltz time of Castiglione's "Serenade," a Swiss song originally published under the title of "Komm Mit Mir."

Billy Thorburn's tuneful and toe-tapping combination of organ, dance band and piano this month puts its distinctive stamp on new American and British tunes. They are "Why Is It?" and "Mamma Knows Best," on Parlophone F2403. For dance fans there is "Dear Hearts and Gentle People" and "If You Could Care," in dance tempo of Joo Loss and his Orchestra on H.M.V. DB6062, and "Best of All" and "Time on My Hands," by Victor Silvester and his Ballroom Orchestra Parlophone FB3550.

THE HOLIDAYS are on the way! And what better company than a Personal Portable, especially one made by yourself to suit the area you are visiting? PERSONAL PORTABLES tells you how, with full data on both T.R.F. and superhets of the loud-speaker type. Order 2/8 post free, from BRADBOOKS, Sennen, Penzance, Cornwall. Watch next month for the details of an amazing new TV book!

BRITISH SHORT WAVE LEAGUE (founded 1935)—over 20 departments (QSL Bureau; DX Certificates; Technical; Translations, etc.) and monthly "Short Wave Review." For membership details send S.A.E. H.Q., 53, Victoria Street, London, S.W.1.

MATCHBOX RADIO SET—With the aid of our full instructions you can build a complete radio set in a matchbox, using parts easily obtainable from your radio dealer. This is made possible by the use of the Crystal-Valve Radar Detector—a wartime discovery. Tuned the B.B.C. wavelengths and works off a short, indoor aerial in many districts. Powered entirely by the incoming signal, no batteries are required. Full step-by-step instructions, working drawings, and theoretical wiring diagram. Price 2/9, post free. JOHN O'BEIRNE (W.), 137, Cotham Brow, Bristol, 6. Mail order only.

NEW R.S.G.B. Amateur Radio "Publications—Simple Transmitting Equipment, 52 p.p., 2/3. Receivers, 96 p.p., 3/9. Both fully illustrated. The Transmitting Licence (3rd Edition), 1/- (below).

R.S.G.B. Technical Publications.—R.S.G.B. Bulletin, current issue, 1/6. Five recent issues, 2/6. V.H.F. Technique, 96 p.p., 3/9. Valve Technique, 104 p.p., 3/9. Microwave Technique, 68 p.p., 2/3. Transmitter Interference, 32 p.p., 1/6. Service Valve Equivalents, 32 p.p., 1/3. Prices include postage. **RADIO SOCIETY OF GREAT BRITAIN**, 28, Little Russell Street, London, W.C.1.

RECEIVERS & COMPONENTS

COMPONENTS, ETC.—Pots, Colverne, 250 ohm, 25K, 1/6; Manganite, 1M., 1M., 1/9; Crystal Diodes, 2/9; Mike Trans., 2/6; 100 assorted Resistors, 10/-; ditto Condensers, 14/-; Stamp for lists. See also this column recent issues. Consult us for HRO Receivers, Coils, etc. 6d. post on orders under E.I. C.W.O. ELDRIDGE, 254, Grove Green Rd., E.11. (Ley. 4986.)

SNIP ! ! ! Don't miss these—FEW only R1116A Battery Double Superhets; 7 bands, 142 K/cs-20 M.c.s. 8 valves, good condition (working order not guaranteed). Bargain price while they last. £5/15/- carriage paid. ANGLIN, 106, Cleethorpe Rd., Grimsby.

S'HET COILS, 3WB 465kc, with dia. gram, 2/6 pair; Kit of Parts for Midget Coil Pack, LMS (iron cored), 465kc, 9/6; IFT's, 6/- pair; ex-RAF Output Trans., 9d.; 1/1.1/1.3d.; Sleeving, 6d. doz. yds., 16-16 x 350v Electrolytic, 2/6; 10 450v TUB. 2/9 doz. Send for cheapest list in England. **SUSSEX ELECTRONICS, LTD.** (P.), Riley Road, Brighton, 7.

2/- DOZ. 20pf. Ceramicons, 2/6 doz. Dubilier .01 mfd. mica, wire ends; 3/6 doz. Sprague .01 mfd. 1000v. Mica-mould, 1 mfd. 350v; 4/- doz. T.C.C. 1 mfd. 500v T.R.F. Coils with re-action winding, boxed, with circuit 4/9 pair, 70-400pf+170-900pf Ceramic Padders, 1/3; .50+.50pf Ceramic Trimmers, 5d. P.K. Screws, 2/- gross; 10s. Sleeving, 1 m.m., 1/- doz. yds., etc. List from T. HOWELL & CO., 29, McWilliam Rd., Brighton.

RATES: 3/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

WE DON'T SELL JUNK but can offer you Collaro AC504 single record unit with magnetic head, £5/3/2, with crystal head £5/17/6; AC47 Induction Motor (less head), but with auto-stop, £7/6/2; RC49 Autochanger, crystal head, £14/6/8; RC500 Auto-changer, crystal head, £10/15/-; Armstrong Chassis, "83," £18/17/1; "103," £24/7/6; "125," £41/1/- Speaker Units: Wharfedale Golden 10in., £3/15/-; Truvox BXII, 12in., £9/5/-; Celestion P44, 12in., £3/15/1; Roal G12, £6/10/-; Extension Speakers with volume control, 5in. unit 39/6; 6in. unit, 49/6; 8in. unit 84/-; Pifco A.C./D.C. Radiometer, 25/- Terms cash, or easy terms. Carriage paid. Lists available. Please stamp and enclose P.O. for 2/6 if you want circuit diagram. Mail order only. **JAMES H. MARTIN & CO.**, 58, Capworth Street, London, E.10.

TR9 TRANSMITTER - RECEIVERS these were formerly sold at £6 each; the remaining few to be cleared at 25/- carriage paid. **THE STAMFORD RADIO CO.**, 199, Stamford St., Ashton-under-Lyne, Lancs.

MIDDLEBROUGH.—Large stocks of Components and Radio Kits: "Osmor" Coil Packs, 30/-; Amplion Test Meters, 1.000 o.p.v. 67/6; Dials, 11/9; Denco Kits from £6/17/6, plus tax. Call in and discuss your problems. **PALMERS**, 114, Waterloo Road, E.17.

5 CORE CABLE, rubber insulated, 9/012 colour coded, rubber covered, 35/- 100 yards; 7 core ditto, but cellulose covered, 45/- 100 yards; stamp samples. Bellng Lee type 5 pin Plugs and Sockets, 80/- per 100; 7 pin ditto, 100/- per 100. High grade Panel Lights, frosted domed red glass crystal, plated bezel, M.B.C. 80/- per 100, £14 for 400. Ceramic EF50 Holders, 25/- per 100; VCR97 Holders, 18/- per dozen. Throat Mikes, 15/- per dozen. A. McMILLAN, 5, Oakfield Road, Bristol, 8.

NEW BOXED VALVES: 1R5, 1S4, 7/6; 807 (U.S.A.), 6J5GT, 6K8M, 6V6G, 5Z4M, 6N7M, 6AG7M, 6J7M, 6SN1GT, 6SL7GT, 6SJ7GT, 6B8G, 5U4G, 6K7G, 174, 1S5. VP21, QP21, 6/- each. Valves unboxed, but guaranteed. EA50, 3/-; EK32, EF39, EF36, EBC233, EL32, EF50, KTW62, VP23, TT11, 12A6M, 12SC7M, 6AC7M, 6SH7M, ML6, 8D2, 4/- each. DH63, L63, 6J5G, 6C5G, 9001, 9003, 5R4GY, HL23DD, 5/- each; X65, X66, ECH35, VU111, VU133, TH233, VP133, 6/6 each; 6L6G, 7/6; FW4/500, 8/6. Miniature 1.E. Transformers, 1/13/16 in. x 1/13/16in. x 1/13/16in., list price 21/- per pair, our price 15/- per pair. New boxed 5in. P.M. Loudspeakers, less transformer, manufactured specially for portable receivers, list price 25/-, our price 15/-. R115 Receivers with two 8D2 valves (guaranteed), LF transformer (3:1), ceramic valveholders, etc., in watertight cases, could be converted to television pre-amp, only 10/-; T154 Transistors, less valves and meters; these cover the amateur bands and can easily be put in working order, or broken up for components, which are worth many pounds, 45/-. TR1196 Transmitters with EF50, EL32, and TT11 valves (guaranteed), etc., 15/-. Volume Controls, less switch, lin. diam., 50K, 100K, 200K, 250K, only 1/6 each. Twin Plastic Flex, various colours, 3/- per doz. yards, or 18/6 for 100 yd. coil, sample sent on request. All goods post free. Send for free lists of other bargains. S.A.E. with inquiries, please. **ELECTRAD-RADIO**, 64, Gt. Victoria St., Belfast.

SIGNAL GENERATOR.—The now famous Homelab Signal Generator, moderately priced at £6/11/-, plus 5/- for postage and packing, has the refinements of an expensive instrument at a fraction of the cost. Check the specification:—1: Frequency coverage 100 kc/s to 130 Mc/s, in 6 ranges; 2: Modulation 30% at 400 c.p.s. with provision for external modulation or unmodulated carrier; 3: Coarse and fine attenuator; 4: Output impedance 10 ohms; 5: Low leakage—R.F. oscillator double screened; 6: Very stable R.F. oscillator protected by buffer stage; 7: Accuracy of calibration 1% (operates from A.C. mains 200-250 volts). 8: Twelve months' guarantee. Do not be deceived by the very low price. This is really a first class instrument, and by dealing directly with the manufacturers you save approximately £8. The high standards of design and workmanship will satisfy the most critical. Send s.a.e. for full technical specification, enclosing P.O. for 2/6 if you want circuit diagram. Owing to the very large demand for the Homelab Signal Generator there is some delay in delivery, but all orders are being dealt with in strict rotation. This instrument can be seen at the following address: Homelab Instruments, 374, High Road, London, E.11. Orders and enquiries can only be accepted by post and these should be addressed to **HOMELAB INSTRUMENTS**, 116, Grove Road, London, E.17.

MIDCO AMPLIFIERS, AA/55 watt hi-fi model, superb chassis £5/10/-, or with bass and treble tone controls. £5/17/1; AA/10 10 watt with twin input faders and tone control. £10; PA12T, superior instrument in smart case, with bass and treble tone controls, twin input faders. £14. These amplifiers are of outstanding value and can be classed with instruments at much higher prices. All amplifiers are guaranteed for 12 months. Trade terms. Catalogue gratis. **MIDLAND RADIO COIL PRODUCTS**, 19, Newcomer Road, Wellingborough, 9/6. Charging Switchboards, 12/32v, 500 and 1,260 watts,amps, cut-outs, fuses, resistances, etc., 4 take-off superb unit, in case, 75/-; Dynamos, 24v, 1,000w, 9in. x 7in., 3in. spindle. Rotary Converters, from 1-12kw, 110 and 220v D.C. to 24/35v D.C., £5-15. Motor Generators, 1-6kw, 110 and 220v D.C. to 24/35v D.C., £5-59. Mains Transformers, 1-200 KVA, from £9/10/-, all types. **POWERCO**, Wandsworth Town Station, London, S.W.18. (BAT. 5234.)

50 ASS. RESISTORS, 5/-: Bakelite Terms, 4d.; Nuts, Bolts, etc., 6d. box, 1/6 lb.; Toggle Switches, 9d.; Midget Output Trans., 2/-; List 2d. **CARTER'S**, 67, Bell Lane, Marston Green, Birmingham.

T.V. LINE O.P. VALVES, KT44, EHT Rects, 5Z4G, 72, VU120, 5/-; CV63, 2/6; CV73, 3/6; Dust Cores, 10d. dozen. Small 4p 2w Rotaries, with knob, 9d. Meter Jacks, 2 break, 6d. Morse Keys, brass, 1/6. **GREEN**, Birmingham. **S.A.E.** lists. **ANNAKIN**, 25, Ashfield Place, Otley, Yorks.

P.M. SPEAKERS (ex-Service), 8in. Tannoy in cabinets, tested; guaranteed. Only 16/6. **C.W.O.** Post paid. **W. JOHNSON**, Radio Corner, Lerwick, Shetland.

PHOTO-ELECTRIC Meter Components.—Selenium Light Cell, 6/6; Micro-amp. Meter Movement, 10/-; Perspex Instrument Case, 9/-; Assembly Instructions, 2/6. **S.A.E.** full details. **G. R. PRODUCTS**, 78, Repton Rd., Bristol, 4.

EVERYTHING for Radio Constructors, Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH**, 98, West End Road, Morecambe. Quick service.

SUPREME RADIO. 746a, Romford Road, Manor Park, London, E.12. (Tel.: ILF 1260). Midget Valves: IT4, 1S5, IR5, IS4, 7/- ea. boxed. 0.0005 mid. Mica Diaelectric Variable Condensers, 2½ in. ea. 2½ in. and 3 in. Moving Coil Speakers, 2-3 ohm, voice coil, 14/11 ea. Midget Personal Output Trans. for DL92, valves, etc. really tiny. 4/- ea. B7.G. Amphenol type Valve Holders. 9d. ea. 1 watt Resistances: 10 ohm, 22, 47, 27, 82, 120, 180, 250, 330, 390, 820 ohms. 1K, 3.9K, 11K, 470K and 10 megohm, 1/9 doz. or assorted doz., 18/16 gross only. 1 watt Resistances, 2.2K ohm, 6.8K, 16K, 18K, 33K, 100K, 150K, 220K ohms, 2½ doz. or assorted doz., 21/- gross only. 1 watt Resistances, 220 ohms, 270, 470, 1K, 3.3K, 8.2K, 18K, 33K, 56K, 68K, 1 meg and 2 megohms, 4/- doz. or assorted doz. only. Mica Cond.: 40PF, 50PF, 60PF, 65PF, 70PF, 305PF, 307, 500, 530, 570, 590, 1,800 and 4,550PF, all at 2/6 doz. or assorted doz. only. CV102 Crystal Diodes, 2/6 ea. 4 in. bore brass bushed brown Knobs, 2/- doz., 200V. 120 M/A Selenium Metal Rectifiers or 250V 75MA, 4/- ea. 1 meg. Carbon and 5 k-ohms W/W Vol. Controls, 1/- ea. 3 meg Var. Carbon Controls, 7/- ea. Noise Suppressor Units consisting of 2, 0.1 mfd. Cond. and Iron-Cored Choke, 6d. ea. 5/- doz. 100k-ohm Long Spindle Vol. Controls with S/P switch, 2½ ea. 0.25 meg Vol. Cont. less switch long spindle, 2/- ea. Terms C.W.O. No C.O.D. Send 6d. extra for postage orders under £5. 2½ d. S.A.E. all enquiries and lists.

A.C./D.C. MULTIMETERS. 17 ranges small size, movement 200 A.M.C. ranges. A.C./D.C. volts 10, 50, 100, 500, 1,000V, at 4,500 ohms per volt. D.C. current, 1, 10, 100, 500mA. Resistance 0-5,000 ohms, 500,000 ohms, 5 megohm. All self contained. Price £5/10/- complete. Send S.A.E. for illustrated leaflet. C. & W. ELECTRONICS, 17, Cross Street, Oswestry, Salop.

MAGNETIC SOUND Recording Wire, stainless steel, temporary wooden spools, approx. 14 hours running time at 21t. per sec., 14/- per spool. A. SMART, 40, Grange Rd., Hale, Owen.

GRAND NEW GOODS: Mains Transformers, fully interleaved and impregnated, primaries 200-230-250V 50 c/s. screened, half shrouded drop through types, 260-260-260V 70ma, 6.3v 3a, 5v 2a, quadrad, 12/11; 350-0-350V 100ma, 4v 4a, 3a, 13/11; 250-0-250V 80ma, 6.3v 6a, 5v 3a, for 1355 conversion, 21/11; 350-0-350V 100ma, 6.3v 5a, 2a, 19/11; 350-0-350V 150ma 6.3v 4a, 5v, 3a, 26/9; midset, 250-0-250V 60ma, 6.3v 2a, 5v 2a, 14/9; fully shrouded, upright mounting types, midset size approx. 24 x 3-3½ in. 15/6; standard 350-0-350V 100ma, 6.3v-4v 3a, 5v-4v 2a, 21/9; 350-0-350V 120ma, 6.3v 4a, 5v 3a, 28/5; 350-0-350V 150ma, 6.3v 4a, 5v 3a, 27/9; 250-0-250V 80ma, 6.3v 6a, 5v 3a, for 1355, 23/9; 425-0-425V 200ma, 6.3v-4v 4a, c.t. 6.3v-4v c.t. 5v-4v 3a, 41/9; drop through type, 350-0-350V 80ma, 6.3v 3a, 5v 2a, 14/11. Resistors, 47K, 1 meg, 1 watt, 9/- per 100. P.M. Speakers, 5in. Plessey, with trans. 1700 ohms, 12/5; 6½ in. Goodmans, 2-3 ohms, 11/9; 8in. Plessey, 2-3 ohms, 13/8; 10in. Truvox, 2-3 ohms, 16/9. Push Pull Output Trans. 8 watt tropicalised, 6½s to 3 ohms, 3/9. Smoothing Chokes, 60ma, 400 ohms, 15h, 4/9; 100ma, 300 ohms, 10h, tropicalised, 6/9. Centralab Volume Controls, .5 meg, with switch and standard length spindle, 3½ in. ea. 36/-doz. Metal Rectifiers, small, HW, 250V 80ma, 4/3. All goods guaranteed. Bargain list 3d. Special list for trade. C.W.O. or C.O.D. over £1. Postage extra. E. POWELL, 15, Queen Square, Leeds, 2. (Callers welcome 9 a.m. to 5.30 p.m.)

DUKE & CO. 219, Ilford Lane, Ilford (0295), Essex. Summer Price List now available. 100 new Resistors, all popular sizes, 1 watt to 1 watt, 10/- Phone bargains: single unit, L.R. Rest, on metal headband, collapsing, 1/9; DLR.5 balance unit type-L.R. pair 3/6; Standard L.R. type, 2/6; Moving Coil, complete with M/C mike, 8/6; Tannoy R.N. pattern with mike, 8/6. Valve Price Reductions: 6V6, 6P6, 6K8, 6K7, 6Q7, KT33C, 5/9 each. S/Het Set T.H.132, VP133, HL1330D, PEN383, at 5/9 each. Enquire for any type you may require. Condensers: Bargain parcel, 25 mfd, 25v, and 4 mfd, 200v, 3 of each for 3/- Best makes. 16 + 8, 450V, 2/6; 16 + 16, 3½, 8 + 8, 3½, 8 mfd, 2/6; E.H.T. 2K trans., 19/6 plus 2-0-2 heater, 27/6. Crystal Sets: You are still ordering these at 8/6. Extension Speakers, in cabinet, new, 14/6. Speaker Trans. Standard matching 2/6. Gram-Motors, A.C. new, complete with turntable, 39/6. P.T. 20/-. Cash with order please, plus postage. Stamps only for lists. All orders have money back guarantee.

SWITCH UNITS. Two switch units complete with knobs mounted in a metal box 8in. x 3½ in. x 1½ in.; each unit consists of a 2-wafer each 21-way, single pole switch and a tapped resistor; by removing one switch and fitting a suitable meter in the case and remaining switch could be turned into a multi-range test meter; these switches and tapped resistors could not normally be obtained at a price approaching ours; each one is brand new and unused, packed in a sealed carton. Price 2/9 each. Postage paid. S.A.E. for a copy of our Super-Detailed List. **WILFLO PRODUCTS**, 222, Gorbals Street, Glasgow, C.5.

P.M. SPEAKERS: 5in. Rola in case 17/6. Condensers, paper block type, 8mfd. 750 volts, 10/6; Co-Axial Cable, 75 ohm, 10/1d. yd.; Valves: 6V6, 7/6; 5U4G, 12/6; EF50, 10/6; F6H, 10/6; W3737 Receivers, 5-Valve Superhet, .4 to 10 M/Cs including valves, less power pack, £3; Voltmeters, 0-300 A.C. moving iron, 2½ in. flush, 17/6; 3½ in. surface type 22/6, 0-250 moving coil rectifier type, 3½ in. flush 30/- **WILCO ELECTRONICS**, 204, Lower Addiscombe Road, Croydon.

ALL-WAVE Diode (batteryless) Kits. 17/6. Gen. and List. 1d. Matchbox size Kits, 3/3; 200-550M. Kits, 3/9. **ALEXTONE**, Hillworth, Longdon, Glos.

SPECIAL RECEIVERS, test gear electronic apparatus, experimental and design work.—If you have a problem which needs expert handling, write in first instance to J. MORT, B.Sc., A.M.I.E.E., B.C.M. HIFIDEL, London, W.C.1.

CLEARANCE SALE Guaranteed Bargains

2 Volt 20 A.H. Accs. 6 11/4 each. Heavy Alnico Magnets, lift 50 lbs., 7/6 each. Contact Studs, 36/4 each. Bowl Cutters, 9/6d. each. Air Pumps, 19/6d. each. Captain's Thermometers, 9/6d. each. K24 Camera Magazines, 2/6d. each. and a large selection of equipment of all types.

S.A.E. for a copy of our Super Detailed List. Something for Everyone.

HAVE A GO WITH WILFLO.
WRITE NOW.

WILFLO PRODUCTS
222. Gorbals Street, Glasgow, C.5

SOUTH 2385.

"TELEVISION SPECIAL!"—In response to 1,000! requests, we now offer the E.S.3 "Foundation Kit"; uses VOR 97 tube (not radar conversion). Send large S.A.E. for illustrated brochure. Dept. P.W. T.H. PRODUCTS, 92, Leathwaite Road, S.W.11.

PRACTICAL WIRELESS Televisor Aladdin Former, with core, 16d.; Tag Ring, 2d.; Set of Coils, London, 16/6; Chassis, 24/-; Mains Transformer, 350-0-350 250ma. 5v 2a, 6.3v 4a, 6.3v 4a, 6.8/6; Choke, S.A.E. Ilist. R. F. SHILTON, 19, Cheltenham Road, Salisbury, Wilts.

2A DROPPERS, 1/6; 50ft. Aerials, 1/-; Plastic Cov. Connecting Wire, 25 yds. 2/6. R. E. HOPE, Benington, Herts.

REPAIRS AND REWINDS

"MOTOWIND SERVICES"—Fractional H.P. Repairs, Armatures, Fields, Coils; 7 day service. 27, Grosvenor Street, Cheltenham.

REPAIRS to loudspeakers. Cones, coils fitted. Fields altered, rewound. Output transformers, clock coils. Prices quoted. Satisfaction guaranteed. L. S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting, S.W.17. (Phone: Balham 2359.)

VACUUM CLEANERS and Gram. Motors, repairs our specialty. Armature rewinds, new bearings and commutators fitted, also transformers rewound. speakers repaired. Competitive prices. Trade enquiries invited. 2 to 5 days c.o.d. service. Send s.a.e. for price lists to: A.D.S. CO. (V.E.M. Dept.), 261-3, Lichfield Road, Aston, Birmingham, 6. Est. 1935.

EDUCATIONAL

TELEVISION.—The Gothic Television School specialises solely in training in television. Courses assume no previous television knowledge and provide guaranteed training for Brit.I.R.E. and R.T.E.B. examinations. All tutors possess university degrees and/or corporate membership of professional institutions and are appointed individually to postal course students to ensure complete and thorough training. Principals, M.B.E., B.Sc., M.Brit.I.R.E., education committee members, etc. Numerous well-known companies have adopted the School's Basic Television Course as standard television training for their staffs. Moderate fees. Details from **GOTHIC TELEVISION SCHOOL**, 13, North Ave., London, W.13.

WIRELESS. Land, Sea and Air. Students, both sexes, from 14 years, trained for good appointments in all branches of radio. Low fees. Boarders accepted. Stamp for Prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

THE INSTITUTE of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E. Service entry and progressive exams. Tuitionary fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the SECRETARY, Fairfield Road, Crouch End, N.8.

MERCHANT NAVY AND AIR RADIO. Here is an opportunity to train as Radio Officer for merchant ships and the air. The big liners are open to you, but you must first qualify for the P.M.G. Certificate. Established 30 years. We can put you through in the minimum time. Day, evening and "Radiolects" postal courses. Prospectus: Director, THE WIRELESS SCHOOL, 21, Manor Gardens, Holloway, London, N.7. ARC 3694.




RECEIVER TYPE 18. With 4. Battery operated valves, this superhet covers from 6-9 mc.s., but may be modified for other frequencies; the 465 kc/s. I.F., and TWO R.F. coils make it the ideal foundation unit for conversion purposes, but it is ready for use, when batteries are connected. Complete with circuit and connecting data. 19.6. Or, complete with phones, H.T. battery and accumulator, 31.6.

MERCURY TYPE H.T./L.T. BATTERIES—THE NEW type of dry battery, with an infinite shelf-life, these sealed units deliver 94v. H.T. and 1.3 v. L.T., sufficient for 1.4 v. valves. Of recent manufacture. OUR PRICE, 6.11.

MIDGET ACCUMULATORS, measuring 11 x 4in., the same made by Exide and Oldham, to rigid specification; 3A capacity, they are BRAND NEW and require only the addition of acid. Price 2.6 each, or a crate of 12. 20.

RADIO EXCHANGE CO. 9 CAULDWELL STREET, BEDFORD Phone: 5568

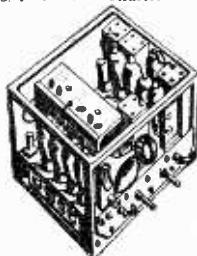RECEIVER TYPE 21. One of to-day's greatest bargains, this miniature communications receiver, complete with 9.2 v. valves, covers from 4.2-7.5 and 18-31 mcs. (465 kc/s. I.F.). Complete with circuit and connecting data, 35.-. Unused condition.



VIBRATOR PACK 21. Designed for the above receiver, the output of this 6 v. input (with 150 v. at 40 mA.) makes it suitable for most small receivers. In new condition. 19.6.

MIDGET MOTORS. Midget (11in. dia. x 21in.) motors, these will operate from 27 v., and develop 1.135 h.p.! They are supplied complete with a small removable fan and will find a variety of uses in every home or workshop. AS NEW. ONLY 9/6. (U.S. manufacturer.)

All goods sold as used unless otherwise stated.

DON'T WANDER IN CIRCLES

**GET THERE
- DIRECT!**

The quickest way to the top is by studying at home in your spare time, guided by the world's most successful correspondence college. Individual tuition by experts fits you for highly-paid key positions, prosperity and an assured future. Write TO-DAY for FREE advice on the work that interests you.

CHOOSE YOUR CAREER

Blue Prints.	Radio Service Engineering.
Book-keeping.	Mathematics.
Carpentry and Joinery.	Matriculation.
Civil Engineering.	Plastics.
All Commercial subjects.	Wireless Telegraphy and Telephony.
Shorthand (Pitman's).	Surveying.
Telecommunications (City and Guilds).	Teachers of Handicrafts.
Draughtsmanship.	Television.

If you do not see your own requirements above, write to us on any subject. Full particulars free.

To DEPT. 104, THE BENNETT COLLEGE, LTD., SHEFFIELD.

Please send me (free of charge) particulars of.....

Your private advice about.....
(Cross out line which does not apply.)

Name

Address

LASKY'S RADIO

L.F.F. RECEIVERS. Brand New and Unused. Supplied in Maker's Original Cartons. Contains 8 new valves: 4 SP41: 1 EA50; 1 VR78; 2 CV6. Also hosts of components, coils, condensers, resistances, switches, etc. A motor generator with an input of 24 volts and output of 480 volts.

LASKY'S PRICE

19/11

Carriage 3/6 extra.

AMERICAN AIR CORPS RECEIVER TYPE B6624A. 10 Valve superhet, frequency 100-156 mc/s. Valve line up: 3 9003; 1 9002; 1 12C8; 3 12SG7; 1 12J5; 1 12A7H. Dozens of useful components, coils, variable condensers, etc. Size: 151in. x 71in. x 6in. Weight 28 lbs. Supplied less the buzzer.

LASKY'S PRICE

19/11

Carriage 5/- extra.

FOR CALIFORNIA ONLY. SPECIAL CLEARANCE OF ODD EX-GOVERNMENT CHASSIS TOO NUMEROUS TO LIST. Some partly stripped, others complete. Indicators, Receivers, Transmitters, Modulators, etc. Prices range from 1/- upwards. We strongly recommend you to pay us a visit and see for yourself the bargains available.

BRAND NEW AND UNUSED. In Maker's Original Carton. Ex.A.M. Unit Type 567 c.w.w. Containing 11 new valves: 2 5ZAG; 2 5UG; 1 VU120; 1 6XSGT; 1 LEF50; 1 EF55; 1 6V6G; 2 VS70 (voltage stabilisers). Dozens of various components, including high voltage condensers, chokes, pot.meters, resistances, condensers (8 mfd., 500 w.v.), etc. Totally enclosed in metal case, size : 12 x 11 x 8 in. Weight 40 lbs.

LASKY'S PRICE

49/6

Carriage 5/- extra.

V.H.F. RECEIVER UNITS. These units are partly stripped but contain a wealth of components, resistances, condensers, coils, I.F., transformers, etc. Also 4 valves; 2 EF39; 1 EBC33; 1 ELC32. Overall dimensions 101 x 74 x 6 in.

LASKY'S PRICE

10/-

Carriage 2 6 extra.

SPECIAL BARGAIN PARCEL FOR PERSONAL SET CONSTRUCTORS. 1 Pair Wearite Miniature I.F. Transformers, 465 kc/s. 4 Button Base Valve Holders. 1 Miniature .0005 mfd. two gang tuning condenser. 1 31in. Miniature Speaker.

LASKY'S PRICE FOR THE PARCEL

35/-

Post Free.

Send a 2d. stamp with your name and address in block letters please for a copy of our current list of Ex-Government Bargains. The Lasky's Radio Bulletin.

LASKY'S RADIO

370, HARROW ROAD, PADDINGTON, LONDON, W.9.
(Opposite Paddington Hospital). Telephone: CUNningham 1979
Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. Half-Day.



The Principles of Television Reception

By A. W. KEEN, M.I.R.E., A.M.Brit.I.R.E.

The author is a practising electronic research engineer and has produced a thorough, systematic work covering American as well as British practice. The entire receiving system is examined stage by stage, with diagrams, and complete circuits are given of four up-to-date commercial receivers. A chapter on colour television is also included. Profusely illustrated. 30/- net.

"Very well written and arranged . . . can be thoroughly recommended to the student and service engineer . . . extremely well illustrated."—WIRELESS AND ELECTRICAL TRADER.

Obtainable from booksellers. Published by

SIR ISAAC PITMAN & SONS, LTD.,
Parker Street, Kingsway, London, W.C.2.

PREMIER RA

MORRIS & CO. (RAL)

We are now supplying

NEW LONG RANGE TELEVISOR KITS
For the London or Birmingham frequencies at the same price as the standard kit. £17 17s. 0d.

5 Easy to Assemble Kits are supplied:

- Vision Receiver with valves, £3 13s. 6d. (Carriage 2/6)
 - Sound Receiver with valves, £2 14s. 6d. (Carriage 2/6)
 - Time Base with valves, £2 7s. 6d. (Carriage 2/6)
 - Power Supply Unit with valves, £6 3s. 0d. (Carriage 5/-)
 - Tube Assembly, £2 18s. 6d. (Carriage and packing 2/6)
- This unit includes the VCR 97 Tube, Tube Fittings, and Socket and a 6in. FM Moving Coil Speaker with closed field for Television.

The Instruction Book costs 2/6, but is credited if a Kit for the complete Televisor is purchased.

Any of these Kits may be purchased separately; in fact, any single part can be supplied. A complete priced list of all parts will be found in the Instruction Book.

20 valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver are a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

WORKING MODELS CAN BE SEEN DURING TRANSMITTING HOURS AT OUR FLEET STREET AND EDGWARE ROAD BRANCHES.

TV PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS.

We can supply the complete kit of parts to make this wide band width Pre-Amplifier, using 2 EF54 Pentodes. Powered by the TV Kit, it is completely screened. With all parts, valves, chassis, diagrams, etc., 2/6. All parts available separately.

The New Premier Catalogue, now ready, includes all the new TV Kits, Receiver Kits and thousands of component bargains. Send 3d. for copy.


POST ORDERS TO 167, LOWER CLAPTON RD., E.S.

CALLERS TO 152/3, FLEET ST., E.C.4. Central 2833.

NEW BRANCH : 207, EDGWARE RD., W.2. Ambassador 4600.

This Branch is open until 6 p.m. on Saturdays.

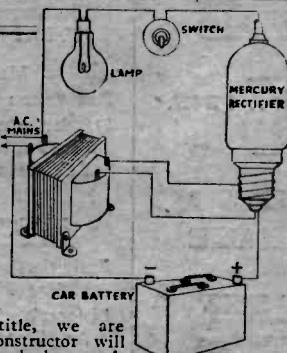A CAR OR WIRELESS BATTERY CHARGER FOR 7/6.



When writing the title, we are assuming that the constructor will already have in his junk box such items as a mains transformer giving 4 v., a lamp holder and odds and ends in the way of wire, etc. If you haven't got these items already, then, of course, it will cost you more than 7/6d., which is just the price of the Mercury Rectifier, but not a lot more, for we can supply a suitable mains transformer for 6/6d., and a switch for 1/6d., a lamp holder for 9d., a pair of bulldog clips for connecting to battery for 1/-, Wire, 1d. per yard.

The Mercury Rectifier is, of course, suitable for many other jobs. Its data is as follows: Filament voltage 4 v. Filament Current 9 amps., peak plate voltage 2,000, peak plate current 2.5 amps. Official price several pounds each, our price, 7/6d., six for £2. All are Brand New and in Original Cartons. Any faulty will be replaced within three days. This is one of our many Sale Bargains. Send 2d. for special "Sale List."



PRECISION EQUIPMENT

7, Electron House, Ruislip Manor, Middx.

MAGI
picture size

WHITE RUBBER

METER KIT. A FERRAR with separate high stability measure, 15, 60, 150 and 600 v. D.C. 2j.in. 10/- the complete kit.

PREMIER MIDGET RADIO KIT

production, we are now able to offer reduced price. Including an attractive long x 5in. wide x 6in. high. The valve 6V6 and a Selenium Rectifier in the A.C. 617, 25A6 and Selenium Rectifier in the A.C. Both are for use on 200 to 250 volt mains. The set and the receiver presents a very attractive coverage is for the medium and long wave. Complete kit of parts with cabinet and including Purchase Tax.

R107. One of the Army's Finest Receivers. (See "W.W." August, 1945) 9 valves, R.F. amp, osc. Frequency Change 2nd Detector, A.V.C. A.F. amp, B.F.O. A.C. or 12 v. accumulator. Frequency range mclis to 2.9 mclis, 3.0 to 1.2 mclis. Complete. Write for full details. Price carriage and packing.

Have you had details of
PREMIER MAGNETIC TE
Using 9in. or 12in.

One-Value Battery
Pyramidal
valver (H)
The Size
Two-value
Three
Sum
T

FREE TO AMBITIOUS ENGINEERS!

Have you sent for your copy?

ENGINEERING OPPORTUNITIES

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £10 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.



--- FREE COUPON ---

Please send me your FREE 176-page
"ENGINEERING OPPORTUNITIES"

NAME

ADDRESS

Subject or Exam.

that interests me

British Institute of Engineering Technology
409B, Shakespeare House,
17/19, Stratford Place, London, W.1

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production
Building
Draughts
Telephony
GET 9/-
LETTER
AFTER YOU—

NAMES

A.M.I.Mech.E.

A.M.I.E.E.

A.M.I.C.E.

A.M.I.P.E.

A.M.I.M.I.

L.I.O.B.

A.F.R.Ae.S.

B.Sc.

A.M.Brit.I.R.E.

CITY & GUILDS

MATRICULATION, etc.

BIET