

AN ECONOMY QUALITY AMPLIFIER




Vol. 29 No. 565

NOVEMBER, 1953

EDITOR:

F.J.CAMM

PRACTICAL WIRELESS

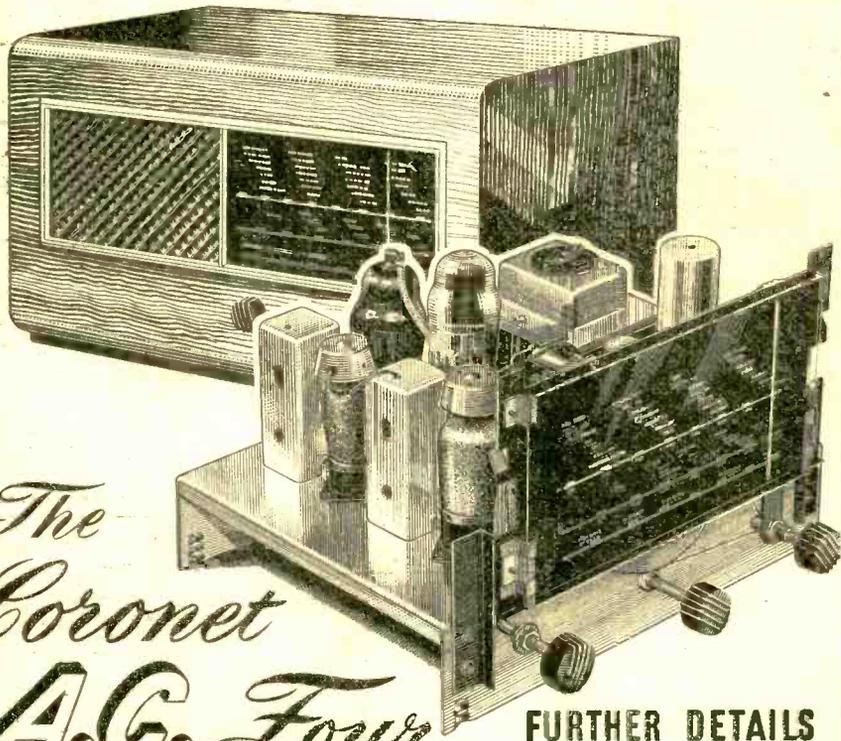

*The
Coronet
A.C. Four*

FURTHER DETAILS

IN THIS ISSUE :

A POLYPHONIC ORGAN
A 27 Mc/s. RECEIVER
EFFICIENCY MODULATION SYSTEMS

THE MINI-AMP,
ADDING A.V.C. TO STRAIGHT
RECEIVERS



OPEN TILL 6 PM SATURDAYS

TELEPHONES: AMBASSADOR 4033 & PADDINGTON 5271/2

PREMIER RADIO COMPANY

(REGD.) B. H. MORRIS & CO (RADIO) LTD. EST. 40 YRS.

THIS IS OUR ONLY ADDRESS (Dept. P.W.) 207 EDGWARE ROAD LONDON W2 THIS IS OUR ONLY ADDRESS

BUILD A PROFESSIONAL LOOKING RADIO SET AT LESS THAN HALF TO-DAY'S PRICE

We can supply all the parts to help you.

- Drum (2 1/2" diam.), 1/6
- Driving head 1/8
- Double pointer 4s.
- Spring 3d.
- Nylon Cord (yard) 6d.
- Dial Front 2/6
- Plate 2/6




- Engraved Glass Dial, 180-550 and 800-2,200 m. With station names, new wavebands ... 1/6
- T.R.F. Coils, 180-550, 800-2,200 metres, pair Punched chassis, 3-valve plus rectifier T.R.F. Cabinet, Bakelite, in Walnut or Ivory or Wooten in Walnut finish ... 3/9
- Packing and Insurance ... 1/6
- SEND 1/6 FOR EASY TO FOLLOW POINT-TO-POINT DIAGRAMS AND TREAT DIAGRAM which shows how YOU can build the Receiver illustrated above.

THE COMPLETE KIT

To construct a 3-valve plus rectifier T.R.F. Receiver for use on 200-250 v. A.C. mains can be supplied at **£5 19/6**, plus 2/6 packing and carriage. Each kit is complete in every detail, nothing has to be made or improvised. Easy to follow point-to-point diagrams are supplied making construction very simple. The Dial is illuminated and the Receiver housed in its Cabinet size 12in. x 5in. x 6in., presents an attractive appearance. The valve line-up is: 717A—H.F. Pentode. VR110—Detector. APT4—Output and Metal Rectifier.

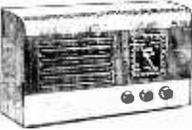Waveband coverage is for the medium and long bands. (Choice of 3 cabinets: Bakelite in Walnut or Ivory, or Wooten in Walnut finish)



WILLIAMSON AMPLIFIER KIT
A complete kit of parts for the construction of the latest version of this famous amplifier complete with valves, output and mains transformers.

15 Gns.

Plus 7/6 p.kg., carr. and ins.

WILLIAMSON AMPLIFIER TRANSFORMERS (To specification)
The Output Transformer 2.6 ohms sec., **£4 4/-**. The Mains Transformer, PREMIER SP425A. **£3 7/6**.

MOVING COIL MICROPHONE

Low impedance. Incorporates press-to-talk switch. Housed in strong black bakelite case. Dimensions: 2in. wide 1 1/2 in. high. 1 1/2 in. deep.
Plus 1/6 post and packing. **19/6**
A matching transformer for high impedance can be supplied at 3/6 extra.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT

As parts to construct an eliminator to give an output of 120 volts at 20 m.A., and 2 volts to charge an accumulator. Uses metal rectifier, **£2.**

Govt. Surplus Ex. W.D. STEEL AERIALS

Also ideal for fishing rods—ALL BRASS VEEV 12ft. 3 1/2 in. sections of copper-plated steel highly flexible tapering 2in. to 1in. Brand new in container. Plug-in type, 9/8. Screw-in type, 7/8. Packing and carriage, 1/6. Insulated base, 3/-. Webbing waterproof carrying case with shoulder sling, 2/6.

ACCUMULATORS

- Lead Acid Celluloid Non-Spill, 2 v., 7 amps. ... 2/8
- 2 volt 10 amp. (the famous maker) 4/11

Famous Set Manufacturer's surplus of ELECTRIC GRAM UNITS

Two-speed, 33 1/3 and 78 r.p.m. For playing Standard and L.P. recordings. Complete with Turntable. For use on 200-250 v. A.C. mains. Each unit is in its original manufacturer's cartoned and is fully guaranteed. Limited quantity only available at approx. half list price.



£4.2.6

Plus 2/6 pkg., carr., ins.

SPECIAL OFFER THE FAMOUS "CHANCERY" HIGH FIDELITY MICROCELL PICK-UP TYPE GPX for Standard and Long Playing



The Chancery Light Weight GPX Pick-up embodies certain unique features achieving a standard of performance not possible with normal magnetic or crystal pick-ups. The secret of the high standard of performance is in the use of the special microcell crystal cartridge assembly which has an unusually wide frequency response. The sapphire stylus is precision ground and semi-permanent. With two cartridges, 1 L.P. and 1 Standard. Price 52/8. Additional L.P. or Standard Cartridges can be supplied from stock at 19/6 each.

Quality Crystal Pick-up Bothwell Type 1143. Price 26/-. Plus 1/6 Pkg. and Carr.

GRAMOPHONE CABINETS—Portable

A fortunate purchase of a manufacturer's surplus stock enables us to offer this first grade Portable Cabinet, made by a famous manufacturer at the remarkably low price of **25/-**. Plus 2/6 p.kg. and carr.



SPECIFICATION.
Substantial Wooten Case. Rexine Covered. Loudspeaker motor heard directly out to take a Gramophone Unit. Almost any make of Rim Drive Unit can be accommodated with ease. Outside dimensions: Height (when closed), 5 1/2 in.; Length, 14 1/2 in.; Depth, 12 1/2 in.; Clearance space under motor board, 2 1/2 in.; Clearance space from motor board to inside lid when closed, 2 1/2 in.

As a special offer for a limited period only the above Gramophone Unit, Pick-up and Cabinet assembled into a complete Portable Electric Gramophone ready to plug-in to your Radio or Amplifier, can be supplied at **£7.19.6** Plus 5/- Pkg., Carr., & Ins.

GRAMOPHONE UNITS

GARRARD Type 75. Latest 3-speed Autochange Unit complete with 2 Acos High Fidelity G.P.19 Pick-up Heads, 1 L.P. and 1 Standard. **£14.19.6**

GARRARD Rim Drive 78 r.p.m., complete with magnetic pick-up and turntable ... **£5.19.6**

COLLARO 3-speed single gram unit complete with lead for L.P. and Standard recordings ... **£8.0.0**

Packing and carriage on each of the above units, 2/8.

TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. OVER £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

PREMIER MAINS TRANSFORMERS

All primaries are tapped for 200-250 v. mains 40-100 cycles. All primaries are screened. All LT's are centre tapped.

- SP175B, 175-0-175, 50 mA., 4 v. @ 1 a. 4 v. @ 2 a. 4 v. @ 3 a. 4 v. ... 25/-
- SP301B, 300-0-300, 120 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. ... 28/-
- SP350A, 350-0-350, 100 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. ... 29/-
- SP351, 350-0-350, 150 mA., 4 v. @ 1-2 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. ... 38/-
- SP352, 350-0-350, 150 mA., 5 v. 2-3 a. 6.3 v. 2-3 a. 6.3 v. 2-3 a. ... 36/-
- SP375A, 375-0-375, 250 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-3 a. ... 55/-
- SP501, 500-0-500, 150 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 2-2 a. 4 v. @ 3-5 a. ... 47/-
- SP501A, 500-0-500, 150 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. 6.3 v. @ 2-3 a. ... 50/-
- SP425A, 425-0-425, 200 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-3 a. 250-0-250, 80 mA., 6.3 v. @ 4 a. 5 v. @ 2 a. ... 19/8
- 350-0-350, 80 mA., 6.3 v. @ 4 a. 5 v. @ 2 a. ... 10/6
- 200-250-250, output 3 v. 50 v. @ 2 a. ... 17/8
- Charger, 250-12 v. @ 1.5 a. ... 12/6
- Mains Transformer, sub chassis mounted, 315-0-315, 70 mA., 5 v. @ 2 a. 6.3 v. @ 2-3 a. ... 10/8

LOUDSPEAKERS

- ELAC—2 1/2 in. dia., Moving Coil 15 ohms impud. ... 15/-
- PLESSEY—3 in. dia., Moving Coil, 3 ohms impud. ... 15/-
- ELAC—3 1/2 in. dia., Moving Coil, 3 ohms impud. ... 15/-
- ELAC—4 in. dia., Moving Coil, 3 ohms impud. ... 14/6
- PLESSEY—5 in. dia., Mains Energised 3 ohms impud. (600 ohms field) with Pentode Transformer ... 22/6
- PLESSEY—8 in. dia., Mains Energised 3 ohms impud. (600 ohms field) ... 18/6
- PLESSEY—10 in. dia., Moving Coil, 3 ohms impud. ... 23/6
- GOODMANS—12 in. dia., Moving Coil, 15 ohms. ... 48/8
- Plus 5/- packing and carriage.
- VITAVOX—K 12 20 12 in. dia., Moving Coil, 15 ohms impud. ... 111/11
- Plus 5/- packing and carriage.

ALL 12in. SPEAKERS TAX FREE.

112A RECEIVER UNITS

11 valve superhet receiver, covering 100 to 121 Mc/s, using four VR53, two VR56, and VR65, VR67, VR70, VR54, and VR57 valves. Fitted with Tuning meter, slow-motion drive, R.F. and L.P. Gain Control, etc. Circuit: R.F. amp. Frequency changer, oscillator and stab., 3-L.F. amps, B.F.O. Det., First audio and output. Brand New with circuit diagram.

PRICE 59/6 plus 7/6 pkg., carr., ins.

C.R. TUBES

VCR 516
5in. Blue picture. Heater Volts 4, Anode 4 Kv., in Manufacturer's original Carton.
PRICE £3/19/6



Plus 5/- pkg., carr., ins. ALL BRAND NEW

VCR 517

6 1/2 in. picture. This tube is a replacement for the VCR57 and VCR57. Guaranteed full size picture. PRICE 35/-, Plus 2/6 pkg., carr., ins.

STOP PRESS!!!

1155 RECEIVERS—Slightly soiled. In original case, complete with 10 valves. Frequency range 18.5 Mc/s - 75 K/cs. **£7.19.6** in 5 wavebands. Pkg. & Carr. 10/6.



NEW - Z 729

Low Noise Voltage Amplifying Pentode



The new OSRAM Z729 is a low hum, low microphony voltage amplifying pentode of all-glass construction on the B9A base. The heater is rated at 6.3V, 0.2A.

The Z729 is of small physical size, rigid construction with effective internal screening and has been designed for use in conditions where the hum and microphony introduced by the valve must be kept to the minimum.

Typical applications include the early stages of high gain amplifiers, particularly where bass boost circuits are used, such as low level tape and disc pre-amplifiers, in sound reinforcement systems and microphone head amplifiers. A variable hum-balancing resistor is not required if the heater winding has an earthed

centre-tap, and using the circuit shown a gain of 110 can be obtained whilst the hum voltage referred to the control grid will not exceed 1.5µV. This figure represents an improvement of at least 17 db over a valve of normal construction with good low hum characteristics used with a hum balancing circuit.

CHARACTERISTICS

V_a	250	V
V_{g2}	140	V
I_a	2	MΩ
I_b	3	mA
G_m	1.85	mA/V


I Send NOW for Data Sheet to-Osram Valve and Electronics Dept.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2

FIRST CHOICE IN ELECTRIC SOLDERGUNS

FOR ECONOMIC AND ACCURATE SOLDERING
You'll be wiser to use
Wolf
 Electric
 SOLDERGUNS & SOLDERING IRONS

Designed for faster, cheaper and easier soldering, Wolf Solderguns and Soldering Irons meet all requirements from fine instrument to heavy industrial work. In addition to the Type 51 trigger feed soldergun which is superb for rapid repair or assembly jobs, there are eight other models to choose from, including three with straight handles. Rapid constant localised heat, low current consumption, perfect balance and utmost dependability are some of the reasons why Industry insists on Wolf.

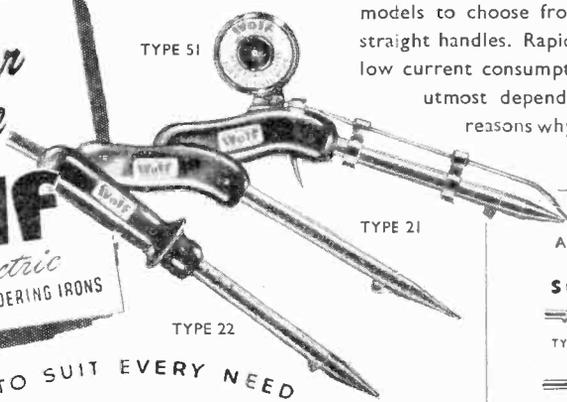


WIDE RANGE TO SUIT EVERY NEED

Obtainable from all leading tool merchants.

Fully descriptive brochure free on request.

ALTERNATIVE TYPES AVAILABLE SOLDERGUNS

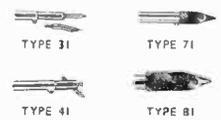

SOLDERING IRONS




WOLF ELECTRIC TOOLS LTD PIONEER WORKS HANGER LANE LONDON S.W.5
 Tel: PERIVALE 5631 4 Branches: BIRMINGHAM MANCHESTER LEEDS BRISTOL NEWCASTLE GLASGOW


BARTON'S (Radio) LIMITED Comes to Town...

BUILD YOUR OWN RADIO!

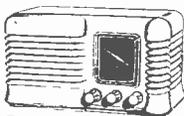We can supply all the parts (including valves, 5in. moving coil speaker, cabinet, chassis and everything down to the last nut and bolt) to enable YOU to build a professional-looking radio at a total cost of



£5.15.0 Plus p. & c. 2/6.

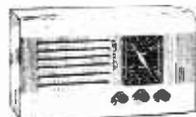

This is a 3-valve plus metal rectifier T.R.F. Receiver with a valve line-up as follows:

6K7 (H.F.), 6J7 (Det.) and 6V6 (Output). The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage

is for the medium and long wavebands. Operates on 200-250 volt A.C. mains. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets: 12in. long, 5in. wide by 6in. high as follows: either Ivory or Brown Bakelite. Wooden finished in walnut. Complete and easy to follow point to point, and circuit wiring diagrams supplied. Circuit diagrams and priced parts list available separately if required at 1-. To those who want the above receiver ready built we can supply it at £6.19.6. Plus 3/6 pkr. carr.

BATTERY CHARGER KIT
Incorporates metal rectifier. Transformer is suitable for A.C. Mains 200-250 volts. Charges either 12, 6 or 2 volt accumulator at 1 amp. Complete with circuit diagram. Price 25 - plus 1/6 post and packing.

CHARGER TRANSFORMER
For charging 6v. at 1 amp. 8/3 plus 1/- p.p.

SEND 2½ STAMP FOR FREE 28p. LIST



LOUDSPEAKER CABINETS

A well-made wooden cabinet of modern design, polished walnut finish with metal mesh speaker net. 2 sizes available: to take 8in. speaker, cabinet size 9 1/2in. L x 9in. H. 17/6; to take 8in. speaker, cabinet size 10 1/2in. L x 10 1/2in. H. 22/6. plus 1/6 pkr. carr.

LOUDSPEAKERS (Suitable for above). PLESSEY 6in. dia. 3 ohms impd., 12/6. Plus 1/6 P. PLESSEY 8in. dia. 3 ohms impd., 13/6. Plus 1/6 P.

LOUDSPEAKERS (3 ohms impedance). ELAC 5in. dia., 13/6; 10in. dia., 22/6. Plus 1/6 P. TRUVON 12in. 8 ohms impd., 59/6.

WE HAVE PLEASURE IN ANNOUNCING THE OPENING OF OUR NEW SHOP, WHERE BOTH OLD AND NEW CUSTOMERS WILL BE CORDIALLY WELCOMED



PLEASE ADDRESS ALL ORDERS AND ENQUIRIES TO: DEPT. P.W.

42 · TOTTENHAM COURT ROAD · LONDON · W · 1

Telephones LANGHAM 1151/2

TERMS OF BUSINESS: Cash with order, or C.O.D. (Post items only) - all orders for small items totalling over £2 post free, unless otherwise stated.

HOURS OF BUSINESS—9 a.m. to 6 p.m. Saturday, 9 a.m. to 3 p.m.

QUALITY GOODS · MONEY BACK GUARANTEE · PROMPT DESPATCH



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY. With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from £1 per month

POST THIS COUPON TODAY

Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 32K 43 Grove Park Road, London, W.4. Phone: Chiswick 4417/8.


NAME

ADDRESS

SUBJECT(S) OF INTEREST

EMI INSTITUTES

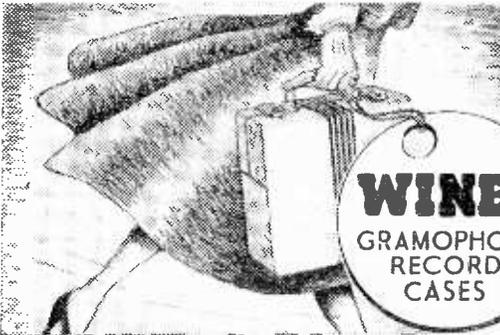The only Postal College which is part of a world-wide Industrial Organisation.



WINEL
GRAMOPHONE
RECORD
CASES

Essential for the Safe Storage. Simple Reference and Handy Carriage of Gramophone Records. Wide assortment of Sizes and Colours. Write for illustrated catalogue, and name and address of nearest Retailer.

HENRY ELWIN LTD.

(DEPT. M2)

Makers of Top Quality Record Cases, Albums, Cabinets and Covers.

NOTTINGHAM

COPPER INSTRUMENT WIRE (ex-stock)

SWG	Inch	ENAMELLED		TINNED		COTTON COVERED		SILK COVERED	
		2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.	4 ozs.
16	.064	1/4	2/1	1/4	2/-	1/4	2/-	1/4	2/-
17	.055	1/4	2/1	1/4	2/1	1/4	2/1	1/4	2/1
18	.048	1/4	2/2	1/4	2/2	1/4	2/2	1/4	2/2
19	.040	1/4	2/3	—	—	1/5	2/3	1/6	2/5
20	.036	1/5	2/4	—	1/5	2/4	1/5	2/4	1/7
21	.032	1/5	2/5	1/6	2/5	1/5	2/5	1/8	2/10
22	.028	1/6	2/6	1/6	2/6	1/6	2/6	1/9	3/-
23	.024	1/7	2/7	1/7	2/7	1/7	2/7	1/10	3/2
24	.022	1/7	2/8	1/7	2/8	1/7	2/8	1/10	3/2
25	.020	1/8	2/9	1/8	2/9	1/8	2/9	1/11	3/4
26	.018	1/8	2/10	1/8	2/10	1/9	2/11	2/-	3/6
27	.0164	1/9	2/11	1/9	2/11	1/10	3/1	2/1	3/8
28	.0148	1/9	3/-	1/9	3/-	1/10	3/2	2/2	3/10
29	.0136	1/10	3/1	1/10	3/1	1/11	3/4	2/2	4/-
30	.0124	1/10	3/2	1/11	3/5	2/-	3/6	2/2	4/2
31	.0116	1/11	3/3	2/-	3/6	2/1	3/7	2/2	4/4
32	.0108	1/11	3/4	2/1	3/8	2/1	3/8	2/2	4/8
33	.010	2/-	3/5	2/2	3/10	2/3	3/11	2/10	5/2
34	.0092	2/-	3/6	2/3	4/-	2/4	4/2	2/11	5/4
35	.0081	2/1	3/7	2/4	4/2	2/6	4/5	3/1	5/8
36	.0076	2/1	3/8	2/6	4/5	2/7	4/8	3/5	6/0
37	.0063	2/2	3/13	2/7	4/1	3/-	5/6	3/5	6/4
38	.006	2/3	4/-	2/9	4/11	3/4	6/2	3/7	6/8
39	.0052	2/4	4/2	2/10	5/2	—	3/10	4/11	7/2
40	.0048	2/5	4/4	3/-	5/6	4/7	8/2	—	7/8
41	.0044	1/6 per oz.	—	1/9 per oz.	—	—	—	2/5 per oz.	—
42	.004	1/9	—	2/-	—	—	—	2/6	—
43	.0036	2/3	—	2/5	—	—	—	3/-	—
44	.0032	3/-	—	—	—	—	—	4/-	—
45	.0028	4/-	—	—	—	—	—	5/6	—
46	.0024	5/-	—	5/-	—	—	—	7/6	—

47 and 48 swg Enam. and 47 swg E.S.S.C. wires in stock. State needs. All above postage extra. POST ORDERS ONLY PLEASE. Send stamp for comprehensive lists.

POST RADIO SUPPLIES

33 BOURNE GARDENS, LONDON, E.4 TEL: GLISSOLD 4E88 & 2021

EUREKA & CONSTANTAN RESISTANCE WIRES
"ALL GAUGES STOCKED"

G.E.C. & B.T.H. GERMANIUM CRYSTAL DIODES

G.E.C. GLASS TYPE 5/16in. x 3/16in. B.T.H. LATEST TYPE MOULDED IN THERMO-SETTING PLASTIC

Both Wire Ends for Easy Fixing. 4/6 each, postage 2½d.

B.T.H. SILICON CRYSTAL VALVE
3/6 each, postage 2½d. Fixing Brackets 3d. Extra.

Wiring instructions for a cheap, simple but high quality Crystal Set included with each Diode and Crystal Valve.

CRYSTAL SET

INCORPORATING THE SILICON CRYSTAL VALVE
Adjustable Iron Cored Coil.

RECEPTION GUARANTEED
Polished wood cabinet, 15/-, post 11d. A REAL CRYSTAL SET. NOT A TOY

CRYSTAL SET

As above, but with Germanium Crystal Diode, 16/-. Postage 11d.

B.A. SCREWS, NUTS, WASHERS soldering tags, eyelets and rivets. EBONITE AND BAKELITE PANELS, TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.

GARLAND BROS. LTD

CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8.
5 OBELISK PARADE, LEWISHAM, S.E.13.

TEL.: TIDEWAY 4412/3
TEL.: LEE GREEN 4038

TRUVOX TAPE DESK MARK III. Incorporating high impedance mu-metal twin-track heads. Two speed capstan, for tape speeds of 7½ and 3½ inches per second. Three heavy-duty motors allowing for fast forward and rewind facilities without tape handling. All controls operated by electrically and mechanically inter-locked push buttons. Price £23/2/- . Plus 10/- carriage, etc. Send S.A.E. for full particulars. Delivery from stock.

THE LATEST LANE TAPE TABLE. Incorporating three heavy duty Lane motors; fast rewind and wind-on without tape handling; automatic braking; high impedance half-track heads; spool locking device. Tape speed 7½ in. per second. Price £17/10/- . Carriage 10/-.

GARLAND UEB7 RECORD PLAY-BACK AMPLIFIER. A revised version of our popular amplifier designed to suit Truvox Tape Desk or Lane Tape Table. New features include magic eye record level indicator, provision for external loudspeaker and for feeding P.A. amplifier. Oscillator and power supplies included. Standard valves throughout. Formica control panel. Supplied complete with 8in. P.M. loudspeaker. Price £13/2/6 plus 7/6 carriage, etc.

MAGNETIC TAPE. Now available, the new Scotch Boy High Coercivity Tape MC2-III, with higher output and signal-to-noise ratio. Price 35/- per 1,200ft. reel. Still available: Scotch Boy MC1-III: 1,200ft., 35/-; 600ft., 21/-; 300ft., 12/3. Spare 7in. spools, 4/3. Ferrovoice, the new

kraft-based medium coercivity tape: 1,200 ft., 22/6. Spare 7in. spools, 4/6. Magnetophone Tape: £2 per 1,200ft. reel.

CRYSTAL DIODES Germanium Vacuum sealed glass type with wire ends, 2/8 each or 30/- per dozen.

TYANA SOLDERING IRONS. Lightweight 40 watt irons with easily interchangeable elements and 3/16in. diameter bits. Voltage ranges, 100/110v., 200/220 v. and 230/250 v. Price 16/9. The iron that makes soldering a pleasure.

VARLEY MAINS TRANSFORMERS. Primary 10-0-200-220-240 volts. Secondary 300-0-300 volts at 150 mA., 5 volt at 3 amps., 6.3 volt at 4 amps., 6.3 volts at 1 amp. Open type construction. Price 45/-, post 2/6.

BRENETTE MICROPHONES. Large sales of these popular microphones have enabled us to make substantial reductions in the prices. The following range is available: **Type 9ND:** Multi-directional ball-type, in black and chrome, £2/2/-, post 2/-. **Type 7D:** Directional type, for instrumental or vocal use; in black and chrome, £3/15/-, post 2/6. **Type IIA:** A wide-frequency-response microphone, in brown cast case with chrome grill, £5/5/-, post 2/6. **Type 13U:** A highly sensitive studio microphone with outstanding frequency characteristics. Flexible mounting enables it to be used directionally or not as required. Black and chrome finish, £6/6/-, post 3/6.

DECALS. 3500 ½ in. high white transfer letters and words for marking electronic equipment. Price 4/9 per book. The new

Decals book for the amateur now available. 29 words per page, 4 pages radio and audio, 4 pages T/V and Scope, 2 pages misc. incl. Tx. and Tape Recording, 3/6 per book. Post 3d. either book.

GENERAL PURPOSE TRIODES. Type 2C/22 (7193), similar to 6J5G, but anode and grid brought out to top caps. Price 11/6 per half-dozen, post paid (minimum quantity).

RADAR REFLECTORS. Type MX138/-A. These consist of 6—2ft. x ½ in. dural tubes covered with fine wire mesh. The whole assembly can be used as an omni-directional aerial, and the mesh has many horticultural applications. Price 3/9 each, post 9d. Type MX137A: similar to above, but also include a telescopic aerial rod, extending from 1½ in. to 3ft. 6in. approx. Price 4/9 each. Post 9d.

WHANDA WIRE AND CABLE STRIPPERS, to take all size flexes and cables up to ½ in. diam. with 3 alternative heads and triple screw adjustment. These are brand new and boxed, and the original price was 15/- each. Our price 5/- each, post paid.

AERIAL RODS. These popular rods, of tough steel copper-plated, are 12in. long, and fit into each other to make any length. Many hundreds of thousands sold to T/V aerial manufacturers and to the public. Price 3/6 per doz. or £1 per 100, post paid. £10 per box of 1,500 carriage paid U.K.

ELECTRO - MAGNETIC CONDUCTORS. Energised at 9.14 volt, ½ Amp.; maximum switched current 40 Amps. In bakelite case. Price 2/9.


BRIMISTORS. Non-linear resistors to protect valves from current surges: CZ1, 0.3 A., 8/6; CZ2, 0.3 A., 2/6; CZ3, 0.2 A., 4/6; CZ4, 1.25 A., 5/-; CZ6, 0.45 A., 3/6.

PRATTS RADIO

1070 Harrow Road, London, N.W.10

Tel.: LADBROKE 1734.

(Nr. Scrubs Lane)

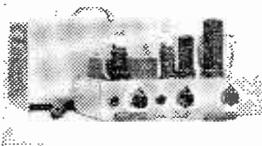

AMPLIFIERS. — College General Purpose Unit, MODEL AC108 (as illustrated) 1½ watt, 4 valve unit. Neg. feedback. SEPARATE mike stage and SIP BAY, mike and gram inputs, 2 faders and tone control. Input volts, mike 003, gram, 35 v., £10.7.6. MODEL AC18E 6 valve unit with P.P. output of 18½ watts. SEPARATE mike stage and gram inputs, 2 faders and tone control. Feedback over 3 stages. Input volts, mike, 003, gram, 3 v. £15.5.0. MODEL AC32E. — Spec. as AC18E, but with a larger output stage of 32 watts, £18.15.0. MODEL U.10E. — D.C. A.C. mains. P.P. output of 10 watts. Spec. as AC18E £12.19.6. All above amplifiers are COMPLETE with metal case, chrome handles, and outputs to match 3, 8 or 15 ohm speakers. All A.C. models have H.T. and L.T. output sockets for tuning units, etc. All amplifiers have sectionised O.Trans. wound on super silicon laminations. Power pack to operate the above from 12v. bat. available.

QUALITY AMPLIFIER CHASSIS FOR RECORDS, ETC. — MODEL Q9C 6 valve unit with bass and treble controls. Inputs for radio L.P., standard records. Output imp. to choice. This amplifier uses a Williamson 18 section output transformer. Output of 9 watts. Adjustable negative feedback, £13.18.6. MODEL Q4C 4 valve unit similar to Q9C. Output 4 watts, £9.15.0.

FULL RANGE OF PLAYERS, MOTORS, ETC. (LIST AVAILABLE). — MICROPHONES, PICK-UPS, SPEAKERS AVAILABLE.

COLLEGE TRANSFORMERS, etc. — Filament, 6 v. 2 a., 6/9; 6 v. 3 a., 8/6; 12 v. 1½ a., 8/6. Mains 2 x 350 v. 80 m.a. 0-45 v., 0-4-6 v.; 2 x 250 v., ditto, 2 x 275 ditto, all 17 6 each. 2 x 450 v. 250 m.a. 6 v., 6 v., 5 v., 49/6. Wt. 10½ lbs. High Quality Output Transformers: Sectionalised C.A.I. 10,000 to 3, 8, 15 ohms (P.P. 6V6, 6F6, etc.) 20 watt rating. Wt. 4½ lbs., 18/6. CA2, 6,600 to 3, 8, 15 ohms, 30 watt rating (P.P. 6L6), wt., 5½ lbs., 27/6. Williamson. Exact to spec. 1.6 or 3.6 ohms types, 75/6.

CHOKES. — 60 m.a. 20 hv., 5/9; 60 m.a. 10 hv., 4/9; 100 m.a. 10 hv., 6/9; 150 m.a., 20 hv., 17/6; 250 m.a., 20 hv., 19/6. All goods are brand new, no surplus used. Amplifiers are carriage paid. Transformers, etc., postage up to 10/-, 6d.; 41, 1/-; above £2 free. Stamp for lists. State interest.

HOME CONSTRUCTORS

£1 JUNK BOX £1

Assorted Condensers, Reactors, Beards, Meters, Valves, Terminals, V. Holders, Chassis, Files, N. Punch, etc. All Packed in Fine Case.

Carriage £1 Paid.

TR1 Receiver (valved) at 15/-, 25/7 11/0. Receiver Complete at 27/6.

VALVES

FW1 500	8/6	EF39	7/8	SP31	2/6	807	7/-
5U4G	8/6	FRC33	7/6	SP11	2/6	HL2K	2/6
5Z4	9/-	EL52	7/-	Pen1	5/-	Pen22	2/6
5Z4	7/6	EL50	7/6	EP54	5/6	KT2	8/-
VU129	3/-	EF36	5/6	EC52	5/-	SG215	2/-
VU111	2/-	EF8	8/-	EC51	5/9	LP211	2/-
VU133	2/6	KT11	6/6	CV6	8/9	IT1	8/-
6X5	7/6	KT8	6/6	6Q7	8/6	1B5	8/-
VR91(Sy)	EA50	2/-	6K7	6/-	1B5	8/-	
Red 63	EP34	2/-	6L5	12/-	IR3	8/-	
VR4	5/-	DI	2/-				

CONDENSERS. — Electrolytic W.E., 450 v. wkg., 8 mid., 2.6, 8+3 mid., 3.9, 16+16 mid., 4.6. Duplicer Drilitic 500 v. wkg., 16 mid. W.E., 3.9.

RESISTORS. — New Erie, etc., 1, 1.1, 2 w. our selection. 12 8 100. Meters, assort. dozen at 30/-, 6 at 15/-, 5, 30, 50, 100, 300, 500 mA., mc., 5, 3.5, 4, 6 amp. T.C. ali at 5/6. 3.3 kV. mc at 9/6. 1.5 kV. elect., 15/-.

VINER'S (Middlesbrough)

Radio Electrical

26, EAST STREET, MIDDLESBROUGH

Tel.: (MID) 2418.

THE "TELE-VIEWER"

5 CHANNEL TELEVISOR

A Design of a Complete 12in. or 9in.


SUPERHET T.V. RECEIVER FOR THE HOME CONSTRUCTOR

This receiver has been developed after most careful research and affords a high standard of Television entertainment by producing a picture of *really outstanding* quality.

We confidently believe that not only have we achieved a T.V. Receiver that surpasses in efficiency any other designed for the home constructor, but that successful construction, even by the most inexperienced is assured by the step by step wiring detail and diagrams provided, and at about half the cost of the nearest comparable commercial receiver.

Here are some of the features which combine to make this such a fine receiver :

- The Superhet circuit easily tuned to any of the five channels, i.e. LONDON, SUTTON COLDFIELD, HOLME MOSS, WENVOE and KIRK-O-SHOTT'S. (The extreme ease of tuning is accomplished by the provision of pre-aligned I.F.T.'s.)
- A lifelike, almost stereoscopic, picture quality made possible by the following factors :
 - (a) Excellent band width of I.F. circuits. (b) A really efficient video amplifier. (c) C.R.T. Grid modulated from low impedance source. (d) High E.H.T. voltage (approx. 10 kV.)
 The picture brilliance is also much above the average and enables comfortable viewing with normal room lighting or daylight.
- FIRM picture "HOLD" circuits (Frame-Line) ensure a steady picture, free from bounce or flicker even under the most adverse conditions met with in "fringe" areas and excellent "interlace" ensures the absence of "liney effect."
- Negative feedback is used in the audio frequency circuits which provide 2/3 watts of High Quality Sound.
- Entire receiver built on two chassis units, each measuring 14½in. x 6½in. x 3½in.
- Rigid C.R.T. mounting enables entire receiver to be safely handled with tube in position.
- All pre-set controls are mounted on side of chassis enabling all adjustments to be carried out whilst facing the C.R. Tube. As no hire purchase terms are available the receiver can be bought in five separate stages (practical diagrams and circuits are provided for each stage) thus enabling hire purchase interest rates to be avoided.

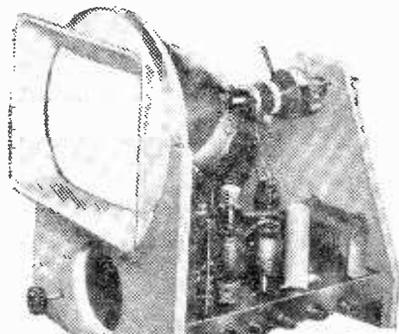

This complete TELEVISOR, including all Valves can be built for only **£28-16-4** (plus cost of C.R.T.)

We can sometimes supply New Mullard 12in. C.R.T. at the specially reduced price of **£13/17/6**. These, when available, are for purchasers of the Televiewer only.

Complete set of ASSEMBLY INSTRUCTIONS is now available, price 5/-. The instructions include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. A CABINET WILL ALSO BE AVAILABLE.

STERN & RADIO LTD.
103 & 115, FLEET STREET, E.C.4.
Tel. : CENTRAL 5812-3-4

R O M

INDUCTANCE BRIDGE KIT 42/6

50u/Hy.—1,000 u/Hy.
1,000 u/Hy.—20 M/Hy.
20 M/Hy.—400 M/Hy.
400 M/Hy.—8 Hy.
5 Hy.—100 Hy.

TREBLE AND BASS BOOST CHOKES
VIDEO CHOKES; SCRATCH FILTERS
R.F. COILS; SMOOTHING CHOKES
WHISTLE FILTERS: AUDIO, R.F.
A.C. INDUCTANCES IN GENERAL

Never before has an instrument capable of checking such a wide range of inductive components been offered at such a ridiculously low price.

RES/CAP. BRIDGE KIT 31/6

5 Megohms—50,000 ohms. 50 mfd.—.2 mfd.
100,000 ohms—1,000 ohms; 1 mfd.—.01 mfd.
1,000 ohms—10 ohms. .01 mfd.—.0005 mfd

As in the Inductance Bridge, each fully variable range is separately scaled for direct reading, AND CALIBRATED FOR YOU.

I.F. ALIGNER KIT, 15/-. Tunes over 465 Kc/s range of I.F. frequencies. Pre-tuned ready for use.

Full instructions and diagrams with all kits. No metal work to be done. Post and packing 1/6 in each case. Stamp with all enquiries, please. Cash with Order or C.O.D

RADIO MAIL 4, RALEIGH STREET, NOTTINGHAM

The solder for all HOME TELEVISION CONSTRUCTOR SETS

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60/40 High Tin Television and Radio Alloy. The size 1 Carton contains 55 feet of solder, costs 5/.



Ersin Multicore Solder

In case of difficulty in obtaining supplies, please write to : MULTICORE SOLDERS LTD. MULTICORE WORKS, MAYLANDS AVE., HEMEL HEMPSTEAD, HERTS. • Boxmoor 3636 (3 lines).

Practical Wireless

EVERY MONTH
VOL. XXIX, No. 565, NOVEMBER, 1953

Editor F. J. CAMM

22nd YEAR
OF ISSUE

COMMENTS OF THE MONTH

By THE EDITOR

Great Success of the "Coronet"

THE "Coronet," free blueprint which was given in last month's special Birthday Number was an immediate and outstanding success, more successful indeed than many of our pre-war receivers. The firms supplying the components report that although they had laid in heavy stocks they were rapidly absorbed. Arrangements have been made, however, for fresh supplies. In order to ease the situation regarding the coil pack we ourselves have made other arrangements, as announced in the further constructional details for the "Coronet" given in this issue.

We greatly value the thousands of letters and telegrams received from readers congratulating us on our Twenty-first Birthday Number, which rapidly sold out.

THE ADVANCE OF TAPE RECORDING

ONE of the outstanding features of this year's Radio Show was the large number of tape recorders exhibited and in which great interest was evinced by the public. It has become a new national hobby and it is now backed by a new and growing industry. Tape recorders must, of course, eventually replace wax discs, but that will not be for many years. Tape recorders will be considered as pieces of auxiliary equipment for many years to come. The combined radio-gram and television receiver with recording apparatus may not, however, be so far away. There is a need for it in these days of cramped home conditions when it is difficult to find space for another piece of apparatus. A kit for constructors was on view and it will shortly be dealt with in this journal.

The use of tape recorders on a national scale raises complicated and interesting questions of copyright. An enthusiast may record a radio programme or a number of gramophone records and play them under conditions which would infringe the copyright laws and the rules of the Performing Rights Society. It may not be general knowledge that almost every public house which has a piano, radio or television set installed must pay an annual fee to the Performing Rights Society to cover copyrights. Those who, therefore, see in tape recording a ready-made means of providing entertainment

at, say, a local hall, either as a part of a concert or to provide dance music, should take particular care over this matter by communicating with the Performing Rights Society.

THE ELECTRICIANS' STRIKE

THE early days of the Radio Show were marred by the strike of electricians which caused a number of stands to be unlit. In this respect we think that next year the Radio Industry Council should ask the Ears Court Authorities to seek assurances from all of the unions concerned that there will not be a strike during the run of the show. Strikes of this nature are attempts to make a rod of third parties—the exhibitors—in order to force employers to submit to claims.

After similar experiences a few years ago, when a strike commenced just before a show opened and lasted for some days after, we are surprised that these assurances have not been sought. One other point whilst we are dealing with the show; the seating accommodation is still inadequate and assurances should be sought also from the Ears Court authorities to ensure that their building is made acceptable to exhibitors and the public.

Apart from these points the exhibition was a great success; attendances were up and exhibitors reported good trade. The stands this year, too, were much more attractive than hitherto.

CAR RADIO LICENCES

THE Postmaster-General recently announced that the Ministry of Transport is co-operating with him by sending a note with motor-car licences setting out the wireless licence requirements. Motorists are being asked when they apply for vehicle licences to state whether their vehicle is fitted with a radio set and, if so, whether it has been licensed separately. A radio set which is installed in a car must have a separate licence, but a portable radio does not.

Car radios are now being sold in much larger quantities than before the war, but rectifier troubles are still common, and thefts of car radios are on the increase.—F.J.C.

ROUND the WORLD of WIRELESS

Atomic Energy Broadcast

IN the atomic city of Oak Ridge, Tennessee, U.S., WATO have been arranging to broadcast a programme on electricity generated from the atomic power station.

The trial transmission is expected to last no more than five minutes and, if successful, would be the first radio station in the world to broadcast on atomic energy.

Fight Broadcast

WE understand that a direct link-up has been arranged between the BBC and the razor-blade company that holds the copyright in New York on all broadcasts from Madison Square Gardens.

The link-up is to enable British listeners to hear the world middle-weight championship fight on October 21st between Randolph Turpin and Carl Olson. Those who do hear the relay will have to stay up until 3.30 in the morning by our time.

Contract for E.M.I.

RECENT orders from the BBC for E.M.I. tape recorders and associated equipment exceed £100,000.

This is part of a re-equipping scheme which the BBC have in hand for their recording department. The models supplied range from large studio recorders, including transportable versions, to the latest type lightweight portable battery-operated recorders now in use by BBC outside commentators. Over 50 of these portable machines have already been supplied.

Tannoy Director Marries

MR. DAVID G. FOUNTAIN, younger son of the noted West Norwood industrialist, Guy R. Fountain, and director of one of the Tannoy group of companies, was married recently to Frances Mary Smith, an occupational therapist, whose father farms The Grange, Elmbridge, near Droitwich, and is also a keen aviator.

Mr. David Fountain, an old Alleynian, who is 23 years old, has now completed his second year at Oxford, and when he comes down from the university, contemplates staying for a few years in Canada.

The wedding took place at Elmbridge Parish Church.

Broadcast Receiving Licences

THE following statement shows the approximate number of sound receiving licences issued during the year ended July, 1953. The grand total of sound and television licences was 13,010,856.

Region	Number
London Postal	... 1,714,093
Home Counties	... 1,459,147
Midland	... 1,309,810
North Eastern	... 1,698,763
North Western	... 1,334,452
South Western	... 1,026,212
Wales and Border	... 664,692
Total England and Wales	... 9,207,169
Scotland	... 1,110,857
Northern Ireland	... 213,376
Grand Total	... 10,531,402

Cable and Wireless Ltd.

New Radio-telephone Service


A DIRECT radio-telephone service was opened on Tuesday, August 18, between Nairobi and Bombay.

It is operated between Cable and Wireless Ltd.'s station at Nairobi and the Overseas Telecommunications Service's station at Bombay. The service will be available to telephone subscribers throughout Kenya, Tanganyika and Uganda at one end, and throughout India at the other end.

"Prix Italia"

THE festival for the award of the "Prix Italia," the grand international competition for original broadcasting works, began at Palermo on October 1st. This is the fifth consecutive year of the festival.

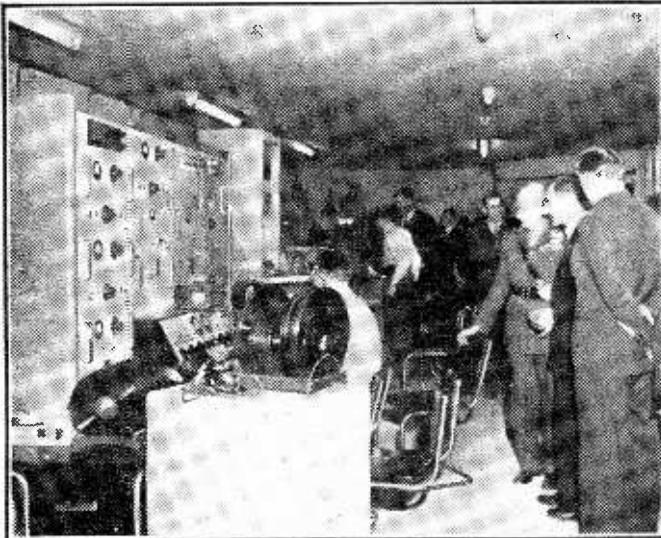Fourteen of the most important broadcasting Corporations of the world participated. They were in



During his visit to this year's Radio Show, Field Marshal Viscount Montgomery in the Radio Industry Council Control Room, examined the Sound Reproduction Equipment designed, manufactured, installed and operated by Standard Telephones and Cables, Limited on behalf of the R.I.C.

order of entry: Ravag (Austria), Radiodiffusion Egyptienne (Egypt), Radiodiffusion et Télévision Françaises (France), BBC (England), RAI-Radio Italiana (Italy), Radio Montecarlo (Monaco), Nederlandsche Radio Unie (Holland), Emissora Nacional de Radiodiffusao (Portugal), Société Suisse de Radiodiffusion (Switzerland), Ente Radio Trieste, Institut National Belge de Radiodiffusion (Belgium), Suddeutscher Rundfunk (Germany), Naeb (U.S.A.), Radio Maroc (Morocco).

Miniature Radio

IT is reported that the American Army authorities have developed a miniature transmitter-receiver radio no larger than a normal wristwatch.

Sets for Bolivia

PYE, LTD., of Cambridge, report that they have received a "substantial order," amounting to several thousand pounds' worth, from Bolivia for a consignment of radio receivers.

Show Boosts Sales


THE Manchester firm of Ferranti received so many orders for radio and television receivers during the first week of the National Radio Show that employees at the company's Moston factory have been guaranteed work for at least a year.

Production has been so completely outpaced by exhibition orders that some prospective buyers have been warned that delivery may be considerably delayed. Sales manager Mr. L. G. Hall reports "Business is terrific. Orders are pouring in."

Pye Records

MR. C. O. STANLEY, chairman of Pye, Ltd., stated at the recent annual meeting that the company intends to enter the gramophone record business.

He said that TV development in the United States had furthered interest in records and predicted that the same would happen in this country. "For a number of years," he said, "your company has wished to have an interest in the gramophone record business. We are at this moment actively planning to enter this new field of manufacture and selling, and we hope to be able to make a definite announcement in the very near future."

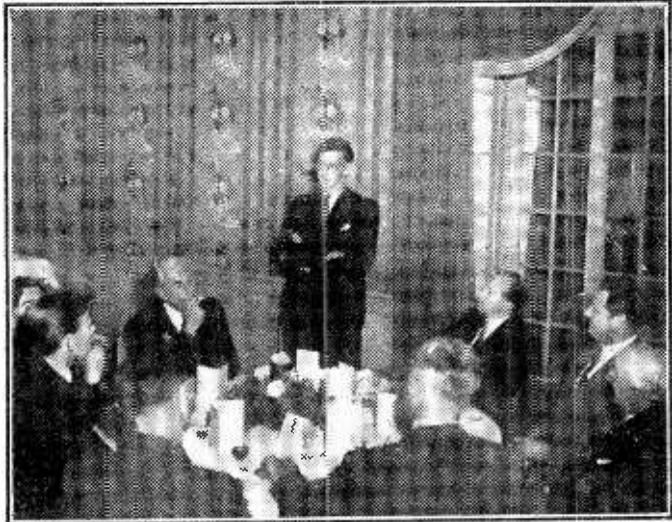

Radio Officer of the Everest expedition, George Band, relates his experiences at a Savoy luncheon, given by Pye, Limited, who announced details of a new naval radio receiver, the 619 Admiralty set. Seated on the right of Mr. Band is Captain K. McCampbell-Walter, R.N., the Director of Radio Equipment at the Admiralty. On Mr. Band's left is Mr. P. M. Threlfall, a director of Pye, Ltd.

"Take It From Here"

ALTHOUGH one of radio's biggest laughter shows, "Take It From Here," is planned to return to the Light programme in November for a run of six months, it is not definite yet whether a successor to Joy Nicholls will be introduced.

Miss Nicholls returned to her home in Australia some months ago and producer Charles Maxwell and scriptwriters Frank Muir and Denis Norden are not sure whether one or two girls will be chosen to provide a feminine touch to the programme. It is believed that they may even introduce a different

sort of girl that would change the shape of the series considerably.

Boxing Night

THE agreement recently concluded between the BBC and the British Boxing Board of Control will enable the big audience for boxing commentaries to hear regular fortnightly broadcasts in the Light Programme.

Beginning on October 13, there will be a forty-five minute Boxing commentary at 8.30 p.m. every other Tuesday until the end of the year. To allow for this, the Forces Show will be moved from 8 p.m. on Tuesdays to 7.30 p.m. on Wednesdays. The period from 8.0-8.30 p.m. on Tuesdays will be filled with a programme of light music. "The Name's the Same" will move from 7.30 p.m. to 9.30 p.m. and its place will be taken by "Ignorance is Bliss."

Autumn Drama

THE BBC state that radio drama this autumn will include "a strong and unusually varied selection of plays, the current output being augmented by the return of "Radio Theatre" and "Curtain Up"; an additional fifteen-minute serial on Saturday evenings, which it is hoped will appeal to the younger generation and, in the Home Service, a new serial on Thursday evenings."

BIRTHDAY GREETINGS

From Harry Richards (Managing Director, Wolf Electric Tools Ltd.).



"CONGRATULATIONS TO PRACTICAL WIRELESS on reaching its 21st Birthday, and to Mr. F. J. Camm on seeing it through to this day. May they both still be going strong at the 50th anniversary."



The Beginner's Guide to RADIO

The Seventh of a Series of Articles Specially
Written for Those Who Have Become
Interested in Radio for the First Time.
Explaining the Principles of Radio
Transmission and Reception

By F. J. CAMM

FIRSTLY, let me deal with one or two points arising out of last month's instalment. I said that it sometimes becomes necessary to increase the ranges of voltmeters and ammeters by the inclusion of resistances. I did not make it clear that in the case of a voltmeter the resistance is connected in *series* and in the case of an ammeter in *parallel*. Also a typing error occurred in the paragraph on page 601 relating to "Increasing Range." The sentence commencing "As already stated the voltage range of *ammeter* . . ." should read "As already stated the voltage range of a *meter* . . ."

In order to dispel some doubts which exist in the minds of beginners concerning the functions of meters, I should point out that basically a voltmeter is the same as an ammeter, and thus it does in effect indicate that a current is flowing through the circuit, although by reference to the dial one reads off the voltage.

Current, Voltage and Resistance

I have already shown that current, voltage and resistance have a definite relation to one another, the relationship being known as Ohm's Law, and in any circuit knowledge of any two factors enables the other to be calculated. Now if a circuit is "opened" and an ammeter is inserted the needle will indicate the amount of current flowing. For example, if the meter is designed for a maximum reading of 1 mA and it is inserted in a circuit so designed that one milliamp current flows, it is obvious that the needle will be fully deflected. This is known as *full scale deflection* or *f.s.d.* But if the voltage is higher or the resistance lower than a current greater than 1 mA will flow, and unless precautions are taken the needle will press hard against the stop pin and the meter mechanism will be damaged. In cases where we wish to take current readings beyond the full scale reading of the meter, we must arrange to by-pass the current which is in excess of that which will give F.S.D. of the meter.

When measuring a voltage the voltmeter is connected across the source or terminals to which the voltage is applied, and in this case if the voltage being measured will result in a current in excess of the full scale reading of the meter resistances will have to be connected in *series* with the meter, and the two are joined in *parallel* with the source. The values of the resistances are such as to limit the current again to 1 mA or less with the type of instrument just referred to. A parallel shunt direct across the meter would not function satisfactorily in this case as it would have

to be practically a dead short-circuit, especially when measuring high values of voltage. Summed up, therefore, whether used for measuring current, resistance or voltage, we do, in effect, actually measure the current flowing through the circuit; and the basis of the ohmmeter or voltmeter is an ammeter. If the current to be measured is in excess of that for which the meter is designed the excess must be by-passed by a shunt-resistance; whilst if a voltage is applied which will result in excess current being passed through the meter the current is restricted by the use of resistance(s) in series with the meter.

I hope I have removed the confusion which has existed in the minds of one or two readers on this matter.

A Practical Test in Measuring

Now, last month I dealt with general testing and we can now proceed with a practical demonstration of these methods by testing the three-valve circuit which has already been described in this series.

The illustration on the next page shows the receiver in pictorial form, but with two meters added. These may be a single instrument in which by means of switches or plugs and sockets the instrument may be made to measure voltage or current. As explained already, voltages may be measured without interrupting the circuit whilst for current readings the circuit must be broken and the meter interposed.

First, then, the meter shown at the foot of the diagram is the voltmeter. The polarity of the leads must be observed, and the negative lead is clipped on to any point on the earth (H.T.—) side of the receiver. The positive lead may then be placed on the points indicated by a X, making quite sure that the setting of the instrument is suitable for the voltage being measured. To obtain the highest accuracy the meter should be set to the highest voltage range. The readings will indicate the voltages actually applied to the valves and thus prove whether the anode circuit is complete or short-circuited, and also the state of the bias circuit where one is fitted. This form of testing may be employed with any receiver.

"A" gives the L.T. voltage which should be checked with the valves switched on.

Next the current may be tested and the meter for this is shown at the top of the diagram. Here the two leads have to be interposed as already stated and to check each stage the circuit must be broken where the broken X is shown and, again, the polarity of the instrument must be observed. The negative

lead should be connected to the valve side of the opened connection. It will be noted that the H.T. lead has been provided with a broken X and if this lead is opened and the meter is inserted it will indicate the total H.T. current taken by the receiver and when the set is switched off it will indicate whether or not there is any leakage. There should be no reading in the "Off" position. Similarly, by adding together the current shown at each stage this should agree with the total in the negative lead—any higher reading indicating a leakage or some additional point which has not been taken into account.

Testing Without Instruments

Certain simple tests can be carried out without the use of instruments. In the case of a simple battery receiver, it may be tested without any instruments in the following manner. Assume that the L.T., H.T. and G.B. batteries are in order. Disconnect the wire which is joined to the detector-valve anode or plate terminal of the valveholder. Connect up one lead of a pair of headphones to the terminal and take the other lead straight to H.T. positive. Switch on the set and see if signals come through. If there are no signals tap the glass bulb of the valve lightly with the tip of your finger. If no noise is heard the valve is broken. To ascertain this simply remove the valve and plug one of the other valves from the set in its place. Supposing that no matter which valve you plug in you can still hear nothing. Remove the wires which are connected to the F terminals of the valveholder and obtain two new pieces of wire and attach them to the "F" terminals

and straight on to the accumulator. If the valve now works, then the filament wiring in the set or the leads from the terminal strip down to the accumulator are at fault.

With all leads of the flexible variety having clamped-on spade connectors or similar devices, it often happens that the wire gets broken, but the connector is held in position by the cotton covering.

Now that leads have been checked over and found correct, there only remain the connections from the L.T. terminals on the set to the valveholder and the terminals on the valveholder itself.

Supposing when joining an accumulator direct to the valveholder nothing is heard in the phones. The only lead left which can cause this trouble is the H.T. negative lead and if this is joined to the set to one side of the fuse only, look at the fuse. If this is in order, remove the H.T. negative lead from the terminal strip and join it to the L.T. negative terminal.

Now take the case where on connecting the phones no signals can be heard, but the valve "pings" on tapping it. This shows that filament and anode circuits are correct and the trouble must lie in the tuning arrangements. Try a different coil, or, if some complicated switching arrangement is used in the set, wind or obtain a simple 60-turn coil and connect one side of it to aerial and one side to earth. Disconnect the aerial terminal to the tuning coil and also the lead from the tuning coil and/or condenser to the grid condenser. Join the aerial terminal to the grid condenser and again observe whether signals come in. If they do, then the tuning coil is at fault. *(To be continued)*


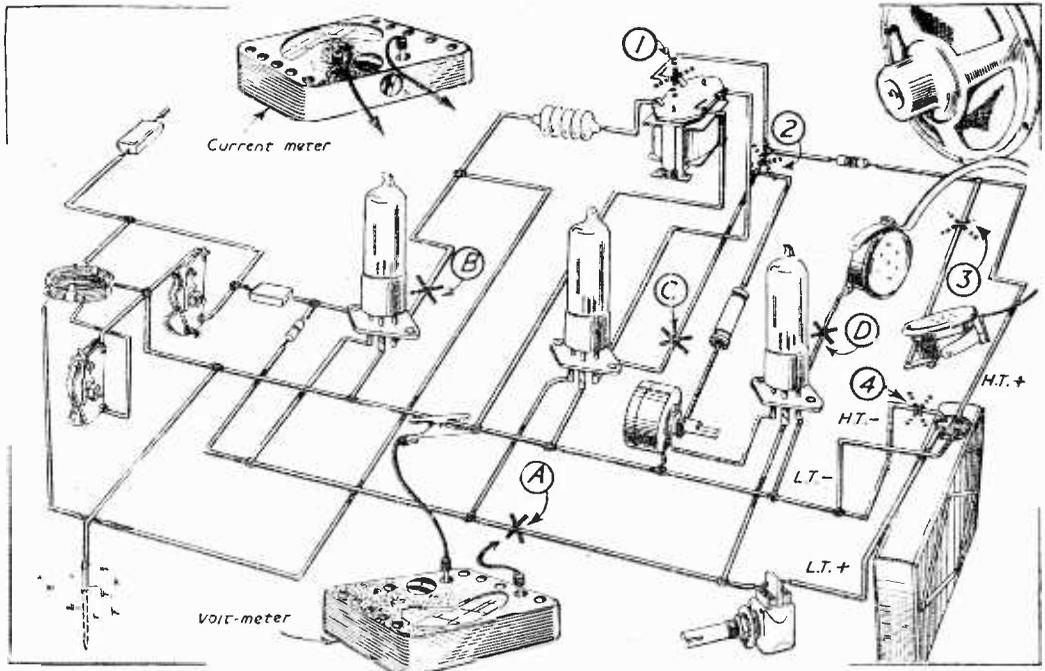


Fig. 31—The three-valve receiver circuit in pictorial form showing the points to which meters are joined for testing.

SHORT-WAVE SECTION

A MODULATION CONTROLLED 27 Mc/s RECEIVER

By F. G. Rayer

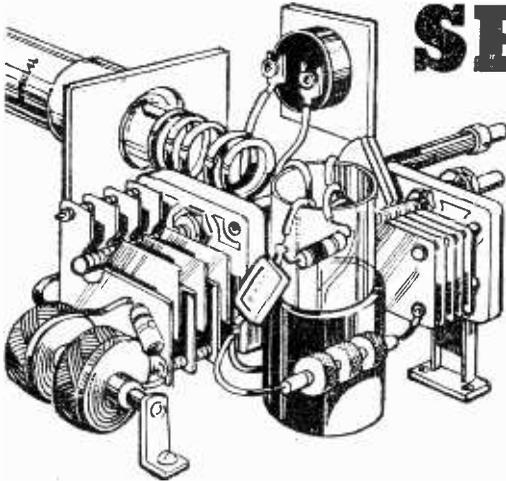

THE usual type of simple single-valve model-control receiver is not suitable for use with a transmitter where control is effected by modulating the transmitter carrier-wave. With a modulation controlled receiver, a number of advantages are present. The most important of these is to be found in the increased degree of control which is possible, and two or three relay circuits may readily be operated with a single transmitter and receiver. This is not so with "carrier only" receivers, where a single relay is controlled by switching on and off the transmitter carrier-wave.

A 2-valve receiver circuit is shown in Fig. 1 and this may be operated in a number of ways. The first valve is used in a self-quenching super-regenerative stage, the 50,000 ohm control enabling the degree of regeneration to be adjusted. High sensitivity is possible with a stage of this type, quenching being achieved by the development of a negative potential on the control grid. As a result, the valve goes in and out of oscillation at a frequency above audibility, in the manner which will be familiar to users of ultra-short wave equipment of this kind.

When the control of a single relay is wanted, the second valve has just sufficient bias applied to it to prevent anode current flowing, when no audio-tone is being received. When the transmitter carrier is modulated, the audio-tone is applied to the control grid of the second valve, which conducts during the section of each cycle when the grid is sufficiently positive. The resultant anode current closes the relay.

"Hard" or vacuum valves may be employed in such circuits, and have a normally long life, which is a great advantage over the use of "soft," or gas-filled, valves, where the valve may have a life of only 15 to 20 hours, yet is essential to secure an adequate change of anode current at range. Using the circuit in Fig. 1, with a 1S4 valve as detector and IT4 valve in the second position, adequate control of the relay was found possible. With about 6v. bias the IT4 valve anode current was .1 mA (insufficient to operate the


relay), rising to 1.5 mA when the carrier was modulated.

Correct quenching is essential for proper operation, as weak regeneration will cause lack of sensitivity, while violent oscillation will cause V2 to conduct during positive peaks. A quench frequency in the neighbourhood of 10,000 cycles per second is suitable, and phones may be included in the anode circuit of the second valve to check operation. If the quench frequency tends to reach V2, causing anode current to flow, this can be prevented by shunting a fixed condenser across the secondary of the coupling transformer.

This type of circuit can also be used with a tuned reed relay. This type of relay usually has three reeds or armatures, each of which is tuned mechanically to operate at a certain frequency. Accordingly, any of the reeds can be made to operate by adjusting the audio-tone radiated by the transmitter to a suitable frequency. In this case V2 only needs to operate as an ordinary amplifier, and excessive bias is not applied.

3-Valve Circuit

Fig. 2 is a development of the circuit in Fig. 1 giving increased range, and a suitable layout is shown in Fig. 3. Here, the audio signal is developed across

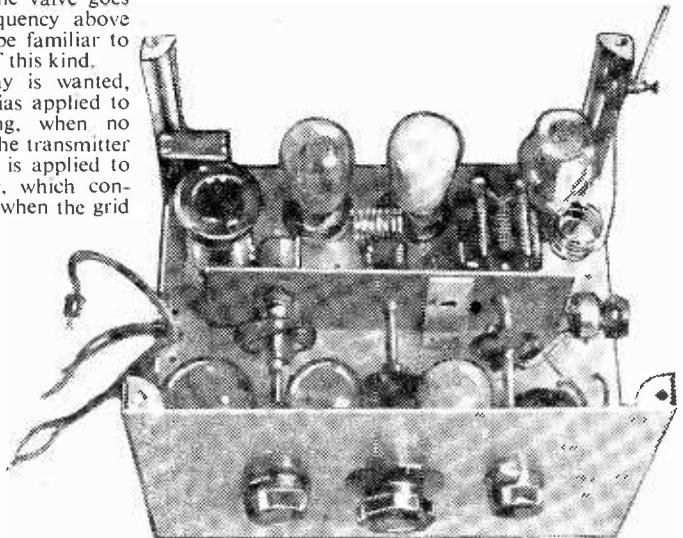

View of the Transmitter which was described last month.

the L.F. choke, and applied to the grid of V3. The control bias voltage arising in this way was found to be from about 15v. down, according to range.

With relays of other than the tuned reed type it is desirable to shunt the relay winding, as in Fig. 2, with a condenser of about .1 μ F upwards, to prevent the armature responding to the audio tone, or "singing." The selection of a specific audio-tone may be achieved by using a L.F. choke of suitable inductance, so that it is resonant at the desired frequency. The circuit will then be unresponsive to tones of other frequencies which may be radiated to control other equipment. If the control of two or more relays of this type is required, the output stage should be duplicated, each valve being wired to a choke of different resonant frequency. The

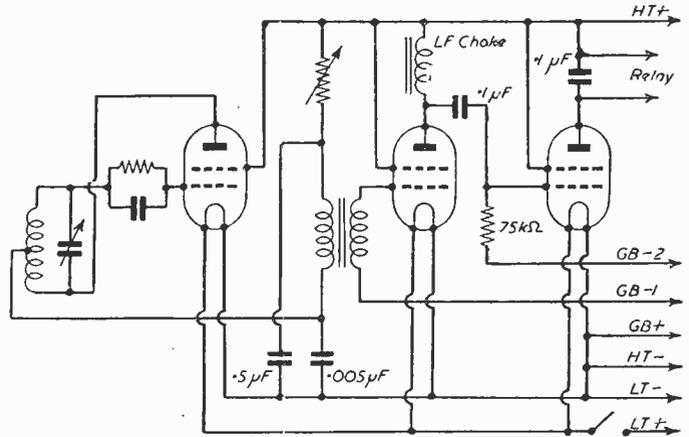


Fig. 2.—A three-valve circuit.

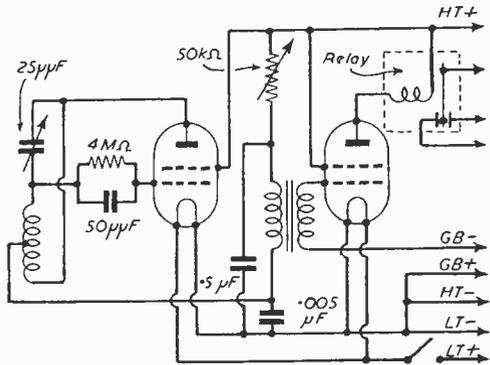


Fig. 1.—Circuit of a two-valve modulation controlled receiver.

various relays may then be controlled as desired by adjusting the frequency of the radiated audio-tone.

This 3-valve circuit can be used with a tuned reed relay, when ordinary bias is applied to V3. When used with the ordinary type of relay, sufficient bias is used to obtain cut-off of anode current, as explained.

Practical Considerations

As mentioned, correct operation of the super-regenerative detector is essential for best results, and it is of great advantage to wire phones temporarily in circuit when initially setting up the receiver.


Details of the coil used will become apparent from Fig. 4, the completed coil being mounted directly above the butterfly tuning condenser in Fig. 3. Here, "A" on the coil is taken to the left-hand section of the condenser, and detector anode.

The tapping (at the 4th turn) is taken to the condenser and transformer primary, while end "B" goes to the grid-leak and condenser.

The IS4 valve type, being intended for output purposes, oscillates most readily in this type of circuit. If a IT4 is used for detector it may be necessary to move the coil tapping nearer to the centre of the coil to obtain oscillation, and to wire anode and S.G. together to use the valve as a triode.

With the transmitter radiating a modulated carrier wave, the receiver tuning and regeneration control should be carefully adjusted for maximum volume in the phones. If the tuning condenser is fully closed without resonance being obtained, the coil may be slightly compressed. If, however, the condenser is fully opened without correct tuning being obtained, the coil should be pulled out slightly to reduce inductance.

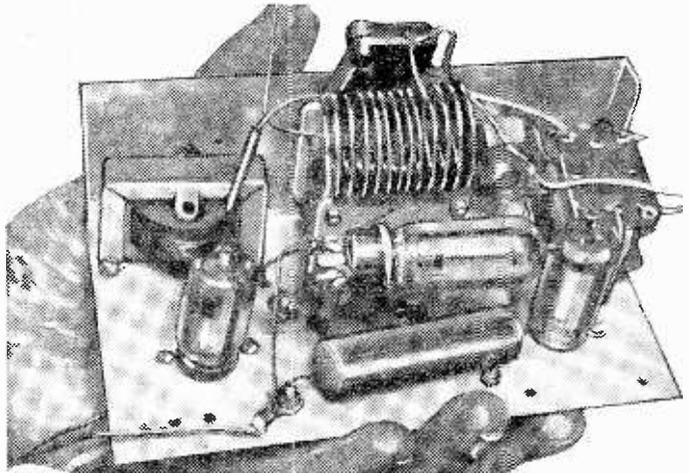When it has been assured that the correct frequency is tunable, the receiver may be removed to a distance of 50 to 100 yds., and regeneration care-



The size of the receiver may be judged from this illustration.

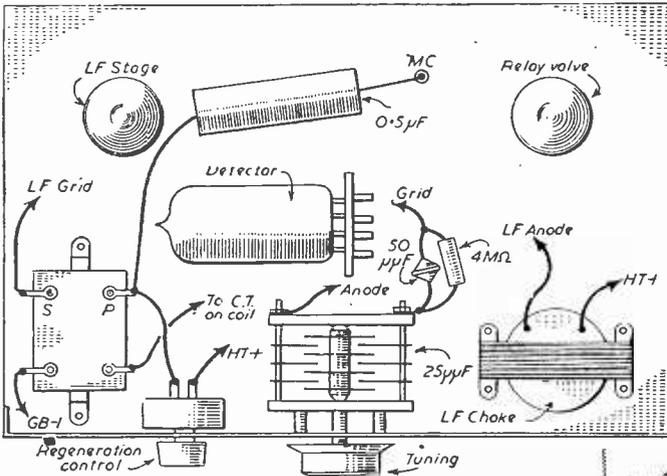


Fig. 3.—Layout adopted in the receiver.

fully adjusted to obtain maximum volume. With the phones wired in parallel with the primary of the coupling transformer, so that only one valve is in use, the transmitter note should be clearly audible at 100 yds. range.

When correct operation has been obtained, the phones should be removed. This may make necessary some slight retuning and adjustment of the regeneration control. Final adjustments should be made by including a meter in the anode circuit of the relay valve, and obtaining the greatest possible change in anode current when the transmitter modulator is switched on and off. The relay is then adjusted to operate in the usual way.


Receiver Aerial

For experimental purposes where transmitter and receiver are close together, no aerial need be used on the receiver. For small ranges an aerial about

9 to 18in. long may be joined to the tuning coil. A stiff vertical wire is suitable. For maximum range a longer aerial should be used, and this may best be coupled by a two or three turn loop near the tuning coil. The free end of this loop is taken to the receiver chassis.

Regeneration

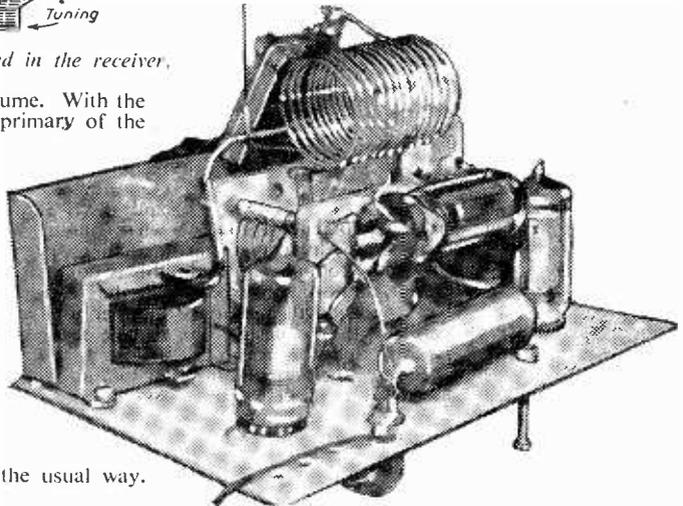It is most convenient to adopt one or two aerials and retain them, since any change to the aerial makes necessary retuning and adjustment of the regeneration control. Long aerials, tightly coupled, will prevent super-regeneration. For normal purposes there is little need to use an aerial exceeding 3ft. in length.



Another view of the completed receiver.

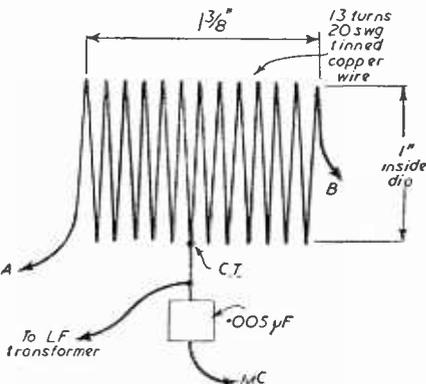


Fig. 4.—Details of the tuning coil.

SOLVE YOUR CHRISTMAS GIFT PROBLEMS THIS EASY AND EFFECTIVE WAY


The choice of Christmas Gifts for friends and relations is always a difficult business. Why not solve the problem this year in a novel, yet practical way?

Look now at your Christmas list and you will see at once more than one relative or friend who would be delighted to receive *PRACTICAL WIRELESS* regularly. It is simple to arrange for we can send subscriptions to any address, at home or abroad, at the annual rate of 13s. 6d. (Canada 13s.).

An attractive Greetings Card will be sent in your name with the first Gift Copy.

Just write to the Subscription Manager (Dept. G.1), *PRACTICAL WIRELESS*, Tower House, Southampton Street, Strand, London, W.C.2, enclosing the names and addresses of your friends, with remittance to cover, and we will do the rest. Remember, a Christmas Subscription for *PRACTICAL WIRELESS* is a Gift which will give pleasure and act as a reminder of your good wishes the whole year through.

AN Economy QUALITY AMPLIFIER

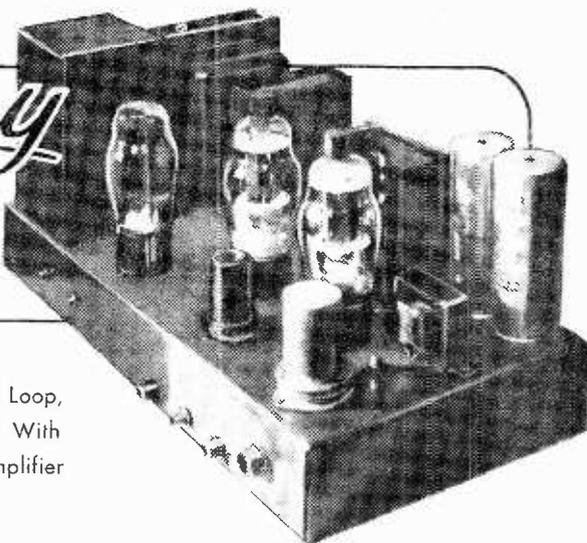

A High Gain, Low Cost, Four Feedback Loop, Main Amplifier. 6/8 Watts Output With Negative Feedback Tone Control Preamplifier

By C. J. White, Assoc. Brit. I.R.E.

IN putting forward a new amplifier for the constructor, a designer has to first consider on what grounds this can be done and then to work out the performance to be expected from the considerations involved.

There are many commercial equipments available having a performance equal to anything that the amateur can produce, but both commercial and amateur face the same end result, they are very expensive. Now why is this? Leaving aside all questions of labour charges and dealing with the design on technical grounds alone, generally speaking it can be said to revolve around the design of the output transformer and the type of output valves used, together with the degree of negative feedback in the main loop. Taking the output transformer and feedback first, it can be seen that the more feedback that is used in order to reduce distortion, the more need for an expensive output transformer to keep down phase changes at the extreme ends of the audio frequency spectrum. If the number of stages in the normal main amplifier is reduced so that, say, a figure of 25db can be fed back; whereas with another stage 25db is sufficient to cause instability, one is faced with another problem, that of securing enough output from the tone-control pre-amplifier, without distortion, to feed the main amplifier fully.

In trying to defeat this vicious circle, the writer feels there are one or two weapons in our armoury which have tended to be ignored, at least in commercial designs, and only partly in designs for amateur use and that is the complete matching of the anode currents of the output valves and the use of a directly-coupled pentode, followed by the phase splitter. Even when an expensive output transformer with high-quality iron and a large cross-section is used, all this goes for very little when the time comes

for a valve to be replaced, at which the anode currents can quite easily differ by 20 to 30 mA. There have been designs where matching has been recommended and provision made, but it is never made easy; what is required is that there should be provision for matching, plus an easy method of checking; if this is done then the iron content of the transformer can be reduced together with the price. There is another way in which the transformer requirements can be reduced, if by some means we can decrease the need for the numerous interleaving or separations of the windings. Now the reason for this separation of the windings is that it is necessary to reduce their self capacity in order to extend the frequency response and additionally when feedback is used to avoid or retard the changeover to positive feedback which occurs when the feedback is over a number of stages. In a nutshell if we can reduce the number of stages, then for the same feedback we can reduce the transformer requirements, for the feedback will easily take care of the slight droop in the frequency characteristic which would result if the transformer were used without feedback.

So far then the problem is to design a very high-gain minimum stage amplifier with a high degree of negative feedback. Now, it is well known that the maximum possible voltage gain of a

pentode is never reached in practice because of the inability to provide an anode load in which this gain can be developed, but there is a way in which gains of up to 1,000 times can be achieved, and using this method we can obtain our desired result. Before going on to describe this high-gain system it would be best to consider what sort of an output stage we are going to require, for whatever it is the early stages have to provide the

TEST FIGURES

Input 0.4 R.M.S. v. at 1,000 c/s per 6 watts output across 15 ohms.

Hum level 90db down (50 c/s and 100 c/s in proportion of approximately 3-2).

Distortion measured on a wave analyser: at 1,000 c/s—no detectable harmonic content; at 50 c/s less than .05 per cent. For 6 W. at 1,000 c/s distortion .27 per cent. (R.M.S. value of harmonic components).

grid volts to drive it and it is no use having a high-gain input stage if it will not provide this voltage without distortion. Push-pull is a *sine qua non* for only in push-pull can saturation of the output transformer be avoided, but the question of how many watts is a very vexed question.

There are many valves available which will easily cover this output, but as this amplifier is to be an attempt to give a high-quality output at low cost, there is one which is very reasonably priced, very reliable and easily available, which will fit the case much better than the others, and that is the 12-volt equivalent of the 807, i.e., the 1625. To get our requisite 6.8 watts this valve will require a grid swing of approximately 33 volts, with an anode volts of 400. This in turn requires an H.T. line volts of approximately 450, which is just what we require for the first stage. Additionally, the current requirements of this valve are quite reasonable, for at the maximum usable output of 11 watts, using the bias arrangement adopted, the total current was 100 mA., which is very reasonable indeed. Assuming a maximum grid swing of 40 volts, i.e., a grid-to-grid volts of approximately 80, we can now go back to consider the first stage in more detail.

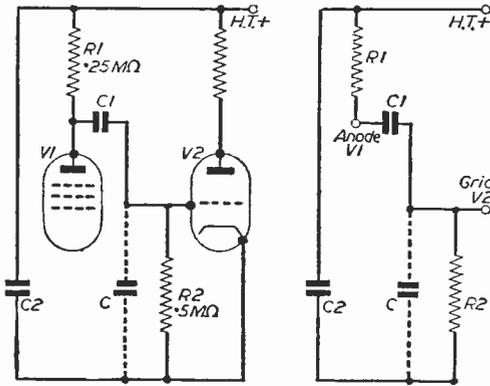


Fig. 1.—It can be seen that R2 forms part of a potentiometer R1 C1 which reduces the potential available at the grid of V2. Additionally at low frequencies the rising reactance of C1 and at high frequencies the stray capacitor C increases the loss.

First Stage

In the normal amplifier, with a pentode followed by another amplifying valve, any attempt to get high gain, say above 200 times, by increasing the anode load is doomed to failure because of the load presented by the grid cathode impedance of the following stage. (Fig. 1). This, then, is the crux of the matter, how to increase the grid/cathode impedance of the following stage. Now, in the amplifier under discussion this following stage will have to be the phase splitter, for one of the requirements is to keep the number of stages to the very minimum, and here in the phase splitter is the solution to the problem. One straightforward reliable phase splitter is known as the concertina (Fig. 2), where the anode load is split in two, with one half in the anode circuit and the other placed in the cathode circuit. Now, because of the feedback across the cathode load the grid/cathode impedance is approximately 10 times the value of the grid leak. Putting a value of 500 KΩ for this, we get a figure of 5 megohms, which is comparatively negligible compared with, say, 100 KΩ, a not unusual figure, particularly if grid current is permitted. It is possible to rearrange this circuit, combining with it

Wattage Output

On technical grounds alone there is a very good case to be made out for a 15-watts output, but there is more to consider than technical grounds. If such an amplifier is to be used with a modern loudspeaker system so that on dance bands and symphony concerts loud passages cause the amplifier to reach its maximum, or even if the general level is much lower than this and the bass tone control is used to compensate for the ear's loudness contour, the general result is that it can be heard some 20 yards away, which is much to be deplored. Looking at the problem in this light it is suggested that an output of 6.8 watts would be ample with the corresponding advantage that the H.T. requirements would be very much reduced.

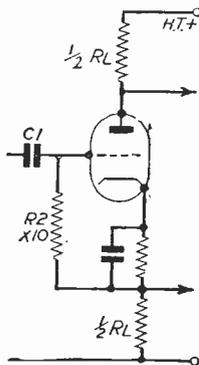


Fig. 2.—The "concertina" phase splitter circuit.

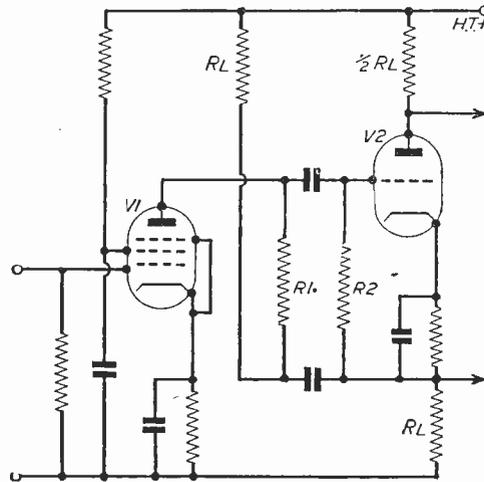


Fig. 3.—A rearrangement of the Fig. 2. circuit to combine the first stage.

the first stage whereby the grid/cathode impedance of V2 is actually the anode load of V1. (Fig. 3). In this way

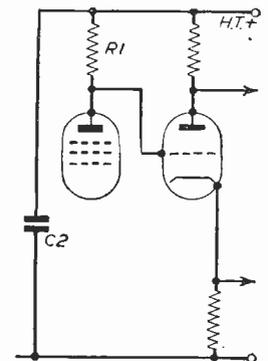


Fig. 4.—The coupling condenser has been eliminated here.

truly colossal gains can be obtained, particularly with modern valves, and a figure of 1,500 could be considered as average. For the purposes of this amplifier, however, this circuit has the disadvantage of containing two coupling condensers. We would be quite content with a gain of approximately 500, particularly if the coupling condensers can be avoided, and this it is possible to do with the circuit of Fig. 4. Here the only limit to the gain of the stage is the value of the anode resistor now that the loading of the following stage has been removed, with the added requirement that it must supply the 36 to 36 volts or so (that is Eg. 3.-Eg. 4), when combined with and multiplied by 0.9 (the gain of the phase splitter), required by the output valves.

One of the limitations of this type of circuitry was that as the anode load resistor was increased so the Miller effect and grid/cathode capacity of the following stage caused a serious droop in the high-frequency response, but in this case not only will this not be so but to ensure complete stability with long loud-speaker lines and the use of networks the capacity will be added to without the frequency response deteriorating.

Final Circuit

Assuming the foregoing to be possible, it can now be seen that our Economy Quality Amplifier should consist of one very high-gain pentode, directly coupled to the phase splitter, which, in turn, is fed to two 1625 valves in push-pull, using an output transformer that, though designed with a view to economy, is able to allow a feedback of more than 20db over the whole of the amplifier from the cathode of V1 to the loud-speaker with complete stability. Using an EF54 for V1, a 6L5 for V2, and the 1625/807 valves for the output stages, a prototype was made up for the preparatory work.

In this work the major aim was that it should be capable of being reproduced by constructors without any test equipment whatever. This is indeed a difficult feat, for in any attempt to get high quality it follows that close tolerance components must be used. In the early work this was so but it has been found that except for two places they can be discarded with beneficial results, and even in these two places close tolerance is not called for—only matching—and good dealers will generally be able to do this if other things are purchased. At the end of this first work the amplifier was checked by an independent, non-com-

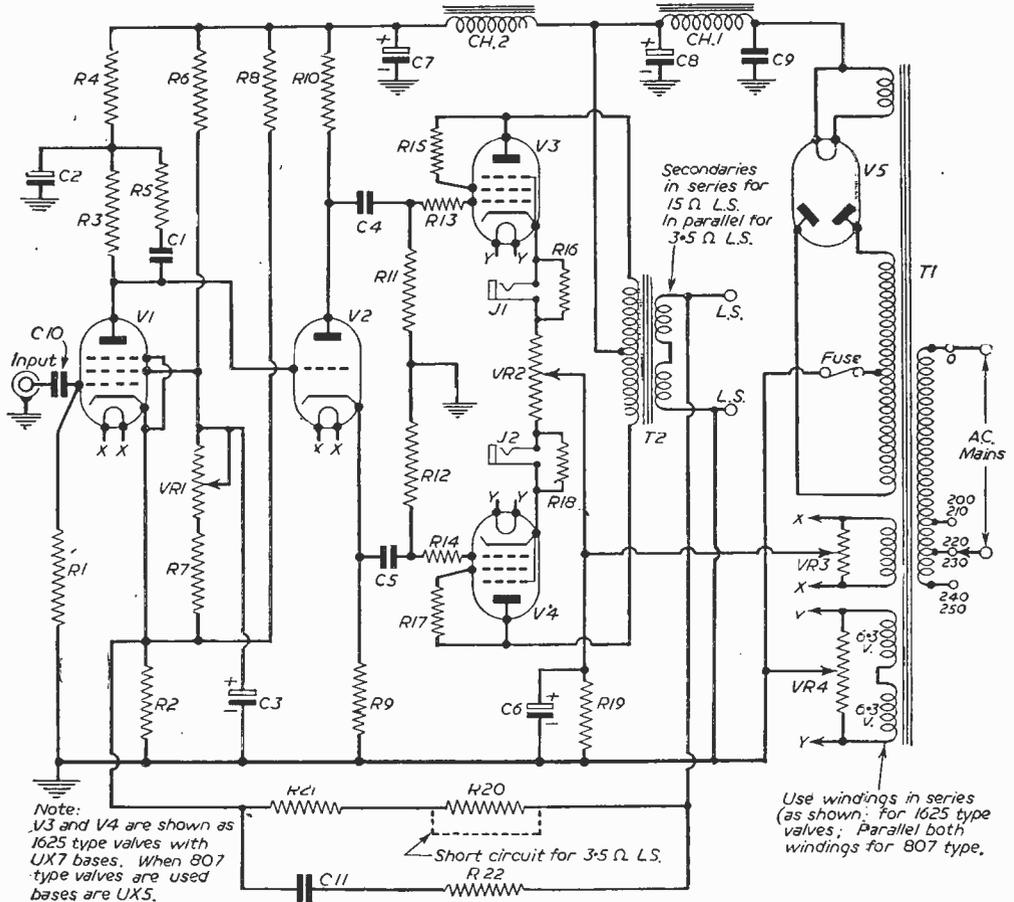


Fig. 5.—Theoretical circuit of the economy amplifier described in this article.

mercial physics laboratory, and using a reliable wave analyser the total distortion second, third and whatever there was of all the other harmonics, plus hum and noise, came out at 0.27 per cent. for six watts

across 15 ohms. This was, indeed, an excellent result, and all this was for an input of 1.1 volts RMS and a total hum and noise of 90db below 6 watts.
(To be continued)

LIST OF COMPONENTS

TRANSFORMERS AND CHOKES

- T1—Mains Transformer.
Primary 0-200/230/250
Secondary 1—425-0-425 at 150 mA. } Wholly shrouded chassis mounting with fly leads. Radio Supply Co., Leeds.
Secondary 2—5 v. at 3 amps
Secondary 3—6.3 v. at 3 amps
Secondary 4—6.3 v. at 1 amp
Secondary 5—6.3 v. at 1 amp
- T2—Output Transformer.
Primary to match 1625 valves in push-pull. Balanced secondaries of 3.5 Ω and 15 Ω L.S. } Chassis mounting with fly leads. Radio Supply Co., Leeds.
- C.H.1—Main Choke.
200 mA. 10 Henry } Chassis mounting. Radio Supply Co., Leeds.
- C.H.2—Secondary Choke.
30 mA. 5/10 Henry } Chassis mounting with fly leads. Radio Supply Co., Leeds.

VALVES

- V1—VR136—EF54.
V2—6J5 (metallised).
V3—1625/807.
V4—1625/807.
V5—5U4G.

RESISTANCES

- R1—1.0 M Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R2—150 Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R3—470 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R4—10 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R5—10 K Ω $\frac{1}{2}$ -1 watt Eric Type 9.
R6—150 K Ω 1-2 watt Eric Type 2.
R7—5 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R8—220 K Ω 1-2 watt Eric Type 2.
R9—15 K Ω 2-3 watt Eric Type 1. } Matched or \pm 5%. See text.
R10—15 K Ω 2-3 watt Eric Type 1.
R11—220 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R12—220 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R13—5 K Ω $\frac{1}{2}$ -1 watt Eric Type 9.
R14—5 K Ω $\frac{1}{2}$ -1 watt Eric Type 9.
R15—100 Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R16—15 Ω 2-5 watt W.W. Eric Silertex Type SKC2400-Y or Welwyn or equivalent } Matched or \pm 2%. See text.
R18—15 Ω 2-5 watt W.W. Eric Silertex Type SKC2400-Y or Welwyn or equivalent }
R17—100 Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R19—400 Ω 5-10 watt W.W. Eric Silertex Type SKC2400-Y or Welwyn or equivalent.
R20—1.2 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R21—1.0 K Ω $\frac{1}{2}$ -1 watt Eric Type 8.
R22—500 Ω $\frac{1}{2}$ watt Eric Type 8.
VR1—50 K. 1-2 watt Eric potentiometer. Linear preferred but not essential.
VR2—25 Ω 1-2 watt W.W. or equivalent (Humdinger type)
VR3—100 Ω 1-2 watt W.W. Humdinger } Radio Spares
VR4—100 Ω 1-2 watt W.W., Humdinger }

CAPACITORS

- C1—30 pF. T.C.C. Type SMWN or 40 SMP or equivalent \pm 5%
C2—32 μ F 450 v. wkg. electrolytic tubular insulated.
C3—8 μ F 450 v. wkg. electrolytic tubular insulated.

- C4—0.25 μ F 500-600 v. wkg. T.C.C. Type 645 or equivalent paper tubular.
C5—0.25 μ F 500-600 v. wkg. T.C.C. Type 645 or equivalent paper tubular.
C6—50 μ F 50 v. wkg. electrolytic tubular insulated.
C7—32 μ F 500 v. wkg. 600 v. surge electrolytic tubular can with insulating washer.
C8—32 μ F 500 v. wkg. 600 v. surge electrolytic tubular can with insulating washer and large solder tag T.C.C. CE15P.
C9—8 μ F 500 v. wkg. paper can type.
C10—0.1 μ F miniature T.C.C. Type 343.
C11—2500pF T.C.C. Type 701 or equivalent.

IRONMONGERY

- 1 chassis, 16in. x 8in. x 2 $\frac{1}{2}$ in. Radio Supply Co., Leeds.
1 Pye plug and socket (input), with large earth tag to fit or equivalent Belling Lec.
1 5-pin plug and socket (pre-amp power).
1 paxolin cartridge fuse holder.
1 250 mA cartridge fuse, Bulgin.
1 earth terminal with chassis insulator. Belling Lee or equivalent.
1 paxolin tag strip, 5 tag (mains).
1 paxolin tag strip, 5 tag, or Greco terminal block (H.T.).
1 4-terminal connector. Greco or equivalent (L.S.).
2 2-circuit jack sockets. Radio Supply Co., Leeds.
1 jack plug. Radio Supply Co., Leeds.
2 octal valveholders.
1 B9G valveholders with locking device.
2 UX7 valveholders for 1625 (UX5 for 807).
2 1625 anode connectors.
16 s.w.g. tinned copper wire, insulated sleeving, 3-core mains flex, 2BA, 4BA and 6BA round-head bolts and nuts, connecting wire, Multicore solder.


VOLTAGE AND CURRENT MEASUREMENTS

- Taken with 20,000 Ω per volt meter and with 230 v. A.C. to 220/230 primary tap.
H.T. across C9 = 455 v.
H.T. across C8 = 450 v.
V3 and V4 anode to H.T.— = 445 v.
V3 and V4 cathode to H.T.— = 38 v.
Balance volts across R16 and
R18 at jacks 1 and 2 = 0.75 v.
V2 anode to H.T.— = 360 v.
V2 cathode to H.T.— = 84 v.
V2 Eg/c = 9.0 v.
V1 anode to H.T.— = 75 v.
V1 screen to H.T.— = 45 v.
V1 cathode to H.T.— = 0.6 v.
Total current measured at fuse = 110 mA.

RESISTANCE OF TRANSFORMERS AND CHOKES

- Output transformer T2
Primary 50 Ω —0—50 Ω
Secondaries both in series = 0.3 Ω
Mains transformer T1
Primary 0-250 = 11 ohms.
Secondary 425-0-425 = 90 Ω —0—90 Ω
Other sees. too low to measure with ordinary ohmeters.
Choke 1 = 60 Ω
Choke 2 = 350 Ω

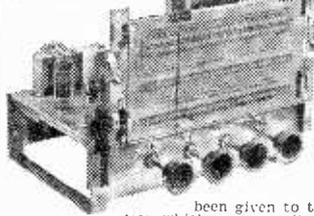A COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS



been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement chassis for that "old Radiogram," etc. Brief specifications:—Model B.3—Valve line up, 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Waveband Coverage, Short 16-50, Medium 187-550. Long 900-2,000 metres. Controls (1) Volume with on/off; (2) Tuning (Hywheel type); (3) Wave change and Gram; (4) Tone (3 position switch operative on Gram and Radio). Negative Feedback is employed over the entire audio stages. Chassis size, 11in. x 7 1/2in. x 8 1/2in. high. Dial size, 9 1/2in. x 4 1/2in. Price, complete and READY FOR USE, excluding speaker, £12 12/-. (Carr. and Pkgs. 7/6 extra.)

MODERNISE YOUR OLD RADIOGRAM FOR

£25

INCLUDING 10" P.M. SPEAKER. Plus 10/- Carriage and Insurance.

MODEL B.3. — A 5-valve 3-waveband Superhet Receiver. for operation on A.C. mains 100-120 volts and 200-250 volts, employing the very latest miniature valves. It is designed to the most modern specification, great attention having

Brand New in makers cartons, complete with mounting instructions.

• These units will auto change on all three speeds 7in., 10in., and 12in.

• They play MIXED 7in., 10in. and 12in. records.

• They have separate sapphires for L.P. and 78 r.p.m., which are moved into position by a simple switch.

• A bulk purchase enables us to offer these BRAND NEW UNITS at this exceptional price. Please include 7/6 packing, and insurance.


A GENUINE SPECIAL OFFER!

A 3-Speed Auto Change Unit by a very famous mfr.

£11. 14. 6
(Normal Price is £18 10/-)



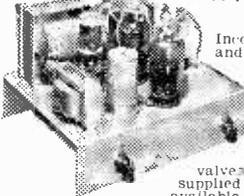A 4-VALVE QUALITY "PUSH-PULL" 6-watt AMPLIFIER for A.C. mains.



Incorporating Negative Feedback. Filter Input Circuit and employing 6V6s in Push-Pull. A simple arrangement is provided to enable either a magnetic-crystal or lightweight pick-up to be used, and is suitable for use with Standard or long-playing records. A zone control is incorporated, and the 10-watt output transformer is designed to match 2 to 15 ohm speakers. The overall size of the assembled chassis is 10in. x 8in. x 7 1/2in. high, and full practical diagrams valves, a complete kit, £8 17/6. Price of assembled chassis, supplied ready for use, £9 12/6. Full descriptive leaflets are available separately for 1/-.


"Personal Set" Battery Eliminator

A complete kit of parts to build an "All-dry" Battery Eliminator, giving approx. 60 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet receiver requiring H.T. and L.T. voltage as above or approx. to 80 volts. The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4 1/2in. x 4 1/2in. x 3 1/2in. Price of complete kit with easy-to-follow assembly instructions, 42/6. In addition we can offer a similar COMPLETE KIT to provide approx. 30 volts and 1.4 volts. Size of assembled Unit 7in. x 2 1/2in. x 1 1/2in. Price 47/6.

A COMPLETE 4 VALVE T.R.F. CHASSIS including a 5" P.M. SPEAKER and VALVES for only


£6/9/6

This receiver is of the very latest design covering both Long and Medium Wavebands, and includes the modern BVA miniature valves. The line up being 12BA6—12AT6—12A6—35W4. It incorporates Permeability Tuned Coils thus ensuring excellent selectivity and sensitivity. The overall size of the complete chassis including Speaker is 10 1/2in. x 4 1/2in. x 6in. An attractive Bakelite Ivory finished Cabinet, size 11 1/2in. x 5 1/2in. x 5 1/2in. is available for 15/6 (plus 2/6 carriage and insurance).

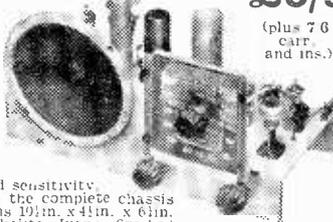

(plus 7/6 carr. and ins.)

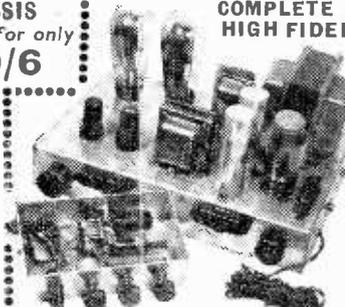COMPLETE KIT FOR 12-watt HIGH FIDELITY "Push-Pull" AMPLIFIER



Designed for A.C. mains 200 to 250 volts, employs 6 valves plus rectifier, with negative feedback, and comprises a main amplifier chassis and a remote controlled Pre-amplifier and Tone Control Unit, incorporating four controls—bass, treble, main volume or mixing control, and a radio, gram, microphone selector switch. This control unit measures only 7 x 4 x 2in. The measured frequency range of the amplifier with this unit shows an excellent response from 14,000 cycles down to 20 cycles, the bass and treble controls allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore, that ample correction is provided to suit any type of pick-up with any type of recording. Input voltage for maximum output is 70 mV, 6.3 volts at 2 amps, and 30 mA. H.T. is provided for tuning unit, etc. Price of complete kit, Amplifier and Control Unit, including drilled chassis and valves, £14. Complete specification and layout, 2/-. We can also supply completely assembled and ready for use at £12. Please add 7/6 carr. and insurance.

THIS AMPLIFIER COMPARES WELL WITH THE WILLIAMSON AND SIMILAR DESIGNS AT A FRACTION OF THE COST

A DUAL CHANNEL PRE-AMPLIFIER and TONE CONTROL UNIT

This comprehensive PRE-AMPLIFIER and TONE CONTROL UNIT provides full control of Bass and Treble in conjunction with a main Volume Mixer Control. Can be used with any Amplifier and any Pick-up the range of frequency control provided by the unit affording ample compensation for all types of Pick-up and all natures of recordings, i.e. English, American and Long-Playing, without recourse to Pick-up correction. The extreme flexibility of the Bass and Treble Controls is such that the level of Bass and Treble can be set to suit any conditions irrespective of the volume output of the Amplifier. The Unit measures only 7in. x 4in. x 2in., including self-contained Power Supply, and can be accommodated either on or away from the main Amplifier, i.e., in the front panel of a Cabinet or any other position. Price, including drilled chassis, valves (6SN7 and 6J5), £3 16/6. Complete assembly data is available separately for 1/3. Completely assembled and ready for use, £5 5/-.

Famous Manufacturer's **SHADED POLE 10/6** GRAM MOTORS (Plus 1/- carriage and Insurance). Clockwise rotaries and incorporates a Mains Adjustment Panel. Could also be used as Recording Take Up or Rewind Motor.

SPECIAL OFFER A 12in. P.M. SPEAKER (23 cm Voice Coil) by a very famous manufacturer for only 49/6 (plus 2/- carriage and Insurance) THESE ARE BRAND NEW IN MAKERS CARTONS

STERN RADIO LTD. 109 & 115, FLEET ST. E.C.4

TELEPHONE: CENTRAL 5812/3/4

RONETTE HIGH FIDELITY CRYSTAL MICROPHONES

The 'Coronation'

puts into it. You need a sensitive wide range mike with a flat response, of sturdy design and of course—trouble free. With this in mind and with an eye on your pocket, Ronette have designed the CORONATION Microphone. We proudly present this extremely low priced crystal microphone incorporating a Ronette vacuum sealed crystal cartridge with a frequency response between 30-13,000 c/s.



- *Output at 1,000 c/s 1.3 MV/ μ Bar in 5 Meg Ω .
- *Highly polished black plastic housing with long connecting cable.


- *Annealed corrosion resistive aluminium diaphragm.
- *As used in many leading tape recorders.

only 52/-
(Fully warranted)

THE MINIWEIGHT CRYSTAL PICK-UP by RONETTE is an extremely lightweight and high fidelity production at a very low price


The Miniweight Standard Pick-up with 2 interchangeable heads for 78 and L.P. 69/6 Attractively styled in lightweight Ivory plastic, this pick-up incorporates a "Finger-tip" quick release cartridge locking screw. It is one of the lightest weight pick-ups yet made giving realistic reproduction, crisp and free of flutter. This extremely high frequency response is unobtainable with any other low priced pick-up.

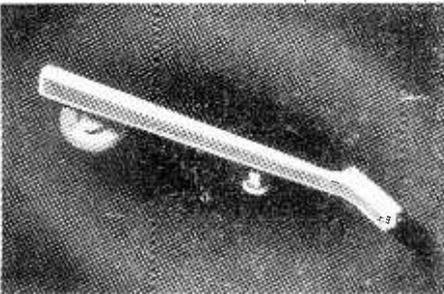MAIL ORDER SUPPLY CO., The Radio Centre, 33, Tottenham Court Road, London, W.1. MUSEum 6667



NEW! RADIO, TELEVISION AND ELECTRONICS

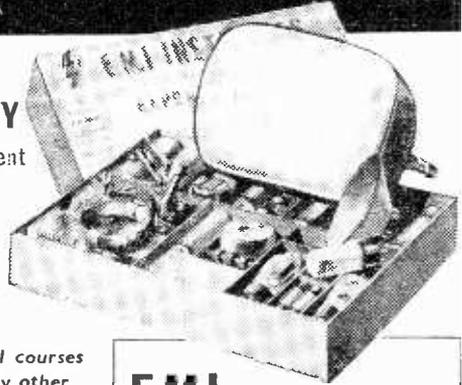LEARN THE PRACTICAL WAY
Instruction and Equipment



Here at last is the only *real* way of making home study really successful. Specially prepared equipment, which remains your property, is supplied thus combining theory and practice in the correct educational sequence. Whether your need be for career, hobby or general interest, here is the most efficient method for acquiring knowledge.

POST THIS COUPON TODAY

Please send me your FREE book on *Practical Courses*
To: E.M.I. INSTITUTES, Dept. 32X
43 Grove Park Road, Chiswick, W.4.

NAME


ADDRESS

We will not worry you with personal visits.

Practical courses in many other subjects including:
Draughtsmanship.
Carpentry. Chemistry.
Photography.
Commercial Art.

EMI INSTITUTES

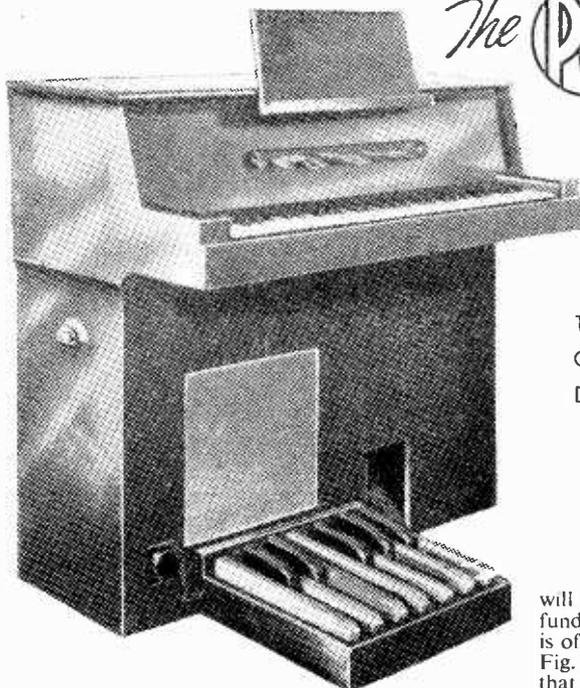the only Postal College which is part of a world-wide Industrial Organisation.




The P.W.M. FULL-COMPASS Electronic ORGAN

This Month the Main Principles of the Organ are Discussed, and Constructional Details are Given of the Mechanical Work Entailed on the Keyboard

By W. J. Delaney (G2FMY)

(Continued from page 600 October issue)

A FULL technical description of the organ would take considerable space and therefore only a brief outline of the arrangement will be given with more detailed information as each part is described. The entire scheme is outlined in block form in Fig. 1, from which it will be seen that the heart of the instrument is the note generator and frequency divider section. This is detailed separately in Fig. 2 from which it will be seen that three double triodes are used (Mullard-ECC83's), the first as the oscillator and buffer, which incidentally converts the output from the oscillator to a saw-tooth waveform, which is the form taken by the output from each of the succeeding dividers. These three double-triodes produce five outputs, each one an octave lower than the frequency fed into it, and thus one chain of three such valves is required for each note of a single octave. For this essential section of the instrument, therefore, 36 valves are needed and these are disposed in groups of nine on four separate chassis, as

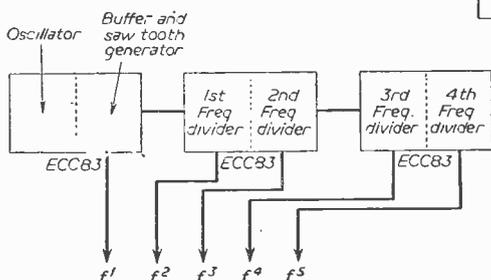

will be seen later. The oscillator which generates the fundamental note (in the top octave of the keyboard) is of the phase-shift type (phase lag), and is shown in Fig. 3, which also includes the buffer. It will be seen that the standard circuit arrangement is used with a variable resistor between the phase-shift components (R1, R2, R3, C1, C2, C3, C4) and earth. This resistor, which has a value of 5,000 ohms, permits the frequency generated by the oscillator to be varied over a fairly wide range, and the condenser C5 is added to prevent interaction between adjacent oscillators. The second half of this first valve converts the output, which is held very constant by its stabilised H.T. supply, into a saw-tooth by the charging and discharging of condenser C9, and the output is taken from the anode through a blocking condenser (C8) in the usual way. The output is also passed to the next triode which is arranged as shown in Fig. 4, which again produces a saw-tooth output at half the frequency. This arrangement is extremely

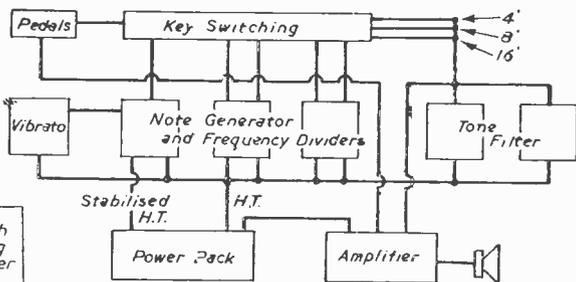


Fig. 1 (above).—Block diagram showing the essential arrangements of the design, and Fig. 2 (left) the manner in which the three double-diode triodes are employed for generating each note for five octaves. Twelve of these assemblies are used on four chassis.

simple and easy to adjust by variation of R1, and each subsequent divider is exactly the same. The arrangement was at one time used in the American Minshall-Estey organ, but has been replaced by a

there are various sources of supply for this, either the purchase of an old American organ or a visit to an organ builder who will be certain to have an old keyboard on hand. It may be of any type provided

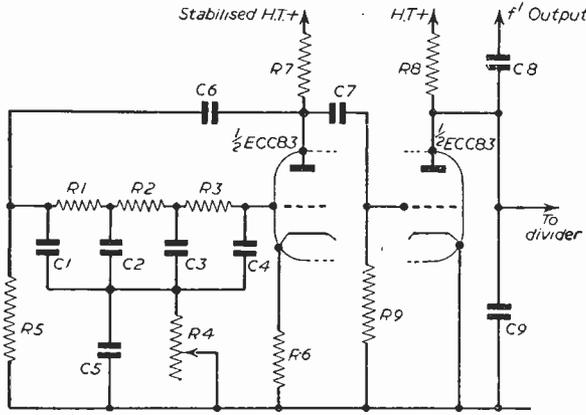


Fig. 3.—Theoretical circuit of the note generator and the buffer and saw-tooth converter. One of these is used for each of the 12 notes of the octave.

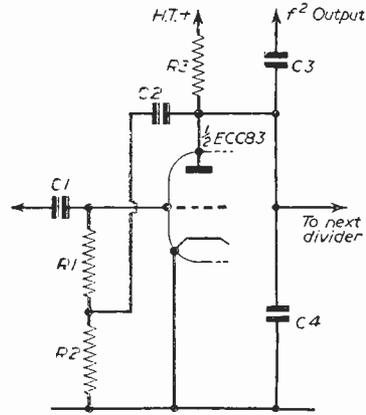


Fig. 4.—Theoretical circuit of the frequency divider. Four of these are used for each of the 12 notes of the octave, the only changes being in the values of condensers C1 and C4. Additional capacitors are used, as will be shown later, for coupling.

more effective circuit which, however, I have not found so simple for the amateur to set up. The scheme shown is very simple, has proved very stable and creates no difficulty in getting it working, and acknowledgment should here be made to the Minshall-Estey Organ company for permission to use the circuit and for assistance given in the design of this instrument.

there are 60 notes. (The top C is not used and may be ignored or cut out.) Across the top of the key-

Keyboard Distribution

It will now be seen how an output for every note of the keyboard may be obtained and all that is needed is some method of switching. In this design three notes are fed to each key (except the upper and lower octaves), the fundamental and the octave above and the octave below. This is shown in Fig. 5, from which it will be seen that the outputs are also taken to separate octave busbars, thence to main busbars and finally to the main amplifier. Decoupling and click-filtering components are included as shown. The resistors shown broken are the remaining components in the various octaves, each complete octave being decoupled.

The majority of the construction is more or less standard radio practice, and the main difficulty will be found on the mechanical side. Each key must be arranged to open three contacts at the same time so that the fundamental and the two accompanying octaves are fed out. These, in turn, may be stopped or passed as desired by the switches marked "Range Switches." Therefore, a three-way switch must be attached to each key, and the outputs from the note generator and dividers must be taken to a three-way distribution strip, and this should be the first part of the work, as it is not possible to test the instrument or carry out any lining up until it is working properly. A keyboard must be obtained and

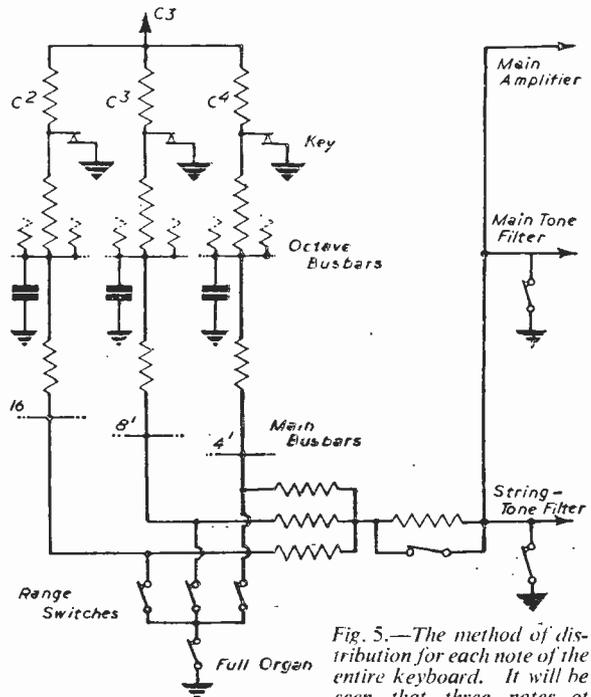


Fig. 5.—The method of distribution for each note of the entire keyboard. It will be seen that three notes in octave intervals are joined to each key which carries a three-contact switch.

board frame should be attached a board of either stout three-ply or stout hardboard, upon which may be mounted the distribution board and later the pre-amp. tone-filter and vibrato chassis.

For the distribution board obtain some $\frac{1}{8}$ in. paxolin sheet and cut strips $1\frac{1}{2}$ in. wide—either one or two strips to the total length of the keyboard. The strip should be drilled as shown in Fig. 6, and small mounting brackets made to stand them upright on the keyboard cover board just mentioned. Another strip or strips should now be made exactly the same size and long enough to stretch from one end of the keyboard to the other, and it should be drilled with a row of $\frac{1}{8}$ in. holes as shown in Fig. 7. Each group of three holes should be the width of the keys, and therefore it is probably best to lay the strip across the keys and mark the positions in pencil before drilling. Some phosphor-bronze strip is next needed for the contacts and contact strips, and if any difficulty is experienced in obtaining this, Atomic draught-excluder strip may be used, obtainable from most ironmongers and builders' merchants. This is sold in rolls of 20ft. (and multiples of 20) and is $\frac{1}{16}$ in. width. It is easily cut with ordinary scissors and may be made as springy as desired by bending, as shown in the upper part of Fig. 7. Cut one strip as shown for each of the keys, and two dozen of them should be given two "fingers" by making a central cut, and the remainder split into three. Drill as shown, and


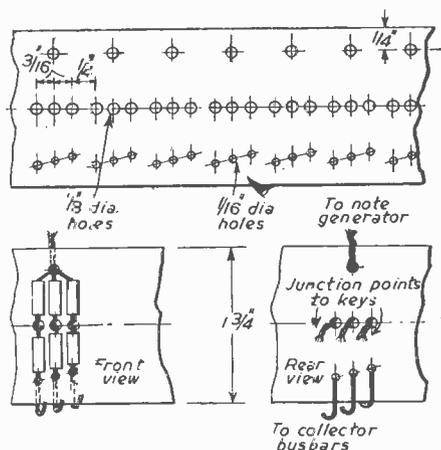


Fig. 6.—Details of construction of the main keyboard distribution board, seen at the rear of the keyboard in the illustration below. Dubilier type BTS resistors are wired as shown in the lower sketch.

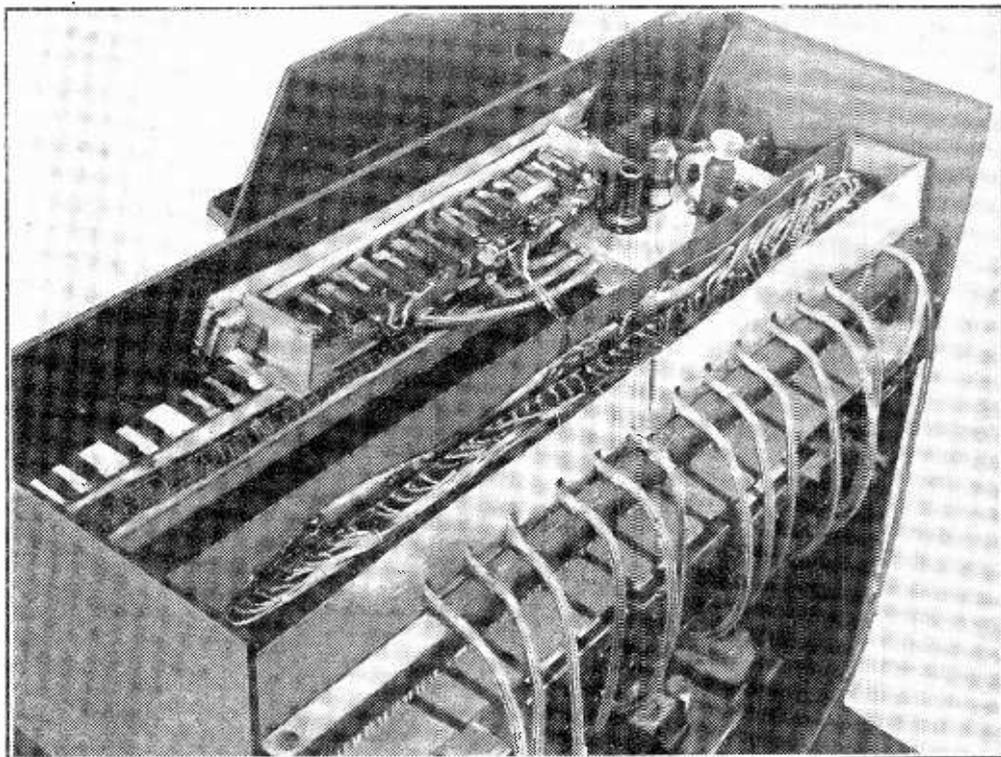
bend to make them have an upward tendency when screwed down. 156 short pieces $\frac{1}{2}$ in. by $\frac{1}{8}$ in. should next be cut off, and the tips bent round with a small



This illustration shows the keyboard with distribution board, main Fe. tabs and the small pre-amp, vibrato and tone-control valve chassis. Twelve screened five-way cables convey the outputs from the tone generators to the distribution board.

pair of thin-nosed pliers, the turn-over being pushed through the holes in the strip and clamped with flat pliers. The strips should be just wide enough to have to be forced through the holes, when the edges will just cut into the sides of the hole and they will not have a tendency to turn. This strip of contacts should now be attached to a $1\frac{1}{2}$ in. by 1 in. length of batten, the ends of which should be cut if necessary so that it may be screwed to the keyboard frame with the

for an even touch and response some time should be devoted to obtaining a nice even action. Lengths of 22 or 24 S.W.G. double-cotton covered wire must now be soldered to each of the contacts and made long enough to pass from the contacts out to the edges of the frame and round to the corresponding position at the back where the distribution board will be mounted. If you can obtain a length of Post Office multi-core cable this will serve admirably as

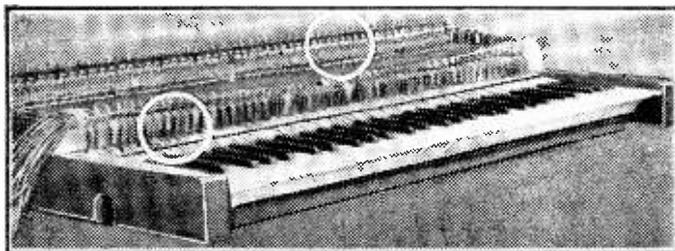

In this illustration of the keyboard during construction, the upper circle indicates the position of the distribution board as shown in Fig. 6, whilst the lower circle indicates the position of the arrangement shown in Fig. 8.

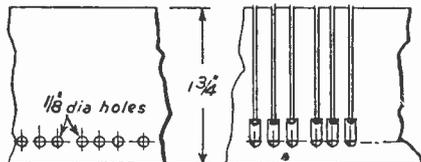
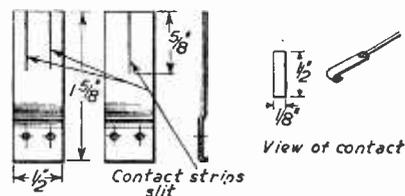


Fig. 7.—Details of construction of the key contact strips and the contacts.

contacts just reaching about $\frac{1}{4}$ in. above the keys. The contacts should be approximately 2 in. back from the ends of the ivory or celluloid covering of the keys, or the rear edge of the black notes (Fig. 8).

Contacts

Next attach the contact strips to the keys by means of two round-head No. 8 $\frac{1}{4}$ in. brass screws, bending the cut ends upward so that they are approximately $\frac{1}{4}$ in. above the keys. A length of wood strip may be rested on the frame to indicate roughly where the contacts will come, and the ends of the strips should be fairly well aligned to provide an even action. The two-contacts strips should be mounted on the end 12 notes at each end of the keyboard, the remainder on the rest of the keys. A length of fine copper braid should now be soldered to the top note and looped for about $1\frac{1}{2}$ in. and attached to the next note proceeding down the keyboard from note to note as shown in Fig. 8. At the extreme left, leave 2 or 3 in. for subsequent earthing.

Attach the support strip to the keyboard frame and run along the keys to make certain that the edges of the contact strips touch the small contacts, and that they open when the key is depressed. Check with a battery and meter or bulb. This action is critical and

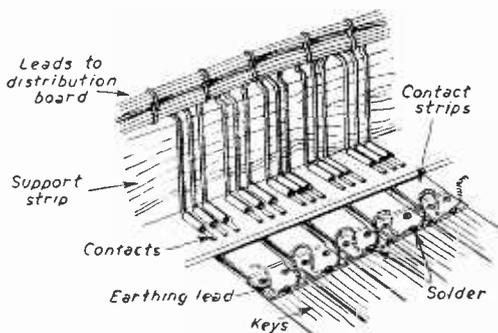


Fig. 8.—Details of the assembly of the key contact mechanism.

it is colour-coded, but it is not essential. Before soldering to the contact strips slip a 1 in. length of insulated sleeving over the end, and after soldering push this back over the soldered joint which will enable the entire assembly afterwards to be made rigid by pouring wax across the strip into the angle formed by the rising lead as shown in Fig. 8. The wires should be laced for neatness.

(To be continued).

As useful as a Tool Kit—

8th (Fully Revised) Edition of the
PRACTICAL MOTORIST'S ENCYCLOPÆDIA
By F. J. CANN

With full section on Car Radio

400 pages, 493 Illustrations

17/6 or 18/- by post from :

GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, W.C.2



My Radio Show Ramble

MY annual pilgrimage to the Radio Show this year was undertaken with rather more than my usual zest and relish. It was a celebratory visit, for our twenty-first birthday number was widely acclaimed by all of the exhibitors, who wanted to waylay me and inveigle me into those back recesses of their stands where various bottles are provided for the delectation of honoured guests. Had I partaken of but a tithe of these generous invitations I fear that I should have seen little of the Show. It was nice, however, to receive so many congratulations, sincere and well meant. These came not only from members of the trade but from callers at our stand. Nostalgia at that stand was the keynote this year. Interest in set-building is as great as ever, although there were general comments on the absence of component manufacturers and our advertisers. I hope next year something will be done to bring them in.

The Show itself was very much better than last year and although the deplorable strike caused many of the stands to open unlit, the public nobly responded and attendance figures this year were up on last year. The stands were most attractive, but I cannot refrain from the comment that it is high time that the exhibition authorities co-operated with the R.I.C. and made the inside of Earls Court more attractive. At present it looks like a half finished factory which has been hastily thrown together. The recent Brussels Exhibition was tastefully decorated and furnished inside and provided a fit setting for the attractive stands. At Earls Court the attractiveness of the stands is not supported by internal decorations. The impression was that of some choice period furniture set in the middle of a cow shed. Exhibition authorities should realise that they have a duty to the industries which stage shows. They should not just take the money from exhibitors and plough none of it back.

Although there was some improvement in accommodation it was inadequate. I noticed women loyally traipsing behind their menfolk, weary footed and unable to be seated when, after waiting in a queue, they obtained a cup of tea. The lack-lustre look of most of the women showed that they are not really interested in the technical aspects of radio. One, however, did brighten up at the mention of the word "interlace." She thought it was some new fabric.

There were no startling developments in radio, and the accent was very naturally on television. Altogether the Show was a great success and, although I was able this year to visit it more often than last, I parted from it reluctantly when it closed its doors on September 12th.

Parlour Games on Radio

I AM sick and sated with this plethora of parlour games which have been plugged year in and year out on radio and television. "What's My Line?," "Down You Go," "Twenty Questions," are examples of the childish nonsense with which we are being fed on both sides of the BBC service. One comedian in one of these programmes is even making a living out of rudeness which he thinks is wit. One of these days, I suppose, they will discover the old games of Postman's Knock and Musical Chairs: These stupid programmes always remind me of that frightful bore to be found at any home party who wants to organise party games. Surely there should be some more originality in the BBC with their vast personnel, large numbers of whom are not kept fully employed?

Tape Recorders

THE Radio Show revealed a great advance in interest in tape recorders and one was shown in kit form for the constructor. This was demonstrated to me and I must say that I was most impressed with its quality and especially with musical recordings. I think it can be taken that wire for this purpose is on its way out, not only because of the poor quality of reproduction on music, for which it is quite unsuitable, but because of the ever-present risk of wire breakage. The wire is usually .003in. thick and frequent stopping and re-starting soon causes fatigue in the metal, which is constantly being bent round the spool. One point I have noted about wire recording is that it is not permanent. I made some records on wire and found that a few weeks later they were too faint to be audible.

Tape, on the other hand, is robust. It may be used for speech and music and it is cheaper. Sales of tape recorders are on the increase. They are not only useful for entertainment purposes (one can record one's favourite records, equivalent to over an hour's playing time, and play back without the bother of changing needles) but also for business purposes. One can dictate to it when a typist is not present. This method of recording must eventually oust the gramophone disc. At some time in the future our radio gramophone, tape recorder and television will be housed in one cabinet. Shall we ever dial GRAM on the automatic telephone and have played over to us for recording on our own tape one of our favourite tunes or concertos?

Tape recording has, indeed, become a hobby ancillary to radio and many thousands of them are being built.

Thanks!

I EXPRESS my thanks to those many readers who have written me personal letters of congratulation. They are too numerous for me to reply to individually, but they have all been read and their sentiments treasured.

An Electrically-operated Coil-winder

FITTED WITH A TURNS COUNTER, THIS INSTRUMENT WILL WIND LAYER OR WAVE-FORM COILS

VARIOUS types of coil winder have been described in these pages from time to time, but a power-operated unit appears to be the most popular. As back numbers describing a versatile motor-operated winder are now out of print, we are, by popular request, reprinting below the essential constructional features.

The main features of the machine are :

- (1) A variable speed control.
- (2) An automatic reversing clutch for the wire guide.
- (3) A turns counter.
- (4) A wire tensioning device.
- (5) An attachment for wave winding.
- (6) Facilities for winding back on to a wire spool.


Operation

For layer winding the winder works as follows :—
The motive power from the main driving shaft is conveyed to the bobbin shaft by belt drives, so that the bobbin or former to be wound is rotated at the desired speed. At the same time the driving shaft is turning the main clutch pulley, which in turn drives the forward pulley or the reverse pulley according to the position of the clutch, the action of which will be described later. These pulleys rotate the 4 B.A. screwed rod in a forward or backward direction, moving the wire guide, and thus the wire, to the right or left. When the wire approaches the end of the bobbin being wound, the clutch reverses and the wire is wound back in the opposite direction. This action is repeated indefinitely, and so even layer-wound turns may be built up.

For wave-winding, the clutch mechanism is rendered inoperative by loosening the screw which secures the main clutch pulley to its shaft. It is then a simple matter to fix the wave-winding attachment in place, the action of which is self-explanatory from the illustrations. A large pulley is fitted to the bobbin shaft in order that a uniform wave-wound pattern may be produced.

Clutch Action

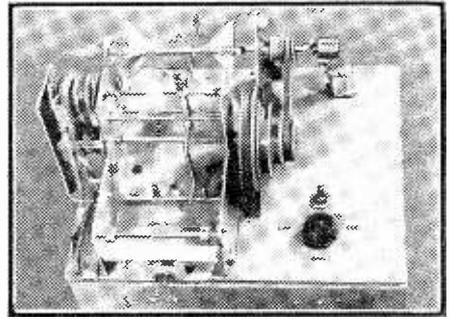The action of the clutch mechanism is as follows:—
After switching on the motor, assume that the wire guide is travelling from left to right. The cranked rod on the wire guide is approaching the reversing stop, finally makes contact with it and gradually pushes the clutch operating rod to the right. This in turn




slowly pulls the first toggle until, at dead centre, the toggle clicks over and, by means of the fork at its end, pulls the second toggle over instantaneously to its opposite position. This action slides the moving clutch plate to the left and so pushes the reverse clutch pulley against its plate. This engages the catch pin and turns the reverse plate and the screwed rod in the opposite direction. At the precise moment when the reverse pulley is engaging, the forward pulley disengages itself from its forward drive plate due to the spring interposed between the two. The wire guide then traverses from right to left until the cranked rod engages the left hand reversing stop and again operates the clutch, and so on.

The reversing stops are adjustable and may be set to any desired length of winding. For construction see Fig. 1 and Fig. 3.

One may imagine that a single toggle would be sufficient to operate the clutch mechanism, but what is needed is an instantaneous changeover. Due to the gradual movement of the first toggle (before it gets to dead centre) one would find that the engaged pulley would disengage itself but the other pulley would not engage until the toggle is finally pulled over. Consequently both pulleys would be running free on the spindle for a while and the wire guide would remain stationary whilst the bobbin would be piling up turns in one place.

This unwanted time-lag is overcome by means of the fork at the end of the first toggle engaging the lower arm of the second toggle at the moment when it (the first toggle) clicks over.

(Continued on page 685)

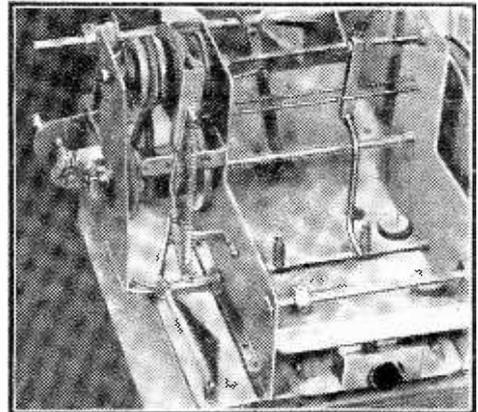

A detailed view of the clutch mechanism.

Great Britain's Valve Mail-Order House



SERVICE SHEETS

The one you require enclosed if available in a dozen assorted of our best choice. 10/6



Q-MAX. Chassis Cutters with Keys

The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: A die, a punch and an Allen screw. The operation is quite simple. Prices: 1in. 12/4; 1 1/2in. 12/4; 1 3/4in. 14/6; 1 1/2in. and 1 3/4in. 16/- each; 1 1/2in. and 1 3/4in. 18/- each; 1 1/2in., 1 3/4in., 2in. and 2 1/2in. 35/9; 1in. square, 24/3. Post 1/-.

TYANA

Soldering Irons Lightweight. Post 1/- 16/9

Atcota Irons, 25/6.

TRUVOX TAPE DESK MARK III. Incorporating high impedance mu-metal twin-track heads. Two-speed capstan, for tape speeds of 7 1/2 and 3 1/2 inches per second. Three heavy-duty motors allowing for fast forward and rewind facilities without tape handling. All controls operated by electrically and mechanically inter-locked push buttons. Price £25 2/- FREE carriage.

TAPEMASTER RECORDING COMPONENTS Suitable for use with either Hartley or Culbitts Circuits.

JUNIOR MODEL
Play Record. Imp. 3,000 ohm at 1 k c ... £1 19 6
Erase ... £1 19 6

SENIOR MODEL
Play Record. Imp. 5,500 ohm at 1 k c ... £2 5 0
Erase ... £2 5 0
Oscillator Coil in can. 10 6
Oscillator Unit incl. Coil and 6V6GT valve ... £2 5 0

TAPE RECORDER MOTORS
Collaro clock or anti-clock 38/6.

B.S.R. Type F.P.10 21 18 0
Type S.R.1 21 12 0

RECORDING TAPE "SCOTCH BOY"
1in. x 600ft., 5in. spool, 21/-
1in. x 1,200ft., 7in. spool, 35/-
Emtape: H30/6 (H/C) 600ft. £1 1 0
H30/12 (H/C) 1,200ft. 35/-
H65/12 (L/C) 1,200ft. 35/-

G.L.C. Tape: 1,200 high or low coercivity ... £1 10 0

Tape Recording Amplifiers for all popular tape units.
EM34 (Magic Eye) 16 5 0
EL41 ... 18 5 0

SOUNDMASTER TAPE RECORDER

W.B. COMPONENTS
W.B.201 Amplifier chassis incl. V holders ... £1 15 0
W.B.202 Power Unit chassis with V holders ... £1 11 6
W.B.203 Brackets, Pillars, Screens ... 11 2 2
W.B.204 Mains transformer ... £3 7 6
W.B.205 Smoothing Choke ... 19 6
W.B.206 Output transformer ... 12 0
W.B.207 Bias rejector coil ... 6 2
HF.610 Loudspeaker (plus 13 - P.T.) ... £1 17 6
Cabinet ... £6 0 0

COLLARO
3 recorder motors (1 anticlock) (1 clock) (1 anticlock special) ... £5 15 0

RADIO RESISTOR CO.
Resistor Pack and Potentiometers (List value £2 12 6) ... £2 7 6

P.C.A.
Condenser Pack (List value £1 13 6) ... £4 3 0

WEARITE
1 "Red Seal" heads (Low Imp.) ... £4 4 0
Head/t transformer type 977 ... £1 10 0
Oscillator coil type 579 ... 7 6
1 Treble boost inductor type 647 ... £1 5 0
List Value ... £7 6 8
Complete price as kit ... £7 0 0

BULGIN
Switches, Fuse holders, Knobs, signal lamps, Jacks, sockets, etc. ... £3 10 0

BRITISH N.S.F.
1-SM20 amplifier switch ... £1 1 0
1-SM21 Tape desk switch ... 7 0
1-SM22 Tape desk switch ... 7 6
£1 15 6

BRENELL ENGINEERING
Tape Desk Kit (unassembled) ... £13 13 0

LUSTROPHONE
Microphone model C51 Z High Imp. ... £5 15 6

VALVES
2-EP40 ... 22 1ea.
1-ECC40 ... 23 9
1-EM34 (Magic Eye) 16 5
1-EL41 ... 18 5 0

Valves - BARGAINS

01B4 4 3
2A6 5 6
2A7 6 5
2B7 5 11
12A 3
6 2B 2 10
3A 4 3
6AB7 5
KTZ41 5
MSPen 5
VP13c 6
PX25 15
854 3 6
Post 9d.



Demebbed Valves 2/3 Manuri

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still some Values left at very old Budget rates (83%) which are actually sold at the old price.

Pfeco Meter, 29/6.
Moree Buzzer Outfits, Air Ministry, 8/-.
Exc-Gal. Mikes, 12/6.
Amplion Test Meters, 25/-
Germanium Crystal Diode w. Circuit, 3/-
PHILLIPS Neon Testers, 100-500 v., only 5/-.
Condenser Tester and Rectifier Units, 39/6.

November VALVE LIST Cancels All Previous Lists.

SUBJECT TO STOCK. WE MAY SEND EQUIVALENTS.


Post 9d.

Post 9d.

0Z4	9/-	6C3	9/-	6X5	10/-	3Z5	11/-	TH30C	14 6	H63	7 6	KTZ41	11 6
1A5	9 3	6C9C	12-	7A3	10 6	37	9-	TH62	10-	HD21	10-	L13	12 6
1B1	10-	6D3	9-	7A7	9 6	41	10 6	UCH42	13-	KL35	10 6	HL4	10-
1C1	8 6	6F6	10-	7H7	9 6	42	10 6	UF41	11 6	N18	10 6	U71	10-
1G5	6 6	6G6G	9 6	7B7	9 6	45	10 6	UY41	10 6	KT2	12 6	U71	10-
1LN5	6 6	6G7	9 6	7C5	12 6	46	10 6	EBC31	9 6	KT32	10 6	U71	10-
1LA5	9 6	6H5	7 6	7C6	11 6	50L6GT	11-	ECC31	12 6	KT32C	10 6	W76	10 6
1P5	9 6	6J5	7 6	7S7	12 6	53	10 6	ECL30	15 6	KT2	10-	W77	10 6
1R1	9 6	6J6	14 6	7V7	10-	72	10 6	EF33	7 6	KT4	10-	X73	11 3
1R5	11 6	6J7G GT	8 6	7Y4	10-	73	10 6	ECS1	12-	KTW1	8 6	Z77	11 3
1S1	11 6	6K6	10 6	12A6M	10-	75	17 6	ECH42	12 6	KTW2	8 6		
1S5	11 6	6K7G GT	8 9	12K3	11 6	75	9 6	EL3	13-	KTW3	10 3	41MPT	8 6
1T4	11-	6K8	13-	12C3	10 6	77	9 6	EL5	7-	DL74	11 6	SU2150A	12 6
1T5	9 3	6L5G	7 6	12H6	6 6	117Z5	11 6	4D1	9 6	ACP33	11 6	VP133	10 6
1V	10 6	6L6	12-	12J5	8-	117L7CT	17-	8A1	11 6	HL3	10 6	SP42	12 6
1C6	9 6	6L7	14-	12Y4	9 6	117N7GT	17-	8D2	11 6	HL23	7 9	VP2330	11 6
2A6	9 6	6N7	14-	12SATGT	10 6	805	42-	9D7	9 6	HL13DD	9 6	P41	9-
2X2	8-	6P5	9-	12SG7	9-	807 Br.	12 6	10D1	7 6	HL3DD	11 6	SP2	8-
3V4	11-	6Q7	12-	12SH7	8 6	807 Am.	14 6	11D3	12 6	HL1320	10 6	SP41	10 6
5X4	12-	6R7	10-	12SJ7	9 6	813	112-	15D2	14 6	HL41	9 6	TH233	13-
5X3	10 6	6SA7	9 6	12SK7	10-	860	14 6	AC6PEN	8 6	HL41DD	11 6	TP1340	12-
5Z3	11-	6SG7	9 6	12SL7	9 6	866A	12 6	ACPI	8 6	Pen15	10-	TP22	12 6
5U1	12 6	6SH7	8 9	12SR7	8 9	84VZ1	9 6	VP23	12-	Pen134	12-	VP23	9 6
5Z4	11-	6SK7	9 6	14F5	10-	9001	7 6	Pen383	12-	VP11	12 6	VP11	12 6
6A7	14 6	6SL7	11 6	15	12-	951	5 6	VP2	9 6	F-D220	12-	MN40 (MH4B5)	13 6
6A8	14 6	6SN7	12 6	13	11-	955	6 6	SG215 (215SG)	10 6	VMP4G	10 6	FW 1500	13 6
6AC5	9-	6SS7	8-	19	9 6	956	6 6	210LF	5 9	DT4	7 6	TDD13	12-
6AC7	8-	6T7	9 6	25AC5	9 6	1299A	8-	210HF	5 6	(MHD1)	14-	FC13	10 6
6AG5	9 6	6TH3	9 6	25L6	10-	1025	9 6	210XP	5 6	MU12	11 6	TH2321	13 6
6AQ5	11-	6U3	9 6	25Z5	10-	1025	9 6	PM22A	6 3	V4G (KTZ41)	9 6	VP13C (9D2)	8-
6AM5	12 6	6U7	9 6	25Z4	10-	7193	6 6	LP2	5 6	U12 BVA216	11 6	AC2PEN (APP1B)	13 6
6B1	8-	6V3G	11-	28D7	8 6			QP22B	11-	51V (HL4)	10 6		
6B7	11-	6ZV3	10-	32	8 6			TDD2A (HD24)	10 6	M14	7 6		
6B8	10 6	6W3	11 3	33	9 6					MSPen (7-pin)	9 6		
6BR7	11-	OD3 VR153	11-	35	9 9								
6BW3	11-		14 6	35L5	10 6								
6C4	8 6	6X4	10-	35Z4	11-								

Kindly mark envelope PW1..



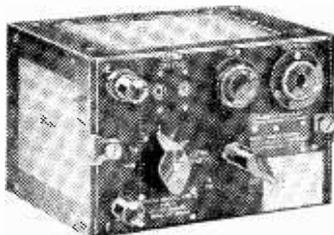

Crystal Monitors

to check Tx and Rx Frequencies, provision for phones, battery operated. Easily adapted for Mains by using 3 6B5's. In attractive cabinet (ideal for housing test instruments) 7 1/2 in. x 5 1/2 in. x 3 in. For use with Amateur band Crystals; less valves, 7.6 each. Mains Conversion and Operating Data. 6d.

VALVES by return :

OZ4	6.6 6BE3	8.8 6EX4	8.8 50L8gt	10 - 1HL2	3/6
1A5gt	7.6 6EA3	8.8 6UX5gt	2.6 75	12.6 KT24	5/6
1LD3	6.6 6C5e	6.6 7C7	7.6 78	7.6 KT44	9/6
1LN5	6.6 6CD6	11.6 7D9	8.8 177	7.6 KT63	8/6
1R5	8.6 6CH6	9.8 7Q7	7.6 215SG	5 - KT66	10.6
1S4	8.6 6P6	8.6 8D2	3 - 184Z1	7.6 KT241	7/6
1S5	8.6 6C6	7.6 8D2	3 - 184Z1	12.6 KTW61	7/6
1T4	8.6 6H6	3.6 10P9	7.6 954	3.6 N78	10.6
1625	4.6 615	6.6 12AT7	10.6 1626	4 - P61	3-
2C26	5 - 6J6	10 - 12BA6	8.6 1632	7.6 PEN13	8/-
2C34	4.6 6J7	9 - 12BE6	8.6 A915	5 - PEN220A	
2V3e	3.6 6K6	7.6 12CB	9 - D1	2.6	
3D3	2.3 6K7rt	6.6 12C1	5 - E1113	3 - QP21	5/6
3S4	8.6 6K7r	6.6 12K7	12.6 EA50	3 - RK31	7.6
4D1	3 - 6K8m	10.6 12SA7	8.6	3 for 5 - S13	5-
5R4z	12.6 6K8r	10.6 12SC7	6 - EB91	9.6 SP41	3/-
5U4z	9 - 6L6z	10.6 12SQ7	5 - ECC32	SP61	3.6
5Y3	10 - 6Q7	10.6 12SH7	5 -	10.6 V1115	3.6
5Z4	10 - 6SA7	9.6 12SJ7	6 - EF39	6 - V39A	3.6
6AB7	6.6 6SH7	6 - 12SK7	8.6 - EF39	6.6	10.6
6AC7	10 - 6SL7	11.6 12SQ7	9.6 EF50	5.6	3/6
6AT6	8.6 6SN7	10.6 12Y4	7.6 EF51	5.6	VU120A
6AL5	8.6 6SQ7	2.6 13D2	4 - EP91	10.6	3/6
6B7	9 - 6SS7	7.6 25L6	8.6 EL32	7.6	VU133
6B8	7 - 6V8z	9 - 35L6	10 - EL35	5 - U21	6/6
6BW5	8.6 6U5	8.6 39-41	5 - EL91	8.6 W77	8/6

Please include small amount for postage.

The Ham's Shop with the helping hand—Tom Gamble (G3DBL)

NORMAN H. FIELD (Dept. B9), 68, Hurst Street, B'ham. 5.

ELECTRICAL ENGINEERING
REFRIGERATION
RADIO ENGINEERING
ELECTRIC POWER & LIGHTING
JIG & TOOL DESIGN
DRAUGHTSMANSHIP
MOTOR ENGINEERING
MECHANICAL ENGINEERING

If you need help on any Engineering subject, ICS will give you intensive, practical home training. Act now! Prepare to step up to a better job, with more money—in the electrical, radio or television fields, in engineering, in a trade, business or profession. ICS courses cover practically every kind of career. All you have to do is write for details. There is no obligation.

I.C.S. also coaches candidates—until successful—for most Tech., Prof., Comm., Civil Service Exams. and Gen. Cert. of Education, etc.

FILL IN THE COUPON and post today, stating which subject or career interests you. Fees include all books required. Reduced Terms to H. M. Forces.

Dept. 170E, I.C.S., 71, Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS,
 Dept. 170E, International Buildings, Kingsway,
 London, W.C.2.

Please send Booklet: cn

Name..... Age.....


(Block letters please)

Address



COMPACT TV.

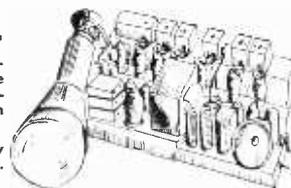The NEW 1355 Conversion data for all five Channels, Sound, Vision, T.B.'s, Power, on one 1355 Chassis
NEW EDITION, now only 2/8! (post free).



1355's in original cases. (carr. 7/6) 35/-

METERS 0/500 µA, scaled in small sloping front black crackle cases. 12/6	TRANSFORMERS multi-purpose components which may be used as H.D. output, intervalve or mains, giving approx. 24 v. at 2 A (4 tapplings) and 300 v. 30 mA. (E.H.T. rect.) Transformer, choke, relay, etc. 9/6	NEW VALVES 5U4G ... 7/6 L63 ... 5/6 H63 ... 5/6 6E5 ... 9/- 6S7 ... 6/6
CHASSIS, with 5Z4, VU120 (E.H.T. rect.) Transformer, choke, relay, etc. 9/6	WILLARD ACCUMULATORS in non-spill transparent plastic cases, with built-in hydrometers. 2 V, 20 AH in sealed maker's cartons (measure 5 1/2 x 3 1/2 x 2 1/2). 15/-	CARBON MIKES, with 5ft. lead and switch (boxed). 3/6 DAMAGED U.S.A. METERS, 5 for 6/- DINGHY Tx CHASSIS (partly stripped), 5/-

RADIO EXCHANGE CO.
 14A ST. MARY'S STREET, BEDFORD
 Phone 5568

G2AK This Month's Bargains G2AK

MULTI-METER BASIC UNIT—400 Microamp. F.S.D., scaled 8 ranges A.C./D.C. volts, HI and LO ohms, complete with rectifier made by Triplett, U.S.A. Only 32/6, post free.

SHADED POLE MOTORS for tape recorders or gram. units. With voltage tapping plate 200/250 volts, 3-hole fixing. Our price 12/6 ea. or 21/- pair. Post and pkg. on either, 1/6.

SPECIAL TRANSFORMER OFFER.—Pri. 115, 210, 240v. Secs. 260/260 v. 100 mA., 6.3 v. 3 A. and 6.3 v. 1 A. for 6X5 rectifier. Universal mounting. Limited quantity. 17/6 ea., post free.

Special Offer. T.V. 1/2 in. Coaxial Cable, 11d. yd. or 9/6 per doz. yds., or 9d. per yd. in 100-yd. coils. P. & P., 1/6.

Special Valve Offer. Kit of 4 midget valves 1.4 v., 1 each 1S5, 1R5, 1T4 and 1S4, 30/- or 8/6 ea. separately. 807's 12/6 ea. or 2 for 22/6. Most of the 1.4 v. range available at 8/6 ea.

L.T. Transformers. 230 v. Primaries. 12 v. 1.5 A., 12/6; 6.3 v. tapped at 4 v. 1.5 A., 8/-; 6.3 v. 2.5 A., 12/6; 6.3 v. 6 A. and 5 v. 4 A., 25/-.

Twin Feeder, 300 ohm 150 watt rating, 6d. yd. Minimum quantity, post free, 20 yards; otherwise, P. & P. 1/6.

Morse Practice Sets, with double action buzzer, output for phones, excellent key, require only 4 1/2 v. battery. As new, 7/6 ea. P. & P. 1/-.

Germanium Diodes, B.T.H., 2/-; G.E.C., 2/6 ea.
Potentiometers, Carbon, 50 K., 100 K., and 1 Meg. spindle Type, 1/6 ea.; 26 K. and 1 Meg., Pre-set Type, 1/- ea.; Wire Wound 20 K. Spindle type, 2/-; 20 K. and 50 K. Pre-set, 1/6 ea.

V.H.F. FANS. Air space Co-axial Cable, 150 ohm, good to 600 Mc/s.; normal price, 3/11 per foot. Our Price, 20 yard coil, £1. Very limited quantity available.

Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

C. H. YOUNG, G2AK

All callers :
 110 Dale End,
 Birmingham (CEN. 1635)

Mail Orders :
 102, Holloway Head,
 Birmingham 1 (MID 3254)

Construction

Although at first sight the machine appears to be somewhat complicated, construction is not really difficult and in actual fact all the materials were collected from odds and ends that happened to be available. Naturally, a little care and patience are required in the construction of the various parts but this is amply repaid in the finished product. A plan view of the machine is shown in Fig. 1. For convenience, and in order to keep it out of harm's way and free from dust, the motor and its associated components are mounted below the brass plate upon which the winder is built. The plate is hinged at its back edge to a wooden box measuring 3 1/2 in. deep. This was actually part of an old portable gramophone case that was available. The base plate measures 12 in. by 11 in. and is of any suitable metal about 3/64 in. thick.

It is essential that the plate provides ample rigidity. The side plates are of similar metal 1/16 in. thick. Their size and shape is shown in Fig. 2. These form the main supports for all the rods and shafts except the bobbin shaft. This is held by separate supports, which may be designed according to material at hand. Those shown in the photographs happened to be available. The bearing centres are approximately 2 1/2 in. from the base plate.

At this point it may be mentioned that although,

in most cases, sizes of the various parts are given, it should be realised that quite a large amount of freedom is permissible in this direction. It is advisable, however, to adhere to the specification of the main pulley bank, the bobbin shaft pulley and the toggles, as the dimensions of these items have proved suitable.

The three shafts may be rod of any suitable metal such as German silver, steel, brass, etc., and those shown are approximately 3/16 in. in diameter. Bearings for these, except the reel shaft, are made from tubing to fit the rod, and 1 in. lengths soldered into the side plates and bobbin shaft supports is sufficient. A simple method of ensuring that the bearings are true is first to drill the side plates and supports and mount them firmly on the base plate. Slip the bearings (longer than required) on the shafts and fit them all in their relative positions. The bearings may now be soldered, after which the shafts are removed and the bearings trimmed to the desired length. By this means it is impossible for them to be out of alignment. The same applies to the clutch-actuating rod which is square (so that it cannot rotate around its own axis) and has square tubing to fit, as bearings. This rod *must* have a relatively easy action and should, of course, be lined up with the end of the first toggle. The rod is connected to it by a stout wire link, one end of which is bent accurately around the

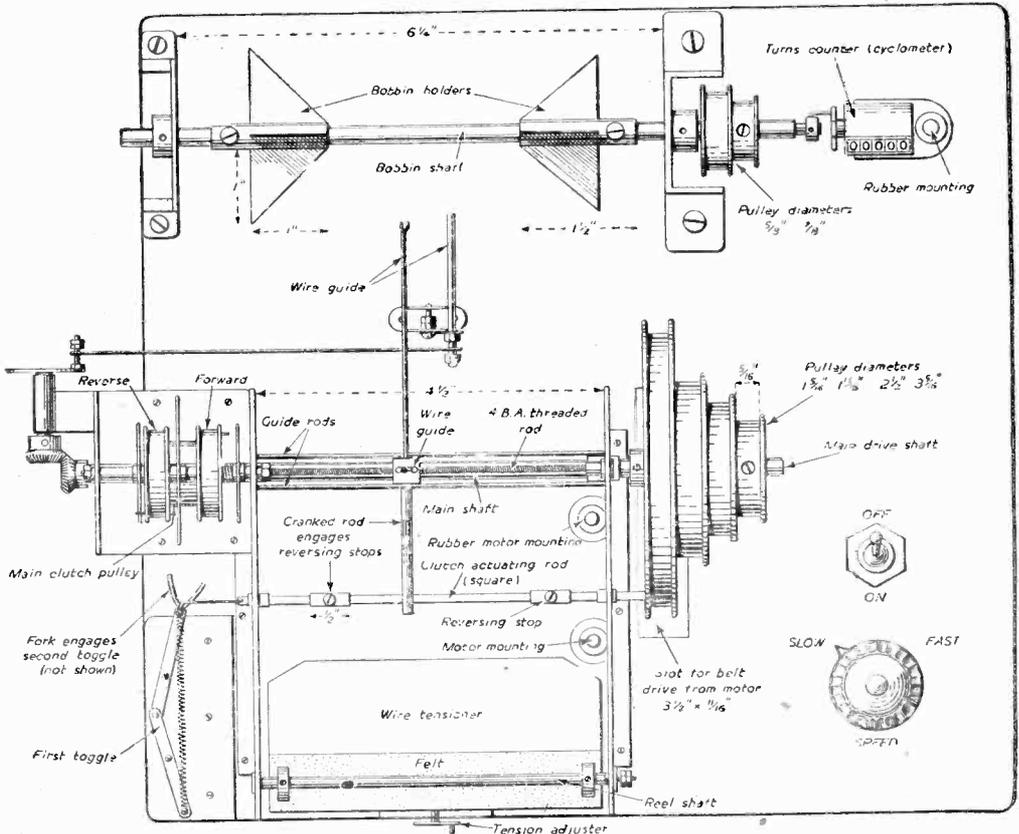


Fig. 1.—Plan of the complete machine with all parts identified.

spacer on the end of the toggle, the other end being bent down to a right angle and inserted into a small hole in the end of the rod.

The reel shaft has a type of quick release method of fixing. A bearing hole is drilled in the left-hand side plate and then a little plate is soldered over the outer side of the hole. The right-hand side plate is similarly drilled and a small swinging plate is arranged to slide over the outside. The shaft, cut to the length of the distance between the outer edges of the side plates, is thus firmly held in position when the

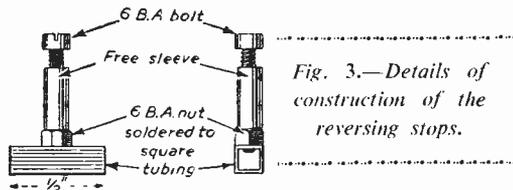


Fig. 3.—Details of construction of the reversing stops.

moving plate covers the hole. A fixing collar each side of the reel prevents any sideways movement.

The construction of the wire guide is shown in Fig. 4, and is self-explanatory. The 4 B.A. threaded rod upon which the wire guide travels must be long enough to pass through the tubing which forms the shaft for the forward and reverse clutch pulleys, etc. A nut at each end of the shaft serves to lock it to the threaded rod. A short length of tubing is soldered to the other end of the 4 B.A. rod so that it may revolve freely in a suitable hole or bearing in the side plate.

The two guide rods serve to keep the wire guide running in a perpendicular plane and may be of small diameter.

Bobbin Holders

The bobbin holders (see Fig. 1), are made by soldering four triangular pieces of metal equidistantly

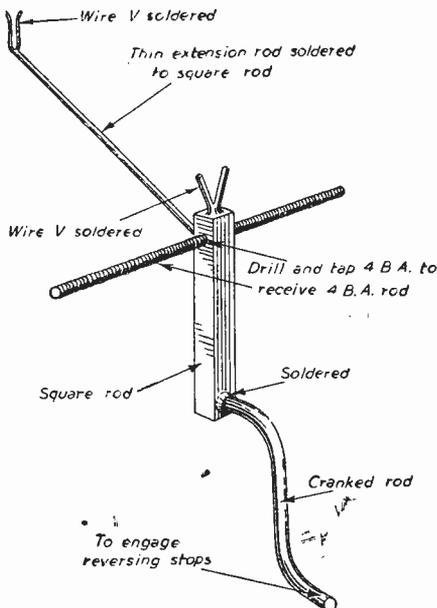


Fig. 4.—Constructional details of the wire guide.

around the axis of a length of tubing which will fit over the bobbin shaft. Fixing to the shaft is provided for by drilling a 4 B.A. clearance hole, soldering a nut over it, and fitting a 4 B.A. bolt.

In use the holders are more or less universal and a round or square bobbin is easily centred and securely held.

The four-bank pulley on the main shaft and the

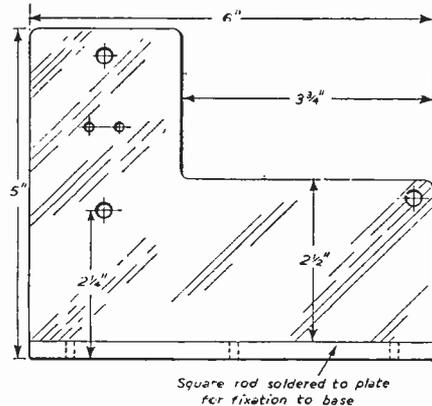


Fig. 2.—Shape and sizes of the sideplates. Two are required.

two-bank pulley on the bobbin shaft are both made from sheet Perspex. Diameters are shown in Fig. 1. Material 5/16in. thick was used to form the actual pulleys and 1/8in. for the flanges. The procedure is to mark out all the discs required and run a pilot hole through each centre. Then cut out the discs with the aid of a hacksaw or keyhole saw and file the edges true. If facilities are available, the discs are fastened to the chuck of an electric grinder or polisher and trued up with file and sandpaper. In any case great accuracy is not essential. The discs which form the flanges should have rounded edges. Next drill each disc centre to the diameter of the main drive shaft. *Note.*—Unless care is exercised in the drilling of Perspex the drill is inclined to wander. For this reason the pilot hole is suggested before cutting out. Next, line up the discs on a length of rod and fix each together with Perspex cement, or if preferred, countersunk machine screws—although this will entail drilling and tapping. When set, drill the centre of the whole pulley bank to a diameter very slightly smaller than the diameter of tubing which fits the main shaft. Then taper the end of a length of tubing and, after heating, push the tube slowly and accurately right through. This will "fuse" the bearing nicely in position. A little experimenting is advisable when heating the tubing, for if too cool it will not slide through and if too hot it will burn and enlarge the hole in the Perspex.

Finally, a shaft fixing is provided for by drilling and tapping through the radius of the smallest pulley and on through the bearing tube.

The Toggles

The construction of the toggles is shown in Fig. 5 and 6, and if made up accordingly will operate satisfactorily. It should be realised, however, that the holes around which each strip swivels should be slightly elongated in order to allow of a free action

through dead centre. In addition, all moving joints should have a free action. With regard to the second toggle it will be seen from Fig. 6, that it is held by brackets A and B, fixed to the side plate. The object of this toggle is to slide the moving clutch plate to the right or left. This is achieved by the one-piece metal tongue attached to the top of the toggle arm and has a swivel joint. The tongue may be bent up from light aluminium and is arranged so that the prongs or tongues engage the outer diameter of the moving clutch plate but do not obstruct the pulleys.

The main clutch pulley which is driven by the main shaft is 1 in. diameter, $1\frac{1}{2}$ in. long and has a flange of

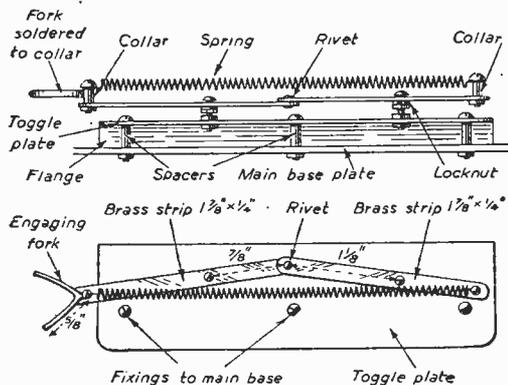


Fig. 5.—The first toggle seen in plan and elevation.

some $\frac{1}{2}$ in. The size of this pulley, however, is not important and something approaching this size will suffice. The one shown was a wooden wire spool or reel which was available. A bearing made from tubing to fit the shaft was pressed through the centre and fixing to the shaft provided for as previously explained.

Fig. 8 (which will be given next month), shows the arrangement of forward and reverse pulleys, their associated drive plates and the moving clutch plate. They are shown spaced for clarity and are mounted on a shaft of tubing of a size that is a good fit over 4 B.A. rod. The drive plates are identical in size and shape, but one is mounted in reverse in respect to the other.

They are both fixed to the spindle either by means of a driving fit or by soldering. The pulleys measure $1\frac{1}{16}$ in. dia., with small flanges and are $\frac{1}{2}$ in. thick. Those shown are small wooden wire spools. Here again the actual diameter is relatively unimportant, so long as something approaching these sizes are used. The pulleys are bushed with tubing to fit the spindle, but not carried right through so that a recess of a little over $\frac{1}{8}$ in. is formed (see Fig. 8). Into this recess fits the spring (when compressed), so that the pulley, when engaged, may lie flush against its drive plate.

A catch pin to engage the drive plate is fitted to the outer edge of both forward and reverse pulleys and may be achieved by driving a little brass pin into the pulley and removing the head. The edge should be slightly rounded so that it disengages freely. These pulleys run free on the spindle.

The moving clutch plate is merely a disc of stoutish gauge metal $2\frac{1}{2}$ in. dia. It is free running on the spindle and bushed so that it may slide either way in a true perpendicular plane.

Belts

Rubber bands or belts are fitted between the main clutch pulley and forward and reverse pulleys, that to the latter being twisted to effect reversal of direction. Due to the pull of these belts it was found necessary to provide a bearing plate for the two spindle ends. This is shown in Fig. 7. It is just a stout, right-angle bracket, bolted to the main base plate. The wire tensioning device consists of two pieces of metal 4 in. x $2\frac{1}{2}$ in., hinged along the 4 in. edge. The

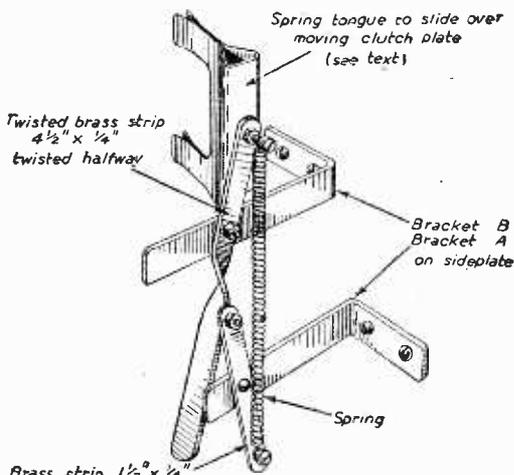


Fig. 6.—Details of the second toggle.

upper plate has a piece of felt stuck to the area that engages the flanges of the wire-reel.

The lower plate lies flat on the base plate and is secured to it by two 4 B.A. bolts screwing into tapped holes. The holes in the wire tensioning plate are elongated to the extent of about an inch so that it may be moved forward or backward, depending on the size of the reel being used. This is the coarse adjustment. The fine adjustment consists of a small, three-sided metal flange of J section made to move inside the angle formed by the two plates.

(To be continued.)

The Entirely New 12th Edition of The Famous Standard Work

THE PRACTICAL WIRELESS ENCYCLOPÆDIA

By F. J. GAMM

Considerably enlarged, amplified and entirely re-written and re-illustrated. Complete Television Section, with theoretical and constructional data.

All the facts, figures, and constructional data of Radio and Television—Definition, Terms—Units—Principles, Circuits, etc.

Over 300,000 copies sold Price 21/- or 21/11 by post from:

GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, W.C.2.

LAST month we gave full details which will enable most amateurs to construct the receiver and obtain satisfactory results. There are, however, a few points which have apparently presented difficulty to some of the more inexperienced constructors. First, the complaint has been made that no top-of-chassis wiring diagram was included on the blueprint. Actually, there are only two leads on the upperside of the chassis—excluding the lead to the top cap of V3 which was indicated on the chassis underside, and to which a top-cap connector is fitted. The two leads in question are to the top caps of V1 and V2, and that for V2 is already provided in the I.F. transformer. It projects from the top of the can and is joined to V2 top cap. The other lead is soldered to the top connecting point on the ganged condenser and provided with a screened top-cap connector subsequently fitted to the top of V1. To assist those who wish to check the performance of the receiver we give below a table of the voltages found at the essential points of the circuit. It must be emphasised, however, that it may not be possible in every case to duplicate these voltages. It is for this reason that we do not give them in all of our constructional articles. First, the actual meter will govern the exact reading which is obtained.

In the case of our measurements, for instance, they were taken with a meter having a resistance of 10,000 ohms

F.J. CAMM'S Coronet


FURTHER CONSTRUCTIONAL
AND LINING-UP DETAILS
WITH ALTERNATIVE COIL-
PACK SUGGESTIONS

per volt. If a low-priced meter having a resistance of only 1,000 ohms per volt is used, however, the readings will be lower. The reason for this is that the meter acts as a shunt across the points measured, and if it takes a current approaching that taken by the circuit being measured, it will obviously give the total reading at that point when the meter is in



This illustration of the completed receiver shows the two top cap leads.

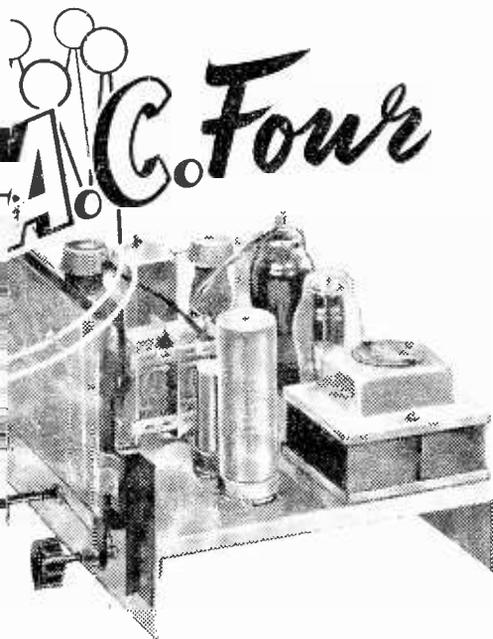circuit, but not the reading of the voltage when the meter is removed. Similarly, if the meter has a higher resistance than the one we used it will show a higher reading.



Therefore, these readings must only be taken as guides. Obviously, if, in the case of the screen grid of V2, a voltage only 80 or so is registered, this will indicate a fault, as the meter could hardly account for such a large difference.

Loudspeakers

Whilst at the Radio Show many readers came and discussed the receiver with us. A point which seems to have given some difficulties is in the choice of a loudspeaker. We recommended a W.B. and these are available in a range of models. The receiver itself will deliver a reasonably high standard of reproduction, but obviously in such a simple design it makes no pretensions to being a high-fidelity receiver. Accordingly there is no justification for purchasing an expensive high-fidelity loudspeaker. The specified 8in. model, a standard Stentorian, will give quite a good standard of reproduction and only costs a little over £1. The hi-fi model costs over £3, and this will, of course, influence the total cost of the receiver. In this same connection arises the question of the parts specified. It has been our policy as readers know, to specify exactly the parts which we used in the prototype, and it is these which are listed in the published list of components. In many cases, however, some deviation is quite permissible. For instance, in this particular model we listed in the condensers two .1 μ F condensers type CP46S. This reference or type number indicates that the particular condenser was

a super tropical "Metalpack" in an aluminium case and that it was designed for a working voltage of 500 at 70 deg. The physical size of this type of condenser is not of great importance in the receiver under consideration, and thus the principal consideration is the working voltage. It would, therefore, be quite in order to use a Type 645 or even a Type 543, but we would not recommend the use of a condenser with a lower voltage rating in the interests of reliability. Similarly, in the case of the main smoothing condensers we used a 30 + 30 type CE37LA electrolytic. This condenser has a peak working voltage of 350 and a surge rating of 400 volts. It would be quite in order to use a 32 + 32 of similar rating, or even two separate 32's.

Lining Up

As mentioned in the issue last month, the main feature of the Roding coils is that they are pre-aligned, but the overwhelming demand has resulted in these being in short supply, and readers who are interested in the general design features have asked whether an alternative could not be used in this position. It must be emphasised, of course, that the fact that the coils are pre-aligned takes away the main drawback to many constructors—namely, the necessity for using a signal generator.

However, provided that a signal generator is available, and that one is prepared to go to the trouble of lining up, a coil pack such as the Osmor Type HO could be substituted. This, also, is a three-band unit and is complete with the necessary tracking condensers. There are no coloured leads on it, however, and these will have to be attached to the five tags on the unit. To facilitate this change the following table shows the comparison—the first column giving the colour code used on the blueprint, and the second column giving the tag number on the Osmor coilpack

RODING	OSMOR
Black	1
Brown	2
Yellow	3
Red	—
Blue	4
Green	—

It will be noted that there are no corresponding numbers for the red and green leads on the original pack, and the 10 k Ω resistance joined to the point marked Green on the blueprint should be connected to terminal 5 via a 100 pF silver-mica condenser, and the .1 μ F condenser ignored. The lead marked Red (the triode anode) should then be joined to the junction of the 10 k Ω resistance and the 100 pF condenser.

Some constructors may like to go over the receiver with a signal generator after construction with the original coils or with the substitute pack, and the procedure should be as follows. First, the generator should be set to 465 kc/s., and with a suitable termination to the generator output leads—dependent upon the particular make—this

TEST VOLTAGES

The following voltage readings were obtained on the receiver with a test-meter having an internal resistance of 10,000 ohms per volt, set to the 500-volt range.

V1—Anode 190 v. G2—120 v. Triode anode 150 v.
 V2—Anode 200 v. G2—120 v.
 V3—Anode 195 v. G2—200 v. Cathode 5 v. (25 v. range).

(Concluded on page 694)



TRANSMITTING TOPICS

EFFICIENCY MODULATION SYSTEMS

By O. J. Russell, B.Sc.(Hons.), G3BHI

NOWHERE is the term "efficiency" more abused than in the electronic field. Various arrangements are almost invariably described as being "very efficient," modern valves are "more efficient" than other types and so on. Mostly, of course, the term "efficiency" is used in a very loose sense, and the expression "a very efficient circuit" usually means no more than a "very convenient" or a "very economical" arrangement. In fact, many radio devices are extremely inefficient. For example, a radio receiver may use up some 50 watts of power from the mains to produce one or two watts of audio-frequency power. This is an efficiency of, say, 2 per cent. to 4 per cent. conversion of energy. Further, this audio-frequency power is then fed to a loudspeaker which has an efficiency of, say, 5 per cent., so that the overall efficiency of mains power supplied to actual sound power output is some .01 per cent. to .02 per cent. Efficiency is thus a relative term, and one that could be used with more discrimination!

The amateur transmitter, however, is less likely to be confused about "efficiency," as the final P.A. stage running under Class C conditions may easily have an actual efficiency of between 50 per cent. and 80 per cent., with 66 per cent. as a nice convenient round figure to represent a good average. The "efficiency" in this case refers to the efficiency with which the D.C. power applied to the anode is converted into radio-frequency power. Thus a Class C

power amplifier of 66 per cent. efficiency when drawing 100 watts of anode input, has an R.F. output of 66 watts. The situation is not altered if for telephony working anode modulation is considered, as an anode-modulated power amplifier operates under normal Class C conditions. However, the beginner is quick to notice that an anode modulator is required to produce large quantities of audio-frequency power, and requires a large and expensive modulation transformer to handle high audio power. In fact, anode modulation is expensive if one is thinking of modulating a 100 watt transmitter. The beginner may then be drawn to consider the "efficiency modulation" systems, which offer the attractive feature of enabling a 100 watt P.A. to be modulated by a watt or so of audio. A modulator for an "efficiency" system can in fact be constructed using ordinary receiving components, and will give excellent results. The cost of a modulator for such a system is very low, particularly as the components are usually to hand in the spares box. Moreover, the term "efficiency modulation" has a reassuring sound, somehow implying that "efficiency modulation" is, in fact, a system of "high efficiency." The earnest enquirer is, in fact, somewhat disconcerted to find that the actual R.F. output available from an efficiency modulated P.A. stage is much less than can be obtained from the P.A. stage under Class C telegraphy conditions. Moreover, the actual R.F. output as compared with the D.C. power input is less. Thus a P.A. stage drawing 100 watts D.C. anode power, under efficiency modulation conditions, will give about 33 watts of R.F. carrier power output. This, then, seems to imply that "efficiency modulation" systems are *not* "efficient."

(Continued on page 693)

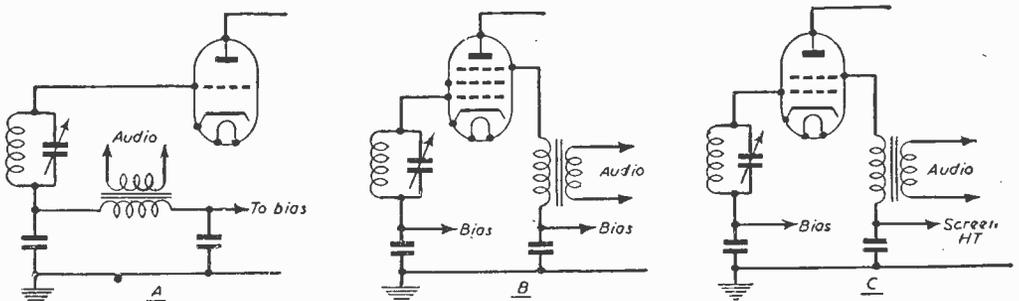


Fig. 1.—(A) Basic grid modulation circuit. (B) Basic suppressor modulation circuit. (C) Basic screen modulation circuit.

RADIO SUPPLY CO.

(LEEDS) LTD.

Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/1 extra under £1. 1/9 extra under £3.

Open 9 a.m. to 5.30 p.m. Saturdays until 1 p.m. FULL PRICE LIST, 5d. TRADE LIST, 5d. Please enclose S.A.E. with all enquiries.

32, THE CALLS, LEEDS, 2

SPECIAL OFFERS. Midget Mains Transformers (size approx. 2 1/2 x 3 x 2 1/2 in.) Screened Primary 220/240 v 50 c/s. Output 250-0-250 v 60 mA, 6.3 v 2.5 a. Only 1/9. Small Filament Transformers, 220/240 v input, 6.3 v 1.5 a output, 5/9. Mains Trans. Drop through type, 220/240 v input, 250-0-250 v 70 mA, 6.3 v 3 a, 12/11.

BATTERY SET CONVERTER KIT. All parts for converting any type of Battery receiver to All Mains. A.C. 200-250 v 50 c/s. Kit will supply fully smoothed H.T. of 120 v 90 v, or 60 v at up to 40 mA, and fully smoothed I.T. of 2 v at up to 1 a. Price, complete with circuit, point to point wiring diagrams and instructions, only 48/9. Or ready to use, 7/9 extra.

PERSONAL SET BATTERY SUPERSEDER KIT. A complete set of parts for construction of a Unit (housed in Metal Case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v 50 c/s. Outputs 90 v 10 mA and 1.4 v 250 mA, fully smoothed. For 4-valve receivers. Price complete with circuit. Only 33/9. Or ready for use, 39/9. Size of unit, 5 1/2 x 4 x 1 1/2 in.

I.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v A.C. Output 120 v 40 mA, fully smoothed, and rectified supply to charge 2 v acc. Price with steel case and circuit, 29/6. Or ready for use, 7/9 extra.

BATTERY CHARGER KITS. For mains 200-250 v 50 c/s. To charge 6 v acc. at 2 a, 25/6. To charge 6 or 12 v acc. at 2 a, 31/6. To charge 6 or 12 v acc. at 4 a, 49/9. Above consist of transformer, full wave rectifier, fuses, fuseholders and steel case. The kits can be supplied fully assembled at an extra cost of 6/9 each.

EX-GOVT. VALVES (NEW)

	Each		Each		Each
1T4	8/9	6Q7G	9/11	1625	5/3
1R5	8/9	6SL7GT	11/9	3524GT	10/6
1R5	8/11	6V6GT	8/9	35L6GT	9/11
3S4	8/9	6V6GT	8/9	D1	1/3
5Y3G	8/9	6X5GT	8/9	EF36	5/11
5U4G	10/6	7V7	6/9	EB91	9/9
5Z4G	9/6	8D2	2/11	EF91	9/9
5AL5	9/9	9D2	2/11	EL32	6/11
718C	7/11	6E6	1/11	MU14	4/6
8AM6	9/9	12H6	2/3	MS Pen 5	9/9
6J5G	5/11	12K7GT10	6	RK34	1/11
5J6	9/6	12K8GT10	6	SP4	5/9
5J7G	7/6	12K7GT10	6	SP61	2/9
6K7G	6/11	12S17	7/11	VU120	2/11
6K8G	11/9	12SR7	7/11		
6L6G	11/9	15D2	5/9		

CATHODE RAY TUBES.

VCR 517 (Full Picture), 29/6, carr. 5/-.
ACR2X (Full Picture), 12/6, carr. 5/-.
VCR139A, with screen and base, 19/6.

EX-GOVT. ITEMS. Pvc coaxial plugs and sockets, 5/9 doz. prs. Belling-Lee moulded type 3 pin and 7 pin plugs and sockets, 1/11 pr. Int. Octal Valve Screening Cans, 3 piece, 1/3 each, 1/9 doz. Bak. Tubulars, .02 mtd. 5,000 v, 1.9. Meters M C 2 in., scale 0-5 amps, 12/6.

ELECTROLYTICS (Current production. Not ex-Govt.)

Tubular Types		8 μF 500 v	2/11
8 μF 450 v	1/9	16 μF 450 v	2/9
8 μF 450 v	1/11	24 μF 350 v	2/11
8 μF 500 v	2/9	32 μF 350 v	2/11
16 μF 350 v	2/3	32 μF 500 v	6/11
16 μF 450 v	2/9	40 μF 450 v	4/9
24 μF 350 v	2/6	64 μF 450 v	3/9
32 μF 350 v	3/9	80 μF 450 v	3/9
25 μF 25 v	1/3	8-16 μF 450 v	3/11
50 μF 12 v	1/3	8-16 μF 450 v	4/6
50 μF 50 v	2/3	16-16 μF 450 v	4/11
		16-32 μF 350 v	5/3
		32-32 μF 350 v	4/11
		32-32 μF 450 v	5/11

Can Types
8 μF 450 v 2/3

WILLIAMSON AMPLIFIER KIT. All parts to Author's Spec. only 14/9s.

A PUSH-PULL 3-4 watt HIGH-GAIN AMPLIFIER FOR £12/6. For mains input 200-250 v 50 c/s. Complete kit of parts including circuit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C./D.C. with "live" chassis, but A.C. only with 400-0-400 v trans. Output is for 2-3 ohm speaker. (We can supply a very suitable 10m. unit by R.A. at 31/-.) The amplifier can be supplied ready for use for £1 extra. Carr. 2/6. Full descriptive leaflet, 9d.

R.N.C. 25-WATT "PUSH-PULL" AMPLIFIER. Complete kit of parts for High Fidelity Amplifier with built-in Preamp. Distortion at 10 watts less than half of 1%. Suitable for home or Large Auditorium. Full descriptive leaflet, 9d. Price with point to point wiring diagrams only 9/9s., or ready for use, 50/- extra.

MASTER INTERCOMM. UNIT with provision for up to 4 "Listen-Talk Back Units". A high gain amplifier enables speech and other sounds emanating from the rooms containing remote control units to be heard at the master control. The unit is in kit form and point-to-point wiring diagrams are supplied. A Walnut Veneered or Brown Bakelite cabinet is included. Mains input is 200-250 v 50 c/s to 300-0-300 v trans. Sound amplifier, 4 watts. Price only £5 19/6. "Listen-Talk Back Units" can be supplied at 27/6 each. Full descriptive leaflet, 1/-.

EX-GOVT. SMOOTHING CHOKES.
250 mA 40 H 200 ohms. trop ... 17/6
250 mA 20 H 250 ohms. potted ... 17/6
250 mA 20 H 250 ohms. trop ... 14/9
200 mA 20 H 200 ohms. trop ... 12/9
150 mA 6-10 H 150 ohms tropicalised 7/9
100 mA 7-10 H 100 ohms ... 6/11
100 mA 5 H 100 ohms. tropicalised ... 3/11

EX-GOVT. BLOCK PAPER MANS. BRIDGE TYPE CONDENSERS.
4 μF 500 v, 2/9; 4 μF 2,000 v, 4/9; 4 μF 1,000 v, 3/3; 8 μF 500 v, 4/9; 4 μF 1,000 v, 3/11; 10 μF 500 v, 5/9.

R.S.C. MAINS TRANSFORMERS (FULLY Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s Screened.)

TOP SHROUDED, DROP THROUGH
250-0-250 v 70 mA, 6.3 v 2.5 a ... 12/11
260-0-260 v 70 mA, 6.3 v 2 a, 5 v 2 a ... 14/11
350-0-350 v 80 mA, 6.3 v 2 a, 5 v 2 a ... 17/9
350-0-350 v 80 mA, 6.3 v 2 a, 4 v 2.5 a ... 14/11
250-0-250 v 100 mA, 6.3 v 4 a, 5 v 3 a ... 23/9
300-0-300 v 100 mA, 6.3 v 4 v 4 a, c.t. 0-4-5 v 3 a ... 23/9
350-0-350 v 100 mA, 6.3 v 4 v 4 a, c.t. 0-4-5 v 3 a ... 23/9
350-0-350 v 150 mA, 6.3 v 4 a, 5 v 3 a ... 29/11
350-0-350 v 150 mA, 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a ... 29/11

FULLY SHROUDED UPRIGHT
250-0-250 v 60 mA, 6.3 v 2 a, 5 v 2 a, Midget type 2-1-3-3in. ... 16/9
350-0-350 v 70 mA, 6.3 v 2 a, 5 v 2 a ... 18/9
250-0-250 v 100 mA, 0-4-6.3 v 4 a, 0-4-5 v 3 a ... 25/9
250-0-250 v 100 mA, 6.3 v 6 a, 5 v 9 a, for R1355 conversion ... 29/9
300-0-300 v 100 mA, 0-4-6.3 v 4 a, 0-4-5 v 3 a ... 25/9
350-0-350 v 100 mA, 0-4-6.3 v 4 a, 0-4-5 v 3 a ... 25/9
350-0-350 v 150 mA, 6.3 v 4 a, 5 v 3 a ... 33/9
350-0-350 v 160 mA, 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a ... 45/9
350-0-350 v 200 mA, 6.3 v 6 a, 4 v 8 a, 0-4-5 v 2 a, 4 v 3 a, for Electronic Eng. Television ... 67/6
425-0-425 v 200 mA, 6.3 v 4 v 4 a, c.t. 6.3 v 4 a, c.t. 0-4-5 v 3 a, suitable Williamson Amplifier, etc. ... 51/-
450-0-450 v 250 mA, 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a ... 65/6

ELIMINATOR TRANSFORMERS
Primaries 200-250 v 50 c/s, 120 v 40 mA 7/9
120 v 40 mA, 6-0-6 v 1 amp ... 14/9
50 v 10 mA, 6-0-6 v 250 mA ... 8/11

EX-GOVT. ITEMS (EX EQUIP.). Mains Trans, 230 v Input, Output 350-0-350 v 160 mA, 6.3 v 6 a, 5 v 3 a, 27/6. Motor Generators, 6 v Input, Output 180 v D.C., 5/9. Auto Trans., 15-10-5-0-195-215-235 v 150 watts, 17/6.

COAXIAL CABLE. 75 ohms, in. 9d. yard. Twin Screened Feeder, 9d. yard.

SELENIUM RECTIFIERS. 230 v 50 mA, H.W. (small), 5/9. 120 v 40 mA, H.W. (small), 3/11. 250 v 1 a H.W., 2/11. 250 v 1 a H.W., 3/11. 612 v 1 a H.W., 4/6. 612 v 2 a F.W. (bridge), 9/9. 612 v 4 a F.W. (bridge), 17/9. 612 v 6 a F.W. (bridge), 22/9.

CHASSIS. 16 s.w.g. Unclipped Aluminium Receiver Type 6 x 3 1/2 x 1 1/2 in., 2/6; 7 1/4 x 4 1/2 in., 3/5; 10 x 5 1/2 x 2 in., 3/9; 11 x 6 x 2 1/2 in., 4/3; 12 x 8 x 2 1/2 in., 5/3; 16 x 8 x 2 1/2 in., 7/6; 20 x 8 x 2 1/2 in., 8/11. Amplifier type (4 sided), 12 x 8 x 2 1/2 in., 7/11; 16 x 8 x 2 1/2 in., 10/11; 14 x 10 x 3 in., 13/6; 20 x 8 x 2 1/2 in., 13/6.

SILVER MICA CONDENSERS. 5, 10, 15, 20, 25, 30, 35, 40, 50, 100, 120, 150, 200, 300, 360, 400, 470, 500, 1,000 (100 mtd.), 2,000 pfd. (.002 mtd.), 5d. each, 3/9 doz., one type.

VOLUME CONTROLS with long (in.) spindles, all values, less switch, 2/8, with S.P. switch, 3/8.

WIRE WOUND POTS. 20 ohms, 5K, 20K, 25K, 50K (medium length spindles), 1/11.

P.M. SPEAKERS. All 2-3 ohms, 5 in. Goodmans, 14/9. 6 in. Elac., 14/11. 6 in. Plessey with 5,000 ohm trans., 14/11; 8 in. Plessey, 15/9. 8 in. R.A. Heavy Duty 18 in. 10 in. Rola 29/6. 10 in. Plessey, 18/6. 10 in. R.A., 31/-. 10 in. Rola with 5,000 ohm output trans., 31/9; 12 in. Traxov, 49/9.

M.E. SPEAKERS. All 2-3 ohms, 6 in. Rola field 700 ohms, 11/9. 10 in. R.A. field 1,000 ohms, 23/9. 10 in. R.A. field 1,500 ohms, 23/9.

EX-GOVT. TRANSMITTER RECEIVERS. Type TR8D. Complete with all valves. Only 47/6, plus 5/- Carr.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s primaries; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/6; 0-2-4-5-6.3 v 4 a, 16/9; 12 v 3 a or 24 v 1.5 a, 17/6.

CHARGER TRANSFORMERS
All with 200-250 v 50 c/s. Primaries: 0-9-15 v 1.5 a, 14/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 6 a, 22/9; 0-4-9-15-24 v 3 a, 22/9.

SMOOTHING CHOKES
250 mA 8-10 H 200 ohms, Potted ... 16/9
250 mA 3-5 H 50 ohms ... 11/9
100 mA 10 H 175 ohms ... 6/11
80 mA 10 H 350 ohms ... 5/6
60 mA 10 H 400 ohms ... 4/11

E.I.T. TRANSFORMERS
2,500 v 5 mA, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a, for VCR97, VCR517, ACR2X, etc. 35/-

OUTPUT TRANSFORMERS

Midget Battery Pentode 66.1 for 35A, etc. to 31A ... 3/9
Small Pentode, 5,000 Ω to 31A ... 3/9
Small Pentode, 8,000 Ω to 31A ... 3/9
Standard Pentode, 5,000 Ω to 31A ... 4/9
Standard Pentode, 8,000 Ω to 31A ... 4/9
Multi-ratio 40 mA, 50 Ω, 45:1, 60:1, 80:1, Class B Push-Pull ... 5/6
Push-Pull 10-12 Watts 6V6 to 31A or 15L2 ... 15/9
Push-pull 10-12 Watts to match 6V6 to 3-5-8 or 15L2 ... 16/9
Push-Pull 15-18 Watts to match 6L6, etc. to 31A or 15L2 Speaker ... 22/9
Push-Pull 20 Watts, sectionally wound, 6L6, KT66, etc. to 3, or 15L2 47/9
Williamson type exact to Author's spec. ... 85/-

HANNEY of BATH offers:—
PRACTICAL TELEVISION "SUPER VISOR"

Kit of 77 T.C.C. Condensers, with C.9 and clips	£ 8. 4.
Kit of 93 Erie resistors to specification	6. 4.
Kit of 4 Wire-around Potentiometers to specification	2. 14. 0
Kit of 7 Erie Carbon Potentiometers	1. 15. 0
Kit of Allen Coils	2. 4. 6
Allen Scan Coils, type DC.300 C	1. 19. 6
Allen Line Linearity Control, type GL.16	7. 6
Allen Width Control and Flywheel Adjustment (2 at 7/6)	1. 12. 6
Allen Smoothing Choke, type SC.312	1. 15. 0
Allen Focus Coil, type FC.302	9. 0
Allen Speaker Transformer, 7,000 3 ohms, type OP.117 ...	1. 10. 0
Allen Mains Transformer, type AT.310	1. 1. 0
Denco Frame Output Transformer, type WA.FMA1	2. 9. 0
Danco Line Output Transformer, type WA.LOT1	13. 0
McMardo Valve Holders, type BM7 U (13 required at 1/5)	2. 9. 9
" " " type BM7 U with screen (one)	0. 0. 0
" " " type BM9 UD (two at 1/5)	9. 9
" " " type BM9 UB (one at 2/6)	6. 0
" " " type BM12 U1 (one at 2/6)	1. 10. 0
" " " type BBU (two at 1/5)	1. 3. 0
Aerial Plug and Socket, Belling-Lee, type L733	2. 0. 0
Clix Mains Adjustment with 2 amp fuse	2. 11. 6
Complete Denco Chassis Kit, brackets, clips, etc.	2. 11. 6
Westinghouse, type WX6 rectifier	6. 0
Westinghouse, type WG4A germanium diode	3. 9. 0
4 Engraved Knobs, Ivory or walnut (1 6 each)	2. 2. 0
W.B. Stentorian 10in. speaker	19. 6
English Electric 16in. double D mask to fit T.901 tube ...	6. 2
" " Perspex filter to fit above mask	5. 0
" " anti-rain ring	
" " plastic tube sheath	
Elac Ion Trap Magnet, type IT.8 for T.901 tube	

COMPLETE KIT, EXACTLY TO SPECIFICATION.
 AS DETAILED ABOVE (sistofex, wire, nuts, bolts, washers and solder tags included) £40 0 0
 English Electric T.901 Picture Tube 22 4 10
 Carriage, packing and insurance on the above tube 10 0

Send 6d. in stamps for our General List, which contains details of Components for Viewmaster, Teleking, Magnaview, Super-Visor, Lynx, Williamson Amplifier and most "P.T." and "P.W." Designs. Please add postage to all orders under 42.

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH. Tel. 3811

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

- T/V TECHNOLOGY
- ADVANCED SHORT-WAVE RADIO
- RADIO ENGINEERING
- RADIO SERVICE ENGINEERING
- RADAR
- ELEMENTARY ELECTRONICS

I.C.S. will also coach you for the following examinations:—

- B.I.R.E.; P.M.G. Certificate for Wireless Operators;
- Radio Servicing Certificate (R.T.E.B.);
- C. & G. Telecommunications, etc., etc.

DON'T DELAY—WRITE TO-DAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful. **Reduced terms for H.M. Forces.**

Dept. 170D, I.C.S., 71, Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS,
 (Dept. 170D), International Buildings, Kingsway,
 London, W.C.2.

Please send booklet on.....

Name..... Age.....
 (Block letters, please)

Address.....



CLYDESDALE
 Bargains in Ex-Services Radio and Electronic Equipment

PRICES SLASHED

RECEIVER UNIT TYPE 25

Ref. 10P/IL part of the TR1196 equipment. Frequency range. 4.3-6.7 Mc/s.

Valves: 2 VR53 (EF39), 2 VR56 (EF36), VR55 (EBC33), VR57 (EK32), 2 IFT 460 Kc/s, plus various microdensers, mic. and output transformers, pots., condensers, resistors, etc., connections brought to 10 pin Jones type chassis plug. Circuits are provided in the unit, which is totally enclosed in case. 8 1/2 x 6 1/4 x 6 1/2 in. Would make the basis of an All Wave Receiver, required tuning pack and power supply.

Price **35/-**

Ask for POST PAID
 No. P/H299

BC-625-A TRANSMITTER CHASSIS

Part of SCR-522. (U.S.A. made).

Less valves, partly stripped by the M.O.S., also less crystal switch and crystals, R.F. section in good order, separate modulation Transformer and Choke supplied, dim.: 15 1/2 x 7 1/2 x 6 1/2 in.

ASK FOR CARRIAGE PAID
19/- Each
 P/E752 Circuit 1/6

CABLE

6 core Rubber covered P/H540A, 8d. per yard. 2 core Metal braided P/H541, 4d. per yard. Post 3d. extra.
 1/2-mile Reels (880 yds.) 23 swg. P.V.C. Covered signal corps wire P/H855. 25/- per reel.

Ceramic Wafer Rotary Wavechange Switch. 3 bank each single pole, 5 ways. Overall length 8 x 2 1/2 in. wide.

ASK FOR POST PAID
3/- Each 6d. EXTRA
 P/E120

Order direct from:
CLYDESDALE SUPPLY CO. LTD.
 2, Bridge St., Glasgow, C.5. Phone: SOUTH 2706/9
 Visit our Branches in Scotland, England and N. Ireland.

BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

- Selective tuning.
- Acorn 'ow drain valve.
- Loud clear tone.
- Long range.
- No earth.
- Short aerial, 2ft.
- Welded steel case.
- Easy to assemble.
- All parts for this set are sold separately

FOR **30/-**
 POST FREE



MAIL ORDER ONLY

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Component Price List.

R. C. S. PRODUCTS

11, OLIVER ROAD, LONDON, E.17

What It Means

However, it would not be correct to reject "efficiency modulation" systems on the grounds of "low efficiency" without further consideration of all the factors. In the first place, the term "efficiency modulation" really means that the efficiency of the modulated stage varies with modulation. In fact, under 100 per cent. modulation the efficiency varies from full Class C efficiency down to zero efficiency. By this means, the 100 per cent. modulation condition in which the R.F. output swings from peak output to zero output is achieved. What is also to be appreciated is that the D.C. input to the modulated stage *also* varies with modulation. Thus, in an amplitude-modulated stage the instantaneous peak output on 100 per cent. modulation peaks is actually *four times* the R.F. carrier level. In an efficiency-modulated stage the efficiency is doubled and the D.C. input is doubled on modulation peaks, thus achieving the instantaneous fourfold increase on modulation peaks. This *immediately* gives the clue to the carrier-operating conditions of an efficiency-modulated stage. The *unmodulated* ("carrier") condition is given by running at *half* the normal Class C efficiency and at *half* the normal Class C input. Thus a P.A. stage capable of 100 watts input at 66 per cent. efficiency for C.W. conditions would be operated at 50 watts input and 33 per cent. efficiency under efficiency modulation conditions with the same H.T. supply. Thus the "efficiency modulated" stage gives only one quarter of the R.F. carrier that can be obtained under Class C telegraphy operation. Providing this limitation is realised, efficiency modulation systems are capable of good quality modulation. In fact, efficiency modulation systems are quite widely employed, particularly in television transmitters for the Video channel. Trouble usually arises in amateur practice from the delusion that increasing carrier output by deviating from the above efficiency modulation conditions will give greater "efficiency." One cannot, of course, obtain something for nothing, and the modulated output of an efficiency modulated stage is obtained by sacrificing the standing carrier efficiency in the unmodulated condition. Thus, if we attempt to modulate a stage running at its full Class C efficiency of 66 per cent., we can only modulate *downwards*, thus creating appalling distortion. The absurdity of modulating to an efficiency of "132 per cent." on positive peaks is obvious.

Three Systems

Three main systems of simple efficiency modulation are used. These are grid modulation, screen modulation, and suppressor modulation. Screen modulation is the most popular method in amateur use, and is somewhat easier to adjust than grid modulation. However, as grid modulation can also be used with triodes, some pointers on adjustment are in order. Similar considerations apply also to screen and suppressor modulation.

For successful grid modulation it is, of course, essential that no high impedance at audio frequency is included in the grid return path. If a grid leak is employed it should have a condenser of some .1 μ F connected across it so as to provide a low-impedance path to audio frequencies. In grid modulated stages it is advisable that the bias be supplied mainly from a fixed battery or a bias pack of low impedance. In any case it is essential that the bias voltage be

readily adjustable. Further, owing to the wide variations of grid impedance, a triode modulator or a pentode with heavy negative feedback is advisable in the modulator. A further refinement is to resistance load the secondary of the modulation transformer. If the secondary is loaded with some 10,000 ohms, and the transformer arranged to match this load to the modulator, it will be found easier to obtain good modulation behaviour. A final refinement is to load the grid R.F. tank circuit with some 15,000 ohms of resistance to improve the R.F. driver regulation.

Setting-up

With the above precautions a start can be made upon modulation adjustment. Initial setting up can very well be made using an artificial aerial load to the transmitter, as until good modulation is achieved it is poor "ham spirit" to inflict tests upon the air. It is, in fact, surprising that advocates of some modulation systems capable, when wrongly adjusted, of causing the most excruciating distortion, do not advise the use of preliminary artificial aerial tests to enable the "feel" of adjustments to be obtained without radiating interference. However, whether a radiating aerial or an artificial aerial is in use, a useful guide will be given by an R.F. ammeter indicating R.F. output current. Starting with normal Class C telegraphy conditions, the first step is to increase the D.C. grid bias to some two and a-half to three times the usual Class C value. The R.F. drive should then be adjusted until the R.F. ammeter indicates approximately half the reading obtained under Class C telegraphy conditions. Under these

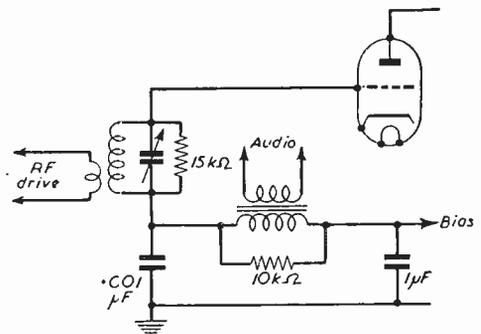


Fig. 2.—Typical values in a grid modulated system.

conditions the P.A. should be drawing approximately half its usual current. In any case one can now apply audio to the modulator, and the audio should be increased until upward kicks occur on the R.F. ammeter. If downward kicks appear on the R.F. ammeter, either the D.C. grid bias is too low or the R.F. drive is too high. Similar indication will be given by the P.A. plate current meter. Upward plate current kicks indicate too high D.C. bias, and downward kicks indicate too little D.C. grid bias. The D.C. grid bias should accordingly be adjusted in accordance with the plate meter indications until the plate meter is nearly steady under modulation. The R.F. drive may then be increased, until plate kicks again occur, and the bias can be adjusted to minimise the plate kicks. However, very high grid bias will necessitate a high R.F. drive, so that practically some three to five times cut-off bias is employed

with grid modulation. When a good depth of modulation can be achieved, the aerial coupling to the P.A. should be carefully adjusted. The final aim is to achieve a reasonable approach to the state in which the R.F. aerial current is approximately half that of the Class C telegraphy condition, and the D.C. plate input is also approximately half. D.C. bias and drive should be adjusted so that little or no plate current "kicking" occurs on modulation peaks. The difficulty with grid modulation adjustment is that both audio and R.F. are applied to the grid. Thus any adjustment of D.C. bias requires a corresponding change in R.F. drive.

With screen and suppressor modulation the same care has to be taken over the R.F. loading of the P.A., as distortionless modulation again depends very much upon the R.F. loading conditions. However, adjustment is very much easier, as R.F. and audio voltages are applied to different electrodes. Thus the R.F. drive adjustments do not interact very much upon the audio adjustments. For suppressor modulation a negative bias (usually specified by the makers) is applied to the suppressor. Here, upward plate kicks on modulation indicate too high suppressor bias, while downward kicks indicate too low a bias. In the case of *screen* modulation the screen voltage is generally reduced to half the value used for Class C telegraphy operation. For screen modulated stages, upward plate kicks indicate too low a screen potential, and downward plate kicks indicate too high a screen potential. Suppressor and screen modulated stages require care in drive adjustment, and generally drive must be reduced below the normal Class C telegraphy value. In all these systems the use of a cathode-ray modulation indicator is invaluable, as the precise effect of adjustments can be readily discerned. The cathode-ray tube allows of trouble-free adjustment for optimum modulation percentage and R.F. output. This is difficult to achieve in any other way except by trial and error methods.

CORONET A.C. FOUR

(Continued from page 689)

signal should be fed into the grid of V2. The lead to the cap should, of course, be removed whilst this is done. The output from the generator should be kept as low as possible to keep down the A.V.C. action, and the volume control of the receiver should also be kept well down so that any changes are more easily heard in the speaker. Carefully adjust the two cores on I.F.T.2 for maximum response and then go from one to the other until both are exactly peaked. There will be slight pulling or changes made in one as the other is altered, but eventually they will both be so adjusted that the slightest movement on either core will result in a weakening of the signal.

Next, clip the generator output leads on to the grid socket of V1 and disconnect the blue lead from the oscillator grid. This is not an essential procedure, but many constructors find that the I.F.T.s may be more accurately aligned if the oscillator section of the mixer valve is rendered inoperative. Any other method may, of course, be used to stop the triode section from oscillating. Peak the two trimmers on I.F.T.1 in the same manner as before and when finally adjusted to maximum, turn one of the cores about a quarter of a turn forwards and the other the same distance in the opposite direction.

Finally, with so much trouble to take, are "efficiency modulation" systems worth while? Taking the case of the owner of a 150-watt station, under anode modulation conditions, an input of 150 watts would give some 100 watts of R.F. carrier. A stage running at 150 watts input under efficiency modulation conditions would give a carrier output of 50 watts. Ideally then only some 3 db. or half an "S Point" of signal strength would be sacrificed. Moreover, the modulator would only be a question of a tetrode capable of some five to eight watts of audio output. The saving over a high level anode modulator would thus be appreciable. However, it would be necessary to use a P.A. stage valve capable of dissipating 100 watts on the anode, and furthermore such a valve would then be capable of an input of some 300 watts under Class C telegraphy conditions. The economy in audio equipment is thus obtained by having to provide for a P.A. valve capable of high peak R.F. output. This admittedly is cheaper than a high output audio modulator.

A further point is that where only *one* power pack is available to drive both P.A. and modulator, the final R.F. output available is about the same for an efficiency modulated stage taking the full power of the pack, and an anode-modulated stage and high level anode modulator sharing the full output of the power pack. It is thus clear that while "efficiency modulation" systems do not provide "something for nothing," there are certain attractive features. Perhaps their chief attraction is for the C.W. man who occasionally requires 'phone for local "rag-chews." The dyed-in-the-wool high-power 'phone operator is certain to want the utmost R.F. output possible, and will accordingly use high-level anode modulation. For obvious reasons, no reference is made to certain "high efficiency" types of "efficiency modulation" systems, which, in skilled hands, can produce modulated R.F. at similar efficiencies to an anode modulated stage at the cost of greater complexity and some difficulty in adjustment.


Tuning Coil Adjustments

Leaving the generator connected to the aerial input, reconnect the oscillator coil or do whatever is necessary to make the triode section function again, and then turn the tuning condenser to the low end of the medium-waveband and set the signal generator to, say, the Light programme. Set the signal generator to this wavelength or frequency, and adjust the oscillator pre-set condenser for maximum results. Then adjust the aerial pre-set condenser and in this way going from one to the other, obtain maximum performance. Then turn to the top of the medium-waveband and adjust the core of the oscillator medium-wave coil, then the core of the aerial medium-wave coil. This is the procedure on the remaining two bands—the pre-set condenser is adjusted at the bottom (low wavelength—high frequency) end of the dial, and the core at the top—high wavelength or low frequency. It will be found that there is a balance between the inductance of the coil, which is, of course, governed by the position of the iron-dust core, and the pre-set condenser, which will enable the dial to remain correct at all settings and also for maximum performance to be obtained right through the tuning range. If the core is not in the correct position, or the pre-set condenser is wrongly adjusted, the performance will vary at different settings.

FLEX AND CABLES

Twin twisted P.V.C. flex 14/36. crystal colour	3d.
per 100 yds.	19 6
Push back wire 7 0076 mauve, white, blue, green	2-1.
per yard	6d.
Twin ribbon feeder 30012	1-
Coaxial cable 7512 7 0076	3d.
Twin flat 14 0076 P.V.C. black	3d.
per 110 yards coil 21-	6d.
Screened cable, single core	7d.
Screened cable, twin core	7d.

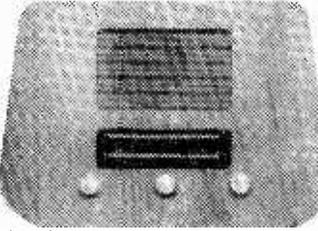"SWAN" RADIO CABINET BUILD A RADIO IN THIS UP TO DATE CABINET



A modern looking radio cabinet complete with drilled chassis; dial drive and drum; back plate; dial; spring; pointer; Size 15 1/2 in. x 11 in. x 5 in.
 Price £1/16 6. Post and Packing, 2/-.
 We can supply a circuit diagram with all instructions for constructing a 3-valve plus metal rectifier T.R.F. receiver to operate on long and medium wave bands for 1 & 2.
 The complete kit can be supplied at £6 6 - plus packing and post, 2 6.

CONDENSERS CAN TYPES

Brand New Stocks.

Dubilier 8 mfd. 450v.	each	1 3
T.M.C. 16 mfd. 450v.	...	2 9
T.C.C. 16 mfd. 450v.	...	3 3
T.C.C. 16 mfd. 350v.	...	2 9
B.E.C. 15 x 16 mfd. 350v.	...	2 9
Dubilier 24 x 16 mfd. 350v.	...	5 9
T.C.C. 16 x 8 mfd. 350v.	...	4 -
T.C.C. 12 x 4 mfd. 450v.	...	3 -
Dubilier 32 x 16 mfd.	...	3 3
B.E.C. 32 mfd. 350v.	...	1 9
B.E.C. 8 mfd. 450v.	...	3 4
B.E.C. 32 x 32 mfd. 450v.	...	1 11
B.E.C. 32 x 32 x 8 mfd. 350v.	...	7 -
B.E.C. 32 x 32 mfd. 350v. 25 mfd. 25v.	...	5 3
Dubilier 32 x 8 mfd. 350v.	...	3 9
Hunts 16 mfd. 450v.	...	3 3
Dubilier 8 x 8 mfd. 350v.	...	3 3
T.C.C. 24 x 8 mfd. 350v.	...	3 6
T.C.C. 24 mfd. 350v.	...	3 -

CARDBOARD TUBULAR WIRE ENDS

25 mfd. 25v.	each	1 9
8 mfd. 450v.	...	2 -
16 mfd. 500v.	...	3 3
50 mfd. 50v.	...	2 3
8 mfd. 500v.	...	2 3
50 mfd. 12v.	...	1 8
4 Position rotary switch 20 amp.	...	3 6
Battery Charger Bulldog clips	...	6d.
465 ke.s I.F. Transformers per pair	...	6 9
Local Valve Holders Percolin each	...	3 4.
Condenser Clips, all sizes	...	3d.
2 Ratio Output Transformer...	...	1 11
1 mm. Sliding, bright colours yard Concordia Bell Transformer.	...	1d.
3v., 5v., 8v., 1 amp.	each	7 6
Reliance Choke 20 H. 250Ω	...	6 -
60 m a	...	1-
H.F. File Wound Chokes	...	6-
Midget Choke 25 H. 500 m a.	...	15 1.
Ceramic Coil Formers, in. dia.	...	2-
1in. long, 4 ribs	...	5d.
Dial Bulbs, small B.C. type, 6.5v. 3a.	...	6d.
Vibrators, 6v and 12v. 4-pin	...	6d.
U.X. type	...	6 6

VALVES
GUARANTEED NEW AND BOXED.

OZ4	6-	6V6G	8-	HL133DD	8 6
1A5GT	7 6	6V6GT	8 -	KT33C	11 -
1C5GT	8 -	6X4	8 -	KTW1	8 9
(DL75)	8 -	6X5GT	7 6	KTZ41	6 9
1G6GT	6 9	6Z5	7 6	KTZ63	3 6
1L4	7 6	7B7	8 6	MH4	5 6
1LD5	6 9	7C5	8 6	MS PEN	5 6
1K5	8 -	7C6	8 6	(SP4)	5 -
1S4	8 -	7H7	8 6	OM9	9 -
1S5	8 -	7R7	8 6	Pen25	8 -
1T4	8 -	7S7	8 6	Pen36	8 -
1U5	10 -	7Y4	8 6	PEN220A	4 9
215SG	4 -	80	8 9	PL82	11 6
2X2	5 3	807	8 9	PY82	11 6
3A4	9 -	8D2	2 9	PY80	11 6
3Q4	9 -	894	2 -	RL2	12 -
3D6	8 -	955	4 9	SP4B	13 -
3S4	9 6	956	3 6	U22	9 -
3V4	9 -	9D2	3 -	UB41	11 6
4D1	3 -	9001	6 3	UBC41	11 6
32	8 -	9002	6 3	UCH42	11 6
5U4G	9 6	923	6 3	UF41	12 -
5V3GT	8 -	9004	6 3	UQ9	9 -
5Z3	8 6	12A6	6 9	UY41	10 -
5Z4G	8 6	12A7T	9 6	VR21	3 6
6A8G	10 6	12C8	9 -	VR35	6 6
6AC7	6 6	12H6	5 -	ER39	7 6
6AG5	8 -	12J5	6 -	EB34	2 6
6AK5	9 -	12K7	10 -	EBC33	3 -
6AL5	8 -	12K8	9 -	EF36	7 -
6AM6	8 -	12S67	5 6	EK32	8 -
6AT6	7 6	12S17	7 6	SP61	3 9
6B4	10 6	12S77	6 6	SP41	3 6
6B8	4 -	12SR7	7 6	EP3	3 9
6BE8	11 -	12SQ7	9 -	EP50	6 6
6C4	8 -	12Q7	9 -	EP50 Svl	8 -
6C5	2 6	12Y4	7 6	EA50	2 -
6D6	2 3	12Z3	8 6	VR116	4 -
6E6	7 6	15D2	4 -	DL4	4 -
6F6G	8 6	25A6G	9 -	EP8	6 6
6F6M	7 6	25L6GT	8 6	VR137	5 -
6FRG	7 -	25Z4G	9 -	VR150 30	5 -
6G6G	6 6	35L6GT	9 6	FL32	0 -
6H6	6 6	35Z4GT	9 -	KT44	7 6
6J5G	5 6	50L6GT	8 6	VT105	4 -
6J5M	6 -	AC6Pen	5 6	6R7	8 -
6J7M	7 6	CRP72	2 -	VT501	8 -
6K7G	6 6	CV71	1 -	VP23	8 -
6K8G	9 6	DD13	4 6	VU39	3 6
6K8GT	9 6	DDL4	4 -	VU111	8 6
6L6	9 -	DH74M	9 -	VU120A	3 6
6L6G	10 6	DH81	10 -	VU133	3 6
6L7M	7 6	DI74M	9 6	W77	8 6
6Q7	9 -	ED41	10 -	XS6	2 -
6Q7G	9 6	ERC41	11 -	HD21	6 -
6Q7GT	9 6	ECH42	10 6	PL35	9 6
6SA7GT	9 -	ECL40	11 6	EL50	10 -
6SG7	8 9	EF35	7 -	HL1320	6 -
6SH7	6 -	EF41	10 -	HL21DD	6 -
6SJ7GT	9 6	EF60	11 6	106	6 -
6SK7	6 9	EL41	11 -	Q122B	8 -
6SL7	8 6	EM31	9 -	Z21	8 6
6SN7GT	10 -	EY31	12 -	811A	9 -
6SQ7	8 -	943	7 9	W21	8 -
6SR7	8 -	HL23DD	8 -	77	8 -
6U5	8 6	HL41	8 -	18	8 -

MAINS TRANSFORMERS
 3-way mounting type

MT1. Standard tapped Primary, 245 250v.	Each	1 6
Secondary's 250-0-250v. 80 m. a., 6.3v. 4 amp. 5v. 2 amp. Both filament windings tapped at volts.	...	17 6
MT2. As above with 350-0-350v. 80 m. a. H.T. winding.	...	17 6
MT3. Standard tapped primary 200 250v.	...	17 6
Secondary 30v. 2 amps. with tapings at: 3v., 4v., 5v., 6v., 8v., 9v., 10v., 12v., 15v., 18v., 20v., 24v.	...	17 6
AC TO 10-120-200-230-250v. 160 watts	...	17 6


EX. GOVERNMENT VOLUME CONTROLS

500Ω, 800Ω, 10 KΩ, 20KΩ, 25 KΩ, 50 KΩ, 100 KΩ, meg.Ω, 1 meg.Ω, 2 meg.Ω	each	1/-
--	------	-----

WIRE WOUND CONTROLS

Pre-set types, 500Ω, 200Ω, 1,000Ω	each	1/9
Standard 5Ω, 200Ω, 1,000Ω, 2,000Ω, 5,000Ω, 10 KΩ, 20 KΩ, 25 KΩ, 50 KΩ	...	2/-
Headphones, High Resistance	...	10/-
Headphones, Low Resistance	...	7 6
Chr.	1 6
Yaxley Switch 1-pole 3-way...	...	1 -
Yaxley Switch, 2-pole 3-way...	...	6d.
Multicore Solder ... per Packet	...	3d.
P.K. Self-tapping Screws No. 4 1/2 in.	doz.	3d.
Rubber Grommets assorted	...	6d.
Microphone Transformer 60-1 ratio	each	1 6
Paper Block Condenser 2 mfd. 1,000v.	...	1 -
Grid Caps Octal Push-on type doz.	...	6d.
Screened Grid Caps. British and U.S.A.	each	3d.
Yaxley Switch, 4-pole 3-way...	...	2 6
Yaxley Switch, 4-pole 2-way...	...	1 9
Electrolytic Block Condenser, 10 4 mfd. 500v.	...	1 6
Crystal Diode	...	1 8
Bridge Rectifier, 12v. 3 a.	...	13 9
Multi-core Solder ... per Packet	...	2 9
T.R.F. Switch	...	1 -
Standard Iron Element, 450 w.	...	1 8
Hydrometer, brand new in wood case	...	8 6
Balkin Toggle Switch I.P.D.T.	...	2 3
Extension Speaker Vcl. Control	...	1 3
Throat Microphones, 2 in box box	...	1 6
G.P.O. type Jack Plug	each	1 3
Car Push with Light	...	1 3
Car Bulb 6v. 18 watt	...	1 3
Car Bulb Suppressors	...	1 3

LOUDSPEAKER CABINETS

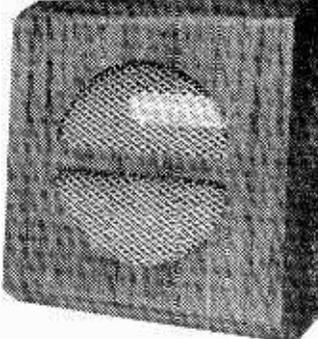

Available for 6 1/2 in. and 8 in. speaker units. Polished walnut finish. A very attractive cabinet, at quarter of to-day's prices. Price, 6 1/2 in. type cabinet, 15 6 each. 8 in. ... 19 6. See under Loud-speakers for suitable speakers units.

LOUDSPEAKER UNITS

3in. Plessey round type for portables	Each	12 9
Elac 3 1/2 in. square type 2 1/2 to 3 1/2	...	13 6
5in. Units by Lectra and Elac	...	12 3
Truvox 6 1/2 in. Wafer Speaker. Only 1 1/2 in. deep	...	20 -
6 1/2 in. Elac with Output Transformer	...	16 6
8 in. Units by Plessey and Elac	...	15 -

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1 6; above 40 - 2 -, unless otherwise stated. Minimum C.O.D. fee and postage, 2 3. Illustrated Catalogue 6d. in stamps.

ALPHA RADIO SUPPLY CO.
5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS, 1.

THE POCKET LOUDSPEAKER SET

Using our clear drawings and instructions you can build a midset loudspeaker receiver small enough to fit in the jacket pocket. This receiver is fully self-contained—no aerial, earth, or external power supply being required. The midset batteries used are of the new layer type specially produced by a famous British maker for this class of receiver. Only one single-gang midset variable condenser is used for tuning, and the receiver requires no alignment. The midset components chosen are current British production, not surplus or foreign. Instructions and Drawings, including Theoretical Circuit and Point-to-Point Wiring Diagram.

PRICE 3/6 POST FREE

This offer applies only to Gt. Britain, Irish Republic and Northern Ireland.

SWIFT RADIO

102, BATH RD., WILLSBRIDGE, Nr. BRISTOL

Orders by post only.

"ADCOLA" SOLDERING INSTRUMENTS

Regd. Trade Mark



Regd. Design No. 800302

(British, U.S. and Foreign Patents)

For Wireless and Television Assembly

The advanced design of the Adcola Instruments meets the modern requirements of Television, Telecommunication and Radar Engineers

SUPPLIED FOR ALL VOLT RANGES FROM 67v. to 230/250v
 3/16in. dia. Bit. Standard Model ... 25/6
 1/4in. dia. Bit. Standard Model ... 28/-
 3/16in. dia. Detachable Bit. Model... 33/6

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED

GENERAL OFFICES & WORKS: CRANMER COURT, CLAPHAM HIGH STREET, LONDON, S.W.4. (MACaulay 4272)

10% DISCOUNT !!!

off the price of non-proprietary goods IF YOUR ORDER EXCEEDS £1. To obtain maximum benefit, send 3d. for list.

VALUES YOU CAN TRUST!

A.—Makers' Cartons. B.—Plain or Service Cartons.
 Type A B Type A B Type A B
 2C25 4/9 4/3 6K7CT 6/6 5/9 EB24 — 2/6
 6AM6 — 10/8 6K7G — 10/9 EB91 — 7/9
 4F64 9/6 — 6K7CT 12/8 10/9 EF54 — 7/6
 6H6 5/0 4/6 68K7 7/3 — EF92 — 8/9
 6J5CT 5/9 — 6V6GT 11/6 — KTW1 — 8/6
 6J5 — 11/0 6V64 — 9/6 KTZ1 — 8/6
 6J7G — 8/6 12H6 — 2/9 KTZ3 — 7/0
 6K6GT 8/6 954 3/6 — KK34 2/3 —
 6K7 7/9 8/9 7H6 2/8 — MU11 3/6 —
 6K7G 8/9 — EA50 — 5/0 VP133 — 6/6

SPECIAL.—6K7 (metal) slightly soiled and ex-imp. condition. Tested. 4/9.

Jones Plugs and Sockets. 10-w. 10d. a pair. Amphenol Valveholders. 1in. 9d.; 8/7c. 11d. Ceramic do. 8/1c. 6d.; 7-pin for KK34, etc. 1/3. Metal tube 0.25in. 8/1c. 6d.; 0.1+0.1in. 4/1c. 5d. Bathbubs 5d. Card Tube. 1. 1/4in. 45w. 3/8 doz. REED & FORD, 2A, BURNLEY ROAD, AINSDALE, SOUTHPORT.

Fidelia

HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10

Hand built high quality radiogram chassis at economic price. 10 valve, model illustrated £38-8-6. De-Luxe 9 valve model £24-6-6. 7 valve £21-12-0. 5 valve £23-18-4.

Technical data sheets free.

Electro Acoustic Developments, 2, Amburst Road, Telecoms Cliffs, Sussex.

WATERLOO RADIO

(Waterloo Bridge Roundabout)
 35, TENISON WAY, LONDON, S.E.1.
 Tel.: WAT 3014.

GERMANIUM DIODES

—Wire caps. 2s. each, 11 for 20s.

VALVES—RK34 2C34, VR78/D1, 2/6; 5 for 10-; 807's, 11/6; 6CH6's (Video amp.), 7/6; 3 for 20-; CV138/6AM6, 8D3, Z71, 6/6; 813's, 70/-; 829B, 72/6; 8012B's, 11/6; 2 for 20-; TX Condensers, Type 161C, ZAL109, 3.000V, wks. 140-; 4 mfd., NEW, PACKED, 2 to a crate, 30+ pair, Carriage 3/6.

METAL RECTIFIERS—H.W. R.M.I. 125v., 2 - 50 mfd. 50v., 2 6; 8 mfd. 450v., 1/9; RM3, 125v., 120 m.A., 5/3; RM4, 250v., 25 m.A., 5/6.

ELECTROLYTICS—25 mfd. 25v., 50 mfd. 12v., 2 - 50 mfd. 50v., 2 6; 8 mfd. 450v., 1/9; 32 mfd. 500v., 5/6; 8+8 mfd. 450v., 4/-; 8+16 mfd. 450v., 4/3; 8+16 mfd. 500v., 5/3; 16+16—450v., 5/3; 16+24—450v., 5/3; 32+32 mfd. 275v., 2/9; 32+32 450v., 5/3; 16+32+32—350v., 5/6.

LOUDSPEAKERS—3in., 5in., 6in., 14/6; 8in., 10in., 22-. Post 2-. And many other fine radio and television bargains. Overseas enquiries invited.

WILCO ELECTRONICS

P.M. SPEAKERS in cases, ideal for extension speakers. 6in., 30-; 5in., 17/6. Post 2/6.
 A.C. 0/300, 25/-; 2in. Flush Electrostatic, 0/2,000, 40/-; All Meters, Post 1/-.
RECEIVERS R1355, as specified, for "Inexpensive Television". In original packing, as new, with 11 valves. 38/6. Carr. 7/6.
MILLIAMMETERS—2in. Flush M.C.C. 0/30, 12/6; 0/200, 12/6; 0/250, 12/6.
VOLTMETERS—2in. Flush D.C. 0/20, 7/6; 0/40, 10/6; 0/200, 10/6; 3in. Surface
VALVES—Guaranteed Govt. surplus.
 1R5 10/6 6J6 12/6 12K8GT 12/6
 1S5 8/- 6J7GT 9/6 25L6GT 10/6
 1T4 8/- 6K7G 8/6 35L6GT 10/-
 3V4 10/6 6K8C 12/6 50L6GT 10/-
 5U4G 8/6 6L6G 11/6 807 10/6
 5Z4G 8/6 6N7G 10/6 B36 10/6
 6AC7 5/6 6SL7GT 9/6 DH77 10/-
 6AL5 7/6 6SN7GT 11/6 EF59 7/6
 6AM6 11/6 6V6G 8/6 KT63 11/8
 6J5GT 6/6 6X5GT 9/6 W77 10/6

COMPREHENSIVE LIST NOW READY 6d. Dept. PW, 204, LOWER ADDISCOMBE ROAD, CROYDON. Tel.: ADD 2027.

UNLIMITED

REED

LOUDSPEAKERS—All new stock. 2-3 6in., 3in., 12-; 3in., 12/6; 5in., 12/6; 12in., 45-; 6in., 12-; 8in., 14/6; 10in., 16/9.

OUTPUT TRANSFORMERS—Standard 7,000-3 ohm. 3 6; Multi-P/pull. 5 11.

ELECTROLYTICS—BR 500 v. Series Card Tub. 8 mfd., 2 6; 16, 3/6; 8 x 8, 3 6; 8 x 16, 4 3; 15 x 16, 4 9; 32 mfd., 4 3; 32 x 32, 6 - Bias 25 25 v., 1 6; 50/25 v., 1 6; 50/50 v., 1 6.

VALVES—1T4, 1S5, 1R5, 5S4, 3V4, IC5, 6V6, 6F6, 6J7, 7S7, 7B7, 7C7, 7Q7, EF39, EBC33, EL32, EF50, all at 7 11 each.
 6K8C, KT36, 12K8, 12K7, 12Q7, 524, 5U4, 9 3 each, 6K7, 6C5, 6J5M, 6D6, 6B8, SP61, D63, 5 11 each. EA50, 9D2, 6H6, 2X2, LP2, 11L4, 1L4, ARP12. Four any type or mixed, 12 - 1 6.

Catalogue free on request.
 ELM ROAD, LONDON, E.17. Tel. 4813.

ASTRAL RADIO PRODUCTS

SPECIAL OFFER—Midset I.F.T.s, 455 kc/s. 13 16in. square x 1 1/2in. high. BRAND NEW, 6/- pr.; High "Q" postage 6d.
H.F. Coils as used in original model, 3-band. All Dry 3 (April '53, P.W.), 6/6 pr., postage 6d.
Dual Wave H.F. Coil as used in original models, Summer All Dry Portable, Modern 1 and 2 Valve, etc., 4/3 each, postage 3d.; or with 5 circuits, 5/-.
Osmor QCI Choke, 4-, postage 3d.
"K" Type Coils, A.E. and H.F., as used in original Model A.C. Bandpass 3, 3/3 pr. coil; Osc. and S.W. Band also available, postage 3d.
M.W. Frame Aerial, unsupported windings, 3/6 each.
M.W. Frame Aerial, Litz wound, high gain on Paxolin, 5- each.
L. and M.W. X-tal Set Coil, 2/6 each.
 All goods brand new and guaranteed.
 Trade enquiries invited.
138, THE RIDGEWAY, WOODINGDEAN, BRIGHTON 7.

SPARKS' DATA SHEETS

Constructional Sheets of Guaranteed and Tested Radio Designs.

ALL-DRY BATTERY DESIGNS

THE "POCKET PAK" 1-valve Med.-wave portable. Good 'phone signals. Self-contained aerial and batteries.
THE "CHUMMY" 2-valve portable. Fine 'phone results M.L. waves. No aerial required. Just switch on.
THE "MIDDY" 2-valver. M/L waves. Fine speaker results. V-popular. All praise its performance.
THE "BOSUN" 3. A more powerful version of the above.
THE "CRUISER" 3-valve T.R.F. circuit. Good range and power. M/L waves. Ideal for caravans camping, etc.
THE "SKIPPER" 4-valver. High sensitivity T.R.F. circuit. Safe any area. M/L waves. A fine set. Range and power.
THE "CORVETTE" 4-valve all-wave Superhet. Great range and very selective. Ideal for a portable. Very compact.

Data Sheets of above, 3/2d. each, post free. Many other designs available. Send 2d. stamp for my latest list.

L. ORMOND SPARKS (P), 49A, HIGH STREET, SWANAGE, DORSET.

AND NOW

The "SOUNDMASTER" Tape Recorder

Designed by the creators of the Viewmaster. Full constructional envelope gives step by step details to enable you to make this super outfit from standard parts. All parts available separately. Get your envelope to-day, price 6/6d.



All enquiries to:—

HOME RADIO OF MITCHAM
 187, LONDON ROAD, MITCHAM, SURREY.

The MINI AMP

By R. Hindle

A VERSATILE MINIATURE AMPLIFIER AND ITS USE AS A BABY ALARM OR INTERCOM. SET

(Concluded from page 592 October issue)

FIG. 6 gives the other dimensions required. It will be seen that the main part of the chassis consists of a strip of metal bent into the shape of a letter "L" and of such dimensions as just to fit into the cabinet. A round hole is cut, 3in. in diameter, and central to the speaker position shown in Fig. 5 and the speaker itself is screwed to the front plate as low as possible. The power pack components are then mounted as indicated in Fig. 7, grouped round the speaker. The exact layout will depend on the actual dimensions of the components used, which must all be reasonably miniature if the resulting unit is to be no larger than the original. The power pack should be completely wired before fitting the upper shelf and three wires left for connecting power to the amplifier. A short piece of twin flex will be needed for the connection between the power pack and the on-off switch, which passes through a hole in the amplifier base-plate when this is mounted before being soldered to the switch connectors. Similarly, a piece of thin twin shielded flex such as is sold for pick-up connections is soldered to the speaker tags, one of which is earthed, and this also passes through a hole in the amplifier base-plate to be connected eventually to the "talk-listen" switch. There is not a lot of room for the two smoothing electrolytics, but it was found that one would fit along the top of the smoothing choke and the second fitted in along the top of the filament transformer.

Amplifier

The layout of the amplifier shelf is given in Fig. 6. The input transformer is one of the miniature ones sold as output transformers for use with small battery valves and is mounted above the chassis so that it is shielded from the power transformer and choke. Before mounting the "talk-listen" switch this should be wired for the connections required between the tags as given in Fig. 2. To convert the three-way switch used for the prototypes for two-way operation all that was necessary was to turn up carefully a prong alongside the previously existing stop. This resulted in four connecting lugs around the switch being unnecessary for the job in hand. These were all connected together, however, and to the chassis and they formed a very convenient point to which the braiding of the connecting wire could be earthed. All the wiring of this switch and the leads to and from it were run in fine screened cable and the braid was soldered to this ring of earthed tags, anchoring the leads firmly as well as earthing them.

Care must be taken, of course, not to damage the inner connector when soldering to the braid but if the iron is at the correct heat it will be found that the solder quickly runs and the iron can be taken away before the heat has penetrated.

With this switch in position the rest of the components can be mounted. Do not fasten the amplifier chassis to the main chassis at this stage or it will be impossible to get underneath. The amplifier should be completely wired, in fact, before assembling the two parts of the equipment. Nor should the change-over switch be wired to input and output until the amplifier has been made to work without it or it will complicate the process of tracing any fault that may be found present. Instead, first wire the amplifier as in Fig. 1, making temporary connections to input and output as shown and connecting longer temporary leads to the power pack output so that for first tests the amplifier can be kept apart from the pack so that its components are accessible.

A tag strip is mounted underneath the amplifier chassis at the output transformer end to take the power interconnections. Otherwise all components are wired directly to the valve tags concerned. They must all be small, of course, and must be fitted snugly so that they do not take up too much room. Care will be required in the placing of the three electrolytics, which are the only sizeable components

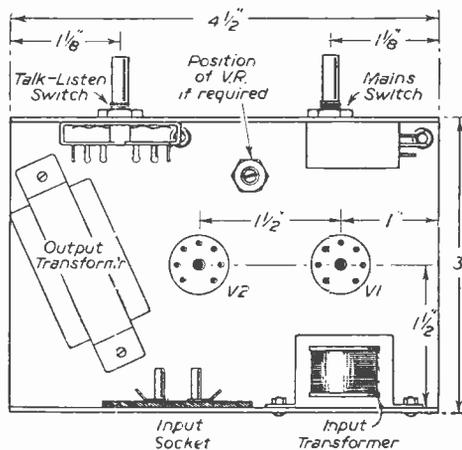


Fig. 6.—Amplifier dimensions and layout details.

used on the amplifier chassis. These were laid at the rear underneath the chassis and there they just cleared the components of the power pack.

At this stage the mains switch need not be fitted, but instead a length of flex should be connected direct from the heater transformer to the power supply. The temporary connections between the power pack and the amplifier can then be made, and the speakers to be used for the first tests should be connected direct to their respective transformers and not through the talk-listen switch. No difficulty should be experienced in getting the amplifier to work when so connected,

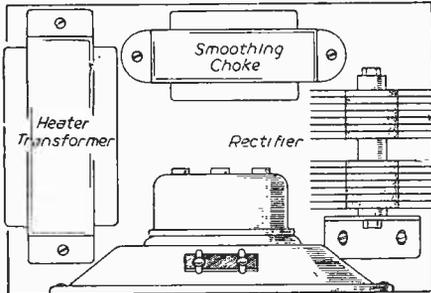


Fig. 7.—Details of the Power section layout.

but whilst working on the unit it should be borne in mind that the chassis is connected directly to the mains and care must always be taken to disconnect the mains completely by withdrawing the mains plug from the socket before making any adjustment or for any purpose touching the chassis.

When satisfied that the amplifier is in order the two parts can be brought together. The temporary leads are removed and wires for permanent connection are fixed to the power pack. As the two parts are brought together the mains lead from the heater transformer and the screened lead from the internal speaker are passed through the holes provided on the amplifier chassis. The amplifier is held on to the main chassis merely by the fixing nuts of the switches. That of the talk-listen switch is taken off, the spindle passed through the corresponding hole in the main chassis and the nut is then replaced to hold the two parts together firmly and in alignment. The mains switch can now be fitted. For use when the mains is connected to the chassis a two-pole switch is preferred, and to match the other switch a rotary operating mains switch is obviously desirable. The type actually used is the Bulgin type S256, which fits in very well. Make the connections to the mains switch at this juncture, but preferably give the amplifier another trial with the speakers connected direct to their transformers, and if all goes well so far the temporary speaker connections can be replaced by the switched connections of Fig. 2 and, if screening has been thoroughly carried out, no difficulty should be experienced.

A word might be said about C3. This should not be too large. Bass reproduction is not to be expected from such a small speaker and cabinet, and there is no point in trying to retain bass notes in the amplifier, particularly as hum is suppressed along with the bass notes. The suggested value is .01 μ F. However, if it was decided to try the method of Fig. 4 to cancel hum a different problem is involved. To be of any use there must be a minimum of phase difference

between the unwanted hum and the heater supply. If the hum is picked up in the first stage of the amplifier C2 will cause some phase shift, and to reduce this to reasonable proportions the condenser should be made as large as possible. Probably a miniature .1 μ F will be the best that can be done.

For interconnection between the distant speaker and the unit lightweight twin PVC mains flex was found most suitable and can easily be run out wherever required. Some hum pick-up is to be expected from this lead, but as the connection is at low resistance it was not found troublesome.

The back of the cabinet will need to be drilled to allow the input plug to be inserted and for the mains lead to pass out. It should be remembered also that there will be more heat inside the cabinet than with the receiver for which it was originally designed, and it will be wise to cut away part of the back to allow ventilation, covering the aperture with fabric to keep out the dust. Another point is that the metal of the unit is connected directly to the mains and consequently precautions should be taken to prevent contact. A metal fabric is provided with the cabinet for the speaker aperture, but for this application it should be replaced by a piece of non-metallic material and the knob grub screws should be well sunk and the holes filled in with wax.

The Third Programme

Aerial Details

THE BBC announces that provisional arrangements have now been made for the Third Programme transmitter at Daventry, 464 metres, to resume operation using the main aerial. This transmitter has recently been operating at reduced power with a reserve aerial because of a fault which developed on the main aerial system.

Transmissions will, for the time being, continue at reduced power but with the main aerial in use there will be some improvement in reception—particularly for distant listeners who have been more affected by the reduction in signal strength.

The date on which the work on the main aerial is completed and the transmitter restored to its full power operation will be announced later.

Programme Times

It is also to be noted that the Third Programme now opens on Sunday afternoons at 3 p.m. To meet the additional cost the service will close daily at 11.30 p.m.

A full-length play or opera will normally fill the greater part of this extra three hours of programme time each Sunday.

STANDARD TEXT BOOKS

By F. J. CAMM

Everyman's Wireless Book, by post, 13/-. Newnes Radio Engineer's Pocket Book, by post 5/3. The Superhet Manual, by post, 6/4. Radio Training Manual, by post, 6/4. Wireless Coils, Chokes and Transformers, by post, 6/4. Refresher Course in Mathematics, by post, 8/10. Mathematical Tables and Formulae, by post, 5/3.

Obtainable from

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2.



SPECIAL CATHODE RAY TUBE OFFER

Brand New 12in. standard T.V. type, c.r. tube, £12/19/6. Carriage 15/- extra.

CONDENSERS

Electrolytic Cans.	
16 mid. 500 v.w.	3/6
24 mid. 450 v.w.	3/11
32 mid. 500 v.w.	5/11
80 mid. 350 v.w.	3/6
84 mid. 450 v.w.	4/11
8+8 mid. 450 v.w.	3/11
2+16 mid. 450 v.w.	3/11
8+32 mid. 450 v.w.	3/11
16+8 mid. 500 v.w.	4/6
16+16 mid. 500 v.w.	4/6
16+24 mid. 450 v.w.	4/11
16+32 mid. 450 v.w.	4/9
20+20 mid. 275 v.w.	2/-
32+32 mid. 500 v.w.	2/6
32+32 mid. 350 v.w.	3/11
60+100 mfd. 350 v.w.	7/6
250 mfd. 350 v.w.	4/11
1,000 mfd. 12 v.w.	3/11
8,000 mfd. 3 v.w.	6/11
Electrolytic Tubular.	
1 mid. 200 v.w.	1/-
1 mid. 250 v.w.	9/-
2 mid. 150 v.w.	1/2
2 mfd. 350 v.w.	1/6
4 mid. 350 v.w.	1/3
4 mid. 450 v.w.	1/6
8 mid. 150 v.w.	1/6
8 mid. 350 v.w.	2/-
8 mfd. 450 v.w.	2/3
8 mid. 500 v.w.	1/9
15 mid. 200 v.w.	2/-
16 mid. 350 v.w.	2/6
16 mid. 450 v.w.	2/9
16 mid. 500 v.w.	3/3
32 mid. 350 v.w.	3/6
32 mid. 450 v.w.	4/9
50 mid. 350 v.w.	4/6
250 mfd. 12 v.w.	2/-
250 mfd. 25 v.w.	2/11
8+8 mfd. 350 v.w.	3/-
8+8 mfd. 450 v.w.	3/11
12+12 mfd. 350 v.w.	2/6

SPECIAL TV CONDENSERS

By T.C.C. 32+100 mid. Type CE15PE. 450 v.w. 7/6. 04 mid. Type CP50V0 12.5 kv. 7/6.

BIAS.	
75 mfd. 12 v.w.	1/-
10 mfd. 25 v.w.	12 mfd. 50 v.w.
50 mfd. 12 v.w.	1 3/4 25 mfd.
25 v.w.	25 mfd. 50 v.w.
50 mfd.	25 v.w.
1/6	50 mfd. 50 v.w.
1/9	100 mfd. 25 v.w.
2/-	100 mfd. 50 v.w.
2/6	

Tubular Waxed, and Miniature Mica. 500 v.w. All values up to .1 mfd., 6d. each, 5/- per doz. .1 mfd., 8d. each.

MAINS TRANSFORMERS

All 200-250 volts c.p.s. primary. Finest quality. Fully guaranteed.

MBA/3. 350-0-350 v. 80 mA. 6.3 v. 4 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans. Price, 18/-.

MBA/6. 325-0-325 v. 100 mA. 6.3 v. 3 a., 5 v. 2 a. With mains tapping board. Price, 22/6.

MBA/7. 250-0-250 v. 80 mA. 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. Price, 18/-.

MBA/8. SPECIAL OFFER. Drop through type. 235-0-235 v. 60 mA. 6.3 v. 3 a., 5 v. 2 a., 12/6. AT/3. Auto transformer. 0-10-120. 200-230-240 volts, 100 watts. Price 17/6.

AT/5. TV Type Mains Auto. 230, 220, 250 auto 375 v. inputs. 250 mA. 5 v. 3 a., 6.3 v. 7 a., 6.3 v. 3 a. 25/-.

FILAMENT TRANSFORMERS

6.3 v. 1.5 a. 7/11.
6.3 v. 3 a., 12/6.
Special Transformer. 2amps., with the following tapings: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts. PRICE 17/6.

FIL.4. Heavy duty filament transformer. 6.3 v. 8 a., 5.3 v. 3 a., 5 v. 3 a. Shrouded drop-through type. With mains tapping board. Price 32/-.

PERSPEN. 131 x 101 x 1in. Neutral shade, slightly marked. 4/11 per piece.

TEST PRODS. Fused, with fully retractable points. Price 4/11 per pair.

ANTENNA ROD SECTIONS
Each rod is steel heavily copper plated. Any number can be fitted together. 12in. long. 1in. diameter. Price 2/6 per dozen post free.

GRAM MOTORS. Rim drive. For 200-250 v. 50 c.p.s. Many uses. 9/6 each.

TANNOY PRESSURE UNITS
10 watts. 7.5 ohms impedance. LAST FEW ONLY. 59/6. Carriage 3/6 extra.

R.1132A RECEIVERS. Complete with all valves. Store soiled. 39/6. Carriage 10/- each extra.

5 WAVEBAND RADIO CHASSIS

LIMITED QUANTITY. (Frustrated Export).
Circuit has R.F. stage, Magic Eye tuning indicator and many other features. For A.C. 100-250 volts. Waveband coverage 11.5 to 550 metres. Valve line up—2 EF39, 1 ECH35, 1 EBC33, 1 EL33, 1 5Z4, 1 EM34.
LASKY'S PRICE £8/19/6. With valves. Less dial. Carriage and packing, 15/- extra.
WILL MAKE A SUPER RADIO-GRAM.

SUPERHET COILS

For 465 Kc/s. 10-30 metres. Aerial and oscillator. 1/11 per pair. With Circuit. Postage 9d. extra.

50L6	...	10/-
35Z4	...	9/-
6AM6	...	9/-
6AB6	...	2/6
EF50, Red		
New Sylvania		
1C5	...	10/6

1S4	...	9/-	1A5	...	9/-	6J7	...	6/6	EF39	...	7/6
35Z4	...	9/-	12K3	...	8/6	HL2	...	3/6	12K7	...	10/2
1T4	...	9/-	12Q7	...	8/6	KT2	...	3/6	6LA	...	10/6
1R5	...	9/-	6AL5	...	8/6	6K8	...	9/6	EA50	...	2/6
1S5	...	9/-	6K7	...	4/6	U50	...	9/-	EBC33	...	7/6
1C5	...	9/-				ECH35	...	13/6	35L8	...	10/-

I.F. TRANSFORMERS

465 Kc/s. Iron dust cores in cans. Midnet type. Size: 1in. x 1in. x 2 1/2in. Price 9/6 per pair.
WEARITE TYPE 530. 450-520 Kc.s. 10/- per pair.
WEARITE TYPE 500. 450-470 Kc.s. 10/- per pair.

P.M. LOUDSPEAKERS

All less o'trans. new and unused. First quality.
3in. Elac. 12/11
3in. Plessey. 12/6
6in. 13/6
8in. 15/-
10in. 25/-

SUPERHET COIL PACKS

3 Wavebands : 15-35 metres : 35-100 metres : 200-550 metres : Size : 4 x 4 x 3in. Price 16/-.

CAR RADIO PLUG SUPPRESSORS. 16 each.

3-SPEED GRAM MOTORS

Complete with motor board, any turntable. NEW AND UNUSED. 49/6. Carriage 3/6 extra.

FAMOUS NAME 3-SPEED AUTOMATIC RECORD CHANGERS

Turnover pick-up head. Brand new in maker's original cartons. Listed at £13/10/0. Auto change on all speeds. Plays mixed 7, 10 and 12 in. records. LIMITED QUANTITY AT £11/10/0. Carriage 7/6 extra.

C.R.T. MASKS. Brand New LATEST ASPECT RATIO

10in.	7/6
12in.	15/-
12in. flat face	15/-
14in. rectangular	21/-
16in. Double-D	31/6
17in. rectangular	21/0
SOILED OLD ASPECT RATIO		
9in.	5/-
12in. with fitted armour glass. (New ratio.) Cream	11/6
12in. with fitted armour glass. (New ratio.) Black	8/6

9in. TABLE TV CABINETS

Medium shade mahogany finish. Complete with back, safety glass, speaker-fret. Internal dimensions : 19 1/2in. high, 16in. wide, 14in. deep.
LASKY'S PRICE 39/6 carriage 7/6 extra.
Adaptor frame available for 6in. C.R. tubes. The aperture can easily be enlarged to take 12in. or 14in. tubes.

VALVES. 10,000 IN STOCK AT THE LOWEST POSSIBLE PRICES. SOME EXAMPLES.

SPECIAL OFFER, 4 Valves : 1 each 1R5, 1T4, 1S5 and 35A.
LASKY'S PRICE 32/6.
POST FREE.

OUTPUT TRANSFORMERS

40 mA. Multi-ratio	6/11
60 mA. Multi-ratio	14/1
60 mA. Pentode	12/6
60 mA. Plessey, 6,000 ohms	5/11
Standard pentode	4/11
Pentode	3/6
Midnet pentode	4/3
Miniature pentode. 3S4	1/84
1S4	4/6
PN4 intervalve	8/6
5:1 intervalve	5/11

15in. C.R.T. MASKS

Latest aspect ratio. New and unused. Rubber. Overall size : 17in. wide, 13in. high. Price 17/8. Post 2/-.

GENERAL PURPOSE FILAMENT TRANSFORMER

6.3 volts tapped at 4 volts. 2 Amps. Price 9/6

SMOOTHING CHOKES

20 mA. 40 H.	3/11
40 mA. 8 H.	3/11
40 mA. 10 H.	4/3
100 mA. 10-20 H.	7/3
120 mA. 10 H.	15/6
200 mA. 5 H. 50 ohms	12/6

TELEVISION SELENIUM RECTIFIERS

The very best "Scentercell" S.T.C. range.
K340. 3.2 kv. 7/6
K345. 3.6 kv. 9/2
K350. 4.0 kv. 8/8
K3100. 8.0 kv. 14/8
K3160. 12.5 kv. 21/6

S.T.G. METAL RECTIFIERS

RM1	3/6
RM2	4/6
RM4	18/-

AMPLIFIERS

4-Watt Model. Ex Government. Complete with 10 valves: 2 25L6; 1 5HG; 1 25Z6; 6 6BK7. For operation on 110 volts A.C.C.D. Balance and push pull. High, medium and low impedance inputs. A.C.C. etc. **LASKY'S PRICE £5/19/6** complete. No circuits available. Carriage 10/- per unit extra.

CRYSTAL DIODES

Germanium. Price 2/3 each. Post Free.

E.H.T. Transformer for VCR97. 45/-.

Screen Enlarger for VCR97. Filter type. 17/6. Postage 2/6.

E.H.T. Condenser.

.1 mfd. 2.5 kv. 2/6.

FULLY ASSEMBLED POWER PACK AND OUTPUT STAGE FOR R1155 RECEIVERS. For use on 200-250 volt A.C. mains. Wired and complete with valves. **LASKY'S PRICE £79/6.** Carriage 5/- extra.

EX-AM. RECEIVER TYPE R1155.

Brand new and unused. 5 Frequency Ranges : 18.5-7.5 Mc/s : 7.5-3.0 Mc/s : 1,500-600 Kc/s : 500-200 Kc/s : 200-75 Kc/s. Supplied in maker's original wood transit case. **LASKY'S PRICE £11/19/6** Complete. Carriage 12/6 extra.

USED MODEL R1155 RE-CEIVERS. Aerial tested before despatch. Complete with 10 valves. **LASKY'S PRICE £7/19/6.** Carriage 12/6 extra.

SECONDHAND R1155. Less valves and faulty. Ideal for breaking up for spares. 50/-, carriage 7/6 extra.

VCR97 C.R. TUBES. new unused. 35/-, Carriage 5/-.

LASKY'S RADIO

Lasky's (Harrow Road), Ltd.,

370, Harrow Road, Paddington, London, W.9

Telephones: CUNningham 1973-7214. All Depts.

MAIL ORDER AND DESPATCH DEPARTMENTS: 485-487, HARROW ROAD, PADDINGTON, LONDON, W.10.

Hours : Mon. to Sat. 9.30 a.m. to 6 p.m. ; Thurs. hal' day. 1 p.m. Postage and packing charges (unless otherwise stated); on orders value £1-15. 0d. extra : £5-25. 0d. extra : £10-35. 6d. extra ; over £10 carriage free unless specifically stated otherwise. All goods fully insured in transit.

"TYANA TRIPLE THREE"

SOLDERING IRON WITH DETACHABLE
BENCH STAND **19/6**

The smallest high power soldering iron. Length only 8½". Adjustable long bit dia. ⅜". Mains voltages, 100/110, 200/220, 230/250.


STANDARD TYANA SOLDERING IRON. Price retails at 16/9. Replacements, Elements and Bits always available. Voltage as above.

MAKE SOLDERING A PLEASURE!

BY USING THE "TYANA" SOLDERING IRON

British made by:—**KENROY LIMITED,**
152/297, Upper Street, Islington, London, N.1.
Telephone: Canonbury 4905-4663

REP HIGH GAIN COILS

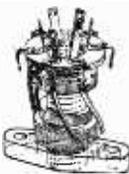

Dual Range Miniature **2/6** with
Crystal Set: Coil Circuit

Dual Range Coil **4/-** with 2 Mains and
w.th Reaction 2 Battery Circuits

Matched Pair Dual Range **8/-** pair With Battery and
T.R.F. Coils Mains Circuits

- All coils wound on low loss formers.
- Individually tested and guaranteed.
- Post 3d. on all orders.
- Trade supplied.

RADIO EXPERIMENTAL PRODUCTS, LTD.
33, MUCH PARK ST., COVENTRY

GUARANTEED VALVES.—AL60. 6J5. 88N7. 6BW5. 6BA6. 6BE6. 6AG. 6SL7. 6K3. 607. 6X5. 6C5. 6D6. 5Y3. EP39. 12BA6. 12BE6. 9/6. 6SU7G1. 7R7. 7U7. PEN303. VP133. KT66. 1P6. 717A. V570. V5J10A. VU508. CV57. CV18. 8012. KT741. 6N7. VT501. 6V6. 6AT5. 6AM6 (EP91. Z77. 6F12). 8-. EP92 (W7. 9D6). IT4. IS5. IU5. 3A4. 3V4. 3S4. 6AG5. 7B. 6B3. PEN46. 12SL7GT. 12J5GT. 15SH7GT. PEN25. 6AL5 (EP91. D77. 6D2). 6/6. VR63. 6VGT23. VR137. VR36. 1239A. 1A5CT. 5/6. 7193. VR51. VR92 (EA50). VR78. 2/6. 12A6 Metal Soldered, but Guaranteed. 5/-.

VALVEHOLDERS.—Int. octal amphenol. 2/6 for 3. EP50 ceramic or micaalex. 1/6 for 3. Mazda octal waxolin or amphenol. 1/6 for 3. B3A amphenol with base screen. 2/6 for 3. British 4-pin ceramic. 1/- for 2. UX 7-pin ceramic. 2/6 for 2. UX 5-pin (for 807. etc.). 1/6 for 2. British 5-pin high voltage type. 1/6 each. EA50 diode type. 4/4. each. VCR97, base, 2/6 each. EP50 valve retainers, screw type, 1/- complete.

TOGGLE SWITCHES.—D.P. D.T. for Mains use. 2/6.

TOGGLE SWITCHES.—S.P. On / Off for Mains use. 1/3.

TRIMMERS.—Postage stamp type. 20 pF. 30 pF and 70 pF. All at 9d. each.

MOVING IRON MIKES.—With switch, 4/6.

TOUCHES.—Light range over 300ft. Ring Focus. Complete with Bulb and two U2 batteries. Brand New. As supplied by us to cinemas, etc., 7/6.

HIVERSACKS.—Brand New Ex. Army. Ideal for Carrying Tools, Meters, etc. approx. 7 1/2 in. x 6 in. x 2 1/2 in. with shoulder strap. 2/-. approx. 1 1/2 in. x 6 in. x 5 1/2 in. with shoulder strap and waist strap. 3/6.

ROUND TINS.—Black Enamel Finish. Approx. 1 1/2 in. diameter 4 1/2 in. high. Push on close fitting lid. Brand New. Useful for containing dials, components, etc. 3 for 1/6 or 5/- dozen, post free. Special Offer.

J. B. SERVICE (BEXLEYHEATH) LTD.,

5, Mayplace Road West, Bexleyheath, Kent



The "Fluxite Quins" at Work

"A good place to plant it, my foot!

You know jolly well where it's put

The wiring's all right

Thanks to me and FLUXITE

But we can't see our T.V. for soot!"

See that **FLUXITE SOLDERING PASTE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards.

FLUXITE

SOLDERING PASTE

A Staunch Companion to Fluxite Soldering Fluid.

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE.

FLUXITE LTD.

Bermondsey Street, London, S.E.1.

AMPLIFIER for 200-250 a.c. in handsome radio cabinet 15in. x 11in. x 7in., provision for 6 1/2 in. speaker, 3 v. (inc. rect.), 3 W. high gain with o.p. trans. Wired ready for use. £4. 12s. 6d. (carr. 7/6).

SPEAKER. 6 1/2 in. P.M. 2-3 ohm for above. 12/6 (carr. 1/6 without amp.).

RECEIVER at £9 18s. (carr. 7/6). 4 v. (inc. rect.), plus crystal detect. for 200-250 a.c. in cabinet above, for high quality reproduction of M.V. local and L.V. stations.

RECEIVER (ex-Govt.) R1124D, with all valves, 17/6 (carr. 5/-).

AUTO-CHANGER. 3-speed £10 (carr. 7/6).

VARIOUS chassis; over 30 components, 3/-; 4/- and 5/-.

VARIOUS wired mats of over 30 condensers and resistors, 3/- and 4/-.

VARIABLE condensers 2-gang, 6/-; 3-gang, 3/6.

HEADPHONES (H.R.), 15/- pair.

DUBILIER 40-40-30 mf. 275 v. can type, 2/-.

SPEAKERS.—P.M. 2-3 ohm 10in., 20/-; 5in., 12/6; 4in., 11/- (post 1/-).

VOL. CONTROLS.—1 M. 2-pole sw., 5/-; 1/2 M. 1-pole sw., 4/-.

METERS (ex-A.M.). 2 1/2 in. square flush 0-1 A. thermo-couple, 6/6; 0-5 mA mov. coil, 9/6.

VIBRATOR transformer (6 v.) 145 v., 28 Ma. with 5 K. load, 10/6.

SEND US YOUR ENQUIRIES. RETURN OF POST SERVICE. SATISFACTION OR MONEY BACK. ALL GOODS NEW EXCEPT R1124D.

GLADSTONE RADIO

Gladstone Place, Newton Abbot, Devon

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925

189, DUNSTABLE ROAD, LUTON

Phone: **LUTON 2677**

We have reprinted our popular 5 valve Super-het Circuit No. 1.

Also our 4 Watt Amplifier Circuit No. 2.

Price: 1/- ea. Plus

Postage 2d.

Our New Comprehensive 50-page Catalogue, Price 6d.

Just released by the Ministry of Supply

ALL DRY H.T. L.T. BATTERIES

72 volt H.T., and 1.5 volt L.T.

Layer type size, 6in. x 5in. x 2in.

ALL TESTED AND GUARANTEED FULL VOLTAGE BEFORE DESPATCH.

OUR SPECIAL PRICE. Only 4/6 each, P.P. 1/3.

2 for 8/-, P.P. 1/6.

WALTON'S WIRELESS STORES,

48, STAFFORD STREET, WOLVERHAMPTON

Programme Pointers



“The Immortal Bohemian”

THIS programme, which I looked forward to in my last article, has come and gone. Written and arranged by Spike Hughes from “The Life of Puccini,” by Father Bante del Fiorentino, it occupied four episodes in the Light Programme, each of an hour’s length. Though not all I had hoped it would be, it was quite an excellent series. Puccini was a figure ready made for Hollywood, Broadcasting House, Radio City, or where you will—a 100 per cent. entertainer—none of your metaphysical-cum-religious philosophical speculations as with Wagner, or your historical romanticism as with Verdi—an unashamed sensualist and the composer of some really magnificent music. That this has been dragged through the mire of cheap entertainment, and has suffered accordingly so that some of it is difficult to take seriously any longer, is partly its own fault. So have Handel’s, Mendelssohn’s and Chopin’s marches through no faults of their own. And much else besides. It nevertheless intoxicates and spellbinds, even when it reminds us, through the association of ideas, with curried mutton and rice at a popular restaurant. Even the summer now closing has been referred to as a Madame Butterfly summer—One Fine Day.

The production rather fell down, I thought, on a shortage of operatic excerpts—a heaven-sent opportunity of which more might have been made. Also, James McKechnie as the maestro and Gladys Young as Elvira Gemignani seemed hardly Latin enough in their respective characterisations. Spike Hughes was his usual excellent self as commentator, and is to be congratulated on a fine and entertaining job. Malcolm Baker-Smith produced.

Voice of the BBC

I have frequently noticed that the reports we get in the news bulletins on different happenings, usually political and industrial, are word for word the same as those given by BBC political and industrial correspondents and experts in “Radio Newsreel.” I suppose this is just one manifestation of the BBC’s vice of repetitiveness in all it produces, of which it doesn’t yet seem to be even conscious.

“Everest, 1953”

This was a thrilling presentation by Sir John Hunt and members of his great team—Tensing excepted through inability to be present—of their historic conquest of the world’s highest mountain. Everest’s 29,002ft., and the mystery of how, if at all, it came by the odd two, was, I think, the first item of general knowledge I came by as a child. It probably was with many another, too. Consequently, the doubts cast upon its exactitude from time to time, coupled with attempts at its correction, seem almost as acts of lese-majesty. The presentation of the story was all the more effective and acceptable for being almost entirely free of commentator’s rust and clogging.

By MAURICE REEVE

Just a plain “Ladies and Gentlemen, Sir John Hunt,” so to speak, and away we went.

“Portraits from Memory”

Bertrand Russell’s new series, “Portraits from Memory,” are as fine as everything this great man and excellent broadcaster gives us over the air. What a pleasure it is to listen to such a rich store of memories quietly and nostalgically unfolded.

Piano

Two piano recitals gave us some gorgeous and rarely-heard music. The “Goyescas” of Granados—both books—played by Eduardo del Pueyo very effectively, and the “Pictures from an Exhibition” of Moussorgsky, done by Rudolf Firkusny quite magnificently. Wonderful music.

“The Weekly Bind”

The new Murdoch-Horne-Costa, etc., feature, “The Weekly Bind,” has got off to an excellent start. The first issues were packed with humour and well up to the best “Much Binding” standard. The cricket match report was enormously funny. How long can it be kept up?

History

“Bella Donna,” by Howieson Culf, from Robert Hitchen’s novel and G. B. Fagin’s play, is an integral link in the chain of Egyptian history—Cleopatra, the Pyramids, Napoleon, the Suez Canal, Fashoda, Ruby Chepstow and so to Farouk and Noguib. Those of us who can remember Mrs. Pat and George Alexander as Ruby and Dr. Isaacson respectively, at the St. James’s in days long past, had our memories usefully and agreeably revived. Mr. Culf was first rate both as the Jew doctor and the driver for broadcasting. And Sonia Dresdel was coldly and ruthlessly lethal as Mrs. Chepstow. A good Edwardian example of liquidation.

Interviews

The series of unscripted interviews, “Frankly Speaking,” continued with bringing Dr. Maude Royden before the microphone. This remarkable woman made a notable contribution.

I cannot refrain from condemning the “Ashes” Test Match comments given in “Radio Newsreel” the evening the game finished. I thought it was in the worst possible taste and more suitable to a revivalist meeting than a game of cricket. The speaker, in trying to be clever, failed lamentably.

Adding A.V.C. to Straight Receivers

A SIMPLE SCHEME FOR THE EXPERIMENTER

By T. W. Dresser

A "STRAIGHT," or T.R.F., receiver is easier to construct and to align than the most simple of superhets: it can be capable of a remarkably good performance using modern valves and iron-cored coils, and from an audio quality angle and that of a quiet background it definitely scores over the superhet.

The principal drawback, hitherto, to the T.R.F. short-wave receiver has been inadequate selectivity and the lack of A.V.C. Using good quality iron-cored coils the selectivity problem can be dealt with easily enough, and there then remains only the question of A.V.C. to be dealt with in order to bring the receiver, still retaining its initial advantages over the superhet, within reasonable measure of the latter in most other respects.

The provision of A.V.C. in a straight receiver is not quite as simple as it would appear on the surface. To begin with there are a multiplicity of detector types to be dealt with and such things as reaction to complicate the matter further. For these reasons, and possibly others, A.V.C. in straight sets has been avoided by the majority of designers and, in fact, in over ten years of perusing the technical journals only one design incorporating A.V.C. has been noted—that being in our pages in 1945.

Over the same period, too, the anode bend and infinite impedance detectors have come very much to the fore by virtue of their manifest advantages over other types, and this has some bearing on our subject. These types of detector, possessing as they do a high input impedance and, therefore, unlike the diode, not liable to affect the selectivity of their tuned input circuits, also have the additional advantage of being less liable to distortion on heavily modulated signals. Despite these definite virtues, however, neither type of detector has succeeded in attaining the popularity it merits and the reason is not hard to find. It is precisely that with which this article is concerned—the difficulty of providing A.V.C., more particularly as A.V.C., rightly enough, is regarded as a necessity in any modern receiver.

Results Obtained

Now if such a detector can be fairly simply combined with an A.V.C. circuit, it will be useful from all viewpoints: the signal quality and selectivity will be improved, fading reduced to a minimum, and listening pleasure greatly enhanced on account of these very factors.

Probably it will not have escaped the notice of readers that in almost all such detector circuits an R.F. choke, together with its associated filtering condensers, is placed in the anode lead, and even where there is no choke invariably there is a resistor serving the same purpose. This gives us the clue to our A.V.C. arrangement. If R.F. were not present at the anode it follows there would be no need for a filtering circuit, but as there undoubtedly is, why not make use of it to provide an A.V.C. supply?


The Circuit

A circuit, based upon these lines of thought, is given on the right, the detector in this case being of

the anode-bend type. The R.F. choke in the circuit functions as a load impedance for the R.F. component of the detector output signal, and the voltage developed across it is applied by means of the coupling condenser C1 to a separate A.V.C. rectifier which may be either a diode valve or a Germanium crystal at the builder's discretion. The resultant A.V.C. is then applied to the grid or grids of the R.F. amplifier or amplifiers. In many cases it will be found that there is already an R.F. choke in the anode lead and all that is necessary then is to disconnect the decoupling condenser on the anode side and connect in its place one side of C1.

With an infinite impedance detector the procedure is just as simple. The choke is connected between the anode of the detector and H.T. plus, and C1 is taken off the anode as in the case of the anode-bend detector.


In conclusion, while the arrangements detailed here are very simple to carry out, they are very effective in every way. The high input impedance of both types of detector is not affected in any way and the A.V.C. action, due to the R.F. amplification in the detector (both these detectors are R.F. amplifiers, although poor ones) is excellent. It would seem that a receiver based upon this circuit would prove extremely good, using, say, two R.F. stages, an infinite impedance detector with A.V.C. as indicated in this article, a low power audio stage and push-pull 6F6's or KT61's in the output stage. Such a receiver would have just those advantages mentioned in the first paragraph—namely, excellent station-getting properties, constancy of signal and good audio quality, and from my own experience I know that those things can contribute much to the enjoyment of short-wave listening.

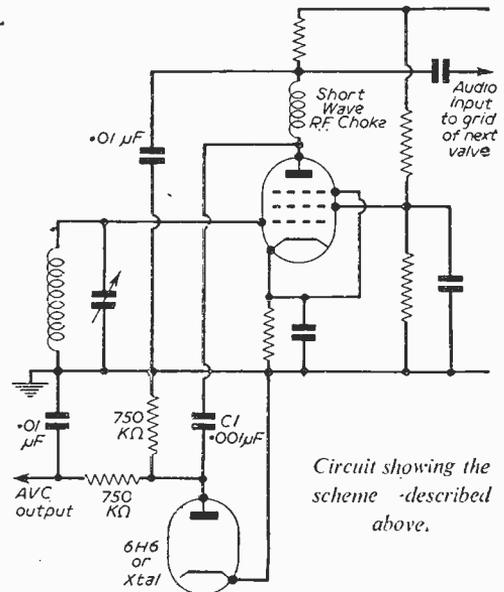



CONNECTING WIRE SNIP

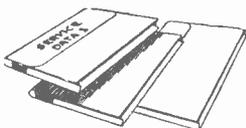P.V.C. insulated 23 s.w.g. copper wire in 100ft. coils, 29 each. Colours available: Black, Brown, Red, Orange, Pink, Yellow, White, Transparent. 4 coils for 10/-.



SERVICE DATA

100 service sheets, covering British receivers which have been sold in big quantities, and which every service engineer is ultimately bound to meet. The following makers are included: Aerodyne, Albe, Bush, Cossor, Ekco, Eyer-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Kolster Brandes, Lissen, McMichael, Marconi, Mullard, Murphy, Philco, Philips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price £1 for the complete folder.

Our folder No. 2 consists of 100 data sheets covering most of the popular American T.R.F. and super-het receivers "all dry," etc., which have been imported into this country. Names include Sparton, Emerson, Admiral, Crossley, R.C.A., Victor, etc. Each sheet gives circuit diagrams and component values, alignment procedure, etc., etc. Price for the folder of 100 sheets is £1. Post free.

SOMWEAVE



very suitable for covering plain wooden cases, for portable radio amplifiers, etc.

This really lovely loud-speaker fabric we offer at approximately a third of today's cost. It is 12in. wide and our price is 12/- per yard or panels 12in. x 12in., 19 each. This is also suitable for covering plain wooden cases, for portable radio amplifiers, etc.

BE PREPARED



for a cold winter by making our low cost Electric Blanket. 27 yards of special heater wire and blueprint. 20/-.



Complete kit comprises Hi-craft 40 watts control unit, starter lamp, lamp holders, clips and wiring diagram. Price less tube, 22 6/- plus 1/8 post. With tube 30/- carriage and insurance 3/6. Tubes 7/6 each, carriage free minimum quantity 6.

TABLE RADIO CABINET

Due to a special purchase, we are able to offer this very fine cabinet, size approx. 16 x 16 x 7 - walnut veneered and satin finished. Complete with 3 colour 3 waveband glass scale at only 37/6 carriage and packing 3/6. We also have a limited quantity of the complete chassis to fit these cabinets, specifications 5 local valves, standard long-medium and short wavebands, A.V.C. 8in. speaker, A.C. mains operation. Price £9.19.6, plus 10/- carriage and insurance. H.P. terms £3.7.0 deposit, or with cabinet £4.0.0.



"MIDGETRONIC" Radio Cabinet



This pleasing small cabinet is in bakelite and is supplied complete with dial rinz, pointer as illustrated but less knobs, also included is metal chassis and hardboard back. Price 15/- plus 2/6 postage and packing. Circuit of £3 radio to fit, 16.



THE SUPERIOR 15in.

Up to the minute TV for only £37-10-0.

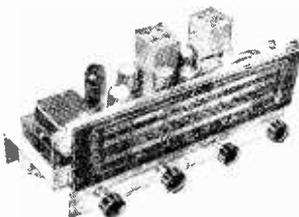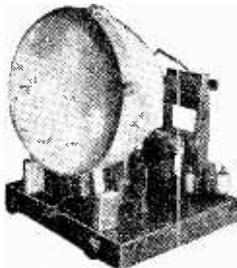A 20 valve television for the amateur constructor, all components, valves and 15in. Cossor Cathode Ray Tube costs £37 10.0 plus £1 carriage and insurance or £12 10.0 deposit and 12 monthly payments of £2.11.6. Constructor's envelope giving full details and blueprint 7/6. Returnable within 11 days if you think you cannot make the set.



This is a 5 valve A.C. super-het, covering the usual 10 n.r., medium and short wavebands. It has a particularly fine clear dial with an extra long pointer travel. The latest type local valves are used and the chassis is complete and ready to operate.

Chassis size 15in. x 6in. x 6in. Price £9.19.6 complete with 8in. speaker. Carriage and insurance 10/- H.P. terms £3 7/- deposit. Table model cabinet to suit—37 6 plus 3/6 postage and insurance.

THE MONTH'S SNIP

Superhet 5-valve three wave-band radio chassis made by BEEHOVAN, A.C. mains working 110 to 250 volts, all MULLARD valves, large illuminated dial, chassis size 9 1/2 x 7 1/2 x 8 1/2 complete with ROLA speaker Ready to work, fully guaranteed price £7.17.6, carriage and insurance, 7/6.

ADJUSTABLE THERMOSTAT

250 v. heavy silver contacts can be adjusted to operate between 70 deg. -300 deg. F. These are suitable for aquarium heaters, electric blankets, etc., etc.



1 Amp. Model 3/6. 2 Amp. Model 5/6. 5 Amp Model 14/6. Post. etc., 6d. extra. Don't be cold this winter, make an Electric Blanket, blueprint 1/6 post free.



also 29, STROUD GREEN ROAD, FINSBURY PARK.




THE ELPREQ GENERAL PURPOSE AMPLIFIER

A self-contained A.C./D.C. mains operated amplifier which has applications such as for dance-band in small halls, factory call system, gram, amplifier, baby alarm, etc., will drive 4 extension speakers. Complete with hand microphone and built-in speaker in portable carrying case, fully guaranteed, 9 gns., or H.P. £3 4/- deposit, plus 5/- carr. and insurance.

LAST FEW £3/19/6 LAST FEW



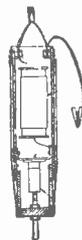The Lectross wardrobe is room as it dries clothes. Size 3ft. wide, 3ft. high and 5in. deep. It has four stove-enamelled rails and works off A.C. or D.C. mains, consuming 800 watts. Fully guaranteed. Price £3.19.6, plus 7/6 carriage.




RADIO STETHOSCOPE

A novel device aptly called a Radio Stethoscope is described in a recent edition of the "Radio Constructor." With it in most districts a receiver can be checked from the grid of the first valve right through to the output. It is a complete fault-finder. The only parts needed to make the simple circuit tracer


are a pair of crocodile clips, a germanium crystal, and a paper tubular condenser, and we will supply whole outfit for 6/6, post free, and with each outfit we will give reprint of the article as it appeared in the "Radio Constructor."

MULTI-SPEED MOTOR

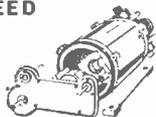Works off A.C./D.C. mains fitted with gear box any speed from 1 r.p.m. 12/6, post and pkg., 1/6.



COIL PACK SNIP

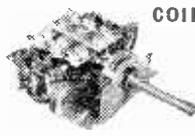

Manufactured by quite a famous company, this 3 wave Coil Pack incorporates a Gram position and Long, Medium and Short wave band, designed for 465 kc/s I.F. Brand new and fully guaranteed, complete with circuit only 10/6. limited quantity so act quickly.

LEWIS RADIO COMPANY

for

Cabinets

Send for our catalogue of R/G, T/V, Table, Speaker and Corner Cabinets.

Components

Send for our FREE 40 pp. catalogue of T/V and Radio components.

Chassis

Leaflet available on our 5V 3 W/B Superhet Radiogram Chassis.

Amplifiers

Send for details of our domestic type Amplifiers. 5 and 4½ watt.

Tape

Recorders

Full details of our new tape recorders available. Also heads, tape and mikes.

120, GREEN LANES,
PALMERS GREEN, LONDON, N.13

BOWes Park 6064

YOU can become a First Class RADIO ENGINEER

We can train you to earn good money in your spare time or start a radio business of your own. Our Home-Study Courses are easy to understand and the f.e.s are very reasonable. Post coupon now and we will send you full details in plain sealed envelope.

T. & C. RADIO COLLEGE

Post in unsealed envelope, 1d. postage

To: T. & C. RADIO COLLEGE
36, Northfield Road,
Ringwood, Hants.

NAME

ADDRESS

Fl1/53

COMMUNICATIONS RECEIVER R.1155
The famous ex. Bomber Command Receiver known the world over to be supreme in its class. Covers 5-wave ranges 18.5-7.5 mc/s, 7.5-3.0 mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s. and is easily and simply adapted for normal mains use, full details being supplied. Aerial tested before despatch these are BRAND NEW AND UNUSED IN MAKERS' ORIGINAL TRANSIT CASES. ONLY £11/19/6.

A few used receivers, also tested working before despatch, are available at £7/19/6. A few of the R.1155 N model can also be supplied. This is the latest version which covers the Trawler Bands, and in addition is fitted with ultra slow motion tuning. Used, but tested working before despatch. ONLY £17/19/6.

A factory made Power Pack, Output Stage and Speaker, contained in a black cracked cabinet, to match the receiver, can be supplied at ONLY £5/10/10. Operates receiver immediately.

DEDUCT 10/- PURCHASING RECEIVER & POWER PACK TOGETHER. Please add carriage costs of 10/6 for Receiver, and 5/- for Power Pack.

COMMUNICATIONS RECEIVER R.1224A. An ex. R.A.F. 5 valve Battery Superhet which covers 1.0-10.0 mc/s (300-30 metres), in switched wave bands. Employs RF stage and 465 kc/s I.F., large Muirhead slow motion tuning dial, aerial trimmer, reaction/BFO control, sensitivity control and H.I. impedance and 600 ohm line outputs. Exceptionally sensitive and selective. Complete with valves in wooden cabinet, with hinged lid, size 14 1/2 in. x 10 in. x 9 1/2 in. Finished in grey, with calibrated chart. Requires only 2 v. L.T., 9 v. G.B., and 5 H.T. BRAND NEW IN MAKERS' PACKING. ONLY £9/19/6 (carriage 7/6).

V.H.F. RECEIVER R.1132A. Covers 100-124 mc/s with variable tuning. Complete with all valves, and in BRAND NEW condition. ONLY 59/6 (carriage, etc., 10/6).

POWER PACK TYPE 3. Used by the Services with the above receiver. A standard 19 in. rack mounting job to match the receiver, this is for 200/250 v. 50 cycle mains with output of 250 v. D.C. 100 ma. and 6.3 v. 4 amps. Is fitted with H.T. current meter and voltmeter, and is a really superb unit, which can be used for a variety of sets. Tested working before despatch. ONLY 90/- (carriage, etc., 5/-).

RECEIVER 25/73. Part of the TR.1196. Covers 4.3-6.7 mc/s., and makes an ideal basis for an All Wave Superhet, full modification data being supplied. Complete with valves, 2 each EF36 and EF39, and 1 each EB32 and EB33. ONLY 25/- (postage, etc., 2/6).

RECEIVER R.1225. Covers 100-150 mc/s, and contains 5 valves EF50, 2 of EF39 and 1 of EB34, together with a multitude of short wave components. An excellent fitting breakdown unit for ONLY 25/- (postage, 2/6).

INDICATOR UNIT, TYPE 95. Exactly the same as the Type 62, but for 50 cycle operation. Built on a two-deck chassis, it contains VCR97 Tube with mu-metal screen, 16 valves SP61, 2 of EB34 and 4 of EA50, also shoals of components. In new condition. A snip at ONLY 59/6 (carriage, 7/6).

INDICATOR 62A. Another two deck chassis job, this contains VCR 97 tube with Mu-metal screen, 12 valves EF50, 4 of SP61, 3 of EA50 and 2 of EB34. IN NEW CONDITION IN MAKERS' TRANSIT CASES. ONLY 99/6 (carriage, etc., 10/6).

TRANSFORMERS, Ex. W.D. & Admiralty. Built to more than 50% safety factor, with normal A.C. Mains Primaries. All Brand New and Unused.
330 v.-0-330 v. 100 ma. 4 v. 3 a. 22/6.
EHT 1,400 v. 2 ma., 520 v. 10 ma., 300 v. 10 ma., 2 v. 15 a. ... 21/-
L.T. 6.3 v. 7.7 a., 4.2 v. 2.5 a., 4 v. 1 a. ... 19/6
L.T. 4 v., 20 amps. C.T. ... 30/-

Please add 2/6 per transformer postage.
AVO MODEL 40 UNIVERSAL TEST METERS. Have had some use but every meter has been thoroughly checked and tested, and is GUARANTEED IN PERFECT WORKING ORDER. An ideal opportunity to acquire a first grade tester at low cost. ONLY £9/19/6.

C. W. O. Print name and address clearly. Amounts given for carriage refer to inland only.

U.E.I. CORPORATION,
138, Gray's Inn Road, London, W.C.1
(Phone: TERMINUS 7937)

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.P.
SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEpherds Bush 1729

RECEIVERS TYPE R.1155.—These popular communications receivers with a frequency range including 20, 40 and 80 metre "Ham" bands and Long and Medium Wave transmissions in "Used" condition but in good working order, complete with seven valves and circuit diagram and data leaflet included. Aerial tested before despatch. PRICE ONLY £8/17/6, carriage 7/6. We can also supply a Power Pack, Output Stage Unit to operate these receivers direct from A.C. Mains. Fitted with moving coil loudspeaker and valves, ready for plugging straight into receiver for immediate use. PRICE, £5/10/0, carriage 3/6.

9/12 v. ACCUMULATORS.—Assembled in metal cases 8 1/2 x 8 1/2 x 6 ins. with carrying handle that folds flat when not in use. Rated at 12 v. 14 amp.-hour. Connections from each cell terminate to a threaded stem so that it is quite easy to re-arrange connections to supply say, 2 v. or 6 v. with, of course, a proportionate increase in amp.-hour capacity. In unused condition although outside of cases may be store soiled. PRICE 26/-, carriage 4/-.

FREQUENCY METERS.—Switchboard mounting, 7 in. dia. for direct connection to 230 v. A.C. mains. Calibrated 40 to 60 cycles. PRICE £4/10/0, post 2/6.

VALVE BARGAINS.—CV138 Services equiv. of 6AM6, EF91 and 8D3. PRICE, 8/- or 3 for 21/- Type 1625 exactly the same as the 807 but 12 v. heaters and 7-pin U.X. base. PRICE 7/6, or 4 for £1 (EF50, 6 for 32/6, or 12 for 59/6. All removed from new, unused equipment which we retest, box and guarantee.

6 v. VIBRATORS.—Standard 4-pin U.X. base Mallory type in brand new condition. PRICE 10/-, post paid.

NEW! OUR LATEST PUBLICATION The "HOME CONSTRUCTOR" Incorporates Circuit and FULL CONSTRUCTIONAL DETAILS

for Building Any or All of these
FIRST-CLASS SUPERHETS

1. 3-Valve Feeder Unit (3 Waveband with R.F. Stage)
2. 4-Valve Feeder Unit (3 Waveband with R.F. Stage)
3. 5-Valve 2 W. band Receiver (a) For A.C. Mains (b) For A.C.D.C. Mains.
4. 5-Valve 3 W. band Receiver (a) For A.C. Mains (b) For A.C.D.C. mains
5. 6-Valve 3 W. band Receiver (a) For A.C. Mains (b) For A.C.D.C. Mains.

Other Contents include
How to Build an Efficient Crystal Set
How to Make a 2 W. band Gram Coil Pack.
Circuits of Two Different TRF Receivers.

Detailed Instructions on Soldering Simple Metalworking for Radio General Constructional and Servicing Notes, Resistance Color Code and How to Use It. Our fully illustrated Catalogue of High Class Components is included.

This is a Booklet no radio enthusiast need be without for the price is

ONLY 2/6 ONLY
SEND FOR YOUR COPY TO-DAY

to our new offices and showrooms
SUPACOILS, 21, Markhouse Road,
London, E.17.

(Buses 685, 687; 3 mins. from St. James St. Riv. Stn., E.17.)

TRADE ENQUIRIES INVITED

The Other Side of Service

SOME INTERESTING EXPERIENCES BY A SERVICE ENGINEER OF OVER
30 YEARS' EXPERIENCE

By F. E. Apps

THE job of a service engineer can be most diverting and often amusing. The most interesting incident of any, to me, happened a few years before the outbreak of the last world war. At the time I was a field service engineer with one of our largest manufacturers, and on reporting one morning to our London depot, the manager sent for me. He informed me he was sending me on a most important job. He gave me a very impressive talk on how I must maintain the high reputation of the firm, etc. etc. I began to think that this is a Buckingham Palace job, or perhaps even the Kremlin! However, it turned out to be a visit to the Empire Nursing Home, and the client was the late His Excellency, The Marchese Marconi. He was on a visit to this country at the time and had been taken ill. One of our associated companies had lent him a set so that he could listen to Rome whilst in bed. This set had, unfortunately, broken down after a couple of days, and it was my job to put it right and ensure that it did not happen again. Of course, I felt rather proud of the assignment, but also a certain amount of trepidation, at having to service a set for, and in the presence of, the "Father of Radio."

His Excellency was in bed when I arrived and greeted me very cordially. The job was quite a simple one. Packing had been left inside the receiver and had shifted slightly, lifting the grid cap off the frequency changer. The DDT also had a slight heater-cathode leak. Changing the valve, replacing grid cap and checking over took only a few moments, and within a quarter of an hour of my arrival Marconi heard "Radio Roma" again. He was very pleased about this, and frankly informed me that he knew very little about present day receivers and could not possibly have serviced it himself. Having completed the job to his satisfaction, he then conversed with me for about half an hour. He told me that he had been conducting research into micro-waves on his yacht *Electra*. He inquired of my experience in radio and was interested to know that I had used his first receiver, the "Magnetic Detector," whilst serving as an operator in the Royal Navy. It was, in fact, a very interesting half-hour, and one that I shall always remember. I have one regret about this job. His Excellency signed my job sheet as being very well satisfied. I had to return this but made application for at least a copy to keep. Somehow it apparently disappeared at the Head Office and could not be traced. Thus I missed having a service sheet signed with the magic signature—G. Marconi.

At St. Martin's

Of the amusing jobs I think the one at St. Martin-in-the-Fields was perhaps the most laughable. My job there was to completely overhaul and, if necessary, rewire the P.A. system of the church. It took a few days to complete, owing to the church being used quite a number of times for services. When these were not occurring, one had to move quite reverently about the church as people were

continually calling in to pray. This meant that testing pulpit and choir microphones was somewhat difficult. However, the job was completed and a final test was necessary. In the crypt there was a receiver and amplifier that was used to broadcast the BBC services to the main church and this, of course, had to be checked. I switched on the receiver in the crypt and heard the BBC broadcasting some chamber music which I considered was not unsuitable for checking the speaker in the main church. I switched on the amplifier and then proceeded up to the church, but on my arrival was met by the verger who in a horrified voice said, "For goodness sake, switch off." I did so and then went to find out what all the trouble was about. Apparently, during the time between when I first heard the BBC and my arrival back at the main church, the programme had changed and hot jazz was being broadcast in the church to the consternation and horror of some old ladies who were praying there. I thought to myself, "I'm for the high jump here," but everything turned out all right. The Vicar, who I believe I am correct in saying was the late Dick Sheppard, came to the church to see me. He said: "What have you been doing in my Church?" I explained it to him and he smiled and said, "It was unfortunate. Well you won't hear any more of this but I will. Probably for the next six months some old dears will remind me about it."

He was right, I never heard any more of it, but the memory of the looks of horror on the old ladies' faces will remain with me always.

Upsetting the Conductor

Another amusing thing happened when a bunch of engineers were installing a complete new set of equipment in the Royal Opera House. This was a rather complex job with many speakers and microphones with appropriate switches and fading apparatus. It was a rush job and we were working late one evening making the final touches. There was a certain amount of hammering going on, and a certain very well-known conductor was conducting a final rehearsal. Apparently, the hammering disturbed him, for he suddenly stopped the rehearsal and shouted out to us to stop everything until he had finished. There was complete silence for a moment, then from the speaker came a tremendous "raspberry." This was caused by the chap on the P.A. switchboard getting a bit panicky and not switching off in proper sequence. When the "raspberry" was heard, the conductor, who was well known for his temperamental ways, went almost white with anger, but the whole situation was saved when the chorus burst into laughter. By this time the conductor saw the funny side of it and he even deigned to smile. In the end he got his own back by keeping that rehearsal going as long as possible, thus keeping us working well into the night to complete the job.

Pot of Earth

Of another job I went on, I had heard many times but I did not believe it until it actually happened to

me. A caretaker in one of the big city business premises had purchased one of our sets which he said was faulty, as he was getting a lot of interference. On switching on his set it was certainly noisy, but this was definitely due to electrical interference. He had an indoor aerial, although he could easily put up an outdoor one, as he occupied a flat at the top of the building. I advised him to do this and then questioned him if the set was earthed. He said yes—and a good earth, too. I checked this and found the lead going to an earthenware vase underneath the table on which the set was standing. This was filled with earth and a copper earth rod embedded in it. He was really surprised when I told him that it was useless, and he informed me he had purchased the best leaf-mould possible. I am happy to say that when he had his outdoor aerial and an earth on to a rising main water pipe, most of his troubles disappeared.

At a Mayfair Flat

Another job that was very intriguing was at a small flat near Shepherd Market. A radiogram had developed a fault on the radio. The lady had a Scottish name, but when she opened the door to me she was Parisienne to the eyebrows. The flat was rather ornate and smelt to the heavens of scent, face-powder, etc. Some rather striking pictures were on the walls, the lighting was dim—in fact the place reminded me of something I had seen somewhere before. I tackled the set and found it was an intermittent fault in an I.F. stage, but before I could locate it, the lady requested me to leave for about half an hour as she had a gentleman calling. Being desirous of a cup of tea, I acquiesced. On returning I carried on with the job, but after about ten minutes I was again asked to leave for half an hour. I had to go, but rang up head office and explained the situation. They said carry on as customer desires. Well, five times I had to leave, but eventually after six hours on the job it was completed. I only hope that her gentlemen friends stood the charge for the time spent on that job.

A Valuable Bowl

One job that was tragic for me in the first case, but later turned out O.K., was when I was sent to install a large radiogram for an M.P. At the time this M.P. was the Chief Whip. An anti-interference aerial had to be fitted at the same time, so a man was sent to do this with me. I went up on the roof, which was easily accessible, and pointed out where the aerial was to be fitted and where the screened down lead was to run. I then went down to the set to remove transit bolts, etc., and check over. By this time the aerial engineer had rigged the aerial and run the down lead outside the room where the set was being installed. I instructed him to wait until I had inspected the aerial before bringing the screened lead into room. I went up to the roof wearing a raincoat and inspected aerial and down lead. Finding everything O.K., I came down, and my coat being wet (it was raining), I went down to the servants' quarters to hang it up. Whilst talking to the butler below stairs, we both heard a terrific crash from up top. On investigation we found that the aerial engineer had ignored my instructions, entered the room and knocked over a glass bowl. The pieces were swept up and I carried on with the job. When finished, I rang up head office and told them of what had occurred. They asked me to estimate the damage. I quoted 4s. 6d. Glass bowls of that description were approximately that price.

Two days later both the aerial engineer and myself were on the carpet. The glass bowl turned out to be a family heirloom, approximate value £2,000. Both of us were sacked by the London manager. Of course, I was not satisfied with this and immediately wrote to the M.P. in question, pointing out that it was in no way my fault as his own butler could testify.

The happy result was that this M.P. wrote to the firm to waive all claims if I was reinstated, and I am glad to say that this was done. So now, of course, I say M.P.s are sometimes quite useful.

Heir to Millions

I once had to make a service call on Barbara Hutton, who at the time was living at Hyde Park Gardens. At the time much publicity was being given her and her baby son. I was shown into a room by the butler and left to get on with the job. When it was completed the butler came back and asked me if I would like to see the baby which was just being taken out for an airing in the park by his two nurses. I went and saw him, but when the butler said "See how he smiles," I could not help saying, "Who wouldn't, if they were worth a couple of millions." The room where the radiogram was installed was practically empty except for a couple of sideboards and a cabinet, on and in which were what appeared to me to be some old vases and bowls. The butler informed me that these were real Chinese jade and worth over £100,000.

Book Received

"GUIDE TO BROADCASTING STATIONS,"
7th edition. Published on September 1st, 1953,
by Hiffe and Sons Limited. Size D16mo, 5½in. by
4½in. 104 pages. Price 2s. (postage 2d.).

This useful little book has been fully revised and enlarged for its seventh edition, and now provides data (corrected to August 1st, 1953) on the world's broadcasting stations. The book lists first in order of frequency and then geographically all the European long- and medium-wave stations, and over 1,600 short-wave broadcasting transmitters working on a power of over 1 kilowatt throughout the world.

The long- and medium-wave list shows the channel allocated to the station under the Copenhagen Plan, the frequency, wavelength and output power. The short-wave list shows the frequency, wavelength, output power and call. Entries have, with the co-operation of the BBC, been checked against frequency measurements made at the Tatsfield Receiving Station.

Other tables give operating details of some 40 television stations in Europe, over 160 European metre-wave stations (four times as many as in the previous edition), consol transmitters and standard frequency stations. Another useful feature is the table of international call sign prefixes covering the world.

WIRELESS COILS, CHOKES & TRANSFORMERS

8th Edition

6/- or 6/4 by Post from

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, London, W.C.2

Volume Controls

Midget Edison type. Long spindles. Guaranteed 1 year. S.P. sw. 3/-. D.P. Sw 4/-. ALL VALUES. — 10K. to 2 MEG.

80 ohm COAX CABLE STANDARD 1/4 in. diam. Polythene insulated. REDD (CFT) PWT. 9d. A YARD. NOT E.C. cert. COAX PLUGS. 12 each. SOCKETS. 12 each. LINE CONNECTOR. 12.

BALANCED TWIN FEEDER per yd. 6d. 80 TWIN SCREENED FEEDER per yd. 1/- 5 ohms 50 OHM COAX CABLE. 8d. per yd.

TRIMMERS, Ceramic. 30, 70 pf., 9d.; 100 pf., 150 pf., 1.3; 250 pf., 1.6; 500 pf., 1.9.

RESISTORS.—All values: 1/4 w., 4d.; 1/2 w., 6d.; 1 w., 8d.; 2 w., 1.1; 3 w., 1.4; 5 w., 1.9; 10 w., 2.6; 20 w., 4.1; 30 w., 5.6; 50 w., 8.1; 100 w., 12.6.


WIRE-WOUND RESISTORS.—Best Makes Miniature Ceramic Type—5 w., 15 ohm to 4 K. 1.8; 10 w., 20 ohm to 6 K. 2/3; 15 w., 30 ohm to 10 K. 2.9; 5 w. Vitreous, 12 K. to 25 K., 3/-.

WIRE-WOUND POTS. 3 WATT, FAMOUS MAKES.—Pre-Set Min. T.V. Type Kurel, Slotted Knob. All values 25 ohms to 20 K., 50 K. and 100 K. (Carbon Track). 3/4 each. 84 ohm size Pots, 2 1/2 in. Spindle. High grade. Ad. Values. 100 ohms to 50 K. 5/6; 100 K., 6/6.

OP TRANSFORMERS.—Tapped small pentode. 3.9. Heavy duty 70 ma., 4.6. D10, tapped, 4.9. L.F. CHOKES 10 h., 65 ma., 4.6. 20 25 h., 100 150 ma., 12.6. 5 h., 250 ma., 16-. 4 h., 100 ma., 10.6. LYNX, choke, 3 h., 250 ma., 13/6.

MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-leaved and impregnated. Heater Trans., tapped prim., 0.290/4/250 v., 6.3 v. 1 1/2 amp., 7.6. 330/0.520, 50 ma., 6.3 v. 4 a., 7.8 v. 2 a., ditto 200-0.300 ditto 250-0.250. 21/-, Viewmaster, auto type, 35/-. Teleking, 30-. Lynx, 30-. Coronet, 30-.

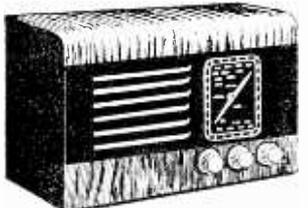QUALITY P.P.O. TRANS. 20 w., special Stavov 4 a. lams. Sectionalised, low leakage windings, primary inductance 70H., leakage inductance 0.057H., secondary impedance 3 and 15 ohms. Primary impedance to individual requirements, fully shielded and terminated. 3 sets. D10's as above 15 v. output, 21 gns. Part Post and Packing (all Chokes & Trans.) 1/- extra p.p.s.



MIDGET WALNUT CABINET.—12in. x 7in. x 5in. complete with punched chassis, dial, back-plate, crum. drive, spring, pointer, etc. 28.6. 6d. per set 2/-.

TYANA.—Midget Soldering Iron. 200-220 v. or 230-250 v., 16/9.

EX GOVERNMENT UNITS.—Our selection, 3 different. All containing useful parts. TO CLEAR crum. paid, 15/-.

TAG STRIPS.—2-way, 2d.; 3 to 5-way, 3d.; 6-way 9d. PLATED Terminals, 6d. each.

TERMINAL BLOCKS.—2-way, 9d.; 4 w., 1.6; 6 w., 2.3, etc., up to 12 w., 4.6.


MARY ANN Vacuum Cleaner Flexible Hoses, plated ends, 1 1/4 in. diam. fitting, 10.6. 12ft. appliance lead, switched-connector and combination adapter, 6/9.

EXTENSION LOUDSPEAKERS.—6 1/2 in. P.M. 3 ohm unit, less transf., attractive wooden cabinet, complete, 35/-.

SCREENED GRID CAPS int. oct. or Mazda, 6d. each.

TV. AERIALS.—Full range popular types in stock, Aerialite, etc. All channels. Indoor lot type Inv. T., 13.6. Outdoor single dipole, 37.6. H type with chimney fastings, etc., 92.6. X type Duplex, 71/-, mast and chimney fastings, etc., 88.6. Fridge models available. Ask for quotation.

TOGGLE SWITCHES EX-GOV. "On-Off," 9d. Moore solder 0040, 10/3, 5.6. 1/4 in. 1d.; 1/2 in. 1d.; 3/4 in. 1d.; 1 in. 1d.; 1 1/4 in. 2d.; 1 3/4 in. 2d. PVC Com. meeting wire, 10 columns. Single or Staggered, 2d. 1/4. B70 Valveholder and Receiving Cam, 1.6. V-holders, octal, pent., 4d.; moulded, 6d.; EP50, B70, 9d.; B8A, B9A, 1d.; B12A (CPT), 1.3. etc. 2 K. 5 w. H.D. w/w Pots, 4/6. 10 K. C50's w/w Pot, 1in. spindle, 3/6.

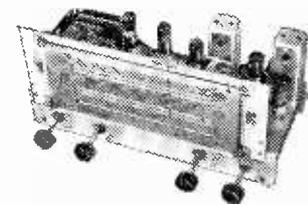

ALL WAVE RADIOGRAM CHASSIS 3 WAVEBANDS LATEST VALVES

S.W. 16 m. — 50m. LATEST MULLARD MIDGET SERIES ECH 42, EF 41, EBC 41, EL 41, LW, 80mm. — 2400mm. EZ 40. Brand New and Guaranteed, complete with 10L1 P.M. Speaker. A.C. Mains 200-250 v. operation. Voltage selector. Parmeko Mains Transformer. Four position Wave-change Switch, short-Medium-Long-Carrier slow Motion Tuning. Provision for E.C. speaker and Pick-up connections. High Q insulated core coils, 465 kc/s I.F. Latest circuit technique incorporating delayed A.V.C. Supplied complete with High Flux 10in. P.M. Speaker. 2 ohm output transformer mounted on chassis. Heavy enameled plated chassis size 12 x 2 1/2 x 2 1/2 in. Attractive glass dial 10in. x 4 1/2 in. horizontal or vertical type available. Edge lit by 2 pilot lamps. Background colour Black with distinctive colouring for station names. L.W. Green, M.W. Red, S.W. White. Four 1 1/4 in. diam. Control Knobs supplied, either Walnut or Ivory to choice. Completely aligned and calibrated, ready to fit in Cabinet. PRICE £10 15.0. Carriage and Insurance, 4/6. (Without 10in. Speaker, £9.15.0. Carr. & Ins., 4/6.)

BARGAIN OFFER

RECOMMENDED FOR ABOVE CHASSIS EDISWAN 73 r.p.m. Single-player Gram Unit, High Impedance Magnetic Pick-up. Press lever started for 10" or 12" records, auto stop. Listed 7gns. Our Price £4/10 Carriage 2/6

Table with columns: NEW EXOD, VALUES, ALL GUARANTEED. Lists various electronic components like valves, capacitors, and resistors with their respective prices.

SPECIAL PRICE PER SET: 1R5, 1P4, 1R5 and 3R4. 32.6. G88, G87, G86, 5Z1 or G85. 40. VIEWMASTER. Set of 12 valves, £8 10/-, With E551, 47. TELEKING.—Set 17 valves, £9 10. LYNX.—Set of 17 valves, 29. CORONET.—Set 17 valves, 45/-. *E.B. DIAL ASSEMBLY, Type S.L.B. 28.6. LINE COIL.—22v., 100 ohms per foot, 30v., 60 ohms per foot, 2-way 1.6 a yard, 2-way 1.8 a yard. SLEEVING.—Various colours, 1, 2 mm. 2d.; 3 4 mm., 3d. yd.; 6 mm., 5d. yd. MAINS DROPPERS.—Glo., x 1 1/2 in., Adl. slides 3 amp. 750 ohms, 2 amp. 1,000 ohms, ea. 4.3. P. and P. 6d. £1 order, post free. Lists 3d

T.R.S. RADIO COMPONENT SPECIALISTS 307, WHITEHORSE ROAD, WEST CROYDON. THE 1953 Mail Order: 71, MEADVALE ROAD, EAST CROYDON

CONDENSERS.—New stock best makes .001 mfd. 6KV. T.C.C., 5.6. Ditto 12.5 kv. 9.6; 902 Mair-head 8 KV., 2.6; 2 pf. to 500 pf., 6d.; 901, .005, .01, T.C.C., 500v., 52 N.S.P. 500 v. Tub., 1 mfd. 350 v. Microfilm Tub. 8d.; 35 N.S.P. or Duffiler, 1 mfd. Hunts 500v., 1.5; 25 mfd. 300 v. Hunts, 1.6; 5 mfd. 500 v. Hunts, 1.9; 01 Sprague short ends, 5d.

ELECTROLYTICS ALL TYPES NEW STOCK. Tubular Wire ends 145 450 v. T.C.C., 3/6 450 v. B.E.C., 2/6 16 500 v. Duffiler, 4/- 27 500 v. B.E.C., 4/- 10 500 v. Duffiler, 2/6 16 500 v. Duffiler, 4/- 20 350 v. B.E.C., 8/6 16 500 v. B.E.C., 3/- 3+8 500 v. Duffiler, 4/6 32 450 v. Duffiler, 4/- 3+16 450 v. B.E.C., 5/- 3+16 500 v. Duffiler, 5/6 16+16 450 v. B.E.C., 5/6 25+16 500 v. Duff., 6/6 50 12 v. T.C.C., 1/9 32+32 275 v. Duff., 4/6 50 25 v. Duffiler, 1/9 32+32 250 v. 2+25 25 v. 50 50 v. T.C.C., 2/- in same can B.E.T., 6/6

SPECIALS.—(Can Types) 500 mfd. 12 v., 3/-; 1000 mfd. 12 v., 5/-; 2,000 mfd. 6 v., 4/6; 16 mfd. 700 v. Hunts, 6/6.

SENTERCEL RECTIFIERS. E.H.T. TYPE—K3 25 2Kv., 4.3; K3 40 3.2 Kv., 6/-; K3 45 3.6 Kv., 6.6; K3 50 4Kv., 7.3; K3/100 5Kv., 12/6; K3/100 14 K., 18/-. MAINS TYPE.—RM1, 125 v. 60 ma., 4/-; RM2, 190 ma., 4/9; RM3, 120 ma., 5/6; RM4, 250 v., 275 ma., 16/-. KNOBS, GOLD ENGRAVED.—Walnut or Ivory. 1 1/4 in. diam., 1.6 each. "Focus", "Contrast", "Brilliance", "Volume", "On-Off", "On-Off", "Volume", "Val.—On-Off", "Tune", "Tuning", "Tribble", "2", "Wavechange", "Radio Gram", "S", "M", "L", "Grant", "Record-Play", "Brightness", Ditto not engraved, 1/- each. COILS.—Wearite "P" type, 2/6 each. Midget "Q" type, adjustable dual core, 3/6 each. All prices.

RECTION COND.—0001, 0003, 0005 5lv., 3.8 ea. SURPLUS MAINS TRANS.—Prim. 0-200/250 v.; Sec. 275-0-275 v., 60 ma. 6v. 3 a., 6.3 v. 1.6, 10.6; ditto, 260-0-260 v., 50 ma., 6.3 v. 3 a., 6.3 v. 1 a., 12.6. Oscilloscope Transf. Prim. 0-230 v. Sec. 0-15 15 ma., 5 v. 2 a., 5 v. 2 a., 4 v. 1 a., 47/6. P.P. All Trans. 1/-.

BATTERY CHARGER.—200-250 v. Output 6 v. and 12 v. 1 1/2 amp., in steel case complete with fuse and leads, ready for use. OUR OWN MAKE. FULLY GUARANTEED, 25/-, P. & P. 1/-.

CHARICER TRANSFORMER.—0-200-250 prim., sec. 0-90-15v. 1 1/2 amp., 18/6.

BATTERY ELIMINATORS.—Trans. 0-200/250 v., 150 v. 30 ma. 4 v. 1 a., 3.16. SPECIAL SMOOTHING L.C. CHOKES MADE TO ORDER.

G.E.C. FULL WAVE BRIDGE TYPE RECTIFIER.—6 to 12 v. D.C. 1 1/2 amp., 8.9. 6v. 1 amp. 9.0-9 v. A.C. 5.6.

C.R.T. HEATER ISOLATION TRANSFORMER.—Low leakage winding with 25% insulation, 2 v., 10.6; 4v., 10.6; 6.3 v., 10.6; 12 v., 10.6.

FUSES.—1 1/4 in. all values 60 ma. to 10a., 6d. H.F. MIDGET CHOKES.—14 M.H. 2.6 each.

BRIMISTORS.—C21 for 3 a. heater chains, 3/6. (C22 for 1.5 a. or 2 a., 2.6).

COPPER ENAMEL WIRE.—1 lb. reels 16 to 20, s.w.g. 2 - 22 to 28 s.w.g., 2.8; 20 to 40 s.w.g., 3/6

WIDE ANGLE SCANNING.—Full range Allen, Teleking, and Viewmaster. Also Soundmaster components in stock. Instruction Envelope, 6/6.

TWIN GANG STANDARD SIZE.—With feet, .0005 mfd., 8.6; D10 midget, 7.6. 375 pf. midget twin gang, 6.6. BARGAIN .0005 mfd. twin gang, slightly soiled, 5.6.

RESISTOR TAG PANELS.—Clearance Bargain from Brand New Units. A fair variety of 1 1/4, 1 and 2 w. and w resistors (average number 45-50). Sold by weight—one price (unless they last, 3/- per lb., P. & P. incl. Satisfaction guarantee or money refunded).

ALADDIN FORMERS and cores, 2in., 8d.; 3in., 10d. SLOW MOTION DRIVES.—Epicyclic ratio 4 : 1, 2.3.

LOUDSPEAKERS P.M., 3 OHM. 3in. Plessey, 12.6. 5in. Plessey, 13.6. 6 1/2 in. Tinsov, 14.8. 8in. Lectrom, 15.6. 10in. Lectrom, 25/-. 5in. C.E.C., Energised 700 1/2 field with trans, 19.6.

WAVELENGTH SWITCHES.—2 p. 2-way, 2/6; 3.6 2 p. 3-way, 4.1. 2-way, 3 p. 3-way, etc.

CRYSTAL DIODE.—Very sensitive. G.E.C., 3.6. B.T.H., 2.6. H.R. PHONES (S. G. Brown), 15.6 a pair.

BARGAIN VALUE I.F. TRANSFORMERS 465 Kcs Slug Tuning Min. Circular Can, 2 1/2 in. and 1 1/4 in. diam. Fits octal V-holder cut out. Very high Q, ex Pye. BRAND NEW 6/9 PAIR

FIRST-CLASS RADIO COURSES . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit., I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of


SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSES

NATIONAL INSTITUTE OF
ENGINEERING

(Dept. 461), 148, HOLBORN,
LONDON, E.C.1

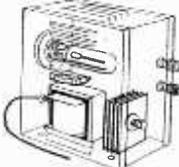

"AUTOMAT" CHARGER KITS

No. 2 kit as shown, built in one hour, simple, foolproof, troublefree. All new material with full guarantee, and ample rating. No. 2 kit, 12/14v. 3 amp. Westinghouse selenium rectifier. 12v. charger, 46"; case, screws, grommets, 12/6 extra, post 2/-.

No. 1 kit, similar but 2 amp. rectifier. 45 watt trans., ballast indicator bulb for 2v., 6v., 12v. charger. 38/6; case 12/6; post 1/10.

Eliminator kit, trans., H.T. rect., 2v. 12v. trickle rect., condensers, case, for 120v., 20 mA. eliminator 37/6 P.P. 1/10.

CHAMPION PRODUCTS,
43, Uplands Way, London, N.21.
Phone: LAB 4457.

STAN WILLETTS

43, SPON LANE, WEST BROMWICH,
STAFFS.

Tel.: WES 2392

R1132A.—U.H.F. receiver (100-124 Mc s). Complete with 11 valves, 4 EF39, 2 SP61 P61, 6J5, V570, EB34, EK32, 5 m.a. meter, with circuit. Brand New, in transit cases, 57/6. Used, good condition, 47/6. Carr. 7/6.

5 VALVES.—Brand New, Guaranteed, 12A47, 6V6G, 6V8GT, 5U3G, EL91, 7.6, 12AX7, 6CH6, 6X4, 8D3, 6AM6, 1R5, 354, W77, 6.9, 5763, 9.6, EA50, 1.9, 3D8, 2.3, EC32, 4.9, RK34, 1.9, 954, 1.6, 65N7, 8.6, ARF12, VFP3, 3.6, SP61, 3.6, VU19, 3.3, ECH35, 11.6, 12U5, 2.9, Red EF50, Sylvania Red, 5-, 53KU, 7/6. Post extra.

TWIN GANG 1 meg. p.d.s., 2.6. Post 3d.


INDICATOR, TYPE 62A, brand new. Complete with valves, 25/10, carr. 0/6.

32 MFD. CONDENSERS, 450 v. Brand new, 6 for 7/6. Post 1/-.

GERMANIUM CRYSTAL DIODES, New, G.C.E.C., wire-end 2 - each; 3 for 5/-. Post 3c.



Magna Cartridge

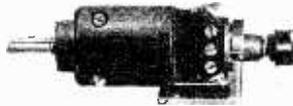

Completely Tropicalised. Tested under extreme conditions of Heat and Humidity (125° F. with 95% humidity) without deterioration and loss of output.

- Output comparable to Crystal Pick-ups.
- Cantilever Stylus Protecting Records and eliminating Needle-talk and surface noise.
- Stylus easily replaceable.
- Will fit three-speed record changers and units.

No. 200. Price £11.10.0. P. Tax 9/9.
Now available as a complete Pick-up.
No. P.200. Price £25.0.0. P. Tax 14/0.

For full technical details write to:

ERWIN SCHARF

49-51a, De Beauvoir Road, London, N.1
Telephone: CLISSOLD 3434.

Best Buy at Britain's

R1224A RECEIVER. A 5-valve battery superhet covering 30-300 Mc/s (includes shipping band). Requires H.T. 120 v. G.B. 9 v., and I.T. 2 volts. Brand new with all valves and circuit. ONLY 79/6, plus 7/6 carriage.

R1132A RECEIVER covers 100-124 Mc/s with variable tuning. Complete with 11 valves and circuit. A bargain at 45/-. plus 7/6 carriage.

R1155A RECEIVER for world wide reception. Brand new and air tested at £11.19.6. A few only soiled at £7.19.6. Carriage 10/6 extra. Send 13 for circuit details.

R1155 POWER PACK and output stage for A.C. mains operation. £4.10.0, plus 3/6 carr. REDUCTION OF 10/- when set and power pack purchased together.

SEND S.A.E. FOR DETAILS OF ALL THE ABOVE.

TR1196 RECEIVER 25 73 complete with 6 valves. Brand new condition with full conversion data. GIVEN AWAY at 22/6, plus 2/6 carr.

AMPLIFIER A1135A, complete with 2 valves and conversion data. 17/6, plus 2/6 carr.

RECEIVER R1225 contains 5-EF50, 2-EF39, 1-EB34 and loads of components. 25/-, plus 2/6 carr.

METERS. 2 1/2 in. square, moving coil, new and boxed. 0-1 mA. at 12.6, 0-20 volt at 7/6, 0-5 mA. at 7.6, 0-500 mA. Thermo-couple at 5/5, 2 1/2 in. barrel 0-200 mA. at 10/6.

AVOMETER MODEL 40. Only slightly used, all tested at £9.19.6.

T.V. PRE-AMP. Uses 2-EF50's, tunes to 45 Mc/s. With valves, 19/6; less valves, 10/-; Post 1/- extra.

RED SYLVANIA EF50 at 8/6 each. British EF50 at 5/-. Post 6d. extra.



CHARLES BRITAIN

(RADIO) LTD.

11, Upper Saint Martin's
Lane, London, W.C.2. TEM 0545

Shop hours, 9-6 p.m. (9-1 p.m. Thursday)

—OPEN ALL DAY SATURDAY—

MICROGRAM AMPLIFIERS



NEW MODEL £3.19.6 P. & P. 2/6d.

Fits inside your record player leaving room for speaker. Dimensions 10in. x 3 1/2in. x 2 1/2in. 4 watts quality output. Suitable for all speakers and with standard or L.P. pick-ups. Built-in powerpack for 200-250 v. A.C. only. Valves 6J7 and 6V6 available at 20/- per pair extra, if required. Other models up to 10 watts.

6d. stamp for illustrated details.
ELECTRO-ACOUSTIC LABS
TAIN—ROSS-SHIRE, SCOTLAND

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH

CALL OR SEND DRAWINGS
FOR QUOTATION

B. KOSKIE

(DEPT. C.)

72-76 Leather Lane,
Holborn, E.C.1

Phone: CHAncery 6791/2

REX RADIO 37, LOUIS STREET, LEEDS, 7.

PLEASE PRINT NAME AND ADDRESS

OPEN TO DISCUSSION

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

The Beginner's Guide

SIR,—After 10 years thinking about radio I have at last been able to make a start through your series "The Beginner's Guide to Radio." Many thanks.—A. HOLT (Doncaster).

Double-triode Mixers

SIR,—Reading J. K. Bradley's letter in the July issue strengthened an opinion I have formed—that miniature valveholders are unsatisfactory. The heterodyne effect, of course, does not require critical conditions, so the probable explanation would be poor contact of the valve pins, put right by re-wiring and so moving the contacts slightly.

I have found that putting in a 12AT7 valve several times may result in loss of contact. One has to ascertain that both filaments are glowing and sometimes even to connect a milliammeter to make sure that the anodes and grids are in circuit.

Miniature valves should really all be made for direct connection by soldering, like deaf-aid valves. Transistors, no doubt, when they come will be soldered permanently in place, thus avoiding erratic contact and time wasted in tracing these faults.—W. CLELAND (Glasgow).

Early Readers

SIR,—With the coming of 25 years of PRACTICAL WIRELESS, I have been wondering just how many qualified engineers owe their grounding to the paper. In my own case I first started taking the paper in 1935, and although there were many things in it I did not then understand, I made my first valve circuit from it and it worked. A month or so later a complete article was devoted to reaction circuits, and I made them all with bits and pieces out of the junk box. In those days it was the regular thing to make your own coils, and what coils they were—perhaps 4in. diameter and wound with 20G wire. The "Q" must have been terrific, and I wonder if the modern so-called High "Q" coils will ever be as efficient, but then one can now make a complete receiver in the same space as the coil alone took up. I have never been over-thrilled with short-wave reception, but then my first short-wave receiver was an old PRACTICAL WIRELESS design with the H.F. choke wound on a test tube and mounted with a nail fixed through the cork, and it was really efficient. These circuits, like most of the PRACTICAL WIRELESS circuits, were ones that really did work if the instructions were followed.

Later I decided that I would like to get away from

the amateur side of radio and really get down to the theory side so that I could do my own research and develop my own circuits. This study was not such hard work as the interest was there, and in many cases old PRACTICAL WIRELESS circuits gave good practical examples of applications of the theory. For instance, whilst studying meter design I looked up an old PRACTICAL WIRELESS and there, sure enough, back as far as 1936, was a series of articles of multi-range meter design, complete with all the calculations.

That is but one example, and although I have progressed to the point where I am now able to write for others, there is one strange thing about the journal—it is always finding something new to teach me!!!!
—JAMES S. KENDALL (Birmingham).

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

SIR,—May I offer my congratulations to PRACTICAL WIRELESS upon its 21st year of publication, and thank you for the many hours of pleasure I have derived from reading it and building apparatus described within its pages.

Like a great many readers I can claim to have bought PRACTICAL WIRELESS since its first issue in 1932, but if my memory serves me right, PRACTICAL WIRELESS is older than its first issue.

At the time of its birth I was a regular reader of *Hobbies Weekly*, which was then being edited by F. J. Camm, and PRACTICAL WIRELESS first appeared as a supplement to *Hobbies*, so I think I can claim that little bit extra.

The number of sets I have built over the years have been many, some very successful (when I kept to specified data) and some complete failures (when I wandered off by myself), but my greatest thrill was when I completed your electronic organ (built strictly to spec.).

Once again congratulations and may you give me the same pleasure over the next 21 years.—A. G. BRIDGE (Ilford).

[The Editor and Staff wish to thank the hundreds of readers who sent letters of congratulation on the occasion of our 21st Birthday and for the good wishes which were expressed. A small selection of these is given above, but they were too numerous either to publish or acknowledge individually, and we therefore take this opportunity of expressing our thanks.]

A Record Amplifier


SIR,—I feel that perhaps you sometimes like to hear from your readers the results of circuits published in your magazine, when built and used by the ordinary amateur such as myself.

DIRECT FROM THE MANUFACTURER

DULCI RADIO/RADIOGRAM CHASSIS

Built to Highest Technical Standards
FULLY GUARANTEED

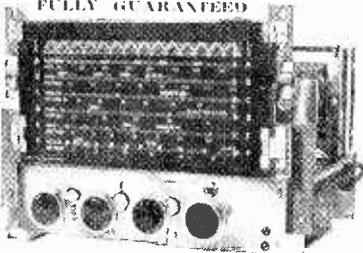All chassis 11 1/2 in. x 7 in. x 8 1/2 in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 tone positions for radio and gram.



For A.C. Mains 100/120 and 200 250 volts

- Model B3.—Long, Medium, Short 5 Valves. Output 3 1/2 watt **£12/12/0**
- Model B3.—Plus Push Pull Stage 6 Valves. Output 6 watt **£15/15/0**
- Model B3.—Double Feature with P Pull & R.F. Stage. 7 Valves. Output 6 watt **£18/18/0**
- Model B6.—Six Wavebands, Med.Long, 4 Short. (3 Bands spread.) 5 valves. Output 3 1/2 w. **£15/15/0**
- Model B6.—Plus Push Pull Stage 6 Valves. Output 6 watt **£18/18/0**
- Model B6.—Double Feature with P Pull & R.F. Stage. 7 Valves. Output 6 watt **£23/2/0**

ALL PRICES TAX PAID

Escutcheon for 9in. x 5in. dial, 4/9 extra. Matching speakers P.M. Type 3 ohms, 8in. or 10in. available. Chassis sent under money back guarantee conditions against re-shipment. Free particulars from the manufacturers.

THE DULCI CO. LTD.,

99 VILLIERS RD., LONDON N.W.2. Telephone: Willesden 7778



for every kind of TAPE RECORDING

"Scotch Boy" Magnetic Recording Tape now comes in six reel sizes, to provide an even wider range of playing times for all private and profession tape recordings.

"Scotch Boy" offers uniform sensitivity, fidelity at low speeds, and high signal noise ratio. Its medium coercivity (250 Oersted's) makes for easy erase. Distortion and transfer are negligible.


Its cellulose acetate base gives strength and smoother operation in all makes of tape recorders.

300 ft.	600 ft.	2,250 ft.	2,400 ft.
1,200 ft.		3,000 ft.	& 3,280 ft.



Another
3M
COMPANY
Product

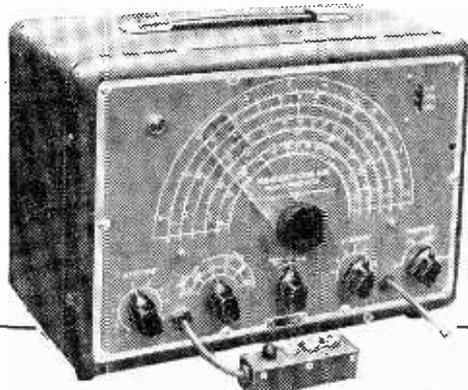Used by the B.B.C.
Write for further particulars to: MINNESOTA MINING & MANUFACTURING CO. LTD
167 STRAND, LONDON, WC2
Temple Bar 6,363



MODEL 66A Signal Generator

A newly designed R.F. Signal Generator of improved performance and reliability. Wide range and accuracy make it the ideal instrument for modern Radio and Television work.

RANGES.

- 100-320 kc/s. 3.2-10 mc/s.
- 320-1,000 kc/s. 10-30 mc/s.
- 1,000-3,200 kc/s. 30-80 mc/s.
- 60-160 mc/s (2nd harmonic).

Ease of reading ensured by direct reading fundamental frequency calibration 100 kc/s to 80 mc/s on long, clearly-marked scales, 5 1/2 inches in total length.

ACCURACY. Frequency calibration accuracy is within ± 1 per cent.

R.F. OUTPUT. Modulated or unmodulated R.F. output is available up to 100 millivolts at all frequencies. A well screened co-axial output lead is provided, 75 ohms impedance. The terminating unit offers choice of two output levels and incorporates an artificial aerial

ATTENUATION. Coarse and fine low impedance attenuators control the R.F. output over a total range of 100 db., minimum output 1 microvolt

MODULATION. Provided by a separate internal oscillator of good waveform, operating at 400 cycles per second and modulating to a depth of approximately 30 per cent. This oscillator is also used to provide an Audio Frequency output variable up to approximately 1 volt.

SCREENING. Scientifically designed double screening eliminates all unwanted R.F. leakage.

PROMPT DELIVERY

£22 . 10 . 0

- Write for Catalogue

or £3.7.6. deposit and 10 monthly payments of £2.3.0. From your usual supplier.

TAYLOR ELECTRICAL INSTRUMENTS LTD.

Montrose Ave., Slough, Bucks. Slough 21381

VIEWMASTER

Complete kits, stage-by-stage, and single components, as specified, supplied immediately from stock. SEND FOR STAGE 1 NOW, £3/2/3 post free. Construction Envelope, 76. Components also for Wide-angle VIEWMASTER, VIEWMASTER Pre-Amplifier, VIEWMASTER Extra E.H.T. Assembly, TELEKING, MAGNAVIEW, and SOUNDMASTER, etc. from stock. ELECTROLYTICS.—450v. wkg. (Gtd. New Stock), 4 mid. 1/6, 8 mid. 2/-, 16 mid. 3/-, 8 3 mid. 3/6, 8-16 mid. 4/-, 16-16 mid. 4/6. P.M. LOUD-SPEAKERS (3-ohms). 3in. 13/6, 5in. 14/6, 6in. 15/6, 8in. 18/6, 10in. 22/6. GERMANIUM CRYSTAL DIODES 3-6. B.I.C., 0.1 mid. 3 kv. TV Condensers, 10/6. H.R. HEADPHONES, 18/6. SOLON Miniature SOLDERING IRONS, 19/6, 6in. ENLARGERS (for VCR97), 17/6, 10 h. 50 mA. SMOOTHING CHOKES, 5/6. 9in. Old Aspect CREAM RUBBER MASKS, 5/6. WEARABLE "P" COILS, 3/-. ALL CHASSIS, 2/1in. deep. 6in. x 4in. 4/6, 8in. x 6in. 6/-, 10in. x 7in. 7/-, 12in. x 8in. 9/-, 14in. x 8in. 13/-, 16in. x 9in. 14/-. B.I.A. FOCUS RINGS, R10 Mk. II 23/6, R20 Mk. II 30/-. R25 Mk. II 32/6. TRANSFORMERS (Mains input, Standard Primaries, 250-0-250v. 80 mA., 0-4-8.3v. 4 A., 0-4-5v. 2 A., 19/6. Ditto but 350-0-350v. 12/6; 250-0-250v. 100 mA., 6.3v. 3.5 A. 2 A., 28/6; Ditto but 350-0-350v. 28/6. MAINS TRANSFORMERS for PRE-AMPLIFIERS, TEST-GEAR, etc. PRIMARY, 230/240v. SECONDARIES, 0-250v. 30 mA. (for 250v. from a half-wave rectifier), and 6.3v. 1 A. Price, new and guaranteed, 14/9.

ORDERS UNDER £1 please add 1/- P. & P. Orders £1 and over please add 1/9. FOR INSTANT SERVICE—WRITE:

CITY & RURAL RADIO,
101, HIGH ST., SWANSEA, GLAM.
Telephone: Swansea 4677.

Amateur Radio Enthusiasts
THE INCOMPARABLE
GLOBE-KING

SINGLE VALVE S.W. RECEIVER
● WORLD-WIDE RANGE 11-100 METRES ● CRYSTAL-CLEAR NOISE-FREE RECEPTION ● ELECTRICAL BAND-SPREAD TUNING ● EXTREMELY LOW RUNNING COSTS
Catalogue Free. Stamp for postage.
JOHNSTON (RADIO)
46, FRIAR STREET, WORCESTER

1-Finger Pianists

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

C & S, 10 Duke St., Darlington, Co. Durham

Aluminium TV Tube.—3in. and 7/16in. dia., 6d. ft., 3in., 7d.
Co-axial Cable.—50 ohms, 9d. yd.; 75 ohms, 10d.
Twin-Feeder.—75 ohms, 6d. yd.; Screened 1/3, 300 ohms (K-25), 9d. yd.
Variable Condensers.—500 pF, 3 gang, 7/6 each.
Carbon Microphone Transformers.—New and Boxed, 1/- each.
Micro-Ammeters.—0-50 microamps, 30/- each.

Orders over £2 Carr. Paid. Under, 1/3. Send 6d. for 24-page Catalogue. Visit our Shop, open 8.30-6, inc. Sats. Tel.: St. Albans 5951.

BOLD & BURROWS (G3HEO),
12-18, Verulam Road (A5),
St. Albans, Herts.

"CORONET FOUR"

FOR GUARANTEED RESULTS AND FIRST-TIME SUCCESS. USE ONLY GENUINE PARTS

AS SPECIFIED BY THE DESIGNER OF THIS FINE RECEIVER!

- We can supply:
- 1 meg. vic with sw. ... 6/6
 - "Coil Pack R.L.30 ... 25.5.11
 - "R.L. I.F. transformers ...
 - "J.B. S.L. assembly ...
 - "J.B. 0003 2-gang ...
- "Aligned and Sealed as Matched Unit as Specified, or*
R.L.30 499. R.L. I.F.'s, 16- pr. Valveholders ... 9d. ea.
Mains Connector ... 3/9 complete
Knobs ... 11d. ea.
- MULLARD valves specified (new BVA) set of four £3.19.8
- Resistors, Silvertex ... 6d. 2-
 - " 1 watt ... 8d. ea.
 - " 2 watt ... 1/- ea.
 - Condensers, paper type ... 9d. ea.
 - " silver mica ... 2/9
 - " 50/pF ... 4/9
 - " 15/pF ... 6/3
 - " 30/pF ... 6/3
 - Clips (2) ... 6d ea
- Sundries: As listed on Blueprint. 3/2 complete. 2 pilot bulbs and holders (if required) to match SL3. 3/4 complete.

2/6 will bring you BY RETURN OF NEW HOME CONSTRUCTOR'S HANDBOOK containing DETAILS for Construction, LARGE blueprint circuits, COMPLETE parts lists, and TECHNICAL descriptions of ALL our famous circuits. (See previous ad.) ONE COPY GIVEN FREE WITH ALL ORDERS OVER £3 FOR PARTS FOR THE "CORONET."

Available only from:

RODING LABORATORIES
(Dept. PW11), BOURNEMOUTH AIRPORT, CHRISTCHURCH.

DECALS

(paint transfers)

Labels for marking controls, etc., on radio and electronic equipment. For direct application to panels, knobs, chassis, etc. No background, hard wearing, professional finish. Ministry of Supply approved.


Available in books containing large selection of carefully chosen words, approx. 8 inch high letters. Decals are applied with water or varnish (for chrome finish), no tools or equipment necessary.

AMATEUR MK. II containing approx. 300 titles covering all aspects of amateur radio including T.V., tape recording, etc. Price, 3/6, plus 3d. post. Available in black or white.

STANDARD MK. II, approx. 750 titles, covering all aspects of electronics, including spare letters and numerals in black or white. Price, 4/9, plus 3d. post.

ALEXANDER EQUIPMENT LIMITED,
CHILD'S PLACE, EARL'S COURT, LONDON, S.W.5
FR 6mante 6792

A TOOL FOR HOME AND WORKSHOP.

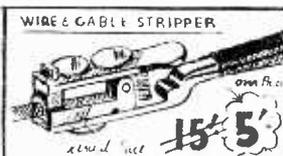

ADJUSTABLE BLADE. THREE-SIZE STRIPPING HEAD. P.P. 6d.
E.H.T. TRANSFORMER.—5-6 Kv., with U22 Rectifier, 37/6 Plus 2/- P.P.
FIRAME TRANSFORMER.—Ratio 10 to 1. MATCHES ALLEN or DENCO wide angle Def. Coils, size 3in. x 3in., 10/- P.P. 1.
A.I.F. (S.C.D) P.L. TRANSFORMERS.—In 230, out 2v. 1.6; in 230, out 6.3v. 2a. 1/6; in 230, out 2v. 3v. 6.5v. 2 a. 24/- plus 1/6 P.P.
Hundreds of bargains. Send stamp for list. JACKSON'S RADIO SUPPLIES, 163, EDGWARE ROAD, LONDON, W.2.

THE MODERN BOOK CO.

- Communications Receiver Manual: CR2, by H. W. Sams. 27s. 6d., postage 1s.
- Audio Anthology (Vols. I & II), by "Radio Magazines." 16s. 0d. each., postage 6d.
- Radio Engineers' Servicing Manual, edited by E. Molloy. 42s. 0d., postage 1s.
- Radio Designer's Handbook, by F. Langford-Smith. 42s. 0d., postage 1s.
- TV Fault Finding, compiled by "Radio Constructor." 5s. 0d., postage 4d.
- The Radio Amateur's Handbook, by the A.R.R.L. 30s. 0d., postage 1s.
- Wireless Servicing Manual, by W. T. Cocking. 12s. 6d., postage 6d.
- Foundations of Wireless, by M. G. Scroggie. 12s. 6d., postage 6d.
- Practical Wireless Encyclopaedia, by F. J. Camm. 21s. 0d., postage 1s.
- Introduction to Valves, by R. W. Hallows and H. K. Milward. 8s. 6d., postage 6d.
- Receiving Tube Manual, by R.C.A. 6s. 6d., postage 6d.
- Radio Valve Data, compiled by Wireless World. 3s. 6d., postage 3d.
- Television Picture Faults, by J. Cura and L. Stanley. 3s. 6d., postage 3d.
- Telephony, by J. Atkinson. Vol. I, 35s. 0d.; Vol. II, 55s. 0d., postage 1s each.

We have the finest selection of British and American radio publications in the Country. New revised catalogue on application.

19-23 PRAED STREET
(Dept. P.10), LONDON, W.2
PADDington 4185

TELETRON SUPER INDUCTOR COILS.

Miniature dust core types. Dual Wave TRF, 7-pr. Super Ind. Coils for all Bands. AE & OSC. 6-pr. Hi-Freq. crystal Transformer coils, triple wound for crystal diodes; 3-pr. ea. I.F.'s HF Chokes, etc. Stamp for list & Circuits.
The Teltron Co., 288, Nightingale Rd., London, N.9



TESTOSCOPE Mains Tester

For high and low voltage testing (1-130 and 100-350) volts A.C. or D.C. Write for interesting leaflet 29/-



RUNBAKEN - MANCHESTER

H.A.C. SHORT WAVE EQUIPMENT

Noted for over 18 years for... S.W. Receivers and Kits of Quality.

Improved designs with Denco coils: One-Valve Kit, Model "C" Price, 25/- Two " " " " " " " " 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.

SIR.—In all sincerity, I class myself as a reader, a regular reader, of PRACTICAL WIRELESS, endowed with the average amount of intelligence.

Imagine my disgust when I read letters pleading for a transmitting licence—but no morse, please!

I wanted a "ham" licence in 1947. I didn't have to learn morse because I already knew it—learned from scratch to 12 w.p.m. in 12 weeks; is that asking too much of anyone with average intelligence who really wants a transmitting licence?

Apart from being of some use in a case of emergency, I maintain that the morse code is our most useful and certainly most consistent means of communication. I'll go further and say that all licensed hams should sit a periodical morse test.

We have quite sufficient "natters" with licences; without another brigade being formed. Thank you for a grand "bob's-worth" of "gen."—V. ROBERTS (Stoke-on-Trent).

SIR.—The argument for the amateur wishing to hold a transmitting licence, which was started by Mr. Hector Coles and backed by myself, tends to get rather distorted as the months roll on.

We are assured, in last month's issue, that if anyone holds a transmitting licence, no interference is likely from that person.

This is, of course, the view of Mr. V. G. P. Williams (G3FTY). Anyone who listens to the amateur bands will, I feel sure, think otherwise. Just listen to 80 metres, when it really gets going, when all these skilled operators (as Mr. Williams calls them) start punching the key. Talk about bedlam, with all the cheeps, bloopers, chirps, clicks, thumps, etc., it ceases to be Communications, and becomes the survival of the fittest.

But to get back to the initial argument, I made it quite clear in my letter that I thought that the inspired amateur should not have to wade through so much restriction in order to get on the "air."

Mr. Williams says that my views are wrong.

Perhaps I can put them a bit more plainly to him.

The Pass Slip from the Theory examination does not convince anyone that an operator will not cause interference to any other users of the air. A knock on the front door is probably the first indication that interference is being caused.

I maintain that with the seven rules I am going to suggest, a band for the novice could be created which would delight thousands.

1. Maximum power: 5 watts.
2. Crystal control with no exceptions.
3. Immediate confiscation of licence for deliberate misuse of station.
4. A five-pound licence fee.
5. The band to be used only by novices.
6. Amplitude modulation only.
7. Holder of licence to be 21 or over.

Now really, Mr. Williams, this isn't asking too much, is it? This band should be V.H.F. or U.H.F.

Mr. Williams makes an example of himself when he points out how "easy" it is to get a licence. All I can say is that he is either a genius, or he has plenty of time on his hands. My working day starts me out at six in the morning, and gets me home at eight at night, with a night shift every fortnight and, believe me, morse would not go down very well with that.

Were all these petty restrictions imposed on the great men who invented radio—Marconi (I beg your pardon, Sir Oliver Lodge)—the gramophone would still be the scoop of the day.

If, sir, my views are still considered wrong, why should model-makers, taxi-cab drivers, road patrol men, gas companies, etc., etc., get free use of the air, while young men who wish to do the same get the ball and chain?

I have heard every rule broken by amateurs. Last night I heard a chappie calling CQ on 4.2 Mc/s., and he wasn't a newcomer to ham radio. I can only think that probably he has spent a lifetime on the key and look what happened when he built a modulator.—C. ROBERTS (Worcester).

Club Reports

BIRMINGHAM & DISTRICT SHORT-WAVE SOCIETY

Hon. Sec.: F. C. Cook, 67, Regent Road, Handsworth, Birmingham, 21.

FOR the month of October the Society will have a discussion by one of their members during the General Meeting, and no doubt a further discussion will be made on the Field-day results held on September 20th.

All visitors will be welcomed, and further details of the Society's activities can be obtained from the Secretary.

LOTHIANS RADIO SOCIETY (EDINBURGH)

Hon. Sec.: L. Stuart, 38, Caledonian Crescent, Edinburgh.

MEETINGS take place on alternate Thursdays, October dates being 8th and 22nd, at 25, Charlotte Square, Edinburgh. An extensive programme of lectures, visits and social activities has been prepared for the 1953-54 session. Visits to Kirk o' Shotts have been arranged for October 11th and 18th. New members will be welcomed at any meeting.

THE WILLEDEN RADIO CLUB

Hon. Sec.: E. Mitchell (G3GZW), 5 Princess Road, Kilburn Park, N.W.6.

WITH the acquisition of new premises at Scout House, Willesden High Road (near bus garage), the club has re-opened with an election of officers:

Chairman, J. Theobald (G3EQM); Secretary, E. Mitchell (G3GZW); Treasurer, T. Stonestreet.

Meetings held fortnightly on a Wednesday at 7.30 p.m. as from September 30th onwards. Technical lectures and morse

classes have been arranged. Junk sales will be held once a month.

New members will be welcome to call.

Other premises have been acquired for use as a workshop and shack for the club transmitter G3BFZ, which will be on the air in October.

THE GRAFTON RADIO SOCIETY

Hon. Sec.: A. W. H. Wennell (G2CJN), 145, Uxendon Hill, Wembley Park, Middx.

THE club has made arrangements with the Local L.C.C. Men's Evening Institute for an official course of instruction for the Radio Amateurs' Examination to be held during the coming winter months.

Classes, including morse instruction, will be held at the Grafton L.C.C. School, Eburne Road, Holloway, London, N.7 (one minute from "Nags Head"), on Monday evenings; application in the first instance should be made to the Grafton Radio Society secretary.

Club nights are Mondays and Fridays. A full programme of talks, demonstrations, etc., by leading "hams" and the trade are being arranged, and with the club transmitter on most amateur bands, Grafton look forward to a most successful season.

ACTON, BRENTFORD & CHISWICK RADIO CLUB

Hon. Sec.: R. Hindes.

WEEKLY meetings are held at the A.E.U. Rooms, Chiswick High Road, W.4, every Tuesday evening from 7.30 to 10 p.m., when the club transmitter G311U is on the air looking for QRP contacts in the 80- and 160-metre bands.

New antennas have been erected and an S640 receiver has been added to the existing club gear. The winter session of morse and general instruction is now commencing.

Membership is not confined to those living in the above three London areas only—all are welcome, "hams" and SWL's alike.

News from the Trade

Miniature Transformers

BEARING in mind the growing importance of transistors, readers will be interested in the two transformers, designed by the J. Bell & Croyden Co., now available for release.

The "O" type unit is, we believe, the smallest transformer at present in production in this country.

Its measurements are $\frac{3}{8}$ in. x $\frac{3}{8}$ in. x $\frac{1}{2}$ in., and it is an inter-stage transistor transformer or general coupling transformer. The inductance is 4H at 0.4 milliamps over the normal A.F. frequency band. The step-down ratio is 4.5 : 1 with a D.C. resistance of 870 ohms primary and 170 ohms secondary. This transformer has a mumetal core, and can be supplied with a screening can if required.

The "A" type unit measures $\frac{1}{2}$ in. x $\frac{3}{8}$ in. x $\frac{1}{8}$ in. across the bobbin.

It is an interstage transformer for matching a high gain pentode to a transistor, and has a primary of 125H at 50 microamps. The step-down ratio is 30 : 1; the D.C. primary resistance is 6,000 ohms; the secondary resistance is 80 ohms.—John Bell & Croyden, 117, High Street, Oxford.

Complete Range of Mullard Noval Based Valves for Audio Amplifiers

TWO additional valves recently introduced by Mullard, Ltd., make possible the design of a complete audio amplifier using valves with the Services' preferred B9A (Noval) base. The new valves are the EL84 high-sensitivity output pentode and the EZ80 full-wave rectifier. The complete series now comprises the EF86 voltage amplifying pentode; three double triodes, Types ECC81, ECC82, and ECC83; the EL84 output valve and the EZ80 rectifier. Details of these are given below.

Type EF86.—For use in the pre-amplifier stages, this valve now replaces type EF37A or EF40. Its mechanical construction has been designed so as to render the valve substantially free from microphonic tendencies, and the bi-filar heater reduces hum to a minimum. The characteristics of the EF86 are similar to those of the EF40, gains up to 180 being obtainable under the recommended operating conditions.

Double Triodes.—The three double triodes permit a choice of characteristics to suit various circuit requirements. Type ECC81 is a medium impedance valve, ECC82 has low impedance, and ECC83 high impedance. All three have independent cathodes and centre-tapped heaters which can be operated at 12.6 volts 0.15 amps or 6.3 volts 0.3 amps.

Type EL84.—This high sensitivity output valve is rated to dissipate 12 watts at the anode, compared with 9 watts for the EL41 which it replaces. The heater rating is 6.3 volts 0.8 amps. With a grid input of less than 4 volts, the EL84 will deliver over 5 watts

of audio power at 10 per cent. total distortion. A push-pull pair of EL84's in Class AB1 will deliver 16 watts output.

Type EZ80.—The characteristics of this full-wave rectifier are identical to those of the EZ40. It is capable of a rectified output of 90 mA, the maximum input voltage being 2 x 350 volts r.m.s. The heater is rated at 6.3 volts 0.6 amps.—Mullard, Ltd., Century House, Shaftesbury Avenue, London, W.C.2.

Sparks' Data Sheets

A CHASSIS section has now been added to the popular data sheet suppliers of Swanage. This makes it possible for those who obtain the data sheets to build the selected design on a ready-drilled chassis. It should be noted that in addition to the supply of data sheets for various types of receiver, Messrs. Sparks can now also supply all of the components specified in the sheets. To the latter have now been added, by special arrangement with Messrs. Mullard, practical constructional details and layout, etc., for the circuits contained in the Mullard booklet, "The Amateur's Guide to Valve Selection." The charts are full size, printed in black and white, complete with the theoretical circuit, all component values and prices. Most of the prints measure 22in. by 15in., but quite a few are larger than this. The prices of the majority are 3s. each and lists of designs are available from Sparks Data Sheets, 48A, High Street, Swanage, Dorset.

New Vidor-Burndept Appointment

H. T. TRAYNOR, formerly Press officer, to Raleigh Industries, Ltd., and editor of the company's house journal, The Raligram, has been appointed P.R.O. to the Vidor-Burndept group.

Mr. Traynor started his newspaper career with Kemsley Newspapers, Ltd., in Scotland, switching to the Scottish Daily Mail in 1947.

During the war he was on the staff of Air Force News in Cairo.

While with Raleigh, Mr. Traynor was closely associated with former world cycling champion, Reg Harris, with whom he travelled extensively in Europe.

The address of Vidor-Burndept's recently established Press Office is 18, Abbey House, Victoria Street, S.W.1. Telephone: ABBey 1328.

Micrograms and Automatic Micrograms

AS from August 1st, the manufacture and sale of micrograms has been discontinued by the Collaro Company, and the sole manufacture and marketing of all portable electric gramophones under this trade-mark is to be made by Electric Audio Reproducers, of 17, Little St. Leonards, Mortlake, S.W.14.

Editorial and Advertisement Offices:


"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

Your set deserves a Mullard Tube

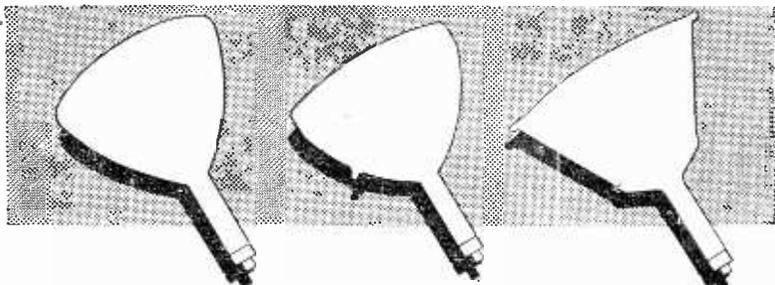

If you are building a television receiver, leave nothing to chance ; choose a Mullard Tube. Mullard Television Tubes owe their high reputation for performance, reliability and LONG LIFE to the unrivalled facilities for research possessed by Mullard ; to the complete control of manufacture from the production of raw materials to the completed product ; and, in particular, to the ion-trap, which safeguards the screen from damage by heavy negative ions produced in the region of the cathode.

Tubes available for home construction include :—

- MW22-16 9-inch screen
- MW31-74 12-inch grey glass screen
- MW36-24 14-inch grey glass rectangular screen
- MW41-1 16-inch screen, metal cone

Mullard *Long Life* T/V TUBES



MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2

MV 31 266

SOUND MASTER SERVICE

The Sound Master is an entirely new Portable Tape Recorder which has been produced especially for the Home Constructor by the designer of the famous View Master Televisor.

Full constructional details are now available.

INSTRUCTION ENVELOPE,

6/6d. post free.

WRITE NOW for our fully detailed price list.

We carry full stocks of all items needed for the Sound Master and can offer a

RETURN OF POST SERVICE.

FULL HIRE PURCHASE FACILITIES

AVAILABLE on complete or part kits.

WATTS RADIO

(Weybridge), LTD.,

8, Baker Street, Weybridge, Surrey.



can help your career through personal postal tuition

in any of these subjects :

- Accountancy Exams. ★ Aircraft Eng. & Radio ★ Architecture ★ Auditing ★ Book-keeping ★ Building ★ Carpentry ★ Chemistry ★ Civil Service ★ Commercial Art ★ Commercial Arithmetic ★ Company Law ★ Costing ★ Draughtsmanship ★ Electric Wiring ★ Engineering (Civil) ; Electrical ; Mechanical ; Motor ; Steam ; Structural ★ Jigs, Tools & Fixtures ★ Journalism ★ Locomotive Eng. ★ Languages ★ Mathematics ★ Mining ★ Modern Business Methods ★ Plumbing ★ Police ★ Press Tool Work ★ Quantity Surveying ★ Radio ★ Salesmanship ★ Secretarial Exams. ★ Shorthand ★ Surveying ★ Telecommunications ★ Television ★ Textiles ★ Works Management ★ Workshop Practice

and GENERAL CERTIFICATE OF EDUCATION

SUCCESS WILL BE YOURS

As a Bennett College Student your own Personal Tutor will coach you until you qualify, at your pace, with no time wasted. You will learn quickly, easily.

SEND TODAY FOR A FREE PROSPECTUS

TO THE BENNETT COLLEGE (DEPT. K.104), SHEFFIELD

Please send me your prospectus on..... (Subject)

NAME


ADDRESS

..... AGE (IF UNDER 21).....

PLEASE WRITE IN BLOCK LETTERS

If it's Components

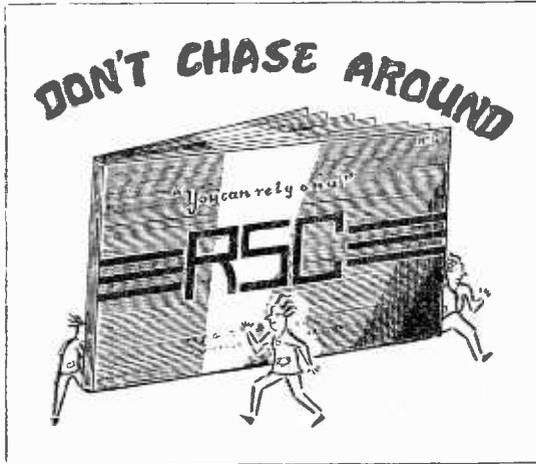AMPLIFIER CABINETS
BRIMISTORS
CABLE PLUGS
CHASSIS
CHASSIS CUTTERS
CHOKES
COAX CABLE
COAX FITTINGS
COILS
COIL CAN-FORMERS
COIL PACKS
CONDENSERS
CRYSTAL DIODES
E.H.T. UNITS COILS
FEEDER CABLE
FOCUS UNITS
FUSE HOLDERS
GROUP BOARDS
HEADPHONES
I.F. FILTERS
INSTRUMENT WIRES
ION TRAPS
INSTRUMENTS
KNOBS
LINEARITY CONTROLS
LINE CORD
LOUDSPEAKERS
MAINS DROPPERS
METAL RECTIFIERS
MICROPHONES



NUTS AND BOLTS
PAX TUBE
PICK-UPS
POTENTIOMETER'S
PUBLICATIONS
PULLEYS, DRUMS
RECORD PLAYERS
RECORDING HEADS
RECORDING TAPE
RESISTORS
SCALES AND DRIVES
SCREWDRIVERS
SOLDERING IRONS
SPOT WOBBLERS
STUDDING
TAPE DECKS
TERMINAL PANELS
TOGGLE SWITCHES
TRIMMERS
TRIMMING TOOLS
TRANSFORMERS
TUBE MASKS
TUBES
VALVE CANS
VALVEHOLDERS
VALVES
VIBRATORS
VIEWMASTER PARTS
VOLT SELECTOR PANELS
WAVECHANGE SWITCHES

Write now for CATALOGUE NO. 12 PRICE 1/-
● 70 PAGES ● 250 ILLUSTRATIONS

RADIO SERVICING CO.

82 SOUTH EALING ROAD, LONDON, W.5.

EALing 5737

Next to Sth. Ealing Tube Station

HENRY'S

We have over 20,000 American and B.V.A. valves in stock.
ALL VALVES NEW AND GUARANTEED.

SETS OF VALVES	
Ten EF50 (Ex-Brand New Units) 6/- each	50 - Set
6K8C, 6K7G, 6Q7G, 5Z4C, 6V6G (or KT81)	37 6 ..
1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4)	30/- ..
TP25, HL23/DD, VP23 PEN25 (or QP25)	25 - ..
6K8C, 6K7G, 6Q7G, 25A6G, 25Z5 or 25Z6G	37 6 ..
12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT or 50L6GT	37 6 ..
12S4GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT or 50L6GT	37 6 ..
PX25, KT33C, KT66, GU50	12 6 each
(PX25's Matched Pairs 25 - pr.)	
TEN 6AM6 (EF91)	80 -

OZ4A	7/-	6K8GT	9/-	14A7	8/6	EF50	5/-	CV54	5/-
1G6	8/6	6L6G	8/6	25Z6GT	8/6	(Ex-Units)	5/-	S130	7/6
1R5	3/-	1822 (6L6)	25Z5	8/6		SP2	8/6	7475(V370)	7/6
1S1	8/-	6L7	7/6	25A6	8/6	VP2	8/6		
1S5	8/-	6N7GT	7/6	35L6	8/6	TDD2A	8/6	CV65	6/-
1T4	10/-	6Q7GT	8/6	50L6GT	8/6	DK40	9/-	VR150.30	8/6
1A7GT	8/-	6S7GT	8/6	42	8/6	UL41	9/-	CK310AX	5/-
1C5	8/-	6R7	8/6	43	8/6	UY11	9/-	DI	2/-
1L1N5	5/-	6X5G	8/6	75	8/6	4D1	4/-	MU-METAL SCREEN for VCR97, 10/-	
2X2	5/-	6SA7GT	8/6	78	8/6	8D2	4/-	AC3/PEND	6/6
3V4	8/-	6SQ7GT	8/6	80	8/6	8D2	4/-	ACS/PEND	10/-
3S4	8/6	6S7GT	7/6	896A	15/-	15D2	10/-	12/6	
5Z1	8/6	6S7GT	7/6	9001	6/-	R3	8/6	PRN35	6/6
5U4	8/6	6S7GT	7/6	9002	6/-	D11	5/-	PRN46	7/6
5Z4	8/6	6SK7GT	7/6	9003	6/-	D42	5/-	QP25	6/6
6A7G	8/6	6SL7GT	9/-	9003	6/-	D63	5/-	QP23	8/-
6AC7	8/6	6SN7GT	9/-	9001	6/-	KT2	5/-	SP61	4/-
6AG7	7/6	6SC7	10/-	9009	6/-	KT61	8/6	SP11	4/-
6A9G	8/6	6SS7	7/6	951	6/-	KTW61	7/6	SP11	4/-
6AM6	9/-	6V6GT	7/6	957	6/-	U52	8/6	HL23/DD	6/6
6B8	7/6	7C5	8/6	956	6/-	U17	10/-	TP25	8/6
6C4	8/6	7A7	8/6	1299A	37 6	V63	8/6	VP21	6/6
6C5GT	5/-	7C7	8/6	TZ40	37 6	U22	8/6	VP41	6/6
6CC	6/6	7H7	8/6	931A	50 -	P2	4/-	U22	8/6
6DB	6/6	7B7	8/6	EA50	2 -	MU14	8/6	ATP4	4/-
6F6G	8/6	7S7	10/-	EP54	6/-	PX25	12 6	TP22	8/6
6G6G	6/6	12A6	7/6	(VR126)	6 -	KT33C	10/-	TP22	8/6
6HG6T	5/-	12C8	7/6	EP55	12 6	KT66	12 6	TH233	10/-
6HM6	6/6	12H6	8/6	EB34	3 6	KT66	12 6	TH233	10/-
6J5GT	5/-	12K7GT	8/6	EB33	8/6	CU50	12 6	41MP	7/6
6J5M	8/6	12K8GT	8/6	EP36	6/6	XP(1.5)	14/-	42SPT	6/-
6J6	8/6	12Q7GT	8/6	EP39	6/6	XH(1.5)	4/-	215SG	4/-
6KA5	9/-	12S4GT	8/6	EP32	6/6	VU111	4/-	MS/PENB	7/6
6J7G	6/6	12S7GT	8/6	EP91	9 -	VU133	4/-		
6J7M	8/6	12S7GT	7/6	EP32	6/6	VU120A	4/-		
6K5	9/-	12SH7	7/6	EL32	7 6				
6K7G	6/6	12S7	8/6	EP50	8 6				
6K7M	7/6	12SK7	8/6	EP50 (Red. SyL.)	10 -				
6K8G	7/6	12SR7	7/6						

SHADED POLE MOTORS. 200/250 volts. Ideal for Tape Decks, etc. 10/6

CATHODE RAY TUBES:
VCR97, Guaranteed full picture: 40/-, carr. 2/-.
VCR517, Guaranteed full picture with Mu-Metal Screen. 40/-.
3BP1, Suitable for 'scopes and Tel. 25/-, carr. 3/-.
MU-METAL SCREEN for VCR97, 10/-.
VCR139A (ACR10), 35/-, Brand new.

25773 TR 1196 RECEIVER UNIT.—Complete with 6 valves. 2 EF91, 2 EF39, 1 EK32, 1 EB33. In new condition. Circuit and Conversion Data Free. 25/-, carriage paid.

RECEIVER R1355. As specified for "Inexpensive Television." Complete with 8 valves VR55 and 1 each 6V6, VU121, VR92. Only 29/-, carriage 5/-, Or Brand new in original packing case 55/-, plus 5/- carr. RF24, 25/-; RF25, 25/-; RF25, 59 6; RF27, 59 6.

VR517C Blue and White 6114 Tube. This Tube replaces the VCR97 and VCR517 without alteration and gives a full Blue and White picture Brand new in original crates, 35/-, carr. free.

SEND POSTAGE FOR NEW 1953 COMPREHENSIVE 23-PAGE CATALOGUE: CONTAINING COMPONENTS & EX. GOVT. BARGAINS. Open Mon.-Fri 9-5. Thurs. 1 p.m.

5, HARROW ROAD, PADDINGTON, LONDON, W.2.

TEL.: PADDINGTON 1008/9, 0401.

THIS MONTH'S BARGAINS

JUST ARRIVED.—Amplifier, 9/6, type 1271. Brand new with valve EF36, 2 transformers, relay 400 ohms, volume controls, condensers and resistors. Case 5in. x 5in., plugs, etc. Post and packing 1/6.

BURGLAR ALARMS.—Made by "Truvoc." Ex W.D. locating device in maker's box. Low voltage and fool proof. 12/9, post 2/6.

TELESCOPIC MAST.—New. Extends to 7ft. 6in., closes down to 12in. Diam. 3/4in. to 1/2in., 7/9, post 1/3.

I.F. TRANSFORMERS.—465 kc/s. 3/9 each, post 6d.

MICRO AMP METERS.—12/9. Made by Westons. 2 1/2in. square centre or normal reading. Soiled but perfect. Also brand new at 28/6, post 1/6.

MICRO SWITCHES.—Latest American midgets 250 volt. 3 A. 1/2in. x 1/2in. x 1 1/2in., 3/6.

VALVE SALE SURPLUS AND SALVAGE.—All at 8/9. 20D1, 20F2, 6AB8, 807, EAF42, 5X4, 5Y4, 5Y3, 6BE6, 6B8, 6G6, 6BW6, 6V6, 6D3, 10P13, 6A7, EF80, X65, KT8, 35Z4, 6X4, 1A3, 1A5, 1LC6, 1T4, 1S4, 1S5, 1R5, 5U4, 5V4, 6B4, 6F6, 6F15, 6L18, 6Q7, 10F1, 3A4, ECC91, EF36, EF50, EL91, EY51, KTZ63, KTW61, X66.

O.P. TRANSFORMERS.—Store Soiled. Match all normal O.P. used to 2-5 ohm speech coil. BARGAIN OFFER, 1/9, post 9d.

TUNING CONDENSERS.—Store Soiled. Two gang, .0005 mfd. Tested, 2/9 each, post 6d. SPECIAL OFFER three for 7/-.

RELAYS.—New and boxed. G.P.O. pattern, break one make three. 1,000 ohms, 3/9 each, post 1/-.


RECTIFIERS.—New Selignium 180 v. 40 m/a. CLEARANCE OFFER, 3/9, post 6d.

RECTIFIERS.—Westinghouse type. 250 v. 250 m/a. Salvage but guaranteed, 11/9, post 9d.

RADIO-GRAM CHASSIS SHOW SALE

3 WAVE-BAND. 5 valve super-het. 12 gns. Brand new valves, 6AT6, 6BW6, 6BE6, 6BA6 and 6X4.

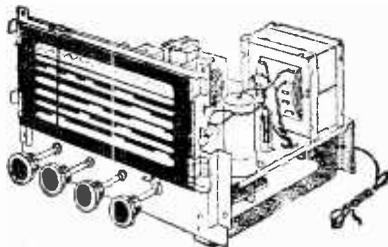6 WAVE-BAND. 5 valve super-het. 15 gns. Brand new. Same valve line up as above.



3 WAVE-BAND. 5 valve super-het, £10.17.6, with gift of FREE Bin. speaker. Valve line-up. ECH42, EF41, EBC41, EL41 and EZ40.

END DRIVE R.G. CHASSIS. 5 valve super-het, 3 wave band. Valve line-up as above, £7.17.6. SALVAGE.

RADIO-GRAM CHASSIS for 6-volt at 2 amps., operation. Ideal for cars, boats or caravans, £9.17.6. Carr. on all R.G. Chassis 4/6 each.

PORTABLE UNIVERSAL CHASSIS.—5 valve super-het. valves, 12BE6, 12AT6, 12BA6, 12A6 and 35W4. Frame aerial included, £5.19.6, plus 3/6 carr.

4 VALVE T.F.R. KIT.—Including the new "Swan" baffle cabinet, size 11in. x 15in. x 5in., £5.19.6, carr. 3/6, or assembled £1 extra.

RADIO TELEPHONE. £9.17.6. Brand new, made by Jefferson Travis (U.S.A.) for the Air Ministry, but never unpacked. Still in canvas covers, and packed in individual wooden transit cases. Model UF/1. As used by many police and fire forces. Ultra high frequency band of 53.75 mc/s. Complete operation for normal telephone handset. Runs completely off batteries, or from one 12-volt supply. Telescopic aerial, non-utility black crackle and chrome finish over all. Power pack, 37/6. Price per pair, £18.17.6, carr. 7/6.

C.W.O.
OR
C.O.D.

DUKE & CO.,

621, ROMFORD ROAD,
LONDON, E.12. GRA. 0677.

STAMP FOR CATALOGUE.
MONEY BACK GUARANTEE.

12" speakers NOW TAX FREE!

Take your pick from these luxury units:

GOODMANS

Audiom 60

£2.12.6 } & £1 monthly
with order } for 7 months
Cash Price £8.12.6

Axiom 150 Mark II

£3.5.6 } & £1 monthly
with order } for 8 months
Cash Price £10.5.6

W.B.

S 12135

£3.2.6 } & £1 monthly
with order } for 7 months
Cash Price £9.2.6

12in. Dual Concentric

£7.11.0 } & £1.8.9 mthly
with order } for 12 months
Cash Price £22.11.0

WHARFEDALE

W 12

£3.5.0 } & £1 monthly
with order } for 7 months
Cash Price £9.5.0

W.12/CS/AL

£5.10.0 } & £1 monthly
with order } for 12 months
Cash Price £16.0.0

Descriptive leaflets of any of above units free on request.

EASY PAYMENT ORDER BLANK

DATE.....

To: Frith Radiocraft, Ltd., Leicester

Please supply.....

No. of Pmts

for which I enclose £ : : Deposit and agree to pay
further monthly payments of £ : : commencing on the first day
of next month.

P.W. Nov. 53. SIGNED (usual signature).....

NAME IN FULL (CAPITALS).....

ADDRESS

State if Householder If over 21 Occupation

CATHODE RAY TUBES

for Home Constructor Designs

12" ○	Standard Types MW 31-16 : 31-74 etc.	£5.13.8 with order
Cash Price £16.13.8	& £2.2.0 monthly for 6 months	
Cash Price £17.14.6	Aluminised Types 6705A, 6706A, etc.	£5.18.6 with order
& £2.5.6 monthly for 6 months		
14" □	Standard Types MW 36-22 : 36-24	£6.9.3 with order
Cash Price £19.9.3	& £2.10.0 monthly for 6 months	
Cash Price £20.10.0	Aluminised Types C14 BM	£6.16.0 with order
& £2.12.6 monthly for 6 months		
16" ○	English Electric T 901	£7.4.10 with order
Cash Price £22.4.10	& £2.17.6 monthly for 6 months	
17" □	Mullard MW 43-64	£7.12.8 with order
Cash Price £23.12.8	& £3.1.6 monthly for 6 months	

ADD 12/6 for crate and insurance to all C.R.T. orders.

Frith
RADIOCRAFT
69-71 CHURCH GATE-LEICESTER Ltd.
PHONE 58927

ALL INTERESTED in Short Wave Reception should obtain the Radio Quarterly, price 4/- post free. American Magazines: CQ, 29/-, QST, 36/-. One year ARRL Handbook 31/-, Radio Handbook, 12th Edn. 26/-, 13th Edn. 49/6. **SHORT WAVE MAGAZINE, LTD.**, 55, Victoria St., London, S.W.1.

I.P.R.E. TECHNICAL PUBLICATIONS: 5,500 Alignment Peaks for Superheterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy The Practical Radio Engineer, quarterly publication of the Institute, 2/-, membership and examination data 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

BOOKLETS: "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2, price 2/6 ea. Ex-Gov. Optical lists free for s.a.e. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

AMERICAN MAGAZINES.—One year Audio Engineering, 28/6; specimen copy, 4/-; High Fidelity, 43/-; Popular Science, 28/6. Free booklet quoting others. **WILLEN, LTD.** (Dept. 49), 101, Fleet Street, London, E.C.4.

RECEIVERS & COMPONENTS

EVERYTHING for radio constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH, 98, West End Road, Moredun, Cambridge.** Quick service.

NORTH LONDON.—Everything for Radio Constructors. Condensers, Coils, Valves, Resistors, etc. Est. 1937. **WARD'S, 86, Tollington Way, Holloway, N.7.**

ACCUMULATORS 2v/16AH, 10/-; 24v Motors, 6/-; Dynamotors, 5.5v/230V, 30 ma, 10/-; HR Double Phones, 12/-; Trans 1085, 3 meters, 37 assid parts, 22/6; Power Unit No. 320, 24 2000v dynamotor, 2 conds, 15H choke, fuse, 5RFC, S130, 17/6. Above post free. Valves at 2/-: VR78, 2C34, VR135; at 2/6; 954, VR65A, VR92, VR21; at 4/-: 45HA, 42SPT, 4TSP, post extra. Free Monthly lists. **ANNAKIN, 35, Ashfield Place, Otley, Yorks.**

VOLUME CONTROLS, lng. sp., 1/2 meg, 2/9, with s.p. sw. 3/6, d.p. sw. 5/6. Special offer: 1/2 meg, d.p. sw., lin. spindle, 3/6; preset 2k, 2k, 100k, 1/2 meg, 1/6; wirewound, 25k, lin. sp., 2/-; preset, 5k, 25k, 1/9. Condensers, 8/450, 2/4; 32/350, 2/9, 16 x 16/275, 3/-, 16 x 32/375, 16/500 card, tub., 1/9, 50/12 1/3, 500/2.2, block, 1/6; U.S.A. surplus, 32/450, large type with mtg. plate, 1/9, 3 1/2 4/6; Mansbridge type, 1 mid. lkv, 1 1/2 1/400, 2/250, 1/-; 5 400 9/-; Mains Droppers, with slider, 1,000 ohms, 2 A. 5/-; 750 ohms, 3 A. 5/-; 4v high-note buzzers, 2/6. Crystal Mike Units, 15/6. Assorted M.C. Meters, 4 for 9/6. Postage 9d. under 2/-; post orders only. **MASSEY, 58, Wakefield Ave., Hull.**

12IN. P.M. SPEAKERS. Heavy magnet "Celestions and Parmecos," in new condition, 15 ohm speech coils, approx. half price, 69/6 (p.p. 7/6). American 2 1/2in. M.C. Meters, 0-500 ma, 7/6 (p. 9d.). 10 pF air-spaced Tuning Condensers, standard spindles, 1/6; R.F. Units, type 27, complete, 39/6; with broken dials, 29/6; with broken dials, less valves, 19/6, p.p. on all types 2/-. Taylor model 65B Signal Generator, as new, 28/10/-, p.p. 7/6; brand new 8-way "Jones," Sockets and Plugs, with covers, 2/6 complete. Most radio and T.V. constructors are now on our mailing list. If you are not, write to-day for our free list. **SERVIO RADIO, 156/8, Merton Road, Wimbledon, S.W.19.** (LIBerty 6525.)

RATES: 5/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

SLIDING RESISTANCES, 33 Ω 9w. 1/6 ea., 15/- doz., 680 Ω 18w. 2/- ea., 18/- doz. Listed 1 and 2/-; toller. resist. vitreous carbon, pots, single and ganged. Condensers, 2pf-2,000 μ F. fittings, motors, chassis with valves, etc. Once again we secured large quantity of ex-equip. 465kcs IFTs, aligned and sealed, bench superhet tested, size 1 1/4in. x 1 1/4in. x 3 1/4in., pair with twin 500pf var. cond. (short spindle), 6/-, post 1/-; dozen sets, 62/-, post paid. var. cond., all 500pf p.g., lin. spindles, single 1/6, superhet twin 3/6, four g. 2/6. List 3d. stamp. Packing free; post extra. **THE RADIO SERVICES, Lr. Bullingham, Hereford.**

INTERNATIONAL Octal Valveholders, brand new, 2/- dz.; Tub., 1 x 500v, 3/- dz.; 1 x 350, 2/9 dz.; 3 W.B. Coil Pack Kit, 11/-; T.R.F. Kit, 25/5/-; Superhet Kit, 26/10/-; 2 W.B., including all parts, valves, cabinet, the lot. Book of instructions 1/6. Latest list 3d. **SUSSEX ELECTRONICS, Princes Street, Brighton.**

ELECTROLYTICS, capacity, voltage, size, type of mounting; price post paid. In that order: 16 + 32, 450/525, 1 1/2 x 1/2 clip, 5/6; 24 + 24 + 16, 350/425v, 1 1/2 x 2 clip, 4/9; 60 + 200, 275/350v, 1 1/2 x 4 1/2 clip, 6/6; 4, 150v 1/2 x 1/2; 1/1; 500, 12v, 1 1/2 x 2 1/2 clip, 2/6; 8, 350v, 1/2 x 2, 2/-; 6,000, 12v, 1 1/2 x 4 1/2, lug, 4/6; 100 + 200, 275/350v, 1 1/2 x 4 1/2, clip, 6/6; 32 + 32, 350/425v, 1 1/2 x 2, clip, 5/-; 8 + 16, 450/525v, 1 x 2, clip, 4/-; 2, 450/525v, 1/2 x 1 1/2 tag, 1/3; 8, 350/425v, 1/2 x 2, clip, 1/9; 16 + 32 + 8, 450/525, 1 1/2 x 3 1/2, lug, 5/9; 3, 450v, 1/2 x 2, clip, 1/11 3/4; 32 + 32, 275/350v, 1 1/2 x 2, clip, 3/6; 40 + 40 + 20, 350v, 1 1/2 x 3, lug, 5/-; 100, 275/350v, 1 1/2 x 3, clip, 3/6. All are Ali cans; some with sleeve; all new stock; all voltages WKG, with surge v where marked. Television! Set of 3 Components, comprising line output trans., with E.H.T. winding to give 1kV, using EY51 heater winding for EY51 also included, and fitted with width control. Scanning coils, low impedance line and frame, focus coil, optional high (10,000 Ω) or low (200 Ω). Set of 3, 42/-, plus 2/- postage. Diagram of line trans. supplied. T.V. Control Panels, Faxolin plate, 4 x 3in., carrying 5 slider type res., 3 "Welwyn" wire wound 10w (1K, 5K, 10K), and 2 carbon (2 x 50K), complete with knobs for sliders 6/- each; post paid. Universal Amplifiers, 8 valve, 20w, AC/DC, 200/250v, black and chrome chassis and cover, overall size, 15 x 7 x 7. First-class components, Partridge O.P.T. and driver, Gardiner choke, Mu metal input trans., wired and tested, complete with all valves (2 x EF37, 4 x CL33, 2 x UR3C), and plugs, 15 Ω output, high/low impedance input, 20/19/6; carr. paid. 2in. square, flush mounting, bakelite cased, 5 ma Moving Coil Meters, brand new, 8/-, post paid. Rotary Transformers, 24v. D.C. input, outputs, 250v, 60 ma, and 6.5v, 2.5 A, both D.C. Perm. Mag. Rotary, mounted on chassis, with cover, overall size, 8 1/4in. x 4 1/4in. x 6 1/4in.; can be run from D.C. mains in reverse to give approx. 15v, 2-2 1/2 A. for chargers, model trains, etc., 7/6, post paid. **RADIO CLEARANCE LIMITED, 27, Tottenham Court Road, London, W.1.** (Telephone: Museum 9188.)

ORGAN KEYBOARDS, 3-octave, on solid base; 19 by 4in.; no key contacts; professional job; ebony and ivory finish; 24/15/-; carriage paid G.B. Send now to **CIRCUTS & SUPPLIES, 10, Duke St., Darlington, Co. Durham.**

MRCI Pr/Pk 90v + 7.5v, 50 mA, 32/-, plus 1/- p. H. HINA, 4, Nittard, Warley.

OSMOR for really efficient coils, coil-packs, and all radio components, as specified for many "Practical Wireless" circuits. See our advert. on page 662 of this issue for free circuit offer, or send 5d. stamp to address below. **OSMOR RADIO PRODUCTS, LTD.** (Dept. PC.10) Borough Hill, Croydon, Surrey. (Tel.: Croydon 5148/9.)

WALNUT Radiogram Cabinets of distinction, stamp details. **R. SHAW, 69, Fairlop Rd., E.11.**

GOLD SPRAYED, expanded metal Speaker, fret 12in. x 12in. 4/6, 12in. x 9in. 3/6, 8in. x 6in. 1/6; add 1/- towards cost of postage and packing. **SHARP'S (RADIO), 252, Chapel St., Salford, 3.**

EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M. Brit. I.R.E., City and Guilds and other professional examinations. Train with the College operated by Britain's largest electronic organisation. Moderate fees. Write to E.M.I. INSTITUTES, Postal Division, Dept. PW28, 43, Grove Park Road, London, W.4. (Associated with H.M.V.)

WIRELESS.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **B.S.T. LTD., 179, Clapham Rd., London, S.W.9.**

RADIO OFFICERS urgently reqd. We train most in shortest period. Training fees payable after appointments. Secd. Scholarships available. Boarders accepted. 2d. stamp for Prospectus. **WIRELESS COLLEGE, Colwyn Bay.**

THE INSTITUTE of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.**

WORLD TRAVEL and Adventure in the Merchant Navy.—Young men, 15 years upward, required for training in Marine Wireless and Direction-finding at Sea. (Trainees in forthcoming Registration Groups are eligible for deferment of Military call-up.) Immediate sea-going positions on completion of training. Suitable candidates will be entered as officers and must be prepared to sail to all parts of the world. Low training fees. Send 1/- P.O. for Prospectus to **OVERSEAS HOUSE** (Dept. P.W.), Brooks' Bar, Manchester, 16. (Tel.: MOSS-side 2047.)

MERCHANT NAVY and Air Radio.—Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. Estd. 30 years; s.a.e. for prospectus from Director. **THE WIRELESS SCHOOL, 21, Manor Gardens, London, N.7.** (Tel.: ARC. 3694.)

"VIEWMASTER" VALVES, exact to specification, guaranteed new and boxed, comprising 5 EF50, 1 6P25, 1 KT61, 1 EBC33, 1 EB91, 2 6K25, 1 6P28, set of 12 26T2/61, with EF91, 7/- extra. (Post and insurance 2/-.) 6AM6, EF91, 6P12, ZL7, 8D3, 6C4, L77, W7, EF92, 6AM5 ELL91, 12AX7, 7/9; any 8 for 56/-; EB91, 6A15, HVR2A, 6/9; 1.4v Miniatures, 1S5, 1R5, 1T4, 3V4, 1L4, 3Q4, 3A4, 7/6; set of any 4. 2/6; 3S4, 8/6; 6V6G, 6V6GT, 6P6G, KT63, Y63, 1C5GT, EF39, EBC33, EF50, 20D1, 7B7, 7C5, 7C6, 7HT, 7S7, 7/6; 5Z4G, 5U4G, 5Y3G, MU14, TX4, U22, U78, DH77, 6AT6, 12A17, ECC88, 6X4, 6BA6 6BE6, 6BW6, 6J6, EC91, Pen46, PY82, 6LD20, 6X5GT, 8/6; EL38, PL38, 22/6; PZ30, GZ32, 6U4GT, 17/6; 6P25, N78, 15/-; UUR, CL33, PL33, U25, 13/6; U16, EAC91, ECC91, 6A7, UBF80, PL83, 6P1, 6P14, 12/-; PL81, PL82, PY81, UCH42, UL41, X63, 10F9, 10LD11, 10C1, 10C2, 11/-; ECL90, EF30, EY31, PY30, 6F15, 6C9, 10F1, 10P13, AZ31, CY31, 43, KT33C, 6K8GT, 12K8GT, EAF42, R10, 10/6; 25Z5, 25Z6GT, EBC41, UBC41, UF41, 10/-; 6SN7GT, 6SL7GT, 6Q7GT, 12K7GT, 25Z4G, 25A6G, EF41, 9/6; 6K8G, U50, 5Y3GT, 25L6GT, 35L6GT, 50L6GT, 35Z4GT, 80, U09, U404, UY41, EZ40, 9/-; 6K7G, EF8, 6/-, All new and boxed. Postage 4d per valve 8/- extra. **READERS RADIO**, 24 Colberg Place, Stamford Hill, London, N.16. (STA. 4587.)

MORSE CODE Training
Send for the Candler
BOOK OF FACTS
It gives details of all Courses which include a Special one for securing Amateur Licence. **CANDLER SYSTEM CO.** Dept. 5LO 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

NEW GOODS ONLY
T-Tubular Wire Ends, C-Can, Tag Ends, Clip Fitting.
CONDENSERS—Electrolytic, 450v. wkg. T. 1 mfd. 2/6; T. 4, 3; T. 8, 6; T. 15, 4; C. 32, 5/10; C. 28, 4/6; C. 16, 5/6; C. 16-16.6; 500v. wkg. T. 2, 2/4; T. 4, 2/8; T. 8, 2/6; C. 16, 4/8; C. 32, 6/9; C. 8, 8; 6; C. 8, 16; 8; C. 16-16, 7/4; T. 25 x 25v. 1/9; T. 25 x 50v. 2/-; T. 50 x 50v. 2/6; T. 50 x 125v. 1/9; T. 100 x 50v. 3/9; C. 100 x 350v., 9/-.
TUBULAR PAPER—300v. wkg. up to .0005, 7d.; to .005, 8d.; to .04, 10d.; .05, 1/-; .2, 2s. 1/4; .5, 3/-; 1, 2/8. 50L Minia. 500v. wkg. up to 100, 2/4; up to 500, 11d.; to 1,000, 1/-; 2,000, 3/00, 1/1.
VOLUME CONTROLS—Lg. Spdls., all values, 2/9; with SW. 4/9; with D.P. SW., 5/6.
RESISTORS—Carbon, all Std. values 20%, tol. 1 watt, 4d.; 1 watt, 5d.; 1 watt, 7d.; 2 watt, 1/-; Wirewound, 3 watt, up to 5K 1/9; 5 watt to 5K, 2/-; to 50K, 2/6.
RADIOLECTRON
22, FRANCES STREET, SCUNTHORPE Lincs.

TELEKOM SUPPLY
INTERCOM NETS.—A.C. D.C. in walnut cases, £5. Extra speakers in cases, 17/6.
RESISTORS—Parcel of 1,000 mixed (and 1) watt, with long wires, £3-10-0.
5in. ELAC SPEAKERS, 11/6.
VIBRATORS—12 v. 4-pin, 5/-.
VALVES, NEW & SURPLUS, GUARANTEED.
CV181 6/- 6X5 7/-
VR21 3/6 6A8 9/-
ATP4 2/6 6B8 9/-
1G8 4/6 6BE6 9/-
EY7 6/- 6BA6 9/-
12J7 7/6 6I5 5/6
OZ4 5/- 6A1.5 8/6
1T4 6/6 1R5 8/6
1S5 7/6 3Q4 8/6
3V4 7/6 1R3 8/6
KTZ73 6/6 12Q7 7/-
6AC7, 12A6, 6SH7 12K7 6/-
(soiled), 5/- each. 15D2 5/6
6K8 9/- EF50 5/6
6X4 8/6 6AM6 8/-
Send your inquiries for ex-W.D. Equipment to:
Chantry Lane Works, Chantry Lane, Bromley, Kent. Phone: Rav. 5845.

PANL (the air-drying black crackle), 3/6 per jar from authorised dealers, or 4/6 direct: 8, Kenton Park Cres., Kenton, Middx.

SITUATIONS VACANT
The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59 inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.

AIRCRAFT Radio Mechanics skilled in workshop practice or aircraft installations to work at Stansted Airport, Essex; hostel accommodation available; minimum hourly rates 3/9. Write to the PERSONNEL MANAGER, 7, Berkeley St., W.1.

THE CORONET AC4
COMPONENTS FOR THIS NEW RADIO RECEIVER IN STOCK
PRICE LIST AVAILABLE ON REQUEST
J. T. FILMER,
MAYPOLE ESTATE, BEXLEY, KENT
Tel.: Bexleyheath 7267

Quixo RADIO Cell Tester
Accurately tests High, Low and Grid Bias Batteries. Write for leaflet 29 M.
RUNBAKEN MANCHESTER

FREQUENCY CRYSTALS, 5.8 to 8.6 Mcs. in 25 Kes. steps. Odd 5/6. Spot 8-.
3-VALVE U.H.F. BATTERY RECEIVERS, 160 Mcs. Easily converted. 15-8.
NEW OLDHAM 2v. 16 A.H. Accumulators 8/6. 71 x 4 x 2.
0-5 AMPMETERS, 2 1/2in. square M. C. 11-1.
GERMANIUM DIODES, 2/9.
P.M. SPEAKERS, 8in., 20.-; 5in., 14/6; 6 1/2in., 16/6; 10in., 27/6.
SELENIUM RECTIFIERS, F.W. 6/ or 12v. 6F7 4 A. 22/6; 6A, 30/-; 3A, 14/6; 1A, 8/6; 24v. 2A, 30.-; 250v. 100 mA H.W., 9/-; 80v. 4A, 6.-; 250v. 275mA, 17/6.
TRANSFORMERS, 200-240 volts, tapped 3-4-5-6-8-9-10-12-15-18-20-24 and 30 volts at 2 A., 21/6. One Year guarantee.
NEW G.E.C. 0-75 MILLIAMMETERS, 1 1/2in. x 1 1/2in. 8/-.
EX-W.D. PHONES, Low Resistance, 8/6.
MINIATURE VALVES, New, 9901, 9002, 9003, 7/6; 6AG5, 1S1, 1S5, 1T4, 1R5, 10/6; 6AL5, 8/6; 12A77, 6AM6, DH77, 6AT8, EY51, 6BE6, 12/6.

NEW VALVES, 35Z4, 35L6, 25Z4, 25L6, U2R1, VP4B, U50, 5Y3GT, 6K7GT, 6V6GT, 5L6, 42, 80, 11.-; 6KGT, 11Z76, 12/6.
0-500. MICROAMMETERS, 2in., 15/6.
MULTIMETER KIT, 2 1/2in. M.C. calibrated meter, D.C. Volts 0-3-30-150-300 and 600, M.A. 0-80. Black ebony case. Also leads 0-5-100 ohms with 1 1/2v. battery, 25/6.
AERIAL RODS, 4ft., 3 sections, 6/-; Base 3/6.
6v. VIBRATOR UNITS, Output 200v. 60 mA, complete in steel case, 22/6.
TR. 1196 TRANSMITTER SECTION, New and complete, less valves, 4-6-8 Mcs., easily converted, 15-.

ALL POST PAID IN U.K.
THE RADIO & ELECTRICAL MART
253b, Portobello Road, London, W.11.
Phone: Park 6026

VALVES
OBSOLETE Radio and Television and Current, over 1,500 different types. **JOHN GILBERT RADIO**, 20, Extension, Shepherds Bush Market, London, W.12. (SHE 3052.)

6V6G AND GT, matched in pairs, new, boxed, 17/- per pair; p. and p. 1/-; R. J. COOPER, 32, South End, Croydon, Surrey.

WINWOOD FOR VALUE—New boxed Valves, 1T4, 1S5, 1R5, 354, 28/- set; 5Z4, 6K7, 6K8, 6Q7, 6V6, 35/- set; 12K7, 12K8, 12Q7, 35L6, 35Z4, 37/6 set; EF91, 7/-; EB91, 6/1; EF50, 6/-; 6K7G 5/6; Metal Recs., RM1, 3/9; RM2, 4/-; RM3, 5/-; RM4, 16/-; 10in. P.M. Spkrs, 16/6, 4-page list available. All goods guaranteed. **WINWOOD**, 12, Carnarvon Road, London, E.10. (Mail only.)

1,000 CHEAP VALVES, etc., list. **ROGERS**, 31, Nelson St., Southport.
VALVES—We will purchase for fair prices any surplus valves you may have. Write with details of quantity, condition, etc. **NORMAN H. FIELD**, 68, Hurst Street, B'ham, 5. (MID. 3619.)

NEW VALVES WANTED, small or large quantities; all Television Valves and ECL80, EF80, EBC33, PW4/500, VU39, KT61, KT66, 6K8, 5Z4, etc., etc. Prompt cash. **WM. CARVIS**, 103, North Street, Leeds, 7.

BENTLEY ACOUSTIC Corp. Ltd.
38, Chatelet Road, N.W.1. *Price/rose* 9090

OZ4	6/-	6Q7	8/6	12SR7	7/-
1A5	7/6	6R7	8/6	6T4	7/-
1G4	7/-	6SA7	8/-	12Z3	10/6
1G8	6/-	6SG7	5/-	14H7	9/-
1L4	7/-	6SH7	4/6	10D3	10/-
1T4	7/-	6SJ7	9/-	15D2	3/-
2C28	4/6	6SK7	4/6	25A8	8/6
2X2	5/-	6SL7	3/-	25L6	8/-
4D1	3/6	6SN7	9/-	25Z4	8/6
5U1	7/-	6SS7	4/-	35L6	7/6
5V4	8/6	6ST7	2/6	45	10/-
6X4	12/-	6U4	17/-	50L6	9/-
6Y3	12/-	6U7	6/-	61P	6/6
5Z4	7/-	6V6	7/-	75	12/-
6A7	11/6	6X5	7/-	77	7/-
6AB7	8/-	6Z4	6/6	80	8/-
6AG7	8/-	7A3	10/6	83	10/6
6B7	8/-	7B6	3/6	210LF	2/-
6B8	6/-	7B7	7/-	867	8/-
6BG6	10/6	7C5	6/6	1619	8/-
6CD6	11/-	7C6	7/-	1622	9/-
6CH6	8/6	7C7	7/-	1625	9/-
6C8	5/-	7D8	7/6	1626	8/6
6C8	13/-	7H7	7/-	5783	8/6
6F6	7/-	7Q7	7/-	ARD53	5/6
6F7	8/6	7R7	8/-	CV21	3/6
6F8	8/6	7S7	7/-	CV130	2/-
6H6	6/6	7Y4	7/-	8	2/-
6J5G	5/-	10D1	4/-	HL133D	9/-
6J5M	5/6	12A77	8/-	KF35	7/6
6J7G	5/-	12AU7	8/-	MH4	5/-
6J7M	5/6	12AX7	10/-	41MTL	6/6
6K8	5/-	12C8	8/6	PT2	3/-
6K7G	4/6	12J5	4/6	OP21	7/-
6K8	9/-	12K8	8/-	VR55	7/6
6L8	9/-	12Q7	4/-	VR56	4/-
6L7	4/6	12SR7	6/-	VR57	7/6
6N7	6/6	12SQ7	8/6	X08	12/6
				133	6/-


All Guaranteed. Post 6d. each.

VIBRATOR PACKS—24 volt input, 110 volt D.C. about 40 MA output. Complete with 12-volt vibrator, stabiliser VS110/A. Complete in metal case. New and boxed. 12/6 each, postage 2/-.

AMERICAN HEADPHONES—Light-weight type headphones complete with plug and lead, 8/6d. per pair, postage 1/3d.
ROTARY CONVERTER—11 volt input, 250 volt at 150 m.amps D.C. output, fitted with chokes and condensers for smoothing, and contained in a sound-proof metal case 18in. x 12in. x 8in. deep, including lid, case black crackle similar to an attaché case, with controls and plugs brought out to side of case. Price 50/- carriage 7/6d.
AMP METERS MOVING COIL—5in. scale, Pressed steel black enamel cases, Range 0-14 amps, with fitted external shunt, Ba-1c meter movement 75 milli volt t.s.d. 30 v. (Post. 1/9d. This is one of the best 5in. meters we have handled for some time.

A. T. SALLIS,
93, NORTH ROAD, BRIGHTON,
SUSSEX. Tel.: B'ton 2806

BLANK CHASSIS IN ALUMINIUM OR STEEL

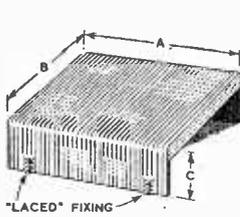

REF.	DIMENSIONS			PRICE	
	'A'	'B'	'C'	ALL	STL.
CH.8	7"	4"	2"	6/-	5/-
9	9"	5"	2 1/2"	7/3	6/3
10	10"	6"	2 1/2"	8/-	7/-
11	10"	8"	2 1/2"	8/9	7/9
12	12"	9"	2 1/2"	10/-	9/-
13	14"	9"	2 1/2"	10/6	9/6
14	16"	8"	2 1/2"	11/-	9/6
15	16"	8"	3 1/2"	12/6	10/9
16	20"	9"	2 1/2"	13/-	11/3
17	17"	9"	2 1/2"	12/-	10/3
18	17"	10"	2"	12/-	10/3

This extensive range of Steel Chassis is manufactured from 19 s.w.g. Steel and finished in Black Matt Cellulose. The Aluminium Chassis are made from 16 s.w.g. material. A feature of both ranges of chassis is the lattice fixing holes which enables the mounting to the cabinet with self tapping or wood screws only, thus saving the constructor a lot of time making brackets and holes, etc., and presenting a much firmer method of fixing.

GOOD NEWS FOR HOME CONSTRUCTORS AND SMALL MANUFACTURERS

Chassis made to your requirements with a scale of charges that enables you to work out the cost of your prototype. Material is in either 16 s.w.g. bright Aluminium or Matt Black 19 s.w.g. Steel at 1d. per square inch plus 3d. per bend, plus 2d. per round hole, plus 2. - per shaped hole, plus 1. - postage.


DENCO (CLACTON) LIMITED,

357/9 Old Road, Clacton-on-Sea, Essex.

Armstrong

Offer to the enthusiast who requires the highest quality reproduction their increasingly popular

2 outstanding new models

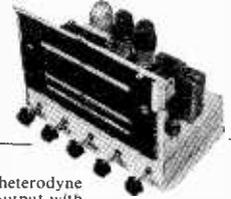

FC.38 8 Valve Superheterodyne chassis giving 8 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls. WAVE RANGE—16-50 metres. 190-550 metres and 1,000-2,000 metres. PRICE—£23 13s. including tax.

RF.41 10 valve Superheterodyne chassis giving 10 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls, also a highly sensitive R.F. stage before the mixer. WAVE RANGE—12-90 metres, 190-550 metres and 800-2,000 metres. PRICE—£31 19s. 8d. including tax.

Both High Class Chassis at an economical price giving AMAZING Realistic Radio and Record Reproduction from the modern records.

ARMSTRONG WIRELESS & TELEVISION CO. LTD.

WARTLERS ROAD, HOLLOWAY, LONDON, N.7.

Telephone NORth 3213/4.

FREE TO AMBITIOUS ENGINEERS!

This 144-page Book



'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---
Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME

ADDRESS

Subject or Exam.

that interests me

British Institute of Engineering Technology,
409B, Shakespeare House,
171/19, Stratford Place, London, W.1

Have you sent for your copy?

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics,
Draughtsmanship
Television, etc.

GET SOME LETTERS AFTER YOUR

NAME!
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
GEN. CERT.
OF EDUCATION
etc... etc.

SOUTHERN RADIO'S WIRELESS BARGAINS

TRANSMITTER-RECEIVERS (Walkie-Talkie) Type 38 Mark II. Complete with 5 Valves. Microphone. Headphones and Aerial. Less Batteries. Guaranteed fully and ready for use. £4 15s. post paid. Extra Junction Boxes for above. 2/6.

TRANSMITTER-RECEIVERS No. 18 Mark III. Complete with all Valves but less Batteries and attachments. Guaranteed Ready for Use. £7 17s. 6d. Carriage Paid. No. 18, Mark III. BRAND NEW Complete in original packing cases with ALL attachments and full set of Spares including duplicate Set of Valves (Less Batteries). £15.

TELESONIC 4-Valve Battery Portable. Complete with 4 Hivac Valves. Contained in Metal Carrying Case. Easily Convertible to Personal Portable. Brand New. £2, including Conversion Sheet and post.

RECEIVERS R109, COMPLETE WITH 8 VALVES. Vibrator Pack for 6-Volts. Contained in metal case with built-in Speaker. 1.8 to 8.5 megs. GUARANTEED. £7. Carriage Paid.

MINISCOPIES, G.E.C. M861R. BRAND NEW, COMPLETE IN CARRYING CASE WITH PLUGS. £12 10s.

RESISTANCES, 100 Assorted useful values wire-end. 12/6.

CONDENSERS, 100 Assorted Mica and Tubular. 15/-.

LUBRA HOLE CUTTERS, Adjustable 1in. to 3 1/4in. For use on Wood, Metal, Plastic, etc.. 5/9.

THROAT MICROPHONES, Brand New Magnetic with Long Lead and Plug. 4/6. American Type. 4/6.

PLASTIC MAP CASES, 14in. by 10 1/2in.. 5/6.

STAR IDENTIFIERS, Type I. A-N. Covers both Hemispheres. Complete in case. 5/6.

WESTECTORS Wx6 and W112, 1/- each.

MARCONI AERIAL FILTER UNITS (P.O. Spec.). 4/6.

CONTACTOR TIME SWITCHES, 2-impulses per sec. Complete in Sound-proof case. Therm Control. 11/6.

REMOTE CONTACTOR for use with above. 7/8.

SPECIAL OFFER TO EXPERIMENTERS, TWELVE METERS and AIRCRAFT INSTRUMENTS. Only needs adjustments or cases broken. TWELVE INSTRUMENTS (including 3 Brand New Aircraft Instruments). 35/-.

Full List of Radio Books 2 1/2d.

HUNDREDS OF FURTHER LINES FOR CALLERS.

SOUTHERN RADIO SUPPLY LTD.

11, LITTLE NEWPORT STREET, LONDON, W.C.2

GERrad 6653

BIET

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

	<i>No. of Blueprint</i>
CRYSTAL SETS	
1/6d. each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set	PW94*
2s. each	
Dual - Wave "Crystal Diode"	PW95*

STRAIGHT SETS

Battery Operated	
One-valve : 2s. each.	
The "Pyramid" One- valver (HF Pen) ...	PW93*
The Modern One- valver	PW96*
Two-valve : 2s. each.	
The Signet Two (D & LF)	PW76*
3s. each.	
Modern Two-valver (two band receiver) ...	PW98*
Three-valve : 2s. each.	
Summit Three (HF Pen, D, Pen)	PW37*
The "Rapid" Straight 3 (D, 2 LF (RC & Trans))	PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet)	PW87*
3s. each.	
The All-dry Three ...	PW97*
Four-valve : 2s. each.	
Fury Four Super (SG, SG, D, Pen)	PW34C*
Mains Operated	
Two-valve : 2s. each.	
Selectone A.C. Radio- gram Two (D, Pow) ...	PW19*
Three-valve : 2s. each.	
Double - Diode - Triode Three (HF Pen, DDT, Pen)	PW23*
A.C. Band-Pass 3 ...	PW99*
Four-valve : 2s. each.	
A.C. Fury Four (SG, SG, D, Pen)	PW20*
A.C. Hall-Mark (HF Pen, D, Push Pull) ...	PW45*

SUPERHETS

Battery Sets : 2s. each.	
F. J. Camm's 2-valve Superhet	PW52*
Mains Operated	
"Coronet" A.C.4 ...	PW100*

SHORT-WAVE SETS

Battery Operated	
One-valve : 2s. each	
Simple S.W. One-valver	PW88*
Two-valve : 2s. each.	
Midget Short-wave Two (D, Pen)	PW38A*
Three-valve : 2s. each.	
Experimenter's Short- wave Three (SG, D, Pow)	PW30A*
The Perfect 3 (D, 2 LF (RC and Trans)) ...	PW63*
The Band-spread S.W. Three (HF Pen, D (Pen), Pen)	PW68*

PORTABLES

1s.	
The "Mini-Four" All- dry (4 valve superhet)	PW

MISCELLANEOUS

2s. each.	
S.W. Converter-Adapter (1 valve)	PW48A*
(2 sheets), 7s. 6d.	
The P.W. 3-speed Auto- gram.	
The P.W. Electronic Organ (2 sheets), 7s. 6d.	

TELEVISION

The Practical Television Receiver, (3 sheets), 10/6	
The "Argus" (6in. C.R. Tube), 2/6	

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated	
One-valve : 2s.	
B.B.C. Special One- valver	AW387*
Two-valve : 2s. each.	
A modern Two-valver ...	WM409*
Mains Operated	
Two-valve : 2s. each.	
Consoelectric Two (D, Pen), A.C.	AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated

One-valve : 2s. each.	
S.W. One-valver for America	AW429*
Two-valve : 2s. each.	
Ultra-short Battery Two (SG, det Pen)	WM402*

Four-valve : 3s. each.

A.W. Short Wave World- beater (HF Pen, D, RC, Trans)	AW436*
Standard Four - valver Short-waver (SG, D, LF, P)	WM383*

Mains Operated

Four-valve : 3s.	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans)	WM391*

MISCELLANEOUS

Enthusiast's Power Am- plifier (10 Watts) (3/-)	WM387*
Listener's 5-watt A.C. Amplifier (3/-)	WM392*
De Luxe Concert A.C. Electrogram (2/-) ...	WM403*

QUERY COUPON

This coupon is available until Nov. 2nd, 1953, and must accompany all Queries, sent in accord with the notice on page 709.
PRACTICAL WIRELESS, Nov., 1953.


Announcing

the new Acos

HGP 40

INTRODUCED AT THE RADIO SHOW

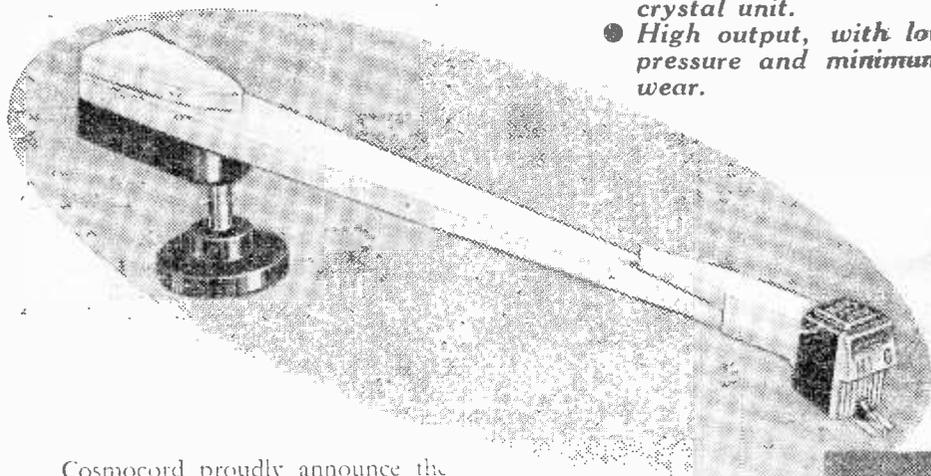
- *Interchangeable heads with easily replaceable styli.*
- *High compliance, low element mass.*
- *Completely hermetically sealed crystal unit.*
- *High output, with low stylus pressure and minimum record wear.*



Cosmocord proudly announce the HGP 40—first of the new Acos Hi-g pick-ups—capable of tracking the highest modulation levels which can be engraved. Incorporating an entirely new clip-on-method, the pick-up heads are designed to couple outstanding performance with extreme physical robustness.

Ask your dealer for details or write to us direct.

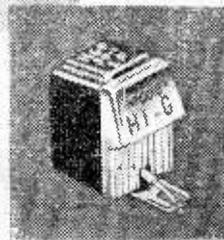Price £2.15. (plus 17/8 P.T.)
Additional HGP 39 Head (Standard or L.P.) £1.12. (plus 10/3 P.T.)



ACOS devices are protected by patents, patent applications, and registered designs in Great Britain and abroad.

COSMOCORD LTD.
ENFIELD, MIDDLESEX

always well ahead

