

BUILDING THE NEW FURY FOUR

# PRACTICAL

DECEMBER  
1954

EDITOR: F.J. CAMM

# WIRELESS



*Making a Valve Tester*

# For super tropical service 'METALPACK' PAPER CONDENSERS

This range has been developed for operation in high humidities and high temperatures. Their ability to withstand variations from -40°C. to +100°C. makes them the obvious choice for the most stringent conditions. Internal construction follows the well-proved T.C.C. technique of winding non-inductively two or more layers of paper dielectric to each layer of solid aluminium foil, all impregnated under vacuum, and finally hermetically sealed in aluminium tubes.

Cap. $\mu$ F	Wkg. Volts D.C.		Dimns. inches		Type No.	List Price Each
	At 70°C.	At 100°C.	L	D		
.005	1,000	750	1 1/2		CP45W	1/10
.01	1,000	750	1 1/2		CP45W	1/10
.02	750	600	1 1/2		CP45U	1/10
.05	500	350	1 1/2		CP45S	2/1
.1	500	350	2		CP46S	2/2
.1	1,000	600	2 1/2		CP47W	2/6
.25	350	200	2		CP48N	2/3
.5	350	200	2 1/2		CP47N	3/-
.5	500	350	2 1/2		CP91S	3/10
1.0	350	200	2 1/2		CP91N	4/-



DETAILS OF COMPLETE RANGES AVAILABLE ON REQUEST



## THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION: NORTH ACTON · LONDON · W.3 · Telephone: ACOrn 0061

# THE WORLD-FAMOUS *Stentorian* CAMBRIC CONE HIGH FIDELITY UNITS *now available with universal impedance speech coil*



● Here is a most notable advance in loudspeaker design acclaimed at the Radio Show by experts and public alike. It provides instant matching of the speech coil impedance at 3 ohms, 7.5 ohms and 15 ohms, and is at present available on the three models marked with an asterisk. This development will add immeasurably to the great popularity already achieved by the Cambric Cone range among Hi-Fi enthusiasts. Your dealer can show you these new units, or they may be heard at our London Office, 109 Kingsway, any Saturday between 9 a.m. and noon.



### BASS REFLEX CONSOLE CABINET

Easily assembled polished walnut veneer cabinet, designed to give maximum reproduction quality from either the 10" or 12" Cambric Cone unit. Supplied packed flat, with screws, ready for assembly. Size 32" x 22" x 16". Price **£10-10-0**

WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS

Prov. Patent 10037/53


### AT REMARKABLY LOW COST

Model HF510	... 5" Steel Unit	... £1.17.6
" HF510	... 5" Die cast Unit	... £1.19.6
" HF610	... 6" Steel Unit	... £2.10.6
" HF610	... 6" Die cast Unit	... £2.12.6
" HF810	... 8" Steel Unit	... £3. 0.6
" HF812*	... 8" Die cast Unit	... £3. 5.6
" HF912*	... 9" Die cast Unit	... £3. 9.6
" HF1012*	... 10" Die cast Unit	... £3.17.6
" HF1214	... 12" Die cast Unit	... £9.15.6


(Tax paid)

**MAXI-Q**  
REGD.

# IMPROVED I. F. TRANSFORMERS

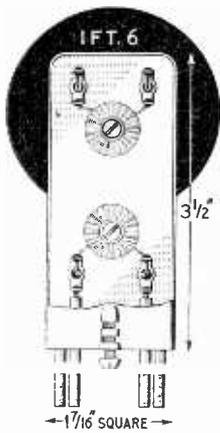

**IFT.6/465 kc/s or 1.6 Mc/s.**—A superior I.F. transformer for use in high quality receivers and tuners. Permeability tuned, Litz wound coils, using Neosid iron dust cores, and high quality silver mica condensers housed in an extruded aluminium can. Termination is made by four coloured leads. Coupling is optimum at 465 kc/s and slightly sub-optimum for increased selectivity at 1.6 Mc/s.  
**IFT.6/465 :** Q at 465 kc/s—130.  
**IFT.6/1.6 :** Q at 1.6 Mc/s—125.  
 The IFT.6A has all leads brought out at the bottom, while IFT.6B has a screened-grid lead. When ordering full details should be given, e.g., IFT.6A/465.  
 Fixing : Two P.K. self-tapping screws on 1-7/16in. centres.  
 Retail Prices : Type A, 9/- each. Type B, 9/4 each.

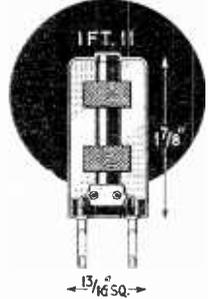

**IFT.11/465 kc/s or 1.6 Mc/s.**—Miniature I.F. transformers for 465 kc/s or 1.6 Mc/s, giving excellent performance at low cost. The coils are Litz wound and permeability tuned with high-grade Neosid iron dust cores. Coupling is critically adjusted to give maximum gain with good selectivity. Ideal for use with Miniature B9A or B7G based valves.  
**IFT.11/465 :** Q at 465 kc/s—75.  
**IFT.11/1.6 :** Q at 1.6 Mc/s—100.  
 Also available for 10.7 Mc/s. Fixing : Two 6 B.A. screws provided. Screening Can : Extruded aluminium.  
 Retail Price : 6/- each.

Obtainable from all reputable stockists, or in case of difficulty direct from Denco (Clacton), LTD. Send 1/- in stamps for General Catalogue.

**DENCO (CLACTON) LTD.,** 357/9 Old Rd., Clacton-on-Sea, Essex  
**Stop Press :** CRYSTAL COIL, PCC.1 (see Brimar leaflet) . . . 7/6. GERMANIUM DIODE BRIMAR GD5 . . . 7/6. MULLARD 5/10 AMPLIFIER CHASSIS . . . 12/6

# BRIMAR VALVES

*More Reliable  
than EVER!*

Brimar's long experience in the manufacture of special quality TRUSTWORTHY valves is now being reflected throughout the entire Brimar range.

Improved production methods, new and better assembly jigs, tighter control on the composition of materials, and the closer supervision of vital processes have resulted in valves with more uniform characteristics, greater mechanical strength and a higher standard of reliability as shown in the 12AT7.

The 12AT7 is a very reliable frequency changer and is widely used in modern TV receivers, VHF and UHF communications equipment. It is also frequently employed in industrial equipment, computers, navigational aids and test equipment.



Use the BRIMAR **12AT7**—with improved performance  
—at NO EXTRA COST



now is the time to

**BRIMARIZE!**

BRIMAR 12AT7	MULLARD ECC81	MARCONI OSRAM B152 & B309	COSSOR EMITRON 12AT7
-----------------	------------------	------------------------------------	----------------------------

Standard Telephones and Cables Limited FOOTSCRAY, KENT. FOOTscray 3333

Great Britain's Valve Mail-Order House

**One Year's Guarantee**

IR5	16/5	ECH25	20/2
IS5	16/5	ECH45	20/2
IT4	14/6	ECL30	20/2
3S4	14/6	ECL80	23/4
3V4	14/6	EF9	19/6
6A4	7/4	EF37A	
1A4	13/3	EF33	22/1
1B4	13/3	EF33	16/5
1F4	10/2	EF40	22/1
1E5G	12/-	EF41	16/5
1F5G	12/-	EF50	22/1
1J6G	12/-	EF90	22/1
5Y3GT		EF91	22/1
6A1	13/3	12A7	22/1
6A25	11/4	12A7	22/1
6A73	15/1	12A7	22/1
6AU6	22/1	12A7	22/1
6BA6	16/5	12A7	22/1
6X4	13/3	12SAGT	22/1
6J6	31/6	12SK7GT	20/2
6SA7GT	20/2	12SK7GT	16/5
6SK7GT	16/5	12SQGT	15/1
6SQ7GT	15/1	12SQGT	15/1
6V6GT	16/5	35Z5G	13/3
7E7	14/6	50L6GT	10/2
AZ1	13/3	10	16/5
AZ3	13/3	12	16/5
AZ50		12	16/5
(DW4)13/3	22	18	3/7
CBL1	21/1	18	3/7
CL1	20/2	18	3/7
CY1	13/3	81	18/11
EB41	11/4	71A	10/2
EB91		112A	8/10
(6AL5)	14/7GT	12SFS	6/2
EBC33	11/4	1C5GT	14/8
EBL1	15/1	1H5GT	14/6
EBF80		1H5GT	14/6
ECC40	18/11	1N5GT	14/8
ECH3	22/8	3A4	16/11
		Post 9d.	6P32

**SALE (2,000 101) TYPES**  
**VALVES FROM 2/-**



**DEMOBDED Valves "Manual" 2/3 Q MAX**

Giving equivalents of British and American Service and (Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still some Valves left at very old Budget Rates (33 1/4%) which are actually sold at the old price. (1951 rate).

**PIFCO**

All in-one Radio - meter A.C./D.C. Tests everything in Radio. Complete with Test prods. 29/6. Post 1/6.



**TYANA TRIPLE THREE**  
Small Soldering Iron Latest development. Complete with detachable bench stand. 19/6. Post 1/-.

**Electric PAINT STRIPPER**

Outdates blow-lamp. It's a unique fool-proof electric cool. Easier and Faster. Clean and safe. Old paint goes like magic. Cost id. per hour. A.C./D.C. Complete. Guaranteed.



**B.T.H. GERMANIUM CRYSTAL DIODE.** Complete with Blueprint and operating instructions. 2/-

**RADIO BULLS VALVES**  
246 HIGH ST. HARLESDEN ROAD



**Chassis Cutters with Keys**  
The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: A die, a punch and an Allen screw. The operation is quite simple. Prices incl. key: 1in. 12/4; 1 1/2in. 12/4; 2in. 13/4; 2 1/2in. 14/6; 3in. 16/- each; 3 1/2in. 18/- each; 4in. 19/6; 4 1/2in. 21/6; 5in. 24/3. Post 1/-.

**TUBES 20/- VCR 97 NEW**

**EMISCOPE**  
Type 4/1  
3" Electrostatic  
20/-

**12" Type 511**  
Electrostatic, same base as VCR 97  
**£4-10-0**

**TAYLOR METERS ON EASY TERMS.** Ask for Catalogue



**Deposit and Monthly 10/- A.C. ELECTRIC PAINT SPRAYER**  
Just plug in and spray. Easier than a brush and twice as fast. Post 2/-. Ceiling Adaptor Free.



**ROD Antennas.** 1ft. sections interlocking and extending. copper plated steel. BARGAIN. dozen 2/6

**"2000" AUTOMATIC BLOWLAMP**

Burns methylated spirit. Completely Automatic. Absolutely safe. Suitable for all kinds of tinman's and silver soldering, glass bending, etc. 2,000 deg. Fahrenheit flame. Post 9d.

**HENRY'S (RADIO LTD.)**

We have over 20,000 American and B.V.A. valves in stock ALL VALVES NEW AND GUARANTEED

1ASGT	10/-	6A85	9/6	35Z4GT	8/6	TDD2A	8/6	PCC81	12/6
1ASGT	12/6	6A7G	6/6	35Z5GT	8/6	DK40	11/-	PCF82	12/6
1N5GT	11/-	6K7G	6/6	25A6	8/6	UL41	11/-	PEN25	6/6
1LD3	7/6	6K8G	9/6	35L6GT	8/6	UY41	11/-	PEN46	7/6
1R5	7/6	6L6G	10/6	50L6GT	8/6	D41	9/-	QP25	6/6
1R5	7/6	6U5	7/6	42	8/6	K72	5/-	SP61	4/6
1S5	7/6	6N7GT	7/6	43	8/6	U52	8/6	SP41	4/6
1T4	7/6	6Q7GT	8/6	75	8/6	U19	10/-	HL23/DD	6/6
1C5	8/6	6S7GT	8/6	80	8/6	Y63	8/6	VP33	6/6
3A4	9/-	6X5G	8/6	886A	15/-	MU14	8/6	VP41	7/6
3V4	7/6	6SA7GT	8/6	TZ40	37/6	PL81	11/-	U22	8/6
3S4	7/6	6SQ7GT	8/6	391A	50/-	PL82	10/-	ATP4	4/-
5Z3G	8/6	6S6G	7/6	EA50	2/-	PX25	12/6	TP22	8/6
504G	8/6	6SK7GT	7/6	ECH35	12/-	PY81	10/-	TH233	10/6
5Z4G	8/6	6SL7GT	9/-	EF54	6/-	PY82	8/6	41MP	7/6
6A7G	8/6	6SN7GT	9/-	EB34	3/6	KT33C	10/6	42SP	6/6
6A8G	8/6	6SCT	10/-	EBC33	8/6	K76	12/6	25SG	4/6
6A8G	8/6	6V6GT	7/6	EF36	6/6	GU50	12/6	MS/PEN	7/6
6AM6	9/6	6AG7	12/6	EF39	6/6	XP2V	4/-	MS/PEN	7/6
6B8	7/6	12K7GT	8/6	EY51	12/-	XH (1.5)	4/-	VT501	7/6
6CSGT	5/6	12K8GT	8/6	EK32	6/6	U111	4/-	ACPEN(7)	7/6
6C6	6/6	12Q7GT	8/6	EF91	9/6	VU134	4/-		
6D6	6/6	12SA7GT	8/6	EL33	10/-	VU120A	4/-		
6P6G	8/6	12SQ7GT	8/6	EL32	7/6	QP230	8/-	DEMID4020	10/6
6G6G	6/6	12S7	8/6	EF50	5/-	VR10530	8/6	FC13C	12/6
6HG6T	5/6	12K7	8/6	Red Syl.	10/-	VR15030	8/6	VP(7)	8/6
6JS5GT	5/6	12SR7	7/6	EF50	5/-	CK510AX	5/6	ID5	8/6
6J6	6/6	25Z6GT	8/6	SP2	8/6	DI	2/-	EF90	10/6
6L7	7/6	25Z5	8/6	VP2	8/6	AC6PEN	6/6	ECL60	10/6

**SETS OF VALVES**

Ten EF50/Ex-Brand New Units). 5/- each

6K8G, 6K7G, 6Q7G, 37/6 ..  
524C, 6V6G, 45/-

1R5, 1S5, 1T4, 1S4, 27/6 ..  
(or 3S4 or 3V4)

TP25, HL23/DD, 37/6 ..  
VP23, PEN25 (or QP25)

6K8G, 6K7G, 6Q7G, 25/- ..  
25A6G, 25Z5 or 25Z6G, 37/6 ..

12K6GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..  
12A7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..

**CRYSTAL MICROPHONE INSERTS**



Ideal for tape recording and amplifiers. No matching transformer required.

**Brand New R.F. UNITS**

RF24 20-30 mc/s. 15/- post free

RF25 40-50 mc/s. 19/6 post free

RF26 50-65 mc/s. 35/- post free

**MORSE PRACTICE**  
H1ZZER  
Complete with Lapper and 4 volt buzzer on baseboard, 6/-, brand new. Post paid.

**R.F. OSCILLATOR COIL UNIT**  
6-18 kv, including EY31 valve, 37/-.

**CRYSTALS**

200 kc's, 2-pin (U.S.A.) ... 10/-  
465 kc's, 2-pin (U.S.A.) ... 10/-  
500 kc's, 2-pin (British) ... 15/-

T.C.C. 1.57,000 v. wkt. Type CP38Q0. Bakelite Case, 7/6 each.

**INDICATOR UNIT TYPE 182A**

This unit contains VCR517 Cathode Ray 6in. tube, complete with W/V metal screen, 3 EF50, 4 SP3 and 15U4 valves, W/V metal controls, resistors and condensers. Suitable either for basis of TV or Oscilloscope. "Scope Constructor" circuit included. 67/6 (plus 7/6 carr.).  
Kit of necessary parts, including "182A" Unit, for constructing "Radio Constructor" Oscilloscope, £8/18/3.

**CATHODE RAY TUBES (Brand New)**

VCR97 (slight cut-off) 15/-  
VCR97, guaranteed full TV Picture ... 40/-  
VCR517C, guaranteed full TV Picture ... 35/-  
VCR39A, guaranteed full TV Picture ... 35/-  
3BP1, guaranteed full TV Picture ... 30/-  
Carr. & packing on all tubes, 2/-.

**DENCO F.M. FEEDER UNIT**

Finest Audio available. Complete kit of parts, including drilled chassis, 5 valves: types 6AM6, 12AH8, EB91 and 2 6AB6. Also complete circuit and wiring diagram, £8/7/6. Or assembled and aligned, £8/10/-, Alignment only, 7/6. Demonstration daily.

**Positively the 2 BEST T/Vs yet built  
for the Home Constructor!**

**The STERN'S "TELE-VIEWERS"**

5 CHANNEL SUPERHET RECEIVERS

Suitable for any transmitting channel and for which commercial adaptors will be available.

**PERFECT PICTURE QUALITY**  
**SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY**

**PERFECT FRINGE AREA RECEPTION**  
**BETTER RECEPTION AT HALF COMMERCIAL COST**

**The "WIDE-ANGLE" TELE-VIEWER**


★ This is the most efficient large screen TV yet offered to constructors.

★ Excellent Time Base efficiency producing 15 to 16 Kv with ample scanning power for C.R.T.'s up to 17 inch.


CAN BE COMPLETELY BUILT FOR

**£33-0-0**

(Plus cost of C.R.T.)

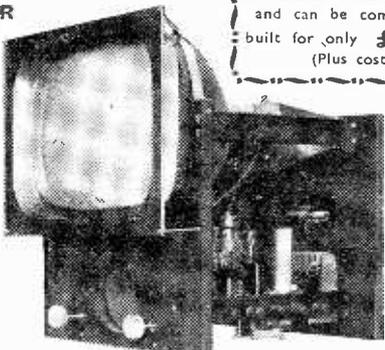

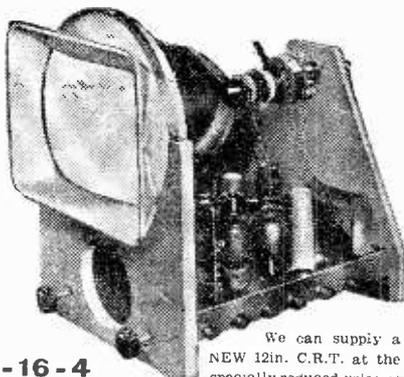This is the 12" TELE-VIEWER and can be completely built for only **£28-16-4** (Plus cost of C.R.T.)



We can supply a NEW 12in. C.R.T. at the specially reduced price of **£12-19-6.** (Carr. & Ins., 15/- extra.)

The complete set of ASSEMBLY INSTRUCTIONS for these T/Vs are available for 5/- each. They include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. AN ATTRACTIVE TABLE MODEL CABINET FOR THE 12in. Model IS AVAILABLE FOR **£6.19.6.**

**STERN RADIO LTD.**

109 & 115, FLEET STREET, E.C.4.

Tel.: CENTRAL 5812-3-4.

**BARTON'S (Radio)**

**BUILD YOUR OWN RADIO!**

We can supply all the parts (including valves, 5in. moving coil speaker, cabinet, chassis, and everything down to the last nut and bolt) to enable YOU to build a professional-looking radio. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets

12in. long, 5in. wide by 6in. high, as follows: either ivory or brown bakelite, or wooden, finished in walnut. Complete and easy-to-follow point-to-point and circuit wiring diagrams supplied.

**MODEL 1. T.R.F. RECEIVER**

This is a 3 valve plus metal rectifier T.R.F. receiver with a valve line-up as follows: **6K7 (HF), 6Z4 (Det) and 6V6 (Output).** The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage is for the Medium and Long Wave bands. Operates on 200/250 volts A.C. Mains.

Plus 2/6 Packing, Carriage, Insur. **£5.10.0**

**MODEL 2. SUPERHET RECEIVER**

This is a powerful midset 4 valve plus metal rectifier Superhet Receiver with a valve line-up as follows: **6K8, 6K7, 6Z4 6V6.** The dial is illuminated and coverage is for the Short Wave bands between 16-50 metres, the Medium Wave bands between 190-540 metres, and the Long Wave bands between 1,000-2,000 metres. Operates on 200/250 volts A.C. mains.

Plus 2/6 Packing, Carriage, Insur. **£7.19.6**

**T.R.F. RECEIVER**

We can supply this Receiver ready built at **£6.15s. 6d.** plus 3/6 p.c.

**ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR**

**NOTE:** We would respectfully suggest to those interested in building this receiver that they send for OUR Instruction Booklet. Intending constructors can then judge for THEMSELVES how comprehensive this Booklet is.

Instruction Booklet and priced Parts List for either of the above available separately at 1/-. This money will be refunded if circuit diagram is returned as NEW within 7 days. When ordering, please state Model No.

**MAINS NOISE SUPPRESSOR KIT**

Consisting of 2 specially designed chokes and 3 condensers. Extremely effective, cuts out all mains noise. Can be assembled in existing receiver or separately as desired. Complete with **4/11** plus 1/- circuit diagram

**WE CARRY LARGE STOCKS OF COMPONENTS AND WELCOME YOUR ENQUIRIES.**

**TERMS OF BUSINESS:** Cash with order (or C.O.D. Post items only); all orders for small items totalling over £2 post free unless otherwise stated.

**BATTERY CHARGER KIT**

Incorporates metal rectifier. Transformer is suitable for A.C. mains 200/250 volts. Charges either 12, 6 or 2 volt accumulator at 1 amp. Complete with circuit diagram. Price **19/11** plus 1/6 post and packing.

(Dept. PW) 34, MONTPELIER RISE, LONDON, N.W.11. Telephone: MEADWAY 1736.

Money Back Guarantee on All Goods

**4-watt AMPLIFIER KIT**

This is a 3 valve 3 stage Amplifier for use with Gramophone, Microphone or Radio. Valve line-up is as follows: **6X17, 6V6, 5Z4.** Negative feed-back. Tone control. Voltage adjustment panel incorporated. 4 watts output. For operation on A.C. Mains 200/250 volts.


The complete Kit includes every item down to the last nut and bolt, drilled and punched chassis, and comprehensive point-to-point wiring circuit diagram. Chassis dimensions: 6in. x 5in. x 2 1/4in.

**ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR**

**PRICE**

**£4.5.0**

Plus 2/6 Pkg. Carr. & Ins.

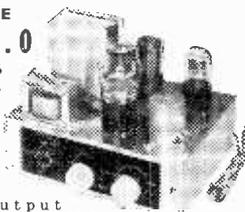


**The Output Transformer**

supplied is for use with a loudspeaker of 9 ohms impedance and we would suggest that the output of the completed amplifier justifies the use of one of the latest W.B. H.F. Speakers which can be supplied as follows: 6in., 80/6; 9in., 67/-; 12in., 73/6. All plus 2/6 pkg., carr., ins.

**Circuit Diagram only, available separately at 1/-.** To those who require this Amplifier ready-built we can supply it at **£5.1.0** plus 3/6 pkg., carr., ins.
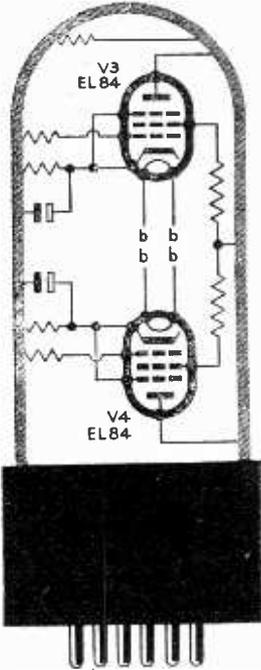
# The MULLARD 5 valve 10 watt High Quality Amplifier Circuit



Mullard have designed a new high quality 10 watt audio frequency amplifier circuit around five Mullard valves. It follows conventional lines and comprises a high gain input stage (Mullard EF86), a cathode coupled phase-splitter (Mullard ECC83) and a push-pull output stage employing two Mullard EL84 pentodes.

Its outstanding advantage is that it achieves really high quality reproduction with simple design

and modest cost of components. Full details of the amplifier and data for the valves are available in booklet form price 2/6 from Radio Dealers.

In case of difficulty write enclosing remittance direct to Valve Sales Dept. at the address below.

*These are the valves for the Mullard 5 valve 10 watt High Quality Amplifier.*

- MULLARD . . . . EF86
- MULLARD . . . . ECC83
- MULLARD . . . . EL84 (2)
- MULLARD GZ30 or EZ80

## Mullard




MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2 MVM 304A

**NEW!**

## RADIO & T.V. OUTFITS
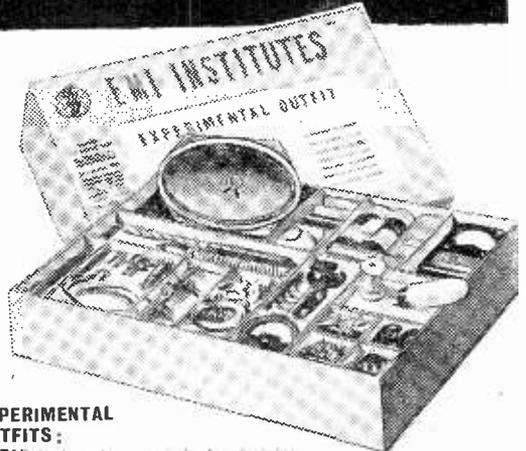
### LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.



**EASY TERMS FROM 15/- A MONTH**

All lessons and equipment supplied immediately and becomes your own property.

**POST THIS COUPON TODAY**

Please send me your FREE book on Practical Courses:

I am interested in.....  
 To: E.M.I. INSTITUTES, Dept. 32X, 43 Grove Park Road, Chiswick, London, W.4.

NAME.....

ADDRESS.....

DEC. ....JC.36

**EXPERIMENTAL OUTFITS:**

**RADIO** basic — A course in basic principles.

**RADIO** — Instruction and equipment from which you build a Radio Receiver.


**TELEVISION** — Instruction and equipment for building a Television Receiver.

Also for Mechanics Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

**E.M.I. INSTITUTES**

The only Postal College which is part of a world-wide Industrial Organisation

# KNOBS *for the practical man*

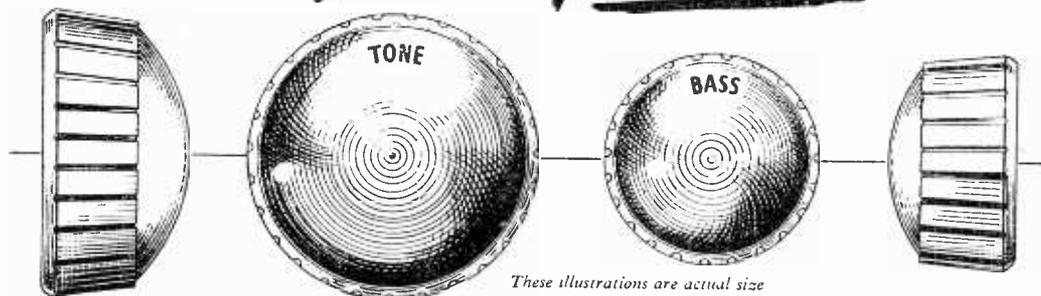

*These illustrations are actual size*

TYPE "A" :—1 1/8" dia. x 3/8" deep. Engraved 1/6. Plain 1/-.

TYPE "B" :—1 1/8" dia. x 3/8" deep. Engraved 1/2. Plain 10d.

## PUTS THE FINISHING TOUCH TO THE JOB.

Make your choice from this modern range of engraved control knobs. 16 special gold-filled inscriptions that will meet your demands. All knobs are suitable for use with 3/16 in. spindles, and firmly held by grub screw and inset locking nut. Available in Walnut or Ivory.

## AN ENGRAVING FOR EVERY PURPOSE.

**RADIO :** "Volume," "Vol/On-Off," "Wavechange," "Tuning," "S.M.L. Gram," "Radio-Gram," "Tone," "On-Off,"  
**TELEVISION :** "Contrast," "Brilliance," "Brilliance/On-Off," "Focus," "Brightness."  
**AMPLIFIER :** "Treble," "Bass." (Plus any of those shown above.)  
**TAPE RECORDER :** "Record-Play."

**YOU CAN OBTAIN THEM NOW FROM YOUR LOCAL COMPONENT STOCKIST**

*If in any difficulty please write direct to :—*

**UNCLES, BLISS & CO. LTD., 139 CHERRY ORCHARD ROAD, E. CROYDON, SURREY.**

# Taylor

## TEST INSTRUMENTS ON 'NO INTEREST' HIRE PURCHASE

We can now offer all Taylor instruments on the easiest of H.P. terms including the new 3 months' scheme where all interest is refunded on completion

of final payment on due date. Alternatively, you can choose to spread the payments over 10 months or 15 months. *Some typical examples are :*

	3 months	10 months	15 months
31A Oscilloscope ...	Deposit £9. 0. 0 and 3 monthly payments of £19. 2. 6	Deposit £6. 0. 10 and 10 monthly payments of £6. 0. 8	Deposit £6. 0. 10 and 15 monthly payments of £4. 5. 5
171A Valve Voltmeter	Deposit £3. 19. 6 and 3 monthly payments of £8. 8. 11	Deposit £2. 12. 11 and 10 monthly payments of £2. 13. 4	Deposit £2. 12. 11 and 15 monthly payments of £1. 17. 9
88A Multirange Meter	Deposit £3. 6. 0 and 3 monthly payments of £7. 0. 3	Deposit £2. 4. 3 and 10 monthly payments of £2. 4. 3	Deposit £2. 4. 3 and 15 monthly payments of £1. 11. 4
77A Multirange Meter	Deposit £2. 5. 0 and 3 monthly payments of £4. 15. 7	Deposit £1. 10. 1 and 10 monthly payments of £1. 10. 2	Deposit £1. 10. 1 and 15 monthly payments of £1. 1. 4
45B Valve Tester ...	Deposit £3. 16. 6 and 3 monthly payments of £8. 6. 4	Deposit £2. 12. 2 and 10 monthly payments of £2. 12. 4	Deposit £2. 12. 2 and 15 monthly payments of £1. 16. 3

**TAYLOR ELECTRICAL INSTRUMENTS LTD.** Montrose Avenue, Slough, Bucks.

Telephone : Slough 21381/3.

Cables : Taylins, Slough.

**acos**


**For  
tape  
and  
disc  
recording,  
P.A.  
and  
amateur  
radio.**

# quality crystal microphones

*at reasonable prices*

A crystal hand or desk omni-directional microphone for the high quality public address and tape recording field, incorporating a specially designed acoustic filter giving a response flat from 30 to 7,000 c/s.  
**RETAIL PRICE £2-10-0d.**

**MIC 33**

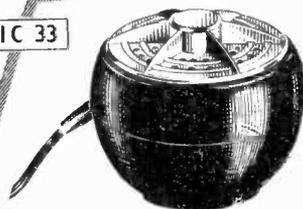


**MIC 36**



A handsome omni-directional instrument of high sensitivity and a substantially flat response from 30 to 7,000 c/s. Alternative models, with or without switch, are available with suitable adaptors for floor or table stands or for hand use.

**RETAIL PRICE: £3-3-0d.**  
without switch or £3-8-0 with switch.

**MIC 35**

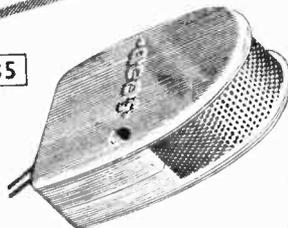

A general purpose hand microphone of robust construction with substantially flat response from 50 to 5,000 c/s. Suitable for recording apparatus. Public Address equipment etc.  
**RETAIL PRICE £1-5-0d.**

*ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.*

*... always well ahead*

**GOSMOGORD LIMITED · ENFIELD · MIDDLESEX**

# PRACTICAL WIRELESS

EVERY MONTH  
VOL. XXX, No. 578, DECEMBER, 1954

EDITOR : F. J. CAMM

22nd YEAR  
OF ISSUE

COMMENTS OF THE MONTH

BY THE EDITOR

## The New "Fury Four"

**T**HIS issue contains preliminary details of the New Fury Four, exhibited for the first time at this year's Radio Show. It attracted a great deal of interest, especially among those who built the original Fury Four in the early 30's. It will, no doubt, be built in large numbers and we propose, as with the original receiver, to produce alternative versions of it. Full-sized blueprints will be available in due course.

### A COMPREHENSIVE VALVE TESTER

**I**N response to requests received over the past two years we this month commence publication of constructional details of a comprehensive valve tester. This instrument although it may be built by amateurs is a professional job, and it will accurately test all of the functions of the valve such as emission, mutual conductance, etc., measurements which are necessary, not only in connection with service work, but in checking up after a receiver has been built.

### LICENCE EVASION

**I**T is often suggested that to prevent wireless licence evasion, people should obtain their licence through the retailer, or at least show him a licence as a preliminary to purchase. This could apply to both sound and TV licences. The Post Office has carefully examined this suggestion, but in making regulations they can only use the powers at present vested in them under the Wireless Telegraphy Act, which makes it an offence to install or use wireless apparatus without a licence. It does not make it an offence to buy or own apparatus without a licence. The Post Office there has no right whatever to demand that a person shall have a licence before he buys a set, unless he actually installs or uses a set which he has bought. Anyone can buy a motor car, but he may not use it without a Road Fund Licence, and he cannot obtain that without a certificate of insurance and a driving licence.

If the law were to be altered so that the P.O. could compel a person to have a licence before he could purchase a set, there still remains the


fact that one licence covers more than one person, and it would be wrong for each man, woman and child in a family to be compelled to possess a personal licence of his own. If that were not done, a great number of people would still be entitled to listen to the wireless and watch TV without having a licence in their own name. If those people were made to show a licence before they bought a set, they would be forced to show somebody else's and this would mean that radio dealers would be given quite

intolerable powers of inquiry into people's private affairs. The public at present are complaining of the incursions which are continually made into the liberty of the subject.

Wireless dealers present another problem. The P.O. has no power whatever to make wireless dealers sell licences or inspect licences. Whilst many of them would cooperate, many would not. Controversial legislation would be necessary to bring wireless dealers into the scheme which would need another band of inspectors to keep the dealers up to scratch. The P.O. has reached the opinion that there seems to be no means of providing by legislation for a direct tie-up. It would impose a great burden on the vast majority of the listening and viewing public in order to bring a comparatively few people to book. No doubt the detector cars are helping to eliminate the problem.
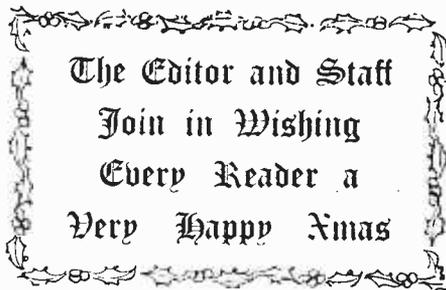
### CAUSES OF ELECTRICAL ACCIDENTS

**T**HE Annual Report of the Factory Department of the Ministry of Labour on Electrical Accidents and their Causes points out that portable electrical apparatus at mains voltage has again been responsible for a high proportion of fatal and serious electrical accidents. The socket outlet, the plug, the flexible cable, the connections and terminal arrangements within the portable apparatus and, last but not least, the earth continuity system and the earthing arrangement in the fixed installation to which the portable appliance is connected, each takes its toll.—F. J. C.



# Round the World of Wireless



## B.I.R.E.

THE following meetings of the above institution will be held during November:

*Scottish Section.*—Thursday, November 11th, 7 p.m., at the Department of Natural Philosophy, The University, Edinburgh. "Nuclear Fission and Nuclear Fusion"—Prof. N. Feather, F.R.S.

*North-western Section.*—Tuesday, November 30th, 7 p.m., at Reynolds Hall, College of Technology, Sackville Street, Manchester. "Electronics and the Wind Tunnel"—G. J. Scoles, B.Sc.(Eng.), (Associate Member).

## By "QUESTOR"

to 5 Mc/s"—G. F. Lawrence.

*London Section.*—Wednesday, November 24th, 6.30 p.m., at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, London, W.C.1. "The Development and Design of Direct-coupled Oscilloscopes for Industry and Research"—M. J. Goddard.

## Transatlantic Calls in 1957

WORK has commenced on a new cable which will link this country with America, supplementing radio telephonic communication and enabling telephone subscribers in Britain and the U.S.A. to talk to each other as easily as on a local call.

The cable is expected to be ready for use by the end of 1957.

## Radio Hire

MANY of Britain's radio sets are earning dollars and other hard currencies without leaving the British Isles. The 500-vehicle London car-hire specialists, Victor Britain, Ltd., are hiring out Pye attache-case battery

portables at a charge of five shillings a day.

The demonstration caused by hiring often results in the sale of a radio or car by British or overseas stores and motor agents.

## Stereophonic Sound Adviser

MISS TESSA FENTON, B.Sc., aged 21, of Claygate, Surrey, has been appointed by Mr. S. L. Bernstein, chairman of Granada Theatres, Ltd., to explain to his patrons how the new stereophonic

sound system works in his cinemas. The new sound device employs four magnetic sound tracks and 24 loud-speakers which enable the sound in a film to be heard from the part of the wide screen where the action is taking place. Miss Fenton can also answer questions put to her by interested cinema patrons on the new development.

## Overseas Airlines Order British Radio

FURTHER evidence that British radio equipment is highly respected throughout the world is reflected in current orders received by Marconi's Wireless Telegraph Co., Ltd.'s Aeronautical Division. They include orders from the U.S.A., India, South Africa and France. More than 40 airlines and over 20 Air Forces now use Marconi aeronautical equipment.

## Broadcast Receiving Licences

THE following statement shows the approximate number of broadcast receiving licences issued during the year ended August, 1954. The grand total of sound and television licences was 13,421,629.

Region	Number
London Postal	... 1,538,506
Home Counties	... 1,419,560
Midland	... 1,218,108
North Eastern	... 1,604,442
North-western...	... 1,239,025
South-western	... 992,623
Wales and Border Counties	... 620,848
Total England and Wales	... 8,633,112
Scotland	... 1,035,209
Northern Ireland	... 219,610

Grand Total ... 9,887,931

## New Branch Office

THE Telegraph Construction and Maintenance Co., Ltd., Telcon Works, Greenwich, announce the opening of a new branch office and depot at 2, St. Nicholas Buildings, Newcastle-on-Tyne, 1, under the management of Mr. R. Fenwick. Stocks are carried of P.V.C. wiring cables and flexibles, radio frequency and broadcast relay types of cables. The branch also handles enquiries for other Telcon products, in-



Miss Tessa Fenton, B.Sc., adjusts the amplifiers on the stereophonic sound system, which has been installed at a Kennington cinema.

*North-eastern Section.*—Wednesday, November 10th, 6 p.m., at Neville Hall, Westgate Road, Newcastle-upon-Tyne. "Stereophonic Sound"—R. A. Bull, B.Sc.(Eng.).

*South Wales Section.*—Wednesday, November 17th, 6.30 p.m., at Cardiff College of Technology, Cathays Park, Cardiff. "The Techniques of Power Measurements from

D. C.

cluding paper-insulated mains cables, having copper or aluminium conductors and with either lead or aluminium sheathing, and products of Telcon's Plastics Division.

**Mr. L. A. Sawtell**

**L**EOARD A. SAWTELL recently celebrated his twenty-fifth anniversary with Mullard Ltd., after more than 30 years in the radio industry.

Mr. S. S. Eriks, managing director of Mullard Ltd., presented Mr. Sawtell with a gold watch and a cheque on behalf of the board of directors and, with other Mullard directors and executives, entertained Mr. and Mrs. Sawtell to lunch. Mr. Sawtell is a Companion of the British Institution of Radio Engineers and a committee member of the Radio Industries Club.

**"Ted Ray Time"**

**T**HE new Ted Ray show, which began in the Home Service on October 25, introduces some new names in sound variety as well as more established favourites. Harold Berens and the multi-voiced Kenneth Connor need no introduction to listeners, but for Audrey Jeans and Don Peters, who have made an impression in other fields of entertainment, it is the first major sound series.

Each week, Ted Ray will have a star guest. Production, as in the last series, is by George Inns.

**Increased Sales in West**

**A**T the official "switching-on" of a new major electricity supply point at Woodcote, near Axminster, recently, Mr. S. F. Steward, chairman of the South Western Electricity Board, said "After years of austerity and restrictions, there is an unprecedented boom in the sales of electricity and labour-saving electric appliances in the West Country."

So far this year, he stated, sales were over 20 per cent. higher than the record set up last year and there appeared to be no letting up in the demand.

**Premium Awards**

**T**HE Council of the British Institution of


Radio Engineers has announced the recipients of Institution Premiums for papers published during 1953.

The premier award, *The Clerk Maxwell Premium*, was presented to three joint authors: W. Saraga, Dr. Phil., D. T. Hadley and F. Moss, B.Sc. for their paper "An Aerial Analogue Computer,"

general meeting of the Institution in London on October 27.

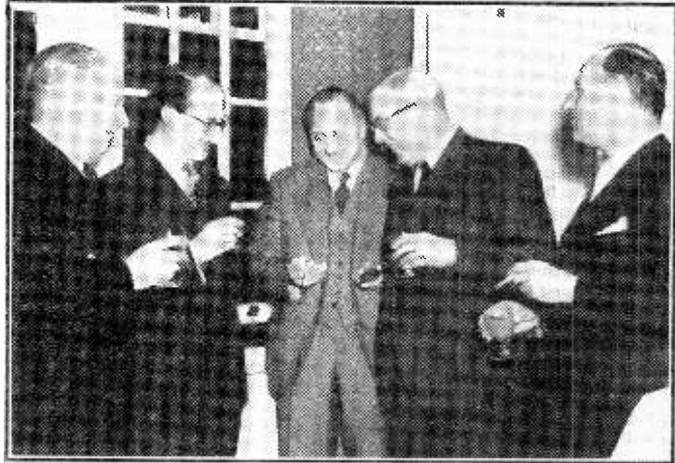**Derby Show Success**

**T**HE Derby Radio Show, organised by the Derby Centre of Radio and Television Retailers, again proved



*Mr. L. A. Sawtell shows some of his colleagues the gold watch presented to him by Mullard, Limited.*

published in the journal for April, 1953. The awards were presented by the president at the annual

a great attraction and attendances were higher than last year.

Traders with stands at the show reported good business and it is estimated that orders taken were three or four times as large as they would have been in the normal course of trade in the shops.

**A "PRACTICAL" Solution to the Gift Problem!**

Have you thought of giving Gift Subscriptions for one of the famous "Practical" Magazines edited by F. J. Camm? They make ideal Christmas presents—and most of your friends are sure to be delighted to receive one of them. Write to-day to the Subscription Manager (G.2.), "PRACTICAL MAGAZINES," Tower House, Southampton Street, Strand, London, W.C.2, enclosing the names and addresses of your friends, the titles of the magazines you wish to send them, and remittance to cover. An attractive greetings card will be sent off, in your name, to announce each gift in good time for Christmas.

A year's subscription to PRACTICAL MECHANICS and PRACTICAL MOTORIST & MOTOR CYCLIST costs 14s., including postage to any part of the world, to PRACTICAL TELEVISION and PRACTICAL WIRELESS 13s. 6d. (Canada 13s.), and to PRACTICAL ENGINEERING £1 12s. 6d. (Canada £1 10s. 4d.).

**Radio Journalism**

**W**HEN the recent newspaper strike began, BBC officials immediately drew up plans whereby leader writers for the different national dailies would be given the opportunity to broadcast their comments over the air, presenting listeners with the political opinions that would have been published normally in the newspapers.



# A VALVE TESTER

A COMPREHENSIVE TEST UNIT WHICH  
MAY BE USED ALONE OR IN  
CONJUNCTION WITH AN OSCILLOSCOPE

By R. Wilkinson

that when "mutual conductance" switch S7 is pressed, a grid "shift" of one volt occurs, and an indication related to the mutual conductance of the valve is obtained by the change in anode current. The filament supply is obtained from a 12-way switch S4, giving a choice of 2 to 50 volts, which covers the most common values in this range. The meter circuit is associated with a range switch S5, giving a choice of milliamps, volts and ohms ranges as follows: milliamps: 1.5, 3, 6, 9, 15 and 30; volts: 150, 300 and 600; ohms: 0 to 50 k $\Omega$ , with two spare positions. Anode, screen, grid and cathode circuits are switched according to the test selected by switch S6 before being connected through to the linking sockets.

## Uses

In position 1 of S6, the meter is connected for use as a simple multimeter, and test leads for external use are connected to the appropriate sockets. Position 2, diode test; position 3, rectifier test;

**T**HE tester has been designed for simple operation, providing a very useful portable instrument. For simplicity A.C. volts are used for the main supplies, and on all tests the meter indicates the average of the current pulses resulting from the self-rectification of the valve under test.

The tester is in two sections, closing together for portability. Circuit connections are made to the valve being tested on the pin-connection panel. This panel, the valve bases, and neon shorts test circuit are fitted in the lid section, connections being made to the other section by an 8-way cord and octal plugs and sockets. Anode and screen supplies from 0 to 250 volts A.C. are in steps of 50 volts, and are supplied from a common winding on the mains transformer. The grid supply is obtained from a 15-volt winding which, after rectification, gives a voltage drop across VR2 of approximately 12 volts; this potentiometer is calibrated in one volt steps for the grid supply. Adjustment of VR1 is made so

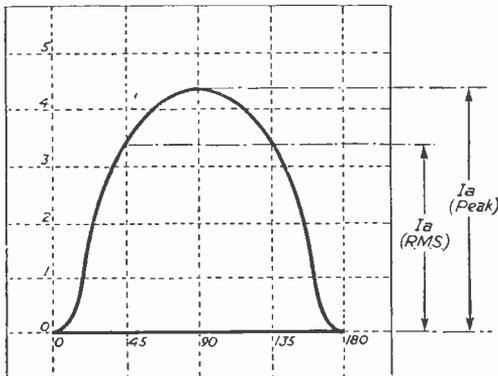


Fig. 3.—The chart for fitting to the "scope

## COMPONENT LIST

- M. Meter. 1.5 mA F.S.D.  
 T.1. Mains transformer (see text).  
 F.1. 1 amp. fuse.  
 L.1. Post Office type lampholder. Wedge type pilot bulb. 12 volt.  
 M.R.1. Bridge rectifier (see text).  
 N.1. Neon, type "G" Osram.  
 Switches :—  
 S1-S2. Single pole 6-way.  
 S3. D.P.D.T. 250 volt, 1 amp.  
 S4-S5. Single-pole 12 way.  
 S6. 7 pole 5-way.  
 S7-8-9. Plunger key switches—spring return.  
 Condensers :—  
 C1. 25  $\mu$ F. 25 volt working. Wire ended.  
 C2. 1  $\mu$ F. Mansbridge type.  
 C3. .001  $\mu$ F. Moulded mica.  
 Resistors :—  
 R1. 1 megohm. R9. 950 ohm.  
 R2. 15 K $\Omega$ . R10. 10 ohm. } Stoppers.  
 R3. 200 ohm. } 1 watt. R11. 100 ohm.  
 R4. 7 K $\Omega$ . R12. 10 K $\Omega$   
 R5. 140 ohm. R13. 5.7 M $\Omega$ .  
 R6. 350 ohm. 1 watt R14. 2 M $\Omega$ .  
 (approx.) R15. 400 K $\Omega$ . (1 watt)  
 R7. 50 ohm. R16. 200 K $\Omega$ .  
 R8. 1 M $\Omega$ . R17. 100 K $\Omega$ .  
 (All  $\frac{1}{2}$  watt, except where stated.)  
 Potentiometers :—  
 VR1. 200 ohm. wirewound.  
 VR2. 2,000 ohm. wirewound.  
 VR3. 100 ohm. wirewound.  
 Miscellaneous :—  
 Plugs and sockets, 2 terminals, neon holder, 2 octal plugs and sockets, miscellaneous valve sockets as required. Hinges, clips and handle.

position 4, cathode leakage test (for indirectly-heated valves only); position 5, valve tests (other than diodes and rectifiers) in which tests are applied for "gas" and "mutual conductance". Facilities are included for the connection of an oscilloscope, for further and more exacting tests. On all tests, filament volts are set and connections made on the pin-connecting panel, as required for the valve under test. For double and triple valves, each section is tested separately; the unused sections being connected to the cathode circuit. Anode, screen and grid volt settings are only required in the "valve test" position of S6.

Test details are as follows:—

**Diodes:** The meter, connected in the cathode circuit of the valve, has a full scale deflection of 1.5 mA. The diode rectified current for an applied 50 volts A.C. is limited to 1 mA. for good valves by load resistors R2 and R4.

**Rectifiers:** The meter is again in the cathode circuit, but shunt R6 is across meter and R4 in series, giving a full-scale deflection of approximately 30 mA. Valve emission is limited to approximately 25 mA. by the values of R3, 4 and 6 for a good valve. On rectifier tests, one side of the filament is connected to the cathode so that direct and indirectly-heated valves may be tested without extra switching.

**Cathode leakage:** anode, screen and grid circuits are strapped together in this switch position. A 50-volt A.C. supply is connected via the meter in series with R5 to one side of the filament of the valve under test; the other side of the supply goes

to the anode. C3 is connected between the filament connection and the cathode and completes the circuit. The valve rectified current is limited by the high impedance of C3, and limited to approximately 1.35 mA. by R2 and R5 when C3 is short-circuited. Any leakage across C3 is indicated on the meter, and can be calibrated by substituting various values of resistance across C3, and marking the scale accordingly. Use any good amplifier valve to supply the rectified current.

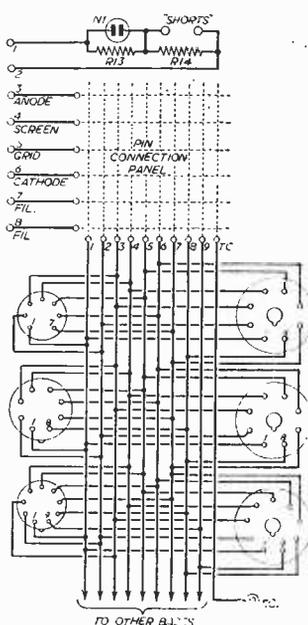


Fig. 2.—Wiring to the valholders.

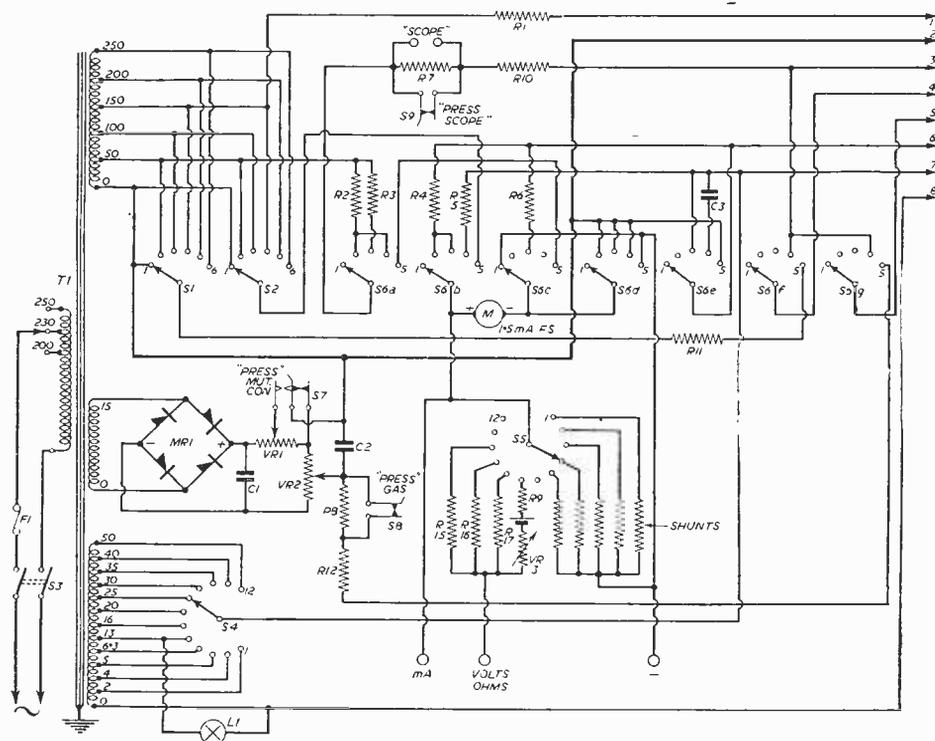


Fig. 1.—Theoretical circuit of the main part of the tester.

**Valve Tests :** All settings are made so that the valve has the correct voltages applied to all electrodes. The meter is connected in the anode circuit and range switch S5 is operative, allowing the milliamps range to be set to cover the anode current for the type of valve being tested.

When switching on, the anode current rises and the meter indicates the average current flowing. Usual tests for softness are included, "gas" switch S8 being pressed to insert a 1 M.Ω resistance in the grid circuit. Indication of a soft valve is given by excessive rise in anode current on this test. On pressing "mut.-con." switch S7, the resulting drop in anode current is related to the mutual conductance of the valve for the applied volts, giving a useful indication of the "goodness" of the valve.

**Working Voltages**

For general tests of valves other than diodes and rectifiers, it must be borne in mind that the meter reading is only the average of the anode current pulses, and a reading should be obtained in the region of half the normal current that would be expected for D.C. working applied volts to the electrodes. When determining the electrode voltages to be applied to compile data, attempts should be made to obtain readings of anode current such that the meter reads 2/3 full-scale deflection for a good valve. The "good," "query," "bad" section of the scale is then operative. The limits of the "query" range representing drops in anode current of approximately 10 to 35 per cent. This can be arranged by choosing normal working anode and screen volts, and reducing the grid volts until a convenient reading is obtained. Lower anode and screen volts can be used if the grid volts have to be reduced too low below the normal working value to get this reading. It is advisable to test power valves at anode and screen settings of about 100 volts in order to keep the anode current low enough for the meter ranges provided.

The values of average anode current and "mut.-con." are tabulated on a data chart, which includes pin-connections and voltage settings for the valve types. These are used as a standard of comparison for future valve tests. (Good valves are necessary when compiling data.) The "scope" sockets are connected across a resistance R7 in the anode circuit which is brought into circuit when the "scope" switch S9 is pressed, on any valve test position.

**Using a 'Scope**

With an oscilloscope connected, the shape of the anode current pulses can be observed, and with the use of a graduated scale, accurate measurements can be made of the anode current and mutual conductance. With a timebase of 100 c.p.s. the pulse shape is shown the full width of the timebase sweep, whilst the non-conducting half cycle provides a base-line trace. Fig. 3 shows the scale for fitting to the oscilloscope screen, the anode current for the applied R.M.S. voltages being measured vertically on the 45 and 135 deg. lines. This application is also useful

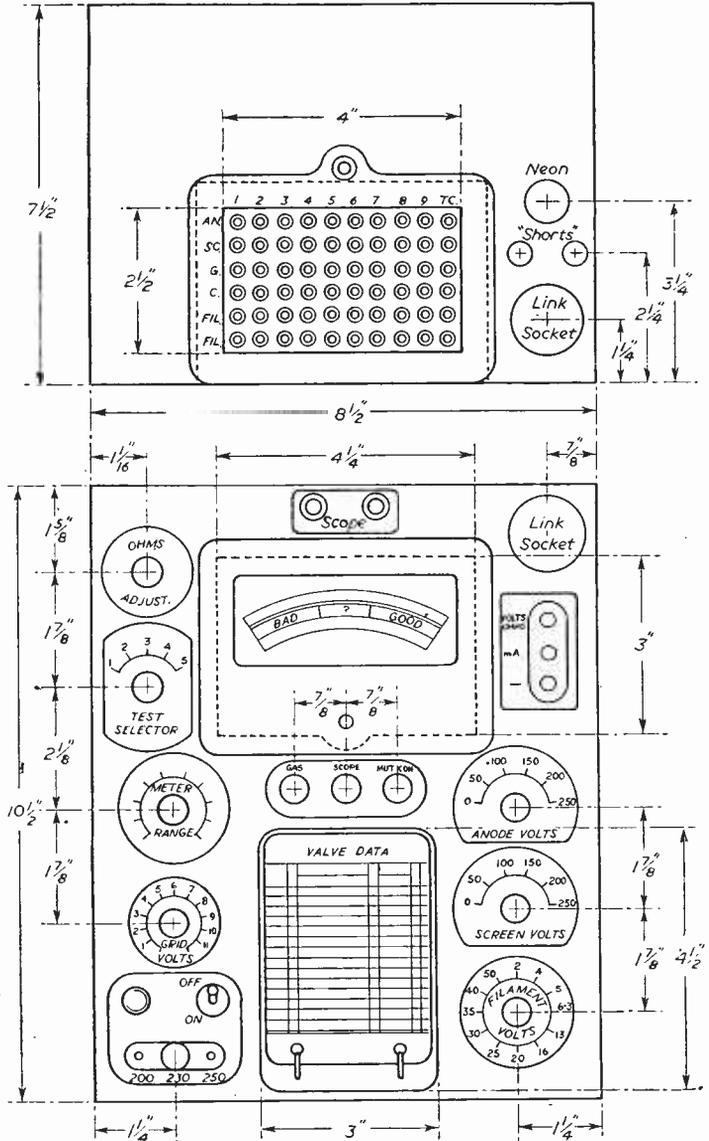


Fig. 4.—Details of the panel layout. See the illustration on page 714.

as an indication of any noise generated in the valve. Directly-heated valves must have one side of the filament connected to the cathode circuit on the pin-connecting panel, as no provision is made for this connection on S6, except for rectifiers. Testing of suspect valves must be preceded by a "shorts" test. Leads are connected to the "shorts" terminals and a search made for electrode shorts on the valve base. This neon circuit is arranged so that a low test voltage is applied and there is no danger of false indicated shorts due to fine wire grids being pulled together.

Any leakage across the test leads results in the few extra volts required being supplied to strike the neon.

**Constructional Details**

The main items required are : 1, Meter. 2, Mains Transformer. 3, Pin-connecting Panel. 4, Rectifier. 5, Switches.

1. Meter. The choice was an ex-Government Western Electrical thermometer marked "air temperature indicator—model 606." This meter encloses a basic 1 mA movement and it is not difficult to fit a new scale, longer pointer, and to zero the pointer to the left-hand end of the scale. The new pointer is a sliver cut from the edge of 18 s.w.g. "hard" aluminium, beaten out and polished with emery paper until a thin section is obtained. The pointer is then cut to shape, and should be 2¼ in. long, and 1/16 in. wide, tapering towards the tip, spade-shaped at the

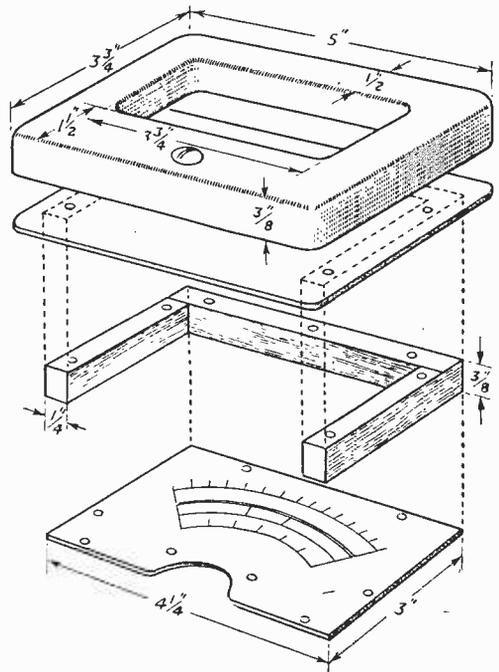


Fig. 5.—Details of the dial mounting.

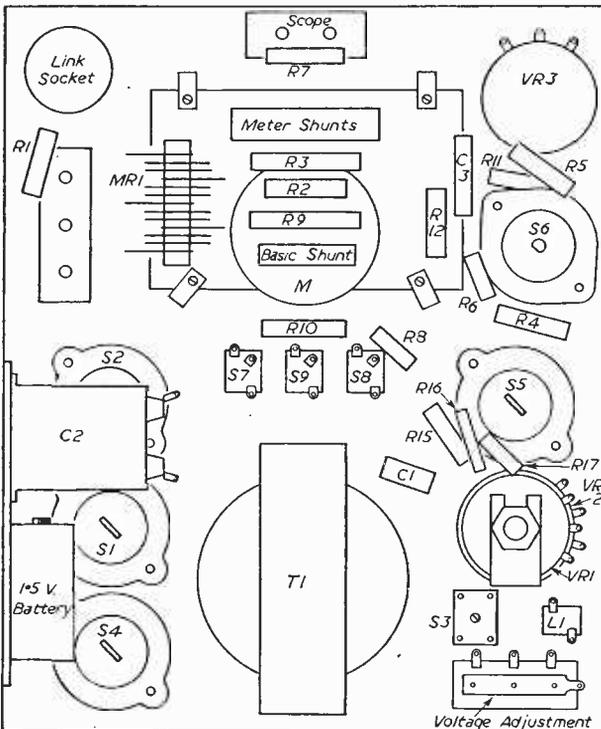


Fig. 6.—General view of the layout of main components.

other end, which is formed to a tube to slide over the pointer stub. A 90 deg. twist is inserted in the pointer ¼ in. from the tube formed. This forms the pointer into a knife edge over the scales. Check the balance before fixing the pointer. The scale can be made in any of several ways, which have been fully covered in previous PRACTICAL WIRELESS articles, after marking it should be fitted to the movement.

Hair springs at each end of the movement balance one another in the zero position, and in shifting the zero to the left-hand end of the scale, both spring anchors must be moved through the same distance in the same direction. This ensures that the torque required to move the pointer off zero remains the same for the new position. Check the balance by tilting the movement from the horizontal to the vertical position, changes in position of the pointer indicating off balance.

Pieces of fuse wire can be wrapped round the balance arms until balance is achieved. Almost certainly after modification, the meter will require more than 1 mA for full-scale deflection, and it will be necessary to shunt the meter with a suitable resistance to give a full-scale deflection of 1.5 mA, this value being the basis on which the scale is designed. The dial is made of hardwood and a Perspex window is fitted, to the dimensions shown, to which movement and scale are fixed.

(To be continued)



DETAILS OF A USEFUL TYPE OF AID FOR THE EXPERIMENTER OR SERVICEMAN

By W. N. Stevens (G3AKA)

IT often happens that a certain component (or combination of components) in a receiver or other piece of equipment being constructed or serviced needs checking to ascertain if it is in good order. Also, and especially in experimental hook-ups, various components may be critical as to value, so that trial and error procedure is adopted until the best all-round practical values have been found. The components concerned are, of course, largely resistors and capacitors.

The experimenter also finds that certain resistance/capacitance combinations can be critical. A combined substitution box, enabling selection of both comparative resistance and capacitance values, is invaluable

Fig. 1. This is, in fact, a capacitor substitution circuit using a British seven-pin valveholder as the "selection panel," with a different value capacitor wired from each pin to a common return line. One test probe is connected to this common return point and the other to a second terminal—the latter also being connected to a short length of flex terminating in a banana plug which is used as the selection plug. To select any of the values provided, the banana plug is inserted into the appropriate valveholder socket. Note that if a metal box is used to house the circuit, the positive test prod terminal must be insulated from the chassis. It is advisable to use the type of valveholder suggested in view of the larger diameter socket holes—octal valve pins are much smaller and some difficulty may be experienced in obtaining suitable plugs to fit the socket holes.

The values shown are merely suggestions; any other combination could be used to suit individual preference. Resistors could also be used if required or a combination type, using two valveholders—one for resistors and one for capacitors—could be easily constructed.

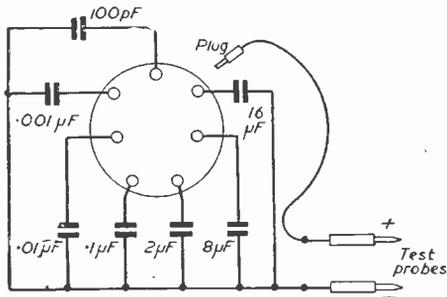


Fig. 1.—The simplest form of capacitor substitution panel.

Switching

A quick-selection substitution box can be built up round a multi-way switch, the only difference being that the switch replaces the plug and socket arrangement (Fig. 2). Two advantages are that selection is easier and quicker and that a greater variety of values are possible in a given space. Assuming the use of a twelve-way rotary switch, the values given in the diagram are probably the most useful for general

in such circumstances and can greatly speed up the preliminary tests—a flick of a switch or the insertion of a plug into a socket is much quicker than tedious soldering and unsoldering of the affected component(s).

Although these notes are written primarily for the guidance of newcomers, the experienced constructor who has never used a substitution box may find them food for thought. Such a simple unit can be of great advantage on the test bench. True, they are about as simple as any piece of equipment can be, yet once built up and put into use they will become one of the "indispensables." Their very simplicity is deceptive and disguises their true usefulness.

The most flexible and easy-to-handle arrangements naturally obtained by building up the selection box around a multi-contact rotary switch, but a very simple idea is shown in

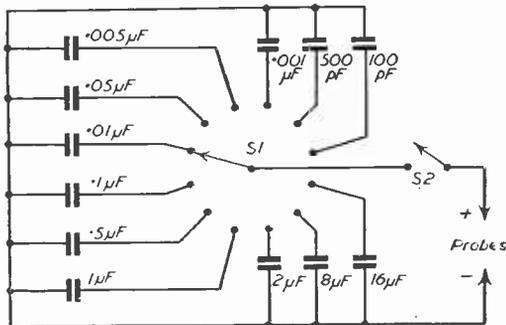


Fig. 2.—A switched version of a capacitor selector.

purposes. The number can be reduced or increased, or the values changed, according to individual taste and requirements.

A similar arrangement for resistors can be used, but here it will be found that for maximum versatility and usefulness a greater range of selection values will be needed. In this case two separate switching units can be used—one for high values, one for low values. The circuit of Fig. 3 shows how this can be arranged; suitable values are given. This arrangement has the

A variation on the theme is the decade box which, as the name implies, provides a selection of values (of resistance usually) in steps of 10 ohms. For this it is usual to use three rotary switches and a collection of resistors as shown in Fig. 4. Although generally used for calibrating test equipment and other precision purposes, it can be used much in the same way as the substitution boxes already described. If accuracy is the aim, the S1 can comprise the "tens" (that is, each resistor is 10 ohms), S2 the hundreds (each resistor 100 ohms), and S3 the thousands. Thus, by suitable adjustment of the three switches any value from 10 to 11,100 ohms (to the nearest 10 ohms) can be selected. Although commercial precision resistors with a tolerance of  $\pm 0.01$  per cent. can be used, this is an expensive way of doing things, and most readers would make up their own resistors using Eureka wire and observing the usual precautions against inductive effects and so forth.

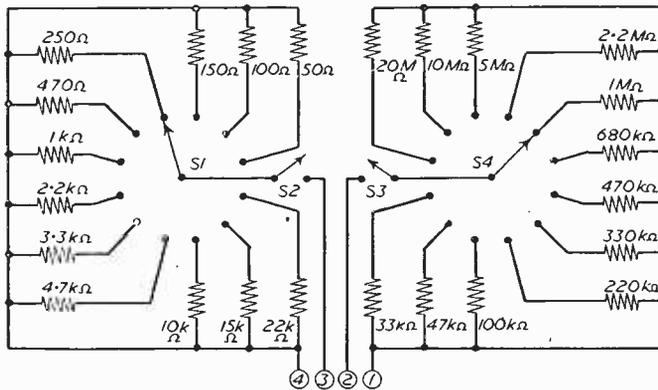


Fig. 3.—Low and high values are selected in this arrangement.

added advantage that by using separate units in conjunction with each other intermediate values can be obtained. Using a shorting link, terminals 1 and 4 are joined together and terminals 2 and 3 become the test connections. By so doing it is possible to place any two resistors (providing they are in separate boxes) in series, thus obtaining extra values not initially provided for.

The resistance substitution box is amenable to a number of variations, despite its simplicity. For instance, if the unit is to be used for the calibration of test equipment, precision resistors could be used. For general-purpose testing, however,  $\pm 10$  per cent. tolerance components are suitable. Generally speaking, one-watt resistors should be used up to values of around 100,000 ohms, thereafter half-watt ratings (or quarter-watt for the megohm values) are usually safe.

**Combined Components**

For a really "self-sufficient" test box, both capacitance and resistance units can be incorporated in one box. It is not intended to discuss the actual housing arrangements since readers will have their own ideas on the subject. One suggestion, however, is to use a small inverted metal chassis with a wooden or ebonite control panel. The switches can be fitted with a simple indicating "dial" marked with the appropriate values. A carrying handle made from webbing or a simple strap will add a nice touch to the finished job if the unit assumes more than vest-pocket proportions.

For more general application, as with ordinary substitution boxes, standard resistors can be used.

One suggestion is that one bank can be used for 100's, one for 1,000's and the third for 10,000's. This would give a range of values from 100 to 111,000 ohms (to the nearest 100 ohms). A fourth switch could be added to increase the overall range of the unit to beyond a megohm. Note that although 10 resistors

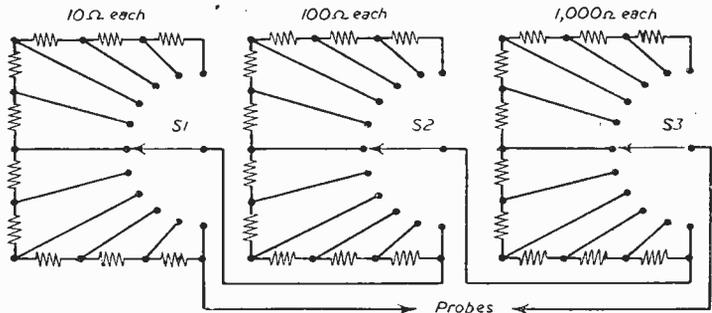


Fig. 4.—A decade selector box.

are used in each section, 11 contacts are required—thus a 12-way switch is generally necessary.

**P.O. Board**

Another way of laying on specific values of resistance is the Post Office resistance board. This has the virtue that only a small number of resistors are needed and in the example shown in Fig. 5 that number is only four. The resistors are mounted on a flat board with the five terminal points provided in addition to a jumper or shorting link. The whole thing is done on the plug-and-socket principle.

To use the board one refers to



a table which depends on the basic resistance values fitted. To take an example from the table shown below: a resistance of 600 ohms is needed. Simply take the test connections to terminals 2 and 4. Again, if a value of 250 ohms is wanted, the nearest on the list is 242 ohms, and to obtain this one test prod is connected (or plugged into) terminal 2 and the other to terminals 3 and 4 (these two having been joined together). In all cases, one test lead is taken to the first terminal given; the second test lead is taken to

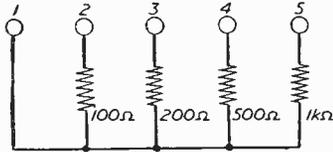


Fig. 5.—The arrangement used in the P.O. box.

Ohms	Test probes to	Ohms	Test probes to	Ohms	Test probes to
55	1 2345	242	2 34	591	4 25
58	1 234	266	2 35	600	2 4
62	1 235	277	3 245	666	4 35
66	1 23	283	3 24	700	3 4
77	1 245	291	3 25	1000	2 5
83	1 24	300	3 2	1058	5 234
91	1 25	333	1 45	1066	5 23
100	1 2	433	2 45	1083	5 24
125	1 345	500	1 4	1100	2 5
142	1 34	533	3 45	1142	5 34
166	1 35	562	4 235	1200	5 3
200	1 3	566	4 23	1500	5 4
225	2 345				

a more representative selection from which to choose. A few simple calculations will enable all manner of variations to this scheme to be worked out. A reference chart (similar to that shown with Fig. 5), could be pasted on the actual board for quick reference.

**Combined Panel**

Going back to substitution boxes, a brief description of a combined resistance/capacitance panel made up by the writer years ago may be of interest. The circuit is given in Fig. 6 and it is so simple that it is a good proposition for beginners. There are 15 resistors and 15 capacitors arranged in much the same way as previously described but with a few extra "spare" terminals. These are very handy because they can be used to provide any arrangement of parallel capacitance, parallel resistance, or a combined parallel R/C combinations. Also, of course, it will be obvious than any series R/C combination can be used.

This type of substitution box or panel proves that although switched units are probably more convenient in use they have certain limitations. For instance, to select any one capacitor (or resistor), the test probes are connected to the "common" socket and to the appropriate socket of the required value. Combined parallel sets of capacitors can be obtained simply by plugging in shorting jumpers where required (i.e., to get 175 pF, join up the 100, 50 and 25 pF outputs). Again, any series pair can be obtained by inserting the test prods into the free ends of the required pair. The fact that series or parallel resistance/capacitance combinations can be obtained on tap will be of great help to those experimenting with filters and similar work.

A very useful test box can be built up in the form

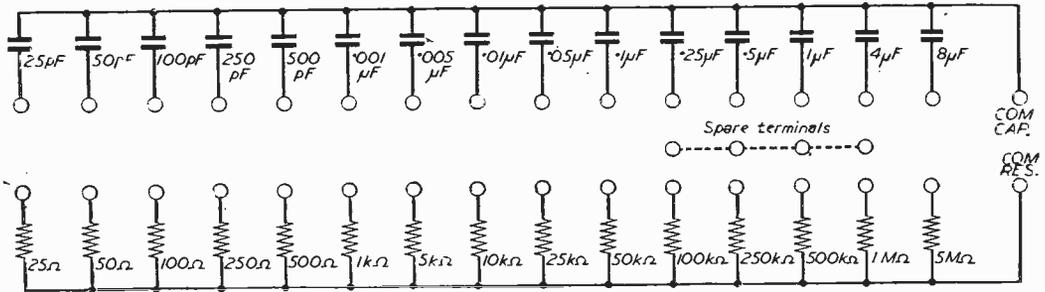


Fig. 6.—Capacitors and resistors are available in this box.

the combined shorted terminals in the second group of figures—assuming that more than one figure is listed. In other words, the four basic resistors are used in a variety of series and parallel connections. With four resistors, 37 different values can be obtained.

Although this system gives a fairly wide range of values to choose from, the overall limits are somewhat small as will be seen from the chart. To overcome this, the answer is to have a series of such boards. Using a simple example, resistance values of 10 times those already shown (and using the same connections) are obtained by using basic resistances of 10 times the value (i.e., 1,000, 2,000, 5,000 and 10,000 ohms). The range can, by this method, be extended in either direction. Perhaps a better scheme would be to use resistors of greater difference so as to obtain



shown in Fig. 7. The basic unit, based on a multi-contact switch, consists of the usual standard resistors and capacitors but has additional provision for two volume (or tone) controls, since it is often desirable to be able to check a suspected variable resistor in a faulty receiver; this enables it to be done without the need to wire in a new control. The various switch positions may, of course, accommodate any component the user considers would be of help. For instance, if a small neon lamp is included this will enable a quick check to be made on "live chassis" receivers that the mains are connected in the safe position. An output transformer could be fitted—this could drive a bench speaker. A choke is another possibility.

With the single switch the unit is quite useful but, it can be greatly improved by the addition of another switch assembly. In the single switch version any

volume controls fitted must have a third separate contact socket. But with the addition of another switch, the third contacts of the potentiometers can be connected to contacts on the second switch—the idea being shown basically in Fig. 7. The main advantage, however, is that by using two switch units (not ganged, of course), two separate components may be inserted into two separate circuits, simultaneously, thus greatly increasing the flexibility of the box. In use, test leads are plugged into the output sockets of the substitution box and placed into the required circuit by their free ends terminating in crocodile clips. Naturally, the purpose of each

switch position should be clearly marked on the panel of the box.

In these few brief notes, various types of substitution boxes have been discussed. No two people have the same ideas on what they consider necessary inclusions in such aids, the final selection of values and scope of the unit being largely dependent on the type of work normally carried out. However, with the suggestions given, the make-up of a substitution box to suit individual tastes should present no difficulties.

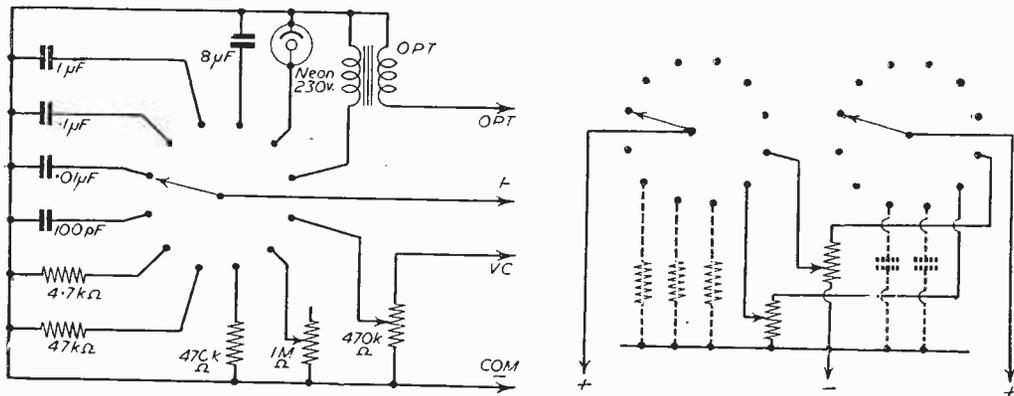


Fig. 7.—A useful basic test unit, and a suggested modification.

## R.S.G.B. Exhibition

THE Eighth Annual Amateur Radio Exhibition, organised by the Radio Society of Great Britain, will be held as in former years at the Royal Hotel, Woburn Place, London, W.C.1, from Wednesday, November 24th, to Saturday, November 27th, both dates inclusive. The exhibition will be opened at 12 noon on the 24th by Mr. H. Faulkner, C.M.G., B.Sc.(Eng.), M.I.E.E., F.I.R.E., director of Telecommunications, Engineering and Manufacturing Association. Mr. Faulkner was, until recently, deputy engineer-in-chief of the G.P.O.

As in past years, the exhibition will be supported by companies who specialise in the provision of valves, components, metal work and publications for the radio amateur. In addition, the Services will be represented.

Members of the R.S.G.B. will exhibit a wide range of home-constructed equipment of modern design, including miniaturised, portable and mobile transmitter-receivers for use in connection with the Radio Amateur Emergency Network. Amateur television will be represented by the actual equipment used by Messrs. W. R. and J. Royle, G2WJ, for their historic 70 cm. tests. Single side-band equipment will be featured, as will V.H.F. and V.H.F. receivers and transmitters.

New editions of "A Guide to Amateur Radio" and the "R.S.G.B. Amateur Radio Call Book" will be on show on the R.S.G.B. stand together with examples of amateur-built equipment, which has been or is to be described in the Society's journal.

The exhibition will open at 11 a.m. and close at 9 p.m. each day. Admission 1s.

## Bel Sound F.M. Tuner

BEL SOUND PRODUCTS have produced a kit for a superhet F.M. tuner, with wide-band I.F. amplifier and stable oscillator, running at 90-110 Mc/s. A ratio detector with infinitely variable A.M. rejection is provided. The first of three identical high-gain V.H.F. R.F. pentodes acts as R.F. amplifier. It is matched by a pi-network to that portion of V2 which acts as I.F. amplifier. The third valve feeds the discriminator, which is the latest type of ratio detector. The A.F. output appears as the in-phase resultant in a bifilar winding, and tertiary winding, and the demodulators are two matched germanium crystals. De-emphasis is incorporated, or can be omitted, resulting in a 6 db octave rising characteristic. Booklets are available at 2s. Weak field strengths do occur, in steel buildings, or immediately behind hills, and an I.F. stage may be added in such cases.

The kit is available with all miniaturised components fully worked chassis finished in Admiralty Blue glossy enamel. The coils are prealigned, although an alignment service is offered at 10s. 6d.

### Miniature Parts

The minimum of valves and components ensures absence of background noise, no drift complications, alignment permanence, incidence of valve failure and small power consumption. In addition the receiver utilises all miniaturised components and a separate Power Pack is available. The price is £7 5s. with valves, or ready assembled and tested for £11 17s. 6d.

# FREQUENCY MODULATION

AN EXPLANATION OF THE PRINCIPLES AND CIRCUITS COMMONLY USED

By A. Thomson

(Concluded from page 686 November issue)

IT is rather early to give a detailed report on the design that FM receivers in this country will follow, and so a short survey of the types of receivers that are being used in the U.S.A. and Germany will be given. These countries have had a FM system operating now for a considerable period.

## Receivers

In the U.S.A. most receivers are of the two-band type capable of receiving the broadcast band (this is equivalent to our Medium Waveband) and the V.H.F. band for FM reception. They are designed to use as far as is possible the same valves for FM as they do for AM, and designers have got up to some very clever schemes. Not all of these receivers are capable of giving the highest fidelity of reproduction that was mentioned at the start of this article. Their big advantage is the freedom from noise and from interfering stations on either side of their carrier frequency, so that FM affords an overall improvement in reception over the congested broadcast bands. Of course, some of the larger sets are designed expressly for the highest quality of reproduction and reproduce faithfully the audio frequencies up to the highest limit (usually 15 Kc/s).

In Germany a large number of super-regenerative receivers have been produced, and the danger from these receivers is the oscillation sent out on the aerial and the interference caused to other sets. However, the authorities have issued stringent regulations to prohibit this oscillation taking place.

The majority of sets in both countries have followed the superheterodyne types and they have been combined to receive AM and FM. The tuning condensers for FM consisting of a unit of approximately 10 to 15 pF are built in with the main tuning condensers. Tuning condensers of this type were shown by British firms last year. There appears to be no difficulty in the designing of I.F. and discriminator transformers and the arrangement in these combined sets is that an I.F. transformer for 470 Kc/s and one for 10.7 Mc/s are used. These are switched into circuit dependent on which Band it is desired to use. Many of these receivers employ a ratio discriminator

and so do away with the limiter stage, but they sometimes have to add an extra I.F. stage so that a large amount of signal will be fed to the ratio discriminator. However, as most of these sets work in the service area the one I.F. stage is usually found sufficient.

A form of permeability tuning used in some German receivers for tuning the V.H.F. band was shown last month. The drive cord is attached to the main tuning drum.

In this country we have not been standing still in the field of FM on the V.H.F. band and our valve manufacturers have given us special valves for use in these receivers. A circuit which will be popular will be the earthed grid input or R.F. stage using a triode valve. The other half of the double triode can be used as an additive mixer stage. This valve, the Mullard ECC85, has very extensive screening between the triode sections and the use of such a valve in the circuits mentioned will reduce radiation from the oscillator to the aerial. Other valves in this range released by Mullard are the ECH81 triode heptode which can be used as a frequency changer on conventional AM bands and switched over to function as 1st I.F. amplifier on FM. A valve specially designed for I.F. work on FM is the EF85. This valve can also be used as an I.F. amplifier for AM reception. Most constructors are familiar with the double diode triode, and now in FM we meet the triple diode triode, the EABC80. The EABC80 can be used in a combined AM/FM set as a ratio detector and 1st AF amplifier when receiving FM, and as an ordinary detector and 1st AF amplifier when using AM.

## Converting A.M. to F.M.

What of converting present-day AM sets to receive this new band? Convertors will most likely take the form of a tuner or feeder unit which will plug into the audio circuit of the present set. The feeder unit will consist of an R.F. stage, frequency changer, I.F. stage, limiter and discriminator stages. Do not forget the need for a power pack as not many sets will supply the power requirements for the feeder unit.

## Aerials

What about aerials? These will for the most part be simple dipoles erected indoors in the loft or outside on the window frame. In the outer areas a dipole with reflector may be necessary for good clear reception, but it is the intention of a FM service that only simple dipoles will be needed to give good reception within the service area of the V.H.F. transmitters. No doubt the aerial manufacturers, who have served us so well with TV aerials, will provide aerials for Band 2 which can be fitted indoors in the room, in the loft, or for attaching to our present TV aerial masts.

FM introduces new problems in the servicing and alignment of these sets, but a description of these must wait until a later article.


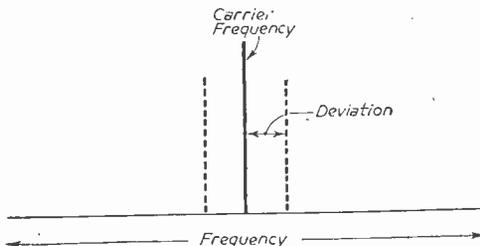


Fig. 9. — Diagram illustrating the deviation obtained in F.M.

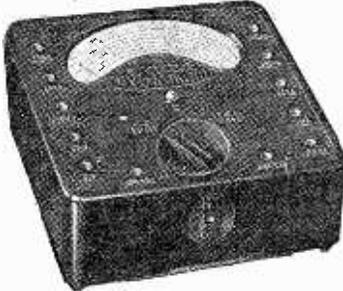

# 'AVO'

Registered Trade Mark.

*Precision*  
**ELECTRICAL TESTING INSTRUMENTS**

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

### The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.

Size: 4½ ins. x 3½ ins. x 1½ ins.  
Nett weight: 18 ozs.

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price: £10 : 10 : 0

### The D.C. AVOMINOR

is a 2½-inch moving coil meter providing 14 ranges of reading of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4½ ins. x 3½ ins. x 1½ ins.  
Nett weight: 12 ozs.

Complete as above  
Price: £5 : 5 : 0

Sole Proprietors and Manufacturers:—

**AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.**  
Winder House, Douglas Street, London, S.W.1. Phone: VICTORIA 3404-9

D.C. Voltage
0—75 millivolts
0—5 volts
0—25 "
0—100 "
0—250 "
0—500 "

A.C. Voltage
0—5 volts
0—25 "
0—100 "
0—250 "
0—500 "

D.C. Current
0—2.5 milliamps
0—5 "
0—25 "
0—100 "
0—500 "

Resistance
0—20,000 ohms
0—100,000 "
0—500,000 "
0—2 megohms
0—5 "
0—10 "

**GUARANTEE:** The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new AvoMinor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

T/V TECHNOLOGY  
ADVANCED SHORT-WAVE RADIO  
RADIO ENGINEERING  
RADIO SERVICE ENGINEERING  
RADAR  
ELEMENTARY ELECTRONICS  
FREQUENCY MODULATION

I.C.S. will also coach you for the following examinations:—

B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

**DON'T DELAY—WRITE TO-DAY** for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful. Reduced terms for H.M. Forces.

Dept. 170D, I.C.S., 71, Kingsway, W.C.2.

**INTERNATIONAL CORRESPONDENCE SCHOOLS,**  
(Dept. 170D), International Buildings, Kingsway,  
London, W.C.2.

Please send booklet on.....

Name..... Age.....  
(Block letters, please)

Address.....




## DIRECT FROM THE MANUFACTURER

**DULCI RADIO/RADIOGRAM CHASSIS**  
Built to Highest Technical Standards

FULLY GUARANTEED

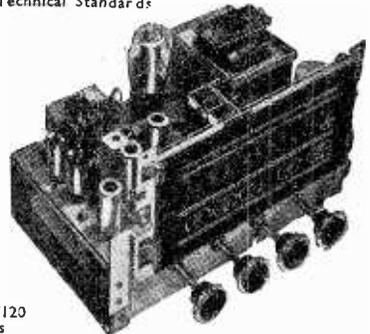All chassis 11½ in. x 7 in. x 8½ in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 tone positions for radio and gram.



For A.C. Mains 100/120 and 200/250 volts


- Model B3.—Long, Medium, Short 5 Valves. Output 3½ watt **£12/12/0**
- Model B3.—Plus Push Pull Stage 6 Valves. Output 6 watt **£15/15/0**
- Model B3.—Double Feature with P/Pull & R.F. Stage. 7 Valves. Output 6 watt **£18/18/0**
- Model B6.—Six Wavebands, Med., Long, 4 Short. (3 Bands spread.) 5 valves. Output 3½ w. **£15/15/0**
- Model B6.—Plus Push Pull Stage 6 Valves. Output 6 watt **£18/18/0**
- Model B6.—Double Feature with P/Pull & R.F. Stage. 7 Valves. Output 6 watt **£23/2/0**

**ALL PRICES TAX PAID**

Escutcheon for 9 in. x 5 in. dial, 4/9 extra. Matching speakers P.M. type 3 ohms. 8 in. or 10 in. available. Chassis sent under money back guarantee conditions against remittance. Free particulars from the manufacturers.

**THE DULCI CO. LTD.,**  
99 VILLIERS RD., LONDON, N.W.2. Telephone: WIllesden 7778

## PATTERN GENERATOR TYPE 4

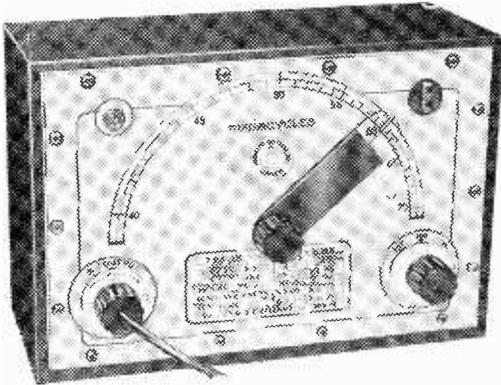


**Price £8.0.0** (Postage and packing 3/6 extra.)

- 40-70 Mc/s. ● A.C. mains operation ● Direct calibration. CHECKS: Frame and line time base frequency and linearity. ● Vision channel alignment
- Sound channel and sound rejection circuits ● Vision channel bandwidth, etc.

**EASY PAYMENT TERMS AVAILABLE ON ALL OUR INSTRUMENTS**

## SIGNAL GENERATOR TYPE 10

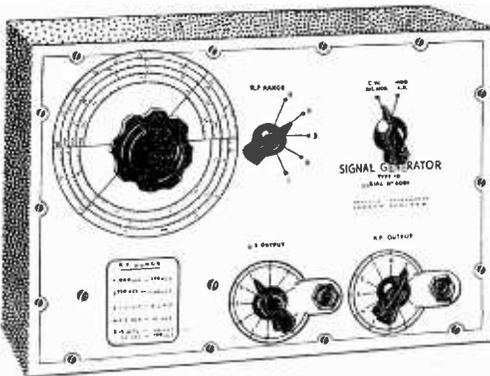

**Price £7.10.0** (Postage and packing 3/6 extra.)

- 100 Kc/s to 100 Mc/s ● Modulated or unmodulated carrier ● Direct calibration ● Adjustable 400 c.p.s. AF signal ● Stable RF oscillator ● Large, easily read scale ● A.C. mains operation.

Obtainable only direct from the manufacturers. Send for full technical details or call at address below.

**HOMELAB INSTRUMENTS LTD.,**  
615-617, HIGH RD., LEYTON, LONDON, E.10

Telephone: LEY 5651

## You can rely on us

**JUST A FEW ITEMS WE STOCK:—**

**NEW JACKSON CALIBRAND SCALE AND DRIVE**, calibrated in figures and self marking scales. Price, 14/6 Twin 25 pF. variable condensers, 10/-. Both are specified for new F.M. receivers.

**TRANSFERS**.—Set for amplifiers and receivers, 3/6. Test equipment, 3/6. Black crackle paint, 3/- tin. Special volume and tone controls for Philips and Mullard receivers, 7/6 each.

Have you built the **OSRAM 912 QUALITY AMPLIFIER**? Book containing full instructions, 3/6. All parts stocked, including 8in. metal speaker G.E.C. £8.15.0. We have Truvox, Lane, Motek and Wearite tape decks available. H.P. ask for details (Also all Avo Instruments.)

**A FEW SURPLUS BARGAIN COMPONENTS:—**  
25 mfd. 25 v. very small, 1/6 each (6 for 7/8); 8 mfd. 450 v., 2/6; 25 mfd. 350 v., 1/- each; 32-32 450 v., 8/-; 32-32 350 v., 6/6; 8-16 450 v., 4/3; 16 mfd. 450 v., 4/-; 4,000 ohm ex-Govt. headphones, 12/6 pair; 6V6G valves, 7/-; 6AM6, 7/-; 3524, 8/6; IC5GT, 12/-; EY51, 19/6; 12AU7, 9/6; 12AT7, 8/6. All the above are brand new and clean.

**WE STOCK** all enamel, silk, cotton, Eureka, tinned copper instrument wires. Resistors, 1 w., 1 w., 4d.; 1 w., 8d.; 2 w., 1/4; 5 w., 1/9; 10 w., 2/-; Midget 1 w., 6d.; 1 w., 8d. All values from 10 ohms to 10 meg. High stab. 2% precision 1 w., 1/6 each; 100 to 2 meg. Over a million in stock. Linear pots, up to 100 K., 5/-; 1, 1.1 mg., 6/8; 1, 1.1 mfd., 2 mg., with centre tap, 7/8.

**Midget** 3-pin plug and socket, 1/-; 4-pin, 1/3; 5-pin, 1/6. Bulgin Midget 3-pin panel fitting — contains three bulbs that can be switched to give any one of three colours, 12/6. Charger transformers 2 v., 6 v., 12 v., at 2 a., 19/6; at 4 amps, plus 24 v. at 2 a., 22/6; 2 a. metal rectifiers, 10/6; 4 amp type, 14/6.

**MIDGET HUNTS HOLDEN CONDENSERS**.—W99 .001, .002, .003, .01, 1 mfd., 1/6. Silver mica, 9d.

**BOOKS**.—"Radio Cadgets," 3/6; "Amplifier Circuits," 2/6; "Oscilloscope Book," 5/-; "TV Faults," 5/-; "Radio Control of Models," 5/-; "Radio Servicing Instruments," 4/6; "TV Test Equipment," 5/-; "Magnet Tape Recording," 4/8.

Write for our 6d. Catalogue and we are pleased to quote any components you may require.

Please add sufficient post and packing fee. Goods sent C.O.D. over £1.

## RADIO SERVICING CO.,

82, SOUTH EALING ROAD, LONDON, W.5. B.A.L. 5737.

## SPECIAL OFFER

G.E.C. & B.T.H.

### GERMANIUM CRYSTAL DIODES

1/- each. Postage 2½d.

Diagrams and three Crystal Set Circuits free.

A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

### POST RADIO SUPPLIES,

33, BOURNE GARDENS, LONDON, E.4.

## EQUIPMENT FOR YOUR WORKSHOP

**BATTERY CHARGERS**. A.C. mains. Charge 2, 6 or 12 volt Batteries at 2 amps. In Grey Steel Case, 8 x 6 x 4 at half normal price. Carriage paid, £3.10.0.

**P.K. SANDBLAST**. Ideal for cleaning valve bases, Sparking Plugs etc. Operates from tyre pump. Instrument, abrasive compound. Instructions, etc. Post paid, 25/-.

**RES./CAP. BRIDGE KIT**. 6 range, 10 ohms to 5 meg.—500 pf. to 50 mfd. Instructions, diagrams, etc., 31/6. Post 1/6.

**INDUCTANCE BRIDGE KIT**. 3 range. 50 μHy., to 100 Hy. 42/6. Post 1/6.


**AUDIO FREQUENCY BRIDGE KIT**. 50 to 16,000 cycles, 38/6. Post 1/6.

**R.M. TWIN MULTIOHMER KIT**. 25/- . Post and packing 1/6.

**I.F. ALIGNER KIT**. 465 kc/s, 17/6. Post 1/6.

**SPOT FREQUENCY SIG. GEN. KIT**. Six switched frequencies, 3 medium and 3 long waves. Fully screened, 35/- . Post 1/6. Illustrated leaflets on request. Trade and Export.

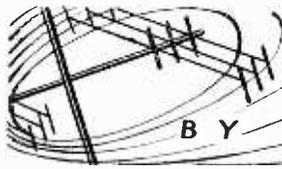**RADIO MAIL, RALEIGH STREET, NOTTINGHAM.**



# On Your Wavelength

BY THERMION

## A Criticism of Critics

EVERY journalist likes to receive not only letters of praise, but letters of criticism. It is his hope that the letters in praise will be greatly in excess of those of criticism. Such has been my experience, and it has been my custom always to deal with the latter, whereas it is *de trop* to deal with the former, on the principle that self praise is no recommendation.

Criticism is stimulating and informative, provided that it is made *bone fide* and couched in reasonable terms. On a very few occasions letters of criticism are received which are neither *bona fide* nor written in reasonable language. Polite letters invite polite replies, but the malicious letter writer, the waspish critic, the critic with the adder fang can hardly expect the contributors concerned to turn the other cheek, even though the gentle answer is expected to turn away wrath.

A few weeks ago a bombastic letter was received from one, C. C. Lewry, who hails from the salubrious district of Hanworth. He says: "I wish to protest in the strongest possible terms on the way in which I and at least three other members of my department were 'caught' to-day by the front cover page of PRACTICAL WIRELESS dated November (on which was depicted the P.W. Tape Recorder). This just advertises the P.W. Tape Recorder, and naturally we expected to be able to construct a tape recorder complete. It turned out, however, that all were disillusioned. The article dealt with an amplifier for a recorder already in existence. The laws of libel forbid me to say more, but I shall be very sure to steer clear of your periodical in the future and I am sure that my friends will do the same."

The cover conveys no such suggestion. It merely says "The P.W. Tape Recorder," several articles on which have already appeared. When our cover draws attention to constructional articles it is the custom to say "Building the. . . ." The constructional details of the P.W. Tape Recorder have already appeared, and therefore Mr. Lewry's letter discloses the fact that he is not, as some might claim, "A regular reader from No. 1." It is obvious that he is just one of those casual readers. Every editor and journalist is accustomed to the phrase "I and my friends are disgusted with etc., etc., and we have all agreed not to take your journal etc., etc." Such letters are never sent by regular readers. They usually emanate from those who haunt free libraries or from those who are not regular readers. Mr. Lewry seeks to ignore the fact that a tape recorder consists of a tape deck and accompanying amplifier. In previous designs, we have utilised commercial tape decks as these are in general beyond the ability of the amateur to construct. A tape recorder design, then, consists of a suitable amplifier with switching gear, to suit the particular tape deck, plus the necessary inter-connection scheme for the heads, etc. In the tape deck design in question, we used the deck specified

for the "Sound Master," as this may be obtained in separate parts by the home constructor and assembled at home, or purchased as a ready-made unit. Our readers, however, have asked for an even cheaper design and the present one has been produced to satisfy those readers. It has the further advantage that it may be converted if desired to the first-class amplifier originally used. Instead of writing a reasonable letter inquiring about the matter, Mr. Lewry dips his pen in vitriol and slashes off the letter I have quoted above. Whilst I as a contributor like to be on the friendliest terms with readers, a state of affairs which has existed for over 21 years, I prefer to be without the casual offensive sort. R. P. Harvey, of Gordon House, Bromsgrove School, Worcs, is another would-be critic of this type. This critic sets himself up as an unpaid corrector of the technical press and in a recent offensive missive criticises in general terms some of our technical matter. He gave no specific examples, but with a supercilious sneer suggested that he would be able to put the matter right. Of course, schoolboys will have their joke, and it turned out that R. P. Harvey is just a schoolboy in the seat of learning I have named. It is obvious that he had not purchased either this journal nor any of our technical books, probably having access to them in the school library. When tackled, this bumptious youth at once caved in, and failed to justify his criticisms when pressed to do so. Naturally, this journal is concerned if criticisms are made, and the matter was taken up with the Principal of Bromsgrove School, who speedily assured us that Master Harvey was merely expressing his own views. It has been pointed out to him that students who write offensive letters on school notepaper can bring discredit on the school, as well as landing them in for other trouble. Splenetic letters are seldom based upon reason. They are conceived in hate and bred in malice, and must be dealt with as such.

Schoolboy Harvey admitted in his letter that he had very little technical knowledge! By this time, I am certain, he has learned the error of his ways.

If you wish to write a letter of criticism, couch it in reasonable language; do not automatically presume that you are right and that the contributor is wrong. There is always the other point of view, and it is my experience that in the majority of cases it has been the critics who are wrong.

## RADIO TRAINING MANUAL

By F. J. CAMM

7th Edition

6/-, by post 6/4

From GEORGE NEWNES, LTD., Tower House,  
Southampton Street, Strand, W.C.2.

# TUNING FEEDERS

SOME SUITABLE DESIGNS FOR USE WITH STANDARD AMPLIFIERS

By F. G. Rayer

THE usefulness of an amplifier can be considerably increased by using a tuner unit to permit radio reception, and such units need not be of complex design. Many amplifiers have a far better frequency response than the usual receiver of general type, and excellent reception with high-quality reproduction can then be obtained. The tuner may have pre-set or fully variable tuning, and be for local station or distant reception. For local stations, a number of T.R.F. circuits can be used, while a superhet circuit is best when occasional long-distance

supply leads have to be arranged. In suitable areas, for local station reception, it has a definite practical utility.

## 1-Valve Tuner

If an earth cannot be provided, and the aerial is poor, a tuner using valves becomes essential. It is also necessary in areas where the BBC transmitters are not well received. If simplicity and low cost are important, the circuit in Fig. 2 can be used with success. It employs a standard medium wave (or dual-wave) tuning coil, with reaction. It is in no way a "quality" tuner, but nevertheless can give good results, while the use of reaction very considerably increases range and selectivity. It is particularly suitable for small two or three valve amplifiers which are not designed to give high quality reproduction. With them local and other stations can be received at good strength and satisfactory quality.

As current for one additional valve can usually be derived from the amplifier, the valve should be chosen with this in view. For 6.3 volt A.C. operation, or .3 amp. A.C./D.C. operation, the 6J7 type is satisfactory. It is desirable to arrange a socket strip or similar connector on the amplifier, so that H.T. and heater currents can be drawn by plugging in the tuner. For A.C. operation from a mains transformer, the heater current will be taken from the 6.3 volt heater secondary of the transformer. For A.C./D.C. operation, such as employed in some very simple amplifiers, the tuner valve heater should be connected between chassis and the heater of the first valve in the amplifier. In this case, the circuit will have to be completed when the tuner is not in use, or the heaters of the valves in the amplifier will

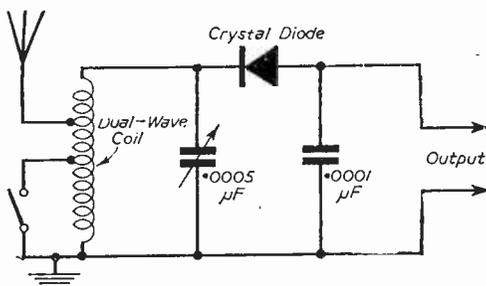


Fig. 1.—A simple crystal diode tuner.

reception is required, or if the BBC transmitters are poorly received in the locality where the equipment is used. With a superhet tuner and a powerful amplifier, a large number of stations can be received at excellent volume, and with a degree of quality satisfactory for all general purposes.

In general, it is possible to derive current for the smaller type of tuner from the amplifier itself, so that no additional mains section is required. But with larger tuners having more than one valve, the transformer and rectifier ratings of the amplifier should be checked to see that no overloading takes place. If insufficient current is available, then a power-pack for the tuner should be made. This can employ a small mains transformer of suitable rating, and preferably a full-wave rectifier.

The simplest circuit is shown in Fig. 1, and employs a crystal diode. It is only suitable for use where a reasonably good aerial and earth can be provided, and in localities where the local BBC stations are well received. Under such conditions, excellent results can be obtained. A dual-wave coil is suggested, for reception of long- and medium-wave stations, but a coil for medium waves only may be used. In some Midland areas reliable reception, at ample volume and interference-free, may be obtained from Light, Home and Third Programme transmitters with such a circuit.

An earth is almost essential, and volume is very much reduced without it. An outdoor aerial is desirable, but quite good results are possible with a fairly long indoor aerial. Apart from its low cost and simplicity, this circuit has the advantage that no current is required from the amplifier, and no power-

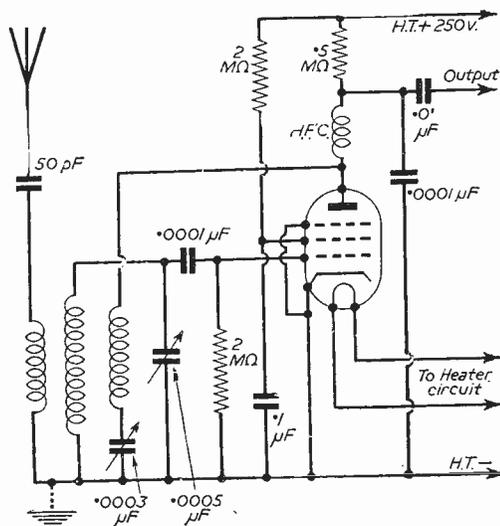


Fig. 2.—A simple one-valve tuner.

remain dead. It is also necessary to take the usual precautions required with all A.C./D.C. equipment, since the supply points (and usually chassis) will be common to one main. Chances of severe shocks will be much reduced by assuring that the low-potential, "earthed" or -ve main is the one going to chassis. With A.C./D.C. equipment, no direct earth must be used on the tuner. If an earth is used, a condenser of about .05  $\mu$ F, 750 volt working, should be included in series with the lead. A condenser of ample voltage working must also be

vided for in this circuit, either by using dual-range coils, or by using separate coils for this band. Additional contacts will be required on the switch, so that the appropriate coils are selected for L.W. or M.W. stations, as the case may be.

**Coupling Circuits**

Some simple amplifiers have no grid input load, it being intended that this be provided externally, by magnetic pick-up or microphone, etc. With these, a grid load must be provided, either in the form of a resistor of about .5 megohms, or a transformer secondary.

Such a stage is shown at "A" in Fig. 4, where transformer coupling between tuner and amplifier is illustrated. The transformer should be of the intervalve coupling type, of about 1 : 3 or 1 : 5 ratio. This is a simple method of coupling the tuner in Fig. 1, when maximum volume is required, and the amplifier is of small type, of moderate gain, and not primarily intended for high-quality reproduction. In these circumstances very satisfying results are obtainable.

The circuit at "B" in Fig. 4 shows capacity coupling, it being assumed that a volume control is already present in the amplifier, as is usual in all but the very simplest equipment. For the tuner in Fig. 1, R1 may be 100 k. The presence of two condensers isolates the tuner from the amplifier voltages. If the amplifier is of A.C. type, with chassis earthed, the .1  $\mu$ F condenser may be omitted.

For coupling the tuner shown in Fig. 2, it is only necessary to take the "Output" lead to the input socket in Fig. 4 "B" to which the .01  $\mu$ F condenser is connected. R1 and the two condensers in Fig. 4 are not required.

With the circuit in Fig. 3, either of the methods given for the tuner in Fig. 1 may be used. However, in order to achieve the highest degree of quality, capacity coupling is desirable, while the .1  $\mu$ F condenser will in any case have to be omitted since a continuous and direct connection is required to furnish H.T. to the valve.

To avoid unnecessary hum and possible instability, the leads from tuner to amplifier should be reasonably short, and leads carrying A.C. should not be near

included in series with the aerial, to keep mains voltages out of this wire.

**An R.F. Tuner**

A circuit for this type of tuner is given in Fig. 3, and though its range is no greater than that of the one-valve tuner in Fig. 2 the standard of reproduction is higher. It may, therefore, be used with high-class amplifiers, and as there is only one valve it should still be possible to derive current from the amplifier.

Pre-set tuning is indicated, stations being selected by means of a push-button switch or rotary switch. This provides simple and accurate tuning, while it should be remembered that the tuner is in any case unsuitable for long-distance results. The pre-sets are switched in in pairs, and each pair adjusted for best results from the appropriate station. For stations of fairly low wavelength, .0001  $\mu$ F to .0002  $\mu$ F maximum capacity pre-sets will be suitable. Those stations of higher wavelength in the medium-wave band (up to about 400 metres) will require .0003  $\mu$ F maximum capacity condensers, while .0005  $\mu$ F will be required to reach the high wavelength end of the band with standard coils. For the latter dust-cored components may be used.

The layout of this tuner is more critical than with those previously described. Leads should be reasonably short and direct, and the coils should be screened or situated one above and one below the chassis. If this is not done, instability is likely, especially when the gain control is set at maximum.

Long waves could be pro-

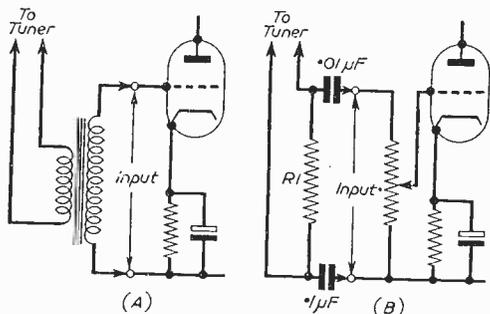


Fig. 4.—Two types of input circuit.

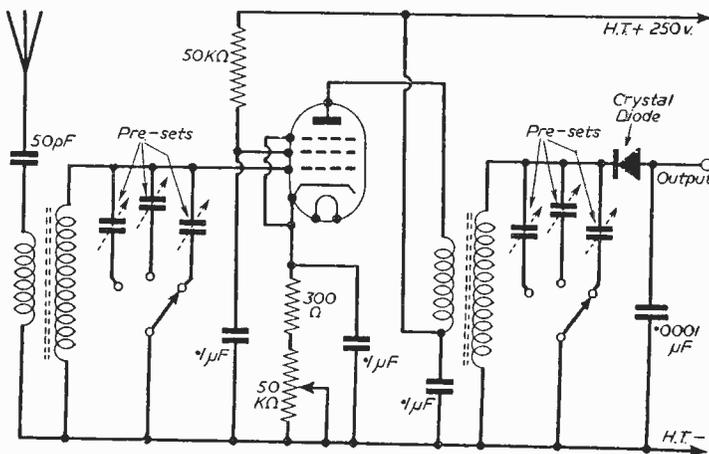


Fig. 3.—An R.F. detector Pre-set tuner.





# The Beginner's Guide to Radio

The Twentieth Article of a Series Explaining the Fundamentals of Radio Transmission and Reception. Further Notes are Given on Valves Characteristics and on the Correct Use of Loudspeakers

By F. J. CANN

**U**NDISTORTED output is the most important of valve details, as it gives a true indication of the power which the valve will deliver. For example, if we know that a particular valve will give an undistorted output of 500 milliwatts (or .5 watts) and that another valve gives an undistorted output of 1,000 milliwatts we know that the latter valve has twice the undistorted output.

## Transformer Curve

In addition to the valve curves the makers of L.F. transformers also publish similar curves which indicate the degree of amplification which may be obtained with those components at various frequencies. It is thus a simple matter to design the amplifier so as to obtain even amplification by choosing two transformers so that the deficiencies of one are compensated for by a high performance of the other. That is to say if one transformer curve shows that that particular component falls off above 2,000 cycles it is possible to choose a second transformer which has a rising characteristic at that point, and by careful matching overall response will be even.

## Pick-up Characteristics

The makers of gramophone pick-ups also publish curves, which are similar in principle to those mentioned above. That is to say, they indicate the level of the response which the pick-up gives, and their use is the same, namely, to enable the amplifier to be designed so that even reproduction of all frequencies is obtained.

The type of the above-mentioned curves is such that they have for their ordinates frequencies usually extending from about 20 cycles to 10,000 cycles, and the co-ordinates are given in terms of amplification. The performance of the component is then indicated by a heavy line running across the graph, and the straightness of the line shows its goodness.

Very few manufacturers of complete receivers or amplifiers issue characteristic curves of the complete apparatus, and manufacturers of loudspeakers are also not, as a rule, willing to issue such a curve. The

design of the set may, therefore, only be worked out with respect to the choice of the transformers, pick-up, valves and, in some cases, the condensers. The above remarks should, however, be sufficient to enable a really straight-line reproducer to be designed in such a manner that all component deficiencies are compensated for.

## The Loudspeaker

The loudspeaker is the instrument in the set which transmits to our ears the result of what has been happening within the set itself. No matter how carefully a set has been designed or made, if the speaker is wrongly matched or unsuitable for the set, the result as far as the ear is concerned is unsatisfactory.

The sounds we hear are set in motion by means of the loudspeaker cone, and therefore the position of the speaker in a room in relation to curtains and furniture is very important. When, as is mostly the case to-day, the speaker is built into the receiver, it is sometimes difficult so to site the set that best results are obtained. Mostly a set is placed near a window to facilitate the fitting of short aerial and earth

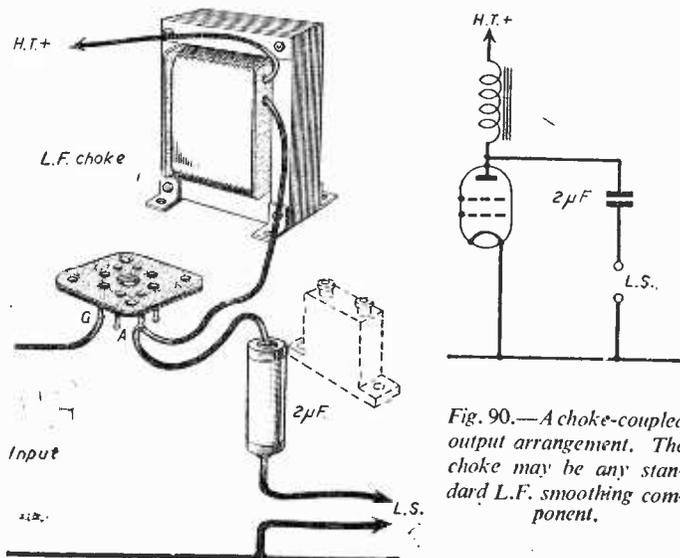


Fig. 90.—A choke-coupled output arrangement. The choke may be any standard L.F. smoothing component.

leads, and so the best position for the set cannot be used. The design of the receiver itself often means that the speaker is not located in the best position in the cabinet. Its position is often decided by that of the tuning control and the gramophone turntable. These are positioned for convenience of operation, and this means that the speaker has to be placed at the bottom of the cabinet and close to the floor.

We are accustomed to hearing the sound of the human voice from a point at an average height of from 5ft. to 6ft. above the ground, and therefore the best height of the speaker is between 5ft. and 6ft. If the speaker is fixed low and the cabinet is standing on a thick pile carpet, close to heavy curtains, as is often the case, the air vibrations are bound to be damped considerably, and will affect the tone of the reproduction. Those who seek after high fidelity reproduction still prefer to have the speaker separate from the set, and away from it, so that the best possible position for it can be found. A corner can often be utilised to advantage owing to the reflection caused by the diverging walls and frequently more pleasing results are obtained when the speaker is placed fairly high so that there is a fair amount of sound reflection from the ceiling.

### The Output Filter

There are two reasons why an output filter is fitted to a set; first, that the filter properly arranged will help to match the impedance of the speaker with that of the output valve and, secondly, the filter isolates the speaker from the anode current flowing in the output valve. Only the low-frequency signal current passes through the loudspeaker, and this is important

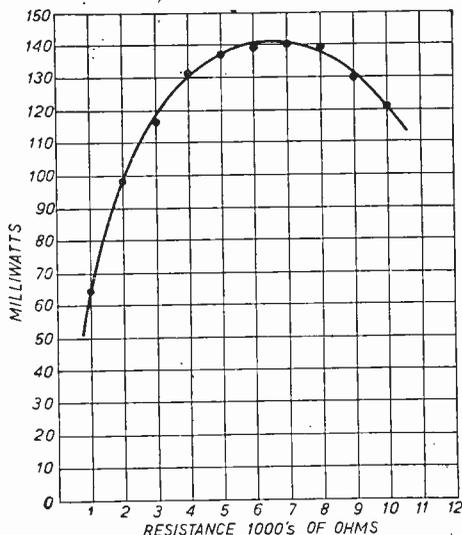


Fig. 92.—Plotting a graph for the output stage.

in mains sets. It not only eliminates all chance of shock if the L.S. terminals are accidentally touched, but in some cases it will minimise hum. Fig. 90 shows a typical output filter arrangement.

There are two types of output filters—the output choke and the transformer.

Fig. 90 shows the choke method which has the

advantage of low cost since the only components required are the output choke and a fixed condenser. The output choke generally should have an inductance of about 20 henrys, and the condenser should be of 2 or 4  $\mu\text{F}$  capacity. The advantage of this scheme is that when long extension leads are used it is only necessary to run one wire from one of the fixed condenser terminals of the output filter to the speaker and the other wire from the speaker to the nearest earth point.

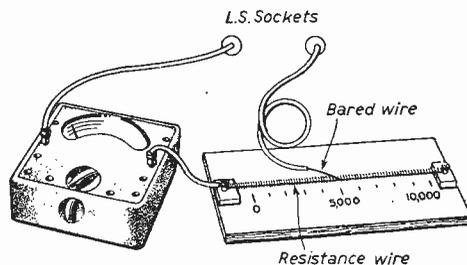


Fig. 91.—A simple output measuring device. The resistance may be made up by using bare resistance wire wound over a thin former.

### The Output Transformer

When a transformer is used the latter component should be of first-class manufacture. The impedance of the secondary is often less than that of the primary, but in some models the primary and secondary are exactly the same. In some cases a drop in signal strength may be noticed when using a 1-to-1 transformer as compared with a choke output. This is often due to a poorly designed transformer.

### Matching the Speaker to the Output Valve

It is first necessary to remember that there is a certain current passing through the speaker, and that there is a certain voltage across its terminals. We have seen in an earlier article that volts multiplied by current in amps equal watts, and that watts are a measurement of power. We want to get as much power or as many watts as possible into the speaker. Take two extremes. If the speaker has a negligible resistance we should obtain a large current but practically no voltage across the terminals and therefore zero watts. But the other extreme is, if the resistance of the speaker is very high, we should get a high voltage but no current. The result as before would be zero watts. Somewhere between these two extremes there is a value which will give maximum watts, and correct matching of the speaker depends upon finding that value, (which depends upon the characteristics of the output valve termed the optimum load) for that valve.

The only instruments required for testing are a milliammeter and a wire-wound resistance of, say, 10,000  $\Omega$ . The meter should have as low resistance as possible so that we can ignore its resistance in arriving at results. The resistance is usually marked somewhere on the instrument but it should not exceed 200  $\Omega$ .

Now, disconnect the speaker, and connect up the milliammeter and the resistance to the output terminals of the receiver as shown in Fig. 91.

(To be continued.)



**The Best Value for money Offered TODAY**  
**ALPHA AMPLIFIER**

This is not a kit of parts. But a fully wired and tested 3-valve amplifier, 7/9s.

- READ THIS SPECIFICATION:**
- \* 3 valves, 6B8G, 6V6GT, 6X5GT.
  - \* A.C. mains fully isolated.
  - \* Dual input network, for crystal or Magna Pick-ups.
  - \* 3 watts output.
  - \* All input and output sockets clearly marked.
  - \* Only 100 per cent. recently manufactured components used.

**MAINS TRANSFORMERS 3-way Mounting Type**

**MTL.** Primary 0-210-230-250 v. Secondary 250-0-250 v. 80 mA., 6.3 v. 4 amps., 5 v. 2 amps., with taps at 4 v. on filament winding. Price 17/6 each.

**MT2.** Primary 0-210-230-250 v. Secondary 250-0-250 v. 80 mA., 6.3 v. 4 amps. 5 v. 2 amps. Both filament windings tapped 4 v. Price 17/6 each.

**MODEL MAKERS. TRANSFORMER FOR TRAIN SETS, ETC.**

**MT3.** 30 volt 2 amp. tappings as follows: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 v. 17/6 each.



**S T A R BARGAINS**

- \* **POCKET TEST METER.** Ex-Govt. volt meter, two ranges, 0-15 volts, 0-250 volts, D.C. 17/6 each.
- \* **COLLAR AC37 GRAM MOTOR.** (Govt) controlled manual adjustment type for 78 r.p.m. Suitable for 100/125 v. 200/250 v. Complete with EMI pattern film, turntable. Price 46/- ea. Post, etc., 2/6.
- \* **TELEVISION PRE-AMPLIFIER.** by Plessey, complete with valve (EF42), a small compact modern unit for London frequency. Price 13/6.
- \* **COMPACT TELEVISION AERIAL** for indoor use London frequency, supplied complete with universal mounting bracket in neutral brown finish. Complete with full instructions. Cat. No. C134. Original price, 50/-. Our price 12/6 ea.
- \* **ROTHERMEL SILENT PILLOW LOUSPEAKER.** Type B4301. List Price, 42/-. Complete with full instructions, 17/6 ea.

**VALVES GUARANTEED NEW AND BOXED**

**LOCTALS.** 7B7, 7C5, 7C8, 7H7, 7Y4, 7H7, 7Q7. All 8/6 ea.

**B7G BATTERY MIDGETS.** 1K5, 1T4, 1K4, 1K5, All 7/6 ea. 2S4, 3Q4, 3V4, All 8/6 ea.

**BATTERY OCTALS.** 1H5GT, 3Q5GT, All 10/6 ea. 1C5GT (D135), 8/6 ea.

**MISCELLANEOUS.** 0Z4, 6/-; 2X2, 5/-; 4D1, 2/9; 954, 2/-; 955, 4/9; 956, 3/6; 9001, 6/-; 9002, 6/-; 9003, 6/-; AC6/PEN, 5/6; E1148, 2/-; EF36, 6/6; H30, 8/-; KT2, 5/-; PX25, 15/-; MS/PEN, 5/-; PLN25, 8/-; VP23, 5/6; PEN46, 8/6; PEN230A, 4/9; QP22B, 7/6; U22, 8/-; U25, 15/-; EF39, 8/6; BBC33, 7/6; 8P61, 3/9; 8P41, 3/6; EF50, 6/-; EF50 (8Y), 8/-; EF54, 7/-; EC52, 5/9; VU111, 3/6; VU120A, 8/6; X65, 10/-.

**B9A RANGE.** PL81, 13/6; PL82, 11/6; PY80, 10/6; EBF80, 11/6; 12P80, 11/6; 12L80, 11/6; PY81, 10/6; PY82, 10/6.

**MAINS MINIATURES.** 6AL5, 7/-; 6AM5, 9/-; 6AM6, 7/6; 6AT6, 9/-; 6B6, 9/-; 6C4, 8/-; 9D6, 9/-; 12AT7, 9/-; 12AU7, 9/-; 12AX7, 9/-; R12 (EY5), 13/6.

**MAINS OCTALS.** 6U4G, 8/6; 5Z4G, 8/6; 6AG, 10/6; 6P6G, 7/6; 6H6GT, 4/-; 6J5GT, 5/6; 6J7G, 6/6; 6K7G, 6/-; 6K8G, 8/9; 6L6G, 9/-; 6L7, 7/6; 681GT, 8/-; 68N7, 9/-; 6U5G, 8/6; 6X5GT, 7/6.

**B9A RANGE.** ECH42, 10/6; EF41, 10/-; EF42, 10/6; EB41, 10/-; EB41, 11/-; EL11, 10/6; EL12, 11/6; EZ40, 10/6; EZ41, 10/6; UAF42, 11/6; UB41, 10/-; UB41, 11/-.

**RECTIFIERS.** VU64 (H14), 8/6; VU39 (M114), 8/6; U18/20 (PW4) 5/9; 9/9; 3Z24GT, 8/6.

**UX RANGE.** 6A7, 10/6; 75, 10/-; 616, 7/3; 6C6, 6/6; 42, 8/-; 80, 8/6.

**B7G RANGE.** EP91, 7/6; P92, 8/6; EB91, 7/-; EL90, 9/-; EL91, 9/-; EY91, 9/-.

**MAINS DROPPERS**

Dubbler type HX7122S, 1.350 Ω with 5 taps, 2/6 ea.  
4.5 Ω Dropper with 5 taps, 2/6 ea.  
Vibrator clips, 4d. ea.  
Dubbler nitrogd condensers 12 mfd. 350 v. D.C., 5/- ea.  
T.C.C. Condenser type CE37PE 100 mfd. 450 v., 4/- ea.

**NYLON DRIVE CORD.** 25 yd. Reel, 2/9.

**AERIAL RODS.** 24in. long. Screw into one another, 6d. each.  
**1 MM. SLEEVING.** Various Colours. 1/- doz. yds.

**MISCELLANEOUS**

6C9	... 2/-	10P9	... 10/6
6L1	... 11/6	10P13	... 11/6
6X4	... 8/6	10P14	... 11/6
6P14	... 12/6	20L1	... 10/-
6P15	... 11/6	20D1	... 10/-
6L13	... 11/-	20P4	... 11/-
6L18	... 11/6	20L1	... 10/6
6L19	... 12/6	H12	... 6/-
8128	... 7/6	PM2B	... 5/6
6T4GT	... 15/-	PM2B	... 5/6
10P1	... 10/-	HP21C	... 7/6
10C2	... 10/6	PCF82	... 11/-

**HEADPHONES**

**Type CLR.** Low resistance 120 Ω, 7/6 pair.  
**Type CHR.** High resistance 4,000 Ω, 11/6 pair.  
**Type DHR.** a super job, 13/9 pair  
**Headbands** wire type, 1/9 each.  
**Headbands** by Trium Radio Mfg. Co., Chicago, U.S.A., 1,200 Ω each earpiece, light headband complete with lead and ligraic jack plug, 13/9 pair.

**CONDENSERS**

The following is a selection from our stocks of manufacturers' surplus condensers all by well-known makers. DUBBLER, B.I., BEC (EDISWAN), SPRAGUE, etc.

Aluminium Can Types, Clip Fixing		
8 x 8 mfd. 450 v. ...	4/-	4/-
8 x 16 mfd. 450 v. ...	4/-	4/-
8 x 24 mfd. 350 v. ...	3/-	3/-
8 x 32 mfd. 475 v. ...	3/6	3/6
12 x 4 mfd. 450 v. ...	2/-	2/-
16 mfd. 450 v. ...	2/-	2/-
16 x 8 mfd. 350 v. ...	2/-	2/-
16 x 16 mfd. 350 v. ...	3/3	3/3
20 x 20 mfd. 500 v. ...	4/9	4/9
24 mfd. 450 v. ...	2/9	2/9
25 x 16 mfd. 350 v. ...	3/6	3/6
32 x 8 mfd. 350 v. ...	3/6	3/6
32 x 16 mfd. 350 v. ...	4/6	4/6
32 x 32 mfd. 450 v. ...	6/11	6/11
32 x 32 x 8 mA. 350 v. ...	5/6	5/6
32 x 32 mfd. 350 v. 25 mA. 25 v. 5/9	6/4	6/4
64 mfd. 350 v. ...	2/-	2/-

**B.R. Range**

B.R.856 8 mfd. 500 v. ...	2/9 ea.
B.R.1520 16 mfd. 500 v. ...	3/3 ea.
B.R.2620 26 mfd. 500 v. ...	3/6 ea.
8 x 8 mfd. 500 v. ...	4/- ea.
B.R.391 50 mfd. 12 v. ...	1/9 ea.

**Midget Metal Types**

2 mfd. 350 v. ...	1/9
5 mfd. 350 v. ...	1/1
8 x 8 mfd. 350 v. ...	3/-
8 x 8 mfd. 450 v. ...	4/-
16 mfd. 350 v. ...	2/9
16 x 8 mfd. 450 v. ...	4/-
16 x 16 mfd. 450 v. ...	4/8
16 x 24 mfd. 350 v. ...	4/9
24 mfd. 350 v. ...	2/9
32 mfd. 350 v. ...	1/9
32 x 32 mfd. 350 v. ...	4/9
250 mfd. 12 v. ...	1/9



**The IDEAL PRESENT**

Walnut finished loudspeaker cabinets. Metal speaker fret, rubber feet fitted, complete with back. Price for cabinet suitable for 6in. speaker, 15/6. Price for cabinet suitable for 8in. speaker, 19/6. Post 1/6 ea.

**ENGRAVED KNOBS**


Control knobs, clearly engraved in gold. Size "A" diameter 1 1/4in. Size "B" diameter 1 1/2in. Both in two colours, Walnut or Cream. Inscriptions available.  
**RADIO** "Volume," "Vol./On/Off," "Wavechance," "On/Off," "Tuning," "S.M.L. Gram"  
**"Radiogram," "Tone"**  
**TELEVISION** "Contrast," "Brilliance On/Off," "Focus," "Brightness."  
**AMPLIFIER** "Trehle," "Bass" (Plus any others).  
**TAPE RECORDER** Record/Play, Prices: Size "A" 1/8; "B" 1/2. Plan knobs can be supplied in either size, 1/- each and 6d. each respectively.

**TERMS:** Cash with order or C.O.D. Postage to be added to orders as follows: 9d. up to 10/-; 1/- up to 20/-; 1/6 up to 40/-; 2/- up to £5. MAIL ORDER ONLY: Send 6d. in stamps or illus. catalogue.

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."



## PRECISION BUILT MATCHED COMPONENTS

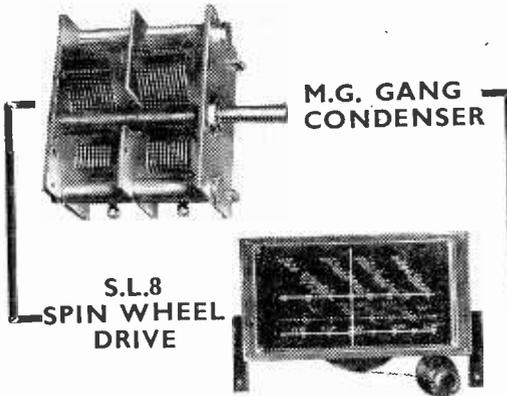

**M.G. GANG  
CONDENSER**

**S.L.8  
SPIN WHEEL  
DRIVE**

### M.G. GANG CONDENSER

Available as 1, 2 or 3 gang, 490 p.F. nominal capacity, matched and standardised to close limits. Supplied with trimmers if required.

Other capacities available—details on request.

Cadmium plated steel frame.

Aluminium Vanes.

Low loss non-hygroscopic insulation.

Spindle  $\frac{1}{8}$  in. dia. projects  $1\frac{1}{8}$  in. from front plate.

Front area  $2\frac{3}{8}$  in. x  $2\frac{1}{8}$  in. including sweep of vanes.

Length excluding spindle :

	Price
1 gang — $1\frac{7}{16}$ in.	9/3d.
2 gang — $2\frac{1}{16}$ in.	14/-d.
3 gang — $3\frac{3}{8}$ in.	18/3d.

### S.L.8 SPIN WHEEL DRIVE

A precision slide rule drive. Complete with 3-band glass scale, 9 in. x 4  $\frac{3}{4}$  in.

Printed—short, medium and long wave bands with station names.

Scale length 7 in.

The spin wheel drive gives easy control through a ratio of 24-1. Fitted with constant velocity coupling, eliminating strain on the Condenser, and providing mechanical and electrical isolation from vibration and noise.

Supplied with florentine bronze escutcheon.

Price — 27/6d. complete.

Write for fully illustrated catalogue.

# JACKSON

**BROS. (LONDON) LTD.**  
KINGSWAY WADDON  
SURREY

Telegrams :  
WALFILCO, SOUPHONE, LONDON  
Telephone : CROYDON 2754-5



L 4679 A

## WEYRAD

### COILS COIL PACKS I.F. TRANSFORMERS AND TV. COMPONENTS

Among the very wide range of components which we produce, types will be found to meet the majority of requirements :

#### "H" TYPE COILS

Individual iron-cored, Aerial, H.F. Transformer, and Oscillator types providing continuous coverage from 12-2,000 metres.

#### "B" SERIES COIL PACKS

Miniature 3-band units covering Long, Medium and Short Wave bands or Medium and 2 Short Wave bands. Alternative tuning capacities 365 pF or 483 pF.

#### P.4. I.F. TRANSFORMERS

Improved types are being introduced to maintain even higher standards of performance and reliability. For frequencies in the range 460-470 kc/s. Dust-core Trimming.

ILLUSTRATED CATALOGUE . 6d.

**WEYMOUTH RADIO MFG. CO., LTD.**  
CRESCENT STREET . . . WEYMOUTH.

## PRATTS RADIO

1070 Harrow Road, London, N.W.10.

Tel. LADBROKE 1734.

(Nr. Scrubs Lane)



**AMPLIFIERS** College General Purpose. Ready to use. units. Model AC10E (as illustrated). 10 watt, 4 valve unit. Neg. Feedback. Separate Pentode Mike Stage and Separate Mike and Gram Inputs, 2 Faders and Tone Control. £10.7.6. Model AC15E 6 Valve Unit with P/Full Output of 14-15 watts. Separate Pentode Mike Stage and Separate

Mike and Gram Inputs, 2 Faders and Tone Control. Feedback over 3 Stages £14.14.0. Model AC32E larger version of AC15E with output of 32 watts £19.15.0. Model U10E for D.C./A.C. Mains. SPEC. as AC15E output 9-10 watts, 6 valves, £12.19.6. All the above amplifiers are complete with cases and chrome handles. Outputs match 3, 8 or 15 ohm speaker. All A.C. models (inc. QOC) have H.T. L.T. outlet for tuning unit, etc. All amplifiers are enclosed and have sectionalised output transformers with Super Silcor Laminations.


**QUALITY AMPLIFIER CHASSIS** for Records/Radio and Crystal Pick-up. Model 99C 6 Valve Unit with Bass and Treble Controls. Williamson 18 Section Output Transformer. Output 9 watts push-pull. Input switching for L.P./Standard/Radio. Adjustable Neg. Feedback. £14.14.0. Stamp for fuller details of above Amplifiers.

**MICROPHONES AND PLAYERS.** Full range for use with our Amplifiers. Latest ACOS, Collaro, B.S.R. and Garrard types available. B.S.R. 3-speed Single Player in Revine Case, £9.9.0. Three-Speed Auto-Changer (mixed) version. Monarch Changer £16.16.0.

**SPEAKERS QUALITY TYPES.** W.B. H.F. 8in. 60/6 : 9in. C7/- : 10in. 73/6. Goodmans Axiom 150 £10.7.6. Audiom 60 £8.12.6.

**TAPE RECORDING.** Complete Recorders from £44.13.0. Tape Amplifiers £15. Truvox Tape Deck £23.2.0. Wearite £35. OSC. Units, etc., available. Send for List TRI.

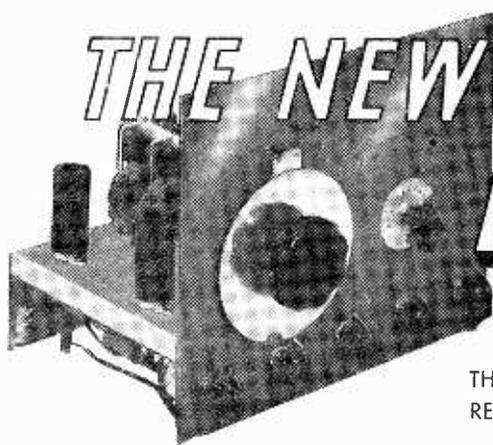**ALL GOODS AVAILABLE ON ONE-THIRD DEPOSIT. BALANCE OVER 12 MONTHS. ALL GOODS ARE BRAND NEW AND CARRIAGE FREE. DEMONSTRATIONS DAILY. NEAREST STATION KENSAL GREEN.**



# THE NEW Fury Four

THE LATEST VERSION OF OUR POPULAR TWO-R.F. RECEIVER, WHICH IS FULLY ADAPTABLE FOR MANY PURPOSES


**I**N introducing the new Fury Four we have endeavoured not only to produce an up-to-date version of the original Fury Four circuit, but also to try to produce a design which may be adapted according to the particular needs of the majority of our readers. In January, 1933, we introduced a receiver circuit employing two H.F. stages, as a large number of readers had expressed a preference for the straight receiver rather than a superhet. Although the superhet is very popular many readers hesitate to build one in view of the probable difficulty of alignment. The question of expense is also often raised. It was, therefore, thought desirable to produce a straight type of receiver which went beyond the usual H.F.-detector arrangement, and again to use two H.F. stages. Normally it is extremely difficult to design a stable receiver with more than one H.F. stage, as elaborate screening becomes necessary, but in the new receiver this difficulty has to a large extent been overcome by using only one tuned circuit in the two stages.

When preparing this design we were also rather concerned to try to cater for a large variety of special needs. When we introduce a design we are usually flooded with inquiries asking how the receiver may be modified to take care of some particular circumstance—one group of readers want tone control, others do not. Some want to use the receiver for record reproduction mainly, whilst others have no interest in this branch of radio but prefer to spend all their spare time searching for long-distance stations. Again, one group of readers want short, medium and long-wave tuning, whilst others have no interest in the short waves. It will be appreciated, therefore, that it is very difficult to design a receiver which can fill all these individual requirements, and usually two or three different models have to be produced. In the new Fury Four we have tried to make the design as flexible as possible, without

introducing unnecessary complication, and we therefore present a circuit which may be built as a three- or four-valve receiver; with or without reaction; with or without tone control; for one band or three, and as a special set for the amateur "den" or as the family radiogram.
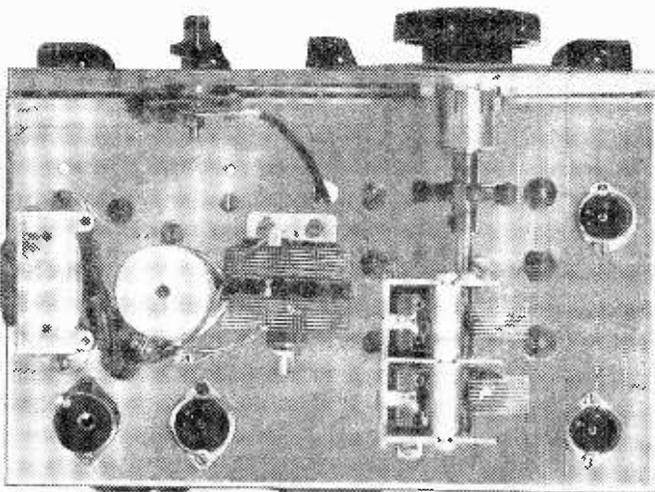
#### The Circuit


Examination of the circuit on page 734 will show that several parts have been indicated in broken lines. These are the optional parts of the circuit and may be included or left out as desired without in any way interfering with the performance of the receiver. Taking the receiver stage by stage we see that it starts off with an untuned H.F. stage using a modern B7G type pentode. Isolation is effected for the aerial and earth leads by fixed condensers which must be rated at 750 volts or more, as the mains side of the receiver employs A.C./D.C. technique which leaves the chassis "live" to one side of the mains. The potentiometer which is used in place of the first




*The top of chassis is clean and tidy with a minimum of wiring.*



tuning circuit enables the first valve to operate with considerable gain at all frequencies, and thus makes up for an inefficient aerial, or, if a good aerial is used, gives an appreciable gain to all signals, rather than to one particular frequency, which would be the case if the aerial circuit were tuned. The signals are tapped off by means of the potentiometer, thus providing an effective H.F. or R.F. volume control, and in order to give full efficiency to this form of control it is linked back to the cathode circuit of the second R.F. stage. Thus, as the input is varied, so is the bias on the second valve, which is of the variable- $\mu$  type, and the combination acts very effectively in preventing overloading of the detector—a necessary feature if one desires good quality. Coupling between the first and second R.F. stages is effected by a normal H.F. transformer, and here we have employed separate coils rather than a commercial coil unit so that the necessary flexibility may be introduced. The coils are the Maxi-Q products by Denco, and they are easily fixed by means of their one-hole fixing nuts, and have an iron-core for matching. They are tuned by a 310 pF condenser instead of the usual 500 pF, and this improves performance on the short waves. It will be seen in the circuit diagram that a three-way switch is used for each coil (these being in the form of a six-position, three-way Bulgin component), and instead of using a

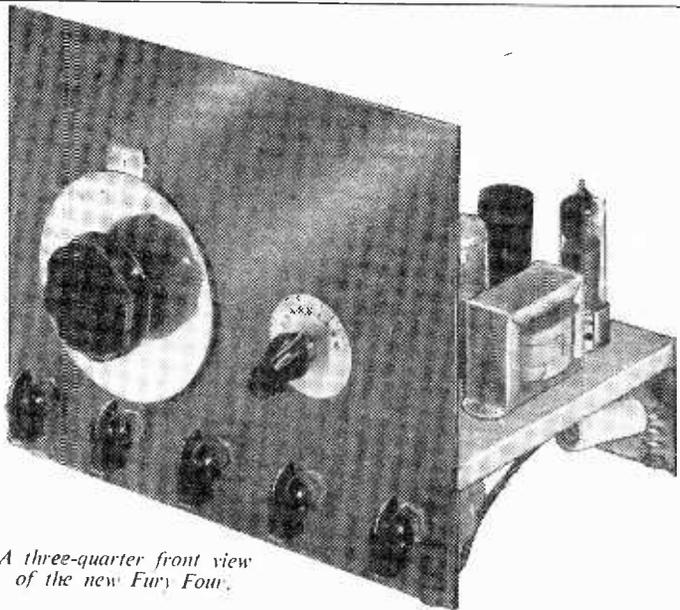

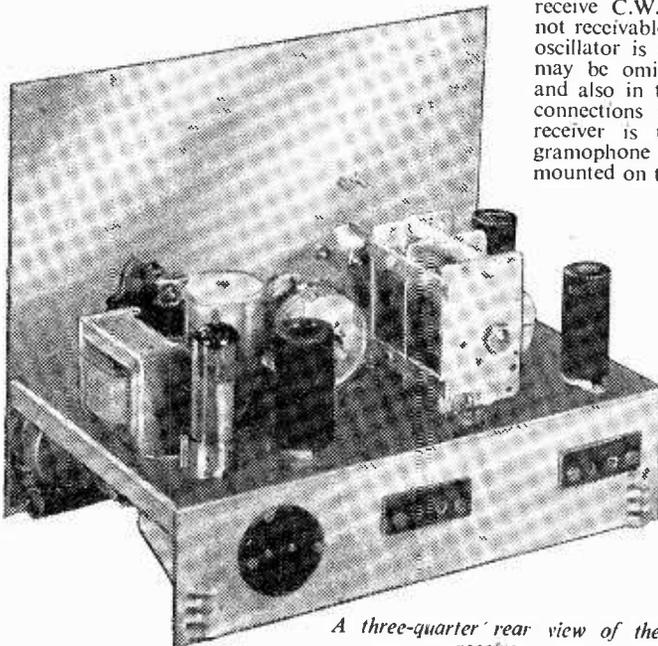*A three-quarter front view of the new Fury Four.*




*A three-quarter rear view of the receiver.*

short-, medium- and long-wave coil at each position, the constructor may use two or three short-wave coils, may cut out the switch entirely and use just the medium-wave coil, or otherwise modify the coil combination. The Yellow range of coils is used between the two R.F. stages, and to feed the detector stage a Green coil is used as this has a reaction winding. Again, this winding can be ignored if desired, and it is included as it enables the user to receive C.W. transmissions—which are, of course, not receivable on a superhet unless a beat-frequency oscillator is employed. The entire reaction circuit may be omitted including the reaction condenser, and also in the detector stage will be seen pick-up connections also shown in broken lines. If the receiver is to be used for the reproduction of gramophone records the pick-up sockets should be mounted on the rear runner and connected between grid and earth. A change-over switch may be included if desired, or the entire previous part of the receiver may be omitted and the receiver built from the pick-up terminals onwards, as a record player.

It has been mentioned that the R.F. gain control is used to reduce the strength of signals fed to the detector stage so as to avoid overloading, and the output from this stage may even still be sufficient to overload the first A.F. stage. The output from the pick-up may also, with some records, be too great for the first A.F. stage, and therefore an audio or A.F. volume control has been included. The detector and first A.F. stage form the two triode sections of a double triode, and although an ECC81 has been specified for this, in some localities it may be possible to use an ECC82,



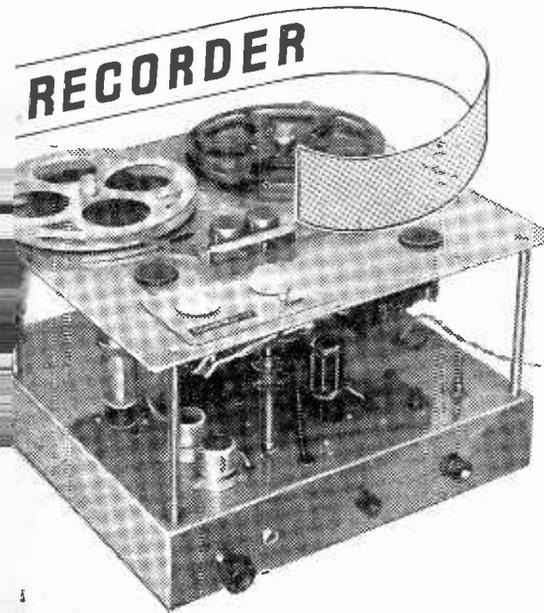

neon. This has been fitted with a piece of rubber sleeving for protection only.

Little more need be said about construction except again to emphasise the fact that the layout and the wiring should be strictly adhered to.

Incidentally in comparing the wiring diagram, Fig. 5 (page 738), with the theoretical diagram, published last month it will be noted that the rectifying valve is shown in one diagram with a cathode and in the other without a cathode. We have actually used a 6X5 which has a cathode, and if an alternative type of valve is employed of the directly-heated type the H.T. positive connection will be taken to one side of the heater instead of to cathode. All other wiring details may be gathered from an examination of Fig. 5, and the illustration of the underchassis view below.

**Testing**

When the amplifier has been completed, tests may be carried out, initial checks being made to ensure that there is no direct short in the H.T. and heater circuits. Valves may then be inserted and with the selector switch in the centre position, checks can be carried out using a microphone or gramophone pick-up. If these checks are satisfactory, the record and erase heads should be connected to the tape deck and preparations made to produce a recording. Perhaps the most important adjustment which has to be carried out is the setting of the level control priming voltage to the neon indicator, but this can only be done after experience has shown to what level the amplifier has to be set. The best way of arriving at the correct level setting is to make several recordings at different levels and determine which is the best, if necessary also making some adjustments


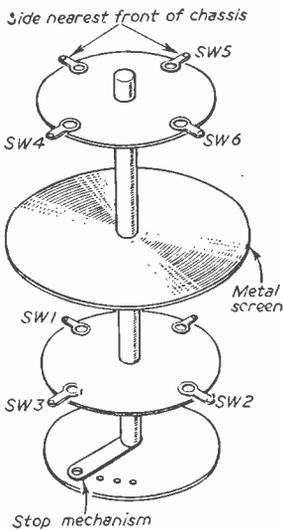


Fig. 6.—How the switch assembly is made up.

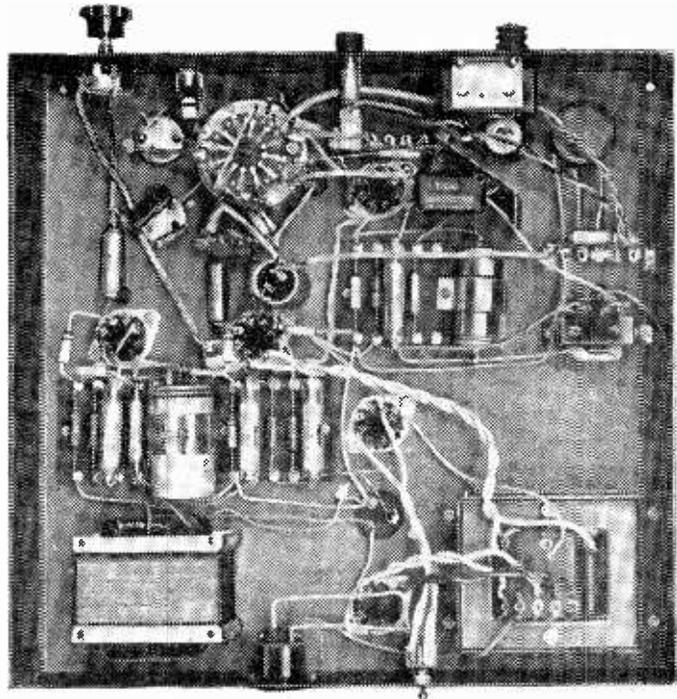

Below chassis view of the wiring.

to the bias control, commencing with this in the mid-position. Having determined the best recording level, then a further recording is made, this time with the level indicator switched in and the control adjusted until the neon flashes on peaks. An incorrect setting of this control will cause the neon to strike continuously or at low audio levels, and it is essential for good recordings that the level control be correctly adjusted. Once this setting has been found it need never again be adjusted unless some modifications are made to the amplifier itself, and in use it is switched in only when first setting up, the recording level adjusted until the neon flashes on audio peaks, the push-button switch released, and so long as there

are no wide variations in the audio input the recordings will be free from overloading yet will have adequate output.

**Performance**

The lack of tone controls has not been found at all serious as in practice there are very few recordings that have shown an excess of top or bass, and in only one case has it been found necessary to reduce the high-frequency response due to the "toppy" nature of the recording, and this was done by connecting a .01 $\mu$ F condenser in series with a 50,000 $\Omega$  variable resistor between the anode of V3b and chassis.


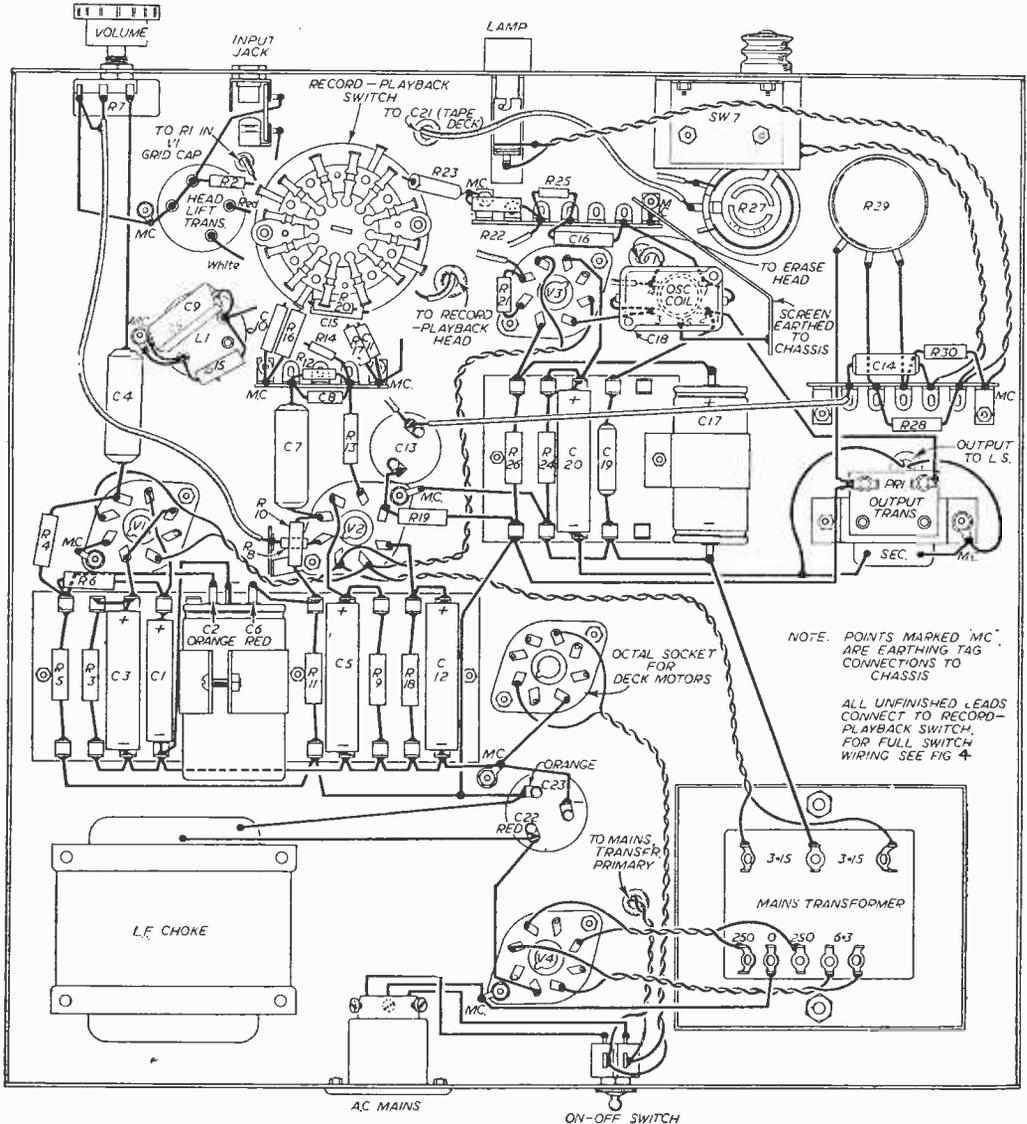


Fig. 5.—Wiring diagram of the amplifier. Note that R24 should be 220 $\Omega$  and not 220K as shown in the list of parts.

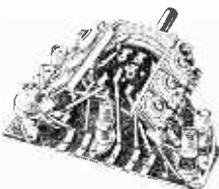

# radio products Ltd.

(Dept. P.54) 418 BRIGHTON ROAD, SOUTH CROYDON, SURREY. Telephone Croydon 5148/9

These really powerful units in compact form give quality and performance right out of proportion to their midget size and modest cost. Osmor "Q" Coilpacks have everything that only the highest degree of technical skill can ensure—extra selectivity, super sensitivity, adaptability. Size only 1 1/2 x 3 1/2 with variable iron-dust cores and Polystyrene formers. Built-in trimmers. Tropicalised. Proven Receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery Superhets and T.R.F. receivers. Ideal for the reliable construction of new sets, also for conversion of the 21 Receiver, TR1193, Type 13, Wartime Utility and others. Send to-day for particulars!

## SEPARATE COILS 4/-

A full range is available for all popular wavebands and purposes. Fully descriptive leaflets and connection data available. (Optional) new simple fixing 2d. extra. Just note these "5 Star" Features. \* Only 1in. high. \* Packed in damp-proof containers. \* Variable iron-dust cores. \* Fitted tabs for easy connection. \* Low loss Polystyrene formers. L or M.W. T.R.F. REACTION COIL TYPE QR 11-12 4/6.


A range of coils for P.M. Receivers shortly available.

A special design of coils now available for reflex circuits.


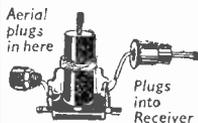
## OSMOR STATION SEPARATOR

The Separator may easily be tuned to eliminate any one station within the ranges stated and fitting takes only a few seconds. Sharp tuning is effected by adjusting the brass screw provided.



7/6

COMPLETE

### NO. METRES

- 1—141-250
- 2—218-233
- 3—267-341
- 4—319-405
- 5—305-492
- 6—455-587
- 7—1450-1550
- 8—110-550 k/c.

## CHASSIS CUTTER



Type	Hole Sizes	Prices
1	1/4. x 1 1/4in.	19/6
2	1/4. x 1 1/4in.	18/9
3	1/4. x 1 1/4in.	22/6
4	1 1/4. x 2in.	27/3

Illustr. list on request.

I.F.s. 465 k/c. Permeability tuned with flying leads. Standard size 1 1/4in. x 1 1/4in. x 3 1/4in. For use with OSMOR coilpacks and others, 14/6 pair. Midget I.F.s 465 k/c. 1 1/4in. x 1 1/4in. x 2 1/4in. 21/- pair. PRE-ALIGNED. 1/6 extra, both types.

**FREE!**

Send 5d. (stamps) for fully descriptive literature including "The really efficient 5-valve Superhet Circuit and practical Drawings," 6-valve ditto, 3-valve (plus rectifier) T.R.F. circuit, Battery portable Superhet circuit, Coil and Coilpack leaflets, Chassis Cutter leaflet, and full radio and component lists, and interesting miniature circuits, etc.

## DIALS—VARIOUS DIALS CALIBRATED TO COILS

Metal dials, overall size 5 1/2in. square. Cream background, 3-colour Type M1, L.M.S. waves, M2, L & M. waves, M3, M, and 2 S. waves. Price 3/6 each. Pointer 1/3; Drum, Drive, Spring and Coed. 3/2. Type A glass dial assembly, measuring 7in. x 7in. (9 1/2x9 1/2 overall). Mounts in any position. Choice of two 3-colour scales, 24/6. P. & P. 1/3.

OUR TECHNICAL DEPT. WILL BE PLEASSED TO ANSWER (BY LETTER ONLY) ANY ENQUIRY RELATING TO CIRCUITS WHICH OSMOR COILS OR COIL PACKS ARE USED OR ARE INTENDED TO BE USED.

WE ENDEAVOUR TO KEEP ABEAST OF THE TIMES BY BUILDING THE VARIOUS CIRCUITS PUBLISHED IN "WIRELESS WORLD," "PRACTICAL WIRELESS," "RADIO CONSTRUCTOR," ETC. WE KEEP STOCKS OF THE COMPONENTS SPECIFIED

### "PRACTICAL WIRELESS"

Coronet Four; Beginners' Superhet; Modern High Power Amplifier 2; Attache Case Portable; R1155 Converter; A.C. Band-Pass 3; Modern 1-Valver; 3-speed Autogram, modern reflex, etc.

### "WIRELESS WORLD"

"No Compromise" TRF Tuner. "Midget Mains Receiver." Sensitive 2-valve Receiver. Television Converter (special coils in cans available). Midget sensitive T.R.F., etc.

### "RADIO CONSTRUCTOR"

Converting the TR1193 receiver to a general purpose s/het receiver simple crystal diode set. Radio feeder units. Economy 8 W.P.P. Amplifier. Circuit and details available for adding push-pull to the 5/6 valve Osmor superhet.


A LIST OF FIXED CAPACITIES AS REQUIRED FOR SWITCH TUNING AVAILABLE ON APPLICATION

# "Q" COIL UNITS MAKE EASY SWITCHING

Wavebands may be added or changed in a few minutes. Switching arrangements can be increased as required. Multi-waveband Coilpacks may be easily made up. The Coil Unit consists of Aerial and Oscillator Coils and Trimmers wired and ready to connect to switch.

THE SIMPLEST AND MOST CONVENIENT METHOD OF SET BUILDING SO FAR DEvised FOR THE AMATEUR.

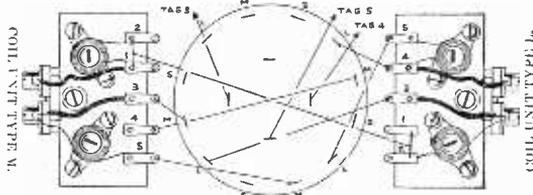15/- PER UNIT including 4 foolproof drawings



DESIGNERS ARE ASSURED OF FULL CO-OPERATION

PLEASE LET US KNOW YOUR REQUIREMENTS

NEWCOMERS TO RADIO. WE HAVE A NEW DEPARTMENT READY AND WILLING TO HELP SEND US YOUR PROBLEMS

## The COMPLETE HOME ENTERTAINER . . . The



### 'EDITOR'

**TWO-SPEED**  
Suitcase  
Tape Recorder

Shown without lid

**H.P. TERMS**  
20% deposit with  
balance spread  
over 12 months.

Easy to carry—Easy to look at. Operating height only just over 5 inches. The 'EDITOR' is the smallest mains-operated fully automatic two-speed portable tape recorder with 7in. spools on the market. Finest value and quality at only **45 Gns.** (C. & P. 15/-) Complete with Microphone & 1200' Tape

**SPECIFICATION** ★ Two speeds 3 $\frac{1}{2}$ in. and 7 $\frac{1}{2}$ in. per sec. ★ Twin track heads ★ Three high-grade specially designed motors ★ INDEPENDENT BASS AND TREBLE CONTROLS FOR RECORDING AND PLAYBACK ★ Overall negative Feedback ★ Amplifier may be used independently for very high quality record reproduction and public address ★ High fidelity Record head ★ Provision for external speaker ★ Speaker muting switch ★ 4 watts output—brilliant reproduction ★ Positive servo braking on all functions ★ Size only 16 $\frac{1}{2}$ in. x 12in. x 5in. (without lid) ★ Radio/Gram and microphone inputs ★ For 200-250 V. A.C. mains ★ Automatic Erasure ★ Eminently suitable for the new pre-recorded tapes.

**E. & G. MAIL ORDER SUPPLY CO.** *The Radio Centre*  
33, Tottenham Court Road, London, W.1. MUSEum 6667

### In full swing !!!

Those on the look-out for full value for their money are getting it at

### The Walk-around Shop

which we recently opened at

**52 TOTTENHAM COURT ROAD, LONDON, W.1**

(A few minutes from Lyons Corner House)

If you have not yet paid us a visit, come along as soon as possible and inspect the wide range of surplus lines displayed, including :

RADIO EQUIPMENT — RECEIVERS — TRANSMITTERS — COMPONENTS, ETC. — LABORATORY INSTRUMENTS — ELECTRICAL ACCESSORIES — AIRCRAFT SUNDRIES, ETC.

#### RECEIVER UNIT Ex 1143A

Suitable for conversion to 2 metres or F.M. Wrotham transmissions.

Valve line-up : (4) EF50 ; (1) EL32 ; (2) EF39 ; (1) EBC33 ; (1) EA50. Supplied with circuit diagrams.

**PRICE 9/-** *Past Paid.*  
(less valves)

It will pay you to pay us a visit.

**PROOPS**

BROS. LTD. LANgham 0141.  
52, Tottenham Court Road, W.1.

OPEN ALL DAY SATURDAY

Shop hours 9 a.m.-6 p.m.

## Smith's for Technical Books




Books on the theory and practice of electronics, new developments, circuit design, and other specialized subjects can be quickly supplied through your local Smith's shop or bookstall.

Your copies of PRACTICAL WIRELESS can be bound into attractive volumes; and all your stationery and printed matter supplied through our local branch.

## W. H. Smith & Son

for SPECIALIST BOOKS

Head Office: Strand House, London, W.C.2

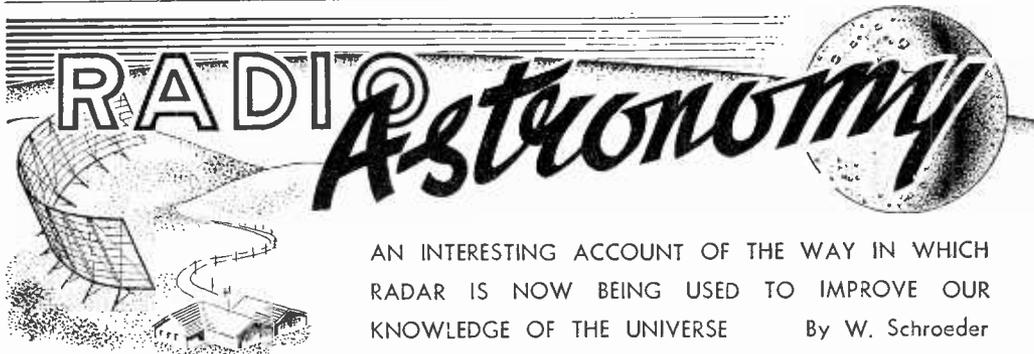

AN INTERESTING ACCOUNT OF THE WAY IN WHICH  
RADAR IS NOW BEING USED TO IMPROVE OUR  
KNOWLEDGE OF THE UNIVERSE By W. Schroeder

SINCE K. G. Jansky, an American scientist, first received a radiation from some source in outer space in December, 1931, radio-astronomy has become a recognised branch of science. The significance of his discovery was not realised at the time, and its development took place only after the last war.

Jansky was investigating atmospheric noise on a wavelength of 15 metres, when he discovered that the intensity of aerial noise did not vary according to the time of the day but with a period of 23 hours and 56 minutes—corresponding with the earth's rotation relative to the stars. The source of the noise was finally traced to the Milky Way, but Jansky failed to detect any emission from the sun.

So far, all our astronomical knowledge had come through the "window" in the earth's atmosphere which admits the visible light, corresponding to a range of wavelengths covering three-and-a-half octaves. It was now evident that there was another, much larger window, covering  $10\frac{1}{2}$  octaves, i.e., wavelengths from 1 centimetre up to 15 metres. Molecular absorption limits the window at the high-frequency end and, towards the longer wavelengths, the ionosphere bars the "view." This wide range is a clear advantage of radio-astronomy over classical astronomy, and there is also the fact that the weather puts no restriction at all on the use of our radio-telescopes.

When in February, 1942, British Army radar equipment, working on a wavelength of 4 to 6 metres, was suddenly and seriously interfered with by the occurrence of an extremely high noise, it was feared that the Germans might have discovered some new form of jamming. The source of interference, however, was traced to be the sun which, just then, showed an extremely large sunspot. The observations made at that time finally gave the impetus to the systematic investigations which began in 1946.

Early radio-telescopes consisted of an array of half-wave dipoles, but their power-gain, even when used with a reflector, rarely exceeded 100. Their resolving power also left much to be desired, but this depended on the nature of the received waves. With increasing wavelength the resolving power decreases and at 60 centimetres it is already about one million times smaller than that of quite a small optical telescope.

Considerable improvement, however, was achieved by using several aerials, widely separated and feeding them to a common input at the receiver. These "interferometers" have been constructed with baselines as long as six miles, and in Australia an inter-

ferometer for the investigation of solar radiations has been erected which consists of 32 aerial systems. The resolving power of this instrument is about one minute of arc.

Naturally, these aerial systems have to be rebuilt every time a change of wavelength is desired. A more versatile type is the parabolic mirror with a half-wave dipole at its focus. These can be easily constructed as the mirror need only consist of tinplate or wire-mesh because of the long wavelength, and deviations of up to  $\frac{1}{8}$  from the true form of the parabola have no ill-effects.

Such a telescope was erected at Jodrell Bank, in Cheshire, in 1947. Its diameter is 218ft., and the receiving dipole at the focus of the mirror is fitted on top of a 126ft. mast which can be tilted in order to displace the direction of the received beam. The mirror of the instrument consists of wire mesh, the separation of the wires being 8in. The leakage of this mirror is 37 per cent. at a wavelength of 2 metres. The fact that the departure of the surface of the mirror from the form of a true paraboloid is about 5in., limits the shortest wavelength receivable at 1 metre.

The rather arbitrary measurements of the instrument were a result of the slender means available to Professor A. C. B. Lovell when he built the mirror, and strangely enough, the height of the rim, which is 23ft. 4in., was actually determined by the height of their ladders.

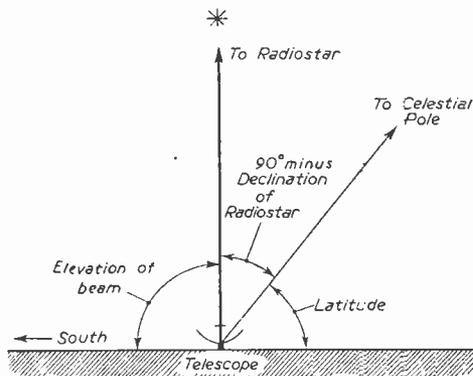


Fig. 1.—Setting up a radio-telescope: The declination of the area of the sky investigated depends on the elevation of the beam and on the latitude of the place of observation.

The results obtained with this telescope were so encouraging that the building of a large, completely adjustable radio-telescope was contemplated which is now actually under construction. Professor Lovell, of Manchester University, is mainly responsible for its design, and the cost of construction is shared between the Nuffield Foundation and the Department for Scientific and Industrial Research.

The mirror of this new radio-telescope will have a diameter of 250ft., and its focal length will be 62½ft. The huge bowl of copper-wire mesh, spaced at 1in. intervals, with its frame and supporting girder weighing in all about 600 tons, can be set to any elevation desired. It is supported by two towers, 185ft. high, which run on a circular railway track, enabling the instrument to be directed towards any part of the sky.

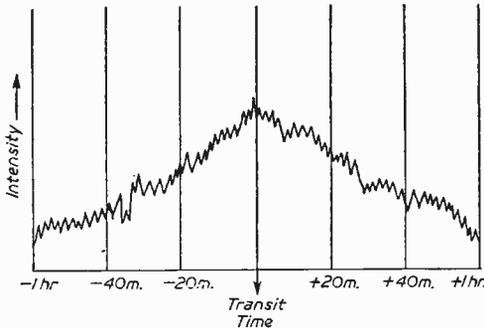


Fig. 2.—Typical recording of the transit of a radiostar, indicating "scintillation."

At a wavelength of 21 centimetres this aerial system will have a power-gain of 100,000, and the beam-width is as small as 12 minutes of arc.

Naturally, these huge instruments are employed to investigate the faintest sources of radio waves reaching us from outer space, but quite small instruments can yield surprising results with nearby sources of the Milky Way and the sun, especially at wavelengths under 1 metre. When receiving very short wavelengths, the dipole at the focus is usually replaced by a wave guide which conducts these microwaves with extremely low losses. The mirrors of these telescopes have diameters of 3 to 6ft., and quite good results have been obtained by amateur radio-astronomers with a 5ft. mirror of 1in. copper-wire mesh, with a dipole at the focus. The wavelengths received were from 15 to 60 centimetres.

The receivers employed in connection with these aerials are always conventional V.H.F. receivers, the only modification being the addition of a field strength recorder either in the anode circuit of an A.V.C. controlled valve, or of the detector valve if a super-regenerative receiver is used. In the latter case, the best circuit is a detector with separate quench oscillator and one R.F. stage, with a valve-voltmeter connected across the anode load resistor of the detector serving as indicator.

#### Aerials

Usually, the aerials—if not adjustable—are mounted to face south, similar to the meridian circles of the great observatories. As the earth, relative to the stars, makes one revolution in 23 hours and 56

minutes, the telescope sweeps out a complete circle in the sky during that period, the width of which depends on the beamwidth of the instrument. The transit of a source of radio waves is then recorded in a fashion similar to that of Fig. 2. It will be noticed that the curve is not a smooth one, showing a gradual increase in field strength up to the maximum at transit time, and afterwards a gradual decrease, but numerous kicks over and below the average position will be recorded. This "Scintillation" is just like the twinkling of visible stars whose light never is steady either, and the reason for this is in both cases the instability—electrical or optical—of the earth's atmosphere.

The discoveries to which the application of radio-telescopes has led are considerable already. Since Bolton and Stanley in Australia detected the first "radio star," an intense source of emission of very small diameter, in the constellation of Cygnus in 1948, over 100 of these point sources have been discovered. The most remarkable feature of these is that they usually cannot be identified with any visible object in the sky, but the use of the great 200in. telescope on Mount Palomar finally revealed very faint nebulae in an intense state of agitation as the probable sources of radio energy reaching us from a part of the constellation Cassiopeia. The radio star in Cygnus was discovered to be a collision of two galaxies of stars, far beyond our Milky Way system, at a distance of one hundred million light years. A third object has been identified to be the remains of a supernova—a star which exploded in A.D. 1054, an occurrence which was recorded by Chinese astronomers.

The scope of radio-astronomy was considerably extended when I. Ewen and M. Purcell, of the Harvard Observatory, discovered a line-emission, similar to the spectrum lines of visible light, on a wavelength of 21.2 centimetres (1,420 Mc/s) after this had been predicted by the Dutch astro-physicist van de Hulst in 1945. Very sharp tuning was necessary to distinguish this from the continuous spectrum of the radio emissions.

The discovery of this line-emission has been instrumental in the research into the structure of our own galactic system of the Milky Way beyond the point where optical astronomy began to fail, and already the actual distance of a radio star has been determined independently from any optical instruments.

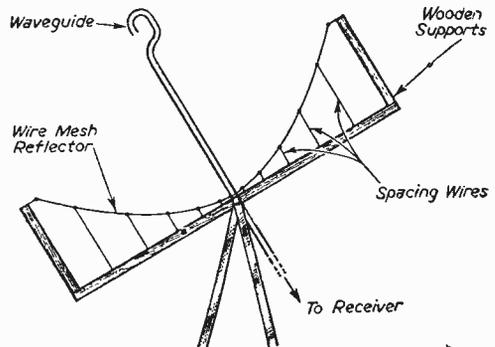


Fig. 3.—Cross-section through a parabolic reflector with waveguide for the reception of radiations in the microwave region.

**PLASTIC CABINET** as illustrated,  $1\frac{1}{2} \times 6\frac{1}{2} \times 5\frac{1}{2}$  in., in walnut or cream, **ALSO IN POLISHED WALNUT**, complete with R.F. chassis, 2 waveband scale, station names, new waveband, backplate, drum, pointer, spring, drive spindle, 3 knobs and back, 22/6. P. & P. 3/6.

As above with Superhet Chassis, 23/6. P. & P., 3/6.

As above complete with new 5in. speaker to fit and O.P. trans. 37/6. P. & P. 3/6 with Superhet Chassis. 39/6. P. & P. 3/6.



Used metal rectifier, 230 v. 50mA. 3/6; gang with trimmers, 6/6; M. & L. T.R.F. coils. 5/-; 3 Govt. valves, 3/6 and circuit, 4/6; heater trans. 6/-; volume control with switch, 3/6; wave-change switch, 2/-; 32 x 32 mfd., 4/-; bias condenser, 1/-; resistor kit, 2/-; condenser kit, 4/-.

**M. & L. Superhet Coils** with circuit, 6/6; iron cored 465 IFS, 7/6; min. kang. 5/6; volume control with switch, 4/-; wave-change switch, 2/6; heater trans., 7/6; 4 v.h. 1/6; 4 Ex Govt. valves, metal rectifier and Xtal diode with circuit, 14/6; 25 x 25 mfd., 1/-; 16 x 16 mfd., 3/3; condenser kit (17), 7/6; resistor kit (14), 3/6.

**Medium and Long Wave Crystal set**, in attractive plastic cabinet incorporating Germanium diode, 16/-.  
Headphones to match above, per pair 7/6.

**COMPLETELY BUILT SIGNAL GENERATOR**

Coverage 120 Kc/s-320 Kc/s., 300 Kc/s-900 Kc/s., 900 Kc/s-2.75 Mc/s., 2.75 Mc/s-8.5 Mc/s., 8.5 Mc/s-25 Mc/s., 17 Mc/s-50 Mc/s., 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in., size of scale 6 1/2 x 3 1/2 in., 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation 400 c.p.s. to a depth of 30%. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. £419/6, or 34/- deposit and 3 monthly payments of 25/-. Post and Packing 4/- extra.



**High impedance Plastic recording tape** by famous manufacturer. 1,200 feet complete on spool, 17/6. P. & P. 1/6. 600 feet 8/-, P. & P. 1/-.

Pri. 200-250 v., secondary 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt at 2 amps. Drop thro' 200-0-200, 200 mA., 6 v. 5 amps., 5 v. 3 amps., 27/6.

Terms of business: Cash with order. Despatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

**D. COHEN, 23, HIGH STREET, ACTON, W.3.** (Opposite Grandda Cinema)

Hours of Business: Saturdays 9-5 p.m. Wednesdays 9-1 p.m. Other days 9-1.30 p.m.

**Heater Transformer.** Pri. 230-250 v. 6 v. 13 amp., 6/-; 2 v. 23 amp., 5/-.

**R.I. MAINS TRANSFORMERS**, chassis mounting, feet and voltage panel. Pri. mains 200/250.

350-0-350 75 mA. 6.3 v. 3 a. tap 4 v. 6.3 v. 1 a. 13/6.

350-0-350 70 mA. 4 v. 5 a., 4 v. 2.5 a., C.T. 18/6. P. & P. on above transformers 2/-.

500-0-500 120 mA. 4 v. C.T. 4 a. 4 v. C.T. 4 v. C.T. 2.5 a., 27/6.

500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a. 4 v. C.T. 4 a., 39/6.

P. & P. on the above transformers 3/-.

32 mfd., 350 wkg. .... 2/-

16 x 24 350 wkg. .... 4/-

4 mfd. 200 wkg. .... 1/3

40 mfd., 450 wkg. .... 3/6

16 x 24 500 wkg. .... 4/6

16 x 16 mfd., 500 wkg. .... 5/9

8 x 16 mfd., 450 wkg. .... 3/9

32 x 32 mfd., 350 wkg. .... 4/-

25 wkg. .... 6/6

25 mfd., 25 wkg. .... 11/4

250 mfd., 12 v. wkg. .... 1/6

16 mfd., 500 wkg. wire ends .... 3/3

8 mfd., 500 v. wkg., wire ends .... 2/6

8 mfd., 350 v. wkg., tag ends .... 1/6

50 mfd., 25 v. wkg., wire ends .... 1/9

100 mfd., 350 wkg. .... 4/-

100 + 200 mfd., 350 wkg. .... 9/6

16 + 16 mfd., 350 wkg. .... 3/3

Ex Govt. 8 mfd., 500 v. wkg., size 3 1/2 x 1 1/2 for .... 2/6

60 + 100 mfd., 280 v. wkg. .... 7/-

16 + 32 mfd., 350 wkg. .... 6/9

50 mfd., 180 wkg. .... 1/6

50 mfd., 220 wkg. .... 1/6

8 mfd., 150 wkg. .... 1/6

60 + 100 mfd., 280 wkg. .... 8/6

50 mfd., 12 wkg. .... 11/4

32 + 32 mfd., min. 275 wkg. .... 4/-

50 mfd., 50 wkg. 8 mfd., wkg. wire ends .... 1/9

Miniature wire ends moulded 100 pt., 500 pf., and .001 ea. .... 7/4

280-0-280 80 mA. 4 v. 4 a., 4 v. 2 a. .... 14/6

250 v. 350 mA. 6.3 v. 4 a. twice 2 v. 2 a. .... 19/6

Auto-trans. input 230/240 HT 500 v. 250 mA. 6 v. 4 a. twice 2 v. 2 a. .... 19/6

250-0-250 60 mA. 6.3 v. 1.3 a., 0-5-6.3 v. 1.5 a. .... 10/6

**PATTERN GENERATOR** 40-70 Mc/s. direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits, and vision channel band width. Silver plated coils, black crackle finished case, 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 200-250 volts. This instrument will align any TV receiver. Cash price, £3.18-0 or £1.9-0 deposit and 3 monthly payments of £1. Post and packing 4/- extra.

**TV. CONVERTER** for the new commercial stations, complete with 2 valves. Frequency—can be set to any channel within the 199-196 Mc/s. band. I.F.—will work into any existing TV receiver, designed to work between 42-68 Mc/s. Sensitivity 10 Mu.v. with any normal TV set. Input—arranged for 300 ohm feeder. 60 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF90 as local oscillator, ECC81 as R.F. amplifier and mixer. The gain of the first stage, required grid R.F. amplifier, 10 db. Requires power supply of 200 v. D.C. at 25 mA., 6.3 v. A.C. at 0.8 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0. Post and packing 2/6.

**Volume Controls.** Long spindle less switch, 50 K., 500 K., 1 meg. 2/6 each. P. & P. 3d. each.

**CR100 Coil packs** 10-2,000 metres, in soiled condition complete with 4-gang tuning condenser. P. & P. 3/6, 19/6.

**CR100 coil packs** in first-class condition less oscillator section, complete with 4-gang tuning condenser. P. & P. 3/6, 19/6.

**CR100 465 Kc IFS**, types 3, 4 & 5 & BE9, new condition, 7/6 each. 465 Kc Xtal for CR100, 12/6.

**4-gang tuning condenser** for CR100, 9/6.

**Volume Controls.** Long spindle and switch, 1, 1 and 2 meg., 4/- each; 10 K. and 50 K., 3/6 each; 4 and 1 meg., long spindle, double pole switch, miniature, 5/-.

**Standard Wave-change Switches.** 4-pole 3-way, 1/9; 5-pole 3-way, 1/9. Miniature 3-pole 4-way, 4-pole 3-way, 2/6. 2-pole 1-way twin wafer, 5/-, 1-pole 12-way single wafer, 5/-.

**Valveholders.** Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded B7G, 7d. Octal amphenol, 7d. Octal pax., 4d. B5A, Mazda Amphen., 7d. Mazda pax., 4d. B5A, Mazda amphenol, 7d. BTG with screening can, 1/6. Duodecal paxolin, 9d.

**Twin-gang .0005 Tuning Condensers,** 5/-. With trimmers, 6/6.

**Midget .00037 dust cover** and trimmers, 8/6.

**RADIOGRAM CHASSIS**—5 valve A.C./D.C. 3-way band superhet, 195-255 volts 16-49, 200/550 and 1,000-2,000 cycles, fly wheel tuning frequency, 470 Kc/s. Iron-cored coils and IFS. Size of chassis, 13 x 6 1/2 x 2 1/2. Complete with valves and bin. P.W. speaker, p. & p. 5/-, £8.17.6.

**Constructor's parcel**, comprising chassis 12 1/2 x 8 x 2 1/2 in., cad. plated, 18 gauge, v.h. IF and trans. cut-outs, back-plate, 2 supporting brackets, 3-waveband scale, new waveband stations names. Size of scale 1 1/2 x 4 1/2 in. drive sp. drum, 2 pulleys, pointer, 2 bulb holders, 5 pax I.F. v.h. 4 knobs and pair of 465 IFS, twin gang, 16 x 16 mfd., 350 wkg., mains trans. 250-0-250 60 mA., 6.3 v. 2 amp., 5 v. 2 amp. grid 6 1/2 in. M.E. speaker wth O.P. trans. P. & P. 3/6, 39/6.

R. & A. M.E. 6 1/2 in. speaker with O.P. trans., field coil 175 ohms, 9/6. P. & P. 2/6.

R. & A. 6 1/2 in. M.E. speaker with O.P. trans., field 440 ohms, 10/6. P. & P. 2/6.

**Battery Charger.** Input 220/250 v., output 6 & 12 v. 1 amp. Black crackle finished case size 10 x 6 x 4 in. P. & P. 3/-, 21/-.

**Potato & Vegetable Peeler**, by famous manufacturer, capacity 4 lbs., complete with water pump. All aluminium construction, white stove-ename finish. Originally intended for adaptation on an electric food-mixer, can be easily converted for hand operation. 39/6. P. & P. 3/-.

**Primary.** 200-250 v. P. & P. 2/-, 300-0-300 100 mA., 6 v. 3 amp., 5 v. 2 amp., 22/6.

**Drop thro'** 250-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

**Drop thro'** 250-0-250 v. 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

**280-0-280, drop through,** 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

**250-0-250 80 mA., 6 v. 4 amp., 14/6.**

**Drop thro'** 270-0-270, 80 mA., 6 v. 3 amp., 4 v. 1.5 amp., 13/6.

**Drop thro'** 270-0-270 60 mA., 6 v. 3 amp., 11/6.

**Auto Trans.** Input 200/240. H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 1 1/2 amp., 5 v. 3 amp. 25/-, P. & P. 3/-.

**Pri.** 200/250. Secondary 9 v. 3.5 amp., 6.3 v. 3 amp., 12/6.

**Pri.** 230 v. Sec. 500-0-500 and 500-0-500 250 mA. both windings, 4 v. 3 amp., 4 v. 3 amp., 39/6. P. & P. 5/-.

**Mains Transformer.** fully impregnated, input 220, 220, 230 and 240. Sec. 600-0-600 275 mA., and 200 v. at 30 mA., complete with separate heater transformer. Input 210, 220, 230, 240. Sec. 6.3 v. 2 amp., three times, 0-1, 6.3 v. at 3 amp. and 5 v. 3 amp., 45/-, P. & P. 5/-.

**Mains Transformer.** fully impregnated, input 210, 220, 230, 240. Sec. 350-0-350, 100 mA., with separate heater transformer. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp. 30/-, P. & P. 5/-.

# Prices slashed at Clydesdale

## RECEIVER UNIT R3801

Ref. : 10DB/6037  
 With valves : 2/VR136 (EF54), VR137 (EC52), 5/VR65 (SP61), 4/VR92 (EA50), VR91 (EF50), 6/VR3, VU39A (R3), etc. I.F. 13 mcs. Dim. : 18 x 9 x 8 in. Wgt. 38 lbs.  
 Ask for **39/6** Carriage Paid  
 P/H493

## POWER UNIT TYPE 266

In Transit Case. Input 80 v. 1.5 K/cps. A.C. Output H.T. 120 v. D.C. bias 3 and 9 v. L.T. 2 v. Smoothed and stabilised. Complete with 504G valves. VU10 stabiliser, 12 v. 1 a. Metal Rectifiers, etc., in attractive metal case with handles. Dim. : 11in. x 9 1/2in. x 7 1/2in.  
 Ask for **22/6** Carriage Paid  
 P/E870

## AERIAL ROD

15in. lengths, copper plates, steel tube, ferruled to interlock an aerial of desired length. 3/16in. dia. Ask for P/H709.  
 1/4in. dia. Ask for P/H710.

## EITHER 4/6

dz. lengths, extra Post 6d.

## SPIDER-WEB MESH AERIAL

Spider-Web mesh aerial in original moisture-proof carton, with assembly instructions.  
 Ask for **4/11** Post 9d.  
 P/E175

## ION TRAP MAGNET ASSEMBLY

Mfg. Surplus  
 Type IT/6 by Elac for 35 mm. tube neck.  
 Ask for **2/6** Post 3d.  
 P/H919

## PAXOLIN WAFER ROTARY WAVECHANGE SWITCH

3 Wafers each, 2 pole, 5-way. Dim. : 3 1/2in. x 2 1/2in. x 2in. Spindle projects 1 1/2in. Single hole mounting.  
 Ask for **2/6** Post 6d.  
 P/E975

Or 3 for 7/6. Post paid.

## PLOTTER FIELD MK.IV

Ref. : O.S.739A  
 A precision made Protractor Unit, first class condition. With 2 scales 0-180 deg. moving crosshairs, scaled 1/25 each, 12 1/2in. long. Straight edge base scaled 0-3500 lengths 25in., fully extended. In soiled leather case, 16in. x 5 1/2in. x 2in.  
 Ask for **9/11** Each Post Paid  
 P/H894

## ELECTROLYTIC CONDENSERS

Metal Can Clip Mtg. Types. Cap. 24-24 mfd. 450 v. D.C. wkg. Dia. 1 1/2in. x 2in.  
 Ask for **3/-** Each Post 3d.  
 P/H971

## MICROPHONE

Ref. 10A/14381  
 (Flying Helmet type.)  
 Electro Magnetic 50 ohms with switch, lead and 2-way socket.  
 Ask for **3/11** Each Post 6d.  
 P/E15

## CARBON HAND-SET MICROPHONE

No. 4A.  
 Ask for **7/6** Each Post Paid  
 P/E13

## HEADPHONES CHIR-2

Pair high impedance 4,000 ohms. With wire headband and leads.  
 Ask for **10/9** Each Post Paid  
 P/H785

## HEADPHONES DLR-1

Pair low impedance 50 ohms, with headband, lead and jackplug.  
 Ask for **7/8** Each Post Paid  
 P/H390

## CORD DRIVE SPINDLE

Ratio 6-1  
 Reverse Vernier Drive, i.e., cord runs outside chassis.  
 Ask for **1/-** Each Post 3d.  
 P/H976

## 5-WAY GROUPBOARDS

Or 3 for 3/-. Post Paid.  
 Paxolin panel 2 1/2in. x 2 1/2in., with tags for mounting 5 condensers or resistors, two-hole fixing.  
 Ask for **6d.** Each Post 3d.  
 P/H981

## CO-AXIAL CABLE

Any length supplies 52 ohms, 12 mm. dia. Price 5d. per yard. Minimum 12 yards at 5/- post paid. Ask for P/E867.

## THROAT MICROPHONE

Ref. : ZA.13935.  
 Pair Electro Magnetic lozenge-shaped pieces (7.5 ohms) with strap, lead and jackplug.  
 Ask for **3/11** Each extra  
 P/E14

## THROAT MICROPHONE

Ref. : ZA.13734  
 Pair Electro Magnetic lozenge-shaped pieces (7.5 ohms) with strap, lead and jackplug.  
 Ask for **4/11** Each extra  
 P/H955

## THROAT MICROPHONE

(U.S.A. made.)  
 Pair Carbon buttons on mounted rubber with strap, lead and miniature 2-pin plug.  
 Ask for **3/11** Each extra  
 P/H57

## MORSE PRACTICE BOARD ONLY


Comprises Key, buzzer and 'phone terminals on board 6 1/2in. x 6 1/2in. x 1 1/2in. with battery clamps.  
 Ask for **5/6** Each extra  
 P/E1X

## PLEASE NOTE.—Carriage and Postal Charges refer to the U.K. only. Overseas freight, etc., extra.

Order direct from —  
**CLYDESDALE SUPPLY CO. LTD.**  
 2, BRIDGE STREET, GLASGOW, C.5  
 Phone: South 2706/9

**W. B. SUPPLIES** 100, Oldham Street, MANCHESTER, 4.  
**TERMS.**—Cash with order. Orders under 20/-, add 6d.; over 20/-, add 1/- postage. Orders dispatched same day.  
**SELECTOR UNIT 10K/13045**, rotary action complete with relay, 3/6.  
**POTENTIOMETERS.**—5 watt type, 15K, 20K, 25K, 50K, wire wound, 1/3 each.  
**SPIRAL COIL AERIALS.**—EX W.D. Pull out any length, complete with insulators, 2/-.  
**CRYSTAL SET KITS.**—Complete set of components and circuit to build simple set, 8/-.  
**H.T. BATTERY.**—Midget 60 volt+11 volt, 2/- ea. (tested).  
**TUBULAR CONDENSERS.**—Wire ends, 1,500 volt test, guaranteed non-leak. .001, .005, .05, .02, .01, 1 mfd. All at 1/- each.  
**VALVE EQUIVALENTS MANUAL.**—Latest publication, giving equivalents for Govt. Surplus and commercial valves, very useful, 5/-.  
**IVORY CONTROL KNOBS.**—1 1/2in. diam., engraved "Tuning," "Bass," "Treble," "Vol-On-Off," "Radio Gram," "Wavechange," 1/6 each.  
**TRANSFORMERS.**—Input 11.5 volts. Output 4.3 v, 2.5 a, 4 v, 2.5 a, 4/6.  
**RADIO INTERFERENCE SUPPRESSORS.**—Complete with instructions, 5/-.  
**CAR AERIALS.**—5ft., stainless, 12/6 with insulators.  
**EXPANDED METAL SPEAKER FRET (Gold),** 12in. x 12in., 4/6; 18in. x 12in., 6/9.  
**H.F. CHOKES, 6d.** Rectifiers, 250 v., 60 mcs, 5/-; Meter Rectifiers, 1 M/A. Half Wave, 3/6. Variable Condensers, air spaced 50 pf, 1/-; 115 pf, 2/6; 500 pf, 5/-. Speaker Transformers, 3/6. Osborn Frame Aerials, Medium Wave, 2/6.  
**TYANA SOLDERING IRONS.**—Light-weight, with fine bit for radio use, 14/11.  
**YAXLEY SWITCHES.**—2-pole, 6-way (2 Bank), 2/9. Toggle Switches, 1/-.  
**COIL FORMERS.**—1in. with feet, 8/6 dozen, complete with cores. Brass Cores, 1in., 6d. each.  
**SOLDERING FLUX.**—Monster size tins, 1/3.  
**NEUVISOL** Switch Cleaner, 3/- Tin.

## RADIO KIT 19/6

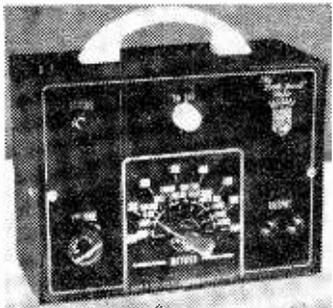

Build this high quality portable radio in 45 mins. Exceptionally sensitive, twin-triode circuit, using unique assembly system, can be built by anyone. Size only 6 1/2in. x 5in. x 3in. in handsome black-crackle steel case with beautiful black and gold dial (stations printed!). Covers all medium and long-waves. Uses one only self-contained dry battery, cost less than 1d. for 5 hrs. 1. Many unsolicited testimonials.  
 Mr. Norton, of Oxford, writes: "Yesterday evening on the medium waveband, I counted 32 separate stations: I am very pleased with the set, which is well worth the money." Mr. Fraiser, of Ipswich, writes: "Its performance is almost unbelievable, it gives me stations I've never been able to get on my large radio."  
**Send To-day Cheque/CWO/COD, 22/- (includes 2/6, post/packing) for Case, Dial, Handle, Plans, Parts Lists, etc. (Cost of Parts to Complete Radio only 30/-). Sent by return. (Overseas orders welcomed.)**  
**BRIGHTON RADIO CO. (Dept. PW7),**  
 69, Preston Street, Brighton, 1.

## VALVES

**SAME DAY SERVICE**  
**All Guaranteed New and Boxed**  
 1.4v. miniatures, 1R5, 1S4, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, 7J3; any 4 for 27/6. 6AL5, 6AM6, 6F12, 6D3, D77, EB91, EF91, Z77, 6/8; any 6 for 50/-.  
 1A7GT 6K8C 8/8 25L6GT EL41 9/6  
 11/6 6K25T 9/6 EL91 7/9  
 1C5GT 7/9 6K25 11/- 25Z4G 9/- EM34 11/-  
 1H5GT 6LD20 9/6 25Z6G 8/6 EY51 12/-  
 11/6 6P25 13/6 35L6GT EZ40 8/6  
 1N5GT 6P28 17/- EZ41 9/-  
 11/6 6Q7GT 35Z4GT 8/6 FW4/50 8/6  
 1R5 7/3 9/- 8/6 14/6  
 1S4 7/3 6SN7GT 35Z5GT 8/6 GZ32 14/6  
 155 7/3 8/6 KT63 7/6  
 1T4 7/3 6U4GT 50L6GT MU14 8/6  
 304 7/3 6V6 17/6 6P45 15/-  
 35GT 6V6 7/6 6P11 10/-  
 10/6 6V6GT 7/6 A231 10/- PL82 9/6  
 3S4 7/3 6X4 7/6 CL33 11/6 PL83 12/6  
 3V4 7/3 6X5GT 6/8 D77 6/9 PY80 9/6  
 5Y3GT 8/8 7C7 7/6 DAC32 10/-  
 5Z4G 8/8 7C5 7/6 7AC32 11/6  
 6A7 10/6 7C7 7/6 DF33 11/6 PZ30 17/-  
 6AL5 6/9 7H7 7/6 DH77 8/6 R12 15/-  
 6AM5 7/9 7S7 7/6 DK32 11/6 T41 13/-  
 6AM6 8/9 7Y4 8/6 DK32 7/3 U22 7/6  
 6AT6 7/9 10C1 12/6 D133 11/6 U24 17/6  
 6BA6 6/8 10F1 10/- DL35 7/9 U25 12/-  
 6BD6 6/6 10LD11 EB91 6/9 U50 7/9  
 6BH6 6/6 10/- EBC33 7/6 U78 8/6  
 6B36 6/8 10P13 10/- EBC41 10/- U404 9/6  
 6BR3 7/9 10F14 11/6 EBF90 8/6 U401 14/6  
 6BW7 9/6 12AH8 10/- 10/6 UBC41 9/-  
 6CH5 8/6 12AT7 9/- EBC81 9/- UBF60 10/6  
 6C4 7/9 12AU6 7/6 ECH42 10/6  
 6C3 8/6 12AU7 10/- UCH42 10/6  
 6F1 10/- 10/6 ECL90 9/- UF41 9/6  
 6F6G 7/6 12K7GT 8/6 EF37A 17/- UF42 13/6  
 6F12 6/9 9/6 6/6 UL1 9/6  
 6F13 11/6 12K9GT EF39 6/6 UL1 9/6  
 6F15 10/8 10/8 EF41 9/- UO3 16/-  
 6F6 8/6 12Q7GT EF50 7/6 UX41 9/6  
 6J7GT 7/6 9/- EF80 10/- WT 5/6  
 6K7G 6/- 20D1 9/9 EF91 6/9 X78 13/6  
 6K7GT 6/- 20F2 9/6 EF92 5/6 Z77 6/9  
 Postage 4d. per valve extra. STA. 4587.  
**READERS RADIO** 24, Colberg Place, Stamford Hill, London, N.15.

# A Versatile High Gain Amplifier

SOME while ago the writer, whilst answering a problem put to him by a student on the subject of negative feedback, wondered if it were possible to use positive feedback to increase the gain of an audio amplifier. Certainly, if positive were substituted in the formulae greater gains could be calculated. When the formulae are used for negative feedback, no case can be made where the amount taken out of the circuit is less than the amount put in, i.e., the gain cannot be reduced past unity. On the other hand, with positive feedback, if the fraction fed back is multiplied by the stage gain, and the result is higher than unity, the amplifier will be of no use as oscillation will occur. The formula for the gain

joining the anode of one to the grid of the other by a condenser, such a circuit is used in resistance-capacity oscillators. A modification of this method has been used. Each valve, or should we say section, has its own cathode resistor and the two cathodes are joined by a suitable resistor. The calculations were made, and the resulting value of resistor for a very high gain tried, but the circuit was very unstable, so one of a lower feedback value was used. It is as

*The details of the use of positive feedback in audio amplifiers to get a greatly increased gain from valves. A practical circuit is included.*

well to note that the higher the resistance the lower the feedback value. In the end it was found that with a 6SN7GT, with 2,000 ohms for each of the cathode circuits, and an anode load of 62,000, a coupling resistor of 20,000 ohms gave very good results. In the layout of the circuit great care should be exercised to see that no extra stray feedback is introduced—or it will oscillate. The layout employed as can be seen from the photograph is of the straight line type, i.e., everything is in a straight line, power transformer, smoothing and the amplifier. The mains transformer used is an Elstone TV pre-amp type as it will give ample power for the job. As the anode current is small resistance capacity smoothing is used and this is surprisingly efficient. The smoothing and reservoir condensers are in one unit, the Dubilier double unit can-type, the 161650, being used, joined with a 10,000-ohm resistor. The complete circuit is shown in Fig. 1. The layout of the base of the 6SN7GT is shown in Fig. 2, and the reader can do no better than follow it as close as possible. All the other wiring should, where possible, be twisted so as to keep down both the hum and the unwanted feedback.

The case and front panel were knocked out in the writer's own press-shop, and the front panel and chassis were aluminium, whilst the case was made out of sheet steel.

## Uses

There are many uses to which the finished unit can be put. As the sensitivity is so very high it can be used as a baby minder; the writer amused himself by joining it up to the house loudspeaker wiring by a multi-ratio transformer of the ratio of 90:1. With


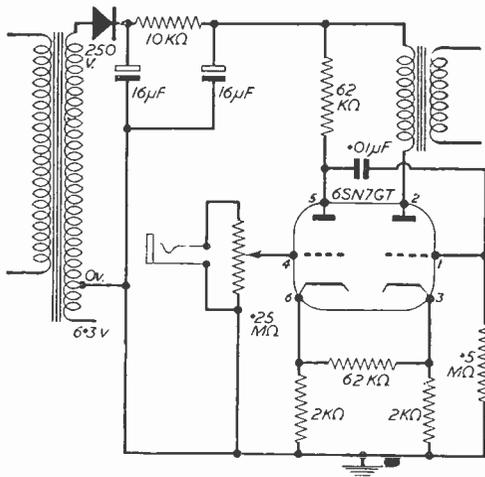


Fig. 1.—Basic theoretical circuit.

of an amplifier with feedback is  $\frac{\mu}{1-\alpha\beta}$  where  $\mu$  is the stage gain without feedback,  $\beta$  the gain to the particular point in the circuit from where the feedback is taken, and  $\alpha$  the fraction of the output feedback. In most cases  $\mu$  and  $\beta$  are equal, but in the case of taking feedback from the cathode circuit it will be seen that the gain across the cathode resistor will be different from the gain across the anode load resistor.
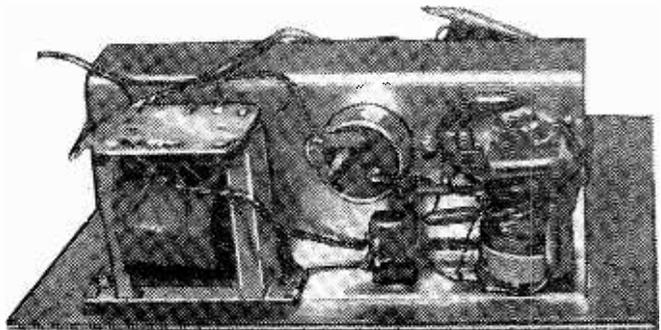
## The Circuit

Looking around the stock of valves in the laboratory, the old friend the 6SN7GT was chosen, as one-half is capable of driving a loudspeaker at a power of about  $\frac{1}{2}$  watt, and this is sufficient for a very wide range of uses. The simplest type of positive feedback with a double valve is to join the two cathodes together and use a common resistor for the cathode circuit, whilst



View of the underside of the chassis.

this, it was possible—with the wireless switched off, to hear every sound in the rooms fitted with loudspeakers. Normal conversation came over very loudly and the length of wire used for input to the amplifier made no difference, providing that it was earthed.

#### As a Signal Tracer

Another use is as a signal tracer. The circuit of a simple probe unit is shown in Fig. 2, and the polarity of the crystal is of no consequence, but the condenser should be of ample working voltage.

#### With a Crystal Set

One final use, of course, is for running a loud-speaker off a crystal set. For the most part components from the junk box can be used, but the resistors should be of the 10 per cent. tolerance.

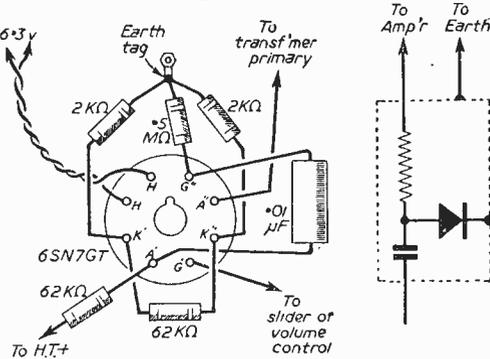


Fig. 2.—Wiring layout and suitable probe unit.

## News from the Clubs

### SOUTHEND AND DISTRICT RADIO SOCIETY

Hon. Sec. : J. H. Barrance, M.B.E. (G3BUJ) 49, Swanage Road, Southend-on-Sea, Essex.

THE opening meeting, after the summer break, was held at the EKCO Canteen by kind permission of the Directors of Messrs. E. K. Cole, Ltd., when Mr. C. G. Collop (G3AXN), a member of the Society, recently returned to U.K. on the Survey ship *John Biscoe* from an Antarctic Expedition, gave a unique account of the doings of these stalwart explorers in that part of the world where the temperature often reaches 40 below zero.

The subject of Mr. Collop's talk was "Radio in the Antarctic" and he illustrated it with about 100 snaps which portrayed the extreme difficulties of radio; where only high-frequency communication was possible and where the whole aerial system was thickly coated with ice. He also acquainted us with that ice-bound part of the world, which was once tropical, and where even now live volcanos still pour out molten lava, which melts the ice in the mountain crevasses into hot lakes.

### ROMFORD AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : N. Miller, 18, Mascalls Gardens, Brentwood, Essex.

THE Society's winter programme includes film shows, lectures, discussions "on the air," evenings with G4KF and the monthly "junk sales."

The Society meets every Tuesday evening at 8.15 p.m. at R.A.F.A. House, 18, Carlton Road, Romford, and all visitors and new members will be warmly welcomed.

Further information can be obtained from the Hon. Secretary.

### BRADFORD AMATEUR RADIO SOCIETY

Hon. Sec. : F. J. Davies, 39, Pullan Avenue, Eccleshill, Bradford, 2.

THE November meetings are as follows: November 9th, Display of Members Gear. On November 23rd, there will be a lecture on "The Human Ear" by an ear specialist. Both meetings are at Cambridge House and will commence at 7.30. Copies of the syllabus may be obtained from the Secretary.

### BRIGHTON AND DISTRICT RADIO CLUB (G3EVE)

Hon. Sec. : T. J. Huggett, 15, Waverley Crescent, Brighton, Sussex.

THE club meets every Tuesday evening at 7.30 p.m. at the "Eagle Inn," Gloucester Road, Brighton. The transmitter is on the air every month on top band and 80 metres, and many interesting Q.S.O.s have been made on both phone and C.W. Phone is used whenever possible to add interest to those who do not know the code. Young members are especially welcome, and demonstrations and talks on simple equipment for the young S.W.L. are being given during the coming winter months. Morse code classes are also held. A new 100-watt transmitter is also under construction for club use.

### CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec. : C. H. Bullivant, G3DIC, 25, St. Fillans Road, Catford, London, S.E.6.

THE Annual General Meeting of the Society was recently held, and the following were re-elected for a further term of office:

Chairman : J. Lambert, G3FNZ; Hon. Treasurer : N.

Moore; Hon. Secretary : C. Bullivant, G3DIC; Committee Members : E. Smith, D. Veasey.

The Club Championship cup for 1953/54 has been won by N. Moore.

Programme for November: 12th, Constructional Evening; 19th, "Metropolitan Police Radio System" by W. H. Andrews. G2YG; 26th, Constructional Evening.

Meetings are held at the clubrooms 225, New Cross Road, London, S.E.14, every Friday at 7.30 p.m. Details of membership can be obtained upon application to the Secretary.

### NEWARK AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : J. R. Clayton, 160, Wolsey Road, Newark, Notts.

A FILM show organised by Messrs. A. Hall and J. Clayton will be held at the "Northern Hotel," on Sunday, November 7th at 7 p.m., at which several interesting technical films will be shown. The mid-monthly meeting at "Northgate House" will be at 7 p.m., on Thursday November 18th, when there will be a demonstration of a commercial trans-receiver.

All interested are invited to attend.

### TORBAY AMATEUR RADIO SOCIETY

Hon. Sec. : L. H. Webber, G3GDW, 43, Lime Tree Walk, Newton Abbot.

AT a recent meeting G3AVF gave a very interesting talk on "Transistors," and brought along his TTX for demonstration. In conjunction with this talk, G3GDW brought along a portable receiver, so that the transistor could be heard working.

At the next meeting, G3GDW will talk on the results of the Low Power Field Day, in which he took part.

A proposal has been made to hold a Dinner Party—at a date near Christmas—for members and their ladies. At the next meeting this will be discussed, and the date, time and place will be fixed.

Meetings are held on the third Saturday each month, at 7.30 p.m., at the YMCA, Torquay. Visitors are always welcome.

### LIVERPOOL AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec. : A. D. H. Looney, 81, Alstonfield Road, Knotty Ash, Liverpool.

DESPITE the summer recess, a fair level of activity can be recorded. A D.F. contest has been held but no one found the transmitter in the required time.

A very interesting talk was recently given by Mr. Fitz-Gibbon of the M.O.S. Radio Inspectorate, and the club received a visit from W60DR, over here for a short while. A determined effort is to be made to win the Warrington Inter-club Fone Contest on Top Band and arrangements have been made to have a lecture on "Portable Equipment for RAEN" by G3FNI, and a talk on "Japanese Morse" by G3CSG.

### READING RADIO SOCIETY


Hon. Sec. : L. A. Hasford (G2BHS), 30, Boston Avenue, Reading, Berks.

AT the annual Hamfest which is to be held on Sunday, November 21st, the Society has been fortunate in obtaining the services of F. J. H. Charman, Esq., B.E.M. (G6CJ), who will give a talk and demonstration on aeriols.
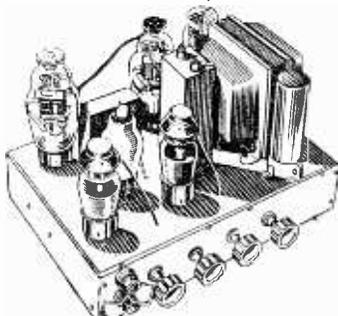
### R.S.C. 25 WATT QUALITY AMPLIFIER 9 Gns.

We firmly believe our All "Push-Pull" Quality Amplifier to be by far the best value in amplifiers offered to-day. The volume of its high fidelity reproduction is completely controllable, from the sound of a quiet intimate conversation to the full, glorious volume of a great orchestra. Its sensitivity is so high that in arc and fair signal strength it can be operated straight from a crystal receiver. Entirely suitable for standard or long playing records in small homes or in large auditoriums. For electronic organ or guitar or for garden parties or dance bands. The kit is complete to the last detail, and includes easy to follow point-to-point wiring diagrams.

Outputs for 3 or 15 ohm speakers. Twin volume controls with twin input sockets allow **SIMULTANEOUS INPUTS** for BOTH MICROPHONE and GRAM, or T.A.P.E. and R.A.C. or T.A.P.E. BASS and TREBLE CONTROLS, giving both **LIFT** and **CUT**. **FOUR NEGATIVE FEEDBACK**



LOOPS with 15 db in the main loop from output transformer to voltage amplifier. Frequency response  $\pm 3$  db. 50-20,000 c.p.s. HUM and DISTORTION LESS THAN 0.5

per cent. measured at 10 watts, comparing favourably with most highest priced amplifiers. Six B.V.A. valves, Marconi/Osram KT series output valves, A.C. only, 200-230-250 v. 50 c/s. input, 42 $\frac{1}{2}$  v. H.T. LINE. Paper reservoir condenser. Compact chassis. Matched components. Size 14-10-9in. Available in kit form at the amazingly low price of 9 gns. Plus carriage 7/6. Or ready for use 50/- extra.

### R.S.C. 10 WATT "PUSH-PULL" HIGH-FIDELITY AMPLIFIER A3

Complete with integral Pre-amp. Tone control stage (as All amplifier), using negative feedback giving humproof individual bass and treble lift and cut tone control. Six Negative Feedback Loops. Completely negligible hum and distortion. Frequency response  $\pm 3$  db. 30-20,000 c.p.s. Two independently controlled inputs. Six B.V.A. valves. A.C. mains 200-230-250 v. Input only. Outputs for 3 or 15 ohm speakers. Kit. Components complete in every detail. £7.19.6. plus 5/- carriage, or ready for use. 45/- extra.

**H.M.V. LONG PLAYING RECORD TURNABLE WITH CRYSTAL PICK-UP** (Sapphire Stylus). Speed 33 $\frac{1}{3}$  r.p.m. For A.C. mains 200-250 v. Limited supply. Brand New. Cartoned. Perfect. v. at up to 40 mA, and fully smoothed L.P. of 2 v. at 0.4 to 1 a. Price, complete with circuit, wiring diagrams and instructions, only 48/9. Or ready to use. 8/9 extra.

**BATTERY SET CONVERTER KIT.** All parts for converting any type of Battery receiver to All Mains. A.C. 200-250 v. 50 c/s. Kit will supply fully smoothed H.T. of 200 v. or 60 v. at up to 40 mA, and fully smoothed L.P. of 2 v. at 0.4 to 1 a. Price, complete with circuit, wiring diagrams and instructions, only 48/9. Or ready to use. 8/9 extra.

**PERSONAL SET BATTERY SUPERSEDER KIT.** A complete set of parts for construction of a Unit (housed in metal case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v. 50 c/s. Outputs 90 v. 10 mA and 1.4 v. 250 mA, fully smoothed. For 4-valve receivers. Price complete with circuit. Only 35/9. Or ready for use, 42/6. Size of unit, 5 $\frac{1}{2}$  x 4 x 1 $\frac{1}{2}$  in.

**BATTERY CHARGER KITS**  
For mains 200-250 v. 50 c/s.  
To charge 6 v. acc. at 2 a. 25/6.  
To charge 6 or 12 v. acc. at 2 a. 31/6.  
To charge 6 or 12 v. acc. at 4 a. 49/9.  
Above consist of transformer, full wave rectifier, fuses, fuseholders and steel case. Any type assembled and tested. 6/9 extra.

**THE SKY CHIEF T.R.F. RECEIVER.** A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point to point wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/16/- including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 $\frac{1}{2}$  x 5 $\frac{1}{2}$  in.

**ELECTROLYTICS** (Current production. Not ex-Govt.).

Tubular Types		200-250 v. 50 c/s.	
8 $\mu$ F 350 v.	1/9	16 $\mu$ F 450 v.	2/11
8 $\mu$ F 450 v.	2/11	24 $\mu$ F 450 v.	2/11
8 $\mu$ F 500 v.	2/11	32 $\mu$ F 350 v.	2/11
16 $\mu$ F 350 v.	2/3	32mfd. 450 v.	4/9
16 $\mu$ F 450 v.	2/9	40 $\mu$ F 450 v.	4/11
24 $\mu$ F 350 v.	3/8	64 $\mu$ F 450 v.	4/9
32 $\mu$ F 350 v.	3/8	84 $\mu$ F 350 v.	2/9
25 $\mu$ F 25 v.	1/3	8-8 $\mu$ F 450 v.	3/9
50 $\mu$ F 12 v.	1/3	8-16mfd. 450 v.	2/11
50 $\mu$ F 50 v.	2/3	8-16 $\mu$ F 450 v.	3/11
Can Types		200-250 v. 50 c/s.	
8mfd. 350 v.	1/3	16-32 $\mu$ F 350 v.	5/9
8 $\mu$ F 450 v.	2/3	32-32 $\mu$ F 450 v.	5/11

**RECORDING TAPE.** Best Quality. Plastic. 1,200 ft. Reels only 18/9.

Terms C.W.O. or C.O.D. No C.O.D. under £1. Post 1/- extra under 10/-, 1/6 extra under £1; 2/- extra under £2; 2/6 extra under £3. Open 9 to 5.30; Sats. until 1 p.m. List 6d. Trade List 5d. S.A.E. please with all enquiries.

## RADIO SUPPLY CO. 32, THE CALLS, LEEDS, 2

(LEEDS) LTD.

**A PUSH-PULL, 3-4 watt HIGH-GAIN AMPLIFIER FOR £3/7/6.** For mains input 200-250 v. 50 c/s. Complete kit of parts including circuit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C./D.C. with "live" chassis, but A.C. only with 400-400 v. trans. Output is for 2-3 ohm speaker. The amplifier can be supplied ready for use for 25/- extra. Carr. 2/6. Full descriptive leaflet, 7d.

**PLESSEY 3-SPEED MIXER AUTO-CHANGERS** with high impedance magnetic pick-up with duo point alloy stylus for long playing standard records. (Will play 2,000 records before replacement stylus required.) Brand new, cartoned, guaranteed. Limited stocks at only 10 gns., plus 5/- carr.

**MICROPHONES.** Crystal type, good quality. Recommended for use with our amplifiers. Hand type, 59/6; Stand type, 19/16/6.

**VOLUME CONTROLS** with long (in.) spindles, all values, less switch, 2/9, with S.P. switch 3/9. D.P. sw. 4/9

### R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries, 200-230-250 v. 50c/s Screened

**TOP SHROUDED, DROP THROUGH**  
250-0-250 v. 70 mA. 6.3 v. 2.5 a. ... 12/11  
250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 14/11  
350-0-350 v. 80 mA. 6.3 v. 2 a. 5 v. 2 a. 17/9  
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 21/11  
300-0-300 v. 100 mA. 6.3 v. 4 v. 4 a. c.t. ... 21/9  
0-4.5 v. 3 a. ... 21/9  
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 21/9  
350-0-350 v. 100 mA. 6.3 v. 4 v. 4 a. c.t. ... 22/9  
0-1.5 v. 3 a. ... 22/9  
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 27/9  
350-0-350 v. 150 mA. 6.3 v. 2 a. 6.3 v. 2 a. 5 v. 3 a. ... 29/11

**FULLY SHROUDED, PRIGHT**  
250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. ... 16/9  
Midjet type 21-3-3in. ... 16/9  
350-0-350 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9  
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 22/9  
250-0-250 v. 100 mA. 6.3 v. 6 a. 5 v. 3 a. ... 29/9  
for R1355 conversion  
300-0-300 v. 100 mA. 0-1-3.3 v. 4 a. ... 22/9  
0-4.5 v. 3 a. ... 22/9  
350-0-350 v. 100 mA. 0-4-6 v. 4 a. ... 22/9  
0-4.5 v. 3 a. ... 22/9  
350-0-350 v. 150 mA. 6.3 v. 4 a. ... 31/6  
0-4.5 v. 3 a. ... 31/6  
350-0-350 v. 250 mA. 6.3 v. 6 a. 1 v. 8 a. ... 69/9  
0-2.6 v. 2 a. 4 v. 3 a. for Electronic Eng. Telesvisor ... 69/9  
6.3 v. 4 a. C.T. 5 v. 3 a. Suitable Williamson Amplifier, etc. ... 47/9  
450-0-450 v. 250 mA. 6.3 v. 6 a. 6.3 v. 6 a. 5 v. 3 a. ... 69/9

**ELIMINATOR TRANSFORMERS**  
Primaries 200-250 v. 50 c/s, 120 v. 40 mA 7/9  
90 v. 10 mA. 7-0-7 v. 250 mA ... 8/11

**SELENIUM RECTIFIERS**  
L.T. Types H.T. Types H.W.  
2/6 v. 1 a. H.W. 1/9 120 v. 40 mA 3/9  
6/12 v. 1 a. H.W. 2/9 RM2 125 v. 100 mA

**F.W. Bridge Type** RM3 125 v. 12 $\frac{1}{2}$  mA  
6/12 v. 1 a. 4/9 5/9  
6/12 v. 2 a. 8/9 250 v. 50 mA 5/9  
6/12 v. 4 a. 14/9 250 v. 60 mA 6/11  
6/12 v. 6 a. 19/9 RM4 250 v. 250 mA  
6/12 v. 10 a. 28/9

**FOUR STAGE FEEDER UNIT.** Design of a High Fidelity Tuner Unit. L. & M. Wave. Full decoupling. Self-contained heater supply. Detailed wiring diagrams parts list, and illustration. 2/6. Total building cost, £3/15/-

**COAXIAL CABLE.** 75 ohms, 1 in., 7d. yard. Twin Screened Feeder, 9d. yard.  
**P.M. SPEAKERS.** All 2-3 ohms. 6in. Goodmans, 10/9. 8in. Plessey, 15/9. 10in. Plessey, 18/6. 10in. R.A., 29/6. 10in. Rola with trans., 29/6. 12in. Truvox, 49/9. 10in. W.B. "Stentorian" 3 or 15 ohm type HF1012 10 watts. Highly recommended for use with any of our amplifiers. £3/13/6.  
**M.E. SPEAKERS.** All 2-3 ohms. 6in. Rola, Field 600 ohms, 11/9. 8in. R.A. Field 600 ohms, 12/9. 10in. R.A. Field 1,000 or 1,500 ohms, 23/9.

**FILAMENT TRANSFORMERS**  
All with 200-250 v. 50 c/s primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6; 12 v. 3 a. or 2.4 v. 1.5 a. 17/6.

**CHARGER TRANSFORMERS**  
All with 200-230-250 v. 50 c/s Primaries:  
0-9-15 v. 1.5 a. 14/9; 0-9-15 v. 3 a. 16/9;  
0-9-15 v. 6 a. 22/9; 0-4-9-15-24 v. 3 a. 22/9.

**SMOOTHING CHOKES**  
250 mA 3-5 H 50 ohms ... 11/9  
150 mA 7-10 H 250 ohms ... 11/9  
100 mA 10 H 175 ohms Potted ... 8/9  
80 mA 10 H 350 ohms ... 8/9  
60 mA 10 H 400 ohms ... 4/11

**E.I.T. TRANSFORMERS**  
2,500 v. 5 mA, 2-0-2 v. 1.1 a. 2-0-2 v. 1.1 a. for VCR97, VCR517, etc. ... 36/8

**OUTPUT TRANSFORMERS**  
Midjet Battery Pentode 66: 1 for 354, etc. ... 3/9  
Small Pentode 5,000  $\Omega$  to 3 $\Omega$  ... 3/9  
Standard Pentode 5,000  $\Omega$  to 3 $\Omega$  ... 4/9  
Standard Pentode, 78,000  $\Omega$  to 3 $\Omega$  ... 4/9  
Multi-ratio 40 mA. 30: 1, 45: 1, 60: 1, 90: 1. Class B Push-Pull ... 5/6  
Push-Pull 10-12 watts 6V6 to 3 $\Omega$  or 15  $\Omega$  ... 15/9  
Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15  $\Omega$  ... 16/9  
Push-Pull 20 watts, sectionally wound, 6L6, KT66, etc., to 3 or 15  $\Omega$  47/9  
Economy Quality Amplifier type ... 47/9

## P. W. TAPE RECORDER

We can supply complete kits for this recorder.

Send for our fully detailed list.

FULL HIRE PURCHASE FACILITIES  
Only 2/- in the £ deposit.

## WATTS RADIO

8 Apple Market, Kingston-on-Thames, Surrey.

Telephone: KINGSTON 4099.

## THE OSRAM NINE - ONE - TWO

AMPLIFIER INSTRUCTION BOOK  
AND HIGHEST QUALITY COMPONENTS

Available from

## COVENTRY RADIO

189, Dunstable Road, Luton. 'Phone: 2677

Price, 3/6, plus 3d. postage  
also

Our 1954/5 COMPONENT CATALOGUE at 1/-

## Best Buy at Britain's

**COMMUNICATIONS RECEIVER TYPE R1155.**—For world-wide reception. WE ARE ONCE AGAIN ABLE TO OFFER THESE FINE RECEIVERS ABSOLUTELY BRAND NEW IN ORIGINAL TRANSIT CASE AT £11/19/6, plus 10/6 carr. This delivery is in really fine condition. If you are contemplating the purchase of one of these receivers in the near future, we advise you not to delay in order to secure a really "MINT" receiver.

A few slightly soiled models still available at £7/19/6, plus 10/6 carr. A.C. Mains power packs for same at £4/10/-, £3/5/- and £6/10/- carr. 3/6. Send S.A.E. for full details or 1/3 for circuit, etc.

**RECEIVER TYPE CR100.**—A super communications receiver covering 60 kc/s to 30 mc/s in six bands. Built-in A.C. mains power pack. 2 R.F. stages, 3 I.F. stages, variable selectivity Xtal Filter, B.F.O., etc. Good condition, complete with new valves and air tested. A bargain at £27/10/-, plus £1 carriage.

**TR.1196 RECEIVERS (25/73).**—This is a six-valve superhet receiver with 465 kc/s I.F.'s. Complete with all valves—2 EF39, 1 EK32, 2 EF36, 1 EBC33. In Good Condition with full conversion data. ONLY 27/6 each, plus 2/6 post.


**POWER PACK TYPE 301.**—Contained in a neat black case size 8 1/2 in. x 4 1/2 in. x 6 1/2 in. high. For 200/250 volts A.C. 50 cps. Outputs 250-0-250 v., 6.3 v. at 2.8 amps., 6.3 v. at 6 amps. for 6X5 rectifier. 31 v. at 3 amps. supplies metal rectifier for bias. The transformer is a massive job. Price ONLY 37/6, plus 2/6 post.

**E.M.I. OUTPUT METER.**—Desk Type. Consists of a 2 1/2 in. 1 mA. meter with full wave bridge rectifier. Ranges 0-500 milliwatts and 0-5 watts. Brand New and Boxed: ONLY 35/- each, plus 1/6 post.



**CHARLES BRITAIN  
(RADIO) LTD.**

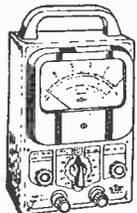11, Upper Saint Martin's  
Lane, London, W.C.2. TEM 0545  
Shop hours, 9-6 p.m. (9-1 p.m. Thursday)  
OPEN ALL DAY SATURDAY




**PULLIN  
SERIES 100  
TEST METER**  
AC/DC 10,000 A/V  
21 RANGES  
100µA to 1000 V  
COMPLETE IN DIE-CAST  
CASE WITH TEST LEADS  
CLIPS AND PRODS  
FULLY GUARANTEED

SENT POST FREE FOR £2.10.S.  
DEPOSIT AND TEN FURTHER MONTHLY  
PAYMENTS OF £1. CASH PRICE 11GNS

Frith  
**RADIOCRAFT Ltd**  
69-71 CHURCH GATE LEICESTER

PHONE 58927

## CABINETS

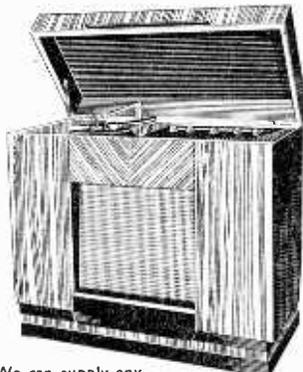

We can supply any Cabinet to **YOUR OWN SPECIFICATION.** The one illustrated can be obtained in Walnut, Oak or Mahogany for £19/15/-, or as a complete **RADIOGRAM** including a 5-valve 3-waveband superhet chassis, 3-speed autochanger and 10in. speaker for £45. (H.P. Terms can be arranged.) Send 1/- for Complete Catalogue of Cabinets, Chassis, Autochangers and Speakers. (Refunded on receipt of Order.)

## LEWIS RADIO CO.

120, GREEN LANES,  
PALMERS GREEN, LONDON, N.13.  
BOWes Park 6064

## J.B. SERVICE (BEXLEYHEATH) LTD.

RADIO COMPONENT SPECIALISTS

5, MAYPLACE ROAD WEST,  
BEXLEYHEATH, KENT.

Phone: BEXLEYHEATH 1000

Wednesday Half Day

44, CHURCH ROAD,  
UPPER NORWOOD, S.E.19

Phone: LIVINGSTONE 6222

Wednesday Half Day

All types of Valves Old or Modern Wanted for Cash. Send Full Particulars for prompt offer. N.B.—Not Secondhand used valves.

## LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.P.  
SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPHERDS Bush 1729

**T.V. SCOPE.** Make this useful instrument as described in the August issue of the "Practical Television" by converting INDICATOR UNIT TYPE 6. Unit fitted with cathode ray tube type VCI397 (Scope tested) Mu metal screen, 6 valves (VR91's, 2 VR54's) pots., resistors, condensers and other useful gear. In used, good condition. PRICE ONLY 57/6 or less valves PRICE ONLY 37/6. Carriage charge 6/6.

**RECEIVERS TYPE R.1155.** One of the best known and most popular of ex-Government communications receivers. Frequency range includes 20, 40 and 80 metre "Ham" bands, long and medium wave transmissions. Valve line-up: VR100, Sig. freq. Amp.; VR99, Freq. changer.; VR100, 1st I.F. Amp. VR100, 2nd I.F. Amp.; VR101, Det. A.F. Amp.; VR101, A.V.C.; B.F.O.; V1103 Tuning Indicator. With 100 to 1 slow-motion drive, 5 switched wave bands, etc. In very good new condition and carefully aerial tested before despatch, supplied in maker's transit case. PRICE £10.17.6, carriage 7/6.

**A.C. MAINS POWER PACK/OUTPUT STAGE UNITS FOR R.1155.** Specially designed to operate these receivers direct from 200/250 v. A.C. Mains and to provide for a speaker output. Fitted with 5Z4 rectifier and 6V6 output valves and connector which plugs direct into receiver for immediate use. PRICE £3.19.6, carriage 3/6.

**SPARE VALVES FOR R.1155.** Types VR99, VR100, VR101. PRICE 8/6 each, post 6d.

**L.T. TRANSFORMERS.** Primary 200/250 v. 50 cps. mains. Secondary 3, 4, 5, 3, 8, 9, 10, 12, 15, 18, 20, 24 or 30 v. at 2 A. Excellent for model railways accumulator charging, etc. PRICE 18/6, post 1/6.

## Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH

CALL OR SEND DRAWINGS  
FOR QUOTATION

## B. KOSKIE

(DEPT. C.)

72-76 Leather Lane,  
Holborn, E.C.1

Phone: CHAncery 6791/2


# AMPLIFIER DESIGN

## 9.—UNTUNED AMPLIFIERS—CONTINUED

By R. Hindle

(Continued from page 666 November issue)

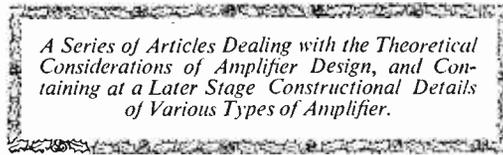UNDER the conditions given last month the time constant is then  $\mu F \times M.\Omega$  i.e.  $.001 \times 50 = .05$  second which is reasonably large compared with the period of a 50 cycle note (.02 second).



factors have to be taken into consideration by the valve manufacturer when determining the optimum load for his product and though we shall find the need later to return to this problem, for the time being we will take the

easier path of following the maker's recommendations.

### Distortion

A table of the values of grid voltage and anode current at the various points of interception of the curves by the load line in Fig. 31 can be made and if these are plotted on a graph of anode current versus grid voltage as in Fig. 32 the distortion can be more readily seen. Without distortion this graph should be a straight line and the deviation from straight (the dotted straight line being drawn in so that the curvature can be seen) indicates the degree of distortion. It will be seen that the curve is at one side of the dotted straight line along its length and that it is a single graceful sweep rather than a somewhat misshapen half-cycle of a sinewave. This indicates that the distortion is second harmonic and in fact it is well-known that the predominant distortion in the case of a triode is second harmonic. This is more tolerable to the ear than the third harmonic of a pentode output valve, which would be represented by a distortion curve that crosses the dotted straight line and is thus more like a full sinewave cycle. The percentage distortion can actually be calculated from the distortion curve by measuring the divergence of the anode current at the quiescent grid voltage point (i.e. 35 volts in the example) which call  $I_0$ . Now, using the maximum anode current  $I_{max}$  and the minimum current  $I_{min}$  passed by the valve during operation the following formula applies:—

$$\text{2nd harmonic} = \frac{\frac{1}{2}(I_{max} + I_{min}) - I_0}{I_{max} - I_{min}} \times 100\%$$

### Output Transformer

One might well wonder why an output transformer is used at all and indeed it would be very convenient beside removing a major source of distortion, if this component could be dispensed with. Unfortunately the practical difficulties in winding the speech coil of a moving coil loud speaker with an impedance approximating to the load required by a valve are too great. The speech coil is carried on the cone as part of the moving system and consequently there are severe limitations on the size and weight permissible. Consequently it is found more satisfactory to accept the disadvantages of the output transformer and to wind the speech coil to a comparatively small impedance. The transformer is then chosen to have a step-down ratio equal to the square root of the ratio of the load required to the speech coil impedance.

A further complication is that the speech coil impedance is not a constant but actually varies with frequency. The value usually quoted and used for determining output transformer ratio is that at a frequency of 1,000 cycles but as will be seen from Fig. 33 at other frequencies it is much higher. These

### Practical Design

Now the first output stage to work with the amplifier previously described will be attempted. This will use a triode to illustrate the principles discussed but later a tetrode design will be given and so, for the sake of economy and to permit the reader to try out both at a minimum of expense a valve that will demonstrate both types of circuit will be chosen. Also, continuing the policy of demonstrating modern technique, the valve will be chosen from the modern miniature range such as is used in all the latest equipment.

A very suitable valve is the Brimar 6AQ5 which is a beam tetrode but by strapping grid 2 to anode the valve works as a triode. There is a further advantage in following this course in that most available output triodes are directly heated and consequently introduce circuit difficulties whereas, of course, the 6AQ5 is indirectly heated. Fortunately also there is an exact equivalent to the 6AQ5 for use in A.C./D.C. circuits and so the basic design that we shall produce will be applicable to this method of working too, and two versions of the amplifier will be given, one using the 6AQ5 in a purely A.C. circuit and the other using the Brimar 19AQ5 in an A.C./D.C. circuit, both operating with the twin-triode amplifier already designed and both capable of being converted for beam tetrode working later for comparison purposes. The Brimar 6BW6 could be used as an alternative on the A.C. version, having the same characteristics but with a B9A base instead of a B7G base.

### Valve Data

Fig. 34 gives the anode characteristics for these two valves working as triode. It is proposed to work the valve with a H.T. of 250 volts, this being a convenient

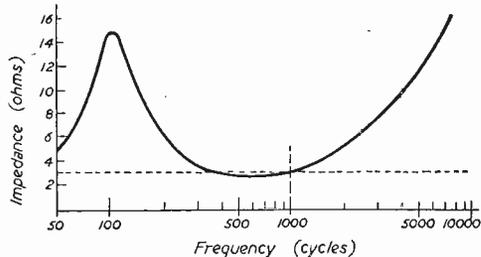


Fig. 33.—Impedance curve of a typical moving-coil speaker, nominally 3 ohms.

and economical value to provide using standard components, and so the working point is on the vertical line representing this voltage. The maximum anode dissipation given by the makers is 12.5 watts and the line representing this dissipation is shown dotted on the diagram. We must see that when the valve is working along the load line this maximum

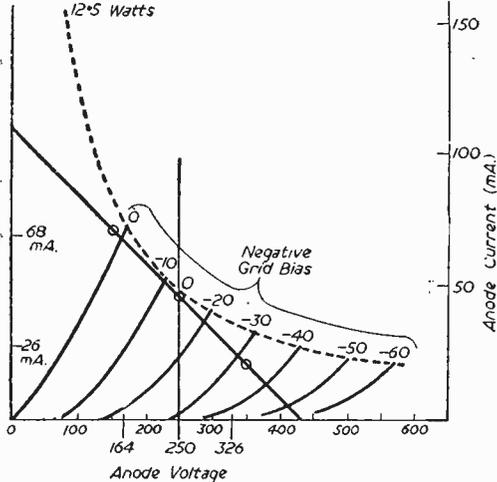


Fig. 34.—Characteristic of 6AQ5 ; 19AQ5 ; 6BW6.

dissipation is not exceeded but we shall go as high as possible up the 250 volt line so as to obtain the maximum output.

Following the 250 volt H.T. line vertically it is seen that the grid bias must be at least about 12 volts if the no-signal condition is not to result in the anode dissipation exceeding the permitted maximum and so we are not in the least surprised to find that the makers specify 13.5 volts for this H.T. voltage.

Point O can therefore be marked in at 250 volts H.T. and -13.5 volts grid bias, where it will be seen that the anode current flowing is 45 mA. The valve lists also give the optimum load as 4,000 ohms. This load, being in the form of a speaker speech coil with its impedance stepped up to the anode of the valve by means of a transformer, has already been seen to have negligible effect on the no-signal condition but from the point of view of the audio signal currents it is very real and it will have an effect on the instantaneous anode voltage which obeys the ordinary principles of Ohm's Law. Thus supposing there were a signal current of 50 mA peak-to-peak produced in the load, then, by Ohm's Law, there would be a signal voltage across the load of :

$$I \times R = 50 \times 4,000 \text{ (divided by 1,000 because } I \text{ is in mA.)}$$

$$= 200 \text{ volts peak-to-peak.}$$

Now this voltage would swing about the no-signal condition, equally below and above it, so the anode voltage would go from 250 + 100 to 250 - 100 and the current from 45 - 25 to 45 + 25 mA (the higher the current the greater the voltage lost in the load and therefore the lower the voltage actually at the anode and vice versa). So these two points can be marked on the curves, i.e., 350 volts 20 mA and 150 volts 70 mA. These points will be on the load line and so the line can be drawn in joining these points and extended in both directions and the accuracy of the work is shown by the fact that the line passes through the static point O, as it should do.

Reasonably linear operation is practicable along this load line down to zero grid bias ; the signal must not be allowed to go beyond this value or grid current will cause distortion. Thus the peak signal that the valve will accept is equal to the static bias i.e. 13.5 volts. The negative half-cycle of the input signal will be of equal amplitude but will swing in the other direction so that the grid goes to 13.5 + 13.5 = 27 volts negative.  $E_{m.in}$  in the formula already given is the anode voltage at the least negative

(Continued on page 753)

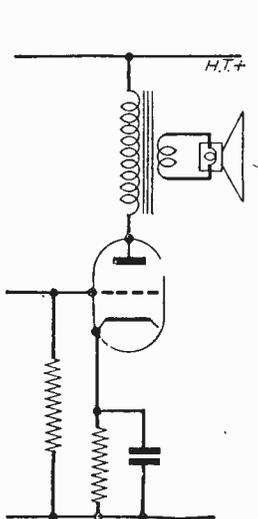


Fig. 35.—Basic circuit of triode output stage.


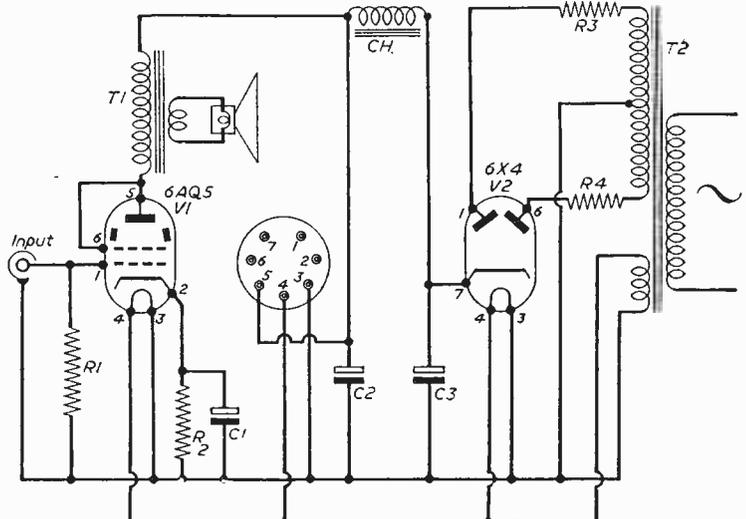


Fig. 36.—Complete circuit for a triode power amplifier—A.C. version.

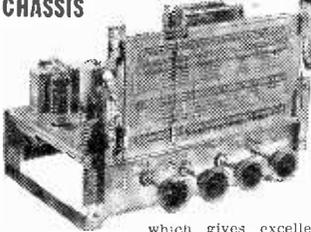
**THREE COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS**



which gives excellent clarity of speech and music on both gram. and radio, making them the ideal replacement chassis for that "old Radiogram," etc.

- Model B3. A 5-valve 3 waveband receiver. £12.12.0. (Plus 7/6 carr. and ins.) H.P. Terms £3.4.0 Dep. and 12 Months at 17/8
- Model B.3.P.P. A 6-valve 3 waveband Receiver with PUSH-PULL OUTPUT. £15.15.0. (Plus 7/6 carr. and ins.) H.P. Terms £3.19.0 Dep. 12 Months at £12.2
- Model B.3.P.P./R.F. A 7-valve 3 waveband Receiver, incorporating an R.F. stage with PUSH-PULL OUTPUT. £18.18.0 (Plus 7/6 carr. and ins.) H.P. Terms £4.13.0 Dep. 12 Months at £16.6

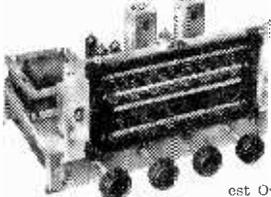**A BULK PURCHASE ENABLES US TO OFFER THIS "PUSH-PULL" 7-VALVE SUPERHET RECEIVER**



for only £12.19.6. (Plus 7/6 carr. and ins.) H.P. Terms £3.4.6 Dep. 12 Months at 18/4.

Model AW3-7 Receivers are made by a well-known manufacturer and incorporate the latest Ostram Valve line-up, having two 7B7's in Push-Pull for approx. 7 watts output. They cover 3 wavebands and are for operation on A.C. mains. They make an excellent replacement radiogram chassis.

THEY ARE BRAND NEW AND FULLY GUARANTEED.

Send S.A.E. for our Illustrated and Descriptive leaflet of various Radio, Radiogram Chassis, Autochange Units, Amplifiers, etc.

**TWO COMPLETE Hi-Fi AMPLIFIER KITS A HIGH QUALITY 8-10 watt AMPLIFIER**



THE IDEAL AMPLIFIER FOR GENERAL HOME USE AND FOR SMALL HALLS, etc.


PRICE OF COMPLETE KIT, INCLUDING VALVES AND DRIILLED

CHASSIS £7.10.0. (Plus 2/6 carr. and ins.) IT COMPLETELY BUILT FOR £9.10.0 (Plus 5/- carr. and ins.) Designed for high quality reproduction up to an output level of 10 watts, having 6V6's in Push-Pull and incorporating negative feedback. Suitable for use with all types of Pick-ups and most types of microphones and the output transformer provides for use of 3 and 15 ohm speakers. BRIEF FEATURES:

- Valve line-up 6J5, 6SN7, 5Z4, with 6V6's in push-pull. • First class reproduction of radio (where a tuning unit is used) and record playing. • Separate Bass Boost and Treble controls provide an excellent range of frequency control.

The ASSEMBLY MANUAL is available for £- and includes detailed layouts and component Price List.

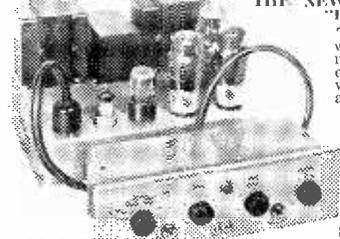**THE NEW "LEAK" TL10 AMPLIFIER AND "POINT ONE" PRE-AMPLIFIER**



This amplifier has a maximum output of 10 watts and maintains in every respect the world renowned LEAK reputation for precision engineering; fine appearance and fastidious wiring. The Pre-Amplifier will operate from any make or type of pick-up.

- (a) THE COMPLETE AMPLIFIER with Pre-Amplifier £28.7.0 or £7.2.0 Dep. and 12 Months at £2.
- (b) THE TL 10 MAIN AMPLIFIER only £17.0 or £4.7.0 Deposit and 12 Months at £15.4.
- (c) The "POINT-ONE" PRE-AMPLIFIER only £10.10.0 or £2.12.6 Dep. and 12 Months at 15/-.

S.A.E. FOR DESCRIPTIVE LEAFLET.

*Modernise your old Radiogram*

The three receivers are for operation on A.C. mains, and employ the very latest miniature valves. They are designed to the most modern specification, great attention having been given to the quality of reproduction



**A GENUINE SPECIAL OFFER!**

**3-SPEED AUTOCHANGE UNITS BY FAMOUS MANUFACTURERS from £9.19.6**

(Plus 7/6 carr. and ins.) (Normal Price £15.10.0). H.P. Terms £2.10.0 Dep. and 11 Months at 15/6


- Complete with High Fidelity Crystal "Turnover" Head which incorporates separate stylus for L.P. and 78 r.p.m. records.
- Will autochange on 7in., 10in. and 12in. records, not inter-mixed.
- Brand New in Maker's Cartons, complete with mounting instructions.



WE ALSO HAVE "MIXER" UNITS

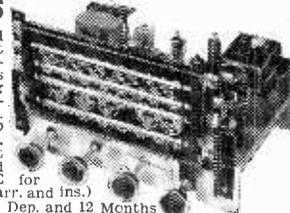**The "SUPER-SIX" A DESIGN FOR HOME CONSTRUCTORS**

A compact and highly efficient superhet Radio-Radiogram chassis of outstanding quality for operation on A.C. mains. YOU CAN BUILD IT FOR £10.7.6.



We will supply it assembled and READY FOR USE for £13.13.0 (Plus 7/6 carr. and ins.) H.P. Terms £3.10.6 Dep. and 12 Months at 19/-.

This receiver incorporates the new B.V.A. miniature valve line-up, and is designed to the very latest specification. Great attention has been paid to the quality of the reproduction of both Radio reception and Record playing, and excellent clarity of speech and music is obtained. • Covers 3 wavebands. • Employs 6 valves having PUSH-PULL for 5-6 watts output. • A 4 position Tone Control operates on both Radio and Gram. THE INSTRUCTION & ASSEMBLY MANUAL is available for 2/-.

**A 12-Watt "HIGH FIDELITY" Push-Pull AMPLIFIER**

Comprising Main Amplifier Chassis and a Remote Control Pre-Amplifier-Tone Control Unit. The remote control unit measures only 7in. x 4in. x 2in. and contains four controls, being: Bass-Treble Volume and a Radio, Gram, Microphone Switch control. It incorporates its own feedback circuit on the Bass Channel. Loop negative feedback is employed on the Main Amplifier which has a valve line up of 6J5-6N7-5U4 with two 6X25's in push-pull and 6J5 and 6SN7 are used. THE COMPLETE UNIT ASSEMBLED AND READY FOR USE £17.0.0. (Carr. and ins. 5/- extra.) H.P. Terms £4.5.0 Dep. 12 Months at £13.11.



THE COMPLETE KIT IS AVAILABLE FOR £14.0.0. (Carr. and ins. 3/- extra.)

WE HAVE IN STOCK THE

DENCO F.M. FEEDER UNIT Consisting of a 4 valve Superhet design incorporating E.F. (6AM6) and F.C. (12AH9) Stages followed by Two I.F.s (6BA6's) and Ratio Discriminator, the coverage provided being 88-100 Mc/s.

THE COMPLETE KIT, including VALVES and DRIILLED CHASSIS available for £6.13.6. (Plus 4/- carr. and ins.)

COMPLETELY ASSEMBLED CHASSIS, READY FOR USE, ALIGNED AND TUNED. £8.17.6. (Plus 6/- carr. and ins.)

Suitable for use with any type of High Fidelity Amplifier. Descriptive manual, including circuit and component layout, etc., available for 1/6.

**STERN RADIO LTD. 109 & 115 FLEET ST., E.C.4.**

Telephone Central 5812/3/4

# FIRST-CLASS RADIO COURSES . .

**GET A CERTIFICATE!**

**QUALIFY AT HOME—IN SPARE TIME**

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

### FREE GUIDE


The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc.,** together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSES**

**NATIONAL INSTITUTE OF ENGINEERING**

(Dept. 461), 148, HOLBORN, LONDON, E.C.1

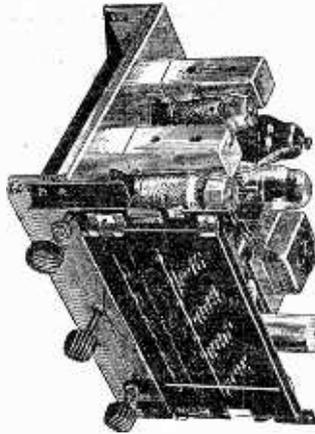

**THE CORONET POWER RODING LABORATORIES**

is but one of the many outstanding receivers, amplifiers and test gear (see previous ads. for list) fully described together with blueprint circuits and complete parts lists in the famous **RODING HOME CONSTRUCTOR'S HANDBOOK**

which for **ONLY 2/6d.** just about represents the finest value the radio enthusiast can get to-day. Printed on finest glossy art paper it also contains Set Building and Servicing Hints, Factors and Formulae, Resistance Colour Code, Symbols, etc. AND our current Catalogue. **SO DON'T DELAY—SEND TO-DAY!**

**REMEMBER!** Our Superhet Tuning Units are pre-aligned and sealed for maximum efficiency—no test gear being required by the Constructor. All components and chassis are available from us at reasonable prices and are fully identified. **FREE "ABC" Construction Sheets** available (see Handbook).

Also obtainable from leading booksellers and component stockists

**RODING LABORATORIES** (Dept. CFI) **BOURNEMOUTH AIRPORT, CHRISTCHURCH, HANTS.**

## COPPER WIRE

COTTON COVERED			SILK COVERED		
S.W.G.	2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.
16	1/4	2 1/2	1/4	2 1/2	1/4
17	1/4	2 1/2	1/4	2 1/2	1/4
18	1/4	2 1/2	1/4	2 1/2	1/4
19	1/5	2/3	1/6	2/5	1/6
20	1/5	2/4	1/7	2/8	1/7
21	1/5	2/5	1/8	2/10	1/8
22	1/6	2/6	1/9	3/—	1/9
23	1/7	2/7	1/10	3/2	1/10
24	1/7	2/8	1/10	3/2	1/10
25	1/8	2/9	1/11	3/4	1/11
26	1/9	2/11	2/—	3/6	2/—
27	1/10	3/1	2/1	3/8	2/1
28	1/10	3/2	2/2	3/10	2/2
29	1/11	3/4	2/3	4/—	2/3
30	2/—	3/6	2/4	4/2	2/4
31	2/1	3/7	2/5	4/4	2/5
32	2/1	3/8	2/7	4/8	2/7
33	2/3	3/11	2/10	5/2	2/10
34	2/4	4/2	2/11	5/4	2/11
35	2/6	4/5	3/1	5/8	3/1
36	2/7	4/8	3/3	6/—	3/3
37	3/—	5/6	3/5	6/4	3/5
38	3/4	6/2	3/7	6/8	3/7
39	—	—	3/10	7/2	—
40	4/6	8/—	4/1	7/8	—

POSTAGE EXTRA.  
POST ORDERS ONLY PLEASE.  
Send stamp for comprehensive lists.

**CRYSTAL SET**  
INCORPORATING THE SILICON  
**CRYSTAL VALVE**  
Adjustable Iron Cored Coil.  
**RECEPTION GUARANTEED**  
Polished wood cabinet, 15/-, post 1/-  
A REAL CRYSTAL SET, NOT A TOY

**POST RADIO SUPPLIES**  
33 Bourne Gardens, London, E.4

## Just Published—TRANSISTORS AND CRYSTAL DIODES

What They Are and How to Use Them  
By B. R. BETTRIDGE

- 5s. 0d. post 3d.
- The A.R.R.L. Antenna Book, NEW EDITION, 14s. 0d. post 6d.
- Hints and Kinks for the Radio Amateur, Vol. 5 by "A.R.R.L.", 10s. 6d., post 4d.
- Basic Electronic Test Instruments, by R. P. Turner, 32s. 0d., post 1/-.
- Wireless Servicing Manual, by W. T. Cocking, 12s. 6d., post 4d.
- Everyman's Wireless Book, by F. J. Camm, 12s. 6d., post 4d.
- Reference Data for Radio Engineers, by "Federal Telephone & Radio Co.", 37s. 6d., post 1/-.
- Principles and Practice of Radar, by H. E. Penrose and R. S. H. Boulding, 50s. 0d., post 1/-.
- Radio Engineering, by F. E. Terman, 50s. 0d., post 1/-.
- Radio Valve Data, new edition, compiled by Wireless World, 3s. 6d., post 3d.
- Radio Designer's Handbook, by F. Langford-Smith, 42s. 0d., post 4/-.

**THE MODERN BOOK CO.,**  
BRITAIN'S LARGEST STOCKISTS OF BRITISH AND AMERICAN TECHNICAL BOOKS  
19-23 PRAED STREET, [Dept. P.12] LONDON, W.2.  
'Phone: PADDINGTON 4185, Open all day Saturday.  
Please write or call for our catalogue.

**BENSON'S BETTER ARGAINS**

**BRAND NEW. ORIGINAL CARTONS. R.F. UNITS. TYPES 26 or 27, 27/6, 24 15/- (Postage 2/6).**

**METERS:** New, boxed, M.C. 2 1/2 in. Fl. rd., 100 microamps, 35/-; 350-700 v. (1 mA F.S.D. only), 20/-; 15/0 to 15 v., 10/6; 10/0 to 10 mA Proj., 10/6; Electrostatic 1,500 v. Proj., 20/-; 10 mA, 7/6; doz. 130 v. (1 mA F.S.D.), Rec., 15/6; 10 mA, 20 mA, 100 mA, 200 mA, 300 mA, M.I. 15 v., 20 a. Proj. T.C. 1 a. M.C. 30 a. All at 8/- each. 2in. sq. M.C. 5 mA. 100 mA. T.C. 3 a. at 7/- each. 2in. Rd. Proj. M.C. 30 mA, 7/-; 2in. sq. F. 20 v. M.C. 8/6. R1155, slow motion drives, 7/6; I.F. Filter, 2/6. Coilpacs, new, 12/6. Used, 9/6.

**CONDENSERS.** Variable min. spindled, 1s. 2s. 50. 75 pls., 1/3. **DYNAMOTORS,** solled cases, D.C. (approx. 250 v. 80 mA, at 6 v.), 8/6. Filters for these, 2/6. I.F.T.'s, new, canned 7 Mc/s. (R1355), or 10/13 Mc/s., 1/6. **POWER UNIT 285,** 230 v. 50 c. input. Outputs D.C. 2 kv 5 mA, 350 v. 150 mA, A.C. 6.3 v. 15 a., 3 valves. New 75/-, cart. paid inland. **TRANSFORMERS,** new, std. mains input; 250-0-250 v. 70 mA, tapped 200 v., 6.3 v. 3 a., 4 v. 2 a., 10/6; 600 v. H.W. 6.3 v. 3 a., 4 v. 2 a., 10/6; 230 v. to 6.3 v. 5 a. and 10 a., 15/-; 2 kv 5 mA, 2 v. 2 a., 25/-; 350-0-350 v. 150 mA, 5 v. 3 a., 25/-; 55 v. 30 mA (twice), 6.3 v. 3.2 a., 9/-; 220-0-220 v. 33 mA, 7.1 v. 8 a., 8.4 v. 10 a., 5 v. 3 a. each C.T., 15/6; 740-0-740 v. 65 v. 470-0-470 v. 220 v. 4 v. 8 a., C.T. (twice), 40/- (cart. 5/-); 350-0-350 v. 120 mA, 6.3 v. 4 a., 4 v. 2 a., 16/-.

**METAL RECS.** Whse. B33, 10/6. **STC H67-34-IE-TF,** 22/6, 600 v. 30 mA, 6/-, 270 v. 80 mA, 6/-.

**POTENTIOMETERS,** carbon, 10/6 doz. ass'd. Postage 2/6 each. List and enquiries S.A.2, please! **Terms:** Cash with order. Postage extra. Immediate despatch. Callers and Post. Callers only

**W. A. BENSON (PW), SUPERADIO**  
308 Rabbone Rd., (Whseps), LTD., 116  
Liverpool 13. Whitechapel, Liver-  
pool 1. ROY 1130  
STO 1804

grid voltage of the working range ( $E_g = 0$  volts), i.e., 165 volts, and  $I_{min}$  is the anode current at the most negative grid voltage (27 volts) and is 27 mA.  $E_{HT}$  and  $I_{HT}$  are respectively 250 volts and 45 mA, so power output is:

$$\frac{250 \times 45}{2 \times 1,000} \cdot \left(1 - \frac{165}{250}\right) \cdot \left(1 - \frac{27}{45}\right) = .765 \text{ watts}$$

or in round figures  $\frac{3}{4}$  watt. The factor 1,000 that appears in the denominator of the first expression above has to be introduced because  $I_{HT}$  is in mA.

**Distortion**

It is meaningless to talk about power output without indicating the degree of distortion present and there must be distortion with the 6AQ5 as with any other valve. If a distortionless state could be set up the anode swing above and below the static voltage would be the same for a given input grid voltage variation. Thus with a sine wave input of the maximum permissible amplitude (as above) of 27 volts peak to peak the grid swings equally  $13\frac{1}{2}$  volts below the steady bias position and  $13\frac{1}{2}$  volts above the static condition and so the anode should swing equally above and below the static 250 volts used for the design. In actual fact, however, it is seen that the anode actually swings from 164 volts to 326 volts, i.e., from 88 volts below to 76 volts above 250 volts, so clearly there is a measure of distortion. The makers specify, in fact, 3.5 per cent. total distortion for the working conditions used for this design and if we doubted that information it could be proved by drawing the distortion curve in the form shown in Fig. 31. This amount of distortion is very satisfactory for this simple type of circuit, for in earlier years it was quite common to work with distortions up to 10 per cent.

**A.C. Version**

The basic power output circuit given in Fig. 35 is developed to include the power and rectifier circuits with the result, for the A.C. case, as shown in Fig. 36. V2 is a normal full-wave rectifying circuit operating from a 250-0-250 volt winding on the mains transformer T2. For the sake of consistency the rectifier valve is chosen from the Brimar range of modern miniature valves and is, in fact, a 6X4. The heater of this valve takes 6.3 volts and not 5 volts, as is provided on the usual mains transformer. The reason is that the heater cathode insulation is made sufficient to withstand up to 450 volts and so the rectifier heater can be connected across the same supply as the other valves in the circuit. From Fig. 36 it will be seen that this is done in the present case and only a single heater winding is required. The transformer chosen has a 5-volt winding as a

matter of fact, and this is left disconnected. The choice fell to this particular component, the Elstone type MT/M1, because of its small size enabling the final design to be compact in keeping with the previous amplifier and with modern practice.

The valve data for the 6X4 stipulates a minimum resistance in each anode circuit of 150 ohms. Quite often the transformer winding itself provides this resistance but to make sure in the present design the resistors R3 and R4 are incorporated. Smoothing is conventional and is found quite adequate.

The rectifier is rated to give a maximum of 70 mA. and the output valve, as we have seen, requires only 45 mA., so there are 25 mA. available for other circuits and consequently a power output socket is provided. The heater winding gives up to 1.5 amps., and the two valves on the chassis require only just over an ampere together, so the heater voltage is also fed to the output power socket. The two-stage voltage amplifier previously described had no power supply incorporated and it is intended to take its supply from the present chassis; its needs are easily provided by this power supply.

The 6AQ5 is seen to be strapped as a triode and is biased by R2, which is by-passed by C1; R1 provides the D.C. grid return path. The input signal required to fully load the output valve was seen to be 13.5 volts peak and this is well within the rating of the valve used for the voltage amplifier. By Ohms Law, R2 to give a bias of 13.5 volts with a current of 45 mA should be 300 ohms.

The chassis used is of similar construction to that of the voltage amplifier except that it is made twice as long to accommodate the power equipment. Even

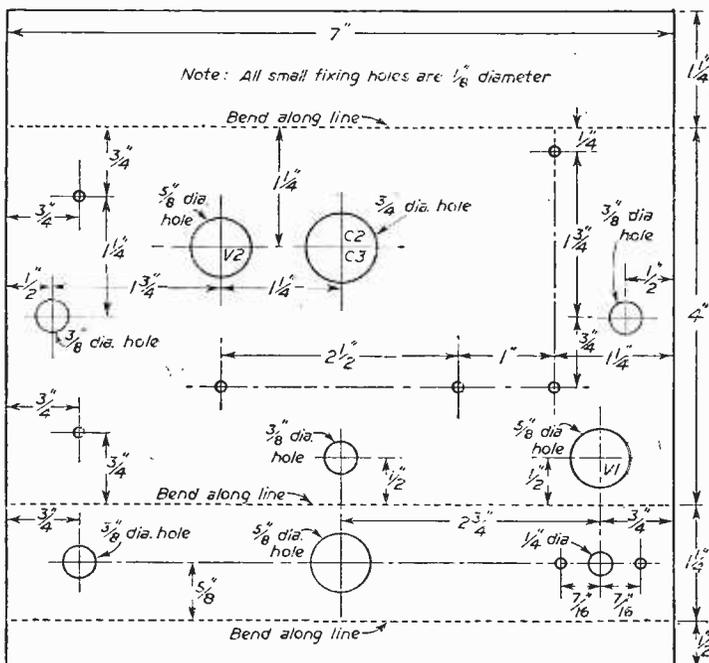


Fig. 37.—Chassis drilling diagram for A.C. amplifier (Fig. 36). Note that the  $\frac{3}{8}$ " holes are for gronimets.

then, it is only 7in. x 4in. Fig. 37 gives the drilling data for the components actually used and, as probably most constructors will obtain their chassis ready folded, the markings are as at the outside of the chassis. Perhaps a warning should again be given that the components should be obtained and measured before drilling the chassis (which in the prototype was of aluminium) because the position of the holes might vary slightly. Probably the neatest way is to make a template of drawing paper, marking the positions of the holes. The components can be tried on this and when satisfied the positions can be punched through the template. Notice that at only one point does the earth line contact the chassis, by the input coaxial socket. Apart from this connection chassis returns are not used except for the electrolytic capacitor C2, C3, the case of which is earthed in the usual way via the mounting clip.

### Wiring

The wiring diagram is given in Fig. 38 and if the following sequence is followed no difficulty will be experienced.

1. Input socket to pin 1 V1.
2. R1. 220K $\Omega$ . From pin 1 V1 to earth tag by input socket.
3. Pin 3 V1 to earth tag to pin 3 output power socket to pin 3 V2.
4. Pin 4 V1 to pin 4 power output socket to pin 4 V2.
5. Pin 6 V1 to pin 5 V1 to tag 3 on output transformer.
6. R2. 300 $\Omega$   
C1. 50 $\mu$ F } Both from pin 2 V1 to earth tag.
7. Pin 5 power output socket to nearest tag on electrolytic to tag 4 on output transformer.
8. Pin 3 power output socket to one side of 6.3 winding on output transformer.
9. Pin 4 on power output socket to other side of 6.3 winding.
10. R3. 150. From pin 1 V2 to pin 2 V2.

11. R4. 150. From pin 6 V2 to pin 5 V2.
12. Centre-tap of mains trf. H.T. winding to pin 3 V2.
13. Outside connections of H.T. winding to pins 2 and 5 V2.
14. Mains lead to tags on mains transformer marked for mains voltage available.

### Using the Amplifiers

To connect the two amplifiers together a coaxial plug is fitted to the coaxial output lead from the voltage amplifier and plugged to the input of the power amplifier. A miniature plug is fitted to the power lead from the voltage amplifier. A four-core cable was used for this purpose in order to offer the maximum flexibility in use but for the present case only three inter-connections are required, one side of both heater and H.T. being earthed. Consequently this interconnection is made in the miniature plug, the lead from the earth busbar of the voltage amplifier and one side of the heater being connected to pin 3 of the plug and so to earth.

A peak signal of a tenth of a volt fed into the voltage amplifier with the volume control at maximum will be found to fully load the output stage.

It is intended that the power amplifier be stowed away in the cabinet of the equipment in which it is to be used rather than placed side by side with the voltage amplifier which has to be so mounted that the control is accessible. Later on, when R.F. amplifiers have been discussed a design will be produced to feed into these amplifiers and to be mounted alongside the voltage amplifier.

### Universal Mains Version

The complete circuit for the universal version will be given next month. It will be seen that the valve heaters are connected in series and, of course, the voltage amplifier must be suitably wired as explained in the wiring data of that chassis. High-voltage heater valves are employed so that the minimum voltage remains to be dropped in the series resistor (R4, R5). V1 is the 19AQ5 and a half-wave miniature rectifier, the 35W4 matches this and so is used. The important characteristic in series wiring of heaters is, of course, the current taken by the heaters, not the voltage, and both these valves take .15 amps. The specified wiring of the voltage amplifier for universal operation results in the same heater current being taken by the 12AU7. The three valves, then, take 67 volts at .15 amps when connected in series and the dropper has to have a resistance to drop the surplus. Thus, supposing the mains are of 240 volts. The voltage to be dropped is now  $240 - 67 = 173$  volts at .15 amps. By Ohm's Law:

$$R = \frac{E}{I}$$

$$= \frac{173}{.15}$$

$$= 1,150 \text{ ohms.}$$

(To be continued.)

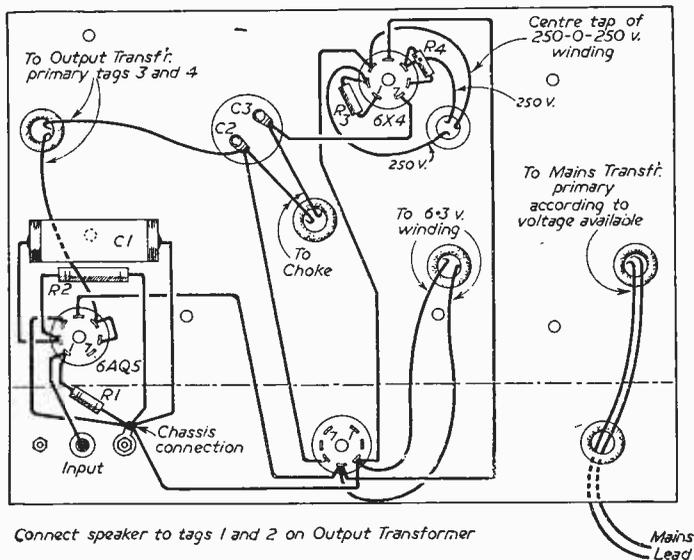


Fig. 38.—Wiring diagram for the Fig. 36 circuit.





# What is HI-FI ?

IS THERE SUCH A THING AS HIGH FIDELITY? A CRITIC EXAMINES THE SITUATION AND MAKES SOME SUGGESTIONS  
By "Grid Current"

**I**T is almost an exception at the present time to find descriptions of sound reproducing equipment without the appended descriptive adjective "Hi-Fi."

One of the most curious attributes attached to this label "high fidelity" is the emphasis placed on the ability of such equipment to reproduce the higher range of frequencies, curious because when the folded horn was introduced into the design of the gramophone, thus allowing a considerable extension of bass range of reproduction, and later when the moving-coil loud speaker and baffle still further extended this range, apparently nobody had the brilliant thought of labelling the new equipment as "high fidelity."

Bass reproduction having been obtained with some degree of success, attention was then directed to reproduction of those higher frequencies which play an important part in giving character to the tone character of individual instruments by reason of adequate coverage of a range of upper harmonics and ability to deal with those transients which are important in the accurate reproduction of certain instrumental effects.

## Limitations

Two basic difficulties arose when this improvement was attempted. In the case of the radio receiver, certain limitations were imposed by the frequency band normally transmitted by the BBC, and in the case of the record reproducer, needle scratch became horribly apparent and could not entirely be overcome by filters.

In the era when attention was focused on the reproduction of bass frequencies, our enthusiastic friends too often subjected us to demonstrations of "perfect" reproduction consisting largely of bangs, thumps and resonant booms! Since attention has been focused on the higher range, we are now subject to demonstrations which assault our ears with squeaks, screams, hisses, and noises often not far different from that piercing horror which sometimes occurs when a knife edge is accidentally drawn across a dinner plate.

The curious thing about this "high fidelity" reproduction, as so often demonstrated to us by enthusiasts, is that the enthusiast himself appears to be transfixed with the glory of the sounds emitting from the equipment, whereas his family appear to be equally transfixed with horror from the dreadful sounds filling the room.

Perhaps a great deal of this may be put down to excess of zeal and enthusiasm, and a perhaps not too full comprehension of what is really meant by high fidelity—so now let us look at another side of this problem by examining some of the components and

circuitry to which this label is from time to time attached. It is obviously impossible in the short space of an article of this nature to analyse such circuits or components, but the reader is invited to spend a few hours carrying out such an examination, and he may well wonder what the term "high fidelity" actually covers. As nobody has set down a definition for the term, it would perhaps be difficult to point an accusing finger in any particular case, and so confusion becomes even more confounded.

Taken literally, high fidelity would mean a high degree of faithfulness of reproduction.

## Aim Unobtainable

It is suggested that this idealistic aim is fundamentally unobtainable in most instances. A matter of individual taste even enters into the question—if you are attending a concert in the Royal Festival Hall it may please you to sit in one particular position rather than in another because you prefer the balance of tone of the music which you hear when listening in that position. When you receive the same concert either via a broadcast or via the medium of a record the broadcaster or the recorder has decided for you your physical situation when listening to the music.

Another curious characteristic of the high fidelity enthusiast is that in a considerable number of cases he is unable to give you a demonstration of the reality of his reproduction without turning up the volume to such an extent that your natural desire is to escape from the onslaught at the earliest possible moment. It is rather as though he desired to drive the possibility of any lack of concentration on your part beyond the realms of possibility, and this may possibly be in some way associated with the cacophony of noise hurled upon you by your local cinema at the commencement of a film. I have never discovered whether, in fact, this is done to make it impossible for you to have your mind diverted by conversation with your neighbour at this crucial moment, or whether it is produced as a form of musical mesmerism!

## A Definition

Any equipment carrying the label "high fidelity" should:

1. Be capable of accurately handling in their correct proportions those frequencies necessary to produce the characteristic tones of all those sounds it may be called upon to produce.

2. That the apparatus should be free from any cross modulation effects.

3. That at the volume at which it is required to be used the tonal balance can be adjusted to that most pleasing for the listener.

4. That it should not reproduce extraneous noises not present in the original performance.

# Programme Pointers



## "The Farmer of Sant' Agata"

**B**ELIEVE it or not, "The Farmer of Sant' Agata" was not the story of a farmer who enriched Italy with crops and herds of cattle and sheep, but the life of Giuseppe Verdi, one of the world's greatest musicians and operatic composers, who enriched not only Italy but the world with masterpiece after masterpiece. The title seemed an awful cliché, comparable to "the Bricklayer of Chartwell" or "the Premier of Poland." Surely "Caro Nome" or "Celeste Aida" would at least have had the merit of immediately directing the attention to the subject in hand, as well as being more poetical and romantic sounding.

But, cliché or no cliché, this biographical novel for the microphone based on the life and works of Verdi, by Spike Hughes, read by Felix Felton and produced by Michael Bell, and in five weekly instalments, each an hour's programme, was truly first class and wholly admirable. I rank it the best thing, at any rate of its kind, for months, and easily Spike Hughes' top achievement to date. The story was well told, the parts interestingly balanced, whilst the whole was bound together with a remarkable collection of gramophone records of excerpts of the glorious music.

May we have from Mr. Hughes' pen the fabulous story of Wagner, with the Wagner, Bulow, Cosima triangle unvarnished and the King Ludwig saga complete? Here would be radio entertainment *in excelsis*. We should have the I.T.A. in full pelt after it for exclusive rights!

Two appearances of Sir Thomas Beecham at the Proms—again, happily, a year distant—produced a volume of applause which made one wonder whether the applauders were not starved of good music adequately performed!

Two programmes, each also of an hour's length, "Prelude to War," dealt very much in the manner of the recent Wickham Steed talks with the origins of the two world wars of our time. One felt that we were only being told what good children were wanted to know. For this child at any rate, I already knew everything that was in the programmes and a good bit more. But then I never was a good child. The programmes themselves imparted nothing new. That was not the fault of either the late Professor Temperley or Sir Lewis Namier, the compilers. The programmes had nothing new to convey, but were very well done and very interesting.

## Plays

I thought the best play of the month was not a "play" at all, but the radio version of Ivan Goncharov's "Oblomov." A wonderful story of a universal character, as all great books should be about. Oblomov is that person, the laziest person in the world who dodges all life's problems and crises, only to

## Our Critic, Maurice Reeve, Reviews Some Recent Programmes

make the best of the baby he is left to carry. The play effectively began with the hero being dragged out of bed and ended with him getting back there to end his story. Robert Eddison was most effective and convincing as Oblomov, Barbara Couper as the girl he lost (although she was wholly "in the bag," as they say) and Susan Richards as the one he gained.

"The Doctor's Dilemma" needs little comment. Even the author's name is too famous to require citation. Jack Allen as Sir Colenso, the Doctor, Maxine Audley as Mrs. Dubedat and Cyril Cusack as Louis Dubedat headed the cast, all of whom put over the play's wit and philosophy with gusto and conviction.

The current serial, "Martin Chuzzlewit," is proceeding with great success. The series of immortal characters are parading before us in all their glory and with great effect.

"Golden Rain" was a pleasant offering from the pen of R. F. Delderfield. A financially harassed country parson is scandalized and morally outraged when he learns that his wife and his cook are sharers in a good slice of the Treble Chance pool. That they have been regular competitors in secret from him only makes his feelings all the more poignant. But religion and love are cleverly reconciled and Ivan Sampson, Ivan Brandt, Rachel Gurney, Kathleen Helme, etc., were very good.

Neville Shute's novel, "No Highway," dealing with the overworking of aeroplanes and their almost certain doom, made good Saturday Night Theatre material for the second time. So did "Random Harvest," James Hilton's story dealing with a first war casualty who loses all recollection of a part of his life until it is brought back by his being cleverly taken to a romantic spot. "Saturday Night Theatre" should be renamed "The Saturday Night Book Club."

## Personal Call

The Saturday evening Sports Report has started one of the silliest imaginable minor features, Personal Call. In return for answering a truly babyish question the correspondent is rewarded, amongst other alternatives, with a microphone appearance. The first question I heard asked was "who won last year's England v. Scotland soccer international?" But, incredible as it may sound, the gentleman, presumably a football fan, else he wouldn't be taking any interest in this particular programme, did not know.

# 'CHIMELITE'



**CHIMELITE**  
It is a hall light as well as a chime and you can make it in a couple of evenings for the total cost of only 19/6, including instructions, Post, etc. 2/-. Data available separately price 2/-.



## CHASSIS ASSEMBLY

3 colour, 3 waveband scale covering standard Long, Medium, and Short wavebands, scale pan, chassis punched for standard 5 valve superhet, pulley driving head, springs, etc., to suit. Scale size 14in. x 31in. Chassis size, 15in. x 5in. x 21in. deep. Price 15.-, plus 1/6 post.

## TABLE RADIO CABINET

Very fine cabinet, size approx. 16 x 16 x 7—walnut veneered and satin finished. 39/6, carriage and packing 3/6. This cabinet is the correct one for the chassis above.



**226 FLUORESCENT LIGHTING**  
40 WATT.  
Kit comprises 40 watt control unit, starter lamp, lamp holders, clips and wiring diagram. Price, less tube, 22/6, plus 1/6 post. With tube, 30.-, plus 3/6 carriage and insurance.

## BE PREPARED



for a cold winter by making our low cost Electric Blanket. 27 yards of heater wire and blueprint. 20/-, Blueprint only 1/6. Alternatively make a Bed Warmer Constructional Data. 1/6.

## CABINET 19/6



You can make an excellent bass reflex cabinet with this well-made veneered and polished walnut cabinet. Limited quantity offered at 19/6. Carriage, etc., 3/6.

## THIS MONTH'S SNIP A.C.D.C. THREE, 19/6



A remarkable bargain (mains operated). Totally self-contained powerful receiver for Long and Medium waves. All parts including valves, coils, resistors, etc., but not loudspeaker and cabinet will cost you only 19/6, post, etc., 1/6. Data available separately 2/-, post free.

## TWO NEW CABINETS THE BUREAU

This is a really beautiful cabinet elegantly veneered in walnut and finely polished. The control board, revealed when the front is dropped down is ample for the larger than average radio chassis or amplifier and alongside there is a space for a tape recorder or auto record changer mechanism. Both the radio board and the control board are left uncut to suit your own equipment, high, 12in. wide, and 16in. deep. Price £16.16.0. Carriage 12/6.



Size approximately 30in. high, 12in. wide, and 16in. deep. Price £16.16.0. Carriage 12/6.

## THE CONTEMPORARY

Also in the modern trend is this very stylish contemporary console. Veneered in oak with contrasting mouldings this has the "G" plan look and is ideal for use with this furniture or with other contemporary fittings or furnishings. The radio and motor board is again uncut and its size 30in. x 15in. provides ample room for all equipment. Price £8.15.0. Carriage, etc. 12/6.



## TAPE RECORDINGS

### ULTRA MODERN TAPE DECK

The latest Trivox incorporates every modern refinement plays H.M.V. and other pre-recorded tapes. Has azimuth head adjustment 50-10,000 c.p.s. response Provision for foot control (dictating letters, etc.) is undoubtedly one of the best tape decks available today. Price £23.0.0. Hire Purchase terms if required. Send a deposit of 15% or more, balance spread over 12 months. Carriage and insurance 10/-.



IN PLENTY OF TIME FOR THESE


## CLEVELAND WIDE-BAND TAPE AMPLIFIER

Trivox co-operated in designing this amplifier and fully approve it. Two separate inputs for mixing programmes. Suitable for radio recordings from crystal set or tuner, crystal or magnetic microphones or pickups. Magic eye indicates depth of recording. 4 watt amplifier—uses five midjet valves—powerpack on separate chassis. Price £15. Hire Purchase terms if required, deposit no less than 15%, balance spread over 12 months. Carriage and insurance 7/6.

## FINE MODERN RADIO
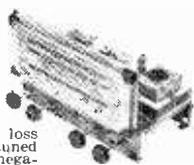
### THE CLEVELAND ORGANTONE

5 valve 3 waveband superhet covering Long, Medium, and Short waves—built to attain highest performance of sensitivity, fidelity and output.—Osram miniature valves—low loss iron coils—permeability tuned I.F.S.—full A.V.C.—variable negative feed-back—gram. position on wave change switch—4 watts output—particularly fine tone especially on gram. Chassis size 7 7/8 approx. scale size 4 1/2 x 4 1/2 approx. Tested in difficult valves where exceptional results have been obtained. Price £11.10.0, or £3.16.0 deposit. Carriage, etc. 7/6.



## MAKE IT YOURSELF AND SO SAVE 25-30%

All parts assemble perfectly into professional portable cabinet. Send for constructional booklet today. Price 2/-.



## INFRAY LAMP

Means real comfort in bed as it emits Infra Red Rays which warm and keep you healthy.  
● Economical.  
● Costs only 1d. per hour (electric at 1d. per unit).  
● Absolutely safe, no health or fire risk.



Price 36/-  
Post & Pack. 2/-  
● Ideal for many other uses—over pet's basket, rearing pup, chicks, over desk, work bench, etc. ● All complete and ready to work

## SELECTIVE FEED-BACK AMPLIFIER



A.C. mains 3 valve amplifier with independent bass and treble controls to vary negative feed-back. Completely made up and ready to work. Price £4.19.8. plus 2/6 post. Demonstrations gladly at all branches.

## EVERLASTING GRAMOPHONE NEEDLES

Jewel (Sapphire) pointed, suit any type of pick-up, precision made—improves quality, eliminates record wear. 3 types. Hard, soft, trailer. 2/6 each.



## MULLARD AMPLIFIER

A high Quality Amplifier designed by Mullard engineers. Robust, high fidelity, with a power output extending 10 watts and a harmonic distortion less than 4% at 10 watts. Its frequency response is extremely wide and level being almost flat from 10 to 20,000 C.P.S.—three controls are provided and the whole unit is very suitable for use with the Collaro Studio and most other good pick ups. The total cost of the amplifier is around £11. For 30/- extra a unit completely made up and tested can be supplied. Carriage in either case is 10/- extra. Data will be provided with all orders for components. Send for the Mullard Amplifier Shopping List."

## ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 7, RUISLIP.

Personal shoppers, however, can call at :

42-46, Windmill Hill, Ruislip, Middx.  
Phone: RUISLIP 5783  
Half day, Wednesday.

152-3, Fleet Street, E.C.4.  
Phone: CENTRAL 2633  
Half day, Saturday.

29, Stroud Green Road, Finsbury Park, N.4.  
Phone: ARCHWAY 1049  
Half day, Thursday.

**BENTLEY ACOUSTIC Corp., Ltd.,**  
38, Chalcot Road, N.W.1. PRImrose 9090.

0Z4	6/-	68N7	8/6	42	8/-	H30	5/-
1A5	6/-	6U5(UX)	7/-	42Mpt	15/-	HL1320	8/-
1D6	8/6	6U7	8/6	43	8/6	KP35	8/6
106	6/6	6Y6g	7/-	57	8/6	KP7	6/-
114	6/-	6X4	7/6	58	8/6	KW62	5/-
11D5	4/6	6X5	7/-	72	4/6	KW63	6/6
11L5	4/6	6Z4	6/-	78	7/-	KZ63	6/6
1R5	7/-	7C5	7/6	77	8/-	K766	12/6
1J5	7/-	7C6	7/6	83	8/-	MH4	5/6
1T4	7/-	7D8	6/-	85A2	10/6	Mospen	5/-
21130	4/-	7H7	7/6	807	7/6	Mrsyuo	7/6
2X2	4/6	7Q7	8/-	955	5/-	N77	6/6
3D6	2/6	7R7	8/6	9763	8/-	N78	10/6
3Y3	10/-	787	7/6	9902	5/6	OM5	7/6
5U4	8/-	812	2/6	9903	5/6	PEN40	7/6
5Y5	7/6	912	3/-	ACT23	10/6	PL39	18/-
6A4	8/6	16C2	10/6	AL60	4/6	PL81	10/-
6A7	8/6	10R1	10/-	AP4	7/6	PL82	10/-
6AB7	6/-	10P13	10/-	ATP4	3/-	PM12	4/-
6AC7	6/6	1113	6/-	B163	7/6	PM12M	7/6
6AK5	7/6	12A5	6/6	CBLL	17/6	PY30	10/-
6AM5	6/6	12A17	7/6	CB37	8/6	PY82	8/6
6AQ5	9/-	12AT7	7/-	EAS0	1/6	Q230	8/-
6AT6	8/-	12AU7	9/-	EAC01	9/-	Q7020	10/6
6BA6	6/6	12AX7	7/-	EB34	1/6	QV647	10/6
6BP6	6/6	12BE6	6/6	BH81	6/-	RM4	12/-
6BR6	6/6	12C8	7/6	BHC33	7/6	SH4	7/6
6BW3	7/6	12E1	30/-	EC93	7/-	SP61	2/6
6C6	6/6	12H6	3/-	ECC35	9/-	SL30	5/6
6CH6	6/6	12J5	6/-	ECC35	9/-	SP41	2/6
6CI6	6/6	12K8	8/6	ECC81	9/-	TP22	8/6
6FI	10/-	12K37	7/-	ECY31	7/6	TAR42	12/-
6F17	9/6	12K47	6/6	ECY42	10/6	UR21	12/6
6F33	9/6	12N07	8/6	EP36	4/6	UF41	9/-
6H04	2/6	12N87	7/6	EP39	6/6	UL41	9/-
6J58	5/-	12Z3	8/6	EP50E	5/-	UG6	10/6
6J6	7/6	1311	8/-	EP50A	8/-	UY41	9/-
6J7E	5/-	1417	10/6	EPY1	5/-	UZ39	10/6
6K52	8/6	1417	10/6	EP80	10/6	U403	10/-
6K74	5/-	1519	4/-	E12	11/6	V22	8/6
6K82	8/-	18	8/-	EL32	6/6	V22B	10/6
6L7R	7/6	16H1	10/-	EP91	6/6	V4	8/6
6N7G	7/6	15114	35/-	EL38	20/-	V22	6/6
6Q7	8/6	20L	11/6	EL51	6/6	V41	7/6
6R7Z	8/-	25L6	8/6	EM34	10/6	V83	5/-
6SA7	6/6	30	7/6	ET51	11/-	VR150	8/6
6SH7	5/6	30L1	11/6	ET91	7/6	VT501	6/-
6SK7	6/-	35L16	8/-	FC2	10/6	X24	10/6

See classified ad. on page 766.

Post 6d. each. 24 hour C.O.D. service. All guaranteed. Complete list free S.A.E.

**NEW 48 PAGE**  
RADIO AND TELEVISION  
COMPONENT CATALOGUE  
available free on request to  
**J. T. FILMER,**  
MAYPOLE ESTATE, BEXLEY, KENT  
Tel: Bexleyheath 7267

Introducing the: —  
**TYANA TRIPLE THREE**  
MAKE SOLDERING A PLEASURE  
SMALL  
SOLDERING IRON  
Complete with detachable  
BENCH STAND 19/6  
The smallest high-power  
soldering iron. Length  
only 8 1/2"; adjustable long  
bit dia. 3/16"; mains vol-  
tages 100/110, 200/220,  
230/250.  
The "STANDARD"  
Popular Soldering Iron  
now reduced to 14/11.  
Replacement Elements and  
Bits for both types always  
available.  
**KENROY LIMITED**  
152/297 UPPER ST.,  
ISLINGTON, LONDON,  
N.1.  
Telephone: Canonbury 4905-4663  
Reg. Desig. No. 867804

**20**  
CIRCUITS  
for 2/6 only  
**ENLARGED AGAIN!**  
Our Super-Handbook, "The Home Constructor" with its supplements (68 pages altogether) now incorporates  
\*20 CIRCUITS—Superhets, T.R.F. Sets, Amplifiers, Feeder Units, Test Equipment, etc.  
\*SUPERBETS—Full constructional details, fully simplified diagrams for building a variety of superhets.  
\*COIL PACK—Full constructional details for a superhet coil pack  
\*CAR RADIO—Full constructional details  
\*RADIO GEN—Pages of information, Resistance Colour Code, Formulae, and know-how.  
\*RADIO CONTROL—Supplement with theoreticals, etc.  
\*RADIOGRAM Supplement.  
\*INFORMATION LETTERS—The latest issues of our popular Information Letters.  
\*CATALOGUE—Profusely illustrated catalogue and price list of components.  
**YOU CAN'T GET BETTER VALUE! IT'S TOPS!**  
The most helpful book in the trade.  
SEND FOR A COPY TO-DAY  
**SUPACOILS (Dept. P.12)**  
21, Markhouse Road, London, E.17

**TELEVISION**  
The advance of Radio Technique will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook. Full details are given of A.M.Brit.H.R.E., City & Guilds Exams, and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc. We guarantee "NO P.A.S.S.—NO FEE." Prepare for to-morrow's opportunities and future competition by sending for this very informative 144-page guide NOW—FREE and without obligation.  
**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**  
(Dept. 242), COLLEGE HOUSE,  
29-31, Wright's Lane, Kensington, W.8

Build a really portable Tape Recorder with the New  
**"CHALLENGER"**  
Three Speed High Fidelity Tape Deck.  
A first-class precision built deck. Beautifully finished in Old Gold stone enamel. Size only 11in. x 7 1/2in. Weight 6 lbs.  
Britain's lowest priced Tape Deck.  
**Price £10.10.0.**  
Ask your dealer or send stamp for details to:—  
**E.W.A.,**  
266, Warbreck Drive, Blackpool.

**CYLDON 5-CHANNEL TV. PRE-TUNER VALVES.** 6BW7 and 12A17. Fit one of these to your set for better pictures. 52/6. Less valves. 15/-.  
**SPECIAL OFFER.** New and boxed AR1P/VP23 valves. 5/6 each. 4 for £1  
**TYPE 6c "SCROPE" UNIT** with VCR 138/31in. C.R. Tube, etc., and Conversion Circuit, 58/6.  
**FISHING ROD AERIALS.** 12ft. Set 3/7/6. Mounting Base, 3/6.  
**0/5 AMPMETERS,** 2 1/2in. square M/c, 11/-.  
**GERMANIUM DIODES,** 3/9.  
**FREQUENCY CRYSTALS,** 9.100 and 4.500 Kc., 10/6; 4.860, 4.800 2.400, 594, 561, 550, 559 Kc., 6/6. 1in. Space Pins.  
**SELENIUM RECTIFIERS,** F.W. 6 or 12 V. 4 A., 22/6; 6 A., 30/-; 3 A., 14/6; 100 mA., 3/6; 1 A., 8/6; 24V. 2 A., 30/-; 250 V., 100 mA. H.W., 9/-; 250V. 275 mA., 17/6; 250 V., 60mA., 6/6.  
**TRANSFORMERS,** 20-240 volts, tapped 3-4-5-6-8-12-15-18-20-22- and 30 volts at 2 A., 21/6. Tapped 17-11-5 volts 5 A., 22/6; at 17-11-5 volt 1 1/2 A., 16/6; 6.3v., 2 1/2 A., 8/6. One year guarantee.  
**M/C MICROPHONES AND TRANSFORMERS,** 15/6.  
**EX-W.D. PHONES.** Low Resistance, 9/6. New OAK 6V. 4-pin Vibrators, 10/6.  
**MORSE KEYS,** 3/-.  
**BUZZERS,** 3/-.  
**24V. BLOWER MOTORS,** 14/6. A.C./D.C. CARBON TWIST DRILLS. Sets of 6. 1/16th to 1/4 or 1/16th to 3/16ths, 3/6.  
**U.I.F. AERIALS,** 190-200 Mc/s. covering band, complete with case, 6/6.  
1 amp. overload switches, 3/6.  
**TR1196.** Transmitter Section. New and complete. 4.6/8 Mc/s. Easily converted. Less valves, 15/-; with valves, £2.  
Throat Microphones with cord, 4/-.  
**ALL POST PAID IN U.K.**  
**THE RADIO & ELECTRICAL MART**  
253b, Portobello Road, London, W.11  
Phone: Park 6026.

**TELETRON SUPER INDUCTOR COILS**  
Originators of Type HAX, selective Xta, diode coil, as Radio unit in Tape and quality Amplifiers, 3/- ea. Dual wave TRF coils (illustrated), matched pair, 7/-.  
**FERRITIC** frame Aerials, MW. 8/9; Dual wave, 12V. E.C.O. Coils, IET's, etc. Stamp for list and circuits. The Teletron Co., Ltd., 268, Nightingale Road, London, N.8. HOW. 2527

**SPARKS' DATA SHEETS**  
**SHORT WAVES**  
All-dry Battery operation. Simplified Band-Spread Tuning. Latest Eddystone Plug-In Coils down to 10 Metres. High-Efficiency Pentode Detector Circuits with Dual Control Reaction Circuit, Thoroughly Tested.  
No. S/W.DX.1. Single Valve.  
No. S/W.DX.2. Two-Valver. (Det., plus pentode output).  
Full-Size Simplified Data Sheet, showing every detail, plus Descriptive and Operational Instructions, 2/6 each, plus 21d. stamp  
**NEW MULLARD AMPLIFIER**  
The 27in. x 22in. Data Sheet shows in detail my version of a Tested Practical LaYout, together with descriptive matter and all values, Etc., Etc., of this outstanding Mullard circuit. The ideal design for the quality enthusiast. Chassis and all parts available. Data Sheet, Etc. 3/9 Post Free.  
**MANY OTHER DESIGNS AVAILABLE**  
Send 21d. stamp for Latest List.  
**COMPONENTS AND DRILLED CHASSIS SUPPLIED**  
**L. ORMOND SPARKS (P),**  
8, Courr Road, Swanage, Dorset.

# Open to Discussion




## Magnetic Braking

SIR,—I have recently built a tape desk with magnetic braking as described in the article "Magnetic Braking on Tape Recorders," PRACTICAL WIRELESS, January, 1953, page 41. The circuit you give can be simplified, however, by eliminating the relay and the rather inconvenient 6 volts D.C. supply. The circuit of my modification, which has proved to be satisfactory, is appended.

The D.C. braking supply is distributed appropriately by the fourth wafer of the rotary switch.

The brakeswitch used was a push-button opening the A.C. and closing the D.C. circuit on pressing. A switch similar to the on/off switch "A" could, however, be used. In the off position, the switch "A" passes D.C. to the spool motors when the rotary switch is turned to the position shown in the diagram. This locks the spools and is useful for tape-threading. No harm

*Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.*

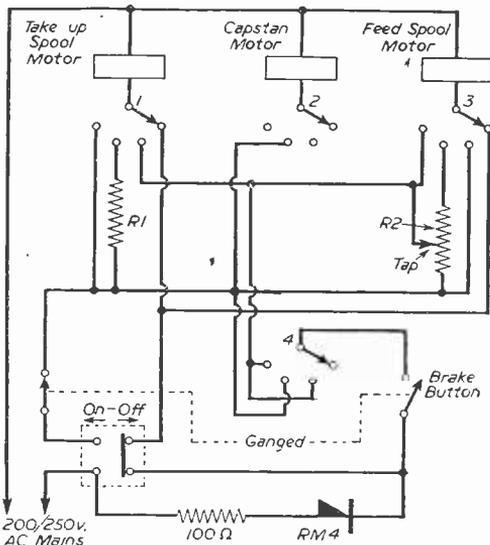

Mr. Johnson's revised magnetic breaking circuit.

is done if switch "A" is pressed as the D.C. is then switched off.

The values of the resistors R1 and R2 were found by experiment; both were about 1,000 ohms. A tap on R2 eliminates a third resistor.

The smoothing condenser in the original circuit was omitted as the smoother D.C. was found to be unnecessary.—

R. P. C. JOHNSON (St. Albans).

## Series Modulation

SIR,—Much has been said, written and thought about modulating a P.A. stage, but I haven't seen a thing about series modulation. It seems to me that if you wish to anode modulate a 150 watt P.A. stage you will have to pay out terrific sums for assorted chokes *ad infinitum*. But in S.M. you will need only a single good choke and a couple of high wattage carbon resistors. A point against it is, however, that you need approximately double the original voltage, but with surplus or otherwise mercury vapour rectifiers that causes very little trouble.


Another point is, why are we restricted to 150 watt I.P.? With some of the surplus valves on the market it is possible to have 200 watt modulated carrier. Two VT104s in push-pull, for instance, with a voltage of 1,250, Ia of 250 mA gives 200 watt carrier and I expect there are a good many others in P.P. or otherwise which would double this figure for carrier O.P. above. Why can't the P.M.G. let us have high power stations?—  
C. MCLEAN (Stoke Poges).

## Changing Listening Conditions

SIR,—As a radio enthusiast I have taken PRACTICAL WIRELESS and your other publications for many more years than I care to remember, although this is the first occasion that I have entered into correspondence. What has prompted me to do so now is the changing and worsening conditions of reception on the medium broadcast band. I am, of course, aware that within the next two years we shall have F.M. and V.H.F. reception which will represent an incalculable change and result in extremely good quality reception.

There are, however, many snags. On these bands we shall be confined to listening to programmes from a local station with a choice of three programmes. For the reception of short and medium wave stations it will still be necessary to retain the present known type of receiver—which, in my opinion, should preferably be an entirely separate unit, although a compromise might be made to connect it to a common amplifier.

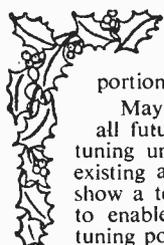The tendency nowadays to build separate tuning units, pre-amplifiers-cum-tone control stages and a main amplifier is a step in the right direction, particularly to an amateur constantly making changes in equipment. It is frequently necessary to alter, rebuild or to construct an entirely new tuning unit which,



with this type of assembly, can be accomplished without alteration to the units succeeding the receiver portion.

May I suggest, therefore, in respect of all future receivers published in which the tuning unit might usefully be used with an existing amplifier that designs should clearly show a termination after the detector stage to enable constructors to make use of the tuning portion of the receiver without having recourse to building the complete set. It is appreciated that this represents no difficulty to the advanced and experienced constructor, but I am sure it would be welcomed by others not possessing the requisite knowledge.

In order to meet present-day conditions, including widespread interference from adjoining stations and television receivers, we have not yet had a design published which includes all features now and in the future more than ever necessary. What I should like to see in PRACTICAL WIRELESS is a receiver with a really elaborate specification.



#### Mains Surges

SIR,—I have been reading with interest the article "Mains Supplies for Battery Valves" in a recent number, and would like to mention that I have solved the problems of surges, etc., mentioned by your contributor in a far simpler way, with many fewer components, by using the circuit on right. The principle of using a power valve as a grid-controlled rectifier is a most useful one for all kinds of supplies, and deserves to be far more widely known than it appears to be.

Assuming 50 mA for the filament chain and, say, 12 mA at 90 volts for the anode supply V may be any indirectly heated output valve capable of the required emission of 62 mA, and will be conductive on alternate cycles. The transformer can be of any type so long as the secondary provides 250 volts or more at the current needed. P is a wire-wound potentiometer of 25 kΩ or 50 kΩ, of which the slider takes off a suitable bias voltage for the grid. The smoothing can be adequate since C2 and C3 need only be of 120 volt working. R1 C1 form a filter in the bias circuit and may be omitted for extreme simplicity and cheapness. R2 drops the volts necessary to run the filament drain from 90 volt. A low-voltage electrolytic condenser may be wired across the chain, but this again is not vital. I have omitted the shunt

resistors in the chain for the sake of clarity.

The slider of P is adjusted so that with the load connected the voltage in the anode line is 90 volt. When switching on the mains the high and low volts rise gradually owing to the time taken for the cathode of V to warm up, and both reach the working figure together. There can be no surges above this figure. When switching off the supply to the rectifier is cut off instantly, and the only energy remaining in the circuit is that stored in C2 and C3, which cannot

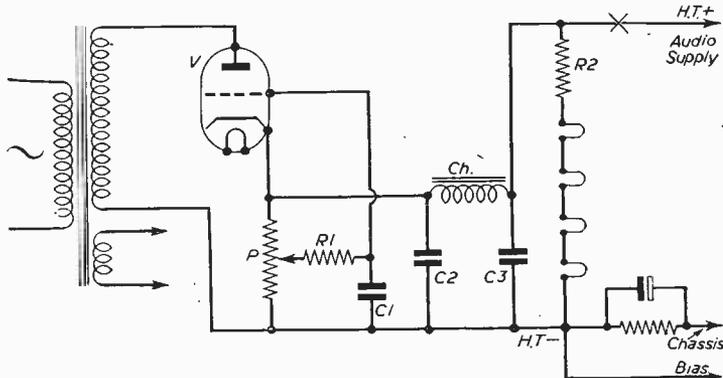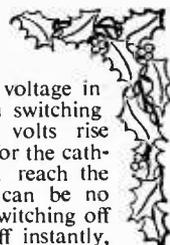

The heater arrangement recommended by Mr. Guest.

rise above 90 volt, so owing to the comparatively heavy drain of the filament chain the H.T. will have fallen to a very low figure by the time the filaments have begun to cool off. Should the filament chain fail while running or at any other time the self-compensating action of the cathode follower arrangement of V will prevent the rectified voltage from rising to a figure likely to cause any harm—it may go as high as 110 volt—but it is absolutely essential that the H.T. should not rise above 90, it is a very simple matter to include in the filament chain the coil of a relay which will break the anode supply to the set at X if the filament current falls too low.

For mains use a mains on/off switch is all that is necessary. For mains-battery use only the simplest of change-over switching is needed.—(Rev.) S. A. R. GUEST (St. Stephen-by-Saltash).

#### Modifying R1132A

SIR,—I have seen much written in "Open to Discussion" on modifying the R1132A, but after obtaining one of these sets I find I can only receive one station and I would like to know if any of your readers can offer any advice as to how I may improve this?—R. W. HILTON (8, Hogshill Lane, Cobham, Surrey).

Editorial and Advertisement Offices:  
 "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4368.  
 Telegrams: Newnes, Band, London.  
 Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

**EX-A.M. RECEIVER TYPE R.1155**



5 Frequency ranges : 18.5-7.5 Mc/s ; 7.5-3.0 Mc/s ; 1,500-600 kc/s ; 500-200 kc/s ; 200-75 kc/s. Supplied in maker's original wood transit case.

**LASKY'S PRICE**

BRAND NEW. £11.19.6.  
Secondhand. Grade 1. £9.19.6  
Secondhand. Grade 2. £7.19.6  
Carriage 17/6 extra, including 10% returnable on packing case.

**ASSEMBLED POWER PACK/OUTPUT STAGE FOR R.1155 RECEIVER**

For use on 200-250 v. A.C. mains. Complete with 2 valves. In metal case size : 12 x 7 x 5 1/2 ins. LASKY'S PRICE 79.6. Carr. 5/- extra.  
Power Pack as above. Fitted with 6 1/2 in. p.m. speaker. LASKY'S PRICE. £55/- Carriage 5/- extra.

**SPECIAL OFFER TAPE RECORDING HEADS STAGE "FIDELITY"**

High impedance, single hole fixing. Twin track. Record/Playback ... 22/6  
Erase ... 22/6  
Low impedance erase 22/6  
Limited quantity only. Size 1 1/2 in. diam., 1 1/2 in. high. FAR BELOW ACTUAL MANUFACTURING COST. LESS THAN HALF USUAL PRICE.

**BAKER'S SELHURST SPEAKERS**

"Stalwart" 12in. 15 ohms impedance. Frequency response 30-13,500 c.p.s. Power handling capacity 15 watts, peak A.C. PRICE £5 10/-  
"Standard" 12in. 15 ohms impedance. Frequency response 30-14,500 c.p.s. Power handling capacity 20 watts, peak A.C. PRICE £5 10/-  
"De-Luxe" 12in. 15 ohms impedance. Re-entry cone. Frequency response 18-17,000 c.p.s. Power handling capacity 15 watts, peak A.C. PRICE £8 10/- Carriage 3/6 per speaker extra.

**RESIN CORED SOLDER.** 7/6 per 1-lb. reel.

**L. & M. WAVE R.F.F. COILS.** With Circuit. 4/6 pair.

**L. & M. DUAL WAVE Superhet Coils.** Aerial and oscillator 5/11 pair.

**100K. CARBON POTENTIOMETERS.** Less switch. SPECIAL OFFER. 1.6 each.

**I.F. TRANSFORMERS** MINIATURE. 4 x 1 1/2 x 1 1/2 ins. PRICE 10/6 pair.  
WEARITE TYPE 550. 445-520 kc/s. 8/6 per pair.  
WEARITE TYPE 500. 450-470 kc/s. 8/6 per pair.

**PLASTIC ESCUTCHEON MASKS** With dark screen filter.  
12in. ... 12/6  
10in. ... 25/6

**BRIWISTORS** Type CZ.1, 1/6 each. CZ.3, 10/4d. each or 9/- doz.

**3-WATT MIDGET AC/DC AMPLIFIERS PUSH PULL VERY HIGH GAIN**

4 valves : 2 6U41 in push pull, 1 6U42 and 1 6U4F42. Input voltage 100-110 A.C./D.C. Very easily converted to 230 volts. Supplied with circuit diagram and full details. Size : 9 x 4 x 4 ins. Uses 2 metal rectifiers, 1 each RM1 and RM2. Ideal for ships' record players, tape recorders, home record players, baby alarms, etc., etc. Supplied complete, fully assembled and wired, with 4 valves, 85/- POST FREE.



**GANGED TUNING CONDENSERS .0005 MFD.**

Standard 2-gang. Size : 2 1/2 x 1 1/2 x 2 1/2 in. 1in. Spindle.....	5/-
Standard 3-gang. Size : 2 1/2 x 1 1/2 x 3 1/2 in. 1in. Spindle.....	7/6
Midret 2-gang with trimmers. Size : 1 1/2 x 1 1/2 x 2 1/2 in. 1in. Spindle.....	7/6
Midret 3-gang with trimmers perspex cover. Size : 1 1/2 x 1 1/2 x 2 1/2 in. 1in. Spindle.....	12/6

**A COMPLETE 5 VALVE RADIO CHASSIS.**




Brand New and Unused. AC/DC. Mains. 200.250 volts. \* I.F. 465 kc/s. \* A.V.C. \* 4 Watts output. \* 3 Station Pre Set. \* Frame aerial. \* Fully aligned. \* Chassis size only 10ins. x 5 1/2 ins. Max. height 5 1/2 ins. Completely wired and ready for use with the addition of a speaker and output transformer Two controls—Volume and Station switch. Valves used : 10C1, 10F9 or UF41, 10LD11, 10P14, U404 or UY41.

LASKY'S PRICE 69/6 less Valves. Postage 3/6 extra.

PRICE COMPLETE. £5.19.6

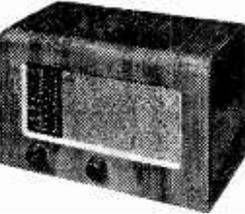**RADIO CABINETS**

Size : 12ins. wide, 6ins. deep, 8ins. high. Finished in medium walnut veneer, with high polish. Complete with back, chassis and dial. LASKY'S PRICE.....16/11 Carriage 2/6 extra.



WE HAVE PLEASURE IN OFFERING YOU HIRE PURCHASE TERMS ON CERTAIN ITEMS. Down payments can be arranged to suit yourself. Send us details of your requirements.

**THE TELE KING**

**5 Channel 16 or 17 inch SUPERHET RECEIVER**


This famous and well tried home constructor set can now be built for £29/10/-. Tube and 1 cabinet extra.

**EVERY COMPONENT CAN BE SUPPLIED SEPARATELY.**

Full constructional data, wiring diagrams and circuits.

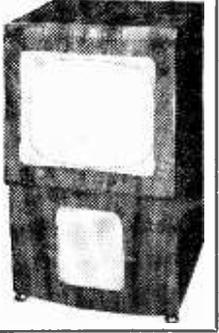**PRICE 6/- POST FREE**

WRITE NOW FOR OUR NEW TELE KING PRICE LIST. WE CAN SAVE YOU MONEY.



**LASKY'S RADIO,**

LASKY'S (HARROW ROAD) LTD., 370, HARROW ROAD, PADDINGTON, LONDON, W.9. Telephones : CUNningham 1979-7214.

Hours : Mon. to Sat. 9.30 a.m. to 6 p.m. ; Thurs. half day. 1 p.m. Postage and packing charges (unless otherwise stated) : on orders value £1-1s. 0d. extra : £5-2s. 0d. extra : £10-3s. 6d. extra ; over £10 carriage free. All goods fully insured in transit.



**CRYSTAL DIODES**  
Wire ends. Glass.....1/6  
Type WX.6. Wire ends.....1/6

**TELESCOPIC PORTABLE AERIAL MASTS**  
Made of lightweight but extremely strong alloy. Extends to 15ft. Guyed at top and centre. Supplied complete with all guy lines.  
LASKY'S PRICE ..... 25/- Carriage free.

**R.F. 25 UNITS.** Complete with 3 valves. New 19/6. Secondhand 15/-. Carriage 2/6. each extra.

**SUPERHET COIL PACKS** With Circuit  
No. 1. L.M.S.G. Size : 4 1/2 x 5 x 2 1/2 ins. With 1in. spindle.....19/6  
No. 2. M.S.S. Size : 4 x 4 x 3 1/2 ins. With 1in. spindle.....16/- Both for use with 465 kc/s I.F.


**LOUDSPEAKERS**  
First Quality. All 3 ohms speech coil. Less output trans.  
5in.....14/8 8in. ....19/11  
6 1/2in.....15/- 10in. ....19/6

**ENERGISED SPEAKERS**  
8in. With O/Trans. 600Ω.....15/6  
8in. Less O/Trans. 600Ω.....12/6  
8in. Less O/Trans. 1,200Ω.....12/6  
6 1/2in. With O/Trans. 600Ω.....14/-

**TELEVISION SELENIUM RECTIFIERS**  
The very latest "Sentencer" S.T.C. range.  
K3/40, 3.2 kV..... 6/-  
K3/45, 3.6 kV..... 8/2  
K3/50, 4.0 kV..... 8/8  
K3/100, 8.0 kV..... 14/6  
K3/160, 12.8 kV..... 21/6  
K3/200, 16 kV..... 26/-

**METAL RECTIFIERS**  
6 and 12 volt F.W.  
2a. ... 9/- R.M.1 ... 3/10  
3a. ... 9/11 R.M.2 ... 4/3  
4a. ... 12/- R.M.3 ... 5/-  
6a. ... 19/6 R.M.4 ... 16/-  
12 Volt  
1 amp. 2/6 1/2 amp. 3/11  
1 amp. 4/6 1 amp. 6/6

**CYLON 5-CHANNEL SWITCHED TELETUNERS**

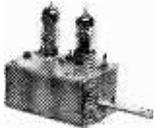


Instant and positive selection of any one of the 5 B.B.C. television channels, by a single control knob. Uses EF.80 R.F. pentode and ECC81 or 12AT7 Double Diode Triode as frequency changer. Tuning by switching incremental inductances. Size : 4 1/2 x 2 1/2 x 2 1/2 ins. Spindle 2 1/2 ins. long. 1in. diameter. I.F. Output 9.5-13 Mc/s. noise figure better than 10.5dB. I.F. rejection better than 45dB. on all channels. Power gain 24dB.  
LASKY'S PRICE.....12/6 Post free.  
Valves for tuner available, at 12/6 each.

**AERIAL ROD SECTIONS.** Steel, heavily copper plated. 12ins. long. 1in. diameter. Any number may be fitted together. PRICE 2/6 per doz. Post free.

THE THREE-IN-ONE TOOL FOR ALL RADIO ENTHUSIASTS

# Bib Wire Stripper and Cutter

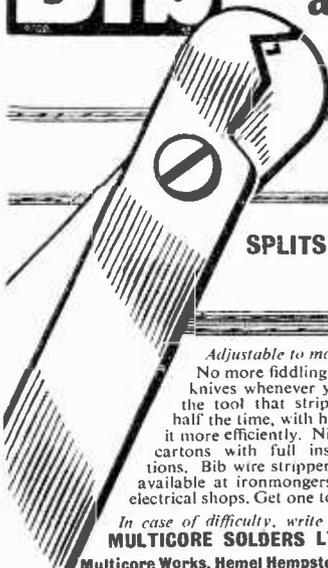

**CUTS** wire cleanly

**STRIPS** insulation

**SPLITS** plastic extruded flex

Adjustable to most wire thicknesses.

No more fiddling with razor blades or pen-knives whenever you make a joint. Here's the tool that strips, cuts and splits flex in half the time, with half the trouble—and does it more efficiently. Nickel plated and packed in cartons with full instructions. Bib wire strippers are available at ironmongers and electrical shops. Get one today.

In case of difficulty, write to —  
**MULTICORE SOLDERS LTD.,**  
Multicore Works, Hemel Hempstead, Herts. (Boxmoor 5636)

**3/6**

## S. R. S.



### The "SUPERIOR FOUR"

4-Valve T.R.F. Receiver  
Long and Medium Wave

Building cost approximately

**£7. 5. 0**

Plus 3/6 post and packing.

Smart looking, outstanding performance, very popular

with home constructors. Circuit latest type T.R.F., using 4 valves (6SG7, 6SG7, 6V6, 6X5). Waveband coverage 180/550 metres Medium, 800/2,000 Long. 3 colour dial, edge lit. Cabinet finished highly polished Walnut Veneer. Sides, Dial and Speaker in Beige. 10in. long, 10 1/2in. high, 5in. wide at base tapering to 3in. at top. Send for S.R. Construction Booklet, with easy-to-follow plans and drawings, 1/6 post free.

### S.R. 3-4 WATT AMPLIFIER The Ideal Record Reproducer

Building Cost **£4. 15. 0** Plus 2/6 post and packing.

Valve line up 6SG7, 6V6, 6X5GT.

Very compact, A.C. Mains 200/250 volt. Comprehensive tone control over Bass, Middle, Treble. Neatly laid out on sturdy chassis, 8in. x 4in. x 5in., hammer finished in bronze, fitted 4 cream knobs engraved Bass, Treble, Middle, Vol. On/Off; Pick-up and L.S. Sockets. Send for Construction Leaflet with wiring diagrams and assembly instructions, 1/- post free. Made up Amplifier complete. £5.5.0, plus 2/6 post and pkg.

### SEND FOR RADIO AND TV. CATALOGUE

with descriptions and illustrations all types Radio and T.V. components in stock, price 6d. post free.

Terms: Cash with order or C.O.D. Please add postage.

Open: 9 a.m. to 6 p.m. Monday to Saturday: 1 p.m. Thursday.

## SUPERIOR RADIO SUPPLIES

37, Hillside, Stonebridge, London, N.W.10. Phone: ELGar 3644

## G2AK This Month's Bargains G2AK

**RACK SIZE CHASSIS.**—17in. long x 2 1/2in. deep x 12in., 16/6; x 10in., 15/-; x 8in., 14/- P. & P. 1/-. All 16 s.w.g. ALI.

**POCKET VOLTMEETERS.** Dual range, 0-15 v. and 0-250 v., 345 O.P.V., M.C. Worth 50/- Our price 17/6 post free.

**CRYSTAL HAND MICROPHONES.** High quality, very sensitive. Chrome finish, complete with screened lead and standard jack plug. Our price only 25/- ea. Few only.

**VALVES.** B7G base, 1T4, 1S5, 1R5, 1S4, 3S4, 3V4, 7/6 ea., or 4 for 27/6. 807's, 10/- ea. or 2 for 17/6. Most of the 1.4 v. B7G range available at 8/6 ea.

**HEADPHONES.** Low resistance type CLR No. 3, 9/6. DLR No. 2, 13/6. High resistance CHR Mark 2, 17/6, and the most sensitive of all DHR, No. 5B, 18/6 per pair. P. & P. 1/- pair.

**METERS.** 0-5 ma. 2in. square, 10/- 0-50 ma., 7/6. 0-10 A., D.C., 7/6. 0-1 ma., 20/- 0-350 ma. thermo, 7/6. 0-4 A., 5/- 2 1/2in. flush 0-100 ma., 0-10 ma., 12/6 ea. Germanium Diodes, 2/- ea., or 6 for 9/- Deaf-Aid Crystal mike units, 12/6 ea.

**V.H.F. FANS.** Air Space Co-axial Cable, 150 ohm, good to 600 Mc/s; normal price, 3/11 per foot. Our Price, 20 yard coil, £1. Very limited quantity available.

**FSK SOLARISCOPEs.**—Complete with charts. Give World time, light and darkness patterns. Invaluable to the DX man. List 21/-, our price 7/6, post free.

**PANL Home Crackle.** Black, Brown or Green, 3/- tin. P. & P. 8d.

**TEST METER.** 7 ranges as follows: 1.5 v. 3 v. 150 v. 6 ma., 60 ma, 5,000 ohms, 25,000 ohms, 2 1/2in. Dia. scale M.C. meter. Rotary selector switch. Black bakelite case, 6 x 4 1/2 x 4 1/2, fitted with removable lid, also provision for internal batteries, ranges can be easily extended. Bargain Price, 30/-, plus 1/6 post.

**PHILIPS CONCENTRIC AIR TRIMMERS.** 8 PF max. 9d. each or 6/- doz. 30 PF max. 1/- each or 10/- doz. Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

### C. H. YOUNG, G2AK

All callers:  
110, Dale End,  
Birmingham 4 (CEN 1635)

Mail Orders to Dept. "P"  
102, Holloway Head,  
Birmingham 1 (MID 3254)

## HANNEY of BATH offers:—

**OSRAM 912** Erie resistor-pot. kit with ceramic tube resistors very highly recommended. 29/8; Lab resistor kit. 32/4; T.C.C. condensers. 55/-; **PARTITION** kit. Components, with loose lead terminations, Mains trans. 44/-; Smoothing Choke, 29/6; Output trans. 78/9. Price includes Partridge carriage/packing charge. Printed panel. 14/6. W.B. chassis. 34/9 (stocks of which should be available current with this advert). Send for complete list.

**MULLARD 5 VALVE 10 WATT AMPLIFIER** T.C.C. Condensers. 45/-; Erie resistor-pot. kit. 37/8; Elstone Mains trans. 39/-; Elstone Output trans. 45/- (both types); Denco chassis. 12/6. Small parts as per our list. Matched pairs of valves are available for both the above designs.

**FREQUENCY MODULATION.** For Wrotham high fidelity Transmissions. DENCO technical bulletin giving circuit and point to point wiring diagram for building an F.M. Feeder unit. 19. We have all components available. Priced parts list on application.

**COILPACKS.** DENCO. CP4/L and CP 4/M. 33/4; CP 3/370 pf. and CP 3/500 pf., 42/8. OSMOR "Q" HO. 48/-; LM. 40/-; Batt., 50/-; TRF. 40/-; HF stage for HO pack. 20/-; ETA 4-Station pack. 43/8. We stock COILS by Weymouth, Osmor, Wearite. Denco, Teletron and R.E.P.

**ELSTONE** Mains Trans. for the SIMPLEX TV. 48/-.

**VIEWMASTER.** WIDE ANGLE VIEWMASTER CONVERSION. Complete set of parts for converting existing Viewmaster to W.A. less valves, tube and mask, £14/18/6. W.A. Conversion instructions. 3/6; WB113. 49/6; BT.314. 15/-; WB115. 42/-; WB116 and WB117. 7/6 each; WB118. 22/6; WB119. 26/9; WB121 3/6; WB124. 10/6; Westinghouse 46/EHT.30. 17/-; Plus condensers and resistors as per our general list.

**WIDE ANGLE COMPONENTS.** ALLEN. Teleking Chassis. 39/-; Coils (TK & Super-Visor). 44/6; L.O.308. 40/-; FO.305. 21/-; DC.300c. 39/6; FC.302. 31/-; GL.16 & 18. 7/6 each; SC.312. 21/-; AT.310. 30/-; OP.117. 9/-; BT.314. 15/-; DENCO Chassis Magnaview. 37/6; Chassis. Super-Visor. 51/6; Coils. Magnaview. 41/2; WA/DCAL. 43/-; WA/FCAL. 31/-; WA/LCI and WCI. 7/6 each; WA/FMAL. 21/-; WA/LOTI. 42/-; WA.FBTI. 18/-; Send 6d. stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Teleking, Magnaview (Brimar & English Electric large screen TV), Super-visor, Mullard Universal, Close tolerance Silver Micas, etc., etc. Please add 1/- postage to orders under £1.

## L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

**MONEY BACK GUARANTEE** **DUKE & Co** **CWO or COD**  
 Tele: GRA 6677  
**621 ROMFORD RD. LONDON, E.12.**

12in. TUBES £5 **3 MONTHS' GUARANTEE**

Mazda CRM121—A or B.—A few other tyres available. As we have been selling for the last three years. Picture shown to callers. INSC-Carr. and Packing 15/6 extra.

**TEST TUBES £1.**—Most makes and types all work Perfectly, but have Cathode to Heater shorts or slight burn, ideal for testing or spares. Insured Carriage 15/6.

**H.T. BATTERY BARGAINS.**—1/9. All dry LT 1.5 and HT minimum 40 volt tested. 3/9, 60 volt + 1.5 LT All dry. 3/9, 67 1/2 volt HT Personal Portable type. 3/9, 60 volt HT. 5/9, 60 volt + 1 1/2 LT (long round type). 5/9, 67 volt. G.E.C. 3-volt 4 1/2 volt, size 9in. x 4 1/2in. square. 3/9. Inert cells. G.E.C. 3-volt twins. 1/-, 4 1/2 volt New Ever Ready LT or Bell, list price 3 3/4. P. & P., 1/9 on HT. 9d. on LT and cells. Plus for Batts., 6d. each.

**SPOTLIGHTS.**—3/9. Butler's ex-W.D., new, 7 1/2in. dia., 6 1/2in. deep. Pre-focus post 1 1/2. Bulbs for above, 6 volt 39 or 48 watt. 12 volt 30, 36 or 48 watt, 4/6, post free.

**REAR LIGHTS.**—1/9. Infra-red glass. Ideal tail or side lamps when glass is changed. Post 9d.

**LADIES ONLY!** Treat the lady and yourself to a heated blanket for the home. 37/6 brings a complete heater kit that a lady can fit by herself unaided—with free drawings.

**FIRESIDE "RIPPINGILLS" HEATER.**—77/6. For the home, works or office. Although these are used ex-W.D. they have been all overhauled and work perfectly (paraffin). Carriage 2/6.

**LIFE JACKET RESCUE LIGHTS.**—1/3 (Batts. 6d., bulbs 1 1/2 v., 3d.). Ideal cycles rear or car parking light. Post 4d.

**MORSE KEYS.**—New ex-W.D., 2/6. Bargain. P. & P. 6d.

**MARCONI HEADPHONES.**—New. Not ex-W.D. light weight, very sensitive, very good quality only 12/6. P. & P. 9d. (less lead).

**100 MICRO-AMP METRES.**—As new, boxed moving coil movements 2in. scale in 2 1/2in. square mounting, 12/6, post 1 1/2, free drawing.

**VALVES.**—New from 1/9 each.

**CAR RADIO TRANSFORMER.**—5/9. 6 v. pri.; centre tapped sec.; made to very high specification and recommended circuit for synchronized power unit 1/- extra.

21d. stamp for Catalogue.

# SHORTAGE OF RADIO & T.V. ENGINEERS

*The demand of Industry for our trained students is still greater than we can supply—and is likely to remain so for many years.*

*We offer*  
**FULL TIME DAY COURSE**

1-year course in Principles and Practice of Radio and Television.

*Next course commences April 19th, 1955.*

Write for **FREE BROCHURES** giving details of the above, of our 3-year course (commencing 29th August) and of others.

**E.M.I. INSTITUTES**—*the only college which is part of a great industry.*

**E.M.I. INSTITUTES (Dept. 32A)**

10, PEMBRIDGE SQUARE,  
 LONDON, W.2.

Tel.: BAYwater 5131/2.

Associated with  
**"H.M.V."**  
**MARCONIPHONE**  
**COLUMBIA**  
**ETC.**

1A 21

## THE HAM'S SHOP

Cheapest Television and Electrical Shop in Gt. Britain  
**70, KING STREET, BELFAST, NORTHERN IRELAND.**

RECEIVER.—TR1196, complete with valves, £1.15.0. RECEIVER 1355. £2. TRANSMITTER.—TR1196, £1.0.0, without valves. 10/-, REC. TRANSMITTER.—Type 38, 35/-, Type 18, £5.0.0. RECEIVERS.—77 Mc with valves, £2.10.0 each. TR. AMPLIFIER.—with valves, £4.0.0 each. AMPLIFIER with valves, £2.0.0. POWER PAK.—12 v., £2.0.0. CONTROL UNIT.—For above, 30/-, UNITS.—R.F. type 24 and 25, with valves, 14/-, Type 6, £2.15.0. Type 62, £2.15.0. HORN LOUDSPEAKERS.—Tannoy for P.A., complete, with Units, £2.10.0. LOUVER HEATERS.—complete with valves, £5.0.0. (Cannot be repeated.) MORSE KEYS.—3/6. T.V. AERIALS.—Indoor, 12.6. SOLDERING IRONS.—220/230, 12/6. (Cost price 25/-) SPEAKERS.—4in. 15/-; 5in. 12/6. METERS.—5 M.amp. 8/6; 50 M.amp. 8/6; 1 amp. 8/6; 3.5 kv. 12/6. (Cannot be repeated.) VCR CHASSIS.—With valves, £1. DIALS.—189, 4/6. DOOR BELLS.—Work off mains.) 3/-. LARGE BRASS TERMINALS.—7/4, each. 7/- per Doz. SPRAY GUNS.—9/6. AERIALS.—Pull out, 7/6. (18in. extends to 8ft.) CUT-OUTS.—12v. and 24v., 8/6. MINIATURE MOTORS.—Work off 12v. or 24v. A.C., 8/6 each. TUBES.—5CP1, £1.0.0. V197 30/- (No cut-offs.) 601, 8/-; 6V6, 7/6. METAL RECTIFIERS.—250/150 m/amps., 5/6; 6v., 1 amp., 2/-. METAL BOXES.—2/-. CHASSIS WITH COMPONENTS.—5/-. (Worth £1 each.) TANOY MICROPHONES.—5/-. TRANSFORMERS.—350/350, 80 m/amps., 4v., 4 amp. and 4v., 3 amp., 14/- each. CHAIRS.—100/100, 2/6 each. FAN MOTORS.—250, 15/- each. RIVETS, ALUMINIUM.—2/6 per box. RESISTORS.—All sizes from 6d. CO-AX CABLE.—8d. per yd. TUB. UNITS.—7/6 each. BELL WIRE, 100 yds., 4/6. BATTERY CHASSIS WITH VALVES.—12/6. SUPERHEAT CHASSIS.—With valves, 25/-, REPLY COUPLERS.—1/6 each. FAN MOTORS.—250, 15/- each. FLEX.—50 yds., 22/6. CONDENSERS.—6 mfd. high voltage, 5/- each. CLOCK MOVEMENTS.—15/-. MORSE KEYS AND BUZZERS.—5/6. PUSH BUTTON UNITS.—With knobs, 2/6. CONTROL UNITS.—2/6 each. PULLEY WHEELS.—6d. each. (Bakelite.) SPEAKER FIELD.—2/2. CRYSTALS.—2/6 each. TELEVISION VIEWING BINOCULARS.—10/-. RELAYS.—2,000 or 5,000 ohms, 7/6 each. 620 ohms, 3/6. BELL TRANSFORMERS.—5/6 each. FILAMENT TRANSFORMERS.—3, 5, and 6v., 1 amp., 5/6 each. CHOKES.—200 m/amp., 10 H., 3/6. BULBS.—10v., 13 amp., 6d. each. ALL SIZES OF VOLUME CONTROL.—2/6 each. With switch, 3/6 each. SIGNAL LAMPS.—7/6 each. PERSPEX DIALS.—All wave, 1/- each. VALVE HOLDERS.—All types, from 6d. ALADDIN FORMERS AND CORES.—6d. HYDROMETERS.—3 Ball type, 1/6. PUMPS.—£1.0.0 each. COMPLETE SETS OF PYE EQUIPMENT FOR T.A.S., etc.—(Mobile), 10 Mobile and one Main Station. (Price on Application.)


**THOUSANDS OF OTHER BARGAINS.**  
 PACKING AND CARRIAGE EXTRA. PLEASE ENCLOSE S.A.E. with Enquiries. DELIVERIES WITHIN 14 days. ALWAYS AT YOUR SERVICE.

## BUILD THIS AMAZING RADIO AN IDEAL XMAS GIFT

FOR **30/-** POST FREE

- Selective tuning.
- Acorn low drain valve.
- Loud clear tone.
- Long range.
- No earth.
- Short aerial, 2ft.
- Welded steel case.
- Easy to assemble.
- All parts for this set are sold separately.

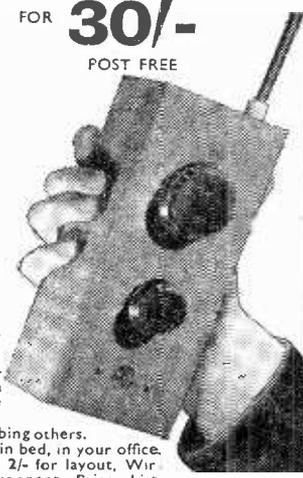- Ideal for :
- Fishing, Camping
  - Cycling, Touring
  - On the beach, etc.



### MAIL ORDER ONLY

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Component Price List.

Details of our 30/- Short Wave Receiver are now ready. Send 2/- for Layout, Circuits and Component Price List.

**R. C. S. PRODUCTS (RADIO) LTD.,**  
 11, OLIVER ROAD, LONDON, E.17

**ELECTROLYTICS**, capacity, voltage, size, type of mounting, price, post paid. 8. 450v. 1 x 2, clip, 2/-; 50, 12v.  $\frac{3}{4}$  x  $\frac{1}{8}$ , tag, 1/6; 150, 25v.  $\frac{3}{4}$  x  $\frac{1}{8}$ , clip, 2/-; 250, 12v.  $\frac{3}{4}$  x  $\frac{1}{8}$ , wire, 2/3; 40 + 40, 275v.  $\frac{1}{8}$  x 2, clip, 3/3; 24 + 24 + 16, 350/425v.  $\frac{1}{8}$  x 2, clip, 4/9; 60 + 200, 275/350v.  $\frac{1}{8}$  x  $\frac{1}{8}$ , clip, 6/6; 4. 150v.  $\frac{3}{4}$  x  $\frac{1}{8}$ , clip, 1/1; 500 12v.  $\frac{1}{4}$  x  $\frac{1}{8}$ , tag, 1/6; 150, 25v.  $\frac{3}{4}$  x 2, clip, 1/9; 32 + 32, 350/425v.  $\frac{1}{8}$  x 2, clip, 5/-; 8 + 16, 450/525v. 1 x 2, clip, 4/-; 2, 450/525v.  $\frac{3}{4}$  x  $\frac{1}{8}$ , tag, 1/6; 8. 450v.  $\frac{3}{4}$  x 2, clip, 1/9; 32 + 32, 450/525v.  $\frac{1}{8}$  x 3, W/E 5/6; 16 + 16, 450/525v.  $\frac{1}{8}$  x 2, W/E 4/6; all alicans. Some with sleeves all voltages wkg., surge where marked, new stock, guaranteed. Set of 3 Components comprising line output trans. with E.H.T. winding to give 7K5, using EY51 (heater winding for EY51 also included), and fitted with width control. Scanning coils, low impedance line and frame, focus coil high (10,000 ohms). Set of 3, 42/- plus 2/- postage. Diagram of line trans. supplied. Mains Trans. PRI 0.210-240, SEC. 250.0-250v. 80ma; 6.3v. 2.5a; 6.3v. 0.6a. 12/-; Mains Trans. PRI. 200-250v. SEC. 305.0-305v. 80ma. 800v. 5ma. 6.3v. 4.2a. 6.9v. 0.4a. 2v. 2a. 4v. 1.1a. 5v. 2.3a. These mains have been taken from ex-Govt. equipment, some may have tag panels broken but guaranteed O.K., 13/- post paid and ideal for scopes. **RADIO CLEARANCE LIMITED**, 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

**ALUM CHASSIS** 4 sided 18 S.W.G. 12in. x 9in x 2in, 6/- plus 10d. postage. Special sizes, prices in proportion. Holes 20 each. Riveted corners 1/- extra. **WOOD & TOY**, 51, Winfield Road, Claines, Worcester.

**R.F. UNITS**, types 26 at 32/6, 25 at 16/6, 24 at 12/6, brand new in original cartons, with valves; postage 2/6. **E.W.S. CO.**, 69, Church Rd., Moseley, Birmingham.

**MODERN RADIO** and T.V. Valves, Components, etc.; brand new; amazing value in range, price and quality. Send for list. **CENTRAL LONDON DISTRIBUTIONS**, 52, York St., London, W.1.

**EVERYTHING** for radio constructors, Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH**, 98, West End Road, Heston, Camber. Quick service.

**SALE BC348R** converted for AC. With LS. Nearest £20. **TAYLOR**, 60, Headley Park Avenue, Bristol, 3.

### BOOKS

**NEW** and Used Correspondence Courses; Educational Books, bought, sold. Catalogue. **COURSES**, 28, Dean Road, London, N.W.2.

**I.P.R.E. TECHNICAL PUBLICATIONS**, 6,500 Alignment Peaks for Super-heterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy The Practical Radio Engineer, quarterly publication of the Institute, 2/- membership and examination data, 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

**AMERICAN MAGAZINES**.—One year "Audio Engineering," 35/-, specimen copy, 3/6; "Popular Science," 28/6; "High Fidelity," 50/-, specimen copy, 4/6. Free booklet quoting others. **WILLEN LTD.**, Dept. 40, 101, Fleet Street, London, E.C.4.

**BOOKLETS**. "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2, price 2/6 ea. Ex-Govt. Optical lists free for s.a.e. **H. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

**RATES: 5/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.**

### SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-54, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.

**SKYWAYS LTD.**, have vacancies as follows: 1. Aircraft inspectors with "A" and/or "C" licences. 2. Sheet metal workers with aircraft experience. 3. Aircraft-radio mechanics and instrument mechanics with practical workshop and maintenance experience. 4. 1 Charge-hand with "X" licence for high voltage electrics. 1 Charge-hand with "X" licence for instruments. 2 Upholsterer/trimmers. Please apply to Administrative Superintendent, **SKYWAYS**, Bovingdon Airport, Herts.

**CITY AND GUILDS** (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. **B.I.E.T.** (Dept. 242A), 29, Wright's Lane, London, W.8.

**ENGINEERS**—Radio/TV. Service—for appointments within the salary range £400-£750, in areas, West End, Acton, Lewisham, Croydon, Chatham, High Wycombe, Aldershot. Reading; Apply **BROADMEAD WIRELESS CO. LTD.**, 123, The Broadway, Wimbledon, S.W.19. (LIB. 2435.)

**T.V. AND RADIO**.—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc. on "no pass—no fee" terms. Over 95% successes. Details of exams. and home training courses in all branches of radio and TV; write for 144-page handbook—free. **B.I.E.T.** (Dept. 242G), 29, Wright's Lane, London, W.8.

**A.M.I.Mech.E.**, A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams. and courses in all branches of engineering, building, etc., write for 144-page handbook, free. **B.I.E.T.** (Dept. 242B), 29, Wright's Lane, London, W.8.

### VALVES

**VALVES**, New, Tested and Guaranteed. Matched Pairs, KT66 25/- 6V6G 17/- per pr. 6K8C. 6Q7G. 6SN7GT 6SL7GT. 6AT6. 6BE6. 6BR7. 6BS7. 6SA7. 6SJ7GT. 6SK7. 6X4. 6X5GT 8/-; 1R5. 1T4. 1S5. 3V4. 6AM6. 5763. Y63. 6U5. 7/6; EBC33. E240. KT33C. 25A6G. 12AT7. 8/6; PL81. PL2. ECL80. 1H5. 1N5. 10/6; 12AX7. 6/9. Coax cable, stranded, 75 ohms lin. 6d. yd. **R. J. COOPER**, 32, South End, Croydon, Surrey. (CRO. 9186.)

**ALL TYPES** of Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcut Road, N.W.1. (PR1mrose 9090.)

**NEW VALVES WANTED**, small or large quantities: PL81, EY51, KT61, 524G. 5R4. 5U4. 3Q5, all television; prompt cash. **WM. CARVIS LTD.**, 103, North St., Leeds, 7.

**EF91 7/6; EF50 5/-; 3A4 4/-; 1A3 3/6; 1L4 6/-**. Stamp for list. **VI-RAD**, 6, Twyford Road, Eastleigh, Hants.

**NEW, BOXED, VALVES**, 8/3, post free, 90/- dozen. 1T4, 1S4, 1S5, 1R5, 3S4. 3V4. 5Z4. 5U4. 5Y3. 6K8C. 6Q7. 6SL7. 6SN7. 6AT6. 6X4. 6BE6. 6BA6. 6A7. 6A8. 6BW6. 6AM6. 6AL5. 12K7. 25L6. 25Z4. 25Z6. 35L6. 35Z4. 80. 12AT7. 12AU7. ECL80. PY80. FY82. UX41. UCH42. Amph. Bases, all types, 6d.; Valves at 6/3, p/Tree, 6V6. 6K7M. 6J7M. 6J5M. EF36. EL32. EF50. 6K5. 6C5. 7C5; At 3/6 each, SP41, SP61. 12J5. 6H6M. Mic. Trans., 2/-; C.diodes, 1/6; V.cntrls., all values, 2/6; SP/sw., 3/6; W.W. cntrls., 3- watt, 5K and 25K, 3/6; Pre-set 250 ohm, 2K, 2.5K, 5K, 10K, 20K, 30K, 1/6; Fil/trans., 200/240v. 6v. at 1.5A. 5/9; I.F. Trans., 45KcCs. midget, 9/6; semi/midget, 9/6; standard, 8/6 pr.; T/gang .0005, 5/6; Elliptical Spkrs., 7in. x 4in., 16/9; 10in. P.M., 23/6; Coilpacks, 3-watt, 1. m. s., 23/6. S.A.E. new lists. 13,000 Valves in stock. **RADIO UNLIMITED**, Elm Road, London, E.17. (KEY. 4813.) New Branch now open at 50, Hoe Street, Walthamstow, E.17. (LAR. 6377.)

**BENTLEY ACOUSTIC** for valves. Orders despatched same day. Refund or exchange guaranteed.—1E7 6/6, 1M1 12/6, 1S4 7/-, 1U5 9/6, 2C34 2/-, 2D4B 16/6, 3AP1 50/-, 3S4 7/6, 471 3/-, 5R4 9/6, 5Z4 8/6, 6AG5 7/-, 6AG7 15/-, 6B7 7/6, 6B8 4/-, 5BR7 8/6, 6C5 5/-, 6C8 8/6, 6F6 7/-, 6F7 14/-, 6F12 6/6, 6G5 6/6, 6J8 10/6, 6SG7 7/6, 6S7 8/-, 6SL7 8/-, 6SQ7 8/6, 6U4 16/6, 7B6 8/6, 10LD11 10/-, 11D5 7/6, 12A8H 10/6, 12AT6 10/6, 12BA6 9/6, 12Q7 8/6, 12SC7 7/6, 12USG 7/-, 13D3 9/-, 19H4 35/-, 24UXG 12/6, 25Y5 8/6, 35Z4 8/6, 35Y5 12/6, 35Z4 9/-, 35Z5 9/-, 39 44 7/6, 50L6 8/-, 50Y6 8/6, 78 8/6, 80 8/6, 202STH 10/6, 210DDT 8/6, 215SG 4/-, 226B 10/6, 240B 10/6, 7193 2/6, 7475 7/6, AC/P 7/6, A/PEN 10/6 AC/DD 4/-, APPAC 12/6, CL4 14/-, CV6 1/6, D1 1/6, D77 6/-, DET 9 2/-, DH30 15/3, DPT 15/6, EA42 9/6, EBC41 10/-, EC52 5/6, EF93 6/6, EK32 7/6, EL41 10/-, FC13 9/6, GTIC 6/6, GZ32 14/-, H63 7/6, HL2 3/-, KBC32 7/6, KT36 17/6, LP2 4/6, MU12 8/6, PEN25 6/6, PEN26 16/-, PEN1340 6/-, PM202 4/6, QP21 7/6, QP25 6/6, QS95 10 10/6, SD6 7/6, SP2 (4 and 7) 8/6, SP4B 11/-, SP41 2/6, TH2IC 10/6, TP23 10/6, TP2620 17/6, U12 8/-, U24 13/6, U52 7/6, VP41 11/-, VU11 3/-, VU20A 3/-, VU132 3/6, X78 13/-, Special offer of sub-miniatures: CK503AX, CK505AX, CK523AX, CK525AX, XFW10, XFW20, XFY10, XFY12, XFY23: all 7/- each. Further selection of valves on page 760.

**45/- OFFERED** for 813 Type Valves; any quantity purchased. Write: **PYPE-HAYES RADIO**, 606, Kingsbury Road, Birmingham, 24.

### EDUCATIONAL

**WIRELESS**.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instructor, only if required, also postal courses. Apply **B.S.T. LTD.**, 179, Clapham Rd., London, S.W.9.

**SEE THE WORLD** as a Radio Officer. Short training; low fees; scholarships; boarding/day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

**MERCHANT NAVY and Air Radio**.—Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. Estd. 30 years; s.a.e. for prospectus from Director, **THE WIRELESS SCHOOL**, 21, Manor Gardens, London N.7. (Tel.: ARC. 3694.)

**WORLD TRAVEL** and adventure in the Merchant Navy. Young Men, 15 years upwards, required for training in Marine Wireless and Direction-finding at sea. (Trainees in forthcoming Registration Groups are eligible for Deferral of Military call-up.) Immediate sea-going positions on completion of training. Suitable candidates will be entered as Officers and must be prepared to sail to all parts of the world. Courses: Full or Part-time, also by Correspondence. Recognised by Ministry of Education. Scholarships available. Boarding and modern canteen facilities; low training fees. Send 1/2 P.O. (stating age and height, etc.) for complete prospectus to **OVERSEAS HOUSE**, (Dept. 14), Brooks' Bar, Manchester, 16. (Tel.: MOSS-side 2047.)

**FREE!** Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics! Courses for the hobby enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the College operated by Britain's largest electronic organisation: moderate fees. Write to Dept. PW28; E.M.I. INSTITUTES, London, W.4.

**YOU CAN** become a first-class Radio Engineer. Our Postal Courses will teach you to earn more money or start a spare-time business of your own. Write now for free details. **T & C RADIO COLLEGE**, 36, Northfield Rd., Ringwood, Hants.

**THE INSTITUTE** of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY, I.P.R.E.**, c/o, Fairfield Road, London, N.8.

**ARE YOU STUCK** on Electrical or Radio Control? Large stock of Transformers, Rectifiers, Lamps, Rotary Converters, Motors, Technical Books. S.A.E. for bargain lists. **LAWRENCE**, 134, Cranley Gardens, N.10. (CLL 6641.)



Don't scrap that failing car battery or radio cell. Try Renewbat conditioner. Works like a charm. Simple and safe to use. Full instructions. Car size 3/-, p.p. 6d.; Radio size 1/9.

**CHAMPION PRODUCTS**, 43, Uplands Way, London, N.21. Phone: LAB 4457

**11/- Midget Coil Pack Kit 11/-**

Comprising chassis 3" x 2" x 1 1/2", switch, LMS iron cored coils, padders, trimmers, nuts and bolts, wire sleeving, circuit diagram, 45c Kc. Brand new Int. Oct. Valveholders, 2 1/4", 2/- doz.; All Can. Electrolytics, 6 x 500, 1/3, 12/- doz.; 2 x 350 8d., 6/- doz.; 200 x 12 6d., 4/6 doz.; 100 x 3 3d., 2/- doz.; Coils, Coils, "P" Type 2-, "Q" Type 2/3, TRF 4, -pr.; MSS Superhet 6 coils with circuit, 4/- set; HF Dual-wave 2 9, Crystal Coil L & M 2/-; Tub Cond., 1 x 500 3/- doz., 1 x 350 2 9 doz.; Asst. Grommets 6d. doz.; 2 4 & 6 BA Nuts 2/- gr.; Brand new BA Nuts & bolts ass. 2/- gr.; Ex-equip. BA nuts, bolts, washers 2/6 lb. (approx. 500 pieces); PK self tap screws 2 6 gr.; 18 SWG Multicores, 2 6 doz. yds.; 1 m m sleeving 1/- doz. yds.; 1 meg. vol. con. with DP sw., 3/-. Latest list 5d. Min. P. & P. 1/-.

**SUSSEX ELECTRONICS**  
5, WHITE LODGE CRESCENT,  
THORPE-LE-SOKEN, ESSEX

**OSMOR** for really efficient Coils. Coilpacks and all Radio Components as specified for many "Practical Wireless" circuits. See advert. on page 739 for free circuits offer or send 5d. (stamps) to **OSMOR RADIO PRODUCTS LTD.**, Dept. PC12, 418, Brighton Road, South Croydon. (Tel.: Croydon 5143 9.)

**SERVICE SHEETS** Hire Sale 1933 to date, S.A.E. Enquiries F.I.E.L.D., 80, Old Field Rd., London, N.16.

**SERVICE SHEETS** for Radio and Television, over 2000 models. S.A.E. enquiries. W. GILBERT, 24, Frithville Gardens, London, W.12.

**COLLARO** 3-speed Autochanger Cream Non-mixer 3RC531, few only at £11, complete with studio "O" pick-up; Tubular Condensers Moulded Case, all 4x.v.d.c. working at 1/- ea. or 10/- for 15 mixed; your selection, 0005mf, 002mf, 003mf, 005mf, 01mf; 03mf; Block Condensers, 4mf 600v.d.c.w. (2in. x 2in. x 4 1/2in. tall), 3/6 ea.; 8mf 400v.w., 4/-; 4mf 1,200v.w., 5/-; 6mf 1,000v.w., 5/-; 0.1mf 5k.v.w., 5/-; 0.5mf 6k.v.w., 10/-; Selenium Rectifier, 230v. 50ma, 4/6; 250v. 30ma, 6/-; **GLADSTONE RADIO**, Gladstone Place, Newton Abbot, Devon.

**WALNUT** Radiogram Cabinets of distinction; stamp details. R. SHAW, 68, Farlow Rd., E.11.

**AMERICAN RADIO** Plans and Devices. Now available. Hundreds of new and startling devices you can make. Only designs of this type available in U.K. Receivers, walkie talkies, amplifiers, recorders, magic eye alarms, etc., etc. Full lists, data illustrations Free for stamp. Send to-day.—A.P.S. (PW), Sedgford, King's Lynn.

**WINWOOD FOR VALUE**—New, boxed, Sylvania, 6L6G, 5U4G, EF50, 6SL7, 6SN7, all at 8/6 each; Valve sets, 524, 6V6, 6Q7, 6K7, 6K8, 29/6; 174, 1S5, 1R5, 2S4, 2B/-; EF91, EB91, 6 for 32/6; EF80, 8/6; Dubilier 8mf-500v 2/3, 8 x 8-500v 3/6, 16 x 16-500v 4/3, Hunts 25mf-25v 1/4, 0.1-350v 6/- doz., 0.1-500v 7/9 doz., 0.05-500v 7/6 doz. Small waxed 01, 04, 001, 002, 005, all at 3/- doz. Lists. **WINWOOD**, 12, Carnarvon Road, London, E.10. (Mail only.)

**1-Finger Pianists**

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

**C & S, 10 Duke St., Darlington, Co. Durham**

**ANNAKINS BARGAINS**

Components for Ringing Choke EHT units, 1355 EHT (High cycle) Transformer, 5/-, P. & P. 1/1. 1355 Chokes, 4/- the pair. P. & P. 1/3. VU111 and most other EHT rectifiers, 2/-. 1 meg. preset pots., 6d. Valves from 1/3 upwards. Hundreds of genuine bargains. So write now for FREE LIST. No SAE required. Money Back Guarantee. C.W.O. only.

25, ASHFIELD PLACE, OTLEY, YORKS.

**MORSE CODE Training**  
Send for the Candler  
BOOK OF FACTS

It gives details of all Courses which include a Special one for securing amateur licence. **CANDLER SYSTEM CO.** Dept. 5LO 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

**LOUDSPEAKERS** repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullingdon Rd., Oxford.

**TAPE DECKS**—Due to cancelled South American export order we have been able to purchase on very favourable terms a limited quantity of a very well-known Tape Deck in kit form which we are offering at a knock-out price of £6/19/6. Full details by return of post from: **HOTAX PRODUCTS LTD.**, 59, Gray's Inn Rd., London, W.C.1.

**HIGH FIDELITY**—Bel FM VHF receivers, from £8, complete and guaranteed. Full constructional kits, £7/5/-, coilsets and separate parts. Lists, 1/-, New "Mullard" point four per cent. amplifier, £19. **BEL SOUND PRODUCTS CO.**, Marlborough Yard, Archway, London, N.19. (Nr. Archway Northern Line, 25 mins. West End.) Tel. ARC. 5078.

**NEW VIBRATOR PACKS** made by "Masteradio"; totally enclosed; size 9 x 4 1/2 x 5 1/2in., input 6 volts D.C.; output approx. 180-200 volts at 80ma and 6 volts. One of the best vibrator units we have had. Price, in brand new condition, 29/6 each, p.p. 2/6; new, but with cases, store soiled, 27/6, p.p. 2/6. If you are not already on our mailing list, send stamp for our latest list of bargains. Better still, call. **SERVIO RADIO**, 156/158, Merton Rd., Wimbledon, S.W.19. (LIBerty 6525.)

**METERS**, M.C. 0-1 M.A. 50 ohms, 2in. sq., 10/- post free.—**MORRISON**, 22, Stacey Ave., Edinburgh.

**TEST EQUIPMENT**. Avon. Model 8 meter, £23/10/- cash or deposit and 8 monthly payments of 57/6. Model 7 meter, £19/10/- cash or deposit and 8 monthly payments of 47/8. Universal Avonimeter, £10/10/- cash or deposit and 8 monthly payments of 25/8. D.C. Avonimeter, £5/5/- cash or deposit and 8 monthly payments of 12/10. Amplion Test Meter, £5/19/6 cash or deposit and 8 monthly payments of 14/8. Pullin Series 100, £11/11/- cash or deposit and 8 monthly payments of 28/3. Desk 70, LAFCO COMPOUNDS LTD., 3, Corbetts Passage, S.E.16. (BER. 4343.)

**TESTOSCOPE Mains Tester**

For high and low voltage testing:—1-30 and 100-850 volts A.C. or D.C. Write for interesting leaflet 29/6. 16 page manual how to make 50 electrical tests) 1/- post free.

**RUNBAKEN · MANCHESTER**

**RECEIVER R1155**

**BRAND NEW. AERIAL TESTED** In maker's original transit case. Now is the chance to get one from the best delivery we have had from the Ministry. £11-19-6. Carr. 10/6


Send S.A.E. for further details or 1/3 for publication giving circuit diagrams, etc. Others available from £9.10.0 according to condition.

**MICROAMMETERS**—250 F.S.D. 3 1/2in. Flush Model S97. Specially scaled for test meters. Knife edge pointers, magnetic shield. Brand New. Not Govt. surplus. Offered about half usual price, 55/-.  
**VOLTMETERS**—0/300 volt A.C. 50 cycles. 2 1/2in. flush moving coil, rectifier type, 30/-. Moving iron with 5in. dia., 60/-.  
**METERS**—0/300 Flush D.C. Moving Coil, 10/6. 0/20, 2in. Flush Moving Coil, 7/6; 0/40 2in. Flush M.C., 10/6, post 1/-.  
**CONDENSERS**—Paper Block, 8 mfd. 750 volts. G.E.C. Brand new, 10/6 each.

**WILCO ELECTRONICS** Dept. P.W., 204, Lower Addiscombe Rd., Croydon.

# HOME RADIO OF MITCHAM

for your  
**EDDYSTONE and DENCO parts**

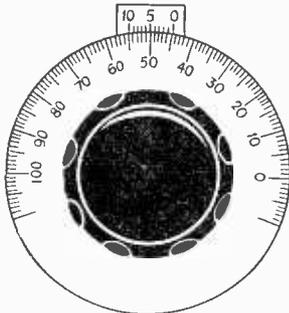

**EDDYSTONE 843**  
**VERNIER SLOW**  
**MOTION DRIVE.**  
Anodised satin finish, hard aluminium dial 4" diameter, with scale having 100 divisions over 180°. Driving head is ballbearing epicyclic type, totally enclosed and giving a reduction ratio of 10 to 1. Price 17/9 No. 841 Pointer Knobs. Price 10d.  
No. 842 Dial, 1 1/2 in. dia. Price 8d.  
**DENCO** miniature dual purpose coils. We have the full range in stock BLUE, YELLOW, RED and WHITE. 3/11 ca. All ranges in GREEN 4/9 ea.

**DENCO No. 11 Chassis.** 10 x 8 x 21, in aluminium. 8/9.  
**DENCO 3 gang 315 pF Tuning Condenser.** Price 18/3.  
Please send 2d. stamp for detailed list of all parts. Despatch by return C.W.O. or C.O.D.


**SPECIAL OFFERS—**  
Valveholders, B9G (EF50), laminated paxolin, 6d. each.  
Sprague Condensers, .1 mfd., .01 mfd., .02 mfd., .9d. each.  
75 pF Air Spaced Variable Condensers, 1/6 each.  
24 brand new Erle Resistors, assorted, 4/-.  
24 brand new assorted Condensers, 6/-.  
Limited quantities available.

# HOME RADIO OF MITCHAM

187 London Road, Mitcham, Surrey MIT 3282

Open every day including Saturday until 6.30 (Weds. 1 p.m.)

# GET ON THE BEAM!

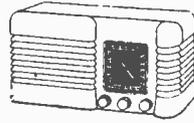

... with the  
**METEOR III**  
**GUARANTEED**  
**A.C. Mains Set.**

## SIMPLICITY ITSELF!

Complete KIT only

# 95/-

plus 2/6 for  
postage & packing.

Instructions, Point to  
point Diagrams and  
Parts List sent for 1/-,  
Post FREE.

You could almost do this job with a knife and fork—it's so simple! Screwdriver, pliers and soldering iron will make this spot-on 3 valve, 2 wave band set. Complete Kit includes valves, Ready-to-use Chassis. Brown or Ivory Moulded Cabinet. A.C./D.C. Universal Model available at 97/6, plus p. & pkg., at 2/5

**NORMAN H. FIELD**  
68, Hurst St., Birmingham 5.

**SATISFACTION—or we REFUND your CASH!**

# FREE!

**to YOU!**  
**—if you seek**  
**SUCCESS!**

**Train your mind to SUCCEED**

**WHAT'S YOUR LINE ?**

Building	Accountancy Exams.
Carpentry	Auctioneer's Exams.
Commercial Art	Book-keeping
Diesel Engines	Civil Service
Draughtsmanship	Costing
Electrical Eng.	English
Fire Engineering	General Education
Mechanical Eng.	Journalism
Motor Engineering	Languages
Quantity Surveying	Mathematics
Radio Eng.	Police Subjects
Surveying	Salesmanship
Surveyor's Exams.	Secretarial Exams.
Telecommunications	Shorthand
Textiles	Short Story Writing
Wireless Telegraphy	and many others

**GENERAL CERT. OF EDUCATION**

If you lack the qualifications which would get you a better job; more pay and quicker progress; if you wish to know how The Bennett College can guarantee to teach you up to qualification stage by one of the easiest, quickest and soundest methods of mind training; if you wish to learn how Personal Postal Tuition can prove that you are cleverer than perhaps you think you are — if you like the idea of studying in your own time, at your own pace, with your own tutor guiding you, helping you, teaching you by post—send at once for this recently published important book—“Train your mind to SUCCEED”. It is quite free. Just fill in the coupon below and name the subject you are interested in (some of the many Courses available are listed here). Then send in the coupon to us TODAY. You will never, never regret it. But do it today. Act NOW!

**BENNETT COLLEGE**  
(DEPT. L 104F), SHEFFIELD

Please send me, without obligation, a free copy of “Train your mind to SUCCEED” and the College Prospectus on:

SUBJECT \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ACB (if under 21)

Please write in Block Letters

**THIS DAY**  
COULD BE THE TURNING-POINT IN YOUR LIFE.

**THIS COUPON**  
COULD BE YOUR PERSONAL PASSPORT TO SUCCESS.

**Send it NOW!**

## 38 SET

WALKIE-TALKIE

Complete with Valves and Circuit Diagram.

Pos. 39/- Paid

No. 22 SET.—Trans. Receiver. Complete with Valves and Power Unit. £4/10/-.  
TX1403.—New Condition. 2-9 Mc. 2 6V6. 1 EBC33. 1 807. 10-40 watt. Less Valves, £3. Mainland Carr. Paid.  
APN4 RECEIVER.—(Radar) Chassis. New Cond. at 15/6.  
48 SET (CANADIAN) WALKIE-TALKIE.—6-9 Mc. TX/RX. Complete with Valves, £4. Less Valves, £2.

## VALVES

4/- EF50 4/-

SP61	2/6	SP41	2/6	EL32	7/-	EF91	7/6
EF36	4/6	EC54	5/-	6K8	11/-	GJ5	5/-
EC52	5/-	6K7	6/-	6SN7	9/-	GNT	8/6
EBC33	7/6	6SK7	4/-	6BW6	8/-	5B7W	8/6
6A5(M)	6/-	6AG5	7/-	12A6	6/6	12J5	5/-
6AM6	7/6	6AL5	6/-	6S.17	6/-	6SA7	8/-
9BW6	9/-	2X2	2/6	1T4	7/-	1S4	7/-
6Q7	8/6	6H6	3/-	3S4	8/-	3A1	7/-
6B4	5/-	1R5	7/-	6SH7(M)	5/-	1A5	6/6
155	7/6	P2	6/-	6X5	7/6	5Z3	8/6
3V4	7/6	5U4G	8/6	Pen220	3/-	35L6	9/-
50L6	8/6	35Z4	8/6	Pen46	5/6	HL2	3/-
LF210	2/6	SG218	2/6	U22	7/-	807	6/-
6V6	8/6	VU39	8/6	PT15	7/-	807 (USA)	8/-
TZ40	10/6	ML4	4/-	S150	5/6	MU2	7/-
6F8	7/6	VT501	6/-	VU133	3/-	832	17/-
CV287	7/-	CV201	6/-	VT62	9/-	CV286	7/-
D1	2/-	CV73	3/6	EB34	2/-	VU111	3/-
EF39	7/-	EF54	5/-	CV19	21	VU508	8/-
5Z4	8/6	EA50	2/-	VT25	8/-	V870	5/6

**CONDENSERS.**—Electrolytic 450 volt wkg. 8 mfd., 2/-; 3-8 mfd., 3/9; 16+16 mfd., 4/6; 32+32 mfd., 6/-; Dabulifer 500 volt wkg. 20 mfd., 3/-; 32 mfd., 5/-; Bias, 25/25 volt or 50 mfd. 50 volt, 2/- each.

**VINER'S (Middlesbrough),**  
28, EAST STREET, MIDDLESBROUGH,  
Telephone: MID 3418

Practical Wireless

**BLUEPRINT SERVICE**

**PRACTICAL WIRELESS**

	<i>No. of Blueprint</i>
<b>CRYSTAL SETS</b>	
1/6d. each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set ... ..	PW94*
2s. each	
Dual - Wave "Crystal Diode" ... ..	PW95*

**STRAIGHT SETS**

<b>Battery Operated</b>	
One - valve : 2s. each	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver ... ..	PW96*
Two-valve : 2s. each.	
The Signet Two (D & LF) ... ..	PW76*
3s. each.	
Modern Two-valver (two band receiver) ...	PW98*
Three-valve : 2s. each.	
Summit Three (HF Pen, D, Pen) ... ..	PW37*
The "Rapide" Straight 3 (D, 2 LF (RC & Trans)) ... ..	PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ... ..	PW87*
3s. each.	
The All-dry Three ...	PW97*
Four-valve : 2s. each.	
Fury Four Super (SG, SG, D, Pen) ... ..	PW34C*

**Mains Operated**

Two-valve : 2s. each.	
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*
Three-valve : 3s. 6d. each.	
A.C. Band-Pass 3 ...	PW99*
Four-valve : 2s. each.	
A.C. Fury Four (SG, SG, D, Pen) ... ..	PW20*
A.C. Hall-Mark (HF Pen, D. Push Pull) ...	PW45*

**SUPERHETS**

Battery Sets : 2s. each.	
F. J. Camm's 2-valve Superhet ... ..	PW52*
Mains Operated : 3s. 6d. each.	
"Coronet" A.C.4 ...	PW100*
AC/DC "Coronet" Four	PW101*

*No. of  
Blueprint*

**SHORT-WAVE SETS**

<b>Battery Operated</b>	
One-valve : 2s. each.	
Simple S.W. One-valver	PW88*
Two-valve : 2s. each.	
Midget Short-wave Two (D, Pen) ... ..	PW38A*
Three-valve : 2s. each.	
Experimenter's Short-wave Three (SG, D, Pow) ... ..	PW30A*
The Perfect 3 (D, 2 LF (RC and Trans)) ...	PW63*
The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen) ... ..	PW68*

**PORTABLES**

1s. 6d.	
The "Mini-Four" All-dry (4-valve superhet)	*

**MISCELLANEOUS**

2s. each.	
S.W. Converter-Adapter (1 valve) ... ..	PW48A*
(2 sheets), 7s. 6d.	
The P.W. 3-speed Autogram ... ..	*
The P.W. Electronic Organ (2 sheets), 7s. 6d.	*

**TELEVISION**

The Practical Television Receiver, (3 sheets), 10/6	
The "Argus" (6in. C.R. Tube), 2/6*	
The "Super-Visor" (3 Sheets) 7/6*	
The "Simplex" ... .. 3/-*	

*All the following blueprints, as well as the PRACTICAL WIRELESS numbers below are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.*

**AMATEUR WIRELESS AND WIRELESS MAGAZINE**

**STRAIGHT SETS**

<b>Battery Operated</b>	
One-valve : 2s.	
B.B.C. Special One-valver ... ..	AW387*
<b>Mains Operated</b>	
Two-valve : 2s. each.	
Consoelectric Two (D, Pen), A.C. ... ..	AW403

**SPECIAL NOTE**

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of  
Blueprint*

**SHORT-WAVE SETS**

**Battery Operated**

One-valve : 2s. each.	
S.W. One-valver for American ... ..	AW429*
Two-valve : 2s. each.	
Ultra-short Battery Two (SG, det Pen) ... ..	WM402*
Four-valve : 3s. each.	
A.W. Short Wave World-beater (HF Pen, D, RC Trans) ... ..	AW436*
Standard Four-valver Short-waver (SG, D, LF, P) ... ..	WM383*

**Mains Operated**

Four-valve : 3s.	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ... ..	WM391*

**MISCELLANEOUS**

Enthusiast's Power Amplifier (10 Watts) (3/-)	WM387*
Listener's 5-watt A.C. Amplifier (3/-) ... ..	WM392*
De Luxe Concert A.C. Electrogram (2/-) ...	WM403*

**QUERY COUPON**


This coupon is available until Dec. 6th, 1954, and must accompany all Queries, sent in accord with the notice on page 761.

PRACTICAL WIRELESS, Dec., 1954.

# 9 Octave

# realism...

# from a single unit

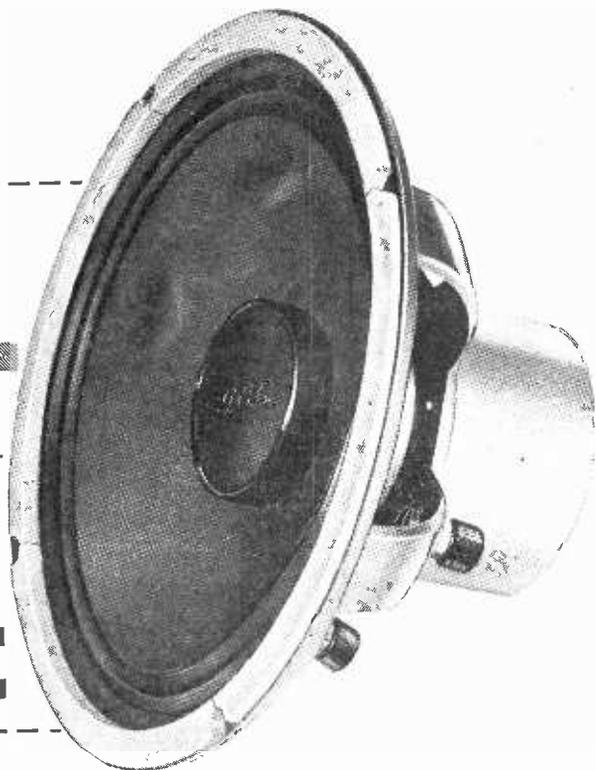

The G.E.C. metal cone loudspeaker gives lifelike reproduction of any type of sound over a range of 9 octaves. This includes the entire musical fundamental range together with overtones which give tonal quality and character to the performance of each musical instrument. The sound engineer will appreciate the simplification and improvement in performance which has been achieved by combining the following attributes in a single unit.

- Smooth response over a range of nine octaves with extremely good low frequency response
- Negligible inter-modulation
- Unequalled transient response due to special coil and cone construction

## £8·15·0

TAX PAID

### For the Home Constructor

This is a professional instrument and must be used under the correct conditions to obtain the optimum results. Cabinets have been designed for use with this loudspeaker, details of which will be available shortly.



## Metal Cone Loudspeaker

THE GENERAL ELECTRIC COMPANY LTD., MAGNET HOUSE, KINGSWAY, W.C.2