

*Making a Valve Voltmeter*

# PRACTICAL WIRELESS

JULY  
1955

EDITOR: F. J. CAMM



**BACK AT LAST**

**PIFCO** ALL-IN-ONE RADIOMETER  
FOR ALL ELECTRICAL TESTS

CIRCUIT TEST  
L.T. TEST  
H.T. TEST  
M.A. TEST  
VALVE TEST

With internal battery and multi-scale the PIFCO All-in-One Radiometer tests everything electrical, Radio and P.A. Equipments, Household appliances of all kinds, Car Lighting Systems, Bell and Teleprinter Circuits. May be used on AC or DC mains.

(Obtainable from your local dealer.  
If any difficulty, write direct to :-

**29/6d.**  
COMPLETE

**PIFCO LTD., WATLING ST., MANCHESTER 4**  
and at 36-37 UPPER THAMES ST., LONDON, E.C.4


**CONSTRUCTORS build these at**  
**DOWN-TO-EARTH PRICES**  
**PERSONAL PORTABLE RADIO 30/-**

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed in your office, or just anywhere.  
Send 2/- for layout, Wiring diagram and Components Price List.



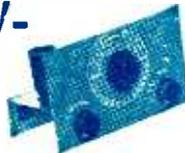**1v SHORT-WAVE RADIO 30/-**

- \* Covers 10-100 metres
- \* World-wide reception
- \* Low drain valve.
- \* Picture diagram and instruction for beginners.
- \* Assembling time 1 hr



This 1 valve S.W. receiver can be built from our list of components for 30/-, including valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required. All components can be purchased separately and are colour-coded so that the beginner can build this set quite easily.  
Send 2/- for specification, wiring diagram, layout and price list to :-

**R.C.S. PRODUCTS (RADIO) LTD**  
11 OLIVER ROAD, LONDON, E.17. Mail order only

*Finest Soldering?* Always specify **ERSIN MULTICORE** to be precise

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

**SIZE 1 CARTON**  
4 specifications for radio enthusiasts.

**5/-**



**HANDYMAN'S CARTON**  
Sufficient for 200 average joints. **6d.**

**TAPE SOLDER**  
MELTS WITH A MATCH!  
Real tin/lead solder containing cores of Ersin Flux. Needs no soldering iron or extra flux.

**1/-**

**PER CARD**



**BIB WIRE STRIPPER AND CUTTER**  
The 3 in 1 tool. For stripping insulation without nicking wire, cutting without leaving rough edges and splitting extruded flex. **3/6 EACH**

MANUFACTURERS ARE INVITED TO WRITE FOR DETAILS OF BULK PACKS AT BULK PRICES

**MULTICORE SOLDERS LTD.**

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS (BOXMOOR 3636)

**We can deliver from stock:**

This **NEW COMPLETE** Tape Recorder at only

**35 gns.**

Complete with Microphone and Tape.




**PLAYTIME PLUS**

by Tape Recorders (Electronics) Ltd.

**EASY H.P. FACILITIES**  
£5.10.0 deposit and 12 monthly payments of 5/4 or any period up to 18 mths.

Complete and ready to use with a self-contained wide range amplifier and high flux elliptical loudspeaker. Simple to operate—joystick control. Elegant 2-tone suitcase only 12½ in. x 10 in. x 5½ in., weighs less than 20lb. A.C. mains. A completely BRITISH MADE Tape Recorder.

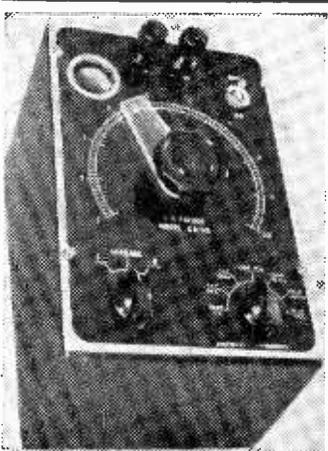**E. & G. MAIL ORDER SUPPLY CO.** The Radio Centre  
33 Tottenham Court Road, London, W.1. Tel. MUS 6667



**CR50 BRIDGE**

Measures capacitance from 10 pFd to 100 mFd and resistance from 1 ohm to 10 megohms in four-teen ranges. Neon leakage test for condensers. Operates from 200/250 volt A.C. mains. Indication of balance is given by magic eye. Specially designed for bench use, with case and panel of steel finished black wrinkle. Complete with all valves and instructions. PRICE £6/19/6, plus 4/6 carr./packing. Hire Purchase: £3 deposit and four monthly payments of 22/-.

**SIGNAL GENERATOR, SG50,** covers 100 kc/s to 80 Mc/s in six bands on fundamentals, either unmodulated or internally modulated with 400 cps. Uses two type Z77 valves and SenTerCel rectifier and double wound mains transformer. In olive green metal case with carrying handle, size 12in. x 8in. x 4in. deep. Front panel of green perspex engraved in white. We claim this to be the best value on the market at only £7/19/6, plus 6/- carr./packing.

Please send stamped, addressed envelope for illustrated leaflets by return post.

Obtainable from sole London stockist: **Charles Britain (Radio), Ltd., 11, Upper Saint Martins Lane, W.C.2,** or direct from the manufacturers—

**GRAYSHAW INSTRUMENTS**  
54, Overstone Road, Harpenden, Herts.

**REPANCO HIGH GAIN COILS**



**DUAL RANGE MINIATURE CRYSTAL SET COIL,** with circuit. Type DRX1, 2/6.

**DUAL RANGE COIL** with reaction. With 2 mains and 2 battery circuits. Type DRR2, 4/-.

**MATCHED PAIR DUAL RANGE T.R.F. COILS,** with reaction; with battery and mains circuits. Type DRM3, 8/- pair.

**STANDARD I.F. TRANSFORMERS.** Type S.E. 1 1/2 in. x 1 in. x 2 1/2 in. Pre-aligned, 465 Kc/s., 13/6 pair.

**MINIATURE I.F. TRANSFORMERS,** Type M.S.E. 1 1/2 in. x 1 1/2 in. x 1 1/2 in. Pre-aligned, 465 Kc/s., 12/6 pair.

**FERRITE ROD AERIAL,** Type FR1. Long and medium wave. Complete with fixing brackets, 12, 6.

- ★ All coils wound on low loss formers.
- ★ Individually tested and guaranteed.
- ★ Post 3d. on all orders. ★ Trade supplied.

Distributed by:  
**RADIO EXPERIMENTAL PRODUCTS LTD.**  
33, MUCH PARK STREET, COVENTRY  
Telephone: Coventry 62572

**BENDIX TX**

T.A. 124  
Covers 300 kc/s-300 kc/s, 3 Mc s-1.8 Mc s, 4 Mc s-6.4 Mc s, 6 Mc s-9 Mc s in 4 Channels. Valve line up: 2 807, 4 12SK7

**BRAND £6 NEW**

- R1155 RX.**—With valves. Nice condition. £8/10 -.
- T1403 TX.**—In Brand New Condition. Less valves, £3 10 -.
- RADIO ALTIMETERS.**—Brand New Chassis, U.S.A., at 22/6 each.
- INDICATOR TYPE 165 A.**—Complete with VCR517C, at £3.
- AMPLIFIER TYPE 1553 A.**—With 2 Battery Valves, at 21 each.
- TR9 RX.**—Battery RX, complete with valves, 15 -.
- RC348L (1 only).**—230-250 A.C. Input. A Bargain, £15.
- RX TYPE 71.**—V.H.F. RX. Break-down value at 9 - 45 MCGS STRIP (Pye).—Less valves at 15 - each.
- R.F. UNITS.**—21 and 25 Unit. at 15 - ; 26 at 35 - Brand new in maker's cartons.
- AMPLIFIER TYPE 1135 A.**—Less valves at 7 6 each.
- RESISTORS.**—Mixed: 1, 1, 1, 2 watts. Carbon, 12 6 per 100.
- CONDENSERS, ELECTROLYTIC.**—B.E.C. 450 v. wkg. 8 mfd., 2 - ; 8 8 mfd., 3 9 ; 8 16 mfd., 4 - ; 16 - 16 mfd., 4 6.

**VALVES**

EF50	4/-	SP61	2 6	6SH7	4 6	EA50	2/-
EF37A	11/-	SP41	2 6	6SK7	4/-	6SL7	7/-
EF36	4/-	EB33	7 6	6Q7	8 6	6SN7	9/-
EF52	5/-	EP30	7 6	5Z4	8 6	1T3	7/-
EL32	6/-	6K7	6	5L4	8 6	15G	7/6
EL50	9/-	6K4	11	VU3	8 6	1R5	7/6
EC52	5/-	6V6	8 6	KT69	12/-	384	8/6

**VINER'S (Middlesbrough)**  
Radio Government Surplus Electrical  
26, EAST STREET, MIDDLESBROUGH,  
Telephone: MID. 3418.

*Electrical Interference?*

IF YOUR RADIO RECEPTION IS MARRED BY NOISE FJT AN

**EDDYSTONE**

**MAINS FILTER**




Cat. No. 732, specially designed for use with receivers covering short and medium wavelengths. This well screened Filter Unit is most effective in suppressing mainsborne electrical interference. Finished ripple Brown and supplied complete with flexible lead and socket.

**£2 15s. 0d.**

For address of nearest stockist please write to:  
**STRATTON & CO. LTD.**  
ALVECHURCH ROAD, BIRMINGHAM 31

Great Britain's Valve Mail-Order House

AC6/Pen	8/6	KL35 11/-	UF41 10/-	VR137 6/6
ACSP3	11/6	KT781 12/6	UU7 10/-	VR150 11/6
ATP4	5/6	KT74 10/-	VP23 9/6	VR52/
ARP4	5/6	KTW62 8/6	VP41 10/6	VL32 9/6
ARP5	8/-	KTW73	VP133 10/6	VU39 10/6
ARP12	7/-	KTW74	VR18/	VU111/
D41	8/6	KTZ41	SG215 8/6	V1907 5/-
D63	8/-	KTZ63 8/6	VR19/	VU120A
DD41	9/6	L13 10/6	FM2 7/6	W17 6/6
DH73	10/-	MSPen	VR35/	W76 10/3
DL2	8/6	(7Pin)13/6	QP21 8/6	W77 10/-
DL63	10/-	N14 8/6	VR37/	W81M 9/-
DL74	10/-	NR45 12/-	MH4 9/-	XH(1.5) 6/-
DDT411/6		P41 8/-	VR53/	XP(1.5) 6/-
DDT13	11/6	PD220 12/-	EF93 9/6	X22 10/6
ECC31	12/6	Pen25 9/6	EB34 5/6	X61 10/6
ECL80	12/6	Pen46 10/6	EBC33 7/6	X63 10/-
EC31	12/-	PenDD	EF36 5/9	X71M 9/-
EF22	9/6	2530 10/6	VR56/	X73 11/6
EL2	11/6	PenDD	EF36N 7/6	Y63 8/-
EL32	9/6	1360 11/-	VR57/	0Z4 6/-
EL35	11/-	QP22B	EK32 9/6	01A 3/-
EL50	7/-	R3 10/6	VR65/	1H6 3/-
H63	7/6	SP4F 10/-	SP61N 6/6	ILA 5/-
HL4	10/-	SP42 10/-	SP81 5/6	1LN5 6/6
HL13	9/6	SP42 10/-	VR85A/	2A3 10/-
HL41	8/-	CV45 6/6	SP41 4/9	2A6 2/-
HL41DD	10/6	TH2321 10/6	VR89/	2A7 3/-
HL133DD	8/6	TTH 3/-	VR78/	6A7 11/-
HL1320 9/6	U21 12/-	HLDD1320 22 11/6	D1 4/6	6AC7 15/-
HLDD1320	11/-	U71 10/6	VR91 (Sollid)	6AK5 10/-
KT32 10/6	74 10/-	VR135 5/6	VR125/	6AK7 15/-
			MSPenB	6AK6 9/6
			6SF5 14/-	6E5 11/-
			6P32 6/-	P2 3/-
			6SF5 14/-	PM12M 5/-
			6P2 5/6	SP2 5/6
			6D12 2/-	SP42 5/-
			6H3 3/-	

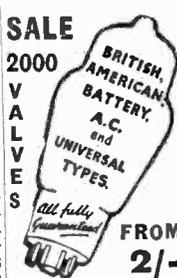

FROM 2/-

DEMOBLED VALVES MANUAL 2/6

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.T.H. Equivalents and Comprehensive Price List. We have still some Valves left at very old Budget Rates (33%) which are actually sold at the old price. (1951 rate.)

B.T.H. GERMANIUM CRYSTAL DIODE. Complete with Blueprint and operating instructions, 2/- Post free.

ROD ANTENNAS. 1ft. sections interlocking and extending, copper plated steel. BARGAIN. Dozen 2 6. Post free.



SERVICE SHEETS The one you require enclosed if available in a dozen assortment of our best choice 10 6.


A.C. D.C. NEON TESTER SALE PRICE 6/- This new model is specially designed for one-pole tests on mains incorporating a highly sensitive neon tube-striking voltage 100/500 v. A.C. D.C. Also suitable for indicating polarity on D.C. current, when the glow of the lower electrode will indicate the negative pole. Post 6d. Limited quantity.

Half Price 6/- Usual 11/3.

**BULLS VALVES**  
476, HIGH ST., HARLESDEN, N.W.10

PIFCO

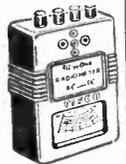All-in-one Radio-meter A.C./D.C. Tests everything in Radio. Complete with Test. prods. 29/6 Post 1/6.



Q-MAX Chassis Cutters with Keys The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: A die, Allen screw, and punch and key simple. Prices incl. key: 1in. 12/4; 1 1/2in. 12/4; 1in. 13/4; 1in. 11in. and 1 1/2in. 16/- each; 1 1/2in. and 1 1/2in. 18/- each; 1 1/2in. 19/8; 2 3/32in. 31/8; 2 1/2in. 36/9; 1in. square, 24/3. Post 1/-.

7/6 REDUCED FROM 21/- 7/6

Pre-heated Electric Soldering Irons 23 v. 36 Watts. Press button switch fitted. Corrosion-free bit. Specially designed for fine work. Limited quantity.

NEW Electric Soldering Iron with NEON indicator in the Handle. NEW. 25 Watts 200/220 v. 230/250 v. 4 ozs. 9 1/2in. long. 6ft. cable. 12 months' guarantee. Complete 19/3 Post 1/-

**NEW!** EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Special prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—these Practical Courses are intended for YOU—and may be yours at very moderate cost.

EASY TERMS FROM 15/- A MONTH

All lessons and equipment supplied immediately and become your own property.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:  
To: E.M.I. INSTITUTES, Dept. 32X, Grove Park Road, London, W.4.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
SUBJECT(S) \_\_\_\_\_




EXPERIMENTAL OUTFITS:

- RADIO (basic)—A course in basic principles.
- RADIO—Instruction and equipment from which you build a Radio Receiver.
- TELEVISION—Instruction and equipment for building a Television Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

**E.M.I. INSTITUTES** The only Postal College which is part of a world-wide Industrial Organisation

# Turn SPARE time to CASH!

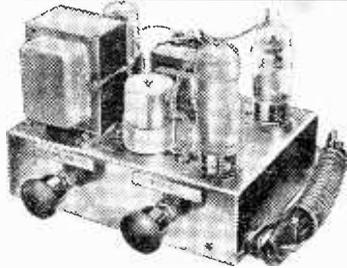

**63/- ONLY**

**PLUS 2/- FOR Postage & Packing**

**EASY TO READ WIRING CHART AND PARTS LIST 6d. (Post Free.)**

**.. FOR THIS MULTI-PURPOSE AMPLIFIER UNIT KIT!**

The CHEAPEST 3-Valve Amplifier on the market—can be built in 2-3 hours WITHOUT previous radio experience! High Gain, Negative Feedback and Ready-drilled Chassis which is not "live." Ideal for amplifying Grams, small P.A. Equipment, Baby Alarms, Office Intercom Sets, etc. An ABSOLUTE BARGAIN at this price—get YOUR order in NOW to avoid disappointment!


.....

## PROFESSIONAL 3 VALVE MAINS SET IN SUPERB CABINET FOR ONLY ..

A straight T.R.F. A.C. or A.C./D.C. Mains Set—requires no radio knowledge to assemble. Easy to read Diagram takes you step by step. Only tools needed are pliers, Screwdriver and Soldering Iron. ALL parts in stock NOW. Order AT ONCE stating which type of set is required A.C. or A.C./D.C. Mains—these are the sets to SHOW to FRIENDS! Wiring Diagram and Parts List, 1/-, Post FREE.

**97/6**

**PLUS 2/6 FOR Postage & Packing.**

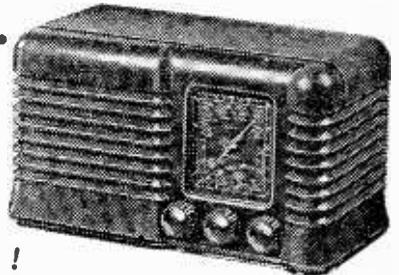

**SATISFACTION OR CASH REFUNDED!**

**WRITE NOW TO B'HAM'S LARGEST WALK-AROUND RADIO STORES!**

**NORMAN H. FIELD**

MAIL ORDERS: 97, STRATFORD RD., BIRMINGHAM 11. Tel: 3619  
CALLERS: 68, HURST STREET, BIRMINGHAM, 5. Mid 3619

# HENRY'S

(RADIO LTD.)

### CATHODE RAY TUBES

(Brand New)

- VCR97 (slight cut-off) 15/-
  - VCR97 guaranteed full T/V Picture ... 40/-
  - VCR17C, guaranteed full T/V Picture ... 35/-
  - VCR139A, guaranteed T/V Picture ... 35/-
  - 3BP1, guaranteed full T/V Picture ... 30/-
- Carr. & packing on all tubes, 2/-.

### B.S.R. 3-SPEED AUTO-CHANGERS

These are brand new in original cartons. Plays mixed records. Cream finish. List price £16.10.0 Our Price **£9.19.6**, carr. 3/-.

### WALKIE-TALKIE SETS TYPE 38

We are able to offer the above "38" sets complete with 5 valves, 4 VP23 and ATP4. Throat Microphone, Junction Box and Whip Aerial, all in good condition. All sets air tested and guaranteed. **59.6**, carr. 5/- (Suitable new batteries and leads, **£1.2.6** set.)

All items sold separately.

### "RF 26" F.M. CONVERTER UNIT 88/100 Mc. s

This well-known RF26 Unit is now adaptable for F.M. reception using 2 I.F. stages and separate local Oscillator and tuned by a Muirhead graduated Ver-

nier drive. Can be converted at low cost of 92.6. Send 1.6 for 8-page Descriptive booklet containing full wiring instructions, circuits and layout diagrams.

#### COMPONENTS OFFERED TO COMPLETE F.M. UNIT

New RF26 UNIT WITH THREE VALVES — VR137, EF54, EF54. Chassis stamped out for easy conversion **£1.15.0**

INSTRUCTION BOOK with technical circuit and complete layout **1/6**

COMPLETE SET OF ALL COMPONENTS FOR CONVERSION. Including 2-6BA6s and EB91, tuning condenser, I.F.T's and OSC. coils, resistors and fixed condensers, pluxs, wire and tag strips ... **£4.12.6**

SPECIAL OFFER OF ALL ABOVE ITEMS, INCLUDING RF26 and book ... **£8. 5.0** postage 3/-

CHARGE FOR ALIGNMENT WHEN COMPLETED **7/6**

COMPLETE SET as above and 6 valves — Aligned and ready for use **£9.10.0**

N.B. VOLTAGE REQUIRED 250v. 50 mA. and 6.3v. 2 amps.

### VALVES — VALVES — VALVES

WE HAVE OVER 50,000 AMERICAN AND ENGLISH VALVES IN STOCK AT VERY LOW PRICES. SEND 3d. FOR 28-PAGE ILLUSTRATED CATALOGUE.


#### TR1196 RECEIVER

Receiver 27.73. This is a six-valve superhet receiver with 465 kc/s I.F.'s. Complete with all valves—2 EF36, 2 EK32, 2 EF36,

1 EBC33. In brand new condition with full conversion data. SPECIAL OFFER 27/6 (plus 2/6 carriage).

### CRYSTAL MICROPHONE INSERTS

**8/6** POST FREE **8/6** POST FREE

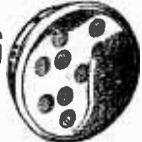

Ideal for tape recording and amplifiers. No matching transformer required.

#### SPECIAL REDUCTION

- 1A7GT, 1N5GT, 1H5GT, 1A5GT (1C5GT or 1Q5GT) 40/- Set
- 10 EF50 (Ex-Brand New Units) 5/- each ... 45/- ..
- 6K8G, 6K7G, 6Q7G, 5Z4G, 5Y8G ... 37/6 ..
- 1R5, 1S5, 1T4, 154 or (3S4 or 3V4) ... 27/3 ..
- TP25, HL23 DD VP23, PEN25 (or QP25) ... 25/- ..
- 6K8G, 6K7G, 6Q7G, 25A0G, 25Z5 (or 25Z6G) ... 37/6 ..
- 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35LGT (or 50L6GT) ... 37/6 ..
- 12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35LGT (or 50L6GT) ... 37/6 ..

#### PACKARD BELL AMPLIFIER

Brand new complete with 2BD7 and 6SL7GT and instruction book 12/6. P. & P. 2/-.



# ALPHA FOR ALL RADIO PARTS...

### METAL TUBULAR CONDENSERS (WIRE ENDS)

Sprague .1 mfd. 350v. ...	9d. ea.
.. .01 .. 1,000v. ...	9d. ea.
.. .02 .. 750v. ...	9d. ea.
.. .05 .. 500v. ...	9d. ea.
.. .001 .. 1,000v. ...	41d. ea.
T.C.C. .01 .. 750v. ...	81d. ea.
Mallory .1 .. 500v. ...	1/- ea.
T.C.C. Metallite, .02 mfd. 350v. ...	9d. ea.
Sprague, .5 mfd. 350 v. ...	6d. ea.

### ELECTRAN TRANSFORMERS

Type No. L.P.6. Rating. 350v/0v, 350v at 80 Ma; 6.3v. at 5 A., 5v. at 3 A. Finish, half shrouded. 21/- ea.
Type No. L.P.1. Rating. 250v/0v, 250v at 60 Ma.; 6.3v. at 3 A., 5v. at 2 A. Finish, fully shrouded. 14/9 ea.

Standard 1 1/2in. brown knobs ...	5/6 doz.
Zenith Dropper, 910 Ω ...	2/6 ea.
Bakelite case. Double coil buzzers ...	2/6 ea.
Eric Dropper, 1,340 Ω, 150 Ω ...	2/6 ea.
Box. 4 BA Nuts and Bolts Intermediate Transformers. Ex. Equip. ...	1/- ea. 2/- ea.

**AMERICAN RELAY**  
45 Ω Impedance with leads No. AZ0545 ... 1/9 ea.

**IRON LEADS**  
Black and white flat iron leads, bonded ends ... 1/3 ea.

**POTENTIOMETER PANEL**  
4 Potentiometers on Panel. 50 K Ω SP; 750 Ω W/W; 25 K Ω Carbon; 5 K Ω W/W. All with long spindle, with leads of different colours terminating in an 11-pin plug ... 7/6 ea.

### SPECIAL PURCHASE!

**B.S.R. MONARCH RECORD CHANGER.**  
Model U6 fitted H.P.G. 37 Cartridge.  
**3 SPEEDS:**  
33 r.p.m., 45 r.p.m., 78 r.p.m.  
Complete with full instructions.  
**£9.19.6** Carriage 3/6.

**HYDROMETER** by Exide (Canada), complete in wood case ... 7/6 ea.

**JUNCTION BOXES**  
Type 5X/234 20-Way ... 1/6 ea.  
**BELL TRANSFORMER "CONCORDIA"**  
3v., 5v., 8v., 1 amp. fused. In bakelite case ... 8/6 ea.  
**EF50 PRE AMPLIFIERS, Less Valve**  
Coaxial input and output complete with plug for H.T. and L.T. ... 6/- ea.

**METERS**  
0-50 Ma. Milliammeter by Ferranti—Panel Mounting ... 7/6 ea.  
**SURPLUS GEAR PARCELS**  
We have found from time to time stocks of components stripped from Ex-Government equipment, along with discontinued lines, etc. These are in small quantities and therefore unprofitable to advertise. To make room for new items we offer at less than cost parcels of these components at ... 10/- ea.

**PUSH BACK WIRE**  
Size 7/012. Available in colours: Blue, Green, Red ... 21d. yd.  
Hand Microphone Bakelite switch in handle ... 7/6 ea.  
High to low impedance headphone units (insert in lead) ... 3/6 ea.  
Rubber grommets, assorted Bakelite Needle Cups ... 6d. doz. 1d. ea.  
Sleeving, various colours. 1 mm. ... 1d. 1/2 ft.  
Mains Switch, 2-hole fixing S.P. ... 1/6 ea.  
Yaxley Switch, 3 P., 3 B., 3 W. ... 1/6 ea.  
Yaxley Switch, 1 Pole 3-Way ... 1/9 ea.  
Waxed Carton, 9 Mel., 450v. ... 1/6 ea.  
Westcoats, WX12, W4, WX6 ... 9d. ea.  
Collaro, Hi-Fi Pick-up ... 32/6 ea.  
Belling Lee, Type L709, Connector. Listed 8/9. Our Price 4/6.

**TERMS:** Cash with order or C.O.D. Postage and Packing charges extra as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage, 2/3. **MAIL ORDER ONLY.**

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."

# ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

## PREMIER RADIO COMPANY

B. H. MORRIS & CO., (RADIO) LTD. Telephone: AMBASSADOR 4033 PADDINGTON 3271-2

OPEN TILL 6 P.M. SATURDAYS (Dept. P.W.) 207, EDGWARE ROAD, LONDON, W.2

BUILD THESE NEW PREMIER DESIGNS

### 3-BAND SUPERHET RECEIVER

MAY BE BUILT FOR **£7.19.6** Plus 2/6 Pk. & Carr.

Latest type Superhet Circuit using 4 valves and metal rectifiers for operation on 200/250 volts A.C. mains. Waveband coverage — short 16-50 metres, medium 180-550 metres, and long 800-2,000 metres. Valve line-up 6X8 freq. changer, 6K7, 1F, 6Q7 Detector AVC and first AF. 6V6 output. The attractive cabinet to house the Receiver size 12in. x 13in. x 6in. high. 6in. deep can be supplied in either WALNUT or IVORY BAKELITE or WOOD.

INSTRUCTION BOOKS 1/- each, (post wiring diagrams, also a detailed Stock

### TRF RECEIVER

MAY BE BUILT FOR **£5.15.0** Plus 2/6 Pk. & Carr.

The circuit is the latest type TRF using 3 valves and Metal Rectifiers for operation on 200/250 A.C. mains. Wave band coverage is 180/550 metres on medium wave and 800/2,000 metres on long wave. The dial is illuminated and the Valve line-up is 6K7 H.F. Pentode 6J7 Detector and 6V6—Output.

(free) which includes Assembly and List of priced components.

### 4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pk. & Carr.

Valve line-up 6SL7, 6V6 and 6X5. FOR A.C. MAINS 200/250 VOLTS. Suitable for either 3-ohm or 15-ohm Speakers. Negative feedback. Any type of pick-up may be used. Overall size 9 x 7 x 5in. Price of Amplifier complete, tested and ready for use, £5.5.0 plus 3/6 pkg. and carr.

### CABINETS—PORTABLE

Model PC/1  
Brown Rexine covered, 15 1/2in. Overall dimensions 15in. x 13in. x 5in. Clearance under lid when closed 2in.

Model PC/2  
Grey Lizard Rexine covered, 45/- Overall dimensions 15in. x 13in. x 6in. Clearance under lid when closed 3in.

Model PC/3  
Rexine type covering in various colours, 60/- Overall dimensions 16 1/2in. x 14 1/2in. x 10 1/2in. Clearance under lid when closed 6in.

All the above Cabinets are supplied with Panel. Carrying Handle and Clips. Packing and Postage 2/6.

Send for details of the Premier Wide angle Television design which may be built for £30.

### ALL-DRY BATTERY PORTABLE RADIO RECEIVER

4 miniature Valves in a Superhet Circuit covering medium and long waves. Rexine covered Cabinets 11 1/2in. x 10in. x 5 1/2in. in two contrasting colours. Wine with Grey Panel, or Blue with Grey Panel, please state choice when ordering. The SET MAY BE USED EVERYWHERE—home, office, car or holidays. INSTRUCTION BOOK, 1/6 (Post free) which includes Assembly and wiring diagrams, also a detailed Stock List of priced components.


**£7.18.0** Plus 2/6 Pk. & Carr.

### DECCA MODEL 37A DUAL SPEED RECORD PLAYER

Includes turn over crystal pick-up with sapphire stylus and a light-weight, plastic, spring-balanced arm. Heavy gauge pressed steel case with brown enamel finish in good quality for operation on A.C. mains 200/250 v. 50 c.p.s. Supplied complete, £6.19.6. Plus pkg. and carr. 5/-.

★SEND 21d. STAMP FOR OUR 1955 CATALOGUE.

# THE NEW **Osram** KT55 output valve

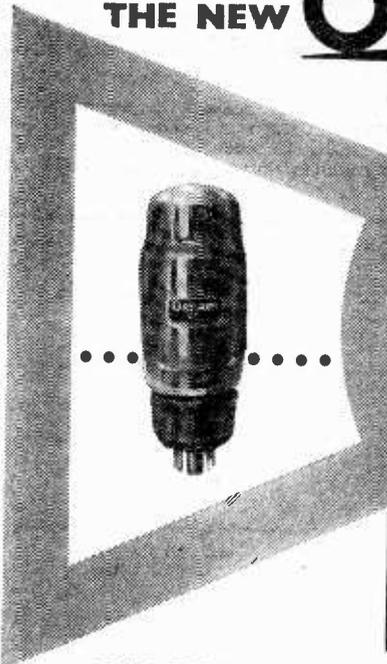

The new Osram KT55 beam tetrode has a heater rating of 0.3A, 52V. It is intended for use in a series heater chain for either DC or AC/DC mains amplifiers.

Outstanding characteristic is its high power output (25 watts per pair) with minimum distortion at comparatively low H.T. voltage (200V).

The Osram KT55 will form a popular companion-type to the well-known KT66. Two valves, type KT55, will supersede the need for four valves, type KT33C, in AC/DC amplifiers required to deliver up to 25 watts at 200 volts.


**KT55. List price: 25/- plus P. Tax 8/2**

**HEATER**

I<sub>h</sub> ..... 0.3 ..... A  
 V<sub>h</sub> ..... 52 ..... V

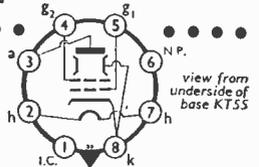**TYPICAL OPERATION**

Tetrode connection. Push-pull.  
 Data per pair unless otherwise stated.



	Quiescent	Max signal	
V <sub>a</sub> (b) .....	225	215	V
V <sub>a</sub> .....	200	190	V
V <sub>g2</sub> .....	200	190	V
V <sub>in</sub> (g <sub>1</sub> -g <sub>1</sub> ) (pk) .....		28.8	V
V <sub>g1</sub> (approx.) .....	20.5	23.5	V
I <sub>a</sub> .....	220	225	mA

	Quiescent	Max signal	
I <sub>g2</sub> .....	15	45	mA
R <sub>k</sub> (per valve) .....	175	175	Ω
RL (a-a) .....	2	2	kΩ
P <sub>out</sub> .....	25	25	W
D .....	2	2	%
Z <sub>out</sub> .....	9	9	kΩ

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2


## !! HOME CONSTRUCTORS !!

*You can assemble the Stern's Fidelity Tape Recorder for only £40*


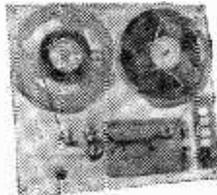
### !! IT ONLY NEEDS CONNECTING UP !!

This 2-Speed Twin Track Recorder although supplied at a Genuinely Low Price, provides absolute Fidelity Recordings, and in addition to being completely dependable has a performance at least equal to Recorders marketed at a far higher price. The actual assembly of the Recorder is simple, and only involves a few connections. The Truvox Tape Deck and the Quality Amplifier are supplied tested and ready for use, and all that is required to complete the Recorder is to connect the two together (a connection chart is supplied for this purpose) and secure them by the screws provided into the Attache Case. The items



Illustrated and described below form the complete equipment.

**TRUVOX TAPE DECK MODEL Mk. III/TR7u**

This is Truvox's new "small" design being only 14in. x 13in. The whole instrument is built to close engineering limits resulting in the minimum of "wow" and "flutter" values. It will play the NEW PRE-RECORDED TAPES and takes all standard tapes up to 1,200ft.

**SCOTSBY MAGNETIC RECORDING TAPE**  
 Supplied complete with a 1,200ft. reel of Scotsboy Tape. In addition, the Recorder will take all standard makes of tapes.


**PORTABLE ATTACHE CASE**

This, as may be judged from the illustration above, is a neat, compact and attractively finished case, being covered with maroon velveteen and having an Ivory coloured speaker escutcheon. It contains concealed pockets to accommodate the Microphone, Mains Lead and a spare 1,200ft. reel of tape.

SEND S.A.E. FOR DESCRIPTIVE LEAFLET INCLUDING PRICE DETAILS & H.P. TERMS

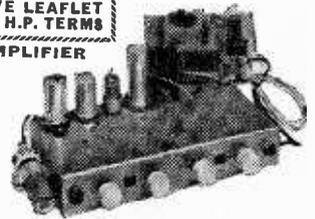**MODEL TRIF QUALITY AMPLIFIER**

Expressly designed to correctly operate with the above Truvox Deck for recording and playback. Supplied complete with Elliptical Speaker and has level response from 60-10,000 c.p.s. Hum level 50 db down at 4 watts. Incorporates efficient tone control arrangement and MAGIC EYE LEVEL INDICATOR. Valve line-up: EF86, EC63, EL84, 6Y3, EM34 provides 4 watts undistorted.



**MODEL MIC33/1 ACOS CRYSTAL MICROPHONE**  
 A highly sensitive Mike which accurately matches the input arrangement of the Amplifier.

It can be supplied complete and ready for use for £50 as illustrated above

## STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4  
 Tel.: CENTRAL 5812-3-4.

# Bring your equipment up to date with **ACOS** REPLACEMENT PICK-UP HEADS

If you already own a fine radiogram or record-player you now have the opportunity of rejuvenating it — of bringing it right up to date for a quite modest sum. Acos Hi-g crystal pick-ups are now available in a range of specially designed "plug-in" models to suit most famous makes of record reproducing equipment.

These Acos "Hi-g" pick-ups, you will find, represent a truly phenomenal advance in pick-up design—with regard to both reproduction and tracking characteristics (so important with many of the new microgroove recordings). Ask your Dealer!

MODEL		
HGP 37-1 Collaro		A Hi-g pick-up head incorporating the HGP 37-1 turnover cartridge with cantilever sapphire styli. Designed for both standard and microgroove records. Will fit Collaro units RC 532 : AC 534 : AC3/534 : 3RC 532 and the Studio pick-up. Available in cream or walnut. <i>Ask for Data Sheet No. 4800.</i>
HGP 37-1 Garrard		A Hi-g pick-up head incorporating the HGP 37-1 turnover cartridge with cantilever sapphire styli. Designed for both standard and microgroove records. Will fit Garrard units RC 75M : RC 80M : RC 90 : RC 111 : Model TA. <i>Ask for Data Sheet No. 4800.</i>
HGP 39-1		Hi-g pick-up heads incorporating cantilever sapphire styli. Separate heads for standard and microgroove records. Will fit the Acos GP 20 pick-up arm and the Garrard C type adaptor. Used on the following units: RC 72A ; RC 75A ; RC 80 ; and the Model M unit. Can be used on any units which at present use the GP 19 heads. <i>Ask for Data Sheet No. 4400.</i>
HGP 35-1		Separate plug-in type Hi-g heads for standard and microgroove records ; fitted with cantilever sapphire styli. The crystal unit is identical to that of the HGP 39-1 above. Can be used on Garrard units RC 75M ; RC 80M ; RC 90 ; RC 111 ; and the TA player. <i>Ask for Data Sheet No. 4000</i>
HGP 41-1		Separate Hi-g plug-in type heads for standard and microgroove records incorporating the crystal unit as used in the HGP 39 pick-up head. Will fit Collaro units RC 532 ; AC 534 ; AC3/534 ; 3RC 532. Available in cream or walnut. <i>Ask for Data Sheet No. 4500.</i>
HGP 45		Separate Hi-g pick-up heads for either standard or microgroove records. The crystal unit is identical to that used in the HGP 39-1 head. Will fit Garrard units RC 80 ; RC 72A ; RC 75A ; and the Model M player. Can be used on any unit which at present uses the Garrard C adaptor with GP 19 heads. <i>Ask for Data Sheet No. 4600</i>



... always well ahead

**PRICE 32/6 (PLUS 10/5 P.T.)**  
for all types except HGP 39  
models which are  
**32/- (PLUS 10/3 P.T.)**

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

**COSMOCORD LTD. ENFIELD MIDDLESEX.** ● Tel :— Enfield 4022

# PRACTICAL WIRELESS

EVERY MONTH  
VOL. XXXI, No. 565, JULY, 1955

COMMENTS OF THE MONTH

EDITOR: F. J. CAMM.

23rd YEAR  
OF ISSUE

BY THE EDITOR

## V.H.F. and F.M.

SINCE the opening of the new V.H.F. station at Wrotham, the first of ten to be completed by the end of next year, we have received a large number of letters on the subject. V.H.F. means very high frequency, or, in other words, very short wavelengths, and the new V.H.F. dials will have a band marked with figures of from 88 to 100. These figures represent frequencies, very high frequencies, in millions of cycles per second, and they are used on the dial because it would be cumbersome to use wavelengths. A frequency of 88 megacycles per second, for example, corresponds to a wavelength of 3.4090 metres, and it would be inconvenient to calibrate a dial in such short wavelengths. The ten V.H.F. stations will be Wrotham, Pontop Pike, Divis, Meldrum, and North Hessery Tor, Sutton Coldfield, Norwich, Blean Plwy, Holme Moss and Wenvoe and they are to operate between 88 and 100 megacycles per sec. There are hundreds of thousands of listeners in the United Kingdom who cannot rely upon interference-free reception of the BBC programmes and, they have to tolerate fading and the interference of unwanted foreign programmes. It is for this reason that V.H.F. stations are being erected. As V.H.F. transmissions cannot normally be received over long distances, it does not matter how many V.H.F. stations may spring up on the Continent because they are unlikely to cause serious interference here.

Frequency modulation reduces still further the likelihood of interference from unwanted programmes and also helps to reduce other forms of interference, caused by domestic electrical appliances, so that the programmes can be heard against a background of silence. It is not practicable to use F.M. on the long-wave or medium-wave bands, but it can be used in the V.H.F. band. When V.H.F. comes to your area you will need either a new set or an adaptor to receive it. We shall describe how to make V.H.F. tuner units and the industry itself is now producing sets which will tune to the new V.H.F. bands, as well as to the present medium and long wave. They are also producing adaptors. In certain circumstances a special aerial will be necessary; it will depend upon local conditions. A V.H.F. aerial will be somewhat similar to a television aerial, although smaller, and it is fixed horizontally. For best results the horizontal

portion should be at right angles to the direction of the transmitting station. Freedom from interference and noise on a V.H.F. set depends partly on the strength of the signal it gets from the transmitting station, which in turn depends on the receiving aerial. It follows that the better the aerial the less will be the unwanted noises. Owing to the nature of the V.H.F. waves you may find that poor reception may be much improved if you move the aerial only a few feet. This can be done quite readily, as the V.H.F. aerial is very much shorter and easier to handle than the aerial required for medium and long wave reception. If you are satisfied with present reception on your receiver there is no need to change over to V.H.F., but it is important to remember that better quality reception, particularly of music, will be generally available from the V.H.F. transmitters. The normal medium-wave receiver needs to be designed to reject as far as possible interference from foreign stations using wavelengths close to those of BBC stations. In designing a receiver selective enough to do this quality suffers, and many of the overtones of music and speech are thus lost. A V.H.F./F.M. receiver gives reception much nearer to the original.

### RADIO AND TV SALES

RADIO and radiogram sales have increased to 133,000 and 132,000 respectively, whilst television has been raised by 6,000 in January to 102,000 and 11,000 in February to 98,000. These figures, of course, relate to the month of March. The latest B.R.E.M.A. retail market survey shows that of receiver sales 41 per cent. were bought on hire purchase terms, as were 62 per cent. of the total sales of radiograms and 59 per cent. of the total sales of television receivers.

Sales remained remarkably stable during the first two months of the year; radiograms and television receiver sales for March fell by 13 per cent. and 23 per cent. compared with February—seasonal falls which could be expected—but radio receiver sales have resisted the normal trend by scarcely declining at all. Compared with the first quarter of 1954, sales of radio receivers and radiograms have risen from 254,500 to 384,000 and television from 168,500 to 286,000.—F. J. C.



# Round the world of WIRELESS



## Broadcast Receiving Licences

THE following statement shows the approximate number of broadcast receiving licences in force at the end of March, 1955. The grand total of sound and television licences was 13,980,496.

Region	Number
London Postal	1,465,488
Home Counties	1,413,123
Midland	1,142,923
North Eastern	1,515,180
North Western	1,165,583
South Western	947,971
Wales and Border Counties	591,786
<b>Total England and Wales</b>	<b>8,242,054</b>
Scotland	1,015,709
Northern Ireland	218,967
<b>Grand Total</b>	<b>9,476,730</b>

## Modifications to Studios

MODIFICATIONS are to be made to the BBC Studios One and Two at 201, Piccadilly, London, and building work is in progress.

Studio One, which is used mainly for dance-band shows, is having its stage enlarged and fixed audience seating installed instead of the loose chairs used previously

by invited audiences. Studio Two will be employed more as a drama studio. It is being sound-proofed and this will necessitate the construction of an inner shell within the existing studio.

## National V.H.F. Coverage

THE BBC announces that it has placed a contract with Messrs. Gee, Walker and Slater, Ltd., of 100, Park Lane, London, W.1, for the building of an extension to the Wenvoe television transmitting station to house the V.H.F. sound transmitters shortly to be installed there. Messrs. Gee, Walker and Slater, Ltd., built the original Wenvoe station.

## Commonwealth Association in Air Radio

THE second meeting of the Commonwealth Association in Air Radio has been held in Sydney, Australia.

This association was inaugurated in 1954 to enable the companies concerned to make an approach in common to the problems encountered in radio.

## Loudspeaker Installation

"STANTEL" column loudspeakers, produced by Standard Telephones and Cables, Ltd., have been installed in the Royal Festival Hall and the Egyptian Hall of the Mansion House.

## New R.I.C. President

SIR EDWARD APPLETON, G.B.E., K.C.B., F.R.S., has accepted an invitation to become President of the Radio Industry Council in succession to Lord Burghley, who has held office since 1952. Sir Edward was awarded the Nobel Prize for Physics in 1947. He has been Principal and Vice-Chancellor of Edinburgh University since 1949, and for ten years before that appointment was Secretary of the Department of Scientific and Industrial Research.

## Gibraltar-Tangier Link

A NEW direct multi-channel V.H.F. radio-telephone service between Gibraltar and Tangier was opened on May 6th. Previously communication could only be offered by a landline and cable route by way of Spain.

Cable and Wireless, Ltd., have installed new V.H.F. equipment to operate the Gibraltar end of the circuit as well as a 110ft. aerial tower.

## BBC Appointment


DAVID BRYSON, senior talks producer in the Midland Region, has been appointed the BBC's East Anglian representative.

He will take up his duties in Norwich next October.
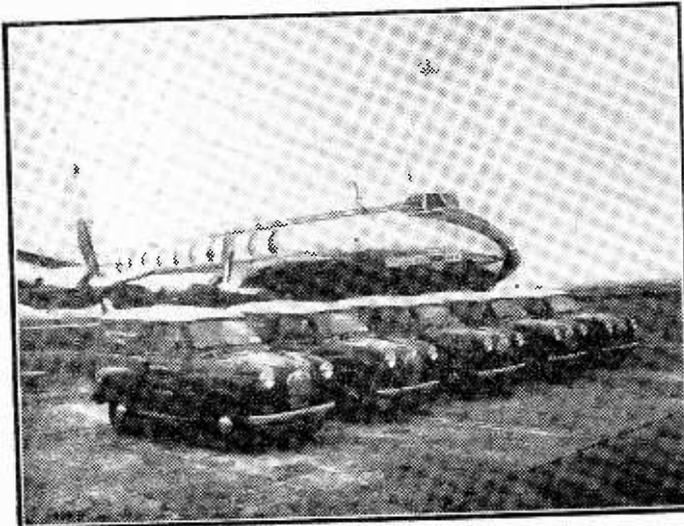
## Aircraft Equipment Service

A FLEET of Austin vans has been put into operation by the Decca Navigator Co., Ltd., for servicing aircraft radio equipment.

The vans operate a service exchange system on the navigator units fitted in aircraft of B.E.A. and other operators.



The fleet of vans used by the Decca Navigator Company Limited. This photograph was taken at London Airport; one of the famous Vickers Viscount aircraft is seen in the background. (See "Aircraft Equipment Service.")

**Radio and Radar for Trawler**

THE radio installation fitted on board the new steam trawler *Marbella* by members of the technical staff of the Hull depot of the Marconi International Marine Communication Co., Ltd., includes radar, echometer, direction-finders, telegraphic and telephonic communication and sound-reproducing equipment.

**Tape Recorders for India**

E. M. I. INTERNATIONAL, LTD., have received an order from the Indian Government on behalf of All India Radio, the official broadcasting organisation, for six Type BTR 2A tape recorders.

**Record Radio Exports**

THE Radio Industry Council has announced that exports of British radio equipment have reached new levels in 1955.

After record-breaking exports last year, valued at nearly £30 million, the provisional value of sales for the first quarter of 1955 is £7,625,000—an increase of more than £650,000.

**Musical Anniversary**

ALAN PAUL celebrated 21 years of writing music for the BBC on May 14th with a programme of his own compositions.

**British Electrical Power Convention**

THE Seventh British Electrical Power Convention and Exhibition is to be held at Brighton from June 27th to July 1st.

The president of the convention is Sir Harry Railing, D.Eng., Hon.M.I.E.E., chairman and managing director General Electric Co., Ltd., and the vice-president is Sir John Dalton, A.M.I.E.E., F.C.I.S., chairman W. T. Henley's Telegraph Works Co., Ltd.

**Export Licensing Control Consolidation Order**

THE Board of Trade announce the making of the Export of Goods Control Consolidation Order, 1955. This new Order incorporates for the convenience of exporters the 1954 Consolidation Order and subsequent amendments.

No change is made in the law but certain simplifications have been introduced in the new Order. In the First Schedule, goods subject to export licensing control to all destinations are marked with the letter A. Goods not so marked are free from export licensing control to the British Commonwealth, the

Irish Republic and the United States of America.

The Second Schedule lists the destinations for which all goods are subject to export licensing control.

**Philips' London and Home Counties Region**

PHILIPS ELECTRICAL, LTD., announce the formation of a London and Home Counties Region which will be concerned with the

aids by technicians of the Glasgow depot of The Marconi International Marine Communication Co., Ltd., on behalf of the Canadian Marconi Company. She has been built at the Linthouse yard of Alexander Stephen and Sons, Ltd.

**British Wireless Dinner Club**

THE 32nd annual general meeting and dinner of the British Wireless Dinner Club at the



The successful E.M.I. trainees. Left to right: T. M. Lawmon, J. Simms, K. A. Battle and W. Arnold. Extreme right are N. A. Robinson and W. W. Egginis, E.M.I. staff instructors. (See "E.M.I. Trainees Win Prizes.")

marketing of all products of the company. It comprises the S.E. section of the country, bounded roughly in the north by the Wash, by the Oxfordshire/Worcestershire border in the N.W. and in the S.W. by Southampton. The area also includes the Isle of Wight and the Channel Islands.

**Union Recognition**

THE BBC announces that under a recently signed agreement the Corporation has recognised the Electrical Trades Union as a negotiating body in addition to the BBC Staff Association on staff matters in respect of all categories of electricians and their assistants employed by the BBC.

**Marconi Installation for Canadian Ferry**

THE new 7,000-ton twin-screw passenger, vehicular and train ferry *Princess of Vancouver* has been fitted with radio communication equipment and navigational

United Service Club on Friday, April 29th, was attended by 126 members under the presidency of Major-General Vulliamy, C.B., D.S.O.

Lord Brabazon of Tara, guest of honour, recalled his early acquaintance with wireless in the first world war.

**E.M.I. Trainees Win Prizes**

OUTSTANDING successes have been scored by E.M.I. trainees in this year's Physical Society Craftsmanship and Draughtsmanship Competition. The official results were:

**Class VI, Senior Grade:**

1st Prize—John Simms.


2nd Prize—Trevor Murray Lawmon.

Equal 3rd Prize—William James Arnold; Kenneth Andrew Battle.

**Class VI, Junior Grade:**

Honourable Mention—Douglas Edward Turner.

# Making a VALVE VOLTMETER

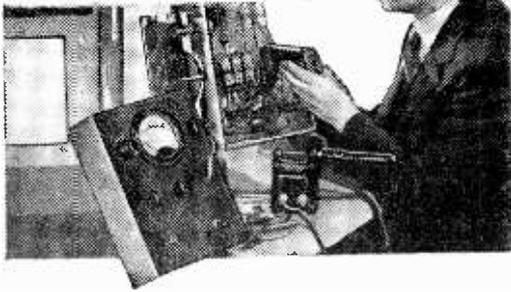

A SELF-CONTAINED INSTRUMENT WITH SCREENED VALVE PROBE. A DOUBLE DIODE AND A DOUBLE TRIODE ARE USED IN THE COMPLETE INSTRUMENT

By F. W. Austin

**B**EFORE proceeding it would be well to compare the performance of a valve voltmeter with a good quality multi-range testmeter. The difference is obvious: the mode of operation. The first depends upon the *vg/ia* curve (or portion of curve) of a valve which is subjected to voltage fluctuations via the mains. The second is limited (ohms per volt) only by the accuracy of the meter movement itself. Thus it would be idle to make claims of *high accuracy* for the instrument about to be described, although a good quality and useful one will be the result.

It is reasonable enough to assume that readers desiring to construct such apparatus are already in possession of a multi-range meter (having provision for ohms measurement), also that they are capable of

interpreting a circuit diagram and have the usual "spares" box.

The circuit diagram is given in Fig. 1, and it will be noted that the meter movement is shown in dotted lines between points marked X(1) and X(2). These actual arrangements are discussed later, where it is proposed to give *practical directions* for utilising any meter movement having F.S.D. of between 100 and 500 microamps. This was undertaken in view of the expensive nature of this item and it is left to the individual to decide what he can afford. The range switch has been omitted from the circuit as this is a simple single-pole type in series with the meter movement (the number of contacts depending on the number of ranges required by the individual). Fig. 2 shows this switch together with the author's layout.

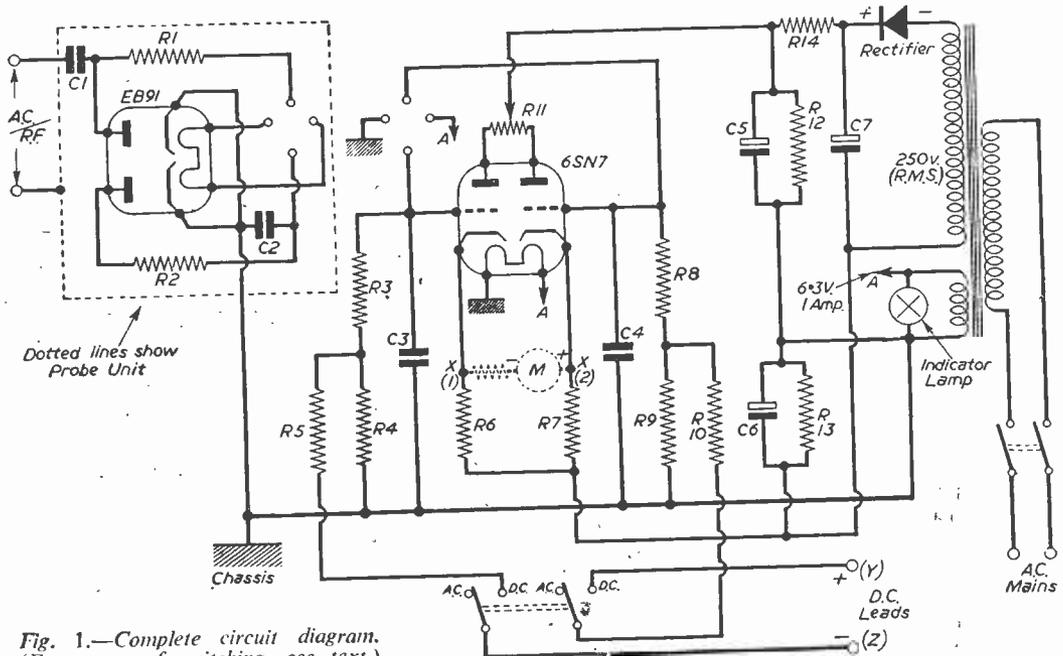


Fig. 1.—Complete circuit diagram. (For range of switching—see text.)

**General Construction**

There is nothing critical about the layout and construction of the main section can go ahead, bearing in mind to leave sufficient space to accommodate probe socket, meter movement and range switch. Having built the main section up to the point of meter connection the various ranges are installed by making use of an external D.C. source.

The actual ranges of the instrument should be between 2.5 volts and 250 volts, but in many cases

resistance across potentiometer for the various ranges. For the 25 volts range (using a 100 microamp movement) a 100K potentiometer will be necessary in this position, but as the author used such a movement correct figures can be given: these are 75K for 25 volts range and *pro rata* for all higher ranges.

Before connecting external voltage to voltmeter D.C. leads these should be "shorted" and the temporary potentiometer opened out to its highest resistance. Set the function switch to D.C. and allow voltmeter to warm up. Adjustment of the "zero-set" control should now be made, at the same time gradually decreasing the resistance of the temporary potentiometer. When the zero has settled the temporary potentiometer should be opened up again and external source applied corresponding to lowest required range (indicated on external voltmeter). The temporary potentiometer is reduced until F.S.D. has been attained on the voltmeter movement; the crocodile clip is removed and resistance across potentiometer is measured and noted. The same procedure holds for other ranges up to 25 volts (beyond which directions have already been given).

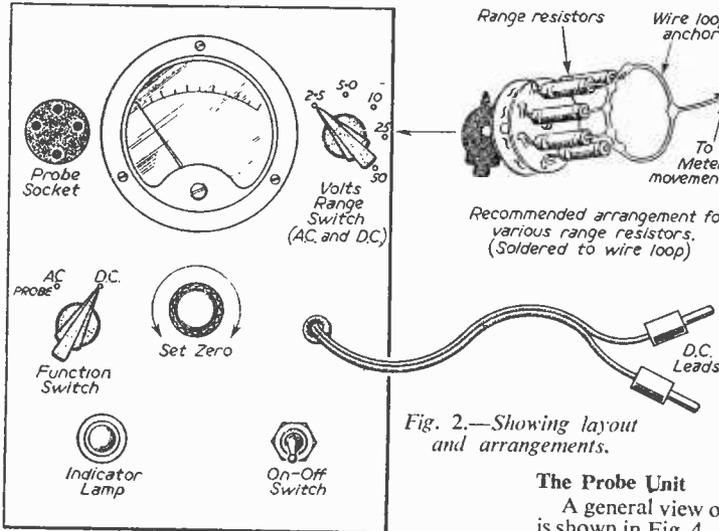


Fig. 2.—Showing layout and arrangements.

(for ease of reading) it would be well to take into account the *divisions* on the movement face. Thus a 250 microamp movement lends itself admirably to ranges of 2.5–25–250 volts, but intermediates of 5 and 50 volts can well be accommodated. An extra position of the range switch is useful for leaving the meter "open" before descending via the highest range to safeguard against component failure.


**"Ranging" the Meter**

The arrangement of Fig. 3 is such as to "tie up" with the circuit diagram proper. The D.C. valve voltmeter leads have been marked (Y) and (Z) to give correct polarity when 6SN7 valveholder is wired strictly in accordance with valve base diagrams (*not* given).

This arrangement (Fig. 3) will be familiar to all those who have "compared" the calibration of one meter against another and the system is strictly analogous. The position shown in Fig. 2 for the range switch should temporarily be occupied by a 50K potentiometer (from "spares" box) for calculating the resistors necessary for lower ranges of volts. A flying lead with crocodile clip is taken from "arm" of potentiometer to negative terminal of meter movement; the clip facilitates removal for measuring

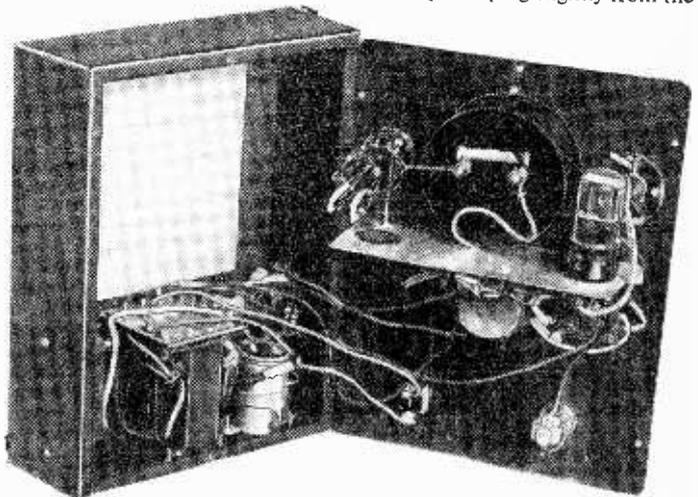**The Probe Unit**

A general view of the probe unit built by the author is shown in Fig. 4. This was made to fit into an empty mustard tin. The bracket and rods were of "Juneero" material (such outfits are sold by most radio dealers) and the rods "take" solder extremely well. When the probe unit is plugged into the main body of the meter, the function switch (set to A.C.) isolates the D.C. leads. The probe leads should be shorted and zero set on lowest range; this should hold good for all other ranges. A useful check on calibration can be made by withdrawing the probe plug slightly from the



A view of the completed instrument. A list of parts is given on page 396.

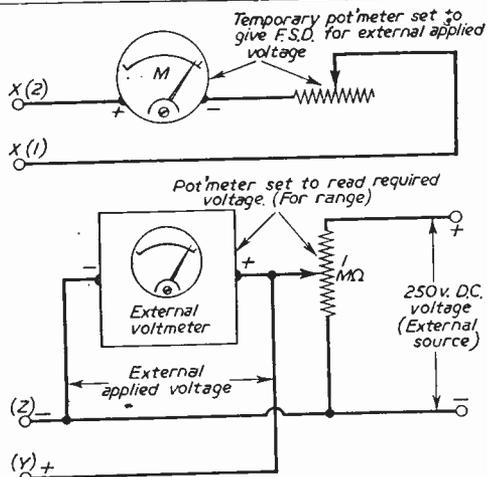


Fig. 3 (above).—Method used for calibrating various meters (100 $\mu$ A—500 $\mu$ A). Fig. 4 (right).—General view of probe (made from a mustard tin).

socket and touching probe on "live" filament pin whilst the meter is set to 10 volts range. The probe should, of course, always be removed for D.C. measurement.

**Notes**


When testing out the probe unit as mentioned above the meter needle may "kick" in opposition to the scale. It is only necessary to reverse the two 6SN7 grid leads on probe socket to give correct "sense."

The case of the instrument should *not* be "earthed." When using the "temporary" potentiometer for the initial measurement of lower ranges it would be

advantageous to leave the meter movement "open" by removing the crocodile clip until the instrument is warmed up. This will guard against the initial "kick" when one section of the 6SN7 heats up in advance of the other. (Many "sticky" movements are caused by the needle being driven "hard-over.")

Where it is found that A.C. readings are slightly on the "high" side a compromise can be made by shunting the meter movement with a suitable resistor. (D.C. will alter in similar degree.)

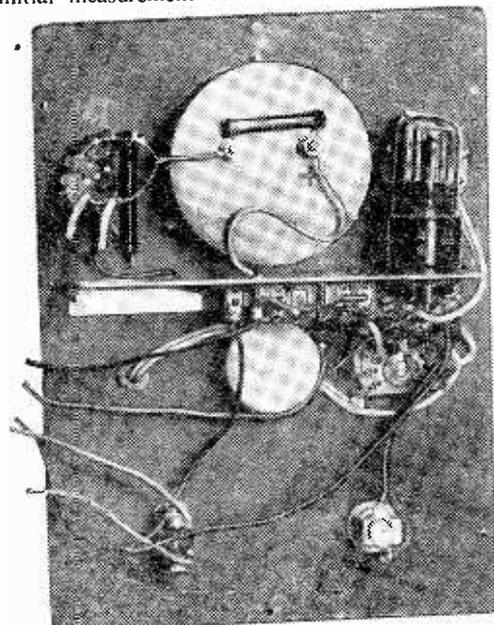Advanced workers can achieve greater accuracy by calibrating against A.C. input (with probe) and experimenting with various values for R5 and R10 for D.C. input. Those given ensure a reasonably accurate D.C. valve voltmeter using the methods outlined.



A rear view of the panel.

**COMPONENT LIST**

**MAIN CHASSIS**

- 1 valve 6SN7
- 1 selenium rectifier (250 v. 60 mA)
- 1 function switch (2-pole 2-way)
- 1 range switch 1 pole/multiple (to suit individual)
- 1 mains transformer : secondary—6.3 v. (1.0 amp.)—250 v. (RMS) 30 mA

**RESISTORS**

- 6 meg/ $\frac{1}{2}$  watt (R5, R10)
- 5 meg/ $\frac{1}{2}$  watt (R3, R4, R8, R9)
- 47K/ $\frac{1}{2}$  watt (R6, R7)
- 5K/ $\frac{1}{2}$  watt (R14)
- 33K/1 watt (R12, R13)
- 5K potentiometer (w/w) (R11)

**CONDENSERS**

- .01  $\mu$ F (350 v. w.) (C3, C4)
- 8  $\mu$ F electrolytic (350 v. w.) (C5, C6, C7)

**SUNDRIES**

- Indicator lamp 6.3 v. (.04 amps.) and holder
- 4-pin probe plug and socket, chassis, case, etc.


**PROBE UNIT**

- 1 valve EB91 (Mullard)
- 1 valveholder (B7G)
- Quantity of threaded brass rod 6BA (or "Juneero")
- Resistors : 15 meg/ $\frac{1}{2}$  watt (R1, R2)
- Condensers : .01  $\mu$ F (350 v. w. small mica) (C1, C2)
- Empty tin : screened lead, paxolin, etc.

# SHORT-WAVE SECTION

SHORT-WAVE NOTES—THE ROCKY POINT AND NEW BRUNSWICK TRANSMITTING STATIONS OF R.C.A. COMMUNICATIONS INC., NEW YORK

By A. W. Mann

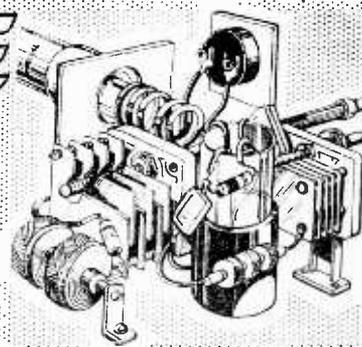

**R**OCKY POINT is one of the radio telephone stations owned and operated by the Radio Corporation of America. This R.C.A. station played an important part in the early and subsequent development of the transatlantic telephone service.

Even in the early days of the service Rocky Point with its forest of aeriels and associated buildings covered an extensive area. In addition a considerable amount of space being available to meet the demands of future expansion.

## Rocky Point To-day

The land area available is 5,234 acres, of which 3,000 acres are in use.

## Aerial Systems

On one site there are 60 aeriels of various types available. They include 24 Rhombic, 52 directive and seven doublet aeriels, together with 28 miscellaneous types and one long-wave aerial. The long-wave aerial is supported on two towers 410 ft. high, and spaced 1,250 ft. apart. These are used in conjunction with 34 short-wave transmitters in one section rating from 1 Kw to 75 Kw, three on phone and the rest on telegraphy. The long-wave transmitter which is A.T. and T.C. property is a 'phone transmitter.

## Control

Station control is carried out from the master control room which houses the general control system and equipment, together with monitoring, automatic call signing and intercommunication equipment. This work is carried out on a four-watch system with two control technicians and two transmitter technicians.

Rocky point is the R.C.A. main transmitting station and is located on Long Island and is approximately 80 miles from the central radio office in Downtown Manhattan.

The land line or wire room is the terminal point of 11 lines from New York City, 8 lines from Riverhead and 67 audio control channels from New York City.

The foregoing data applies to the equipment associated with building No. 1. Before passing to building No. 2 a few details concerning the equipment in use at the terminal office, which was illustrated last month, and which is located at 66, Broad Street, New York City, may be of interest.

One piece of apparatus used is known as a package

set. This apparatus keys the transmitters automatically by means of perforated tapes which pass through the transmitter distributors. The top section receives incoming messages while being monitored and recorded in a centre section.

There is also installed electro-mechanical equipment which permits several radio channels to be imposed on one frequency. This is known as multi-plex equipment. The main speaking room and other departments are also located at 66, Broad Street, N.Y., together with the programme and radiophoto control room.

## Solar Observations

R.C.A. Communications Inc. have made extensive investigations relative to solar activity and magnetic storms which at certain periods disrupts radio communications. John H. Nelson, an R.C.A. radio engineer and astronomer, took solar readings daily over a period of five years, and in doing so discovered new evidence concerning the cause of magnetic storms which interfere with world-wide communications. This evidence has proved extremely valuable to R.C.A., and Mr. Nelson, by plotting the position of the planets and the sun, can predict many months in advance when and where magnetic storms will occur. Thus R.C.A. Communications Inc. are able to use these forecasts to select suitable radio channels with the assurance that they will be least affected by magnetic storms.

## Building No. 2

Reverting to the Rocky Point transmitting station we pass to building No. 2. Here there are 20 short-wave transmitters. These range from 1.4 Kw to 75 Kw telegraphy types, while the 'phone transmitters are from 3 Kw to 15 Kw.

The programme service equipment located in this section consists of a five-channel audio control board, monitoring equipment limiting amplifiers and portable modulators, with two programme lines to New York. Two technicians are on duty per watch.

The total number of aerial systems associated with this section is 54. There are 38 directives, including 12 Rhombic, 26 miscellaneous types and 16 doublets.

## Power Supplies

The public utility 23,000 volts 3 phase 60 cycles supply is fed to Rocky Point by two independent feeders at a distance of 10 miles from the generating station.

This voltage is stepped down to 2,200 volts and is then regulated, after which it is further reduced to 230 volts 3 phase for distribution to the short-wave transmitters. The operating staff at the Rocky Point transmitting station total 80.

#### New Brunswick, New Jersey, Transmitters

R.C.A. also own and operate a telegraphy transmitting and receiving station at New Brunswick, New Jersey. This is located on an 858-acre site, of which 160 acres are in use.

The buildings are the power house and the main operating building in which are housed eight short-wave telegraphy transmitters. These are as follows:

- Three 20/40 Kw two frequency sets, type F2F.
- One 20/40 Kw type ED two frequency sets.
- Two 15 Kw type X single frequency sets.
- One 1 Kw type F two frequency sets.
- One 1 Kw type X single frequency set.

#### Aerial Systems

Two V beams, three type R Rhombics, three harmonic wire, two extended dipole curtains and one doublet aerial.

#### Control

The master control room contains the communicating equipment and monitoring apparatus. Amongst

this apparatus is tone signal converters, communicating and intercommunicating, and other apparatus including monitors, three short-wave receivers covering 550 kc/s to 30 Mc/s, one FSK monitor unit 2.4 to 26 Mc/s, one frequency expander 28 to 60 Mc/s, one printer monitor and one 80 to 170 Mc/s frequency measuring set.

#### Power Supply

Two public service 26 KVA 3 phase 60 cycle feeders which are automatically switched are utilised. Power is transformed to 2,200 volts, regulated and stepped down to 110 to 220 volts single and three phase for transmitter power and station lighting.

#### Staff

One engineer in charge, five technicians, one per shift. In addition there is a small outside staff of three riggers, one groundsman, one outside maintenance man, one shop mechanic and a station caretaker.

#### Land Lines

These are leased from the A. T. and T. Co., and are: One 5,000 cycle signal control line and one 2,300 cycle communication line.

## RADIO-CONTROLLED TRAIN


SOME INTERESTING NOTES ON THE  
WORLD'S FIRST TRAIN TO BE OPERATED  
BY RADIO, WITHOUT A DRIVER

ON Monday, April 18th, 1955, a train composed of four carriages hauled by the French Railways BB 9003 electric locomotive and without driver or passengers reached a speed of 74.5 m.p.h. between Connerré-Beillé and La Ferté Bernard on the main line between Paris and Le Mans.

This locomotive is a sister engine of the BB 9004 which three weeks previously reached a new world record rail speed of 205.6 m.p.h. Running alongside on a parallel track was a diesel railcar carrying Monsieur Corniglion-Molinier, French Minister of Public Works and Transport, Monsieur Louis Armand, the Chairman of the French National Railway Company, and Monsieur Charles Boyaux, the General Manager of the French Railways, accompanied by forty technicians and representatives of the Press.

Orders to release the brakes, to control the supply of current to the traction motors of the locomotive, and to apply the brakes at the end of the run, were given verbally by radio telephone from the accompanying railcar to a radio control post set up on the sub-station at Sceaux-Boëssé about half-way between the starting and finishing points of the run. The radio-wave transmissions to carry out these orders were made from the control post to a receiving set which actuated a relay on the locomotive which in turn set the necessary mechanisms in motion.

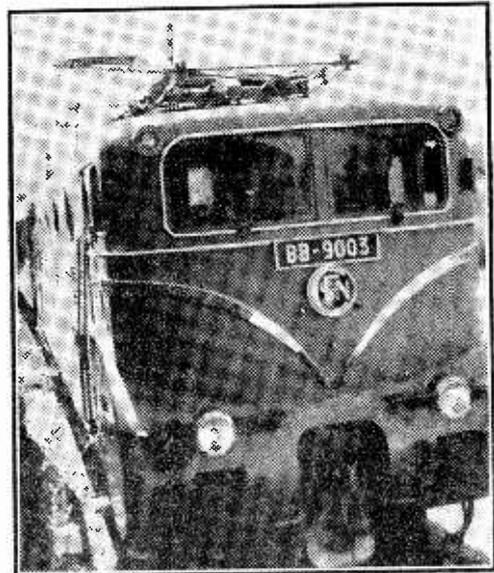At the end of the war, appreciating the growing



View of the train taken from the accompanying diesel railcar during the trial run on April 18th.

value and importance of radio communications, the French Railways applied for and obtained from the French General Post Office an allocation of wavelengths for railway operation. These wavelengths were around 1 metre and eminently suitable from a technical point of view.


In 1945, the French Railways commenced equipping their big marshalling yards with a radio-telephone installation which within a radius of from 1½ to 1¾ miles, in practice more than sufficient, enabled communications to be maintained between the hump

control tower and the shunting engines. The amount of work accomplished by these engines was thereby considerably increased and all the big marshalling yards are now equipped with similar apparatus at modulated frequency of French manufacture and bearing comparison with the best installations of the kind in use in other countries.


A new installation, unique of its kind throughout the world, has been tried out in a marshalling yard and is now being tested at Miramas, near Marseilles. It is a very light transmitting and receiving set carried on the back of the checker taking the numbers of goods waggons. Instead of inscribing them in the open on a sheet of paper, not always an easy task in bad weather or a high wind, he dictates them to the control tower, where they are either taken down on paper by a clerk or, more usually, on a magnetised wire recording machine. Having thus resolved the problem of short range communications, attention was then turned towards that of communications along the whole length of a railway line from the railway carriage to any telephone subscriber in France or abroad. French Rail-
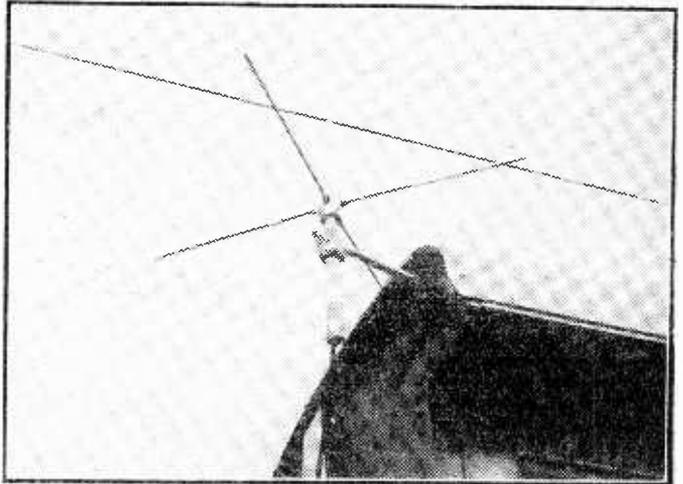
### Two Types of Remote Control

As starting and acceleration up to maximum speed of the BB 9003, in common with some other types of French Railways electric locomotives, only two types of remote control were necessary, one



*The receiving aerial on the train.*

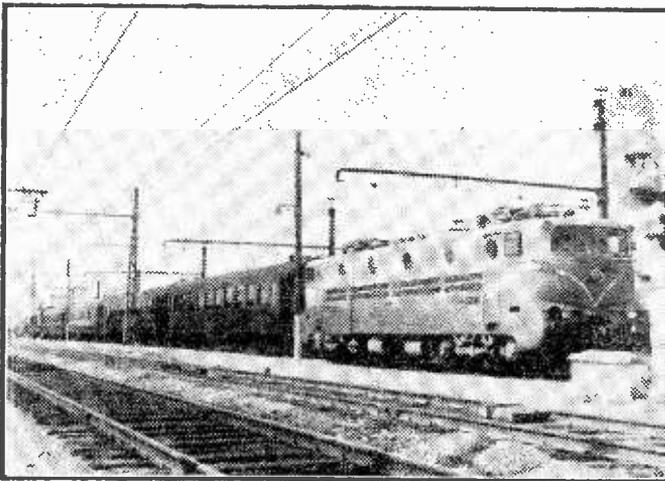

*The world's first radio-controlled train hauled by the electric locomotive BB 9003.*


ways have now perfected a system that makes possible a continuous telephone communication. It does so at a very low cost and reception is excellent even on an electrified line where screening effects and parasitic currents abound. Trials of this system have recently been carried out between Hirson and Charleville on the section of line electrified with monophase current at industrial frequency.

The present trials of the radio control of a train without human intervention on the train itself represent a further step forward beyond what has already been achieved.

to operate the brakes and the other to regulate the supply of current to the traction motors. Two kinds of current were necessary for the transmission of orders to the robot train. One of the orders was given by the carrier frequency without modulation and the other by the carrier frequency with modulation at approximately 1,000 periods per second. The wavelength used was 1.9 metres. The relay on the locomotive which carried out the movement ordered and which received the order through an aerial of very limited length and a receiver very light in weight, can easily be placed in the waistcoat pocket.

For these trials which were prepared in a few days only, existing equipment had to be used, that is to say radio telephony adapted for radio control. This equipment gave excellent results during the preliminary trials. With special equipment designed for the purpose complete reliability is certain. The French General Post Office, which made the necessary frequencies available for these trials, gave every other assistance in its power to ensure their success. The French electrical manufacturers who have collaborated with the railways for the provision of radio communications are the Société Française Radio Electrique for the Hirson-Charleville line, and the Société N.O.R. for the Bordeaux-Dax speed trials and the present radio-control trials.

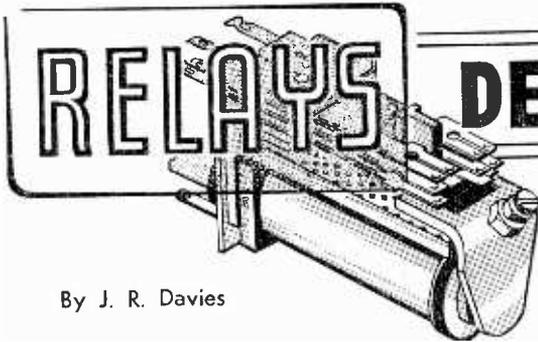These trials were supervised by Monsieur Fernand Nouvion, an engineer of the Electric Traction Research Department of the French Railways.



# DESIGN & USES

By J. R. Davies

THE FIFTH ARTICLE IN A SERIES DEALING WITH A MOST USEFUL TYPE OF RADIO ACCESSORY

(Concluded from page 341, June issue)

**L**AST month we described the design and use of the uniselector. We showed also that, due to the bulk and relatively heavy current consumption of the standard manufactured model, it cannot be used for the control by radio of small models. We discussed also the construction at home of a smaller and less complicated type of uniselector which would have a lower weight and current consumption.

Even this small uniselector had one or two disadvantages, however, and so in this month's article (the last in this series) we shall discuss several entirely different methods of remote control. Although we shall regard the subject primarily from the point of view of model control by radio we shall indicate also how the arrangements described may be used for the control of static equipment over interconnecting lines as well.

### Carrier Control

The simplest type of remote control by radio would employ a receiver and a relay, the relay operating only on the presence or absence of a transmitted carrier. Thus when the transmitter was switched on the receiver would either energise or de-energise the relay. When the transmitter was switched off the relay would return to its original state.

A control of this sort would offer very little scope; although it could, nevertheless, be used to give a fairly reliable control of a function such as steering. If, for instance, the controlled model were fitted with a rudder which was spring-loaded to turn to the left, the presence of a transmitter carrier could be used to operate a solenoid which would pull it over to the right. When it was desired to bring the rudder to the centre a series of "fifty-fifty" pulses could be sent, these supplying an average voltage to the rudder solenoid equal to half the full voltage. (The term

"fifty-fifty" means that the length in time of each transmitted pulse would be equal to the period between pulses.) Should the rudder system have sufficient inertia (and the pulses be sent quickly enough) the rudder should answer to this average solenoid voltage and move to a mid-way position.

Apart from the use of a uniselector or something like the steering scheme just mentioned the single receiver relay operating from the carrier does not offer a great variety of control. When the transmitter is modulated, however, it is possible to increase the number of controllable circuits considerably.

### Control by A.F. Tones

Control by audio tones of different frequencies is both practicable and relatively easy to incorporate into amateur-built equipment. The transmitter can be modulated by one or more tones, these being selected and separated in the receiver by A.F. filters. After selection each tone can be made to operate a relay (this being done usually by causing the anode current of a valve to alter), and thus actuate different mechanisms in the controlled equipment. By using combinations of tones it is possible to obtain a considerable number of different effects, as will be shown later.

Whilst these A.F. tones may be used to operate different circuits it is still at the same time possible to employ the carrier for control purposes as well. It can, for instance, be used to switch on the main driving motors of the controlled model. These will then run all the time the model is performing, and will stop only when the transmitter is switched off.

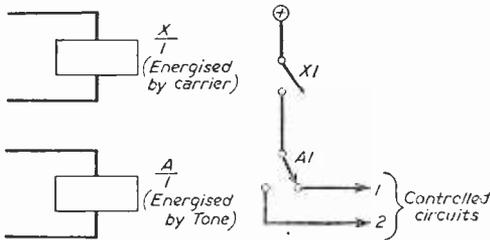


Fig. 25.—A simple receiver relay circuit operated by a carrier and single A.F. tone. The carrier by itself operates circuit 1, the carrier plus the tone operates circuit 2.

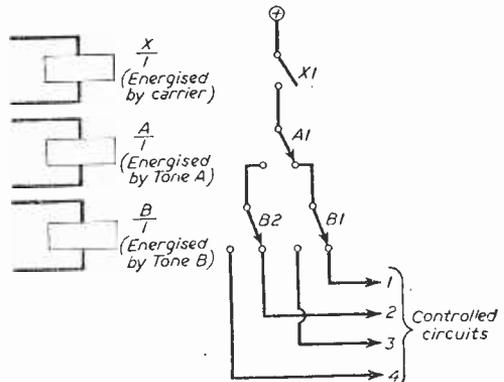


Fig. 26.—Illustrating how a carrier and two tones may be used to control four circuits.

The additional filter circuits and valves needed at the receiver to select the A.F. tones will be too bulky for such things as model aircraft; but there seems little reason why, with careful design, they could not be used in model boats or land craft. The control of remote stationary objects by tones (which could be transmitted either over a single pair of lines or by the radio link) is quite feasible.

The most elementary form of control by A.F. tones would employ a single tone only. A suggested receiver relay circuit is shown in Fig. 25. This employs two relays, one operated by the carrier, the other by the tone. It is assumed that the relays shown in the diagram are energised on reception of the carrier or the tone. (If, due to the particular receiver circuit employed, it should happen that they de-energise, their contacts would, of course, have to be altered accordingly.)

Fig. 25 offers two alternative controls: these being given by the reception of the carrier by itself, and by the carrier with the tone. The diagram shows how these two alternatives are used to switch either one of two circuits in the model itself.

When two tones are used it is possible to obtain four controls. It will help here if we refer to the two tones as tone A and tone B. The combinations possible consist then of the following: carrier by itself, carrier plus tone A, carrier plus tone B, and carrier plus tone A plus tone B.

Fig. 26 shows how these various combinations may be "sorted out" by the receiver relay contacts. (It is again assumed that the reception of a carrier or tone causes the appropriate relay to energise.) The

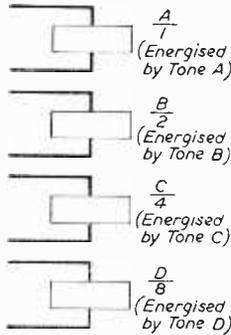


Fig. 29.—Showing how the combinations offered by four tones are capable of operating 15 different circuits.

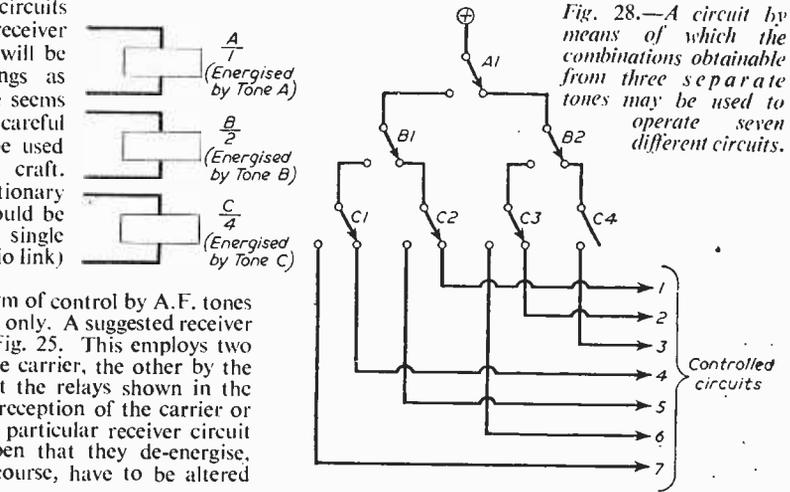



Fig. 28.—A circuit by means of which the combinations obtainable from three separate tones may be used to operate seven different circuits.

purpose of the relay contacts in the diagram is to pass the positive source of supply to whichever external controlled circuit has been selected. The numbered outlets (1 to 4) to these circuits correspond respectively to the combinations just mentioned.

As stated previously, the carrier need not be employed in the tone combinations, but can be used by itself in order to switch on the main motors of the model. If this procedure were adopted in this case our two tones would now give us three combinations only: these being tone A, tone B and tone A plus tone B. A circuit showing how these combinations could be selected by the receiver relay contacts is given in Fig. 27.

Three Tones

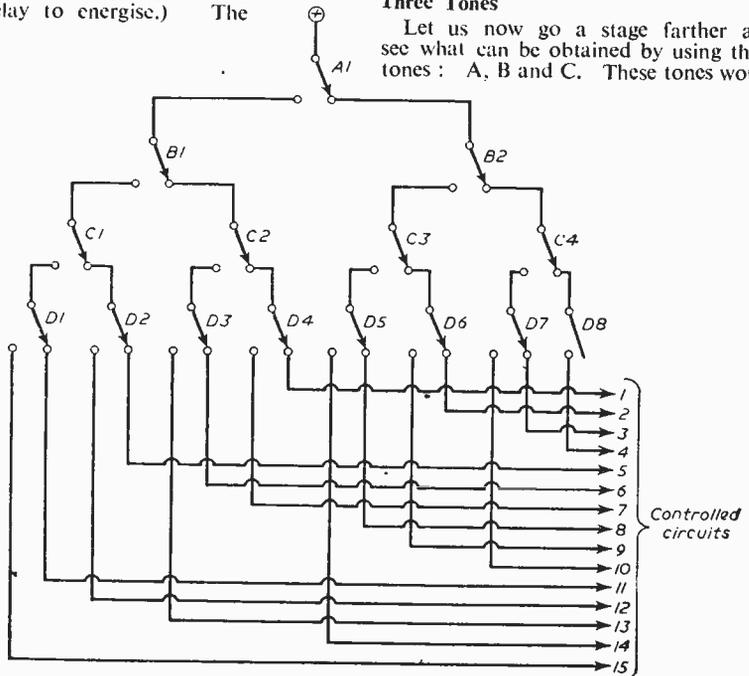Let us now go a stage farther and see what can be obtained by using three tones: A, B and C. These tones would



offer us seven combinations: A, B, C, A plus B, A plus C, B plus C, and A plus B plus C. This time it would not be worth while employing the carrier in combination with the tones as it would give only one extra combination (carrier by itself) and would necessitate an additional contact unit on each relay. There is nothing, however, to prevent the carrier from being used to operate the main driving motors, etc., in the manner mentioned previously.

A relay control circuit capable of selecting out the seven combinations from the three different tones is shown in Fig. 28. Once more the control output terminals (1 to 7) correspond to the tone combinations mentioned in the preceding paragraph. The reader will probably find it of interest to trace out the way in which the various contact units "sort out" each particular combination.

It will be seen in this diagram that relay  $\frac{C}{4}$  has one make and three changeover contact units. Four contact units on one relay may present rather a heavy load if the relay is operated from a switching valve; particularly if low-voltage receiver batteries are used in the model. In such a case it may be necessary to use a light relay in the anode circuit of the valve, this operating another relay (bearing the four contact units) energised from the main driving battery.

Fig. 29 illustrates a circuit capable of selecting 15 different operations with the use of only four tones. The tone combinations are: A, B, C, D, A plus B, A plus C, A plus D, B plus C, B plus D, C plus D, A plus B plus C, A plus B plus D, A plus C plus D, B plus C plus D, and A plus B plus C plus D. It will be noticed that, once again, the carrier does not appear in the combinations. The extra control afforded by it is not worth the added relay contacts required.

It will also be observed that relay  $\frac{D}{8}$  has eight contact units, one make and seven changeover.

Although it is possible to obtain a single relay fitted with eight contact units, it would very probably be better to use two separate ones with four contact

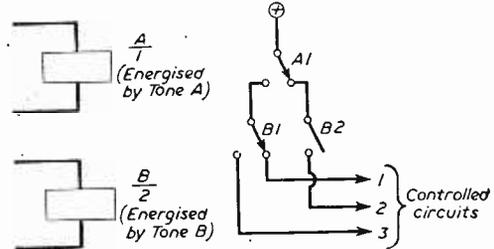


Fig. 27.—Two tones (without making use of the carrier) are capable of controlling three circuits, as shown here.

units each. If the receiver battery supplies are sufficient to allow the switching valves to operate four-contact-unit relays these two relays could then be operated by having their coils connected in series. Alternatively, it would be necessary to use light-action relays for both C and D switching valves, these relays operating the  $\frac{C}{4}$  and  $\frac{D}{8}$  relays proper from the main driving batteries.

#### Line Operation

It should be pointed out, before concluding, that the circuits of Figs. 27 to 29 are all capable of being operated by D.C. over interconnecting lines instead of by using the radio link.

Thus, Fig. 27 allows three operations to be obtained with the three lines (two and a common line). Fig. 28 allows seven controls to be obtained with four lines, and Fig. 29 allows fifteen controls to be obtained over five lines. In each case the common line could be eliminated, if desired, by using a reliable earth return instead.

## Plessey Pre-selectors

TWO new pre-selectors, the PV98 and PV98A, are announced by Plessey. They are designed for use in conjunction with a single channel fixed frequency H.F. receiver, such as the Plessey PR53A, PR53C or PR51C, to provide switched selection of any one of five pre-set crystal-controlled channels in the frequency range 2.7 to 27 Mc/s.

The PV98 is fitted with a crystal-controlled B.F.O. for use when receiving C.W. signals, while the PV98A is designed for M.C.W. and R/T working. Both are extremely versatile and may be used in conjunction with Plessey or other manufacturers' units in commercial communication networks. In an F.S.K. installation, for example, the use of a PV98 in conjunction with stable oscillators PG81 and PG82, provides five-channel reception with the same high stability as the standard PVR80 equipment, and is, therefore, suitable for unattended operation.

When the stability requirements are less critical, the PV98 may be used with its own internal oscillators, making an F.S.K. installation available at very moderate cost. Operational trials have shown that extremely good performance can be achieved if the vernier controls are periodically adjusted.

Both pre-selectors comprise an R.F. stage, a

crystal-controlled H.F. oscillator and a mixer, giving a low impedance co-axial output at a fixed frequency of 2.1 Mc/s. The R.F. stage is tuned by pre-set circuits and the oscillator stage crystal controlled, the appropriate circuits being selected by a single five-position rotary switch manually operated from the front panel. Alternatively, the selector switch may be motor-driven from the rear, thus permitting remote control.

Additional facilities are available on the PV98 for operation from external oscillators. The tuned circuits are mounted as plug-in units, six ranges being provided to cover the frequency band.

Two pre-selectors and two receivers may be connected to form a dual-diversity combination, the receiver outputs feeding a conventional path selector or diversity switch unit. Under these conditions, the channel frequency crystals need only be fitted in one of the pre-selectors, as the two may be operated with H.F. oscillator circuits cross-coupled, and similarly for diversity telegraphy, two B.F.O. outputs are provided for the operation of both receivers driven by a single crystal fitted in one only of the pre-selectors.

Each pre-selector contains an in-built power supply; operating from 50-60 c/s A.C. mains. Tropically rated components are used throughout.

ADVERTISER'S ANNOUNCEMENT

**FREE!** Send 5d. (stamps) for fully descriptive literature including Circuit and practical Drawings. The really efficient 5-valve Superhet., 6-valve hot, 3-valve (plus rectifier) T.R.F. circuit. Battery portable Superhet. circuit. Coil and Coilpack leads, and full radio and component lists, and interesting miniature circuits, etc.

SPECIAL EDITION  
**Osmor**  
**News**

**OSMOR**  
**RADIO PRODUCTS**  
LIMITED  
(Dept. P.61)  
418 BRIGHTON ROAD,  
SOUTH CROYDON,  
SURREY.  
CROYDON S148 9.

PUBLISHED MONTHLY

Vol. 1. No. 3.

JULY, 1955

**FAMOUS FIRM'S BRILLIANT TECHNICAL RESEARCH RESULTS IN IMPROVED COIL DESIGN!**

Osmor High "Q" Coils are the outcome of manufacturing experience plus constant experiment... universal preference proves their undoubted superiority!

**F.M.** Frequency Modulation comes to stay! OSMOR does its share in the design of coils and a really first-class circuit of complete receiver and tuner. Free circuit, point to point wiring diagram, and full constructional information for the amateur. (Send 5d. in stamps.)

**OSMOR 'Q' COIL PACKS**

Size only 1 1/2 x 3 1/4 x 2 1/2 with variable iron-dust cores and Polystyrene formers. Built-in trimmers. Tropicalised. Prealigned Receiver. Guaranteed. Only 5 connections to make. All types for Mains and Battery Superhets and T.R.F. receivers. Ideal for the reliable construction of new sets, also for conversion of the 21 Receiver. TR1196, Type 18, Wartime Utility and others.




**The NEW OSMOR "SWITCH PACK" is now ready!**

Complete and Prealigned full circuit included. State which station required. 2 M.W. 1 L.W. or 3 M.W. 48/- incl. P. Tax.

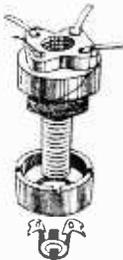**SUPER 'Q' CUP COILS for MAXIMUM SELECTIVITY**

A full range is available for all popular wavebands and purposes. The magnetic screening of the cup prevents other components from absorbing the Coil's power, thus maintaining the high 'Q' value. Simple one-hole fixing. \* Only 1/4 in. high. \* Packed in damp-proof containers. \* Adjustable iron-dust cores. \* Fitted tags for easy connection. L. or M.W.



**5/- inc. CIRCUIT.**

**CHASSIS CUTTER**

Type	Hole Sizes	Price
1	1in. x 1 1/4in.	19 6
2	1 1/2in. x 1 1/4in.	18 9
3	1in. x 1 1/4in.	22 6
4	1 1/4in. x 2in.	27 3



100 ton High tensile bolt now supplied with No. 2. Allen Key, 2 6.

**OSMOR STATION SEPARATOR**

The Separator may easily be tuned to eliminate any one station within the ranges stated and fitting takes only a few seconds. Aerial Sharp tuning is effected by adjusting the brass screw provided.



**7/6**

Type	Metres	Type	Metres	Type	Metres
1-141-257		4-519-405		7-1450-1550	
2-218-281		5-285-492		8-410-550 kc's.	
3-287-341		6-655-567			

Special Separator to clear Radio Luxembourg, 10/6 each.

**READERS' QUERIES!**

Dear Sirs,  
Please tell me which side of a Crystal Diode is red.  
*The positive side is red and is represented by the perpendicular line at the point of the negative cone. Also the red is equivalent to the cathode of a diode valve.*

Dear Sirs,  
There is an annoying whistle very close to the Home Station which ruins my reception. How can I get rid of this?  
*An improvement can generally be made by fitting a whistling filter. Full details on application.*

Dear Sirs,  
I wish to receive the Trawler band on 70-230 metres. Could I replace the 15-50 m. band in your coilpack and obtain this coverage?  
*Yes. Coils Q.15, Q.01 (aperiodic type) may be used.*

Dear Sirs,  
Shortly after I switch on my 5-valve superhet the station disappears, and I have to retune. Can you assist, please?  
*This sounds like frequency drift, and is usually caused by overheating, causing a change in the value of one or more of the capacitors associated with the I.F. or Osc.*

**Calling all amateurs!**

Have you a problem involving circuits in which Osmor Coils or Coil Packs are used, or intended to be used? Let our Technical Team solve it—just write us a letter. We're right up-to-date—we build the various circuits given in "Wireless World," "Practical Wireless," "Radio Constructor," etc., and we stock the components specified. Most Technical Colleges, Universities, etc., use Osmor Coils for research.

**"PRACTICAL WIRELESS"**

Coronet Four; Beginners' Superhet; An Economical Quality Receiver; A Six Valve A.C. Superhet; Attaché Case Portable; R1155 Converter; A.C. Band-Pass 3; Modern 1-Valve; A 2-Valve Feeder; Fury Four, Standard A.C. Power Pack; 3-speed Autotrum; Modern reflex, etc.

**"WIRELESS WORLD"**

DESIGN FOR F.M. TUNER. "No Compromise" T.R.F. Tuner. "Midget 3-valve A.C. Mains Receiver." Sensitive 2-valve Receiver. Reflex Push-Pull 3-valve Receiver. Miniature Beside Receiver. Midget sensitive T.R.F., etc.

**"RADIO CONSTRUCTOR"**

Converting the TR1196 receiver to a general purpose s'het. Receiver simple crystal diode set. Radio feeder units. Economy 8 W.P.F. Amplifier. Whistling Filter. Circuit and details available for adding push-pull to the 5 1/2 valve Osmor superhet, a progressive receiver.

# HOME RADIO OF MITCHAM

187, LONDON ROAD, MITCHAM, SURREY. MIT. 3282.


## F.M. TUNERS.

All parts in stock and demonstration models working.

DENCO full details, 1/6.

JASON " " 2/-.

W.W. components stocked.

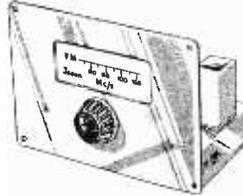

**POWER UNIT.** Ideal for F.M. tuners, etc. For A.C. mains. Output 250 v. 50 mA. 6.3 v. 1.5 a.

Complete kit with wiring diagram, etc.

**PRICE £2.**

**MULLARD "5/10" and G.E.C. "912" Amplifiers.** All specified components in stock including Partridge transformers. Mullard 5/10 book, 2/6. G.E.C. 912 book, 3/6. S.A.E. for price list.

**STROBOSCOPES.** 33½, 45 and 78 r.p.m. for A.C. mains in high grade ivorine. **PRICE 1/6.**

**CONDENSERS.** Large stocks of T.C.C. Hunts, Dubilier, etc. S.A.E. for list.

**HI-FI LOUDSPEAKER.** The new W.B. HF1012 10in. speaker with universal 3 and 15 ohm speech coil in stock. **£3-17-6.**

The full range of

## EDDYSTONE

short wave components in stock. Eddystone catalogue price 1/-.

## SPECIAL OFFER

A limited number of high quality crystal microphones with table stand at less than half usual price. Few only, 39/6.



## PRACTICAL TV AERIAL MANUAL

For bands I and III. **PRICE 4/6.**

**"MONARCH" 3-speed auto-changers.** New and boxed. **£10-10-0** carriage paid.

**RESISTANCES.** Enormous stocks of all types, including high stability and wire-wound.

# Bigger and Better Pictures

WITH

# BRIMAR

Shortly available—The **BRIMAR**  
21-in TELETUBE **C21HM**

This Rectangular Wide Deflection Teletube with Aluminized Screen and external Conductive Coating, operates at 16 kV. It is fitted with an improved tetrode gun assembly giving excellent overall focus and minimum astigmatism.

**Brimar have developed powerful valves suitable for use with existing or future types with larger screen areas**

**6CD6G/50CD6G (AC/DC)**—Line Output Valves with a peak current of ½ amp. and plenty of power in hand for wide angle scanning.

**6U4GT**—Efficiency Diode—The high working peak heater to cathode potential renders a separate highly insulated heater supply unnecessary.

**R19**—E.H.T. Rectifier—A replacement for the American IX2A but with higher Ratings.

**RM5**—H.T. Rectifier—A worthy successor to the RM4, with a rating of 300 mA. This rectifier has a reserve of power and should be used initially in equipment so that additional valves may be added if required without redesigning the power supply stages.

## Valves for the BAND III CONVERTOR (for 6 volt operation)

\***ECC84**—Consists of two separate high slope triode units designed for use as a V.H.F. cascode amplifier.

\***ECF82**—is a triode pentode frequency changer featuring a high slope triode and a high slope pentode with a high input impedance.

**6BW7**—The 6BW7 is recommended in areas where extra sensitivity is required. It has a slope of 9.3 mA/V with anode and screen voltages of 180v.

\* The PCC84 and PCF82 are .3 amp equivalents of these tubes and are suitable for equipments where series connected valves are used.

Standard Telephones and Cables Limited **FOOTSCRAY, SIDCUP, KENT. Footscray 3333**

# TRANSMITTING TOPICS



## END AND TOP LOADED AERIALS FOR TOPBAND

By O. J. Russell, B.Sc.(Hons.), G3BHJ

PREVIOUSLY the base-loaded aerials have been considered, particularly from the point of view of the amateur faced with a restricted location for aerial erection. It may be tacitly understood that by implication the amateur with room for 100ft. or so of wire has no difficulties. However, the length of the wire is nothing like so important as its height.

To show the importance of height rather than length, consider a 100ft. length of wire. That is overall, from the far end right back to the base-loading coil at the TX. With this length of wire, consider three typical set-ups. The first amateur, relying on the value of length, erects his aerial only 20ft. high. Thus he has in effect an 80ft. top length and a 20ft. lead in vertical proportion. The second amateur decides on a little extra height, a mere extra 10ft., so he has a 70ft. top length and a 30ft. lead in. The third amateur (with the shortest garden) has only 50ft. of length, but due to two conveniently placed tall trees can raise the wire to 50ft. high, so his aerial is a 50ft. top with a 50ft. vertical lead in. These aerials are illustrated in Fig. 1.

Unfortunately for the amateur with the longest run of wire, the radiation resistance of his aerial is only about 2 ohms. Thus, with an earth resistance of 10 ohms, only 2/12 of his power is radiated, some 17 per cent. With possible loading-coil resistance added, only about 15 per cent. of power will be radiated on topband. The second amateur, with an additional 10ft. of height, has a radiation resistance of 6.5 ohms, so that he will radiate about 40 per cent. of his power, more than twice the efficiency of the first amateur's aerial. The third amateur with the tall trees, however, is luckier still, as his aerial has a radiation resistance of just over 12 ohms, so he radiates more than 55 per cent. of his available R.F. power. It is clear, however, that even the 10ft.

increase in height of the second amateur has resulted in a worthwhile increase in radiation efficiency.

### Earth Resistance

The above figures would be more dramatic

Fig. 1.—Three 100ft. aerials of very different topband efficiency.

still if the earth resistance were higher, say, 20 ohms. As a single earth may have a resistance of around 30

ohms it is clear that even the possessor of a long wire on topband cannot be sure of effective and efficient radiation. The necessity in a Marconi system of a low resistance earth by paralleling multiple earth connections spaced widely apart is, therefore, emphasised. Where the soil is sandy or of high resistance, a counterpoise is often a much more efficient solution. In its simplest form, a counterpoise consists of a wire insulated from earth, but strung a few feet above earth, and running underneath the "top." This is shown in Fig. 2. For vertical aerials a radial array of wires radiating from the base of the aerial may be used. In some cases the ends of the counterpoise wires may be terminated in earth rods. Virtually this system is, of course, supplied by the suggested arrangement of multiple widely spaced earth points previously recommended.

The use of end-loading methods may now be considered in more detail than in previous descriptions. The end or centre loaded aerial is shown in Fig. 3. We can consider the purpose of the centre-loading coil is to tune the top part of the wire to


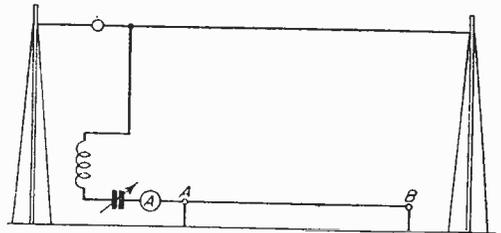


Fig. 2.—A counterpoise, AB, replaces the earth return. In some cases the end B may be earthed. Extra counterpoises may be added in a fan centred on A.

resonance. Considering the curve of Fig. 4, which shows the approximate inductance required to tune the quoted length of wire to resonance, a coil may be designed to top or end load the aerial. In the case of short wires where the coil becomes a "centre" loading coil, the coil is, in fact, twice the inductance needed for base loading, as it is tuning the top half of the aerial, i.e., half the length of wire, which has half the capacity of the full length. However, this would appear to offer little advantage over base loading, as more wire (and hence more loss resistance) is needed in the coil. The "centre" loading, however, doubles the radiation resistance of the aerial. Thus, when earth losses are considered, a net gain occurs even if the coil resistance were doubled. In fact, however, the coil resistance need not double for doubled inductance, so that a further gain occurs.

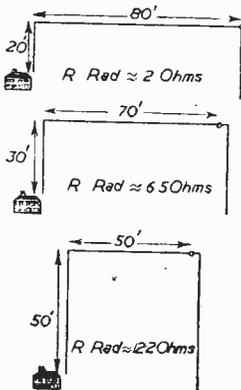The curve of Fig. 5 shows the efficiency obtained with short, centre-loaded vertical aerials, with an



assumed ground resistance of 10 ohms, and with centre-loading coils of various Q values. In practice these figures show an improvement over the values obtainable with base-loaded vertical aeri- als that is worthwhile, especially for the very short aeri- als. It should by now be crystal

is ideal, particularly the freedom from QRM, so that attention to increasing radiation efficiency when using short aeri- als is very necessary. While a change to 80 metres would quadruple the efficiency of a very short-loaded aerial, the QRM problem makes 80 metre operation virtually useless for RAEN purposes. Further measures to increase radiation efficiency are therefore needed for topband aeri- als when only a short whip aerial is possible.

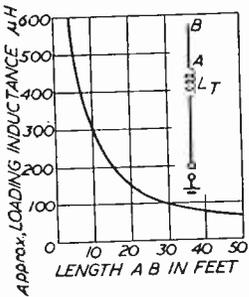


Fig. 3 (inset).—Centre-loaded aerial. Length AB and  $L_T$  should resonate to operating frequency. Fig. 4.—Centre-loading inductance values.

clear that mobile or similar topband operation with short whip aeri- als results in a very serious loss of radiation efficiency even with centre loading. In fact it is clear that, with the present 10-watt power limit, only fractional efficiencies can be expected with short aeri- als.

**Mobile Operation**

As mobile operation is now permitted, and particularly as RAEN exercises with mobile gear are now an important new amateur activity, it is clear that the topband does not provide a very suitable band for portable handset and car mobile operation, due to the low aerial efficiencies that are inevitable. Thus RAEN organisers must carefully consider the merits of other bands . . . such as 10 metres or even 2 metres, where small radiators are very much more efficient, and in fact virtually all power can be radiated. However, as local propagation conditions offer special problems on the higher frequencies, the choice of band for RAEN operation is not an easy one. In part because of the fact from some points of view the topband

One method is the use of capacity loading to reduce the size of loading coil needed to resonate the aerial system. The extra capacity loading means a reduction in coil size, so that there is less actual loss resistance introduced for the same Q value. As, moreover, a coil of smaller inductance can be wound with larger wire, a gain in Q is possible, so that a further gain in efficiency results. It must be stressed, of course, that it is the preponderance of earth and coil losses that reduces the overall radiation efficiency of the whip aerial. The radiator itself radiates 100 per cent. of the power that reaches it, but unfortunately only a fraction reaches the aerial, as most of the R.F. power is dissipated in ground and loading-coil losses. Were it possible to reduce ground and coil losses to zero, the shortest aerial would radiate with 100 per cent. efficiency! For topband operation with short aeri- als, the size of loading coil required is so large

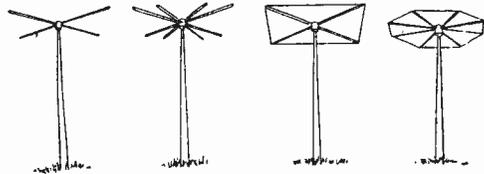


Fig. 6.—Various forms of top-loading skeleton capacities.

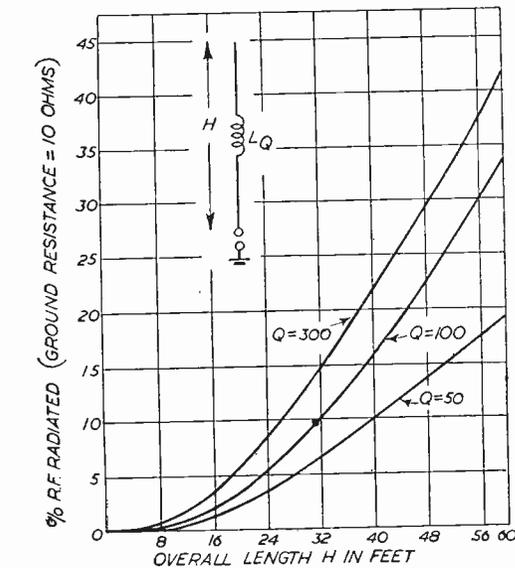


Fig. 5.—Topband efficiency of centre-loaded wires.

that the loss resistance of the coil completely swamps the radiation resistance of the short aerial. However, it should be noted that even a 50ft. vertical aerial is, technically speaking, "short" on topband, so much so that it is difficult to radiate much more than half the power supplied from the TX. This, however, is a vast improvement on the few per cent. of available R.F. radiated by shorter wires.

Top capacity loading offers yet another means of increasing the radiation efficiency of very short whip aeri- als. Spheres, cylinders and discs may be used to provide the capacity loading. However, the only really feasible system is a skeleton disc arrangement of wires fanned out radially, as shown in Fig. 6. In Fig. 7 the capacities, represented by circular discs of various sizes, are given. Even a disc of 1ft. diameter gives a worthwhile improvement. Also for mobile use with a car, a collapsible fan of wires forming a skeleton disc could be used, or jointed rods closing up to half diameter when not in use, or telescoped tubes offer other means of providing a top-loading capacity that is practicable for mobile or portable topband working. It is also entirely practicable to use top capacity loading at fixed stations, using larger aeri- als. One method of doing this, if four support poles or trees are available, is to suspend the vertical wire from the crosspoint of wires slung from pole to pole. The perimeter of the fanned wires may be connected by wires also. Where such a large fan is not practical, a number of parallel wires may

be strung between spreaders to give an effective top-loading capacity.

While this arrangement (Fig. 9) may seem reminiscent of the early days of radio, it is necessary to point out that these means were adopted for the very specific aim of providing efficient operation, so that even a crystal set could perform feats of DX reception.

**Capacity Loading**

In the case of mobile operation, a skeleton capacity disc of a foot or so diameter is a worthwhile addition to a short whip. While the capacity loading disc should be as high up the whip as possible, preferably at the top, for mobile use it may be impracticable to mount it at the end of the whip for mechanical reasons. However, as centre loading is used, the disc may be mounted just above the loading coil, and thus provide a rigid structure.

In the case of the centre-loaded short aerial the loading coil should resonate the top of the aerial to resonance. Thus from the curve of wire length capacities, the capacity of the top whip is determined. The curve of Fig. 8 gives the inductance required to resonate various capacities to the topband. When a top-loading disc is used the capacity of the disc is determined from the curve of Fig. 6, and added to the capacity value of the top whip length above the loading coil. The loading-coil inductance to resonate this total capacity is obtained from Fig. 8.

Generally the inductance values are approximate, and will need adjustment. Also, as the system is a high Q resonant system, retuning is necessary when only a small shift in frequency is made. One way of loading and tuning is to use a variable inductance of the "roller coaster" type for the centre-loading inductance. A further method is to adjust the length

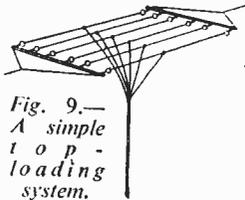


Fig. 9.—A simple top-loading system.

or the spacing of the rods forming the capacity fan to obtain resonance. Where it is desired to have frequency control at the base, as, for example, when operating on the move, one method is to use a smaller centre-loading coil than needed for resonance, and using the usual base tuning circuit. The presence of the centre-loading coil in this latter case makes the size of loading coil at the base very much smaller than with a plain whip aerial.

However the final loading and tuning are effected, some local tests with and without loading will give useful guides to aerial performance, and to the correctness of adjustments. In general, a base-loading coil may be used, as a tuned circuit link coupled to the coaxial line output of a transmitter. In other cases a matching inductance may be used, consisting of a small coil across which the coaxial line output of the TX is tapped. It is even possible to feed the base of the aerial directly with coaxial,

matching and tuning being controlled at the TX output coupling end. However, many will find the convenience of some form of base-loading circuit employing a tuning condenser and coil the best solution. This does enable tuning adjustments to be made in comfort at the base of the aerial, whereas it is not always convenient to make tuning adjustments

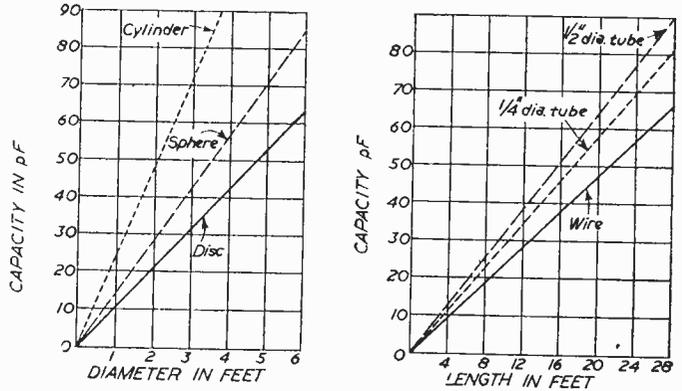


Fig. 7 (a) (left).—Capacities of spheres, discs and cylinders. (Cylinder has its length equal to its diameter.) Fig. 7 (b) (right).—Capacities of wires, rods and tubes.

at the centre-loading position. In any case spectacular increases in aerial current must be regarded with suspicion, as this may often be due to a spurious local capacity to ground accidentally introduced near the base-loading circuit. This will not greatly affect efficiency, but may cause a large current to circulate in the aerial ammeter. Thus the efficiency changes are best monitored by means of signal reports from reasonably local amateurs. In many cases the same aerial may be used on 80 metres as well by adjusting the size of centre-loading coil. The top-capacity loading used need not be changed, of course. Generally, the top-loading coil should be one-quarter of the topband inductance for 80 metre operation. However, if only a small amount of centre loading has been introduced, thus leaving a sizeable base-loading coil, it may then be possible to load up on topband and eighty merely by adjustments of the base-loading inductance. Radiation efficiency on 80 metres will in any case be noticeably higher for short aerials than upon topband.

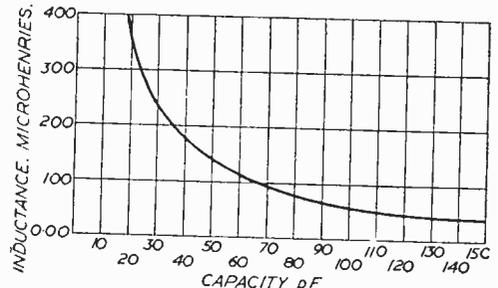


Fig. 8.—Inductance to resonate a given capacity to the middle of topband (1,900 Kc/s).

# Using TEST INSTRUMENTS



Part 7 of a New Series of Articles  
Dealing with the Practical Application  
of Standard Test Equipment

(Continued from page 344 June issue)



FROM this reasoning it will be realised that by disconnecting the test leads and applying them across an unknown capacitance the meter will deflect to something less than full scale. The actual deflection will, of course, depend on the C to Cx ratio, which, by employing the following formula, can be used to determine the value of the unknown capacitor.

Capacitance (Cx) in  $\mu\text{F} = \text{Ec} \times \text{C} / \text{E}$  minus Ec, where Ec = the voltage measured across C, C = the value of C in  $\mu\text{F}$ , and E = the applied A.C. voltage.

Since the resistance of the A.C. voltmeter is bound to have a shunting effect on the reactance of C and generally disturb the reactive balance of the circuit, a high-resistance A.C. voltmeter should be used for this test, particularly when relatively low capacitances are to be measured—a valve-type voltmeter is ideally suited for a test of this kind.

Because the reactance of a capacitor rises as the frequency is reduced, the lowest capacitance that can be successfully measured by the above methods is somewhat limited by reason of the relatively low frequency of the mains supply.

## Estimating Inductance (21)

The measurement of inductance is a little more involved than the measurement of capacitance, and essentially a specialised bridge instrument is needed to provide an accurate indication.

Nevertheless, a rough indication, which is usually sufficient for the service engineer or constructor, is possible by measuring the A.C. voltage developed across an unknown inductance and comparing the reading obtained against the voltage developed across a resistor which is connected in the same circuit.

A circuit set-up for a test of this kind is shown in Fig. 26. From this it will be seen that a battery is

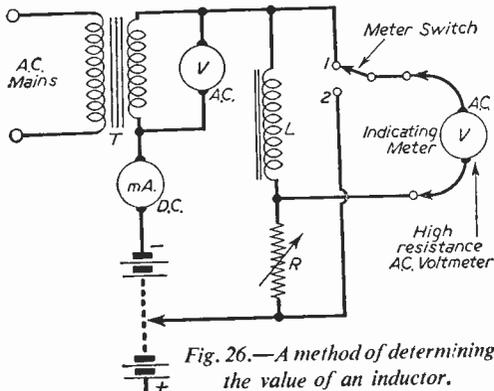


Fig. 26.—A method of determining the value of an inductor.

also employed to drive a desired direct-current through the inductor under test. This is necessary because the value of inductance is somewhat affected by the presence of a direct-current, and when estimating the value of a smoothing choke, for example, it is usually of benefit to know its value under normal direct-current working conditions.

A transformer will be seen to supply A.C. to the circuit, the secondary of which is arranged to provide in the region of 30 to 50 volts, depending on the sensitivity of the indicating meter.

Initially, the battery tapping is adjusted to give the required direct-current indication on the D.C. milliammeter. Next, the meter switch is set on position 1 and a careful note taken of the voltage registered on the indicating meter. The meter switch is then set on position 2 and the variable resistor R adjusted until the indicating meter reading coincides with the reading taken on switch position 1. Finally, R is measured and the following formula used to find the inductance value:  $L = R/314$ , where L is the inductance in henrys, and R the value of the resistance in ohms. This test is made on the assumption that the impedance of the circuit is equal to the inductance, and that a 50 cps. A.C. supply is used.

## The Valve Voltmeter (22)

The valve voltmeter, sometimes called the electronic testmeter or electronic multimeter, is progressively becoming more demanded for the testing and maintaining of sensitive electronic apparatus and television receivers. Generally speaking, the valve voltmeter in equivalent form to the multimeter is endowed with all the features of the latter, coupled with extremely high sensitivity approaching that of a delicate galvanometer.

With a valve voltmeter the voltage to be measured is applied to the grid circuit of a valve, and for this reason the resulting relatively high input resistance/impedance renders the instrument particularly suitable for use upon electronic circuits, and high-resistance networks, which are usually incapable of supplying sufficient energy to drive directly a normal moving-coil meter without causing a serious voltage drop and alteration in the power distribution of the circuit under test. As will be remembered, this aspect of the multimeter was fully dealt with in Part Two of this series, under Instrument Sensitivity (3).

Essentially most valve voltmeters are designed in a valve bridge circuit, a typical arrangement being that shown in Fig. 27. Here a double triode valve is used, with each section operating as a cathode follower. Its mode of working simply relies upon the measurement of the difference in potential obtained

between the two cathodes as the result of comparing two voltages between the grids.

The voltage applied to the grid of section (b) is obtained from the potential divider network connected across the H.T. supply. This voltage can be controlled by the two variable potentiometers R1 (giving a coarse control) and R2 (giving a fine control). Initially both controls should be adjusted, with the instrument input terminals shorted, to provide a zero reading on the milliammeter connected between the cathodes.

It follows, therefore, that the application of a *negative* voltage to the grid of section (a) will reduce the voltage drop across the corresponding cathode resistor R3; this will disturb the balance between the two valves and thereby permit a flow of current through the milliammeter.

We can now well realise, then, how the relatively high input impedance of the triode successfully isolates the circuit under test from the low resistance of the moving-coil milliammeter.

It is as well to bear in mind at this point that the test voltage is not usually applied directly to the grid of the valve, but it is general practice to make use of a bank of switched series resistors for voltage selection, and a bank of switched parallel resistors for current selection, the same as the function of the multimeter. The actual value of the resistors employed will, of course, be considerably higher than those used in the same positions in an ordinary multimeter, because they will need to correspond to the higher input impedance of the valve voltmeter.

From the D.C. application aspect most of what has already been said in respect to the multimeter applies equally to the valve voltmeter. If a commercial model is being used the instruction manual should be care-

fully studied to avoid disappointing results, for each particular instrument, although from the same family tree, possesses individual characteristics.

Even though most valve voltmeters have the robustness of a multimeter, they should, nevertheless,

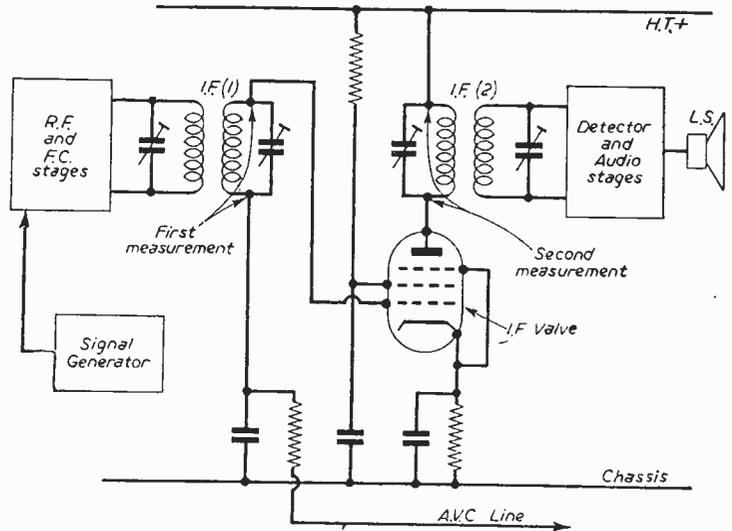


Fig. 28. — Showing the points in a typical I.F. amplifier stage at which comparative R.F. voltage measurements can be taken with a valve voltmeter.

always be handled with respect. It is desirable to look on such an instrument as a somewhat delicate multimeter of very high sensitivity; the same applies, of course, when the instrument is being used for servicing and testing.

Instead of using an internal metal rectifier for A.C. applications as with the multimeter the electronic testmeter or electronic multimeter invariably employs an external diode probe. As the result of the probe's low capacitance construction it is ideally suitable for measuring high-frequency voltages without loading the circuit under test to any serious degree.

Moreover, unlike the universal multimeter, most valve voltmeters respond to the *peak* value of the applied A.C. voltage, although it will, of course, be scaled to read in R.M.S. values, the same as a multimeter.

This is all very well provided the applied voltage is of sine waveform, but should it deviate from the ideal the possibility of an error in reading should always be recognised. Such an error would be of different calibre from that given on a universal multimeter subjected to the same conditions, since, as we have previously considered in some detail (see Parts Three and Four of this series), a rectifier moving-coil instrument is calibrated on A.C. proportional to the *mean* value of the waveform with which it is presented.

A valve voltmeter, being calibrated on A.C. proportional to the *peak* value of the applied waveform, will thus actually measure 1.4 volts due to an A.C. sine wave of one volt R.M.S. The main point to remember here is that even though the instrument will measure the amplitude of the positive peaks the

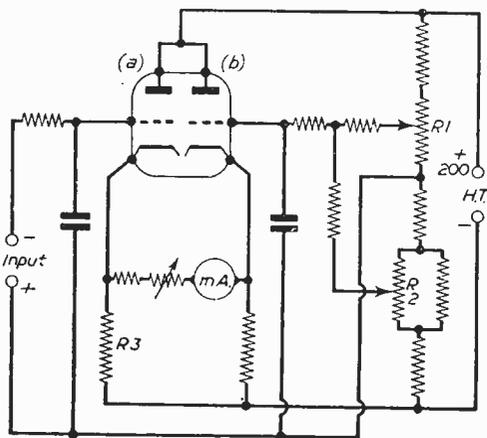


Fig. 27.—A typical valve voltmeter circuit.

reading will be in R.M.S. values, that is because the scale is calibrated for peak *divided* by 1.414 (i.e., R.M.S. values).

### Comparative R.F. Measurements (23)

As already intimated, the low capacitive construction of the external probe (generally in the region of a few picofarads only) readily permits the measurement of quite high-frequency voltages. In fact, a number of commercial valve voltmeters cater for the measurement of A.C. voltage up to and, in some cases, above 100 Mc/s.

Such a feature enables the signal voltage actually appearing across the various tuned circuits in a broadcast or television receiver to be measured either by injecting a signal from a signal generator into the receiver aerial sockets or into the grid circuit of the stage under examination, or by making use of the signal picked up by the aerial in the usual way.

Clearly, this not only represents a desirable method of tracing the actual R.F. signal through a receiver—perhaps as a quick way of pin-pointing a defective

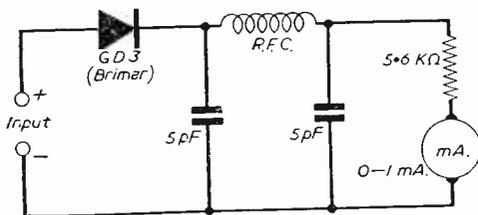


Fig. 29.—A circuit of a typical crystal voltmeter or crystal type R.F. probe.

stage—but, since precise readings can be obtained, it also has the advantage of giving the operator some idea of the gain of the various stages and whether or not they are amplifying the signal to the best of their ability.

Fig. 28 depicts a typical I.F. stage of a broadcast receiver. Now let us suppose that a valve voltmeter is connected across the secondary winding of the first I.F. transformer, the points corresponding to the "first measurement," and that the receiver is tuned to accept a signal given by the signal generator, which is either connected to the aerial terminals and adjusted to the signal frequency or connected to the signal grid of the frequency changer valve and adjusted to the intermediate frequency.

Let us further suppose that under these conditions a reading of, say, 0.5 volts is given by the valve voltmeter. Now, leaving the signal generator set at the original R.F. output, we remove the valve voltmeter from across the secondary winding of I.F. (1) and connect it across the primary winding of I.F. (2). We shall obviously hope to obtain a somewhat higher voltage reading as the result of the I.F. valve's amplification. Let us suppose that we measure, say, 25 volts, then, straightaway we know that the valve is giving a voltage amplification of 25/0.5 volts—something like 34 db.

Incidentally, these figures should not be taken as wholly representative of the possible amplification of a stage of this kind—a lot depends on the actual circuit and the quality of the valve voltmeter used. Nevertheless, it serves admirably to illustrate the ease by which relative measurements of this kind

can be taken, and also provides a good idea of the scope of application of a valve voltmeter.

One or two precautions must, of course, be observed when using such an instrument for this purpose. In the first place, it is essential to employ the shortest possible length of wire to connect the probe to the test-points—it being sometimes desirable to connect the earth terminal of the probe to a true earth on the chassis under test.

Further, one must always recognise the possibility of the capacitances of the probe and associated wiring disturbing the balance of the tuned circuit across which it is connected. For this reason, especially if an accurate reading is demanded, the associated tuned circuits should be peaked up after the probe has been connected, making sure, of course, that the circuits are retrimmed back to normal after the test has been performed.

Do not forget that the valve voltmeter used may be insufficiently sensitive to measure small R.F. voltages, such as those present at the grid of an early stage. If the signal generator voltage is stepped up in an endeavour to procure a reading of reasonable magnitude under such a condition it might well be powerful enough to overload the associated valve, and thus give rise to a reading which is far from true.

### R.F. and High Voltage Probes (24)

The probe itself is usually self contained and embodies an R.F. diode valve which picks up its heater voltage from the valve voltmeter's power-pack. Germanium crystal diodes are adequately suitable for detecting R.F. voltage, and these are sometimes used in place of a valve. Such diodes have the advantage, on the one hand, of not requiring a heater supply, but the disadvantage, on the other hand, of not being able to withstand the application of very high peak voltages. For this reason, therefore, a diode valve is nearly always employed in valve voltmeter probes where they may be subjected to a potential in excess of, say, 20 volts peak.

A typical crystal voltmeter is shown in Fig. 29. As will be seen, this is virtually a detector circuit, the load resistor of which has been broken and a milliammeter inserted in series. Such an inclusion makes the device self contained, and obviates the necessity of connecting it to a valve voltmeter for voltage measurement within the sensitivity range of the milliammeter. Quite a good indication can be obtained on a 0-1 milliammeter in conjunction with a 5.6 K ohm resistor for R.F. inputs of up to 10 volts.

A diode valve permits the application of higher peak voltages, but, even so, an ordinary R.F. diode has a limited rating—usually in the region of 250 volts peak—so one should never be tempted to procure an indication of the pulse voltage existing at, say, the anode of the line output valve or the anode of the E.H.T. rectifier valve in a television receiver by means of a conventional diode probe in conjunction with a valve voltmeter.

For tests of this nature a more substantial probe is essential, making sure that the associated diode valve is well able to withstand a large pulse voltage. It is often a good idea to make use of one of the E.H.T. rectifier valves in this position. The Brimar E.H.T. rectifier valve type R19, for example, represents a valve which is ideal for this purpose.

(To be continued)

# ALPHA FOR VALVES

## GUARANTEED NEW AND BOXED

ACP	0/9	U10	9/-	6AK5	6/8	7B7	8/8
AC6/PEN	5/6	U16	12/6	6AL5	7/-	7C6	8/6
ATP1	6/6	U22	8/-	6AM5	5/-	7H7	8/-
BD11	4/2	U25	14/6	6AM6	7/8	7J7	8/-
PH75M	10/-	U281	10/8	6A05	8/8	7K7	8/6
DH81	10/-	U403	10/-	6AT6	6/-	7S7	8/6
EA50	8/-	U401	10/-	6B4	6/-	7Y4	8/6
EB31	2/-	UAF42	12/-	6BRG	4/-	75	10/-
EB41	11/-	UB41	9/-	6B46	8/8	77	8/-
EB533	7/8	UBC41	11/-	6B15	8/-	80	8/6
EB541	11/-	UCB42	13/6	6B17	9/8	81	8/6
EBF50	11/6	UF41	11/6	6B18	8/8	807	7/6
EC52	6/3	UL41	11/6	6BX6	14/8	8D2	2/9
EC91	9/-	UU6	10/-	6C3	8/-	9061	5/6
EBH55	13/-	UY41	10/6	6V5GT	7/8	9062	5/6
EC142	10/6	VP23	8/-	6C6	6/6	9063	5/6
EC180	14/6	VR10530	5/6	6C8	7/-	9064	5/6
EF36	8/-	WR116	6/-	6C9	9/-	9066	6/-
EF39	8/6	VR150300	9/-	6D6G	13/6	954	2/-
EF41	10/-	VT28 (LE22)	6/3	6D3	7/8	955	4/9
EF508yi	8/-		6D6	7/3	956	3/6	
EF50	6/6	VT301 (TT11)	6/-	6P6G	7/8	10C2	13/6
EF80	11/6		6P6M	8/6	10F1	10/-	
EK82	6/-	VU39 (MU12)	8/6	6C9	9/-	10P9	13/6
EL12	12/8	14)	8/6	6P13	13/6	10L011	11/-
EL41	11/6	VU111	3/6	6P14	12/6	10P13	11/6
EL42	13/6	VU120A	3/-	6P60	6/6	10P14	11/6
EL54	12/3	W81	9/-	6H6	3/8	12A6	6/9
EM31	9/-	W77	8/6	6F5G	8/-	12AH3	11/6
EV51	14/6	OZ4	6/-	6B4GT	5/8	12AT7	9/-
EZ40	10/-	1A3	9/-	6J5M	6/8	12AX7	10/-
EZ41	11/-	1A5GT	6/6	6J6	6/8	12C5	8/-
EL148	2/-	1A7	11/6	6J7G	6/8	12C6	8/-
H20	5/6	1C5GT	8/-	6K6GT	6/8	12H6	5/-
H63	7/8	1L4	7/8	6K7G	8/-	12J7	8/-
HL1320	5/8	1L15	8/8	6K7M	6/9	12K7	6/6
HL23DD	7/6	1R5	7/6	6K7M	6/9	12K7	6/6
K732	10/-	1R5	7/6	6K80	8/-	12K8GT	9/-
K733C	11/6	1T4	7/8	6K8GT	9/8	12Q7GT	9/-
K736	11/6	1U5	8/-	6L19	11/8	12RGT	7/8
K7W61	7/9	220V53	6/8	6L19	12/8	12RH7	5/6
K7W63	7/9	2A3	6/9	6L6G	9/-	12RH7	5/6
MR12EN	6/-	2X2	5/-	6L7M	7/8	12RK7	6/6
P01	3/9	3A4	8/-	6X7	7/8	12ML7	9/-
PC384	12/6	3D6	6/-	6K7G	8/-	12Q7	8/6
PCF80	12/6	3Q4	9/-	6K7GT	8/-	12RH7	7/8
PCF82	12/6	305	10/-	6AG7	7/8	20H1	10/8
PCN25	8/-	3B4	8/8	6SH7	8/-	20P2	12/6
PCN46	8/8	3V4	8/-	6SH7GT	8/-	20L1	10/8
PL81	14/8	41P1	3/-	6SK7	6/3	20P3	11/-
PL82	11/6	42	8/-	6SL7	8/-	20P4	11/-
PL83	13/-	5U4 (T52)	8/8	6SN7GT	9/-	25AG6	10/8
PM12M	10/-	5Y3GT	8/8	6RGT	9/-	25L0GT	8/-
PY80	11/-	5Z3	8/6	6U5G	8/6	25T4GT	12/-
PY81	11/8	5Z4G	8/6	6V6G	7/8	25Z4G	9/-
PC35	15/-	6AT	10/8	6V6GT	7/8	25Z5	8/-
MS30	8/6	6AG6	10/8	6X7	15/-	35L6GT	8/9
SP41	3/6	6AC7	8/8	6X4	8/-	35W4	10/8
SP61	3/9	6AG5	7/8	6X5GT	7/9	35Z4GT	8/6
TP26	9/-	6AJ5	9/-	7B6	9/8	50L6GT	8/8

**SPECIAL OFFER**  
1 Pair 866A VALVES, 12/6 PAIR POST 1/8.

**SPECIAL OFFER**  
VR697 TUBES PICTURE TESTED. 20/-EACH. CARRIAGE 3/6.

**MAINS TRANSFORMERS 3-WAY MOUNTING TYPE**

MT1	Primary: 200-220-240 v. Secondaries: 250-0-250 v. 80 mA 0-6 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. .... 17/8 ea.	MT2	Primary: 200-220-240 v. Secondaries: 350-0-350 v. 80 mA. 0-4 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. .... 17/8 ea.
-----	--	-----	---

**TERMS:** Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage 2/3.

### MAIL ORDER ONLY

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."

**CHASSIS**  
Aluminium Unfilled with Reinforced Corners. Available in the following sizes:  
6in. x 4in. x 2 1/2in. .... 4/6 ea.  
8in. x 6in. x 2 1/2in. .... 7/3 ea.  
10in. x 7in. x 2 1/2in. .... 8/8 ea.  
12in. x 8in. x 2 1/2in. .... 9/6 ea.  
14in. x 8in. x 2 1/2in. .... 12/- ea.  
16in. x 9in. x 2 1/2in. .... 12/- ea.  
All are four sided—ideal for radio receivers—amplifiers—powerpacks, etc.

**SENTREX RECTIFIERS**  
RM1, 3/9 ea.; RM2, 4/2 ea.; RM3, 5/- ea.; RM4, 16/- ea.

**METAL RECTIFIERS**  
12 v. 1 amp., 1/6 ea.; 12 v. 1 amp. 4/6 ea.; 2 v. 1 amp., 3/- ea.; 250 v. 45 mA., 6/3 ea.; 250 v. 75 mA., 7/6 ea.; 300 v. 60 mA., 7/6 ea.

**GOLDING PICK-UP HEADS.** Pick-up head type No. 112 (2/00 ohms), complete with lead. Price 17/8 each.

**NYLON DRIVE CORD**  
25 yard reel nylon drive cord on wooden reel, 2/9 ea.

**BI CONDENSERS**  
Waxed cartons, with flying leads. 4 mfd., 500 v., 1/6 ea.; 4 x 4 mfd., 500 v., 3/4 ea.

**LOUDSPEAKER UNITS**  
R. & A. 10in. unit. .... 25/6 ea.  
Plessey 6in. lightweight unit. .... 18/6 ea.  
R.E.M. 5in. standard type. .... 17/8 ea.  
Electroba 6in. with transformer. .... 15/- ea.  
Trox 6in. water type. .... 20/- ea.  
Plessey 5in. lightweight unit. .... 17/8 ea.  
Mains energised 5in. unit, 1,000 Ω 21/- ea.  
Mains energised 6in. unit, 600 Ω. .... 17/8 ea.  
Rola 5in. unit. .... 17/8 ea.  
Goodmans 5in. unit. .... 18/6 ea.  
Plessey 12in. lightweight unit. .... 37/6 ea.

**CRYSTAL DIODES**  
Plastic case, wire ends, 2 for 2/1.

**HEATER TRANSFORMERS**

230 v. Input 2 volt 5 amp. .... 4/6
230 v. Input 2 volt 3.0 amp. .... 7/9
230 v. Input 4 volt 1.5 amp. .... 5/-
230 v. Input 4 volt 3.0 amp. .... 10/-
230 v. Input 5 volt 2.0 amp. .... 10/-
230 v. Input 6.3 volt 1.5 amp. .... 6/-
230 v. Input 6.3 volt 5 amp. .... 6/-
230 v. Input 6.3 volt 3.5 amp. .... 5/-
230 v. Input 12 volt 7.5 amp. .... 5/-
L.E.M. Silver Mica, 1,000 PF 10% 3 1/2 ea.
L.E.M. Silver Mica, 100 PF, 5% 3 1/2 ea.
T.C.C. Silver Mica, 100 PF, 10% 3 1/2 ea.
L.E.M. Silver Mica, 300 PF, 10% 3 1/2 ea.
Hunts Silver Mica, 374 PF, 1% 3 1/2 ea.
L.E.M. Silver Mica, 320 PF, 10% 3 1/2 ea.
L.E.M. Silver Mica, 25 PF, 20% 3 1/2 ea.
T.C.C. Silver Mica, 1,000 PF, 10% 3 1/2 ea.
Tabular Construction, 5mfd., 500 v. 6d. ea.
Yaxley Switch, 1 pole, 8 way, 1 1/2in. Spindle. .... 1/9 ea.
Arrow Toggle Slotted Dolly 8 P.... 1/9 ea.
Single Screened Cable. .... 6d. yd.

**PUBLICATIONS**  
Midget Radio Construction Manual 3/6 ea.  
Radiofideo "F" An inexpensive tape recorder. .... 2/8 ea.  
Radiofideo "B" A practical Oscilloscope. .... 2/8 ea.  
Radio Calculations Manual. .... 3/6 ea.  
Practical Circuits Manual. .... 3/9 ea.  
Radio & Television Laboratory Manual. .... 2/6 ea.  
Wire Wound Controls R.C.A. Pre-set, 25 pins. .... 2/8 ea.  
Colvern CLR1001, 10 K ohms. .... 2/- ea.  
Colvern CLR1232/298, 500 ohms. .... 2/8 ea.  
Colvern 1,000 ohms, spindle 1in. .... 2/6 ea.  
Eric Mains Dropper, 7 1/2 ohms, 1 1/2in. Tapped. .... 1/4 ea.  
Dubbler Mounted Mica APW 1005 4 1/2 ea.  
HF Pipe Wound Chokes. .... 1/- ea.  
Vibrator Clips. .... 3/6 ea.  
Dubbler Nitrogen B45, 12mfd 2.0. 5/6 ea.  
International Octal Valve Holders. .... 1/- ea.  
Faxolin. .... 4 1/2 ea.  
Vitronics Enamelled Resistors. .... 1/- ea.  
12 v. Vibrators, 4 pin. U.X. 1. .... 6/6 ea.  
T.C.C. 10 mfd., 450 v. C14. 1/6 ea.  
Wire Ends. .... 1/11 ea.  
T.C.C. 24 mfd., 350 v. Ceigle Tag ends. .... 2/8 ea.  
Cyllin Trimmers, No. 37, 500PF. 1/6 ea.  
Faxolin Trimmers, 100/0. .... 6d. ea.  
Walter Trimmers, 250/20. .... 6d. ea.  
Ceramic Trimmers, 100/100. .... 6d. ea.  
Ceramic Trimmers, 80/400. .... 6d. ea.

### EX GOVERNMENT AND SURPLUS CONTROL

This popular range is suitable for all Television constructors, etc. Keep your costs down when building the "Arrow" or "Simplex" receivers. Available: 500 Ω, 600 Ω, 1,000 Ω double types, 2 K Ω, 5 K Ω, 10 K Ω, 20 K Ω, 25 K Ω, 50 K Ω, 200 K Ω, 100 K Ω, 4 meg. Ω, 1 meg. Ω, 1 meg. Ω, 2 meg. Ω, 60 K Ω double type. All 1/2 each.

**PENCIL RECTIFIERS**  
K3 25, 5/3; K3 40, 7/6; K3 45, 8/2; K3 50, 8/8; K3 90, 9/8; K3 100, 14/8.

**SELF-TAPPING SCREWS (PK)**  
No. 4, 2in. long, 3 1/2 doz.

**"CLEM" TRAVELLING IRON WITH ASBESTOS STAND**  
Size 4in. x 2in. x 2 1/2in., including handle complete with lead and switch to enable it to be used on any voltage (rated on the lead). 1/8 each. 4 mud Block Condensers, 1,500 v. 4 - 4 each.

**FUSES**  
1, 1, 1, 2, 3, 5 amp. 1 1/2in. Standard Cartridge Fuses, 3/8 doz. Insud Mounting Press switch, 1/3 each.

**"SATCHELWELL" THERMOSTAT**  
Complete with mounting bracket and including 2 space heating units 230 v. and 250 v., 32.6 set.

**CARRYING CASE**  
Suitable for use as a projector or recording case size 15in. x 9in. x 1 1/2in. Internal dimensions: 14in. long, 1 1/2in. deep, 5 1/2in. front H.T., 8 1/2in. rear H.T. With a black rexine finish. Weight 5 1/2 lbs. 13/6 each. Post & Packing 2/6.

**"Arrow" Condenser Clips, 1 1/2 ea.**  
Paper Block 10 mfd. 450 v. 3/- each.  
EF50 PRE-AMPLIFIERS, LEAD VALVE  
Conical input and output complete with plug for H.T. and L.T. 6/- each.


**METERS**  
0-50 to 5 Milliammeter by Ferranti—Panel Mounting, 7/6 each.

**JUNCTION BOXES**  
Type 5X 22x24 30W, 1/6 each.

**OSMOR COIL PACKS**  
Type H.O., 48/- each. Type L.M., 40/- each. Type T.H., 50/- each. Type TRP, 40/- each.

**SPRAGUE CONDENSERS**  
.05 mfd., 500 v.; .01 mfd., 1,000 v.; 1 mfd., 500 v.; .02 mfd., 750 v. All 8/- doz.

**LOUDSPEAKER CABINETS**

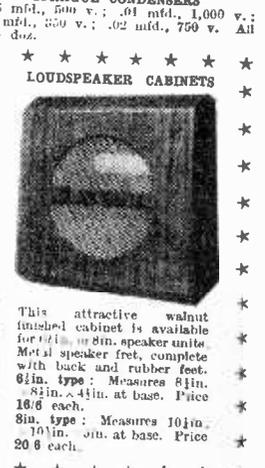

This attractive walnut finished cabinet is available for 6in. or 8in. speaker units. Metal speaker fret, complete with back and rubber feet. 6in. type: Measures 8 1/2in. x 8 1/2in. x 4 1/2in. at base. Price 10/6 each. 8in. type: Measures 10 1/2in. x 10 1/2in. x 5in. at base. Price 20/8 each.

**SPECIAL OFFER**  
ACOS CRYSTAL MICROPHONE, TYPE 22, COMPLETE WITH TABLE STAND. LISTED 48NS. OUR PRICE 55/- POST 1/8.

# ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

# RADIO SUPPLY CO. (Leeds) LTD.

32, THE CALLS, LEEDS, 2 (For Terms see full page advert)

**CHASSIS** (Undrilled Aluminium)  
 18 s.w.g. amplifier (4-sided).  
 14in. 10in. 3in. 7 1/2in. 10in. 3in. 8/3  
 18 s.w.g. receiver type.  
 6in. 3 1/2in. 1 1/2in. 1 1/2in. 5 1/2in. 2in. 3/3  
 7 1/2in. 4 1/2in. 2 1/2in. 1 1/2in. 6in. 2 1/2in. 3/11  
 16 s.w.g. receiver type.  
 12in. 8in. 2 1/2in. 5/3 16in. 8in. 2 1/2in. 7/6  
 20in. 8in. 2 1/2in. .... 8/11  
 16 s.w.g. amplifier type, 4-sided.  
 12in. 8in. 2 1/2in. .... 10/11  
 16in. 8in. 2 1/2in. .... 13/6  
 20in. 8in. 2 1/2in. .... 13/6  
 14in. 10in. 3in. .... 13/6

**EX-GOVT. TRANSFS.** 230 v. 50 c.c.s.  
 8.8 v. 4 a. 9/9; 0-11-22 v. 30 a. 72/6;  
 0-16-18-20 v. 35 a. 79/6; 7.7 v. 7 a. C.T.  
 4 times. 25/9. Carr. 5/-  
 48 v. 1 a. 9/9. Carr. 5/- extra on following  
 types: 460 v. 200 mA. 6.3 v. 5 a. 27/9;  
 400 v. C.T. 150 mA., 4 v. 6 a., 6.3 v. 6 a.,  
 6.3 v. 0.6 a., 4 v. 6 a., 4 v. 3 a., 4 v. 3 a.  
 a., 5 v. 2 a., 22/9; 1,220 v. 350 mA. 810-0-810  
 v. 150 mA. 300-0-300 v. 150 mA. 29/9;  
 250-0-250 v. 200 mA., 6.3 v. 8 a., 5 v. 3 a., 22/9.

**AMMETERS** Moving Coil (EX-GOVT.)  
 G.E.C. 0-5 amps. 2in. scale. 11/8.

**SILVER MICA CONDENSERS.** 5, 10, 15, 20, 25, 30, 35, 40, 50, 100, 120, 150, 200, 220, 300, 400, 500, 1,000 (.001 mfd.), 2,000 pfd. (.002 mfd.), 6d. each; 3/9 doz. One type.

**MIDGET MAINS TRANSFORMER.**  
 Manufacturer's Surplus. Primary 220/240 v. Secs. 220-0-220 v. 60 mA., 6.3 v. 2 a. Only 11/8.

**VOLUME CONTROLS** with long (1in. diam.) spindles, all valves less switch. 2/9; with S.P. switch. 3/9; with D.P. switch. 4/6.

**TV. PREAMPLIFIER** (Plessey)  
 For Fringe Areas. Brand New. Complete with 6F13 valve. Only 22/6.

**EX-GOVT. AUTO TRANSFORMERS**  
 Double Wound, 50 c.c.s.  
 10-0-200-240 v. to 10-0-275-295-315 v.  
 1,000 watts. 69/6. Carriage 5/- extra.  
 Single Winding.  
 15-10-5-0-195-215-235 v. 500 w. 27/8.

**EX-GOVT. SMOOTHING CHOKES**  
 250 mA, 10 H 50 ohms ... 14/9  
 250 mA, 10 H 100 ohms ... 14/9  
 150 mA, 10 H 100 ohms ... 11/9  
 150 mA, 6-10 H 150 ohms Trop. ... 6/9  
 100 mA, 10 H 150 ohms Trop. ... 5/11  
 50 mA, 5-10 H 200 ohms... 2/9  
 L.T. type 1 amp. 2 ohms ... 2/8

**EX-GOVT. METAL BLOCK (PAPER) CONDENSERS**  
 4 mfd. 500 v. 2/9; 4 mfd. 1,500 v. 4/9;  
 4 mfd. 2,000 v. 7/9; 6-6 mfd. 400 v. 5/11;  
 8-8 mfd. 500 v. 6/9; 4 mfd. 400 v. plus  
 2 mfd. 250 v. 1/11; 8 mfd. 500 v. 5/9;  
 15 mfd. 500 v. 6/8.

**EX-GOVT. E.H.T. SMOOTHERS**  
 .02 mfd. 8,000 v. cans. 1/11; .25 mfd. 4,000 v. Blocks, 4/9; .5 mfd. 2,500 v. Blocks, 9/9; .5 mfd. 3,500 v. cans. 3/3;  
 1.5 mfd. 4,000 v. Blocks, 5/9; .1 mfd., plus .1 mfd. large Blocks, 8,000 v. 9/6.

**EX-GOVT. VALVES (NEW)**

	Each	Each	Each
IT4	7/9	6V6GT	7/9
IR5	7/9	6X5GT	8/9
IS5	7/9	607	7/11
5Y3G	9/6	12A6	7/9
5Z4G	9/6	12BD	4/9
6K7G	5/11	25Z4G	9/6
6K8G	9/9	35Z4GT	10/6
6SN7GT	9/9		
		AC5PenDD	9/9
		EF36	5/9
		EB91	8/9
		EF91	7/9
		EL33	9/6
		SP41	1/11
		SP61	2/9

**I.L.T. ELIMINATOR AND TRICKLE CHARGER KIT.** Input 200-250 v. A.C. Output 120 v. 40 mA, fully smoothed and rectified supply to charge 2 v. acc. Price with steel case and circuit. 29/6. Or ready for use. 8/9 extra.

## R.S.C. 4.5 WATT A5 HIGH GAIN AMPLIFIER



A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads, in addition to all other types of pick-ups and practically all mikes. Separate Bass and Treble controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 D.B. down. 15 D.B. of negative feedback is used. H.T. of 300 v. 25 mA, and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape Deck preamplifier. For A.C. mains input of 200-230-250 v. 50 c.c.s. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate), with green crackle finish, and point-to-point wiring diagrams and instructions. Exceptional value at only 24/15/-, or assembled ready for use 25/- extra, plus 3/6 carr.

**RF28 UNITS BRAND NEW, CARTONED.** Only 39/6. Carr. 2/6.

**SPECIAL OFFER.** Ex-Equip. Goodmans 3in. P.M. Speaker with Battery pentode output trans., 12/9.



**POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES.**

**PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME**

City and Guilds Grouped Certificates in Telecommunications: A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

**The advantages of E.M.I. training.** ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

**NEW LEARN THE PRACTICAL WAY.**  
 With many of our courses we supply actual equipment. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.


**Courses from 15/- per month**

**POST THIS COUPON TODAY**

Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 32K  
 43 Grove Park Road, London, W.4.  
 Phone: Chiswick 4417/8.

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 JULY \_\_\_\_\_  
 SUBJECT(S) OF INTEREST \_\_\_\_\_

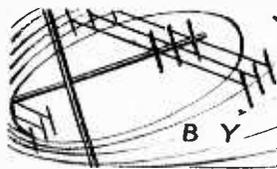**EMI INSTITUTES**  
 The only Postal College which is part of a world-wide Industrial Organisation.



# On Your Wavelength

BY THERMION

## Evangelism on the Air

I LISTENED to the perfervid rambling religious rantings of 15,000-dollar-a-year hot-gospelising William Graham who likes to be known as "Billy" (to be known by a pet contraction of a Christian name is, of course, to give an impression of popularity!). I have come to the conclusion that the BBC made a grave mistake in granting programme time to this American evangelist, with his minatory criticism of the whole of mankind as sinners, as if he were the only man in step. He keeps on and on about sin, without defining what it is, and prescribes cures for all our spiritual ills, rather like a doctor prescribing a cure for measles for a patient who is entirely healthy.

We have had these hot-gospellers before, from the time of Sankey and Moody. Not so many years ago, Mrs. Aimie McPheerson stumped the country on a similar mission, but evidently the effects of early evangelism were short-lived. I am tempted to ask who is Mr. William Graham that he should sit in judgment on the rest of the world and endeavour to reform them. He may be wrong! In any case, I should have thought that the reformation of sinners in his home country of America would be a full-time, life-time job.

The hysterical crowds who attend his meetings and the larger audience who listen to him on the air and on television are not stray sheep who have wandered from the fold and are in need of spiritual uplift. They are mainly curious sightseers, attracted to the meetings by the banging of the big publicity drum, posters worthy of a circus and publicity bally-hoo more in keeping with the film industry than with religion.

In my view, it is particularly regrettable that the BBC has been guilty of this lack of judgment, which is a studied slight on English preachers. I understand that William Graham's entourage consists of producers, assistant producers, advance publicity managers, etc. As a religious scholar myself, I found his sermons circumlocutory and full of periphrase. Would the BBC have given the same programme time to such a mission organised, say, by the Archbishop of Canterbury?

Graham is a self-appointed saviour of mankind anyhow!

## One-Man Bands

I HAVE always criticised the policy of the BBC in presuming that one man only should conduct a feature programme—Philip Harben, for example, as the cookery expert. All of the housewives of this country will, if they take his advice, become Harbenised cooks. There are other experts in the culinary art who may differ from Mr. Harben and his methods of appealing to our gustatory organs. If it is necessary to teach women how to cook by means of lessons on the television screen, let us have a variety of chefs for variety is the spice of gastronomy.

Readers will remember my criticism of that most stupid programme, *The Brains Trust*, which was any-

thing but brainy. The BBC presumed that a small panel with an occasional guest could answer any question sent in by listeners. The fact is that they never answered any questions but expressed opinions on topics where they could never be right or wrong. I, for one, am thankful that this particular programme finished when Joad was forced to vacate it for reasons which are well known. Let us have fewer one-man bands, BBC!

## The Parlour Game Craze

THE BBC continues to develop the parlour game style of programme because it says its listener research bureau indicates that they have a very large audience. Are they not, however, becoming played out and boring?

## Misuse of Callsigns

I RECEIVED a letter from a member of the Nottingham University Students' Radio Society criticising my comments on I.S.W.L. It was signed "R Bastow (G3BAC)". I accordingly wrote to Mr. Bastow, who also lives in Nottingham. He denies authorship of the letter. I then accordingly wrote to the address given on the original communication and received an anonymous reply from a member of the Society admitting that he had misused Mr. Bastow's callsign. I will report developments. Incidentally, the I.S.W.L., to whom I wrote, did not have the current address of Mr. Bastow! I have since informed them of it.

I have also received a number of other inspired letters concerning the I.S.W.L., but they promptly went into the W.P.B.

My paragraphs have had the effect of gingering up the organisation of a large number of clubs who were unaware of their legal obligations, and I should be glad to receive details of any club which readers think is not run on constitutional and democratic lines.

## Radio Research

THOSE interested in the progress of radio research should certainly read a booklet on that subject published at 2s. 6d. by the Department of Scientific and Industrial Research. It is a most interesting booklet and surveys the work the D.S.I.R. has conducted during the past year. The main emphasis of the research programme of the Radio Research Board for the year has been on the problems of wave propagation, especially at very high and ultra-high frequencies.

## The Radio Show

WITHIN a few weeks we shall all be making our annual pilgrimage to Earls Court. Frequency-modulation and I.T.A. will be very much to the fore but, at the moment of going to press, I have not heard of any startling innovations. This journal will, of course, be represented there as hitherto, and our stand will be the meeting place for those thousands of amateurs who continue to build rather than buy.

# A Telephone Attachment for a Tape Recorder

A NOVEL DEVICE FOR RECORDING TELEPHONE CONVERSATIONS

By J. Brown

TELEPHONE attachments for tape recorders are rather expensive pieces of apparatus to purchase, so the writer decided to experiment in building one. After various attempts, there matured the unit explained below, and the results are certainly proving well worth while. Calls at

The aluminium tube was next to be drilled, one hole for the leads to the recorder and one hole for the suction cup. The suction cup was originally for holding some tooth-brush holder or similar toilet device, and had a flange on it. This was  $\frac{3}{8}$  in. in diameter, so a  $\frac{3}{8}$  in. hole was drilled in the tube for the cup, and  $\frac{1}{4}$  in. hole for the lead. These holes were opposite each other.

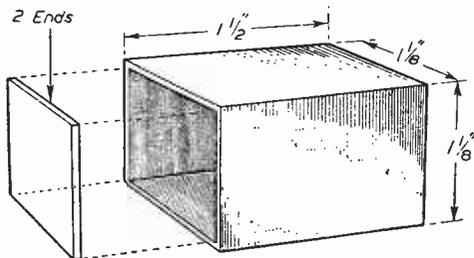


Fig. 1.—The base, made from aluminium tube.

3-400 miles come in clearly and both sides of the conversation are recorded.

The base was made from aluminium tube of square section  $1\frac{1}{8}$  in. and about  $1\frac{1}{2}$  in. long. This was originally from a cross-bar of a TV aerial. Two ends were made to be a tight press fit in the ends of the tube. Then a piece of silver steel was filed so as to make it a good tight fit inside the tube,  $\frac{1}{4}$  in. diameter and approximately 1 in. long. This was fitted into 2 pieces of bakelite approximately  $\frac{3}{4}$  in. diameter and  $\frac{1}{4}$  in. thick to serve as cheeks for the solenoid or winding. In each of the 2 bakelite washers were drilled a  $\frac{1}{16}$  in. hole, the purpose of which will be shown later. Next came the winding. This was approximately 450 turns of 30 s.w.g.,. One end of the winding came through one hole, and the end of the winding after 450 turns were wound on came through the other hole. These were used for the output leads connection.

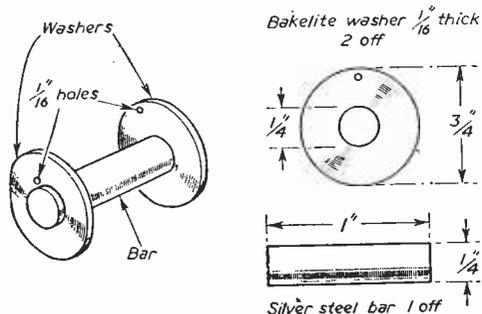


Fig. 2.—The solenoid or winding, fitted with bakelite cheeks.

## Assembly

First, one end is pressed in the aluminium tube, and filed up to make it look clean, then the suction cup was fitted. The silver steel core and its associated coil is pressed into the tube, and the output leads connected up to the ends of the coil, the whole of the box is filled with wax or pitch. After cooling, press in the other end into the tube.

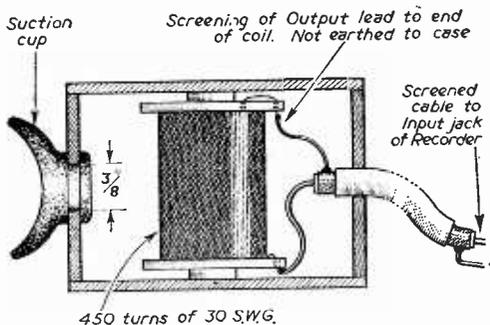



Fig. 3.—The completed attachment.

With the recorder switched on, and the lead from the completed unit plugged in to high gain input socket of recorder, and the unit held by suction cup to back of 'phone, the handset can be removed and the dialling tone recorded. The recording level indicator, whatever type, will fluctuate with the dialling tone. The position of unit on the 'phone was found to be best at the back, the opposite side to the dialling system, and this unit can be a great asset, both for business and entertainment.

## MATERIALS NEEDED

- 1 piece square Aluminium Tube,  $1\frac{1}{8}$  in. section,  $1\frac{1}{2}$  in. long.
- 2 pieces  $1\frac{1}{8}$  in. square for ends
- 1 piece silver steel  $\frac{1}{4}$  in. diameter, approx. 1 in. long.
- Bakelite for washers.
- Wire for Solenoid.
- 1 Suction Cup.
- Screened Cable.
- Wax for filling to keep damp-proof.

# Servicing Radio Receivers

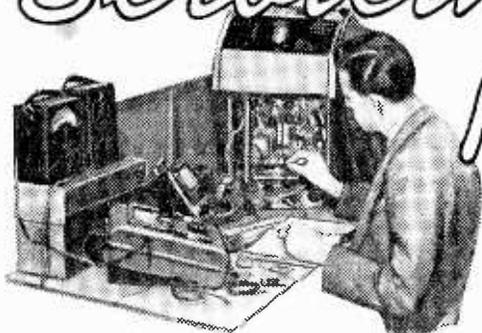

By Gordon J. King, A.M.I.P.R.E.

No. 2.—PYE MODEL P.43

**T**HIS receiver is contained in a small moulded cabinet. It is designed for operation on A.C. mains supplies only, and its self-contained frame aerial brings it into the category of a mains portable.

## Circuit Description

As will be seen from the circuit diagram at Fig. 1, it uses three valves, plus a rectifier, in a superhet arrangement. Coil L1 is the medium-wave frame aerial, and coil L2 (frame aerial) is also brought into circuit when switched to long wave; a short-wave band is not incorporated. The circuit is shown switched in the long-wave position.

Waveband switching is performed by means of a wafer-type rotary switch, but for the sake of simplicity, each switch function is shown separately on the diagram. Switch S1 arranges correct resonance of the frame aerial circuit, as we have already seen, whilst switch S2 connects the long-wave trimmer T2 into the aerial circuit; switches S3, S4 and S5 function to select the corresponding oscillator coil.

T1 is the medium-wave aerial trimmer and T3 the medium-wave oscillator trimmer; variable capacitors C1 and C2 comprise the main tuning gang.

L3 and L4 constitute the medium-wave oscillator coils, feedback being maintained by the anode coil L4 and the coupling capacitor C5. On long wave a single coil only—1.5—is used, feedback being maintained by coupling between the anode and the grid, via C5 again, of the triode section of the frequency changer valve V1 (ECH42).

Mixing occurs within this valve, and the intermediate frequency (470 kc/s) is developed across the first I.F. transformer (I.F.T.1). A voltage at I.F. is thus conveyed to the signal grid of V2, where it is amplified, and developed across the second I.F. transformer (I.F.T.2).

This amplified intermediate frequency signal is carried to the signal diode in V2 (EBF80), where it is demodulated and developed in A.F. form across the load resistor R2. It is coupled from here, through C6 and the volume control R1, to the signal grid of the output valve V3 (EL41). From here it is amplified and converted into power, in the normal manner, to drive the loudspeaker L.S.

A portion of the I.F. signal is taken by way of C7 to the A.V.C. diode of V2, where it is rectified

and passed on as A.V.C. bias to valves V1 and V2.

The H.T. rectifier valve V4 (EZ41) is arranged in a full-wave circuit, smoothing being achieved by C3, C4 and R3. The H.T. tap on the primary winding of the output transformer T1 also aids in reducing mains hum disturbance.

A fixed degree of negative feedback is introduced to the output valve from the coupling between the output transformer and V3's control grid, through C8 and R1.

## Servicing Remarks

Early receivers in this series exhibited rapid failure of the scale lamps. This can be overcome by removing the existing 3.5 volt 0.3 amp bulbs, rewiring the bulb holders in parallel across the heater winding on T2, and installing 6.5 volt 0.3 amp type bulbs.

A rather elusive kind of instability sometimes occurs on these receivers. It probably may not develop until after the receiver has been operating for a considerable time, and even then it may not reveal itself until the receiver is detuned slightly or tuned to another station—this having the effect of reducing the A.V.C. bias and thus causing a rise in the gain of V1 and V2. The disturbance generally starts as a "bubbling" noise which develops into pure oscillation as the receiver is de-tuned slightly off the carrier.

In nearly all cases the trouble is due to a defect in V2, and this can be proved only by valve substitution as a normal valve test most often shows the valve as one hundred per cent. efficient—probably too efficient!

Another cause of instability which this time is unmistakable, is the result of C9 becoming either open-circuit or high in value.

Intermittent loss of volume on early receivers in this series can sometimes be attributed to faulty I.F.

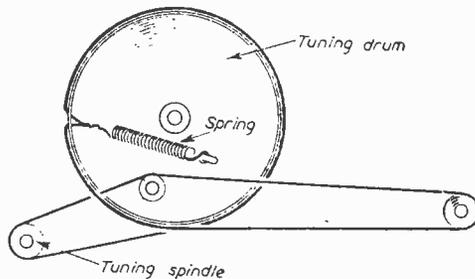


Fig. 4.—Drive cord details.

transformers, or to a fault in one or more of the fixed 100 pF tuning capacitors; a capacitor fault, though, more frequently results in a general fall-off of overall sensitivity. If the defect is definitely occasioned by

the receiver goes dead apart from a hum from the loudspeaker. R3 should be suspected for open-circuit; this fault will, of course, cut off the screen potential to V3, but even so, a hum is generally heard if the ear is placed close to the speaker.

Low volume may mean that C10 is open-circuit, whilst excessive distortion may mean that it is short-circuit. C8 becoming "leaky" also gives rise to excessive distortion.

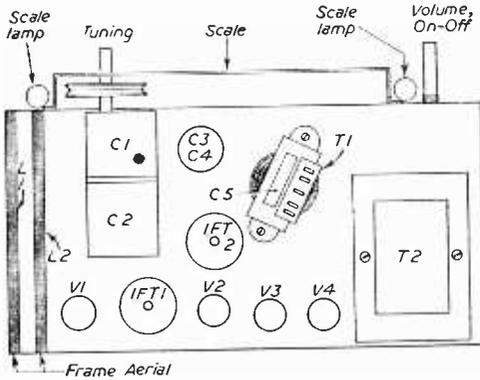


Fig. 2.—Top view of the chassis.

one of the transformers, we would mention that improved replacement types are now available through a Pye dealer.

No signals, but general liveliness throughout the set, should lead one to suspect trouble in the oscillator section. For instance, C5 may become open-circuit or high in value, or R4 may increase in value. If the effect occurs only on one band, then the appropriate oscillator coil and associated capacitors should be carefully examined. In this case, one should also always ascertain that the wavechange switch contacts are making properly. If the switch becomes noisy or intermittent in operation, a few carefully applied drops of "switch clean" works wonders.

A noisy volume control can also be treated in a similar manner, but in this case, to avoid ruining the carbon track, a few drops of "switch clean" should be instilled down the spindle bush, the control given one quick turn and then left for about ten minutes, after which time the control should be actuated vigorously for about one minute with the receiver disconnected from the mains.

If this procedure does not result in noise-free operation, then control replacement is long overdue.

If the receiver suddenly goes completely dead and the valves remain alight, C5 should be suspected for short-circuit and the primary of T1 for open-circuit. If

**Alignment Procedure**

It should first be established that the tuning pointer coincides with the locating dot marked at the long-wave low-frequency end of the tuning scale when the tuning gang is fully closed. Next, the A.V.C. should be made inactive by shorting the A.V.C. decoupling capacitor C11 with a short length of wire. A correctly loaded output meter may be substituted for the loudspeaker, and throughout the alignment process the A.F. output should not be allowed to exceed 50 mW, it being necessary progressively to reduce the signal generator output as the various circuits are brought into tune.

**I.F. Alignment**

This is a straightforward process which simply

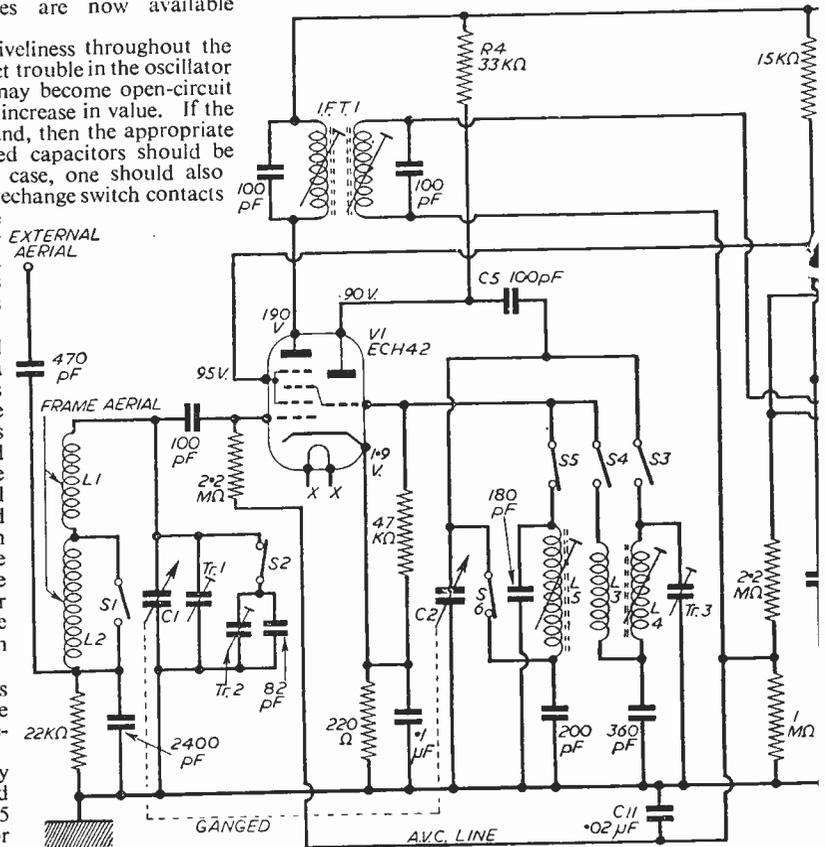


Fig. 1.—Circuit diagram



# MECHANICAL STATION SELECTION

VARIOUS METHODS OF TUNING A RECEIVER TO PRE-DETERMINED SETTINGS FOR QUICK PROGRAMME CHANGES

By F. G. Rayer

**T**HOUGH many arrangements for the automatic, or "push-button," selection of stations employ switch-selected pre-set condensers, other methods, of a "mechanical" character, exist and are used by some manufacturers. In some cases these have advantages. For example, a very large number of pre-sets becomes necessary if a fair number of stations are to be provided for, and the chances of interaction are then increased. If a R.F./F.C. type of circuit were used, three pre-sets would be required for each station. This becomes troublesome if 10 or 12 auto-selected stations are desired, as no less than 30 and 36 pre-set condensers would then be required.

This disadvantage, applicable particularly to large receivers, may be overcome entirely by mechanical means of station selection. Such methods usually permit the gang tuning condenser to be set at once to any of a number of selected positions. The "push-button" tuning is thus accomplished by means of this component and no pre-set condensers whatever are required, as would be so with the switch-selected pre-set method of tuning. Possible losses and instability from switch and condenser wiring are also avoided.

Mechanical methods are thus worth considering with such receivers, and some may be built up without much difficulty.

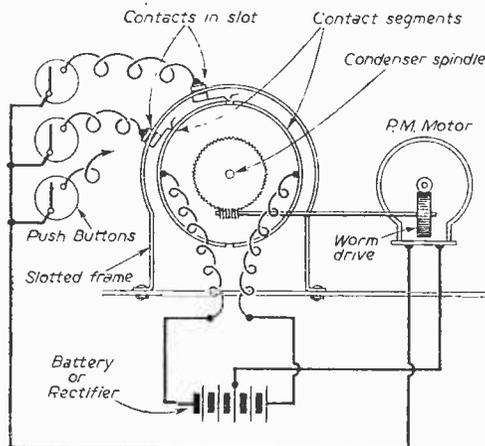


Fig. 1.—A motor-driven selector.

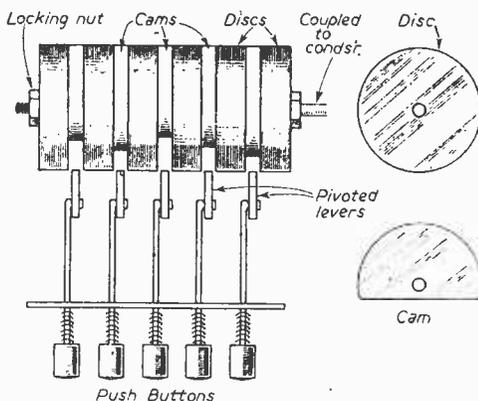


Fig. 3.—A disc and cam actuator.

## Motor-operated Tuning

This method is in several ways an attractive one, and the usual type of tuning drive and dial can be retained, with manual tuning, if desired. For auto-selection, a push-button switch with the desired number of buttons is used. When a button is operated the pointer moves smoothly round on its own, halting at the required station.

A circuit for this type of selector is shown in Fig. 1. The motor is of small permanent magnet type, and turns the gang condenser through a worm or other reduction drive. If manual tuning is used the motor may drive the ordinary tuning knob spindle through a friction drive. (A solid drive is not possible if manual tuning is to be permitted.) An overall ratio of about 500:1 is suitable, and the motor must be of P.M. type so that it can be reversed by reversing the polarity.

Current is taken to the two contact segments by flexible pigtails or brushes. When a push-button is operated the motor commences to run, stopping only when the contact falls into the space between the contact segments. Since completion of the circuit with the other contact segment would reverse polarity, the condenser spindle will always be rotated in the correct direction to bring the space to the contact which has been switched in by the push-button. The latter unit is of the usual type, any button remaining down until a further button is operated. Connections to the switch may be of any length, and multi-core colour-coded flex can be used.

Dry battery operation is feasible because a small motor will have a moderate consumption and will only be drawing current for a short time. With mains sets a rectifier can be used to obtain current from a convenient transformer winding.

To set up, the desired station is tuned in and the related contact moved in the slotted member until it is positioned in the gap between the segments. The contact is then locked, and the condenser will then always return to this position when the button is operated. Should rotation always tend to be away from the gap, then the two leads to the motor are reversed.

## Lever Selector

Some commercial systems are difficult to build, but Fig. 2 shows a simplified method quite easy to arrange. Here, each push-button presses a lever back

(Continued on page 421.)



**COMPLETELY BUILT SIGNAL GENERATOR**

Coverage 120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8.5 Mc/s-25 Mc/s, 17 Mc/s-50 Mc/s, 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in., 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4/19/6, or 34/- deposit and 3 monthly payments 25/- P. & P. 4/- extra.

**Heater Transformer.** Pri. 230-250 v. 6 v. 14 amp., 6/-; 2 v. 24 amp., 5/-; 13 v. 1 amp. 7/6.

500-0-500 120 mA. 4 v. C.T. 4 a. 4 v. C.T. 4 a. 4 v. C.T. 2.5 a., 27/6.

500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a. 4 v. C.T. 4 a., 39/6. P. & P. on the above transformers 3/-.

Pri. 200/250. Secondary 9 v. 3.5 amp., 6.3 v. 3 amp., 12/6.

Pri. 230 v. Sec. 500-0-500 and 500-0-500 250 mA. both windings, 4 v. 3 amp., 4 v. 3 amp., 39/6. P. & P., 5/-.

**T.V. CONVERTER** for the new commercial stations, complete with 2 valves. Frequency — can be set to any channel within the 186-196 Mc/s band. I.F. — will work into any existing TV receiver, designed to work between 42-68 Mc/s. Sensitivity 10 Mu/v. with any normal TV set. Input — arranged for 300 ohm feeder. 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF80 as local oscillator, ECC81 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier, 10 db. Requires power supply of 250 v. D.C. at 25 mA., 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2/10/0. Post and packing 2/6.

**Volume Controls.** Long spindle less switch, 50 K., 500 K., 1 meg. 2/6 each. P. & P. 3d. each.

**Constructor's Parcel: Medium & Long-Wave A.C. Mains 230/250 2-valve plus Metal Rectifier, 22/6.** Comprising chassis 10 1/2 x 4 1/2 x 1 1/2 in., 2 waveband scale, tuning condenser, wavechange switch, volume-control, heater trans., metal rectifier, 2 valves and v/holders, smoothing and bias condensers, resistors and small condensers, and medium- and long-wave coil, litz wound. Circuit and point-to-point, 1/3. Post and packing, 2/6 extra.

**Volume Controls.** Long spindle and switch, 1, 1, 1 and 2 meg., 4/- each, 10 K. and 50 K., 3/6 each. 1 meg., long spindle, double pole switch, miniature, 5/-.

**Standard Wave-change Switches.** 4-pole 3-way, 1/9; 5-pole 3-way, 1/9. Miniature 3-pole 4-way, 4-pole 3-way, 2/6. 2-pole 11-way twin waver, 5/-, 1-pole 12-way single waver, 5/-.

**Constructor's parcel,** comprising chassis 12 1/2 x 8 x 2 1/2 in., cad. plated, 18 gauge, v/h. IF and trans. cut-outs, back-plate, 2 supporting brackets, 3-waveband scale, new wavelength stations names. Size of scale 11 1/2 x 1 1/2 in., drive sp. drum, 2 pulleys, pointer, 2 bulb holders, 5 pax I.O., v/h. 4 knobs and pair of 465 I.F.s, twin gang, 16 x 16 mfd. 350 wkg., mains trans. 250-0-250 60 mA. 3 v. 2 amp., 5 v. 2 amp. and 6 1/2 in. M.E. speaker with O.P. trans. P. & P., 3/6. 39/6.

**Fluorescent Ballast Unit.** Frustrated export order, by very famous manufacturer, at an original cost of approximately £3. VERY LIMITED QUANTITY. Twin 40-watt, both of which are in parallel, can be used as one single 40 watt. The unit comprises of 2 chokes and power-factor condenser in metal case, size 13 x 3 1/2 x 2 in. Completely sealed and fully impregnated. Four-lug fixing. A.C. Mains 230/250 volts. Fully guaranteed. P. & P., 2/6 each. 15/-, 20 watt A.C. or D.C. 200/250 v. fluorescent kit, comprising trough in white-stoved enamel, two tubeholders, starter, holder and barretter. P. & P. 1/6. 12/6.



**PLASTIC CABINET** as illustrated, 11 1/2 x 6 1/2 x 5 1/2 in., in walnut or cream. ALSO IN POLISHED WALNUT. Complete with T.R.F. chassis, 2 waveband scale, station names, new waveband, back-plate, drum, pointer, spring, drive spindle, 3 knobs and back. 22/6. P. & P., 3/6. As above with Superhet Chassis, 23/6. P. & P., 3/6. As above complete with new 5 1/2 in. speaker to fit and O.P. trans. 37/6. P. & P. 3/6. With Superhet Chassis, 39/6. P. & P. 3/6. **Constructor's 3-valve plus Metal Rectifier T.R.F. Parcel.** Complete with gang, valves, v/holders, metal rec., heater-trans., wave-change, volume-control, electrolytics, resistors and condensers. Medium- and long-wave coils, litz wound. P. & P., 3/-, 27/6. Circuit and point-to-point, 1/-.

**Used metal rectifier,** 230 v. 50 mA., 3/6; gang with trimmers, 6/6; M. & L. T.R.F. coils, 5/-; 3 Govt. valves, 3 v/h and circuit, 4/6; heater trans., 6/-; volume control with switch, 3/6; wave-change switch, 2/-; 32 x 32 mfd., 4/-; bias condenser, 1/-; resistor kit, 2/-; Condenser kit, 4/-; Complete A.C. Mains 3 Valve plus metal rectifier T.R.F. kit. In the above cabinet, £23/15/0, plus 3/6 P. & P.

**Used A.C. Mains.** 5 valve, 3 wavebands. Superhet chassis, 11 1/2 x 8 1/2 in. x 3 in. Complete with 3 waveband scale, 10 1/2 in. x 5 1/2 in. Pair 465, K.C.I.F., tuning condenser, main transformer, volume control with switch, Tone Control, 3 waveband coil pack. (This is a completely detachable unit on small chassis.) Various small condensers and resistors biasing condensers. 19/6. P. & P., 3/6. As above 2 wavebands, 15/- P. & P., 3/6.

**Valveholders.** Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded BTG, 7d. Loctal amphenol, 7d. Loctal pax., 7d. Mazda Amph., 7d. Mazda pax., 4d. B8A, B9A amphenol, 7d. BTG with screening can, 1/6. Duodecal paxolin, 9d.

**Twin-gaug. .0005 Tuning Condensers,** 5/- With trimmers, 6/6. Midget .00037 dust cover and trimmers, 8/6.

**Polishing attachment** for electric drills. Quarter-inch spindle, chromium-plated, 5 1/2 in. brush, 3 polishing cloths and one sheep-skin mop, mounted on a 3 1/2 in. rubber cup. P. & P., 1/6. 12/6. Spare sheep-skin mops, 2/6 each.

**Potato & Vegetable Preter,** by famous manufacturer, capacity 4 lbs., complete with water pump. All aluminium construction, white stove-enamel finish. Originally intended for adaption on an electric food-mixer, can be easily converted for hand operation. 39/6. P. & P., 3/-.

**Primary,** 200-250 v. P. & P., 2/-.

**300-0-300 100 mA.,** 6 v. 3 amp., 5 v. 2 amp., 22/6.

**Drop thro' 350-0-350 v. 70 mA.,** 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

**Drop thro' 250-0-250 v. 80 mA.,** 6 v. 3 amp., 5 v. 2 amp., 14/6.

**280-0-280, drop through,** 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/3.

**250-0-250, 80 mA.,** 6 v. 4 amp., 14/-.

**Drop thro' 270-0-270, 80 mA.,** 6 v. 3 amp., 4 v. 1.5 amp., 13/3.

**Drop thro' 270-0-270 60 mA.,** 6 v. 3 amp., 11/6.

**Auto Trans. Input 200/250. H.T. 350 v. 350 mA. Separate L.T.** 6.3 v. 7 a., 6.3 v. 14 amp., 5 v. 3 amp., 25/- P. & P. 3/-.

**Mains Transformer, fully impregnated.** Input 210, 220, 230, 240. Sec. 350-0-350, 100 mA., with separate heater transformer. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp. 30/- P. & P., 5/-.

32 mfd., 350 wkg. ...	2/-	50 mfd., 180 wkg. ...	1/9
16 x 24 350 wkg. ...	4/-	65 mfd., 220 wkg. ...	1/6
4 mfd., 200 wkg. ...	1/3	8 mfd., 150 wkg. ...	1/6
10 mfd., 450 wkg. ...	3/6	60 + 100 mfd., 280 wkg. ...	8/6
15 x 8 mfd., 500 wkg. ...	5/6	50 mfd., 12 wkg. ...	11d.
16 x 16 mfd., 500 wkg. ...	5/9	32 + 32 mfd., min. 275 wkg. ...	4/-
16 x 16 mfd., 450 wkg. ...	3/9	50 mfd., 50 wkg. ...	1/9
32 x 23 mfd., 350 wkg. ...	4/-	Miniature wire ends	...
25 mfd., 25 wkg. ...	11d.	moulded 100 pft. ...	...
250 mfd., 12 v. wkg. ...	1/-	and .001 ea. ...	7d.
16 mfd., 500 wkg., wire ends ...	3/3	280-0-280 80 mA. 4 v. 4 a.,	...
8 mfd., 500 v. wkg., wire ends ...	2/6	4 v. 2 a. ...	14/6
8 mfd., 350 v. wkg., tag ends ...	2/6	250 v. 350 mA. 6.3 v. 4 a.	...
100 mfd., 350 wkg. ...	4/-	twice, 2 v. 2 a. ...	19/6
16 + 16 mfd., 350 wkg. ...	3/3	Auto-trans. input 200/250	...
60 + 100 mfd., 280 v. wkg. ...	7/-	HT 500 v. 250 mA. 6 v.	...
16 + 32 mfd., 350 wkg. ...	6/-	4 a. twice 2 v. 2 a. ...	19/6
		250-0-250 60 mA. 6.3 v. 1.5 a.	...
		0-5-6-3 v. 1.5 a. ...	10/6

Terms of business: Cash with order. Despatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5s. each.

**R. AND T.V. COMPONENTS (ACTON) LTD. 23, HIGH STREET, ACTON, W.3**  
(Opposite Granada Cinema)

Hours of Business: Saturdays 9-5 p.m.  
Wednesdays 9-1 p.m. Other days 9-4.30 p.m.

**NEWNES**

# Radio & Television SERVICING 1953-1954 Models



This single volume gives you in compact form all the essential data you need for dealing with faults and for tuning—circuit diagrams, valve voltages, alignment procedures, component lay-outs, etc.

The book constitutes a special limited edition for those who require only part of the Servicing data in Newnes Radio and Television Servicing Library (five volumes). CLAIM A COPY NOW on coupon below.

## Free for 7 days' EXAMINATION

**TELEVISION MODELS** by . . .  
Ace, Alba, Ambassador, Argosy, Baird, Beethoven, Bush, Champion, Cossor, Decca, Ekcovision, English Electric, Ferguson, Ferranti, G.E.C., Invicta, K-B, McMichael, Marconiphone, Masteradio, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Pye, Raymond, Regentone, R.G.D., Sobell, Stella, Ultra, Vidor.

**RADIO MODELS** by . . .  
Ace, Ambassador, Beethoven, Bush, Champion, Cossor, Decca, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Invicta, McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Peto Scott, Philco, Philips, Pilot, Pye, Raymond, Regentone, R.G.D., Sobell, Ultra, Vidor.

**385 Pages**  
of Television Servicing Data.

**215 Pages**  
of Radio Servicing Data.

"A great help and worth a fortune!" says owner of Newnes previous Servicing books.

POST THIS COUPON TO-DAY!

**GEORGE NEWNES, LTD.,**  
66-69, Great Queen Street, London, W.C.2.

Please send me Volume of Newnes RADIO AND TELEVISION SERVICING (1953/54 Models). It is understood that I may return the work within eight days. If I keep it I will send a first payment of 10s. eight days after delivery, and 10s. 0d. monthly thereafter, until the sum of 50s. has been paid. Cash price within eight days is 45s.

Name.....

Address.....

Occupation.....

Signature.....

(Or your Parent's Signature if under 21)

Place X where it applies

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

R.8

**COMMUNICATIONS RECEIVER R.1155.** Another purchase from the Air Ministry enables us to once again offer this superlative Communications Receiver at prices to suit every pocket. A World Station Gekter, this covers 5 wave ranges: 18.5-7.5 mc/s, 7.5-3.0 mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply adapted for mains use. Full details with circuits of receiver being supplied. New In Maker's Cases and aerial tested. **£11.10.6.** Ditto but slightly used for demonstration purposes. **£9.10.6.**  
**A.C. MAINS POWER PACK OUTPUT STAGE.**—In black metal case enabling the receiver to be operated immediately without any modification, can be supplied as follows:—Less Speaker, **£4.10.0.** with 6in. P.M. Speaker, **£5.5.0.** **DEDUCT 10/- IF PURCHASING RECEIVER & POWER PACK TOGETHER.** Please add carriage costs of 10/6 for Receiver and 3/6 for Power Pack.

**POCKET VOLTMETERS,** not ex-Govt.—Read 0.15 v. and 0-300 v. A.C. or D.C. BRAND NEW & UNUSED. **ONLY 18/6.**

**CRYSTALS.**—British Standard 2-pin 500 kc/s, 15/-. Miniature 200 kc/s and 135 kc/s, 10/- each.

**SPRAGUE.**—1 mfd. 600 v. metal tubulars. 10d. ea., 9/6 dozen (add post).

**R.F. UNITS TYPE 26 & 27.**—For use with the R1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves, EF54, and 1 of EC52. Type 26 covers 65-60 mc/s (3-6 metres) and Type 27 covers 85-65 mc/s (3.5-5.0 metres). Complete with valves and BRAND NEW IN MAKER'S CARTONS. **ONLY 29/6 each.**

**CHOKES.**—1011 60 mA, 4'-, 5H 200 mA, 7/8, 10H, 120 mA, 10/6 (post 1/- ea.).

**SPEAKERS.**—P.M. 6in. less trans., 19/6; 8in. less trans., 16/6; 10in. with trans., 27/6 (postage 2/- ea.).

**CHASSIS OF INDICATOR 233.**—Contains VCR97 C.R.T. holder, 11 valveholders, resistors, condensers, etc., etc. BRAND NEW. **ONLY 10/-** (carr., etc., 5/-).

**E.H.T. TRANSFORMER.**—Normal 230 v. Primary, with Secondary of 2,000 v. r.m.s. (approx. 2,800 v. D.C.). A special offer of interest to all using the VRC97 or similar tube. Size 2 1/2in. W. x 2 1/2in. D. x 3in. H. + 1in. for tag panel. AN UNREPEATABLE ABLE SNIP, and well worth buying as an insurance against failure of existing E.H.T. supplies. **ONLY 15/-** (postage etc., 2/-).

Amounts given for carriage refer to inland only.

**U.E.I. CORPORATION** 138, Gray's Inn Road, London, W.C.1.  
(Phone: T.E.I:minus 7837)  
(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

## G2AK This Month's Bargains G2AK

**METERS.**—2 1/2in. Scale Flush Mounting. 0-10 mA, 0-30 mA and 0-100 mA, 12/6 ea. 2in. Scale Square Flth., 0-50 mA, 0-150 mA, 0-3A Thermo, 0-20 v. d.c., and 20/0/20 A. d.c., 7/6 ea. 2 1/2in. Scale Proj. Type Thermo, 0-15 A, 7/6 ea. 2in. Scale Round Flush 0-1/2 A. Thermo and 0-350 mA ditto, 7/6 ea.

**RACK SIZE CHASSIS.**—17in. long x 2 1/2in. deep x 12in., 16/6; x 10in., 15/-; x 8in., 14/- P. & P. 1/- All 16 s.w.g. ALL.

**VALVES.**—B7G base, 1T4, 1S5, 1R5, 1S4, 354, 3V4, 7/6 ea., or 4 for 27/6. Most of the 1.4 v. B7G range available at 8/6 ea.

**HEADPHONES.**—Low resistance type CLR No. 3, 9/6. DLR No. 2, 13/6. High resistance CHR Mar. 2, 17/6, and the most sensitive of all DHR, No. 5B, 18/6 per pair. P. & P. 1/- pair.

**V.H.F. FANS.**—Air Space Co-axial Cable, 150 ohm, good to 600 Mc/s; normal price, 3/11 per foot. Our Price, 20 yard coil, £1. Very limited quantity available.

**FISK SOLARISCOPEs.**—Complete with charts. Give World time, light and darkness paths. Invaluable to the DX man. List 21/-, our price 7/6, post free.

**PANL Home Crackle.**—Black, Brown or Green, 3/- tin. P. & P. 8d.

**CONDENSERS.**—3uF, 600 v. (Trop), 750 v. (Normal). New Ex-W.D. Stock, 5/6 ea., p. & p., 1/6.

**SPECIAL OFFER. DEAF AID CRYSTAL MIKE INSERTS.** 10/- ea., or 2 for 17/6.

**UNREPEATABLE VALVE OFFER**

Genuine American 807's, 6/- ea. or 4 for £1. Photo-multipliers. Type 931A, 35/- ea. or 2 for £3.

Postage free on all orders over £1 except where specifically stated. PLEASE PRINT YOUR NAME AND ADDRESS.

**C. H. YOUNG, G2AK**

All callers Mail Orders to Dept. "P"  
110, Dale End, 102, Holloway Head,  
Birmingham 4 (CEN 1635) Birmingham 1 (MID 3254)

against projections on a crank. The crank is thus turned until both projections bear against the lever, when further movement is impossible.

A rigid construction is necessary. The cranks can be made from some type of shaft-coupler or by soldering metal strips to bushes with  $\frac{1}{4}$  in. hole and set-screw. If manual tuning is used, it must present no appreciable resistance. A fairly large control knob, fitted directly to the spindle, can be used in most long and medium wave sets. Where a reduction drive is essential, means must be available for putting it out of action when the push-buttons are used. A clutch can be used for this, or a jockey pulley used to keep the driving cord tight, and moved to slacken the drive when required. A further button, for manual tuning, may be arranged to return tension upon the cord, when depressed.

To adjust, the desired station is tuned in and the related crank turned upon the spindle by depressing the button. The crank is then locked in place. Afterwards, the condenser will always return to this position when the button is depressed. All buttons spring out again after use.

If soundly made, this system is accurate and simple. It has the disadvantage that stations at the extreme ends of the wavebands cannot be selected, as the levers cannot then operate. This can be overcome, if necessary, by employing a spring-loaded 2 : 1 step-up gear between crank spindle and condenser. The rotation of the cranks will then be limited to 90 deg.

Fig. 3 illustrates a system which operates in exactly the same way, the levers riding in slots between discs. Each cam is turned until its flat face is presented to the lever, when the latter is pressed in. These rubbing surfaces should be smooth and true. All the discs and cams are loose upon the spindle and are locked up, with the flat surfaces of the cams in the required positions, by means of the locking nut. As with Fig. 2, it is only possible to obtain a limited amount of rotation. If full band coverage is essential a step-up gear is required on the gang condenser spindle.

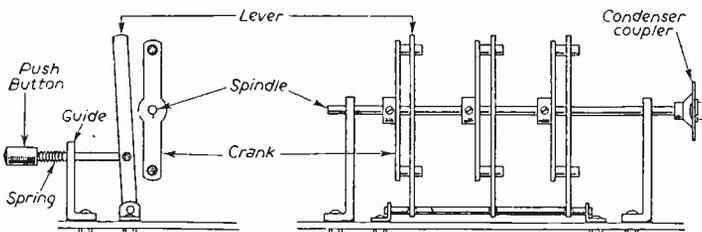


Fig. 2.—System operated by levers.

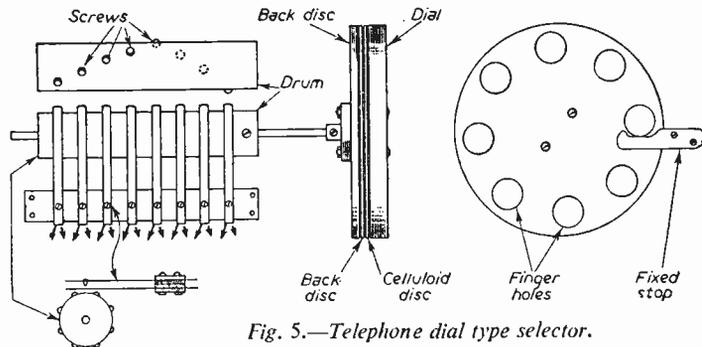


Fig. 5.—Telephone dial type selector.

**A Simple Indicator**

A method which has the advantage of great simplicity is shown in Fig. 4, and is usually provided for two or three stations only. Suitable windows, on the tuning dial or near it, have transparent coverings marked with the names of the most-used stations. For example, "Home," "Light" and "Third." Indicator lamps are fitted behind these windows, current being drawn from the transformer.

A small disc is provided on the condenser spindle for each lamp circuit, and is so positioned that the contacts are only closed by the small projection when the station is accurately tuned in. In use the ordinary tuning knob is rotated until the required window lights, which thus clearly shows the desired station to be tuned in.

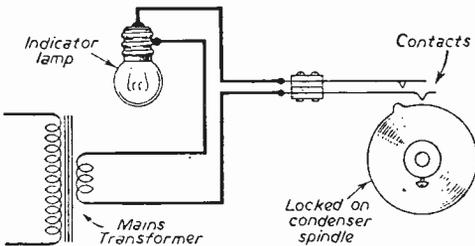


Fig. 4.—Tuning with a bulb indicator.

**"Telephone Dial" Systems**

These have the advantage of novelty and may be mechanical or electrical. One typical arrangement is shown in Fig. 5, making provision for up to eight stations. The station names are printed on the "station disc" which is protected by celluloid, the names showing through holes in the dialling disc. To choose a station the finger is inserted in the desired hole and the disc turned until the finger reaches the fixed stop.

A drum about 1 in. in diameter, with eight round-headed screws, is fitted to the axle. Any set of eight pairs of contacts will thus be closed, according to the station dialled. Closure of the contacts may operate the tuning condenser through a selector of the kind shown in Fig. 1 or may switch in pre-set condensers which are adjusted for the desired stations. No return or spring mechanism is required, as the dial may be turned clockwise indefinitely. In effect the dial acts as an eight-way push-button or automatic switch.

An alternative is to provide holes round one-half of the dial only and to fix the latter to the condenser spindle. This has the disadvantage that the holes will require to be unevenly spaced. In addition, the condenser setting

obtained by moving the finger round to the stop will only be sufficiently accurate for simple, local-distance sets of comparatively low selectivity. The only means to overcome this is to provide

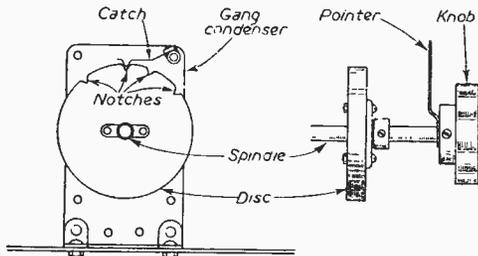


Fig. 6.—Catch selector for local station set.

a spring plunger in each hole. When dialling the plunger is pushed in with the finger and comes into contact with a fixed stop behind the dial. Accurate settings will thus be obtained. There is, however, the difficulty of returning the condenser to zero to

permit further clockwise dialling, which requires a spring and friction device to hold the condenser at the dialled position until the dial is again operated.

### Simple Catch Selector

This method is convenient for the simple type of T.R.F. or superhet where a definite tuning point is required for a number of stations at once. For such purposes it is extremely simple and handy.

As shown in Fig. 6, an ebonite or metal disc is fixed to the condenser spindle. No reduction drive is used, but a fairly large knob with pointer and scale. A strong spring catch, fixed to the gang condenser, bears on the disc.

The desired stations should be tuned in and the exact point where the catch bears is scribed on the disc. The station names are marked opposite the pointer. The disc then has small notches made in its circumference with a triangular file. The chosen stations are then found, easily and exactly, by turning the knob until the catch is felt to click into position. The notches should have sufficient depth to give a clear indication and any slight error can be corrected initially by filing a little one way or the other.

## News from the Clubs

### EAST GRINSTEAD AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: R. A. Burnett, 19, Stockwell Rd., East Grinstead, Sussex.

THE Club held its annual meeting on March 24th. The treasurer reported that the club, in spite of low membership (10 members) was in a very sound position financially.

At the time of writing the club had to share a hall with other clubs, and so restrict its activities, but in the near future it is hoped to have premises of its own.

The club transmitter is now under construction and should be on the air this year.

Although, as stated, the membership is low, the individual interests cover practically the whole range of electronics.

Morse classes are held once a week, and soon three more members hope to be licensed to share this branch of amateur radio with the present lone licensed operator, Mr. R. A. Lord (G3DSK), who is also the backbone of the club.

### TORBAY AMATEUR RADIO SOCIETY

Hon. Sec.: L. H. Webber, G3GDW, 43, Lime Tree Walk, Newton Abbot.

THE Annual General Meeting of the Society was held at the Y.M.C.A., Torquay, at 7.30 p.m. on Saturday, April 16th, under the Chairmanship of G2GK. The President, G5SY, was also present. The present officers and committee of the Society were all re-elected, with the addition of Les Mays, G2CWR, as Hon. Auditor.

The President, G5SY, spoke of the sound position of the Society, which he referred to as a "happy family" of a Society, and although small in numbers was fairly representative of the membership in the area. He also said that he had just built a new transmitter, after the style of the "Elizabethan," which works on all bands from 3.5 mc/s to 28 mc/s.

A hearty welcome was extended to Ron Brown, G3GMQ, from York, who is blind, and who will be in the district for about three months. He is doing a course at a local Blind Home. The Society was therefore in the unusual position of having two blind members present—the other being Geo. Western, BRS, No. 20605. A programme of lectures for the coming year is being prepared by G2GK and the Hon. Secretary.

### NEWARK AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: J. R. Clayton, 160, Wolsey Road, Newark, Notts.

MUCH interest was shown in the lecture by C. L. Wright, B.Sc., on "Transistor Circuitry." It was attended by amateurs from several towns.

In March the Society heard a talk by A. Hall on "Valve-voltmeters" and one by G. Bark (G3ITG) on "N.F.D.—Reflections and Suggestions."

The annual general meeting and dinner on Sunday, April 3rd, was well attended. Meetings are at Northgate House at 7 p.m. on the first Sunday of each month.

### SOUTHEAST AND DISTRICT RADIO SOCIETY

Hon. Sec.: J. H. Barrance, M.B.E. (G3BUJ), 49, Swanage Road, Southend-on-Sea, Essex.

MR. P. BALDWIN, gave a most interesting talk at a recent meeting in the Eko Canteen on "Electronic Musical Instruments." He pointed out that there were at least 12 different types of electric organs. The general principle is a controlled revolving disc, which can be caused to rotate at certain speeds in magnetic field, thus creating the required frequency which produces the desired note. Speeds must be constant in order to avoid distortion. One method of obtaining the correct speed is by the use of a system of pulleys.

### BARNESLEY AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: Mr. P. Carbutt, G2AFV, 33, Woodstock Road, Barnsley.

THE programme for June is as follows:

June 10th. A quiz.  
June 24th. A talk by P. Denison, G8OK, on "Fifty Years of Ham Radio."

The annual subscription for members is 7s. 6d. for adults and 2s. 6d. for juniors.

### SHEFFORD AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: G. R. Cobb, G3IXG, 7, Hitchin Road, Shefford, Beds.

THE Society, now in its seventh year, meets regularly on Friday evenings at 8 p.m. at Digswell House. New members and visitors are always welcome. The programme includes a general coverage of all radio and allied electronics. Film shows and junk sales are a regular feature and refreshments are available on the premises.

The Society receives the regular attention of G2DUS/T whose lectures are always well received. His latest demonstration was that of his TV monoscope. Other recent talks included "Wire Recording" by G3GDH, and "The Manufacture and Use of Quartz Crystals" by Mr. J. Johnson.

### ROMFORD AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: N. Miller, 55, Kingston Road, Romford.


A WORKSHOP for the use of club members is now available, and after participation in N.F.D. it is hoped to take part in the Two-Metre Field Day. Meetings are held at R.A.F.A. House, Carlton Road, Romford, every Tuesday, at 8.15 p.m., and all visitors will be welcomed.

### HAWICK RADIO SOCIETY

Hon. Sec.: G. Shankie, 17, Etrick Terrace, Hawick.

RECENT activities of the above have been lectures on "1 Valve Receivers" and "Adding the 2nd Valve." These lectures, given by Mr. Walter (President) in an effort to cater for the members (young and old) who are not yet too familiar with the working of a receiver.

**STERN'S AMAZING BARGAIN OFFER!!**

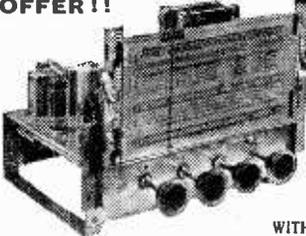

# Modernise your old Radiogram

WE HAVE BOUGHT THE ENTIRE STOCK OF THE FAMOUS MODEL B3 PP RADIO OR RADIOGRAM CHASSIS.

A 6 VALVE 3-WAVEBAND SUPERHET WITH PUSH-PULL OUTPUT

Thousands of these successful and very popular Receiver Chassis have been sold for £15.15.0 each.

WE CAN NOW OFFER THEM FOR **£11/19/6** (plus 7/6 carriage and Insurance).

H.P. Terms: Deposit £3.0.0 and 12 Monthly Payments of 17/5. These Receiver Chassis have proved to be about the most popular and successful yet offered. Designed to most modern specification, with great attention given to quality of reproduction, giving excellent clarity of speech and music on both Radio and Gram.

They are the ideal replacement chassis for that "Old Radiogram," etc. ALL CHASSIS ARE BRAND NEW AND GUARANTEED FOR 12 MONTHS (I.V.A. VALVES 90 DAYS).

## A BULK PURCHASE ENABLES US TO OFFER THIS "PUSH-PULL" 7-VALVE SUPERHET RECEIVER

for only £12.19.6. (Plus 7/6 carr. and ins.) H.P. Terms £3.0.0 Dep. 12 Months at 18/4. Model AW3-7 Receivers are made by a well known manufacturer and incorporate the latest Osram Valve line-up, having two Nibs in Push-Pull for approx. 7

watts output. They cover 3 wavebands and are for operation on A.C. mains. They make an excellent replacement radiogram chassis. THEY ARE BRAND NEW AND FULLY GUARANTEED.

THE CHASSIS ON THE LEFT AND THE RECORD PLAYER ON THE RIGHT WILL MAKE A REALLY FINE RADIOGRAM.




We have other NEW 3 SPEED Auto-Changers IN STOCK.


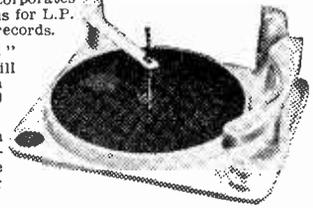
## A GENUINE SPECIAL OFFER!


This **THREE SPEED AUTOCHANGER** is by a famous manufacturer and is offered for **£9.19.6.** (Plus 7/6 carr. and ins.) Normal price £16.10.0. H.P. Terms £2.9.6. Dep. and 9 months at 19/-.

- Complete with High Fidelity Crystal "Turnover" Head which incorporates separate stylus for L.P. and 78 r.p.m. records.
- A "MIXER" Unit that will accommodate on 7in., 10in. and 12in. records.
- Brand New in Maker's Cartons, complete with mounting instructions.


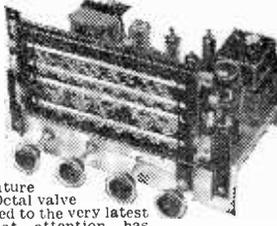
## The "SUPER-SIX." A DESIGN FOR HOME CONSTRUCTORS

A compact and highly efficient superhet Radiogram chassis of outstanding quality for operation on A.C. mains. YOU CAN BUILD IT FOR £10.7.6. This receiver can be made to incorporate the new B.V.A. miniature valve line-up or the Octal valve line-up, and is designed to the very latest specification. Great attention has been paid to the quality of the reproduction of both Radio reception and Record playing, and excellent clarity of speech and music is obtained. • Covers 3 wavebands. • Employs 6 valves having PUSH-PULL for 5-6 watts output. • A 4 position Tone Control operates on both Radio and Gram. THE INSTRUCTION & ASSEMBLY MANUAL is available for 2/-.



### Send S.A.E. for our illustrated and descriptive leaflet; it includes details of various KITS and ASSEMBLED MODELS as follows: AMPLIFIERS AND TONE CONTROL UNITS

- (a) WILLIAMSON, models G.W.18 and G.W.12, together with Tone Control Units, etc.
  - (b) LEAK model T.L.10, together with Pre-Amplifier Tone Control Unit.
  - (c) OSRAM "B12" AMPLIFIER available as an assembled amplifier.
  - (d) MULLARD AMPLIFIER, also available completely assembled.
  - (e) STERN'S PRE-AMP. TONE CONTROL UNIT. Can be used with any amplifier.
- STERN'S TELE-VIEWERS. 5 CHANNEL SUPERHET TV RECEIVERS. 12 in. Model can be completely built for £28.16.4 (plus cost of C.R.T.). "Wide-Angle" Model can be completely built for £33.0.0 (plus cost of C.R.T.). Complete set of Assembly Instructions are available for 5/- each, and include Practical Layouts, Wiring Data and Component Price List.

#### RADIO SETS

- (a) THE NEW ARMSTRONG F.C.48 CHASSIS . . . an 8 valve 4 waveband chassis having provision for the attachment of an F.M. UNIT
  - (b) 4 VALVE SUPERHET PORTABLE in small Attache Case . . . for Battery or Mains operation.
  - (c) 2 or 3 VALVE BATTERY PORTABLE all dry T.R.F. design.
  - (d) CAR RADIO. A superhet design for 6 or 12 volt supplies.
  - (e) 4 VALVE T.R.F. CHASSIS. Completely assembled for £6.9.6. Bakelite Case 16/6 extra if required.
  - (f) DENC0 F.M. Unit. Consisting of 5 Valve Superhet design incorporating R.F. and F/C Stages followed by two I.F.s and Ratio Discriminator.
- STERN'S MAINS UNIT KITS. Two types available: (a) For 69 volts and 1.4 volts 42/3; (b) For 90 volts and 1.4 volts 47/6.

## TWO COMPLETE Hi-Fi AMPLIFIER KITS

**A HIGH QUALITY 8-10 watt AMPLIFIER**  
The ideal Amplifier for General Home Use and for Small Halls, etc.



PRICE OF COMPLETE KIT, INCLUDING VALVES AND DRILLED CHASSIS £7.10.0. (Plus 2/6 carr. and ins.) WE WILL SUPPLY IT COMPLETELY BUILT FOR £9.10.0 (plus 5/- carr. and ins.) Designed for high quality reproduction up to an output level of 10 watts, having 6V6s in Push-Pull and incorporating negative feed-back. Suitable for use with all types of Pick-ups and most types of microphones and the output transformer provides for use of 3 and 15 ohm speakers. BRIEF FEATURES: • Valve line-up 6A5, 6SN7, 5Z4, with 6V6s in push-pull. • First-class reproduction of radio (where a tuning unit is used) and record playing. • Separate Bass Boost and Treble controls provide an excellent range of frequency control. THE ASSEMBLY MANUAL is available for 1/- and includes detailed layouts and component Price List.

## A 12-Watt "HIGH FIDELITY" Push-Pull AMPLIFIER

Comprising a Main Amplifier Chassis and a Remote Control Pre-Amplifier/Tone Control Unit. The remote control unit measures only 7in. x 4in. x 2in. and contains four controls, being: Bass-Treble, Volume and a Radio, Gram, Microphone Switch control. It incorporates its own feed-back circuit on the Bass Channel. Loop negative feed-back is employed on the Main Amplifier which has a valve line up of 6A5-6N7-5U4 with two 6X25s in push-pull and 6A5 and 6SN7 are used in the remote control unit. THE COMPLETE UNIT ASSEMBLED AND READY FOR USE £17.0.0. (Carr. and ins. 5/- extra.) H.P. Terms £4.5.0 Dep. 12 Months at £1.3.11. This Amplifier compares well with the Williamson and similar designs at a fraction of their cost. The complete set of assembly instructions are available for 2/-.



THE COMPLETE KIT IS AVAILABLE FOR £14.0.0. (Carr. and ins. 3/- extra.)

**STERN RADIO LTD. 109 & 115 FLEET ST., E.C.4.**

Telephone Central 58123/4

## TWO WONDERFUL BARGAINS

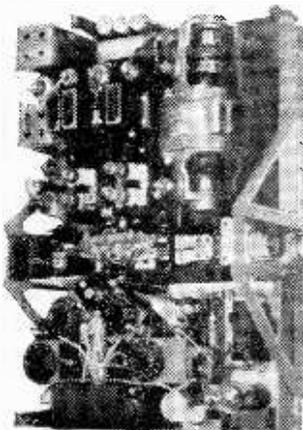


Photo is with covers removed



### ELECTRO-VOICE MOVING COIL MICROPHONES

**No. 600.C.**

With built-in matching transformer for direct connection to grid of amplifier valve. These mikes are ex the famous DC 610 Transmitter and give perfect speech quality. they are all brand new with 9ft. screen lead and 3-pin plug, packed in original carton.

**Price £2**

plus 1/6 postage and packing.

We are offering **AS NEW, COMPLETE TR.1196 RECEIVERS**, as illustrated. Outfit comprises, 6 Valve Superhet, 3 Valve Transmitter, Power Unit and Relay Unit. All complete on Chassis. Present range 4-8.5 mc/s and output 2 watts. Can be easily converted to cover 1.5 mc/s-7 mc/s and power output up to 8 watts. It has a most versatile Receiver which can be easily adapted to cover any band of frequencies from medium broadcast to 30 mc/s. The Transmitter range can also be easily extended and by simply adding 200 pF condenser to tank circuit will cover 1.5 mc/s. Circuit and conversion details included with each unit. Each outfit is despatched in transit case at the amazing low price of **£3**, plus carriage 10/-. If despatched without Transit Case. **£2/10/-**, plus 8/6 carriage.


**Large Quantities of Our Unused Component Bargains still available at Prices below Manufacturing Costs.**

Ceramic Variable Condensers split stator 15/15 Pf., 2/6 each. Ceramic Trimmers 22 Pf., 5/- per doz. Variable Condensers 100 Pf. ceramic insulation, 2/- each. Variable Condensers in screening case 50 Pf., 1/- each. Permaloid Steeving coils of approx. 1 gross yds. 1 mm. and 1.5 mm.. 8/6 per coil. Ferranti M/c. M/Amp Meters Boxed 0-150 Flush Square 2in., 7/6, 0.5 do., 9/- Wave Change Switches 2 wafer 6 pole 3-way standard 1 spindles, 1/3 each. Porcelain Stand-offs, insulators only, miniature 1in., 2/- doz. Pots 100 K and 1 meg. 1 spindle and 3-gang each 70 K, all at 1/- each. Hum-dinger Pots 100 ohm. miniature wire wound and Colvern do. 200 Ohms. 5 w., 2/- each. 100 K Miniature Pots 1in. long spindle, 1/- each. Erie Resistors 47 K 2 watt boxed in 50's & 5's. 2 watt 150 K 1 watt, 22 K 1 watt, 70 K 1 watt : price, 2 watt 3d., 1 watt 2d., 1 watt 1d.. Wire Wound Vitreous 10-watt wire ends 500  $\Omega$ , each, 9d. Add sufficient for postage.

**WOOLLEYS RADIO & ELECTRICAL SUPPLIES LTD.**  
**615 BORDESLEY GREEN, BIRMINGHAM, 9.** Phone: **VIC 2078.**
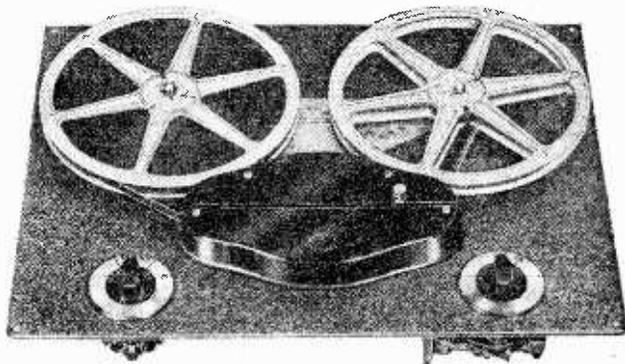
# New!

A QUALITY  
 TAPE DECK  
 for only **18 gns**



#### BRIEF SPECIFICATION:

- Heavy Duralumin Baseplate 15" x 11½"
- Three independent motors
- Three speeds: 3¾, 7½ and 15 i.p.s.
- Twin-track recording, 7" reels (1,200 ft.)
- Foolproof "drop in" tape loading
- Simple two-knob control
- Positive mechanical braking
- Interlocked switching
- Visual playing time indication
- Fast forward or reverse in 45 seconds
- Plays all makes of pre-recorded Tapes
- Azimuth adjustment to Record/Playback Head

# Brenell

**BRENELL RECORDING AMPLIFIER ALSO AVAILABLE 16½ GNS.**  
 From your Wireless Dealer or in case of difficulty write to sole manufacturers:  
**BRENELL ENGINEERING CO. LTD., 2 NORTHINGTON ST. LONDON, W.C.1**

# A Three-channel Mixer Fader Unit

A UNIT FOR THE AMATEUR WHO WISHES TO WORK WITH MORE THAN ONE INPUT AT A TIME

By H. W. Jeffries

THE unit described in this article was developed for use in the sound effects department of a local amateur dramatics society. Very few readers will be interested in this branch of reproduction, but as the unit is virtually a Three-channel Mixer Fader, some of the circuiting may prove useful to those wishing to work with more than one input at a time.

### Facilities

A three-channel input was decided upon, as this met the writer's requirements, but, as will be seen, the circuit is readily adaptable to control two or four channels. Facilities include one high-gain channel (Channel I) and two medium-gain channels (Channels II and III), each with separate switching and input level controls. Control of levels of Channels II and III together, and all channels at once is included. Monitoring of all channels is provided for, using headphones.

A block schematic layout (Fig. 1) shows the various stages. It may appear that not all the stages are really needed, but in practice all channel input levels are independent; insertion of monitor 'phones has no effect on output level, and inputs from crystal or carbon microphones, radio feeder or gramophone are catered for at the same time.


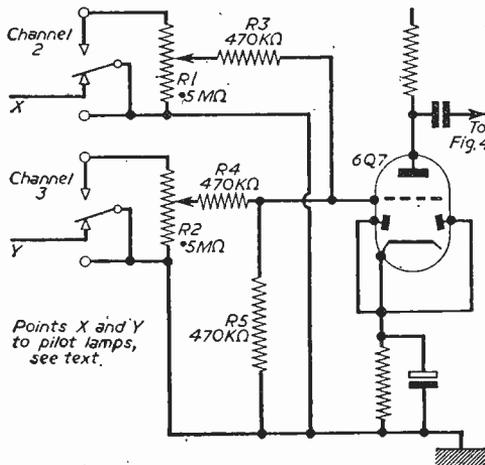


Fig. 2.—The inputs of Channels II and III.

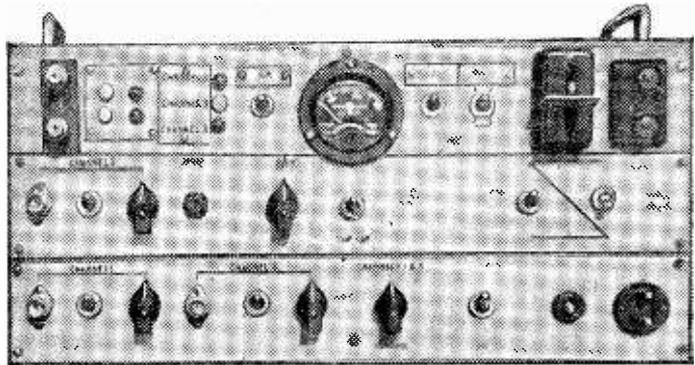

This illustration shows the unit in use by the writer. The engraving is done on Perspex. Terminals at the top left-hand corner are for "prompt" purposes when the unit is used for stage work. Top right, are the speaker-terminals and H.T. fuses, below these output-matching switches. Bottom right, are the mains input and mains fuse.

### Amplifier

The amplifier proper is quite conventional and has a push-pull output, using 6V6's working in class AB1, giving an output of some 12 watts audio. Pure quality enthusiasts may decry this form of output, but it is found that in a small cinema sufficient volume of quite good quality is delivered.

### Circuitry

The inputs of Channels II and III (Fig. 2) are mixed by a potentiometer circuit. Leads were kept short, the casings of potentiometers R1 and R2 were joined to the chassis and resistors R3, R4 and R5 were mounted immediately under the valveholder.

Stability and smoothing of H.T. supply received attention (Fig. 3) in an effort to keep hum level at a

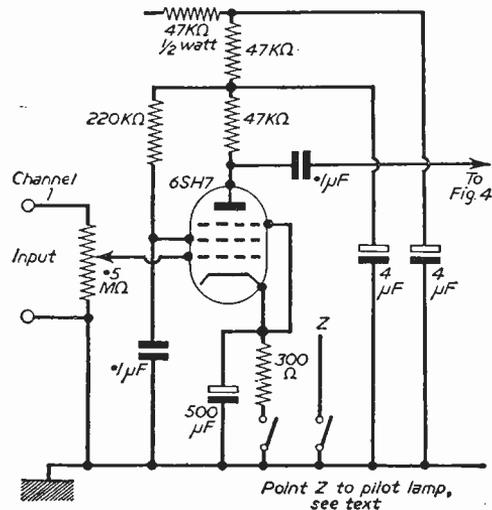


Fig. 3.—Channel I input.






# BUILD THIS HIGH QUALITY LOW COST AMPLIFIER

★ Circuit designed by Mullard research engineers.

★ Specified components available from most radio dealers.



Here's an entirely new amplifier circuit which brings high quality sound reproduction within the reach of thousands more enthusiasts. It has been designed by Mullard research engineers with special regard for easy construction and low cost. Full details of the circuit are included in the 2/6 book which is obtainable from radio dealers or direct from Mullard Ltd. Valve Sales Department — 2/10 post free. Get your copy now.

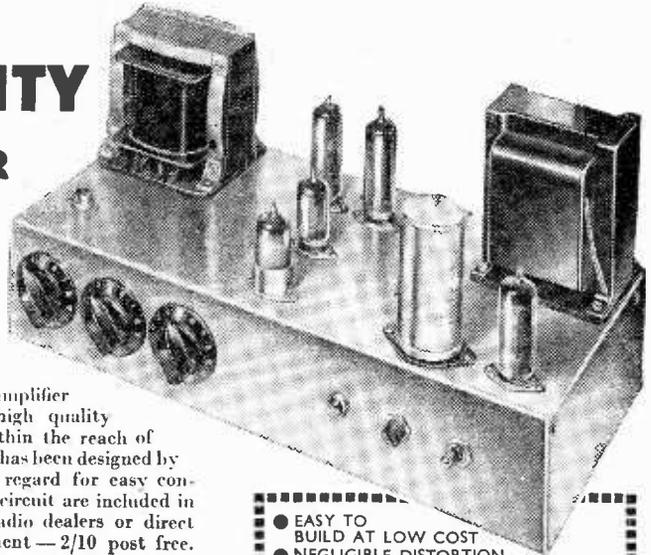

- EASY TO BUILD AT LOW COST
- NEGLIGIBLE DISTORTION AT ALL OUTPUT LEVELS
- UNIFORM FREQUENCY RESPONSE IN AUDIBLE RANGE
- GOOD TRANSIENT RESPONSE
- LOW OUTPUT RESISTANCE
- LOW HUM AND NOISE
- DESIGNED ROUND 5 MULLARD MASTER VALVES — EF86, ECC83, 2 x EL84, GZ30 or EZ80



MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2

## LASKY'S RADIO

*Don't miss these Special Summer Bargains*

**SAVE POUNDS ON THIS FINE 6-valve RADIOGRAM CHASSIS**

Famous Maker's Surplus. Brand New and Complete. 6 valve, 3-wave Superhet. 13-50 m. short, 200-550 m. medium, 1,000-2,000 m. long. Brand new Mullard valves: ECH42, EF41, L63, EB41, 6V6 g.t., EZ40, and finest quality components. Gram. switch, 465 Kc/s I.F., tone control, 3-colour dial. Overall size: 13 1/2 x 5, height 12 1/2 in. Aperture required for dial and controls, 11 x 9 1/2 in. Complete with valve, output trans., knobs, etc.

**LASKY'S PRICE, £10.19.6**  
Carr. & Pkg. 7/6 extra.

**SPECIAL OFFER • DRILLED CHASSIS & DIAL ASSEMBLY**

Chassis, 13 1/2 x 7 x 2 1/2 in., drilled for five latest type miniature valves, mains trans., I.F., etc. Dial, 13 x 4 1/2 in., for horizontal or vertical mounting. Spin wheel tuning. All pulleys and spindle supplied.

**LASKY'S PRICE, 19/6**  
Post 3/-.

**SPECIAL OFFER !  
MULTI-TEST METERS**

1,000 ohms per volt. Basic movement, 400 micro-amp., 3in. AC/DC 0-5,000 v. 0-1 amp. 11 switched ranges: 100,000 ohms and 1 meg., also decibel range. In polished wood carrying case (6 x 6 1/2 x 4 1/2 in. closed), with leather handle and space for test leads.

**LASKY'S PRICE 95/-** Post & Ins., 3/6.  
BATTERY 6d. extra. TEST LEADS, 3/6 extra.

**FOR PERSONAL PORTABLE CONSTRUCTORS**

<p><b>SETS OF 4 VALVES</b></p> <p>Set 1. One R5, T4, S5 and 38A. Price 27/6. Post 1/6.</p> <p>Set 2. One DK96, DF96, DAF96, DL96. Price 39/6. Post 1/6.</p> <p><b>CONDENSERS.</b>—1,000 etc.....Each, 7d.</p> <p>25 mfd., 25 volts.....1/6</p> <p>8 mfd., 150 volts.....1/-</p> <p style="text-align: center;">Post extra.</p> <p><b>TUNED CONDENSERS.</b>—(0005 mfd.)</p> <p>2-gang, with trimmers, 7/6</p> <p>2-gang, less trimmers, 6/6</p> <p>3-gang, less trimmers, 10/6</p> <p style="text-align: center;">Post extra.</p>	<p><b>3-in. P.M. SPEAKERS, 12/6.</b></p> <p><b>OUTPUT TRANSFORMERS, 3/6.</b></p> <p><b>TELETRON FERRITE ROD AERIALS</b></p> <p>Med. wave, 5in. long, 8/6.</p> <p>Dual wave, 3in. long, 12/6.</p> <p style="text-align: center;">Post extra.</p> <p><b>OSC. COILS.</b>—Iron dust cores.</p> <p>Medium wave, HO2, 3/-.</p> <p>Long wave, HO1, 3/-.</p> <p style="text-align: center;">Post extra.</p> <p><b>MINIATURE BATTERIES</b></p> <p>All types in stock.</p>
--	--

**F. M. COMPONENTS**

Full range available from stock. Write for List.

PLEASE ADDRESS ALL MAIL ORDERS TO HARROW ROAD

Open all day SAT. Half day Thurs.

**LASKY'S (HARROW ROAD) LTD.,**  
370, HARROW ROAD, PADDINGTON, W.9.  
Telephone: CUNningham 1979-7314.

**42, TOTENHAM COURT ROAD, W.1.**  
Telephone: MUSEum 2865.


# Modifying the R1132A

## COIL DETAILS AND A POWER PACK

**F**OLLOWING publication of details for this conversion in the March issue, we have received a number of queries concerning the new coil data. Above will be seen a sketch of the coils which are required, in which from A to B is two complete turns, with a  $\frac{1}{8}$  in. addition at each end for insertion into the soil sockets, where they are soldered. This covers all the coils.

I have since modified the receiver to include a power pack, details of which are now given. As will be seen from Figs. 1 and 3, T1 is mounted on top of chassis, to the rear. V1 (5Z4) is mounted centrally between T1 and the voltage stabiliser. In Fig. 3 the choke CH can be seen mounted on the rear drop of chassis, directly under the mains transformer. Smoothing condensers C1 and C2 are mounted on the front drop of the chassis, directly under the 5Z4 and stabiliser. Also in Fig. 3 the mounting positions of F1, F2, SW1, SW2 can be seen, which are on the front panel proper. SW1, SW2 are the

Bulgin types which are mounted sideways owing to lack of space. Fig. 2 shows the arrangement of F1, F2, SW1, SW2. Rubber grommets are used where leads pass through chassis. H.T. + is connected to H.T. + side of output transformer, and HT - connected to the nearest earthing tag. 6.3v. is connected to the nearest valveholder. This modification was carried out in four hours. All holes can be drilled without dismantling anything. A series of holes will need to be drilled in the case for ventilation. An aluminium screen is fitted between T1 and the

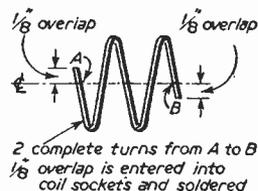

Coil Details.

### LIST OF COMPONENTS

- T1—350-0-350, 150 mA, 5 v. 2 a., 6.3 v. 4 a.
- CH—150 mA, 500 $\Omega$ .
- C1 } 16+16 $\mu$ F, 500 v.
- C2 } wkg.
- V1—5Z4G.
- SW1—D.P.S.T. } Bulgin
- SW2—S.P.S.T. } Type
- F1 } Panel Type Holders.
- F2 }
- F1—1 amp.
- F2—250 mA.

rectifier, bolted to the chassis to help dissipate away the heat generated by the 5Z4, as this is considerable. The 6J5 output valve could be left in place by the reader who does not need the increased output, as this valve loads a 5 in. speaker satisfactorily. An 11 K 10 watt resistor in the H.T. + would lower the H.T. volts to a suitable value. The bias resistor and condenser in this case should be left unmodified. The approximate frequency of this modified version is 85 mc/s to 123 mc/s.—L. H. Cox.

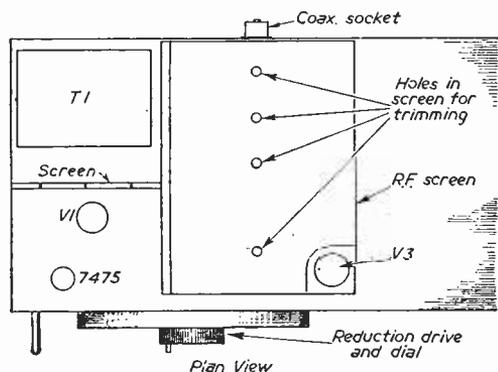


Fig. 1.—Top chassis lay-out.

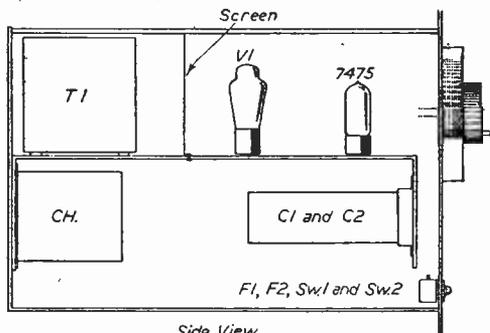


Fig. 3.—Side view of chassis.

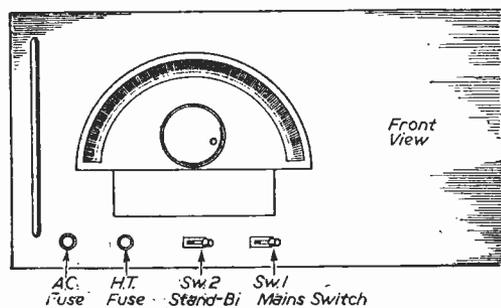


Fig. 2.—Front panel view.

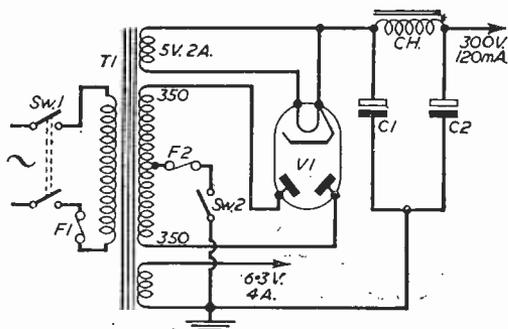


Fig. 4.—Theoretical circuit.

# A Case of Modulation Hum

By J. H. H.


READERS engaged in radio servicing may be interested in the following account of a case of modulation hum.

A customer living within 40 miles or so of the Daventry transmitter installed a good amplifier for record reproduction and to this he added a two-band tuner. After this addition he complained of a hum on the Home programme, moderate hum on the Third and reported no trouble on the long-wave Light. Everything pointed to modulation hum, for the tuner took its power from the main amplifier and this, by itself, was dead quiet.

Accordingly a deputy with suitable condensers was sent off with instructions to wire the condensers across the rectifier. He was gone for some considerable time and on his return reported that, though he had tried all the variants shown in Fig. 1, the result was merely to transfer the hum, now marked, to the long-wave band. As this could hardly be regarded as a piece of successful servicing, further condensers were provided, the instruction this time being to connect them in any of the ways shown in Fig. 2. The method shown at (b) was later reported as giving the best results, but the capacitance had to be over 1  $\mu$ F for a worthwhile reduction of hum, and the on/off switch then gave trouble through arcing.

The cure had by now become a matter of prestige and was accordingly placed in the hands of an experienced man. For a proper understanding of what he found Fig. 3 is needed. The shaded areas are internal brick walls, the thick line indicates 7/0.29 T.R.S. cable run under the floor and not in conduit, while the dotted line shows the run of the aerial. R1 and R2 are 2 kWh heaters.

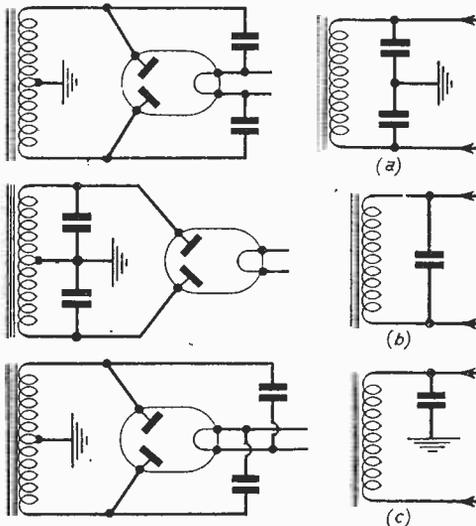The expected hum was found on the long waveband



Figs. 1 & 2.—By-pass connections for the transformer secondary. The connections tried on the primary.

when the set was switched on. An investigation of aerial and earth sockets showed them to be in order, so the lighting switches were operated in an effort to find the source of the induction. The only result was the usual slight click until R1 was switched on, when the hum vanished completely and reappeared again when R1 was switched off. The fittings, connections and insulation of the heater and the outlet were in order and the switch was properly wired in the live lead. The earth wire was also effective, but when the plug from R1 was removed operation of the switch had no effect on the hum.

The course of the supply cable was traced and this revealed the presence of the second heater R2 also in proper order and also effective in removing hum when switched on. Capacitors were therefore tried across various parts of the circuit with the final result that a value of 0.02  $\mu$ F directly across the switch gave an adequate reduction of hum.

This seemed at variance with the fact that the earth pin of each plug was effective, until tests showed a difference of nearly nine volts between the local and the mains earth. This might indicate the presence of sufficient impedance at R.F., particularly as the cable length was very nearly that of the seventh harmonic of the transmitter. The condenser was accordingly moved to the junction box end of the cable and proved equally effective when wired to the phase lead and the local earth. This is a much better arrangement because there can be no possibility of even a slight shock when the switch is in the off position.

A final look round the system showed that the amplifier was earthed via the conduit to the mains earth so most of the hum must have been induced from the aerial. This seemed to indicate that most of the R.F. was being conveyed by the phase lead so that when this was effectively earthed by switching on R1 or R2 the induction ceased.

That completed the job. No hum remained on either band and there was a barely noticeable drop in signal strength that was more than compensated by the lack of hum. But why the hum was transferred from one band to the other in the first place we simply do not know!

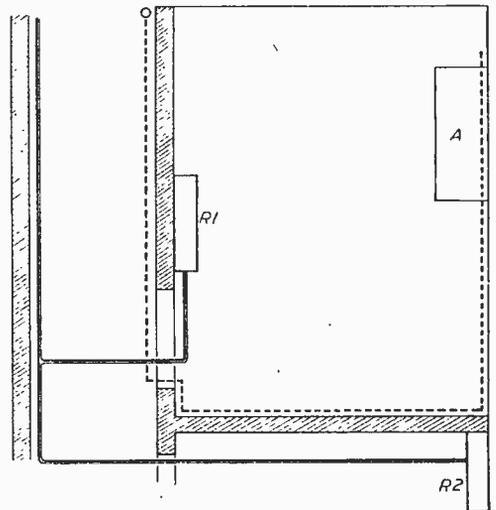



Fig. 3.—The layout of cables, heaters and amplifier and the run of the aerial.



**COST UNDER £4 MINI MAINS**

Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet, valves, in fact, everything, £3/19/6 plus 2/- post. Constructional data free with the parts, or available separately 1/6.

**SUPERSCOPE**

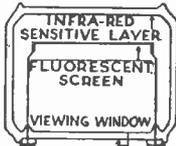

Famous wartime "cats eye" for seeing in the dark. This is an infra-red cell with a screen which lights up (like a cathode ray tube) when the electrons strike it. It follows that as light is rich in infra-red these cells will work as photo cell for burglar alarms, counting circuits. Price 5/- each. Data will be supplied with cells if requested.

**COMMUNICATIONS RECEIVER RI155 YOURS FOR 30/-**



The Ri155 is considered to be one of the finest communication receivers available to-day. Its frequency range is 75 kc/s to 18 Mc/s. It is complete with 10 valves and is fitted in a black metal case. Made for the R.A.F. so obviously a robust receiver which will give years of service. Completely overhauled and guaranteed in perfect working order. Price £3/19/6, or will be sent on receipt of deposit of 30/-. Balance by 12 monthly payments of 16/3. Carriage and Transit Case 15/- extra. Mains Power Pack, £5/10/-.



**CHASSIS ASSEMBLY**

3 colour, 3 waveband scale covering standard Long, Medium and Short wavebands, scale pan, chassis punched for standard 5 valve superhet, pulley driving head, springs, etc., to suit. Scale size 1 1/2 in. x 3 1/2 in. Chassis size, 15 in. x 5 in. x 2 in. deep. Price 15/-, plus 1/6 post.

**BAND III**

**A SIGNAL AND BAR PATTERN GENERATOR, COMPLETE WITH CALIBRATION EQUIPMENT 25/- POST FREE**

With the inception of Band III the home constructor is working on new ground and accurate checking instruments are a MUST. THE "ELFPREQ" Band III SIGNAL GENERATOR is the very efficient and inexpensive answer. It—

1. Will provide the signal for tuning to any Band III station.
  2. Can be used as a grid-dip meter for checking the frequency of Band III T.V. aerials. Coils, etc.
  3. Can be made to give a pattern on T.V. Receiver screen.
  4. Can be accurately calibrated with included equipment.
- All the parts including valves, tuning condenser and metal chassis are available as a Kit at 25/- post free. Constructional data free with Kit or available separately price 2/6.

**RECORD PLAYER BARGAINS**



3-speed record player with pick-up using the famous Acos "Hi G" turnover crystal—motor also by very famous maker—speed selection is by Bakelite knob. All on unit board ready for installation. A wonderful bargain at £6/10/- plus 5/- carriage. Hire Purchase 15/- deposit.

**LATEST MODEL AUTO CHANGER**

Turnover pick-up—3 speed—mixes 7 in., 10 in. or 12 in. records—Price £9/19/6, or £3 deposit and 5 monthly payments of £1.10.0.

**THE BENDIX RA-1 B COMMUNICATIONS RECEIVER**



American Forces receiver for C.W. or T.R. uses probably the finest band spreading arrangement possible, and covers:—

Band 1	15 to	.315 mc/s	} i.e., 20 to 200 metres
Band 2	.315 to	.680 mc/s	
Band 3	.680 to	1.5 mc/s	
Band 4	1.8 to	3.7 mc/s	
Band 5	3.7 to	7.5 mc/s	
Band 6	7.5 to	15.0 mc/s	

The Sensitivity is 4 micro volts for full output. Uses 8 valves and operates from batteries (12 or 24 volt) or from a mains power pack. It has a built in output stage. Controls are all brought to the front panel. These sets are brand new and in perfect working order, £14/10/0 each, or 45/- deposit, balance over 12 months—carriage and insurance 10/- Circuit diagram and component data free with sets, or available separately price 2/6 post free.

**POWER PACK** for mains working £3/10/0 or £17/10/0 both items.

**STOP PRESS**

**BAND III CONVERTER KIT**

suitable for any type of T.V. £3/10/0 complete. Instructional data available separately for 2/6 post free.

**FINE MODERN RADIO THE CLEVELAND ORGANTONE**




5 valve 3 waveband superhet covering Long, Medium and Short waves. Osram miniature valves—low loss iron coils—permeability—tuned I.F.S.—full A.V.C.—variable negative feedback—gram. position—4 watts output—particularly fine tone. Chassis size 12 in. x 7 in. x 7 in. approx. Tested in difficult areas where exceptional results have been obtained. Price £11/10/0 or £3.16/0 deposit. Carriage, etc., 7/6.

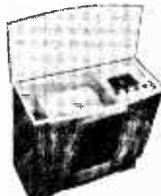**CABINETS FOR ALL**

We undoubtedly hold the largest stock of cabinets in the country. All are made of the finest plywood, veneered and polished and all radio and motor boards are left uncut to suit your own equipment. The top one



is The Bureau, walnut finished and highly polished, size approximately 30 in. high, 32 in. wide, and 16 in. deep. Price 16 guineas or 32/- deposit, carriage 12/6. The centre one is The Em-



press, our most popular cabinet, size 32 in. high 36 in. wide, and 16 in. deep, walnut finished, lined sycamore. Price 15 guineas, or H.P. deposit 32/-, carriage 12/6. The lower one is The Contemporary, size 29 in. high, 30 in. wide and 15 in. deep. Oak finished with contrasting mouldings. Price £8/15/-, H.P. deposit 19/-, carriage, 12/6.

**BATTERY 3-VALVER**

Good reception on both medium and long waves. All parts including three valves, resistors, tuning condensers, in fact, everything except loud-speaker, cabinet and chassis (available if you haven't something suitable) costs only 19/6; data available separately, price 1/6.



**19/6**


**SPEAKERS**

5 in. p.m. ...	19/6
6 in. p.m. ...	17/6
8 in. p.m. ...	19/6
10 in. p.m. ...	25/-
12 in. p.m. ...	35/-

**ELECTRONIC PRECISION EQUIPMENT, LTD.**

Post orders should be addressed to Dept. 7, RUISLIP.

42-46, Windmill Hill, Ruislip, Middx.	152-3, Fleet Street, E.C.4.	29, Stroud Green Rd., Finsbury Park, N.4.	249, Kilburn High Road, Kilburn, MAIda Vale 4921
Phone : RUISLIP 5780	Phone : CENTRAL 2833	Phone : ARCHWAY 1049	
Half day, Wednesday.	Half day, Saturday.	Half day, Thursday	

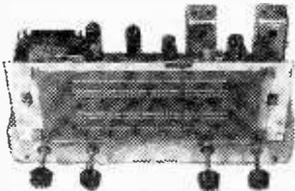

**ALL WAVE RADIOGRAM CHASSIS**

**THREE WAVEBANDS FIVE VALVES**  
 8.W. 16 m.—50 m. LATEST MULLARD  
 M.W. 200 m.—550 m. R.H.42, EP41, EBC41  
 L.W. 800 m.—2,000 m. EL41, E240.

12 month Guarantee, with 10in. P.M. Speaker.  
 A.C. 200/250 v. Switch. Short-Mid-Long-  
 (Grav. A.V.C. and Negative feedback. 4.2 watts.  
 Chassis 1 1/2 x 2 1/2 in. Glass Dial—10in. x 4 1/2 in.  
 Horizontal or vertical available. 2 Pilot Lamps.  
 Four Knobs. Walnut or Ivory, aligned and cali-  
 brated. (Chassis isolated from mains. PRICE £10 15 0.  
 Without 10in. Speaker, £9/15 0. Carr. & Ins. 4.0.

**CONDENSERS**—New stock. 500 mfd. 6 kV.  
 T.A.C.C. 5/6. Ditto, 12.5 kV. 9/6; 2 mfd. to 500 pf.  
 Micas. 6d. x .001, .01, .02, 500 v. 1 mfd. 550 v. 9d.  
 Hunts Moldseal 500 v. .005, .01, .02, .05 mfd.  
 and 1 mfd. 1-; 25 mfd. 1/6; 5 mfd. 500 v. 1/9.  
**SILVER MICA CONDENSERS**—100 v. 5 pf. to 500  
 pf. 1/-; 500 pf. to 3,000 pf. 1/3. DITTO 100 v.  
 1.5 pf. to 500 pf. 1/9; 510 pf. to 1,000 pf. 2/-.


**Tubular Electrolytics**—Can Type. Clips. 3d. ea.  
 4/50 v. Hunts 2-3 16/450 v. T.C.C. 3/6  
 8/450 v. B.E.C. 2-3 60/550 v. T.C.C. 8/6  
 16/500 v. Dubilier 4/- 8/- 16/450 v. B.E.C. 6/-  
 8/450 v. Dubilier 4/6 16/450 v. B.E.C. 5/6  
 16/16500 v. Dub. 6/- 16/450 v. T.C.C. 6/-  
 32/500 v. Dubilier 5/- 32/350 v. Dubilier 5/-  
 25/25 v. Hunts. 1/8 60/450 v. 11/6  
 50/50 v. Plessey 2/- 100/450 v. 12/6

**SPECIALS**—500 mfd. 12 v. 3/-, 1,500 mfd. 4 v. 4/6  
 1000/4500 mfd. 6 v. 6/-, 1 mfd. 1.5 kV. 3/6.  
**T.C.C. SCREW BASE TYPE 512**—8 mfd. 500 v. 3/-;  
 16 mfd. 500 v. 4/-.

**C.B.T. LOW LEAKAGE ISOLATION TRANS.** Ratio 1:  
 1.25, 25% boost, 2 v. 10/6; 4 v. 10/6; 6.3 v.  
 10/6; 10.8 v. 10/6; 15 v. 10/6.

**MAINS TYPE Multi Output**—2, 2 1/2, 2 1/2, 3 v.  
 2 amp., 17/6.

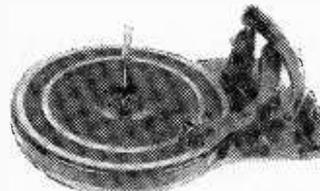**MAINS TYPE Multi Output**—2, 4, 6.3 v. 7.5 v.  
 10 v., 18 v., two tap boost output 25% or 50%, 21/6.



Brand new Plessey 3-speed Autochanger Mixer Unit  
 for 7, 10 and 12in. Records. Twin Hi-Fi Xtal Head  
 with Duopoint sapphire stylus. Plays 4,000 records.  
 Sprung mounting. Baseboard required, 15in. x  
 12in. Height 5 1/2 in. Depth 5in. Superb Quality.  
 Bargain Price, 9/-, post free.  
**SIMILAR MODEL**—3 speed Single Record unit  
 with Acos 37 Turnover Head, each Sapphire Stylus  
 plays 2,000 records. Starting Switch Automatically  
 places Pick-up on records, 7in., 10in. or 12in. Auto  
 Stop. Baseplate 12in. x 9in. Height 2 1/2 in. Depth  
 1 1/2 in. Price £7 15/6, post free.

**TV. PRE-AMP.**—Channel 1, easily modified to  
 other channels or converter use. Midset chassis.  
 Grid x 3in. x 1 1/2 in. Complete with coax lead,  
 plug and EP42 valve. Brand new (boxed).  
 Listed £3/15/-. Special clearance, 21/-.

**WIRE-WOUND POTS. 3 WATT. FAMOUS MAKES**  
 Pre-Set Min. T.V. Type. Standard Size Pots, 2 1/2 in.  
 All values 25 ohms to 30 Spindle. 1001 ohms to  
 K. 3/- ea. 50 K, 4/- 50 K, 5/6; 100 K, 8/6.  
 Ditto Carbon Track 50K. W W EXT. SPEAKER  
 CONTROL 10/4 2/-.

**L.F. CHOKES**—15 H 60 ma, 5/-, 20H 120 ma, 11/6.  
 15 H. 160 ma, 12/6. H.F. Choke, 14 mH. 2/6.  
**HEATER TRANS.**—Tapped prim., 200, 250 v. 6.2 v.  
 11 amp., 7/6. Tapped sec. 2, 4, 6.3 v., 11 amp., 3/6.  
**MAINS TRANS.**—550/450, 30 ma., 6.3 v., 4 v., 4.4 v.,  
 3 v., 4 v., 2.5 v., ditto 550-0-250, 21/-, 3-way mounting.  
 No connection with any other firm. Please address  
 all correspondence correctly as below.

**Radio Component Specialists**  
 307, Whitehorse Road, West Croydon.  
 THO 1865  
 Post Gd. £1 orders post free. C.O.D. Vjo. Lists a.s.p.

**7/6 VALVE SALE 7/6**

New boxed. All guaranteed  
 1R5, 1R5, 1T4, 1R4, 3R4, 5V4, 6AM6, 6F12,  
 6BE6, 6BW6, 6K7M, 6K8, 6SA7, 6SL7, 6V6,  
 6X4, 6X5, 757, 81C, 12AX7, 607, E91,  
 EF92, EP91, EF92, EL92, HVR2A, PEN26,  
 U22, UP41. AT 8/6: 6U4, 6Z4, 6AK5, 6AT6,  
 6B9, 6L6, 6Q7, 6SN7, 80, EC42, Sylvania  
 EF50, MU14. AT 10/6: EC150, EF80, EL41.

**Volume Controls** 80 ohm **COAX**  
 CABLE  
 Semi-air spaced Poly-  
 ethene insulated. 1in. diam.  
 Stranded core. 1in. diam.  
 Losses cut 50%.  
**STANDARD** 9d. yd.  
**COAX** 8d. yd.

**COAX PLUGS** ... 1/2 DOUBLE SOCKET 1/2  
**SOCKETS** ... 1/- OUTLET BOXES ... 4.6  
**BALANCED TWIN FEEDER** per yd. 6d. } 80  
**TWIN SCREENED FEEDER** per yd. 1/- } ohms  
**50 OHM COAX CABLE**, 8d. per yd.  
**TRIMMERS**, Ceram. 30, 70 pf., 9d.; 100 pf.,  
 150 pf., 1/3; 250 pf., 1/6; 600 pf., 1/9.

**TYANA**—Midset Soldering Iron. 200-250 v. or  
 200-250 v., 14/11. Triple Three metal, with detach-  
 able bench stand. 19/8. Solder, Midset Iron, 19/8.  
**XTAL DIODE**—Sensitive G.E.C. type. 3/6. H.R.  
 Phones (S. G. Brown) or Hi-grade Amer., 15/6 pair.

**STOP PRESS**—B.S.B. MONARCH 8-SPEED  
**PIANO CHANGER**, ACOS XTAL HEADS—  
 Baseboard, 14in. x 12in. Height 5 1/2 in. Brand  
 New in Maker's Boxes. £9/19/6, post free.

**ALADDIN FORMERS** and core, 1in., 8d.; 1in., 10d.  
**KNOBBS GOLD ENGRAVED**—Walnut or Ivory  
 1 1/2 in. diam., 1/6 each. Not engraved, 1/- each.  
**SENTERCEL RECTIFIERS**—BHT Type. Ply-  
 back Voltage.—K3/25 2 kV., 4/3; K3/40, 3.2 kV., 6/-;  
 K3/45, 3.6 kV., 6/6; K3/50 4 kV., 7/3; K3/100 8 kV.,  
 12/8; K3/100 14 kV., 18/-. **MAINS TYPE**—RM4,  
 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3,  
 120 ma., 5/9; RM4, 250 v., 275 ma., 16/-.

**LOUDSPEAKERS P.M. 3 OHM**—5in., 16/6; 6in.,  
 17/6; 8in., 19/6; 10in., 25/-; 6in. with transf., 19/6.

**T.V. AERIALS**—All channels. Indoor Inv. T., 15/6.  
**CHARGER TRANS.** for 2, 6 or 12 v. 14 amp., 13/6;  
 4 amp., 21/-; Bridge rectifiers, 1 1/2 amp., 8/9;  
 4 amp., 17/6.

**RECORDING TAPE**. Exclusive Bargain, 1,200 ft.  
 reels High Coercitivity. Brand new, 17/6.

**SUPERIOR RADIO SUPPLIES**  
 (P.W./Jy) 37 HILLSIDE, STONEBRIDGE, LONDON, N.W.10. Tel.: ELGar 3644.

High Class Cabinets  
**SUPERIOR BUREAU**

An elegant cabinet in richly figured walnut veneer. Internal panels in polished sycamore. A drop front lid covers a sloping, uncut control panel (14in. long x 10 1/2 in. high) along side which is an uncut baseboard (17 1/2 in. long x 13 1/2 in. back to front). The inside of the drop front lid is panelled in beige leatherette. In the lower part of the cabinet are two large storage cupboards (13 1/2 in. high, 7 1/2 in. wide, 16 1/2 in. deep). The lid and cupboard handles are in chased Florentine bronze. Overall dimensions (33in. high, 41in. long, 16 1/2 in. deep). Price £17.0.0. plus 15/- carr. Send for Cabinet Leaflet.

The Home Constructors  
**BATTERY PORTABLE!**  
 The  
**SUPEREX**  
 55 ATTACHE  
 Building Cost £7.15.0, plus 3.6 P.P.

- Outstanding Quality.
- 7in. x 4in. Elliptical Speaker.
- First Class Reception.
- 4 Valve Battery Superhet.
- Long and Medium Waves.
- Cabinet 10 1/2 in. x 8 1/2 in. x 5 1/2 in.

Send 1/6 for "Superex 55" Construction Booklet.

**IDEAL FOR TAPE RECORDERS**  
**S.R. BUREAU**

A fine multi-purpose cabinet, finished in well figured walnut veneer and built to the highest standards of workmanship. A blank motor-board size (16in. long x 15in. deep) and radio panel size (16in. long x 11in. high) is revealed when the front is pulled down. Two large storage cupboards are located one on each side of the cabinet. Size of these compartments is 12in. wide x 15in. deep. Overall outside dimensions of the cabinet are 36in. long x 33in. high x 17in. deep. Available prepared Unpolished or Polished.

Price £16.10.0 Polished. £13.10.0 Unpolished.

Plus 15/- carr. Send for Cabinet Leaflet.

**TERMS:** Cash with order or C.O.D. Extra charge for C.O.D. U.K. and N. Ireland only.  
**PERSONAL SHOPPERS WELCOME** Shop open 9 a.m. to 6 p.m. Monday to Saturday. 1 p.m. Thursday.

# A Dial Modification

A SIMPLE ADAPTATION TO ENABLE A DIAL SETTING TO BE ASCERTAINED BY TOUCH

By W. Nimmons

**T**HIS dial modification was the result of expediency. It was found, when I was laid up by illness, that a certain amount of difficulty was experienced in selecting the Home, Light and Third Programmes by touch. That is, one never knew what part of the dial the pointer was at in the darkness of the bedroom. To add to my difficulties, the receiver was placed on a small table behind my head. I determined, therefore, as soon as I was up and about again I would see what could be done to circumvent the difficulty.

The result is eminently satisfactory, and should be of particular use to blind persons, since one can tell by feel what part of the dial the pointer is at.

I should mention that the scheme is applicable to those receivers which have a celluloid or glass front on the dial. It is nothing more or less than an extension of the pointer to the outside of the celluloid or glass, so that one can tell by the touch just where it is located. Stops or pointers can be placed at the main stations.

The first thing to do, if the dial has a celluloid front, is to cut a slit right along its length, or at least as far as the pointer travels. Examine the escutcheon to see if it can be taken off, exposing the loose celluloid. It may be necessary to remove the chassis. If the celluloid can be taken right out and laid on the workbench it is a simple matter to cut the slit; otherwise it will have to be cut in situ. With a sharp pointed knife make two scores  $\frac{1}{16}$  in. apart in the direction of travel of the pointer, for the requisite distance. Continue scoring until the material is cut through.

When the front is of glass it will be necessary to divide the glass into two separate parts; these can then be spaced  $\frac{1}{16}$  in. apart to give the slit. There is usually sufficient play in the holder for this to be done. If the glass is engraved with station names, etc., choose a part which gives the least dislocation when cutting the glass lengthways.

If it is found that the glass is no longer secure in its holder, strips of cardboard glued at the extreme ends (still preserving the slit) will make all secure. Tighten the screws holding it in place so that it will not rattle.

## Pointer Extension

Next it will be necessary to fit the small extension to the pointer which will carry it out beyond the glass. Most pointers are of metal, painted black, so they should be easy to solder; but if you should strike one made of a material other than metal it will have to be glued. The length of this extension cannot be given; some

pointers are just behind the glass while others are a quarter or even half an inch behind it. It may happen that an extension  $\frac{3}{4}$  in. long may be clear of the glass on the outside; it should project at least  $\frac{1}{4}$  in.

The extension itself may be made of brass rod of about 2 B.A. thickness, with a slot cut in each end. The slot in one end is to fit over the pointer for soldering, while the slot in the other end is for an indicator on the outside of the glass, which will be mentioned later.

Scrape or sandpaper the paint off the pointer at a spot exactly opposite the slit in the glass and tin the metal, then solder the end of the extension to this point. This should, of course, be done with the chassis out of the cabinet. The slot at the pointer end of the extension, by the way, should be at right angles to the slot at the other end, for reasons which will be explained later. When the extension is soldered to the vertical pointer the chassis should be returned to the cabinet, making sure that the extension is projecting through the slit in the glass or celluloid.

Now that we have some indication which, by tactile methods tells us where the pointer is set, the rest belongs to the domain of refinements. We can attach an elongated indicator extending to top or bottom of the dial, and place stops or small excrescences out of the area of its travel, either fastened to the escutcheon or simply stuck on the glass. These will doubtless be determined by the nature of the material on hand, but a practical solution is depicted in Fig. 1. By this it can be seen that the indicator (not to be confused with the original pointer incorporated in the receiver) is in close proximity to one of the three cone-shaped stops which indicate the positions of the Home, Light and Third Programmes respectively. These can be fashioned from wood, bakelite or similar light material and simply stuck in place. The tuning knob, is of course operated to tune in the desired station in the usual way.

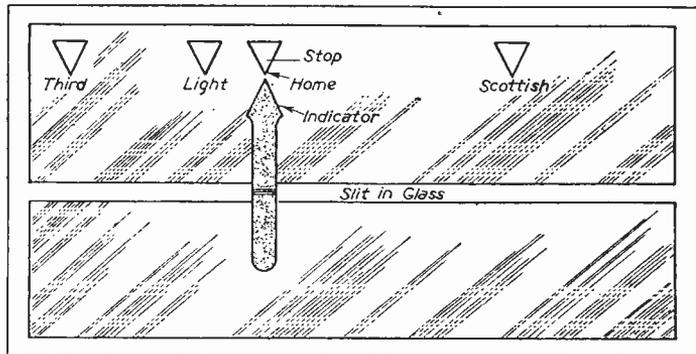


Fig. 1.—The finished modification. Here the indicator is pointing to the Home Service.

The method of fastening the elongated indicator to the 2 B.A. rod previously mentioned should be one that puts no unwanted strain on the cord which carries the pointer of the receiver. This can be done easily enough by soldering it on, but a better way is illustrated by Fig. 2.

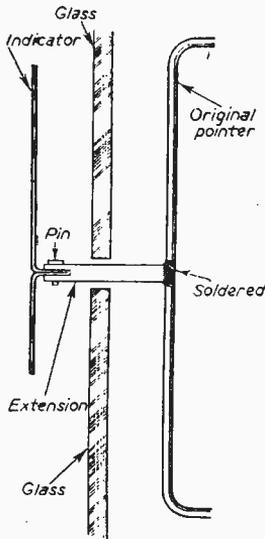


Fig. 2.—Extension Details.

### Indicator

The indicator in this case consists of thin metal strip, suitably shaped, and pinched in the vice or pliers to form a projection at right angles which can be accommodated in the slot cut in one end of the 2 B.A. rod. In this case the rod should have a small hole drilled at this end before cutting the slot. The projection on the indicator should also have a hole of the same diameter drilled through its double thickness. When inserted in the slot the indicator will probably be somewhat loose, but a pin which can be freely inserted (and as freely with-

drawn should the receiver need servicing!) can be inserted through the hole in the 2 B.A. rod. This pin can be made somewhat broader at the top end to prevent it falling out. The slot in which the indicator is accommodated is at right angles to the slot at the other end of the extension piece, for while the slot in the end which is soldered to the original pointer is vertical, the slot accommodating the indicator is horizontal.

Another way of attaching the indicator is by means of a metal collar and grub screw. But in view of the fact that the cord drives of the older receivers are notoriously very difficult to repair once they get out of order the above method, is preferred since the act of tightening the grub screw might upset things.

A further refinement would be the gluing of a small patch of felt or velvet to the underside of the indicator if it rubs against the glass in its travel; this will prevent rattling at loud volume or on certain notes of the piano.

It is not pretended that this dial modification will enable the blind and the sick to tell by a touch to which station the receiver is tuned, apart from the "recognised" stops. Nevertheless it is of some small help in these cases and an improvement over existing receivers.

*NOTE.—If it should happen that the original pointer is connected to chassis, suitable precautions should be taken to guard against shock from A.C./D.C. receivers. In this case the extension should be of insulating material, or the indicator be made of bakelite or similar stuff.*

## International Radio Controlled Models Society

THE International Radio Controlled Models Society has pleasure in announcing that its annual international contests for radio controlled models will be held this year in the north-east of England on Saturday, Sunday and Monday, July 30th, 31st and August 1st respectively.

Due to the large number of entries received last year, it has been decided to spread the contest for radio controlled boats over two days and these will be the 30th and 31st July. The contest will take place at Saltwell Park, Gateshead-on-Tyne, and will be split into three classes:

- Model boats with any form of power.
- Model yachts.
- I.C. or steam driven model boats—points being awarded for steering only with a bonus for speed.

The radio controlled model aircraft competition will be held at Croft aerodrome, nr. Darlington, on Monday, 1st August in conjunction with the S.M.A.E. Northern Gala and will be split into classes for power driven aircraft and gliders. In the power driven class, a separate prize will be offered this year for aircraft controlled through a single channel, i.e., not tuned reeds, audio or similar systems. This is planned to encourage those competitors who have not progressed to the more complex systems.

Entrance forms, copies of the rules and further information will be available shortly.

For any further particulars readers should contact the Hon. Contest Publicity Secretary, D. W. Aldridge, 1, Fowberry Crescent, Fenham, Newcastle-on-Tyne, 4.

## Technical Training Scheme

### First Students Ready for Radio Industry

THE first of the students who entered three-year technical training courses started in 1952 are now about to enter the radio industry.

The courses were organised by the Ministry of Education, following consideration of training problems by the Radio Industry Council's Technical Training Committee and the Radar Sub-committee of Lord Hankey's Technical Personnel Committee, at five London and provincial centres. These are the Bolton Technical College, Manchester Road, Bolton; the Coventry Technical College, The Butts, Coventry; and, in London, Northern Polytechnic, Holloway Road, N.7; Norwood Technical College, King's Hill, West Norwood, S.E.27, and E.M.I. Institutes, Ltd., Pembroke Square, W.2.

The object of the courses is to provide students so well trained in the theory and practice of electronics that they will be able, on completion, to take their places at once as assistants to qualified research and development engineers.


Entry age is between 16 and 18 normally (although older candidates will be considered). While the appropriate examinations of the City and Guilds of London Institute, the Institution of Electrical Engineers and the British Institution of Radio Engineers can be taken in the courses, the syllabuses are wide in their general scope in addition to giving specialised training in radio engineering and electronics.

In most cases successful completion of the course carries a diploma.

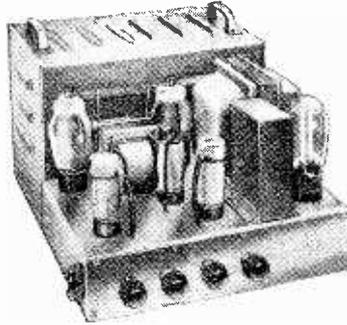**R.S.C. A4 HI-FIDELITY 25 WATT AMPLIFIER**

A new design for 1955. "Push-Pull" output. Built-in Tone Control Pre-amp. stages. Increased sensitivity. Even further improved performance figures. Includes 7 valves, specially designed sectionally wound output transformer, block paper reservoir condenser and reliable small condensers of current manufacture. TWO SEPARATE INPUTS CONTROLLED BY SEPARATE VOLUME CONTROLS allow simultaneous use of "Mike" and Gram., or Tape and Radio, etc. etc. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lit" and "Cut." Frequency response  $\pm 3$  db. 30-30,000 c/c. Six negative feedback loops. Hum level 66 db. down. ONLY 20 millivolts INPUT required for FULL OUTPUT. Certified harmonic distortion only 0.35% measured at 10 watts. Comparable with the very best designs.

ENTIRELY SUITABLE FOR SMALL HOMES OR LARGE HALLS, CLUBS, GARDEN PARTIES, DANCE HALLS, etc. etc. For ELECTRONIC ORGAN or GUITAR. For STANDARD or LONG-PLAYING RECORDS. FOR ANY "MIKE" or PICK-UP. H.P. TERMS ON ASSEMBLED UNITS. DEPOSIT 26/- and ten monthly payments 20/-.



Size approx. 12.9-7in. For A.C. mains 200-230-250v. 50 c/c. Outputs for 3- and 15-ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value at 9 1/4/-, or ready for use, 50/- extra. Carriage 10/- If required, cover as illustrated can be supplied for 17/6.

**9 GNS.**

**A PUSH-PULL 3-4 watt HIGH-GAIN AMP. PICK-UP 25/7/6.** For input 200-250 v. 50 c/c. Complete kit of parts including circuit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C.D.C. with "live" chassis, but A.C. only with 400-0-400 v. trans. (Output is for 2-3 ohm speaker.) Supplied ready for use for 25/- extra. Carr. 2/6. Descriptive leaflet, 7/6.

**PLESSEY 3-SPEED MIXER AUTO CHANGER.** Takes 7in., 10in. and 12in. records, standard or long playing. Crystal Pick-up with Duo-point sapphire stylus changed from standard to long playing position by simple switch movement. For A.C. mains 200-250 v. 50 c/c. Miter number. Brand New, cartoned, at only 10 gns., carr. 5/-.

**BATTERY SET CONVERTER KIT.** All parts for converting any type of Battery receiver to All Mains. A.C. 200-250 v. 50 c/c. Kit will supply fully smoothed H.T. of 120 v. 90v. or 60 v. at up to 40 mA. and fully smoothed L.T. or 2v. at 0.4 to 1 a. Price, complete with circuit, wiring diagrams and instructions, only 48/9. Or ready to use, 8/9 extra.

**PERSONAL SET BATTERY SUPER-FEEDER KIT** A complete set of parts for construction of a Unit ( housed in metal case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v. 50 c/c. For 4 valve receivers requiring 90 v. 10/20 mA. and 1.4 v. 250 mA., fully smoothed. Price complete with circuit. Only 35/9. Or ready for use, 42/6. Size of unit, 5 1/2 x 4 x 1 1/2 in.

**BATTERY CHARGER KITS** For mains 200-250 v. 50 c/c. To charge 6 v. acc. at 2 a. 25/6. To charge 6 or 12 v. acc. at 2 a. 31/6. To charge 6 or 12 v. acc. at 4 a. 49/9. Above consist of transformer, full wave rectifier, fuses, fuseholders and steel case. Any type assembled and tested, 6/9 extra.

**THE SKYFOUR T.R.F. RECEIVER.** A design of a 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable Mu high gain H.F. stage followed by a low distortion audio bend detector. Power pentode output is used. Valve line up being 6K7, 6F6, 6F6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point to point wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of 24/19/6 including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

Terms : C.W.O. or C.O.D. NO C.O.D. under £1. Post 1/- extra under 10/-; 1/6 extra under £1; 2/6 extra under £3. Open 9 to 5.30; Sats. until 1 p.m. Catalogue 6d., Trade List 5d. S.A.E. with all enquiries.

**R.S.C. 10 WATT "PUSH-PULL" HIGH-FIDELITY AMPLIFIER A3**

Ideal for the quality enthusiast in the home or small hall. Two different inputs can be simultaneously applied and controlled by separate volume controls. Any kind of Pick-up is suitable and most microphones. Tone controls give full Long Playing record equalisation for uncorrected Pick-ups. Sensitivity is very high. Only 130 millivolts required for full output. H.T. and L.T. available for Radio Feeder unit.

Complete with integral Pre-amp. Tone control stage (as A4 amplifier), using negative feedback, giving humproof individual bass and treble lift and cut-tone control. Six Negative Feedback Loops. Completely negligible hum and distortion. Frequency response  $\pm 3$  db. 30-20,000 c.p.s. Six valves. A.C. mains 200-230-250 v. Input only. Outputs for 3 and 15 ohm speakers. Kit of parts complete in every detail, plus 7/6 carriage. Or ready for use, 45/- extra.

Illustrated leaflet 6d. Cover as for A4 is suitable. H.P. TERMS ON ASSEMBLED UNITS. DEPOSIT £1/13/4, plus 7/6 carriage, and nine monthly payments £1.

**7 GNS.**

**H.V. LONG PLAYING RECORD PICK-UP** Suitable with Crystal Pick-Up (Sapphire Stylus). Speed 33 1/3 r.p.m. For A.C. mains 200-250 v. limited supply. Brand New Cartoned. Perfect. Only £3/19/6. Plus carr. 5/- (Normal price £3 approx.).

**COLLARO HIGH-FIDELITY MAGNETIC PICK-UPS.** High impedance type. Limited stocks at fraction of normal price. Only 35/- Brand New.

**FOUR STAGE RADIO FEEDER UNIT.** Design of a High Fidelity Tuner Unit T.R.F. L. & M. Wave. Full decoupling. Self-contained heater supply. Only 250-400 v. 10-15 mA. H.T. required from main amplifier. Three valves and low distortion Germanium diode detector. Flat-topped response characteristic. Loaded H.F. coils. Two variable-Mu controlled H.F. stages. 3-Gang condenser tuning. Detailed wiring diagrams, parts list, and illustration, 2/6. Total building cost, £3/15/-.

**P.M. SPEAKERS.** All 2-3 ohms, 6in. Plessey, 16/9. 8in. Plessey, 16/9. 10in. Plessey, 19/6. 12in. R.A. 26/9. 10in. Rola with trans. 29/6. 10in. W.B. "Stentorian" 3 or 15 ohm type HF1012 10 watts, high-fidelity type. Highly recommended for use with any of our amplifiers, £3/17/6.

**MICROPHONES.** Crystal high fidelity types. Recommended for use with our amplifiers. Acos, Hand or Desk type, 50/- Stand type, with heavy floor base and adjustable stem, £8/19/6. H.P. TERMS ON "MIKES," SPEAKERS, etc., when supplied with our amplifiers.

**COAXIAL CABLE,** 75 ohms, 3 in., 7d. Yard. Twin Screened Feeder, 9d. yard.

**SELENIUM RECTIFIERS**

L. T. Types	H.T. Types H.W.
6/12 v. 4 a. H.W.	150 v. 40 mA 3/9
	250 v. 50 mA 6/9
F.W. Bridge Type	250 v. 80 mA 7/9
6/12 v. 1 a.	RM4 250 v. 250 mA 11/9
6/12 v. 2 a.	

**R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)**

Interleaved and impregnated. Primaries 200-230-250 v. 50 c/c Screened

**TOP SHROUDED, DROP THROUGH**

200-0-250 v. 70 mA, 6.3 v. 2.5 a	13/9
260-0-260 v. 70 mA, 6.0 v. 2 a, 5 v. 2 a	16/9
350-0-350 v. 80 mA, 6.3 v. 2 a, 5 v. 2 a	18/9
230-0-250 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
300-0-300 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
350-0-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
350-0-350 v. 100 mA, 6.3 v. 4 a, C.T.	
0-4-5 v. 3 a	23/9
350-0-350 v. 150 mA, 6.3 v. 4 a, 5 v. 3 a	29/9
350-0-350 v. 150 mA, 6.3 v. 2 a, 6.3 v. 2 a, 5 v. 3 a	31/6

**FULLY SHROUDED UPRIGHT**

250-0-250 v. 60 mA, 6.3 v. 2 a, 5 v. 2 a	
Midget type 21-31in.	17/6
350-0-350 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a	19/9
250-0-250 v. 100 mA, 6.3 v. 4 v. 4 a, C.T.	27/9
C.T. 0-4-5 v. 3 a	
250-0-250 v. 100 mA, 6.3 v. 6 v. 6 v. 3 a	31/-
For R1355 conversion	
300-0-300 v. 100 mA, 6.3 v. 4 v. 4 a	27/9
C.T. 0-4-5 v. 3 a	
350-0-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	27/9
350-0-350 v. 100 mA, 6.3 v. 4 v. 4 a	27/9
C.T. 0-4-5 v. 3 a	27/9
350-0-350 v. 150 mA, 6.3 v. 4 a	33/9
0-4-5 v. 3 a	
425-0-425 v. 200 mA, 6.3 v. 4 a, C.T.	
6.3 v. 4 a, C.T., 5 v. 3 a. Suitable Williamson Amplifier, etc.	49/9
450-0-450 v. 250 mA, 6.3 v. 6 a, 6.3 v. 6 a, 5 v. 3 a	69/9

**ELIMINATOR TRANSFORMERS**  
 Primaries 200-250 v. 50 c/c. 120 v. 40 mA 7/9  
 130 v. 50 mA, 6 v. 3 a ... 14/9

**FILAMENT TRANSFORMERS**  
 All with 200-250 v. 50 c/c primaries 6.3 v. 1.5 a, 5/9; 6.3 v. 2 a, 7/6; 0-4-6.3 v. 2 a, 7/9; 12 v. 1 a, 7/11; 6.3 v. 3 a, 8/11; 6.3 v. 6 a, 17/6; 12 v. 3 a or 2.4 v. 1.5 a, 17/6.

**CHARGER TRANSFORMERS**  
 All with 200-230-250 v. 50 c/c Primaries:  
 0-9-15 v. 11 a, 11/9; 0-9-15 v. 3 a, 18/9;  
 0-9-15 v. 5 a, 19/9; 0-9-15 v. 6 a, 22/9.

**SMOOTHING CHOKES**  
 250 mA 3-5 H 109 ohms ... 11/9  
 150 mA 7-10 H 250 ohms ... 11/9  
 100 mA 10 H 175 ohms Potted ... 8/9  
 80 mA 10 H 350 ohms ... 5/6  
 60 mA 10 H 400 ohms ... 4/11


**E.H.T. TRANSFORMERS**  
 2,500 v. 5 mA, 2-0-2 v. 1.1 a, 2-0-2 v. 1.1 a for VC197, VCR517, etc. ... 38/6

**OUTPUT TRANSFORMERS**  
 Midget Battery Pentode 66 : 1 for 354, etc. ... 3/9  
 Small Pentode 5,000  $\Omega$  to 3  $\Omega$  ... 3/9  
 Standard Pentode 5,000  $\Omega$  to 3  $\Omega$  ... 4/9  
 Standard Pentode, 78,000  $\Omega$  to 3  $\Omega$  ... 4/9  
 Standard Pentode, 10,000  $\Omega$  to 3  $\Omega$  ... 4/9  
 Multi-radio 40 mA, 30 : 1, 45 : 1, 60 : 1, 90 : 1, Class B Push-Pull ... 5/6  
 Push-Pull 10-12 watts 6V6 to 3D or 15  $\Omega$ . Sectionally wound ... 16/9  
 Push-Pull 10-12 watts to match 6V6 to 3-5 or 15  $\Omega$  ... 16/9  
 Push-Pull 20 watts ... sectionally wound 6L6, KT66, etc., to 3 or 15  $\Omega$  47/9  
 Williamson type exact to spec. ... 85/-

**RADIO SUPPLY CO. (LEEDS) LTD. THE CALLS, LEEDS, 2**

# Amazing Offer—

## AN ELECTRIC MOTOR WITH REDUCTION GEAR

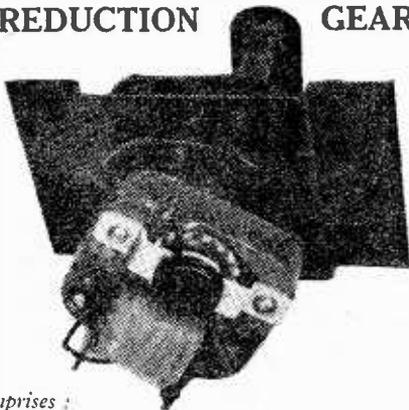

Comprises:

200/240 v. A.C. Shaded Pole Motor with a Reduction Gear giving final speed of 6 r.p.m. This drives a reciprocating arm at 6 times per minute. Gearing easily removed—motor speed approx. 2,000 r.p.m. These motors are powerful and can be used for: Models, Tape Recorders, Gram Drives, Display Purposes, Beam Aerials and many more uses.

Offered at a fraction their cost.

Each, 12/8. Two for 22/6. Carriage 1/6.

### RADIO SERVICING CO.

82, SOUTH EALING ROAD, LONDON, W.5. EAL 5737

# FREE TO AMBITIOUS ENGINEERS!

This 144-page Book



Have you sent for your copy?

### 'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---  
Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME .....  
ADDRESS .....

Subject or Exam. that interests me .....  
British Institute of Engineering Technology  
409B, College House, 29-31, Wright's Lane,  
Kensington, W.8.

### WHICH IS YOUR PET SUBJECT?

Mechanical Eng.  
Electrical Eng.  
Civil Engineering  
Radio Engineering  
Automobile Eng.  
Aeronautical Eng.  
Production Eng.  
Building, Plastics, Draughtsmanship  
Television, etc.

### GET SOME LETTERS AFTER YOUR

NAME!  
A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.P.E.  
A.M.I.M.I.  
L.I.O.B.  
A.F.R.Ae.S.  
B.Sc.  
A.M.Brit.I.R.E.  
CITY & GUILDS  
GEN. CERT.  
OF EDUCATION  
etc., etc.

# BIET

WONEY BACK GUARANTEE **DUKE & CO** Tele: GRA 6677 CWO OR COD  
621 ROMFORD RD. LONDON. E.12.

**RADIO GRAM CHASSIS, 29/9.**—Including Speaker. 5 valve s/het. 3 w/band, A.C. mains, complete, but less valves. All used, tested, guaranteed. P. & P. 4/6. Drawings 2/6 or free with order. Knobs 1/6 set extra. Complete with valves 97.6.

**RADIO CHASSIS, 7/9.** A.C. or universal, s/het receivers. Less valves dial and electrolytics. Otherwise believed to be in working order. Note. —Our 8in. M.E. speaker fits some of these sets, we match on request with order. P. & P. 3/6.

**RADIO CHASSIS, 14/9.**—As above with 3 band coil packs, 465 I.F.'s. All used bargains. P.&P. 3.6.

**SPEAKERS, 10/9.**—8in., 6½in., 5in. or 3½in. std.; P.M. 3-5 ohms. or with O.P. trans.; 14/9. Used, tested, guaranteed. Post 1/9.

**SPEAKERS, 2/9.**—8in. M.E. field 1k, 2k, 5k ohms. With O.P. trans., 4/9. Post 1/9. Used, tested, guaranteed.

**V.H.F. RECEIVER 1124, 17/6.**—With 6 valves. Ex-W.D. good condition 6 channel switching. Receives TV sound, police, fire and amateurs 30.5 to 40 mc's. I.F. 7 mc/s. Post 2/6. Drawings and conversion data free with each set.

**V.H.F. 1125 SET, 7/9.**—New and boxed. This little set is a V.H.F. receiver. Requires a little modification to put it into service. Complete with valves. Post 2/-.

**R.F. UNIT 24, 12/6.**—New and packed. Tuning 20-30 mc/s. Including 3 valves. Post 2/-.

**12in. TV TUBES, £5.—14in., £8/10/-; 17in., £12/10/-.** GUARANTEED SIX MONTHS. Ins. Carr., 15.6. C.W.O. 12in. Mullard, 6 mth. guarantee; other makes 3 mths. guar.

**21in. TV MASKS, 8/9.**—Brand new, white rubber. Carr. 3/9.

**12in. TV MASKS, 3/9.**—Brand new, white rubber. Post 1/9.

**12in. TV MASKS, 1/9.**—Used but O.K. Post 1/9.

**12in. PLATEGLASS, 2/9.**—Complete with polished wood escutcheon. Post 1/9. 9in. at 1/9, plus post.


**O.P. TRANSFORMERS, 1/9.**—Used, tested, guaranteed. Std. size. Post 9d.

**TWO GANG CONDENSERS, 2/9.**—Std. size .0005. Used, tested, guaranteed. Also 3 gang, 2/9. Post 9d.

**TV CONDENSERS, 9/9.**—Electrolytic. 120 mfd. plus 64 mfd. 350 volt. Post 1/-.

**MAINS TRANSFORMERS, 5/9.**—350-0-350v., 12v. plus 4v. Primary. 100, 120, 200, 250. Make ideal auto trans. Post 2/-.

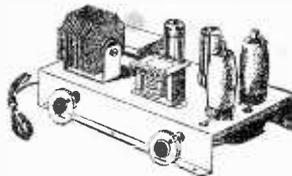**AMPLIFIERS, 57/6.**—3 valve, 4 watt output, A.C. or universal. Post 2/6.



**AMPLIFIERS, 77/6.**—4 valve, 7 watt output, A.C. or universal. Post 3/6.

**AMPLIFIERS, 97/6.**—5 valve, 10 watt output, A.C. only, with extra pre-amp stage, 3 controls. Post 3/6.

2½d. stamp only for complete catalogue.

# News from the Trade

## A New H.F. Point Contact Transistor

THE General Electric Company, Ltd., has developed a new high frequency germanium point contact transistor known as type EW51. Its main value is in pulse circuits (e.g., amplifying, forming and shaping of pulses) and it is therefore of considerable importance in the field of digital computers. Used as a pulse amplifier, its speed of response is such that, if the rise time of the input waveform is 0.05 microsecond, the rise time of the output waveform is less than 0.15 microsecond (usually less than 0.10 microsecond).

If the input waveform does not cause the transistor to "bottom" (a condition of high collector current, low collector voltage, in which further increase in the amplitude of the input signal does not increase the amplitude of the output signal) the fall time of the output waveform will be approximately equal to the rise time. If bottoming occurs, the fall time will be increased because of the "hole storage" effect; the actual increase will depend on the degree of bottoming and the duration of the pulse.—General Electric Co., Ltd., Magnet House, Kingsway, W.C.2.


## "Osmor" Coil Type QA81 ( $\frac{1}{2}$ Cup)

THIS is the aperiodic or mutual-inductance coupling type of medium wave superhet coil. The appropriate oscillator coil is QO8. Only the half-cup is employed with this type of coil to obtain optimum inductive coupling which is not possible with the full iron-dust cup, owing to the cup forming an inductive seal. The half-cup provides the required inductive coupling and may be so placed in a circuit for the half-cup to act as an electrostatic screen, and thus eliminate or minimise the amount of other screening required. The "Q" factor of these coils is considerably higher than normal and they are, therefore, particularly useful in the search for selectivity when losses for selectivity are usually inevitable.—Osmor Radio Products, Ltd., 418, Brighton Road, South Croydon, Surrey.
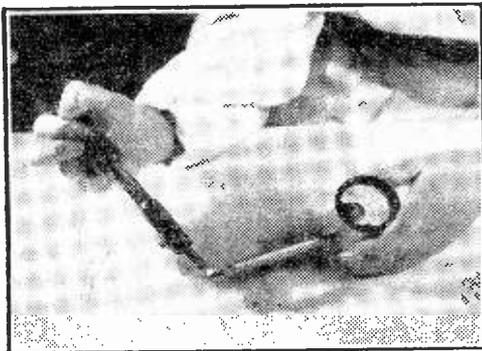
## Multicore Introduce Solder Thermometer

A RECENTLY introduced item by Multicore Solder is a solder thermometer.


The instrument is completely self-contained and



The new Multicore Solder Thermometer in use.

comprises a meter movement which is connected to a thermo-couple mounted at the end of a tube attached to the meter. A scale is graduated in degrees Centigrade and Fahrenheit and the maximum temperature to which the instrument should be subjected is 400 deg. C. (752 deg. F.).

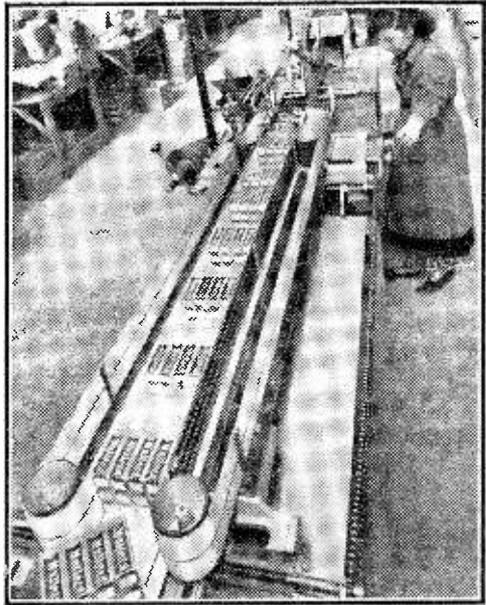The solder thermometer will be supplied direct by Multicore to factories already using Multicore Solder at a net price of £6 12s. 6d. Delivery is stated to be approximately two months.—Multicore Solders, Ltd., Multicore Works, Maylands Avenue, Hemel Hempstead, Hertfordshire.



The Mullard machine which automatically wraps the valves in cellophane.

## New Cellophane Wraps for Mullard Valves

AS from April 1st, a new valve carton wrapping system was brought into operation by Mullard, Ltd. Valves will be cellophane wrapped in batches of six or twelve, according to size of carton.

The new system is designed to overcome, as far as possible, inconvenience and time waste.

The advantage of the new cellophane wraps will primarily be felt by those who normally order valves in large quantities.

To obtain maximum benefit from the new system, they have only to order stock in multiples of six or twelve. A new type of availability sheet, issued at the end of March, indicates which valves are wrapped in batches of six and which in batches of twelve. There is, of course, no obligation to order in these quantities.

A special machine which automatically wraps the valves in cellophane packets has been installed at the Mullard Valve Service Department, Waddon, Surrey.

# Programme Pointers



## Music Notes

**W**EBER'S music has always had a fascination for me. Lacking the majesty of Beethoven and the peerless beauty of Mozart, it nevertheless has a charm all its own. It is redolent of its time and possibly that is why it is not great as the two aforementioned masters and Schubert are great. But it has sweetness, dignity and character, whilst the "Invitation to the Waltz" is unrivalled in its own sphere.

Five Saturday morning programmes have been given of his piano music which were wholly delightful. The pianists, Ronald Jones, Liza Fuchsova and Paul Hamburger (duettists), Natalia Karp, Natasha Litvin and Robin Wood, brought out the full flavour and sentiment of the music.

*Music Magazine* has fallen off a lot lately. Truth to tell, I suppose all the really original and thought-provoking subjects have been exhausted, leaving little left over. After all, the compilers went through music with a pretty fine toothcomb and the result has been some mighty fine programmes. Now, with a constant stream of "profiles" of current virtuosi, and such items as "The Things They Teach," etc., it looks as though the "What can we give them next week?" stage has been reached.

## Egyptian Pyramids

"The Mountains of Pharaoh," the Arab name for the Egyptian pyramids, made an attractive programme about the greatest of the seven wonders of the ancient world. Many were the quotations from famous explorers and travellers. So many, in fact, that it was all the stranger that there was no mention of Lord Carnarvon's and Mr. Howard Carter's opening of Tutankhamen's tomb which made the headlines in 1922-23. Some of the voices reading the excerpts were, as they always are in these programmes, sanctimonious sounding and stuffed-shirtish, but it was a pleasing programme none the less. It was written and produced by Leonard Cottrill.

Is it necessary or desirable for the announcer to preface the Light Programme at 9 a.m. with the remark, "White rabbits, white rabbits, white rabbits. Ladies and gentlemen, here begins another day of broadcasting"? Surely, it couldn't raise a smile even among the youngest or silliest children?

The gentle art of being in two places at once is not given to many people. Its accomplishment, even on the BBC, must be very rare. But it is not surprising that that most versatile comedian Vic Oliver performed it recently, being on both the Home Service and the Light Programmes simultaneously. It was on a Saturday evening, in the weekly *Music Hall*, and as the "beat the expert" visitor in "What Do You Know?" at 8 till 9 p.m. and 8.30 till 9 p.m. respectively. Mr. Oliver, the comedian, was his usual gifted self. On Mr. Oliver, the "serious musician," being cross-questioned on Schubert's Unfinished Symphony we will draw a veil.

## Our Critic, Maurice Reeve, Reviews Some Recent Programmes

"The Key of the Garden," by Naomi Mitchison and Lewis Gleigud, is a pleasant play about the events which led up to the Crucifixion, culled from the Gospels. Merely a narrative, it would be unfair to accuse it of what it was never meant to be—a play of ideas. It contained some fine acting by a longish cast. The thunderstorm which in the story accompanied the End was frightfully artificial; each peal of thunder was an exact replica of the preceding one.

*Calling Miss Courtneidge* is a weekly series as good as most now running. Cicely herself is very versatile and on the last occasion I heard it did sketches with Graham Stark, Victoria Campbell and Donald Wolfitt. This programme can be recommended.

During the football season *Sports Report* and *Sports Parade* are excellent programmes for the football fan every Saturday and I am full of admiration for Eamonn Andrews, who conducts them. But if only he would "cut his own cackle" by half, how much more could be covered and how much pleasanter it would be! He tells us regularly that there is hardly time to cover all that is due to be covered, yet he talks on and on and on, all of it irrelevant, irritating and time wasting. I am glad to see that the absurd weekly "competition" has apparently been dropped.

## Plays

Marcel Pagnol's "Marius," a delightful French confection set in the great seaport of Marseilles, came over excellently in Barbara Bray's translation and radio adaptation in the *Monday Night Theatre* series. Telling of the love of a charming girl for a fellow whose love for the sea, she is convinced, is greater than his feelings are for her, and who renounces her happiness in consequence, it has most of the ingredients of a first-class radio play. "Fanny" and "Caesar"—the other chief characters—form a trilogy of plays which I hope we shall soon hear. Patric Boonan, Carol Marsh, James Hayter, Frank Atkinson and others gave it a salty and reasonably Frenchy atmosphere.

We can trust Enlyn Williams to maintain our interest and sustain the excitement throughout a play and his "Someone Waiting," in *Saturday Night Theatre*, was no exception. How the father of an innocent man, wrongly hanged, got his own back gripped me to the end. Richard Williams took the place of Laidman Browne and he and James Thomason, Catherine Salkeld, Martin Starkie, Miriam Karlin and Pamela Gordon, etc., thoroughly curdled our blood.



## SOUTHERN RADIO'S WIRELESS BARGAINS

**TRANSRECEIVERS.** Type "38" (Walkie-Talkie). Complete with 5 Valves. In Metal Carrying Case. Ready for use. Less external attachments, 30/- per set. **ATTACHMENTS** for use with "38" **TRANSRECEIVER:** HEADPHONES, 15/6; THROAT MICROPHONE with Lead & Plug, 4/6; JUNCTION BOX, 2/6; AERIAL, 2/6; SPECIAL OFFER of used "38" **TRANSRECEIVERS** less valves but complete with ALL COMPONENTS. Excellent for SPARES, 11/6 per set.

**TRANSRECEIVERS.** Type "18" Mark III. TWO UNITS (Receiver & Sender) contained in Metal Case. Complete with Six Valves, Microammeter, etc. LESS EXTERNAL ATTACHMENTS, 44/10/-.

**RECEIVERS.** Type "109". 8-Valve S.W. Receiver with VIBRATOR PACK for 6 Volts. Built-in Speaker, METAL CASE, 45.

**BOMBSIGHT COMPUTERS.** Ex-R.A.F. BRAND NEW. A Wealth of Components. GYRO MOTORS, REV. COUNTERS, GEAR WHEELS, etc., etc. Ideal for Model Makers, Experimenters, etc., 43.

**LUBRA HOLE CUTTERS.** Adjustable  $\frac{1}{2}$  in. to  $3\frac{1}{2}$  in. For Metal, Wood, Plastic, etc., 6/6.

**RESISTANCES.** 100 ASSORTED USEFUL VALUES. Wire Ended, 12/6 per 100.

**CONDENSERS.** 100 ASSORTED. Mica, Metal Tubular, etc., 15/- per 100.

**PLASTIC CASES.** 14in. x 10 $\frac{1}{2}$ in. Transparent. Ideal for Maps. Display, etc., 5/6.

**STAR IDENTIFIERS.** Type 1 A-N. Covers both Hemispheres. In Case, 5/6.

**CONTACTOR TIME SWITCHES.** In Sound-proof Case. Clockwork Movement. 2 Impulses per sec. Thermostatic Control, 11/6.

**REMOTE CONTACTORS** for use with above, 7/6.

**MORSE PRACTICE SET** with Buzzer on Base, 6/9. Complete with Battery, 9/6. **MORSE TAPPERS.** Std, 3/6; Midget, 2/9.

**METERS & AIRCRAFT INSTRUMENTS.** Only need Adjustment or with broken Cases. TWELVE INSTRUMENTS, including 3 brand new Aircraft Instruments, 35/- for 12.

**CRYSTAL MONITORS.** Type 2. New in Transit Case. Less Valves, 8/-.

Postage or Carriage extra. Full List of RADIO BOOKS, 21d.

## SOUTHERN RADIO SUPPLY LTD.,

11, LITTLE NEWPORT ST., LONDON, W.C.2. GERrard 6653.

## HANNEY of BATH offers:—

**OSRAM 912** Eric resistor-pot kit with ceramic tube resistors, very highly recommended, 29/6; Lab. resistor kit, 32/4; T.C.C. condensers, 55-. **PARTIMING** Components, with loose lead terminations, Mains trans., 44/-; Smoothing Choke, 29/6; Output trans., 76 9. Price includes Partridge carriage/packing charge. Printed panel, 14 6. W.B. chassis, 28/6. **DENCO** 16 S.W.C. All-Chassis with beautiful Bronze Front Panel, 21/- (Printed.) S.A.E. List.

**MULLARD 5 VALVE 10 WATT AMPLIFIER.** T.C.C. Condensers, 45-; Eric resistor-pot kit, 37/6; Elstone Mains trans., 38/-; Elstone Output trans., 45/- (both types); Denco chassis, 14/6; Printed bronze panel 14in. x 5in., 6/6. Small parts as per our list. Matched valves available for both the above designs.

**FREQUENCY MODULATION.** For Wrotham high fidelity transmissions. DENCO technical bulletin giving circuit and point to point wiring diagram for building an F.M. Feeder unit, 1/9. post free. We have all components available. Printed parts list on application.

**HIGH FIDELITY SPEAKERS.** W.B. HF810, 60/6; W.B. HF912, 67/-; W.B. HF1012 (3.75 and 15 ohm. coil), 77 6. G.E.C. type FR metal cone, 28 15-. Goodmans "Orilia III", 29/15-.

**COILPACKS.** DENCO, CP 4/L and CP 4/M, 33/4; CP 3/70 pf. and CP 3/50 pf., 42 8. OSBORNE "Q" HO, 48/-; LM, 40/-; Batt., 50/-; RRF, 40/-; HF stage for HO pack, 20/-. We stock COILS by Weymouth, Osmor, Wearite, Denco, R.E.P.

**WIDE ANGLE COMPONENTS.** ALLEN, Teleking Chassis, 50/-; Coilssets (TK and Super-Visor), 44/6; LO.308, 40/-; FC.305, 21/-; DC.300-, 39 6; FC302, 31/-; GL.16 and 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OP.117, 9/-; BT.314, 15/-; DENCO Chassis Magnaview, 37 6; Chassis Super-Visor, 51/6; Coilssets Magnaview, 41 2; WA DCA1, 43/-; WA/FCA1, 31/-; WA/LC1 and WCL, 7/6 each; WA FMAL, 21/-; WA/LOT1, 42/-; WA/FBT1, 16/-.

Send 6d. stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Teleking, Magnaview (Brimar and English Electric large screen TV), Super-Visor, Mullard Universal Close Tolerance Silver Micas, etc., etc. Please add 1/- postage to orders under £1 and 2/- above.

## L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

## A REALLY SMALL RADIO RECEIVER

This radio receiver, although as small in size as a matchbox, gives loud, clear reception of the BBC Home, Light and Third Programmes on the medium waveband, about 180-550 metres. The set also tunes the Light Programme on the long waves, 1,500 metres. No catwhiskers, valves, or batteries are required, and the receiver works off a short indoor aerial in many districts.

PRICE **9/-** POSTAGE **3d.**  
EXTRA

This offer applies only to Gt. Britain, and Northern Ireland.

## SWIFT RADIO

102, BATH RD., WILLSBRIDGE, Nr. BRISTOL

## TESTOSCOPE MAINS TESTER



For high and low voltage testing.  
Standard Model: range 100/850 volts A.C. or D.C. Dual Model: range 1/30 and 100/850 volts A.C. or D.C.  
Write for interesting leaflet 29F.

Runbaken  
BENNETTS

## TAPE RECORDERS P.W. and SOUND MASTER

We can supply complete kits or separate components for both the P.W. and Sound Master Tape Recorders.

Sound Master Instructions, 6/6.

FULL HIRE PURCHASE FACILITIES  
3/- in the £ deposit.

## WATTS RADIO,

8, Apple Market, Kingston-on-Thames, Surrey. Phone: KINGston 4099.



NOW AVAILABLE WITH  
THE REMARKABLE NEW  
**PERSONALITY**

Details of full range now comprising  
29 models in folder No. S.P.10 sent  
on request.

Sole Manufacturers and Distributors:

**LIGHT SOLDERING DEVELOPMENTS LTD.,**  
106, GEORGE STREET, CROYDON, SURREY.

Tel. CROYdon 8589

The soldering bit which lasts indefinitely, does not become pitted or lose its face and requires no reshaping, filing or maintenance. Fixed bit models and replaceable bits available in all sizes.

- NO TRANSFORMER NECESSARY.
- FOR MAINS OR LOW VOLTAGES.

Rapid Heating—Extreme Lightness—Twenty models—Bit sizes, 1/8in., 3/16in., 1/4in., 5/16in., 3/8in.—Prices from 18/6. All voltages from 0/7 v. to 230/50 v. (State voltage when ordering.)

# Open to Discussion



Long-range F.M.

**SIR**,—I have a similar set to that described by C. B. Hanson in your May, 1954, issue, covering (at the time of writing) 85/100 Mc/s.

Using one R.F. stage and a vertical dipole I receive Police and Fire Service signals from as far away as Warwickshire, Buckinghamshire and Sussex.

As these transmitters are only 250 watts, and Wrotham's output is, I believe, considerably more, I think my office set will stand comparison with Mr. Hanson's.

With the quench control down to almost zero I get a readable signal from Radio Moscow.

The valve line-up of my set is Z77 R.F., 9002 super-regenerative detector, 9001, 6J5 audio, and 6F6 output. With these, little or no aerial is necessary for local stations.—L. J. WILSON (Great Bentley).

## Cathode Follower

**SIR**,—With reference to the number of letters published in your magazine recently from O. G. Kirslake (Orpington), I would like to point out that the circuit which he loosely describes as "cathode follower output" is nothing like a cathode follower.

This kind of circuit (cathode follower), as most people know, has a low impedance output and a gain of less than unity, but he matches his speaker to the valve and uses the normal O/P. transformer; after that he says that the output is as great, if not greater, than with the normal arrangement.

The cathode follower is designed to have a low impedance output which he doesn't take advantage of, and if, as he says, he uses a cathode follower, then why doesn't he dispense with the output stage altogether? He should be better off.—E. W. BONES (L.A.C.) (St. Annes).

## S.W. Bands

**SIR**,—The editorial of the March issue of PRACTICAL WIRELESS refers to the fact that "the so-called short-wave band has never proved popular on commercial receivers."

Can anyone explain just why this should be?

Surely no one can say that nothing of interest is to be found on these lower wavelengths (19 m.—49 m.). From such stations as Australia, Canada, France, U.S.S.R., Switzerland, Germany, Sweden, the Vatican and Holland just about every taste in politics, religion, music and mood, etc., can find satisfaction. Admittedly, though some of these stations daily pollute the band with political propaganda, the majority prove of great interest and education. Most of these stations publish schedules of their broadcasts monthly or quarterly or every six months, and some of these make very interesting reading.

However, the popular belief appears to be that

from these "names on the dial" nothing is to be obtained but unintelligible jabber! Why is it that so many are ignorant of the fact that most of these stations operate a round-the-clock service in English with musical request programmes, competitions and information services?

Can it be that many still regard the controls of a radio set as being as sacred as the seal on the gas meter?—BRIAN E. BALDWIN (Bradford).

## Time Checks

**SIR**,—I read with interest Mr. J. F. B. Elder's letter in PRACTICAL WIRELESS for May, concerning the lack of frequent time checks.

In a similar manner my job also entails the resetting of radio beacon clocks on light vessel.

I would like to point out that these vessels, heard on trawler band, use M.F., so do not have receivers covering W.W.V. station,

on approximately 2 Mc/s, nor GBIRS station, nor Rugby on 2.5, 5, 10, 15 Mc/s, so this method is not practical.

The procedure I use is to synchronise, first, a stop-watch with the BBC time signal 1300 or 1800 daily. On arrival on board the light vessel, the timing contacts of the special clock can be set to the stop-watch at any hour of the day or night.

On shore the radio beacon can be checked daily by listening on the appropriate wave band, again using the stop-watch.—E. A. VALENTINE (Dundee).

## Tape Amplifiers

**SIR**,—Some time ago you were good enough to answer some queries regarding the tape amplifiers. I have only just found time to complete the modifications, and so have been somewhat tardy in writing to thank you and to say that these are very successful.

Altering the bias components produced a slightly larger output, but as I had previously used a lower value for R53 the audible results were not really noticeable.

I had provided switching for altering the equalisation in the recording amplifier, and the results are now quite good at  $3\frac{1}{2}$  in. per sec. As a "purist" I doubt if I shall use this speed very much, but for some applications this is very useful.

I think you were right in saying I had become used to over-correction on L.P. It is surprising how quickly one gets used to a type of reproduction. I am now in the process of "re-educating" myself with the aid of a wide-range loudspeaker.

Following your March Editorial I have done a little computing to compare the cost of tape with gramophone. Aiming at similar standards there is not a great deal of difference in the cost of setting up. But in use, so far as popular "hit parade"

*Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.*

numbers are concerned, the advantages are overwhelmingly in favour of tape. Sixty "popular" records, all bought in the last eighteen months, were examined and no less than 50 were bought for one side only. At 5s. 4½d. a time, this works out at approx. 4s. 6d. a number. I average 24 such numbers on a 1,200ft. reel (2 tracks, 7½in. per sec.). Even with Ferro-tape at 45s. this works out at 1s. 10½d. per number, whilst with Easitape it is 1s. 6d. To this comparison must be added the facility of erasing and recording another item at no extra cost.


To the man with a taste for classical records, tape is not such a good proposition. The cost is roughly the same, with the added difficulty of having to wait for the right work to be broadcast, and the collector will not wish to erase.

Personally, I am completely sold on tape. I am still awaiting delivery of a second deck and will enjoy myself taking off what I want to keep.—A. A. WOMPRA (Conway).
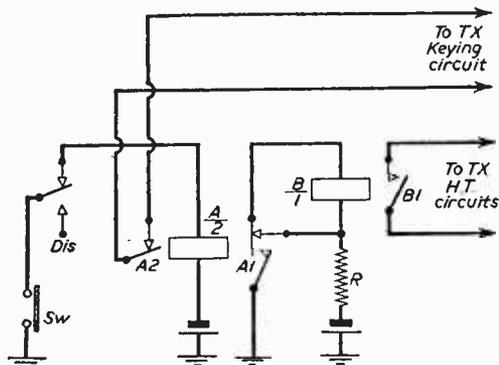
### Relays

SIR,—With reference to Fig. 14 of Mr. J. R. Davies's article on "Relays" in the May issue. Mr. Davies states further on in his article that two disadvantages exist on the use of this system for remote control of a transmitter: (1) An initial pulse is necessary to operate the B relay before keying; (2) The transmitter is always on load when the H.T. is switched on.

In the hope that it may be of some use I submit



The diagram described by P. L. B.

the following suggested rearrangement, which, I think, will overcome these difficulties. Very briefly, the arrangement works as follows:

Use is made of a key with a contact made in the normal position. To switch on the H.T., switch is thrown to "on" which operates relay A. Contact A1 removes the short-circuit from B, and connects earth via a "make before break contact" which operates B. During keying relay A releases, and contact A2, releasing, completes the TX keying circuit, while

A1 places a short-circuit across B, thus making it slow to release. Upon release of the key, A operates again, A2 disconnects the TX keying set, and A1 re-energises B again.

With this arrangement an ordinary relay can be used for B, and be made slow to release by placing a short-circuit across it. R prevents a short-circuit being put on the battery when A1 bunches.

Mr. Davies also states that "earth returns do not always give reliable results." I should like to point out that very extensive use is made in telecommunications of earth return for relay operation over considerable distances.—P. L. B. (Leominster).

### The 6AG7

SIR,—I feel that the remark, "This circuit would no doubt be popular over here but for the fact that supplies of the 6AG7 are difficult, so that it is virtually unobtainable" (made by Mr. O. J. Russell in his article on "Overtone Crystal Circuits" in the May edition of PRACTICAL WIRELESS) should not be allowed to pass, since, if one refers to the advertisement columns of the same issue it will be found that this valve is advertised at a moderate price no less than three times.

It may also be of interest to readers to know that, whilst experimenting with this circuit (Fig. 2) in which the use of a 6AG7 is advised, I substituted an EF50, and using a "surplus" crystal rated at 2.115 Mc/s (without an aerial coupled to the oscillator) found that, by using the second harmonic of the oscillator frequency, a strong enough signal was radiated so as to produce a marked "fishtail effect" on a television receiver in the room above. Judging by this result, I think that it is a reasonable conclusion to draw that an EF50 would give a good output on most frequencies, working on either the fundamental or any harmonic up to the sixth. I hope this information will prove useful.—R. E. HALL (Moseley).

### "Maximum Economy"?

SIR,—As a subscriber to your magazine for a number of years, I cannot help but notice the apparent policy of, as it were, "maximum economy."

I appreciate that in these days of high costs, etc., none of us are able to delve too expensively into our hobby. However, I feel that economy can be overdone.

The amplifier outlined in the June issue is a case in point. Can a good audio amplifier be built for £5, using valves designed for V.H.F. circuitry? Further, the eight-valve radio-gram chassis recently described uses air-cored tuning coils. Surely it is worth an extra pound or so to take advantage of all the improvements to be gained from dust-cores.

It is my experience that for a slight increase in outlay, a far greater degree of success is assured for most items of equipment for home construction. I feel I am echoing the sentiments of a large section of the amateur fraternity when I quote the old cliché—"Don't spoil the ship, etc."—J. R. MADLEY (Fife).

Editorial and Advertisement Offices:

"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. 'Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

**MULTIMETER KITS**

All kits consist of top quality components, 1% High Stability Resistors, 1% Shunts, Wirewound Pot., instructions, circuit, scale calibration for Ohms and Low A.C. Volts ranges; Westinghouse meter, Rectifiers in A.C. kits. Sundries include all switches, knobs, plugs and sockets needed and are extra.

100  $\mu$ A Kit 28/-, 23 D.C. Ranges. 0.5, 1, 2.5, 5, 10, 25, 50, 100, 250, 500 mA and Volts; 100, 250  $\mu$ A; 0.2 Volts. Sundries 12/1.  
100  $\mu$ A Kit 26/-, 3 Ohms Ranges. Ohms X1, X10 and X100 to measure Resistance between 10 ohms and 5 megohms. Separate zero adjustment each range. Sundries 7/4.  
100  $\mu$ A Kit 54/-, 26 D.C. Ranges. Above two kits combined. Sundries 13/4.


100  $\mu$ A Kits (meter scaled 0-15). As above. Ranges slightly different.  
1 mA Kit 28/-, 17 D.C. Ranges. 0.1, 0.2, 5, 10, 25, 50, 100, 200, 250, 500 Volts; 1, 2, 10, 50, 200 mA, 1 Amp; Ohms 10-50K. Sundries 10/8.

1 mA Kit 19/6, 4 A.C. Ranges. 10, 50, 250, 500 Volts A.C. Sundries 3/7.  
1 mA Kit 45/6, 21 A.C./D.C. Ranges. Previous two kits combined. Sundries 14/6.  
500  $\mu$ A Kit 26/-, 17 D.C. Ranges. 0.1, 0.2, 5, 10, 25, 50, 125, 250, 500, 1,000 Volts; 0.5, 1, 5, 25, 100, 500 mA; Ohms 200-100K. Sundries 10/8.

500  $\mu$ A Kit 19/6, 4 A.C. Ranges. 10, 100, 250, 500 Volts A.C. Sundries 3/7.  
500  $\mu$ A Kit 45/6, 21 A.C./D.C. Ranges. Previous two kits combined. Sundries 14/6.  
UNIVERSAL SHUNTS 1% accuracy for any 1 mA or 500  $\mu$ A meter. Only one simple adjustment to make, no calibrating meter being required. With instructions. Guaranteed one year. 5505 (1 mA) covers 2, 10, 50, 100 and 500 mA. 551 (1 mA) covers 2, 10, 50, 200 mA and 1 Amp. Price 15/-.

RESISTANCE BOX STANDARDS. Twelve 0.5% Wirewound Resistors, giving 1 to 1110 ohms in 10 ohm steps. 30/-.  
BRIDGE RATIO ALMS. 100 Ohms. Ratio 1 to 1 accuracy 0.1%, 4/6.  
PRECISION RESISTORS. Any value 1 to 1,500 ohms, accuracy 0.5%, 2/9.

**MASSEY** 25, Dominion Ave., Leeds 7.

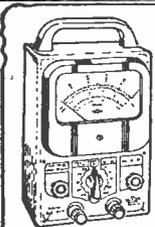

**PULLIN**  
SERIES 100  
TEST METER  
AC/DC 10,000  $\mu$ V  
21 RANGES  
100  $\mu$ A TO 1000V  
COMPLETE IN DIE-CAST CASE WITH TEST LEADS CLIPS AND PRODS FULLY GUARANTEED

SENT POST FREE FOR £2.10s. DEPOSIT AND ELEVEN FURTHER MONTHLY PAYMENTS OF £1. CASH PRICE £12.7s.

*Frith* **RADIOCRAFT Ltd**  
69-71 CHURCH GATE LEICESTER

**TELEKIT SUPPLY**

Chantry Lane, Bromley, Kent.

Please mention P.W. and enclose 6d. postage.

**VALVES GUARANTEED**

OZA	4/-	6BR7	8/6	12A6 1299	
ILA	5/6	6BS7	7/6	15D2 (soiled)	5/-
ILN5 (soiled)	3/-	6BW6	6/6	15D2	4/-
IS5	6/-	6CH6	6/6	EF50	5/-
IU5	6/-	6J5	5/-	W77	5/-
5763	8/-	6V6	7/-	1B24	35/-
6A8	8/-	6X4	6/6	6AKC	6/6
6AL5	6/-	6X5	7/-	6AQ5	8/-
6AM6	6/-	7D5	6/-	6U5	8/-
6AT6	7/8	7D8	6/-	12AT6	7/6
6B8	6/-	7H7	6/-	13D1	7/-
6BA6	6/-	9D2	5/-	50C5	8/-
6BE6	6/-	11D3	6/-	TT11	6/-
		12BE6	6/8	12BH7	7/-

BECKENHAM, KENT  
THE SHOP FOR THE CONSTRUCTOR  
NOW OPEN AT 104, HIGH STREET  
BECKENHAM 3720

**ALFRED PADGETT**

40 MEADOW LANE, LEEDS 11

Established 21 years

1155 RECEIVERS.—New condition, complete with Valves. £6-12-6, carriage 8/6.  
APNT.—Brand new RX with 14 Valves and Motor. Silly Price, £3-2-6, carriage 7/6.  
1154 TX.—Brand new complete with valves and meters. 17/6, carriage 10/6 (including transit case).

CLASS B BATTERY AMPLIFIER.—Complete with two valves. Types CV1035 and Det. 210. Condition fair. Valves O.K. 5/-, post 1/10.

EX.-U.S.A. DINGHY TELESCOPIC AERIAL.—Complete with umbrella reflector. Brand new. 5/-, post 1/9.

ANOTHER LOAD of the famous Type 17 Sets, less valves. Rough condition, but all guaranteed to work. 3/6, post 2/6.

METAL BOX with three silver mica capacitors 470 pF. Brand new. 1/-, post 4d.

VALVEHOLDERS.—Removed from new ex-W.D. units. EF50 type pot. base, 6d., post 3d.; 5/- dozd., post free. Amfipal type Mazda and standard, 41d., post 3d.; 4/- dozd., post free.

SUPPRESSOR BOXES.—Complete with four chokes and four 1 condensers. 1/9, post 1/9.

MU-METAL SCREEN for VCR97 tubes. 2/-, post 1/9.

VALVE-SCREENING CANS.—Removed from 1124 set. 5d. each, post 3d.; 4/9 dozd., post free.

SMALL METAL BOX.—Complete with Yaxley switch and knob. Also toggle switch. Brand new. 1/-, post 8d.

BARGAIN PARCEL, 5/-, post 2/6 (mains or battery). Over 30/- worth of spares.

Money back guarantee.

**STAN WILLETTS**

43, Spon Lane, West Bromwich, Staffs.

Tel.: WES 2392.

"CONNOISSEUR" Miniature moving coil pick-up. New with transformer 27/6. List price 90/- P. & P. 1/-.

ACOS CRYSTAL PICK-UP (GP10). New and boxed. 19/11. list price 44/- P. & P. 1/-.

GERMANIUM CRYSTAL DIODES. G.E.C. 1/- each. 9/6 doz. P. & P. 3d.

"VALVES" BRAND NEW GUARANTEED. 504G, EBC33, 6SN7, 6SL7, 6K9G, 7/6 each. 6V6CT, 6/-, 6K7M, 6S67M, 613C, E132, 4/9, each. 6X5GT, 6X4, 6/9, 6K7G, 4/6, 6F6G, 5/6, Z77, 6J6, 5/-, 4D1, 8D2, 1/9, 9D2, 15D2, 3/6, RK34, EA50, 1/9, EY51, ECL80, 10/6, 10F1, UL41, UBC41, UCH42, 9/6, UY41, 8/6, UF41, 7/9, IT4, 5/-, P. & P. 6d.

DF91, DAF91, DK2, DL24, 1R3, 1R5, 1R4, 1T4, 3S4, 6/9 each. 4 for 24/9. P. & P. 6d. RM4, 14/-, RM3, 5/-, RM2, 4/-, P. & P. 6d.

CONDENSERS. Brand New. 900 mfd. 12 v., 2/-, 8 mid. 450 v., 1/9, 15 x 16, 450 v., 3/6, 25 x 32 450 v., 4/9, 24 mid. 450 v., 2/-.

VALVES WANTED—BEST PRICE PAID

**DECCA RECORD PLAYERS**

Standard or L.P. List Price £12/1/6

**OUR PRICE**

**6 GNS.**

Packing, carriage, insurance, etc., 10/6.

RICHARD ALLEN 3 SPEED RECORD PLAYERS in handsome walnut finish cabinets, fitted Colloar motor with dual purpose Acos hevis. List price, £19/5/6. Our price £8/19/6. Packing, carriage, insurance, etc., 10/6.

Send stamp for bargain list of record players.

**RONALD WILSON & CO.**  
12, BRIDGE ST., WORCESTER

**COPPER WIRE**

COTTON COVERED

S.W.G.	2 ozs.	4 ozs.	SILK COVERED	
			2 ozs.	4 ozs.
16	1/6	2/3	1/6	2/3
17	1/6	2/4	1/6	2/4
18	1/6	2/5	1/6	2/5
19	1/7	2/6	1/8	2/8
20	1/7	2/7	1/9	2/11
21	1/7	2/8	1/10	3/11
22	1/8	2/9	1/11	3/13
23	1/9	2/10	2/-	3/15
24	1/9	2/11	2/-	3/15
25	1/10	3/-	2/1	3/7
26	1/11	3/2	2/2	3/9
27	2/-	3/4	2/3	3/11
28	2/-	3/5	2/4	4/1
29	2/1	3/7	2/5	4/3
30	2/2	3/9	2/6	4/5
31	2/3	3/10	2/7	4/7
32	2/3	3/11	2/9	4/11
33	2/5	4/2	3/-	5/5
34	2/6	4/5	3/1	5/7
35	2/8	4/8	3/3	5/11
36	2/9	4/11	3/5	6/3
37	3/2	5/9	3/7	6/7
38	3/-	6/5	3/9	6/11
39	—	—	4/-	7/5
40	4/8	8/3	4/3	7/11

POSTAGE EXTRA.  
POST ORDERS ONLY PLEASE.  
Send stamp for comprehensive lists.

**CRYSTAL SET**

INCORPORATING THE SILICON CRYSTAL VALVE

Adjustable Iron Coated Coil.

RECEPTION GUARANTEED

Polished wood cabinet, 15/-, post 1/-

A REAL CRYSTAL SET, NOT A TOY

**POST RADIO SUPPLIES**

33 Bourne Gardens, London, E.4

**Television, Radio, Record CABINETS MADE TO ORDER**

ANY SIZE OR FINISH  
CALL OR SEND DRAWINGS FOR QUOTATION

**B. KOSKIE**  
(DEPT. C.)

72-76 Leather Lane, Holborn, E.C.1.  
Phone: CHANCERY 6791/2

**ANNAKIN**

Mike Trans., 100-1, 1/6; 173 pF two ranges. 1/-; 135 pF var. cond., 9d. M116, 2/8; P.T.15, 3/8. Large W.W. Res., 50 K., 20 K., 12 K., 2 K., 1/- ea. Medium W.W. Res., 75 K., 5 K., 350 ohms, 1/- ea. All-Wave Chokes, 1/-; 8+8 mfd., 350 v.w., D.C., 2/-; Unit with two large I.P. 17 w. switches, useful for Model Railways, 3/6 ea., plus 2/- P. & P. Money Back Guarantee.

Please send plenty of postage, surplus refunded. C.W.O. only. Free Lists.  
25, ASHFIELD PLACE, OTLEY, YORKS.

**1-Finger Pianists**

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

**C & S, 10 Duke St., Darlington, Co. Durham**

Just Published!

### SIMPLE ELECTRONIC MUSICAL INSTRUMENTS FOR THE CONSTRUCTOR

by Alan Douglas

5s. 0d. Postage 4d.

The Radio Amateur's Handbook, by "A.R.R.L.", 30s. 0d., postage 1s. 0d.  
Radio and TV Test Instruments, Gernsback Library, 12s. 0d., postage 4d.

Telecommunications, by A. T. Starr, 35s. 0d., postage 1s. 0d.

CHF Circuits and Components, by Milton S. Kiver, 45s. 0d., postage 1s. 0d.

Electronic Musical Instruments, by Richard H. Dorf, 55s. 0d., postage 1s. 0d.

Radio Engineers' Servicing Manual, by E. Molloy, 42s. 0d., postage 1s. 0d.

Wireless for Beginners, by C. L. Boltz, 8s. 6d., postage 6d.

Single Sidedband for the Radio Amateur, by "A.R.R.L.", 14s. 0d., postage 6d.

Radio Valve Data, compiled by "Wireless World", 3s. 6d., postage 3d.

### THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST OF British and American Technical Books.

19-23, PRAED STREET

(Dept. T.6), LONDON, W.2.

\*Phone: PADDINGTON 4185.

Open 6 days 9-6 p.m.

## LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.P., SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPHERDS Bush 1729

### RECEIVERS, TYPE R.1155 "B."

These are an improved version of the well-known R.1155 "A." Frequency range 18-7.5 Mc/s. 7.5-3 Mc/s. 1.5 Mc/s-600 Kc/s. 500-200 Kc/s. and 200-75 Kc/s. Fitted with 10 valves (3 VR99, 3 VR100, 2 VR101, and 1 each VR102 and VR103). These receivers are fitted with a superior type of slow-motion drive which is a considerable improvement on the type fitted to the models of earlier design. In good, new condition and aerial tested before despatch to ensure in first-class working order. PRICE £11.11.0, or in soiled condition, tested, etc., as above, £9.9.0. Carriage charge 7/6.

### POWER PACK OUTPUT-STAGE UNITS.

—Specially designed to operate the R.1155 receivers direct from A.C. mains and to provide for a speaker output. Fitted with 5Z3 rectifier and 6V6 output valves and connector which plugs direct into receiver for immediate use. PRICE £4.4.0, or £4 with receiver. Carriage 3/6.

12 VOLT VIBRATORS.—Standard 4-pin non-synchronous type in good working order. PRICE 8/6, post 9d.

INDICATORS, TYPE 182.—Fitted with cathode ray tube, type VCR517 (TV picture tested) 3 VR91's, 1 5U4, Mu-metal screen, wire-wound pots and a mass of other useful components. In used, good condition. PRICE 65/- or less valves. PRICE 37/6, carriage 6/-.

BARGAINS FOR CALLERS.—Resulting on tidying up one of our Warehouses we are finding many useful chassis, meters, transmitters and radio units, etc. Quantities are too small to advertise, but callers can inspect these items, which will all be available at CLEARANCE PRICES.

## BENSON'S BETTER ARGAINS

BRAND NEW. ORIGINAL CARTONS. R.F. UNITS. TYPES 28 or 27, 27/6; 24, 15/- (Postage 2/6). R.F.25. Soiled, 12/6. High Stability, Close-tolerance Resistors, mainly 1/4 and 1 watt, from 10Ω to 5.1MΩ in pref. values; 1/- each. DYNAMOTORS, D.C. (approx. 250 v. 80 mA., at 6 v.), 8/6. 12 v. input, 250 v. 60 mA. and 6.3 v. outputs, P.M. field, 7/6. Filters for these, 2/6. I.F.T.'S, new, canned 10/11 Mc/s., 1/3. POWER UNIT 28S, 230 v. 50 c. input, Output D.C. 2 kv. 5 mA., 350 v. 150 mA. A.C. 6.3 v. 15 a., 3 valves. New 75/-, carr. paid inland. TRANSFORMERS, new, incl. mains input; 6.3 v. 3 A (twice), tapped 4 v., 2.5 v., 0/6; 250 v. to 6.3 v. 5 a. and 10 a., 17/6; 2 kv. 5 mA., 2 v. 2 a., 20/-; 350-0-350 v. 150 mA., 5 v. 3 a., 25/-; 55 v. 30 mA. (twice), 6.3 v. 3.2 a., 0/7; 220-0-220 v. 33 mA., 7.1 v. 8 a., 8.4 v. 10 a., 5 v. 3 a. each C.T., 15/6; 740-0-740 v. 165 mA., 470-0-470 v. 220 mA., 4 v. 8 a., C.T. (twice), 30/- (carr. 6/6). 350-0-350 v. 120 mA., 6.3 v. 4 a., 4 v. 2 a., 16/- (post 2/- each). METAL RECS. 600 v. 30 mA., 6/-, H.W. 400 v. 1 a., 22/6. 240 v. 250 mA., 10/-, FW 24 v. 2 a., 12/6. MOTORS, tiny 24 v. driving switch, 8/6. R.1155, coil packs, 12/6.

### FSD METERS—BRAND NEW—BOXED

FSD	Scale	Size	Type	Price
500 μA		3 1/2 in.	MC Fl.Rd.	25/-
1mA		3 1/2 in.	MC Fl.Rd.	18/6
2mA		2 in.	MC Pr.Rd.	10/6
10mA		3 1/2 in.	MC Fl.Rd.	7/-
10mA		4 1/2 in.	MC Fl.Rd.	20/-
20mA	200A	3 1/2 in.	MC Fl.Rd.	7/-
20mA	50A	3 1/2 in.	MC Fl.Rd.	7/-
30mA		2 in.	MC Pr.Rd.	6/-
40 & 120mA		2 in.	MC Fl.Sq.	7/6
100mA	200mA	2 in.	MC Fl.Sq.	5/-
100mA		3 1/2 in.	MC Fl.Rd.	7/-
200mA		2 in.	TC Fl.Sq.	6/-
200mA		3 1/2 in.	MC Fl.Rd.	7/-
250mA		3 1/2 in.	MC Fl.Rd.	7/-

List and enquiries, S.A.E. please! Terms: Cash with order. Postage extra. Immediate despatch.

Callers and Post  
W. A. BENSON (FW) 308 Rathbone Rd., Liverpool 13.  
Callers  
SUPERADIO (W'chapel) LTD., 116 Whitechapel, Liverpool 1. ROY 1130.

# Commercial TV

## GRAVE SHORTAGE OF TRAINED TECHNICIANS an opportunity for enterprising men

The Independent Television Authority's TV transmitters are due to start from London in September and from Birmingham and Manchester early in 1956. The whole Television Industry is growing rapidly. There is room for many more TRAINED men in transmitting stations, in producing and manufacturing companies and in the service and maintenance of receivers. Is this your opportunity? If you get up-to-date TV training NOW from ICS, you will find your services in great demand and you will establish yourself as a qualified technician.

I.C.S. offer courses of instruction in:

- TV TECHNOLOGY
- RADIO ENGINEERING
- RADAR
- ADVANCED SHORT-WAVE RADIO
- RADIO SERVICE ENGINEERING
- BASIC ELECTRONICS
- FREQUENCY MODULATION

I.C.S. will also coach you, until successful, for the following examinations: B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. and G. Telecommunications, etc., etc.

Fees include all books. POST THIS COUPON TODAY for free descriptive booklet on the subject which interests you.

INTERNATIONAL CORRESPONDENCE SCHOOLS (Dept. 170F), International Buildings, Kingsway, London, W.C.2.

REDUCED SUMMER TERMS—This coupon will save you money.

Please send booklet on.....


Name..... Age.....

(Block letters, please)

Address.....



## TAPE THE VESPA DECK

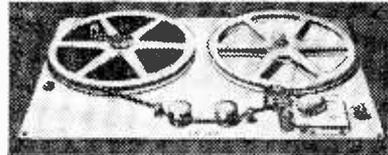

2-SPEED—3 1/2 in. & 7 1/2 in. TWIN TRACK

MODEL 521. Compact Deck. 7 1/2 in. x 1 1/2 in., 5in. reels. Kit, £7.10.0.

MODEL 721. Standard Deck. 10 1/2 in. x 1 1/2 in., 7in. reels. Kit, £8.10.0.

Easy to assemble, precision-machined parts, latest high-fidelity heads, first-class motors, full assembly instructions. Either model fully built and tested, 27/6 extra. Send stamp for full details.

E.W.A., 266, WARBRECK DRIVE, BLACKPOOL.

## COVENTRY RADIO

189, DUNSTABLE ROAD, LUTON, BEDS.

Phone: Luton 2677

The Quality Component Specialists offer you Kits of Parts for the following:—

	Manual
Osram "912" Amplifier	3/6
Mullard 10-watt Amplifier	3/6
The Coventry	
2-watt Amplifier	} 1/-
4-watt Amplifier	
6-watt Quality Amplifier	
The Coventry A.M. Tuner Unit	1/-
Denco F.M. Tuner Unit	1/6

Complete Component Price Lists will be supplied with each Manual. Have you had a copy of our 1954/5 60-page illustrated Component Catalogue, price 1/- plus 3d. postage?

THE VALVE SPECIALISTS

**Bentley Acoustic Corp. Ltd.**

38, CHALCOT ROAD, N.W.1.

PR1mrose 9090

024	6/-	98J7	8/-	956	3/6	KT41	7/-
1A5	6/-	68K7	6/-	1203	7/6	KT74	12/6
1D6	8/6	68L7	8/-	2031	10/6	KTW61	7/-
1E7	6/6	68N7	8/6	4033X	7/6	KTZ41	6/6
1G6	6/6	6887	7/6	5763	9/-	LP2	4/6
1L4	8/-	6U5(UC)	7/-	7183	2/6	M4	5/6
1LA4	9/6	6U5(10)	7/6	9001	5/6	M4	6/6
1LD3	7/6	6V8G	7/-	9002	5/6	M6	6/6
1LN5	6/-	6V8GT	7/6	9003	5/6	MU12	8/6
1R5	7/-	6X4	7/6	9006	5/6	N77	7/6
1S5	7/-	6X5	8/6	AC/FL	6/6	N142	10/-
3D6	2/6	7C5	8/-	3309	8/-	N150	10/6
2C26	4/-	6Y7	15/-	ACP4	8/-	OM5	7/6
2D13C	4/-	6Z4/84	8/6	ACT23	10/6	OM5A	10/6
2D21	8/6	7A7	8/6	ARF3(A)	5/-	OM5B	10/6
2X2	4/6	7AN7	11/-	ATP1	3/-	OC3	9/-
3A1	7/6	7B7	7/6	BL53	8/-	OL3	9/6
3D6	2/6	7C5	8/-	B309	8/-	PL1	3/6
3Q5	9/6	7C6	8/-	BL19	11/-	PC84	11/-
3S4	7/-	7I18	6/-	BL6	7/6	PCF80	11/-
3V4	7/-	7H7	7/6	CK505	6/6	PCL83	12/6
4D1	3/-	7Q7	8/-	CK523	6/6	Pen 25	6/6
5U4	8/-	7K7	8/6	CK525	6/6	Pen 48	7/-
5X4	10/-	7V7	8/6	D77	6/-	Pen 1340	6/6
5Y4	10/-	8A3	11/-	DA90	8/6	PL1	10/-
5Y3	7/6	8D2	2/6	DAP91	7/-	PL3	9/6
5Z3	8/6	10D1	4/6	DFP1	7/-	PL3	11/6
5Z4	8/6	10L1D11	10/-	DF72	8/-	PM13	6/6
6A3	10/6	12A5	6/6	DI30	15/6	PM12M	6/6
6A7	8/6	12AH7	12/6	DH11	8/-	PM256	6/6
6AB7	6/-	12AT6	10/6	DH142	10/-	PY90	10/-
6AB9	10/-	12AT7	8/-	DH150	10/-	PY81	10/6
6AC7	6/6	12AU7	9/-	DK92	7/-	PY82	7/6
6A13	6/6	12RA6	9/6	DK96	8/6	QP21	7/6
6ABGT	12/6	12B6	8/6	DL72	7/-	Q85/110	7/6
6AK3	7/6	12BL7	12/6	DL63	7/6		10/6
6AL5	6/-	12B1	30/-	DL94	7/-	Q875/20	10/6
6AM5	6/6	12H6	3/-	DL810	10/6	Q8150/15	
6AM6	6/6	12J5	8/-	EL148	2/-		10/6
6AQ3	8/6	12K3	8/6	EAS9	2/-	Q704/7	8/6
6AT8	8/-	12M7	7/6	EAT6	9/6	RK34	2/-
6B4	6/-	12M67	5/6	EAC91	9/-	RL37	6/6
6B7	7/6	12SJ7	8/-	EB34	2/-	RM1	12/-
6BA6	7/6	12SK7	8/-	EB41	11/-	R130	8/6
6B81	4/-	12SQ7	9/6	EB81	6/-	SP47	8/6
6B9M	4/6	12ST7	7/6	EB87	6/6	SP61	8/6
6BE6	6/6	12USG	7/-	EBC41	10/-	TP22	8/6
6BE6	6/6	14H7	10/6	EC91	7/-	TP220	17/6
6BQ5	11/-	14R7	10/6	ECS7	5/6	U16	12/-
6BR7	9/-	16A5	9/6	ECC32	10/6	U25	12/-
6BWS	7/6	17Z3	10/-	ECC35	8/6	U31	8/6
6BW7	10/-	18	8/-	ECC35	8/6	U50	7/6
6BX6	10/6	19H1	10/-	ECC81	9/-	U52	8/6
6C4	7/6	19Y3	8/6	ECC82	10/6	U78	7/6
6C6	6/6	26A6	8/6	ECC83	10/6	U142	9/6
6C8	8/-	25L6	8/6	ECC91	7/6	U159	9/6
6C10	10/-	20	7/6	ECC92	10/6	U163	10/-
6CH6	6/6	35L6	9/-	ECL80	10/-	U154	8/6
6D6	6/6	35W4	10/-	EF22	9/-	U319	8/6
6PG6	7/6	35Z4	8/6	EF26	4/6	U329	10/6
6PM6	8/-	35Z5	8/6	EF37	10/6	U404	9/6
6K7	6/6	42	8/-	EF74	12/6	UB341	9/6
6F8	7/-	50C3	10/-	EF39	6/6	UCH32	9/6
6F12	6/6	30L6	8/-	EP41	9/-	UCH81	12/6
6F17	9/6	50Y6	8/6	EF50(A)	8/-	UF41	8/6
6F23	6/6	57	8/6	EF50(B)	5/-	UF85	12/6
6F33	9/6	58	8/6	EF54	5/-	UL41	20/-
6G6	6/6	61BPT	15/-	EF35	12/6	UL14	20/-
6H6G	2/6	62DDT	10/-	EF73	10/6	UL46	10/6
6H6M	3/6	62TH	10/-	EF80	10/-	UU9	9/6
6J56	5/-	62VP	9/-	EP1	6/6	UY41	9/6
6J5M	6/6	64ME	10/6	EP3	7/6	VL84924	8/6
6J6	7/6	66UJ	8/6	EP5	7/6	VP17	8/6
6J7G	5/-	67PT	10/6	EL11	10/6	VP47	8/6
6J7GT	5/6	72	4/6	EL84	11/-	VP13K	8/6
6J7M	5/6	75	8/6	EL91	6/6	VP23	6/6
6K6	7/-	76	7/-	EM34	10/-	VR53	6/6
6K7G	5/-	77	8/-	EY51	11/-	VT501	6/6
6K7GT	6/6	78	8/-	EY91	7/6	VU111	3/6
6K7M	6/-	83	8/-	EY91	7/6	VU133	4/6
6K8G	8/-	85A3	10/6	EZ40	9/-	W150	9/6
6K8GT	8/6	121VP	9/-	EZ41	9/-	W150	9/6
6L6G	9/-	141TH	10/-	GU50	12/6	X66	7/6
6L7	7/6	210LF	8/-	H30	5/-	X142	8/6
6L83	10/-	218H	10/6	HL22	3/-	X150	10/6
6N7G	7/6	301	10/-	HL13C	7/6	XPW10	6/6
6N7M	8/-	311BU	10/6	HL23DD/6	6/6	XPY10	6/6
6Q7	8/6	451PT	10/6	HL41	7/6	XPY12	6/6
6R7	8/-	807	7/6	HL130	6/6	XH(1L5)	4/6
6S4	8/-	813	70/-	HY25A	7/6	XSG1.5	6/6
6SG7	10/-	832	25/-	KF35	9/-	Y63	7/6
6SG7	6/6	866A	15/-	KL23	9/-	Z77	6/6
6S17	6/-	885	10/6	KT2	5/-	Z719	10/3

All boxed and guaranteed. Post 6d. each. Same day service. Shop hours 8.30 to 5.30, Sat. 1 p.m. Why not phone or wire that urgent order for immediate despatch C.O.D.?


**76 PAGES 20 CIRCUITS**

**OUR 1955 SUPA-HANDBOOK "THE HOME CONSTRUCTOR" FOR 2/6 ONLY**

- incorporating these star attractions
- ★ 20 CIRCUITS—Superhets, T.R.F. Sets, Amplifiers, Feeder Units, Test Equipment, etc.
  - ★ SUPERHET—Full constructional details, supra-simplified layout and point-to-point wiring diagrams for building superhets.
  - ★ COIL PACK—Full constructional details for building a superhet coil pack.
  - ★ CAR RADIO—Full constructional details.
  - ★ BATTERY CHARGER, complete details for building a CHEAP CHARGER.
  - ★ RADIO GUN—Pages of information, Resistance Colour Code, Formulae, and "know-how."
  - ★ RADIO CONTROL—General information and list.
  - ★ RADIOGRAM Constructors' list.
  - ★ BOOKS—Comprehensive list of Radio Books.
  - ★ CATALOGUE—Profusely illustrated catalogue and price list of components and price list.
  - ★ SUPACOILS—Including:
    - cored coils. 10-30, 16-50, 30-75, 190-550, 800-2,000 metres.
    - 30 SUPACIL Pack—3/ each.
    - (L/M/S) SUPERHET PACK—All-wave fixing—recommender pack—single hole receivers—ready aligned. 47s. to above. For use with superhets having an R.F. stage. Ready aligned. 82/-.
- (Either of above can be supplied to order to cover any 3 wavebands EQUIPMENT LEAFLET 10 gives full easy instructions for YOU to make both these packs. 1/8. \* "The most helpful book in the Trade.")

**SUPACOILS (Dept. P7.)**  
21, Markhouse Road, London, E.17  
KEY 6866

**TELETRON SUPER INDUCTOR COILS**

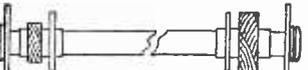


**FERRITE ROD AERIALS**



Wound on high permeability Ferroxcube rod. Medium wave 8/9. Dual wave 12/9. Type HAX. Selective crystal diode coil for tape and Quality amplifiers. High Q. Litz wound. \* Dust coated. 3/- ea. HAX.L. (L.W.) 3/6 ea. dual wave TRF. coils. matched pairs (as illustrated). 7/- pr. Transistor coils—L.F.T.'s, etc., etc. Available from leading stockists. Stamp for complete data and circuits. THE TELETRON CO. LTD. 266, Nightingale Road, N.9. ROW 5227

**Armstrong**  
Specialists for over 20 years in the manufacture of

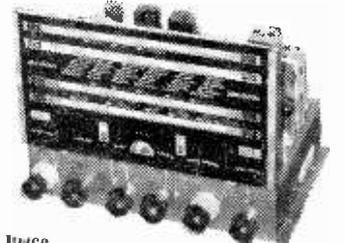**HIGHEST QUALITY CHASSIS**  
Hand made by Craftsmen



Price £23.18.0 (inc. tax)

**F.C. 48 RADIOGRAM CHASSIS**  
with provision for F.M. Tuner

- 8 VALVES including 2 double triodes.
- 8 WATTS output from push-pull tetrodes.
- NEGATIVE FEED BACK—20 dB. resulting in negligible distortion and high damping factor.
- BASS and TREBLE controls independent and continuously variable. LIFT as well as cut. Unique Thermometer Visual Indicators ensure positive setting of these controls.
- MAGIC EYE Tuning Indicator.
- 4 WAVE BANDS: 16-50, 49-120, 190-550, 900-2,000 metres.
- Large 4-colour illuminated dial.
- Overall size 12 1/2 in. x 9 in. x 9 1/2 in. high.

**F. M. 56 TUNER**



Price £21 (inc. tax)

- PERMEABILITY TUNING
- FREEDOM FROM DRIFT
- AUTOMATIC LIMITING
- MAGIC EYE TUNING

COVERAGE: 85-95 Mc/s. IMAGE REJECTION: 28 dB. I.F. REJECTION: 60 dB. R.F. Stage is coupled to a high stability frequency changer. This is followed by two I.F. Stages and a triple diode triode ratio detector and A.F. Stage. VALVES: Mullard ECC83, EF85, EF85, EAB60, EM34.

All our models are sold under full and unconditional money back guarantee of satisfaction. Prices include Purchase Tax. FREE PURCHASE facilities are available. Demonstrations at your local High Fidelity specialists or at our Showrooms in Holloway, special High Fidelity Demonstrations each Thursday evening from 7 p.m.

Write to us for descriptive literature mentioning P.W.  
**ARMSTRONG WIRELESS & CO. LTD.**  
TELEVISION  
Wartlers Road, London, N.7.  
Telephone: NORTH 3213

## RECEIVERS &amp; COMPONENTS

**ELECTROLYTICS**, capacity, voltage, size, type of mounting, price, post paid. 8, 450v, 1 x 2, clip, 2/-; 50, 12v, 4 x 1 1/2, tag, 1/6; 250, 12v, 3 x 1 1/2, wire, 2/3; 40, 40, 275v, 1 1/2 x 2, clip, 3/3; 24 + 24 + 16, 350/425, 1 1/2 x 2, clip, 4/9; 4, 150v, 2 x 1 1/2, clip, 1/4; 500, 12v, 2 x 1 1/2, tag, 2/3; 32 + 32, 350/425v, 1 1/2 x 2, clip, 5/-; 2, 450/525, 2 x 1 1/2, tag, 1/6; 8, 450v, 2 x 2, v-clip, 1/9; all alicans. Some with sleeves, all voltages, wkg. Surge where marked, new stock, guaranteed. Television Chassis, cadmium plated, steel, size 14 x 13 x 2 1/2, complete with 13 valveholders (9-B9A, 9-9A, 1-B9A Cer., 2-B7G Cer., 1-12v. Oct. Amph.), 20 various tag strips, cut away for metal rec. line trans, etc. 9/4 each, post paid; front and rear tube mounts to fit above chassis. 3/- pair, post paid. P.M. focus Magnets, wide angle, tetrode tube, fully adjustable, 12/-, post paid. Mains Trans. PRI. 0.210-240. SEC. 250-0.250v. 8ma. 6.3v. 2.5a; 6.3v. 0.6a. 12/-.

**RADIO CLEARANCE LIMITED**, 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

**MIDDLESBROUGH**. Largest stocks on N.-East coast. Radio/TV components, FM Kits, Gram. Cabinets, Tape Decks, Leak Amplifiers, Valves, etc. Callers only. **PALMERS**, 106, Newport Road. (Phone: 3096.)

**LOUDSPEAKERS** repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullingdon Rd., Oxford.

**SERVICE SHEETS**, T.V. and Radio, over 2,000 models, sale or hire; Valves and Components. S.A.E. with enquiries. **W. J. GILBERT**, 24, Frithville Gardens, London, W.12.

**OSMOR** for really efficient Coils, Coilpacks and all Radio Components as specified for many "Practical Wireless" circuits. See advert on page 403 for free circuits offer or send 5d. (stamps) to **OSMOR RADIO PRODUCTS LTD.** (Dept. PCT P403), 418, Brighton Road, South Croydon. (Tel.: Croydon 5148.9.)

**EVERYTHING** for Radio Constructors. List from **SMITH**, 98, West End Road, Morecambe.

**F.M. QUALITY RECEPTION**. Amplifiers, Valves, Condensers, Coils, Resistors, Transformers; everything for the amateur. Stamp for lists. Immediate service. **C. MICHEL**, 88A, Cleveland St., Euston Road, W.1. (EUS 8121.)

**ALUMINIUM CHASSIS** made to your requirements; 16 & 18 gauge; any quantity, large or small. We will be pleased to quote. **MACHINE CONTACTS**, Building 336, Hurn Airport, Christchurch, Hants.

**WALNUT** Radiogram Cabinets of distinction; stamp details. **R. SHAW**, 69, Fairlop Rd., E.11.

**BARGAIN SALE**. A number of small SW Receivers, cover all bands, fully calibrated spread, etc. and other gear; all excellent condition; in full working order; very cheap. All enquiries welcomed with s.a.e. for full descriptions. Box No. 254. c/o **PRACTICAL WIRELESS**.

**OSRAM 912 AMPLIFIER**, Soundmaster Tape Recorder, Denco FM Feeder Unit, all specified items stocked. Stamp details. **FRANKLIN & HALL**, 371, Havant Road, Farington, Portsmouth, Hants.

**RATES**: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1 - extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., Strand, London, W.C.2.

**AMERICAN RADIO** Plans and Devices. Now available. Hundreds of new and startling devices you can make. Only designs of this type available in UK. Receivers, walkie talkies, amplifiers, recorders, magic eye alarms, etc. etc. Full lists, data, illustrations Free of stamp. Send to-day. — A.P.S. (PW), Sedgford, King's Lynn.

**I.F. TRANS.**, 465kc, 6/6 per pair (post 9d.); 1mf 2,500v, d.c. wkg. Condenser, 4 1/2in. x 2 1/2in. x lin., 5/6; Electrolytics, 8 mf 500v 1/9, 32-32mf 275v 2/6, 25mf 25v 1/3; 40mf 450v 3/-; 12v 4-pin Vibrator. 6/6 (60/- doz.); 30H 175ma Choke (120 ohm) 10/-; 20H 100ma Choke (200 ohm) 7/6; Battery Charger, 2v, 6v and 12v, 1 amp, 35/-; Battery Eliminator, 90v, 15ma, and 1.4d. 125ma. 45/-.

**GLADSTONE RADIO**, 57, East St., Newton Abbot, Devon.

**R.F. UNITS**, Types 26 at 27/6, 25 at 12/6, 24 at 11/-; brand new with valves; post 2/6. **E.W.S. CO.**, 69, Church Road, Moseley, Birmingham.

**FM HIGH FIDELITY**; Kits and completed Receivers from £75/-. **BEL**, Marlborough Yard, N.19. (ARC 5078.)

**THE HIWAYMAN**. A new super Portable Radio for the home constructor; all-dry 4-valve superhet with Ferrite rod aerial; easy wiring diagrams and instructions, 1/6 (post 3d.). **RADIO EXPERIMENTAL PRODUCTS LTD.**, 33, Much Park St., Coventry.

## SITUATIONS VACANT

*The engagement of persons answering these advertisements must be made through the Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.*

**T/V AND RADIO**.—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert. etc., on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T/V; write for 144-page handbook—free. **B.I.E.T.** (Dept. 242G), 29, Wright's Lane, London, W.8.

**A.M.I.Mech.E., A.M.Brit.I.R.E.**, City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook—free. **B.I.E.T.** (Dept. 242B), 29, Wright's Lane, London, W.8.

**PYE TELECOMMUNICATIONS LTD.**, Ditton Works, Cambridge, offer excellent opportunities for Junior and Senior Development Engineers in the Electronics and Communications field. Duties include development work on H.F., V.H.F., microwave and recording equipments. Applications from persons possessing B.Sc. Higher National or Ordinary National Certificates are especially welcomed. Good facilities are available, however, to keen young men wishing to train and study in these fields. Pleasant working conditions in modern factory. Single accommodation available. Write, giving fullest details to Personnel Manager.

## VALVES

**ALL TYPES** of Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

**WANTED**, large or small quantities of new Valves, Loudspeakers, Components, Receivers, etc.; prompt cash paid. **R.H.S. LTD.**, 155, Swan Arcade, Bradford, 1.

**WANTED**, Valves, EY51, ECL80, KT61, 6U4GT, PL81, 35Z4, etc., etc.; prompt cash. **WM. CARVIS LTD.**, 103, North Street, Leeds, 7.

**VALVES**, new, tested and guaranteed: Matched pairs, 6V6G and GT. 17/- per pair; EF92, W77, 4/6; EB91, 6AL5, 6/6; 6F12, EF91, 6AM6, 6V6G, 6V6GT, 5763, 7/6; 6BE6, 6BW6, 6BR7, 6K8G, 6SL7GT, 6SN7GT, 6X4, 6X5GT, 8/-; 5U4G, 12AX7, 12AT7, 6BC41, UL41, UY41, X65, 8/6; PL82, PY82, 10/6; ECH42, UCH42, EF80, EF85, 11/6; ECL80, EY51, 12/6. 10ax Cable, 7v ohm, lin, stranded, 7d. yd.; and p. 6d. **R. J. COOPER**, 32, South End, Croydon, Surrey. (CRO 9186.)

**VALVE SALE** (see also page 432). EA50, 1/6; 3D6, 6H6M, 3/6; 1A5, 6A65, 6B8, 12SH7, SP61, SP41, Pcn46, 5/6; 6AL5, 6J5, 6K7, 6SK7, EB91, 6/6; OZ4, 6BA6, 6K6, DK91, DF91, DAF91, DL92, DL94, 7/6. WC Switches, 2p. 2-way, 3p. 2-way, 2/6; 2p. 6-way, 4p. 2-way, 4p. 3-way, 3/6; 3p. 4-way, 1p. 12-way, 3/6; High Stability 3w Res., 1% all values, 2/-; Specified Soundmaster Switches, 25/6; wide angle Focus Units, 25/-; Ion Traps, 2/6; Line Cord, 2a. 100 ohms per ft., 3a. 60 ohms per ft., 2-way 1/6 yd., 3-way 1/8 yd., Mains Droppers (3in. x 1 1/2in.), adj. sliders, 3 amp, 750 ohms, 2 amp, 1,000 ohms, 4/3; Mike Transf. 50:1, 3/9; Acid Hydrometer, Tin. x lin. dia., 4/6; VCR97, guar. full picture, £2; O/P Transf., small pentode tapped, 3/9; Ersin M'core Solder, 60/40, 16g, 5/6 lb., 4d. yd.; P.V.C. connecting wire, 8 colours, 2d. yd.; BTG v-holder and screening can, 1/6; Vholders, Octal Pax 4d., moulded 6d., EF50, B7G, 9d., B8A, B9A, 1/-; Slow Motion Drives, 4.1, 2/3; Coils, Wearite "P" 2/6, Osmor "2" 3/6; Variable Solid Dielectrics, 0001, 0003, 0005 mid, 3/6 ea. 8in. M.E. Speakers, 2,500 or 2,000 ohms field, with transf. new, boxed, 24/6; 10in. 10w, P.M. heavy duty, famous make, 3 ohm aluminium voice coil new, boxed, 39/6. **RADIO COMPONENT SPECIALISTS**, 307, Whitehorse Rd., West Croydon. (THO 1665.) Buses 133 or 68 pass door. Post 6d. Open all day Saturday. Lists s.a.e.

**VALVES WANTED**, all types, state quantity, condition, and price. **HERMES RADIO**, Glazebury, Manchester.

## WANTED

**WANTED**, Back Numbers **PRACTICAL WIRELESS**, issue Oct., 1953, to April, 1954. 23, Woodkind Hey, Bebbington, Cheshire.

## BOOKS

**I.P.R.E. TECHNICAL PUBLICATIONS**, 6,500 Alignment Peaks for Superheterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy. The Practical Radio Engineer, quarterly publication of the Institute, 2/- membership and examination data, 1/4; Secretary I.P.R.E., 23, Fairfield Rd., London, N.8.

**AMERICAN MAGAZINES.**—One year "Audio Engineering," 35/-, specimen copy, 3/6; "Popular Science," 31/6; "High Fidelity," 50/-; specimen copy, 4/6. Free booklet quoting others. **WILLEN LTD.,** Dept. 40, 101, Fleet Street, London, E.C.4.

**MAKING YOUR OWN ?** Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets, "How to use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 each; also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive lists of lenses, optical, radio and scientific gear, free for s.a.e. **H. W. ENGLISH,** Rayleigh Road, Hutton, Brentwood, Essex.

### EDUCATIONAL

**COVENTRY TECHNICAL COLLEGE.** Session 1955-56: Electronic Engineering.—Applications invited for entry to next three-year full-time course commencing September, 1955, from those requiring comprehensive training to an advanced level in Electronic Engineering, qualifying for technical posts in radio, telecommunications, television and industrial electronics. Syllabus will cover requirements of City and Guilds, Brit.I.R.E. and I.E.E. examinations. Entry age 16 or over. Application forms and further information from **PRINCIPAL,** Coventry Technical College, Educational Office, Council House, Coventry.

## FREE CATALOGUE

New guaranteed components by the leading makers. 58 pages illustrated on fine art paper. Over 2,000 items listed with over 100 photographic illustrations. Special features for service work. Orders dealt with day received.

## SOUTHERN RADIO & ELECTRICAL SUPPLIES

SORAD WORKS, REDLYNCH SALISBURY

Telephone: Downton 207

## MORSE CODE Training

Send for the Candler

### BOOK OF FACTS

It gives details of all Courses which include a Special one for acquiring amateur licence. **CANDLER SYSTEM CO.,** Dept. 510 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

**BUILD YOUR OWN TV** and learn about its operation, maintenance and servicing. Qualified engineer-tutor available whilst you are learning and building. Free Brochure from **E.M.I. INSTITUTES,** Dept. P.W.58, London, W.4. (Associated with H.M.V.)

**MERCHANT NAVY.** Train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" Postal Courses. Est. 36 years. S.A.E. for prospectus from Director, **THE WIRELESS SCHOOL,** 21, Manor Gardens, London, N.7.

**FREE!** Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M. Brit.I.R.E., City and Guilds R.T.E.B., and other Professional examinations. Train with the college operated by Britain's largest Electronics organisation; moderate fees. Write to **E.M.I. INSTITUTES,** Dept. PW.28, London, W.4.

**WIRELESS.** See the World as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Send 2d. stamp for prospectus. **WIRELESS COLLEGE,** Colwyn Bay.

# 160 or 240

Pity the poor output valve! These are the possible values of a 200 ohm 20" Cathode Bias Resistor. They can mean low output, distortion, a short unhappy life for your valve. Accuracy in all components is essential for 100% results. Fortunately you can check every resistor and condenser in a few seconds with the Radio Mail Res./Cap. Bridge at only 3/6 complete.

5 megohms—50,000 ohms 50 mfd.—.2 mfd. 100,000 ohms—1,000 ohms 1 mfd.—.01 mfd. 1,000 ohms—10 ohms .01 mfd.—.0005 mfd. (500 pF.)

**NO CALIBRATING.** An accurately calibrated panel with each kit. **EASILY ASSEMBLED.** Instructions, circuit and diagrams.

**OTHER KITS INCLUDE:**

Spot Frequency Sig. Gen., 35/- Tunable I.F. Aligner, 17/6. Inductance Bridge, 42/6. Audio-Frequency Bridge, 33/6. Twin Multi-omer, 25/-

Post and packing 1/6 on all kits.

Stamp for illustrated lists.

**RADIO MAIL, Dept. K,**

**6, RALEIGH ST., NOTTINGHAM.**

## ASTRAL RADIO PRODUCTS

'HOME RADIO,' 32 page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d.

**TRF COILS,** Specified for 'Bedside Pushbutton, 4' All Dry 3 Band, 'Pushbutton 4' etc., 6/6 pr., post 6d. Pushbutton Unit with modification data 7/-

**DUAL WAVE HF Coil,** Specified for 'Summer All Dry Portable,' 'Modern 1 Valver,' 'Modern 2 Valver,' 'B 7 G Battery Miniature,' etc., 4/3, post 3d.

**I.F.'s Miniature,** 1 1/2 x 1-1/16 round in cans. Extra high 'Q'. Special offer, 8/6 pr., post 6d.

**K COILS,** 'A.C.B.' pass 3, 3/3 each, post 6d. **FRAME AERIALS,** M.W., 5/-, post 4d. **H.F. Choke (Osmer Q.C.1),** 4/-, post 4d. **Crystal Set Coils, L. & M.W.,** 2/6, post 3d.

**82 Centurion Road, Brighton.**

**THE INSTITUTE of Practical Radio Engineers** Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY, I.P.R.E.,** 20, Fairfield Road, London, N.8.

**WIRELESS.**—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **B.S.T. LTD.,** 179, Clapham Rd., London, S.W.9.

**CITY AND GUILDS** (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. **B.I.E.T.** (Dept. 242A), 29, Wright's Lane, London, W.8.

**MERCHANT NAVY** Wireless School, Overseas House, Brooks' Bar, M/cr 16.

## RADIO AND TELEVISION COMPONENTS

All parts in stock for: **Viewmaster, Soundmaster, Teleking, etc.** Easy Terms available. 21d. stamp (only) for Catalogue.

**JAMES H. MARTIN & CO.,**  
FINSTHWAITE, NEWBY BRIDGE,  
ULVERSTON, LANCs.

**BENDIX RECEIVER TYPE RA10.** Brand New. 8 valves, all metal types, one each 6K3, 6M7, 6X5, 6C5, 6H6, 3 of 6SK7. Complete with all valves, only £3, 10.0, post 7/6.

**TRF RECEIVERS BATTERY.** Type RI545. 4 valves, type ARP12 "VP23" distress band. Coils could be added for Medium and Short Waves, with valves in wood case. New condition, 27/6, post 2/6.

**PACKARD BELL PRE-AMPS.** Brand New in original cartons, with instruction book and valves 6SL7, 2BD7, 12/-, post 1/6.

**WAVE METERS,** 150 mc/s to 220 mc/s. New condition with valves, 500 c.p.s. power pack, and 0-1 mA., 2 1/2 in. R.D.F.L. Meter in metal case, basis of a valve voltmeter, 35/-, post 5/-.

**MICROAMP METERS** 0 to 100  $\mu$ A. New boxed, with special scale, max.-min., 27/6, postage paid.

**RELAYS.** Post Office type, 3,000 series, 1,000 $\Omega$ -2,000 $\Omega$ , 3/6; 5,000 $\Omega$ -6,500 $\Omega$ , 6/-; 800 series, 250 $\Omega$ , 2/6.

**JACK PLUGS,** 2 standard fitting Jack plugs, 3-way, tip and ring, with 3 to 4 yds. of twin flex, screened, 3/6, post 6d.

**VALVES,** 6AK5 6/-, 6SS7A 6SK7, with .15 heater, 5/6, ARP12 4/-, EB34 1/6, VR92 1/6, VT104 PT15 2/6, 6V6G6 or CT 7/-, 6 for 1155, 3 VR100, one each VR93, VR101, VR102, 35/-.

**SWITCHES,** Yaxley type, 3 p, 6 w., 3 b, 4 p, 5 w., 2 b, 1 p, 10 w., 1 b, 6 p, 3 w., 2 b, at 1/8 ea.

**TOGGLEs,** 2 p, on, off and S.P.D.T., 250 v., 3 a., 1/- ea.

**PILOT'S HELMET MIKES,** 2/- ea. **BATES SURPLUS STORE**  
49, IVY ST., BIRKENHEAD, CHESHIRE  
By Main Tunnel Entrance.

## KENDALL & MOUSLEY LIMITED

Catalogue with Radio Hints and Advice for the Constructor.

**PRICE 1/-.** Refunded Double with First £1 order. Highest Quality Only.

**18, Melville Road, Edgbaston, Birmingham, 16.**

# F.M. IS HERE

Many of our Tuners for the B.B.C. V.H.F. programmes are in use up to 80 miles from Wrotham. All parts available to build the Tuner featured recently in the *Radio Constructor*.

Details of fringe area version also given.

Booklet complete with photos and point-to-point diagram	£	s.	d.
Chassis, fully punched	...	8	0
Coil Set	...	1	2
G.E.X.34 Crystal	...	6	6
Jackson Dial	...	14	6
Jackson V101 25 pF + 25 pF Jason Dial calibrated in Mc/s complete with bulbholders	...	1	7
All parts with Jason Dial less valves. Complete with nuts, screws, solder, tags	...	5	14

## THE JASON MOTOR & ELECTRONIC CO.,

328 (rear), Cricklewood Lane, London, N.W.2

Tel.: SPE 7050 Demonstrations given.  
Evening Demonstrations by Appointment

## RADIO/RADIOGRAM CHASSIS

BUILT TO HIGHEST TECHNICAL STANDARDS.  
FOR THE CONNOISSEUR OF QUALITY  
MUSIC REPRODUCTION

NEW RANGE OF MODELS WITH LATEST FEATURES  
FERRITE ROD AERIAL

MINIATURE (BYA) VALVES. STEEL CHASSIS

3 WAVEBANDS. A.C. MAINS, 200/250 VOLTS. ASSEMBLED  
AND READY FOR USE. FULLY GUARANTEED.


Model F.3. 5 valves chassis, 4 watt output. £13/18/3  
Wide range tone control

Model F.3. Push-Pull chassis. 7 valves, 6 watt output, separate  
bass and treble controls £17/17/9

Negative feedback applied  
from output transformer  
secondary.

Gram switching  
on wave-  
change switch.  
Plug-in  
connections for  
pick-up,  
speaker, gram  
motor.

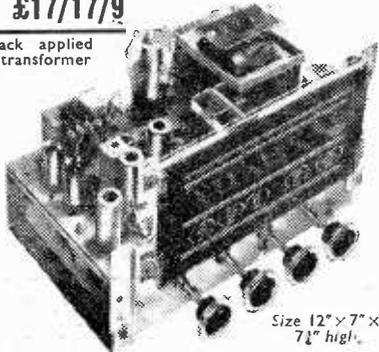Choice of horizontal  
or vertical  
dial.  
Also magic eye  
fitment, dial  
escutcheon,  
matched 8in.  
and 10 in.  
speakers.



DETAILED LIST AND DIMENSIONS.

DIRECT FROM THE MANUFACTURER

**THE DULCI CO. LTD.,**

93, VILLIERS RD., LONDON, N.W.2. Telephone: Willesden 6678

FULL TRADE FACILITIES

## BUILD THIS RADIO FOR 49/6



Build this exceptionally sensitive twin-triode radio. Uses unique assembly-system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all Medium and Long Waves—uses one only all-dry battery which lasts many months, as H.T. consumption is only 1 to 1 1/2 mA. Ideal for Bedroom, Garden, Holidays.

etc. Read a few of our many unsolicited testimonials: Mr. Robinson of Harrogate, writes: "The set is working very well. It gets all the stations I need." It is also very loud "I am greatly pleased with it. Will you please send me details of anything else you have." Mr. Norton of Oxford, writes: "Yesterday evening on the medium waveband, I counted 32 separate stations; I am very pleased with the set, which is well worth the money." Mr. Beckwith, of London, W.3, writes: "I must say that I was rather surprised and very pleased indeed with the performance for such a small set. I do not think there is anything on the market to beat it! The tone is perfect, reception very clear, and the stations just roll in. Up to now I have received about 20 stations and all very clear. I may add I am more than satisfied."

Build this powerful, long-range set. Total cost of all parts, 49 6 post free with free pocket phone. All parts sold separately. (Parts lists, and full set of easy-to-follow, crystal-clear plans, 2/-). Note.—We stock full range of components and valves. Orders despatched by return. Overseas orders welcomed—but regret no C.O.D. abroad. SEND TO-DAY!

**BRIGHTON RADIO & TELEVISION CO.**  
(DEPT. 69), PRESTON ST., BRIGHTON, 1

## The Walk-around Shop

### MULTIRANGE AC/DC TESTMETER of well known American manufacture.

This testmeter has a basic movement of 400 microamps and is calibrated for use on the following ranges:—

A.C. and D.C. Volts 0 to 5,000 v. in 6 switched ranges.  
D.C. Current. Ranges 0-1 mA, 1-10 mA, 10-100 mA and 100 mA-1 A. Use as an OHMMETER (Resistance Measurements). .1 ohm to 1 megohm.

Decibels from -10 db to +15 db. For line load impedances from 1 to 1,000 ohms (directly calibrated for 500-ohm line).

This instrument is contained in a well-finished polished wood case with leather carrying handle. Leads and test probes are housed in the case which measures 6 1/2 in. x 6 1/2 in. x 4 1/2 in.

All meters fully tested before despatch.  
Supplied complete with moulded test probes, full operating instructions and circuit diagram. £4. 19. 0  
(Packing and postage 3/-)

70 C.M. UNIT. Brand New, consisting of pair of tuned lines; 2 acorn valveholders, coarse and fine tuning. Suitable for mixer or oscillator unit. Size 5 in. x 3 1/2 in. x 3 in. 6 6. Post paid.

### ABSORPTION WAVEMETER

In metal case, 3 1/2 in. x 4 1/2 in. x 5 1/2 in. with calibrated dial 0-100 covering approximately 190-210 Mc/s; 80 volt Neon tube. 6 6. post paid, or with transit case, 9 -, post paid.

SPECIAL PURPOSE VALVES: 807 R.C.A. (boxed) 6 6; 6C4, 5 -; 6U4G, 7 6; 713A V.H.F. triode (D or knob type), 9 -; 6146A, Disc Sealed triode (Lighthouse Tube), 25 -; 6SN7, 6 9; 6SL7, 6 9; 6X07, 7 -; VT52 (EL32), 7 -; T111 (VT501), 5 -. NOTE: Prices include postage.

NEON TUBES. Miniature bayonet type. 80 v. striking (1 megohm in series for mains), 1 6. Post paid.

BENDIX COMMUNICATIONS RECEIVER RA-101R. £5.10.0 and 10 -, carriage.

NOTE: ORDERS AND ENQUIRIES TO DEPT. 'P'

**PROOPS BROS. LTD.** Telephone LANgham 0141.  
52 Tottenham Court Road, London, W.1.

Shop Hours: 9-6 p.m. Thursday: 9-1 p.m. Open all day Saturday.

Practical Wireless

**BLUEPRINT SERVICE**

**PRACTICAL WIRELESS**

*No. of  
Blueprint*

*No. of  
Blueprint*

**CRYSTAL SETS**

- 1 6d. each
- 1937 Crystal Receiver ... PW71\*
- The "Junior" Crystal Set ... PW94\*
- 2s. each
- Dual - Wave "Crystal Diode" ... PW95\*

**STRAIGHT SETS**

**Battery Operated**

- One - valve : 2s. each
- The "Pyramid" One-valver (HF Pen) ... PW93\*
- The Modern One-valver ... PW96\*

- Two-valve : 2s. each.
- The Signet Two (D & LF) ... PW76\*

- 3s. each.
- Modern Two-valver (two band receiver) ... PW98\*

- Three-valve : 2s. each.
- Summit Three (HF Pen, D, Pen) ... PW37\*

- The "Rapide" Straight 3 (D, 2 LF (RC & Trans)) ... PW82\*

- F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ... PW87\*

- 3s. each.
- The All-dry Three ... PW97\*

- Four-valve : 2s. each.
- Fury Four Super (SG, SG, D, Pen) ... PW34C\*

**Mains Operated**

- Two-valve : 2s. each.
- Selectone A.C. Radiogram Two (D, Pow) ... PW19\*

- Three-valve : 3s. 6d. each.
- A.C. Band-Pass 3 ... PW99\*

- Four-valve : 2s. each.
- A.C. Fury Four (SG, SG, D, Pen) ... PW20\*
- A.C. Hall-Mark (HF Pen, D, Push Pull) ... PW45\*

**SUPERHETS**

- Battery Sets : 2s. each.
- F. J. Camm's 2-valve Superhet ... PW52\*

- Mains Operated : 3s. 6d. each.
- "Coronet" A.C.4 ... PW100\*
- AC/DC "Coronet" Four ... PW101\*

**SHORT-WAVE SETS**

**Battery Operated**

- One-valve : 2s. each.
- Simple S.W. One-valver PW88\*
- Two-valve : 2s. each.
- Midget Short-wave Two (D, Pen) ... PW38A\*

- Three-valve : 2s. each.
- Experimenter's Short-wave Three (SG, D, Pow) ... PW30A\*

- The Perfect 3 (D, 2 LF (RC and Trans)) ... PW63\*

- The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen) ... PW68\*

**PORTABLES**

- 1s. 6d.
- The "Mini-Four" All-dry (4-valve superhet) \*

**MISCELLANEOUS**

- 2s. each.
- S.W. Converter-Adapter (1 valve) ... PW48A\*
- (2 sheets), 7s. 6d.

- The P.W. 3-speed Autogram ... \*
- The P.W. Electronic Organ (2 sheets), 7s. 6d. \*

**TELEVISION**

- The Practical Television Receiver, (3 sheets), 10/6
- The "Argus" (6in. C.R. Tube), 2/6\*
- The "Super-Visor" (3 Sheets) 7/6\*
- The "Simplex" ... 3/6\*

*All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94 are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.*

**AMATEUR WIRELESS AND WIRELESS MAGAZINE**

**STRAIGHT SETS**

**Battery Operated**

- One-valve : 2s.
- B.B.C. Special One-valver ... AW387\*

**Mains Operated**

- Two-valve : 2s. each.
- Consoelectric Two (D, Pen), A.C. ... AW403

**SPECIAL NOTE**

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of  
Blueprint*

**SHORT-WAVE SETS**

**Battery Operated**

- One-valve : 2s. each.
- S.W. One-valver for American ... AW429\*

- Two-valve : 2s. each.
- Ultra-short Battery Two (SG, det Pen) ... WM402\*

- Four-valve : 3s. each.
- A.W. Short Wave World-beater (HF Pen, D, RC Trans) ... AW436\*

- Standard Four - valver Short-waver (SG, D, LF, P) ... WM383\*

**Mains Operated**

- Four-valve : 3s.
- Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ... WM391\*

**MISCELLANEOUS**

- Enthusiast's Power Amplifier (10 Watts) (3/-) WM387\*
- Listener's 5-watt A.C. Amplifier (3/-) ... WM392\*
- De Luxe Concert A.C. Electrogram (2/-) ... WM403\*

**QUERY COUPON**

This coupon is available until July 4th, 1955 and must accompany all Queries, sent in accord with the notice on page 441.

PRACTICAL WIRELESS, July, 1955.

**MAXI-Q**  
REGD.

## AND NOW THERE ARE NINE

THE CP.3F/G BEING THE LATEST ADDITION AND AGAIN IN RESPONSE TO POPULAR REQUESTS.

This 4 waveband Coil Pack complete with Gram position is for use with a 500pF. 2-Gang, Condenser. It covers the standard Long, Medium and Short wavebands with the addition of the Band 50/160 metres, 1.85/6 Mc/s. This covers the Trawler Band, 105/160 metres, Shipping 68/74 metres, Aeronautical 52/55 and 95/105 metres, and the 80 and 160 metres Amateur Bands. The CP.3F/G comprises of Aerial and Oscillator coils complete with iron dust tuning cores, Wavechange switch and Mica Compression Trimmers mounted on an aluminium plate. Fixing is effected by an additional nut on the Wavechange switch. The I.F. is 465Kc/s. For use with any standard frequency changer.

Retail Price : 57/- plus 19/- P.T.—Total 76/-.

The following Coil Packs are also available.

CP.3/F. As above less the Gram position.

Retail Price : 49/- plus 16/4 P.T.—Total 65/4.

CP.3/370 and 500pF. Three Waveband Coil Packs for use with either 370 or 500pF. tuning condensers.

Retail Price : 32/- plus 10/8 P.T.—Total 42/8.

CP.3/G. Three Waveband Coil Pack for 500pF. tuning condensers with provision on the Wavechange switch for gramophone position.

Retail Price : 39/- plus 13/- P.T.—Total 52 -.

CP.4/L and CP.4/M. These compact 4-station Coil Packs are available for either 1 Long and 3 Medium wave stations (CP.4/L) or 4 Medium wave stations (CP.4/M).

Retail Price : 25/- plus 8/4 P.T.—Total 33/4.

CP.4L/G and CP.4M/G. As above but with provision for gramophone pick-up on the Wavechange switch. Retail Price : 31 - plus 10/4 P.T.—Total 41/4. See Technical Bulletin DBT.9 for details of all coil packs, I/6.

Obtainable from all reputable stockists or in case of difficulty direct from works. Send 1-2 in stamps for General Catalogue.

Retail Price : 25/- plus 8/4 P.T.—Total 33/4.

CP.4L/G and CP.4M/G. As above but with provision for gramophone pick-up on the Wavechange switch. Retail Price : 31 - plus 10/4 P.T.—Total 41/4. See Technical Bulletin DBT.9 for details of all coil packs, I/6.

Obtainable from all reputable stockists or in case of difficulty direct from works. Send 1-2 in stamps for General Catalogue.

**DENCO (CLACTON) LTD.** 357/9 Old Road, Clacton-on-Sea, Essex


Stop Press : " Osram " " 912 " and " Mullard " " 5-10 " Amplifier Chassis and Bronze finished Front Panel—21/- each. The " Practical Wireless " " Fury Four " uses the " Maxi-Q " Yellow (3/11) and Green Chassis Mounting Coils (4/9) (please state frequency range when ordering). Also available are the " Fury Four " Chassis and Paxolin Front Panel—19/6. Long and Medium wave T.R.F. Coils, wound on Polystyrene Formers—9/- per pair IFF.1, Improved 465 Kc/s. I.F. Filter, wound on Polystyrene Former—4/1.

Obtainable from all reputable stockists or in case of difficulty direct from works. Send 1-2 in stamps for General Catalogue.

Obtainable from all reputable stockists or in case of difficulty direct from works. Send 1-2 in stamps for General Catalogue.

Obtainable from all reputable stockists or in case of difficulty direct from works. Send 1-2 in stamps for General Catalogue.

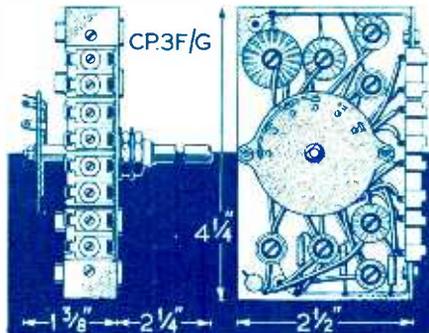Obtainable from all reputable stockists or in case of difficulty direct from works. Send 1-2 in stamps for General Catalogue.



## THE "WEYRAD" SIGNAL GENERATOR

AN INSTRUMENT OF HIGH ACCURACY AT LOW COST



- Coverage 100 Kc/s-70 Mc/s (on fundamentals).
- Accuracy better than  $\pm 2\%$  on all ranges.
- Large, clearly calibrated scale.
- Modulated or C.W. output.
- 500 c/s A.F. source.
- S.G.M.I.—A.C. mains operation. Double wound, varnish-impregnated transformer, tapped 210/225 250 volts.
- S.G.B.I.—All dry battery operated.
- All components are by well-known manufacturers ensuring maximum reliability.
- Both types in quantity production.
- Illustrated leaflet available, price 2d.

**WEYMOUTH RADIO MANUFACTURING CO., LTD.**

CRESCENT STREET, WEYMOUTH, DORSET