

• A NOVEL C/R BRIDGE •

PRACTICAL

JANUARY

1956

EDITOR: F.J. CAMM

WIRELESS



You can own the PLAYTIME PLUS

on the **M.O.S. PERSONAL CREDIT PLAN**

Simple to operate—Single joystick control for all operations. Gives a full hour's playing time. Elegant 2-tone suitcase 12 in. x 10 in. x 5 in. Complete with High Fidelity Microphone and 1 hour spool of tape. Price



35 gns.

THE M.O.S. PERSONAL CREDIT PLAN

Used by all discerning and careful buyers, the M.O.S. Personal Credit Plan provides easy repayment terms coupled with low service charges. For example, you can buy the above tape recorder in this way and the deposit is still only 15%. Please let us know your requirement and we will quote details by return. Send your deposit with your order, allowing sufficient for carriage and packing extra, in order to secure your needs. Please specify over what period (up to a maximum of 18 months) you wish to repay and the necessary forms will be sent to you immediately.

CREDIT SALE TERMS are also available if you prefer these. Repayment by 9 equal monthly instalments. Send for details.

M.O.S. Personal Credit Plan facilities are available on all equipment sold by us.

E. & G. MAIL ORDER SUPPLY CO. The Radio Centre, 33, Tottenham Court Road, London, W.1. MUSEum 6667.

CONSTRUCTORS build these at

DOWN-TO-EARTH PRICES

PERSONAL PORTABLE RADIO 30/-

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Components Price List



1v SHORT-WAVE RADIO

- ★ Covers 10-100 metres.
- ★ World-wide reception
- ★ Low drain valve.
- ★ Picture diagram and instructions for beginners.
- ★ Assembling time 1 hr.



This 1 valve S.W. receiver can be built from our list of components for 30/-, including valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required. All components can be purchased separately and are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list to :-

R.C.S. PRODUCTS (RADIO) LTD
11 OLIVER ROAD, LONDON, E.17. Mail order only.

Finest Soldering? Always specify **ERSIN MULTICORE to be precise**

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SIZE 1 CARTON
4 specifications for radio enthusiasts.

5/-



HANDYMAN'S CARTON
Sufficient for 200 average joints. 6d.

TAPE SOLDER
MELTS WITH A MATCH!
Real tin/lead solder containing cores of Ersin Flux. Needs no soldering iron or extra flux. 1/- PER CARD



Bib GIFT PACK

The ideal present for any electrician or handyman—a Bib Stripper, Tape Solder and Insulated Screwdriver on a presentation card—all for 5/-

MANUFACTURERS ARE INVITED TO WRITE FOR DETAILS OF BULK PACKS AT BULK PRICES

MULTICORE SOLDERS LTD.

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS (BOXMOOR 3836)

SOLDERING ?

You can't beat a

PRIMAX!

72/6 post free



Balanced grip soldering gun in unbreakable case

Can be used intermittently without overheating. Easy soldering on hard-to-reach jobs. Ready for action in 6 seconds. Permanent alloy tip—lasts indefinitely with normal use and care. Weighs only 24 ozs. Special loop for hanging. Available in 110, 200/220, 220/250 v. for A.C. only. 50/60 cycles (60 w.).


The ideal tool for any Radio—TV—Telephone Mechanic or Amateur. **One Year's Guarantee**

Sole Distributors :-

S. KEMPNER LTD.

(Dept. P.W.), 29, Paddington St., London, W.1
Phone : HUNTER 0755

What's all this about Hi-g?

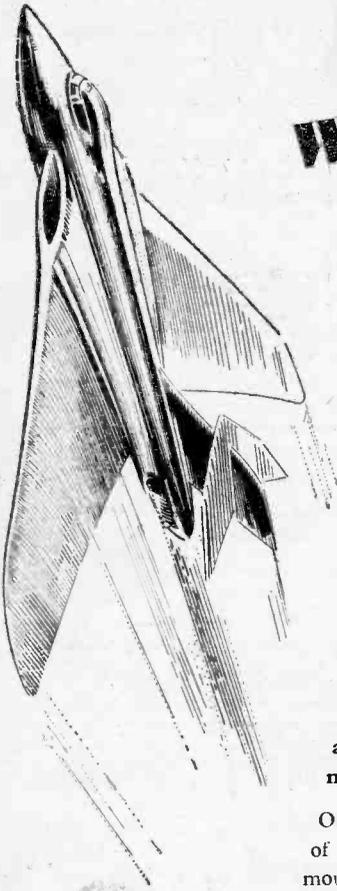

"g" is the symbol for acceleration which, to the technical, is defined as the differential of velocity with respect to time. More simply this means the rate of change of speed.

When "g" is too great, damage will be done. A locomotive leaves the rails when it takes a curve too fast. At only 6 "g" a pilot blacks out when he pulls out of a dive; at 20 "g", which is very much more than any plane can possibly encounter, the plane would disintegrate.

The stylus tip of a pick-up is subjected to the same acceleration but to an infinitely greater extent. The undulations of a record groove cause the stylus to vibrate as much as 10,000 times per second or more. It moves to one side of the groove, stops, moves to the other, stops again and so on throughout the record. **The accelerations acting upon the stylus tip are measured in "g" and with modern recordings may be well over 1000 "g".**

Obviously a light freely suspended stylus will follow rapid changes of direction in record grooves more easily than a heavy, stiffly mounted one. On a heavily recorded record a "stiff" pick-up will tear through record grooves or even jump right out of them. Result: rapid record and stylus wear and poor reproduction.

Correct tracking of modern electrical recordings with their great musical and dynamic range calls for pick-ups specially designed to cope with very high "g". They are available, after much patient research and development, under the name "Hi-g". **ACOS "Hi-g" pick-ups perform perfectly at any multiple of "g" they are called upon to meet,** representing a truly revolutionary advance in pick-up design. If you want your valuable records to reproduce as well as the makers intended—and to go on doing so for a long time—use an "ACOS Hi-g" pick-up.

(Write for a free copy of the new Cosmocord booklet "The ABC of Hi-g".)



... always well ahead



ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

COSMOCORD LIMITED • ENFIELD • MDDX • Tel: ENField 4022

PREMIER RADIO COMPANY

B. H. MORRIS & CO., (RADIO) LTD.

OPEN TILL
6 P.M. SATURDAYS

(Dept. P.W.) 207, EDGWARE ROAD, LONDON, W.2


Telephone:
AMBASSADOR 4033
PADDINGTON 3271-2

BUILD THESE NEW PREMIER DESIGNS

3-BAND SUPERHET RECEIVER

MAY BE BUILT FOR **£7.19.6** Plus 2/6 Pk. & Carr.

Latest type Superhet Circuit using 4 valves and metal rectifiers for operation on 200/250 volts A.C. mains. Waveband coverage — short 18-50 metres, medium 180-550 metres, and long 900-2,000 metres. Valve line-up 6K9 freq. changer 6K7 1P, 6K7 Detector AVC and first AF. 6V6 output. The attractive cabinet to house the Receiver size 12in. long, 6 1/2in. high, 5 1/2in. deep can be supplied in either WALNUT or IVORY BAKELITE or WOOD. **INSTRUCTION BOOKS 1/- each, (post wiring diagrams, also a detailed Stock**

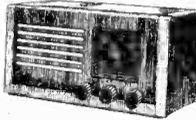

TRF RECEIVER

MAY BE BUILT FOR **£5.15.0** Plus 2/6 Pk. & Carr.


The circuit is the latest type TRF using 3 valves and Metal Rectifiers for operation on 200/250 A.C. mains. Waveband coverage is 180/550 metres on medium wave and 800/2,000 metres on long wave. The dial is illuminated and the Valve line-up is 6K7 H.P. Pentode 6J7 Detector and 6V6—Output. **List of priced components.**

illuminated and the Valve line-up is 6K7 H.P. Pentode 6J7 Detector and 6V6—Output. **List of priced components.**

4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pk. & Carr.

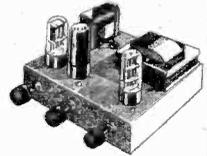Valve line-up 6SL7, 6V6 and 6X5. FOR A.C. MAINS 200/250 VOLTS. Suitable for either 3-ohm or 15-ohm Speakers. Negative feedback. Any type of pick-up may be used. Overall size 9 x 7 x 3in. Price of Amplifier complete, tested and ready for use. **£5.5.0 plus 3/6 pkg. and carr.**



CABINETS—PORTABLE

Model PC/1

Brown Rexine covered. 15 1/2in. Overall dimensions 15in. x 13 1/2in. x 5in. Clearance under lid when closed 2 1/2in.

Model PC/2

Grey Lizard Rexine covered. 45 1/2in. Overall dimensions 15in. x 13in. x 6in. Clearance under lid when closed 3in.

Model PC/3

Rexine type covering in various colours. 69 1/2in. Overall dimensions 16 1/2in. x 14 1/2in. x 10 1/2in. Clearance under lid when closed 6 1/2in.

All the above Cabinets are supplied with Panel, Carrying Handle and Clips. Packing and Postage 2/6.

Send for details of the Premier Wide angle Telesistor design which may be built for £30.


ALL-DRY BATTERY PORTABLE RADIO RECEIVER

MAY BE BUILT FOR

£7.8.0

Plus 2/6 Pk. & Carr.

4 miniature Valves in a Superhet Circuit covering medium and long waves. Rexine covered Cabinets 11 1/2in. x 10in. x 5 1/2in. in two contrasting colours. Wine with Grey Panel, or Blue with Grey Panel, please state choice when ordering. The SET MAY BE USED EVERYWHERE—home, office, car or holiday. **INSTRUCTION BOOK, 1/6 (Post free) which includes Assembly and wiring diagrams, also a detailed Stock List of priced components.**

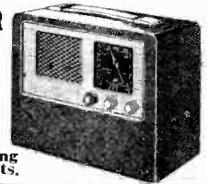

DECCA MODEL 37A DUAL SPEED RECORD PLAYER Includes turn over crystal pick-up with sapphire stylus and a light-weight, plastic, spring-balanced arm. Heavy gauge pressed steel case with brown enamel finish in good quality for operation on A.C. mains 200/250 v. 50 c.p.s. Supplied complete, **£6.19.6.** Plus pkg. and carr. 5/-. ***SEND 2 1/2d. STAMP FOR OUR 1955 CATALOGUE**

!! HOME CONSTRUCTORS !!

You can assemble the *Stern's* Fidelity Tape Recorder for only **£40** !!! IT ONLY NEEDS CONNECTING UP !!!




This 2-speed Twin Track Recorder although supplied at a Genuinely Low Price, provides absolute Fidelity Recordings, and in addition to being completely dependable has a performance at least equal to Recorders marketed at a far higher price. The actual assembly of the Recorder is simple, and only involves a few connections. The Truvox Tape Deck and the Quality Amplifier are supplied tested and ready for use, and all that is required to complete the Recorder is to connect the two together (a connection chart is supplied for this purpose) and secure them by the screws provided into the Attache Case. The items illustrated and described below form the complete equipment.

SEND S.A.E. FOR DESCRIPTIVE LEAFLET INCLUDING PRICE DETAILS & H.P. TERMS

TRUVOX TAPE DECK

MODEL Mk. III/TR7u

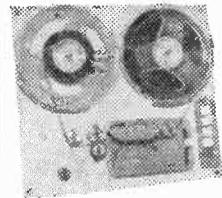This is Truvox's new "small" design being only 14in. x 13in. The whole instrument is built to close engineering limits resulting in the minimum of "wow" and "flutter" values. It will play the NEW



PRE-RECORDED TAPES and tapes up to 1,200ft.


SCOTSBOY MAGNETIC RECORDING TAPE Supplied complete with a 1,200ft. reel of Scotsboy Tape. In addition, the Recorder will take all standard makes of tapes.

PORTABLE ATTACHE CASE

This, as may be judged from the illustration above, is a neat, compact and attractively finished case, being covered with maroon rexine and having an ivory coloured speaker escutcheon. It contains concealed pockets to accommodate the Microphone, Mains Lead and a spare 1,200ft. reel of tape.

MODEL TRF QUALITY AMPLIFIER

This amplifier has been expressly designed to meet the requirements of enthusiasts for fidelity reproduction, and in particular to CORRECTLY operate the above TRUVOX DECK. It is supplied complete with a matched Elliptical 3 ohm P.M. Speaker, it incorporates an efficient Tone Control arrangement and has a Magic Eye Level Indicator (Operative on Record). It can also be used as a general purpose Amplifier for high quality reproduction of gramophone records direct from a Gram Unit.

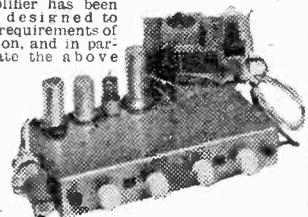

MODEL MIC33/1
ACOS CRYSTAL MICROPHONE
A highly sensitive Mike which accurately matches the input arrangement of the Amplifier.


It can be supplied complete and ready for use for **£43.** H.P. Terms available.

STERN RADIO LTD.


109 & 115, FLEET STREET, E.C.4

Tel.: CENTRAL 5812-3-4.

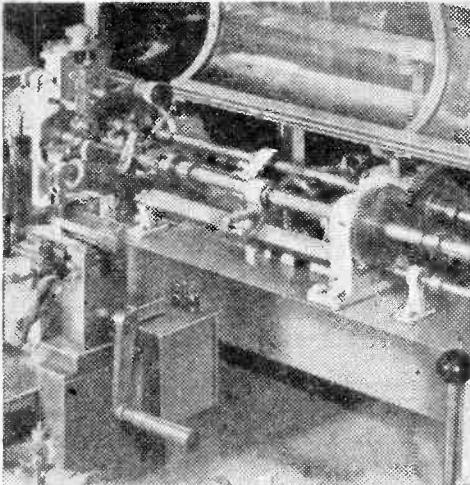MODERN MINIATURE VALVE PRODUCTION...an **Osram** series



Grid winding machine

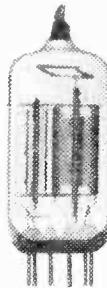


X-Ray photograph of modern miniature valve, Osram LN 3L9

Precision tooling

In high-grade miniature valve production, tooling is an art in itself. Closer clearances, finer gauge wires, even the electrodes themselves all require most careful handling. The assembly of Osram miniature valves is carried out by skilled workers under most favourable conditions. Every detail of production has been studied to make Osram miniatures pass the most exacting tests. This overall care — from raw materials to the finished product — results in these valves being specified by discriminating designers.

Osram VALVES — *characteristically good*

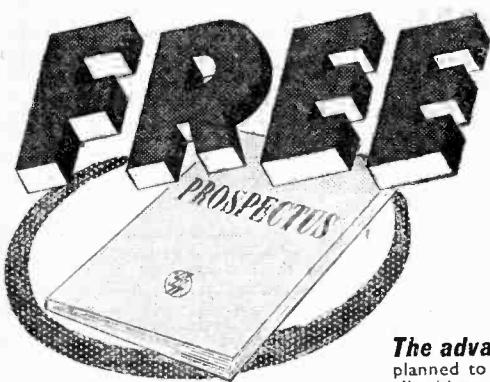THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

NEW LEARN THE PRACTICAL WAY
With many of our courses we supply actual equipment. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from 15/- per month

POST THIS COUPON TODAY


Send without obligation your FREE book, E.M.I. INSTITUTES, Dept. 32K, 43 Grove Park Road, London, W.4. Phone: Chiswick 4417/8.

NAME _____
ADDRESS _____
JAN. _____
SUBJECT(S) OF INTEREST _____

EMI INSTITUTES
The only Postal College which is part of a world-wide Industrial Organisation

THE "WEYRAD" SIGNAL GENERATOR

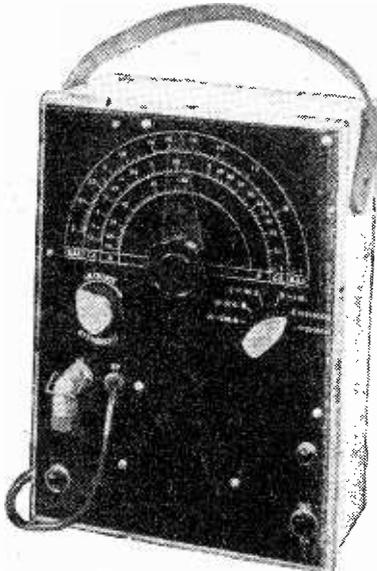AN INSTRUMENT OF HIGH ACCURACY AT LOW COST



- Coverage 100 Kc/s-70 Mc/s (on fundamentals).
- Accuracy better than $\pm 2\%$ on all ranges.
- Large, clearly calibrated scale.
- Modulated or C.W. output.
- 500 c/s A.F. source.
- S.G.M.I.—A.C. mains operation. Double wound, varnish-impregnated transformer, tapped 210/225/250 volts.
- S.G.B.I.—All dry battery operated.
- All components are by well-known manufacturers ensuring maximum reliability.
- Both types in quantity production.
- Illustrated leaflet available, price 2d.

WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET

COPPER INSTRUMENT WIRE

S. W.G.	ENAMELLED		TINNED		COTTON COVERED		SILK COVERED	
	2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.	4 ozs.
16	1/8	2/6	1/8	2/6	1/8	2/6	1/8	2/6
17	1/8	2/7	1/8	2/7	1/8	2/7	1/8	2/7
18	1/8	2/8	1/8	2/8	1/8	2/8	1/8	2/8
19	1/9	2/9	1/9	2/9	1/9	2/9	1/10	2/11
20	1/9	2/10	1/9	2/10	1/9	2/10	1/11	3/11
21	1/10	2/11	1/10	2/11	1/10	2/11	2/-	3/3
22	1/10	3/-	1/10	3/-	1/10	3/-	2/1	3/5
23	1/11	3/1	1/11	3/1	1/11	3/1	2/2	3/7
24	1/11	3/2	1/11	3/2	1/11	3/2	2/2	3/8
25	2/-	3/3	2/-	3/3	2/-	3/3	2/3	3/10
26	2/-	3/4	2/-	3/4	2/1	3/5	2/4	4/-
27	2/1	3/5	2/1	3/5	2/2	3/6	2/5	4/2
28	2/1	3/6	2/1	3/6	2/2	3/8	2/6	4/4
29	2/2	3/7	2/2	3/7	2/3	3/10	2/7	4/6
30	2/2	3/8	2/3	3/10	2/4	4/-	2/8	4/8
31	2/3	3/9	2/4	4/-	2/5	4/1	2/8	4/10
32	2/3	3/10	2/5	4/2	2/5	4/2	2/11	5/2
33	2/4	3/11	2/6	4/3	2/7	4/5	3/2	5/8
34	2/4	4/-	2/7	4/6	2/8	4/8	3/3	5/10
35	2/5	4/1	2/8	4/8	2/10	4/11	3/5	6/2
36	2/5	4/2	2/10	4/11	2/11	5/2	3/7	6/6
37	2/6	4/4	2/11	5/2	3/4	6/-	3/9	6/9
38	2/7	4/6	3/2	5/5	3/9	7/-	3/11	7/2
39	2/8	4/8	3/2	5/8	4/3	8/-	4/2	7/8
40	2/9	4/10	3/4	6/-	4/10	9/-	4/5	8/2
41	1/8 per oz.		2/- per oz.				2/6 per oz.	
42	2/-	"	2/6	"	3/-	per oz.	2/9	"
43	2/6	"	2/9	"	3/6	"	3/3	"
44	3/3	"	3/3	"	"	"	4/3	"
45	4/3	"	"	"	"	"	5/9	"
46	5/3	"	5/3	"	"	"	7/9	"

47 and 48 swg Enam. and 47 swg E.S.S.C. wires in stock. State needs. All above postage extra. POST ORDERS ONLY PLEASE. Send stamp for comprehensive lists.

POST RADIO SUPPLIES

33 BOURNE GARDENS, LONDON, E.4

TEL: CL1880LD-4688

RESISTANCE WIRES

Prices Per ounce
SWG Enam. D.A.S.C.

16	1/6	1/6
17	1/6	1/6
18	1/6	1/6
19	1/6	1/6
20	1/6	1/6
21	1/6	1/6
22	1/6	1/8
23	1/6	1/10
24	1/8	2/-
25	1/10	2/2
26	2/-	2/4
27	2/-	2/4
28	2/2	2/6
29	2/2	2/6
30	2/2	2/6
31	2/3	2/8
32	2/3	2/9
33	2/4	3/-
34	2/6	3/-
35	2/8	3/3
36	2/9	3/6
37	3/-	3/9
38	3/3	4/3
39	3/9	4/9
40	4/-	5/3
Up to 50 swg available		

SPECIAL OFFER

G.E.C. & B.T.H. GERMANIUM CRYSTAL DIODES

1/- each. Postage 2½d.

Diagrams and three Crystal Set Circuits Free with each Diode.

A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

CRYSTAL SET

INCORPORATING THE SILICON

CRYSTAL VALVE

Adjustable Iron Cored Coil.

RECEPTION GUARANTEED

Polished wood cabinet, 15/-, post 1/-, A REAL CRYSTAL SET, NOT A TOY

CRYSTAL SET

As above, but with Germanium Crystal Diode, 16/-, Postage 1/-.

B.A. SCREWS, NUTS, WASHERS
soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS,
TUFNOL ROD, PAXOLIN TYPE COIL
FORMERS AND TUBES,
ALL DIAMETERS.



FOR VALVES—GUARANTEED NEW AND BOXED



B.S.R. MONARCH AUTOMATIC RECORD CHANGER

These units will interchange on all three speeds, 33 1/3, 45, and 78 r.p.m. They play MIXED 7in., 10in. and 12in. records.

They have separate sapphires for L.P. and 78 r.p.m., which are moved into position by a simple switch. Minimum baseboard size requires 14in. x 12in., with height above 5 1/2in., and height below baseboard 2 1/2in. A bulk purchase enables us to offer these BRAND NEW UNITS at this exceptional price. These units are beautifully finished in cream enamel with cream bakelite arm.

COMPLETE WITH FULL INSTRUCTIONS 47.17.8. Carriage change 3/-.

MAINS TRANSFORMERS 3-WAY MOUNTING TYPE

MT1
Primary: 200-220-240 v.
Secondaries: 250-0-250 v. 80 mA.
0-6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. 17/6 ea.

MT2
Primary: 200-220-240 v.
Secondaries: 350-0-350 v. 80 mA.
0-6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. 17/6 ea.
Model makers' transformer for train sets, etc.

MT3, 30 volt 2 amp. tappings at 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20 24 volts from 200-250 v. Mains input. Price 17/6 each.

HEATER TRANSFORMER:

230 v. Input 2 volt .5 amp. 4/6
230 v. Input 2 volt 3.0 amp. 7/9
230 v. Input 4 volt 1.5 amp. 5/-
230 v. Input 4 volt 3.0 amp. 10/1
230 v. Input 5 volt 2.0 amp. 10/-
230 v. Input 6.3 volt .5 amp. 5/6
230 v. Input 6.3 volt 1.5 amp. 6/-
230 v. Input 6.3 volt 3.0 amp. 9/-
230 v. Input 12 volt .75 amp. 5/-


TYANA SOLDERING IRONS

Lightweight 40 watt irons with easily replaceable elements and bits. Voltage 100/110 v., 200/250 v. Price, 18/9 ea.

HEADPHONES

CLR Low resistance type 120 ohms. 7/8 pr.

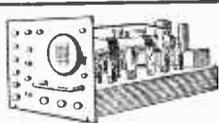COLLARO High Fidelity Pick-up for standard records. Listed 46/6. Our Price, 30/- ea.



AMERICAN INDICATOR UNIT TYPE EC929A

Brand new incorporating 3in. tube 3BP1, with mu-metal shield, 2-6SN7GT, 2-6HG4T, 6X4, 2X2, 6G4, 9 potentiometers, 24 v. aerial switch motor, transformer, and a host of small components. The whole unit which measures only 8 1/2in. x 8 1/2in. x 1 1/2in. is brand new, enclosed in black crackle box, and can be supplied at £2/6, plus 3/- p. & p.

2 RANGE POCKET VOLTMETER

Ex Ministry, brand new, 0-15 volts, 0-250 volts moving coil 345 ohms per volt, complete with leads 16/6 each.



LOUDSPEAKER UNITS

All PM 2 to 3 OHMS UNLESS OTHERWISE STATED.

each
ELAC 5in. Round Type..... 17/6
LECTRONA 5in. Round Type 17/6
PLESSEY 5in. Round Type... 17/6
GOODMANS 4in. x 7in. ELIPTICAL UNIT..... 21/10
GOODMANS 8in. UNIT..... 18/6
GOODMANS 10in. UNIT..... 25/8
R & A 10in. UNIT..... 25/8
TRIVOX 6 1/2in. VALVE UNIT 20/-
PLESSEY 12in. LIGHT-WEIGHT 37/6
R & A 8in. UNIT 17/6
LECTRONA 6 1/2in. with output transformer 18/6
R & A 4 1/2in. mains energised 600 ohms 17/6
PLESSEY 8in. mains energised 600 ohms 21/-
DEFIANT EXTENSION LOUD-SPEAKERS
6 1/2in. speaker unit in wooden cabinet with volume control..... 42/6 each.

EX GOVERNMENT HAND MICROPHONES

Complete with lead, switch incorporated in the metal case... 12/6 each.

VOLUME CONTROLS

Single Pole Switch, 200K. 1/2 meg., 1/4 meg., 1 meg., 2 meg., 3/9 each.
Double Pole Switch, 50K, 1/2 meg., 1 meg., 4/6 each.

CONNOSSEUR PICKUP

At a fraction of original price. Complete with matching transformer, 29/6.

IRON LEADS


Black and white flat iron leads, bonded ends ... 1/- ea.

LOUDSPEAKER CABINETS

This attractive walnut finished cabinet is available for 6 1/2in. or 8in. speaker units. Metal speaker frct. complete with tack and rubber feet.

6 1/2in. type:
Measures 8 1/2in. x 8 1/2in. x 4 1/2in. w base. Price 16/6 each.

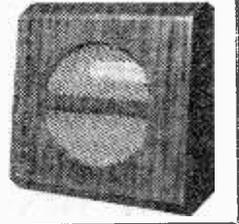8in. type:
Measures 10 1/2in. x 10 1/2in. x 5in. w base. Price 20/6 each.



CONDENSERS

TUBULARS WITH WIRE ENDS.
6 mfd. 50 v., 1/9 each; 16 mfd. 500 v., 2/- each; 25 mfd. 25 v., 1/3 each; 50 mfd. 50 v., 2/5 each; 100 mfd. 50 v., 1/9 each; 8 x 8 mfd. 450 v., 4/- each; 50 mfd. 12 v., 1/8 each; 20 mfd. 500 v., 3/3 each.

CLEM TRAVELLING IRON

With asbestos stand. Attractive colours. Blue, Green, Red, 110-250 volts. 16/6 each.

PUBLICATIONS

Wireless Amplifier Manual No. 2, 3/-.
Radio and Television Manual, 2/8.
Listeners Guide to Radio and T.V. Stations of the World, 2/6.
Wide Angle Conversion for Home Constructed Televisors, 3/6.
Radio and Television Pocket Book, 2/6.

SOLDERING IRONS

Solon soldering irons, pencil or oval bit. Please state type required. 65 watts 230-250 volts, complete with length of 3-core cable, 18/6 each.

VARNISHED COTTON SLEEVING

1 mm. to 2 mm. 1/6 per doz. yards
3 mm. to 5 mm. 2/6 per doz. yards
6 mm. to 8 mm. 3/6 per doz. yards
10 mm. to 14 mm. 5/6 per doz. yards
VARIOUS BRIGHT COLOURS.

THE COMPACT TELEVISION AERIAL BY ANTIFERREON LTD.

Supplied complete with universal mounting and back-plate in neutral brown finish. Overall length 5ft. 6in. Packed in carton 3ft. 4in. long. Complete with full instructions. (Cat. No. CD4. List price 50/- ... 13/6 ea.

DRYDEX TORCHES AT BIG REDUCTIONS

2PT5, Pentlight, chrome, clips into pocket like a pen..... 17/ ea.
2N3 Handyrite (coloured) suitable for ladies' hand-bags 17/ ea.
N15 Candelite (coloured) ideal for child's bedroom... 3/6 ea.
Prices include bulb but exclude batteries.

CHOKES

20H, 250 Ω, 60 M/A. Clamp Construction ... 6/- ea.
10H, 200 Ω, 90 M/A. Clamp Construction ... 9/8 ea.
10H, 200 Ω, 150 M/A. Clamp Construction ... 13/- ea.
5H, 250 M/A, 200 Ω. Fully Shrouded ... 18/3 ea.
10H, 300 Ω, 40 M/A. Midget Clamp Construction ... 5/3 ea.

FLEX MAINS TYPE

Twin 14/0075 P.V.C. covered ... 3d. per yd.

SCREENED CABLES

Single Type ... 6d. per yd.
Twin Core ... 7d. per yd.
Three Core ... 6d. per yd.

MAINS DROPPING RESISTORS

725 Ω Erie tap at 600 Ω ... 1/6 ea.
650 Ω taps at 375 Ω, 500 Ω, 5 Ω, 30 Ω ... 2/8 ea.
770 Ω Mains Dropper for Midget Radios with a tap at 125 Ω size 3in. long x 3in. dia. ... 1/3 ea.
Daggle Mains Dropper 3A. Cement coated with 2 sliders 3/0 ea.
2 amp as above 1.200 Ω ... 3/9 ea.
Green Vitreous Mains Dropper 1.225 Ω 2 taps ... 1/3 ea.
Zeuth Mains Dropper 910 Ω ... 2/- ea.

TRANSFORMERS FOR BATTERY CHARGERS

230v. Input Tapped 6-12v. 1 amp ... 13/6 ea.
230v. Input Tapped 6-12v. 3 amp ... 18/- ea.
(Both with tap on Primary for 2.5v. Pilot light)

THE GRADIENT F.M. TUNER

FT14. Introducing our latest F.M. Tuner. Of advanced design, employing new technique. ★Tuned resonator H.F. Stage. ★Ultra-stable co-axial oscillator. ★High sensitivity. ★Gertor I.P.T.s. and discriminator. This tuner is completely stable with no warm-up drift. Easy to construct and align. The ready-drilled chassis not only includes dial and drive assembly, complete with tuning condenser, but volume control ready mounted. Attractive finished in bronze, black and gold, dial ready calibrated in megacycles. Front panel measures 8 1/2in. x 5in., dial 5 1/2in. x 1 1/2in., chassis 7 1/2in. x 4 1/2in. x 1 1/2in. Valve line-up is 4-6AM6 or equivalent. Illustrated comprehensive instruction booklet with individually-priced component list 1/8 post free. Or, the kit complete right down to the last nut and bolt. 25/19/6, plus 2/6 postage and packing.

G.E.C. CABINET LOUDSPEAKERS
Cat. No. BC1955. 8in. P.M. Moving Coil Loudspeaker Unit, 2/4 ohms, with Volume Control. Price 60/- each.

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."



5/6 VINCES CHAMBERS
VICTORIA SQUARE
LEEDS 1.


TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage 2/3.

MAIL ORDER ONLY

MAXI-Q RECEPTION OF F.M. PROGRAMMES IS MADE EASY WITH MAXI-Q COMPONENTS

REGD.

PDT.1

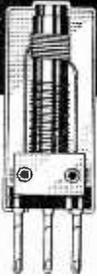

Components for the MAXI-Q F.M. TUNER
Full constructional details, point-to-point wiring diagram and alignment instructions are given in Technical Bulletin DTB.8, 1/6.
Ratio Discriminator Transformer, RDT.1/10.7, 12/6.
Phase Discriminator Transformer, PDT.1/10.7, 9/-.
I.F. Transformer IFT.11/10.7, 6/-.
I.F. Transformer IFT.11/10.7/L, 6/-.
F.M. Scale, 9/- Chassis and Screens, 7/6. Variable Condenser 3.5/15 pF, 6/6.

"MAXI-Q" F.M. TUNER UNIT, completely assembled with valves, £7.2.6, plus P.T., £2.17.0.

Exhaustively tested components for the "OSRAM" F.M. TUNER
Chassis, Base Plate, Gold finished Front Panel, Printed Dial Plate, Drum, Drive Spindle, Pointer, Brackets, Glass Clips, Screws, Spring and Cord, 37/6.

Aerial Coil 0/T1, 2/9. R.F. Coil 0/L1, 2/6. Oscillator Coil 0/L2, 2/-.
1st, 2nd and 3rd. IFT'S, IFT.11/10.7, 6/- each. Ratio Discriminator Transformer, 0/T2 (T5), complete with crystals, 19/6. Polythene Coupling, 2/6. Extension Spindle, 6d. Spin Wheel, 3/6. Variable 2-Gang Condenser 6-17.5 pF., 17/6.


Specially prepared components for the "MULLARD" F.M. TUNER
Aluminium Chassis, completely punched, 12/- I.F. Rejectors, Ref. 510/1FF, 2/6. Aerial Coil L1/L2, Ref. 510/AE, 4/6. Choke L3, Ref. 510/RFC, 2/- R.F. Coil L4, Ref. 510/RF, 2/6. Oscillator Coil L5/L6, Ref. 510/OSC., 4/6. 1st IFT. L7/L8, Ref. 510/IFT1, 7/6. 2nd IFT. L9/L10, Ref. 510/IFT2, 7/6. Ratio Detector Transformer L11/12/13, Ref. 510/RDT, 12/6.

Components obtainable from all reputable stockists or in case of difficulty direct from works. GENERAL CATALOGUE covering technical information on full range of components, 1/-, post free.

DENCO (CLACTON) LTD. 357/9 Old Road, Clacton-on-Sea, Essex

Stop Press :

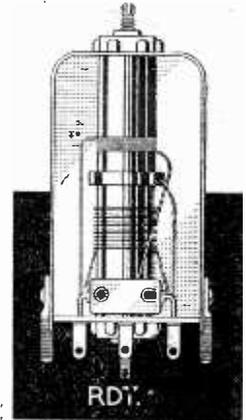Please note that Purchase Tax has now been increased by 10 per cent. and customers should provide for this when sending C.W.O.



BUILD THIS HIGH QUALITY LOW COST AMPLIFIER

★ Circuit designed by Mullard research engineers.

★ Specified components available from most radio dealers.




Here's an entirely new amplifier circuit which brings high quality sound reproduction within the reach of thousands more enthusiasts. It has been designed by Mullard research engineers with special regard for easy construction and low cost. Full details of the circuit are included in the 2/6 book which is obtainable from radio dealers or direct from Mullard Ltd. Valve Sales Department—2/10 post free. Get your copy now.


Mullard



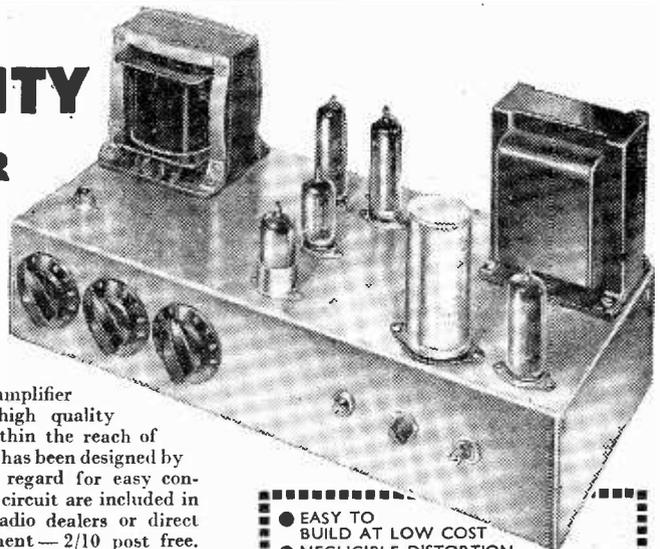MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2



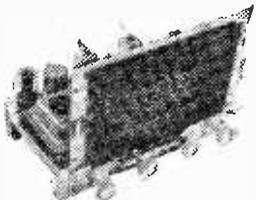- EASY TO BUILD AT LOW COST
- NEGLIGIBLE DISTORTION AT ALL OUTPUT LEVELS
- UNIFORM FREQUENCY RESPONSE IN AUDIBLE RANGE
- GOOD TRANSIENT RESPONSE
- LOW OUTPUT RESISTANCE
- LOW HUM AND NOISE
- DESIGNED ROUND 5 MULLARD MASTER VALVES — EF86, ECC83, 2 x EL84, GZ30 or EZ80



15" long x 8 1/2" overall depth x 7" high (approx.)
Packing and Carriage 12/6.

TYPE A (5 Valves)

Three-wavebands Superhet with full negative feedback and A.V.C. Full-range tone-control.

10 Gns.

RADIO RECEIVER CHASSIS


Built to the highest specifications, these chassis offer the finest value to the enthusiast. Supplied with set of selected knobs. Socket panels for aerial, earth, speaker, Pick-up and Gram motor, 200/250 v. 50 cycles only.

TYPE B (7 Valves)

Three-wavebands Superhet with specially designed push-pull output stage.

£15.14.6.

SPECIAL F.M. TUNER

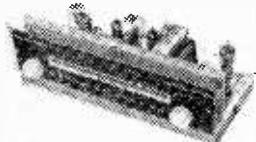

A completely self-contained unit transforms an old A.M. set into a modern F.M. receiver. Circuit contains six valves; Grounded grid R.F. stage followed by additive mixer using a FCC85 Twin Triode valve combine these two functions in a completely sealed permeability tuned unit. Two I.F. stages give maximum gain followed by EBG1 double diode as ratio detector. Frequency coverage of 85 to 101 megacycles allows adequate overlap at each end of the band and covers all existing and proposed V.H.F. transmissions in the U.K.

Cat. No. FMT/A.
Complete Unit in Cabinet with Magic-eye tuning. **17 Gns.**

13" long x 6 1/2" overall depth x 7 1/2" high (approx.)

Packing and Carriage 12/6.

Cat. No. FMT/B.
Chassis only excluding Magic-eye. **£13.15.0.**

11 1/2" long x 5 1/2" overall depth x 4" high (approx.)

AM/FM CHASSIS


A nine-valve AM/FM chassis with 4 wavebands (Long, Medium, Short and F.M.), push-pull output stage and magic-eye for precision tuning. Specially designed, with permeability-tuned F.M. circuit and a very high degree of I.F. amplification for fringe-area reception, it offers the finest quality regardless of price. Automatic volume-control and a special wide-range tone control. Push-pull output stage and compensated network for electrostatic treble speaker, with an output of 5 watts and the widest possible audible frequency range. Special large 10in. high flux-density F.M. Speaker with hyperbolic cone plus matched high-tone electrostatic Speaker. Co-axial socket for dipole aerial. A.C. 50 cycles only. Provision for external **25 Gns.** speaker.

Packing and Carriage 15/-.
12" long x 8 1/2" overall depth x 8" high (approx.)

A.M. CHASSIS (Specially Recommended)

Five-valve Superhet. Two waveband (Medium and Long) A.C./D.C. 200-250 volts. Output 4 watts. Controls: tuning, on/off volume, wavechange. Developed to meet the demand for an inexpensive instrument with no sacrifice in the quality of its reproduction and output. **8 Gns.**

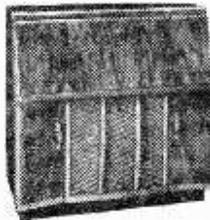12in. long x 8 1/2in. overall depth x 8in. high (approx.). Packing and Carriage 12/6.



CABINETS

The magnificent Bureau type Cabinet illustrated is in specially selected walnut veneered exterior with light sycamore interior with matching Rexine lining. Two full-sized compartments. Overall measurements: 34in. x 17in. x 33in. high. **Price £17.0.0.**

Other high quality cabinets are available at prices ranging from **10 guineas**. Packing and Carriage 25/-.

*** SPECIALLY RECOMMENDED DISC PLAYER**

Specially designed for the amateur builder, these Disc Players consist of the latest three-speed Automatic Record Changers, complete with crystal turn-over pick-up head for long-playing and standard records, mounted on sycamore-lined base. Supplied complete with fitted mains lead and screened pick-up lead, ready for connecting up.



Packing and carriage 12/6.

Price **£11.5.0.**

AUTOMATIC RECORD CHANGERS

Cat. No. RC/A—Latest fully-automatic 3-speed mixer changer made by a famous manufacturer. **£9.15.0**
Cat. No. RC/B—Garrard RC80, 3-speed, automatic A.C. mains. **£13.0.0**
Cat. No. RC/C—Garrard RC80, 3-speed, automatic A.C./D.C. Universal. **£26.10.0**

Packing and Carriage 12/6.

UNBEATABLE VALUE TAPE RECORDER



In a superbly fitted moroccan-grained carrying case, this instrument is the very finest of its class, regardless of price. Latest type TRUVOX twin-speed Tape Deck. Input for Radio, Gram., and Microphone. Built-in selected elliptical Speaker of the very finest quality. Recording (with recording level indicator) or Play-back. 200/250 volts 50 cycles, A.C. mains only. Supplied complete with selected Microphone and Recording Tape. **42 Gns.**

Packing and Carriage 25/-

TAPEDECKS

TRUVOX 2-speed, twin track, Tape Deck of the latest type, with push-button controls. **£23.2.0.**

Packing and Carriage 10/-.

TAPE RECORDER, Amplifier only. Built to the highest standards, magic eye for indicating recording level. **12 Gns.**

Packing and Carriage 12/6.

LOUDSPEAKERS

Cat. No. LS/10—10in. Standard **£1.10.0**
Cat. No. LS/E74—7in. x 4in. Elliptical **£1.1.0**
Electrostatic Loudspeaker LSH75 for treble response **11/6**
Packing and Carriage 3/-

ALL FULLY GUARANTEED
GENEROUS HIRE PURCHASE TERMS

All correspondence and remittances to 36, Southampton Street, Strand, London, W.C.2. Personal Callers only at 90, Judd Street, London, W.C.1. Telephone enquiries **TERminus 9876.**

HOME RADIO OF MITCHAM

187, LONDON ROAD, MITCHAM, SURREY

MIT. 3282


The full range of
EDDYSTONE

short wave components in stock.
Eddystone catalogue price 1/-.


Crystal Microphone Inserts Special Offer!

Brand new ex-M.O.S. Ideal for tape recorders, amplifiers, etc.

ONLY 5/6 EACH
Limited number.

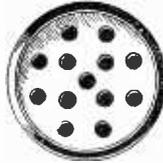

COMMERCIAL TELEVISION—Converter Kit

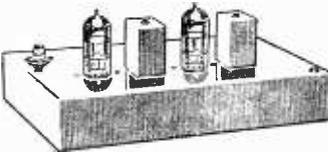

Complete kit of parts including valves, ready wound coils, punched chassis, down to the last nut and bolt. Suitable T.R.F. or superhet receivers. PRICE £2 15s. 0d. Circuit details, 6d. post paid.

MK. II CASCODE CIRCUIT. Specially suitable for fringe areas as it provides high gain and low noise level. **COMPLETE KIT, £3 1s. 6d.**

DEMONSTRATION MODELS WORKING

MIDLANDS READERS. These converters have been carefully tested on the Lichfield pilot transmissions—Build Yours Now and be ready for the start of this exciting new service.

SPECIAL OFFER OF 3-SPEED GRAM UNITS


Comprises heavy duty A.C. induction motor for 200/250v. Complete with heavy steel cream-enamelled turntable and rubber mat. With 3-speed selector lever. Ideal for modernising that old gram. Limited offer only. **£3 each, plus 2/6 postage.**

NEW MCCARTHY FM/VHF CHASSIS

Complete A.M. reception on short, medium, and long wavebands PLUS F.M. reception over the whole of Band II. A.C. mains, 8 valves, gram pick-up, ext. L.S. This latest McCarthy chassis is without doubt to-day's finest value. Full details on request.

CALL TO-DAY FOR A DEMONSTRATION.


PRICE £22

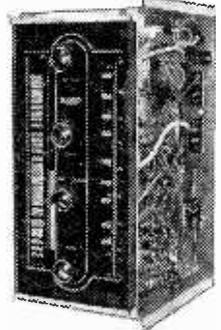

FREQUENCY MODULATION TUNERS

All parts in stock and demonstration models working.

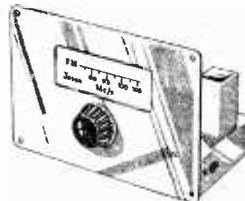Detailed price lists available for the DENCO, JASON and MULLARD F.M. Tuners. Full constructional details: DENCO 1/6 JASON 2/- MULLARD 3/6



FM AERIALS { Loft or room dipole ... 11/6
Wich mast clamp ... 26/-
Wall mounting ... 33/-

TR1196 UNITS. FINAL OFFER AT PRICES WHICH CANNOT BE REPEATED

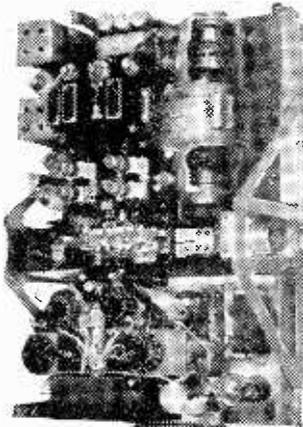


ILLUSTRATION above is the complete TR1196 comprising 3 units and is shown without covers. This complete outfit is available in transit case in perfect order, slightly stock soiled at only £2.12.6, carriage 10/-.

RECEIVER UNIT

On 8" x 6" x 2½" chassis complete with six valves (2 EF30, 2 EF36, 1 EK32, 1 EBC33) converts to ideal broadcast or short wave superhet. Circuit and conversion details included, 25/-, post 2/6.

TRANSMITTER UNIT

On chassis 10½" x 7½" x 1½" complete with 3 valves (TT1, EL32, EF50), coils, etc., all complete, 12/6, post 2/-.

RELAY UNIT

Contains solenoid impulse motor, heavy duty relay, sensitive relay, three Jones sockets, condensers, etc., 7/6, post 1/-.

GENERATOR UNIT

Complete with smoothing, 6v. in. gives 24 v. and 230 v. D.C. out. Normally 24 v. in. giving 6 v. and 230 v. out. On chassis 8" x 4" x 2" with cover. 7/6, post 2/6.

RECEIVER UNIT

On chassis as described opposite, all complete but without valves, containing 6 octals, 2 I.F.'s, 465 Kc, seven mansbridge type condensers, transformers, pots, tubular condensers, resistors, etc., 12/6, post 2/6.

TRIMMER UNIT

Chassis 5" x 4" x 2½" contains four air spaced 75 pF trimmers, two-gang Yaxley type four-way switch coil, condensers, etc., 5/-, post 1/-.

COMPLETE TRANSCIEVER

As previously advertised and illustrated opposite but slightly stock soiled. Despatched without transit case but with conversion data and circuit diagram, £2.2.0, carriage 10/-.

OTHER ODDMENTS

465 I.F.'s complete in can, 3/6 ea., 3 gang pots ca. 70K boxed, 1/- ea. Ferranti m/amp meters 0-5 m/a, 9/- ea. Ceramic condensers split stator 15/15 pF, 2/6 ea. 100 pF variables ceramic insulation, 2/- ea. (Add for post on these items.)

WOOLLEYS RADIO & ELECTRICAL SUPPLIES LTD.

615 BORDLESLEY GREEN, BIRMINGHAM, 9.

Phone: VIC 2078


PROFESSIONAL 3 VALVE MAINS SET IN SUPERB CABINET FOR ONLY . . .

A straight T.R.F. A.C. or A.C./D.C. Mains Set—requires no radio knowledge to assemble. Easy to read Diagram takes you step by step. Only tools needed are pliers, Screwdriver and Soldering Iron. ALL parts in stock NOW. Order AT ONCE stating which type of set is required, A.C. or A.C./D.C. Mains—these are the sets to SHOW to FRIENDS!

Wiring Diagram and Parts List, 1/-, Post FREE

97/6


**PLUS 2/6 FOR
Postage & Packing.**

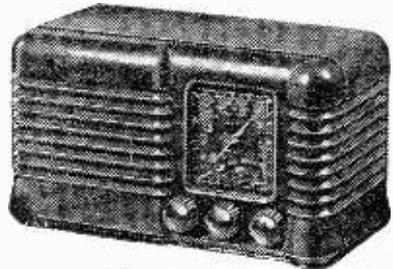

... AND NOW, THE SUPERHET—REALLY SELECTIVE, TERRIFIC DRAWING POWER AND VOLUME!

Complete parts available for this fine SUPERHET Receiver. Similar cabinet to that illustrated above but with really terrific power and volume on both Long and Medium Waves. Specially designed for "fringe" areas! Only £6.6.0 plus 2/6 postage and packing.

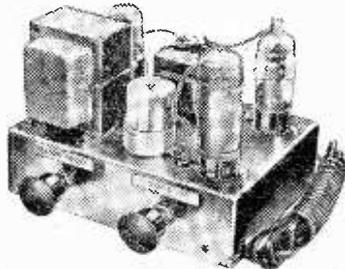EASY INSTRUCTIONS and "Know-how" Diagrams 1/- post FREE. Send TODAY!



63/- ONLY

**PLUS 2/- FOR
Postage & Packing**

**EASY TO READ
WIRING CHART
AND PARTS
LIST 6d.(Post Free.)**

FOR THIS MULTI-PURPOSE AMPLIFIER UNIT KIT!

The CHEAPEST 3-Valve Amplifier on the market—can be built in 2-3 hours WITHOUT previous radio experience! High Gain, Negative Feedback and Ready-drilled Chassis which is not "live". Ideal for amplifying Grams, small P.A. Equipment, Baby Alarms, Office Intercom Sets, etc. An ABSOLUTE BARGAIN at this price—get YOUR order in NOW to avoid disappointment!

SATISFACTION OR CASH REFUNDED!

WRITE NOW TO B'HAM'S LARGEST WALK-AROUND RADIO STORES!

NORMAN H. FIELD

MAIL ORDERS: 97, STRATFORD RD., BIRMINGHAM, 11
CALLERS: 68, HURST STREET, BIRMINGHAM, 5
Tel: Mid 3619



BRIMAR
for best results

- Use
- BRIMAR**
- RADIO VALVES
- TELETUBES
- METAL RECTIFIERS
- GERMANIUM DIODES
- BRIMISTORS
- TRANSISTORS

OSMOR offer an unique SERVICE

TO THE PRACTICAL WIRELESS ENTHUSIAST



Whichever published circuit you decide to construct, first ask Osmor for a practical wiring diagram with full lists of components required. We cannot provide diagrams for all circuits just yet, but in due course we will. We keep right up to date in building the latest circuits published in PRACTICAL WIRELESS—"Wireless World" and "Radio Constructor" and we stock the components specified, including a design for F.M. TUNER, BAND III TELEVISION CONVERTER, VARIOUS SUPERHET CIRCUITS (using some miniature valves), 5 & 6 valve superhets, 3 valve (plus rectifier) T.R.F. Circuit, Battery/Portable Superhet, T.R. 1196 Conversion, Coronet Four, Attache Case Portable, 3-speed Autogram, Amplifiers, Whistle Filters, F.M., A.M. Gram. Switching Circuit, and many others. Send 7½d. in stamps for circuits, fully descriptive literature together with coil and coilpack leaflets, component lists, chassis drawings and templates. Osmor also offer a Free Advisory Service for enthusiasts—just write a letter to our Technical Dept. (See "Readers' Queries" below.)

OSMOR BAND III CONVERTER


Designed to receive Band III Channel 9 and effectively reject Band I Channel 1. The design takes into account the very high power transmissions due to start on Band I Channel 1. Wiring diagrams, chassis templates and full details, 2/-.

MULLARD 3 valve 3 watt AMPLIFIER

(or quality back-end) on application. Circuit and wiring diagrams for Tuner in conjunction with above using Osmor coils, available on request.

SCRATCH FILTER. For Crystal or Low impedance Pick-ups. Complete Unit, 15/-.

OSMOR Station Separator

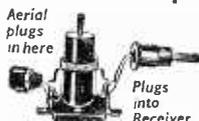

The problem of the overlapping station generally completely solved, and always minimised. Effective within the ranges stated. Fitting takes a matter of seconds.

Metres	Metres	Metres
141 to 250	319 to 405	1450 to 1550
218 to 263	395 to 492	410 to 550 Kc/s
287 to 341	455 to 567	7½ each.

Special Separator to clear Radio Luxembourg 10/6. Also a special 90 Mc/s Unit to reject Band II (F.M.).

T.V. Sound & Vision I.F. Unit

Wiring diag., circuit, coils, chassis and components, etc. Sound I.F. 39.15 Mc/s. Vision I.F. 34.65 Mc/s. (Available shortly.)

To convert your T.R.F. T.V. receiver to a superhet and avoid several forms of interference.

"MAKING A CAR RADIO"

Osmor Dual Range Superhet Coils Type QA170 and Q.O.S.170, 12/6 pair. As specified by PRACTICAL WIRELESS. Nov. 1955.

9 Kc/s WHISTLE FILTER

Three simple adjustments are made to obtain optimum rejection—the sharpness of response is adequate to reject the unwanted frequency. Complete Unit, 20/-.




OSMOR miniature "Q" COILS

A complete range is available for all wavebands and purposes and ideally suitable for all circuit positions. All high "Q" values. Iron-dust cored. Easy connection tags. Simple "press home" fixing. "Q" of "Potted" types up to 300.

The success of Frequency Modulation receivers is due in no small measure to the efforts of Osmor technicians in co-operating in advanced coil designs. Technical Colleges, Universities and large-scale Manufacturers, also use Osmor Coils for research. COILS NOW AVAILABLE for Whistle and Scratch Filters, Tape Recorder Oscillators, Chokes, etc. List of coil types on application.

OSMOR "Q" COIL PACKS

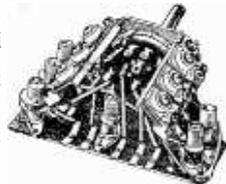Size only 1½ x 3½ x 2½ with variable iron-dust cores and Polystyrene formers. Built-in trimmers. Tropicalised. Prealigned. Tested and guaranteed. All types for Mains and Battery Superhets and T.R.F. Ideal for the construction of new sets, conversions, etc.



Ultra Small Ceramic Neg. Ten. Co-eff. Capacitors for V.H.F., etc., from 1 pf to 0.5 pf to 10,000 pf +10% - 20%. 10d. each.

Small ½ watt Resistors 10% ± 10% to 10 m. ± 20%. 6d. each.

Full list of types, co-eff. and values on application.

READERS' QUERIES

Let us solve your problem!

Dear Sirs,

When I peak the I.F.'s there are no stations. When I detune them I get the main stations but poor sensitivity.

Probably I.F. instability. Further decouple H.T. line and try increasing value of I.F. and F.C. bias resistors.

Dear Sirs,

I have at times received signals on a crystal set from a Continental station. Can you explain the reason for this?

A near-by receiver with re-
action on the point of self-
oscillation, the oscillations in
the aerial are "re-radiated"
and can be picked up in a
crystal set.

418, BRIGHTON RD.,
CROYDON, SURREY

Dear Sirs,

I have constructed the "P.W." Sensitive 2-Valver and now wish

to add the L.W. Please advise coil types.

Q49 or Q491 (pot-coil).

Dear Sirs,

I am much troubled with whistles on every station. My I.F.'s are correctly aligned. Your help please. Fit 45 Kc/s Whistle Filter which may consist of one winding I.F. transformer between aerial and earth.

Dear Sirs,

I have constructed a s'het circuit which is good except for valve noise which I think comes from a 6K7 I.F. valve. Can you suggest a simple thing to try?
Fit low-noise pentode (6A5).

Telephone:
CROYDON 5148/9

OSMOR

RADIO PRODUCTS LTD.

PRACTICAL WIRELESS

EVERY MONTH
VOL. XXXII No. 591, JANUARY, 1956
COMMENTS OF THE MONTH

EDITOR: F. J. CANN

24th YEAR
OF ISSUE
BY THE EDITOR

Advice to Contributors

WE invite our readers to submit articles of a practical as well as technical nature for publication in this journal and our associated journal "Practical Television." These articles should not be more than 1,500 words in length, be accompanied by sketches and where possible photographs, where necessary a list of components and a list of sources of supply, be written on one side of the paper only and contain the author's name and address on the first folio. Articles of a highly theoretical text-book nature are not required. Preference is given to articles of a constructional nature, describing receivers or equipment which has actually been made. We do not want empirical designs. When submitting technical articles, submit details of your qualifications and experience. Payment is made on a generous scale for all articles accepted for publication, each manuscript is carefully considered and promptly accepted or rejected. Enclose a stamped envelope with all manuscripts. These brief instructions are given as a guidance to intending contributors because quite often we receive promising manuscripts which have to be rejected because they are either incomplete, omit important details, or are designed round a piece of apparatus or a component which is not readily available. In general, we do not accept articles which may be described as "special" to the contributor concerned, and making use of parts which involve a search around the radio shops. We do not require purely descriptive articles. All articles should live up to the title of this journal. We also welcome items of news for our "Round the World" feature, and letters of an interesting nature containing information or criticism will be published. Letters, however, should be kept brief—preferably not more than 200 words, as space is short.

ADVICE TO QUERISTS

WE should like also to offer advice to querists. We cannot, through our Advisory Service, undertake to prepare special designs for readers, nor to supply information which requires the preparation of an illustrated article. All questions must relate to subjects which can be dealt with reasonably by post. We cannot, moreover, undertake to modify designs for readers, nor to answer questions relating to designs published

by our contemporaries, some of whom have not an advisory service. Such queries should be properly addressed to the journal concerned, and no telephone queries please! It is essential for every query to be accompanied by a stamped and addressed envelope and the query coupon cut from the current issue.

Our Advisory Service is free, and we are always delighted to help readers in difficulties, but we often receive a query which has been answered several times herein. We hope readers, whether they have their copies bound or not, will purchase the annual index which we publish at 1s. 1d., so that they can consult past issues before sending in a query.

A NEW VOLUME STARTS

INCIDENTALLY, this issue is the first of a new volume, and signals our entry into our 24th year of publication and our 32nd volume. A volume consists of 12 monthly issues, and we shall shortly be publishing the index for Volume 31. An announcement will be made herein when it is ready.

AWARDS FOR TECHNICAL WRITING

THE R.I.C. scheme of annual awards to the authors of published material which it is considered enhances the reputation of the British Radio Industry abroad is an excellent one, but judging from past awards we wonder whether some of them have really achieved this object, and whether the R.I.C. is not insisting upon a too high standard of technical writing. Could not the awards be made for anything which enhances the reputation of the British Radio industry? It is possible that someone will invent some new piece of circuitry who is not an accomplished writer. After all, mathematical dissertations are not widely read either in this country or abroad, as the circulations of the journals in which they appear indicate. If the R.I.C. therefore wishes to pay honour to those who help to enhance our reputation in the foreign market it should go outside the sphere of technical writing, or enlarge it to include technical developments. It is an excellent scheme, but now that it has been in operation for a few years we think the terms under which the awards are made are in need of readjustment. At present they only appeal to those who have scholastic qualifications.—F. J. C.



Round the world of WIRELESS



Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast receiving licences in force at the end of September, 1955, in respect of stations situated within the various postal regions of England, Wales, Scotland and Northern Ireland. The numbers include licences issued to blind persons without payment.

Region	Number
London Postal ...	1,441,502
Home Counties ...	1,390,807
Midland ...	1,119,500
North Eastern ...	1,471,958
North Western ...	1,130,331
South Western ...	916,094
Wales and Border Counties ...	577,472
Total England and Wales ...	8,047,664
Scotland ...	1,004,659
Northern Ireland ...	218,267
Grand Total ...	9,270,590

Licence Totals

BROADCAST receiving licences, numbering 14,154,439, including 4,883,849 for television, and 284,549 for sets fitted in cars, were current in Great Britain and Northern Ireland at the end of September, 1955.

Marconi Transmitters for Iraq

AN order has been received by Marconi's Wireless Telegraph Co., Ltd., for a complete new high-power broadcasting station, to be sited at Abu Ghraib, near Baghdad. The contract was placed by the Iraq Posts and Telegraphs Department.

Four Marconi 100 kW. air-cooled transmitters are included in the order, together with programme input equipment, automatic monitoring equipment and a 4-channel Super High Frequency music link for use between the Baghdad studios and the transmitting station. A 165-metre half-wave mast radiator and an H.F. aerial system forms another part of the order.

Two of the transmitters, Type BD.253, will operate on the high-frequency band and two, Type BD.206, on medium-frequency. The latter two will work in parallel.

By "QUESTOR"

Change of Telephone Number

BRITISH INSULATED CABLE LENDER'S CABLES, LTD., announce that as from November 2nd the telephone number of their Lincoln Branch Sales Office, 113, Canwick Road, Lincoln, has been changed to Lincoln 21351/2.

Mr. Butler to Open London B.I.F.

MR. R. A. BUTLER, the Chancellor of the Exchequer, is to open the British Industries Fair at Olympia on April 23rd. This B.I.F. will be the second held in London in 1956.

The first, in Earls Court, will be opened by Lady Eden, wife of the Premier, on February 22nd.

In accepting the invitation to perform the opening ceremony at Olympia, Mr. Butler said the B.I.F. performed a vital role in bringing British goods to the notice of overseas buyers and in furthering world trade.

He referred to the determination of the Fair's management to broaden the scope of the B.I.F. so that it would go from strength to strength in size and representation.

New Radio Telephone Service between Bahrein and Karachi


CABLE AND WIRELESS, LTD., announce that a new radio telephone service has been opened between Bahrein (Persian Gulf) and Karachi (Pakistan).

The service was inaugurated by Shaikh Isa Bin Sulman, eldest son of the Ruler of Bahrein, who spoke with the Postmaster General in Karachi.

The rate is 25 rupees (£1 17s. 6d.) for a three-minute call.

British Industrial Yachts at Copenhagen

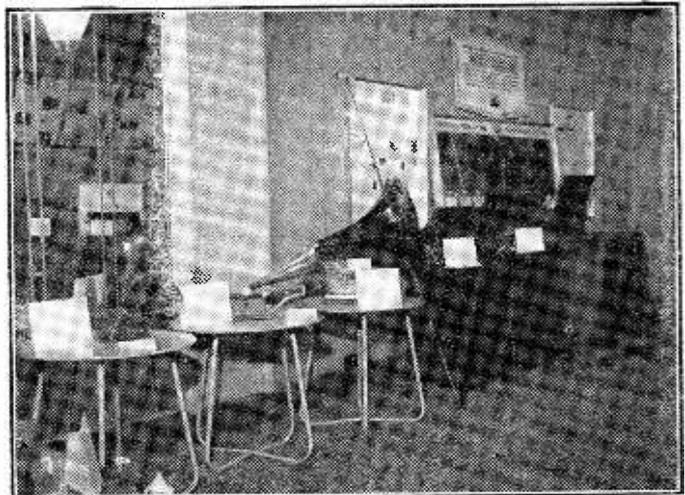THE Marconi Marine research and demonstration vessel *Elettra II*, representing the English Electric Group of Companies, was among the five British industrial yachts honoured by a visit from H.R.H. the Duke of Edinburgh at



An exhibition of gramophones, from the Berliner 1888 hand model up to the latest H.M.V. Model 3001. These were to be seen at an Exhibition of Entertainment at Wood Green.

Copenhagen recently. The yachts, which were in Denmark in connection with the British Trade Fair, were also privileged to go out to meet the Royal Yacht *Britannia* when she arrived off the port.

The 100th Mullard Film Meeting

SINCE 1953 Mullard Limited have been organising film meetings for Dealers at the invitation of and in co-operation with Trade Associations, Institutions and Radio and Television Societies.

On October 27th, the hundredth

Remote Presentation of Radar Information." G. J. Dixon and H. H. Thomas.

Scottish Section, *Thursday, December 8th, 7 p.m.*, at the Institution of Engineers and Shipbuilders, Elmbank Crescent, Glasgow. "Automatic Control of Machine Tools." H. Ogden.

West Midlands Section, *Wednesday, December 14th, 7.15 p.m.*, at Wolverhampton and Staffordshire Technical College, Wulfruna Street, Wolverhampton. "Television Aerial Design, with emphasis on Band

The radar installations have been designed to meet the stringent requirements of modern naval strategy. The radio communications installations are likewise to be of the very latest types.

Monaural Delay

TESTS which have been conducted in Ohio State University show that radio messages received under noisy conditions were 22 per cent. clearer when they were heard by one ear before the other. It is stated that the reason for this is not understood, but that a delay of .06 seconds in the reception of sound by one ear produces this greater clarity—presumably because the brain receives two impressions of the sound. To obtain the delay a tape recording device is used and splits the sounds fed to a pair of headphones.

Lamps Controlled by Radio

IN Coventry a system of lamp control by radio has been tested and found to be highly efficient. Each lamp is fitted with an 8in. aerial on the top, and inside the column a two-valve receiver is housed. By means of a small transmitter at the control station it is possible to switch on or off all lights which is more effective than existing systems. It is also claimed that the arrangement would permit traffic lights to be controlled, for instance by police in an emergency such as the pursuit of another car which could be stopped by placing all lights on the route being followed at red. The only snag at the moment is that the G.P.O. will not issue a licence for a fixed station. It could be operated by a mobile set-up.

Tape Recorder Contest

GRUNDIG dealers are to co-operate in a music contest in conjunction with Selmers. Entrants have to submit a recorded performance of a Clavoline concerto, and where they do not own a Grundig, dealers are to be asked to co-operate.

No TV Relay at Brighton

AT a recent meeting Brighton Town Council rejected a recommendation that Relay Circuits, Ltd., should establish a wired TV service in the town. Rediffusion had also applied, and objection was made to the unsightly wiring which would result.



Mr. C. H. Gardner, of the Mullard Valve Sales Department, speaking at the 100th Mullard Film Meeting at Caxton Hall in October.

Mullard film meeting for radio and television dealers held in conjunction with R.T.R.A. took place at Caxton Hall, London.

It was appropriate that the Chair was taken on this occasion by Mr. H. A. Curtis, Director and Secretary of the R.T.R.A., who addressed the first meeting also held at Caxton Hall.

The Mullard film meetings are designed to provide a means of bridging the gap between the dealer and the manufacturer. From their inception they were acclaimed as a success. By February, 1955, the total attendance had passed the 10,000 mark.

B.I.R.E.

THE following meetings will be held during December:

London Section, *Wednesday, December 14th, 6.30 p.m.*, at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1. "The

III problems." I. A. Davidson.


North-Eastern Section, *Wednesday, December 14th, 6 p.m.*, at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Road, Newcastle-upon-Tyne. "The Metal Cone Loud-speaker." W. I. Heath, B.Sc.

New Type Radar for Chilean Warships

A CONTRACT worth more than £250,000 has been awarded to Marconi's Wireless Telegraph Co., Ltd., for the complete Radar and Communications' equipment for two destroyers now under construction by Vickers-Armstrongs, Ltd. These warships, which are being built for the Chilean Government, will be among the most modern of their class in the world.

Our next issue, dated Feb. 1956, will be on sale on Friday, January 6th.

An 8 Valve A.M./F.M. Receiver

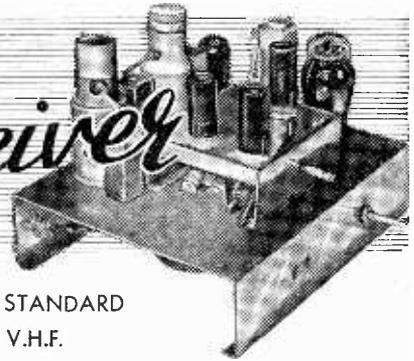

A NOVEL DESIGN OF RECEIVER FOR THE RECEPTION OF STANDARD BROADCAST SIGNALS AS WELL AS THOSE ON V.H.F.

(Continued from page 761, December issue.)

Decoupling

CERTAIN decoupling components which are represented below the circuit diagram are for decoupling valve heaters. In this receiver one pin of each valve heater is connected to the earthing tag for that stage. In addition, the other heater pin of the oscillator, frequency changer and detector valve is connected to the earthing tag through a decoupling capacitor of ceramic or mica type. 1,500 pF is used for the diode heater, while 250 pF was found adequate for the F.C. and oscillator. The usual rule about shortest-path connections should be followed.

Circuit Omission

It should be noted that in the circuit, Fig. 1, in last month's issue the 'top' of the tuned circuit, L4, C11, C13 and C14, should be connected to V2 anode.

A.F. and Output Stages

These are conventional in character. A small amount of negative feedback is provided, sufficient to afford good quality of reproduction.

Alignment

For those who possess no signal generator a quickly hooked-up oscillator is essential. The circuit diagram of a suitable instrument is given in Fig. 6, and this may be modulated at 100 c.p.s. when necessary by returning R2, the grid leak, to the live side of the heater terminals. Another CV1065, connected as a triode, is used.

The following are the coil details.

Coils

Anode: 30 turns 32 s.w.g. enamelled wire, Aladdin former 0.4 in. diameter.

Grid: 10 turns 32 s.w.g. interleaved in earthy end of anode coil.

This signal generator does not need to be connected at all to the receiver, but a short length of wire (6 in. or so) is attached to the grid cap of V4 to pick up the signal. It is first set to 10.7 Mc/s by using the short-wave band of a domestic receiver as an indicator. It may be necessary to put it in the next room to reduce the signal received to a handleable amount later on in alignment.

To align the receiver first remove the oscillator valve.

voltmeter of 1,000 ohms per volt or better, 0-10 volt range, connected across C32, tune the I.F. amplifier for maximum output by adjusting the transformer cores. Rock the tuning capacitor of the generator a little each side of 10.7 Mc/s and observe the voltage across C32. The aim should be to get a response curve like that of Fig. 2. A peaked response may be due to feedback in the I.F. amplifier or to inaccurate I.F. transformer construction. The former can be dealt with perhaps by adjustment of wiring, checking over for "dry" joints, or by adding screening. The second trouble is difficult to eradicate without rewinding the transformers; but careful construction should result in no trouble from either source.

Remove the voltmeter from across C32 and connect across C33. With the generator set to 10.7 Mc/s and R19 in the middle of its travel adjust the core of the secondary of T3 to give zero voltage. Remove the voltmeter and reconnect across C32. Remove the 6 in. aerial from the grid of V4 and realign as above—by now the I.F. gain will obviate the need for any aerial and stray pick-up can be relied upon to give sufficient signal. Reconnect the voltmeter across C32 and replace the oscillator valve.

If a calibrated signal generator is available, A.F.

modulated, connect to the aerial input and set to 100 microvolts at 85 Mc/s. Set the tuning gang to maximum capacitance and rotate the core of L3, L4 to tune in the signal. If the signal is found at two settings of the core use the setting giving least inductance. Adjust the core of L2 for maximum signal. Set the tuning gang at the minimum capacitance and the signal generator to 105 Mc/s. Adjust C13 to receive the signal and C7 for maximum output. Repeat the inductance trimming at 100 Mc/s—the capacitance trimming at 87.5 Mc/s, and using these frequencies readjust inductance and capacitance in turn until no further

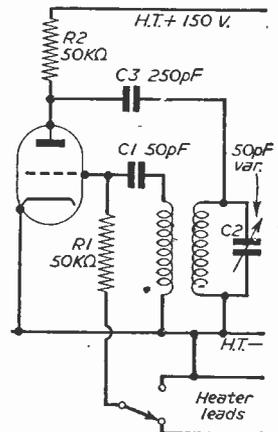


Fig. 6.—Circuit of a test oscillator which may be made up for alignment purposes.

Power Supplies

This receiver needs 300-315 at 100 mA, and 6.3 volts 3 amps. Good smoothing is needed, and it is also a good plan to decouple the mains input leads with 0.05 μ F 1,000 volts, preferably mica capacitors. R30 should be mounted for free ventilation well away from any circuitry and above chassis level. Otherwise the power supplies can be of any convenient design the constructor chooses.

Note.—If by any chance you happen to receive a police broadcast on this receiver you are reminded that in no circumstances are you allowed to discuss what you hear with anyone.

A.M. Reception

So far, the emphasis has been on the alignment and construction for F.M. broadcast reception. For constructors who wish to receive any amplitude-modulated signals with this receiver, the following modifications are incorporated :

(a) The anode load resistor of V5 should be increased by placing in series with R15 another resistor of value 100,000 ohms. A switch should be arranged to short-circuit this for F.M. reception. At the same time, the lead joining C35 to the junction of R21 and C34 should be broken, and a single-pole double throw switch inserted as shown in Fig. 9 on the right.

(b) The loose end of C35 should be joined to the switch, and the two contacts to the junction of R21 and C34 on the one hand, and to the junction of R15 and C27 on the other. Fig. 9 makes this clear.

(c) The two switches referred to above can conveniently be of the Yaxley type, and ganged together.

By careful alignment of the R.F., F.C. and oscillator

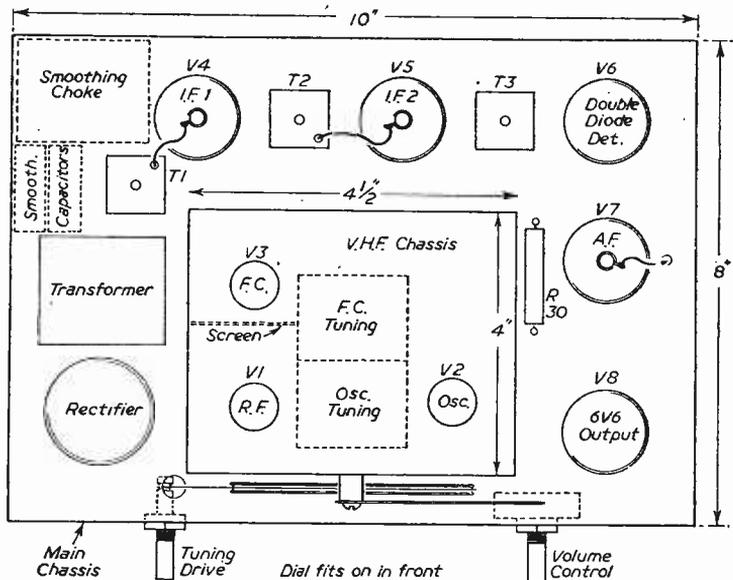


Fig. 7.—Plan of the layout showing valve positions.

circuits the frequency range covered may be extended down to about 60 Mc/s, which includes some of the television "sound" frequencies.

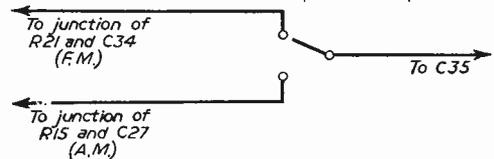


Fig. 9.—Switching to enable A.M. signals to be obtained.

Brema Monthly Survey

RADIO sales during September appear to have been affected by two opposing forces. During the early part of the month sales in all groups continued to be depressed as the result of the hire purchase restrictions imposed in July, whilst towards the end of the month sales of products in the higher price groups (radiograms and television) were stimulated as the result of the rumours of a possible increase in purchase tax.

The depressing effect of the hire purchase regulations was first noted in the August sales figures. Normally sales in September are considerably in excess of August, but, in fact, the figures for radio (79,000 sets) show that sales were only up 8 per cent. on the previous month. Radiogram sales rose from 11,000 to 19,000—a rise of 73 per cent. Television sales were lower than for last September.

Radio receiver sales at 756,000 from January/September, 1955, are 2 per cent. lower than last year, whilst radiogram sales are 2 per cent. up at 179,000, and television sales have increased by 12 per cent.

Ferroxcube Beads

THE inductance and H.F. resistance of a straight wire can be increased appreciably by threading it through a small bead of Ferroxcube. This fact is made use of in a variety of H.F. decoupling applications, including simple "grid stoppers" to prevent parasitic oscillation, and decoupling circuits in heater leads.

The use of Ferroxcube beads for decoupling heater wiring is particularly attractive in that there is no increase in resistance at D.C. or supply frequencies, though the H.F. resistance may be increased by an appreciable amount by the addition of a single 3 mm. bead. This large resistive component also reduces the risk of the decoupling elements themselves causing parasitic oscillation, since any tuned circuit formed by them will be heavily damped.

Two types of Ferroxcube bead are available from the Component Division of Mullard, Limited—type FX1666, which is suitable for applications involving relatively low radio frequencies, and type FX1667, for high-frequency circuits.



Making a Car Radio



DETAILS OF AN ECONOMICAL RECEIVER FOR THE CAR, INCLUDING NOTES ON ITS CONSTRUCTION AND INSTALLATION

By A. E. Pardy, B.Sc.

(Continued from page 737, December issue)

Preselector Tuning

MANY motorists prefer to employ preselector tuning in a car radio as this eliminates the need for accurate setting of the tuning condenser (which may move under a violent jolt) and, if all the components have to be purchased, the cost may actually be less.

The use of preset condensers for tuning a fixed inductance is not recommended because of vibration, but the use of tunable inductances offers a very satisfactory solution.

For preset tuning the adjustable inductances manufactured by E.T.A., Limited, appear the most suitable. The chassis drilling and cutting in the vicinity of the twin-gang should be modified to that shown in Fig. 9 and an aluminium bracket as shown should be cut to bolt over the opening and carry the inductances L4 to L9.

The inductances should be bolted in position by 2 B.A. bolts and the wiring to the tags nearest the adjusting screws carried out before mounting the bracket. Wiring can now be completed according to Fig. 11.

It is important when using these inductances to have C30 and C31 close tolerance to obtain full cover-

age of the waveband. C26, however, may need to be reduced in capacity to compensate for the capacity effects of the aerial and cable.

If a four station preselector arrangement is required it may be easier to buy a complete unit (TS42 is suitable) and wire it according to the diagrams supplied with it.

The manufacturers of these coils recommend that for better second channel reception the aerial should be capacity coupled by connecting it to the junction of R20 and L4, L5 and L6. This arrangement also reduces the capacity effect of the aerial and makes the receiver almost independent of aerial characteristics. It is a matter of experiment, therefore, to find the best arrangement.

The setting of the inductances is carried out by screwing the cores to approximately the position for the station required, remembering that each medium-wave coil covers 190 to 530 metres, each long-wave coil 850 to 2,000 metres, and that as the core is screwed out the wavelength decreases.

Thus when both induct-

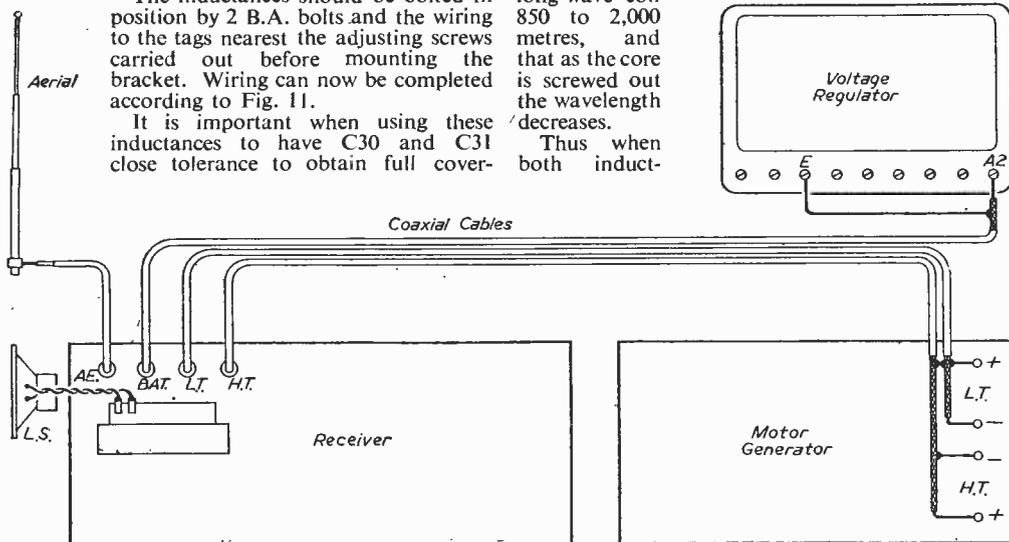


Fig. 8.—Complete installation wiring details.

Using TEST INSTRUMENTS



Part 13 of a Series of Articles
Dealing with the Practical Application
of Standard Test Equipment



(Continued from page 774 December issue)

Phase Measurement (43)

It will be remembered from our discussion of Lissajous' figures earlier in this series that the character of the more complex figures depends not only upon the frequency ratio of the two applied signals but also upon their relative amplitude and phase. We found that if the "X" and "Y" signals are of equal frequency and phase a straight diagonal line is produced. It was also illustrated that the diagonal line opens up to form an ellipse as the phase between the two signals alters, and that the width of the ellipse is a maximum when there is a 90 deg. phase angle between the two voltages. Moreover, it was shown that the width of the ellipse decreases as the phase angle further increases until the signals are exactly out of phase, when the diagonal line merely takes up the opposite slope.

This feature can be most useful for determining the magnitude of phase shift occurring, for example, in the phase-splitter stage of an audio amplifier. To check that the two signals appearing between the grids of the output valves are exactly out of phase, the "X" and "Y" plates should be connected between them, as shown in Fig. 50. The common earth terminal on the scope should be connected to the chassis of the amplifier and a signal, preferably a pure sine-wave, should be applied to the input of the amplifier in the usual way. If the correct phase shift of 180 deg. is taking place, then a straight diagonal line will resolve on the screen; furthermore, if the line is set at an angle of exactly 45 deg. it means that an equal voltage is being applied to each output valve grid.

This principle can be applied to check the overall phase shift of an amplifier by connecting the scope as shown in Fig. 51. It will be appreciated, of course, that for tests of this kind it is necessary to switch off or disconnect the timebase from the "X" plates.

Fig. 51 shows that the output of the A.F. oscillator is connected direct to the "Y" plate terminal, and that the oscillator is connected to the amplifier input terminals, via a variable potentiometer P. The output of the amplifier is connected to the "X" plate terminal, ensuring that the amplifier is correctly loaded for resistor R.

The potentiometer should be adjusted until the "X" and

"Y" voltages are approximately equal, the actual slope of an ellipse or a line indicating the ratio of the "X" to "Y" voltages. If the "X" and "Y" sensitivities are not equal, however, the difference will need to be counteracted by putting the "X" "Y" voltages slightly out of balance, by means of P, to correspond.

Zero or 180 deg. phase shift through the system will be revealed, as we have already seen, by the formation of a diagonal line on the screen. An ellipse indicates that a phase shift is occurring, and the magnitude of this shift can be calculated quite easily by centring the trace behind a graticule, as shown in Fig. 52. The sine of the phase angle will then be equal to $Y1/Y2$.

The phase shift may be taken over the entire audio-frequency range if necessary. Frequency distortion over the range will show as an alteration in the slope of the line or ellipse, while the presence of harmonic distortion will cause the line or ellipse to kink, provided, of course, that a pure sine wave is used to start with.

Testing with Square Waves (44)

Square waves are made up of a sine wave equal to the fundamental frequency plus a spectrum of frequencies, or sine waves, consisting of odd harmonics of the fundamental—that is frequencies three, five, seven, etc., times the fundamental. Since a perfect square wave consists of odd harmonics up to infinity it is never obtained in practice. Nevertheless, a good representation of a square wave is obtained provided harmonics of the fundamental

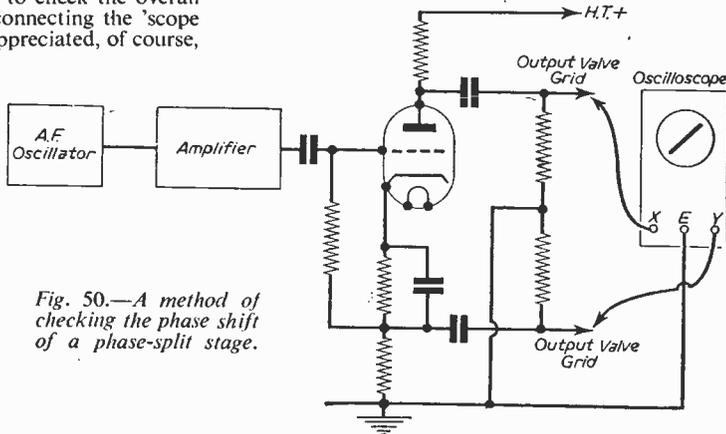


Fig. 50.—A method of checking the phase shift of a phase-split stage.

up to about 10 are present. Some idea how a square wave is formed is illustrated by Fig. 53. Here the effect of adding consecutive odd harmonics up to the seventh to a sine wave is shown. It will be observed that as each harmonic is added so the waveform resembles more closely a square wave.

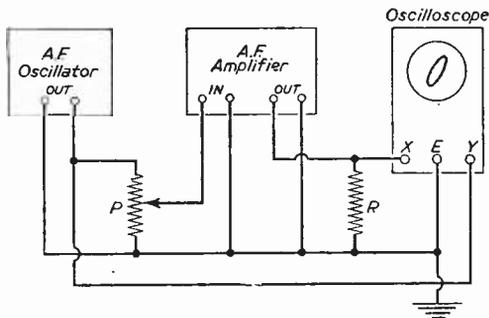


Fig. 51.—Checking the overall phase shift of an amplifier.

It will be seen that the "body" of the square wave is formed mainly of the lower frequencies and the sharply rising and falling leading and trailing edges occur as the result of the higher order harmonics. Clearly, then, if we use a fairly good representation of a square wave as a test signal and observe the signal on a 'scope after it has passed through a network of circuits, or an amplifier, we can get a good idea as to how the circuit or amplifier is behaving.

For example, if the circuit has a poor low-frequency response, instead of the square wave appearing as shown in Fig. 54, it will reflect such conditions by tilting as shown in Fig. 55(a). The concavities in the top of the wave, as illustrated in Fig. 55(b), indicate that, apart from a poor low-frequency response, the circuit is giving rise to a low-frequency phase shift.

Poor high-frequency response is revealed where the corners are rounded, as in Fig. 55(c); excessive attenuation of the higher frequencies is indicated when the wave deteriorates to that shown in Fig. 55(a).

Excessive high-frequency response in the circuit would produce a wave similar to that at Fig. 55(e), where "ringing" of the circuit is provoked.

Excessive low-frequency response in the circuit is indicated by the wave at Fig. 55(f). Such occurs in circuits which are designed to boost the lower


frequencies and attenuate the higher frequencies.

Waveforms G and H show differentiation as the result of progressive worsening low-frequency responses, coupled with degrees of phase shift. This effect is, as is well known, purposely introduced into certain circuits, such as the synchronising section of a television receiver. In an audio-frequency amplifier, however, the effect might well be produced by one of the inter-stage coupling capacitors becoming very high in value, and thus permitting the passage of only the highest frequencies.

Test Precautions (45)

When a 'scope is used for square-wave testing it is essential in order to get a true picture of the resulting waveform to keep the capacitance between the 'scope test leads to an absolute minimum.

Fig. 52.—Measuring phase shift.

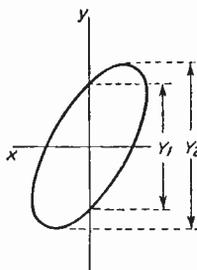

We have already seen how attenuation of the higher frequencies can distort a square wave, and such attenuation is liable to result due to excessive shunt capacitance being introduced across the input terminals of the 'scope itself.

In this respect, therefore, the 'scope leads should be as short as possible and orientated for maximum separation. It is pointless to endeavour to obtain a true indication if the test instrument and wiring themselves are responsible for distortion. It is always best to secure mechanically the 'scope leads to the test points in the equipment under examination, as opposed to holding the leads with one's fingers, for this latter procedure often results in undesirable shunt capacitances which are liable to provoke misleading traces.

If the test demands rapid tracing round the circuit with the 'scope leads, then a low-capacitance probe unit should be connected to the high-impedance test lead so that the normal working of the circuit is not severely disturbed.

Unfortunately, these requirements often conflict with those necessary to minimise hum pick-up in the 'scope test leads. By hum in this respect is meant 50 c.p.s. mains voltage which is induced into the "Y" connecting lead, considerably magnified by

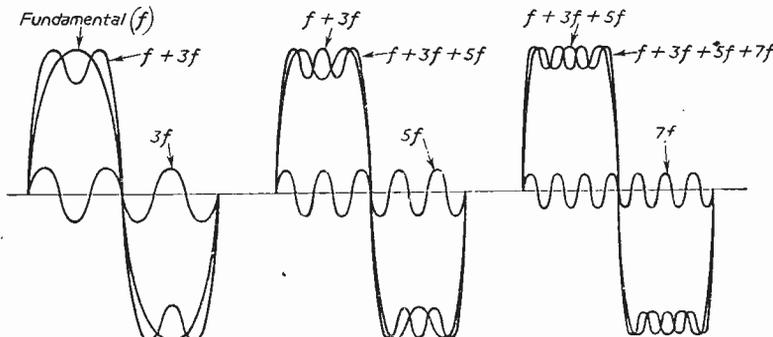


Fig. 53.—Curves showing the formation of a square-wave.



Fig. 54.—A good square-wave.

the deflection amplifier, and superimposed on the main image in various forms.

The effect is largely aggravated as the result of the high impedance input to the "Y" plate and deflection amplifier, and is well demonstrated simply by touching

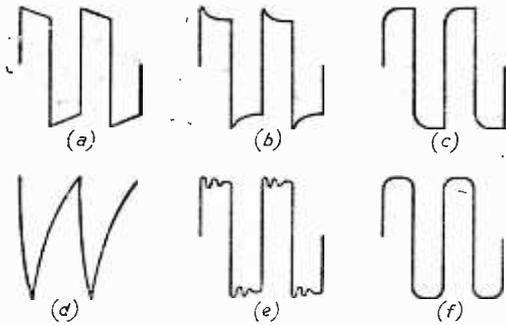


Fig. 55.—Distorted square waves.

the "Y" input terminal and turning up the gain of the deflection amplifier.

Any mains frequency picked up this way will cause a movement of the spot in addition to the deflection due to the main image. The waveform produced, therefore, will be the sum of these two waves. If the main image is below the frequency of the mains the presence of this ripple voltage will introduce harmonics which may or may not be an exact multiple of the waveform under examination. If the examination frequency is equal to the mains frequency mains hum might well introduce a distortion content to the waveform under examination and consequently give rise to very misleading results. When the examination frequency is slightly higher than the mains frequency, but still within the audio range, the amplitude of the waveform under examination will continually change at a rate depending on the beats between the two frequencies (see Fig. 56).

As the examination frequency rises the increasing beat between the two frequencies will result in a somewhat blurred image, in some cases two entirely distinct waves may resolve, and to add to the confusion each wave often hobs up and down with respect to each other (see Fig. 57.)

Disturbances of this nature are more prone to develop when the examination frequency is of very small amplitude, and when it is necessary to employ

a high gain setting on the deflection amplifier in order to obtain sufficient vertical deflection of the trace.

In most cases it can be eliminated by using a screened lead to connect the 'scope to the test point in the circuit, but this, of course, conflicts with the previous stipulation we made regarding shunt capacitances. Nevertheless, a compromise can often be found in practice which reasonably satisfies both conditions.

Detecting Hum (46)

While we are on the subject of hum it is interesting to note that a 'scope can very successfully be employed for detecting and tracking down hum caused by

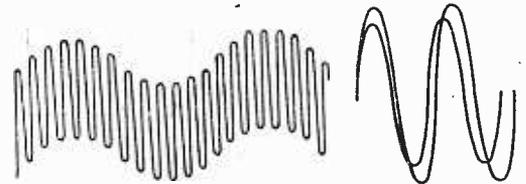


Fig. 56.—Showing the effect of 50 c.p.s. mains hum superimposed on an examination waveform.

Fig. 57.—The formation of two distinct waves as the result of hum pick-up.

inadequate smoothing, leakages, inductive pick-up, etc., in a broadcast or television receiver.

For tests of this kind the 'scope should be properly earthed to the receiver chassis, and the "Y" terminal, via the deflection amplifier, connected, through an isolating capacitor, to various points along the H.T. line starting at the output or cathode of the H.T. rectifier. The effect of the H.T. filter circuits will be readily seen if the T.B. is adjusted to give two or three waveforms. The desirability or otherwise of adding additional smoothing components can be assessed without much trouble, and a defective component used in the H.T. smoothing circuits will be quickly revealed by this means.

The presence of modulation hum will be shown on the screen by applying an unmodulated signal from a service oscillator, or signal generator, to the aerial terminals of the receiver, and adjusting the tuning of the receiver to correspond to this frequency.

Figs. 58 and 59 respectively show full- and half-wave rectifier circuits together with ripple waveforms

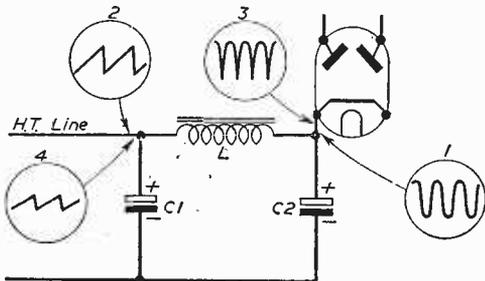


Fig. 58.—A full-wave rectifier circuit; waveforms 1 and 2 normal, 3 due to C2 becoming open-circuit and 4 due to L becoming open-circuit. Ripple frequency 100 c.p.s.

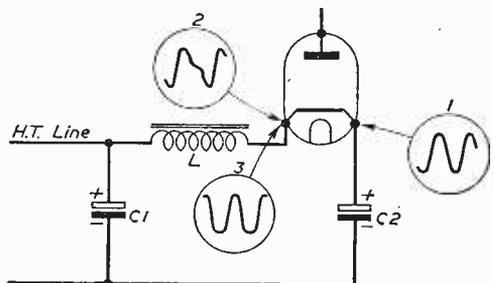


Fig. 59.—A half-wave rectifier circuit; waveforms 1 and 2 normal, and 3 due to L becoming open-circuit. Apart from the 50 c.p.s. ripple frequency, waveforms on the H.T. line are similar to those in the full-wave circuit.

to be expected at either side of the filter choke under both normal and fault conditions.

R.F. and I.F. Applications (47)

Apart from A.F. applications, the relatively high input impedance of the 'scope's deflection amplifier

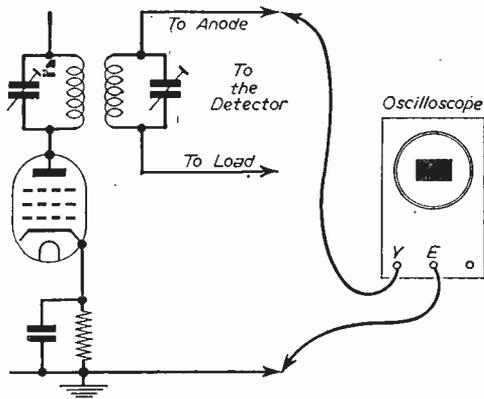


Fig. 61.—A method of connecting an oscilloscope for observing a modulated R.F. waveform.

makes the instrument ideally suitable for testing in the R.F. and I.F. circuits of a broadcast receiver. The instrument can be applied across the tuned circuits without imposing severe loading, and can thus be used to check R.F. stage gain by using a method similar to that already described.

As when making comparative R.F. measurements with a valve voltmeter, a certain degree of additional capacitance will be reflected across the tuned circuit, and for this reason the associated circuit may require adjustment when the 'scope is connected. It should, of course, be restored to normal after the test has been performed.

Owing to the higher frequencies involved in the R.F. section of a receiver, as opposed to the A.F. section, and the relatively low high-frequency response of the deflection amplifier in standard 'scopes, it is seldom possible to obtain a waveform representing one or two complete cycles of R.F. (I.F.). Also, in some oscilloscopes the maximum repetition frequency of the T.B. is insufficient to permit the resolution of less than about six complete waveforms at low R.F.

Nevertheless, even in its limited form the 'scope represents a valuable aid for checking at R.F., since observation of the R.F. waveform itself is of no particular importance. Indeed, it is generally desirable to adjust the T.B. to a frequency which is

a submultiple of the actual modulation frequency so that the individual cycles of the R.F. signal are so close together as to appear on the screen as a rectangle of illumination. Then when the R.F. is modulated the modulation signal will appear as an envelope at the top and bottom of the R.F. signal, as shown in Fig. 60.

The modulated R.F. signal can thus be traced through the various stages of a receiver, and the

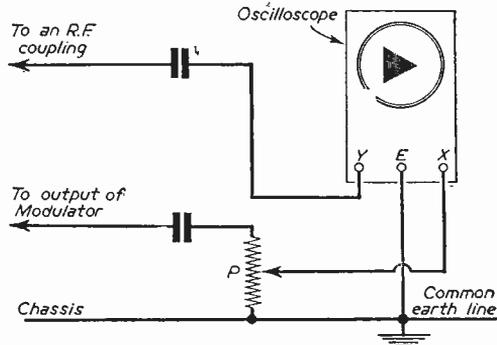


Fig. 63.—The circuit arrangement for checking modulation depth.

final signal observed at the output of the final I.F. (R.F.) amplifier, with the 'scope connected as shown in Fig. 61. Ideally, the waveform should correspond to that at Fig. 60, but before it is concluded that distortion is occurring in the I.F. (R.F.) stages the waveform should be checked at the generator itself.

The trace at Fig. 62 (a) indicates distortion as the result of overloading of the I.F. (R.F.) amplifiers, possibly caused by faulty biasing or failure of the A.V.C. system. If the waveform has a rough sawtooth edge on it, after the style of that depicted at Fig. 55(b), it can be assumed that the I.F. (R.F.) stages are oscillating, either as the result of faulty decoupling or screening.

Checking Depth of Modulation (48)

The C.R.T. provides a simple method of checking the depth of modulation of a transmitter or modulated oscillator. The T.B. is switched off and the "X" and "Y" plates connected to the circuit as shown in Fig. 63. The oscillator is modulated with a constant frequency in the region of 400 c.p.s. A trace whose dimensions may be modified by adjusting the potentiometer P will then form on the screen. Traces to be expected will be shown next month; the depth of modulation may be calculated from the expression $x-y \times 100$ per cent./ $x+y$. Trace b shows 100 per cent. modulation, trace c over 100 per cent. modulation, and trace d severe modulation distortion as the result of over-modulation and non-linear operation.

(To be continued)

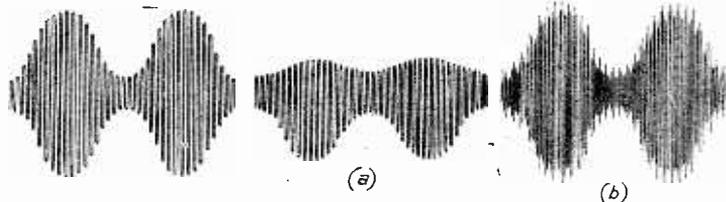


Fig. 60.—A modulated R.F. waveform (ideal).

Fig. 62.—Showing a distorted modulated R.F. waveform at (a), and at (b) the waveform indicates R.F./I.F. instability.

OUR COMPANION JOURNAL
PRACTICAL TELEVISION
 1]- Every Month

Pye Telecommunications Announce a NEW TWO-WAY RADIO EQUIPMENT

Demonstrations of a new equipment, designed in Cambridge, have been given in London recently to representatives of Police and Fire Services, Local Authorities and Industrial Organisations. This equipment has been designed to defeat the chronic shortage of two-way radio channels.

Known as the Pye "Ranger" it is the solution to the frequency shortage which is hamstringing mobile radio users in Great Britain!

The new equipment operates on a channel spacing of only 25Kc/s—a quarter of the customary spacing—thus potentially quadrupling the number of mobile radio channels. Robust construction, excellent performance and carefully selected components make it capable of operating under arduous conditions and in any weather.

This mobile radio is designed for fitting in the dashboard of ordinary cars and vehicles. The price of the equipment, notwithstanding its many-times improved specification, is approximately the same as that of earlier equipments which it now replaces.

Please write for full details



Telecommunications

CAMBRIDGE ENGLAND



PYE TELECOMMUNICATIONS LTD., NEWMARKET ROAD, CAMBRIDGE. TELEPHONE TEVERSHAM 3131

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and impregnated. Primaries 200-230-250 v. 50 c/s Screened. TOP SHROUDED DROP THROUGH

250-0-250 v. 70 mA, 6.3 v. 2.5 a	13/9
250-0-250 v. 70 mA, 6.3 v. 2.5 a	16/9
300-0-300 v. 70 mA, 6.3 v. 2.5 a	16/9
350-0-350 v. 80 mA, 6.3 v. 2.5 a	18/9
250-0-250 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
300-0-300 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
350-0-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
350-0-350 v. 100 mA, 6.3 v. 4 a, C.T.	23/9
0-4-5 v. 3 a	23/9
350-0-350 v. 150 mA, 6.3 v. 4 a, 5 v. 3 a	29/9

FULLY SHROUDED UPRIGHT

250-0-250 v. 60 mA, 6.3 v. 2 a, 5 v. 2 a	17/6
Midget type 2i-3-3in.	17/6
350-0-350 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a	19/9
250-0-250 v. 100 mA, 6.3 v. 4 v. 4 a	26/9
C.T. 0-4-5 v. 3 a	26/9
250-0-250 v. 100 mA, 6.3 v. 6 a, 5 v. 3 a	31/-
for R1355 conversion	31/-
300-0-300 v. 100 mA, 6.3 v. 4 v. 4 a	28/9
C.T. 0-4-5 v. 3 a	28/9
350-0-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	23/9
350-0-350 v. 100 mA, 6.3 v. 4 v. 4 a	27/9
C.T. 0-4-5 v. 3 a	27/9
350-0-350 v. 150 mA, 6.3 v. 4 a, 5 v. 3 a	33/9
425-0-425 v. 200 mA, 6.3 v. 4 a, C.T.	49/9
6.3 v. 4 a, C.T., 5 v. 3 a. Suitable William Amplifier, etc.	49/9
450-0-450 v. 250 mA, 6.3 v. 6 a, 5 v. 3 a	69/9

E.H.T. TRANSFORMERS

2,500 v. 5 mA, 1.1 a, 2-0-2 v. 1.1 a for VCR97, VCR517, etc.	36/6
--------------------------------------------------------------	------

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c.s., 120 v. 40 mA	7/9
130 v. 50 mA, 6 v. 3 a	14/9

SMALL POTTED MAINS TRANSF. Removed from New Ex-Govt. units. Primary 0-200-250 v. Secs. 250-0-250 v. 80 mA, 6.3 v. 2 a, 5 v. 2 a. Size 3i x 4i x 3in.

FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/s primaries 6.3 v. 1.5 a, 5/9; 6.3 v. 2 a, 7/9; 0-4-6.3 v. 2 a, 7/9; 12 v. 1 a, 7/11; 6.3 v. 3 a, 8/11; 6.3 v. 6 a, 17/6; 12 v. 3 a or 2.4 v. 1.5 a, 17/6.

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 1 a, 11/9; 0-9-15 v. 3 a, 16/9; 0-3.5-9-17 v. 4 a, 17/9; 0-3.5-9-17.5 v. 4 a, 18/9; 0-9-15 v. 5 a, 19/9; 0-9-15 v. 6 a, 22/9.

SMOOTHING CHOKES

250 mA 5 H 100 ohms	11/9
150 mA 7-10-250 ohms	11/9
100 mA 10 H 200 ohms	8/9
80 mA 10 H 350 ohms	5/6
60 mA 10 H 400 ohms	4/11

OUTPUT TRANSFORMERS

Midget Battery Pentode 66; 1 for 35A, etc.	3/9
Small Pentode 5,000Ω to 3Ω	3/9
Standard Pentode 5,000Ω to 3Ω	4/9
Standard Pentode 7,000Ω to 3Ω	4/9
Standard Pentode 10,000Ω to 3Ω	4/9
Multi-ratio 40 mA, 30; 1, 45; 1, 60; 1, 90; 1 Class B Push-Pull	5/6
Push-Pull 10-12 watts 6V6 to 3n or 15Ω. Sectionally wound	16/9
Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15Ω	16/9
Push-Pull 15-18 watts, 6L6, KT66	22/9
Push-Pull 20 watts, sectionally wound 6L6, KT66, etc., to 3 or 15Ω 47-9	22/9
Williamson type exact to spec.	85/-

SILVER MICA CONDENSERS. 5, 10, 15, 20, 25, 30, 35, 40, 50, 100, 120, 150, 200, 230, 300, 400, 500, 1,000 (.001 mfd.), 2,000 pfd. (.002 mfd.). 6d. each; 3/9 doz. One type.

H.T. ELIMINATOR AND FRICKLE CHARGER KIT. Input 200-250 v. A.C. Output 120 v. 40 mA. Fully smoothed and rectified supply to charge 2 v. accumulator. Price with louvered metal case and circuit, 29/6. Or ready for use, 8/9 extra.

EX-GOVT. TRANSFS, 230/250 v. 50 c/s. 8.8 v. 4 a, 9/9; 460 v. 200 mA, 6.3 v. 5 a, 27/9; 325-0-325 v. 150 mA, 6.3 v. 4-6 a, 5 v. 2-3 a, 28/9; Carr. on following types, 5/- extra. 400 v. C.T. 150 mA, 4 v. 6 a, 6.3 v. 6 a, 6.3 v. 0.6 a, 4 v. 6 a, 4 v. 3 a, 4 v. 3 a, 4 v. 3 a, 5 v. 2 a, 22/9.

EX-GOVT. AUTO TRANSFORMERS 50 c/s. Double wound 10-0-200-220-240 v. to 10-0-275-295-315 v. 1,000 watts. Suitable for 100 v. to 230-250 v. or reverse if windings series connected. 59/6.

EX-GOVT. SMOOTHING CHOKES 250 mA, 10 H 50 ohms ... 14/9 150 mA, 10 H 100 ohms ... 11/9 150 mA, 6-10 H 150 ohms Trop. ... 6/9 100 mA, 10 H 150 ohms Tropicalised ... 3/11 L.T. type 1 amp, 2 ohms ... 2/9

EX-GOVT. METAL BLOCK (PAPER) CONDENSERS 4 mfd. 500 v. 2/9; 4 mfd. 1,500 v. 4/9; 8 mfd. 500 v. 6/9; 8 mfd. 500 v. 5/9; 15 mfd. 500 v. 6/9.

EX-GOVT. E.H.T. SMOTHERS 42 mfd. 8,000 v. cans, 1/11; 25 mfd. 4,000 v. Blocks, 4/9; 5 mfd. 2,500 v. Blocks, 3/9; .5 mfd. 3,500 v. cans, 3/3; 1.5 mfd. 4,000 v. Blocks, 5/9.

CONTROL PANEL with six position, 3 wafer Yaxley switch, pointer knob, 2 S.P.S.T. switches, various plugs and sockets. Only 1/6.

EX-GOVT. BLOCK ELECTROLYTIC'S. 16-16 mfd. 350 v. 1/9; 8-16 mfd. 550 v. 1/11; 1,000 mfd. 6 v. Can with clip, 1/9.

EX-GOVT. VALVES (NEW)

1T4	7/9	6V6GT	6/9	6AT6	7/9
1R5	7/9	6X5GT	7/9	EL32	3/9
1S5	7/9	807	7/9	EF36	4/9
5Y3G	8/11	12A6	7/9	EB91	8/9
5Z4G	9/9	15D2	4/9	EF91	7/9
6KT7	5/11	25Z4G	9/9	KT66	11/9
6K6G	9/9	35Z4GT	10/6	KT34	8/9
6SN7GT	8/9	6L6G	11/9	SP41	1/11
6P6G	7/9	MH4	4/9	SP61	2/9
EF39	5/9	EBC33	6/9	PX25	14/9

RF26 UNITS BRAND NEW, CARTONED. Only 29/6. Carr. 2/6.

RADIO SUPPLY CO. (Leeds) LTD.

32, THE CALLS, LEEDS, 2 (For Terms see full page advert.)

VALVES

EF50	4/-	VU39	8/6
EF39	7/-	VU134	8/-
EF36	4/-	VU508	8/6
EF37A	9/-	EF50(Syl)	
EF54	5/-	Pen 25	5/-
EC52	5/-	VP23	4/-
EC54	5/-	12J5	5/-
EL32	6/-	VU120	4/-
EL50	8/6	1A3	4/-
EBC33	7/6	CV286	7/-
8D3	8/6	6AG7(M)9/-	
6AM6	8/6	6AC7	7/-
EB34	2/-	717A	9/-
EA50	2/-	6H6	2/6
D1	2/-	RK34	2/6
1T4	7/-	VU111	3/-
3S4	8/6	VU133	3/-
1R5	7/6	VR66	3/6
1S5	7/6	SP61	2/6
3A4	6/-	SP41	2/6
CV201	7/-	6X5	8/6
6SA7	7/6	6B4	4/-
6V6	8/6	U22	8/-
6SN7	8/-	HL2	4/-
6SL7	6/-	Pen 220	4/-
6SK7	4/-	6J5	5/-
6SJ7	6/-	6J7	7/6
6SH7	6/-	12SK7	6/-
6N7(M)	8/-	807	6/-
6L6(M)	12/-	1L4	4/6
5Z4	8/6	CV287	7/6
5U4G	8/6		

TRANSFORMERS

- ALL INPUTS. 230-250 volt. 50 c.p.s.
- (1) 350-350 v. 150 ma. 6.3 v. 4 a., 6.3 v. 2 a., 5 v. 3 a. 30/-.
 - (2) 350-350 volt 200 ma. 6.3 4 a., 5 v. 3 a. £2.
 - (3) 275-275 volt. 6.3 v. 4 a., 6.3 v. 2 a. £1.
 - (4) 350 v. 250 v.—250 v. 350 v. 6.3 v. 4 a., 4 v. 2 a. £1.
 - (5) 350-350 volt. 100 ma. 0-700 volt. 4 volt 4 a., 4 volt 2 a., c.t. 22/6.
- 5/- Carriage on all above Transformers.

CHOKES for above:
 (1.) 10/- (2.) 15/- (4.) 9/- (5.) 9/-

BATTERY CHARGER TRANSFORMERS
 Outputs: 5, 11, 17 volt, 1½ amp. 13/6. Same output 4 amp. £1.

VINERS

MIDDLESBROUGH
 26, EAST STREET, MIDDLESBROUGH
 (Tel.: Mid 3418)

TA 12G

U.S.A. BENDIX TX. (Brand New) £6. Carr. paid (mainland).

TX 1403

Tx covers 2-9 m/c. Valve line-up 2 6V6, 1 EBC33, 1 807. (Less valves.) £13.10.0.

RADIO ALTIMETER

U.S.A. (New Condition) Less Valves & Dynamotor £1. Beautiful job and cheap.

F.M. WALKIE-TALKIE

38/43 m/c. "88" Set. (Less valves.) £15.0. Battery Boxes 10/- each.



On Your Wavelength

BY THERMION

What's in a Name ?

I OCCASIONALLY receive a letter from a reader who disagrees with my views, complaining that I hide behind a nom-de-plume. My view would be no different if they appeared under the name of Bill Smith, Dick Jones, or Harry Brown. You must presume, therefore, that my name is Thermion, and as the name is associated with an address, it is a misnomer to say that I write anonymously. Even contributions which are published without an author's signature can hardly be called anonymous contributions, since they appear under the sponsorship of the editor and publisher, and any correspondence ensuing is received and dealt with.

Anonymous letters, however, are in a totally different category. The slimy creatures who resort to the reprehensible practice of writing letters without a name or address or with a false name and address are those who really shield behind anonymity, and that is why their communications are always consigned to the waste-paper basket.

There is also the fierce critic who wants to let off steam and ends with the words, "I dare you to publish this." Such communications are never published. No one has a right to demand publication of offensive letters. Courteous letters receive courteous replies and courteous treatment in print. If you have the courage of your convictions, sign your proper name and address. Write in a calm frame of mind. To lose your temper is to lose your case. It is an old saying that, "if the cap fits, wear it," and those readers who like wearing caps should not suffer from swollen heads. I like to have letters of criticism and realise that not everyone will agree with my viewpoint. Discussion is stimulating, and both sides can be wiser after a friendly debate.

TV. versus Radio

I AM not surprised that the number of people who listened to the radio between 6 and 11 p.m. from July to September last year was very much lower than in the corresponding period in 1954. According to the BBC Audience Research Department, only 11.6 per cent. of the adult population were listening at any moment compared with 13.6 per cent. the year before. "This decrease is partly due to a further flow of listeners to television." It is estimated that the average size of the listening audience is 23½ million in the July-September quarter, against 26 million the previous year. That is, of course, to be expected.

One outstanding fact, however, is this. The interest in experiment and the construction of receivers is as strong to-day as it ever was, and the circulation of this journal and the volume of business done by our advertisers provides ample evidence of it. Each year a new generation of constructors enters the field, and as a few drop out there is a corresponding influx of new recruits. The number of people building television receivers continues to increase. There are far more home-built television receivers in operation than is realised by the BBC. I do not think that

sound radio will ever die out, but I think that within 10 years very much less listening will be done. The novelty, to a large extent, has worn off. The new generation was born to radio and television, and it is of little novelty to them. Their interest will be in space travel. How interesting it will be when the first radio signals are received from the moon—far more exciting and epoch-making than those famous first signals radiated between Poldhu and Newfoundland by Marconi in 1897. Indeed, it is radio which has made space-travel possible.

Unfair Competition

IT is said that the BBC television programmes are more than holding their own with ITA and, having looked in to some of the ITA programmes, I can well believe it. ITA are not finding it too easy to sell programme time. I think, however, that the BBC has an advantage over ITA in that it is able over the radio to advertise its television programmes, a facility denied to ITA. It is true that most newspapers to-day give the ITA programmes, but some of the latter have been poorly supported. Some of the viewers may have seen the Editor of this journal on a recent Saturday in a programme entitled "Winter Motoring." He was appearing as editor of our companion journal, *Practical Motorist and Motor Cyclist*.

Tape Recorders

INTEREST in tape-recording continues to increase judging from the number of letters we receive on this subject. It is still, however, an expensive instrument, and unnecessarily so, in my opinion. I can understand that in the early days, with a very limited demand, tooling and production costs had to be covered on a comparatively small output, but to-day the demand is large and it will grow even larger. The manufacturer of tape decks who takes the bold stroke of lowering his price will reach a large public and reap the benefit. Who will be the first to make the move ?

Midget Receivers

MY recent appeal for designs of midget receivers produced some ingenious designs, one of which has been published herein. They all, however, exhibited the usual defect—the power supply was altogether too large to make the receiver a real midget. Yet in America there are large numbers of really small commercial battery-operated receivers which can easily be slipped into the pocket. Cannot our battery manufacturers over here get down to this and produce a real midget layer-laid battery for L.T. and H.T.? Cannot our valve manufacturers get down to producing some really tiny valves which require a very low voltage? I can assure them that the demand for such a receiver, which can be very handy on special occasions, is enormous. This journal will undertake, I am certain, to issue a blueprint for such a receiver if the components are made available.

A NOVEL Phase INVERTER

ECONOMICAL CIRCUIT FOR CLASS B WORK

By Hugh Guy

THE rather unusual circuit about to be described was developed primarily for use with a portable and lightweight high-power public address system, in which the high-tension supply for the amplifier up to but excluding the output stage was of the order of 200 volts. Furthermore, to keep the weight down, intervalve transformers were ruled out in the design, coupling being purely of the resistance-capacity type throughout.

The output stage itself consisted of two medium power triodes working in push-pull, under Class B conditions, this class of working being superior to Class A or AB from an efficiency point of view.

Class B has one major disadvantage, however, particularly when applied to triode output stages, and this lies in the amount of drive required. Since under these conditions the valves are normally maintained at cut-off, the drive supplied must carry the grids from cut-off to within a volt or two of zero grid bias. This drive, of which only the positive excursions are utilised in the actual production of signal output, is normally supplied through a step-up transformer to the grids of the output valves, but as such transformers were taboo in the design in question it was necessary to resort to alternative means, a difficult problem with the limitations imposed by the low H.T. voltage.

The circuit finally produced, however, provides a neat way of overcoming the difficulties, and can in fact produce drive which exceeds the value of H.T.

voltage. The circuit will therefore be of interest to builders of amplifiers working in Class B, particularly if the latter are to be used as modulators for amateur transmitters.

Phase Inverter

The circuit is a development of the simple phase inverter which uses equal anode and cathode loads. This basic circuit is shown in Fig. 1.

By using equal values of resistor for anode and cathode loads, the gain to the anode is the same as that to the cathode, and is approximately one. The signals appearing at the anode and the cathode are also 180 degrees out of phase with each other, and thus a push-pull drive is developed. As explained above, however, for Class B work that portion of the signal which is negative-going is not contributing any useful effort to the final output, being below cut-off in the final stage, and it could therefore be dispensed with. The available H.T. could then be utilised to the full in producing as much single peak positive-going drive as was formerly available as peak-to-peak drive.

Referring to the circuit of Fig. 1 again will enable the explanation which follows to be understood more clearly. If we label the anode and cathode loads R_L and R_K respectively, then the gain to the anode is:

$$G = \frac{\mu R_L}{(\mu + 1)R_K + R_a + R_L}$$

where μ is the amplification factor of the valve and R_a is the anode impedance.

Similarly the gain to the cathode is:

$$G = \frac{\mu R_K}{(\mu + 1)R_K + R_a + R_L}$$

It is thus easily seen why making the anode and cathode loads equal results in equal amplitude signals at the anode and cathode.

These formulae also make it apparent that if we could arrange for the loads to be switched off, as it were, each time a positive output becomes negative, then it would be possible to arrange that only positive outputs appeared, thereby dispensing with the unnecessary negative portion of the signal.

This discrimination between positive and negative outputs may be accomplished by means of a small diode, and in the circuit of Fig. 2 we see how this task is performed.

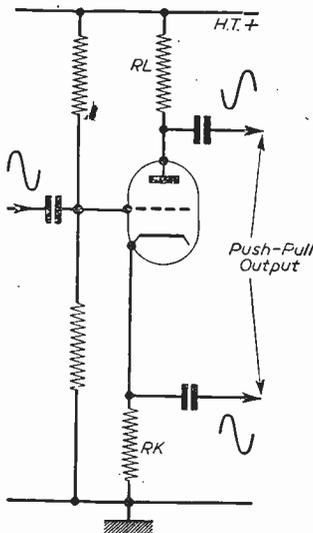


Fig. 1.—Basic phase inverter.

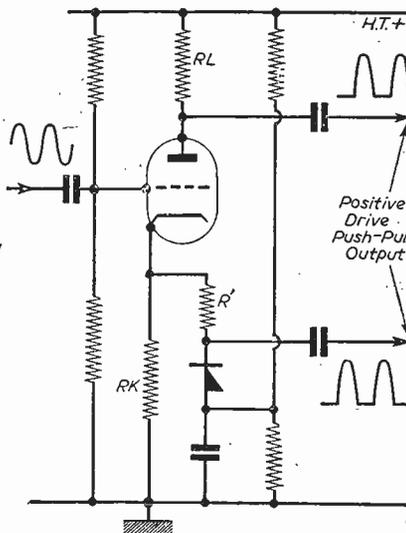


Fig. 2.—Modified phase inverter.

The cathode resistor is now two resistors, one of which (R_k) is about 10 times the value of the anode load R_L , while the other, R' , is approximately the same value as R_L . A diode is in series with R' to a decoupled point and the cathode output is taken from the junction of R' with this diode.

The Action

For the sake of simplicity consider the action of applying a simple sine wave to the grid of the phase inverter. On positive excursions of the grid the current in the valve will increase, thus producing a drop in anode voltage and an increase in the voltage across R_k . No current will flow in R' and the diode, as the latter is non-conductive to positive signals in the manner in which it is connected at present. Now if the value of R_k is much greater than that of R_L , then ten times as much signal will appear at the cathode as at the anode. To all intents and purposes, then, the anode signal is negligible by comparison.

On the negative excursion of the grid, however, the diode conducts and thus the output from the cathode will be shorted through the diode to the decoupled point, and will hence be zero. The effective cathode load is now R' in parallel with R_k , and is approximately equal to the anode load. Across the latter, therefore, will be developed nearly the same voltage as that across the cathode load.

If indeed R_k is made ten times the value of R_L , then using the formulae the relative signals at the two outputs can be determined for the two conditions, expressing the anode and cathode loads in terms of R_L .

When the input is positive-going the gain to the anode is :

$$G1 = \frac{\mu RL}{(\mu + 1) 10RL + Ra + RL}$$

while the gain to the cathode is :

$$G2 = \frac{\mu 10RL}{(\mu + 1) 10RL + Ra + RL}$$

The ratio of these two gains $G2/G1$ is seen to be the specified 10 to 1, and hence the unwanted output from the anode is only one-tenth of the useful output at the cathode.

Now when the input is negative-going the gain to the anode is :

$$G3 = \frac{\mu RL}{(\mu + 1) R' + Ra + RL}$$

and that to the cathode is :

$$G4 = \frac{\mu R'}{(\mu + 1) R' + Ra + RL}$$

Sticklers for accuracy will point out here that the cathode load is really the parallel combination of R' and R_k , but the expression for $G4$ is a good enough design approximation.

It is the ratio $G2/G3$ which we require to be as near to one as possible, since this ratio decides the relative amplitudes of the positive-going outputs from the cathode and anode respectively.

It will be seen that by equating $G2$ and $G3$ a value for R' can be found which

makes the outputs equal. This value is given by : $R' = RL - 0.9Ra/\mu$ approximately.

Hence, having selected a particular valve, and chosen a convenient value for R_L , the other values are determined from the formula and conditions set by it.

This information will enable the experimenter to design such a circuit using any triode, whilst for those who prefer a complete example a circuit is given below using the EC91 valve. This valve has a U.S.A. equivalent in the 6L34 valve, whilst on the surplus market the valve may be identified as the CV417.

How it Functions

A value is selected for R_L , 1 K ohms being suitable as it makes the calculations simple. The value of R_k is therefore made 10 K ohms, and on the $1a/Va$ characteristic curves for the valve is drawn this load-line of 11 K ohms through the H.T. point of 200 volts. A suitable bias point is chosen by inspection ; -1.5 volts will give an anode current of 3.2 mA. In turn, this current flowing through R_k will drop 32 volts across the cathode load. Hence, to maintain a grid-cathode bias of -1.5 volts, the grid must be biased to 30.5 volts. This is achieved by the use of two resistors, $R1$ and $R2$ in Fig. 3, of value 1 M and 180 K respectively. This working point on the curves gives an amplification factor of 90 and an anode impedance of 20 K ohms.

If R' is determined from its formula above it will be found that the nearest available value is 820 ohms, a value which gives only a slight inequality in anode and cathode gains.

Under no signal conditions no current is required to flow through R' , and the decoupled point to which the diode is connected at D in the figure should therefore be maintained at the cathode potential of 32 volts. This voltage can be obtained using the two resistors $R3$ and $R4$ as shown. The by-pass condenser is included to decouple the point D to earth, thereby shorting out any A.C. signal passing through the diode.

The values of gains $G2$ and $G3$ may now be

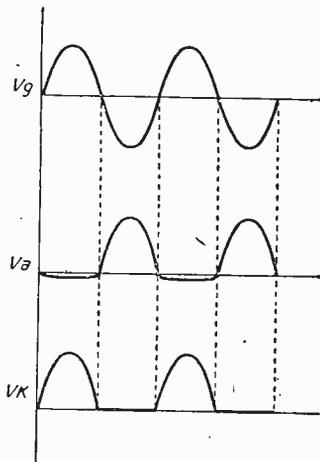
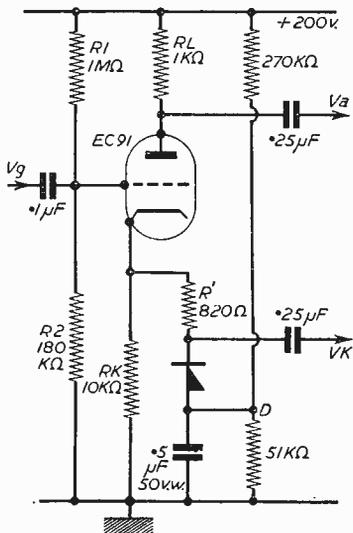


Fig. 3 (Left).—Practical Class B phase inverter. (Right).—Half sine-wave at anode and cathode for sine-wave at grid.

checked to see that there is no wide divergence between them, which would cause out-of-balance in the drive to the output stages.

The values used in this design give gains of 0.966 and 0.94 for G2 and G3 respectively. The out-of-balance resulting from so small a discrepancy is, of course, negligible. The maximum signal that can be obtained from each of the output terminals is of the

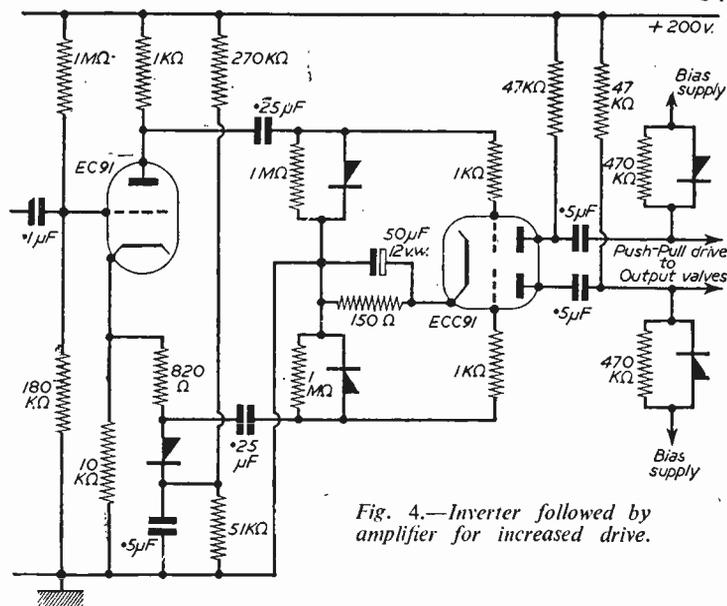


Fig. 4.—Inverter followed by amplifier for increased drive.

order of 18 volts peak without undue distortion.

Producing More Drive

It was mentioned earlier that the circuit can be used to produce drive which can be in excess of the H.T. voltage available. This remark as it stands is perhaps a little misleading, what is meant being that if the two halves of a sine-wave produced in this manner are added to re-form the original sine-wave after amplification, then the peak-to-peak value of such a sine-wave could be greater than 200 volts.

With the circuit as it stands at present, the peak output of 18 volts, a limit imposed by the cramping of the grid voltage/anode current characteristic of the valve, may be insufficient for the larger type of output triode, where, to produce Class B drive, the peak signal may have to exceed 100 volts.

If this were the case, it would be necessary to interpose a stage of amplification for each of the two drives between the inverter and the two output valves. Since each of the two amplifiers would only be handling unidirectional drive, approximately twice the normal swing would be available at each grid of the output valves.

The circuit to achieve this result is shown in Fig. 4, where it will be seen that in addition to the double-triode amplifying stage following the inverter, a slight modification is necessary to the phase inverter. The amplifier produces an unwanted phase reversal at the output, and to correct this the outputs from the inverter must be reversed. This is the purpose of the modification, which consists merely of reversing the connections of the diode.

The valve used as the drive amplifier is the ECC91, a double-triode with a shared cathode, on a B7G base.

The standing current in each triode is made high by use of a low value of cathode bias resistor, in order that the drive to each grid will enable the maximum use to be made of the available grid swing. This results in a large positive-going half sine-wave at each anode, these being passed to the output valves.

The ECC91 in Fig. 4 is biased to -1 volt when, with an anode load of 47 K and an H.T. of 200 volts an anode current of 3 mA flows. By using a common cathode resistor the average value current from both triodes is made to maintain the grids at -1 volt with respect to the cathodes. Hence, a bias resistor of 150 ohms is used, this being the nearest practical value to the desired resistor. The by-pass condenser of $50\mu\text{F}$ gives effective decoupling down to about 20 cps.

With this circuit arrangement the signal output from each anode will be 100 volts peak for an input to the phase inverter of about 4.5 volts. Thus, the peak-to-peak output equals the value of the H.T. voltage.

If the input is increased to 6 volts, then a composite signal of 240 volts will be obtained, illustrating what at first seems to be the impossible in the way of drive from a transformerless driver.

Any tendency for either triode to give a greater output than the other can be compensated for by making the anode load to the inverter a 1 K potentiometer. The output is then taken from the slider to the grid of the appropriate triode amplifier. The potentiometer is then varied until no signal is heard in a pair of phones connected in series with the H.T. lead to the centre-tap of the output transformer in the power stage. This latter test procedure is, of course, the one normally applied to any push-pull stage for correcting out-of-balance working.

Only one feature of the circuit remains to be explained: the presence of the diodes across the input grid-leads to the stages.

These diodes are D.C. restorers and are necessary to set the level of working of the half sine-waves. In the absence of these diodes the signal, which has now been "chopped in half" by the inverter, would tend to sit at its mean level at the following grids after passing through the coupling condensers. With the changing nature of the signal, which up to now for the sake of simplicity we have thought of as a sine-wave, the mean level will vary, and a lot of the unidirectional drive will be lost. By restoring the level at each grid to the "chopped-off" edge, however, the working level can never vary appreciably, and at all times the full unidirectional drive is utilised, regardless of the shape of the waveform.

The small crystal variety of diode, such as the CG-1-E, is quite suitable for all the diodes in the circuit.

Receiver Analyser/Valve Tester

A UNIT WHICH HAS WIDE APPLICATION IN THE WORKSHOP AND AMATEUR DEN

By "Experimenter"

WHILST carrying out repairs on radio receivers, the writer has often felt the need for a speedy means of checking the voltage or current of valves in their operating condition.

This has meant the removal of the chassis from the cabinet and breaking leads to valve pins or trying to measure voltage in difficult and inaccessible places.

The removal of a chassis can often be a tedious and time-wasting affair, and the breaking and subsequent repair of leads to valve pins almost impossible.

After some thought it was realised that the only solution to the problem was to construct an adaptor whereby the valve under test could be removed from the chassis and placed, still operating, in an easier and more accessible position.

The arrangement finally decided upon is shown in Fig. 1.

Design

The analyser consists of a panel of some insulating material such as paxolin upon which are set a number of valveholders of the type required by the individual constructor. These will be the actual test sockets into which the valve under examination will be plugged.

An input plug is mounted on the panel and is made up of the base of an international octal valve, firmly

secured and with the pins upwards, ready to receive the lead which will connect the chassis under test to the analyser.

A lead is taken from No. 1 pin of this plug to No. 1 pin of the first valveholder on the analyser and from there to No. 1 pin of the next holder and so on until all the No. 1 pins are wired in line. The same procedure is followed with No. 2 pin and so on until all the test sockets are wired up.

A closed circuit jack is then inserted in series between No. 1 pin of the input plug and No. 1 pin of the first test socket and this is continued with each lead until all the valveholders have been provided with a jack.

A lead is then taken from pin 1 of the input socket to the first of a series of plug holes of the aerial/earth type and this is continued until each pin of the input socket is connected to one of the eight plug holes.

One final terminal must be provided which may be connected to the chassis of the set under test to provide a negative reference point for use with valves where no direct connection is made with earth through the valve electrodes.

A connector must be made for each type of valveholder provided for on the analyser panel and these are made up as in Fig. 2. The connector consists of a

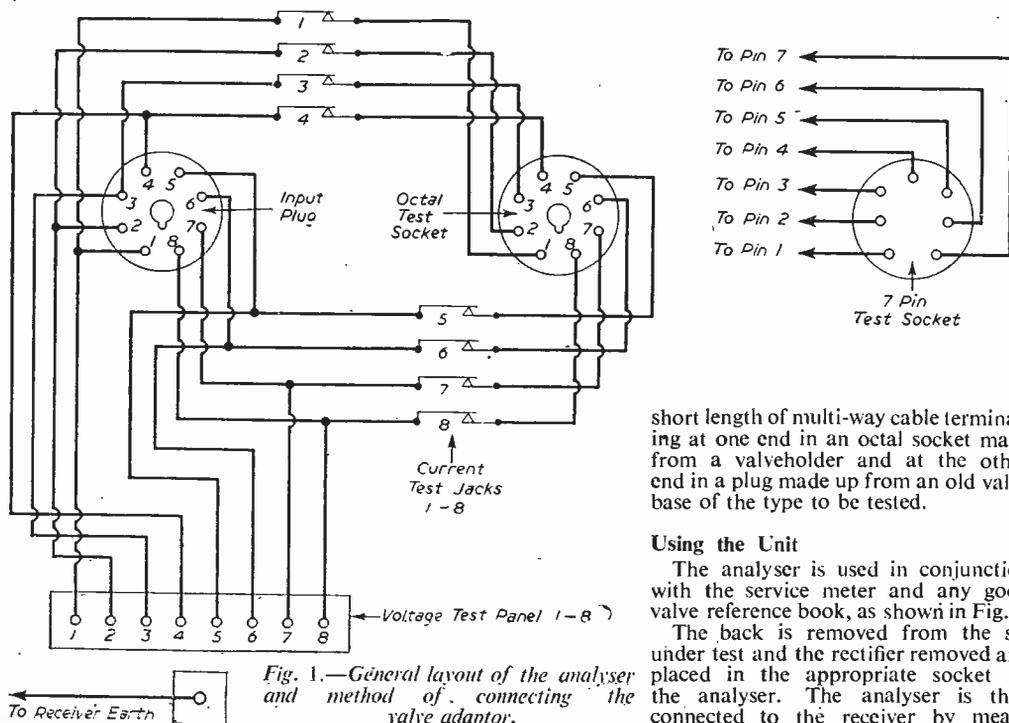


Fig. 1.—General layout of the analyser and method of connecting the valve adaptor.

short length of multi-way cable terminating at one end in an octal socket made from a valveholder and at the other end in a plug made up from an old valve base of the type to be tested.

Using the Unit

The analyser is used in conjunction with the service meter and any good valve reference book, as shown in Fig. 3.

The back is removed from the set under test and the rectifier removed and placed in the appropriate socket of the analyser. The analyser is then connected to the receiver by means

of the multi-way lead inserted in the vacant valve base.

Voltage measurements are made from the earth terminal of the analyser to the plug hole corresponding to the number of the valve pin as given in the reference tables.

Current can then be measured in any of the valve leads by the insertion of a jack plug connected to the meter in the jack socket corresponding to the valve pin number.

This procedure is then followed with any or all of the remaining valves, each one being replaced in the set after test.

When testing valves with top cap grids it is not normally required to make the grid connection although this

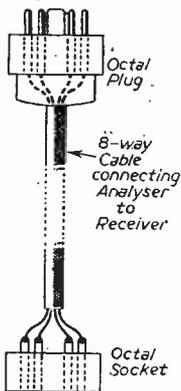


Fig. 2.—Details of the adaptor.

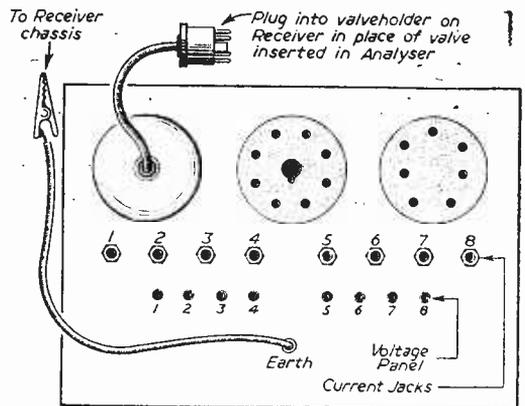


Fig. 3.—Panel layout of the instrument.

can easily be done with a crocodile clip on a short piece of wire.

Sound-reproducing Equipment on Show

A DISPLAY featuring a wide range of "Mimco" sound-reproducing equipment by Special Products Division of The Marconi International Marine Communication Co., Ltd., is on view in Marconi House, Strand, the site of London's old broadcasting station, 2LO. The exhibit embraces specimens of everything required for sound-reproduction systems on board ship or ashore, and illustrates how individual installations can be "tailored" to meet specialised needs, whether marine or industrial.

A typical central control for a medium sized installation feeding up to 60 loudspeakers is shown. This consists of a single cabinet containing an all-wave broadcast receiver, pre-amplifier, power amplifier and loudspeaker switching panel with built-in monitoring loudspeaker. A rotary switch selects any one of three independent microphone positions, or inputs from the broadcast receiver, a gramophone unit, or tape player.

For smaller installations supplying up to 10 loudspeakers the "Mimco" receiver, with built-in 10 watt audio amplifier, is available. The "Pantenna" communal-aerial system is also shown. This permits the independent use of as many as 80 individual receivers from one common aerial, thus avoiding an unsightly array of personal aerials on board ship, where they may exert an undesirable influence on direction finding. It also enables broadcast programmes to be distributed to positions below decks where it would be impracticable to erect aerials. The "Pantenna" is also suitable for similar systems in large blocks of flats.

Tape Music Libraries

A new emphasis on "Music at Sea"—or ashore—is seen in the display of tape players and reproducers. For some years now gramophone record players have been available to provide music for ships' crews and passengers, but bad weather can have an adverse effect on record playing, despite "floating" turntables and other refinements—and also on brittle

gramophone records. The "Mimco" display at Marconi House features different types of tape player and a more elaborate tape reproducer in a console cabinet which can be painted or polished to harmonise with the decorative scheme of a ship's smokeroom or lounge. The output from a tape player can be played over the loudspeaker system, while the tape reproducer, with its own built-in amplifier and loudspeaker, is a self-contained unit suitable for use in one public room.

With these instruments available, the Marconi Marine Company has introduced a new service. This is a library of 50 tapes, carrying a selection of orchestral and instrumental items to suit all tastes, which can be placed on board ship and exchanged or renewed after each voyage as required. Each tape gives an hour's playing—more than a long-playing record—and reproduction is of a very high quality with, of course, no surface scratch. This new service has only just been introduced, and the "Mimco" tape library will be expanded to include a still wider selection of musical items. Record playing units are, of course, still available, and there is one assembly composed of two record players and a tape player, providing full flexibility of choice for long or short items.

The well-known "Jericho" power megaphone and a variety of microphones, loudspeakers, loudhailers and ancillary equipment are on view.

Our Latest Handbook

A BEGINNER'S GUIDE TO RADIO

By F. J. CAMM

7.6, by post 7.10

From

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2.


MAKE A SOLDER GUN



A 7 - second solder gun was described in "Practical Mechanics." Only two essential parts are required: (a) the transformer and (b) the push switch. These can supply at 13/6, plus 2/- post. The rest of the parts you will have in your own "junk" box. Copy of the article concerned given free with the kit.

TRANSFORMER SNIP

11/6
Post 2/-

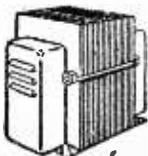


Fully shrouded - standard 200-250 v. primary 280-0-280 at 80 m.a. 6.3 v. at 3 amp. 5 v. at 2 amp.




THE TWIN 20

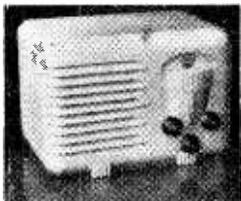This is a complete fluorescent lighting fitting. It has built-in ballast and starters - stove enamelled white and ready to work. It is an ideal unit for the kitchen, over the work-bench, and in similar location. It uses two 20-watt lamps. Price, complete less tubes, 29/6, or with two tubes, 39/6. Post and insurance 5/-. Extra 20-watt tubes, 7/8 each.



MAINS-MINI

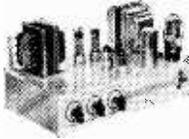Uses high-efficiency coils - covers long and medium wavebands and fits into the neat white or brown bakelite cabinet - limited quantity only. All the parts, including cabinet, valves, in fact, everything, 24/10/0, plus 3/6 post. Constructional data free with the parts, or available separately 1/6.




MULLARD AMPLIFIER "510"

A Quality Amplifier designed by Mullard. Power output exceeds 10 watts. Frequency response almost flat from 10 to 20,000 C.P.S. For use with the Aco's "Hi-G" and other good pick-ups. Made up and ready to work is £12/10/- or 95/- deposit, plus 10/- carr. and insurance. Available in kit form. Send for Mullard Shopping List.

THIS MONTH'S SNIP

offered for less than value of coil pack

7-VALVE CHASSIS ONLY 75/-

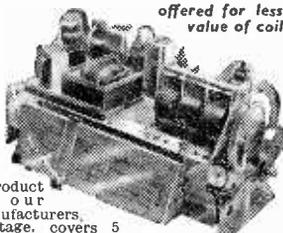


This set, a product of one of our famous manufacturers, has H.F. stage, covers 5 wavebands including short waves to 11 metres. Offered less valves, power-pack, scale and drive, otherwise complete and unused. Price £3/15/-, plus 7/6 carriage.

BAND 3 AERIAL KIT



An interesting aerial, "The Folded V," was described in the July number of this magazine. We tried this and found it to be most efficient. The kit comprises alloy elements and connectors, neat plastic centre piece and saddle for mounting. 8/6 post 1/6.


W.W. Band III Kit

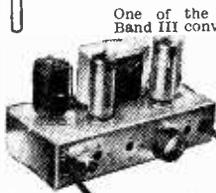

One of the most successful circuits for Band III conversion at aerial frequency. We offer a complete kit of parts including the specified EF90 valves, wound coils, drilled chassis, in fact, everything including a copy of the circuit diagram. Price only 42/6, post 2/6 extra. Mains components if required 25/- extra. Data available separately, price 1/-. Ready to work models, 59/6, plus 2/6 post, or main model, 79/6.

ENTIRELY NEW CIRCUIT

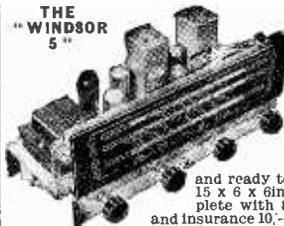Redesigned and now built by the Cleveland Company - very good reports received.



THE "WINDSOR 5"

This is a 5-valve A.C. superhet covering the usual long, medium and short wavebands. It has a particularly fine clear dial with an extra long pointer travel. The latest type local valves are used and the chassis is complete and ready to operate. Chassis size 15 x 6 x 6in. Price £9/19/6, complete with 8in. speaker. Carriage and insurance 10/-. H.P. terms if required.

TABLE RADIO CABINET

Due to a special purchase, we are able to offer this very fine cabinet, size approx. 15 1/2 x 14 x 6in. Walnut veneered and satin finished 37/6, carriage and packing 3/6. Note - This cabinet is the correct one for the Windsor chassis above with 6in. speaker.

RECORD PLAYER £4 - 10 - 0

3-speed Gramophone Motor

Latest rim drive 3-speed motor with metal turntable and rubber mat. Small mod. makes speed easily variable for special effects and dance work.



Hi-Fi Pick-Up

Using famous CosmoCORD Hi-G turn over crystal. Separate sapphire for each speed. Neat bakelite case with pressure adjustment.


Special Snip Offer This Month

The two units as illustrated £4 10/- or made up on board as illustrated £5/10/- plus 5/- post and insurance.

CAR STARTER/CHARGER KIT

All parts to build 6- and 12-volt charger which can be connected to a "flat" battery and will enable the car to be started instantly. Kit comprising the following: Mains transformer... 19/6 5-amp. rectifier ... 17/6 Regulator Stud Switch ... 3/6 Resistance Wire ... 2/- Resistance Former ... 2/6 Mains on/off Switch ... 1/0 0.5 amp. Moving Coil Meter ... 9/6 Constructional Data ... 1/6 or if bought all together price is 52 5. plus 2/- post and packing.

ALL MAINS THREE

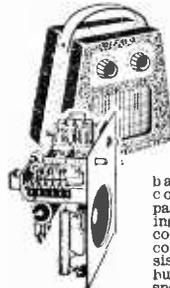

Build yourself a handy midget 3-valve mains receiver giving powerful reception over medium wave band.

All component parts, including valves, coils, tuning condensers, resistors, etc., but not loud-speaker, metal chassis or cabinet (available if required) will cost you only 22/6, plus 1/6 post - data available separately 2/- post free.

22/6

cost you only 22/6, plus 1/6 post - data available separately 2/- post free.

5-VALVE SUPERHET YOURS FOR ONLY 40/- DOWN

Chassis size approx. 9 1/2 x 8 1/2. First-class components. A.C. mains operation. Three wave (medium and two shorts) complete with five valves, ready to work. New and unused. Cash price £5/19/6, or 40/- deposit and 9 monthly payments of 10/- (carr. and ins. 7/6).

THE CLEVELAND F.M. TUNER

Chassis size approx. 9 1/2 x 8 1/2. First-class components. A.C. mains operation. Three wave (medium and two shorts) complete with five valves, ready to work. New and unused. Cash price £5/19/6, or 40/- deposit and 9 monthly payments of 10/- (carr. and ins. 7/6).



This tuner is based upon the very successful circuit published by Data Publications. We have made up models at all branches and will gladly demonstrate. Stability is extremely good and making and aligning most simple. Cost of all parts, including valves, prepared metal chassis, wound coils and stove enamelled scale, slow-motion drive, pointer, tuning knob, in fact everything included, is £8/12/6. Data is included free with the parts or is available separately, price 2/-. Extra for fringe area model, 20/-.


ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to E.P.E. LTD., Dept. 7, 123 Terminus Road, Eastbourne.

Post enquiries to Eastbourne with stamped envelope, please.

42-48, Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5780 Half day, Wednesday.
152-3, Fleet Street, E.C.4. Phone: FLEET 2833 Half day, Saturday.
29, Stroud Green Rd., Finsbury Park, N.4. Phone: ARCHWAY 1049 Half day, Thursday.
249, Kilburn High Road, Kilburn. MAIDA VALE 4921.

7 Days' FREE Examination

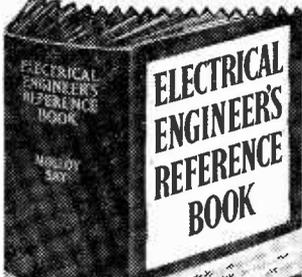

New Edition
JUST OUT

Prove its technical excellence and value to you by claiming Free Examination now. There is no cost or obligation. And it is sent post paid.

- ★ 2,184 PAGES OF WANTED ELECTRICAL DATA
- ★ MANY NEW FEATURES
- ★ LATEST REGULATIONS
- ★ NEW BRITISH STANDARDS

Newnes ELECTRICAL ENGINEER'S REFERENCE BOOK is the most up-to-date work of its kind, and many thousands of copies of previous editions are in daily use. If you have never seen it, now is your chance—a big New Edition has just been published, and you are invited to examine it free of charge.

This rich store of Electrical knowledge has been written and compiled by 71 Specialists. It provides wanted information immediately—there is no time-wasting or searching books for the facts you must have.

32 Data-Filled Sections—facts you need always at your fingertips.

2,184 PAGES and 2,059 Diagrams prepared by expert draughtsmen.

281 SPECIAL PHOTO-GRAPHS.

STRONGLY BOUND IN HARD - WEARING BLUE MOROQUETTE. Size 7½" x 5". WEIGHT 3½lb.

ALL THESE NEW FEATURES!

Details of 400 new products and developments.

New British Standards.
E.L.M.A. Tables.

New Articles on:
GAS TURBINE POWER PLANTS. COPPER. SILICONES. MECHANISM OF ARG EXTINGUISH. METAL RECTIFIERS. EARTHING. NUCLEAR POWER FOR ELECTRICITY GENERATION. ROTATING AMPLIFIERS.

Latest Practice in Mining. Details of I.E.E. Wiring Regulations (1955). Motors—Important new British Standard 2613:1955. Latest Information on Regulations and Exams of the professional organisations.

POST COUPON NOW

George Newnes Ltd., 66/69 Great Queen St., London, W.C.2.

Send me Newnes ELECTRICAL ENGINEER'S REFERENCE BOOK without obligation to purchase. I will either return it in 8 days or send 7s. 6d. deposit 3 days after delivery, then 10s. 0d. monthly, paying £317s. 6d. in all. Cash price £312s. 0d.

Name

Address

Occupation

Your Signature.....


(Or your Parent's Signature if under 21)

EERB 69

Place X where it applies

<input type="checkbox"/>	HouseOWNER
<input type="checkbox"/>	Householder
<input type="checkbox"/>	Living with Parents
<input type="checkbox"/>	Lodging Address

ASPDEN TWO SPEED TWIN TRACK Tape Deck

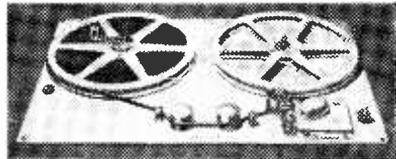

Compact Deck, 7½in. x 11in. 5in. Reels, KIT £7.10.0.

Standard Deck, 10½in. x 15in. 7in. Reels, KIT £8.10.0.

EASY TO ASSEMBLE, PRECISION MACHINED PARTS. SUPER HIGH QUALITY FERROXCUBE HEADS. FINEST MOTORS, FULL ASSEMBLY DRAWINGS.

Either Deck fully built and tested 27/6 extra.

BUILD YOUR OWN HIGH QUALITY TAPE RECORDER


with the **NEW RECORD/REPLAY AMPLIFIER KIT**

MAKE YOUR OWN TAPE RECORDINGS OF YOUR FAMILY, FRIENDS OR FAVOURITE PROGRAMME

Send stamp for full details.

W. S. ASPDEN 10, Market St., Wesham KIRKHAM, LANCs.

A Complete range of BAND 3 CONVERTORS

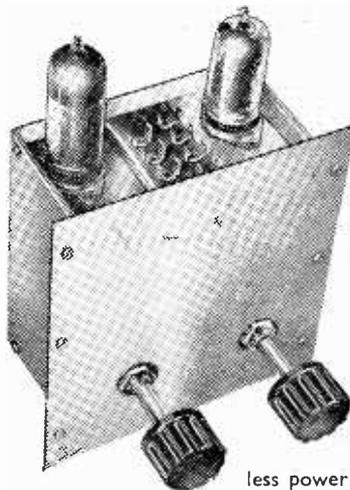

is now available, either with or without power supplies. Careful design and layout, together with efficient filter circuits ensure high attenuation of Band 1 and freedom from break-through. All our units are fitted with pre-set Band 3 contrast controls and manual oscillator trimmer.

less power supply **£5.15.0**
with power supply **£7.10.0**

PRICES : Plus post and packing 2/6d.

Send for details of our full range of test equipment

HOMELAB INSTRUMENTS LTD.
615/617, HIGH RD., LEYTON, LONDON, E.10.
Phone : LEYtonstone 5651

Loudspeakers of the Past

OUR CORRESPONDENT RECALLS SOME OF HIS EARLY EXPERIENCES

By C. H. Gardner

A RECENT note in a trade journal to the effect that the annual production of loudspeakers in this country was in the neighbourhood of 150,000, brought to mind some of the interesting, and in some cases amusing, types of loudspeakers which have been produced during the past 40 years or so.

The necessity for some form of loudspeaker became apparent to some of us as far back as 1912. At that time, with a long enough aerial and a sensitive crystal, it was possible to receive the morse signals from the Eiffel Tower at an appreciable strength. In order to introduce the wonders of wireless to our feminine admirers some method had to be found that would enable them to hear these signals without disarranging their hair with the elaborate contraption of metal headbands attached to the ear-pieces.

Eventually, it was discovered by quite a lot of people at the same time that by detaching one of the ear-pieces and laying it in the bottom of a pudding basin it provided quite an effective loud-speaker under conditions of deathly silence and with

the listener's ear conveniently placed just inside the rim of the basin. However, not a great deal of development took place until after the conclusion of the first World War, when the advent of the valve dithered the diaphragm of the ear-piece sufficiently to warrant its being attached to some form of trumpet. An idea which extended beyond the amateur and into the hands of manufacturing concerns, who still further improved matters by increasing the diameter of the diaphragm and mounting the whole outfit on an artistic pedestal or legs.

Somewhat fierce competition began to arise at this time and the search for efficiency got well under way. Efficiency at that time had nothing whatever to do with fidelity of reproduction, but was more intimately concerned with the total amount of noise a loud-speaker could produce.


I well remember a loudspeaker manufacturer, who later became world famous, bringing one of his prototypes to my radio den with a request that it should be tested against another well-known make. The test consisted of putting the two loudspeakers side by side at the open window and walking down the road in order to see which could be heard at the farthest distance. Memory seems to recall that the prototype beat the other by about five yards.

It was, however, much easier effectively to design the outward appearance of the loudspeakers than to increase its musical or electrical efficiency, with the result that some of those earlier speakers were really attractive and later caused considerable trouble with the feminine members of one's family, as a moving-coil loudspeaker and baffle was considered quite unsuitable in the drawing-room, appearing like an up-ended version of an article of domestic utility which I forbear to mention by name.

It is extremely difficult after this space of time to be chronologically accurate, but memory seems to tell me that really wealthy enthusiasts acquired a horn type loudspeaker with a battery-excited field. I seem to recall that this instrument originally came from the United States. It did, at any rate, produce a distinctly nasal twang to even the beautiful pronunciation of the BBC announcers of that period. Shortly after this a loudspeaker arrived from France. This consisted of a very artistically pleated paper diaphragm driven by a neat little magnetic unit. It was, however, somewhat fragile and, although much loved by the ladies, was not too greatly appreciated by the amateur



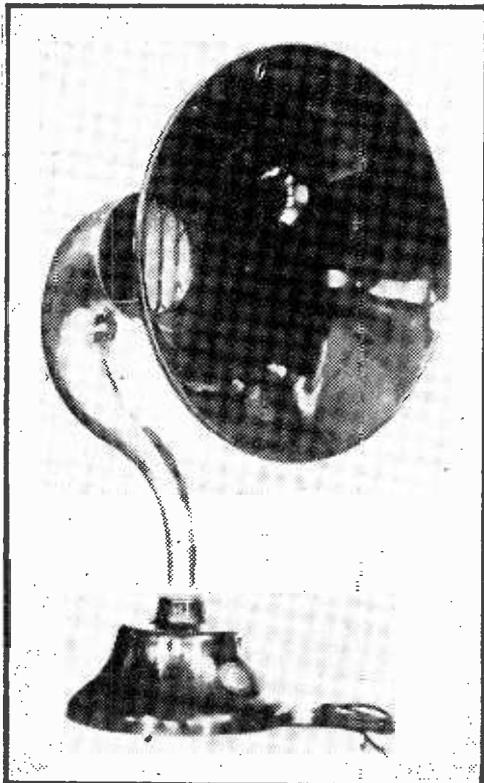*An early Cone type speaker
by S. G. Brown.*



An early Horn by the B.T.H. Company. Note the gauze to prevent dust getting into the movement.

radio engineer, being in appearance much more suitable for a boudoir than the amateur's radio den.

Cone Design

Quite a number of what were known at the time as "cone" loudspeakers then made their appearance on the market. These invariably consisted of a strong paper cone driven by a stylus from a balanced armature magnetic unit. Careful choice of material and choice also of the initial frequency of some of the component parts enabled these speakers to produce a certain amount of bass and this type of speaker was considerably used by the BBC for monitoring purposes.

There was a theory prevalent at the time that the larger the cone the better the bass reproduction, and in a determination to reproduce lower notes than my fellow enthusiasts I managed to acquire one no less than 6ft. in diameter. The trouble with this loud-speaker was that it had to be hung from the ceiling, and it was apt to cause a little disturbance to the normal passage of the occupants of the room in which it was used.

Unfortunately for me, having mortgaged at least a year of my radio hobby funds, the moving-coil speaker made its appearance at about the same time. But before bringing matters quite so up to date I must relate that a certain well-known manufacturer who produced quantities of these H armature cone speakers used them in a most ingenious way for a public address system, which was in very considerable demand. I cannot recall the exact number, but I think twenty-four of these cone speakers were mounted on a large baffle measuring some 6ft. square or more and a number of these baffles complete with speakers were erected by slinging them between large poles.

The procedure in the case of an air display or some other outdoor occasion requiring a public address system was for the van to arrive 24 hours or so before the event and the first evening would then be spent digging holes and erecting the required number of poles. On the day of the event the baffles were then hoisted between pairs of poles. It was, however, essential to ensure that all the speakers were in phase, and on one occasion when they had been wrongly connected the P.A. engineer decided to rectify matters by resting a ladder against one of the poles and mounting it in order to cross over the connections. Unfortunately the ground was soft and the supporting poles quite slowly leant over from a vertical to horizontal position.

The leap for life which the engineer gave from the top of the ladder over a baffle of 20 loudspeakers had to be seen to be believed. Whether this was the cause or not I do not know, but very shortly afterwards he changed his job to the sales staff of the company concerned, and in fact is still operating on their staff and will no doubt be recognised by many of the readers of this article.


You, who to-day buy a moving-coil loudspeaker and mount it in a cabinet, have no idea of the trials and tribulations which beset those of us who tried to do the same with the earlier version of this type of speaker. Our amplifiers were by no means Hi Fi, nor were the speakers by any means free from resonant peaks. Rattles and dithers in the treble were a considerable difficulty, with the result that it was quite common practice to use top filters which made the

music "mellow" but the speech almost unintelligible.

Mechanical Design


Mechanically the construction of the speakers could not keep pace with the number of watts which became available through the good offices of the valve manufacturer, and it was not uncommon for enthusiastic demonstrators to finish up with the cone hanging loose in the frame and the speech-coil parted from it lying somewhere up the magnet tunnel. The search for efficiency as determined by the ratio of noise output to watts input still became something of a fetish and once again I was called upon to take part in an "efficiency" test; only on this occasion the manufacturer's moving-coil loudspeaker was placed alongside a competitor's on the roof of his factory, and instead of walking down the road as on the earlier occasion this time we went for a ride in the manufacturer's car. The test concluded at a distance of half a mile from the factory. I might mention that the amplifier which fed the speaker was quoted as being one of 50 watts output.

I have no intention of bringing this article more up to date by discussing the various designs of speakers that have been produced within the last decade. It only remains to be said that the truly scientific and engineering approach which has been made to the problem has resulted in loudspeakers at a most ridiculously low price and capable, properly used, of giving H-Fi results which make it difficult to believe that such improvement is possible.

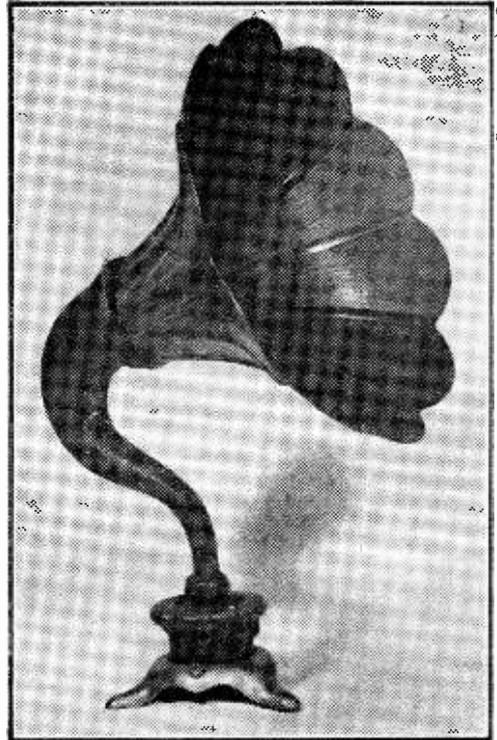

This Amplion had a wooden flare fitted to the cast throat and gave very good tonal balance for its period.

A NOVEL C/R BRIDGE

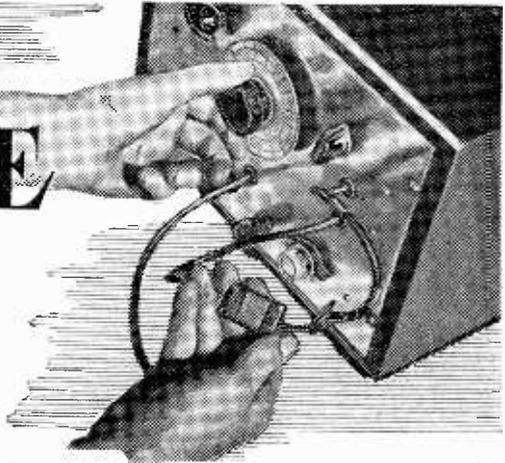

CHECK YOUR CONDENSERS AND RESISTORS
WITH THIS NOVEL TEST INSTRUMENT

By F. W. Austin

ALTHOUGH the popular conception of a resistance/capacity bridge makes use of a "magic-eye" tuning indicator for indication of balance, the author felt the need for an instrument giving a more positive and definite indication.

To qualify this remark, if a small neon tube is employed as an indicator and reaches the point of extinction at the balance setting of the instrument, this indication is obviously more discernible to the average eye than the minute reduction in "shadow-angle" afforded by the cathode-ray tuning indicator. Moreover, the "region of doubt" of the latter is reduced so as to lie between the point of extinction of the neon at one side of balance and the "strike" of the neon as the ratio arms come out of balance on the other side.

Some people are more fortunate than others in this optical respect, but all can be certain between light and darkness; this arrangement is as simple as that and is suitable justification for its existence.

The neon is also cheap and, in the arrangement employed, indestructible.

Features

Certain features are worthy of mention. The neon serves as a normal instrument panel warning indicator when actual measurement is not being undertaken. It is also used as a rough guide to condenser insulation at the plus and minus terminals when the bridge/insulation switch is operated and also discharges the capacitor when the switch is returned to the bridge position. It will be noted that no potential exists across these leads in the bridge position and the switch should not be turned to insulation until the condenser has been connected. (See circuit diagram below.)

In order to simplify switching and comprehension


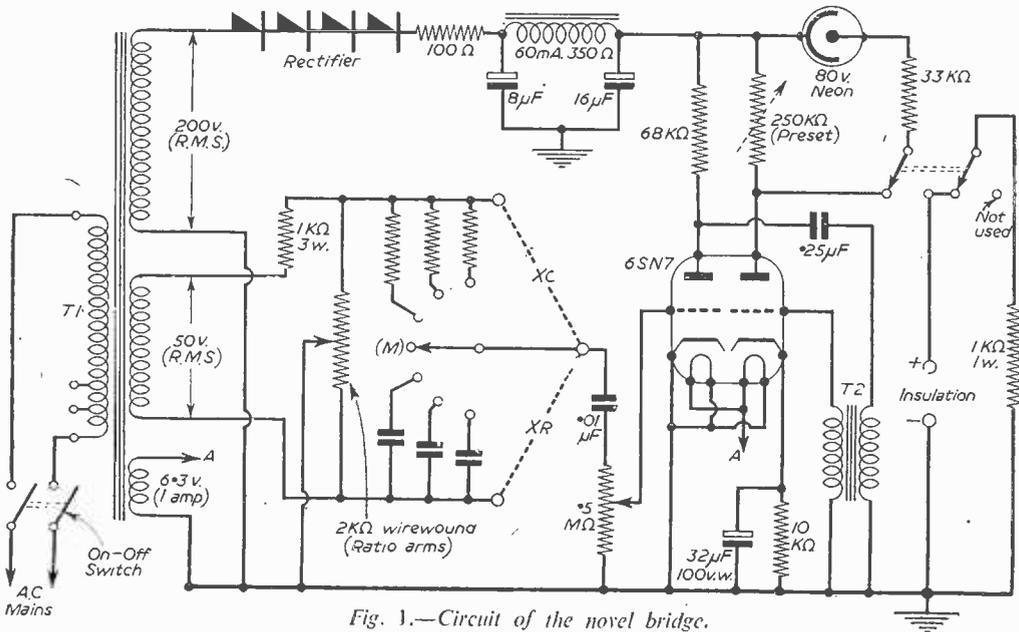


Fig. 1.—Circuit of the novel bridge.

there are three test terminals set in pyramid formation. Resistor standards are taken to one end of the ratio arms and the condenser standards to the other end. The range switch is wired from smallest to largest condenser standard and the next position of the switch is left vacant (and vertical in relation to panel) for "match" position. Resistors in similar formation follow the vacant position. This enables us to use a single dial calibration for both condensers and resistors.

With the switch turned to the left of centre position, condensers are measured between the left-hand terminal and "apex" of pyramid, the other terminal being ignored. With the switch central any two condensers or resistors are matched by taking both

possible reasonably to determine stray capacities. This balance point has a slight "spread", and when calculating small capacities it is advisable to take the centre reading of the spread and to subtract this quantity from the point of balance with the condenser under test connected to the bridge. The answer should approximate the value of the condenser. The sensitivity control has a large measure of control over the indication and should be kept retarded as much

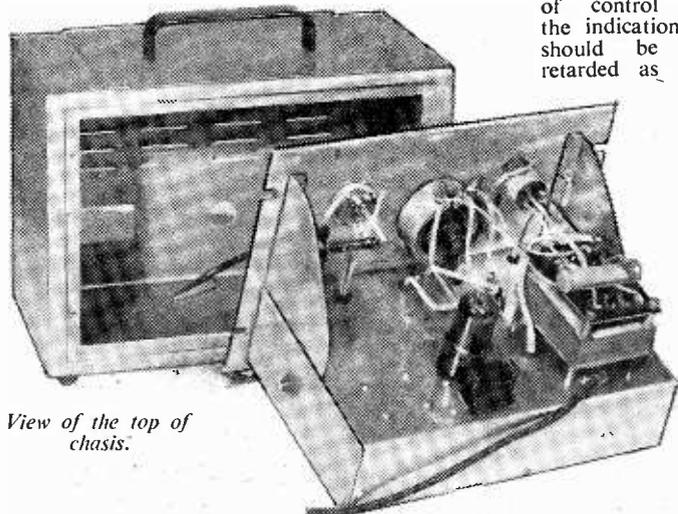

View of the top of chassis.

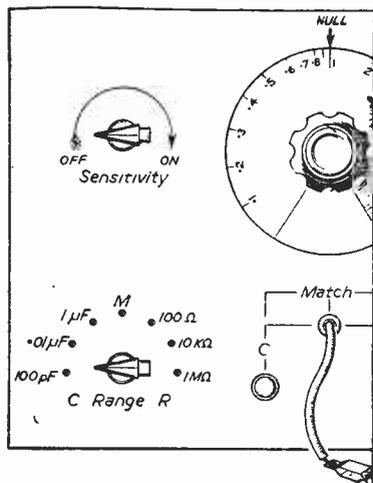


Fig. 2.—Panel layout

to the apex and connecting the free ends to the feet of the pyramid (one either side). In the case of external standards being employed the standard condenser is connected between the "R" terminals (see Fig. 2). A standard resistor, on the other hand, is connected between the "C" terminals; the

balance point on the dial then gives the ratio of the unknown "C" or "R" with respect to the standards used.

Sensitivity

It is only fair to state that the indication given on the 100 pF range is not so precise as that obtaining on other ranges, although it is

as possible consistent with sharp response from the neon. On some ranges the neon may not become extin-

guished unless this is done, owing to the larger signal available.

Construction

A layout of the components as used in the original model is given in Fig. 5. It will be noticed that a screened lead is

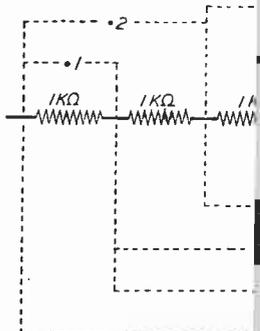


Fig. 3.—Alternative method using resistors


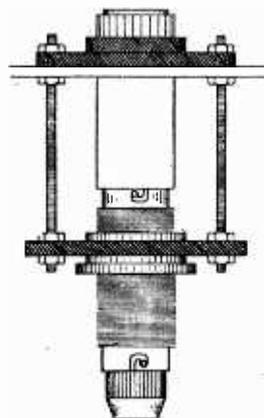


Fig. 4.—Details of the neon holder.

LIST OF CO

- 1 mains transformer—secondaries : 200 v. (r.m.s.) 50 mA, 50 v. (r.m.s.) 50 mA, 6.3 v. (1 amp.) : T1
- 1 smoothing choke—350 ohms 60 mA.
- 1 Bulgin push-pull intervalve transformer ratio 1 : 4, List No. L.F.36 : T2.
- 1 valve 6NS7. 1 octal valveholder. 1 metal rectifier 60 mA.
- 1 electrolytic condenser 8-16 µF (350 v.w.).
- 1 w/w potentiometer 2 k ohms (ratio arms).
- 1 volume control with double-pole switch (half-megohm).
- 1 condenser .01 µF (350 v.w.). 1 condenser .25 µF (350 v.w.).
- 1 electrolytic condenser 32 µF (100 v.w.).
- 1 switch—1 pole 7-way. 1 switch—2 pole 2-way.

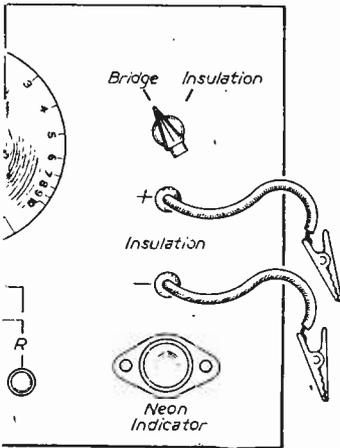taken from the sensitivity control to the first grid of the 6SN7 valve. This is to guard against stray "pick-up" in the lead (in view of its length) and to ensure adequate operation of this control.



The parallel-fed transformer (T2) between the first anode and second grid of the 6SN7 was a surplus push-pull input component having high D.C. resistance windings, but a high ratio of secondary to primary turns is more important. The centre tap of the secondary winding is not used, the two others going to grid and chassis respectively. Using a transformer of

push-pull intervalve transformer ratio 1 : 4, List No. L.F.36). Some readers may be slightly puzzled about this, but the reasons are that we need amplification at *only one frequency* (50 c.p.s.) and not normal audio practice. Response on the smallest ranges is affected to quite an extent by this section, therefore "peak" must be the aim.


.1=182/1818	10=1818/182
.2=332/1668	9=1800/200
.3=460/1540	8=1776/224
.4=570/1430	7=1750/250
.5=666/1334	6=1715/285
.6=750/1250	5=1668/332
.7=824/1176	4=1600/400
.8=888/1112	3=1500/500
.9=946/1054	2=1334/666

Unity : 1=1000/1000

Internal Standards


These were removed from a partly assembled surplus bridge chassis and were 5 per cent. components of 100 pF, .01 μF, 1 μF, 100 ohms, 10 k, 1 megohm.

out details.

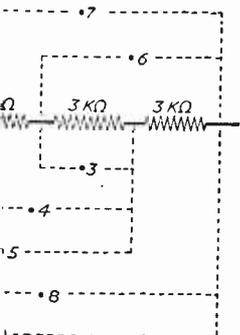

nd for calibrating scale (see text).

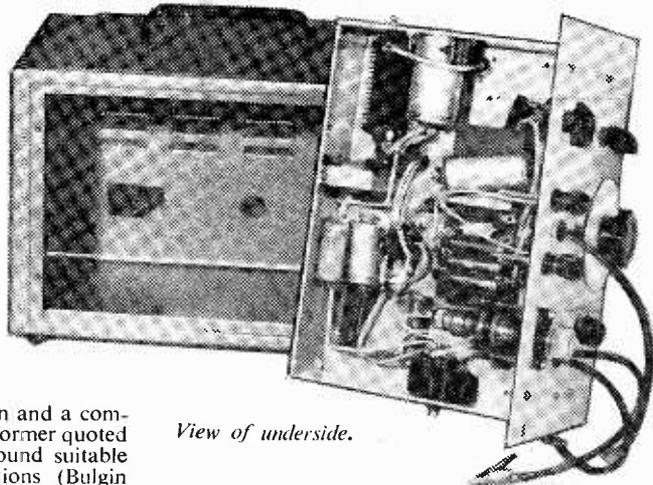the constructor's own choice may necessitate adjustment of the anode resistor in the first section of the valve in order to obtain maximum voltage gain across the secondary winding. In the components list a fixed value is given and a commercial type transformer quoted which has been found suitable without modifications (Belgin



View of underside.

The 1 μF standard was of the waxed paper variety and was found to be leaking. A metal-clad hermetically-sealed component was substituted for this range. The scale was simply marked in tenths to unity and upwards to "ten times" the standard, giving range continuously from about 10 pF to 10 μF and 10 ohms to 10 megohms. These can be extended upwards if desired.

Calibration

It is possible to calibrate the scale by simple resistance measurement of the ratio arms, and if a good meter is at hand this is a cheap (and accurate) means to adopt. It is not possible to give a printed template of the scale as potentiometers vary a great deal in their arc of travel and the only point of accuracy would be at unity. In the table given, the

COMPONENTS

- 1 resistor 68 k ohms (1 watt). 1 resistor 10 k ohms (1 watt). 1 resistor 33 k ohms (1 watt). 1 resistor 1 k ohms (1 watt). 1 resistor 1 k ohms (3 watt). 1 resistor 100 ohms (1/2 watt).
- 1 variable potentiometer 250 k ohms. 2 insulated terminals.
- 1 neon 80 volts (surplus 10 E/6) with holder.
- 1 chassis 10in. x 6 1/2in. x 2 1/2in. 2 chassis angle brackets 3 1/2in.
- Panel and case (to suit individual), crocodile clips, heavy rubber-covered test lead, tag strips, screws, etc.
- Internal standards (all 5 per cent. components) : 100 pF, .01 μF, 1 μF, 100 ohms, 10 k ohms, 1 megohm. (Condensers 450 v.w. if possible.)

figures from left to right indicate the ratio in ohms. The total figures, both left and right, equal the resistance of the potentiometer.

These figures must not be taken too literally but are given to show the relationship between the arms. An alternative method, for use with the bridge under operating conditions, is given in Fig. 3. Six close tolerance resistors are necessary, five being shown in the illustration. If the bridge is set to the 10k ohm range the chain of resistors will give balance points at the settings shown by the dotted lines. When the .9 calibration mark has been reached the sixth resistor (a 1k component) is used as an external standard between the "C" terminals and the switch turned to "match" position. The resistor chain then provides remaining markings from 1 to 9. For the "ten

times" position the 1k resistor is removed from the "C" terminals and inserted in the "R" terminals. The switch is set to the 100 ohm range when the balance point will be found.

Neon Adjuster

It has been left until now to explain this control (pre-set 250k potentiometer) as it is of no moment until the instrument has been constructed and actual operating begun. This control will be found at the side of the chassis labelled "neon adjuster." The instrument should be switched on and the range switch set to 100 pF range. When warmed up turn the control in whichever direction may be necessary to extinguish the neon. The balance arms are then swung back and forth (with sensitivity at maximum) adjusting this side control so that the neon just extinguishes itself within a very small compass. This is the stray capacity of the instrument and all control necessary after this initial setting up should be within the scope of the sensitivity control on the front panel.

Bridge/Insulation Switch

It is felt desirable to advise the constructor that when purchasing the two-pole, two-way switch this should be of such type as will definitely break contact before making contact in the secondary position. No harm is likely even if this is not the case, but the neon will flash at each changeover of the switch. The isolating type will prevent this minor annoyance.

The Neon Holder

As the neon holder is of the single-pole bayonet cap variety it is important that the outer conducting rim be adequately insulated from the chassis, and Fig. 5 illustrates the method used by the author in the original model. Use was made of a commercial high quality (and high priced) chromium-plated product: this was fitted into a sawn-off ex-government inspection lampholder of plastic material with a screw-on perspex window which came through the front panel to serve as indicator. Since making the original model it has been discovered that the neon quoted in the parts list can be obtained complete with an insulated holder from some surplus component dealers.

Earth Connection

Finally, it must be realised that an earth connection is essential if hand-capacity effects on the lowest capacity range are to be avoided.

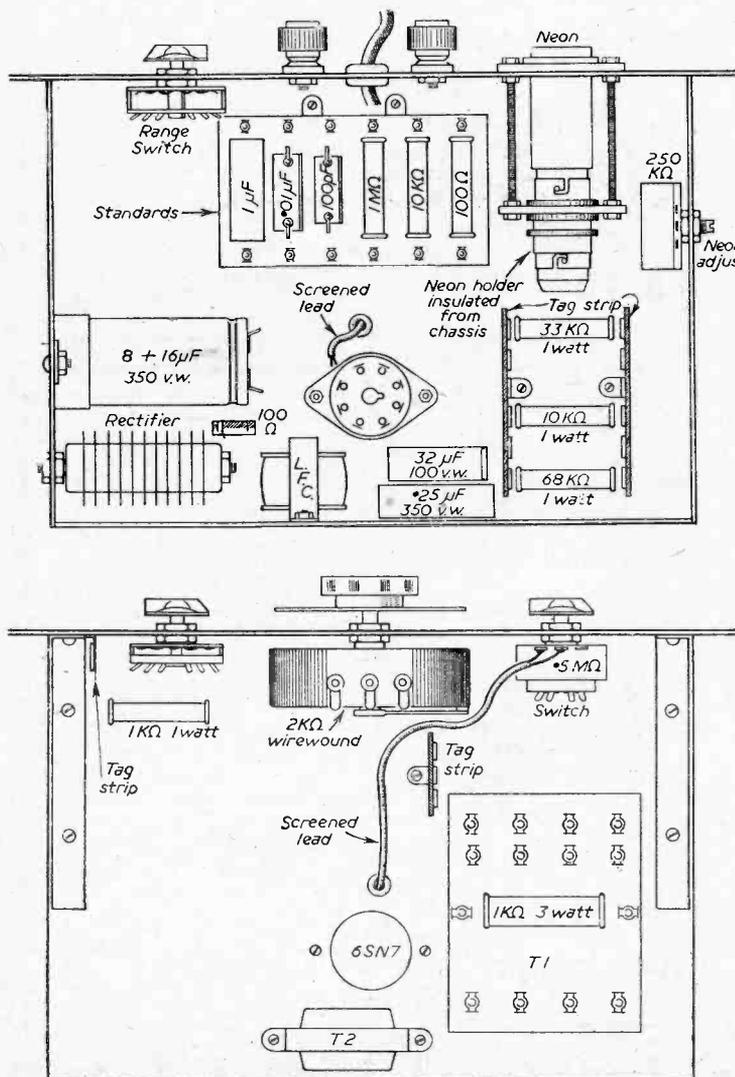


Fig. 5.—Above and below chassis wiring details.

C.R.T ISOLATION TRANSFORMERS

Type A. Low leakage windings. Ratio 1:1:25 giving a 25% boost on Secondary.
2 v. 10/6; 4 v. 10/6; 6.3 v. 10/6; 10.9 v. 10/6; 13.3 v. 10/6.
Ditto with mains primaries. 12/6 each.
Type B. Mains Input 220/240 volts. Multi Output 2, 4, 6.3, 7.3, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tag Panel. 21/- each.
Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 230/240 volts. Output 2.1-2.1-21-3 volts at 2 amps. With Tag Panel. 17/6 each.
All Isolation Transformers are individually boxed, labelled and clearly marked with relevant data.

TRIMMERS. Ceramite, 30 50, 70 pf., 9d., 100 pf., 150 pf., 1.3; 250 pf., 1.6; 600 pf., 750 pf., 1.9.

RESISTORS. All values. 10 ohms to 10 meg. 4 w., 4d.; 1 w., 6d.; 1/2 w., 6d.; 2 w., 1/-.

HIGH STABILITY. 1 w. 1%, 2/- Preferred values 100 ohms to 10 meg.

WIRE-WOUND RESISTORS (1.3 10 watt) 25 ohms—10,000 ohms. 1/2 15,000 ohms—50,000 ohms. 5 w. 1.9; 10 w. 2/3

KNOBBS, GOLD ENGRAVED. Walnut or Ivory, 1 1/2 in. diam., 1.6 each. Not engraved, 1/- each.

RECORDING TAPE

1,200 ft. on standard fitting 7" Plastic reels. Brand new boxed 17/6.

O.P. TRANSFORMERS. Heavy Duty 50 mA., 4/6. Ditto, tapped primary, 4/9. Multitap, push pull, 6/6. Tapped small pentode, 3/9. Miniature 384, etc., 3/9.

L.F. CHOKES 15/10 H. 60/65 mA., 5/-; 25/20 H. 100/120 mA., 11/6; 20/15 H. 120/150 mA., 12/6.

MAINS TRANS. 350-0-350, 50 mA., 6.3 v. tapped 4 v. 4 s., 5 v. tapped 4 v. 2 a., ditto 250-0-250, 21/-.

HEATER TRANS. Tapped prim., 200/250 v., 6.3 v. 14 amp., 7/6; 4 tapped sec., 2, 4, 6.3 v., 14 amp., 6/6.

COPPER PLATED AERIAL RODS. 1/2 2 1/2 in. push fitting, 2/6 doz. p. & p. sd. Aerialize Earth rods, 4/-.

ALADDIN FORMERS and core, 1/2 in., 8d.; 3/4 in., 10d.; 1 in. FORMERS with Core and Core. 1 in. sq. x 1 1/2 in. and 1 in. sq. x 2 1/2 in., 2/- each.

TYANA.—Midget Soldering Iron. 200/230 v. or 230/250 v., 14/11. Triple Three mod. with detachable bench stand, 19/6. Solon Midget Iron, 22/-.

MIKE TRANS. Ratio 50:1, 2.9 ea.

MAINS DROPPERS. 3 x 1 1/2 in. Adj. Sliders, 3 amp. 750 ohms, 4/3. 2 amp. 1,000 ohms, 4/3.

LINE COED. 3 amp., 60 ohms per foot, 2 amp., 100 ohms per foot, 2 way, 6d. per foot, 3 way, 7/2. per foot.

LOUDSPEAKERS P.M. 3 OHM.
10 in. R.A., 16/8. 7 in. x 4 in. Goodmans, 21/- 6 in. x 4 in. R.A., 19/6. 8 in. Goodmans, 22/6. 6 in. Goodmans, 18/6. 10 in. Rola, 30/- 6 in. ditto w/Trans., 21/- 12 in. Plessey, 30/- 8 in. M.E. 2.5 k. or 2 k. field, tapped O.P. Trans., 24/6.

CRYSTAL DIODE. 6.3 v. 6.6. Circuit Book, 1/6.

HIGH RESISTANCE PHONES. 4,000 ohms, 15/6 or COPPER ENAMEL WIRE. 1 lb. to 16 to 20 s.w.g., 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/6.

SWITCH CLEANER Fluid, spirit, spot, 3/9 1/2.


TWIN GANG TUNING CONDENSERS. .0005 mfd. midget with trimmer, 8/6; .001 pf. midget, loss trimmers, 6/6; .0005 standard size with trimmer and feet, 9/-; loss trimmers, 8/-; ditto, solder, 2/8.

SPEAKER PRET. Woven Plastic TYGAN. Walnut tone, 1 1/2 in. wide, 2/- per foot. Expanded metal, gold or silver, 14 x 1 1/2 in., 2/- each.

VALVES

A SMALL SELECTION FROM OUR STOCKS

All Boxed	3/6	New & Guaranteed
6/8	1.6	2/6
6AL5	EA50	6B6M
6J5		2N2
6K7	7/6	6X5
6BD4	6/6	6AM6
6/6	1/6	6G6
6AT7	1/4	6K8
6AT6	1/4	6F92
6C9	1/4	6F92
6L6G	3/4	6X4
6N7	6B6	6X5
6V4	6B6	12AX7
12/6	15/-	
6Y31	6P25	6C84, 6CF82

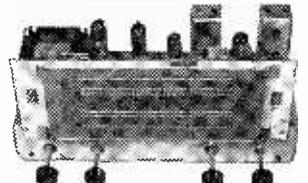


ALL WAVE RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES
S. W. 16 m.—50 m. LATEST MULLARD
M. 200 m.—550 m. ECH42, EF41, EB41,
L. W. 800 m.—2,000 m. EL41, EZ40.

12 month Guarantee.
A.C. 200/250 v. 4-way Switch: Short-Medium-Low-Gram. A.V.C. and Negative feedback.
1.2 watts. Chassis 1 1/2 x 5 1/2 2 1/2 in. Glass Dial 10 x 4 1/2 in. horizontal or vertical available.
2 Pilot Lamps, Four Knobs, Walnut or Ivory aligned and calibrated. Chassis isolated from mains. £9.15. Carr. & Ins., 4/6.

RECOMMENDED FOR ABOVE CHASSIS

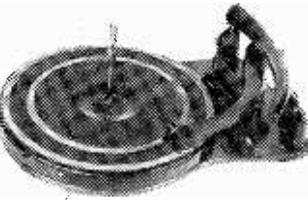


£8-19-6 (Limited Period)

Post Free.

Brand new Plessey 2-speed Autochanger Mixer Unit for 7, 10 and 12 in. Records. Twin Hi-Fi Xtal Head with Dupont sapphire stylus. Plays 4,000 records. Spring mounting. Baseboard required 15 x 12 1/2 in. Height 5 1/2 in. Depth 2 in. Super Quality

FAMOUS MAKE. 3-speed Single Record unit with Acos 37 Turnover Head, each Sapphire Stylus plays 2,000 records. Starting Switch. Automatically places Pick-up on records 7 in., 10 in. or 12 in. Auto Stop. Baseplate 12 x 8 1/2 in. Height 2 1/2 in. Depth 1 1/2 in. Price £7/15/6, post free.

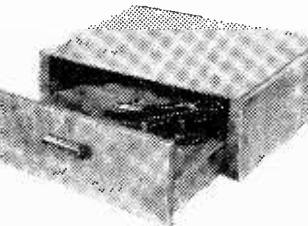B.S.R. MONARCH 3-SPEED MIXER CHANGER ACOS GP.37 XTAL HEADS. Baseboard 14 x 12 in. Height 5 1/2 in. Brand new in Markets Boxes. £9.19.6, post free.



£4.19.6. CONVERT YOUR RADIO. Playing Desk 15 x 22 x 7 1/2 in. Walnut finish, inner front with 7.5 k. ohm. motor, formidable and pick-up. Press lever start places High Impedance Mantic pick-up on records 10 in. or 12 in. Auto Stop. Brand new in original markets boxes. 200 250 v. A.C. £4/19.6. carr. free. 10/- extra Scotland, Ireland, Wales.

SUPERHET COIL PACK 27.6 Miniature size 2 1/2 x 2 1/2 x 1 1/2 in. High Q dust core coils. SHORT, MED., LONG, GRAM switching with connection diagram and circuit.

BAND 3 T.V. CONVERTER KITS

For London, Midland and Northern Transmissions.

Suitable all T.V. makes. T.R.F. or Superhet. Ready wound coils, B.V.A. EF80 valves, all components, punched chassis, circuit diagram, wiring plans. COMPLETE KIT for mains operation 200-250 v. A.C. £3/10/-.

AS ABOVE less POWER PACK. Requires 200 v. 20 mA. H.T. 6.3 v. 6 mA. I.T., £2/5/- Mains Transformer to above Spec., 10/6.

PUNCHED CHASSIS and WOUND COILS, component list, circuit diagram, wiring plans, only 19.6. Full Plans and Circuit details, 6d.

Volume Controls 80 ohm CABLE COAX

Long spindles, Guaranteed 1 year. All values 10,000 ohms to 2 Meg. S.W. S.P.S.W. D.P.W. 2 1/2 in. dia. 4/- 3/8 EXT. SPKR. TYPE 3 7d. vd.

COAX PLUGS ... 1- DOUBLE SOCKET ... 1-3 SOCKETS ... 1- OUTLET BOXES ... 3-0

BALANCED TWIN FEEDER, yd. 6d. 80 or 300 ohms. DITTO SCREENED per yd. 1/- 80 ohms only.

T.V. AERIALS. Band I. Indoor Inv. T., 13/6. Band 3 Dipole indoor, 6/6. Band 3 Twigs, 7/6 pr.

WIRE-WOUND POTS, 3 WATT. FAMOUS MAKES. Pre-Set Min. T.V. Type. All values 25 ohms to 30 K, 3- ea. 50 K, 4/- Ditto Carbon Track 50 K to 2 meg, 2/- Standard Pots, 2 1/2 in. Spindle. All Values, 100 ohms to 50 K, 5/6; 100 K, 6/6.

W/ EXT. SPEAKER CONTROL, 10 ohm, 3/-.

CONDENSERS. New stock. .001 mfd. 7 kV. T.C.C. 5/6; Ditto. 12.5 kV. 8/6; 2 pf. to 300 pf. Mica, 6/6; Tubular 500 v., .001 to .01 mfd., 9d.; .05, .1, 1/-; .25, 1.6, .5, 1/9; 1/350 v., 9d.; 1/600 v., 1.3; 1/1,500 v., 3/6.

CERAMIC CONDS., 500 v., 3 pf. to .01 mfd., 1/-.

SILVER MICA CONDENSERS.—10% 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3. DITTO 1% 1.5 pf. to 500 pf., 1/9; 315 pf. to 1,000 pf., 2/-.

I.F. TRANSFORMERS 10/6 pr. Wearite type 500 465 kc's. Midget Plessey, 8/9 pr.

NEW ELECTROLITICS. FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES
1.275 v. 2-	100/25 v. 2/-	84/16430 v. 5/-
2.550 v. 2/3	84/8500 v. 4/6	164-16450 v. 5/6
3.450 v. 2/3	164-16500 v. 4/6	164-16500 v. 4/6
8.450 v. 2/3	324-32450 v. 6/6	324-32450 v. 6/6
8.500 v. 2/3	CAN TYPES	324-32450 v. 6/6
16.500 v. 4	6 1/2 pins	324-32450 v. 6/6
16.500 v. 4	4-16/500 v. 4/-	644-120/350 v. 11/6
22.500 v. 5	5/6	100-200/275 v. 4/6
22.500 v. 5	1.9-60/350 v. 5/6	1,000-1,000/6 v. 10/3
30.25 v. 1.9	250/350 v. 5/6	1,000-1,000/6 v. 6/6
30.25 v. 2	150/12 v. 3/-	

Screw Base Type 312. 8/500 v. 3/-; 16,500 v. 4/-.

SENTERCEL RECTIFIERS. E.H.T. TYPE FLY-BACK VOLTAGES. K3/25 2 kV., 4/3; K3/40 3.2 kV., 6/-; K3/45 3.6 kV., 6/6; K3/50 4 kV., 7/3; K3/100 8 kV., 12/6; MAINS TYPE. 1M1, 125 v., 5/9 mA., 4/-; RM2, 100 mA., 4/9; RM3, 120 mA., 5/9; ERA, 250 v., 275 mA., 16/-.

COLLS. Wearite. "P" type, 2/6 each. Osborn Midget "Q" type adj. dust core, 4/- each. All values. H.F. MIDGET CHOKES. 14 M.H., 2/6 each.

ALUMINIUM CHASSIS. 18 s.w.g. un drilled. With 4 sides, riveted corners and lattice fixing holes. 2 1/2 in. sides, 7 x 4 in., 4.6; 9 x 6 in., 5.9; 11 x 7 in., 6.9; 13 x 4 in., 8.6; 14 x 10 in., 10.6; 18 x 16 x 3 in., 16.6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 2, 6 or 12 v. 1/2 amp., 8/9; 2 a., 11/3; 3 a., 17/6

CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1/4 amp., 13/8; 1 amp., 21/-.

ACID HYDROMETER. New Ex Govt. Unbreakable. Packed in metal case 7 x 1 1/2 in. dia., 4/6.

F.M. TUNER COIL KIT. 27/8. H.F. coil, Aerial coil, Oscillator coil, two I.F. Transformers 10.7 Mc's., Detector transformer and heater choke. With circuit and component list using four 6AM6 Chassis and Dial. 19/6.

RADIO COMPONENT SPECIALISTS 307 WHITEHORSE RD., WEST CROYDON
OPEN ALL DAY—(Wed. 1 p.m.) 10 page list S.A.E
Tel. THO 1665, after 6 p.m. 4198. Buses 133 or 68 pass door. 48-hour postal Service, P. & P., 6d. £1 orders post free. C.O.D. Service 1/6

FRAME AERIALS

DETAILS OF A MUCH NEGLECTED TYPE OF SIGNAL PICK-UP

By F. G. Rayer

FFRAME aerials have two main applications, one based on their portability and one upon their directional properties. Their use in portable receivers is well known, as no external aerial or earth is required when a frame aerial is provided, so that the set can be operated anywhere at will. With both portables and fixed receivers the strongly directional effects of such aerials can also be of advantage. An example of such use arises with broadly-tuned "local station" receivers, where interference from European or other stations may cause whistles, etc. Such interference is becoming increasingly troublesome. As it is not feasible to increase selectivity with "quality" tuners, some other means of eliminating the undesired station is necessary. A directional frame aerial, set for minimum pick-up from the offending station, is one solution.

A frame aerial consists of a winding of such inductance that it can be used as the first tuned circuit, replacing the aerial tuning coil otherwise present. When the axis of the winding is directed at a station a similar signal is induced in all sections of the frame, and the signal output from the frame is theoretically zero. (In practice an ordinary frame aerial will not have an absolute zero position, due to stray pick-up in connections, etc.) When the frame is turned so that its side faces the station, a phase difference arises in opposite sides of the frame, giving maximum output. In use, therefore, the frame is turned so that one side faces a desired station, or so that its axis points to an undesired, interfering station.

For ordinary listening purposes there is no need to rotate the frame for each station, since pick-up is good in all directions other than those in line with its axis. However, it may be adjusted for maximum volume from a weak station, if necessary. Similarly, it may be adjusted for minimum signal from an

interfering station, when required, and pick-up from such a transmitter may be very small indeed, with a flat frame having screened leads.

Other things being equal the larger the perimeter of the frame the greater its output, and this should be remembered when the receiver is of rather low sensitivity. Signal strength is also improved by keeping the frame windings away from any conductive or screening parts—chassis, batteries, loudspeaker, etc. Because of this, a free-standing aerial, gives maximum results. Almost equal in efficiency is the type of winding in the lid of suitcase portables, since this is well clear of batteries and metal parts. Aerials wound round the receiver case give slightly reduced signal strength, especially when near chassis or other metal parts.

In addition to the foregoing, it should be remembered that the frame winding should be situated vertically, or nearly so. Frame aerials can be used with crystal sets.

Medium-wave Frame Aerial

The circuit of this is shown in Fig. 1, and it consists of a single winding tuned by .0005 μ F condenser. This winding replaces the M.W. aerial coil. With the R.F.-Detector type of set, the M.W. frame will tune with a M.W. coil in the detector stage. With a superhet without R.F. stage, frame aerial and oscillator coil will be used. In each case accurate ganging will be required. This can be achieved by employing a ready-made frame, such as supplied by various coil manufacturers, or by using an oscillator coil with adjustable dust core, and setting this to suit the inductance of the frame winding. Or a panel trimmer of about 100 pF may be used in parallel with the frame winding, to secure correct ganging at all points of the tuning scale. Alternatively, two separate condensers may be used for tuning, instead of a two-gang condenser. This introduces a further control, but avoids at once all ganging difficulties.

If the receiver is a "straight" type with no R.F. stage, no tuning coil at all will be used, and reaction will be added as shown. It is also possible to join points B and C, and wire the reaction condenser between D and the detector anode, though the condenser spindle and moving plates cannot now be "earthed" to the H.T.—line.

All-wave Operation

Both M.W. and L.W. tuning is often required, and may be obtained by having a long-wave loading coil in series with a frame wound for M.W. only, as in Fig. 2. Such coils may be purchased, and have adjustable cores so that the circuit can be ganged with detector or oscillator tuned circuits. To do this, the M.W. detector or oscillator coil should first

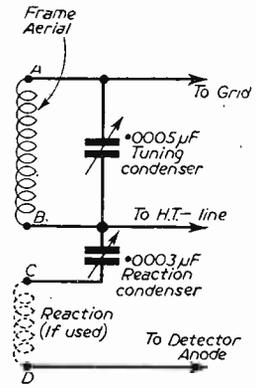


Fig. 1.—Connections for a M.W. frame aerial.

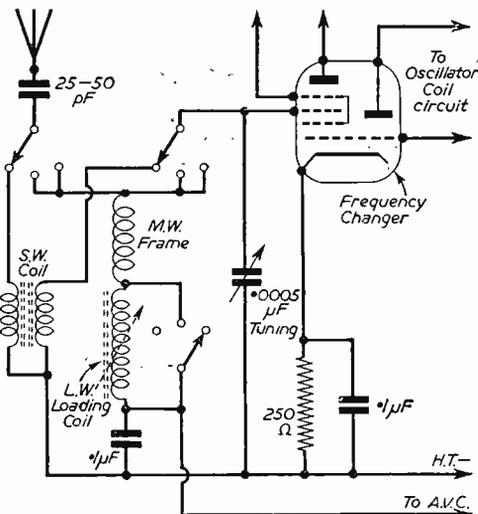


Fig. 2.—Typical all-wave circuit.

be adjusted, by modifying its core position, until it gangs correctly with the frame, on the M.W. band. The set is then switched to L.W. and loading coil and detector or oscillator L.W. coil adjusted.

This type of circuit avoids the necessity for winding a L.W. section on the frame, but gives slightly reduced signal strength, on the L.W. band, compared with a frame wound for both M.W. and L.W. tuning. It is, however, the method used in most commercial portables of small type.

Where S.W. reception is required, any attempts to use a frame aerial will give poor results, and provision is usually made for attaching an external aerial, as shown in Fig. 2. With the popular M.W. and L.W. type of portable, the S.W. coil, 25-50 pF condenser and associated switching would be omitted.

The actual aerial may be made up in various forms, and Fig. 3 illustrates a simple box-type of aerial. This may be quite narrow, so that it can be accommodated in a shallow suitcase type lid, or it may be some inches wide, being inside the receiver cabinet. Connections are marked to agree with Fig. 1.

The number of turns required to tune the M.W. band will depend on the gauge of wire, spacing, and perimeter of frame. For fairly large frames, about 70ft. to 75ft. of wire will be required. The number of turns will be found by dividing the frame perimeter in feet into this. A slight space should be left between turns.

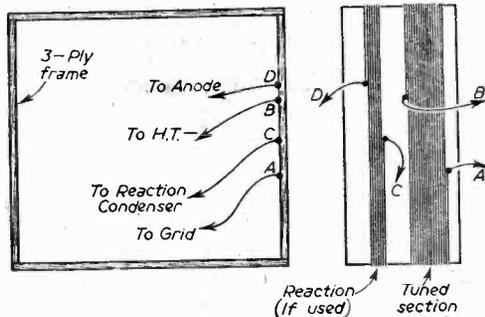


Fig. 3.—A medium-wave frame aerial.

As spacing and perimeter are reduced, less than 70ft. of wire will be required. Suggested M.W. tuned sections, for various frames, are as follows:

Frame size	Wire gauge	No. of turns
18in. x 18in.	24 d.c.c.	10 side by side
9in. x 9in.	26 s.w.g. enam.	18 side by side
6in. x 6½in.	32 s.w.g. enam.	23 side by side
5½in. x 6in.	26 s.w.g. enam.	25 side by side

Frames much smaller than 6in. square are best avoided as signal pick-up becomes relatively poor. To match up with existing coils, with ganged tuning, turns may be added to increase inductance, or removed to reduce it.

When reaction is used a space of about ¼in. should be left, and the winding put on, as shown in Fig. 3. About one-third the number of turns used on the tuned section will be satisfactory. As the reaction obtained will depend to some extent on the detector valve and H.T. voltage, a few turns may be removed if oscillation is too violent. But about one-third the number of turns on the tuned section will be satisfactory for all-dry type valves with 45 volts to 60 volts H.T. supply.

With a dual-wave frame, the M.W. section is put on as described, and a L.W. section added as in Fig. 4. For large frames, about 200ft. of wire will be required, somewhat reduced as the size of the frame falls. For the frame sizes already mentioned, suitable L.W. sections will be:

Wire gauge	No. of turns
32 s.w.g. enam.	32 side by side
34 s.w.g. enam.	52 side by side
34 s.w.g. enam.	60 turns pile wound
34 s.w.g. enam.	75 side by side

The L.W. section must be in the same direction as the M.W. section, as shown in Fig. 4. If reaction is used, the reaction winding must be very near the L.W. section, or reaction will be weak on the L.W. band. If required this can be overcome by using a few more turns on the reaction winding, and keeping it ¼in. or so from the M.W. winding.

For M.W. reception the L.W. section is shorted out, as shown in Fig. 2. The wavechange switch is thus returned to point B in Fig. 4, which will go to H.T. — line or A.V.C. circuit, according to the type of receiver.

It may be necessary to choose the aerial winding to suit the winding width available, as well as the perimeter. The 18in. x 18in. aerial described would require about ¾in. winding width. The 9in. square aerial would require 2in. width, the 6in. x 6½in. aerial ¾in. only, and the smallest perimeter aerial given approximately 2in. This is for dual-wave type with reaction. When reaction is not used at least ¼in. should be left between M.W. and L.W. sections, when practicable.

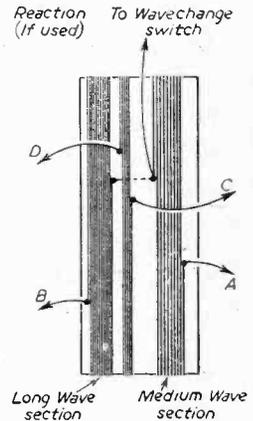


Fig. 4.—Disposition of windings on a dual-wave frame.

Other Forms

When space is limited a flat aerial such as shown in Fig. 5 can be used successfully, wound upon stout card or thin paxolin. This type requires very little width and may be fitted at the back of a cabinet or chassis. For a frame about 10in. by 5in. 21 turns

(Concluded on page 66)


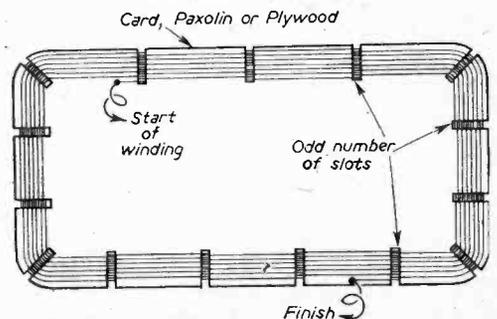


Fig. 5.—Details of a flat frame.

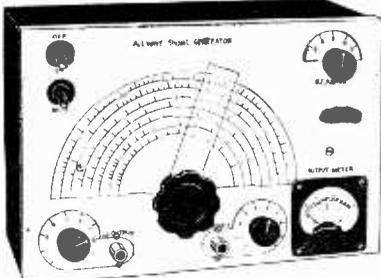

COMPLETELY BUILT SIGNAL GENERATOR

Coverage 120 Kc's-320 Kc's, 300 Kc's-900 Kc's, 900 Kc's-2.75 Mc's, 2.75 Mc's-8.5 Mc's, 8 Mc's-26 Mc's, 16 Mc's-56 Mc's, 24 Mc's-84 Mc's. Metal case 10in. x 6 1/2in. x 4 1/2in. Size of scale, 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4 19.6 or 34.- deposit and 3 monthly payments 25.-. P. & P. 4.- extra.

Heater Transformer, Pri. 230-250 v. 6 v. 1 1/2 amp., 6/-.

Three-speed automatic changer, B.S.R. Monarch, current model. Will take 7in., 10in. or 12in. records mixed. Turn-over crystal head, cream finish. VERY LIMITED QUANTITY. A.C. mains 200 250. £7/15/0. P. & P. 3/-.

T.V. CONVERTER for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s band. I.F. will work into any existing T.V. receiver between 42-68 Mc/s. Input arranged for 80 ohm feeder. EF80 as R.F. amplifier, ECC81 as local oscillator and mixer. The gain of the first stage, R.F. amplifier 10DB. Required power supply of 200 D.C. at 25 mA., 6.3 v. A.C. at 0.6 amp. Input filter ensuring freedom from unwanted signals. Simple adjustments only, no instruments required for trimming. Will work into any T.R.F. or Superhet. Incorporating Band switch, and wire-wound gain control. Fully screened in black crackle finished case, size 5 1/2in. long, 3 1/2in. wide, max. overall height 4 1/2in. £2.19.6. P. & P. 2.6. As above with built-in power supply, £3.19.6. P. & P. 2.6. A.C. mains 200 250.

Extension Speaker cabinet in polished walnut, complete with 10in. P.M. P. & P. 3.-, 24.6.

8in. P.M. Speakers, 4 removed from chassis, fully guaranteed. All by famous manufacturers. P. & P. 1.6. 12.6.

Volume Controls. Long spindle less switch, 50 K., 500 K., 1 meg., 2.6 each. P. & P. 3d. each.

Used A.C. Mains 200 250 volts, 4-valve plus Metal Rectifier, medium wave superhet in polished walnut cabinet, size 14 x 9 1/2 x 7 1/2in., complete with valves 6X8, 6X7, 6C7 and 6D9. 6 1/2" PM speaker. Fully guaranteed. P. & P. 7.6. £3.15.-

Constructor's Parcel: Medium & Long-Wave A.C. Mains 230-250 2-valve plus Metal Rectifier, 22.6. Comprising chassis 10 1/2 x 4 1/2 x 1 1/2in., 2 waveband scale, tuning condenser, wavechange switch, volume-control, heater trans., metal rectifier, 2 valves and v holders, smoothing and bias condensers, resistors and small condensers, and medium- and long-wave coil, litz wound. Circuit and point-to-point, 1.3. Post and packing, 2.5 extra.

Volume Controls. Long spindle and switch, 1. 2. 1. and 2 meg., 4.- each, 10 K. and 50 K., 3.6 each. 1 & 1 meg., long spindle, double pole switch, miniature, 5.-.

Standard Wave-change Switches, 1-pole 3-way, 1.9; 3-pole 3-way, 1.9. Miniature 3-pole 4-way, 4-pole 3-way, 2.6. 2-pole 11-way twin wafers, 5.-. 1-pole 12-way single wafers, 4.-.



20 watt A.C. or D.C. 200 250 v. fluorescent kit, comprising trough in white-stoved enamel, two tubeholders, starter, holder and barretter. P. & P., 1.6. 12.6.

1.200ft. High impedance recording tape on aluminium spool 12.6 post paid.

Polishing attachment for electric drills. Quarter-inch spindle, chromium-plated, 5in. brush, 3 polishing cloths and one sheep-skin mop, mounted on a 3in. rubber cup. P. & P., 1.6. 12.6. Spare sheep-skin mops, 2.6 each.

R. & T.V. COMPONENTS (ACTON) LTD.

23, HIGH STREET, ACTON, LONDON, W.3


SPECIAL OFFER — VERY LIMITED QUANTITY
7 valve push-pull A.C. Mains 200/250 v.

RADIOGRAM CHASSIS

3 wave band, coverage short wave 16-50 m., medium wave 187-550 m., long wave 600-2,000 m., 4 controls, volume control on-off, tone control, tuning and wave change with gram position. Valve line up X79, W27, two DH77's, two EL41's and EZ30, Output 7 watts. Size of chassis 16in. x 7in. x 2 1/2in. Size of scale 12in. x 4in. Overall height including back plate 7 1/2in. BRAND NEW. Fully guaranteed. P. & P. 7/6. **£9. 19. 6**

PATTERN GENERATOR

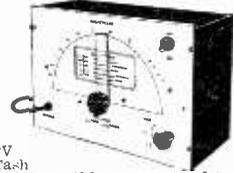40-70 Mc/s direct calibration, checks frame and line time-base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver-plated coils, black crackle-finished case 10" x 6 1/2" x 4 1/2" and white front panel. A.C. mains 200/250 volts. This instrument will allow any TV receiver accuracy 1%. Cash price £3.19.6 or 29.- deposit and 3 monthly payments of £1 P. and P. 4.- extra.



Complete A.C. Mains 3 Valve plus metal rectifier T.R.F. kit. In the above cabinet, £3 15 0. plus 3 6 P. & P.

PLASTIC CABINET as illustrated, 11 1/2 x 6 1/2 x 5 1/2in., in walnut or cream. ALSO IN POLISHED WALNUT, complete, with T.R.F. chassis, 2 waveband scale, station names, new waveband, back-plate, drum, pointer, spring, drive spindle, 3 knobs and back, 22.6. P. & P. 3.6.

As above with Superhet Chassis, 23.6. P. & P., 3/6.

As above complete with new 5in. speaker to fit and O.P. trans., 40.-. P. & P. 3.6. With Superhet Chassis, P. & P. 3/6. 41.-.

Used Metal Rectifier, 230 v. 50 mA., 3.6; 4 gang with trimmers, 6.6; M. & L. T.R.F. coils, 5.-; 3 Govt. valves, 3 v.h. and circuit, 4.6; heater trans., 6.-; volume control with switch, 3.6; wave-change switch, 2.-; 32 x 32 mfd., 4.-; bias condenser, 1.-; resistor kit, 2.-; condenser kit, 4.-.

P.M. SPEAKERS, 6 1/2in. closed field, 13.6. 8in. closed field, 20.6. 10in. closed field, 25.-. 3 1/2in., 16.6. P. & P. on each, 2.-.

Valveholders, Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded B7G, 7d. Octal amphenol, 7d. Octal pax., 7d. Mazda Amphen., 7d. Mazda pax., 4d. B8A, B9A amphenol, 7d. B7G with screening can, 1.6. Duodecal paxolin, 9d.

Twin-gang .0005 Tuning Condensers, 5.-. With trimmers, 6.2.

32 mfd., 350 wkg. ...	2.-	16 1/2 mfd., 350 wkg. ...	3.3
16 x 24 350 wkg. ...	4.-	60 - 100 mfd., 280 v. wkg. ...	7.-
4 mfd., 200 wkg. ...	1.3	50 mfd., 180 wkg. ...	1.9
40 mfd., 450 wkg. ...	3.6	65 mfd., 220 wkg. ...	1.6
16 x 8 mfd., 500 wkg. ...	4.6	8 mfd., 150 wkg. ...	1.6
16 x 16 mfd., 500 wkg. ...	5.9	50 mfd., 12 wkg. ...	11d.
16 x 16 mfd., 450 wkg. ...	3.9	50 mfd., 50 wkg. ...	1.9
32 x 32 mfd., 350 wkg. ...	4.-	Miniature wire ends	
25 mfd., 25 wkg. ...	11d.	moulded 100 pt., 500 pt.,	
250 mfd., 12 v. wkg. ...	1.-	and .001 ca. ...	7d.
16 mfd., 500 wkg., wire		280-0-280 80 mA., 4 v. 4 a.,	
ends ...	3.3	4 v. 2 a. ...	14.6
8 mfd., 500 v. wkg., wire		250 v. 350 mA., 6.3 v. 4 a.	
ends ...	2.6	twice, 2 v. 2 a. ...	19.6
8 mfd., 350 v. wkg., tag		Auto-trans., input 200 250	
ends ...	1.6	11T 500 v. 250 mA. 6 v.	
1000 mfd., 350 wkg. ...	4.-	4 a. twice 2 v. 2 a. ...	19.6

Potato & Vegetable Peeler, by famous manufacturer, capacity 1 1/2 lbs., complete with water pump. All aluminium construction, white stove-enamel finish. Originally intended for adaptation on an electric food-mixer, can easily be converted for hand operation. 39.6. P. & P. 3.-.

Where post and packing charges are not stated, please add 1/6 up to 19.-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.



FOR ALL RADIO PARTS | **VALVES—GUARANTEED NEW AND BOXED**

024	6/-	5U4G	8/6	6F13	12/6	6U7G	9/-	10F9	12/6	25Z6GT	8/6	EZ40	10/-	PCF80	13/6	VR57	8/-
1A3	3/-	5Y3GT	8/6	6F14	12/6	6V6G	7/6	10P13	11/6	35L6GT	9/-	EZ41	11/-	PCF82	12/6	VR55	3/6
1A5GT	8/6	Z2S	8/9	6F15	13/-	6V6G/GT	7/6	12A6	6/9	35W4	10/-	EZ80	10/6	PL81	13/6	VR65A	3/3
1A7	11/6	5Z4	8/9	6G6G	4/6	6X4	8/-	12A7	6/9	35Z4GT	9/-	E148	2/-	PL82	11/6	VR66	3/6
1C5GT	8/6	6A7	10/6	6H6	3/6	6X5G/GT	7/9	12AT7	9/-	50L6GT	9/-	FW4/500		PL83	13/-	VR91	5/9
1H5	10/6	6ARC/GT	10/6	6J5G/GT	5/-	7B6	9/6	12AU7	9/6	A231	11/6			PP225	5/-	VR918YL	7/6
1L4	6/6	6AC7	6/6	6J5M	6/6	7B7	8/-	12AX7	10/-	AC/PE	6/9	GZ82	12/6	PY80	10/-	VR92	2/-
1LD5	6/9	6AG5	6/6	6J6	7/6	7C5	8/6	12B6	10/-	AC/PEPEN	5/6	H30	5/-	PR31	11/6	VR105/30	7/-
1N5	10/-	6AK5	6/6	6J7G	6/6	7C6	8/6	12C8	8/-	ATP4	6/6	H12	5/6	PY82	10/6	VR116	4/-
1R5	8/-	6AL5	7/-	6K6GT	6/6	7H7	8/-	12H6	8/-	DH73M	10/-	H123DD	7/6	QP21	7/6	VR119	4/-
1T4	7/6	6AM5	5/-	6K7G/GT	5/9	7Q7	8/-	12J5	8/-	EAF42	12/6	H141	5/-	SP22	6/-	VR123	9/-
1U5	7/6	6AM6	7/6	6K7	6/9	7R7	8/6	12J7	9/6	EB41	9/-	HP211C	6/9	SP220	6/9	VR136	7/-
2X2	4/-	6AQ5	8/6	6K8G	8/9	787	9/-	12K7	9/6	EM41	11/-	K135	8/6	U16	9/-	VR137	6/6
3A4	7/-	6AT6	8/6	6K8GT	9/6	7Y4	8/6	12K8	11/-	EBF80	11/6	K2	5/-	U22	8/-	VR150/30	9/-
3D6	5/6	6B4	5/-	6L1	13/6	75	10/6	12Q7	9/-	ECC81	8/6	KT33C	6/9	U25	13/6	VR70	8/-
3Q4	9/6	6B8G	4/-	6L6G	9/-	77	8/-	12R07	7/6	ECH35	13/6	KT66	10/6	U29	13/6	V870	3/-
3Q5	10/-	6BA0	8/6	6L7M	7/6	80	8/6	12R07	7/6	ECH42	10/6	KT74	8/6	U403	10/-	VT2	8/-
3V4	8/6	6BB6	8/-	6N7	7/-	807	7/6	12S7	7/6	ECL80	11/6	KTW61	7/9	U404	9/-	VT501	6/9
4D1	3/-	6BE7	9/6	6Q7G/GT	9/-	8D2	2/9	12S7	8/6	EP22	8/6	KTW63	8/6	UB41	8/-	VTU39	8/9
42	8/-	6BW6	8/6	6SA7GT	8/-	9D2	3/9	12SK7	6/6	EP41	11/6	KTZ41	6/-	UC-41	11/-	VU64	8/6
		6CJ	7/-	6SG7	7/6	9001	5/6	12SQ7	8/6	EP42	13/6	LP220	6/9	UCH42	11/-	VU66	8/6
		6CSGT	7/6	6SH7	6/-	9003	5/6	12SR7	7/6	EP80	11/6	MH4	5/9	UC41	11/6	VU111	3/6
		6C6	6/6	6S17GT	8/-	9004	5/6	12SX7	12/6	EL2	12/6	M9/PEN	5/-	UL11	11/6	VU120A	3/-
		6C9	9/-	6SK7	6/6	9006	6/-	20D1	10/6	EL35	7/6	N70	12/-	UY41	10/6	W61	8/-
		6D3	7/6	6SL7	8/-	954	2/-	20P2	12/6	EL41	11/6	P215	8/-	VR21	3/-	W77	8/6
		6D6	7/3	6SN7	8/-	955	4/9	20L1	12/6	EL84	12/-	PN25	8/-	VR33	6/-	X65	10/-
		6F1	12/6	6SQ7	9/-	956	3/6	25L6GT	8/6	EM34	11/6	PN46	8/6	VR52	3/6	X66	11/6
		6F6G	7/6	6SR7	8/-	10C1	12/6	25U4GT	9/6	EM80	11/-	PEN220A		VR54	2/-	Y63	9/-
		6F9M	8/6	6U44T	15/-	10C-9	12/6	25Y5G	9/-	EY51	13/6			VR55	7/6	Y63	9/-
		6F11	13/-	6UG5	8/6	10P1	11/6	25Z4G	9/-	EY91	7/-	PC84	13/6	VR36	6/-	150A(B)	4/9

● POSTAGE EXTRA. SINGLE VALVES 6d.

Build this Excellent Kit for Yourself



ALPHA 3 VALVE T.R.F. KIT

£5.10.0

- ★ Easy to build.
- ★ Valves 6J7, 6K7, 6V6GT plus metal rectifier.
- ★ Walnut Cabinet.

Full instructions, point-to-point wiring diagram. Circuit diagram, and full shopping list 1/-. All components may be purchased separately.

Mail Order only. For terms see our advertisement on Page No. 5.

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."




5/6 VINCES CHAMBERS
VICTORIA SQUARE
LEEDS 1.

Do you want VHF and 3D sound ?

Easy to fit and install components to make your Radio as modern as this year's models.

Fit one or more TSL hi-fi electrostatic speakers to your set and get that all around, balanced, high quality 3D sound. Capture the beyond-aural-range sounds in the very high frequencies of the sound spectrum. These speakers with the GOLD coated diaphragms are an absolute MUST for FM reception, high quality L.P. recordings and television sound reproduction. Their output from 8 to 20 Kc/s is plus 16 dB over their nominal response at 3 Kc/s. Can be fitted to any Receiver, Radiogram or T.V. Receiver.

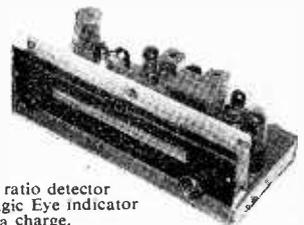designed, the TSL Adaptor is self powered and only one connection is required to turn your old A.M. set into a modern VHF Receiver.



SPECIFICATION. The TSL FM/VHF tuner contains 5 valves and 10 tuned circuits. Grounded grid R.F. stage, additive mixer, two high gain I.F. Stages, ratio detector stage and rectifier. A Magic Eye indicator is available at a small extra charge.

SENSITIVITY. 0.9 MV. This extreme sensitivity enables this unit to be used up to 120 miles radius from FM Transmitters operating on VHF.

SIGNAL TO NOISE RADIO. Better than 30 dB for input of 1.8 microvolts.

RADIATION. At extreme minimum and is lower than any other available equipment.

TUNING DRIFT. Negligible, due to all capacitors and resistors being high stability type.


BANDWIDTH. Design enables unit to receive absolutely free from distortion audio range from 15 to 20,000 cycles.

OUTPUT. Up to 40 volts r.m.s. available depending on input signal.

FREQUENCY COVERAGE. 85 to 101 megacycles.

This unit can be supplied complete for **£14.8.0** (incl. P.T.) completely valved and aligned. Alternatively, all essential components are available for home construction to published specification.

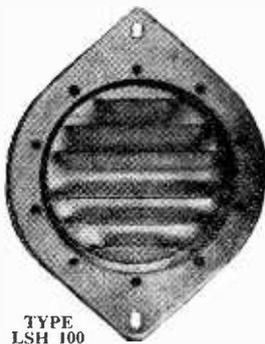Ask your Local Retailer or in case of difficulty write, call or phone:



TYPE LSH 100

TYPE LSH 75 for single-ended output and small push-pull amplifiers ... **12/6**

TYPE LSH 518 High output wide-angle model for medium power amplifiers ... **17/6**

TYPE LSH 100 High power diffused model for ALL classes of amplifiers ... **21/-**

(None of the above prices is subject to Purchase Tax.)

NO INTERFERENCE

The TSL FM/VHF unit will transform your present radio receiver or radiogram and enable you to hear radio under absolutely perfect conditions free of interference from ignition, electrical apparatus, heterodyne whistles or static. Laboratory

TECHNICAL SUPPLIERS LTD., Hudson House, 63, Goldhawk Rd., W.12. SHE 2581 & 4794.

TRANSMITTING TOPICS



DESIGNING THE POWER PACK

By O. J. Russell, B.Sc.(Hons.), G3BHJ

IN the case of the choke input circuit we determine the ripple across a condenser connected to the output of the choke (Fig. 7). This means that we must multiply the effective choke inductance in henries by the value of the following condenser in microfarads and use this figure to determine the ripple from Fig. 7. If a swinging choke is used, clearly the lowest value of choke inductance (i.e., 5 henries) must be used to give the value of ripple at full load output.

It will be seen that the output ripple may be quite low at low output currents. However, for practical high-power outputs, the ripple must be reduced in both the choke input and the condenser input circuits. A filter circuit must be used as shown in Fig. 8. The addition of this filter to the condenser input circuit gives the familiar "power pack" circuit of Fig. 9. The result of adding a filter to the choke input circuit gives the less familiar circuit of Fig. 10. The ripple reduction possible with a single filter is shown in Fig. 11. Thus, once the rectified output ripple is determined from Fig. 6 or Fig. 7, according to the type of circuit used, the ripple reduction factor needed is chosen to reduce this to a given value. Thus, if we start with 10 per cent. ripple, and need a final ripple of 0.2 per cent., we need a ripple reduction factor of 50. The curve of Fig. 11 shows that the product of filter choke inductance multiplied by filter capacitance must be 90 to give the ripple reduction factor of .02 (i.e., one-fiftieth). Thus, a 9 μ F condenser and a 10 henry choke might be used. Practically, a standard value of condenser such as 8 μ F would be chosen,

and this with a 12 henry choke would actually give a little greater smoothing action.

It will be noted that if a great reduction of ripple is needed two cascaded filter stages (Fig. 12) may be used. Thus two cascaded stages giving each a ripple reduction of 20 (i.e., a factor of .05) will together give a factor of .0025—a reduction of 400 times. Actually the use of two cascaded stages is a very economical means of achieving a high degree of smoothing. Thus, a single stage to give a reduction of 100 times in ripple needs a value of L.C.=180. So that approximately an 8 μ F condenser and a 25 henry choke might be used. For heavy currents the choke would be quite expensive. Two cascaded stages of ripple factor 0.1, need each an L.C. of 20. Thus two 5 henry chokes and two 4 μ F condensers would suffice to make a cascaded two section filter giving an overall reduction of 0.01 or 100 times. Two 5 henry chokes would be appreciably cheaper than one 25 henry choke, while two 4 μ F condensers cost about the same as one 8 μ F condenser. It will also appear with a little use of Fig. 11 that when hum is appreciable, and a further reduction is needed, stepping up the filter condenser in value is an expensive way of effecting hum reduction. It will be found very much more effective to use an additional small filter with a small choke and condenser to effect a large hum reduction. This applies forcibly to high voltage packs, where cheap electrolytics cannot be used. In any case one hesitates to use electrolytics in the TX pack for fear of the disastrous results of breakdown—even although 900 volt (but not cheap!) electrolytics are now available.

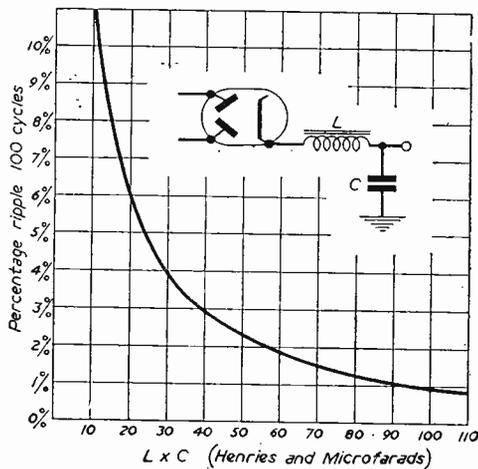


Fig. 7.—Ripple output of a choke input circuit across the following condenser. The product of L and C determines the ripple percentage.

Voltage Rating

This brings us to the voltage rating of the condensers. In the condenser input pack the output voltage at "no load" may soar to the A.C. peak value. Thus the *minimum* working voltage must be for safety at least 1.5 times the transformer voltage. Thus a pack using a

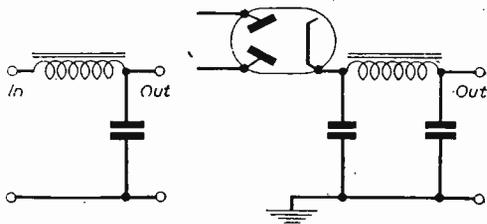


Fig. 8 (left).—A filter stage used to reduce hum. It follows the input circuit. Fig. 9 (right).—Adding a filter section to the condenser input circuit gives the familiar "power pack" circuit as used in many small power supplies.

600-0-600 transformer needs condensers of 900 volt working—or, say, 1,000 volt working for a good safety margin. In the case of the choke input circuit, provided the calculated bleeder resistance is used, the working voltage may be the nominal transformer voltage., i.e., for the above case 600 volts working. Thus it will now be apparent that the choke input circuit, if correctly used, has many advantages over the condenser input circuit. Incidentally, while a bleeder resistance is an integral part of the design of the choke input circuit it should also be used on *any* power pack. The bleeder resistance by discharging the condensers when the pack is switched off, acts as a very useful safety measure, as the filter condensers may hold enough charge to do serious damage—to equipment or operator. Good condensers may hold a charge for days, so that a serious shock might be received long after the pack has been switched off. The provision of a bleeder resistor obviates this difficulty.

There is one other trifling precaution to be noted

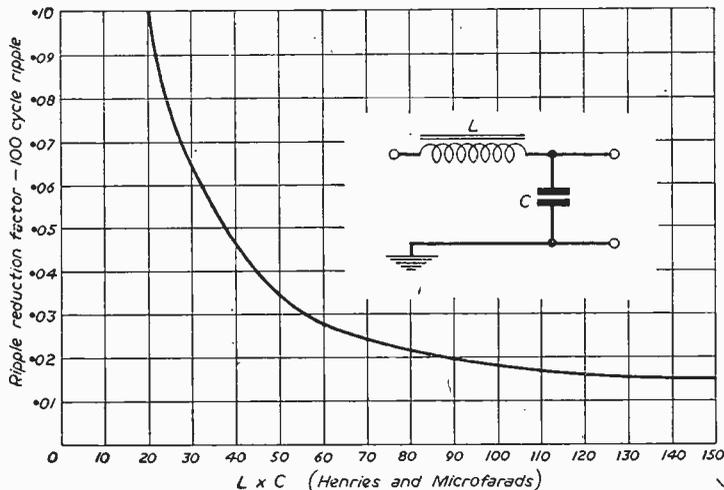


Fig. 11.—Ripple reduction factors for an LC filter stage.

in selecting filter components for a power pack design. It is advisable to select values of choke and condenser which do not resonate at ripple frequency. If resonance at ripple frequency occurs hum may be vastly exaggerated, or dangerous ripple voltages and currents may build up in the resonating components. The value of L.C. (where L is in henries and C is in microfarads) at which resonance occurs for 100 cycle ripple (as is obtained from a full wave rectifier

on 50 cycle A.C. mains) is given by $L.C. = 2.53$. This value, or values near it, should be avoided. It is, of course, a very low value of filter components, which,

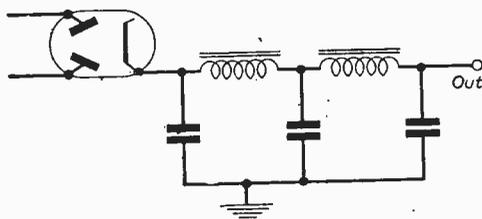


Fig. 12.—A condenser input circuit, followed by two cascaded filters for very great reduction of hum level.

however, might be accidentally approached—say, by using a surplus 2.5 henry choke plus a 1 μ F. condenser to add a little extra filtering. However, examination of Fig. 11 shows that these values would give only a very little reduction of ripple. The value is not shown on Fig. 11, but it does indicate it would be small—say, only cutting hum by a half. Due to the resonance effect, however, such values would probably increase hum! Here, again, then the danger of “hit and miss” methods is illustrated. The precise design to the last decimal dot is, of course, unnecessary, and the curves and data given have been intended to reduce the labour of designing a reasonable power supply of low ripple content to the minimum. If the material results in an overhaul of existing power packs it will also have been useful!

Books Received

WIRELESS WORLD DIARY, 1956. Published October 7th, 1955, by Iliffe and Sons Ltd. Size 4½ in. x 3½ in. 79 pages of reference material—plus the usual diary pages of a week to an opening. Leather 5s. 10d. (inc. 10d. P.T.); Rexine 4s. 1d. (inc. 7d. P.T.). Postage 2d.

ELECTRICAL ENGINEERING RADIO & TELEVISION DIARY, 1956. 92 pages technical information, including radio and television, road map section. 5s. 6d. leather; 4s. 3d. leather cloth, including postage. Published by H. O. Quinn, Ltd., 151, Fleet Street, E.C.4.

QUESTIONS AND ANSWERS ON RADIO AND TELEVISION. By E. Molloy. 148 pp. Illustrated. Published by Geo. Newnes, Ltd. Price 6s.

RADIO SERVICING POCKET BOOK. By E. Molloy and J. P. Hawker. 212 pp. With 188 tables and illustrations. Published by Geo. Newnes, Ltd. Price 10s. 6d.


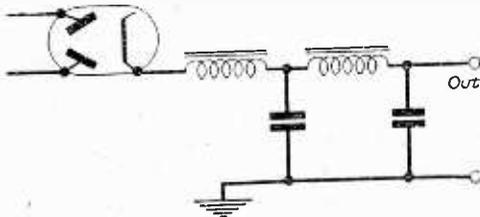


Fig. 10.—A choke input circuit followed by a filter stage gives a complete choke input power pack circuit for practical use.

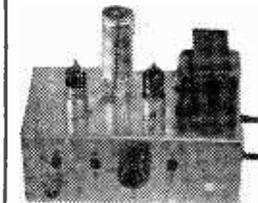BAND 3 T/V CONVERTER—186 M/cs - 196 M/cs £2-5-0 post free.



This Unit comprising drilled chassis, 7in. x 4in. x 2 1/2in., two miniature valves and met. rect., wound coils, res., cond., etc., is a slightly modified version of the circuit shown in *Wireless World*, May, 1954. It has proved itself highly successful—over 3,000 sets have already been sold to buyers all over England. We invite you to visit us and see it in operation for yourselves. Suitable for most types of T/V sets. T.R.F. or Superhet. Blueprint and circuit details will be sent on application by


return of post. 1/6, post free. Supply voltages required 200-250 v., 20 mA. H.T. 6.3 v. 1 a. L.T. Power pack components to fit chassis as illustrated, 30/- extra. Complete set wired, tested and aligned ready for use, 20/- extra. Band 1, Band 3 Ae switching can now be added, switch kit, 6/6. Full range of Band 3 aerials in stock. Adaptors from 7/6 per set, Dipoles-indoor 6/6, outdoor with cable 13/6, Band 1-Band 3 Cross-over filter unit, 10/6.

Volume Controls

Midget Edisonian type. Long spindles. Guaranteed 1 year. All values. 10,000 ohms for 2 Meg. ohms.
No Sw. S.P.Sw. D.P.Sw. 3/-. 4/- 4/9
COAX PLUGS ... 1/2
SOCKETS ... 1/-
COUPLER ... 1/3
OUTLET BOXES ... 4/6

80 ohm COAX

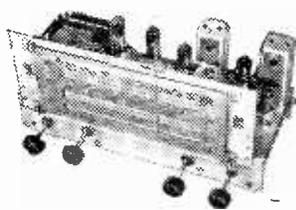STANDARD 1/4 in. diam. Polythene insulated. GRADE "A" ONLY.
8d. yd.
SPECIAL—Semi-air spaced polythene. 80 ohm Coax 1/4 in. diam. Stranded core. Losses cut 50%.
9d. yd.



ALL WAVE RADIOGRAM CHASSIS THREE WAVEBANDS FIVE VALVES

S.W. 1 m.—50 m. LATEST MIDGET
L.W. 800 m.—550 m. B.V.A.
L.W. 800 m.—2,000 m. SERIES
Brand New and Guaranteed. A.C. 200/250 v. Four positions. Wavechange switch. Short-Medium Long-Range. Pick-up connections. High Q iron-stud core coils. Latest circuit technique, delayed A.V.C. and Negative feedback. Output approx. 4 watts. Chassis size 13 1/2 x 5 1/2 x 2 1/2 in. Glass Dial—10 in. x 4 1/2 in. horizontal or vertical type available, 1st or 2nd Pilot Lamp. Four Knobs supplied. Walnut or Ivory to choice, aligned and calibrated ready for use. Chassis isolated from mains. **PRICE £9.15.0**
Carriage and Insurance, 4/6. **PRICE £9.15.0**
8in. or 10in. spacers to match available.

TWIN FEEDER, 80 ohms, 6d. yd.; 300 ohms, 8d. yd.
TWIN SCREEN FEEDER, 80 ohms, 1/- yd.
50 OHM COAX CABLE 8d. per yd. 1/4 in. dia.


TRIMMERS, Ceramic, 4 pf.—70 pf., 9d. 100 pf., 150 pf., 1/3; 250 pf., 1/6; 500 pf., 1/9. PHILIPS Beehive Type—2 to 8 pf. or 3 to 30 pf., 1/8 each.
RESISTORS.—Pref. values 10 ohms 10 megohms.

CARBON WIRE WOUND
20% Type. 1 w., 3d.; 5 w., 25 ohm—1/3
1 w., 5d.; 1 w., 6d.; 10 w., 10,000 1/6
2 w., 9d.; 15 w., ohms 2/-
10% Type. 1 w., 9d.; 5 w., 15,000—1/9
5% Type. 1 w., 1/-; 10 w., 33,000 2/6
1% Hi-Stab. 1 w., 2/-; 10 w., ohms 2/3

WIRE-WOUND POTS.
Pre-set Min. T.V. Type. Knurled Slotted Knob. All values 25 ohms to 30 K., 3/-; 50 K., 4/-; 100 K., 5/6. Carbon Track 50 K. to 2 Meg., 3/-.

CONDENSERS—Mica or S. Mica. All pref. values. 3 pf. to 680 pf., 6d. ea. Ceramic types, 2.2 pf.—5,000 pf. as available, 8d. each. Tubulars, 450 v., Huns and T.C.C., .0005, .001, .003, .01, .02, and 1.550 v., .0d., .05, 1.500 v., Huns Molded, 1/-, .25 Huns, 1/6. 5 Huns, 1/9. 11 1,500 v. T.C.C. (Simplex), 3/6. .001, 8 kv., T.C.C., 5/6. and 12.5 kv. T.C.C., 9/6.

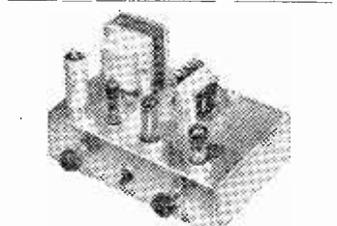SILVER MICA CONDENSERS—10/-
3 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3.
1 pf., 1.5 pf. to 200 pf., 1/9. 513 pf. to 5,000 pf., 2/-.



3 VALVE AMPLIFIER

With variable Tone and Volume controls. 3 Midget B.V.A. valves, 4 watts output. Neg. feedback. Chassis isolated from Mains. A.C. 200/250 v. A quality amplifier at an economical price. **PRICE £3.19.6** Carr. 2/6. Wired and tested, 15/- extra. Blueprint, circuit and instr., 1/6 (free with kit).

BARGAIN VALUE IN RECORD CHANGERS

Recommended for above chassis
B.S.E. MONARCH—Latest Model 3 sp. Auto-Changer Mixer Unit. Famous Magidisc, 7, 10 and 12 in. Record Selector. Modern Cream Styling Dual Xtal Cartridge stylus for 2 Hi-Fi reproduction. As used by leading manufacturers. Bargain Price.
£8.19.6 Carr. 4/6
ins.

NEW BOXED	VALUES	ALL GUARANTEED
1R5	7/6 6Q7	8/6 EL80 12/6 MU14 8/6
1S5	7/6 6N7	9/- EP41 10/6 PCC84 12/6
1T4	7/6 6V6	7/6 EF50 PCE80 12/6
1S4	7/6 6X4	8/6 Mullard 10/- PCE82 12/6
3S4	8/- 6X5	8/- EP50 PL41 12/6
3V4	8/- EA50	2/- Equip. 5/6 PL82 10/-
3D6	3/6 EBC41	10/6 EPS9 10/6 PL83 12/6
5Z4	8/6 EB91	7/6 EP86 13/6 PY80 11/-
6AM6	8/6	6/6
6AT6	8/6 EBC33	8/6 EL41 11/6 PY82 10/-
6CH6	10/6 ECC83	12/6 EL84 12/6 SP41 5/6
6HM6	3/6 ECC84	13/6 EM90 12/6 SP61 8/6
6K7	6/6 EBF29	13/6 EY51 12/6 T22 8/6
6K8	9/- ECH42	10/6 E240 10/- U25 12/6


SPECIAL PRICE PER SET.
1R5, 1T4, 1S5, and 2S1 or 3V4 ... 27/6
6K8, 6K7, 6Q7, 6V6, 3Z4 or 6X5 ... 35/-
SPEAKER FRET—Expanded Bronze anodised metal sin. x sin., 2 3/4; 1 1/2 in. x sin., 3/-; 1 1/2 in. x 1 1/2 in., 4/3; 1 1/2 in. x 1 1/2 in., 6/-; 2 1/4 in. x 1 1/2 in., 8/6, etc.
TYGAN FRET (Murphy pattern)—1 1/2 in. x 1 1/2 in., 2/-; 1 1/2 in. x 1 1/2 in., 3/-; 1 1/2 in. x 2 1/4 in., 4/- etc., etc.

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	Can Types, Chps. 3d. ea.
25/25 v., 50 12 v.	1/9 8+8/450 v. T.C.C. 4/6
50/50 v., 4,500 v.	2/- 8+16/450 v. Huns 5/-
100 25 v.	2/- 16+16/275 v. T.C.C. 4/6
8/500 v., Dub.	2/6 16+16/450 v. B.E.C. 5/6
8+8 500 v., Dub.	4/6 16+16/450 v. T.C.C. 6/-
8+16 450 v. Huns	5/- 16+24/350 v. B.E.C. 5/6
16/450 v. B.E.C.	3/6 32+32/450 v. B.E.C. 6/6
16/500 v. Dub.	4/- 60/350 v. B.E.C. 6/6
32/450 v. T.C.C.	5/6 60+100/350 v. 11/6
32/350 v. B.E.C.	4/- 60+250/275 v. 12/6
32/500 v., Dub.	5/- 100+200/275 v. B.E.C. 12/6
32, 32/350 v. B.E.C.	5/6

MAINS TRANSFORMERS

Made in our own Workshops to Top Grade spec. Fully interleaved and impregnated. **RADIO AND AMPLIFIER TYPE**—250 v., 60 ma. P.W. sec. 5 v. or 6.3 v. 1 a. rect. 6.3 v. 2.5 a. set Htrs., 21/-, etc. C.R.T. HTR., **ISOLATION TYPE**—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1:2.5, 2 v. 10/6; 4 v. 10/6; 6.3 v. 10/6; 13.3 v. 10/6. Ditto with mains primaries 200/250 v. 12/6. Specials to order. **SPECIAL TYPES**—To de-icers spec. Simplex, 35/-; Viewmaster, 35/-; 15va, 30/-; P.W. Tape Deck, 22/6; Soundmaster, 35/-; Mullard Amp., 35/-; Osram 912, 35/-; **HEATER TRANSF.**—Prim. 200/250 v. 6.3 v. 1.1 a. or 1 v. 2 a., or 12 v. 7.5, 7.6; 8.3 v. 3 a. or 5 v. 3 a., 10/6. **L.F. CHOKES**—10 H. 65 ma., 5/-; 15 H. 100 ma., 10/6; 10 H. 120 ma., 10/6; 20 H. 150 ma., 15/6; Simplex, 10/6; Soundmaster, 10/6; P.W. O.R. gram., 13/6. **OUTPUT TRANSF.**—Soundmaster 6/6; P.W. Quality R gram., 35/-; Osram 912 sectionalised windings, £3.10.0. Mrs. surplus types, standard pentode, 4/6; ditto tapped priv., 4/9; small pentode, 3/9; Midget battery pentode (1-4, 3V4, etc.), 4/6. **SOLID SOLDERING IRONS** (200-220v. or 230-250v.) 25 watt, instrument type, 21/-; 65 watt, Pentil Kit Type, 26/8; 85 watt, Oval Kit Type, 25/-; Comprehensive stock of spares available. **CRYSTAL DIODE**—Very sensitive. (G.E.C. 2/-). **RECORDING TAPE**—120ft. reels, Scotch boy, 30/-; competitive paper type 12/6.

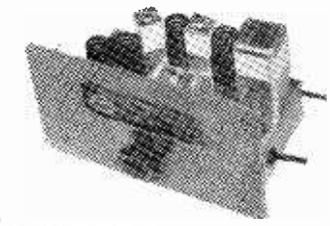

F.M. TUNER-UNIT 87 mc/s—105 mc/s, by Jason. —As tested and approved by Radio Constructor. Complete kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, coils and cans, 4 B.V.A. miniature valves and all components, etc. for only **£6.10.0**, post free. **SUPERIOR TYPE**—GLASS DIAL—Calibrated in Mc/s and edge lit by 2 pilot lamps, 12/6 extra. Illustrated hand-book with full details, 2/-, post free

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station. Buses 130A, 133, 159, 166 & 190

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain list.

Hours: 9 a.m. — 6 p.m. 1 p.m. Wed. OPEN ALL DAY SAT.

Terms C.W.O. or C.O.D. Kindly make cheques, P.O.s. etc., payable to TRS. Post/Packing up to 1 lb. 6d., 1 lb. 1/-, 3 lb. 1/6, 5 lb. 2/-, 10 lb. 2/6.



F.M. IS HERE

Many of our Tuners for the B.B.C. V.H.F. programmes are in use up to 80 miles from Wrotham. All parts available to build the Tuner featured recently in the *Radio Constructor*. This Tuner is often known as the Jason Circuit because the booklet was written by G. Blundell of Jason Motor & Electronic Co.

Details of fringe area version also given.

Booklet complete with photos and point-to-point diagram	£ s. d.
Chassis, fully punched	2 0 0
Coil Set	1 2 6
G.E.X.34 Crystal	4 0 0
Jackson Dial	14 6
Jackson V101 25pF + 25 pF	10 9
Jason Dial calibrated in Mc/s complete with bulbholders, already attached to Jackson condenser and fitted to chassis	2 6 3

All parts with Jason Dial less valves. Complete with nuts, screws, solder, tags... 5 14 0

THE JASON MOTOR & ELECTRONIC CO.

328 (rear), Cricklewood Lane, London, N.W.2
 Tel.: SPE 7050 Demonstrations given.
 Evening Demonstrations by Appointment

£5—T.V. TUBES 12" GUARANTEE 6 months

17in. Rectangular, £12.10.0; 14in. rectangular, £7.10.0. All makes 12in. Mullard £5 plus 15/6 insured carriage.

9in. Mullards with slight burns, 3 months guarantee, 18/6 carriage paid. Enquire other types.

9in. Mullards—22/18, 17 or 14C, perfect, 3 months' guarantee, £3.2.6 (Carriage paid).

Stocktaking clearance of 14in. and 15in. round tubes, £5, 3 months' guarantee. *Callers only.*

T.V. CHASSIS 97/6

S/Het., 3 separate chassis (Power, S/vision and time base). R.F., E.H.T., Drawing 2/6 or free with order. Carriage: 5'-London; 10'-Provinces. Valves, tube and speakers extra. Power Pack, 29/6, 5 kv., E.H.T., 325 v., 250 ma. Smoothed H.T. heaters, 6 v., 5 amp., 4 v., 5 amp., with extra winding for 2 or 4 v. tubes. Carr., 4/6.

Time Bases, 10/6. Containing scanning coil, focus unit, line trans., 10 controls, etc. Famous mfr. Drawing FREE. Post 2/6. T.V. SOUND AND VISION STRIP, Birmingham only, 27/6. Superhet, 10 valve holders. Post 1/6.

V.I.F. 1124 RECEIVER, 17/6, with 6 valves ex-W.D. new condition, 3 channel switching. Receives T.V. sound, police, fire and amateurs, 30 Mc's. to 40 Mc's. I.F. 7 Mc's. Post 2/6.

LINE TRANSFORMERS, Ultras, Ferguson, Derwent. Not E.H.T. type. 7/6, plus 1/6 post.

"DENCO" RADIOGRAM CHASSIS, 67/6, S/het. complete with 8in. P.M. speaker, dial and knobs. Famous turret coil tuning, front controls, 4 wave band. Set of Int., octal valves to suit, 50/- extra, carr. 4/6.

100% MONEY BACK GUARANTEE

DUKE *Tele: GRA 6677*

CWO COD

621 ROMFORD RD. LONDON, E.12.

FREE TO AMBITIOUS ENGINEERS!

This 144-page Book



'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

FREE COUPON
 Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME
 ADDRESS

Subject or Exam, that interests me

British Institute of Engineering Technology
 409B, College House, 29-31, Wright's Lane, Kensington, W.8.

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
 - Electrical Eng.
 - Civil Engineering
 - Radio Engineering
 - Automobile Eng.
 - Aeronautical Eng.
 - Production Eng.
 - Building, Plastics, Draughtsmanship
 - Television, etc.
- GET SOME LETTERS AFTER YOUR NAME!
- A.M.I.Mech.E.
 - A.M.I.C.E.
 - A.M.I.P.E.
 - A.M.I.M.I.
 - L.I.O.B.
 - A.F.R.Ae.S.
 - B.Sc.
 - A.M.Brit.I.R.E.
 - CITY & GUILDS GEN. CERT. OF EDUCATION etc., etc.

BIET

"You can rely on us"

LARGE STOCKISTS OF RADIO AND ELECTRONIC COMPONENTS

H.P. on INSTRUMENTS, "912" and MULLARD AMPLIFIER KITS, SOUND-MASTER, VIEWMASTER, Etc., Etc.

RESISTORS — STANDARD, MIDGET, HIGH STABILITY, PRECISION; TAPPED VOL. CONTROLS, Etc., Etc.

SEND FOR LIST.

Proprietary catalogues available to Manufacturers' Laboratories, Education Authorities, etc.

RADIO SERVICING CO.,

82, SOUTH EALING ROAD, LONDON, W.5.

EAL 5737

Voltage Stability in Power Units

ONE of the most deplorable faults in home-constructed power packs is the rapid fall-off of voltage as current is increased. This is due, as most people know, to the action of the reservoir condenser; a surprising number of people are, however, ignorant of the basic principles which govern this action.

The reservoir condenser is connected directly to the cathode of the rectifier, and is, therefore, fed with fluctuating D.C. On an open circuit the voltage across the condenser rises immediately to the peak value, and stays there. If now, however, a resistive load is connected across the condenser, after one of the D.C. peaks has passed, it will start to discharge in the usual manner. It will, during this discharge, receive no further charge from the rectifier until the voltage from it becomes greater than the residual voltage on the condenser. When this happens the rectifier will pass a high charging current to the condenser until the rectifier voltage falls again. This state of affairs is illustrated in Fig. 1.

It can be seen, then, that as the current becomes greater in the load, the discharge rate of the condenser increases and the mean voltage level on it falls. A partial remedy for this trouble is, of course, to use a larger reservoir condenser; but the greater the size of this component the shorter the time available in which to charge it, so the current supplied by the rectifier, instead of being a series of long, weak pulses, becomes a series of short, powerful pulses. Although the actual quantity of electricity passed is no greater, the R.M.S. value, which is the effective value of it for producing heat or other form of energy, rises considerably, and if too large a reservoir condenser is used the heat dissipated in the transformer and the rectifier becomes excessive and damages these components. (The maximum size of the reservoir condenser permissible is generally given with rectifier data in valve books.) The reservoir condenser should, however, be made as large as practically possible. The actual voltage obtainable from the conventional smoothing circuit may be calculated from the formula:—

$$V = Ep / \left(1 + \frac{1}{2RfC} \right)$$

where V is the voltage obtainable, Ep is the peak applied voltage, R is the load resistance in ohms, f is the rectified pulse frequency, and C is the reservoir capacitance in farads. This equation is not strictly accurate for small condensers, as the charging time is not allowed for, but it is sufficient for most purposes.

However large our R.C. factor is, however, the supply is still inherently unstable (a voltage drop of 20 per cent. on full load is considered good) and needs some further apparatus to stabilise it more efficiently. It is found that certain types of gas discharge tube—the gas is usually neon—possess the

fundamental property of keeping a constant voltage across them when lit, to within plus or minus a volt or two. These are useful for many purposes which do not require an absolutely accurate stabilisation, e.g., they are often used in V.F.O.'s. As the circuitry involved is simple, and the cost is fairly low, they have gained much popularity. The basic circuit is shown in Fig. 2.

Basic Circuit

The operation of it is simple; what current the load does not take the stabiliser uses, so that the total current taken remains constant and equal to the current taken by the tube with the load disconnected. Provided that the current taken by the

load does not exceed this, and so extinguish the neon, the voltage will be almost constant except for a slight fall-off in voltage of about five volts for an average tube as the current increases to a maximum. This is, of course, much better than the normal arrangement.

The normal neon stabiliser does not take more than about 120 volts; to obtain higher voltages it is necessary to connect two or more in series. This may be an advantage, however; it enables one to tap off various voltages from the supply without having to use dropping resistors. There is a tube on the market, the Stabilivolt, designed specifically for this purpose.

The series resistor to the stabiliser is calculated so as to have the tube passing maximum current under no-load conditions (the maximum current will be found in a valve data book) according to the formula:—

$$R = \frac{V_{in} - V_{stab.}}{I_{max.}}$$

where V_{in} is the voltage supplied from the smoothing circuit.

For more stable supplies, however, such as are necessary for D.C. amplifiers, neon stabilisers are not really good enough. An electronic stabiliser is then used.

These fall mainly into two divisions; the series type, where a variable load is put in series with the supply in order to stabilise it, and the parallel type, where the variable load is shunted across the true load to take up any current it does not want, so to speak.

MAINTAINING CONSTANT
OUTPUT IRRESPECTIVE OF
THE CURRENT LOAD
By J. McCartney

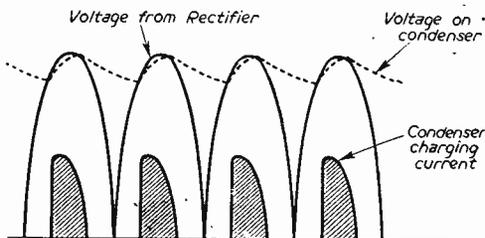


Fig. 1.—Rectifier and condenser charges.

The neon stabiliser is an example of the latter. Parallel stabilisers, unless carefully designed, are inclined to be more unstable than the simple neon, and are invariably difficult to design well, so the home constructor would be well advised to adhere to the series type.

Operation

The operation of it is as follows. An increase in the current taken by the load is followed by a decrease in the voltage across it, as explained previously. This produces a proportional drop in the potential divider R1 R2, which causes a decrease in the current in V1. This causes the grid of V2, which is connected to the anode, to become more positive with respect to its cathode, thereby lowering the resistance of the valve, and causing a greater voltage to be available at the cathode. As the output voltage rises, due to this effect, the grid voltage on V1 also rises, and the valve rapidly returns almost to its previous state. As, however, V2 must now be of a lower resistance, the grid voltage on V1 must still be slightly below its original voltage, and so, therefore, must the output voltage. If V1 is a sufficiently good amplifier, the decrease involved will be negligible. By substituting a D.C. amplifier for this valve, the decrease can be made still smaller if necessary, though this is rarely required. The action of the stabiliser is, of course, exactly the opposite for an increase in load voltage, and is instantaneous, although, for the sake of simplicity, it has been represented as a series of actions in the above description.

The reference voltage must be very stable, and be able to supply the current necessary for V1 at the same time. As the valve in question need only take a very small current, a neon stabiliser connected to the

for a supply of 350 to 450 volts without alteration.) An EF37A is used for V1, as it has a very high amplification factor and takes little current, and an EL37 is used as V2 as it can easily take as much as 100 mA.

The normal bias on V1 is 3.4 volts, when it takes only .5 mA. This value should be adjusted accurately,

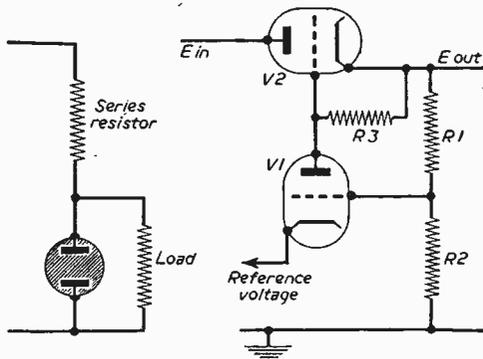


Fig. 2 (left).—Basic circuit, and Fig. 3 (right).—Basis of the new circuit.

by means of R5. The anode load, R2, is 27 kilohms, producing an amplification of about 70 in this valve, and a bias of -13.5 volts on V2 grid. This value should also be checked in setting up. The current taken by V2 should now be about 90 mA with the load connected. It is preferable that a 7475 stabiliser be used, but this may be difficult to obtain, and an ST11 may be used.

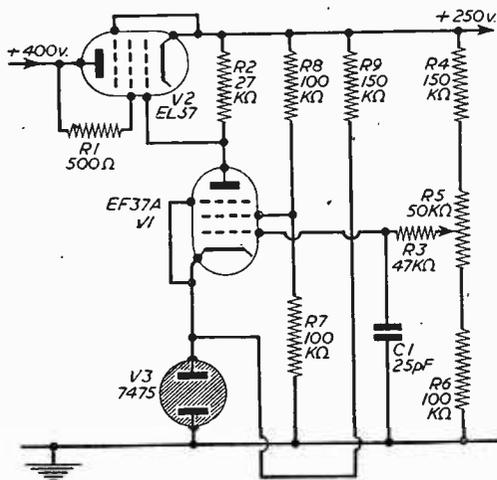


Fig. 4.—Final circuit.

stabilised side of the supply will generally be quite good enough. It should burn at minimum current when the valve is disconnected.

Typical Design

A typical design is shown in Fig. 4. This is arranged to give 250 stabilised volts from a supply of about 400 volts on full load. (It should work satisfactorily

PRACTICAL TELEVISION

December issue

Now on sale. Price 1/-.

The December issue of our companion paper, "Practical Television," has, as the main constructional feature, an article on the construction of a two-valve Pre-amplifier for Band III. The commercial transmissions on this band are not well received in some areas, and additional amplification is called for, in spite of the most elaborate aerial array. The Pre-amplifier for this purpose must have the minimum of losses, and the design which is described utilises the Cascode circuit, with two valves in a miniature totally screened assembly. The design is in keeping with the Band III converter which was the subject of the Free Blue Print in the October issue.


Other articles in this issue deal with the Alignment of TV Receivers, Receiving the I.T.A., Servicing the Ferguson 983T and 988T, further notes on TV DX (a collection of data of transmitters in various countries), Coil Data tabulated for the Band III Converters already described, and details for modifying the View Master for use with a Band III converter. This will be followed in the January issue with details of a special Converter for this and similar types of receiver. Our other regular features are also included.

NEW! THE PRACTICAL WAY of learning RADIO • TELEVISION • ELECTRONICS



COMPLETE EXPERIMENTAL COURSES in RADIO ENGINEERING and SERVICING

An entirely new series of courses designed to teach Radio, Television and Electronics more quickly and thoroughly than any other method. Specially prepared sets of radio parts are supplied and with these we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio receivers, etc. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are ideal and may be yours at very moderate cost. With these outfits, which you receive upon enrolment and which remain your property, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to designing, testing and servicing of complete Radio and Television Receivers.

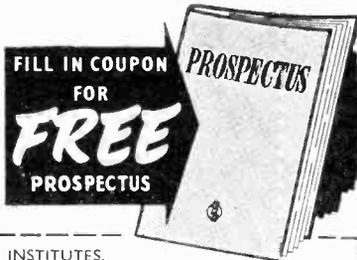

NEW — TELEVISION COURSE
including a complete set of equipment dealing with the design, construction and servicing of a high quality television receiver.
Courses (with equipment) also available in many other engineering subjects.

COURSES FROM 15/- PER MONTH

TO E.M.I. INSTITUTES,
Dept. 32X, Grove Park Road, London, W.4.
Please send me your FREE book on Practical Courses.

NAME _____


ADDRESS _____

JAN.

(We shall not worry you with personal visits.)

E M I I N S T I T U T E S
An educational organisation associated with the E.M.I. Group of Companies which include "HIS MASTER'S VOICE," MARCONIPHONE, COLUMBIA, ETC.

IC.68A

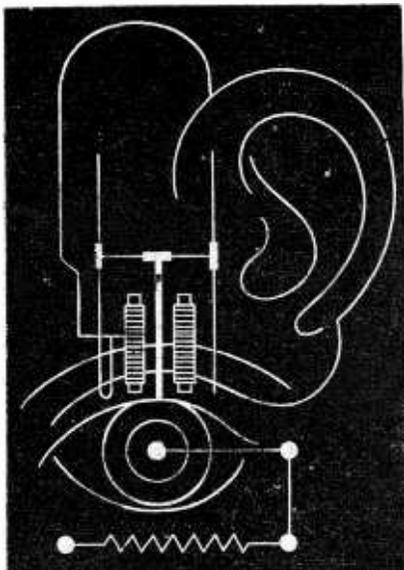

SMITH'S FOR TECHNICAL BOOKS


Books on radio theory, practice and maintenance for the beginner and books on new developments in circuit design, new components, methods of application, and the established text books can be obtained through your local Smith's shop or book-stall. Books not in stock at the branch can be quickly obtained from Head Office.

★ *Your stationery and printed matter can also be supplied through our local branch.*

W. H. SMITH & SON FOR BOOKS ON ELECTRONICS

Head Office: STRAND HOUSE, LONDON, W.C.2

REPANCO HIGH GAIN COILS

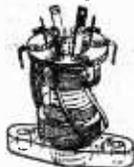

DUAL RANGE MINIATURE CRYSTAL SET COIL, with circuit. Type DRX1, 2/6.

DUAL RANGE COIL with reaction. With 2 mains and 2 battery circuits. Type DRR2, 4/-.

MATCHED PAIR DUAL RANGE T.R.F. COILS, with reaction; with battery and mains circuits. Type DRM3 8/- pair. *(Regd. Design)*

STANDARD I.F. TRANSFORMERS. Type S.E. 1½in x 1in. x 2½in. Pre-aligned, 465 kc/s., 13/6 pair.

MINIATURE I.F. TRANSFORMERS. Type M.S.E. 13/16in. x 13/16in. x 1½in. Pre-aligned, 465 Kc/s., 12/6 pair.

FERRITE ROD AERIAL. Type FR1. Long and medium wave. Complete with fixing brackets, 12/6.

- ★ All coils wound on low loss formers.
- ★ Individually tested and guaranteed.
- ★ Post 3d. on all orders. ★ Trade supplied.

Distributed by :

RADIO EXPERIMENTAL PRODUCTS LTD.

33, MUCH PARK STREET, COVENTRY

Telephone : Coventry 62572

"RE-VIEW" CONVERTERS

FOR ALL AREAS

LONDON.—LI. Complete with built-in Power Supply and Crossover Box £9 6 0

LONDON.—Fringe Areas. LII. Built-in Power Supply £9 9 0

MIDLANDS.—MI. Built-in Power Supply and Crossover Box £9 6 0

MIDLANDS.—Fringe Areas. MII. Built-in Power Supply £9 9 0

SOUTH COAST.—Channel 3. Especially developed high gain model £9 18 0

LOW LOSS CROSSOVER BOX ... 13/6

Finished in stove-enamelled steel case. Instructions for fitting enclosed. Carriage and Insurance Free.

TELEVISION TUBES

MULLARD—COSSOR—MAZDA or equivalents. 12in., £6 10s. ; 14in., £7 10s. ; 15in., £8 10s. ; 17in., £10

3 MONTHS' GUARANTEE

TUBES IN SHORT SUPPLY. ORDER NOW.
Carriage and Insurance 12/6. Cash with order or C.O.D.


RE-VIEW (London) LTD.

85 PARK ROAD, COLLIER'S WOOD, S.W.19

Terms to the Trade.

Phone LI Berty 2825.

Servicing Radio Receivers

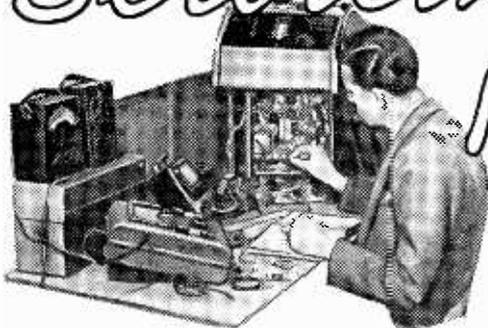

VIDOR PORTABLE CN396

By Gordon J. King, A.M.I.P.R.E.

THE Vidor Model CN396 comes under the category of an A.C. mains and battery suitcase portable. The whole of the receiver, the loudspeaker and the batteries, are housed in the case proper, while the frame aerial is installed within the lid. A unique feature of this model is a warning device which causes a loud buzz to emit from the loudspeaker if the lid is closed while the receiver is switched on.

Batteries

The correct type batteries for this receiver are: L.T. Vidor L5048 7.5 volt all-dry, and H.T. Vidor L5512 90 volt all-dry. It is impossible to connect the batteries the wrong way round, or inadvertently change their positions, owing to the type of sockets used, but extreme care should be taken to prevent the L.T. plug or wire coming into contact with the H.T. battery connections.

The Circuit

Full details of the circuit are shown in Fig. 1. From this it will be seen that the normal valve line-up is used, that is: V1-DK91—working as frequency changer; V2-DF91—as I.F. amplifier; V3-DAF91—as detector, a.v.c. and audio amplifier; V4-DL94—as output, and V5-EZ41—as full-wave H.T. rectifier.

The signals induced into the frame aerials (A1 by itself is for L.W. operation and A1 shunted by A2, by operation of S1, is for M.W. operation) are mixed in V1 with the local oscillator voltage and give rise to an intermediate frequency signal at 456 kc/s across the first I.F. transformer in the anode.

The aerial circuits are tuned by C1 section of the tuning gang and pre-tuned on L.W. by trimmer T1. The oscillator circuits are tuned by C2 section of the tuning gang, and pre-tuned on M.W. by trimmer T2; for L.W. operation the oscillator grid coil is shunted by a 540 pF capacitor through switch S3.

The I.F. signals appear on the control grid of V2 and in amplified form across the second I.F. transformer in the anode. These signals are demodulated by the diode in V3, and the A.F. content is developed across the 1 M. volume control R1. The mean D.C. level of the rectified I.F. signal is also reflected along the a.v.c. line connected to R2; this biases V1 depending on the amplitude of the signal. No a.v.c.

bias is applied to V2. R3 and associated 100 pF capacitors form an I.F. filter circuit.

The A.F. signal is thus tapped off R1 and fed through the coupling capacitor C3 to the control grid of V3. This appears in amplified form across R4 and is fed through C4 to the control grid of V4, which is operating as an output valve and energises the loudspeaker in the usual way. Fixed tone correction is provided by C5 and negative feedback by means of R5.

Switch S4 operates the warning device and is brought into operation by the metal check-strap of the lid, making contact between two springs fixed on the inside of the case. This results in positive feedback, via C6, between the screen-grid of V3 and the anode of V4.

On mains operation H.T. is fed from the cathode of V5 through R8 and switch S8 to the H.T. line, and L.T. through R7, R6 and S7. Grid-bias for V4 is obtained from the H.T. volts drop across R9 in the H.T. negative circuit. H.T. and L.T. smoothing is performed by electrolytic capacitors C7, C8, C9 and C10. The filament resistors R12, R13 and R14 tend to provide an even distribution of voltage over the filament chain.

Removing the Chassis

It is first necessary to remove the batteries and also the clip which secures the mains lead to the right-hand front corner of the battery compartment. Next, the two large knurled-head nuts, located either side of the battery compartment, should be slackened, and the chassis-retaining brackets released. With some models the two metal feet beneath the carrying case also have to be unscrewed before the chassis can be withdrawn.

The chassis can now be taken from the case, but is

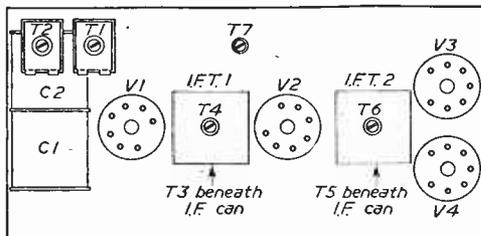


Fig. 2.—Top view of chassis showing trimmer positions.

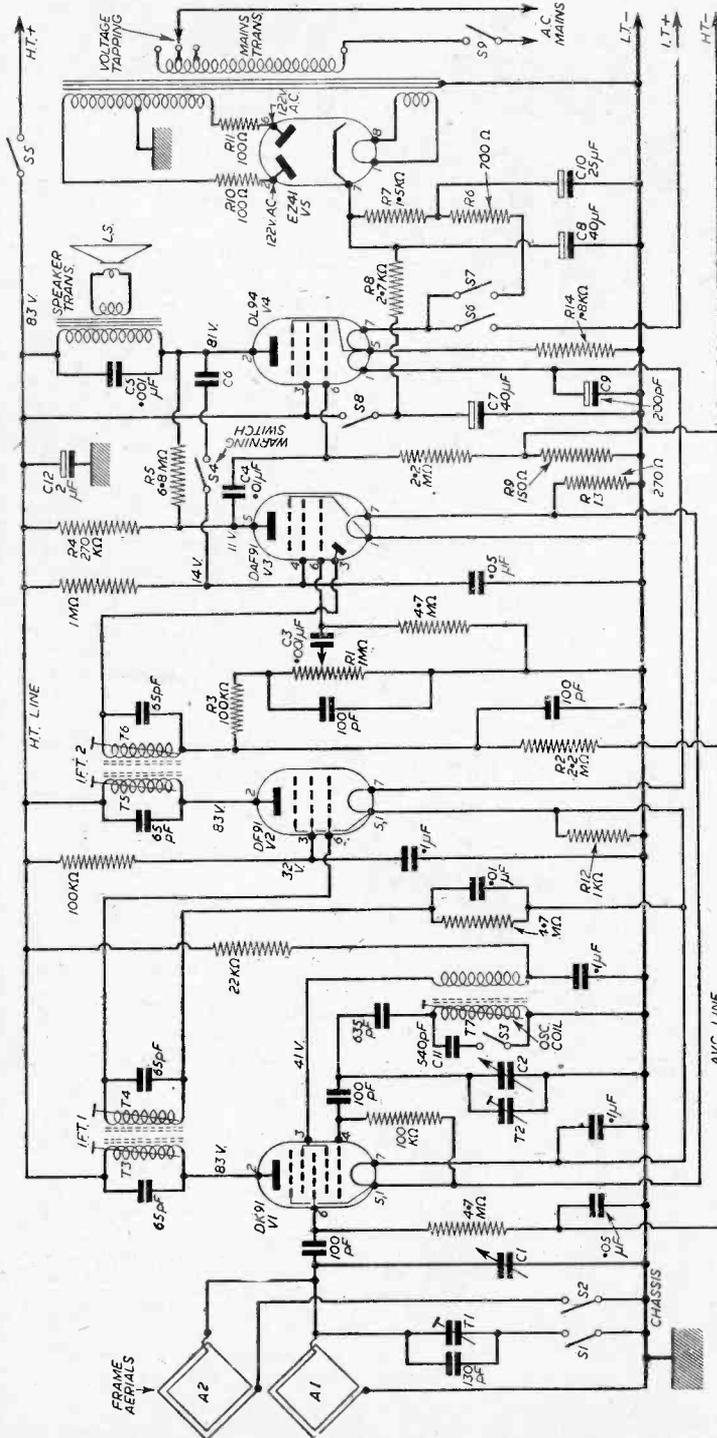


Fig. 1.—Theoretical circuit of the Victor Portable CN396.

limited by reason of the frame aerial connecting cables. Therefore, in order to remove the chassis for detailed examination it is necessary to disconnect the frame aerial. This is best performed by prising out the frame aerial cover in the lid, after first removing the two metal clips, and then unsoldering the three connections inside.

Alignment Data

The I.F. stages should be aligned, or checked, before making trimmer adjustments in the R.F. and oscillator sections. The earthy side of the generator output should be connected to the receiver chassis, and the "live" side to pin 6 of V1 through an 0.1 μ F local capacitor. The local oscillator should be muted by shorting C2, and preferably an output meter should be used to indicate optimum trimmer settings. In order to avoid alignment error as the result of overloading and operation of the a.v.c. system, the smallest possible generator output voltage should be used for all adjustments consistent, of course, with usable deflection in the output meter.

A modulated 456 kc/s signal should be applied and trimmers T6, T5, T4 and T3 should be adjusted in that order for maximum output, reducing the input signal as the circuits approach correct alignment.

Next, the short across C2 should be removed and the signal generator output leads transferred to the region of the frame aerials to provide a degree of coupling without actually making a direct connection. After having ensured that the tuning pointer is operating properly, tune the receiver to 200 metres

(Continued on page 57)

TO BE SURE

GET
THE
RODING
22-circuit
HOME



"If you
want
to
save
time and
money!"



CONSTRUCTOR'S HANDBOOK

Our latest issue is beautifully printed on glossy art paper with a full colour cover! Still packed with technical data, set building and servicing hints, facts and formulae, resistance colour code, soldering hints, etc., together with descriptions, full parts lists and circuits of 22 famous outfits as listed below. Send 2/6 (plus 3d. post).

- *3-valve superhet Feeder Unit.
- *4-valve Feeder unit (R.F. stage), with hi-fl and gram. switching.
- *Amplifier/Power pack for both above.
- *5-valve superhet A.C. (with gram).
- *5-valve superhet A.C./D.C.
- *6-valve superhet A.C. (R.F. stage).
- *6-valve superhet A.C./D.C. (")
- *Simple Continuity Tester.
- *Magic Eye unit.
- *Modified 40 Feeder Unit Circuit.
- *"P.W." Coronet AC4 Superhet.
- *"P.W." Coronet A.C./D.C. 4 Superhet.
- *Tape Recorder
- *3in. Oscilloscope.
- *8-valve Communications Receiver.
- *Signal Tracer.
- *5-watt quality amplifier.
- *10-watt high-fidelity push-pull amplifier.
- *Signal Generator.
- *Crystal Set.
- *Local station high-fidelity T.R.F. feeder unit.

Our famous "Easy-as-A.B.C." FULL SIZE Construction Sheets are available for the above enabling even the beginner to get first-class results at first time! Coil Packs and I.F.T.s pre-aligned. We can supply ALL parts for ALL circuits.

NEVER BEFORE HAS THERE BEEN A BOOK SO VALUABLE TO NOVICE AND EXPERT ALIKE!

RODING LABORATORIES

(Dept. TC5), Bournemouth Airport, Christchurch, Hants

BUILD THIS FOR 49/6



Build this exceptionally sensitive triode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6in. x 5in. x 3in. Covers all Medium and Long waves—uses one only all-dry battery which costs 7s. 9d. and lasts many months, as H.T. consumption is only 1 to 1.5 ma. Ideal for Bedroom, Garden, Holidays, etc. Many unsolicited testimonials. Mr. Norton, of Oxted, writes: *Yesterday evening on the Medium waveband I counted 32 separate stations: I am very pleased with the set, which is well worth the money. Total building cost 49s. 6d., including post, etc., with full set of clear, easy-to-follow plans. (For Headphone Reception.) Cost of Extra Valve, Speaker, Parts, etc. 34s. 6d. All these fit inside. Case or parts sold separately. (Priced Parts List, etc.) Orders despatched by return. Overseas orders welcomed. SEND TO-DAY.*

Note: We stock complete Range of Components and Valves.
CONCORD ELECTRONICS (Dept. PW3),
39, Queens Road, Brighton, 1.

G2AK This Month's Bargains G2AK

ABSORPTION WAVEMETERS.—3.00 to 35.00 Mc/s in 3 switched bands. 3.5, 7, 14, 21 and 28 mc/s Ham bands marked on scale. Complete with indicator bulb. A MUST for any Ham Shack. **ONLY 15/-** each. P. & P. 1/-.

TEST METER.—7 ranges as follows: 1.5 v., 3 v., 150 v. 6 mA., 60 mA., 5,000 ohms, 25,000 ohms 2 1/2 in. dia. scale M.C. meter. Rotary selector switch. Black bakelite case, 6 x 4 1/2 x 4 1/2 fitted with removable lid, also provision for internal batteries, ranges can be easily extended. Bargain price 30/-, plus 1/6 post.

VALVES.—Genuine American, brand new, ex-W.D. stock, boxed 807's, 7/6 each, or 4 for 25/-.

HEADPHONES.—Low resistance type CLR No. 3, 9/6. DLR No. 2, 13/6. High resistance and the most sensitive of all DHR, No. 5B, 18/6 per pair, P. & P. 1/- pair.

FISK SOLARISCOPEs.—Complete with charts. Give World time, light and darkness paths. Invaluable to the DX man. List 21/-, our price 7/6, post free.

PANL Home Crackle.—Black only, 3/- tin. P. & P. 8d.

XTAL HAND MICROPHONES in Silver Hammer Case with polished grille, Handle and 4 ft. Screened lead. 21/-.

SPECIAL OFFER. DEAF AID CRYSTAL MIKE INSERTS. 7/6 ea., or 2 for 12/-.

UNREPEATABLE OFFER

POWER UNITS in Black Metal Case. With input and Output sockets. For 200/260 v. 50 c. Input. Output 200/250 v. 60/80 ma. Fully Smoothed and Fused. Also gives 31 v. 3 A. D.C. and 6.3 v. 3 A. A.C. fitted with 6X5 rectifier. 50/- ea. Carr. Paid.

Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

C. H. YOUNG, G2AK

All callers
110, Dale End,
Birmingham 4 (CEN 1635)

Mail Orders to Dept. "P"
102, Holloway Head,
Birmingham 1 (MID 3254)

HANNEY of BATH offers:—

COMPONENTS FOR F.M.

DENCO 'MAXI-Q' F.M. Feeder Unit. Instructors Manual 1/9. P.F. : Chassis 7/6; Coilset 11/9; ten 7 Mc/s I.F.s 6/- each; Ratio discrim. trans. R.D.T. 12/6. Scale and drive complete for assembly 9/-.

MULLARD F.M. TUNER COILS (Denco). 510/1FF 2/6 each; 510/AE 4/6; 510/REC 2/-; 510 RF 2/6; 510 Osc. 4/6; 510 IFT1 7/6; 510 IFT2 7/6; 510 RDT 12/6; All Chassis punched with all holes. 12/-.

OSRAM F.M. TUNER COMPONENTS (Denco). O T1 2/6; O L1 2/6; O L2 2/6; I.F.s 6/- each; OT2 with crystals 19/6. Chassis complete with printed dial, front panel and drive mechanism 37/6.

OSMOR F.M. COILS. QAFM 7/-; QRFM 5/-; QOFM 7/6; QICD with crystals 25/-; QIFM 7/-.

OSRAM 912 Erie resistor-pot kit with ceramic tube resistors, very highly recommended, 29/6; Lab. resistor kit, 32/4; T.G.C. condensers, 55/-; PARTRIDGE Components, with loose lead terminations, Mains trans., 44/-; Smoothing Choke, 29/6; Output trans., 76/9. Price includes Partridge carriage/packing charge.

W.B. OUTPUT TRANS., 32/-; W.B. smoothing choke, 18/9. DENCO 16 s.w.g. All-chassis, 14/6. Bronze finished printed panel, 6/6; 912 Plus printed front panel, 7/6; 912 Plus pre-amp chassis, 6/-.

MULLARD 5 VALVE 10 WATT AMPLIFIER. T.C.C. Condensers, 45/-; Erie resistor-pot kit, 37/6; Elstone Mains trans., 36/-; Elstone Output trans., 45/- (both types); Denco chassis, 14/6; Printed bronze panel 14in. x 6in., 6/6. Small parts as per our list. Matched valves available for both the above designs.

HIGH FIDELITY SPEAKERS. W.B. HF810, 60/6; W.B. HF912, 87/3; W.B. HF1012 (3, 7.5 and 15 ohm coil), 97/6. C.E.C. type FR metal cone, 28/15/-; Goodmans' Orlin 11L, 29/15/-.

COIL PACKS: DENCO CP 31L and CP 41M, 33/4; CP 3/370 p.f. and CP 3/500 p.f., 42/8. OSMOR "G" HO, 48/-; LM, 40/-; Batt., 50/-; TRF, 40/-; HF stage for HQ pack, 20/-.

We stock COILS by Weymouth, Osmor, Wearite, Denco, R.E.P.

WIDE ANGLE COMPONENTS. ALLEN. Teleging Chassis, 50/-; Coilsets (TK and Super-Visor), 44/6; L.O.308, 40/-; P.O.305, 21/-; D.C.300, 39/6; FC302, 31/-; CL15 and 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OP.117, 9/-; BT.314, 15/-; DENCO Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/6; Coilsets Magnaview, 41/2; WA/DCA1, 43/-; WA/PCA1, 31/-; WA/LCI and WCL, 7/6 each; WA/FMAL, 1/-; WA/LOT1, 42/-; WA/FBT1, 16/-.

BAND 3. Teletron Coilset, 15/- with circuit; Punched chassis 39/9. Send S.A.E. for our General List. Please add 2/- postage to orders under £3 (excess refunded).

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

and the generator to 1,500 kc/s, and adjust T2 for maximum output. Retune the receiver to 550 metres and the generator to 545.45 kc/s and adjust T7 for maximum output whilst "rocking" the receiver tuning slightly.

Finally, tune the receiver to 1,200 metres and the generator to 250 kc/s, and adjust T1 for maximum output.

Servicing Hints

In some districts heterodyne whistles may be experienced on M.W. stations; this can generally be cured by readjusting the I.F. tuning to 470 kc/s. This will, of course, necessitate retrimming the

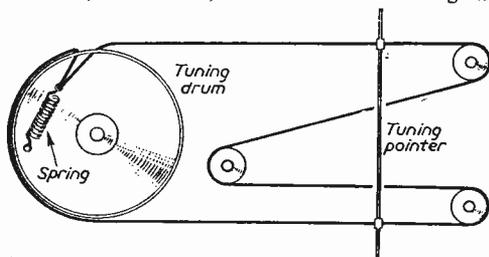


Fig. 3.—Details of the tuning drive arrangement.

receiver, and in some cases it may be found necessary to alter the value of the L.W. shunt capacitor C11 to 515 pF.

Instability accompanied by low volume is often caused by deterioration of the 2 μ F electrolytic capacitor C12—this should be checked on a bridge or by direct substitution.

Low volume and apparent lack of sensitivity, whilst remaining stable, the 65 pF I.F. tuning capacitors should be suspected of low "Q" or alteration in value; conclusive proof in this connection is if the I.F. tuning does not peak properly during the alignment process. If the transformers

tune very flatly and the associated capacitors check normal, the windings themselves should be suspected for low "Q"—replacement is generally demanded in this case.

Low volume is also sometimes caused by V2 screen decoupling capacitor becoming low in value, V3 screen resistor becoming high in value, and R4 becoming high in value.

Excessive distortion is often provoked by C4 developing a very slight D.C. leak—this fault also causes the H.T. battery to run down quicker than normal.

On some specimens of this receiver a disconcerting mains hum at high volume settings with the receivers working from the mains was found to be caused by the close proximity of the mains transformer primary leads to the volume control—re-routing the leads solved the problem.

General fault checking for no signals can be aided by testing whether the warning signal can be produced by closing the lid. If it is not present, stages V3 and V4 should be carefully investigated—one of the valves may be faulty, or it may be found that the H.T. unit or batteries are responsible.

If, on the other hand, the warning signal can be produced, stages V1 and V2 should come under investigation, paying particular attention to V1. This valve often becomes soft and fails to oscillate when the L.T. voltage falls slightly.

General

Fig. 2 shows the top of the chassis and all trimmer positions as viewed from the battery compartment.

A plan of the tuning drive arrangement is shown at Fig. 3; for cord replacement approximately 30in. of nylon drive cord is required. Replacement can be carried out by removing the receiver chassis from the metal panel by extracting the control knobs and three 4 B.A. nuts and bolts. Care should be taken to ascertain that the pointer is reset to the 550 metre mark on the scale when the tuning capacitor is at maximum capacitance.

Hydrogen Thyratrons

By E. G. Bulley

THE hydrogen thyatron falls into the category of gas-filled types, and should not be confused with the conventional inert gas-filled designs such as argon, xenon or helium. They do, however, utilise oxide coated cathodes, and can be classified as grid-controlled gas-filled rectifiers.

The hydrogen thyatron was originally designed for use as a switching valve for pulsing magnetrons necessary in radar. They are, however, to-day, now being used in many fields, such as industrial research, etc., especially where precise triggering is required.

Fast Operation

Hydrogen thyratrons have characteristics which make them preferred to the conventional type, these being their capacity of high peak currents, fast operation, positive grid control and a very wide ambient temperature range without affecting the electrical characteristics. These thyratrons, unlike other types,

can be operated in more or less any position, and are found to operate at high altitudes under stringent conditions of repetition rates and high peak currents. Such operation naturally depends upon the actual design of the valve but, nevertheless, they have the advantage of very short de-ionisation times. This characteristic is the time required to bring about the de-ionisation necessary to regain control, and is dependent upon the anode voltage, grid voltage, temperature and instantaneous anode current. Such a characteristic is a factor which decides the maximum frequency at which these valves will operate.

Advantages

An advantage of these thyratrons is that they will operate without negative bias, thus they prove extremely useful in applications requiring zero bias with positive triggering pulses.

On the larger types of hydrogen thyratrons many designs include an integral gas reservoir, that is to say, they have a hydrogen reservoir incorporated in the valve. This ensures freedom from failure should the gas clean up, the reason being that any gas consumed during the operation of the valve is replaced from the reservoir.

Programme Pointers



HENRY JAMES'S great novel, "The Golden Bowl," made an enthralling play on the "Third." Running, with a short interval, for three and three-quarter hours, it was treated quite spaciouly by the dramatiser, Mary Hope Allen. Largely symbolical, it compared the lives of a father and daughter and her husband and step-mother with a golden bowl that turned out to be only gilt over porcelain, plus a crack. Whilst in existence, affairs seem about to crack, too. But as soon as it is smashed its influence ends and things come out all right.

Packed with James's insight into character and motive, it was sympathetically and knowingly handled by Irene Worth, Peter Wyngarde, Clare Austin, Barbara Couper, John Gabriel, Macdonald Parke and others. Leon Quartermaine compered excellently.

"Put Out More Flags," by Evelyn Waugh, was another famous novel skilfully dramatised, this time by Christopher Sykes. Describing the reactions of various strata of society to the first world war, plus an evacuee scandal, it was amusingly and realistically acted by, amongst others, Mary Wimbush, Roger Snowdon, Felix Felton, Patience Collier, Betty Hardy, Hugh Burden, Joan Hart and Richard Williams.

Sunday Newsreel

"From our Correspondents," on Sunday mornings, whilst interesting, seems little other than a Sunday edition of Radio Newsreel, except for the fact that there is little or no home news in it and plus a vast amount of "calling up" and buzzing wires. Useful, perhaps, for those who cannot be "called up" during the week. Some of the telephoning from the farthest corners of the earth may sound very up-to-the-last-minute and dramatic, but it is sometimes very unclear and trying. Some of them could well be read in the studio.

"Antic Hay"

Aldous Huxley's novel, "Antic Hay," created something of a sensation when it first appeared in the disillusioned twenties. Chiefly concerned with the invention of trousers with pneumatic seats, plus much of the gay and shallow chatter of those days, the story, made into a play by Lance Sieveking for the Monday evening "Between Two Worlds" series, seemed to have dated and aged considerably: much more so than many of Wells's and Bennett's, which go back a decade or two earlier. A huge cast contained many well known names.

At the other end, one wonders how either "The Great Gatsby" or "From Morn to Midnight" found their way into this admirable series.

The Goons

"The Goon Show" remains the noisest, and "Take It From Here" the wittiest, of all the regular

Our Critic, Maurice
Reeve, Reviews Some
Recent Programmes

weekly features. When listening to the former, we seem to pass through a London Underground railway, a Clyde shipyard, the Elephant and Castle in the heyday of the tram, and heaven knows what else. I admit there are some laughs as well. But Denis Norden and Frank Muir remain the best comedy script writers, and whilst I, personally, get a little tired of the sameness of some members of the cast—as I do with all these shows—they are a pretty good team for getting the wit and sparkle of the thing over. There is plenty of this.

The "Third"

The "Third" regaled us with Wycherley's uproarious, promiscuous, libidinous and generally disreputable but very true to life comedy, "The Country Wife." It was great fun. What a time those Restoration folks must have had of it! For there is no doubt that, in his much smaller way and lacking Shakespeare's genius, Wycherley faithfully recorded the life of his times, just as W. S. did. Much the same caperings go on nowadays, but we seem to prefer space-ships and gangsters in our entertainment.

Politics

It has become a practice to engage an M.P. from each of the greater parties to "observe" the party conference and then "discuss" it for half an hour each evening while it is in progress. This year the two M.P.s were Mr. Enoch Powell for the Tories and Mr. Wedgwood Benn for the Socialists. Both give the impression of "agreeing to differ" for entertainment purposes; "but my dear Benn" follows "but my dear Powell" in regular sequence, with an occasional agreement that lends sincerity to the party divisions. All rather artificial and stagey. I wonder what the size of its listening panel is?

Space Travel

"Journey Into Space," in no fewer than twenty episodes, is one of those speculative, empirical things that Wells and Jules Verne so excelled in 50 or more years ago. But is the present spate of this sort of thing likely to appeal to such a wide range of ages as they did? Will the youth of to-day witness the same high proportion of correct forecast and assumption in 50 years' time as the youth of their day is now doing? "Increase your speed three thousand miles," "No. 6 ship be prepared to leave for Mars immediately" as well as "All change for Clapham Junction," show the wide range of both drama and cliché employed. One or two of the episodes made me feel all the more eager for "The Woodlanders" on Sunday evenings!



We cannot show the complete contents on these pages, but we give a brief summary and some examples. COMPLETE DETAILS OF: AN ILLUSTRATION and DESCRIPTION IS GIVEN OF EACH ITEM.


- **AMPLIFIERS.** By Armstrong, Goodsell (Williamson), Leak, W.B., THE MULLARD 5-10 (Grampian), Stern's Kits of Parts for a High Quality 8-10 watt and a High Fidelity 12-watt Amplifier having separate Pre-amplifier/Tone Control Unit.
- **A CHOICE OF 9 RECORD PLAYERS.** 3-SPEED AUTOCHANGERS—NON-AUTOCHANGERS and TRANSCRIPTION PLAYERS. By COLLARO, GARRARD and B.S.R.
- **Replacement RADIO-RADIOGRAM CHASSIS.** Only dependable and good quality Chassis are stocked.
- **RADIO TUNING UNITS.** FM and AM Models. By STERN'S, GOODSSELL, ARMSTRONG, CHAPMAN, DULCI and the DENCO or JASON designs for the HOME CONSTRUCTOR.
- **LOUDSPEAKERS.** Full data of the very popular W.B. "STENTORIAN" Speakers. The WHARFEDALE range, various GOODMAN'S Speakers and a selection of well-known makes at REDUCED PRICES.
- **LOUDSPEAKER SYSTEMS.** Suggested arrangements for the "Hi-Fi" enthusiast.
- **PREFABRICATED CABINETS.** THE CONSOLE CABINET and two types of BASE REFLEX SPEAKER CABINETS.
- **BAND I—BAND III TV CONVERTERS.** By AERIALITE, DULCI, VALRADIO.
- **AERIALS.** A complete range of Band I and Band II(FM), Band III Aerials, Indoor and Outdoor types.

... AND OTHER INTERESTING ITEMS!

MODERNISE YOUR OLD RADIOGRAM


HERE ARE TWO EXCELLENT BARGAINS AT

£12/19/6 each

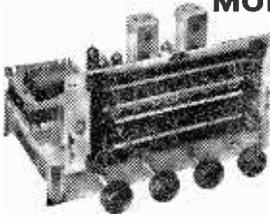

The Model AW3-7. A 7-valve 3-waveband design having a "Push-Full" stage to provide approx. 7-watts output. H.P. Terms: £4/6/6 Deposit and 10 monthly payments of 19/4.

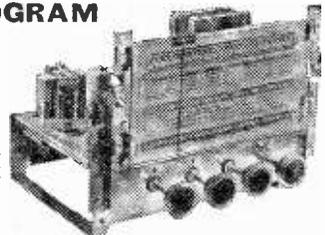The Model B3PP. A 6-valve 3-waveband Superhet with "Push-Full" stage for approx. 6-watts output.




The DULCI FM TUNER

A self-contained Tuning Unit providing complete FM coverage. Performance is really outstanding and is equal to many Units offered at far higher prices.

PRICE £16/16/0

(plus 7/6 carr. and ins.)

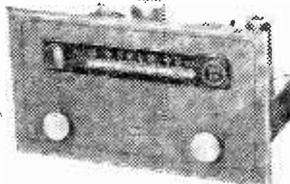

H.P. TERMS: Deposit £5 12/8 and 12 monthly payments of £1/0/5.

AN EXCEPTIONAL OFFER FOR CASH ONLY

The B.S.R. "MONARCH" 3SPEED AUTOCHANGER
NORMAL PRICE £13/10/-

£7/19/6

Plus 7/6 carr. and ins.)

- Complete with High Fidelity Crystal Turn-over Head which incorporates separate stylus for L.P. and 78 r.p.m. records. ● A "MIXER" Unit that will auto-change on 7in., 10in. and 12in. records.
- Brand New in Maker's Cartons, complete with mounting instructions.



STERN RADIO LTD. 109 & 115 FLEET ST., E.C.4.

Telephone
FL eel 5812/3/1

YOU can become a First Class RADIO ENGINEER

We can train you to earn good money in your spare-time, start a radio business of your own or qualify for well-paid employment. Our Home-Study Courses in Radio, Television and Mathematics are up-to-date and easy to understand. The fees are very reasonable and can be paid by instalments.

T/C RADIO COLLEGE ESTABLISHED IN 1933

Send for free details, which will be sent in plain sealed package. Simply write your name and address inside the flap of an unsealed envelope (postage 1½d.) or on a postcard (postage 2d.) and address it to the Principal:—

R. HEATH BRADLEY,
DUART HOUSE, ASHLEY ROAD,
NEW MILTON, HANTS.

FREE CATALOGUE

New, guaranteed complete by the leading makers. 58 pages illustrated on fine art paper. Over 2,000 items listed with over 100 photographic illustrations. Special features for service work. Orders dealt with day received.

SOUTHERN RADIO & ELECTRICAL SUPPLIES SORAD WORKS, REDLYNCH SALISBURY

Telephone: Downton 207

CUT OUT THE CRACKLE

Use Metal Screened Twin Flex—6ft. lengths' tagged ends, 2/6 each. Twin Braided Flexible leads—6ft. lengths, tagged, 1/- each. Single Braided Flexible leads—2ft. lengths, tagged, 6d. each. Instrument Copper Wire—finned .025 P.V.C. Insulated. Various colours, 6d. per yard. Coil Winding enamel wires 35, 36, 37, 39, 39 S.W.G.—any quantity, C.P.

S.A.E. for further particulars.
"ONLY" COMPONENTS LTD.
Llanerch-y-Mor, Holywell, Flintshire

THE WAVE SPECIALISTS

Bentley Acoustic Corp. Ltd.

38, CHALCOT ROAD, N.W.1.

Primrose 9090

1st grade goods only. No seconds or rejects.

024	6/-	6Z4/84	8/6	AP4	7/6	KK32	10/6
1A5	6/-	6Z5	12/6	ATP4	3/-	KL35	9/-
1C5	11/-	7AN7	11/-	AZ31	10/6	KT2	5/-
1D3	10/6	7AT	8/6	B309	9/-	KT44	7/-
1E7	9/6	7B4	7/6	B319	11/-	KTW61	7/-
1G6	6/6	7C5	8/-	BL63	7/6	KTW62	5/6
1H5	11/-	7C6	8/-	CK505	6/6	KTZ63	6/6
1L4	6/-	7D5	10/6	CK523	6/6	L63	6/-
1LD5	5/-	7D8	6/-	CK525	6/6	LN152	10/6
1LN5	5/-	7H7	7/6	CK538	12/6	LP2	6/6
1N5	11/-	7Q7	8/-	DI	7/6	ML4	6/6
1R5	7/-	7R7	8/6	D77	6/-	MU12	8/6
1T4	7/-	7V7	8/6	DA90	8/6	N78	11/6
2C26	4/-	7Y4	8/6	DA32	11/-	N150	10/6
2D21	8/6	818	2/6	DAF91	7/-	OC3	9/-
2X2	4/6	81D3	6/6	DC90	10/-	PC153	12/6
3A4	7/6	10C2	10/6	DP33	11/-	OM6	7/6
3A5	10/-	10D1	4/6	DP91	7/-	PC084	11/-
3B7	8/6	10F1	10/-	DF92	6/-	PCF80	11/-
3D6	2/6	10LD3	8/-	DH77	8/-	PCF82	12/6
3E9	9/6	10P15	10/6	DK96	8/6	PCN25	6/6
3H4	7/-	12ASGT	10/6	DK96	8/6	PCN25	6/6
3V4	7/-	12AH7	12/6	DL2	15/-	Pen46	7/-
5U4	8/-	12AT7	8/-	DL35	11/-	Pen383	15/-
5Y4	10/-	12AU7	8/-	DL72	7/-	PL81	10/-
6B2	10/6	12AX7	8/6	DL85	7/6	PL82	9/6
5Y3	7/6	12BE6	6/6	DL810	10/6	PL82	9/6
5Y4	10/-	12BH7	12/6	E1148	2/-	PM12	4/6
5Z4	3/6	12E1	30/-	EA50	2/-	PM12M	6/6
6A3	10/6	12H6	3/-	EA76	9/6	PY25	7/6
6B56	12/6	12I5	6/-	EABC80	9/6	PY80	8/6
6AB5	10/-	12NC7	7/6	EBC3	10/6	PY81	10/6
6AC7	6/6	12NSG7	5/6	EB31	2/-	PY92	7/6
6AG5	6/6	12NSJ7	8/-	EB41	10/6	PY83	10/6
6AL5	6/-	12NK7	6/-	EB91	6/-	QP21	7/6
6AM6	6/6	12NQ7	8/6	EBC3	12/6	QP22B	12/6
6B76	8/6	12NR7	7/6	EBC41	6/6	QF25	6/6
6B4	6/-	13VPA	8/6	EBC41	10/6	Q30070	10/6
6BA6	7/6	14R7	10/6	EFB80	10/-		
6B8G	4/-	19H1	10/-	EC52	5/6	Q150/15	
6BRM	4/6	20L1	10/-	EC54	6/-		10/6
6B56	6/6	20P3	11/6	EC70	12/6	QV047	9/6
6B16	6/6	20P4	12/-	EC92	10/6	RK34	8/6
6BW6	7/6	25A6	10/-	ECC33	8/6	S180	8/6
6BW7	10/-	25L6	8/6	ECC35	8/6	SD6	7/6
6BX6	10/6	25Z4	8/6	ECC81	9/-	SP4(7)	8/6
6C6	6/6	25Z5	8/6	ECC82	10/6	SP41	3/6
6C8	8/6	30	7/6	ECC82	10/6	SP61	3/6
6CH6	6/6	30C1	11/-	ECC84	12/6	T1D2A	8/6
6E6G	7/6	30L1	11/-	ECC85	10/-	TH233	10/6
6P6GT	8/-	35L6	8/-	ECC91	6/6	TP22	9/6
6F1	12/6	35Z4	8/6	EOH42	10/-	TZ40	35/-
6F2	7/6	35Z5	8/6	EOH42	10/-	N16	12/6
6F12	6/6	38	8/6	EL42	10/-	U17	7/6
6F13	12/6	45Z5	12/6	EP35	4/6	U19	9/6
6F17	9/6	50C5	10/-	EP37A	10/6	U25	12/-
6F32	6/-	50L6	8/6	EF39	6/6	U31	8/6
6F33	9/6	50Y6	8/6	EP41	9/6	U30	7/6
6G6	6/6	61BT	12/6	EP42	10/6	U32	8/6
6H6M	3/6	61SP7	15/-	EP50(A)	8/-	U78	7/6
6J50	5/-	62TH	10/-	EP50(B)	5/-	U50	9/6
6J56T	5/6	72	6/6	EF54	5/-	U53	10/6
6J6	9/6	76	7/-	EF73	10/6	UBC41	9/6
6J7G	5/-	77	8/-	EF80	10/-	UCH42	9/6
6K6	7/-	78	8/6	EF85	10/-	UF41	8/6
6K7G	5/-	80	8/6	EF86	12/6	UF42	13/-
6K7M	6/-	83	8/6	EP91	6/6	U09	9/6
6K8G	8/-	85A2	10/6	EL32	6/6	UY41	9/-
6K8GT	8/6	80A3	30/6	EL41	10/6	VS492A	2
6L5	7/6	150B2	12/6	EL42	13/-		
6LD3	10/-	201A8	10/-	EL81	11/-	V88	23
6N7G	7/6	210LF	3/-	EL91	6/6	VMP4	10/6
6N7M	8/-	301	10/-	EM34	10/-	VP2B	10/6
6N7	9/6	307	7/6	EX31	11/6	VP27	8/6
6N8GT	9/6	308	25/-	EX47	12/-	VP47	8/6
6R7	8/6	613	7/6	EY91	7/6	VP13K	6/6
6SA7	8/-	866A	15/-	EZ40	9/6	VP41	7/6
6SF5	10/6	883	10/6	EZ41	9/-	VP133	10/6
6R47	9/6	956	3/6	EZ80	9/-	VR53	6/-
6SH7	6/-	1203	7/6	H30	5/-	VT01	6/-
6S8T	8/-	1229	7/-	H32	11/-	W40	4/-
6SK7	8/-	2101	10/-	HL13C	7/6	X66	7/6
6SL7	8/-	4022AR	5/-	HL23DD	X150	10/-	
6RN7	8/6	4033	12/6		6/6	XFW10	6/6
6SS7	7/6	3763	9/6	HL41	7/6	XFX10	8/6
6UGX	7/6	7193	2/6	HL41DD	XFX12	6/6	
6U7	8/6	9002	5/6		12/6	XH(7.5)	4/-
6V6G	7/6	9003	5/6	HL133DD	XHG1.5	4/-	
6V6GT	7/6	9006	7/6		12/6	YG3	7/6
6X4	7/6	ACP4	8/-	HVR2A	7/6	YG5	10/6
6X5	6/6	ACVP1C	8/6	KK32	6/6	Z77	6/6
6Y7	15/-		10/6	KP31	9/-	Z719	10/6

CRYSTAL DIODES.—0171, GEX31, CG6E, M1, CG10E, all 7/- each.

All boxed and guaranteed. Post 6d. each. Same day service. Shop hours 8.30 to 5.30, Sat. 1 p.m. Why not phone or wire that urgent order for immediate despatch C.O.D.? Complete list free S.A.E.

RADIO SCIRING

Pocket Book 10/6 Post 6d.

By MOLLOY and HAWKER

This NEW book provides essential information and data needed in the work of repairing and servicing modern receivers, including a special section on V.H.F./F.M. receivers.

TELECOMMUNICATIONS PRINCIPLES AND PRACTICE. By W.T. Perkins. 21s.0d. Postage 6d.

ELECTRONIC AND RADIO ENGINEERING. By F. E. Terman. £3 11s. 6d. Postage free.

TELEVISION ENGINEERS' POCKET BOOK. By E. Molloy and J. P. Hawker. 10s. 6d. Postage 4d.

SECOND THOUGHTS ON RADIO THEORY. By "Cathode Ray," of "Wireless World." 25s. 0d. Postage 8d.

ELECTRONIC MUSICAL INSTRUMENTS. By R. H. Dolf. 55s. 0d. Postage 1s.

RADIO VALVE DATA. By "Wireless World." 3s. 6d. Postage 3d.

The MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books. Please write or call for our new 1956 catalogue.

19-23, PRAED ST., LONDON, W.2

Phone: PADdington 4185.
Open 6 days 9-6 p.m.

BENSON'S BETTER BARGAINS

R.F. UNITS. TYPES 26 or 27, 27/6; (Postage 2/6); RF24, RF25. Soiled, 10/8, RX161. 150/220 mc/s with 2V1R136, 1V1R137, 1V1C96, 12/6; L.F. PAMPLER, 17/8 (for this) 16.5 mc/s, with valves 22/6 (post 2/- each). R1155 Coil-packs, new, 12/6. AERIAL RELAYS (co-axial) e/o 12/24 v., 7/8. DYNA-MOTORS, D.C. 12 v. input, 250 v. 60 mA. and 6.3 v. outputs, P.M. held, 7/8; 6 v. 2 to 250 v. 80 mA. 10/- (Post 2/- each). Filters for these, 2/6. CLOCKWORK (contactors) 2 im-pulses per sec., 8/6. USA type, small, 9/6. R1355, new improved type, 37/8 (carr. 7/6). R1392A 100/150 mc/s, 13 valves, used, good cond., 24/10/- (carr. 10/-). VIBRAPACKS P.C.R. D.C. 12 v. to 250 v. 80 mA. smooth, filtered, 17/6 (carr. 7/-). RT-34/APS-13. Brand new. Black crackle case. Valves: 5/6/8, 8/6/AG5, 1V1R105. 30 m/cs. min. I.F.T.s. (carr. 9/-). Throat mics. U.S.A. new 2/6. GOLDENBERG, electrolytic: 13 samples, range 4 mfd. to 1,000 mfd., 7/8 (post 2/-). Bak. tubular, 0.11/2 kV; /5800 v. 2; 25/800 v., 8d. each; /032.5 kV; /057.35 kV; /23.15 kV; /11. kV. each. 1/23.5 kV, 3/6; 1/13.5 kV, 4/6. USA Bathing, 500 v., 2 mfd., 1/6; single, 1 or 25, 8d.; double, 1 or 25, 1/6; 1 mfd., 1/3; treble, 1, 1/6. SLD, new condition, with valves, 30/- (carr. 9/6). TRANS-FORMERS 500-6-500 v. 350 mA., 40/- (carr. 7/6). RESPONSE RFL. New, 160/220 mc/s. 12 valves, 25/- (carr. 7/6) or 7/6 9391, 9 valves, good condition, less DF valves; with im-proved drive, 99/6 (carr. 10/-). R1355 I.F. strips, new, complete, 25/-; less valves, 12/6 (post 2/6).

List and enquiries, S.A.E. please! Terms: C.W.O. Postage extra. Immediate despatch.

Callers and Post: W. A. BENSON (PW) 303 Bathhouse Rd., Liverpool 13.

Callers: S U P E R A D I O (W) chaps! LTD., 116 Whitechapel, Liver-pool 1. ROY 1180.

Experiences with Vibrator Supplies

THE writer, who travels around the country with a trailer-caravan, has to depend upon current supply from his car battery for all-wave listening on a five-valve superhet. The problem is slightly different from that of a car radio, however, because the "generating noise" in a car is not noticed, being drowned by the engine. Moreover, the short-wave bands are not normally used in car radio, whereas the caravan radio has to have a silent background from 13 to 2,000 meters, and it is surprising how difficult this is to achieve.

This quest has resulted in an extensive survey of methods of transforming 12 volts D.C. into 200 A.C. in a reasonable quantity of milliamps.

It was found that a dynamotor provided the least difficult current to smooth, but owing to the need to leave enough current in the battery to start the car on a frosty morning, this proved to take too much current, in the region of 4 to 5 milliamps. Besides, a dynamotor makes a considerable amount of aural noise, and although it could be mounted outside, that would call for a long H.T. lead, and also detract from portability of the radio, which is a desirable feature at times.

Noise

A number of commercial and surplus vibrator units were tried and others built from scratch. All tended to create "hash" on some part of the band, until by trial and error with the judicious addition of H.F. chokes and condensers, the hash was hushed! Synchronous vibrators were found to be inefficient and harder to silence.

Even a truly sumptuous vibrator unit gave trouble. It has two H.F. chokes (high current) in the L.T. lead, and two smoothing chokes in the H.T. plus, from the "bridge" of metal rectifiers. Presumably, it was designed for a P.A. amplifier, where perhaps R.F. interference would not matter, for it gives an output of 300 volts at 100 milliamps. As can be seen from the circuit, only 8 μ F condensers are used for smoothing, and despite the chokes, it is found that condensers around 20 μ F are better.

Designers appear to think unidirectionally, that is, from L.T. to H.T. whereas H.F. interference tends to go the other way and gets into the receiver along the L.T. leads and the battery. Therefore, it found an immense improvement to insert at least 100 μ F across the input of the unit, as indicated by the dotted lines. It is also noticed that the A.V.C. circuits of receivers can pick up the "hash," and they should be well by-passed by large enough condensers.

It is not necessary, however, for such an ambitious unit to be used for normal reception, particularly if L.T. current must be kept down, for even a unit giving 200 v. at 50 mA consumes about 2½ amps at 12 v. For the same reason, metal rectifiers are preferred, in order to dispense with the heater current of a valve rectifier.

Chokes

Although one does not need more than one high current H.F. choke and one L.F. smoothing choke, an all-wave H.F. choke in the H.T. lead in front of the smoothing choke, by-passed with two .001 μ F condensers, is found very effective.


It is possible to obtain smooth enough H.T. to feed a battery-receiver from a 2 v. vibrator unit. But it must be remembered that grid bias in the receiver is usually taken by a dropping resistor between the H.T. minus terminal and the L.T. lead which is connected to the chassis. Therefore, the H.T. minus of the rectifier circuit must not be connected to the vibrator unit chassis, as is customary when used with indirectly-heated valves, so it must be brought to a separate terminal.

Hum

In conclusion it must be said that the low-frequency hum generated by a vibrator, is easily smoothed, but the H.F. content, set up by the minute arcing of the vibrator contact points, is the main problem. Incidentally, it would be a boon if some inventor could design a means of providing A.C. from low D.C. voltages that consumed very much less current than at present possible. Perhaps some reader who has experimented in this connection could let other readers have the benefit of his experiences.

A READER DESCRIBES THE RESULTS OF HIS EXPERIMENTS WITH MOBILE POWER SUPPLIES OBTAINED FROM VIBRATORS

By F. Neville Hart

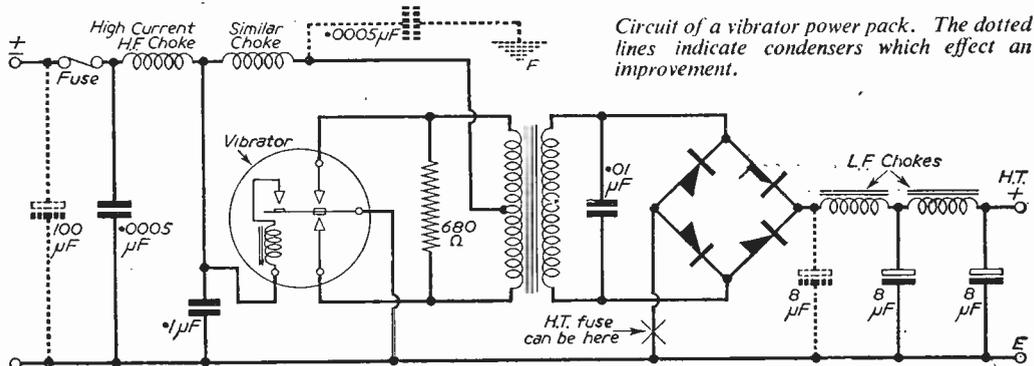

Circuit of a vibrator power pack. The dotted lines indicate condensers which effect an improvement.

BBC Audience Research

IN the tables below the July/September quarter, 1955, is compared with the corresponding quarter of 1954.

Sound

Table I.—Average level of evening (6-11 p.m.) listening among the whole adult population of the United Kingdom (approximately 37,600,000 persons).

	% of the adult population
July/September, 1955	11.6
July/September, 1954	13.6

Table II.—Average level of evening (6-11 p.m.) listening among the sound public.

	% of the "sound public"
July/September, 1955	15.7
July/September, 1954	17.3

It is estimated that the average size of the adult "sound public," i.e., those who live in homes where there is a sound, but not a television, receiver, in the July/September quarter of 1955 was approximately 23,500,000 and in the same quarter of 1954 was 26,000,000.

The level of evening listening during the period 6 p.m. to 11 p.m. was substantially lower in July/September, 1955, than in the corresponding quarter of 1954. Whereas on the average 13.6 per cent. of the adult population were listening at any given moment last year, this year the corresponding figure

was 11.6 per cent. (see Table I). This decrease was partly due to a further flow of listeners to television, but there can be little doubt that the good weather this year also reduced listening. That the diversion of listeners to television was not the only cause can be seen from Table II, which shows that there was appreciably less listening in July/September of this year even amongst people who do not possess television sets.

All Services

Table III.—Average levels of listening and viewing among the whole adult population during those evening hours when all BBC Services are on the air.

	Sound Television Total		
	%	%	%
July/September, 1955	10.3	11.2	21.5
July/September, 1954	12.3	10.5	22.8

During the evening hours of July/September this year, when TV was being broadcast, 11.2 per cent. of the adult population were, on the average, viewing and 10.3 per cent. were listening to either the Home, Light or Third Programme (see Table III). This means that rather more than a fifth of the population were either listening or viewing—48 per cent. of them listening and 52 per cent. viewing. In July/September last year the total number listening or viewing was somewhat greater, but of them, 54 per cent. were listening and 46 per cent. viewing.

News from the Clubs

SOUTH MANCHESTER RADIO CLUB (G3FVA)

Hon. Sec.* M. Barnsley (G3HZM), 17, Score Street, Bradford, Manchester, 11.

AT the Annual General Meeting all the officials were re-elected, i.e., Mr. N. Potter (G3GNC), chairman; Mr. M. Denny (G6DN), vice-chairman; Mr. N. Ashton (G3DQU), treasurer; M. Barnsley (G3HZM) as secretary.

The future programme will be as follows:

December 16th.—Junk Sale and Rag Chew.

December 30th.—Open Evening.

January 13th.—"Hints on Soldering," "How to Solder Aluminium."

SWINDON AMATEUR RADIO CLUB

Hon. Sec. : G. R. Pearce (G3AYL), 102, Kingshill Road, Swindon, Wilts.

A VERY successful first meeting was held and it has been decided to hold monthly meetings.

Weekly classes of instruction for the amateur radio licence examination are being held at the College, Swindon, with Mr. G. R. Pearce as instructor.

Dec. 9th.—Film evening. Showing of Mullard valve films and R.S.G.B. films.

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec. : C. H. Bullivant (G3DIC), 25, St. Fillans Road, Catford, S.E.6.

MR. R. J. SLAUGHTER of the Telegraph Construction and Maintenance Co., Ltd., came to the clubrooms in October to talk to members on radio frequency cables.

Programme for December :

9th and 23rd.—Constructional Evening and Rag Chew

16th.—Christmas Party.

30th.—Junk Sale

Meetings are held every Friday at 7.30 p.m. at the clubrooms, 225, New Cross Road, London, S.E.14. Details of membership can be obtained upon application to the hon. secretary.

STOKE-ON-TRENT AMATEUR RADIO SOCIETY

Sec. : A. Rowley (G3JWZ), 37, Leveson Road, Hanford, Stoke-on-Trent.

MEETINGS continue on Thursday nights at 7.30 p.m. Members are eagerly awaiting the day when the club's new TX goes on the air.

Morse lessons are given on Thursday nights to those interested from 7 to 7.30 p.m.

Future lectures include : Oscilloscopes, Amplifiers, Transistors and an Electronic Key.

WARRINGTON AND DISTRICT RADIO SOCIETY (G3CKR)

Hon. Sec. : J. Williams, 22, Ackers Lane, Stockton Heath, Warrington.

A SEPTEMBER D.F. contest was won by the club's youngest member Roger Dykis. Meetings are held 1st and 3rd Thursdays, Kings Head Hotel, at 7.30 p.m.

A winter programme of films and lectures is being arranged.

LOTHIANS RADIO SOCIETY

Hon. Sec. & Treasurer : John Good (GM3EWL), 24, Mansion-house Road, Edinburgh, 9.

RECENT lectures included "Building a Transmitter," "70 CM DX peditions to Drumore" and "Model Control."

Morse classes are now being arranged for beginners.

Meetings are held at 7.30 p.m. at 25, Charlotte Square, Edinburgh. Visitors and new members welcomed.

EAST KENT RADIO SOCIETY

Hon. Sec. : D. Williams, "Llandogo" Bridge, Canterbury, Kent.

THE East Kent Radio Society still meets at The Two Brothers, Northgate Street, Canterbury, fortnightly at 8 p.m. Films, lectures, sales, swap nights, etc. New members welcome and visitors in the district.


PLYMOUTH RADIO CLUB

Hon. Sec. : Cyril Teale (G3JYB), 3, Berrow Park Road, Peverell, Plymouth.

THE club meets, each 3rd Saturday in the month at 7.30 p.m. at the Tothill Community Centre, St. Judes, Plymouth (17th Dec.).

Newcomers welcome for a rag chew—nothing special laid on for the winter.

LASKY'S PAGE OF MONEY-SAVING OFFERS

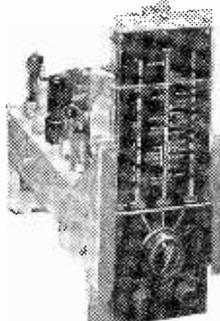

PORTABLE GRAM. AMPLIFIER
 Uses 3 latest min. valves, U78, N78, DH77. Vol., bass and treble controls, ext. L.S. socket and internal L.S. switch. Indicator lamp mounted on wood baffle, size 14 x 4 1/2 in., speaker centralised. All top quality new components. For A.C. mains 200-250 v. Ideal for portable record players, input will match Monarch, RC54, RC3554, etc. Price, complete with 3 new Osram valves, 7 x 4 in. Goodman's elliptical Speaker, mains lead and knobs. **£5/9/6**
 Post and packing, 5/-

ACOS CRYSTAL CARTRIDGES, complete with styli GP29. List 42/11. **LASKY'S PRICE 18/6**. Post 1/-.

LATEST COLLARO RC54 3-speed High Fidelity Mixer Changer. Studio O crystal turnover p.u. **LASKY'S PRICE 59/19/6**. Carr. 3/6. Also supplied with Studio P crystal p.u. 15/- extra.

PLATED MICROPHONE FLOOR STANDS, telescopic, folding base, height 3ft. x 5ft. 3in. **LASKY'S PRICE 32/6**. Post 3/6.

ALUMINIUM CHASSIS, 18 S.W.G., undrilled, 4 sides, reinforced corners, Depth 2 1/2 in. 6x4 4 - 12x8 7/- 16x10 8/3 8x6 14x9 7/6 12x3 4/9 10x7 9/- 16x9 8/- 12x6 6/6 Post 1/- per chassis extra.



SPECIAL OFFER OF TAPE DECK CASES. Will take Truvox Desk with space for amplifier, feeder unit and speaker. Overall size, lid closed, 19in. x 14in. x 13in. **LASKY'S PRICE 35/-**. Carr. 5/-.

TRUVOX TAPE DECK, latest Mk. III U, press-button control. **£23/2/0**.

COMBINED OFFER. Above Tape Deck Case together with Truvox Tape Deck, **£24/10/0**. Carr. paid.

6 VALVE RADIOGRAM CHASSIS COMPLETE WITH VALVES

Famous Manufacturer's Surplus. 6 valve 3-wave Superhet. 13-50 m. short. 200-550 m. medium. 1,000-2,000 m. long. Brand new Mullard valves: ECH42, EF41, L63, EB41, 6V6 g.t., E240 and finest quality components. Gram switch, 465 Kc s.f., tone control, three-colour dial. Overall size: 13 1/2 x 5 1/2 in., 1 1/2 high 12 1/2 in. Aperture required for dial and controls 11 x 3 1/2 in. Complete with valves, output trans., knobs, etc. **£10/19/6**
LASKY'S PRICE
 Carriage and packing 7/6 extra.

B.S.R. MONARCH 3-SPEED AUTO-CHANGERS

LATEST 1955 MODEL NEW AND UNUSED. Takes 10 records of all sizes (mixed) in one loading. HGP.37 crystal turnover pick-up. Handspine cream or light beige finish. Supplied complete in maker's carton. **LASKY'S PRICE £7/19/6**
 Post 3/6

★ **CABINET** to take above Radiogram Chassis and Auto-Changer, attractive design, oak veneer, **£9/15/-**. Carriage 17/6.

LASKY'S RADIO CONSTRUCTOR PARCELS

PARCEL No. 1
 Contains everything to build a 4-valve, 3-wave superhet for 200/250 A.C. mains. Uses 6K8, 6K7, 6Q7, 6V6 valves. Attractive wood cabinet, walnut veneer, or plastic cabinet. Size 12 x 6 1/2 x 5 1/2 in. deep. **CAN BE BUILT FOR £7/19/6**. Carr. and pkg. 2/6.

PARCEL No. 2
 Contains everything to build a T.R.F. 3-valve set for 200/250 A.C. mains, med. and long wave. Uses 6K7G, 6J7, 6V6, and metal rectifiers. Neat plastic cabinet, walnut or ivory finish, or wood cabinet. Size 12 x 6 1/2 x 5 1/2 in. deep. **CAN BE BUILT FOR £5/10/-**. Carr. and pkg. 2/6.

PARCEL No. 3
4-WATT A.C. AMPLIFIER.—Uses 1 each 6SL7, 6V6 and 5Z4. All components, chassis, valves, output trans., mains trans. **LASKY'S PRICE, 4/5/-**. Post & pkg. 2/6 extra. Instruction Book, 1/- post free.

F.M. UNITS & COMPONENTS

DENCO F.M. Feeder Unit. Complete parcel including valves, 66 7/6, Post extra. Data Book, 1/6, post free. All components and valves available separately.
JASON F.M. Tuner. Special parcel containing chassis, data book, complete set of coils, tuning condenser, dial drive, front plate & knob, 68 9. Post 2/6.
 This Tuner can be built for **£6/15/0** plus 2/6 post. Book only, with our fully itemised list, 2/- post free. Full range of **GORLER (Continental) F.M. Components**.
DULCE F.M. Tuner, incorporates its own power supply and provides complete F.M. coverage. Operates with most makes of radio receivers and any make of amplifier. **Price 16/6s.** Carriage and packing, 7/6.

BAND III CONVERSION FOR ALL!



CYLDON TURRET "TELETUNER"

OFFERED FOR THE FIRST TIME

Previously supplied to Set manufacturers only.

This 12 channel Tuner consists of a turret having 12 clip-in aerial and mixer coil strips.

When turret is rotated the appropriate strip locates on a contact panel providing the necessary connections Bands I and II London and Birmingham, BBC and ITA. (4 Sets of Coils.)

This type of tuner enables you to clip in pre-aligned coils for the reception of any station not already provided for in Bands I, II and III, while affording maximum gain, high stability and minimum noise, which are essential in a modern tuner. I.F. output 33-38 Mc/s. Easily modified to other I.F. outputs.

Valves used: PCC84, R.F. double triode, cascode R.F. amplifier, PCF80 triode pentode f.c. and mixer. Will work with most sets. Full instructions and circuit diagram supplied. Price **99/6**
 Post 2/6. Knob, 3/6 extra.

TELETRON BAND III CONVERTER COIL SET for use with TRF and superhet Band I receivers. Uses 2 7/19. Circuit, wiring diagram, alignments with each set. **15/-**. Post 1/6.

Mk. II COIL SET, cascode, 17/6.

TELETRON BAND III CONVERTER. Complete kit, drilled chassis, condensers, resistances, coils, valves, etc., with full instructions. **48/6**
 Post 1/6.

Drilled Chassis only, 3/9. All components available separately.

12-CHANNEL TV TUNER

Famous make. Covers Bands I and III. Complete with valves EF80 and EC81. Ceramic valveholders, finest quality components, precision made. Switch and fine tuning. I.F. output 20-25. Freq. coverage 50 87 Mc/s and 175-215 Mc/s. Supplied with full details and circuit diagram.

89/6 Post 3/6. Knob, 2/9 extra.

THE "UNIVERTER" for all areas

A Band III Converter for home-constructed or factory-made Band I receivers. Uses two Z77, one E390, one U78. Contains its own power supplies. Walnut cabinet. With all instructions. **£9/9/0**
 Post free.

IMMEDIATE DELIVERY All Types Band III Aerials

All Channels, 3-, 4-, 5- and 6-element outdoor, indoor and loft. A few examples—
 Wolsey Minor, indoor, 12/6.
 King Pin, indoor, 7/6.
 Aerialite 4-element loft, 42/6.
 Wolsey Combined Bands I, III, 17/6.
 Aerialite outdoor for fitting to existing mast, 3-ele., 30/-; 4-ele., 36/6; 5-ele., 42/6.
 Chimney lashing and wall fitting equipment available, extra.
 Co-axial Cable, semi-air-space, yd. 9d.
 Aerial, yd. 10d. 300 ohms Feeder, yd. 9d.
 Duplexes, 12/6. Wolsey Crossover Boxes, 15/-.
 Co-axial Plugs, standard type, 1/4.
 Chassis mounting Co-axial Sockets, standard type, 1/-.




LASKY'S (HARROW ROAD) LTD.,

42, TOTTENHAM COURT ROAD, W.1.
 Between T.C.R. and Goudge St. Stas. MUS. 2605
 370, HARROW ROAD, PADDINGTON, W.9.
 Opposite Paddington Hospital. CUN 1979 & 7214
 Open all day Saturday, early closing Thursday.

HIRE PURCHASE
 Terms available on certain items. Please write stating your requirements.

ALL MAIL ORDERS TO HARROW ROAD PLEASE

BUILD THIS FOR £5.7.6.!

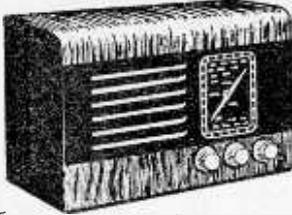

Total building cost including choice of beautiful walnut veneered cabinet or ivory or brown bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple, easy-to-follow diagrams. This terrific new circuit covers all medium and long waves with optional negative feedback, has razor-edge selectivity, and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! All parts sparkling brand-new—no junk! Every single part tested before despatching. Uses standard octal-base valves: 6K7G high-frequency pentode feeding into 6J5G anode-bend detector triode, coupled to 6V6G powerful output beam-power tetrode, fed by robust rectifier. For A.C. Mains, 200-250 Volts (low running costs—approximately 18V Watts!). Size 12in. x 6in. x 5in. Build this long range powerful midget NOW. Send 2/- for priced parts list, testimonials, etc., or send £5.7.6 for all parts and set of plans. (Add 2/6 for packing and post.) C.O.D. 1/6 extra. All orders despatched by return carefully packed.

CONCORD ELECTRONICS (Dept. PK3),
39, Queens Road, Brighton, I.

ANNOUNCING

THE "CAPITAL" BAND III T.V. CONVERTER KIT FULLY GUARANTEED

COMPLETE KIT, including drilled chassis, power pack, ready wound coils, valves, ALL components, screws, nuts, tags, etc., co-axial plugs, sockets and cable. The whole housed in an attractive stove-enamelled metal cabinet, measuring 7½ins. x 4½ins. x 2½ins.

NOTHING ELSE TO BUY FOR A.C. MAINS 200-250 VOLT OPERATION

SUITS ALL T.V. MAKES
T.R.F. or SUPERHET
CIRCUIT DIAGRAM and DE-
TAILED EASY-TO-FOLLOW
WIRING PLANS

SEND £3/19/6 for complete kit and plans. Add 2/- postage and packing.

POST RADIO SUPPLIES
395 Queensbridge Rd.,
London, E.8

Best Buy at Britain's

AMAZING OFFER!
RECEIVER TYPE CR100—A super 11 valve communications receiver covering 30 Kc/s to 30 Mc/s in six bands. Built-in A.C. Mains power pack, 2 R.F. stages, 3 I.F. stages. Variable selectivity crystal filter, B.F.O., etc. **SUPERB CONDITION, OUTSTANDING PERFORMANCE. ONLY £21.** plus 1/- carriage.

R.C.A. AMPLIFIER—For A.C. mains operation 190/250 v. 12 watts output into 600/157/5/5 ohms, input impedances of 250 and 30 ohms, suitable for mike and gram. Brand new, in handsome case, size 14in. x 9in. x 11in. deep. Uses 4-6J7, 2-6L6 and 5U4. Price ONLY £9.19.6, less valves, or £12.19.6, with boxed valves, carriage 10/6.

SPECIAL THIS MONTH
R1155 B RECEIVERS—This is the model with the super slow-motion geared drive. In excellent condition, thoroughly checked and tested. A unique opportunity to acquire a first-class communications receiver for ONLY £6.19.6. CALLERS ONLY.

A.C. MAINS POWER PACK & OUTPUT STAGE—These enable the R1155 type on the main **WORLDWIDE ANY MODIFICATION**. Three types available. £4.10.0, £5.5.0, and de-luxe model with 8in. speaker, £6.10.0. Carriage 5/-. All Power Packs guaranteed six months.
3-VALVE 400L METERS—Latest type, rectangular, 4½in. x 4½in. 0-500 microAmps. Resistance 200 ohms. 79/6. 0-1 milliAmp. Resistance 100 ohms. Has uncalibrated scale of 50 equal divisions. 75/-.
METER BARGAIN—2½in. Projection type. Two ranges, 12 and 120 volts, with multiplier. Brand New and Boxed, 5/9 each.
E.M.I. OUTPUT METER—Desk Type, consists of 2½in. 1 mA. meter with full wave bridge rectifier. Range 0-500 milli-watts and 0-5 watts. Brand New and Boxed. ONLY 35/- each, plus 1/6 post.

METER RECTIFIERS—1 mA. Salford Instruments, 8/6. 2 mA. S.T.C., as used in E.M.I. Output Meter, 5/6. All full wave bridge and brand new.

HEAVY DUTY TRANSFORMERS—200-250 v. Pri. Type (A), 30 v, 50 amp. or Type (B), 50 v, 15 amp. 4½in. x 4½in. x 8in. high. Wt. 24 lbs. BRAND NEW, not ex-Govt. Suitable for chargers, soil heating, etc., 55/- each, plus 5/- carriage.

SELENIUM RECTIFIERS, Funnel cooled. A.C. input 45 v, 2½in. D.C. output 30 v, 10 amps. Can be used with transformer (B) above, 47/6 each, plus 2/6 postage.

HEAVY DUTY SLIDER RESISTORS—250 watts rated to carry 25 amps. 4 ohms resistance. For charging boards, etc. Worm drive. On metal stand 9in. x 4in. x 6in. high, 7/6 each. BRAND NEW.

HEAVY DUTY FIXED RESISTORS—150 watts, 12 amps 1 ohm resistance. 8½in. x 2in. x 2½in. high, 4/6 each. BRAND NEW.

AVO ALL DRY BATTERY ELIMINATOR—Government surplus. For A.C. mains 200/250 volts, output 1.4 v. at 300 mA and 65 volts at 10 mA. Employs metal rectifiers and V570 stabiliser. Size 8½in. x 5in. x 3½in. Suitable for all personal portable type sets. Full instructions supplied. New in cartons and all tested prior to despatch. Price 39/6, plus 2/6 post.

BAND III CRYSTAL CALIBRATORS—By Marconi Instruments. A.C. mains. Directly calibrated, 170-240 Mc/s. 5 Mc/s crystal check. Grey instrument case, 15½in. x 10in. x 10in. Complete with crystal valves, spare set of valves and instruction manual. BRAND NEW in original transit case. SNIP. £5.19.6, plus 10/6 carriage.

PACKARD BELL PRE-AMPLIFIERS—Suitable for conversion to baby alarm, amplifier, etc. Contains miniature relay. Complete with 6SL7, 2D7. Circuit Instruction Book, etc. BRAND NEW. U.S.A. 12/6 each.
EDDYSTONE ROTARY POWER UNITS—In grey metal case. Input 12 v., output 180 v. at 60 mA. Complete with all smoothing and filtering. BRAND NEW, 19/6, plus 2/6 carriage.

CHARLES BRITAIN (RADIO) LTD.
11, Upper Saint Martin's Lane, London, W.C.2. TEM 0555
Shop hours 9-6 p.m. (9-1 p.m. Thursday)
OPEN ALL DAY SATURDAY

ALFRED PADGETT

40, MEADOW LANE, LEEDS 11

Tel.: Clockheaton 99

Bring your T.V. set up to date with the ZC1312 R.D.F. No. 1 set. These sets are Brand New in makers' metal case. R.F. osc. and mixer stages. Suitable for I.T.A. 4 I.F. stages and they are tunable. Valve line up: 13 in all—5 VR65, 1 CV63, 1 VR137, 2 VR60, 1 VR54, 3 VR92, less power pack, but otherwise complete. This is offered at the very low price of 15/- only, with 13 valves. Less valves, 8/6. Carriage and packing 7/6.

Condenser Bargain, 6 x 8 x 8 450 volts working and surge proof, neat and compact. 2/6, post 9d. £1.5.0 per doz. lots, post free. Small 5 Henry (10kva) at 80 mills. 2/-, post 9d. Doz. lots 2/-, post free. Special purchase of Crystal Diodes, 10d. each, post 2d. These are the Real McCoy, with long wire ends, and will put real pep into any crystal set. Small 24-Volt A.C. D.C. Motor, 1.800 revs. p.m. Good torque on 12 volts. Brand New. 3/6 (scrap price), post 1/9.

Small Ball Races for model maker, etc., 6d. each, post 3d. Doz. lots 5/-, post free. Small Metal Rectifiers, 12 months' guarantee. 250 volts at 100 mills. 6/6, post 1/3. Indicator Tube Unit Type BR929A. Complete with 3BP tube, less valves. Brand New. This is a scope all but made, 25/-, 8/- carriage. Case and parts less tube 10/-.

Brand New 3BP1, complete with base and screening case. Just the job for a scope or bedside T.V., 15/-, insurance and packing 4/-. Radio Valves with 90 days' guarantee, post 9d. per valve. Doz. lots post free less 5 p cent.

6V6, 6/6; 6K7G, 4/-; 6K8, 7/6; 6H6G, 1/3; 6HM, 1/9; 6C6, 3/6; 6SH, 6/6; 6SL7, 6/6; 6X5, 5/-; 2X2, 1/6; 6Y11, 1/6; 954, 1/3; 955, 2/6; 900L, 1/-; CV6, 1/-; VR137, 1/3; VR65, 1/6; VR66, 1/-; VR54 9d.; CV63, 1/-; VR92, 9d.; 12SH7M, 2/6; 12SJ7M, 2/6; 12HF6M, 1/3.

Handy Box of Mixed B.A. Nuts and Bolts, etc., 1lb. weight, 1/-, post 9d.

FIRST-CLASS RADIO COURSES . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams, Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**. Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSES

NATIONAL INSTITUTE OF
ENGINEERING
(Dept. 461), 148, HOLE CRN,
LONDON, E.C.1

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents

Morse Practice Set

SIR,—I decided to build the L.F. oscillator as shown in your booklet, "Mastering Morse," and found to my surprise that if the circuit was changed to that below, the H.T. lead could be joined to the positive terminal of the L.T. supply; and, by adjusting the controls, the oscillator gave quite sufficient volume and clear tone for headphone use.

The modified circuit may be of use to morse fans who require a low current consumption oscillator, as the total drain from a three volt battery was .14 amps.—SYDNEY ALLAN (Jnr.) (Belfast).

A Radio Jack

SIR,—Re Rev. A. Morgan's request for article on Radio Jack for Tape Recorder, I, too, am anxious to see an article in PRACTICAL WIRELESS on this circuit, having made some experiments myself with Xtal diode and coil fixed tuned on the M.W. station (Third Programme being the choice in my case). But I find difficulty in obtaining crystal set results in this locality with miniature dust-cored coils. I cannot get anything like the sensitivity obtained with "Lissenagon" 60X coil of 1925 vintage, but, of course, this old favourite does not permit one to make a compact radio jack. I would be very much interested to see in PRACTICAL WIRELESS a compact radio jack, say switch tuned to 208 metres, 330 metres, and 646 metres that would load a tape amplifier in this district.—W. BINGHAM (Grantham).

[We shall shortly be describing a Radio Jack using a crystal diode.—ED.]

Atomic Power

SIR,—With reference to Mr. Benson's letter on Atomic Power in this month's "Open to Discussion."

I believe I am correct in saying that there are the two following objections to his idea:—

(1) As the air used to turn the turbine would have to be brought into close proximity to the highly radio-active pile, to ensure an efficient exchange of heat, it would become highly radio-active. It would therefore be impossible to allow it to enter the atmosphere. That is why a closed cycle is always used.

(2) The power and speed of the turbine depends on the amount of gas which strikes the blades and the force with which it strikes them. Therefore a light gas such as air would be inefficient unless moving at a high speed, which implies high temperature. A heavier gas such as steam, or as is being considered mercury vapour, would only need work at a lower

temperature for the same efficiency.—R. TRING (16) (N.4).

SIR,—Surely Mr. Benson ("Open to Discussion," PRACTICAL WIRELESS, December, 1955), has presented nothing but an alternative method of heat exchange, and one virtually impossible at that; at least the utilisation of heat generated in the pile to drive a steam turbine has the advantage of simplicity.

By modern scientific standards any system which involves mechanical generation of electricity must be obsolete in terms of atomic energy which is in itself pure electricity.

Now a recent discovery has demonstrated the practicability for the first time of generating electricity in quantity without the use of power-driven generators.

I refer to the process of mixing oxygen and hydrogen which under certain conditions may be converted directly into electricity.


To my way of reasoning this is where the atomic pile can fulfil its true function. I refer to its ability to alter the atomic structure of materials.

If the pile can be used to convert, either by heat or atomic radiation, material (water most likely, consisting as it does of oxygen and hydrogen), a true utilisation of atomic energy is achieved, i.e., conversion of atomic energy into usable electricity without a single moving part.

I have no knowledge of the exact method used to mix the gasses, but I should very much like to know if anyone can oblige.—D. HANCOCK (Ashford).

A Recording Critic

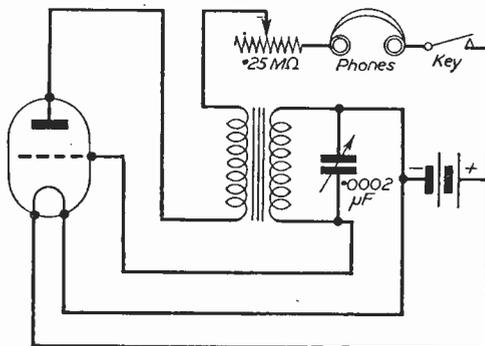SIR,—I am just contemplating taking the plunge into L.P. I have many 78 r.p.m. records which give me great pleasure, but several items which



The circuit referred to in Mr. Allan's letter above.

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

I should like to own, I find are available only on L.P. Looking through the advertisement pages of PRACTICAL WIRELESS, I find that, although I have the choice of dozens of three-speed changers, only one firm markets three-speed single players. Now the weakest link in the chain of music reproduction is the record itself. (By weakest I mean most likely to be damaged. Admittedly the needle is more vulnerable, but a needle replacement is much simpler and cheaper than the replacement of a favourite disc which has become damaged.) We take great care of our records, letting them live in dust-proof polythene envelopes and buying expensive lint—and grit-free cloths and cleaning solutions for their toilet—and then we let them fall Crash! Bash! on to others of their kind from an auto-changer. "Slip-starting" of records on to soft turntable surfaces does enough damage, goodness knows; how much worse will "slip-starting" on to a hard and abrasive surface like that of another record be? It seems, to say the least, a trifle illogical. Am I alone in this view, and if not, why are there so many changers on the market and so few single players?

Also, are sapphire styli all they are cracked up to be? I admit that I have had no experience of L.P., but I have used sapphires of several different makes on 78's in both heavyweight and lightweight pick-ups—the correct type for the pick-up in use in every case, I hasten to add. In every case, without exception, I have found that reproduction has deteriorated and record wear has increased to an alarming extent. I know I am not alone in this experience. Have I simply been unlucky, or are sapphires actually inferior to metal needles? If they are, why are sapphires used exclusively for L.P. reproduction? I know that the optimum combination of new L.P. record and new sapphire stylus is capable of magnificent reproduction; I must believe my own ears. The question is, how long will this state of affairs last? How long before my (very expensive) L.P.s will be worn to such an extent that they are painful to listen to, as I have heard 78s become very quickly under sapphires?—B. L. KERSHAW (Leeds, 16).

Car Radio

SIR,—In reply to inquiries I have received concerning the Constructional Car Radio, I should like to point out that the value of R12 has been omitted, and this should be 50K ohms.

Concerning the output valve on the six volt system, an omission has occurred on this, in that the valve should be 6AG6, which would probably give satisfactory performance, or alternatively the 6V6, which is the closest matching valve for six volt operation, and has a relatively low heater current. Some readers have queried the unusually high bias for this valve, but in actual fact this bias was determined by reference to the unit from which the valve was taken, namely the BC459 receiver. Probably

experiments with bias values may effect an improvement over the six volt types, but I find that the 1.5 is satisfactory for the 12A6.—A. E. PARDY (Pengam).

Ex-Service Sets

SIR,—In answer to the query in the August issue of your magazine, I enclose the following frequencies of a few more ex-W.D. transmitters and receivers. Also, I would like to correspond with a radio enthusiast of my own age (thirteen).—M. C. SYKES, 32, Priory Road, Gloucester.

Rx.	Frequency.
RF24 ...	20-30 Mc/s.
RF25 ...	40-50 Mc/s.
RF26 ...	50-65 Mc/s.
RF27 ...	60-80 Mc/s.
CR100 ...	60 kc/s—30 Mc/s.
Type 109 ...	1.8-8.5 Mc/s.
Type 38 ...	6-9 Mc/s.
Type RA10 ...	150-300 kc/s, 16-5 Mc/s, 5-10 Mc/s.
Type 1403 ...	2-9 Mc/s.
DST100 ...	50 kc/s-30 Mc/s.
Type 58 ...	6-9 Mc/s.
M361 ...	100 kc/s-8,500 Kc/s.
2C1-Mk. 1 ...	35-150 m.
17-Mk. 2 ...	40-61 Mc/s.
3547 ...	45 Mc/s.
TX	Frequency
T1403 ...	2-9 Mc/s.
TX21 ...	4.2-7.5 Mc/s.
T1154B ...	10-5.5 Mc/s, 5.8-13 Mc/s.
T1196 ...	4-6 Mc/s, 6-8 Mc/s.

FRAME AERIALS

(Concluded from page 42)

of 24 s.w.g. silk-covered wire will be suitable for M.W. with 85 turns of 34 s.w.g. wire for L.W., if used. It is desirable to wind M.W. and L.W. aerials on separate formers, and keep them separated, or M.W. signal strength will be very poor with the adjacent L.W. section switched out.

With sensitive mains receivers the aerial may be very small—down to 3½ in. in diameter being feasible. Such an aerial, made as shown in Fig. 5, but with a circular former, will require about 55 turns for M.W.

Other methods of arranging the windings will come to mind. Any insulated type of former or support is suitable. In the free-standing type of aerial illustrated, a simple wooden cross, jointed at the middle, is used, and pivoted so that it can be turned in any direction.

It should not be overlooked that all such frame aerials replace the first tuned circuit tuning coil. An aerial winding such as described, with one end left free and the other connected to the aerial terminal of the set, would have no directional properties, and would only give a signal similar to that from a few feet of wire in a "throw out" aerial.

Editorial and Advertisement Offices: "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363. Telegrams: Newnes, Eand, London. Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

SOUTHERN RADIO'S WIRELESS BARGAINS

TRANSRECEIVERS. Type "38" (Walkie-Talkie). Complete with 5 Valves. In Metal Carrying Case. Ready for use. Less external attachments, 30/- per set. **ATTACHMENTS** for use with "38" TRANSRECEIVER: HEADPHONES, 15/6; THROAT MICROPHONE with Lead & Plug, 4/6; JUNCTION BOX, 2/6; AERIAL 2/6; SPECIAL OFFER of used "38" TRANSRECEIVERS less valves but complete with ALL COMPONENTS. Excellent for SPARES, 11/6 per set. P. & P. 2/-.

TRANSRECEIVERS. Type "18" Mark III. TWO UNITS (Receiver & Sender) contained in Metal Case. Complete with Six Valves, Microammeter, etc. LESS EXTERNAL ATTACHMENTS, 4/10/-.

RECEIVERS. Type "109". 8-Valve S.W. Receiver with VIBRATOR PACK for 6 Volts. Built-in Speaker, METAL CASE, 45.

BOMBSIGHT COMPUTERS. Ex-R.A.F. BRAND NEW. A Wealth of Components. GYRO MOTORS, REV. COUNTERS, GEAR WHEELS, etc., etc. Ideal for Model Makers, Experimenters, etc., 45.

LUBRA HOLE CUTTERS. Adjustable 2 1/2 in. to 3 1/2 in. For Metal Wood, Plastic, etc., 6/6.

RESISTANCES. 100 ASSORTED USEFUL VALUES. Wire Ended, 12/6 per 100.

CONDENSERS. 100 ASSORTED. Mica, Metal Tubular, etc., 15/- per 100.

PLASTIC CASES. 14in. x 10 1/2 in. Transparent. Ideal for Maps, Display, etc., 5/6.

STAR IDENTIFIERS. Type I A-N. Covers both Hemispheres, in Case, 5/6.

CONTACTOR TIME SWITCHES. In Sound-proof Case, Clockwork Movement. 2 impulses per sec. Thermostatic Control, 11/6.

REMOTE CONTACTORS for use with above, 7/6.

MORSE PRACTICE SET with Buzzor on Base, 6/9. Complete with Battery, 9/6. **MORSE TAPPERS**, Std. 3/6; Midget, 2/9.

METERS & AIRCRAFT INSTRUMENTS. Only need Adjustment or with broken Cases. **TWELVE INSTRUMENTS**, including 3 brand new Aircraft Instruments. 35/- for 12.

CRYSTAL MONITORS. Type 2. New in Transit Case. Less Valves, 8/-.

Postage or Carriage extra. Full List of RADIO BOOKS, 2/3d.

SOUTHERN RADIO SUPPLY LTD.,

11, LITTLE NEWPORT ST., LONDON, W.C.2. GERrard 6653.

COVENTRY RADIO

189, DUNSTABLE ROAD, LUTON, BEDS.

Phone: Luton 2677

The Quality Component Specialists offer you Kits of Parts for the following:—

	Manual
Osram "912" Amplifier	3/6
Mullard 10-watt Amplifier	2/6
The Coventry	
2-watt Amplifier	} 1/-
4-watt Amplifier	
6-watt Quality Amplifier	
The Coventry A.M. Tuner Unit	1/-
Denco F.M. Tuner Unit	1/6

Complete Component Price Lists will be supplied with each Manual.

Have you had a copy of our 1954/5 60-page illustrated Component Catalogue, price 1/- plus 3d. postage?

Solder with
LITESOLD
NOW AVAILABLE WITH THE REMARKABLE NEW
PERMANETT
Details of full range now comprising 20 models in folder No. S.P.10 sent on request.
Sole Manufacturers and Distributors
LIGHT SOLDERING DEVELOPMENTS LTD.,
106, GEORGE STREET, CROYDON, SURREY.
Tel. CROYdon 8589


The soldering bit which lasts indefinitely, does not become pitted or lose its face and requires no resharpening, filing or maintenance. Fixed bit models and replaceable bits available in all sizes.

- NO TRANSFORMER NECESSARY.
- FOR MAINS OR LOW VOLTAGES.

Rapid Heating—Extreme Lightness—Twenty models—Bit sizes, 1/8in., 3/16in., 1/4in., 5/16in., 3/8in.—Prices from 19/6. All voltages from 6/7 v. to 250/50 v. (State voltage when ordering.)

DIRECT FROM THE MANUFACTURER

F.3.P.P

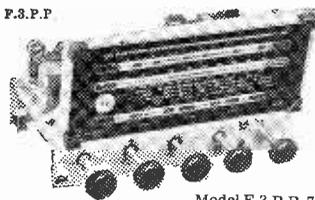

FULLY GUARANTEED
RADIO - RADIOGRAM CHASSIS

ASSEMBLED and READY FOR USE

Model F.3. 5 Valves, 4 watt output, wide range control.
£14.11.11

Model F.3.P.P. 7 Valves. 6 watt output with a "Push-Pull" stage. Separate Bass and Treble controls.
£18.15.4

Model H.4. "AM-FM" Chassis. **£27.16.0**

4 Wavebands including F.M. 7 Valves with latest miniature Cathode Ray Tuning Indicator. General details of F.3 and F.3.P.P.

- Waveband Coverage: 16-50, 190-550 and 900-2,000 metres.
- Ferrite Rod aerial.
- Latest B.V.A. Miniature valves.
- For use on A.C. Mains 200/250 volts.
- Plug-in connections for Pick-up, Speaker and Gram motor.
- Gram switching on wavechange switch.
- Negative feedback applied from output transformer secondary.
- Choice of horizontal or vertical dial.
- Size of Chassis 12in. x 8in. high x 7in.

Write also for details of: F.M. Tuner Units, T.V. Converters, Amplifiers for Truvox Tape Deck.


THE **Dulci** CO. LTD.,

97, VILLIERS ROAD, LONDON, N.W.2.
Telephone: WILlesden 6678.

THE FAMOUS BENNETT COLLEGE can train your mind to SUCCESS

THROUGH PERSONAL POSTAL TUITION
A FREE book vital to your career!

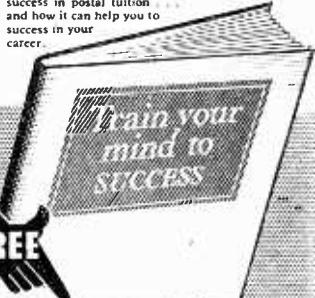Read how the famous Bennett College can help you to success! Send now for this recently published FREE book, "Train your mind to SUCCESS", which tells you about The Bennett College proven success in postal tuition and how it can help you to success in your career.



- WHAT CAREER DO YOU WANT?**
- Building
 - Carpentry
 - Commercial Art
 - Diesel Engines
 - Draftsmanship
 - Electrical Eng.
 - Fire Engineering
 - Mechanical Eng.
 - Quantity Surveying
 - Radio Eng.
 - Surveying
 - Telecommunications
 - Television
 - Accountancy Exams.
 - Auctioneer's Exams.
 - Book-keeping
 - Civil Service
 - Domestic Education
 - Journalism
 - Languages
 - Mathematics
 - Police Subjects
 - Salesmanship
 - Secretarial Exams.
 - Shorthand
 - Short Story Writing
 - and many others
 - GENERAL CERT. OF EDUCATION

To The Bennett College (Dept. A.104N), Sheffield
Please send me, without obligation, a free copy of "Train your mind to SUCCESS" and the College Prospectus on

SUBJECT _____
NAME _____
ADDRESS _____
AGE (if under 21) _____ Please write in Block Letters

THIS COUPON
COULD BE YOUR PERSONAL PASSPORT TO SUCCESS.
Send it NOW!

RECEIVERS & COMPONENTS

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors or, in fact, anything that needs lenses. Then get our booklets, "How to use Ex-Gov. Lenses & Prisms." Nos. 1 & 2, price 2/6 each; also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive lists of lenses, optical, radio and scientific gear, free for s.a.e. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullingdon Rd., Oxford.

AMERICAN RADIO Plans and Devices. Now available. Hundreds of new and startling devices you can make. Only designs of this type available in UK. Receivers, walkie talkies, amplifiers, recorders, magic eye alarms, etc., etc. Full lists, data, illustrations free for stamp. Send to-day.—A.P.S. (PW), Sedgford, King's Lynn.

MIDDLESBROUGH. Largest stocks on N-East coast, Radio/TV components. FM Kits, Gram. Cabinets, Tape Decks, Leak Amplifiers, Valves, etc. Callers only. PALMERS, 106, Newport Road. (Phone: 3096.)

ENGRAVING.—Amateurs and trade surplus can be undertaken by getting in touch with A. G. ENGRAVING, now at 88, Bedford Hill London, S.W.12. (Tel.: BAL 7085.) (Engravers to well-known makers of Electronic Equipment used by the Aircraft Industry, A.W.R.E., etc.)

WALNUT Radiogram Cabinets of distinction; stamp details. R. SHAW, 69, Fairlop Rd., E.11.

R.F. UNITS, Types 27 or 26. 25/-; 25 or 24. 10/- brand new with valves. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

ALUMINIUM CHASSIS made to your requirements; 16 or 18 gauge; any quantity, large or small. We will be pleased to quote. MACHINE CONTACTS, Building 336, Hurn Airport, Christchurch, Hants.

SERVICE SHEETS, T.V. and Radio, over 2,000 models, sale or hire. Valves and Components. S.A.E. with enquiries. W. J. GILBERT, 24, Frithville Gardens, London, W.12.

B.S.R. Monarch 3-speed Autochange Units, new, in maker's sealed carton, guarantee, complete with instructions, template, suspension springs. £9/15/-; carriage paid; immediate delivery. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

TELEVISION, 9in. Models. £6/10/-; 12in. Models. £15; all makes working; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

S/W CLEARANCE! A few portable bat. S/W T.R.F. Rcvrs., crazy prices! Free gear given away! Send large s.a.e. quickly. Box 262, c/o PRACTICAL WIRELESS.

CATHODE RAY TUBES. A limited number of selected slightly used tubes (no burps) which are tested to give good picture with booster transformer. 17in. at 70/-; 15in. 50/-; 4in. 60/-; 12in. 35/-; carr. 7/6 per tube. Picture shown to callers. Booster Transformers. 15/-. GLIKOR RADIO SERVICE LTD., 47, Westgate St., Cardiff.

ONE G.E.C. MINISCOPE, complete, working, in case, instruction manual. £10. 362, Leeds Rd., Bradford 3.

PATENTING, Advice. Service. C. L. BROWNE, 114, Greenways Ave., Banstead, Surrey

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1—extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

F.M. RECEIVERS from £5. BEL. F.M. Pioneers, Marlborough Yard, N.19. (ARC 5078.)

FREQUENCY METER BC221, nearest £30. BERRY, Mill of Forest, Stonehaven.

R3170A UNIT P.T. conv'er. Ch.3. Copies P.W., July, '49-July, '50, Jan. '51-Dec., '54 (ex Jan. '52), offers? 240, Chichester Rd., Portsmouth.

T/V in perfect working order, all makes, many sets from £12; sets available for use any part of the country. T/V requiring attention from £7. Send s.a.e. for lists. 13-Channel Tuners, suitable wiring into receivers, with full instructions. £6/5/-, incl. packing and postage. When ordering state make and model No. of receiver. Orders are dealt with in strict rotation. Few only. Monarch B.S.R. 3-speed Magidisk Autochangers, new in carton. template supplied. £9/10/-. carr. paid. HIGH STREET RADIO, 284-6, High Street, Croydon, Surrey. (Tel.: CROYdon 8030.)

ELECTROLYTICS, capacity, voltage, size, type of mounting, price, post paid. 400, 6v, lin. x 2in., lug. 1/6; 250 + 250, 6v, lin. x 2in., lug. 1/6; 1,000 + 2,000, 6v, 1 x 3, clip. 3/9; 250, 12v, 1/2 x 1 1/2, clip. 1/9; 500, 12v, 1/2 x 1 1/2, W/E, 2/-; 10, 25v, 1/2 x 1 1/2, clip. 1/3; 25, 25v, 1/2 x 1 1/2, W/E, 1/6; 500, 50v, 1 x 3, clip. 3/6; 100, 50v, 1/2 x 1 1/2, W/E, 2/3; 50 + 50, 150v, 1 1/2 x 2, clip. 2/9; 40 + 40, 275v, 1 1/2 x 3, clip. 3/3; 100, 275/350v, 1 1/2 x 3, clip. 3/3; 24, 275v, 1/2 x 2, clip. 3/-; 60 + 250, 275/350v, 1 1/2 x 3, clip. 3/3; 32 + 32, 275v, 1 1/2 x 3, W/E, 3/3; 24, 275v, 1/2 x 2, clip. 3/-; 16 + 16 + 8, 350/425, lug. 4/3; 32 + 32, 350/425v, clip. 1 1/2 x 2, 4/3; 8 + 8, 350v, 1 x 2, clip. 3/3; 16 + 32, 350v, 1 1/2 x 2, clip. 3/9; 8, 450v, 1 x 2, clip. 1/9; 15 + 15, 450v + 20, 25v, 1 x 3, lug, 4/3; 64 + 120, 275v, 1 1/2 x 4 1/2, clip. 5/6; 20 + 10, 450v, 1 x 3, clip. 4/-; 100 + 200, 350/425v, 2 x 4 1/2, clip. 6/9; 8, 500v, 1 1/2 x 2 1/2, clip. 2/6; 8 + 8, 500v, 1 1/2 x 2, clip. 4/-; all All Cans, some with sleeves, all voltages, w.g., sure where marked, new stock, guaranteed. Television Chassis, cadmium plated, steel, size 14 x 13 x 2in. complete with 13 valveholders (9-9BA Pex. 1-9BA Cer. 2-B7G Cer. 1-Int. Oct. Ampl.). 20 various tag strips, cut away for metal rec., line trans. etc., 9/11 each, post paid; front and rear tube mounts to fit above chassis, 3/- pair, post paid. P.M. focus Magnets, wide angle, tetrotube tube, fully adjustable. 12/-, post paid. Scanning Coils, wide angle, with mounting lugs. 19/6, post paid. Mains Trans. PRI 0-210-240. SEC. 250-0-250v. 8ma. 6/5v. 2.5a; 6.3v, 0.6a. 12/- Mains Trans 340-220-0-220-340v. 220-mA. 4v 6.5A. 4v 3A. 4v 1.5A. 2v 1.5A. 4v 6.5A. PRI 0-205-225-245v. 30/-, postage paid.

RADIO CLEARANCE LIMITED, 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

GOVERNMENT SURPLUS Illustrated Catalogue, No. 12, containing over 400 items of electrical, mechanical and radio equipment for experiments, etc. Price 1/6, post free. ARTHUR SALLIS, 93, North Road, Brighton, Sussex.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B. and other Professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to E.M.I. INSTITUTES, Dept. PW28, London, W.4.

RAND III TV CONVERTER, complete, tested and guaranteed, in attractive case; will convert any TV. TRF or Superhet; London or Birmingham Models available. £6/15/-. Make it yourself and save money! Complete kit of parts down to last nut, bolt and screw and comprehensive instructions. £5/5/-. Terms: Cash with order; we pay carriage; immediate despatch. B. FRANKS, 97, Amhurst Road, London, E.8.

SERVICE SHEETS for Hire. Radio, T.V. Components, Valves, etc. supplied. Send stamp for list. M. ROY, 6, Wykebeck Gardens, Leeds, 9.

BUILD YOUR OWN T/V and learn about its operation, maintenance and servicing. Qualified engineer-tutor available whilst you are learning and building. Free Brochure from E.M.I. INSTITUTES, Dept. PW58, London, W.4. (Associated with H.M.V.)

COIL PACKS, 3/9, including 465 I.F.s (p.r.) and 2-gang condenser, post 1/3; V.H.F. 24 set, 10/6, complete with valves, post 2/6; H.F. 1125 set, 7/9, complete with valves, post 2/3. DUKE & CO., 621, Romford Rd., London, E.12.

BAND III CONVERTERS.—Complete kit of parts for "WW and Teletron" Converters, including Teletron or Osamor coils, 2 EF80 valves, drilled chassis and wiring diagram. 45/-, p. and p. 1/-; as above, with power pack kit, 70/-, p. and p. 1/6; Teletron and Osamor Coil Sets. 15/-; Drilled Chassis, 3/9, p. and p. 9d.; Matched Pairs. 6V6G and GT. 17/- per pair, p. and p. 6d. R. J. COOPER, 32, South End, Croydon, Surrey. (CRO 9186.)

OSMOR would like you to have Free Practical Wiring Diagrams of the latest published circuits with full lists of components required. Send 7d. (stamps) to OSMOR RADIO PRODUCTS LTD., 418, Brighton Rd., Sth. Croydon, Croydon 5148. (See advert., page 10.)

RECONDITIONED Taylor Test Instruments with factory guarantee for Students and Amateurs at low prices. A small quantity of various old models available. Write for details to TAYLOR ELECTRICAL INSTRUMENTS LTD., Montrose Avenue, Slough.

RADIO UNLIMITED offer: Mullard 5-10 Amplifier, to spec., complete kit, incl. valves, £10, ready for use. £11/5/-; 3-stage amplifier for AC or AC/DC mains, kit, incl. valves, 49/6, wired 59/6; 5-valve p/pull Amplifier, for AC mains, kit, incl. valves, £6/10/-, wired £7/10/-; Teletron Converter kit, incl. valves and coilset. 55/-, with p/pack 72/6; Mains Trans. 200/0/300, 80ma, 6.3v and 4v, 16/6; Valves, EL32 6P6, 6V6, 5U4, 7/- each; ECL80, EF80, PCC84, PCL80, 11/- each; Diode Crystal Receiver, 11/6; Diodes, 1/3; 0005 3-gangs, 7/6; twin-gangs, 6/6; ultra modern Cabinet, with all fittings and drilled chassis for T.R.F. 32/6, listed at 45/-, 12in. P.M. Speakers at 27/6. RADIO UNLIMITED, Eim Road, London, E.17. (KEY 4813.) Also at 50, Hoe Street, E.17. (LAR 6377.)

EDUCATIONAL

WIRELESS.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply B.S.T. LTD., 179, Clapham Rd., London, S.W.9.

WIRELESS. See the World as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay.

T/V AND RADIO.—A.M.Brit.I.R.E.E. City and Guilds, R.T.E.B. Cert., etc., on "no pass—no fee" terms. Over 95% successes. Details of exams, and home training courses in all branches of radio and T/V; write for 144-page handbook—free. B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. B.I.E.T. (Dept. 242A), 29, Wright's Lane, London, W.8.

THE INSTITUTE of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

MERCHANT NAVY. Train as Radio Officer. The big liners are open to you, but you must qualify for the F.M.G. Certificate. Day, Evening and "Radiocerts" Postal Courses. Est. 36 years. S.A.E. for prospectus from Director, THE WIRELESS SCHOOL, 21, Manor Gardens, London, N.7.

MERCHANT NAVY Wireless School, Overseas House, Brooks' Bar, M/cr 16.

A.M.I.Mech.E., A.M.Brit.I.R.E.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook free. B.I.E.T. (Dept. 242B), 29, Wright's Lane, London, W.8.

FOR SALE

GUARANTEED TELEVISION, 12in. Models, all identical, new, 5 channel. £24 each; carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, Forest Hill, S.E.23.

SEVERAL EARLY MODELS 9in. Television, complete and mostly working, £5/5/- each; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

THE HIWAYMAN. A new super Portable Radio for the home constructor; all-dry 4-valve superhet with Ferrite rod aerial; easy wiring diagrams and instructions 1/6 (post 3d.). **RADIO EXPERIMENTAL PRODUCTS LTD.,** 33, Much Park St., Coventry.



Don't scrap that failing car battery or radio cell. Try Renewbat conditioner. Works like a charm. Simple and safe to use. Full instructions. Small 6 v. car size, 3/6, 12 v. size, 5/-. Post free.

CHAMPION PRODUCTS,
43, Uplands Way, London, N.21.
Phone: LAB 4457.

WANTED

PROMPT CASH offered for your surplus brand new Valves, Loudspeakers. Components, etc. Send list and prices to R.H.S. LTD., 155, Swan Arcade, Bradford, 1.

WANTED, a "Ham" or someone of similar qualification to repair amateur-built "Hi-Fi" set, now in other hands, in spare time. GREY, Mayfair 9181 during day.

WANTED, Admiralty Handbook of Wireless Telegraphy, Vol. 1. Box 261, C/O PRACTICAL WIRELESS.

When replying to
advertisements please
mention
"PRACTICAL WIRELESS"

BOOKS

I.P.R.E. TECHNICAL PUBLICATIONS. 6,500 Alignment Peaks for Super-heterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy. The Practical Radio Engineer, quarterly publication of the Institute, 2/-; membership and examination data, 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

AMERICAN MAGAZINES—One-year "Audio Engineering," 35/-, specimen copy, 3/6; "Popular Science," 43/-; "High Fidelity," 50/-; specimen copy, 4/6. Free booklet quoting others. WILLEN LTD., Dept. 40, 101, Fleet Street, London, E.C.4.

VALVES

WANTED, Valves, EY51, ECL80, KT61, 6U4GT, PL81, 35Z4, etc., etc., prompt cash. WM. CARVIS LTD., 103, North Street, Leeds, 7.

KENDALL & MOUSLEY LTD.
(Technical Books Dept.)
OFFER THE FOLLOWING

BOOKS

Practical T.V. Aerial Manual for Bands I and III (R. Laidlaw). T.V. Preamplifiers Bands I and III (B. L. Morley). Television Circuit Refinements (C.H. Bantborne). Unit Constructed T.V. Receivers (E. N. Bradley). We can supply all parts for the Single-Ended Direct Coupled Amplifier. The "Univertor" Converter for Band III T.V. (Anderson and Torrance). WE CAN SUPPLY ANY GOOD COMPONENTS, VALVES, TRANSFORMERS, ETC., AS WELL AS 1% RESISTORS AND CONDENSERS FROM STOCK. 18, MELVILLE ROAD, EDBASTON BIRMINGHAM 16

ASTRAL RADIO PRODUCTS

'HOME RADIO,' 32 page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d. TRF COILS, Specified for 'Bedside Push-button, 4', 'All Dry 3 Band, 3', 'Push-button 4', etc., 6/6 pr., post 6d. Push-button Unit with modification data 7/-. DUAL WAVE HF Coil, Specified for 'Summer All Dry Portable,' 'Modern 1 Valve,' 'Modern 2 Valve,' 'B7 G Battery Miniature,' etc., 4/3, post 3d. I.P.T.'s Miniature, 1 1/2" x 2 1/2" round in cans. Extra high 'Q'. Special offer, 8/6 pr., post 6d. COILS, 'AC. B' special 3', 3/3 each, post 6d. FRAME AERIALS, M.W., 5/-, post 4d. H.F. Choke (Osmor Q.C.1) 4/-, post 4d. Crystal Set Coils, L. & M.W., 2/6, post 3d.

82, Centurion Road, Brighton

ALL TYPES of Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.,** 36, Chalcot Road, N.W.1. (PR1mrose 9090.)

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

TO MEN who are interested in Working Overseas. A large electronics organisation is prepared to offer short-term engagements from one to three years to skilled Radio Mechanics for work overseas. Vacancies particularly suitable for ex-Service N.C.O.s. Rates of pay are high and average £75 per month, plus all found when abroad. Suitable training given in U.K. Permanencies will almost certainly be offered to men who show exceptional aptitude and keenness with a view to further training as Team Leaders. Candidates must be single, medically fit and willing to work anywhere in the world. Box No. 263, c/o PRACTICAL WIRELESS.

DENCO (GLACTON) LIMITED, due to expansion, require the services of an Engineer able to design coils and coil packs in keeping with modern technical requirements. Permanent employment and participation in pension scheme is offered to a first-class designer. 357/9, Old Road, Clacton-on-Sea, Essex.

DENCO (GLACTON) LIMITED, due to expansion, require the services of a Foreman skilled in setting Douglas Wave and other Coil Winders and the intelligent control of labour. Permanent and pensionable employment is offered to a man between the ages of 25 and 50 years. 357/9, Old Road, Clacton-on-Sea, Essex.

ELECTRONICS—First-class openings for young men with service or amateur radio experience on work which introduces them to television technique. Apply in writing to the Personnel Officer, PYE LTD., St. Andrew's Road, Cambridge.

SCHOOL OF MARINE RADIO AND RADAR (A.S.T.), Hamble, Southampton, approved by Ministry of Education, offers courses for Merchant Navy Radio Officers, M.T.C.A. Radar certs. Marconi Scholarships available. Apply COMMANDANT, quoting A.12.

RADIO INSPECTOR required to cover the overhaul and testing of modern aircraft Radio and Radar equipment. The post is both permanent and pensionable. Free transport to local towns. Canteen facilities. Write fully stating experience and qualifications. **AIRTECH LIMITED,** Aylesbury & Thame Airport, Haddenham, Bucks. (Telephone: Aylesbury 1363.)

TELEVISION OFFERS CAREERS for young men, previous experience not necessary as training is given. Apply in writing to the Personnel Officer, PYE LTD., St. Andrew's Road, Cambridge.

RADIO MECHANICS

Ferranti Limited have vacancies for Skilled Radio Mechanics, preferably with Radar experience for a variety of work in production and research departments. Good opportunities exist especially for those who have, or are willing to study for, the City and Guilds Certificates. Please write, giving details of career to date, to the Personnel Officer, Ferranti Limited, Ferry Road, Edinburgh, 5, quoting Ref. RM.110.

TESTOSCOPE MAINS TESTER



For high and low voltage testing.
Standard Model
range 100/850 volts A.C. or
D.C. Dual Model: range 1/30 and
100/850 volts A.C. or D.C.
Write for interesting leaflet 29F.

Runbaken
WARRINGTON

BOOKLET—"Hints on Electrical Testing," post free 1/-.

VIEW MASTER BAND III CONVERSION

Send for our fully detailed list for
the View Master Band III Converter
described in Practical Television.

WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey.
Telephone: KINGston 4099.

CLEARANCE SALE (LAST MONTH!)

Special offer new valves, in makers' cartons:—
6K7G, 4/3; 3 for 11/9. 6K7 (metal), 5/9. 6SK7
(metal), 5/9. 2 for 14/9. 6F6G, 5/9; 2 for 10/6.
P.W. "ECONOMICAL AMPLIFIER" VALVES.—
Two RK34s (double triodes) with holders, 5/6.
(Use for push-pull output and/or full wave rectifiers.)
Single valves, 2/3.
KTZ83 (not in makers' cartons, but unused), 4/3.
Other Types —
A—Makers' cartons. B—Unused, boxed.

Type	A	B	Type	A	B		
6H6	2/9	6K8G	—	7/8	12H6	—	2/9
6J5	6/-	6Q7G	—	7/8	7193	—	2/6
6J5GT	3/9	6Q7GT	—	7/8	1B33	—	1/9
6J6	—	6SH7	—	5/6	6C31	—	2/9
6J7	—	6X5GT	—	6/9	6C31	—	2/9
6J7	—	6-18D3	—	—	6F92	—	4/9
6K6GT	5/9	—	6AM6	—	6-1VU11	—	3/-

POTENTIOMETERS, 5K, 500K. All with
spindle, mostly original cartons, 1/3 (6 for 5/6).
MICAS, 2/- doz. 1 50, 75, 200, 400, 600, 2,000, 3,000,
5,000 pt. (Midget 100 pt., 6d. each.)
DOUBLE 50 pt. TRIMMERS. Postage stamp type
two trimmers for the price of one. 6d. pair.
MIDGET TUBULARS.—0.04, 0.01 mfd., 3/6 doz.
6 MFD. 2,000 V. TEST (metal block), 2/9, post 1/-.
DOUBLE 0.5 MFD. 6 for 2/- (5d. each). Small
metal block—can save space and neatens layout.

COAX Low Loss 9d. yd.
Standard 25 yd. 12 6

Both types 75 Ω. Approx. 1/4 in. dia.
COAX FITTINGS.—Solderless plug, 1/2; socket, 1/3;
outlet box, 4/6; coupler (double socket), 1/6.
Line connector (one two lengths permanently), 1/3.
SYSTOLEX SLEEVING.—1, 11, 2 n.m.m. 5 colours,
assortment of 36 yds. for 2/6.
SILVERED CERAMICS (wire ended). Take up less
room than resistors, and give a quality job. 4.7,
7.5, 10, 15, 20, 22, 27, 33, 39, 47, 56, 75, 100, 150,
200, 270, 330, 390, 470, 1,000, 2,000, 3,000, 5,000 pt.
9d., 8/- doz.

BOOKS OF THE FUTURE! (post 4d.)
Practical Transistors and Transistor Circuits. Build
these new exciting circuits now using your own
cheaply made transistors, 2/6.
Practical F.M. F.M. fully explained, with lots of
circuits for home construction.
Radio Controlled Models for Amateurs. Just published!
Gives simple explanations and practical data
for all types of control systems.
Please allow post and packing on orders under £1.
REED & FORD 2a, BURNLEY ROAD, AINSDALE, SOUTHPORT

ARE YOU SURE?

Only one in a hundred home-built receivers,
amplifiers and so on give their best.
Remember, just one inaccurate component
will ruin performance. Is that 1,000-ohm
resistor 800 ohms or 1,200 ohms—or some-
thing in between? With 20 per cent. toler-
ance it could be any of these values.
Our Res/Cap. Bridge complete in every
detail for only 31/6, will check every resistor
and condenser quickly and accurately.
Here are other items from our range of
famous test gear kits, at the lowest prices
in the world.
Spot Frequency Sig. Gen., 35/- Inductance
Bridge, 42/6. Audio-Frequency Bridge,
38/6. Twin Multi-ometer, 30/-.
Post and packing 1/6 on all kits.
Stamp for illustrated lists.

RADIO MAIL, Dept. M
6, Raleigh Street, Nottingham

MORSE CODE Training

Send for the Candler
BOOK OF FACTS
It gives details of all Courses which include
a Special one for acquiring amateur licence.
CANDLER SYSTEM CO. Dept. 5L0
52b, Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

RADIO AND TELEVISION COMPONENTS

All parts in stock for:
Viewmaster, Soundmaster, Teleking, etc.
Easy Terms available.
21d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.,
FINSHWAYE, NEWBY BRIDGE,
ULVERSTON, LANCs.

ANNAKIN'S BARGAINS

Infra Red Image Converters. New in
transit case, 15/- ea., post 1/10 less (Zamboni
Pile). R.A.F. Box Kites. 3611n. x 17in. x 17in..
new (less string), 17/- post free. Metal box
with 16 Toggle Switches, etc., new, 6/-
post 1/6. 350 Metal Pencil Rectifiers. 2/6,
post 3d. 2-Gang USW Variable Condensers,
1/-, post 4d. RDF-1 Trans-Receiver, with
5 VR65, 1 VR54, 1 CV63, 1 VR137, 2 VR66,
3 VR92 (less 5Z4), new, 30/-, carr. free.
Money back guarantee. C.W.O. only. Free
Lists.
25, ASHFIELD PLACE, OTLEY, YORKS

1-Finger Pianists

Build your own electronic keyboard
and play everything! Send for free
leaflet. Cuitar, cello, flute and trumpet
are all easy. Write now...

**C & S, 10 Duke St., Darlington,
Co. Durham**

Broadcast In Your Own Home



The New Highly
Sensitive Micro-
phone incorporating
a specially wound
transformer de-
signed to match any
Radio or Radiogram,
mains or battery.
Hours of amusement
at a party, good fun
for all the family.
Suitable for baby
alarms and many
other purposes. Not
a toy but a guaranteed working instrument.
Full instructions enclosed.
Made to sell at 21/-.
OUR PRICE 15/- POST
FREE.
Trade supplied.
E. CLAPSHAW
369 Alexandra Rd., London. N.10

The "TYANA" Standard Soldering Iron



- Adjustable Bit.
- Weight approx. 4 oz.
- Heating Time 3 min.
- 40 Watt economy Consumption.
- Standard Voltage Ranges. 14/11

Replacement Elements and Bits
always available.

"DIPLOMA" HEADPHONES



Lightweight
High Resistance
(4,000 ohms). Com-
plete with
cord. 17/6

Ideal for CRYSTAL SETS
KENROY LIMITED
152/297 UPPER ST., ISLINGTON,
LONDON, N.1.

Telephone: Canonbury 4905-4663

F M and HI-FI Components

DENCO F.M. TUNER	circuits	1s. 6d.
RADIO CONST'R. F.M.	..	2s. 0d.
MULLARD AMPLIFIERS	..	3s. 6d.
OSRAM 912 PLUS	..	4s. 0d.

Separate price lists available on request to
**J. T. FILMER MAYPOLE ESTATE,
BEXLEY, KENT.**
Tel. Bexleyheath 7267.

BROOKS (Radio)

4 Charles St., Morecambe, Lancs

Tested VALVES		Guaranteed	
1R5	7/6	6K8GT	9/-
1T4	6/6	7S7	8/6
155	6/6	7B7	8/-
384	7/6	7Y4	7/6
3V4	7/6	7C5	8/6
5U4G	8/6	7C6	8/6
5Z4G	8/6	12K7GT	8/6
5Y3G	7/6	12Q7GT	8/6
6X5G	6/6	12K8GT	9/-
6V8GT	7/-	25Z4GT	8/6
6K7/GT	5/6	35Z4GT	8/-
6Q7	9/-	35L6GT	8/6

80 8/6
VU39
(MU12/14)8/6
UY41 8/-
UL41 9/6
EY51 12/6
EF90 10/-
ECL80 11/-
PL81 11/6
6AM6 7/-
6AL5 6/6
6SN7 8/-

Post and packing 6d. per valve.
Gold sprayed expanded metal fret up to 24"
x 24", 1d. per sq. in., post and packing 1/-

STAN WILLETTS

43 Spon Lane, West Bromwich, Staffs

Tel.: WES 2392

SPECIAL OFFER.—ANY 5 VALVES FOR

12/6. EF39, EF36, EBC33, EL32, TT11, SF81, ATP4, EA50, 4D1, 8D2, 9D2, P. & P. 9d, 6V6GT, 6/-; 6X5, 6J6, 12B6E, N77, EL91, EF39, EBC33, Sylvania red EF50, 807, 5/6 each; EF37A, 10/6; 6X4, 6/9; 6A5, 7/6; EF54, 4/6; 1N5, 2/9; UY41, UL41, UBC41, UCH42, 9/6 each; 10F1, PCL43, 9/6; 6SN7GT, 6SL7GT, 7/6; 1S5, 174, DAF91, DF91, 6/9; U25, 12/6; ECL80, 10/6; 12AU7, 7/6; 5U4G, 7/6; EC52, 4/9. P. & P. 6d.

"TRIPLET" 1 mA meter rectifiers, brand new with circuit, 5/6. P. & P. 4d.

GERMANIUM CRYSTAL DIODES.—

G.E.C., 1/- each, 9/6 doz., P. & P. 3d.

VIBRATOR PACKS for 12 or 24 volts, fully smoothed with circuit, 14/6. P. & P. 2/6.

PRE-AMPLIFIERS (Packard-Bell).

Brand new with valves 6SL7, 2BD7, and circuit, 12/6. P. & P. 1/-.

WANTED: NEW VALVES

TELEKIT SUPPLY

CHANTRY LANE, BROMLEY, KENT

Please mention P.W. and enclose 6d. postage

VALVES GUARANTEED

OZ4	5/-	6BS7	7/6	12BA6	7/-
1LN5	(Soiled) 3/6	6BW6	6/6	12BE6	6/-
1S5	6/-	6B8	5/-	12BH7	10/6
1U5	5/-	6KT7M	6/6	15D2	5/6
3D6	(Soiled) 3/6	6KTG	4/6	50C5	5/6
6AK5	6/6	9D6	5/-	TT11	5/6
6BA6	7/-	12A6	5/-	UW111	4/6
6BH6	6/6	(Soiled) 5/-	W77	5/6	

Most other types of valve (BVA and Surplus) also available.


Kits:—F.M. from £5.18.6.

Band III Converter from £2.8.0.

104, HIGH STREET, BECKENHAM, KENT.

Shop Exclusively for the Home Constructor.

Phone: Beckenham 3720.

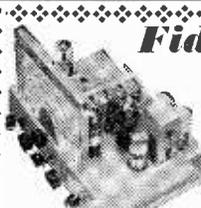

Fidelia

HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10

Fidelia AM/FM models give reception of V.H.F. High quality transmissions plus normal wavebands. Major AM/FM 12 valves, £44. De-Luxe AM/FM 11 valves, £33/12/-, F.M. Tuner, £14/3-. Data sheets free. Electro Acoustic Developments, 2, Amburst Road, Teiscombe Cliffs, Sussex.

SHORT-WAVES!

An addition to the noted World-wide service given to radio constructors by

SPARKS' DATA SHEETS

From the Workshops of L. Ormond Sparks comes the first of a new series of:

CRAFTSMAN BUILT AND TESTED

Radio Receivers & Amplifiers.

The "KESTREL" Short-Wave 3
A highly efficient receiver for battery operation. H.F., Det. and Pen. output. Electron-coupled regeneration. Bandspread Tuning. 9in. Scale. Slow-motion drive. Rigid construction. Plug-in Coils. 9.5 Metres upwards. Latest B.V.A. valves.

Individually Hand Built and Tested. Send Stamp for full specification and price. Only a very limited number of orders can be accepted in any one month.

L. ORMOND SPARKS (P)
8, COURT ROAD, SWANAGE, DORSET

BEST

VALUE YET!

Our Super-Handbook, "The Home Constructor" (76 pp.) now incorporates:—

- *20 CIRCUITS.—Superhets, T.R.F. Sets, Amplifiers, Feeder Units, Test Equipment, etc.
- *SUPERHETS.—Full constructional details, supra-simplified diagrams for building a variety of superhets.
- *COIL PACK.—Full constructional details for building a superhet coil pack.
- *CAR RADIO.—Full constructional details.
- *BATTERY CHARGER, details for building a CHEAP charger.
- *RADIO GEN.—Pages of Information, Resistance Colour Code, Formulae, and "know-how."
- *RADIO CONTROL.—General information and list.
- *RADIOGRAM.—Constructor's list.
- *CATALOGUE.—Profusely illustrated price list of components. All for 2/6 (plus 2d. post).
- *Examples from our really extensive stock —
- SUPACOILS.**—Variable iron-dust cored coils. 10-30, 16-50, 30-75, 75-200, 190-550, 800-2,000 metres Aerial H.F., or Osc. 3/- each. (L.M.S) superhet pack—single hole fixing—recommended for numerous receivers—ready aligned. 47/5.
- 40 SUPACOIL PACK.**—Similar to above. For use with superhets having an R.F. stage. Ready aligned. £2/-.
- (Either of above can be supplied to order to cover any 3 wavebands from our range.)
- EQUIPMENT LEAFLET 10** gives full easy instructions for YOU to BLACK & DECKER BRIDGES and WOLF CUB EQUIPMENT. —Full range for 30/- down—ask for particulars.

* "The most helpful book in the Trade."
SUPACOILS (Dept. Pl.)
21, Markhouse Road, London, E.17
Telephone: KEY 6896

GRAM-PAK AMPLIFIERS




£3.19.6 P. & P. 2/6d.

Fits neatly inside your record player or portable gramophone leaving room for speaker. Dimensions 10in. x 3 3/4in. x 2in. 4 watts quality output. Suitable for all speakers and with standard or L.P. pickups. Built-in power pack, 200-250 v. A.C. Valves 6J7 and 6V6 available at 20/- for the pair if required.

ELECTRO-ACOUSTIC LABS
TAIN — ROSS-SHIRE — SCOTLAND

TELETRON SUPER INDUCTOR COILS

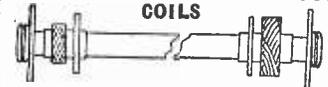

FERRITE ROD AERIALS

Wound on high permeability Ferroxcube rod. MW.8/9. Dual wave, 12/9.

BAND III CONVERTER COILSET, 15/-
Wiring diagram, circuit and constructional information 3d. (free with coilsets). Selective Crystal diode coil, Type HAX, 3/-.
For tape and quality amplifiers. Dual wave T.R.F. Coils, matched prs., 7/-.
Transistor coils, IPT's etc. available from leading stockists. Stamp for complete list and circuits.

THE TELETRON CO. LTD.
246, Nightingale Road, London, N.9
HOW 2527



DECCA RECORD PLAYERS

Standard or L.P. list price £12.1.6 our price 8 gna. Packing, carriage, etc., 10/6.

PLUS - A - GRAM

CONSOLE and Table models at less than half price. 3-speed, variable speed, auto-change and AC/DC models available.

DECCA 78 r.p.m. variable speed players. Garrard motors. Plug-in heads. Sapphire styl. List price £12.18.5. Our price £8.18.6. Packing and carriage, etc., 10/6.

Send stamp for bargain list of record players.
RONALD WILSON & CO.
12, BRIDGE STREET, WORCESTER.

H.A.C. SHORT WAVE EQUIPMENT

Noted over 18 years for... S.W. Receivers and Kits of Quality.

Improved designs with Denco coils:
One-Valve Kit, Model "C" Price, 25/-
Two " " " " "E" " 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. TH), 11, Old Bond Street, London, W.1.

NEW BOOKS

- (All prices include postage)
- "A Beginner's Guide to Radio," by F. J. Camm. 8/-.
 - "Radio Servicing Pocket Book," by Molloy & Hawker. 11/-.
 - "Telecommunications Principles and Practice," by W. T. Perkins. 22/-.
 - "Practical TV Circuits," by F. J. Camm. 15/6.
 - "Practical Aerial Manual for Bands I & III," by Laidlaw. 4/9.
 - "TV Receiver Servicing, Receiver and Power Supply Circuits," by Spreadbury. 22/-.

PLEASE WRITE OR CALL FOR LISTS.
UNIVERSAL BOOK CO.
12 LITTLE NEWPORT ST., LONDON, W.C.2
(adjoining Lisle St.)

Trace the Trouble
in a Trice



PIFCO
ALL-IN-ONE
RADIOMETER

- * Circuit Test
- * L.T. & H.T. Tests
- * mA Test
- * Valve Test

Use the PIFCO All-in-One RADIOMETER for the practical testing of all types of radio and electrical apparatus. You can carry out continuity and resistance tests, check H.T., L.T., and G.B. voltages, also Household Appliances, Car Lighting Systems, Bell Circuits, etc. May be used on A.C. or D.C. mains.

Obtainable from your local dealer.
Write for informative folder to:—


★ ONLY
32/6
COMPLETE

PIFCO LTD., WATLING ST., MANCHESTER 4
and 36-37, UPPER THAMES ST., LONDON, E.C.4

We're Happy and Proud
to report

THE GOLDRING VARIABLE RELUCTANCE
CARTRIDGE NO. 500 WAS RATED

"BEST CARTRIDGE"
"BEST BUY"

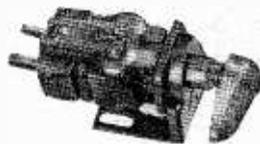

Tested against 25 competitive cartridges including those of variable reluctance, magnetic, ceramic, moving coil, crystal and capacitance types.

By a leading consumer product testing organization
in the U.S.A.

Price complete with two Sapphire Styli for Standard and L.P. £2.10.0 plus 19/6 P. Tax.
Cartridge fitted with Diamond L.P. and Sapphire Standard Styli. £6.0.0 plus £2.6.10 P. Tax.
Cartridge fitted with Diamond L.P. and Standard Styli. £9.10.0 plus £3.14.2 P. Tax.

The
Goldring Manufacturing Co. (Great Britain) Ltd.
486, HIGH RD., LEYTONSTONE, LONDON, E.11
Telephone: LEYtonstone 1252 and 1081.

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

T/V TECHNOLOGY
T/V SERVICING
ADVANCED SHORT-WAVE RADIO
RADIO ENGINEERING
RADIO SERVICE ENGINEERING
RADAR
ELECTRONICS
FREQUENCY MODULATION

I.C.S. will also coach you for the following examinations:—

B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

DON'T DELAY—WRITE TO-DAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful. Reduced terms for H.M. Forces.

Dept. 170D, I.C.S., 71, Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS.
(Dept. 170D), International Buildings, Kingsway,
London, W.C.2.

Please send booklet on

Name Age

(Block letters, please)

Address



PROOPS BROS. LTD.

SOME OF THE MANY BARGAINS AT

The Walk-around Shop

2 Metre Receiver Type 1392. Air Tested 15 Valve Superhet. Frequency 95-150 Mc/s. (2-3 metres). Slow-motion tuning over 95-150 Mc/s or can be Crystal controlled. Power supply required: 240-250 v. at 80 mA. 6.3 v. at 4 a. Size: 19in. x 10in. x 10in. Standard rack mounting. **PRICE £6.19.6.** Complete with valves and circuit diagrams. Pkg. & Pstg., 17/6. 10/- returnable on packing case.

R.1132 Receiver. Suitable for conversion to F.M. Original Frequency 100 to 120 Mc/s. Valve line up: VR65 (2), VR66, VR67, VR53 (2), VR57. Switchable A.G.C. and A.V.C. Variable B.F.O. Circuit diagram with unit. Standard Rack Mounting. In first-class condition. £3.7.6, packing and carriage 15/-. 10/- returnable on packing case.

R.F. Units. R.F.24 20/30 Mc/s Switched Tuning, Fully Valved, 9/6 ea. R.F.25 40/50 Mc/s Switched Tuning, Fully Valved, 9/6 ea.

Absorption Wavemeters. In metal case, 3½in. x 4½in. x 5½in. With calibrated dials 0-100, covering approximately 190-210 Mc/s 120 v. Neon Tube, 6/6, p.p. Or with transit case, 9/-. p.p.

1 m/a Miniature Meter Rectifier (Full Wave). Brand new, of well-known manufacture. 8/6, p.p.

Make a Miniature Pocket Radio. Incorporating high "Q" technique using the New Ferrite rod. Made possible by simple conversion of an ex-Govt. Hearing Aid. £2.6.0 post paid, with circuit diagram and full instructions. Batteries extra: 1.5 v. L.T. (Type D18) 8d.; 30 v. H.T. (Type B119), 4/3.

F.L.B Radio Filters, 10/- ea., 1/6 p.p.

Aerial Rods. 12in x ½in. sections, copper plated. 2/3 per doz

NOTE: ORDERS AND ENQUIRIES TO DEPT. "P."

PROOPS BROS. LTD. Telephone LANGham 0141
52 Tottenham Court Road, London, W.1.

Shop Hours: 9-6 p.m. Thursday; 9-1 p.m. Open all day Saturdays

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

- 1/6d. each
1937 Crystal Receiver ... PW71*
The "Junior" Crystal Set ... PW94*
2s. each
Dual - Wave "Crystal Diode" ... PW95*

STRAIGHT SETS

Battery Operated

- One-valve : 2s. each
The "Pyramid" One-valver (HF Pen) ... PW93*
The Modern One-valver ... PW96*
Two-valve : 2s. each.
The Signet Two (D & LF) ... PW76*

- 3s. each
Modern Two-valver (two band receiver) ... PW98*
Three-valve : 2s. each
Summit Three (HF Pen, D, Pen) ... PW37*
The "Rapid" Straight 3 (D, 2 LF (RC & Trans)) ... PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ... PW87*

- 3s. each.
The All-dry Three ... PW97*
Four-valve 2s. each.
Fury Four Super (SG, SG, D, Pen) ... PW34C*

Mains Operated

- Two-valve : 2s. each.
Selectone A.C. Radiogram Two (D, Pow) ... PW19*
Three-valve : 3s. 6d. each.
A.C. Band-Pass 3 ... PW99*
Four-valve : 2s. each.
A.C. Fury Four (SG, SG, D, Pen) ... PW20*
A.C. Hall-Mark (HF Pen, D, Push Pull) ... PW45*

SUPERHETS

- Battery Sets : 2s. each.
F. J. Camm's 2-valve Superhet ... PW52*
Mains Operated : 3s. 6d. each.
"Coronet" A.C.4 ... PW100*
AC/DC "Coronet" Four ... PW101*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : 2s. each.
Simple S.W. One-valver ... PW88*
Two-valve : 2s. each.
Midget Short-wave Two (D, Pen) ... PW38A*
Three-valve : 2s. each.
Experimenter's Short-wave Three (SG, D, Pow) ... PW30A*
The Perfect 3 (D, 2 LF (RC and Trans)) ... PW63*
The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen) ... PW68*

PORTABLES

- 1s. 6d.
The "Mini-Four" All-dry (4-valve superhet) *

MISCELLANEOUS

- 2s. each.
S.W. Converter-Adapter (1 valve) ... PW48A*
(2 sheets), 7s. 6d.
The P.W. 3-speed Autogram ... *
The P.W. Electronic Organ (2 sheets), 7s. 6d. *

TELEVISION

- The Practical Television Receiver, (3 sheets), 10/6
The "Argus" (6in. C.R. Tube), 2/6*
The "Super-Visor" (3 Sheets), 7/6*
The "Simplex" ... 3/-*

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94 are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : 2s.
B.B.C. Special One-valver ... AW387*

Mains Operated

- Two-valve : 2s. each.
Consoelectric Two (D, Pen), A.C. ... AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amateur Wireless*, W.M. to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : 2s. each.
S.W. One-valver for American ... AW429*

- Two-valve : 2s. each.
Ultra-short Battery Two (SG, det Pen) ... WM402*

- Four-valve : 3s. each.
A.W. Short Wave World-beater (HF Pen, D, RC, Trans) ... AW436*

- Standard Four-valver Short-waver (SG, D, LF, P) ... WM383*

Mains Operated

- Four-valve : 3s.
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ... WM391*

MISCELLANEOUS

- Enthusiast's Power Amplifier (10 Watts) (3/-) WM387*
Listener's 5-watt A.C. Amplifier (3/-) WM392*
De Luxe Concert A.C. Electrogram (2/-) WM403*

QUERY COUPON

This coupon is available until Jan. 5th, 1956 and must accompany all Queries, sent in accord with the notice on our "Open to Discussion" page.
PRACTICAL WIRELESS, Jan., 1956.

Season's Greetings!! from

SUPERIOR RADIO SUPPLIES

THE "PRINCESS" CONSOLE

A very attractive walnut veneered cabinet with internal panels and inside lid in polished sycamore. A lift-up lid covers a centrally mounted motor board size 16½ in. long, 14 in. back to front. On either side of the motor board there is a storage compartment size 4 in. wide, 7 in. deep, 14 in. back to front. Clearance between underside of lid and top of motor board is 5½ in. Overall size of cabinet is 32 in. high, 26½ in. wide, 15½ in. back to front. An ideal cabinet for a console type tape-recorder or quality amplifier.



Price £11.15.0, plus 15/- carriage.

The SUPEREX "55" ATTACHE BATTERY PORTABLE

!! The Portable—
That's Popular !!
Building Cost £7.15.0, plus 3/6 p.p.



- Really outstanding quality.
- Four Valve Battery Superhet.
- Perfect Reception in All Areas.
- Refined Cabinet 10½ in. x 8½ in. x 5 in.
- Very Simple Construction.

During the past year this receiver has been built and tried by a number of P.W. Constructors who, by an overwhelming majority, have acclaimed it as a real winner! Performance is of the highest standard and will compare equally well with portables of three and four times the price. We make no idle claims, as a good circuit with new components can always produce a first-class result. Send 1/6 for "Superex 55" Construction Booklet.

BRAND NEW VALVES—Mullard "tested"—EF91 at 8/6, EF80 at 10/6, 6BW7 at 12/6, 12AT7 at 12/6, ECF82 at 10/6, PCC84 at 12/6, PCF82 at 12/6, PCF80 at 12/6.

WAVECHANGE SWITCH, single wafer 3p. 3 way wide spacing. Price 3/-.

0-9 pf TRIMMERS—Phillips "bee-hive" type at 1/9 each.

TERMS: Cash with order or C.O.D. Extra charge for C.O.D. U.K. and N. Ireland only.

GRADIENT F.M. TUNER FMT4 (Building Cost approx. £7.5.0, plus p.p.)



- Tuned Resonator R.F. Stage.
- Ultra Stable Co-Axial Oscillator.
- Gorker I.F.T.'s and Discriminator.

This unit is a 4 valve superheterodyne comprising R.F. amplifier, oscillator-mixer, I.F. amplifier, second I.F. amplifier-limiter and ratio detector using crystal diodes. It is a highly sensitive and stable adapter covering the range 87-102 mc/s and provides an output suitable for feeding into the pick-up terminals of a normal broadcast receiver or audio amplifier. All parts available separately. Send 1/6 for Construction Booklet and Price List.

THE S.R. 3-4 WATT AMPLIFIER



Treble, Bass and Middle Tone controls. For crystal or magnetic pick-up. A.C. Mains 200/250 volt. Valve line-up: 6V6GT, 6SG7, 6X5GT. Negative feedback. Built on stove enamelled steel chassis, measuring only 8 in. x 4 in. x 1½ in. Four engraved cream knobs. Supplied assembled, tested and ready for use. Price £5.5.0, plus 2/6 p.p.

AUTOMATIC RECORD CHANGERS

B.S.R. Monarch, or latest Collaro, 3-speed £9.15.0
Garrard RC.80, 3-speed, automatic A.C. Mains £13. 0.0
Garrard RC.80, 3-speed, automatic A.C./D.C. Universal £26.10.0
Carriage and packing, 7/6 extra.

BAND III COMPONENTS SET OF ELECTRON MKII COILS, complete with wiring diagram. Price 17/6, plus 6d. p.p.

PUNCHED TINPLATE CHASSIS for use with above coils—size 7 in. long, 1½ in. high, 3 in. wide. Price 3/9, plus 1/- p.p.

COMBINED CONVERTER AND POWER PACK CHASSIS for above size 7 in. long, 1½ in. high, 5 in. wide. Price 6/-, plus 1/- p.p.

Also available—full range of Belling, Aerialite and Antiference aerials, co-axial plugs, sockets and junction boxes. Please quote type numbers.

Minimum Postage on any of the above items, 1/-.

The SUPERIOR BUREAU



An elegant cabinet in richly figured walnut veneer, internal panels in polished sycamore. A drop front lid covers a sloping, uncut control panel (16 in. long x 10½ in. high) alongside which is an uncut base-board (15½ in. long x 13 in. back to front). The inside of the drop front lid is panelled in beige leatherette. In the lower part of the cabinet are two large storage cupboards (13½ in. high, 7½ in. wide, 16½ in. deep). The lid and cupboard handles are in chased Florentine bronze. Overall dimensions (33 in. high, 34 in. long, 16½ in. deep). Price £17.0.0, plus 15/- carriage. Send for Cabinet Leaflet.

SAVE YOURSELF £ £ £'s THE "EVERYMAN" BAND III CONVERTER

Housed in a neat brown/beige rexine covered cabinet size 9½ in. long, 6 in. high, 3½ in. deep, this unit is complete and self-contained with its own power supply. Only connections required are Aerial and Mains, thereby making the installation simplicity itself. A well tried high gain circuit (suitable for all receivers) is employed ensuring excellent reception in all parts of the service area of either Channel 9 (London) or Channel 8 (Birmingham). Switching is by a single knob control on the front of the unit. The latest miniature type valves are used and each converter is supplied with full installation instructions. Fully guaranteed. No technical knowledge required.

Price £7.15.0, plus 3/6 p.p. Send for full details of other types of converters which are available ready built or in kit form.



BAND III AERIALS

We strongly recommend the use of the "LABGEAR" 301 Loft Aerial with the above converter. A most inexpensive, but highly efficient, three element array. Price 19/6, plus 1/6 p.p.

SMALL MAINS TRANSFORMERS

240 input, 180 volts at 25 m/a output. 6.3 volt at 6 amp. Price 12/6, plus 1/- p.p.

Shop open 9 a.m. to 6 p.m. Monday to Saturday. 1 p.m. Thursday. Personal Shoppers Welcome.

(PW/J) 37 HILLSIDE, STONEBRIDGE, LONDON, N.W.10. Tel.: ELGar 3644