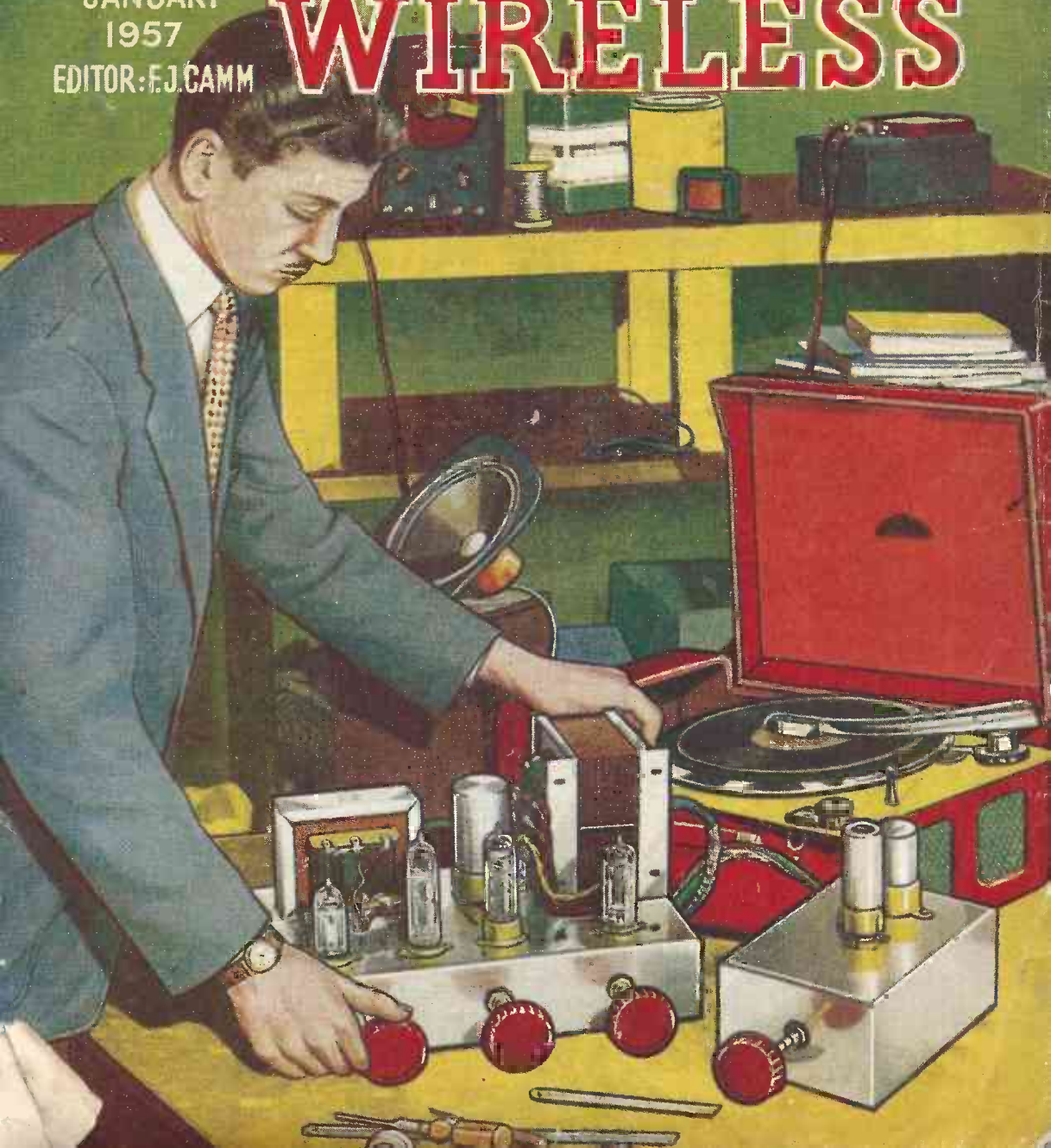


A 10 w. DIRECT-COUPLED AMPLIFIER


PRACTICAL ^{1/3} WIRELESS

JANUARY
1957

EDITOR: F. J. CAMM



MAXI-Q
REGD.

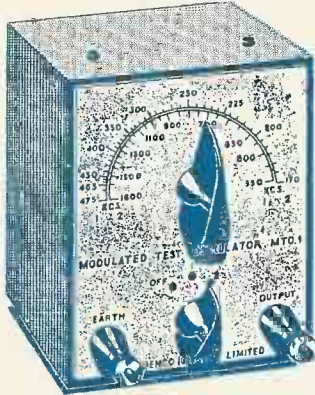

WE PROUDLY PRESENT OUR LATEST HIGH STANDARD LOW PRICED INSTRUMENT WHICH WE KNOW WILL BECOME A PRIZED AND INDISPENSABLE POSSESSION IN EVERY CONSTRUCTOR'S SHACK

MODULATED TEST OSCILLATOR MTO.1

- ★ Provides a modulated signal suitable for I.F. alignment also trimming and tracking R.F. circuits.
- ★ Frequency is continuously variable from 170-475 kc/s and 550-1,600 kc/s.
- ★ Operates from a single 9 volt grid bias battery (not supplied) which is housed within the unit.
- ★ The case is manufactured from steel and is finished in matt black cellulose. The front panel is gloss black bearing white lettering. Dimensions are $5\frac{1}{4}'' \times 4\frac{1}{16}'' \times 3''$.
- ★ Supplied with full operating instructions.

PRICE £3 . 15 . 0

Obtainable from all reputable stockists or from works. General Catalogue covering technical information on full range of components, 1/- post paid.

DENCO (CLACTON) LTD
357/9 Old Road • Clacton-on-Sea • Essex

STOP PRESS: "OSRAM F.M. TUNER" completely assembled and valved at £30.16.0.
"MULLARD TAPE RECORDER" Amplifier Chassis, Type "A" 31/6; Type "B" 31/6. Power Pack Chassis 11/6.
"MULLARD 20-WATT AMPLIFIER" Chassis and Base 34/-. Pre-Amp Chassis 25/-. Transformer Covers (3) 32/-.

"You can rely on us"

LARGE STOCKISTS OF RADIO AND ELECTRONIC COMPONENTS

H.P. on INSTRUMENTS, "912" and MULLARD AMPLIFIER KITS, SOUND-MASTER, VIEWMASTER, Etc., Etc.

RESISTORS — STANDARD, MIDGET, HIGH STABILITY, PRECISION; TAPPED VOL. CONTROLS, Etc., Etc.

SEND FOR LIST.

Proprietary catalogues available to Manufacturers' Laboratories, Education Authorities, etc.

RADIO SERVICING CO.,

82, SOUTH EALING ROAD,
LONDON, W.5.

EAL 5737

MAKE SOUND JOINTS SIMPLY BY USING Multicore

ERSIN MULTICORE

Contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON

5/-

HANDYMAN'S CARTON

Suitable for 200 average joints, 6d.



HOME CONSTRUCTORS 2/6 PACK

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloy) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

ARAX MULTICORE

FOR METAL FABRICATION

(Not wire-to-tag joints)

Contains 2 cores of Arax flux. Flux residue is easily removed with water.

SIZE 8 CARTON

5/-

Handymans Carton 6d.



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruded flex 3/16 each



MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)



FOR VALVES GUARANTEED ALL TESTED BEFORE DISPATCH

Table listing various vacuum tubes with their types, prices, and stock status. Includes models like 0Z1, 1A5, 1A7, 1A9, 1C9, 1H5GT, 1L4, 1LD5, 1N3, 1N5, 1N6, 1N7, 1N9, 1N10, 1N11, 1N99, 1N100.

TRANSFORMERS, ETC. HEATER TRANSFORMERS

Table listing transformer specifications including primary/secondary voltages, current ratings, and prices. Examples: 230 v. Input 2 v. 5 amp, 5/-; 230 v. Input 2 v. 2.0 amp, 5/3.

OUTPUT TRANSFORMERS

Multi Ratio. Suitable for all ordinary receivers, giving six single ratios. 6/6 each.

HEATED AUTO TRANSFORMERS

Designed to adapt common low tension voltages 4, 5 v., 6.3 v. at 3-amps, centre tapped and inter-changeable, each, 7/9.

TELESCOPE TRANSFORMERS TYPE TEB

SMALL MAINS TRANSFORMERS Suitable for suitable for

TELEVISION CONVERTERS, Etc. SPECIFICATION OVERALL SIZE

Primary: 230 v. Clamp Construction 50's 410n Secondary: 1250 3.5in. x 2.4in. x .40 in.A. 2in. Over Windings. Price 15/-

KNOBBS - BAKELITE LARGE PURCHASE - GOOD QUALITY

Type JK1 Cream 1 1/2in. diameter. Spring Filing. Plated Grip. Type JK2 Brown 1 1/2in. diameter. Spring Filing. Plated Grip. Type JK3 Brown 1 1/2in. diameter. Spring Filing. Plain Grip. (This one has White Ring on Knob Face). All have a small finger flange to avoid marking table top.

MAINS TRANSFORMERS 3-way Mounting Type

Table listing mains transformer specifications: Primary: 200-220-240 v., Secondary: 250-0-250 v., 80 M.A., 0-6.3 v. 4 amp, 0-4 v. 2 amp, both tapped at 4 v., each. Price 19/8.

Table listing various electronic components like valves and transformers with their part numbers and prices. Includes models like VRS5, VRS6, VRS7, VRS8, VRS9, VRS10, VRS11, VRS12, VRS13, VRS14, VRS15, VRS16, VRS17, VRS18, VRS19, VRS20.

COMMERCIAL ALPHA CONVERTOR Price: 45.15.0

- *Tunable over Band III Range. *Single Knob Channel Changing. *4-Valve Circuit. *Hammer-Tone BRIDGE Finish. *NOTE THE PRICE: 45.15.0. Fully Guaranteed against Faulty Workmanship or Materials (other than valves) for 12 Months.

Our 1956/57 44 page Catalogue is now available. Please send 1/- in stamps.

SWITCHES

Table listing switch specifications: WAVE CHANGE SWITCHES, ETC. 3 pole, 3 way: 2/9 each; 4 pole, 3 way: 2/9 each; 4 pole, 1 way: 1/9 each; 4 pole, 12 way: 2/9 each; 2 pole, 6 way: 1/9 each; TRF Switch 2 pole Change: 1/8 each; 3 pole, 3 way: 2/9 each; 2 pole, 5 way, 3 bank, 1/9 each; 4 pole, 2 way, 3 bank, 1/9 each; 4 pole, 2 way, 1/9 each; Xaxley Type, 1 pole, 9 way 1/9 each; Xaxley Type, 2 pole, 3 way 1/9 each; Xaxley Type, 4 pole, 3 way: 2/8 each; 2 bank: 1/8 each; We have large stocks of Xaxley Type Switches. ALL BRAND NEW. With Long Locating Spindles. Various numbers of switch and Water Combinations. To call for the SPECIAL PRICE, 9/- Per Dozen, Post 1/6.

HEADPHONES - MICROPHONES

CHR Low Resistance type 120 ohms - 7/6; Throat Microphones, American surplus. Complete with strap, lead and plug type 30B. 3/- set; High Resistance Phones, 4,000 ohms. Complete with Jack plug. 13/6; High Resistance DLR Phones 15/-

PUBLICATIONS

- No. 134 - F.M. TUNER CONSTRUCTION by W. J. May. *Easy to Build, Point-to-Point Wiring *Super High Fidelity Response *22 Pages *All Components for This Circuit available ex stock... No. 135 - ALL DRY BATTERY PORTABLE CONSTRUCTION. *8 Simple and cheap to build *A Point-to-point wiring *Dual Points-aerial for high sensitivity... No. 100 - A COMPREHENSIVE VALVE GUIDE Book No. 1. No. 121 - A COMPREHENSIVE VALVE GUIDE, Book No. 2 (Characteristics and Base Connections... No. 102 - RADIOFOLDER "A" The Master Colour Code Index for Radio and Television... No. 114 - RADIOFOLDER "B" An inexpensive Type Resistor... No. 128 - PRACTICAL TRANSISTORS and TRANSISTOR CIRCUITS... No. 100 - PRACTICAL F.M. CIRCUITS FOR THE HOME CONSTRUCTOR... No. 140 - T.V. SERVICING FOR BEGINNERS... No. 142 - MODERN T.V. CIRCUITRY AND GENERAL FAULT FINDING GUIDE... SERVICING THE MODERN RADIO RECEIVER... Price include ad. postage per copy.

CHOKES


Table listing choke specifications: 20H, 250 ohms, 60 M.A. Clamp construction, each 8/-; 10H, 200 ohms, 30 M.A. Clamp construction, each 5/6; 10H, 200 ohms, 150 M.A. Clamp construction, each 13/-; 10H, 200 ohms, 30 M.A. Midget Clamp construction, each 5/3.

TRANSFORMERS FOR BATTERY CHARGERS

230 v. Input Tapped 0-12 v. 1 amp, each 19/8; 230 v. Input Tapped 0-12 v. 3 amp, each with tap on Primary for 2.5 v. Pilot light, each 18/-

LOUD SPEAKERS All P.M. Types Less Transformer

Table listing speaker specifications: WATERHOUSE 5in. Unit: 17/6; PLESSEY 6in. Unit: 18/6; R. & A. 8in. Unit: 18/6; PLESSEY 12in. Unit: 35/-; LECTRONA 5in. Unit: 17/6; GOODMANS 6in. Unit: 18/6; GOODMANS 8in. Unit: 19/6; GOODMANS 4in. x 7in. Unit: 19/6; R. & A. 6in. Unit (with Energised 600 ohms field) 17/6; PLESSEY 5in. Unit (with Energised 600 ohms field) 21/-; GOODMANS or LECTRONA 8in. with Output Transformer: 21/8

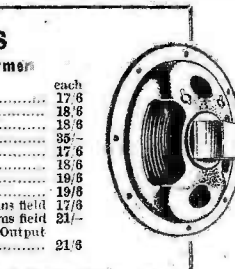

PACKING AND POSTAGE, 6d. per valve

SAME DAY SERVICE.

ALPHA RADIO SUPPLY CO. logo with a stylized 'A' and 'ALPHA' text.

5/6 VINCES CHAMBERS VICTORIA SQUARE LEEDS I.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. All single valves posted 6d. per valve. MAIL ORDER ONLY


LASKY'S RADIO

LASKY'S BATTERY PORTABLE FOR HOME CONSTRUCTION ON PRINTED CIRCUIT

CAN BE BUILT FOR

7 GNS.

Car. & Packing 3/6 extra.

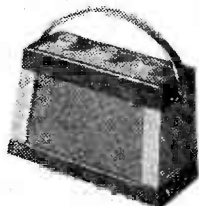

10 Star Features make this the finest Portable Radio ever offered to the home constructor. Extremely simple to build—the printed circuit eliminates wiring errors. SEND FOR CIRCUIT DIAGRAM, assembly data, all instructions and shopping list. 1/6 post free.

*** YOU CAN BUILD A POWER UNIT FOR THIS PORTABLE RADIO.** Complete Kit containing printed circuit, all components, full instructions, 45/-. Full details on request. Also suitable for other battery portables.

NOW! A FIRST CLASS F.M. TUNER FOR HOME CONSTRUCTION ON PRINTED CIRCUIT

Note these star features:—

- ★ High Sensitivity.
 - ★ All Brand New T.C.C. Condensers.
 - ★ Aerial Coil and R.F. Coupling Coil Printed on circuit.
 - ★ 5 Valves & 2 Germanium Diodes.
- By the use of a printed circuit the I.F. and R.F. amplifiers are extremely stable at maximum gain and results are consistent on all tuners.

Valve line-up:—

- R.F. Amplifier, Z719 or EF80.
- Mixer and Osc., B719 or ECC85.
- 1st I.F. amp., W719 or EF85.
- 2nd I.F. amp. W719 or EF85.
- 2 Germanium Diodes GEX.34.
- Driver Limiter, Z719 or EF80.



CAN BE BUILT FOR

8 GNS. approximately.

Full instructions, data, and illustrations, 2/6 post free. All parts available separately.



BARGAINS IN RECORD PLAYERS

- GARRARD RC.110, 3-spd., auto-changer. £7.19.6. Car. 3/6.
- COLLARO RC3/554, 3-spd., single player. £6.10 post free.
- B.S.B. TU8, 3-spd., single player, £2.6, post 3/6.

MAIL ORDERS TO HARROW ROAD, PLEASE

LASKY'S (HARROW ROAD) LTD.

42, TOTTENHAM COURT ROAD, W.1.
Telephone: MUSEum 2605.

370, HARROW ROAD, PADDINGTON, W.9.
LADbroke 4075 and CUNNINGHAM 1979.

Open all day SATURDAY. Half day Thursday.

TV • VALVES • RADIO

6J5	5/-	7C5	8/6	EF50	4/-
6J7	7/6	5Z4	8/6	EF54	5/-
6V6	8/6	5U4G	8/6	EF91	8/6
6K7	6/-	80	9/-	EF37A	
6K8	11/-	VU39	8/6		
6SN7	8/6	5Y3	8/6	EL32	6/-
6SL7	8/6	8D2	3/6	EL91	5/6
6SK7	4/6	12A6	7/-	EY51	13/6
6SJ7	7/6	12AH7		EZ80	8/6
6SG7	7/6		12/-	HL23DD	8/6
6N7	8/6	12AT7		ECC81	10/6
6AL5	7/6		10/6	ECC82	10/6
6J6	7/6	12AU7		ECC83	10/6
6C4	6/-		10/6	ECC84	12/6
6X5	7/6	12AX7		ECC85	10/6
6X4	7/6		10/6	ECL80	10/6
6AG7	9/-	12SH7		PCC84	10/6
6AK5	6/6		7/6	PCF82	12/6
6AG5	6/6	12Q7	9/-	Pen46	6/6
6AJ5	7/6	12K7	7/6	U25	15/6
6AC7	5/6	35Z4	8/6	IR5	8/6
6H6	2/6	28D7	9/-		
6A7	11/6	21D2	9/6		
6B4	6/-	807	7/-		
6Y6	8/6	832	22/6		
6U4	15/6	954	4/-		
6L6	12/-	955	5/-		
6AM6	8/6	EF36	4/-		
7H7	8/6	EF39	7/6		
7Y4	8/6	EF42	12/6		

R1155 RECEIVER

EX R.A.F.

NICE CONDITION **£6** AIR-TESTED
10/- Carriage.

POWER UNIT

For above RX, with 6V6 output stage. Input 200-250 A.C.

£4 Carriage 5/-

BENDIX TA 12G TX

£4.10.0

New condition. With 3 807, 4 12SK7 Valves. A Bargain while they last.

TELEPHONE HANDSETS

Sound-powered, no batteries required.

£1 Per Pair.

DYNAMOTORS

Ex U.S.A. Surplus, new condition.
Input 28 v. D.C. 1.6 amp. **£1**
Output 230 v. D.C. 100 mA.
Input 27 v. D.C. 1.4 amp. **22/6**
Output 285 v. D.C. 60 mA.

CONDENSERS

100 Assorted 1, mfd. 5 pF. 15/-.

RESISTORS

100 Assorted 1, 1/2, 1, 2 watts, 12/6.

METERS

8 Assorted m/i, m/c, T.C. £12.6

30, 50, 100, 200, 300, 500 mA. Meters, 5/6 each. 1.5 kV. Electrostatic, 12/6. 250-0-250 micro-amp., £1. 0-500 micro-amp. Meter, 15/-.

TELESCOPIC AERIALS

Extend from 12in. to 14ft., 8/-.

CONDENSERS.— Electrolytic. 450 volt working. 8 mfd.; 2/6; 16 mfd., 3/3; 8+8 mfd., 3/9; 20 mfd., 3/-; 8+16 mfd., 4/6; 16+16 mfd., 4/6; 32+32 mfd., 6/-; Bias, 25/25, 50/50, 2/- each.

POTS.—W/W or Carbon to 2 meg., 2/6 each. with Switch, 100 K., 1, 1/2, 1, 2 meg., 4/- each.

SP41, SP61, RK34
2/6 each.

VINERS

(MIDDLESBROUGH)

26, East St., Middlesbrough

TEL.: 3418.



KT88

A NEW AUDIO OUTPUT VALVE WITH AN ANODE DISSIPATION OF 35 WATTS




An addition to the well-tried and popular range of G.E.C. Audio Valves, of which the KT66 has set a standard in its class the world over, the new G.E.C. KT88 is now available to meet conditions of use requiring higher power.

POINTS ABOUT THE KT88

- 1 The KT88 is a beam pentode with aligned grids for maximum efficiency.
- 2 50 watts output is available from a pair connected in the ultra linear circuit with auto bias and an H.T. line voltage not exceeding 500.
- 3 100 watts output is available from a pair connected in the ultra linear circuit with fixed bias and an H.T. line voltage not exceeding 560.
- 4 25 watts output is available from a pair triode connected with auto bias and an H.T. line voltage not exceeding 500.
- 5 The mutual conductance of the KT88 is 11 mA/V.
- 6 An all glass ring seal replaces the conventional pinch seal giving increased strength, higher rating and reduced dimensions.
- 7 The valve is mounted on an international octal base and has a heater rating of 6.3 volts., 1.8 amps.

Full particulars of these valves can be obtained from the G.E.C. VALVE & ELECTRONICS DEPT.

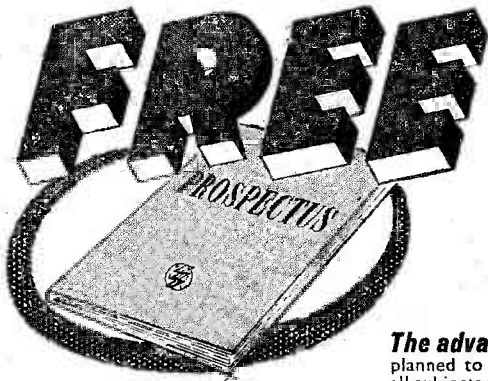THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY
 With many of our courses we supply actual equipment. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from 15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book, E.M.I. INSTITUTES, Dept. 32K, 43 Grove Park Road, London, W.4. Phone: Chiswick 4417/8.

NAME _____
 ADDRESS _____

 JAN. _____
 SUBJECT(S) OF INTEREST _____

EMI INSTITUTES
 The only Postal College which is part of a world-wide Industrial Organisation



INFRAY LAMP

Means real comfort in bed as it emits Infra Red Rays which warm and keep you healthy.

- Economical.
- Costs only 1d. per hour (electric at 1d. per unit).
- Absolutely safe, no health or fire risk.
- Ideal for many other uses—over pet's basket, rearing pup, chicks, over desk, work bench, etc.
- All complete and ready to work.

Price 36/-

Post & Packing 2/-



F.M. TUNER


This tuner is based upon the very successful circuit published by Data Publications. We have made up models at all branches and will gladly demonstrate. Stability is extremely good and making and aligning most simple. Cost of all parts, including valves, prepared metal chassis, wound coils and stove enamelled scale, slow-motion drive, pointer, tuning knob. In fact, everything needed is 46/12/6. Data is included free with the parts or is available separately, price 2/-. Extra for fringe area model, 20/-.

SOMWEAVE




This really lovely loud-speaker we offer at approximately a third of to-day's cost. It is 4 1/2 in. wide and our price is 12/- per yard of panels 12 in. x 12 in., 1/9 each. This is also very suitable for covering plain wooden cases, for portable radio amplifiers, etc.

The "ESTRONIC" Band III Converter

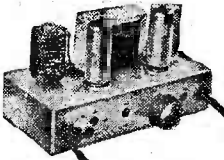

To-day's best value in Band III converters suitable for your T.V. or money refunded. Complete ready to operate, 49/6 non-mains or 69/6 mains, post and insurance 3/6.

CABINETS FOR ALL

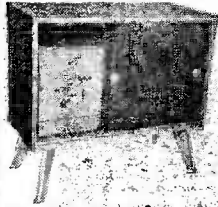

The CONTINA

Another addition to our range of cabinets. This is of new revolutionary design, styled after the best of continental radios. Externally, it is finished in highly polished dark walnut veneer, with pagelling picked out in gold. Interior is of same very high standard, its veneer being light mahogany which contrasts nicely with the dark walnut and generally gives a very pleasing appearance. The doors slide on metal runners and are fitted with gold-inset finger plates. A really excellent cabinet for any home—size 3ft. 1 1/2 in. long, 1 ft. 3 in. deep, 2ft. 1 1/2 in. high, including legs which are 10 in. from floor. Motor board 12 1/2 x 17 in. equipment aperture 17 1/2 x 9 in. gives ample space for 6 in. speaker. Ample storage space for recordings. Price £19.19/-, carriage and insurance 20/-.



TRANSISTORS


Red spot replaces Mullard OC71, etc., 10/-.
Blue spot suitable R.F. up to 1.6 Mc.s, 15/- each.



POCKET TRANSISTOR RECEIVER


All the parts to build cigarette box receiver, £2.17.6, includes Ferrite aerials but not the earpiece, battery or case.

RADIO SCALES 6/6 DOZEN

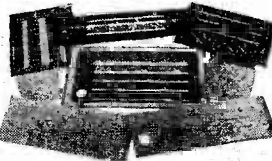

An exceptional bargain this month is our assorted parcel of radio scales. A most useful collection for all who make up experimental or other radios. We offer twelve assorted scales mostly in two or three colours for 6/6, plus 2/6 post and packing. Limited quantity only.

INSTANTUS HEATER

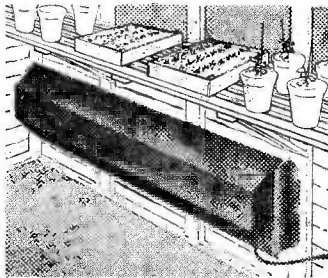

Practical Convectocor heater 1 kW. 4ft. long, made from heavy gauge sheet steel (galvanised). Can be used for any size house, up to three heaters can be controlled by one thermostat. Price £2.10.0 or with thermostat £4.5.0, carriage 5/-.



Wrap our heater cable around the pipes in your loft to prevent a freeze up. 21 yards with full instructions; 30/-, plus 1/- post and packing.

COMPONENT BARGAINS

1 mfd. 350-volt metal cased condensers by Dubilier—small size 3/6 doz. or 36/- gross.

Philips Trimmers 0-30 pf. 1/- each or 11/- doz.


Moulded Mica Condensers, well mixed assortment 8/- doz., 30/- gross.

Silver Mica, well mixed assortment, 3/- doz., 30/- gross.

50 mfd. 50 v. Bias Condensers T.C.C. 1/6 each, 15/- per doz.

Ceramic Trimmers, 5 to 30 pf., 6d. each, 5/- doz., 20 to 80 pf., 9d. each, 8/- doz., 20 to 100 pf., 1/3 each, 12/- doz.

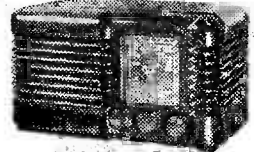Earpiece microphone. American midget type 3/6 each, 36/- doz.



NEW CIRCUIT

OCCASIONAL 56. We have evolved a new T.R.F. circuit and have had really good results, equal in fact to many superhets. You really should try this circuit. All parts including valves (6K7, 6J7, 6F6 and 6X5) and bakelite case with back cost only £5.10/-, plus 2/6 post and insurance. Data included with the parts is also available separately, price 2/-.

DON'T STUMBLE IN THE DARK




Install 2-way switches. Our outfit comprises: 30 yds. Multi-core cable, two 2-way switches, two wood blocks. Full instructions, 19/6 each (post and insurance 2/6).

ELECTRIC BLANKET WIRE

Waterproof P.V.C. covered, so blanket washable. 18 ohms per foot—1/6 per yard. 14 yards, ideal for average blanket, £1 post free.

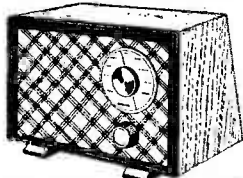THE SKYSEARCHER
An all mains set for 19/6




This is a 2-valve plus-metal rectifier set useful as an educational set for beginners, also makes a fine second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker, 19/6. Post & ins. 2/6. Data free with parts or available separately 1/6. 8-valve battery version also available at the same price.

FLUORESCENT LIGHTS



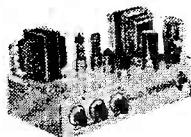These are a complete fluorescent lighting fitting. Built-in ballast and starters—stove enamelled white and ready to work. Ideal for the kitchen, over the workbench and in similar locations.
Single 40. 4ft. 3in. long, uses a 40 watt tube. Price 39/6 complete with tube. Carriage and ins. 5/6.
Twin 20. Uses 2 20-watt standard tubes. Price 29/6 less tubes. Carriage and ins. 4/6.



MULLARD AMPLIFIER "510"


A Quality Amplifier designed by Mullard. Power output exceeds 10 watts. Frequency response almost flat from 10 to 20,000 C.P.S. For use with the Acos "Hi G" and other good pick-ups. Made up and ready to work is £12/10/- or 85/- deposit, plus 10/- carriage and insurance.

19/6 AMPLIFIER



Construct a powerful three-valve mains amplifier. Ideal for dances, parties, etc. Complete less chassis, cabinet and speaker (available if required). Data 1/6 (free with parts).

THE UNI-T.V.

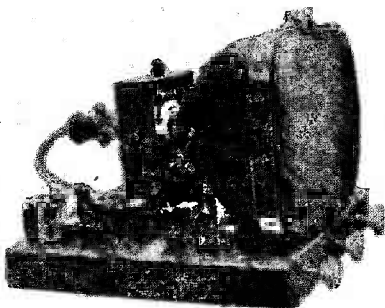

Undoubtedly the most up-to-date television for the home constructor. You can build all or only part and the set when finished will be equal to a factory-made equivalent. What other constructor T.V. has all these features?

- ★ Made up units if required.
- ★ All miniature valves.
- ★ Metal rectifier.
- ★ No expensive transformers.
- ★ 13-channel circuitry.
- ★ Multi-vibrator time bases.
- ★ Ferruxcube, E.H.T. and scan coils.
- ★ 34/38 Mc/s I.F.
- ★ Suitable for any modern 12, 14 or 17in. tube.
- ★ Modern contemporary cabinet if required.

The building cost (less tube) is only £31/10/0, plus 10/- carriage and insurance. All parts guaranteed 12 months. Full information and data free with parts or available, separately, price 3/6.

T.V. Commercialising Outfit

Do it yourself—it's really quite easy.

You will manage it in an evening and we guarantee


SUCCESSFUL RESULTS OR MONEY BACK

- Our parcel contains:—
I.T.A. Aerial £2/5 0
3ft. I.T.A. Down
Lead 12/-
I.T.A. Converter £6/0 0
Full instructions 1/6

A special bargain price for all the above items if bought together is £8/10/- (Post and Insurance 4/6) Or £2/10/- down and 7 payments of £1.



THERMOSTATS

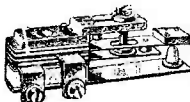

Useful for the control of appliances such as convector, glue-pots, vulcanisers, hot plates, etc. Adjustable to operate over the temperature range 50-550 deg. F. 1) amp. 3/6; 5 amp. 8/6; 2 amp. QMB, 5/6; 15 amp. QMB, 15/-.

CHASSIS ASSEMBLY



Supernet Chassis, 3-waveband, coloured scale scale pan, pulleys, driving head, springs, drum etc. Scale size 14 1/2 in. x 3 1/2 in. Chassis size 15 in. x 15 in. x 2 in. Price 15/- plus 1/6 post. Note: We can supply cabinet for this. Price 39/6 plus 5/- carr. and insurance.

MAINS-MINI



Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet, valves in fact, everything, £4/10/0, plus 3/6 post. Constructional data free with the parts, or available separately 1/6.

HUGE MINISTRY PURCHASE
R.1155—yours for £2 down.

Frequency 75 kc/s to 13 mc/s—10 valves—metal case—robust receiver

—cost over £60 to make—will give years of service, very little used.



Price £10 or 5 payments of £2. Carr. & transit case 15/- ex.

CAR STARTER CHARGER KIT

All parts to build 6- and 12-volt charger which can be connected to a "flat" battery and will enable the car to be started instantly. Kit comprising the following:—
Mains transformer 19/6
5-amp. rectifier 17/6
Regulator Stud Switch 3/6
Resistance wire 2/-
Resistance Former 2/6
Mains on/off Switch 1/-
0.5 amp. Moving Coil Meter 9/6
Constructional Data 1/6
or if bought all together price is £2/6, plus 2/- post and packing.

T.R.F. CONVERTER

New this month is a converter for T.R.F. Set Viewmaster Electronic Engineering, etc. Small mods. to the T.V. are necessary as this must be turned into a superhet to stop re-radiating. Price complete with two valves £6/10.0 assembled.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to E.P.E., LTD., Dept. 7, Sutton Road, Eastbourne.

Personal shoppers to one of these addresses please.


266, London Road, Croydon.
Half day, Wednesday.

42-46, Windmill Hill, Mids.,
Phone: RU1SLIP 5780
Half day, Wednesday.


152-3, Fleet Street, E.C.4.
Phone: FE1Est 2833
Half day, Saturday.

29 Stroud Green Rd., Finsbury Park, N.4.
Phone: ARChway 1049
Half day, Thursday.

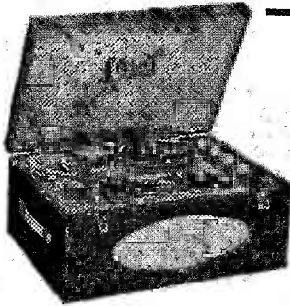249, Kilburn High Road, Kilburn, MA1da Vale 4921.



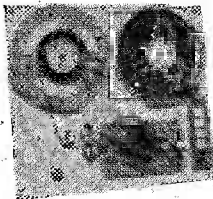The Truvox Tape Deck and the Quality Amplifier are supplied tested and ready for use. The actual assembly of the Recorder is simple and only involves a few connections (a connection chart is supplied for this purpose). The items illustrated and described form the complete equipment and each are available for sale separately.



TRUVOX TAPE DECK MODEL Mk. 111 TR7/u

This is Truvox's new small" design, being only 14in. x 13in. The whole instrument is built to close engineering limits resulting in the minimum of "wow" and "flutter" values. It will play the NEW PRE-RECORDED TAPES and takes all standard tapes up to 1,200ft.

UNDOUBTEDLY THE BEST VALUE YET OFFERED

Stern's "fidelity" Tape Recorder

ASSEMBLED & READY FOR USE £43

(Plus £1.10.0 Carr. and Insurance. £1 is refunded when packing case is returned to us.)
Terms £21.10.0 deposit and 12-monthly payments of £1.10.10 or £11.0.0 deposit and 9 months of £3.13.3

IMMEDIATELY AVAILABLE TO MAIL ORDER CUSTOMERS

!! HOME CONSTRUCTORS !!
YOU CAN BUILD IT YOURSELF FOR £40

MODEL TR/F QUALITY AMPLIFIER

This amplifier has been expressly designed to meet the requirements of particular to CORRECTLY operate the above TRUVOX DECK. It is supplied complete with a matched Elliptical 3 ohms P.M. Speaker. It incorporates an efficient Tone Control arrangement and has a Magic Eye Level Indicator (Operative on Record). It can also be used as a general purpose Amplifier for high quality reproduction of gramophone records direct from a Gram Unit.
Price £14.14.0.



PORTABLE ATTACHE CASE
Neat, compact and attractively finished. It contains concealed pockets for Mike, Mains Lead and reel of tape.

SEND S.A.E. FOR DESCRIPTIVE
LEAFLET INCLUDING PRICE
DETAILS & H.P. TERMS

SCOTSBOY MAGNETIC RECORDING TAPE Supplied complete with a 1,200ft. reel of Scotsboy Tape. Price 35/- MODEL MIC33/1 ACOS CRYSTAL MICROPHONE

A highly sensitive Mike which accurately matches the input arrangement of the Amplifier. Price £2.10.0.

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4

Tel.: FLEet 5812-3-4.

TRANSISTOR PUSH-PULL AUDIO AMPLIFIER

(100 Milliwatts Output)
Build this Push-Pull Amplifier which is ideal for Crystal or Magnetic Pick-up Amplification: Baby Alarm, Microphone Amplifier, etc. Powered by 6-volt Dry-Battery lasting for months.

Complete Kit of Parts including 4 Transistors and all Components with Circuit (less speaker), £4.10.0

TRANSISTOR SQUARE WAVE GENERATOR

Ideal for signal tracing. Complete Kit with 2 Transistors and Components and Circuit, 25/-.

TRANSISTOR SIGNAL TRACER

Complete Kit with 2 Transistors, Components and Phones with Circuit, 42.6.

CATHODE RAY TUBES

VCR138A £1.15.0.
VCR139A, 2in. £1.15.0.
VCR197, Guaranteed full T.V. picture (carr. 2/-) £2.0.0.

VCR517C, Guaranteed full T.V. picture, £1.15.0.
M-METAL SCREENS

For VCR97 or 517, 10/-.
6in. ENLARGER for VCR97 or 517, P.P. 1/6, 17.6.

TRANSISTORS

JUNCTION TYPE (Red-Spot) (P.N.P.)
OFFERED AT LESS THAN HALF-PRICE.

Designed for A.F. application up to 800 Kc/s and are suitable for use in amplifiers, Signal Tracers, Local Station Receivers, Radio Control, Oscillators, Transistor Voltmeters, Baby Alarms, Microphone Pre-Amplifiers, etc.

10/- EACH

(Tested and complete with Data & Circuits)

N.B. These Transistors may be used in place of Mullard OC71 or similar Transistors.

R.F. TRANSISTORS (BLUE SPOT) 1.6 Mc/s 15/- each.

PRE-SELECTED TRANSISTOR-SIX PUSH-PULL PORTABLE SUPERHET

Just switch to your favourite Station. No tuning, no aerial or earth. Pre-select 3 stations. Complete with all components and six Transistors. 7 x 4 Elliptical speaker. Teleton Superhet Coils and I.P.T.S. Powered by 7.5 v. dry battery which lasts for months. 150 Milliwatts output. All the above with Circuits, etc. Ready to assemble. £9.0.0.

Or with Matched Mullard OC72's (200 Milliwatts Output) and 7 x 4 Elliptical High Resistance Speaker 30/- extra.

Suitable Plastic Cabinet. Easy to assemble 18.6.

Call and hear demonstration model workings.

Please note that these Red Spot Transistors are ideal for most circuits including "W.W." Pocket Transistor Receiver and Transistor Amplifier. All Transistors are British Manufactured and Guaranteed. Send for Circuits and Data.

INDICATOR UNIT TYPE 182A

Unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-Metal screen 5-EP50, 4-SP61 and 1-5U4G Offered BRAND NEW (less relay), at 67/6. Plus 7/6 carr. "Radio-Constructor" scope circuit included.

62A INDICATOR UNIT

Containing VCR97 with Mu-Metal Screen, 21 Valve 12-EP50, 4-SP61, 3-EA50 2-EB94, Plus P.T.S., Switches, H.V. Cond., Resistors, Muirhead S/M Dial, Double Deck Chassis and Crystal. BRAND NEW ORIGINAL CASE, 67.6. Carr. free.

1955 RECEIVER


Complete with 11 valves 4-SP61, 5U4G, VU120, VU92, 4-SP61. Guaranteed for inexpensive T.V.
In absolute new condition, 27/6, carr. 5/-
R.F. 24 10/- R.F. 25 12.6.
R.F. 26 25/- Brand new with valves, carr. 2.6.

MINIATURE I.F. STRIP TYPE "373" 9-72 MEG.

Brand new miniature I.F. Strip size 10 1/2in. x 2 1/2in. x 3in. high. Valve line-up: 2-EP92; 3-EP91 and EB91. With circuit.
With valves 45/- (less valves 8/- Post free.)

HENRY'S
(RADIO LTD.)

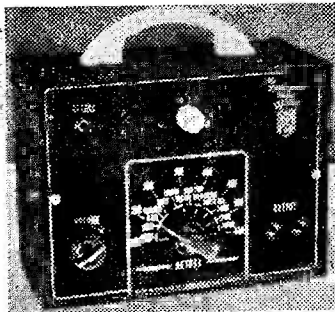BEGINNERS!—BUILD A CHEAP EASY-TO-MAKE SET



47/6

Build this exceptionally sensitive double triode radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes.


Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all Medium and Long waves—uses one only all-dry battery. H.T. consumption only 1 to 1.5 mA. Uses personal phone. Ideal for Bedroom, Garden, Holiday, etc. Many unsolicited testimonials. Mr. Norton of Oxford, writes: "Yesterday evening on the Medium wavelength I counted 32 separate stations. I am very pleased with the set, which is well worth the money. BUILD THE "SKYROMA" NOW! Total building cost—Everything down to 1st nut and bolt—47/6 (Postage, etc. 2/-) with full set of clear, easy-to-follow plans. (Parts sold separately. Priced Parts Lists, etc., 1/6.)

LOOK!




BUILD THIS POCKET RADIO FOR ONLY 37/6

AT LAST! In response to many requests we now present the **DOUBLE TRIODE "SKYPOCKET"** a beautifully designed precision **POCKET RADIO**. No radio knowledge needed!—**EVERY SINGLE PART TESTED BEFORE DESPATCH**; our simple, pictorial plans take you step-by-step. This set has a remarkable sensitivity due to painstaking design. Covers all medium waves 200 to 550 Metres. Size only 5 1/2 in. x 3 in. x 2 in. In Strong, Transparent case with panel, cover and ivoryine dial. A really personal-phone, pocket-radio **WITH DETACHABLE ROD AERIAL**. Self-contained all-dry battery operation. Average building time 1 hour. **Total Building Cost—including Case, Double Triode Valves, etc., in fact, everything down to the last nut and bolt—ONLY 37/6**, with plans. Postage, etc., 2/- C.O.D. 1/6 extra. (Parts sold separately. Priced Parts List, etc., 1/6.) Demand is certain to be heavy—so **SEND TODAY!**

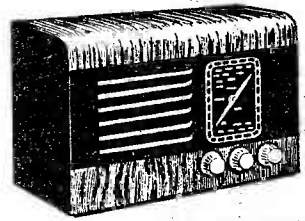

107/6

Total building cost including choice of beautiful walnut veneered cabinet or ivory or brown bakelite. This is the **lowest possible price consistent with high quality.** No radio knowledge whatever needed... can be built by anyone in 2-3 hours, using our very simple easy-to-follow diagrams. The terrific new circuit of the "**OCEAN-HOPPER**" covers all medium and long waves with optional negative feedback, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple easy-to-follow plans—in fact, everything! All parts sparkling brand new—no junk! Every single part tested before despatching. Uses standard octal-base valves: 6K7G high-frequency pentode feeding into 6J5G anode-bend detector triode, coupled to 6V6G powerful output beam-power tetrode, fed by robust rectifier. For A.C. Mains, 200-250 Volts (low running costs—approximately 18 Watts!). Size 12 in. x 6 in. x 5 in. **Build this long range powerful midget NOW.** All parts and set of plans, 25.7.6. (Post and packing 3/6.) Parts sold separately. Priced Parts List, 1/6.

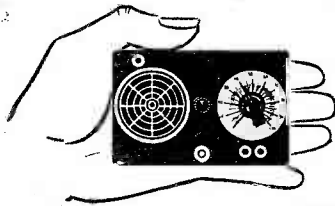

WE'VE DONE IT AGAIN! our design department in response to a great many requests have designed this "**SKYPINIE**" Vest-Pocket **TRANSISTOR RADIO** which gives a superb performance. It is powerful and highly sensitive. Size only 4 1/2 in. x 3 in. x 1 1/2 in. weight under 7 ozs. —yet it is a **TWO-STAGE** receiver covering all medium-waves, working entirely off a tiny "penlight" battery, which costs 6d.—fits inside the case—and lasts many months. Uses personal phone and has push-button **LUMINOUS On/Off Switch**. Every part tested before despatch! **SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS.** Total building cost including case, transistors, etc., everything down to the last nut and bolt—**ONLY 57/6** with plans. Postage, etc., 2/- C.O.D. 1/6 extra. (Parts sold separately. Priced parts list, etc., 1/6.) As the building cost is absolutely "rockbottom" (it might increase later) **DEMAND WILL BE VERY HEAVY—SO SEND TODAY!**


CAN BE BUILT FOR 57/6

BUILD THIS 'FRYING-PAN' SET FOR


ONLY 77/6

BUILD YOUR MOTHER OR WIFE this 'Frying-pan' radio! Highly sensitive circuit covering all Medium and Long-Waves.

Has normal size speaker and gives excellent tone due to wall "baffle" effect. Costs only 1d. for about 75 hours use. Ideal for the kitchen, bedroom, etc. Robust design. For A.C. mains 200-250 volts. **TOTAL BUILDING COST** including mirror-finish frying-pan, double-triode valves, step-by-step beginner's plans, nuts, bolts, etc., **ONLY 77/6**, Postage, etc., 2/6. C.O.D. 1/6 extra. (Parts sold separately. Priced parts list, etc., 1/6.) **PRICES MAY GO UP!—SEND NOW.**

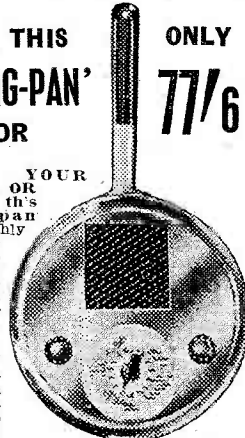

BUILD THE 'MINIATOM' FOR 59/6

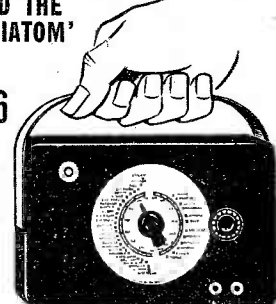

INTRODUCING THE 'MINIATOM'—to fill a big need! An exceptionally powerful all-mains one valve. Size only 6 1/2 in. x 4 1/2 in. x 3 1/2 in. **NO AERIAL OR EARTH NEEDED!** Costs approximately 1d. for 250 hours use. Uses latest contact-cooled rectifier and works headphones—completely hum-free—for personal listening, hear all the Continental programmes in bed without disturbing others—it has **LUMINOUS** push-button on/off switch and station printed dial. For A.C. mains 200-250 volts. Covers all Medium-Waves (provision for including Long-Waves). **REALLY LOW BUILDING COST OF ONLY 59/6**, including Case, Valve, Nuts, Bolts, Step-by-Step Beginner's Plans, etc.—**EVERYTHING!** Postage, etc., 2/6. C.O.D. 1/6 extra. (Parts sold separately. Priced parts list, etc., 1/6.) **THIS WILL BE A WINNER—SO SEND NOW!**



CONCORD ELECTRONICS
69, PRESTON STREET BRIGHTON

Dept. PWE

Orders dispatched by return of post. Cheques accepted. Cash on delivery 1/6 extra. Suppliers to Schools, Universities Establishments. Complete range of components and valves stocked. **CALLERS WELCOME!** Shop Hours: 9 a.m. to 6 p.m. (1 p.m. Thursdays).

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. MAINS 200-250 v., 50 c./cs. Guaranteed 12 months.

ASSEMBLED CHARGERS

- 6 v. 1 amp 19/3
 - 6 v. or 12 v. 1 amp. 25/3
 - 6 v. 2 amps. 28/3
 - 6 v. or 12 v. 2 amps. 33/3
 - 6 v. or 12 v. 4 amps. 56/3
- Above ready for use. Carr. 2/9. With mains and output leads.

HEAVY DUTY KIT

12 v. 30 amp. Suitable for Garage or firm with a number of vehicles. Mains input 200/250 v. 50 c/s. Outputs 12 v. 15 amp. twice. Consists of Mains Trans. 2 Metal Rectifiers. 2 Meters. 4 Fuses. 4 Terminals. 2 Rheostats and circuit. Only 9 gns., carr. 15/3.

BATTERY CHARGER KITS

- Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuse holders. Grommets, panels and circuit. Carr. 2/6 extra.
- 6 v. or 12 v. 1 amp. 22/9
- 6 v. 2 amps. 25/9
- 6 v. or 12 v. 2 amps. 31/6
- 6 v. or 12 v. 4 amps. 49/9

BATTERY CHARGER KIT

Consisting of F.W. Bridge Rectifier 6/12 v. 5 a. Mains Trans. 0-9-15 v. 6 a. output and variable charge rheostat with knob. Only 45/9.

ASSEMBLED CHARGER

- 6 v. or 12 v. 2 amps.
- Fitted Ammeter and selector and selector plug for 6 v. or 12 v. or 12 v. Louvred metal case, finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Only Carr. 3/6. **46/9**



Assembled 6 v. or 12 v. 4 amps. Fitted Ammeter and variable charge selector. Also selector plug for 6 v. or 12 v. charging. Double fused. Well ventilated steel case with plus hammer finish. **69/9**
Ready for use with mains and output leads. Carr. 3/6.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and impregnated. Primaries 200-250 v. 50 c/s. Screened. **TOP SHROUDED DIP THROUGH**
250-0-250 v. 70 mA. 6.3 v. 2.5 a. 13/9
250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 16/9
300-0-300 v. 70 mA. 6.3 v. 2.5 a. 16/9
300-0-350 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 22/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 22/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 22/9
350-0-350 v. 100 mA. 6.3 v. 4 a. C.T. 0-4-5 v. 3 a. 23/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 29/9

F.H.T. TRANSFORMERS
2,500 v. 5 mA. 2-0-2 v. 1.1 a. 2-0-2 v. 1.1 a. for VCR97, VCR517, etc. 36/6

ELIMINATOR TRANSFORMERS
Primaries 200-250 v. 50 c/s 14/9
120 v. 40 mA. 5-0-5 v. 1 a. 15/9
90 v. 15 mA. 4-0-4 v. 500 mA. 9/9

CHARGER TRANSFORMERS
All with 200-250 v. 50 c/s Primaries :
0-9-15 v. 11 a. 11/9 ; 0-9-15 v. 3 a. 16/9 ;
0-3-5-9-17 v. 3 a. 17/9 ; 0-3-5-9-17.5 v. 4 a. 18/9 ;
0-9-15 v. 5 a. 19/9 ; 0-9-15 v. 6 a. 22/9.

SMOOTHING CHOKES
250 mA 5 H 100 ohms 12/9
150 mA 7-10-250 ohms 11/9
100 mA 100 H 200 ohms 8/9
80 mA 10 H 350 ohms 5/6
60 mA 10 H 400 Ohms 4/11

OUTPUT TRANSFORMERS
Midget Battery Pentode 60 ; 1 for 3S4, etc. 3/9
Small Pentode, 5,000 Ω to 3 Ω 3/9
Small Pentode 78,000 Ω to 3 Ω 3/9
Standard Pentode, 5,000 Ω to 3 Ω 4/9
Standard Pentode 78,000 Ω to 3 Ω 4/9
Multi-ratio 40 mA. 30 : 1. 45 : 1. 60 : 1. 90 : 1. Class B Push-Pull
Push-Pull 10-12 watts 6V6 to 3 Ω or 15 Ω 15/9
Push-Pull 10-12 watts to match 6V6 to 3-5 Ω or 15 Ω 16/9
Push-Pull 15-18 watts, 6L6, KT66 22/9
Push-Pull 20 watts, sectionally wound 6L6, KT66, etc., to 3 or 15 Ω 47/9
Williamson type exact to spec. 85/-

MANUFACTURERS' SURPLUS MAINS TRANSFORMERS. Primaries 250-250 v. 50 c/s. Fully shrouded upright mounting 425-0-425 v. 150 mA. 6.3 v. 3 a. 5 v. 3 a. 29/11, post 2/9. Wearite 305-0-325 v. 100 mA. 6.3 v. 2 a. 19/9. Drop Through Chassis type 250-0-250 v. 70 mA. 6.3 v. 2.5 a. 10/9.

EX-GOV'T. TRANSSES. 230/250 v. 50 c/s 8.8 v. 4 a 9/9; 460 v. 200 mA. 6.3 v. 5 a. 25/9; 300-0-300 v. 150 mA. 4 v. 3 a. 9/9 ; 0-16-16-20 v. 35 a. 69/6, carr. 7/6.

EX-GOV'T. SMOOTHING CHOKES
250 mA. 5 H 50 ohms 12/9
150 mA. 10 H 100 ohms 11/9
150 mA. 6-10 H 150 ohms Tron. 6/9
100 mA. 5 H 100 ohms Tropicalised. 3/11
L.T. type 1 amp. 2 ohms 2/9

EX-GOV'T. METAL BLOCK (PAPER) CONDENSERS
4 mfd. 500 v. 2/9 ; 4 mfd. 1,000 v. 4/9 ;
4 mfd. 1,500 v. 5/9 ; 8 mfd. 500 v. 6/9 ;
8 mfd. 500 v. 4/9 ; 10 mfd. 500 v. 4/9 ;
4 mfd. 400 v. plus 2 mfd. 250 v. 1/11.

EX-GOV'T. ELECTROLYTICS. Removed from unused equipment. 8-16 mfd. 550 v., 1/3 ; 16-16 mfd. 350 v. 1/3 ; 1,500 mfd. 6 v., 1/9 ; 80 mfd. 50 v. with clip. 6d.

EX-GOV'T. DOUBLE WOUND STEP UP/STEP DOWN TRANSFORMER
10-100-200-220-240 v. to 5-0-75-115-135 v. or REVERSE. 80/100 watts. Only 11/9 plus 2/9 post.

EX-GOV'T. CASE. Well ventilated black crackle finished, undrilled cover. Size 14 x 10 x 8 1/2 in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/6, plus 2/9 postage.

EX-GOV'T. VALVES (NEW)

1J4	7/9	6F6G	7/9	6AT6	7/9
1S5	7/9	6F9	5/9	EC83	9/9
354	8/9	6V6GT	6/9	EF80	7/9
5X3G	8/9	6X5GT	7/9	EB91	8/9
5Y4G	8/9	6L6G	11/9	EF36	4/9
5Z4G	8/9	607	7/9	EL32	5/9
6K7G	5/9	12A6	7/9	EL91	5/9
6K8G	9/9	12AD	7/9	KT44	8/9
6SJ6GT	6/9	15D2	4/9	KT66	11/9
6SLGT	8/9	2Z2AG	8/9	SP61	2/9
6SN7GT	8/9	MH4	4/9	35Z4	8/9

EX-GOV'T. UNIT RDEL. Brand new, cartoned. Complete with 14 valves, including 5Z4, F.H.T. rectifier, Trans. Choke, etc. Only 29/9, carr. 7/6.

ELECTROLYTICS (current production) NOT EX-GOV'T.

Tubular Types	Can Types
5µF 450 v. 1/9	8 mfd. 500 v. 2/11
8 mfd. 500 v. 2/6	18 mfd. 500 v. 3/9
16µF 350 v. 2/9	16 mfd. 350 v. 1/11
10µF 450 v. 2/3	16µF 450 v. 2/9
16µF 500 v. 3/9	32µF 350 v. 2/11
32µF 350 v. 3/9	32 mfd. 500 v. 4/9
32 mfd. 500 v. 5/9	100 mfd. 450 v. 4/9
25µF 25 v. 1/3	8-16µF 450 v. 2/9
50µF 12 v. 1/3	8-16µF 450 v. 2/11
50 mfd. 25 v. 1/6	16-16µF 450 v. 3/11
50µF 50 v. 1/9	16-32µF 350 v. 4/9
100 mfd. 12 v. 1/9	32-32µF 350 v. 4/9
100 mfd. 25 v. 2/3	32-32µF 450 v. 4/9
6,000 mfd. 6 v. 3/9	60-100 mfd. 6/9
	350 v. 6/11
	64-120 mfd. 350 v. 7/9
	100-200 mfd. 6/9
	275 v. 6/9

Many others in stock.

HUNTS MOULDSEAL CONDENSERS. 486 mfd. 400 v., .01 mfd. 400 v., .04 mfd. 500 v., 5/6 doz. (one type) ; 1 mfd. 350 v., 8d. ea. ; 25 mfd. 500 v., 1/3 ; .5 mfd. 500 v., 1/8 ea.

FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/s Primaries 6.3 v. 1.5 a. 5/9 ; 6.3 v. 7/6 ; 6.3 v. 2 a. 9/9 ; 12 v. 1 a. 7/11 ; 6.3 v. 3 a. 9/11 ; 6.3 v. 6 a. 17/6 ; 12 v. 3 a. or 24 v. 1.5 a. 17/6.

SMALL POTTED MAINS TRANSF.
Removed from Ex-Gov't. units.
Primary 0-200-230-250 v. Secs.
250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. Size 3 1/2 x 4 1/2 x 3 1/2 in. **11/9**

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all dry battery eliminator. Size 5 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s. Is available. Suitable for all battery receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams, 39/9, or ready for use, 46/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120 v., 90 v., and 60 v., 40 mA and 2 v. 0.4 a to 1 amp. Fully smoothed. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators. When connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEI-**

VERS normally using 2 v. Accumulator. Complete kit of parts with diagrams and instructions 49/9, or ready for use 56/6.

EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet.

- 6In. 2-3 ohms, 29/6.
- 8In. 2-3 ohms, 35/9.
- Very limited number.



VOLUME CONTROLS with long (1in. diam.) spindle, all values less switch, 2/9 ; with S.P. switch, 3/9 ; with D.P. switch, 4/6.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v. A.C. Output 120 v. 40 mA. Fully smoothed and rectified supply to charge 2 v. accumulator. Price with louvred metal case and circuit, 29/6. Or ready for use, 8/9 extra.

SPECIAL OFFERS 8-8 mfd. 450 v. small can electrolytics, a lots of six, 1/6 ea. Small .0005 mfd. 2 Gans. 4/9 ea.

T.V. CABINETS. Leading manufacturers surplus. Attractive designs. Walnut veneered, with doors for 15, 16, or 17In. Tube. 43-19-6. Carr. 7/6.

R.S.C. A8 ULTRA LINEAR 12 WATT AMPLIFIER

NEW 1856 Model High-Fidelity Push-Pull Amplifier with "Built-in" Tone Control, Pre-amp stages. High sensitivity. Includes 5 valves, 307 outputs. High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS, AND TREBLE "Lift" and "Cut." Frequency response ± 3 db. 30-30,000 c/s. Six negative feedback loops. Hum level 7 db. down. ONLY 70 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

For STANDARD or LONG-PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS, etc. OUTPUT SOCKET with plug provides 300 v. 20 mA. and 6.3 v. 1.5 a. For supply of a RADIO FEEDER UNIT, Price approx. £12-7/6. For A.C. mains 200-250-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value at £7/15/-, or factory built 45/- extra. Carriage 10/-. If required louvered metal cover with 2

£7-15-0

SUPERHET FEEDER UNIT

Desigs of a high quality Radio Tuner Unit (specially suitable for use with any of our Amplifiers). A Triode Heptode F changer is used. Pentode I.F., and double Diode Second Detector. Delayed A.V.C. Ae./ Grid F/C Coupling is by bottom end condenser Coupling giving freedom from alignment troubles when Ae. of varying lengths and capacity are used. Both Frequency Changers and I.F. valves are A.V.C. controlled from the very low distortion Double Diode so arranged that the very high Percentage modulation of the Transmitter can be handled without distortion. The Feed for the delayed A.V.C. is arranged so that A.V.C. distortion is avoided. The Ch. Sw. incorporates Gram. position. Controls are Tuning, W. Ch. and Vol. Output will load most Amplifiers requiring 500 M.V. input depending on Ae. location. Only 250 v. 15 mA. H.T., and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6-7/16. Simple alignment procedure. Point-to-point wiring diagrams, instruction and priced parts list with illustration, 2/6. Total building cost, £4/15/-. For descriptive leaflet send S.A.E.


GARRARD 3-SPEED MIXER AUTO-CHANGER MC10. For Standard A.C. mains 200-250 v. 50 c/s. Current Model. Brand new, cartoned. Provision for taking 10 records. Fitted High-Fidelity turnover pick-up head with dual sapphire point stylus for Standard or Long-playing records. Very limited number at only £7.19.6. Carr. 3/6.

B.S.R. TUS 3-SPEED SINGLE RECORD PLAYING UNITS for 7in., 10in. or 12in. records at 33 $\frac{1}{3}$, 45, or 78 r.p.m. Supplied with high-fidelity crystal pick-up with dual sapphire point turnover stylus for standard or long-playing records. Only £4.12.6. plus 3/6 carr.

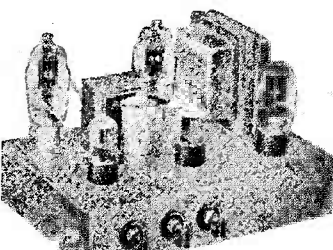3-4 WATT QUALITY AMPLIFIER. Designed for use with B.S.R. or Garrard Autochanger. Fitted separate Bass and Treble controls, Vol. Control and mains switch. Latest type B.V.A. valves used. For 200-250 A.C. mains chassis is not "alive." Output for 2-3 ohm speaker. Ready for use. Only £4.10/-. carr. 3/6.

ELLIPTICAL P.M. SPEAKER. 7x 3in. Goodmans. Suitable for above, 19.6.

PICK-UPS. Collaro high-fidelity high impedance magnetic type. Only 31.3. Brand New.



carrying handles can be supplied for 17.6. Additional input socket with associate Vol. Control so that two different inputs such as Gram and "Mike" or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months. TERMS on assembled two input model. DEPOSIT 25/6 and nine monthly payments 22/4. HIGH-FIDELITY MICROPHONES and SPEAKERS in stock. Keen cash prices or H.P. terms if supplied with amplifier.

R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads, in addition to all other types of pick-ups and practically all mikes. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down. 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape Deck preamplifier. For A.C. mains input of 200-250-250 v. 50 c/s. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4/15/-, or assembled ready for use 25/- extra, plus 3/6 carr.



PLESSEY 10in. P.M. 3 OHM SPEAKER with High Flux Density Magnet. Recommended for use with above or A7 Amplifier. Only 28/9.

B.S.C. TA1 HIGH QUALITY TAPE DECK AMPLIFIER. For ALL Tape Decks with High Impedance, Playback and Erase Heads, such as Lane, Truvox, etc. (Unit can now Ready for be supplied for use with latest Use. ONLY Collaro Tape Transcripser; refer to TA1C.) For A.C. Mains 230-250 v. 50 c/s. Positive compensated identification of recording level by Magic Eye. Recording facilities for 15.74 or 31in. per sec. Automatic equalisation at the turn of a knob. Linear frequency response of ± 3 db. 50-11,000 c.p.s. Negative feedback equalisation. Minimum microphony and hum. High output with completely effective erasure and distortionless reproduction. Sensitivity is 15 millivolts so that any kind of crystal microphone is suitable. Only 2 millivolts minimum output required from recording head. Provision is made for feeding a P.A. amplifier. Unit can also be used as a gram-amplifier requiring input of 0.75 v. R.M.S. Carriage 7/6. Illustrated leaflet 6d.

11 GNS.

R.S.C 30 WATT ULTRA LINEAR HIGH-FIDELITY AMPLIFIER A6

A highly sensitive Push-Pull, high output unit with self-contained Pre-amp Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 30 db. down. Frequency response ± 3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, and separate Bass and Treble controls. Minimum input required for full output is only 30 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for RECORDING UNIT. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has outputs for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for A8 can be supplied for 17/6. An extra input with associated vol. control so that two separate inputs such as Gram and Mike can be mixed, can be provided for 13/- extra. The amplifier can be supplied, factory built with 12 months' guarantee, for 50/- extra. TERMS for assembled two input model: DEPOSIT 28/9 and 9 monthly payments of 28/9.

9 GNS.

P.M. SPEAKERS. All 2-3 ohms. 5in. Goodmans, 17/9. 6in. Plessey, 16/9. 8in. Plessey, 16/9. 8in. Rola, 19/9. 10in. Plessey Heavy duty, 28/9. 10in. Elco 25/9. 12in. Plessey, 29/11. 10in. W.B. "Stentorian" 3 or 15 ohms type HF1012 10 watts, high-fidelity type. Highly recommended for use with any of our amplifiers. £4/10/9. 12in. Plessey 15 ohm 10 watts, 3 Gns.

PLESSEY DUAL CONCENTRIC 12in. 15 ohm HIGH FIDELITY SPEAKER with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.) providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price complete, only £5/17/9.

M.F. SPEAKERS 2-3 ohms. 8in. R.A. Field, 600 ohms, 11/9. 19in. R.A. Field, 1,000 ohms, 25/9. 10in. R.A. Field, 1,800 ohms, 23/9.

COAXIAL CABLE 75 ohms, 3in. 8d. yard. Twin Screened Feeder, 11d. yard.

SELENIUM RECTIFIERS

6/12v. 1a.	4/11	6/12v. 1a. H.W.	2/9
6/12v. 2a.	8/9	H.T. Types H.V.	
6/12v. 4a.	11/9	150 v. 40 mA.	3/9
6/12v. 4a.	14/9	250 v. 50 mA.	5/9
6/12v. 6a.	19/9	250 v. 80 mA.	7/9
6/12v. 10a.	25/9	250 v. 150 mA.	9/9
L.T. Types H.V.		300 v. 250 mA.	12/9

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

For 230-250 v. 50 c/s. Mains input. Adjustable tone and equalisation. With exception of output wattage, as A5. Complete kit with diagrams, £2 15/- Assembled 22/6 extra. Carr. 3/6.

THE "SKYFOUR" T.R.F. RECEIVER A design of a 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable-Mu high-gain H.F. stage followed by a low distortion audio bend detector. Power pentode output is used. Valve line up being 6K7, 6SP6, 6P6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-point wiring diagrams, instructions and parts list. 19. This receiver can be built for a maximum of £4/19/6 including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 $\frac{1}{2}$ x 5 $\frac{1}{2}$ in.

Terms: C.W.O. or C.O.D. NO C.O.D. under £1. Post 1/9 extra under £2: 2/9 extra under £5. Open 9 to 5.30; Sats. until 1 p.m. Catalogue 6d., Trade List 5d., S.A.E. with all enquiries.

RADIO SUPPLY CO. 32, THE CALLS, LEEDS, 2



still only 5/-

Get your

BRIMAR MANUAL

The
LATEST EDITION
has
276 Pages
of **VALVE and**
TELETUBE DATA
CIRCUITRY
& SPECIAL
COMPONENTS

SUMMARY OF CONTENTS

Valve ratings and base connection symbols.
Classified lists of nearly 300 valves, teletubes and selenium rectifiers.
Germanium diode section including ratings in various circuits.
Brimistors section.
Radio engineering formulae and NEW circuits.
Brimarize section. Valves and teletubes.
Up-to-date substitution list of American types.
Equivalents and C.V. numbers.
Details of Trustworthy types.
Valuable information on Transistors.

Send 5/- for your copy to: *Publicity Dept.*

Standard Telephones and Cables Limited FOOTSCRAY SIDCUP KENT Footscray 3333

PREMIER RADIO COMPANY

B. H. MORRIS & CO. (RADIO) LTD.

OPEN TILL
6 P.M. SATURDAYS

(Dept. P.W.) 207, EDGWARE ROAD, LONDON, W.2


Telephone:
AMBASSADOR 4033
PADDDINGTON 3271-2

BUILD THESE NEW PREMIER DESIGNS

2-BAND T.R.F. RECEIVER

MAY BE BUILT FOR **£5.15.0** Plus 3/- Pk. & Post.

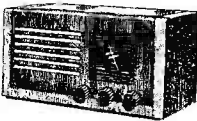3-Band Superhet Receiver may be built for £7.19.6 plus pk. & carr. 3/-. These two receivers use the latest type circuitry and are fitted into attractive cabinets 12in. x 6 1/2in. x 5 1/2in. in either walnut or ivory bakelite or wood. Individual instruction books 1/- each, post free.



MULLARD AMPLIFIER KIT

Why not make the Best!

All the components for model 510, PLUS preamplifier on one chassis (total six valves) may be purchased for £12.12.0, plus pkg. & post 7/6, or preamplifier and tone control in a separate unit, £14.14.0 plus pkg. & post 7/6.

NOW SUPPLIED WITH
ULTRALINEAR OUTPUT
TRANSFORMER

Send for the Premier WIDE ANGLE TELEVISOR booklet, 3/6 post free.


ALL-DRY BATTERY PORTABLE RADIO RECEIVER

MAY BE BUILT FOR **£7.8.0**

Plus 3/- Pkg. & Postage
4 Miniature valves in a superhet circuit covering medium and long waves. Re-line covered cabinets 11 1/2in. x 10in. x 5 1/2in., in contrasting colours, wine with grey panel. Instruction book 1/6 post free, which includes full constructional details and list of priced components.



COMPACT GRAM AMPLIFIER

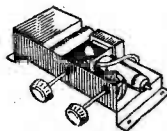

Suitable for any type of Pick-up. Volume and tone control fitted with knobs. Overall size 7 1/2in. long x 3 1/2in. wide x 2 1/2in. high. Complete and ready for use.

£2.19.6

Plus packing & postage 2/6.


GRAM
UNITS

B.S.R. 4-Speed Autochanger. £9.15.0 plus 5/- pkg. & post.
B.S.R. TUS 3-Speed £4.12.6 plus 2/6 pkg. & post.

4-WATT AMPLIFIER

MAY BE BUILT FOR **£4.10.0** Plus 2/6 Pkg. & Carr.

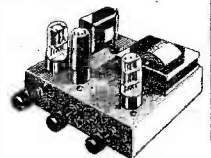Valve line-up 6SL7, 6V6 and 6X5, FOR A.C. MAINS 200-250 VOLTS. Suitable for either 3-ohm or 15-ohm Speakers. Negative feedback. Any type of pick-up may be used. Overall size 9in. x 7in. x 5in. Price of Amplifier complete, tested and ready for use, £5.5.0 plus 3/6 pkg. and carr.



A STEEL CASE IS NOW AVAILABLE, COMPLETE WITH ENGRAVED PANEL, 15.6 EXTRA.

A NEW TAPE RECORDER

CREDIT TERMS DEPOSIT **£5**
and 8 monthly payments of £4.18.6

H.P. TERMS 1 DEPOSIT **£20**
and 12 monthly payments of £1.17.1

Cash price £40 plus packing and carriage 2/- Case finished in Brown and Antique Fawn. Size 15in. x 12 1/2in. x 7 1/2in. with the very latest type Continental fittings. For A.C. mains 200-250 volts, 50 cycles.

SEND FOR LEAFLET

PRACTICAL WIRELESS

EVERY MONTH
VOL. XXXII, No. 601, JAN., 1957

EDITOR: F. J. CANN

24th YEAR
OF ISSUE

COMMENTS OF THE MONTH

BY THE EDITOR

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4392.
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by Canadian Magazine Post.

Transistor Circuits

READERS will have noted that in recent issues we have devoted considerable space to transistors. It is natural that our readers, all of whom are practical constructors, and therefore interested in experiment, should press for more articles on this subject, and we shall continue to publish articles on transistors and their application, increasing the amount of space devoted to the subject as transistors become more readily available. At the present time manufacture is hardly equal to the demands of the industry. They are also at present more expensive. Because of the comparatively low stage gain more of them are required to provide a given output than would be necessary with an ordinary valve circuit. It would be idle for us to publish designs for which transistors are not readily available. Whilst transistorised circuits are the inevitable development and must eventually replace the valve, that time is far distant.

TAPE RECORDERS

THE sales of tape recorders continue to advance with the growing interest in this fascinating branch of electronics. As with radio, clubs are being formed all over the country, many of them operating lending libraries. As with radio clubs, however, we should like to issue a warning. It is that readers should be particularly careful to investigate the bona fides of any club before they part with their money. Especially is this necessary with clubs claiming nation-wide membership. Readers should ask the following questions: Is the club a proprietor's club (that is to say, a club where the founders remain the proprietors and cannot be voted out of office)?—avoid joining any club where the officers are not elected at an Annual General Meeting; ask whether an independently audited balance sheet is to be issued to members; enquire whether the officers are paid or honorary; ascertain what are the real benefits of membership; a duplicated news-sheet hardly warrants an annual subscription. If in doubt write to us.

Before any club notice is permitted to appear in this journal we first investigate along the lines of the foregoing.

RADIO FILM SHOW

AS briefly announced last month, there will be a radio film show at the Caxton Hall (Great Hall Site) on Thursday, February 21st, 1957. Admission is free, but by ticket obtainable from the offices of this journal. Seating accommodation is limited so you should apply now. Address your letters to: "Film Show," PRACTICAL WIRELESS, address as on this page. The meeting will commence promptly at 8 o'clock in the evening, and there will be an interval for refreshments. Dropping the editorial "we" for a moment, I shall be in the chair. The films to be shown are fascinating and will provide an entertaining evening of educational value.

BINDERS FOR P.W.

LAST month we published details of our self-binders for PRACTICAL WIRELESS. A large number of readers have ordered them, but many of them have omitted to indicate the number of the volume that they required blocked on the spine. When placing an order, therefore, please indicate the number of the volume. Details of these self-binders were given on page 689 of our December issue.

"AMPLIFIERS: DESIGN & CONSTRUCTION"

WE have had a large number of requests during recent years for a book on amplifiers. Readers will be interested to know, therefore, that on February 14th we shall publish "Amplifiers: Design and Construction." It will cost 17s. 6d., by post 18s. 3d. (280 pages and 167 illustrations.) It will contain the cream of the articles on this subject which have been published herein. If you wish to reserve a copy of this limited edition send your remittances to the Book Department, George Newnes, Ltd., address as above.—F. J. C.

**OUR NEXT ISSUE, DATED FEBRUARY, WILL BE
PUBLISHED ON JANUARY 14th**

Round the World of Wireless



Broadcast Receiving Licences

THE following statement showing the approximate number of Broadcast Receiving Licences in force at the end of September, 1956, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

The numbers include Licences issued to blind persons without payment.

Region	Total
London Postal	1,278,772
Home Counties	1,278,277
Midland	990,586
North Eastern	1,292,412
North Western	980,001
South Western	807,910
Wales and Border Counties	509,832
Total England and Wales ...	7,137,790
Scotland	915,652
Northern Ireland	204,508
Grand Total	8,257,950

EMI Telemetry

IT can now be announced that EMI Electronics Ltd. have been commissioned to provide the vital telemetry equipment for the series of experimental high altitude test vehicles (rockets) which will be used in the upper atmosphere rocket research programme to be undertaken by the Gassiot Committee of the Royal Society during the forthcoming International Geophysical Year (1957-58).

The project, which is sponsored by the Ministry of Supply and the Royal Aircraft Establishment, will study a wide range of meteorological, atmospheric and solar phenomena in the upper atmosphere, as well as many aspects of high altitude rocket performance.

The specialised telemetry equipment provided by EMI Electronics will transmit a wide variety of information concerning test vehicle performance and scientific experiments.

BBC Engineering Division Appointments

MR. G. K. DRAKE has been appointed Engineer-in-Charge of the BBC's Television and V.H.F. Transmitting Station at Blaen Plwy in Wales. Mr. Drake joined the BBC at the Alexandra Palace television station in 1938. He subsequently served at a number of the Corporation's trans-

By "QUESTOR"

mitting stations and was appointed Senior Maintenance Engineer at the BBC's V.H.F. Transmitting Station at Wrotham, Kent, in 1949. He remained at Wrotham until taking up his present appointment.

Remote Control for Tankers

A REMOTE control device, operated from a tanker moored at the end of submarine cargo loading lines $3\frac{1}{2}$ miles out at sea, which is capable of stopping the cargo loading pumps on shore, has recently been installed at a cost of Malayan \$85,000 (£10,000) at Lutong Refinery in Sarawak, British Borneo. This equipment, now in service, was developed jointly by Shell and the General Electric Company Limited, London.

The shallowness of the water prevents tankers from coming close to the shore, and the four loading moorings are situated $3\frac{1}{2}$ miles out. They are connected to the shore by underwater pipelines.

As a tanker approaches the moorings a portable transmitter/receiver is taken aboard. In addition to providing a radio-telephone service with the shore terminal this portable set can transmit on a special "pump control" channel.


Should it be necessary to stop the pumps in an emergency the pressing of a control button on the operating panel of the portable set overrides the telephone channel and brings the pump control channel into operation. On reaching the shore pumphouse the signal is fed to the particular engines pumping to the tanker on which the button was pressed. Electrically operated valves are then activated and stop the engines.

Lutong refinery, owned by Sarawak Oilfields Limited, one of the Royal Dutch/Shell Group of oil companies, has been completely rebuilt since the war and is now processing crude oil at a rate of some 2.4 million tons a year. The majority of the crude comes from the Seria field in the State of Brunei, which, with an annual output of about 5 million tons a year, is one of the largest single oilfields in the British Commonwealth.

Pye Radio for King Hussein

A PYE radio has been installed in the Royal compartment of the Vickers Varsity aircraft which has just been converted by Eagle Aircraft Services Ltd. for the personal use of His Majesty King Hussein of Jordan.

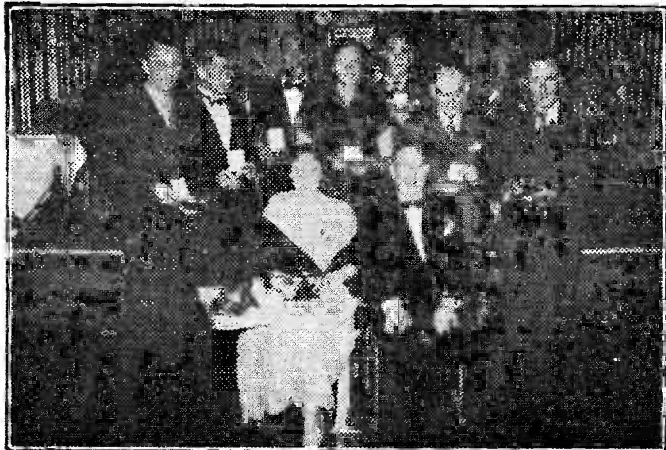The radio is a Pye "Continental" car radio which has been adapted to work from the aircraft's 24-volt power supply. It has five wave-



The Whiteley presentation group referred to on the opposite page.

bands—long, medium and three short—and was specially designed for long distance reception and Continental motoring.

The "Continental" is normally available for both 6 and 12 volt systems, and costs 30 gns. inclusive of purchase tax.

V.H.F. for Southern Gas Board

IN an effort to add to all-round efficiency, the Southern Gas Board's Southampton Group is to equip its fleet of maintenance vehicles with very high frequency radio-telephones.

The equipment, which is being supplied by Automatic Telephone & Electric Co. Ltd., is of the latest frequency modulated type. The system will permit full duplex working (simultaneous two-way conversation) and at the base station at the Marine Parade Gas Works there will be three telephone control points. Initially eight vehicles are being fitted with 10-15 watt RL equipment.

Before the order was placed comparative trials were carried out in the area covered by the group using both F.M. and A.M. types of equipment, the marked superiority—both in range and performance—of the F.M. system leading to its adoption.

V.H.F. radio-telephone systems are already extensively used by gas boards in other areas for a wide variety of assignments, including emergency repairs and the laying of new gas mains.

British Research into Tropospheric Scatter

IN common with other countries, intensive research into the possibilities of tropospheric scatter is being carried out in the United Kingdom. It will be recalled that earlier in the year General Gruenher stated that the radar stations of N.A.T.O. from the Arctic to the Mediterranean would be co-ordinated by the use of such techniques.

Marconi's, who have been conducting propagation tests for many years, have now brought into operation a tropospheric scatter link between Gt. Bromley, Essex, and Sutton Bank, near Thirsk, Yorkshire, the distance involved being about 200 miles.


Field strengths are recorded continuously over this link; various types of modulation are available so that studies can be made of multi-path effects, the effect of aircraft and other relevant prob-

lems. Preliminary tests have already been made over a 400 mile circuit to Aberdeen, and it is hoped later to establish a link over this distance.

Plans are currently in hand to set up high power (10 kW) transmitters and associated receivers at Newcastle and in the London area with the object of being able to

Talking with Antarctica

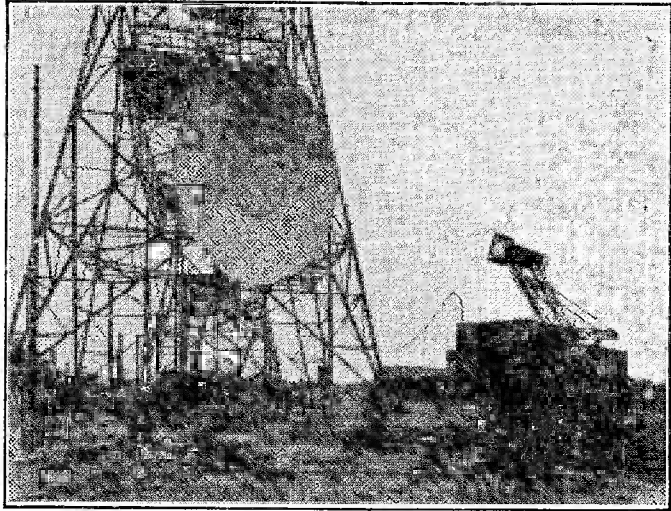DIRECT contact was established for the first time on the evening of Wednesday, October 31st, between members of the Commonwealth Transantarctic Expedition in Broadcasting House and their comrades at Shackleton Base—a distance of nearly 10,000 miles.



The first picture to be issued of the Marconi tropospheric scatter experimental equipment.

operate up to 36 simultaneous telephone channels or a television link between these points. The equipment is being designed and constructed by Marconi's as a private venture and the link would be used for tests and demonstration only.

Whiteley Presentations

SEVEN members of the staff of Whiteley Electrical were recently presented with gold watches on completion of 21 years' service with the company.

The presentations were made at a Party Dance held at the local Palais de Danse in Mansfield which was attended by over 450 of the staff and workpeople. The names of the recipients were: Miss C. M. Parkin (Sales Accountant), Messrs. T. Barnes (Departmental Manager), T. A. Barrow (Press Shop Foreman), C. F. Gison (Transport Dept.), H. W. Read, M.S.M.A. (Sales Director), C. Smith (Maintenance Engineer) and L. Thorpe (Plating Shop).

In addition cheques were handed to the wives of the male staff who received gold watches.

The following evening a congratulatory message on behalf of the Government, recorded by the Rt. Hon. the Earl of Munster, Minister without Portfolio, was transmitted to the base.

Reception was perfect during most of the half-hour that the circuit was open on that night. The Shackleton Base area is one of the most difficult parts of the world with which to establish radio contact, not so much on account of the great distance but because of the exceptional atmospheric conditions—the "auroral zone"—in which the base is situated.

Obituary—Mr. P. V. Hunter

IT is with deep regret that British Insulated Callender's Cables Limited announce the death of Mr. Phillip Vassar Hunter, C.B.E., Hon.M.I.E.E., a director and former deputy chairman of the company. Mr. Hunter, who was 73, retired from the deputy chairmanship in 1952, but remained on the board as a non-executive director and retained his positions on the boards of several subsidiary companies.

Autochanger Maintenance

HINTS FOR THE SERVICE ENGINEER AND EXPERIMENTER

By H. W. Hellyer, A.I.P.R.E.

A GOOD deal of fine equipment has been built by readers from guidance given in these pages. Much of it is probably superior in performance to and certainly cheaper than the equivalent commercial product. And any enthusiast will testify to the advantage of knowing one's own kit down to the last nut and bolt. But there is one item of equipment that is beyond the scope of the average constructor; that he has to buy ready made. This is the automatic record changer.

It is an item that is often a source of trouble, prone to baffling mechanical faults which are difficult to locate without the aid of a service manual.

The following notes are offered as a possible aid in the maintenance of these autochangers.

Fault finding can be a tedious business amid the perplexing array of cogs, cams, gears, springs and levers. However, a logical approach to the problem will usually show results. A knowledge of the general principles used in autochanger technique can be a help to the constructor who has to work "in the dark."

First, it should not be necessary to work literally in the dark. The unit plate can be supported at eye level on a table or bench, by employing two similar boxes, making sure that the edges of the plate are firmly seated, level and with switch levers, etc., not fouling. A mirror flat on the table beneath the autochanger is helpful, if one is able to work mirrorwise—not always an easy task. The unit can then be connected, switched on, and all movements studied. The best method is to switch to 33 r.p.m. and lift the platform arm so that the stop mechanism is eliminated and continuous cycling takes place.

The automatic record changer can be regarded as an instrument of three stages:

1. The motor and main drive.
2. The secondary drive and cycling mechanism, and
3. The pick-up head and associated circuits.

The first stage, the motor, is not likely to be very troublesome. Most modern units employ synchronous or induction motors. The circuit of a typical A.C. motor is given at Fig. 1. Apart from obvious short or open circuits in the coils, there is little electrically to go wrong. The condenser is usually a good quality type in these units. Mechanically, the principal points are lubrication and clean bearings. Most are self lubricating, requiring only an occasional spot of oil on the felt pads at the seat of the main bearing.

Motors using commutators, brushes, etc., are probably well known. It need only be mentioned here that the most prevalent faults are dirty armatures, "clogging" of carbon between segments, worn brushes, tight brushes or springs that are distorted, displaced governors, excessive friction at governor.

Tests for faulty armature windings—suspected if overheating or sparking is excessive—can be made by taking resistance readings between segments. Any meter will do for this, it only being necessary to ensure that readings are similar.

The drive from the motor is usually via a rubber-tired wheel held on a spring bracket so that it engages both with a capstan on the motor spindle and the inner edge of the turntable rim. Fig. 2 shows the system. Faulty rim-drive mechanism can usually be diagnosed by the frequency of the sound, the slowest "knock" indicating roughness of the turntable itself, a faster "knock" pointing to a faulty drive wheel and a very rapid "flutter" or "rumble" indicating that the motor spindle or its capstan are the possible culprits. A frequent fault with the type shown, the popular B.S.R. autochanger, is the slipping down of the capstan on its shaft, causing slow running. Two grub screws hold it in place and resetting is a simple matter. Speed changing is effected by raising or lowering the rubber primary drive wheel by a set of levers actuated by a knob.

There are alternative methods to the one shown, but all work on a similar principle; a reducing gear engaged by friction forms the primary drive. Sometimes the change of speed is gained by engaging separate drive cams of different diameters.

Care should be taken that oil does not get on the rubber drive wheels or slipping will occur. Indeed, it is a general rule on the modern autochanger to avoid indiscriminate oiling. Loss of friction is a common fault.

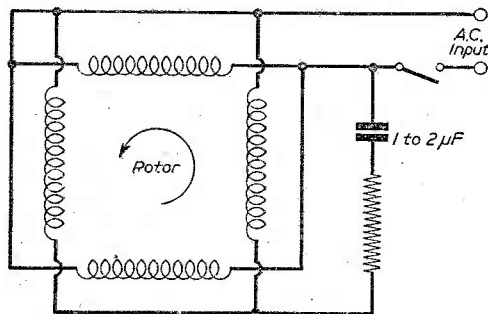


Fig. 1.—Standard motor circuit.

The Secondary Drive

In order to obtain the necessary set of movements of pick-up arm and record spindle a rotating cam-gear is employed. This could, rightly, be called the heart of the machine. It is a gear wheel of fairly large diameter and has various "hills" and "valleys" on its face, with rods and pivots which engage levers at the appropriate point of rotation. There are three principal methods of driving the cam-gear. First, directly from the motor spindle. Secondly, from the turntable rim, and thirdly, from the turntable hub.

The third method is most popular, being used by B.S.R., Garrard, Plessey and Philips and in a modified form by E.M.I. Fig. 3 shows the relative positions and shape of the B.S.R. cam-gear and drive. When the unit is at rest or the mechanism disengaged, i.e.,

the pick-up actually playing, the gap in the teeth of the cam-gear is opposite the turntable hub.

Starting is effected by movement of a pawl and link unit which is pushed by a lever linked to the starting switch and also to the trip mechanism. This latter feature will be considered later.

The action of starting engages the pawl with a raised spline on the turntable hub boss and moves the cam-gear sufficiently for the teeth to engage.

This pawl and friction link is a frequent offender and can cause erratic action. The usual trouble is clogging, due to dirt and grease or looseness of the 6 B.A. locknut, allowing the link to ride over its small stop. Between the two items pawl and link is a fine, circular spring, easily lost if the assembly is dismantled.

Other types of cam-gear and start mechanism vary widely in general design, but all function on the same principle. Initial movement is obtained by engaging a subsidiary mechanism which drives the cogs of the main cam into mesh. (In the case of E.M.I. changers, the cam-gear has a rubber tyre, driven by a milled brass bush, instead of cogs, but the principle is similar.)

Some Collaro units employ a secondary drive wheel

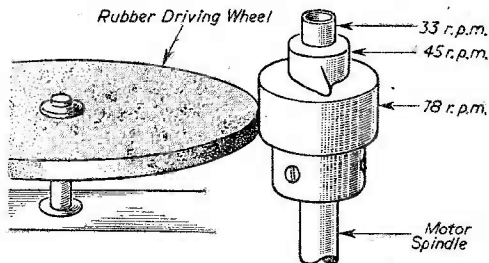


Fig. 2.—The B.S.R. capstan drive (not to scale).

in contact with the turntable rim. Cogs on the hub of this secondary wheel base then engage the main cam. Starting is obtained by a catch lever system on which the secondary drive wheel is mounted.

Other types engage with the motor spindle when starting takes place and some Garrard units use the system of double drive, via two rubber belts. Plessey use an intermediate gear wheel, engaging with the turntable hub and "sprung" out of mesh until the start button is pressed or the trip action operates. Philips have a different method, a subsidiary cog on a swivel arm which is brought into mesh to initiate cam-gear movement. E.M.I. autochangers use a lever with a pivoted end-piece which actually pushes the cam-gear into engagement with the milled brass bush of the hub.

The Cycling Mechanism

Having reached the stage where the motor has been switched on, the speed selected, the primary drive to the turntable and the secondary drive to the cam-gear engaged, we now come to the more complicated part of the mechanism.

It will assist in the general understanding of the various operations if we break down the complete cycle into a series of actions as follows:

1. Start, switch on and engage drives.
2. Next record drops.
3. Pick-up lifts and moves inward.

4. Setting down position of pick-up selected.
5. Pick-up "runs-off" at end of record, operating
 - (a) auto-trip, or
 - (b) auto-stop mechanism.

In addition there are subsidiary operations: repeat, reject, stop and so on, but these are mainly extensions of those listed above.

Stage 1: Starting.—The action of switching on moves a double set of levers, completing the circuit to the motor and engaging the cam-gear. The principal aspects have been discussed above. Faults to look for are: erratic switch action; loose levers; weak or dislodged return springs; stiff or loose pawls (described above, see Fig. 3); worn cogs or rubber tyres.

The cam-gear now takes over and drives further levers by the action of the various hills and valleys. Different manufacturers employ their own methods and some manufacturers use several varying types of action. There are too many to discuss in detail here,

Note: Link and Pawl are exaggerated in size

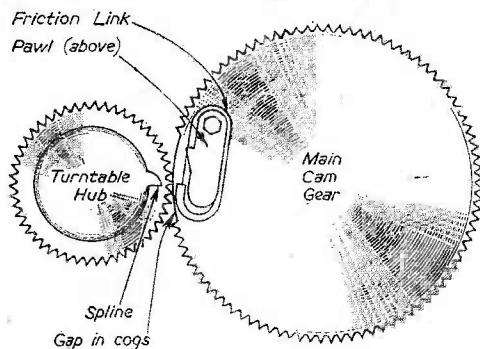


Fig. 3.—The drive cam gear.

but the principle is similar. The writer will be glad to discuss any individual problems which may perplex readers. The B.S.R. autochanger, which is widely used, is a good example on which to illustrate the various actions. Details of its cam-gear are shown in Fig. 3.

As the gear-wheel revolves, an eccentric cam pushes a sliding carriage, bringing about movement of pick-up and Stage 2.

Record Dropping

As the carriage slides laterally a small slot in its underside moves a pivoted spindle lever against the tension of a spring, imparting a "kick" action to a shaped arm just level with the lowest record of the stack (see Fig. 4). The records rest on a step of the centre spindle and are fed to this step by a shaped, slotted pawl in the upper section. Erratic record dropping can be caused by: weak spring at base, loose or dislodged pivot pins (a) and (b), jammed knocker arm, due to grit between arm and spindle wall, or jammed upper pawl, causing two or more records to drop.

Other manufacturers use similar methods, the initial motion being sometimes vertical (Collaro and Plessey), or rotary (E.M.I.), or by pushing the records from the edge (some Garrard models).

Stage 3: Pick-up Arm Movement.—The necessary sequence of movement is vertical, to raise the arm

from rest, lateral, to bring the head over the record, and vertical, to lower stylus to the record. These movements are brought about by the rotation of the main cam-gear. As the carriage (described under Stage 1) moves along it engages with the pick-up base assembly and moves the pick-up inwards; a U-shaped link pivoted to a bracket on the carriage raises the arm via a central spindle and further movement of the link past its fulcrum lowers the arm to the record.

While the record is being played, the lower part of the base assembly is disengaged.

Other methods of imparting these motions are by rods, rollers or pivoted levers "riding" in shaped depressions

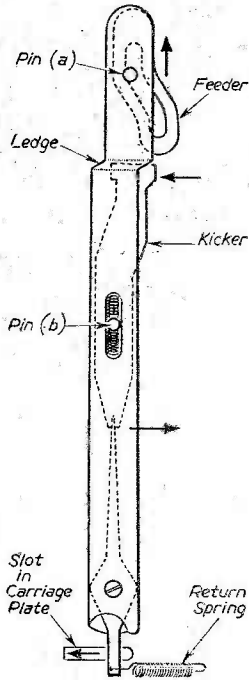


Fig. 4.—The B.S.R. spindle. This drawing as well as Fig. 2 is not to scale.

in the cam-gear (E.M.I., Plessey and Collaro), or pivoted levers (Philips, Garrard and some Collaro models). Principal causes of failure are jamming of the pick-up lead in the base assembly impeding lateral

motion, fouling of rods, etc., in cam-gear groove, binding at pivot points, and cam-gear action failing, to disengage at end of travel, causing repeat action before record plays.

Stage 4: Pick-up Setting Down Position.—The point at which the pick-up head descends to the record is selected by the size of the record on most autochangers, manually on others. As a 10in. or 12in. record drops its edge depresses a lever, setting a limiting stop in the path of the pick-up base assembly. The B.S.R. models use a plastic lever sprung in a sliding plate with a stepped lower portion which stops the movement of the assembly. Failure of its action causes records to be played in the 7in. position. Chief cause of failure is loose pin, relaxed or dislodged spring at upper end of pivoted arm, or a jammed sliding lever.

Other methods are: a swinging arm which rests against the edge of the records (some Collaro and Garrard models), a raised lever-tripped by the edge of 12in. records (Philips), a hinged flap raised for 12in. records at the steadying platform (E.M.I.), a small lever for 12in. records, and automatic selection of the 7in. position by the 45 r.p.m. speed switch (Plessey).

Stage 5: The Run-off (a) Auto-trip.—After the record has been played the stylus enters the run-off grooves. These are more widely spaced, causing a rapid oscillatory movement of the arm. Advantage

is taken of this rapid movement to actuate a velocity trip in many models.

B.S.R. use the same pawl and link described previously and shown in Fig. 3. Position of the arm relative to centre spindle moves the pushing lever via the pick-up base assembly. The full purpose of the friction link and spring is now seen. When normal playing is in progress the friction link resists the

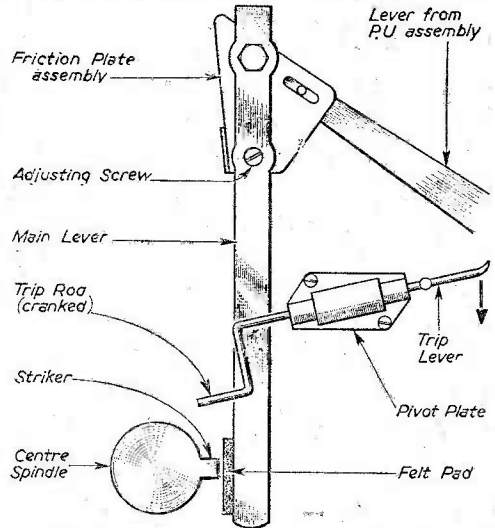


Fig. 5.—Auto-trip mechanism, as used by Garrard. Main lever moves by P.U. lever movement, via friction plate assembly. At ultimate (run-off) groove, lever is thrown into path of striker which makes contact with the felt pad. Owing to the shape of the end an upward and backward movement is imparted, causing rotation (partial) of the trip rod which is angled at its farther end so that eventual movement of the trip lever is in the direction of the arrow in diagram.

inward movement to a certain extent, preventing premature changing. But the action of the run-off groove causes the push lever to overcome this slight resistance, engage the pawl with the spline on the turntable hub, and initiate cam-gear movement. Thus, it is apparent that a loose link will cause premature rejection and a faulty pawl action will fail to actuate the trip.

The velocity trip usually employs a striker on the turntable boss, which hits a pad on a lever placed in its path by the "throwing" movement of run-off grooves. An idea of the principle can be obtained by a study of Fig. 5. This is the method employed by some Garrard models.


The striker catches the felt pad, which is pushed upwards (due to its pivoted mounting). Thus, the associated rod twists, lifting its cranked end, swinging a trip lever which then moves the secondary drive into gear. A friction clutch is employed to prevent premature rejection. Looseness of the pivot bracket and maladjustment of the setting screw which controls the height of the arm on which the felt pad is mounted are frequent causes of faulty action. The pads of the friction clutch grow smooth with time and may require "roughening."

(To be continued.)

A Quality DIODE - TRANSISTOR Receiver

A NOVEL RECEIVER UTILISING
TWO DIODES AND THREE
TRANSISTORS

By R. V. Moore, B.Sc.

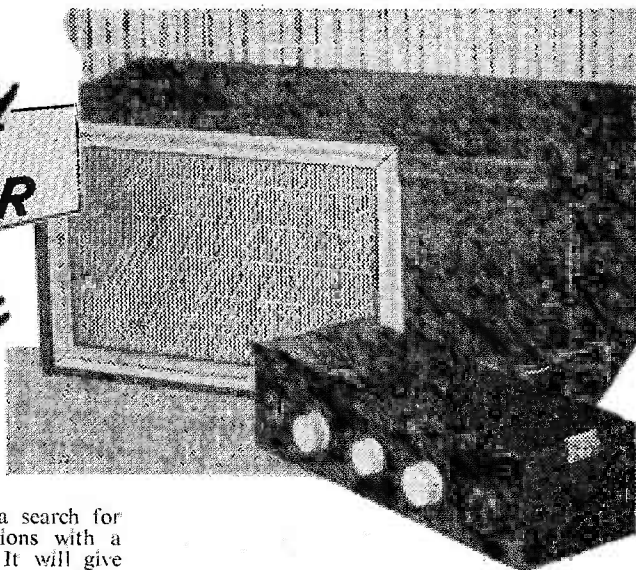

THIS receiver is the outcome of a search for quality reception of local stations with a diode-transistor combination. It will give results which will satisfy those readers who require a receiver for regular use. The quality and volume compare favourably with that of a three-valve T.R.F. receiver.

It should be made clear at the outset that it is essential to employ a good aerial, either outdoor or indoor, and a good earth. The strength of the signal fed into the amplifier from the detector stage influences quality and also volume to a marked degree.

The Circuit

Most of the experimental work carried out was in connection with the detector stage. Consideration was given to employing either transistors or diodes in this stage. Valves were eliminated because of their power requirements. The final circuit is shown in Fig. 1, page 738.

The Detector Stage

A push-pull circuit employing two G.D.3 diodes was used. This proved to be more efficient than any circuit employing only one diode. The circuit was first made using a home-constructed coil, this being wound for medium-wave reception only. However, it was necessary to incorporate long-wave tuning also, because reception of the Light Programme on medium-wave in the author's district is not satisfactory. Efforts were made to construct a dual-wave coil, but results were not satisfactory due chiefly to medium break-through on the long waves. It was necessary, therefore, to have separate coils for the two wavebands. The author has to thank Messrs. Teletron Co., Ltd., for supplying the coils specially to his requirements. They can now be purchased from the firm at 4s. 6d. each, complete with two slugs. As will be seen from the circuit diagram each coil has

two tuned windings with a coupling coil between. Switching from medium to long wave is by means of a four-pole two-way rotary switch. A twin gang .0005 variable condenser tunes the two windings on each waveband. The two slugs in the former of each coil are adjusted for maximum volume. Although cheap diodes can be used in this circuit it is not advisable to do so. Better quality and a stronger signal will be obtained by using good diodes. G.D.3, G.D.5, or G.E.X.34 are recommended.

As is well known it is difficult to reach a satisfactory compromise between selectivity and sensitivity in a crystal receiver. Whilst this receiver is better than most, it was nevertheless found necessary to introduce a further measure of control by arranging for means of increasing or decreasing the coupling between aerial/earth coupling coil and the tuned winding. For this purpose a .0005 μ F variable condenser of the mica dielectric type was connected across the coupling coil. A small coil (100 turns of No. 30 enamelled or D.S.C. wire on a $\frac{1}{4}$ in. diameter Alladin former) tuned by a 100 pF trimmer may also be inserted in the aerial lead as an alternative connection to vary the coupling. Thus means were provided for obtaining sufficient selectivity without a marked diminution of sensitivity for what is essentially a local station receiver.

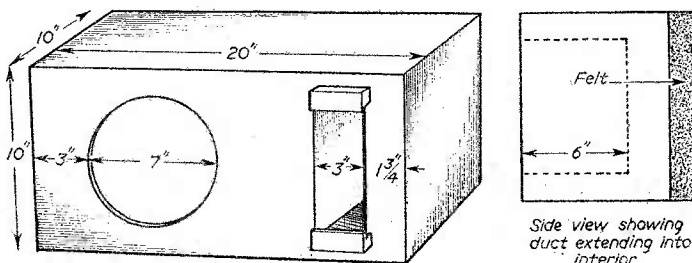


Fig. 3.—Details of the cabinet.

The Amplifier Stage

The amplifier employs three junction transistors, one Mullard OC71 in the driver stage and two Mullard OC72's in push-pull in the output stage. The output from the detector is matched into the amplifier by a step-down transformer, ratio 5 to 1. A small fixed condenser, value 50 to 100 pF, is connected across the primary to eliminate a slight whistle which may sometimes be noticeable. Volume-control is provided by the variable resistance across the secondary of the same transformer. This should have a total resistance of 5,000 to 10,000 ohms and, unless provision is to be made for a separate on/off switch, it should have a double-pole on/off switch incorporated.

A similar type transformer, ratio 5 to 1 step-down, but with a centre-tapped secondary winding, is used in the output stage. Both transformers can be supplied by Messrs. H. Ashworth, of Bradford, at

modest prices. The output transformer needs a centre-tapped primary winding and should also match the speech coil of the loudspeaker used. However, matching is not critical, and for a 3-ohm P.M. speaker ratios between 25 and 45 to 1 have proved satisfactory. A fixed condenser across the primary of the output transformer improves quality and tone. The value of this is best found by trial and error, but a

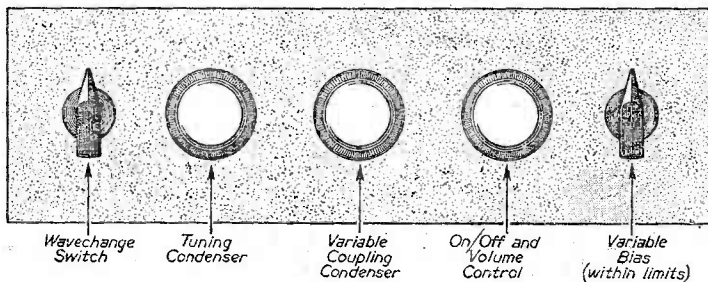


Fig. 2.—The panel layout and controls.

value somewhere between .0005 and .005 μF should prove satisfactory. Biasing arrangements are as

LIST OF COMPONENTS

L1—100 turns of No. 30 wire on $\frac{1}{4}$ in. Alladin former.

L2—Teletron coil HD2.M.

L3—Teletron coil HD2.L.

Trim 1—100 pF trimmer.

C1—.0005 twin gang variable condenser, miniature type.

C2—50 to 100 pF fixed condenser.

C3—8 to 12 μF electrolytic type condenser, test 25 volts upwards.

C4—.0005 to .005 fixed condenser.

C5—.0005 mica dielectric variable condenser.

SW—4-pole 2-way rotary switch.

2 diodes, G.D.3 or similar.

T1—Step down transformer, ratio 5 to 1 (H. Ashworth, Bradford).

T2—Step down transformer, ratio 5 to 1, centre tapped secondary (H. Ashworth, Bradford).

T3—Output transformer, centre tapped primary, to match speaker.

R1—220 K ohms.

R2—18 K ohms.

R3—1.5 K ohms.

VR1—5,000 to 10,000 ohms variable resistance with 2-pole on/off switch.

VR2—1 K ohms variable resistance.

One Mullard O.C.71 junction transistor and two Mullard O.C.72 transistors (to be purchased as a matched pair).

Three $\frac{1}{2}$ volt flat flashlamp batteries.

Aluminium sheet, insulating tape, connecting wire, wood screws, plywood, Bostik, nails, grille, knobs, sockets, plugs, flex from receiver to speaker.

Loudspeaker 8 in. P.M. type, although any similar speaker irrespective of size is suitable.


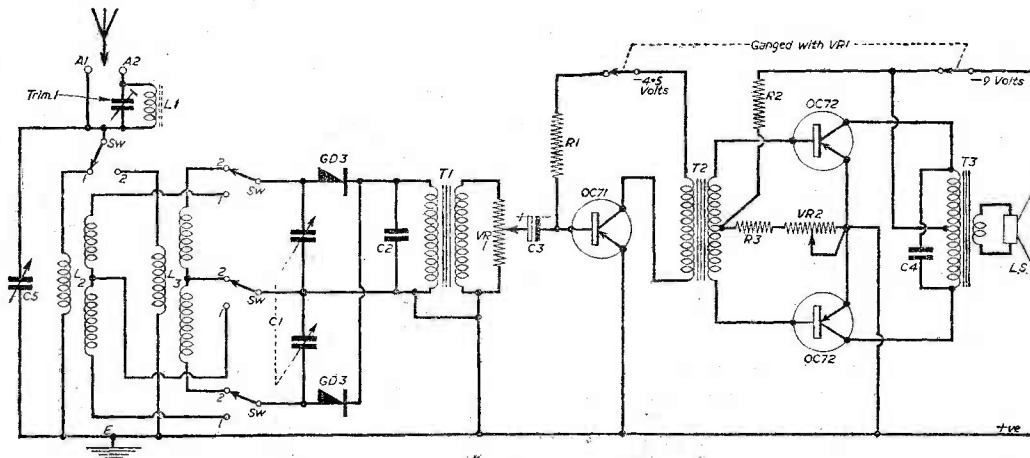


Fig. 1.—Theoretical circuit of the quality diode-transistor receiver.

follows : a 220 K Ω resistance supplies fixed bias to the OC71 from the 4½-volt battery, whilst bias to the push-pull stage is controlled by a fixed resistance of 18 K Ω (R2) and a combined fixed resistance of 1.5 K Ω and a variable resistance of 1,000 ohms (R3 plus VR2). It should be noticed that separate batteries are used for the driver stage and push-pull stage. The latter requires a nine-volt battery which may be two flashlamp batteries, each 4½ volts con-

4½in., cut out of 5/16in. and 3/16in. plywood respectively. It was arranged for the top to be sliding (see details later).

First of all the front panel was drilled to take the controls and then the bottom and side pieces nailed on. The various components were mounted in the positions shown in Fig. 2. However, this layout may be varied to suit the components since an ordinary size .0005 twin gang variable condenser may be used in place of the miniature type specified. The transformers should be placed away from the coils and also as far apart from one another as possible. A clip was made to hold the three flashlamp batteries. This was made out of aluminium sheet-size 6½in. by 2in. bent twice at right angles to leave a space 2½in. between to take the 3 batteries. Two holes were drilled in the base of the clip to enable it to be screwed to the wood base of the cabinet. One coil was mounted on the base and the other on the

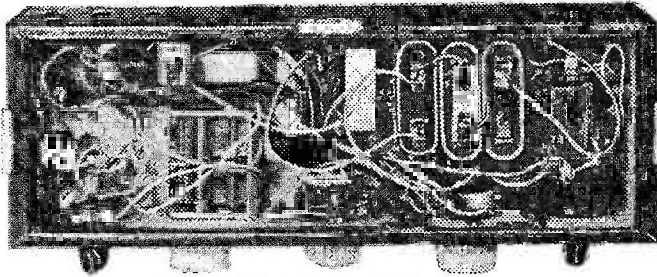

A view of the inside of the receiver.

nected in series. Separate batteries were decided upon for the two stages in order to avoid the extra drain which would have occurred on the first 4½ volts had a tapping been made use of.

Constructional Details

Since the object in producing this receiver was to obtain quality, it was considered necessary to use separate cabinets for the receiver and loudspeaker. A great advantage of transistor receivers is that they can be made very compact. Accordingly, a small oblong receiver unit was decided upon. This was constructed of plywood and covered with rexine cloth after mounting the components and completing all the wiring except the wires leading to the aerial and earth and loudspeaker sockets on the back panel. These were wired later.

The dimensions of the cabinet were as follows : front and back panels, 12½in. by 3½in., cut out of 3/16in. plywood ; side panels, 3½in. by 3½in., cut out of 5/16in. plywood ; bottom and top, 12½in. by

side of the cabinet. Holes were drilled in the back of the cabinet to take the aerial and earth sockets and loudspeaker sockets but the back was not nailed on until all the wiring had been completed, leaving just the connections to these sockets to be completed. The wiring is straightforward ; the only precautions to be observed are in the soldering of the diodes and the transistors, and battery connections. Transistors can easily be damaged by heat and the leads should be held with pliers until the soldering is completed, and allowed to cool. Needless to say a method of soldering should be adopted which allows for speed. Thus the leads should be well tinned first and strip soldered by holding the two connections side by side with pliers and applying the soldering iron quickly and removing quickly. Although the need for taking care in the soldering of transistors has been mentioned several times previously in PRACTICAL WIRELESS it cannot be too strongly emphasised that carelessness in soldering transistors will result in irreparable damage.

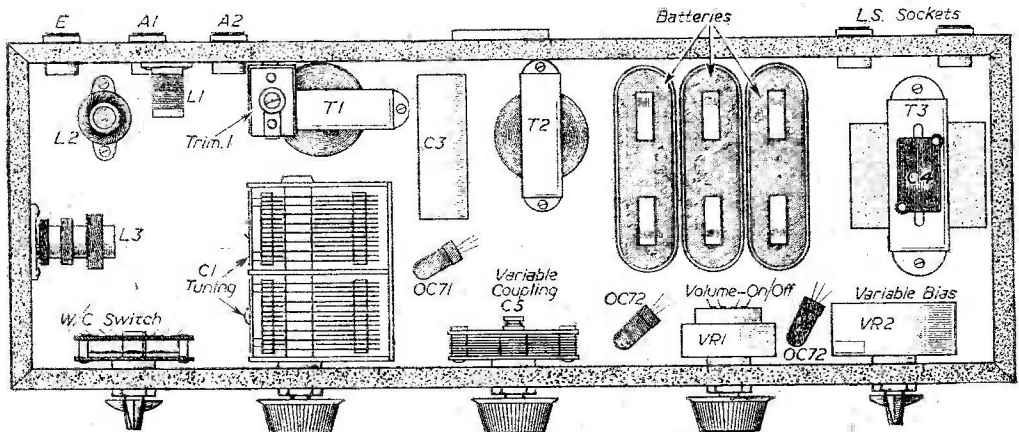


Fig. 4.—This diagram identifies the parts illustrated in the picture above.

Care must also be taken when making the battery connections. Polarity must be strictly observed. If the batteries are connected the wrong way round the transistors will almost certainly be useless afterwards. Connections to the battery prongs were soldered to obviate any unwanted noise due to loose connections in the course of time. After the final connections to the sockets on the back panel had been made the panel was nailed on and the cabinet covered with rexine cloth taking care to make holes in the correct positions for the control spindles. The top was also covered with rexine. Finally, to complete the receiver cabinet three clips were made out of aluminium sheet, each being $1\frac{1}{2}$ in. by $\frac{1}{2}$ in. and bent over $\frac{1}{2}$ in. at the top. These were fixed with small screws, one at the back and one at each side in such a position that the top panel could slide under them.

Testing and Adjusting

Before switching on the receiver the wiring should be carefully checked, being particularly cautious in noting that the battery and transistor connections are correct. The local station should be tuned in first on the long and then medium wave and the iron-dust slugs of the coils adjusted for maximum volume. The adjustable (variable) bias resistance, VR2, should be turned to give clearest reception. It should be noted that the bias to the push-pull stage is only variable within certain limits, and it has been so arranged that there is no possibility of exceeding working limits for the transistors, provided the power supply does not exceed 9 volts. If a continuous howling sound occurs when the set is switched on the set should be switched off and the fault located. Possible causes are interaction between transformers and coils if these have been fixed too close, secondary winding of transformer not connected to earth, bias resistances not being of the correct value. As the wiring is not complicated it should not be difficult to trace the fault.

Quality and volume from this receiver are surprisingly good and it is advisable to take some trouble with the loudspeaker arrangements.

The Loudspeaker Cabinet

It was decided to use an 8in. P.M. speaker. First of all experiments were carried out with the speaker mounted on a large baffle board constructed of $\frac{1}{2}$ in.

plywood. The results were compared with those obtained by mounting in a bass reflex cabinet. The latter proved very satisfactory but as space was at a premium it was desired, if possible, to obtain similar results with something less cumbersome. Accordingly a so-called Helmholtz type of resonator cabinet was constructed and this proved very satisfactory indeed. This type of cabinet is similar to an ordinary bass reflex kind but behind the port is a duct leading into the interior of the cabinet. The size of opening has to be found by trial and error or else means adopted to enable one to vary the size at will.

An examination of Fig. 3 will provide the reader with all the necessary details to make a similar cabinet. Whilst the method of varying the opening adopted by the author is satisfactory it does not result in such a pleasing appearance as would be obtained by inserting the sliding panel at the side of the cabinet and extending the grille over the entire front of the cabinet. It is also suggested that covering with Formica would be better than rexine.

The cabinet requires two panels of $\frac{1}{2}$ in. plywood 20in. by 10in. for the back and front, two side pieces of the same plywood size 9in. by 10in., and two pieces 19in. by 9in. for the top and bottom. The front panel requires a hole 7in. in diameter for the speaker and an opening at the other end 7in. by 3in. for the duct. The duct was made out of $\frac{1}{2}$ in. plywood, two pieces 3in. by 6in. and two pieces $7\frac{1}{2}$ in. by 6in. The slide was $\frac{3}{16}$ in. plywood, size 4in. by 8in., held in position by two grooved pieces of $\frac{1}{2}$ in. plywood. A piece of $\frac{1}{2}$ in. felt, size 7in. by 9in. was stuck on the inside surface of the back panel behind the duct. The duct is "tuned" by means of the sliding panel. The cabinet was completed by fastening a grille over the front with beading.

The results from this arrangement were most pleasing to the ear and many P.W. readers who have not tried this type of enclosure would no doubt find it of advantage to do so, particularly where good response from a speaker is sought without an unduly large cabinet.

In conclusion it should be pointed out that there is nothing to prevent the reader from assembling the transistor receiver and the speaker in the same cabinet. However, by keeping them separate the speaker can be at one side of a room whilst the tuning is near at hand, say at the side of one's armchair.

News from the Clubs

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec. : C. H. Bullivant (G3DIC), 25, St. Fillans Rd., Catford, S.E.6.

THE annual Christmas Party is being held on 14th December, and as usual a Constructional Contest will form one of the many attractions. A fine selection of useful prizes is being offered and a good entry is expected.

December diary :

7th—Ragchew.

14th—Christmas Party.

21st—Constructional Evening.

28th—Quiz.

Meetings are held every Friday at 7.30 p.m., at the clubrooms, 225, New Cross Road, S.E.14, when visitors and new members will receive a warm welcome. Details of membership can be obtained from the Hon. Secretary.

EAST KENT RADIO SOCIETY

Hon. Sec. : D. Williams, Llandogo Bridge, Nr. Canterbury.

THE above society is now meeting at Headquarters, Technical College, Longport St., Canterbury, after holidays. Several new members have enrolled and one member has received his call sign, G3LIG. R.A.E. classes have started, given by the

Hon. Sec. Several members have reached speed of 20 W.P.M. in O.W. classes. It is hoped to have a Tx on the air next year. New members and visitors are welcome.

WALSALL AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : F. J. Merriman (G2FPR), 123, Wolverhampton Road, Walsall.

THE Club meets at the Bradford Place Technical College Annex, in Walsall, on the second and fourth Wednesday in each month. There is a free room, under adult education schemes. Fee is 5s. per annum and the only requirement for membership is a genuine interest in radio or TV. The Club has six licensed members and accent is usually given to practical aspects of the art when possible, and visits are also arranged to places of radio interest.

RAVENSBOROUGH AMATEUR RADIO CLUB

Hon. Sec. : J. H. F. Wishaw, 4, Station Road, Bromley, Kent.

THE members recently saw the film on Mullard C.R.T. construction. One member has passed the R.A.E. recently; another is building a television Tx gear; and a further one is active with a Panda Cub Tx. The Club operates as G3HEV. Meetings held every Wednesday, 8 p.m. in Science Room, Durham Hill School, Downham—S.W.L.s welcomed

Operating Battery Sets from the Mains

SIMPLE CIRCUITS FOR THE CONVERSION UNITS TO TAKE THE PLACE OF BATTERIES

WHEN mains become available it is often worth while operating an existing battery-type receiver from them, and this is also of great advantage with a portable which is only used out-of-doors during the summer. With mains operation the trouble of replacing batteries is avoided and running costs are very greatly reduced, becoming so small as to be almost negligible. When the cost of a suitable eliminator is balanced against that of the batteries normally used in 12 months, the saving will be very apparent. In addition there is no need to make any alterations to the receiver, which can be used again with a battery when necessary. A portable may thus be mains operated in the winter and serve its usual function, with battery, in the summer.

Two supplies will be necessary to replace the high-tension and low-tension batteries. The older type of battery set will require 2 volts for filaments (to replace accumulator) and 120 volts for H.T. All-dry receivers will usually require 90 volts H.T., and 1.4 volt or 7.5 volts L.T. The voltages necessary will immediately be seen from the usual battery portables often using combined H.T. and L.T. batteries. For satisfactory mains operation the eliminator will have to provide

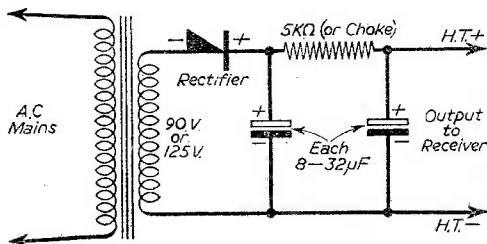


Fig. 1.—The H.T. unit circuit.

these voltages. A little change in H.T. voltage will be of no importance, but the filament voltage will require to be carefully adjusted if the valves are to have a normal life. In any case, it is best to deal with H.T. and L.T. sections of the eliminator separately. There is, of course, no reason why a simple circuit providing H.T. or L.T. only should not be used; when this is done the eliminator is usually for H.T. only in view of the simplicity with which this may be obtained.

H.T. Section

Though current may be derived directly from the mains, this is not recommended, since a transformer isolates the receiver. A suitable circuit appears in Fig. 1. Due to the small current drain, half-wave rectification is satisfactory and no smoothing difficulties arise. Eliminator transformers usually have H.T. secondaries of 90 or 125 volts, and the appropriate voltage is selected for the receiver. A 90- or

125-volt half-wave metal rectifier is satisfactory and occupies little space. If space is unimportant, a 250 volts or similar rectifier, if to hand, is equally suitable. A 20 mA type will deliver sufficient current, though there is no reason whatever why 40 mA or 60 mA rectifiers, if available, should not be used instead.

The capacity of the smoothing condensers is not very important, and they can be of 150 volts or higher voltage-working rating. It is essential that the correct polarity be observed in all the circuits, both as regards rectifier and smoothing condenser wiring. No H.T. smoothing choke is usually required, and a 5-K. 1-watt resistor replaces this. The actual value may be adjusted if necessary, as this will modify the H.T. output voltage to some extent.

The amount of smoothing required, both in the H.T. and L.T. sections of the eliminator, will depend largely upon the receiver. With a sensitive receiver more smoothing will be required than with a simpler set. Insufficient smoothing will be revealed by background hum. Should this arise it is usually quite easy to add further smoothing. Whether the hum arises from H.T. or L.T. supplies can readily be established

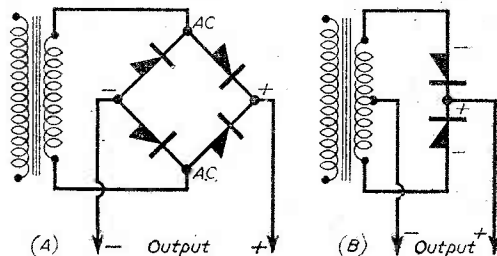


Fig. 2.—Details of L.T. supply circuits.

by drawing H.T. only from the eliminator, and L.T. from a battery, then vice versa. Only in exceptional circumstances (such as a faulty rectifier or condenser) will the H.T. system be responsible.

If the H.T. output voltage is measured with a meter it should be around that provided by the transformer secondary when the set is switched on. For all such tests (including L.T. measurements) a reliable test-meter of the type intended for radio servicing should be used. The cheap, low-resistance type of meter is not suitable and will give misleading readings, due to the current it consumes.

L.T. Supply

Full-wave rectification is best here to simplify smoothing, and "A" in Fig. 2 shows a bridge rectifier. The rectifier shown at "B" is a little cheaper for a given rating, but needs a centre-tapped secondary. The secondary also requires to be of twice the overall voltage—e.g., 12 volts centre-tapped for

6 volts output. As voltage drop arises later in the circuit it is desirable to provide an output of 6 to 9 volts from the rectifier for 1.4- and 2-volt receivers.

The current rating of the rectifier should be equal to, or larger than, the demands of the receiver. A $\frac{1}{2}$ -amp. type will suit small sets; few receivers will require more than $\frac{1}{2}$ amp. A 6- or 8-volt $\frac{1}{2}$ -amp rectifier would thus do well for almost any receiver. As with the H.T. circuit, larger rectifiers can be used if already to hand. With many types red and black will indicate positive and negative respectively, with green for the "A.C." tags in the bridge type.

The usual eliminator transformer will have the two secondaries required, so that only one transformer is necessary for both H.T. and L.T.

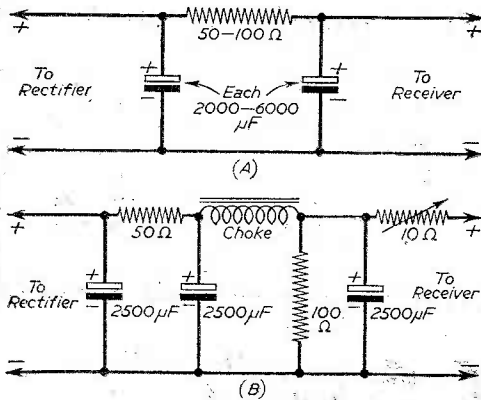


Fig. 3.—Smoothing circuits for L.T. supplies.

Considerable smoothing of the L.T. supply is necessary, to avoid hum, and the relatively heavy current makes minimum series resistance necessary with very large condenser capacities. The simplest circuit which can be employed with success is shown at "A" in Fig. 3 and is quite largely used. The exact value of the resistance depends upon transformer, rectifier and receiver, and is adjusted to obtain the correct filament voltage. With 2-volt valves, operation is less critical, but the filament voltage should be maintained within .2 volt of the correct figure. Normally, better than this will be possible, and a long valve life can then be expected. With the 1.4-volt type the actual filament voltage should lie between 1.25 volt and 1.4 volt. High filament voltages will cause rapid deterioration to the valves; while low voltages are also detrimental in due course. The actual voltage should thus be checked with a reliable meter and adjusted to 2 volts for 2-volt valves; and 1.3 volt for the 1.4-volt valve types. The meter must not be of a type taking a large current, or the voltage actually applied to the valves will rise when the meter is removed. Initially, it is wise to make a provisional voltage test with a dummy

load, such as a 2½-volt torch bulb, to avoid possible damage due to excess filament voltage.

At "B" in Fig. 3 a 10-ohm wire-wound resistor enables the filament voltage to be adjusted. This is of great advantage, though not provided in cheap, ready-made eliminators. In use, the resistor is reduced in value from maximum, until the filament voltage is brought up to the correct figure. No other adjustment is then necessary.

When further L.T. smoothing is required, a choke is helpful, but it must have a low D.C. resistance. The H.T. type of smoothing choke is useless, for this reason, but will serve well if rewound with wire of about 24 s.w.g. Here, some smoothing and further voltage-dropping is provided by the 50-ohm resistor. The 100-ohm resistor helps to keep the voltage down when no L.T. current is drawn. This is necessary when using condensers of very low rating, such as 3-volt and 4-volt types. The condenser wired to the rectifier should be of a high enough rating for this position—usually 8-volts to 12-volts. Any condensers of higher voltage rating will be perfectly satisfactory, but the high capacities shown are usually of very low voltage rating.

Initially, the circuit at "A" in Fig. 3 can be tried, and will often suffice. If difficulty arises in obtaining the correct filament voltage, the 10-ohm variable resistor can be introduced in one output lead. Should hum be troublesome, a choke or further smoothing condensers can be added. The more sensitive the receiver the greater will be the degree of smoothing required.

Complete Eliminator

Fig. 4 shows a complete circuit and will also help to make rectifier connections clear. It will usually be feasible to build up the unit to such dimensions that it can fit in the position previously occupied by the battery. If a socket from an old battery is fixed to the eliminator case, appropriately wired, it will only be necessary to plug in the receiver when mains operation is required, and a battery may at once be used again when wanted. The socket or sockets will depend upon the battery types. Correct wiring, here, will be absolutely essential.

The case is best made from insulating material, though metal can be used.


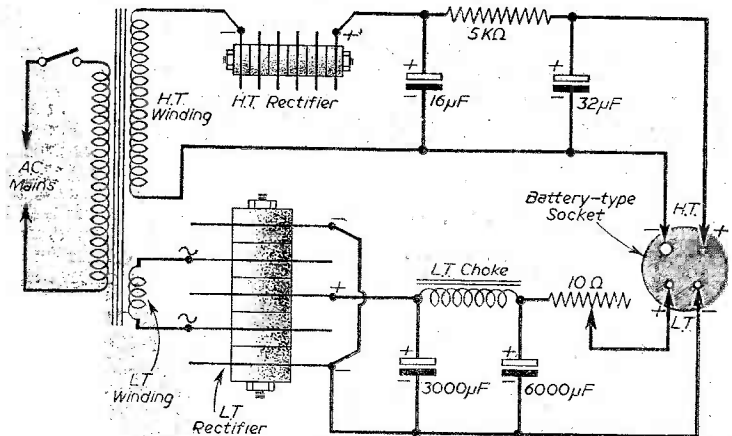


Fig. 4.—A complete H.T./L.T. battery eliminator.

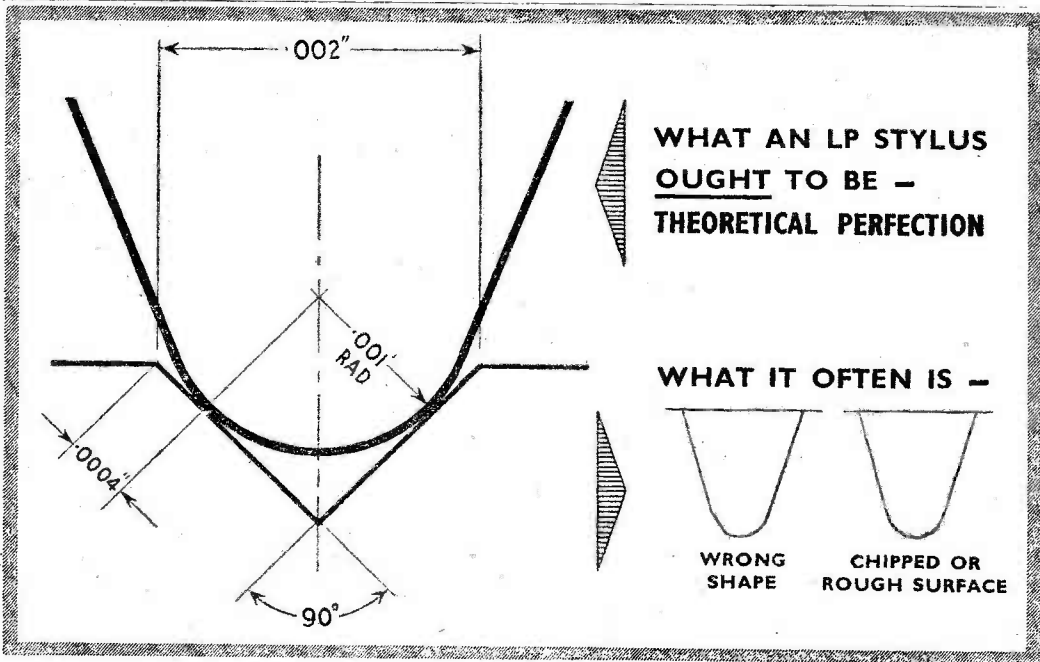

acos X 500 *


REPLACEABLE STYLI, AS FITTED TO ALL ACOS CRYSTAL AND CERAMIC PICK-UP CARTRIDGES HAVE PERFECT SHAPE, SIZE AND FINISH


* ACOS Styli have to pass a quality inspection at x 500 magnification. Only in this way can some faults, which may have important effects on reproduction or record or stylus wear, be reliably detected. The standards we set ourselves are high but practical. They are reflected not only in ACOS products but also in the record reproducing equipment in which ACOS pick-ups or cartridges are fitted.



always well ahead

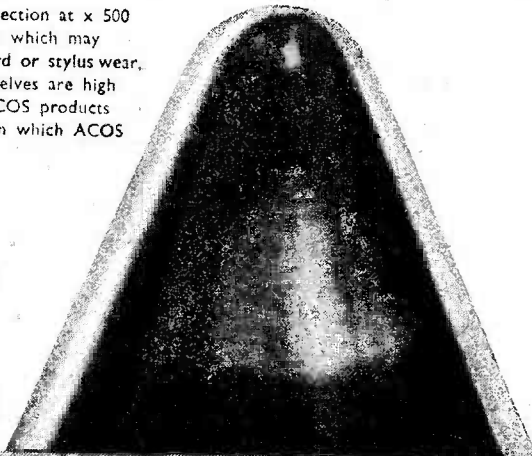COSMOCORD LIMITED. Eleanor Cross Road, Waltham Cross, Herts. Waltham Cross 5206



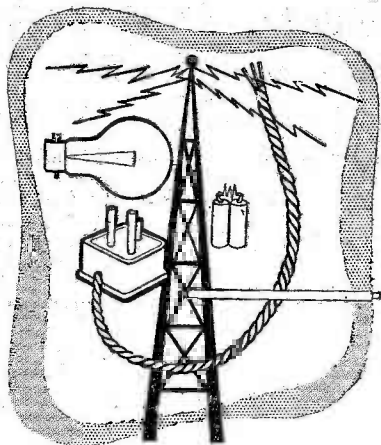

ON THE BEAM

Smith's have books on the newest developments in radio and television circuit design, construction and servicing. No matter what your problems or interests are, you can be sure of getting the books you need through your local branch of Smith's. Books not available on demand can be quickly obtained from Head Office. Lists of the standard works on any subject gladly supplied.

• Stationery and printing can also be supplied by your nearest Smith's branch.

W. H. SMITH & SON

for technical books

HEAD OFFICE: STRAND HOUSE, LONDON, W.C.2

GLADSTONE RADIO—

Again the Lowest price

QUALITY F.M. TUNER UNIT

SPECIAL PRICE

(P. & P. 2/6—C.O.D. 1/6)

£5-12-6

Circuit similar to that described in Data Publications, Ltd., Radio Reprint No. 2 (3rd Edition). Price includes all components, including chassis, dial, drive, diodes, valves, nuts, bolts and, in fact, everything needed. This is a kit.

Extra components for Fringe Area, 15/-.
Power Pack Components, 30/- extra.

WHY PAY MORE?

Booklet, 2/3 (supplied with orders). Write for details (S.A.E., please).

GLADSTONE RADIO

P.O. BOX 8, 82B, HIGH ST., CAMBERLEY,
SURREY

Open Saturdays to 5 p.m.

COMMUNICATIONS RECEIVER R.1155.—The famous Bomber Command Set. Covers 18.5-7.5 Mc/s, 7.5-3.0 Mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s. BRAND NEW. ONLY £11.19.6, tested working before despatch and supplied with 14-page booklet which gives technical information, circuits, etc. (available separately 1.3).

A.C. MAINS POWER PACK OUTPUT STAGE.—In black metal case. Enables receiver to be operated immediately by just plugging in. Supplied WITH built-in 6 $\frac{1}{2}$ " speaker, £5.5.0 or De Luxe Model with 8 $\frac{1}{2}$ " speaker, £6.10.0. LESS speaker £4.10.0. DEDUCT 10/- IF PURCHASING RECEIVER & POWER PACK TOGETHER.

Add carriage costs of 10/6 for receiver, 5/- for power pack.

AMERICAN "COMMAND" RECEIVERS.—Huge purchase from the Air Ministry. These famous compact receivers which can be used for a variety of purposes are offered at ridiculously low prices while stocks last. Complete with 6 metal type valves, 1 each of 12K8, 12SR7, 12A6, and 3 of 12SJ7, in aluminium case size 11" x 5" x 5". Used, but in very good condition, although cases may be somewhat dented. Circuits supplied. First come first served. Choice of models. BC454 (3-6 mc/s), 27/6. EC553 (190-450 kc/s, the renowned "A" Filter), 59/6, and a few of the 1.5-3.0 mc/s. model 65/- (Carriage, etc., 3/-).

COLLINS TCS TRANSMITTERS.—Special offer of these famous American Transmitters. Frequency range 1.5-12.0 mc/s. In 3 bands. Employs 7 valves, 2 of 12Z6 in P.A. Stage, 12Z5 buffer and 16Z5 modulator Stage, 3 of 12A6 in oscillator stage. Radio telephone or radio telegraph. Provision for VFO or Crystal Control. 4 crystal positions. Has plate and aerial current meters. In BRAND NEW CONDITION, ONLY £12.10.0. Matching receivers available £8.10.0, or THE PAIR £20. (Carriage 10/- each.)

CLASS D WAVEMETER

Another purchase of this famous crystal-controlled wavemeter which has been repeatedly reviewed and recommended in the "R.S.G.B." Bulletin as being suitable for amateur transmitters. Covers 1.5-9.0 mc/s, and is complete with 100,000 kc/s crystal, 2 valves EC935, two 6-volt vibrators and instruction manual. Designed for 6 v. D.C. operation, but simple mod. data for A.C. supplied. BRAND NEW IN MAKER'S TRANSIT CASES, ONLY £5.19.6. Transformer for A.C. modification, 7/6.

U.E.I. CORPORATION 138, Gray's Inn Road, London, W.C.1. (Phone: TERMINUS 7937)
Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station), and 5 mins. by bus from King's Cross.



On Your Wavelength

BY THERMION

More Swanky Pronunciations

DURING my month's listening, my blood pressure has again risen on a number of occasions, to hear announcers refer to Field Marshal Montgomery and Sir Crompton Mackenzie, and Fay Crompton. Now Crompton is a good old Scottish name, and all those possessing it either as a Christian name or as a patronymic are known as the name is spelt. There may be those who like to give the impression that they are a very special brand of Crompton, by calling themselves Crompton, but it is pure snobbery and it is incorrect. Dennis Crompton resented being addressed as Crompton and made a public protest about it. So all of the Cromptons must take note that they will not be referred to by me as Crompton. Most of the announcers seem to have difficulty, like the Yanks, with the vowel sounds. Our announcers like to "put it on," whereas the Yanks especially those who cannot speak let alone sing, like to refer to Rark 'n Rawl. Could not the BBC rehearse them a bit before they are allowed to offend the ear on the air?

Magnetic Tape Player

THE Radio Corporation of America has developed a magnetic tape player which can produce recorded sound and pictures through an ordinary television receiver. Details, however, have not been published, although it is now well-known that this company has developed a method of recording television signals on tape. The problem is the high speed of the tape—something like 15ft. per second.

It is inevitable that we must be able to record television programmes as we can now record sound programmes. The expense of staging a live broadcast of a television play can only be reduced by some such system.

Hot Gospelling

I AM gratified that a large number of readers agree with my views on the hot gospellers who spout their nonsense night by night from Radio Luxembourg. After all, most of this hot gospelling is a highly profitable business, some of it existing to sell religious newspapers. As it is therefore just a commercial business, it is proper, I suppose, that it should buy programme time from this commercial radio station. These ranting, religious revivalists and would-be spell binders do not achieve much. When W. Graham was over here for example, the effect of his perfervid oratory was very short lived. People flocked to see him, not because they wanted their souls saved, or that they were in need of spiritual redemption, but purely as a matter of curiosity. Of the large number who attended one of his gatherings here, only a hundred or so remained afterwards as converts. I have always considered it a shocking thing that the Archbishop of Canterbury should have appeared with W. Graham on the platform at Wembley Stadium. If Cantuar has some

time on his hands there are plenty of English institutions, longer established which could do with his support. Be it noted that W. Graham did not accept my challenge to a public debate, so that I could pulverise the stupid beliefs which he is trying to promote. One or two readers have profoundly disagreed with my views, and like the revivallists have quoted the Bible at me, but the devil can cite scriptures and such quotations leave me cold, because I could find a biblical quotation which cancels any one of them out. Really I feel quite sorry for those who believe in the trash which these vain spouters put over. They have inordinate conceit under their outward façade of modesty. They believe that they are great orators when some of them are just humbugs, earning a fat annual fee for it. I wonder if they would remain if the fee were to be withdrawn?

There is one thing which can be said about the BBC religious programmes, they are conducted in accord with the tenets of Christian teaching. They are sincere, and free from ballyhoo. My only fear is that some of them may try to imitate the Yankee hot-gospellers, the modern Sankeys and Moodys, and the Aimee Macphersons. They found it very profitable; but where is the effect of their hot-gospelling today. It soon wears off. Take Graham's campaign over here. It is obvious that it has had no enduring effect. As a form of entertainment or as a variety show it can be justified, just as a crowd will find interest in flocking to see Siamese twins.

Transmitters for Tyre Pressures

AN interesting application of radio to automobile practice is the use of tiny transmitters to indicate tyre pressures. Fixed to each wheel of the car are miniature radio transmitters which are actuated by a switch which is closed when the tyre pressure drops to the danger level. A small receiver fixed to the fascia receives impulses radiated by these transmitters. It is an American invention giving a different frequency to each tyre, represented on the fascia by coloured light indicators.

Save Us From It

THE Burroughs Corporation of America has announced that it has built an electronic brain melody maker, an electronic device, which, by a series of electronic permutations will produce a melody at the press of a button. This has caused consternation in that home of raucous cacophony Tin-Pan-Alley. No longer, if this machine comes into general use, will it be necessary to publish music composed by Al this, Ed that, and Lou the other. It is claimed that the device can produce at least 1,000 melodies an hour, and that it can turn out more than 10,000,000,000 different tunes without human intervention of any sort. Let us hope, however, that the machine gets the pronunciation right and that it learns to speak English!

EQUALISING CIRCUITS

USEFUL DESIGN DATA FOR THE A.F. ENTHUSIAST

By Hugh Guy

Introduction

A SEEMINGLY endless topic in the field of radio engineering concerns the design of frequency correcting circuits. In audio frequency work they are found in their simplest form as tone control circuits in radios and radiograms, while the more sophisticated versions are widely used in "hi-fi" reproducers, where they are known as equalisers. In video apparatus, too, particularly in television camera circuitry, they are extensively employed this time labelled compensating networks. Whatever their title, and whatever their function, however, each and every one basically performs the same task—namely, that of correcting frequency distortion.

Many mistaken ideas exist about frequency correction, with the result that the enthusiast is sometimes at a loss to know how to design a circuit to correct for any inconsistency in a particular piece of equipment.

This short series sets out to explain the process, and one or two simple design formulæ and practical examples are given to enable the constructor to devise his own circuits without the customary hit and miss approach, which, though sometimes successful, so often leads to frustrating results. Though confined principally to audio frequency circuitry, the techniques outlined in this article are nevertheless identical in some cases to video work, a fact which the enterprising reader will be able to utilise, be he a television enthusiast.

Mechanism of Equalisation

The term "poor frequency response" is often applied to, say, an amplifier to indicate not that the bandwidth of the amplifier is small, but rather than the band of frequencies which the amplifier handles are not all amplified to the same extent. It may be that the middle frequencies from, say, 400 cycles to 3,000 cycles per second are amplified equally, but that as one approaches either the low or the high frequency part of the frequency spectrum the amplification becomes progressively less. This type of response is usually the case with a poor amplifier and is shown in the response curve of Fig. 1. Ideally, all the frequencies must be amplified equally, when

the straight characteristic of Fig. 1 would represent the response.

However, the requirements of high gain and constant amplification over a wide band are incompatible and usually ineffective in the case of audio frequency amplifiers, where the source feeding the amplifier does not itself have a flat characteristic. It is customary, therefore, to incorporate networks in A.F. amplifiers whose function it is to alter the frequency characteristic of the incoming signal, so that, in conjunction with the response of the amplifier itself, the final output is as nearly constant at all frequencies as possible. If, for example, the signal fed to an amplifier was finally reproduced with the frequency response of Fig. 1, then a network would be included having the inverse characteristic shown dotted in Fig. 1. The effect would be to allow greater amplification of those frequencies attenuated most in the reproducing equipment resulting in a flat overall output.

In most cases the A.F. amplifier is built to be fed not by one specific type of input, but usually by an input or inputs with unknown characteristics. Therefore, the equalising network incorporates controls to give it a variable equalising characteristic, allowing near-perfect compensation for a variety of inputs.

Estimation of Response

Fundamentally the problem confronting the constructor is, what is the frequency characteristic that is to be compensated? The best way of ascertaining this is by means of a variable frequency source and an oscilloscope or valve-voltmeter.

Either or both of the latter two instruments are connected across the output terminals of the amplifier, which at this stage incorporates no equalising network.

Now the variable frequency source can take a variety of forms: if the amplifier is to be used principally in conjunction with a pick-up, then the source should be a frequency test record. If it is a tape recorder amplifier, then obviously a frequency run on tape should be available. The amplifier alone may be tested by using an audio oscillator of variable frequency. Whatever the source, however, its one

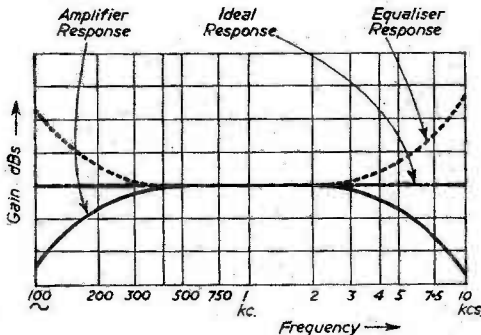


Fig. 1.—Amplifier and equaliser responses.

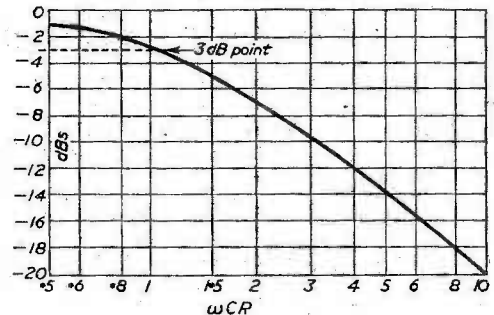


Fig. 2(b).—Impedance versus frequency design curve. Note that the 3dB point is at $\omega CR1$.

important feature must be that of having a constant signal amplitude over the band of frequencies it is reproducing.

In the absence of expensive monitoring apparatus such as the oscilloscope and valve-voltmeter, the enthusiast with a discriminating ear can readily detect changes in level of 2 db. and can, therefore, act as his own monitor. The justification here is that in the end it is the human ear which will be the final judge of performance.

The results of a frequency run should be presented in graphical form, plotting gain against frequency, thereby simplifying the task of devising correcting networks by having available a picture of the response and its deficiencies.

It is at this stage invariably that the enthusiast is at a loss. Very often he knows the shortcomings of his gear, but is unable to hit upon a suitable method

same valve can be the equalising stage in a pre-amplifier.

Fig. 2(a) shows the circuit as described. In parallel with the anode load R is a condenser C. Being a pentode stage the gain is $G_m Z$ where G_m is the mutual conductance of the valve and Z is the impedance of the parallel combination. Examination of this impedance shows why the circuit acts as a treble attenuator.

The impedance is :

$$Z = \frac{R}{\sqrt{1 + (\omega CR)^2}} \quad \text{where } \omega = 2\pi f$$

and f is the frequency.

As the frequency increases the term in the square root increases and thus Z diminishes. The gain therefore reduces at high frequencies, and the effect of treble attenuation is produced.

Fig. 2(b) shows a graph, the horizontal axis of which is plotted in terms of the product ωCR , illustrating the way in which Z becomes progressively less as ωCR increases. The vertical scale is $\frac{1}{\sqrt{1 + (\omega CR)^2}}$

and is given in decibels. This graph shows clearly that while ωCR is less than one, the impedance is nearly constant. When ωCR equals one, however, the impedance starts to reduce. This point is known as the 3 db. point as the impedance is 3 db. down on its level at zero frequency, and is used to define the turning point or upper limit of impedance. Beyond this point the graph shows a nearly steady fall, and Z reduces at approximately 6 db. per octave.

To design a simple treble attenuator, the designer must know the required 3 db. limit, and the gain desired from the stage at low frequencies. Here ωCR is arranged to be very much lower than one, and hence can be ignored. The gain is then simply $G_m R$.

Design Example

If a stage giving a low frequency gain of 100 were required, using a valve with a G_m of 3 mA/v, then the value of R would have to be 33K. If the 3 db point were fixed at 5 kc/s, then the necessary value of capacitor C would be approximately 1,000 pF, quoting the nearest available value. This is easy to verify since at the 3 db. point, the gain is 0.707 of its original value, and $\omega CR = 1$. In other words, the 3 db. point occurs when the reactance of the condenser $1/\omega C$ and the resistance of the anode load R are equal.

If the 3 db. point is not known, but the amount of treble attenuation desired at a particular frequency has been decided, then the graph of Fig. 2(b) can be used to assist the design.

Quoting the example above, if the treble response must be attenuated, say, 20 db. at 15 kc/s on the low frequency gain of 100, then the graph shows that $\omega CR = 10$ approximately.

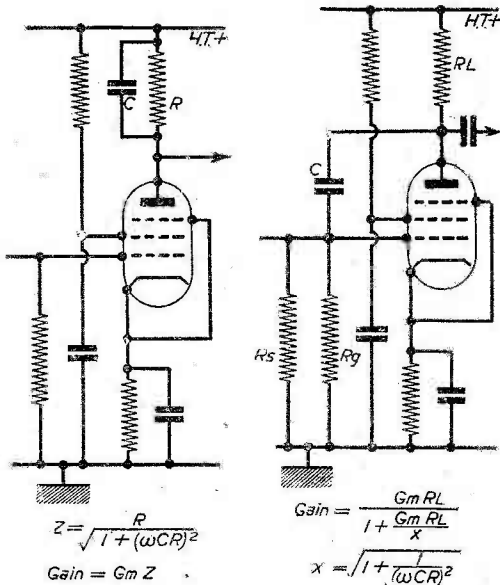


Fig. 2(a).—The R.C. circuit referred to.

Fig. 3.—Treble cut using negative feedback.

of improving the response. However, by examining the characteristics of one or two simple networks it is possible to draw some interesting conclusions leading to the design of equalising circuits to meet a wide variety of requirements.

Treble Attenuation

The simplest method of limiting the treble response of an amplifier is to connect a condenser across the terminals of the source. Now the "source" can be one of several things. If we are considering the amplifier alone, then it can be the anode load or grid leak of any of the stages in the amplifier. If it is a pick-up, then this is the source, and likewise with any other form of input. To simplify the process and to obtain the most useful result we will consider a valve with a resistive anode load as a source. This valve might very well be part of a resistance-capacity coupled stage in the amplifier, and later we shall see that this

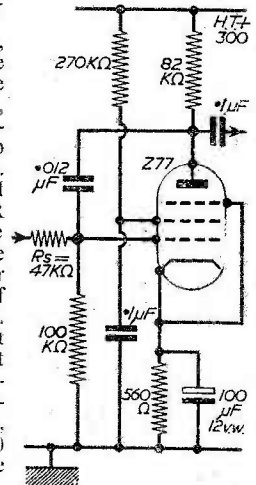


Fig. 4(a). — Practical treble cut circuit.

The value of C may be determined from this product since ω and R are both known, and the nearest available value that would be used in practice this time would be 3,300 pF. As a matter of interest, with this value the 3 db. point would be 1.465 kc/s.

Naturally the same rules apply for treble attenuation across any resistive load and therefore the above method may be used to design a treble attenuator in the grid circuit of a valve which is fed by a pick-up. Here the value of R will be the resistance of the pick-up in parallel with the grid leak.

The practical version of the circuit of Fig. 2(a), must have a well decoupled cathode resistor. It is also customary to connect the condenser C either from the anode to earth or in parallel with the grid leak of the following stage. In either case the condenser is still effectively in parallel with the anode load.

This circuit is not by any means the only one that will produce a treble cut effect, but being the simplest is ideal for quick and easy design.

Furthermore it may be used with triode stages as well as pentodes if it is remembered that in the triode case resistor R consists of the anode load in parallel with the anode impedance, R_a , of the triode. This is easily explained by examining the expression for the gain of a triode stage. This is given by

$G = \frac{\mu R}{R_a + R}$ where μ is the amplification factor of the valve.

But $\mu = G_m R_a$. Substituting for μ gives

$$G = G_m \frac{R_a R}{R_a + R}$$

And the "resistance" part of this formula is the parallel combination of the anode impedance R_a and the anode load R.

Bass Boost Circuit

The name "bass boosting circuit" is something of a misnomer really. All such circuits, if they employ nothing more than resistors and condensers in a network, do no more than attenuate the treble frequencies, creating the effect of an increased bass response. The circuit just described is therefore really a bass boosting circuit, but a far better method of achieving this effect is to attenuate the high frequencies by frequency selective negative feedback.

It is well known that an amplifying stage with a gain G will have a reduced gain when negative feedback is applied. Consider the circuit of Fig. 3, for example. This consists basically of a pentode amplifier of much the same type as shown in Fig. 2. The difference here, though, lies in the condenser C, which feeds a large proportion of the anode signal back to the input. Thus condenser C forms a negative feedback path from output to input. The signal fed back will vary from very little at low frequencies to nearly all of the output at high frequencies, depending directly on the reactance of condenser C.

The expression for the gain of the amplifier in this mode of connection is shown in the figure, and is:

$$G = \frac{G_m R L}{1 + \frac{G_m R L}{x}} \quad \text{or} \quad \frac{x}{1 + \frac{x}{G_m R L}}$$

$$\text{where } x = \sqrt{1 + \frac{1}{(\omega C R)^2}}$$

If the gain of the amplifier, $G_m R L$, is very high,

say, 200 or more, then the gain of the equaliser is approximately equal to x , and thus decreases with frequency. It should be made clear here that R is the parallel combination of the grid leak resistor (R_g in Fig. 3) and the anode load of the preceding stage, or the impedance of the input source if this is not a previous stage.

That is why the source impedance R_s is shown dotted in the circuit in Fig. 3.

A practical circuit of such an equaliser is shown in Fig. 4(a), and its response indicated in Fig. 4(b),

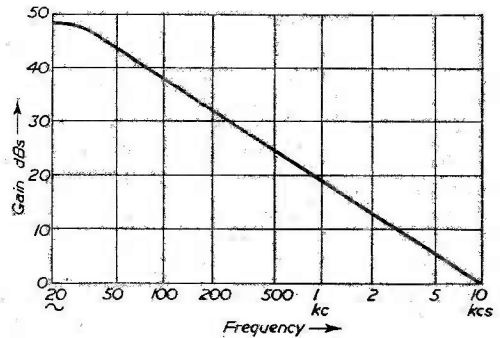


Fig. 4(b).—Response of treble cut circuit.

where the similarity in response with that of Fig. 2(b) may be seen.

The valve used in the circuit is the Osram Z77, a high slope pentode on a B7G base. Triode valves may also be used in the circuit, with less success, however. This is due to the difficulty of obtaining a high gain from a triode stage and the more accurate triode formula given earlier would have to be used, once again remembering that R_L is the parallel combination of anode load and anode impedance.

Either of the two types of circuit discussed so far is capable of producing treble cut and bass boost, since the overall effect is the same, as the graphs clearly show; the name by which each form of equalisation is known is largely fixed by the frequency at which the effect the circuit produces becomes apparent.

This similarity of function also exists between treble boost and bass cut circuits. The more precise collective title for these networks is that of "bass cut." Once again it is the 3 db. point frequency which decides the name, a high frequency 3 db. point giving rise to the term "treble boost," and a low frequency point to the second term.

(To be continued)

JOIN THE PRACTICAL GROUP

Edited by F. J. CAMM

PRACTICAL TELEVISION 1/3
Every Month.

PRACTICAL MECHANICS 1/3
Every Month.
Devoted to Mechanics, Science and Invention.

PRACTICAL MOTORIST & MOTOR CYCLIST 1/3
Every Month.

PRACTICAL HOUSEHOLDER 1/3
Every Month.

The Leak "Trough-line" F.M. Tuner

DETAILS OF A NEW IDEA IN F.M.
RECEPTION


AS a result of both modifications and tests over many months, besides user-tests with some 50 equipments, the Leak Frequency Modulated Trough-line Tuner is now in production.

It is radically different from any other F.M. receiver in its engineering design and circuitry. It overcomes the many disadvantages and faults of many other F.M. tuners or receivers. The quality of short-wave frequency modulated (F.M.) transmissions is better than that of the best recordings, provided the transmitted programme is "live" and that good land-lines are used between the studio and transmitter.


To get the utmost advantage of such superior transmissions, a first-class F.M. tuner is required. It must be sensitive, selective and have no drive after tuning into a station. The listener merely switches on, tunes in and then sits back in comfort.

The prevailing failures of many equipments are :

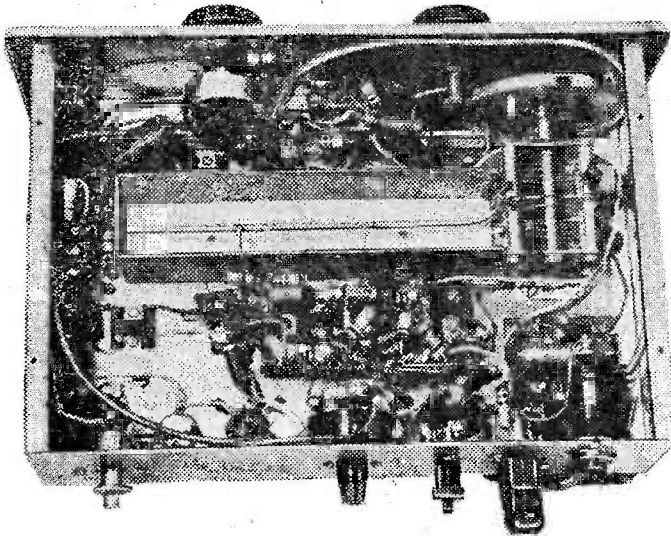1. Tuning drift so severe that the station will disappear as the set warms up unless the tuning knob is continually adjusted. This usually means a total drift over 100 kilocycles. For the quality of sound to remain unimpaired, it should not exceed 10 kilocycles per second.



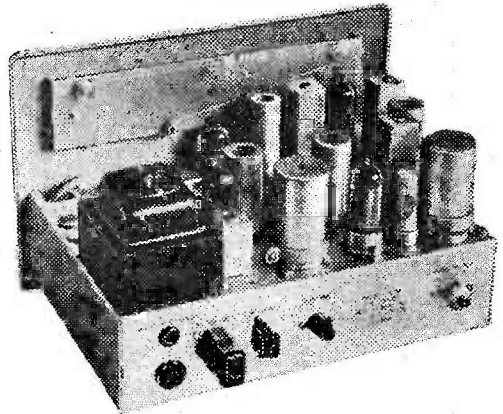This illustration shows clearly the novel "Trough Tuner" in the centre of the chassis.



General view of the new tuner.

2. The re-radiation from the tuner should be so low as not to interfere with TV sets in the house or, as is known, with neighbours' sets.
3. A tuning indicator or "magic eye" is often missing. It is impossible to be sensitive by ear to variations of 2-5 kilocycles per second when tuning or find the optimum tuning point. The tuning indicator enables it to be done.
4. The power supply should be built into the receiver.

What is Meant by "Trough-line"

The tuning inductor of the oscillator is a metal trough with a piece of metal passing the length of the trough without touching the bottom or sides. Certain connections are made to the long piece of metal.

The trough-line is employed by the oscillator. This set-up makes the Leak F.M. tuner, so H. J. Leak & Co. Ltd. believe, unique in the world.

The trough-line tuning inductor in conjunction with the application of automatic frequency control results in tuning stability within 5 kilocycles per second from the instant of switching on. The trough occupies much of the space under the chassis and provides some radio-frequency screening.

The oscillator operates on the high side of the signal frequency. Its output is injected into the coupling between the radio-frequency stage and the mixer with second channel signals attenuated at this point.

The intermediate frequency (I.F.) is 12.5 Mc/s. Usually it is 10.7 Mc/s. The 12.5 Mc/s is chosen because it ensures two things. First, the oscillator frequency never operates in Band II and cannot therefore cause interference with other receivers. Secondly, the harmonics of the I.F., generated in the later stage of the I.F. amplifier, do not fall within Band II. At an I.F. less than 12.5 Mc/s

such harmonics can be received as "dead" carriers.

The sensitivity is such that excellent reproduction is given whenever the signal appreciably exceeds noise level and is claimed to be the highest on the market. Full limiting for a signal is obtained at 4 microvolts per metre.

The "Magic Eye" connected to the discriminator output is a very sensitive indicator of mis-tuning. The eye input is short-circuited 50 times per second by small metal rectifiers supplied from the L.T. windings. When accurately tuned, the discriminator output is nil and the magic eye gives a very sharply defined crisp display. On mis-tuning, the discriminator output causes a blurred display.

Power supplies must be built into a low-distortion, sensitive F.M. tuner, because some 60 mA of H.T. and a few amps of L.T. current are used, and this demand is too great for the tuner to be powered from the "spare supply" socket of any available power amplifier.

Valves

The functions of the valves are :

Pentode radio-frequency amplifier; triode oscillator; triode A.F.C. reactance valve; pentode mixer; pentode first I.F. amplifier; pentode second I.F.

amplifier; pentode limiter; double-diode Deeley-Foster discriminator; triode cathode follower audio-output stage; magic-eye tuning indicator; full-wave H.T. rectifier.

To give the highest possible quality, the radio-detector valve is not used. The Seeley-Foster discriminator employing thermionic diodes has the preceding stage with a limiter, which eliminates amplitude-modulated signals. Thus, the receiver is not affected by ignition and other forms of impulse interference.

The output impedance is low. Long, screened leads can be used to connect the tuner to the amplifier without fear of attenuating or distorting the high audio-frequencies.

The output is approximately 1 volt peak. The tuner, therefore, can be used with any high-fidelity audio amplifier.

The field tests have brought in the opinion that this is the best British F.M. tuner there is, and every user was delighted with its sensitivity and selectivity, particularly in the fringe areas of V.H.F. transmissions.

Dimensions: 10½ in. by 7 in. by 7 in.

Weight: 10 lbs.

Price (retail): £25. Purchase Tax, £10 10s.

Power Supplies for Transistors

THOSE concerned with developments in the field of electronics have been aware for some time that the use of transistors would involve new techniques and that new sources of power would be needed to operate equipment containing them.

The first transistors commercially available here were small and low powered. They were well suited for hearing aid use where miniaturisation is a predominant feature. Since size is the determining factor and power is a secondary consideration, miniature and subminiature single cell and two cell batteries are commonly used.

To meet these needs the Ever Ready Company designed and developed the D20, D21, D22 and D23 Transistor Hearing Aid range. They now issue the following information.

During the current year in the United Kingdom transistors suitable for use in radio receivers, etc., and having a greater power output than those used in hearing aids have become commercially available. Though some types—particularly R.F. transistors—are scarce at the moment, it is expected that adequate supplies will become available during the next 12 months or so.

As a result a considerable expansion in the use of transistor operated equipment may be anticipated in that period. Included in this will be portable receivers of the brief-case type, personal and pocket radios, and in all probability a special set for use in the home. Their use in amplifiers has already commenced and the transistor record player may well become as familiar a household article as the present radio receiver.

To operate these appliances reasonably small low voltage power sources will be needed. For this purpose the appropriate dry battery offers a virtually ideal solution, combining reliability with low running costs. With these factors in mind the Ever Ready Company has developed and is now marketing a full range of transistor batteries capable of operating the various types of transistor equipment which will

be available in the foreseeable future. These batteries have the well-known "Batrymax" construction and consequently combine maximum performance with minimum size and weight. Reliability and economy in running costs are features of equal importance.


In connection with transistor equipment and the power sources employed, it is necessary to bear in mind that at the present time we are at the beginning of an era of great expansion. It is inevitable, therefore, that over the next few years considerable development and changes should occur. These changes in transistors and transistor equipment may well call for modification in the sources of power required to operate them. However, we can be reasonably certain that with the knowledge and experience at its disposal the Ever Ready Company will be able to meet those requirements adequately and provide suitable batteries for the purpose.

Bought All Your Christmas Presents Yet?

No? Then here's an idea. Why not send your friends who are radio-enthusiasts a gift you'd be delighted to receive yourself—a year's subscription for PRACTICAL WIRELESS? For twelve whole months your gift will bring them repeated pleasure, and each new issue will be a renewed reminder of your good wishes.

But the days are flying—you must order now to ensure that first copies arrive before Christmas. Simply send your friends' names and addresses with your own and remittance to cover (an annual subscription for PRACTICAL WIRELESS—12 issues, including postage—costs 18s. 0d.) to Subscription Manager (G.2) George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. An attractive Christmas Greetings Card, made out in your name, will be sent to announce your gift.

Build yourself a 75gns Radiogram for

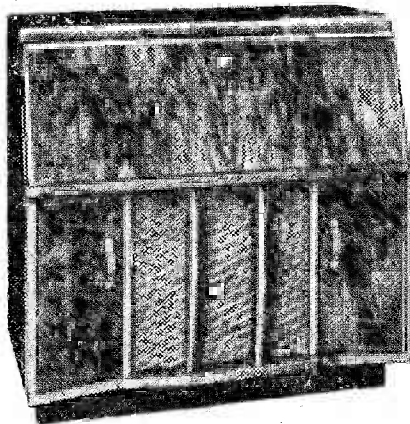

£54-7-6 only

CABINET CAT. NO. CAB/03

A magnificent Bureau-type Cabinet of the very highest quality in specially selected Walnut veneered exterior. Light Sycamore interior with Resine lining to match. Outside dimensions: length, 24in., depth 17in., height 33in. Sloping control panel on right-hand side approx. 16in. x 10in. Removable baseboard on right side approx. 15in. x 15in. *Packing and carriage 25/-.*

CASH **£17.6.6**
Or on Credit Terms.

CHASSIS CAT. NO. CR/AFM40/PP



9-valve Superhet with F.M./V.H.F. Band (4 wavebands). Push-pull output. Slow-motion tuning drive. Full provision of Automatic Volume Control. Sockets provided for Aerial, Earth, Gram, Pick-up and Extension Speaker. Connections provided to Gram. Motor controlled by Chassis On/Off switch. The tone-controls have been given an extra wide range to embrace all types of recordings. A.C. 200/250 volts 50 cycles only. *Packing and carriage 15/-.*

CASH **£27.6.0**
Or on Credit Terms.

AUTOMATIC RECORD CHANGER

CAT. NO. RC/A. The latest multi-speed changer incorporating 16 r.p.m. for "talking-books," and arrangement for manual control. Fitted with high-fidelity Crystal Turnover Pick-up Head. A.C. mains 200/250 volts 50 cycles only. *Packing and carriage 12/6.*

CASH **£9.15.0**

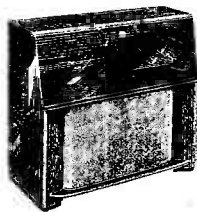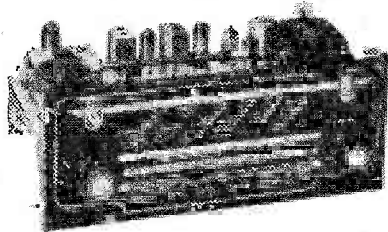

CABINET CAT. NO. CAB/02 ★

A well-designed Bureau-type Cabinet in a medium size. Veneered in a highly figured Walnut. Outside dimensions: length 20in., depth 16in., height 32in. Sloping control panel on right-hand side approx. 13in. x 10in. Removable baseboard on right-hand side approx. 13in. x 18in. Large record compartment inside the cabinet, located at the top on left-hand side.

CASH ONLY **12 Gns.**
Packing and carriage 20/-.

OTHER CHASSIS

CAT. NO. CR/A. 5-valve Superhet, 3 wavebands. **12 Gns.** *Packing & carr. 12/6.*

CAT. NO. CR/AFM47. 7-valve Superhet with F.M./V.H.F. Band (4 wavebands). **23 1/2 Gns.**

Or on Credit Terms.
Packing and carr. 15/-.

★ F.M. TUNERS ★

CAT. NO. FMT/A. Complete Unit in Cabinet with Magic-eye tuning. **16 1/2 Gns.**
Or on Credit Terms. *Packing and carriage 12/6.*

CAT. NO. FMT/B. Chassis only excluding magic-eye. Unboxed, 11in. long x 5in. overall depth x 4in. high. **CASH £13.15.0**

Packing and carriage 12/6.

★ L.C. SPEAKERS, GRAM, AMPLIFIERS, TAPE-RECORDER equipment, etc., available at keenest prices. Send for large illustrated Catalogue.

ALL FULLY GUARANTEED. Generous extended credit terms on orders exceeding £15. Dealers supplied at full discounts.

All enquiries to:

DOMESTIC

DIRECT SALES

LTD.

90 JUDD ST., LONDON, W.C.1


Telephone: FER. 9876

For a regular
smooth response curve

You need a PHILIPS

dual-cone loudspeaker

Made in Holland



The Philips dual-cone loudspeaker comes in two sizes: 8" and 12", price 63 gns. (tax paid) and 10 gns. respectively. There is also a single-cone loudspeaker, available in the same two sizes: price £6.2s. 6d. (tax paid) and £10.0s. 0d. respectively.

A special dual-cone design distinguishes Philips high fidelity speakers, resulting in energy transmissions almost independent of frequency. This ensures that, in an ordinary room, sound pressure within an angle of 90 degrees varies by not more than six decibels; while the excellent spatial distribution of acoustic energy—even at the highest frequencies—is obtained by Philips choice of coupling factor between high-range and low-range cones.



The small cone acts as a high note radiator for frequencies above 10,000 cycles and as a diffuser for frequencies below 10,000 cycles from the large cone. The large cone itself acts as a low note radiator below 10,000 cycles, and as a reflector for the high notes above this frequency. The distribution of sound over the entire frequency range is thus much wider than on a normal loudspeaker. These loudspeakers have a very smooth response curve combined with a low resonance frequency.

N.B. Any of these speakers may be used on their own or with another suitable loudspeaker using a crossover unit.

For full details write to:



PHILIPS ELECTRICAL LTD
Musical Equipment Dept. • Century House
Shaftesbury Avenue • London • WC2

(PR436)

FREE TO AMBITIOUS ENGINEERS!

This 144-page Book

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

FREE COUPON
Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME
ADDRESS
Subject or Exam
that interests me

British Institute of Engineering Technology
409B, College House, 29-31, Wright's Lane,
Kensington, W.8.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics,
Draughtsmanship
Television, etc.

GET SOME LETTERS AFTER YOUR

NAME!
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
I.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
GEN. CERT.
OF EDUCATION
etc., etc.

BIET

HANNEY of BATH offers:—

VIEWMASTER 3-STATION TV TUNER (P. Television).—Denco coilset with screens, can and screws, 30/-; Denco switch, Fine Tuner, Coil mounting plates and tag panel, 27/-; Kit of resistors, 7/6; TCC condensers kit with 2 printed circuits, valveholders, etc., 43/-; Gain controls, 3/3 each; Co-ax P/Skit, 2/6; Valve cans, 1/3 each. Complete kit of parts for the TUNER, with the 2 Genuine MULLARD Valves, nuts, bolts, wire co-ax, etc., £8/12/6. Denco Coilset for conversion of the V-Master S/V chassis to the I.F. amplifier, 20/-, OR Complete kit of S/V conversion components, 39/6. All Standard V-Master items in stock. Full list available.

MULLARD 510 AMPLIFIER.—Erie Resistors, 27/-; TCC Condensers, 45/-; Elstone Mains Trans., 36/- (100 m.a.); 42/6 (120 m.a.); Output Trans., 45/- (6K. or 8K.); Gilson mains trans., 60/- (140 m.a.); Output trans., 47/6 (5K. or 8K.); Ultra linear type, 52/6; Partridge Mains trans., 65/6; Output trans., P.3667, 55/6; Partridge Ultra Linear type P.4014, 98/6; Denco punched chassis, 19/6, with base plate; Printed front panel, 6/6; Type "A" and "B" Chassis (panel not printed), 8/6 and 12/6 respectively; condensers, "A" 15/6; "B" 24/6; Resistors, "A" 17/6; "B" 35/6 (with pots.). Full list available, giving details of complete kits.

OSRAM 912 PLUS AMPLIFIER.—Erie resistor kit, 17/4; Erie 1 meg. pots., 4/6 each; TCC condenser kit, 53/-; PART-RIDGE components with loose lead terminations (includes packing charge). Mains trans., 65/6; choke, 34/6; output trans., 85/6; W.B. components. Choke, 18/9; output trans., 32/-; Denco drilled chassis, 14/6; Denco 912 Plus printed panel, 7/6; pre-amp or passive chassis, 6/-. Full list available.

COMPONENTS are still available for the following F.M. TUNERS; Wireless World, Mullard, Osram 912, Denco Maxi-Q. List available.

WIDE ANGLE COMPONENTS. DENCO Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/6; Coil sets Magnaview, 41/2; WA/DCA1, 43/-; WA/FCAL1, 31/-; WA/LCL1 and WCL1, 7/6 each; WA/FMA1, 21/-; WA/LOT1, 42/-; WA/FBT1, 16/-.
Send stamp for lists. Please add 3/- postage to all orders under £5 (excess refunded).

L. F. HANNEY
77, LOWER BRISTOL ROAD, BATH
Tel.: 3811

POWER SUPPLIES

CONSIDERATIONS OF DESIGN WITH CONDENSER INPUT FILTERS

By E. G. Bulley

THIS article covers the essentials of what may be termed low power supplies necessary for the rectification of A.C. in radio receiver practice and similar equipments. Before proceeding, therefore, it is essential that the reader familiarises himself with the fundamentals of rectification using the condenser input filter. Fig. 1 is a typical half-wave supply, wherein, when the voltage on the anode is positive to that of the cathode, a current will flow. Now, as and when the voltage becomes high enough the condenser will become charged. On the next half cycle however, that is, when the anode is negative to that of the cathode, no current will flow, but the

termed a choke input filter, and such are used with mercury vapour rectifiers in transmitting practice. It is not, therefore, intended to mention these further, as they have already been dealt with in this journal by O. J. Russell under the title of "Transmitting Topics."

Mathematics

The reader will appreciate that the mathematics entailed in the design of suitable power supplies

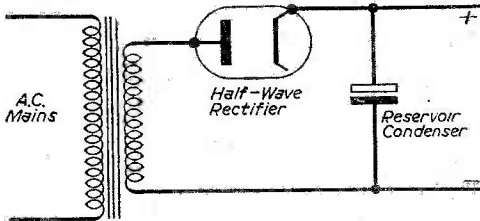


Fig. 1.—Basic half-wave rectifier.

condenser discharges, thus maintaining the output voltage until the next half cycle when the cycle is repeated. So much for half-wave rectification. Now let us analyse Figs. 2 and 2A, which are typical full-wave rectifier power supplies.

In this case, when the voltage on one anode is positive, the voltage on the other is negative, consequently, current flows in the same direction for each half of the valve. The condenser in this case discharges its stored energy in half the time as in the case of half-wave rectification.

Full-wave rectification is, therefore, most commonly used in radio receiver practice, and one will also appreciate that there is much less ripple and therefore the D.C. output is easier to filter or smooth. Before proceeding, however, it is as well to mention, for the benefit of newcomers to radio, that another type of filter exists other than that being discussed. This is

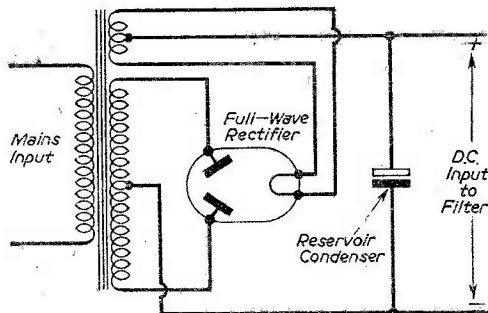


Fig. 2.—Basic full-wave rectifier.

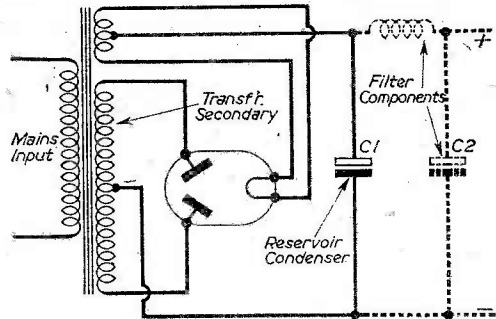


Fig. 3.—The filter components.

using the condenser input filter are very complex, and they are outside the scope of this article, but for the benefit of the newcomer or the radio constructor who requires a quick reference, Table 1 has been compiled. This table should be used in conjunction with Fig. 3. These values assume low transformer resistances and reactances, as the valves are of high impedances. One must bear in mind, of course, that the value of C1 must not be increased beyond that

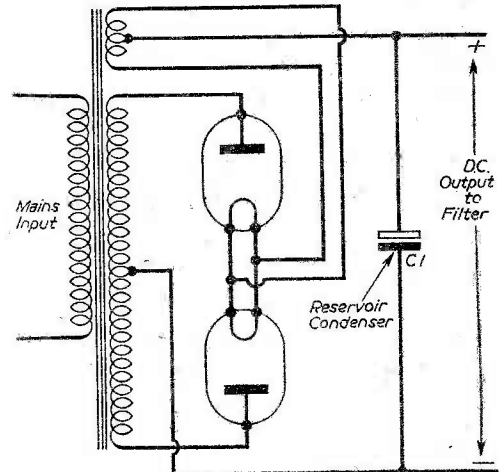


Fig. 2A.—Basic full-wave rectifier using two valves.

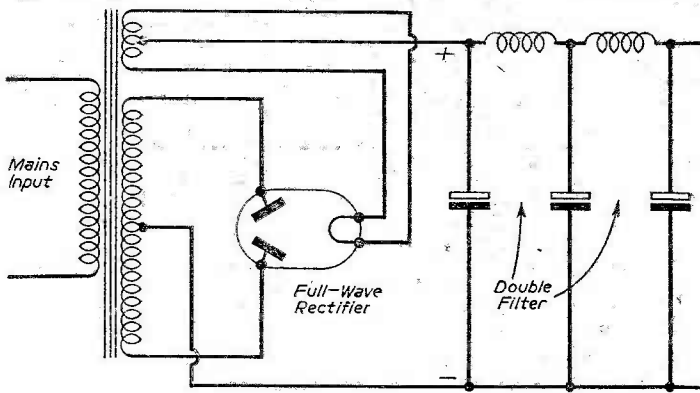


Fig. 4.—A double filter circuit.

filter. Reference once again to Fig. 3 will aid the reader to appreciate the following résumé.

The choke should be rated to withstand the current taken by the load. Here again, a higher current rated choke is better, so one has a safety factor. The purpose of the choke is to reject any A.C. component that may have superimposed itself upon the direct current. This will be appreciated when one realises that a choke has an impedance to A.C. The A.C. component is, however, commonly known as the ripple voltage and it is therefore essential that this be reduced to an absolute minimum. To
(Concluded on page 786)

stated, otherwise pulses of charging current with peak values will be produced and will be in excess of those specified for the rectifier in question. Failure to observe this will overload the rectifying valve and cause its destruction. One must bear in mind that the rectifier should never be operated above its maximum rated anode voltage, and should be operated within its maximum current rating specified by the manufacturer.

Components

The components necessary for such supplies should be of good quality, for instance the mains transformer should be such that it is rated correctly as well as having good insulation. Condenser C1, as shown in Fig. 3, is termed the reservoir condenser, this being of the electrolytic type. Such condensers are, however, readily available and require little comment, with the exception that they combine both high capacity with fairly small physical size, not forgetting fairly high working voltages.


The working voltages of these condensers are an important characteristic, and it is advisable to adopt one with a higher working voltage than the actual voltage it will have to withstand, that is to say, allow a greater safety margin. For instance, assume the working voltage the condenser will have to withstand is 350 volts, it is far better to have one with a working voltage of 500 volts than one just rated to withstand 350 volts.

The Filter

It only remains to give a brief description of the smoothing

TABLE I

Type	Transformer Sec.	Max. Load D.C. mA	C1 μ F	Approx. D.C. output volts
5V4G	350-0-350	175	8	390
83V	350-0-350	175	8	390
GZ32	350-0-350	175	8	390
5V4G	350-0-350	175	4	370
83V	350-0-350	175	4	370
GZ32	350-0-350	175	4	370
5V4G	300-0-300	120	8	350
83V	300-0-300	120	8	350
GZ32	300-0-300	120	8	350
5V4G	300-0-300	120	4	340
83V	300-0-300	120	4	340
GZ32	300-0-300	120	4	340
5U4G	300-0-300	150	4	300
U52	300-0-300	150	4	300
GZ31	300-0-300	150	4	300
53KU	300-0-300	150	4	300
5W4	350-0-350	100	4	370
5Y3	350-0-350	125	4	350
5Z4	350-0-350	100	4	400
R52	350-0-350	100	4	400
U50	350-0-350	100	4	400
GZ30	350-0-350	100	4	400
6X5	350-0-350	60	4	400
EZ3	350-0-350	60	4	400
U70	350-0-350	60	4	400
UU9	300-0-300	60	8	360
EZ40	300-0-300	60	8	360
66KU	300-0-300	60	8	360
UU9	350-0-350	60	8	425
EZ40	350-0-350	60	8	425
66KU	350-0-350	60	8	425
UU5	500-0-500	120	8	580
1W4/500	500-0-500	120	8	580
APV4	500-0-500	120	8	580
R4A	500-0-500	120	8	580
UU6	350-0-350	60	8	425
UU6	300-0-300	120	8	310
UU6	350-0-350	120	8	385
UU8	300-0-300	250	16	320
UU8	250-0-250	250	16	250
5Y4	300-0-300	125	4	290
80	250-0-250	125	4	220
5W4	300-0-300	100	4	300

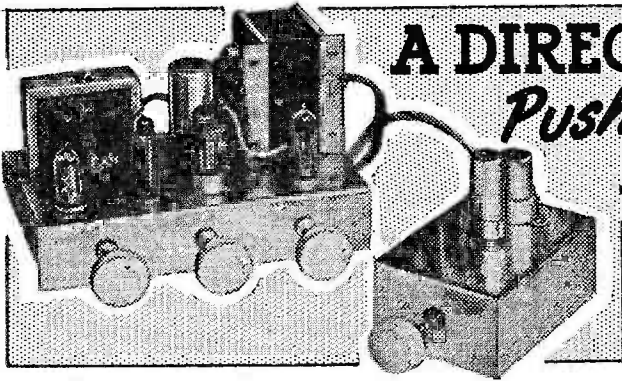

A DIRECT-COUPLED *Push-Pull* AMPLIFIER

A USEFUL AMPLIFIER, WITH TONE CONTROL AND PRE-AMPLIFIER

By J. S. Kendall

THERE are many design problems with this type of circuit. One is the matter of the "balanced conditions" of the output valves, as every valve takes a certain small grid current. This develops a positive voltage when passed through a high resistance such as a grid resistor. The normal circuit has two grid resistors of equal value, but this type has a low resistance in one grid circuit and in earlier circuits a strap was made between the two grids with the aid of a resistor of about $.5M\Omega$. This gave a difference of grid voltage of a volt or so; thus one valve was always running with a higher anode current than the other. This gave rise to distortion due to the unequal anode currents in the output transformer. The circuit to be described has a very simple means of setting a perfect balance of anode currents, and thus compensation can be made for valve unbalance or wear.

The Circuit

The theoretical circuit is shown in Fig. 1. The anode load of the first valve is rather high— $1M\Omega$ in fact and the screen is fed from the cathode of the output valves, thus the circuit is to a very large amount self compensating for wear in the EF86 and also for changes in H.T. and mains voltages. The static balance control circuit is shown in Fig. 6, and consists of R8, VR1, R9 and R10. The circuit is a simple tapped potentiometer, variable over a small part of the range only, thus the correct bias voltage for the second EL84 can be found correctly.

Tone Control

The layout of the tone control components is shown in Fig. 2. The choice of components for the circuit is not over-critical, but silver ceramics were chosen for the prototype, as they are very reliable

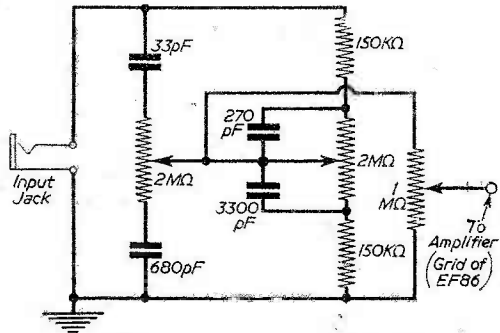


Fig. 3.—The tone control circuit.

and the price is lower than the silver mica types; type "T" 20 per cent. resistors can also be used with good results. One point that was found was that the tag strip can well be soldered direct to the case of one of the tone control potentiometers. The cases of all controls must be earthed, or a large amount of interference can be picked up, enough to cause instability in spite of the heavy feedback.

The theoretical circuit is shown in Fig. 3 for those who require a circuit to check against. Various pick-ups require various compensation filters and these will be set out next month.

H.T. Supply

The chassis can be obtained ready punched from Kendall & Mousley Ltd. It is drilled for a choice of two mains transformers, one for use with a feeder and the other without. The spare current when the heavy current transformer is used is a matter of 40 mA which is


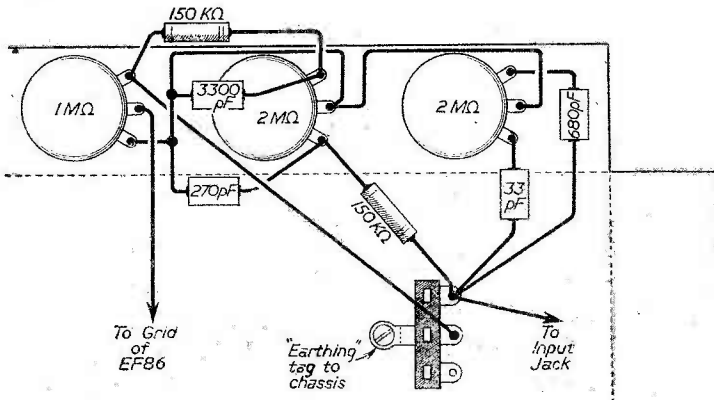


Fig. 2.—Wiring details of the tone control section.

ample for most feeders including F.M. The smoothing is of the resistance capacity type and consists of 40 μ F reservoir, and a further two 50 μ F for the other sections. The anodes of the output valves

valves are joined in parallel and the heater winding centre tap is joined to the cathodes of the two EL84s; this ensures that the heater of the EF86 is positive to the cathode, thus keeping the hum level of the valves to a minimum. A separate earth *must not* be used on the heater centre tap of the cathode coupling resistor or the two valves will be shorted out, thus causing the valves to be very seriously overloaded.

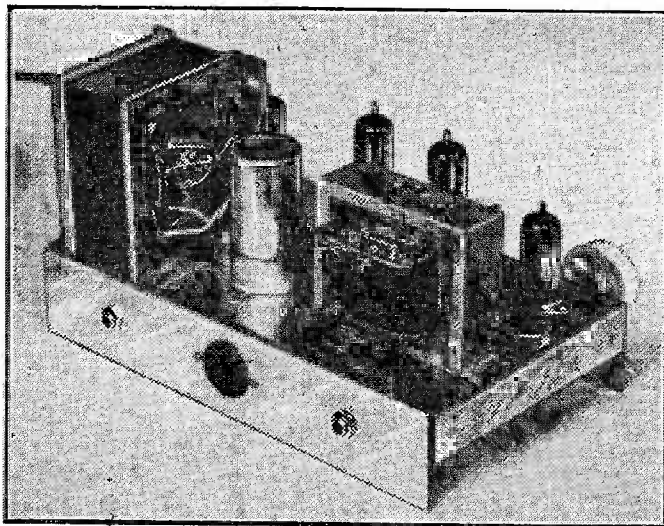

Three-quarter rear view of the amplifier.

are fed from the first section of the 50 μ F and the EF86 is fed from the other 50 μ F.

A separate resistance capacity filter is used for the supply to the feeder or pre-amplifier unit. The circuit is of the distributed load type of push-pull amplifier, thus there are four wires from the valves to the output transformer and one lead from transformer to H.T. The under chassis layout is shown in Fig. 6. The heater wiring of the EF86 and the two EL84s is not shown in full, but the heaters of these

The Layout

The top chassis layout is shown in Fig. 4. The tags on the output transformer are in two layers as it were, the two marked CT are strapped and on each layer are T1 and A1, and on the other T2 and A2. It is not over-important which pair is joined to which valve, but the Rs are taken to the Ts and the Gs are taken to the As. However, the leads from either valve must be joined to the same set of tags, i.e., V1 to T1 and A1, and V2 to T2 and A2 or vice versa. The tags on the secondary are either joined in parallel for 3.75 ohms or in series for 15 ohms. The side of the mains transformer is shown in Fig. 5

LIST OF COMPONENTS FOR THE 10-WATT DIRECT-COUPLED AMPLIFIER

- 2 EL84 valves, Mullard.
- 1 EF86, Mullard.
- 1 EZ81, Mullard.
- R1—250 Ω 10W Lab.
- R2—2.7K Ω 10W Lab.
- R3—1.5K Ω 10W Lab.
- R4—33 ohms, type "T" Lab. 10 per cent.
- R5—3.9K Ω type "T" Lab. 10 per cent.
- R6—470K Ω type "T" Lab. 10 per cent.
- R7—1 m Ω type "T" Lab. 10 per cent.
- R8—47K Ω High Stability 1W 2 per cent.
- R9—10K Ω type "T" Lab. 10 per cent.
- R10—10K Ω High Stability 1W 2 per cent.
- R11—See text for value.
- R12—750 ohm, 10W Lab.
- VR1—25K Pre-set wire wound Lab.
- C1—Hunts type JF408T 40 μ F 350 volt.
- C2-C3—Hunts type KN418A 505 + 50 μ F 350 volt.
- C4—Hunts type JD37T 50 μ F 50 volt.
- C5—Hunts type A300 0.1 μ F 150 volt.
- C6—Hunts type JF403T 8 μ F 350 volt.
- 2 Three-way tag strips (Kendall & Mousley Ltd.)
- 3 McMurdo B9A valve holders.

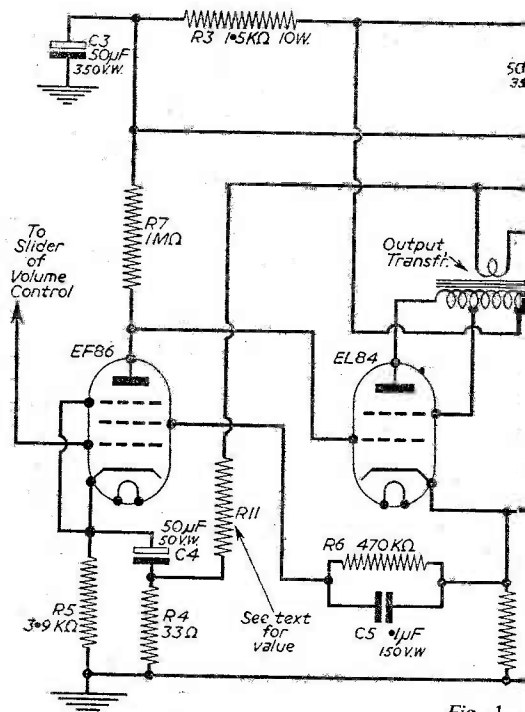


Fig. 1.—

to simplify the wiring of the amplifier. Having constructed the amplifier the first thing is to plug in the speaker and switch on. If a howl results the N.F.B. is incorrectly wired and the leads to the output transformer secondary will have to be reversed. The balance of the currents to the two valves can best be carried out with the aid of a milliammeter; this is joined between the two anodes and the resistor VR1 adjusted until the reading is zero. Here it is better to start on a high range and then switch to a lower range as one gets nearer to a perfect balance.


The negative feedback resistor (R11) will be 390 ohms for a 3.75 ohm output and 680 ohms for a 15 ohm output.

A Pre-amplifier Unit


Whilst the amplifier just described has a first-class tone control, it does not incorporate "frequency correction." This latter is required as the bass of the standard records is cut below certain frequencies, these frequencies differing with 78, 45 and 33½ recordings. Radio on the other hand is usually not cut so much, and the required

amount of correction can be obtained from the tone control of the amplifiers.

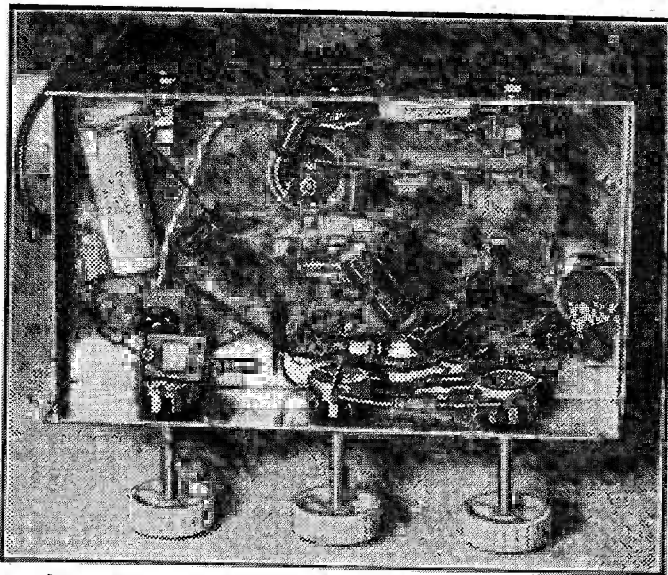The method of obtaining the correction is by providing the amplifier with a large amount of negative



A view of the underside of chassis.

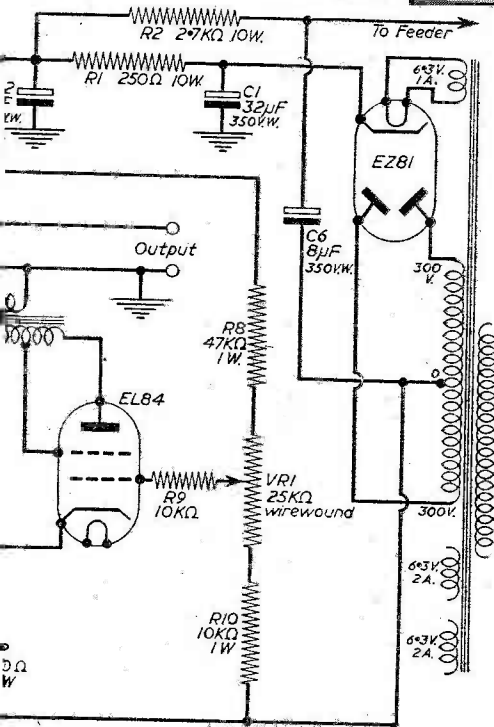

The theoretical circuit.

feedback and making that feedback frequency selective. That is, at the higher frequencies the gain is quite low, but at the lower frequencies the increased impedance of the capacitors reduces the N.F.B. and allows the gain to rise.

The pre-amplifier unit described here is only 4in. x 6in. x 2½in., with the valve and the capacitor projecting through the top. The valve chosen is the

- 1 McMurdo B9A valve holder with skirt and screen.
- 1 McMurdo International Octal valve holder.
- 1 McMurdo International Octal Plug (optional).
- 3 Bulgin K108 pointer knobs or similar.
- 2 Bulgin J6 closed circuit jacks.
- 2 Bulgin P.38 jack plugs.
- 1 Elstone O1/ML output transformer.
- 1 Elstone MT/MU Mains transformer, but if no feeder unit is required the Elstone MT/5/10 can be used.
- 1 Special chassis—Kendall & Mousley Ltd.
- 1 type "9-12" Instrument Case—Kendall & Mousley Ltd.

LIST OF PARTS FOR TONE CONTROL

- 1 1M Pot. "Lab."
- 2 2M Pots. "Lab."
- 1 33pF Ceramicap "Lab."
- 1 680 pF Ceramicap "Lab."
- 1 270 pF Ceramicap "Lab."
- 1 3,500 pF Ceramicap "Lab."
- 2 150K 20 per cent. type "T" "Lab."
- 1 triple tag strip.

The tone control unit is suitable, owing to its high impedance, for feeding direct from the pre-amplifier circuit.

Mullard EBC41. The gain is certainly not very high, but quite high enough for the crystal types of pick-up head as well as a radio feeder taken direct from the diode.

The Chassis

The chassis can be obtained in aluminium fully

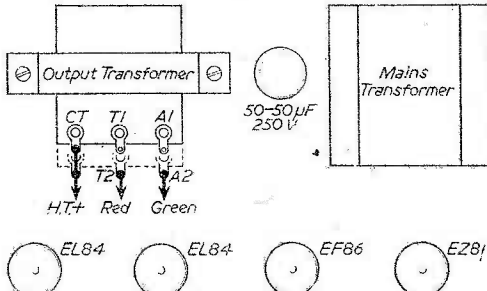


Fig. 4.—Plan of the chassis layout.

punched for assembly. It will be seen that the valve-holder has a raised "blob" of insulating material between two of the pins. The holder should be fixed in place so that the "blob" is as shown. The two orange wires are taken so that one is soldered either side of the "blob" to the pins. The switch can be wired away from the pre-amplifier chassis and dropped in place and soldered to the tags. The jacks can be put in place and the 220 K resistors soldered across them, then the wires from them to the switch wired in and soldered. These latter wires can best be run around the sides of the chassis. The components

on the two solder tags can then be wired and soldered in place. Care must be taken in the soldering of the screening of the screened cable. Strip the insulation off the outside of the cable, then by pushing the screening wires to one side, make a hole in the screening, then draw the two wires through the hole. The spare screening can then be soldered to the tag and the ends of the flexible wires wired to the end tag of the solder strip. The anode lead from the .05 μF capacitor can be wired to the valve tag, also from the same tag a 100 K resistor is joined to the 16 μF

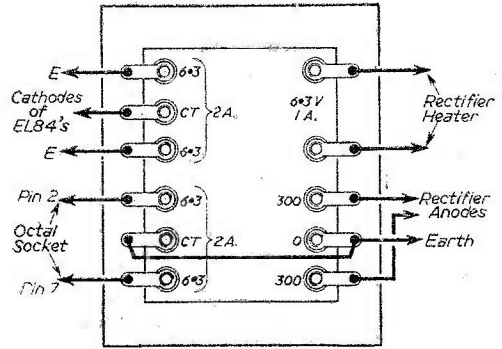


Fig. 5.—Mains transformer connections.

capacitor, another 100 K is joined between the 16 μF and the tag strip along with the red lead.

The cathode connections of the valve can then be wired in, and consist simply of a 2.2 K resistor in parallel with a 50 μF 12 volt electrolytic capacitor.

The orange twin, the red lead and the screened lead can be led out through the hole at the rear of the chassis and laced together to form a cable. For those not experienced in the art of lacing cables, the simplest method of securing at 2in. intervals, with Sellotape can be used. The effect is quite neat.

The fixing of the plug is the last item and the actual connections will be shown next month.

(To be continued)

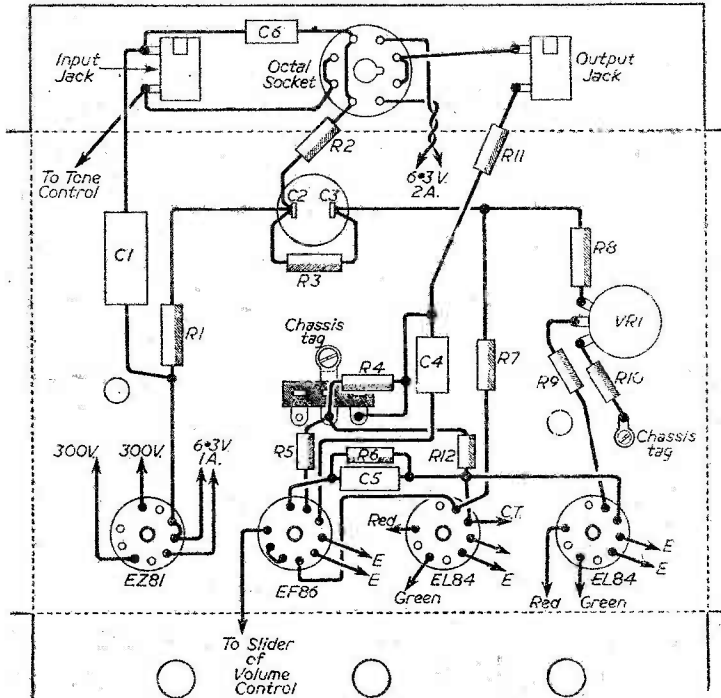


Fig. 6.—Wiring diagram of the amplifier.

A HANDBOOK FOR HANDYMEN

THE HOME ELECTRICIAN

By F. J. CAMM

(Editor: Practical Householder)

206 pages, 149 illustrations.
 12/6, or 13/- by post from
 George Newnes, Ltd.,
 Tower House, Southampton St., Strand, W.C.2.

RADIO COMPONENTS—RETURN-OF-POST SERVICE

Details of some of the items from our extensive stock of Radio and Television components and accessories are given below. All items are usually held in stock and all orders are dealt with on the day they are received.

MULLARD TAPE AMPLIFIERS

We stock all the components for the Amplifiers as described in the Mullard Tape Recording Booklet.

RESISTOR KITS.—LAB. All fixed and variable resistors as specified. Model A, 33/3. Model B, 31/3.

CONDENSER KITS.—Model A, 33/-; Model B, 35/-. These kits are made up for the Brenell and Collaro decks. If the Lane or Truvox coils are required, this must be stated when ordering.

OUTPUT TRANSFORMERS.—For Model A: Elstone OT3, 21/-; Gilson W0767, 25/6; Partridge SVO1, 60/-.

ELCUM PLUGS AND SOCKETS.—PO4 Chassis Plug, 3/6. SO4T Chassis Socket, 5/3.

IGRANIC JACK SOCKETS.—PT1, 3/4; PT2, 3/10. Bulgin Jack Plugs to fit, 3/-.

BELLING LEE PLUGS AND SOCKETS.—Speaker Sockets: L316, Red and Black, 1/- each. Plugs to fit, 101, each. Co-Ax. Socket L734S, 1/3. Co-Ax. Plug L734P to fit, 1/3.

McMURDO VALVEHOLDERS.—BM9/U, 10d.; XM9/U, 1/7; XM9/U, 1/3.

SWITCHES.—Specialist Switches. Set of three for the Model A Amplifier, 32/6. One switch for Model B, 16/6.

BULGIN TAG BOARDS.—C120, 1/3; C121, 2/3.

EQUALIZER LEAD AND SOCKET.—For Model B. Octal Plug and socket, 2/3.

CERAMIC STAND-OFF PILLAR.—Polar, 1/-.

OSCILLATOR COILS.—Brenell, 8/-.

CHASSIS.—Denco. Ready drilled. Model A, 51/6; Model B, 31/6.

VALVES.—EP7C Mullard, 24/4. Alternative 15/-, ECC83 Mullard, 19/6. Alternative 10/-, 8M1 Mullard, 18/1. Mullard EL94, 16/-.

Alternative 12/-, OAT1 Crystal Diode, 6/-.

POWER PACK.—Chassis Denco, 11/6. Condenser, 50-50 mfd. 350 v. 9/8. Resistor 820 ohm, 3 watt, 2/3. Valveholder BM9/U, 10d. Valve Mullard E290 or 61, 11/10. Mains Transformer, Elstone MT3M, 35/-.

Switch, DP Toggle, 5/-; Voltage Selector Panel, 2/-; Fuseholder, 3/9. Fuses 4d. each. Pilot Lampholder, 2/-; 6.3v. Lamp, 9d.

Kits or part kits for the above can be supplied on Credit Terms. Send for our fully detailed lists.

MULLARD 510 AMPLIFIER

Full details of all components for this Amplifier were given in our advertisement in the December issue. Fully detailed price list will be sent upon request.

OSRAM "FM PLUS" TUNER PRINTED CIRCUIT VERSION

TCC PRINTED CIRCUIT AND CONDENSER KIT.—Contains the Printed Circuit Panel and all the condensers. £4.4.7.

RESISTOR KIT.—LAB. Kit for Tuner containing R1 to R28, 15/-.

COILS.—Denco. Oscillator Coil, O/L2, 2/-; I.F. Transformers, IPT11/10.7, three required, 6/- each. Ratio Detector Transformer (complete with crystal diodes) O/T2, 19/-; Note: The O/T1 and the O/L1 coils are not required with the printed circuit.

CHASSIS.—Denco. Complete metalwork including Gold Front Panel, Scale Assembly, Drum, Drive Spindle, Pointer, Glass Dial and all fittings, 37/6.

TUNING CONDENSER.—Jackson 17pf. 5096-17-DS, 17/6.

VALVEHOLDERS.—McMurdo Printed Circuit Type, 1/- each. Skirt and can for V2, 1/3.

BELLING LEE PLUGS AND SOCKETS.—Co-ax. Sockets, L804S, two required, 1/3 each. Plugs L734P to fit, 1/3 each.

VALVES.—Osram Z719, 24/4. Alternative 10/- each. Two required. Osram B719, 20/10. Osram W719, 19/6. Alternatives 12/3. Two required.

NOISE SUPPRESSION AND TUNING INDICATOR CIRCUITS.—Osram B309 valve, 19/6. Alternative 10/-, Osram EM80 valve, 18/1. Osram L77 valve, 13/11. Alternative B3. Resistor Kit containing R29 to R40, 13/-; Condensers, .02 mfd. 350 v., 1/- each. .1 mfd. 350 v., 9d. .05 mfd. 150 v., 1/8. Valveholder B9A, 10d. each. B7G, 9d.

INSTRUCTION MANUAL.—The manual for the normal wired version is required, 2/6. PRICE LIST FREE. Kits or part kits for the above can be supplied on Credit Terms.

OSRAM 912 PLUS AMPLIFIER

Full details of all components were given in our advertisement in the December issue. Fully detailed Price List available upon request.

GRAMOPHONE EQUIPMENT

BSR U8 MONARCH RECORD CHANGER.—The latest 4-speed model. Acos turn-over cartridge. Price £9.15.0. Credit Terms Deposit £1.13.0 and seven monthly payments of £1.6.0.

COLLARO STUDIO PICK-UP.—This famous pick-up is now available with one piece arm as well as plug-in head. Can be supplied with the "O" (high output) or "P" (low output) Cartridge. Price £2.19.6.

BSR T8 MOTOR AND PICK-UP.—Three speed motor and separate pick-up. The pick-up is fitted with the Acos turn-over crystal cartridge. £4.17.6.

COLLARO TRANSCRIPTION MOTOR.—Complete with the Transcription pick-up and insert, £19.10.0. Can be supplied less pick-up at £14.18.0.

TV PATTERN REMOVAL UNIT

Spencer West Type 54. These units will give considerable assistance in removing patternings on the ITA picture. Complete with instruction leaflet, 25/-.

Osram Band 1 Filter. For removing BBC signal when it is entering the converter via the ITA aerial, 10/-.

TRANSISTORS

MULLARD.—OC70, 21/-; OC71, 24/-; OC72, 36/-. Matched Pairs, 60/-; STC, T11 (8X309N), 40/-; T12 (8X309N), 45/-; T13 (8X302N), 50/-; T51, 18/-; T52, 21/-; T53, 24/-; TP1, 40/-; TP2, 40/-.

CRYSTAL SET COMPONENTS

COILS.—Teletron Co-Ax 3/6. Specially made for use with Crystal Diodes. Suitable diodes 2/6.

TUNING CONDENSER.—0005 mfd., 3/10.

CHASSIS.—Small metal chassis with tuning scale and sockets for aerial, earth and phones, 2/3.

TUNING KNOB.—1/-.

CONDENSERS AND RESISTORS

We carry a wide range of these and fully detailed lists are available free of charge.

VIEW MASTER CONVERTER

INSTRUCTION MANUALS are now available. The Manual is a reprint of the articles in "Practical Television." Price 2/6. postage 3d.

TELEVISION ATTENUATORS

Belling Lee Co-Axial plug-in Type. Available in 6db, 12db, 18db, 24db and 35 db. 4/6 each.

CO-AXIAL CABLE

The very best quality semi-airspaced. Entirely suitable for Band III and F.M. 10d. per yard; 82/6 per 100 yard drum.

CREDIT TERMS.—Anything we sell can be supplied on Credit Terms. The deposit is 3/- in the £ and the balance payable over 7 months. Send details of your exact requirements and we will submit a quotation.

TERMS OF BUSINESS.—Cash with order or C.O.D. Please add postage under £3. We charge C.O.D. fees on C.O.D. orders under £5.

WHITELEY CABINETS

All these Cabinets are packed flat for easy home assembly. The new Junior Bass Reflex Corner Console, £9.9.0. Bass Reflex Console, £10.10.0. Senior Bass Reflex Corner Console, £11.11.0. All the other Whiteley types are available. Illustrated leaflet available free. Credit terms on these cabinets with a speaker if required.

WHITELEY SPEAKERS

The Whiteley Hi-Fi range of speakers. 10in. HF1012, 93/3. 9in. HF912, 88/6. 6in. HF812, £4.3.6. 8in. T816, the new Treble speaker, £5.10.0. Whiteley Cross Over Unit CX1500 for the T816, 38/6. 8in. HF816, £6.17.0. T10 Tweeter, 84/-; Cross-over Unit CX300 for this tweeter, 30/-. Detailed leaflet on all W.B. Speakers available.

TEST INSTRUMENTS

AVO Meter Model 8, £23.10.0. **AVO Meter** Model 7, £19.10.0. **RADAR** Kilovoltmeter for E.H.T. Measurements, 3 to 30 kv., £3.17.6.

TSL TWEETER SPEAKERS

The new Moving Coil LSH35, 59/6. Cross-over chokes, .84 mH, .9 mH, .6 mH, 1.75 mH, all 3/6 each. Electrostatic, LSH75, 12/6. LSH318, 17/3. LSH100, 21/-; 65 mH cross-over chokes, 7/6 each.

PAPER BLOCK CONDENSERS

Very high grade 2 mfd. 250 v. Paper Block Condensers. Ideal for making up the capacity required for cross-over networks. 2/- each. Brand new. Not ex-Government.

**8, APPLE MARKET
KINGSTON-ON-THAMES, SURREY**

Telephone: KINGSTON 4099

Shop Hours: Monday, Tuesday, Thursday—9 a.m. to 5.30 p.m. Wednesday—9 a.m. to 4 p.m. Friday, Saturday—9 a.m. to 6 p.m.

WATTS RADIO

Still only 5 connections
Smaller in size
many 'plus' features

The New
AMAZINGLY ROBUST

Q'pack
FROM 42/-

FREE

CIRCUITS & WIRING DIAGRAMS

JIFFY PUNCH

FERRITE ROD AERIALS

For cutting smaller holes neatly with one blow of a light hammer

HOLE	RETAIL
1/4 in.	6/6
3/8 in.	7/6
1/2 in.	8/9

HIGH "Q" M.W., 8/9
M. & L.W., 12/9

BAND I FILTER
Rejects B.B.C. from I.T.A. aerial. Suitable for all makes.

10/- inc. instructions

Fitted in 2 minutes

Entirely New Design

POTTED COILS
HIGH "Q"

Simple press home fixing 5/-

CHASSIS CUTTER

HOLE SIZES	RETAIL
1 in. x 1 1/2 in.	19/6
1 in. x 1 1/4 in.	18/9
1 in. x 1 1/2 in.	22/6
1 1/2 in. x 2 in.	27/3

BAND III Converter

Kit £3.5.0
Ready wired £4
Postage and packing 3/-

OSMOR NEW ASSEMBLY DIAL

Calibrated for Osmor Coils and Coil-packs 24/6

Bronze Finish Escutcheon 4/-

Price 10/6

STATION SEPARATOR

Send 7d. in stamps for circuits, wiring diagrams, coil-pack leaflets, component lists, chassis drawings, templates, and switch tuned frequency controlled FM Tuner, price lists.

OSMOR RADIO PRODUCTS LTD. P.W.6 418 Brighton Road, South Croydon, Telephone Croydon 5148/9.

THE F.A.M.O.U.S. BENNETT COLLEGE

can train your mind to SUCCESS

THROUGH PERSONAL POSTAL TUITION
A FREE book vital to your career!

Read how the famous Bennett College can help you to success! Send now for this recently published FREE book, "Train your mind to SUCCESS," which tells you about The Bennett College proven success in postal tuition... and how it can help you to success in your career.

WHAT CAREER DO YOU WANT?

Architecture
Building
Carpentry
Chemistry
Commercial Art
Diesel Engines
Draughtsmanship
Electrical
Engineering
Electric Wiring

Forestry
Locomotive
Engineering
Machine Design
Mechanical
Engineering
Motor Engineering
Plumbing
Power Station Eng.
Quantity Surveying

Radio Engineering
Sanitary Science
Surveying
Telecommunications
Television

Accountancy Exams
Book-keeping
Civil Service
Commercial Arith.
English
General Education
Geography
Journalism
Languages
GENERAL CERTIFICATE OF EDUCATION

Mathematics
Modern Business
Methods
Police Subjects
Salesmanship
Secretarial Exam
Shorthand
Short Story Writing
and many others

FREE

Train your mind to SUCCESS

TO THE BENNETT COLLEGE (DEPT. A.104-N), SHEFFIELD

Please send me, without obligation, a free copy of "Train your mind to SUCCESS" and the College Prospectus on:

SUBJECT.....

NAME.....

ADDRESS.....


AGE (if under 21)..... Please write in black letters.

THIS COUPON
COULD BE YOUR
PERSONAL PASSPORT
TO SUCCESS.
Send it NOW!

A Superhet PORTABLE 4

A SIMPLE-TO-MAKE BATTERY RECEIVER

By F. G. Rayer

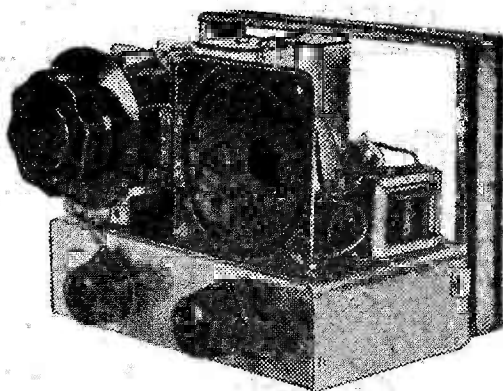

IN addition to its sensitivity the main advantage of the superhet type of receiver lies in the fact that no reaction control is required. With portables, where the signal pick-up is small, the reaction control in a non-superhet receiver can be quite critical, but this is wholly avoided in the superhet, where a L.F. volume control can be employed. The receiver described here is accordingly easy to operate by anyone, while ganged tuning does away with difficulties in that direction. If the specified oscillator coils are used, and the frame wound as described, correct alignment throughout the wavebands will be obtained. The oscillator coils have adjustable dust-iron cores, thus enabling the inductance to be adjusted to the required value, and this type of coil is essential in the present case.

It is also recommended that the other specified components be used to avoid difficulty. A W.B. midget speaker is used, this gives excellent results, and as a small output transformer specially for use with this model is available from the same manufacturer no possibilities of mis-matching (and consequent loss of volume) need arise. The specified I.F. transformers, besides providing high gain, have adjusting screws at the top. If transformers with side

adjusting screws were used, it would be very difficult to get at these for aligning purposes. It is, therefore, recommended that the speaker, with transformer and coils and I.F. transformers all be obtained from the suppliers listed. If alternatives are used it is necessary to assure that they can be accommodated in the small space available and have suitable characteristics.

Fig. 1 shows the circuit. Long and medium wave coils are quite separate and selected by a three-way switch. One position of the switch provides the "Off" setting, additional contacts taking care of battery and frame aerial connections. A measure of A.V.C. is applied to the I.F. valve, and the diode detector is followed by two stages of L.F. amplification.

Winding the Frame

This was made with 1/2 in. wood for sides, and 3/16th wood for top and bottom. However, the thickness of the material does not matter, provided the pieces are cut so that the outside dimensions are 5 1/2 in. high by


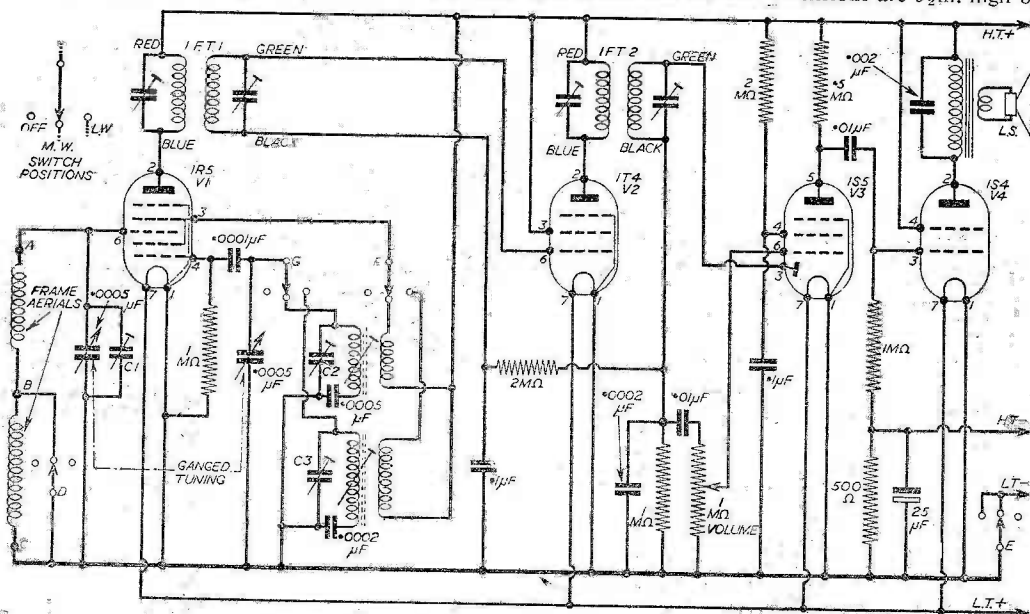


Fig. 1.—Theoretical circuit of the Superhet Portable 4.

7in. wide. Three 6 B.A. bolts are screwed tightly in position for points "A," "B" and "C." The 18-turn section has turns side by side; the 45 turns of the larger section are wound in a pile occupying about $\frac{1}{2}$ in. width. The ends of the windings are soldered to the bolt heads, and point "B" consists of the junction between both windings. The wire should be wound on tightly. Afterwards the corners may be varnished to hold the turns in place. The whole of the frame windings should *not* be varnished in this way, however.

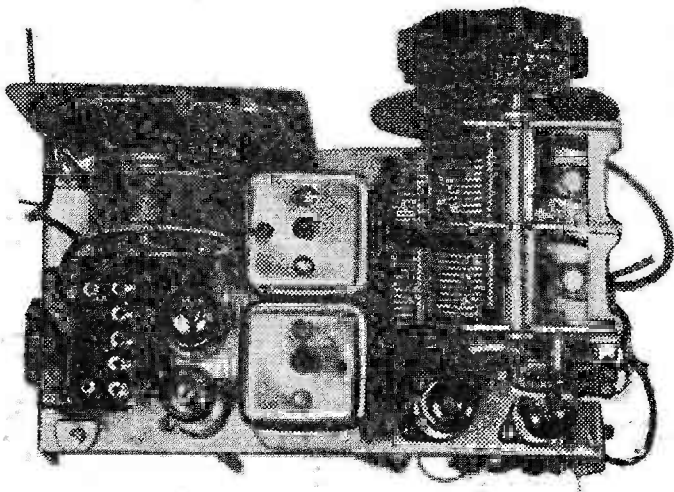The completed frame is mounted on the rear of the



Plan view of the completed set without the frame aerial.

chassis, by two small brackets, when the receiver has been wired up.

Two short lengths of flex run to terminals "A" and "B," from the fixed plates of the tuning condenser (rear section), and wavechange switch, respectively. Lead "C" is taken to one bracket, thus being returned to the chassis.

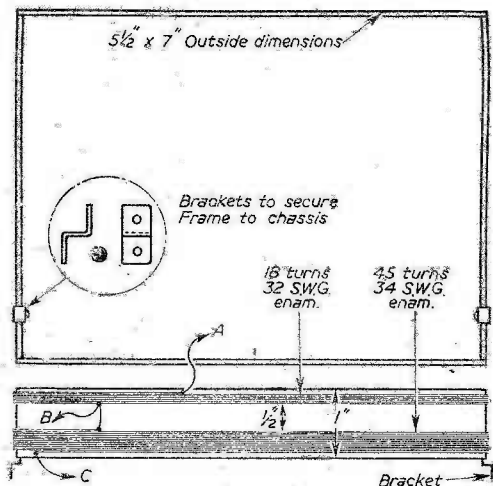


Fig. 2.—Details of the frame aerial.

Chassis Layout and Wiring

The chassis, shown in Fig. 3, is 1 1/2in. deep, and was bent up to the dimensions given from 20 s.w.g. aluminium. All the drilling should be done before any components are mounted. The tuning condenser is secured by two small brackets, the rear one coming under C1. The speaker is similarly mounted. Holes are drilled under the positions to be occupied by the I.F. transformers, so that leads may pass through. (These will be seen in Fig. 4.)

Only four leads pass through the chassis, except for those already mentioned. These are those from output valve to output transformer, and from each fixed plates section of the gang condenser.

When the valveholders are screwed down position the sockets as in Fig. 4, so that wiring may be followed with no difficulty. All the connections shown in Fig. 4 may then be put on, and a reasonable amount of space exists for the smaller parts. The two .01 μ F coupling condensers should preferably be of the mica type, while $\frac{1}{2}$ watt resistors can be accommodated with more ease than the larger 1 watt type.

The lead issuing from the top of one I.F. transformer is not used because the B7G valve types do not have a top cap in any instance.

Coil and Switch Wiring

The switch is mounted on the front runner, with the coils on the side runner, as seen from Fig. 4. Wiring for these parts is shown in Fig. 5, which is a plan view of the side runner and switch. The coils are notched, to identify the tags, and mounted by drilling $\frac{1}{8}$ in. diameter holes and pressing on the clips provided. The slotted ends of the core adjusting screws project outside the chassis.

The two trimmers C2 and C3 are bolted to the chassis, as illustrated, and can be adjusted from behind the receiver. The .0002 μ F and .0005 μ F condensers in Fig. 5 are fixed padders, returned to the chassis. As in Fig. 4, points marked "M.C." are taken to a tag bolted to the chassis itself.

As a guide, connections are as follows, for the three
(Continued on page 765)

LIST OF COMPONENTS

- W.B. Stentorian Type S.3.57 Speaker.
- W.B. Miniature Universal Output Transformer.
- Long Wave dust-iron core oscillator coil; ditto for Medium Waves (Supacoils).
- Pair I.F. transformers with top trimmers (Astral Radio Products, 82, Centurion Road, Brighton).
- 1R5, 1T4, 1S5 and 1S4 valves. 4 B7G holders.
- 2 gang .0005 μ F tuning condenser.
- 3-way 4-pole small-sized rotary switch.
- Three .00005 μ F postage-stamp trimmers. .0001 μ F, two .0002 μ F, .0005 μ F, .002 μ F, two .01 μ F, two .1 μ F and 25 μ F condensers. 500 ohm, .1 megohm, .5 megohm, three 1 megohm, and two 2 megohm resistors. 1 megohm volume control.
- Knobs, wire for frame aerial, and aluminium for chassis.

C.R.T. ISOLATION TRANSFORMER

Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary. 3 v., 10/6; 4 v., 10/6; 6 v., 10/6; 10.8 v., 10/6; 13.3 v., 10/6.
Type B. Mains input 220/240 volts. Multi Output 2, 4, 6.5, 7.3, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50%, respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tag Panel: 21/- each.
Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220/240 volts. Output 2-21-22-23 volts at 2 amps. With Tag Panel, 17/6 each.
NOTE.—It is essential to use mains primary types with T.V. receivers having series-connected heaters.

TRIMMERS, Ceramic. 50, 50, 70 pf., 8d. 100 pf., 50 pf., 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/9.
RESISTORS. All values. 10 ohms to 10 meg. 1/4 w., 4d.; 1/2 w., 6d.; 1 w., 8d.; 2 w., 1/-
HIGH STABILITY. 1/2 w., 1/5; 2/- Preferred values 10 ohms to 10 meg.
WIRE-WOUND RESISTORS 1/3 10 watt, 25 ohms—10,000 ohms 1/3 15 watt 1/2
15,000 ohms—50,000 ohms, 5 w., 1/9; 10 w., 2/3.
KNOBS, GOLD ENGRAVED.—Walnut or Ivory. 1/4 in. diam., 1/8 each. Not engraved, 1/- each.

12/6 PURETONE RECORDING TAPE

1,200 ft. on standard, fitting 7" Plastic reels. Brand new, boxed, 12/6. Spools 5" metal, 1/6; 7" plastic, 4/6.

OP TRANSFORMERS, Heavy Duty 50 mA., 4/3. Multiratio, push-pull 6/6. Tapped small pentode, 3/9. L.F. CHOKES 1.5/10 H. 60/65 mA., 5/-; 10 H. 120 mA., 10/8; 15 H. 150 mA., 12/6.

MAINS TRANS. 350-350, 80 mA., 6/3 v. tapped 6/3 v. 5 v. tapped 4 v. 2 v. 2.4 v. 2.8 v. 3.2 v. 3.6 v. HEATER TRANS. Tapped primary, 200/250 v., 6.3 v., 11 amp., 7/6; tapped sec. 2, 4, 6.3 v., 11 amp., 8/6; 230 v. to 6.3 v. 3 amp., 10/6.
VCR7 TESTED FULL PICTURE, 25/-.
COPPER PLATED AERIAL RODS. 3/4 x 12 in. push fitting, 3/-; 1/2 x 12 in., 2/-; 3/8 x 12 in., 1/6.

ALADDIN FORMERS and core, 1 in., 8d.; 1 in., 10d., 3 in. FORMERS 5937/8 and Cans TVL 2. 1 in. 8/- x 2 1/2 in. and 1 in. sq. x 1 1/2 in., 2/- each with cores.

TYKA.—Midget Soldering Iron, 200/240 v. or 250/250 v., 16/9. Solen Instrument Iron, 24/-. MIKE TRANS. Ratio 50:1, 3/9 ea., 100:1, 10/6. MAINS DROPPERS. 3 x 1 1/2 in. Adl. 3/1ers, 3 amp. 7/60 ohms, 4/3; 2 amp., 1,000 ohms, 4/3. LINE CORD. 3 amp., 60 ohms per foot, 2 amp., 100 ohms per foot, 3-way, 8d. per foot, 3-way, 7d. per foot.

LOUDSPEAKERS, 2 1/2" OHM. 5 in. Goodman's, 17/8; 7 in. x 4 in. Goodman's, 21/6; 3 1/2 in. square, Elac., 21/-. 4 in. Elac., 22/6. 6 in. Goodman's, 28/6. 10 in. R. & A., 20/-. 7 1/2" Tweeter, LS175, 8/6. 12 in. Plessey, 30/-. 15" L.F. 2.5, 6 or 2 k. bell, tapped O.P. Trans., 24/6. CRYSTAL DIODE, G.E.C., 2/- Crystal Box, 1/6. GEX34, 4/-.

HIGH RESISTANCE PHONES. 4,000 ohms, 17/6 pr.

CRYSTAL MIKE INSERT by Acos, precision engineered. Size only 1/8 x 3/16. Bargain Price 6/6. No transformer required.

SWITCH CLEANER Fluid, squirt spout, 4/3 tin. TWIN GANG TUNING CONDENSERS. 0.005 mfd. midget, less trimmers 9/6; 0.005 Standard size with trimmers 9/-; less trimmers, 8/-; ditto, soiled, 2/6; 0.005 mfd. 3-gang, 7/6. GOLD CLOTH. 1 1/2 in. x 2 1/2 in., 5/-; 3 1/2 in. x 3 1/2 in., 10/-.

VALVES

Table with columns: All Boxes, New & Guaranteed, Valves. Lists various valve types and prices.



1957 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES. 9 W. 16 m. — 30 m. LATEST MULLARD. M.W. 200 m. — 530 m. ECH42, EP41, EBC41, L.W. 500 m. — 2,000 m. 12 month guarantee. A.C. 200/250 v. 4-way Switch; Short-Medium-Long Converter. A.V.C. and Negative feedback 4.3 watts. Chassis 3 1/2 x 5 1/2 x 2 1/2 in. Glass Dial 10 x 4 1/2 in. horizontal or vertical available. 2 Pilot Lamps, Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains. T.S.L. Tweeter Supplied Free!

10 gns.

TERMS: Deposit £5.5.0 and six monthly payments of 31. MATCHED SPEAKERS FOR ABOVE CHASSIS 5 in., 19/6; 10 in., 25/-; 12 in., 30/-.

R.C.S. SCOOP

Collaro Auto-changer RC531 for 78 r.p.m. 10 in. and 12 in. records. Brand new in makers boxes! High impedance lightweight Pick-up with sapphire needle, will match any Amplifier or Radio. Less than half price. 5 gns. Carr. and Ins. 3/6. Sorry—No. C.O.D.



£7-19-6

Post Free.

Terms: Deposit £4 and six monthly payments of 15/-. Brand new Plessey 3-speed Autochanger Mixer. Xtal Head with Duopoint sapphire stylus. Board required 15/- x 12 in. Height 5 1/2 in. Walnut Veneered Playing Desk 10/6 extra.

EXCEPTIONAL OPPORTUNITY

COLLARO 4-speed Single Record Player, including heavy-weight turntable and lightweight Mtdio Turnover Xtal Pick-up mounted on baseplate. Auto-stop fitted.

GUR PRICE 6 gns. carriage 4/-. Player Cabinet, 49/6, post 2/6.

ALDRY UNIT POWER PACK

Replaces Battery B14, etc., 69 v. plus 1/2 v. Size 4 1/2 in. x 4 1/2 in. x 1 1/2 in. 4-pin Socket. Same as battery. ONLY 1/- a year to run on A.C. 200/250 v. FAMOT-4 MARK B. LIST PRICE, 55/-. OUR PRICE, 39/6. Ready for use.

B.S.E. MONARCH. 3-speed Motor and Turntable with selecting switch for 23, 45 and 78 r.p.m. records. 100-120 v. and 200-230 v. A.C. 50 cps. Also B.S.E. MONARCH Lightweight Pick-up with Acos Xtal turnover head, separate sapphire stylus for L.P. and Standard records. SPECIAL OFFER, THE TWO! £4.12.6 post 2/6.

T.V. PRE-AMP (McMICHAEL). Tunable Channels 1 to 5. (Will Amplify Output of your Band 3 Converter.) Midget size. High Gain Triodes, B.V.A. Valve. Full Instructions. Ready for use. (H.T. 300 v., L.T. 43 v., 3 amp., required.) BRAND NEW, 25/- each. MAINS POWER PACK for above, 25/- extra.

SUPERHEAT COIL PACK. 27/5. Miniature size 2 1/2 in. x 2 1/2 in. x 1 1/2 in. HIGH "Q" Dust cored Coils. Short, Medium, Long, Gram Switching. Single hole fixing. Complete with connection diagram and circuit.

TELETRON BAND III CONVERTER

For London, Midland and Northern Transmissions. Suitable all T.V. makes. T.R.F. or Superhet. Ready wound coils, two EF80 valves, all components, punched chassis, circuit diagram, wiring plans. COMPLETE KIT for mains operation 200-250 v. A.C. £3.10.0.

As ABOVE less POWER PACK. Requires 200 v. 20 mA. H.T. 0.3 v. 6 a. L.T., £2.5.0. Mains Transformers to above spec. 10/6 Min. Contact Rect. 250 v. 50 mA. 3/8 B.V.C./I.T.A. Aerial crossover unit 7/6 Punched and drilled chassis 3/6 L.V.C. chassis for Mains Model 3/6 Teletron Coilet with plans 15/- Full plans and circuit details 6d.

Volume Controls 80 ohm CABLE COAX

Long spindles. Guaranteed 1 year. Midget. 10,000 ohms, 2 to 2 Meg. Stranded core. 9d. yd. No. 50, S.F. Sm. B.D. 35w. 3/- 4/- 4/9 Lin or Log Tracks. 1 in. Coax. 8d. yd.

COAX PLUGS... 1/- DOUBLE SOCKET... 1/3 SOCKETS... 1/- OUTLET BOXES... 4/3 BALANCED TWIN FEEDER... 6d. 50 or 300 ohms. DITTO SCREENED per yd. 1/8. 50 ohms only. WIRE-WOUND POTS. 3 WATT. Pre-Set Min. T. Type. All values 20 ohms to 30 K., 3/- ea. 50 K., 4/- (Carbon 50 K. 4.20 2m)

WIRE-WOUND 4 WATT. Pots. 2 1/2 in. Spindle. Values, 100 ohms to 50 K., 5/8; 100 K., 6/6. CONDENSERS. New atock. .001 mfd. 7 kV. T.C.C., 5/6. Ditto, 20 kV., 9/8; 100 pf. to 500 pf. Mica, 6d.; Tubular 500 v., 500 pf., 6d.; 6d.; .05, .1, .25, 1/6; .5, 1/8; 1, 1/6; 1,500 v., 9d.; 1,600 v., 1/3; 1 mfd. 2,000 volts, 4/6. CERAMIC CONDS., 500 v., .5 pf. to .01 mfd., 10d. SILVER MICA CONDENSERS. 10%, 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3. DITTO 1/3 pf. to 500 pf., 1/-; 515 pf. to 3,000 pf., 2/6.

I.F. TRANSFORMERS 7/6 pair 465 Kcs Slug tuning Miniature Can 2 1/2 in. x 3/4 in. High Q and good bandwidth. By Eye Radio: Data sheet supplied.

NEW ELECTROLYTICS. FAMOUS MAKES

Table with columns: TUBULAR, TUBULAR, CAN TYPES. Lists electrolytic capacitor values and prices.

Screen Base Type 512, 8/500 v., 3/-; 16/500 v. 4/-; SENTRECEL RECTIFIERS. E.H.T. TYPE. FLY-BACK VOLTAGES. K323 3 kV., 5/-; K340 3.2 kV., 7/-; K345 3.6 kV., 7/6; K348 4 kV., 8/-; K3100 8 kV., 14/8; MAINS TYPE, RM1, 125 v., 60 mA., 5/-; RM2, 100 mA., 6/-; RM3, 120 mA., 8/-; RM4, 250 v., 275 mA., 26/-.

PANEL LAMPS (Neon Lit), 250 v., A.C./D.C. 3/6. COILS Wreath, "P" type, 3/- each. "O" type, 4/- each. "Q" type, add dust core, 4/- each. All ranges. TELETRON, L & Med. T.R.F., with reaction, 3/6. FERRITE ROD AERIALS. M.W., 8/9; M. & L., 12/6. T.E.F. COILS 4/HF, 7/- pair.

H.F. CHOKES, Iron cored. 14 M.H., 3/- each.

ALUMINIUM CHASSIS. 13 s.w.g. un drilled.

With 4 sides, riveted corners and lattice fixing holes. 2 1/2 in. sides, 7 x 4 in., 4/6; 9 x 6 in., 5/8; 1 1/2 x 7 in., 6/9; 1 1/2 x 9 in., 8/6; 1 1/2 x 11 in., 10/6; 1 1/2 x 14 in., 12/6; 1 1/2 x 18 in., 14/6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS.

250 v. 12 v., 11 amp. 8/9; 250 v. 12 v., 11 amp. 12/6. CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 11 amp., 13/6; 4 amp., 21/-. VALVE MANUALS I & II, 5/- each.

VALVE and TV PUP equivalent boxes, 5/- each. HYDROMETER, New Ex Gort. Tubercle-able. Packed in metal case 7 x 1 1/2 in., dia., 4/6. WAVECHANGE SWITCHES. 5 p. 4-way 2 water, long spindle 6/6 2 p. 2-way, 3 p. 2-way, short spindle 2/6 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle 3/6 3 p. 6-way, 1 p. 2-way, long spindle 2/6

VALVE HOLDERS, Pat. Int. Oct., 4d. EF50, EA50, 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6, 7, and 9 pin, 1/- MOULDED Mazda and Int. Oct. 6d. B7G, B8A, B8G, B9A, 9d., B7G with can, 1/6. VCR7, 2/6. B8A with can 2/6. CERAMIC, EF80, B7G, B8A, Int. Oct. 1/-, B7G with can 1/9. BLACK CRACKLE PAINT, air drying, 3/- tin.

Merry Christmas to all. Please post your Orders by Monday, 17th December.

RADIO COMPONENT SPECIALISTS 307 WHITEHORSE RD., WEST CROYDON

SHOP CLOSED 24th DEC. 10 page list 3d. Tel. THO 1555, Buses 133, or 68 pass door. 48-hour postal Service. P. & P., 1/- £2 orders post free. (Export Extra.) C.O.D. Service 1/6

FREQUENCY MODULATION ENGINEERING

T/V ENGINEERING

RADIO SERVICING

RADIO ENGINEERING

RADAR ENGINEERING

BASIC ELECTRONICS **INDUSTRIAL ELECTRONICS**

ELECTRONIC ENGINEERING

PRACTICAL, UP-TO-THE-MINUTE I.C.S. training . . .

can help you to attain one of the many well-paid posts that exist today in the radio world. Prepare yourself now, at home and in your own time, with the expert help of I.C.S. tutors. The cost of an I.C.S. Course is moderate and includes all books.

Complete the coupon below and post it to us today for further details of the Course which interests you. Write to : Dept. 170F, I.C.S., 71 Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS

DEPT. 170F, INTERNATIONAL BUILDINGS, KINGSWAY, LONDON, W.C.2.

Please send **FREE** book on

NAME AGE
(Block letters please)

ADDRESS


OCCUPATION.....I.57

INTERNATIONAL CORRESPONDENCE SCHOOLS

BUILD YOUR OWN TAPE RECORDER NOW

with the
" ASPDEN "

Tape Deck and Amplifier Kits

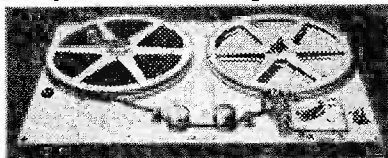

TAPE DECKS :

Compact model 521, 5in. reels £7/10/-.
Standard Model 721, 7in. reels, kit, £8/10/-.
Two speed, twin track, precision machined parts, easy to assemble, full assembly drawings and instructions, finest motor. High quality Ferroxcube Heads. Either deck fully built and tested, 27/6 extra.

AMPLIFIER :


Record/replay, 2½ watts, neon indicator, 2 recording positions, kit, £5/18/-.
Power pack for above, kit, £2/18/6 (both without valves).
Carr. & packing extra.

" . . . would like to express my appreciation of the quality and workmanship of this job at a most attractive price."—C. H. R., Sheffield.

Send stamp for full details to :—

W. S. ASPDEN 10, Market St., Wesham, KIRKHAM, LANCs.

BUILD THIS JASON QUALITY F.M. KIT

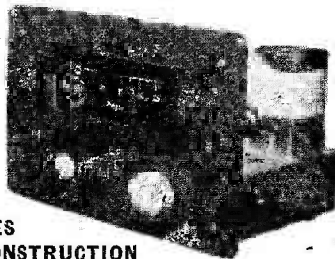

- **STABLE**
- **4 VALVES**
- **EASY CONSTRUCTION**
- **FREEDOM FROM DRIFT**

When built the Jason F.M. Tuner provides good sensitivity with freedom from drift and highest quality reproduction. Output 0.5 v. Chassis supplied ready punched. Useful range—50 miles; fringe area version available. Book of the Jason F.M. Tuner (Data Publications, 2/-, or 2/3 post free. Detailed price list on application.

Complete kit of quality components less valves, £5.5.0. Fringe-area version (less valves), £6.0.0. Power-pack kit, £2.1.9.

● **JASON "ARGONAUT" A.M.-F.M. KITS**
For building as a tuning unit or complete self-powered receiver. Book by Data Publications, 2/- (2/3 post free).

FROM LEADING STOCKISTS, or in cases of difficulty :

JASON MOTOR & ELECTRONIC CO. Phone : SPE 7050
328, Cricklewood Lane, London, N.W.2.

switch positions: 1—Off. 2—L.T. switched on, B on frame switched to chassis, oscillator grid switched to grid winding of M.W. coil, and oscillator anode to anode winding of same coil. 3—L.T. on, oscillator grid to grid winding of L.W. coil, and oscillator anode to anode winding of same coil.


Operational Notes

A 1.5 volt dry battery is used for filament supply. A 45 or 67½ volt standard or midget H.T. battery is used—many types of these are available. Best quality and volume of reproduction will not be obtained until the set is installed in a cabinet, as the lack of a baffle slightly reduces efficiency of the speaker. A 2½ in. diameter milled knob was used for tuning, and there was no difficulty in operating. A small knob is useless, here, as it will make tuning very critical and awkward. The condenser is set sufficiently far back for a small reduction drive to be added, if desired.

The four screws on the I.F. transformers should be screwed right down, avoiding undue force, however. Each screw should now be unscrewed two complete turns. All the three trimmers should be set at a midway position, and the core adjusting screws of the coils set so that about eight threads protrude. Upon switching on, the local station should be received. Tune this in accurately with the control knob, and adjust the four I.F. trimmers, one at a time, for maximum volume. (As this is done, it will be necessary to reduce volume by means of the volume control.) Once all the I.F. trimmers have been carefully peaked for maximum volume they may be left untouched.

A station near the low wavelength end of the M.W.

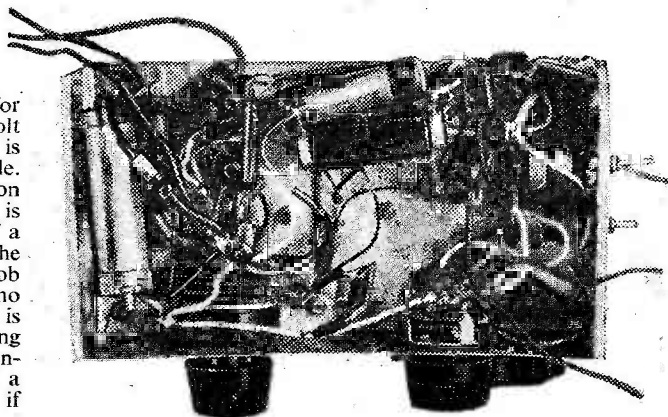band can now be tuned in and C2 adjusted for maximum volume, the gang condenser control knob being moved slightly, as required, to keep the signal correctly tuned in. When this has been done a



Underside view of the set.

high wavelength station is tuned in and the core of the M.W. coil adjusted, in conjunction with the tuning knob for maximum volume. The same procedure is carried out on L.W. The procedure should then be repeated to balance out any small differences which may have arisen.

If the coil cores are adjusted at the high wavelength end of the bands, and the trimmers at the low wavelength ends, it is not likely that any difficulty will arise. When this is done C1 may be adjusted, low on the M.W. band, for maximum volume, the tuning knob *not* being moved.

As with all portables the frame aerial is directional,

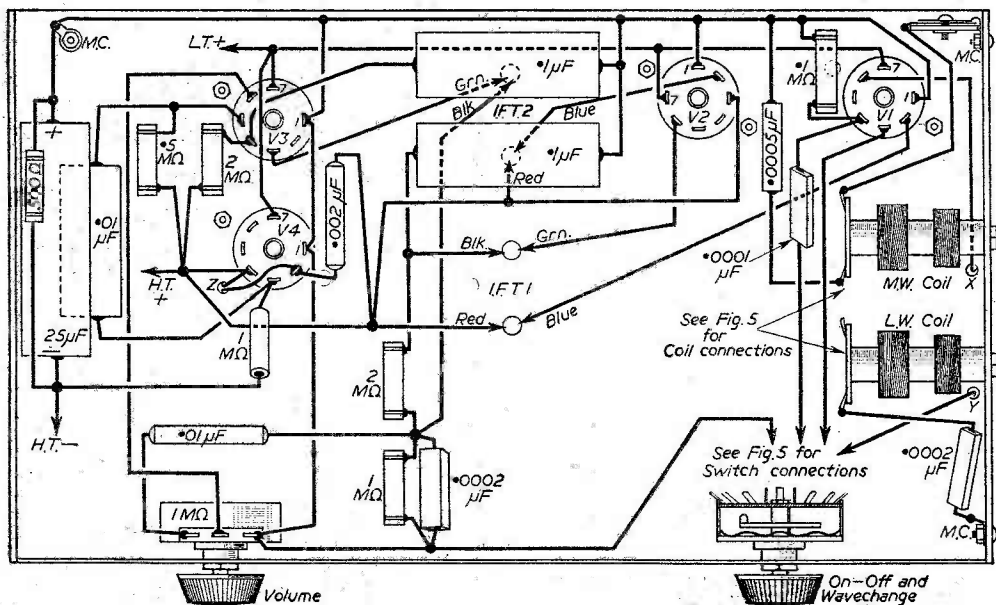


Fig. 4.—Underchassis wiring diagram.

though the sensitivity of the circuit renders this comparatively unimportant. In the localities where the set was used quite a number of stations were well received. Some overloading, causing distortion, arises when receiving local stations, unless the volume control is turned well back. Under these conditions, measured with a 10,000 ohms per volt instrument, nearly 2 volts A.V.C. bias is developed. (This voltage cannot be measured with a meter having a low internal resistance.) Used with a short, throw-out aerial a large number of quite distant stations were received. However, this is not, of course, required for normal purposes.

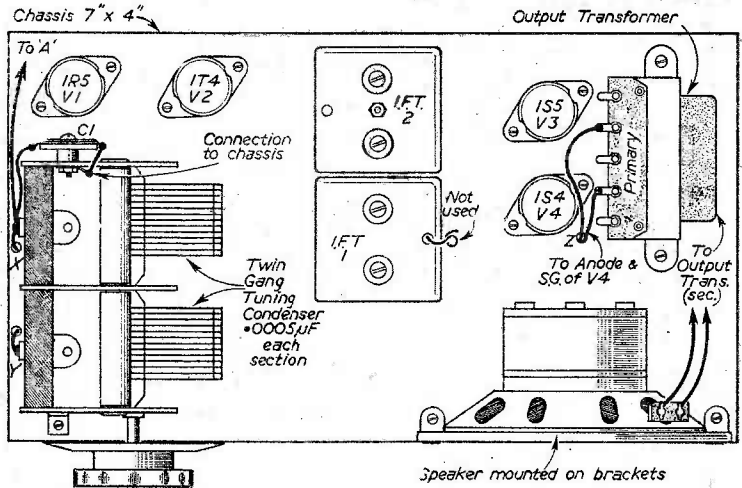


Fig. 3.—Above chassis data.

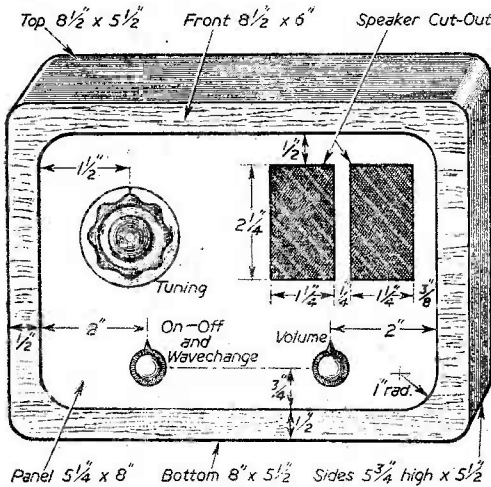


Fig. 6.—Details of the case and controls.

Cabinet for the Superhet Portable Four

The dimensions shown are for 1/4 in. plywood, and the use of wood of this thickness results in a strong cabinet, and avoids difficulties due to splitting. The receiver panel itself is of thinner material, secured to the chassis by the fixing nuts of the switch and volume control. When the cabinet is completed the receiver, with panel, can be inserted from behind. The panel then comes up against the cut-out front of the cabinet. This form of construction simplifies adjustment to the receiver, as it can be removed, complete, without disconnecting any leads.

The pieces should be sawn accurately, and glass-papered smooth. They are secured together by 1/4 in. panel pins, the heads being sunk by using a small punch, and the holes filled with plastic wood. The top overlaps the side pieces, but the bottom goes inside the latter. All the edges and joints are smoothed down quite level and afterwards rounded to improve appearance. Varnishing completes the cabinet. A small carrying handle might be secured to the top if this is preferred.

The panel should pass fairly easily into the cabinet


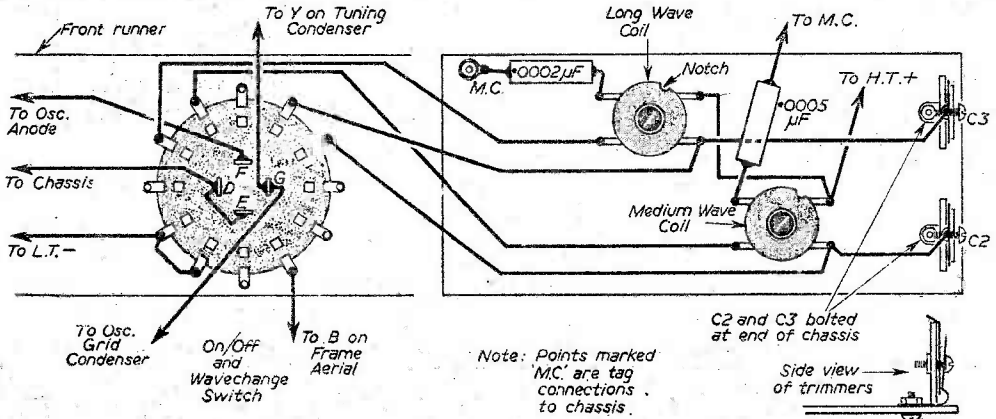


Fig. 5.—Switch wiring details.

RISF

Quality reproduction

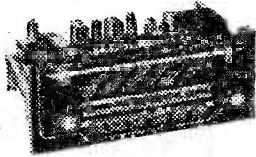


RADIO AND RADIOGRAM CHASSIS

Designed to the highest standards. General specifications applicable to all models: 200/250 volts A.C. 50 cycles. Horizontal multi-coloured glass dial. Slow motion tuning. Full Automatic Volume Control. Negative feed-back from output transformer secondary. Aerial, Earth, Gram, Pick-up and Extension Speaker sockets provided. Connections provided to Gram. Wide range tone controls for all types of recordings.

WESTFIELD. 5-valve superhet. 3 wavebands. **12 Gns.**
Packing & Carriage 12/6.


MANSFIELD. 7-valve superhet. 4 wavebands, including F.M./V.H.F. Band. **23½ Gns.**
Packing & Carriage 15/-.

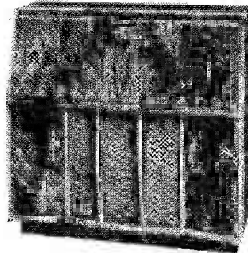HEATHFIELD. 9-valve superhet. 4 wavebands, including F.M./V.H.F. Band. Push-pull output. **26 Gns.**
Packing & Carriage 15/-.



THE APEX CABINET

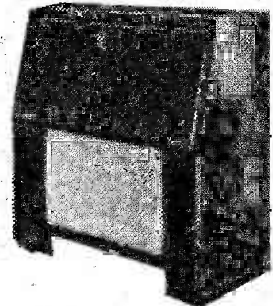High quality Bureau-type cabinet in selected Walnut veneered exterior with Light Sycamore interior and matching Rexine lining. Dimensions: Width, 34 ins. Depth, 17½ ins. Height, 33 ins. Sloping control panel on right-hand side, 16 ins. x 10½ ins. approx. Removable baseboard on right side, 15½ ins. x 15 ins. approx. **16½ Gns.**
Packing & Carriage 25/-.



THE EXCEL CABINET


Medium size, high quality Bureau-type cabinet in highly figured Walnut veneer. Dimensions: Width, 29½ ins. Depth, 16 ins. Height, 32 ins. Sloping control panel on right-hand side, 13 ins. x 10 ins. approx. Removable baseboard on right side, 13½ ins. x 13 ins. approx. Record compartment inside cabinet. **15 Gns.**
Packing & Carriage 15/-.

AUTOMATIC RECORD CHANGERS ★

Latest-type four-speed auto-changer, incorporating 16 r.p.m. for "talking-books" and arrangement for manual control. Fitted with high-fidelity H.G.P. 37. Crystal Turn-over Pick-up head, A.C. mains 200/250 volts. 50 cycles only. **£9.15.0.**
Packing & Carriage 12/6.

Latest Garrard R.C. 88 Model fitted with G.C.2 Crystal Turn-over Pick-up head. A.C. 200/250 volts. 50 cycles. **£13.0.0.**
Packing & Carriage, 12/6.

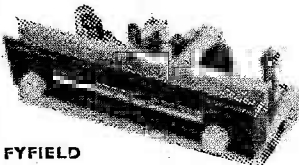★ **LOUDSPEAKERS, Gram Amplifiers, etc.**
Available at keenest Prices



F.Y. FIELD

F.M./V.H.F. Tuner in chassis form suitable for building into existing Radiograms or Receivers. **£13.15.0**
Packing & Carriage, 12/6.

F.M./V.H.F. TUNERS

These tuners are designed for maximum sensitivity and best signal to noise ratio. Eminently suitable for fringe-area reception. High stability capacitors are used at all critical points and drift is less than 20 kilocycles on any part of the band. 200/250 volts A.C. 50 cycles only.



CHESTERFIELD


F.M./V.H.F. Tuner Unit with automatic Magic Eye tuning, fitted in high-grade dark Walnut cabinet. Self-powered and completely self-contained. **16½ Gns.**
Packing & Carriage, 12/6.

ALL FULLY GUARANTEED

COMPLETE CATALOGUE AVAILABLE ON REQUEST

RADIO INSTRUMENT SUPPLY FACTORY

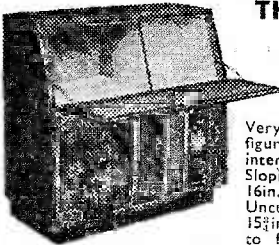STATION ROAD · HAROLD WOOD · ESSEX · INGREBOURNE 2935



THE SUPERIOR BUREAU
PRICE 16½ Gns.
 Plus 25/- carriage


Very elegant in highly figured walnut veneer with internal panels in sycamore. Sloping radio panel size 16in. long x 10½in. high. Uncut motorboard size 15½in. long x 13½in. back to front. Lid panelled

in beige leatherette. Two large storage cupboards. Speaker chamber large enough for 12in. speaker, overall cabinet size 35in. high, 34in. long, 16½in. deep.

BAKELITE CABINET

Ideal for midget construction. Available in Walnut or Green. Size 12in. long, 7in. high, 5½in. deep. Complete with handle, back, dial and two knobs.

PRICE
15/6
 Plus 3/-
 p.p.

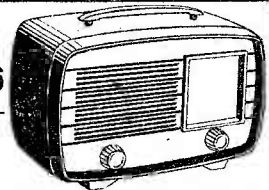

THE SUPEREX "55" BATTERY PORTABLE


Four valve superhet covering L. and M. waves. Attractive two-colour attache case size 10½in. x 8½in. x 4½in. Large elliptical speaker.

PRICE **£7-15-0**

Plus 4/- postage and packing


SEND 1/6 FOR FULL BUILDING INSTRUCTIONS.

S.R. 3-4 WATT AMPLIFIER

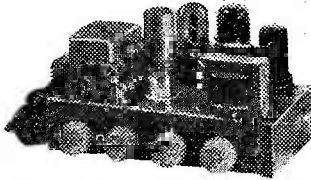

PRICE **£5.15.0** Plus 3/6 postage and packing.

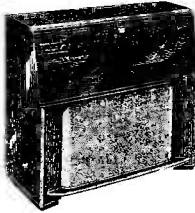High quality three valve three watt amplifier for A.C. Mains 200/250 volts. Four controls give a wide tone variation. 3 ohm speaker output. Chassis fully isolated. Valve line-up: 6SG7, 6V6, 6X5. Bronze finished chassis size 8in. x 4in. x 5in. high. Supplied built and tested, and guaranteed for twelve months (90 days valves).



THE OMP CT BUREAU
12 Gns.

Plus 20/- carriage

A well-designed cabinet veneered in highly figured walnut. Outside dimensions 29½in. long, 16in. deep and 32in. high. Sloping control panel on right hand side approximately 13in. x 10½in. Removable base board size 13½in. x 13in. on left-hand side. Large storage compartment located in side cabinet above baseboard.

PERSONAL SHOPPERS WELCOME

SHOP OPEN : 9 a.m. to 6 p.m. Monday to Saturday ; 1 p.m. Thursday.
 TERMS : Cash with order or C.O.D. (U.K. and N. Ireland only).

Superior
Radio supplies
37 HILLSIDE, (HARROW ROAD)
STONEBRIDGE, N.W.10. Elgar 3644


data for AUDIOPHILES*

Audiophiles all over the world are demanding Mullard audio valves for their high quality sound equipment. And who can blame them

when they know that the Mullard World Series of Audio Valves is the finest in the world. Fill in the coupon below for free data on Mullard World Series Audio Valves.

* *Audiophile - Enthusiast for high quality sound reproduction who is satisfied with nothing but the best.*

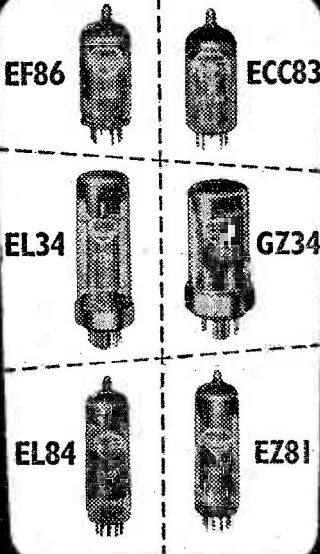This popular book is available now from most dealers, price 3/6d. It contains designs and full constructional details of the new Mullard EL34 High Quality 20 Watt Amplifier, a Mullard Band II F.M. Tuner, pre-amplifiers for the Mullard EL34 Amplifier and for the popular Mullard 5 Valve 10 Watt Amplifier, together with other useful technical information.



Mullard
 WORLD SERIES
 AUDIO VALVES



Mullard Ltd., Publicity Division,
 Mullard House, Torrington Place,
 London, W.C.1.

COUPON

To Mullard Ltd., Publicity Division
 Please send me, free of charge, leaflets on the Mullard World Series of Audio Valves, and details of "High Quality Sound Reproduction".

NAME

ADDRESS

TRANSMITTING TOPICS

COMPACT AND MULTI-BAND AERIALS

By O. J. Russell, B.Sc.(Hons.), G3BHJ



RECENT articles on compact aerials have evoked considerable correspondence, revealing the deep interest that exists in such systems. This is not surprising in view of the restrictions on space that handicap so many in this age of austerity. While few readers are likely to be in quite such a parlous plight, the writer recently had a few local QSO's on Topband using an indoor aerial of some 15ft. This is just to encourage those faced with difficult site problems!

Almost any location *can* be worked on some band or the other, and a study of aerial considerations may often enable efficient operation with very restricted sites. In fact, the writer was able to work some 20 countries upon 40 metres with an indoor aerial in a few weeks of operation, so that DX working is, in fact, possible even under "difficult" conditions. Indeed, with the recent resurgence of conditions, 10-metre DX may be easily worked with indoor aerials and limited power. However, before considering the questions of bands where small aerials are efficient due to the higher frequency, we may consider the plight of the Topband and Eighty enthusiast who is not able to erect even a 132ft. top for 80 metres. In fact, his "clear-run" may be much less than this. The sovereign remedy for "short" gardens is the "All Band" aerial shown in Fig. 1. Basically, this has a 100ft. top and 38ft. feeders. This may be resonated upon all bands from Topband downwards, as has been shown in previous articles, and there is no need for the radiating portion to be *in itself* an exact resonant length. Dispensing with the "fetish" of resonant lengths enables aerials to be tailored into the most unlikely spaces. However, the

Even 100ft. of clear run is often impracticable, even when the aerial is run over the house to obtain the maximum length that can be put up. The old solution may then be resorted to—that is allowing the "excess" length to be disposed of. One way is to run the excess length horizontally at right angles to the main length of the middle of the aerial. Another method in vogue is to allow the excess lengths to "hang down" at each end of the system, as shown in Fig. 2. Thus, with 25ft. hanging down at both ends, some 50ft. of length is saved, and the aerial may be accommodated in the majority of suburban gardens. However, if space is *really* limited, some of the excess length may be doubled back on itself, as shown in Fig. 3, so that in the limit the top section might be reduced to as little as 30ft. or 25ft. Remember that the dangling ends are "hot" from the R.F. point of view, so they should be carefully insulated, and preferably stood off from the aerial pole. Further, the hanging lengths will also act as vertical radiators, and it is quite feasible to adjust the top length so that the two vertical lengths are actually in or out of phase on some bands to give a vertically polarised directive pattern on these bands. Also, while it may seem absurd to reduce the top length to some 25ft. or 30ft. and still use it on Topband and 80 metres, remember that where space is limited a loaded aerial would be necessary. Even a highly efficient loading coil will introduce appreciable loss into a small loaded aerial, quite apart from earth-loss considerations. By utilising the extra aerial lengths as "loading," both excessive coil and earth losses are largely avoided. Hence the advantage of using such an arrangement even in very restricted spaces. Indoor

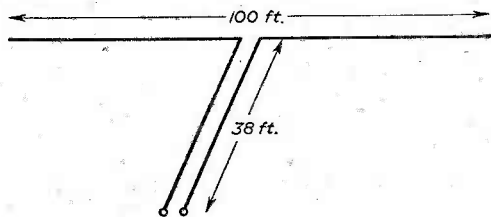


Fig. 1.—The "All Band Special" permits efficient operation upon all the usual amateur bands, performing well on 1.8 Mc/s, despite being shorter than the usual 80 metre half-wave dipoles. It is recommended as a useful standby aerial for all band working, even when separate aerials are available for the higher frequency bands.

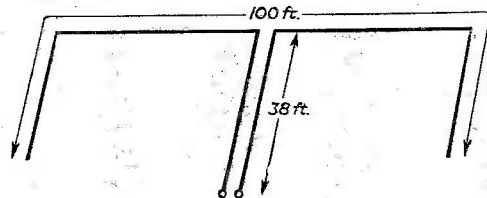


Fig. 2.—In restricted locations the "All Band Special" may be shortened by hanging the ends downwards.

reader is warned that the correct tuning network to resonate the "All Band" aerial is necessary. In practice this merely means the selection of either series or parallel tuning as shown by the tabulated instructions in Fig. 1.

and loft aerials for Topband have been used by the process of zigzagging as much wire as possible to fill a restricted space. Here again the idea was to obtain as much "length" of wire as possible to reduce coil and loading circuit losses. Strange as it seems, within a short range of the writer's present QTH, no fewer than three stations have operated with indoor aerials upon Topband! Needless to say however, Topband is easily the most difficult band for indoor aerials, and generally this is the last resort when an outdoor system is out of the question.

Higher Frequencies

However, upon the higher frequencies the outlook for indoor aerials steadily improves. Upon 40 metres, one highly efficient radiator is the "square loop" system. This is shown in Fig. 4, and is really a centre-fed half-wave aerial bent into a square loop. The main feature, however, is that on 40 metres this aerial fits fairly well round the picture-rail of an average room! In fact, of course, aerials of the correct resonant length could be built for outdoor use on any given band. It is actually an elementary form of Turnstile aerial, its value being that the 40-metre version fits the average room size! Of course, those

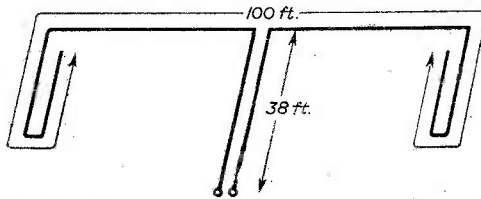


Fig. 3.—In very restricted spaces the "Allband Special" may be further compacted by doubling the ends back. The aerial may then be fitted into a very short space, while retaining better topband efficiency than a short Marconi type aerial.

with very restricted rooms might only be able to work with a 20-metre version. Where the room is such that not all the aerial can fit round the picture-rail, the spare length can either hang down at the open ends, or be formed into an extension of the feed end, so that they are, in effect, a lengthening of the feed length. Feed is exactly as for a centre-fed dipole—that is the shortest feedlength of, say, 300 ohm line is a quarter-wave length of tuned line. It is important to note, however, that this particular aerial is a "one-band" device—on its second harmonic it fires vertically through the roof—so that separate aerials have to be constructed of the correct dimensions for

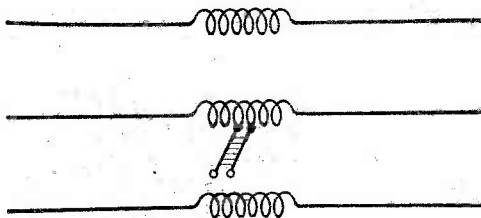


Fig. 5.—A beam array may be compacted by using loading coils. The elements may be reduced to about half their normal length. The element spacing should, however, not be reduced.

multiband operation. However, this need not be an insuperable snag, as the aerial itself is unobtrusive due to its convenient picture-rail fixing, and it is of good performance, being equivalent to a standard half-wave dipole in its radiating properties. In fact, it is upon an aerial of this type that the writer was able to work some 20 countries upon 40 metres from an indoor location. No great importance need be attached to exact squareness either, so that by various compromises such an aerial may be used in the average room for 40-metre operation or, of course, in small rooms for 20-metre operation!

Beam Arrays

The ambition of every amateur is to have some form of beam array. In fact, since the early description by the writer of methods of "compacting" beam arrays, these have become popular in the States, and, more recently, over here as well, and newer developments may be of interest. The "classical" method of shortening aerial elements is by the use of loading coils, and this may be applied to the standard forms of two and three element arrays as shown in Fig. 5. However, it should be noted that practically one runs into trouble if too great a shortening is attempted. Thus a reduction of element length by half is the most that should be attempted, as otherwise tuning adjustments become very critical and losses may become high. Also, of course, one cannot scale down the element spacings for a compact beam array without running into insuperable difficulties. With full-sized beam arrays the spacing is seldom less than a tenth of a wavelength, and tuning is very critical despite the full length elements. With "compacted" elements, a safer minimum spacing is 0.15 of a wavelength, that is, around one sixth of a wavelength. Moreover, due to the critical nature of adjustments, the simpler "compacted"

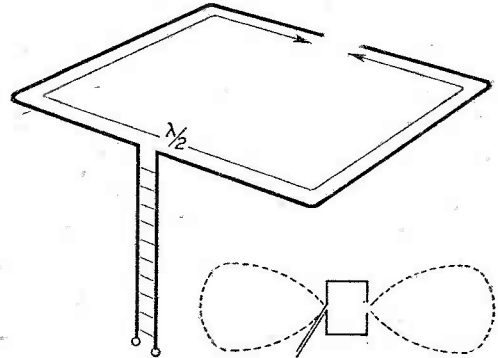


Fig. 4.—A half wavelength of wire, bent into a horizontal square loop, may be centre-fed, and behaves as a dipole. The small figure shows the radiation pattern. This aerial is a "one-band" device, however. Its advantage is that it is a "natural" for fixing round the picture rail of an average room.

beams are usually two-element affairs, as the addition of a third element gives relatively little extra benefit for the increase in size. For 20-metre operation the overall length of 15ft. to which elements may be reduced enables a two-element indoor beam to be used. One method is to use wire elements clipped to the picture-rail so that one can quickly orientate the beam in varying directions.

Stacking

Ambitious amateurs with adequate room may consider emulating the American amateurs who have erected three-element beams for 40 metres using compacted elements. However, once a beam for one band has been erected, the improvement in DX working effected leads to a desire for beams for use on the three highest frequency DX bands. With restricted space, the problem resolves into the difficult one of multiband compacted beam arrays. One solution is the "stack" array as shown in Fig. 6.

(Continued on page 773.)



BAND 3 T/V CONVERTER—185 Mc/s - 199 Mc/s

Suitable for London, Birmingham and Northern Transmissions

£2-5-0 post free.

A highly successful unit (*W/World* circuit), incorporating variable oscillator tuning, Midget BVA valves, etc. Chassis size 7 x 4 x 2 1/2 in. Thousands already in use. Suitable for most types of T/V sets. TRF or Superhet. Kit of parts 45/-, Blueprint 1/6, Power pack kit 30/-, Switch kit (Band 1—Band 3 Ae switching),

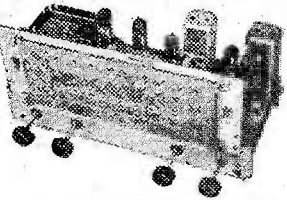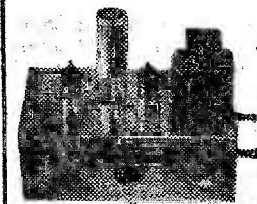6/6—all Post free. WIRE and aligning of above 20/- extra. Full range of Band 3 aerials in stock. Adaptors from 7/6 per set. Indoor dipoles 6/6. Outdoor with cables, 13/9. Band 1—Band 3 cross-over; filter unit, 7/6. Variable attenuators 6 db—36 db, 7/6. BBC Break-through Filter, suitable for BBC pattern rejector, 8/6.



ALL-WAVE RADIOGRAM CHASSIS

3 WAVEBANDS, 5 VALVES
S.W. 14 in. x 30 in.
8 or 1000 speakers to match. 21/6 and 25/6
L.V. 800 m. 2,000 m. 4 V.A. SERIES
Brand new and guar. A.C. 200/250 v., 4 pos. W/C sw. Short-Medium-Long-Gram. P.U. socket. High Q dust core coils. Latest circuit technique, delayed AVC and neg. feedback. O/P 4 watts. Chassis size, 12 1/2 x 2 1/2 x 2 1/2 in. 4 in. dia. top or vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost.
Chassis isolated from mains **BARGAIN 9/2 gns.**
Car. and ins., 4/6.

BARGAIN VALUE IN AUTO CHANGERS
3 speed auto change mixers for 7 in., 10 in., & 12 in. sections. Lightweight X-10 P.T. with turnover Diopoint magnetic stylus for Hi-Fi reproduction. Latest models—Modern styling. All brand new, boxed and guar. A.C. 200/250 v. only.
4 SPEED AUTO-CHANGERS—Latest 4 speed Collaro autochanger with Studio 9 pick-up, 10 in., 4 speed CARBARIU auto-changer, 91 gns. All suitable for above Radiogram chassis.

ALUMINIUM CHASSIS—18 s.w.g. Plain, un-drilled, folded 4 sides and riveted corners lattice fixing holes. Strong and soundly constructed with 2 1/2 in. sides. 7 in. x 4 in., 4/6; 9 in. x 6 in., 5/9; 11 in. x 7 in., 6/8; 13 in. x 9 in., 8/6; 14 in. x 11 in., 10/6; and 18 in. x 10 in., 3 in., 16/6.
SPECIAL OFFER—Goodmans 12 in. P.M. Speaker Audio 50. Brand new, boxed and guar. FEW ONLY, £4/10/-, Carr. 3/-.

Volume Controls—80 ohm COAX
Log. ratios, 10,000 ohms - 2 Megohms. Long spirals. 1 year guarantee. Midget Edis. wan type.
No Sw. S.P. Sw. D.P. Sw. 3/- 4/- 4/9
Linear Ratio, 10,000 ohms - 2 Megohms. Less switch, 4/- each. Coax plugs, 1/2. Coax sockets, 1/-. Couplers 1/3. Outlet boxes, 4/6.


TWIN FEEDER, 80 ohms, 6d. yd.; 300 ohms, 8d. yd.
TWIN SCREEN FEEDERS, 80 ohms, 1/3 yd.
50 OHM COAX CABLE, 8d. per yd., 4 in. dia.
TRIMMERS, Ceramic, 4 p.f.—70 p.f., 6d. 100 p.f., 1/0 p.f., 1/3; 250 p.f., 1/6; 500 p.f., 1/9. **PHILIPS** Resistor Type—2 to 8 p.f. or 3 to 20 p.f., 1/3 each.
RESISTORS—Pref. values 10 ohms 10 microuhms.

CARBON WIRE-WOUND
20% Type, 1 w., 3d.; 1 w., 3d.; 1 w., 3d.; 2 w., 9d.
10% Type, 1 w., 9d.; 5% Type, 1 w., 1/-; 1% Hi-Stab., 1 w., 2/-

WIRE-WOUND POTS
Pre-Set Min. T.V. Type. Knurled slotted knobs. All values 25 ohms to 50 K., 3/- ea. 50 K., 4/-. Ditto Carbon Track 50 K. to 2 Meg., 3/-.

CONDENSERS—Mica or B. Mica. All pref. values. 3 p.f. to 650 p.f., 6d. ea. Ceramic types, 2.2 p.f. to 5,000 p.f. as available, 9d. each. Tubulars, 450 v., Hunts and T.C.C., 100 p.f., 0.01, 0.05, 0.1 and 1 250 v., 9d., 0.2, 0.5, 1 500 v. Hunts T.C.C., 1/-, 25 Hunts, 1/6. 5 Hunts, 1/9. 1, 1,500 v. T.C.C. (Simplex), 3/6. 600 v., 6 K.V., T.C.C., 5/6. 100 to 20 K.V. T.C.C., 9/6.

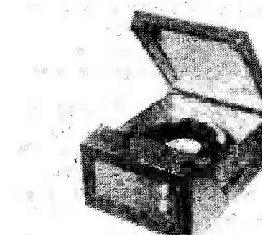STANDARD 3 WAVEBAND COIL PACK. Size 2 1/2 in. x 2 1/2 in. x 1 1/2 in. depth, 4 pos. switching, Long Med. Short, Gram. Dust-core coils prealigned for 465 Kcs I.P. Compatible with trimmers, ready to use. A very sensitive and efficient Coil Pack.
Manufacturer's Surplus. Bargain Offer, 27/6.



3 SPEED COLLARO RECORD PLAYER Complete with amplifier and speaker (as illustrated) A.C. 200-250 v. Bargain value—**KIT PRICE ONLY £12 10/0**, carr. and ins. 5/-
UNIT PRICES—Cabinet, etc., £3 3/0, carr. 3/6. Amplifier and bin. speaker, wired and tested, £3 12/6, carr. 2/6. 3 Speed Collaro Gram unit with Studio Hi-Fi pick-up, £6 19/6, carr. 2/6.


ELECTROLYTICS ALL TYPES NEW STOCK
Tubular Wire Ends
25/25 v. 60/75 v. 1/9
30/30 v. 4/500 v. 2/-
100/25 v. 2/450 v. 2/-
8/450 v. B.E.C. 2/3
8/500 v. Dub. 2/6
8-8/500 v. Dub. 4/6
8-10/450 v. T.C.C. 5/6
10/450 v. B.E.C. 3/8
10/500 v. Dub. 4/-
10/16,450 v. T.C.C. 5/6
12/350 v. Dub. 4/-
12/500 v. Dub. 5/-
10/4/50/550 v. B.E.C. 6/8

CHARGER TRANS. Prim.—0.200/250 v. sec., 0-9 v. 2 v. (for charging 6v. and 12 v.), 1.5 a., 18/6; 3 a., 18/8; 4 a., 22/6; 6 a., 25/8.
FULL WAVE BRIDGE SELENIUM RECTIFIERS—6 or 12 v. 1.5 amp., 3/8; 8 a., 15/6; 4 a., 18/6; 6 a., 24/6.

MAINS TRANSFORMERS—Made in our own Workshops to Top Grade spec. Fully interleaved and impregnated. **RADIO AND AMPLIFIER TYPE**—250 v. 60 Hz., F.W. sec., 5 v. or 0.3 v. 1 a. rect. 6.3 v. 2.5 a. set Htrs., 21/-, etc. **G.R.T. HTR ISOLATION TYPE**—Low leakage with or without 25% sec. boost voltage. Ratio 1:1, 25:2, 4:1, 6 v. or 12 v., 10/6 ea. Ditto with mains primaries 200/250 v., 12/6. Special to order. **SPECIAL TYPES**—To designers spec. Viewmaster, 35/-, Mullard Amp., 35/-, Osram, 91/2, 35/-. **HEATER TRANS**—Prim. 200/250 v., 6.3 v., 13 a. or 1 v. 2 for 12 v.; 750 or 10 v. 3 a. 2/8; 6.3 v. 3 a. 3 v. 9 a., 16/6. **L.F. CHOKES**—10 H. 95 ma., 6/-; 15 H. 100 ma., 10/6; 10 H., 120 ma., 10/8; 10 H., 150 ma., 15/6; Simplex, 10/6; Soundmaster, 10/6. **OUTPUT TRANS**—Standard pentode, 4/8; ditto tapped, pencil, 4/9; small pentode, 3/9; Midget battery pentode (1.5 a.) etc., 4/6.

SOLID SOLDERING IRONS (200/220 v. or 250/250 v.) 25 watt instrument type, 21/-; 65 watt, Pencil Bit Type, 26/8; 65 watt. Oval Bit Type, 25/-
Comprehensive stock of spares available.

LOUDSPEAKER P.M. 2 OBM 3 in. Celest., 17/6; 4 in. Celest., 18/6; 7 x 4 in. Goodman's Elliptical 18/6; Sin. Blac. 20/-; Sin. Goodman's special, 21/6. 10 in. B. and A., 25/-; 12 in. Plessey, 35/-; Sin. M.E. 3 K. 6 ohm field, tapped O.P. Trans., 24/6; 3 in. Blac., 17/6.
SOOTH BOY EMITAPE, etc., 1,200 ft., 30/-; Long playing, 1,800 ft. reels, 45/-; Paper tape, good quality, 1,200 ft., 12/6. Reels only, 6 in., 3/8; 7 in., 4/3

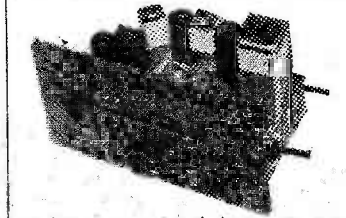

F.M. TUNER-UNIT (87 mc/s—105 mc/s), by Jason. As described (with components). Designed. Approved Kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, coils and cans. 4 BVA miniature valves and all components, etc., for only 26/10/0, post free. **SUPERIOR TYPE GLASS DIAL** (as illustrated)—mounted in 30 x 40 and edge lit by 2 pilot lamps, 19/6 extra. Illustrated handbook with full details, 2/- post free.

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2183)
50 yards Thornton Heath Station.
Buses, 130A, 133, 159, 165 & 193
Listed above are only a few items from our very large stock.
Hours: 9 a.m.—6 p.m. 1 p.m. Wed.
Send 31 stamps today for Complete Bargain list.
OPEN ALL DAY SAT.



Terms C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1/6. 7d., 11b. 1/11, 3/6, 1/6, 5/6, 2/-, 10/6, 2/9.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS

EXPRESS SERVICE!!!
C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER
BY LETTER, PHONE, OR WIRE, DESPATCHED
SAME AFTERNOON.

38 CHALGOT RD., LONDON, N.W.1
PRImrose 9090

UNIQUE OFFER
ANY PARCEL INSURED AGAINST DAMAGE
IN TRANSIT FOR ONLY 6d. EXTRA. SAVES
TIME IN CLAIMS AND WORRY.

074	6-1	6A8S	10F	6P1R	12G	6V6GT	7-	12K7	9-	61MP	10-8	D77	6-6	ECC81	8-	EZ80	8/6	N77	5-	R12	10-6	UY41	8-6
1A9	3-	6ACT	6/6	6P1R	12G	6X4	7-	12K7	14-	618PT	15-1	DAC52	11-	ECC82	10-6	EZ81	11-6	N142	10-8	RD6	7-6	V1507	5-6
1A5	6-	6A05	6/6	6P1R	12G	6X3GT	6/6	12K7	3/6	613B	10-6	DAP91	7/6	ECC83	9/6	FO15	12-6	N150	10-6	SP267	8/6	V15492A	2-6
1A7	12-6	6AG7	12/6	6P17	12G	6Z4S4	12/6	12K8T	7/6	72	4/6	DAP96	9/6	ECC84	12/6	EZ86	8/6	N152	11/6	SP61	3/6	V15848	15-6
1C2	9/6	6AJS	8-	6P2R	10/6	6Z7	12/6	12K6T	7/6	76	7-	DCC90	7-	ECC85	10-	GZ32	12/6	N154	9/6	TD02A	8/6	VP4	12-6
1C6	8/6	6AK6	5-	6P3S	12G	6A	12/6	12K8T	5/6	77	8-	DFP2	11-	ECC91	8-	GZ33	14-	N306	12-	TH233	12/6	VP27	8-8
1H5	11/6	6AKN	7/6	6P6	8/6	6B7	8/6	12K7	8-	78	8/6	DFP6	9/6	ECC96	12/6	H30	5-	N325	8/6	TH303	25-	VP133	7-8
1D4	6/6	6AL5	6/6	6P6G	8/6	7CC	8-	12K7	8-	80	8/6	DFP3	8/6	ECC92	14-8	I03	12-6	N700	10-8	TP22	10-6	VP23	6-6
1D5	5/6	6AM3	5/6	6P6M	3/6	7CC	8-	12K7	8-	83	8/6	DFH5	7/6	ECC83	10-	HR30	10-	OC9	9/6	V16	12/6	VP41	7-8
1N5	5-	6AM6	9/6	6P3S4	6-	7HT	8-	12K8T	7/6	85A2	12/6	DFH7	8/6	ECC42	10-	H2	3-	OD3	8-	V17	12/6	VP133	10-6
1N3	11-	6AQ5	7/6	6P36	6-	7HT	8-	12C56	7/6	150B2	12/6	DFH42	8/6	ECC81	8/6	HL130	7/6	PABCS0	15-	T27	7/6	VT801	5-6
1N1	8-6	6AQ8	10/6	6P36	6-	787	9-	12C4	10/6	210L1	3-	DK91	8/6	ECC80	10-	HL23	10/6			V27	12/6	W75	9-6
1S5	7-6	6ATG	8/6	6P3GT	6/6	7V7	8/6	12C12	10/6	307	6/6	DK93	9-	ECC	10/6	HL41	7/6	PC654	8-	V31	9/6	W77	6-6
1F4	7/6	6B4	6/6	6P3GT	6/6	7V7	8/6	12K7	10-6	308	25-	DS66	9/6	ECC	4/6	HL41D		PC685	12/6	V50	7/6	W132	9-6
1F6	10/6	6B7	10/6	6P36	6-	8A8	10-	12K7	14-	813	70-	DL2	15-	ECC7A	9-		12/6	PCF93	7-	V72	8-	W160	9-8
2A3	12-6	6B8G	4-	6P80	8-	8A2	2/6	19R1	10/6	806A	12/6	DL3	9/6	ECC99	6-	HVR2A	7/6	PCF83	11/6	U76	8-	WD142	11-
2C26	4-	6B8M	4/6	6P80	8-	8D9	3-	20L1	10/6	885	10/6	DL92	7/6	EP40	11-8	HVR22	8/6	PCF83	12/6	U76	7-	X61	10-6
2D13C	7/6	6B8G	7/6	6P1D3	10-	9D2	3-	30P1	10/6	956	3-	DL91	8/6	EP41	3/6	KP33	9/6	PEN25	8/6	V142	8/6	X65	10-6
2X2	4/6	6B8E	7/6	6P1D3	10-	9D2	3-	30P1	12/6	1203	7-	DL95	9/6	EP42	12/6	KL55	8/6	PEN40DD	U130	8-	X66	10-6	
3A4	7/6	6BFGG	12/6	617	7/6	10L1	8/6	12C56	8/6	3783	12/6	DL810	10/6	EP60(A)	7-	KT2	5-	855	U132	9/6	X142	10-8	
3A5	7-	6B6	8-	8N7	7-	10L3	9-	2324G	9-	7193	2/6	EL145	2/6	EP60(B)	5-	KT33C	10-	PEN43	6/6	U153	10/6	X150	10-6
3B7	8/6	6BWD	7/6	6P7H	8/6	10P13	11-	35Z3	8/6	7475	7/6	EA50	2/6	EP54	5-	KT41	10/6	PL81	11/6	U154	7/6	XPW10	6-6
3D6	2/6	6BWD	9/6	6P7H	8/6	10P13	15-	35Z	7/6	9002	5/6	EA70	9/6	EP80	10/6	KT63	7/6	PL82	9/6	U251	12/6	XFY12	6-6
3Q4	9/6	6B8X6	6/6	6P7G	8/6	12A6	8/6	24D7	7-	9003	5/6	EAC039	7/6	EP83	8/6	KT71	8/6	PL83	11/6	U319	7/6	XH145	4-6
3Q5	9/6	6B8Y7	8/6	6P8A7	8/6	12A8GT13	8-	20	7/6	9006	6/6	EAC42	11-	EP86	12/6	KTW81	7-	PM2B	12/6	U329	12/6	XSG(1.5)	
354	7/6	6C4	7/6	6SG7	6/6	12A87	8-	30C1	8-	ACDPEN	6/6	EB31	2-	EP89	10-	KTW93	7-	PM13	4-	U401	8/6		4-
3V4	8/6	6C3	6/6	6SH7	6-	12A88	12/6	30L1	8-	ACHL4		EB41	3/6	EP91	8/6	KTW52	7/6	PM12M	6/6	EAC42	11-	V62	7-6
3U4	8-	6C8	8-	6S7	8-	12A77	6/6	31	7/6	DDD15	3-	EB91	6/6	EP92	6/6	KTZ41	6-	PM40	9-	UBC41	8/6	V65	10-6
5V4	10/6	6C0D	10/6	6K87	5/6	12A07	8-	35S1	12/6	AC7P3	8-	EBCC	12/6	BL32	6/6	KTZ63	6/6	PM61	9/6	UBF90	10-	Z67	6-
5X4	10-	6C10	7/6	6N1GT	8-	12AX7	10-	35L6	9/6	AP4	7/6	BBC29	7/6	EL11	10/6	L63	6-	PM82	7/6	UCH32	10/6	Z77	9/6
5Y2	7/6	6D8	6/6	68N7GT	7/6	12BA6	8-	35Z4	8-	ATP4	3/6	EBC41	10/6	EL42	13-	LN122	10/6	PM3	10/6	UC41	9/6	Z142	13/6
5Y4	10-	6P1	12/6	6887	7/6	12B24	10-	35Z5	8/6	AZ31	12/6	EBF90		ELX1	15-	LN309	12/6	PM1	7-	UC42	13/6	Z150	12/6
5Z4	8/6	6E84	7/6	6T4GT	14/6	12E1	30-	41MP	12/6	3309	9/6		10-	EL51	10/6	LN316	10-	PM2B	12/6	UC41	10/6	Z152	9/6
6A4	8/6	6F7	10/6	6U3G	7/6	12H6M	3/6	41MT	12/6	3329	10/6	EL52	5/6	EL01	5-	MH4	5/6	QP25	6/6	UL16	12/6	Z170	9-6
6Z8	10-	6F8	10/6	6U7	8/6	12J5GT	4-	45Z5	12/6	BL65	7/6	EC54	6-	EM34	10-	MH11	7/6	QP50(15)	U05	8/6	Z229	12-3	
6AB7	8-	6P12	9/6	6V6G	7/6	12J7	8/6	50C5	10-	CK523	6/6	ECC81	16-	EY41	10/6	M84B	15-		10-6	U9	8-	ZD12	10-

Terms of business:—Cash with order or C.O.D. only.
Orders value £5 or over sent post/packing.
Orders below £5 please add 10% p.v.c.
C.O.D. orders:—Minimum fee, including post and packing, 3s. We are open for personal shoppers, Mon.-Fri. 8.30-5.30. Sats. 8.30-1 p.m.

CRYSTAL DIODES (1st Grade) OA71, GEN34, CG8E, M1, CG10S, all 7/- each.


All valves new, boxed, tax paid, and subject to makers' guarantee. First grade goods only, no seconds or rejects. All orders received by first post despatched same day. S.A.B. for free complete list, with terms of guarantee and conditions of sale.

A NEW *Armstrong* AM/FM RADIOGRAM CHASSIS

Specialists in high quality reproduction for over 20 years

PB 409

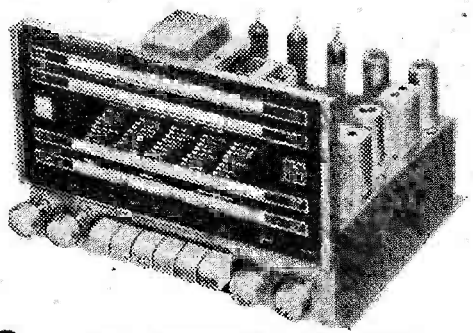- ARMSTRONG quality at an economical price
- ★ 9 valves-6 watts peak output *Within 2dB*, 20-20,000 c/s at 4 watts (double normal room volume)
- ★ Full VHF band (88-108 Mc/s) plus Long, Medium and Short
- ★ Push-Pull Output with Negative Feedback
- ★ Quick-action "Piano-Key" selectors
- ★ Independent Bass and Treble controls
- ★ "Magic Eye" tuning
- ★ Latest Mullard preferred-type valves



28 GUINEAS DIMENSIONS: 13" x 9 1/2" x 8" high

ARMSTRONG WIRELESS & TELEVISION CO., LTD.
WALTERS ROAD, LONDON, N.7. NOR 3213

Post this coupon for descriptive literature and details of Hire Purchase, Home Trial facilities and Guarantee.

BLOCK CAPITALS PLEASE.

NAME

ADDRESS

PW409

We have been making replacement radiogram chassis for nearly 25 years and have concentrated exclusively on the requirements of those who want the best. This is your guarantee of first-class performance and reliability. We shall be pleased to give you a full demonstration of this and other models at our Walters Road Showroom (open 9-6 weekdays and Saturdays).

This is intended to provide gain through stacking, together with a reduced angle of radiation so that DX working is facilitated. By making the stacking distance equal to 5/8ths of a wavelength at 10 metres, and using centre-fed elements that are half-wave on 21 Mc/s, we achieve the following: The array on 10 metres consists of two "extended" elements stacked at the optimum spacing of 5/8ths of a wavelength. On 21 Mc/s we have a stack of two half-wave elements spaced at slightly less than a half wavelength. On 14 Mc/s the array is two compressed stacked dipoles stacked at almost one-third wave-

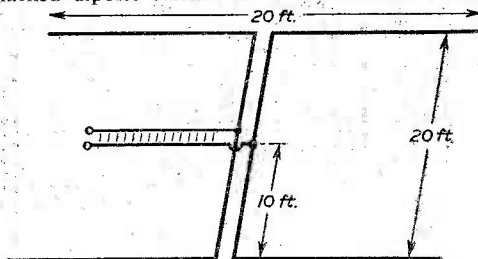


Fig. 6. — A simple stack array, usable on 14, 21 and 28 Mc/s. It improves low angle radiation and provides useful gain on all three of the bands.

length. This gives a measure of improvement over simple dipoles on all three bands. Moreover, as reflectors are not used, the array need only be turned through an arc of 180 deg. to cover all directions. By feeding in the centre of the vertical bridging feedline with a tuned line, the two elements are fed equally on all three bands, so there are no complicated matching devices at the aerial end. For restricted spaces such an array is well worth experimenting with, particularly if the lower element can be raised at least 16 ft. (and preferably 20 ft.) above ground level.

The saga of compact and indoor aerials can be extended almost indefinitely. This wire aerials of the W8JK type may be slung indoors, the writer has encountered at least one indoor 20-metre W8JK fixed beam and 10 metre wire W8JK beams are so compact that they may be erected on light bamboo spreaders in very restricted gardens. "Flop-over" wire beams of the reflector and director type may also be used in the form of wire elements slung on bamboo spreaders. In fact, wire element

arrays have possibilities for restricted outdoor use, especially when only one or two directions can be covered due to space limitations. However, an interesting three-element rotating beam design evolved by G4ZU, and commercially available seems to have solved the question of a reasonably compact three-band beam array. For those who have not seen this array described elsewhere, the following brief description is appended.

G4ZU Beam Array

The G4ZU design utilises an ingenious combination of the properties of transmission line sections with loading coils. The centre radiator is approximately half-wave for 21 Mc/s. Thus it acts as an "extended" dipole on 28 Mc/s, a half-wave dipole on 21 Mc/s, and a compressed dipole on 14 Mc/s. The director operates on 28 and 21 Mc/s, and consists of a 16 ft. element split in the centre. The loading coil is inserted in the centre, and is shunted by an open quarter-wave stub at 10 metres. Thus on 10 metres the quarter-wave stub is an effective short-circuit to the loading coil, and the element behaves as a simple director on 10 metres. On 21 Mc/s the director is loaded by the inductance of the loading coil plus the capacity due to the stub, and this is arranged to load the element so it behaves as a director on 21 Mc/s also. On 14 Mc/s the director still has a slight director action.

The reflector is a three-band device, and the loading coil is shunted with a stub quarter-wave long at 21 Mc/s. Thus, on 21 Mc/s the stub short-circuits the coil, and the reflector behaves on 21 Mc/s as a straightforward reflector. On 14 Mc/s, the reflector is effectively loaded by the coil and stub, and also operates as a coil loaded reflector on 14 Mc/s. On 10 metres each half of the reflector tends to act as a reflector, the system being effectively two phased reflectors. Thus the beam varies from a 14 Mc/s two-element beam, to a three-element 21 Mc/s beam, and a five-element 10-metre beam, due to the action of the coils and stubs. This ingenious system has been patented by G4ZU and is commercially marketed. It is clear

TUNING REQUIREMENTS

Band Mc/s	1.8	3.5	7 and 14	21	28
Tuning	Series	Parallel	Series	Parallel	Series or Parallel

that this beam array represents a very neat and effective solution of the problem of designing an effective and compact three-band rotary array. Moreover, the same principles might be applied to make simpler versions where space is extremely limited.

"The Elements of Mechanics and Mechanisms"

ARE you a designer? A mechanical engineer? A draughtsman? An inventor? Do you wish to know how a particular mechanism works? Do you wish to know the laws of nature, the laws of motion? Are you a student of mechanical engineering? Are you a teacher of mechanical engineering? If you are any of these, a new and important work, by F. J. Camm, entitled: *The Elements of Mechanics and Mechanisms* (30s., or 30s. 9d. by post from the offices of this journal) is the book you require. In its fully-indexed 433 pages with 481 illustrations, it explains the natural forces, the laws of motion,

horse power, the measurement of force, the units of pressure, force, energy and power, conduction, convection, radiation and heat, the lever, the wheel and axle, pulleys, the inclined plane, wedge and screw, compound machines and liquid pressure, hydraulics, the hydrometer and viscosimeter, the siphon, the buoyancy of liquids, pumps and water wheels, the Geneva and other intermittent mechanisms, the principle of the gear and power transmission methods, whilst a very lengthy and well illustrated chapter deals with miscellaneous mechanisms.

This will become a standard work on a subject of great importance at the present time, and upon which there is a great scarcity of literature.—A. N. J.

Converting a Portable to Car Radio

AN INTERESTING CONVERSION WHICH IS APPLICABLE TO MOST PORTABLES

By W. B. Cooper

OWING to the cost of car radios it was decided to convert a small battery portable for use as a car radio. Several of my friends, each possessing portables of differing makes and sizes, had used them in their cars, but with only partial success. To place a set of this type on the car seat or parcel shelf is asking rather too much of it, for the set is virtually screened by the car body, and the frame aerial, being directional, is not capable of receiving a steady signal at all times during the car's progress.

Some two years ago I purchased an Ever Ready Sky Queen portable radio and used it only when stationary or when picnicking, etc., for I was afraid to attempt conversion of anything so new. However, when the newness wore off, I considered modifying this receiver for use when the vehicle was in motion, and without disturbing anything in the receiver itself made the first simple modification. This merely consisted of a coupling coil placed in close proximity to the frame aerial; one end of the coil being earthed, the other attached to a telescopic type of aerial. This was done simply by winding six turns round the cabinet itself as shown.

The wire used was fine cotton covered copper wire taken from an old coil. The two ends were taken through small holes drilled in the bottom of the cabinet and terminated on a miniature socket strip at the back. A piece of twin flex with wander-plugs on each end was then taken from the sockets in this strip to a small two-pin socket mounted in an accessible place in the car. A pair of wires was then taken from the rear of this latter socket to earth and aerial respectively. The telescopic aerial was fixed temporarily to the vehicle for the initial test. The result was so good that I mounted the aerial (single hole fixing) immediately and enjoyed many hours of good reception. Reversing E or A on the coupling coil made no difference.

The car was a small Austin Seven Ruby Saloon and

the set rested on the back seat (passenger side). It was a very simple matter to switch on or off or tune with the left hand. The radio functioned most satisfactorily in this way for well over a year and was still, to all intents and purposes, a portable, for on arriving at a destination it was an easy matter to remove the wander plugs from the rear of the set and lift it out if it was required on the beach or other place inaccessible by the car itself. The six turns of wire were neatly covered by a strip of contrasting passe-partout. The obvious disadvantage was the partial loss of space on the back seat, but as invariably

6 turns of wire round cabinet and covered by passe-partout

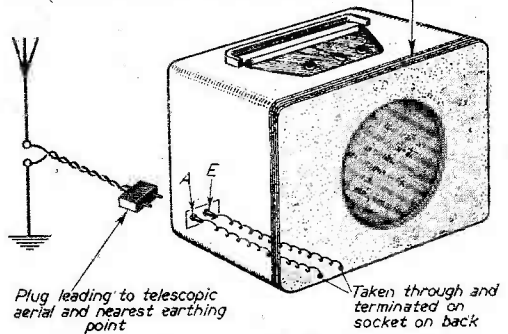


Fig. 1.—How to add the car aerial.

only one person travelled in the back of the car this did not trouble us. Owing to lack of space in the front of the Austin it was not possible to suspend the set from the dashboard or other frontal position.

Suppression

The only equipment required for complete suppression of R.F. was one 5,000 ohm resistor in the main H.T. lead to the distributor, the resistor being placed as near to the distributor cap as possible (screw in type). There are many different kinds of small portables on the market to-day and nearly all are capable of being used in the way described. Ascertain the place and position of the frame aerial and then wind the coupling coil over it, near it or even on the detachable back. Naturally one will need to experiment a little with the turns ratio for the various positions tried in order to obtain the best signal strength, but this is very interesting work. The Sky Queen, by virtue of its design, and many of the smaller Bush models with frame aerials at the front of the cabinet are ideal for this type of modification. If space is not the all important consideration and portability is still required I feel this is the simple answer to the question of whether or not a

(Continued on page 777)


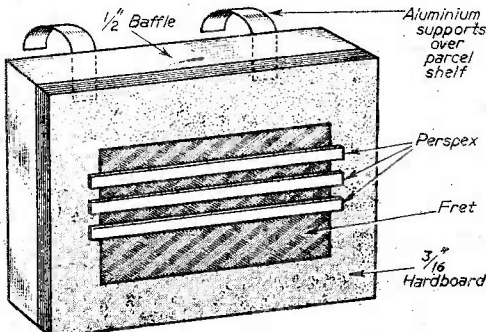


Fig. 5.—The home-made case for the speaker.

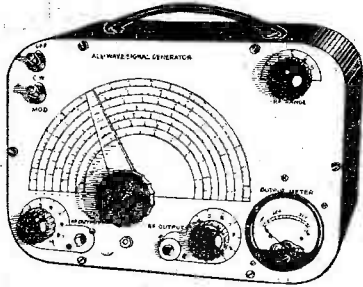


COMPLETELY BUILT SIGNAL GENERATOR

Coverage 150 Kc/s-250 Kc/s. 300 Kc/s-900 Kc/s. 600 Kc/s-2.75 Mc/s. 2.75 Mc/s-8.5 Mc/s. 8 Mc/s-28 Mc/s. 16 Mc/s-56 Mc/s. 24 Mc/s-84 Mc/s. Metal case 10in. x 8in. x 4in. Size of scale, 6in. x 3in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%. £4/19/6 or 24/- deposit and 3 monthly payments 25/- P. & P. 4/6 extra.

SIGNAL & PATTERN GENERATOR

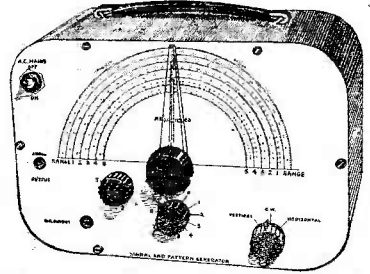Coverage 7 Mc/s-210 Mc/s. in five bands, all on fundamentals, slow-motion - tuning, audio output. 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy $\pm 1\%$. A.C. mains 200-250 v.



£6. 19. 6


P. & P. 5/6.

Or £3 deposit and 3 payments of 30/-.

COMMERCIAL TELEVISION CONVERTER SUITABLE ANY T.V. ALL CHANNELS NO ALTERATIONS TO SET

Complete with built-in power supply 230-250 v. A.C. mains. Crackle finish case 5in. long, 3in. wide, 4in. high. Incorporating gain control and bank switch. Illustrated with cover removed.

£3. 19. 6 Plus P. & P. 2/6.

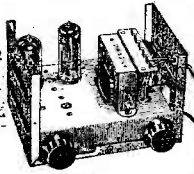

Heater Transformer. Pri 230-250 v. 6 v. 1 1/2 amp., 6/-.
Extension Speaker cabinet in polished walnut, complete with 8in. P.M. P. & P. 3/- 24/6.
8in. P.M. Speakers, removed from chassis, fully guaranteed. All by famous manufacturers. P. & P. 1/6, 12/6.

FAMOUS MAKE TURRET "TELETUNER"

Covers all Channels, Bands 1 and 3. Valves used : PCC84, R.F. double triode, cascade R.F. amplifier, PCF80, triode pentode f.c. and mixer, I.F. output 63-50 Mc/s. Easily modified to other I.F. outputs. Full instructions and circuit diagram supplied. Complete with 12 Coil Sets. **99/6** post Knobs, 3/6. 2/6.

Volume Controls. Long spindle less switch, 50 K., 500 K., 1 meg., 2/6 each. P. & P. 3d. each.

Volume Controls. Long spindled and switch, 1, 1, 1 and 2 meg., 1/- each, 10 K. and 50 K., 3/6 each. 1 and 2 meg., long spindle, double pole switch, miniature, 5/-.

Standard Wave-change Switches. 4-pole 3-way, 1.9 : 5-pole 3-way, 1/9. Miniature 3-pole 4-way, 4-pole 3-way, 2/6. 2-pole 11-way twin wafers, 5/-, 1-pole 12-way single wafers, 4/-.

1,200 ft. High Impedance recording tape on plastic spool, 12/6, plus 1/- P. & P.

GARRARD RC/110

3-SPEED AUTOMATIC MIXER CHANGER



Will take 10 records, 7in., 10in. or 12in. mixed, turnover crystal head, brand new, current model. A.C. mains 200/250 v. (List price £14/10/-).

£7. 19. 6

P. & P. 3/6.

COLLARO RC54 3-SPEED AUTOMATIC CHANGER

will take 10 records mixed.

STUDIO "O" PICK-UP A.C. mains 200/250 v.

£7.19.6 Plus P & P 5/-.



P.M. SPEAKERS, 6in., closed field, 18/6. 8in. closed field, 20/6. 10in. closed field, 25/-, 12in., 25/-, P. & P. on each 2/-.
Valveholders, Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded BTG 7d. Loctal amphenol, 7d. Loctal pax, 7d. Mazda Amph., 7d. Mazda pax., 4d. B9A, B9A amphenol, 7d. BTG with screening can, 1/6. Duodecal paxolin, 8d.
Twin-gang .0005 Tuning Condensers, 5/- With trimmers, 6/6.

AC/DC MULTI-METER KIT




Comprising 2in. moving coil meter, scale calibrated in AC/DC volts, ohms and milli-amps. Voltage range AC/DC 0-10, 0-100 and 0-500. Milli-amps 0-10, 0-100. Ohms 0-1,000 and 0-10,000. Front panel, range switch, wire wound pot. (for ohms zero setting) two toggle switches, resistors and meter rectifier. Complete in case, grey hammer finish. **19/6** Plus P. & P. 1/6

Point to point wiring diagram 1/- free with Kit.

Potato & Vegetable Peeler, by famous manufacturer, capacity 4 1/2 lbs., complete with water pump. All aluminium construction, white stove-enamelled finish. Originally intended for adaptation on an electrical food-mixer, can easily be converted for hand operation. 89/6. P. & P. 3/-.

T.R.F KIT in PLASTIC CABINET

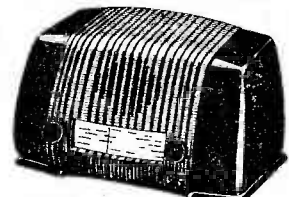3 valve plus metal rectifier, A.C. mains 200-250 v. Medium and Long waves. In pastel blue or brown. Valve line-up : 2 VR65s and VT52. Size 15in. long by 9in. high by 7in. deep. **£3. 19. 6** P. & P. 4/6.



Point to point wiring diagram 1/6 free with Kit.

Where post and packing charge is not stated, please add 1-6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

RADIO & T.V. COMPONENTS (Acton) LTD.
23, HIGH STREET, ACTON, LONDON, W.3

YOU CAN MAKE MONEY!

Our 'Know-How' shows the easy way
NO RADIO KNOWLEDGE NECESSARY

... for the

"GOOD COMPANION" Portable

Use long nights and spare time profitably. Make these superb Battery Portables for yourself and your friends—our 'Faultless Technique' makes it so easy.

- 4 VALVE SUPERHET
- MEDIUM & LONG WAVES
- ONLY SCREWDRIVER, PLIERS
- & SOLDERING IRON NEEDED
- 7 GNS. COMPLETE WITH EASY INSTRUCTIONS



YOU CAN'T GO WRONG WITH THE NEW

"FAULTLESS" TECHNIQUE—WRITE FOR DETAILS

NOW—ONLY 1/6 POST FREE!

The **SIMPLE SUPERHET** at ONLY 139/6

A perfect 5 Valve Superhet for (plus 2/8 p. & p.)

Home Construction—just the job!

The **METEOR III TRF** at ONLY 109/6

The 3 Valve with the BIG output (plus 2/8 p. & p.)

—ideal for the beginner!

Send for 'Know How' Diagrams—ONLY 1/6 POST FREE.

(Tell us which set you prefer)

NORMAN H. FIELD Electronics

Dept. PH., 68, Hurst St., Birmingham, 5. Birmingham's Largest Constructors' Store

UNIVERSAL SHUNTS. 1% accuracy for any 1 mA or 500 μ A meter. Only one simple adjustment to make, no calibrating meter being required. With instructions. Guaranteed one year. S505 (1 mA) covers 1, 5, 25, 100 and 500 mA. S51 (1 mA) covers 2, 10, 50, 200 mA and 1 amp. Price 15/6.

Shunts for all meters with ranges to your specification. Reasonable prices. Please give meter details, accuracy required, etc.

21 Range A.C./D.C. MULTIMETER KIT for 500 μ A meter. Kit of 14 High Stability Resistors 1%, Shunt \times 505, Potentiometer, Westinghouse Meter Rectifier, and other resistors to give 4 A.C. volts, 10 D.C. volts, 6 Current and a resistance range. With circuit and instructions, 46/-. Switches available.

Resistance Box Standards. Twelve wirewound resistors, 1, 2, 2, 6, 10, 20, 20, 50, 100, 200, 200, 500 ohms to give any value between 1 and 1,110 ohms in 1 ohm steps 0.5% accuracy 30'; 0.2% 41'. Ditto but 10 to 11,100 in 10 ohm steps 0.5% 32'; 0.2% 43'. Ditto but 1 to 11,110 in 1 ohm steps (18 resistors) 0.5%, 42'; 0.2%, 53'.

Bridge Ratio Arms. 1,000 ohms tapped at 100 and 10 ohms. Pair gives ratios of 100, 10, 1, 0.1, 0.01 to 1, accuracy 0.1%, 19/6 pair.

Precision Wirewound Resistors. Any value 1 to 1,000 ohm, 0.5% 2/9; 0.2% 3/9, 1,000 to 5,000 ohms 0.5% 3/3; 0.2% 4/3.

Calibrated Potentiometers for RC Bridges. A few Wirewound pots, complete with hand calibrated scale suitable for workshop RC Bridge, 10/6.

High Stability Resistors. Your enquiries invited for the above, especially non-standard values. S.A.E. with enquiries please.

PLANET INSTRUMENT Co.

25, Dominion Ave., Leeds, 7.

Best Buy at Britain's

TWO-WAY MORSE TRAINING SETS, W.T Mk. 3. Consists of two valve oscillators (ARPI2's) (one with pitch control), for one or two operators. Has provision for creating 'Atmospherics.' In polished oak case 12 1/2 in. x 10 in. x 8 in., wt. 16 lbs. Complete with valves, leads, 2 keys, 7-way terminal board, circuit and instructions but less batteries and phones. Ideal for Cadets, Scouts, etc. SNIP. 19/6. Headphones for above, 10/6 pair.

RESISTORS. Latest miniature insulated Dubilier $\frac{1}{2}$ watt type B.T.S. Wire ends. Useful values. ONLY 10/- for 100 assorted! 1 and 1 watt, Eric, etc., 1 gross assorted, 10/-.

FIELD TELEPHONES, Army type D, Mk. 5. Buzzer calling. Ideal for building sites, farm, workshops, etc. Complete with handset and batteries. Tested before despatch. 39/6 each.

SOUND-POWERED HANDSETS.—Similar to telephone. Balanced armature microphone and earpiece. No batteries required. 10/6 each. Breast mike and pr. headphones, as above. 12/6 set.

LORAN INDICATOR CHASSIS.—Complete with 5CP1 CRT and screen, but less valves and crystal. New condition, 29/6.

RT37 PPN2 BEACON TRANSMITTER-RECEIVER, 214-234 Mc/s. Size 18 in. x 10 in. x 5 in. Contains 5 3A5, 3 1R5, 1 1R5, and 2.2v. synchronous vibrators. Operates from 2 v. accumulator via 2 built-in vibrators. Complete with telescopic mast antenna system (9 ft.), lightweight headphones, Technician's Manual, super quality carrying haversack, cords, co-ax. cables plugs, etc. Total wt. 28lb. BRAND NEW, boxed, American equipment, 72/6.

THREE-CORE CABLE.—23/6, rubber ins., circular, padded, cotton covered, maroon 12 yds. 9/- or 100 yds. 59/6.

RCA SPEAKER.—An 8 in. P.M. unit contained in beautiful black crackle cabinet, suitable for AR88, etc. BRAND NEW. Price only 45/-.

DEAL VOLTAGE BLOWERS.—12 and 24 v. Ideal for hair driers etc. heaters, etc. 25/- plus 2/6 postages.

INSTRUMENT TRANSFORMERS, Parmeko.—230 v. A.C. input, 0.65-130-195 v., 85 mA, 6.3 v. 5 Amp., 6.3 v. .3 Amp. output, Shrouded, 3 1/2 in. x 3 1/2 in. high, 15/-.

HEAVY DUTY L.T. TRANSFORMERS.—200-250 v. A.C. input, 30 v. tapped at 10 v. 30 Amps output, 5 1/2 in. x 6 in. x 7 in. high, wt. 24 lbs., 55/-.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS

CHARLES BRITAIN (RADIO) LTD.

11, Upper Saint Martin's Lane, London, W.C.2.


TEMPle Bar 0545

Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday.

CONVECTOR FIRES

£4. 19. 6

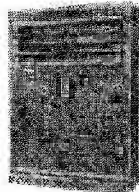2 k/watt (1 or 2 units per hour) Switched. Gilt finish. Illuminated grille. Size 26 in. x 18 in. x 7 1/2 in. deep. 200-250 volt AC/DC. Famous mfr. Ideal for home, office, works. Ins., Carr. 5/6 London; 10/6 Provinces.



FIRES 19/6

Ideal present, hammered finish, 200-250 volt. Wattage 500, 750, 1,000. (Please state preference.) Carr. 3/6.

17" RECTANGULAR T.V. TUBES 14"

£7.10.0. 6 month guarantee. £5.10.0.

15/6 Ins., Carr.

16" - 15" - 14" ROUND £5

3 month guarantee.

Remember most 9 in. and 12 in. sets can be fitted with a 15 in. tube with little or no alteration to the set. Ins., Carr. 15/6.

8" P.M. SPEAKERS 8/9

Ideal for fitting in small cabinet or cupboard door for the lady of the house so follow that T.V. or radio programme. Buy now. While stocks last. P. & P. 1/9.

REMEMBER SATURDAY OPEN ALL DAY

DUKE & CO.

621, Romford Rd., Manor Park, London, E.12

GRA. 6677-8

small portable radio will work in a car. From my experience the answer is very much in the affirmative. Anyone is quite capable of experimenting in this way and all car owners who do possess portable radios will, I am certain, be as pleased as I was if they experiment on similar lines. Those who do not possess portables can easily purchase good second-hand ones cheaply and effect this type of addition to the set for a few shillings.

Further Modification

Last October, however, I changed vehicles and purchased a Morris Minor. Being so used to having such a good travelling companion I decided to carry out an extensive modification to the portable and install it permanently in the car. I therefore decided

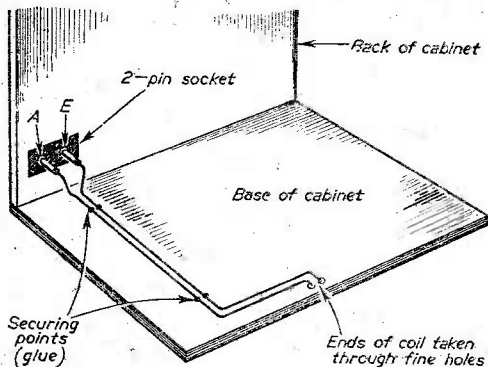


Fig. 2.—How to mount the aerial/earth socket.

to break the set down into three sections—receiver, speaker and power supply—and dispense with the cabinet altogether. This permitted a much more compact arrangement and a proper installation to be carried out. First, therefore, the frame aerial was removed. This was replaced by an aperiodic coupling coil (Osborn QAF5 medium wave aerial coil), this coil being directly coupled to the telescopic aerial, which had been mounted on the nearside front wing.

Directly coupling the coil gave more gain than when wired in the conventional way. The grid tapping of the coil was therefore paralleled to the grid of the mixer valve and the centre of the aerial socket (coaxial type), which had been mounted on the chassis (on an existing screw), the other end of this winding being taken to earth.

In this state the aerial was plugged in and with the set resting on the floor of the car it was trimmed to suit the aerial employed (Ekco CA224).

The Home Service (434 m.) was brought in strongly by adjusting the dust core of the coil, the Light Programme (247 m.) by adjusting the existing trimmer on the set. On switching to the long-wave band no adjustment was necessary as the long-wave loading coil had not been interfered with. The signal strength of the medium-wave Home and long-wave Light Programmes is sufficient to overload the speaker employed. In actual practice these are the two stations used.

Having done this it was necessary to make an attractive box for the set. This was done by using a sheet of tinplate and cutting it as shown to receive the set.

Soldering was easy, the set sliding in and being

secured by small self-tapping screws through the base of the box into the existing brackets on the set. The actual size of the box was $10\frac{1}{2}$ in. \times $5\frac{1}{2}$ in. \times $4\frac{1}{2}$ in., care being taken to allow enough space for the dial pointer to move freely when the Perspex front was mounted. A separate piece of aluminium to which was affixed a double socket was then fastened to the back of the box with self-tapping screws. To this socket ran the wires which had previously been connected internally to the speaker. A hole had been cut to allow the aerial plug to be inserted into the aerial socket on the chassis. Mounting the speaker socket in this way enabled the speaker to be placed anywhere in the car. The speaker normally used is mounted on hardboard and suspended from the parcel tray.

Actually, I have two speakers, the second having a long length of fine flex attached to it. This I use when we wish to listen to a programme when not in the car, the internal speaker merely being unplugged and the extension speaker plug being inserted in its place. (This, I am sure, would also be most useful to people towing caravans.)

There is much to be said for this type of arrangement, for when the car is stationary one can listen for lengthy periods without worrying about the possibility of over discharging the car battery. It is worth mentioning that the battery at present in use was purchased last January, is in use very day, and is still doing all that is required of it.

For the front and sides of the cabinet Formica was used to cover the tinplate, for it toned well with the interior paintwork. (It was not necessary to cover the top, bottom or back for these when mounted were out of sight.)

The Perspex front was removed from the original cabinet, mounted behind the Formica with six small nuts and bolts as shown and then fixed with four self-tapping screws to the lugs on the front of the tin box. When drilling the Perspex to take the small bolts use a sharp drill and drill over wood on a flat surface. The sides were also fastened to the tin, using small self-tapping screws, the top two screws on each side being used to hold the two brackets which were needed to suspend the box under the glove tray (passenger side).

The battery lead was brought out through a slot in the back panel and plugged into the battery, which rests out of sight behind the set itself on the parcel shelf. I did make a tin box to house the battery, thinking that it would be necessary to screen it, but this was found to be unnecessary. Having an independent power supply in this way makes the job of suppression

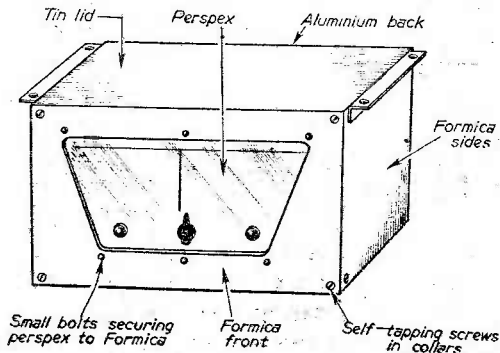


Fig. 3.—The receiver containing case.

easier, and the only suppression used is a resistor in the H.T. lead to the distributor and a .5 μ F pigtail condenser placed on the coil between the S.W. terminal and earth. It may be found necessary to suppress the dynamo and this again is done by using a pigtail condenser connected between the larger terminal (charging terminal) and earth. If there is any uncertainty as to which is the right terminal reference to the circuit diagram in the car handbook will be helpful. When making these tests always have the car in the open with bonnet closed and making a good electrical connection to earth. In new vehicles little suppression equipment is required, but in older cars it may be necessary to bond engine to chassis and exhaust system to chassis. This can easily be done using heavy copper braid. If any staccato type of interference persists it may be necessary to fix a resistor (5,000 ohms) in each plug lead, but as indicated, it is usual that only one will be required in the distributor lead.

Interference

I was troubled with interference which persisted on the long-wave band when the car was coasting with engine switched off. This interference gained in intensity on application of the brakes, and from its frequency it was readily discernible as static interference from a brake shoe or shoes binding in the drum. On examination, one wheel was found to be binding slightly and slacking off the shoes produced the necessary cure.

An important point to remember, too, is to see that the set when mounted on its brackets is making a good earth with the car body for much unnecessary interference can result if this is not the case.

As will be seen from the illustration, the finished set is quite compact and reasonably attractive in its appearance, and I am more than pleased with its performance.

I was at one time a little afraid that mounting the set rigidly in the way outlined would have serious effects on the miniature valves employed in it from the point of view of vibration causing internal breakdowns. I need not, however, have been worried for the valves have stood up to the test of time in a most remarkable way. Only one valve, the frequency changer, has been replaced in the past two years and that was due to the emission falling off, and not to mechanical breakdown as a result of vibration.

Many of the new portable radios have similar valve

Tin box made in one piece All bends $\frac{1}{2}$ " wide

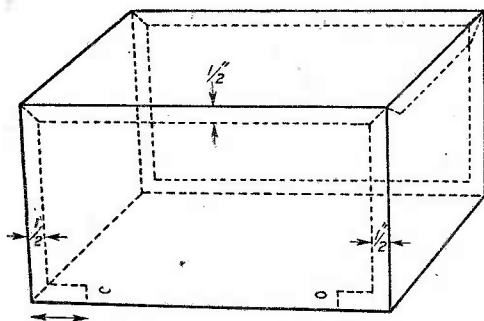


Fig. 4.—Details of the metal box for the set.

line-ups which work so efficiently at low cost and no one need hesitate in setting about converting these receivers for use as car radios, for I am confident their efforts will be rewarded with unqualified success.

The cost to me of this conversion was approximately 5s., i.e., 3s. for the coil, 1s. for a piece of Formica (off-cut) and 1s. for the small self-tapping screws. Fortunately I found the tin, aluminium, wire and sockets, etc., in my spares box, but it is quite possible buying every item required to do the job for approximately 15s. A good aerial costs about 35s.; this you would need in any case if you contemplated music in your car whether from converted portable

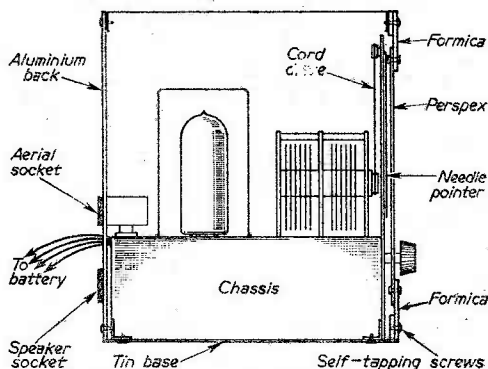


Fig. 6.—Details of the complete assembly.

or new car radio sources, but here again second-hand bargains are often procurable or a keen experimenter may like to make his own, or mount a simple form of running-board type of aerial (the latter, however, I do not recommend for the type of set in mind).

Practical Television

December Issue • Now on Sale • Price 1/3

THE amount of work involved in outside broadcasts is little appreciated by the average viewer, and in the December issue of our contemporary, **PRACTICAL TELEVISION**, a detailed article on this subject is given together with a map diagram showing how the Blackpool Lights relay was sent to London and the other BBC channels. The introduction of the rival network has led to considerable difficulty in some areas in eliminating breakthrough between the two stations, and an article on this subject is also included in the issue with particular reference to the Spencer-West Patterning Remover.

The fitting of a Turret Tuner is a most popular subject with many constructors and there is also an article on this subject, illustrated in a practical manner by describing the adaptation of one of our own receivers—the Lynx.

Other articles in this issue deal with Colour Television (No. 9 in the Series on a Beginner's Guide to Television), Servicing the RGD 2351T, the new Riverside Studios, and a new series of Data Sheets giving details of commercial receivers. The first deals with the Marconiphone Models VT68DA and series, and the H.M.V. 1840 and series.

NEW! THE PRACTICAL WAY

of learning **RADIO · TELEVISION · ELECTRONICS**
AMATEUR S.W. RADIO · MECHANICS · PHOTOGRAPHY · CARPENTRY · ETC.



DO IT YOURSELF!
IN YOUR OWN HOME — IN YOUR OWN TIME

An entirely new series of courses designed to teach Radio, Television and Electronics more quickly and thoroughly than any other method. Specially prepared sets of radio parts are supplied and with these we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio receivers, etc.

Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—these Practical Courses are ideal and may be yours at very moderate cost.

With these outfits, which you receive upon enrolment and which remain your property, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to designing, testing and servicing of Complete Radio and Television Receivers.

Photograph of E.M.I. factories at Hayes—our industrial background.

OTHER COURSES WITH PRACTICAL EQUIPMENT INCLUDE : RADIO (Elementary and Advanced) · TELEVISION MECHANICS · ELECTRICITY · CHEMISTRY · PHOTOGRAPHY · CARPENTRY.

Also Draftsmanship · Commercial Art · Amateur S.W. Radio · Languages · Simple Electrical Repairs in the Home · Painting and Decorating · Etc · Etc.

With these outfits, you are given instructions that teach you the basic principles in the subject concerned.

NEW TELEVISION COURSE including a complete set of equipment dealing with the design, construction and servicing of a high quality television receiver.


COURSES (with equipment) also available in many other Engineering subjects.

COURSES FROM 15/- PER MONTH



To E.M.I. INSTITUTES,
 Dept. 32, 43 Grove Park Road,
 London, W.4.

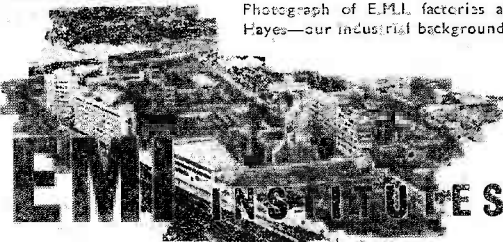NAME.....
 ADDRESS.....
 SUBJECT(S) OF INTEREST.....
 JAN. (We shall not worry you with personal visits) 1276




An Educational Organisation associated with the E.M.I. group of Companies including:
 "HIS MASTER'S VOICE", COLUMBIA, etc.

HOME RADIO OF MITCHAM

187, LONDON ROAD, MITCHAM, SURREY

MIT. 3282

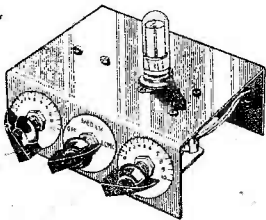Build the R.E.P. 1 valve battery set for an exciting Christmas gift. Complete kit of parts including valve 33/6. H.T. and L.T. battery 8/3, Head-phones 14/- pair. Full constructional details and price list price 9d. post paid.



TWO SPECIAL GIFT LINES

OLON 625 RADIO SOLDERING IRON
Ideal for all radio and T.V. work. Heats up in 2½ minutes. Detachable bit. Please state voltage. PRICE 22/6 post paid.

LONG-RANGE FOCUSING 3-COLOUR TORCH

A delight for any boy, boy scout, girl guide or motorist. Gives powerful white, red, or green beam at the touch of a button. Complete with two U2 batteries, 9/- post paid.

ORDER EARLY TO AVOID POSSIBLE DELAY IN POST DUE TO CHRISTMAS MAILS.

SPEAKER FRET MATERIAL


Attractive heavy gold/fawn as used by famous manufacturer. Any size cut to order at 2/- per sq. ft. Send S.A.E. for sample.

EXPLORE THE WORLD ON SHORT-WAVES WITH THE "PRACTICAL WIRELESS" BEGINNERS' SHORT-WAVE THREE

This fine little set will bring the world to your fire-side, all parts in stock and detailed price list sent on receipt of S.A.E.

THE "JASON" F.M. TUNER KIT

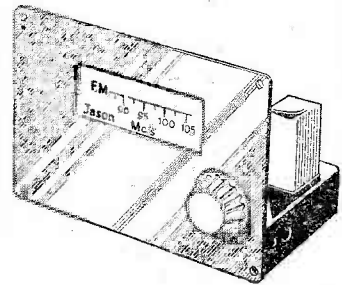The most successful Home Constructor design ever produced. Build yours today and enjoy the thrill of Hi-Fi crystal clear reception. All parts standard and in stock. Full constructional data including point-to-point and price list. PRICE 2/-.



COPPER WIRE

ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED, RESISTANCE WIRES.

1 oz., 2 oz. & 4 oz. REELS.

All gauges available.

B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets. EBONITE AND BAKELITE PANELS. TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES. ALL DIAMETERS.

Latest Radio Publications. SEND STAMP FOR LISTS

SPECIAL OFFER

G.E.O., B.T.H. & WESTINGHOUSE
**GERMANIUM
CRYSTAL DIODES**

1/- each. Postage 2½d.

Diagrams and three Crystal Set Circuits Free with each diode.

A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

CRYSTAL SET

INCORPORATING THE SILICON CRYSTAL VALVE

Adjustable Iron Cored Coil.

RECEPTION GUARANTEED

Polished wood cabinet, 15½" post 1/3 A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES

33 Bourns Gardens, London, E.4

Radio Ham Shack LIMITED

COLLARO TAPE TRANSCRIPTION. High Fidelity at low cost. 3 speeds, 3½, 7½ and 15 in. per sec. Twin track operation. £20, plus 5/- carriage.

Special Microphone for above. £25.0. **SCOTCH BOY MAGNETIC RECORDING TAPE.** 5in. spools: 600ft., 21/-; 900ft., 32/-; 7in. spools: 1,200ft., 35/-; 1,800ft., 54/-.

THE NEW UAS MONARCH 4-SPEED AUTOCHANGER. With High Fidelity crystal pickup with dual sapphire stylus, £9.15.0, plus 3/- carriage.

WHITELEY ELECTRICAL WR12 HIGH FIDELITY AMPLIFIER. With separate pre-amplifier Tone Control Unit. It has a low noise input circuit feeding the double triode phase splitter and a push pull output stage using a specially designed Whiteley Output Transformer. Overall 25 db negative feedback is taken over the main amplifier. £25, plus 5/- carriage.


We are also stockists of the W.B. High Fidelity Speakers and Cabinets. Send 6d. for our latest list of valves, components, tools, books, etc.

155, Swan Arcade, Bradford 1 1-Finger Pianists

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

C & S, 10 Duke St., Darlington, Co. Durham

TELETRON FERRITE ROD AERIALS

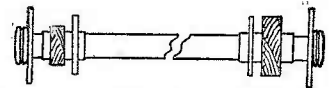

Wound on high permeability Ferroxcube rod. MW., 8/9; Dual-wave, 12/9.

TRANSISTOR COILS

315 kc/s, I.F.T.s and Osc. coils in cans (1 x ¾ in.), 6/6 each. MW. Transistor Ferrite Aerial (type FRM/2), 10/- each.

Stamp for complete list and circuits.

THE TELETRON CO., LTD.


266, Nightingale Road,
London, N.9
HOW 2827

News from the Trade

NEW PLESSEY PAPER CAPACITOR

A NEW type of paper dielectric capacitor which has a performance comparable with the more expensive metal-cased types is now being manufactured by The Plessey Company Limited.

It is anticipated that the new capacitor, called "Plesseal," will be widely used in domestic radio, television receiver circuits and industrial electronics equipment, and it has been specially designed for long service in conditions of extreme humidity and temperature. Operative temperature range is -30 deg. C. to $+85$ deg. C., and the component complies with tropical storage requirements R.C.S.11, Grade H2.

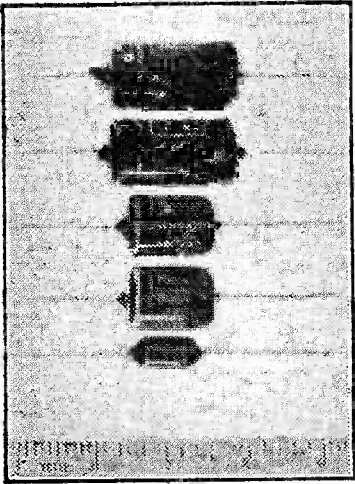

The New Plessey Paper Capacitors.

The range extends from $0.005 \mu\text{F}$ to $1.0 \mu\text{F}$ and they can be supplied in either standard or logarithmic ranges. Normal capacitance tolerance is ± 20 per cent., but tolerances of ± 10 per cent. or ± 5 per cent. are available at slightly higher cost. Voltages covered are 150, 250, 350, 500, 750 and 1,000 D.C. at 20 deg. C. and

for operation at temperatures over 70 deg. C. it is necessary to derate these by 25 per cent.

The component is wound with the outer foil extended to provide an electrostatic screen, and the tinned copper terminal lugs are inserted simultaneously to produce a non-inductive unit. Lugs are shaped and connected to the foils in a manner which allows the contact resistance to be reduced to a minimum. The terminal wire is spot-welded to the lug which is then folded around it and the complete assembly is soldered to provide a solid, electrical and mechanical joint which forms an excellent, moisture-resistant seal.

The finishing process, applied after impregnation, is such that each coat provides a key for, and is effectively bonded to, the next, thus producing a homogeneous covering which extends just past the soldered joint and forms a complete seal around the component. A flexible lacquer final seal completely envelops the capacitor and assists in completely excluding all moisture from the unit.

The Plessey Company Limited, Components Division, Kembrey Street, Swindon, Wilts.

EDISWAN TRANSISTORS

EDISWAN MAZDA have released in this country the first complete range of metal-clad transistors. The strongly welded metal to metal seal ensures that

they are completely impervious to moisture penetration even with high humidity.


The Edison Swan Electric Co., Ltd., 155, Charing Cross Road, London, W.C.2.

NEW MULLARD PULSE MODULATOR VALVE

THE QQV5-P10 is a new Mullard double tetrode valve for use in the pulse modulators of radar and radio equipment. It is capable of delivering pulses of 5 kV, 10 amperes when both sections are connected in parallel. The valve is suitable for pulse durations up to 3 micro seconds and duty factors of 0.001. The anode dissipation is 15 watts maximum and under typical conditions the total power input to the stage is 85 watts.

NEW PLUG-IN END-VIEWING PHOTOCELLS

IN some applications the use of end-viewing photocells with wire-in connections is inconvenient or undesirable. Mullard Ltd. have therefore introduced plug-in versions of two of their wire-in photocells. Both have B3A ("pee-wee") bases. The 53CG is a gas filled photocell equivalent to wire-in type 58CG, and the 53CV is a vacuum type equivalent to wire-in type 58CV. Both are sensitive to incandescent and near infra-red light.—Mullard Ltd., Century House, Shaftesbury Avenue, London, W.C.2.

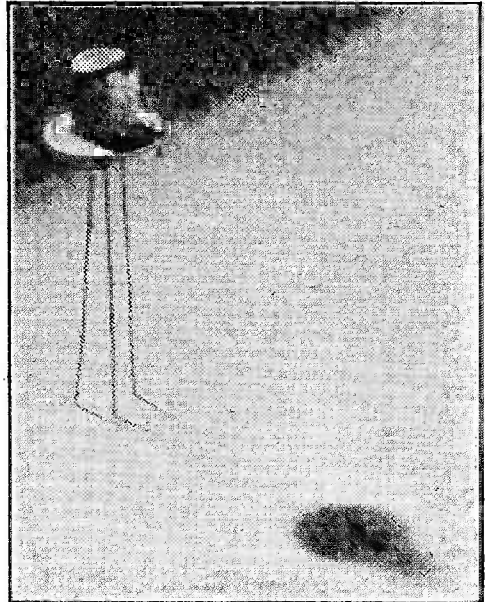


The Edison Swan Metal-clad Transistor.

OSMOR TRANSFER INDICATORS

OSMOR are now offering stick-on transfer indicators for the Light, Home and Third programmes. This enables an ordinary dial to be calibrated for F.M. Also, these indicators are very useful for small battery portables for which a small length of Perspex may be used as a dial. The retail price is 1s. 6d. per set.—Osmor Radio Products, Ltd., 418, Brighton Road, South Croydon.

Programme Pointers

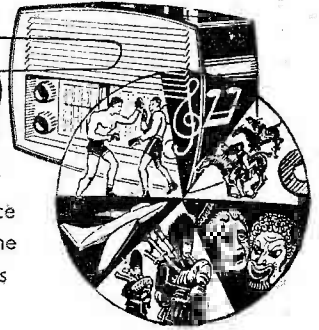

Plays

THE Burning of the Maid," a reconstruction of the immortal story of Joan of Arc by Stanley Baron to celebrate the 500th anniversary of her rehabilitation, was an excellently compiled programme, very well produced by Rayner Heppenstall and acted beyond reproach by a lengthy cast of some of radio's most notable names.

As it was mainly concerned with the details of Joan's life and work, all of which Shaw handles so brilliantly in "St. Joan," it shouldn't have been put on only two days after G.B.S.'s masterpiece. Biographically one was made to feel one was listening to the same thing all over again. But it was a fine slice of radio which I enjoyed thoroughly.

Thank heaven there was a total absence of "music," and if ever an argument could be deduced to defend the views on this subject I have so often expressed herein, it was here! "Not a sound was heard, not a funeral note." And not a note was missed! Not even Joan's voices were simulated. The whole story passed serenely by—uninterrupted, unspoiled and unrepentant. Get thee behind me thou infernal noises, whose unwelcome interpolations, preludes and postludes only inflame the nerves and destroy the thread of the piece.

That great play, "Journey's End," was given a very good performance in the first of a Sherriff Festival. John Westbrook, as Stanhope, brought out his "dutch" courage at the expense of his native brand rather a little too much, and a few of his more testy passages seemed a little "recited." Brewster Mason's Osborne was excellent in every way, and made us feel that, as soldiers, we could place just as much trust and confidence in his type of leadership as in Stanhope's. David Enders as Raleigh was also very good. I liked all the others: Ronald Sidney as Mason, Eric Anderson as the Colonel, Richard Gray as the Sgt.-Major, James Thomason as Trotter, and Alan Edwards as Hibbert. Frank Partington was Hardy and Peter Neil a German prisoner.

A new ending was given to the play, greatly inferior to the wonderful one in stage, live productions. Instead of the dugout getting a direct hit—the end of everything for all the protagonists—Stanhope was made to say to the dying Raleigh, "Don't worry: I'm getting you sent down to the field dressing station," or words to that effect. Everybody apparently overlooked the fact that the Germans, having completely broken through and overrun the whole show, Stanhope himself would have been on his way with everyone else to a "cage," and that, if anyone dealt with Raleigh at all, it would not have been Stanhope!

It really didn't matter, of course. The play's great message of the crime, blunders and uselessness of war came over just the same.

Interviews

Gilbert Harding's new series, "On the Spot," is vastly superior to his last one based on telephone interviews. This time he discusses a subject each week

Our Critic, Maurice
Reeve, Reviews Some
Recent Programmes

with his reporters who, in their turn, have been out in suitable parts of the country fact finding and laying a basis for the programme. I last heard "Farmers and the Harvest," with Robert Reid and Edward Ward, and thought it very interesting. I hope it works up into a successful item.

Quiz and Questions

Quiz and question programmes are always among the most popular with all ages. Whilst the young like to test out their prowess and puff their chests out if successful; their seniors, I doubt not, derive their satisfactions from having escaped from the ordeal of being tested on the Ming Dynasty in China or the XVIIIth in Egypt.

The latest in the former group and wholly topical, is styled "The Floor is Yours," in which a guest is invited to answer listeners' questions put to him by a panel in the studio under a chairman. Telephonic communication was established with the questioner if further elucidation should be required. The first number was based on "Higher Wages For Ever?" The guest was Sir Thomas Williamson, C.B.E., President of the T.U.C.; the panel, Honor Balfour, Stephen Parkinson and George Scott, and the chairman Robert Reid.

Questioners had their queries recorded in their own voices at three guineas per question—why they were not paid three guineas instead of having to stump up, I cannot think.


Variety

Ted Ray's voice can, without any aid from the *Radio Times*, be recognised through open window or door as easily as any other now before the listening public. His particularly forceful brand of humour is entirely his own, but his "radionic" marital perplexities are everyone's. His script writers and supporting artists invariably serve him well. In short, a half-hour spent in his genially bamboozling company is bracing, rewarding and thought provoking. (One can seldom come away from his turns without having gathered some new ruse for disguising our "having been late at the office, dear.")

In "The Spice of Life"—each of 45 minutes' duration—Mr. Ray is more of a master of ceremonies than a central figure: consequently there is rather less of him and more of a lengthy supporting cast which features June Whitfield, Deryck Guyler, Gene Crowley, Therese Burton and many others. There is much fun, music, quizzes, many questions, discoveries and what have you with, the ubiquitous Mr. Ray always there or thereabouts.

COMPLETE KITS of PARTS for the "HI-FI" ENTHUSIAST


The MULLARD "5-10" MAIN AMPLIFIER

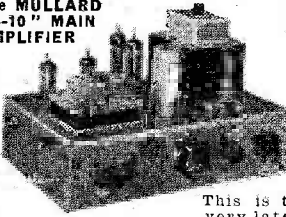

This is the very latest design and needs no recommendation from us. Our Kit is complete to Mullard's specification, including the latest GILSON ULTRA LINEAR OUTPUT TRANSFORMER and the entire MULLARD Valve line up. ALL SPECIFIED COMPONENTS are supplied. **PRICE OF COMPLETE KIT OF PARTS £11.11.0.** (Plus 5/- carr. & ins.)

The full SPECIFICATION and PRACTICAL BUILDING INSTRUCTIONS for these Units are available for 1/6 each. SPECIAL PRICE REDUCTION. We supply the two complete Kits—Mullard 5-10 and "Fidelity" Preamplifier—for £16.16.0. We also supply both fully assembled and ready for use for £19.19.0.

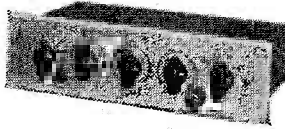STERN'S "Fidelity" PRE-AMPLIFIER-TONE CONTROL UNIT
"A design for the music lover"



Briefly it has inputs for all types of MICROPHONES, HIGH and LOW GAIN PICK UPS and a RADIO TUNING UNIT. It incorporates: (a) GRAM EQUALISING CONTROL. (b) STEEPCUT FILTER. (c) Continuously variable BASS and TREBLE CONTROL and a variable OUTPUT CONTROL which enables its use with any type of Amplifier. **PRICE OF COMPLETE KIT OF PARTS (Plus 5/- carr. and ins.) WE ALSO OFFER IT ASSEMBLED, READY FOR USE, £8.0.0.**

STERN'S "HIGH QUALITY" 8-10 WATT AMPLIFIER



Has power supply for Radio Tuning Unit.

PRICE OF COMPLETE KIT OF PARTS (Plus 5/- carr. & ins.) **£7.10.0.**

SUPPLIED ASSEMBLED AND READY FOR USE. **£9.10.0.**

Proved one of the most popular models yet offered to the HOME CONSTRUCTOR. Provides excellent reproduction 'up to 8 watts, employing 6V6's in push-pull, incorporating negative feedback. Provides for use of both 3 and 15 ohm speakers.

MODERNISE YOUR OLD RADIOGRAM


- ★ THE LATEST A.M./F.M. RADIOGRAM CHASSIS.
- ★ A NEW 4-SPEED AUTOCHANGER.

The NEW ARMSTRONG PB.409 A.M./F.M. Radiogram Chassis

"A chassis for those who want the highest quality." • A 9 valve line up employing the latest MULLARD preferred-type valves. • Provides complete coverage of the V.H.F./F.M. Transmissions plus the Short, Medium and Long Wavebands. • Has Push-Pull Output, with Negative Feedback, for 6 watts peak Output. • Quick Action "Piano Key" Selectors and separate Bass and Treble Controls. • Has "Magic Eye" Tuning Indicator. • Dimensions 13in. x 9 1/2in. x 8in. high. Dial size 11 1/2in. x 5 1/2in.

PRICE £29.8.0. TERMS: Credit £7.7.0 and 9 monthly payments of £2.14.0. H.P. £17.14.0 and 12 monthly payments of £1.7.8.

SEND S.A.E. FOR ILLUSTRATED LEAFLET

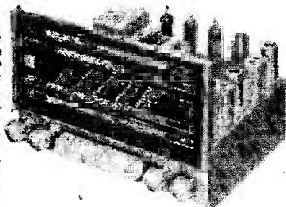


STERN'S NEW "Fidelity" COMBINED AM/FM

Radio gram Chassis. A genuinely hand-made chassis providing really high quality on both Radio and Gram.

PRICE **£26.15.0.**

(Plus 7/6 carr. & ins.) TERMS: Credit Deposit £8.14.0 and 9 monthly payments of £2.9.0. H.P. Deposit £13.7.6. and 12 monthly payments of £1.4.10.

BRIEFLY IT HAS: An 8 valve line up incorporating the latest MULLARD preferred-type valves. • Provides complete coverage of the V.H.F./F.M. waveband plus the SHORT, MEDIUM and LONG waves. • Has EL84's in Push-Pull with negative feedback of 6 watts output. • Employs "Piano Key" Selector Switches and a Variable Tone Control. • Contains Gram Input socket for both Crystal and Magnetic Pick-ups. • Provides for use of either 3 or 15 ohm Speakers. • Has "Magic Eye" Tuning Indicator. • Dimensions 13in. x 9 1/2in. x 8in. high. Dial size 11 1/2in. x 5 1/2in. SEND S.A.E. FOR ILLUSTRATED LEAFLET.

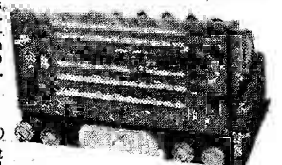

RECORD PLAYERS THE VERY LATEST MODELS ARE OFFERED AT GREATLY REDUCED PRICES

• TRANSCRIPTION UNITS. • 3 and 4 SPEED AUTOCHANGERS. • AUTOCHANGERS with MANUAL CONTROL POSITION. Send S.A.E. for ILLUSTRATED and DESCRIPTIVE LEAFLET.

STERN'S "F.M." TUNING UNIT

A 5-valve Tuner incorporating the latest Mullard Permeability Tuning Heart and a "Magic Eye" Tuning Indicator.

PRICE ASSEMBLED & READY FOR USE: £14.10.0.

(Plus 7/6 carriage and Insurance). TERMS: (a) Hire Purchase: Deposit £7.5.0 and 9 monthly payments of 18.4. (b) Credit: Deposit £3.12.6 and 9 monthly payments of £1.6.7.

THE COMBINED AM/FM TUNER is precisely similar in appearance to the above and incorporates 7 valves. It provides complete coverage of F.M. Transmissions and MEDIUM WAVEBAND giving a good selection of foreign stations.

PRICE £18.18.0 (Plus 7/6 carr. & ins.) TERMS: (a) Hire Purchase: Deposit £9.9.0 and 10 monthly payments of £1.1.0. (b) Credit: Deposit £4.15.0 and 9 monthly payments of £1.14.7.



AN EXCEPTIONAL


"CASH ONLY" OFFER

£7.19.6.

(Plus 5/- carr. & ins.)

THE NEW 4-SPEED B.S.R. MONARCH

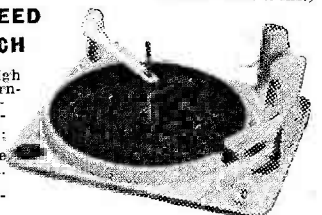• Complete with High Fidelity Crystal "Turn-over" Head which incorporates separate stylus for L.P. and 78 r.p.m. records. • A "MIXER" Unit that will autochange on 7in., 10in. and 12in. records of same speed. • Incorporates the Manual Control position.




Expressly developed for very high quality reproduction of Gram. Records and particularly suitable for high quality reproductions of the F.M. transmissions. Two models are available:

(a) The "COMPACT 5-2" A Two-stage high sensitivity Amplifier having SEPARATE BASS and TREBLE CONTROLS and designed to give up to approx. 5 watts with very pleasing quality. **PRICE £5.15.0.** (Plus 5/- carr. & ins.)

(b) The "COMPACT 5-3" A Three-stage version of the "5-2" model but in this case having an additional stage and incorporating Negative Feedback. **PRICE £6.16.0.** (Plus 5/- carr. & ins.)

STERN'S "COMPACT 5" AMPLIFIERS

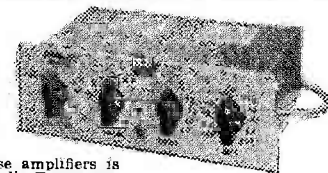

CALLERS ONLY


We have in stock various Kits of Parts including F.M. Tuners, A.M./F.M. Tuners, Midget Battery Portable, Mains Units, etc., etc.

A separate 'POWER' SUPPLY UNIT to operate with these amplifiers is available for £2.10.0. Has additional supply available for Radio Tuner, etc.

STERN RADIO LTD. 109 & 115 FLEET STREET, LONDON, E.C.4.

Telephone: FLEET 5812,3,4

I DID IT MYSELF!

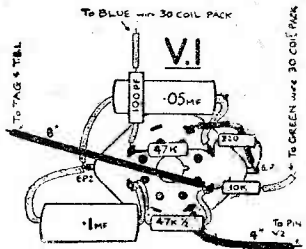

YOU will say—it is so easy.

GET THE RODING HOME CONSTRUCTOR'S HANDBOOK

This very small reproduction of a sub-assembly from one of our series of unique LIFE-SIZE, "EASY-AS-A.B.C." CONSTRUCTION SHEETS* illustrates how really simple radio assembly can be for the Home Constructor! If you have average ability and could follow this simple layout then you could tackle any, or all, of our LARGE RANGE of GUARANTEED OUTFITS knowing that with the help of our pre-aligned units failure is virtually impossible!! No previous knowledge necessary.

The latest issue of our Handbook is beautifully printed on glossy art paper with a full colour cover! Packed with technical data, set building and servicing hints, facts and formulae, resistance colour code, soldering hints, etc., together with descriptions, full parts lists and circuits of at least 22 modern receivers, tape recorders, feeder units, etc., etc. (for list see previous ads.) Send 2/6 (plus 4d. post).

★ AND our renowned "Easy-as-A.B.C." FULL SIZE Construction Sheets are available FREE with orders enabling even the beginner to get professional results first time! Coil packs and I.F.T.s pre-aligned. We supply ALL parts for ALL circuits. NEVER BEFORE HAS THERE BEEN A BOOK SO VALUABLE TO NOVICE AND EXPERT ALIKE! GET YOUR COPY—DON'T DELAY—SEND TODAY!

RODING LABORATORIES

(Dept. TC17) Bournemouth Airport, Christchurch, Hants

B ENSON'S BETTER BARGAINS

BC624A. (SCR522). New condition, with 10 valves, 100/150 mcs. Less tubes and relays, 45/- (rail 5/-). VALVES at 5/6: 6C4, 6AG5, 9001, 9002, 6AM6, EL91, VR90, VR102, 3A5, 12SK7M, 12A6, 807E, 12SL7, EF34, 6AG7, TT11, EC92, 6K7GT, 6SR7M, 6AC7, Pen46; at 8/-: EF50, RK36, EF83, VP23. Morse key, large, covered, 10/8; small 2/8. SWITCHES, knife, large, DPCO, 15/-; COMMAND RXE, 1.5-3.0 mcs. Brand new, with valves, 55/-; BC454, 3-6 mcs., 45/- (post 3/-). Condensers, var. spindled, ceramic, 15, 25 or 50 pfs., 1/3; 75 pfs., 1/8; butterfly 25 pfs., 1/8. SPEAKERS, new 8Ω, 1¼ round grey metal case, 2/6 (p.p. 3/-). RXS-121114 (TRP1987), with 3/EF91, 2/EL91, 5 gang tuner, new, 3/7s. less valves, 7/6. Circuit 1/-. MOTORS: Gram., 250 v. Induction, 78 r.p.m. with governor (Garrard), 30/- (post 2/9); SYNCH. 230 v. geared to 1 r.p.m. final, new, 2/8; Synch. 100 v. 3,000 r.p.m., 10VA., 10/-; SUPPRESSORS, radio interference, ex-A.M., 5/6 (post 2/-). BRAND NEW R.F. 26, 27/6 (postage 2/0); RF24, RF25, 10/8. DYNAMOTORS (post 3/-). 12 v. to 250 v. 65 mA. and 5.3 v. 2.5 A., 10/8. EDDY-SPOKE 12 v. to 120 v. 75 mA., cased, 15/-; 12 v. to 300 v. 200 mA., cased, 15/- (carr. 8/6). CLOCKWORK Contactors, 2 impulses per sec., 8/8. U.S.A. type, small, 9/8. R1822A, 100/150 mcs., 13 valves, used, good condition (damaged meters), 24 (carr. 10/-). THROAT MICS., U.S.A., new, 2/6. METAL RECTIFIERS: 240 v. 30 mA., 3/6; 600 v. 30 mA., 8/-; 500 v. 500 mA., 10/8; 1,000 v. 30 mA., 7/8. WAFER SWITCHES, 1 pole 11 way 2 Bank, 3/8; 4 P 2 W, 4 P 2 W, 1 P 6 W 5 B, 2/8. SPLITTERS, 15 A., G.E.C. D.P. switch, 4 fuses, new, 15/6. IF AMPLIFIER 178, 150 mcs., with valves, 15/6 (postage 2/6) each. RELAYS, 6 v. 2 break, 1/6. I.F.T.'S 3013 mcs., cased, new, 1/3. R1155 Coilpacks, new, 12/6. Used, 9/8. CHOKES, L.F. Ferranti, 10H, 120 mA. Screened, 7/8. 10H, 200 mA., 8/6; 5H, 200 mA., 5/6. HEADPHONES, L.R. super lightweight HS 30B, 17/6. List and enquiries, E.A.E. please! Terms: C.W.O. Postage extra. Immediate despatch. *Callers and post:* W. A. BERSON (PW), 136 Rathbone Road, Liverpool 15. NEP 6833. *Callers:* SUPERADIO (W'chapel) LTD., 116 Whitechapel, Liverpool 1. ROY 1130.

The completely automatic tape recorder . . .

. . . available NOW



TAPE RECORDER

only 55 gns.



On Credit Sale
Terms, yours for the
first of 9 payments of
£7. 2. 0., or on our Personal
Credit Plan—payments
over any period up to 18 months.

E. & G. MAIL ORDER SUPPLY CO. The Radio Centre.
33, Tottenham Court Road, London, W.1. MUSEUM 6667.

G2AK This Month's Bargains

Don't miss this one!

CRYSTAL HAND MICROPHONES



As illustrated, in silver hammer case with polished grille, handle and 4 feet screened lead. ONLY 21/-.

12 V. MINIATURE ROTARY TRANSFORMERS. Output 360 v. 30 mA. Cont. or 316 v. 70 mA. intermittent. Only 4 1/2in. x 2 1/2in. overall. Ideal for car radio, mobile TX, etc. Only 21/- Post 2/-.

HEADPHONES. H.R. Type 4,000 ohms, very sensitive. Only 12/6 pr. Post 1/6. C.L.R. type (low res.) 8/6. Post 1/6.

AMERICAN BREAST MIKES, swivel head, push to talk and lock-on switch. Excellent job. Only 12/6. Post 1/6.

BRITISH BREAST MIKES complete with pr. of H.R. 4,000 ohm phones in wooden carrying case. New W.D. stock, unrepeatable at 17/6. Post 2/-.

AERIAL WIRE. Copper, 7/25 stranded: 140ft., 10/-; 70ft. 5/-. Hard Drawn 14g.: 140ft., 17/-; 70ft., 8/6. P. & p. 2/-.

GLASS INSULATORS. 1/6 each. Small shell ditto. 4d. each or 4/- doz. plus postage.

CONDENSERS. 8uF 600 v. Trop. 750 v. normal condensers. NEW, ex W.D. stock, 5/6, p. & p. 1/6.

New TCC Type III. 8 mfd. 1,000 v. D.C. wk'g. (List over £3). OUR PRICE 10/6, p. & p. 1/9.

No C.O.D. on orders under £1.

PLEASE PRINT YOUR NAME AND ADDRESS

CHAS. H. YOUNG LTD.

Dept. 'P' 110, Dale End, Birmingham 4. (CEN 1635)

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents

Club Wanted

SIR,—Having been a regular reader for some time I have read with interest much of what has passed in "Open to Discussion," technical and otherwise.

I should like to take advantage of this widely read column by asking if there are any radio, etc., clubs in the Walthamstow district catering for beginners (I am 18½). If so, could I contact anyone by means of your journal or otherwise. — B. JENKINSON, 27, Byron Road, Walthamstow, E.17.

Contacts Wanted

SIR,—Having for a long time past been a regular reader of PRACTICAL WIRELESS, I now wish to make use of "Open to Discussion." I would like, through this medium, to get into touch with a fellow reader who has a Command Receiver Type BC454B, as I would like to know the modification this set will need to get it working.—G. E. SMITH, 6, Woodland Close, Trimdon Village, Co. Durham.

SIR,—I am twelve years old and very interested in radio, but I am only a novice and I would be pleased to contact someone about my own age who is interested in this subject.—R. YEATES, The Moorings, Martock, Somerset.

I.F. Strip 373

SIR,—Recently there has been advertised an I.F. Strip 373, of 9.72 Mc/s. They sounded so good at the price (7s. 6d.) that I decided to buy one. They are indeed a wonderful bargain, and from the circuit (included) it seems to me that very few alterations are necessary to make it into a F.M., I.F. and audio O/P strip.

There are a number of ways of using it, depending on the location of the receiving station, but the best I should think is exactly as it was designed, with the necessary alterations for a discriminator.

An article about this Strip, I should think, would be of interest to many of your readers, and I shall certainly be on the look-out.—W. S. HANWAY (Cheltenham).

[Has any reader any helpful information on this? —EDITOR.]

F.M. Car Radio

SIR,—Having built a F.M. feeder unit with moderate success, the performance of which is up to my expectations and pleasing, I have been thinking of constructing a complete F.M. receiver

for mobile operation, that is for use in a car. As far as I can see there should be no drawback to this technically, but I am not quite clear as to what would constitute a suitable aerial, bearing in mind the horizontal polarization of the signal, also the directional properties of the dipole I am now using.

I find that if the aerial is not directed there is a great loss of the frequencies received and distortion on speech and music.

Therefore, with a car which is constantly changing direction, I think a really efficient aerial system must be thought up.

I would be pleased to have other readers' comments on the project.

I would also like to add my comment on a paragraph on "Car Radio," by "Thermion" in the

August issue.

If the set mentioned is an eight-valve superhet it must obviously be one of the well-known push-pull output jobs, possibly with twin speakers, by one of the best manufacturers, and from my experience as an auto-electrician I have found these sets very good.

If the quality is as bad as he said, it is high time he did something about it!!! (and with fewer valves!). —J. C. REVELL (S.W.11).

Licence Fees

SIR,—Is there any way open to us to protest against the monstrous idea that our licence fees are merely taxation and that the BBC is lucky to get any of the money so raised?

More and more of this money has been filched on the grounds that this form of entertainment must bear its share—a feeble excuse which utterly ignores the time given to Government advertising and money diverted to overseas propaganda—and now we have the complete "Nasserisation" of all the licence money.

It is obvious to any listener that the BBC funds drying up—otherwise why the "vain repetitions" of programmes of more generous days?

This looks like an even better version of the political confidence trick, if no protest at all materialises.—WILLIAM B. WEST (Deal).

[Motorists are in the same position with the Road Fund.—ED.]

Wattage Rating

SIR,—When I buy a condenser the safe voltage is marked on it; but with a resistor I am given a "wattage" and have to do a division sum and extract a square root before I can find out the same information. Should the reason for this be obvious to me or might it be "Open to Discussion"? —R. L. WYNNE (Wallasey).

Training Courses

SIR,—The Doncaster Technical College offers part-time day courses (one day per week) for Radio and TV apprentices up to the Final R.T.E.B. TV Servicing Certificate. In addition a Practical Radio class meets on Monday evenings, 7-9 p.m. This is run for those who do not seek professional qualifications, but are interested in learning more about radio receivers and their operation from a hobby point of view. Supporting classes in electrical theory and mathematics are available if required. Further information is available from the Head of the Electrical Engineering Department at the College.—S. EDWARDS (Head of Department).

"Mouse"

SIR,—I fully support Mr. Buchanan, whose letter was published in PRACTICAL WIRELESS, October issue. The artificial satellite "Mouse" is not bound up with military objectives, and there is no reason why amateurs should not be able to do useful work in connection with it. With a project of this sort the more information gained the better, and the experience obtained in designing and constructing equipment to receive signals from the satellite would in itself be worth the trouble taken.—M. J. S. QUIGLEY (Liverpool, 23).

A Moral?

SIR,—As an old reader I know that PRACTICAL WIRELESS does not encourage letters of a frivolous nature, but the following has a moral which I am sure will be appreciated by the fraternity.

I was listening during last week on the 80-metre band, and came across a very learned discourse on the training of the well-known Alsatian breed of dog, a subject on which the operator was evidently well qualified to speak.

It was very appropriate, therefore, when a morse operator chipped in with a well merited reference to "Shaggy dog" stories, and I should like to send both these gentlemen my compliments on their excellent readable signals, with a sly emphasis on the moral.—B. G. ASHMAN (Stevenage).

Stereophonic Recording

SIR,—I am wondering if there are amongst your readers any other tape recording enthusiasts who have become a little more ambitious and have turned to stereophonic recording.

I have personally experimented in this field for several years. My first attempt was far too big, but after altering circuits, layout, etc., and rebuilding completely four times, I arrived at its present form, only 17½ in. by 15½ in. by 7½ in. This includes two built-in speakers, but it will be appreciated that external speakers, conveniently spaced, produce a far better effect. Two speaker units, fitting together for portability, therefore complete the equipment.

I originally commenced by converting a Truvox tape deck, but have since completely rebuilt it. All

switching for motors and amplifiers is synchronised in a press-button unit. This caters for recording from microphones, gram or wireless and playback. The amplifiers may also be used for playing records, bass being amplified by one and treble by the other. (This arrangement is incorporated in certain radio-grams on the market to-day wrongly advertised as 3D sound. Though quite pleasing to the ear, this, of course, is not true 3D.) A meter is incorporated for signal level in recording and balancing of the two amplifiers.

At the recent radio show I asked one exhibitor if it was possible to record on his stereophonic unit, a very large and elegant piece of furniture, and he informed me it was not a practical proposition for anyone to make stereophonic recordings. The pre-recorded tapes which have been on the market for about twelve months are excellent and one was being played on this same unit. I could not help but try and compare this with my own efforts. My volume was not as great, but it is more than sufficient for the average home, quality was near enough equal. Added to this, mine is portable and it records, too.—J. S. GILBERT (Knowle).

The Novices' Licence

SIR,—Being a regular reader of PRACTICAL WIRELESS I have followed with special interest views concerning a granting "by the G.P.O." of a licence for the short-wave listener who wishes to transmit by the ownership of a novice licence. The views of some readers condemn this by saying that the amateur bands are overcrowded, and morse, which many like myself would wish to have withdrawn, although necessary when 150 watts or so is used.

The use of the 27 Mc/s band for model control could be used, as I am sure the revenue collected by such a licence would far exceed that collected for model control licences. The power could be limited to five watts, and the use of frequency measurement essential. I sincerely hope that these views and including those of Mr. H. F. Barker, November issue, will have attention by the R.S.G.B. or G.P.O.—F. WALKER (Cambridge).

POWER SUPPLIES

(Continued from page 754)

assist in smoothing out this ripple, another condenser, C2, is connected, the value of which usually lies between 8μF to 32μF, dependent upon the amount of ripple and hum that is to be filtered.

It may well be that the constructor or experimenter prefers to construct or adopt a double type of filter as shown in Fig. 4. This naturally depends upon the individual, the ratings of the extra components being more or less the same as those used in the single filter.

The inductance of the choke can be estimated at being between 10 and 20 henries, although one can use those of higher inductance so long as the current rating is correct. Such chokes are, however, plentiful upon the surplus market.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Neveles, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

14v. midget.	1R5, 1S5, 1T4, 1U5, 3S4, DAF91, DF91, DK91, DL92, DL94	any 4.19	27/6
1A7GT12/6	6V6GT 7/6	DK93 8/6	BY51 10/6
1C5CT11/1	6X4 7/6	DL33 9/6	BY38 11/6
1H5GT	6X5GT 6/9	DL35 11/6	EZ49 8/6
1N5GT	11/7	8T 8/6	DL96 8/6
	7C5 8/6	EAB80	EZ80 8/6
	11/7	7C6 8/6	RW4500
1R5	8/6	7E7 8/6	EAC91 9/6
7S5	7/6	7S7 8/6	EA421 9/6
1T4	7/3	7Y4 8/6	EB91 6/9
3A5	6/6	10C2 10/6	EBC33 7/6
3Q5GT	9/6	10F9 9/6	EBC41 10/6
3S4	7/6	10P14 13/6	EBF80 9/6
3V4	8/6	12AH8 10/6	ECC40 11/6
5U4G	8/6	12AT7 8/6	ECC81 9/6
5Y3GT	7/6	12AU7 7/6	ECC93 6/6
5Z4G	9/6	12J7GT	ECC91 6/6
6AK5 5/6	10/6	ECCF8012/6	PEN46 6/6
6AL5 5/9	12K7GT	ECCF8213/6	PL81 11/9
6AM36 7/6	8/6	ECC8310/3	PL82 9/6
6AQ5 7/6	12K8GT	ECC842 12/3	PL83 11/9
6AT8 8/6	14/8	10/1	PY80 11/9
6BA6 7/6	12Q7GT	ECC81 8/6	PY82 9/6
6BE6 7/6	8/6	ECC8L10/0	PY82 7/8
6BW6 7/6	14S7 14/6	EF37A	PZ30 18/6
6C93 10/6	25L0GT	9/6	U250 12/6
6E1 13/6	9/6	EF39 9/6	U50 7/6
6F6G 6/6	25Z4G 9/6	EF40 12/6	U78 7/6
6F13 13/6	35L0GT 9/6	EF41 9/6	UAF42
6F15 13/6	35Z4GT 8/6	EF42 12/6	10/6
6J8 6/6	50L6GT 8/6	EF50 7/6	UBC41 8/6
6J7C 7/6	B36 15/6	EF80 9/6	UBF8011/6
6K73 6/6	CL33 14/6	EF85 8/6	UCH42 10/6
6K7GT 6/6	CY1 11/9	EF86 12/6	10/3
6K8G 7/9	DAC3211/1	EF91 7/6	UF41 9/6
6K8GT 9/6	DAF96 8/6	EF92 6/6	UL41 10/6
6S7GT 9/6	DCC90 6/6	EL32 6/6	UY21 14/6
6SN7GT	DF33 11/6	EL33 14/6	UY41 8/6
6U4GT	7/9	DK32 8/6	EF41 10/6
		DH77 14/6	X78 12/6
		EL36 12/6	EL84 10/6
6V6G 7/6	DK32 9/6	EM34 10/6	Z77 7/6

Postage 6d. per valve extra.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

LYONS RADIO LTD.

Dept. M.P., 3, GOLDHAWK ROAD, SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPherds Bush 1728.

CABINET SPEAKERS.—10 in. P.M. moving coil speaker housed in wooden cabinets 17 1/2 in. sq. x 6 in. deep, with carrying handle. Slightly soft condition. PRICE ONLY 19/6, carriage 4/6.

WAVEMETERS TYPE W-1230.—Frequency range 155 to 220 Mc/s. Operate from 200/250 v. A.C. mains. Beautifully made and fitted in copper lined wooden instrument cases. Overall size 18 x 11 x 10 in. Complete with valves and test prod. PRICE ONLY £37.6, carriage 7/6.

MICROPHONE/HEADPHONE SETS.—Made by T.M.C., type AP12500, microphone hangs on chest or is suitably based for wall or desk mounting. Double headphones are rubber cushioned with headband. On/off switch to mike. Fitted with long connecting cord. Very strongly made. Ideal for two-way communication. Just link up together with flex as required. Sound powered. Batteries not required. PRICE per Set 19/6, post 1/9, or per pair 37/6, post 2/6.

AMPLIFIER UNITS TYPE A-1368.—Two-stage audio amplifiers which can be used without modification as a gramophone amplifier, as a crystal receiver amplifier, mike pre-amp. and for intercom. purposes, etc. Valves fitted are one each VR21 and VR35. Operate from 2 v. L.T. 90 or 120 v. H.T. and 9 v. G.B. In neat metal cases 7 x 5 x 4 in. New condition with connection details provided. A REAL SNIP AT ONLY 12/6, post 2/6.

MICROPHONE FLOOR STANDS.—Strongly made ex-A.M. sectional, extend to nearly 5 ft., and can be closed down to approx. 21 in. Plain finish. PRICE ONLY 19/6, post 2/6.

MILLIAMETERS.—2 1/2 in. sq. bakelite cased, moving coil type. PRICE 7/6, post 9d.



MANCHESTER'S LARGEST STOCKISTS OF RADIO AND T.V. ACCESSORIES, VALVES AND COMPONENTS

"BY RETURN" SERVICE

POWER UNITS.—H.R.O. 115 v. or 230 v. input. 6.5 v. 3 amp. A.C. 1.225 v. 75 mA. D.C. Crackle metal case 7 in., 7 in., 6 in. Suit HRO. 1155, any standard Receiver. 63/- carr. paid.

TEST SET 102.—250 v. 50 c. A.C. emits 25-50 ops. In metal carry-case, 11 in. x 9 in. x 10 in. Leather handle. Excel. comp. value: Trans. 300 v. 60 mA. 6 v. 2 a., 12 v. 1 a., 1 each 15, RK34 Met. Rect., Plugs, skts. Ind. lamp. 29/6 (carr. 2/-).

RF25.—New. In carton: 40-50 mc/s. Switch tuned. All valves, 10/6 (carr. 2/-).

NIFE ACCUMULATORS.—3 in. x 2 1/2 in. x 1 in. 1.5 v. 57 AH. for models, portables, etc. Each, 4/9, post 9d. Lots of 1 doz., 54/- carr. paid.

Typical VALVES

from our stock of thousands.

ALL NEW

954. 1 6; 6K7G. 2/9; EF50. 3/6; ARP12. 4/6; Pen 25. 4/6; 6SL7 6/6 (all post free). Set of five: 6K3, 6K7, 6Q7, 5Z4, 6V6, 35/- set. Set of four Battery valves: 1R5, 1T4, 1S5, 3S4 (or 1S4 or 3V4), 27/6 set. All post paid.

RECORD PLAYERS.—Many models in stock at advantageous prices: e.g. E.M.I. 331 Table Player, complete, ready to plug in to Radio, 63/-, carr. 2/6.

COLLARO RC54.—3 Spd. Mixer auto-ch. 'O' Pick-up, 200/50 A.C., £77.0. Carr. etc. 5/-. BOTH LIMITED QUANTITY.

CRYSTAL (Germanium) DIODES, 1/- each.

CRYSTAL RECEIVERS.—Dual wave comp. set. EVERYTHING incl. phones and chassis, instructions, NO cabinet. 29/-, Post 2/-.

COMM. TRANSmitters.—2-1-3 Mc/s. Pair 1825s. 1 ea. 1825 (magic eye). 2.500 Kc/s Oct. base Xtal. 3 var. conds., 220 pps. ea., Relays, Flex, Drive, etc. Brand New, Boxed, 35/-, Post 2/-.

CO-AX CABLE.—75/80 ohms, 6d. yard.

TRANSFORMERS.—All types mains, output, step-down, etc., e.g. Filament transformer 6.3 v. 2 amp., 7/-, P. & Post 9d.

METERS.—Large range available: e.g. 0-200 MA. 2 1/2 in. R.M.C. ... 7/6
0-1 amp. 2 1/2 in. R.M.C. ... 12/6
Post on each 9d. New Sealed Cartons. TEST METERS ALSO IN STOCK.

E.M.I. PICKUPS.—Cream, Magnetic. Uses Col. 99 needles, 16/6. Post 2/6. Matching transformers. 5/-, Post 1/-.

BATTERY CHARGERS.—Brand new, 12 mchs. guarantee, with meter, fuse, lead and clips, 2, 6, 12 v. 1 amp., 45/-, Carr. 2/-. Higher ampages available. All goods supplied by us whether Ex-Govt. or otherwise are fully guaranteed—replaced or cash refunded if received back as supplied within 7 days. Cash with Order only. No C.O.D. No lists at present but all enquiries promptly dealt with.

Callers very welcome.

Open 9 a.m. to 6 p.m. Mon. to Saturday. OUR ONLY ADDRESS.

(Dept. PW)

53, SHUDEHILL, MANCHESTER, 4

(BLAckfriars 4073)

TRADE ENQUIRIES INVITED.

FIRST-CLASS RADIO COURSES...

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M. Brit. I.R.E., City and Guilds: Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I. Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148, HOLBORN, LONDON, E.C.I.

WHY WASTE TIME

Give that set its best chance FIT QUALITY COMPONENTS

Catalogue 1/-

Parts for the following:	Manual
Osram "912" Plus Amplifier	4/-
Mullard 10-watt Amplifier	3/6
The Coventry	
2-watt Amplifier	} 1/-
4-watt Amplifier	
6-watt Quality Amplifier	
The Coventry A.M. Tuner Unit	1/-
Denco F.M. Tuner Unit	1/6

Complete Component Price Lists will be supplied with each Manual

COVENTRY RADIO

EST. 1925

109, DUNSTABLE ROAD, LUTON, BEDS.

Phone: Luton 2677

RADIO AND TELEVISION COMPONENTS

All parts in stock for: Viewmaster, Soundmaster, Teletek, etc. Easy Terms available. 21d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO., FINSTHRWAITE, NEWBY BRIDGE, ULVERSTON, LANCs.

RECEIVERS & COMPONENTS

1,000s & 1,000s of Service Sheets. Large purchase enables us to offer Service Sheets for sale this month at hire charges. Take advantage of this sensational offer. Send s.a.e. with enquiry now! 60-page Catalogue: Engineers! Experimenters! Labs! It's packed with new servicing components, exact replacements and fully guaranteed. Don't take chances—fit the best. Price 1/-, post free. Full Elstons Transmitter Range, incl. C.R.T. Isolation Trans., 2v, 4v, 6.3v, 10.8v, 13.3v; 20% boost optional; state heater voltage required; mains prim.: 18/-, p.p. 9d. Attention! Northern customers: "Labgear" Band III 3-element Aerial, 22/6, post free. "Labgear" Cross-over Units, 12/6, post free. "Air Spaced Co-axial Cables, 3d. per yd., p.p. 6d. 12 yds. Orders by return. M. Foy, 6, Wykebeck Gdns., Leeds, 9, Yorkshire.

THE HIWYMAN. A new super Portable Radio for the home constructor; all-day 4-valve superhet with Ferrite rod aerial, easy wiring diagrams and instructions, 1/6 (post 3d.). **RADIO EXPERIMENTAL PRODUCTS LTD.,** 33, Much Park St., Coventry.

COMPLETE COMPONENTS. Spark's Skipper 4, unused, 61, Pelham St., Ashton-under-Lyne.

TELEVISION.—9in. Models, £7/10-; 12in. Models, £15; all makes, working carriage paid. **TOMLINS,** 127, Brockley Rise, Forest Hill, S.E.23.

SEVERAL EARLY MODELS 9in. Television, complete and mostly working. £5/5/- each; carriage paid. **TOMLINS,** 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

GUARANTEED TELEVISION, 12in. Models, first-class picture, 5-channel, £25 each; carriage paid. **THE GRAMOPHONE SHOP,** 19-21, Brockley Rise, Forest Hill, S.E.23.

TELEVISION.—12in. Televisions, £13/10/- each; carr. paid. **TOMLINS,** 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

OSMOR would like you to have Free Practical Wiring Diagrams of the latest published circuits with full lists of components required. Send 7id. (stamps) to **OSMOR RADIO PRODUCTS LTD.,** 418, Brighton Rd., Sth. Croydon. (Croydon 5148.) (See advert., page 760.)

OSMOR NEWS. F.M. Switch-tuned Coilpack. Circuits and full information available shortly on request. **OSMOR RADIO PRODUCTS LTD.,** 418, Brighton Road, S. Croydon.

SERVICE MANUALS/SHEETS. Tel./Radio for hire, sale and wanted. S.A.E. enquiries. **W. J. GILBERT (P.W.),** 24, Frithville Gardens, London, W.12.

ENGRAVING.—Amateurs and trade surplus can be undertaken by getting in touch with **A. G. ENGRAVING,** now at 292, Earlsfield Rd., London, S.W.18. (BAT 9697.) (Engravers to well-known makers of Electronic Equipment used by the Aircraft Industry. A.W.R.E., etc.)

ALL TYPES of new radio valves wanted, small or large quantities; cash payments. **R. H. S. LTD. (W),** 155, Swan Arcade, Bradford, 1.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1 extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

ELECTROLYTICS, capacity, voltage, size, type of mounting, price post paid. 1,000 + 1,000, 6v, 1 x 3, clip. 3/3; 1,000 + 2,000, 6v, 1 x 3, clip. 1/0; 12v, 1 x 1 1/2, tag, 1/9; 500, 12v, 1 x 1 1/2, W/E, 2/5; 2,000, 12v, 1 x 1 1/2, W/E, 3/6; 10, 25v, 1 x 1 1/2, W/E, 1/3; 25, 25v, 1 x 1 1/2, W/E, 1/3; 50, 25v, 1 x 1 1/2, W/E, 1/9; 100, 25v, 1 x 1 1/2, W/E, 2/-; 1,000, 25v, 1 x 3, clip. 4/-; 3,000, 25v, 1 1/2 x 4 1/2; 5/6; 5,000, 25v, 1 1/2 x 4 1/2, clip. 6/6; 500, 50v, 1 x 3, clip. 3/9; 1,000, 50v, 1 1/2 x 4 1/2, clip. 6/6; 5, 150v, 1 x 1 1/2, W/E, 1/3; 8, 150v, 1 x 1 1/2, tag, 1/3; 40 + 40, 1 x 2, clip. 2/9; 200, 250v, 1 1/2 x 3, clip. 3/6; 100, 275-350v, 1 1/2 x 3, clip. 3/-; 16 + 16, 275v, 1 x 2, clip. 3/-; 32 + 32 + 32, 1 x 2, clip. 4/3; 16 + 8 + 4, 1 x 2 lug, 3/3; 200 + 250 + 250v, 2 x 4 1/2, clip. 8/6; 60 + 250, 275/350v, 1 1/2 x 4 1/2, clip. 6/3; 16 + 16 + 8, 350/425v, 1 1/2 x 2, lug, 4/3; 32 + 32 + 8, 350/425v, 1 1/2 x 3, clip. 5/-; 16 + 16, 350v, 1 x 2, clip. 3/6; 32 + 32, 350v, 1 1/2 x 2, clip. 4/-; 2, 350v, 1 x 2, tag, 1/-; 100, 350/425v, 1 1/2 x 3, clip. 4/-; 50 + 50, 350/425v, 1 1/2 x 3, clip. 4/6; 100 + 200, 350v, 1 1/2 x 4 1/2, clip. 7/6; 8, 450v, 1 x 2, clip. 1/3; 20 + 10, 450v, 1 x 3, clip. 4/-; 8 + 8, 500v, 1 1/2 x 2, clip. 4/-; all cans, some with sleeves, all voltages, tag strips where marked, new stock guaranteed. Television Chassis, cadmium plated steel, size 13 x 13 x 2 1/2in., complete with 13 valveholders (9-B9A Pax. 1-B9A Cer., 2-B7G Cer., 1-Int. Oct. Amph.), 20 various tag strips, cut away for metal rec. line trans., etc., 9/11 each, post paid; front and rear tube mounts to fit above chassis. 3/- pair, post paid. P.M. focus Magnets, wide angle, tetrode tube, fully adjustable 9/11, post paid. Scanning Coils, wide angle, with mounting lugs, 4/6, post paid. Vision I.F.s (2nd, 3rd and 4th), freq. 34 mc/s; slug tuned, size 13/16 x 13/16 x 2 1/2in. can. set of 3, 5/6, post paid. T.V. Rectifiers, H.W., 250v, 250mA, 2 1/2in. fins x 4in. long, 12/6, post paid. Mains trans., 250-0-250v, 120mA, 6.3v, 2.5A, 6.3v, 0.6A, Pri. 0-110-125-150-205-225-245v, 17/-, post paid. 100µ W/W Pots, 3v, 1in. spindle, 2/6, 8 min, 600/750v, Paper Conds., 4 x 2in. x 4 1/2, 6/6. **RADIO CLEARANCE LIMITED,** 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

MIDDLESBROUGH. Largest stocks on N.-East coast, Radio, TV components, FM Kits, Gram. Cabinets, Tape Decks, Leak Amplifiers, Valves, etc. Callers only. **PALMERS,** 106, Newport Road. (Phone: 3095.)

SEND TO-DAY for our stock list of T.V. and Radio Bargains. C.R.T.s, Valves, Speakers and all Components. We are the cheapest people in the trade. All goods sold by us are guaranteed. **VIDEO ELECTRONICS (LONDON) LTD.,** Dept. P.W., 15/23, Bacon Street, London, E.1.

AMERICAN RADIO Plans and Devices. Now available. Hundreds of new and startling devices you can make. Only designs of this type available in UK. Receivers, walkie-talkies, amplifiers, recorders, magic eye alarms, etc. Full lists, data, illustrations. Free for stamp. Send to-day.—**A.F.S. (PW),** Sedgford, King's Lynn.

MAKING YOUR OWN? Telescopes, Enlargers, Projectors, or, in fact, anything using lenses. Then get our booklets "How to use Ex-Gov. Lenses & Prisms," price 2/6 ea. Comprehensive lists of optical, radio and scientific equipment free for s.a.e. **H. W. ENGLISH,** Rayleigh Rd., Hutton, Brentwood, Essex.

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE,** Bullingdon Rd., Oxford.

PANL, the air-drying black crackle paint, 3/6 per 1/8th pt. can. **G. A. MILLER,** 8, Kinton Park Cres., Kinton, Middx.

TAN IN 24 HOURS. Super-tonic Sunray Lamps, ultra-violet infra-red combined; automatic exposure; controlled emission; all mains; listed £7/10/-, our price 80/- S.A.E. brochure. Dept. 14, **SCIENTIFIC PRODUCTS,** Cleveleys, Lancs.

AMERICAN MAGAZINES. Year's subscription "Audio" 35/-. High Fidelity "50/-, Spec. copies 4/- & 5/- ea. Cat. free. **WILLEN LTD. (Dept. 40),** 9, Drapers Gdns., London, E.C.2.

WANTED

TRANSMITTER / RECEIVER STATIONS TR-1934, TR-1935, TR-1936, ARC-1, ARC-3, and Wireless Sets 62. **R. GILFILLAN & CO. LTD.,** 7, High Street, Worthing. (Tel.: 8719.)

VALVES

WANTED, Valves EY51, ECL60, KT61, 6U4GT, PL81, 3524, etc., etc., prompt cash. **WM. CARVIS LTD.,** 103, North Street, Leeds, 7.

ALL TYPES of Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.,** 38, Chalcut Road, N.W.1. (PR1RMO 9090.)

VALVES.—1R5 7/6, 1S5 7/-, 3A5 6/-, 6D6 6/-, 6Q7G 8/6, 6Q7 8/-, 6A7 10/6, 6C6 6/-, 6N7 6/6, 6SK7 5/6, 6SA7 7/6, 6C5 5/6. Enquiries for other types welcomed. **MOSLEY,** 107, Prescott St., Liverpool, 7.

EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B., and other Professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to **E.M.I. INSTITUTES,** Dept. PW28, London, W.4.

LEARN IT as you do it—we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to **E.M.I. INSTITUTES,** Dept. PW47, London, W.4.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE,** Colwyn Bay.

A.M.I.Meoh.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams. and courses in all branches of engineering, building, etc.: write for 144-page handbook, free. B.I.E.T. (Dept. 242B), 29, Wright's Lane, London, W.8.

MERCHANT NAVY Wireless School, Overseas House, Brooks' Bar, M/cr 16.

WIRELESS.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **BST, LTD.** 179, Clapham Rd., London, S.W.9.

T.V. and RADIO.—A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "no pass—no fee" terms. Over 95% successes. Details of exams. and home training courses in all branches of radio and T.V.; write for 144-page handbook free. B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

Continental A/M-F/M Gram Chassis

Complete with 3 Speakers Internal Dipoles and Magic Eye Escutcheon—6 Valves and Rectifier, Variable Ferrite AE, Brand New, £25.0.0. Including Tax.

M.C.V., 3 Farrington Road, E.C.1. CHA. 4131.

VALVES—Guaranteed

DAF91	6/6	VU111	3/8	6BW6	6/6	6X4	8/6
EA50	2/-	W77	5/-	8C5	6/-	6X5	7/6
EEC33	7/6	OZ4	7/6	8CH6	7/6	7HT	7/6
EEC33	8/6	LS5	6/6	8F12	7/6	8D2	7/6
EF36	5/6	IU5	6/6	8J5	6/-	8D3	7/6
EF39	7/-	3D6	4/6	8K7G	4/6	9D2	6/-
EF50	5/-	4D1	4/-	8K7M	6/-	9D6	7/6
EF91	7/-	6A8	7/6	8SA7	9/-	7D8	5/6
EL32	6/-	8AK8	7/6	8SG7M	7/6	12BA6	7/6
PC84	11/-	8AM6	7/6	8SNTGT	7/6	12BE6	7/6
PY81	10/-	8AQ5	7/6	8/6	12BH7	7/6	8/6
TH11	4/-	8B8	6/-	8U5(UX)	12K7	8/6	8/6
VR6A	3/6	8B9	6/-	7/6	15D2	5/6	8/6
VR66	3/6	8B8	7/6	6U7	7/6	80C5	8/6
VT20	3/6	8BS7	7/6	6V6	7/-	50L6	8/6

Postage 6d. extra. (Also all components)
"Jason" F.M. Tuner Kit, complete, £6.17.6, plus 2/6 post.

TELEKIT SUPPLY

104, High Street, Beckenham, Kent
Phone: BEC 3720.

F M and H-F-I Components

DENCO F.M. TUNER	circuits	1s. 6d.
RADIO CONST'R. F.M.		2s. 0d.
MULLARD AMPLIFIERS		3s. 6d.
G.E.C. 912 PLUS AMPLIFIER		4s. 0d.
G.E.C. F.M. PLUS TUNER		2s. 6d.

Separate price lists available on request to
J. T. FILMER MAYPOLE ESTATE, BEXLEY, KENT.
Tel. Bexleyheath 7267.

Morse Code operating . . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.
Send 21d. stamp for Payment Plans and Full Details of all Courses.

CANDLER SYSTEM CO. Dept. 5L.O. 52D, Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

INCORPORATED Practical Radio Engineers' home study courses of Radio and TV Engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. "The Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peaks for Superhets. 5/9. Membership and Entry Conditions booklet. 1/-. All post free from the **SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.**

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. B.I.E.T. (Dept. 242A), 29, Wright's Lane, London, W.8.

GALPIN'S Electrical Stores


Send for Free List for Small Power Transformers, Electric Light and Slot Meters, Volt, Amp and Milliampmeters, etc., Transformers made to order.

Radio Bargains for Visitors
OPEN ALL DAY SATURDAY.

468 HIGH ST. LEWISHAM LONDON, S.E. 13 (Nr. Station Lewisham Junc.)

OSCILLOSCOPE

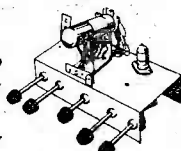for workshop or laboratory use. Can use power supply from most AC mains domestic receiver equipment.
Price £10 (Post 2/6)
or send stamp for further details



E.M.I. INSTITUTES, Dept. 32, LONDON, W.4

NEW BOOKS

- Frequency Modulated Radio, by K. R. Sturley. 15/-, postage 6d.
- Frequency Modulated Receivers, by T. D. Jones. 17/6, postage 1/-.
- H.F. Television Receivers, by D. H. Fisher. 21/-, postage 1/-.
- Practical Mechanics Handbook, by F. J. Camm. 8th edition. 16/-, postage 1/6.
- T.V. Timebase Circuits, Principles and Practice, by C. H. Banthorpe. 5/-, postage 4d.
- Practical Transistors and Circuits, by J. S. Kendall. 3/6, postage 4d.
- Correcting T.V. Picture Faults, by J. Cura. 3/6, postage 4d.
- Certificates and Awards, by R. S. G. B. 2/6, postage 3d.

UNIVERSAL BOOK CO.
12, Little Newport Street, London, W.G.2
(adjoining Lisle Street)

VACANCIES FOR SKILLED CRAFTSMEN IN GOVERNMENT SERVICE AT CHELTENHAM

Experienced in one or more of the following:—

1. Maintenance of radio communication receivers.
2. Sub-assembly lay-out, wiring and testing of radio type chassis.
3. Cabling, wiring and adjustment of telephone type equipment.
4. Fault finding in, and maintenance of, electronic apparatus.
5. Maintenance of Teleprinters or Cypher Machines and associated telegraph equipment.

BASIC PAY: £8 11s. 4d., plus up to £2 10s. merit pay, assessed at interview and based on ability and experience.
Opportunities for permanent and pensionable posts.
Five-day week, good working conditions, single accommodation available.
Apply to: **Personnel Officer G.G.H.Q. (FOREIGN OFFICE)**
53, Clarence Street, Cheltenham.

REQUIRED

for Domestic Television Production:

Experienced Final Tester
Several Alignment & Functional Testers.

Male & Female Electrical/Mechanical Inspectors.
(youths would suit).

Continuous employment for suitable personnel. 44-hour, 5-day week, with opportunities for overtime. Top rates of pay. Clean working conditions. Canteen, Social Club.

APPLY: Personnel Officer, Peto-Scott Electrical Instruments Limited
Addlestone Road, Weybridge, Surrey

ASTRAL RADIO PRODUCTS

- "HOME RADIO," 32 page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves. 7/-, post 3d.
- TRF COILS. Specified for 'Bedside Push-button 4', 'All Dry 3 Band, 3', 'Push-button 4', etc. 6/6 pr., post 6d. Push-button Unit with modification data 7/-.
- TRAFAL WAVE HF Coils. Specified for 'Summer All Dry Portable', 'Modern 1 Valver', 'Modern 2 Valver', 'B 7 G Battery Miniature', etc. 4/3, post 3d.
- HF'S Miniature, 1" x 1" x 2" in cans. Extra high Q. Special offer, 3/6 pr., post 6d.
- R COILS. AC, B pass 3, 3/6 each, post 6d.
- FRAME AERIALS. M.W., 5/-, post 4d.
- H.F. CHOKE (Osmor C.C.1), 6/9, post 4d.
- Crystal Set Coils, L. & M.W., 2/6, post 3d.

ANNAKINS BARGAINS

- Rect. and Radar Units. R1355 25/-, R3515 45/-, I25 8/9. Amplifier No. 445 32/-. Modulator IC456 (less dynamotor) 22/6. Amplifier I25A 7/6. Waveform Gen. type 40 22/3.
- RF28, RF27 (damaged dials) 17/6. Indicator type 95 (dam. dials) 43/-.
- Misc. R.A.F. Kites 17/6. Box with 16 toggles 7/9. Power Unit No. 173 12/6. P.U. 296 14/6. All above Carriage Free, Mainland only. Money Back Guarantee. Free Lists.

25 ASHFIELD PLACE, OTLEY, YORKS.

TRANSISTOR TECHNIQUES

The book technicians and experimenters have been clamouring for—Transistor Techniques—a new, complete, practical book on Transistors. Here are all the facts you always wanted on how to work with Transistors in practical circuits.

Now you can build Transistorized Test Instruments, Amplifiers, D.C. Transformers, Auto Light Control, Geiger Counters and hundreds of other devices.

This book not only shows how to build practical transistorized equipment, but warns you about pitfalls.

Valuable construction details on a unique transistor tester which alone is worth many, many times the low price of the book.

GERNSBACK LIBRARY

PRICE 12s. POSTAGE 9d.

The MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23, PRAED ST., LONDON, W.2

Write or call for our catalogues.

Phone: PADDDING 4185.

Open 6 days 9-6 p.m.

W. B. SUPPLIES

95, OLDHAM STREET, MANCHESTER, 4

Terms.—Cash with order. Orders under £1 add 9d. postage. orders over £1 add 1s. unless otherwise stated.

SPECIAL OFFER.—Collaro RC54 Record Changers, 3 speed, auto change, brand new in maker's sealed cartons, £7 7s. carriage 5s.

RELAYS, G.P.O. TYPE.—250Ω 2 make 2 break, 250Ω 1 make 2 break, 500Ω 1 make 1 break, 3/6 each.

CAN CONDENSERS.—8 mfd. 500 v. 300 mfd. 50 v. 500 mfd. 12 v. 100 mfd. 40 v. 300 fd. 12 v. 250 mfd. 25 v. 100 mfd. 50 v. 30 mfd. 350 v. All at 1/3 each.

TELEPHONE TYPE SWITCHES.—Centre off position, 2/- each.

HEADPHONES.—Low resistance, 8-6 pair, high resistance, 16/11 pair. Midget I.P. Transformers, 445 fcs., brand new in maker's cartons, 9/- pair.

SPAKER FRET (Gold, metal), 12" x 12" 4/6; 18" x 12", 6/9. Filament Trans., 230 volt, 6.3 v. 2 a., 6/6. L.F. Chokes 10 Hys. 80 mls., 6/-; 15 Hys. 150 mls. (heavy duty), 9/-; Postage 2s.

YANLEY TYPE SWITCHES.—2 pole 6 way, 5 bank 6 way, 4 pole 3 way, 6 pole 5 way, 4 pole 2 way, 3 pole 6 way, all at 2/3 each. Semi-midget long spindle 2 pole 3 way, 2 pole 6 way, 1 pole 12 way, 4 pole 3 way, 3 pole 4 way, all at 3/6 each.

BOOK ON HOW TO MAKE T.V. AERIALS. Bands 1 and 3 and V.H.F., 2/9 post paid.

WESTINGHOUSE.—9 amp. Meters, 7/6; Valves EF50, 4/-; 3 for 11/6; EF55, 5/6; Solid Dielectric Variable Condensers, .0003 mfd., .0005 mfd., 3/11 each.

T.V. AERIAL INSULATORS. bored for 3/8in. tube, 3/-; Pre-set wire-wound pots, 3 K., 1/-; Germanium Diodes (G.E.C.), 1/8; Flexible signal type, 70in., 1/6.

AMPLION POTENTIOMETERS. with single pole switch, long spindle, semi midget, 100 K., 1 meg., 2 meg., all at 3/6 each.

ILLUSTRATED CATALOGUE No. 10

6^D. Post free

(U.K. only)

Over 2,000 guaranteed components by the leading manufacturers. Short wave, broadcast and transmitting components, valves, etc. Special items for the serviceman. 135 photographic illustrations on art paper. Complete list of Amateur prefixes and world zones. Orders are dealt with the day received.

SOUTHERN RADIO & ELECTRICAL SUPPLIES

SO-RAD WORKS
REDLYNCH, SALISBURY

Telephone: Downton 207.

6/12 volt Rectifiers. 1 amp., 7/6; 2 amp., 10/-; 3 amp., 12/6; 8 amp., 35/-; P. & P. 1/6. Charger Transformer. 1 amp., 14/6. P. & P. 2/-.

Special Heavy Duty Transformer. 400-0-400 v. 200 mA. 5 v. 2.5 a. 4 v. 2.5 a. 6.3 v. 5 a. 4 v. 4 a. 25/-; P. & P. 3/-.

Mains Radio Transformer. 250-0-250 v. 80 mA. 6.3 v. 4 a. Suitable for use with 6X5 rectifier, 7/6. P. & P. 2/6.

.25 H.P. Electric Motors. Single phase. Self-starting. Brand new by E.D.C.C. Foot mounted. Guaranteed, 97/6. Carriage 5/-; .5 mA Relays. 2 windings, 1,000 ohms and 4 ohms. Adjustable contacts, 3/6. P. & P. 1/-.

12 volt Mobile Public Address Equipment. Complete with loud speaker and crystal mike. 12 watts output. New condition. **£17.10.0.** C.P.

Money back guarantee on everything.

When in Exeter call and see our large stocks.

ELECTROSURP

120, Fore Street, Exeter

Phone 56657.

VALVES

New Tested and Guaranteed

165	7/6	8BR7	8/6	ECH35	9/-	EL84	10/6
185	7/6	8BW6	7/6	ECH42	8/-	EY51	11/6
174	7/6	8J5G	5/6	10/-	EZ40	8/-	
354	7/6	12AT7	9/-	ECL80	10/-	KT33C	7/6
3V4	7/6	12AU7	9/-	10/6	UBC41		
5Z4G	8/6	807	6/9	EF39	5/6	10/-	
6AL5	6/6	5763	8/6	EF41	10/-	UCH42	10/-
6AM6	7/6	EBC41	9/6	EF80	9/6	UT41	10/-
6AT6	8/-	EBF80	8/6	EF82	4/9	UL41	10/-
6BE8	7/6	10/-	EL41	10/-	UY41	8/-	

MATCHED PAIRS. EL84, 28/-; 6V6 and GT. 17/-; 6BW6, 18/-; KT33C, 19/6; 807, 14/6 per pair.

VOLUME CONTROLS. small, long spds., L.S. 3/-; S.P. 4/-; D.P. 4/6. All values.

PAPER BLOCKS. 4 mfd., 1,000 v. wkg., 2/3. P. & P. 9d.

R. J. COOPER (GBX)

32, SOUTH END, CROYDON, SURREY
Croydon 9188

NEW VALVES

(From Government and Trade Surplus Sources, Bankrupt Stocks, etc., No Rejects, All Guaranteed, Unused and Boxed.)

DF91	7/6	EK32	8/6	11T4	7/6	6SQTGT	
DF91	7/6	EK90	8/-	354	7/6		8/-
DL91	7/6	EL32	6/6	8V4	7/6	6SS7	7/6
DL92	7/6	EL41	10/6	2C34	4/6	6V6	7/6
DL94	7/6	EL94	10/6	2X2	4/6	4X4	7/6
DK92	7/6	EY51	11/6	504	8/-	6X5	6/6
DK90	9/-	EZ35	8/-	5Z4	8/6	12A6	7/6
EBT19	1/6	EZ40	8/-	6AG5	6/9	12AH7	6/-
EB50	1/-	KT30	9/6	6AK5	6/8	12AT7	9/-
EB34	2/6	KT44	5/6	6AL5	6/8	12AX7	9/-
EB91	6/-	KT66	10/-	6AM6	6/8	12AX7	9/-
EB33	8/6	PL81	10/6	6AT3	8/-	12H6	2/6
EB41	9/6	PL82	10/6	6BE6	8/-	12J5	5/-
EBF90	9/-	PV81	6/6	6BA9	8/-	12J7	7/6
ECC81	9/-	PCF82	11/-	6BR7	8/6	12KTGT	
ECC84	11/6	PCC81	10/-	6BW6	8/6		7/6
ECH35	8/6	PCC84	11/6	6B8G	7/6	12K3CT	
ECH81	9/-	RK34	3/6	6B8S	7/6		10/-
ECH42	10/-	RL37	6/-	6C4	6/-	12Q7GT	
ECF82	11/-	SP61	4/-	6C6	5/-		8/6
ECL80	9/-	UBC41	10/-	6J5	2/6	12SC7	7/6
EC52	5/-	UP41	10/-	6J6	5/-	12SQ7	7/6
EC90	6/-	UL41	10/-	6K7	7/-	12SK7	7/6
ET36	6/-	UY41	8/-	6K8	5/6	35L6	9/-
EF81A	12/6	VL22	5/-	6L6	10/-	332	40/-
EF93	6/-	6Q7	6/-	6Q7	9/6	807	7/6
EF41	10/-	VR116	6/-	6R7	7/6	954	60/-
EF50	5/-	VR150	30	6SA7	8/-	955	5/-
EF65	9/6			6SA7	8/-	955	5/-
EF80	8/6	VU111	7/6	6SH7	7/6	6763	10/-
EF85	10/6	X85	10/6	6SJ7GT	7/6	8013	2/6
EF91	6/6	OZ4A	6/6	6SK7	7/6	901	5/-
EF92	5/6	IR5	7/6	6SL7	6/6	9002	5/-
EF95	6/6	IR5	7/6	6SN7	7/6	9003	5/-

MATCHED PAIRS.—EL84, 28/-; 6V6, 17/-; KT33C, 22/-; 6BW6, 17/3; EL32, 14/-; 807, 16/6; KT33C, 19/6.

OBsolete TYPES.—Large range available. British, U.K., Side Contact, Continental, etc., S.A.E. please with enquiries. No lists available.

C. LAWRENCE (Dept. 8)

15b, Chipstead Valley Road, Coulsdon, Surrey

Post and packing 6d., free over £1. Mail order only.

ALFRED PADGETT

40, MEADOW LANE, LEEDS 11

TEL.: CLECKHEATON 93

RADIO VALVES with 90 days' guarantee, post 9d. per valve. 10c. lots post free. Less 5%. EF36, 4/-; 6K7, 2/-; 807 (British), 4/-; DL94, 2/6; 6SN7, 6/-; 6X5, 4/9; 6C6, 3/6; 854, 1/3; 9004, 6d.; CV63, 1/-; 6BE, 9d.; 6H6 Metal, 1/3; 2X2, 1/3; VU111, 1/6; VR137, 1/3; VR50, 1/6; VR54, 1/-; VR54, 9d.; 8D2, 1/-; 6B, 2/-; 6D6, 3/-; 6J5, 3/6; KT33C, 6/-; UB, 1/-; Pin. 8/-; PEN46, 2/6; AC6PN, 2/6; U17, 1/3; Type 46, 2/-; Type 75, 4/-; 12SC7, 1/-; 12S7, 3/-; 12H6, 1/-; ME4, 2/6; 61T6, 7/6; PX25, 9/-; VR150, 30.

TUBE UNIT BC929A. Complete with 3BP1 3in. tube, less valves, this is a scope all but made £1.5.0. Carriage 7/6, tube guaranteed.

R.D.F.1 SETS. New complete with 5 VR55, 1 CV83, 1 DR137, 2 VR56, 1 VR54, and 3 VR92, less power pack, 15/-, carriage 7/6.

GEN. SHEET for mod. to I.T.A. 2/- post free. **MIXED RADIO PANELS.** Full of resistors and condensers 12 for 4/6, post free.

SPECIAL PURCHASE OF CRYSTAL DIODES. 10d. each, post 2d.

These are the real McCoy, with long wire ends and will put real pep into any crystal set.

NEW STOCK of lin. 75 ohms coax cable, suitable for any band, 6d. per yard, any length cut, post free.

NEW EF50 VALVE BASES. Ceramic, 3d. each, post 3d. 2/6 do. Post free.

MIXED B.A. NUTS AND BOLTS. 1 lb. weight 1/6, post 3d.

SWITCHES. toggle, 6d. VAC Handle Type 1W Electric Fire Type 1 Bar, 1/-, 2 Bar, 1/6. Post 9d.

PARTS REMOVED FROM NEW T.V. UNITS. Micrometer drive complete, 2/6. Post 1/-. Handies, 9d. Post 6d. Coil formers, (10/-) 6d. Post 6d. Switch and Knob, 9d. Post 3d.

SELENIUM METAL RECTIFIERS. 250 volts 100 mills., 5/-; 120 volts, 60 mills., 2/-; J50, 1/6. All 12 months' guarantee.

SMALL 24-VOLT A.C. D.C. MOTOR. 1,200 revs. P.M. good torque on 13 volts. Brand New, 3/6 (3p. carriage). Post 1/3.

Broadcast in Your Own Home



The New Highly Sensitive Microphone incorporating a specially wound transformer designed to match any Radio or Radiogram, mains or battery. Hours of amusement at a party, good fun for all the family. Suitable for baby alarms and many other purposes. Not a toy but a guaranteed working instrument. Full instructions enclosed. Made to sell at 21/- POST OUR PRICE 15/- FREE. Trade supplied

E. CLAPSHAW

369, Alexandra Rd., Muswell Hill, London, N.10.

GRAM-PAK AMPLIFIERS

Complete £3.19.6 P. & P. 2/6

This midget 4-watt amplifier fits neatly into any record player leaving ample room for speaker 7" x 2 1/2" x 1 1/2". Suitable with any speaker and all modern crystal 3-speed pick-ups. For 200-250 v. A.C. Perfect, distortionless, quality guaranteed.

ACCESSORIES:

BSR crystal turnover P.U., £1.14.5. 7" x 4" elliptical speakers, 19s. 6d. BSR 3-speed player unit with above P.U., £4.12.6d.

The complete outfit ready for your cabinet, £9.10.0 post free.

6d. stamp for details of this and other models.

ELECTRO-ACOUSTIC LABS. TAIN: ROSS-SHIRE: SCOTLAND

SPARKS' DATA SHEETS

Constructional plans of Guaranteed and Tested Radio Designs

THE "SEAFARER"

A New Low-consumption battery-operated 2-Valver with unique features.

SEE WHAT IT OFFERS


UNLIMITED TRIPLES & INTEREST ON 80-160 M. AMATEUR BANDS. AERONAUTICAL BANDS. THE FULL TRAWLER BAND NEAR-TO-SHORE TRAFFIC. MEDIUM- & LONG-WAVE.

Plus Simplicity of Operation and Construction and Low Upkeep Costs. Full-size Data Sheet with generous Instructions and Comp. Lists. 3/- Chassis and all Components in Stock.

L. ORMOND SPARKS

Valley Road, Corfe Castle, Dorset

PORTABLE TEST PANEL

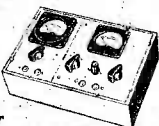

for workshop or laboratory use

Two separate moving coil meters, one for voltage and the other for current measurement. Supplied in wooden case with metal front and with test leads.

Ranges (AC & DC)
0-30 mA
0-10v, 0-25v
0-500v
0-10,000 ohms
Size 8 1/2" x 5 1/2" x 2"
light and portable

Price £6.10.0 (incl. post/pkg.)

Order now from—
E. H. I. Institutes, Dept T.P.32, London, W.4

G.W. SMITH & CO (RADIO) LIMITED

3-34 LISLE STREET, LONDON, W.C.2
TELEPHONE: GERRARD 8204/9155

AMERICAN GEARED MOTORS

Brand new 24 v. D.C. motors with built in precision gear box with twin shaft outputs, 20 r.p.m. and 6 r.p.m. Size 7in. x 1 1/2in. Shaft dia. 3/16in. Will also operate on 12 v. giving reduced outputs. Only 29/6 each.

CRYSTAL MICROPHONE INSERTS.

Extra sensitive, 4/6 each.

MORSE BUZZERS. Brand new, 3 v., 2/6 each.

DEAF AID EARPIECES. Brand new, 30 ohm, 3/6. Deaf aid valve, CK505, new, 2/6. 1 meg. pots w/switch, 1/- Midget switch, 1 pole 3-way, 1/- Midget output transformers, 2/6 each.

ROTARY CONVERTERS. Input 24 v. D.C. Output 230 v. A.C. 50 cycles, 100 watts, new, 92/6 each.

MODULATOR TYPE 67

Bargain instrument containing a complete A.C. mains power pack, 230 v. input. Output 350 v. 120 mA., and 6.3 v. 5 amps. Choke and condenser smoothed, uses 5Z4 rectifier. Many other useful components, including 11 valves, 5 5P61, 1 VR116, 2 EB34, and 3 EA50. Brand new, 49/6 each.

MODEL MAKERS MOTORS. P.M. type reversible. Operates from 5-24 v. D.C. Size 2in. x 1 1/2in. with 1/2in. spindle. Brand new, 8/6 each.

AR.88 WAVECHANGE SWITCHES. Brand new and boxed, 17/6 each.

YAXLEY METER SWITCHES. 1 pole, 12-way, 8 banks, 7/6 each.

SOUND POWERED EARPIECES. Ideal for intercommunication, no batteries required, new, 3/6 each.

AMERICAN ROTARY GENERATORS

Input 12 v. D.C. Output 250 v. D.C. 80 mA. Brand new, 22/6 each. Ditto 6 v. input, 22/6 each.

COPPER AERIAL WIRE. 300ft. reel, 3/6.

CHARGING TRANSFORMERS. Input 200/250 v. Output 9 or 15 v. 1 amp, 9/9; 3.5, 9 or 17 v. 2 amp., 14/3; 3.5, 9 or 17 v., 4 amp., 16/6.

METAL RECTIFIERS. Full wave and bridged. 12 v. 1 amp., 6/3; 12 v. 2 amp., 9/3; 12 v. 4 amp., 13/9.

SLIDER RHEOSTATS. 14 ohm 4 amp., 7/6; 1 ohm 12 amp., 6/6.


GRAM MOTORS. Garrard 200/250 v. A.C. gram motors complete with turntable. Speed adjustable by governor 0-45 r.p.m. Only 22/6 each.

HEADPHONE ADAPTORS. High to low impedance matching, 1/3.

POWER UNIT 285. Input 230 v. A.C. Output 2,000 v. 5 mA., 350 v. 200 mA., 6.3 v. 7 amps. Fully smoothed, ideal for scope, etc., 59/6 each.

FIELD TELEPHONES. Type Don Mk. 5. Buzzer calling. Ideal for inter-house or office communication. Supplied complete with two 1.5 v. cells ready to operate. Only 39/6 each.

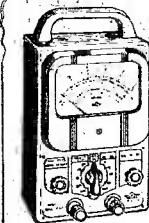Hours of Business: 9 a.m.—6 p.m., Thursday, 1 p.m. Open all day Saturday. Please print name and address clearly and include postage or carriage on all items.



PULLIN
SERIES 100
TEST METER
AC/DC 10,000 A/V
21 RANGES
100µA to 1000 V
COMPLETE IN DIE-CAST CASE WITH TEST LEADS CLIPS AND PRODS FULLY GUARANTEED

SENT POST FREE FOR £2.10.0 AND NINE FURTHER MONTHLY PAYMENTS OF 14.6. CASH PRICE £12.7.6.

FRITH RADIOCRAFT LTD

69-71 CHURCH GATE LEICESTER & 28 HIGH ST NEWPORT PAGNELL Bucks

Fidelia
HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10
AM/FM models give reception of V.H.F. high quality transmissions plus normal wavebands. Major AM/FM 12 valves, £44 De-Luxe AM/FM 13 valves, £39/12/- P.M. Tuner, £14.3/-. Data sheets free. Electro Acoustic Developments, 2 Amburst Road, Telscombe Cliffs, Sussex.

H.A.C. SHORT WAVE EQUIPMENT

Noted for over 18 years for S.W. Receivers and Kits of Quality.

Improved designs with Denco coils: One-Valve Kit, Model "C" Price, 25/- Two " " " " "E" " 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH), 11, Old Bond Street, London, W.1.

BROOKS (RADIO)

4 CHARLES STREET, MORECAMBE, LANCs.


New - VALVES - Guaranteed

1A7	11-6K7	5/6	35Z4	8/6	EZ40	8/6		
1C5	9/6	6K3	8/180	8/-	EZ80	8/6		
1H5	9/6	6Q7	9/-	EABC80	PCCB4	11/6		
1N5	9/6	6SN7	8/-	10/-	PCFR212	11/6		
1R5	7/6	6V6	7/6	EAP4210	PL81	11/6		
1S5	7/-	6X4	7/6	EBC41	PL81	11/6		
1T4	7/-	6X5	6/6	10/6	PL82	9/6		
3S4	7/6	7B7	8/-	EBF8010	PL83	12/6		
3V4	8/-	7C5	8/6	ECC8111	PY30	9/6		
5U4	8/6	7C6	3/6	ECC8111	PY81	10/-		
5Y3	7/6	7S7	8/6	ECC8311	PY82	9/6		
5Z4	8/6	7Y4	8/-	ECH4211	PY83	11/6		
6AL5	6/6	12K7	8/6	ECH4211	UBC41	9/6		
6AM6	8/6	12K8	9/-	EBF8910	ECH4211	11/6		
6AT5	8/-	12Q7	8/6	EF86	11/6	UF41	10/6	
6BA6	8/6	25Z4	8/6	EL11	10/6	UL41	10/6	
6BB5	8/6	35L5	8/6	EM54	10/6	UT41	8/6	
				8/6	EM59	12/6	VU39	8/6

Pct and packing 6d. per valve extra.

A NEW Dulci TRIUMPH

IN SOUND REALISM—AT LOWEST COST

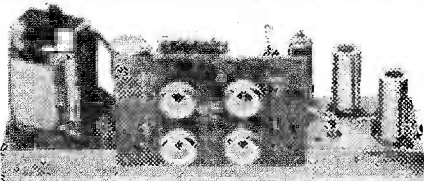

MODEL G.A.4. HIGH FIDELITY AMPLIFIER

4 watt 4 valve circuit with a frequency response of 40-15,000 c.p.s. Neat Control Panel size 6" x 4" on fly leads for individual mounting (main chassis 12" x 4" x 6"). Input selector switch matching to Radio, L.P. and 78 r.p.m. records. Separate Bass and Treble Controls giving wide range of cut and lift. Volume Control. Rotatable Mains Transformer for hum cancellation. Price £9.9.0.

H.4. RADIOGRAM CHASSIS AM/FM



7 valve 4 waveband superhet with F.M. (V.H.F.). Magic eye tuning indicator. High sensitivity. Bell-clear quality. Dial size 11" x 5". Sockets to connect Speaker (3 & 15 ohm), Pickup, Aerial, Earth, V.M.I. Dipole and providing power for Gram Motor from mains. Price £24.8.6. inc. tax.

F.M. (V.H.F.) TUNER £17.10.3

ALL DULCI PRODUCTS ARE FULLY GUARANTEED. Write for details to Ref. PW.

DULCI COMPANY LTD, 97 Villiers Rd, London, N.W.2 WILLESDEN 6678

TECHNICAL TRADING CO.

4 AMP. CHARGERS, meter, rheostat, high finish 12in. x 12in. x 5in., £4.10.0. MIRROR GALVOS, new, 15 sec. damping, high sens., all adjustments top make, case, £6. TIME SWITCHES, 7 day, 2 scale automatic, 25 amp. mercury switches, 27.6. WAVE CONDENSERS, 10 pf., 5 mfd., our assortment 50 for 6.6; 100 12.-

IMPERIAL F.M. AM CHASSIS. Latest gold black finish. "piano-keyboard" switching. special F.M. unit. E3C85, E3C81, E3E9. EABC90 output EL41, plus rect., unusual opportunity at 15 Gns., carr. 5/-

AMERICAN SCREWS TRANSFORMERS, complete, including two 82's, £4. carr. 6/- THROAT MIKS, 2.6. SINGLE HEAD- PHONES, headband, new, 2.6. DISTRESS TRANSMITTERS, all dry, dipole telescopic aerial, weight 11lb., 12.6. 10.20 WATT 12-VOLT AMPLIFIERS, high gain push pull. Ideal cars, compact untested, £4.10.0., carr. 6.-. 1 meg. Pots. D.P., S.W. 3in. spindle, small, 3.6.

SPECIAL BARGAIN! 12 v. 4 amp. rectos, 9/6 ea., £5 doz. Full wave iron selenium heavy compact type.

TECHTRAD SUPERHET COILS, polystyrene formers, high finish, Med. and Long (both aerial and osc.) Wave coils, full instructions, 7/6. Pair Quality Midget IFS, 8/6. Or both items, 15/6. ALUMINUM CHASSIS, 6in. x 4in. x 1 1/2in., 2.-. 8in. x 6in. x 1 1/2in., 3.8. 8in. x 6in. x 2 1/2in., 4/9. 8in. x 10in. x 2in., 5/9. 8in. P.V. SPEAKERS.—Top Makes, 12.6. Ditto, tested ex. eqpt., 8.6. 7in. x 4in. Ellipticals, 18.-. 6 1/2in. P.M., 10.-. HEAVY 12in. P.M., hi flux, hammer finish, £4.19.0. CHOKES, 15H, 150 mA., 9/6. RECORDING TAPE.—Known make, 1.200ft. Big Purchase enables sale at 18.- reel, 2 1/2 hour, 0005, Long, 4in. sp., 3.6.

CONDENSERS.—Latest ceramic, 10, 20, 50, 300, 1,000, 3,000 pf., 5.- doz.; LATEST ELECTROLYTICS.—100 mfd., 6 vw., 1.-; 8 mfd., 250 vw., 1.3; 16-16, 350 vw., 3.-. RESISTANCES.—1 w.-2 w., 47 0-1 m. 2.- doz., our assortment, 10-100. AMPHENOL VAIN- HOLDERS.—Occal, BSA, B7C, B7A, B9C, 6.- doz., BPA w-screen, 1.3; 12.- doz. W.W. PRESET POTS.—500 0-1K, 2K, 2.5K, 5K, 10K, 20K, 25K, 2.- ea.

AMPRO 16 mm. TALKIE PROJECTORS.—U.S.A. senior model U.A., push-tuft amp., heavy 12in. spide, 150 210 v. A.C., 750 w. lamp, tested v.g. cond. snip price £65 complete. DITTO G.B.L.516. Sound/silent, cond. £33, excel. cond. £38

GUARANTEED VALVES, EBB, 1/6; SP6A, 2/6; SP6, 3.-; SP210, 3/8; 6AK5, 6J5, 4.-; 6SK7, 4/6; 6AR, 6J7G, EF92, PEN25, 5/-; 6AG5, 807, EL81, 5.-; 6KT6, VR150,30, gd., 5/6G, 6C5CT, 6C4, 6F6G, 6K6, 6/6; ECC81, 3.-; 12A7, U22, 8/6; 6F33, 9/6; 6L6 (Metal), 11.-; 813, 39.-. Postage 1/- in £1 (10 in £1 Speakers Trans., Min. 6d. No C.O.D. 1,000 BARGAINS TO CALLERS AT:

350/352, FRATTON ROAD, PORTSMOUTH
PORTSMOUTH'S RADIO, TV AND TOOL SHOP

Taylor

JUNIOR UNIVERSAL METER



Model 120A

A small 21-range instrument ideal for the enthusiastic amateur. Sensitivity is 1,000 o.p.v. A.C. and D.C.; Accuracy: 2% D.C.; 3% A.C.

RANGES

Volts D.C.: 0-25-10-50-250-500-1,000-2,500.

Volts A.C.: 0-10-50-250-500-1,000-2,500.

Milliamps D.C.: 0-1-10-50-500-5,000.

Resistance: 0-2,000 ohms, 0-200,000 ohms. Can be extended to 20 megohms. Automatic overload protection fitted to meter movement.

PRICE £9.15.0. PROMPT DELIVERY

CREDIT TERMS: Nine monthly payments of £1.4.4.

TAYLOR ELECTRICAL INSTRUMENTS LTD.

Montrose Avenue, Slough, Bucks.
Telephone: Slough 21381. Cables: Taylins, Slough

The Walk-around Shop for—

EMI TEST EQUIPMENT For AMATEURS

SPOT FREQUENCY MARKER. Type AD/U405. Operating on a frequency of 1 Mc/s and generating harmonics at 1 Mc/s intervals up into the V.H.F. range.

V.H.F. GRID DIP OSCILLATOR. Type AD/U406. Frequency may be varied over the range 65-150 Mc/s and accuracy is within 2% at all frequencies within this range. Consumption 0.3 amp. at 6.3 volts and 3 mA at 150-250 volts. A stabilised power supply is not essential.

ABSORPTION WAVEMETER. Type AD/U408. This consists of a variable tuned circuit, across which is connected a germanium crystal in series with a 500 microammeter. Frequency range is continuous from 1.6-30 Mc/s. Accuracy is within 2%.

V.H.F. ABSORPTION WAVEMETER AND FIELD STRENGTH METER. Type AD/U409. Similar design to Absorption Wavemeter, but for operation in frequency range 65-150 Mc/s. Accuracy is within 2% over specified range. External coupling element consists of a single turn loop connected to instrument by 2ft. of co-axial cable. Terminal provided for connecting a short rod aerial, to enable comparative field strength checks to be made. Dimensions: 8 1/2in. x 4 1/2in. x 2 1/2in.

GENERAL PURPOSE POWER SUPPLY UNIT. Type AD/U410. L.T. supply being isolated from earth. A separate H.T. "On/off" switch is provided. Input: 200-250 volts, 50 cycles A.C. only. Output: 6.3 volts at 2 amps, approx. and 250 volts at 60 mA (unstabilised). Dimensions: 8 1/2in. x 4 1/2in. x 5 1/2in. All above Units New and Boxed. AD/U405-406-408-409 £13.10.0 ea. AD/U410 Power Unit £4.0.0. Postage and Packing 3/-.

DESYNN TYPE Antenna or Beam Position Indication System. This comprises a Transmitter unit and Indicator which will operate on 12 or 24 volts D.C. and will indicate with instantaneous and smooth pointer movement. The Transmitter is a specially designed potentiometer and will operate the Receiver on a simple three wire system and the receiver in this instance is calibrated, in gallons, but dial could be easily altered to indicate a 360 deg. sweep. Transmitter and Receiver with full instructions. Price 12/6, p.p.

PROOPS Dept. 'P', 52, Tottenham Court Road,
BROS. LTD. London, W.1. LAngham 0141
Shop Hours: 9-6 p.m. Thursday: 9-1 p.m. Open all day Saturday.

Practical Wireless

BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

2/- each		
1937 Crystal Receiver ...	PW71*	
The "Junior" Crystal Set ...	PW94*	
2/6 each		
Dual-Wave "Crystal Diode" ...	PW95*	

STRAIGHT SETS

Battery Operated

One-valve : 2/6 each		
The "Pyramid" One-valver (HF Pen) ...	PW93*	
The Modern One-valver ...	PW96*	
Two-valve : 2/6 each		
The Signet Two (D & LF) ...	PW76*	

3/6 each		
Modern Two-valver (two band receiver) ...	PW98*	

Three-valve : 2/6 each		
Summit Three (HF Pen, D Pen) ...	PW37*	

The "Rapide" Straight 3 (D, 2 LF (RC & Trans)) ...	PW82*	
--	-------	--

F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ...	PW87*	
---	-------	--

3/6 each		
The All-dry Three ...	PW97*	
Four-valve : 2/6 each		

Fury Four Super (SG, SG, D, Pen) ...	PW34C*	
--------------------------------------	--------	--

Mains Operated

Two-valve : 2/6 each		
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*	

Three-valve : 4/- each		
A.C. Band-Pass 3 ...	PW99*	

Four-valve : 2/6 each		
A.C. Fury Four (SG, SG, D, Pen) ...	PW20*	

A.C. Hall-Mark (HF Pen, D, Push Pull) ...	PW45*	
---	-------	--

SUPERHETS

Battery Sets : 2/6 each		
F. J. Camm's 2-valve Superhet ...	PW52*	

Mains Operated : 4/- each		
"Coronet" A.C.4 ...	PW100*	
AC/DC "Coronet" Four	PW101*	

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

One-valve : 2/6 each		
Simple S.W. One-valver	PW88*	

Two-valve : 2/6 each		
Midget Short-wave Two (D, Pen) ...	PW38A*	

Three-valve : 2/6 each		
Experimenter's Short-wave Three (SG, D, Pow) ...	PW30A*	

The Perfect 3 (D, 2 LF (RC and Trans)) ...	PW63*	
--	-------	--

The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen) ...	PW68*	
---	-------	--

PORTABLES

2/-		
The "Mini-Four" All-dry (4-valve superhet)	*	

MISCELLANEOUS

2/6 each		
S.W. Converter-Adapter (1 valve) ...	PW48A*	
The P.W. 3-speed Autogram ...	(2 sheets), 8/-*	
The P.W. Monophonic Electronic Organ (2 sheets), 8/-		

TELEVISION

The "Argus" (6in. C.R. Tube), 3/-*		
The "Super-Visor" (3 sheets), 8/-*		
The "Simplex" ...	3/6*	
The P.T. Band III Converter	1/6*	

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94 are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

One-valve : 2/6		
B.B.C. Special One-valver ...	AW387*	

Mains Operated

Two-valve : 2/6 each		
Consoelectric Two (D, Pen), A.C. ...	AW403	

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

One-valve : 2/6 each		
S.W. One-valver for American ...	AW429*	

Two-valve : 2/6 each		
Ultra-short Battery Two (SG, det Pen) ...	WM402*	

Four-valve : 3/6 each		
A.W. Short Wave World-beater (HF Pen, D, RC, Trans) ...	AW436*	

Standard Four-valver Short-waver (SG, D, LF, P) ...	WM383*	
---	--------	--

Mains Operated

Four-valve : 3/6		
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ...	WM391*	

MISCELLANEOUS

Enthusiast's Power Amplifier (10 Watts) (3/6)	WM387*
Listener's 5-watt A.C. Amplifier (3/6)	WM392*
De Luxe Concert A.C. Electrogram (2/6)	WM403*

QUERY COUPON

This coupon is available until Jan. 6th, 1957 and must accompany all Queries, sent in accord with the notice on our "Open to Discussion" page. PRACTICAL WIRELESS, Jan. 1957.

BUILD IN A BJ ARM

AND add fidelity to your installation.

BY OVERCOMING TRACKING ERROR IT MEANS

LONGER RECORD LIFE
EXTENDED OVERALL FREQUENCY RESPONSE
FREEDOM FROM DISTORTIONS

FRACTICAL WIRELESS says:—

Test records appeared to sound even better than with our hitherto standard equipment, "rumble" which was previously audible on an organ test record, appeared non-existent. Every serious "hi-fi" enthusiast should try to make this part of his installation.



3' ARM ... £2.4.11
 P.T. ... 18/-
 BJ PLUG-IN SHELL 17/3
 P.T. ... 6/11
 EJ SUPER 90 ARM
 (Studio Model) 11 gns.
 P.T. ... £4.12.5

Send for Fully Illustrated Leaflets:

(Dept. D) BURNE-JONES, MAGNUM HOUSE, SUNNINGDALE ROAD, CHEAM, SURREY.

CONSTRUCTORS build these at
DOWN-TO-EARTH PRICES

**PERSONAL
 PORTABLE
 RADIO**

30/-


This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere.
 Send 2/- for layout, Wiring diagram and Components Price List.



1v SHORT-WAVE RADIO

30/-

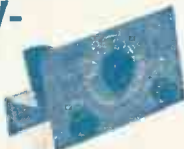- ★ Covers 10-100 metres
- ★ World-wide reception
- ★ Low drain valve.
- ★ Picture diagram and instructions for beginners.
- ★ Assembling time 1 hr



This 1 valve S.W. receiver can be built from our list of components for 30/-, including valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required. All components can be purchased separately and are colour-coded so that the beginner can build this set quite easily.
 Post and Packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE.

Send 2/- for specification, wiring diagram, layout and price list to:—

R.C.S. PRODUCTS (RADIO) LTD
 OLIVER ROAD, LONDON, E.17. Mail order only.

REPANCO HIGH-GAIN COILS

DUAL-RANGE MINIATURE CRYSTAL SET COIL with circuit. Type DRX1. 2/6.

DUAL-RANGE COIL with Reaction. With 2 mains, 2 battery and transistor circuits Type DRR2. 4/-.

MATCHED PAIR DUAL-RANGE T.R.F. COILS with Reaction. With battery, mains and feeder unit circuits. Type DRM3. 8/- pair.

PAIR DUAL-RANGE SUPERHET COILS with mains and battery circuits. Type SH4. 8/- pair.

FERRITE ROD AERIAL Long and Medium wave. Complete with fixing brackets. Type FR1. 12/6.

MINIATURE I.F. TRANSFORMERS. Pre-aligned 465 kc/s. 13/16in. x 13/16in. x 1 1/2in. For battery or mains receivers. Type MSE. 12/6 pair.

"R" COILS. Miniature Iron Dust Cored

Range	Aerial	H.F.	Osc.	Price
800-2,000 m	RA1	RHF1	RO1	3/3 each
190- 550 m.	RA2	RHF2	RO2	3/3 each
70- 230 m.	RA3	RHF3	RO3	3/3 each
15- 50 m.	RA4	RHF4	RO4	3/3 each

(Trade Supplied.) Post 3d. on all orders.

RADIO EXPERIMENTAL PRODUCTS LTD.

33, Much Park Street, Coventry

Telephone: 62572