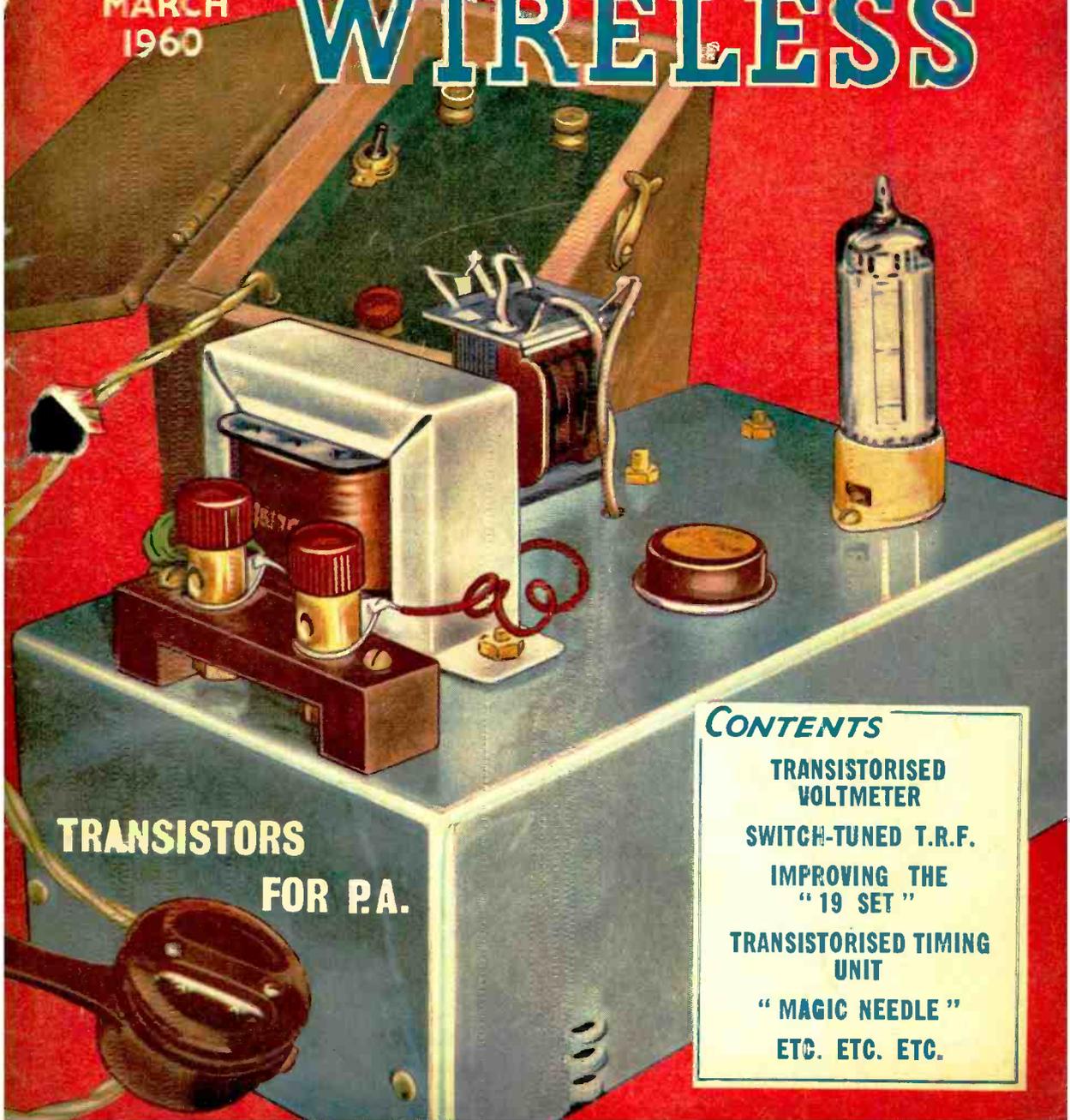


A COMPREHENSIVE PRE-AMP
PRACTICAL 1/6
WIRELESS

MARCH
1960



**TRANSISTORS
FOR P.A.**

CONTENTS

- TRANSISTORISED
VOLTMETER
- SWITCH-TUNED T.R.F.
IMPROVING THE
"19 SET"
- TRANSISTORISED TIMING
UNIT
- "MAGIC NEEDLE"
- ETC. ETC. ETC.

PORTABLE TRANSMITTER RECEIVER No. 18


Entirely self-contained 6-valve Transmitter Receiver for voice and C.W. Frequency: 6-9 Mc/s (50-33 metres). The Transmitter signal is generated by a master oscillator circuit followed by a power amplifier. The aerial is auto-coupled to the power amplifier by aerial taps to a parallel tuned output circuit. The Receiver is a 4-valve superhet, comprising signal frequency amplifier, frequency changer, I.F. amplifier, 2nd det. —A.V.C.—A.F. Stage. Selectivity: The resonance curve of the I.F. amplifier has a width of 7 kc/s. with

an average cut-off of 5 db/kc/s. Full netting facilities. circuit set for full modulation, operated by standard dry batteries, range approximately 10 miles. Incorporates Test Meter for aerial loading. readings. Supplied Brand New complete with Power Microphone, Headphones, Morse Key, Aerials, Webbing and full instruction book all for only 80/- Carriage 10/- 18 Set as above less attachments 80/- Carriage 10/-



80/-
Carr. 10/-

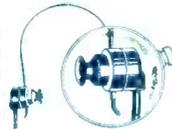LIGHT-WEIGHT HEADSET
These H.S. 30 phones are the smallest used by the U.S. Air Force. 2500 imp.



using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Supplied free is a small transformer unit with cord and plug which steps impedance up to 4,000Ω. ONLY 15/- P. & P. 2/6

CONVERT TO V.H.F. Within minutes you can extend the frequency of your receiver to cover V.H.F. by using our brand new V.H.F. Converters.

R.F.26. covers 50-65 Mc/s. vernier calibrated tuning. 20/-

R.F.25 covers 40-50 Mc/s. Switched tuning. 8/6. Circuits supplied. P. & P. 3/6 on each.

CRYSTAL DIODES 6/- per doz. P. & P. 1/-

MICROPHONES — BRAND NEW. Throat magnetic 4/6; Throat carbon 3/6; No. 8 carbon with switch 6/6; No. 7 moving coil 6/6. Tannoy power mikes only 8/-

U.S.A. WHIP AERIALS. 12ft. 12/6. P. & P. 2/6

V.H.F. MOBILE AERIAL and base, as used by Faxis, Police, etc.. 7/8. P. & P. 2/6


COSSOR DOUBLE BEAM OSCILLOSCOPE 339. 10-position time base, 6 c.p.s. to 250,000 c.p.s. Amplifier 10 c.p.s. to 2 mill. c.p.s. Used condition but in working order. £22.10.0. Carr. 2/-

PRINTED CIRCUIT KIT
Easily and quickly you can make miniature professional printed circuits. Complete with illustrated manual. 19/6. P. & P. 1/6



EAGLE INSTANT CHECK OFF MULTI-PURPOSE VALVE FILAMENT TESTER VT41

WIRELESS SET NO. 19 MK. II

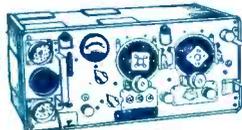

Incorporates "A" Set —TX/RX covering 2-8 Mc/s (37.5-150 metres). "B" Set—VHF TX/RX covering 230-240 Mc/s (1.2-1.3 metres) and intercom amplifier. Complete with 15 valves, 500 microamp check and tuning meter, circuit and instruction book. (American manufacture.) In used condition. 65/- carr. 10/-

MONITOR TYPE 28.

Consists of VCR138. G-SP61, 1-5U4, 1-VU120; 3-EA50. 1 mA meter scaled 100-0-100 volts. Incorporates Y shift. X shift in usecs. Focus, sync. Bias. Input to X plates switched X 20, X 5 and direct, requires only suitable power pack for use as oscilloscope. carr. 10/-



PORTABLE TRANS/RECEIVER SET



ONLY 60/- EACH
P. & P. 4/-

Consisting of trans receiver covering 7.4-9 Mc/s, range up to 10 miles, complete with 5 valves, headphones, microphone, junction box & 8ft. telescopic aerial. Only requires 120 v. & 3 v. dry battery. These magnificent trans/receiver sets (as used by H.M. Forces) are ideal for any application and can be operated with ease.

TWO FOR £6 POST FREE

POCKET MULTIMETER BRAND NEW

2,500 o.p.v. Multi range 630/120/300/120 v. A.C. ditto D.C. 0-1 K. 0-1 megohm: 400 Micro-A., 12 mA., 300 mA. —0 to +64 db 5 ranges: 3in. x 4 1/2in. x 1 1/2in. Large clear dial. Leads supplied. List Price £8.19.6. **OUR PRICE** £4.7.6. Saving you £2.12.0. P. & P. 2/6



MULTI-PURPOSE VALVE FILAMENT TESTER VT41

Pocket size! Battery operated! **GIVES INSTANT CHECK OFF**—

- All Radio Valves.
- All Television Valves.
- Circuit Continuity.
- All TV and Radio Fuses.
- Built-in 7- and 9-pin Valve straighteners.
- Built-in Battery Test.
- All Pilot Lamps.

Finished in black hammer case with gold front panel. Complete with internal batteries and ready for immediate use. **FULLY GUARANTEED.**

30/- P. & P. 2/6

80% of Radio and Television faults are caused by Valves and Fuses which are the first components tested by a Service Engineer when examining a faulty set. Now, with this completely new and revolutionary precision instrument, you can test your own Valves, Fuses, Continuity and a large range of other radio parts. Each component tested is shown "Good" or "Faulty" by a panel light.

CONTROL BOX—B.C. 602-

Complete push-button control box 4 position and on/off with dual coloured indicators for instant channel check.



In black crackle case 5 1/2in. x 3 1/2in. x 1 1/2in. Bargain price, 5/- each. P. & P. 1/6. T. for 8/- P. & P. 2/6.

COLLIS T.C.S. EQUIPMENT.

T.C.S. Transmitter. £9.10.0. carr. 15/- T.C.S. Receiver. £8.10.0. carr. 15/- S.A.E. for further details.

HIFI CO-AX SPEAKERS BRAND NEW—U.S.A. MADE. 12in. Co-axial Speaker. The magnet, Has 3in. tweeter and an electronic crossover network to separate the speaker functions. Frequency response: 40-17,000 cycles. Output 12 watts, impedance 8 ohms. ONLY 160/- 16in. 2 1/2in. tweeter, 10 watts. etc.. 90/- P. & P. 4/- on each.

SIGNAL GENERATOR

Coverage 100 kc/s-100 Mc/s. on fundamentals and 100 Mc/s. to 200 Mc/s. on harmonics. Metal hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated. F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%. ONLY £6.19.6. Carr. 6/-

HAND NEW VARIABLE TRANSFORMERS. Input 230 volts. Output 0-240 volts, 5 amps. Brand new, only £8. Carr. 12/6

MARCONI CR100 RECEIVER 60 kc/s-30 Mc/s. Internal A.C. power supply, crystal and audio filters, variable selectivity. Output for phones and speaker. Fully guaranteed. £18.10.0. Carr. 30/-

ACCUMULATORS. 2 volts, 16 A.H. (unspillable). Ideal for 6 and 12 volts supply, etc. Brand new, Original cartons. Size 7in. x 2in. 5/8 each. P. & P. 1/6. 3 for 15/- P. & P. 3/6. 6 for 27/6. P. & P. 5/-




Callers: 87, Tottenham Court Road, London, W.1.
Mail orders: (Dept. P), 32a, Coptic Street, London, W.C.1
Telephone: MUSEum 9607

FULLY ILLUS. CATALOGUE.
1/3 Post Free.

HARVERSON SURPLUS CO. LTD.

48, Beddington Lane, Croydon, Surrey.

PHONE: THORNTON HEATH 2577.

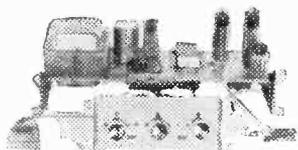

MONAURAL AMPLIFIER

This amplifier as illustrated, made by a leading manufacturer. Mullard Valves—ECC83, EL84 x EL84, EZ80. Bass, Treble and Volume on remote panel. Elegant Knobs.


OUR PRICE **£6. 19. 6.** Plus P. & P. 3/6.



500 MICROAMETER


A 4 1/2" panel mounting 500 Microameter marked in ohms and ideal for building into a multi-range meter.

Price **£2.10.0.** Plus P. & P. 3/6.

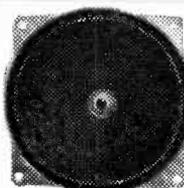

PLESSEY TWEETER

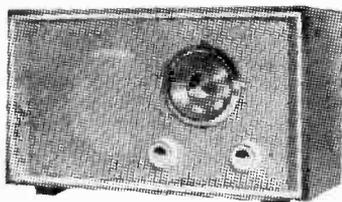This well-known Plessey 3-ohm Tweeter at our amazing price of **10/6.** Tax Paid. Plus P. & P. 1/6.



HARVERSON T.R.F. EASY FOUR KIT

All parts and point-to-point wiring diagram.

Our Price, **£4. 12. 6.**

Plus P. & P. 3/6.

TRANSISTOR by leading manufacturer. First Grade Equivalent OC44. **11/6** each—**6** for **60/-**.

THE WORLD FAMOUS E.M.I. ANGEL TRANSCRIPTION P.U. (Model 17A)

A Pick-up for the connoisseur originally priced at £17.10.0. The last remaining few offered at **£5.10.0.** Plus P. & P. 5/-.




CHANNEL TUNER

12 Channel T.V. Turret Tuner by Clydon. 35 Mc/I.F. PCC84 x PCF80. Band 1—1-5
Band 3—8-11

BRAND NEW. Plus P. & P. **39/6.**

F.M. TUNER HEAD

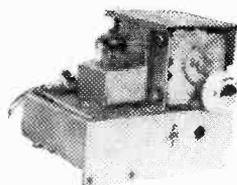As illustrated — uses ECC83. Less Valve at **14/6.** Plus P. & P. 1/6. Regret no diagrams available.



THIS MONTH'S OFFER

Small generator or motor. 12 v. with reduction gear. Has dozens of applications, ideal for the model maker. Don't miss this. **12/6** each. Plus P. & P. 2/-.

Twin Padded, Grey, with Maroon Tracer Mains Lead. Usually 10d. per yard. Our Price **25/-** per 100-yard coil.

Printed circuit pots in banks of two or three :

400 K. x 2 Meg., **5/-** each. 2 Meg. x 200 K. x 2 Meg., **7/-** each.

60 Milliamp Chokes at per **6/-** each.

AMAZING SCOOP—Cossor 10" Tubes. 108 K. New and Boxed. **21/-** each. Plus P. & P. 12/6.

Few Only—Taylor Windsor Circuit Analysers. Reconditioned. A Snip at **£12.0.0.** Plus P. & P. 5/6.

Woden P.P. O.P. Transformers. 20 watt. 4,500 ohm load. A bargain at **27/6.**

Taylor Windsor 240A Pattern Generator. Not new but perfect. **£8.10.0** each. Plus P. & P. and Insurance 10/-.

12 Assorted Pots. Wire wound and carbon. Switched and unswitched—all useful sizes at **21/-** the dozen. Plus P. & P. 1/-.

Taylor Signal Generators. Type 65A or B.

Not New—but Perfect. **£8.10.0** each. Plus P. & P. and Insurance 10/-.

Few only, **12" 3 ohm R.A. 8120P Mk. 2** at **32/6.** Plus P. & P. 2/- . Midget 2 gang .0005 at **4/-** each. Plus P. & P. 10d.

IF YOU DO NOT SEE WHAT YOU WANT ON THIS PAGE—WE WILL GET IT FOR YOU

Write for our list of small parts and accessories for the Constructor. Trade willingly supplied.

R.S.C. HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN 1 HOUR. The Recorder incorporates the Latest Collaro Mark IV Tape Transcriber listed £25. The Linear LT45 High Quality Tape Amplifier listed £12.12.0. High Flux P.M. Speaker listed 30/-, empty Tape Spool, a Reel of Best Quality Tape listed 22/6. and a Handsome Portable carrying Cabinet finished in veneered walnut, size 18in. x 13in. x 9in. high, listed £4 10/0. and circuit. Total cost if purchased individually approx. £45. Performance equal to units in the £60-£80 class. Send S.A.E. for leaflet.

29 1/2 GNS. H.P. TERMS. Deposit 3 gns. and 12 monthly payments 53/9. Cash price if settled in 9 mths. 17/6


HI-FI 10 WATT AMPLIFIERS

Slightly store soiled but guaranteed unused and in perfect order. Fitted Mullard valves. Dual inputs for "mike" and gram, etc. Bass and Treble Controls. High sensitivity and quality For 200-250 v. A.C. mains.

£5-19-9 Carr 7/6

R.S.C. A8 HIGH FIDELITY 12 WATT AMPLIFIER

Ultra Linear Push-Pull Amplifier with "Built-in" Tone Control. Pre-amp stages, high sensitivity, includes 5 valves (807 outputs). High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut."** Frequency response ±3 db. 20-30,000 c/c.s. Six negative feedback loops. Hum level 71 db. down. **ONLY 70 millivolts INPUT** required for **FULL OUTPUT.** Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

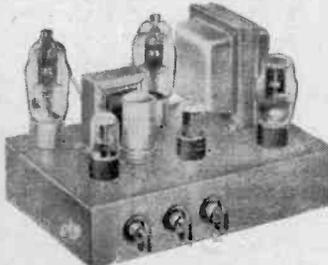

For STANDING or LONG - PLAYING RECORDS. For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc. OUTPUT SOCKET** with plug provides 300 v. 30 mA. and 6.3 v. 1.5a. For supply of a **RADIO FEEDER UNIT.** Size approx. 12-9-7in. For A.C. mains 200-230-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value. at £715/- or factory built 45/- extra. Carriage 10/-.

£7-15-0

carrying handles can be supplied for 18/9. Additional input sockets, with appropriate Vol. control so that two different inputs such as Gram and 'Mike' or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months.

TERMS on assembled two input model : **DEPOSIT 18/9** and 12 monthly payments 18/9.

HIGH FIDELITY MICROPHONES and SPEAKERS in stock. Keen cash prices or credit terms if supplied with amplifier.

STAAR GALAXY 4-SPEED MIXER AUTO-CHANGERS
Brand new, cartoned. Turnover sapphire styl. Many exclusive features. Unique design motor virtually free from rumble. For 200-250 v. A.C. mains. Only £5.19.6.

PORTABLE CABINETS
Full range of attractive designs from **15/9**

SPECIAL OFFER. Two tone Portable cabinet, Gram amplifier, Staar, Changer and 7in. x 4in. P.M. Speaker. 10 gns. Carr. 10/- or with B.S.R. UA8. 12 gns.

THE SKYFOUR T.R.F. RECEIVER. A design of a 3-valve Long and Medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Power pentode output. Valve line-up 6K7, 6P61, 6V6G. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-Point wiring diagrams, instructions and parts list, 2/9. Maximum building costs £4.19.6, inc. attractive Walnut veneered wood cabinet 12in. x 6in. x 5in.

R.S.C. PORTABLE TAPE RECORDER

A completely assembled unit in attractive two-tone rexine covered carrying case. Acompletely assembled unit in attractive two-tone rexine covered carrying case. Acompletely assembled unit in attractive two-tone rexine covered carrying case. Acompletely assembled unit in attractive two-tone rexine covered carrying case.

Excellent frequency response. Auto-erase. Fast rewind. Takes up to 5 1/2 in. tape spools. High Flux speaker. 3 watts output. Inputs for Radio/Gram and 'Mike'. For 230v. 250 v. 50 c.p.s. A.C. mains. Sensational value! Price. Including 'Mike' Reel of best quality tape and empty spool. Usual 12 months' guarantee. H.P. Terms: Deposit 44/- and 12 monthly payments of 33/4.

19 GNS. Carr. 10/6

PICK-UP ARMS complete with Hi-Fi turnover crystal head. Acos GP54. Limited number brand new, perfect, at approx. half price. Only 29/11.

ACOS CRYSTAL MICROPHONES. Mic 40 hand or desk. Listed 45/- Only 29/9. Type 33-1, hand or desk. Listed 45/- Only 29/9. Brand new, cartoned. 35/9. 39-1 Stick type, list price 5 gns. Brand new 39/6.

EXTENSION SPEAKERS
Ready for use in walnut veneered cabinet.
6in. 2-3 ohms. 29/11.
3in. 2-3 ohms. 35/9.
10in. 2-3 ohms. 58/9.
Very limited number.



RECORDING TAPE AT BARGAIN PRICES. Leading makes. Brand New. P.V.C. based. 3in., 150ft., 5/11 225ft., 7/9 5in., 600ft., 15/11 850ft., 22/6 7in., 1700ft., 35/-.

EMPTY SPOOLS. (Plastic.) 3in., 2/9 5in., 2/11 7in., 3/9.

COSSOR VHF/FM RADIO RECEIVER KITS

Including 6 valves. Printed Circuit and Goodman's 10" x 6" Elliptical Speaker. Pre-aligned I.F.T.'s Made to retail at 15 GNS. Limited number at **£8-19-6**

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BML All-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-230 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams. 39/9. or ready to use. 46/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120v. 90 v. and 60 v., 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/9. or ready for use. 33/6.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c.p.s. Screened **TOP SHROUDED DROP THROUGH**

250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 3 a. ... 17/9
350-0-350 v. 80 mA. 6.3 v. 2 a. 5 v. 3 a. ... 19/9
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 25/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 25/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 25/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 4 a. C.T. 0-4-5 v. 3 a. ... 25/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. ... 29/9

FULLY SHROUDED UPRIGHT

250-0-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. ... 17/9
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 26/9
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 28/9
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. ... 28/9
300-0-300 v. 130 mA. 6.3 v. 4 a. 6.3 v. 1 a. ... 28/9
for Mullard 510 Amplifier ... 35/9
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. ... 35/9
425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a. Suitable Williamson Amplifier, etc. ... 49/9

FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-1-3.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 3.3 v. 5 a. 17/6.

OUTPUT TRANSFORMERS

Midget Battery Pentode 66:1 for 3S4, etc. ... 3/9
Small Pentode, 5000Ω to 3Ω ... 3/9
Small Pentode 778,000Ω to 3Ω ... 3/9
Standard Pentode 5,000Ω to 3Ω ... 5/6
Standard Pentode, 778,000Ω to 3Ω ... 5/6
10300 to 3Ω ... 5/6
Push-Pull 10-12 watts 6V6 to 3n or 15Ω ... 18/9
Push-Pull 10-12 watts to match 6V6 Co 3-5-9 or 15Ω ... 19/9
Push-Pull E184 to 3 or 15Ω ... 19/9
Push-Pull 15-18 watts 6L6, KT66 ... 22/9
Push-Pull for Mullard 510 Ultra Linear ... 29/9
Push-Pull 20 watts, sectionally wound 6L6, KT66, etc., to 3 to 15Ω ... 47/9

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s.
120 v. 40 mA. 5-0-5 v. 1 a. ... 15/9
90 v. 15 mA. 4-0-4 v. 500 mA. ... 9/9

SMOOTHING CHOKES

130 mA. 7-10 H 250 ohms ... 11/9
100 mA. 10 H 200 ohms ... 8/9
80 mA. 10 H 350 ohms ... 5/9
60 mA. 10 H 400 ohms ... 4/11

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries :
0-9-15 v. 11 a. 12/9 ; 0-9-15 v. 8 a. 16/9 ;
0-9-15 v. 5 a. 19/9 ; 0-9-15 v. 6 a. 23/9.

AUTO TRANSFORMERS. 50 watt 0-110/115-230 250 v. 8/11 each.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER with high fidelity Studio pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c.p.s. A.C. mains. Our price £7.11.8. Carr. 5/9.

COLLARO 4-SPEED SINGLE PLAYER UNITS. Types AC/4564 with turnover crystal head. £6. .6. Carr. 4/6.

R.S.C. A12 STEREOGRAPHIC AMPLIFIER KIT

A complete set of parts to construct a Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied. Only good quality components and latest high grade valves used. Exceptionally realistic reproduction can be obtained at ample volume for the home, as can be demonstrated in typical surroundings at our County Arcade premises. A really sensational offer.

£3-19-6

STEREO EQUIPMENT OFFER.
Comprising A12 Kit. 2 matched 8in. L/Speakers, and Acos T/O Stereo head with diamond stylus suitable most pick-ups.

£6-19-6
Carr. 7/6

BUILD A TRANSISTORISED RECORD PLAYER to operate from 6 v. Dry Batteries. Total cost of parts Only £7-19-6
Unit is housed in attractive portable cabinet and will play standard 7in. 45 r.p.m. records at ample output level. All parts available separately, i.e. Garrard Player Unit with pick-up, £3.19.6. Portable Cabinet 29/6.

R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response +3 db. 30-30,000 c/c.s. A specially designed sectionally wound ultra linear output transformer used with 807 output valves. All components are chosen for reliability. Six valves are used. EF86, EF95, ECC83, 807, 807, GZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT. An extra inrad with associated vol. control is provided so that two separate inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover for A8 can be supplied for 18/9. The amplifier can be supplied, factory built with 12 months' guarantee, for £13.19.6. TERMS: DEPOSIT 24/9 and 12 monthly payments of 24/9.

11 GNS.

Carr. 10/-

LINEAR 'DIATONIC' 10-14 WATT HIGH FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250 v. A.C. mains. Valves ECC83, ECC83, EL84, EL84, E2B1. Self-contained Pre-amp Tone Control stage. Separate Bass and Treble controls. Independent 'Mike' and Gram input sockets. Outputs for 3 and 15 ohm speakers. Only 12 GNS. or Deposit 22/3 plus 10/- carr. and 12 monthly payments of 22/3. Send S.A.E. for leaflet.

LINEAR L50 50 WATT P.A. AMPLIFIER. High quality and sensitivity. 19 GNS. Send S.A.E. for leaflet.

GARRARD 4-SPEED AUTO-CHANGERS. Type RC120H. Very limited number at only £10.19.6. Carr. 5/6.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

For 200/250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5 amplifier. Complete Kit with diagrams. £3.15.0. Carr. 3/6.

R.S.C. BRADFORD, MANCHESTER and LEEDS
(Leeds) Ltd.

LINEAR L45 MINIATURE 4.5 WATT QUALITY AMPLIFIER. Suitable for use with any record playing unit, and most microphones. Negative feed-back 12 db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 6.5-5 1/2 in. high. Guaranteed for 12 months. Only £5/19/6. Send S.A.E. for illustrated leaflet. Terms. Deposit 22/6 and 5 monthly payments of 22/6.

R.S.C. 4.5 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the best high fidelity pick-up leads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 70db. down, 15 db. of negative feedback is used. L.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with blue hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4/15/-, or assembled ready for use 25/- extra, plus 3/6 carr. or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

R.S.C. PORTABLE GUITAR AMPLIFIERS


Junior 5 watts High Quality output. Separate Bass and Treble 'Cut' and 'Boost' controls. Sensitivity 15 m.v.. Twin inputs. High Flux 8in. Loudspeaker 'built-in'. Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in satin walnut, and fitted carrying handle. H.P. Terms. Deposit £1 and 9 monthly payments of 2/.

£8-19-6
Carr. 7/6

Senior 10 watts High Fidelity output. Separate Bass and Treble 'Cut' and 'Boost' controls. Individually controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a high Flux 12 in. for Bass notes and a 7 x 4 in. elliptical for Treble. Cabinet is well made and finished satin walnut. Size approx. 18 x 18 x 8 in. H.P. Terms. Deposit £3/6 and 12 monthly payments of 23/6. Both models for 200-250 v. A.C. mains. Carr. 10/-

15 GNS.

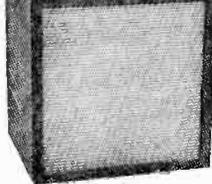12in. 10 WATT HIGH QUALITY LOUD-SPEAKERS IN POLISHED WALNUT FINISHED CABINET



Gauge 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6. Carr. 3/- Terms: Deposit 11/- and 9 monthly payments of 11/-


12 in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS. Size 18 x 18 x 8 in. Finish as above. Terms: Deposit 13/10 and 12 monthly payments of 13/10. Only £7.19.6. Carr. 8/6.

PHILIPS CONCENTRIC (Dual Cone) 10in. P.M. SPEAKERS. 3-5 ohms. Limited number at only 29/9.

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 extra under £2: 2/9 extra under £5. Open 9 to 6: Weds. until 1 p.m. Trade supplied. S.A.E. with all enquiries.

AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT

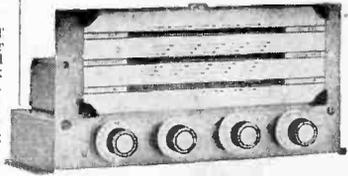For 200-250 v. Mains. Long wave, Medium, F.M. and Gram. Complete with 8 B.V.A. valves. Guaranteed 12 months. Only 22 GNS. Or Deposit £2.12.0 and 9 monthly payments of £2.12.0.



PLESSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER (12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke condensers etc.) providing extremely ordinary realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price only £5/17/6.

Hi-Fi CRYSTAL PICK-UP HEADS. (Turnover type with sapphire stylus). HCP59. Standard replacement for Garrard and B.S.R. B.S.R. Ful-L, Garrard GC2. 19/9.

POWER PACK KIT. Output 250 v. 50 mA. fully smoothed and 6.3 v. 1.5 a. Consisting of Mains Trans., Selenium Rectifier, Smoothing Choke, Double Electrolytic Condenser. Chassis 6in. x 3in. and Circuit. Only 18/9.

P.M. SPEAKERS. 2-3 ohm. 2in. Perdio 23/9. 5in. 17/9. 6in. 16/9. 8in. 19/9. 8 x 5in. 25/9. 10in. 26/9. 10 x 6in. 29/9. 12in. 29/11. 10in. W.B. Stentorian. 3 or 15 ohms type HP1012 10 watts. Hi-fidelity type. Recommended for use with our A8 Amplifier, £4.10.9. 12in. Plessey 3 ohms 10 watts (12,000 lines). 59/6.

TWEETERS. Plessey 3 ohms 19/9.

GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. 50 c.p.s. A.C. mains. Over-all size 1 1/2 in. x 2 1/2 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 59/6.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner unit (specially suitable for use with any of our Amplifiers). Delayed A.V.C. employed. The W.Ch. Sw. incorporates Gram position. Controls are Tuning, W.Ch. and Vol. only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6 in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustration. 2/6. Total building cost £4/15/-. For descriptive leaflet send S.A.E.

E.M.I. 4-SPEED SINGLE RECORD PLAYER UNITS with turn-over crystal head for Stereo and Monaural. Only £6 19.9. carr. 4/6.

Mail Orders to 29-31 Moorfield Rd., Leeds 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1, and 8-10 Brown St. (Market St.), Manchester 2, or 56, Morley Street, (Next to Majestic Ballroom) Bradford.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

ANY ORDER INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA.																				
0A2	17/6	6C8	12/6	6X4	6/6	198B6G	7475	7/6	EABC80	9/-	EL41	9/-	LN152	10/6	Q5150/15	10/6	UCH81	9/6		
0B2	17/6	6C9	12/6	6X5GT	6/-	23/3	9002	5/6	EAC91	7/6	EL42	13/11	LN309	11/6		10/6	UCL82	11/6		
0Z4	6/-	6C10	10/6	6/30L2	10/-	19H1	10/-	AC/PEN	9/6	EL43	9/6	EL82	13/11	MH4(C)	7/-	R12	9/6	UCL83	9/6	
1A3	3/-	6CD6G	36/6	7A7	12/6	20D1	15/3	5-pin	23/3	EB34	2/6	EL84	8/6	MHL4	7/6	R18	14/-	UF41	9/6	
1A5	6/-	6CH6	12/6	786	21/3	20F2	26/6	7-pin	15/-	EB41	8/6	EL85	13/11	MHLD6	12/6	R19	19/11	UF42	12/6	
1A7	15/-	6D3	19/11	787	8/6	20L1	26/6	AC2PEN/		EB91	5/6	EL91	5/-	ML4	12/6	S130	15/-	UF80	10/6	
1C5	12/6	6D6	6/6	7C5	8/-	20P1	26/6	DD	26/6	EBC3	23/3	EL95	10/6	MU14	9/-	SD6	12/-	UF85	10/6	
1D5	9/-	6E5	12/6	7C6	8/-	20P3	23/3	AC5PEN		EBC33	7/-	EM34	10/-	MX40	15/-	SP4(7)	15/-	UF86	17/11	
1D6	13/6	6F1	26/6	7D8	23/3	20P5	23/3			EBC41	8/6	EM71	23/3	N37	19/11	SP41	3/6	UF89	9/-	
1HS5T	11/-	6F6G	7/-	7H7	8/-	25A6G	11/-	AC6PEN	7/6	EBC81	8/-	EM80	9/6	N78	19/11	SP42	12/6	UL41	9/-	
1L4	6/-	6F6GTM	8/-	7R7	12/6	25L6GT	10/-	AC/5G	23/3	EBF80	10/-	EM81	9/6	N108	19/11	SP61	3/6	UL44	26/6	
1LD5	5/-	6F8	12/6	757	10/6	25U4	16/7	AC/TP	3/3	EBF83	13/11	EM84	10/6	N308	20/7	SU25	26/6	UL46	14/6	
1LNS	5/-	6F11	17/3	757	8/6	25Y5	10/6	AC/VP1	15/-	EBF89	9/6	EN31	37/-	N339	29/10	SU61	9/6	UL84	8/6	
1NS5T	11/-	6F12	5/6	7Y4	8/-	25Y5G	10/6	AC/VP2	23/3	EEL21	23/3	EY51	9/6	P61	3/6	T4	23/3	UM4	17/3	
1R5	7/6	6F13	11/6	7Z4	18/7	25Z4G	9/6	ATP4	5/-	EB121	23/3	EY81	9/6	PAB80		TDD4	24/7	UM80	15/3	
1S4	9/-	6F14	26/6	8D2	3/6	25Z6G	10/-	AZ1	18/7	EC52	5/6	EY84	14/7	13/11	TH4B	15/-	URIC	9/6		
1S5	7/6	6F15	15/3	8D3	5/6	25Z6G	10/-	AZ31	10/-	EC54	6/-	EY86	10/-	PCC84	8/-	TH41	26/6	UU6	19/11	
1T4	6/-	6F16	9/6	9BW6	15/3	25Z6GT		AZ41	13/11	EC70	12/6	EZ35	6/-	PCC85	9/6	TH233	3/3	UU7	16/7	
1U5	10/-	6F17	12/6	9D2	4/-	16/7		B36	24/7	EC92	13/3	EZ40	7/6	PCC88	23/11	TH2321	20/-	UU8	26/6	
2A7	10/6	6F32	10/6	10C1	12/-	27SU	19/11	BL63	7/6	ECC32	10/6	EZ41	7/6	PCC89	14/6	TP22	15/-	UU9	7/6	
2P	26/6	6F33	7/6	10C2	26/6	28D7	7/-	CI	12/6	ECC33	8/6	EZ80	7/6	PCF80	8/-	TP25	19/6	UY1N	18/7	
2X2	4/6	6G6	6/6	10D2	12/6	30C1	8/-	CIC	12/6	ECC34	24/7	EZ81	7/-	PCF82	11/6	TP2620	33/2	UY21	16/6	
3A4	7/-	6H6GTTG	3/-	10F1	17/6	30F5	7/-	CLB1	26/6	ECC35	8/6	FC2A	24/7	PCL82	12/6	TY86F	13/3	UY41	7/6	
3A5	10/6	6H6GTM	3/-	10F9	10/6	30FL1	10/-	CLB31	23/3	ECC40	23/3	FC4	15/-	PCL83	11/6	TY12/14	12/3	UY85	7/-	
3B7	12/6	6I5G	5/-	10LD3	8/6	30L1	8/-	CCH35	23/3	ECC81	8/-	FC13	26/6	PCL84	12/6	U16	12/-	VM54L	23/3	
3D6	5/-	6I5GTTG	5/6	10LD11		30L15	14/-	CK506	6/6	ECC82	7/6	FC13C	26/6	PEN4A	23/3	U18/20	9/-	VP2(7)	12/6	
3Q4	7/6	6I5GTM	6/-		15/11	30P12	8/-	CL33	19/3	ECC83	8/-	FW4/500		PEN4B	26/6	U22	8/-	VP4(7)	15/-	
3Q5GT	9/6	6I6	5/6	10P13	15/6	30P16	8/-	CV63	10/6	ECC84	9/6	9/-		PEN4DD	U24	29/10	VP2B	14/6		
3S4	7/6	6I7G	6/-	10P14	19/3	30P11	11/6	CV271	10/6	ECC85	8/6	FW4/800		U25	26/6	U25	17/11	VP4B	23/3	
3V4	7/6	6I7GT	10/6	11D3	24/7	31	7/6	CV428	30/-	ECC88	23/11	9/-		PEN25	19/11	U26	10/-	VP13C	7/6	
5R4Y	17/6	6K6GT	8/-	12A6	6/6	33A/158M		CY1	18/7	ECC91	5/6	GZ30	10/6	PEN36C	U31		9/6	VP23	6/6	
5U4G	8/-	6K7G	5/-	12AC6	15/3	30/-		CY31	16/7	ECCF80	11/6	GZ32	12/-		10/6	U33	26/6	VP41	6/6	
5V4G	11/-	6K7GT	6/-	12AD6	17/3	35/51	12/6	DI	3/-	ECCF82	10/6	GZ34	14/-	PEN40DD	U35		26/6	VR105/30	3/6	
5Y3G	8/-	6K8G	8/-	12AE6	13/11	35A5	21/3	D15	10/6	ECH3	26/6	H30	5/-		25/-	U37	26/6		9/-	
5Y3GT	7/6	5K8GTTG	12A7H	8/-	35L6GT	9/6	D63	5/-	ECH21	23/3	H63	12/6	PEN44	26/6	U43	9/6	VR150/30			
5Z3	12/6	5	12/6	12AH8	12/6	35W4	7/6	D77	5/-	ECH35	9/6	HABC80		PEN45	19/6	U45	9/6		9/-	
5Z4G	10/6	6K25	19/11	12A7E	7/6	35Z3	10/6	DAC32	11/-	ECH42	10/6	13/6		PEN45DD	U50		8/-	VT61A	5/-	
5Z4GT	12/6	6L1	23/3	12A77	8/-	35Z4	6/6	DAP91	7/6	ECH81	9/-	HL23	10/6		26/6	U52	8/6	VT501	5/-	
6A7	26/6	6L6G	9/6	12AU6	23/3	35Z5GT	9/-	DAP96	9/-	ECH83	13/11	HL23DD		PEN46	7/6	U54	19/11	W61M	26/6	
6A8	10/6	6L6M	12/6	12AV7	7/6	41MTL	8/-	DD41	13/11	ECL80	10/6	17/3		PEN383	23/3	U76	6/6	W76	6/6	
6A87	8/-	6L7GT	12/6	12AV6	12/7	42	23/3	DF33	11/-	ECL82	10/6	HL41	12/6	PEN453DD	U78		16/7	W81M	6/-	
6A88	10/6	6L18	13/-	12AX7	8/-	43	12/6	DF66	15/-	ECL83	19/3	HL41DD			33/2	U107	16/7	W107	10/6	
6AC7	6/6	6L19	23/3	12BA6	8/-	50C5	12/6	DF70	15/-	EF9	23/3	19/3		PEN/DD	U191		16/7	W729	18/7	
6AG5	6/6	6LD3	8/6	12BE6	10/-	50CDS6G		DF91	6/-	EF22	14/-	HL42DD		4020	33/2	U201	16/7	X24M	24/7	
6AK5	8/-	6LD20	15/11	12BH7	21/3	36/6		DF96	9/-	EF36	6/-	19/3		PL33	19/3	U251	14/-	X31	26/6	
6AL5	5/6	6N7	8/-	12E1	30/-	50L6GT	9/6	DF97	9/-	EF37A	8/-	HN309	24/7	PL36	14/-	U281	19/11	X41	15/6	
6AM6	5/6	6P1	19/3	12J5GT	4/6	53KU	19/11	DH30	15/6	EF39	5/6	HVR2	20/-	PL38	26/6	U282	22/7	X61(C)	12/6	
6AQ5	8/6	6P25	12/6	12J7GT	10/6	72	4/6	DH63	8/-	EF41	8/-	15/-	HVR2A	6/-	PL31	12/6	U301	23/3	X61M	26/6
6AT6	8/6	6P28	26/6	12K5	17/11	75	24/7	DH76(Met)	17/6	EF41	9/6	KF35	8/-	PLB2	8/-	U329	14/6	X63	10/6	
6AU6	10/6	6Q7G	8/-	12K7GT	6/6	77	8/6	DH76	17/6	EF42	11/6	KK32	21/11	PLB3	9/-	U339	16/7	X65	12/6	
6AV6	12/7	6Q7GT	11/-	12K8GT	14/6	80	9/-	DH77	8/6	EF50(A)	5/-	KL35	8/6	PLB4	12/8	U403	16/7	X66	12/6	
6B7	10/6	6R7G	10/-	12Q7GT	6/6	80	9/-	DH77	8/6	EF50(E)	5/-	KLL32	24/7	PLB20	18/7	U404	8/6	X76M	14/-	
6B8G	4/6	6SA7GT	8/6	12S7	8/6	83	15/-	DH101	28/6	EF54	5/-	KT2	5/-	PM2B	12/6	U801	29/10	X78	21/3	
6B8GT	5/-	6SC7	10/6	12SC7	8/6	83V	12/6	DH107	13/11	EF73	10/6	KT33C	10/-	PM12	6/6	U4020	16/7	X79	21/3	
6BA6	7/6	6SG7GT	8/-	12S7G	8/6	85A2	15/-	DK32	15/-	EF80	7/6	KT36	29/10	PM12M	6/6	UABC80	9/-	X101	33/2	
6BE6	7/6	6SH7GT	8/-	12SH7	8/6	150B2	15/-	DK40	21/3	EF85	7/6	KT41	26/6	PM24M	21/3	UAF42	9/6	X109	17/3	
6BG6G	23/3	6S1GT	8/-	12S17	8/6	185B2	33/2	DK91	7/6	EF86	12/6	KT44	15/-	PX4	10/6	UB41	12/-	XID(1.5)	6/6	
6BH6	9/-	6SK7GT	8/-	12SK7	8/6	185B4	33/2	DK92	10/6	EF89	9/-	KT61	12/6	PX25	16/8	UBC41	8/6	XFG1	18/-	
6BH6	7/6	6SL7GT	8/-	12S7G	12/6	304	10/6	DK96	9/-	EF91	5/6	KT63	7/-	PY31	16/7	UBC81	11/4	XFY12	9/6	
6BQ7A	15/-	6SN7GT	6/6	12SR7	8/6	305	10/6	DL33	9/5	EF92	5/5	KT66	15/-	PY32	17/11	UBF80	9/-	XFY34	17/6	
6BR7	23/3	6SG7GT	9/-	12Y4	10/6	40ZPenA		DL66	15/-	EF97	13/3	KT88	22/6	PY80	7/6	UBF89	9/6	XH(1.5)	6/6	
6BW6	10/6	6SS7GT	8/-	14B6	19/3	23/3		DL68	15/-	EF98	13/3	KTW61	8/-	PY81	9/-	UBLL21	23/3	XSG(1.5)	5/6	
6BW7	7/6	6U4GT	12/6	14H7	23/3	307	7/6	DL92	7/6	EFK32	8/6	KTW62	8/-	PY82	7/-	UCC84	14/7		6/6	
6BX6	7/6	6U5G	7/6	14S7	27/10	956	3/-	DL94	7/6	EL32	5/6	KTW63	8/-	PY83	9/5	UCC85	9/-	Y63	7/6	
6C4	7/6	6U7G	8/6	15D1	26/6	1821	16/7	DL96	9/-	EL33	12/6	KTZ41	8/-	PB30	19/11	UCCF80	16/7	Z63	10/6	
6C5G	6/6	6V6G	7/-	18	23/3	5763	12/6	DM70	7/6	EL34	15/-	KTZ63	10/6	QP21	7/-	UCH21	23/3	Z66	20/6	
6C6	6/6	6V6GTTG	8/-	19A05	10/6	7193	5/-	EA50	2/-	EL38	26/6	L63	6/-	QP25	15/-	UCH42	9/6	Z77	5/6	

FULL RANGE OF TRANSISTORS AND GERMANIUM DIODES IN STOCK. TECHNICAL DATA AND PRICES FREE ON RECEIPT OF SELF-ADDRESSED ENVELOPE.

NEW METAL RECTIFIERS—FULLY GUARANTEED				Technical leaflet on Metal Rectifiers free on receipt of S.A.E.							
DRM-1B	15/4	RM-1	7/-	VX3	3/6	14A100	27/-	14RA 1-2-8-2	17/6	16RE 2-1-8-1	8/6
DRM-2B	16/2	RM-2	9/-	VX4	3/6	14A124	28/-	14RA 1-2-8-3	21/-	1BRA 1-1-8-1	4/6

D.C. OSCILLOSCOPE

A.C. MAINS 200-250 VOLTS



SIMPLIFIED SERVICING PROBLEMS WHEN USING THE 'TESTGEAR' SCOPE
3in. D.C. OSCILLOSCOPE

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transients for operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line O/P Transformers, etc.; Provision for external X 1/10 and CRT Brightness Modulation. Size 10in. high, 6 1/2in. wide, 8in. deep. Wgt. 1 1/2 lbs. £15.15.0. plus P. & P. 7/6, or 30/- deposit, plus P. & P. 7/6 and 12 monthly payments of 26/6.

FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.


Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transients for operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line O/P Transformers, etc.; Provision for external X 1/10 and CRT Brightness Modulation. Size 10in. high, 6 1/2in. wide, 8in. deep. Wgt. 1 1/2 lbs. £15.15.0. plus P. & P. 7/6, or 30/- deposit, plus P. & P. 7/6 and 12 monthly payments of 26/6.

8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUSPEAKER

A.C. mains 200-250 v. Size 10 1/2in. x 6 1/2in. x 2 1/2in. Incorporating 6 valves, H.F. pen. 2 triodes. 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feedback. Two inputs, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 K c/s.

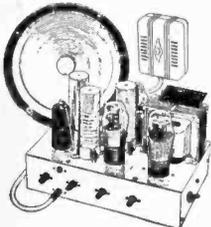Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as Guitars, etc. £4.19.6 Plus P. & P. 7/6. Or 20/- deposit plus P. & P. 7/6, and 4 monthly payments of 23/-.




2-TRANSISTOR POCKET RADIO

Plus Germanium diode, fully tuneable over medium and long waves. Size 3 1/2in. x 4 1/2in. x 1 1/2in. Complete set of components including case, 2 transistors and earpiece (less batteries).

19/6 Plus P. & P. 1/6.

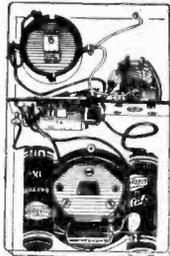Point to point wiring diagram 1/6, free with kit.




PUSH-FULL OUTPUT STAGE

Inclusive of transistors with input and output transformers to match 2 ohm speech coil, suitable for use with the above kit. Complete kit of parts including transistors.

19/6 Plus P. & P. 1/6.

Point to point wiring diagram 1/6, free with kit.

A.C./D.C. POCKET MULTI-METER KIT

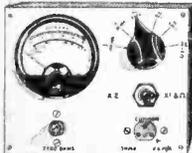


Comprising 2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus P. & P. 1/6. Built and tested 7/6 extra.

Point to point wiring diagram 1/-, free with kit.

SIGNAL GENERATORS

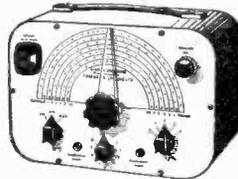


Cash £6.19.6 or 25/- deposit and 6 monthly payments of 21/6. Post and Packing 5/- extra.

Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2in. x 5 1/2in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 cps. to a depth of 30%; Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magnetic eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing, 5/-.

Coverage 120 Kc/s-84 Mc/s. Metal case 16in. x 6 1/2in. x 4 1/2in. Size of scale, 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 cps. to a depth of 30%, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.D. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

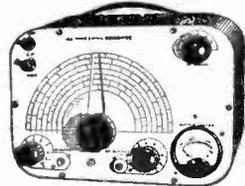

B.S.R. MONARCH UA8 WITH FULL-FI HEAD




4-speed plays 10 records 12in. 10in or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12 1/2in. x 10 1/2in. Space required above baseboard 4 1/2in., below baseboard 2 1/2in. Fitted with Full-Fi turnover crystal head.

£6.19.6 Plus 5/- Postage & Packing.

With Stereo Head, £7.19.6, plus 5/- P. & P.

CHANNEL TUNER

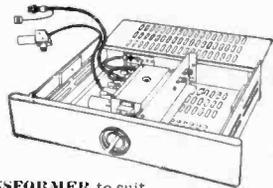Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with PCC84 and PCF80 valves (in series) I.F. 16-19 or 33-38. Also can be modified as an aerial converter. (instructions supplied).



Complete with knobs.

22/6 Plus 3/6 P. & P.

HEATER TRANSFORMER to suit the above. 200-250 v., 6/- Plus 1/6 P. & P.

MAINS TRANSFORMERS

All with tapped primaries. 200-250 volts. 0-160, 180, 200 v., 60 ma., 6.3 v. 2 amps. 10/6. 320-0-320 v. 75 ma., 6.3 v., 2.5 amp., 5 v., 2 amp., 10/6. 280-0-280. 80 ma., 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. Postage and packing on the above 3/-.

RADIO CHASSIS

A.C. MAINS 200/250 v. Medium & Long Wave Superhet. 4 valve and rectifier. Complete with 8in. P.M. speaker. Valve line-up 6K8, 6K7, 6Q7, EL32 and rectifier. These have been used but fully serviced with new Electrolytics and valves. FULLY GUARANTEED. 42/6 Plus 7/6 P. & P.

F.M. TUNER UNIT

Permeability tuned, by famous German Manufacturer. Coverage 88-100 Mc/s. Complete with ECC85. Plus 25/- P. & P. 1/6. Size 4in. x 2in. x 2in. Circuit diagram 1/-, free with unit. 10.7 Mc/s I.F. and Discriminator Coil, 2/6 pair.

RADIO & T.V. COMPONENTS (Acton) LTD.

23 HIGH STREET, ACTON, LONDON, W.3.


All enquiries S.A.E.

Goods not dispatched outside U.K.

COMPLETE V.H.F./A.M. RADIO FOR

Brand new set, in superb walnut cabinet (size 19" x 8 1/2" x 14 1/2" high). Covering 80-100 Mc/s. 16-49 M., 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tapings. Ferrite rod aerial for A.M. Controls: volume on/off tone, tuning, w/change, Gram. and ext. speaker position provided. Fully guaranteed. Post and packing 5/- extra.

£12.12.0

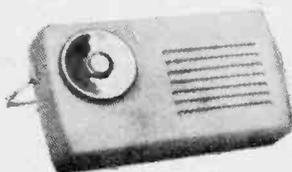

TRANSISTOR KIT


A six Transistor pocket radio, can be built for

£9.19.6

plus 3/6 post. Full medium and long wave superhet. Printed circuit construction, using latest miniature components, 2 1/2" moving coil speaker, Ferrite Aerial. Choice of an attractive plastic cabinet in Cream, Blue or Red. Complete easy-to-build instruction book included. All Parts Sold Separately.

AMPLIFIER AND CABINET

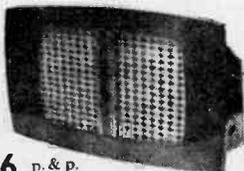3-watt Amplifier, using an ECL82 Valve and Metal Rectifier, housed in a modern attractive styled walnut cabinet with 5" P/M Speaker and on/off and tone controls.



£4.12.6 p. & p. 3/6.

AUTO-CHANGERS BRAND NEW OFFER

COLLARO 4-SPEED AUTO-CHANGERS


Incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus. Plus 3/6 p. & p.

OUR PRICE

£7.9.6


COSSOR MELODY MINOR MODEL 565

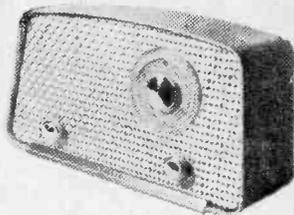A transportable Model of Ultra Lightweight design for use on 200/250 v. Mains D.C. or A.C. 40/100 c/s. Using 4 valves UCH81, UBF89, UY85, UCL82 and Internal Ferrite Aerial.



LIST PRICE 14 1/2 gns.

OUR PRICE £8.17.6
p. & p. 2/6

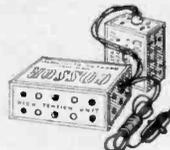

AMPLIFIER KIT

This is the famous Cossor 562K, 3-watt Audio Amplifier Kit, using 1 EF86, 6BQ5 and 5V4 valves, a 10" x 6" elliptical speaker and a 4" round speaker. This kit can be easily assembled to provide a compact and versatile printed circuit amplifier suitable for operation from radio microphone gramophone inputs. The circuit design includes negative feed-back and high performance loudspeakers, an easy-to-build instruction pamphlet. Original list price £9.15.0.

OUR PRICE £5.19.6 P. & P. 2/6.

Convert your Battery Set to Mains with a **COSSOR BATTERY ELIMINATOR**

MU2. For operation on 200/250 v. 50 c/s A.C. mains. Output: L.T., 1.5 v. 125 mA.; H.T., 90 v. 10 mA.
LIST PRICE 3 gns.
OUR PRICE 37/6 p. & p. 2/6

SPEAKERS

3 1/2 in. Speaker ...	17/6
5 in. " " " " " "	15/-
6 1/2 in. " " " " " "	16/6
8 in. " " " " " "	17/6
6 x 4 in. " " " " " "	15/-
8 x 5 in. " " " " " "	19/6
10 x 6 in. " " " " " "	25/-
12 in. " " " " " "	32/6

SUB MINIATURE CONDENSERS

8 µF x 6 volt.
10 µF x 6 volt.
30 µF x 6 volt.
50 µF x 6 volt.
100 µF x 25 volt.

ALL AT 2/3 EACH

B.S.R. 4-spd. mixer Auto-changer type UA8, complete with latest B.S.R. "ful-fi."
Carr. & Pkg. 3/6. **£6.19.6.**

MAINS TRANSFORMERS

- M.T.1 250/250 80 m/a, 19/6.
- M.T.2 350/350 80 m/a, 19/6.
- M.T.3 0/30 volts tapped, 19/6.
- M.T.4 150 watt Auto Transformer, 19/6.
- M.T.5 Battery Charger 4 amp., 19/6.
- M.T.5a Battery Charger 1 1/2 amp., 16/6.

STANDARD ELECTROLYTICS

- 8 µF x 450 volt, 1/8.
- 8 x 8 x 450 volt, 2/4.
- 16 mf. x 450 volt, 2/3.
- 16 x 16 x 450 volt, 3/6.
- 32 µF x 450 volt, 3/6.
- 32 x 32 x 450 volt, 5/6.

BARGAIN OFFER

17" Tube by well-known manufacturer Type CME/1702 (Sub-standard). Price **£5.19.6.** (Callers only.)

WIRECOMP ELECTRONICS

ARROW ROAD, LONDON, W.9. TEL.: CUNNINGHAM 9530

Hours of business: 9 a.m.-6 p.m. Open all day Saturday.

Stern's "fidelity" TAPE EQUIPMENT

A SELECTION OF HIGH FIDELITY PORTABLE TAPE PREAMPLIFIERS

Adds "Hi-Fi" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION

IN ALL MODELS WE INCORPORATE THE TYPE "C" PREAMPLIFIER

AND OFFER IT COMPLETE IN CASE WITH

- (a) The new COLLARO "STUDIO" 3 Speed Deck H.P. Deposit: £7.6.0, 12 months £2.13.6. **£36.10.0**
- (b) The COLLARO Mk. IV "Transcripitor" 3 Speed Deck H.P. Deposit: £8.6.0, 12 months £3.0.11. **£41.10.0**
- (c) The New TRUVOX Mk. VI Tape Deck H.P. Deposit: £3.14.0, 12 months £3.3.10. **£43.10.0**
- (d) The BRENNELL Mk. V 3 Speed Deck H.P. Deposit £10.6.0, 12 months £3.15.7. **£51.10.0**
- (e) The WEARITE MODEL 4A Tape Deck Deposit: £12.4.0, 12 months £4.9.5. **£61.0.0**

STERN'S MULLARD TYPE "C" TAPE PREAMPLIFIER-ERASE UNIT

INCORPORATING THE NEW FERROXUCUBE POT CORE PUSH-FULL OSCILLATOR and 3-SPEED TREBLE EQUALISATION by means of the latest FERROXUCUBE POT CORE INDUCTOR.

PRICES... INCLUDING SEPARATE SMALL POWER SUPPLY COMPLETE KIT **£14.0.0**
 OF PARTS ASSEMBLED AND TESTED **£17.0.0**

Dep. £3.8.0 and 12 of £1.4.11.
 ALSO AVAILABLE EXCLUDING POWER SUPPLY UNIT FOR £11.15.0 and £14.10.0, respectively.
 WHEN ORDERING PLEASE STATE MAKE OF TAPE DECK TO BE USED. We present this "Hi-Fi" Preamplifier strictly to Mullard's specification incorporating ONLY NEW HIGH-GRADE COMPONENTS and the SPECIFIED NEW MULLARD VALVES. It comprises a COMPLETELY SELF-CONTAINED UNIT, neatly finished in Hammered Gold with a very attractively engraved PERSPEX FRONT PANEL.

FOR PERMANENT HIGH QUALITY

INSTALLATIONS WE ALSO OFFER (excluding case)

- (a) The COLLARO "STUDIO" TAPE DECK and our Mullard Type "C" PREAMPLIFIER and Power Unit Assembled and Tested. **£32.10.0**
- (b) As above but TYPE "C" PREAMPLIFIER supplied as complete KIT OF PARTS. H.P. Deposit £6.10.0, and 12 months £2.7.8. **£29.0.0**
- (c) The COLLARO Mk. IV TAPE DECK and the MULLARD TYPE "C" PREAMPLIFIER & Power Unit assembled, tested. H.P. Deposit £7 and 12 months £2.11. **£32.0.0**
- (d) As (c) but Type "C" as COMPLETE KIT OF PARTS. H.P. Deposit £3.0.0, and 12 months £2.18.3. **£32.0.0**
- (e) The TRUVOX Mk. VI DECK and the assembled Type "C" Preamplifier and Power Unit. H.P. Deposit £3.0.0, and 12 months £2.18.3. **£40.0.0**
- (f) As above but Type "C" as complete KIT OF PARTS. H.P. Deposit £3.0.0, and 12 months £2.18.3. **£36.10.0**
- (g) The BRENNELL Mk. V DECK and the assembled Type "C" PREAMPLIFIER and POWER UNIT. H.P. Deposit £9.4.0, and 12 months £3.7.6. **£46.0.0**
- (h) As (g) but Type "C" as complete KIT OF PARTS. (i) The WEARITE 4A DECK with TYPE "C" assembled and tested. H.P. Deposit. £11.4.0 and 12 months £4.2.1. **£43.0.0**
- (j) As (h) but Type "C" as complete KIT OF PARTS. H.P. Deposit. £11.4.0 and 12 months £4.2.1. **£56.0.0**

(Carriage and Insurance on above quotes 10/- extra.)
 PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE.

STERN RADIO LTD.

109 & 115 FLEET ST. LONDON, E.C.4

Telephone: FLEET-STREET 5812/3/4

YOU CAN BUILD A COMPLETE TAPE RECORDER

for **£36.0.0**

H.P. TERMS Deposit £7.4.0, 12 months £2.12.10.

FOR THIS WE SUPPLY:

- ★ COMPLETE KIT OF PARTS TO BUILD THE HF TR3 TAPE AMPLIFIER.
- ★ THE NEW COLLARO "STUDIO" TAPE DECK.
- ★ PORTABLE CARRYING CASE (as illustrated)
- ★ ROLA CELESTION 10in. x 6in. P.M. LOUDSPEAKER.
- ★ ACOS CRYSTAL MICROPHONE. 1.200ft. SPOOL E.M.I. TAPE.

For those who prefer another type of TAPE DECK we will supply precisely as

above—but IN PLACE OF THE COLLARO "STUDIO" DECK—WE INCLUDE

- (a) The Mk. VI COLLARO "TRANSCRIPTOR" TAPE DECK H.P. Deposit £8.0.0 and 12 months £2.18.2. (£1 extra to wire up the Transcripitor Switch Banks.) **£39.15.0**
- (b) The New TRUVOX Mk. VI DECK H.P. Deposit £9.0.0, and 12 months £3.6.0. **£45.0.0**

(Carriage and Insurance on all above is 12/6 extra)

For Constructors with their own Cabinet WE OFFER

- (a) COMPLETE KIT to build the HF/TR3 Amplifier together with the COLLARO "STUDIO" DECK... **£28.0.0**
- (b) As above but with HF TR3 supplied ASSEMBLED and TESTED H.P. Deposit £6.6.0, and 12 months £2.6.0. **£31.10.0**
- (c) COMPLETE KIT to build the HF TR3 together with the Mk. IV COLLARO "TRANSCRIPTOR" TAPE DECK. (£1 extra if we are required to wire up Deck Switch Banks.) **£30.15.0**
- (d) As above but HF/TR3 supplied ASSEMBLED and TESTED (£1 extra if we are to wire up Deck Switch Banks.) **£34.10.0**
- (e) COMPLETE KIT to build the HF/TR3 together with the NEW TRUVOX Mk. VI TAPE DECK... **£36.0.0**
- (f) As above but HF TR3 supplied ASSEMBLED and TESTED H.P. Deposit £7.18.0, and 12 months £2.17.11. **£39.10.0**
- (g) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENNELL Mk. V TAPE DECK... **£41.10.0**
- (h) As above but HF/TR3 supplied ASSEMBLED and TESTED H.P. Deposit £9.0.0, and 12 months £3.6.0. **£45.0.0**

Carriage and Insurance on each above is 10/- extra.
 Attractive PORTABLE CASE is available to accommodate the TRUVOX or COLLARO TAPE DECKS and we offer it, together with ROLA CELESTION 10in. x 6in. LOUDSPEAKER—ACOS CRYSTAL MICROPHONE—and 1,200 ft. SPOOL E.M.I. TAPE—ALL FOR £9.0.0. Carriage and Insurance 5/- extra.

WE HAVE THE NEW 2 SPEED TWIN TRACK TRUVOX Mk VI TAPE DECK IN STOCK £26.5.0

DEPOSIT: £5.5.0 and 12 MONTHS: £1.18.3


THE MODEL HF/TR3 TAPE AMPLIFIER

INCORPORATING 3-SPEED TREBLE EQUALISATION by means of the latest FERROXUCUBE POT CORE INDUCTOR.

PRICE FOR COMPLETE KIT OF PARTS **£12.15.0**

PRICE FULLY ASSEMBLED & TESTED **£16.10.0**

HIRE PURCHASE. Deposit £3.6.6 and 12 monthly payments of £1.4.2. A very high-quality Amplifier based on the very successful TYPE "A" design completed in the MULLARD LABORATORIES. ONLY NEW HIGH-GRADE COMPONENTS are incorporated including MULLARD VALVES and a GILSON OUTPUT TRANSFORMER. Other features are—Magic Eye Recording hand indicator—Effective Tone Control—Monitoring and Extension Speaker Sockets—Has own Power Supply and can be used as independent Amplifier for direct reproduction of Gram Records or from Radio Tuner. Overall size 11in. x 6in. x 6in. Can be supplied for use with Truvox Collaro—Lane—Brenell or Mark Decks. Please specify which. Send S.A.E. for leaflet or 2/6 for complete Assembly

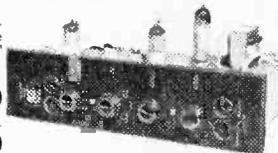


STERN'S MULLARD DESIGNS

Designed by MULLARD—presented by STERNS strictly to specification.
COMPLETE KIT OF PARTS—

MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-stage pre-amplifier (described below) with which an undistorted power output of up to 10 watts is obtained. This combination is thoroughly recommended to "Hi-Fi" enthusiasts who contemplate a versatile and very high quality home installation. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES, including PARMKO MAINS TRANSFORMER (which has extra Power available to drive Radio Tuner) and the choice of the latest Ultra-Linear PARMKO or the PARTRIDGE Output Transformer. **PRICE COMPLETE KIT (PARMKO £10.0.0**

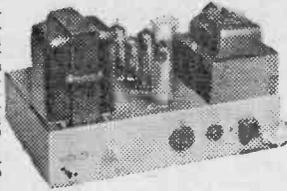

MULLARD'S PRE-AMPLIFIER TONE CONTROL UNIT


Employing two EF86 valves, and designed to operate with the MULLARD 3-3 and 5-10 MAIN AMPLIFIERS, but also perfectly suitable for other makes. **PRICE, COMPLETE KIT OF PARTS, £6.6.0**



Alternatively we supply **ASSEMBLED AND TESTED, £8.0.0** (Carriage & Insurance, 5/- extra.)
 Our kit is strictly to MULLARD'S SPECIFICATION and incorporates:
 • Equalisation for the latest R.I.A. characteristics.
 • Input for Crystal Pick-ups, and variable reluctance magnetic types.
 • Input, (a) Direct from High Imp. Tape Head, (b) From a Tape Amplifier or Pre-amplifier.
 • Sensitive Microphone Channel.
 • Wide range BASS and TREBLE Controls.

COMPLETE MULLARD 5-10

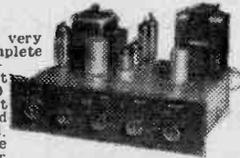Watts high quality reproduction. Input channels for high output pick-ups and all modern Radio Tuning Units only. Specified Components and new MULLARD VALVES are supplied, including PARMKO MAINS TRANSFORMER and choice of the latest PARMKO or PARTRIDGE ULTRA-Linear Output Transformers. Adequate power available to drive Radio Tuner. **£11.10.0**



OR ASSEMBLED and TESTED **£13.10.0**
 HIRE PURCHASE (Assembled Amp. only) DEP.: £2.14.0. 12 Months: 19/10.

COMPLETE MULLARD 3-3

THE IDEAL AMPLIFIER FOR SMALL HIGH QUALITY INSTALLATION

COMPLETE KIT OF PARTS **£7.10.0** OR ASSEMBLED and TESTED **£8.19.6**
 (plus 6/6 coverage and insurance) H.P. Terms: Deposit £2.0.0 and 8 Months at £1.0.0. Developed from the very popular 3-valve 3-watt design. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMKO OUTPUT TRANSFORMER.

MULLARD — STERN STEREO DESIGNS

DUAL "3-3" MAIN AMPLIFIER


Comprises two "3-3" MULLARD MAIN AMPLIFIERS on one chassis and is designed to operate with our DUAL CHANNEL PRE-AMPLIFIER for both STEREOPHONIC or MONAURAL operation. **PRICE: COMPLETE KIT OF PARTS £10.0.0**



Alternatively ASSEMBLED AND TESTED **£11.15.0** H.P. Terms: Deposit, £2-7-0 & 12 months at 17/4. Its output power is 6 watts (3 watts per channel) and together with our PRE-AMPLIFIER provides a very acceptable STEREO installation.

COMPLETE STEREO AMPLIFIER

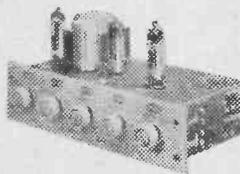A thoroughly recommended design that very effectively meets the many requests for a low-priced but good quality DUAL CHANNEL STEREOPHONIC AMPLIFIER. **PRICE: COMPLETE KIT OF PARTS £8.10.0**



Alternatively ASS. AND TESTED **£10.10.0**
 The EXL82 Triode Pentode Valves are incorporated in a "CLASS A" single-ended output stage in each channel. Sensitivity is 300 mvolts, therefore when used with Crystal Pick-Ups, or Radio Tuning Units, an excellent reproduction is achieved, or similarly when switched to a combined output of 4 watts is

DUAL CHANNEL PRE-AMPLIFIER

This model incorporates two 2-valve Pre-Amplifiers (described above) combined into a Single Unit enabling it to be used for both STEREOPHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 mvolts. **COMPLETE KIT OF PARTS £12.10.0**



AND TESTED **£15.0.0**
 It will operate equally well for MONAURAL only operation with one "5-10" Main Amplifier to which the second Main Amplifier can at any time be added, thus very easily providing for both STEREO or MONAURAL reproduction. Recommended combinations for STEREO operation:

- (a) The DUAL CHANNEL PRE-AMPLIFIER together with the Dual "3-3" MAIN AMPLIFIER.
 - (b) The DUAL CHANNEL PRE-AMPLIFIER together with two "5-10" MAIN AMPLIFIERS.
- THE ASSEMBLY MANUAL is available for 3/-.

Please enclose S.A.E. if ILLUSTRATED and DESCRIPTIVE LEAFLETS are required... alternatively the COMPLETE ASSEMBLY MANUALS are available at 1/6 each.

STERN RADIO LTD.

Stern's "fidelity" TAPE RECORDERS



BEFORE YOU BUY — YOU SHOULD HEAR THESE RECORDERS. THEY ARE COMPARABLE TO THE MUCH HIGHER-PRICED MODELS

There are no better value for money Tape Recorders on the market—if you can't call and hear them, send S.A.E. for fully descriptive leaflets.

MODEL CR3 S. Incorporates the New COLLARO "STUDIO" TWIN TRACK 3-Speed Deck H.P. Terms: Deposit £8.4.0 and 12 months of £3.0.2.

MODEL CR3 T. Incorporates the very popular 3-Speed COLLARO Mk. IV "TRANSCRIPTOR" Deck which has both upper and lower tape tracks. H.P. Terms: Deposit £9.15.0 and 12 months of £3.12.7.

MODEL TR3/Mk. VI. Incorporates the New TRUVOX Mk. VI TWIN TRACK 2-Speed Tape Deck H.P. Terms: Deposit £9.18.0 and 12 months of £3.12.7.

All prices quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200 ft. Spool of Tape

Each Model incorporates the highly successful HF/TR3 Amplifier (described opposite) thus ensuring truly "Hi-Fi" record and playback facilities.

!! RADIOGRAM CHASSIS !!

ARMSTRONG MODEL AF/208 £23.2.0
7 valve AM/FM Chassis producing Max. 5 watts output.

ARMSTRONG "STEREO TWELVE" £37.16.0
The most complete AM/FM unit yet produced for Stereo, giving 6 watts high-fidelity push-pull output on each channel, 12 watts for monaural.

ARMSTRONG "JUBILEE" £29.8.0
An AM/FM chassis with nine valves and with push-pull output stage providing 6 watts.

ARMSTRONG AM/FM "STEREO 44" £28.7.0
Provision is made for Stereo and monaural playback from pick-up or tape. Outputs provided for Stereo or Monaural tape recordings.

RADIO TUNING UNITS

DULCI MODEL FMT/2 £19.17.6
A complete self-powered F.M. Tuner incorporating automatic frequency control.

ARMSTRONG "S.T.3" AM/FM UNITS £27.6.0
A self-powered high-fidelity Tuner covering full VHF, medium, and long wavebands with automatic frequency control on VHF.

DULCI "H4T" AM/FM UNIT £25.15.2
A 4 waveband self-powered high-fidelity tuner covering the VHF/FM transmissions plus the long, medium and short wavebands.

NEW HIRE PURCHASE TERMS are available on all above. Illustrated leaflets available—send S.A.E. (Carr. and Ins. 5/- extra.)

A SPECIAL CASH ONLY OFFER !!
This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER.

ALL for ONLY £8.7.6 (Plus 7/6 Carr. & Ins.)
The Amplifier consists of a 2-stage design incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS.

The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexine.

WE ALSO SUPPLY SEPARATELY:

(a) The 2-stage (plus Rectifier) AMPLIFIER £4.2.6

(b) THE PORTABLE CARRYING CASE £3.17.6

(c) P.M. SPEAKER 18/9 Carriage and Insurance 4/- extra.

— SPECIAL CASH ONLY BARGAIN —

A bulk purchase enables us to offer a very useful

INTERCOM SET OR BABY ALARM for only £5.5.0

(Plus 5/- carriage & Insurance).

Consists of MASTER UNIT and one EXTENSION, providing 2-way TALK-LISTEN facility. Complete in polished wood cases, size of each only 7 1/2 x 4 1/2 x 6 in. high.

STERN'S MK. II "fidelity" F.M. TUNING UNIT

PRICE £14.5.0 (Plus 5/- Carr. and Ins.)

HIRE PURCHASE: Deposit £2.17.0 and 12 Monthly Payments of £1.0.11.

Incorporates the latest MULLARD PERMEABILITY TUNING HEART and the corresponding MULLARD VALVE LINE-UP. A really first-class Tuner, very attractively presented and comparable to many offered at much higher prices. Power consumption is only 1.5 amps. at 6.3 volts and 25 m/a at 250 volts.

HOME CONSTRUCTORS! YOU CAN BUILD THIS TUNING UNIT FOR ONLY £10.10.0 (Plus 5/- Carr. & Ins.) Please send S.A.E. for fully descriptive leaflet, or the Assembly Manual is available for 1/6.



!! RECORD PLAYERS !!

THE LATEST MODELS ARE IN STOCK MANY AT REDUCED PRICES !!
SEND S.A.E. FOR ILLUSTRATED LEAFLET

B.S.R. MONARCH UA8 4-speed mixer Autochanger with Crystal Pick-up **£6. 19. 6**

The **NEW COLLARO MODEL RP594** 4-speed Single Record Player. Studio Cartridge **£9.18.9**



The **COLLARO "CONQUEST"** 4-speed Autochanger, Studio Pick-up **£7.10.0**

The latest **COLLARO "CONTINENTAL"** 4-speed MIXER Autochanger Studio "O" Pick-up **£8.10.0**

The **COLLARO** 4-speed Single Record Player, Studio Pick-up **£6.6.0**

THE NEW B.S.R. Model UA12 is in Stock. A 4 "SPEED" MIXER AUTOCHANGER **£8.7.6**

UA12 also available incorporating the **B.S.R. STEREO** Pick-up, plays L.P. and 78 Records **£10.10.0**

B.S.R. MODEL TU9 4-speed Single Record Player, complete with separate Crystal Pick-up **£4.4.0**

GARRARD MODEL TA/MK. 11 4 Speed Player fitted high output Crystal Pick-Up **£8.10.0**

GARRARD MODEL RC/12/14. Autochanger 4 speeds, High Output, Crystal Pick-Up **£10.0.0**

"Hi-Fi" LOUDSPEAKERS

WE HAVE IN STOCK A COMPLETE RANGE BY GOODMANS—WHARFDALE—W.B. Illustrated and Priced Leaflets on request.

THE "ADD-A-DECK" incorporating the **NEW B.S.R.**

"MONARDECK" and Matched Pre-amplifier

Carriage and Insurance on each above. 5/- extra.
Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Designed to operate through the Pick-Up Sockets of the standard **RADIO RECEIVER** through which first-class results are obtained. It consists of a Twin Track Tape Deck, incorporating matched Pre-amplifier, and operates at 3 1/2 in. sec. speed.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Designed to operate through the Pick-Up Sockets of the standard **RADIO RECEIVER** through which first-class results are obtained. It consists of a Twin Track Tape Deck, incorporating matched Pre-amplifier, and operates at 3 1/2 in. sec. speed.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.

Supplied fully tested and completely assembled on an attractive wood plinth and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated.



109 & 115 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 5812/3/4

PLEASE ENCLOSE S.A.E. WITH ALL ENQUIRIES.

guaranteed Tubes

13 CHANNEL TV's

Carriage and Insurance 12/6
 CRM92, MW22-7, MW22-14, MW22-14C, MW22-17, MW22-18
 CRM121, CRM121A, CRM122, MW31-14C, MW31-17, MW31-18
 121K, 141K, AW36-21, C14FM CRM123, CRM141, CRM142, MW31-16, MW31-74, MW36-24, MW36-44
 171K, C17FM, CRM171, CRM172, MW43-64, MW43-69
 AW43 80, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, MW43-80, MW41-1
 CRM212, MW53-20, MW53-80

GUARANTEED 3 MONTHS	GUARANTEED 12 MONTHS	REVACUUMED	REGUNNED	NEW
£2/15/-	—	—	—	—
£3/-	£5/10/-	—	—	—
£3/10/-	£5/15/-	£7/19/-	—	—
£4/5/-	£6/15/-	£8/19/-	—	—
£5/5/-	£6/15/-	—	—	—
£6/15/-	£9/10/-	—	—	—

TABLE MODELS, FAMOUS MAKES. Complete with all valves and tubes. These sets are unequalled in value due to being purchased direct from source. They are untested and are not guaranteed to be in working order.

12" — £3.19.
 14" — £7.10.

ALSO 12" 5 CHANNEL TV's

Complete Table Models including valves and tubes untested. **55/-**
CARRIAGE FREE

NEW 108K TV TUBES SPECIAL OFFER: £2/19/-
 Many other types not listed available. S.A.E. enquiries.

COLLARO "CONQUEST"
 Hi-Fi 4 spl. 10 record Auto. **£6/19/-**
 Limited Quantity.
100 CONDENSERS 10/-
 A must for your spare box. A well-balanced assortment of miniature silver mica and ceramic condensers. 3-10,000 PF. List values over £3.
PM SPEAKERS Standard 8 ohms, excitements, top makes. performance guaranteed. Quotations quantities.
 91 in. 8/- 5in. 11/- 10in. 13/-
 8in. 7x4 10x6
100 RESISTORS: 7/6
 A magnificent assortment. 1-2 wats.
VALVES ALL GUARANTEED 3 MONTHS
PL81 SOILED AMAZING 5/-
VALUE AT ONLY
EY51 SHORT 5/- U25 SHORT 8/-
ENDS ENDS
4-SPEED RECORD PLAYERS
 Latest Turntable, together with lightweight Staar Galaxy dust sapphire crystal turnover pick-up head. Amazing value. **£3/10/-** Carr. 3/-. (Pick-up only 18/-).

TRANSISTORS: RED SPOT 4/6
 I.F., I.F. and Output up to 800 kc/s. (4/- each in dozens.) **WHITE SPOT** R.P. and I.F. 2.5 Mc/s, 6.8, 69/- per dozen. **XA103, 15/-; XA104, 17/6; XB104, 10/-; GET15, 25/-.**
DIODES General purpose, famous make. 9d. 8/- doz. **GEX** Black type, 3/9.
RECTIFIERS Full wave bridge, 12 volt 3-4 amps, 9/6. (Carr. 1/-) £5 per doz. 250 v. 80 m.a., 5/-, RM1, 6/8; RM2, 9/-; RM3, 9/-; RM4, 15/6; RM5, 21/-, 14A86, 17/-; 14A87, 25/-; 14A100, 25/-.
CONTACT 16RC1-1-10-1, 7/9; 16R1-1-10-1, 7/9; 16RD2-2-8-1, 14/-; 14RA1-2-3-2, 17/-; 14RA1-2-3-3, 20/-.
SINGLE RECORD PLAYERS
 COLLARO 4-speed 4/546 ... £6 19 0
 GARRARD 4-speed 45P ... £7 7 6
 GARRARD 4-speed 4A MKII ... £9 10 0
 GARRARD 4-speed 4HF ... £17 15 0
10 RECORD AUTOCHANGERS
 GARRARD KC75A Senior ... £7 10 0
 GARRARD RC120D MKII ... £9 7 6
 GARRARD RC121/4 MKII ... £9 19 0
 Carr. and Pack. 4/-.

FREE TRANSFORMERS
 With each manufacturer matched pair of GLT15 POWER 1 watt output. Transformers, price 50/- we give free the correct Push-Pull INPUT AND OUTPUT TRANSFORMERS of High Grade construction and 4 Transformer Amplifier circuit. Will transform your existing receiver or amplifier into a truly "Main Volume" outfit.
INFRA RED HEATERS
 At Half Price. **800 w. £3/-**
 Super finish.
1,200w. £3/5/-, 2,000w. £3/10/-
PICK-UP CARTRIDGES
 AGOS 25/8. POWER POINT 18/8.
 STEIG AND REUTER 15/- SONOTONE 17/8.
B.S.R. TAPE DECKS £9/10/-
PORTABLE RECORD PLAYERS
 Collaro 4 speed auto-changer. 21 watt high gain amplifier. Super two- **13 Gns.**
 Or case only 59/-, 21-watt Amplifier complete on baffle with Speaker. £310/-.

VALVES BY RETURN OF POST

10% DISCOUNT SPECIAL OFFER TO PURCHASERS
 of any SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d.; 2-11, 1/-.

OZ4	5/6	6B7	8/6	6J7GT	7/9	6X0G	5/6	12Q7GT	6/-	50L6GT	9/3	DF96	8/3	EC82	6/6	EN108	18/-	T41	7/6	UCH81	9/8		
1A3GT	5/-	6B8X	3/6	6K6GT	6/6	6X0GT	6/6	12N6GT	6/-	53K10	10/6	DH63	6/8	EC84	7/6	EM34	8/8	N152	10/6	TH30C	12/6	UCL82	11-3
1A7GT	12/6	6B9A	6/6	6K7	5/6	7B5	12/6	12N47	5/6	54K10	9/9	DH70	6/-	EC84	8/8	EM80	9/3	P41	4/8	U14	6/8	UCL83	13-3
1D5GT	11/6	6B9B	6/6	6K7G	2/3	7B4	9/6	12N57K	5/6	61BT	11/-	DE77	7/-	EC85	8/3	EM81	9/3	P61	2/3	U18	8/6	UF41	8/6
1D5	9/6	6B9C	12/6	6K7GT	6/-	7B7	7/3	12N7GT	8/6	61SPT	11/-	DK32	12/6	EC89	10/6	EM84	9/9	PABCA01/1	U22	6/9	UF42	7-9	
1HG7	9/6	6B9H	6/6	6K8G	6/-	7C5	7/6	14A47	14/9	7/5	8/-	DK91	6/8	EC89	9/9	EM53	10/6	PCCR4	7/8	U24	7/6	UF80	9/-
1L4	3/9	6B9J	6/-	6K8GT	11/-	706	7/3	19A95	7/6	7/7	8/-	DK92	8/8	EC92	14/-	EN31	16/-	PCCR5	8/3	U25	13/6	UF85	9/-
1N9GT	9/6	6B9R	10/6	6K25	7/6	7H7	7/8	19B6GG	15/-	7/8	7/8	DK99	8/8	EC93	7/6	EY51	9/9	PCCR9	13/9	U26	12/-	UF86	14/6
1R5	8/9	6B9W	8/9	6L1	12/6	7K7	8/-	20D1	9/6	8/0	8/8	DL33	8/8	EC94	8/8	SMALL	9/-	PCCR9	7/8	U31	8/6	UF89	7/6
1S4	8/9	6B7	6/8	6L8	8/9	7S7	9/6	20P2	8/6	8/3	9/6	DL35	11/6	EC91	8/3	EY84	9/-	PCFR2	9/-	U33	11/-	UL41	7/6
1S5	6/-	6B8X	5/6	6L6G	7/6	7Y4	7/6	20P1	9/6	90AV	4/6	DL82	9/6	EC90	8/3	EZ35	6/6	PCLR2	3/3	U35	8/9	UL44	12/6
1T4	4/9	6C4	3/6	6L7	9/-	7Z1	7/6	20L1	11/6	185BT	16/-	DL81	8/8	EC98	12/-	EZ40	7/3	PCLR3	11/8	U37	26/8	UL46	9/6
2D21	4/6	6C5	5/6	6L18	9/-	8D3	3/9	20P3	12/6	723A	35/-	DL82	6/6	EC98	14/8	EZ41	7/6	PCLR4	9/9	U43	9/-	UL84	8/-
3A4	5/6	6C6	4/3	6L19	11/8	10C1	11/-	20P4	17/-	807A	5/-	DL84	7/8	EF22	12/-	EZ80	6/9	PEN25	4/6	U50	6/8	UM80	9/6
3A4	7/3	6C9	8/6	6L23	5/6	10C3	13/8	20P5	16/-	807B	3/9	DL86	3/8	EF36	3/3	EZ81	7/3	PEN45	7/3	U52	5/6	UL6	12/6
4A5GT	8/9	10	8/9	6L12	7/6	10C14	9/-	25A6G	8/-	808	15/-	EAS0	9d	EF39	4/3	GTIC	7/7	PEN48	5/3	U76	6/8	U7	9/-
384	6/6	6CD4G	18/6	6L20	8/6	10F1	6/9	25L6F	6/9	955	2/8	EAC80	7/8	EF40	13/6	GZ32	8/9	PL33	9/-	U78	6/8	U78	16/6
3V4	7/6	6CH6	9/3	6N7	8/6	10F9	10/3	25L6GT	9/-	956	2/8	EAC91	4/9	EF41	8/9	GZ34	12/6	PL38	12/-	U91	9/6	UY11	11/-
5B4G	11/-	6D1	9d	6P1	14/-	10L14	8/-	25V7G	9/-	2050	3/6	EAF42	7/8	EF42	7/6	GZ37	10/6	PL38	14/8	U281	8/6	UY41	8/6
5U4G	5/6	6D2	3/9	6P23	9/9	10L13	8/3	25Z4G	8/-	5763	10/-	EB34	1/6	EF50	8B-2	HA80	9/6	PL51	10/6	U282	15/-	UY81	7/-
3V4G	9/9	6D3	11/6	6P26	6/-	10L12	8/9	25Z5	5/6	5801	4/6	EB31	7/6	EF50A	11/-	KT44	9/6	PL52	7/9	U301	14/-	VR150/30	9/6
5Y3G	6/-	6D6	4/9	6Q7G	9/9	10L13	9/9	25Z6	9/-	9003	4/6	EB31	3/9	EF51	3/9	KT32	7/6	PL83	8/8	U309	12/6	W6	5/6
5Y3GT	6/6	6F1	6/9	6Q7GT	9/3	10P14	9/6	27R5U	16/-	ATP4	2/9	EB33	9/-	EF54	3/3	KT32	6/9	PL84	11/-	U329	12/6	W6M1	11/-
6Z4G	8/6	6F6G	6/6	6R7G	9/8	10P18	8/-	30C1	7/6	AZ91	9/-	EB33	5/-	EF80	5/9	KT33C	6/8	PX25	16/-	U339	11/-	W76	6/6
5Z4GT	11/-	6F9M	7/-	6SA7	5/8	12A6	5/8	30P15	7/9	B36	8/6	EB34	8/6	EF85	7/7	KT38	9/-	PY31	8/3	U403	9/8	W77	4/8
6A7	11/-	6F12	3/9	6S0T	4/9	12AHT	6/8	30P14	9/6	B85	4/9	EB31	7/6	EF86	11/-	KT44	9/6	PY32	11/-	U404	6/8	W81	5/9
6A8G	9/6	6F13	6/9	6S7H	4/8	12AHS	9/9	30L11	7/9	CB131	23/3	EBF80	8/6	EF89	8/6	KT45	8/6	PY80	7/-	U801	17/-	X61M	12/6
6A9GT	13/6	6F14	9/6	6S7J	6/6	12AT6	7/9	30P24	12/6	COH35	7/6	EBF89	8/6	EF91	3/9	KT47	9/6	PY81	7/-	U802	14/6	X61M	12/6
6A8B	8/3	6F15	9/6	6S8K	5/3	12A7	6/6	30P13	8/-	CL33	13/-	EBL21	14/8	EF92	4/9	KT60	12/6	PY82	7/-	UAF42	9/8	X65	11/6
6A07	4/3	6F16	8/9	6S8LGT	6/6	12A7	8/6	30P16	7/9	CV31	9/9	EBL31	18/6	EF93	6/9	KT61	14/8	PY83	8/6	UB41	8/8	X66	11/6
6A05	4/3	6F19	7/-	6S9GT	4/9	12AX7	7/6	30P17	10/6	D63	13/6	EC32	3/9	EF94	4/6	KT61	5/6	PZ30	12/6	UB41	8/8	X76M	9/6
6A07	8/6	6F23	6/9	6S9T	6/3	12BA8	8/-	35L6GT	9/-	D77	3/9	EC90	3/6	EL33	9/-	KT63	4/9	R18	12/6	UBC81	10/-	X78	14/6
6A05	6/9	6H6	2/-	6S8T	6/6	12B6	9/9	35W4	6/9	D152	6/6	EC91	4/6	EL35	11/6	KT233	5/-	R19	12/6	UBF80	8/9	X79	16/6
6A15	3/9	6J5	4/3	6T4GT	10/6	12BH7	10/6	35Z4GT	6/-	DA90	2/6	EC91	9/6	EL37	11/6	L63	2/9	SD9	8/8	UBF89	8/6	X83	6/6
6A05	4/6	6J5G	2/9	6U5G	4/3	12C8	6/8	35Z5GT	8/6	DA93	9/9	EC93	4/6	EL38	12/6	LN152	8/6	SP6	3/9	UBL21	14/6	Z83	5/6
6A06	3/9	6J5GT	3/9	6V8G	5/8	12E1	12/6	34Z	7/8	DAF91	6/6	EC93	4/9	EL41	9/-	LN151	7/9	SP41	2/8	UC95	8/-	Z96	7/8
6A05	6/-	6J6	4/6	6V9GT	6/8	12S6GT	3/8	4Z3	7/8	DAF96	8/3	EC93A	3/9	EL42	8/6	MU14	8/-	SP81	2/6	UC980	16/-	Z77	3/9
6A7E	7/-	6J7	7/9	6X2	9/-	12K7GT	6/-	50C5	9/6	DF33	9/9	EC93	6/8	EL84	8/-	N37	11/-	SU23	15/-	UC921	14/6	Z152	5/9
6A06	8/6	6J7G	5/3	6X4	6/-	12K8GT	12/-	50C8G	16/-	DF91	5/9	EC91	6/6	EL81	4/9	N78	15/-	SU20A4	6/8	UC942	8/6	Z719	5/9

NEW LOW PRICES GUARANTEED 3 MONTHS
 L.F., I.F. and Output up to 800 kc/s. (4/- each in dozens.) **WHITE SPOT** R.P. and I.F. 2.5 Mc/s, 6.8, 69/- per dozen. **XA103, 15/-; XA104, 17/6; XB104, 10/-; GET15, 25/-.**
DIODES General purpose, famous make. 9d. 8/- doz. **GEX** Black type, 3/9.
RECTIFIERS Full wave bridge, 12 volt 3-4 amps, 9/6. (Carr. 1/-) £5 per doz. 250 v. 80 m.a., 5/-, RM1, 6/8; RM2, 9/-; RM3, 9/-; RM4, 15/6; RM5, 21/-, 14A86, 17/-; 14A87, 25/-; 14A100, 25/-.
CONTACT 16RC1-1-10-1, 7/9; 16R1-1-10-1, 7/9; 16RD2-2-8-1, 14/-; 14RA1-2-3-2, 17/-; 14RA1-2-3-3, 20/-.
SINGLE RECORD PLAYERS
 COLLARO 4-speed 4/546 ... £6 19 0
 GARRARD 4-speed 45P ... £7 7 6
 GARRARD 4-speed 4A MKII ... £9 10 0
 GARRARD 4-speed 4HF ... £17 15 0
10 RECORD AUTOCHANGERS
 GARRARD KC75A Senior ... £7 10 0
 GARRARD RC120D MKII ... £9 7 6
 GARRARD RC121/4 MKII ... £9 19 0
 Carr. and Pack. 4/-.


FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

Post: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6. No C.O.D. ALL ITEMS LESS 5% & POST FREE IN DOZENS. LIST OF 1,000 SNIPS, 6d.

TECHNICAL TRADING CO. P.O. BOX 21 (W) 350-352, FRATTON, PORTSMOUTH.

EASY AS A.B.C. TO BUILD


The new, exciting De Luxe "Gold Star" Pocket Radio in beautiful moulded plastic case—**37/6**
This model is a highly sensitive, self-contained set covering all medium waves. Uses modern miniature "button-base" valve and specially designed high efficiency coil. Exceptionally easy to build from our step-by-step plans—the case is supplied ready drilled! Size of radio only 4 1/2 in. x 2 1/2 in. x 1 1/2 in. — and batteries fit inside. We can supply all parts including case, detachable aerial, instruction book, wire, screws, etc., for only **37/6**, plus 2/6 Post and Packing. C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/6.)

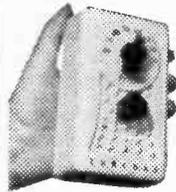

2/- extra. (Parts sold separately, priced parts list 1/6.)



Our engineers have designed a novel Wrist-Watch Radio using latest Transistor Techniques. Size only 1 1/2 in. x 1 in. x 1 1/2 in. Feather-weight—yet gives clear, crisp, personal-phone reception over all medium waves. Tiny battery inside lasts months—costs 5/-, No Snags, anyone can build it in an hour or two using our pictorial step-by-step simple plans. All parts supplied (including case and strap) for only **29/6** (add 2/6 Post, etc.). C.O.D. 2/- extra. (All parts sold separately, priced parts list 1/6.) Send Now!

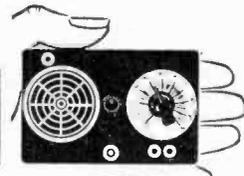

Can Be Built for **47/6**. Build this exceptionally sensitive high efficiency personal phone radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 1/2 in. x 3 in. Covers all medium and long waves. H.T. consumption only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holiday, etc. BUILD THE "SKY-ROMA" NOW! Total building cost—everything down to the last nut and bolt, **47/6** (Postage, etc., 2/-)—with full set of clear, easy-to-follow plans. (Parts sold separately. Priced parts list and plans 1/6.) C.O.D. 2/- extra.



47/6



The sensational "Silver-Tone" model! A highly compact self-contained miniature "button-base" valve pocket radio at absolute "rockbottom" building cost! Covers all the medium waves with the very latest circuitry bringing in stations from all over Europe—without fuss. Easy as A.B.C. to assemble, using our step-by-step instruction manual. Size only 4 1/2 in. x 2 1/2 in. x 1 1/2 in.—a fascinating little pocket radio. We can supply all the parts including beautiful two-tone case, detachable aerial, instruction book, screws, wire, etc., for only **29/6** (plus 2/- post and packing). C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/9.)



Anyone can build this beautiful precision Pocket Radio in an hour or two. No knowledge whatever needed. Our simple pictorial plans take you step-by-step! Remarkably sensitive—covers all medium waves. Inc. Luxembourg, Home, Light. Size only 2 1/2 in. x 3 in. x 5 1/2 in.—Not a Toy! But a Real Personal-Phone Valve Radio With Detachable Aerial! IDEAL FOR BEDROOM, GARDEN, etc. We supply ALL parts necessary, together with plans, etc., for the special price of **39/6**, plus 2/6 post and packing. (C.O.D. 2/- extra.) BUILD YOURS NOW! (All parts sold separately, priced parts list 1/9.) Send Today! Money refunded if parts returned intact within 7 days.

39/6

THIS TRANSISTOR SET Can Be Built For Only **29/6**. The "Sky-Scout" Pocket, two-stage transistor set, size only 1 in. x 3 1/2 in. x 1 1/2 in. Covers all medium waves and works entirely on tiny "penlight" battery which costs 6/-, and fits inside case. All parts tested before despatch. Can be built for **29/6**, plus 2/- Post and Packing. INCLUDING CASE, TRANSISTOR, STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS, nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list and plans 1/6. VERY SIMPLE TO BUILD.

Choice of beautiful walnut or veneered cabinet or ivory bakelite. This is the




lowest possible price consistent with high quality. No radio knowledge whatever needed can be built by anyone in 2-3 hours, using our very simple, easy-to-follow diagrams. The terrific new circuit of the "Ocean-Hopper" covers all medium and long waves, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple-to-follow plans—in fact everything! Parts tested before despatch! Uses standard octal-base valves. (Low running costs—approximately 18 watts.) Size 12 in. x 6 in. x 5 in. Build this long-range powerful midget NOW. TOTAL BUILDING COST INCLUDING PLANS, ETC., **£5/7/6**. (Post and Packing 3/6.) Parts sold separately. Priced parts list and plans 1/9. C.O.D. 2/- extra.

107/6



This amazing "Tiny-Tim" model—no larger than a matchbox—costs nothing to run—ever! No batteries! No Valves! No electricity! Will never run down or burn out. Uses the latest TRANSISTOR TYPE GERMANIUM DIODE, receives local stations anywhere—without extra aerial. Clear, Crisp Tone. No snags, anyone can build it within an hour using our step-by-step instruction book, etc., for only **15/-**, plus 2/- Post and Packing (C.O.D. 2/- extra). (Parts sold separately, priced parts list 1/9.)

15/-

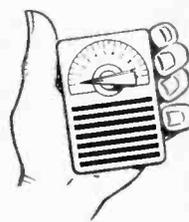

45/-

TWO-TRANSISTOR POCKET SET. Can Be Built for **45/-**. BUILD THE "SKY-GNOME" WEST-POCKET TWO TRANSISTOR RADIO which gives a superb performance and is highly sensitive. Weight under 7 ozs.—yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a "penlight" battery. Every part tested before despatch! SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS. Total building cost, including case, transistors, etc.—everything down to the last nut and bolt—ONLY **45/-** with plans. Postage, etc., 2/-. (C.O.D. 2/- extra.) (Parts sold separately. Priced parts list and plans 1/6.) RUSH YOUR ORDER TODAY!

CONCORD ELECTRONICS
210, Church Road, Hove, Sussex
Dept. PW16

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad.

NO DEPOSIT - INTEREST FREE - 20 or 36 WEEKS TO PAY!



4/1
DEPOSIT

R.P.2.

Balance at 2/11 per week for 19 weeks.

A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½ in. deep. Will take B.S.R. Monarch 4-speed Autochanger and 7 x 4 in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6. Cash Price. 59/6.

AMPLIFIERS

12 Months Guarantee
ALL PORTABLE

AMPLIFIER MK. D.1. 59/6

Brand new. Latest design with printed circuit. Dimensions 7 x 2½ x 5 in. A.C. only. Mains isolated 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

AMPLIFIER MK. D.2. 79/6

Printed circuit. Latest design. Dimensions 7 x 2½ x 5 in. A.C. only. Mains isolated. 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve giving higher undistorted output. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

AMPLIFIER MK. D.3. 89/6

De-luxe model. Printed circuit. Latest design. Dimensions 7 x 2½ x 5 in. A.C. only. Mains isolated. 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve, giving higher undistorted output. Volume, treble and bass control. Knobs 3/6 extra. P. & P. 3/6.

AMPLIFIER MK. D.5. 39/6

Simple circuit employing ECL80 triode pentode output valve giving 2-3 watts output. A.C. only. Mains isolated. Single control for volume and on/off switch with knob. P. & P. 3/6

P.L.10 CABINET


Size 14½ x 12½ x 6 in. Takes B.S.R. T.U.9 4-speed record player unit. 8 x 3 in. elliptical speaker. Single control amplifier. Carr. & Ins. 4/6.

39/6



STEREOPHONIC PLAYER CABINET

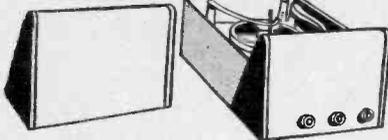6/1
DEPOSIT
Balance at 4/11 for 19 weeks.



S.T.I.
99/6
Cash

Continental style cabinet including extra clip-on speaker cabinet. 15½ x 10½ x 24½ in. deep Takes B.S.R. 4-speed stereo Autochanger. Printed circuit amplifier. Two 8 in. speakers. Carr. & Ins. 6/6.

STEREOPHONIC AMPLIFIER

9/1
DEPOSIT.
Balance at 7/11 for 19 weeks.
12 MONTHS GUARANTEE

Beautifully made for portable stereophonic record players. Latest design with printed circuit. Dimensions 3 x 5½ x 9½ in. A.C. only. Mains isolated. Twin amplifiers each side giving 3-4 watts output. Incorporating ECL82 triode pentode valve. Full tone, volume and balance controls. Complete and ready to fit. Knobs 3/6 per set extra. Carr. & Ins. 3/6.

Cash price £7.19.6.

B.S.R. MONARCH U.A.8 4-SPEED AUTOCHANGER

£6.19.6




4-speed Autochanger. Incorporating auto and manual control complete with turn-over crystal P.U. and Sapphire stylus. A.C. Post & Ins. 5/6, or Initial Payment 8/1, plus post and & Ins. and 19 weekly payments of 6/11.

T.U.9, B.S.R. 4-speed single player, £4.9.6.
Collaro Conquest 4-speed Autochanger, £6.19.6.
Collaro Conquest Stereo Autochanger, 11 gns. P. & P. on all the above 5/6.

STURDY CASE, 12/6

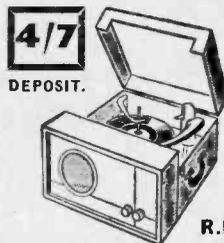8½ x 7½ x 3½ in. deep. Covered in burgundy and grey washable rexine. Strong clasp, hinges and handle. Ideal for portable radio chassis or transistor set. Can be adapted as a record carrying case to hold 18 seven-inch long-playing records. P. & P. 2/6.



4/7
DEPOSIT.

R.P.3.

Balance at 3/5 per week for 19 weeks.

A delightful looking cabinet 14½ x 17½ x 8½ in. in 2-tone leatherette. Will take a B.S.R. Monarch 4-speed Autochanger and 6 in. round speaker. Carr. & Ins. 4/6. Cash Price, 69/6.

EXTENSION SPEAKERS

19/9



Polished oak cabinet of attractive appearance. Fitted with 8 in. P.M. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms.) Switch and flex included. Ins. carr. 3/9.

8 in. P.M. SPEAKER 8 9
Std.; 2-5 ohms. With O.P. Trans., 10/- P. & P. 2/6.

ELLIPTICAL SPEAKER 19 6
7" x 4"


ELLIPTICAL SPEAKER 22 6
9½" x 4½"

B.S.R. FUL-FI Crystal Turn-over cartridges 19 6

Brand new, including sapphire needles for L.P. and Standard, giving fullest range and finest tone obtainable for any player. Can be fitted to all standard pick-up arms. P. & P. 9d.

TAPE RECORDER CABINET

19/6

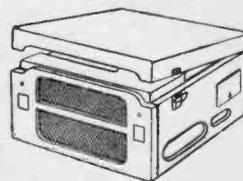


A MUST if you are building your own tape.

Suitable for the Truvox Tape Recording Desk. Less front cast speaker panel. Size 13½ x 15 x 8½ in. deep. Detachable lid with compartment for spare tape. Covered in green washable plastic material. P. & P. 4/6.

DUKE & CO. (Dept. D1), 621/3, Romford Road, Manor Park, E.12. Tel.: ILF. 6001/3.

Send for FREE catalogue.

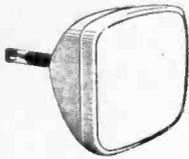

**REPLACEMENT
RE-BUILT
T/V TUBES**

Yours for initial
payment of

8/6

Balance at 8/6 for 19 weeks.

12 months' Full Guarantee

All sizes except 10in. Completely rebuilt gun assembly, new cathode, heaters, etc., giving the high standard required for long picture life, quality and value. Carr. & ins. 15/6.

EXPRESS DESPATCH SERVICE

Please phone to confirm Tube in stock. Send Telegraph Money Order. Tube despatched Passenger Train same day. This service only available with remittance by a Telegraph Money Order and cash sales, not terms.

**A CHASSIS FOR SPARES ALL
THIS FOR ONLY 9/6**

56 Resist ; incl. 7 variable. Controls. Condensers, incl. electrolytics. Coils, 7 I.F. and R.F. Trans. 14 valve holders. 9 B7G, 5 B5G, 3 octal, 4 Trans. Mains—O.P.P.—Line—Frame. Chokes. 250 m.a. Metal rec. 300 volt 250 m.a. Fuse panel—scanning coils—focus magnet. Plugs—sockets—switch—chassis screws—tag strips, etc. I.F. strip in separate Power Pack can be used without dismantling. Chassis have been used, but were working when stored. 7 pages of circuits and instructions showing position of each component. Carriage. 10/6.

BAKELITE CABINETS 5/9


Brand new. Colour brown. Attractive design. Size 12 x 7 x 5 1/2 in. Ideal for small receivers, converters, etc. P. & P. 3/9.



**MODERN
17" T/V
CHASSIS
COMPLETE
AND
WORKING
24 GNS.**

Latest chassis including 17in. tube, permanent magnet speaker, 13 channel Turret Tuner (any two selected channels fitted). Other channels supplied on request at 7/6 each. 13 valves. Chassis and valves guaranteed for three months. M.V. 43-69 CRT. 2 months' full guarantee. Sound I.F. 19.5 Mc/s. Vision 16 Mc/s. A.C. only. Ready and working to fit into your own cabinet. Carr. & Ins. 25/- As above, with 14in. tube, complete and working. £19.19.0.

**SUPER CHASSIS
3/11 PER WEEK**

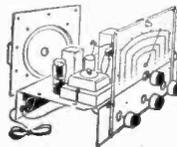

On the initial payment of 5/11 plus carr. of 5/6, this chassis will be despatched. Balance at 3/11 for 19 weeks. Cash Price 79/6. 5-valve Superhet chassis including Bin. P.M. speaker and valves. Four control knobs (tone, volume, tuning, w/change switch). Four wavebands with position for gram p.u. and extension speaker. A.C. Ins.. carr. 5/6.

**SOLO SOLDERING TOOL
12/6**



110 v. 6 v. 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.

T.V. AERIALS 23/6

For all I.T.A. channels. Outdoor or loft. 3 elements; P. & P. 2/6

AERIALS 15/6

B.B.C. indoor type. Folded dipole with 12ft. co-ax. cable fitted.

Post 1/9.

T.V. AERIALS 35/-

COMBINED I.T.A. or B.B.C. New. L/SD. P. & P. 2/6.

CAR AERIAL 6/9

Plated. Whip antennae. 50in. long collapsing to 11in. One hole fixing. P. & P. 1/-. (Not telescopic.)

SOUND VISION and I.F. STRIP 7/9

Plessey. I.F.s 10.5 Mc/s sound. 14 Mc/s vision. 8 valve holders.

Less valves. Size 8 1/2 x 5 x 4 1/2 in. Circuit incl. The tuner unit plugs directly into this chassis. P. & P. 2/6.

SOUND VISION and I.F. STRIP 2/9

Brand new. Complete sound and vision strip. 8 valve holders.

Less valves. I.F.s 16-19.5 Mc/s. Size 8 1/2 x 4 1/2 x 4 1/2 in. Drawings free with order. P. & P. 2/6.

TIMEBASE 2/9

Containing scanning coils, line transformer, etc., less valves.

Drawings free with order. P. & P. 2/6.

CO-AX. CABLE, 6d. YARD

Good quality. Cut to any length. 1/6 post on 20 yds.

INSULATING TAPE 1/6

75ft. x 1/2 in. In sealed tins. Post 9d.

SUPER SUPERIOR RADIO 89/6

4 waveband. 5 valve superhet radio. 2-tone covered metal cabinet size 24 1/2 x 12 x 10in. 4 control knobs. Positions for gram., p.u. and extension speaker. A.C. only. Ins. carr. 8/6.



FOCUS MAGNETS 9/9

Brand new. 38 mm. incorporating picture shift control.

P. & P. 1/3.

FOCUS MAGNETS 12/6

38 mm. Brand new. P. & P. 1/3.

SCANNING COILS 10/6

Low impedance. 38 mm. Brand new. P. & P. 1/3.

SCANNING COILS 15/9

Wide angle 90 deg. 38 mm. Low impedance. P. & P. 1/3.

T.V. MASKS 2/9

Gold plastic for 15in. tubes. Post 1/3.

CHASSIS 1/-

6 or 8 valve latest type midget valve design for A.M. or F.M.

Brand new. Cadmium plated. Size 12 1/2 x 7 1/2 x 2 1/2. P. & P. 1/9

MAINS TRANSFORMERS 7/9

Primary 200-250. Secondary 300-0-300. 6 v. at 3.3 amps. P. & P. 2/9.

MAINS AUTO 0-205-225-245 VOLTS AT 300 m.a. 8/9


Isolated windings of 6.3 v. at 2.6 amp. 6.3 volt at 3.6 amp. 2 v. at 1.4 amp. P. & P. 3/9.

O.P. TRANSFORMERS 1/3

Standard size. 2-5 ohms. P. & P. 1/-. 20 for £1. P. & P. 5/6.

HOME RADIO A.C. or Universal 79/6

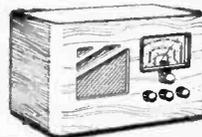A.C./D.C. Universal mains 5-valve octal superhet. 3 waveband receiver can be adapted to gram p.u. In attractive wooden cabinet. 9 1/2 x 18 1/2 x 11 1/2 in. Ins., carr., 4/6. Terms available.



DUKE & CO. (Dept. D.1),
621, ROMFORD ROAD, MANOR
PARK, E.12. ILF 6001-3

**★ CARRIAGE AND INSURANCE MUST BE SENT WITH
INITIAL PAYMENT. WEEKLY EASY PAYMENTS.**

Details on Request.

GOVERNMENT SURPLUS AND MANUFACTURERS' CLEARANCE


METERS. 500-0-500 Microamp. 3 1/2 in. dia. 37/6 ea. Dual Range 0-5 v. 0-100 v. FSD 1 m.a. 20/- ea. ; 50-0-50 Microamp. 2 1/2 in. 30/- I.T.A. AERIALS. New 3 element 22/6. 5 element 27/6.
CO-AX CABLE 84 yd. AIR SPACED 94. DIPLXERS 12/-
GERMANIUM DIODES 1/-, 10/- doz. TRANSISTORS from 5/-
VOLUME CONTROLS. Long Spindle Midget. 10,000 ohms-2 meg. Less Switch 3/-. D.P. switch, 4/6.
CONDENSERS. Twin Gang .0005 Standard 5/6. Midget 6/6.
VENNER SYN. METRS. 200/250 v. with gear train driving. 5 dials. 1/10-1,000 hrs. 25/- ea.
REL. RECTS. 12 v. 1 amp. 5/-, 2 amp. 11/8. 4 amp. 15/-, 500 v 8 amp. containing 30/35 mm. discs. 10/- ea.
12 WAY P.A.C. CABLE. Screened & P.V.C. covered. 2.6 yd.
ELECTROLYTICS. Canned. 20 x 20 mfd. 450 v. 2/6 ea. 25/- doz.
VAR. SLIDERS. 10 ohm 30 w. for chargers, trains. 3/- ea.
FERRITE Rod Aerials. Med. & Long Wave. 10/- ea.
CONNECTING WIRE. P.V.C. 100 ft. 2.6 various colours.
RELAYS. Large stocks. assorted sizes. from 2/6 ea.
VENNER SILVER-ZINC ACCUMULATORS. H.105. New. 15/-
SLEEVEING. 2. 3. 4. 5 mm. 3d. yd. 2.6 doz.
P.P. OUTPUT TRANSFORMERS. For EL34, 3 ohm. 8/6.
VALVES TESTED ON MULLARD'S ELECTRONIC TESTER

1L4	5/-	6D2	8/-	6X4	7/-	E450	1/6	EY51	5/-
1T4	6/6	6E1	7/6	6X5	7/-	E4BC90		EY51	8/-
1U4	6/-	6F6	7/-	8D2	4/6			P61	4/-
3A4	6/-	6F13	7/6	9D2	5/-	EB41	7/6	PEN45	7/6
4D1	4/-	6J5	6/-	10P1	7/6	EB91	5/6	PEN46	7/-
5Z4	9/-	6J8	6/6	12A6	7/8	ECH42	8/-	SP41	4/6
6AG5	5/-	6J7	6/6	12AH8	8/-	ECL90	9/-	SP61	3/6
6AL5	5/-	6K7	4/6	12AT7	6/-	EP36	5/-	VR150	30/-
6AM5	5/-	6L6	6/6	12AU7	7/-	EP37	9/-		5/-
6AM6	6/-	6SA7	6/-	12AX7	7/-	EP39	5/6	UL84	9/-
6AQ5	6/-	6SC7	4/6	12BH7	10/-	EP50	3/6	VCR37	15/-
6AU6	7/-	6SJT	5/-	12SH7	5/-	EP70	5/-	VCR139A	15/-
6BA6	8/-	6SK7	5/-	12SJ7	6/6	EP90	8/-		25/-
6BE6	5/6	6SL7	6/-	12SK7	5/-	EP91	6/-	VCR139A	25/-
6BH6	5/-	6SN7	7/-	15D2	6/-	EP92	7/-		25/-
6BW6	6/8	6U5	6/6	50C5	10/-	EL32	5/6		
6C4	5/-	6V6	6/6	807	6/-	EL91	5/6		

SECOND-HAND VALVES, YOUR CHOICE. £1.0.0 for EIGHT. ECL80, 6C1, 6AM6, 6AG6, 6J6, EP50, 6BE6, 3A4, EP90, SP61, P61, 6J5, PY90, PY92, Z77, 6AL5, 6K7, 6STJ, EL32, 6F42, 6D2, 20P1, 6F13, SP41, EY51, EB91, EP91, EP39, EP96, PEN45, PEN46.

HUGGETT'S LIMITED 2-4 PAWSONS ROAD, WEST CROYDON

AMPLIFIER IN CABINET

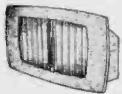


70/-

(3/- P. & P.)

Beautifully finished wood cabinet with "gold" and brown dividing strip and "gold" finished fabric front. Size 13" x 7 1/2", front to back 4 1/2". 5" P.M. speaker. ECL82 valve with metal rectifier. Vol. tone, on-off. 70/- (3/- p. & p.). Cabinet only 20/-, plus 2/- post.

COMPLETE V.H.F./A.M. RADIO FOR £12.12

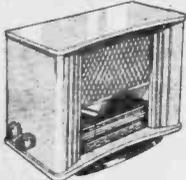


Brand new set, in superb walnut cabinet (size 19" x 8 1/2" x 14 1/2" high). Covering 80-100 Mc/s, 16-49 M., 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tappings. Ferrite rod aerial for A.M. Controls : volume on/off, tone, tuning, w/change. Gram and ext. speaker position provided. Fully guaranteed. Post and packing 10/- extra. Terms : £3.12.0 down (inc. carr.) and 5 monthly payments of £2. Indoor V.H.F. aerial 10/- extra, cash.

OR CHASSIS TERMINATING IN OUTPUT TRANS. (2-3 OHM) WITH DIAL BUT WITHOUT SPEAKER OR CABINET—ONLY £10 (7/6 CARR.). TERMS AVAILABLE.

UNIC SHIVERS LTD., 25, Wordsworth Road, Worthing, Sussex.

Fully Guaranteed Components

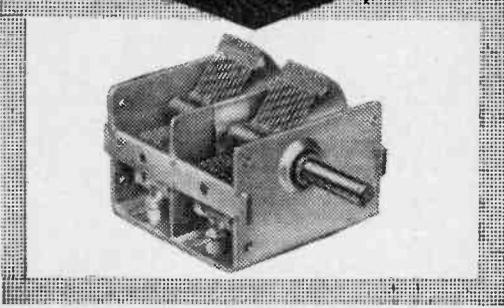

F. GANG CONDENSER

A good general purpose gang. Robust but small in size. "E" law to match our S.L.8 Full Vision, Square Plane and Air Plane Drives. Size 2 1/2 in. x 1 21/32 in. x 2 9/16 in. long (3 gang 3 11/16 in.). Price for 2 Gang, 13s. 3d. 3 Gang, 17s. 6d. Complete with trimmers.

JACKSON BROS. (London) Ltd. PRECISION BUILT COMPONENTS KINGSWAY · WADDON · SURREY



Telephone : Croydon 2754 5

GENUINE GUARANTEED BRITISH TRANSISTORS

FAMOUS MAKES . . . LOWEST PRICES EVER
"TRI" L.F./I.F./General purpose 800 kc/s. 4/6.
RED SPOT—L.F./I.F. General Purpose 900 kc/s. 5/-
WHITE SPOT—R.F. Osc./I.F. 3-4 mc/s. 8/6.
Green Yellow—Audio/Output 125 mW. 7/6.
TS3—Special Offer, a few only. 12/6.
EDISWAN—XA104, 18/-; XB102, 10/-; XB104, 10/-; XA103, 15/-
EDISWAN—Set of Seven Transistors. XA102, two XA101, XB102, XB103, two XC101. ONLY 80/6 per set
MULLARD—OC16, 54/-; OC44, 28/-; OC45, 23/-; OC65, 22/6; OC68, 25/-; OC70, 14/-; OC71, 14/-; OC72, 17/-; 2 OC79 (Matched Pair), 34/-; OC170 (70 mc/s), 50/-; OCP71, 50/-
ANY TYPE OF TRANSISTOR CAN BE SUPPLIED.

TRANSISTOR HOLDERS. 1.3. ARDENTE sub-miniature. 1.9.
CRYSTAL DIODES. 1-. GEN34, 4/-; Mullard OA81, 4/-; OA70, 4/-
FERRITE ROD—5" x 1". 2/6; 6" x 1". 2/9; 8" x 5/16". 1/6.
COILS—Repenco DR22, 4/-; DRX1, 2/6; Teletron HAX, 3/- . All complete with circuits.
TUNING CONDENSERS—Solid, dielectric, 500 pF (4,000 mfd.). 4/-; 300 pF. 3/8; 100 pF. 3/-. **MINIATURE** 500 pF. 5/-
TRANSISTOR CIRCUITS—MINI 3, 1/3; Mini 7, 1/6; Major 7, 1/8; MAXI 3, 1/8. 8d. Teletron Transdyne, 11d. (Full Kit, £11.17/6). Three Dec. 11d. (Full Kit, 67/6).
BEGINNERS 1 VALVE—Circuit and plans. 11d. Kit. 37/6.
RESISTORS—All values 10% 1 w. 8d.; 1 watt. 9d.
HI-STAB RESISTORS—Special offer 100K 5% 1 w. 9d.
CONDENSERS—Miniature. .001 mfd. . . .002 mfd./100 v. 8d.; .01/100 v. 10d.; .1 mfd./100 v. 1/2; .005/200 v. 10d.; Standard size. .01/1,000 v. 8d.; 1,350 v. 9d.; 1,500 v. 10d.; 5/350 v. 1/10.
ELECTROLYTICS—(Can Only) 32-32/450 v. 6/6; 100-200/275 v. 9/9; 60-250/275 v. 8/9; 64-120/350 v. 9/8; 60-300/275 v. 7/-; 24-24/350 v. 4/6; 100-100/200/275 v. 13/-; 60-50-50/350 v. 9/10; Wire ended, 16 mfd./450 v. 2/4; 16-16/450 v. 4/-; 8-8/450 v. 2/9; 8-16/450 v. 2/9; 50 mfd./50 v. 1/6; 25 mfd./25 v. 1/9; 100 mfd./6 v. 2/3.
Miniature, 25 mfd./2/6; 50 mfd./2/3; 8 mfd./2/9; 2 mfd./2/6.
8 UP MINIATURE—32 mfd./25 mfd./16 mfd./8 mfd./4 mfd./2 mfd. All 3/8; 100 mfd. 2/9; 1 mfd. TCC 4/-
CONNECTING WIRE. Six assorted colours. 1 yard of each colour 1/9; 2 yards of each colour 2/9.
TERMS : Cash with Order (or C.O.D. on orders over £2).
ALL OUR PRICES ARE POST PAID.

OAKFIELD RADIO THE TRANSISTOR PEOPLE

Mail Order Only
44 Oakfield Road, Stockport, Cheshire.

Taylor 21st ANNIVERSARY Special Offer!!

We wish to thank all our friends for their best wishes on the occasion of our 21st Anniversary.

As a gesture we are offering our extremely popular Model 127A on 10 monthly Credit payments without interest charges, i.e., £1.0.0 per month. This special offer is applicable to orders received during February and March only.

CONSIDER THESE OUTSTANDING FEATURES


- ★ Sensitivity 20,000 o.p.v. D.C., 1,000 o.p.v. A.C.
- ★ Very robust shock-proof moulding.
- ★ Centre pole movement mounted on sprung jewels, magnetically shielded.
- ★ Portability—slips comfortably into the pocket.
- ★ 20 ranges—50 microamps, 1 milliamp, 10 milliamps, 100 milliamps, 1 amp. Volts D.C. 0.3, 2.5, 10, 25, 100, 250, 1,000 (25 kV. by probe). Volts A.C. 10, 25, 100, 250, 1,000.
- ★ Three resistance ranges : 0-2,000 ohms ; 0-200 k. ohms ; 0-20 megohms, self-contained.
- ★ 37 microamp movement, 3¼ in. 3-coloured scale.
- ★ Accuracy : D.C. 3%, A.C. 4%.

Write for full details and catalogue

TAYLOR ELECTRICAL INSTRUMENTS LIMITED

MONTROSE AVENUE, SLOUGH, BUCKS.

Member of the METAL INDUSTRIES Group of Companies

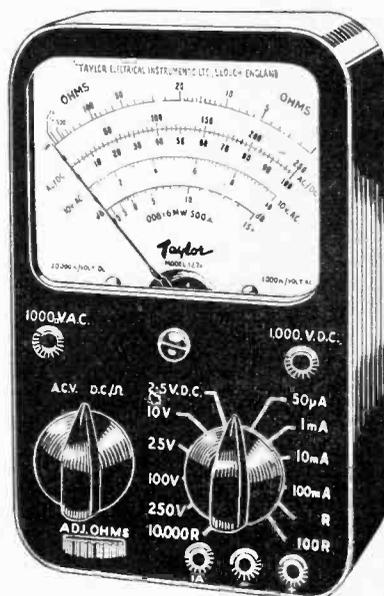

MODEL 127A

PRICE

£10.0.0


Complete with Instruction Manual and Interchangeable Test Prods and Clips. High quality leather case, if required, £1.12.0. H.V. Probe for 25 kV. £4.15.0.

Telephone : SLOUGH 21381
Cables : TAYLINS, SLOUGH.

For Your Lab.

Resistance substitution boxes are great time savers and you really cannot have too many of them; here then, is an opportunity to acquire these at a very low rate. Our R.S. kit available for only 8.6, plus 1/6 postage, comprises one 50 W. precision variable resistor 0-100 K., six 2-3 watt fixed resistors, one 6-position switch, one pointer knob and one ordinary knob and instructions. This unit when made up will give an infinite variability over the range 100 ohm to 2 meg.

12-CHANNEL TURRET TUNER

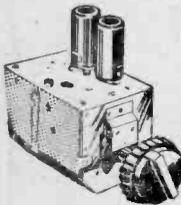

Ideal for converting an old or building into new T.V. These are brand new stock, not surplus, supplied complete with valves and coils for local Band I and Band III stations. Model 1. I.F. Output 33.33 Mc/s series heaters (parallel heaters, 5/- extra).

Model 2. I.F. Output 16.19 Mc/s parallel heaters (series heaters, 5/- extra). With instructions and circuit diagram, 79.6. knobs 3/6 extra, postage and insurance 2/6.

Avo Proddclips

The advantage of these test prods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price 15/- Pair.



Our 68-page Hi-Fi Catalogue is now being sent out to customers—gives details of the latest and best Hi-Fi equipment with over 400 illustrations. Price 2/6 per copy which is refundable from purchases.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500 0-1,000. A.C. volts 2.5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50, 0-500 with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. Price 19.6, plus 2/6 post and insurance.




Miniature Microphone

American made. Dynamic type, real bargain at 2/6, plus 6d. postage.



FOUR ITEMS FOR PRICE OF ONE

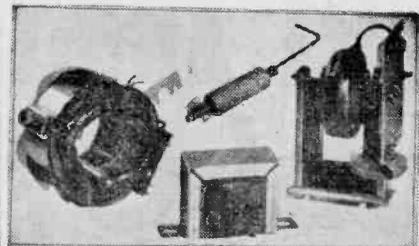

Set of modern T.V. parts suitable for modernising old television or for a new one. For wide angle 14in. or 17in. tubes comprises: (1) Line output E.H.T. transformer. (2) 70 scanning coils on ferrite yokes. (3) Width control with ferrite core. (4) Frame output transformer. (5) Circuit diagram of a modern television. Offered at the price of the Line output transformer only, namely, 57.6, plus 2/6 post and insurance.

Unique Opportunity to build Fine Transistor Set

Constructor's parcel: to build Pocket 6 Transistor Set as currently being sold at £17.17.0. Parcel comprises Motified two-tone cabinet as illustrated, tuning dial, two gang tuning condenser, combined bakelite chassis / printed circuit and easy to follow circuit. Costing value 57.6—offered while supplies last at only 29.6, plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss the tremendous bargain.



ASSURE YOUR FUTURE

The ownership of a good instrument has been the turning point in many a career, it could easily be yours, for you can own the latest Avo Test Instrument for the initial payment of only 10/-. This test instrument is ultra-modern, has a sensitivity of 10,000 Ohms per Volt, measures A.C. Volts 0-1,000 in 5 ranges, D.C. Volts 0-1,000 in 7 ranges, D.C. current at 1 Amp. in 5 ranges and resistance up to 2 Megs. in two ranges. Free Gift. To extend the uses of this instrument, for instance, to measure capacity, inductance, E.H.T., etc., we have developed a range extender scale and operating notes, these will be sent free to purchasers of this instrument. All sent immediately for 10/- deposit, balance by 21 payments of 10/- which includes free insurance against accidental damage for 12 months. Non-callers add 3/6 post and insurance. Cash price, £9.10.0.




MULTIMINOR

Free Gift. To extend the uses of this instrument, for instance, to measure capacity, inductance, E.H.T., etc., we have developed a range extender scale and operating notes, these will be sent free to purchasers of this instrument. All sent immediately for 10/- deposit, balance by 21 payments of 10/- which includes free insurance against accidental damage for 12 months. Non-callers add 3/6 post and insurance. Cash price, £9.10.0.

Rectifier Bargains

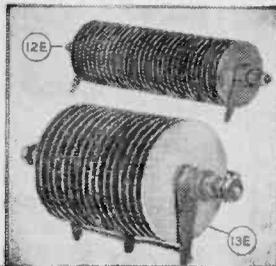
Selenium rectifier type 12, 500 v. I.A. half-wave, easily rebuilt into full wave or multiple type, contains 30 35 mm. discs. Price 3/6, plus 1/6 post. Type 13, 36 volt 9 amp. easily rebuilt into six full wave charger rectifiers suitable for 6 or 12 volt batteries at 3 amps. contains 24 84 mm. discs.



Real bargain at 19.6, plus 1/6 post.

FOR ADDRESS SEE OPPOSITE PAGE

Fluorescents

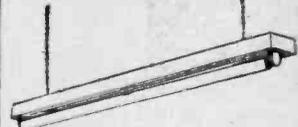

All complete with polyester filled choke and interference suppressors, starters and fluorescent tube—all ready, in fact, to switch on. 5ft. 80 watt, 54.9 plus 5/6 carriage and insurance. 4ft. 40 watt, 39.6 plus 5/6 carriage and insurance. 3ft. 40 watt, 39.6 plus 4/6 carriage and insurance. 2ft. 20 watt, 39.6 plus 4/6 carriage and insurance. Circular 40 watt, 87 - plus 5/6 carriage and insurance. Circular 80 watt, 104.6 plus 5/6 carriage and insurance. These fittings are suitable for hanging or direct fixing—carriage and insurance applies for distances up to 250 miles, over and above this carriage will be extra.

Connecting Wire




P.V.C. covered in 100ft. coils—2.9 a coil or four coils different colours. 10/- post free.

Yaxley Switches

1 Pole 3 way	1/6
1 Pole 5 way	2/-
1 Pole 11 way	2/6
2 Pole 2 way ceramic	2/6
2 Pole 4 way	2/6
2 Pole 6 way	3/6
2 Pole 11 way	3/6
2 Pole 12 way	4/6
3 Pole 3 way	1/6
3 Pole 6 way	3/6
4 Pole 4 way	3/-
6 Position shorting	2/-
6 Pole 3 way	2/6
6 Pole 3 way ceramic	3/6
8 Pole 2 way	2/-
9 Pole 3 way	2/6
12 Pole 2 way	2/-

Building A Scope ?

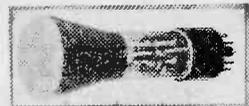

3in. oscilloscope tube American made Type No. 3FP7. Octal base 6.3 v. 4 amp. heater, electrostatic deflection. Brand new and guaranteed, 15/- each, plus 1/6 post and insurance. Complete with circuit diagram.

Battery Charger, Rectifier. Selenium 12.15 v., 5 amp., 12/6

Metal Chassis. Punched for Mullard 5V1 Amplifier, complete with inner screening sections and stove enamelled, 12/6 set.

Geiger Counter Tubes. 20th Century type, Type No. G24, with circuit of geiger counter, 29.6.

Heavy Duty Test Prods. Red and black with plug-in lead attachments, 8/6.

Metal Rectifier

80 mA, 300 volt, 5/6 each, plus post 1/-

Band III Converters



Suitable Wales, London, Midlands, North, Scotland, etc. All the parts including 2 EF90 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately. 1/6.

Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Luminous Switch, double pole designed for electric blankets, neon indicators glow when appliance is switched on. 10/-

Radio Stethoscope

This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete fault-finder. All the necessary parts to make this tracer 8/6, post 1/-.



Crystal Mike by Acos




Model 391, this is ideal for tape or general amplifiers, complete with screened lead 39/6, plus 1/- post.

"Dim and Full" Switch


Particularly useful for controlling photofood lamps which have only a short life at full brilliance. This toggle switch has three positions: the first position puts two lamps in series at half brilliance for setting up, the second position is off and the third position full brilliance for the operation shots. Also useful for controlling night lights, heaters, etc. etc. Price 3/9 each, post 9d. Circuit diagram included.

**Hi-Fi Snip
Infinite Wall Baffle**

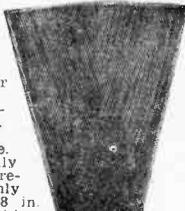Nicely veneered and polished. Corner fitting attaches to picture rail. Takes up no floor space. Gives really fantastic results with only low-priced 8 in. speaker. Fitting for tweeter. Only 45/- each, carriage and insurance 3/6.



£100 Worth of Equipment 19/6

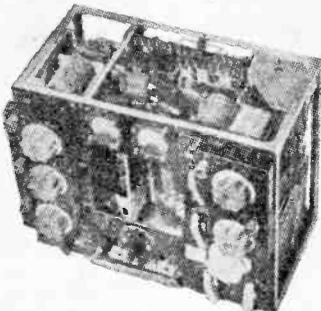

The famous R1154—unused but slightly soiled. Covers 200-500 kc/s, 3-5.5 Mc/s and 5.5-10 Mc/s. Has unique "click stop" mechanism. Wonderful breakdown value—meters, relays, switches. Complete with valves—real bargain at 19/6, plus 10/- carriage.

Car Battery Charger

Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 5 amps, and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.



Philips AG2009 Transcription Unit



Philips AG2009 Record Player, a modestly priced 4-speed unit with many outstanding features, is ideal for the enthusiast who is assembling his own equipment or modernising an older installation. The pick-up arm is wired for stereo and the Philips stereo head is available as an optional extra. Eddy Current Brake gives ±2% fine adjustment on all four speeds. Continuously variable pick-up playing weight (0-12 gms.). Supplied with Philips Hi-Fi crystal head, type AG3019 for microgroove and 78 r.p.m. Frequency response 30-15,000 c/s. Pick-up lifting and lowering device. Individually balanced heavy turntable. Muting switch fitted. Can be used with any amplifier or radio set. Complete with monaural pick-up, £10.10.0, or £1 deposit and 21 fortnightly payments of 10/-.



Available also with stereo head, diamond or sapphire stylus. Prices on request.

INFRA-RED HEATERS

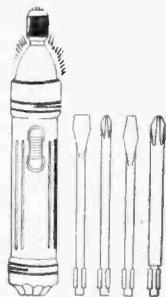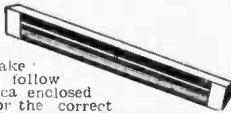These latest type heaters are ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and instructions 15/6, plus 2/6 post and insurance. Or made up heater 52/6 plus 3/6 post and insurance—fully tested and guaranteed.




**For Your
Service Department**

An invaluable tool for working inside a dark cabinet or cupboard. This is a screwdriver with torch and has four interchangeable bits, two for the ordinary slotted screws and two for Philips heads. The torch section operates from 1 1/2 v. batteries in the handle and will save its cost in frayed tempers alone. Why not treat yourself to one of these now? Only 10/6, plus 1/6 post and packing.

Morganite Potentiometers

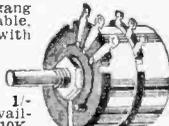Single and 2-gang types available, standard size with good length spindle, all new and boxed. Single types, 1/- each, values available: 5K, 10K, 25K, 50K, 100K, 250K, 1 meg., 2 meg. Gang type 3/- each—values available: 5K + 5K, 10K + 100K, 1 meg. + 1 meg., 2 meg. + 2 meg.




This Month's Snip

8in. P.M. Speaker in fabric-covered cabinet—size 10in. x 8in. x 4in. Price 29/6, plus 2/6 post and insurance.

Versatile Wire

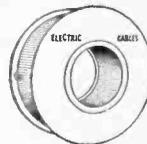Single-strand 18-gauge with P.C. covering which makes it rustproof. Extra strong, will stand tremendous strain. Ideal for gardening, clothes lines, indoor aerials, etc. Also being steel alloy and having a resistance of approximately 1 ohm per yard this can be used for electrical work, soil heating, wrapping round water pipes, etc. New on drum containing 3,000ft. Price 8/6, plus 3/6 carr.



T.V. Service Sheets

200 sheets covering most popular post-war televisions by leading makers—Cosor, Ekco, Ferguson, Pye, etc., £2, post free. PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200, £1, or 150-200, 10/-.

ELECTRONIC PRECISION EQUIPMENT LTD.

66, GROVE ROAD, EASTBOURNE, SUSSEX.

This is the correct address for post orders and for prompt attention please mark your envelope Dept. 7, also enough for postage.

Electronics (Manor Park) Ltd.
520, High St., North, Manor Park, E.12.

Electronics (Ruislip) Ltd.
32-46, Windmill Hill, Ruislip, Middx.
Phone: RUISLIP 3780.
Half day Wednesday.

Electronics (Croydon) Ltd.
266, London Road, Croydon.
Phone: CRO 6558.
Half day Wednesday.

Electronics (Finsbury Park) Ltd.
29, Stroud Green Rd., Finsbury Park, N.4.
Phone: ARCHWAY 1049.
Half day Thursday.

Every keen radio man must see it!

NOW COVERS RADIO-ASTRONOMY

FREE for 7 days
AND WITHOUT OBLIGATION

The long-awaited New Edition of this practical engineering and servicing work is now ready for you. If you are a Radio Engineer, Technician, Mechanic, Instructor, Student or Keen Amateur, this great wealth of data will prove invaluable. Newest developments and techniques are included—from latest transistors to low noise micro-wave devices: from advances in quality reception to radio-astronomy and space probe communication. Be up-to-date by sending to-day for **FREE EXAMINATION**. This New Edition is of absorbing interest to you—*post coupon to-day!*


PACKED WITH DATA FOR DAY-TO-DAY NEEDS—WRITTEN BY 50 SPECIALISTS

Formulae. Calculations. Communication Theory, Electron Optics. Colour, Projection and Industrial T.V. Materials. Studio Equipment. Transmitter Power Plant. V.H.F. Transmitter-Receiver Equipment. Amateur Equipment. Waveguides. Receiver Design. Radio Links. Broadband Systems. Radio Navigation & Radar. Radio Astronomy & Satellite Communication. Valves. Cathode-Ray Tubes. Transistors. Crystal diodes. Resistors. Capacitors. Inductors. Transformers. Microphones. Gramophone Mechanisms. Loudspeakers. Interference. Recording. Measuring Instruments. Installation & Servicing. Ionospheric Forecasting. Units & Symbols. Developments, etc.

SEE THESE PRACTICAL FEATURES

Latest types of Transistors and their use • Single-Sideband Transmitters • V.H.F. Scatter & Meteor Burst Communications Systems • Travelling Wave Tubes • Radio Astronomy • Modern Car Radio Receivers • Stereophonic Reproduction and Recording Techniques • T.V. & Radio—latest Practice in Receiver Installation and Servicing • New Air Navigation Aids.

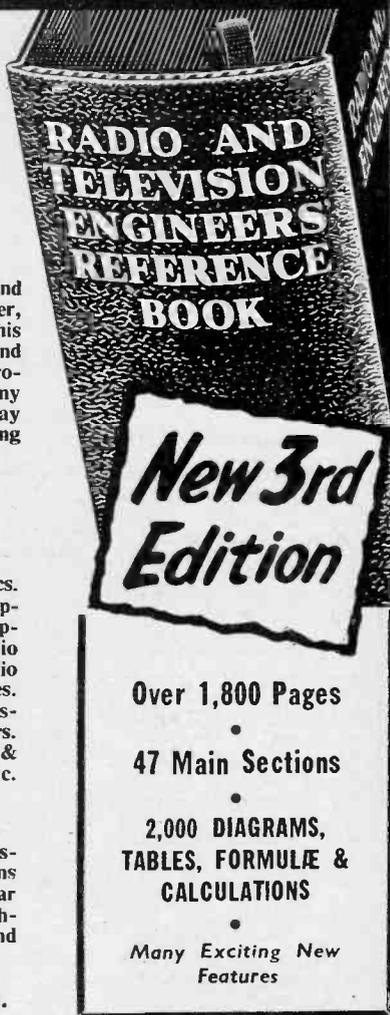Broadcasting • Communications • Navigation • Radar, etc.



Over 1,800 Pages
•
47 Main Sections
•
2,000 DIAGRAMS,
TABLES, FORMULAE &
CALCULATIONS
•
Many Exciting New
Features

JUDGE FOR YOURSELF
Post Now for 7-day Free Test!

GEORGE NEWNES, LTD., 15-17, LONG ACRE, LONDON, W.C.99.
Please send me Newnes RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK without obligation to purchase. I will either return the work within eight days or I will send the first payment of 5/- eight days after delivery, then ten monthly subscriptions of 10/-, until the sum of 105/- has been paid. Cash price within eight days is 100/-.

Name
Address

Occupation
Your Signature
(Or your Parent signs if you are under 21)

Tick (✓) where applicable

HouseOWNER	
Householder	
Living with Parents	
Lodging Address	

RB28

Here are some new models



F.M. TUNER
£13.12.6

R.F. TUNING UNIT
and I.F. AMPLIFIER AVAILABLE SEPARATELY



RP-1U
£12.10.0



"PACKAGED DEALS"

The above models and others can be obtained as parts of "packaged deals" of **MATCHED STEREO HI-FI EQUIPMENT**, thereby saving you additional money.

FREE DELIVERY IN U.K.
DEFERRED TERMS AVAILABLE
OVER £10.

TRANSCRIPTION RECORD PLAYER. Embodies new Collaro RP594 unit with the Ronette Stereo Pick-up. Gives excellent results on stereo or mono. (16, 33 $\frac{1}{2}$, 45 L.P. or 78 r.p.m.) discs. Detachable head and supplied with wooden plinth.

THE "COTSWOLD." An acoustically designed 3-unit Speaker System capable of doing justice to finest programme sources. Range 30-20,000 c/s. All parts left "in the white" for finish to personal taste.



THE "COTSWOLD"
£19.18.6

THE "GLOUCESTER" cabinet has been specially designed to meet the varying needs of different homes. Mk. I houses Record Player Stereo Amplifier, F.M. Tuner and records, etc. The Mk. II will house a Tape Deck in addition.



THE "GLOUCESTER"
Mk. I £15.18.6
Mk. II £17.8.6

Why not send for Free Catalogue !

Other models include

TRANSISTOR PORTABLE model UXR-1. This dual-wave, 6 transistor portable radio, strikingly styled in handsome solid leather case, is universally admired. The tone is rich and brilliant and it performs well everywhere, including in a car. Easily built in 6 hours. **£15.18.6**

(Car aerial attachment available 5/- extra)
TRANSISTOR JUNIOR RADIO model UJR-1. Ideal for youngsters. Novel circuit gets lots of stations. **£2.16.6**
N vel headph ne circuit gets lots of stations. (Additional amplifier stage, 16/6 extra)

HI-FI 16 W. STEREO AMPLIFIER model S-88. World's finest 16 Watt Stereo amplifier regardless of price. 0.1% distn. at 6 W./chnl. The attractively styled S-88 has many excellent features **£25. 5.6**

HI-FI 6 W. STEREO AMPLIFIER model S-33. World's best value in low-price Stereo. 0.3% distortion at 2.5 W./chnl. ideal for average room. **£11. 8.0**

HI-FI SPEAKER SYSTEM model SSU-1. Ideal for Stereo in average living-room where cost must be low. Two speakers in the enclosure. Legs, £1.7.0 optional extra **£10. 5.6**

R/C BRIDGE MODEL C-3U. Measures Capacitance. 10 pF (0.0001 μ F) to 1,000 μ F ; Power Factor ; Resistance. 100 Ω to 5 M Ω and indicates leakage. Automatic Discharge Safety-Switch **£7.19.6**

AUDIO SIGNAL GENERATOR model AG-9U. 10 c/s to 100 Kc/s. Sine-wave output 10V f.s.d. down to 3 mV f.s.d. Less than 0.1% distortion (20 c/s to 20 Kc/s). Decade frequency selection. Decibel ranges, -60 to +22. 1% precision resistors **£19. 3.0**

VALVE VOLTMETER model V-7A. World's most popular VVM. Measures volts, ohms and decibels. D.C. sensitivity 7.3 megohms per Volt. D.C. input resistance 11 megohms. **£13. 0.0**

5 in. OSCILLOSCOPE model O-12U. This fine general-purpose 'scope has "Y" sensitivity of 10 mV/cm, and covers 3 c/s to over 5 Mc/s. Rise time is 0.08 μ secs or less. Timebase 10 c/s to 500 Kc/s in 5 steps. Electronically stabilised. Voltage calibrator **£34.15.0**

DIRECT READING CAPACITANCE METER model CM-1U. 4 $\frac{1}{2}$ in. meter scale calibrated in μ F and pF. Full scale deflection 100 micro-microfarads, 1,000 micro-microfarads. 0.01 microfarad, 0.1 microfarad **£14.10.0**

DX-100U AMATEUR TRANSMITTER. The most popular Amateur transmitter in the world. 100-140 watts output. 160, 80, 40, 20, 15 or 10 metres. **£78.10.0**

DX-40U AMATEUR TRANSMITTER. 40 Watts to aerial. Input power 75 W. C.W., 60 W. pk. C.C. 'phone. Provision for V.F.O. Designed by "Hams" for "Hams" **£29.10.0**

VARIABLE FREQUENCY OSCILLATOR model VF-1U. 10V output. Covers 10 to 160 metres. **£10.12.0**

JUST OUT! 12 W. Monaural Amplifier, Balun Coil Set, Tape Deck, 3" Service Oscilloscope.


Without obligation please send me **FREE CATALOGUE** (Yes/No).....

Full details of model(s)..... Deferred Payments (Yes/No).....

NAME (BLOCK CAPITALS).....
ADDRESS.....

DAYSTROM LTD., DEPT. PW. 3,
GLOUCESTER, ENGLAND
A member of the Daystrom Group, manufacturers of
THE LARGEST-SELLING ELECTRONIC KITS IN THE WORLD.

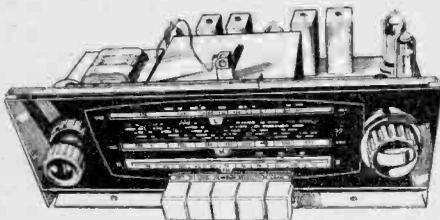BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.68. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price?

Tapped input 220-225 v. and 226-250 v. A.C. ONLY.

Chassis size 15" x 6 1/2" x 5 1/2" high. New manufacture.

Dial 14 1/2" x 4" in gold and black.

Pick-up, Extension Speaker, Ab. E. and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested.

With all valves & O.P. Transformer. Tone Control Fitted.

Covers 1,000-1,900 M. : 200-500 M. : 88-98 Mc/s.

Valves EZ80 rect., ECH81, EF89, EABC80, EL81, ECC85.

Speaker & Cabinet to fit chassis. 47 6/-

10" x 6" ELLIPTICAL SPEAKER, 20/-

TERMS:—(Chassis) £4.16.8 down + 10/- carr. and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.8.2 down and 7 Monthly Payments of 32/-.



COMPLETE RADIO FOR ONLY £10.10.0 carr. pd.

Size 19" x 13" x 7 1/2" or Chassis and dial for £8 (carr. pd.). Chassis Size 15" x 6 1/2" x 5 1/2"; 1,000-2,000 M.; 200-500 and 16-54 M. Mains (200-250 v. A.C.) and O.P. Trans. (3 ohm); Gram., Aer., E., Ext. L.S. Sockets; New Mullard Valves ECH42, EF41, EBC41, EL41, EZ40 and Magic Eye EM81. Dial 15" x 3". Fully aligned. Fantastic value for money.

3 1/2" or 6" x 4" speaker fitted to cabinet.

BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK range). 90 v. 15 ma. and 1.4 v. 125 ma. 42/6 (2/6 post). 200-250 v. A.C. Size 5 1/2" x 3 1/2" x 2". Also for 250 ma. 1.4 v. and 90 v. 15 ma. at same price. Specify which, or give valve line-up.


TELERECTION. "Twenty-20" adjustable set top or table aerial for Bands 1, 2 and 3. "Gold" finished rods and mounting. List Price 42/- . Our price 30/- (carr. paid).

50 SILVERED MICA AND CERAMIC CONDENSERS, 10/- . 50 RESISTORS, 5/- . ALL DIFFERENT VALUES.



COMPLETE TAPE RECORDER FOR ONLY £19.19.0

B.S.R. deck. Two-tone leatherette case. Acos crystal mike, 850ft. tape extra spool. On/Off Tone and Vol 7 in. x 4in. Speaker, 1 1/2 hrs. playing time. Single speed 3 1/2 in./sec., fast forward and reverse, mike and radio inputs, ext. speaker socket; cannot be accidentally erased. 13 1/2 in. x 12 in. x 8 in. Weight 20 lbs. 12 months' guarantee. Carr. 7/6 extra. Terms: £8 down and 6 monthly payments of 50/-.

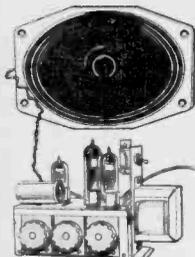

3-VALVE AMPLIFIER (INCL. RECT.).

Capable of giving 6 watts. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2" x 3" x 2 1/2". 6 1/2" round or 6" x 4" elliptical speaker, state which.

67/- (3/- p. & p.).

Large selection of complete Radiograms, ready built in cabinets, with 4-speed Autochanger. Write for details, giving approximate size required. Price from £25 for A.M. only, or £32 for A.M./F.M.

GLADSTONE RADIO—58A, HIGH STREET, CAMBERLEY, SURREY. Tel. 22791



LISTEN WITHOUT INTERFERENCE

Fully built V.H.F./F.M. Tuner for £5.10.0 (3/- post). Covers 88-98 Mc/sec. Wired, aligned and tested. 4 Mullard valves; for use up to 40 miles from transmitter. FRINGE MODEL for above this (5 valves), £8 (p. & p. 3/-). External H.T. and L.T. supplies road for both of foregoing. BUT, a complete V.H.F. set, fringe model, with mains transformer, amplifier, rectifier and speaker (with above frequency coverage) can be supplied for ONLY £8.8.0 (4/- carr.). Cheap room dipole 10/- . 300 ohm twin feeder, 6d. yd. All with 12 months' guarantee.



GRAMOPHONE

AMPLIFIER with 5 in. SPEAKER. On Fabric-covered Baffle 12 1/2" x 5". Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.

ONLY 57/-, post 3/-

BERIC "PIONEER" RADIO IN MAKER'S CARTON.


Valves DK96, DF96, DAF96, DL96. Beric Ever-Ready Battery B103, 18/6 extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12" x 7 1/2" x 6". ONLY £4.10.0 (2/6 p. & p.) (MW and SW £4.15.0 plus 2/6 p. & p.). In kit form with instructions and fully wired coil pack. Two Short Wavebands £4. One M.W. and S.W. £4.5.0. Plus 2/6 p. & p. Separate items supplied.



TAKE A CHANCE. We have surplus to present manufacturing requirements (tens of thousands of resistors, silvered mica, tubulars, volume controls, electrolytics, valve holders, etc.) SEND US 20/- for a bargain parcel of new goods. Our good name is your guarantee. Money back if not satisfied. State preference of types of goods.

SIX TRANSISTOR SUPERHET KIT £8.19.6

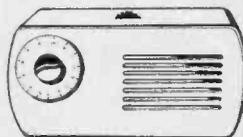Med. and L.W.; Printed Circuit; Instruction Book. Internal aerial. All items supplied separately. Write for price list. Battery, 3 v., PP4, 2/6.



Send 6d. (stamps will do) for our illustrated catalogue of the above items and others. All New Goods. Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.) SEE SPECIAL TERMS FOR A.M./F.M. CHASSIS AND TAPE RECORDER.

Practical Wireless

VOL. XXXV, No. 637, MARCH 1960

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1960.

Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year
Inland - - - - £1.3.0 per annum
Abroad - - - - £1.1.6 per annum
Canada - - - - 19s per annum

Contents

	Page
Editorial ...	925
Round the World of Wireless ...	926
The D.C.2. Stereo Amplifier ...	928
A Quality F.M. Receiver ...	931
An Inductance Measuring Instrument ...	933
A Novel Circuit Technique... ..	936
On Your Wavelength... ..	939
Measurements with Multi- range Meters ...	940
Experimental S.W. Three ...	943
A 6K7 Superhet... ..	947
The Magic Needle ...	949
Versatile V.F.O. ...	951
A Comprehensive Pre-amp ...	952
Transistors for P.A. ...	955
A Transistorised Voltmeter... ..	958
The "No. 19 Set" ...	961
Transistorised Timing Unit ...	965
Switch-tuned T.R.F. ...	966
Club News ...	973
News from the Trade ...	977
Open to Discussion ...	981

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

RADIO TELESCOPES

DURING the course of this year, wireless will play an important part when the first practical steps are taken to try to discover whether or not life exists elsewhere in the universe. The radio telescope at Green Bank, U.S.A., will be used by scientists who will listen for radio signals coming from other solar systems. Ever since scientists first made optical telescopes and probed the heavens, the great size of the universe has become more and more apparent, and now it is realised that its enormity cannot be comprehended. It has been supposed that there must be many other worlds similar to our own in which live intelligent beings similar to ourselves, and it is reasonable to assume that any signals transmitted from such worlds would aim at establishing contact with others and therefore would consist of definite sequences.

Naturally, it would be difficult to monitor more than one specific frequency and it is assumed that the wavelength used for the transmissions would be 1,420Mc/s. This frequency is known as the hydrogen line frequency and could be called the most popular frequency in creation since most of the matter in space is neutral hydrogen. Once the frequency of transmission has been assumed, the problem of monitoring becomes easier, although the difficulty now arises of detecting any deliberate modulation at that frequency. Owing to inter-galactic noise and other sources of signals, the detection of pulses may not prove easy. If, therefore, any of the other radio telescopes in the world were tuned to this frequency during their normal programme of work it is unlikely that signals would be detected, even if they were being transmitted. It is unlikely that the Jodrell Bank radio telescope will be used for monitoring space signals in the near future as it is heavily committed to its programme of research in radio astronomy and the tracking of earth satellites and moon probes. Jodrell Bank has a much larger range than the Green Bank telescope and will receive signals from at least 700 light years away and perhaps more and may be at present less suitable than Green Bank for the purpose in mind. The Green Bank telescope will be focused first on the nearest suitable stars. These are some 11 light years away—about 66 million million miles from us.

If there is intelligent life elsewhere in the universe it is reasonable to assume that radio will be the medium used for communication, although the speed of communication will not be as great as might at first be thought. Radio waves travel at 186,000 miles per second but even at this speed it might take 11 years for the signal to reach us and we might have to wait 22 years before we would receive a reply to any signals which we might transmit. In view of the delays involved, the transmission of signals at this juncture seems hardly worthwhile unless a very far-sighted policy is envisaged. The programme at the moment must be one of passive reception and the most that can be expected in the near future is the confirmation that some form of life exists elsewhere in the universe.

Our next issue, dated April, will be published on March 4th

Round the World of Wireless

POTENTIAL AND CURRENT NEWS

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of November, 1959, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include licences issued to blind persons without payment.


Region	Total
London Postal... ..	846,739
Home Counties... ..	817,455
Midland... ..	604,910
North Eastern... ..	691,772
North Western... ..	558,805
South Western... ..	485,796
Wales and Border Counties... ..	299,837
Total England and Wales	4,305,314
Scotland... ..	507,208
Northern Ireland... ..	148,266
Grand Total	4,960,788

British Equipment for Peru

THE Smethwick (Staffs) firm of Hadley Telephone and Sound Systems Ltd., is providing a staff location installation for a new hospital in Mollendo, Peru. The equipment, which consists of an amplifier, a moving coil microphone, 16 cabinet and 15 spherical type loudspeakers has been ordered from the British firm by Sociedad Relojera SA, of Lima, and will go into the Arcequipa Hospital in Mollendo.

British Standard 448

THE B.S.I. announces the publication of another two Sections (B5G/F and B7E/F) to B.S. 448, "Electronic valve bases, caps and holders." The new sections specify the base and bulb outline dimensions of the B5G/F and B7E/F sub-miniature valves with flexible connecting leads. Gauges for checking the lead spacing and the bulb outline dimensions are also specified. Copies of this Standard may be obtained from the British Standards Institution, Sales Branch, 2, Park Street,

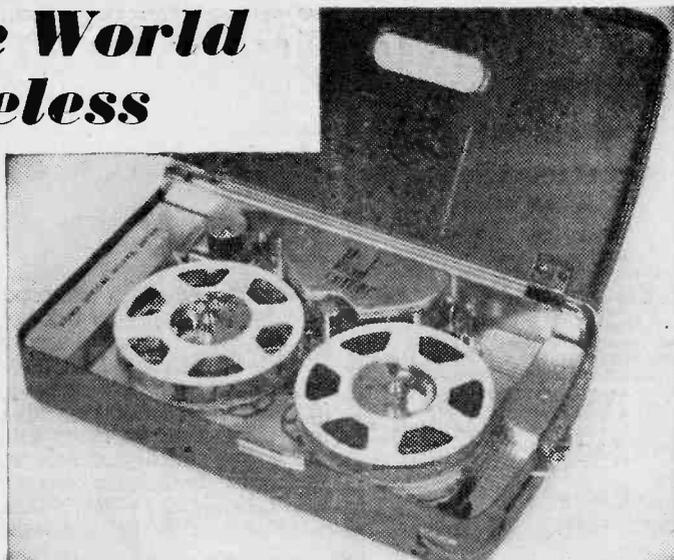

This Kowa Microrecorder is claimed to be the smallest tape recorder in the world. Developed by the Kowa Optical Works of Japan, and produced by the Kowa Electric Laboratory in Nagoya, it can be used for 30 minutes uninterrupted recording on a double-track tape, which is reversed automatically when recording on one track has been completed. It is an all-transistor recorder with playback, and weighs 780 grams. Accessories include a telephone pick-up, "secret" wristwatch microphone, earphones and speaker.

W.I. Price 2/- each. (Postage extra to non-subscribers.)

Electronic Computing for B.P.C.

AN order for one of the largest electronic computing systems in the United Kingdom has been placed with Ferranti Ltd. by the British Petroleum Company Limited. The system, costing over £1 million, will also be one of the fastest in the United Kingdom for processing data as it is based on the Ferranti Mercury computer, at present the fastest machine manufactured in Western Europe. The extensive ancillary equipment includes a converter unit which transfers information from magnetic tape to punched cards and vice versa, and facilities for printing data from magnetic tape on very high speed printing units. The system will be used by the British Petroleum Co. for both scientific and commercial applications. It is anticipated that the system will be installed in one of the company's head office buildings in London around the turn of the year 1960/61.

U.H.F. Systems for S.A. Navy

A SUBSTANTIAL order for a multi-channel medium and high power communication equipment has been placed with Plessey International Limited by the South African High Commissioner in London. The equipment will be installed on South African Navy fighting ships for ship-to-ship and ship-to-shore communication. The placing of this important order follows the success of similar Plessey U.H.F. sets on ships of the British and Commonwealth navies. The order was negotiated in South Africa by representatives of Plessey International Limited.

Radio Trades Examination Board

AT the annual general meeting of the board on December 30th last, Mr. Edwin Arthur William Spreadbury, M.Brit.-I.R.E., was elected chairman in succession to Mr. E. M. Lee, B.Sc., M.I.E.E. (Belling and Lee Ltd.). Mr. Spreadbury has been associated with the R.T.E.B. since June, 1943, when he was appointed an examiner and a

member of the examinations committee. Subsequently, he became a member of the committee which drafted the scheme of examination in television work, the first examination being held by the board in 1950. In recognition of this work Mr. Spreadbury was elected to the council of management of the board in 1947.

By reason of his technical articles and books, Mr. Spreadbury is well known to the industry and the trade for his interest in promoting higher standards of servicing efficiency. He has been connected with the radio industry since 1922. He joined the staff of the Wireless Trader in 1937 and is now the technical editor.

Radio-telephones for Mexico

AN initial contract has been signed with Pye Telecommunications Limited for 500 two-way units and fixed station equipments. Many of these radio-telephones will be used for the extension of the existing public correspondence scheme, whilst others will be used for new private radio-telephone systems. It is anticipated that 1,000 mobile units will be required by Mexico this year, to a total value of £100,000. Pye has already supplied over 3,000 mobile radio-telephone units to Mexico.

Electrical Engineers Exhibition

THE Ninth National Electrical Engineers Exhibition will be opened by the President of the Board of Trade, the Rt. Hon. Reginald Maudling, M.P., at 12 noon on April 5, 1960, at Earls Court. Part of the "Marine Electrics" feature will be devoted to electrical and electronic equipment from Britain's renowned aircraft carriers, H.M.S. Victorious and H.M.S. Hermes. Also featured will be equipment as used in the S.S. Canberra, the largest liner built in British shipyards since the war. Exhibits will include the latest navigational aids, radar and radio communications equipment. An electroliner, believed to be the world's largest, will be suspended from the 110ft. high roof of the Exhibition Hall. It is built by William McGeoch & Co. and measures 75ft. in circumference. Its total loadings will be around

18,500W. Visitors will walk on the world's largest electrically heated carpet. Made by Thermanlay Ltd., it covers over 1,000 sq. ft. and will have a loading of more than 11,000W. For the first time there will be a feature of outdoor electrical equipment. An area of over 5,000 sq. ft. will be devoted to heavy transformers built by the English Electric Co. Ltd.


East Pakistan Contract

THE Commissioners of the Port of Chittagong, East Pakistan, have placed an order with Marconi's for the establishment of a V.H.F. radio-telephone network to improve ship-to-shore communications within the port area and the Kharnaphuli river. Besides the installation of duplicate V.H.F. transmitters and

equipped to enter or leave the port in full radio communication with the port authorities.

Change of Name

ON the 1st January, 1960, the British Thomson-Houston Company, Metropolitan-Vickers Electrical Company and Siemens Edison Swan Ltd. changed their names to Associated Electrical Industries (Rugby) Ltd., Associated Electrical Industries (Manchester) Ltd., and Associated Electrical Industries (Woolwich) Ltd., respectively. At the same time five new product divisions of Associated Electrical Industries were announced. They are as follows: (1) Cable Division; (2) Construction Division; (3) Telecommunications Division; (4) Radio and Electronic Components Division; (5) Instru-

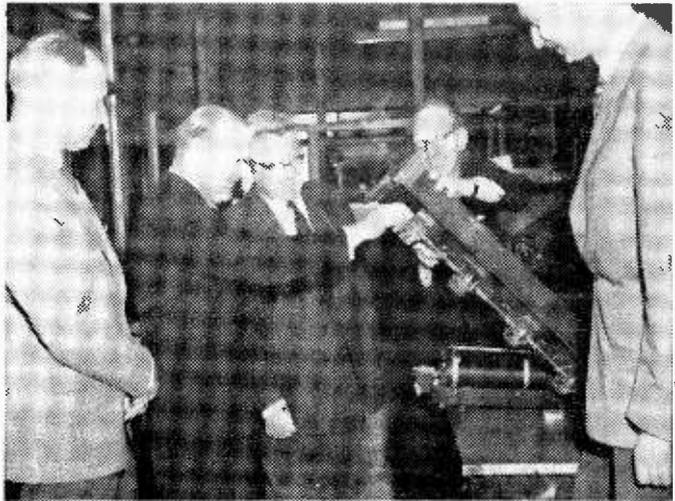

Marconi's Wireless Telegraph Co. Ltd., are designing and supplying the electronic equipment for a new air defence system for Sweden. Contracts worth approximately £1,500,000 have already been placed with the company. Recently a delegation of senior officials of the Royal Swedish Air Board visited the Marconi Works at Chelmsford and the Research and Development Laboratories at Great Baddow, in connection with the contract. Photograph shows (L. to R.) Colonel Hamilton and General Rapp of the Royal Swedish Air Board, Dr. E. Eastwood (Chief of Research, Marconi's), Mr. Keall (Marconi's) and Colonel H. Lindgren (Royal Swedish Air Board).

receivers in the shore stations at the port office and at the signal station at Juldia, the order also includes the supplying of mobile stations for use in two harbour tugs and a pilot launch. This installation will enable all visiting ships which are suitably

mentation Division. From the 1st January the total of A.E.I. Product Divisions to be established became 12, and the famous companies whose names are to change will cease to trade, but will manage a number of A.E.I. Product Divisions.

The D.C.2. Stereo Amplifier

A DIRECTLY COUPLED CIRCUIT

By J. S. Kendall

THE power required for listening in the average room is not great—in fact 2W is usually more than enough and even then this is only required on peaks. This stereo amplifier, the D.C.2, is directly coupled with negative feedback and an output of just over 3W per

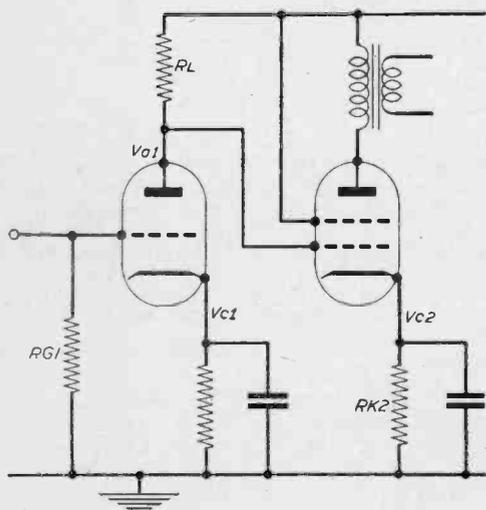
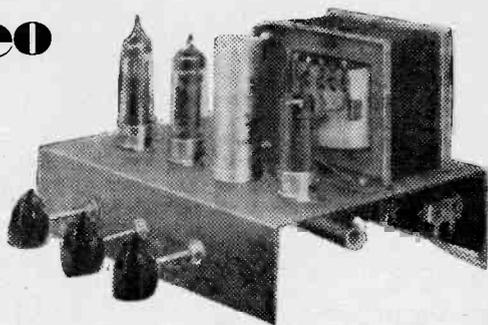


Fig. 1.—Theoretical circuit diagram.

channel. The distortion and noise levels are low. Three controls are provided: volume, tone and stereo/mono. This latter allows one single input to be fed to both channels so that they act in parallel.

Circuit

For this circuit twin direct-coupled amplifiers have been chosen. There are several reasons for this, one of the main being that from the grid of the input section to the anode of the output valve there is negligible phase shift from the lowest frequency to the highest. There is thus only one component in which phase shift can occur: the output transformer. Again, this phase shift has been reduced by the use of negative feedback. The total number of components is also low and construction for the beginner is simplified.

The basic circuit of each amplifier is shown in Fig. 1. It is drawn as a separate triode and pentode, which is correct although they are in the same glass envelope. The anode of the triode is strapped across to the control grid of the pentode section, and no stopper is used—the lead

is only about $\frac{1}{8}$ in., so none is required. Thus the anode voltage of the triode appears at the grid of the pentode.

If the reader is thinking of constructing his own directly-coupled amplifier, he should be warned not to attempt to work the drive valve at too low a voltage to allow it enough swing to drive the output valve correctly, and then attempt to clear up the matter with very heavy negative feedback. Allow an anode voltage of at least twice the r.m.s. drive voltage required by the output valve—within reason, the higher the better. The average power supply unit with a 250-0-250V transformer will give about 300-320V smoothed. Remember that the anode voltage of the drive valve and the normal bias voltage of the output valve have to be subtracted from this figure. A good figure for the anode voltage of the drive valve is 25 to 50V. The voltage at the cathode of the voltage output valve has to be the anode voltage of V1 plus the bias voltage of V2, i.e., $V_{k2} = V_{a1} + (\text{bias for } V_2)$. For example, H.T. line voltage is 300, the anode resistor for V1 is 220k and the anode current of V1 is 1.2mA. Thus, the voltage dropped across R1 would be 260. Thus, at the anode of V1 we would have $300 - 260 = 40V$. To this we have to add the value of the bias for the output valve—say, 6V which gives 46V. This, to the nearest 10 per cent., is 50V. Looking up the valve, we find, say, $V_a = 250V$, $I_a = 36mA$, $V_{g2} = 250V$, $I_{g2} = 4mA$. We add the currents together: $36 + 4 = 40mA$ and we can now, by a further

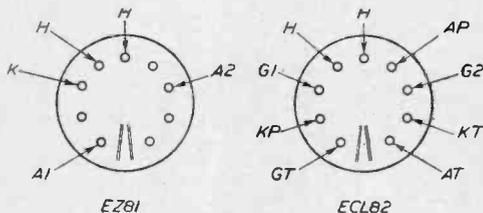


Fig. 2.—Valve base details.

simple calculation, calculate the value of the cathode resistor of V2 (Rk2). We have the voltage as 50V and the current at 40mA. Therefore, $R_{k2} = 1.25k$. Now, 1,250 ohms is not a preferred value of resistor. Therefore, we must

find the nearest 5 per cent. preferred value, which is 1.2k. The wattage rating is next to be found. In this case $W=EI$ is the formula to use. We have found E to be 50 and I as 0.04A (converting mA to amperes), so $50 \times 0.04=2W$. In this instance, as in all others where low drift is required, use a resistor that is well within its rating, say, 5W 5 per cent. wire wound. Next, having built the unit we have to test it. The

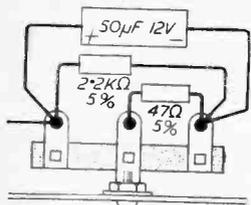


Fig. 3.—Wiring of the sub-assemblies for the triode stage.

critical reading is the one at the cathode of the output valve. The reading here is very rarely just as calculated even if we have made all our calculations correctly. The currents through the valves vary from valve to valve by quite a large amount, and also the conditions of the first valve circuit are reflected into the circuit of the second valve. It is the current through the output section of the valve that we have to watch, and bear in mind that we can expect a change in bias of 10V on the output valve for every 8mA change in Ia. Calculate the voltage drop across the valve and work out the power dissipated by it and check that this is not outside the ratings given by the manufacturers. If the errors are large, then corrections can best be made at the cathode resistor of the drive valve. To increase the resistance here will have the effect of increasing the cathode voltage of the output valve, a decrease will also cause a decrease in the output cathode voltage.

Readings

When taking voltage readings on direct-coupled amplifiers, remember always to have the volume control set at the same point. All valves take a minute amount of grid current by what is known as secondary emission. This minute current, so small that it can usually be ignored, gives a voltage across the input resistor of the amplifier—usually the volume control, and is amplified by the first valve. Thus, say, the current is one-hundred-millionth of an ampere, and we use a 1M volume control, then the voltage is 1/100th and this amplified, say, 50 times by the valve gives 1/2V. With a modern output valve that can cause a definite change in current. However, with a new valve, it can be ignored, but with a valve that is older and softer, the figure will be ten times as high.

Construction

First the valveholders should be fitted to the chassis. Then, as all the transformers are also

associated with tag strips, next fit the mains transformer, and under the two nuts of the fixing bolts at the valveholder side, fix a three-way tag strip. The transformer should be fixed so that the H.T. and heater windings are at the valveholder side, and the mains tags to the rear of the chassis. Shake-proof washers should be used under the tag strips in order that a good connection to the chassis is made—simple, but important. The H.T. and heater wiring may now be made. Fig. 2 shows the base of the EZ81 rectifier valve. Run two wires (twisted for preference), one from each of the 300V secondary to one of the anodes of the EZ81—i.e., one 300V to A1 and the other to A2. Next, take a pair of wires from the 6.3V heater winding (top right-hand set of tags on the transformer) to the heater tags of the valveholder; ignore the tag marked 5V and use the common and the 6.3V tags.

Next, take a wire from pin 3 to pin 4 of the valveholder, and solder all the leads so far wired except the wire to pin 3. Next come the heaters of the other two valves—the ECL82s. The base wiring is shown in Fig. 2. Run a pair of twisted wires from the centre tapped 6.3V on the transformer to the heater tags of the valveholders—pins 4 and 5—then solder them. Next solder a wire on the mains transformer from the centre tag of the 300-0-300V winding to the centre-tap tag of the 6.3V winding and then on and solder to one of the fixing bolts of the mains transformer.

Sub-assemblies

Next make up two small sub-assemblies—these consist of a three-way tag strip, with an electrolytic and two resistors. They form the bias and negative feedback resistor for the triode sections of the ECL82 valves. 50µF, 12V electrolytics have

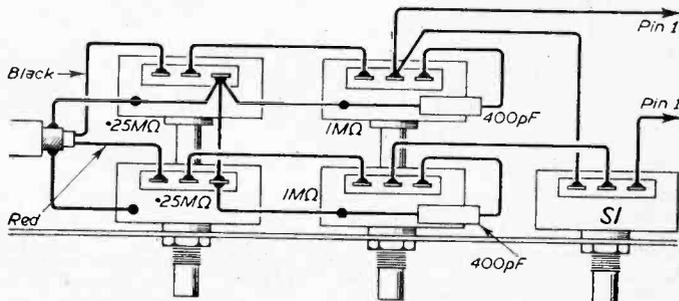


Fig. 4.—Tone and volume control stages.

been chosen and the resistors are of 5 per cent. tolerance. The reason for the use of 5 per cent. resistors has been explained earlier. The method of wiring the tag strips is shown in Fig. 3. A very neat job can be made of these if the wires are kept short—the view is as seen from the front edge of the chassis and the earthing tag is to the rear. At the right-hand end—the end with only the 2.2k and the electrolytic—solder a short length of wire—2in. is ample and it should be insulated. Next fix the four jacks in place, one in each of the four 1/4in. holes at the rear of the chassis.

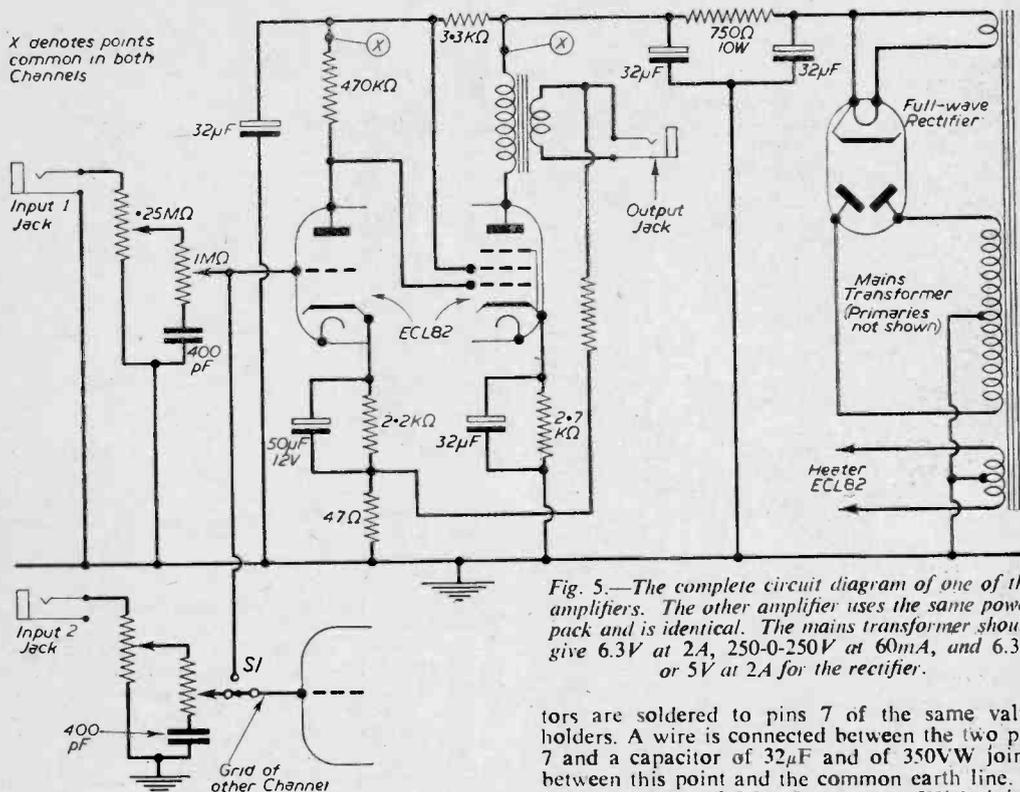


Fig. 5.—The complete circuit diagram of one of the amplifiers. The other amplifier uses the same power pack and is identical. The mains transformer should give 6.3V at 2A, 250-0-250V at 60mA, and 6.3V or 5V at 2A for the rectifier.


It is best to have the tags pointing in the same direction as the flange of the chassis. We can now fix the two output transformers in place. They are bolted in place with the tags pointing to the centre of the chassis. The small sub-assemblies are bolted one under each of the fixing bolts of the output transformers at the end nearest to the valveholders. We can now take the wiring a few steps further. Join the running wires from the sub-assemblies to pin 8 of the nearest ECL82. Join a wire from the inner tag of an output jack to the tag at the valve end of the nearest output transformer, and a 100Ω resistor from the same transformer tag to the junction on the sub-assembly of the capacitor, the 2.2k and the 47Ω resistor. Solder and repeat with the other transformer.

Final Wiring

Next, run a length of tinned copper wire through the four sleeve tags of the jacks (those are the tags at the fixing end of the jacks) and solder. Join the two nearest tags of the output transformers to this common earth line and solder. Take two 470k, 5 per cent. resistors and bend the wires sharply back about $\frac{1}{4}$ in. from the body of the resistors and solder the bend to pin 9 of the two output valves—one on each—the free end of the wire is taken to pin 3 and soldered. This fixes the resistors in position and joins pins 3 and 9. The wires from the other ends of the resis-

tors are soldered to pins 7 of the same valveholders. A wire is connected between the two pins 7 and a capacitor of 32μF and of 350VW joined between this point and the common earth line. A further resistor of 3.3k, 5 per cent., 3W is joined between the same point (+ve side of electrolytics, two 470k resistors and two tags 7 on the ECL82 valves) and one of the pins of the 32 + 32μF block electrolytic. Do not solder this last wire yet. At the inner side of the inner output transformer, the tag of a double 32μF capacitor is joined and soldered to the common earth line. It is simplest to follow if the two tags are placed in a horizontal plane so that one can be referred to as the left and the other as the right. To the left and nearly touching the capacitor is a three-way tag strip. From the right-hand tag of this, fix a wire to the left-hand tag of the 32 + 32μF, and between the same tag and the earth line fix a 2.7k wire-wound 5 per cent. resistor of 7W rating. Strap pin 2 of the nearest ECL82 to the junction of the resistor and capacitor and solder. Between the right-hand tag of the same capacitor and the centre (earthed tag) of the adjacent tag strip join a 2.7k, 5 per cent., 7W wire wound resistor, and from the junction of the 2.7k and the capacitor join a wire to pin 2 of the other ECL82 and solder. To complete the H.T. circuit wiring, take a 750Ω 10W wire wound resistor and join one end of it to the right-hand tag of the extreme left tag strip, run a wire to the cathode of the EZ81 and a further wire from the same cathode to the unoccupied tag of the 32 + 32μF 450VW electrolytic. Then solder these. The other end of the 750Ω 10W resistor should be against

(Continued on page 944)

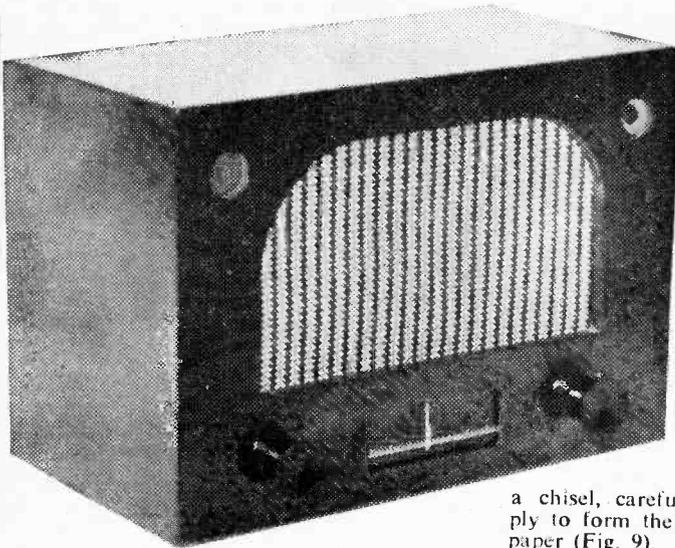

A Quality F.M. Receiver

MAKING THE CABINET

(Continued from page 848 of
the February issue)

By V. E. Holley

As stated in the previous article, a suitable cabinet for this receiver may be made from five-ply wood, $\frac{3}{8}$ in. thick, having an oak, walnut or similar facing.

Procedure

First mark out and cut the front, $13\frac{1}{2}$ in. \times 9 in. (Fig. 8) and cut the apertures for the speaker, tuning scale, etc. Those for the tuning indicator and panel light should first be cut from the faced side of the wood with a $\frac{7}{8}$ in. centre bit to a depth of about $\frac{1}{4}$ in. and completed from the other side with a $1\frac{1}{8}$ in. bit. The larger holes can be cut with a fret saw or hacksaw blade, working from the faced side. Sand the edges of all the

Cut next two pieces for the sides, 9 in. \times $7\frac{1}{2}$ in. each. Check that they are exactly rectangular and of correct and identical measurement—the fit of the joints and consequently the strength of the cabinet depend on it. The top and bottom of each side must now be rebated to receive the top and bottom of the cabinet. On the unfaced side of the wood draw lines very slightly more than $\frac{1}{8}$ in. from the edges and with a tenon saw cut carefully along the lines to a depth of three layers of ply, keeping the saw at right angles to the surface. If the constructor is not too confident with a tenon saw, it is a good idea to tack a strip of wood with a straight edge along the line of cut to act as a guide for the saw. With

a chisel, carefully remove the three layers of ply to form the rebate and finish off with glass-paper (Fig. 9).

Assembly

An exactly similar rebate must now be formed all round the four edges of the front of the cabinet, on the unfaced surface. Now assemble the front and two sides and measure the exact length of top and bottom required to fit into the rebates. Cut the top and bottom to this length and $7\frac{1}{2}$ in. wide; no rebating is required.

The top, bottom and sides should now be assembled temporarily on a flat surface, front downwards, using three lin. panel pins, driven not more than half-way home at each corner. The rebated front should be a good push fit. Dismantle, apply a good resin glue to all mating surfaces and reassemble, driving the panel pins

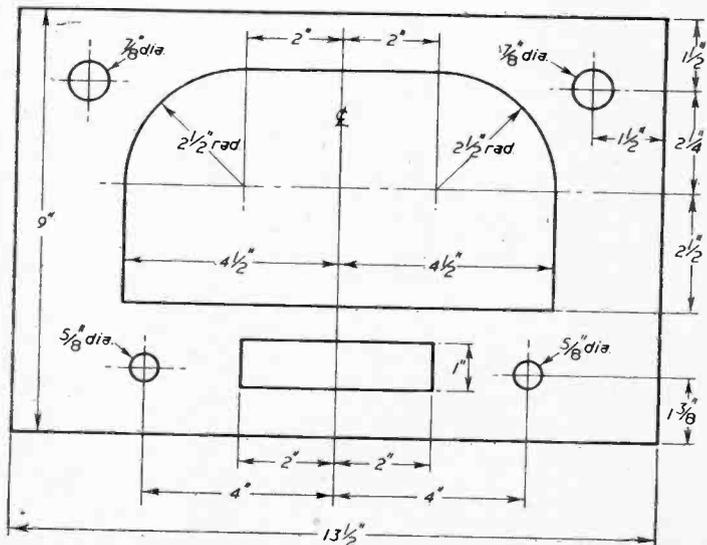


Fig. 8.—The front panel.

right home. Glue alone is sufficient to secure the front. Place the cabinet front up with a weight on top to keep the front firmly in position till the glue is hard.

Polishing

First punch in the panel pins till the heads are below the surface. A small wire nail with the point sawn off flat makes a good punch. Fill in the holes and any other blemishes with plastic wood of a suitable colour and when the filling is hard, give the whole cabinet a good rub down with No. 2 glass-paper, squaring off the corners and removing any old polish. Finish off with No. 0 glass-paper. The final result depends very largely on this preparation so make sure that no scratches or blemishes remain. Wood dye of the desired colour may now be rubbed in with a rag wad.

There are three methods of obtaining the final finish. The first and best is french polish, which is also the quickest. There is no need to view this with alarm as there are plenty of french polishes to be had which are specially compounded for amateur use and nothing more is required of the operator than that he should follow the comparatively simple instructions enclosed with the polish.

Another Method

The second method is to apply three or four coats of clear varnish, rubbing down with No. 0 glass-paper between each. A period of 24 to 48 hours must be allowed for the hardening of each coat. Varnish does not darken the wood. It should be applied and allowed to dry in a dust-free atmosphere.

Another alternative is shellac, which is an ingredient of most french polishes. Dissolve an ounce or so of gum shellac in methylated spirits to produce a liquid about the consistency of paraffin and apply rapidly with a brush. Do not

attempt to spray it. About six coats will be required with a rub down between each. The mixture dries rapidly and has some darkening effect on the wood.

Finally, a back should be made for the cabinet. This may be of $\frac{1}{4}$ in. plywood with suitable openings for connections and ventilation. To secure it, two $\frac{1}{2}$ in. panel pins may be driven into the bottom edge so that they project $\frac{1}{4}$ in. The heads

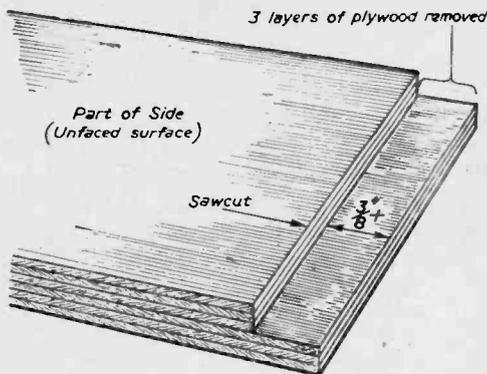


Fig. 9.—Forming the rebate.

can then be sharpened and pressed into the bottom of the cabinet. The top may be secured to small brackets or wood fillets fitted in the top corners of the cabinet.


Fitting the Receiver

Glue a piece of Tygan or other suitable material over the speaker aperture and cut a piece of thin plywood to shape and size to cover the aperture with $\frac{1}{16}$ in. to spare all round. In the plywood cut a $\frac{1}{2}$ in. diameter hole for the speaker in such a position that when fitted, the speaker will lie at the right-hand end of the aperture, looking from the rear, and three of the four securing screws will pass through the ply into the front of the cabinet. Attach the speaker to the ply at the fourth securing point, using a 4B.A. counter-sunk bolt, and fit the assembly into the cabinet with wood screws of suitable length.

The tuning indicator should be fitted to a bracket in the top left-hand corner, looking from the rear, and the panel light similarly in the opposite corner, a piece of coloured plastic being fitted into the hole through which the lamp is viewed.

The receiver may be secured in the cabinet by means of four self-tap-

(Continued on page 970)

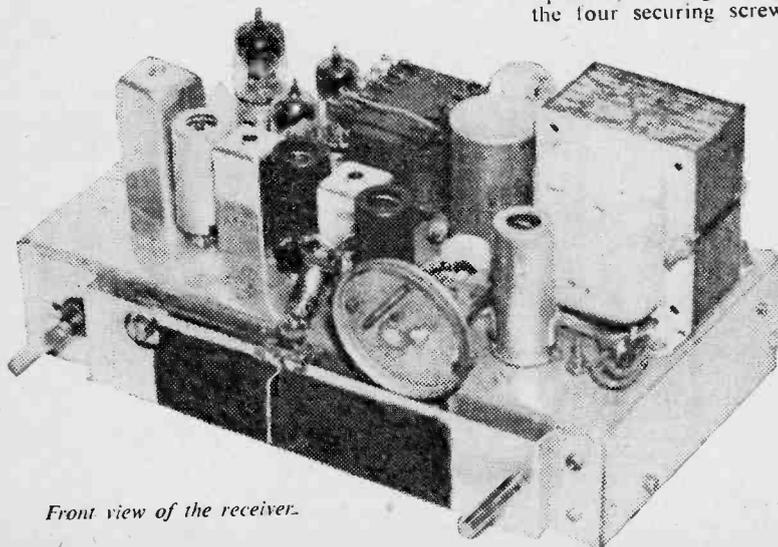

Front view of the receiver.

An Inductance Measuring Instrument

A D.C. BIAS SUPPLY IS INCLUDED

INTERSTAGE, and output transformers for use in transistor circuits are not difficult to make. The A.C. voltage applied across their primary winding is very much smaller than those used in valve circuits, and consequently the number of turns on the core is very much fewer than for a similar transformer used in valve circuits. If an output stage transistor is, say, working Class B from a 6V battery supply, the maximum collector voltage swing will be from 0 to -6 (see Fig. 1),

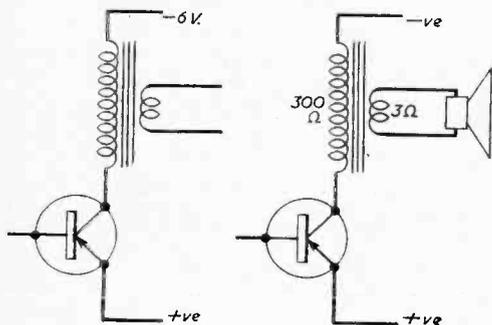


Fig. 1 (Left).—Amplifier circuit.
Fig. 2 (Right).—Transformer matching.

a total of 6V peak swing. This would correspond to a signal output of 6×0.707 —a little over 4V r.m.s. In practice, an output stage would not work Class B single ended, but in push-pull, but this example does serve to show the low voltage swing in transistor applications compared with similar valve circuits where the anode voltage swing may be of the order of 200 or more.

There are two main considerations in the design of such an output transformer:—

- (a) The correct matching of the transistor impedance to the, lower, loudspeaker impedance.
- (b) The shunt impedance of the transformer windings must be sufficiently high in order not to shunt the lower frequency output signals past the speaker.

These two latter points require expanding.

(a) Impedance Matching (A.C. Conditions)


Consider an OC72 output transistor working, single ended, Class A, into a 3Ω speaker (Fig. 2).

The equivalent circuit as far as the transistor is concerned is as shown in Fig. 3.

So, looking into the primary from the transistor, 300Ω should be seen. However, looking into the secondary from the speaker 3Ω should be seen.

This condition is achieved by impedance matching with a transformer of the correct turns ratio, which is given by

By D. Saul

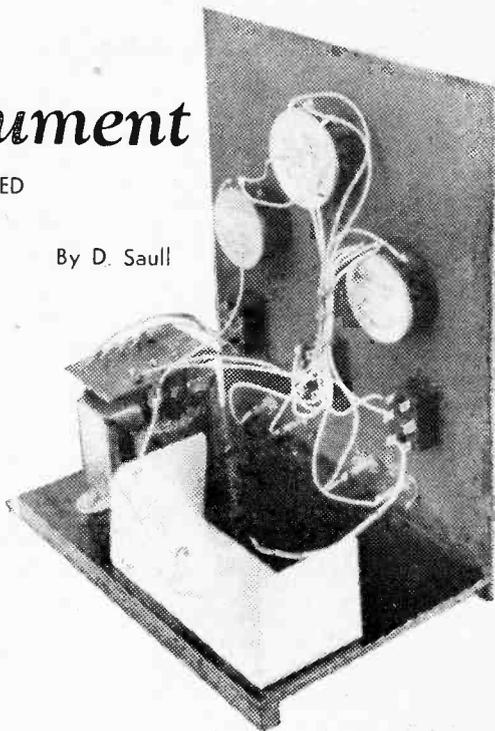

$$\text{Turns ratio} = \frac{\text{Load impedance}}{\text{Speaker impedance}} = \sqrt{\left(\frac{300}{3}\right)} = \sqrt{(100)} = 10$$

The primary must, therefore, have ten times more turns than the secondary, or, another way of putting it, the secondary winding requires ten times less turns than the primary. But, how many turns must the primary winding have in the first place? The answer to this question brings us to expansion (b).

(b) Shunt Inductance

An output transformer has a bandwidth, that is a range of frequencies which it will pass with

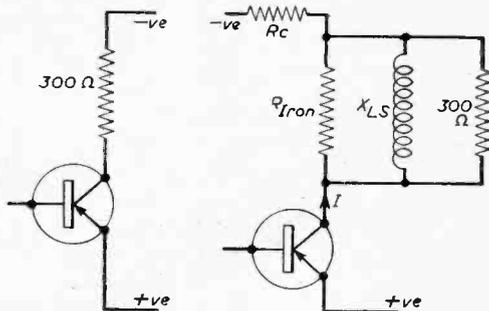


Fig. 3 (Left).—Equivalent circuit for transformer coupling. Fig. 4 (Right).—Simplified equivalent circuit for transformer loading.

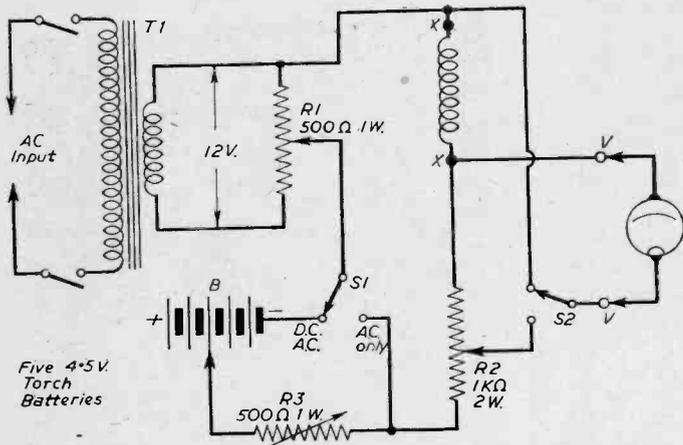


Fig. 5.—Complete circuit of the instrument.

The copper losses (D.C. resistance of the transformer windings), R_c , waste the signal output power (I^2/R_c). The resistance R_{IRON} (the iron losses in the transformer laminations) waste power also.

The power delivered to the 300Ω resistance represents the useful power that is delivered to the speaker.

X_{LS} represents the shunt inductance, the current which by-passes the 300Ω resistance and is not available for transfer to the speaker. This value requires to be kept as high as possible, and it will be noticed that X_{LS} is lowest for the lower frequencies of the signal (i.e., $X_{LS} = 2\pi fL$). In practice X_{LS} should not be less than twice the load impedance. For the transformer we have been considering about 250mH (this

equal attenuation. A moderate general purpose amplifier with single speaker will have a frequency range of approximately 100c/s-4kc/s.

The frequency response falls off at the higher end owing to leakage inductance and capacity between windings. At the lower frequency end this frequency fall off is due to shunt inductance.

The leakage inductance may be reduced by ensuring tight coupling between the windings and the core.

The shunt inductance effect may be reduced by ensuring that the primary inductance is high as possible.

Consider the simplified equivalent circuit for a transformer (Fig. 4) in the OC72 output stage being considered.

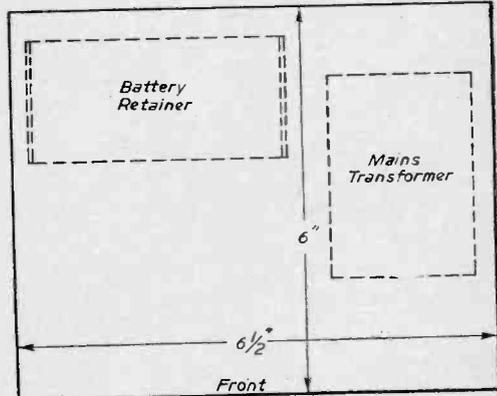


Fig. 7.—Chassis details.

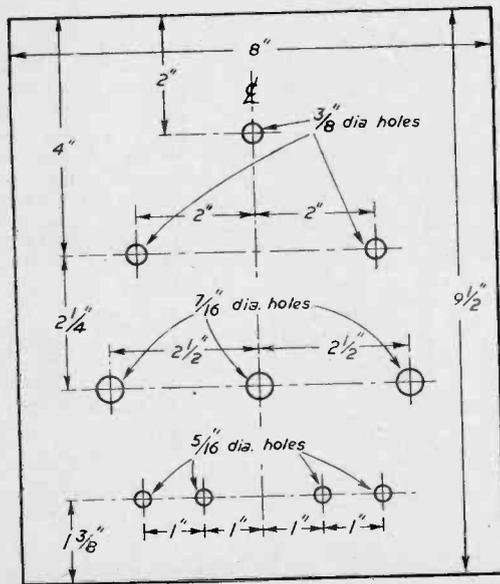


Fig. 6.—Drilling details of the front panel.

gives about 6dB down at 100c/s).

It should be remembered that the inductance of an iron-cored winding may vary considerably with the A.C. applied voltage although it is nearly independent of frequency over the audio range.

Besides the A.C. component in the primary of a transformer, there may be a steady value of D.C. which will tend to lower the inductance of the winding.

Circuit of Inductance Measuring Instrument

Difficulties arise when measuring the impedance of iron cored windings on conventional inductance bridges, for the following reasons:—

(a) The A.C. applied voltage to the test component is usually unknown.

(b) There is usually no provision for any D.C. component.

The circuit of the instrument (shown in Fig. 5) does measure reasonably accurately the reactance of iron-cored windings with a D.C. component flowing in the windings, up to 1k (3H) at 50mA D.C.

The circuit values may be amended if desired to cover other ranges.

The mains transformer T1 is a 12V filament transformer. Resistor R1 regulates the required A.C. voltage appearing across terminals X to which the unknown winding is connected.

The battery "B" provides the D.C. component and is made up of five 4.5V torch batteries in series (22V). The 500Ω resistor R3 is the fine control of the D.C. component, and should be kept at a low value, the coarse control of current being achieved by altering the battery tapping.

Switch S1 throws the measuring conditions from A.C. only to A.C. plus D.C. component.

Resistor R2 is a 1k wire-wound potentiometer which is calibrated in ohms against an ohmmeter.

Switch S2 is used alternately in the measure-

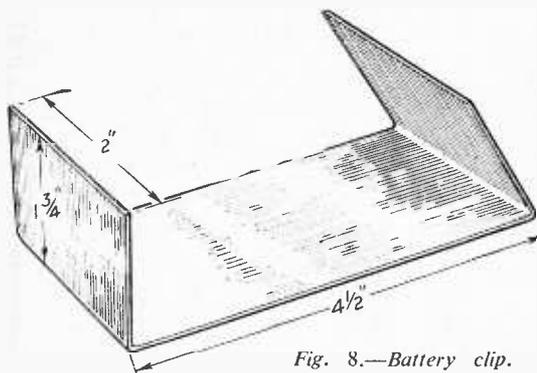


Fig. 8.—Battery clip.

ment of the A.C. voltage drop across R2 and the test winding. The voltmeter connected to the terminals "V" ideally should be a value voltmeter (an ordinary voltmeter may be used if of high resistance).

The accuracy of the instrument is dependent upon the calibration of R2.


Use of the Instrument

The inductance required to be measured is connected to terminals "X"; S1 is switched to A.C. plus D.C. position and the required battery tap selected to give the appropriate D.C. current. This value is measured by a current meter inserted in one of the battery leads.

The main switch is closed and with a value voltmeter connected to terminals "V," switch S2 is thrown from one position to the other and R1 and R2 adjusted until the value voltmeter gives the same reading in both positions of switch S2, and the voltmeter reading is at the voltage at which the component under test will normally operate under circuit conditions. The reactance of the winding is then read off the calibrated scale on R2.

Practical Layout and Construction

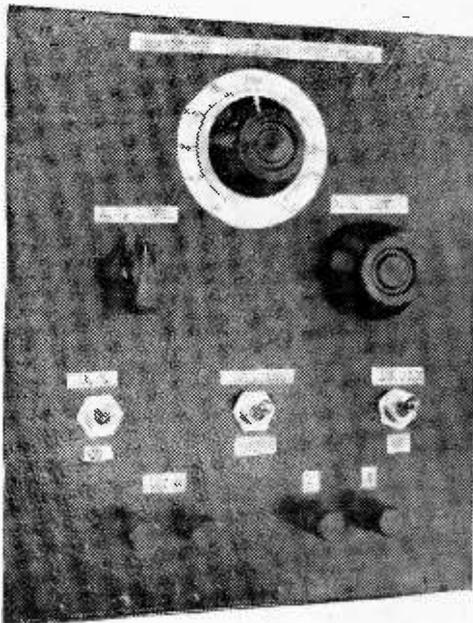The material used for the panel and base was hardboard, the marking out being shown in Fig. 6. The base was secured to the panel by means of a strip of $\frac{1}{8}$ in. \times $\frac{1}{2}$ in. wood glued and pinned to the base.



The front panel.

The panel after cutting to size and drilling, etc., was painted black. A suitable hardboard case could be made to enclose the instrument and covered with an adhesive-backed plastic material.

Radio Trades Examination Board Fifteenth Annual Report

THE Council of Management has pleasure in presenting this report which covers the work of the board for the year ended 31st August, 1959.

The main object of the board, which is to promote technical courses in radio, television and electronic servicing, has met with considerable success—measured in terms of the number of candidates entering for the board's examinations. In 1959 a total of 2,310 candidates sat the radio and television servicing examinations and this represents an increase of 33 per cent. on the number of candidates sitting the same examinations in 1958.

Unfortunately, this larger number of candidates did not provide the same increase in the number of successes, and in fact, in the Radio Servicing Examination there was a drop in the number of candidates qualifying for a certificate.

The relatively poor results in the Radio Servicing Examination have, however, been the cause of much discussion.


The written papers were very much below the normal standard and were the main cause of failure, and this inability to cope with theory undoubtedly resulted in many candidates failing the practical examination.

A Novel Circuit Technique

AN ALTERNATIVE TO PRINTED
CIRCUITS

By J. D. Ingleby

WITH the coming of "Hi-Fi" and the transistor, the home constructor is finding that the only stage at which he can exercise his skill and experience is in the assembly of a given circuit. Whether for better or worse, the art of improvising one's own circuit and components is rapidly becoming outdated, and the focus is increasingly on a neat and compact circuit. The printed circuit is the answer to this trend, and indeed most transistor superhet kits use this technique. However, making one's own printed circuit is an expensive and elaborate

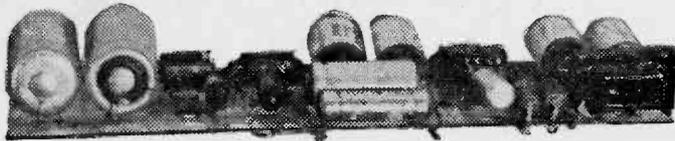

Another view of the transistorised amplifier.

procedure. This article describes a technique which retains the advantages of printed circuits, their economy of size and weight, strength and neatness.


Circuit Materials

This circuit technique uses, in place of a printed circuit board, ordinary celluloid or transparent plastic sheeting. This is obtainable at reasonable prices from model shops, hardware stores, radio dealers, or motor-cycle repair shops. It has the advantage that wiring can be done with the components in view, and furthermore that the components can be inserted simply by pushing the bent wire ends through the sheet with the tip of a hot soldering iron. This method of fixing is quite rigid, as the celluloid sets hard round the inserted end.

Method of Assembly

The transparent sheeting may be of any kind, with the following limitation: it must be rigid enough to hold the components firmly, but thin enough to allow them to pass through easily, 1/32in celluloid or "Corbex" sheeting is ideal. Most dealers have conveniently-sized offcuts, but large sheets are more economical in the long run.

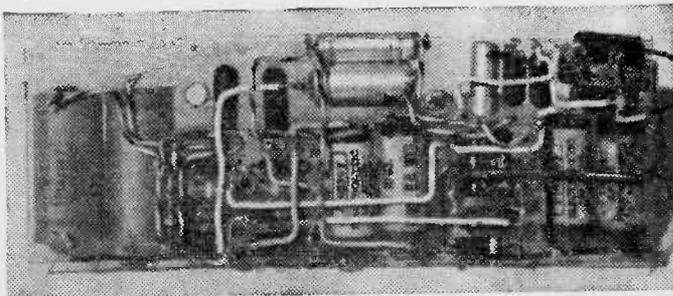The next step is to work out the layout of components from the circuit diagram. In doing this a compromise must be made between compactness and convenience, for the most



A transistorised amplifier built using the technique described.

symmetrical layout is seldom the easiest to wire. However, one advantage of transistorised equipment is that the components have all a more or less equal size, and thus a neat design is often practicable. The layout should be worked out on a piece of paper, which can be slipped under the board during construction.

When the celluloid has been cut to the required shape, using scissors, the components are shaped for insertion. This is done with a small pair of pliers, taking care not to damage the components. Transistor leads should not be bent too close to the seal, and resistors can crack if not handled carefully. Light pressure should be applied until the component sinks into the board; hold it in place until the celluloid sets firm. This may be done by using the plan as a guide underneath the board. It may be necessary to heat-shunt transistor leads with pliers or a crocodile clip, but with experience only a moment's heat need be applied. Transformers, coils, etc., may be either glued or bolted on. When all the components have been fixed on, turn the board over and trim all wire ends down to about 1/16in. long.

(Continued on page 948)

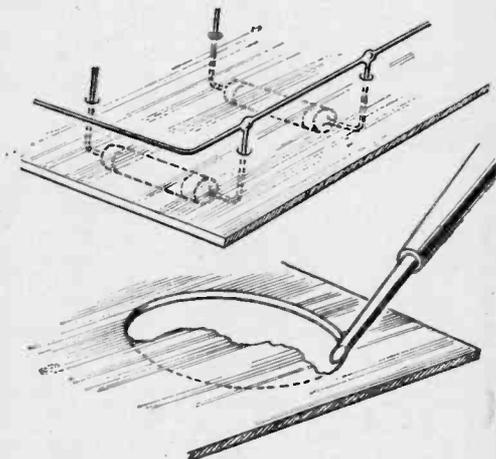


Fig. 1.—Method of fixing resistors and making holes in the plastic sheeting.


A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone
- ★ Erase and fast rewind

£13.12s

Special moving-coil microphone and tape extra.

EASY TERMS

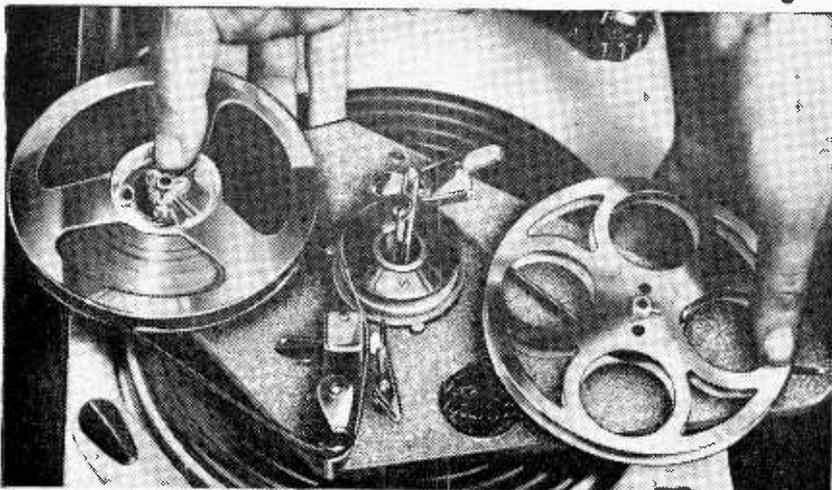

Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely new . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get a quality that has to be heard to be believed! Everyone is praising the Gramdeck.

"The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER. "A British challenge to Continental tape recorder firms—DAILY EXPRESS.

"Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."—BRITISH RADIO & TV RETAILERS REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

WORKS FROM ANY RECORD-PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.

MADE BY THE FIRM THAT MAKES RADAR EQUIPMENT FOR VISCOUNTS & BRITANNIAS



FREE BOOK—POST NOW!

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

(Write if you prefer not to cut page)

NAME

ADDRESS

Gramdeck

GRAMOPHONE TAPE RECORDER
HIGH QUALITY TAPE-RECORDING FOR EVERY HOME

Gramdeck (Dept. PA/806) 29 Wright's Lane
Kensington, London, W.8

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER

Brand new, individually checked and guaranteed VALVES

AC/DD 2/6	DH76 4/9	EM4 4/-
AC/CP 4/6	E1323 25/-	EY91 3/6
AC/PI 2/6	EA50 1/6	EZ40 7/6
ACSPENDD	EAC91 4/6	EZ80 7/6
	EB34 1/6	FW4/500 6/6
AC6/PENS/-	EBC33 6/-	H30 5/-
AC/SP3 4/6	EC52 3/-	H63 3/6
AL60 2/6	EC54 3/6	HP4101 6/-
AR6 2/6	ECC32 4/-	KBC32 5/-
AR8 5/-	ECC81 6/6	KF35 5/-
ARDD5 2/-	ECC82 6/6	KT2 4/6
ARP3 3/-	ECC83 7/-	KT31 8/-
ARP4 3/9	ECC88 7/9	KT33C 7/-
AR12 2/9	ECC91 4/-	KT44 9/-
AR24 3/6	ECL80 9/6	KT241 9/-
ARP31 3/6	EF22 7/3	KTW63 6/6
AV4 5/-	EF32 5/-	L30 4/6
SRP34 4/6	EF36 3/6	MH4 3/6
STP4 2/9	EF39 4/6	ML4 4/-
ATP7 5/6	EF50 2/6	ML6 6/-
AUI 5/-	EF52 5/-	MC/PEN 6/-
AW3 4/-	EF54 3/6	MC/PEN/6/-
BL63 6/-	EF55 6/-	MS/PEN/T
BT45 40/-	EF70 4/9	
BT9D 40/-	EF80 6/-	N34 8/-
D41 3/3	EF85 6/10	NR15A 3/-
D42 4/-	EF89 8/9	MT37 3/-
D77 4/3	EF91 4/10	(4033A) 10/-
DA30 12/6	EF92 5/10	OD3 5/-
DD41 4/6	EL32 3/9	OZ4 5/-
DETS 15/-	EL35 9/-	OZ4A 5/-
DET18 30/-	EL41 8/3	P61 4/6
DET19 2/6	EL84 8/3	PCC84 8/-
DET20 2/6	EL91 7/6	PCC85 8/-

PEN25 4/6	U18 6/-	3E29 6/6	6L6GA 6/6	15E 8/-	956 2/-
PEN46 5/6	U19 7/-	(829B) 60/-	6L34 4/6	15R 7/6	1619 5/-
PEN65 6/6	U27 8/-	3Q5GT 9/-	6N7GT 7/-	30 5/-	954 2/-
PEN141 4/-	UL84 8/6	4A1 4/6	6Q7G 6/3	35T 30/-	1625 6/-
PEN220A 3/-	UU4 4/6	4D1 2/6	6R7G 1/6	35Z3GT 7/-	1626 3/6
PEN1340 6/-	UY85 7/-	5U4G 7/-	6S7G 5/6	39/44 6/-	1629 4/6
PENDD/	V2D33B 8/-	5V4 7/-	6S7GT 6/-	53A 3/-	4242A 6/-
1360 9/6	VP23 3/6	5Y3GT 8/6	6S7 5/-	58 6/-	7193 1/9
PL81 11/-	VR78 4/-	5Z3 9/6	6SH7 5/-	59 6/-	7475 5/-
PL82 8/-	VR99 8/-	5Z4G 8/-	6S7J 6/9	71A 4/6	8010AR 22/6
PL83 9/-	VR105/30 7/6	6A6 5/-	6S7G 6/6	77 6/6	8013A 10/-
PM4DX 3/-		6AB7 5/-	6S7K 5/6	80 6/3	8020 6/-
PT25H 7/6	VR150/30 4/3	6AC7 4/3	6S7LGT 6/6	82 8/-	9001 5/-
PY82 6/-		6AG5 4/6	6SN7GT 4/6	83 9/6	9C03 5/6
QP21 6/-	VR150/30 6/-	6AG7 8/6	6SQ7 6/6	88V 12/-	90C4 4/-
QP25 5/3	VS110 4/-	6AK6 7/6	6SR7 6/6	84 12/6	90C6 4/-
QS75/20 6/9	VT25 8/6	6AK7 8/-	6SS7 5/-	89 6/-	
QS95/10 6/9	VU111 3/-	6AM5 5/-	6V6G 5/6	210LF 3/-	
QS108/45 6/9	VUI20 3/3	6AM6 6/3	6V6GT 6/-	210VPT 3/-	
	VUI33A 3/-	6BG4 4/6	6X5G 5/6	2/6 pin 2/6	
QSI50/15 6/9	W31 7/-	6B8 5/6	6X5GT 6/6	217C 17/6	
	W42 7/-	6BB2 2/6	75AZ 6/9	220VSG 3/-	
R10 12/6	Y63 5/-	6C4 4/-	8D2 2/6	446A 14/-	
REL21 25/-	Y66 8/-	6C5 6/-	8V08 5/-	446B 14/-	
RG1-240A 17/6	Z31 6/-	6C6G 4/6	9D2 3/-	705A 17/6	
		6C8G 5/-	12A6 2/-	715B 97/6	
RG3-250 17/6	1A3 3/6	6F6 7/-	12AH7 7/-	717A 8/6	
	1ASGT 5/-	6F8 6/6	12AT7 6/6	801 6/-	
RG4-1250 17/6	1CSGT 7/6	6F12 4/6	12AU7 6/9	803 22/6	
	1D8GT 6/-	6F12 4/6	12AX7 7/-	805 30/-	
	1E7GT 7/6	6G6G 3/3	12CB 7/6	807 30/-	
RK34 2/6	1L4 3/9	6H6M 2/6	12E1 22/6	807BR 5/3	
RL37 3/6	1L5 3/6	6H6GT 1/9	12H6 2/6	813 70/-	
SP2 4/-	1R5 6/9	6HA7 4/3	12J5GT 3/6	815 80/-	
SP4B 7/6	1S5 6/-	6J5 3/6	12SC7 4/6	816 30/-	
SP13C 4/6	1T4 4/-	6J6 4/6	12SG7 6/6	829A 30/-	
SP21 4/-	2A3 8/-	6K6GT 2/3	12SH7 4/9	833A £14	
SP41 2/6	2A6 7/-	6K7G 2/6	12SJ7 6/-	843 7/6	
SP61 2/6	2C34 2/6	6K7GT 5/3	12SK7 5/-	866A 10/-	
SU2150A 4/9	2DA4 4/-	6K8G 6/6	12SL7 7/-	827A 35/-	
T41 19/-	2X2 4/-	6L5G 6/-	12S7 6/-	930 8/-	
TP25 15/-	3A4 6/-	6L6 9/-	15D2 6/-		
TT11 3/-	3B34 3/-	6L6G 6/6			


AND MANY OTHERS IN STOCK, INCLUDING CATHODE RAY TUBES AND SPECIAL VALVES. All U.K. Orders below 10/-. P. P. & 1/-; over 10/-, 1/6; Orders over £2 P. & P. free. C.O.D. 2/- extra. Overseas Postage extra at cost.

Brand new original spare parts for AR88 Receivers.
Tuning Mechanism (gear), £2/10/-, post free.
 Please write your other requirements.
Low Resistance Headphones, brand new, type CLR, 5/-. Balanced Armature, 7/6. P. & P. 1/-.
Microphone Transformers. Balanced input 30 or 250 ohms. U.S.A. manufacture 7/6. P. & P. 1/6.
813 Ceramic Valveholders, 3/- each. P. & P. 1/6.
Vacuum Condenser 32,000 V. 50 pF 15/-. Post free.
Modulation Transformers (U.S.A. Collins), primary imp. 6,000 Ω, C.T., secondary 6,000 Ω 20W. 9/6 ea. Post free.
Carbon Inset Microphone, G.P.O. Type 2/6. P. & P. 1/-.
Telescopic Aerial Masts. 7 sections, total 11 yards. Immediate erection. £4/10/- each or £8 per pair. Post free.
Light Headgear Assembly. Ideal for mobile use. Headphones 600 ohms carbon microphone, 18/- P. & P. 3/-.
Signal Generator Type TS. 14/AP. 3,200-3,370 mc/s. Fully guaranteed, £85.
Rotary Transformer. 171 W 12v input, 1,600 v 100 mA output, 30/- P. & P. 7/6.
R109 Receiver. Covering 2-8 mc/s 6 v. D.C. New and Tested, £45/- C. P. D.
R109A Receiver. Covering 2-12 mc/s 6 v. D.C. New and Tested, £55/-.
Variometers for W/S No. 19. Fully tested and working, 12/6. P. & P. 2/6.
Complete V.F.O. Unit from TX53. Freq. range in 4 switched bands from 1.2-17.5 Mc/s. Two V.T. 501s as oscillator and buffer, 807 as driver, two 5130s as voltage stabilizers. Output sufficient to drive two 813s in parallel. Slow motion drive directly calibrated in Mc/s. Provision for crystal control, metering of buffer and driver stage. Power requirements 400 v. and 6.3 v. D.C. Can also be used

as low power transmitter. In excellent condition with valves and circuit diagram, £5. P. & P. 15/-.
R.C.A. Master Oscillator (V.F.O.) with stability of 0.0007%. Frequency range 2-20 Mc/s with built-in constant frequency tone generator. Regulated A.C. power supply 115/230 v. and fitted with plate and volt meters. Valves line-up Electronic coupled oscillation 3Q5(2). Buffer amplifier—807, tone generator—6AB7(1), 6F6(1), regulated power supply—5U4(2), 6Y6(5), 1B52(1), VR150/30(2). Brand new, complete in grey crackle steel cabinet size 67in. x 22in. x 17 1/2in. Fitted with full-length door at rear with standard 19in. panels. Can be used as complete TX with existing 807 output. The bottom half of the cabinet with 3 blank panels being empty ready for installation of complete R.F. modulator and power unit, thus making a complete totally enclosed compact TX. Circuit diagrams and working instructions supplied. Price complete with valves, £27.10.0 ea. Supplies strictly limited.
Filament Transformers. Primary 0-190-210-230-250 v., 50 C. Sec. 1 2.5 v. C.T. at 10 amps.; 2.2.5 v. C.T. at 10 amps.; 3 10.5 v. C.T. at 11 amps., 4,000 v. insulation. Price £2.19.0. P. & P. 5/-.
 Primary 0-190-210-230-250 v., 50 C. Sec. 1 10 v. C.T. at 4.5 amps.; 2 10 v. C.T. at 4.5 amps., 4,000 v. insulation. £1.16.0. P. & P. 5/-.
 Primary 230 v. 50/60 c 67 v. amps. Sec. 1 6.3 v. 1-6 amps.; 2 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 4 6.3 v. C.T. 3 amps. £1.12.0. P. & P. 5/-.

Driver Transformers. Primary 500 ohms imp. Sec. to match two 805 in push pull, £1.7.6. P. & P. 5/-.
Transformers. Relay supply. Primary 230 v. Sec. 0-27-28-31 v. at 0.5 amps. 15/- P. & P. 5/-.
I.F. TRANSFORMERS 4.5 mc/s, American made in black crackle finish housing, 6/- P. & P. 1/-.
SCR.522. Receivers (BC624). 100-156 mc/s, including all valves, 25/- P. & P. 5/-.
SCR.522. Transmitter (BC624) including all valves 22.6. P. & P. 5/-.
Vibrator Unit. 12 v./160 v. 35 mA. Exceedingly well filtered and smoothed, excellent for car radios. New, including 6X5G valve and vibrator. 17/6. P. & P. 5/-.
Famous U.S.A. Field Telephones in canvas or leather case, type EEB, £9 per pair. Post free.
Marconi Signal Generator. TF144G; 85 kc/s, 25 Mc/s. Made up to new standard, £70, delivered free.
Complete Set of Strong Aerial Rods (American). Screw-in type MP49, 50, 41, 52, 53, total length 15ft. 10in., top diameter 0.615in., bottom diameter 0.185in., together with matched aerial base. MP37 with ceramic insulator, ideal base for car or roof insulation, £2/10/-, post free.
AR88D and L.F. Receivers, completely overhauled and tuned, £60 and £57/10/- respectively. Completely rebuilt with P.V.C. wiring, £85.
HRO Mains power pack, input 115/250 v. A.C.; output 250 v., 75 mA, and 6.3 v., 3.5 amps. £3, inc. carb.
Non Inductive Carbon Resistance. 800Ω about 30 watt 1 in. dia. 10in. long, 7/6. P. & P. 1/6.
Avomomers. Leather case. With leads, fully tested and guaranteed. With batteries. A.C./D.C. volt range to 500 v. As above but to 2,000 volt, D.C. Either model only £3.19.6. P. & P. 2/6.
Personal Callers Welcome

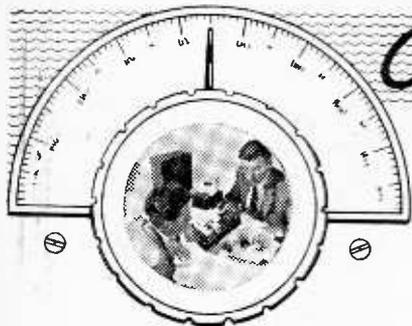P. C. RADIO LTD.
 170 GOLDHAWK RD., W.12
 SHEPHERDS BUSH 4946



On Your Wavelength

BY THERMION

MANY of my friends who are radio amateurs construct items of radio gear in their spare time. The majority, to ensure domestic harmony, perform their operations in a shed outside the house, in a cellar or in a spare room. Most of the sheds and cellars used are damp and cold and although much of the apparatus built is for use on the domestic mains supply, few constructors appreciate the dangers encountered when working in such surroundings. Now the pundits among my readers will say that the remedy for this state of affairs is simple; all exposed metalwork including the chassis under construction should be earthed and 3-pin plugs should be used with all gear. This procedure is not easy to carry out, however, and if the earth wiring is not perfect, dangers may be created, as well as removed.

Some amateurs do not appreciate that there is a danger of shock when working in damp surroundings with apparatus connected to the domestic mains. One side of the mains (the neutral) is earthed at the source of supply and the other side is therefore at a potential of some 200-250V above earth. Thus, if it is possible during the constructional work to touch the live side of the mains and at the same time to make contact with the earth, either directly or indirectly, an electric shock will be experienced. The severity of the shock and its effects upon the recipient naturally depend upon the degree of electrical contact. Metal chassis can easily be connected by accident to the live side of the mains and would constitute a grave danger in workplaces such as sheds and cellars. However, if the chassis were earthed and inadvertently the live side of the mains made contact with it there would be, in effect, a short across the supply which would blow the fuses (always provided that the fuses had not been replaced with 18 gauge copper wire!).

If the constructor works in a room at, for instance, the top of the house where there are no earthed objects, it may not be necessary to earth the apparatus being used. In fact it may be an advantage to leave all chassis "floating"; when chassis are earthed the mains potential appears between the live mains lead and the chassis and it is all too easy to hold the chassis with one hand to steady it and touch live leads—H.T., mains, etc.—and receive a shock. My own practice as I do most of my constructional work

in the topmost room of the house nowadays, is to leave all metalwork "floating." I have removed all earthed objects from the room; the floor is wooden and is covered in duck boards and I make a point of wearing rubber-soled shoes. There is no risk of shorting the H.T. when making wiring adjustments with a soldering iron while the apparatus is switched on; if the iron body and the chassis were earthed, contact between the iron and any part of the H.T. line would cause a partial or total short. No doubt this procedure of mine will be frowned upon by those who set themselves up as technical authorities, but as far as I can see there is less danger of shock with this system, if one can be quite sure that there are no earthed objects within reach of the test bench. Of course, the finished apparatus is fitted with a 3-wire mains lead and a 3-pin plug for safety.

The hazard of electric shock has come to be looked upon as something to ridicule. It is not. All electric shocks can be prevented if due attention is paid to the installation and the procedure employed. The commonest cause of workshop shocks is holding the chassis with one hand and touching a live point with the other, thus receiving a shock across the chest—one of the most dangerous paths for the current. The remedy is obvious.

A press notice from the Institution of Electrical Engineers was printed in the previous issue and I think it is worthwhile to reprint the most important parts of it which concern imported electrical apparatus and the dangers of mis-connection.

"The attention of vendors and users of imported domestic electrical apparatus, photographic and projection equipment, tape recorders, etc., is urgently directed to the risks which may ensue if the colour coding of the cores of the flexible cord with which such apparatus is furnished differs from the established British coding set out in The Institute's Regulations for the Electrical Equipment of Buildings, that is to say:

- Green—earth connection.
- Red—phase (live) connection.
- Black—neutral connection.

"The risk is most acute if the flexible cord provided with the apparatus has a core coloured red which serves as its earth connection; because if the user, following established British practice, connects this core to the terminal of a British connecting plug which may itself be marked red, and then inserts the plug into a normal British socket, the result will be that any exposed metal parts of the imported apparatus connected to the red core will be charged at mains voltage, and represent a serious hazard."

Measurements with Multirange meters

ACCURACIES TO BE EXPECTED

By B. Sexton

THE most common voltmeter used for normal circuit measurements is undoubtedly the moving coil type. There are many manufactured and home-made instruments in daily use. Unfortunately the operation of this type of movement draws current from the circuit under test. This may alter the true circuit conditions and give misleading results. A study of the effects which are caused is both interesting and instructive and may save time normally wasted in trying to interpret a seemingly impossible result.

The errors caused by connecting the voltmeter to the circuit depend mainly upon two facts.

(a) the resistance of the meter or the "ohms per volt" figure.

(b) the source impedance of the voltage at the circuit test points.

"Ohms per Volt" (Ω/V)

This term is used for calculating the resistance that the connection of the meter effectively places in parallel across the test points. Normally, the lower this value of resistance, the more severe the effect of connecting the meter becomes. Basically the moving coil voltmeter is a milliammeter, or microammeter, with an externally added, high value series resistor. The Ω/V figure is proportional to the value of the added resistor which in turn depends upon the sensitivity or current required for f.s.d. (full scale deflection) of the meter. The more sensitive the meter, the less the current required for f.s.d. and the higher the value of the added series resistor. The higher the value of the series resistor the higher the Ω/V figure. Thus the Ω/V figure is indirectly related to the sensitivity of the meter.

Practical examples will make this clear. supposing the basic meter movement has an f.s.d. of 1mA and it is required to use the meter in conjunction with a series resistor to measure voltage up to 100, i.e., f.s.d. is to represent 100V. The value of series resistor is found to be $100V/1mA=100k$. Or, in other words, when a 100k resistor is connected across 100V it will pass a current of 1mA and with the meter connected in series with the resistor it will indicate 1mA or if the scale is calibrated in volts, 100V. Now if the series resistor of value 100k is divided by the f.s.d. voltage of 100V we get $100k/100V=1,000$. This is the ohms per volt figure for the particular meter in the example. As stated above, this figure is governed by the basic current required for f.s.d. and is not altered by the value of D.C. voltage chosen for f.s.d. For example, supposing a value of 250V was chosen for f.s.d. Then the added value of series resistor required to limit the current to 1mA is $250V/1mA=250k$. Dividing this value by the f.s.d.

voltage of 250 gives $250k/250V=1,000$. Thus the Ω/V figure is the same as that for an f.s.d. of 100V.

Meter Movement

It should be noted that when obtaining the value of series resistor in previous examples the inherent resistance of the basic meter movement has not been taken into consideration. The resistance is usually so small in comparison with the large value of series resistor that it may safely be disregarded unless the meter is to be used with an f.s.d. of a very low voltage.

Now consider a more sensitive meter movement, one which requires, say, only $50\mu A$ for f.s.d. or is 20 times more sensitive than one requiring 1mA for f.s.d. To use this meter as a voltmeter with f.s.d. of 100V will require a series resistor of $100V/50\mu A=2M$. The Ω/V figure would then be $2M/100V=20,000$. If the meter is used with an f.s.d. of 250V then calculations will give the

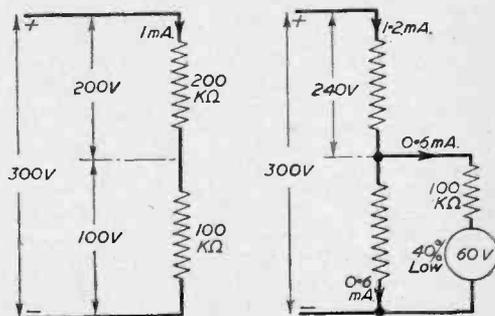


Fig. 1 (Left).—Simple circuit and calculated current and voltages. Fig. 2.—(Right).—The result of connecting a 1,000 Ω/V meter on the 100V range.

value of series resistor as 5M and the O.P.V. figure as 20,000. Thus, using a meter which is 20 times more sensitive has increased the Ω/V figure by 20.

Thus the higher the sensitivity of the meter the higher the Ω/V figure. The Ω/V figure of any movement can quickly be found by dividing 1V by the f.s.d. current of the basic meter movement. A meter of f.s.d. 1mA has an Ω/V figure of $1V/1mA=1,000$ and a meter of f.s.d. $50\mu A$ has a Ω/V figure of $1V/50\mu A=20,000$. These figures agree with those found by the longer method in the previous examples.

Normally the Ω/V figure is stated on the instrument, but if not then simply divide by the lowest direct current range. This assumes, of course, that the lowest direct current range is the basic, unshunted, meter movement.

Readings

Fig. 1 illustrates a simple circuit consisting of two resistors in series across a 300V supply. The true, calculated circuit conditions of current and voltage are shown. It is desired to measure the voltage of 100V across the junction of the two resistors and H.T. negative. The separate use of two meters with different Ω/V figures will be considered and illustrates the errors introduced by meter connection to the circuit. It should be noted that two resistors are shown for simplicity. The bottom resistor could represent the static D.C. resistance of a valve and the top resistor the anode load. The 100V would then represent the anode voltage.

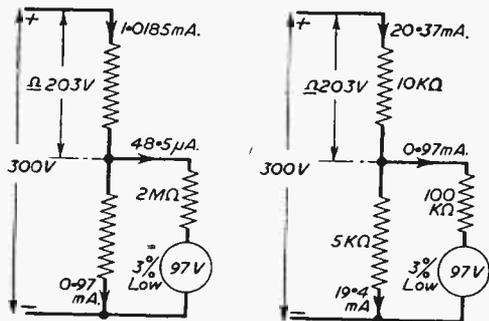


Fig. 3 (Left).—Result of using a meter of 20,000 Ω/V .
Fig. 4 (Right).—Effect of 1,000 Ω/V meter on accuracy when the source impedance is low.

be measured, i.e., the reading is now only 3 per cent. low. The meter draws only 48.5 μA , the 100k resistor passes 0.97mA and the total current is 1.0185mA or an increase of 18.5 μA . This increase in current is much less than the increase caused by the 1,000 Ω/V meter and consequently the voltage drop across the 200k resistor is increased by approximately 3. The calculated percentage errors show the superior accuracy obtainable with the higher Ω/V meter.

It must be emphasised that the errors obtained apply only to the circuit considered in Fig. 1. The impedance of the circuit at the test point also has an effect, as mentioned earlier; this effect will vary with different circuits.

Source Impedance

Consider the circuit shown in Fig. 4. Note that the resistors are now 10k and 5k. Before connecting the meter a calculation will show that the true voltage across the 5k resistor was 100V and the current 20mA. The meter connected is 1,000 Ω/V and switched to the 100V range. As in Fig. 2 the meter appears as a 100k resistor, but is now in parallel with a 5k resistor giving a resultant value of 4.76k. The circuit conditions adjust as shown, the voltage is now measured as 97, i.e., the error is 3 per cent. The current drawn by the meter is 0.97mA and that passed by the 5k resistor is 19.4mA. The total current of 20.37mA flows through the 10k resistor. The extra 0.37mA causes the increased voltage to drop across the 10k resistor.

Thus comparing the circuits of Fig. 2 and Fig. 4 it will be seen that in both cases a 1,000 Ω/V meter, switched to the 100V range, was used to measure a potential of 100V, but with widely differing results. This illustrates the importance of source impedance. When a voltage is being measured via a high resistance the current drawn by the meter can cause large errors owing to the voltage drop that this current produces. As the source impedance decreases, so does the voltage drop, and consequently the measurement becomes more accurate.

H.T. Battery

A practical example of this is the H.T. battery. A new battery, in perfect condition, has a low internal resistance and when measured with a low Ω/V meter will indicate correct voltage, but after use towards the end of its working life, the internal resistance will have increased and then there may be a marked difference between the measured voltage and the actual, no-load, voltage.

The higher the Ω/V figure of the meter the less important the effect of source impedance becomes. This point is illustrated by comparing Fig. 3 and Fig. 4. The voltage of Fig. 3 may be considered to have a high source impedance, but by using a meter of 20,000 Ω/V , the accuracy is the same as that obtained in Fig. 4 where the voltage has a low source impedance, but is measured with a meter of only 1,000 Ω/V . The accuracy could further be increased by using the 20,000 Ω/V meter to measure the low source impedance voltage of Fig. 4.

The result of connecting a multi-range 1,000 Ω/V meter, switched to the 100V range, is shown in Fig. 2. The resistance of the voltmeter is represented by the series resistor and will be $100 \times 1,000 = 100k$. Note that the meter movement resistance is considered so comparatively small that it is neglected. The meter will appear as a 100k resistor in parallel with the 100k circuit resistor giving a resultant value of 50k. The 300V supply now "sees" a 200k resistor in series with an effective value of 50k. The circuit conditions, calculated from Ohm's Law, will adjust accordingly and are as shown. The original voltage of 100V will now be measured as 60V; the reading error is 40 per cent. low. The meter is drawing 0.6mA and the fixed 100k resistor is passing 0.6mA. This total current of 1.2mA is flowing through the 200k resistor causing a drop of 240V across it. It is interesting to note that although the meter is drawing 0.6mA, the original current has increased by only 0.2mA. It is this "extra 0.2mA flowing through the 200k resistor which increased the volts drop by 40 thus subsequently decreasing the voltage across the bottom resistor.

Increased (Ω/V)

Fig. 3 shows the result of using a meter with a higher Ω/V figure of 20,000. On the 100V range the meter appears as a 2M resistor in parallel with the 100k circuit resistor giving a resultant value of 95.5k. Circuit conditions are as shown. The voltage can be calculated and now 97V will

Advantage

Thus the high Ω/V meter is far superior to the low Ω/V meter, but owing to the use of a more sensitive meter movement it is usually more expensive. By switching to a higher range, greater accuracy can be obtained with the low Ω/V meter although the reading of the scale becomes more difficult. Fig. 5 shows how the original circuit conditions of Fig. 2 would change if the meter is merely switched to a higher range. Assuming the meter has a 1,000V range it will then appear as a 1M resistor which, in parallel with the fixed 100k, gives a resultant of 91k. Note that the original current has increased by only 0.034mA. This increases the voltage drop across the 200k resistor to approximately 206. Thus the meter will indicate 94V. The reading error is then only 6 per cent. Compared to the original error of 40 per cent., this is a large increase in accuracy and illustrates the fact that it is always best to make a voltage reading on the highest convenient range. It must be realised, of course, that to read 94V accurately on a 1,000V scale may present difficulty. The number of divisions on the scale will be governed by the width of the scale and probably each division will represent 10V on the 1,000V range. Thus accurate interpolation is required. Whilst this becomes easier with experience it is obviously not so accurate as reading on the 100V scale where each division would then represent 1V.

This change in voltage reading when changing meter ranges of a low Ω/V meter can be used as an indication of the source impedance at the test point. If the reading changes drastically when the meter range is switched then a high source impedance is evident and obviously affecting the accuracy of the readings. If the meter reading changes only slightly with range switching, then the source impedance is low and readings are then much more reliable.

Measurement Methods

It is possible to read the voltage of Fig. 1 without causing any effect on the circuit conditions as no current is drawn from the circuit under test. Fig. 6 illustrates the method. Two meters and a potentiometer are required. The potentiometer is connected in parallel with the two original resistors. Note that connecting the potentiometer across the original 300V supply may cause the 300V supply to decrease slightly due to the extra load. This effect has, for simplicity, been ignored. If in practice it could not be ignored, then a separate power supply for the potentiometer would be required. The negative side of each supply would be joined. The voltage between the slider and H.T. negative is measured by the voltmeter VM2. Voltmeter VM1 is connected between the slider of the potentiometer and the junction of the two resistors. The position of the slider is varied until VM1 reads 0V. The voltage at the junction of the two resistors is then given by the reading of VM2, this will be the true voltage of 100. Although VM2 will be drawing current it will all pass through the added potentiometer circuit and not through the

original circuit. It should be noted that VM2 is not reading the true voltage at the slider of the potentiometer, i.e., if VM2 was removed the true voltage at the slider would be higher than 100V. This is of no consequence as all we are interested in is obtaining a voltage which we can read easily that will be the same voltage as that at the junction of the two resistors. That it is the same is shown by the fact that the voltmeter VM1 indicates 0V thus proving that the two points are at the same potential.

The accuracy of reading then depends only on the calibration accuracy of VM2. This method, of course, can be applied to the measurement of almost any high impedance point where meter current would give a false impression of the true reading.

Changes

Another difficulty sometimes encountered is the measurement of the change in a high potential. An example of this would be the change in output voltage of a power pack between no load and load conditions. With good regulation the change may be very small and consequently difficult to read on the high voltage range of the meter. Assume a practical example of a power pack which has a no load output voltage of 300. When a certain load is connected the output voltage may drop to say 299. If the output voltage was measured on the 1,000V meter range this change of 1V would be difficult to discern

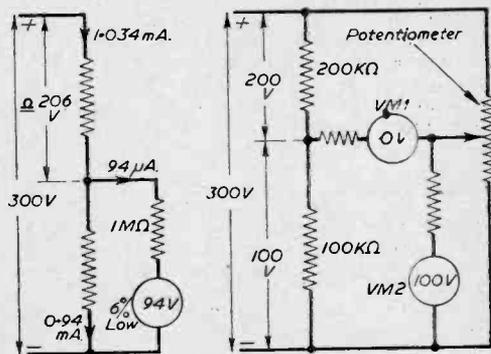


Fig. 5 (Left).—Effect on the circuit conditions of Fig. 2 when the meter is switched to a higher range.
Fig. 6 (Right).—Making the measurement without drawing any current.

and practically impossible to read to any real degree of accuracy.

Fig. 7 (page 984) shows a simple but accurate method. The 300V no load output can be switched on load as shown. A second H.T. supply and resistor network are required. The voltage of this second H.T. supply must be within a volt or two of 300. The resistance of the potentiometer should be low, so that only a few volts are developed across it. Between the slider of this potentiometer and the original 300V supply is connected a voltmeter, the full scale reading of which is only a few volts. In the diagram 0-2.5V is shown. Note that the negative sides of the voltage supplies are common. Now by

(Continued on page 984)


An Experimental S.W.

Three

OPERATING THE RECEIVER

By F. G. Rayer

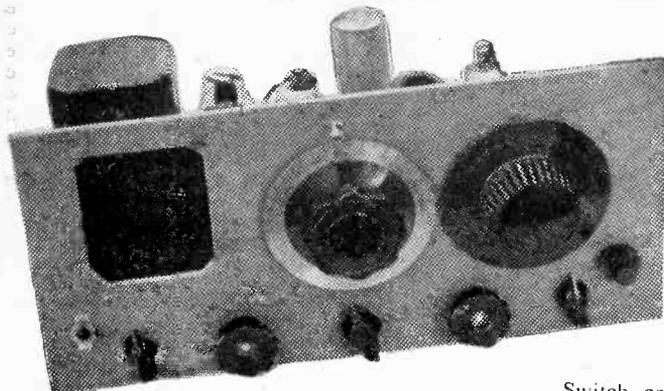(Continued from page 858 of the February issue)



For single band tuning, the aerial coil can be wound to match the detector coil. Leads should be short and direct in both tuned circuits.

Switch connections are shown in Fig. 5. In one position, the 470k resistor is in circuit from valve grid to chassis, and the 150pF tuning condenser is disconnected. The other four switch positions bring in the tuning condenser and one coil.

THE number of turns in the coils used in this receiver were given in the previous article. The detector coils are shown in Fig. 4. In each case the primaries can be wound with 26 to 30s.w.g. wire, with turns side by side, about 1/4 in. space being left between this winding and the earthed end of the tuned section, as in Fig. 4.


In the diagrams "G" indicates the grid end of the tuning coil, "C" the cathode tap, and "E" the chassis or earth connection. "A" is the R.F. anode connection, and "H.T." the high tension line lead. The circuit will work well with no R.F. stage. "A" then being taken to the 50pF aerial condenser, and "H.T." to chassis.

Operating the Set

Though distant reception is easily possible with a poor indoor aerial, an outdoor aerial will improve results. The aerial circuit switch is normally left at the untuned position. The detector regeneration control should be so operated that the valve is just on the point of oscillation. This position is easily found as increasing

Aerial Coils

These can be wound, or be ready-made S.W. coils. Using 1/4 in. diameter formers, seven and a-half turns of 20s.w.g. wire, spaced to occupy 1 in. winding length on the former, will do for 10 to 20m. For 18 to 30m 20 turns of 24s.w.g. will be satisfactory, with 30 turns of 26s.w.g. for 30 to 60m, and 50 turns of 30s.w.g. for 60 to 100m. The three larger coils are fitted with dust cores, and the tuning range can be adjusted with these to match the appropriate plug-in coils in the detector stage.

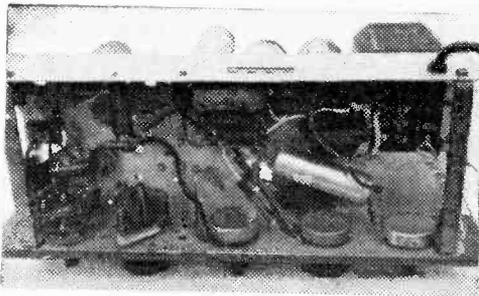

Underchassis view of the receiver.

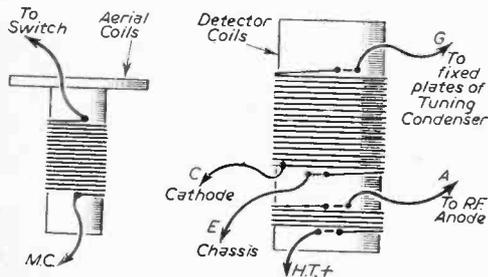



Fig. 4.—Construction of the aerial and detector coils.

the screen grid voltage with this control will build up volume until the set oscillates when tuned through a station. The control knob should then be turned slightly back. With weak signals the correct setting of this control becomes very important.


Tuning is normally carried out with the 15pF condenser. The 100pF condenser can be moved 10degrees at a time, this breaking up each wave-band into many smaller bands, each of which is covered with the 15pF condenser, with some overlap. Provided the 100pF condenser is set accurately, as described, it will be quite easy to find any particular station logged against the 15pF condenser dial.

When necessary, an aerial coil can be switched in, and it is then quite easy to find the correct tuning position for the 150pF condenser. Selectivity in this circuit can be increased, when needed, by turning the 50pF aerial condenser to a low capacity. The R.F. gain control can best be set at about three-quarters full gain, but this can be adjusted as circumstances require.

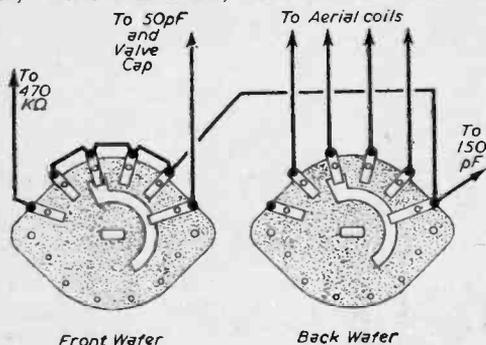Amateur stations will be heard on the 10, 15, 20, 40 and 80m bands, USA and other non-local



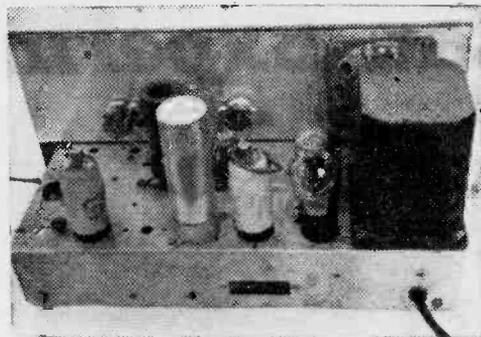Front Wafer Back Wafer
Fig. 5.—Switched wafer wiring.



Rear view of the receiver.

stations coming in best on 10, 15 and 20m bands. Long distance reception of commercial broadcast stations will often be best on 19 and 25m bands, until evening, when 31 and 41m bands will often give very good reception of African, American, and Far East stations. Conditions vary according to the season and time of day, but very many transmissions are made in English, from localities all over the world, and it will generally be reasonably easy to log a number of these.

D.C.2. STEREO AMPLIFIER

(Continued from page 930)

the free tag of the next tag strip. Run two wires from this tag—securing the 10W resistor to it at the same time—one to the tag of the 32 + 32μF 450V with the 3.3k wire wound on it, and the other to the two tags on the output transformers that are situated second in from the rear of the chassis, then solder. We now have three of the four tags of the output transformers soldered. Between the remaining one and the last ones soldered, solder a 0.01μF 400VW paper capacitor, and join the same tag—free before the fixing of the 0.01μF—to pin 6 of the nearest ECL82. This should now leave both ECL82 valves with pin 1 free and a tag on each of the two left-hand (power unit end) jacks free.

We can now fix the volume control, tone control and the stereo/mono switch in position. With the chassis still inverted, the left-hand socket is for the volume control—a twin bank 250 + 250k log. The centre hole is for a similar type, but is 1M + 1M. The other control is the stereo/mono control, and is made by Kendall and Mousley Ltd. It is a single-pole two-position switch. The actual wiring of the tone and volume control circuit is shown in Fig. 4. Note that the wires from the input jacks are in screened twin cable and that the braiding is joined at one end to the common earth at the rear of the chassis, and at the other end to the various cases of the pots (four points) to two tags on the volume control, and also the two tone control capacitors are joined to the cases of the tone control pot. The colour of the wires in the screened twin is important, as if they are reversed the channels will be reversed in the amplifier.

Servicing Printed Circuits

By "SERVICEMAN"

IT is essential that when soldering or making good any dry or loose connections, that the heat applied is carefully controlled, the reason being that excessive heat will result in the base material blistering, thus causing the metallic conductors to lift from it. Such base materials comprise phenolic impregnated papers, epoxy impregnated fabrics, or woven glass cloth treated with silicones or epoxy resins. The use of any particular base material depends mainly upon its final use, an important factor being the maximum working temperature.

As in the conventional type of radio circuit dry joints will result in poor electrical connections, not forgetting any break in the metallic conductor. Such breaks, however, in the printed circuit, may be only a very small crack, resulting in intermittent operation. Such faults can best be traced by continuity checks, but in doing so it is advisable to bend the printed circuit to assist in tracing the break or dry joint in the conductor.

It is as well to mention, however, that when soldering new connections, or making good any dry joints, it is necessary to ensure that no splashes of surplus solder short-circuit the metallic conductors or components, bearing in mind that with this type of circuit miniature components are used.

The insulation resistance between the conductors is usually fairly high, something in the order of 50,000M, but this value will be greatly reduced if the printed circuit is allowed to become damp, oily or dirty. Any dust collecting between the conductors will eventually result in tracking or electrical leakage.

...and NOW


THE TOURIST PORTABLE

4 valve, 2 waveband Lightweight Battery Radio. Size only 8in. x 5 1/2 in. x 4in. Wt. 3 1/2 lbs., incl. Battery.

Complete Receiver Component Kit ... 56/6 P. & P. 1/6
 Set 4 miniature valves (96 series) ... 35/- P. & P. 9d
 5in. Speaker & O/p. Trans. ... 21/- P. & P. 1/6
 Cabinet, Dial & Knobs, etc. ... 19/6 P. & P. 2/-
 Complete Kit. **BARGAIN** Only **£6. 8. 6** post free

Latest circuitry, delayed AVC & A.F. Neg. feedback.
 Instruction Booklet, 1/6. (Free with Kit.)

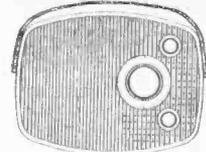Terrific performance—Remarkable size—Staggering value



Record Player Bargains

Latest 4-speed Models

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and mono-arm Xtal cartridge and dual sapphire stylus. Auto stop and start. A fidelity unit and bargain buy at only **£6.19.6**.

SINGLE PLAYERS BSR (TU9), 90/-; COLLABRO (1/564) 6 gns.; GARRARD (18P), **£7.10.0**; GARRARD (PA Mk. II) de Luxe Model. **£8.19.6**. Carr. and Ins. 3/6.

AUTOCHANGERS. BSR (U4B), **£6.19.6**. COLLABRO, **£7.19.6**; GARRARD (RC121 4P Mk. II) 14-gun hand, stereo adapted, 10 kns. Stereo head **£2** extra.

RECORD PLAYER CABINETS. Contemporary styled 16in. x 13in. x 5in., 3 gns. Carr. and Ins. 3/6.

RECORD PLAYER CABINETS

Contemporary style, rexine Cabinet covered cabinet. Price in lawn and brown with cream **£3.3.0**.

interior. Size 18 1/2 x 13 1/2 x 5 in. Carr. and Ins. 3/6. 9H. accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, etc. Unique record player mounting board 14 x 13in. supplied.



NEW BOXED VALVES GUARANTEED ALL
 1R5, 1T4 7/6 DP96 9/- EP286 13/6 PCF80 10/6
 1R5 7/6 DK96 9/- EP91 8/6 PCF83 12/6
 6X3, 3V4 8/- DL96 9/- EL141 10/6 PLS1 12/6
 5Z4 9/6 EA8C80 9/6 EL84 9/6 PL82 9/6
 6X7 5/6 HC34 10/6 LX51 10/- PL83 11/6
 6K8 8/6 ECF80 11/6 EY86 10/- PY80 7/6
 6Q7 8/6 ECH42 10/6 EZ81 7/6 PV81 9/6
 6V6 7/6 ECH80 10/6 MU14 9/6 PY82 7/6
 1A96 9/- EP80 9/6 PCC84 10/6 U25 12/6

SPECIAL PRICE PER SET
 1R5, 1T4, 1R5, or 3R4 or 3V4, 27/8. 1DK96, DP96, DAF96, DL96, 35/- 6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5, 35/-.

COAX 80 OHM CABLE


Stand 3in. dia. Low Loss Semi-Air Spaced Aeraxial. Special Reduced Prices.
 20 yds. 12/6, p. & p. 1/6; 60 yds. 32/6, p. & p. 3/-; 40 yds. 22/6, p. & p. 2/6; All other lengths 8d. per yard.
 Coax Plugs 1/-. Sockets 1/-. Couplers 1/3.
 Cable End Sockets 1/8. Outlet Boxes 4/6.

Manufacturer's Surplus Bargain

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve Line-up: ECC85, ECH81, EF89, EA8C80, EL84, EM81, EX80.

Three Waveband and Switched Gram positions. Med. 200-500 m. Long 1,000-2,000 m. VHF/PM 88-95 Mc/s. Philips Continental Tuning insert with permeability tuning on FM and combined AM/PM IF transformers, 460 Kcs and 16.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 12 1/2 x 6 1/2 in. Height 7 1/2 in. Edge Illuminated glass dial 1 1/2 x 3 1/2 in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250 v. operation.

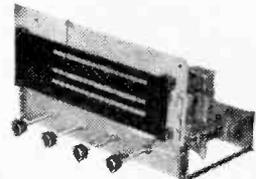

Aligned and tested ready for use £13. 10. 0 Carr. & Ins. 5/-
 Complete with 4 Knobs—walnut or ivory to choice.

Three ohm P.M. speaker only required. Recommended quality speakers.
 8in. Goodman's special cone.....21/6 10in. Roia (Heavy Duty).....30/- Post & Pkg. 1/6.
ONLY A FEW ITEMS ARE LISTED FROM OUR COMPREHENSIVE STOCK.
WRITE NOW FOR FULL BARGAIN LISTS, 3d.

RADIO COMPONENT SPECIALISTS

70 Brigstock Road, Thornton Heath, Surrey

Phone: THO 2188. Hours 9 a.m.—5 p.m. 1 p.m. Wed.
 Open all day Saturday. By Thornton Heath Station.

Terms: C.W.O. or C.O.D. post and packing up to 1/6. 7d.: 11b. 11/: 31b. 11/6: 51b. 2/-: 101b. 2/9.

2-VALVE 12-WATT AMPLIFIER

Twin stage 12CL22 with vol. and neg. feedback. Tone controls AC. 200/250 volt with double-wound Mains trans. Complete with knobs, etc., ready wired to fit above cabinet.

£2.17.6 P. & P. 1/-

6-in. Speaker and matching trans. 22/- P. & P. 1/6.

COSSOR VHF/FM CONSTRUCTORS KIT (Model 701K).

This is a 6-valve (UCC85, 2UF89, UAH809, U184, UY85) FM Radio Kit of high quality, design and superb reproduction, with pre-aligned coils and printed circuit complete with Power Pack for AC/DC 200/250 v. operation. Kit includes High Performance 10in. x 5in. Goodman's Speaker for quality response. Complete in every detail, including calibrated Tuning Dial, Slow Motion Drive and Pilot Lamp and comprehensive instruction details and circuit diagram this Kit is a genuine recommended buy.

BARGAIN OFFER

Listed at 15 gns. **Only £8.19.6** Carr. and Ins. 4/6.

JASON FM TUNER UNITS (87-105 Mc/s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows.

STANDARD MODEL (FM1)—as previously extensively advertised. **COMPLETE KIT, 5 gns.**, post free. Set of 4 spec. valves, 30/-, post free.

LATEST MODEL (FM2)—attractively presented shelf mounting unit to enclosed Metal Cabinet with Built-in Power Supply. **COMPLETE KIT, £7, p. & p. 3/6.** Set of 5 spec. valves, 39/6.

NEW JASON COMPREHENSIVE P.M. HANDBOOK, 2/8 post free. 48 hr. Alignment Service, 7/6, p. & p. 2/6.

CONDENSERS.—Silver Mica. All pref. values. 2 pf. to 1,000 pf., 6d. each. Ditto, ceramics 9d. each. Tubulars 450 v. T.C.C., etc., .001 mid-.01 and 1/350 v., 9d. each. .02-1/500 v., 1/- each. 25 Hunits, 1/8. 5 T.C.C., 1/9, .001 6 kv., 5/6, .001 20 kv., 9/8.

RESISTORS.—FULL RANGE 10 ohms—10 megohms 20% 1/2 w. and 1/2 w. 3d., 1/2 w. 5d., (Midjet type modern rating), 1/2 w., 6d., 1/2 w., 9d., 10%, Hi-Stab, 1/2 w., 5d., 1/2 w., 7d., 5%, 1/2 w., 9d., 1% HI-STAB, 1/2 w., 1/8 (10-100 ohms 2/-).



UNIVERSAL AVOMETER MODEL D

Just released by the Air Ministry, these famous AC/DC Test Meters are a "snip" for anyone requiring a First Grade General Purpose Instrument. Normal Avometer size. 7 1/2 in. x 6 1/2 in. x 3 1/2 in. with carrying strap. Indication being given on a 5 in. Mirror Scale. Thoroughly overhauled and complete with batteries and instructions. Provides 34 ranges of current, voltage and resistance, as follows:

D.C. Voltage	A.C. Voltage	D.C. Current	A.C. Current
150 mv.	7.5 v.	15 ma.	75 ma.
300 mv.	15 v.	30 ma.	150 ma.
1.5 v.	75 v.	150 ma.	750 ma.
3 v.	150 v.	300 ma.	1.5 amp.
15 v.	300 v.	1.5 amp.	7.5 amps.
30 v.	600 v.	3 amps.	15 amps.
150 v.	750 v.	15 amps.	
300 v.	1,500 v.	30 amps.	Resistance
750 v.			1,000 ohms
1,500 v.			10,000 ohms.

ONLY £8.19.6 (carriage 3 6d).

25,000 OHMS PER VOLT TEST METER. Made by TRIP-LETT, the famous American meter manufacturers. Full bench size 7 1/2 in. x 6 1/2 in. x 6 1/2 in., and incorporates a unique tilting bakelite container size 5 1/2 in. x 3 1/2 in., which has 2 meters, a 25,000 ohms per volt moving coil for D.C. Measurements, and a First Grade moving iron for A.C. Reads Resistances up to 40 Meg. ohms. A.C. and D.C. volts to 1,000 D.C. Current to 250 mA., and also has 0-50 Microamps range. Facilities for measuring Condenser Capacity and Audio Output. Completely portable, with protective face cover. Complete with Test Leads, Instruction Book, and Batteries. Ex-Ministry of Supply. New Condition and thoroughly checked and overhauled. ONLY £10.10.0 (post. etc. 3/6).

CARRYING CASES. Solid leather. Brand New. Internal measurements 8 1/2 in. x 8 1/2 in. x 4 1/2 in. Fitted lock and key, and shoulder strap. Ideal for Test Instruments, Camera and Accessories, etc. ONLY 35/- (postage 2/-).

POWER UNITS TYPE 234. Designed for R.A.F. R1132 Receiver. Primary 200 250 v. 50 cycles. Outputs of 250 v. 100 mA., and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 19 1/2 in. x 7 1/2 in. BRAND NEW. ONLY 59 6 (carriage 7 6).

POWER PACK FOR R1155 RECEIVERS. Fitted with Output Stage and 8 in. P.M. Speaker. Operates receiver immediately without any alteration. In black crackle case size 11 in. x 10 in. x 6 in. ONLY £6.10.0 (carriage 5/-).

CANADIAN MOVING COIL PHONES. Low resistance, fitted noise excluding chamois ear muffs, and leather covered head band. Lead terminates to jack plug. Supremely comfortable. BRAND NEW. ONLY 19 6 (post 1 6).

TCS RECEIVERS. The renowned American set designed for static or mobile use. Coverage 1.5-12.0 Mc/s (25-300 metres) in 3 switched bands. Complete with valves. Size 11 in. x 13 in. x 1 1/2 in. Power required 12 v. LT and 225 v. HT. IN BRAND NEW CONDITION. ONLY £10.10.0 (carriage 15/-).

RCA 8 in. P.M. SPEAKER. In heavy black crackle metal case. Can be used as normal 3 ohms extension. Size 11 1/2 in. x 10 1/2 in. x 6 in. NEW IN MAKER'S CARTONS. ONLY 45/- (post 3/6).

"Q FIVER" COMMAND RECEIVER. The famous American BC453, covering 190-550 kc/s. I.F.s being 85 kc/s. Complete with all 6 valves and circuit. NEW IN MAKER'S CARTONS. ONLY 89 6 (post 3 6).

R1155 SUPER SLOW-MOTION TUNING ASSEMBLY. As used on all late model 1155s. Easily fitted to "A" sets, etc. BRAND NEW. ONLY 12 6.

EHF TRANSFORMERS. 5.5 kV (Rect.) with 2 v. 1 a., 79 6. 7 kV (Rect.) with 2 v. 1 a., 89 6. 2.5 kV (Rect.) with 2-0-2 v. 1 1 a., 2-0-2 v. 2 a. (for VCR97 tube, etc.). 47 6 (postage 2/- per trans.).

POCKET VOLTMETERS. Read 0-15 volts and 0-300 volts A.C. or D.C. BRAND NEW and UNUSED. ONLY 18 6.

CRYSTALS. British Standards 2-pin 500 kc/s. 15/- Miniature 200 kc s. 10/-.

MAINS ISOLATING TRANSFORMER. Manufactured by Vortexion. Fully shrouded. Will provide true 1:1 ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY 22 6 (post 2 6).

SPRAGUE CONDENSERS. Metal cased, wire ends. New .01 mfd. 1,000 volt, and .1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.I.

(Phone TERminus 7937)

Please include carriage costs on all items.
(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

Let **I.C.S.**

train YOU!



COURSES ON:—

- RADIO and TELEVISION
- SERVICING · ELECTRONICS


EXAMINATION COURSES FOR:—

- C. & G. Radio Servicing Certificate (R.T.E.B.)
 - C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence)
 - British Institution of Radio Engrs., etc. C. & G. Telecom Technicians.
- Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.

LEARN-AS-YOU-BUILD


Practical Radio Course

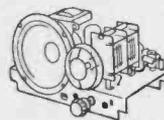- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.
- Other Learn-as-you-Build radio courses are available



MULTI-TESTER
(Sensitivity 1,000 ohms per volt)

- 5-VALVE SUPERHET RECEIVER

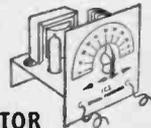

- RF/AF SIGNAL GENERATOR

Post this Coupon TODAY!

for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171), Intertech House, Parkgate Road, London, S.W.11.

Name..... Age.....
(Block Letters please)
Address.....
Occupation..... 3-60

INTERNATIONAL CORRESPONDENCE SCHOOLS

A 6K7 Superhet

ALIGNMENT OF THE RECEIVER


By J. Heath

(Continued from page 837 of the February issue)


WHEN wiring up the I.F. transformers, note that leads or tags are often marked according to the points to which they are normally connected. If so, then "anode" and "H.T. positive" leads will be the primary, with both transformers, and they are connected to anodes and H.T. positive line. With the first transformer, the bottom secondary lead or tag will often be marked "A.V.C." and this is taken to chassis, as in Fig. 3. With the second transformer, this lead is often marked "diode load" and it is also taken to chassis, as shown.

Coils

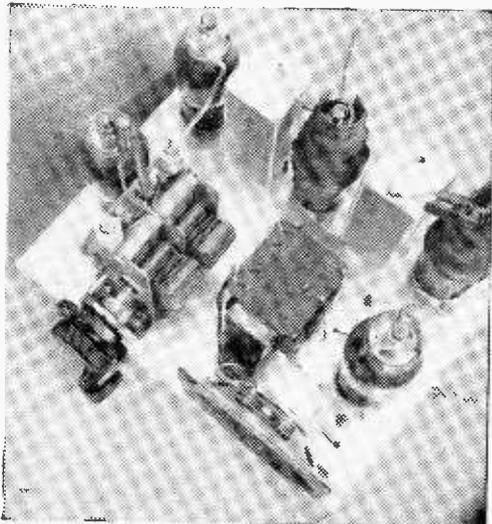Aerial and oscillator coils are fitted to a small piece of aluminium, as with some types the core adjusting screws are otherwise inconveniently situated under the gang condenser. Coil tags are numbered in Figs. 1, 3 and 4. With the aerial coil, tag 3 is wired to the rear fixed plates of the gang condenser, marked "Y" in Fig. 2. A lead also passes down through the chassis from the



Plan view of the receiver.

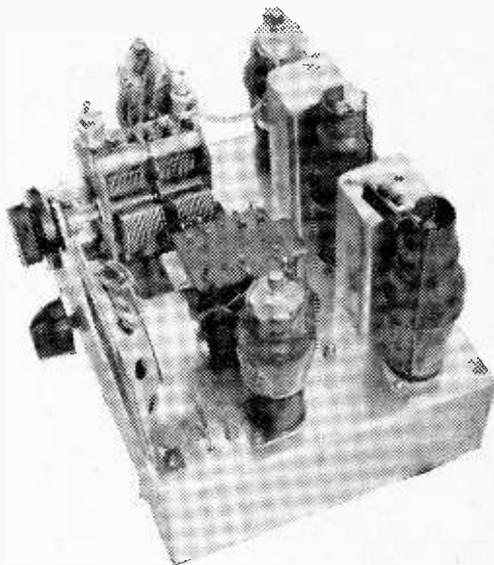

front plates "X" to tag 7 of the oscillator coil.

The tag connections shown in Fig. 4 are for the coils given in the components list (Astral Radio Products). The aerial and oscillator coils produced by other manufacturers will be equally satisfactory, but the maker's tag data must then be followed, as connections will not be the same as those in Fig. 4. The padder indicated in Fig. 1, must also be of the value specified by the coil maker. If long waves are also provided, a separate padder will be needed with the long wave oscillator coil, and will often be 150pF. Correct ganging of the tuned circuits will be impossible if the padder is omitted, or of the wrong capacity.

A tag board with two tags joined is used for H.T. positive connections, as in Fig. 3. A second small tag strip provides an aerial connection, the 500 pF condenser and 10k resistor forming a modulation hum filter. Trouble from modulation hum is unlikely, but in localities where this is severe, a 0.05 μ F 750V condenser can be wired in parallel with the primary of the mains transformer. The 500pF aerial condenser must also be of good make, and 500V or 750V rating, as it prevents mains voltages reaching the aerial.

Using and Adjusting the Set

If clear glass valves with no external or internal screening are fitted in the mixer and I.F. positions, instability is likely when the I.F. transformers are correctly aligned, and when the volume control is turned towards maximum. Valves of this kind should thus be provided with screening cans, of ready-made type, or bent up from aluminium. The cans are connected to the chassis.

Alignment is carried out as with a standard superhet. If a signal generator is available, set this to give a 465kc/s modulated output, and place the output lead near the anode connection of the mixer. The I.F. transformer cores are then adjusted for maximum response. The aerial and

oscillator trimming condensers are then adjusted for best volume with a signal around 230m, and the cores are adjusted for best volume with a signal of about 500m.

Another Method

If no generator is available, it should be possible to tune in the local station. The I.F. transformers can then be adjusted for best volume, taking care that no core is at the limit of its travel. A station of fairly low wavelength is

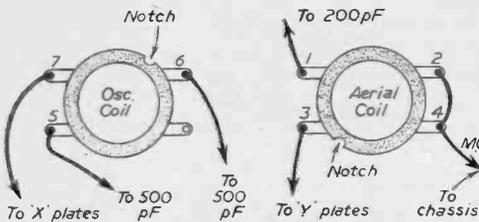


Fig. 4.—Aerial and oscillator coils.

then tuned in, and the gang condenser trimmers are adjusted for best results. The set is then tuned to a station of fairly high wavelength, and the coil cores are adjusted.

The procedure should be repeated two or three times, until no further improvement is possible. An insulated blade is most suitable, because the presence of a metal blade in the coil or transformer windings will upset adjustments.

A baffle board or cabinet is required if the loudspeaker is to give best reproduction. A cabinet is recommended, and can easily be made from $\frac{1}{2}$ in. thick or similar wood, with a 3-ply front. An aperture to match the speaker cone should be cut in the front, and covered with silk or speaker gauze. A clearance hole for the com-

A NOVEL CIRCUIT TECHNIQUE

(Continued from page 936)

Wiring

Do not use thick or multi-strand wire for wiring up the circuit. A diagram is often helpful, though most transistor circuits are relatively straightforward. A fixed order should be followed, starting, for example, with earth points, negative points, etc. Although transistor circuits are generally free from stray wire pick-up troubles, wires should be quite short.

Fig. 1 shows how to connect up the wire ends underneath the board. Time spent on good soldering pays dividends later on!


Installation

The completed circuit can be glued or bolted into place. Avoid looseness in equipment like car radios, which must be firmly constructed.

Removal of components for replacement is effected by melting the joint and levering out the loosened part.

Other Applications

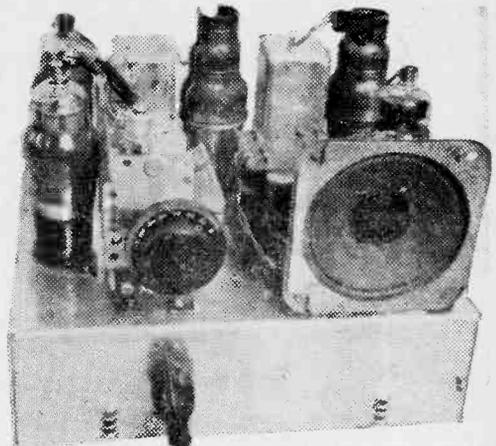
Of course, transistor circuits are not the only application of this technique: many valve circuits can be constructed using celluloid sheeting, though large components often need to be more




Front view of the receiver.

binized switch and volume control, and an opening to suit the dial used, are also required. The completed receiver can then be placed in the cabinet from behind. If a back, with rows of holes for ventilation, is screwed on, this will protect the receiver and prevent chassis or other parts being touched, and thereby avoid the chance of mains shocks from this cause. For the same reason there should be no exposed metal, such as the volume control bush or spindle, or knob grub screws, which might be touched. This can be arranged by using a knob which covers the bush and nut, and having the grub screw well recessed, or filling the grub screw hole with an insulating compound such as sealing wax. Similar precautions should be taken with the tuning control.

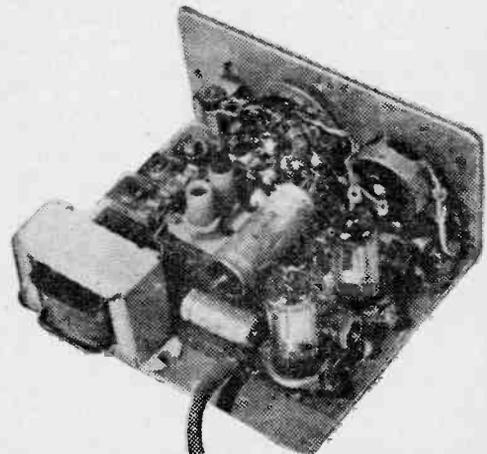firmly secured. However, celluloid is an obvious replacement for tag boards, for components can be arranged as required, and the board bolted where it is most convenient. Fig. 1 shows how to cut out large holes for valveholders, which are then bolted on in the usual way.



A receiver built on plastic sheeting.

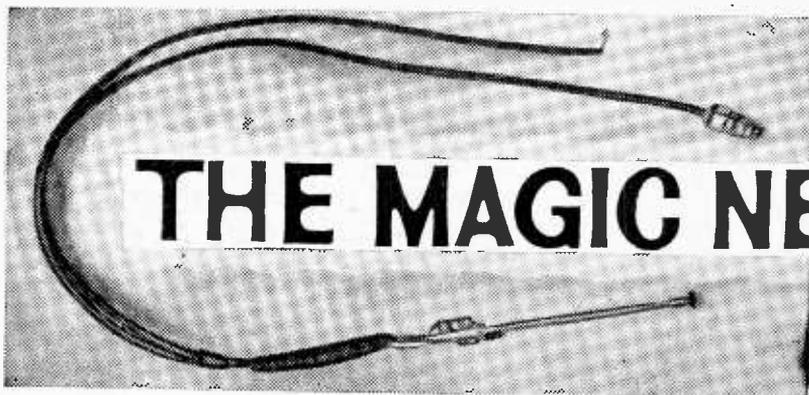

THE MAGIC NEEDLE

A DEVICE FOR CHECKING FREQUENCIES By G. Tomassett

THIS instrument, with its somewhat pre-
sumptuous name, is intended to facilitate
frequency measurements. The accuracy
obtainable, even at 200Mc/s, is of the order
of $\pm 5c/s$ or so. These figures are relative.
Explicitly, you can evaluate an unknown frequency
with the mentioned accuracy relative to
your R.F. signal generator.

Uses

The Magic Needle is operated in conjunction
with a reliable R.F. generator. A sensitive A.F.
amplifier may, sometimes, be dispensed with.
Obviously, if you work on a tape recorder, you
should not need a sensitive external audio
amplifier. The same applies if you are dealing
with a radio or TV set. The use of an external
separate amplifier does, however, simplify things,
particularly for the beginner.

The instrument has been successfully used for:—

(a) Radio sets, when, because of a defective
component or because of a serious misalignment,
the frequency has departed from its correct value.
Its use has been of invaluable help with faulty
transistor sets.

(b) TV sets, particularly in instances of channel
changes. In these cases, the instrument is really
indispensable. The line frequency can be
measured utilising the harmonics produced in the
output stage.

(c) Tape recorders to determine the erase
frequency which can be of some significance. In
this connection, owing to the relatively low
frequency, the harmonics must be used. In one
instance, where the frequency was 60kc/s, the
15th harmonic still gave an audible signal. (Zero
beats were found in this succession: 600, 660, 720,
780, 840kc/s.)

(d) Experimental oscillators of
any kind.

Operating the Test Gear

This is the sequence of the
operations to be carried out in
order to determine the value of an
unknown frequency:

(a) Connect cable Y to input of A.F. amplifier
and cable X to output of R.F. generator.

(b) Switch on all components. Allow five
minutes or more for warming up.

(c) Set R.F. generator to maximum output and
internal modulation to "off."

(d) Set A.F. amplifier to full volume.

(e) Pick up the needle, holding it where the
cables are clamped together and, as a first attempt,
put the tip of the needle as near as possible to
the coil of the oscillator under test. Often, how-
ever, this proximity is not necessary; it can some-
times be detrimental, especially when high
accuracy is required.

(f) Move the generator, operating both range
and dial until the typical approximation of the
zero beat is heard. If the sound produced is
very loud, reduce the coupling by drawing the
tip of the needle away from the circuit. When
zero beat is obtained, the frequency sought will
be within the region of $\pm 5c/s$ compared with the
frequency recorded by the R.F. generator.

It must be realised that both the R.F. oscillator
under test and the R.F. generator produce
harmonics which might be misleading. As a rule,
when more than one zero beat is heard, the
loudest will be the right one (the one to be taken
into account).

The Circuit

The R.F. current set up in R_g (internal
resistance of generator) will flow through coil "C,"
diode D1 which rectifies it and, finally, return to

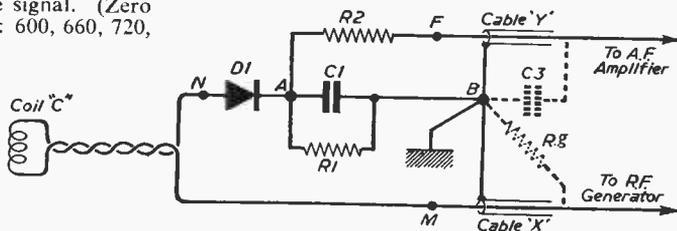


Fig. 1.—The circuit diagram.

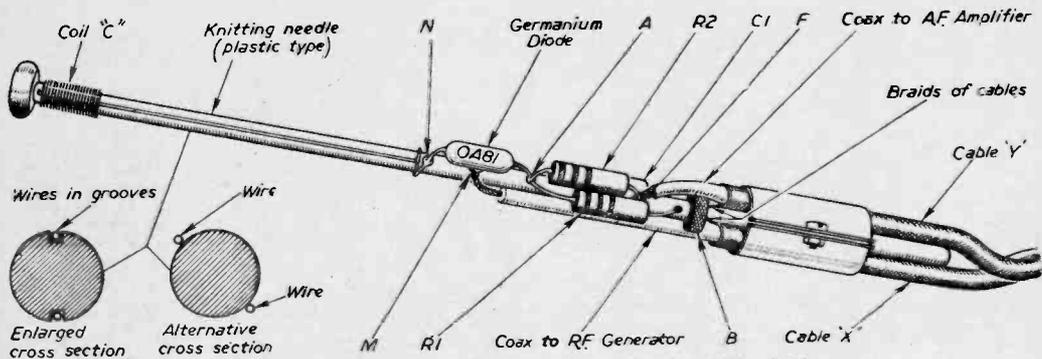


Fig. 2.—Construction and wiring of the "Needle."

Rg passing through the R1-C1 group. If any audible signal were superimposed on this current, the audible part would be taken from point A by R2, filtered by C3 (which is not physically present) and, finally, amplified by the A.F. amplifier. Obviously, if the R.F. generator is not internally modulated, nothing will be heard at the amplifying end. When, however, the tip coil "C" is

Assembly of the Parts

All the components are attached to the needle through small holes (see Fig. 2). The distance between the holes is not given because it is dependent upon and varies according to the length of the components used. Some five holes are needed and two extra ones are advisable to fix the ends of coil "C," thus preventing turns from slipping.

The wire used for the coil is also used for its connection to the rest of the circuit. In order to carry the two terminal wires of the coil to the components, it would be advisable to make two grooves along the needle (see cross section).

The coax cables are clamped together around the end of the needle by means of a bracket or simply by adhesive tape.

COMPONENTS LIST

- D1=Germanium diode (OA70 or similar).
- R1=0.47M., 1/8W.
- R2=0.1M., 1/8W.
- C1=100pF, mica or ceramic.
- Coil "C"—10 turns 25-30 s.w.g. enamelled (the number of turns is not critical; neither is the diameter of the wire used).
- Plastic needle=Any diameter in the region of 1/4in.
- Coax cables=Two short lengths (about 2ft.).

immersed in an electromagnetic field, an induced current will circulate in it. Through the rectification process of D1, the two currents (the induced one and the one delivered by the generator) are mixed so that at point A there will appear as many as four currents of the following frequencies:

(1) (fg)=frequency of generator; (2) (fx)=value of unknown frequency; (3) (fg+fx); (4) (fg-fx).

As (fx) is likely to be a radio frequency (not audible) and as (fg) is definitely a radio frequency, it is clear that only the term (fg-fx) can give an audible frequency. Further, from (4), if (fx) equals (fg) the result of the subtraction will be zero or zero beat which is, in fact, the principle upon which this instrument works. The aim, then, is to find a frequency in the range of the R.F. generator which, because of its being equal to (fx), gives a zero beat through the Magic Needle.

The "difference" current of frequency (fg-fx) or (fx-fg), feeds the audio amplifier and is carried there by means of the low-pass filter R2-C3 (C3 is not physically present but represents stray capacitances). The low-pass filter will convey to earth the other three components, namely (fg), (fx), (fg+fx). The incoming R.F. signal and the outgoing audio signal are both carried by coax cables not longer than about 2ft.

Transistorised Mixer Unit

IN the article by A. M. Shafford which appeared on page 765 of the January issue no definite details were given of the type of microphone for which the mixer is suited. The author assumed that it would normally be used with the crystal microphones supplied with popular tape recorders, that is, high impedance types. The method of gain control employed has given rise to a certain amount of criticism, but although it is not ideal, it is the simplest which can be achieved when only one transistor stage is employed and in practice gives very satisfactory results. The low amplification of the mixer makes it unnecessary to control gain after amplification; no significant improvement in signal-to-noise ratio would be achieved and a separate transistor amplifier would be needed in each channel before mixing. This procedure would complicate the design of the pre-amplifier which was aimed at simplicity and low power consumption.

The value of 10 μ F for the output coupling condenser may seem rather high, but it ensures that the unit is suitable for coupling into all valve amplifiers and as in the writer's case a fully transistorised amplifier. There is no point in choosing (say) a 0.01 μ F coupling condenser unless the unit is always to be used with amplifiers having high input impedances.


Versatile V.F.O.

FURTHER CONSTRUCTIONAL DETAILS

(Continued from page 844 of the February issue)

By R. H. Wright

THE original V.F.O. unit was constructed on an 8 in. × 8 in. × 2½ in. chassis, not because such a size was necessary, but rather because such a size was at hand. Actually, the whole unit, including the buffer valve, could be constructed easily on a 4 in. × 8 in. chassis. Eddystone have a chassis measuring 8½ in. × 5¼ in. × 2½ in. and this is designed to fit inside their type No. 644 metal cabinet. Use of this cabinet would give a very professional finish to the unit. Paxolin group panels can be used with

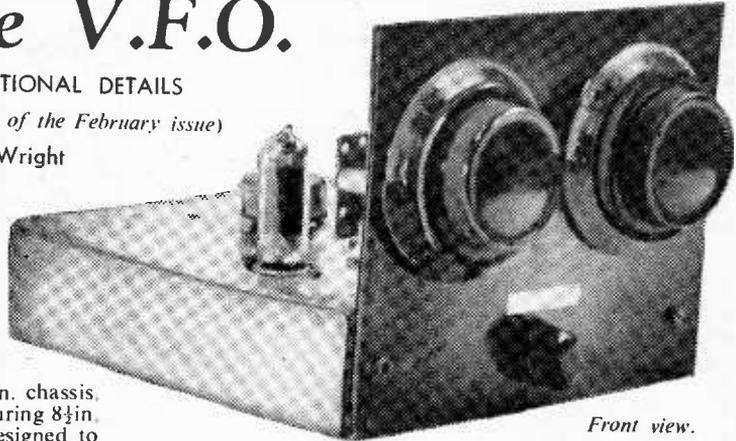

Front view.

signal and so causing interference. When the key is finally pressed it is only a moment's operation to make any final adjustment to the transmitter tuning before commencing a call.

If the full transmitter circuit suggested in the first section of the article has been built up, incorporating the V.F.O. and amplifier sections (Figs. 1 and 3) the following tuning procedure should be followed.

(i) Set the V.F.O. to the required frequency and tune the grid circuit of the buffer (C5/L2 or L3) to the second or fourth harmonic of 3.5Mc/s if final output is required on 7 or 14Mc/s. Correct tuning of this circuit would produce maximum grid current in the final amplifier circuit.

(ii) With the key pressed and the V.F.O. in operation, set C5 of the amplifier section to full capacitance value and, with the correct coil in the L1 (amplifier) position,

(Continued on page 957)


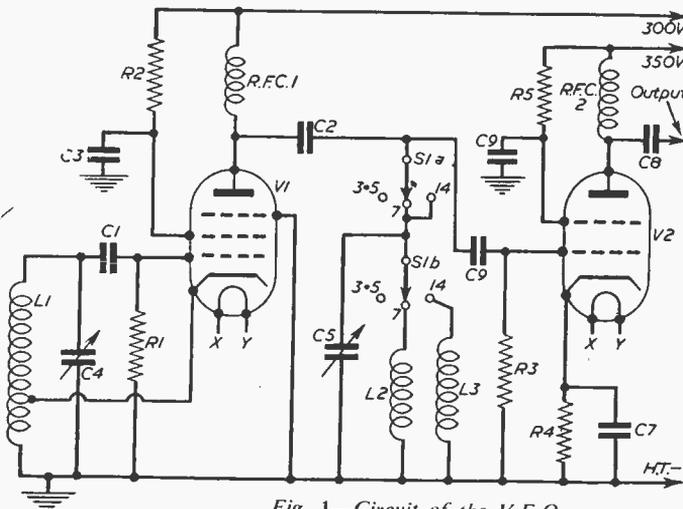


Fig. 1—Circuit of the V.F.O.

definite advantage for the mounting of many of the individual capacitors and resistors and apart from making construction actually easier (since much inter-component wiring can be carried out on the panel itself) neaten the final unit and does away with the "spiders' web" of resistors and capacitors radiating out from each valveholder.

Operation of the V.F.O.

The writer has found that, generally speaking, it is bad policy to key the V.F.O. together with the main transmitter and such action makes a chirpy note very hard to eliminate. A better method is to fit a switch in the cathode line of the oscillator valve so that the oscillator can be switched on without operation of the full transmitter. This permits the oscillator to be adjusted to the required frequency without radiating a full

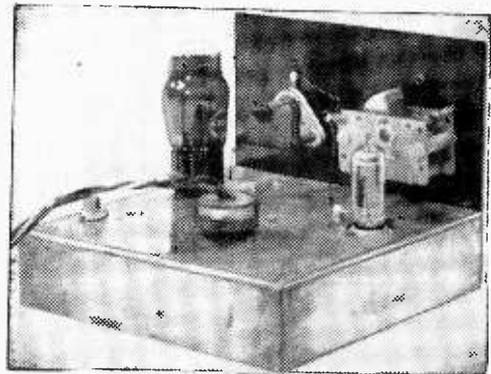


Rear view.

A Comprehensive

A THREE-VALVE CIRCUIT WITH TREBLE, BASS, VOLUME AND FILTER CONTROLS

By R. Taylor

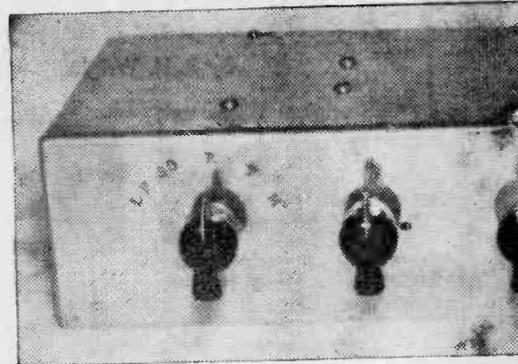

The front panel.

An ideal pre-amplifier may be stated to fulfil the following requirements: (a) to accept an electrical input from a gramophone pick-up, radio or other similar source; (b) to correct this input for amplitude and frequency, and (c) to supply a suitably amplified voltage to the main amplifier.

The main audio amplifier usually supplies low impedance loudspeaker. Very few loudspeakers have an entirely satisfactory frequency response, and dimensions, shape and furnishing of a room may again influence and colour the sound issuing from the loudspeaker. It is thus often possible to improve the overall result by the judicious use of variable tone (or frequency) correcting networks which are most conveniently situated in the pre-amplifier.

The pre-amplifier about to be described is designed to fulfil as many of the essentials tabulated above as possible, while retaining the advantage of compactness and reliability.

Specification

Three coaxial inputs are shown in the theoretical diagram (Fig. 1) for gramophone pick-up, radio and tape, but constructors not possessing a tape recorder may choose to omit the third. It must be stressed that this pre-amplifier does not contain correction networks to enable direct replay

from the tape deck playback head, and the input should be taken from a signal source after the frequency correction stage of the tape recorder pre-amp.

The inputs are taken via a selector switch to the grid of the first valve (6BR7) for voltage amplification. The load resistance RA of the pick-up input as shown in Fig. 1 will only be suitable for a magnetic type of pick-up, with an output of less than 50mV, such as the Goldring 500/600 cartridges, etc. For magnetic types of pickup with greater output, or crystal types of pickup, alternative input networks are recommended (Fig. 2).

Equalisation

A negative feedback resistance/capacity network in the anode/grid circuit of the first stage provides the necessary frequency correction for most L.P.


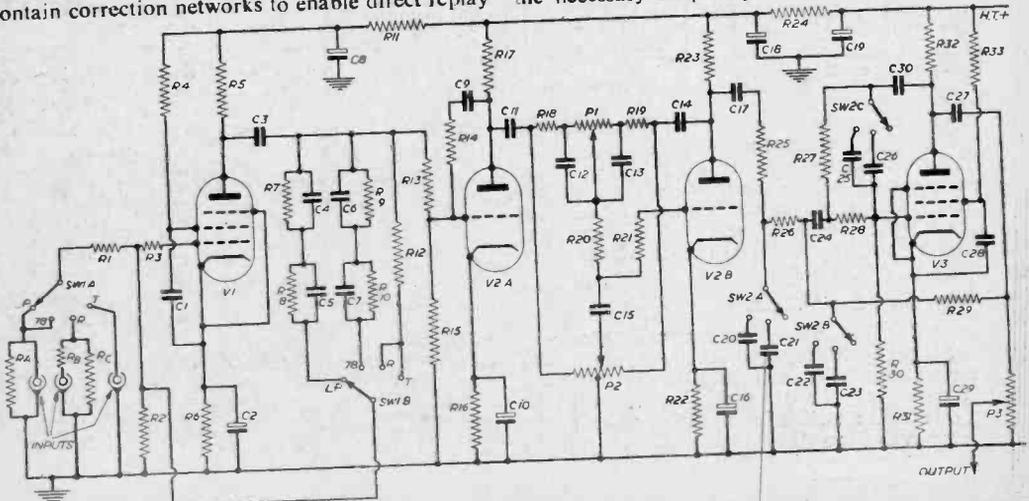


Fig. 1.—The complete circuit diagram.

Pre-amp

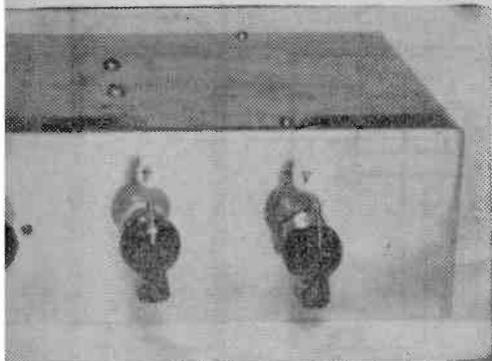

off frequency of about 35c/s with a slope greater than 12dB/octave, and is permanently in circuit. The low-pass filter can be switched from level response to frequency cuts at 7.5kc/s or 5kc/s with a slope approaching 18dB/octave.

Construction

The chassis is formed from a sheet of aluminium, preferably of 3/32in. thickness, to make a box 12in. \times 5in. \times 2½in. Apart from the input power supply junction box and coaxial sockets mounted on the rear of the chassis, the only projections are the controls on the front. As the valves run very cool, they are mounted with all the other components within the chassis, which makes a very neat, yet efficient unit.

To make construction easy, most of the resistors and capacitors are soldered on to group boards and tag strips, which can be assembled outside the chassis, with lengths of wire for connections

and 78rev/min recordings, while a resistance negative feedback circuit in combination with the potential divider Rb and Rc, attenuates the radio tuner signal sufficiently to avoid overloading the first valve stage.

The second stage (12AX7) incorporates a well known variable tone control circuit with independent cut and boost in both treble and bass frequencies, as referred to a frequency of 1kc/s.

This stage feeds into the final stage (6BR7) which includes both high- and low-pass filters. The high-pass, or "rumble," filter is useful for attenuating the irritating low frequency rumble associated with so many turntables, and has a cut-


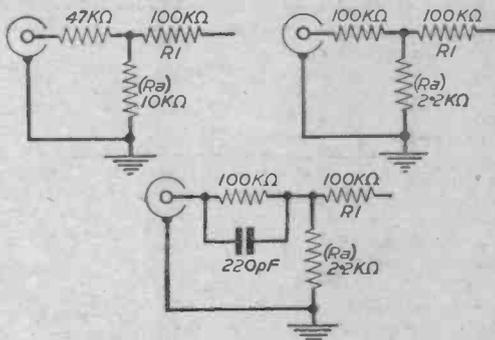


Fig. 2.—Alternative pick-up input circuits.

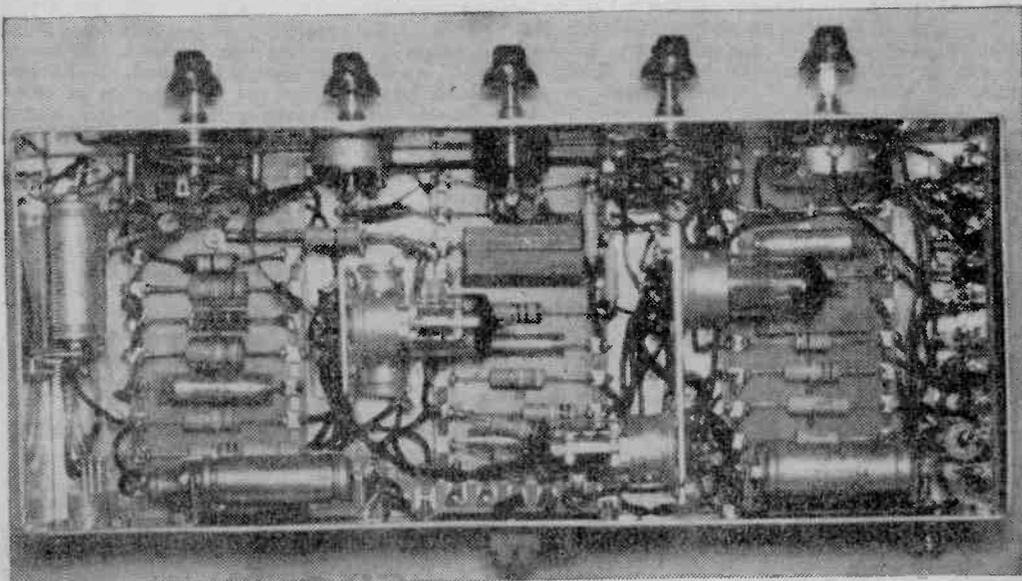

This view shows the compact layout employed

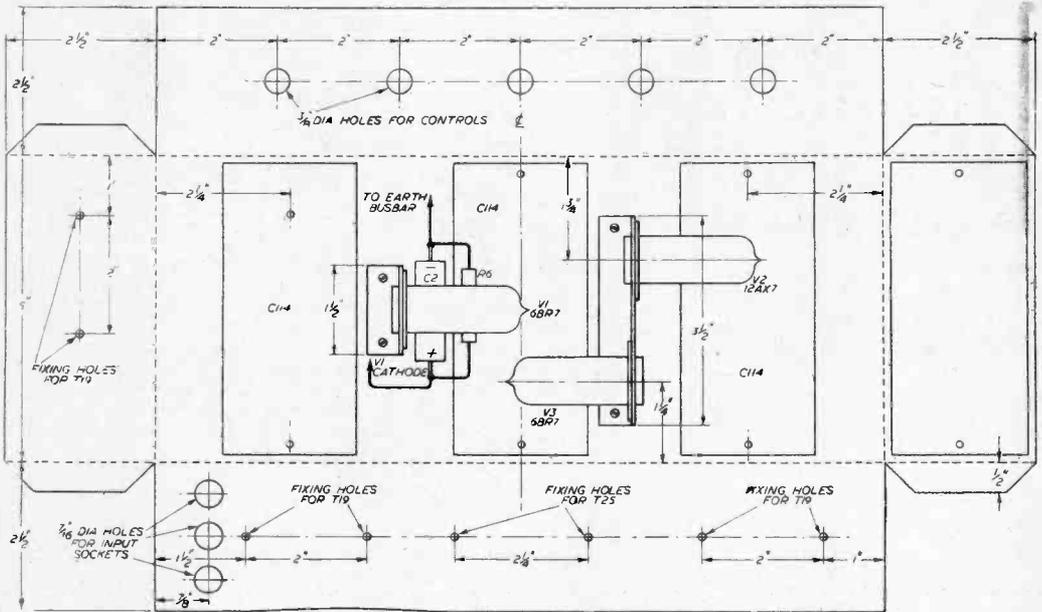


Fig. 3.—Chassis drilling details and layout.

to other units attached, before bolting into position.

Only one earthing point to chassis is used, and all connections to earth in the circuitry are made to this one point, via a heavy gauge copper busbar, the farthest end of which is insulated from chassis by connecting it to a spare terminal on a group board.

Chassis

The plan of the chassis, and approximate disposition of group boards, tag strips, etc., is shown in Fig. 3. The valveholder brackets should be made of aluminium of similar gauge to the chassis, with a 3/8 in. to 1/2 in. width right angle to bolt to the chassis. The valve sockets should be positioned to allow reasonable clearance between

the valve and the components mounted on the group boards, and a distance of approximately 1 1/8 in. from the floor of the chassis to the valve centre line will be found suitable. The group boards are raised slightly from the chassis by a spacer nut, which enables the passage of insulated wiring between board and chassis, thus making a neater appearance.

It is suggested that the assembly and wiring of the pre-amplifier be undertaken very carefully to minimise the possibility of any mistake. If care is taken in following the diagrams and instructions, no difficulty should be found. It should be noted, however, that the construction of such a compact unit demands care and patience, and the use of a pencil bit soldering iron is almost an essential.

(To be continued)

COMPONENTS LIST

Resistors :

- R1 100k
- R2 2.2M
- R3 3.3k
- R4 1.5M
- R5 220k
- R6 1.5k
- R7 470k
- R8 6.8M
- R9 3.3M
- R10 3.3M
- R11 22k
- R12 330k
- R13 100k
- R14 270k
- R15 470k
- R16 2.7k
- R17 100k
- R18 100k
- R19 470k
- R20 470k
- R21 1k
- R22 2.2k
- R23 100k
- R24 22k
- R25 68k
- R26 68k
- R27 3.3M
- R28 100k
- R29 390k
- R30 470k
- R31 560
- R32 100k
- R33 470k
- Ra) see
- Rb) text
- Rc)

Capacitors :

- C1 0.1 μF paper 350VW
- C2 25 μF electrolytic 25VW
- C3 0.05 μF paper 350VW
- C4 220pF ceramic
- C5 830pF ceramic
- C6 50pF ceramic
- C7 470pF ceramic
- C8 8 μF electrolytic 350VW
- C9 0.01 μF 350VW
- C10 25 μF electrolytic 25VW
- C11 0.05 μF paper 350VW
- C12 4,700pF ceramic
- C13 4,730pF ceramic
- C14 0.05 μF paper 350VW
- C15 100pF ceramic
- C16 25 μF electrolytic 25VW
- C17 0.05 μF paper 350VW
- C18 8 μF electrolytic 350VW
- C19 8 μF 350
- C19 8 μF electrolytic 350VW
- C20 680pF ceramic
- C21 470pF ceramic
- C22 1,500pF ceramic
- C23 1,000pF ceramic
- C24 4,700pF ceramic
- C25 15pF ceramic
- C26 10pF ceramic
- C27 0.02 μF paper 350VW
- C28 0.1 μF paper 350VW
- C29 25 μF electrolytic 25VW

- C27 0.02 μF paper 350VW
- C28 0.1 μF paper 350VW
- C29 25 μF electrolytic 25VW

Sundries :

- SW1 2-pole, 4-way switch
- SW2 3-pole, 3-way switch
- B9A valve bases
- Coaxial sockets
- P1 1M pot. (linear)
- P2 500k pot. (linear) with tap at 50% rotation
- P3 250k pot. (log.)
- Group boards (Bulgin C114)
- Tag strips (Bulgin T19 and T25)


Valves :

- V1 6BR7
- V2 12AX7
- V3 6BR7

Transistors for P.A.

ADEQUATE OUTPUTS CAN BE
OBTAINED FROM SIMPLE CIRCUITS

By J. Gray

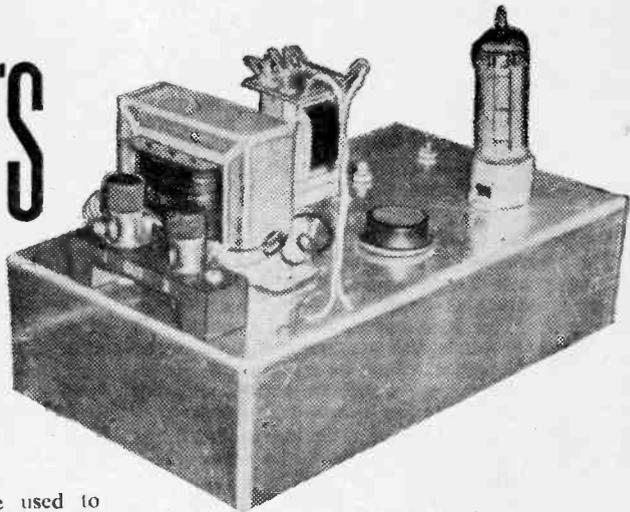

A TRANSISTOR amplifier can be used to work a loudspeaker for sports, outdoor events, and similar functions, and this type of equipment can be independent of the need for mains or accumulator supplies. It is not practicable to obtain volume equalling that of a large mains-operated public address amplifier, which may deliver many watts, but a useful output can nevertheless be obtained.

In general, one of two purposes will be in view. First, it may be necessary to work a loudspeaker situated some distance from the microphone, so that the person using the latter can be at the best observation point. Or it may be necessary to obtain a good, easily audible signal without the person having to raise his voice. Transistor equipment will easily meet these needs, but ordinary transistor circuits will not give sufficient output for several loudspeakers, or very high volume coverage over a wide area.

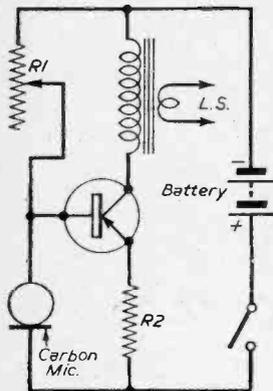


Fig. 1.—Directly coupled circuit.

Simple Circuit

A very simple circuit is shown in Fig. 1, using a microphone directly connected to a transistor. In this circuit, as in the others described later, a carbon microphone is essential to secure enough output. Various surplus microphone inserts and hand mikes may be used. Carbon microphones do not themselves produce any current, but present a varying resistance to a current obtained from a battery. When the switch is closed,

current flows through the microphone and R1. R1 and the microphone act as a voltage divider supplying the transistor base. To secure a satisfactory base voltage, R1 is thus best of variable type. It should be set to a fairly high resistance at first, this being reduced until best results are obtained.

Best output will be obtained with a microphone of low resistance, preferably not over 50ohms. A wire-wound resistor of some 250ohms can then be used for R1. If the microphone is of high resistance then R1 must be increased in value to suit. The total resistance of R1 and the microphone then becomes rather high, so that the current through the mike is small, and the signal obtained from it is much reduced. Enough output will not be obtained with a high resistance carbon microphone unit.

R2 limits current, and can be about 20hms for a power transistor such as the V30/20P. It is also wire-wound. A power transistor output transformer is essential, transformers intended for valve circuits being unsatisfactory. For the

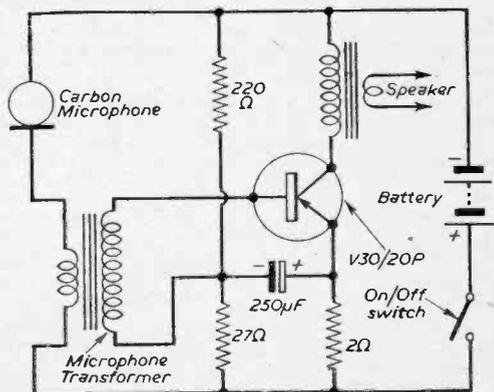


Fig. 2.—Adding a coupling transformer.

V30/20P and a 3ohm speaker, the transformer ratio should be about 3.2:1.

The battery voltage may be anything up to 12. Current is only drawn when the switch is closed. To save current, and let the transistor cool, a spring-loaded push switch may be used, and held down when announcements are being made. Dry batteries with large cells can be used, but for long periods of operation at best volume, an accumulator is recommended.

Transformer Coupling

The sensitivity of the circuit can be improved, especially with a microphone of fairly high resistance, by using an input transformer, as shown in Fig. 2. The base circuit of the transistor is completed through the secondary, and correct operating voltages can thus be maintained. Resistor values are for the transistor shown, but can be changed to suit other power transistors.

For maximum volume, the primary of the transformer should have about the same resistance as the microphone. If primary and mike are of rather dissimilar resistance, it will be found that no increase in volume is achieved. Best possible volume is obtained when both primary and microphone are of quite low resistance, so that a large microphone current passes through the primary. This is most easily assured by using one of the various "power" type microphone units. As with Fig. 1, any battery voltage

grid of which requires an input voltage and negligible current. A valve pre-amplifier thus allows a high-ratio microphone step-up transformer to be used. This gives a very great increase in sensitivity, because the valve itself also provides more amplification.

A circuit of this kind is shown in Fig. 3, the valve being of a type intended for 12V heater and H.T. supply, so that only a 12V accumulator will be needed. Intermittent operation is, in fact, possible from a 12V dry battery made up of large cells.

Transformer Ratio

For best sensitivity, microphone transformer primary and mike should be of similar resistance, as explained. The ratio is not very important, 50:1 being average. A lower ratio may be needed with high resistance microphone units. Surplus microphone transformers of suitable type will do well, and will have a very high secondary resistance. Some speaker output transformers will function, with the low resistance winding used as primary.

The valve anode transformer is of the transistor coupling type, and this also applies to the output transformer. Both these transformers are wired so that the larger winding is primary, because a step-down ratio is necessary to match speaker to transistor, and transistor to valve. Wiring any of the transformers incorrectly will result in little or no output at all.

A switch completes the valve heater circuit, so that the cathode can be maintained at operating temperature. Talking is then possible immediately the push switch is closed. With only one switch it would be necessary either to leave the microphone and transistor drawing current, or to wait for the valve to heat up.

Underchassis wiring for the circuit in Fig. 3 is shown in Fig. 4. The secondary of the output transformer goes to speaker. The exact layout of parts is of little importance, provided the transformers are some distance apart, and preferably with their cores at right angles, to avoid howling.

The 220ohm resistor is best of 1W rating. It can be made up by wiring two 440ohm $\frac{1}{2}$ W resistors in parallel, or two 110ohm $\frac{1}{2}$ W resistors in series. The low value

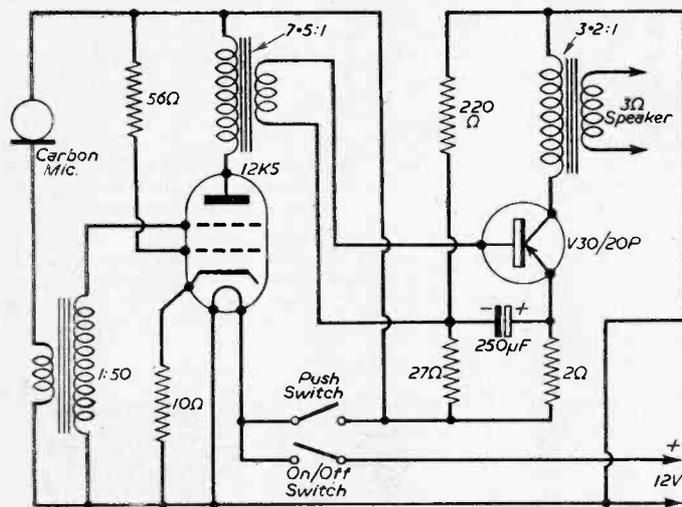


Fig. 3.—Circuit with valve pre-amplifier for 12V operation.

may be used, but a 12V supply from accumulator or large dry cells will be best.

A Valve Pre-amplifier

A transistor requires power, in the form of current, to drive its base circuit. This means that a step-up transformer cannot be used from the microphone, because the transformer could only increase signal voltage at the expense of current. This difficulty does not arise with a valve, the

resistors are best wire-wound.

Transistor Mounting

When anything approaching maximum output is being obtained, the transistor will become hot. This heat must be conducted away. A metal plate, or the metal chassis, is thus used for this purpose. In Fig. 4, the transistor is bolted to the chassis, but is not in electrical contact with it. To obtain the required electrical insulation,

A Transistorised Voltmeter

HIGH INPUT RESISTANCE IS A FEATURE

By G. Connor

THE meter described in this article is intended for the measurement of voltages in circuits where very small currents are to be found.

If a conventional moving coil or moving iron instrument is connected to a circuit in which only a few micro-amps current flow, then the high current drawn by the meter will result in extremely inaccurate readings. To overcome this effect, it is necessary to use a voltmeter with a very high impedance. The valve voltmeter is an example of such a device.

It was decided that as transistors are cheap and need only a low voltage battery supply we would use them, therefore making the meter port-

instrument can be used over a wide temperature range.

The meter is adjusted initially as follows:

1. Switch on and after short circuiting the input adjust the set-zero R1 control for zero

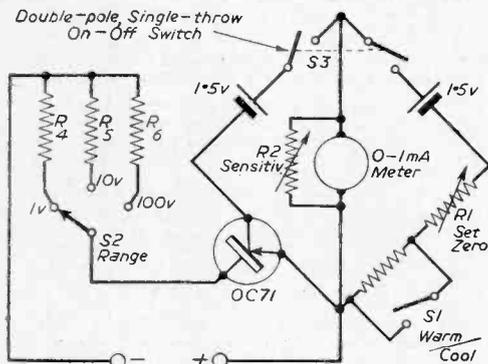


Fig. 1.—Circuit of the meter.

able in all ways. When transistors are used in the common emitter configuration, it shows a high impedance between the base and emitter and this fact has been made use of in the design of this apparatus.

Circuit

The circuit shown in Fig. 1 may be considered as a bridge circuit with the meter in the centre arm. Once the circuit has been balanced by adjusting R1 and S1, any variation in the impedance between transistor collector and emitter will destroy the bridge balance and cause the meter to be deflected. The control R2 acts as a shunt to the meter and can be used as a sensitivity control.

The base of the transistor draws current from the supply to which the instrument is connected and since the emitter to collector impedance varies as the base current varies, then changes in the meter deflection occur. To increase the range of the instrument and to increase its impedance, series resistors are switched into the base circuit by S2. In the circuit a warm/cool switch has been provided, this is necessary owing to the dependence of the transistor operating conditions upon temperature. By the use of this switch, the

COMPONENTS

Transistor	OC71 or equivalent.
Meter	0-1mA.
R1	50k linear variable.
R2	25k " "
R3	47k fixed carbon.
R4	22k " "
R5	220k " "
R6	2.2M " "
S1	Two-way, single-pole, toggle switch.
S2	Three-way, single-pole, rotary switch.
S3	Two-way, two-pole, toggle switch.

reading on the required range. If this proves difficult, it may be necessary to use the warm/cool switch.

2. Connect the instrument to source of known potential and set the pointer of the meter by means of the sensitivity control.

Silicon Controlled Rectifiers

By E. G. Bulley

THESE devices can be said to be a development from both the silicon transistor and rectifier. They are in fact neither transistor nor rectifier but are analogous to the grid controlled rectifier or thyatron, and are p-n-p-n semi-conductors. They can, therefore, best be described as a controlled switching device. Such devices will, however, become more common and available to the constructor and experimenter as in the case of the transistor.

Silicon controlled rectifiers have a low forward voltage drop which permits high current ratings and high efficiency with low voltage requirements. Considering these devices, one will appreciate that they have three rectifying junctions, as can be seen from Fig. 1. The first "n" is known as the cathode, whereas the first "p" is known as the "gate." This termination acts as a grid as in thyatron practice and does not, therefore, need further explanation. The second "p" type is known as the anode and likewise, the reader will appreciate its use.

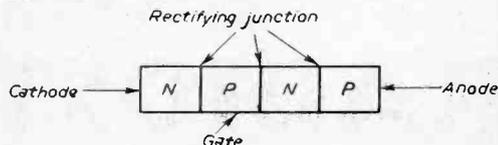


Fig. 1.—Diagram of the device.


LEARN Train at home in your spare time
RADIO & T.V. SERVICING
 this new, easy, practical way!



**YOUR OWN... BUSINESS...
 CAREER... OR
 FASCINATING HOBBY**



Electronics is rapidly becoming a great new industry with far reaching applications into every field of modern activity.

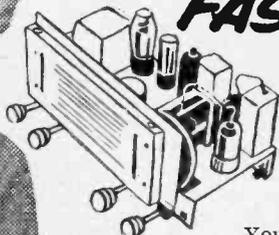You can learn all the essentials of this new science at home in your spare time and turn your knowledge to good purpose! Now is your chance to set up your own business and be your own boss!



**RADIOSTRUCTOR EQUIPMENT COURSES
 MAKE LEARNING SO SIMPLE**

You learn by building actual equipment with the big kits of components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments—there are no complicated mathematics! Instruction manuals and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner; in fact, you really have fun whilst learning! And you end by possessing a first-rate piece of home equipment with the full knowledge of how it operates, and how to maintain it afterwards. In fact, for those wanting help with their radio career training, to set up their own full or part-time servicing business, or the hobbyist, this new and instructional system is exactly what is needed, and it can be provided at very moderate cost with payments available. Post the coupon now, for full details. There is no obligation of any kind.

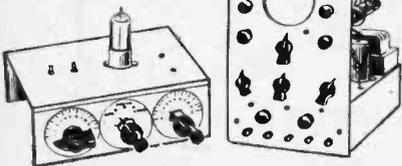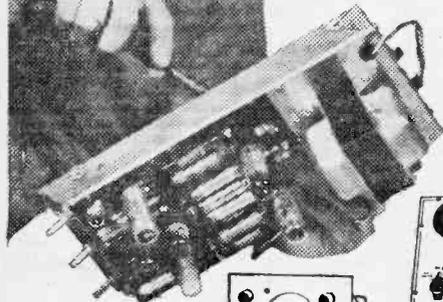

- NO MATHEMATICS
- EASY TERMS AVAILABLE
- ALL TEST EQUIPMENT SUPPLIED
- PERSONAL TUITION
- FINEST EQUIPMENT

POST TODAY FOR FREE brochure

To RADIOSTRUCTOR (Dept. G82)
 46 MARKET PLACE, READING, BERKS.
 Please send Brochure without obligation to:



Name

Address

BLOCK
 CAPS
 PLEASE

(827) We do not employ representatives 3-60

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

LASKY'S RADIO

LOWEST PRICED TAPE RECORDER EVER OFFERED!

For A.C. Mains 200/250 v. Few only left. Foreign make, brand new in maker's cartons. 2-speed. 3 $\frac{1}{2}$ and 7 $\frac{1}{2}$ twin track, 60 min. playing time at 3 $\frac{1}{2}$: 30 min. at 7 $\frac{1}{2}$. Inputs for mike and tuner. 5in. speaker. Smart duotone blue-grey carrying case, 12 $\frac{1}{2}$ x 9 $\frac{1}{2}$ x 7 $\frac{1}{2}$ in. Weight approx. 6 $\frac{1}{2}$ lbs. TODAY'S VALUE £35.

LASKY'S PRICE including 5in. Spool of Tape and empty Spool, Crystal Hand Mike and Radio Jack,

21 Gns.

Carr. & Ins. 12/6.

Now Ready! The Finest Components Catalogue

for the home constructor.
100 pages, 8 $\frac{1}{2}$ x 5 $\frac{1}{2}$ in.,
copiously illustrated.
PRICE 2/-. Post 6d.

With free Bargain Bulletin.

TAPE DECK OFFERS

Latest **MOTEK K.10**, press-button controls, 3 motors, 3 speeds, rev. counter, frequency response better than 40 to 12,000 c/s at 7 $\frac{1}{2}$ i.p.s. 2-tone grey finish. Limited number only. Listed at £22. LASKY'S PRICE £13.19.6.

Latest **COLLARO Studio Tape Transcripator**, 3 motors, 3-sp.d., 1 $\frac{1}{2}$, 3 $\frac{1}{2}$, 7 $\frac{1}{2}$ i.p.s. Fitted digital counter. Takes 7in. spools. Push-button controls. £15.15.0.

COLLARO MK. 4 Tape Transcripator, fitted digital counter. Few only. £17.19.6.

Carriage and Insurance all Tape Decks, 12/6.

Latest **B.S.R. "MONARDECK"**. Single speed, 3 $\frac{1}{2}$ i.p.s. Takes 5 $\frac{1}{2}$ in. spools. Simple controls. LASKY'S PRICE £9.19.6.

SPECIAL OFFER OF RECORDING TAPE
Famous make. P.V.C. base on latest type plastic spools. Brand new, perfect and guaranteed. 1,200ft. on 7in. spool, 21/-; 1,200 ft. on 5 $\frac{1}{2}$ in. spool, 22/6.

GEVAERT L.P. PLASTIC TAPE. 1,700 ft. (7in. spool), 35/-; 850 ft. (5in.), 18/6; 210 ft. (3in.), 6/6.

SCOTCH plastic base, 1,700 ft. (7in. spool). 25/-.
All orders for Tape post free.

SINGLE PLAYER BARGAINS

E.M.I. 4-speed, wired for STEREO and fitted Acos stereo t.o. cartridge. £6.19.6. Post 5/-.

COLLARO 4/564 or **GARRARD 4SP.** 4-sp.d., auto stop, t.o. crystal pick-up. £6.9.6. Post 5/-.

COLLARO Junior 4-speed Motor and separate crystal pick-up. 75/- Post free.

4-SPEED MIXER AUTO-CHANGERS

Brand New
in makers'
cartons



B.S.R. type UA8, complete with latest "ful-fi" pick-up. £6.19.6. Post 5/-.

Ditto, wired for STEREO and complete with stereo cartridge, £7.19.6.

B.S.R. latest type UA12, wired for STEREO and complete with stereo cartridge. £8.19.6. Post 5/-.

COLLARO, complete with Studio crystal pick-up and sapphire stylus. £7.19.6. Post 3/6.

GARRARD 4-sp.d. Auto-changers, monaural, from £9.19.6.

Wired for STEREO and complete with stereo cartridge, from £11.19.6.

LASKY'S (HARROW ROAD) LTD.

Open all day Saturday. Early Closing Thurs. Mail Orders to Edgware Road, please.
42. TOTTENHAM COURT ROAD. W.1. 207. EDGWARE ROAD. LONDON. W.2.
Telephone: MUSeum 2808. PADDINGTON 32712.

THE WORD **MAXI-Q** IS THE REGISTERED
TRADE MARK
OF DENCO (CLACTON) LIMITED
IT IS ALSO A GUARANTEE OF
WORKMANSHIP & TECHNICAL PERFORMANCE

OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1/4d. FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 1/4 IN STAMPS.



MODULATED TEST OSCILLATOR MTO.1

- ★ Provides a modulated signal suitable for I.F. alignment, also trimming and tracking R.F. circuits.
- ★ Frequency is continuously variable from 170-475 kc/s and 550-1,600 kc/s
- ★ Suitable for the alignment of transistor receivers.
- ★ Operates from a single 9-volt grid-bias battery (not supplied) which is housed within the unit.
- ★ The case is manufactured from steel and is finished in silver hammer. The front panel is gloss black bearing white lettering. Dimensions are 5 1/16in. x 4 1/16in. x 3in.
- ★ Supplied with full operating instructions.

PRICE £3/17/6

PLEASE SEND S.A.E. WITH ALL ENQUIRIES.

DENCO (CLACTON) LTD.


(DEPT. P.W.)

357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX

The "No. 19" Set

FURTHER IMPROVEMENTS

By D. W. Dillon

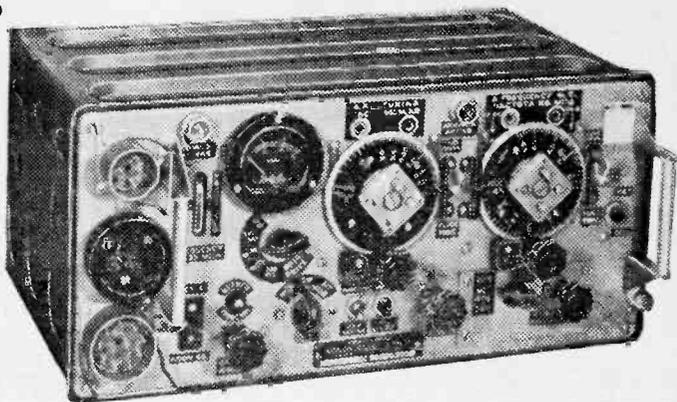

THE recent release of thousands of ex-army American-built W.S. No. 19 Mk.2's has resulted in almost every enthusiast's shack in the country containing one. While they are generally used in their original condition, several major defects soon become apparent. The first and most important of these is a great lack of selectivity—the subject of a recent PRACTICAL WIRELESS article. The second fault is that too much associated equipment is necessary for the operation of the set: power unit, accumulators, junction box, microphone, headphones and heavy connectors! The AVC action is too heavy and sluggish and the signal to noise ratio is very poor. It is very difficult to transmit good CW because of the lack of sidetone facilities. On telephony the output power is very low, the modulation invariably downward, and the speech quality poor. It is therefore fortunate that by the removal of the "B" set and "I.C." amplifier, much space is available for modifications. Although several amateurs have modified the "B" set for local two-metre use, in the majority of sets, this space simply goes to waste.

Modifications

The first part of this article should be of interest to all 19 set owners, and the carrying out

of the simple modifications described results in transformation into a highly sensitive, selective and inexpensive mains-operated receiver. The second part of the article concerns the transmitter modifications and is of particular interest to licensed radio amateurs and those who hope to obtain a licence shortly. It should, however, be noted that, as with any radio transmitter, no matter how low the power, a Post Office licence is necessary before any attempt is made to transmit into an aerial.

The transmitter modifications will allow fully automatic sidetone monitoring on CW. The original circuit allowed only 12W input at about 30 per cent. efficiency on telephony, which does not usually result in flattering signal reports! This article will describe the addition of a 15W modulator stage requiring few extra components and which will allow 30W of good quality 100 per cent. modulated phone output to be run to the 807 P.A. Alternatively series-gate modulation is also described which gives carrier controlled output. The advantage of this method are the small space and few components required, but the disadvantages are lower efficiency and the necessity for 67½-90V negative bias on the modulator.

Testing

Having received the set, it is strongly recommended that it be tested in its original form, by obtaining the loan of the associated equipment. After it has been proved to be working satisfactorily, the B set and I.C. amplifier are stripped out. All the components to the left of the above-chassis screen (when looking at the front panel) should be removed, as should also those to the left of the below-chassis relays, with the exception of the key jack leads, the leads to pin 4 (green) on the 12-way plug and those to pins 4 (red) and 6 (speckled red) on the six-way plug. The B set gain control also remains. The six- and 12-way plugs are removed, the 12-way one being discarded and replaced by a British five-pin socket. The inside "plug" part of the five-way plug is discarded, the outside casing being once again bolted on to the panel, with a Mazda octal valve-holder bolted behind the panel to receive the speaker and remote control plug. The braided earth lead is connected to tag 3 on the holder.

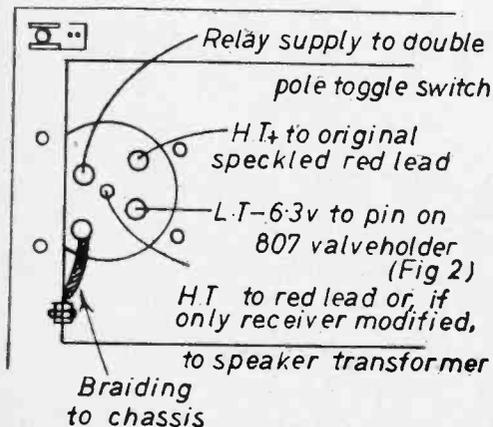


Fig. 1.—Wiring of the five-pin holder.

while the original red (H.T.) leads are re-routed under the chassis, being connected to the five-pin socket as shown in Fig. 1. A closed circuit jack is substituted for the "quench control" grommet.

6V Operation

The 12V line is earthed at the 807 valveholder (Fig. 2), and a lead taken from the other heater tag to the five-way socket. This allows 6V operation of the heater chain. The green lead (ex-pin 4 is attached to the headphone jack socket. The

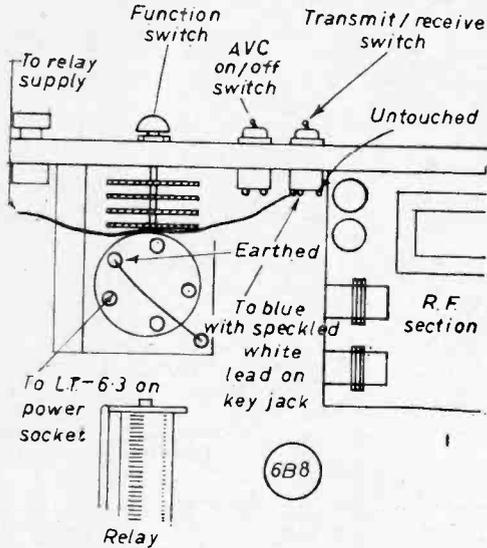


Fig. 2.—L.T. circuit rewiring.

leads to the single-pole toggle switch on the front panel are removed, as are also the left-hand section leads on the double-pole toggle switch.

The green and blue leads on the other section should not be disturbed. The large 0.1μF paper condenser fixed to the chassis beside the P.A. tuning condenser is replaced by a 750VW, 0.0005μF type. The 10Ω variable resistor (het tone) is removed and the leads insulated. In its place is mounted a 10k wire-wound potentiometer. The resistor between the cathode (pin 8) of V1A (6K7) and earth is disconnected from the chassis tag, and joined to the potentiometer slider. The left-hand tag of the potentiometer is earthed. This is the new R.F. gain control. The single-pole toggle switch on the front panel is used as the AVC on/off switch, being connected between chassis and the AVC line (white) on the tagboard near the 6B8 valveholder.

The bracket which originally

supported the B set tuning condenser is modified to support a miniature air-spaced 0.0005μF variable condenser. This bracket is replaced in its original position, together with the calibrated knob. A 1½in. diameter 3in. coil former 3in. long is wound with 18 turns 22s.w.g. tinned-copper wire, evenly spaced over 2½in., is mounted directly on the old E1148 valveholder. One end is joined to a soldering tag on the tuning condenser frame, and the other to the fixed vanes. The B set aerial socket is removed and replaced by a small ceramic feed-through insulation. This is joined to the fixed vanes. A four turn insulated link is fixed around the earthed end of the coil, and connected to a short piece of 80Ω coaxial cable, which passes directly under the condenser spindle and meter to the tank coil. The original screened box is replaced over the aerial tuning components.

Diode

A crystal diode is connected, with the black end to the fixed vanes and the red end to the small tagboard in the screened box. A wire is taken from this in the direction of the tank coil and marked for later described modifications. The lid of the box is fixed in position. The lead to the A set aerial socket is removed, together with the connection to C1A and the R.F. C12B.

The tank coil L3A is removed, the connections being noted. The tapping point is ignored, and about three turns removed from the upper end. A four-turn insulated link is wound on the lower end and connected to the coaxial cable. The coil is replaced, the coaxial cable outer sheath being earthed to chassis at its base and all the original leads, with the exception of that to the tapped point, being reconnected to the coil. The set is now ready for testing.

(To be continued)

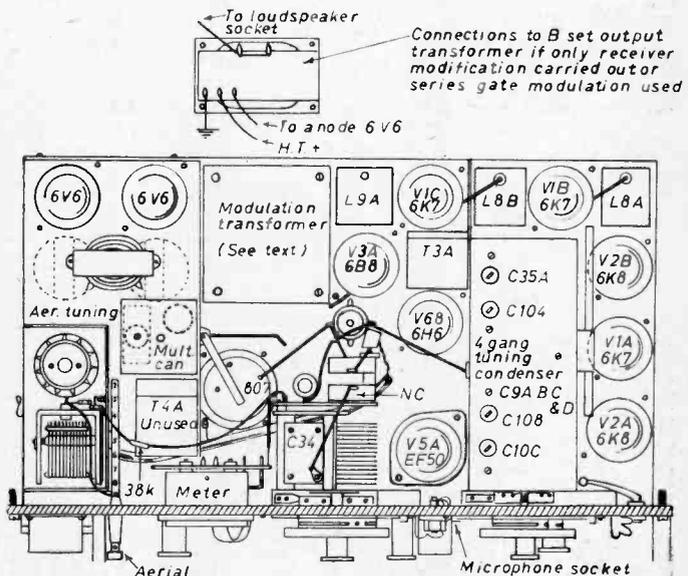


Fig. 3.—Top view of modified 19 set.

CIRCUITS FOR AUDIO AMPLIFIERS

-a book every enthusiast will want!



This new Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction.

Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives just the sort of information you need.

This informative book costs only 8/6. The demand for it is high, so get your copy now from your local radio dealer.



Mullard

MULLARD LIMITED • MULLARD HOUSE • TORRINGTON PLACE

LONDON W.C.1
MVM1423A

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
"NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng..
- Electrical Eng..
- Civil Engineering.
- Radio Engineering.
- Automobile Eng..
- Aeronautical Eng..
- Production Eng..
- Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I. Mech. E.
- A.M.I.C.E.
- A.M.I. Prod. E.
- A.M.I.M.I.
- L.I.O.B.
- A.F.R.Ae.S.
- B.Sc.
- A.M. Brit. I.R.E. City & Guilds
- City & Guilds
- Gen. Cert. of Education
- Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"

(Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME (SE/21)



THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

Transistorised Timing Unit

AN INEXPENSIVE CIRCUIT

By L. Baker

THIS photographic process timer is simple to use, inexpensive to build, and small in size, making it a useful accessory in any amateur's darkroom. There are very few parts, and the average constructor will have many, if not all, of these already to hand. The circuit uses a single transistor of the red spot surplus type which makes possible the small size of the finished unit. The size of the case of the prototype is $3 \times 5\frac{1}{2} \times 2$ in. This case was originally intended as a food box of the plastic type and is obtainable from all multiple stores. Other types of box or case can, of course, be used, but it is best to use insulating materials such as wood or plastic for the case of this unit so as to prevent any possibility of electrical shock.

Relay

Generally, the size of the relay used will govern the actual size of the finished unit. The relay must have a coil resistance of 2,000 Ω . In the original model, a surplus type of relay was used, although the P.O. type 3000 works just as well, as indeed will any relay having the required coil resistance. The contacts of the relay must be capable of carrying a reasonably large current dependent on the lamp type in the enlarger. The condenser C1 in the diagram (500 μ F) is made up of two units of 250 μ F each. However, any number of condensers may be connected in parallel in order to obtain the required 500 μ F. The positive side of all the condensers used must be connected together as should the negative sides. The small transistor capacitors now on the market will suit admirably and any number of these connected in parallel to give the 500 μ F will suit.

The 2k potentiometer should preferably be a wire-wound type in the interests of accuracy and long service. In the prototype the on/off switch is ganged with this potentiometer, but a separate on/off switch could be fitted if it is considered desirable. The tag strip fitted inside the case serves the useful purpose of providing anchoring points for the wiring and transistor. The resistor R2 in the diagram is 100 Ω and rated at $\frac{1}{2}$ W. A larger wattage component could be used here if $\frac{1}{2}$ W type is not to hand. The output socket mounted at the side of the plastic case in the prototype was taken from an old L.T. battery of the "dry" type. The writer used this socket as it was small and neat and easily mounted. Other two-pin sockets will suit just as well.

The relay should be mounted first and holes should be drilled in the case for the fixing bolts. Holes should be then drilled for the potentiometer, S2, the tagstrip, and the output socket. Having drilled the holes, all the parts should

be removed from the case which should be covered with one of the thermoplastic materials now available. Alternatively, if a plywood case is used, this can be covered in rexine or similar material. Readers who are skilled in woodwork-ing may care to sand and polish the case. All parts may now be mounted again and the wiring completed. It is best to wire in the transistor last and a heat shunt should be applied to the wires of this component while the iron is applied in order to avoid damage to this component. A pair of tags on the tagstrip are utilised to secure the mains flexible lead; one lead (neutral) from the mains is wired from the tagstrip directly to the output socket, the other lead being taken also to the output socket via the relay contacts.

Batteries

The batteries in the prototype unit were enclosed in the case of the unit. These batteries consisted of two transistor power supply batteries (each of 9V) wired in series to give 18V. One terminal of the on/off switch serves as the anchor point for the positive connection to the batteries. The negative connection to the batteries is taken from one terminal of the relay coil. The other parts are suspended in the wiring. Some of the tags on the strip are not used at all and some serve the purpose of

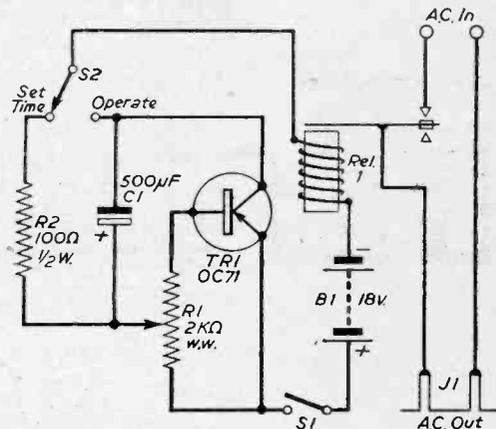


Fig. 1.—The circuit diagram.

anchoring the tagstrip to the plastic case by means of small nuts and bolts. Good quality plastic insulation wire should be used throughout. All wiring on completion should be double checked with batteries disconnected, for possible mistakes or short circuits. It is a good idea to include a 0.5mA meter in series with the positive lead to the batteries as a temporary check. On switching on a small current should flow: approximately 1 to 2mA, certainly no more.

To test and calibrate the instrument, the dial must be marked out and attached to the face of the instrument temporarily. It is not possible to mark in the seconds time on the dial accurately without at first experimenting with the completed unit.

(To be continued)

The decision is **YOURS**. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Technical Training in Radio, Television

and Electronics Engineering with

Choose the **RIGHT** course:

- RADIO & TELEVISION ENGINEERING
- INDUSTRIAL TELEVISION
- RADIO & TELEVISION SERVICING
- RADIO SERVICE AND SALES
- VHF/FM ENGINEERING : ELECTRONICS
- COMPUTERS & PROGRAMMING


ICS provides thorough coaching for professional examinations:

Brit. I.R.E., City and Guilds Telecommunication Technicians. C. & G. Radio Servicing (R.T.E.B.); C. & G. Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Courses

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

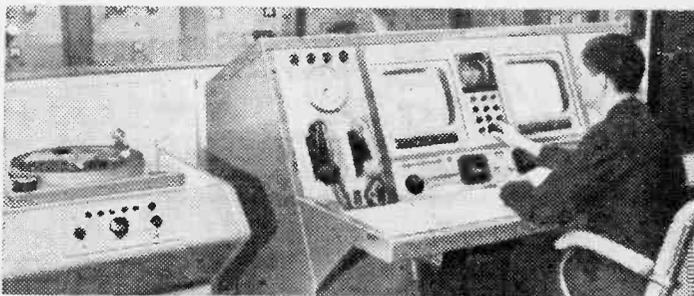

THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING. FARMING, GARDENING. ARCHITECTURE & WOODWORKING. SELLING & MANAGEMENT. ART. PHOTOGRAPHY, etc., etc.

PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . . .



INTERNATIONAL CORRESPONDENCE SCHOOLS
(DEPT. 170 N), INTERTEXT HOUSE, PARKGATE RD., LONDON, SW11

PLEASE SEND FREE BOOK ON

NAME

ADDRESS

.....

OCCUPATION AGE.....

3.60

WEYRAD

COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL

LONG AND MEDIUM WAVE AERIAL—RA2W

On 6in. rod, 7/16in. diameter, flying lead connections, 208 pF tuning 12/6

OSCILLATOR COIL—P50/1AC

Medium wave in screening can. For 176 pF tuning condenser 5/4

1st AND 2nd I.F. TRANSFORMERS—P50/2CC

470 Kc/s operation with 250 pF tuning in cans. 11/16in. diameter by 3/4in. high 5/7

3rd I.F. TRANSFORMER—P50/3CC

Last stage transformer to feed diode detector. Size as P50/2 6/-

DRIVER TRANSFORMER—LFDT2

Upright mounting with six connecting tags—1 1/16 in. x 7/8 in. x 1 1/4 in. 9/6


PRINTED CIRCUIT—PCAI

Size 2 1/4 in. x 8 1/4 in. Ready drilled and printed with component positions 9/6

THESE COMPONENTS ARE APPROVED BY TRANSISTOR MAKERS AND PERFORMANCE IS GUARANTEED.

Constructor's Booklet with full details, 2/-.

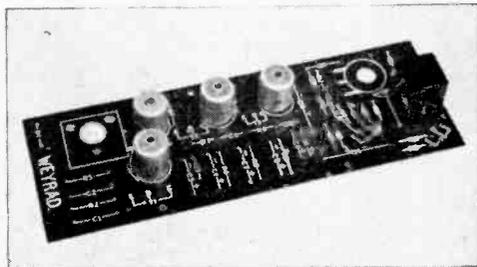WEYMOUTH RADIO MANUFACTURING CO., LTD.
CRESCENT STREET, WEYMOUTH, DORSET



The only Shop in London!

where you can buy

LEKTROKIT

This remarkable chassis construction system which is widely used by the Electronics Industry is now available to the Radio Amateur and can be purchased from :

super **RADIOTECH** *limited*

38 MONMOUTH ST., UPPER ST. MARTIN'S LANE, LONDON, W.C.2

We are proud to have been appointed the sole retail distributors in LONDON and invite you to visit our bright new premises where our Manager, Mr. Jack Cunningham, will be pleased to demonstrate the system. We can, of course, supply most of your component requirements at the keenest prices.

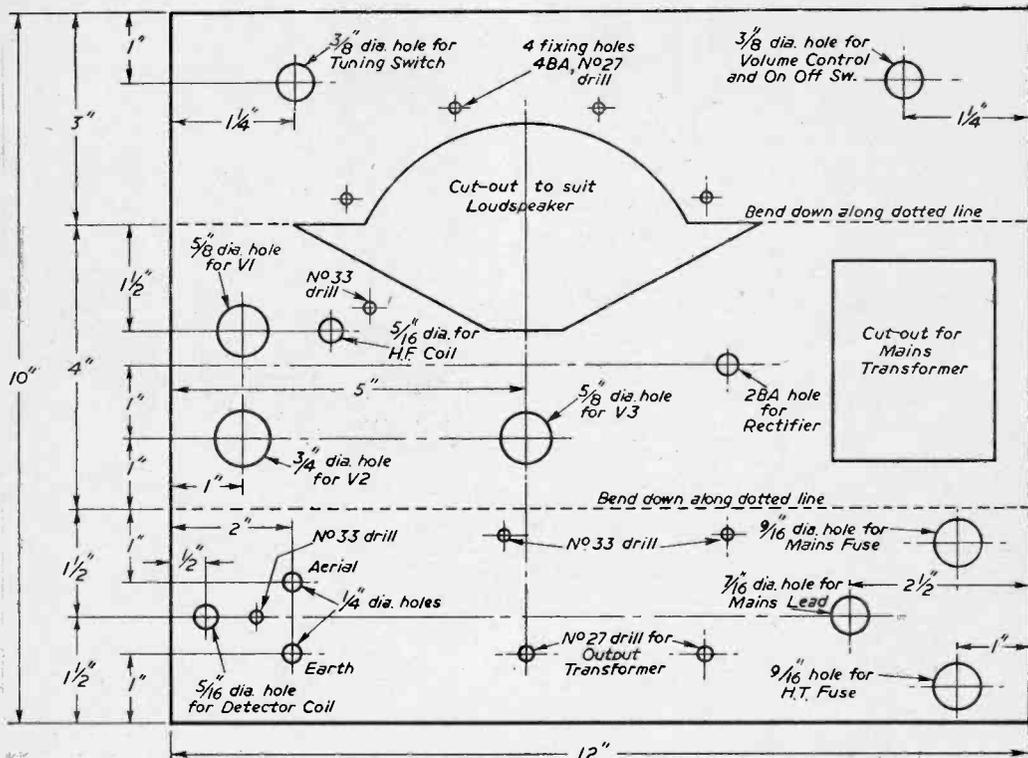


Fig. 3.—Chassis drilling details. (This diagram is not to scale.)

enabled the switch to be mounted underneath the valveholder wiring.

The Circuit

This is very simple. The first valve is connected as a tuned R.F. amplifier, feeding the first section of a 12AX7, which is connected as an infinite-impedance detector. The advantage of this type of detector is the very low loading which it imposes on the tuned circuit which feeds it. The result is that this tuned circuit tunes sharply, resulting in a great increase in selectivity.

The A.F. output is developed across the 47k detector cathode resistor. Residual R.F. is removed by the filter C3, R4, C4, and the D.C. component blocked by C5. Thereafter the signal passes to the second half of the 12AX7, which operates as a high gain A.F. amplifier, and to the output valve. This is an N78, rated to give 4W output into a 7k load, with 250V H.T.

The power supply circuit is also very simple, consisting of a half-wave metal rectifier, resistance-capacity smoothing, and mains transformer. Two

47Ω resistors are fitted in series with the rectifier; these can be of the 1/2W carbon type, and their function is to protect the rectifier from the initial surge which occurs when the electrolytic condensers charge up as the set is switched on. The main smoothing resistor is R11, and it is recom-

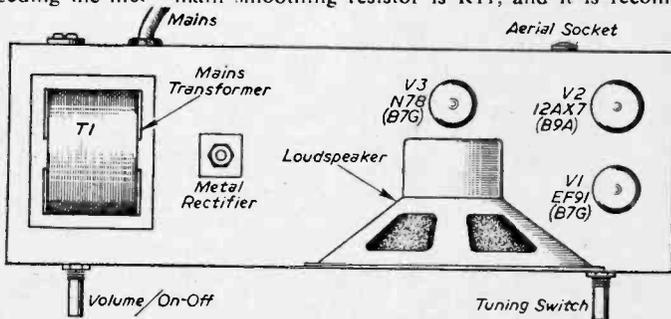


Fig. 4.—Above-chassis layout.

mended that this be a vitreous wirewound type, as it becomes quite hot.

Performance

As can be expected, this receiver is not particularly sensitive, being a T.R.F. without reaction. However, it does give very good reproduction of the stronger signals put out by the BBC in the

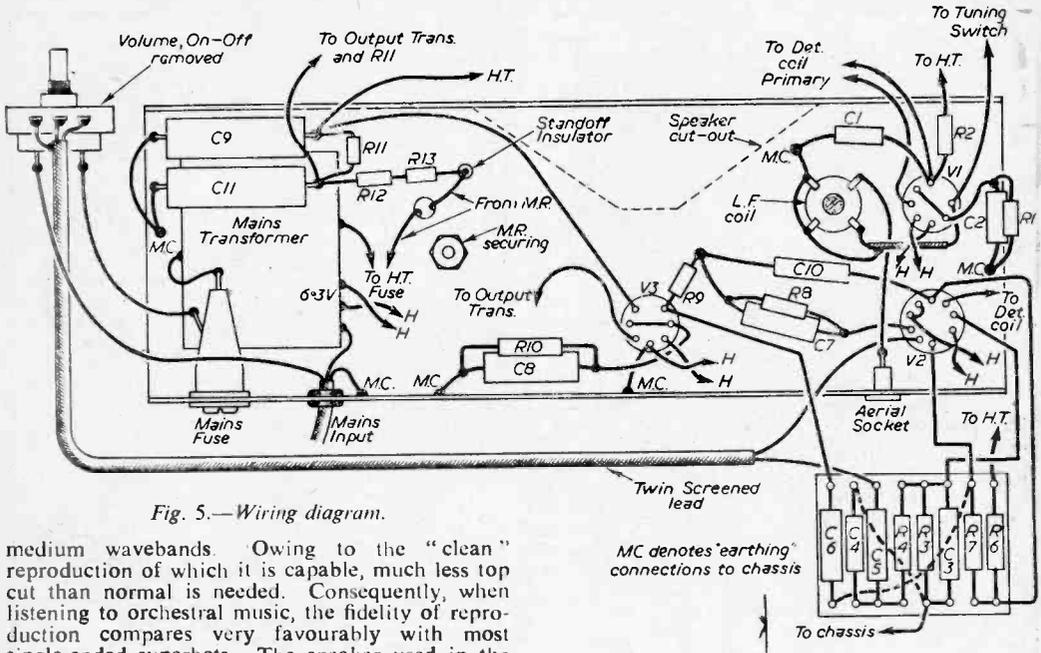


Fig. 5.—Wiring diagram.

medium wavebands. Owing to the "clean" reproduction of which it is capable, much less top cut than normal is needed. Consequently, when listening to orchestral music, the fidelity of reproduction compares very favourably with most single-ended superhets. The speaker used in the prototype was an 8in. wafer type, measuring less than 2in. back to front, and it was mounted on the chassis.

The results quoted were with 3ft. of 18s.w.g. copper wire used as an aerial and the chassis connected to mains earth (a very desirable feature

when the set is housed in a cupboard, not a cabinet!). With a picture-rail aerial, some 15ft. long, volume is much increased, but selectivity becomes a problem, the longer aerial damping the first tuned circuit.

A QUALITY F.M. RECEIVER

(Continued from page 932)

ping screws passing through the bottom into the chassis flanges.

Although the values of the various components used in this receiver can be determined from the

text and the circuit diagrams, some readers may find it easier to buy components from the list which is given below. When ordering, it may be found that some components are temporarily out of stock and if this is so the advice of the dealer should be taken concerning suitable equivalents.

COMPONENTS LIST

Resistors : (All $\frac{1}{2}$ W unless otherwise stated.)	C3—1,000pF ceramic.	C29—0.01 μ F 300VW
R1—18k.	C4—1,000pF ceramic.	C30—0.01 μ F 300VW
R2—4.7k $\frac{1}{2}$ W	C5—1,000pF ceramic.	C31—16 μ F electrolytic 350VW
R3—6.8k $\frac{1}{2}$ W	C6—47pF ceramic.	C32—16 μ F electrolytic 350VW
R4—150 Ω .	C7—47pF ceramic.	C33—See text (p. 848 February issue).
R5—100k.	C8—33pF ceramic.	Sundries :
R6—47k $\frac{1}{2}$ W	C9, C10—25+25pF ganged.	IFT1, IFT2, 10.7Mc/s I.F. trans-
R7—4.7k $\frac{1}{2}$ W	C11—1,000pF ceramic.	formers.
R8—4.7k $\frac{1}{2}$ W	C12—10,000pF ceramic.	RDT ratio detector transformer.
R9—47k.	C13—10,000pF ceramic.	L1—See text and Fig. 3b.
R10—150 Ω .	C14—10,000pF ceramic.	L2—See text and Fig. 3a.
R11—47 Ω .	C15—47pF ceramic.	L3—See text and Fig. 3a.
R12—47k $\frac{1}{2}$ W	C16—10,000pF ceramic.	L4—L.F. choke 10H 60mA.
R13—47 Ω .	C17—Not used.	T1—Output transformer Wharf-
R14—6.8k.	C18—300pF mica or ceramic.	dale GP8.
R15—6.8k.	C19—300pF mica or ceramic.	T2—Mains transformer 250-0-250V
R16—1M.	C20—300pF mica or ceramic.	60mA 6.3V 4A.
R17—27k.	C21—50 μ F electrolytic 25VW	Valves :
R18—1M.	C22—50 μ F electrolytic 25VW	V1, V2, V3, V4—EF91.
VR1—2.2k pot. wire-wound.	C23—2,000pF ceramic.	V5—ECC81 or ECC83.
VR2—1M log.	C24—0.01 μ F paper 200VW	V6, V7—EL91.
Capacitors :	C25—8 μ F electrolytic 350VW	V8—6X5.
C1—1,000pF ceramic.	C26—50 μ F electrolytic 25VW	V9—EM34.
C2—1,000pF ceramic.	C27—0.01 μ F 300VW	
	C28—8 μ F electrolytic 350VW	

HOME RADIO OF MITCHAM


(Dept. P), 187 LONDON ROAD, MITCHAM, SURREY. MIT 3282

Shop Hours : 9 a.m.—6.30 p.m. Wednesday 9 a.m.—1 p.m.

DON'T MISS THIS BARGAIN OFFER

Of special interest to all constructors—12 new assorted volume-controls (some with switch) for **ONLY 6/-**. Send NOW while they last. Post Paid.

NEW ARMSTRONG CHASSIS AF208

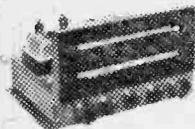

Medium wave plus full FM/VHF. 7 valves and 5 watts output. Separate treble boost and bass boost controls. There is no similar chassis on the market today to

equal the AF208. Full instructions, circuit, etc., supplied with each set. PRICE 22 gns., carriage 2/6. S.A.E. for leaflet.


"GLOBE KING" SHORTWAVE KITS



Reception from every country in the world on this wonderful little one-valve short-wave set. Easy to assemble and amazing results. High grade quality components. Start


this instructive and fascinating hobby today and explore the world on short waves. Kit of parts including three matched coils £3.19.6. post 1/-. S.A.E. for leaflet.

NEW GOODMAN'S LOUDSPEAKERS

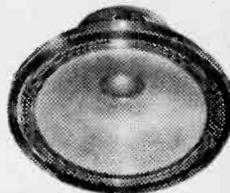

Model AXIOM 110, £50.0.
Model AXIOM 112, £8.10.0.
Send S.A.E. for leaflet.

JASON FM/VHF TUNER

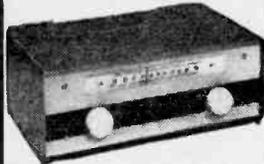

Enjoy crystal clear Hi-Fi radio reception with an F.M. tuner and the best one is without doubt the JASON FMT2. Full constructional data with detailed price list 2/9, post paid. Easy to assemble with punched chassis and pre-aligned coils. Set of parts costs £8 (power pack parts. 28/- extra).

HAVE YOU HAD OUR CATALOGUE?

This is essential to all home constructors, engineers, etc. 128 pages listing over 4,000 items and lavishly illustrated. This is EXCLUSIVE to Home Radio and cannot be bought elsewhere. PRICE 2/-, plus 9d. post.

"DESIGNS FOR AUDIO AMPLIFIERS"


This latest Mullard book from stock, price 8/6, post 1/-. We also carry all parts in stock for these designs including punched chassis, ganged controls, switches, etc.

"INSTANT" TAPE ERASER


Enables a complete reel of tape to be erased in a few seconds. Eliminates background noise and leaves tape as new. Will also deflux heads. S.A.E. for leaflet. PRICE £1.7.6, post 1/-.

AG2009 PHILIPS RECORD PLAYER UNIT

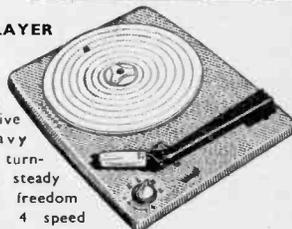Transcription quality at a very competitive price. Heavy machined turntable ensures steady running and freedom from wow. 4 speed with variation. Hi-Fi crystal pick-up. PRICE £10.10.0, plus 2/- post. Stereo plug-in head. 30/- extra.




LINEAR L3/3 STEREO

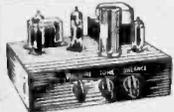

Full two channel STEREO amplifier. 3 watts each channel. Response 50 to 15,000 cycles. Matched for 3 ohms. 200/250 volts A.C. Illustrated leaflet on request with S.A.E. PRICE 7 gns., plus 2/6 post.

MULLARD '3-3' and '510' AMPLIFIERS

The famous MULLARD '3-3' and '510' amplifiers are still the most popular home constructor Hi-Fi designs available. We can offer both these superb equipments in kit form with printed circuit ensuring guaranteed results every time. Easily adapted for stereo. Price list of parts free on receipt of S.A.E. Constructional data and drawings 1/6 for each amplifier. Call and inspect and hear these two excellent amplifiers.

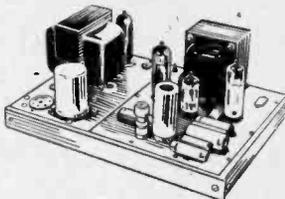

HI-FI EQUIPMENT

We have a range of sensible Hi-Fi equipment on demonstration in our showroom. Both ready built systems and in kit form. Amplifiers, tuners, gram units, speakers, etc. Send s.a.e. for our list of Hi-Fi systems.

"PERSONAL TWO" PORTABLE



2 valve dry battery personal portable. With rod aerial and ideal for bedroom, holidays, etc. Smart metal case and easy to build from data sheets price 2/-, post paid. Parts for set cost 41/-. Price list on request with s.a.e.

SPECIAL OFFER: TEST METERS

A limited number of superb moving coil test meters at well below cost price. Specially designed for testing all types of battery equipment. Ranges 6 volts D.C., 150 volts D.C., 30 mA D.C. and ohms. Basic movement 5 mA F.S.D. DEFINITELY CANNOT BE REPEATED ONCE STOCKS CLEARED. PRICE, 19/6, post 1/-.



Miniature high grade insulated resistors 10% tolerance in all preferred values from 10 ohms to 10 megohms. Type R5, 1/2 watt (1/2 watt max.), 4d. each. Type R6, 1 watt (1 watt max.), 6d. each. Type R7, 1 watt (2 watt max.), 9d. each.

LINEAR BATTERY CHARGERS




For A.C. mains and all fitted with ammeter. Strongly-made and guaranteed for 12 months. Send s.a.e. for illustrated leaflet. MODEL CL1, 6 volt at 1 Amp, 35/9. MODEL CL2, 6 or 12-volt at 1 1/2 Amps, 49/11. MODEL CL3, 6- or 12-volt at 3 Amps, 75/-. MODEL CL5, 6- or 12-volt at 5 Amps, 99/6. Add 2/- packing and postage.

SOLDERING IRONS



E541. Tyana medium instrument iron, 16/9. E522. Rempoly instrument iron (illus.), £1.2.6. E530. Solon 25-watt instrument iron, £1.4.0. E57. Adcola 25-watt instrument iron, £1.13.6. E516. Litesold for very fine work. 10 watts, £1.1.6. Please state voltage and add 9d. post.

S.W. TUNING CONDENSERS

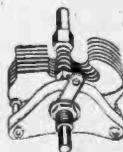

Wavemaster High Grade tuning condensers with brass vanes and ceramic insulation. Single hole fixing and individually boxed. 15pf, 4/3, 25pf, 4/6, 40 pf, 4/9, 50 pf, 5/-, 60pf, 5/3, 75pf, 5/6, 100pf, 5/9, 160pf, 6/-, 200 pf, 7/6. Add 9d. packing and post.

TAPE DECKS

We now have reasonable stocks of all the popular tape decks, including B.S.R. Monardeck, Collaro Studio deck, Collaro Mk. IV transistor, Truvox Mk. IV, Brenell Mk. V, etc., etc.

RECORDING TAPES

STANDARD. 5in., 15/6, 5 1/2in., 19/6, 7in., 25/-. LONG PLAY, 3in., 6/6, 5in., 19/6, 5 1/2in., 25/-. 7in., 32/6. All brand new and guaranteed. Send for list. Add 1/- postage to order.

SHORT WAVE RECEIVERS

WE ARE MAIN STOCKISTS FOR EDDYSTONE COMMUNICATIONS RECEIVERS AND SHORT WAVE COMPONENTS. SHIPPING ARRANGED TO ANY PART OF THE WORLD.

Visit the City's popular acoustically designed

HI-FI Centre

Electronics (FLEET ST.) Ltd

Dept. B.

152/3 Fleet St., London, E.C.4. Tel. FLE 2833
Business Hours: Weekdays, 9-6. Saturdays, 9-1.

STOCKS FOR THE FOLLOWING

AMPLIFIERS BY	V.H.F. TUNERS BY	HI-FI SPEAKERS BY
VERDIK	ARMSTRONG	GOODMANS
ARMSTRONG	LEAK	PLESSEY
ROGERS	QUAD	WHARFDALE
DULCI	T.S.L.	W.B.
GOODSELL	DULCI	T.S.L.
QUAD	GOODSELL	G.E.C.
LEAK	ROGERS, etc.	LORENZ, etc.
W.B., etc.		

TWO SNIPS FOR THE CONSTRUCTOR

The famous R.C.A. equipment in limited numbers

- (1) Completely assembled with attractive control panel. Just connect units together.
R.C.A. 10-watt p/pull amplifier, less than 1% distortion. Valve line-up 6BR7, 12AX7, 6BV6, 6BW6.
Frequency response 25-20,000 c.p.s., bass, treble and balanced loudness feature. Ideal for good quality reproducer.
AT THE VERY LOW PRICE OF £7.19.6. Post & Pkg. 4/6.
- (2) The Junior R.C.A. 5.8 watt push/pull amplifier.
Valve line-up 12AX7, 19AQ5, 19AQ5, 35W4.
Frequency response 40-20,000 c.p.s. Completely assembled with attractive control panel. Just connect amplifier to power supply. ONLY £6.19.6. Post & Pkg. 4/6.

SPECIAL OFFER IN TRANSISTORS

Audio PNP transistors type, 5/- each.

Sensitive diodes type GD3, 2/6 each.

Ediswan x B104, 9/6.

" x B103, 12/6.

" x A104, 17/6.

General-purpose diodes, 10d. each.

Single earphones, 4/6 each, 1/- P. & P.

Crystal earpieces with lead and ear plugs. Our price, 12/6, 1/- P. & P.

BUILD THIS YOURSELF

The Transette Medium Wave, 2 transistor, pocket portable. Neatly designed, using 2 transistors and diode. Simple to assemble. Enlarged working diagram. All components colour coded. Ferrite wound aerial. Will play indoors and outside with self-contained aerial. All components and diagram, complete, 62/6. Post & Pkg. 1/6.
Plug-in ear piece, 12/6.
Single 'phone, 4/6.
Battery, 2/-.
All components available separately. Stamped, addressed envelope for details.

PERSONAL PORTABLE

A wonderful little set that you can take anywhere. Ideal for camping, picnics, etc. Telescopic aerial rod supplied. Covers Medium Waveband 200-500 metres. Can be built in approx. 1 hour. All necessary components available at the following SPECIAL INCLUSIVE PRICES: 1-valve version ONLY 35/-, 2-valve version ONLY 41/-. Plus 2/- P. & P. Send for point-to-point wiring diagram and parts price list 2/-, post free.

SNIPS IN TAPES AND ACCESSORIES

Brand new and guaranteed.

7in. reels of 1,200ft.	P.V.C. base tape	21/- plus	1/6 post and pkg.
5in. " " 600ft.	" " "	14/6	" " " "
4in. " " 300ft.	" " "	9/6	" " " "
7in. " " 1,800ft. LP	" " "	32/6	1/6 " " " "
5 1/2 in. " " 1,200ft.	" " "	25/-	" " " "

New E.M.I. t/up spools in polythene bag, 3/6 each, post free. 6 for 20/-.

FEW ONLY. The famous R.C.A. 4-speed auto-changer attractively finished in maroon and gold. Manual and auto switch, A.C. 200/250 v. ONLY £7.19.6. Post & Pkg. 4/6.

Build your own TAPE RECORDER "ASPDEN"

Tape Deck and Amplifier Kits



TAPE DECKS. 2-speed, twin track, easy to assemble kits with finest motor. Ferroxcube heads and full instructions.

Reduced Prices:—

Model 582 for 5in. spools, kit £7.10.0.

Model 782 for 7in. spools, kit £8.10.0.

Either model assembled and tested, 30/- extra.

AMPLIFIER kit. 21 watt. record/replay. 2 recording positions, neon indicator, etc. £5.18.0. Power Pack kit for above, £2.18.6 (both without valves). Carr. and packing extra.

Mr. R. White of Omagh, N. Ireland, writes:

"The performance of the recorder is very good, and I recommend it to all those who wish to get first class performance at approx. half the cost."

Send **STAMP** for full particulars to:—

W. S. ASPDEN Stanley Works, Clevedon Road,
Blackpool, Lancs.

Build your own HI-FI!

At last! A specially selected and designed HI-FI Sound installation for your home at really reasonable cost!



You save because you assemble everything yourself following our step by step instructions. You gain because you learn about the equipment as you build and are able to service and maintain it afterwards. Best of all—you'll have fun building it and be thrilled with the finished instrument which will bring you an entirely new experience in the enjoyment of sound. No previous skill or experience is needed. Post coupon now for full details, without any obligation. Easy terms available.

Equipment Includes: Luxury Cabinets · Top Quality Amplifier suitable for stereo or non-stereo reproduction · VHF/FM Radio Units · Record Player · Tape Recorder · Hi-FI Speaker system.

FREE BROCHURE — POST TODAY

Radiostructor: (Dept. H34), 46 Market Place, Reading, Berks.

Please send Brochure without obligation to:

Name _____ **BLOCK**
Address _____ **CAPS**
_____ **PLEASE**

3.60

309

We do not employ representatives

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

Club News

ALDERSHOT & DISTRICT AMATEUR RADIO SOCIETY
 Signals Wing, No. 4 Training Regiment, Royal Engineers,
 Gibraltar Barracks.
 Hon. Sec.: A. M. Laidler.

MEETINGS are held every Wednesday at the above address at 7.30 p.m. with the exception of the second Wednesday in each month when the meeting is held at "The Cannon," Victoria Road, Aldershot.

A technical course of training to R.A.E. standards was started in January in readiness for the May examination. It is also hoped to run Morse training periods for those persons requiring this type of training.

The society requires instructors and lecturers to give instruction to R.A.E. standards and licensed amateurs who are willing to devote a little time to instruct new members. All correspondence should be addressed to the hon. sec. at "Pondside," Sandy Lane, Churt, nr. Farnham, Surrey.

BRIGHTON AND DISTRICT RADIO CLUB
 Home Guard Club, British Legion, 76, Marine Parade, Brighton.
 Hon. Sec.: H. R. Henly (G3HR).

ON January 6th Mr. D. Hemsley gave a talk on "A Home-built Oscilloscope for TV Servicing," and on January 20th a filmshow was held at the H.Q.

Future events:
 February 10th.—Informal evening.
 February 17th.—Filmshow.
 February 24th.—"A Home-built Tape Recorder," by Mr. D. Hemsley.

March 2nd.—Informal evening.
 March 9th.—"The Design of Communication Receivers," by H. R. Henly.

March 16th.—Filmshow.
 March 23rd.—Informal evening.
 March 30th.—Demonstration of the Gelo G209R Receiver, by R. Smith.

BRITISH INSTITUTION OF RADIO ENGINEERS
 9, Bedford Square, London, W.C.1.

MEETINGS for February, 1960
LONDON Section.—Meetings are held at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1.

Tuesday, February 9th.—At 6.30. Computer group. "Drift Correction of D.C. Amplifiers," D. Leighton Davies.

Wednesday, February 24th.—At 6.30 p.m. Medical electronics group. "The Unification of Electronic Clinical Instruments," Dr. F. D. Stott.

Bristol, South-western Section.—Meetings are held at the School of Management Studies, Unity Street.

Wednesday, February 24th.—At 7 p.m. "Industrial Magnetic Recording and Playing Machine Design," J. Elliot.

Cardiff, South Wales Section.—Meetings are held at the Welsh College of Advanced Technology.

Wednesday, February 10th.—At 6.30 p.m. "Low Noise Low Drift D.C. Amplifiers," V. L. Devonald, B.Sc.

Newcastle-upon-Tyne, North-eastern Section.—Meetings are held at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Rd.

Wednesday, February 10th.—At 6 p.m. "Instrumentation in Rocket Propulsion," Raymond E. Ross (Associate Member).

Wolverhampton, West Midlands Section.—Meetings are held at the College of Technology, Wulfruna Street.

Wednesday, February 10th.—At 7.15 p.m. "Electronic Reading," I. W. Merry.

BRITISH SOUND RECORDING ASSOCIATION

LONDON Meetings.—Meetings are held at the Royal Society of Arts, John Adam Street, Adelphi, London, W.C.2.

Future events:
 February 19th.—At 7.15 p.m. "The Sounds of Music," W. H. George. M.Sc., Ph.D., F.Inst.P.

March 18th.—At 7.15 p.m. Talk by R. S. Roberts, M.Brit.I.R.E. Sen.M.I.R.E.

April 22nd.—At 7.15 p.m. "Sound Radiation from Loud-speaker Cabinets," James Moir. M.I.E.E.

May 21st.—Amateur competition display—annual general meeting to be held in the evening at the Overseas League, St James's, S.W.1.

South-western Centre.
 Centre Organizer: D. W. Aldous, "Alderbourne," Greenways Road, St. Marychurch, Torquay, Devon. Meetings are held at Callards Cafe at 7.45 p.m.

REPORTS OF CURRENT ACTIVITIES

March 3rd.—"High Fidelity Sound Reproduction," N. Mordaunt (Tannoy).

CALCOT RADIO SOCIETY
 Hon. Sec.: C. Aldous, 3, Oliver Drive, Calcot, Reading, Berkshire.

Future events:
FEBRUARY 18th.—Lecture and demonstration of Hi-Fi equipment by a representative of E.M.I. Sales.

March 17th.—Lecture on the suppression of electrical interference in TV and radio sets, by Mr. Richardson of the G.P.O.

April 21st.—A lecture and demonstrations by a representative of Truvox.

May 19th.—Lecture and demonstration on the Design of Hearing Aid Equipment, by Mr. Williams, of Belclere Ltd.

CHILTERN AMATEUR RADIO CLUB
 Hon. Sec.: R. Barton, 25, Hillside Road, Marlow, Bucks.

MEETINGS are held at the British Legion Club, St. Mary's Street, High Wycombe, on the last Thursday of each month.

Future events:
 February: "Some Aspects of Aerial Design"—G3LSK.
 March: Mullard Film Show—G3INZ.
 April: Junk sale and Quiz.
 May: Mobile gear for the Amateur Band.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY
 Hon. Sec.: F. C. Ward (G2CVV), 5, Uplands Avenue, Littleover, Derby.

MEETINGS are held in Room No. 4, 119, Green Lane, Derby.

Future events:
 February 7th, at 7.30 p.m.: Proposed date for contest for G5Y.
 March 18th, at 7.30 p.m.: Proposed date for annual dinner and dance.

August 14th, at 7.30 p.m.: Third annual mobile rally.

HALIFAX AND DISTRICT AMATEUR RADIO SOCIETY
 Hon. Sec.: A. Robinson (G3MDW), Candy Cabin, Ogden, Halifax.

ON December 8th members heard a lecture dealing with radio astronomy by Mr. Doiity, of Halifax, and on February 2nd H. Makin (G3FDC) gave a lecture on the S.W.R. Bridge.

Future events:
 February 16th: Informal meeting.
 March 1st: Film show.

NOTTINGHAM CO-OPERATIVE AMATEUR TAPE RECORDING SOCIETY

OWING to accommodation difficulties the meeting night has been altered to Thursday. A fairly detailed programme has been planned for the first few months of 1960 and, as several members have expressed the desire to know more about tape recorders, a series of informal discussions have been arranged to be given by experienced members. Alternate subjects deal with technical aspects and this means that the club will have meetings every other Thursday on February 18th, March 3rd, 17th, 31st, April 14th and 28th, etc.

THE RADAR AND ELECTRONICS ASSOCIATION
 Hon. Sec.: C. W. Knight, 83, Portland Place, London, W.1.

MEETINGS are held at the Royal Society of Arts, John Adam Street, Adelphi, London, W.C.2, at 7.30 p.m.

Future events:
 February 9th: "Transistors—Today and Tomorrow," by E. Wolfendale, B.Sc.(Eng.), A.M.I.E.E.
 March 28th: "Computers—Some Design Problems of Large-scale Computers," by Peter D. Hall, of Ferranti Ltd.

THE READING AMATEUR RADIO CLUB
 Hon. Sec.: R. J. Nash (G3EJA), "Peacehaven," 9, Holybrook Road, Reading.

ON January 30th a meeting was held on morse instruction, following the discussion on field day activity for the new year. A junk sale was held afterwards.

Future events:
 February 27th: Film on the manufacture and application of transistors.

March 26th: Talk on the application of transistors to ham gear, in particular receivers and transmitters.
Meetings are held at Palmer Hall, West Street, Reading, at 7.30 p.m.

REIGATE AMATEUR TRANSMITTING SOCIETY

Hon. Sec.: F. D. Thom (G3NKT), 12, Willow Road, Redhill, Surrey.

MEETINGS are held at The Tower, High Street, Redhill, usually on the third Saturday in the month at 7.30 p.m.
The club visited the BBC station at Tatsfield on January 9th and the first annual general meeting was held on January 16th.

Future events:
February 7th: Annual dinner to be held at Laker's Hotel, Redhill. Tickets 15s, each.
February 20th: "The Story of Paul Bates (G3MAC)," by G2DVD, assisted by G3HCU.
March 19th: "TVI" by G4ZU.

THE SLADE RADIO SOCIETY

Hon. Sec.: C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

MEETINGS are held at the Church House, High Street, Erdington, at 7.45 p.m. The club station (G3JBN) at the Church House is available for the use of members for constructional purposes.

Future events:
February 12th: Sale of surplus equipment.
February 26th: "Electronics in the Search for Oil," by G. T. Peck, M.B.E.
March 4th: Mullard film meeting, to be held at the Bennett Hall, Y.M.C.A., Snow Hill, at 7.45 p.m.
March 11th: Modern broadcast reception.
March 25th: "Electronic Digital Computers," by M. D. Fowler (G3GKZ).

THE TEESIDE AMATEUR RADIO CLUB

Hon. Sec.: A. L. Taylor (G3JMO), 12, Endsleigh Drive, Acklam, Middlesbrough.

MEETINGS are held at Settlement House, 132, Newport Road, Middlesbrough, every alternate Friday from February 5th until the Easter break.

WELLINGBOROUGH AND DISTRICT RADIO AND TELEVISION SOCIETY

Hon. Sec.: D. J. Trusler, 87, Irchester Road, Rushden, Northants, Club room above W.I.C.S. fruit shop in Silver Street.

MEETINGS are held in the club room every Thursday at 7.45 p.m.
Future events:
February 18th: Film night in the club room.
March 3rd: Talk on "Electronics and Radiation," by R. Mitchell, B.Sc.

Third Conference on Medical Electronics

To be held at Olympia, London, 21st-27th July, 1960

THE human body is made up of a number of inter-related systems—brains and nerves, heart and blood vessels, stomach and intestines, lungs and windpipe—and different electronic techniques can be used for their measurement and control.

In the respiratory system, one of the things the physician may need to know is the velocity with which air flows through the windpipe, and the volume of air respired at each breath. This may be measured by a device called a pneumotachometer. In this, the airstream passes through a piece of metal gauze. This causes a change in pressure which is related to the rate of flow. The change in pressure is minute, but it can be measured by an electronic-pressure gauge. The electric signal obtained is passed through a "black box" which instantaneously computes the volume of air breathed in a given time, and records it as a line on moving paper.

The physician may need to know the amount of carbon dioxide which is being excreted as a waste product into the expired air. This information can be obtained by chemical analysis, but a single determination would take a skilled technician half an hour or more. The modern method uses infra-red rays which are passed through a sample of the breath. The carbon dioxide present abstracts some of the energy from the rays. The lost energy can be measured, and because of the terrific speed of electronic techniques the breath can be analysed in this way in a few hundredths of a second. Thus not only can the amount of carbon dioxide be measured, but also the concentration in each fraction of the expired air, and this can be very helpful in the diagnosis of respiratory disease.

In poliomyelitis, the breathing muscles may be partly paralysed, and the patient's respiration may then have to be assisted by a machine. Electronic

devices can now measure the patient's disability, and control the degree of assistance provided by the machine. In this way the volume of breathing is automatically adjusted to suit the need of the individual patient.

During anaesthesia, drugs may be used which produce a temporary paralysis of the breathing muscles, and here again an electronically controlled machine may take over the patient's breathing and keep its volume at the right level.

Servo systems are common in electronics, and a "servo-anaesthetiser" has been devised at the Mayo Clinic. This is worked by the activity of the patient's brain. This activity is measured electronically. An increase in this measurement indicates that anaesthesia is becoming lighter. This increase sets off a relay which raises the rate at which the anaesthetic is being delivered. Conversely, deepening anaesthesia results in a decrease in the rate of delivery. In this way the depth of anaesthesia is automatically held at any desired level.

These are but a few examples of the impact of electronics on two aspects of medicine. New uses are continually being found, and so rapid is the progress, in a dozen different countries, that international conferences to exchange ideas and to tell of new techniques are needed every year.

The next such conference is being organised by the Electronics and Communications Section of The Institution of Electrical Engineers in London next July. Doctors, biologists and electronic engineers from all over the world are being invited to attend. The proceedings are designed to appeal not only to the medical and electronic experts but also to those who are not themselves specialists, but who wish to get a general background to the many new techniques. It is expected that from this meeting of British and foreign talent, new methods of measurement and control, of diagnosis and treatment, will emerge to heal the sick.

Great Money-Making Opportunity!

DO NOT MISS IT — STOCKS ARE RUNNING LOW
NEWNES

Radio and TV Servicing

Complete in 1 Volume
300 MODELS (1958-1959)

Covering many of the newer models now in use all over the country, this volume fills an urgent need for technical data. It contains the circuits, component and chassis layout diagrams for 300 popular Models—672 pages of invaluable data.

TELEVISION SERVICING DATA FOR—

Alba, Argosy, Beethoven, Bush, Cossor, Cydon, Decca, Defiant, Ekco, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B., McMichael, Marconiphone, Masteradio, Murphy, Pageant, Pam, Peto Scott, Philco, Pilot, Portadyne, Pye, Raymond, Regentone, R.G.D., Sobell, Spencer-West, Stella, Ultra.

**300
MODELS**

**672
PAGES OF
WANTED
DATA**

RADIO, RECORD & TAPE SERVICING DATA FOR—

Alba, Berc, Bush, Champion, Collaro, Cossor, Decca, E.A.R., Eddy-stone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B., McMichael, Marconiphone, Masteradio, Murphy, Pam, Perdio, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Regentone, R.G.D., Roberts' Radio, Sobell, Stella, Vidor, Walter.

RECENT DEVELOPMENTS SECTION

Includes: Picture Tube Repair, Car Radio Interference Suppression, Valve and Picture Tube Data.

HEATER RATINGS, BASE CONNECTIONS, EQUIVALENTS

Full set in 7 Volumes
2,300 MODELS (Pre 1953-1959)

(Including the 300 models and data in the volume on left) Here you have Newnes Complete Servicing Library—early popular models to 1959. It's packed with invaluable data and will pay for itself over and over again.

TELEVISION SERVICING DATA FOR—

Ace, Alba, Ambassador, Argosy, Baird, Banner, Beethoven, Brayhead, Bush, Champion, Cossor, Cydon, Decca, Defiant, Ekco, E.M.I., English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Pageant, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Rainbow, Raymond, Regentone, R.G.D., Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, White-Ibbotson.

RADIO, RECORD & TAPE SERVICING DATA FOR—

Ace, Alba, Ambassador, Argosy, Armstrong, Banner, Beethoven, Berc, Bush, Champion, Collaro, Cossor, Decca, Defiant, E.A.R., Eddy-stone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radio mobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Stella, Strad, Ultra, Vidor, Walter, Webcor.

Also—Large Fold-out Charts on TV Troubles.

**2,300
MODELS**
**4,150
PAGES**
**4,250
CIRCUITS
ETC.**
2 YEARS' Free Postal Advisory Service



EXAMINE EITHER —
Free for 7 days without obligation!

PLACE TICK AGAINST YOUR CHOICE

Radio and Television Servicing
(Pre-1953 to 1959 Models)
SEVEN VOLUMES
10/- Deposit. 15 monthly payments of 15/- . Paying £11.15s. in all. Cash price in 8 days £11.5s.

Radio and Television Servicing
(1958-1959 Models)
SINGLE VOLUME
12/6 Deposit. 4 monthly payments of 10/- . Paying 52/6 in all. Cash price in 8 days 50/-.

GEORGE NEWNES, LTD., 15-17 Long Acre, London, W.C.99

Send me the book or books I have selected, without obligation to purchase. I will either return the book or books in 8 days or send the deposit 8 days after delivery, then the monthly subscriptions as set out on left, until the total subscription price of the book or books I have selected has been paid.

Mr., Mrs., Miss.....

Address.....

Occupation.....

Your Signature.....
(Or Parent signs if you are under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

R65/RV96

AND NOW . . . RADIO CLEARANCE LTD. proudly presents the greatest ALL-TRANSISTOR CIRCUIT of our time

BUY AS YOU BUILD the "MIRACLE" Super Six Plus

ANY PART SOLD SEPARATELY

Makes up to a portable transistor superhet embodying all the latest design developments including a self-oscillating mixer, two double-tuned IF stages, audio amplifier and a matched push-pull output stage. Also two germanium diodes are incorporated, additional to the six Mazda transistors, one as detector and the other to assist the AGC as a variable damping element.

12 Good Reasons why the Miracle has no equal

- ★ Printed Board engraved with component locations
- ★ Special provision for use as a CAR RADIO
- ★ Double-tuned IF Transformers
- ★ 6 First Grade Mazda transistors plus 2 Mazda hi-gain diodes
- ★ Hi-flux 5in. (12000 lines) 25-ohm loudspeaker
- ★ Full coverage Medium and Long wavebands
- ★ 3½in. tuning dial with 5:1 slow motion
- ★ Long life dry battery. 150/200 hours
- ★ Internal high-Q Ferrite Aerial
- ★ Push-pull matched output stage 400-milli-watts
- ★ 3½in. x 7½in. x 10in. two-tone vyanide covered case—total weight approx. 4 lb.
- ★ Comprehensive Manual supplied—so easy to build

Our inclusive price for all components, cabinet and battery, complete in every detail:

£11.10.0

plus 3/6, Regd. p.p.

or any component part supplied separately at the published prices.

INSTRUCTION MANUAL AND CIRCUIT BOOK containing itemised list of all component prices, 3/6 post free. See and hear a complete working model at

RADIO CLEARANCE LTD., 27, TOTTENHAM COURT ROAD, LONDON, W.1.

Telephone Museum 9188

☆ 'PERTH' PLAYER CABINET WITH STEREO EXTENSION



5/9 Deposit

As shown at the "Radio Show." In two-tone colour. Extension speaker cabinet to match, which is secured in lid (arrow indicates position when fixed). Size 18in. x 14in. x 8½in. high. P. & P. 5/6.

CASH PRICE

79/6

Amplifier/Elliptical speaker can be obtained from us to make this a player to be envied by your friends. Complete player normally retails at 35 gns. 5/9 deposit. Balance at 4/11 for 15 weeks.

EXTENSION SPEAKER 19/6

In polished cabinet. Fitted with 8in. P.M. speaker, 2-5 ohms, switch and flex. P. & P. 3/6.



8in. P.M. SPEAKER, 5/9 Had a slight cone repair not affecting the quality. Tested and Guaranteed. P. & P. 2/9.

8in. P.M. SPEAKER, 8/9. For extension to kitchen, workshop, garage, etc. Work while you listen to your favourite programme.

With O.P. trans. 10/- Ideal for stereo. P. & P. 2/9.

BAKELITE CABINET



5/9 Brand new. Attractive design. Size 12in. x 7in. x 5½in. Colour brown. Ideal small receivers, etc. P. & P. 3/3.

ONLY 9/6

PLESSEY CHASSIS FOR SPARES

56 resistors: 7 variable. Controls. Condensers, including Electrolytics; Coils; 7 I.F. and R.F. Transformers; 14 Valve-holders. 9 B7G, 5 B5G, 3 Octal. 4 transformers. Mains: O.P. Line, frame, Chokes, Metal Rectifier; 300 v. 250 mA. Fuse panel. Scanning coil. Focus Magnet. Plug sockets. Switch. Chassis screws. Tag strips, etc. I.F. strip in separate Power pack can be used without dismantling. Chassis has been used, but were working when stored. 7 pages of circuits and instructions showing position of each component. Carr. 10/6.

TELEPHONE SETS, 7/9. Ex W.D. Wireless remote control unit. E. MK11. New condition, morse tapper, switched, jack plugs, etc. Less phone. P. & P. 3/6.

SCANNING COILS, 10/6. Low imp. 38 mm. Brand new. P. & P. 1/3.

FOCUS MAGNET, 9/9. Brand new 38 mm. Incorporating picture shift controls. P. & P. 1/3.

ELAC FOCUS MAGNET, 12/9. 35-38 mm. Brand New. P. & P. 1/9.

PLESSEY FOCUS MAGNET, 3/9. 35 mm. Permanent magnet type. Salvage. P. & P. 1/9.

COIL PACK SETS, 3/9. Bargain including 2 w/band coil pack, 2 gang cond. and pr. 465 I.F.'s. P. & P. 2/3. (Limited number of 4 w/bnds. State w/bnd. required.)

PRESS BUTTON COIL PACK, 5/9. 3 w/band F.M. and gram. P. & P. 1/6.

(Dept. 2), Stamp for FREE Catalogue.



COMPONENTS LTD.

219, Ilford Lane, Ilford, Essex. ILF 0295.

NEWS FROM THE TRADE

SOLDERING IRON STAND



A NEW soldering iron stand is announced by Antex Ltd., and is suitable for bench mounting as well as for wall mounting. A reel of solder can be accommodated on the back. The iron shown in the illustration is of the mains type, and fitted with one of the five interchangeable bits. Soldering transistors without risk of damage is now possible by using the latest bit of only 0.040in. in diameter (1mm).

It is necessary to touch the lead of a transistor for only a few seconds with this needle-type bit to solder or unsolder. The stand retails at 12s. 6d. *Antex Ltd., 7/8 Idol Lane, London, E.C.3.*

NEW TAPE RECORDER


A NEW tape recorder, Model 808, has been announced by Ferrograph. The purpose of the machine is to give both mono and stereo recording and reproduction on conventional tracks. There are complete recording amplifiers

The "Antex" soldering iron stand.

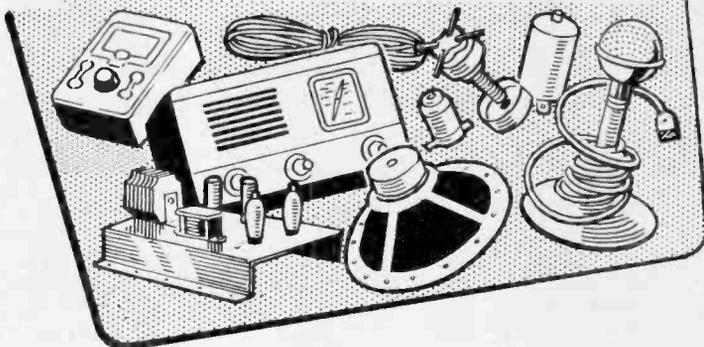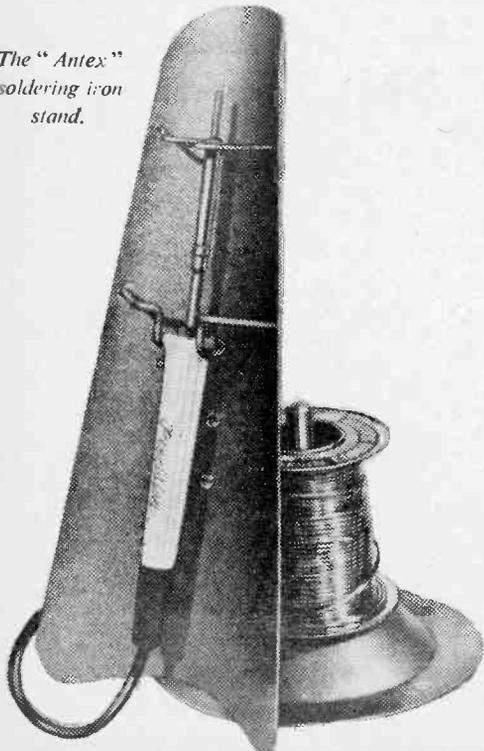

in both cases. Playback is at low level on all output channels: 1.5V across 5,000 ohms. The reason for this is twofold; in the first instance, it would not be possible to include two audio amplifiers in an already full portable case, and, secondly, the majority of serious users would be in possession of standard stereo amplifiers, and

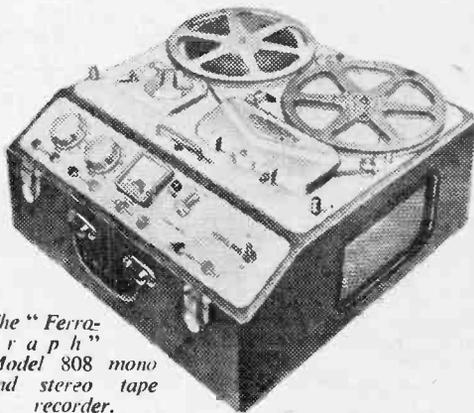The "Ferrograph" Model 808 mono and stereo tape recorder.




would have no need of further amplifiers of this type. In a two-tone, grey transportable cabinet, this model retails at 105 guineas. *British Ferrograph Recorder Co., Ltd., 131, Sloane Street, London, S.W.1.*

A.M./F.M. Signal Generator

A SIGNAL GENERATOR designed mainly for the servicing of A.M. and F.M. high frequency receivers and the intercarrier I.F. stages of television receivers was released in January by Taylor Instruments. This model (61A), provides in conjunction with an oscilloscope complete facilities for the sweep alignment of the R.F., I.F. and discriminator or ratio detector stages of A.M. and F.M. receivers. The A.M. generator covers the range 4-120Mc/s in five bands, all on fundamentals. The F.M. and sweep bands cover the frequencies 4-12Mc/s and 70-120Mc/s in three bands. Deviation on F.M. is variable up

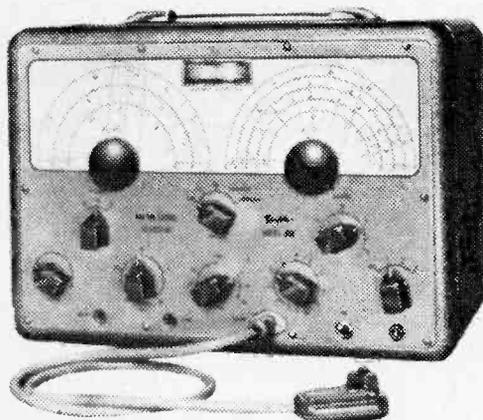to 100kc/s from the mean carrier frequency at a modulation rate of 400c/s. All the facilities offered in the 61A model may be selected by



The "Taylor" A.M./F.M. signal generator.

internal switching. Taylor Electrical Instruments Ltd., Montrose Avenue, Slough.

"THERMONIC OSCILLATORS"

THE second of the new series of filmstrips introduced recently by the Mullard Educational Service to assist the teaching of electronic engineering in technical colleges and similar establishments has now been completed. The first strip in the series, parts 1 and 2, dealt with the basic principles of oscillation and the various forms of sinusoidal oscillators. "Thermonic Oscillators—parts 3 and 4" resumes the story with an exposition of non-sinusoidal oscillators. It explains the generation of pulses, square-waves, and sawtooth waveforms for television and oscilloscope timebases, and describes in detail the various forms of relaxation oscillator, blocking oscillator and multivibrator. The filmstrip comprises 22 frames in colour and may be obtained from the distributors, Unicorn Head Visual Aids Ltd., 42, Westminster Palace Gardens, London, S.W.1. price 25s.


"RADIO AMATEURS' HANDBOOK"

THE 27th edition of the *Radio Amateurs' Handbook* is to be published in 1960 and will remain the same price as the previous edition, which is 32s. 6d. For further information readers should contact Arthur F. Bird, 66, Chandos Place, Strand, London, W.C.2.

TRANSISTORISED STABLE D.C. SUPPLY

A TRANSISTORISED dual stabilised D.C. unit which provides two 0-30V, 1A stabilised supplies from a single instrument has been produced by "Advance." Both sections of the supply are floating and may be operated separately, or connected in series to provide a maximum output of 60V A.C. at 1 A. Similarly, both positive and negative voltage supplies may be drawn simultaneously up to a maximum of 30V each. The range of 0 to 30V in each section

is covered in three 10V steps by means of a variable control directly calibrated in volts and the output is monitored by an ammeter and voltmeter which can be independently switched to either circuit as required. Four terminal output networks are incorporated which enables the effects of resistance of the connecting leads to the load to be virtually eliminated and overload protection is afforded by an electronic circuit which provides complete protection against both progressive overloads and short circuits. Protection against internal failure or excessive mains surges is provided by a panel-mounted fuse in the mains circuit. Advance Components Ltd., Roebuck Road, Hainault, Ilford, Essex.

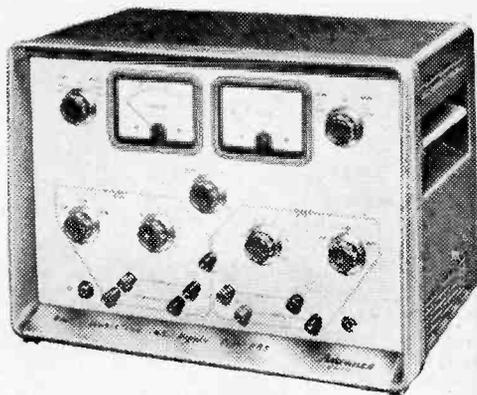

The "Advance" stabilised D.C. unit.

TV SET FOR DESIGN CENTRE

A C.W.S. Defiant television set has been chosen by the Council of Industrial Design for exhibition in the Design Centre. Slimline model V101, it is a 17in. table model with 12 valves and a wide angle 110deg. tube.

CAREERS IN RADIO AND TELEVISION SERVICING

CAREERS, for boys about to leave school, in the repair and maintenance of radio and television receivers, are described in *Radio and Television Servicing* (H.M. Stationery Office, No. 66, price 1s. 6d. net), a revised booklet in the "Choice of Careers" series published by the Central Youth Employment Executive.

A systematic approach is the basis of good servicing, and the booklet shows how the young trainee learns to identify the many different radio components, and to use hand tools and special test equipment, developing his knowledge of electrical theory at the same time.

The most common form of training in the industry is apprenticeship, and details are given of the national apprenticeship scheme drawn up by the trade and of the schemes operated by the Airways Corporations and the Service departments. Among the qualities needed for this occupation are dexterity, patience, perseverance and resourcefulness.

RETURN-OF-POST SERVICE

NEW ILLUSTRATED LISTS

New Illustrated lists are available on all the following. Any will be sent free upon request.

GRAMOPHONE EQUIPMENT. Details of many types of Auto Changers, Single Record Players and Transcription Units including all the latest models. Many at special prices.

TEST GEAR. Test meters, Signal Generators, etc., by AVO, Jason, Pullin and Taylor.

LOUDSPEAKERS. Full details of Goodmans, Whitely, Wharfedale and Elac types.

TAPE DECKS. All popular makes with a special offer.

RECORDING TAPES. A very wide range of all tapes and accessories.

RECORDING TAPE

DOUBLE PLAY

BASF. 300ft. (3in.) 14/-; 600ft. (4in.) 25/-; 1,200ft. (5in.) 42/-; 1,600ft. (5 1/2in.) 52 6/-; 2,400ft. (7in.) 77 6/-.
SCOTCH BOY 200. 400ft. (3 1/2in.) 17/-; 1,200ft. (5in.) 45/-; 2,400ft. (7in.) 80/-.
TELEFUNKEN. 1,200ft. (5in.) In plastic container. 40/-; 1,800ft. (5 1/2in.) in plastic container. 50/-; 2,400ft. (7in.) 75/-.
SPECIAL OFFER. 1,200ft. Standard Tape. Brand new. Famous maker. Fully guaranteed. 25/- Four for 85/- Full range of standard and L.P. tape and accessories also stocked. Send for list. All tape post free.

MULLARD LUMENAR CATHODE RAY TUBES

● ATTRACTIVE PRICE. ● 12 MONTHS' GUARANTEE. ● AVAILABLE ON HIRE PURCHASE
 12in. MW31/74. 14in. MW36/24. MW36/44. AW36/20. AW36/80. All £8.19.6. Hire Purchase Deposit £1.15.6 and 12 monthly payments of 13 9/-.
 17in. MW43/69. MW49/80. AW43/80. All £10.7.6. Hire Purchase Deposit £2.1.6 and 12 monthly payments of 15 6/-.
 ALL OTHER TUBES can be supplied at list prices. Many recently reduced. Send for free list or ask for quotation. H.P. available. ALL SENT CARRIAGE AND INSURANCE FREE.

GRAMOPHONE EQUIPMENT

ALL LATEST MODELS	Cash Price	Hire Purchase	RECORD CHANGERS
		Deposit	Mthly. Pmts.
COLLARO Conquest (Studio O PU)	£7.19. 6	£1.12. 0	6 of £1. 4.7
GARRARD RC121 (GC8 PU)	£9.19. 6	£1.19. 6	12 of 15/-
GARRARD RC88 (GC8 PU)	£16. 8. 0	£3. 6. 0	12 of £1. 4.0
GARRARD RC88 (GC8 PU)	£18.12. 8	£3.15. 8	12 of £1. 7.3
B.S.R. UAB Monarch (TC8 PU)	£7. 5. 0	£1. 9. 0	6 of £1. 2.8
BSR UA12 Monarch (TC8 PU)	£9.19. 6	£1.19. 6	12 of 15/-
BSR UA12 Monarch (TC8S Stereo PU)	£10.17. 6	£2. 3. 6	12 of 16/2
SINGLE RECORD PLAYERS			
GARRARD EA (GC8 PU)	£8.10. 0	£1.14. 0	12 of 13/-
BSR TU9 (TC8 PU)	£4.10. 0	£1. 5. 0	3 of £1. 5.0
COLLARO RP584 (O. P. or TPU)	£8.18.11	£1.15.11	12 of 13/7
COLLARO RP594 (O. P. or TPU)	£9.18. 9	£1.18. 9	12 of 15/-
E.M. (Acos Stereo P.U.)	£6.15. 0	£1. 7. 0	12 of 10/8
TRANSCRIPTION UNITS			
COLLARO 4T/200	£18.13. 0	£3.15. 0	12 of £1. 7.4
COLLARO 4TR/200 Motor only	£13.18. 3	£2.15. 3	12 of £1. 0.5
GARRARD 4HF (GC8 PU)	£18. 9. 9	£3.15. 9	12 of £1. 7.0

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

MULLARD TAPE PRE-AMPLIFIER

This unit is intended for use with an existing amplifier and provides all the circuits necessary for tape recording and play-back. Instruction manual, giving full constructional information is available price, 2/10, post free.

COMPLETE KIT containing every item required down to the last nut and bolt. First-class items only included. £14.7.0. H.P. Deposit £2.17.0 and six monthly payments of £2.2.6. Kit less valves, £10.19.6. H.P. Deposit £1.19.6 and six payments of £1.13.4. Power Unit kit, £3.19.6.

LATEST CABY TEST METERS

Now in stock. CABY SUPREME MULTI-RANGE METERS. Made abroad. We can confidently recommend these meters as being accurate, well made and very good value for money.

MODEL A-10. Sensitivity 2,000 ohms per volt A.C. and D.C. Five voltage ranges 10-1,000 volts A.C. and D.C. Three D.C. current ranges .5-250 ma. Two resistance ranges. Size 5 1/2in. x 3 1/2in. x 1 1/2in. Price, £4.17.6. H.P. Deposit £1.7.6 and three monthly payments of £1.6.8.

MODEL B-20. Sensitivity 4,000 ohms per volt A.C. and D.C. Voltage ranges—Five D.C. 10-1,000 volts. Four A.C. 10-1,000 volts. Four D.C. current ranges. .5-250 ma. Four resistance ranges. Price £6.10.0. H.P. Deposit £2 and three monthly payments of £1.13.4.

Illustrated leaflet giving full details of both models free upon request.




LATEST AVO TEST METERS

AVO METER MODEL 8. The finest multi-range meter available. 20,000 ohms per volt on D.C. ranges. Eight D.C. Voltage ranges 2.5 v. to 2,500 v. Seven D.C. current ranges 50 microamps. to 10 amps. Seven A.C. Voltage ranges 2.5 v. to 2,500 v. Four current ranges 100 mA. to 10 amps. Three resistance ranges. Fully detailed leaflet available. Price £23.10.0. H.P. Deposit £4.14.0 and 12 monthly payments of £1.4.6. Price with leather carrying case, £27.8.0. H.P. Deposit £5.8.0 and 12 payments of £2.0.4.
 Other AVO Meters available include the Model 7 £19.10.0. H.P. Deposit £3.18.0 and 12 payments of £1.8.8 and the Multi-minor price £9.10.0. H.P. Deposit £1.18.0 and 12 monthly payments of 14/4.

JASON FM TUNER

There are no less than four different Jason FM Tuner Kits now available to the Home Constructor. Brief details are given here and individual lists on any are available free.

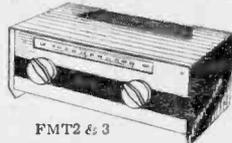MOST IMPORTANT. We take great pains to see that the kits we supply are absolutely complete in every detail and also that all components supplied are entirely suitable in every way. This accounts for differences in price you may notice between our prices and those of some of our competitors. **THIS SHOULD BE BORNE IN MIND WHEN COMPARING PRICES.**



Hire Purchase Terms available. FMT2 & 3

STANDARD TUNERS

STANDARD TUNER, FMT1. The very popular tuner which is supplied with a chassis assembly fitted with a cold hammer finish front panel and glass dial. Employs four EF91 valves. External power supply is required. Complete kit £6.19.6. Power pack kit, 39/-.

STANDARD TUNER IN SHELF MOUNTING CASE, FMT2. This is a new version of the above tuner. The circuit has been brought up to date and is built into the very attractive shelf mounting case of the new Fringe Tuner mentioned below. The circuit uses four EF90 valves and the power supply can be built into the case if desired. Complete Kit £7.17.6 without power supply components. £9.16.0 with power supply.

MERCURY SWITCHED TUNER. This is a tuner in chassis form which has a three position switch for the three BBC programmes. Uses one ECF90 and four EF90 valves. External power supply is required. Complete Kit £9.19.0. Power Pack Kit 39/-.

FRINGE TUNERS

NEW FRINGE TUNER IN SHELF MOUNTING CASE, FMT3. This is an entirely new Fringe Tuner and is supplied complete with a very attractive green shelf mounting case with Perspex dial. The tuner is fitted with variable AFC. Internal power supply if desired. Valves used are one ECC81 and five EF90. Complete Kit £9.19.6 without power supply components. £11.19.0 with power supply.

INSTRUCTION MANUALS

All our kits include the appropriate instruction manual. All available separately as follows:
 Manual covering both Standard Tuners and the new Fringe Area model, 2/10. "Mercury," 2/3. All post free.

Hire Purchase Terms are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows:
 Three months; Deposit 6/- in the £. Service charge 5%, but minimum charge 10/-. Six and Twelve months; Deposit 4/- in the £. Service charge 10%, but minimum charge 20/-.

Terms of Business.—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows. Up to £3. Postage and C.O.D. fee minimum 2/8. Over £3 and under £5. C.O.D. fee only 1/6. Over £5 no charge.

WATTS RADIO
(MAIL ORDER) LTD.


54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone: Weybridge 4556

Please note: Postal business only from this address.

**CONSTRUCTORS
CORNER**

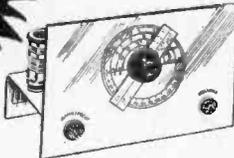Construction price includes valve and one coil covering 40-100 m.
 Ⓢ Can be converted to 2v. or 3v.
 Ⓢ Receives speech and music clearly from all over the world.
 Send 2/- for diagram and price list.



Explore the world on short-wave radio (10-100 m)

FOR ONLY **35/-**

TRANSISTOR POCKET RADIO

Two-stage circuit using variloopstick coil.

- Ideal for the beginner.
- Can be built in 30 minutes.
- Works for months off 7d. battery.
- Fits into palm of your hand.



The ideal low-cost transistor pocket radio for the beginner.
 Send 2/- for data and list of components.

ONLY **30/-**

CRYSTAL RECEIVER
Covers M/W Band


All components including case for **10/6**
 Ideal for the beginner.

Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE

ENSURE SUCCESS WITH R.C.S.

SENSATIONAL RESULTS WITH 2 TRANSISTORS

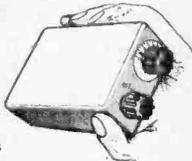- ★ No aerial or earth.
- ★ Dial tuning with mini .0005.
- ★ Drilled chassis, colour coded, components, simple layout for beginners.
- ★ Special small case fits shirt pocket.
- ★ Soldering iron and pliers are only tools needed.



Finest results ever obtained with 2 transistors and diode layout. The ideal radio to carry with you everywhere.
PARTS PRICE LIST & EASY LAYOUT PLANS, 2/-.
 Total building cost, including transistors, wire, etc., **62/6**

BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

- ★ Sturdy metal case.
- ★ No holes to drill.
- ★ Detachable rod aerial.
- ★ All batteries self contained.
- ★ Can be built in 1 hour.
- ★ Covers medium waves.
- ★ Loud clear tone.
- ★ Selective tuning.
- ★ All parts are sold separately.

This delightful set is designed to give you a completely personal portable radio.
 Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.
 Send 2/- for wiring diagram and component price list.

FOR ONLY **35/-**



Trade Enquiries Welcomed

R.C.S. PRODUCTS (RADIO) LTD. 11, OLIVER RD., LONDON, E.17.

Mail Order Only

Premier RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1.

TEL.: MUSEUM 3451/2

The "Petite" PORTABLE

MAY BE BUILT FOR

£7.7.0

Plus p. & p. 3/-

BATTERIES EXTRA.
 H.T. 10/- (Type B126) or equivalent L.T. 1/6 (Type AD35) or equivalent.

- ★ Size only 8in. x 8in. x 4in.
- ★ Instruction book 1/6.



THE BEREC

The 'Berec' Battery Receiver for only **£4.19.6** plus 5/- p. & p. or **£10.0** dep. and 5 mthly pymts of 19/-. Suitable for use in the home or where normal electricity supply is not available, remarkable reception on med. and short wavebands, using DK92, DF92, DAF96, DL96, latest type min. Battery Valves: operates on an external B.103 Battery or equiv. Housed in an attractive, two-tone metal case. Size 11 1/2 x 7 1/2 x 5 1/2 in. **BATTERY EXTRA 13/6**



VISIT OUR NEW BRANCH AT 309 EDGWARE ROAD, W.2.

Telephone PAD 6963



The Famous Cossor 3 watt **AUDIO AMPLIFIER KIT 562K**
 Original Price £9.15.0

OUR PRICE **£5.19.6**, p. & p. 2/6

This Kit assembled will provide a compact versatile Amplifier which incorporates the most up-to-date pre-assembled printed circuit and is suitable for operation from Radio, Microphone or Gramophone. The circuit design includes negative feedback, valve line-up 6V4, 6BQ5, EF86. Two Loudspeakers are used, i.e., 10in. x 6in. Elliptical and 4in. Treble, ensuring high quality output, suitable for use on 200/250 v. A.C. mains. All items are supplied, including Loudspeakers, Knobs and Escutcheon, with full assembly instructions and in maker's original cartons.

Convert your Battery Portable to A.C. mains operation with the Cossor MU2 Battery Eliminator.

This unit is assembled and supplied with 4ft. of Mains Lead and unit Torpedo type of On/Off Switch. Housed in 2 metal containers approximately the same size as the AD.35 and B.126 batteries and suitable for Receivers using 1.4 volt L.T. and 90 volt H.T.

ORIGINAL PRICE 3 gns.

OUR PRICE for a limited period, 37/6, plus 2/- p. & p.

Open to Discussion



The Editor does not necessarily agree with opinions expressed by his correspondents.

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

Interference

SIR,—I think you are right in your comment in the December, 1959, issue, by saying that interference on A.M. medium and long waves can only be stopped (or partly stopped) by closer control of frequencies and number of stations operating. All this deserves a conference of all countries concerned and must include the USSR (which has hundreds of stations). The chance of any agreement is very small, I think. What is needed is as follows: each country should be given three or four channels to broadcast high-powered transmissions. The main part of listening to home transmissions should be done on V.H.F. which at present is cheap. The medium wave perhaps could be made larger say 165-700m and each country should do its part to stop interference from morse, etc. We can only hope that something will be done sooner or later about the problem which grows worse each year.—M. REYNOLDS (Nailsea).

The "Old Days"

SIR,—It is obvious that amateur radio is not all that it used to be. This is because all "modern" components have to be soldered. In many cases there is very little of anything left, to solder on to! Many amateurs have no facilities for soldering. Many are not allowed to solder. Again, modern components are dull and uninteresting in appearance. An article is described as a "capacitor" and has much wonderful scientific data tagged on. The latter no doubt is correct. But it will appear to be just a plain common roll, covered in paraffin wax, and with a wire sticking out of each end.

"Condensers" used to be well designed and interesting-looking pieces of apparatus. They had screwing-down holes, efficient terminals, and soldering tags. They were brand new in appearance, wrapped in tissue paper, and packed in attractive cartons. Therefore they sold well!

Resistances had metal cones at each end. To change a resistance, one had only to remove one from its clips and replace it with another. What magnificent iron-shrouded transformers there were. Variable condensers were veritable masterpieces. Coils were composite and shielded triumphs!

In those days there was also the sense of the marvellous to attract the amateur. I well remember the excitement which reigned when the "giant" 5XX station, with its 14kW, was about to take the air. I listened in with a crystal set, based on a 12 × 4in. cardboard former wound with 24 gauge D.C.C. wire. I think we half expected loud speaker results! I was gratified, however, to receive loud and clear telephone signals; much better than those previously received from the London station.

Valves were quite good in those days. Especially when the new "dull-emitters" were introduced.

The experimenter with battery and transistor sets, who does not wish to solder, should obtain some small oblong electrical connectors. These have a central hole, which enables them to be bolted to the chassis with small gauge bolts. They completely obviate the need to bend wires on condensers and resistances and can also be removed and replaced at will.

Use a larger chassis! One with components widely spaced gives a set a quite impressive appearance. Far more so than does a small chassis, containing all the wires and components, in more or less a jumbled heap.—A. TROWBRIDGE (Staines).

Capacitors

SIR,—I am a beginner to radio and I would like somebody of your readers to help me. Suppose that I need an 8 μ F, 600VW condenser and that nothing of the kind is available. Can I put two 16 μ F, 300VW condensers in series so that I will obtain an 8 μ F 600VW condenser from them? In my opinion I am right and I wonder if any of your readers will agree.—JOSEPH MIRSUD (Flat 1, Block XI, Hubbard Flats, Cospicua, Malta, G.C.).

Radio Sound

SIR,—There have been numerous letters about radio sound on A.F. amplifiers. The radio sound in most cases is due to the fact that anode bend rectification is taking place. This is most probably due to the fact that the bias resistor in one stage has deteriorated so that the valve is biased up to nearly cut off point and is hence acting as an anode bend detector. It could also be due to wrong choice of bias resistor value in the first case. The fact that different stations are received can only be due to the fact that the "mike" head is acting as a tuned circuit and with difference in the length of cable there will be a difference in frequency received.

If any other SWL. of my own age (14) could take the trouble to correspond with me I should be pleased to hear from him.—W. J. WHITE (14, Pollard Close, Chigwell, Essex).

27Mc/s Transmitter

SIR,—I constructed the 27Mc/s pocket transmitter as published in the December edition of PRACTICAL WIRELESS, and found it to work quite satisfactory. I then converted the transmitter for mains use, using an R.F. pentode triode connected, cathode keying. I found that a 50c/s mains hum was being transmitted, so I included an A.F. choke in the anode circuit. This worked extremely well, but when I was working the transmitter I noticed that another signal was behind my own. I then sent out a continuous signal, and found that when my transmitter was in operation other stations transmitting speech and music came in behind, but when I switched my transmitter off they stopped. This did not only occur on 27Mc/s but on many frequencies. Can any reader give an explanation of this?—C. GODDARD (Wallington, Surrey).

Using the RF24

SIR,—Several queries have been received regarding the coil data of the RF24 unit. Several of the RF24 and RF25 units on the surplus market have been modified to cover the frequency ranges of the RF26 and RF27 units. The coil details required are as follows:

R.F. grid coil. $14\frac{1}{2}$ turns 22s.w.g. tinned copper with three turn link interwound at earth end.

Mixer coil: $8\frac{1}{2}$ turns 22s.w.g. tinned copper.—D. PRATT, G3KEP and D. NOBLE, G3MAW (Yorkshire).

Mains Polarity

SIR,—With reference to G. F. Watt's letter on mains polarity (December, 1959, issue), I should say that there would be no possibility of the Supply Authority changing the phases over at the Power Station or Sub-station, for that matter, as this would have disastrous effects, such as three-phase motors being reversed. Also on a single-phase supply the polarity of the switching of lights, also plugs, would be reversed; this also would result in the neutral being broken at the switch positions instead of the live side.

There is a possibility of the mains round G. F. Watt's area being out of balance; this could be caused by too many consumers on the same phase, causing a leakage on the neutral, which could have a potential of several volts between neutral and earth, depending on this out of balance. This may be the explanation for the ripple of which Mr. G. F. Watts complains.

I was also interested in Mr. G. Y. Kingdon's letter in the November issue, and fully agree with him regarding earthing and more stress being placed on the correct connections of live and neutral and earth terminals of plugs, as all modern three-pin plugs and socket outlets are marked "L," "N" and "E." It is always advisable to test the socket outlet to find the polarity, as

quite often these are connected the wrong way round, even when the job has been done by a so-called electrician.

I was also interested in Mr. W. Pascoe's comments on earth connections, and he makes a rather interesting point where miniature circuit breakers are employed on some modern installations. Where the radio set is an A.C. type with the three core lead connected to a mains earth system and also an independent outside earth, it does appear that this would create a parallel earth depending on the resistance of the two earths, therefore, affecting the working of the miniature circuit breaker. I intend taking this matter up with someone who is an authority on circuit breakers.—A. DEARDEN (Johannesburg, S. Africa).

Transistors v. Valves

SIR,—Being an ardent supporter of the valve, I would like to make a few points in its favour.

Transistor sets cannot beat F.M. mains valve sets as far as reproduction and good tone are concerned, because as yet transistors do not work so well at high frequencies, and it would be difficult for a transistor set to beat the tone and volume of an ordinary five-valve superhet.

Although mains sets do not work as soon as they are switched on, one should not compare transistor sets with mains superhets. Battery sets, on the other hand, work instantaneously like transistor sets.

Although transistors have many points in their favour, such as small size and low power consumption, valves are being made smaller, and are taking less current. Perhaps a power supply to heat the cathode could be completely eliminated by further research into "cold-cathode" valves. If there was no need for a filament battery, there would be few advantages for transistors.—D. C. HAIGH (Bradford, York).

SIR,—Recent letters from readers prompt me to offer a few remarks. On transistors, I would say that I have experimented with them for the past three years, having always tried to get a lot from the least, and like them.

I have achieved a certain success, being able to receive stations from all over Europe, plus Tangier, on all wavelengths down to 30m; this on a crystal and transistor circuit with a 75ft. aerial about 20ft. high, and a counterpoise type earth, as I find it very much better than a "grounded" earth. Tapped coil and switch are employed in both aerial and tuned circuits and output is boosted by a transformer.

I have tried many of the circuits which have been published in previous issues of PRACTICAL WIRELESS and have made many very good receivers—some without resistors.

The volume from the two circuits is terrific. But, like Capt. Graham and others remark, break-through persists from powerful stations, and in my area the local Third tries to swamp everything.



FOR VALVES - TUBES AND COMPONENTS - BY RETURN POST SERVICE

AC6PEN 6/6	ECF80 12/-	EM34 9/6	PCL83 14/6	UCC84	IDS 12/6	6BW7 8/6	6SN7GT 7/6	12SH7 6/-
ATP4 3/6	ECF82 13/-	EM80 10/-	PL36 15/-	10/11	ID6 12/6	6C4 6/-	6SQ7 9/3	12S17 6/-
AZ1 10/-	ECH21 23/3	EM81 10/6	PL81 12/6	UCC85 10/6	IH5GT 10/6	6C5GT 6/6	6U4GT 12/-	12SK7 6/-
AZ31 10/-	ECH35 23/3	EY51 10/-	PL82 8/6	UCF80 16/7	IL4 6/6	6C6 5/6	6G5G 8/6	12SL7 8/-
AZ41 13/11	ECH42 9/6	EY81 13/3	PL83 11/6	UCH21 23/3	IN5 10/6	6C31 7/6	6U7G 8/6	12SN7GT
B36 15/-	ECH81 9/11	EY86 10/-	PX25 12/6	UCH42 10/6	IR5 7/6	6CD6G	6V6G 6/-	15/-
CL4 12/6	ECH83 13/11	EZ40 7/6	PY32 17/11	UCH81 10/6	IS4 10/6	29/10	6V6GT 7/9	12SQ7 8/6
CL33 19/3	ECL80 10/6	EZ41 7/6	PY80 7/6	UCL83 13/6	IS5 6/6	6D6 5/-	6X4 7/6	1457 17/-
CY31 16/7	ECL82 12/6	EZ80 7/-	PY81 8/6	UF41 9/-	IT4 6/-	6CH6 10/6	6X5G 7/-	15D2 7/9
CV73 4/-	ECL83 19/3	EZ81 7/-	PY82 7/-	UF89 9/-	2C26 1/6	6F6G 7/6	6X5GT 7/-	19AQ5 9/9
DAF96 8/9	EF22 8/6	E1148 2/-	PY83 8/6	UL41 10/-	2X2 4/6	6F6M 7/6	6/30L2 12/6	20D1 15/3
DF96 8/9	EF36 5/-	FW4/500	QZ1 7/-	UL44 26/6	3A4 7/-	6F1 14/-	7B6 10/6	20P1 26/6
DH63 7/6	EF37A 15/-	GZ32 12/-	QZ81 7/-	UL46 26/6	3A5 12/6	6F13 14/-	7B7 8/6	25A6G 10/6
DK96 8/9	EF39 5/9	H30 5/-	QZ82 7/-	UL48 26/6	3A8GT 6/-	6F15 14/-	7B8 6/-	25L6GT 10/-
DL96 8/9	EF40 14/6	H63 10/-	PEN25 6/-	UL49 26/6	3A8GT 6/-	6F33 7/6	7C5 8/-	25Z4 9/6
DM70 7/6	EF41 9/9	H63 10/-	PEN46 3/-	UL49 26/6	3A8GT 6/-	6H6 2/6	7C6 8/-	25Z5 8/-
EA50 1/6	EF42 11/6	HL23DD 8/6	PEN220A	UY1N 12/6	3Q5GT 9/6	6H6GT 2/6	7D6 13/6	25Z6 10/-
EABCB0 9/6	EF50 4/-	HL22 6/6	PEN44 12/6	UY41 7/6	354 7/6	6H6GT 5/6	7H7 9/6	275U 19/11
EAF42 10/6	EF50SYL 7/-	K40N 9/-	PEN45 6/-	UY85 7/-	3V4 8/6	6J5M 6/6	7Q7 9/6	30C1 10/6
EB34 2/-	EF54 6/-	KF35 8/6	PEN46 3/-	VP13C 3/6	4D1 3/-	6J6 6/6	757 9/6	30F5 10/6
EB41 8/6	EF55 10/6	KT2 5/-	UCC84	VP23 4/6	5R4G 9/6	6J7G 6/6	7Y4 2/6	30FL1 10/6
EB91 6/6	EF80 7/6	KT24 5/-	UCC85 10/6	VP41 8/6	5U4G 6/6	6J7M 9/6	8D2 2/9	30P4 15/-
EBCC33 6/9	EF85 7/6	KT25 10/-	UCC86 10/6	VP41 8/6	5V4 11/6	6K7G 4/9	9D2 3/6	30P12 12/6
EBCC41 9/6	EF86 13/6	KT36 29/10	UCC87 10/6	VP41 8/6	5Y3G 8/-	6K7M 6/9	10C1 17/3	30P16 9/6
EBCC81 11/4	EF89 8/9	KT61 13/6	UCC88 10/6	VP41 8/6	5Y3GT 8/-	6K8G 7/6	10C2 17/6	30P1L 12/6
EBCC90 12/7	EF91 5/9	KT63 7/6	UCC89 10/6	VP41 8/6	5Z4G 9/-	6K6GT 7/6	10D2 12/6	35L6GT 10/-
EBC91 12/7	EF91 (BVA)	KT66 17/6	UCC90 13/3	VP41 8/6	6A7 10/-	6K7GT 5/9	10F1 12/6	25Y5 9/6
EBF80 9/9	EL32 5/6	KT66 17/6	UCC91 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	10LD11 12/-	35W4 7/6
EBF89 9/6	EL33 14/-	KT66 17/6	UCC92 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	10P13 17/6	35Z4GT 8/-
EBL21 23/3	EL38 26/6	KT66 17/6	UCC93 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12A6 6/6	42 8/-
EBL31 23/3	EL41 10/6	KT66 17/6	UCC94 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12A7 10/6	35Z3 16/7
ECC81 8/-	EL42 10/6	KT66 17/6	UCC95 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12AT6 7/6	35Z5GT 9/-
ECC82 7/6	EL42 10/6	KT66 17/6	UCC96 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12AU7 8/-	50C5 11/6
ECC83 9/-	EL81 16/7	KT66 17/6	UCC97 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12AU7 8/-	50L6GT 8/6
ECC84 10/-	EL83 19/11	KT66 17/6	UCC98 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12B6 8/-	75 11/6
ECC85 9/6	EL84 9/-	KT66 17/6	UCC99 13/3	VP41 8/6	6A7 10/-	6K8GT 10/6	12B6 8/-	77 7/6

RECORD PLAYER UNIT

BSR Monarch Model UAB. 4-speed 10 records capacity, Full-Fi turnover crystal cartridge. £6.19.6.

DPDT TOGGLE SWITCHES (BY CUTLER HAMMER) 2/6 ea.

100 Resistors Assd. 1/2 and 1 watt, 12/6 packet. Wireless World Valve Data Book 5/- ea. Post 4d. Data TV fault finding book (illustrated), 5/-, post 4d.

MICRO SWITCHES, 3/9 ea.

BATTERY BUZZERS, 3/9 ea.


MORSE KEYS, 3/- each.

0-1 mA. Panel Mounting Meters, 22/6.

MULTI-WAY CABLE, 5 colour coded cables—one screened for inter-chassis connection, 1/- per yard.

ACOS CRYSTAL PICKUP TYPE GP 54/2, complete with turnover crystal cartridge and crystal styli HP37/1 or HGP59/50, 29/6 complete.

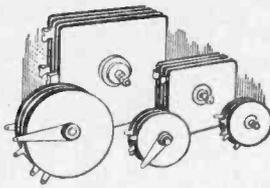BEST QUALITY RECORDING TAPE, 600 foot reel, 15/-; 1,200 foot reel, 23/-; 1,800 foot reel, extra play, 37/6.



ALPHA MISCELLANEOUS TRANSFORMERS AND CHOKES HEATER TRANSFORMERS
+Primary 220/240 volts.

2 volt 1/2 amp.	5/-
2 volt 3 amp.	8/3
4 volt 1 1/2 amp.	5/6
6.3 volt 1 1/2 amp.	6/9
6.3 volt 3 amp.	10/-
12 volt 3 amp.	5/9
4 volt 3 amp.	10/-
5 volt 2 amp.	10/-
6.3 volt 3 amp.	5/6

CHARGER TRANSFORMERS
Tapped Primary 200/240 v. Secondary 3.5 v., 9 v. and 17 v.

1 amp. type	13/6
2 amp. type	15/6
4 amp. type	21/-
6 amp. type	32/6
Post 2/-.	

RECTIFIERS FOR BATTERY CHARGERS

12 v. 1 amp.	4/3
12 v. 2 amp.	7/-
12 v. 3 amp.	10/6
12 v. 4 amp.	12/-
12 v. 5 amp.	14/6

OUTPUT TRANSFORMERS

ELSTONE OT/3 for Mullard.	3 watt amplifier, 25/-
ELSTONE OT/6 (Low Load), 45/-.	
ELSTONE OT/8 (Normal Load), 45/-.	

ACOS MICROPHONES

Acos Mic 39/1. Crystal Stick Microphones for use as a hand, desk or floor stand units, for high quality recording, broadcasting and public address work. List price £5.50. OUR PRICE 39/6, with stand 47/6 with floor stand adaptor 52/6, postage 1/6. Acos Mic 40, as supplied with most modern tape recorders, with folding rest and 8ft. lead, response 40-6,000 c.p.s. Listed at 35/-. OUR PRICE 25/-.

TELEVISION TUBES

Regunnet Tubes 12 months guarantee. Most types available, e.g., MW 43/64, £6, CRM 141, £5.10.0. CRM 171, £6. Carriage and Insurance 10/-.

CATALOGUE.

Our 1960 catalogue is now available, please send 1/- in stamps for your copy.

ALPHA
-RADIO SUPPLY CO

103 LEEDS TERRACE
WINTON STREET
LEEDS 7

TERMS: Cash with order or C.O.D. Postage and Packing charges extra; as follows: Orders value 10/- add 1/-, 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday; Saturday 10 a.m. to 1 p.m.

For "Thermion's" information, until last week when I had a check and change, I was using as long wave coupling, a coil I wound by hand in 1923 and I have more components of that vintage. I also held one of the 15s. experimental licences of that time, and I listen to ships on a one valve circuit using a very old 2V valve and can log every ship, shore station including Scottish.—W. M. MACKENZIE (Gosport, Hants).

Correspondents Wanted

SIR,—I am 21 years of age and I am a qualified radio engineer. I am also working in the Police Radio Office as a radio engineer. I want to correspond with any boys of any age who

are interested in radio subjects.—ASHAK KAPUR (Ph. Police Radio Office, Simla—2).

SIR.—I am 25 years of age and am very interested in radio and record changer repairs. I would like to correspond with radio technicians of any age anywhere. All letters received will be answered promptly.—DOLAT DESAI (P.O. Box 8333, Johannesburg, South Africa).

Information Required

SIR,—I am seeking information on converting RF26 unit to 10m. Would anyone who can help please contact me?—G. FOSTER (4, Thompson Avenue, Ormskirk, Lancs).

MEASUREMENTS WITH MULTI-RANGE METERS

(Continued from page 942)

adjusting the potentiometer the voltmeter should be set to read full scale, i.e., 2.5V. The potential between the slider and H.T. negative then has a reference value of 297.5V. The resistance value of the potentiometer is made low so that the adjustment is fine otherwise a slight movement of the slider would represent many volts and the voltmeter could not be accurately adjusted.

The load is now switched on and if the change in voltage is from 300V to 299V then the meter reading will decrease from 2.5V to 1.5V. This change can then easily be read to a high degree of accuracy.

A.C. Measurements

The basic moving-coil instrument may be modified to measure A.C. by first rectifying the A.C. before passing it through the meter movement.

Unfortunately the resistance of the rectifier varies with the amount of current flowing; at low values of current, low scale readings, the forward resistance of the rectifier is greater than at high scale readings. This effect is unimportant when using high voltage ranges as then the required high value of series resistor "swamps" the resistance variations of the rectifier. On low voltage ranges the rectifier resistance variation become proportionately greater when compared

to the total circuit resistance and result in a non-linear shape of the low end of the scale.

With the better, and subsequently more expensive, instrument the difficulty is overcome by using a voltage transformer on the low ranges. The low input voltage is stepped up and then the higher value of series resistor is large enough to swamp rectifier resistance variations.

Quoted Accuracies

In the cheaper instruments the inaccuracies are tolerated but are indicated by quoting the calibra-

Voltage	Accepted Variation	Error
80	76V to 84V	5%
40	36V to 44V	10%
20	16V to 24V	20%
8	4V to 12V	50%

tion accuracy of the meter as a percentage of full scale reading. Consider a meter, the accuracy of which is quoted as, say, 4 per cent. of full scale reading. On the 100V range this means a reading may vary by $\pm 4V$. At f.s.d., the percentage error is, of course, only 4 per cent. but the table above shows how the percentage error increases at voltages less than f.s.d.

This point should be borne in mind before wasting time trying to make a too accurate reading. The accuracy cannot be better than the accuracy of the instrument.

Another point to remember is that the moving coil instrument measures the mean value of the rectified A.C. The value normally required is the r.m.s. The average value when multiplied by the form factor gives the r.m.s. value. The form factor for a sine wave is 1.11 so during calibration all mean values are multiplied by 1.11 and scale readings are then read as r.m.s. values.

If the waveform of a measured voltage is not a pure sine wave, the form factor will not be 1.11 and the meter calibration will not be maintained. Two vastly different waveforms may have the same mean value but as the form factors would be different the r.m.s. values would be different although the meter deflection would be the same in each case. In practice the error is not very great but is mentioned mainly to emphasise the errors present when the waveform is not a pure sine wave.

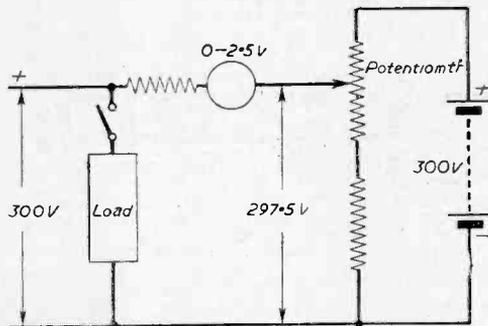


Fig. 7.—An accurate method for measuring small changes in voltage.

"PRACTICAL WIRELESS" MOTORISTS!

SAVE £20 A YEAR AT LEAST!
WITH THIS AMAZING DO-IT-YOURSELF GUIDE

ODHAMS MOTOR MANUAL



FOURTH EDITION ENTIRELY REVISED

HOW YOUR CAR WORKS AND HOW TO SERVICE IT



Servicing Carburettor

Learn how to get MORE M.P.G.

In addition to showing how you can do your own maintenance and repair jobs, this comprehensive manual is packed with practical guidance and useful tips that will help you to get more miles per gallon, longer life from batteries and tyres, etc.—the vital "know how" that will save you pounds!

Learn How Your Car Works

In order to be a perfect driver and before you can learn how to carry out adjustments of any kind, you need a complete understanding of how and why every part of your car works. Experts explain, in crystal-clear detail, with unique "see how" illustrations and "exploded" drawings, the exact construction and working of the various engine parts, the gearbox, transmission, electrical and fuel systems, brakes, etc.

Make sure YOUR car is roadworthy!



Whether or not your car is liable to undergo compulsory testing, it is vital that you take steps NOW to ensure that your brakes, lights, steering, etc., are in thoroughly

roadworthy condition. Simply and clearly, this book shows you just HOW to set about it!

KEEP YOUR CAR YOUNG

Learn how to reduce wear and tear, obviate the risk of breakdown—add years to your car's life! A complete trouble-tracing chart enables you to recognize the danger signals of impending trouble and trace them to their source—a step-by-step procedure that never fails.



BUYING A CAR?

Experts tell you what to look for when buying a new or secondhand car, what tests to make, points to consider for maximum comfort and running economy. The £.s.d. of car ownership.

Here's the amazing book that will help you to **SAVE POUNDS—ENJOY BETTER MOTORING!** Already proving itself indispensable to thousands—experienced motorists and "L"-drivers alike! The most helpful, easy-to-follow book of its kind. Tells, in clear text and "see how" pictures, all you need to know about how your car works and how to keep it in perfect condition. Saves its low cost hundreds of times over! Reserve NOW! Standard Ed., 16/-, or De Luxe, leathercloth, nominal extra cost of only 2/-. Prices include postage, packing, etc.

NEARLY **300** "SEE HOW" PICTURES 320 PAGES



THE BIGGEST MONEY-SAVER EVER!

Learn from this grand, lavishly illustrated volume how to maintain and repair your car, and safeguard your valuable investment. Shows how YOU can tackle all kinds of minor repairs and adjustments (many major jobs, too!) with complete SUCCESS!

CONTENTS INCLUDE: The car simply explained; Learning to drive; Carburettors and fuel systems; Engine maintenance; Fault tracing; Engine repairs and overhaul; Electrical equipment; Transmission; Chassis and Suspension; Brakes; Steering; Wheels and Tyres; Bodywork, etc.

Get MAXIMUM PERFORMANCE

Experts show you how to care for your car so that you get the best possible performance from it. How to service and tune the carburettor, simple decarbonizing, timing the engine, ignition servicing and adjustment, etc.



Ignition adjustment for peak performance

EXPERT ADVICE for 'L'-DRIVERS

All you want to know about the car and how to drive it. Valuable advice that will help you pass the Driving Test.

DO THIS NOW!

Simply fill in form, indicating Edition required, and post in 2d. stamped, unsealed envelope to Dept. E.B.23, People's Home Library, Basted, Sevenoaks, Kent. Offer applies in U.K. and Eire only, closes March 31. Hurry!

SEE HOW YOU SAVE!

These maintenance costs, for an average "popular" model are on the modest side. Now check your own savings on 12,000 miles' motoring.

	s. d.	£ s. d.
Every 1,000 miles		
Oiling & greasing	12 0	7 4 0
Every 3,000 miles		
Wheel change	5 0	1 0 0
Every 6,000 miles		
Change gearbox and rear axle oil	7 0	14 0
Clean & adjust plugs, check and adjust tappets	10 0	1 0 0
Ignition and carburettor check—tune engine	35 0	3 10 0
Check & adjust brakes	15 0	1 10 0
Every 12,000 miles		
Decarbonize and grind in valves	5 10	0
TOTAL SAVING	£20	8 0

SEND NO MONEY NOW!

To: Dept. E.B.23, People's Home Library, Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION reserve me "Odham's Motor Manual" and send Invoice with "100% Satisfaction or No Charge" Guarantee.

Cross out Edition NOT required: STANDARD/DE LUXE

BLOCK LETTERS

NAME

Full Postal ADDRESS

Firmly affix 2d. stamp in margin

E.B.23/March 1960

R.S.C. MANCHESTER BRADFORD & LEEDS

(Leeds) LTD. Terms C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 under £2. 2/9 under £5.

EN. GOVT. MAINS TRANSFORMERS

Primaries 200-250 v. 50 c.p.s. A.C.	
250 v. 60 m.a., 6.3 v. 2 a.	10/11
275-0-275 v. 100 m.a. 6.3 v. 7a. 5 v. 3a.	21/9
330-0-330 v. 60 m.a., 6.3 v. 2 a.	11/9
330-0-300 v. 100 m.a., 6.3 v. 2 a., 5 v. 2 a.	18/9
350-0-350 v. 160 m.a. 6.3 v. 5 a., 5 v. 3 a.	27/9
450-0-450 v. 250 m.a. 6.3 v. 3 a., 6.3 v. 1 a.	
5 v. 6 a.	49/9

SELENIUM RECTIFIERS

F. W. BRIDGE	
6/12 v. 1 a.	3/11
6/12 v. 2 a.	6/11
6/12 v. 3 a.	9/9
6/12 v. 4 a.	12/3
6/12 v. 6 a.	15/3
6/12 v. 10 a.	25/9
6/12 v. 15 a.	35/9
2 v. 2 a.	14/9

Mail Orders to 29-31 Moorfield Rd., Leeds, 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1, 8-10 Brown St. (Market St.), Manchester 2, or 56, Morley Street (Next Majestic Ballroom), Bradford.

SENATIONAL TRANSISTOR OFFER.

3 for 10/9. A huge purchase enables us to offer Brand New, Guaranteed Brimar TSL Audio Transistors at a small fraction of list price. **TELEVISION RECTIFIERS.** 250 v. 200 m.a. small size. Only 6/9 ea. **RE-ENTRANT SPEAKERS.** Tannoy, 8 watt, 7.5 ohms. Only 19/6 each. Or 35/- per pair. **ARDENTE DEAF AID EAR-PIECES.** Brand new, complete with ear insert and lead. Only 15/6 each.

R.S.C. BATTERY CHARGING EQUIPMENT

ASSEMBLED CHARGERS

6 v. 1 amp.	29/9
6 v. or 12 v. 1 amp.	29/9
6 v. or 12 v. 2 amps.	38/9
6 v. or 12 v. 3 amps. with ammeter	59/9

Above ready for use. With mains and output leads. Carr. 3/6.



Assembled 6 v. or 12 v. 4 amps.

Fitted Ammeter and variable charge rate selector. Also selector plus for 6 v. or 12 v. charging. Louvered steel case with stoved blue hammer finish. Fused 69/9 and ready for use with Car. 5/- mains and output leads. Terms: Deposit 13/3 and 5 monthly payments 13/3.

ASSEMBLED CHARGER

6 v. or 12 v. 2 amps. Fitted Ammeter and selector plus for 6 v. or 12 v. charging. Louvered metal case, finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Carr. 3/9. 49/9

HEAVY DUTY CHARGER KIT.

6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-230-250 v.; F.W. (Bridge) Selenium Rectifier; Ammeter, Multi Position Switch with Knob; Panels, Fuses, Fuseholder, and circuit. 59/9. Carr. 4/6.

EX-GOVT. CASES. Size 11-10-8 1/2 in. high. Well ventilated, black crackle finished, undrilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/8. plus 2/9 postage.

2 v. 16 a.h. EX-GOVT. ACCUMULATORS. New, boxed. Only 5/6 each. 3 for 15/-, post 2/6. 6 for 27/8, carr. 3/8.

D.C. SUPPLY KIT. 12 v. 1 a. consisting of partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains, etc. Limited number available at 33/9.

All for A.C. Mains 200-250 v., 50 ccs. Guaranteed 12 months.

BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grommets, panels and circuit. Carr. 3/6 extra.
 6 v. or 12 v. 1 amp. 24/9
 As above, with Ammeter 32/9
 6 v. or 12 v. 2 amps. 25/9
 6 v. or 12 v. 2 amps. inclusive of Ammeter 31/6
 6 v. or 12 v. 2 amps. inclusive of Ammeter 42/9
 6 v. or 12 v. 4 amps. 59/9
 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 59/9.
CHARGER AMMETERS.
 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a., 0-60 a., 8/9.

STANDARD JACK PLUGS. With 4ft. screened lead. 1/11 ea. 5 **CORED FLXS.** Rubber insulated. 14/26, 13 v. 50-50 yds. **TRANSISTORS.** Audio Type. 6/6; R.F. 12/6; Power type. 2 watts. V151DF. 17/9. Mullard OC71. 10/-, OC72. 16/9, X8102. X8104. 10/-, Most types at bargain prices. Diodes 0A81, GD3, 3/9.

REPARCO CONSTRUCTIONAL ENVELOPES AND PARTS IN STOCK. Parts for 3 Dee 3 Transistor Radio, £3-6-6. Mini-Seven 7 Transistor Pocket Portable, 10 Gns. **TURNOVER STEREO MONAURAL PICK-UP HEADS.** Acos. Suitable for normal 78, 45, or 33 1/3 r.p.m. records or for stereo type. Sapphire Stylus. Will fit Garrard B.S.R., Collaro and Star Galaxy Record Changers. Only 49/9.

be TRANSISTOR-WISE! be POCKET-WISE!



"RECO" MIDDY ONE

(Medium and Long Waves.) Size 4 1/2 x 3 1/4 x 3/4 in. Variable sensitivity control. High gain Vari Q Ferrite Rod Aerial. "Sonotone" Dynamic Earpiece. Months of listening pleasure from 1 1/2 volt pencil. Complete Kit with EDISWAN TRANSISTOR and easy build plans; 39/6, post free.

AMAZON THREE TRANSISTOR POCKET RADIO

Covers 100 to 500 metres and Short Waves. New improved, super sensitive 5-stage reflexed circuit. EDISWAN transistors. Pocket sized case 4 1/2 x 3 1/4 in. Ferrite rod aerial. Case body in black polystyrene with contrasting grille in red. Complete kit with easy build diagrams and "Sonotone" dynamic miniature earpiece with moulded insert, 72/6 p.p. 2/6. "The tonal quality and bass response is surprisingly good."—Midlands customer.

"RECO" PUSH - PULL FOUR TRANSISTOR KIT

(Medium and Long Waves with two Short Wave Coils FREE.) Case size as PP5. New improved circuit. 3in. High Grade Moving Coil Speaker. Bias sensitivity volume control. Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with 4 1st grade EDISWAN TRANSISTORS and 3 volt battery, £5.3.6, p.p. 2/6.



"RECO" PUSH-PULL FIVE TRANSISTOR KIT

(Size 6 1/2 x 4 1/2 x 1 1/2 in.) Medium, Long Waves and Trawler Band. Indoors or outdoors this brilliant radio brings Home and Continental Stations to your fingertips. High Grade 3in. Moving Coil Speaker. Regenerative receiver with EDISWAN TRANSISTORS, Push-Pull Output Stage, High Gain Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with Pencil battery and easy build diagrams, etc., £6.9.6; p.p. 2/6. A customer in Dorset writes—"Makes fine car radio."

"RECO" TRANSIGEN THREE TRANSISTOR KIT

(Case as PP5.) (Medium, Long Waves and Trawler Band.) Entirely self-contained, no external aerial required. Fitted Super High Gain Ferrite Rod Aerial, R.F. Stage, EDISWAN TRANSISTORS. On test: tuned in Home, Light, Third, Radio Luxembourg, A.F.N. and many others at good listening level. The Prototype was tested at approximately 50 miles from nearest transmitter. Complete Kit with Super B.A. Reprodacer and battery, 75/-, p.p. 2/6. Or with "Sonotone" super dynamic miniature earpiece. 79/6.



"RECO" INJECTOBOOST

Add an R.F. stage to your receiver; bring in those weak stations, improve selectivity. Complete kit with XA102 (list 26/9) regeneration control, switches, Plastic case, wiring diagram, etc. Simple—effective. 29/6, p.p. 1/6. (Not suitable for valve or superhet receivers.)

AFTER SALES SERVICE.


Circuits and price list for above kits, 2/6.

RADIO EXCHANGE CO. 27 HARPUR ST., BEDFORD. Telephone 2367
 Closed 1 o/c Saturdays.

KINGSMERE SUPPLIES LIMITED

Insured Post 1/-, over £2 Free. (Export extra.) MAIL ORDER HOUSE TERMS: Remit with Order or C.O.D.

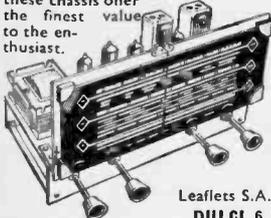Built to the highest specifications, these chassis offer the finest value to the enthusiast.



Leaflets S.A.E.

ALL BRITISH RADIOGRAM CHASSIS. 3 WAVEBANDS 5 MULLARD VALVES
ECH81, EF89, EBC81, EL84, EZ80
 Brand new and guar. A.C. 200/250 v. Short-Medium-Long-Gram. P.U. High Q dust core coils. Latest circuit technique. AVC and neg. feedback. 4 watts. Chassis size 13 1/2 x 6 x 7in. high. Aligned and calibrated ready for use. Quality at Low Cost. Chassis isolated. H.P. Dep. £5 and five monthly of £1.

OUR PRICE £9-9-0

DULCI 6 VALVE AM-FM MODEL £18-18-0

Matched Speakers, Sin., 6 1/2in., Bin. 17/6 ea. 10in. 25/-.



The Brilliantly Successful

Monarch

U.S.A. WORLD'S FINEST 4-SPEED AUTOCHANGER

IDEAL FOR USE WITH OUR CHASSIS
 H.P. Dep. £3.10.0 and four monthly of £1.

Stereo-monaural model £1 extra

BRAND NEW AND BOXED

OUR PRICE

£6-19-6

90-DAY GUARANTEE VALVES		ALL BRAND NEW	
6/6	7/6	1/6	5/6
5U4	6Q7G	954	1S5
6K8G	12AX7	EA50	1T4
6N7M	EF41	E1148	6K6GT
6V6G	EL41	6H6GT	807
6X5G	EL84	2/6	SP61
6AM6	EZ40	6K7G	6AC7M

SPECIAL PRICE PER SET

6K8G, 6K7G, 6Q7G, 6V6G, 6X5G ... 27/6
 1R5, 1T4, 1S5, 3V4 or 3S4 ... 27/6
 Matched Pairs 6V6G, 1S5, EL84, 17/6
 Valve Boxes, All Sizes ... 2/- doz.
 Carbon Pots. 5K to 2M, 2/6; DP, 4/-.

BSR 4-SPEED SINGLE PLAYER
 Model TU9. Our bargain price, 90/-.
 Cut out board, 12 1/2in. x 16 1/2in., 5/-.

ALFA MULTIMETER

Pocket size 5 1/2 x 3 3/8 x 1 1/2in.

300 microamp F.S.D. 3in. Scale.
 17 Ranges. 3,330 ohms per volt.
 A.C. Volts. 0 to 1,200 v. in 5 ranges.
 D.C. Volts. 0 to 1,200 v. in 5 ranges.
 D.C. Current. 0 to 300 m.a. in 3 ranges.
 Resistance. 0 to 20 K and 0 to 2 meg.
 Decibels. -20 to +23 db. and +20 to +37 db.

Complete with leads and prods. Uses No. 8 battery. Fully Guaranteed.

REDUCED PRICE £5-19-6

FAMOUS MAKE LONG PLAY PLASTIC RECORDING TAPE

On universal fitting plastic spools, for all recorders single and double track. 50% extra play at standard prices.
 7in. spool 1,700ft. tape, our price 35/-
 5 1/2 in. spool 1,200ft. tape, our price 28/-
 5in. spool 850ft. tape, our price 21/-
 MSS 3in. spool 225ft., price 7/6

STANDARD PLASTIC TAPE

7in. spool 1,200ft. tape, 21/-
 5in. spool 600ft. tape, 15/-
 Spare Plastic Reels. All sizes 3/- each.

FOAMCOURT WAYE, FERRING, WORTHING, SUSSEX

THE PEMBRIDGE COLLEGE OF ELECTRONICS offers training in RADIO TELEVISION AND ELECTRONICS

(a) Full-time One Year Course in Radio and Television. College course in basic principles for prospective servicing engineers.

The next course commences on 26th April, 1960, and enrolments are now being accepted. Following course commences on 6th September, 1960.

(b) Home-Study Courses in Radio, Television and Telecommunications Engineering up to City and Guilds Final Certificate. Some courses include constructional kits and practical exercises.

(c) Kits-of-parts with full constructional instructions.

For details of the above, write to:

The Principal, P.10,
THE PEMBRIDGE COLLEGE OF ELECTRONICS
 34a Hereford Road, London, W.2

RST

MAIL ORDER DEPARTMENT
 211 Streatham Road, Mitcham, Surrey.
ALL VALVES LISTED ARE NEW STOCK
 • Terms C.W.O. or C.O.D. Postage 3d. per valve.
MITCHAM 6201.


AC/TH1 34/9	ECC85 9/8	FW4.500	PY32 15/6	X78 21/-
AC/TP 32/6	ECF80 12/6	GZ30 10/6	PY80 8/6	X79 21/-
AZ1 15/6	ECF82 12/6	GZ32 11/6	PY81 7/6	Z77 5/-
AZ31 10/6	ECH3 12/6	GZ34 13/6	PY82 8/-	1A7 14/6
B36 21/-	ECH3 12/6	HABC80	PY83 8/6	1C1 9/-
C1C 8/6	ECH21 27/10	HF93 10/-	PZ30 18/6	1C2 9/6
CBL31 21/-	ECH21 22/-	HK90 9/-	SP41 3/6	1N5GT 10/6
CCH35 14/6	ECH35 9/-	HL41DD 13/6	(Ex. Gov.)	1P11 9/-
CL33 18/6	ECH42 10/-	HL133DD 10/-	(Ex. Gov.)	1R5 9/-
CY1 15/9	ECH81 9/6	HY90 10/-	TH4B 27/6	1S4 9/6
CY31 15/9	ECH83 9/6	1W1350 10/-	TY66F 18/6	1S5 9/-
D41 12/6	ECL80 9/-	1W4.500 10/-	U10 12/6	3Q4 8/-
D77 6/-	ECL82 12/6	ECL83 15/-	U14 15/9	3V5GT 10/6
DAC32 10/6	EF3 21/-	EF37A 8/6	U18/20 3V4 9/-	5U4 7/-
DAF91 7/6	EF37A 8/6	EF39 5/-	U24 29/6	5V4G 9/6
DAF96 9/6	EF39 5/-	EF40 15/-	U25 18/6	5Y9GT 8/6
DF33 10/6	EF40 15/-	EF41 9/8	U26 12/6	5Z4 10/-
DF91 5/-	EF41 9/8	EF42 10/6	U52 7/-	6A7G 18/6
DF92 7/-	EF42 10/6	EF50A 4/6	U78 7/-	6AM6 5/-
DF96 9/6	EF50A 4/6	EF59 E 4/6	U79 20/-	6BW7 6/6
DH77 8/3	EF59 E 4/6	EF83 7/-	U83 11/6	6BX6 7/-
DK32 21/-	EF83 7/-	EF85 7/-	U709 5 pin 17/6	6D2 5/-
DK91 9/-	EF85 7/-	EF86 11/-	U801 29/-	6F12 5/-
DK92 9/6	EF86 11/-	EF89 10/-	UABC80 6/6	6J5GT 4/6
DK96 10/6	EF89 10/-	EF91 5/-	UAF42 8/6	6J7GT 9/6
DL33 9/-	EF91 5/-	EF92 5/-	UB41 9/6	6K7C 4/-
DL35 12/6	EF92 5/-	EF93 7/6	UB42 9/6	6K9G 7/6
DL91 9/6	EF93 7/6	EF95 15/-	UBC41 9/6	6Q7G 8/-
DL93 8/6	EF95 15/-	EF98 10/-	UBC81 10/-	6SL7GT 8/6
DL94 9/-	EF98 10/-	EL33 18/6	UBF90 9/6	6SN7GT 5/6
DL96 9/6	EL33 18/6	EL37 18/6	UBF89 8/6	6U4GT 11/6
DW4/500 12/6	EL37 18/6	EL38 23/9	UCC84 18/6	6V6G 5/-
EABC80 7/6	EL38 23/9	EL42 10/6	UCC85 10/-	7B7 8/-
EAF42 10/6	EL42 10/6	EL41 14/9	UCF80 18/6	7C5 8/-
EB41 7/6	EL41 14/9	EL84 7/-	UCH21 21/-	7C6 8/-
EB91 5/-	EL84 7/-	EL90 8/6	UCH21 21/-	7S7 10/6
EBC33 5/-	EL90 8/6	EM34 10/-	UCH42 9/-	7Y4 7/6
EBC41 9/6	EM34 10/-	EM80 10/-	UCH31 9/-	12A1H8 10/-
EBC81 10/6	EM80 10/-	EM81 10/-	UCL82 12/6	12AT7 8/-
EBC90 8/3	EM81 10/-	EM85 12/6	UCL82 12/6	12AU7 9/-
EBF80 9/6	EM85 12/6	EM85 12/6	UCL82 12/6	12AX7 9/6
EBF83 9/6	EM85 12/6	EM85 12/6	UCL82 12/6	12BH7 15/-
EBF89 9/-	EY51 9/-	EY83 14/6	UCL82 12/6	25A6 12/6
EBL21 22/6	EY83 14/6	EZ35 7/-	UCL82 12/6	25L6GT 10/6
EBL31 21/6	EZ35 7/-	EZ40 7/6	UCL82 12/6	25Z4G 9/6
ECC34 15/6	EZ40 7/6	EZ41 7/6	UCL82 12/6	25Z5 9/6
ECC40 21/-	EZ41 7/6	EZ80 7/6	UCL82 12/6	25Z6GT 10/6
ECC81 8/-	EZ80 7/6	EZ81 7/6	UCL82 12/6	35L6GT 15/-
ECC82 9/6	EZ81 7/6	EZ90 7/6	UCL82 12/6	35W4 8/-
ECC83 9/6	FC2 21/-	FC2A 21/9	UCL82 12/6	40SUA 15/-
ECC84 9/6	FC2A 21/9	FC2B 21/9	UCL82 12/6	50CD6G 21/-
	FC2B 21/9	FC2C 21/9	UCL82 12/6	50L6 9/-
	FC2C 21/9	FC2D 21/9	UCL82 12/6	813 50/-

RECTIFIERS

RM1 6/-	RM4B 18/6	DRM2B 14/6	14A97 23/6	(14RA1-2-8-3)
RM2 8/-	RM5 22/-	DRM3B 21/-	14A100 24/-	FC101 18/8-2)
RM3 9/-	DRM1B 12/6	14A96 17/-	FC31 21/-	(14RA1-2-8-2)
RM4 16/6				

SEND FOR LISTS. Quotations given for any types not listed. Obsolete and old types a speciality.

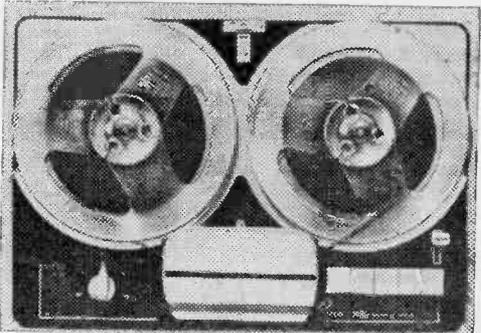the NEW Patents pending
MOTTEK K10
 ★ ★ ★ ★ ★
TAPE DECK



Incorporating many new features and a greater frequency response.

Look



Now restyled in two tones of grey—you must see the new, attractive Mottek K.10.

★ Frequency response better than 40 c/s-12,000 c/s at 7.5" per sec. with extremely low hum pick-up.

★ Enlarged drive wheel on the rev. counter ensures accurate tape positioning.

MOTTEK

makes a better Recorder

21GNS

MODERN TECHNIQUES

Wedmore St., London, N.19. Tel: ARChway 3114.
 Please send for brochure of K.10.

JUST RELEASED
REPANCO TRANSISTOR AMPLIFIER
 AND
FEEDER UNIT CIRCUITS

Envelope of theoretical and practical layout diagrams or 350/500 milliwatt Transistor Amplifier.
 Simple T.R.F. Band Pass Feeder Unit.
 Medium wave T.R.F. Feeder Unit with R.F. Stage.
 Medium and Long wave Unit with R.F. Stage.
 Medium and Long wave Superhet Feeder Unit.
 Microphone Preamplifier.

Send now 2/- (post free) for envelope.

RADIO EXPERIMENTAL PRODUCTS LTD.
 33, MUCH PARK STREET, COVENTRY

REPANCO

EASY-TO-BUILD RECEIVERS

	Envelope
The R.E.P. One-valve Radio	9d.
The Hiwayman. A 4-valve Portable Radio	1/6
F.M. Tuner Unit. 5 Valves plus Tuning Indicator	1/6
Three Dec. 3-transistor Radio	9d
Mini-3, 3-transistor Pocket Radio	1/3
Mini-7, Mk. II. 7-transistor Pocket Receiver	1/6
Transveen. 7-transistor Portable Receiver	1/6
Major-7. 7-transistor Portable Receiver	1/6
Transistor Car Radio Receiver	2/-
Transistor Amplifier and Feeder Unit Circuits	1/6

Please add towards postage.

COMPONENTS

COILS: DRX1, DRR2, DRM3, SH4, "R," X08, X015, F.M., XLI, XMA16, XMF17, XLA18, XLF19.
AERIALS: FRI, FS2, FS3, FS4.
I.F.T.'S.: MSE, TCG, SE, OT1, TT2, TT3, XT6, XT7.
TRANSFORMERS: MOT1, TT4, TT5, TT9, TT10, TT11, TT12, TT13, TT14, TT20, TT21, TT22, TT23, TT24, TT25.

For details of these and other Components send 6d. in stamps for our 1960 Catalogue.

Mail Order and Trade
RADIO EXPERIMENTAL PRODUCTS, LTD.
 33 Much Park St.,
 COVENTRY
 Tel.: 62572

Wholesale Enquiries and Exports:
REPANCO, LTD.
 O'Brien's Buildings,
 203-269 Foleshill Rd.,
 COVENTRY
 Tel.: 40594

G2AK: This Month's Bargains

VARIABLE CONDENSERS

All Brass with Ceramic End Plates and Ball Race Bearings. 50 pf., 5/9; 100 pf., 6/6; 160 pf., 7/6; 250 pf., 8/6 and 300 pf., 9/6. P. & P. 1/6. Designed for the S.W. constructor.

REPANCO MINIATURE COMPONENTS

Full Range in Stock.

TRANSMITTER/RECEIVER AN/PPN-2. Frequency 214/234 Mc/s. Complete in carrying pack, with 9 valves (5-3A5, 3-155, 1-1R5).

DUAL VIBRATOR PACKS (2 v.), HS 30 'PHONES and ANTENNA. full instruction book, £3.19.6, carr. 7/6.

HEADPHONES H.R. TYPE. 4,000 ohms, very sensitive. **ONLY 12/6** pr. P. & P. 1/6. C.L.R. Type (low res.), 8/6. P. & P. 1/6.

ABSORPTION WAVEMETERS. 300 to 3,500 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. **ONLY 19/6**, post: free.

2 METER 5 ELEMENT BEAM, W.S. Yagi, complete in box with 1"-2 1/2" masthead bracket. **PRICE 49/-**. P. & P. 3/6.

SUPER LOW LOSS AERIAL CABLE, 1/8 yd. P. & P. 1/6.

ROTARY CONVERTERS. 6 v. input, 250 v., 125 mA output. **ONLY 17/6**. P. & P. 3/-.

CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS

Dept. "P," 110, Dale End, Birmingham, 4. (CEN 1635)
 (No C.O.D. under £1 please.) (By return Service.)

VALVES

SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS	1R5 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any DAF96, DF96, DK96, DL96 6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G	4 for 25/-	4 for 31/6	5 for 27/-
------	--------------------------------------------------------------------------------------------------------------------------------	------------	------------	------------

1A7GT 12/-	8L1 16/9	25Z4G 9/-	EBC41 8/6	EY86 8/3	PZ30 17/-
1D5 9/6	8L18 12/3	25Z6GT 9/6	EBF80 9/-	EZ40 6/9	SP61 3/6
1HG5T 10/-	6P25 7/6	30C1 8/6	EBF89 8/9	EZ41 7/8	T41 15/6
1NSGT 10/-	6Q7G 9/6	30L1 8/-	EEL21 20/6	EZ80 6/3	U25 12/-
1R5 6/9	6Q7GT 9/6	35LGT 10/-	EC92 11/-	EZ81 7/-	U50 7/6
1S4 8/-	6S17GT 8/6	35Z4GT 9/6	ECC81 5/9	FW4/500 3/-	U52 5/3
1S5 6/3	6SN7GT 4/9	35Z5GT 9/6	ECC82 6/6	G232 9/-	U76 6/6
1T4 5/3	6U4GT 11/-	43 12/6	ECC83 7/-	K733C 7/-	U78 6/9
1U5 6/6	6V6G 5/6	50CD6G 26/9	ECC84 8/9	K741 14/6	UAB80 8/6
3A5 10/6	6V6GT 7/6	50L6GT 9/-	ECC85 9/8	K761 10/-	UAF42 9/6
3Q4 8/6	6X4 8/6	AZ31 8/6	ECF80 11/6	K783 6/6	UBC41 7/9
354 6/9	6X5GT 6/-	B36 8/9	ECF82 10/-	K771 12/6	UBF80 9/6
3V4 7/8	7B7 8/-	CL33 13/9	ECH21 20/6	MH4 6/-	UBF89 8/6
5U4G 5/3	7C5 8/-	DAC32 10/-	ECH35 6/9	MU14 8/8	UBL21 20/6
5V4G 7/3	7C6 8/-	DAF81 6/3	ECH42 9/6	MX30 12/6	UC84 12/9
5Y3GT 10/8	7H7 8/6	DAF86 10/6	ECH81 8/6	N18 8/6	UCC85 8/-
5Z4G 9/6	757 9/9	DCC90 10/6	ECL80 8/6	PCC84 8/-	UCF80 14/-
6A15 3/9	7Y4 8/-	DF33 10/-	ECL82 10/-	PCC89 14/-	UCH21 20/6
6AM5 5/-	10C1 14/6	DF91 5/3	EF39 5/6	PCF80 8/-	UCH42 9/-
6AM6 3/9	10C2 17/6	DF96 8/6	EF41 9/6	PCF82 9/3	UCR81 8/6
6AQ5 7/-	10F1 15/6	DH76 6/6	EF42 11/8	PCL82 9/-	UCL82 11/6
6AT6 7/3	12A8H 10/6	DH77 7/3	EF80 8/6	PCL83 11/9	UCL83 13/3
6BA6 6/6	12A7 9/9	DK32 12/-	EF85 6/9	PCL84 8/-	UF41 9/3
6BE8 8/-	12AUG 7/6	DK40 14/-	EF86 11/-	PEN44 11/-	UF42 8/6
6BH6 6/9	12AU7 6/6	DK91 6/9	EF89 8/9	PEN36C 9/6	UF89 7/6
6BJ6 6/-	12AX7 7/-	DK92 8/6	EF91 8/-	PEN45 8/-	UL41 8/-
6BR7 10/6	12BA6 8/-	DK96 8/6	EF92 4/6	PEN46 5/6	UL84 8/-
6BW6 10/6	12BGT 5/8	DL33 9/-	EL38 10/-	PL36 13/-	UR1C 8/-
6BW7 6/6	12K8GT 11/6	DL35 11/6	EL38 21/6	PL38 14/6	UY21 14/-
6CD6G 26/9	12Q7GT 5/8	DL92 6/6	EL41 9/-	PL81 10/-	UY41 9/6
6F1 14/6	12Z3 7/6	DL94 7/6	EL42 10/6	PL82 7/8	UY86 6/9
6F6G 6/6	14S7 18/9	DL96 8/6	FL84 8/-	PL83 8/8	VP4B 9/6
6F13 12/8	18AQ5 7/6	EACB90 8/9	EM34 8/6	PY32 12/-	VP41 6/-
6F14 17/8	20F2 17/8	EAC91 6/9	EM80 9/-	PF80 7/6	W76 6/6
6K7G 3/9	20L1 17/6	EAF42 9/6	EM81 9/-	PY81 6/9	W77 4/6
6K7GT 6/-	25A8G 6/-	EB91 3/9	EM84 10/-	PY82 7/-	X78M 11/6
6K8G 6/9	25L6GT 9/6	EBC33 7/-	EY51 9/3	PY83 8/-	Z77 3/9

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

FIRST-CLASS RADIO COURSES...

GET A CERTIFICATE!
 QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A. M. I. Mech. E., Draughtsmanship (all branches)** etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES.

NATIONAL INSTITUTE OF ENGINEERING
 (Dept. 461), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Johannesburg.
 Australia: P.O. Box 4570, Melbourne

Post 6d. per valve extra.
 Any Parcel Insured Against Damage in Transit 6d. extra.
 Any C.O.D. Parcel 2/9 extra.

Modernise Your Radiogram with an *Armstrong Chassis*



STEREO 44 (illustrated) **27 GNS.**

8 watts output, 4 each channel ● Full VHF band and medium wave ● Stereo and monaural inputs for all crystal pick-ups, tape record and playback ● Separate bass and treble controls ● Mullard EL84 output valves ● Dual volume control for stereo balance.

AF 208 **22 GNS.**

5 watts output ● Full VHF band (87-108 mc/s) and medium wave ● Switched inputs for different crystal pick-ups ● Inputs for tape record and playback ● Separate bass and treble controls ● Dimensions (as for Stereo 44) 12in. x 8in. x 7in. high.

It is not at all difficult to fit a new chassis into an old radiogram or even to build a completely new radiogram into the cabinet of your choice. Why bother? Well, it's less expensive than all but the cheapest commercial radiograms and you get incomparably better quality into the bargain. Aren't those two splendid reasons? It's cheaper AND it's better.

The name **ARMSTRONG** is the registered trade mark of **ARMSTRONG WIRELESS & TELEVISION Co. Ltd.** WALTERS ROAD, LONDON, N.7 Tel.: NOR 3213

Post this coupon or write for descriptive literature or call at our Holloway Showroom for full, unhurried demonstration and professional advice on your installation. Open 9-6 weekdays and 9-5 Saturdays.

NAME

ADDRESS

PMC

LYONS RADIO LTD.

Dept. M.P., 3, GOLDHAWK ROAD, SHEPHERD'S BUSH, LONDON, W.12

Telephone: SHEpherd's Bush 1729

TRANSISTOR RADIO RECEIVERS. Circuit, Germanium diode D12 transistor stage of amplification, permeability tuned with ferrite rod covering medium and long wave transmissions. Requires aerial and earth system, short indoor aerial sufficient in most areas. Uses pen-light battery, amazingly low consumption (0.2 mA.), lasts for months. Suitable for use with high or medium impedance earphones. Finished in attractive plastic case. **PRICE ONLY 32 6.** post 1/6. Extras if required. Double headphones 7/6. Single earpiece 3/9. Battery 6d., post free with Rx.

POWER UNITS TYPE 325. As fitted in many types of Marconi Test Instruments. Chassis 7 1/2 in. long by 4 1/2 in., extends from back of front panel which is 10 x 5 in. Fitted with fuse holders, on/off switch, pilot light holder, etc. Input 200-250 v. 50 cps. A.C. mains. Output approx. 220 v. D.C. (un-smoothed) at 75 mA., 6.3 v. A.C. at 3 1/2 A., and 4 v. at 2 A. (for standard 4 v. rectifier valve MU12 or equiv.). **PRICE ONLY 35/-** (mint condition) or 17 6 (Good Condition). Rectifier valve, 8/6. Post 3/6. Smoothing easily added, details supplied if requested.

PRINTED CIRCUIT KITS. For etching your own, these Kits contain over 60 sq. in. of laminated board and sufficient chemicals to make dozens of printed circuits. The comprehensive instruction book supplied contains advice and examples on translating theoretical circuits into practical layouts for etching. **PRICE ONLY 19/6.** post 1/6.

IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE



PRICE **30/-**

Post, packing,

& ins. 2/6.

C.W.O. C.O.D.

● **NO SOLDERING**
● **NO WIRING** ● **JUST PLUG IN** ● **IT'S AUTOMATIC** ● **IT'S GUARANTEED!**
We can offer these units for any make of set. **IMPORTANT.** State name, address, & make and model no. of set. & tube in block caps.

SINCLAIR ELECTRONICS,
Dept. P.W., 33, BERWICK ST., W.1.
Callers Welcome—Trade Enquiries Invited.

WORLD RADIO HANDBOOK 1960

By Hans Johansen, 15/6, postage 1/-. Stereo a new book by Briggs, 10/6, postage 1/-.
Practical Transistor Receivers, Book 2. by Sinclair, 7/6, postage 3d.

Servicing Transistor Receivers, by Pettit, 6/-, postage 6d.

Mullard Circuits for Audio Amplifiers, 8/6, postage 10d.

Amateur Radio Call Book, 1960, by R.S.G.B., 3/6, postage 6d.

Stereo and Hi-Fi as a Pastime, by Gardner, 15/-, postage 1/-.
The Oscilloscope Book, by Bradley, 5/-, postage 6d.

Short Wave Receivers, for the Beginner, by Data, 6/-, postage 6d.

Trimar Valve and T.V. Tube Manual, No. 8, 6/-, postage 8d.


UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2.

(adjoining Lisle Street)

CABINETS & HI-FI EQUIPMENT

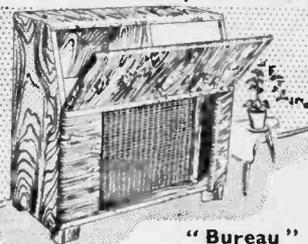We can supply any Cabinet to your own specification.



"Bureau"
£16.16.0

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on:

THE LARGEST RANGE OF CABINETS IN THE COUNTRY.

Equipment is also our speciality and we now offer, in a novel book form: **A NEW EQUIPMENT COMPARATOR** illustrating our range of radio chassis, speakers, tape decks, single players and autochangers.

SEND TODAY for a copy of these two books, which are absolutely FREE.

LEWIS radio

120 (PW360) Green Lanes, Palmers Green London, N.13. BOWes Park 1155/8 (Nr. The Cock Tavern)

SOLDERING EQUIPMENT

BY



PRECISION SOLDERING INSTRUMENTS for the ELECTRONICS INDUSTRY

- Comprehensive range
- Robust & Reliable
- Light weight!
- Rapid heating
- Bit sizes 3/32in. to 3/8in.
- 'Permagit' or Copper bits
- All voltage ranges 6/7v. to 230/250v.
- Prices from 19/6

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield. British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.10 sent free on request. Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS LIMITED

28, Sydenham Road, Croydon, Surrey.

Phone: CROYdon 8589 Grams: Litesold Croydon



EXPRESS ELECTRONICS ROSEDENE LABORATORIES KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW, TESTED AND GUARANTEED REDUCED PRICES

1C1 7/8	6BW6 7/6	16A3 9/-	EBD41 10/-	N18 8/-
1C3 8/-	6BW7 7/-	25A6G 10/5	EBP80 8/8	N19 7/6
1F1 8/-	6C10 9/-	25L6GT 9/-	EC81 7/6	PC84 9/-
1F3 7/6	6D2 5/8	25Z4G 8/-	EC82 7/6	PCF80 10/6
1FD1 8/-	6P12 4/8	30C1 8/-	EC83 7/6	PCF82 10/6
1FD9 7/6	6J7 8/6	30L1 8/-	EC84 9/8	PCL82 9/8
1L4 8/9	6K70 5/6	35L6GT 9/-	ECF80 10/8	PL48 22/6
1P1 8/-	6K80 7/8	35W4 8/8	ECF82 10/6	PL81 12/-
1P10 7/8	6L6 10/6	35Z4GT 8/-	ECH82 9/-	PL82 9/-
1P11 7/8	6Q7 7/8	43K1 11/6	ECH81 10/-	PY81 8/6
1R5 7/8	68L7GT 7/6	5783 9/6	ECL80 10/8	PY82 7/6
1R5 7/8	68N7GT 5/-	DAF91 7/6	EF41 9/-	R19 12/6
1T4 7/8	6V6G 7/8	DAF96 8/-	EF80 8/6	U92 7/6
1U5 6/-	6X4 7/-	DF91 7/6	EF96 11/-	U78 7/6
2Q4 8/-	6X5GT 6/-	DF96 8/-	EP91 4/8	U78 7/6
2S4 7/6	803 4/6	DH76 7/6	EP92 5/6	UB41 8/6
3V4 7/6	12A8H 10/6	DH77 7/-	EL88 22/6	UC42 9/8
3U4G 7/8	12AT6 8/6	DH142 8/6	EL41 9/8	UF41 8/8
5Y3GT 7/8	12AT7 7/8	DH150 10/-	EL84 8/6	UF41 8/8
5Z4G 8/6	12AU7 7/6	DK91 7/6	EY41 10/8	UY41 7/8
6AL5 5/8	12AX7 7/8	DK92 9/-	EZ40 7/6	W142 8/6
6AM6 4/6	12RH7 14/6	DK96 8/-	EZ80 7/6	X17 7/6
6AT6 7/6	12V7GT 10/-	DL92 7/8	EZ81 8/-	X152 9/-
6BA6 7/8	12K7GT 6/8	DL94 7/6	EZ81 8/-	XT50 9/6
6BE6 7/8	12K8GT 12/6	D486 8/-	KT66 11/6	Z77 4/6
6BR7 9/6	EAD90 8/6	EB91 5/6	N17 7/8	ZD17 7/6
6BS7 10/8	19Q7GT 7/8			

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES D.P. switch. 3/9; S.P. 3/3; Less switch. 2/6. Values 10K to 2M. Pre set 2/6.

MATCHED PAIRS

EL84 21/-, 6V6G 17/-, KT66 27/6, 6LW6 18/- per pair. Push Pull O.P. Transformers for above 3-45Ω 1/6, 12" P.M. speakers 3/9 21/6.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94.....	23/6
DK96, DF96, DAF96, DL96.....	32/-
1C3, 1P1, 1F1, 1P10.....	32/-
1R5, 1T4, 1S5, 2S4, or 3V4.....	23/6
6K8, 6K7, 6Q7, 6V6, 3Z4G or 6X50.....	27/6

Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

HIGH GAIN TRANSISTORS

BRAND NEW AND GUARANTEED Red/Yell. (6 mc/s). 8/6. White Spt. (4 mc/s). 7/6. Yell./Grn.. 6/6 (Matched pr. 250 mW), 13/6. Red Spt., 6/6.

MINIATURE AMPLIFIER

3-stage 4 TRANSISTORS. p.p. output, 250 mW, for 2-3 ohm speaker. Ideal for Gram., Radio, etc. High gain. Excellent quality, uses small 6 v. batt. Easy assembly. Full kit, matched Ediswan Transistors, complete instructions. Brand New Components, 59/6. p. & p. 1/6. Circuit diagram assembly details. 2/6.

SUB-MIN. ELECTROLYTICS, 2, 4, 8, 25, 50, 100 mfd., 15 vv., 2/9.

MIDGET RESISTORS, 3/4 wt. Approved values, 3 1/2 d.

MIDGET VOL. CONTROLS. Standard values, 2/10. With S.P. switch, 4/-.

MIDGET ACCUMULATORS. About 1 1/2 in. x 1 in. x 1 1/2 in., 2/6, p.p. 1/-; 5 1/2 in. x 3 1/2 in. x 1 1/2 in., 3/3, p.p. 1/-; 7 1/2 in. x 3 1/2 in. x 1 1/2 in., 4/9, p.p. 1/3.

PLASTIC BOXES with hinged lids: 4 1/2 in. x 3 in. x 1 1/2 in., 2/6, p.p. 1/-; 5 1/2 in. x 3 1/2 in. x 1 1/2 in., 3/3, p.p. 1/-; 7 1/2 in. x 3 1/2 in. x 1 1/2 in., 4/9, p.p. 1/3.

PERSPEX. 6 in. x 3 in. x 1/2 in. Ivory. 1/-, p.p. 6d.

LOUDSPEAKERS. Perm. mag. 2 1/2 in., 19/6.

Please include sufficient postage when ordering. Send 3d. stamp for list of New Components.

BURLAND RADIO ACCESSORIES

Est. 1947 G3JZ ANN'S PLACE, SOUTHWICK, SUSSEX

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (BAND 1). Tele-scopic loft, 19/6. External, S/D. 26/3.

I.T.V. (BAND 3). 3 Element loft array, 24/-; 5 Element, 32/8. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H" 28/-. 3 Element loft, 52/6. S/D loft, 12/8. External S/D 28/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.) 3B, Godstone Road, Kenley, Surrey

Quality Components FOR CONSTRUCTORS

capacitors, resistors, coils, valves, diodes, controls, chassis, transformers, speakers, pickups, cartridges, styli and all types of components in stock.

52 Page Catalogue Available on Request J. T. FILMER 82 Dartford Road, Dartford, Kent Tel. Dartford 4057

Morse Code operating . . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans and full details of all Courses. CANDLER SYSTEM CO. Dept. 5LO 20, Abchurch Lane, London, W.3. Candler System Co., Denver, Colorado, U.S.A.

H.A.C. SHORT-WAVE EQUIPMENT

AND SHORT WAVE KITS

Famous for over 25 years for S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-wave Kit, Model "C." Price 25/- Two-wave Kit, Model "E." Price 50/- New Addition: Model "K." Super sensitive "All Dry" Receiver. Special incl. price. Complete Kit. 77/-

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.

Please send me FREE and without obligation your 1960 literature.

NAME

ADDRESS

**Get these
FREE
CIRCUITS
&
WIRING DIAGRAMS**

T.R.F. Circuits
Battery Circuits
Portable Circuits
S'het Circuits
Mains Circuits
Filter Circuits
F.M. Tuner

Single Valve F.M. Tuner.
2 Valve F.M. Complete Set.
Same on Printed Circuit, etc., etc.

Send Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

"Q Coils"
All ranges
Potted Coils
F.M. COILS
Speaker Cross-over Coils
ROD AERIALS
Circuits
Coils and I.F.s
for Transistor
SUB-MINIATURE COILS
Midget I.F. Trans.
With ferrite cores



418 Brighton Road,
South Croydon.

Telephone: CRO 5148/9



**Solve
that
Circuit
trouble!**

PIFCO
Radiometer

Not only circuit tests but everything electrical can be tested with this handy compact meter. Tests H.T. & L.T., Valves, components, electrical appliances and car lighting systems, etc. May be used on A.C. & D.C. mains.

See the Radiometer at your dealer or write for illustrated leaflet to:—

only
32/6
complete

PIFCO LTD.
WATLING STREET · MANCHESTER · 4.

Special Bargain Offers

AVOMETER MODEL 'D' 34 range testmeter. D.C. volts to 1,500 v. (10 ranges). A.C. volts to 1,500 v. (8 ranges). D.C. current to 30 A (8 ranges). A.C. current to 15 A (8 ranges). Ohms 0-1 k. 0-10 k. A robust instrument with 5in. mirror scale and cut out. With battery and leads. Guar. £9.19.6. Post 3/6.

FERRANTI TESTMETER TYPE Q. An extremely compact self-contained multimeter. Volts 0 to 30, 150, 600 AC/DC with additional 0.3 v. DC and 0-15 v. AC ranges; milliamperes 0 to 7.5, 30, 150 and 750 DC; ohms 0-25 KΩ. Accuracy BSS first grade. Knife-edge pointer and clearly calibrated 2 1/2 in. scale. 500 Ω/volt. With leads, prods. battery and instructions. In fitted velvet-lined 4 x 7 x 3 1/2 in. case. Brand new condition. Tested, 52/6, post 2/6.

ADVANCE SIGNAL GENERATORS. Type 20. Ex-Govt. These fine instruments cover 100 Kc/s to 30 Mc/s in 6 bands. Mod. R.F. C.W. and 400 cps audio outputs are provided. Individual charts are missing but guidance charts will be provided. A.C. Mains. Not new but in good cond. & wkg. order. As only a limited no are available **CALIFERS ONLY.** £5-10-0.

65'er. (BC-453 Command Receiver). Covers 190-550 Kc/s (1F 85 Kc/s). Ideal for double superhet conversion, etc. Supplied BRAND NEW in original cartons, with all 6 valves and CIRCUIT, 89/6. Post 3/6.

R-1155-B, with latest drive, first-class condition, £7.19.6.
R-1155-L, £12.19.6. Power Packs, £6.10.0. S.A.E. details.
CR100 COMMUNICATION RECEIVERS. Covers 60 Kc/s—30 Mc/s in 6 bands. 11 valves, 2 R.F. and 3 I.F. stages. Crystal rate. BFO, etc. Ready for 200-250 v. A.C. mains 2 1/2 watts output for 3 ohms speaker. **SUPERB CONDITION AND OUTSTANDING PERFORMANCE for ONLY £21.** S.A.E. for illustrated details.
HRO COMMUNICATION RECEIVERS. complete with 9 coils. From 18 gns. S.A.E. for full particulars.

BCA AR-88 SPEAKERS. 3Ω 8in. P.M. speaker in heavy gauge black cracked steel cabinet 11 x 10 x 6in. with rubber feet. A SUPER QUALITY unit. BRAND NEW, for ONLY 45/- Post 3/6.

MINIATURE 373 I.F. STRIPS.—For F.M. tuner described in P.W. With 3 of EF91, 2 of EF92 and EB91. A fresh release enables us to offer these once again. BRAND NEW with circuit and full P.W. Reprint, 35/- OR less valves, 12/6. Post either, 2/6.

MOVING COIL PHONES.—Finest quality Canadian, with Chamois ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable. 19/6, post 1/6.
R.F. UNITS. R.F.26, 17/6; R.F.27, 22/6. Good condition. Post each 3/6.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS
CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martin's Lane, London, W.C.2

TEMPle Bar 0545

Shop Hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday.

**A television course
for you to study at home**

*Entirely new! Practical!
Bang up to date!*

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all that you need to know!

This is what you've been looking for! A home-study course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The IV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost little, the book you need is included in the cost.

—TO THE BENNETT COLLEGE (Dept. C104TV Sheffield)

Please send me details of the new TELEVISION SERVICING COURSE

NAME _____

ADDRESS _____

AGE _____

VALVES

INDIVIDUALLY BOXED, BRAND NEW, FACTORY TESTED

FULLY GUARANTEED

Selection of our stocks of hundreds of types

MAIL ORDER SERVICE ONLY

1A3	3/-	6F8G	8/-	12K8	8/6	EL41	7/6
1A5GT	6/-	6F32	8/6	12SC7	7/6	EL84	7/-
1E7G	6/6	6H6M	3/6	12SG7	7/6	EL95	8/-
1L4	5/-	6J5G	4/6	12SH7	7/6	EM80	8/-
1LD5	4/3	6J5GT	5/-	12SJ7	7/6	EM81	8/-
1S5	5/-	6J6	4/9	12SK7	7/6	EZ40	6/-
1T4	4/-	6J7G	5/-	25A6G	8/6	EZ80	5/3
2A7	9/-	6K7G	4/-	25Y5	8/6	KT33C	6/-
2X4	4/-	6K7M	5/9	25Z6G	7/-	KT44	12/6
3A4	6/-	6L7	7/6	DAF91	5/-	KTW61	6/-
3V4	7/-	6Q7G	6/-	DAF96	7/-	MHLD6	10/-
5U4G	5/-	6SA7	7/-	DF91	4/6	OZ4	9/6
5Z4	7/6	6SC7GT	6/6	DK96	7/6	OZ4A	10/-
6AB7	7/-	6SG7	5/-	DH76	5/6	PCC84	6/9
6AC7	5/6	6SH7	6/6	DL94	6/6	PCF80	6/9
6AG5	5/6	6SJ7	5/6	DL96	7/-	PL81	9/3
6AJ7	5/-	6SJ7M	5/6	EABC80	6/6	UAF42	8/-
6AK5	7/-	6SL7GT	7/-	EAF42	7/6	UBC41	7/-
6AM6	3/-	6SN7GT	6/-	EBF80	7/6	UL84	7/-
6B7	8/-	6V6G	5/-	ECC85	7/6	UY85	5/9
6BP6	3/6	6X5G	5/-	ECH81	7/3	VR105/30	
6C4	6/-	7B7	6/6	ECL82	5/-	VR150/307	7/-
6C6	5/6	7S7	9/6	EF50	5/-	W76	8/-
6D6	6/-	12A6	6/-	EF80	5/6	X24	8/-
6F6G	5/-	12J5GT	7/-	EF91	3/6		

WESTMINSTER TECHNICAL SUPPLIES,
20/21, LAWRENCE LANE, LONDON, E.C.2.

Telephone : WAT. 2111.

Terms : Cash with Order or C.O.D.

Add Post & Packing 6d. per Valve, Plus 2/6 per parcel C.O.D.



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free 15/- per pair.

AVO LTD AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
Victoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

NEW 1960 EDITION

WORLD RADIO HANDBOOK

for listeners

15/6

Postage 1/-

by O. L. Johansen

VADE-MECUM, 1959. By P. H. Brans. 38/-, Postage 2/-.

HOW TO INSTALL AND SERVICE AUTO RADIOS. By J. Darr. 26/-, Postage 1/-.

STEREO HANDBOOK. By G. A. Briggs. 10/6, Postage 1/-.

TAPE RECORDING AND HI-FI YEARBOOK, 1959-60. 6/-, Postage 1/-.

RAPID RADIO REPAIR. By G. W. Heath. 23/-, Postage 1/-.

A GUIDE TO AMATEUR RADIO. An RSGB Pub. 3/6, Postage 6d.

RADIO VALVE DATA, 6th Ed. Compiled "WW." 5/-, Postage 9d.

NEW 1960 CATALOGUE, 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2.

Phone : PADdington 4185. Open 6 days 9-6 p.m.

ASTRAL RADIO PRODUCTS

'HOME RADIO.' 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valvers. 2/-, post 3d.
TRF COILS. 7/-, pr., post 6d. **DEAL WAVE HF** 4/- with REACTION.
Specified for 'Summer All Dry Portable', 'A.C. Double Triode 1', etc., 4/6, post 3d.
IFTs Miniature, 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q'. Special offer, 9/-, pr., post 6d. Crystal Set Coils, L. & M.W. 2/8, post 3d.

82 Centurion Road, Brighton

TRANSISTOR SPECIALISTS

OUR NOTES WILL HELP THE BEGINNER AND MANY OTHERS

If you have been disappointed with Transistor circuits try the Morco Reflex Circuit.

This and other simple circuits are described in our notes sent to anyone sending 8d. in stamps to

MORCO EXPERIMENTAL SUPPLIES

8 and 10, Granville Street, Sheffield, 2

Tel. 27461

NEW VALVES !

Guaranteed Set Tested 24 HOUR SERVICE

1R5, 1S5, 1T4, 3A4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, SET of 4, 24/6. DAF96, DF96, DK96, DL96, SET of 4, 31/-.

1D5	9/-	DL33	9/-	PCF82	9/-
1R5	6/6	DL35	10/6	PCL82	9/-
1S5	6/-	DL92	6/9	PCL83	11/6
1T4	4/9	DL94	7/3	PEN84	11/-
3A4	6/9	DL96	7/11	PEN86C	8/6
3V4	7/3	EBG41	8/6	PL36	13/-
5U4G	5/3	EBF80	8/-	PL38	14/6
5Y3GT	7/-	ECC81	5/6	PL81	10/-
5Z4G	9/6	ECC82	8/6	PL82	7/6
6K7G	3/6	ECC83	7/-	PL83	8/6
6K8G	6/6	ECC84	8/9	PY32	11/9
6Q7G	7/-	ECC85	8/6	PY80	7/-
6SL7GT	6/8	ECH35	6/9	PY81	6/9
6SN7GT	4/6	ECH42	8/9	PY82	7/-
6V6G	5/-	ECL80	6/6	U52	5/3
6V8GT	7/-	EF41	9/-	U78	8/-
6X5GT	6/-	EF80	5/6	UABC80	8/3
12K7GT	5/6	EF85	6/6	UAF12	9/6
12K8GT	11/6	EF88	11/6	UBC41	7/9
12Q7GT	5/6	EF89	8/-	UCH81	8/-
35L6GT	9/6	EL33	10/-	UC94	12/9
3Z4GT	6/-	EL41	9/-	UCC85	7/9
AZ31	8/9	EL84	8/-	UCF80	14/-
B36	8/6	EY51	9/-	UCH42	8/6
CL33	13/-	EY86	8/-	UCH81	8/-
DAF92	9/9	EZ40	6/9	UCL32	11/6
DAF91	6/-	EZ41	7/6	UCL83	12/6
DAF96	7/11	EZ80	6/3	UF41	8/9
DF33	9/9	EZ21	7/-	UF42	8/-
DF91	4/9	GZ32	9/-	UF99	7/6
DF96	7/11	KT61	10/-	UL41	7/6
DH77	7/3	KT63	6/6	UL84	7/6
DK32	12/3	MU14	7/9	UY21	13/6
DK91	6/6	MX40	12/6	UY85	6/9
DK92	8/6	PC84	8/-	UZ5	11/6
DK96	8/3	PCF80	8/-	VP18	9/6

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra C.O.D. Parcel 2/6 extra.

Any Office address no callers.

GERALD BERNARD
90 CARR MANOR AVENUE.
LEEDS 17

SKILLED MEN!

USE YOUR KNOWLEDGE IN A WORTHWHILE JOB

VACANCIES
FOR
**LINEMEN
DRIVERS
DISPATCH RIDERS
DRAUGHTSMEN
DRIVER
ELECTRICIANS
RADIO
MECHANICS
TECHNICAL
STOREMEN
TELEGRAPH
MECHANICS
OPERATORS**
in
**THE ROYAL
SIGNALS**

*Up to £25 tax-free Bonus
plus first-rate wages for
two weeks of your time*

ARE you in a skilled trade? Then you can probably add a tidy sum to your income by joining the Army Emergency Reserve. For one thing, you get pay and allowances at full Regular Army rates whilst in camp. And the more your skill's worth in civilian work, the higher your Army rank and pay. Better still, you also get £9-£25 bonus tax-free.

For this you just spend 14 days a year at a camp, working on your own speciality. And money's not the only profit you get from that. You get a grand refresher course, giving you a lot of new ideas, and putting you right in touch with the latest Army developments. And you

get a welcome break from the usual routine, with sports, games and a great social life. For the place is full of people with the same interests as yourself. Don't miss this chance! Send off the coupon now to: Col. W. B. Rowett, H.Q., A.E.R., R. Sigs., Blacon Camp, Chester. Tel: Chester 21144.

POST THIS OFF RIGHT AWAY!

*Please send me—without obligation—the illustrated booklet telling me
all about the Army Emergency Reserve.*

NAME _____

ADDRESS _____

TRADE _____ (PW/AER)

RADIO

BENDIX RECEIVERS.—RA-10, 4-band superhet, 150kc/s-10Mc/s. Valves: 6SK7-RF; 6K8-Mixer; 2-6SK7-IF; 6RT-2nd det.; 6C5-PFO; 6K6-OP; 6K6-diode. Built-in PU 24v. Clean. Size 6 1/2 in. x 15 1/2 in. Easily converted to mains as described on p. 453 of Sept., 1957. P.W. £4, p.p. 10/-. American Beacon Tx-Rx RT-37/PPN-2, brand new, composed of Tx-Rx with 9 valves (5-3A5; 3-1S5; 1-1R5); built-in 2v. vibrator pack, spare vibrator, headset, connector leads and 10ft. collapsible aerial instr. book. 214-238Mc/s. £3/15/-. p.p. 7/6. National HRO Crystal Filter Units. 455kc/s with crystal set and phasing controls, new boxed. £1, p.p. 2/-. E.W.S. CO., 69, Church Rd., Moseley, Birmingham, 13.

RECEIVERS & COMPONENTS

CALLING 9IN. TELEVISION OWNERS.—Brand new factory fresh 9in. Ferranti Tubes, originally £14/10/-. will replace Mazda, Brimar, G.E.C., etc., £4/10/- each; 6 months' guarantee. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

TRANSISTORS: OC71/72, 12/6 each; OC44, 15/- each; OC72, matched pairs, 24/-; return of post service. A. W. WARD, 142, Raiton Rd., London, S.E.24.

TURRET TUNERS. brand new, famous make, 12 channel, coils 1 to 5 and 8/9 fitted, 34/38 mc/s, complete with P.C.F. 80 and P.C.C. 84, circuit diagram included. £1/17/6, p. end p., 3/6; discounts for quantities, cash with order. SOUTH SUPPLIES (ELECTRICAL) LTD., 95, Old Kent Rd., London, S.E.1.

RECLAIMED VALVES, tested and perfect; huge stocks; all one price, 5/- plus 6d. postage each. Delivery by return. LEWIS, 57, Chalford Walk, Woodford Green, Essex.

ANNAKIN

Phononic Hi-Fi Amplifiers. £15 15s., post free.
 Fine Speakers. 3in., £3 15s.; 12in., £9; 15in., £18.
 Motors. Small, 4.5 v. D.C. 1 1/2 oz. New. Boxed, 6/- ea., post 7d.
 Valves. New. Boxed. 6V6G, 7-, 6K8G, 7/6. Frost Warning Thermostats. Low voltage type. Only 1/6 ea., post 7d.
 Receiver No. 114-Strip. Has 3-EP91, 2-EL91, 5 gang condenser. 124-150 Mc. New., 25/-, post 1/6.
 Relays. 8,000 ohm, 1 make, 3/6 ea., post 1/-.
 Mains Transformers. 100-250 v. mains. 140 v., 250 ma. with various tappings. 6/-, post 2/6.
 Vibrator Power Pack. New. 6 v. input, 250 v. 50 mA. out. Fully smoothed and filtered. Very well made, 20/-, carr. 5/-.
 Throat Mikes. New. Electromagnetic, 1/8, post 6d.
 Smoothing Chokes. 10 H. 60 mA., 1,000 ohm. 1 1/2 lb. A really fine bargain, 2/-, post 1/6.
 Switch. Slider toggle. Useful for Vacuum cleaners, etc. 3 A. 250 v. Only 1/-, post 6d.
 Filamentics. 20-20 mid., 450 v. cans. 2/-, p. 17.
 Potentiometers. W.W. double, 100K+10K. New. Boxed. Quality job, 5/- ea., post 1/-.
 500 ohm W.W. knob. In metal case, 1/- extra, post 1/6.
 Nife Cells, 1.2 v. 5 AH. New. 3/-, post 1/3.
 Plessey Speakers. 7in. x 4in. elliptical. 3 ohm. New. Special price, 17/6 ea., post 1/6. Mainland only. No Export. C.W.O. only. Send stamped, addressed envelope for Lists.
 25 ASDFIELD PLACE, OTLEY, YORKS.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

RECEIVERS & COMPONENTS

(Continued)

"WEYRAD" TRANSISTOR RECEIVER

COMPLETE KIT—LONG & MEDIUM-WAVE P.C.F.—FULL O.P. £9/12/6
CONSTRUCTORS BOOKLET 2/-
 Send S.A.E. for Shopping List.

WESTHAM RADIO SUPPLIES
Rear of 176, Abbotsbury Road
WEYMOUTH, DORSET

VALVES FOR OLD SETS. 1/- and 2/6 (tested, working). List stamp. 85, Charnminster Ave., Bournemouth.

SAVE ON REPAIRS.—100,000 Salvaged Radio and TV spares. Valves, Tubes for practically any set made since 1936. Prices from: Lot. 17/6; P.O.T. 7/6; Osc. Tr. 6H/-; Sound, 2/6; Mains, 10/-; EHT; Mains, 50/-; Def. Coils, 12/6; Speakers, 5/-; Tubes, Mullard, Mazda, etc., 9-10in., 30/-; 12-14in., £2/19/6; 17in., £3/19/6; all picture tested, fitted free or sent subject to 14 days money-back guarantee. Mullard 6 months' guarantee. Valves: 1,000 types from 1/6; EP91, EB91, 6J5, 2/6; EF80, UF42, 10P1, 6F1, 6SN7, 3/6. We can save you pounds! Send s.a.e. with enquiries or for complete list. ST. JOHN'S RADIO, 156, St. John's Hill, S.W.11. (Bat 9838.)

RESISTORS.—100 new, wire ended, assorted, all types, 7/6 box, post free. COOK'S OF BEDFORD, 29, St. Mary's St., Bedford.

SPEAKER REPAIRS, Cones/Fields fitted. Clock Coils Wound. L.S. REPAIRS, Pluckley, Ashford, Kent.

50-WATT POWER AMPLIFIERS, rack mounting, input 200-250 v. A.C. only 35/- (15/- less valves, requires 1-MH, 2-PX25, 1-5U4; 2-in. MILLIAMMETERS, 2in. 0/1, 20/- (2/6). **TYPE 3 POWER UNITS,** de luxe model with 2 meters, 55/- (17/6 includes 10-returnable case). **MONITOR 56** (Indicator 248 and Power Unit 675). £8 (20/-). **VIBRA-PAKS** 6 v. D.C. to 250 v. 100 mA., smoothed, in case. 15/- (3/6). **MOTOROLA POLICE CAR TRANSMITTERS,** 20 40 mc/s., F.M. 6V input, 10 valves, 30 watts, £12 10/- (12/6). **PC-6591 TRANSMITTER RECEIVERS,** 6, 12, or 24 v. input, with separate Power Unit, £12 10/- (15/-). **PLESSEY 6 FT. TRANSMITTER CABINETS,** open front for standard 19in. panels, full length rear door with latch, ventilated top and sides. £4/10/- (20/-). **R-201 BRIDGE UNITS** give D.C. output from Radio Receiver for teleprinters, modulators, etc., 230 v. input, £12 10/- (15/-). **DA-30 OFFER TALKING AERIALS,** one piece, with loading coil in base effectively increasing length to 12ft..

SEND FOR 40-PAGE LIST OF OVER 1,000 DIFFERENT ITEMS.

American super fin. sh. 35-(5/-). **AMPLIFIERS AMERICAN,** 40/250 ohms input, 300 and 2,000 ohms output with 2-12J5 and 2-12A6; 28 v. input, with dynamotor, 9in. x 5in. x 5in., 20-(5/-).

Amounts in brackets are carriage England and Wales.

We have large quantities of "bits and pieces" and can probably help your needs. Please enquire—everyone answered.

P. HARRIS, Organford, Dorset

RECEIVERS & COMPONENTS

(Continued)

POWER IN PACKETS.—Another Super Snp this month. Control Units, Type 426A. Ref. 101b/6299. All brand new, containing 9 valves and 6 Xtals. 3 slow-motion drives, tuneable inductors, etc. Delivered B.R.S. 38/6. Stamp for details. Also brother to above, similar but 1 ktal. Delivered B.R.S. for 24/6. These are really good snips, so send for leaflet now. H.T. Batteries as usual. R. J. DIGGINS, 129/133, Radnor St., Hulme, Manchester, 15.

TRANSISTORS. OC71, 6/6 each; OC44, 10/6. Superb Instrument Cases. 1 1/2 x 7 1/4 x 6, new, 7/6. B.S.R. 4-spud TUG single players, 67/6, plus 3/6 p.p. D. B. CARTER, 347, Ladywood Road, Birmingham, 11.

COMPONENTS. Valves, Tubes, etc. Write or phone for free list. ARION TELEVISION, 4, Maxted Rd., Peckham, S.E.15. (New X 7152.)

FM-AM STEREO

Radiogram chassis-CB8

Paired output 6 watts Plain or Stereo Records. A hand-built quality unit with two speakers

ONLY £20.

BEL SOUND PRODUCTS CO., Marlborough Yard, London, N.19. ARC. 5078.

H.M.V. 15IN., English Electric 15in., Ultra, etc. Televisions, not working, originally £175 each. £5/10/-. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

VALVES FROM 1/6; all guaranteed. Radio, T.V. Components. Lists 3d. HAMILTON RADIO (W), 237, Sedlescombe Rd. N., Hastings.

VALVES, Components, everything to be cleared: s.a.e. for list, please JOHNSON, Claylake, Endon, Stoke-on-Trent.

KINGSLAND

ELECTRONIC COMPONENTS

Stupendous Offers

HURRY—A Must—while stocks last: Set of 4 Files with Handles. Set of 13 Drills from 1/16-1/4. Set of 4-piece, 2-way Screwdrivers in Plastic Cases, one Neon Mains-driver, 6-piece Saw Set consisting of Hand, Tenon, Keyhole etc. one Junior Hack-saw, Bargain Price 21/-, P.P. 2/6.

FREE! Small Bench Vise OR Ratchet Screwdriver, with bargain pack consisting of: pair throat microphones, 50 assorted resistors approx. 150 assorted capacitors, 2in. 2in. screened lead with sockets, one 5 Henry 200 mA. choke, two electrolytic condensers, knobs, toggle switches, Octal valve bases, Vibrators, headphones, waveband switch, four Co-Ax. Plugs, assorted coils, cartridge fuses, three potentiometers, WW multiplier, 24 assorted condensers, Festoon lamp and holder, coil PVC wiring-up wire.

All this for 35/-, p.p. 4/6.

100 ASSORTED RESISTANCES, including W.W., 10/-, p.p. 1/9.

100 ASSORTED CONDENSERS, 10/-, p.p. 1/9.

5X ASSORTED POTENTIOMETERS, 5/-, p.p. 1/6.

Open Saturday until one o'clock. Personal callers welcome.

182, KINGSLAND RD., SHOREDITCH, E.2. Tel.: SHO 6572. *Sony, D.K. only.*

FOR SALE

SATISFACTION ASSURED.—12in. Televisions £9/10/-, 14in. £16, 17in. £19/10/-. Write for quotation, stating requirements. We guarantee satisfaction. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep; stove enamelled, dark green; sent unassembled; 6-shelf Bay £3/15/-; sample delivered free; quantity discounts. N. C. BROWN, LTD., Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)

AMAZING VALUE. Philco Shortwave Car Radio Converters, originally £10; fit to any existing car radio and add six extra wavebands, 16-19-25-31-49 metre bands, also standard broadcast, 6/12 volts; compact under dash counting; chromium control panel with six press-buttons. Complete all fittings and instructions, easily fitted, 45/- post free. Each instrument brand new with Mullard valves. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

SUB-MINIATURE SOLDERING INSTRUMENTS

Ultra-lightweight—only 1 oz. ! The most efficient tool for all Transistor and other delicate soldering, 6 volt 9 watt, 10/9 post free, or with isolating transformer for A.C. Mains, 14/6 plus 1/9 p. & p.

KENNETT & COMPANY

Doe Park, Denholme, Yorks. Trade enquiries invited.

ASTOUNDING VALUE.—9in. Televisions 45/-. 12in. Televisions 70/-. 14in. £9/10/-. 15in. £5/10/-. 17in. £14. Complete but not guaranteed working, as received in part exchange. TOMLINS, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available, carriage 7/6.

VALVES.—96-807s. Many others. Offers. 10, Marnell Way, Hounslow West.

AMERICAN MAGAZINES.—Year's subscription. "High Fidelity," 50/-; "Electronics World," 43/-; "Audio," 35/-. Specimens, 5/- each. Full catalogue free. WILEN LTD. (Dept. 40), 9, Drapers Gdns., London, E.C.2.

SPECIAL PURCHASE! 1,800ft. Agfa-Wolfen L.P. Tape on 7in. spools, only 32/6; 1,200ft., 7in., Ferrotape, 26/6, p. and p. 1/6. Send for complete list of Tape bargains (including American Audio Tape, BASF, etc.) and list of new and secondhand Tape Recorders. E. C. F. KINGSLEY & CO., 132, Tottenham Court Rd., London, W.1. (EUS 6500.)

CABINETS, EQUIPMENT & SPEAKERS

Write for CATALOGUE.

A. L. STAMFORD LTD., Dept. M.29, 84 Weymouth Terrace, London, E.2.



GP59 16 Gns.

WANTED

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford, 1.

URGENTLY REQUIRED, new Radio, Television or Industrial Valves. Also old and obsolete types. Cash prices offered for any quantity. Write call or phone: MIT 6202, 201, Streatham Rd., Mitcham, Surrey.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.

103, North Street, Leeds, 7.

WANTED. Service Sheets and Manuals. No quantity too large, or too small. Highest prices paid. SULTAN RADIO, 6, Mount Ephraim Rd., Tunbridge Wells, Kent.

ALL TYPES of Valves wanted, PL61, ECL80, EY51, U25, PCF80, PZ30, U801, etc., etc., best cash price by return. STAN WILLETTTS, 43, Spon Lane, West Bromwich, Staffs. (Tel.: WEST 3392.)

MISCELLANEOUS

YOU READ MUSIC ?

Then how about making yourself an electronic organ? Constructional data available—full circuits, drawings and notes. It has 8 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swings.

Write NOW for free booklet and further details to C. & S., 20, Maude Street, Darlington, Durham.

MAKING YOUR OWN TELESCOPES. Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc., then our booklets "How to Use Ex.Gov. Lenses and Prisms," Nos. 1 and 2 at 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

PROTECT YOUR CAR AT NIGHT

"LITON" PHOTOELECTRIC PARKING LIGHT SWITCH

will switch your lights on at dusk—off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Avoid accidents, fines. Save your battery.

KIT OF PARTS, 52/6 BUILT AND TESTED, 57/6

Pat. Pending. Send 6d. stamp for pamphlet. "St. John's Radio," 156, St. John's Hill, S.W.11. BATTERSEA 9838

SERVICE SHEETS

FAULTFINDER FILES (TV), showing common faults that each receiver is prone to, and other useful receiving information, 2/- ea. List 9d. plus postage. S. P. DISTRIBUTORS, 11, Old Bond St., London, W.1.

SERVICE SHEETS, Radio, T.V., 5,000 models, Lists 1/-. S.A.E. enquiries, TELRAY, 11, Maudland Bk., Preston.

SERVICE SHEETS

RADIO and Television

Over 100,000 S.A.E. for List. Large stock of obsolete Radio and Television Valves.

JOHN GILBERT RADIO

20, Extension Shepherd's Bush Market, London, W.12 SHE 3052

SERVICE SHEETS.—Huge stock at 4/- ea. List 1/-. Immediate delivery. GLOBE SUPPLIES, 33, Fairfield Close, Sidcup, Kent.

SERVICE SHEETS for sale, all types, from 1/-. Free fault-finding guide with all service sheets. 100 T/V Service Sheets covering 330 popular models, 18/6. Radio, T/V, Electronic Books; s.a.e. lists/enquiries. HAMILTON RADIO (W), 237, Sedlescombe Rd. N., Hastings.

SERVICE SHEETS (trade type).—TV 4/-, Radio 3/-. List 1/-. All orders dispatched on day received. C.O.D. if desired. Also Manuals for sale and hire. S.A.E. SULTAN RADIO, 6, Mount Ephraim Road, Tunbridge Wells, Kent.

SERVICE SHEETS.—We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- ea. Why tolerate delay in obtaining your supplies when we will dispatch by return? Also Manuals for sale and hire. Service sheet list 1/-. Manuals list 9d. S.A.E. please, S.P. DISTRIBUTORS, 11, Old Bond Street, London, W.1.

38 SET WALKIE TALKIE

CIRCUIT INFORMATION

Alignment Procedure. Typical faults in Ex W.D. Sets. Component location diagrams. Circuit diagram. Complete Circuit description. Instructions for use, etc. P.O. 5/-. Address in block capitals, please.

CAMPBELL

Laundry Lane, Hungerford, Berks.

BOOKS & PUBLICATIONS

BOOKS for C. and G. exams: Tels. Principles, A and B, 9/6; Tels. (Principles), 1 and 2, 10/6; Maths for Tels., 1, 7/-; Maths for Tels., 2, 5/-; all post free. RIDDIFORD, 384, Tilehurst Rd., Reading.

SOUND RECORDING

TAPE/DISC/TAPE transfer, 1,800ft. new L.F. Tape, 32/6. Unmixer Mixing Units for quality. SOUND NEWS, 10, Clifford St., London, W.1.

(Continued on next page)

SITUATIONS VACANT

OVERSEAS Oil Exploration Company with world-wide seismic parties, offers permanent career to Electronic Technicians. Work consists in maintaining and operating electronic recording equipment under field conditions. Live generally in camp. Qualification: H.N.C. or equivalent essential, with practical experience in electronics. Home leave every 2 years. Box No. 24.

TV AND RADIO, A.M.Brit.I.R.E.E. City and Guilds, R.T.E.B. Cert. etc., on "No pass—no fee" terms. Over 95% successes. For details of Exams and Courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free, B.I.E.T. (Dept. 242G), 29, Wright's Lane, London, W.8.

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation— I.C.S. Courses for the enthusiast and for those seeking examination qualification. Brit.I.R.E.E., City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write today for Free book: **INTERNATIONAL CORRESPONDENCE SCHOOLS**, Intertext House, Parkgate Rd. (Dept. 541A), London, S.W.11.

A.M.I.Mech.E., A.M.Brit.I.R.E.E. City and Guilds, G.C.E., etc., bring high pay and security. "No pass—no fee" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook free, B.I.E.T. (Dept. 242B), London, W.8.



A career on good pay in a skilled, expanding trade

RADAR OR WIRELESS MECHANIC
in the

Royal Air Force

Immediate vacancies; full training for suitable applicants in skilled radar and wireless maintenance, etc., full allowances and all found; month's leave a year; chance to travel, plus all the wider interests of Service life. Call or write for details to: Central Recruiting Office, (PW 525a) Victory House, Kingsway, London, WC2

CITY AND GUILDS (Electrical, etc.), on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free, B.I.E.T. (Dept. 242a), 29, Wright's Lane, London, W.8.

ELECTRONIC TECHNICIAN; H.N.C. with Electronics or exceptional practical experience; maintenance and operation magnetic playback systems; geophysical field or playback experience an advantage; Hayes/Orpington area. Box No. 25.

EDUCATIONAL

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The "Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet, 1/-, all post free from the **SECRETARY, I.P.R.E.E.** 20, Fairfield Road, London, N.8.

AT LAST—at a reasonable cost—quality Hi-Fi in your home by building it yourself under our new system. Free brochure from: Dept. 21 P.W. **RADIOSTRUCTOR**, 40, Russell St., Reading, Berks.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

LEARN RADIO AND ELECTRONICS the new practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11 P.W. **RADIOSTRUCTOR**, 40, Russell St., Reading, Berks.

LEARN-AS-YOU-BUILD Course in basic radio, electronic and electrical theory with practical training building a 4-valve TRF and 5-valve superhet radio receiver; Signal Generator and High-quality Multi-tester. Write for free book: **INTERNATIONAL CORRESPONDENCE SCHOOLS**, Intertext House, Parkgate Road (Dept. 541), London, S.W.11.

**★ LEARN ★
RADIO & T/V
SERVICING
for your OWN
BUSINESS/HOBBY**

● by a new exciting no-maths system, using practical equipment, recently introduced to this country.

FREE Brochure from:—

**RADIOSTRUCTOR
DEPT. G77, 46, MARKET PLACE,
READING, BERKS. 3/60**

EDDY'S (Nottm.) LTD.

172 ALFRETON ROAD, NOTTINGHAM

Surplus New and		Guaranteed Valves			
DAF96	8/3	EF80	6/6	U25	12/-
DF96	8/3	EF85	7/-	U31	7/9
DH63	7/6	EF86	11/-	U35	8/6
DK91	7/-	EF91	4/-	UB41	8/-
DK92	8/6	EL41	9/3	UY41	6/6
DK96	8/6	EL42	9/6	1A7GT	12/6
DL96	8/3	EL64	8/3	1D5	9/6
EABC80	7/9	EL85	10/6	1L4	3/9
EB34	1/6	EL91	4/9	1R5	7/-
EB41	7/-	EY51	9/6	155	6/6
EB91	4/-	EY86	9/6	1T4	4/9
EBC41	8/9	EZ80	6/9	5U4G	5/9
EBF80	8/6	GTIC	7/6	6C4	3/6
ECC81	6/-	MU14	8/-	6K7G	2/3
ECC82	7/-	P61	2/6	6K8G	6/-
ECC83	7/6	PCC84	8/6	6S7GM	2/-
ECC84	8/9	PCF80	9/-	6SN7GT	2/9
ECC85	8/6	PEN36C	9/6	6XS7G	6/6
ECH42	8/9	PEN46	5/-	6V6G	5/9
ECL80	9/6	PL81	11/6	6V6GT	6/6
ECL82	10/6	PL82	7/9	6X4	6/-
EF36	2/6	PY31	8/6	12A6	5/6
EF37	4/-	PY80	6/9	25A6G	8/-
EF41	8/6	PY81	8/6	807 (B)	3/9
EF42	7/6	PY82	7/6	954	1/6

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11. Post 6d.

THROAT MIKES. 1/-, Post 6d. Could be used for electrifying musical instruments.

JACK PLUGS. Standard. 1/11. Post 6d.

DIMMER SWITCHES. Ideal for train speed regulators. 1/11. Post 9d.

HANDMIKES. Carbon. 3/11. Post 1/-.

SPECIAL OFFER—CAR RADIO KITS. 7 transistors, long and medium. 2 watts output, R.F. stage and automatic gain control. 6 or 12 volts. Complete kit with cabinet. 10 gns. Post and Packing 5/-.

VARIABLES. 12 v., 4 pin. 4/11. Post 1/-.

NIFE ACCUMULATORS. Midget Single Unit. Size 3" x 2 1/2" x 3/8". 7 amp. hours. 1.25 volts. 1/11. Post and Packing 1/6.

HEADPHONE CORDS. High Quality. 6 ft. lengths. 1/11 Pair. Post 6d.

SPEAKER GOLD GRILLE. 6 1/2" x 4". 1/-, Post 6d.

GERMANIUM DIODES. 1/- each, 9/6 dozen. Post 4d.

NEON MAINTESTER/SCREWDRIVERS. 3/11. Post 9d.

RECTIFIERS. RM1 4/9, RM2 6/6, RM3 7/6, RM4 15/-, RMS 19/6. Contact cooled. 200-60 m.a., 7/6. Post 1/-.

CONDENSERS. Tubular wire end (not ex-govt.). 8 mfd., 450 v., 1/9; 8-8, 450 v., 2/6; 16 mfd., 450 v., 2/9; 16-16, 450 v., 3/9; 16-8, 450 v., 4/-; 32 mfd., 450 v., 3/9; 32-32, 350 v., 4/-, Post 1/-.

CRYSTAL SETS. Complete 2-wave bands. High Gain. Good quality. 19/11 Post and packing 2/-.

HEADPHONES. High Resistance to suit above crystal set. Good quality. 12/11 pair. Post and packing 1/6.

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and packing 6d. per valve extra. Over £3 free. C.O.D. or C.W.O. only. C.O.D. charge 3/- extra.

S.A.E. with all enquiries.

PADGETTS RADIO STORE

40, MEADOW LANE, LEEDS, II

Indicator Units.—Type 166A or Type 116. Complete with tube and all Valves, EF50s, etc. Good condition, 25/-. Carr. 7/6.

1154 Transmitters.—Model M. Four wave band. Good condition, complete with Valves, Meters, etc., 16/-. Carr. 12/6.

Tube Unit BC929H.—Complete with 3BP1 tube (guaranteed tube), less Valves, Switch Motor and Transformer. 18/-. Carr. 8/-. Condition of case. Store soiled. Spare tube, 10/-. Carr. 12/6.

VCR97 Tubes new. 7/6. Carr. insurance 7/-. Mu-metal Screens 4/-. Post 2/-. Carr. 12/6.

Special Offer of Reconditioned Ultra T.V. Sets. Model 815. 14in. T.V. for all B.B.C. and I.T.V. Stations. Perfect results and sold with a Money Back Guarantee. For £12 only. Tube sent in separate carton. Carriage per B.R.S. 17/-. Carr. 12/6.

Receiver Type 3645.—The cleaned-up 1355, complete with 7 VR65, 1 VR91 Valves. With valves, 12/-. Less Valves, 6/-. Carriage per B.R.S. 7/6.

Bush T.V. 24C. 12in. T.V. B.B.C. and I.T.V. Perfect Pictures, £9. Carriage 17/-. Carr. 12/6.

Bush Pvc. Ultra. 12in. B.B.C. only. Perfect Pictures, £8. Carriage 17/-. Carr. 12/6.

Twelve Inch T.V. Chassis. Complete with L.O.T., Focus Coils, etc. Less valves, 15/-. Pvc. Ultra, Plessey Banner, Ekco, Marconi, etc. Carriage per B.R.S. 5/-. Chassis less L.O.T. and Focus Coils for 5/-. Carriage 4/-. Carr. 12/6.

Speakers from T.V. Sets. All Perfect. 7 x 4, 10/-. 8in., 6/6. 6in., 6/6. Post 2/6. Send 3d. Stamp for Bargain List of Valves and Small Components.

12 v. D.C. MAGNETIC SWITCH. Cuts out on 2 a. overload or dead short. 13/6.

CUT PRICE TOOLS. 5in. side cutters, 5/-. 5in. plated round nose tapered pliers, 5/-. 7in. flat-nosed tapered pliers, 8/6. Pocket neon testers with retractable screwdriver, 5/-. Carr. 12/6.

NEW BOXED BSR UAG 4-SPEED AUTO-CHANGERS. 200/250 v. A.C. £8/19/6. Carriage 5/-. Carr. 12/6.

OUR FAMOUS TRANSFORMERS. Input 200 250. Output tapped 3 to 30 v. 2 a. or 5, 11, 17 v. 5 a. Each 24/6.

F.W. METAL RECTIFIERS. 12/6 volt. 1a., 7/6. 3a., 13/-. 4a., 17/6. 6a., 27/6.

TOGGLE SWITCHES DPDT. 3/6.

MICRO SWITCHES. Make & Break. 5/6.

MAINS TRANSFORMER & RECTIFIER. Output 12 v. 1 a. D.C. 19/6.

NICKEL NIFE BATTERIES. 1.2 v. 2.5 a. Size 3 x 21 x 1in. 6/-. or 3 for 16/-. 4 for 21/-. Carr. 12/6.

ARMY MORSE KEYS. 3/-. P.P.

RELAYS. We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-. Carr. 12/6.

KEY SWITCHES from 3/-. Carr. 12/6.

FULL SIZE H/S CHROME VANADIUM STEEL TWIST DRILLS. Sets 7-1/16 to 1in. 6/6. Small sets, 4/-. Carr. 12/6.

6 OR 12 v. RELAYS. With 4 make contacts. 6/-. 2 for 11.6. 3 for 16/-. 4 for 21/-. Carr. 12/6.

VERY POWERFUL GEARED SMALL 12 v. D.C. MOTORS. Instant stop. 3 x 11in. 16/6.

All items new, guaranteed & post free except where stated.

Lists sent on request. Post orders only to

THE RADIO & ELECTRICAL MART
29 STATION APPROACH, SUDBURY TOWN, WEMBLEY, MIDDX.

WIRING ACCESSORIES

Return of Post Service. Lowest Possible prices consistent with high quality. Money back guarantee.

PVC Cable Flat Twin with E. 3 Core

1.044	£2. 1. 8	£2.15. 1	£2.19. 4
3.029	£2.14. 9	£3. 6.11	£3.19. 0
3.036	£3.16. 5	£4.10. 9	£5.10.10
7.029	£4.19.11	£6. 1.11	£8.18. 3

TRS CABLE

1.044	£2. 3. 5	£2.13.11	£3. 0.10
3.029	£2.15. 9	£3. 6.10	£4. 5. 4
3.036	£3.15. 2	£4. 6. 5	£5. 8. 7
7.029	£4.13.10	£5.18. 2	£6.16. 7

Prices per 100 yds. All sizes stocked. Supplied in 25, 50, 75 or 100 yd. lengths. 7.029 and above cut to length—no cutting charge. Carriage paid on all orders over £2. Full range of accessories available. Send for complete lists.

ELECTROSURE 118, FORE STREET, EXETER Phone: Exeter 56687.

TRANSFORMERS

Suppliers to B.B.C., I.T.A., and leading radio manufacturers. Single or long runs. Prompt delivery. Home and export. Rewinds to all makes.

FORREST TRANSFORMERS LTD.,
SHIRLEY, SOLIHULL, WARWICKS
Tel: SHI 2483

PETHERICK'S RADIO SUPPLIES

22, High St., Bideford, N. Devon.
4/6 TRANSISTORS 4/6

RED SPOTS. 4/6; **WHITE SPOT.** 5/6; Yellow/Green, 5/6; Red/Yellow, 10/9;
CRYSTAL DIODES. 1/- each; **GEX 34.** 4/-; Mullard OA70 or OA81 Diodes, 4/- each.
CRYSTAL SET COILS M.L. With Circuit, 2/6; **DRB2** Coils, 4/-; **VARI-LOOP-STICK** MW Coil with Transistor Circuit, 4/-; 2 Mfd. 150 volt Electrolytics, 1/6;
REACTION CONDENSERS. 0001, 3/-; .0008, 3/9; .0005, 4/-; Miniature .0005, 4/-.
HEADPHONES for Crystal Sets, Lightweight, 14/- pr. British Volume Controls, less Switch, 3/3; D.P. Switch, 5/9.

All sent POST FREE IN U.K.
FREE MULTIMETER CIRCUITS for 100 μ A., $\frac{1}{2}$ mA. or 1 mA. meter. Send stamp only.

PRECISION WIREWOUND RESISTORS

1 Watt, 1 to 1,000 ohms, 1%, 2/9; 0.2% \pm 0.01 ohm, 4/3 to 5 K. 1%, 3/3; 0.2%, 4/9. Your value wound to order.
Wirewound Resistors. 1 W, 1% at 1/6. 1 ohm, 10, 20, 50, 100, 200, 500, 1 K., 2 K., 5 K. High Stab. Resistors. $\frac{1}{2}$ W, 1% at 1/6; 9 K., 50 K., 100 K., 220 K., 225 K., 500 K., 1 M., 1.5 M., 2.2 M., 6.8 M.
Leather Meter Case with shoulder strap, 6 x 4 $\frac{1}{2}$ x 2, int. with partition, 5/-, p. & p. 1/-.

1% Shunt for 1 mA. 100 ohm Meter. Ranges 10, 100, 1,000 mA., 8/6. For 500 μ A. 500 ohm meter, ranges 5, 50, 500 mA., 8/6. We can quote for special shunts. 100 pF, 1,000 pF, 0.01 μ F, all 2% S.M. 1/- ea.

PLANET INSTRUMENT CO.,
25, Dominion Ave., Leeds, 7.



TRANSISTOR AUDIO AMPLIFIERS

250 mW Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (Transformerless) using GET114 transistors, operating from a 9V supply.

500 mW Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 9V supply.

1 W Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 12V supply.

2 W Class B push-pull using GET116 transistors, operating from a 12V supply.

3 W Class B single-ended push-pull (transformerless) using GET115 transistors (mounted on 3" x 3" fins) operating from a 12V supply.

These are a selection from the range of audio amplifier circuits using G.E.C. transistors. For details of any of these circuits or information on the wide range of G.E.C. transistors, please write to:

G.E.C. SEMICONDUCTOR DIVISION

School Street, Hazel Grove,

STOCKPORT, CHESHIRE.

FREE LISTS

BY RETURN

SUB-MINIATURE TRANSISTOR COMPONENTS: A SELECTION
 2 mfd. 1½ v.w., 4 mfd. 6 v.w., 30 mfd. 6 v.w., 2/- each; 500 mfd. 6 v.w., 1/6 200 mfd. 3 v.w., 2/3.
 2 p. 2 w. Slide Switch, 2/6; Push-button on/off, 1/6.
 Jack Plugs, 4/-; Socket, 4/-; with Switch, 5/-.
 2½ in. Speaker, 11/16 in. deep. 3 ohms. 17/6. P.P. 9d.
 7-Section Chromed Telescopic Aerial 3ft. 6 in. open, 12/6.
 Perdio Type moulded Cabinet with gold trimmings. Size 5½ x 3½ x 1½ in. (Red or Blue), 12/6. P.P. 9d.
 Sub-miniature Magnetic Microphones (List 30/-), 15/-.

EX-UNIT CONTROLS

5K Sub-min. Printed Circuit with Switch (List 12/6), 5/-.
 20K Sub-min. Printed Circuit with Switch (List 12/6), 5/-.
 5K Sub-min. Printed Circuit less Switch (List 12/6), 3/-.
 20K Sub-min. Printed Circuit less Switch (List 12/6), 3/-.

SEND FOR FREE COMPLETE TRANSISTOR COMPONENT LIST: Includes Transformers, Ferrite Aerials, Speakers, Tuners, Chassis, Cabinets, Phones, Switches, Controls, Coils.

THE LARGEST RANGE IN THE COUNTRY

VALVE REDUCTIONS

(WHEN PURCHASED IN SETS)
 TP25, VP23, HL23/DD, PEN25 (or QP25) 25/-
 1A7GT, 1N5GT, 1C5GT, 1Q5GT (or 3Q5GT) ... 35/-
 X66, KTW61, DH43, KT63, U50 ... 30/-
 6K8G, 6K7G, 6Q7G, SZ4G, 6V6G ... 32/6
 1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4) ... 25/-
 DK96, DF96, DAF96, DL96 ... 35/-
 6K8C, 6K7G, 6Q7G, 25L6GT, 25Z5 (or 25Z6G) ... 35/-
 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50LGT) ... 40/-
 12S47GT, 12SK7GT, 12S07GT, 35Z4GT, 35L6GT (or 50L6GT) ... 32/6

P.P. 1/6 per set of Valves.
FREE VALVE LIST BY RETURN.

CAR RADIO VIBRATOR UNITS

2 volts 7-pin Synchronous ... 7/6
 12 " 6 " " " ... 12/6
 12 " 7 " " " ... 12/6
 6 " 7 " " " ... 12/6
 6 " 4 " non-synchronous ... 7/6
 12 " 4 " " " ... 5/-

PACKARD

BELL PRE-AMPLIFIER


Low Impedance Mic, Pre-Amp. 65L7GT and 28D7. Complete in screened box with leads, jack-plugs and handbook.
BRAND NEW IN CARTONS, 12/6, P.P. 2/-.

8-IN. HIGH-FLUX SPEAKER

Complete in Black Crackle Case. 3 ohms Speaker, 45/-. P.P. 2/6.

TRADE ENQUIRIES INVITED ON ALL ITEMS AND DO-IT-YOURSELF UNITS

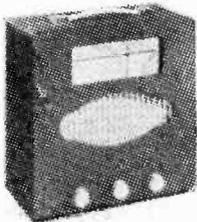LARGE RANGE OF VALVES, TUBES, MAINS TRANSFORMERS, QUARTZ CRYSTALS, METERS, TEST UNITS, TRANSISTORS, POTS, MINIATURE COMPONENTS, RECTIFIERS.



Chassis Size 10 x 10 x 4 in.

SHORT-WAVE RADIO

- ★ 3 Wavebands (10 to 550 metres)—650 kc/s to 2 Mc/s, 3 to 11 Mc/s to 30 Mc/s.
- ★ 5-valve Marconi Superhet.
- ★ A.C./D.C. 200 to 250 v. mains.
- ★ 7 x 4 in. Speaker; Gram. input.
- ★ Slow-motion Drive. ★ Frame Aerial.

NOW £6.15.6 P.P. 3/6.

OR COMPLETE IN PORTABLE CABINET, £7.12.6, P.P. 4/-.

★ ALTERNATIVE MODEL: MEDIUM, LONG AND SHORT

— THE WORLD IN YOUR HOME —

A.C., D.C., R.F. METERS

0-15 v.	2½" M.I. (AC) F.R.	8/6
0-40 v.	2" M.C. (DC) F.S.	7/6
0-150 v.	2" M.C. (DC) F.R.	12/6
0-200 v.	2½" M.C. (DC) F.R.	12/6
0-1½ kv.	2½" M.C. (DC) P.	15/-
0-2½ kv.	2½" M.C. (DC) P.	15/-
0-500 UA	3½" M.C. (DC) F.R.	59/6
0-400 UA	3½" M.C. (DC) F.R.	59/6
0-1 mA	2½" M.C. (DC) F.R.	22/6
2½-0-2½ mA	2½" M.C. (DC) F.R.	12/6
0-50 mA	2" M.C. (DC) F.S.	7/6
0-100 mA	2" M.C. (DC) F.S.	10/-
0-150 mA	2" M.C. (DC) F.S.	7/6
0-500 mA	2½" M.C. (DC) F.R.	12/6
0-750 mA	2" T.C. (RF) P.	6/-
0-1 amp.	2" T.C. (RF) P.	6/-
0-3 amp.	2" T.C. (RF) F.S.	6/-
0-12 amp.	2" T.C. (RF) P.	10/-
0-30 amp.	2" M.C. (DC) F.S.	7/6
5-0-5 amp.	2½" M.C. (DC) P.	10/-

FREE COMPLETE LIST ON REQUEST. (INCLUDES MULTI-METERS, AVO & CABY, TRIPLET, ETC., AT EASY PRICES.)

TRANSISTORS

PRICES DOWN !!

FROM 5/- EACH

SHORT-WAVE, AUDIO, R.F., I.F. AND POWER.

SB078	20 Mc/s	6mW H.F.	10/-
SB305	25 Mc/s	10mW H.F.	15/-
SB231	30 Mc/s	10mW H.F.	22/6
SB231R	50 Mc/s	10mW H.F.	30/-
XB104	1 Mc/s	120mW Audio	10/-
XC101	matched pairs	325mW	32/- pr.
XA104	6 Mc/s	90mW Osc/Mixer	18/-
XA103	4 Mc/s	90mW RF, IF	15/-
XC121	—	200mW Power	17/-
XC131	Matched pairs only	500mW pr.	34/-
OC170	70 Mc/s	70mW S.W.	35/-
OC16	8 watts	Power	54/-
OC44	15 Mc/s	60mW Osc/Mixer	19/6
OC45	6 Mc/s	60mW RF, IF	18/6
OC71	600 kc/s	100mW Audio	10/-
OC72	matched pairs	350mW	32/- pr.
Red Spot	800 kc/s	125mW Audio	5/-
White Spot	5 Mc/s	125mW RF, IF	7/6
Photo Transistor	100mW	—	10/-
V15/10P	10-watt	Power	15/-

FREE DATA AND COMPLETE LIST ON REQUEST. ALL TYPES ARE FULLY GUARANTEED.

CRYSTAL MICROPHONES AND INSERTS

ACOS AND OTHER WELL-KNOWN MAKES BRAND NEW.

1½ in. Square	7/6
1½ in. Square	7/6
1½ in. Round	7/6
1½ in. Round	8/6
1½ in. Round	14/-
2 in.	12/6
1½ in. Square, ex-units	3/6

Acos 39-1 Stick Mic. with Stand 39/6, P.P. 1/6

Acos 40 Desk Mic. 25/-, P.P. 1/6
 All guaranteed. P.P. 6d. any type.

TRANSMITTER/RECEIVER

Army Type 17 Mk. II. Complete with Valves, High Resistance Headphones, Hand Mike, Instruction Book and Circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120 v. H.T. and 2 v. L.T. Ideal for Civil Defence and communications.


BRAND NEW 45/- P.P. 5/-.
 44-61 Mc/s calibrated wavemeter for same. 10/- extra.

TYPE 38 TRANSMITTER/RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s **22/6** P.P. 2/6.
 Headphones 7/6 pair. Junction Box 2/6.
 Throat Mike 4/6. Canvas Bag 4/- Aerial Rod 2/6.

AVO MINOR TESTMETER

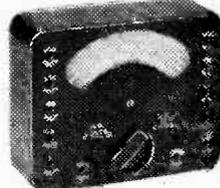

A.C./D.C. 0-500 volts. (in 5 Ranges) D.C. 0-500 mA (in 5 Ranges). RESISTANCE 0-20 K.

COMPLETE WITH LEADS AND LEATHER CASE 79/6 P.P. 2/-.
FULL GUARANTEE.

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station. PADDington 1008 9

5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.
 OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock

SEE BACK PAGE

Practical Wireless

BLUEPRINT

SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets, are now out of print, an asterisk in the list below denotes that constructional details are available free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price	Title	Number	Price
CRYSTAL SETS					
Junior Crystal Set	PW94*	2/-	A.C. Fury Four	PW20*	2/6
Dual-wave Crystal Diode	PW95*	2/6	Experimenter's Short Wave	PW30a*	2/6
STRAIGHT SETS					
Battery Operated					
Modern One-valver	PW96*	2/6	Midget Short Wave Two	PW38a*	2/6
All-dry Three	PW97*	3/6	Band-Spread Three (Battery)	PW68*	2/6
Modern Two-valver	PW98*	3/6	Crystal Receiver	PW71*	2/-
SUPERHETS					
Mains Operated					
A.C. Band-pass Three	PW99*	4/-	Signet Two (Battery)	PW76*	2/6
A.C. Coronet-4	PW100*	4/-	Simple S.W. One-valver	PW88*	2/6
A.C./D.C. Coronet	PW101*	4/-	Pyramid One-valver	PW93*	2/6
MISCELLANEOUS					
The PW 3-speed Autogram	—*	8/-	BBC Special One-valver	AW387*	2/6
The PW Monophonic Electronic Organ	—	8/-	Short-Wave Two	AW429*	2/6
TELEVISION					
The PT Band III Convertor	—*	1/6	Short-Wave World Beater	AW436*	3/6
TELEVISION					
			Standard Four Valve S.W.	WM383*	3/6
			Enthusiast's Power Amplifier	WM387*	3/6
			Standard Four Valve	WM391*	3/6
			Listener's 5-Watt Amplifier	WM392*	3/6
TELEVISION					
			Argus Television Receiver	—*	3/-
			Simplex Television Receiver	—*	3/6

QUERY COUPON

This coupon is available until 5th March, 1960 and must accompany all queries in accordance with the notice on our "Open to Discussion" page.

PRACTICAL WIRELESS, MARCH, 1960

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEAIGHT & SONS, Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTCH (A/sia), LTD. South Africa and Rhodesia: CENTRAL NEWS AGENCY, LTD. Subscription rate including postage for one year: Inland £1.3.0. Abroad £1.1.6 (Canada 19s.). Registered at the General Post Office for the Canadian Magazine Post.

Entirely New Design in Transistor Portable Radios !

“CONTINENTAL—6” Combined Portable/Car Radio.

“For Style, Quality Performance and Value for Money.”


Medium and Long Wave Full Tuning.

- ★ Plessey Printed Circuit
- ★ 6 Ediswan Transistors
- ★ 5" High Fidelity Speaker
- ★ 400mW Push-Pull Output
- ★ Internal Ferrite Aerial
- ★ Slow Motion Tuning
- ★ Full Instructions
- ★ Printed Circuit marked with Component Numbers
- ★ Trimming Tool Supplied
- ★ Double Tuned I.F.s

Total Cost of all Components

£11.10.0 p.p. 3/6

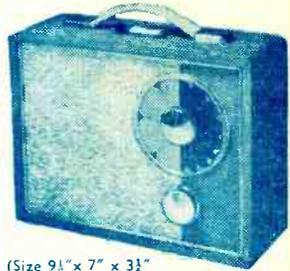including Cabinet, Battery, Transistors, Car Radio, AVC and all necessary items.



A highly sensitive and selective portable fully tuneable on medium and long waves. Performs equally well as a car radio. Low running costs, good looks and care of construction combine to produce a radio equal to commercial receivers in the 20 gns. class.

(Size 9 1/2" x 7" x 3 1/2"
Weight 4 lbs.)

All components available separately. Send for descriptive leaflet and prices. **CALL AND HEAR DEMONSTRATION MODEL**

All Components for the Popular **“TRANSISTOR 8”** £10.19.6 .p. 2/6 **FREE BOOKLET**

MAJOR—2

(Two-transistor Pocket Radio)



69/6 TOTAL COST
P.P. 1/6.

- ★ 4-stage reflex !
- ★ Medium wave tunable !
- ★ Very sensitive !
- ★ No aerial or earth !
- ★ Complete lay-out !
- ★ Over 6 months on one battery.
- ★ 4 1/2 x 3 x 1 1/2 in.
- ★ Weight only 4 ozs.
- ★ Personal phone.

RED-SPOT TRANSISTORS

5/- EACH

WHITE-SPOT

7/6

NEW FREE LIST ON REQUEST

MAJOR—3

(THREE TRANSISTOR POCKET RADIO)



(As Described in "R.C." Sept. '59)

- ★ 5-stage Reflex Circuit.
- ★ No Aerial or Earth.
- ★ Min. Volume Control.
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning.
- ★ Size 4 1/2 x 3 x 1 1/2 in.
- ★ Personal phone.

TOTAL **87/6** P.P. 1/6 NEW BOOKLET FREE COST
FANTASTIC OUTPUT, TERRIFIC RECEPTION. GUARANTEED ANYWHERE

NEW BOOKLET FREE : All components sold separately. (Beware of Imitations.)

GOOD RECEPTION ANYWHERE !

SUPER 6

SIX TRANSISTOR MEDIUM AND LONG WAVES



- ★ Plessey Printed Circuit.
- ★ Mullard Transistors.
- ★ 3-inch Sensitive Speaker.
- ★ Full Medium & Long Waves.
- ★ Size 7 x 4 1/2 x 2 in.

Recommended by us as being one of the easiest to build 6-Transistor printed circuit superhet receivers ever offered.

(LIMITED QUANTITY ONLY.) **FREE LIST ON REQUEST**

TOTAL COST OF ALL COMPONENTS, INCLUDING CABINET AND BATTERY.

£9.10.0 P.P. 2/6

All parts sold separately.

THE MINOR



- ★ 3 x 2 x 1 1/2 in.
- ★ Medium wave.
- ★ 3-stage reflex.
- ★ Internal aerial
- ★ Smallest yet.
- TOTAL COST WITH CASE AND MINIATURE EAR-PIECE
- All parts sold separately. **49/6**
- Diagram and List Free. P.P. 1/6

“ PRACTICAL TRANSISTOR CIRCUITS ”

	ALL TRANSISTOR UNITS DESCRIBED	Total Cost	P.P.
1	RADIO CONTROL RECEIVER (27 Mc/s)	50/-	1/-
2	R.F., I.F. GENERATOR (450 kc/s to 3 Mc/s)	25/-	1/-
3	LIGHT OPERATED SWITCH	27/6	1/-
4	SQUARE WAVE GENERATOR (Audio)	20/-	1/-
5	SIGNAL TRACER (Audio I.F. R.F.)	37/6	1/6
6	HEARING AID AMPLIFIER	95/-	1/-
7	3-CHANNEL AUDIO MIXER	42/6	1/-
8	AUDIO GENERATOR	25/-	1/-
9	ADDON AMPLIFIER (250mW powerstage)	59/6	1/6
10	2 WATT POWER STAGE (for Continental)	52/6	2/-
11	BABY ALARM—100% SAFE	92/6	2/-
12	TOP BAND TRANSMITTER (1.8 to 2 Mc/s)	57/6	1/6
13	3 TO 12 MC/S XTAL OSC.	22/6	1/-
14	35 METRE C.W. TRANSMITTER	27/6	1/-

A BOOKLET PRODUCED FOR THE HOME CONSTRUCTOR CONTAINING TRANSISTOR CIRCUIT DIAGRAMS, PRACTICAL LAYOUTS, DATA AND INFORMATION. ALL COMPONENTS USED ARE READILY OBTAINABLE FROM US.

(1st Edition) ONLY **2/-** POST FREE.

TO HENRY'S (RADIO) LTD.

Enclosed please find remittance value 2/- for "Practical Transistor Circuits," Radio Receiver Leaflets and Components Lists.

NAME
(BLOCK CAPITALS, PLEASE)

ADDRESS

P.W.

SEE OTHER ADVT. INSIDE

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station. PADDINGTON 1008/9

5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.
OPEN MONDAY TO SAT. 9-6, THURS. 1 o'clock.

718