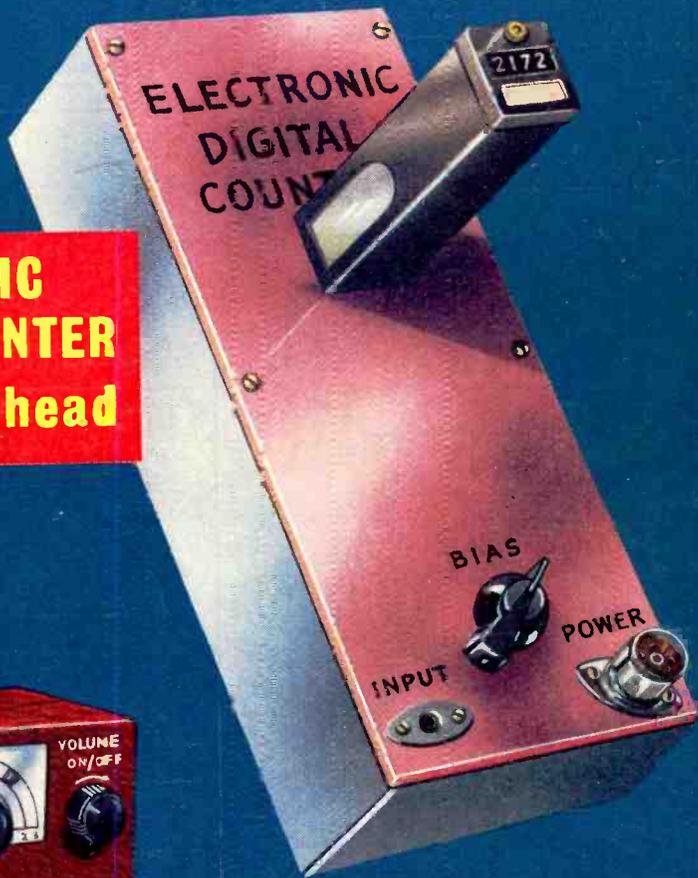


FEBRUARY  
1962

# Practical 2/- WIRELESS

**ELECTRONIC  
DIGITAL COUNTER  
with Geiger-head**




**16m TO 175m TRANSISTOR  
S.W. TUNER**



**MIDGET MAINS SUPERHET**
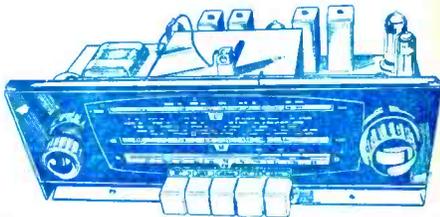
## BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £14 (Carriage Paid)

A.C. ONLY. Chassis size 15 x 6½ x 5½ in. high. New manufacture. Dial 14½ x 4 in. in black and gold. Pick-up. Ext. Speaker. Ae., E., and Dipole Sockets. Five push buttons—O.P. L.W., M.W., P.M. and Gram. Aligned and tested O.P. Transformer. Tone Control. 1,000—1,900 M.; 200-500 M.; 88-98 Mc/s. Valves EZ80 rect., EC81, EF89, EAB80, EL84, ECC85. Speaker and Cabinet to fit chassis (table model). 47/6 (post 2/6). 10 x 6 in. ELIPTICAL SPEAKER. 20/-, to purchasers of this chassis. **TERMS**—(Chassis) £5 down and 5 Monthly Payments of £2, or with Cabinet and Speaker £5.10.0 down and 6 Monthly Payments of £2. Cheap Room Dipole 10/- Feeder 6d. yard.




## THE "CANTATA" 6-TRANSISTOR AND DIODE PORTABLE

COMPLETE KIT FOR ONLY

**£7.19.6**

(post 3/6)

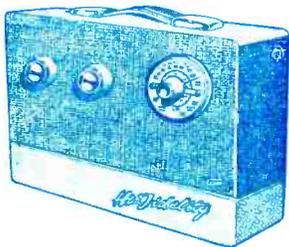


- ★ 500mW push-pull output. ★ Ferrite rod aerial.
- ★ Car aerial socket and coil. ★ M.W. and L.W. full coverage.
- ★ Operates on two 4.5v cells. ★ Printed circuit board 8½ x 2½ in.
- ★ All holes drilled and component positions marked on reverse side of board.
- ★ Booklet of full instructions 2/6 for 16p. (refunded on purchase of kit).
- ★ Size 9 x 3½ x 7 in. ★ 8 x 2½ in. P.M. high quality speaker.
- ★ Attractive Vinyl covered cabinet, two tone.
- ★ Two batteries 5/6 the pair.
- ★ High Sensitivity. ★ Good selectivity.
- ★ Mullard transistors OC44, 2 x OC45, OC81D, and 2 x OC81.
- ★ Top grade Weymouth Radio Coils and transformers.
- ★ Alignment service if required 17/6 (inc. post).
- ★ Write for list of prices.
- ★ All parts supplied separately.
- ★ Note the total cost—no extras at all.
- ★ Built in two hours.


**BATTERY ELIMINATOR.** For 4 Low Consumption Valves (80 range), 90 v. 15mA. and 1.4 v. 125mA. 42/6 (2/6 post). 200-250 v. A.C. Size 8½ x 3½ x 2 in. Also for 250 mA. 1.4 v. and 90 v. 15 mA at same price.

**AUTOMATIC RECORD CHANGERS.** ALL 4-SPEED WITH TURN-OVER CRYSTAL CARTRIDGE (carr. 5/- extra). Latest UA14. £7.10.0. Collaro C.60 Studio model, plays any records 7-12 in. only £7.15.0. Motor board for UAB, UA14 or Collaro 3/6 (post 1/6). Both UA14 and C.60 fitted monaural cartridge but wired for stereo.

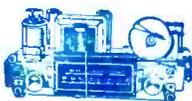**BEEBEE BATTERY RADIO IN MAKERS' CARTON.** Valves DK98, DF96, DA F96. DL96. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet 12 x 7½ x 6 in. ONLY £5 (2/6 p. & p.); MW and SW £5.4.0 (plus 2/6 p. & p.).



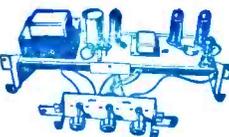**SELF-POWERED VHF TUNER CHASSIS.** Covering 88-95 Mc/s. Mullard permeability Tuner. Dims. 10½ x 4½ x 5 in. high ECC85, EF91, EF91 and 2 diodes. Metal Rectifier. Mains transformer. Fully wired and tested. Only £7.14.0 (carr. pd.). Room dipole 10/-, 300 ohm twin feeder. 6d. yd. Tuner without power pack £8.14.0 (carr. paid).



### PUSH-PULL AMPLIFIER £4.15.0

(4/- Carr.)

Brand new 200-240 A.C. mains. Bass, treble and vol. controls. With valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3½ x 3½ in. With o.p. trans. for 2-3 ohm speaker.

Front panel (normally screwed to chassis) may be removed and used as "flying panel". Stereo version 2 x 4 w. same price.

Send 6d. (stamps will do) for 20 page illustrated catalogue.

ALL ITEMS GUARANTEED 12 MONTHS—B.V.A. VALVES 3 MONTHS.—CLOSED SATURDAY.

## GLADSTONE RADIO "SCALA", CAMP ROAD, FARNBOROUGH, HANTS.

(See other advertisement on page 918)

### COMPLETE V.H.F./A.M. RADIO FOR £12.10.0

(carr. paid)



Brand new set, in superb walnut cabinet (size 19 x 8½ x 14½ in. high). Covering 80-100 Mc/s. 16-49 M., and 200-500 M. Mains trans. 200-250 v. with 2 tapings. Ferrite rod aerial for A.M. Controls: volume on/off, tone, tuning, w/change. Gram and ext. speaker position provided. Valves 12AT7, 12AH8, 6B6, EAB80 6BW6 and metal rectifier. Fully guaranteed. Today's Value £20.

**COLLARO STUDIO TAPE TRANSCRIBER. 3 MOTORS. 3 SPEED. 1½, 3½ and 7½ I.P.S. Push buttons. £10.17.6 (10/- carr.) incl. spoon.**

### SUPERIOR GRAMOPHONE AMPLIFIER 3 valves, 4 watt


13½ x 7 in. (2½ in. front to back). 3 front controls, bass, treble, vol./on-off. 6 in. circ. or 8 x 5 in. speaker; UY85, UF80 and UL84. Mains trans. 200-240ac; "gold" fret front. ONLY 70/- (p.p. 3/6).
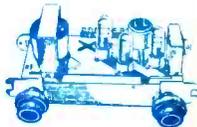
### GRAMOPHONE AMPLIFIER

With 5 in. SPEAKER Baffle 12½ x 6 in. EZ40 and EL41. Tone and Volume On/Off switch. Two Knobs. Ready to play. Useful for Stereo. ONLY 57/-, post 3/-.




**3-VALVE AMPLIFIER (INC. RECT.).** 2½ watts. ECC83, ECL82 and EZ80. Controls, volume bass and treble. On/Off switch. Overall size 10 x 4 x 4 in. over valves. Mains and O.P. trans. and 6½ x 4 in. Celestion speaker. Suitable for microphone input and for guitar amplifier. A.C. only.



70/- P. & P. 4/-.
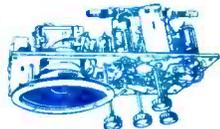
### MAINS OPERATED RADIO CHASSIS AND AMPLIFIER OF FAMOUS MANUFACTURE

Chassis 10 x 5½ x 4 in. front to back. Valves: UBC41, UCH41, UF89, UL84 with metal rectifier. 5 in. speaker. Ferrite rod aerial. Tone, vol. and gram. position. Covers L. and M. waves. Limited quantity at only £8 (5/- carr.) complete with small dial. Unused and in working order.



### UNREPEATABLE OFFER OF AM-FM CHASSIS AT ONLY £9.9.0 carr. pd.

A small quantity of Printed Circuit chassis by famous manufacturer. Valves UY85, UCH81, UF89, UAB80, UL84 and UCC85. O.P. trans. for 2-3 ohm speaker. Chassis 14 x 7 x 7 in. Front controls concentric, left—Vol. and Tone; right—W/C and Tuning. "Gold" centre knobs provided. 2-dial bulbs. Sockets, AE; E; Ext. sp; P.U. Mains isolating transformer free. Covers Long, Med., VHF (87-101 Mc/s). Unused slightly tarnished, but not dirty; New Mullard Valves; not our manufacture, so no guarantee. Dial in gold and brown, size 13 x 9 in.

Farnborough 3371

Tel: Mitcham 6201  
Open Daily to Callers

# R S T

All Valves Brand New  
and Fully Guaranteed

211 STREATHAM ROAD, MITCHAM, SURREY

Special 24 Hour Express Mail Order Service

AC2PEN 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
AC2PEN 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DD 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ACTP 32/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ACVP1 17/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
AZ1 15/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
AZ31 10/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
B36 10/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
C1C 12/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
CEB31 10/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
CC35 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
CL33 18/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
CY1 15/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
CY31 15/9	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
D77 4/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DAC32 9/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DAF91 7/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DAF96 8/9	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DDC90 14/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DF33 10/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DF91 4/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DF92 7/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DF96 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DF97 9/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DH63 6/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DH77 7/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DK32 11/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DK91 8/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DK92 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DK96 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DL33 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DL35 10/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DL92 7/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DL93 7/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DL94 8/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
DL96 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EAS0 2/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EABC80 6/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EAC91 4/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EAF42 9/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EB34 2/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EB41 7/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EB91 4/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBC3 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBC33 4/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBC41 9/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EB81 10/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBF80 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBF83 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBF89 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
EBL31 22/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC34 15/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC35 4/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC40 21/-	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC81 5/9	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC82 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC83 7/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC84 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC85 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC85 8/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6
ECC88 17/6	ECC91 4/-	EZ35 6/-	PCF80 9/6	U12 9/-	UY85 7/-	5Z4GT 12/6	6LD20 14/-	12C8 8/6

METAL RECTIFIERS

RM1 5/3	14RA 1-2-8-2	17/6 (FC31)	14A97	25/-
RM2 7/6	16RC 1-1-16-1	8/6	14A100	27/-
RM3 7/9	14RA 1-2-8-3	19/- (FC31)	16RD 2-2-8-1	12/-
RM4 14/-	18RA 1-1-16-1	6/6 (FC116)	16RE 2-1-8-1	8/6
RM5 19/6	18RA 1-2-8-1	11/-	18RA 1-1-8-1	4/6
14A86 17/6	18RD 2-2-8-1	15/- (FC124)		


SPECIAL OFFER

EABC80 6/-, EAC91 4/-, EB91 4/-, EBF89 8/6, ECC81 5/9, ECC85 8/-, ECC91 4/-, ECH81 8/-, EBC33 4/6, EF39 4/-, EF50 3/6, EF80 5/-, EF85 5/-, EF91 4/-, DF91 4/-, EL84 6/9, PCC89 9/6, PL84 9/-, UABC80 7/-, UBF89 7/6, UF41 7/6, UL41 8/6, UF89 6/6, UL84 7/-, UY85 7/-, W81 6/-, OZ4 5/-, 5U4 4/-, 6AQ5 6/6, 6BA6 6/-, 6BE6 6/-, 6D2 4/-, 6K7 2/-, 6K8 5/-, 6L6 7/6, 6Q7 6/6, 6SL7 6/6, 6SN7 5/6, 6V6 4/6, 6X5 5/-, 8D3 4/-, 807 5/-, 12AT7 5/-, 12AH8 9/-, 12BA6 7/6, 12BE6 7/6, 12K7 5/-, 12Q7 6/6.

TERMS OF BUSINESS C.W.O. or C.O.D.  
219 PACKING CHARGE ON ALL C.O.D.  
ORDERS. POSTAGE 6d. PER VALVE

OBsolete VALVES A SPECIALITY.  
QUOTATIONS GIVEN ON ANY TYPE  
NOT LISTED

**Fluorescent Lighting**

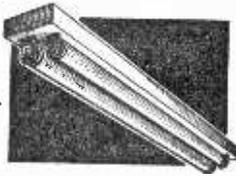

Complete lighting fittings. Built-in ballast and starters—stove enamelled white and ready to work. Ideal kitchen, workshop—anywhere. Twin 20 approximately 27in. long complete with two 20W tubes, 49/6. Single 40 approximately 4ft. long complete with one 40W tube, 39/6. Inductor 80 approximately 5ft. long complete with one 80W tube, 49/6. Carriage and insurance up to 150 miles 7/6, up to 250 miles 8/6. 21in. Miniature complete with 13 watt tube. Ideal for showcase or position where miniature fitting is required. Complete with latest 1/4in. diameter tube, 49/6 each. Circular. Complete with 40 watt tube, 24.19.6.


Carriage and ins. 7/6 any type.

**Smallest Possible 2-gang**



With built in trimmers, polystyrene cased, size only 1 x 1 x 7/16in., price 12/6. Smallest IF and oscillator to match. 21/- P.P. input and P.P. output transformers, 12/6. Circuit diagram free with any of above.

**Transistor Set Cabinets**

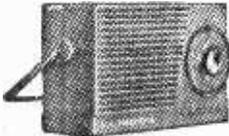

Very modern cream cabinet, size 5 1/2 x 8 x 1 1/4in. with chrome handle, tuning knob and scale. Price 7/6, plus 1/6 postage and packing. Special quotations for quantities.

**Miniature Earphones**



For Transistor Circuits or Deaf Aid Very lightweight and easy to wear. cord almost invisible, good quality production of music and voice, complete with miniature plug and socket, ready to use—correct impedance OK for red spot and similar transistors. Crystal and Magnetic, 9/-. Post and Insurance 1/-.


**SPECIAL TV SNIP!**

**BRAXHEAD TURRET TUNER**  
With valves 39/6  
Less valves 19/6  
Both plus 2/6 postage and insurance.

**TRANSFILTERS**

Save alignment problems and improve performance. Use instead of I.F. transformer. Complete with circuit 8/6 each.

**CHARGING SWITCHBOARDS**

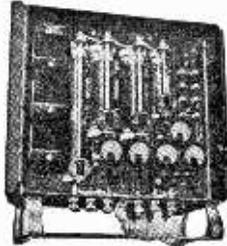

Type A. 550 w. 18 v.—contains three reverse current relays, one voltmeter rated 25 v. f.s.d., one main ammeter rated 40 amps. f.s.d., one secondary ammeter rated 15 amps. f.s.d. and two secondary meters rated 20 amps. f.s.d., one 2 ohm variable resistor, one 11 ohm variable resistor and two 1.2 ohm variable resistors. Complete in metal case 2ft. 6in. x 2ft. 8in. approx. Price £2.15.0. carriage and ins. 15/-.  
Type B. 1250 w. 60 v., 0.12 amps.—contains one 14 ohm variable resistor and four 1 ohm variable resistors, one main ammeter rated at 40 amps. f.s.d., four secondary meters rated at 20 amps. f.s.d. and one voltmeter rated at 50 volts, and two reverse current relays. Complete in metal case—size approximately 2ft. 6 in. x 2ft. 8in. Price £4.15.0, carriage 15/-.  
Connecting Leads for these switchboards with Nifam plugs 30/- each.

**BATTERY CHARGER BARGAIN**

**Components Would Cost More**

Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 5 amps. and variable rate selector for trickle charging. Also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.



**INFRA-RED HEATERS**

Make up one of these latest type heaters ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and instructions 15/6, plus 2/6 post and insurance.



**LIMITED QUANTITY ONLY!**

**Waterproof heater wire. 16 yds. length, 70 watts. Self regulating temperature control. 10/-. Post Free.**

**THIS MONTH'S SNIP!**


**"SUNVIC SIMMERSTAT" HEATER REGULATOR**, suitable to control elements or heaters up to 2,500 watts on A.C. The unit which is a ceramic body with bakelite case comprises a thermostat, adjustable for various temperature settings and in addition there is a heater coil so that the thermostat can be used as an intermittent make or break (simmerstat arrangement), thus giving complete control. **SPECIAL SNIP PRICE** of this unit is 12/6, plus 1/6 postage and insurance. **COPPER CLAD ELEMENT**, 1,500 watts, 230 volts, 2ft. long, 17/6 each. Post 2/6. Ideal for convector heater, which could be controlled by the above.

**"Dim and Full" Switch**

Particularly useful for controlling photohood lamps which have only a short life at full brilliance. This switch has three positions; the first position puts two lamps in series at half brilliance for setting up, the second position is off and the third position full brilliance for the operation shots. Also useful for controlling night lights, heaters, etc., etc. Price 3/6 each, post 3d. Circuit diagram included. Ditto but without the off position, i.e. d.p.d.t., 10 amp. 2/9.

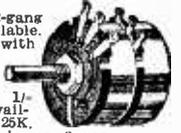**Morganite Potentiometers**

Single and 2-gang types available. Standard size with good length spindle, all new and boxed. Single types, 1/- each, values available: 5K, 10K, 25K, 50K, 100K, 200K, 1 meg., 2 meg. Gang type 3/- each—values available: 5K±5K, 10K±100K 1 meg. ± 1 Meg. 2 meg. ± 2 meg.



**Component Storage Drawers**



Stout board construction these drawers are ideal for small parts. Supplied complete with simple erection instructions—1/8 each or 12 drawers each 6 x 2 1/2 x 6 1/2in., 13/6, post 2/-.


**Waxley Switches**

1 Pole 3 Way	1/6
1 Pole 8 Way	2/6
1 Pole 8 Way	2/6
1 Pole 12 Way	3/6
2 Pole 2 Way	2/6
2 Pole 4 Way	2/6
2 Pole 6 Way	2/6
2 Pole 12 Way	4/6
3 Pole 3 Way	1/6
3 Pole 8 Way	3/6
4 Pole 4 Way	3/6
6 Position Short	3/6
6 Pole 3 Way	2/6
6 Pole 3 Way	3/6
6 Pole 2 Way	2/6
9 Pole 3 Way	2/6
12 Pole 2 Way	2/6

**All parts for the "P.W. CITIZEN" available**

Price as one parcel or separately. Please send for list.

**750mW TRANSISTOR AMPLIFIER**

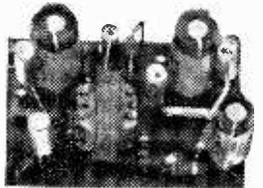


4 transistors including two in push-pull—input for crystal or magnetic microphone for pick-up—feed back loops—sensitivity 5 mV—output 1 watt, peak into 35 ohm speaker. Speakers available. Price 52/6. Postage and Insurance 2/6.

# A NEW LOOK FOR The "GOOD COMPANION" CAR RADIO & PORTABLE


One of the finest of its kind available. The design is the combined efforts of our technicians and of those of several of the leading manufacturers in the country, and the resulting set has a performance as good as, if not superior to, those selling at £20 and more—it has the eight transistor set performance. Features include American Philco R.F. transistors and Mullard A.F. transistors—Q.P.P. output giving 750 mW—full coverage on Medium and Long—very fine tuning arrangement—excellent reception of difficult stations like 208—variable feed-back control—full tonal qualities—really superior looking cabinet size 11 x 8 x 3in. approximately—car aerial attachment—several months' operation from battery costing only 3/6.

Circuit employs six transistors and two diodes, it incorporates all latest refinements, and oscillator. I.F. Transformers are pre-aligned so no instruments are necessary. Anyone who can solder competently can make this set. The instructions are fully comprehensive with plenty of illustrations. Service is available in the unlikely event of your getting into difficulties. All components fully guaranteed.

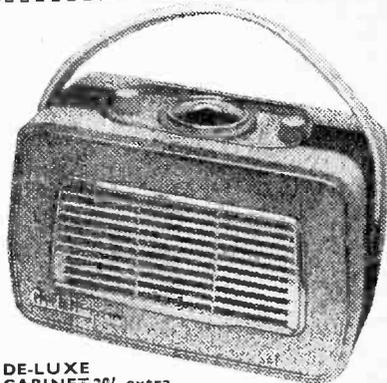**Price of all components £9.19.6** Post and Insurance 5/-  
and Standard Cabinet Battery 3/6 extra.  
or with De Luxe Cabinet £1 extra.



DE-LUXE CABINET 20/- extra

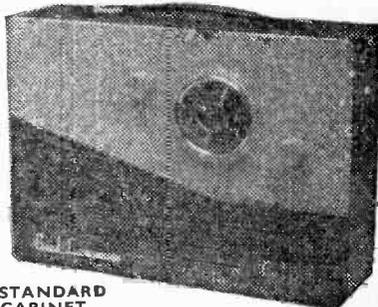

STANDARD CABINET

**MK. 2** uses latest ceramic transistors in place of the normal I.F. transformers. This saves alignment problems and improves performance. Price 10/- extra.

**AGENTS** wanted to build up our Companion Receivers. Send addressed envelope for full particulars.

## The "POCKET COMPANION" is now ready!


This is without doubt the most modern and best pocket set available. It uses the very latest I.F. transistors. Philco R.F. transistors, airspaced tuning condenser in Superhet circuit covering M.W. and L.W. Complete building cost £6.15.0. Battery 2/-. Post and Ins. 2/6. Data free with parts or separately 2/6.

## MOST AMAZING BARGAIN!

All components for the  
**IMPROVED PIMPERNEL**  
**5 Transistor Radio**  
that works really well!

ONLY  
**69/6**

Postage and Insurance 2/6  
Battery 2/-

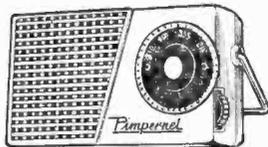


This remarkable little receiver uses 5 transistors and 2 diodes. 3in. Moving Coil Speaker. Tuning Condenser. Volume Control with On/Off switch, latest type circuitry giving excellent station separation and ample volume at good tone. Push-pull output circuit ensures long life from PP4 battery.

All components included for Medium Wave operation in handsome plastic case with carrying handle as illustrated. **Demonstrations at all branches** Circuit diagram FREE with parts or 2/- separately.

**OPTIONAL EXTRAS**  
All components and switch for Long Waves 8/6  
Motit "Pimpernel" 2/-
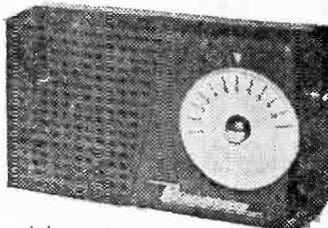
## THE POCKET "4"

Proved without  
doubt the  
easiest of all  
to make!



Circuit comprises 2 HF transistors reflexed to equal 4 stages. Permanent germanium diode and high gain AF output stage, fitted with miniature speaker, proper tuning condenser, volume control and in case with handle as illustrated (less monogram), completely portable. No aerial or earth required. **Pocket 4** uses 3 transistors and 1 diode, price 42/6, plus 2/6 post and Insurance.

**Pocket 5** uses 4 transistors and 1 diode and has feedback control, price 55/-, plus 2/6 post and insurance. Prices are for medium wave models; long or medium versions 6/6 extra.

### GOOD RESULTS EVERYWHERE

Nothing can be more disappointing than to find that despite care in making up, your radio just will not work or needs a long high aerial and water pipe earth. We can prove good results in all areas and we guarantee all components for 12 months. Hundreds of testimonials received. Send in confidence. Plans free with parts, or separately 1/6. Demonstrations at all branches.

## ELECTRONIC PRECISION EQUIPMENT LTD.

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road, Eastbourne, marked Department 7. Callers may use any one of the Companies below.

288 London Road,  
Croydon.  
Phone: CRO 5558  
Half day Wednesday

29 Strand Green Rd.,  
Finsbury Park, N.4.  
Phone: ARChway 1049  
Half day Thursday

520 High Street North,  
Manor Park, E.12.  
Phone: ILFord 1011  
Half day Thursday

42-48 Windmill Hill,  
Ruislip, Middx.  
Phone: RUISlip 6730  
Half day Wednesday

246 High Street,  
Harlesden, N.W.10.  
Phone: ELGar 4444  
Half day Thursday

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

OA2	17/6	6F1	27/2	12AC6	15/3	77	8/-	DL68	15/-	EF50(A)	7/-	HVR2	20/-	PY32	12/6	UBL21	23/10	Transistors
OB2	17/6	6F6G	7/-	12AD6	17/8	78	6/6	DL72	15/-	EF50(E)	5/-	HVR2A	6/-	PY80	7/6	UCC84	14/11	and diodes
OZ4	5/-	6F12	4/6	12AE6	14/3	80	6/6	DL94	7/6	EF54	5/-	KF35	8/6	PY81	8/6	UCC85	9/6	CGIC
IA5	6/-	6F13	11/6	12AH7	8/-	83	15/6	DL94	7/6	EF73	10/6	KL35	8/6	PY82	7/6	UCF80	17/-	CG46
IA7GT	12/-	6F23	10/6	12AH8	12/6	85A2	6/6	DL96	8/6	EF80	6/-	KLL32	25/2	PY83	8/6	UCH21	23/10	CG66
IC5	12/6	6F24	12/6	12AT6	7/6	90AG	6/6	DL96	8/6	EF86	10/6	KT2	5/-	PY88	13/7	UCH42	9/6	CG76
ID6	10/6	6F33	7/6	12AT7	6/-	90AV	6/6	DL96	8/6	EF86	10/6	KT33C	5/-	PZ30	20/5	UCH81	9/6	CG10E
IG6	17/6	6H6	3/-	12AU7	6/6	90C1	6/6	EB3F	30/-	EF89	9/-	KT36	30/7	QP21	7/-	UCL82	11/6	CG12E
IHSGT	10/6	6J5	5/-	12AX7	7/6	90C3	37/6	EB3F	30/-	EF91	4/6	KT41	23/10	QP25	14/6	UCL83	19/9	GD3, 4, 5
IL4	3/6	6J6	5/6	12BA6	8/-	101	13/6	EA50	2/-	EF92	4/6	KT44	12/6	QS150/15		UF41	9/-	6, 8
ILD5	5/-	6J7G	6/-	12BE6	9/-	150B2	18/-	EA76	9/6	EF97	13/7	T61	12/6	R12	14/-	UF42	12/6	OA70
ILN5	5/-	6J7GT	10/6	12BH7	21/9	185BT	34/-	FABC80	9/6	EF98	13/7	KT53	7/6	R18	14/-	UF80	10/6	OA73
INSGT	10/6	6K7G	5/-	12J5GT	4/6	304	10/6	EAC91	4/6	EF183	19/11	KT66	15/-	R19	20/5	UF85	9/6	OA79
IR5	6/6	6K7GT	6/-	12J7GT	9/6	305	10/6	EAF42	9/6	EF184	12/6	KT88	24/-	RG1/240A		UF86	10/6	OA81
IS4	9/-	6K8GT	10/6	12K5	18/4	807	7/6	EB34	2/6	EK32	8/6	KTW61	6/6	SP4(7)	14/6	UL44	27/2	OA86
IS5	6/-	6K8G	6/6	12K7GT	5/6	956	3/6	EB41	8/6	EL32	5/-	KTW62	7/6	SP41	3/6	UL46	14/6	OA95
IT4	3/6	6K25	20/5	12K8GT	14/-	1821	17/6	EB91	4/-	EL33	12/6	KTW63	6/6	SP42	12/6	UL84	8/6	OA211
IU5	6/-	6L1	23/10	12Q7GT	5/-	4033L	12/6	EB33	23/10	EL34	15/-	KZT41	8/-	SP43	3/6	UL84	17/8	OC19
3A4	27/2	6L6G	8/-	12SA7	8/6	5763	12/6	EBC33	5/-	EL38	27/2	KTZ63	7/6	SP44	12/6	UM4	17/8	OC22
3A5	10/6	6L6GT	9/6	12SC7	8/6	7193	5/6	EBC41	8/6	EL41	9/-	L63	6/-	SP45	3/6	UM4	17/8	OC22
3B7	12/6	6L8	13/-	12SH7	8/6	7475	7/6	EBC81	8/-	EL42	10/6	MHL4	7/6	SP46	3/6	UM34	17/8	OC19
3D6	5/-	6LD20	16/4	12S17	8/6	AC/PEN		EBF80	9/-	EL81	17/-	MHLD6	12/6	SU25	27/2	UM80	15/8	OC22
3Q4	7/6	6M7	8/-	12SK7	8/6	5-p-pin	23/10	EBF89	9/6	EL83	20/5	ML4	8/6	T41	9/-	URIC	19/11	OC23
3Q5GT	9/6	6P28	27/2	12SQ7	6/-	7-p-pin	15/-	EBL1	30/6	EL85	14/3	M54B	23/10	TDD4	12/6	UU6	20/5	OC26
354	7/-	6Q7G	6/6	12SR7	8/6	AC/PEN		EBL21	23/10	EL86	17/8	MU12/14	8/-	TH41	27/2	UU8	27/2	OC28
3V4	7/6	6Q7GT	11/-	12Y4	10/6	AC/PEN		EBL31	23/10	EL91	5/-	N78	20/5	TP25	15/-	UYIN	19/11	OC29
5R4Y	17/6	6R7G	10/-	19AQ5	10/6	AC/PTP	34/-	EL95	10/6	EL820	19/11	N108	23/10	TP2620	34/-	UY41	7/6	OC35
5U4G	6/6	6S7AGT	8/6	19H1	10/6	AC/PTP	34/-	EL821	27/2	EL822	19/6	N339	15/11	TY86F	13/7	UY85	7/6	OC45
5V4G	10/6	6SCT	7/6	20D1	15/8	ATP4	5/-	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
5Y3	6/6	6S7GT	8/-	20F2	27/2	AZ1	19/1	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
5Z3	20/5	6H7GT	8/-	20L1	27/2	AZ31	10/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
5Z4G	9/-	6S7GT	8/-	20P1	27/2	AZ41	14/3	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6A7	10/6	6S7GT	8/-	20P3	23/10	B36	15/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6A8	9/-	6S7GT	8/-	20P4	27/2	BL63	7/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AC7	4/-	6SN7GT	5/6	20P5	23/10	C1	12/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AG5	5/6	6SQ7GT	9/-	25A6G	10/6	CIC	12/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AG7	7/6	6S7GT	8/-	25L6GT	10/-	CBL1	27/2	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AK5	7/6	6U4GT	12/6	25Y5G	10/-	CBLL31	23/10	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AL5	4/-	6U5G	7/6	25Z4G	9/6	CCH35	23/10	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AM6	4/6	6U7G	8/6	25Z5	9/6	CK506	6/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AQ5	7/6	6V6G	7/-	25Z6G	10/-	CL33	19/9	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AT6	7/-	6V6GTG	8/-	27S5	20/5	CV63	10/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6AU6	10/-	6X4	5/-	28D7	7/-	CY1	11/1	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6B8	5/6	6XS7G	6/-	30C1	8/-	CY31	11/1	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6BA6	7/6	6Y30L2	10/-	30F5	6/-	D15	10/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6BE6	6/-	7B7	8/6	30L1	10/-	DAC32	10/6	EL821	27/2	EL822	19/6	P61	3/6	U16	10/6	VMS45	15/8	OC66
6BG6G23/10	7C5	8/-	30L1	8/-	DAF91	6/6	ECH21	23/10	FC4	15/6	PEN45	4/6	U201	17/-	X41	15/12	TJ1	40/-
6BH6	8/-	7C6	8/-	30L15	11/6	DAF96	8/6	ECH35	6/6	FV4/500	8/6	PEN46	7/6	U281	20/5	X61(C)	12/6	TJ3
6BJ6	6/-	7H7	8/-	30P4	12/-	DD4	14/3	ECH42	9/-	FV4/800	8/6	PEN383	U282	23/2	X66	12/6	TP2	40/-
6BQ7A	15/-	7R7	12/6	30P12	7/6	DF25	7/6	ECH81	9/-	GU50	4/16	PEN/DD	U329	14/-	X76M	14/-	TS2	12/6
6BR7	12/6	757	9/6	30P11	10/6	DF33	7/6	ECH83	14/3	GZ30	9/-		U339	17/-	X78	23/10	TS3	15/1
6BR8	19/1	7V7	8/6	30PL13	13/6	DF66	15/6	ECH89	9/-	GZ32	10/5		PL33	19/9	U403	17/-	X79	23/10
6BW6	8/6	7Y4	7/6	35A5	21/9	DF91	3/6	ECL82	19/9	GZ34	14/-		PL36	12/-	U404	8/6	X109	17/8
6BW7	6/-	8D2	3/6	35L6GT	9/6	DF96	8/6	ECL83	19/9	GZ37	20/5		PL38	27/2	U801	30/7	XD(1.5)	6/6
6C4	5/-	89W6	15/8	35V4	7/6	DF97	9/6	ECL86	17/6	GZ37	20/5		PL81	10/6	U4020	19/11	XFG1	18/5
6C5	6/6	9D2	4/-	35Z3	19/1	DH63	6/6	EF9	23/10	HABC80			PL82	7/6	UABC80	9/-	XFY12	9/6
6C6	6/6	10C1	13/-	35Z4GT	6/-	DH76	5/6	EF22	14/1	HL2	13/6		PL83	9/-	UJAF2	9/6	XFY34	18/-
6C9	13/6	10C2	27/2	35Z5GT	9/-	DK32	12/6	EF36	4/-	HL2	13/6		PL84	13/-	UB4	12/-	XG(1.5)	6/6
6C10	9/-	10F1	27/2	43	10/-	DK91	6/6	EF37A	4/-	HL23	15/8		PL84	13/-	UB4	12/-	XG(1.5)	6/6
6CD6G	37/5	10LD11	16/4	50C5	10/6	DK92	9/-	EF39	5/6	HL23DD	7/6		PL820	19/11	UBC41	8/6	XG(1.5)	6/6
6CH6	9/-	10P13	15/-	50CD6G		DK96	8/6	EF40	15/6	HL42DD			PMB4	17/8	UBC81	11/6	Z66	7/6
6D6	6/6	10P14	19/9			DL33	9/6	EF41	9/-				PX4	10/6	UBF80	9/6	Z66	7/6
6E5	12/6	12A6	5/-	50L6GT	9/6	DL66	17/6	EF42	10/6	HN309	27/2	PY31	17/-	UBF89	9/6	Z77	4/6	XCT10

PLEASE NOTE THAT WE DO NOT SELL SECONDHAND GOODS OR MANUFACTURERS' RESISTORS

Resistors, 1/2 watt 5d., 1 watt 6d., close tol. 1/-; Standard tubular condensers, .001-0.1mFd 9d.; Midget ceramics, any size, 9d.; Low voltage electrolytics 1/6; Sub-miniature electro-lytics, 3/-; Wire-wound resistors, 5 watt 1/3, 10 watt 1/6; Filament transformers, 6.3 v. tapped at 4 and 2 v., 10/6; Valveholders from 5d.; Volume controls, less switch 3/- with double pole switch 4/6; Mains droppers, 1 amp, 2000 ohm, .15 amp, 1500 ohm 6/-, .2 amp, 1000 ohm, .3 amp, 1000 ohm, 6/6.

Line output transformers, scan coils, horizontal and vertical output TX's, horizontal and vertical blocking TX's. Delivery from stock. S.A.E. for quote or sent C.O.D. Prices from 39/6.

### ALL GOODS BRAND NEW, SUBJECT TO FULL MAKERS' GUARANTEE, AND ACTUALLY IN STOCK.

WAVE CHANGE SWITCHES. ALL 5/3		METAL RECTIFIERS Full List with ratings free for S.A.E.									
1 pole, 3 way, 2 pole, 6 way	DRM18 13/-	RM-1	7/3	14A86	17/6	14B130	33/-	14RA 1-2-8-3	21/-	18RA 1-1-16-1	6/6
1 pole, 12 way, 3 pole, 4 way	DRM28 15/6	RM-2	5/6	14A97	25/-	14B261	11/6	(FC31)		(FC116)	
4 pole, 2 way, 4 pole, 3 way	LW7 21/-	RM-4	14/-	14A100	27/-	14RA 1-2-8-2	17/6	16RD 2-2-8-1	12/-	18RA 1-2-8-1	11/-
	RM-0 7/11	RM-5	19/6	14A124	28/-	(FC101)		16RE 2-1-8-1	8/6	18RD 2-2-8-1	15/-
				14A163	38/-	16RC 1-1-16-1	8/6	18RA 1-1-8-1	4/6	(FC124)	

### JUST OUT. MIDGET SILICON RECTIFIERS. OUTPUT 120 VOLTS AT 1 AMP. TWO IN SERIES GIVE 240 VOLTS AT 1/2 AMP. NO LARGER THAN A RESISTOR. 8/6 EACH.

ELECTROLYTIC CONDENSERS		Wire-ended tubular	
Standard Can	32 x 32 mid., 450 v. 5/9	200 mid., 275 v. 9/6	8 x 8 mid., 450 v. 3/-
	50 x 50 mid., 350 v. 7/1	100 x 400 mid., 275 v. 12/6	16 x 16 mid., 450 v. 4/-
	64 x 120 mid., 350 v. 8/3	100 mid., 275 v. 3/-	32 x 32 mid., 350 v. 4/-

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the *RIGHT* course

RADIO & TELEVISION ENGINEERING  
INDUSTRIAL TELEVISION

RADIO & TELEVISION SERVICING  
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC  
COMPUTERS & PROGRAMMING

ICS provides thorough coaching for professional examinations:


Brit. I.R.E., City and Guilds Telecommunication Technicians, C. & G. Radio & TV Servicing (R.T.E.B.); C. & G. Radio Amateurs.

## LEARN AS YOU BUILD

### Practical Radio Courses

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-meter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.
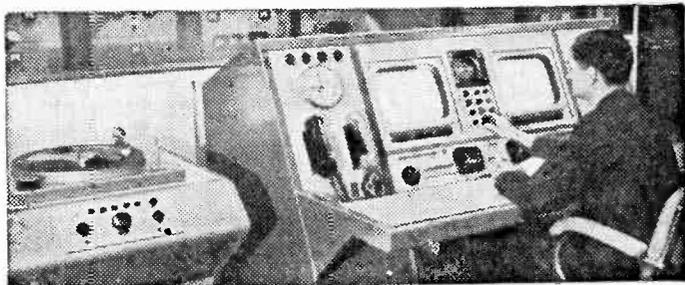
# Technical Training in Radio, Television and Electronics Engineering with



**THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.**

You will receive the **FREE** 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialised subjects.

Other ICS courses include: **MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING, FARMING, GARDENING, ARCHITECTURE & WOODWORKING, SELLING & MANAGEMENT, ART, PHOTOGRAPHY,** etc., etc.

**PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . .**



**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
(DEPT. 170) INTERTEXT HOUSE, PARKGATE RD., LONDON, SW11

PLEASE SEND FREE BOOK ON.....

NAME .....

ADDRESS .....

.....

OCCUPATION..... AGE.....

2,62

# GREAT OBSOLETE VALVE LIST

**DON'T DISCARD THAT OLD SET! GET A NEW VALVE FROM US AND KEEP IT WORKING.**  
**—ALL VALVES NEW GUARANTEED IN ORIGINAL BOXES & GENUINE MULLARD, MAZDA, MARCONI, ETC. POSTAGE & PACKING 6d. PER VALVE.**


AS30D 9/6	D4	5/-	EL3	5/-	KT36	28/-	P41	9/-	R3	9/-	U951	11/-	X24	21/-	6AG5	4/-	68J7	8/-	19X3	8/80	9/-		
AS5A 9/6	D41	10/6	EL31	5/-	KT41	17/6	P215	8/-	RG1	35/-	U282	18/6	LA6 C	11/-	614	5/-	68J7GT	8/-	20P2	18/83	12/-		
AS5N 12/6	CV140	10/6	EL32	5/-	KT42	22/-	PA20	9/-	R11A	9/-	U309	18/6	X81	10/-	6B5	5/-	68K7	6/-	20P1	18/84	12/-		
AT0B 12/6	D42	10/6	EL33	12/6	KT44	12/-	PO/PEN	8/11D	9/-	U339	14/-	X71M	12/-	617	6/-	68K7M	6/-	20P4	18/85AI	12/-			
AT0C 17/6	D03	5/-	EL34	15/-	KT45	12/-	(Terminal)	8/13DM	10/-	U403	15/-	X89	5/-	617M	7/6	68Q7GT	9/-	25AG6	10/87	12/-			
AT0D 17/6	D03	5/-	EL35	18/6	KT46	12/6		8/13DM	10/-	U420	9/-	Y83	6/-	688G	5/-	85Y8	8/-	25L6	10/89	12/-			
AC/PEN	D433	10/-	EL37	18/6	KT66	12/6		8/13DM	10/-	U420	9/-	Y83	6/-	688G	5/-	85Y8	8/-	25L6	10/89	12/-			
AC/HL 23/3	DA41	10/6	EL38	18/6	KT71	12/6	PL33	18/-	SD20	9/-	U441	10/-	Z31	12/-	689G	12/-	679T	12/-	25V3G	10/-	117Z6GT		
AC/ME 15/6	DC/HL	10/6	EM1	12/6	KT76	12/6	PM2	7/-	SD61	9/-	U441	10/-	Z31	12/-	689G	12/-	679T	12/-	25V3G	10/-	117Z6GT		
AC/PC 16/6	DC SG 10/6		EM4	12/6	KT76	12/6	PM2A	7/-	SD61	9/-	U441	10/-	Z31	12/-	689G	12/-	679T	12/-	25V3G	10/-	117Z6GT		
AC/SP1 12/6	DC/PEN	EN/1	EN/1	32/-	KT241	7/-	PM2HL12	12/-	SP4 (5 Pin Side)	8/13DM	10/-	U441	10/-	Z31	12/-	689G	12/-	679T	12/-	25V3G	10/-	117Z6GT	
AC/SG 10/6		EN/2	EN/2	9/-	KT263	7/-	PM2M 9/-	Me/8	12/6	U11C	14/6	Z8159	12/-	6C8	12/-	6X5	5/-	60P4	11/-	202STH	16/6		
AC/62PEN	DD138	18/6	EZ3	9/-	L12	6/-	PM3	9/-	SP4B	12/6	UR3	16/-	Z8160	12/-	6C8	12/-	6X5	5/-	60P4	11/-	202STH	16/6	
AC/52 18/6	DD43	12/6	FC2	15/-	L21	6/-	PM3A	9/-	SP6	12/6	U7	15/-	LA4E	9/-	6C15	8/-	6X5G	6/-	31	12/-	202VPB	16/6	
AC/8XV17	DD207	10/6	FC13	15/-	L63	6/-	PM4	9/-	SP13	12/6	U8	13/-	LA3GT	6/-	6C15	8/-	6X5G	6/-	31	12/-	202VPB	16/6	
AC/7E 30/-	DD620	10/6	FC13C	15/-	L2	6/-	PM4DX	9/-	SP13C	12/6	U30/250	18/6	IC5	5/-	6C15	8/-	6X5G	6/-	31	12/-	202VPB	16/6	
AC/TH18/6	DD4020		FW4/500		LP4	6/-	PM5B	9/-	SP14	12/6	U60/250	18/6	IC5GT	12/-	6D8	6/6	625/12Z5	35A5	17/6	190THA	16/6		
AC/VP15/-	DDL-4	8/6	GTIC	8/6	LV136	12/6	PM12M	9/-	SP43	12/6	(4 Pin)	18/6	IC6	10/-	618G	6/6	635E	5/6	17/6	210DG	16/6		
AC/HL 10/6	DDT2	8/6	GTD4B	10/6	ME41	12/-	PM22D	10/-	SP132	12/6	Y11	15/-	IF5	10/-	6P1	18/6	7A7A	17/6	30ZA	17/6	210LP	16/6	
AC/SPEN	DDT13	10/6	GTDC4C	10/6	ME91	12/-	PM24A	10/-	SP141	12/6	Y14	12/-	IF6	10/-	6P6G	7/6	78	14/6	30	12/-	201VA	16/6	
AC3 17/6	DDT19	5/6	G11	22/-	MH4	7/6	PM24M	10/-	SP210	12/6	VL8631	11/-	IF7	10/-	6P7	7/6	7C5	7/6	3944	11/-	215SG	16/6	
AC4 10/6	DDT22	5/6	G12	22/-	MH4	7/6	PM25	10/-	SP215	12/6	VM84B	12/6	IG6GT	10/-	6F8	9/-	7C8	7/6	40	11/-	220HT	16/6	
AC5/PEN	DL63	18/-	H30	12/6	(5 Pin)	14/6	PM220	10/-	SP120	12/6	Y04	12/6	IL6A	12/6	6F8G	9/-	713	9/-	408UA	14/-	18/6		
AC5/PEN	DL72	12/6	H42	12/6	MH14105	10/6	PM2410	10/-	SP220	12/6	Y04	12/6	IL6A	12/6	6F8G	9/-	713	9/-	408UA	14/-	18/6		
AC5/PEN	DL72	12/6	H42	12/6	MH14105	10/6	PM2410	10/-	SP220	12/6	Y04	12/6	IL6A	12/6	6F8G	9/-	713	9/-	408UA	14/-	18/6		
DD 12/6	DL810	10/6	H24	12/6	MH14105	10/6	PM2410	10/-	SP220	12/6	Y04	12/6	IL6A	12/6	6F8G	9/-	713	9/-	408UA	14/-	18/6		
AG5 10/6	DN41	7/6	H24	12/6	MH14105	10/6	PM2410	10/-	SP220	12/6	Y04	12/6	IL6A	12/6	6F8G	9/-	713	9/-	408UA	14/-	18/6		
AGX2270	DC20	10/6	HP4101	10/6	(5 Pin)	14/6	PP13A	9/-	SU2150A	10/6	(6 Pin)	10/6	1Q5	9/-	6P15	14/6	707	11/-	41MHL	12/-	304	10/6	
AL 10/6	DC25	10/6	HP4106	10/6	(7 Pin)	14/6	PP321	9/-	SU2150A	10/6	(6 Pin)	10/6	1Q5	9/-	6P15	14/6	707	11/-	41MHL	12/-	304	10/6	
APP4 8/6	DW2	12/6	HP4106	10/6	(7 Pin)	14/6	PP321	9/-	SU2150A	10/6	(6 Pin)	10/6	1Q5	9/-	6P15	14/6	707	11/-	41MHL	12/-	304	10/6	
APP4B 17/6	DW4/500		HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4 8/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9/-	41MPC	12/-	402P	18/6	
APP4B 17/6			HP4115	10/6	M14	7/6	PT230	10/-	T4D	10/6	VP23	5/6	1W4/500	14/6	6H16	3/6	81A	9					

# HARVERSON SURPLUS CO. LTD.

PLEASE TURN OVER FOR ADDRESS AND MORE BARGAINS
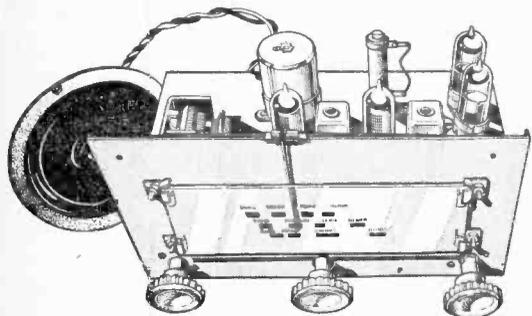
## 2 BAND SUPERHET CHASSIS with Speaker

**ONLY £4.19.6**  
Plus 6/6 Post & Packing.




A quality 4 valve AC/DC superhet chassis made by a world famous manufacturer. Long and Medium wave coverage. Fitted with a cord and drum reduction tuning drive and attractive illuminated glass dial (size 6½ x 2½in.). Controls: Volume on/off, tuning and wave change. The receiver is self-powered, employing a mains dropper and a valve rectifier. Chassis dimensions 6½ x 9 x 5½in. high. Supplied complete with a good quality 5-inch loudspeaker, valves (UCH42, UAF42, UL41, UY41), AC/DC mains input lead, ivory knobs, etc.

**DON'T HESITATE, ORDER NOW!** This unbeatable bargain is bound to sell out quickly at only £4.19.6, plus 6/6 post and packing.


## 4 STATION PRESET CHASSIS with Speaker

**ONLY £4.17.6**  
Plus 6/6 P. & P.

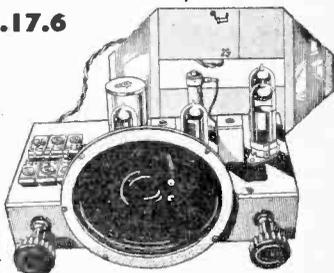


A compact, 4 station preset mains transportable receiver for operation from AC/DC mains. Two simple controls, volume on/off and 4 position station selector. The latter is set to Light Programme (Long Wave), Third Programme, Home Service and Light Programme (Medium Wave), but may of course be adjusted to alternative selections if required. A frame aerial with throw-out extension is supplied, making this receiver ideal as a general purpose transportable set for the home. A fully smoothed power supply is provided from AC/DC mains input by a mains dropper and a valve rectifier. The good tonal qualities are assisted by the provision of a quality 5in. speaker, which is ready-mounted on the chassis (this is easily detachable if alternative positioning is required). Valve line up, UCH42, UAF42, UL41, UY41. This chassis (size 9 x 6½ x 5½in. high) is supplied complete with valves, knobs, mains lead, aerial, etc. It is beautifully made by a famous maker, and is a first-class buy at the rock bottom price of only £4.17.6, plus 6/6 post and packing.

## A.M. RADIOGRAM CHASSIS

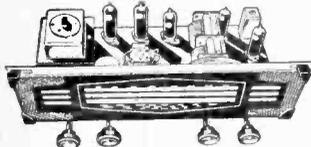

A chassis of distinction, by a famous maker. Covering Long, Med. and Short Waves, plus gram position, this chassis (size 15½ x 7 x 6½in. high) incorporates the latest circuitry, using fully delayed A.V.C., and negative feedback. Controls: Tone, Vol. On/Off, W/Change (L.M.S. and Gram), Tuning. Tapped input 200-250 v. A.C. only. An attractive brown and gold illuminated dial with matching knobs, make this one of the most handsome, in addition to being one of the best performing chassis yet offered. Complete with valves (ECH81, EF89, EBC81, EL84, EZ81), knobs, output transformer, leads, etc. **OUR PRICE ONLY £9.19.6**  
4/6 post plus & picking.


## HARVERSONS' F.M. TUNER

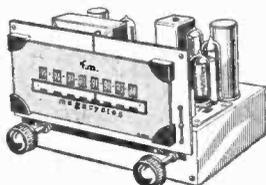

At last a quality F.M. Tuner Kit at a price you can afford. Just look at these fine features which are usually associated with equipment at twice the price.

- ★ F.M. Tuning Head by famous maker.
- ★ Guaranteed Non-drift.
- ★ Permeability Tuning.
- ★ Frequency coverage 88-100 Mc/s.
- ★ OAB1 Balanced Diode Output.
- ★ Two I.F. Stages and Discriminator.
- ★ Attractive maroon and gold dial (7 x 3in. glass).
- ★ Self powered, using a good quality mains transformer and valve rectifier.
- ★ Valves used ECC85, two EF80's, and EZ80 (rectifier).
- ★ Fully drilled chassis.
- ★ Everything supplied down to the last nut and bolt.
- ★ Size of completed tuner 8 x 6 x 5½in.
- ★ All parts sold separately. **£4.19.6**
- Plus 8/6 P.P. and Ins.
- ★ Circuit diagram and illustrations, 1/6 post free.

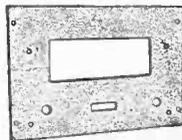**NOW AVAILABLE** A robust cabinet made from heavy gauge metal which has been specially designed to house the above F.M. Tuner. Beautifully finished in a choice of glossy hammer green, or hammer grey enamel, or black crackle. The front panel (illustrated) has holes for control spindles, and apertures for tuning dial and magic eye.  
**PRICE 25/-** P. & P. 1/9. (Front panel only 10/6, P.P. 9d.).



## SPECIAL OFFER

### MIDGET 2 GANG CONDENSERS

Polystyrene cased, with built-in trimmers. Size 1 x 1 x 1/8 ins. Not used, but removed from printed circuit boards.

**UNBEATABLE VALUE 2 for 9/-**  
P. & P. 1/-


## MAINS PORTABLE SOLDERING IRON

Probably one of the most outstanding soldering instruments yet produced, this iron has a detachable handle which can be placed over the bit and barrel, enabling it to be carried in complete safety even when hot. The provision of an extremely stable 30w element makes this ideal for transistor and all similar lightweight applications. Brand new in P.V.C. bag, with lead and plug. **ONLY 18/9**, plus 1/3 P. & P.

## MINIATURE EARPHONE WITH CORD SUB-MINIATURE PLUG AND SOCKET

A deaf aid type earpiece of top grade quality. Gives an exceptionally crisp reproduction of both speech and music. Brand new and fully guaranteed. Two types available. CR-5 high impedance crystal, MR-4 low impedance magnetic. **ONLY 7/6** Plus 1/- P. & P.

## F.M. TUNER HEAD

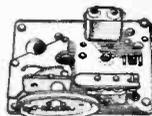

A permeability tuned tuner head by a famous maker, supplied without valve (ECC85) 18/6 plus 1/9 P. & P. Valve 8/6 extra.

# HARVERSON SURPLUS CO. LTD.

## Introducing HARVERSON'S Monaural Amplifier Kit

### 39/6

In response to numerous requests from delighted purchasers of our "SUPER STEREO KIT" we have produced a "MONAURAL AMPLIFIER" on similar lines.

★ A UCL 82 valve provides a triode amplifying stage, and a pentode output stage (3 watts), enabling good amplification and sparkling reproduction to be combined with physical compactness (amplifier size, 7 x 3½ x 8½in. high).

★ Modern circuitry design, good quality O.P. transformer (to match 3Ω) keep hum and distortion to a low level.


★ The controls, volume on/off, and tone, are complete with attractive cream and gold knobs.

★ The amplifier has a built-in fully smoothed power supply, using a good quality mains transformer (A.C. mains only) and metal rectifier.

★ All you need is supplied including easy to follow instructions which guarantee good results for the beginner and expert. All components, leads, chassis, valve, knobs, etc., are first grade items by prominent manufacturers.

**OUR PRICE 39/6**  
Plus 1/6 Post and Packing.

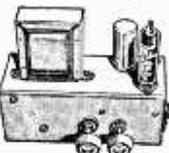5in. LOUDSPEAKER TO SUIT 14/6 —EXTRA  
ALL PARTS SOLD SEPARATELY



## THE HARVERSON 6 TRANSISTOR & DIODE SUPERHET KIT

A first class 2 wave band transistor superhet in kit form.

- ★ Printed circuit panel (size 8½ x 2½ins.)
- ★ 3 Pre-aligned I.F. Transformers.
- ★ Output Transformer.
- ★ 5 inch 5 Ω Speaker.
- ★ High gain Ferrite rod aerial.
- ★ First grade G.E.C. transistors.
- ★ Car aerial socket.
- ★ Push/Pull output.

All parts down to the minutest item with simple instructions. ONLY

**£6.19.6** Plus 2/6 P. & P.

Cabinet to Suit (if available) 15/- extra.



## BARGAIN MONTH FOR TRANSISTORS

POWER	GET15 ... .. 9/-
OC36 ... .. 10/-	GET15 (matched pr.) ... 16/6
OC44 ... .. 9/-	GET102... .. 7/6
OC45 ... .. 8/-	XAI03 ... .. 8/6
OC71 ... .. 5/-	PXA101 ... .. 9/6
OC75 ... .. 6/6	PXA102 ... .. 9/6
OC76 ... .. 6/6	
OC78 ... .. 6/6	<b>DIODE</b>
OC78D ... .. 6/6	OA81 ... .. 3/-

Please add 6d. postage for each transistor.

### TRANSISTOR SPEAKER

Western Electric 3Ω or 80Ω speaker. Size 2½ x 1½in. deep. 12/6 p.p. 1/-.

### SUPERHET CHASSIS—less Valves & Cabinet

Modern AC/DC chassis with printed circuit and ferrite rod aerial. Although not completely built, the main components are mounted. L. & M. wave coverage, 4 valves (UBF89, UCL83, UCH81, UY85). Everything supplied except valves and cabinet. With speaker and simple instructions. **£3.6.6** plus 3/6 P. & P.

### COIL and TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. Transformers, one oscillator coil, one driver transformer, and wound ferrite aerial (Med., Long and aerial coupling) 28/6 complete, post 1/-. 6 transistor printed circuit board to match 8/6, post 9d. Circuit diagram 1/6 extra.

### CONDENSER/RESISTOR PARCEL

50 mixed P.F. Condensers and 50 mixed Resistors. An assortment of useful valves. All popular sizes—all new—a must for the serviceman and constructor **ONLY 10/-** P. & P. 1/-

## THE HARVERSON COMPLETE F.M./V.H.F RECEIVER KIT £6.19.6

AT LAST—A COMPLETE F.M. RECEIVER IN KIT FORM!

Specially designed with the home constructor in mind, this kit enables the construction of a completely self-contained V.H.F. receiver, at fraction of the normal cost of comparable equipment. This is basically a quality self-powered F.M. tuner plus 2 separate audio amplifier stages, and output transformer and speaker.

- ★ F.M. Tuning Head by famous maker.
- ★ Guaranteed Non-drift.
- ★ Permeability Tuning.
- ★ Frequency coverage 88-130 Mc/s.
- ★ OA81 Balanced Diode Output.
- ★ Two I.F. Stage and Discriminator.
- ★ Self powered using a good quality mains transformer and valve rectifier.
- ★ Valves used ECC85, two EF80's, ECL82 and EZ80 (rectifier).
- ★ Fully drilled chassis.
- ★ Good quality speaker.
- ★ Well designed output transformer.
- ★ Attractive maroon and gold glass dial.
- ★ Two output stages (using ECL82).
- ★ Everything supplied, down to the last nut and bolt.
- ★ Compact size.
- ★ All parts sold separately.


**OUR PRICE £6.19.6** Plus 1/6 P. & P.



# 83 HIGH STREET, MERTON, S.W.19

CHerrywood 3985/6

## 14 WATT HI-FI AMPLIFIER KIT

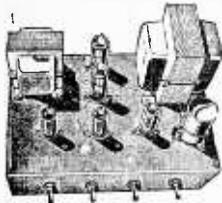


A kit designed to meet the exacting requirements of the audio enthusiast, yet remain within the price range of the average constructor. A stylishly finished monaural amplifier with an output of 14 Watts from 2 EL84's in push pull. Super reproduction of both music and speech

(Frequency response  $\pm 3\text{dB}$  c/s-60 Kc/s with negligible hum.) Separate inputs for mike and gram allow records and announcements to follow each other and make this amplifier ideal for small halls, youth clubs, etc. Fully shrouded Ultra Linear output transformer (to match 3-15 $\Omega$  speaker), and fully shrouded mains transformer (these alone are worth over £3.10.0). 2 independent volume controls, and separate Bass and Treble controls are provided, giving good life and cut. Valve line up 2 EL84's, ECC83, EF86 and EZ80 rectifier. All parts down to the last nut and bolt, including valves, knobs, heavy gauge metal chassis finished in glossy hammer green enamel, mains and output transformers finished to match.  
P. & P. 6/6 (simple instruction booklet 1/6, free with kit).

ONLY **£6.19.6**
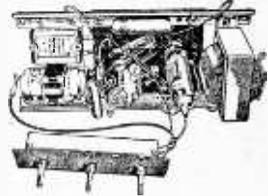
## QUALITY RECORD PLAYER AMPLIFIER KIT


A top quality record player amplifier in kit form. This amplifier (which is used in a 29-gn. record player) has a printed circuit and has an internal fully smoothed power supply (input AC/DC Mains) using a mains dropper and contact cooled rectifier. A flying panel is supplied accommodating BASS, TREBLE AND VOLUME — ON/OFF controls. 2 valves (UL84 and UF89) and linear output transformer give crisp reproduction from all records at 4 watts. Our price for the complete kit of parts (including valves) ONLY plus P. & P. 6/6. Simple instructions 1/6. (Free with kit).



**59/6**
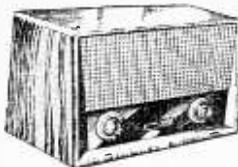
## SUPER TABLE RADIO CABINET

A very fortunate purchase allows us to offer this quality table radio cabinet for only 18/6 (this cabinet cost the manufacturers 35/- each to make). The positions of the controls make it ideal for housing our 6 TRANSISTOR SUPERHET KIT described opposite. Beautifully finished in walnut and tygan.




OUR PRICE ONLY **18/6** Plus 1/6 P. & P. ins.


## SUPER STEREO KIT MK. II

A kit of ready-built units only requiring interconnection. Comprising two midget 3W amplifiers, push button switch, transformer, control unit (bass, treble and vol.), power pack, two speakers, indicator light valves (ECL82, EZ80 range), and comprehensive instructions.

**£3.19.6** Plus 6/6 P. & P.

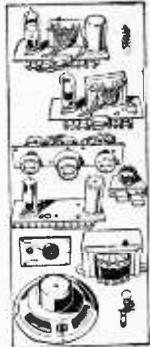

## E.M.I. 4-speed Player and P.U.

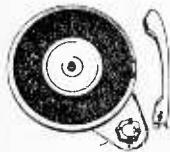

Heavy 8 $\frac{1}{2}$ in. metal turntable. Low flutter performance 200/250V shaded motor with tap at 80V for amplifier valve filament if required. Turnover LP/78 head.

PRICE 89/6 Plus 4/6 P. & P.

## VALVES

WE HAVE 20,000 IN STOCK—ALL AT BARGAIN PRICES. See our list in December "Practical Wireless", write, phone or call for your requirements. Don't miss our bargain OBSOLETE VALVE LIST—turn back to page 878

## SPECIAL OFFER... 6 TRANSISTOR RADIO IN KIT FORM

Special offer. Limited quantity only of new ex-manufacturers' parts to make a 6 transistor 2 wave band superhet chassis. Ideal for portable or table radio. All parts including transistors, ferrite aerial, printed circuit, etc., but EXCLUDING speaker and cabinet. **£4.19.6** P. & P. Few Only. 2/6 Simple instructions 1/6 (Free with kit).

**SPECIAL OFFER 54-in LOUDSPEAKER SILKS**  
Heavy woven in ivory and gold. Original price 35/- per yard length. OUR SPECIAL PRICE, 13/6 per yard length. P. & P. 1/6.

## TAPE DECKS

B.S.R. Monardeck (single speed) 3 $\frac{1}{2}$ in. per sec., simple control, uses 5 $\frac{1}{2}$ in. spools. **£7.5.0**, plus 5/6 carr. and ins. (tapes extra).  
COLLARO STUDIO DECK £10, plus 5/6 carriage and ins. (tapes extra).

**CRYSTAL MIKES**  
T.S.L. Stick Mike.....22/6  
ACOS (latest model).....18/6

**PLESSEY SPEAKER**  
8 x 5 inch 8 $\Omega$  Speaker.  
Large Pot .....12/6, P.P. 1/6

## HI-FI STEREO MONAURAL AMPLIFIER

A 5 valve HI/FI amplifier with switched stereo/monaural operation. Output 3 watts per channel, provision for bass and treble speakers on each. Volume and tone controls fitted both channels. All housed in stylish blue/grey metal case, with gold finished knobs and trimmings. **£9.19.6** Plus 4/6 P. & P. 1/6.

## PUSH-BUTTON TRANSISTOR SWITCH

A 3 push-button switch, specially designed for transistor radios. Button functions provided are on-off, long and medium wave. The back of switch is also equipped with a rack for mounting a Ferrite Aerial. Easily worth 15/-.  
OUR PRICE ONLY **5/6** Plus 1/6 P. & P. 1/6.

**Brand new, individually checked and guaranteed VALVES**

AC5PENNDD	EAC91	4/6	EM34	9/-
AL60	EB34	1/6	EN31	22/6
AP4	EB91	3/9	EP71	6/6
AR8	EB21	8/1	EP72	5/-
ARDDS	5/-	EB4C1	7/9	ESU208
AR3	2/-	EB90	5/1	EY51
AR3	3/-	EB91	3/9	EY86
AR4	3/6	EC52	8/-	EY91
AR12	2/9	EC70	10/-	EZ40
AR21	3/6	EC90	10/-	EZ41
AR24	4/6	ECC81	5/6	EZ80
AR34	5/6	ECC82	6/6	EZ81
ARTH2	7/-	ECC83	7/-	GL450
ATP4	2/9	ECC84	7/-	GL464A
AUI	5/-	ECC85	7/9	GZ32
AU4	5/-	ECC91	4/-	HL23
AW3	4/-	ECF82	8/6	HL23DD
AZ31	8/-	ECH42	7/6	HVR2
BL63	6/-	ECH81	7/9	KF35
BS44	5/6	ECL80	8/-	KRN2A
BT45	40/-	ECL82	9/-	KT31
BT83	22/6	EF22	7/3	KT32
BT98	25/-	EF36	3/6	KT33C
CV54	5/-	EF37A	8/-	KT44
CV264	35/-	EF39	4/3	KTW62
D31	7/6	EF50	2/6	KTW63
D41	3/3	EF54	3/3	MH4
D77	4/3	EF55	6/-	MH41
DA30	12/6	EF70	4/-	ML4
DAF86	8/-	EF73	6/-	ML6
DAF91	6/-	EF80	5/6	MS/PEN
DET5	15/-	EF85	6/10	NT37
DF72	7/6	EF86	9/-	(4033A)
DF91	3/3	EF89	7/9	NU12
DK96	7/3	EF91	3/6	OB3
DF96	8/-	EF92	4/6	OC3
DL92	6/-	EF95	7/6	OD3
DL94	6/-	EL32	3/9	OZ4
DL96	8/-	EL33	8/-	PCC84
DX25	9/-	EL35	8/3	PCC85
E1232	5/6	EL41	8/3	PCF80
E1323	25/-	EL42	9/-	PCF82
E1436	3/6	EL84	7/6	PCL82
E1524	6/6	EL85	10/-	PCL84
EAS0	1/6	EL91	7/6	PEN25
EABC80	7/3	EM80	8/-	PEN46

PEN65	6/6	UU9	5/6	6AC7	3/6	6SN7GT	4/6	58	6/-	7193	1/9
PEN220A	3/-	UY41	6/-	6AG5	3/6	6SQ7	6/-	59	6/-	6475	5/1
PENDD	1360	UY85	6/6	6AG7	6/6	6SS7	6/-	75	8/-	8013A	25/-
		VP23	3/6	6AJ7	4/3	6V6G	5/6	76	5/-	8020	6/-
		VP41	5/6	6AK5	5/-	6V6GT	6/-	77	6/-	9001	4/6
		VR78	4/-	6AK7	8/-	6X4	5/-	78	7/-	9002	5/6
		VR99	8/-	6AM6	6/3	6X5GT	6/6	80	6/3	9003	6/-
		VR105/307/6	6/6	6AT6	5/-	6Y6G	8/-	82	8/-	9004	4/1
		VR150/307/3	7/6	6AQ5	7/-	6Z4	8/-	8V3	12/-	9006	4/-
		PV7	7/6	6B8A	6/-	7B7	7/6	84	3/-		
		PX4	19/-	6B8	5/6	7C6	7/-	85A3	15/-		
		PX25	10/-	6BB	2/6	7C7	6/6	89	3/-		
		PY83	7/3	6C4	3/6	7H7	7/3	210LF	3/-		
		PY80	6/9	6C5	6/-	7Q7	7/3	210VPT	3/-		
		PY81	7/-	6C6	5/6	7V7	5/-	7 pin	2/6		
		PY82	8/-	6C8G	4/3	7Y4	6/-	250TH	£9		
		QP21	6/-	6D6	4/6	7Z4	2/6	274B	3/-		
		QP25	5/3	6F6	7/-	8D2	2/6	350B	8/-		
		QS75/20	6/9	6F6G	4/6	9D2	3/-	393A	15/-		
		QS95/10	6/9	6F8G	6/6	12A6	5/-	705A	17/6		
		QS108/45/6/9	1/6	6F12	4/6	12AH7	7/-	715B	9/6		
		QV04/7	12/6	6G17	7/6	12AU6	5/6	717A	8/6		
		QV05-25	5/-	1G6GT	12/-	12A7	6/6	801	22/6		
		R3	8/-	1LD5	3/6	12AU7	6/-	804	55/-		
		R3/10	4/-	1R5	5/9	12AX7	7/3	805	30/-		
		R10	12/6	1S5	5/9	12C8	3/-	807	30/-		
		REL21	25/-	1T4	4/-	12E1	22/6	807AMER	6/-		
		RK34	2/6	1W4	6/-	12H6	2/-	807BR	5/-		
		RX235	10/-	2A3	8/-	12J5GT	3/6	808	8/-		
		SP2	4/-	2A5	8/-	12K7GT	4/6	810	80/-		
		SP13C	4/6	2A6	7/6	12K8M	9/1	813	67/6		
		SP41	2/6	2034	2/6	12S47	7/6	815	40/-		
		SP61	2/-	2D21	6/-	12SC7	4/6	816	30/-		
		5TV280/80		2D4A	4/-	12SH7	6/6	826	10/-		
				2X2	4/-	12S7	3/-	829A	30/-		
		SU2150A	4/9	3A4	5/-	12SJ7	6/-	832	15/-		
		TH41	7/-	3B7	5/-	12SK7	4/6	832A	35/-		
		TP25	15/-	3B24	8/-	12SL7	7/3	843	7/6		
		TT11	3/-	3E89	6/-	12SN7	8/-	866A	12/6		
		TT20	16/-	(889B)	60/-	12Q7GT	4/6	872A	35/-		
		U17	5/-	3Q5GT	7/6	12SR7	6/-	930	8/-		
		U18	5/-	3S4	5/-	15D2	6/-	954	2/-		
		U27	8/-	3V4	6/-	15R	5/-	956	2/-		
		U52	5/-	5T4	9/-	65C7G	5/6	20A2	7/6		
		UHC42	7/6	5U4G	5/-	65C7GT	5/-	21B6	9/-		
		UL11	5/-	5V4G	8/-	65G7	5/-	30	5/-		
		UL12	5/-	5Y3GT	6/-	65H7	4/6	35L6GT	8/-		
		UL41	7/-	5Z3	8/6	65H7	5/9	35T	30/-		
		UL42	7/6	5Z4	8/6	65J7GT	5/9	35Z4GT	7/-		
		UL84	7/6	5E80	6/-	65K7	5/3	37	4/-		
		UL85	7/-	6AB7	4/-	65L7GT	6/6	38	4/-		

65N7GT	4/6	58	6/-	7193	1/9
6SQ7	6/-	59	6/-	6475	5/1
6SS7	6/-	75	8/-	8013A	25/-
6V6G	5/6	76	5/-	8020	6/-
6V6GT	6/-	77	6/-	9001	4/6
6X4	5/-	78	7/-	9002	5/6
6X5GT	6/6	80	6/3	9003	6/-
6Y6G	8/-	82	8/-	9004	4/1
6Z4	8/-	8V3	12/-	9006	4/-
7B7	7/6	84	3/-		
7C6	7/-	85A3	15/-		
7C7	6/6	89	3/-		
7H7	7/3	210LF	3/-		
7Q7	7/3	210VPT	3/-		
7V7	5/-	7 pin	2/6		
7Y4	6/-	250TH	£9		
7Z4	2/6	274B	3/-		
8D2	2/6	350B	8/-		
9D2	3/-	393A	15/-		
12A6	5/-	705A	17/6		
12AH7	7/-	715B	9/6		
12AU6	5/6	717A	8/6		
12AU7	6/-	801	22/6		
12AU7	6/-	804	55/-		
12AX7	7/3	805	30/-		
12C8	3/-	807	30/-		
12E1	22/6	807AMER	6/-		
12H6	2/-	807BR	5/-		
12J5GT	3/6	808	8/-		
12K7GT	4/6	810	80/-		
12K8M	9/1	813	67/6		
12S47	7/6	815	40/-		
12SC7	4/6	816	30/-		
12SH7	6/6	826	10/-		
12S7	3/-	829A	30/-		
12SJ7	6/-	832	15/-		
12SK7	4/6	832A	35/-		
12SL7	7/3	843	7/6		
12SN7	8/-	866A	12/6		
12Q7GT	4/6	872A	35/-		
12SR7	6/-	930	8/-		
15D2	6/-	954	2/-		
15R	5/-	956	2/-		
20A2	7/6	958A	5/-		
21B6	9/-	1616	3/-		
30	5/-	1619	5/-		
35L6GT	8/-	1625	6/-		
35T	30/-	1629	4/6		
35Z4GT	7/-	4120	4/-		
37	4/-	6064	10/-		
38	4/-				

AND MANY OTHERS IN STOCK, INCLUDING CATHODE RAY TUBES AND SPECIAL VALVES. below 10/-, 1/- P. & P. 2/6 over 10/-. Orders over £3, P. & P. free. C.O.D. 2/6 extra. Overseas Postage extra at cost.

**FREQUENCY METER BC221 TECHNICAL MANUAL 22/6.**  
**FIELD TELEPHONE TYPE "L"**  
 Excellent guaranteed condition, £5.50 per pair, carriage paid.  
**B.P.5 TRANSRECEIVERS.** Specially built for Parachutists during the war. Receiver superhet Transmitter crystal controlled. C.W., and phone. 2-8 Mc/s. 829 valve as output. 60 w. on C.W. 15 w. on microphone together with mains power pack 120/220 v. Two rotary converters to work from 12 v. battery, microphone, key and dipole aerial. Price £15. Carriage 30/-.  
**RECEIVER TYPE BC342.** 110 v. A.C. 1.5-18 Mc/s. £22.10.0, carriage 30/-.  
**RECEIVER TYPE BC312.** As above but 12 volt battery. £22.10.0, carriage 30/-.  
**R109 RECEIVER.** Covering 2-8 Mc/s 6 v. D.C. with set of spare valves and carrier. Brand new in original packing case, £6.18.0, including delivery in U.K.  
**VIBRATOR UNIT.** 12 v./160 v. 35 mA. Exceedingly well filtered and smoothed. Excellent for car radios. Including one 6X5G valve and vibrator 17/6. P. & P. 7/-.  
**MARCONI SIGNAL GENERATOR.** TF144G. 85 kc/s, 25 Mc/s. Made up to new standard. £70 delivered free.  
**SPECIALLY BUILT POWER PACK** for TC5 Receiver. 230 v. A.C. mains, including 6X5GT valve, £3.10.0. Carr. 5/-.  
**TELEPHONE HANDESET,** standard G.P.O. type. New 12/-, P. & P. 1/6.  
**VACUUM CONDENSER.** 32,000 v. 50pF. 12/6 P. & P. 3/6.  
**AR 88's.** Completely rebuilt with new PVC wiring. Type "D" £75; Type "L" £70.

**BRAND NEW ORIGINAL SPARE PARTS FOR AR88 RECEIVERS**  
**I.F. Transformers.** 1st, 2nd, 3rd, 4th (for type D), 12/6 each or complete set of 6, 60/-.  
**I.F. Transfs.** Crystal Load, 12/6 each.  
**Plates** escutcheons (for D and LF), 15/- each.  
**Dials** (for type D), 10/- each.  
**Logging Dial** (for D and LF), 10/- each.  
**Filter Chokes** (for D and LF), 22/6 each.  
**Output Transformers** (for LF), 30/- each.  
**Antenna Trimmers** (LF and D), 2/6 each.  
**Filter Condenser** 3 x 4µF, £2.10.0  
**Condensers:**  
 3 x .25µF (D and LF), 2/6 each.  
 3 x .01µF (D and LF), 2/6 each.  
**RF Antenna Inductors** (D and LF), 7/6 each.  
**Mains Transformers** (LF), £3 each.  
**Small Trimming Tool,** 7/-.  
**Small Mica Condensers,** various values, 1/6 each.  
**Instruction Manual for AR88D,** £1.

**19 SET OWNERS.** To increase output of your set to 10 times use **RF Amplifier No. 2** with built-in rotary converter for 12 v. input. Four 807 valves output. Simple connection with transmitter. Fully tested condition, £9.15.0, including necessary connectors and instructions. Carriage and packing 15/-.

**P.C. RADIO LTD.**  
**170 GOLDHAWK RD., W.12**  
 Shepherds Bush 4946

**POWER SUPPLY UNIT.** Input 200/250 v. A.C., 50 cycles. Output: 1, H.T.280/350 v. 300mA smoothed; 2, M.T. 150/200 v. 40mA (positive earthed); 3, L.T. 10/25 v. 4 amp. D.C. smoothed (negative earthed). 2 relay switching. H.T. & M.T. safety switch fuses on A.C. and all D.C. Two 5Z3 for H.T., one 6X5 for M.T., Selenium rectifier for L.T. Ideal for Ham transmitters. Weight 45 lb. Dimensions 14 x 8½ x 18in. Price £12.10.0 including valves. P. & P. 25/-.  
**R209 RECEPTION SET.** A 10-valve High-Grade Super Heterodyne Receiver with facilities for receiving R/T (A.M. or F.M.) and C.W. Frequency 1-20 Mc/s. Hermetically sealed. Built on miniature valves and incorporating its own vibrator power supply unit driven by a 6 v. battery (2-point connector included). The set provides for reception from rod, open-wire or dipole aerial with built-in loud-speaker or phone output. Overall measurements: Length 12in., width 8in., depth 9in. Weight 23 lb. In as new,

# STERN'S MULLARD DESIGNS

Designed by MULLARD—presented by STERN'S strictly to specification

## COMPLETE KIT OF PARTS

### MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-valve pre-amplifier with which undistorted power output of up to 10 watts is obtained. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES, including PARMEKO MAINS TRANSFORMER and choice of the latest Ultra-Linear PARMEKO or the PARTRIDGE Output Transformer. COMPLETE KIT OF PARTS (PARMEKO Output Trans.) **£10.00**

Alternatively we supply ASSEMBLED and TESTED. **£11.10.0** INCORPORATING PARTRIDGE OUTPUT TRANSFORMER. **£1.6.0** EXTRA.

### MULLARD'S PREAMPLIFIER TONE CONTROL UNIT


Employing two EF85 valves, and designed to operate with the MULLARD MAIN AMPLIFIERS, but also perfectly suitable for other makes. PRICE COMPLETE **£6.6.0** ASSEMBLED AND TESTED **£8.0.0** KITS OF PARTS

Supplied strictly to MULLARD'S SPECIFICATION and incorporating:  
 ● Equalisation for the latest R.L.A.A. characteristics.  
 ● Input for Crystal Pick-ups, and variable reluctance magnetic types.  
 ● Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.  
 ● Sensitive Microphone Channel. ● Wide range BASS and TREBLE Controls.
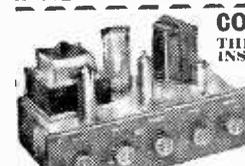
### COMPLETE MULLARD "5-10" AMPLIFIER

The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 watts high quality reproduction. Only Specified Components and new MULLARD VALVES are supplied including PARMEKO MAINS TRANSFORMERS and choice of the latest PARMEKO or PARTRIDGE ULTRA-Linear Output Transformers.

KIT OF PARTS **£11.10.0** OR ASSEMBLED AND TESTED **£13.10.0**  
 H.P. Dep. £2.6.0, 12 months at 17/- Dep. £2.14.0 12 months at 19/10  
 ABOVE incorporating PARTRIDGE OUTPUT TRANS. **£1.6.0** extra.



**COMPLETE MULLARD "3-3"**  
 THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION PROVIDING EXCELLENT REPRODUCTION OF UP TO 3 WATTS OUTPUT  
 COMPLETE KIT **£7.10.0** OR ASSEMBLED AND TESTED **£8.19.6**  
 (plus 8/6 carriage and insurance) H.P. Terms: Deposit **£2.0.0** and 3 months at **£1.0.0**. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMEKO OUTPUT TRANSFORMER.






**STERN'S INTER-COMM BABY ALARM**  
 A small versatile Unit employing the new MULLARD ECL86 valve and designed to provide two (or three) way conversation up to extreme distances. Operates from A.C. mains 200 to 250 Volts.  
 PRICES . . . MASTER UNIT and ONE EXTENSION **£8.0.0**  
 KIT OF PARTS **£6.17.6** ASSEMBLED AND TESTED **£8.0.0**  
 Consists of a MASTER UNIT, size only 8 1/2 x 5 1/2 x 6 in. and ONE EXTENSION (a second extension may be added to any time). The Master Unit incorporates switching and power supply and with the chassis completely isolated from the mains is operated in absolute safety. Cases covered in quality leatherette.

**ARMSTRONG RADIOGRAM CHASSIS**  
 FULL RANGE IN STOCK, please enclose S.A.E. for descriptive leaflets

**STEREO 12 (MK. 2)**  
 (Illustrated) **£44.15.0**  
 Deposit, **£9.0.0**, 12 months at **£3.5.7**  
 The most complete chassis ever produced, combines AM and FM Tuners, a Stereo Control Unit and two High Fidelity Amplifiers in one compact unit, provide a total of 18 watts for both mono and stereo. Other features include: inputs for tape and recording, play back, pick-ups and stereo radio (should this come about); separate wide range bass and treble controls and balance control.

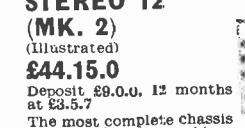**STEREO 55** **£33.15.0**  
 Deposit **£6.15.0**, 12 months at **£2.9.6**  
 A fun version of the Stereo 12 Mk. 2 providing ten watts output, five watts from each amplifier and covering the VHF and Medium wavebands.



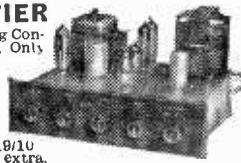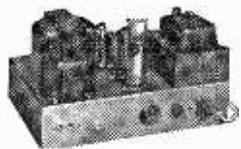

## COMBINED ORDER PRICE REDUCTIONS

(a) THE KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-valve PRE-AMP CONTROL UNIT H.P. Dep. **£3.7.0** and 12 months at **£15.15.0**  
 (b) The "5-10" and the 2-stage PRE-AMP both ASSEMBLED and TESTED H.P. Dep. **£3.16.0** and 12 months at **£18.18.0**  
 with PARTRIDGE OUTPUT TRANSFORMER **£1.6.0** extra

## RECORD PLAYERS


The Latest Models are in stock, many at reduced prices.  
 Send S.A.E. For Illustrated Leaflet.  
 THE NEW GARRARD "AUTO" with Crystal Pick-up .... **£8.10.0**  
 COLLARO "JUNIOR" 4 SPEED SINGLE RECORD PLAYER with separate Crystal Pick-up Carriage and Insurance 5/- Above Pick-up separately for **£1.6.6**  
 THE NEW COLLARO 60 4-speed Autochanger unit with Studio "O" Pick-up..... **£7.19.6**  
 The F.M.I. 4-speed Single Record Player with crystal Pick-up..... **£6.9.6**  
 B.S.R. MODEL UA14. A 4-speed mixer Autochanger with Crystal Pick-up ..... **£7.10.0**  
 Available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 Records ..... **£8.13.10**  
 GARRARD MODEL TA/MKH 4-speed Player fitted high output Crystal Pick-up.. **£8.10.0**  
 GARRARD MODEL RC210. Autochanger 4-speeds. High output. Crystal Pick-up.. **£10.10.0**  
 Carriage and Insurance on each above 5/- extra.

## SPECIAL CASH OFFER



This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER.  
 ALL for ONLY **£8.7.6** (Plus 7/6 Carr & Ins.).  
 The Amplifier consists of a 2-stage design incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS.  
 The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexine.  
 WE ALSO SUPPLY SEPARATELY—  
 (a) THE 2-stage (plus Rectifier) AMPLIFIER **£4.2.6**  
 (b) THE PORTABLE CARRYING CASE **£3.17.6**  
 (c) 6in. P.M. SPEAKER 18/8. Carriage and Insurance 4/- extra.

## MULLARD FOUR CHANNEL MIXER UNIT

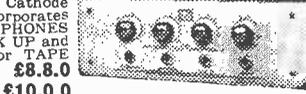

Self powered with Cathode follower output. Incorporates Two inputs for MICROPHONES One for CRYSTAL PICK UP and a fourth for RADIO or TAPE  
 Complete Kit of Parts **£8.8.0**  
 Assembled and Tested **£10.0.0**  
 TERMS: Deposit **£2** and 12 months at 15/-  
 MODEL I.L. one microphone input matched for moving coil or Ribbon Mike, **£1.17.0** extra

**JUBILEE MK. 2** **£31.15.0**  
 Deposit **£6.7.0** 12 months at **£2.6.7**  
 A Hi-Fi mono chassis giving eight watts push-pull output and covering VHF, medium and long bands. Tape recording and play back inputs.

**AF208** **£23.15.0** Deposit **£4.15.0** 12 months at **£1.14.10**  
 An AM/FM chassis providing 5 watts output and covering the full VHF and medium wavebands. Tape recording and playback inputs.

**STERN RADIO LTD.**  
 Dept. F.V. 109 FLEET ST., LONDON, E.C.4  
 Telephone: FLEET STREET 5812/3/4



# Stern's "fidelity" TAPE RECORDERS

For truly "Hi-Fi" Recordings

**MODEL GR3/S** Incorporates the COLLARO "STUDIO" TWIN TRACK 3-speed Deck, operating at 1 1/2-in., 3in. and 7in. speeds. . . . . **£39.10.0**  
H.P. Terms: Deposit £7.18.0 and 12 months at £2.17.11.

**MODEL TR3/Mk.VI** Incorporates the New TRUVOX Mk. VI TWIN TRACK 2-speed Tape Deck operating at 3in. and 7in. speeds. . . . . **£44.0.0**  
H.P. Terms: Deposit £8.18.0 & 12 months at £3.4.7.



**The MODEL HFG/2R PORTABLE TAPE RECORDER**  
(Original Price £33.0.0)  
**FOR ONLY 22 gns.**

H.P. Dep. £4.14.0. 12 months at £1.13.9. (Carr. and Ins. 10/- extra). Incorporates THE LATEST GARRARD "MAGAZINE" TAPE DECK and a HIGH QUALITY AMPLIFIER which is entirely based on the very successful MULLARD TYPE "A" DESIGN and specifically developed to operate the GARRARD TAPE SUPPLY OF DOUBLE PLAY TAPE. Comprises a Twin Track Recorder operating at 3in/sec. speed and providing up to 1 hour 10 mins. playing time. Truly "Portable", weighs only 22 lbs. Outstanding features are excellent performance and simplicity of operation.

**ADD "HI-FI" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION WITH MULLARD TYPE "C" TAPE PRE-AMPLIFIER—ERASE UNIT**

The "Hi-Fi" link to add full tape recording facilities to High Fidelity home installations. Incorporates FEROCUBE POT CORE PUSH PULL OSCILLATOR and 3-speed treble equalisation by FEROCUBE POT CORE INDUCTOR FOR WEARITE-COLLARO-TRUVOX OR BRENELL TAPE DECKS. Includes separate power Supply Unit.




**KIT OF PARTS** OR **ASSEMBLED**  
**£14.0.0** Deposit £2.16.0. 12 mths. at £1.0.8  
(Excluding power unit £1.15.0 and £1.4.10 respectively.)  
**£17.0.0** Deposit £3.8.0. 12 months at £1.4.11

- "SPECIAL COMBINED ORDER" PRICES**
- (a) The COLLARO "Studio" Deck with the Model "C" Preamplifier and POWER SUPPLY UNIT ASSEMBLED AND TESTED . . . . . **£29.10.0**  
Deposit £5.18.0. 12 monthly payments of £2.3.3
  - (b) As above but the TYPE "C" UNIT and POWER UNIT supplied as COMPLETE KIT OF PARTS . . . . . **£26.10.0**  
Deposit £5.8.0. 12 monthly payments of £1.18.10
  - (c) The TRUVOX Mk. VI Deck (Incorporating Pause Control and Rev. Counter) with the Model "C" PREAMPLIFIER and POWER UNIT ASSEMBLED AND TESTED . . . . . **£35.0.0**  
Deposit £7.0.0 and 12 months at £2.11.4
  - (d) As above but the Model "C" PREAMPLIFIER and POWER UNIT supplied as a COMPLETE KIT OF PARTS . . . . . **£31.10.0**  
Deposit £6.0.0. 12 monthly payments of £2.6.2
  - (e) The BRENELL Mk. V Deck with the Model "C" PREAMPLIFIER and POWER UNIT ASSEMBLED AND TESTED . . . . . **£46.0.0**  
Deposit £9.4.0 and 12 months at £3.7.6
  - (f) As above but the Model "C" PREAMPLIFIER and POWER UNIT supplied as a COMPLETE KIT OF PARTS . . . . . **£43.0.0**  
Deposit £8.12.0. 12 monthly payments of £3.3.1
  - (g) The WEARITE MODEL "4" DECK with ASSEMBLED AND TESTED Model "C" PREAMPLIFIER AND POWER UNIT incorporating WEARITE HEAD LIFT TRANSFORMER, ETC. . . . . **£56.0.0**  
Deposit £11.4.0 and 12 months at £4.2.1  
(Carriage and Insurance on above is 10/- extra.)

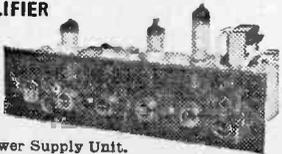**HF/TR3 MK.II TAPE AMPLIFIER**

(Mullard Type "A" design)  
A very high quality Amplifier incorporating 3-speed treble equalisation by the latest FEROCUBE POT CORE INDUCTOR. FOR COLLARO-TRUVOX - BRENELL WEARITE Tape Decks, has GLISEN Output Transformer. Includes separate Power Supply Unit.



There are no better value-for-money Tape Recorders on the market—if you can't call and hear them send S.A.E. for fully descriptive leaflet.

EACH MODEL INCORPORATES THE MODEL HF/TR3 MK.II TAPE AMPLIFIER (Described below)

Each price quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200ft. Spool of Tape.



**THE "ADD-A-DECK"**

Incorporating GARRARD "MAGAZINE" TAPE and the MATCHED MODEL HF/GSP PIRE-AMPLIFIER Supplied on ONE CHASSIS (as illustrated) READY FOR USE **18 Gns.**  
(Carr. & Ins. 10/- extra.)

Price includes Garrard Magazine and a 4in. Spool Double Play Tape H.P. Deposit £3.16.0, and 12 months at £1.7.8. Provides complete tape recording facilities and designed to operate through the pick-up sockets of the standard type of RADIO RECEIVER, or an AMPLIFIER, from which really first class reproduction is obtained. It consists of a Twin Track Deck connected to the Preamplifier and operates at 3in/sec. speed providing up to 1 hr. 10 mins. playing time.

## BUILD A HIGH FIDELITY TAPE RECORDER



◀ LIKE THIS for £35.0.0

Deposit £7.0.0  
12 months at £2.11.4

**FOR THIS WE SUPPLY**

- ★ Complete Kit of Parts to Build the HF/TR3 Tape Amplifier
- ★ The New Collaro "Studio" Tape Deck.
- ★ Portable Carrying Case (as illustrated)
- ★ Rolm-Celestion 10 x 6in. p.m. Loudspeaker.

★ ACOS Crystal Microphone and 1,200ft. Spool E.M.I. Tape. Alternatively for those who prefer another make of Tape Deck—we will supply precisely as above—but in place of the Collaro "Studio" Deck. We will include: **£40.10.0**

- For Constructors with their own cabinet—WE OFFER—
- (a) COMPLETE KIT to build the HF/TR3 Amplifier together with the COLLARO "STUDIO" DECK . . . . . **£26.0.0**  
Deposit £5.18.0. 12 monthly payments of £1.18.2
- (b) As above but with the HF/TR3 supplied ASSEMBLED AND TESTED . . . . . **£29.10.0**
- (c) COMPLETE KIT to build the HF/TR3 together with the TRUVOX Mk. VI TAPE DECK . . . . . **£31.10.0**  
Deposit £6.8.0. 12 monthly payments of £2.6.2
- (d) As above but with HF/TR3 supplied ASSEMBLED AND TESTED . . . . . **£35.0.0**  
Deposit £7.0.0. 12 monthly payments of £2.11.4
- (e) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENELL Mk. V TAPE DECK . . . . . **£42.0.0**  
Deposit £8.8.0. 12 monthly payments of £3.1.7
- (f) As above but with HF/TR3 supplied ASSEMBLED AND TESTED . . . . . **£45.10.0**  
Deposit £9.2.0. 12 monthly payments of £3.8.9
- (g) THE ASSEMBLED AND TESTED HF/TR3 AMPLIFIER with the WEARITE MODEL 4A DECK. Incorporates Wearite Head Lift Transformer etc. . . . . **£56.0.0**  
Deposit £11.4.0. 12 monthly payments of £4.2.1.  
(Carriage and Insurance on each above is 10/- extra.)

KIT OF PARTS **£13.13.0** H.P. Deposit £3.8.0 and 12 months at £1.4.11. OR ASSEMBLED **£17**

# STERN RADIO LTD.

# Stereophonic Sound by Stern's


## THE "STP-1" STEREO TAPE PREAMPLIFIER DESIGNED TO OPERATE WITH

● **TRUVOX Mk. VI TAPE DECK** incorporating the latest 4-TRACK MINI-FLUX TAPE HEADS.

● **BRENELL Mk. V TAPE DECK** incorporating similar 4-TRACK MINI-FLUX TAPE HEADS.

● **COLLARO "STUDIO" TAPE DECK** incorporating the latest 4-TRACK RECUTTER TAPE HEADS.

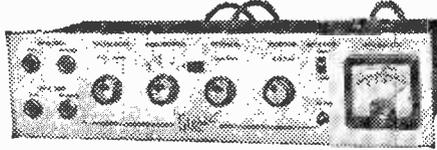- PUSH PULL OSCILLATOR CIRCUIT
- 4-SPEED EQUALISATION
- FERROXUBE OSCILLATOR TRANSFORMER
- SENSITIVE METER FOR SIGNAL LEVEL
- SEPARATE GAIN CONTROLS IN EACH CHANNEL
- MULLARD VALVES INCORPORATED



OVERALL SIZE CASE 18 1/2 x 3 1/2. FRONT PANEL (Choice of Black or White) 14 x 3 1/2.

PRICE

**£ 26.0.0**

including separate Power Supply Unit.  
Deposit £5.4.0, 12 months £11.8.2.

### COMBINED PRICE SCHEDULE

#### THE "STP-1" PREAMPLIFIER is offered

- WITH TAPE DECKS AS FOLLOWS:
- TRUVOX Mk. VI 4-TRACK MODEL..... **£47.0.0**  
Deposit £9.8.0, 12 months at £8.3.11.
  - BRENELL Mk. V 4-TRACK MODEL..... **£65.0.0**  
Deposit £13.0.0, 12 months at £4.15.4.
  - COLLARO "STUDIO" 4-TRACK MODEL..... **£43.0.0**  
Deposit £8.12.0, 12 months at £3.3.1.

#### THE MULLARD "10+10" STEREO AMPLIFIER

(described below) with the "STP-1" PREAMPLIFIER and one of the TAPE DECKS provide a COMPLETE STEREOGRAPHIC INSTALLATION. **WE OFFER**

- "10+10" AMPLIFIER "STP-1" PREAMPLIFIER and the TRUVOX Mk. VI DECK..... **£67.0.0**  
Deposit £13.8.0, 12 months at £4.18.3.
- As above with BRENELL Mk. V DECK..... **£85.0.0**  
Deposit £17.0.0, 12 months at £6.4.8.
- As above with COLLARO "STUDIO" DECK..... **£63.0.0**  
Deposit £12.12.0, 12 months at £4.12.4.

Please enclose S.A.E. with all enquiries.

**STEREOGRAPHIC RECORD PLAYER UNITS MICROPHONES & TWIN LOUDSPEAKERS ARE AVAILABLE FROM STOCK**

### MULLARD'S "10 PLUS 10" STEREO POWER AMPLIFIER

A high fidelity design based on the famous Mullard "4-10". Provides up to 10 watts (per channel) Superh reproduction. Frequency response flat to within 3 db from c/s. to 60 Kc/s at 50 Mw.



Total Harmonic Distortion at 10 watts 0.1%.  
a) ASSEMBLED COMPLETE AMPLIFIER, including CONTROL UNIT (as illustrated)..... **PRICE: £21.0.0**  
Deposit £4.4.0, 12 months at £1.10.10.

b) A complete KIT OF PARTS..... **£18.10.0**  
Deposit £3.14.0, 12 months at £1.7.2.

Built to the very highest technical standards and presented strictly to MULLARD'S specification. Incorporates complete Mullard valve line-up including two of the new valves, type ECL86, in each channel. Two specially designed GILSON OUTPUT TRANSFORMERS with 2% tape are used for ultra linear operation.

The matching CONTROL UNIT is designed to be either attached to the Amplifier (as illustrated, or can be detached for separate mounting on a Cabinet panel. Provides inputs for CRYSTAL PICK-UPS, RADIO TUNING UNIT, and TAPE RELAY.

AS AUDIO SPECIALISTS WE CONFIDENTLY RECOMMEND THIS DESIGN. It is a MUST to the serious minded sound enthusiast. We can also supply the assembled MAIN AMPLIFIER only (excludes control unit) or operation with our DUAL CHANNEL PREAMPLIFIER, this provides for a more versatile or elaborate installation and would be essential if a low output Magnetic Pick-Up, such as the Decca, is to be used.

a) THE ASSEMBLED MAIN AMPLIFIER with the ASSEMBLED DUAL CHANNEL PREAMPLIFIER..... **PRICE: £30.0.0**  
Deposit £6.8.0, 12 months at £2.4.0.

b) A complete KIT OF PARTS for both Units..... **£26.0.0**  
Deposit £5.4.0, 12 months at £1.15.2

### DUAL CHANNEL PREAMPLIFIER

Incorporates two Mullard 2-valve Preamplifiers combined into a single unit enabling it to be used for both STEREOGRAPHIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Ampifiers requiring an input of 250 mV/OLTS.



COMPLETE KIT **£12.10.0** ASSEMBLED **£15.0.0**

H.P. £2.10.0 & 12 mths. at 18/4 H.P. £3.0.0 & 12 mths. at £1.2.0

### STEREO "TWIN THREE" AMPLIFIER with specially designed PORTABLE CASE

A most compact portable design consisting of TWIN CHANNEL AMPLIFIER based on the latest design by MULLARD LTD. incorporating top grade Output Transformers, and the new audio Triode-Pentode Valves Mullard E.C.L.86. Separate Bass and Treble controls. Suitable for use with Crystal Pick Ups, and capable of genuine high quality reproduction up to 3 Watts per channel. An attractive and contemporary portable Case in two tone colours. The unique feature of the design is the loudspeaker mounting. Two 8 x 5in. p.m. elliptical loudspeakers are separately baffled and mounted in the lid, which is detachable, allowing for each speaker to be individually positioned. A very versatile stereo arrangement tested and guaranteed which can be assembled in the minimum of time.



PRICE for the ASSEMBLED AMPLIFIER, Two 8 x 5in. ROLA SPEAKERS and PORTABLE CASE **£14.0.0**

Deposit £2.16.0, 12 months at £1.0.8. **£7.15.0**

ASSEMBLED AMPLIFIER supplied for..... **£1.1.0**

8 x 5in. ROLA LOUDSPEAKERS (3 ohms) each. **£5.0.0**

PORTABLE CASE.....

A CHOICE OF SINGLE RECORD PLAYERS and AUTOCHANGERS is available from Stock (Send S.A.E. for details)

**!! A BARGAIN !!** We are able to offer BRAND NEW and FULLY GUARANTEED-TRUVOX MK. VI TAPE DECKS. List Price **£18.18.0** £26.5.0 (or £26.0.0) Deposit **£3.16.0** and 12 months at **£1.7.8** (Carr. & Ins. 7/6 extra)

A twin track model operating on 31 and 7 1/2 in./sec. speeds and incorporating pause Control and Rev. Counter.

Dept. P.W. **109 FLEET ST., LONDON, E.C.4**

Telephone **FLEET STREET 5812/3/4**

Illustrated and Descriptive Brochures available. Please enclose S.A.E.



# Valves by return post

EF86	12/6	GZ32	11/6	PY83	b/o	UL84	9/-	5R4GY	9/6	6F6M	7/6	6X5GT	7/-	12SL7	8/-
EF89	8/9	HL23DD	8/6	PEN4VA		UU6	19/3	SU4G	5/-	6J5GT	5/-	6J30L2	12/6	12SN7GT	10/-
EF91	5/9	HL42DD			10/-	UY1N	12/6	SV4	11/6	6J5M	6/6	7B5	10/6		
EF91 (BVA)				PEN25	5/-	UY41	6/6	5Y3G	8/-	6J6	4/-	7B7	8/6	15D2	7/9
	7/6	KT2	5/-	PEN45	8/-	UY85	7/6	5Y3GT	7/6	617G	6/6	7C5	8/-	25A6G	8/-
EF92	6/-	KT33C	6/-	SP4	5/-	VP23	5/-	SZ4G	9/-	6K7G	3/6	7C6	8/-	25L6GT	10/-
EF183	15/-	KT61	10/-	TP22	8/-	VR105/30	8/-	6A7	10/-	6K7M	6/9	7H7	8/-	25Z4	9/6
EF184	15/-	KTW61	6/6	U0	9/6	VR150/30	7/6	6A8G	9/-	6K8G	6/6	757	9/6	25Z5	7/-
		EL33	10/-	U25	13/6	VU39 (MU)	6AK5	5/-	6K7GT	5/9	7Y4	6/6	25Z6	10/-	
		EL41	9/-	U50	12/-	(12/14)	8/9	6AL5	4/-	6K8GT	10/-	10F1	12/6	30FL1	10/6
		EL81	9/-	U63	8/-	Y63	7/6	6AM5	7/6	6L6G	8/-	10P13	22/3	30L15	23/3
		EL91	4/6	UABC80	9/-	IA7GT	13/6	6AM6	4/-	6L6M	9/6	12A6	5/-	30P4	15/-
EAF42	9/6	ECF82	10/6	UAF42	9/6	IC2	11/6	6AQ5	7/6	6L18	11/6	12AH8	12/-	30P12	12/6
EB91	4/6	ECH42	9/6	UBC41	8/6	IC5GT	12/6	6AT6	8/6	6N7GT	7/6	12AT7	7/6	30P11	12/6
EB33	6/9	ECH81	9/-	UBC81	11/4	IH5GT	9/-	6BA6	7/6	6Q7G	7/6	12AU7	8/-	35L6GT	10/-
EB41	8/9	ECL80	9/6	EY51	9/6	PL36	13/6	UCC84	9/-	IN5	10/6	6BE6	7/6	6Q7GT	9/6
EB39	8/6	ECL82	10/6	EY86	10/-	PL81	11/6	UCC85	9/6	IR5	7/6	6BH6	9/-	6SK7	6/-
EB91	8/6	ECL83	15/6	EZ40	7/6	PL82	8/6	UCH42	9/6	IS5	6/6	6BJ6	9/-	6SL7GT	8/-
EBF80	9/9	EF36	3/6	EZ41	7/6	PL83	9/6	UCH81	9/6	IT4	5/6	6BW6	9/-	6SN7GT	7/6
EBF83	13/11	EF41	9/6	EZ80	7/6	PL84	9/6	UCL82	11/6	306	5/-	6C4	4/6	6S07	9/3
EBF89	9/6	EF50	5/-	EZ81	7/6	PX25	12/6	UCL83	13/6	3Q5GT	9/6	6C6	6/6	6U4GT	12/-
EBL21	23/3	EF50SYL	7/-	FC13	5/6	PY80	7/6	UF85	9/-	354	7/6	6D6	5/-	6V6G	5/-
EBL31	23/3	EF80	7/-	FW4/500		PY81	8/6	UF89	9/-	3V4	8/-	6CH6	7/6	6V6GT	7/9
EC90	4/6	EF85	7/-		10/-	PY82	7/-	UL41	9/-	4D1	3/-	6F6G	7/-	6X4	7/6
														12SQ7	6/6
														210DDT	4/6
														210PT	3/6

### MULLARD TRANSISTORS

OC19	48/-	OC77	10/-
OC35	25/6	OC78	8/-
OC44	11/-	OC78D	8/-
OC45	10/-	OC81	8/-
OC70	6/6	OC84	11/-
OC71	6/6	OC170	13/6
OC72	8/-	OC171	14/6
OC72pr	16/-	OC171	14/6
OC73	16/-	OC201	12/6
OC75	8/-	OC202	36/6

**A SPECIAL OFFER OF SIX MULLARD TRANSISTORS**  
 1 OC44, 2 OC45, 1 OC81D, 2 OC81. Only 37/6 set.

**EDISWAN TRANSISTORS**  
 XA104 12/-, XA103 10/-, XB102 6/6 ea.

**RECORDING TAPE**  
 Special Offer of Top quality recording tape, 3 1/2 in. spool 200ft, 5/3, 5 in. spool 600ft, 13/9, 5 1/2 in. spool 850ft, 18/6, 7 in. spool 1200ft, 23/-, Extra-play tape, 3 1/2 in. spool 300ft, 7/-, 5 in. spool 900ft, 21/-, 5 1/2 in. spool 1275ft, 26/6, 7 in. spool 1800ft, 37/6. Empty spools, 3 1/2 in., 1/6, 5 in., 2/-, 7 in., 3/-.

**RECTIFIERS**  
 RM1 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 14A86 19/6, 14A97 19/6, 14A100 19/6, LW7 17/6, 18RA 1-1-16-1 6/-, FC31 (14RA 1-2-8-3) 22/6, FC101 (14RA 1-2-8-2) 16/6.

**HIGH RESISTANCE PHONES**  
 High Resistance Phones, 4,000 ohms, 13/6 pair.

**LOUDSPEAKER UNITS**  
 All brand new  
 2 1/2 in. square EMI 18/6  
 4 in. square Elac  
 Tweeter 12/6  
 5 in. round Plessey  
 with O.P.T. 16/6  
 6 1/2 in. round Celestion 17/6  
 8 in. round Richard Allen 18/6  
 12 in. round Plessey 29/6  
 6 in. x 4 in. Plessey 19/6  
 7 in. x 4 in. Plessey 19/6  
 8 in. x 5 in. Celestion 19/11  
 10 in. x 6 in. Celestion and Plessey 21/6

**STENTORIAN HF 1012**  
 10 in. die-cast unit, incorporating 12,000 gauss magnet. Handling capacity, 10 watts. Frequency response, 30 c.p.s.-14,000 c.p.s. Bass resonance, 35 c.p.s.  
 Total price, £5.2.6

**MARTIN RECORDAKIT**  
 Model C for Collaro Studio Deck. Amplifier 8311/V assembled and tested with 5 BVA valves, controls, switches, transformers, knobs and full instructions. £11.11.0  
 Smart 2 tone leatherette covered wooden case and 9 x 5 in. high quality loud-speaker, type C6659/V. £5.5.0.  
 Circuit diagram, full instructions, shopping list, etc. 3/6 ea.  
 Collaro Studio Deck, £12.12.0.  
 Illustrated leaflet available.

**AUTOMATIC RECORD CHANGERS**  
 ★ UA14  
 Four speed motor. Magdisc selector enabling 7, 10 and 12 in. records to be selected automatically. "Flu-Fi" turnover crystal cartridge. Attractively styled in cream and grey. Suitable for A.C. mains, 100/125 v. 50 cycles. Unit plate. £6.19.6  
 ★ Garrard Autoslim  
 The latest 4-speed automatic Record Changer from Garrard-Autoslim, £9.0.0.

**SINGLE PLAYERS**  
 ★ EMI 985  
 4-speed Turntable Unit complete with Pickup. An extremely reliable and inexpensive Unit suitable for Record Players and Radiograms; a heavy 86 in. dia. Metal Turntable with low flutter performance, 5-position switch, 4 speeds and off, ivory finish with red T/T mat. 89/6.  
 ★ Garrard TA/Mk II  
 4-speed single player. Diecast aluminium pickup with GC2 cartridge. Automatic stop. 9 1/2 in. dia. turntable. £8.10.4

All components for the "Practical Wireless" Blue Prints — "Mini-Amp", "Tutor", "The Citizen", available from stock. Please send stamped addressed envelope for detailed price lists.

**TEST METERS CABY A.10**  
 D.C. or A.C. Resistance ohm: 10K ohms. Will also measure decibels. Price £4.17.6. Inclusive of test prods, instruction book and batteries.

**CABY B.20**  
 D.C. or A.C. Will also measure decibels. Price £6.10.0. Inclusive of test prods, instruction book and batteries.

**THE PRACTICAL WIRELESS SCOPING TRANSISTOR SUPERHET**  
 A new version in a re-designed cabinet with carrying strap, complete kit of parts, £7.19.6. Detailed price list available on request.

**"THE CONTESSA"**  
 A 2-band 6-Transistor Superhet for long and medium waves, 2-colour case, 10 x 7 1/2 x 3 1/2 in. £10.19.6. Send for comprehensive manual and parts list, 3/6.

**TWO NEW BOOKS FROM BERNARDS**  
 No. 173. PRACTICAL TRANSISTOR AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR. Book 1. Thirty-two Diagrams and Plans. 3/6 each.  
 No. 172. INTERNATIONAL RADIO STATIONS LIST. Lists more than 14,000 facts on Radio Stations throughout the World. 2/6 each.


**CATALOGUE**  
 OUR 1962 CATALOGUE IS NOW AVAILABLE. PLEASE SEND 1/- IN STAMPS FOR YOUR COPY. TRADE CATALOGUE ALSO AVAILABLE, FOR WHICH PLEASE ATTACH YOUR BUSINESS LETTER HEADING.

**TERMS:** Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

**ALPHA**  
 RADIO SUPPLY CO.  
 103 LEEDS TERRACE  
 WINTOUN STREET  
 LEEDS 7


# CHECK with these

# BARGAINS

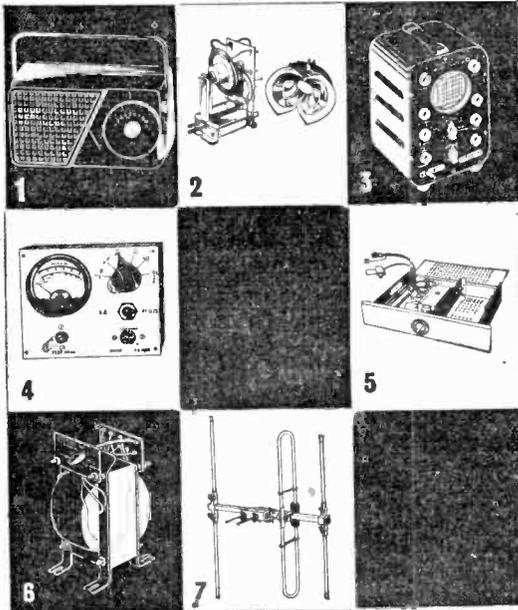

1. **3-TRANSISTOR POCKET RADIO** with MINIATURE SPEAKER, FERRITE ROD, and 2 GERMANIUM DIODES. The only 3 transistor radio available at the price. Built in 1 evened Tunable over M/L waves. Complete with easy-to-follow instructions and all components (less batteries obtainable anywhere 1/3), 27/6. P. & P. 2/6. (All parts available separately.)
2. **LINE E.H.T. TRANSFORMERS.** Built-in line width control, 14kV, scan coil, 90m. deflection on ferrite yokes. Frame O.P. transformer pl. 18kV smoothing condenser, suitable for 14in., 17in. or 21in. tubes. With circuit diagram. 29/6 plus 4/6 P. & P. As above, but for 625 lines, £2.10.0, plus 4/6 P. & P. Suitable Focus Magnet (gate tube), 10/- plus 3/- P. & P.
3. **OSCILLOSCOPE** for D.C. and A.C. APPLICATIONS. A high gain, extremely stable differential Y-amplifier (30 mV/C.M.). Provide ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurements of transient operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external -1/2 and C.R.T. Brightness Modulation. A.C. mains 200/250 v. £15.15.0. P. & P. 8/- or 30/- deposit, plus P. & P. 8/- and 12 monthly payments of 28/6. **FULL 12 MONTHS' GUARANTEE INCLUDING VALVES and TUBE.**
4. **A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wirewound pot. (for ohms zero setting), toggle switch, resistor and rectifier. 19/6. P. & P. 2/-. Wiring diagram 1/-, free with parts.
5. **CHANNEL TUNER.** Will tune to all Band I and Band III stations. Complete with P.C.C.84 and P.C.F.80 valves (in series) L.F. 16-19 or 33-38. Can be modified as an aerial converter (instructions supplied). 32/6, plus 4/- P. & P. **HEATER TRANSFORMER** to suit above, 200-250 v., 6/-, plus 2/- P. & P.
6. **MAINS TRANSFORMERS.** All with tapped primaries, 250-500 v. 70 mA, 6.3 v. 2 amp. 10/6. P. & P. 3/-, 250-0-250 v. 70mA 6.3v. 2A, 6.3v. 1A 10/6. P. & P. 3/-, 250-0-250 120mA 6.3v. 2A, 6.3v. 3A, 17/6. P. & P. 3/6.
7. **WOLSEY 3-ELEMENT FOLDED DIPOLE.** I.T.V. Aerial less mounting bracket for external use, complete with 12 yds. of coaxial cable, 15/-, P. & P. 4/-.
8. **SIGNAL GENERATORS.** Cash £4.10.6. P. & P. 5/6. Coverage 120 kc/s to 84 Mc/s. Case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ± 2 per cent.

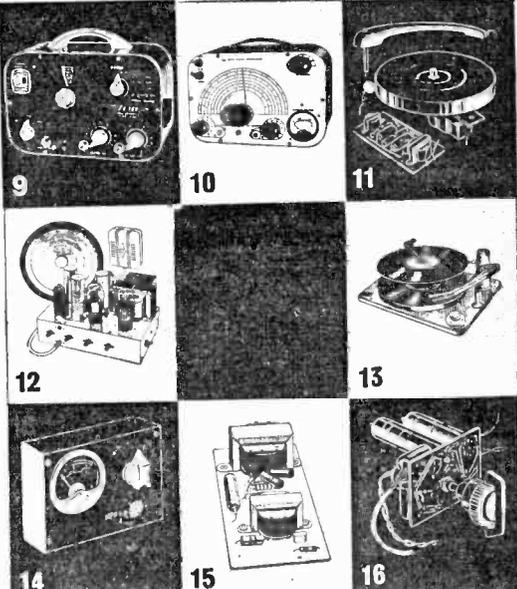9. **BATTERY RECORD PLAYER AND AMPLIFIER.** 45 r.p.m. "Star" motor "Acas" crystal pick-up, 3 transistor push-pull amplifier complete with transistors. Output 500 milliwatts, 49/6. P. & P. 4/-.
10. **8-watt PUSH-PULL 5 VALVE AMPLIFIER.** A.C. mains 200-250 v. Size 10 1/2 x 5 1/2 x 2 1/2 in. 5 valves. For use with all makes and type of pick-up and mike. Negative feed back. Two inputs, make and gram. and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. ± 2 db; 4 db down to 20 kc/s. Output 8 watts at 5 per cent total distortion. Noise level 40 db down all burn. Output transformer tapped for 3 and 15 ohms speech coils. For use with std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls. £3.19.6 P. & P. 6/-. Crystal mike to suit 15/-, P. & P. 2/- 8in. P.M. Speaker to suit 12/6, P. & P. 2/-.
11. **B.S.R. MONARCH US WITH PUL-PI HEAD.** 4-speed, plays 10 records 12in., 10in., or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position: colour, brown Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in. below baseboard 2 1/2 in. Fitted with Pul-Pi turnover crystal head. £6.19.6, P. & P. 6/6 With Stereo Head £7.19.6. P. & P. 6/6.
12. **TRANSISTOR TESTER.** For both P.N.P. and N.P.N. transistors incorporating moving coil meter. In metal case, size 4 1/2 x 3 1/2 x 1 1/2 in. Scale marked in gain and leakage. 19/6. P. & P. 3/-.
13. **PUSH-PULL OUTPUT STAGE** inclusive of transistors with input and output transformers to match 3 ohms speech coil, suitable for use with the **POCKET RADIO.** Set of parts, including transistors. 19/6. P. & P. 2/-. Wiring diagram 1/6, free with parts.
14. **PORTABLE AMPLIFIER.** On printed circuit for A.C. Mains 200/250 v: Size 4 x 3 in. with tone and volume control. Complete with Valves, ECL82 and EZ80. Output 2 watts. 39/6, P. & P. 3/-.



**RADIO & T.V. COMPONENTS**  
(Acton) LTD.

**23B HIGH STREET, ACTON LONDON, W.3.**

ALL ENQUIRIES S.A.E.  
GOODS NOT DISPATCHED OUTSIDE U.K.

**A 6-TRANSISTOR RADIO FOR ONLY £7.19.6**

The "Leeco"—a compact pocket portable. Carefully designed and precision built to give sharp station selection and good fidelity. Size only 4" x 2 1/2" x 1 1/2". Built-in Aerial, 6 transistors plus 1 diode and thermistor. 2 1/2" P.M. Speaker and socket for earphone. Supplied complete with 9V. battery in attractive presentation box. Optional extras: Miniature earphone 8/6. Plastic cover 2/6. P. & P. 2/6.



**ANOTHER RELDA SPECIAL!**

**PORTABLE TAPE RECORDERS**

Weight only 2 1/2 lbs. Operated by standard dry batteries. These beautiful machines are supplied complete with earphone for monitoring or playback, ultra sensitive microphone and ready for immediate use. S.A.E. for further details.



**ONLY £11.19.6**

P. & P. 3/6.

**CF-221 HETERODYNE CRYSTAL CONTROLLED FREQUENCY METER**

Frequency range: 125 Kcfs to 20 Mcfs. Calibration. Individual Calibration Books and numerous Crystal Check Points. Accuracy: 0.01% or 25 cycles. Power supplies: 6 v. and 135 v. batteries. Size 1 1/2 x 1 1/2 x 9 1/2 in. Weight 43 lbs. Offered at the ridiculous price of only **£16 CARR. PAID.**

**SF-30 RADIO HEADPHONES**

Hi-impedance—2,000 ohms—general use headset. Black and ivory plastic cased electro-magnetic units with adjustable headband for comfortable fit. Individual listening for all types of applications. Individually packed, with flexible cord attached. 14/6. post paid.



**ONLY 60/- Per Set P. & P. 4/-**

**PORTABLE TRANS/RECEIVER SETS**

Consisting of trans/receiver covering 7.4-9 Mcfs range up to 10 miles, complete with 5 valves headphones, microphone, function box and 6ft. telescopic aerial. Only requires 120 v. and 3v. dry battery.

**TWO FOR £6. Post Free. BATTERIES 20/- per set.**

**ALL TRANSISTOR 3-STATION INTERCOM & BABY ALARM**



**MODEL T1. 30/2**

**10 Gns.** Complete with battery and 60ft. of wire.

An intercom system for both calling and conversing, operated from a single battery. Ideal Baby Alarm. Brief spec: 3 transistors, 200 mW output, 2 1/2 in. speakers etc., etc. S.A.E. for further details.

**TRANSISTOR SET "MUST" TUBULAR RAFFLE EXTENSION SPEAKER MODEL ST-30** Designed for use with transistor radios etc. Complete with 12ft. extension cord, fitted with miniature plugs. Size 3 1/2 in. x 3 1/2 in. dia. As fully described January issue, ONLY 57/6. P. & P. 2/6.

**12v. VIBRATOR PACK.** (Supply Unit No. 9.) As used with P.C.R. Receivers giving 250 v. output at 80 mA. Fully smoothed. Size 10 x 8 x 8 in. ONLY 25/- Each. P. & P. 5/-.

**19 SET MK. III POWER SUPPLY.** With 2 dynamotors. H.T. 31. 12 v. input, 250 v. output at 125 mA. H.T. 32. 12 v. input, 450 v. output at 60 mA. DON'T MISS THIS BUY! ONLY 25/- P. & P. 5/-.

**OPERATORS UNIT.** Fantastic Bargain, exceptional offer! As illustrated. 3/6. **POST PAID.**




**"BOAT SHAPE" AERIALS.** Ideal model control aerial. Complete with 3-pin connector and EASD diode. Must be tried at 2/6. **EACH P. & P. 1/-.**

**V.H.F. MOBILE AERIAL** and base with PYE connections, 27in. overall, as used by Taxis, Police, etc., 7/6.

**U.S.A. WHIP AERIALS** 12ft. 10/- **COMPLETE HEADPHONE and MICROPHONE ASSEMBLY** 10/- P. & P. 3/6.

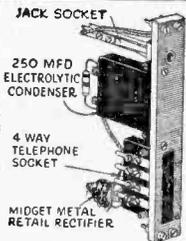**INSTANT VALVE FILAMENT TESTER, MODEL VT-41.**


Pocket-size, battery operated. Gives instant check of: All radio valves; All TV valves; All TV and Radio tubes; Circuit continuity; All Pilot lamps. Has built-in miniature 7- and 9-pin valve straighteners and battery test. \*International Octal, B.8, B.9, B.7. Battery and Mats types. Beautifully styled—precision made. Supplied complete. Fully guaranteed. **ONLY 30/- Post Paid.**



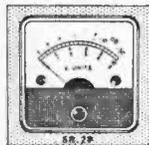**MINIATURE CLEAR PLASTIC PANEL METERS**

**"S" METER MODEL SR. 2P.** Standard "Ham" Signal strength indicator. Calibrated in "S" units from 0-8 with scale terminating in + 10 to + 30 db calibrations. Additional full scale calibrations of 0-5 + 0-10 in linear scale divisions. A "must" for radio amateurs for conversion of any Communication Receivers with A.V.C. action to give calibrated signal strength action, 35/-.

**VU METER MODEL VR. 1P.** Calibrated and damped in accordance with standard VU Meter Practice. Upper scale reads -20 to +3VU. Lower scale 0-100% modulation. Uses precision carbon film multiplier resistor and full wave rectifier. 42/6.



**DC MICROAMMETERS** Model MR.25 0 to 50 uA. 39/6  
Model MR.250 0 to 500 uA. 32/6  
**DC MILLIAMMETER** Model MR.21 0 to 1mA. 27/6  
All models Individually Boxed and Fully Guaranteed. P. & P. 2/6 each.

**EP.10K MULTI-METER**

10,000 O.P.V. on BOTH A.C. and D.C. Ranges; D.C. Voltage: 0-6-30-120-600-1,200 v. (10,000 o.p.v.). A.C. Voltage: 0-6-30-120-600-1,200 v. (10,000 o.p.v.). D.C. Current: 0-120 uA. 0-12-300 mA. Resistance: 0-20K. 0-2 Meg. (150 ohm, 15K at centre scale). Capacitance: 0.005 to 0.15 uF (at A.C. 6 v.). Decibels: -20 to +63db (600 ohms 1 mW, odsm -0.775 v.). Accuracy: D.C. voltage and current ± 2% f.s. A.C. Voltage ± 4% f.s. Resistance ± 3% of total scale length. Size: 4 1/2 in. x 3 1/2 in. x 1 in. Complete with test leads, battery and instructions. **ONLY £5-19-6. Post Paid.**



**PORTABLE MAINS SOLDERING IRON MODEL SPI**



30 watts. Designed on an entirely new principle for lightweight applications. Highly stable heat characteristics ensure long life and safety in use. The Model SPI features a removable handle that may be used to cover the tip and barrel to permit the iron to be carried safely even while hot. Supplied complete with Vinyl bar, mains lead and plug. All for only 18/6.

MAIL ORDERS TO  
(DEPT. P.), 32a COPTIC STREET,  
LONDON, W.C.1



CALLERS WELCOME AT  
87 TOTTENHAM COURT ROAD,  
LONDON, W.1  
MUS 8606

# REDA OFFERS THE GREATEST VALUE IN MINIATURE COMPONENTS FOR THE 'KIT FAN'

**MAINS 3 AMP. DP/DT TOGGLE SWITCH** with on/off plate. 4/- each.

**LAPEL MICROPHONE M178**  
Precision engineered Crystal Microphone —for lapel or hand use. Only 1 1/2 in. diameter. Exceptionally sensitive. Chrome plated case and clip includes 5ft. shielded cable. Only 17/6.



**TRANSISTOR SPECIAL! 5K. EDGEWISE MINIATURE VOLUME CONTROL MODEL K2.16.** with switch and ivory knob. As used in all miniature transistor radios. 4/6 each.

**P217A.**

**MINIATURE 3 1/2 in. S P E A K E R**

A miniature Hi-Fi speaker that outperforms all others. Designed to meet today's requirements for transistor, miniature and sub-miniature applications. Size 2 1/2 in. sq. x 1 in. deep. Voice coil impedance 18 ohms. Freq. range: 150-5000 c/s. Power: 200mW. 15/6.

**NO. 7 MOVING COIL MICROPHONE INSERTS.** Ultra sensitive. As used in many Govt. Microphones! Size 1 1/2 in. dia. x 1 1/2" deep. Brand new and guaranteed. 8/6 each.

**HOOVER ROTARY TRANSFORMERS**  
12 v. input, 500 v. output at 65 mA. or 8v. input 250 output at 75 mA.  
Only 10/6 each. P. & P. 2/-.

**HI-FI HEADPHONES**  
These miniature Hi-Fi phones use high quality permanent magnetic speakers with regulated voice coil. The soft rubber ear moulds give correct spacing for optimum acoustic load. Each unit has a built-in miniature Hi-Fi transformer to ensure the finest music and voice reproduction. Supplied free in a small impedance up to 4000 ohms. Only 15/- P. & P. 2/6.



**JUST ARRIVED!**

**9V. BATTERY CHARGER & A.C. ELIMINATOR MODEL LA.6P**

A "MUST" for every transistor set owner!



Save those batteries during the winter by running your transistor set direct from A.C. Mains. Reactivate all your old 9V batteries.

Unit contains neon indicator and standard battery connections with nearly 2 yards of mains lead and plug. Also snap cord for connection to set.  
**LIMITED QUANTITY OFFERED FOR THE FIRST TIME IN THIS COUNTRY!** **29/6** P. & P. 1/6




**MINIATURE EARPHONE**

A really sensitive dynamic earphone of exceptionally fine quality. Provides clear reproduction of music as well as speech. Fully Guaranteed and complete with transparent ear insert, 3 feet cord, sub-miniature plug and socket.  
CR-5 High imp. crystal **8/-** Each  
MR-4 Low imp. magnetic **8/-** Post 1/-

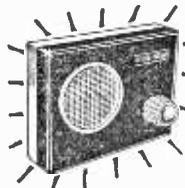**SUB-MINIATURE TRANSFORMERS**

Here is outstanding value in transistor transformers consisting of one Driver Transformer and one Output Transformer. Ideal pair for miniature transistor portables, etc.  
Driver Model LT44: Primary: 20k. Secondary: 1k. Centre Tapped. Ratio: 5:1.  
Output Model LT700: Primary: 1.2k. Centre Tapped. Output: 3.2 ohms. Ratio: 2:1. Complete with detailed instructions. Only 9/6 per pair. P. & P. 1/6.



**SUPER TRANSISTOR RADIO With Miniature Speaker.**

Simple instructions enable anyone to build this miniature radio. Gives reception over the entire broadcast band. Each kit is supplied with all latest miniature parts including:  
★ two transistors ★ ferrite rod speaker ★ coloured plastic case ★ step by step illustrated instructions. Size 4 x 3 x 1 1/2 in.  
**ONLY 27/6** P. & P. 1/6. Battery 1/- ex.


★ Made available owing to public demand! ★

**CRYSTAL MICROPHONE INSERTS MODEL MCL1.** Precision disc type crystal microphone cartridge. Output: -53dB. Response: 100-6,000 c.p.s. PRICE 6/6.



**MINIATURE DP/DT SLIDE WAVE-CHANGE SWITCH** 2/6 each.

**SUB-MINIATURE PLUG AND SOCKET**

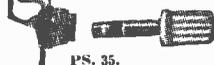

PS. 35.

Two-way bakelite barrel Jack Plug only 1 in. long. Socket only 1 in. long. 3/6 per pair. Post paid.

**CIL305 CHROME MINIATURE PLUGS AND SOCKETS**

Size: plug barrel 1", socket 1". These will give your equipment that expert finish! 3/6 Per Set.

**SLIM RADIO PLUGS AND SOCKETS**

Two-way, black bakelite, solder terminal PLUG and STURDY standard SOCKET. 5/6 per pair. Post Paid. Panel mounting, neat finish.

**AERIAL VARIOMETERS**  
These magnificent instruments will enable you to receive maximum signal strength on all S.W. receivers. Precision, calibrated control 12/6. P. & P. 2/6.



**SPARE VALVE KIT**

Here's a gift for all 38 and 18 Set owners! Case containing 4 ARP2 & 1 A T P 3 valves. Only 10/- P. & P. 2/6.



**ACCUMULATORS.** 2 volts 16 A.H. (unsplittable). Ideal for 6 and 12 volts supply, etc. Brand new. Original cartons. Size 4 1/2 in. x 2 1/2 in. 5/6 each. P. & P. 1/6. 3 for 15/- P. & P. 3/6. 6 for 27/6. P. & P. 5/-.



## PYE COMMUNICATION RECEIVERS

World coverage on these famous Communication Receivers. They are the simplest type to use yet bring in stations that will amaze you. The ideal domestic receiver for medium wave during the day with Amateur stations at night. All have been converted to 230 v. A.C. mains and are guaranteed to work immediately. Incorporate Wave Switch, Audio gain aerial trimmer, high and low tone control, station locking device, aerial and earth inputs, speaker output sockets, etc. Size 17 x 8 x 9 1/2 in. Black crackle finish front panel. On demonstration at 87 Tottenham Court Road.

**P.C.R.2.** Medium and long waves and 6-23 Mc/s. Less speaker.  
**P.C.R.** Medium and long waves and 6-18 Mc/s. With speaker.  
(All the above P.C.R. Receivers Have been completely reconditioned).

**ONLY £8.19.6**  
EACH TYPE



Plus Carriage 10/6 ★ Order Early!

MAIL ORDERS TO  
(DEPT. P.) 32a COPTIC STREET,  
LONDON, W.C.1



CALLERS WELCOME AT  
87 TOTTENHAM COURT ROAD,  
LONDON, W.1 MUS 9806

## R.S.C. HI-FI TAPE RECORDER KIT


**REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN HALF AN HOUR**  
The Recorder Incorporates the Latest Collaro Studio Tape Transcriber, The Linear LT45X High Quality Tape Amplifier listed £12.12.0 High Flux P.M. Speaker listed 30/-, empty Tape Pool, a Reel of tone polychrome finish, size 18 x 13 x 9in. high, a Handsome Portable carrying Cabinet with latest attractive two-tone individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflet.



## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

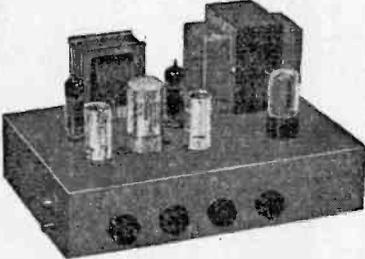**PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES**

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, 5Y3. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response +3 D.B. 30-30,000 c/s. Six negative feedback loops. For 2 and 15 ohm speakers. ONLY 3 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For STANDARD or LONG PLAYING RECORDS For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS, etc. OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a RADIO FEEDER UNIT. Size approx. 12-9-7in. For A.C. mains 200-250 v. 50 c.p.s. Output instructions and point-to-point wiring diagrams supplied. Only 8 Gns. Carr. 10/-



**25 1/2 GNS.**  
Carr. 17/6

**H.P. TERMS.** Deposit £5.7.6 and 12 monthly payments of 2 gns. Cash price if settled in 3 months.

**TELEVISION RECTIFIERS** 250 v. 200 mA. small size. Only 6/8 each.  
**COLLARO CONQUEST 4-SPEED AUTO-CHANGER**, with high fidelity Studio pick-up. Latest model. For 200-250 v. 50 c.p.s. A.C. mains. Our price £6.19.6. Carr. 5/6.


**COLLARO RC 457 4 SPEED MIXER AUTO-CHANGERS**, Turnover Studio Pick-up head, for 200-250 v. A.C. £7.19.6. Carr. 4/6

**THE SKYFOUR T.R.F. RECEIVER.** A design of a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6X7, 5P81, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-point wiring diagrams, instructions and parts list, 1/9. maximum building costs £4.19.6. inc. attractive Walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

**6.3A MINIATURE 2-3 WATT GRAM AMPLIFIER.** For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. A.C. mains. Size 11 x 2 1/2 x 2 1/4 in. Controls: Vol. and Tone with switch. Only 5/6.

If required louvred metal cover with 2 carrying handles can be supplied for 19/8. TERMS S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets. Speakers. Microphones, etc., with cash and credit terms.
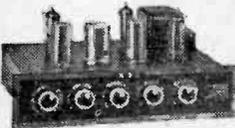
## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 30 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" (monaural) 10 watt amplifier. Is made for use as straight "mono" and "out". Provision for 2-3 ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/-

Kit can be supplied assembled, ready for use, for 59/6 extra.

## R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250v., 50c/s. Guaranteed 12 months.

**HEAVY DUTY CHARGER KIT** 6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-230-250 v. F.W. (Bridge) Selenium Rectifier. Ammeter. Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit, 59/6. Carr. 4/6



**Assembled 6/12v. 4-5 amps.**  
Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with stoved blue hammer finished. Fused, and ready for use with mains and output leads. Terms: Deposit 13/3 and 5 monthly payments 12/3. 6/12 v. 3-4a., all facilities as above. 59/9. carr. 3/9

**ASSEMBLED CHARGERS**  
6 v. or 12 v. 2 amps.

**BATTERY CHARGER KITS** Consisting of Mains Transformer. F.W. Bridge. Metal Rectifier well ventilated steel case. Fuses. Fuse-holders, Chromels, panels and circuit. Carr. 3/6 extra

**DEAF AID EARPIECES.** Low Impedance with lead. 8/9. High Impedance Crystal 6/9.

**MICROPHONE INSERTS.** Crystal type 6/9.

**SOLDERING IRONS.** 230-250 v. 30 watts. First quality. For Radio work, 19/9. Spare elements and bits available.

Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case finished attractive hammer blue. Ready for use with mains and output leads.  
Double Only Fused. Carr. 3/9 **49/9**

6v. or 12v. 1 amp. .... 24/9  
As above, with Ammeters 32/9  
6 v. or 12 v. 2 amps. .... 25/9  
6v. or 12v. 2 amps. .... 31/6  
6v. or 12 v. 2 amps. including Ammeter ..... 42/9  
6v. or 12 v. 4 amps. with Ammeter and variable charge rate selector ..... 59/9  
**CHARGER AMMETERS.** 0-15 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a., 0-60 a. 8/9.

## R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

**Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened TOP SHROUDED DROP THROUGH**  
250-0-250 v. 70 mA. 6.3 v. 2 a. 5 v. 2 a. 17/9  
350-0-350 v. 100 mA. 6.3 v. 2 a. 5 v. 2 a. 18/9  
230-0-230 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 19/9  
250-0-250 v. 100 mA. 6.3 v. 2 a. 6.3 v. 1 a 21/9  
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 25/9  
300-0-300 v. 130 mA. 6.3 v. 4 a. 6.3 v. 1 a. for Mullard 510 Amplifier ..... 29/9  
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9  
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 26/9  
0-4-5 v. 3 a. .... 26/9  
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 29/9  
**FULLY SHROUDED UPRIGHT**  
250-250 v. 60 mA. 6.3 v. 2 a. 5 v. 2 a. Midget type 21-3-31n. 17/11  
250-0-250 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 27/9  
300-0-300 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 27/11  
350-0-350 v. 100 mA. 6.3 v. 4 a. 5 v. 3 a. 27/11  
350-0-350 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 35/9  
425-0-425 v. 200 mA. 6.3 v. 4 a. C.T. 5 v. 3 a. 6.3 v. 4 a. C.T., 5 v. 3 a. .... 49/9

**MIDGET MAINS** Primaries 200-250 v. 50 c/s.  
250 v. 60 mA. 6.3 v. 2 a  
250-0-250 v. 60 mA. 6.3 v. 2 a. .... 11/9  
Both above size 21 x 21 x 2 1/4 in. .... 12/9  
**SMOOTHING CHOKES**  
150 mA. 7-10H 250 ohms ..... 11/9  
100 mA. 10 H 250 ohms ..... 8/9  
80 mA. 10 H 350 ohms ..... 5/9  
120 mA. 10 H 400 ohms ..... 4/11  
**PARMEKO POTTED TYPES**  
200 mA. 12 H 200 ohms ..... 16/9  
120 mA. 30 H 200 ohms ..... 16/9  
120 mA. 8 H 500 ohms ..... 13/9  
**CHARGER TRANSFORMERS**  
All with 200-230-250 v. 60 c/s Primaries:  
0-9-15 v. 1 a. 11/9; 0-9-15 v. 2 a. 14/9; 0-9-15 v. 3 a. 16/9; 0-9-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 23/9; 0-9-15 v. 8 a. 28/9.  
**ATU (step up/step down) TRANS.**  
0-110/120-220/250 v. 50 watts, 13/9;  
150 watts, 27/9. 250 watts, 39/9.  
**MICROPHONE TRANSFORMERS**  
120:1 high grade, clamped, 6/9; 120:1 Potted. Mu-metal screened, 9/9.

# R.S.C. (Manchester) Ltd. HULL, LIVERPOOL, LEEDS, BRADFORD, MANCHESTER

## R.S.C. A12 STEREOGRAPHIC AMPLIFIER KIT WITH TWIN SPEAKERS

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied.

**STEREO EQUIPMENT OFFER:**  
Comprising A12 Kit, 2 matched 8in. L/Speakers, and Acos T70 Stereo head suitable most pickups.  
**£6.19.6**  
Carr. 7/6.

**PICK-UP ARMS** complete with Hi-Fi turnover crystal head. Acos GP54. Limited number brand new. perfect at approx. half price. Only 29/11.

**ACOS CRYSTAL MICROPHONES.** Micro stand or desk. Listed 35/-, Only 27/9. 39-1 8" Stick type. Listed 3 gns. Only 39/6.

**R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10**  
A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response  $\pm 3$  db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen or available. Six valves are used EF86, EF86, EC83, 807, 807, GZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. It can be used with ORGANS, GUITAR, STRING BASS etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT.

An extra input with associated vol. control is provided so that two separate inputs such as Gram, and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 or 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months guarantee, for 14 Gns.

**TERMS: DEPOSIT 39/9 and 9 monthly payments of 39/9.**

Suitable microphones and speakers available at competitive prices.

**FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.**

**COLLARO JUNIOR** 4-speed single player units and Hi-Fi crystal pick-up with turn-over head, £3.19.6.

**B.S.R. UAS 4-SPEED AUTO-CHANGERS** with Hi-Fi turnover pick-up head, £6.19.6. Carr. 5/-.

**TERMS: DEPOSIT 39/9 and 9 monthly payments of 39/9.**

Suitable microphones and speakers available at competitive prices.

**FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.**

**COLLARO JUNIOR** 4-speed single player units and Hi-Fi crystal pick-up with turn-over head, £3.19.6.

**B.S.R. UAS 4-SPEED AUTO-CHANGERS** with Hi-Fi turnover pick-up head, £6.19.6. Carr. 5/-.

**TERMS: DEPOSIT 39/9 and 9 monthly payments of 39/9.**

Suitable microphones and speakers available at competitive prices.

**FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.**

**COLLARO JUNIOR** 4-speed single player units and Hi-Fi crystal pick-up with turn-over head, £3.19.6.

**B.S.R. UAS 4-SPEED AUTO-CHANGERS** with Hi-Fi turnover pick-up head, £6.19.6. Carr. 5/-.

**TERMS: DEPOSIT 39/9 and 9 monthly payments of 39/9.**

Suitable microphones and speakers available at competitive prices.

**FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.**

**COLLARO JUNIOR** 4-speed single player units and Hi-Fi crystal pick-up with turn-over head, £3.19.6.

**B.S.R. UAS 4-SPEED AUTO-CHANGERS** with Hi-Fi turnover pick-up head, £6.19.6. Carr. 5/-.

**TERMS: DEPOSIT 39/9 and 9 monthly payments of 39/9.**

Suitable microphones and speakers available at competitive prices.

**FULL RANGE OF LINEAR AMPLIFIERS ALWAYS IN STOCK.**

**COLLARO JUNIOR** 4-speed single player units and Hi-Fi crystal pick-up with turn-over head, £3.19.6.

**B.S.R. UAS 4-SPEED AUTO-CHANGERS** with Hi-Fi turnover pick-up head, £6.19.6. Carr.

# SENSATIONAL NEW 1961 DESIGNS—BY CONCORD

## LOW PRICES ★ PICTORIAL STEP-BY-STEP PLANS ★ EASY AS A.B.C.

### THE NEW "LISBON"

#### TRANSISTOR SET

This is a pocket 2-stage transistor set not much larger than a matchbox. **19/6**

Excellent clear reception covering all medium waves, works for months on a tiny 1½ or 3 volt battery costing only 3½d. Easy to build and an excellent introduction to transistor circuitry. Everything can be supplied down to the last nut and bolt incl. **SIMPLE PICTORIAL STEP-BY-STEP PLANS FOR ONLY 19/6**, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.



### THE NEW "FLORIDA" VALVE RADIO

This sensational "FLORIDA" model is one of our most sensitive valve radios. It is a highly compact, self-contained miniature push button base, valve pocket radio at absolutely rock bottom building cost. Covers all medium waves with very latest circuitry including 10 stations from all over Europe without fuss. Size only 4½ x 2½ x 1½ in. A fascinating pocket radio. We can supply all the parts including beautiful 2-tone case and **SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS**, screws, wire, etc. Can be built for the exceptionally **LOW PRICE OF 27/6**, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.


**27/6**



### OUR NEW 4 STAGE "MINUETTE"

Build this newly-designed "MINUETTE" 4-STAGE transistor set in very strong readily drilled **ULTRA-MODERN CASE**, size only 6 x 3½ x 1½ in. Uses three transistors and diode and **SELF-CONTAINED LOUD SPEAKER**. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening on an 8d. battery. Can be built **FOR ONLY 39/6**, including **PROPER CASE**, mature speaker, etc. **SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS** etc., plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**39/6**

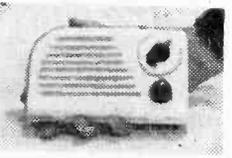

### THE NEW "SAN REMO" ONLY 32/6

This All Transistor Speaker Radio—the "San Remo"—covers all medium waves including "Home," "Light," etc. Reliable and lightweight—Slips easily into the Pocket or Handbag—size only 4½ x 2½ x 1½ in! Works for Months on 8d. Battery! Ideal for holidays, Camping, Bedroom, etc. Anyone can assemble it in an hour or two with our **simple-as-ABC PLANS!** Complete set of parts including miniature speaker—everything—only 32/6, plus 2/6 P. & P. (C.O.D. 2/- extra.) Parts can be bought separately.



**CONCORD ELECTRONICS Dept. PW39**  
210, Church Road, Hove, Sussex

Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and values stocked. Regret no C.O.D. abroad. **DEMONSTRATIONS DAILY AT WORKS.**

# FREE TO AMBITIOUS ENGINEERS

## — THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

**Have you sent for your copy?** **ENGINEERING OPPORTUNITIES** is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the **B.I.E.T. School of Electronics**, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee**  
**"NO PASS — NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Incorporating E.M.I. Institutes)  
(Dept. SE/21), 29 Wright's Lane, London, W.8

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

### WHICH IS YOUR PET SUBJECT ?

- Mechanical Eng.,
- Electrical Eng.,
- Civil Engineering,
- Radio Engineering,
- Automobile Eng.,
- Aeronautical Eng.,
- Building, Plastics,
- Draughtsmanship,
- Television, etc.

### GET SOME LETTERS AFTER YOUR NAME!

- A.M.I. Mech. E.
- A.M.I. C.E.
- A.M.I. Prod. E.
- A.M.I. M.I.
- A.I.O.B.
- A.F.R. Ac. S.
- B.Sc.
- A.M. Brit. I.R.E.
- City & Guilds
- Gen. Cert. of Education
- Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of **B.I.E.T.** (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

### B.I.E.T. SCHOOL OF ELECTRONICS

### POST COUPON NOW!

- Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
- (Write if you prefer not to cut page)

NAME .....

ADDRESS .....

SUBJECT OR EXAM THAT INTERESTS ME ..... (SE/21)



★ VALVES BY RETURN OF POST ★ THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in block type (15% in dozen), Post: 1 Valve, 6/-, 2-11, 1/-.

NEW LOW PRICES GUARANTEED 3 MONTHS

FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-export origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

Table listing various vacuum tube types and their prices, including models like 6X4, 6X5, 6X6, 6X8, 6X9, 6X10, etc.

Tubes HIGHEST QUALITY—COMPARE OUR PRICES... GUARANTEED... Table with columns for tube types and prices.

13 Channel TV's—Absolutely Complete... These Sets are unequalled in value... 12" £21.90... 14" £41.90... "NUMATIC" CAR RADIO... HEADPHONES... AMPLIFIERS


LOUDSPEAKERS... PM SPEAKERS... 1,000 YDS. ASSAULT CABLE... VALVES ALL GUARANTEED 3 MONTHS... COMPLETE RECORD PLAYERS... RENEW YOUR PICK-UP

B.B.C./I.T.A. AERIALS... RECORDING TAPE... TORCHES... AERIAL OSCILLATOR COILS... SILICONE DIODES... RECTIFIERS

EXTENSION LOUDSPEAKERS... POWER CABLE... P.V.C. WIRE SPECIAL BARGAIN... GO-AX... 100 RESISTORS... 100 CONDENSERS

Post: 2 lbs. 2/-. 4 lbs. 2/6. 7 lbs. 3/-. 15 lbs. 4/-. etc. No C.O.D. ALL ITEMS 5% & POST FREE IN DOZENS (Callers always welcome). LIST OF 1000 SNIPS 6d. P.O. BOX (21)W 350-352 FRATTON ROAD, PORTSMOUTH.

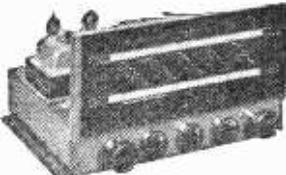**ARMSTRONG AF208 AM/FM RADIOGRAM CHASSIS**



★ Full VHF Band (87-108 Mc/s and Medium Band, 187-570M) ★ 7 Valves ★ 5 Watts Output ★ 15db Negative Feedback ★ Separate wide range Bass and Treble Controls ★ 2 Compensated Pick-up Inputs ★ Frequency Response 30-22,000 c.p.s. +2db ★ Tape Record and Playback Facilities ★ Continental Reception of Good Programme Value ★ For 3, 7, and 15 ohm speakers. Send S.A.E. for leaflet.

**PRICE 22 GUINEAS Carr. Free**

**LATEST "EMI" 4 SPEED SINGLE RECORD PLAYER**

Acos Hi-Fi Pick-up for LP. and/or 78, 7, 10 and 12in. records. Silent motor. heavy turntable, auto stop. Complete on Baseplate.

Special offer **£6.5.0** post free.

or with Stereo/Monaural pick-up **£8.19.6**.

**SINGLE-PLAYER BARGAIN**

Ready-built, complete with BSR T9 4-speed gram pick-up unit. Handsome portable case. 3-watt amplifier with 2 valves and speaker. List price **£12.12.0**. OUR PRICE **£9.9.0**. Post 4/- Fully guaranteed in manufacturer's sealed cartons.

**New Boxed VALVES 90-day Guarantee**

1R5	7/6	6K9Q	7/6	EA50	1/6	EZ80	7/8
1R5	7/6	6L6G	10/6	EAB080	8/6	E1148	1/8
1T4	8/-	6N7M	8/6	EB91	6/-	HABC80	
2X3	3/6	6QT9	8/6	EB333	8/6		12/6
3R4	7/6	6SA7	6/-	EB341	3/6	HV22A	6/8
3V4	7/6	6SL7M	6/6	EBF80	10/-	MU14	9/-
5U4	7/6	6N7	6/6	ECC34	9/6	PC084	9/6
5Y3	7/6	6V6G	6/6	ECP80	9/6	PCF90	9/6
5Z4	9/6	6X4	7/6	ECH42	10/6	PL82	11/6
6AM6	5/-	6X5	6/6	ECL30	10/6	PEN25	6/6
6B8	5/-	12A6	7/6	ECL32	10/6	PL81	12/6
6BE9	7/6	12AT7	8/-	EF39	5/6	PL82	10/6
6BH6	9/6	12AU7	8/-	EF41	9/6	PY80	7/6
6BW6	9/6	12AX7	8/-	EF50	5/6	PX81	9/6
6C6	8/-	12BE6	8/6	EP80	8/-	PY93	7/6
6F4	7/6	12K7	6/6	EP86	12/6	SP61	3/6
6H6	3/6	12Q7	6/6	EP92	5/6	UCD41	9/6
6J3	5/6	35L6	9/6	EL32	5/6	UCH42	9/6
6J6	5/6	35Z4	7/6	EL41	9/6	UL41	9/6
6J7G	6/6	35Z4	9/6	EL44	9/6	UL41	9/6
6K6GT	6/6	807	5/6	EY51	9/6	UY41	8/6
6K7G	5/-	954	1/6	EZ40	7/6	UZ22	8/-

**SETS OF VALVES**

DK95, DF96, DA96, DL96, 8/6 each or 27/6 set.
1R5, 1T4, 1R5, 3R4 or 3V4. 19/6
6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5. 27/6
ECH42, EF41, EBC41, EL41, EZ40. 37/6
ECH81, EF80, ECH81, EL84, EZ80. 39/6
12K9, 12K7, 12Q7, 35L1, 35Z4. 35/-

**NEW ELECTROLYTICS FAMOUS MAKES**

TUBULAR	TUBULAR	CAN TYPES	
1350V	2/-	30/350V	5/6 16/45V
2350V	2/6	100/25V	3/- 32/350V
4450V	2/8	250/25V	3/- 100/270V
8450V	3/5	500/12V	3/- 2,000/8V
8500V	2/9	8+8450V	3/6 5,000/8V
16450V	3/-	8+8500V	5/- 32+32/350V
16500V	4/-	8+16450V	3/9 32+32/450V
32450V	3/8	8+16500V	5/6 32+32+32/350V/7-
25/25V	1/9	16+16/450V	4/3 50+80/350V
50/25V	2/-	16+16/500V	6/- 64+120/350V
50/60V	2/-	32+32/350V	4/6 100+200/270V

**C.R.T. BOOSTER TRANSFORMERS**

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission. Full instructions supplied.

Type A. Optional 25% and 50% Boost. 2V or 4V or 6.3V or 10.8V or 13.5V Mains input. 12/6  
Type A2. High quality, low capacity. 10/15pF. Optional boost 25%, 50%, 75%. Mains input. 16/6

Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 10 and 18V. Boost 25% and 50%. This transformer is suitable for all TV tubes, 21/- each.

**COMPLETE RADIO**

**£4.19.6 post free**



4 Mullard valves, 5in. speakers, frame aerial, 4 pre-set stations, 1 long, 3 med. wave. Superhet Circuit. Size 9 x 6 x 5 1/2 in. high. Tested ready for use. 200/250 v. A.C.—D.C. Mains.

**MAINS TRANSFORMERS 200/250 v. A.C.**

STANDARD, 250-0-250, 80 mA, 6.3 v. 3.5 a. tapped 4 v. 4 a. 22/6
2 in or 4 v. 2 a. 22/6 ditto, 350-0-350 .. 28/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a. .. 10/6
MIDGET, 220 v. 45 mA, 6.3 v. 2 a. .. 15/6
SMALL, 220-0-220, 50 mA, 6.3 v. 2a .. 17/6
STD., 250-0-250, 65 mA, 6.3 v. 3.5 a .. 17/6
HEATER TRANS. 6.3 v. 1 1/2 amp. .. 7/6
Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. .. 8/6
Ditto, sec. 6.3 v. 3 amp. .. 10/6
GENERAL PURPOSE LOW VOLTAGE, 2a, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. .. 22/6
AUTO TRANSFORMERS, 150 w. .. 22/6
0, 120, 200, 230, 250 v., 500 w. .. 22/6

O.P. Transformers, Heavy Duty 50 mA, 4/6. Miniature, push-pull, 7/6. Ditto, 10 w., 15/6. Miniature, 354m etc., 5/9. L.F. CROKES 15/10/11. 60/65 mA. 5/-; 10 H. 85 mA, 10/6; 10 H., 100 mA, 14/-.

**TELEVISION REPLACEMENT**

**Line Output Transformers**

from 45/- each, New Stock and other timebase components. Most makes available. S.A.E. with all enquiries.

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 3, 4, 5, 6, 8, 11 amp., 8/9; 11, 13, 17, 4 a. 12/6  
CHARGE TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps., 15/6. 2 amps., 17/6; 4 amps., 22/6. Circuit included.  
4 AMP CAR BATTERY CHARGER with amp meter Leads, Fuse Case, etc., for 6 v. or 12 v., 69/6.

**BOOKS list S.A.E.**

48 Circuits for Germanium Diodes 3/-  
"V.V.W." Radio Valve Data, 6/-  
High Fidelity Speaker Enclosure, 5/-  
Valve and TV Tube Enclosures, 9/6  
TV Fault Finding, 5/-  
Quality Amplifiers, 4/6  
Radio Valve Guide. Books 1, 2, 3 or 4 5/- each.  
Transistor Superhet Receivers, 7/6.  
Practical Radio for Beginners, 3/6.  
Master Colour Code Chart, 1/6.

**PYE STEREOPHONIC PLAYER**

Complete with Garrard TA MkII Stereo unit and self contained quality stereo amplifier, size 14 1/2" wide x 17" deep x 8 1/2" high. Brand new in maker's box with full instructions and guarantee. OUR PRICE **£12.10**. Carriage and insurance, 10/- Suitable for use with any two 8 ohm loudspeakers.

LOUDSPEAKER P.M. 3 OHM. 2 1/2, 2, 4in. 18/6. 5in. Rola, 17/6; 8in. Plessey, 19/6; 7in. x 4in. Rola, 18/-; 6 1/2in. Rola, 18/6, 10 x 6in. E.T.G. 10in. Rola, 30/-; 4in. Tweeter, 25/-; 12in. E.A. 30/-; 12 1/2 x 8in. 46/-  
STENTORIAN HP1012. 10in. 3-15 ohms, 10 w., 96/-.

**BAKER SELHURST LOUDSPEAKERS**

Details S.A.E.

12in. Baker 15w. Stalwart 3 or 15 ohms, 46-13,000 .. 90/-  
12in. Baker Stalwart, foam suspension, 15 ohms, 40-13,500 c.p.s. .. 86/-  
12in. stereo, 12w., 56-16,000 c.p.s. .. 28/-  
12in. Baker Ultra Twelve, 20 c.p.s. to 26 kc/s, £17.10  
15in. Auditorium, 35 w., Bass. 20 c.p.s. to 12 kc/s, £15



TWIN GANG TUNING CONDENSERS. 365 pF miniature lin. x 1 1/2 in. x 1 1/2 in., 10/-, 500pF Standard with trimmers, 9/-; midget, 7/6; with trimmers, 9/-  
SMALL 3 gang 500 pF, 17/-

SINGLE 25 pF, 50 pF, 75 pF, 100 pF, 160 pF, 5/6. Solid dielectric 100, 500, 500 pF, 3/6; CONDENSERS. New stock, 0.003 mfd. 7 kv; T.C.C., 5/6; Ditto, 50 kv, 9/6; 0.1 mfd., 7 kv, 9/6; Tubular 500 v. 0.001 to 0.05 mfd., 9d., 0.1, 1/-; 0.25, 1.1/8; 0.5/500 v., 1/9; 0.1/350 v., 9d.; 0.01/2,000 v. 0.1/1,000 v., 1/9; 0.1 mfd., 2,000 volts, 3/8  
CERAMIC CONDS. 500 v., 0.3 pF to 0.01 mfd., 9d. SILVER MICA CONDENSERS. 10% 5 pF to 500 pF, 1/-; 400 pF to 3,000 pF, 1/8. Close tolerance. (< 1 pF) 1.5 pF to 47 pF, 1/8. Ditto 1% 50 pF to 815 pF, 1/9; 1,000 pF to 5,000 pF, 2/-.

**465 kc/s SIGNAL GENERATOR**

Total cost 15/-. Uses B.F.O. Unit, ZA 30038 ready made. POCKET SIZE 2 1/2 x 4 1/2 in. Slight modifications required, full instructions supplied. Battery 7/6 extra 69V +14V. Details S.A.E.

Wavechange Switches, 2 p. 2-way, 3 p. 2-way, short spindle, 2/6; 8 p. 4-way 2 water, long spindle, 6/6; 3 p. 5-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 6 p. 4-way, 1 p. 2-way, long spindle, 3/6;

Wavechange "MAKITS". Wafers available: 1 p. 12 wafer, 2 p. 6 wafer, 3 p. 4 wafer, 4 p. 3 wafer, 6 p. 2 wafer, 1 wafer, 8/6; 2 water, 12/6; 3 wafer, 16/6; additional wafers up to 14, 3/6 each extra.

Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-. Ex. Gov. s.p.d.t., 1/-.

**CRYSTAL MIKE INSERT**

By Acos 8/6 Precision engineered. Size only 1 1/2 in. dia. x 1 in.

ACOS CRYSTAL MIKE 40 .. 25/-  
DE LUXE STICK MIKE .. 35/-

Valveholders. Pax. int. oct., 4d. EA50, 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6, and 7 pin. 1. MOULDED Mazda and Oct., 6d.; 1. BTG, B8A, B9A, B9A, 9d. BTG with can, 1/8. B8A with can, 1/9. Ceramic EF50, BTG, B9A, int. oct., 1/-; BTG, B9A cans, 1/- each.

**THE ORIGINAL RADIO COMPONENT**

Our written guarantee with every purchase. Bus 133 or 68 pass door S.R. Stentorian Selhurst

**Volume Controls** 80 ohm **COAX**  
CABLE spaced  $\frac{1}{2}$  in.  
Semi-air spaced  $\frac{1}{4}$  in.  
Long spindle. Midget 2/-  
5 k ohms to 2 Meg. 4/6  
No. Sw. D.P.Sw. 6d. yd.  
3/- 4/6  
Linear or Log Tracks. Air Spaced. 1/- yd.

**TRIPLEXERS** Bands I, II, III ... 12/6  
**COAX PLUG** 1/- **LEAD SOCKET** 2/-  
**PANEL SOCKETS** 1/- **OUTLET BOXES** 4/6  
**BALANCED TWIN FEEDER** yd. 8d. 80 or 300 ohms.  
**DITTO SCREENED** per yd. 1/8. 80 ohms onlv.  
**WIRE-WOUND POTS**, 3 WATT. Pre-set Min. TV Type. All values 10 ohms to 25 K. 3/- ea. 30 K., 50 K., 4/-, (Carbon 30 K., to 2 meg., 3/-).  
**WIRE-WOUND 4 WATT Pots**, Long Spindle. Values, 50 ohms to 50 K., 6/6; 100 K., 7/6.  
**PHILIPS TRIMMERS**, 30 pF 1/-, TRIMMERS, Ceramic, 30, 50, 70 pF., 9d.; 100 pF., 15p pF., 1/3; 250 pF., 1/8; 500 pF., 750 pF., 1/6.  
**RESISTORS**, Preferred values, 10 ohms to 10 meg., 1 w., 4d.;  $\frac{1}{2}$  w., 4d.; 1 w., 6d.; 1 1/2 w., 9d.; 2 w., 1/-; **HIGH STABILITY**,  $\frac{1}{2}$  w., 1/-, 2/-, Preferred values, 10  $\Omega$  to 10 meg. Ditto 5%, 100  $\Omega$  to 5 meg., 9d. 5 watt **WIRE-WOUND RESISTORS** 1/8  
1 watt 25 ohms-10,000 ohms 2/-  
15 watt 25 ohms-10,000 ohms 2/-  
12.5K to 50K 10w ... .. 3/-

**AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE**

Double Play 7in. reel, 2,400ft	60/-	Spare Plastic
5in. reel, 1,200ft	37/8	Reels
Long Play 7in. reel, 1,800ft	35/-	3in. 1/8
5in. reel, 1,200ft	23/6	4in. 2/-
5in. reel, 900ft	18/6	5in. 2/-
Standard 7in. reel, 1,200ft	25/-	5 1/2in. 2/6
5in. reel, 800ft	16/-	7in. 2/6

"Instant" Bulk Tape Eraser and Head Defuzzer, 200/250 v. A.C. 27/6. Leaflet. S.A.E.

**Radio Screwdriver 5 in. 6d.**  
**Neon Mains Tester Screwdriver, 5/-**  
**Solder Radioread, 4d. yd., 1lb. 5/-**  
**Black Crackle Paint. Air drying, 3/- tin.**

**HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.**  
Tunable channels 1 to 5. Gain 18db. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCC84 valves if preferred.)  
**BAND III L.T.A.—Same prices.**  
Tunable channels 8 to 13. Gain 17db.

**Paxolin Panels, 10 x 8in., 1/8.**  
**Miniature Contact Cooled Rectifiers, 250V 50mA, 7/6; 250V 60mA, 8/6; 250V 85mA, 9/6; 200mA, 21/-; 300mA, 27/6.**  
**Selenium Rect. 300V 85mA, 7/6.**  
**Coils. Wearite "P" type, 3/- each. Osrom Midget "Q" type, add. dust core, from 4/- each. All ranges.**  
**Teletron D.W.R. L. and Med. T.R.F. with reaction, 3/6.**  
**Ferrite Rod Aerials. M.W., 8/6; M. and L., 12/6.**  
**Osrom Ferrite Rod Aerials. L. and M. for transistor circuits, 10/- each.**  
**Ferrite Rods, 8 x 1in., 2/6.**  
**H.F. Chokes, 2/6. Osrom QCI, 6/6.**  
**T.R.F. Coils, A/HF, 7/- pair; HAX, 3/-; Repanco DR2, 4/-; DRX1, 2/6.**

**Aluminium Chassis, 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in. 4/6; 9 x 7in., 5/8; 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6; 16 x 16 x 3in., 16/6.**  
**Aluminium Panels, 18 s.w.g., 12 x 12in. 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/3, 8 x 6in., 2/-.**

**AUTOCHANGER ACCESSORIES**  
Suitable player cabinets (except 4 H.F.) ... 49/6  
Amplifier player cabinets (except 4 H.F.) ... 63/-  
2-valve amplifier and 6tin. speaker 85/-  
3-valve amplifier and 6tin. speaker 105/-  
Wired and tested ready for use with above.

**CRYSTAL SET BOOKLET, 1/-.**  
**CRYSTAL DIODE G.E.C., 2/-.** GEX34, 4/-, OA91, 3/-.  
**HIGH RESISTANCE PHONES, 4,000 ohms, 15/-; pr.**  
**MIKE TRANSF. 50 : 1, 3/6 ea.; 100 : 1, Potted, 10/6.**  
**SWITCH CLEANER.** Fluid squirt sprout, 4/3 tin.

**JASON FM TUNER COIL SET, 29/-.** H.F. coil, aerial coil, oscillator coil, two i.f. transformers, 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. Complete Jason FMT.1 Kit. Jason chassis with calibrated dial, components and 4 valves, 56.5.0.

**JACKS.** English open circuit, 2/6. Closed circuit, 4/3. Grundig type, 3 pin, 1/3.  
**JACK PLUGS.** English, 3/-; Grundig, 3 pin, 3/6.

**Wire-wound Ext. Speaker Control, 10/-, 3/-.**  
**ALADDIN FORMERS** and cores. 1in., 8d.; 1in., 10d.  
**FORMERS 5937** or 8 and cans TV1 or 2, tin. sq. x 2 1/2in. or tin. sq. x 1 1/2in., 2/- with cores.

**SLOW MOTION DRIVES.** Epicyclic ratio 6-1, 2/3.  
**SOLDAN IRON, 25W, 200V or 230V, 24/-.**  
**MAINS DROPPER, 3 x 1 1/2in.** With adjustable sliders, 0.3A, 1,000 ohms, 4/3; 0.2A, 1,000 ohms, 4/3.

**LINE COILS, 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 1/- per foot; 3-way 1/- per foot.**  
**MIKE TRANS. 50-1, 3/8; 100-1, potted, 10/6**  
**P.V.C. Conn. Wire, 8 colours, single or stranded, 2d. yd. Sleeving, 1.2mm, 2d.; 4mm, 3d.; 6mm, 5d. yd.**

**SPEAKER FRET.** Gold cloth, 17 x 25in., 5/-; 25 x 35in., 10/-; Tygnn, 52in. wide, 10/-; 25in. wide, 5/- ft. Samples, S.A.E.  
**Expanded Metal, Gold, 12 x 12in., 6/-.**

**L.F. Transformers 7/6 pair**  
465 kcs slug tuning miniature can 1 1/2 x 1 1/2 in. High Q and good band width. Data sheet supplied.

**"REGENT" 4 VALVE**



**"96" RANGE VALVES**  
**£6. 6. 0.**  
carr. 4/-

**PRINTED CIRCUIT BATTERY PORTABLE KIT**  
Medium and long wave. Powerful 7 x 4in. high Flux speaker, 1 C.C. Printed Circuit and condensers. Components of finest quality. Clearly identified with assembly instructions. Osrom Ferrite Aerial Coils. Resine covered attaché case cabinet, size 12in. x 5in. x 4in. Batteries used B128 (L5512) and a D86 (L5046), 10/- extra. Instructional 9d. (free with kit). Mains Unit ready made for above 39/6. Mold separately. Details free.

**MONARCH RECORD PLAYER**



**BUILD IT YOURSELF** using 4-SPEED BSR MONARCH AUTOCHANGER  
**READY BUILT 3W. AMPLIFIER, HANDSOME PORTABLE CASE. HIGH FLUX LOUD-SPEAKER. FULL INSTRUCTIONS SUPPLIED.**  
Total Price **£12.10.0**  
Carr. and Ins. 5/-.

**RECORD PLAYER BARGAINS**  
Post 2/- each.  
4 Speed Autochangers:  
BSR, U.A.14 ... .. £7.10.0  
Collaro Autochanger ... .. £7.19.6  
Garrard "Slimline" ... .. £3.17.6  
Garrard RC208 ... .. £9. 8. 0  
Garrard RC209 ... .. £10.10.0  
4 speed Single Players:  
Garrard TA Mk. 11 ... .. £8. 8. 0  
Model 4SP ... .. £6.17.6  
Garrard 4 HF Transcription ... £17.19.6  
Garrard Stereo Heads £2 extra.  
All Sapphire Stylis available from 6/-.

**ARDENTE TRANSISTOR TRANSFORMERS**

Type D3035, 7.3 CT: Push Pull to 3 ohms for OC72, etc., 1 x 1 x 1 in., 9/6.  
Type D3034, 1.75: 1 CT. Push Pull Driver for OC72, etc., 1 x 1 x 1 in., 9/6.  
Type D3038, 11.5:1 Output to 3 ohms for OC72, etc., 1 x 1 x 1 in., 9/6.  
Type D167, 18:2:1 Output to 3 ohms for OC72, etc., 1 x 1 x 1 in., 12/-.  
Type D239, 4.5:1 Driver Transformer, 1 x 1 x 1 in., 10/-.  
Type D240 8.5:1 Driver Transformer, 1 x 1 x 1 in., 10/-.

**ARDENTE TRANSISTOR VOLUME CONTROLS**

Type VC1545, 5K with switch, dia. 0.9in., 8/-  
Type VC1760, 5K with switch, dia. 0.7in., 10/6  
Deal air ear piece xtal or magnetic 7/6.

**WEYRAD**

**COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL**  
**Long and Medium Wave Aerial—RA2W.** On 8in. rod, 7/16in. diameter, 208pF tuning, 12/6.  
**Oscillator Coil P50/1AC.** Medium wave. For 1760F tuning, 5/4.  
**1st and 2nd I.F. Transformers—P50/2CC.** 470 kc/s, 1 1/16in. diameter by 1in. high, 5/7.  
**3rd I.F. Transformers—P50/3CC.** to feed diode detector, 6/-.  
**Driver Transformer—LFDT2.** 1 5/16 x 1 x 1 1/2in., 9/6.  
**Printed Circuit—PCAL.** Size 2 1/2 x 8 1/2in. Ready drilled and printed with component positions, 9/6.  
**7 x 4in., 5 ohm Speaker, 25/-.**  
These components are approved by transistor makers and performance is guaranteed.  
Constructor's Booklet 2/-.

**NEW MULLARD TRANSISTORS**  
T Audio OC1 6/- R.F. OC4 10/6  
OC72 7/6 OC45 9/6  
**Sub-miniature Electrolytics (15V).**  
1uF, 2uF, 4uF, 5uF, 8uF, 25uF, 50uF, 100uF, 2/6. Diodes OA71, OA81, 3/-, GEX 34, 4/-.

**B.B.C. Pocket 2 Transistor, M.W. and L.W. Radio Kit, 22/6.** Phones 7/6 or deal air earpiece, 7/6. Batt. 2/-

**"P.W." POCKET 6 TRANSISTOR KIT MK.II WITH LATEST OSMOR MODIFICATIONS. ALL PARTS, PRINTED CIRCUIT AND CABINET. OSMOR DESIGNED KIT, £8.15.0.**

**COMPONENT SHOP SPECIALISTS**

**337 WHITEHORSE ROAD WEST CROYDON**  
Telephone: THO 1665


P. and P. charge 1/-, over £3 post free. C.O.D. 2/-.

(Export welcome. Send remittance and extra postage).


**NOW**  
**YOU can MASTER ELECTRONICS!**

**BRITAIN'S MOST COMPREHENSIVE PRACTICAL COURSE IN RADIO • ELECTRONICS TELEVISION!**

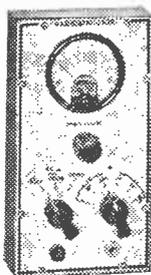
**THESE SPECIAL TRAINING KITS — YOURS TO KEEP**



Multi-Range TEST METER

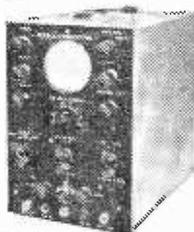

CATHODE RAY OSCILLOSCOPE

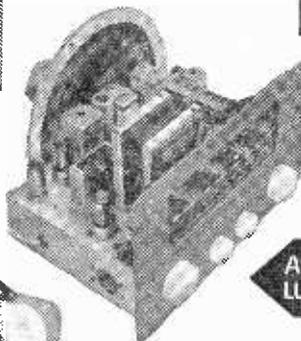

AM and VHF/FM LUXURY RECEIVER



SIGNAL GENERATOR



Complete set of Picture Way books and Experimental Manuals

**LEARN BY BUILDING NOW for your CAREER • HOBBY OWN BUSINESS**

**YOU RECEIVE**

- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.



**FREE BROCHURE NOW**

**RADIOSTRUCTOR**

TO RADIOSTRUCTOR (DEPT. M.82) READING, BERKS.

Name \_\_\_\_\_ **BLOCK**

Address \_\_\_\_\_ **CAPS**

\_\_\_\_\_ **PLEASE**

(We do not employ representatives) 2/62

# Practical Wireless

Vol. XXXVII No. 660 FEBRUARY, 1962.

Editorial and Advertisement  
Offices:

PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,  
Southampton Street, W.C.2.

© George Newnes Ltd., 1962

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.9.0 per annum  
Abroad - - - - £17.6 per annum  
Canada - - - - £15.0 per annum

## Contents

	Page
Editorial ... ..	897
Round the World of Wireless	898
Midget Mains Superhet ...	900
Transistor S.W. Tuner ...	903
Experimenter's Power Pack ...	905
Transmitting Topics ...	911
Improving Broadcast Receivers	914
On Your Wavelength ...	916
All about Cathode Follower Circuits ... ..	919
Short-wave Section ...	922
A Digital Counter ...	924
Faults in Transistor I.F. Stages	928
Trade News ...	933
Short-wave Listeners' Log ...	937
The Citizen ... ..	938
The Condenser ... ..	945
The Bass Reflex Cabinet ...	950
P.W. Minuettes ... ..	953
Faults in VHF/F.M. Receivers	957
Club News ... ..	962
Letters to the Editor ... ..	965

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

## Wired Wireless and Commercial Radio

IT seems only a short time ago that the "wired wireless" was as prominent a topic for conversation as 625-line TV is today, and yet little has been heard of it since. Surely the idea deserves much greater attention and, in fact, the time is fast approaching when a practical application of this form of transmission, in its fullest sense, must be found. Sending a radio signal over a wire is, in fact, what is meant by the term "wired wireless", and one very well-known application of this is the employment of voice-operated carrier systems, over coaxial cables, on the trunk telephone systems. By this means hundreds of simultaneous telephone conversations can be carried on a single cable, without interaction.

A really practical development of this form of radio, would be that in which the normal house wiring systems, which after all, are in effect "networked" and serve the majority of homes in the country, could be used to carry not only normal radio programmes, but commercial or sponsored radio, as well as television on various channels. It would not be a very great step to make these systems of such a type that coin-operated selecting devices could be incorporated to provide not only revenue but various forms of 'exclusive' programmes. Both the telephone system and the lighting services in this country are operated on a national basis, and therefore there would be no difficulty about using the existing wiring. The actual development of a technique which would permit the use of all forms of broadcasting, including what we now know as V.H.F., or F.M., together with television, should not present insurmountable difficulties. It would, of course, limit programmes to each country and perhaps render unnecessary such developments as resulted in the superhet receiver. It would also remove many difficulties, not the least of which would be the fringe area, the need for interference suppressors, and last, but by no means least, the mass of unsightly decorations on our roof tops. (The forthcoming television development on Bands IV and V will lead to greater congestion on our roof tops and it appears highly probable that the Pilkington Committee will recommend some form of "wired wireless" or "carrier wireless" for sound only to enable commercial sound programmes to be inaugurated.)

There may be a limit to the number of transmissions which could be dealt with in this manner, and perhaps the inclusion of television may complicate matters, but surely this is one very good ground for development of radio, and the day must come when radio and television programmes will form part of the domestic service supply systems, taking their place with the electric light, water and other essential services.

Our next issue dated March, will be published on February 7th

# Round the World of Wireless

## POTENTIAL AND CURRENT NEWS

### Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of October, 1961, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London .. .. .	679,407
Home Counties .. .. .	635,389
Midland .. .. .	483,496
North Eastern .. .. .	494,695
North Western .. .. .	427,159
South Western .. .. .	374,467
Wales and Border Counties .. .. .	218,547
<b>Total England and Wales .. .. .</b>	<b>3,283,176</b>
Scotland .. .. .	361,335
Northern Ireland .. .. .	114,503
<b>Grand Total .. .. .</b>	<b>3,769,108</b>

### Swedish Orders Eighty-two Transmitters


THE Royal Board of Swedish Telecommunications has placed another order for sound and television broadcasting transmitters with Marconi's Wireless Telegraph Company Limited.

The new contract calls for the supply of 21 vision transmitters, 21 sound transmitters, 40 frequency-modulated sound transmitters and a considerable quantity of programme input, paralleling, feeder and ancillary equipment.

The transmitters are intended to augment Sweden's already extensive television and VHF frequency modulated sound broadcasting systems by providing first-class reception in the northern area and in what are at the moment fringe areas throughout the country. Deliveries, at the request of the Royal Board of Swedish Telecommunications, are to be spread over the next four years.
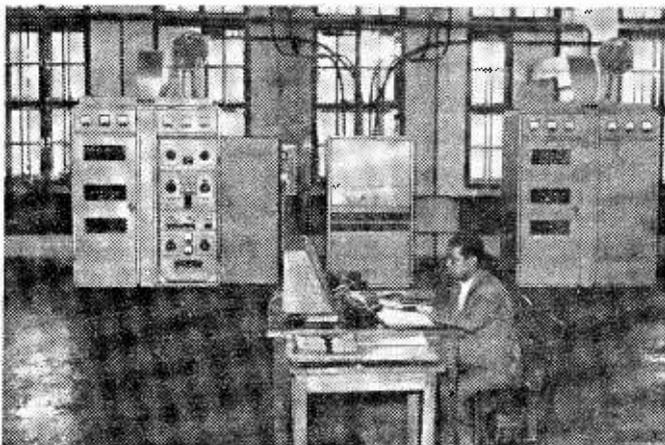
### Transmitter for Satellite Communications Project

A CONTRACT for the supply of a transmitter for use by the GPO in satellite communication experiments, to be carried out next year in co-operation with the American authorities, has been awarded to Standard Telephones and Cables Limited.



These two independent sideband transmitters and aerial exchange were installed in a station outside Ankara, Turkey.

The equipment will be installed in a room built into the 85ft diameter steerable aerial now being erected at a site on Goonhilly Down, in Cornwall. The transmitter will operate in the 2000Mc/s communication band, and will deliver a frequency-modulated output of 10kW.

Additional items to be supplied by the company include power equipment for the transmitter and a water-to-air heat exchanger unit.

The present programme calls for the whole transmitter to be installed on the site and fully operational by April, 1962. An active repeater communication satellite to be launched by the U.S.A. authorities will enable tests to be conducted on television transmission and two-way speech communication between Cornwall and the American ground station at Rumford, Maine.

### Communications Transmitters in Turkey

AS part of its programme of technical assistance to member countries of the Central Treaty Organisation, the British Government have presented radio communications equipment to Turkey. Two independent sideband transmitters, aerial exchange, and matching transformers were among the pieces of equipment presented, and these were made by Marconi's.

The installation is at a transmitting station outside Ankara, Turkey.

### Royal Navy Order

THE Admiralty has awarded a contract for the supply of a number of 500W medium-frequency/high-frequency independent sideband communication transmitters to Marconi's Wireless Telegraph Company Ltd., together with high-stability master oscillators and remotely controlled aerial matching units.

### Weather Radar Orders

THE new duplicate version of the Type E190 airborne weather radar, which is a product of Ekco Electronics, has been ordered by Short Brothers and Harland Ltd. for installation in ten of their new Belfast air freighters. This equipment employs a dual transmitter/receiver and indicator system, in keeping with the current practice of duplicating essential services which are the subject of mandatory requirements. Fully "fail-safe" conditions are thus provided, either transmitter/receiver operating with either indicator unit.

Ekco airborne weather radar is also to be installed in the de Havilland Comet 4 airliner recently ordered by King Saud of Saudi Arabia.

### VHF Sound Broadcasting Station for Northern Ireland

THE BBC's new VHF sound broadcasting station at Londonderry which is on the same site as the BBC's television station at Sherriffs Mountain was brought into service on 23rd October. This is one of the twenty-one new VHF satellite stations so far approved for extending the coverage of the VHF sound service to over 99% of the population of the United Kingdom.

Londonderry radiates the Northern Ireland Home Service on 92.7Mc/s, the Light Programme on 88.3Mc/s, and the Third Programme together with Network Three on 90.55Mc/s. The signals are horizontally polarized, which means that receiving aerials should be horizontal. The programmes are fed by Post Office cable from a special receiving site at Glenderowen where they are received by radio from the BBC's VHF station at Divis.

The new station brings the BBC's VHF sound broadcasting service within reach of some 120,000 additional people in the counties of Londonderry and Tyrone.

### 4th Jamboree-on-the-Air

FROM 00.01 hours GMT on Saturday, 21st October until 23.59 hours GMT on Sunday, October 22nd radio hams from forty countries all over the world took part in the Boy Scouts' 4th Jamboree-on-the-Air.

In this country alone there were over forty stations operating. One of these was in the recently opened Baden-Powell House in South Kensington.

This year Scout stations were on the air in Australia, Canada and the Philippines. In previous years contact has been made with Scouts in America, Canada, Holland, Sweden, Finland, Germany, Bermuda, France, Norway and New Zealand.

### Changes in Times of International Time Signal

FOR over one hundred years, the Royal Greenwich Observatory has been responsible for providing exact time signals for a wide variety of users both at home and abroad.

In recent years this service has become increasingly important in various fields of scientific research where extreme accuracy is essential.

In order to provide the various users with more frequent opportunities for checking the time, on 1st December, the daily transmissions from Rugby were increased from two to four.

This means that the transmissions on the low frequency of 16kc/s until recently radiated at 10 a.m. and 6 p.m. are now superseded by signals at 3 a.m., 9 a.m., 3 p.m. and 9 p.m. There is, however, no change in the form of the signals.

To ensure a world-wide coverage, the 10 a.m. and 6 p.m. broadcasts have also been transmitted on short wave. This service is continuing, but the times have been changed to 9 a.m. and 9 p.m.

The transmissions from Rugby are proving to be indispensable to users all over the world. Such persons as marine surveyors and scientists engaged in tracking artificial satellites will undoubtedly find the new and more frequent transmissions of great value.


### Ten High Power Short Wave Transmitters

THE British Broadcasting Corporation has placed an order with Marconi's Wireless Telegraph Company Ltd. for the


supply and installation of ten high-power (250kW) short-wave sound broadcasting transmitters of a new type which, when they come into service, should very materially improve overseas listeners' reception.

Six of these transmitters will be installed at the "Voice of America" relay station at Wooferton. Two more will go into service at the BBC station at Rampisham and the remaining two at Daventry.

The transmitters are specially designed to combat the ever increasing amount of interference experienced by overseas listeners on the short waves. This is achieved by employing a method of modulation which cuts through the interference to bring the signal to the listener. Intensive experiments have shown that the use of this trapezoidal modulation, as it is called, gives an intelligibility at the receiving end which could only otherwise be brought about by more than doubling the transmitter power—that is, in this instance, from 250kW to 550kW. The overall efficiency of the new type of transmitter is approximately double that of the older equipments supplied to Rampisham and Daventry.

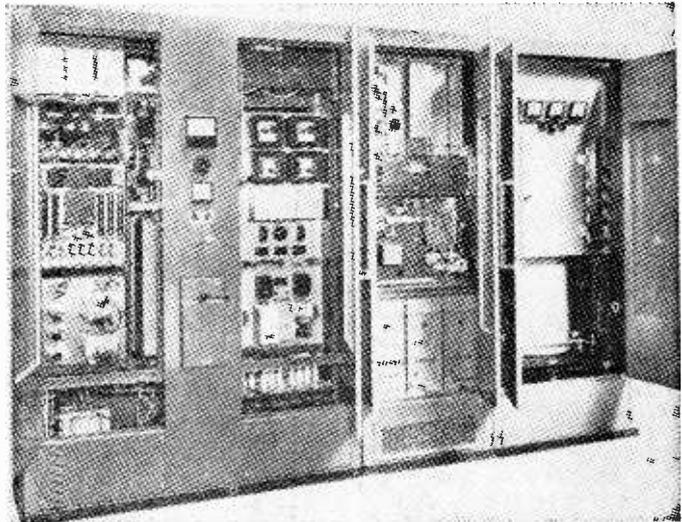

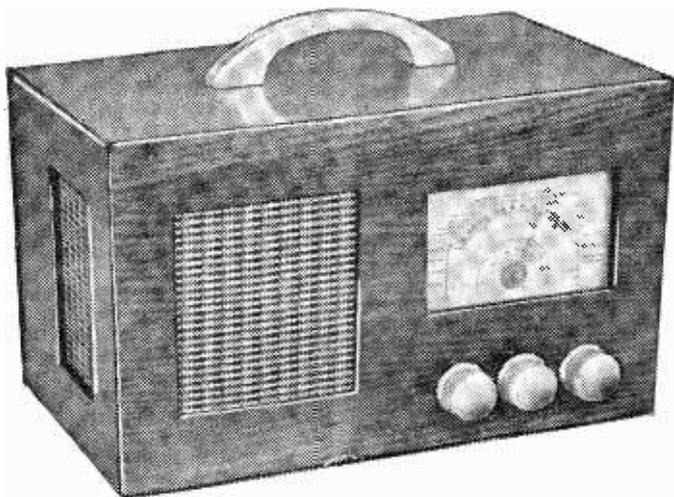A transmitter of the type to be supplied by STC to the GPO for use in satellite communication experiments. On the left is the power control cubicle (double width), with the drive unit in the centre and the klystron power amplifier cubicle on the right. This transmitter operates in the 2000Mc/s communication band, and will deliver a frequency-modulated output of 10kW.



## A HIGHLY SENSITIVE DOMESTIC RECEIVER

By V. E. Holley

**T**HIS receiver will perform satisfactorily in most parts of the country. Though small in size, its overall sensitivity is above average and unless reception conditions are very unfavourable it will work quite well on two or three feet of wire as a "throw-out" aerial. The valves, which at first sight may seem an odd assortment, have been selected (as will be explained) for low cost and high performance.

### Aerial Circuit

Referring to Fig. 1, the signal from the aerial is passed first through the I.F. rejector, L1, C1, which is an iron-cored inductor tuned to the intermediate frequency. It will be found useful in coastal areas where morse transmissions around 500kc/s are apt to find their way into the I.F. amplifier; in other areas it will probably not be required and can be omitted. The filtered signal passes via the switch S1 to the appropriate aerial coil and thence via S2 to the grid of the first valve.

### Output Stage

In order to economise in the bulk, weight and cost of the power supply, a Mazda octal valve SP61, is used in the output stage. This valve can be obtained very cheaply indeed and although intended for R.F. amplification it makes a very satisfactory small power valve. It has a high slope and an output of one watt can be obtained in return for a modest signal at the grid. Grid and cathode resistors are 1M and 150Ω respectively.

If the greatest gain is required in the output stage the resistor R16 can be by-passed by an electrolytic capacitor of 100μF and this will increase the sound output. The output transformer in the anode circuit should have a ratio of about 70:1 for a 3Ω speaker and can be of the type usually described as "small pentode."

### Negative Feedback

The SP61 is a very efficient amplifier of radio frequencies and it is necessary to arrange that any such frequencies reaching it shall be excluded from the output. Accordingly, frequency selective negative voltage feedback is taken from the anode via the capacitor C21, to the cathode circuit of V3.

### Second Negative Feedback

If maximum overall gain is not required, a second negative feedback loop, effective at all frequencies, can be formed by connecting a resistor of from 200 to 1,000Ω between points X and Y in Fig. 1.

### Power Supply

The total H.T. current in the absence of a signal is 35mA at about 220V, while the valve

midget  
mains

# SUPERHET

heaters and dial lamp need approximately 0.15A at 6.3V. This is supplied by a miniature mains transformer, the high voltage half-wave secondary of which feeds a metal rectifier, DRM1. A contact cooled rectifier is equally suitable. The rectified current is taken first through a fuse, which is in fact a 6.3V, 0.15A bulb; though not essential. This is a useful safeguard against the consequences of short circuits, catastrophic failure of capacitors, etc. Smoothing is provided by the capacitors C22, C23 and C24, and the resistors R17 and R18. This double stage arrangement gives good smoothing with negligible voltage drop, an important point if as in the prototype, the transformer voltage is only 220. The values of these resistors must be

adjusted according to the output of the transformer-rectifier combination so that the H.T. line voltage in the receiver is  $220 \pm 10$  in the absence of a signal. Miniature transformers do not usually have tapped primaries so the mains supply voltage must also be taken into account.

**Components**

The tuning scale and the gang condenser must be selected for compatibility if the transmissions are to be received at the points indicated on the scale. The coils may be any standard dust-cored components covering the long and medium wavebands and the trimming and padding capacitors should be of the values recommended by the

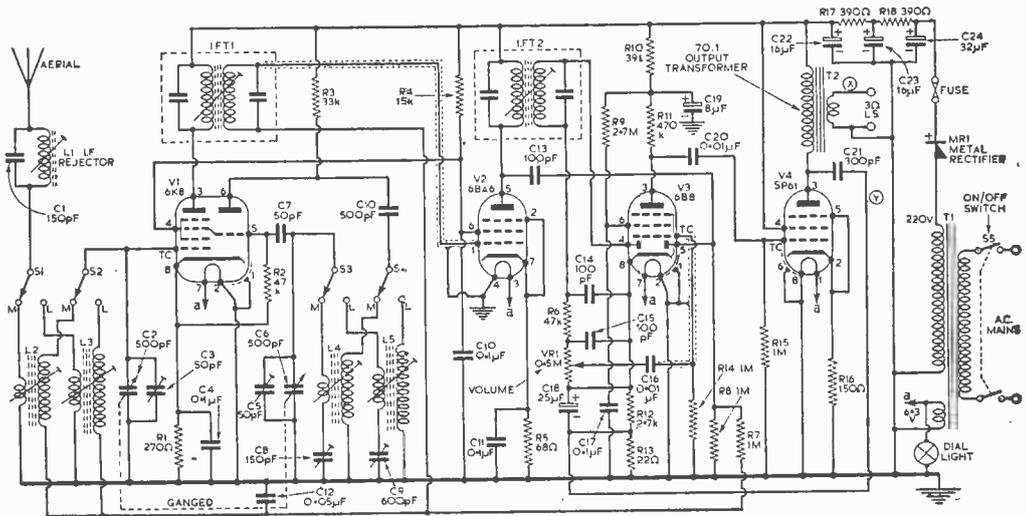


Fig. 1—The circuit of the receiver.

**LIST OF COMPONENTS**

Resistors ( $\frac{1}{2}$ W unless otherwise stated)

- R1 270  $\Omega$
- R2 47k
- R3 33k
- R4 15k (1W)
- R5 68  $\Omega$
- R6 47k
- R7 1M
- R8 1M
- R9 2.7M
- VR1 0.5M with switch
- R10 39k
- R11 470k
- R12 2.7k
- R13 22  $\Omega$
- R14 1M
- R15 1M
- R16 150  $\Omega$
- R17 390  $\Omega$  1W
- R18 390  $\Omega$  1W

- C18 25  $\mu$ F electrolytic, 25WV
- C19 8  $\mu$ F electrolytic
- C20 0.01  $\mu$ F
- C21 300pF
- C22 16  $\mu$ F electrolytic
- C23 16  $\mu$ F electrolytic
- C24 32  $\mu$ F electrolytic

**Valves**

- V1 6K8, octal base
- V2 6BA6, B7G base
- V3 6B8, Octal base
- V4 SP61, Mazda octal base

**Transformers**

- Mains—220V, 40mA,  $\frac{1}{2}$ -wave; 6.3V, 2A
- Output—Pentode type, 70 : 1
- I.F.—1 pair, 465kc/s
- Dial light 6.3V, 0.15A
- Fuse 6.3V, 0.15A bulb
- Rectifier 250V, 50mA, half-wave, DRM1 or contact-cooled
- Coils standard iron-cored, aerial and oscillator for long and medium-wave bands
- Switch 4-pole, 2-way

Capacitors (350VW unless otherwise stated)

- C1 150pF
- C2, C6 2-gang, 500pF with  $\frac{1}{2}$ in. drive drum
- C3 50pF trimmer
- C4 0.1  $\mu$ F
- C5 50pF trimmer
- C7 50pF
- C8 150pF padder
- C9 600pF padder
- C10 0.1  $\mu$ F
- C11 0.1  $\mu$ F
- C12 0.05  $\mu$ F
- C13 100pF
- C14 100pF
- C15 100pF
- C16 0.01  $\mu$ F
- C17 0.1  $\mu$ F


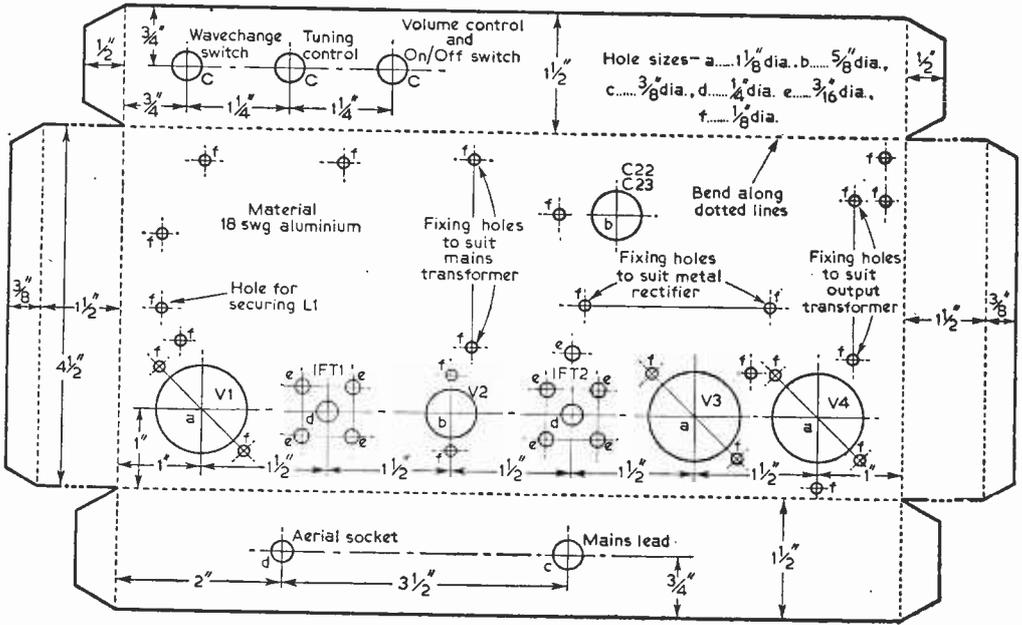


Fig. 2—The drilling details of the aluminium chassis.

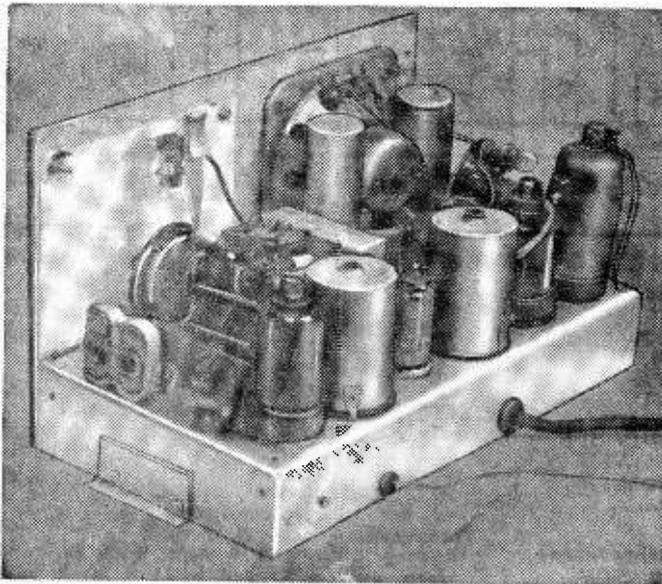

The completed receiver without the cabinet.

makers. The values given in Fig. 1 are fairly typical and may be used in the absence of more authoritative information. Most manufacturers feature a suitable I.F. rejector coil in their range, either with or without the parallel fixed capacitor, C1.

**Tuning Drive**

The tuning drive can be made from an old volume control. Remove the body and fit to the rear of the spindle a brass coupler in which a groove has been cut for the drive cord. Holes must, of course, be cut in the chassis for the cord to pass up to the drive drum and down again.

The resistors may be 1/2W except for R4, R17 and R18, which should be of 1W rating and, because the H.T. comes on through the metal rectifier before the valves are warmed up and ready to receive it, all the capacitors should be 350VW except for C18, for which 25VW working will be adequate.

**Mains Transformer**

The mains transformer must be a miniature type and it is convenient though not essential that the tuning condenser be semi-miniature. All other components can be standard. The trimmers C2 and C16 should be fitted to the top of the gang condenser, which also carries a bracket for the dial light.

**Construction**

The receiver is constructed on a chassis of 18s.w.g. aluminium sheet, 9 1/2in. x 4 1/2in. x 1 1/2in. (Fig. 2).

(To be continued)

16m  
TO  
175m



# TRANSISTOR S.W. TUNER

A UNIT DESIGNED TO BE USED WITH A SEPARATE AMPLIFIER

By  
F. Neville Hart

Now that short-wave transistors have become about as cheap as valves and there are coils on the market for frequencies as high as the VHF bands, the simplicity of transistor circuits opens up an attractive field for the experimenter.

The set described here is a portable tuner which can be plugged into any amplifier, such as a tape recorder, or radio provided with 'gram' input terminals. It has a 3ft 6in. telescopic chromium plated aerial fixed in a 3-ply, leather cloth-covered cabinet, which was built to house the set. The construction of this is not described as readers may have their own ideas on carpentry.

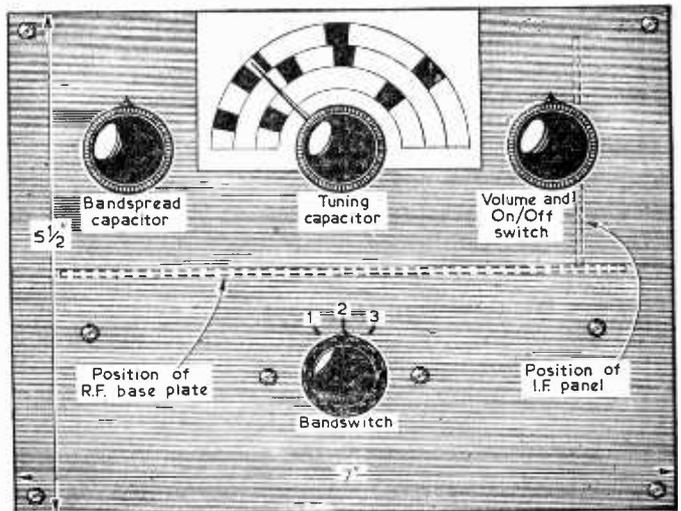


Fig. 1—The front panel layout.

COMPONENTS LIST

Resistors (all 1/2W)

- |                            |          |
|----------------------------|----------|
| R1 15k                     | R9 8.2k  |
| R2 2.2k                    | R10 1.2k |
| R3 1k                      | R11 680Ω |
| R4 2.2k or 3.3k (see text) | R12 22k  |
| R5 10k                     | R13 4.7k |
| R6 2.2k                    | R14 3.9k |
| R7 1k                      | R15 1k   |
| R8 68k                     |          |

Capacitors:

- |                    |                         |
|--------------------|-------------------------|
| C1 0.01 μF         | C11 56pF                |
| C2 0.001 μF        | C12 0.1 μF              |
| C3 0.01 μF         | C14 0.1 μF 12VW         |
| C4 0.003 μF        | C15 18pF                |
| C6 0.01 μF         | C16 0.1 μF 12VW         |
| C7 750pF           | C17 25 μF or 50 μF 12VW |
| C8 8 μF 12VW elec. | C18 8 μF 12VW elec.     |
| C10 0.25 μF 150VW  | C19 0.25 μF 150VW       |
- (C5, 9 and 13 are inside the I.F. cans)

- VR1 5k potentiometer  
 Tr1, 2 OC170  
 Tr3 OC45  
 Tr4 OC45

- D1 WG4B, OA81 or equivalent  
 VC1 Jackson "00" three gang 208-176-208pF  
 VC2 Three gang bandpass 30pF (or 2 gang, see text)

TC1-8 30pF beehive trimmers

Tuning coils (Repanco)

Range 1—

- Aerial type XTA31 blue mauve spots  
 R.F. type XTF32 blue black spots  
 Oscillator type XOT33 blue brown spots

Range 2—

- Aerial type XSA34 red yellow spots  
 R.F. type XSF35 blue yellow spots  
 Oscillator type XOS36 blue red spots

Range 3—

- Aerial type XSA37 blue green spots  
 R.F. type XSF38 blue white spots  
 (Oscillator uses range 2)

I.F. transformers—2 XT26 and one XT27(465kc/s)  
 2 blue spots, 2 green spots

A battery plug for 7.5V battery

Extending Aerial; 9-pole 3-way wafer switch,  
 2in. in diameter (H L Smith Ltd, 287 Edgware  
 Road, W2)

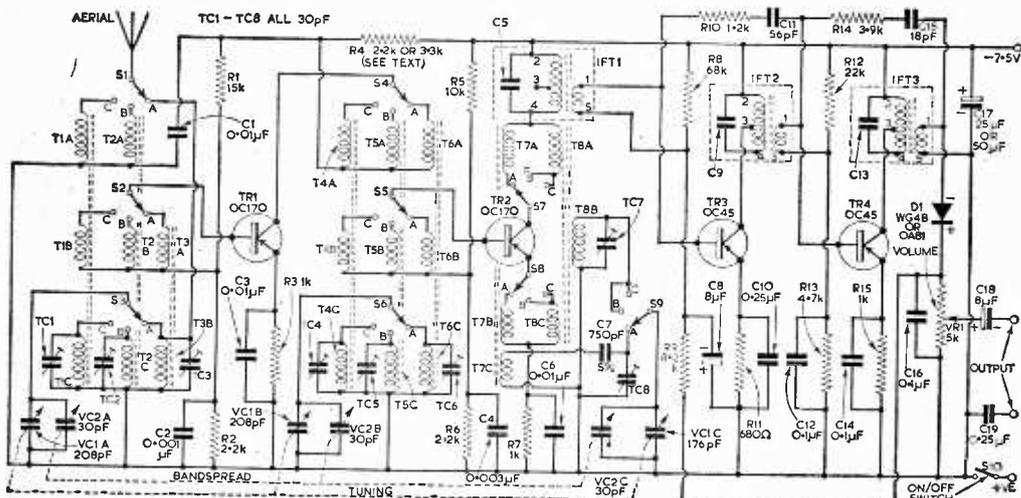


Fig. 2—The complete circuit diagram. Note that if instability occurs in the R.F. Stage, C4 should be reduced in value from 0.003 μF to 0.001 μF.

Frequency Coverage

The coverage is approximately from 16m to 175m, in three ranges, using a nine-pole three-way switch with three wafers. A number of these are obtainable as "surplus," but switch makers will make them up for about 15s. each.

Any I.F. coils for use with transistors can be employed, but since the short-wave tuning coils are made by Repanco, the use of their I.F. coils is described here. Although an R.F. stage rather complicates adjustment and trimming, it assists the rejection of second channel interference and gives better selectivity and volume.

The set compares favourably with the author's battery superhet with R.F. and two I.F. valves. Volume depends upon the amplifier following, but the output part of a transistor radio using driver and push-pull OC72's gives sufficient volume in the author's caravan, where, indeed, most of the construction was carried out.

Aerial

Although its own aerial is normally used, pick-up can be improved by using a longer aerial.

(To be continued)

# Experimenter's

# POWER-PACK

## THE FINAL DESIGN AND CIRCUIT

(Continued from page 824  
of the January issue)

By M. L. Michaelis

**T**HE power unit is extremely versatile, giving outputs of almost all types normally required in the experimenter's workshop. Whilst the unit is definitely advanced in nature, and thus not advisable for the beginner, it is felt that it will meet a long-felt requirement for the more experienced constructor, who, once he has built it, will find virtually all of his power supply problems solved in one.

The outputs provided are the following:—

(a) *A stabilised H.T. output, continuously variable from 120V to 350V, at a nominal maximum current of 100mA.*

This output can thus be used for virtually any H.T. requirements, from battery-valve circuits requiring 120V H.T. at the one extreme, to mains-valve circuits requiring the higher voltages up to 350. Stabilisation is such that the remaining effective internal impedance is about 50Ω, so that in most cases several pieces of apparatus can be fed without mutual interference.

(b) *An unstabilised H.T. output of about 300V, fully independent and capable of supplying some 50mA.* This is intended for operating various pieces of apparatus, such as a valve voltmeter or a test oscillator, etc., at the same time as the experimental circuits being worked on are being fed from the main stabilised H.T. supply.

(c) *Two neon-stabilised output voltages, one at plus 90V and the other at minus 100V, relative to earth (chassis).* These are capable of being loaded up to about 1mA each. Their purpose is for providing facilities for any bias-bleeder chains that may be required in advanced experimental circuits, and to this end they may be used together or independently.



The author's unit

(d) *A.C. heater outputs at 4V, 6.3V, 10V and 12.6V.* All are rated at 4A maximum continuous loads. By simultaneous loading at various of these voltages, the total current must not exceed 4A.

(e) *Low-voltage D.C. output at a maximum of 18V and a maximum of 2A.* This output is intended for a variety of uses. It is not stabilised, but it is fully smoothed, and is variable by means of a variable wire-wound resistance. It can be used for the following purposes:—

- heating battery valves of 1.4V or 2V type;
- heating mains valves with D.C. in circuits requiring this;
- charging accumulators (anything from a single 2V cell to a 12V car-battery);
- feeding transistorised apparatus. On account of this last envisaged use, the positive pole of the supply is earthed, and not the negative pole, as is otherwise more usual. This does not in any way impair the other uses named.

(f) An output at 110V A.C. up to about 100W. for feeding any 110V apparatus that may come in for attention. (It is assumed that the power unit is to be built for 230/250V mains, but if readers' local mains have other voltages, then it is merely necessary to purchase transformers with the appropriate primary windings.)

A comprehensive system of indicator pilot-lamps, fuses and other protective measures are incorporated, and a definite orderly plan has been devised and followed in the allocation of switch-functions. These features will all become apparent in the course of the circuit description below.

### Checking Output

A multi-purpose monitor system is built-in, for metering any of five important voltage outputs and any of five important current outputs. Two moving-coil meters are used, with suitable switching, shunts and multipliers. One meter functions as voltmeter and the other as current meter. Any one voltage and any one current may be displayed at any one time. The meter may be switched on to voltages and currents on load, and this process does not disturb the functioning of the power unit. Thus if all five outputs are simultaneously loaded, the meters may be switched successively to read off all circuits in turn, without disturbing them.

All outputs are fully independent. Thus, for example, the low-volts D.C. output may be connected to charge accumulators, and at any time the other sections of the power supply used for feeding electronic circuits. After checking for correct charging current, the meters may be switched over to monitor the H.T. and other circuits being used. At any time the meters may be switched momentarily back to the accumulators on charge, to check that charging is still correct. This is only one example of possible simultaneous uses of the power supply, so that in actual fact the power supply serves the purpose of several smaller power units. This represents a considerable saving in space and expense, compared to the actual construction of the equivalent range of separate power units.

### Heat

Attention has been given to the question of adequate heat dissipation. This has been successfully achieved whilst at the same time satisfying the apparently contradictory requirements of maintaining as compact a form as possible. In the author's unit the front panel is approximately one foot square, and the cabinet is 6in. deep. To make the best possible use of the space available, the usual chassis construction has been rejected in

### COMPONENTS LIST

#### Resistors ( $\pm 20\%$ unless otherwise stated)

R1	22k 10W	R16	10k 2W $\pm 5\%$	
R2	82k 10W	R17	33k 2W $\pm 5\%$	
R3	820k 2W	R18	82k 2W	
R4	820k 2W	R19	1.8k 6W	
R5	6.8k 2W	R20	5 $\Omega$ w.w. $\pm 1\%$	
R6	1M 2W	R21	5 $\Omega$ w.w. $\pm 1\%$	
R7	18k 2W	R22	} 100k 2W $\pm 5\%$	
R8	18k 2W	R23		
R9	185 $\Omega$ $\pm 5\%$	R24		
	w.w., 5W	R25		
R10	100k 1W	R26	5k 2W $\pm 5\%$	
R11	100k 1W	R27	Shunt	
R12	220k 1W	R28	Shunt	
R13	1M 1W	R29	150 $\Omega$ 1W	
R14	82k 2W	R30	150 $\Omega$ 1W	
R15	150k 1W	R31	Shunt	

(R20 to R31 are in the meter circuits to be described)

#### Condensers

C1	} 8 $\mu$ F metallised paper, 500/750 VW	
C2		
Alternatively, C1 and C2 can be 8 $\mu$ F 500VW electrolytics (as on the circuit diagram)		
C3	8 $\mu$ F 450VW electrolytic	
C4	8 $\mu$ F 450VW electrolytic	
C5	} 0.1 $\mu$ F 500VW paper	
C6		
C7	0.02 $\mu$ F 1000VW high insulation	
C8	0.1 $\mu$ F 500VW paper	
C9	8 $\mu$ F metallised paper 350/500 VW	
C10	0.1 $\mu$ F 500VW paper	
C11	} 25 $\mu$ F 350VW electrolytic	
C12		
C13		
C14		
Variable Resistors		
VR1	100k 1W lin.	
VR2	10 $\Omega$ w.w. lin., 25W	
VR3	} 1k w.w. lin., 5W	

#### Valves

V1	EL34
V2	ECC83
V3	90C1 neon (90V)
V4	90C1 neon (90V)
V5	108C1 neon (100-108V)
V6	90C1 neon (90V)
D1	Four E250C130 selenium elements
D2	Selenium E250C50
D3	Selenium B300C75
D4	Copper oxide E12C2000


} see text

#### Switches

S1	Single pole toggle
S2	Double pole toggle
S3	Double pole toggle
S4	2-pole/2-pole on/on toggle
S5	Single-pole double-throw toggle
S6	Single-pole toggle
RLY1	Three-phase A.C. relay 2A, 10-12V coil, 400V contacts
MS1	} Meter wafer switches 2-pole, 6-way, break-before-make
MS2	
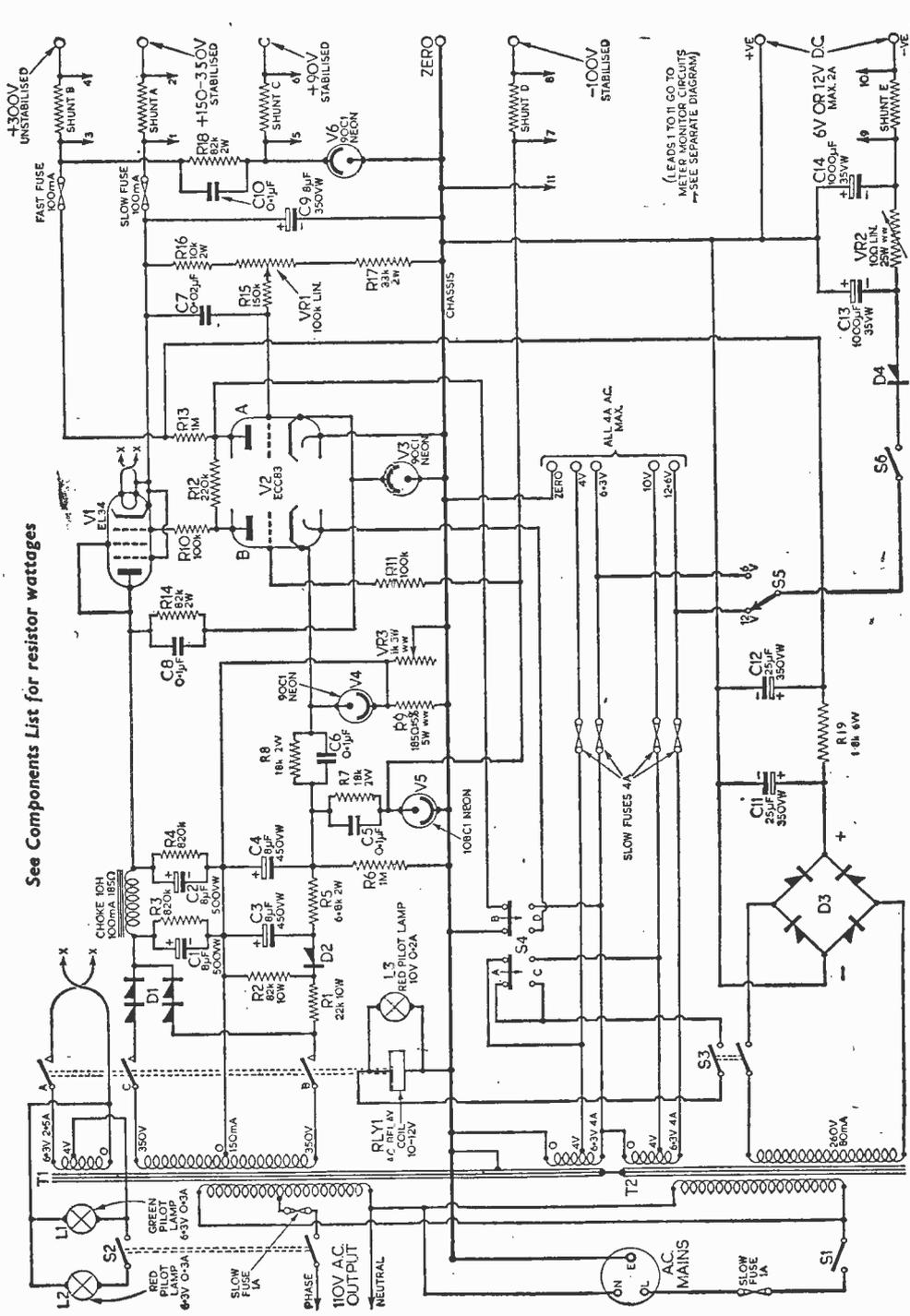
#### Sundries

Two mains transformers as specified in text  
 Eight panel-fuses, single hole, insulated  
 Three pilot lamps: two red, one green  
 Two bulbs 6.2V 0.3A  
 One bulb 10V 0.2A  
 Fourteen insulated wanderplug-sockets  
 Two moving coil meters as specified  
 One octal, one noval, four B7G valveholders (ceramic)  
 Four pointer knobs  
 One yard tagstrip  
 Bolts, wire, sleeving, etc.  
 Sheet aluminium, wood, screws, etc.  
 Mains lead (3 core) and 3-pin plug



See Components List for resistor wattages

(LEADS TO TL GO TO MAINS AND NEON LAMPS SEE SEPARATE DIAGRAM)

Fig. 6—The complete circuit diagram of the power-pack. Notes:—The mains transformers used should have primary windings to suit the local mains voltage, or, alternatively, 10-0-200-220-240V primary windings (the latter is to be preferred). The primary winding of T1 will in any case require a tap at 110V if a 110V A.C. output is to be provided from the power-pack. The rectifier symbols follow convention and the 'bar' of the symbol represents the end of the rectifier which becomes positive when A.C. is applied.

favour of a "spatial-construction". This latter form of construction is more difficult than conventional chassis construction, but has the advantage of complete utilisation of the available cabinet space, thereby reducing the size of a unit by at least a factor of two. However, the layout of the whole circuit is in all respects fully non-critical, so that those constructors who can tolerate a larger final size of unit may use the normal chassis form of construction, with any convenient layout. Adequate insulation is more important than any particular layout.

then to make a small chassis containing all the valves and associated circuitry, and mount this on the right-hand side panel of the cabinet, again taking all points to be connected elsewhere to a suitably positioned tagstrip. The fourth stage was then to mount the few remaining components (in this case the A.C. relay, the smoothing choke and the output condenser) on the left-hand side panel. Nothing is mounted on the top-piece or the back of the future cabinet.

#### Inter-wiring

Four separate sub-units have now resulted, on four pieces of the future cabinet. These are now laid on the workbench in such a position relative to each other that (a) all parts of all of them can be reached comfortably for repairs and alterations, and (b) they are nevertheless as close as possible to their proper relative positions in the final assembled cabinet. The units are now inter-connected by neat bunches of insulated wires, of the correct lengths, running between the tagstrips of the various units. After completion of this work, the power unit is electrically complete, and may be switched on and tested. If all is found satisfactory, the four sub-units and the top-piece of the cabinet are screwed together with wood-screws, to form the cabinet. All cable-bunches are neatly tucked away in positions where they cannot chafe or otherwise be damaged. After cutting suitable ventilation holes in the back panel, this is screwed on too. It remains to label all items externally on the front panel and to paint the cabinet as desired, and the power unit is then ready for service.

#### Interlocking

The geometrical arrangement of the components on the four sub-units is such that complete spatial interlocking (without, however, touching and shorting of components) is achieved within the cabinet after assembly. The arrangement used by the author satisfies some further points, too:—


(a) All valves are immediately accessible for quick replacement if ever required. Thus the valve chassis is at the rear, reached as soon as the back is removed, without further dismantling.

(b) All components generating much heat, principally the transformers, choke and valve chassis, are mounted at the rear, so that they induce a strong convection current through the generous ventilation holes in the rear panel, and do not heat up the rest of the circuitry unnecessarily.

(c) The build-up otherwise avoids horizontal layering, and stresses vertical channelling, to give full freedom to convection cooling; the author's prototype has been on non-stop operation for periods of up to one week without the slightest indication of undue heating.

The detailed building plans to be given will bear out these points, but it must be borne in mind that *considerable* modifications may be necessary according to the actual shapes and sizes of components individual constructors may purchase or have available. For this reason it was stated above that this type of construction is more difficult than a conventional chassis. It is absolutely essential that the constructor should collect all essential components together, and then sit down and very carefully envisage the complete final construction.

(To be continued)

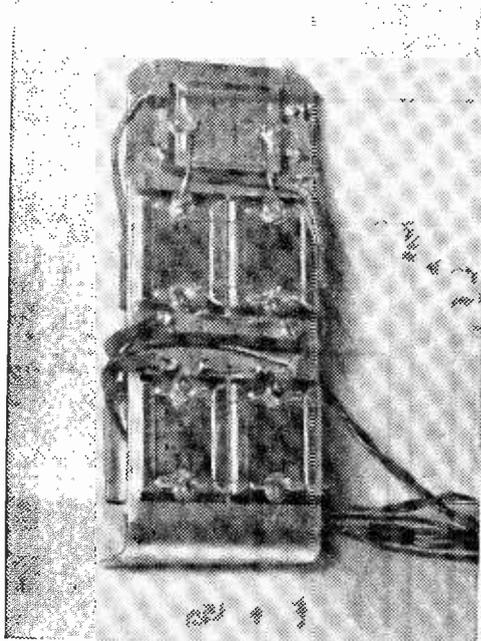

Front view of the rectifier sub-chassis.

#### Procedure

The "spatial-construction" consists of building the unit in the form of several sub-units. A wooden cabinet is used, with two sides, top, bottom, front panel and back. Any one of these six pieces of wood is independently removable, by means of loosening the appropriate screws. Construction is started on the basepiece of the cabinet, on which all larger components are mounted and wired up (transformers, etc.). In the case of the power unit here described, the next step was to make a small bracket-chassis on which the metal rectifiers and associated circuitry were mounted. This rectifier-unit was then also mounted on the basepiece. When all the wiring of the basepiece was complete, all points to be connected to other components not on the basepiece were wired to suitably positioned tagstrips. The next stage was to make the front panel, on which all outlets, switches, fuses, lamps, controls, etc., were mounted and wired up. A sub-unit containing the low-volt D.C. rectifiers and smoothing was also mounted on this. All points to be connected elsewhere were again taken to tagstrips. The third stage was

Examine it  
**FREE**  
on 7 DAYS  
APPROVAL

# RADIO, TELEVISION & ELECTRICAL REPAIRS



## AMAZING 'KNOW HOW' BOOK *Saves You Pounds*

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install lighting points, or repair any domestic appliance, from a bell or an iron to a vacuum cleaner or washing machine. Explains basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults, carry out maintenance and repairs by the most modern methods. Special section on frequency modulated receivers. See this great volume NOW on 7 days' FREE TRIAL. Yours (if kept) for 21/- (Standard Edition) or 23/- (De Luxe, leathercloth). Or on Easy Terms: 5/- down, and 3 monthly payments (total credit prices: Stnd. 22/-; De Luxe 24/-).

**ALL THIS—AND MORE  
IN ONE GREAT  
VOLUME!**

*Comprehensive Contents Include*


Current, Voltage and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-Amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging. Testing and Repairs, etc.

### ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN!

#### Getting the best from RADIO AND TV SETS

Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set.
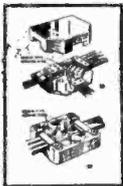
#### All you need know about DOMESTIC WIRING



Learn from these helpful pages how to carry out all kinds of installations and extensions—with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.

#### BASIC RADIO CIRCUITS

All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set: gives circuits for 1-valve receiver, 3-valve receiver, battery TRF receiver 4-valve superhet, Universal sets, etc.


See how to maintain

**Vacuum Cleaners  
and Floor Polishers,  
Refrigerators, Cookers  
and Boiling Plates,  
Washing Machines, etc.**

Do your own

**BATTERY CHARGING**

Here are clear, complete instructions.

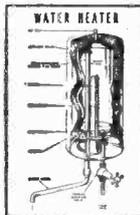

#### FIRES & SPACE HEATERS


Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

#### WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!
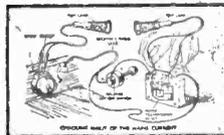
#### TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the causes of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loud-speakers and how to deal with any faults that may develop.



### DO THIS NOW!

Fill in form and post in 2d. stamped, unsealed envelope. Book comes to you on FREE APPROVAL; if satisfied you send remittance, otherwise return book in 8 days. Approval offer applies in U.K. only, closes Feb. 28. Eire customers please remit full cash with order—refunded in full if not completely satisfied.

## POST FORM TODAY!

To: Dept. E.B.35, Odhams Press Ltd., Basted, Sevenoaks, Kent.

Without obligation to purchase, please send me "Radio, Television and Electrical Repairs" in Edition indicated. Within 8 days I will either return book in good condition, postage paid, OR remit full cash price. Alternatively, I will send correct down payment as detailed in advertisement. Cross out Edition NOT wanted: STANDARD/DE LUXE. Delete Words NOT applicable. I wish to pay CASH/BY TERMS. I am (a) houseowner (b) tenant in house or flat (c) temporary resident (d) single (e) married (f) over 21 (g) under 21.

Signature \_\_\_\_\_

(If under 21, signature of parent or guardian)

BLOCK LETTERS BELOW

NAME \_\_\_\_\_

Full Postal ADDRESS \_\_\_\_\_

E.B.35/Feb. 1962



This splendid AVO Instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment. Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust, clearly marked rotary switch of the characteristic Avo Meter type. Measurements of A.C. and D.C. Voltage, D.C. Current and Resistance are made by means of only two connection sockets.

Designed and Manufactured by

**AVO LTD**



**AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON - S.W.1**  
A member of the Metal Industries Group of Companies

Telephone: VICTORIA 3404 (12 lines)

MM2

# Just Right for your pocket!

## THE MULTIMINOR

### 19 Ranges

D.C. Voltage: 0-1,000V in 7 ranges

A.C. Voltage: 0-1,000V in 5 ranges

D.C. Current: 0-1A in 5 ranges

Resistance: 0-20,000 Ω, 0-2M Ω.

Pocket Size: 5½ x 3½ x 1½ inches.

Weight: 1 lb. approx.

List Price **£9 : 10s.**

Complete with Test Leads and Clips.  
Leather Case if required 39/-.

**Sensitivity:**  
10,000 ohms per volt on D.C. voltage ranges.  
1,000 ohms per volt on A.C. voltage ranges.

**Accuracy:**  
On D.C. 3% of full scale value.

On A.C. 4% of full scale value.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.



### The "PIRETTE"

**TWO TRANSISTOR SET  
DESIGNED FOR  
PERSONAL LISTENING**

An amazing little set, with built in ferrite rod aerial bringing in medium wave at wonderful volume.

Sturdy case. Size only 1½ x 3 x 4in. Fits into palm of the hand. Drilled chassis colour coded for easy assembly. Two top grade transistors plus diode. Supplied with earpiece.

Total Building Costs **50/-** P. & P. 2/-.

**The "BIJOU"**  
EASY TO BUILD TWO-STAGE  
TRANSISTOR SET

"The set that looks like a Radio set."

Attractive case. Mini .0005 Tuner. High Q Litz coil. Works for months off No. 8 battery. Simple to construct in 15 min. You can't go wrong. We guarantee good results.



Total Building Costs **25/-** P. & P. 2/-.

### The "RENETTE"

**THREE TRANSISTORS PLUS  
TWO DIODES**

A highly sensitive receiver using top grade transistors and components. Fully tunable over medium waves. High flux moving coil speaker. Built in ferrite rod aerial. Specially designed coils for maximum signal strength. Volume/on/off control.



Earpiece socket. Easy to follow building plans. Ideal for the beginner in transistor set construction.

Total Building Costs **70/-** Plus P. & P. 2/6.

Earpiece 9/- extra if required (as above but push-pull output 85/-, plus P. & P.).

## R.C.S. for MINI-SETS

**1-4 TRANSISTOR SETS  
FOR  
HOME CONSTRUCTION**

*This is a Build it Yourself year!*  
ENSURE SUCCESS WITH R.C.S.  
THE ORIGINAL AND THE BEST!

All parts available separately. Wiring diagrams and parts lists supplied free with orders or separately 1/6 each item.

### CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components including case for only 12/6. P. & P. 1/6. Easily converted to 1-transistor or 2-stage transistor receiver.


**The "BOBETTE"**  
5 - STAGE SUPER SENSITIVE  
TRANSISTOR PORTABLE  
Simple to Build. All First Grade Components.

A truly portable transistor radio giving full medium wave reception. Incorporates 8in. High Flux Speaker, push-pull output, first grade

transistors, High-Q ferrite aerial, socket for car aerial, pre-tagged circuit board for easy construction. Attractive two-tone case.

Total Building Costs

**£5.2.6** P. & P. 2/6.

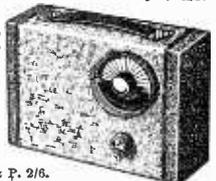

Trade Enquiries Welcomed **R.C.S. PRODUCTS (RADIO) LTD.** 11 OLIVER RD., LONDON, E.17 Mail Order Only

# TRANSMITTING TOPICS



## A CLASS "A" MODULATED MINIATURE VALVE TRANSMITTER.

By  
Amateur Transmitter

THE transmitter described here is a single, compact unit with its own modulator and power supplies, and is constructed on a chassis 7½ in. x 11½ in. x 2½ in. Send/Receive switching is incorporated, so that it is only necessary to add a receiver to obtain a complete table-top type of

station. There is no need for an aerial change-over relay, or separate control of the receiver. Instead, the one control on the transmitter provides complete change-over from transmit to receive, and this is found very convenient when working.

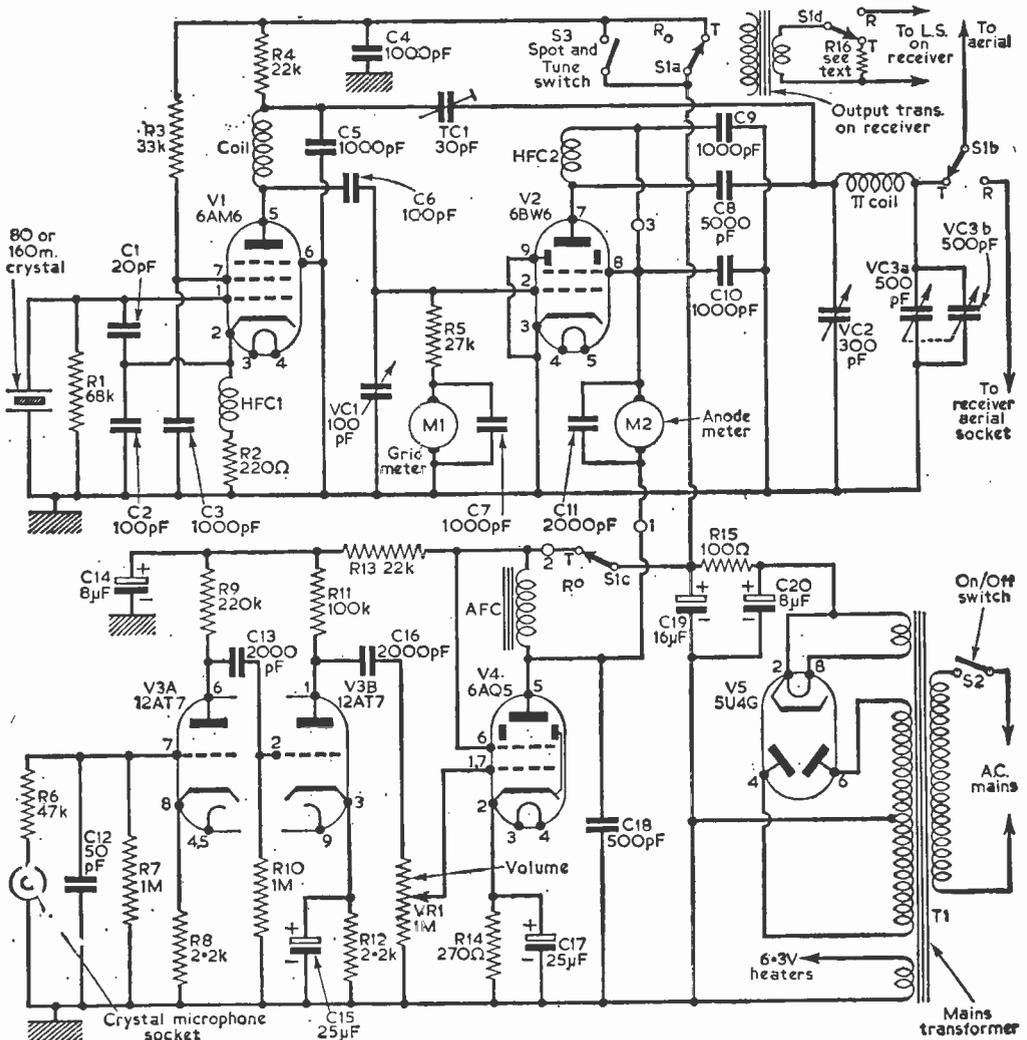


Fig. 1—The complete circuit diagram of the transmitter.





# Improving Broadcast Receivers

By K. Berry

A SMALL INVESTMENT IN A FEW NEW COMPONENTS WILL REJUVENATE AN OLD SET

(Continued from page 853 of the January issue)

**I**N all of the additional R.F. circuits described last month, no extra AVC voltage was used, i.e. in all the circuits which were given, the AVC was applied either to the original frequency changer or to the new amplifier. This is in fact completely satisfactory except where the receivers are operated very close to a transmitter—under these circumstances some overloading could occur. This possibility could be eliminated by always applying the AVC voltage to the R.F. stage (see Fig. 6, last month).

It is perhaps worth mentioning that whilst the circuits given in Figs. 3 and 5 were untuned, it is very easy to include a single, fixed-tuned circuit which will have the result of increasing the R.F. gain at (and close to) the resonant frequency of this tuned circuit whilst retaining the general increase in gain over the whole band. This will thus enable any particular desired frequency to receive extra amplification—e.g. a circuit tuned to 208m would give a considerable increase in gain for reception of Radio Luxembourg.

If it is desired to fit such a tuned circuit, it should be connected between the grid of the R.F. stage and the 10k grid leak resistor.

### Components

Components values are given only for those components shown in the circuit which are additional to those already in the receiver. The valve recommended is an EF92.

If the layout of the receiver will allow it, extra gain may be obtained in the circuits given in Figs. 3 and 5 by using an EF91 or EF80. In this case, the screen is taken straight to H.T.+ and the cathode resistor should be reduced to 150Ω. Since these valves give a very high gain it might be necessary for the H.T. supply to the R.F. stage to be decoupled—a resistor of 2.7k in series with the supply to the anode and screen, with a 0.1μF capacitor to chassis should suffice.

### Increased I.F. Gain by Additional I.F. Stage

A typical superhet I.F. stage is shown in Fig. 7. This is shown again in Fig. 8 with the addition of another stage of amplification preceding the original I.F. stage. This additional I.F. stage may be mounted directly on the receiver chassis; alter-

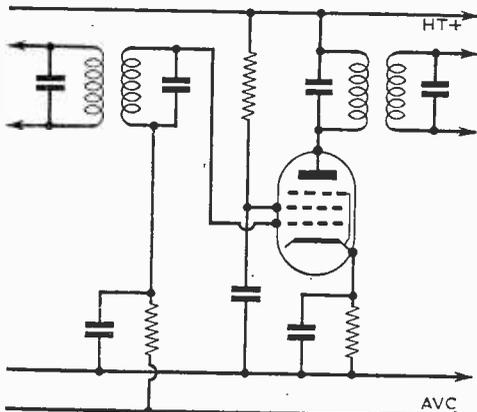


Fig. 7—Circuit of a typical superhet I.F. stage.

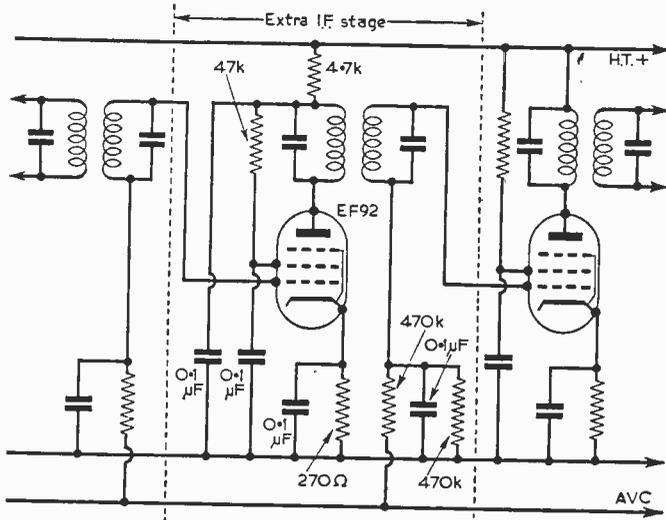


Fig. 8—The circuit of Fig. 6 with the addition of an extra I.F. stage.

natively it may be mounted on a small sub-chassis which is in turn bolted to the main chassis.

This new I.F. stage is controlled by the set's AVC, thus no overloading problems should occur. The normal techniques associated with the R.F. wiring must be employed if instability is to be avoided, i.e. short, direct leads—anode and grid leads kept away from existing "hot" wiring, etc.

**Components**

As previously, component values are given only for those components shown in the circuit which

additional component required for this modification, but a considerable improvement is effected.

**Tone controls**

It will normally be found that "tone" controls of the top-cut variety operating on the primary of the output transformer will be virtually inoperative when feedback is applied in this manner (or indeed in any manner). The reason for this is that negative feedback tends to "straighten out" the frequency response of an amplifier whilst the effect

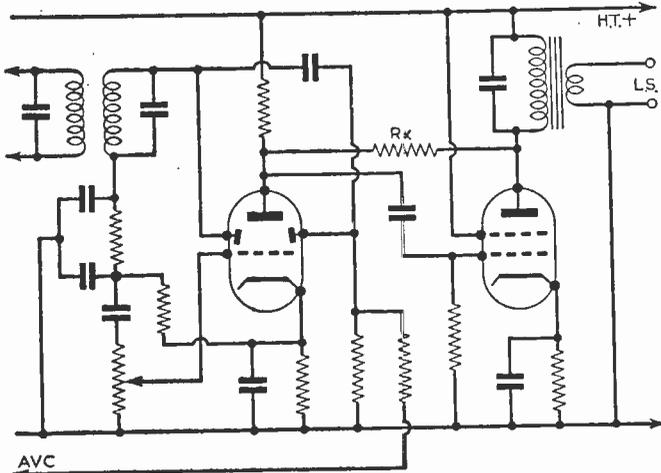


Fig. 9—A typical audio output stage with a resistor Rx added to give negative feedback.

are additional to those already in the receiver. Once again the valve recommended is an EF92. The use of an EF91 or EF80 here should not be attempted as neither of these valves has a vari- $\mu$  characteristic, thus preventing the use of AVC.

**Improving the Frequency Response of the Audio Stage**

This is a very simple modification, and in the author's opinion, the most worthwhile one. Most commercial domestic receivers have a triode L.F. stage followed by a pentode or beam tetrode output stage. It is not usual to employ negative feedback, and "tone correction" is effected by shunting the primary of the output transformer with a capacitor. This sometimes has a fixed resistor in series with it, or sometimes a potentiometer which serves as a "tone" (or top-cut) control. The average receiver of this type has a considerable excess of audio gain, and this can be reduced considerably by the use of negative feedback. This will result in reduced distortion and improved frequency response—particularly at the L.F. end.

In Fig. 9 is shown the L.F. side of a typical domestic receiver. This receiver has fixed "tone correction" by means of the capacitor across the primary of the output transformer. Shown connected between the anodes of the L.F. and output valves is a resistor, Rx. This is the only

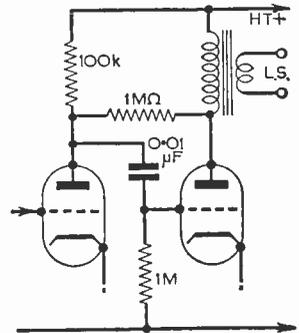


Fig. 10—This circuit shows how the extra feedback resistor forms the upper part of a potential divider (see text).


of the "tone control" is to distort the frequency response so that the net result is that the influence of the tone control will be very much reduced.

**Potentiometer**

The method of operation of the feedback circuit is shown in Fig. 10. It will be seen that the feedback resistor forms the "upper" part of a potentiometer which divides the output of the valve. The "lower" part of the potentiometer is formed by the anode load of the previous valve and the grid leak of the output valve in parallel. The exact value of Rx will depend on how much gain can be "thrown away" and the values of the anode load of the previous valve and the grid leak of the output valve. As a rough guide, the ratio of the potentiometer should be about 10:1, so if for example, the anode load is 100k and the grid leak resistor is 1M, the shunt value of these is 91K; hence the feedback resistor Rx will be about  $10 \times 91k = 910k$ . The nearest value to this in 20% resistors would be 1M.

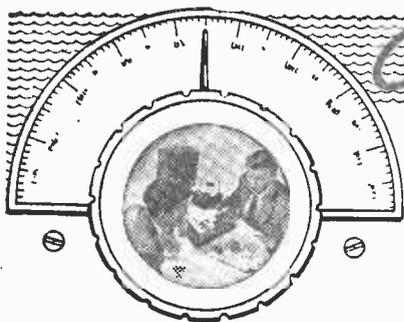**Applying Feedback**

It must be emphasised that applying feedback in this manner will result in reduced A.F. gain, so if your radio has no gain to spare—do not try this. If there is no gain to spare, it is possible to obtain more by removing the existing double diode triode and fitting a pentode valve in its place. The diodes can be replaced by germanium crystal diodes. ■



# On Your Wavelength

## BY THERMION

### Experimental Hardships

IT is surprising what a lot of time can be wasted when you are carrying out experiments and are not in a position to have parts properly checked before use. I recently heard of an engineer who was a keen radio experimenter and who owned both R and C bridges with which he used to check all components before using them. The one big thing he lacked, however, was a valve tester. He tells me that he was carrying out some experiments with a new instrument in which were three double triode valves. He wired them up and commenced his tests, only to be met with failure. Altogether, he tells me, he spent nearly three weeks on this circuit, the valves in use having been removed from a piece of equipment which was working satisfactorily. To sum-up, after fruitless endeavours, he removed the valves for some fresh wiring, and apparently replaced them in different sockets. The circuit worked! The difficulty had been due to one of the triodes being low emission, and of such a character that it failed to work in one stage only. It was one of the high- $\mu$  triodes, and he found later that in the particular stage in which it had originally been plugged, it would not oscillate. It functioned quite well elsewhere and is, in fact, still in use as an audio amplifier, but it will not oscillate in that particular circuit. I suppose a good valve tester would have revealed the fault and prevented so many wasted hours, but I think there is a moral here, and that is, not to rely on a first test, but to either change all the parts or have them tested, especially if it is some new arrangement which has not before been used or tried out.

### Printed Circuits

My comments, some time ago, about the printed circuit have brought many letters and I think it is true to say that opinion is equally divided. I had many interesting suggestions sent to me as to mending or repairing them and it would certainly appear that broken foils are a keen source of trouble. One manufacturer suggested that cracks should not be bridged over, but a new length of wire should be used for the entire run of the broken conductor. One very interesting suggestion was made by a reader to simulate the printed circuit board in ordinary wiring, and I have tried this out and certainly think that it has merits. He takes a sheet of paxolin and drills it to suit the particular layout in which he is interested. First of all he draws out the layout and wiring, arrang-

ing for all earth connections, for instance, to be in one line, and so so. The wire ends of resistors and condensers are then passed through the very small holes which he has drilled in the sheet and a wire run along the other side of the board to tie together all parts which are linked in the circuit. In this way he finally has an insulated board on which the components are on one side, and all connections on the other, and he tells me that testing is facilitated, the final construction is much neater, and the set can be practically prefabricated. I must admit that I tried out the idea and certainly found it had its merits.

### In the U.S.A.

Do the Americans take their radio more seriously than we do in this country? I am prompted to ask this after seeing an American magazine, sent to me by one of my friends who has left this country. With the magazine he also sent two or three "men only" types, and some domestic (home) magazines. I am greatly struck by the large amount of space which is devoted to radio in these magazines, one having about five pages on the subject of loud-speakers. It is a most exhaustive account of the development of this "beast" in all parts of the world, and gives some details which I had not seen in print before.

The amount of space which is devoted to radio, in all of these magazines, leads me to think that they are much more radio-minded in America, and as a result this must lead to a much greater development in the art. Current market items do not, however, seem to bear this out, and there are not so many items on the American market which cannot be seen here, although they are more advanced in such things as colour television. Of course, with all the channels which are available in every part of their country, I suppose the man-in-the-street must be more radio minded, but I would have thought this increased public interest would have led to much greater developments. Considering how lacking in general knowledge the majority of people are here, I think we have done a really good job in both the radio and the television fields, although I still would like to see someone come along with something new in the way of aerials. After all, the unsightly mess on the roofs of houses both here and in the U.S.A. will grow still worse as more channels are opened, and some new "receptor" covering from centimetric to long wavelengths would earn a pretty penny for the inventor and the blessings of every householder.

### PRACTICAL WIRELESS CIRCUITS

17th Edition

By F. J. C.A.M.M.

17/6 by post 18/7

from

**GEORGE NEWNES, LTD.,**  
Tower House, Southampton Street, London W.C.2.

# LASKY'S RADIO

## MINIATURE DISTLER ELECTRIC MOTORS



6 v. high speed (as used in Clarion Tape Recorder). Ideal for all electric models, speedboats, railways etc. Size 2 1/2 in. long x 1 in. diameter.

LASKY'S PRICE **7/11** Post 2/6.

## TRANSISTOR RECORD PLAYER

CAN BE BUILT FOR **£9.19.6**

Carr. free



6 v. operation. For all L.P. and standard records. All components available separately.

**AMPLIFIER.** 300 milliwatts push-pull output using two OC71 and two OC72 transistors. Fully assembled. 70/6. Knobs, 3/6 extra. P. & P. 2/6.

**LOUDSPEAKER.** 30 ohms, 7 x 4 in. elliptical, matched to Amplifier. 25/-.

**3-SPEED TURNABLE.** 6 v., complete with t.f. crystal cartridge and two sapphire st.VII. 70/6. P. & P. 3/6.

**CARRYING CASE.** smart two-tone finish. 17 x 14 x 5 1/2 in. High. 40/6. P. & P. 7/6. Batteries extra.



## 'CLARION' TRANSISTOR BATTERY TAPE RECORDER

Capstan drive, push-button controls. Constant speed 3 1/2 i.p.s. using 3 in. spools. Size 9 1/2 x 5 x 3 1/2 in. with transparent upper. New in maker's carton. LIST 25 Gns.

LASKY'S PRICE with mike and tap. **16 1/2** Gns. Carr. 7/6.

# ★ SPEEDY MAIL ORDER SERVICE ★

IF YOU CANNOT CALL AT EITHER OF OUR ADDRESSES




## THE NEW 'ALBERTA 5' TRANSISTOR POCKET RADIO

Push-pull, 200 milliwatts output. Five transistors and one diode. 2 1/2 in. moving coil speaker, ferrite rod aerial. Med. and long wave. Smart plastic Case. 4 1/2 x 3 1/2 in. overall. CAN BE BUILT FOR **59/6** Post 3/6.

All components available separately. Full details, circuit diagram, 1/6 post free.
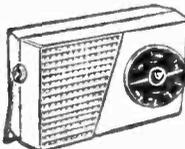
## THE 'TORONTO 3' TRANSISTOR POCKET RADIO



Size 5 1/2 x 3 x 1 1/2 in. Uses 3 transistors plus germanium diode, ferrite rod aerial. Tunable over med. and long waves. Can be built for **32/6**

Post 3/6.

All components available separately.

## BUILD THE NEW LASKY FM TUNER FOR £4.19.6 P. P. 3/6

Non-drift permeability lining pack by famous manufacturer. Frequency 88/100 Mc/s. OA81 balanced diode output 2IF stages and discriminator. Smart gold and maroon glass dial 7 x 3 in. Self powered. Valve line up ECC85, two EF80's, E280 rectifier. Everything ready for assembly. All components available separately. Dimensions: 8 x 6 x 5 1/2 in. Optional extra EM84 magic eye tuning indicator. 8/6. Circuit diagram and full data supplied 1/6 post free.

## POSITIVELY YOUR LAST CHANCE !!

### RE-BUILDING CLEARANCE BARGAINS

at 42 Tottenham Court Road, 'numerable oddments and components clearing at silly prices. Callers only. Do not delay, pay an early visit!

**THE SALE OF THE YEAR**



## LESS THAN HALF PRICE TELEFUNKEN STEREO HIGH FIDELITY AMPLIFIER

A complete stereo amplifier of unsurpassed quality with inputs for radio, tape recorder, P.M. tuner, etc., either mono-aural or stereo. 5 watts output (21 watts each channel, but actual power fed to speaker equals a normal 10-watt amplifier. For A.C. mains 100/250 v. Size: 12 in. wide, 9 in. deep, 2 in. high, green grey enamel finish with gold trim, cream push-buttons. New in maker's cartons, fully guaranteed. LIST 16 Gns.

LASKY'S PRICE **£7.19.6** Post 8/6.

## THE TRANS TRONIC CONSTRUCTION KIT

Make your own transistorised transmitter and receiver. With components supplied, you can build 7 different circuits. Full size wiring diagrams for mounting on peg board 15 x 9 in. supplied. Two transistors OC44 and OC72. 1 XTAL Diode. No soldering necessary.

**IDEAL GIFT FOR YOUNGSTERS** All components marked for absolute simplicity, attractively packed in multi-coloured gift box. 15 page instruction booklet. Originally intended to retail at **£4.4.8**

LASKY'S SPECIAL OFFER **49/6** complete. P. & P. 4/6. Money refunded if dissatisfied.

## RECORD PLAYERS

Complete with p.u. and crystal cartridge. **COLLARO Junior** 4-spd. auto turntable and separate p.u.. 75/-.

**B.S.R. TU9** non-aut turntable and separate p.u.. 79/6. Post free.

**4-spd. AUTO-CHANGERS:** B.S.R., Collaro, Garrard. All types in stock. Send for money-saving list.

## NEW TAPE RECORDER KIT

Handsome 2-tone blue carrying case, 17 1/2 x 8 x 16 1/2 in., goldline fittings, removable lid, cut to fit Collaro studio tape deck. Amplifier uses 4 Valves—EF86, ECC83, EL84, EM81, level indicator, 2 inputs, mike and radio, low level output jack, separate power pack, contact cooled rectifier. All component parts sold separately. Amplifier complete with valves and power pack. **£8.19.6** P. & P. 3/6.

LASKY'S PRICE **£8.19.6** P. & P. 1/6.

7 x 7 1/2 x 4 1/2 in. Loudspeaker, 18/6. P. & P. 1/6. Carrying Case 75/- P. & P. 1/6.

LASKY'S SPECIAL PRICE for the above 3 items **£12.19.6** Carr. 12/6.

**COLLARO Studio Tape Deck,** 3 motors, 3 speeds, etc. **£10.19.6** Carr. 12/6.

LASKY'S PRICE **£10.19.6** Carr. 12/6.

## SAVE ON COMPONENTS !!!

Send for the new 1961-2 edition of Lasky's 100-page COMPONENTS CATALOGUE. Price 2/-, post 6d. Our latest 12-page Bargain Bulletin included free.

Full stocks at both addresses

207 EDGWARE ROAD, LONDON, W.2

Few yards from Praed Street. PADDington 3271/2

33 TOTTENHAM COURT ROAD, W.1

Nearest station Goudge Street. MUSeum 2605

Both addresses open all day Saturday. Close 1 p.m. Thursday.

PLEASE ADDRESS ALL MAIL ORDERS TO DEPT. P.V., AT ABOVE EDGWARE ROAD ADDRESS

# TECHNICAL

# TRAINING

in radio

television and

electronics

Whether you plan to have your own business, to become an electronics engineer, to take up a career in industry, or to brush-up your knowledge and study new developments, transistors, etc., an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.

## EXAMINATION COURSES FOR:—

**C. & G. Radio and TV Servicing Certificate**  
(R.T.E.B.)

**C. & G. Radio Amateurs' Exam.**  
(Amateurs' Transmitting Licence)

British Institution of Radio Engineers, etc.  
C. & G. Telecom. Technician's Cert.

## LEARN AS YOU BUILD

### Practical Radio Servicing Course

A basic course in radio electronic and electrical theory backed by thorough practical training. You build radio receivers, signal generator and multimeter.



**Post this Coupon TODAY!** for FREE book on careers in Radio, and full details of other I.C.S. Courses

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
(Dept. 171), Intertext House, Parkgate Road, London, S.W.11.

Please send book on \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_  
(Block Letters Please)

Address \_\_\_\_\_

Occupation \_\_\_\_\_ 2.62

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

### MINIATURE SOLDERING IRON


Suitable printed circuit work; bakelite handle unscrews to cover element when not in use. P.V.C. case. Our Price, 17/6 post paid.

### A FEW MAINS OPERATED JAP TAPE RECORDERS

Magnetic erase; 11 x 8 x 5 1/2 in. Rexine type covered cabinet; with mike and tape (5in.) and spare spool. Single speed £14; two speed £15. Usual Prices £22 and £24.
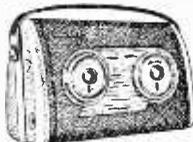
### THIS SUPERB SET FOR £10

A really elegant 6-transistor radio covered in sponge clean Duracour fabric, in latest two tone shades. M.W. and L.W. ferrite rod, provision for car aerial. 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4 lbs. With carrying handle. 12 x 7 1/2 in. high x 4 1/2 in. at base tapering to 2 1/2 in. at top. Brand new, fully guaranteed. £10. Carr. paid. Worth £18.




**TRANSISTORS, Top Grade.** Two matched OC78; 1—OC78D; 1—OC44 (yellow); 2—OC45 (orange and blue). THE LOT of 6 for 37/6 (registered 1/- extra).

**SPECIAL OFFER OF GOODMAN 10 x 6in. SPEAKER** high gauss, with doped cone specially suitable for high fidelity work. Price 27/6 (post 2/6).

### TAPE RECORDER FOR ONLY

**£17.17.0**

(10/- carr.)

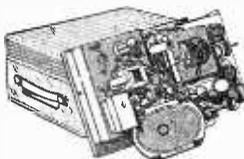

**A QUALITY ARTICLE.** Valves EZ80, ECC83, ECL82, DM70. Acos crystal "mike", 850ft. Tape and extra spool. 3 1/2 in./sec. Mike and Radio inputs; Vol. on/off tone, Ext. L.S. and Monitor. Fast forward and reverse. Cannot be accidentally erased. Magic Eye Indicator. 8 x 4 in. Speaker. Cabinet 14 x 11 x 7 1/2 in.

Supplied completely built and in cabinet.

**PANEL OF 7 POTS.** 10 x 1 1/2 in.—4 x 1 M and 3 x 2 M. 4/- (post 1/-).



**6 DIFFERENT PRE-SET POTS.** 2K to 500K. 3/- (post 1/3).

**MAINS TRANSFORMER.** 6.3 v. 1 1/2 A and 200 v. 30 mA. 7/- (post 1/6).

### THE "CABY" TEST METERS

Prices include Test Prods. Batteries, Instruction Book. Also measure dB. Accuracy: A.C., 3 per cent. D.C., 2 per cent.

A-10 **£4.17.6** B-20 **£6.10.0**

A.10—2K ohms/v. on A.C. and D.C. volts (10, 50, 250, 500 and 1000 v.); 10K and 1M ohms; 1mA, 25mA and 250mA. D.C. Size. 5 1/2 x 3 1/2 x 1 1/2 in. Weight 17 oz.

B.20—10K ohms/v. on 0.5 v. and 2.5 v.; 4K ohms/v. on 10, 50, 250, 500 and 1000 v.; A.C. and D.C. Resistance, 2K, 200K, 2M and 20M ohms; D.C. current, 100 microA, 2.5 mA, 25 mA, 250 mA. Size 5 1/2 x 3 1/2 x 2 1/2 in. Weight 24 oz.



**PERSPEX.** 15 x 12 x 1 1/2 in., tinted blue/grey, 6/6; 12 1/2 x 9 1/2 x 1 1/2 in., Clear, 5/-; 16 x 14 x 3/16 in., Clear 7/6. Postage 2/- on 1; 3/- on 2 or more; 6 post paid.

### ELECTRIC SHAVER BARGAIN

**SAVE 10/-.** Swiss made Unic Shaver operating from 1.5 v. battery, usual price 59/8. Our price 50/- with battery. Takes U2 battery. Not a toy, but a first-class shaver (carr. paid).

## GLADSTONE RADIO

For additional advertisement and address—  
see inside front cover

# All about CATHODE FOLLOWER circuits

By E. McLoughlin

## PRINCIPLES AND USES OF THIS TYPE OF CIRCUIT

(Continued from page 808 of the January issue)

**T**HE last example of the use of cathode followers which we discussed in the January issue was in circuits where pulses of high voltage are required, for example, in the synchronisation of timebases.

### Calculations

In all high-amplitude uses, it is very simple to decide whether a certain combination of valve,  $R_k$  and H.T. voltage, is capable of handling an intended signal. Let  $V_n$  be the peak negative signal amplitude. Then the grid leak (Fig. 6, last month) is returned to a point at about plus  $V_n$  to chassis. It follows that the cathode will also rise to about plus  $V_n$  (just a little more). By Ohm's Law, the current flowing in  $R_k$  is then easily calculated. This represents the "resting" anode current of the valve, and must not exceed the rated value for the valve used. Furthermore, let  $V_p$  be the peak positive signal amplitude. The sum of  $V_p$  and  $V_n$  must not exceed one half of the rated H.T. voltage of the valve used. The H.T. voltage chosen should thus be double the peak-to-peak signal, or more, within the rating of the valve, and the smallest possible value for  $R_k$  be chosen which neither causes the anode current rating of the valve to be exceeded, nor lies below about 50 times the reciprocal of the mutual conductance. It is desirable to make  $R_k$  as small as tolerable within these limits, because the voltage fluctuation with further external loading is then as small as possible. Normal operating anode current ratings, and not peak values, should be consulted in the above design procedures.

It should be mentioned that the signal frequency response of a normal cathode follower is virtually linear over the entire video spectrum, including pure D.C., and goes right up to many megacycles.

### Cathode Followers as Signal Generator Output Stages

As the output stage of an Audio or R.F. Signal Generator, one often finds a cathode follower. The reason lies in most cases in the use of the property that the output voltage is largely independent of the exact value of the external load resistance connected. This enables an output calibration to be made for the signal generator which can be relied upon to hold, with tolerable accuracy, for the most varied external loads connected. We are thus mainly concerned with 1:1 voltage-transfer cathode followers here, with their typical high value of  $R_k$  of about 10,000 $\Omega$  to 20,000 $\Omega$ , or more.

Power-output cathode followers are normally not in question for signal generators, at any rate for audio and broadcast R.F. signal generators. But, for extreme VHF signal generators, such as are used for the high television channels, as well as for video-waveform test-signal generators, where maintenance of accurate waveform is essential, new factors play a role, which necessitate the use of a power cathode follower in many of these cases. If any disturbance is made in an electrical circuit, then the effects of that disturbance are not felt immediately at all other parts of the circuit, but spread out with the velocity of light or less. In particular, if we have a length of coaxial cable, and switch on a signal at the input end, it is not present at once at the output end, but only after a time corresponding to a definite speed of travel of the signal down the cable, which is of the approximate order of the velocity of light. Now, this high speed means that, for reasonable lengths of cable, and audio or broadcast radio frequencies, signal transfer down the cable may be considered, for all intents and purposes, instantaneous. But at very high frequencies, such as are met in modern television techniques, the transit time of even a

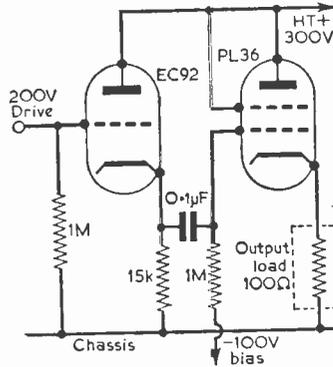


Fig. 7—100W pulse-power cathode follower.

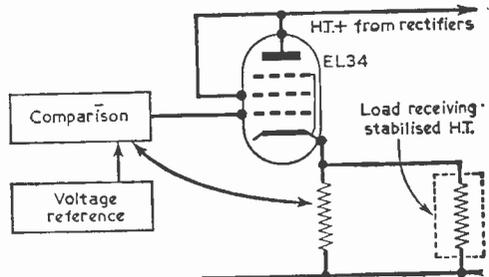


Fig. 8—H.T. voltage stabiliser.

few inches of cable is an appreciable fraction of a cycle. If impedances are not properly matched at all cable/apparatus junctions, a partial reflection giving signals travelling in the opposite direction to that intended occurs as well as loss of power. Reflections from separate ends of a cable will not be in phase, on account of the transit time. Moreover, the phase difference will depend upon the

a drive of 200V to give an output signal of 100V in the matched condition with a 100Ω cathode load, we just run up to the permissible 1A peak anode current. The output power realised in the external 100Ω load is then given by  $1A \times 100V$ , i.e. 100W. Let us assume, typically, that the maximum mean current rating of the valve is 100mA. Then the peak 100W condition may be operated only for one tenth of the total time. For example, one 100W output pulse, lasting a tenth of a second, is permissible once every second. In between times the valve would be resting at its set D.C. operating point, and we can now consider where this will have to lie. At the pulse-peak, when 1A anode current is flowing, the grid-cathode signal will be virtually zero. Thus the grid will be at the same voltage as the cathode, i.e. 100V positive. We are using a 200V positive drive, and thus the D.C. resting point will have to be with the grid at 100V negative to chassis. In other words, the valve is heavily cut off when no signal is present, and thus we see that the pulse power cathode follower is a special case of a Class-C amplifier.

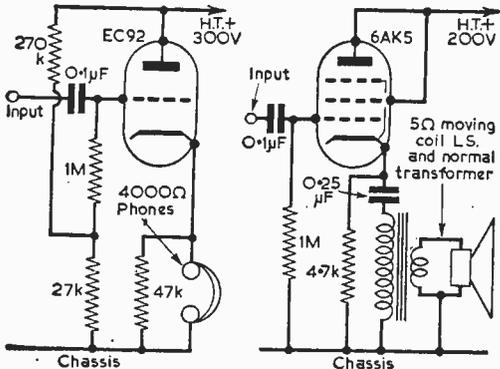


Fig. 9 (left)—Circuit of a "safe" output stage for phones using a cathode follower.

Fig. 10a (right)—Simple cathode follower output stage.

frequency of the components of a complex waveform. The net result will be a complete change in the waveform. It is thus essential to match a television waveform signal generator output to the intended load, and thus one finds power cathode followers in many cases in such apparatus.

**The Pulse Power Cathode Follower**

It is indeed possible to obtain very considerable power out of specially designed cathode followers. If we take a valve of high mutual conductance and having a pulse cathode capable of one amp or so peak current (although, of course, the mean current rating is much smaller), such as are found among modern line-output valves in television receiver circuitry, then short pulses of high power can be generated with such a valve connected as a cathode follower. Let us assume a typical mutual conductance of 10mA/V, giving an output impedance, as cathode follower, of 100Ω. Using

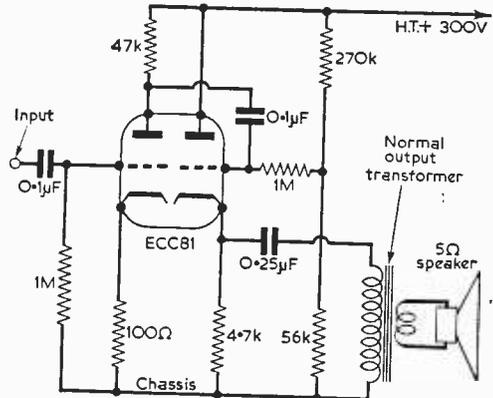


Fig. 11—A double triode cathode follower output stage.

**Cathode Follower Drive**

The drive for such a power cathode follower naturally consumes no appreciable power, it is a pure voltage drive. Nevertheless, just in case grid-current flows at the pulse-peaks, the drive can be from a smaller cathode follower, this time in 1:1 transfer circuit with the usual high RK. Fig. 7 shows a typical complete circuit. The chief use of such a circuit is for firing grid-controlled hydrogen thyratrons in large radar installations, which consume considerable power at the grid. It is also known to the author that such a system has been used to modulate the output stage of a transmitter. The power output cathode follower supplies the entire H.T. power for the P.A., simply by making the P.A. itself take the place of the cathode load. Such modulation circuits, also known as series-modulation, are used in several pulsed radar transmitters.

Finally in this group, it should be pointed out that the usual H.T.-stabiliser circuits using a series-regulator valve (such as in several designs recently published in this magazine) are virtually a special form of D.C. power cathode follower. Redrawing

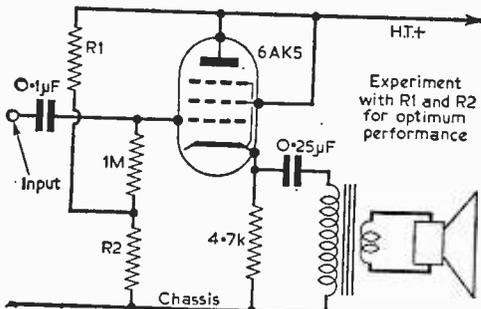


Fig. 10b—Improved cathode follower output stage. R1 is 220k, R2 is 100k, and the H.T.+ is 200V.

the circuit of such a stabilised power supply in the form of Fig. 8 immediately brings out this point.

**Continuous Power (Class A) Cathode Followers**

These are the true members of the "power" class of cathode follower, in that they can supply output power, say at audio frequency, in much the same way as a conventional output stage delivering power from the anode circuit.

**High Impedance Loudspeakers**

Those experimenters still possessing large moving-iron loudspeakers of former days in their junk boxes, having coil impedances of some few hundred ohms, may like to try one direct as cathode load, without transformer, in such a cathode follower output stage. Any small R.F. pentode can be used, strapped as triode. In many cases the constructor will very likely be astonished at the results. Apart from good volume, the

tone is generally much better than with the same speaker used in an anode circuit, as the extremely low internal impedance of the cathode follower damps the unpleasant resonances of this type of loudspeaker to a high degree. It is even worthwhile, just for this last reason, trying a conventional output valve such as the 6V6 or the EL84 as a cathode follower. In such a case, however, it is necessary to pay special attention to the correct D.C. operating point, so that the valve does not run at low or excessive anode current. The D.C. resistance of the transformer winding or speaker coil in the cathode circuit must equal the normal cathode bias resistor of the valve used. If it is less than this, then an appropriate series resistor must be used to make up the difference. If it is a little more, that does not matter much, as long as it is not excessive.

Naturally, the voltage drive required by a cathode follower output stage is high, being about 10 to 100V in most cases. Thus, the audio amplifier preceding the stage will have to have higher gain than is otherwise normal. An extra triode stage can often provide this gain. It is often convenient to use one triode of a double triode to give this extra gain, and the other as the cathode follower. In this way, a valve such as the ECC81 can replace a conventional output valve (see Fig. 11), the rest of the audio amplifier being unchanged. In the case of the author's 6AK5 output cathode follower of Fig. 10a the necessary drive was present anyway, as the Y-deflection of the tube in the oscilloscope requires a similar drive, so that sufficient voltage to drive the cathode follower was present at the Y-amplifier output.

**The White Cathode Follower**

Fig. 12 shows a further development of the cathode follower principle, to give even lower internal impedance. It is possible to achieve an impedance of a few ohms with this circuit, so that in principle, a moving coil speaker would match direct without transformer into it. This is true in practice, too, but the power output is then poor in comparison with the H.T. consumption and size of the valves. This is simply because of the restriction that the valves may not be permitted to run up to the necessary anode current. Thus using a PL36 triode-strapped in each position, only 50mW is possible into a 15Ω moving-coil speaker.

*(To be continued)*

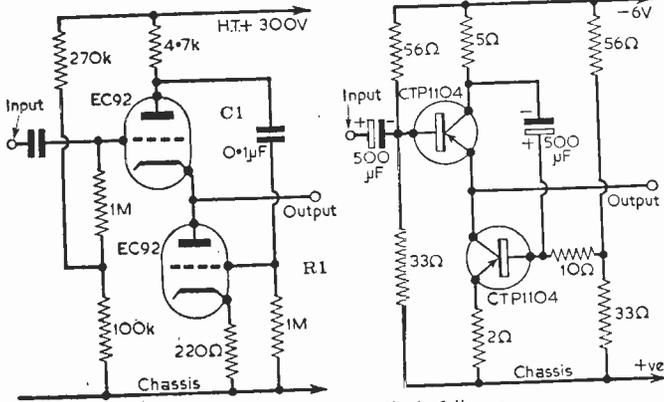


Fig. 12 (left)—A White cathode follower.

Fig. 13 (right)—The transistor equivalent of the White cathode follower (or all resistors increased by the same factor).

It is little known by experimenters that sometimes considerable advantages are to be gained by using an output stage feeding a loudspeaker or headphones in the form of a cathode follower. The first and obvious advantage is that the problem of isolation of the phones from the H.T. voltage is automatically absent (Fig. 9).

The second great advantage is apparent in circuits requiring a small monitor-speaker, but where for reasons of power economy or heat dissipation limits, a conventional output valve is undesirable. In such cases, constructors have often used simple A.F. triodes or R.F. pentodes, frequently with relatively poor results because of the very high anode matching impedances generally required in such circuits, which cannot always be realised with normal loudspeaker transformers. Much improved results are often possible using the same valves as cathode followers, with the normal loudspeaker transformer primary forming Rk. In many cases the D.C. resistance of the transformer primary is sufficient to set a proper D.C. operating point of the stage without further attention to the matter. Fig. 10a shows a typical circuit example which the author has had in operation for a long time. A tiny 6AK5 R.F. pentode strapped as triode cathode follower delivers over 50mW into a small moving coil loudspeaker. The circuit is a small addition to an oscilloscope, to monitor the Y-signal audibly. There was not room, nor spare H.T. power, nor heat dissipation facility, for operating a conventional audio output stage. But this tiny cathode follower output stage draws only some 5 or 6mA H.T. current.

# SHORT-WAVE SECTION


## A PRACTICAL PRE-SELECTOR

By A. Sydenham

(Continued from page 833 of the January issue)

**I**N the previous article, the circuit was described and it now remains to assemble the complete unit and build a cabinet for it. It may then be tested.

A diagram that shows practically all the chassis drilling is given in Fig. 4, the coil mounting apertures being those required for the coils specified. Should the tuning capacitor in contact the coil bases when in position, washers should be fitted to provide clearance. Alternatively, the coils may be fitted to a rectangular piece of paxolin held by spacers. Most of the wiring can be made so short that small items are easily

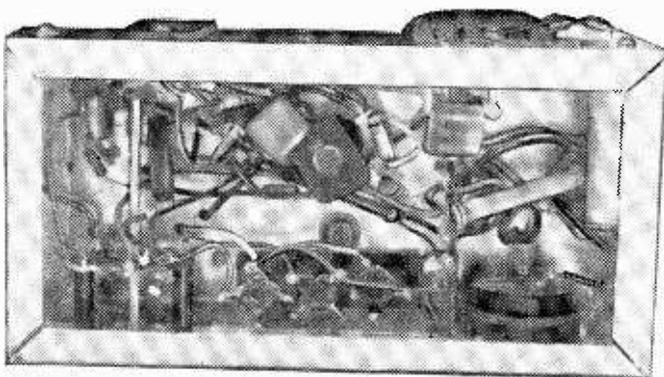

Underchassis view of the pre-selector.

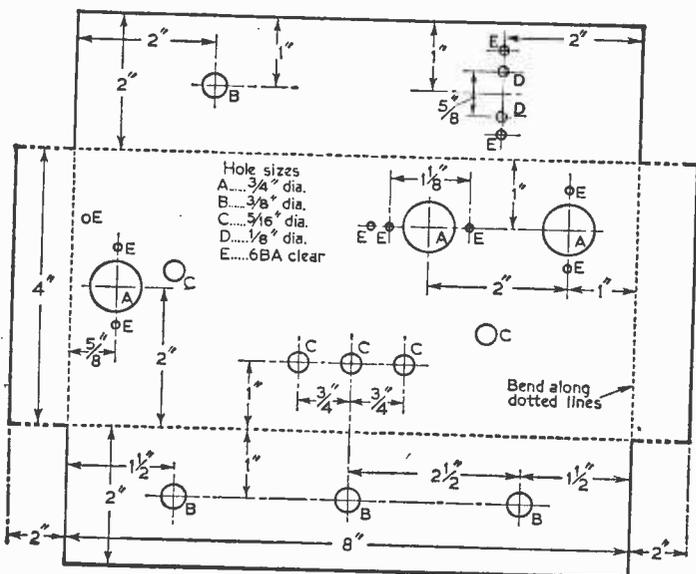


Fig. 4—The chassis drilling diagram.

suspended in the leads and the orientation of the coils and valvoholders assists in this respect. Electrolytic condensers C9/C10 and C11 are held against the chassis by clips.

### Assembly

The front panel is secured to the chassis by means of the nuts securing VR1 and S1/S2 and reference to Fig. 5 will show the locations of the various apertures. The tuning condenser spindle also projects through the front panel and a coloured warning lens is fitted to the lower central aperture. It will be found when the panel is firmly bolted in position that the assembly slopes backwards slightly and this not only brings the controls to a more convenient operating height but also improves the general appearance. Mitred sections of quadrant glued firmly to the panel edges further assist in this respect.

### Wiring

Use of a soldering iron with a pencil bit is essential and modern miniature resistors and condensers are needed to avoid congestion of sub-chassis components. The use of differently coloured sleeving will also assist final checking considerably.

### The Cabinet

The simple design is shown in the semi-exploded diagram of Fig. 5 and may easily be made from  $\frac{1}{4}$  in. plywood held together with reinforcement strips, pins and glue. Strips of veneer (obtainable from some model supplies shops) may be glued using Bostik No. 1 adhesive to the edges where joins appear if desired, and the finish may be chosen to suit one's personal taste. The prototype is lacquered in ivory. The slots cut in the sides serve as carrying handles and also provide


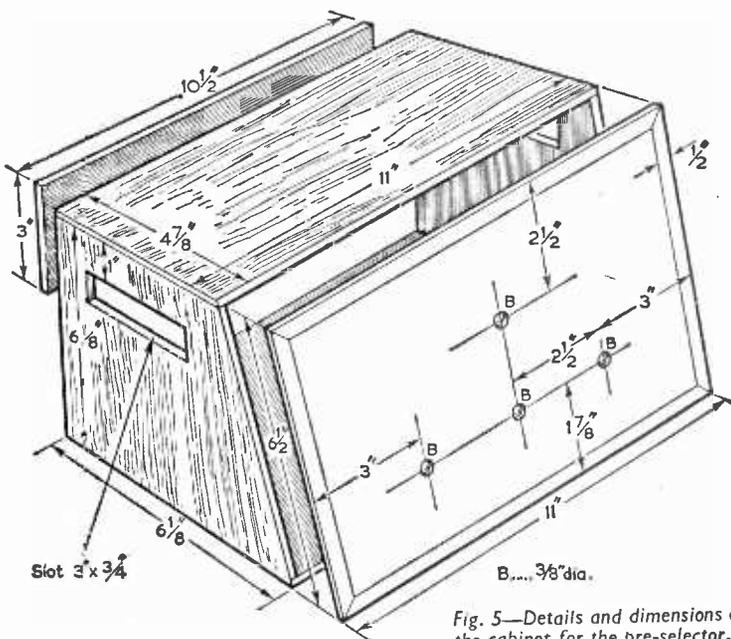


Fig. 5—Details and dimensions of the cabinet for the pre-selector.

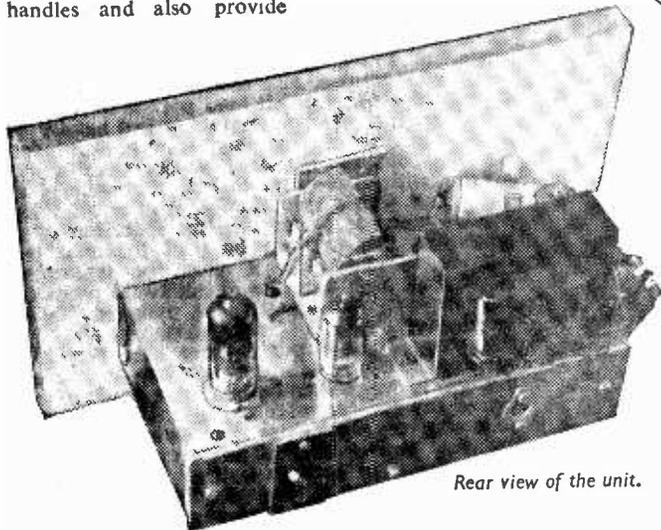

Rear view of the unit.

ventilation as cool air is convected from the rear. Four small rubber feet may also be fitted.

### Using the Pre-selector

When the unit has been completed and checked the aerial and earth leads should be removed from the receiver with which it is to be used and plugged instead into the sockets provided for them on the pre-selector.

A length of coaxial cable should then be prepared, aerial and earth plugs being fitted at one end (the braiding being connected to the earth plug) and a coaxial plug at the other. This lead

should then be plugged into the appropriate sockets on each piece of apparatus. Control VR1 on the pre-selector should now be set to "off" and the wave-change switch turned to position 4. The main receiver should then be switched on and adjusted to receive a transmission in a band also available to the pre-selector. The receiver should now act normally, since the aerial is effectively connected to it direct. The pre-selector may then be switched on and allowed to warm up when its wavechange switch may be rotated to select the appropriate band in use. The received signal should now improve in strength considerably and, as the tuning control of the pre-selector is adjusted, it may be found necessary to back off the sensitivity control, VR1, to avoid overloading. A little practice will soon reveal the best method of use but it should be remembered that too strong a signal fed to the receiver may bring the AVC circuit into action too strongly. Once the user has familiarised himself with operation of the unit it may be calibrated.

When it is desired to use the main receiver on its own it merely becomes necessary to turn the wavechange switch, S1/S2, to position 4 and rotate VR1 to "off" when the indicator lens will become dark. By then, however, the advantage of R.F. gain will have been made apparent.

(Continued on page 942)

THIS UNIT WAS ORIGINALLY  
DESIGNED FOR USE WITH  
A SIMPLE GEIGER HEAD,  
BUT IT WILL OPERATE  
SATISFACTORILY FROM ANY  
SUITABLE INPUT SOURCE

By A. Cole


# A DIGITAL 2505 COUNTER

**W**ITH the reintroduction of frequent atomic bomb tests recently, it is an interesting—and possibly useful—occupation for the electronically minded experimenter, to monitor the degree of radioactivity in the air, rainwater, drinking water, or any other samples of interest. Contrary to common belief, this is neither difficult, nor does it require any unusual or expensive circuit components, except for a suitable small Geiger tube. There are some excellent small tubes on the market now, available in the United Kingdom from Messrs. Mullard. The author uses a tube of type number MX146. These small tubes have the great advantage that they require only about 450 to 500 operating voltage, which is easily obtainable from ordinary mains transformer/rectifier circuits.

For checking atmospheric radioactivity, etc., a pure counting of the pulses is required, and the present article describes a suitable automatic electronic counter, giving a direct numerical display of the result on a type of digital relay used by the GPO for counting telephone calls and easily obtainable for about 15s. to £1 at many surplus stores.

The digital counter unit may, of course, also be used for any other appropriate purpose. It will count accurately the number of times a voltage of at least plus 10 is switched on into the input. It does not react when this voltage is switched off again, but counts one more when it is switched on again, and so on. So long as this voltage is 10 at least, and positive, and capable of delivering a current of about 1mA, it does not matter exactly how large it is. Thus a morse key and battery in series connected to the input can be used for manual counting of large numbers of small articles, without the need to keep the numbers in one's head, with consequent danger of error. With a relay wired to contacts on the space bar of a typewriter, the unit can be used to count the number of words in a piece of typescript. But for all such uses, the circuit could probably have been a lot simpler: the main use is in conjunction with a Geiger counter, and for this purpose the circuit features have primarily been developed, as will be seen below. Above all, the unit is designed to be as fast as possible, and free of any grid-current-blocking so that two pulses following very rapidly one after the other are both counted individually. The actual resolution achieved in the author's unit is better than 15 counts per second at the upper limit, which is far greater than the pulse-rate ever obtained with the type of Geiger tube specified with atmospheric radioactivity. In fact, the normal atmospheric count with this tube is about 20 counts per minute, i.e. only about one count every three seconds on the average. But these counts are fully irregular—

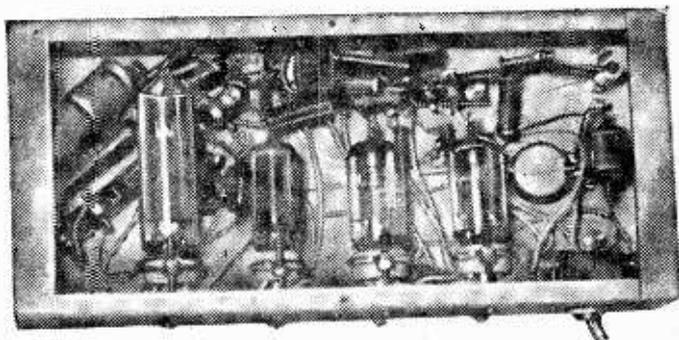Internal construction of the digital counter unit.



there may suddenly be many close together, and then for a long time absolutely none, yet it is virtually impossible for a whole minute to pass without any counts at all.

**Principle of the Digital Counter Circuits**  
(see Fig. 1)

This is a four-valve triggered pulse-amplifier circuit. V1 is the input amplifier, comprising two stages—V1A is an earthed-grid input stage, meeting the three requirements (a) freedom of feedback, (b) keeping the same signal polarity (positive), and (c) good gain, so that the stage is over-driven, giving very steep output pulses to V1B, which is a cathode-follower decoupling V2 from V1A as far as feedback is concerned. V1B also returns the signal to

low impedance, and now delivers a good steep pulse of at least 100V amplitude. The tiny value of C3, the coupling condenser to V2, differentiates this pulse, so that only a very brief but very steep spike of about 100V is applied to the grid of V2A.

Valve V2 is a monostable multivibrator, the purpose of which is to provide a good squarewave pulse of current, starting exactly at each 100V "trigger" spike from V1, and lasting about one twentieth of a second, which is the optimum switching-time for the counter relay. V2A is normally cut off, because its grid is on a bleeder chain from the low voltage at the anode of the normally conducting section V2B down to a variable negative bias from VR1. The other section, V2B, is, as just stated, normally conducting

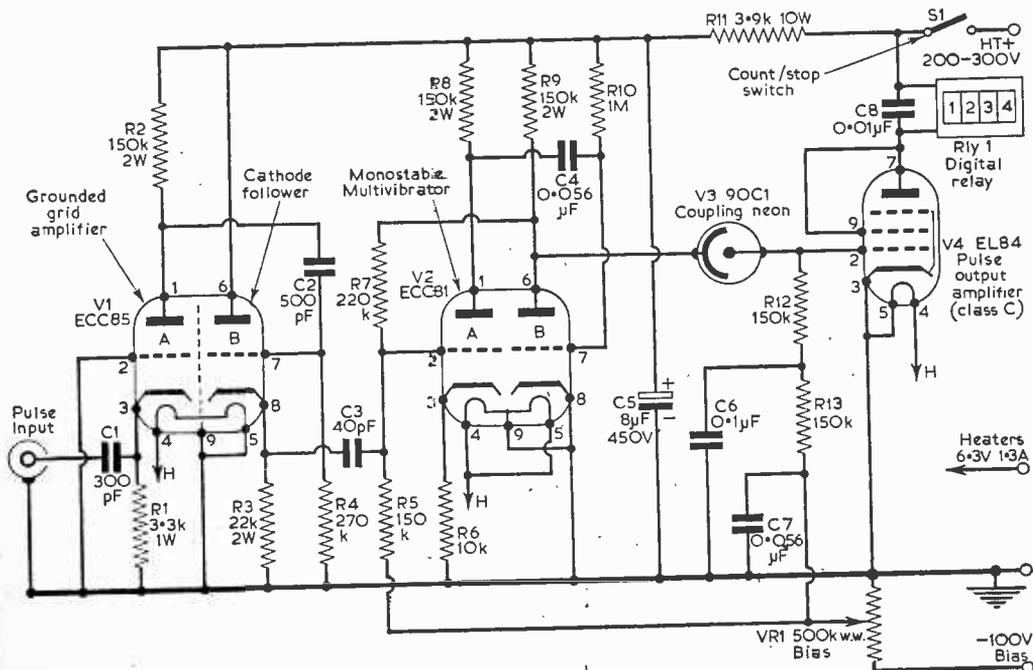


Fig. 1—The circuit of the digital counter. (All resistors are 1W rating except where stated.)

heavily because its grid leak is returned to H.T. positive. This condition is perfectly stable for any length of time until the circuit is suitably disturbed. This disturbance is the short positive 100V spike applied to V2A grid. This lifts it to cut-on and above, which causes an equivalent voltage drop at the anode, which is fed via C4 to the grid of V2B, thus tending to cut off V2B. This causes the anode potential of V2B to rise, which is fed as a further rise to V2A grid on the bleeder. The net result is that the formerly cut-off V2A has suddenly been tuned hard on, and the formerly conducting V2B has been cut off.

Maintenance of this new condition depends upon maintenance of the signal at V2B grid, which remains only as long as C4 is charging via R10. As soon as C4 has charged sufficiently, which takes about one twentieth of a second, V2B cuts on again, and reverses the procedure back to the previous stable state with V2A cut off and V2B conducting, until the next trigger spike arrives. The net result is thus a positive-square-wave pulse of about 100V amplitude and about one twentieth of a second duration at V2B anode.

V4 is a class-C amplifier, i.e. the bias-point is beyond cut-off, applied via R12 and R13 from VR1. In the normal, stable, resting state of V2, with V2B anode at a low voltage because of the heavy conduction of V2B, the voltage difference between V2B anode and V4 grid is not sufficient to strike the neon tube V3; thus V4 is fully disconnected from V2 and resting, cut-off. But during the temporary

change-over position of V2, when V2B is cut off and thus the anode voltage high, the neon V3 is struck, driving V4 grid heavily positive. The surge of anode current in V4 moves the digital relay RLY1 one unit on. As soon as V2 reverts to the stable condition, V2B anode potential falls again and the neon V3 extinguishes. V4 grid returns at once to beyond cut-off, and anode current ceases instantaneously. This sudden stoppage of anode current could cause high inductive voltage peaks across the coil of RLY1, if C8 were not there. Thus it is essential not to omit C8, as otherwise the relay could be damaged by flash-over in the coil. On the other hand, do not make

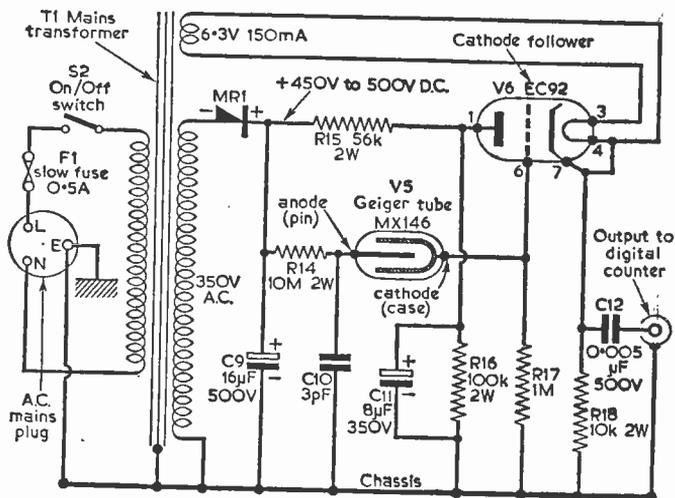


Fig. 2—The circuit of the Geiger head.

### COMPONENTS LIST

#### Resistors (All $\pm 20\%$ Carbon):

R1 3.3k 1W	R10 1M 1W
R2 150k 2W	R11 3.9k 10W
R3 22k 2W	R12 150k 1W
R4 270k 1W	R13 150k 1W
R5 150k 1W	R14 10M 2W
R6 10k 1W	R15 56k 2W
R7 220k 1W	R16 100k 2W
R8 150k 2W	R17 1M 1W
R9 150k 2W	R18 10k 2W
VR1 500k Pot. 1W (w.w.)	

#### Condensers:

C1 300pF ceramic 500VW
C2 500pF ceramic 500VW
C3 40pF ceramic 500VW
C4 0.056µF paper, 500VW
C5 8µF 450VW electrolytic
C6 0.1µF paper, 500VW
C7 0.056µF paper, 500VW
C8 0.01µF paper, 500VW
C9 16µF 500VW electrolytic
C10 See text next month
C11 8µF 350VW electrolytic
C12 0.005µF ceramic 500VW

#### Valves:

V1 ECC85
V2 ECC81
V3 90C1 (neon)
V4 EL84
V5 MX146 Geiger Tube (Mullard)
V6 EC92
D1 Metal rectifier 350V A.C./25mA D.C.

#### Sundries:

Three B9A valveholders, ceramic  
 Two B7G valveholders, ceramic  
 Two coaxial plugs and connecting lead  
 One digital relay, GPO, approximately  
 2000  $\Omega$ /25mA (Service Trading Co., 47-49 High  
 Street, Kingston-on-Thames, Surrey.)  
 Two toggle switches on/off, single pole  
 One panel fuse, complete  
 Chassis material, wire, solder, tagstrips, bolts,  
 sleeving, etc.  
 Test tubes, rubber cork.  
 Power supply (preferably stabilised) 200-300V/  
 100mA 6.3V 1.3A A.C. (heaters)  
 Bias supply: about (-100V) on above power  
 unit, or otherwise a small 90V H.T. battery  
 Mains lead and plug

C8 appreciably larger than specified, as this would then destroy the steepness of the current rise at the start of each pulse, possibly leading to erratic counting. It is of interest to discuss why a neon, V3, is used to couple V2 to V4 instead of the usual coupling condenser. The reason is simple. The signal from V2 is of such a high amplitude that V4 is driven from beyond cut-off right up to heavy grid current by it, and such grid current would charge any coupling condenser heavily and very rapidly during the pulse. After termination of the pulse, this would leave V4 at a correspondingly greater negative voltage at the grid than the intended operating point. This would have the result that the circuit would be more or less blocked at V4 for any pulse coming in subsequently before the coupling condenser had discharged, and would also block the circuit at V2A grid, because the excess negative voltage at V4 grid would react via VR1 and R5 to pull down V2A grid too. The neon thus prevents the amplifier blocking when working at counting-rates approaching the limit of resolution. The alternative method of preventing large-current blocking of amplifiers handling large signal amplitudes, namely the insertion of grid-stoppers, is not usable here, because it causes signal loss due to voltage drop across the stoppers, and thus makes the anode current rise in V4 too slow for stable counting.

It should be mentioned in passing, that the use of neons as coupling elements in amplifiers receives far too little attention by experimenters. They have

Returning to the digital counter circuit. A supply of about minus 100V is required on the bias line input (the exact value is not critical, but should be stabilised preferably—if the constructor has no power unit supplying this output in addition to normal H.T. and heaters, then a small 90V H.T. battery will serve the purpose excellently. This battery may be very small, as the current drain is only about a fifth of a milliamp (but do not forget to switch this battery off after use). The actual value of optimum bias taken to V2A and V4 is quite critical, and also dependent on the H.T. voltage used. The circuit operates excellently with any H.T. voltage between 200 and 300, but requires a different bias value with each H.T. voltage. Consequently the potentiometer VR1 has been incorporated, to set the bias to the optimum value. This potentiometer should be used more or less as a reaction control is used on a simple radio. Bias should first of all be increased until counting stops altogether even when the Geiger-head is supplying pulses at the input, and should then be reduced sufficiently to be quite certain of counting all pulses received. It is too difficult to make this adjustment with the mere 20 pulses per minute of the normal atmosphere, and thus it is advisable to place an alarm clock with luminous figures, or a pocket-watch with substantial luminous figures, near the Geiger tube. The radioactive content of any such luminous paint is sufficient to raise the counting rate of only 20 per minute right up to possibly several hundred per minute, which is

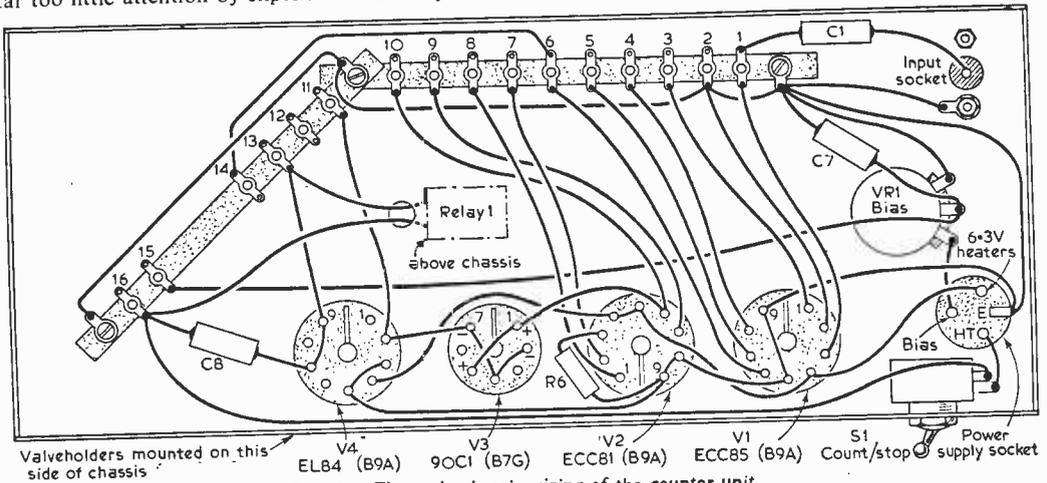


Fig. 3a—The underchassis wiring of the counter unit.

a number of advantages over condensers. In a normal class-A audio frequency amplifier, the coupling neons would be permanently struck, and thus represent D.C. coupling and theoretically freedom of all gain variation with frequency. Such an amplifier would amplify D.C., could have many stages, yet use otherwise conventional A.C.-amplifier circuitry with a single common H.T. supply on which all stages run in parallel as usual. And, as seen above, neon-coupling is free from blocking on transients. Of course, the value of cathode resistors, etc. would have to be modified in such an amplifier. But the principle is clear, and might interest more experienced constructors.

sufficient to make bias adjustments conveniently. At the slower counting rates, the bias setting is not in the least critical. If too high, counting stops altogether and if too low, then V4 runs at heavy anode current which will soon destroy it. Between these two points lies at least one third of the travel of VR1, and slow counting is equally good at any point within this range. But if fast counting is desired, e.g. when checking the radioactivity of luminous paints, or possibly X-rays from poor or defective television cathode-ray tubes, it will be found that if the bias is set too far below the critical value, many counts will be missed.

(To be continued)

# Faults in Transistor

ALIGNMENT AND CIRCUITRY

By J. Christy

**T**RANSISTOR superhets usually have two intermediate frequency stages, and faults in these may cause lack of sensitivity, or oscillation and other troubles. The I.F. amplifier should be able to provide a very high gain, and if it does not do this, good reception of distant or weak stations will be impossible.

## Alignment

Correct alignment of the I.F. transformers is easily achieved. If a signal generator is available, this may be set to the correct intermediate frequency (often 470kc/s) and coupled to the I.F. amplifier at a convenient point. If the circuits are out of tune, a fairly strong input may be needed, or it may be necessary to take the generator output directly to one of the transformers, a small isolating condenser being included in circuit. However, if the alignment is approximately correct, a very small signal will suffice. Merely placing the end of the generator prod or output lead a few inches from the mixer collector circuit should then give enough coupling.

When receivers have the popular type of push-pull output stage, battery current depends directly on the volume of the audio signal. If the generator is delivering a modulated output, a 15mA or similar meter in one battery lead is thus a convenient means of checking for maximum output.

When a good output is being obtained, when the I.F. stages are aligned approximately, the input from the signal generator should be reduced. Accurate adjustment is then easily achieved.

An insulated tool (made from an ebonite rod, for example), is used to adjust the I.F. transformer cores. They are simply screwed in or out, as needed, to obtain best results. Each core should have a fairly sharp tuning point.

If no generator is available, a local station should be tuned in, and the cores adjusted for best results. A weak station should then be found, with the audio volume control at maximum, and final adjustments should be made.

If all cores are in a reasonable position, it should generally be possible to align the aerial and oscil-

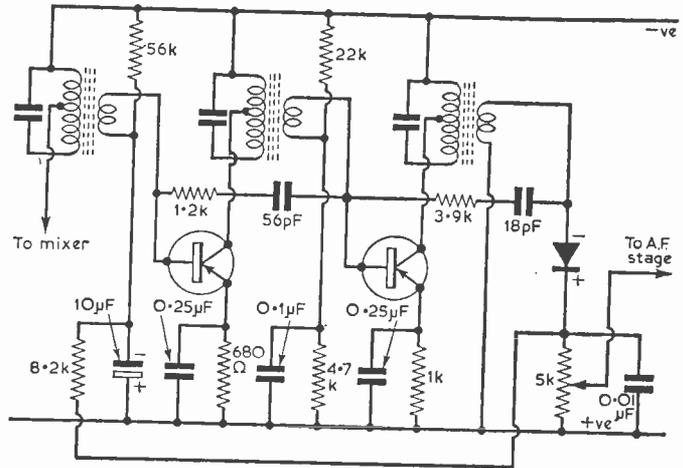


Fig. 1—A typical transistorised I.F. amplifier circuit.

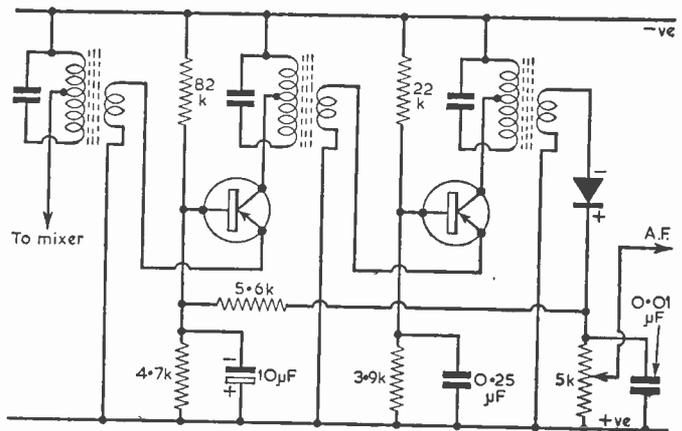


Fig. 2—An I.F. amplifier in which the transistors are used in the common base mode.

lator stages satisfactorily, even if the I.F. does not fall exactly at 470kc/s, or the correct frequency; if the frequency is much in error, correct ganging of aerial and oscillator circuits may be impossible.

When the I.F. transformers are adjusted without the aid of a signal generator, check that no core is fully in, or too far out. If one of the cores is not in the correct position, all of the cores should be readjusted by an approximately similar amount, and the stages are then realigned for best results at the new frequency.

# I.F. Stages

## Neutralisation

Neutralisation is generally required, to maintain stability. In Fig. 1, the 1.2k resistor with 56pF condenser, and the 3.9k resistor with 18pF condenser form the neutralising circuits.

The values required can only be varied by a very small amount, if sufficiently accurate neutralisation is to be achieved. The values also depend on the transistors, and are a function of the transformer ratio. This means that with a given circuit, neutralisation can only be ensured if the transistors, I.F. transformers, and values in the neutralising circuits are as specified.

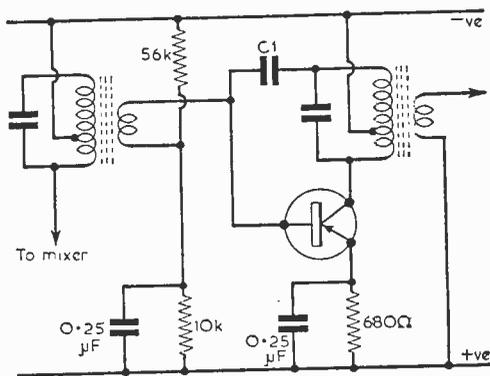


Fig. 3—An alternative neutralisation circuit.

As accurate values are so necessary, components of 2% tolerance may be specified. Individual 5% or wider tolerance components could be suitable, but other samples might be too far from the correct value, so that neutralising is incomplete. The overall feedback is small, and can easily be modified by stray capacity in wiring, especially if leads are long, or base and collector wires are close together.

If the receiver breaks into oscillation when the I.F. transformers are being adjusted for maximum sensitivity, this indicates instability in this section. This oscillation may appear as a continuous whistle or heavy background hiss, or it may only arise when tuning through a weak station. If the instability ceases on tuning in a powerful signal, so that AVC reduces gain, or if it ceases with one or more I.F. transformers only very slightly de-tuned, its cause is probably not serious.

## Common Base Circuit

A typical I.F. amplifier of this type is shown in Fig. 2. The gain can be expected to be less than with the common emitter type. This circuit is given because it will be found in some receivers. Each base is supplied through a potential divider, and is earthed to intermediate frequencies by the condensers wired from the base to the positive line.

The emitters are connected directly to the transformer secondaries, these components being designed for this type of circuit.

## Decoupling

In Fig. 1, each emitter resistor is by-passed with a 0.25μF condenser. In midget sets, lower values, such as 0.1μF or 0.04μF, may be encountered. These lower values usually give an increased possibility of instability, which may show as oscillation, motor-boating, or whistles on weak signals only. In such cases, it may be worth increasing the by-pass values. This can easily be done by temporarily wiring a larger capacity condenser in parallel with the existing condenser. If this cures the trouble, the larger value may be permanently incorporated.

In Fig. 1, the first I.F. transformer secondary is decoupled by the 10μF condenser. A large value is required here, as audio frequencies will be present in the automatic volume control line from the diode. Such condensers may deteriorate, and need replacing when they no longer offer a low-impedance path for intermediate frequencies. If so, a 0.1μF or similar condenser may be shunted in parallel.

In the second stage, a 0.1μF condenser is used, in parallel with the 4.7k resistor. Midget receivers may use 0.04μF here, but 0.1μF or 0.25μF can often be more suitable. If the I.F. stages are unstable, the capacity can be temporarily increased, to see if results improve, as already mentioned.

## Modified Neutralising and By-passing

In some circuits, neutralisation is obtained by using a small capacity, C1 in Fig. 3, from transformer to base. The value will depend on the transistor, but may be in the region of 5pF. Such small capacities are sometimes obtained by means of twin insulated wires, or a twin-lead wire, reduced in length until the required value is reached.

When the neutralising condenser is in this position in the circuit, its value is not influenced much by the transformer ratio, but will depend on the transistor, and position of the I.F. transformer primary tap.

In some circuits, by-pass condensers are not taken to the earth line afforded by the battery positive circuit. Instead, the by-pass condensers for any

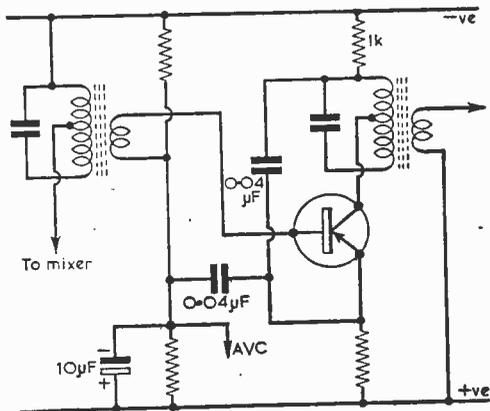


Fig. 4—An example of a circuit in which the by-pass condensers are taken to the emitter of the transistor instead of to the positive line.

stage are taken to the emitter of the transistor, as in Fig. 4. This can be a little confusing, if not expected, but otherwise the circuit is practically the same as that in Fig. 1.

**Diode Detector**

Receivers of this type use a diode, as detector, and to provide AVC. If this diode has a low efficiency, good results will never be achieved. If no means of testing the diode are to hand, and it is suspected, it should be replaced by a new one such as the OA81 or GEX58.

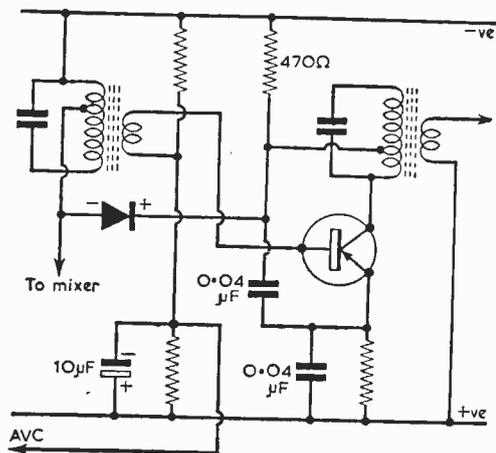


Fig. 5—The typical circuit arrangement for a damping diode.

The diode must be wired in the right way round, as shown. When signal strength increases, an increased positive voltage is developed at the positive end of the diode (Fig. 1). This is transferred to the first I.F. stage, through the 8.2k resistor, and makes the base voltage more positive, reducing amplification. This provides some measure of AVC (Automatic Volume Control) action, but the effect is much less than with most valve receivers.

If the set is stable on loud signals, but unstable on weak signals, this probably arises from the AVC action, as already explained. That is, the instability is not severe, so that the reduced gain on a strong signal temporarily clears the fault.

Some receivers employ a damping diode, in addition to the AVC diode. One method of connecting this is shown in Fig. 5. The collector current through the 470Ω resistor results in the positive end of the damping diode being slightly positive, and the diode has little effect on the mixer I.F. transformer, but, when signal peaks exceed the damping diode potential, the diode conducts, loading the transformer and reducing gain. This gives increased AVC efficiency, and in particular avoids overloading on very strong signals.

**Reflexed Amplifier**

A circuit similar to that in Fig. 6 is used in some receivers. Here, one transistor acts as both I.F. and A.F. amplifier. This gives improved results, from a given number of transistors, but is somewhat less effective than the use of separate transistors.

In this circuit, the first I.F. transformer secondary is by-passed to the emitter (see Fig. 4) by the 0.01μF condenser. Instability at intermediate frequencies may arise from this condenser being defective or disconnected. The primary of the second transformer is similarly decoupled to the emitter. The values used (0.01μF) are rather small, but cannot very well be much increased, because they are in parallel with the audio signal, and thus reduce top response.

After detection in the normal way, by the diode, the signal passes from the 5k volume control slider, through the 6μF condenser and 3.9k resistor, and the secondary of the I.F. transformer, which has negligible impedance at audio frequency. The transistor then acts as an A.F. amplifier, and the A.F. signal is developed across the 1.2k resistor.

A large emitter by-pass capacity (50μF) is required, as this stage is acting as an amplifier at audio frequencies, as well as intermediate frequencies.

Oscillation at audio frequency is not very likely. The stage can be tested at A.F., if necessary, by temporarily disconnecting the diode, and feeding in an A.F. signal from an outside source.

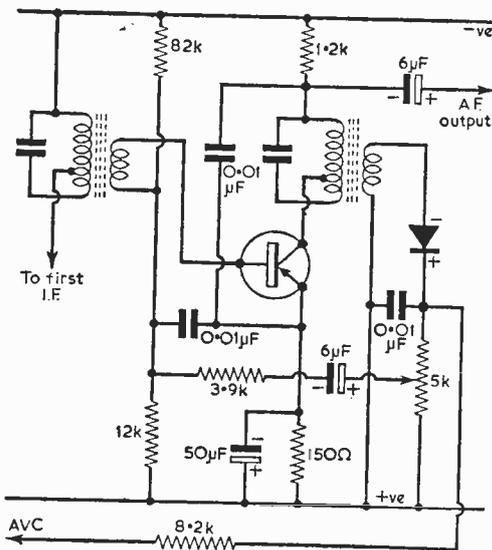


Fig. 6—A reflexed circuit—here, one transistor is used to amplify both I.F. signals and A.F. signals.

After any of the points described have received attention, it should be possible to adjust the I.F. transformer cores for best results.

If it is necessary to connect the generator directly to the receiver, this may be carried out by taking a 0.01μF or similar isolating condenser to the base of the first transistor (the mixer). If the generator signal is taken to a transformer or collector circuit, the core will probably need slight readjustment after the generator lead is removed.

The transistors used in such stages should have a cut-off frequency of 5Mc/s or higher, so reliable transistors, designed for such purposes, should be employed. General lack of sensitivity may arise from poor transistors in these stages.

## UNIQUE COMMUNICATIONS RECEIVERS

Never before offered in this condition, brand new and unused in original Army transit cases.


**MARCONI C.R. STOCK 100/8** covers 60 Kc/s to 30 Mc/s. Complete with all valves, instruction manual and internal A.C. power unit for 200/250 v. **ONLY £35** (carr. etc. 40/-).

**NATIONAL H.R.O. SENIOR** covers 480 Kc/s to 30 Mc/s. Using 6 general coverage plug-in coil sets. Complete with all valves and instruction manual, uses external power unit (available 5/6 extra, P.P. 4/-).

**ONLY £25** (carr. 30/-).

All receivers tested and guaranteed perfect working order before despatch. Further details on each sent on request.
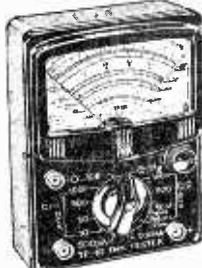
## TEST METERS FOR EVERY PURPOSE & POCKET



**2,000 O.P.V. MODEL TP-10.** Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output Jack for Audio Measurements. Size 3 1/2 in. x 5 in. x 1 1/2 in.

£8.19.6



**20,000 O.P.V. Model TP-5S.** Reads voltages up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 1,000 o.p.v.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in.

£5.19.6



**30,000 P.O.V. Model 500.** Volts to 1,000 D.C. at 30,000 O.P.V.; A.C. at 20,000; 12 Amps D.C. Current; 60 Megs Resistance; -20 to +56 Dbs; Internal buzzer short circuit warnings. Size 3 1/2 in. x 6 1/2 in. x 2 1/2 in.

£8.19.6

All New Stock, with leads, prods, and internal batteries. Fully guaranteed. Details S.A.E.

**CRYSTAL CALIBRATOR No. 10.** A superb Crystal Controlled Wavemeter just released by the Ministry of Supply. Has directly calibrated dial for nominal coverage of 1.5-10.0 Mc/s but may actually be used from 500 Kc/s. up to 30 Mc/s. Complete with 500 Kc/s. Crystal, 2 valves type 1T4, 1 or 1R5 and 1 of CV286 (Neon Stabiliser), and instruction Book. Size 7 in. x 7 1/2 in. x 4 in., weight 5 lbs. Used but in first class condition. **ONLY £2.19.6**, Carr. 3/6.

**B.C. 22 FREQUENCY METERS.** The famous American crystal controlled portable frequency measuring standard. Coverage 125 kc/s-20 Mc/s. With original calibration book. Perfect order. Illustrated details on request. **ONLY £16.**


**10/- CONSTRUCTION PARCEL.** 10 yards each of 6 colours wiring wire, solder, 24 each assorted Resistors and Condensers. **RESISTORS.** 100 assorted values. **NEW 10/- CONDENSERS.** 100 assorted mica and silvermica. **NEW 1/6. SPRAGUE CONDENSERS.** Metal cased, wire ends. New 0.01 mfd. 1,000 volt, and 0.1 mfd. 500 volt. 7/6 per dozen. Special quotes for quantities.

**MINIATURE MOTORS.** Ideal for models. Operates on 3-8v. D.C. Size 1 1/2 x 1 1/2 in. plus 1/4 in. spindle. Brand New 5/-.


### PCR COMMUNICATIONS RECEIVERS

Manufactured by Pye & Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of I.F., using 6 British I.O. type valves. Large 180 degrees illuminated and Calibrated Dial. Flywheel Tuning with locking device. Aerial Trimmer. Tone and Vol. Controls. Band Switch from panel jacks for speaker or phones. In black metal case, size 17 in. L x 8 in. H x 10 in. D. Model PCR covers 6-18 Mc/s. 200-550 metres and 850-2,000 metres and has internal 5 in. speaker. REME reconditioned as new. £6.19.6. Model PCR2 has similar L & M waveband coverage. Short wave 6-22 Mc/s. but no speaker. Used, but excellent condition £5.19.6. Every receiver aerial tested before des. Add 10/6 carr. all models. Any set can be fitted with bulky EXTERNAL power supply, but NAL PACK for 200/250 v. A.C. at an extra cost of £2. S.A.E FOR ILLUSTRATED LEAFLET
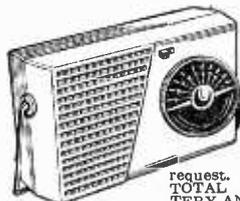
### "P.W." 6 TRANSISTOR PERSONAL RECEIVER



Designed by the technical staff of Practical Wireless; easy to build, using printed circuit and 1st Grade Matched Transistors and Diode. Full Medium and Long Wave coverage to internal speakers. All parts sold separately (new components only) enabling you to buy as required and full detailed price list will be sent on request. Constructional details 1/6. **TOTAL COST INCLUDING BATTERY AND CABINET £8.19.6.**

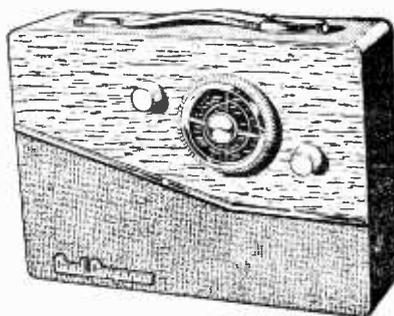

### THE "GOOD COMPANION"

THE FINEST COMBINED PORTABLE & CAR RADIO YET DESIGNED FOR THE HOME CONSTRUCTOR

- ★ 750 mW output.
- ★ 6 transistors and 2 diodes.
- ★ Full Medium and Long Wave coverage.
- ★ Quality speaker.
- ★ Pre-aligned I.F.T.'s.
- ★ Brilliantly styled 2 tone cabinet, size 11 x 8 x 3 ins.
- ★ Very fine tuning with calibrated dial.
- ★ Latest printed circuit.
- ★ Internal high gain aerial, with car aerial socket.
- ★ Easy to follow construction data (available separately 3/6).

All parts sold separately and full illustrated details will be sent on request.

**£9.19.6** plus 5/- post and ins. (Battery 3/6 extra.)

### "POCKET 4" TRANSISTOR RECEIVER

Attractive cabinet as illustrated for "P.W. 6". Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components for only 42/6 (p. & p. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.

**HARRIS ELECTRONICS** 138 Gray's Inn Road, London, W.C.1  
(LONDON) LTD (Phone TERminus 7937)

Please include carriage costs on all items (Open until 1 p.m. Saturdays). We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.

# COMPACT HI-FI

by *Armstrong*


STEREO 55 £33.15.0

(illustrated)
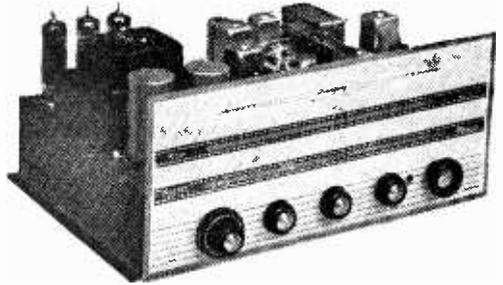
## TUNER-AMPLIFIER CHASSIS

A comprehensive and attractively styled chassis combining AM and FM Tuners, a Stereo Control Unit and two High Fidelity 5 watt Amplifiers in one compact unit. In all its functions the Stereo 55 is designed for mono as well as stereo use so that up to 10 watts output is always available.

Full VHF and medium bands. ● Inputs for tape recording and playback. ● Alternative pick-up inputs. ● Booster unit available for low output pick-ups. ● Input for possible future stereo radio. ● Separate bass and treble controls and dual volume control for ease of balance. ● Free instruction booklet with every model.



STEREO 12 Mk. 2 £44.15.0

A total of 16 watts output is available from the two 8 watts push-pull amplifiers. VHF, with automatic frequency control, medium and long bands. Inputs for tape recording and playback and for stereo radio if required in the future. The most comprehensive unit ever produced, a hi-fi system on one compact chassis.

AM/FM Mono Chassis are also available.

The name ARMSTRONG is the registered trade mark of ARMSTRONG WIRELESS & TELEVISION Co. Ltd. WARLTERS ROAD, LONDON, N.7. Tel.: NOR 3213

Post this coupon or write for free catalogue, or call at our Showroom for full demonstration and professional advice on your installation. Open 9—5 including Saturdays.

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 PFC

## Introducing the New ▶

We proudly claim that this highly efficient and compact signal generator is the finest value in instruments anywhere in the world.

Designed after months of research in our own laboratory, and custom-built to the highest standards in our own factory.

### NOTE THESE FEATURES!

- ★ Compact and portable—height only 4½"
- ★ Truly lightweight—under 2 lbs.
- ★ Operates from standard transistor battery.
- ★ Fully transistorized—negligible consumption.
- ★ 8 ranges, fully covering 200 Kc/s—220 Mc/s.
- ★ Accuracy better than 2% (average 1%).
- ★ Modulated or unmodulated R.F. output—100 mV.
- ★ Audio output, sine wave, approx. 1000 Kc/s.


COMPLETE WITH OUTPUT PLUG ONLY

Send your order in now for earliest possible delivery.

S.A.E. for leaflet.

Trade and Export Enquiries Invited

## NOMBREX

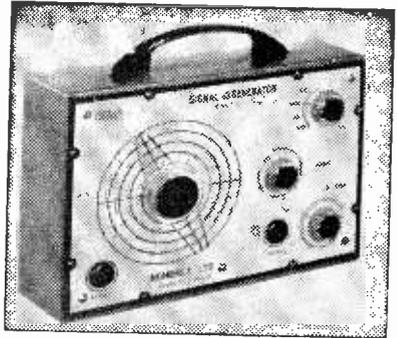

TRANSISTORIZED WIDE-RANGE SIGNAL GENERATOR 27  
 200 Kc/s to 220 Mc/s.

RETAIL £7.10.0 P. & P. 3/6  
 Battery 2/-


Cash with order. Regret no C.O.D.

Deliveries Commence 10th Jan.

All orders in strict rotation.

**NOMBREX LTD.** Instruments Division 20

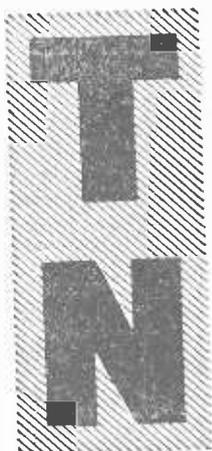ESTUARY HOUSE, CAMPERDOWN TERRACE, EXMOUTH, DEVON. Phone: 3515.



# Trade News

## NEW WIDE RANGE OF 1.5W ZENER DIODES FROM G.E.C.


THE SZA/C series of silicon zener diodes made by the General Electric Co. Ltd., formerly of  $\pm 10\%$  tolerance, now has a nominal tolerance of  $\pm 5\%$  and ranges from 5.6V to 33V. Maximum mean power dissipation at 40°C is 1.5W and the diodes are enclosed in a double-ended case with wire leads and a threaded base.

The diodes are numbered SZ56A to SZ91A and SZ10C to SZ33C with nominal zener voltages of 5.6V to 33V, graded according to the international preferred values of the 10% increment series.

The General Electric Co. Ltd., Semiconductor Division, School Street, Hazel Grove, Stockport, Cheshire.
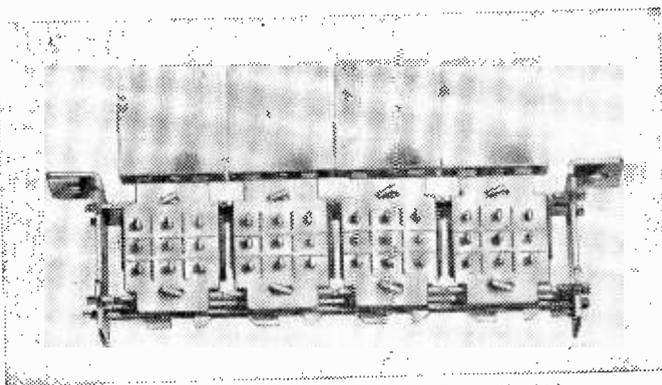
## MINIATURE PUSH BUTTON SWITCH

THE Plessey Company Limited announces the introduction of a miniature push button switch which is available with one to twelve buttons. The switch is of a compact design which makes it highly suitable for inclusion in small domestic radio receivers, tape-recorders, etc. Each button can provide up to 6-pole change over switching per side, giving a possible total of 12 poles per button.




A new push button switch from the Plessey Co. Ltd.

The switch is available for standard chassis mounting or for printed circuit applications.

This switch is made by *The Plessey Co. Ltd., Ilford, Essex.*
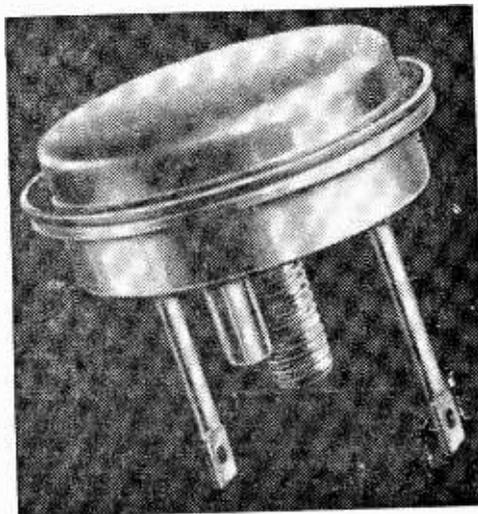
## NEW TRANSISTORS

THE NKT 501-504 series of transistors, recently announced by Newmarket Transistors Ltd., are very high current, high power, pnp alloy-junction germanium components, designed for amplification, control and switching applications in the industrial and services field.



One of the new range of transistors from Newmarket Transistors Limited.

There are four types, ranging from the NKT501, a high-voltage, very high-current transistor with a voltage rating of 60, to the NKT504, a medium-voltage, high-current transistor with a voltage rating of 30.


The distinguishing features of the NKT 500 range are the very high current ratings (up to 25A), a guaranteed minimum current gain of 12 at the maximum rated collector current, high power rating and voltage ratings of 60 and 30. The low saturation voltage results in low self dissipation when used for switching applications. The drive voltage for peak collector current is low and distortion is minimised by controlled beta fall off.

These transistors are manufactured by *Newmarket Transistors Limited, Exning Road, Newmarket, Suffolk.*
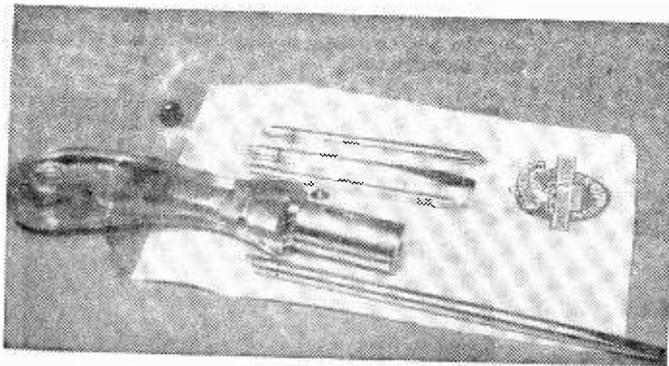
## MULTI-BLADE RATCHET SCREWDRIVER

A MULTI-BLADE ratchet screwdriver has been added to the Darwins Tool Division range of J. Stead and Company Limited.

The screwdriver has an amber plastic pistol-grip handle and it is supplied in a plastic wallet with four blades: electricians' type; engineers' type, and Nos. 1 and 2 cross-point types. The latter two blades are of special use to the amateur TV enthusiast who services his own or his friends' TV sets, since cross-headed screws are often found in the chassis construction of TV receivers.



A multi-blade ratchet screwdriver made by J. Stead and Co. Ltd.


The complete screwdriver with four blades costs 19s. 6d. from most hardware and tool dealers. Replacement blades can be obtained at 2s. 3d. each. J. Stead and Co. Ltd., Manor Works, Cricket Inn Road, Sheffield 2.

#### MINIATURE SOLDERING TWEEZERS

A NEW type of soldering instrument has recently been developed to meet the need for precision soldering in laboratories and on production lines with micro-miniature circuits modules, diodes, transistors, relays, etc.

Designed, developed and manufactured in the U.K. by Oryx Electrical Laboratories Ltd., the instrument is in the form of a pair of tweezers having separate heating elements to both tips. The elements operate at up to 554°F tip temperature from 6V supply.

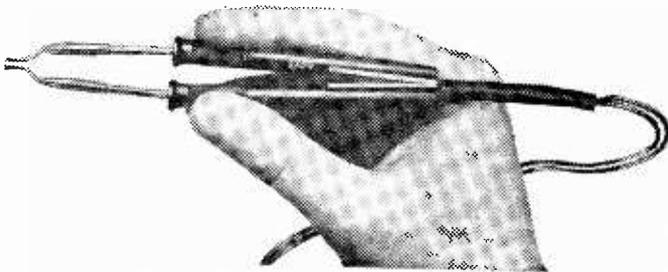Light to handle and requiring only minimum finger pressure, these tweezers provide unobstructed view at all times for close precision soldering. These soldering tweezers are marketed in the U.K. by W. Greenwood Electronics Ltd., 667 Finchley Road, London, N.W.2.



Oryx soldering tweezers

#### CERAMIC-CASED TUNNEL DIODES

THE operating frequency of tunnel diodes has been raised by a technique of miniature ceramic encapsulation developed by Standard Telephones and Cables Limited.

The extremely small size of these new devices and their tab-ended configurations, have reduced their inductance to such an extent, that a typical limiting frequency of oscillation of 900Mc/s is now attainable.

A single version, known as the JK30A, is now in production. It is being followed by a new version incorporating a matched pair of tunnel diodes and forming a single integral unit having three tabs. These units are matched for peak current and capacitance and are intended for applications in the computer field. They may be used in high speed logic and counting circuits or as the threshold amplifier/gate at the input of a pulse amplifier. Standard Telephones and Cables Limited, Connaught House, Aldwych, London, W.C.2.

#### 5-DIGIT VOLT/OHM METER

A NEW addition to the Ferranti range of digital instruments is the type D201, 5-digit volt/ohm Meter. This instrument, which makes extensive use of semiconductor elements, has been designed to measure D.C. voltage and resistance over a wide range to an accuracy of better than 0.03% of reading of  $\pm 3$  digits, whichever is the greater.

The voltage range is 0.0001 to 1000V D.C. and the resistance range 000.01 $\Omega$  to 1299.8k. The ranging is automatic on both inputs, except for the most sensitive range in each instance, which is selected by a "divide by 10" switch. D.C. current can be measured from full scale readings of 1.9999 $\mu$ A to 1.9999mA after slight modification to the instrument. The conversion time is normally 250 milliseconds—irrespective of reading—and the input impedance is 4.44M on all ranges, although this can be increased to 10M if required.

Servicing of the instrument has been simplified by using detachable sub-units which are easily maintained, printed circuit cards being used for the transistor circuitry.

The instrument is housed in a cabinet measuring 20in.  $\times$  15in.  $\times$  14in. and weighs 35lb approximately. A rack mounted version is also available.

The type D201 meter is made by Ferranti Ltd., Ferry Road, Edinburgh 5, Scotland.


# THIS MONTH ONLY !

"SONOTONE" MIN. EARPIECE free with all parts totalling £4.10.0 or over

## TRANSONA-6

(6 Transistors plus 2 Diodes)

M/L & T. BAND

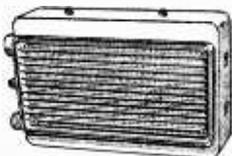

350 Mw XC101's push-pull output Transistors. Powerful magnet 3in. high grade speaker. Push-pull transformers. This is a top performing receiver. Nearly 30 stations listed in one evening including Luxembourg loud and clear. A pleasure to listen to. **FERRITE ROD AERIAL.** All parts sold separately, including pale blue gleaming polystyrene case with duo-diffusion grilles in red. Uses 9 volt battery. Sockets for car aerial.


Total building cost **£5.19.6** P.P. 3/-. Size 6½ x 4½ x 1½in.

"Agreeably surprised with Trawler Band reception. Luxembourg as loud as local. Your easy build diagram helped a lot... my first attempt."—H.S., Penzance, Cornwall (poor reception area). **PARTS PRICE LIST AND EASY BUILD PLANS 1/6**
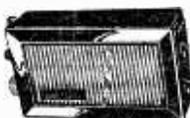
## TRANSONA-4

(4 Transistors, plus 2 Diodes)

Miniature speaker. **FERRITE ROD AERIAL.** MW/LW and Trawler Band coverage down to 80 metres. On test tuned in nearly 30 stations inc. Luxembourg. Easy-build plans 1/3. Handsome pocket case.



May be built for **£2/6** P.P. 3/-.

"Best transistor set I have ever built—dozens of stations."—A.G.H., Deal, Kent. **PARTS PRICE LIST AND EASY BUILD PLANS 1/6**

## BEGINNERS PUSH-PULL FIVE

(5 Transistors, plus Diode)



- ★ 2½in. M/C Speaker
- ★ Ferrite rod aerial
- ★ Tuning condenser
- ★ Volume/oscillator control
- ★ Case with speaker grille in red.
- ★ Fully tunable over med/long waves
- ★ Simple assembly diagrams
- ★ 250 Milliwatts output stage


★ Can be built for **59/6** P.P. 3/- **PARTS PRICE LIST, etc. 2/-.**

With 3" speaker 68/- post free

## BEGINNERS POCKET 5

(MW/LW and TRAWLER BAND)

(5 Transistors, plus 2 Diodes)

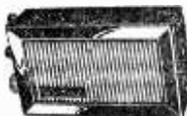

Designed round supersensitive **FERRITE ROD AERIAL** and 3in. speaker. Attractive case in black with speaker grill in red. On test Home, Light, Radio Lux., and many Continental stations we received.


Total cost of all parts **£2.19.6** P.P. 3/-.

**EASY BUILD PLANS AND PARTS PRICE LIST 1/6**
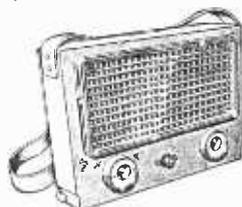
## NOW THE SUPER SEVEN 4-WAVEBAND RADIO

(7 Transistors plus 2 Diodes)

- ★ 3 R.F. STAGES
- ★ Mullard and Surface Barrier Transistors
- ★ Coverage of Medium, Long Waves, Trawler Band and approximately 20-60 metres short wave
- ★ Use as domestic radio, car radio or fit with strap (not supplied) for carry-about.
- ★ No aerial required except for use as car radio and for short waves
- ★ 3-inch speaker but will drive a larger speaker
- ★ Performance comparable to many receivers costing treble
- ★ 400 milliwatts output stage
- ★ Minimum of 30 stations tuned in excluding S.W.




May be built for **£6.19.6** plus 3/6 post, etc. **SIZE: 7½ x 5½ x 1½in.**

**PARTS PRICE LIST AND EASY BUILD PLANS 2/-**
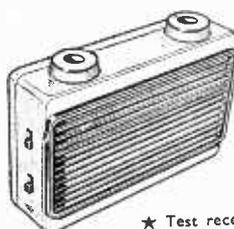
## NEW SUPER SIX DESIGN

MED/LONG WAVES, TRAWLER BAND AND S.W. TO APPROX. 40 METRES



- ★ 6 1st grade Transistors (inc. Mullard and Surface Barrier) plus 2 DIODES.
- ★ Top grade 3in. L/speaker.
- ★ 2 R.F. Stages for extra boost.
- ★ High Q 7in. Ferrite Rod Aerial.
- ★ Easy-build diagrams
- ★ No aerial or earth required (except as car radio).
- ★ Attractive pale blue case with speaker grilles in red.
- ★ 350 Milliwatts output stage
- ★ Sockets for car radio.

★ Test receiver tuned in over 30 stations (inc. Luxembourg loud and clear.)

THIS FINE RECEIVER MAY BE BUILT FOR **£6.9.6** Plus 3/- P.P. **PARTS PRICE LIST AND EASY BUILD PLANS 2/-**

ALL PARTS SOLD SEPARATELY

AFTER SALES SERVICE YOUR PROTECTION

# RADIO EXCHANGE COMPANY

27 HARPUR STREET, BEDFORD

PHONE 2367

(Opposite Co-op)

10 a.m. to 1 p.m. SAT.

ALL TAPE SENT BY RETURN OF POST

**DON'T MISS THIS SUPER QUALITY HI-FI AMERICAN "CBS" TAPE**  
*BRAND NEW AND GUARANTEED*




CIP-8	600ft. 5in.	Standard Play	13/-
LP-9	900ft. 5in.	Long Play	17/6
CMXP-12	1,200ft. 5in.	Double Play	22/-
CIP-9	900ft. 5 1/2in.	Standard Play	18/-
LP-12	1,200ft. 5 1/2in.	Long Play	19/6
CMXP-13	1,800ft. 5 1/2in.	Double Play	31/-
CIP-12	1,200ft. 7in.	Standard Play	25/6
LP-13	1,800ft. 7in.	Long Play	26/6
CMXP-24	2,400ft. 7in.	Double Play	47/-

**SPECIAL "GEE BRAND" TAPE OFFER!** 1,200ft. P. 1/- (2 or more sent post paid.)

Many other types available including "Scotch," "EMI," "Trilon," "Synchronape," B.A.M., etc. Send s.a.c. for our huge money-saving literature on Tapes and Accessories.

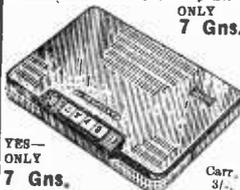**BARGAIN OF THE MONTH!**  
Telefunken Stereo Hi-Fi Amplifier  
**ONLY 7 Gns.**



YES—  
ONLY  
**7 Gns.**

Carr.  
3/6

110/250 v. A.C. input. 5 watt undistorted output (10 watts nominal) size 12 x 9 x 2in., weight 9lb, illustrated leaflet available.

**CRYSTAL MICROPHONE**

**MODEL BM.3**  
Three-way mike for hand, desk or floor stand use. Response 100-8,000 c/s. Sensitivity —62dB. Length 7in. Head dia. 1 1/2in. Supplied with neckband. Terrific performance. Outstanding value at **ONLY 39/6**. P. & P. 2/-.

**AVO MODEL 7**  
Latest Ministry release of this well-known test instrument supplying 50 ranges of current, voltage and resistance tests. Complete with leads and batteries. Ready for use. Perfect condition. **£11/10/-**. Carr. 5/-.

**SUPER QUALITY TEST LEAD KIT**  
No. 520  
**10/-**



Post Paid  
Comprises leads and prods, English and Continental type plugs, spade terminals and crocodile clips. Complete in attractive case

**TELESCOPIC FLOOR STD.**  
**HEAVY 9in.** chrome chromium base, chromium stand with screw top. Extends to approx. 6ft. Suitable for our mikes, etc.; **£21.50**, Carr. 2/-.

**POCKET TEST METER**  
**MODEL "CASIE H.20"**

(4,000 O.P.V.) FOR **£4** POST FREE

A pocket size individual circuit tester with bakelite panel and metal cabinet. Complete with test leads batteries and ready to use. Ranges: D.C. Volts: 10-50-250-1,000 v. A.C. Volts: 10-50-250-1,000 v. D.C. Current: 250µA/10 mA/250 mA. Resistance: 0-10 K ohms/0-1 M ohms (by 3V internal battery). Decibels: —20 to +22db (0dB — 0.775v. —600 ohms).



size: 4 1/2in. x 3 1/2in. x 1 1/2in.  
Also available: **MODEL TK.50**

1,000 o.p.v. Ranges: D.C. mA: 1-250 mA, D.C. and A.C. Volts: 10-250-500-1,000 v. Ohms: 0-10K ohms 0-100K ohms, **£3.7.6**.


**AVO VALVE TESTER**

Outstanding offer of this fine test instrument. Supplied in good condition. Equipment in two parts—valve panel with selector switch and meter with voltage adjustment controls, etc. 12 valve bases and 3 blanks. Very simple to operate. **ONLY £5.19.8**. Carr. 7/6. (Adaptors available for testing valves not listed). Data Manual 20/- extra. Also complete instrument with data manual and latest type panels with 7B7, 88A and 89A bases. **£10**. Carr. 7/6.

**SPEAKER BARGAIN!**

Goodman's Hi-Fi AX10M 110, 15 ohm Few o.ly at **£4.15.0**. Carr. 3/6. Brand New and Boxed.

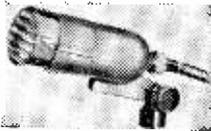**SUPER QUALITY HI-FI DYNAMIC (M/C) MIKE**



with built-in Transformer 200 ohm or 80 k. impedance Suitable for hand or stand use. Complete with screened lead. **OUTSTANDING VALUE** MODEL **£4.15.0** (State M.D.180 imp. reqd.) Post Free

**GEE BROS. (RADIO) LTD**

15 LITTLE NEWPORT STREET, LONDON W.C.2.  
Telephone: GERrard 8794/1453

Adjoining Letchester Square Tube Station Open 9-6 Mon.-Fri. 9-1 Sat.

**SPECIAL FOR THE "HAMS"**  
**RADIO STATION**

*Illustrated*

1/2 Inch detachable bit soldering instrument  
**List No. 70**

Combined Protective Unit with Wiper/Abrasion Pad and Solder Reel  
**List No. 700**


Apply **SALES & SERVICE**



**ADCOLA HOUSE**  
**GAUDEN ROAD**  
**LONDON, S.W.4**

Telephones:  
**MACaulay 4272-3101**

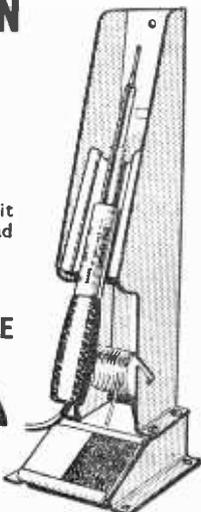Telegrams:  
**"SOLJOINT, LONDON, S.W.4."**




British & Foreign Patents, Registered Designs, etc.

**SOUND REPRODUCERS (LONDON) LTD.**

The **Transtor** Component Specialists  
Dept. P.W. 15, 7 Jephson Road, Forest Gate, London E7. (Mail Order Only)

**AGENTS REQUIRED**

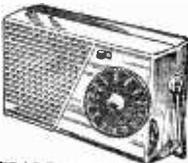

**TRADE SUPPLIED**  
Our well-known **Traveller** is now supplied with printed circuit, 3 top quality transistors, 2 diodes in latest circuitry, **£3.17.6**.

**INTRODUCING... THE ROVER £4.19.6**

The second of our **Transtor** Radio designs. 4 Mullard transistors in a circuit specially designed around the new AF117 diffused alloy R.F. transistor. OCB1D-20C81. Push-pull output on printed circuit. Sensitivity approx. 1 m/v per metre. Air-spaced tuner. Luxembourg guaranteed at excellent volume (if normally receivable).

Both sets of components have following outstanding features. Supplied complete with full Easy-to-follow Instructions. Physical layout and theoretical circuits. 3in. Moving Coil Speaker. Fully tunable on Medium Waves. Ferrite Rod Aerial. Solenoid Wound Coils. Plug in 9 v. Battery. Fully portable. No Aerial or Earth required. All components tested and guaranteed 12 months. Complete satisfaction or money refunded. All components supplied separately. Instruction Book 1/6 post free. Supplied free with set of components. **ALL PARTS and BLUE PLASTIC CASE AS ILLUSTRATED.** Post and packing 3/6. Personal epiexce with instructions 9/-, Battery extra 2s 6d. P. & P. 3/6.

**SNIPS**

G.E.C. SI, 3/6; G.E.C. S3, 3/6; SB078, 8/6; Mullard AF117, 12/6; Matchd. Pr. OCB1 and OCB1D 22/6; 6 ins. Ferrite Rod ± or ±ins., 1/9; Litz Wire 3rd. yd. 5K Edgewise V/C with S/W, 5/-; 32 mfd., 50 mfd., 100 mfd., 1/8 each. Guaranteed 5 ins. 3 ohm Moving coil Loudspeaker, 10/-. Plus P.P. 2/6.

Complete range of Caby Test Meters, prices 54/-, 97/6, 130/-. S.A.E. for Descriptive Leaflets.

# Short-wave Listeners' Log

**T**HE choice of a suitable receiver is not always easy, as prices and specifications vary so much. With home-built receivers, improvements and additions can, of course, be made. There are also a number of current communications receivers available, and full details of these can be obtained from the makers. The price is generally quite high.

When a ready-made receiver of high efficiency, at relatively low cost, is required, a second-hand, used, or surplus model is probably the only choice. Brief details of some of the most popular and suitable receivers of this kind are given here.

R1155. About 16½in. × 9in. × 9in. Seven valves, plus two in unused direction-finding circuit, and magic eye tuning indicator. BFO (beat frequency oscillator for C.W. morse) Needs separate power pack and output stage for speaker. Many cover 17-4000m, with gap between 100 and 200m, but other coverages available. Frequency calibrated dial.

R1224A. About 19in. × 14½in. × 9½in. Battery 5-valver: R.F./F.C./I.F./DET/output, tuning 30-300m in 3 bands. Charts for numbered dial.

CR100 and B28. About 16in. × 16½in. × 12½in. Ten to 5,000m in 6 switched ranges. Frequency calibrated and logging scale. Eleven octal valves. Internal power pack. Controls: Tuning, band-change, pass-band (6,000-100c/s) crystal filter, aerial trimmer, H.F. gain, A.F. gain, BFO, function switch, on/off switch, and noise limiter on some models.

CR150. About 16½in. × 17in. × 13½in. Double superhet model. 5-150m in 5 switched bands. Noise limiter, crystal calibrator, S-meter. Small triode output stage. Separate power unit.

AR88D. About 19½in. × 19½in. × 11in. About 9.5 to 550m in 6 switched bands. Twelve valves, plus rectifier and voltage regulator, full communications facilities. Internal power supply. Companion models with different coverage.

HRO. About 17in. × 11½in. × 8½in. Nine general coverage plug-in coil units over 10 to 6,000m. In some cases special coil units giving bandsread tuning over amateur bands are available. Numbered dial tuning. Ten UX type valves, but octal valves in later models. Separate power pack. BFO, S-meter, and full communications facilities. Some models have fewer coils.

Collins T.C.S. About 13in. × 11in. × 11in. For use with companion transmitter, 25 to 200m. Octal valves. May be run from separate rotary generator.

BC312. About 18in. × 10½in. × 9½in. Nine valves, covering 17 to 200m. BFO and other facilities. Intended for 12V accumulator supply.

Any of these receivers will provide very good results. The band coverage available may be

important, as some receivers have a more limited short wave coverage than others. Those sets which include normal long and medium wave bands will provide very good long-distance reception, on these bands, in addition to covering S.W. bands. Receivers which require a separate power unit, or are intended for accumulator or battery running, are not suitable when a single, self-contained set, for A.C. mains operation, is required. In all cases a separate, moving-coil permanent magnet speaker is necessary.

Actual models naturally vary somewhat in age, condition, and exact details, but it is nearly always possible to obtain a reasonably complete specification in advance.

A brief description of features which will be found in detailed specifications should be helpful. Those generally present are as follows:

### Pass-band Selector

A control giving variable selectivity, typically from 100 to 6,000c/s, in a high-grade set. The very high degrees of selectivity can only be used for C.W. (morse) reception, as a rule.

### Function or Operation Switch

A control bringing the AVC in or out, possibly bringing the BFO in, for C.W. reception, and leaving the receiver standing by with heaters on but H.T. off.

### H.F. or R.F. Gain

Control of the R.F. stage or stages, and possibly the I.F. stages.

### A.F. Gain

The usual type of audio volume control.

### BFO Pitch

Control adjusting the pitch of the beat frequency oscillator, to give best results through interference when receiving C.W. (morse).

### Crystal Filter or Phasing Control

This allows adjustment of a crystal filter, giving high selectivity, and allowing an interfering C.W. signal to be rejected or reduced.

### Aerial Trimmer

A control, frequently panel operated, allowing the first circuit to be trimmed manually, to compensate for stray aerial capacity.

JOIN THE PRACTICAL GROUP	
PRACTICAL TELEVISION ... ..	1/9
Every Month	
PRACTICAL MECHANICS ... ..	1/6
Every Month	
Devoted to Mechanics, Science and Invention	
PRACTICAL MOTORIST ... ..	1/6
Every Month	
PRACTICAL HOUSEHOLDER ... ..	1/3
Every Month	

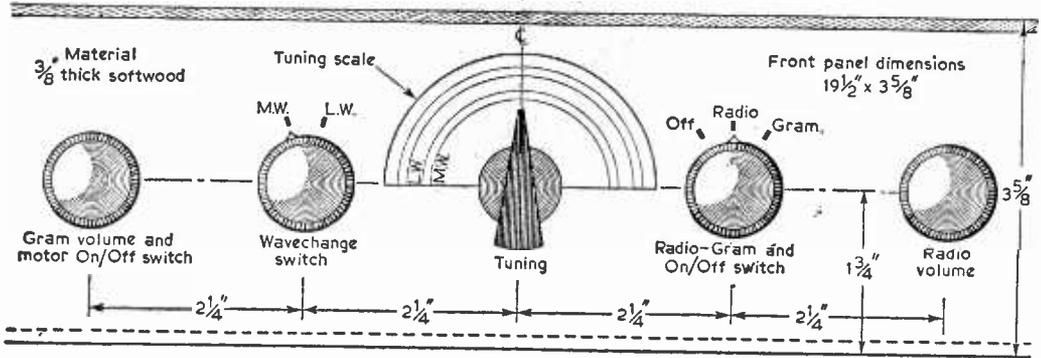


Fig. 24—The layout of the front panel of the radiogram.

## Wiring the three sections of the

# CITIZEN

## together, to form the complete radio or radiogram

(Continued from page 817 of the January issue)

LAST month, the construction of a cabinet for the 'Citizen' was described; it now remains to describe the mounting and inter-wiring necessary when the units are incorporated in the cabinet. The cabinet described last month was designed to provide a modern housing for the 'Citizen' and a battery record player to make a complete battery-operated radiogram. However, for those readers who require only a battery operated radio set, the wiring needed to connect the 'Mini-Amp' to the two units of the 'Citizen' will also be described.

### Wiring for the radiogram

Before this can be carried out, the 'Citizen' must be tested and aligned as described in the December issue (on pages 718 and 719). It is very important that the units should work correctly before starting to mount them in the cabinet.

The control panel of the radiogram is shown in Fig. 24. From this it can be seen that six control knobs are provided. There are: a 'gram volume and

'gram motor on/off switch (this switch ensures that the 'gram motor cannot be left running when the radio is in use); a wavechange switch; a tuning condenser; a three-position switch for radio/gram change-over and (in the third position) radio off switch, and a radio volume control.

(Continued on page 941)

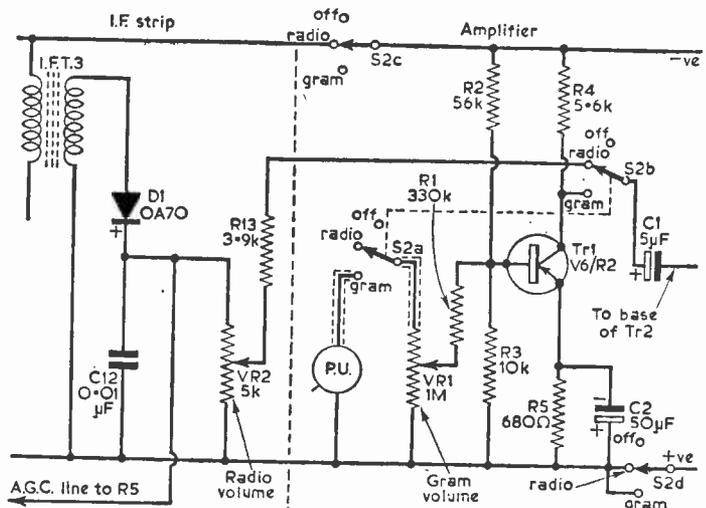


Fig. 25—The theoretical diagram of the connections needed for wiring the units as a radiogram.

**Easy-to-build kit-sets of**



**highest quality at lowest cost**

**THE "MOHICAN" GENERAL COVERAGE RECEIVER Model GC-1U** Fully transistorised, 4 piezo-electric transistors. Excellent portable or Fixed Station receiver for the amateur and short-wave listener. **£38.15.0**

**SHORT-WAVE TRANSISTOR PORTABLE Model RSW-1** Extending aerial, leather case, four band (2 short-wave, Trawler and Medium). **£22.10.0**

**6-TRANSISTOR PORTABLE Model UXR-1** Pre-aligned I.F. transformers printed circuit, 7 x 4in. high-flux speaker. Real hide case. **£14.18.6**

**DUAL-WAVE TRANSISTOR RADIO UJR-1** This sensitive headphone set is a fine introduction to electronics for any youngster. **£2.16.6**

**HI-FI F.M. TUNER** Tuning range 88-108 Mc/s. For your convenience this is available in two units sold separately: Tuning Unit (FMT-4U) with 10.7 Mc/s I.F. output **£3.5.0** (inc. P.T.) I.F. Amplifier (FMA-4U) complete with cabinet and valves **£14.16.0** (£11.11.0).

**HI-FI 16W STEREO AMPLIFIER Model S-88** 20mV. basic sensitivity (4 mV. available, 716 extra.) Ganged controls. Stereo-Monaural gram. radio and tape recorder input. Push-button selection. Two-tone grey metal cabinet. **£26.12.6**

**6W STEREO AMPLIFIER Model S-33** 3 watts per channel, 0.3% distortion at 2.5 w/chn 20dB N.F.B. Inputs for Radio (or Tape) and Gram. Stereo or Monaural, ganged controls. Sensitivity **£12.8.6** 200 mV.

**TRANSCRIPTION RECORD PLAYER, GL-58** Goldring—Lenco four speed unit. G.60 pick-up arm and infinitely variable speed adjustment between 33½ and 80 r.p.m. with fixed speed at 16 r.p.m. Balanced turntable (3½ lb.). Stereo. **£20.12.2**

**HI-FI SPEAKER SYSTEM Model SSU-1** Ducted-port bass reflex cabinet "in the white". Twin speakers. With legs, **£11.18.6** **£10.17.6**

**"COTSWOLD" HI-FI SPEAKER SYSTEM KIT** Acoustically designed enclosure "in the white" 26 x 23 x 15½in., housing a 12in. bass speaker with 2in. speech coil, elliptical middle speaker and pressure unit to cover the full frequency range of 30-20,000 c/s. Complete with speakers, cross-over unit, **£21.19.0** level control, etc.

**COMPLETE MATCHED STEREO OUTFIT** includes record player, amplifier and twin speaker systems (pedestal speaker legs optional **£2.2.0** extra). **£44.9.4**

**STEREO CONTROL UNIT USC-1** Luxury model with press-button inputs to suit any pick-up or tuner and most tape-heads. Output 1.3 v. R.M.S. per channel. Printed circuit construction. **£18.18.6**

**MULTIMETER Model MM-1U** Measures wide range of voltage, current resistance and dB in over 20 ranges. Sensitivity 20,000 ohms/volt D.C. and 5,000 ohms/volt A.C. 0-1.5, 1,500 volts A.C. and D.C. 0-150µA, 15 A D.C. Resistance 0.2Ω to 20MΩ. 4½in. **£11.18.6** meter, 50µA f.s.d.



F.M. TUNER

S.33



S.88



DX-40



UXR-1




OS-1



SSU-1



AG.9U

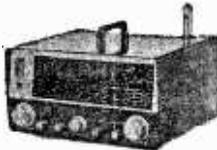

GC.1U

**AMATEUR TRANSMITTER Model DX-100U** Covers all amateur bands from 160-10 metres. 150 watts D.C. input. Self-contained including Power Supply Modulator V.F.O. **£81.10.0**

**AMATEUR TRANSMITTER Model DX-40U** From 80-10 m. Power input 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Compact and self-contained. Prov. for V.F.O. **£32.10.0**

**VAR. FREQ. OSCILLATOR VF-1U** Calibrated 160-10 m. Fundamentals on 160 & 40 m. Ideal for our DX-40U and similar transmitters. **£11.2.0**

**R.F. SIGNAL GENERATOR Model RF-1U** Up to 100 Mc/s fundamental and 200 Mc/s on harmonics and up to 100 mV. output on all bands. **£11.18.0**

**AUDIO SIGNAL GENERATOR Model AG-9U** 10 c/s to 100 kc/s. switch selected. Distortion less than 0.1% 10 v. sine wave output metered in volts and dB's. **£19.19.6**

**VALVE VOLTMETER Model V-7A** Measures volts to 1,500 (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.1Ω to 1,000MΩ. D.C. input impd. 11MΩ. Complete with test prods leads and standardising battery. **£13.0.0**

**Portable 2¾in. SERVICE 'Scope Model OS-1** Compact portable scope ideal for servicing and general work. Y amplifier sensitivity 10 mV/cm; response ± 3 dB 10 c/s-2.5 Mc/s. Time base 15 c/s-150 kc/s. Printed circuit. Case 7½ x 4½ x 12½in. **£19.10.0** Wt. only 10½lb.

**5in. OSCILLOSCOPE Model O-12U** Wide-band amplifiers, essential for TV servicing. F.M. alignment, etc. Vertical freq. response 3 c/s. to over 5 Mc/s. without extra switching. T/B covers 10 c/s to 500 kc/s. in 5 ranges. **£36.10.0**

**RES-CAP BRIDGE Model C-3U** Measures resistance 100Ω to 5MΩ, capacity 10pF to 1000µF, and power factor. Test voltages 5-450 v. **£8.6.6** with automatic safety switch.

**SINGLE CHANNEL AMPLIFIER, MA-12** 10-12 watt Hi-Fi amplifier, low distortion and wide frequency range. **£10.19.6**

**HI-FI EQUIPMENT CABINETS** Range of cabinets available with at least one to suit your particular needs. From small to large, housing Tape Deck, Record Player and full equipment. In the white for finishing to personal taste. **From £11.5.6 to £17.18.6**

**GRID DIP METER Model GD-1U** Coverage from 1.8 Mc/s to 250 Mc/s Complete set of plug-in coils provided. **£10.9.6**

**TAPE RECORDING/PLAYBACK AMPLIFIER Model TA-1** Monaural (TA-1M) **£18.2.6**. Conversion unit to Stereo **£6.10.0**. Stereo (TA-1S). **£23.6.0**

**'PACKAGED DEALS'** of Hi-Fi Equipment including TAPE DECKS, RECORD PLAYERS and DECCA ffs PICK-UPS. Write in to see how these deals save you further money. **All prices include free delivery to UK Deferred Terms available on orders over £10**

Please send me FREE CATALOGUE (Yes/No) \_\_\_\_\_  
 Full details of model(s) \_\_\_\_\_  
 \_\_\_\_\_  
 NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 \_\_\_\_\_

PW2

**DAYSTROM LTD.**

Dept. P.W.2, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

**UNIVERSAL AVOMETERS**

Guaranteed perfect order. Supplied complete with Leads, Batteries and Instructions.  
 Model "1", 34 range ..... £8.19.6  
 Model "7", 50 range ..... £11.10.0  
 Model "8", 20,000/volt ..... 15 Gns.  
 Registered Post 5/- extra.

**P.C.R. COMMUNICATION RECEIVERS**

8 valves. Frequency coverage on three bands: 850-2,000 metres, 180-550 metres, 6-18 Mc/s. Super slow motion drives. A.E. trimmer. AS NEW built-in speaker £6.18.6, carriage 7/6.

P.C.R. 3 Communication Receiver. 190-550 metres, 2-7 Mc/s, 7-23 Mc/s. Output for phone or 3 ohms speaker. AS NEW. 8 trans. carr. 7/6. Both above models are available with Internal Power Pack to operate on 230/250 v. A.C. at 39/6 extra or alternatively plug-in external power units are 35/-.

**R.C.A. AR88D. L.F. RECEIVERS**

World famous, 14 valves. Frequency coverage 75-550 Kc/s and 1.5-30 Mc/s. Operation 110/230/250 v. A.C. Supplied in perfect working order, £32.10.0 each, carr. 30/-.

**NATIONAL H.R.O. RECEIVERS**

Senior Model. Table Mounting. Supplied with a complete set of 9 coils covering 50 kc/s to 30 Mc/s. Perfect condition throughout. 21 Gns. Carriage 15/-. Power Units available, 59/6 extra.

**AMERICAN "C.B.S." TAPES**

First-grade quality. fitted Leader Tape and Stop Foll. Fully guaranteed.

5in., 800 ft. Std. .... 13/-      5 1/2 in., 1900 ft., D.P. .... 21/3  
 5in., 900 ft., L.P. .... 16/6      7in., 1200 ft., Std. .... 7/-  
 5 in., 1200 ft., D.P. .... 18/6      7 in., 1900 ft., L.P. .... 23/6  
 5 1/2 in., 1200 ft., L.P. .... 18/6      7 1/2 in., 2400 ft., D.P. .... 47/-  
 Spare Spool: 3 in., 1/8; 5 in., 2/-; 5 1/2 in., 2/3; 7 in., 2/6.  
 Spool Containers: 5 in., 1/8; 5 1/2 in., 2/-; 7 in., 2/3.  
 Please add Postage. S.A.E. for Full Tape Lists.

**"TRANSISTORS" ALL BRAND NEW GUARANTEED**

EDISWAN MAZDA SPECIAL OFFER. XA103 I.F. 3/6, XA104 I.F. 4/6, XB112 L.F. 3/-, XC141. Power Output 10/-, DRIFT TRANSISTORS. XA121 6/6, XA123 7/6, XA124 7/6, XA125 7/6, XA126 7/6.

MULLARD. OC44 10/-, OC45 9/-, OC70 8/-, OC71 8/6, OC72 7/-, 2OC72 14/-, OC76 7/-, OC78 7/-, OC81D 8/-, OC81 7/-.

SET OF MULLARD TRANSISTORS. OC44, 2 x OC45, OC81D, 2 x OC81 37/6. YELLOW/GREEN. A.F. 3/6, RED/YELLOW. R.F. 4/6. Yellow spot, 2/6. Red Spot, 3/6. White Spot, 3/6.

DIODES. G.P. 6d. OA81 Equiv. 2/-, OA81, 3/-. Postage 6d. extra.

**G. W. SMITH & CO. (RADIO) LTD**

3-34 LISLE STREET, LONDON, W.C.2.

Telephone: GERRARD 8204/9155  
 Hours of business: 9-6. Thursday 9-1. Open All Day Saturday.

**SELENIUM L.T. METAL RECTIFIERS**

Full Wave bridge connected.  
 12/18v. 1A. 4/3    24/36v. 2A. 13/6  
 12/18v. 2A. 6/9    24/36v. 4A. 18/6  
 12/18v. 4A. 9/9    24/36v. 10A. 45/-  
 12/18v. 5A. 12/6    24/36v. 15A. 47/6  
 12/18v. 6A. 13/6    36/40v. 6A. 32/6  
 12/18v. 10A. 22/6    48/60v. 2A. 18/6  
 24/36v. 1A. 9/6    48/60v. 10A. 32/6  
 Please add postage.

**L.T. TRANSFORMERS**

All Primaries tapped 200/250 volts.  
 3-5, 9 or 17 volts. 1 amp. .... 8/9  
 Ditto 2 amp. 14/3. Ditto 4 amp. 18/6  
 12 or 18 v., 6 amp. .... 22/6  
 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or  
 30 volt. 2 amp. .... 18/6  
 Ditto 4 amp. .... 27/6  
 Please add postage.

**FIELD TELEPHONES TYPE F**

Generator ringing. 2 line connection. Supplied complete with Batteries, Wooden Carrying Case. Fully tested. £4.19.6 per pair. P. & P. 5/-.

**CADMIUM SULPHIDE PHOTO CELLS**

Miniature wire ended, extremely sensitive. Brand new with full data. 15/- each. P.P. 6d.

**MINE DETECTORS No. 4A**

Will detect all Types of Metal. Complete equipment with Instructions. 39/6. Carriage 10/6. Batteries 8/- extra.

**COLLARO STUDIO TAP TRANSCRIPTORS**

Latest Model, 3 speeds, 14, 34, 74. Supplied complete with Spare Spool and Instructions. £10.10.0. Carr. 3/6

**BC211 FREQUENCY METERS**

Complete £7.19.6 for callers only.

**4-SPEED SINGLE PLAYERS**

H.S.R. TU9 ..... 75/- P. & P. 2/6  
 Collaro Junior ..... 75/- P. & P. 2/6

**PARMEKO TABLE TOP TRANSFORMER**

230 v. Primary. 620-0-620 v. 250 mA. Tapped 550 and 375 v. 2 x 5v. 3 amp. 45/- P. & P. 5/-

**SPARES KITS FOR CR.100 RECEIVERS**

Contains 15 valves, R & C Kits. Pots. O/P Transl. etc. Brand New. 59/6 P. & P. 3/6

**INSTRUMENT TRANSFORMERS**

PRIMARIES 220/240 v.  
 220 v. 25 mA 6.3 v. 1 amp. .... 10/6  
 220 v. 45 mA 6.3 v. 1.5 amp. .... 11/6  
 Ditto, Half Shrouded, 12/6. Fully Shrouded, 13/- Post extra.

**AUTO TRANSFORMERS**

Step Up, Step Down. 115-200-250 v. 15 w. 9/-, 60 w. 12/6, 150 w. 18/6, 220 v. 45 mA 6.3 v. 1.5 amp. 10/6, £7.10.0, 7500 w. £15. Postage extra.

**PAINTON MINIATURE JONES PLUGS/SOCKETS**

2-pin, 2/6 pr.; 4-pin, 3/6 pr.; 6-pin, 4/- pr.; 8-pin, 4/6 pr.; 12-pin, 5/6 pr.; 18-pin, 7/6 pr.; 33-pin, 10/6 pr. Postage extra.

**Well paid to see the world**

A really interesting and worthwhile job as a Radio Officer in the Merchant Navy awaits you if you are the holder of a current P.M.G. certificate. Salary and allowances are good from the start, rising by regular increments to well over the four figure mark with all found. Your job can take you all over the world, and you get generous annual leave besides off-duty time in foreign ports. Sea service offers ample opportunity to study for further technical qualifications and many well-paid shore appointments are open to you later on.

**A tradition second to none**

Marconi Marine Radio Officers have a long and proud tradition of service extending back to the early years of this century. Among them are to be found names hallowed in the history of the sea. Moreover, many men in the highest public and administrative positions today began their careers as Radio Officers in the Marconi Marine Company.

Write for particulars to: F. E. ASH, Esq.

**THE MARCONI INTERNATIONAL MARINE COMMUNICATION CO. LTD.**

English Electric House, Strand, London, W.C.2

**FRADAN RADIO**

One-Valve Receiver with Bandspread tuning. Covers 20-60 metres. Amazing performance. Can be built in 1 hour. No drilling. All parts supplied. ONLY 39/6 P. & P. 2/6.

Other Plug-in Coils available, 10-2000 metres.



**Introducing:—'THE CALYPSO'**



A 5-stage Transistor Pocket Portable, 6 x 3 x 1 1/2 in. Attractive two-tone Rexine covered case (unbreakable). Genuine 2 1/2 in. high flux loudspeaker. No external aerial needed.

**79/6** Complete kit of parts P. & P. 2/6 extra.

Two-Stage Amplifier, 230-250 volt A.C. 3 watts output at 3 ohms. Using ECL82 and EZ90. Separate Tone and Volume controls. Ready built. Just plug in and use.

Only 63/- P.P. 3/-  
 5in. Loudspeaker 12/6.



36 LEIGH ROAD, LEIGH, LANCs.  
 Personal Shoppers Welcome.

(Continued from page 938)

The effects of the switching can be seen from the circuit in Fig. 25. This shows the output from the 'Citizen' and the input stage of the 'Mini-Amp' and the associated inter-connections. It should be noted that a separate 9V battery is used for the motor of the 'gram deck' to prevent interaction and an unduly short battery life.

**Modification to the 'Citizen'**

The only modification required is the replacement of a fixed resistor by a variable type. The resistor concerned is R10 (the I.F. amplifier on the 'Citizen' blueprint) and this is replaced by an equivalent wire-wound potentiometer to form the radio volume control (VR2 in Fig. 25).

The actual interwiring required in the 'gram cabinet' is shown in Fig. 26. This is a view of the underside of the motor-board and front panel of the cabinet (note that it does not show all of the underside, but only the section where wiring is present). Note that the connection between the two

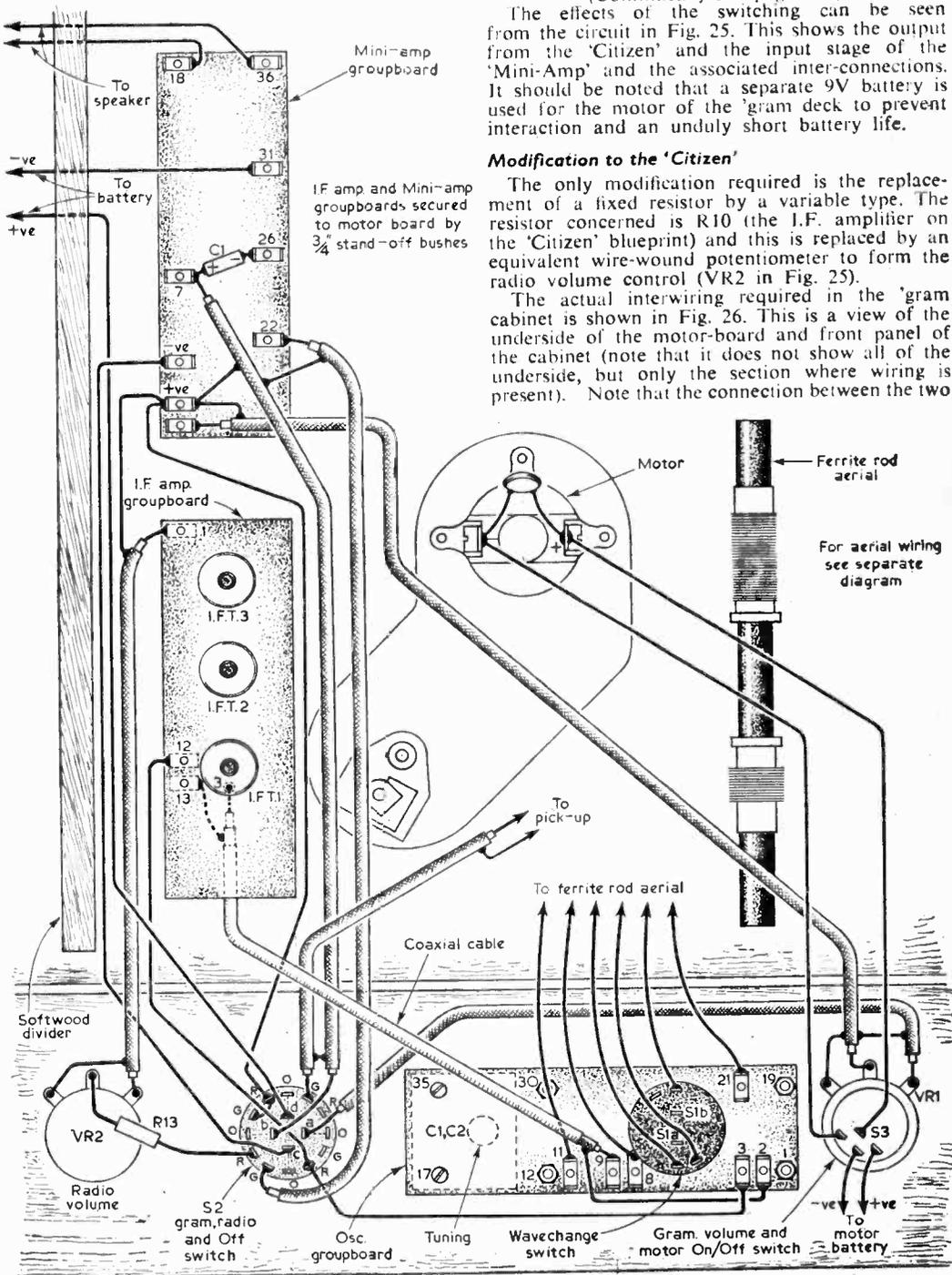


Fig. 26—The radiogram wiring.

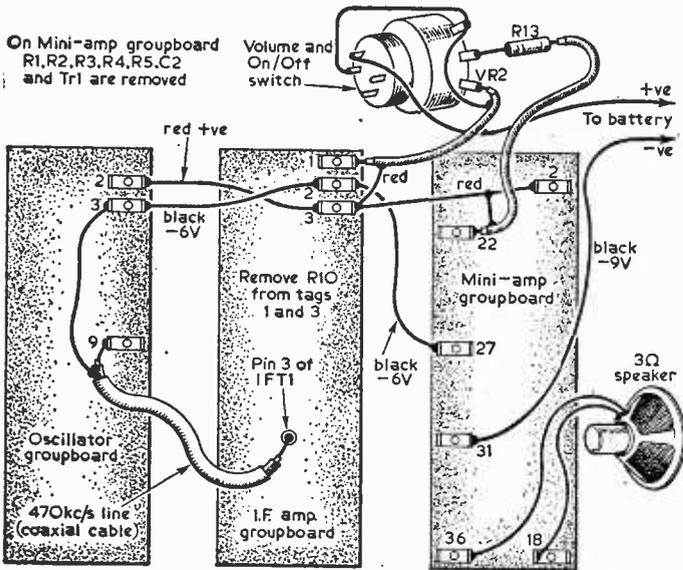


Fig. 27—The interwiring for the tree sections as a radio.

group boards on the 'Citizen' which carries the I.F. signals is made of coaxial cable to reduce the capacity of this link. The wiring of the ferrite rod aerial windings is not shown since it was given earlier (Fig. 17 on page 718 of the December issue). The three tag-boards are mounted by the means of stand-off bushes as stated in Fig. 26. A diagram of the mounting of the oscillator section of the 'Citizen' was given in Fig. 22 in the January issue.

As in the radiogram, the connection between the two group boards on the 'Citizen' which carries the I.F. signals is made of coaxial cable to reduce the capacity which the interconnection places across the I.F. output coil.

When the three units have been mounted in the cabinet (which may be of any form) the alignment should be carried out again.

as good as they were before mounting the units in the cabinet and the alignment procedure may be gone through again now that the units are occupying their final positions. The alignment was described in detail in the December issue on pages 719 and 720—it starts at the side-heading 'The Alignment'.

**The 'Citizen' without the gram unit**

The interconnection for using the 'Citizen' with the 'Mini-Amp' to form a superhet radio set are shown in Fig. 27. The three group boards are shown viewed from the tag sides and not from the riveted sides. As in the radiogram, it is necessary to replace R10 on the 'Citizen' with a variable resistor—see Fig. 28. Since the 'Citizen' gives a high-level output, certain components can be removed from the 'Mini-Amp' and these are listed in Fig. 27. (They are R1, R2, R3, R4, R5, C2 and Tr1.)

## SHORT-WAVE SECTION

(Continued from page 923)

**Conclusion**

Although the unit described is an efficient one it is open to improvements. It would not be difficult, for example, to tune the grid circuit of V1 to improve sensitivity and the spare section of C6 could be employed in this connection, aerial coils being mounted in front of V1 for this purpose above chassis.

**V1 Substitute**

A valve of different type may be used for V1 if desired provided it has variable- $\mu$  characteristics and that attention is paid to the basing which might well be different. A metal rectifier may also be used in place of V3 if preferred and in some cases it might be possible to link the receiver AVC line to the pre-selector.

**NOTE**—The isolating transformer, T1, should not be omitted or exchanged for a heater transformer, neither should the pre-selector be used in conjunction with a receiver of the A.C./D.C. class or danger to life might result.

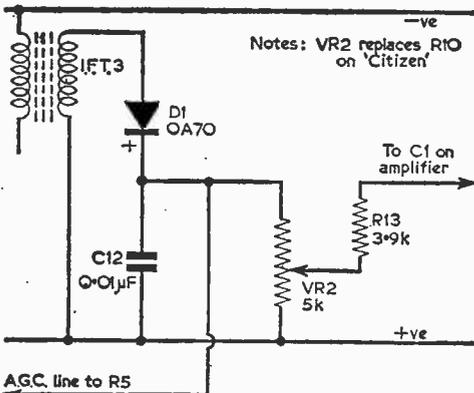


Fig. 28—The circuit of the radio wiring. Note that R4 has been removed.

The inter-wiring can be carried out and then checked most carefully—if, for example, the battery feeding the 'Citizen' and 'Mini-Amp' were wired incorrectly, the transistors would be ruined. Following this check, the unit can be switched on and tested. Results from the radio may not be

# CLYNE RADIO LTD.



18 TOTTENHAM COURT ROAD, W.1  
162 HOLLOWAY ROAD, LONDON N.7  
9 CAMBERWELL CHURCH STREET, S.E.5

MUSEum 5929/0095  
NORth 6295/6/7  
RODney 2875

All post orders and correspondence to 162 HOLLOWAY ROAD, LONDON N.7

## THE COMPONENT SPECIALISTS

OPEN: Tottenham Court Rd., 9 a.m. to 6 p.m. Mon. to Fri., Sat. 1 p.m. Holloway Rd. and Camberwell: 9 a.m. to 6 p.m. daily. Thurs. 1 p.m. Sat. 5.30 p.m. Our Advantageous H.P. and Credit Sale Terms are available on any single item over £5. Your enquiries invited. Please print your name and address.

### The "CLYMAX"




At last a 6-transistor pocket size superhet for Medium and Long Wave at a price you can afford. All required components

ONLY **£6.16.6**

Nothing more to buy! Plus 3/6 P. & P. \* Completely self contained. No external aerial or earth required. \* Full medium wave coverage, plus switched Light programme on Long Wave. \* Push pull output—250 milliwatts. \* Matched set of latest type Mullard transistors. \* Genuine 3in. P.M. Speaker. \* High-Q Coils. \* Ferrite rod aerial with high selectivity. \* Size: 5 1/2 x 3 1/2 x 1 1/2. Two tone cabinet. \* Precision etched printed circuit with components references clearly marked. Alignment service available. All parts available separately. Full assembly instructions and individually priced parts list. 2/- post free.
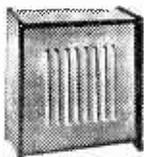
### P.W. "TUTOR"

COMPLETE KIT AS SPECIFIED. Stages 1-4, 65/-, plus 2/- P. & P. All parts available separately. Send stamp for list.



### EXTENSION SPEAKER CABINETS


New design in light oak. Two sizes available. For 6 1/2" or 8" speaker at 22/6. For 10" speaker at 25/- only.

Each plus 2/6 P. & P. Suitable reconditioned 8" P.M. unit at 13/6 only, plus 1/6 P. & P.

Full range of competitively priced new speakers in stock. Ask for list.

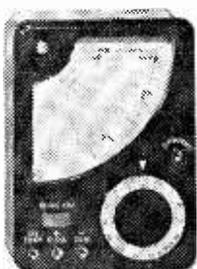
### OUTSTANDING METER IMPORT!

20,000 ohms per volt!  
MODEL 200H. Volt-ohm-Milliammeter




Ranges: A.C. Voltage: 10, 50, 100, 500, and 1000 volts (10,000 ohms per volt). D.C. Voltage: 5-25, 50, 250, 500, and 2.5k. (20,000 ohms per volt). D.C. Current: 0-50 microamps. 0-2.5 mA. 0-250 mA. Resistance: 0-5k, 0-5 meg. (300 ohm and 30k at centre scale). Capacitance: 10 pF to .001 mfd. to .001 mfd. Decibels: -20 to +22 db.

A fully guaranteed pocket size meter (actual size: 4 1/2" x 3 1/2" x 1 1/2") knife edge pointer, top quality supplied complete with test leads and full operating instruction at £8.19.6 ONLY. Post Free. Optional extra. Attractive carrying case 15/- only. (Bona-fide trade enquiries invited.) Leaflet available. ALSO AVAILABLE: MODEL 1F19. Identical in appearance and size with rotary type switch but 10,000 ohms. Ranges: D.C. Voltage: 0-6-30-120-600-1200 volts (10,000 ohms per volt). A.C. voltage: 0-6-30-120-600-1200 volts (10,000 ohms per volt). D.C. Current: 0-30 microamp. 0-3-30mA. Resistance: 0-30k. 0-3 Mez. (150 ohm and 15k at centre scale). Capacitance: 50 pF to 0.01 mfd., 0.001 mfd. to 0.15 mfd. Decibels: -20 to +63 dB in 5 ranges. PRICE £5.19.6. Post Free.

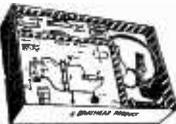
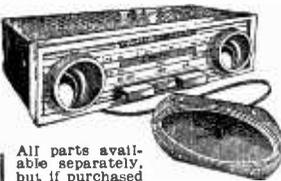
### The "HIGHWAYMAN"

At last a quality Car Radio to build yourself, at an economical price. Look at these features: \* Attractive styling. \* Push pull output. \* 3 latest Mullard transistors plus valves type EBF 83 and ECH 83. \* No Buzz. High Output and sensitivity. \* Printed circuit (newest type). 7" x 4" High flux p.m. speaker. \* Medium and Long Waves. \* Push Buttons for fingertip control. \* Extremely low Battery consumption (less than 1 amp). \* Easy to fit any make car (Positive earth only). \* 12 volt operation. \* Compact size measures only 7" x 7" x 2" deep. \* Easy assembly, supplied with dial and drive already mounted.




All parts available separately, but if purchased at one time, the whole will be supplied at a special

inclusive price of only **£10.19.6** Plus 4/- P. & P.

Parts list and comprehensive instruction booklet 2/6, post free. (Deducted from cost if complete parcel purchased later.)

### "POPULAR FOUR"

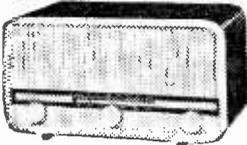

### IMPROVED APPEARANCE AND PERFORMANCE

A new three valve plus miniature contact-cooled rectifier, mains T.R.F. Receiver is now available. New Deluxe Cabinet polished walnut finish, cream trim, attractive horizontal dial (as illustrated). Quality 5in. P.M. speaker. Specially wound high gain super-sensitive Denco coils. Medium and Long Wavebands. Excellent Continental reception! Overall dimensions: 12in. x 8in. x 6in. A.C. 200/250 v. Simple construction with guaranteed results. Easy to follow practical and theoretical diagrams supplied. All necessary components, down to the last nut and bolt, are offered at a SPECIAL INCLUSIVE PRICE OF £5.5.0, plus 3/6 P. & P. 1/6, post free. The same circuit is available in attractive White or Brown Bakelite Cabinet with rectangular dial at 9/7.6 ONLY, plus 3/6 P. & P. ALL PARTS AVAILABLE SEPARATELY.

### LAST CHANCE TO BUY!

The Well-known Brayhead Trans Tronic "SUPER 60" Radio Kit. A complete kit to make your own transistorised Transmitter and Receiver. No soldering reqd. 7 different circuits to build. In original manufacturers coloured box with instructions. Ideal gift for the electronically minded youngster. (As nationally advertised at £5.4.8.) Few only at 48/6. P. & P. 4/-.

### THE "CITIZEN" NEW LOW PRICE 85/-

Our Sensitive 5 Stage (5 transistor plus diode) pocket transistor receiver, for full medium wave reception—with the following outstanding features:



\* Completely self-contained—No external aerial or earth required. \* Genuine 2 1/2in. High Flux P.M. Speaker. \* Push-pull Output—250 milliwatts. \* Genuine Mullard transistors. \* Socket provided for personal listening. \* Socket provided for connection to Car Aerial. \* Volume Control with on/off switch—Condenser tuning. \* Easy assembly on pre-tanged circuit board. \* Attractive red polystyrene cabinet measures 5 1/2 x 3 1/2 x 1 1/2. chrome handle, attractive dial. All required components including full instructions, solder, etc., and battery at special inclusive price of only 85/- (Yes, Eighty-Five Shillings Only!) Plus 2/6 P. & P. Nothing more to spend. Suitable crystal dead-air type miniature earpiece fitted with miniature jack plug at 7/6 extra! if req. All parts available separately. Semised list and full assembly instructions, sent for 1/6 post free. Hear this amazing little receiver working, at any of our branches.

### THE "WAVEMASTER" 7-TRANSISTOR LUXURY PORTABLE

NEW LOW PRICE £9.19.6

400 Milliwatt Output

To build yourself. Medium and Long Waves. Push-Pull Superhet A.V.C. Perfect Car Radio reception on Size 10in.




6 1/2in. x 4 1/2in. at base tapering to 4in. at top. Very attractive two-tone grey/ivory covered cabinet with black and gold printed escutcheon plate, cream and gold knobs, handle and cabinet fittings. \* Weight—with long-life 7 1/2 v. battery—4 1/2 lb. \* Mullard high-grade transistors throughout. \* High-Flux 7in. x 4in. Elliptical Speaker. \* Slow motion tuning. \* Co-axial socket at rear for direct connection to Car Radio Aerial. \* Improved reception by use of five-section plated telescopic aerial disappearing into cabinet when closed. 34in. above Cabinet when fully extended. Construction simplified by Bakelite chassis board with the following components already mounted: I.F. Transformers (3), Oscillator Coil, Trimmer Bank, Output Transformer, Interstage Transformer, Aerial Brackets and Earth Bar. SPECIAL INCLUSIVE PRICE for all required components. Full assembly instructions—nothing more to buy—is £9.19.6, plus 3/6 P. & P. Alignment service available. Full assembly instructions and individually priced parts list, any of which are available separately, 2/6 Post Free.

# HOME RADIO OF MITCHAM

(Dept. P), 187 London Road, Mitcham, Surrey.  
 MIT 3282  
 Shop hours 9 a.m. to 6.30 p.m. Wed. 9 a.m. to 1 p.m.,
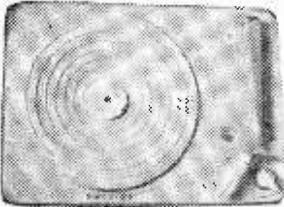
## NEW PHILIPS AG1016 HI-FI STEREO RECORD UNIT




Four-speed playing deck specially designed for the Hi-Fi enthusiast building his own radiogram. Superb reproduction of mono and stereo records of all sizes and speeds. Precision engineered, robust construction, arm lifting and lowering device, negligible wow, flutter, or rumble. Compact and easy to instal. Send for full details and specification. PRICE 13½ gns. Post 3/6.

## P.W. BLUE-PRINTS

ALL PARTS IN STOCK FOR THESE NEW DESIGNS INCLUDING "TUTOR", "MINI-AMP", "CITIZEN", TRANSISTOR SIX, ETC.

DETAILED PRICE LISTS ON REQUEST

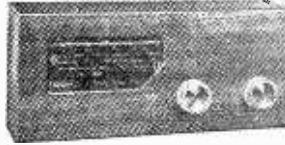


## JASON "ARGUS" A.M. TUNER

Three transistor superhet AM tuner for medium and long waves. self contained high efficiency ferrite rod aerial gives good reception of main continental stations. Complete in neat wooden case size 9 x 4 x 2½ in. Ideal for use with tape recorder, or in conjunction with FM tuner and amplifier to bring in Luxembourg and Hilversum, etc. PRICE OF KIT £7.10s. Post 1/6. All other Jason tuners for FM/VHF also in stock.
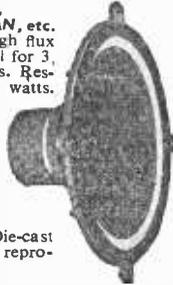
## HIGH FIDELITY LOUDSPEAKERS

FULL RANGE OF GOODMAN'S, WHARFEDALE, WB STENTORIAN, etc. STENTORIAL HF1012 10in. high flux speaker with universal speech coil for 3, 7, and 15 ohms. Die-cast chassis. Response 30 to 14,000 cycles. 10 watts. PRICE £5.2.6 Post 2/-. GOODMAN'S AXIOM 110 Full range 10in. unit with hyperbolic diaphragm giving smooth response 40 to 15,000 cycles. Aluminium voice coil and 12,000 gauss magnet. 15 ohms only. PRICE £5.2.6 Post 2/-. WHARFEDALE GOLDEN 10 Die-cast chassis, foam suspension, superb reproduction as used by B.B.C. PRICE £8.6.7 Post 2/-. SUPER COMPONENT CATALOGUE 2/- Post 1/-



## WE ARE ACTUAL STOCKISTS FOR HEATH KITS

### HEADPHONES

Famous "Royal" light weight high resistance (4000 ohms) headphones. Ideal for crystal sets, short wavers, etc. Brand new boxed 15/- Post 1/6. Also S. G. BROWN type "F" 37/6. Post 1/6.



### TRANSISTORS

Brand new boxed MULARD transistors at new low prices:  
 OC44 11/-, OC45 10/-, OC70 6/6, OC71 6/6, OC72 8/-, OC75 8/-, OC76 8/-, OC78 8/-, OC81 8/-, OC170, 13/6, OC171 14/6, OA70, OA79, OA81 all 3/- each. Matched pairs output transistors and OA79 diodes available. Add 6d. Postage to Order.

# SOLDERING EQUIPMENT

by



## PRECISION SOLDERING for the ELECTRONICS INDUSTRY

Comprehensive range - Robust & Reliable - Light weight - Rapid heating - Bit sizes 3/32in. to 3/8in. - 'Perma-bit' or Copper bits - All voltage ranges 6/7v. to 230/250v. - Prices from 21/-.

Also

- Plastic Cable Strippers
- Miniature Solder Pots
- Heat Guards
- Long Life Bits

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.

ADAMIN—the new range of precision micro-soldering instruments— Have you had details?

Brochure No. S10 sent free on request. Sole proprietors and manufacturers: LIGHT SOLDERING DEVELOPMENTS LTD. 28 Sydenham Road, Croydon, Surrey Phone: CR0ydon 8589 Grams: Litesoid Croydon



# FIVE-TRANSISTOR POCKET RADIO

COMPLETELY PORTABLE NO AERIAL OR EARTH REQUIRED

- ★ Size 4½ x 3½ x 1½ in.
- ★ Output 200m/W
- ★ 5 First quality transistors
- ★ Push-pull output
- ★ Fitted 2½ in. high-flux moving coil speaker



- ★ Medium and long wave
- ★ Internal high gain ferrox aerial
- ★ Twin coloured case in red and black
- ★ All parts available separately
- ★ Circuit-diagram 1/6. Free with parts

PRICE

ONLY £2/19/6 plus 3/6 post and packing

RADIO & TV LTD. (Dept. 5T) High Street, Acton, London, W.3.

# The CONDENSER

This article is expressly written for a particular type of amateur constructor: the beginner who, though perhaps familiar with condensers and their use in practice, may not yet know what a condenser actually is, how it functions as it does and why.

By  
S. R. Vella

**B**EFORE explaining what constitutes a condenser, we have to distinguish between a conductor and an insulator. A conductor allows electricity to pass through it, while an insulator does not. For example, copper, silver and most metals are conductors; while air, mica, glass, paxolin are insulators. A conductor allows electricity to pass through it by virtue of its free electrons (the electrons in its atoms' outer shells).

### The Dielectric

When two conductors are separated by an insulator, we have what is called a capacitor or condenser—a device capable of storing electricity. The insulator separating the two conductors, which might be a vacuum, air, glass etc., is called the dielectric. For the purpose of discussion, let us imagine the two conductors constituting our condenser in the form of two separated metal plates to which are connected suitable lengths of flexible wire so that we can connect them in a circuit as will be explained later on. This arrangement (Fig. 1) constitutes the simplest form of condenser.

It should be noted that the capacity of the condenser (i.e., the ability to store electricity) in Fig. 1 is very small, the condenser being made up simply of two relatively small metal plates with air as the dielectric.

The capacity of a condenser depends on:

- (1) the area of the plates.
- (2) the distance between the plates.
- (3) the material of the dielectric.

The capacity of a condenser increases as the area of the plates is increased and the distance between them is diminished. In practice, the dielectric is

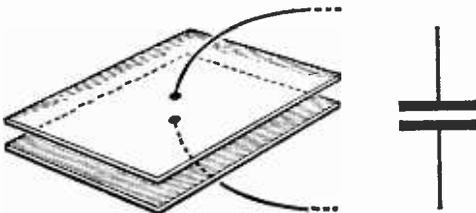


Fig. 1 (left)—The simplest form of condenser, or capacitor.

Fig. 2 (right)—The theoretical circuit symbol for a condenser.

very rarely air. It is usually either mica or paper. Fig. 2 shows the theoretical representation of a condenser.

### Storage of Electricity

We have stated above that a condenser is a device capable of storing electricity. But how exactly is this effected we ask? Why and where is electricity stored in the condenser?

Let us try to visualise what happens when we connect our condenser to a battery. This is shown in Fig. 3. Free electrons from plate 1 will be attracted to the positive side of the battery, thus leaving plate 1 with a deficiency of electrons i.e. positively charged. The electrons attracted from plate 1 of the capacitor to the positive side of the battery will appear (after flowing through the battery) on the negative side. This surplus of electrons or negative charge will therefore also

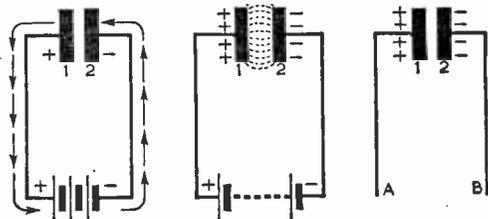


Fig. 3 (left)—When a condenser is connected to a battery, it becomes charged, as shown.

Fig. 4 (centre)—The charged condenser—the electric field between the two plates is represented by the lines from one plate to the other.

Fig. 5 (right)—Even if the battery is removed from the circuit, the condenser remains charged.

appear on plate 2 of the condenser since this is directly connected to the negative side of the battery. We may now say that the condenser is charged; and the situation is represented in Fig. 4. In other words, we may say that what actually happened during the charging process is a flow of electrons from plate 1 to plate 2 as indicated by the arrowed path in Fig. 3. The electrons on plate 2 try to move further on and reach plate 1 but they are impeded by the dielectric which is a non-conductor (insulator). This tendency of the electrons to reach plate 1 from plate 2 across the dielectric exerts a kind of pressure, force or strain on the dielectric. We call this the dielectric strain. When a condenser is charged, an electric field is

set up between the two plates. This electric field is represented in Fig. 4 by a number of hypothetical lines from one plate to the other. These lines are as imaginary and hypothetical as the lines of force representing the magnetic field around a magnet.

It is interesting to ask what would happen if the battery were removed from the circuit after the condenser is fully charged. This is shown in Fig. 5. The negative charge on plate 2 can in no way reach plate 1. It is prevented from doing so by the dielectric in one direction and by the fact that the circuit is open (between A and B) in the other. Therefore plate 1 retains its positive charge and plate 2 its negative charge. The resulting accumulated energy from the charging process is stored in the electric field. This potential energy is ready to be released as soon as a conducting path between A and B is provided.

### The Charging Cycle

Fig. 6 reproduces the charging cycle. Essentially, the circuit is the same as that of Fig. 3. The only additions are a switch and a sufficiently sensitive centre-zero current measuring device. Current flow is here assumed to be identical with flow of electrons. Hence the direction of flow is from the negative to the positive terminal of the battery.

#### A. Capacitor Uncharged

This is the initial stage of the cycle. The switch is open. The battery is not yet connected across the capacitor. The meter cannot indicate any current flow.

#### B. Capacitor charging

The switch is closed with the result that the battery is connected across the capacitor. Current flows until the condenser plates are charged to practically the same potential as the battery. We have discussed the charging process above, and the result is a positive charge on A and a negative charge on B. The centre-zero ammeter shows a flow of current (indicated by arrows). This flow ceases and the pointer returns to the zero position in the centre when the condenser is fully charged. In the present case, the charging (indicated by a sharp to-and-fro kick of the pointer) is instantaneous as, for simplicity's sake, no resistance has been provided for the condenser to charge through.

#### C. Capacitor charged

The switch is opened. The condenser retains its charge (theoretically, at least). Again, the meter cannot indicate any current flow.

#### D. Capacitor discharging

The battery is removed and instead a direct path is provided by a conductor (or a resistance). The switch is closed. The surplus of electrons on plate B rush out to meet the positive charge on plate A until both charges cancel out each other and the condenser is uncharged once again. The ammeter this time deflects to the left thus showing that during discharge the direction of current flow is in the opposite direction to that during the charging of the condenser.

After the condenser is completely discharged, the pointer returns to the zero position; we are back again to where we started (Fig. 6a) and the whole cycle can be repeated over again.

### A Condenser Blocks D.C. but not A.C.

We have said that a condenser blocks D.C. because of the dielectric which is an insulator. Now keeping this in mind, let us consider Fig. 7. When the switch is thrown to position 1, the lamp lights for a very brief interval and then remains extinguished. This is due to the charging current. The same thing happens again with the switch in position 2. This time it is due to the discharging current. If, however, we could flick the switch from position 1 to position 2 very rapidly, say 50

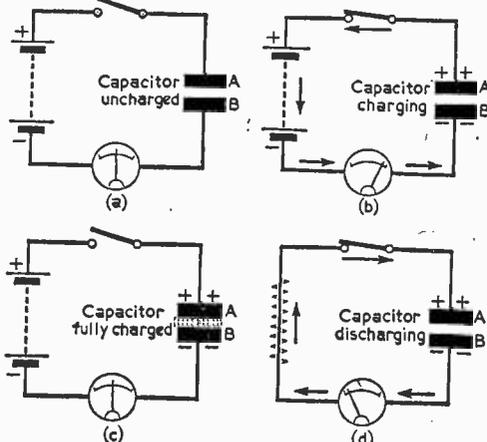


Fig. 6 (a to d)—The condenser charging cycle (see text).

times per second, the lamp would be lit and extinguished at the same frequency; but we would not be able to perceive this and the lamp would appear to be continually lit just as if the condenser were not there at all. Why is this? The reason is that the current is no longer direct but pulsating. Fig. 8a and 8b help us to understand this more

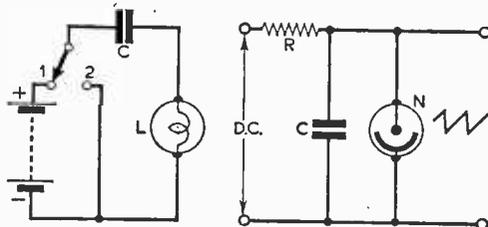


Fig. 7 (left)—A switched circuit which shows the effects of applying A.C. to a condenser.

Fig. 9 (right)—The circuit of a simple neon relaxation oscillator.


easily. In the first case, a 1-pole 4-way rotary switch is provided. The wiper, rotating in a clockwise direction, successively makes contact with the four positions. Notice the crude triangular waveform with a positive peak above and a negative peak below the zero axis.

(Continued on page 949)

# The P.W. POCKET SUPERHET

## NEW CONTEMPORARY CASE

WITH BUILT-IN DIAL CONTROL

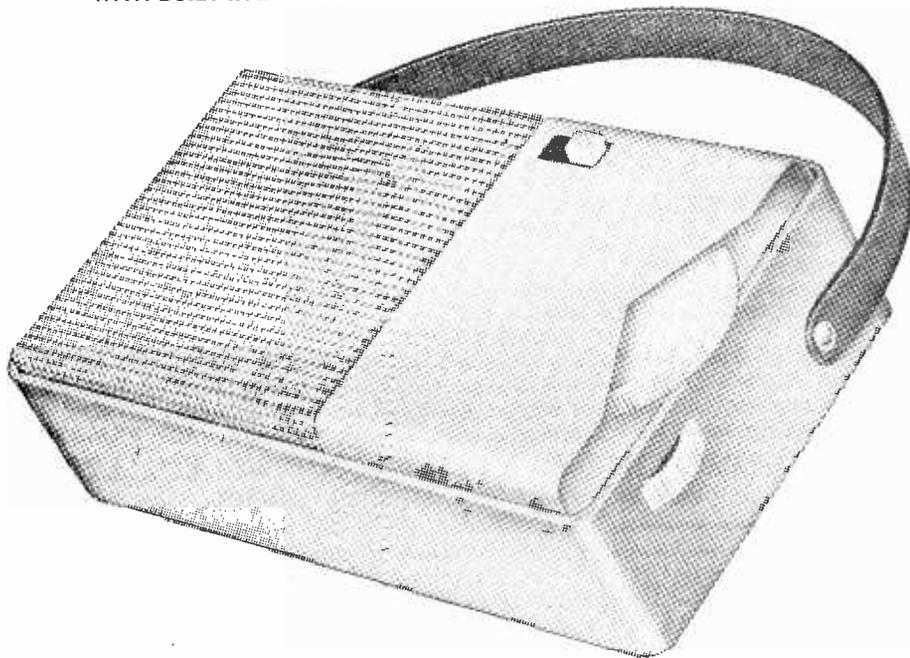

*Photo: Illustration on request.*

The Pocket Superhet is a high quality miniature receiver for operation on Medium and Long Waves. The circuit uses 6 special transistors and incorporates modern miniature matched components of the best quality which combine to give superb performance normally associated with much larger sets. The printed board construction ensures success to every enthusiast able to follow the simple Step by Step instructions.

**SIMPLE A-Z MODIFICATION TO BOOST  
AND IMPROVE THIS SET AS  
ORIGINALLY ISSUED**

**SIMPLE "STEP-BY-STEP"  
INSTRUCTIONS  
INCLUDING  
WIRING DIAGRAMS  
THEORETICAL CIRCUIT  
AND PHOTOGRAPHS  
BLOWN UP DGM  
1/6d.**

**ALIGNMENT & FAULT FINDING SERVICE**

(Details on Request)

**OSMOR**

(Trade & Retail)

418 BRIGHTON ROAD, S. CROYDON, SY.

# WEYRAD

**IMPROVED COMPONENTS FOR THE 6-TRANSISTOR 2-WAVE SUPERHET RECEIVER**

**NEW ROD AERIAL AND DRIVER TRANSFORMER FOR SIMPLER ASSEMBLY AND HIGHER PERFORMANCE**

**ROD AERIAL—RA2W**

6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208 pF tuning capacity ... .. 12/6  
Car Aerial coupling Coil ... .. 1/-

**OSCILLATOR COIL—P50/1AC**

M.W. covered with 176 pF tuning capacity. L.W. by extra padder ... .. 5/4

**I.F. TRANSFORMERS**

1st and 2nd Stage—P50/2CC ... .. 5/7  
(2 required)  
3rd Stage—P50/3CC ... .. 6/-

**DRIVER TRANSFORMER—LFDT4**

redesigned to reduce size and improve performance. Six spills for mounting and connections 9/6

**PRINTED CIRCUIT—PCA1**

Size 2 3/4 in. x 8 1/4 in. Ready drilled and printed with component positions ... .. 9/6


**WE CAN NOW OFFER A CIRCULAR TUNING SCALE PRINTED IN BLACK ON GOLD FOIL PRICE 6d.**

**CONSTRUCTOR'S BOOKLET WITH FULL DETAILS AND FREE SCALE ... 2/-**

**COILS, TRANSFORMERS AND ROD AERIAL FOR THE P.W. "CITIZEN" 35/- PER SET**

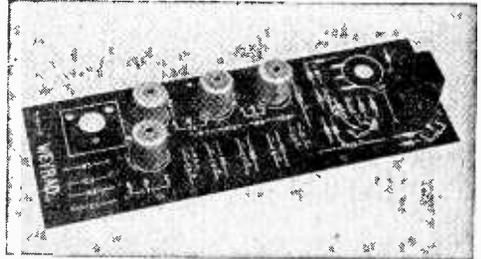**WEYMOUTH RADIO MANUFACTURING CO., LTD.**

**REGENT FACTORY, SCHOOL STREET,  
WEYMOUTH, DORSET**



**EXTENSION SPEAKERS**


**19/9**



8in. P.M. Speaker fitted into polished cabinet. Complete. Switch and flex included. P. & P. 4/3.

**TAPE RECORDER AMPLIFIERS**

**£7.19.6**

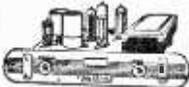

Compact, well designed 5 valve amplifier. Output 3.5W. Input for Microphone, Radio and Gram. Size 8 1/2 x 3 x 4 1/2 in. Ins., Carr. 5/-. 12 months' guarantee. Terms available. Extras: Dial plate, including sockets and superimpose switch, 3/6. Knobs 2/6.

**£9.15.6**

By famous manufacturer. Superb 4-valve amplifier. Two controls and super-impose switch. Sockets for Mike and Gram. Size 11 x 4 x 6 in. Ins., Carr. 5/-. Drawings FREE with order.

**LOOK! EX-RENTAL SETS**

**17 in. £11.10.0**

Excellent table models. ITA/BBC. Famous manufacturer. Personal collection advised. Ins., carr., 25/-. (Regret some delay.)  
12 months' guarantee on tubes. 3 months' guarantee on chassis and valves.

**14 in. £7.10.0**

ITA/BBC. As 17in. Ideal for caravans, chalets, weekend bungalows, etc. Personal collection advised. Ins., carr. 20/-.  
Various makes and sizes available for inspection.



**TRANSISTORS**

Per Set **47/6** Post Free

Mullard

1 OC81D 6/9, 2 OC81 6/9,  
1 OC44 9/9, 2 OC45 8/9,  
Diode 1/9

GEC

114 6/9  
873 8/9  
2-874 9/9

Ediswan

XC121 8/9  
XB113 8/9

**VALVES**

Salvage Guaranteed  
2/9 Each 30/- Dozen  
6AB8, 6C10, 6L18, 6U4G, 10F1, 10P13,  
12A17, 12AU7, 20D1, 20P3, B152, B309,  
B329, DH76, EBC80, ECC81, ECC82, ECL80,  
EF80, EF92, EY51, KT36, N145, LNI52, PL33,  
UCH42, U152.  
5/9 Each 60/- Dozen  
6F6, 6Q7, 12AX7, 12Q7, 15A6, 16A5,  
17Z3, 19Y3, 20L1, 20F2, 20P1, 21A6, B339,  
DH63, EBC33, EBF80, ECC83, EL33, EL38,  
EL42, EY85, KT63, N152, N153, N154,  
N309, N339, PCC82, PL38, PL81, PL82, PL83,  
PL820, PY80, PY81, PY82, PZ30.

Postage on 1, 7d. 6—1/6, 12—2/6.

**DUKE & CO. (LONDON) LTD.**

621/3 ROMFORD ROAD, MANOR PARK E.12.  
ILF 6001/3

9 a.m.—6 p.m.  
Half Day Thursday

STAMPS FREE  
CATALOGUE

**TV TUBES**



**12 MONTHS GUARANTEE**

21in. - - - 99/6  
17in. - - - 90/-  
15, 14, 12in - - 70/-

★ Insurance and carriage 15/6  
£1 extra without old bowl, refundable if same received within 14 days.

**14in. TV TUBES 35/-**  
Due to purchase of rental replacement 38/24 stocks. Carr. 5/6. 14KP4

(Continued from page 946)

Fig. 8b provides a smoother rise and fall by the insertion of other batteries supplying intermediate potentials. This waveform is nearer the familiar sine wave. In actual fact, an alternating voltage is produced by a coil rotating in a magnetic field at constant speed, the amount of voltage induced at any instant being proportional to the speed at which the coil cuts the magnetic lines of force. One cycle represents one complete revolution. Moreover, the speed of rotation determines the frequency of the alternating voltage.

Another important point with respect to Fig. 8b is that the faster the switch rotates, the brighter the lamp lights; just as if the resistance offered by the condenser is progressively diminished. This brings us to the important concept of Reactance.

**Reactance**

Although, as explained above, the condenser does not block A.C., it offers a resistance to it, as is shown by the fact that the battery voltage (supplying the lamp) has to be much higher than the actual voltage across the lamp. The reactance of a condenser is the resistance it offers to alternating current at a given frequency. Reactance ( $X_c$ ) is measured in ohms. The formula is:

$$X_c = \frac{1}{2\pi f c}$$

Where  $f$  = frequency in c/s.  
 $c$  = capacitance in Farads.

Reactance, therefore, is inversely proportional to the frequency and the capacitance.

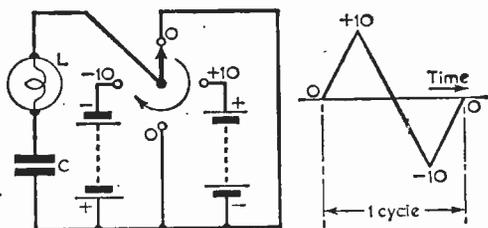


Fig. 8a—Using a rotating switch to give a crude form of A.C.

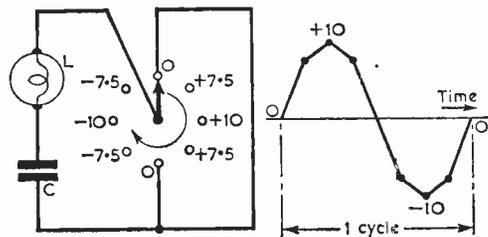


Fig. 8b—If more batteries are added to the circuit of Fig. 8a, a smoother waveform is obtained.

If the capacitance is constant, the higher  $f$  is, the lower  $X_c$  is. The reactance of a  $2\mu\text{F}$  condenser at 50c/s is 1591 $\Omega$ . But at 100kc/s, it is 0.795 $\Omega$ .

If the frequency is constant, the higher  $C$  is, the lower  $X_c$  is. The reactance of a  $2\mu\text{F}$  condenser at 50c/s is 1591 $\Omega$ . But the reactance of a  $10\mu\text{F}$  condenser at 50c/s is 318 $\Omega$ .

Therefore, reactance is lowered either by increasing the frequency or by increasing the capacitance.

**The Condenser in Use**

The peculiarities of the condenser are put to practical use in all kinds of circuitry, from the simplest crystal set to the most complex of electronic computers. Fig. 9 shows the circuit of a simple relaxation oscillator. The condenser  $C$  is charged through  $R$ . As soon as the voltage across  $C$  is equal to the striking voltage of the neon lamp  $N$ ,  $C$  is discharged through it. The process of charge and discharge is repeated over and over again as long as D.C. continues to be supplied.

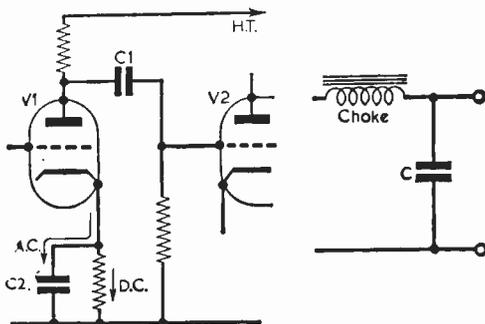


Fig. 10 (left)—Resistance-capacity coupling between valves.

Fig. 11 (right)—An H.T. smoothing circuit.

Two other important and common uses of the condenser are shown in Fig. 10 where we have resistance-capacity coupling between  $V1$  and  $V2$ . The coupling condenser  $C1$  prevents the D.C. voltage present at the anode of  $V1$  from reaching the grid of  $V2$  and driving it positive, while at the same time allowing the A.C. signal to reach the grid of  $V2$  for further amplification. The bias condenser  $C2$  bypasses the fluctuating A.C. signal component which prefers to pass through the condenser rather than through the resistance, the capacitance of the former being chosen so that its reactance is much lower than the value of the resistance. The purpose of bypassing the A.C. signal is to maintain a steady D.C. bias voltage at the cathode of the valve.

The condenser  $C$  in the choke-input smoothing circuit (Fig. 11) filters out any trace of A.C. ripple which manages to pass through the choke. (The choke offers a high resistance to A.C. while it allows D.C. to pass through it quite easily; its function is opposite that of the condenser).

It has not been possible here to give more than a few basic applications of the condenser in common circuits. The constructor will no doubt be able to find other uses for himself by carefully studying the various circuits which appear in every issue of "Practical Wireless".

# The

## BASS

### THEORY AND PRACTICAL DESIGN

# Reflex Cabinet

By J. B. Dance

(Continued from page 850 of the January issue)

**L**AST month, the theoretical aspects of the bass reflex cabinet were given; some details on construction were also given and it was stressed that to achieve good results, care must be taken to ensure that the cabinet is strong and rigid. If the cabinet walls are allowed to flex, then the sound output will be coloured by cabinet resonances.

#### Damping

The cabinet should be at least partially lined with a coating of heavy felt to subdue resonances—about  $\frac{1}{2}$  in. in thickness. The felt should not be thick enough, however, to damp sound waves at frequencies below about 200c/s. It is probably wise not to use too much felt at first, as the amount can always be increased later, if desired.

No allowance should be made for the volume of the felt when calculating the cabinet volume. It is the low frequency response which is affected by the cabinet volume and low frequency sound waves can travel through the felt to the walls.

It is usual to place a piece of expanded aluminium (which is sometimes given a gold coloured finish) over the loudspeaker and vent openings, but care should be taken that this will not produce an irritating rattle when the loudspeaker is producing sound of one particular frequency.

If a piece of cloth is used to cover the grill openings, it is important to use a type of cloth which presents little resistance to the sound waves. Closely interwoven threads should be avoided. Cotton or plastic cloth which is very loosely woven and which has hard threads is ideal.

#### Finish

It is well worthwhile taking great care over the finish of the cabinet so that one can take a pride in its appearance as well as its acoustical characteristics. A very neat finish can be obtained by staining the wood to the desired colour and then applying a solution of shellac in methylated spirit carefully. The shellac solution should be allowed to dry and several more coats may be applied to give the finished article a high polish.

#### Testing

The ultimate and most important test for any loudspeaker system is undoubtedly that of the human ear and the amount of satisfaction obtained by the owner and his friends. Nevertheless there are some measurements which can be carried out.

It is worthwhile to measure the loudspeaker impedance-frequency characteristic at low frequencies with the unit mounted in its cabinet. The apparatus for measuring this characteristic was given in Fig. 3, last month but an A.C. voltmeter

should be connected across the output terminals of the amplifier. Using low power, values of the voltage and current passing to the loudspeakers at various frequencies between about 25c/s and 200c/s can be found and the impedance at each frequency can be calculated from Ohm's law. The impedance should then be plotted against the frequency as in Fig. 1 (last month).

When the loudspeaker is mounted in a well designed cabinet, the characteristic should no longer look like that of Fig. 1 (last month). The one large peak at the fundamental resonant frequency of the loudspeaker should have completely vanished and two much smaller peaks on either side of the original peak should be found. If the original peak is still present, the cabinet has not been tuned correctly. The characteristic should be replotted with blocks of wood of about 100cu.in. in volume placed inside the cabinet. If it is impossible to remove the peak due to the loudspeaker resonance by raising the frequency in this way, the characteristic should be plotted with the vent reduced in size by a piece of wood. This will lower the frequency at which the cabinet resonates.

If peaks other than the two already mentioned are found in the response curve of frequency between about 80c/s and 150c/s, they are probably caused by standing waves in the loudspeaker cabinet. The area of the walls covered by the damping felt should then be increased until they vanish. It is not possible to remove standing waves completely at very low frequencies, but it is possible to remove them from the loudspeaker resonance curve.

#### Results

The performance of a correctly designed bass reflex cabinet system at low frequencies is much better than that of the more common and cheaper methods of mounting loudspeakers. Some of the advantages are listed below:—

(1) Improved bass response. The bass range may be improved by several dB over a range of nearly two octaves when compared with the same loudspeaker mounted in a closed cabinet or on a very large baffle.

(2) The impedance curve will be much flatter and hence the frequency response curve will be much more level in the low frequency region.

(3) The cone will vibrate with a much smaller amplitude when the input is at the resonant frequency of the loudspeaker than it would if the loudspeaker were mounted in an open cabinet. This will result in reduced distortion at the same power output, or alternatively more power will be available for the same degree of distortion.

(Continued on page 961)

# TRANSISTOR KITS

FULLY-PORTABLE

EVERYONE IS MAKING THEM!

IT'S TIME YOU STOPPED THINKING OF THEM

**SEND YOUR ORDER NOW!**

Our kits are unbelievably powerful—giving full coverage of medium and long waves. Luxembourg is guaranteed! At Wolverhampton we have often received Radio Moscow.

- ★ ELEGANT DIAL GRADUATED IN MEDIUM AND LONG WAVES
- ★ BUILT-IN WAVECHANGE SWITCH (NOT PRE-SET)
- ★ PRINTED CIRCUIT
- ★ FERRITE ROD AERIAL
- ★ EARPHONE AND SOCKET IF REQUIRED 12/6 EXTRA
- ★ CREAM RED OR BLUE CASE WITH CHROME HANDLE, SIZE 5½" x 3½" x 1½"
- ★ BUILT IN SPEAKER

ALL THIS FOR ONLY ..... **52/6**  
P.P. and Ins., 2/6.

If you want EVEN GREATER VOLUME, have the HIGH POWER MODEL at **59/6**  
P.P. and Ins. 2/6.

We are the Specialists who will help you with building, and give the service if you would like your set already built—include 30/- extra on all models. After sales service absolutely guaranteed.

## CAR RADIO PORTABLE KIT

two cabinets ★ wonderful quality—as good as a £20 commercial set ★ Money back guarantee  
 1 watt output ★ choice of  
 ★ Send for illustrated leaflet.

### Transistors - Miniature Components, etc.

G.E.C. S1, audio black—S2, low consumption audio or driver, S3, Red R.F. all 4/-.

EDISWAN XA116 5/-, XA141 power output 12/6.

MULLARD OC44 5/6, OC71 5/6, OC76 5/-. Most other types at these low prices.

PRINTED CIRCUITS Four transistor amplifier, 2/- with circuit.

Four transistor L & Med. Wave TRF Receiver with full instructions, 6/6.

Five transistor L & Med Wave TRF Receiver with full instructions, 7/6.

BELOW ARE LISTED A FEW OF THE OTHER LINES WE CATER FOR

Valves, Aerials (Radio and T.V.). 12ft. screw in tank Whips new, 12/6.

Gun collecting (antique or modern) shot or firearms bought and sold.

Model railway model making.

TV Cabinets all sizes and types £1 only.

Tapes, Recorders and Records (45 rpm unsorted £1 per dozen.).

Government surplus equipment radio, Radar, Geigers, Telescopes, etc.

Geology, we stock most British mineral samples at 3/- each.

S.A.E. FOR OUR 1962 LISTS

## WOLVERHAMPTON RADIO & T.V. SUPPLIES

43 BIRMINGHAM ROAD, WOLVERHAMPTON. Tel: Wolverhampton 20315.

**A MUST FOR THE BEGINNER!**  
**THE WIRECOMP**  
**'JUNIOR 5'**

**TRANSISTOR POCKET RADIO**

**WIRECOMP'S BARGAIN PRICE**

**£2.19.6** P. & P. 2/-

An easy "first step" set for the young constructor. This miniature marvel with the BIG performance has an internal Ferrite rod aerial—5 transistors and 1 diode—separate medium and long waveband control—200 milliwatt push pull output—2½in. moving coil speaker—unbreakable plastic case with carrying handle. Complete with full instructions.



Circuit diagram 1/6 Free with all parts  
 All parts sold separately.


**STOP PRESS!!!**  
**COMPLETE STEREO/**  
**MONO SYSTEM**  
 BY WORLD FAMOUS MAKER

**£12.19.6**

Limited quantity only.  
 P. & P. 10/-  
 Uses the Garrard TA Mk. 2 4-speed Single Player with Diamond Stereo Cartridge. Incorporated in one unit with 4-watt per channel stereo amplifier—supplied complete with two separate audio balanced column enclosure speakers. For use on 200/250 v. A.C. mains. SIZE—DECK 16½ x 14 x 8in. SPEAKERS 5' x 1' x 6½" deep. (For corner mounting.)

**ONLY A FEW LEFT IN STOCK!!!**  
**HIGH QUALITY V.H.F./A.M. RADIO**

**£12.12.0**

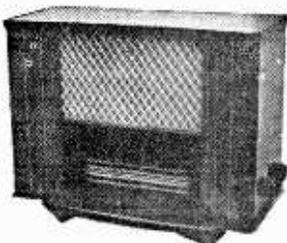

Brand new set, in superb walnut cabinet (size 19 x 8½ x 14in. high). Covering 80-100 Mc/s. 16-49 M., 200-500 M. and 1,200-2,000 M., Mains trans. 200-250 v. with 3 tapings. Ferrite rod aerials for A.M. Controls: volume on/off tone, tuning, w/change, gram, and ext. speaker position provided. Fully guaranteed. Post and packing 5/- extra.

**LOUDSPEAKERS**

5in. 14/6, 6½in. 16/-, 8in. 16/6, 6 x 4in. 14/6, 7 x 4in. 15/-, 8 x 5in. 23/-, 10in. 30/-, 10 x 6in. 25/-, 12in. 32/6. All above 3 ohms impedance. P. & P. 2/6.  
 12in. 15 ohms. Hi-Fi Celestion .. .. . £4.7.6

**RECORDING TAPE OFFER**

<b>STANDARD</b>	<b>LONG PLAY</b>
600ft. on 5in. spool 15/-	900ft. on 5in. spool 18/6
850ft. on 5½in. spool 16/6	1200ft. on 5½in. spool 21/-
1200ft. on 7in. spool 21/-	1800ft. on 7in. spool 32/6

P. & P. 1/-

**WIRECOMP ELECTRONICS**

378 HARROW ROAD, LONDON, W.9  
 TEL: CUNNINGHAM 9530  
 Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital.  
 Buses 18B and 36 pass the door.

**THERMIONIC VALVE CIRCUITS**


by Emrys Williams, Ph.D., B.Eng., M.I.E.E. M.Brit.I.R.E.

Students and teachers, as well as practising electronic engineers will welcome this, the fourth edition of this well-known work, which has already established a solid reputation as both text and reference book. Valve circuits in all their complexity are related to the simple bases of underlying theory. Numerous graphs and circuit diagrams add clarity to a highly readable text. An interesting new feature of this edition is the inclusion of numerous problems and exercises, many of them discussed at length. 27/6 net.

**PITMAN**

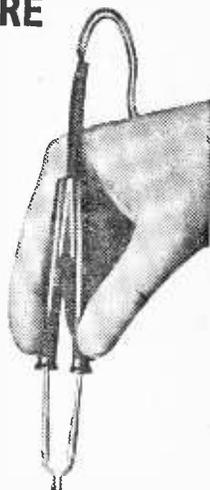**MICROMINIATURE SOLDERING TWEEZERS**

- ▶ One Hand Operation
- ▶ Heats Both Sides at Once
- ▶ Maximum Visibility
- ▶ Minimises Risk of Dry Joints
- ▶ Weighs Only 1 oz.
- ▶ Low Voltage
- ▶ The Revolution in Soldering



**ORyx**


**MICROMINIATURE SOLDERING TWEEZERS**

For the first time, one hand operation can hold the circuit module and apply direct heat to both sides simultaneously, thus virtually eliminating dry joints and reducing heating times. At your local store or write for free leaflet to:

**WG** W GREENWOOD ELECTRONIC LTD  
 677 FINCHLEY ROAD LONDON N.W.2  
 Tel: Swiss Cottage 3203/4

A TRF  
POCKET PORTABLE RECEIVER  
WITH  
FOUR TRANSISTORS

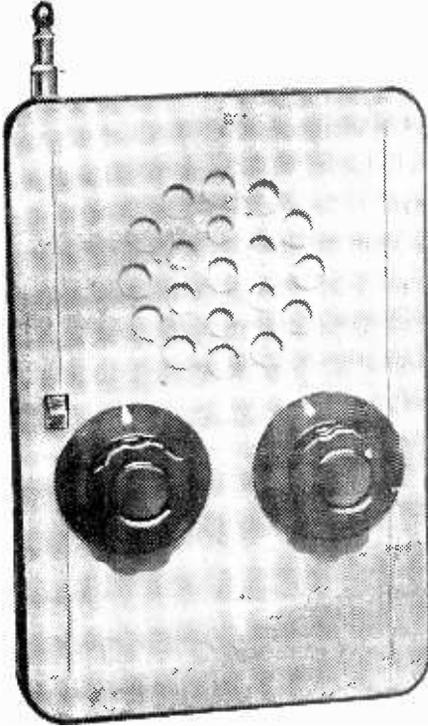(Continued from page 798  
of the January issue)



HAVING carried out the constructional work described last month, the detector stage can then be built up complete, and tested. Counting the tags from the top (in Fig. 4, last month), connections can be checked as follows: 1, Collector. H.F. Choke. lead 5; 2, Base, lead 2; 3 Emitter, 10k (R3), 500pF pre-set condenser (C1), tuning condenser frame and battery positive; 4, H.F. Choke, 5.6k (R1), 0.25 $\mu$ F condenser (C5); 5, 0.1 $\mu$ F condenser (C2), 10k (R3) and 100k (R2) resistors, lead 3 from ferrite slab.

The 500pF pre-set is held in position by soldering one of its tags directly to tag 3. All the transistor leads can be left long, but should be covered with sleeving. The transistor can be added last, the joints being quickly made, and the iron removed.

#### Testing

If desired, this part of the receiver can be tested with phones. To do this, connect the phones from the free end of the 0.25 $\mu$ F condenser (C5), to the tuning condenser frame, marked M.C. in Fig. 4. Take a lead from the 50k regeneration control to battery negative.

Smooth regeneration, right up to oscillation point, should be obtained with the 50k control. If oscillation cannot be obtained, screw down the 500pF pre-set slightly. If oscillation is too violent, unscrew this condenser. The correct setting is not very critical, and should allow adequate, yet smooth, regeneration with any battery supply of 4½V to 9V. If a regeneration winding has been added to an existing slab or rod, it might be necessary to adjust the position of this winding, to secure satisfactory results. If no regeneration at all can be obtained, the winding may have been reversed in error.

Reproduction in the phones should be free from distortion, and of reasonable volume. When the receiver is adjusted for maximum sensitivity, tuning is sharp, and both controls should be operated carefully together. The regeneration control should never be merely turned fully clockwise (as if it were a volume control) as this will not give satisfactory reception.

#### Audio Amplifier

This is built as a separate unit. A piece of paxolin is shaped as shown in Fig. 4, so as to clear the tuning condenser, regeneration control, and leave space for the battery.

Small holes are drilled, and the resistors and other parts are placed with their leads through the holes, as shown in Fig. 4. The reverse side

P. W.  
MINUETTE

By F. G. Rayer

of the audio panel is shown in Fig. 5.

The colour coding of the driver transformer T1, and output transformer T2 applies to the transformers listed. Other driver and output transformers would be equally satisfactory, and the maker's connecting data should be followed. The leads pass straight down through small holes, and are bent over. A little adhesive under the transformers will hold them to the panel, in conjunction with the leads. Leave the two secondary leads of the output transformer free, for connecting to the speaker.

**Lead Lengths**

All transistor leads can be left quite long, as mentioned, but the soldered joints should still be made quickly. Cover all wires, including the ends of resistors, with sleeving. A few inches of thin flex are used for battery connections, terminating with the appropriate positive and negative clips.

When the audio amplifier panel is finished, it is placed in the position shown in Fig. 4. Two short bolts hold it there, with spare nuts so as to obtain about ¼ in. space between the audio panel and the receiver panel.

**Connections**

The leads shown in Fig. 5 can then be connected to their correct points: one lead goes to the switch (battery negative); a second lead passes to the 50k regeneration control; transistor Tr2 base, which is joined to the 33k and 10k resistors (R4 and R5), goes to the 0.25µF condenser (C5), and, finally, a lead connects the battery positive side of the circuit to M.C., or the frame of the tuning condenser.

After connecting speaker and battery, the receiver can be tested. Reproduction should be

clear and distinct. No further adjustments should be necessary, if the 500pF pre-set has been adjusted as described. If a meter is included in one battery lead, the resting (quiescent) current (no signal) should be around 5mA. This should rise to about 8mA to 15mA on peaks, with average speech or music, according to volume.

**Case and Rod**

A piece of silk or other thin material about 4in. square is placed over the speaker, and held with adhesive. Fit the threaded bush for the back screw, tightening it securely. The control knobs are removed, together with the nut of the 50k potentiometer, and one screw of the tuning condenser. The receiver is then inserted in the case, and the nut and screw replaced, and tightened. Pointer knobs of reasonable size will be best for tuning.

The aerial rod has a bracket to take two 6B.A. bolts, with ¼ in. spacers, or spare nuts, between bracket and case, as shown in Fig. 4. A clearance hole is drilled in the case above the top of the rod. An insulated lead passes from the rod to the fixed plates of the tuning condenser. A small terminal on the side of the case would do for an external aerial connection instead.

**Equivalents**

The circuit will work satisfactorily with transistors of similar type, including surplus transistors in proper condition. Tr1 must be an R.F. transistor, or regeneration may not be obtained. Tr2 is an audio amplifier, and other types may need a change in value of R4, R5 or R6. Tr3 and Tr4 are best a matched pair for push-pull output. Some transistors may need

(Continued on page 962)

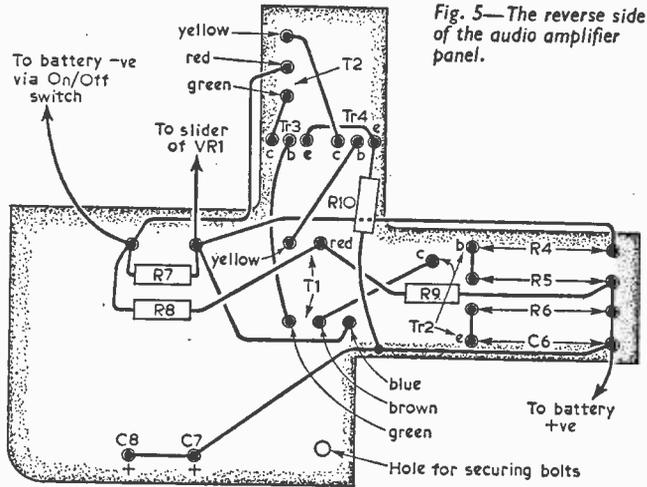


Fig. 5—The reverse side of the audio amplifier panel.



Rear view of the 'Minuette'.

# RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt.

★ Hire purchase orders are subject to slight delay but this is kept to the absolute minimum

## ● "P.W. TUTOR"

Everything in stock. Stage 1 including brand new light-weight headphones, 39/6. Less headphones, 23/6. Stage 2 19/-; Stage 3 21/6. Stage 4 11/6. All Stages 1 to 4 £4.8.6. Less headphones £3.13.6. All post free. Please note that the hardboard, wood, Terry Clips and cement not included. All items available separately—send for list.

## ● "P.W. MINI-AMP"

Complete kit for amplifier 24.2.6. Whiteley Speaker F2.585. £1.4.0. Greencoat Gramophone Unit £5.8.0. All parts available separately. send for list.

## ● "P.W. CITIZEN TUNER UNIT"

Kit for R.F. Unit, 57/-; Kit for I.F. Unit, 54/- Both k/ts together £5.7.8. L.P. POST FREE. Separate components available. Send for list.

## ● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510. Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer, GEC 912 Plus. Fully detailed list on any of these sent upon request. Instruction Manuals: All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. GEC 912, 4/6. All post free.

## ● MAINS TRANSFORMERS

GILSON: W0741AB, 83/-, post free; W0839, 48/9, post 2/9; FARRIDGE: H300/110, 77/6, post free; P4132, 78/6, post free; P3877, 26, post free; P4013, 86/-, post free. ELSTONE: M7/MU, 45/-, post 3/3; M73/M, 35/-, post 3/-. PARMEKO: P2631, 32/8, post 1/6.

## ● OUTPUT TRANSFORMERS

GILSON: W0696A, W0696B, 50/6, post 2/6. W0710, W0710EK, 55/6, post 2/6. W0692, 62/3, post free; W0767, 27/-, post 1/6. W0176A, 57/6, post 2/6. FARRIDGE: P3687, 52/6, post 2/6; P4014, 98/6, post free; P4131, 60/-, post free; P3591A, 99/-, post free; P5222, P5203, 95/-, post free. PARMEKO: P2641, 28/-, post 2/-.

## ● "BRAND FIVE" RECORDING TAPE

Standard Play: 800ft. (5") 18/-; 1,200ft. (7") 25/-; Long Play: 800ft. (5") 18/8; 1200ft. (5") 23/8; 1800ft. (7") 35/-; Double Play: 1200ft. (5") 37/6; 2400ft. (7") 60/- (All Post Free.)

## ● B.A.S.F. RECORDING TAPE

Long Play: 210ft. (3") 9/-; 800ft. (5") 28/-; 1200ft. (5") 35/-; 1800ft. (7") 50/-; Double Play: 300ft. (3") 14/-; 800ft. (4") 25/-; 1200ft. (5") 42/-; 1800ft. (5") 58/-; 2400ft. (7") 77/6. All post free.

## ● TAPE RECORDING EQUIPMENT

ALL CARRIAGE FREE	TAPE DECKS	Hire Purchase
		Cash Price Deposit Mthly/Pmts.
B.S.R. TD2 ..	£8.19.6	£1.16.6 12 of 13/7
Latest COLLARO Studio ..	£12.19.6	£2.12.6 12 of 19/-

We now stock the Martin Recorder Kits. These are partly assembled kits for complete tape recorders. The Amplifier Printed Circuit panels are completely wired, but the assembly of this and external components is left to the constructor. Very complete instructions are supplied. Send for leaflet.

MODEL C for Collaro Studio Deck £11.11.0. MODEL B for BSR TD2 Deck £8.8.0. CARRYING CASES: Smart carrying cases are available to take the above amplifiers and decks. Fitted with speaker. For Model C Amplifier and Collaro Deck, £5.5.0. For Model B Amplifier and BSR Deck, £4.4.0. H.P. Terms available for amplifiers, cases and decks.

## ● TAPE PRE-AMPLIFIERS

ARMSTRONG PA80-3. This is a ready made version of the Mullard Tape C Pre-amplifier. Price £16.16.0. Hire Purchase Deposit £3.8.0, and 12 monthly payments of £1.4.7. MULLARD TAPE C PRE-AMPLIFIER. We stock complete kits and all components. Send for list. MARTIN Kit for Collaro Studio Deck £8.8.0.

## ● LOUDSPEAKERS

GOODMANS: Axiom 110 10in. £5.2.0; Axiom 112 10in. £6.14.0; Axiom 8in. £8.15.0; Axiom 300 12in. £11.5.9; Axiom 400 12in. £18.1.0; Axiom 60 Bass, 12in. £9.12.9; Trebas Tweeter £6.4.0; CX 500 Cross-over unit £1.19.0. WHITELEY: HF 10in 10in. £8.4.0; HF 10in 12in. £5.2.6; HF8in 8in. £7.0.9; TS 9in. £6.10.0; T10 Tweeter £4.8.3; T359 Tweeter £1.15.10; CX3000 Cross-over unit £1.1.1.6; CX1500 Cross-over unit £2.0.0. H.P. Terms available.

## ★ TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows. Up to £5, minimum of 3/2. Over £3 and under £5, 1/8. Over £5 and under £10, 1/8. Over £10, no charge. Postage extra on CASH orders under £3 except where stated. Postage extra on Overseas orders irrespective of price.

## ● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS Hire Purchase  
ALL POST FREE Cash Price Deposit Mthly/Pmts.

	Cash Price	Deposit	Mthly	Pmts.
GARRARD AUTOSLIM (GC PU) ..	£8.5.0	£1.13.0	12 of	12/8
COLLARO C80 (GP67 PU) ..	£8.5.0	£1.13.0	12 of	12/8
GARRARD RC210 (GC8PU) ..	£10. 6.0	£2. 2.0	12 of	15/4
B.S.R. UA14 (TC8 PU) ..	£7.19.6	£1.12.6	12 of	12/3
B.S.R. UA14 Monarch (TC8 Stereo/E775) ..	£8.19.6	£1.16.6	12 of	13/7

SINGLE RECORD PLAYERS  
GARRARD TA (GC8 PU) .. £8.10.0 £1.14.0 12 of 13/-  
B.S.R. TU12 (TC8 PU) .. £4.10.0 £1. 5.0 3 of £15.5.0  
E.M.L. (Acos Stereo/Mono PU) £6.15.0 £1. 7.0 12 of 10/6

TRANSISTOR AMPLIFIERS  
GARRARD 41F (GC8 PU) .. £18.18.0 £3.16.0 12 of £1.7.8  
PHILLIPS AG1016 .. £11. 3.6 £2.17.6 12 of £1.0.9  
Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

## ● STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard circuits. ● Low/ANTI-LOG, 500k, 1 meq., 2 meq. ● Log/Log, 50k, 250k, 1 meq., 12—81 other parts brand new. All 10/6 each. Pick-up cartridges. B.S.R. TC8 £2.5.11. Turn-over type for Stereo. L.P. and 78 records. List of all components for Mullard Stereo Designs is available.

## ● TRANSISTORS

MULLARD. Reduced prices. Current production types, not rejects. All in makers' boxes. OC44, 11/-; OC45, 10/-; OC70 and OC71, 6/6; OC72, 8/-; OC72 Matched Pairs 18/-; OC78, 6/-; OC81, 8/-; OC170, 13/6; OC171, 14/6. Postage 3d. on each transistor.

TRANSISTORISE YOUR CRYSTAL SET  
We have two new designs for Transistor amplifiers which can be used to greatly improve the signal from any crystal set. Leaflet available.

RLD4 Kit. One stage 19/- post free.  
RLD5 Kit. Two stage 21/- post free.  
The kits are easy to build and very detailed instructions are supplied.

● MULLARD CATHODE RAY TUBES  
ALL AT THE NEW REDUCED PRICES  
We supply both Mullard Radiant Screen (Brand new factory fresh) and Mullard Lumenar (re-builds by Mullard with re-claimed built-in brand new). List of types available at the prices and hire purchase terms.

## ● LATEST TEST METERS

	Cash Price	Deposit	Mthly	Pmts.
AVO Model 8 Mark II	£24. 0.0	£4.16.0	12 of	£1.16. 2
AVO Model 8 with leather carrying case ..	£27.18.0	£5.12.0	12 of	£2. 0.11
AVO Model 7 Mark II ..	£21.6.0	£4. 4.0	12 of	£2.10.10
AVO Multimeter ..	£9.10.0	£1.18.0	12 of	14/4
AVO Multimeter with leather carrying case ..	£11. 9.0	£2. 5.0	12 of	17/-
TAYLOR MODEL 127A ..	£11. 0.0	£2. 0.0	12 of	15/-
CARY A-10 ..	£4.17.6	£1. 7.6	3 of	£1. 6.8
CARY B-20 ..	£6.10.0	£2. 0.0	3 of	£1.13.4

Full details of any of the above supplied free on request. The AVO Models 7 and 8 are both latest models from current reduction—not to be confused with Government Surplus.

## ● JASON FM TUNER KITS

We supply kits for all the Jason FM Tuners. Fully detailed lists available. Kits are complete with all valves and instruction manuals—definitely nothing else to buy. FM1 Standard Tuner with ext. power supply. £6.19.6. Power pack kit. £2.12.6 extra. FM2 Standard Tuner with internal power supply. £10.9.6. Less power supply. £9.9.6. FM3 Fringe power supply. £12.7.6. Less power supply. £12.7.6. Less power supply. £10.9.6. Mercury 2 FM/TV Sound Switched Tuner. External power supply. £11.7.6. Power pack Kit. £2.12.6 extra. JTV2 FM/TV Sound Switched Tuner, Internal Power supply. £15.17.6. IMPORTANT.—Please state TV Channels required when ordering Mercury or JTV Kits. INSTRUCTION MANUALS. Booklet for FM1, 2 and 3. £1/0. Mercury 2, 3/10. JTV2, 3/10. All post free. HIRE PURCHASE terms available on any kit.

## ● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, RECORDING TAPES, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● HIRE PURCHASE TERMS  
are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 1/6 in the £. Service charge 5 per cent but minimum charge 6/-. Six and Twelve months: Deposit 4/- in the £. Service charge 10 per cent, but minimum charge 20/-.

**WATTS RADIO**

(MAIL ORDER) LTD.

54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone: Weybridge 4556

Please note: Postal business only from this address


# CODAR "CLIPPER" ALL BAND RECEIVERS 10-2000 METRES

LISTEN TO AMATEURS, AIRCRAFT, SHIPPING, SHORT, MEDIUM, LONG WAVE BROADCAST STATIONS THROUGHOUT THE WORLD.

## THE MINI-CLIPPER

The miniature valve radio with the BIG SET features. Covers all Short, Medium, Long waves 10-2000 metres (5 coils). Smart all satin silver ali. front panel with engraved dials, etc. Ball bearing, air spaced variables. Size only 6½ x 3½ x 4in. Battery lasts months. No drilling. Total building cost including punched chassis, valve, front panel, one coil for 20-60 metres, nuts, bolts, wire, Step-by-step pictorial plans, 39/6. P. & P. 2/-. Additional coils and electrical bandspread optional extras. Parts sold separately. Full plans, parts list, 2/-.

39/6

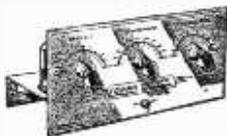

## THE SUPER CLIPPER 88/6

This world-famous hybrid receiver has achieved remarkable success. Tremendous performance with Hi-gain valve detector PLUS two Ediswan transistor amplifiers which are supplied assembled, only 3 wires to connect. Large precision dial, 7 x 4in., with 2 pointers, bandset and bandspread, dual slow-motion drivers, air spaced variables. Punched chassis 8 x 5½in. Batteries last months. Covers 10-2000 metres (5 coils). Total building cost including chassis, valve, 2 transistor stages, 2 coils 20-60 and 55-190 metres. Step-by-step pictorial plans, nuts, bolts, wire 88/6. P. & P. 2/6. Plans only, 2/6. **THE CLIPPER.** As above but one transistor stage, 79/6. P. & P. 2/6. Optional Front Panel, Silver Hammer finish, all holes, 6/9.



## THE CLIPPER CR 45

£6.17.6



This A.C. Mains receiver is the latest model in the famous CLIPPER Series and combines really top performance with superb professional finish. It is the finest ALL BAND receiver at the price with a new high gain circuit using ECC81 double triode, EL84 output, EZ80 full wave rectifier. Power output 3½ wats for 2/3 ohm speaker. Covers 10-2000 metres (5 coils). World-wide reception. Outstanding features include 3 planetary slow motion drives, separate electrical bandspread, air spaced low loss variables, satin silver dials, silver hammer front panel. Total building cost, including 10 x 5½in. punched chassis, valves, front panel, 2 coils 20-60 and 55-190 metres, nuts, bolts, wire, etc., 10 pages pictorial plans, £6.17.6. P. & P. 3/6. Optional extra. Modern styled Cabinet, rear panel, silver hammer finish, 27/6. Parts sold separately. Full plans, parts list, 10 pages, 3/6 post free.

No technical knowledge required to build these fine receivers. Send 3d. stamp for illustrated leaflets, testimonials, etc. Advance details now available for the NEW 1962 CR 66 A.C. SUPERHET COMMUNICATION RECEIVER.

**CODAR RADIO COMPANY, COLEBROOK ROAD, SOUTHWICK, SUSSEX**

G31RE

Tele. 3600.

G31PA

*"There is no Virtue without Courage—  
No Reward without Labour"*

Not simply a school motto but at B.N.R.S. a creed and a way of life. We owe to it all we have and are. If you are prepared to make it your motto and live up to it, we can help you to get to the top. It will take time, it will take effort, it will take courage, and on top of all this you will actually be charged fees.

If we haven't succeeded in putting you off, write for details, today, to:

**Mr. J. SYKES**

(M.I.E.E., M. Brit. I.R.E., M.I.N.)

Principal:

**BRITISH NATIONAL RADIO SCHOOL**  
Red Lion Court, Stalbridge, Dorset

Britain's premier Radio Correspondence School specialising in City and Guilds examinations.

## EXPRESS ELECTRONICS ROSEDEEN LABORATORIES KINGSWOOD WAY, SELSDON, SURREY

### VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/8 6BA5	6/- 5D3	4/- DF96	8/- EF41	9/- PCL84	7/-
1C6	8/- 6BE6	7/- 12A8H	10/- DH76	7/6 EF80	8/- PL81	12/6
1F1	8/- 6BH5	8/6 12AX7	8/- DH77	6/- EF86	9/- PL82	7/-
1F8	7/8 6B8	8/6 12AU7	6/6 DH142	8/6 EF91	4/- PL83	7/8
1FD1	8/- 6BR7	8/6 12AX7	8/- DH150	10/- EF92	5/6 P381	6/6
1FD9	7/8 6BS7	10/6 12BE6	8/6 DK91	7/6 EL41	9/6 PY82	9/6
1L4	8/6 6BW8	7/6 12BH7	10/6 DK92	7/6 EL84	7/- PY83	7/6
1P1	8/- 6BW7	7/- 12K6G11	8/6 DK96	8/- EM84	10/- R19	11/6
1P10	7/8 6C10	9/- 12Q7GT	7/8 DL92	7/6 EM85	10/- U28	9/6
1P11	7/8 6D2	4/- 18A5	5/- DL94	6/6 EY51	7/6 U52	7/8
1R5	6/- 6F12	4/- 25A8G	8/6 DL96	8/- EY81	10/- U78	7/8
1R5	6/- 6H6GT	2/- 25L8GT	7/6 EB91	4/- EZ40	7/6 U78	5/-
1T3	7/8 6J7GT	7/8 25Z4G	9/- EBC41	10/- EZ80	6/- UBC41	8/6
1U5	5/6 6K7G	5/6 30C1	6/6 EBF80	8/6 EZ81	6/6 UCH43	8/6
3Q4	8/- 6K8G	6/- 30L1	7/- ECK31	6/- KT36G	6/- UB41	8/6
3V4	7/8 6Q7G	5/6 35L8GT	9/- ECK82	5/6 KT66	11/6 UL41	8/6
3V4	8/6 6S17GT	6/- 35W4	8/6 ECK83	6/- N17	7/6 UY41	7/6
6U4G	7/8 6V6GT	6/- 35Z4GT	8/- ECH24	7/8 N18	8/- W78	6/6
5Y3GT	5/- 6V9G	7/8 35Z4U	10/6 ECF80	8/6 N18	7/6 W143	8/6
5Z4G	9/6 6X4	5/- 5783	7/6 ECF82	8/6 N709	7/- X17	7/8
6AK6	6/6 6X5G	5/- 80	6/- ECH42	9/- PCF84	6/6 X142	9/6
6AL5	4/- 6X5GT	6/- DAF91	7/8 ECH81	10/- PCF80	6/6 X160	9/-
6AM6	4/- 7B7	7/8 DAF96	8/- ECL80	8/6 PCF82	7/- Z77	4/-
6AT8	6/- 787	9/6 D91	7/6 ECL82	9/- PCL82	8/- ZD17	7/8

High Stability Resistors 1W 5% 50 Ω to 1M, 9d. Midret Ceramics 500 v. 9d. Coax. Super quality 1in., 6d. rd. Plug 9d. Sockets 9d. holders 9d., screens 9d. 250v. 300 MA 1in. x 1in. 17/6. Contact Cooled 250v. 60 MA 6/6. 85 MA 8/6.

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES. D. P. switch 4/- Less switch 2/6. Values 10K to 2M, B9A BTG v. holders 9d., screens 9d.

### VALVES MATCHED IN PAIRS

EL84 17/-, N709 17/-, 6Y6G 17/-, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15 Ω 14/6, P. & P. 1/6. 12in. P.M. Speakers 3 Ω 24/6. Baker's "Selhurst" 12in. 15 Ω 15W, 90/-, 12in. Stereo Model, 27.7.0.

### SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94 ..... 19/6  
 DK96, DF96, DAF96, DL96 ..... 27/6  
 1C3, 1F1, 1FD1, 1P1 ..... 27/6  
 1R5, 1T4, 1R5, 3R4, or 3V4 ..... 18/6  
 Postage and packing 6d. Over 21 post free.  
 ECH42, EF41, EBC41, EL41, EZ40 ..... 87/6  
 UCH42, UF41, UBC41, UL41, UY41 ..... 85/-  
 C.O.D. 2/6.

# FAULTS IN VHF/F.M. RECEIVERS

## 4-Transistor Sets

By G. J. King

(Continued from page 826 of the January issue)

SEVERAL of the more common faults in the final stages of VHF/F.M. receivers were dealt with last month, but a confusing symptom is the presence of hum and distortion. The treble-diode-triode valve (see Fig. 9, last month) often produces the above symptom, particularly that type of valve which is designed for A.C./D.C. operation, such as the UABC80. One complaint in this respect was that hum and distortion occurred, on F.M. only, a little while after the receiver has been switched on. It was discovered that the fault was fairly consistent and that it could be almost cleared by detuning. Replacing the valve cleared the trouble completely, but a subsequent check on a valve tester failed to reveal the trouble.

This is one of those cases where a faulty valve can only be discovered by substitution. Once the faulty stage has been located, quite a lot of time can often be saved simply by substituting the associated valve before detailed tests are carried out.

If distortion is present on both A.M. and F.M., attention should be given to the common A.F. stages. A typical cause of such trouble is a leak in the A.F. coupling capacitor (C58 in Fig. 9). This puts a positive voltage on the grid of the output valve and causes it to pass much more anode current than is good for it. The valve thus becomes very hot and the voltage across the cathode bias resistor rises above that given in the service manual.

Similar distortion, particularly at high volume levels, should lead to a check of the A.F. amplifier load resistor, such as R24 in Fig 9. If this goes high in value the distortionless output of the stage is considerably limited.

### Balance

Severe distortion on F.M. only, which can be reduced by detuning slightly, is often caused by unbalance in the ratio detector. This may be due to one of the ratio detector diodes going out of balance. Some sets use germanium crystal diodes for the ratio detector instead of the diodes in a multi-electrode valve. These are more prone to unbalance effects; in fact, one of the crystals may go open-circuit completely. This not only causes severe distortion but it also considerably reduces the output on F.M.

The ratio detector can be balanced by applying an amplitude-modulated F.M. I.F. signal (usually at 10.7Mc/s) to the control grid of the last I.F. valve and recording the output either on the speaker or on an output meter connected across

the speaker or across a resistor connected in place of the speaker. The resistor should have a value equal to the impedance of the speaker which it is to replace.

The signal generator should be accurately adjusted to the F.M. I.F., after which the core in the ratio detector winding of the transformer (e.g., L29 in Fig. 9) should be carefully adjusted for minimum output. The ratio detector is in correct balance when it does not respond to an amplitude-modulated signal. In practice, however, there is usually some residual frequency-modulation of the generator signal so zero output is rarely accomplished.

A series on VHF/F.M. receivers would be incomplete without reference to combined F.M./A.M. models using transistors, and the remainder of this series will be devoted to such sets.

There is no doubt now that transistors are going to take the place of valves in almost all types of electronic equipment of the domestic category. Industry is already using vast quantities in special instruments, control systems, computers and the like, and there has also been an almost complete changeover from valves to transistors in the popular A.M.-only portable sets.

### Noise and Reliability

The new alloy diffusion technique has made the manufacture of VHF transistors possible. These, which are able to operate up to 200Mc/s, are finding their way into VHF/F.M. receivers and television sets. A fully transistorised television turret is already available.

Apart from the smaller power requirements and resulting improved efficiency, transistors are also proving to be far more reliable than valves. This means that, while, in the past, transistors were employed essentially for miniaturisation, their use in the future will also be for reliability, and for that reason they will be exploited on an increasing scale in equipment which, by reason of its nature, does not particularly require to be made smaller, such as television receivers, radiograms, audio and hi-fi amplifiers, tape recorders and so on.

For the present we will concentrate on the transistorised VHF/F.M. set. In Fig 11 is shown the circuit of the VHF tuner of such a receiver. The two transistors are of the alloy diffused type and the circuit is based on the popular Perdio Portable, Model 95 which uses a total of nine transistors and five crystal diodes and is designed for A.M. and F.M. reception.

### Common Base Mode

Transistors Tr1 and Tr2 are operated in the common base mode. That is to say the base is earthed to the signal while the input signal is applied to the emitter. The collector is loaded in the usual way with the tuned circuits, across which the output signal is developed.

This arrangement, of course, is analogous to the valve earthed grid circuit, where the grid is earthed so far as the signal is concerned and the input signal is applied to the cathode circuit and the anode loaded with a tuned circuit across which the output signal is developed. For those not fully conversant with transistors, it should be noted that a transistor can be likened to a triode valve in certain respects, with the base being equivalent to the grid, the emitter to the cathode and the collector to the anode.

Transistor Tr1 is the R.F. amplifier for VHF. The aerial signal is coupled through C1 to the wide-band input circuit comprising L1 and C2. The loaded Q of this circuit is quite low, so the circuit responds to the whole of Band 11. The base is held at chassis potential (earth) so far as the signal is concerned by C3 (it should be noted that battery negative is, in fact, the chassis or earth line, this being the opposite to the circuitry in most transistor portables).

**Biasing**

The base of Tr1 is biased by the potential divider formed by R1 and R2 across the battery and thermal stability is maintained by the emitter resistor R3. Coil L2, C4 and C5 form the collector tuned load, and the R.F. tuning section of the gang C5 is coupled to the oscillator counterpart in the usual way. The capacitor, C6, connected between the emitter circuit and base provides a degree of feedback.

The amplified signal is fed to the frequency-changer stage, Tr2, through C7. In this particular receiver, it will be seen that the signal can either be applied to a conventional aerial socket from an outside aerial or, in good signal areas, from a simple telescopic rod aerial.

For the sake of completeness and to help newcomers to transistor circuits achieve a better under-

standing on the basis of comparison, the equivalent valve earthed-grid R.F. amplifier is given in Fig. 12.

**The Frequency-Changer Stage**

Transistor Tr2 performs the dual functions of local oscillator and mixer, and for this reason the stage is often called a "self-oscillating mixer". Again, the input signal is applied to the emitter, but this time across L3. The base is connected to chassis through C8 and is biased by the potential divider R4 and R5. The emitter resistor, R6, provides thermal stability (to prevent thermal runaway) and C9 gives a little feedback. Further feedback is provided by C10.

The oscillator tuned circuit comprises L4, C12 and C13, and is coupled to the collector through C11. C12 is the oscillator section of the tuning gang which is ganged with the R.F. section. Capacitors C4 and C13 respectively are R.F. and oscillator trimmers.

**10.7Mc/s Intermediate Frequency**

The stage is caused to oscillate at the frequency governed by the tuned load described above by regenerative feedback provided by C14, between emitter and collector.

The collector is also loaded by the tuned circuit L5, which forms the primary of the I.F. output transformer, L6 being the secondary across which the coupled I.F. signal is developed for feeding to the I.F. stages of the receiver. In common with most F.M. receivers, the intermediate-frequency is 10.7Mc/s which, of course, is obtained by the VHF signal heterodyning with the oscillator signal in Tr2.

When the receiver is switched to "F.M.", switch S1 is closed, so that the VHF tuner section is working normally, but when the set is switched to "A.M." S1 is open. This, of course, cuts off col-

*(Continued on page 961)*

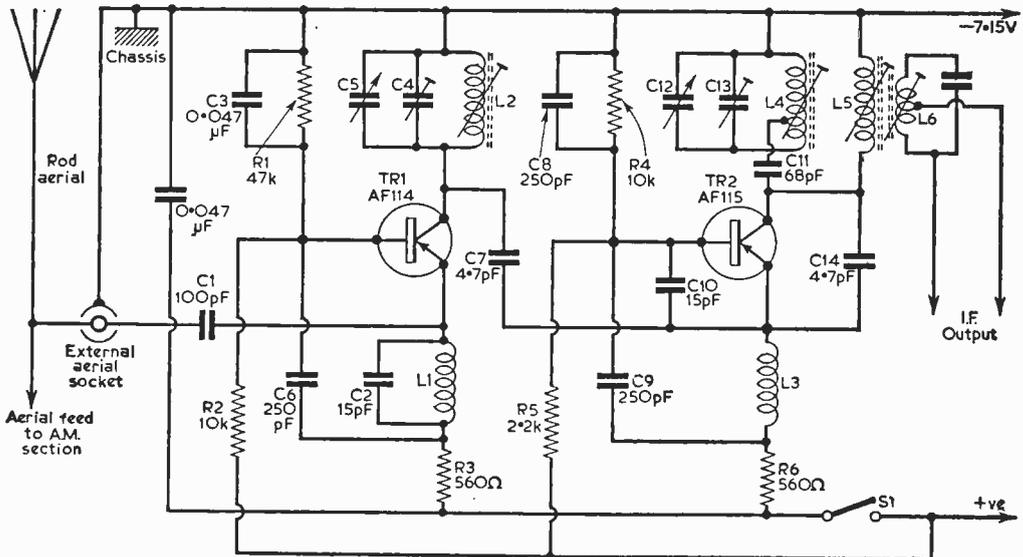


Fig. 11—The VHF section of a combined F.M./A.M. transistorised portable set.

# SURBITON PARK RADIO LTD

## for POST HASTE-POST FREE SERVICE

### F.M. TUNERS

**JASON F.M. TUNER KITS** We are the Authorised Jason Dealer and the whole kit is as supplied by them. You can therefore safely return to Jason for alignment without them rejecting it for non-standard components. We can also align for the standard charge.

<b>FMT1</b>	Is the standard variable tuner for cabinet mounting, un-powered. Supplied complete with four EF91 valves	<b>£6.17.6</b>
	Hire purchase deposit £1.7.6 and 6 monthly	<b>£1.1.8</b>
<b>FMT1</b>	Power pack ready drilled chassis complete	<b>£2.12.6</b>
<b>FMT2</b>	Is a new tuner in a modern case, green, which can be used for shelf or cabinet mounting, and has the space for power supplies if required. Supplied complete with four EF80 valves	<b>£7.17.6</b>
	Hire purchase deposit £1.11.6 and 6 monthly	<b>£1.4.4</b>
<b>FMT2</b>	With power. Complete kit	<b>£9.15.0</b>
	Hire purchase deposit £1.18.0 and 6 monthly	<b>£1.9.4</b>
<b>FMT3</b>	Is the fringe version and should be used when farther than 70 miles from the transmitter. Supplied complete with 6 valves	<b>£9.12.6</b>
	Hire purchase deposit £1.18.6 and 6 monthly	<b>£1.9.0</b>
<b>FMT3</b>	With power. Complete kit	<b>£12.0.0</b>
	Hire purchase deposit £2.8.0 and 8 monthly	<b>£1.8.6</b>

The instruction book is included in all kits, but otherwise 2/6.

### JASON SWITCHED TUNERS

The JTV/2 and Mercury 2 are both of the pre-set station type with the addition of BBC and ITA sound. They use the latest "Fireball" turret and the A.F.C. ensures freedom from drift. The Mercury 2 is for cabinet mounting with external power, the JTV/2 has the same tuning head, with power supplies mounted in a case, and can be used for shelf or cabinet.

<b>JTV/2</b>	Complete with valves and book	<b>£14.15.0</b>
	Hire purchase deposit £3.0.0 and 12 monthly	<b>£1.1.8</b>
<b>Mercury 2</b>	Complete with valves and book	<b>£10.15.0</b>
	Hire purchase deposit £2.3.0 and 8 monthly	<b>£1.4.0</b>
	Power pack kit for Mercury 2 ready drilled chassis	<b>£2.12.6</b>

Instruction book for switched tuners 4/- each.

**REQUIRED CHANNELS MUST BE SPECIFIED FOR SWITCHED TUNERS**  
A more detailed list can be sent upon request.  
**ALL JASON TUNERS ARE ON DEMONSTRATION, AND ALWAYS IN STOCK.**

### READY BUILT TUNER

F.M. Tuner Aligned and assembled, using Philips tuning head with EC85, EF85, EF86, EZ81 and EM81, with 2 diodes. SELF POWERED. In enamelled metal case.  
**UNREPEATABLE BARGAIN. CASH £8.80**

### JASON ARGUS

Transistor 2 wave band A.M. Tuner in attractive wooden case. Kit **£7.10.0**  
Book 3/6. Less transistors. **£6.10.0**

## MARTIN RECORDAKITS

We are able to offer for the first time, a proprietary range of Recorders in kit or assembled form. This enables you to take advantage of mass production techniques and prices, should you wish to assemble yourself. The components used are the finest available, with BVA valves, and the decks are the latest having all the improvements B.S.R. and Colmar make from time to time, heads, etc. The amplifiers are packed in special cartons with instructions which enable anyone to build. We are confident you will find these Recorders very good value, they have been built up to a standard and not down to a price.

<b>B.S.R. TD3</b>	Monardeck, latest model 5 1/2 in. spools	<b>CASH £9.90</b>
	Hire purchase deposit £1.19.0 and 6 monthly	<b>£1.8.4</b>
<b>Tape Amplifier</b>	for B.S.R. deck, printed circuit ready wired, with EC85, EC82, EM85 and EZ81. Complete with all plugs, sockets, panels, knobs, etc. The whole amplifier mounts on to the deck, making a self-contained unit.	<b>CASH PRICE £8.80</b>
	Hire purchase deposit £1.14.0 and 6 monthly	<b>£1.5.8</b>
<b>Cabinet for above</b>	including 7 x 4 in. speaker	<b>£4.4.0</b>
	Total kit as above	<b>CASH £22.0.0</b>
	Hire purchase deposit £4.10.0 and 12 monthly	<b>£1.12.1</b>
	The above recorder can be supplied complete with Mic: tape assembled and tested for	<b>CASH PRICE £25.0.0</b>
	Hire purchase deposit £5.0.0 and 12 monthly	<b>£1.18.8</b>
<b>Collored Studio Deck</b>	Very latest model 3 speeds	<b>£12.10.0</b>
	Hire purchase deposit £2.10.0 and 8 monthly	<b>£1.7.8</b>
<b>Tape Amplifier for studio Deck</b>	with ready wired printed circuit, control and input panels, mains and output trans., complete with knobs, piano, screws, etc., EF86, EC83, EM84, EZ81, OA81 and 2 EL84, 3 watts output. Masc eye, Radio and Mic. inputs. EX L/s socket. Tone control. Can be used as an amplifier.	<b>COMPLETE CASH £11.11.0</b>
	Hire purchase deposit £2.7.0 and 8 monthly	<b>£1.5.6</b>

<b>Cabinet for above</b>	including 9 x 5 in. speaker	<b>£5.5.0</b>
	Total kit as above	<b>CASH £29.0.0</b>
	Hire purchase deposit £6.0.0 and 12 monthly	<b>£2.2.2</b>
We can supply the above recorder, complete with tape and Mic, in a DE LUXE cabinet, assembled for		
		<b>£35.0.0</b>
<b>THIS MACHINE IS LISTED £41.00 BY MAKERS AND IS A VERY GOOD BUY.</b>		
	Hire purchase deposit £7.0.0 and 12 monthly	<b>£2.11.4</b>
<b>Tape Pre-amplifier</b>	for recording and playback, as above less output stage, with power supplies	<b>£8.8.0</b>
	Hire purchase deposit £1.14.0 and 6 monthly	<b>£1.5.8</b>
<b>Microphone</b>	for the above recorders, Accos MIC 40, 25/-, 8 1/2" plug 4/6.	
<b>Synchrotape</b>	5 in. 600ft. 15/- 5 in. 900ft. 19/8	
	Finest 5 1/2 in. 850ft. 19/6 5 1/2 in. 1200ft. 22/8	
	Boxed 7 in. 1200ft. 22/8 7 in. 1800ft. 32/8	
<b>Tape Recorder Speaker Cabinet</b>	corner, 20 x 10 in. High class finish in two-tone Grey "Vynair"	<b>£2.15.0</b>
	With 8 x 5 in. high flux speaker	<b>£4.0.0</b>
<b>Marriott Tape Heads</b>	4 track R/P/B & Frase with mounting plate for Collored deck.	<b>£4.4.0</b>
	List price for this head set is £3.14.0	pair

### GRAMOPHONE EQUIPMENT

<b>B.S.R. UA14</b>	TC8/II cartridge	<b>£7.15.0</b>
	Hire purchase deposit £1.11.0 and 6 monthly	<b>£1.4.0</b>
<b>Collored</b>	OOO Autochanger "O" cartridge	<b>£8.15.0</b>
	Hire purchase deposit £1.15.0 and 6 monthly	<b>£1.8.8</b>
<b>Garrard</b>	"Autoslin" 672 cartridge	<b>£9.3.4</b>
	Hire purchase deposit £1.17.4 and 6 monthly	<b>£1.7.8</b>
<b>Philips AG1018</b>	New semi-auto player	<b>£14.3.8</b>
	Hire purchase deposit £3.3.6 and 12 monthly	<b>£1.0.2</b>

**MINI AMP** P.W November issue, Resistors 6/-, V/C 6/-, Condensers 9/-, Transformers V6/R2 8/-, OC71 9/6, OC72 9/6, OC73 12/-, T72 9/6, PP 3/6, Press studs 1/-, Speaker 7 x 4 in. 17/6, Group B 2/9. All the above, if ordered at one time, £4.15.0. Diagram may be obtained from "Practical Wireless", 5/-.

**CITIZEN** P.W. Transistor tuner, December issue, Resistors 5/-, Condensers 11/-, W/C 3/6, OA70 3/-, Group boards 2/9 ea., Transformers 31/-, set, Coil set 22/6, RAZW 12/6, J.B. 12/6 with trimmers.

### TRANSISTORS

**MULLARD** HAVE REDUCED THE PRICE OF MANY TYPES TO OC4 11/-, OC45 10/-, OC70 9/6, OC71 8/6, OC72 8/-, OC73 8/-, OC76 8/-, OC78 8/-, OC81 8/-, ABOVE ARE THEIR NEW LIST PRICES. WHY BUY SURPLUS? MATCHED PAIRS ONLY. Mullard OC72 at 16/- pair.

### TRANSISTOR SUPERHET KITS

#### "PRACTICAL WIRELESS" POCKET SUPERHET

OSMOR printed circuit version. Osmor Rod aerial 10/-. I.F.T.s and Osc. Coils, 22/6. Osmor Output, 11/6. Osmor Output, 10/8. Set MULLARD transistors, 53/8, OA81 Diode 3/-. J.B. Gang, 11/-, Trimmers, 2/8 pr. Set Condensers, 15/-, Set Resistors, 8/6. Ardente Vol. Control, 8/-, Ardente W/C, 3/6. Speaker, 19/10. Hardware, 4/8. Primed Circuit, 9/-. Case and Knob, 7/6. Dial, 8d. Battery PP4, 2/-, Leadset giving full illustrated details, 1/8. All the above components purchased at one time £3.0.0. OSMOR undertakes to sign this power for a charge of 10/-, Modification Kit, 10/-, New contemporary case, 12/6.

#### "WEYRAD"

**WEYMOUTH RADIO** 6 Transistor Superhet using the P50 coils, as they advertise in this journal. P50/LAC Osc. Coil, 5/4. P50/2CC Ist and 2nd I.F.T.s, 5/7 ea. P50/3CC 3rd I.F.T., 6/-, RAZW Rod Aerial, 12/6, LFDT4 Driver, 9/6, PCA1 Printed Circuit, 9/6, Instruction Book, 2/-, Set Resistors, 7/6, Vol. Control D.P., 5/6, Set Condensers, 20/-, J.B. Gang, 11/-, Beehive Trimmers, 1/8 ea. W/C, 3/6, Dial and Knob, 3/6, Battery PP11, 5/8, OA81, 3/-, set MULLARD transistors, 53/8. 35 ohm 5 in. round L/s, 15/-, Car Aerial Coupling Coil, 1/-.

## 48 SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

Established over 30 years Telephone KIN 5549  
We pay all postage and insurance. All orders despatched same day. Money refund guarantee.  
Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday) We do not close for lunch. Open all day Saturday.

THE WORD **MAXI-Q** IS THE REGISTERED TRADE MARK  
 OF DENCO (CLACTON) LIMITED  
 IT IS ALSO A GUARANTEE OF  
 WORKMANSHIP & TECHNICAL PERFORMANCE

OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1/6 FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 1/6 IN STAMPS.

COMPONENTS FOR USE WITH THE "PRACTICAL WIRELESS"  
**AN AMATEUR COMMUNICATIONS RECEIVER**

PUBLISHED JULY/AUGUST 1961

**COIL TURRET—CT7/B**

This turret is the basic portion of the CT7. It comprises cadmium plated steel frame (size 5½" deep x 4½" high x 3½" wide), silver plated contacts, polystyrene insulation and a rotary turret movement incorporating Aerial, Mixer and Oscillator coils for the three bands 1.5-4 Mc/s, 4-12 Mc/s and 10-30 Mc/s.

PRICE 75/-

Coil strips for the long and medium wavebands may be purchased separately for incorporation in the turret.

PRICE 10/6 each

The turret requires a 315pF tuning capacitor. A suitable 3-gang component with ceramic insulation is available.

PRICE 19/-

Air spaced concentric trimmers, 3/30pF.

PRICE 3/6 each

**SCALE ASSEMBLY—S1**

Comprising basic 5 waveband glass scale for use with 315pF tuning condenser, back plate, pulleys, rubber scale mounts, pointer, cord, drum, spring, drive spindle, screws, nuts and spacers.

PRICE 19/-

**BEAT FREQUENCY OSCILLATOR COIL—BFO.2/465/kcs.**

A compact coil wound on a bakelite former and enclosed in an aluminium screened can.

**I.F. TRANSFORMER—IFT.11/465 kc/s**  
 (Four required)


A miniature I.F. Transformer for 465 kc/s. Permeability tuned, litz wound coils, enclosed in an aluminium screening can 1½" high x ¾" square.

PRICE 6/6 each

PLEASE SEND S.A.E. WITH ALL ENQUIRIES

**DENCO (CLACTON) LTD.,** (Dept. P.W.) 357/9 Old Road, Clacton-on-Sea, Essex

# KITS THAT 'BUILD THEMSELVES'

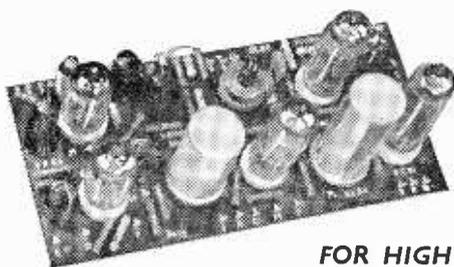

- HI-FI quality printed-circuit amplifiers, supplied checked and assembled
- Complete with valves, transformers and everything down to wire cut to length.

Produced by the makers of amplifiers for some of today's best known recorders and backed by years of experience in audio design. The specially designed kits offered here set entirely new standards of performance and finish for the home constructor. Amplifier available separately or with case and speaker and deck. EASY TO FOLLOW INSTRUCTIONS. All equipment complete and guaranteed.

From radio dealers, or in cases of difficulty please write direct

## FOR HIGH QUALITY TWO & FOUR TRACK TAPE RECORDERS

- AMPLIFIER 'C'** for Collaro Studio Deck (illustrated above). 11 gns.  
 Case and Speaker for above. 5 gns.  
**AMPLIFIER 'A'** (4-TRACK) for BSR Monardeck. 9 gns.  
**AMPLIFIER 'B'** (TWO TRACK) for BSR Monardeck. 8 gns.  
 Two-tone covered wooden case with speaker for above. 4 gns.  
**KIT 'A'** with Deck, Case and Speaker. 24 gns.  
**KIT 'B'** with Deck, Case and Speaker. 21 gns.  
**KIT 'C'** with Case, Speaker and Deck (as illustrated). 28½ gns.

All amplifiers supplied assembled on printed circuit boards with valves.



MODEL C

# MARTIN RECORDAKITS

Leaflet free on request.  
 Set of full instructions for any one model 2/6d. post free. (Allowable on purchasing kit).

COUPON BRINGS DETAILS ▶

MARTIN ELECTRONICS LIMITED,  
 155 HIGH ST., BRENTFORD, MIDDIX.

Leaflet on Martin Recordakits please

NAME.....


ADDRESS.....

(In Block Letters.)

P.W.2.

(Continued from page 958)

Fig. 12—The valve equivalent of the R.F. stage in Fig. 11. Here, R1 is for bias and R2 is the grid return resistor.

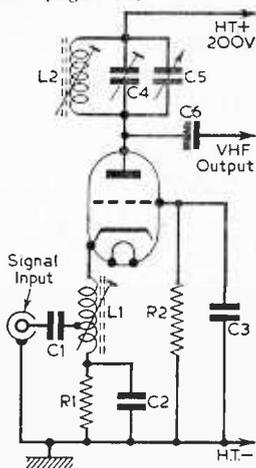

lector current on Tr1 and Tr2, but it will be noted that the bases remain biased since the bottom ends of the potential dividers, R2 and R5, are connected to the battery side of S1. This is done to prevent damage to the transistors, which might otherwise occur owing to a rise in base voltage.

#### Tracing Faults in the VHF Section

The VHF section is often built into a self-contained screened box, and intermittent troubles on VHF/F.M. due to poor connections, dry joints and so on occur equally in transistor units as they do in valve units. However, owing to the cool operation of transistors, frequency drift is not so troublesome as it is with valve circuits, but printed circuits and inter-connections still give trouble, and should be investigated as described in previous articles should intermittent symptoms on VHF/F.M. develop.

The alignment of a transistorised VHF tuner is sometimes more important than in valve units, for if the I.F. or oscillator alignment is misplaced by a small amount, the local oscillator may fall over a section of the tuning range.

#### Aerial

Excessive "noise" on F.M. when a station is tuned in should lead to a check of the aerial system for, although the new VHF transistors are endowed with remarkably good noise figures, one is often tempted with a portable to use the smallest aerial possible, and while this is perfectly in order in areas of reasonably high signal where there is little local shielding, something better is required in shielded locations.

If the VHF section fails completely, and the set operates normally on A.M., there is every possibility that the VHF tuner is faulty. This can be

proved speedily by switching the set to "F.M." and injecting the F.M. I.F. from a signal generator across L6, for example. If the output from the speaker is loud and clear, then the tuner is definitely faulty. If there is no output, attention should be directed to the F.M./A.M. changeover switching.

In most cases of VHF unit failure, apart from dry joints and poor connections, the local oscillator section is to blame. This invariably gives rise to a "hiss" when the set is switched to "F.M." and the volume control turned up full and, in some cases, there may be a sudden restoration of signals at certain settings of the tuning gang.

#### Readings

Much information on the operation of the transistors can be obtained by measuring the voltage across the emitter resistors (R3 and R6 in Fig. 1). The voltages will be low normally, not much more than one volt, so a low reading voltmeter is essential, and to avoid loading the circuits unduly the voltmeter should also have a fairly high resistance or sensitivity. A 20,000 $\Omega$ /V meter with a full-scale deflection on the "low volts" range of 2.5V to 5V is ideal.

Tests are best made with meter positive connected to battery positive. With the negative lead connected to Tr1 emitter a reading of around 0.85V would indicate that the transistor is passing collector current. On the same electrode of Tr2, the reading should be about 1.1V. Zero voltage would indicate either that the transistor is open-circuit or that the negative supply to the collector is missing. This supply should next be checked, if necessary, by connecting the negative of the meter to the collector. The voltage here should be almost equal to the negative line voltage, since the collector loads are of low resistance, though it may not be equal to the battery voltage owing to the voltage dropped across decoupling and filter resistors in the negative circuit from the battery to the VHF tuner. A value of about 7V is typical for VHF collectors.

The base voltage can also be checked by connecting the meter negative to base (positive still connected to battery positive). Base bias for VHF transistors is around 1V though it may be slightly higher on the frequency changer when oscillating properly.

If the voltages deviate substantially from the above examples, the feed components should first be checked for continuity and value, and if normal, the associated transistor will, in most cases, be found responsible. ■

## The BASS Reflex Cabinet

(Continued from page 950)

(4) The radiation resistance will be greater at low frequencies, and therefore the power will be more efficiently transferred to the surrounding air. When compared with a similar loudspeaker mounted in a closed cabinet, a power gain of about 3dB might be expected, as half of the power from a loudspeaker in a closed cabinet is wasted by being trapped in the cabinet. In actual practice the gain may be greater than 3dB when a bass reflex cabinet is used owing to the more efficient transfer of energy to the air.

The only possible disadvantage of the use of a bass reflex cabinet is that if the amplifier feeding the loudspeaker contains any hum, this will sound much more prominent than before, but the remedy for this is obvious.

Care should be taken not to obstruct the vent or the front of the loudspeaker; at the loudspeaker resonant frequency the sound is radiated almost entirely from the vent.

The frequency response should extend down to half the loudspeaker resonant frequency or less; with conventional mounting, the bass output from a loudspeaker is almost negligible below its resonant frequency. ■

# Club News

## REPORTS OF CURRENT ACTIVITIES

### AMATEUR RADIO MOBILE SOCIETY

Hon. Sec.: G3FPK, 79 Murchison Road, London, E.10.

At this year's Radio Hobbies Exhibition in London, the society had their own stand, manned entirely by A.R.M.S. members.

### BRADFORD RADIO SOCIETY

Hon. Sec.: M. T. G. Powell, G3NNO, 28 Gledhow Avenue, Roundhay, Leeds 8.

The society's last spares sale in 1961 was held on November 28th. On December 12th, the development of time measurement was discussed by W. Barton, and amateur receiver construction was the subject of the lecture given by D. M. Pratt at the meeting on January 2nd.

#### Future Events:

January 30th—Use of simple test gear, by D. G. Enoch.

February 13th—Field-day discussion and informal meeting.

### DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

The society's Open Night on December 13th was also appointed as the management committee meeting. On December 20th, members enjoyed the Annual Christmas Party. As there was no meeting on 27th December, those members who wanted to joined in a 160 metre net instead. Yet another surplus sale was held at the first meeting of the new year, on January 3rd.

#### Future Events:

January 30th—The year in retrospect—an opportunity for members to see some of the activities of 1961 in photograph form.

January 17th—A selection of communication receivers will be shown for members to compare.

### GUILDFORD AND DISTRICT RADIO SOCIETY

Hon. Sec.: J. R. Barker, G3PDX, 35 Banders Rise, Merrow, Guildford.

All the entrants for the car treasure hunt, held on October 1st, managed to complete the course. The proposed 2-metre equipment for the club net, was the subject of a talk given by Harry Mead at the meeting on October 12th. It was at this meeting that the society decided to enter the MCC top band contest, and so on November 11th, 12th, 18th and 19th, the club took an active part in the contest, using the call sign G3FZC. On October 24th the club visited the Dorking group for a ragchew and films.

Four club members took part in the R5GB top band contest which was held on November 11th and 12th.

### DUDLEY AMATEUR RADIO CLUB

Hon. Sec.: S. E. Plumtree, G3OSP, 11 Wallows Wood, The Straits, Lower Gornal, Dudley, Worcestershire.

On October 13th, members payed an outside visit to attend a demonstration of closed circuit television, hi-fi, tape recorders and audio equipment, and to see a film show.

A committee meeting was held on 20th October and another was held on 3rd November. On November 10th, members enjoyed a film show and on December 8th the Christmas dinner was held.

### NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Roninson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

Recent activities have included a talk on 2 metres by G8CB and a demonstration of hi-fi and stereo. On December 13th members took part in a ragchew.

#### Future Events:

January 10th—Informal meeting.

January 24th—Tape recorders.

### PETERBOROUGH AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: D. Byrne, G3KPO, Jersey House, Eye, Peterborough.

At the annual general meeting of the society, on the 3rd November, S. Hunting was elected president, C. J. Guscott was elected chairman, and D. Byrne was elected secretary and treasurer.

### ROTHERHAM RADIO CLUB

Hon. Sec.: S. J. Scarbrough, 25 Crawshaw Avenue, Sheffield 8.

During November members took part in the MCC top band contest. In December the club's own Annual Competition for the G3KUH shield was held.

The annual general meeting was held on January 3rd.

### SALISBURY AND DISTRICT SHORT WAVE CLUB

Hon. Sec.: E. J. Spicer, 43 Vale View Road, South Newton, Salisbury, Wiltshire.

Arrangements have been made for the club to show a series of films, fortnightly to members, and the first of these were shown on November 21st. Taped lectures are also a fortnightly attraction, and Morse classes are given most weeks.

### SILVERTHORN RADIO CLUB

Hon. Sec.: K. Marley, G3EIO, 17 Luctons Avenue, Buckhurst Hill, Essex.

Meetings are held every Friday at 8 p.m. at the South Chingford Community Centre. A club station is operated at constructional meetings on alternate Fridays.

### SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Nr. Leeds.

The society's Brains Trust was held on December 20th and the meeting on January 3rd was taken up by a ragchew.

#### Future Events:

January 17th—Electronic timing devices, by S. Marsden.

January 31st—Safety in the shack.

### WANSTEAD AND WOODFORD RADIO SOCIETY

Hon. Sec.: K. Smith, G3JIX, 82 Granville Road, Walthamstow, London, E.17.

At every Tuesday evening meeting, G3JIX gives a lecture on the requirements of the G.P.O. Radio Amateur's Examination.

The "constructional project" at the moment is a C-R bridge, and each member is constructing one from the same basic design.

## P.W. MINUETTE


(Continued from page 954)

values other than 220Ω for R9 and 5Ω for R10, to obtain full gain and distortion-free reproduction.

### Miniature H.F. Choke

A miniature H.F. choke can be made by taking a ferrite slug and winding several hundred turns of fine gauge wire upon it. For good results, there is little latitude in resistor values, but condenser values are less important. Typical possible values, with marked values in brackets, are: 0.1μF to 0.5μF (0.1μF); 0.25μF to 6μF (0.25μF); 1μF to 6μF (2μF); 6μF to 50μF (30μF).

Another view of the set.

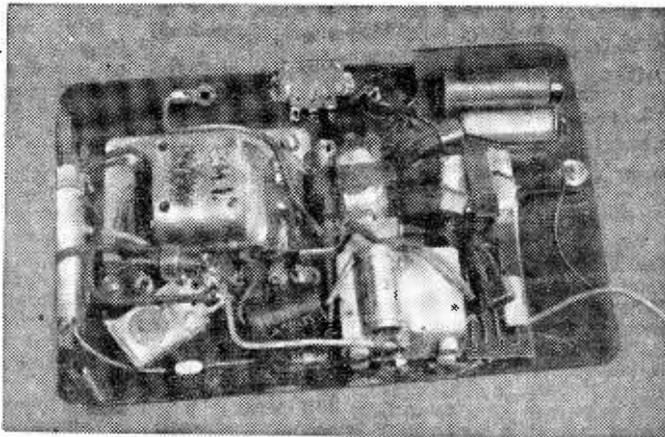

**SPECIAL BARGAIN OFFER!**  
**RECORD PLAYER KITS**

**AUTO CHANGER KIT**—Comprising three units, Contemporary styled Cabinet—2 valve, 2 watt amp. and 7 x 4in. quality speaker. Variable tone and Volume Controls with feedback circuit and B.S.R. 4-speed 10 Record Mixer, Auto Changer Unit.

**BARGAIN PRICE, £12.10s.** only. Cabinet Size: 17 x 14 x 8 1/2 ins. Carr. 7/6.

**SINGLE PLAYER KIT**—Similar spec. to Autochanger Kit except Player is 4-speed B.S.R. T.U.3, Single Record Player Unit. Attractive Contemporary Styled Cabinet. Size: 13 1/2 x 13 x 6 ins. with splendid volume and reproduction.

**BARGAIN PRICE £8.19.6** only Carr. 5/-

**ALL UNITS READY WIRED, SIMPLE SCREWDRIVER ASSEMBLY ONLY FULL SATISFACTION—REFUND GUARANTEE**  
Send for leaflet. Full details—3d. stamp.

**7 VALVE AM/FM RADIOGRAM CHASSIS**

Valve Line-up: ECC85 ECH81 EF89 1ABC80 EL84 EM61 EZ80.

Three Waveband and Switched Gram position. Med 200-500 m., Long 1,000-2,000 m., VHF/FM 85-96 Mc/s. Philips Continental Tuning insert with permeability tuning on FM and combined AM/FM IF transformers, 460 Kcs and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including A.V.C. and Neg. Feedback. Three watt output. Sensitivity and reproduction are of a very high standard. Chassis size 13 1/2 x 4 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/4 x 3 1/4 in. Vertical position. Horizontal station names. Gold on brown background. A.C. 200/250 v. operation.



Aligned and tested ready for use £13.10.0 Carr. & ins., 5/-.

Complete with 4 Knobs—violet or ivory to choice. Indoor FM Aerial, 2/6 extra.

Three ohm F.M. speaker only required. Recommended quality speakers. 10in. Bola (heavy duty), 30/- 8in. Bola or Elac (heavy duty), 25/- p. & p. 2/-.

**BARGAINS 4-SPEED PLAYER UNITS**

Single Players Carr. 3/6	Auto-Changers Carr. 5/-
Garrard 4 S.P. £6.18.6	Garrard C.D. £10.0.0
Garrard T.M. Mk.2 £7.11.6	Collaro "C 60" £7.15.0
Collaro "Junior" 7/5-	B.S.R. (UA14) £7.15.0
B.S.R. (TU9) 7/9/6	Latest Model Garrard
E.M.I. Junior 8/9/6	"Auto-slim" £8.12.6

**TURRET TUNER—BAND 1/BAND 3.**

Ex. mtrs. current production offer—std. type 13-channel unit. 35-38 Mc/s I.F. Complete with PCC84 and PCF80 Valves and coils for channels 1-3-9. No knobs or circuit diagram, but connection data supplied. Clearance Bargain Only 32/6. Carr. 3/6. Worth 5 gms.

**Speaker Fret**—Expanded bronze anodised metal 8x8in.

2/3, 12 x 8in. 3/-, 12 x 12in. 4/6, 12 x 16in. 6/-, 24 x 12in. 9/-, 36 x 12in. 13/6 etc. etc.

**Electrolytics All Types New Stock**

TUBULAR		CAN TYPES	
25/25V	1/9	8+8/450V	4/6
50/12V	1/9	8+16/450V	5/-
50/50V	2/-	32+32/275V	4/6
100/25V	2/-	50+50/350V	6/-
4/50V	3/3	60+250V	2/6
16/450V	2/6	275V	12/6
16+16/450V	5/6	100+200V	2/6
32+32/450V	6/6	275V	12/6

Erskin Multicore Solder 80/40, 3d. per yard. 1lb. 2/6, etc.

**SLEEVEING—Various Colours**

1mm. 2mm. 2d. vd.; 3mm. 4mm. 3d. vd.; 6mm. 5d. vd.

**CRT HTR ISOLATION TRANSFORMERS**

New improved types, low capacity (small size) and tag terminated a.c. 200/250V. Secondaries n.c. +25% +50% BOOST for 2V, 4V, 6.3V, 10.5V, 12V or 13V tubes. Each type 12/6 each. P. & P. 1/6.

**TRIMMERS, Ceramic (Compression Type)—30PF 70PF 100PF 150PF; 1/3 250PF, 1/6; 600PF 1/9.**

**PHILIPS, Bee Hive Type (Conc. Air Spaced)—2-3PF 1/-; 3-3PF 1/-**

**TUNING COND.—Twin Gang** by J.B., etc. 365PF Midget, 8/6; 0.005 mfd. Midget, 7/8. Transistor Type, J. Bros. 00. Midget Twin Gang 206PF+176PF, 9/6.

**SINGLE TUNING COND.—Reaction Type, Mica Dielectric** 0.001 mfd. 0.003 mfd., 0.005 mfd., 3/6 each.

**Wavechange SWITCHES** Midget Type—2 pole 2 way, 1 pole 6 way, 2/6 each; 1 pole 12 way, 2 pole 6 way, 3 pole 4 way, 4 pole 2 way, 4 pole 3 way, 3/6 each.

**SINGLE SCREENED LEAD:** Standard size 8d. vd.; Ditto Lightweight for Pick-up, etc. 7d. vd.; ditto lightweight PVC sheathed, 9d. vd.; Twin screened sheathed, 1/- vd.

**ENAMELLED COPPER WIRE**—1lb. reels, 14g-20g, 2/6; 22g-28x, 3/-; 30g-40g, 3/9. Other gauges quoted for.

**PVC CONNECTING WIRE**—10 colours (for chassis wiring, etc.)—Single or stranded conductor, per yd., 2d.

**RECORDING TAPE—SPECIAL BARGAIN OFFER**

Famous American Columbia (CBS) Premier Quality Tape at New REDUCED PRICES. A genuine recommended Quality Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted with leader and stop foils.

	Standard	Long Play	Double Play
5in.	600ft. 17/6	900ft. 18/6	1,200ft. 31/6
5 1/2in.	900ft. 15/6	1,200ft. 22/6	1,800ft. 39/6
7in.	1,200ft. 21/6	1,800ft. 32/6	2,400ft. 47/6

Post and Packing, per reel, 1/-, plus 6d. each for additional reels.

**SPECIAL OFFER**—3in. mtrs. surplus tape, 225ft. 5/6. P. & P. per reel. 6d. Plastic Tape Reels, 3in. 2/6, 5in. 3/-; 5 1/2in. 3/3, 7in. 3/6.

**Volume Controls—5K-2 Meg-ohms, 3in. Spindles**

Morganite Midget Type, 11in. diam. Guar. 1 year. LOG or LIN ratios less Sw. 3/-, DP. Sw. 4/8. Twin Stereo less Sw. 6/6. DP Sw. 8/-.

**COAX 50 OHM CABLE**

High grade low loss Cellular air spaced Polythene—1in. diameter. Stranded cond. Famous mtrs. Now only 6d. per yard. Bargain Prices—Special Lengths—20 yds. 9/- P. & P. 1/6. 40 yds. 17/6. P. & P. 2/-. 60 yds. 25/-. P. & P. 3/-. Coax Plugs 1/-, Sockets 1/-. Connectors 1/3, Outlet Boxes 4/6



**TAPE RECORDER KIT**

Special Offer. Latest 5 valve circuit based on Mullard's design. Magic eye and tone controls. Printed circuit already wired. A sensitive quality recorder B.S.R. Amp Kit 95/-, B.S.R. Tape Deck £21.0.0. Collaro Amp, Kit £5.5.0. Collaro Tape Deck £12.10.0. Set of 5 valves 45/-, Special Unit Kit Prices—Send stamp for detailed list. Construction and circuit details 2/6. Bargain Complete B.S.R. Kit £16.10.0. Carr. 4/6.

**METAL RECTIFIERS, STC Types—RM1, 4/9; EM2 5/6; RM3, 7/6; RM4, 16/-; EM5, 21/-; RM4B, 17/6.**

**SIEMENS TYPES**—Contact Coated; 250V, 50mA, 7/6; 250V, 85mA, 10/-; 250V, 12mA, 15/-; 250V, 300mA, 26/6.

**Condensers—Silver Mica**

All values, 2PF to 1,000PF, 6d. each. Ditto. Ceramics 9d. Tub. 450V T.C.C., etc., 0.001 mfd., 0.01 and 0.1/500V 1/-, 0.25 Etc. 1/6. 0.5 T.C.C. 1/9, etc., etc. Close Tol. S/Micas—10% 5PF-500PF 8d. 600-5,000PF 1/-, 1% 2PF-100PF 9d. 100PF-500PF 11d. 575PF-5,000PF 1/6. Resistors—Full Range 10 ohms-10 meg-ohms 20% 1 and 1W 5d., 1W 5d. (Midget type modern ratings) 1W 6d., 2W 9d. H-Stub 10% 1W 5d., 1W 7d. 5% 1W 9d., 1% 1W 1/6. W/W Resistors 2% ohms to 10K, 5W 1/3, 10W 1/6, 15W 2/-, Preset 1/3 Pots, W/W 25 ohms —50 K 3/-, 50 K-2 Meg. (Carbon) 3/-.

**JASON FM TUNER UNITS**

Designer-approved kits of parts: F.M.I. 5 gns. 4 valves, 20/-; F.M.I.2 27.5 valves, 37/6. JTV MERCURY 10 gns. JTV £13.19.8. 4 valves, 32/6. NEW JASON FM HAND-BOOK, 2/6. 48 hr. Alignment Service 7/6. P. & P. 2/6.

**Speakers P.M.—3 ohms 28in.** Elac. 17/6. 3in. Goodmans 18/6. 5in. Bola 17/6. 8in. Elac 18/6. 7 x 4in. Goodmans 18/6. 8in. Rola 20/-, 10in. R. A. 25/-, 10 x 6in. Goodmans 25/-, E.M.I., Tweeter 29/6.

**KNOBBS—Modern Continental types: Brown or ivory with Gold Ring, lin. dia., 9d. each; 1 1/2in., 1/- each; Brown or ivory with Gold Centre, lin. dia., 10d. each; 1 1/2 in. 1/3 each.**

**LARGE SELECTION available. TYGAN FRET (contemp. pat.)** 12 x 12in. 2/-, 12 x 18in. 3/-, 12 x 24in. 4/-, 18 x 24in. 6/- etc.

**New Boxed VALVES All Guaranteed**

1T4	8/-	ECC83	8/-	PCC84	9/6
1R5	7/8	ECL82	9/6	PCF80	9/6
185	7/8	ECL50	10/6	PC153	12/6
384	7/8	ECL50	8/6	PC184	12/6
3V4	7/8	EF86	12/6	PL81	12/6
DAF96	9/-	EL84	8/6	PL82	9/6
DF96	9/-	EY51	9/6	PL83	10/6
DK96	9/-	EY80	10/-	PY82	12/6
DL96	9/-	EZ61	7/6	PY81	9/6
ECC81	8/-	GZ32	12/6	PY82	7/6
ECC82	8/-	EM81	9/6	U25	12/6

**TRANSISTOR COMPONENTS**

Midget I.F.'s—485 Kcs, 5/6 9/16in. dia. Osc. Coil—M/W, 9/16in. dia. 5/3 Osc. Coil—M., & L.W. 5/6 Midget Drive Trans. 3.5:1 6/9 Midget O/Put Trans. P.P. to 3 ohms 6/9. Ferrite Aerial M. & L.W. Car. aerial coil. 9/3. Elect. Condensers—Midget Type 1 mid-50mfd. ea. 1/9. 100 mfd. 2/-, 6V 12V w/g. Condensers—0.1mfd., .03mfd. 9d., .05mfd. 1mfd. 1/-, .25mfd. 1/3; .5mfd. 1/6. Vol. Controls—Midget Type with edge Contact Knob. 47K, 1 M/ohm, ea. 2/6. Speakers P.M.—24in. E.M.I. 3 ohms 17/8, 7 x 4 in. Plessey 35 ohms 23/6. Ear Plug Phones—Min. Continental type. 3ft. lead, jack plug and socket. High Imp. 8/-. Low Imp. 7/6.

**TRANSISTOR BARGAINS**

Brand New—BVA 1st Grade			
OC44	10/6	873	9/-
OC45	9/6	GET114	6/6
OC81	7/6	OC72	7/6
2OC81	15/6	OC70	5/6
XA102	10/-	OC71	6/-
XA101	9/6	OC73	7/6
XB103	7/6	GEX34	2/9
XC101	6/6	GA70	2/9
874	9/6	OA81	2/9
SE305 Surface	GEX30	2/9	
Barrier Type	9/6	each.	

All Post Free.

Send for detailed bargain lists, 3d. stamp.

We manufacture all types Radio Mains Transf. Chokes, Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotation by return.



**RADIO COMPONENT SPECIALISTS**

79 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m.—6 p.m., 1 p.m. Wed. TH 2188. Trunk C.F.O. or C.O.D. Post and Packing up to 7d.; 1lb., 11s.; 11s.; 3lb. 1/6; 5lb., 2/-; 10lb., 2/6.

# THE LINEAR L1/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 5ins.

In addition two high impedance input sockets are provided for microphone and gram., etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81, H.T. and L.T. power supply point is included for a radio tuner.

**FREQUENCY RESPONSE**

± 1 d.b., 30-20,000 c.p.s.

**MAXIMUM POWER OUTPUT**

in excess of 14 watts.

**SENSITIVITY**

L.P. 220 m.v. for 10 watts. 78 r.p.m. 220 m.v. for 10 watts. Radio/Microphone 40 m.v. for 10 watts.

**TREBLE LIFT CONTROL**

+ 10 d.b. to -22 d.b. at 12,000 c.p.s.

**BASS CONTROL**


+ 14 d.b. to -10 d.b. at 50 c.p.s.

**HUM LEVEL**

Referred to maximum output and including integral pre-amp.—70 d.b.

**NEGATIVE FEEDBACK**

21 d.b. in main loop.

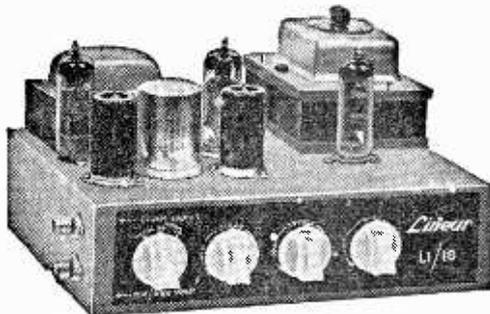

**HARMONIC DISTORTION** Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3-and 15-ohm speakers. Chassis finish stoved Gold hammer.

**HIGHEST QUALITY** Retail Price

**MAXIMUM RELIABILITY** **13**

**AT A PRICE YOU CAN AFFORD** **GENS.**

Send S.A.E. for descriptive literature

**TRADE ENQUIRIES to**

Also Available—THE L45.A compact High Quality 4.5 watt amplifier. Size approx. 7.5-5.5in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner etc. B.V.A. valves used are ECC83 EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5.19.6.

**THE LT45 TAPE DECK AMPLIFIER.** A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loud-

speaker and practically any make of deck. Negative feedback equalisation adjustment by multi-position switch for 1½, 3½ and 7½in. per second. Retail price 12 gns.

**DIATONIC 10-14 WATT.** High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

**CONCHORD 30 WATT.** Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

**L50 50 WATT AMPLIFIER.** Size approximately 14 x 10 x 8in. Sensitivity 25 m.v. Output for 3 and 15 Ω speakers. Retail price 22 gns.

**L5/5 STEREO AMPLIFIER 5 + 5 watt** 12 gns.

## LINEAR PRODUCTS LTD.

ELECTRON WORKS, ARMLEY LEEDS

# VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

<b>SETS</b>	1R5, 1S5, 1T4, 3B1, 3V4, DAF91, DF91, DK91, DL92, DL94 ..	Set 4 for 19/6
	DAF96, DF96, DK96, DL96 .. .. .	4 for 27/6

1A7GT 11/-	6L19 12/-	30C15 13/6	BBF80 9/-	EZ80 6/3	U52 4/6
1T5 17/5	6L20 9/-	30FL1 10/-	BBF89 8/9	EZ81 6/5	U78 4/6
1B5GT 9/-	6P1 10/-	30L15 11/-	EBL21 13/6	KT3C 7/-	U91 14/6
1N6GT 9/-	6P25 9/-	30PL1 7/0	ECC40 15/-	KT41 11/6	U251 12/-
1R5 6/-	6Q7G 6/-	30P12 10/6	EJC81 5/-	KT44 5/9	U281 17/-
1R4 9/-	6Q7GT 8/6	30PL13 11/9	ECC82 6/3	KT61 9/6	U281 16/6
1S5 5/3	6S17 3T 5/9	35A5 14/-	ECC83 7/-	KT63 6/6	U301 18/9
1T4 3/6	6SN7G1 4/9	35L6GT 8/3	ECC84 8/3	MU14 6/6	UABC90 8/6
1U5 5/9	6J4GT 9/9	35Z4GT 8/9	ECC85 7/9	MX30 9/6	UAF42 8/6
3A5 9/-	6V6G 4/6	35Z5GT 8/3	ECC90 7/6	N18 7/-	UB41 8/6
3Q4 7/-	6V6GT 6/3	50L6GT 8/3	ECCF82 8/6	PC86 10/-	UBC41 7/6
3S4 6/-	6X4 4/6	AC/TH1 18/9	ECH21 13/6	PCC84 7/6	UBP90 8/3
3V4 7/-	6X5GT 4/9	A/31 9/6	ECH35 6/3	PCCR8 9/3	UBF89 7/-
5U4G 4/6	6Y0L2 9/9	B36 8/6	ECH42 8/9	PCF80 7/9	UCC44 13/3
5V4G 7/6	7B3 9/-	CL33 12/3	ECH41 7/9	PCF82 8/9	UC85 7/6
5Y3GT 9/-	7B7 7/6	DAC32 9/-	ECL80 7/6	PCF86 14/-	UCF90 14/6
5Z4G 9/-	7C5 7/6	DAF91 5/3	ECL82 9/-	PCL82 9/-	UCH21 13/6
6AL5 8/9	7G8 7/6	DAF96 7/6	EFL36 4/6	PCL83 11/6	UCH42 8/-
6AM9 3/6	7H7 7/6	DCC90 9/-	EF40 12/6	PCL84 10/-	UCH81 8/-
6AQ5 6/-	7S7 9/-	DF30 9/-	EP41 7/9	PCL85 13/6	UCL82 9/6
6AT6 6/9	7Y4 7/-	DF91 3/6	EP80 4/9	PEN44 11/-	UCL83 13/3
6BA6 5/9	10C2 17/-	DF93 7/6	EP85 4/9	PEN36C 8/-	UF41 7/-
6BB5 5/9	10E13 14/6	DF78 4/9	EP86 4/6	PL45 11/6	CF42 5/6
6BH6 5/9	12A7 7/-	DH77 6/9	EP89 7/6	PL81 9/6	UF85 7/-
6BJ6 5/9	12AT7 5/-	DK32 11/-	EF91 3/-	PL82 7/9	UF89 7/-
6BR7 12/6	12AU7 6/3	DK91 9/-	EF92 3/9	PL83 7/6	UL41 8/-
6BW6 6/9	12AX7 7/-	DK92 7/6	EF93 8/6	UL84 8/6	UL84 16/6
6CDG 27/3	12XGT 4/9	DK96 7/6	EL41 9/6	PY32 11/6	UM4 4/6
6F1 10/-	12K8GT 9/6	DL33 8/-	EL42 9/-	PY30 7/6	UR1C 9/6
6F8G 7/6	12Q7GT 4/9	DL35 9/6	EL84 6/6	PY31 7/9	UL21 13/6
6F13 10/-	12Z3 7/6	DL82 6/-	EM34 6/9	PY82 6/6	UY41 6/6
6F14 10/-	15A7 19/6	DL84 7/-	EM80 8/-	PY83 7/9	UY85 6/6
6F23 10/-	20F2 17/-	DL96 7/6	EM81 8/-	T41 9/6	VF43 9/6
6K7G 1/11	20L1 17/-	EABC80 5/6	EM84 9/6	U22 7/3	VP41 5/-
6K7GT 5/-	20P4 20/-	EAF42 5/6	EY51 7/6	U24 17/6	VP1321 16/6
6KBG 5/-	25A6G 8/-	EB91 3/9	EY86 7/9	U25 12/-	W76 4/9
6KBGT 9/-	25L9GT 7/9	EHC33 5/-	EZ40 6/9	U26 11/6	W77 3/9
6L18 10/-	25Z4C 4/6	EHC41 8/-	EZ41 7/-	U50 6/-	Z77 8/6

**READERS RADIO**  
24, COLBERG PLACE, STAMFORD HILL,  
LONDON, N.16 STA. 4587

# Mullard

## MAINTENANCE MANUAL

This is a completely new and up-to-date edition including all current replacement types. It contains valuable new material and is an essential source of reference for every Service Engineer. 16/- Postage 1/-.

**RADIO CONTROL MANUAL** by E. L. Safford Jr., 25/-, Postage 1/-.  
**BAS-C PRINCIPLES OF ELECTRONICS & TELECOMMUNICATIONS** by M. D. Armitage, 22/6 Postage 1/3.

**RECORDS & GRAMOPHONE EQUIPMENT** by E. N. Bradley 8/6. Postage 6d.  
**TRANSISTORS. How to Test Them** Gernsback Lib. 16/-. Postage 9d.

**RADIO VALVE DATA** by "WW" 7th Ed. 6/-. Postage 10d.  
**GUIDE TO BROADCASTING STATIONS** 13th Ed. Compiled by "WW" 3/6. Postage 6d.

**LOUDSPEAKERS** by G. A. Briggs. 19/6. Postage 1/-.  
**INTRODUCTION TO HI FI** by C. Brown, 21/-. Postage 1/-.  
**COMPLETE CATALOGUE 1/-**

# THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books  
**19-21 PRAED STREET LONDON, W.2**  
Phone: PADDington 4185  
Open 6 days 9-6 p.m.

Post 6d. per valve extra.  
Any Parcel insured Against Damage in Transit 6d. extra  
Any C.O.D. Parcel 3/- extra.

# Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his' correspondents

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

## CORRESPONDENTS WANTED

**SIR,**—I am a regular reader of PRACTICAL WIRELESS. I am very much interested in the radio technology and have started my own shop of radio repairs. I would like to correspond with any radio technician from anywhere. I will answer all the letters received promptly.—B. S. GULSHAN, Falcon Radios, Kota JN, India.

## VALVE-TRANSISTOR SHORT-WAVER

**SIR,**—I have been gratified that so many people have enquired about the above receiver described in the July issue of PRACTICAL WIRELESS. A large proportion of these are concerned with the winding of the coils. These few notes should remove any difficulties.

L3 consists of 10 spaced turns over 2in., tapped at 5 turns and 7½ turns. The latter figure unfortunately appeared in the issue as 2½ turns.

Extensions to any of the coils to cover different wavebands is possible, only at the expense of losing other sections of the frequency spectrum. No experiments have been carried out which concern the fixing of a fourth coil.

The actual positions of the coils on the baseboard or chassis are not important as the three coils each carry their own reaction winding and aerial section.—P. K. CRIPPS (Liverpool).

## RECORD 'WOW'

**SIR,**—With reference to the article by L. E. Higgs in the September issue on record player faults, may I suggest that the fault of wow and slurring owing to records being warped can very simply be cured. The seven-inch records seem to be the chief offenders. If eight strips of Sellotape, about ¼in. x ¼in. wide, are placed at 45° intervals across the driving serrations, making certain they are clear of the run-off grooves, it will be found that even a badly warped record does not skid. I do this to every record regardless of its condition and have consequently had no trouble.—W. D. HESELTINE (Wallsend-on-Tyne).

## VINTAGE MODELS

**SIR,**—I was very interested in the letter in the December issue, by Mr. Mansell, as I too think that some of the old radios in true reproduction were very good indeed. I am sure anyone who has not heard one, tuned in to a good concert, would be very much surprised by the good quality obtained.

I have a very old tuned R.F. set which first had come from Chicago, U.S.A., 1931 to 1932, and was called the Zenith Autovox. This set had five tuned stages of H.F. and double push-pull output stages. These, working into a 15in. energised loudspeaker, resulted in a very powerful output and the quality of reproduction was amazing.

I have recently had to rebuild the set as the old valves gave out and could not be replaced. The set is still working well and it will pull in any station on a short piece of wire as the aerial, and the tuning is very selective.—D. J. FORWARCH (Watford).

## L.F. INSTABILITY

**SIR,**—I should like to report an interesting case of L.F. instability and its cure, in the hope that it may be of interest to others who may come across a similar unexplained fault.

The circuit was a simple mains amplifier, with a push-pull output stage fed from two audio stages (EF86's; one strapped as a triode and acting as phase splitter for the push-pull output stage). When switched on a very loud hum was experienced and the usual cursory tests failed to disclose the cause. Eventually the two EF86's were removed but the hum still persisted. The phase splitter had just a single resistor to the H.T. line and there was adequate smoothing (60μF). It was eventually found that a large electrolytic from the anode of the phase splitter to earth stopped the hum and finally the cure was a simple resistor (10k) between the anode resistor and the H.T. line, with a 32μF condenser to earth. — F. G. ROBERTS (Torquay).

## SOLDERING TRANSISTORS

**SIR,**—I should like to pass on a small hint which others may not have seen and which I feel is very important for those who are building the latest types of miniature transistor sets. As most readers now know these components are easily damaged, or even completely ruined, in the act of soldering them into a set. Fitting a heat sink is one very good idea, but I have met cases where the compactness of the set is such that there was no room to fit the shunt unless the leads were left extremely long. In addition whilst the heat shunt may protect the actual component being soldered there is also the risk that nearby parts may be damaged by the radiated heat from a soldering iron. Therefore, when constructing this small type of receiver I have found it a good idea to wind a length of ordinary copper wire, not heavier than 24s.w.g. round the bit and to draw off the remaining two inches, this giving in effect a two inch projection to the bit of thin copper and I find that it carries just sufficient heat to melt the very fine printed circuit solder without risk of damage. I even dispense with heat sinks when using this iron.—F. WALTERS (Hampstead).

MISCELLANEOUS

ELECTRONIC MUSIC ?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 23 stops—uses 41 valves. With its variable attack you can play Classics and Swing.  
Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham.

RECEIVERS & COMPONENTS

COMPONENTS, VALVES, Tubes, etc. Write or phone for free list. ARION TELEVISION, 4 Maxted Road, Peckham, S.E.15 (New X 7152).

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. PW/7/1, 138 Lewisham Way, S.E.14. Tideway 6666.

CRYSTAL SETS, sensitive, selective, in luxury Rexine covered case, 18/6 complete, p and p 1/- RADMORE, 11a Westmorland Street, Wakefield, Yorks.

TRANSISTOR SETS. OC44, 2OC45, OC81D, 2OC81 35/6. OC44 9/-. OC45 8/6. OC71 6/3. XA102 9/-. XA101 8/6. XB103 6/3. Red Spot 3/6. White Spot 4/-. Diodes General 1/- OA79 3/-. OA70 3/-. OA71 2/8. OA81 2/9. GEX34 2/8. Ear Pieces complete with plug and jacks 100, 250 and high Z 7/9 each. Min. Caps. 1 to 32 MFD. 1/9 each. P. and P. paid by CHAPPLE RADIO, 107 Neasden Lane, N.W.10.

KITS BUILT Complete. "Good Companion" £11/18/6. S.A.E. details. J. A. KINDER, 6 Hooker Road, Heartsease, Norwich, Norfolk.

SOUND VISION

BARGAIN PARCEL

Electrolytic Condensers, Volume Controls, asserted Condensers, etc. £2 value for 5/-, P. & P. 6d.

Red Spot, 3/-; White, 3/9; Yellow (6 volt), 2/3; Yellow/Green, 3/9; Red/Yellow, 5/-; STC/TS1 (OC71), 4/3; TS17 (OC72), 6/- each; XA101, 10/2; XB102, 10/3; OC81D 6/6; OC81, 7/6; OC170, 10/6. P. & P. 6d.

E.M.I. 4-SPEED PLAYER and P.U., 8/9/6. P. & P. 2/6.

"VERDİK QUALITY TEN"

10 watt, push-pull ultra linear Hi-Fi amplifier with pre-amp control. OUR PRICE £14 19s. 6d. P. & P. 7/6.

MARTIN RECORDER KITS

Model 'C' for Collaro Deck, £11 11s. 0d. P. & P. 2/6.  
Collaro Studio 3-speed Deck, £11 15s. 0d. P. & P. 5/-.  
Dynamic Mic. DM-175, 49/6. P. & P. 2/6.

JASON F.M. TUNER KITS

F.M.T.1 with valves ... £6.10.0  
F.M.T.2 with valves ... £7.17.6  
F.M.T.3 with valves, powered ... £12.0.0

PRINTED BOARDS

Mullard 3-3 ...	£ s. d.	
Mullard 5-10 ...	11 9	P. & P.
Mullard Stereo 5-10 ...	1 3 6	6d.
Mullard 5-20 ...	11 9	

Illustrated Catalogue 1/-  
137 MOULSHAM STREET  
CHELMSFORD, ESSEX

Phone 56815

RATES: 6/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., London W.C.2.

TELEVISION TUBE SHOP

now stock

Tubes for every make of set  
OVER 600 TUBES IN STOCK

12 inch Mullard type ...	£4. 5.0
12 inch Mazda type ...	£4. 15.0
14 inch Mullard type ...	£5. 5.0
14 inch Mazda type ...	£5. 10.0
15 inch Mazda type ...	£5. 15.0
16 inch G.E.C. & Mullard type	£6. 12.6
17 inch Mazda & Mullard type	£6. 10.0
17 inch G.E.C. & Brimar type	£6. 15.0
21 inch Mullard type ...	£8. 0.0

Add 10/- for insured carriage to your door within 48 hours, or 5/- via B.R.S. Terms £2 down (plus carriage). All tubes tested before despatch and guaranteed for 12 months. Guarantee cards enclosed with each tube.

Special Purchase of 110", 17 inch tubes—

Slight mark, Guaranteed for 12 months. Mazda CME 1703 } replace AW43-88, GEC 7405A } £6.

Shop Soiled Tubes.

(Slight scratches or marks) Guaranteed 12 months. Ideal for second set. 12in. 3/18, 3/31 37/6. MW31-74 50/-, 14in. MW 36-44 52/6. CRM141 55/-, 17in. CRM171, MW 43-64 60/-.

Others available from time to time. Please enquire.

Service Engineers  
Our Rebate Scheme shows real savings—send for details.

Television Tube Shop  
48 Battersea Bridge Road, S.W.11  
BAT 6859

Just South of the Bridge. Open Saturdays. until 4 p.m.

Your Hobby is Our Hobby

At Organford the commercial side takes second place. We carry on our work because we love our hobby and because we value so much the friendships that arise from it. Our aim is to be of help. We want to assist those whose circumstances prevent them from having easy access to the goods we sell and it is our constant desire to help them find the items that interest them. Items that will provide hours of happy relaxation in pursuit of their hobby. A Hobby Unique in that it can provide countless items of commercial manufacture in new condition that cost pounds to produce for as many shillings or even less. Every year we sell to enthusiasts many unusual items, and in this way the hobby they love is perpetuated, and their pleasure forms the foundations on which younger generations can build.

That this Hobby of ours forms a bond between different nations is visualised—there is not a country in the world where a Radio Ham cannot be sure of finding a friend—and through this hobby of ours which knows no international barriers we play our own small part in promoting good will.

Our lists of 40 Footscep pages containing details of over 1,000 different items in stock are available. Many of these items are unavailable elsewhere.

P. HARRIS, ORGANFORD, DORSET.

RECEIVERS & COMPONENTS (continued)

NEW AND Surplus Valves, fully guaranteed. S.A.E. for List. Also Reclaimed Valves, perfect. 5/- maximum. Genuine bargains. valves bought. LEWIS, 46 Woodford Avenue, Ilford, Essex.

TUBES! NEW 12in. 75/-, Most re-builders 75/-, new guns, guaranteed. Seconds 30/-, Finest value. 3 Pank Avenue, New Barnet, BAR 1934.

2 METER RECEIVER Type R1392(D) 95-155Mc/s. 15 valve Superhet. As New condition. Still used on many airways. D type being later model. Valve line up. 1st and 2nd RF AMP. EF54, 1st local osc. SP61, 2 osc. Multipliers EF54, 3 IF Amp. EF39, AGC67, Output 6J5. Muting EA50. Noise Limiter EA50, BFO 6J7, Mixer EF54, DE Mod 6Q7. Tuning meter, slow motion tuning. Normally crystal controlled or tunable over 95-155Mc/s. Power R-qd. 240, 80 mA, 6.3, 4 amps. Size 19 x 10 x 10in., £2.18.6, plus 7/6 carr., or as new, air tested, £6.18.6, plus 7/6 carr. Mains Power Supply 1st class condition, £4.5.0, or 6 volt Power Unit 19 x 10 x 10in., new £3.10.0.

ALL TESTED.

J. T. SUPPLY

309 MEANWOOD ROAD, LEEDS 7

MANUFACTURER'S STOCKS of radio cores, components and measuring instruments for disposal, send for free lists, enclosing S.A.E. to: S.E.I. Stock Disposals, Gee Street, Heywood, Lancs.

TUBES—VALVES—SPARES

TUBES 6 mon. Guar. FITTED FREE 9-10-12in. 30/-, 14in. 40/-, 17in. 50/- VALVES. 50,000 in stock. 1,000 types. All set tested before despatch. Examples:

51A	4/6	EBC41	6/-	N37	4/6
5V4	4/6	EBC90	4/6	N108	10/-
5Z4	4/6	EBF90	6/-	PCC84	4/6
6A6F	6/-	EB91	2/-	PCF80	7/6
6A45	4/6	ECC81	3/-	PC183	4/6
6B8	4/6	ECC82	4/6	PenA4	5/-
6BE6	4/6	ECC83	4/6	PL38	10/-
6BG6	10/-	ECC84	4/6	PL81	4/6
6BW6	4/6	ECC88	4/6	PL82	4/6
8D08	17/8	ECC91	4/6	PL83	4/6
8C18	4/6	ECH35	6/-	PY31	4/6
6C9	6/-	ECH42	6/-	PY80	4/6
6K25	7/6	ECF80	4/6	PY81	4/6
6L18	4/6	ECL30	4/6	PY82	4/6
6P25	4/-	EK90	4/6	PZ50	4/6
8V6	4/6	EF80	2/-	R19	7/6
6X4	4/6	EF92	4/6	MU14	5/-
757	4/6	EF95	4/6	SP61	2/-
7C5	4/6	EL38	4/6	U22	4/6
10C2	6/-	EL81	4/6	U24	7/6
10A18	3/-	EL40	4/6	U25	14/6
10B13	6/-	EY51	4/6	U37	12/6
12BH7	6/-	EY86	4/6	U31	4/6
20L1	6/-	FC4	5/-	U35	4/6
20P1	4/6	FC13	4/6	U191	7/6
20P2	6/-	KT36	4/6	U281	6/-
185BT	12/6	KT86	7/6	UL41	4/6
B36	4/6	KT81	4/6	UL44	6/-
DDT4	5/-	KT67	7/6	UU8	10/-

Most Pre-war 4, 5, 7 and 9 pin valves of British, European and American manufacture 5/- each. Postage and packing 6d. per valve. Orders over £1—free.

NEW TRANSISTORS. Red Spot 2/6, OC45, OC72, OC76, 7/6, OC35 (1 watt power), OC201 (Silicon) 20/-. Postage 3d. each.

SPARKERS: 6in. 5/-. Postage 2/-.

LINE OUTPUT TRANSF. from 20/-.

CONSTRUCTOR'S PARCEL. 2lbs. assorted components from TV Sets, resistors, condensers, pots, electrolytics, valves, etc. 7/6. Postage 2/6.

VALVE PARCEL. 12 valves, all different, as taken out of TV sets, ideal spares. 8/6. Post and Packing 1/6.

Send stamp with enquiries or for full list of 1,000 valves, tubes, transistors, etc. to: "ST. JOHN'S RADIO", 3 Jews Row, London SW18. Phone: VAN 8832

**RECEIVERS & COMPONENTS**

(continued)

**KINGSLAND**

**ELECTRONIC COMPONENTS**

**Stupendous Offers**

5in. Speaker, new. 3 ohms., 15/9.  
High Gain Transistors and Ferrite Aerials 3/9 each. Diodes, 1/9. All with circuits.  
KA118 Transistors. Ideal I.F. amp. 455 k/c/s. or L.F. driver, gain 12.5, 5/6 each.  
New, lightweight Headphones, 2000 ohms. General use, adjustable ready for use, 14/6.  
Driver and Output Transformers, sub-miniature, 10/6 pair. Volume control, edgewise movement with switch 5K, 20K, 1 meg., miniature, 8/6 each.  
Earpieces, crystal, 9/6. Magnetic, 9/-, complete with sub-miniature Jack and Socket or Jack and Socket, only 3/9.  
P.W. Pocket 6 Transistor Kit. Complete with printed circuit, cabinet, transistors and speaker. Osrom designed kit and full instructions, all parts guaranteed new. This is the Kit for the Ambitious constructor. 29.10.0.  
Try our surprise pack of accessories. If not satisfied return within seven days and money will be refunded, 7/6, p. & p. 2/6. 6 assorted voltage diodes, 5/-, p. & p. 1/6. 100 assorted condensers, 9/-, p. & p. 1/9. 6 volt or 12 volt vibrators, 3/6 each p. & p. 1/6. Mike and pick-up transformers ideal for baby alarms, 4/6, p. & p. 1/-.  
5 assorted potentiometers, 5/-, p. & p. 1/9. 50 assorted resistances and condensers, 6 miniature valve holders, 2 tax strips, 40 separate contacts each 4/9, p. & p. 1/9.  
182 KINGSLAND RD., SHOREDITCH, E.2, Tel: SHO 6572. Sorry! U.K. only.

**SPEAKER REPAIRS.** Cones/Fields fitted. Clock Coils Wound. L. S. REPAIRS, Pluckley, Ashford, Kent.

**A.1. BARGAINS.** Post free. OC70. OC71 5/9. OC72. OC78. OC81 8/9. OC45 8/9. OC44 9/9. OC 171. OC170 12/9. OC65 20/-. OC66 22/-. OC19. OC16w42/-. 2-OC72 13/3. OA70. OA79. OA81 2/9. OA91. OA95 3/3. EF80. 6D2. EB91. EF91 1/3. ECL80 4/3. 6F1 1/9. 10F1 2/3. RTC, crystal mikes hand/table 19/6. Few last months bargains available. Let us quote for any of your needs. C.W.O. A.1 RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

**FOR SALE**

**ASK** your dealer for American Ferro-dynamics. "Brand Five" Recording Tapes—the best tape value!

**100 BAYS** of Brand New adjustable Steel Shelving, 73in. high by 34in. wide by 12 in deep, stone enamelled dark green. Sent unassembled. Six shelf bay £3/15/0. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

**MORSE TRAINING RECORDS.** The latest Rhythm Method of teaching morse is the quickest and cheapest known. For full details and special beginners offer. S.A.E.: "MORSE-REC", 45 Green Lane, Purley, Surrey.

**CABINETS, EQUIPMENT & SPEAKERS**

Write for CATALOGUE

A. L. STAMFORD Ltd.  
Dept. S.28.  
84 Weymouth Terrace,  
London, E.2.



GP57 18 Gnt.

**FOR SALE (continued)**

**MAKERS' SEALED CARTONS**

- GARRARD R.C. 210 ... .. £9. 8.6
- NEW GARRARD "AUTOSLIM"  
4-SPEED CHANGER ... .. £8. 5.0
- B.S.R. UA14 ... .. £7.15.0
- B.S.R. TU9 ... .. £4. 5.6

Valves, Transistors, Condensers,  
Etc., Etc.

**AUTUMN LIST NOW READY**

**H. F. JAMES**

21 Claremont Road, Twickenham,  
Middlesex.

Tel. POPesgrove 3579.

**WANTED**

**WANTED** New valves and transistors, any quantity. S. N. WILLETS, 43 Spon Lane, West Bromwich, Staffs. Tel: WES 2392.

**NEW VALVES** bought, state price. A.D.A. MANUFACTURING CO., 172 Aldreton Road, Nottingham.

**A PROMPT CASH OFFER** for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

**WANTED VALVES**

All types for prompt cash. Must be new. State quantity.

**WILLIAM CARVIS LTD.**

103 North Street, Leeds 7

**WANTED, TEST GEAR.** Meters, Valves, Components, Communication sets, Amplifiers. HUGGETTS LTD., 2-4 Pawsons Road, West Croydon, Surrey.

**ENGLISH CANADIAN.** electrical instrument experience, sales, import-export, both here and Canada. Seeks subcontract, assembly wiring, small electronic electro/mechanical devices. Cornwall area. BOX 33.

**NEW VALVES WANTED**

Any type, any quantity

**CASH PAID**

R.S.T. 211 Streatham Road,

Mitcham, Surrey.

Telephone: MITCHAM 6201

**BOOKS & PUBLICATIONS**

**FIND TV SET TROUBLES IN MINUTES** from that great book 'The Principles of TV Receiver Servicing' 10/6 ad book houses and radio wholesalers. If not in stock, from Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

**SERVICE SHEETS**

**SERVICE SHEETS** for all makes of radio and TV, 1930-1962. Prices from 1/- with free fault-finding guide. Catalogue of 6,000 models 1/6. 125 Radio/TV sheets covering 370 popular models 20/-. S.A.E. inquiries HAMLTON RADIO, Western Road, St Leonards, Sussex.

**SERVICE SHEETS.** Radio and Television 4/- each, list 1/-. All old and modern receiver sheets available. Faultfinder files 2/- each. List now available 1/- KAYBRO PUBLICATIONS, 44 Old Bond Street, London W.1.

**SERVICE DATA LIBRARY:** All Models—TV, Radio, Tape Recorders, Amplifiers, etc.

**ADVISORY SERVICE:** send for specially developed Fault Diagnosis Questionnaire.

**PRACTICAL BOOKS:** TV, Radio, Tape Recorders, Hi-Fi, Test Instruments, Servicing, etc.

**IMMEDIATE SERVICE:** S.A.E. to

**GORDON J. KING**

"KINGSFORD", SOUTH FURZEHAM ROAD, BRIXHAM, DEVON. Tel: Brixham 2304

**SERVICE SHEETS.** Radio and TV 4/- each. List 1/-. All orders despatched on day received. Also manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**SERVICE SHEETS.** Radio , TV. 5.000 models. List 1/-. S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

**SERVICE SHEETS;** also Current and Obsolete Valves for sale. — JOHN GILBERT RADIO, 20 Extension, Shepherd's Bush Market, London W.12. (Phone: SHE 3052).

**38 SET WALKIE TALKIE**

**CIRCUIT INFORMATION**

Alignment procedure. Faults, Components, Diagrams etc. P.O. 5/-.

**18 SET TRANSMITTER RECEIVER**

**CIRCUIT INFORMATION**

Description. Operation. Values. Diagrams. Tests, etc., P.O. 5/-. Your address in block capitals, please.

**CAMPBELL**

Everland Road, Hungerford, Berks.

**SITUATIONS VACANT**

**CITY AND GUILDS** (Electrical, etc.) on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 20 Wright's Lane, London, W.8.

**TV AND RADIO, A.M.Brit.I.R.E., City and Guilds, R.T.E.B., Cert., etc., on "No pass—no fee" terms.** Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London, W.3.

**A.M.I.Mech E., A.M.Brit.I.R.E., City and Guilds, G.C.E., etc., brings high pay and security.** "No pass — no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. B.I.E.T. (Dept. 242B), London W.8.

(Continued on next page)



# Fly as an Air Electronics Officer in the R.A.F.

The domain of the Air Electronics Officer is the whole range of electrical and electronics equipments in an operational aircraft. This covers high frequency long range communication equipment (both voice and wireless telegraphy), VHF communications (short range radio telephone), ASV (air to surface vessel) radar, and the 'black boxes' for the electronic defence of the aircraft.

Having completed your highly-specialised training courses—during which you do about 123 hours flying, including two flights abroad—you fly in the V-bombers of Bomber Command or on Coastal Command reconnaissance.

You are a key man doing a key job—where success depends entirely on your own skill, training and flexibility. There is nothing run-of-the-mill about it. You have a career you can be proud of—and there lies satisfaction.

You are well paid from the very beginning—you earn £950 as a Flying Officer of 21. At 25 as a Flight Lieutenant, drawing full allowances, you could earn over £1,750. You travel the world, meeting old friends on almost every airfield, making new friends wherever you go. You live well in the Officers Mess, and have the opportunity of taking part in almost any sport you can name.

If you are under 26, fit, and hold or expect to gain, G.C.E. at 'O' level (or equivalent) in 5 acceptable subjects including mathematics and English language, you are eligible for a Direct Entry commission. Write for further details, giving date of birth and educational qualifications to Group Captain J. A. Crockett, R.A.F., Air Ministry (PW 841A) Adastral House, London, W.C.1.

THE FUTURE IS WITH THE R.A.F.

The Royal Air Force

## SITUATIONS VACANT (continued)

### CITY AND COUNTY OF BRISTOL BRISTOL TECHNICAL COLLEGE SCHOOL OF NAVIGATION

Technician required for School of Navigation and Marine Radio and Radar. Duties include servicing and maintenance of radio and electronics equipment, including Marine and Aircraft communication sets and demonstration equipment, issuing and recording spares and stores. Salary £555—£685 p.a. Grade Miscellaneous III/IV: superannuable.

Particulars and application forms from:— REGISTRAR.

BRISTOL TECHNICAL COLLEGE,  
ASHLEY DOWN, BRISTOL 7.

Quote: BTC 61/28.

**UNIVERSITY OF GLASGOW** — Biological Electronics Technician wanted to construct research equipment. Experience with valve and transistor amplifiers and/or pulse equipment desirable. Salary within the range of £490-£675 p.a. Applications should be sent to the Head of the Physiology Department, The University, Glasgow W.2.

**SERVICE ENGINEER** for Electric Organs required, to deal with the servicing of the Hammond Organ, both in this factory and at customers' premises. The suitable applicant must be thoroughly experienced in this type of work and good conditions are offered to the right man.—Apply Boosey & Hawkes Ltd., Deansbrook Road, Edgware, Middx. Tel: EDGware 5581.

### UNITED KINGDOM ATOMIC ENERGY AUTHORITY ATOMIC ENERGY ESTABLISHMENT, WINFRITH

Vacancies exist at the A.E.E., Winfrith, for

#### ELECTRONIC and INSTRUMENT MECHANICS

Applicants should have experience of electronic equipment and industrial process control instruments, and of work involving fault diagnosis, repair and calibration for a wide range of instruments used in nuclear reactors and associated experiments. The work requires a good knowledge of instruments for measuring and automatically controlling flow pressures and temperatures of liquids and gases, as well as pulse techniques, wide band and D.C. amplifiers, counting circuits and associated test equipment.

Excellent working conditions including sick pay and pension scheme. Housing may be available to the successful applicants, but this would be determined at time of interview.

Further details and an application form may be obtained on request from

THE LABOUR DEPARTMENT,  
A.E.E., WINFRITH, Dorchester, Dorset,  
quoting ref. IM/JAN.

### EDUCATIONAL

**WIRELESS.** See the world as a Radio Officer in the Merchant Navy: short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE,** Colwyn Bay.

**EDUCATIONAL (continued)**

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**DON'T FUMBLE** with Formulae. Master Mathematics quickly and easily the Understandable Way.



The Dryden School of **UNDERSTANDABLE MATHEMATICS**

11F Dryden Chambers, Oxford St. London, W.1.

Name \_\_\_\_\_  
Address \_\_\_\_\_

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths practical way. Postal instruction based on host of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. P.W., 12 RADIOSTRUCTOR, Reading.

**Radio Television & Electronics**

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE** prospectus stating subject to

**I.C.S.**

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11

**ELECTRONICS**

Key to YOUR future? An exciting career - A new Hobby - Your own spare or full-time BUSINESS!



New experimental course includes big kits for building test gear and a complete AM/VHF receiver.



**FREE** brochure from

**RADIOSTRUCTOR**  
DEPT. E77, READING, BERKS.

**EDUCATIONAL (continued)**

**LEARN RADIO AND ELECTRONICS** the new and practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault-finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11 P.W. RADIO-STRUCTOR, Reading.

**THE Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd.**, Membership Conditions booklet 1/- Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, 20 Fairfield Road, London. N.8.

**HANDICRAFTS**

**JEWELLERY** Simply made. Brooches. Rings. Marcasites. List Free. WEBBS, 46 Buraway, Hornchurch, Essex.

**SOUND RECORDINGS**

**RECORDING TAPE**, save up to 30% and for stock; also 50 second-hand recorders in stock. E. C. KINGSLEY & CO., 132 Tottenham Court Road, London. W.1. EUS6500.

**THE FAMOUS "TELEFUNKEN" TAPE HEADS**, 30/20 Kcs. TWIN TRACK. RECORD/REPLAY AND ERASE. BRAND NEW 30/- The Pair. LIST 5 Gns.

A. Fanthorpe Ltd., 6-8 Hepworth's Arcade, Hull, Yorkshire.

**NEW VALVES!**

Guaranteed Set Tested

**24-HOUR SERVICE**

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6. DAF66, DF66, DK96, DL96, SET of 4 26/-.

1D5	7/-	DL35	9/6	PCC89	9/-
1R5	6/-	DL42	5/11	PCF90	7/9
1S5	4/6	DL84	6/9	PCF82	7/6
1T4	3/3	DL96	9/-	PCL92	9/3
3S4	5/11	EB91	3/-	PCL83	11/6
3V4	6/9	EB41	7/9	PCL84	9/9
5U4G	4/6	EBF90	7/9	PL36	10/9
5Y3GT	5/9	ECL21	12/6	PL81	8/6
6Z6G	8/6	KCC40	14/6	PL82	8/6
6AM6	2/8	ECC81	4/9	PL83	6/8
6K7G	1/9	ECC82	5/9	PL84	8/-
6K8G	4/9	ECC83	6/9	PY32	11/-
6Q7G	5/8	EC94	3/-	PY30	7/-
6V6G	4/-	EC98	7/6	PY81	7/-
6V6GT	6/6	EC94	7/3	PY82	6/-
6X5GT	4/6	ECC82	8/3	PY83	7/3
12K7GT	4/3	ECH21	12/6	U25	11/6
12K9GT	3/-	ECH42	7/9	UABC90	8/6
12W7GT	4/8	ECC81	6/9	UAF42	8/-
12SN7GT	7/9	EF40	12/3	UBC41	7/-
35Z6GT	3/-	EF41	7/6	UBF90	8/-
35Z4GT	5/9	EF90	4/3	UCC86	7/-
AZ31	8/8	EF95	4/6	UCH21	12/6
CK35	11/9	EF98	8/3	UCH42	7/6
DAC32	8/6	EF98	6/9	UCH81	7/6
DAF91	4/8	EF91	2/9	UCL82	9/3
DAF96	8/9	EL41	9/-	UCL83	13/-
DF93	8/6	EL84	6/8	UL41	6/8
DF93	3/3	EY51	7/3	UF89	6/9
DF96	6/9	EY88	7/6	UL41	7/6
DH77	6/-	EZ40	6/-	UL84	6/6
DK32	10/8	EZ41	6/9	UY21	13/-
CK91	6/-	EZ90	5/8	UY41	5/8
DK92	7/3	EZ81	6/-	UY85	6/3
DK96	7/3	MU14	6/-	VP4B	8/6
DL83	7/6	PCC84	7/-	Z77	2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra Any C.O.D. Parcel 3/- extra. Office address, no callers.

**GERALD BERNARD**  
(Note new address—formerly of Leeds)  
83 OSWALDESTON ROAD,  
STOKE NEWINGTON, LONDON, N.16

**TRY ANY THREE BOOKS ON NO RISK FREE TRIAL**

No. 9  
**Pin-Point**  
**Transistor**  
**Troubles in**  
**12 minutes**



Trouble-shoot every type of circuit in ALL transistorized equipment! 525 pages; hundreds of illustrations; 120 check charts. 47/6.

No. 39 **LOOK!** NOW YOU CAN TAKE A COURSE IN RADIO AND ELECTRONICS FOR ONE TENTH THE USUAL COST!

By special arrangement, we are able to offer for the first time a new comprehensive course consisting of 35 lessons bound into a manual size 8in. 11in. Each page is divided into two columns. A wide column features the usual text, while a narrow column has the instructor's comments, helpful suggestions, additional pictures and remarks to simplify the difficult parts. We feel that many readers of *Practical Wireless* who require a basic course of instruction will find this manual of considerable assistance in their studies, 216 pages. Paper covers. Cash price 35/-. Time payment price 10/- cash with order and two monthly payments of 13/8.



No. 8  
**Pin-Point**  
**TV Troubles**  
**in 10 minutes**

Find the exact sound or picture trouble in ANY TV set from 700 possibilities, 300 pages; 300 diagrams; check charts, 31/8.

No. 16. REFRIGERATION SERVICE MANUAL. H. P. Manly.

Learn Refrigeration! This manual is a course in itself packed with solid information to enable you to do that repair job yourself. Used by many leading refrigeration firms as a standard reference. Postage 3d; pages together with 157 illustrations bound in cloth. An excellent buy at only 24/- plus postage.

No. 1 **SPECIAL OFFER!** COYNE ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES, total 1,088 pages, sturdy Vinyl washable covers, £3.18.6d. the set.

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point.

You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations. To get this special offer, send no money now, then 12/6 plus postage after free examination, and 20/- per volume.

**LIMITED OFFER! ACT NOW!**

Just mail coupon for free trial. After 7 days send off at low price or return unused and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books value not exceeding £5.0.0). To buy one book send one-half in 7 days, and one-half in 30 days.

TO SIM-TECH BOOK COMPANY (UK),

Mail Order Division, DEPT. A8, Gaters Mill

West-End, Southampton, Hants.

Please send me the Elementary Radio TV Set as per special offer.

RUSH (insert Book number here) ( ) ( )

Tick here if enclosing full price, we pay postage. Same 7 day money-back guarantee.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ County \_\_\_\_\_

Postage charges: Orders up to £3 allow 1/6,

£3 or over allow 2/- OVERSEAS ORDERS

**PROMPTLY SHIPPED** on receipt of full amount. Same guaranteed satisfaction.

# D. & B. TELEVISION

Phone: Cherrywood 3955  
Dept. A2 131 & 131a KINGSTON ROAD  
SOUTH WIMBLEDON, LONDON, S.W.19

"Compare our prices with any others"

For the **FINEST, FASTEST SERVICE** in the **COUNTRY** We are open from 10 a.m. Until Midnight. (1 p.m. Wednesday.) For any information or problems you have, Call or Phone, we are always pleased to help.

## NEW!

SEND FOR OUR COMPREHENSIVE L.O.P.T. Scan Coil L.B.O., F.B.O., F.O.P.T. LIST. Prices of nearly all makes and models, 2/6, post 6d. Invaluable as a service aid. The finest list ever compiled.

## HUGE PURCHASE ENABLES US TO SELL TRANSISTORS AT THESE ASTONISHING PRICES

Mullard: OC44, 9/-; OC45, 8/-; OC70, 6/-; OC77, 5/-; \*OC72, 6/-; OC76, 7/-; OC78, 7/-; \*OC81, 7/-; OC81D, 6/-; G.E.C.: GBT874, 8/-; GBT873, 7/6; \*GET114, 5/-.  
\* Available in matched pairs at 1/- extra.  
Mullard Diodes: OA70, 2/9; OA79, 2/9; OA81, 2/9; OA91, 3/6. G.E.C.: GEX34, 3/3.  
TURRET TUNERS, Various Makes: 10, 16, 38 Mc/s, 40/-

## EXAMPLE OF TRANSFORMER LIST

		L.O.T.		SCAN COILS	
	(New)	(Used)	(New)	(Used)	
FERGUSON:					
103T, 105T ...	69/9	35/-	60/-	35/-	
992/4/6/8 ...	69/9	35/-	60/-	35/-	
PYE:					
V4, VT4, V7,...	55/-	35/-	55/-	35/-	
VT7, CTM4 ...	55/-	35/-	55/-	35/-	
MURPHY:					
V214, V240, V250 ...	68/6	35/-	45/-		

## REGUNDED CATHODE RAY TUBES

all with 12 months' Guarantee  
ALL MAKES: 12in., £3.15.0; 14in., £4.5.0; 17in., £4.15.0.  
ADD: 10/- for 90°, 15/- for 110°, 5/- for Electrostatic Types.  
SECONDS, with 12-month Guarantee—ALL MAKES: 12in. £2.15.0; 14in., £3.5.0; 17in., £3.15.0.  
SECONDS. No Guarantee—ALL MAKES: 12in., £1.5.0; 14in., £1.15.0; 17in., £1.15.0.

10/- allowance on old tube if in good condition.  
**HUGE PURCHASE! Again passed on to you**  
T/V or coffee tables, veneered in walnut. Complete with 4 screw-on legs. Many other uses. Size: 15 x 18in. Amazing offer at only 14/6. P.P. 3/-.  
SPECIALLY made cabinets for the REPANCO JOURNEYMAN KIT, complete with 3 ohm speaker, dial and knobs. Well made in wood and covered in Vynidic. Colours: Yellow, White, Red. State second choice. 30/- each. P.P. 3/-.  
**HURRY WHILE STOCKS LAST!**

ALL VALVES ARE SOLD SUBJECT TO FULL GUARANTEE

## CURRENT VALVE LIST

AZ81	8/6	BCX84	7/8	KT33C	6/-	818	10/-	UL44	10/9	8U4	10/-
B36	5/6	BCX85	6/6	8P11	2/3	UL84	4/3	7C7	7/3	7C8	6/9
OB131	19/1	ECH21	12/3	KT61	8/3	8P3	2/8	UO8	14/6	7O9	7/-
OCB33	12/6	ECH35	9/-	KT68	6/3	U22	8/6	UO9	8/3	7T7	8/9
CL33	10/-	ECH42	7/8	KTW61	5/9	U24	10/-	UY41	6/-	7Y4	8/9
D77	3/-	ECH81	7/8	KTW63	5/9	U25	12/-	UY35	6/6	10P1	14/-
DAF91	4/6	ECL82	9/3	PC28	2/9	U28	8/8	W77	4/-	10C1	10/-
DAF96	6/6	ECL82	9/3	PC28A	7/-	U31	7/-	Z77	8/-	10C2	7/-
DF91	3/3	ECL83	11/9	PC289	8/9	U37	18/9	SU4	4/9	10P13	8/9
DF96	6/9	EP79	4/3	PCF90	7/-	U50	5/6	SV4	8/9	10P14	8/9
DB83	6/-	EP30	1/3	PCF92	7/9	U52	6/-	SX3	5/9	12A7B	7/3
EB77	4/6	EP80	4/6	PCF96	14/6	U11	9/-	SZ4	1/9	12A7C	4/6
DK91	6/6	EP91	3/-	PCL82	7/9	U281	9/-	6AL5	3/-	12A7U	5/6
DK92	7/-	EP92	4/-	PCL83	9/9	U282	14/6	6AM6	3/-	12AX7	6/3
DK96	6/9	EP95	6/3	PCL84	7/9	U301	17/8	8A7B	6/9	19BG6	14/6
DL91	7/9	EP98	8/9	PCL35	15/-	U901	22/-	8BG6	12/-	20P2	8/3
DL92	5/9	EP89	6/6	PL33	8/-	UA808	6/6	8EW6	7/6	20L1	12/6
DL94	6/6	EL33	7/9	FL36	9/9	UAF42	8/-	6CD6	25/6	20P1	9/6
DL96	6/6	EL38	12/-	PL38	14/6	UB41	7/9	6D2	3/-	20P3	12/6
EABC80	7/3	EL41	7/9	PL11	6/6	UBC41	7/9	6P1	4/6	20P4	16/6
EAF42	7/9	EL84	6/9	PL82	8/9	UBF99	7/9	6P12	3/-	20P5	14/6
EB91	6/9	EL80	6/9	PL83	6/9	UCB84	12/6	6P13	3/-	20P6	14/6
EB91	3/-	EM81	8/6	PL84	8/9	UCC85	7/9	6P14	9/-	30C1	7/-
EB93	4/6	EM84	8/6	PY31	7/-	UCF90	14/6	6P15	9/-	30FL1	9/3
EBC41	7/6	EV51	7/9	PY32	10/-	UCH21	12/3	6P38	6/3	30L1	7/-
EBF90	7/6	EX98	7/9	PT30	6/-	UCH42	7/-	6L11	12/-	30P4	10/9
EBF99	8/9	EZ40	6/9	PY81	6/-	UCH51	8/3	6L6	5/6	52KU	4/6
EEL31	20/-	EZ41	6/9	PY82	6/-	ULC83	12/6	6V6	5/-	52KU	10/9
ECC81	4/6	EZ80	6/-	PY83	8/-	UF42	3/9	6L18	8/-	55K10	10/9
ECC82	5/6	GZ32	8/9	PY88	12/-	UL41	7/9	6L19	12/-	54K10	8/6
ECC83	8/3	GZ34	12/8	PT30	8/-	UL46	7/-	6SN7	4/6	18B2T	14/-

These are only examples of our valves; if you do not see what you require send stamped addressed envelope for special quotation.

We pride ourselves that we can obtain and supply any TV spare. **OUR GIGANTIC STOCKS INCLUDE:** Line, Frame and Sound Output, Line and Frame Blocking, Osc., Trans., and Scan Coils for any make or model Television. Please ask us for ANY components you may require we are almost certain to have them. TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.s 12/6 inc. insurance. **SATISFACTION ASSURED. RETURN POST SERVICE.**

# AVO METERS

MODEL 7 £11.10.0. MODEL 8 £15.15.0. MODEL 9X £17.10.0. Guaranteed perfect. Complete with leads and batteries. Registered post and packing 5/- extra.

**AVO VALVE TESTERS.** Roller panel type. Can be used with adaptors for all types. Circuit data supplied. Tested. £5.19.6. 7/6 carriage. Details S.A.E.

**FERRANTI TESTMETER TYPE Q.** An extremely compact self-contained multimeter. Volts 0 to 30, 150, 500 AC/DC, with additional 0.3 v. DC and 0-15 v. AC. ranges; millamps 0 to 7.5, 30, 150 and 750 DC; ohms 0-25 KΩ. Accuracy BSS first grade. Knife-edge pointer and clearly calibrated 2 1/2 in. scale. 500 μV/ohm. With leads, prods, battery and instructions. In fitted velvet-lined 4 x 7 x 3 in. case. Brand new condition, tested. 49/6. P.P. 2/6.

**CRYSTAL CALIBRATION No. 10.** Good condition, tested, with instruction manual. ONLY 59/6 or AS NEW with three spare valves. Leads, etc. £4.10.0. P. & P. 3/6.

**PCR COMMUNICATIONS RECEIVER**  
Type PCR. Has self-contained speaker. Covers 850-2000, 200-550 and 16-50 metres.  
AS NEW CONDITION ..... £8.19.6  
Type PCR-2. Requires external speaker. Covers 850-2000, 200-500 and 13-50 metres.  
USED (Good condition) ..... £5.19.6  
Carriage (any type) 10/6. Full details S.A.E. Any model fitted with BRAND NEW INTERNAL POWER SUPPLY, guaranteed ready for use on A.C. mains £2 extra.

**Moving Coil Phones.** Finest quality Canadian, with Chamois ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable, 19/6, post 1/6.

We now stock The Pocket 4, a neat little job which can be made for 42/6. (Printed Circuit Version 52/6), and The Good Companion (a super job equal to the best). Easily constructed for only £9.19.6. Gladly demonstrated to callers.

# CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martins Lane, London, W.C.2

TEmple Bar 0645 Shop Hours 9-6 p.m. (9-1 p.m. Thursday) Open all day Saturday.

# GZAK: This Month's Bargains

## SCREENED CABLES

Screened Microphone Cable, 1st Grade, 9d. yd. 12-Core  
Screened Cable, 2 1/2 yd. 10-Core (5 Pairs) Screened Cable, 1/8 yd. All plus 2/- P. & P.

## AERIAL EQUIPMENT

**TWIN FEEDER.** 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telecon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.  
**COPPER WIRE.** 14 G., H/D 140it. 17/-; 70it. 8/6. P. & P. 2/-.  
Other lengths pro rata.  
**RIBBED GLASS.** 3in. aerial insulators, 1/9 each. P. & P. 1/6 up to 12.  
**CERAMIC FEEDER SPREADERS.** 6in. type F.S. 10d. each P. & P. 2/-.  
**CERAMIC "T" PIECES.** Type A.T. for centre of dipoles, 1/6 each. P. & P. 1/-.  
**2 METRE BEAM 5 ELEMENT W.S. YAGI.** Complete in box with 1 x 25in. mast head bracket. PRICE 49/-, P. & P. 3/6.  
**SUPER AERAXIAL CABLE.** 75 ohm, 300 watts, very low loss, 1/8 per yard. P. & P. 2/-.  
50 ohm, 300 watt coax, very low loss, 1/9 yd. P. & P. 2/-.

**Absorption Wavemeters.** 3.00 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham Bands marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. 22/6 post free.

**VARIABLE CONDENSERS.** All brass with ceramic end plates and ball race bearings. 50 pF, 5/9. 100 pF, 6/6. 160 pF, 7/6. 240 pF, 8/6, and 300 pF, 9/6. All fitted with rear extension for ganging. P. & P. 1/-. Also Flexible Couplers, 1/- each. B.I. 8 MFD, 1,200 v. D.C. Wkg. Capacitors, 12/6 each. P. & P. 2/-.

# CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS  
Dept. "P", 110 Dale End, Birmingham 4. (EN 1635)  
(No C.O.D. under £1 please.) (By return service.)

**EDDY'S (NOTTM) LTD.**  
116 ALFRETON ROAD  
NOTTINGHAM

**NIFE ACCUMULATORS.** 1.25 v. size 3 x 2½ x ¾ in. 7 amp hrs., weight 13ozs., 2/6 each. P. & P. 2/-. one only add 9d. per cell.  
**POCKET RADIO.** 2 transistor with speaker. Complete with all parts, wiring diagram and full instructions, 27/6. Batteries 1/-. P. & P. 2/-.  
**DIMMER SWITCHES.** Ideal for train speed regulators, 1/11, Post 1/3.  
**THROAT MIKES.** 2/- ea., Post 10d. Could be used for electrifying musical inst. etc.  
**VIBRATORS.** 12 volt, 4 pin, 4/11. 6 volt, 4 pin, 8/11. Post 1/6.  
**GERMANIUM DIODES.** 9d. each. 7/- dozen. Post 6d.  
**V.H.F. AERIALS.** 6/11, Post 1/-. Easy to fit. No technical knowledge required.  
**ACOS CRYSTAL PICK-UPS.** Turnover head (2 sapphire styli) 29/11. P. & P. 2/6.  
All Above are New and Guaranteed.

**New or Surplus VALVES**

Guaranteed and Tested by Return Post.

AC2	OZ4	5/11	6F15	8/6
PENDD	PY81	6/11	6F33	6/6
	PY82	6/6	615G	2/9
C1C	PZ30	9/6	615GT	3/9
CY31	PCC85	9/6	615M	4/3
DM70	PCL84	12/6	617G	5/-
DF91	PCL85	12/6	6K7G	1/11
DF92	PEN36C	8/-	6K8G	5/6
DK91	PEN46	5/11	6P25	9/6
DL93	P61	3/6	6Q7G	5/11
DAF91	R19	15/6	6SA7M	5/9
EAC91	SP61	2/6	6SG7M	4/9
EB34	TDD4	7/6	6S17M	5/9
EB41	TY86F	11/6	6SL7GT	6/6
EB91	U26	10/-	6SN7GT	4/3
ECC81	U35	9/6	6U4GT	12/6
ECC82	UF41	8/11	6X5G	5/11
ECC85	VP23	6/6	7C5	6/6
ECH42	VT52	2/6	10F1	6/6
ECL82	W5	7/6	10P13	9/6
EF36	IL4	3/6	12A6	5/-
EF37	IR5	5/6	12AH8	12/6
EF37A	IS5	4/9	12AH7	2/6
EF39	IT4	3/6	12K8	12/6
EF40	3A4	4/11	12AT6	7/6
EF42	5U4G	4/9	12K7	5/3
EF50	5Z4G	7/6	12Q7	5/3
EF86	6AC7	4/-	12BH7	10/11
EF91	6AU6	10/6	20D1	8/6
EF92	6A7	10/6	20P1	9/6
EF95	6AG6	3/6	25A6G	8/-
EL32	6B16	7/11	25L6GT	8/6
EL38	6B8M	7/11	30PL13	13/6
EL85	6BW6	7/6	35Z4	5/3
EL91	6BW7	7/6	50CD6G	
GT1C	6CH6	8/-		29/6
HL23DD	6C4	3/6	80	6/11
KT33C	6C5	4/9	954	1/6
KT36	6F1	6/11	955	3/6
L63	6F6M	6/6	956	2/11
MU14	6F13	6/11		

**BUILD YOUR OWN CAR RADIO!**



12 volts, please state). full instructions at Size: 7½ x 7½ x 2½ in. Speaker 17/11 extra (7 x 4 ellipt.) if required. Postage and packing 5/- extra per kit.

**10½ Gns.**

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers risk. Post and Packing 6d. per valve extra. C.W.O. or C.O.D. only. C.O.D. charge 3/- extra, S.A.E. with enquiries.

**RADIO CLEARANCE LTD.**

The oldest Component Specialists in the Trade

27 TOTTENHAM COURT ROAD, LONDON, W.1.

Telephone: MUSEUM 9188

TRADE ENQUIRIES INVITED

EST. 30 YRS.

IN THE HOME, IN THE CAR, BY THE SEA, IN FIELDS AFAR, THE

**"CONTESSA"**  
IS VOTED BEST OF ALL



A really remarkable 2-Band 6-Transistor Superhet Kit—25,000 satisfied customers and still in huge demand.

The Contessa is the professional looking set with the professional performance.

Study these brilliant features which cannot be found in any other kit—

- Waveband coverage of 530 kc/s to 1,620 kc/s and 160 kc/s to 270 kc/s.
- Assured reception of at least a dozen stations in daylight!
- Large clearly-calibrated station-named dial.
- Internal high-gain. FerroX aerial.
- 5 : 1 ratio slow motion tuning.
- Fitted with the latest 12,000-line high flux loudspeaker.
- Power of 410 milliwatts from the single-ended push-pull final stage.
- Specially designed aerial matching coil for use in a CAR.
- Only first-grade fully guaranteed matched transistors and diodes are used.
- Double tuned IF transformers for maximum gain and knife-edged selectivity.
- Fully drilled printed circuit panel marked with component numbers.
- The two-colour case measures 10 x 7½ x 3½ in. and weighs approx. 4 lbs. when assembled.
- Battery lasts 4 months with normal usage.
- Book supplied with detailed assembly instructions, diagrams and circuitry.
- Anyone can build this set—everything supplied just a soldering iron required.

Inclusive price for all associated components, cabinet and battery, complete in every detail, or our BUY AS YOU BUILD SCHEME, any parts sold separately. Send for comprehensive descriptive Manual and Parts List, 3/6 post free Plus 3/6 P. & Pkg.

**£10.19.6**

And now this is what you have been eagerly waiting for—

**THE "CAPRI"**



A MINIATURE pocket transistor kit that REALLY works, retaining the most attractive features of the famous "Contessa". SIX first-grade Mullard transistors and diode are employed in a highly sensitive superhet MW and preset LW circuit embodying the most modern design practice. A special 2½ in. high gauss loudspeaker provides surprising volume and a personal earpiece socket is also available. An attractive two-tone plastic case is supplied in two colours, Ivory/Red or Ivory/Blue, the full constructional details being given with each set of parts. The total MEASUREMENTS of the "Capri" are 4½ x 2½ x 1½ in.

SEE AND HEAR A WORKING MODEL TODAY

Inclusive price for all associated components, case and constructional data, complete in every detail on our BUY AS YOU BUILD SCHEME, ANY PARTS SOLD SEPARATELY. 9 v. battery 2/6 extra.

**£7.10.0**

plus 2/- P. & Pkg.

STAMPED and ADDRESSED ENVELOPE with any enquiry please. But regret no lists or catalogues—our stocks move too quickly!

PLEASE ALLOW FULL POSTAGE AND PACKING CHARGES

Terms of Business:

CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-

**SOUTHERN RADIO'S WIRELESS BARGAINS**

**PORTABLE TEST METERS.** (As featured in March issue, pages 1005 to 1010) 0-5000 ohms; 0-60 mA; 0-15 v., 0-3 v., 12/6 each.

**TRANSMITTER RECEIVERS.** "Type 38" with 5 valves. New but untested. No guarantee, 25/- each. Post paid.

**ATTACHMENTS FOR "38" TRANSMITTER-RECEIVER;** Headphones 15/6; Throat Microphones, 4/6; Junction Boxes, 2/6; Aerials, No. 1, 2/9, No. 2, 5/3; Webbing, 4/-; Haversacks, 5/6; Valves—A.R.P.12 4/6, A.T.P.4, 3/6. Set of five valves, 19/-. Postage on each item 1/6 extra (except valves).  
**ATTACHMENTS FOR "18" TRANSRECEIVER.** Headphones, 15/6; Microphone 4a, 12/6; Aerials, 5/-; Morse Key, 6/6; Valves—A.R.P.12, 4/6, A.T.P.4, 3/6, A.R.8, 7/6; Set of six valves, 25/-. Official booklet "18" T.R. Circuits, etc., 6/6 post paid. Postage extra (except valves) 1/6 each item.

**QUARTZ CRYSTALS.** Types F.T.241/F.T.243 2 pin 1/4 in. spacing. F.T.241 20 to 38.9 Mc/s (54th and 72nd Harmonic). F.T.243 5700 to 8650 kc/s (Fundamental), 4/6 each. Lists of available frequencies on request. Crystal Holders for F.T.241/243, 1/3. F.T.241/243 Crystals. New but not guaranteed (ideal for using the case or regrading). 12/6 per dozen. Post paid.

**RECORDING BLANKS.** New 13in., 6/- each or 15 complete in Tin, 6/4.

**BOMBSIGHT COMPUTERS.** Ex-R.A.F. Wealth of gears, motors, blowers, etc. Ideal for experimenters, £3.12.6, carr. paid.

**RESISTANCES.** 100 Assd. Useful values, new. 12/6 per 100.

**CONDENSERS.** 100 Ass. Mica Elec., Tub., etc. New 15/- per 100.

**MORSE PRACTICE SETS.** Key with Buzzer on Base, with battery. 12/6, postage 2/-.

**LUFBRA HOLE CUTTERS.** Adjustable. 1/4 in. to 3/4 in., 7/3.

**STAR IDENTIFIERS.** 1-AN. Covers both hemispheres, 5/6.

**VISUAL INDICATORS (10Q4).** Type 3 with 2 meter movements, 2 neons. New 12/-.

**MAGNETS.** Strong Bar, 2in. x 1/4 in. 1/6 each.

**COMMAND RECEIVERS B.C. 455 6-9 Mc/s.** Complete with 6 valves, 47/6 each.


POST OR CARRIAGE EXTRA, FULL LIST OF RADIO BOOKS, ETC., 3d.

**SOUTHERN RADIO SUPPLY LTD.**

11 LITTLE NEWPORT ST., LONDON W.C.2. GER. 6653

**NEW MODIFIED VERSION!**

'PW' 6-TRANSISTOR

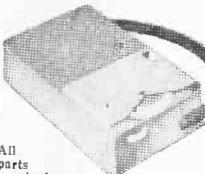

All parts required  
**£8.19.6**

**NORCOL LTD.**  
Castle Road, Camberley, Surrey  
Phone: Camberley 22760.

**MEDIUM AND LONG WAVE POCKET SUPERHET**

The latest version of this fine performer incorporates improvements giving even greater sensitivity and all round performance.

- ★ 250 mW Push-Pull Output on 2 1/2 in. P.M. Speaker.
- ★ Guaranteed first grade Matched Transistors.
- ★ High Q Internal Ferrite Rod Aerial
- ★ Printed Circuit and full instructions.

**ALIGNMENT & SERVICING**

We have tested and aligned many hundreds of these receivers, and are now offering this service to all purchasers of our kits. Details on request.

All parts sold separately. Send for illustrated building plans, 1/6 plus post. (Free with kit). Every item down to the last nut and bolt is supplied together with easy to follow, step by step instructions—no extras to buy.

**SURPLUS RADIO SUPPLIES**

2 LAING'S CORNER, MITCHAM, SURREY

SEND TO-DAY FOR OUR CATALOGUE

**400 BARGAINS**

At prices below manufacturing cost

Price 1/6 post paid

50µA METERS

by Sangamo Weston 19/6 p. and p. 1/6

**H.A.C. SHORT-WAVE EQUIPMENT AND SHORT-WAVE KITS**

Famous for over 25 years for S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C", Price 25/-. Two-valve Kit, Model "E", Price 50/-. New Addition: Model "K", Super sensitive "All Dry" Receiver. Special inc. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

**POST THIS COUPON NOW!**  
 "H.A.C." SHORT-WAVE PRODUCTS  
 (Dept. TH), 44 Old Bond Street, London W.1  
 Please send me FREE and without obligation your 1961 literature.  
 NAME.....  
 ADDRESS.....

**WORLD RADIO AND TV HANDBOOK 1962**

for listeners by Johansen 18/9, postage 1/-; Guide to Broadcasting Stations 1962, 3/6, postage 6d.

Amateur Radio Call Book 1962 by R. S. G. B. 4/6, postage 6d.

Mullard Maintenance Manual, 1962 edition, 16/-, postage 1/-.

Transistorised Test Equipment and Servicing Manual by Sinclair, 3/6, postage 6d.

Transistor Subminiature Receivers for the Constructor, 5/-, postage 6d.

Using an Oscilloscope by Easterling, 6/6, postage 6d.

Records and Gramophone Equipment by Bradley, 8/6, postage 8d.

Brimar Valve and T.V. Tube Manual No. 9, 6/-, postage 8d.

**UNIVERSAL BOOK CO.**  
 12 Little Newport Street, London, W.C.2 (adjoining Lisie Street)

**TRANSISTORS**

**RED SPOT 3/-**  
**WHITE SPOT 3/3**

XA102, 9/-; OC70, 6/6; OCT1, 6/6; OCT2, 8/-; (matched pair 16/-); OC44, 11/-; OC45, 10/-. All other types in stock.  
**CRYSTAL DIODES, 1/-;** Mullard OA70, OA81, 3/-; Miniature condensers for all transistor sets—0.01 mfd., 0.02 mfd., 0.03 mfd., .01 mfd., .02 mfd., .04 mfd., .05 mfd., all 1/- each. .1 mfd., 1/3; sub min., 2 mfd., 8 mfd., 2/6. Connecting wire, 6 colours, 1 yd. each 1/8; 2 yds. each 2/6.  
**Resistors:** All Values 10% watt, 6d. ea. The New JOURNEYMAN "6". Its amazing; plans etc., 1/6, or send S.A.E. for lists.

**OAKFIELD RADIO**  
 121 MACCLESFIELD ROAD,  
 HAZEL GROVE, STOCKPORT, CHESHIRE  
**MAIL ORDER ONLY**

**THE PUNCH YOU NEED!**

**HOLE PUNCHES**

<b>Instant Type</b>			
3 1/2" diameter	...	...	5/6 ea.
<b>Screw-up Type</b>			
1 1/2" diameter	...	...	6/8 ea.
1 1/2" diameter	...	B7G	7/2 "
1 1/2" diameter	...	B8A, B9A	7/8 "
1 1/2" diameter	...	...	8/3 "
1 1/2" diameter	...	...	8/7 "
1 1/2" diameter	...	...	9/6 "

Postage and packing 1/-

1 1/2" diameter int. Octal	...	10/11 ea.
1 1/2" diameter	...	13/3 "
1 1/2" diameter	...	15/6 "
1 1/2" diameter	...	B9G ... 17/11 "
1 1/2" diameter	...	... 20/4 "
2 3/8" diameter	...	Meter ... 27/8 "

Postage and packing 2/3


Complete set including postage and packing £7.10.0d.

**OLIVER & RANDALL LTD**  
 Dept. 7.  
 40 Perry Hill, London, S.E.6  
 Tel.: BECKenham 8262
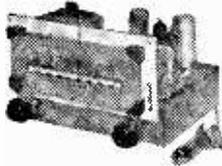
# Premier RADIO

23 TOTTENHAM COURT ROAD, LONDON W.1  
and at 309 EDGWARE ROAD, LONDON W.2

Tel: MUSEUM 3451/2  
Tel: PADDINGTON 6963



## A COMPLETE SELF POWERED FM TUNER

May be built for only **£4.19.6** plus 4/- p. & p.

This tuner has been designed to the highest possible modern standards with all the features found only in the more expensive Units and yet still within a price range that all can afford. No extras required.

### STAR FEATURES:

- ★ Permeability Tuning.
- ★ Philips FM Tuning Unit.
- ★ Absolutely no drift.
- ★ Frequency coverage: 88-100 Mc/s.

- ★ Two L.F. Stages and Discriminator.
- ★ OA81 balanced diode output.
- ★ Valve line up: ECC85, 2—EF80, EZ80 Rectifier.

Attractive full vision maroon and gold Glass Dial, size 7 x 3in., overall dimensions of Tuner 8 x 7 1/2 x 6 1/2in.

## THE TELEFUNKEN STEREO HI-FI AMPLIFIER

Original price 16 gns.

NOW ONLY **£7.19.6** p. & L. 5/-



### BRIEF SPECIFICATIONS:

- ★ Power Output 5 watts total (2 1/2 watts per channel).
- ★ Total harmonic distortion less than 1% at 1 watt output.
- ★ Frequency Response: 30 c/s to 40 Kc/s 20dB, 45 c/s to 30 Kc/s 4dB.
- ★ Sensitivity sufficient for all normal inputs from Tape Recorders. Pick-ups. Microphones. Radios.

- ★ Power Requirements 110, 125, 150, 220, 240 volts A.C.
- ★ Piano key action.
- ★ Preset/one tone control.
- ★ Size: 12in. wide x 9in. deep x 2in. high.
- ★ Weighs 9lbs.
- ★ Finish: Hammered enamel in grey/green with gold trimmings. Controls and press buttons in cream with black, blue and red lettering.

## STAR FEATURE PURCHASE

WE CAN OFFER THE FABULOUS SAVILLE DOUBLE 12 STEREO POWER AMPLIFIER AND MATCHING SAVILLE 12P CONTROL UNIT FOR ONLY **25 Gns.** p. & p. 12/6. Original Price 49 gns.

*Brief specifications:*  
Input sensitivity P.U. 3 and 45 mv, Tape 1 and 20 mv, Radio 50 mv. Output 12 watts per channel, 20 watts peak, 2 EL84 push-pull output per channel.  
Controls 6-pos. sel. volume on/off, bass, treble and balance. THIS ARTICLE IS BRAND NEW AND GUARANTEED.

Why not convert your battery portable to mains operation with the **COSSOR MU2 BATTERY ELIMINATOR!** This Eliminator is completely assembled and supplied with 4ft of Mains Lead and Torpedo Type of On/Off Switch. It is housed in 2 Metal Containers approximately the same size as the AD35 and B126 Batteries, and suitable for receivers using DK96 range values for use on 200-250V A.C. mains. Size: L.T. Unit 3in. x 2 1/2in. x 1 1/2in. H.T. Unit 4in. x 2 1/2in. x 2in. Original price 3 gns. **39/6** plus 2/- P. & P.

## STOP! LOOK! TRANSISTORS from 2/6

**YELLOW SPOT A.F.** 6 volt, 2/6 each.  
**RED SPOTS 3/-** each, 3 for 8/6.  
**WHITE SPOTS 3/-** each.  
**YELLOW/GREEN 3/3** each, 3 for 9/-.  
**RED/YELLOW R.F.** 5/- each.  
**SURFACE BARRIER SB305 9/-** each.  
**XA10 4s 4/6** each, **XB1 12s 4/-** each.  
**POWER TYPE XC141 10/-** each.  
Few only G.E.C. Transistors S1 A.F. S2 Low R.F. S3 Output, All one price 2/6 each.

**MULLARD TRANSISTORS**  
OC71 6/6, OC72 8/-. matched pair 16/-.  
OC78 8/-. OC81 8/-. OC45 10/-. OC44 11/-.  
OC170 13/6, OC171 14/6.  
**DIODES OA70, OA79 or OA81 3/-, OA91 or OA95 Miniatures 3/6** each.  
**TRANSISTOR HOLDERS, 1/3** each, 3 for 3/6.  
**GERMANIUM DIODES, 1/-** 3 for 2/6.  
**MINIATURE TRANSISTOR TRANSFORMERS, P-P Driver 4.5 : 1 P-P Output 20 : 1.** Boxed with Spec., 9/6 pair.  
**CRYSTAL SET COILS DRX1 2/6.**  
**REPANCO DRR2 Dual Range Coils, 4/-.**  
**REACTION CONDENSERS, .0001, 3/-, .0003 3/9, .0005, 4/-.**  
**J.B. DILECON TYPE, .0001, .0003 Or .0005** all 4/9 each.  
**CRYSTAL EARPIECES** with Lead and Plug, 8/6.  
**LOW IMP EARPIECES, 8/6.**

All Parts available for P.V. "Tutor" MINI-AMP and the "CITIZEN Circuits."

ALL SENT POST FREE IN U.K. by  
**PETHERICK'S RADIO SUPPLIES**  
22 High Street, Bideford, N. Devon  
Tel.: Bideford 1217  
S.A.E. WITH INQUIRIES PLEASE

## TV TUBE RESTORER EXTRA LIFE, EXTRA BRILLIANCE

PLUGS ON TO YOUR  
TV TUBE  
ANY SIZE  
PATENTED



Important! State Make, Model No. Name and Address in Block Letters Please.

STANDARD MODEL .. 22/8  
DE LUXE MODEL .. 30/-  
Postage 2/6 either model.

**SINCLAIR ELECTRONICS** Dept. P.W.5  
18 Newport Court Charing X Rd. WC2  
Terms: C.W.O., C.O.D.

## BBC - ITV - F.M. AERIALS




**B.B.C. (BAND 1).** Telescope loft, 18/6. External S/D, 26/3.  
**I.T.V. (BAND 3).** 3 Element loft array, 24/-. 5 Element, 32/6. Wall mounting, 3 Element, 33/8. 6 Element, 41/3.  
**COMBINED B.B.C. + I.T.V.** Loft 1+3 Element, 41/3. 1+5 Element, 48/6. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

**F.M. (BAND 2).** Loft "H" 28/-. 3 Element loft, 52/8. S/D loft, 12/6. External S/D, 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable. 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept.P.W.)**  
3B, Godstone Road, Kenley, Surrey.
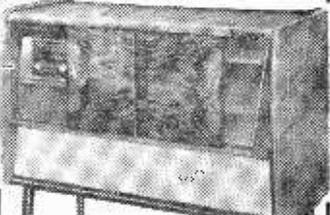
## CABINETS & HI-FI EQUIPMENT

We can supply any Cabinet to your own specification



### "Grosvenor" £22.1.0

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on:  
**THE LARGEST RANGE OF CABINETS IN THE COUNTRY**

Equipment is also our speciality. **SEND TODAY for a free copy of the Lewis Radio cabinet catalogue—the most comprehensive ever prepared.**



100 (P.W.22) Chase Side, Southgate, London, N.14. Pal 3733/9666

# RADIO BOOKS

**NEW PICTORIAL APPROACH TO LEARNING.**  
**BASIC ELECTRICITY, 5 parts.**  
**BASIC ELECTRONICS, 6 parts.**  
 The Complete Set sent on payment of first instalment.  
**LEARN WHILE YOU PAY FOR ONLY 2/6 PER WEEK**  
 Write for FREE Illustrated Prospectus giving details of instalment plan.

**RADIO, TELEVISION AND ELECTRONIC DATA BOOK 4/-**  
**EXTRA EQUIPMENT FOR YOUR TAPE RECORDER.** Describes Mixer-amplifier, Monitor-amplifier, Programme meter etc. 6/6.  
**PRACTICAL TRANSISTOR AUDIO AMPLIFIERS** for home constructor. 4/-  
**HI-FI TRANSISTOR SET TECHNIQUE.**  
**TRANSISTOR CIRCUITS** for Radio Controlled models. Howard Boys. 8/-  
**SUPER SENSITIVE TRANSISTORISED POCKET RADIO.** 4/-  
**INTERNATIONAL STATION LIST.** 3/-  
**TRANSISTOR CIRCUITS** Nos. 1, 2, 3, 4, 3/- each. Each book gives instruction for building ten different Transistor Units.  
**COIL DESIGN AND CONSTRUCTION MANUAL.** 5/6.  
**HI-FI TAPE RECORDER.** 3/-  
**ONE VALVE RECEIVERS, TWO VALVE RECEIVERS, THREE VALVE RECEIVERS, FOUR VALVE RECEIVERS.** 1/9 each. Each book gives full comprehensive instructions, diagram, etc.  
**BOY'S BOOK OF CRYSTAL SETS.** 2/-  
 4 different circuits fully illustrated. 3/-  
**HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER.** By Guy. 9/-  
**HIGH FIDELITY LOUDESPEAKERS ENCLOSURES.** 5/6.  
**TRANSISTOR SUPERHET RECEIVERS** Includes circuit diagrams of 50 different Receivers. 8/-  
**40 CIRCUITS USING GERMANIUM DIODES.** 3/6.  
**RADIO VALVE DATA** (Wireless World) 7th edition. 7/-  
**BRIMAR VALVE MANUAL** No. 9. 7/-  
**GUIDE TO BROADCASTING STATIONS** (Wireless World) 12th edition. 4/-  
**MULLARD REFERENCE MANUAL OF TRANSISTOR CIRCUITS.** 13/6.  
**ELECTRONIC NOVELTIES.** Bradley 5/6.  
**ELECTRONIC GADGETS.** Bradley 4/-  
**RADIO CONTROL OF MODELS.** By Sommerhoff 5/6.  
**SERVICING TRANSISTOR RECEIVERS.** Pettit. 6/6.  
**USING AN OSCILLOSCOPE.** 7/-  
**BEGINNERS GUIDE TO RADIO.** Camm. New and Revised Edition. 8/6.  
**RADIO TEST GEAR MANUAL 3/-**  
**TRANSISTOR SUB-MINIATURE RECEIVERS MANUAL 5/6.**  
**RADIO SERVICING.** By Patchett. Vol. I. Basic Electronic Technology. 5/6.  
 Vol. II. Intermediate Radio Theory. 9/-  
 Vol. III. Final Radio Theory. 6/6.  
 Vol. IV. Fault Finding. 5/6.  
 All above titles include postage.  
 SEND STAMP FOR LISTS

**SELRAY BOOK CO.**  
 60 HAYES HILL, HAYES, BROMLEY KENT.  
 Tel. HURStway 1818

## 18,000 O.P.V. MULTIMETER KIT

Ranges 0-0.25 and 2.5 V DC; 10, 25, 100, 250, 500, 1000 V AC DC, and output volts; Ohms 100 ohms to 10 Meg. (two ranges); 0.25, 2.5, 25, 250 mA DC (2.5A range 4/- extra). Kit comprises new 3 x 2 1/2in. Weston 0-50 microamps m.c. meter, all 1% multipliers, 1% ready adjusted shunt, potentiometer resistor, 1% adjusted for each meter, 3 other resistors, 1 condenser, meter rec., knobs, switches, sockets, pots, circuit, instructions, wiring diag. scale (ohms, dB, uF, mA & V. 10V AC scales) i.e. everything except case and battery. Details of 200 pF-0.5uF range. Price 69/11, post free. Circuit, scale etc. 9d. free with kit. 0-50uA meter as above, with circuit, etc. 25/- post 1/6. Multimeter scale fitted to meter 2/6 extra.  
 1% High Stability Resistors. S.A.E. list.

**PLANET INSTRUMENT CO.**  
 25 DOMINION AVE., LEEDS, 7

**POCKET RADIO**  
**ASTOUNDING RESULTS**  
 Covers medium and long waves.  
 No aerial or earth required.  
 Very compact; personal earphone.  
**ALL PARTS 59/6, plus post 2/-.**  
 Write for details (3d. stamp) before you buy elsewhere.

Red Spot Transistors 2/3, White Spot 2/3; Bargain set, 6 Ediswan Transistors (1-XA102, 2-XA101, 1-XB103, 2-XC101) and Diode for Superhet, 39/6. All parts "P.W." Pocket Superhet (Mullard transistors), £8.5.0; Sub-min. Electrolytics 2, 4, 8, 10, 16 mfd, 2/-; 50, 100 mfd, 2/9. M.C. Earpiece (used as speaker), 5/-; Mullard, OC71, 6/-; OC72 7/6; OC44 9/6; OC45 9/-; Silicon Rectifier bargain 70 p.i.v. 1/2 amp., 3/3; Westlake Contact Rectifier 250 v., 60 mA, 7/6; Transformer 250-0-250 v., 6 v. and 5 v., 15/-; Packard Bell Amplifiers, new 12/6; Garrard Portable Record Player, cabinet, battery turntable 45 r.p.m. and P.U., takes trans. amplifier, £3.10.0, plus carr. 3/9. Real bargain. Limited quantity.  
**TERMS.**—C.W.O. Post extra, excess refunded. Our Reflex Rx., best 2-transistor Receiver. Send 10d. stamps for notes.

**MOORE'S EXPERIMENTAL SUPPLIES**  
 8 & 10 Granville Street, Sheffield 2  
 Tel.: 27461

# 2 METRES!

The thrills of 144 Mc/s can now be yours for only 39/6, complete kit! Tunable range 150-100 Mc/s, simplified construction, etc., write today for descriptive literature. Also if a newcomer-beginner to Amateur Radio, ask for free copy of the world-famous "Globe-King" kits and receivers—stamp to cover postage costs appreciated. Write now to makers:

**JOHNSONS (Radio)**  
 St. Martins Gate, Worcester

**NEW REPANCO TRANSISTOR TRANSFORMERS**  
 Type TT45 Push Pull Driver Ratio 4-5:1 +1  
 Type TT46 Push Pull Output Ratio 4+4:1  
 Type TT49 Interstage Ratio 4-5:1  
 All with High Permeability Nickel Iron Cores  
 Size: 3/8" x 5/8" x 5/8"  
**5/- Each**

**Radio Experimental Products Ltd.**  
**33 MUCH PARK STREET, COVENTRY**

# PADGETTS RADIO STORE

40 MEADOW LANE, LEEDS 11  
 Phone: Cteckheaton 2886.

**SCR522, 1X and TX.** Less valves and crystals, otherwise complete. 15/- carriage 7/6. Receiver only 7/6, carriage 5/-.

**Complete TV Chassis.** For spares less valves 12in. four for 10/-, carriage 5/-. 14in. chassis, four for 15/-, carriage 7/6.

**TV Tubes Regunned.** 12 months guarantee. Old glass not required. 12, 14, 15, 18 and 17in. Any make all one price, £3.15.0. Carr. & Ins. 7/6.

**Perfect Reclaimed Tubes.** Six months guarantee. 12in. 17/-, 14in. Mullard only £1.10.0 carriage and insurance 7/6.

**P.M. Speakers.** All perfect, removed from TV sets. 3 ohms coil. Goodman, Phillips, Rola, R. and A. etc. 5in. 6/6. 6in. 4/-, 6 x 4in. 5/-, 7 x 4 6/-, 8in. 6/-. Post 2/6 extra.

**Crystal Diodes.** Now only 6d. post 3d. 5/- doz. post free.

**NEW VALVES, Ex-units. All post free.**  
 6K7 2/-, 6X5 4/-, 6V6 3/-, 6V6GT 4/-, 6AQ5 3/6, 6C4 2/-, KT88 4/-, DH63 4/-, EF81 1/9, EL81 1/9, EF92 1/9, EF50 1/6, 8/- doz. VR150/30 4/-, IS4 2/-, 5U4 4/6, 954 1/6, EB91 1/6, 9001 9d., 5/- doz. DLS10 1/-, 6/- doz. VR50/VR52 6d., 4/6 doz. Valves removed from TV sets. Tested on a Mullard Valve Tester, and are 100% as new. They carry a 3 months' unconditional guarantee.

EF80 1/9, 10/- per doz. EF80, Grade 2. 6d., 4/- per doz.

ECL 80	4/8	6G6	2/6	U25	5/-
ECC82	5/-	6X3	2/6	U281	5/-
EL38	4/6	6LD20	5/-	U329	5/-
EY51	4/-	6SN7	2/9	KT38	5/-
EBF80	4/8	10C2	2/-	PL81	5/-
EB91	1/-	10F1	3/-	PY81	5/-
EF91	1/-	or 15/-	doz.	PL82	5/-
EL91	1/-	10P14	5/-	PY80	5/-
6P25	4/-	10P13	5/-	PL38	5/-
6P28	5/-	20D1	3/-	PZ30	5/-
6F1	2/-	20P1	5/-	B36	4/6
6F14	2/-	20L1	5/-	N37	5/-
6SS7	2/-	185BT	8/6	L63	3/-

**TV Converters** less valves and knobs. Coils fitted 2 and 10. Ekco, Ultra, Marconi, etc. 2/6, 2/- post.

**Cyclon Converters.** Complete with valves and knobs. 25/-, post 2/-. Coils fitted 2 and 10.

**Tube Unit** with 3in. tube, valves and A.C. mains transformer, this will make a good scope. These units are not new, but condition good. £2.5.0. Carriage 8/6.

**Small Speaker Transformer** ex TV chassis. 1/6. Post 1/3. Doz. lots 15/-, post free.



## 19'9 EXTENSION

Ideal for kitchen, bedroom etc. In polished cabinet with 5in. speaker and lead. Carr. 4/3.

### SPEAKERS

8/9. 6in. and 7 x 4ins. Ex. manufacturers salvage. P. & P. 3/3. Elliptical 15/9. Brand New. 7 x 4 and 8 x 3ins. Slot type. P. & P. 3/3. Miniature 16/9. Brand New 3in. P. & P. 1/-.

### 18'9 SOLDERING IRON

6ins. long. 30w. 230V. A.C. For lightweight applications. Can be carried easily while hot. In vinyl bag, with lead and plug. Carr. FREE.

### 15% TUBES

31/74, 124, 153. Ex-rental stock. Guaranteed working. Carr. 6/-.

**35/-** 14KP4-38/24. Ex-rental replacements, guaranteed working. Carr. 5/-.

VALVES 9d. 6d1, 6d2, 6F12, 6F13, 6F14, 6F15, 8D3, 9D2, 15D2, 75, D77, D152, EA50, EB91, ECC81, Post 1-9d, 6-1/6. Many more.

**P. P. COMPONENTS LTD.**  
 628 Romford Road, Manor Park, E.12.  
 MAIL ORDER ONLY  
 Stamp for FREE catalogue.

**D.C. SUPPLY KIT**, 12 v. 1 a. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses, Chanke Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 33/9.

**SELENIUM RECTIFIERS**

F.W. BRIDGE	H.T. Types H.W.
8/12v. 1a. ... 3/11	150 v. 40 m.a. ... 3/9
8/12v. 2a. ... 6/11	250 v. 50 m.a. ... 3/11
8/12v. 3a. ... 9/9	250 v. 80 m.a. ... 4/11
8/12v. 4a. ... 12/3	250 v. 80 m.a. ... 5/11
8/12v. 6a. ... 15/3	250 v. 250 m.a. ... 11/9
8/12v. 15a. ... 35/9	<b>CONTACT COOLED</b>
24 v. 2a. ... 14/9	250 v. 80 m.a. H.W.
	8/11. 250 v. 50 m.a. F.W. (Bridge) 8/11

**B.S.R. MONARDECK TAPEDECKS** Speed 3 1/2 in. per sec. High quality recording heads, 26/19/6. Carr. 5/-  
**SPECIAL OFFER OF BRAND NEW BRIMAR TRANSISTORS.** TS1 Audio lots of three, 8/11; TS7 R.F. three for 14/9.

**EX. GOVT. CASES.** Size 14-10 1/2 in. high Well ventilated, black crackle finished, undrilled cover. **IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE OR COVER** COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/- postage.

**LINEAR TREMOLO/PRE-AMP UNIT** Type TPUI with 2 controls volume, amplitude and frequency. Inputs for guitar and microphone. Requires power supply of 250 v. 10 m.a. and 6.3 v. 1 a., available from any R.S.C. or LINEAR amplifier. The unit is merely connected to normal input socket of hi-f amplifier or Guitar amplifier. Only 5 gn.

**R.S.C. GRAM. AMPLIFIER KIT.** 3 watts output. Negative feedback. Controls Voi. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit etc., supplied. Only 38/9. Carr. 3/9.

**HI-FI 10 WATT AMPLIFIERS**  
Brand new. Manufacturer's discontinued line. Fitted latest Mullard valves. Dual inputs for "make" and gram. etc. Bass and Treble Controls. High sensitivity and quality. Output for 3 ohm or 15 ohm speaker. For 230-250 v. A.C. **£7.19.6**  
Carriage 7/6.

**PORTABLE TRANSISTOR RADIO DESIGN** with 7 x 4 in. loudspeaker and Car Aerial Socket. Attractively designed and covered cabinet, size 8 x 10 1/2 x 3 in. Gold dials with revolving perspex covers. M. and L. wavebands. Six first grade Brimar Transistors and Printed circuit. Easy to follow instructions and diagrams. 2/6. Total cost of parts only 49/10/6, carr. 3/9. Demonstration models at all branches.

**R.S.C. TRANSISTORISED GRAM AMPLIFIER.** Output 1 watt, for 3 ohm speaker. Transistors Rdswan XB13, XB13, XC101A, XC101A. Suitable for any normal crystal pick-up. Only 8/9.

**MULTI-METERS.**  
**CARY A10.** Basic Meter sensitivity 155 micro-ohms. A.C. and D.C. range £4.10. **CARY H20.** Sensitivity up to 10,000 ohms per volt. A.C. and D.C. £6.10.0.  
**S.A.E. will bring leaflets on A10 or B20.**

**RELAYS.** Carpenters' Type. Polarised 2 times 9,500 turns at 1,685 ohms. 13/9. Miniature Type G.E.C. 670 Sealed, wire ends, 4 covers, platinum M1095, 12/9.

**SPECIAL OFFER EX. GOVERNMENT SELENIUM RECTIFIERS.** 12 v. 15 amp. with large square cooling fins. 19/9 each.

**EX. GOVT. SMOOTHING CHOKES.** 230 mA. 3-5 H. 50 ohms. Farmeko 8/9; 100 mA. 5 H. 100 ohms 3/11; 150 mA. 10 H. 50 ohms 9/9; 80 mA. 20 H. 900 ohms 5/9; 120 mA. 12 H. 100 ohms 8/9; 50 mA. 50 H. 1,000 ohms 6/9; 100 mA. 10 H. 100 ohms 6/9; 60 mA. 5-10 H. 250 ohms 2/11.

**EX. GOVT. MAINS TRANSFORMERS**  
Primaries 200-250 v. 50 c.p.s. A.C.  
250v. 60mA 6.3v. 2a ... .. 11/9  
250-0-250v. 60mA 6.3v. 2a ... .. 15/9  
270-0-275v. 100mA 6.3v. 7a. 5v. 3a ... .. 22/9  
300-0-300v. 60mA 6.3v. 2a ... .. 12/11  
300-0-300v. 100mA 6.3v. 2a. 5v. 2a ... .. 18/9  
3,500v. 5mA 2v. 2a ... .. 39/9  
0-35-40-45-50v. 300mA 6.3v. 3a ... .. 17/9  
12v. 20a. (carr. 7/6) ... .. 49/9

**EX. GOVERNMENT ACCUMULATORS.** Size 7 1/2 x 4 x 2 in. 2v. 16 A.H., brand new, 6/9 ea., 3 for 15/6.

**R.S.C. BABY ALARM or INTER-COMM. KIT.** Complete set of parts with diagrams, etc. Master Unit housed in veneered walnut cabinet. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Only 79/6, carr. 5/-. Or assembled ready for use £5.15.0.

**COMPLETE POWER PACK KIT, 19/11-** Consisting of Mains Trans., Metal Rectifier Double electrolytic, smoothing choke, chassis and circuit. For 200-250v. A.C. mains. Outputs 250v. 60mA. 6.3v. 2a.


**R.S.C. POWER PACK, 39/9.** Louvred metal case only 8 x 5 1/2 x 2 1/2 in. Stove enamelled. For 200-250v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA. fully smoothed and 6.3v. 2a. Suitable for power requirements of almost any Pre-amp or Radio Tuner.

**R.S.C.**  
(Manchester)  
Ltd.

Personal Shoppers to: **LIVERPOOL:** 73 Dale St., 2. **BRADFORD:** 58 Morley St. (above Alhambra Theatre)  
**BULL:** 51 Saville St. (8 mins. from Lime St. or Exchange Stations)  
**MAIL ORDERS to:** 29-31 Moorfield Road, Leeds 12. **TERMS:** C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/9 extra, under £5 3/8 extra, under £5. Open 9 to 6, Weds. until 1 p.m. except Manchester, open all week. Trade supplied. B.A.R. with all enquiries

**MANCHESTER:** 18 Brown St. (Market St.)  
**LEEDS:** 5-7 County (Meeces) Arcade, Brigstae.

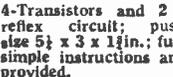**The NEW 'SAVOY'**  
**4-TRANSISTOR**  
**POCKET RADIO**  
WITH MOVING COIL SPEAKER  
ABSOLUTELY NO SOLDERING  
**NO DRILLING**  
**NO AERIAL REQUIRED**



4-Transistors and 2 diodes; 5-stage reflex circuit; push-pull output; size 5 1/2 x 3 x 1 1/2 in.; full medium wave; simple instructions and assembly tool provided.  
**95/-** Plus battery 2/- extra Postage and packing 3/- All parts sold separately  
**(PW) SAVOY ELECTRONICS LTD.**  
15 Maiden Lane, Strand, London W.C.2 (Back of Adelphi Theatre)

**FIRST-CLASS**  
**RADIO COURSES . . .**  
**GET A CERTIFICATE!**  
**QUALIFY AT HOME—IN SPARE TIME**

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

**FREE GUIDE**  
The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-proving qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches)** etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**  
Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.  
**FOUNDED 1885—OVER 150,000 SUCCESSES**

**NATIONAL INSTITUTE OF ENGINEERING**  
(Dept. 461), 148 HOLBORN LONDON, E.C.1  
S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.

**3-TRANSISTOR**  
**POCKET RADIO**  
WITH MINIATURE LOUDSPEAKER  
ABSOLUTELY NO SOLDERING  
REQUIRED

**39/6** Superb appearance. Simple instructions. Built in an evening. No drilling. No soldering. Complete in every detail. Receives entire broadcast band. Aerial required in certain areas. Pocket size 4 1/2 x 2 1/2 x 1 1/2 in.

Or the more powerful **SAVOY SUPER 3 55/6**  
Three transistors and 2 diodes in a 5 stage reflex circuit.  
ALL PARTS SOLD SEPARATELY  
Battery 1/- extra. P. & P. 2/-  
**(PW) SAVOY ELECTRONICS LTD.**  
15 Maiden Lane, Strand, London W.C.2 (Back of Adelphi Theatre)

**RES/CAP. BRIDGE** 38/- p. & p. 2/6  
Checks all types of resistors, condensers 6 RANGES  
Built in 1 hour. Direct reading.  
**READY CALIBRATED**  
Stamp for details of this and other kits.  
**RADIO MAIL (DEPT. UP)**  
Raleigh Mews, Raleigh Street, Nottingham

**JAMES H. MARTIN & CO.**  
Radio & Television Component Service  
Finthwaite, Newby Bridge  
Ulverston, Lancs.  
Lists available. Inland 3d, stamp only  
Overseas, airmail 5/- refundable.

**FIDELITY "CORONET"**



Inc. Battery

**£9.19.6** Reg. Post 2/6

**6-TRANSISTOR MEDIUM & LONG WAVE POCKET RADIO**

- Size 2½ x 4½ x 1½in.
- Quality Push-Pull Speaker Output.
- Guaranteed for 12 months.
- Phone and Tape Sockets.
- Carrying Case.

**ALL BRITISH DESIGN AND CONSTRUCTION**

Attractive Two-tone Moulded Cabinet. Very sensitive. Ideal present for any occasion. Built and Ready to Use.

**AVO-7 MULTIMETER**



Famous AVO Multimeter. Reconditioned and fully Guaranteed.

Supplied with batteries, test leads, instructions. At the NEW LOW PRICE

**£11.10.0** Reg. Post 5/-

● LEATHER CASE 30/- EXTRA ●



**CRYSTAL LAPEL MICROPHONE**  
Ideal for portable tape recording, etc. 17/6. P.P. 1/-.



**4000 Ohm Headphones**  
Lightweight very sensitive. 12/6. P.P. 1/-.

**RECORD PLAYER AMPLIFIER**

- 2-watt output.
- Ready built with Valves and 8 x 5 Speaker, Tone and Volume controls. Printed circuit.

**75/-** P.P. 2/-

Ideal for Portable Record Player.

- UA8 4-speed Record Changer, ideal for above. £6.19.6. P.P. 3/6.

**STEREO AMPLIFIER**

**BARGAIN OFFER**

- 2 watts per channel.
- Full tone, balance and volume controls.
- Complete with sockets, dials, etc

**97/6** P.P. 2/6

Suitable Speakers, 9 x 5in., 49/6 pair. UA14 Stereo Deck, £8.19.6. P.P. 3/6.

READY BUILT AND TESTED



**POCKET TESTER MODEL TE10**

Volt-Ohm-Milliammeter ★ Size 4½x3½x1½in. Over 20 Stars

**10,000 ohms/volt**

Price, inclusive of Test Prods, Battery and instructions.

**£5.19.6** P.P. 1/6

**Top Quality Meter—Fully Guaranteed.**

Also Model 200H, 20,000 ohms/volt. Same size SEND FOR DETAILS OF COMPLETE RANGE OF METERS. **£6.19.6** P.P. 1/6.

**POCKET IRON**

★ Pocket Soldering Iron, 220/250 v. A.C./D.C. 30 watts, complete with mains plug, case, etc. Handle unscrews to cover element, enabling iron to be carried in pocket. 18/6. P.P. 1/-.

**Telephone Adaptor**

★ Ideal for recording telephone conversations. Supplied with screened cable. Fitted rubber sucker. 14/- P.P. 9d.

**CRYSTAL MICROPHONES**

PRICES DOWN FULLY GUARANTEED



ACOS 39-1. Stick Microphone with screened cable and stand (list 5 gns.), 32/6, P.P. 1/6. **ACOS 40** Desk Microphone with screened cable and built-in stand (list 50/-), 15/-, P.P. 1/6. **ACOS 45** Hand Microphone with screened lead, very sensitive, 25/-, P.P. 1/6. **100 C** Stick Microphone with muting switch and screened cable, detachable desk stand, cord, etc. 39/6. P.P. 1/6.

**1 WATT TRANSISTOR AMPLIFIER**

★ EMI 4-Transistor Amplifier with speaker, tone and volume controls. Ready assembled for use with crystal pick ups. 7½ to 9 volt operated. 89/6. P.P. 1/6.

**BATTERY RECORD PLAYER**

★ 6-7½ volt Garrard Turntable with crystal pick-up. Plays 45 r.p.m. Ideal for above amplifier. 65/-, P.P. 1/6.

**3-TRANSISTOR AND DIODE PERSONAL POCKET RADIO**



ALL PARTS 37/6 P.P. 1/6

Quality Output on Personal Earphone. A simple to build local station radio with personal earphone output. Built-in Ferrite Aerial and Battery lasting 9 months. Size 4½ x 3 x 1½in.

**BABY SITTER**



**ALL TRANSISTOR BABY OR INVALID ALARM**

NOW HOUSED IN ATTRACTIVE GOLD HAMMER FINISH PORTABLE CABINET Battery operated, push-pull, 400MW output. Low impedance microphone enables unit to be used up to 200 yards. Output on quality speaker.


★ GUARANTEED FOR 12 MONTHS and 100% SAFE.

★ Microphone is placed within 10ft. of baby; twin flex is taken to amplifier unit and placed in any room required. COMPLETELY BUILT & TESTED.

**£5.10.0** P.P. 2/6

★ Used All Night, Every Night. Battery Life 3 to 4 months.

**Transistor 2-Way Intercomm**

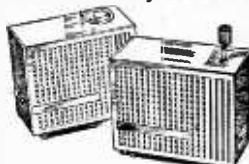

10 Gns.

- Unit Sizes 3½ x 1½ x 3½in. (Approx.)
- 2-way Talking.
- Internal Buzzing System
- Full Volume Control
- Long Life Built-in Battery
- Built-in 2½in. Speakers housed in attractive moulded cabinets. Supplied in presentation carton. Complete with Battery and 60 ft. wire.
- Fully Guaranteed and Tested

**SPECIAL OFFER**

COMPLETE SET OF PARTS FOR "P.W." CITIZEN AS PER DEC./JAN. EDITIONS OF "PRACTICAL WIRELESS."

**79/6** P.P. 1/6.

**TRANSISTORS**

We Stock Transistors FROM We Stock Transistors and Components for Every Purpose. Enquiries Welcomed **3/6**

**1st GRADE—FULLY GUARANTEED** SEND FOR LATEST PRICE LISTS

COMPLETE SET OF PARTS FOR "P.W." MINI-AMP AS PER NOVEMBER EDITION OF "PRACTICAL WIRELESS" **65/-** P.P. 1/6

★ Suitable Battery Record Player 65/-, P.P. 1/6.

**Henry's Radio Ltd**

5 HARROW ROAD - LONDON W.2

Opposite Edgware Road Tube Station OPEN MON. to SAT. 9-6, THURS. 1 o'clock Telephone PADDDINGTON 1008/9.

PLEASE TURN TO BACK PAGE

**OUR SPECIALITIES** Transistors, Valves, Quartz, Crystals, Components at Competitive Prices. Let us quote for your circuit.

# Practical Wireless

## BLUEPRINT

## SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for the PW Monophonic Electronic Organ and the PW Roadfarer.

The Index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2

### SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price	Title	Number	Price
<b>CRYSTAL SETS</b>					
Junior Crystal Set .. .. .	PW94	2/-	A.C. Fury Four .. .. .	PW20	2/6
Dual-wave Crystal Diode .. .. .	PW95	2/6	Experimenter's Short Wave .. .. .	PW30a	2/6
<b>STRAIGHT SETS</b>					
<b>Battery Operated</b>					
Modern One-valver .. .. .	PW96	2/6	Midget Short Wave Two .. .. .	PW38a	2/6
All-dry Three .. .. .	PW97	3/6	Band-Spread Three (Battery) .. .. .	PW68	2/6
Modern Two-valver .. .. .	PW98	3/6	Crystal Receiver .. .. .	PW71	2/-
<b>SUPERHETS</b>					
A.C. Band-pass Three .. .. .	PW99	4/-	Signet Two (Battery) .. .. .	PW76	2/6
A.C. Coronet-4 .. .. .	PW100	4/-	Simple S.W. One-valver .. .. .	PW88	2/6
A.C./D.C. Coronet .. .. .	PW101	4/-	Pyramid One-valver .. .. .	PW93	2/6
The PW Pocket Superhet .. .. .	—	5/-	<hr/>		
<b>MISCELLANEOUS</b>					
The PW 3-speed Autogram .. .. .	—	8/-	BBC Special One-valver .. .. .	AW387	2/6
The PW Monophonic Electronic Organ .. .. .	—	8/-	A One-Valver for America .. .. .	AW429	2/6
<i>(No constructional details are available with this blueprint)</i>			Short-Wave World Beater .. .. .	AW436	3/6
The PW Roadfarer .. .. .	—	5/-	<hr/>		
<i>(No constructional details are available with this blueprint)</i>			Standard Four Valve S.W. .. .. .	WM383	3/6
<b>TELEVISION</b>					
The PT Band III converter .. .. .	—	1/6	Enthusiast's Power Amplifier .. .. .	WM387	3/6
			Standard Four Valve .. .. .	WM391	3/6
			Listener's 5-Watt Amplifier .. .. .	WM392	3/6

### QUERY COUPON

This coupon is available until 7th February, 1962, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, FEBRUARY, 1962

★ **RANGER 3** ★  
NO EXTERNAL AERIAL OR  
EARTH—3-TRANSISTOR and  
2 DIODES



Personal Pocket Radio with 5 stages giving clear reception on medium wave, amateur top band and shipping. No station overlap.

Size  $4\frac{1}{2} \times 3 \times 1\frac{1}{4}$  in.

All Components

**79/6** P.P. 1/6  
Everything Supplied

● Easy to follow instructions with pictorial layout free on request.

● Reception of Radio Luxembourg guaranteed.

ANNOUNCING A COMPLETELY NEW 6-TRANSISTOR  
POCKET SUPERHET RADIO

THE  
"CAPRI"  
POCKET  
SIX



Size only  
 $4\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{4}$  in.

REALLY  
POCKET SIZE

- ★ Full medium wave tuning—preset light on long wave.
- ★ 6 Mullard transistors and diode.
- ★ Push-pull output.
- ★ Printed circuit construction.
- ★ High flux speaker.
- ★ Fitted earphone/record socket.
- ★ Moulded two-tone cabinet with mesh grille.

A REMARKABLE EASY TO BUILD POCKET RADIO GIVING OUTSTANDING RESULTS

● Fully Descriptive Leaflets on request ●

TOTAL COST OF ALL PARTS **£7.10.0** P.P. 2/-  
Battery 2/6 extra



Size  $8\frac{1}{2} \times 6\frac{1}{2} \times 3\frac{1}{2}$  in.

● Full coverage on Medium and Long wavebands. Excellent quality with full station separation. Car aerial socket.

● BUILDING PLANS & PRICES FREE ON REQUEST ●

"TRANSFIVE" PORTABLE  
MEDIUM AND LONG WAVE  
PORTABLE RADIO

- 325mW Push-Pull Output on 5-inch Speaker.
- Pictorial Building Plans.
- Easy to Build Printed Circuit.
- Carded Components.
- 5 Mullard Transistors and diode.

AFTER SALES SERVICE  
and  
FULLY GUARANTEED

TOTAL COST OF ALL PARTS

**£6.19.6** P.P. 2/6

NO EXTRAS TO BUY

"QUINTET"  
MEDIUM AND LONG WAVE  
POCKET LOUDSPEAKER  
RADIO

- 250mW Push-Pull Output.
- Plainly marked Printed Circuit Board and Carded Components.
- 5 Mullard Transistors and diode.
- Illustrated Plans.

A new printed circuit design fully tunable on both wavebands. Guaranteed reception of Continental and local stations including Luxembourg, anywhere with full station separation. Fitted Car Aerial & Earpiece Sockets

● Illustrated Instructions FREE ON REQUEST ●



Size  $5\frac{1}{2} \times 3 \times 1\frac{1}{2}$  in.

TOTAL COST OF ALL PARTS

**£5.10.0** P.P. 2/-

NO EXTRAS TO BUY

VERY EASY TO BUILD AND USE.  
After Sales Service and Guarantee  
All Parts Sold Separately

★ **P.W.-6 SUPERHET** ★

Now available the modified version of the previously advertised P.W.-6 Transistor Medium and Long Wave Superhet. Cabinet Size now  $5\frac{1}{2} \times 3\frac{1}{2} \times 2$  in.

● ALL PARTS SOLD SEPARATELY  
● DETAILS ON REQUEST  
TOTAL COST OF ALL PARTS  
**£8.10.0** P.P. 2/-

TRANSISTOR PORTABLE  
TAPE RECORDER

Size

$6 \times 8\frac{1}{2} \times 2\frac{1}{2}$  in.

**12**  
Gns.



- Over 1 hour play/record.
- Quality Reproduction on Built-in Speaker.
- Fast Rewind—Full Volume Control.

SUPPLIED COMPLETE WITH MICROPHONE, BATTERIES, PERSONAL PHONE AND TAPE.

**Henry's Radio Ltd**

Paddington 1008/9

5 HARROW ROAD, LONDON W2

Open Monday to Sat. 9-6, Thurs. 1 o'clock

Send 1/- Stamp for New Illustrated Price Lists

← PLEASE TURN PAGE

★ **RANGER 2** ★

All Parts

**59/6**

P.P. 1/6



PERSONAL POCKET RADIO

- Two Transistor Two Diode fully tunable over medium waves. Good reception of Radio Luxembourg. Size  $4\frac{1}{2} \times 3 \times 1\frac{1}{4}$  in. No extras to buy.
- PICTORIAL PLANS AND DETAILS FREE ON REQUEST

DETAILS

- High "Q" Internal Ferrite Aerial.
- Car Radio Adaptation and AVC
- "Hi-Fi" Quality Speaker.
- Slow Motion Fingertip Tuning with Station names clearly marked.
- 425mW Push-Pull Output.
- 6 "Top-Grade" Ediswan Transistors.
- New Type Printed Circuit with all components marked.
- Full Medium and Long Wave Tuning.

TOTAL COST OF ALL PARTS

**£10.19.6** P.P. 3/6

● NO EXTRAS TO BUY ●


- Attractive Rexine Covered Cabinet Red/White or Blue/White,  $10 \times 7\frac{1}{2} \times 3\frac{1}{2}$  in.

UNBEATABLE IN PERFORMANCE AND APPEARANCE

Employs the latest techniques. Double tuned IF's, AVC and first-grade components are standard features. Excellent tone, sensitivity and selectivity on both wavebands guaranteed.

● THE BEST OBTAINABLE ●  
Descriptive Leaflets on request.

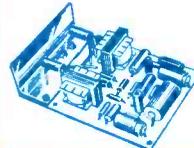★ **3/4 WATT 4 TRANSISTOR  
AMPLIFIER** ★



- 1 watt peak output.

±3db 70c/s to 12 kc/s.

Output to 3 ohm speaker.

9 volt operated.

Details on request.

Built and Tested

**69/6** P. & P. 1/6

A printed circuit high gain amplifier size  $4 \times 2\frac{1}{2} \times \frac{1}{2}$  in. using Mullard OC71/OC81D and 2-OC81 Transistors. Ideal for Intercomm., Record Player, Tuner Amplifier or any application requiring a quality and reliable amplifier.

● **CONTESSA** ●  
6 TRANSISTOR MEDIUM AND  
LONG WAVE SUPERHET



COMBINED  
PORTABLE AND CAR RADIO