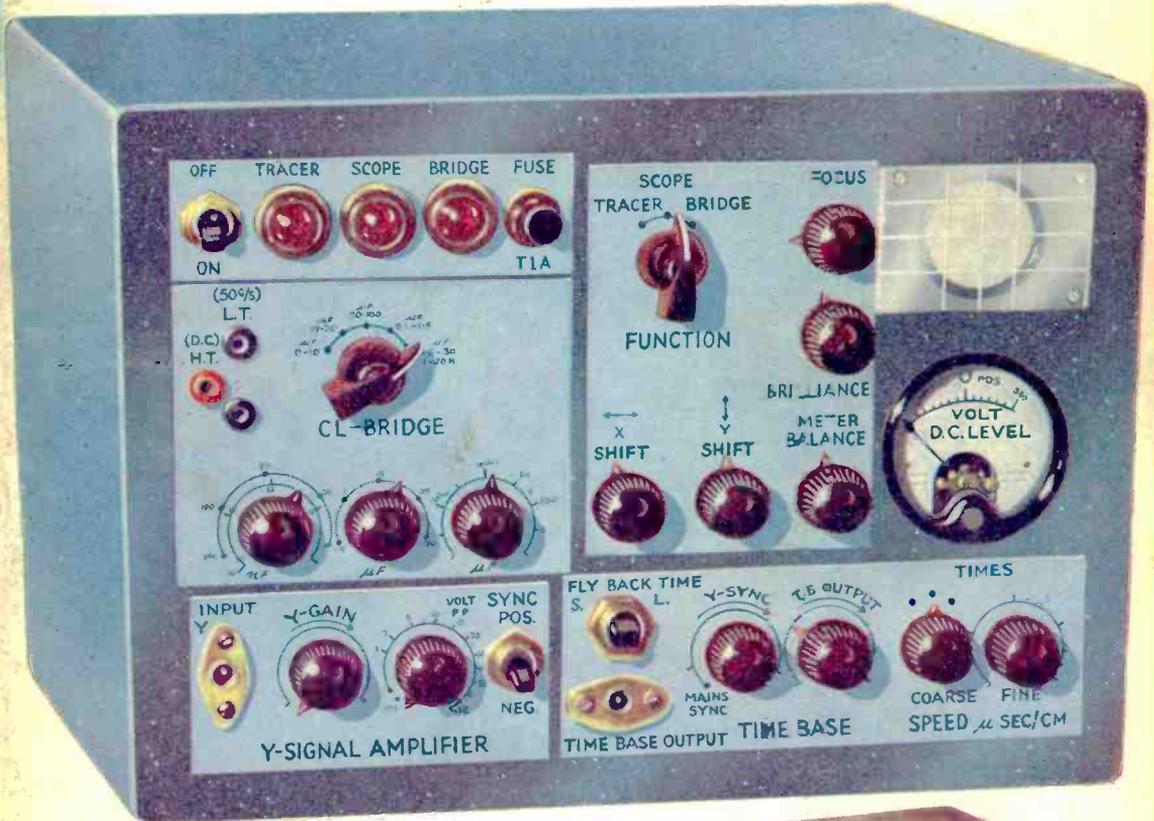


SEPTEMBER
1962

Practical 2/- WIRELESS

The MINISCOPE



The **TUDOR**
4-valve
battery portable



BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.13.0 (Carriage Paid)


A.C. ONLY. Chassis size 15 x 6½ x 5½ in. High. New manufacture. Dial 14½ x 4½ in. in 2 colours predominantly gold. Pick-up. Ext. Speaker. A.e., E. and Dipole Sockets. Five push buttons—OFF L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1,000-1,00 M.; 200-500 M.; 88-98 Mc/s. Valves EZ80 rect., ECC81, EF89, EAB80, EL84, ECC85. Speaker and Cabinet to fit chassis (table model). 47/6 (post 2/6). 9 x 6 in. ELLIPTICAL SPEAKER, 20/-, to purchasers of this chassis. **TERMS:**—(Chassis) £5 down and 4 monthly payments of £2, and 1 of £1.13.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. yard. Circuit diagram 2/6.



THE "CANTATA" 6-TRANSISTOR AND DIODE PORTABLE

COMPLETE KIT FOR ONLY

£7.19.6 (post 3/6)

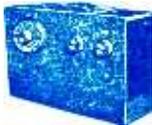

500mW push-pull output. Ferrite rod aerial. Car aerial socket and coil. M.W. and L.W. full coverage. Operates on two 4.5v. cells. Printed circuit board 8½ x 2½ in. All holes drilled and component positions marked. Instructions 2/6 (or 16p. (refunded on purchase of kit). Size 9 x 3½ x 7½ in. 8 x 2½ in. P.M. high quality speaker. Attractive Vynair covered cabinet, two tone. Two batteries 5/6 the pair (Ever Ready 126). Mullard transistors OC44, 2 x OC45, OC81D, and 2 x OC81. Top grade Weymouth Radio coils and transformers. Alignment service it required 17/6 (inc. post). Write for list of prices. All parts supplied separately. Built in two hours.

BUILD YOUR OWN RECORD PLAYER

Price £12 carr. paid


Fully built 2 valve amplifier

B.S.R. 4-sp. autochanger, case 17 x 15 x 8½ in. Assembled in 15 mins. Similar cabinet for tape recorder with plain board only £3. carr. paid. Attractive colours.

or with 3 valve amplifier 15/- extra


AUTOMATIC RECORD CHANGERS—LATEST MODELS. 4 SPEED. CRYSTAL CARTRIDGE. All 5/- (extra carr. B.S.R. UA14. £7.10.0. Garrard Slimline, Mono £8. Stereo. £8.5.0. Motor Board for UA8. UA20. UA14. Slimline. 5/- (post 1/6) or 3/6 post paid when purchased with Autochanger. Motor Board for Collaro C60. 4/-, post paid.

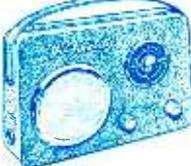TELEPHONE STEREO AMPLIFIERS. 2 ECL82—2 x 2½ watts. 12 x 9 x 2½ in. piano keys, £7, post paid.



6 TRANSISTOR PORTABLE—FULLY BUILT. The "SCALA" for only £7.19.6, carr. paid. 8½ x 2 x 5½ in. high. Choice of colours. Rexine. M.W. and L.W. Ferrite aerial. P.P.4 battery 2/3 extra. Printed circuit. Nicely styled. A professional job 3½ in. speaker.

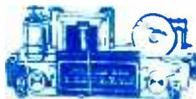SELE-POWERED VHF TUNER CHASSIS. Covering 88-95 Mc/s Mullard permeability Tuner. Dims 10½ x 4½ x 5½ in. high. ECC85, EF91, EF91 and 2 diodes. Metal Rectifier. Mains transformer. Fully wired and tested. Only £7.10.2 (carr. pd.) Attractive Vynair Cabinet 20/-, Room dipole 12/6. Feeder. 6d. vd.



PUSH-PULL AMPLIFIER £5.5.0

(5/- Carr.)

Brand new 230-240 A.C. mains Bass, treble and vol. controls. With valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3½ x 3½ in. With o.p. trans. for 2-3 ohm speaker.

Front panel (normally screwed to chassis) may be removed and used as "flying panel." Stereo version 2 x 4 w. same price.

THIS SUPERB SET FOR £10

6-transistor radio covered in sponge clean Duracour fabric, in latest two tone shades. M.W. and L.W. ferrite rod, provision for car aerial. 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4 lbs. With carrying handle. 12 x 7½ in. high x 4½ in. at base tapering to 2½ in. top. Brand new, fully guaranteed. £10 Carr. paid. Worth £16.



SUPERIOR GRAMOPHONE AMPLIFIER

Valves UY85, UF80 and UL84. Mains trans. 200-240 a.c. Covered baffle 13½ x 7½ in. (6½ in. speaker) or 11 x 7½ in. (8 x 5 in. speaker). 3 front controls bass, treble, on-off/vol. 74/- (post 4/-) either type. Rexine cabinet to fit, with carrying handle, and lid (detachable) 14 in. or 12 x 8½ x 5½ in. 16/- extra.

GRAMOPHONE AMPLIFIER. With 5 in. SPEAKER Baffle 12½ x 6 in. ECL82 and Rectifier. Tone and Volume On/off switch. Two knobs. Ready to play. Useful for Stereo. 57/- (post 4/-).

TEST LEAD KIT. Leads, Prods. Terminals, Clips, in case. 10/-, post paid.

TAPE TOP QUALITY BOXED. 5½ in.—850ft., 15/-; 1,200 ft., 17/6; 7 in.—1,200 ft., 17/6; 1,800 ft., 28/6 (all plus 1/6 post. 2/- for 2).

SPECIAL OFFER

Brand new tape recorder, two tone belt case, "gold" trimmings. Magic eye, monitor, ext. speaker sockets. With 5½ in. tape and mike. Fully guaranteed. Price usually £19! Now. Very high gain with low noise. Price £13 carr. paid

COLLARO STUDIO TAPE TRANSCRIBER, 3 MOTORS, 3 SPEED, 11, 3½ and 7½ I.P.S. Push buttons. £10.17.6 (10/- carr.) incl. spool.

3-VALVE AMPLIFIER (Inc. RECT.)

2½ watts. ECC83, ECL82 and EZ80. Controls, volume, bass and treble. On/off switch. Mains and O.P. trans. Size as for Push-Pull Amp. Suitable for microphone 95/- P. & P. 5/- Input and for Guitar.

Also acts as telephone amplifier using pick-up coil price 14/- Chassis 12 x 3½ x 3½ in. Fixed front panel. Price includes handsome walnut finish polished cabinet 13 x 7½ in. (facia containing high quality 3 ohm P.M. speaker 5½ x 4½ in. (20/- less without cab and speaker).

BATTERY ELIMINATOR

For 4 Low Consumption Valves (96 range). 90v. 15mA and 1.4v. 125mA. 45/- (2/6 post). 200-250v. A.C. Also for 250mA, 1.4v. and 90v. 15mA at same price.

TAPE RECORDER AMPLIFIER

Type TR3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 11 in. Height 5½ in. overall. Front to back 5½ in. Vol. and on/off-tone. Mike, radio, monitor and ext. speaker jacks. Valves ECC83, ECL82, EZ80. Mains trans. Ready to bolt to B.S.R. Deck. Complete with switch water wired. Our Price ONLY £8.2.6 (6/- Packing and Carr.) Similar model without magic eye. Type T.R.I. 3" instead of 1½" £5.15.0. (6/- Carr.)

CHASSIS BATTERY RADIO

Valves DK96, DF96, DAF96, DL96. Two Short Wavebands 16 to 49 M. and 25 to 75 M. Size 10½ x 4½ x 5 in. £4.16.0, carr. paid. MW and SW. £5, carr. paid. Or as Kit 75/-.

TERMS AVAILABLE ON ITEMS OVER £5

Send 6d. (stamps will do) for 20 page illustrated catalogue. All New Goods. Delivered by return. (C.O.D. 2/- extra.)

ALL ITEMS GUARANTEED 12 MONTHS

VALVES 3 MONTHS

Farnborough Closed Sat. Portsmouth Closed Wed.

GLADSTONE RADIO

"SCALA," CAMP RD., FARNBOROUGH, Hants.

Farnborough 3371 and 347 New Road, Copnor, Portsmouth.

★ VALVES ★

by return of post

THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

10% DISCOUNT
SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozen). Post: 1 valve, 6d., 2-11, 1/-.

NEW LOW PRICES GUARANTEED 3 MONTHS

FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government origin. Satisfaction or Money Back Guarantee on Goods if returned unused within 14 days.

024	5/-	6J3GT	4/-	12K6GT	9/6	DF35	9/9	EM80	7/9	SP41	2/6
1A5GT	5/-	6J6	4/-	12Q7GT	5/-	DF91	9/6	EM81	8/6	SP61	2/6
1A7GT	11/-	6J7	8/6	12S47	7/-	DF96	7/9	EM84	9/-	SD25	16/-
1C5GT	9/-	6J7B	4/9	12S77	5/-	DF97	8/6	EM83	10/-	SD2150	4/6
1D1	8/-	6J7GT	7/6	12S817	3/6	DF98	6/-	ENX31	16/-	T4	7/6
1D6	9/9	6J8	9/6	12S47	5/6	DF99	5/-	EY51	11/-	TD44	7/6
1H5GT	9/9	6K6GT	6/6	12S67	4/9	DK32	11/-	Small	7/9	U14	8/-
1L4	3/6	6K7	5/9	12S7GT	7/9	DK91	5/6	EZ26	7/6	U14	8/-
1LD5	3/6	6K7G	2/3	13D1	9/-	EL32	7/-	EY50	5/6	U22	6/9
1LN5	4/9	6K7GT	4/6	14S7	14/6	EL96	7/-	EZ25	6/6	U24	16/-
1N5GT	9/9	6K8GT	8/9	19A05	7/6	EL33	8/-	EZ41	7/-	U25	11/6
1R5	5/6	6K25	7/6	19B66	19/-	EL35	9/-	EZ20	6/-	U26	9/9
1S4	8/-	6L1	12/6	20D1	9/6	EL45	6/-	EZ21	6/6	U31	7/-
1S5	4/6	6L40	6/6	20P2	9/6	EL75	6/-	FW4300	8/6	U32	14/-
1T4	3/6	6L18	9/-	20L1	18/-	EL82	6/-	FW4300	8/6	U35	12/6
2A3	6/6	6L19	11/-	20P1	8/9	EL91	8/-	GT1C	7/-	U37	26/-
2A7	9/6	6L18	8/-	20P3	12/6	EL92	6/-	GT22	8/9	U39	5/9
3A4	4/9	6L1D12	6/9	20P4	14/-	EL94	6/9	GT24	12/6	U52	4/9
3A5	9/-	6L20	7/9	20P5	15/-	EL94	7/3	HL41D1	7/6	U53	6/9
3D4	4/6	6N7	7/6	25A6	8/6	EL96	8/9	IB280	8/3	U78	5/6
3E4	7/-	6P1	8/6	25B6	8/6	EL97	8/6	IB280	8/3	U78	5/6
3Q3GT	8/-	6P25	8/6	25L6GT	7/9	EA42	4/6	IN309	19/-	U91	12/6
3S4	6/-	6P28	12/6	25Y3G	8/-	EB41	7/-	IW4350	7/6	U92	15/-
3V4	4/9	6Q7G	8/6	25Z4G	8/-	EB41	3/-	IW4500	7/6	U93	15/-
5R4GY	12/6	6Q7GT	8/6	25Z4G	8/-	EB41	3/-	KT32	4/6	U99	14/-
5T4	8/-	6H7G	8/6	25Z6G	8/-	EB41	8/-	KT32	4/6	U99	14/-
5U4G	4/9	6S47	5/6	30C1	7/6	EB41	7/9	KT33C	4/6	U99	11/-
5V4G	7/9	6S7	4/9	30C15	11/6	EB41	7/9	KT33C	4/6	U99	11/-
5Y3G	5/9	6S87	3/-	30F5	6/6	EB41	7/9	KT33C	4/6	U99	11/-
5Y3GT	5/9	6S87	5/-	30P1L	9/6	EB41	7/9	KT33C	4/6	U99	11/-
5Y4G	11/-	6S17GT	5/9	30L1	6/9	EB41	7/9	KT33C	4/6	U99	11/-
5Y4	6/6	6S18GT	5/9	30L15	9/6	EB41	7/9	KT33C	4/6	U99	11/-
5Z4G	7/6	6S27	5/9	30P4	9/6	EB41	7/9	KT33C	4/6	U99	11/-
5Z4T	11/-	6S37	3/6	30P12	7/6	EB41	7/9	KT33C	4/6	U99	11/-
630L2	9/-	6U4GT	10/6	30P16	6/6	EB41	7/9	KT33C	4/6	U99	11/-
6A5	4/9	6V8G	5/6	30P19	17/6	EB41	7/9	KT33C	4/6	U99	11/-
6A55	10/-	6V8GT	6/-	30P1	9/6	EB41	7/9	KT33C	4/6	U99	11/-
6A6G	8/6	6X2	7/6	30P1L13	13/6	EB41	7/9	KT33C	4/6	U99	11/-
6ANGT	10/6	6X4	5/-	35L6GT	8/6	EB41	7/9	KT33C	4/6	U99	11/-
6A84	7/-	6X5G	5/6	33T	25/-	EB41	7/9	KT33C	4/6	U99	11/-
6A87	3/6	6X5GT	5/6	33W4	9/6	EB41	7/9	KT33C	4/6	U99	11/-
6A85	3/-	6X8G	7/6	33Z4GT	5/6	EB41	7/9	KT33C	4/6	U99	11/-
6A87	7/6	7A7	8/6	33Z6GT	8/-	EB41	7/9	KT33C	4/6	U99	11/-
6AK5	5/-	7B6	9/-	41	7/6	EB41	7/9	KT33C	4/6	U99	11/-
6AL5	3/-	7B7	7/9	42	7/6	EB41	7/9	KT33C	4/6	U99	11/-
6AM8	3/-	7C5	7/9	30C16	9/6	EB41	7/9	KT33C	4/6	U99	11/-
6A25	6/-	7C8	9/6	30C19	19/6	EB41	7/9	KT33C	4/6	U99	11/-
6A75	5/9	7I17	7/9	50L6GT	8/6	EB41	7/9	KT33C	4/6	U99	11/-
6A96	7/6	7K7	9/6	52K10	10/6	EB41	7/9	KT33C	4/6	U99	11/-
6B7	8/6	7Q7	8/6	53K10	10/6	EB41	7/9	KT33C	4/6	U99	11/-
6B8G	3/-	7K7	17/6	61B1P	11/-	EB41	7/9	KT33C	4/6	U99	11/-
6B8B	5/9	7A7	9/6	62B1T	13/6	EB41	7/9	KT33C	4/6	U99	11/-
6B85	5/9	7A7	7/9	60	8/6	EB41	7/9	KT33C	4/6	U99	11/-
6B86G	15/-	7Y4	6/9	78	6/6	EB41	7/9	KT33C	4/6	U99	11/-
6BH6	6/-	7D4	7/-	80	5/9	EB41	7/9	KT33C	4/6	U99	11/-
6B96	9/-	8D3	3/-	83	9/6	EB41	7/9	KT33C	4/6	U99	11/-
6BR7	9/6	10C1	11/6	145BT	19/6	EB41	7/9	KT33C	4/6	U99	11/-
6B96	7/6	10C2	14/6	60	19/6	EB41	7/9	KT33C	4/6	U99	11/-
6B97	5/6	10C4	8/-	807A	5/9	EB41	7/9	KT33C	4/6	U99	11/-
6B98	4/9	10F1	5/9	808	7/6	EB41	7/9	KT33C	4/6	U99	11/-
6C5	5/6	10F18	10/6	822	14/-	EB41	7/9	KT33C	4/6	U99	11/-
6C9	9/9	10L14	7/-	866A	11/6	EB41	7/9	KT33C	4/6	U99	11/-
6C9	11/-	10B28	7/9	954	2/6	EB41	7/9	KT33C	4/6	U99	11/-
6CD6G	19/6	10L11	14/6	956	2/6	USA	3/-	PL33	8/3	VR105	6/9
6CH6	7/6	10LD12	8/6	9901	4/6	EP54	3/-	PL33	9/6	VR105	6/9
6D2	3/-	10P13	11/6	9902	4/6	EP59	10/6	PL33	14/6	WG11	11/-
6D6	4/9	10P18	9/-	ATP4	2/9	EP35	6/6	PL81	8/6	W75	4/9
6D8	4/3	10P18	7/-	AZ31	8/9	EP86	9/-	PL82	6/6	W81	7/3
6F1	4/9	12A6	1/9	AZ41	11/-	EP89	6/9	PL83	6/6	W81	11/-
6F6G	5/9	12A18	8/-	AZ6	7/9	EP91	3/-	PL84	8/6	W85	11/-
6F12	3/-	12A18	6/6	DA31	11/6	EP92	4/6	PL20	8/6	W85	11/-
6F14	9/9	12A18	9/6	CH11	21/6	EP96	3/-	PL24	12/6	W86	11/-
6F14	9/6	12A18	9/6	CH11	21/6	EP96	3/-	PL24	12/6	W86	11/-
6F15	9/6	12A18	9/6	CH11	21/6	EP96	3/-	PL24	12/6	W86	11/-
6F16	8/-	12A18	8/6	CH11	21/6	EP96	3/-	PL24	12/6	W86	11/-
6F19	8/6	12B46	7/6	91	9/6	EL33	4/6	PY21	10/-	X79	21/-
6F23	6/9	12B46	7/6	91	9/6	EL33	4/6	PY21	10/-	X79	21/-
6F24	12/-	12B47	9/9	D152	5/9	EL33	7/-	PY81	6/6	X83	6/3
6F25	13/-	12C8	6/6	DA30	12/6	EL42	8/9	PY83	7/-	Z66	9/6
6F32	6/6	12P1	17/6	DA32	9/9	EL41	11/-	PY88	9/9	Z152	4/9
6F33	6/6	12G7G	9/-	DA91	4/6	EL33	11/-	Z299	9/9	Z152	4/9
635	4/3	12K7	11/-	DA96	7/9	EL34	7/-	R18	11/-	Z719	4/9
6356	8/-	12K8	11/-	DET19	2/9	EL91	4/-	R19	11/-	ZD152	7/9

Tubes

Arr. & Inc. 12/6

HIGHEST QUALITY— COMPARE OUR PRICES	GUARANTEED	NEW TYPES																												
MOST MULLARD, MAZDA, CORDOR, EMITRON, EMISCOPE, BRIMAR, FERRANTI TYPES, PROCESSED IN OUR OWN FACTORY	<table border="1"> <tr> <td>12in.</td> <td>6 Months</td> <td>12 Months</td> <td>MW 21/74</td> </tr> <tr> <td>14in.</td> <td>£2. 0. 0</td> <td>£3. 5. 0</td> <td>£4-0-0</td> </tr> <tr> <td>15/17in.</td> <td>£3. 5. 0</td> <td>£4. 10. 0</td> <td>MW 36/24</td> </tr> <tr> <td>21in.</td> <td>£3. 15. 0</td> <td>£5. 15. 0</td> <td>£5-0-0</td> </tr> <tr> <td></td> <td></td> <td></td> <td>CRM 172</td> </tr> <tr> <td></td> <td></td> <td></td> <td>MW 42/84</td> </tr> <tr> <td></td> <td></td> <td></td> <td>£6-0-0</td> </tr> </table>	12in.	6 Months	12 Months	MW 21/74	14in.	£2. 0. 0	£3. 5. 0	£4-0-0	15/17in.	£3. 5. 0	£4. 10. 0	MW 36/24	21in.	£3. 15. 0	£5. 15. 0	£5-0-0				CRM 172				MW 42/84				£6-0-0	
12in.	6 Months	12 Months	MW 21/74																											
14in.	£2. 0. 0	£3. 5. 0	£4-0-0																											
15/17in.	£3. 5. 0	£4. 10. 0	MW 36/24																											
21in.	£3. 15. 0	£5. 15. 0	£5-0-0																											
			CRM 172																											
			MW 42/84																											
			£6-0-0																											

SPECIAL TEMPORARY OFFER.
Due to huge Bulk Special Purchase we are offering MW 31/74 Tubes at the unreplicable price of 29/-, MW 36/24 ditto, 39/-, P.P. 12/6. The above are guaranteed for 6 months.

RECORDERS. "Verlik" 4 Track Collins 3 Speed Transcription Deck, Superior reproduction, Streamlined Portable Case. Complete with Mike. Market value approx. £45. OUR SPECIAL PRICE 29 gns.

CO-AX. standard and low loss, 25 yds., 12/6, 50 yds., 22/6; 100 yds., 42/6. Co-ax Phx 1/3. Wall outlet boxes 3/6.

4-SPEED RECORD PLAYERS. Latest Turntable, together with lightweight Staal Galaxy dual sapphire crystal turnover pick-up head. Amazing value (pick-up only 19/-). £3.10.0. Carr. 5/-.

PORTABLE RECORD PLAYERS. Takes all sizes Records, all speeds, amplifier, auto-changer, Garrard new "slimline" Gram. In two-tone Case. All absolutely new. 14 gns.

MIRROR GALVANOMETERS. Ever-shed and Vignoles, 45 second swing, high sensitivity, heavy gunmetal cases, with spares, in transit case, unused. £3.10.0.

F.M. SPEAKERS. 3 ohm, top makes. Performance guaranteed. 6 1/2in., 8in., 8", 6in. 7 x 4in., 11/-.

13 CHANNEL T.V.s

Table Models, Famous Makes. Absolutely Complete. These sets are unequalled in value due to huge purchase direct from source. They are untested, and not guaranteed to be in working order. Carr. etc. 15/-.

12in.	£2.19.0	14in.	£4.19.0
-------	---------	-------	---------

TRANSISTOR PORTABLES. 6 + diode lightweight, approx. 1lb., slightly larger than pocket set, but much greater volume, better quality, complete battery, amazing sensitivity worth £1. Our price only £7.10.0.

F.M. TUNER KITS. Well-known make. Comprising F.M. Tuning Head, guaranteed none drift, Frequency coverage 85-100 mc/s. OASL balanced diode output, Magic Eye Tuning, Two I.F. Stages and discriminator, £69.6.

P.V.C. CONNECTING WIRE. 100 yds., 30 mil; special price 7/6. 200 yds. 30 mil; special price, 12/6. 25ft. Coil, 1/-.

5 Coils different colours, 4/-. Connecting flex. Prices as above.

TRANSISTORS. Red spot 3/6 ea. White Spot 4/6 ea. Yellow Spot 2/9 ea. (Germanium diodes 9d. ea. 8/- doz. TAG STRIPS. From 3 way to 12 way. Mixed parcels of 25-3/9. The best and cheapest way to buy!

B.B.C./I.T.A. TUNERS

Famous makes complete with PCF80, PC084 valves. 38 M/L I.F. Fantastic value 19/-.

CONDENSERS. 25 Mixed, Electrolytic. Many popular sizes. List Value 65 Our Price 10/-.

GET 15. G.E.C. High Power. Contact cooled, manufacture matched per Transistor with Push-Pull Input & Output Transformers. Knock out price 29/-.

NEW SPEAKER CABINETS, covered in attractive Rexine, Gold Metal front 11/-. Or complete with 7 x 4 Speaker, 19/-, P.P. 1/6.

UA20 Autochangers. Latest B.S.R. 10 mixed records. Brand New. Unrepeatable. £2.18.0. Also UA14. A Proven Choice £7.18.0. P.P. 4/-.

"GARRARD" Slimline. Very latest Compact Autochanger. Just released. Amazing value, £2.19.0. Also available, Garrard Model 209. £2.17.6. P.P. 4/-.

100 RESISTORS 6/6

100 CONDENSERS 10/-
Miniature Ceramic and Silver Mica Condensers 3 pF to 5,000 pF. LIST VALUE OVER 65

IVORY/GOLD KNOBS 1" Diameter, half price 1/2, 5 for 4/8; 1 1/2" 1/8, 5 for 5/-.

VALVE HOLDERS. 376, 6d. ea., with Screen 8d. ea. 39A, 6d. ea. with Screen 8d. ea.

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/- etc. No C.O.D. ALL ITEMS LESS 5% AND POST FREE IN DOZENS. LIST OF 1000 ENIPS, 6d.

TECHNICAL TRADING CO.

RETAIL SHOP
350-352 FRATTON ROAD, PORTSMOUTH
MAIL ORDER ONLY DEVONIAN COURT,
PARK CRESCENT PLACE, BRIGHTON 7, SUSSEX

What! A TV in a Caravan?

To operate your razor from car battery or suitable for many other uses, we offer Motor Generator 12v. Input, 200 v. output, which must have cost at least £10 to make, for only 17/6, plus 4/6 post and insurance.

The J.B. Tangential Air Conditioner

The displacement caused by the new Tangential fan is quite amazing, but what is more amazing is the almost complete absence of noise.

Stand the J.B. Air-Conditioner on a window ledge near an open window and you can have either extraction of bad air, or input of clean, new air, depending upon which way you turn it.

In addition to a fan for moving the air, the unit also contains a heater and control switch, wired such that 500, 1,000 or 2,000 watts of heating may be used.

The total building cost of this air-conditioner is £7.10.0, but is offered at a specially low price during the summer months, this price namely £6.10.0, plus 5/- carriage and insurance. The case is very nicely finished in hammered enamel, and when assembled, the unit is indistinguishable from those selling at £12 and more.

Don't miss this special summer offer.

Adjustable Thermostat

Suitable for Industrial or domestic purposes, such as controlling furnace oven, Immersion heater etc. Can also be used as a flamestat or fire alarm. Made by Sunvic these are approximately 17" long and adjustable over a range 0 to 550 F. The contacts are rated at 15 amp., 250 volts, and the adjustment spindle, which comes to the top, can be fitted with a flexible drive for remote control or just a pointer knob for local control. Listed at 23 or 24 each, these are offered at only 12/6 plus 2/6 postage and insurance.

Introducing the J.B. Range of Transistors

Try these, you will be very pleased—

JB1. All wave mixer (replaces OC45 etc.) .. 6/6

JB3. I.F. Amplifier (replaces OC44 etc.) .. 4/6

JB4. A.F. Driver (replaces OC81D etc.) .. 5/-

JB6. Output matched pair (replaces OC81 etc.) .. 13/-

Special offer set of six matched for Superhet .. 25/-

Special offer set of four matched for Amplifier (1 watt) .. 17/-

Transistor Components
Send S.A.E. for our new price list, just printed.

"A jolly fine set but deserving a better case."

This is a comment which many constructors have voiced and therefore we now offer a De Luxe version of the Pocket Companion. This uses a solid hide case of very pleasant red with fold letting and our Pocket Companion now has the 15 guinea look.

The most up-to-date Superhet portable of its type. It uses a transfiler in conjunction with Philco R.F. transistors and Mullard output transistors. Complete building costs with plastic case £6.15s. or with solid hide case, £7.15s.

If you have already built and want to change your case, then return the plastic case with a postal order for £1 or if you wish to retain the plastic case then send 26/-, plus 1/6 Post and Ins. for the hide case only. AGENTS WANTED TO BUILD OUR COMPANION PORTABLES. SEND S.A.E. FOR FULL DETAILS.

ROMANTICA 7

Cheaper than you can possible make it, we offer a completely made up transistor Pocket Superhet. Uses all first made miniature parts and is complete with leather case, earphone and battery. 535-1065 kc/s. sensitivity 300 micro volts/M, output 160 mW, ferrite slab aerial. Size approximately 4 1/2 x 2 1/2 x 1 1/2 in. Price £6.19.6. Post and Ins. 3/-.

**Cabinet & Pick-up**

Cabinet for battery record player. Size approx. 9 x 11 x 5 in. allows for 7 x 4 in. speaker and amplifier.

Nicely covered two tone. Must have cost at least £2 to make. New and perfect. Offered whilst stocks last 19/6, plus 4/6 post and insurance.

Cosmocord Pick-up

As illustrated with cartridge and headrest. Ready, new and perfect. Suitable for 45 or 33 records. Price



9/6, plus 2/6 post and insurance.

CLOSED CIRCUIT TV

If you feel like taking a day out we invite you to our studio here at Eastbourne and will demonstrate 405 and 625 systems, as well as under water and other types of installations. We have equipment for sale or loan, and will be glad to discuss any proposals which you may have. You will be interested to note that a transistorised camera for working direct into a domestic TV receiver can now be purchased for little more than the cost of a good photo camera.

The 'Good Companion' Mk.II using**Transistors**

In the 'de-luxe' cabinet as illustrated it costs £10.19.6 to build—but what a set!

Scan these pages: you will find nothing to compare with its specification. It uses transistors instead of I.F. transformers, has variable feedback as well as all the usual features. A.V.C., Push-pull output, Ferrite Aerial, Slow Motion Tuning, etc. etc. and is a very powerful Medium & Long Wave set, conservatively rated at 750 mW. Every component used is by a famous maker, such as American Philco M.A.D.T. R.F. transistors—Mullard A.F. transistors—Jackson Brothers tuning condensers—Rola-Celestion loudspeaker—Dubilier—T.C.C.—Morganite resistors and controls. Also full after sales service available.

You will definitely be doing the right thing if you buy a Good Companion.


**Yaxley Switches**

All new and unused and in first class condition

1 pole, 2 way	1/6;	1 pole, 3 way	1/6
1 pole, 4 way	1/6;	1 pole, 5 way	2/6
1 pole, 7 way	3/-;	1 pole, 9 way	3/-
1 pole, 11 way	3/-;	1 pole, 12 way	3/6
2 pole, 2 way	2/-;	2 pole, 4 way	2/6
2 pole, 5 way	3/6;	2 pole, 6 way	3/6
2 pole, 12 way	5/6;	3 pole, 3 way	2/-
3 pole, 6 way	2/6;	3 pole, 12 way	8/6
4 pole, 2 way	2/-;	4 pole, 3 way	3/6
4 pole, 4 way	3/6;	4 pole, 5 way	4/6
4 pole, 6 way	5/6;	4 pole, 11 way	10/6
4 pole, 12 way	11/6;	5 pole, 3 way	3/6
5 pole, 6 way	7/-;	5 pole, 12 way	14/6
6 pole, 2 way	2/6;	6 pole, 3 way	3/6
6 pole, 6 way	8/6;	6 pole, 11 way	18/6
6 pole, 12 way	17/6;	8 pole, 2 way	3/6
6 pole, 4 way	4/6;	8 pole, 6 way	11/6
8 pole, 12 way	23/6;	12 pole, 2 way	3/6
12 pole, 5 way	16/6;	12 way fader	3/6
6 pole, 6 way, shorting	3/6		

Big stocks of most types

Special prices for quantities.

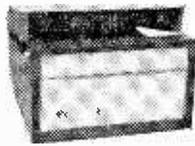Philco Record Player Cabinet

Two-tone, covered with high grade rexine, fitted with rubber feet. The front is particularly nice being made of tygan with a horizontal gold bar. Size approximately 14 1/2 in. wide, 8 1/2 in. deep, 18 1/2 in. long. Will take BSR or similar record player or tape deck and amplifier. Must have cost at least £3 each, our special snip price 35/- each, carriage and insurance 6/6.

"Coolerstat"

Works in reverse to normal—for switching fans, freezers, air conditioning etc. By famous Pullin Company. One of the best available. For controlling room temperature between 30°-90°F. Switch 15 amps. Regular price over £3, we offer standard model at 22s. 6d. or with Neon on/off indicator at 27s. 6d. Do not miss this unrepeatable bargain.

**Power Unit**


A useful source of D.C. for experimenting, energising instruments, electroplating, reactivating batteries etc. This power unit can be made in a few hours and due to the availability of the rectifier valve at a very low price, we can supply the complete kit of parts with ABC instructions, fits into any box for 9s. 6d. plus 1s. post and insurance.

Building A 'Scope ?

3in. oscilloscope tube. American made type No. 3FP7, 6.3 v. 0.6 amp. heater, electrostatic deflection, brand new and guaranteed with circuit diagram of scope. 15/- each, plus 2/6 post and insurance.

**Last of these
Brayhead
Turret Tuner**

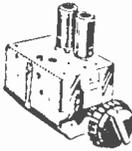Complete with Band 1 and Band 3 coils. New but removed from unused equipment. Less valves 15/- each or with valves 25/- each. Post 2/6 (Knobs 3/6 extra).



Fishing Rod from Dinghy Mast

Tubular aluminium not separate sections, extends like telescope from 15ins. to 9ft. 6/6 each.

Transfilters

These ceramic devices save alignment problems and improve performance. Use instead of I.F. transformer. Complete with circuit. 8/6 each.

**Miniature
Microphone**

American made. Dynamic type, real bargain at 2/6, plus td. postage.



**Blueprint Receiver
The International SW2**

All components to make up this receiver as described in the April issue are available. Price 39/6, plus 2/6 postage and insurance. Note this price does not include cabinet, baking tin or headphones.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000 A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000 D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries, 0-500,000 with external batteries Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. Price 24/6, plus 2/6 post and insurance.



Transistor Set Cabinets



Very modern cream cabinet, size 5 1/2 x 3 x 1 1/2in. with chrome handle, tuning knob and scale. Price 7/6, plus 1/6 postage and packing. Special quotations for quantities.

MULTI-METER BARGAINS!

MODEL 200H (illus. on right). 20,000 ohms per volt, 20 ranges comprising A.C. volts, 5 ranges up to 1,000V D.C. volts, 6 ranges up to 2.5KV. C.C. current, 3 ranges up to 26 ohms, resistance, 2 ranges up to 6 meg. capacity 2 ranges up to 0.1, decibels —20 to +22. Scale cornerwise to the equivalent of 4 in. movement is a pocket size instrument measuring 4 1/2 x 3 1/2 x 1in. Complete with test prods, battery and operating instructions. price £6.19.6, post free.

MODEL EP10K. Similar in size and appearance to 200H except that this is 10,000 ohms per volt and maximum D.C. volts 1,200 instead of 2.5K, also no capacity range. Price £5.19.6. Post free.



**ALL METERS BRAND
NEW AND FULLY
GUARANTEED**


MODEL TP55. (illus. on left). 20,000 ohms per volt, D.C. volts, 5 ranges up to 1,000 A.C. volts, 5 ranges up to 1,000 resistance, 2 ranges up to 10 meg., capacity 2 ranges up to 0.1 decibels —20 to +26. One switch control really beautifully made precision instrument, size only 3 1/2 x 5 1/2 x 1 1/2in., price only £19. Post free.

MODEL TP10. Similar in size and appearance to TP55, but sensitivity 2,000 ohms per volt, price £3.19.6. Post free.

MODEL UI. A robust instrument of 1,000 ohms per volt sensitivity. A.C./D.C. volts up to 1,000 D.C. current up to 500, resistance up to 200K, size 5 1/2 x 3 1/2 x 2 1/2ins. complete with test prods, single switch control, large easily read scale, price only £2.19.6. Post free.



Building An Amplifier?

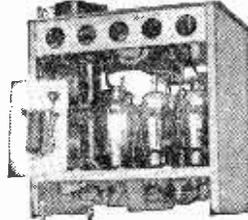

Here is a buy for you! Modulator Unit Type 20. Contains parts ideal for building a large output amplifier and already set out in metal case. To name a few:— Four high output valves Type KT44. Drive valve Type MH41. Iron cored choke for up to 200 milli-amps. Dozens of wire wound and carbon resistors, paper and mica condensers.

Terminals and tag panels, etc. etc. Three other items of interest to everybody and well worth the price asked for the unit are:—

1. Transformer Reference 10K/143. This can act as auto transformer to convert 230 to 110 or 230 to 400, and also as a filament transformer 230 to 6.3 or 230 to 12.6 volts.
2. Miniature Circuit Breaker. For breaking 10 amps A.C. reset by pushing knob.
3. Steel Case. With heavy gauge chassis, already cut out and fitted valve holders etc.

Price for complete unit is 18s. 6d., carriage 5/-.

Portable Tape Recorder for only



£6.19.6

You'll be really thrilled at its performance. Superior to many selling at £12 to £15. Supplied as sub-assemblies which go together in about an hour. Three transistor amplifier with centre switch-forward-stop-rewind with microphone input record play-volume control etc. Complete in most modern carrying case in two-tone and with microphone reel of tape and spare reel. Nothing else to buy. Do not miss this bargain! Only £6.19s. 6d., plus Post & Ins. 5/-

**Making An Extension
Speaker?**




The cabinet illustrated, although intended for T.V. makes ideal extension speaker. Only needs fabric on front. Size 16 x 16 x 14in. deep. Could be cut through middle to make two stereo cabinets. Bargain at only 9/6, plus 4/6 post.

**Parcel of Electric Switches
and Switch Plugs**

All bakelite types, suitable for normal housewiring. Parcel comprises, 6 oblong 1 way 5 amp, 4 oblong 2 way 5 amp, two 5 amp 3 pin switch socket. Value easily 25/-, yours for 10/-, plus 2/6 postage etc.

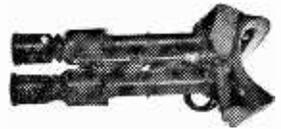Parcel of Mica Condensers
50 all very useful valves. Total list price over £5 and yours for 5/-, plus 1/6 post.



**Lens system for direct TV
Infra-Red Binoculars**

See in the dark for night hunting etc. You get 2 complete optical systems (could be used for T.V. camera) and 2 camera cells. Part of the Tabby equipment. Unused, believed in good order, but no guarantee at this silly price of £2.17.6, plus 10/- carriage.

ELECTRONIC PRECISION EQUIPMENT LTD.

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road, Eastbourne, marked Department 7. Callers may use any one of the Companies below.

266 London Road,
Troydon,
Phone: CRO 6558
Half day Wednesday

29 Stroud Green Rd.,
Finsbury Park, N.4.
Phone: ARCHway 1049
Half day Thursday

520 High Street North
Manor Park, E.12
Phone: ILFord 1011
Half day Thursday

42-46 Windmill Hill
Ruislip, Middx.
Phone: RUislip 3780
Half day Wednesday

John Bull
246 High Street,
Harlesden, N.W.10.
Phone: ELGar 444
Half day Thursday

CLYNE RADIO LTD.



18 TOTTENHAM COURT ROAD, W.1
162 HOLLOWAY ROAD, LONDON N.7
19 CAMBERWELL CHURCH STREET, S.E.5

THE COMPONENT SPECIALISTS

MUSEum 5929/0095
NORth 6295/67
RODney 2875

All post orders etc. to 162 HOLLOWAY ROAD, LONDON, N.7

NEW! NEW! The "COURTESAN"

Our New 3 transistor plus 2 diode pocket receiver with full Medium and Long Wave Coverage.



- ★ No external aerial and earth required.
- ★ Latest 24"-75 ohm speaker.
- ★ First grade Mullard transistors.
- ★ Condenser tuning.
- ★ Volume control with on/off switch.
- ★ Easy assembly on pre-tagged circuit board.
- ★ Attractive red polystyrene cabinet measures 5 1/2 x 3 1/2 x 1 1/2", chrome handle, attractive gold and black dial.
- ★ Luxembourg, Hilversum, etc., guaranteed in reception areas.

ONLY 63/- Plus 2/6 P. & P.


All parts available separately, itemised parts list and full assembly instructions 1/6, post free.

THE SMALLEST TRANSISTOR AMPLIFIER
Size only 2" x 1" x 1/2" high. Three transistor, printed circuit, 125 milliwatts output. From 100-25,000 cycles, ± 1.5 dB. Will operate from 4.5 v. to 9.0 v. Output to any speaker 35 ohm to 80 ohm. Complete with free leaflet showing variety of uses. Radiogram amplifier, baby alarm intercom, door answering device, etc. Price Only 45/-, post free.

INEXPENSIVE TEST GEAR

Two Ideal Pocket Instruments for Amateur or Student

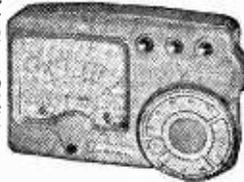MODEL TI1
Size only 3 1/2" x 2 1/2" x 1 1/2"
Meter Size 1 1/2" x 1 1/2"
Sensitivity 285 microamps -1000 ohms per volt AC/DC DC Current 1.25, 250 mA, and AC volts 10, 50, 250, 1,000 v. Resistance 50 ohms-100 K Battery 1.5 v-U12. Complete with test prods, battery and full instructions. Outstanding Value at 57/6 Plus 2/6 P. & P.



MODEL TK.50
Size 5" x 3 1/2" x 1 1/2" 1000 ohms per volt AC/DC. DC Current 1-250 mA DC and AC volts, 10, 250-500 and 1000 v. Resistance 0-10K, 0-100K. Complete with test prods, battery and full instructions. Outstanding buy at 63/- Plus 2/6 P. & P.



ALSO AVAILABLE:
MODEL 500, 30,000 o.p.v., £8.19.8. 10% Deposit H.P.!

"FAMILY FOUR"


Our supersensitive T.R.F. Receiver for home construction. Covers Long and Medium Wavebands. It is housed in very smart plastic table cabinet in Brown or Black, 3 valve plus contact cooled rectifier. For A.C. mains 200/250 v. Comprehensive assembly instructions provided including practical and theoretical diagrams, which are easy to follow and will enable you to complete this receiver which will be the envy of your friends. ALL NECESSARY COMPONENTS ARE BEING OFFERED FOR LIMITED PERIOD ONLY at the REMARKABLE PRICE of ONLY 79/6, plus 2/6 P. & P. Instruction book available separately if you wish to study before purchase at 1/8 post free.



The "CRUSADER"

Our new four transistor plus diode portable with big set quality!

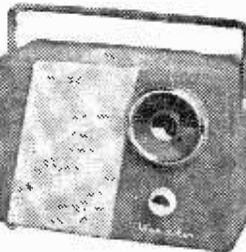- ★ Full Medium Wave coverage.
- ★ Completely self contained.



- ★ Five inch P.M. Speaker. ★ Genuine high grade Mullard or Ediswan Transistors. ★ New components throughout. ★ Attractive two-tone blue/grey Vynil-covered cabinet size 8 x 5 1/2 x 3 1/2 in. with adjustable carrying handle.
- ★ Eyletated chassis simplifies construction.
- ★ Longer life with larger size PP7 battery.

SPECIAL FEATURES!
SUPPLIED WITH JACK SOCKET FOR DIRECT CONNECTION TO CRYSTAL MICROPHONE FOR USE AS BATTERY ALARM WITHOUT ANY MODIFICATION! ALSO FOR DIRECT CONNECTION TO CRYSTAL PICK-UP FOR USE AS A GRAMOPHONE AMPLIFIER! SUPPLIED COMPLETE WITH RECESSED SOCKET FOR DIRECT CONNECTION TO CAR AERIAL!

All required components including full instructions, solder, battery, etc. at special inclusive price of ONLY 95/- Plus 3/6. All parts available separately 95/- P. & P. Itemised parts list and full assembly instructions 1/8 post free.

NEW IMPORT! Large quantity shipments enable us to offer keenest meter value yet! 20,000 ohms per volt

MODEL ITI-2. Volt-ohm-Milliammeter
(Similar to Model 200H originally advertised)
Ranges: A.C. Voltage: 10, 50, 100, 500 and 1000 volts (10,000 ohms per volt). D.C. Voltage: 5-25, 50, 250, 500, and 2.5k. (20,000 ohms per volt). D.C. Current: 0-50 microamps, 0-2.5 mA, 0-250 mA. Resistance: 0-6k, 0-6 Megs. (300 ohm and 30k at centre scale). Capacitance: 10 pF to .001 mfd. to 1 mfd. Decibels: -20 to +22 dB.

A fully guaranteed pocket size meter (actual size: 4 1/2" x 3 1/2" x 1 1/2") knife edge pointer, top quality supplied complete with test prods and full operating instructions. ONLY 55.5.0 FREE

ALSO AVAILABLE! MODEL TE10. Identical in appearance and size with rotary type switch but 10,000 o/v. Ranges: D.C. Voltage: 0-8-30-120-600-1200 volts (10,000 ohms per volt). A.C. voltage: 0-8-30-120-600-1200 volts (10,000 ohms per volt). D.C. Current: 0-120 microamp, 0-3-300 mA. Resistance: 0-30k, 0-3 Meg. (150 ohm and 15k at centre scale). Capacitance: 50 pF to 0.01 mfd., 0.001 mfd. to 0.15 mfd. Decibels: -20 to +63 dB in 5 ranges. ONLY 89/6 POST FREE

Optional Extra
Attractive carrying case suitable for either meter, 13/6 only. (Bonafide trade enquiries invited.) Leaflet available.

NEW! NEW! "AIR KING"

A New Six transistor luxury portable with the new "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio, with full MEDIUM wave and LONG wave coverage. Look at these features!



- ★ 500 milliwatt output to high flux 8 x 3 1/2 in. high fidelity loudspeaker.
- ★ Six selected Mullard Transistors in latest super sensitive circuit, plus germanium diode. ★ Compact size—only 9 1/2 x 3 1/2 x 6 1/2 in. (high).
- ★ Attractive three tone cabinet, Black, Dark Grey, and Silver Grey, with gilt control knobs and all gilt fittings.
- ★ Coax socket for car aerial. ★ Brand New guaranteed components. ★ Push pull output. ★ Automatic volume control. ★ Long life battery. ★ Super sensitive internal ferrite rod aerial. ★ Nothing more to buy. Cabinet included.


Special inclusive price for £7.19.6 Plus P. & P. 4/-

Alignment services available. Full assembly details and individually priced parts list, all of which are available separately, price 1/8, post free.

The "HIGHWAYMAN"

At last a quality Car Radio to build yourself, at an economical price. Look at these features:

- ★ Attractive styling. ★ Push-pull output. ★ 3 latest Mullard transistors plus valves type EBF8 83 and EOH 83.
- ★ No Buzz. High Output and sensitivity. ★ Printed circuit (newest type). 7" x 4" High flux p.m. speaker. ★ Medium and Long Waves. ★ Push Buttons for fingertip control. ★ Extremely low Battery consumption (less than 1 amp). ★ Easy to fit any make car (Positive earth only). ★ 12 volt operation. ★ Compact size measures only 7" x 7" x 2" deep. ★ Easy assembly, supplied with dial and drive already mounted.

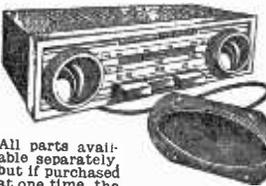

All parts available separately, but if purchased at one time, the whole will be supplied at a special inclusive price of only

£10.19.6 Plus 4/- P. & P.

Parts list and comprehensive instruction booklet 2/6, post free. (Deducted from cost if complete parcel purchased later.)

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Technical Training in Radio, Television and Electronics Engineering with



Choose the *RIGHT* course:

RADIO & TELEVISION ENGINEERING
INDUSTRIAL TELEVISION

RADIO & TELEVISION SERVICING
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC
COMPUTERS & PROGRAMMING


ICS provides thorough coaching for professional examinations:

Brit. I.R.E., City and Guilds Telecommunication Technicians, C. & G. Radio & TV Servicing (R.T.E.B.); C. & G. Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Courses

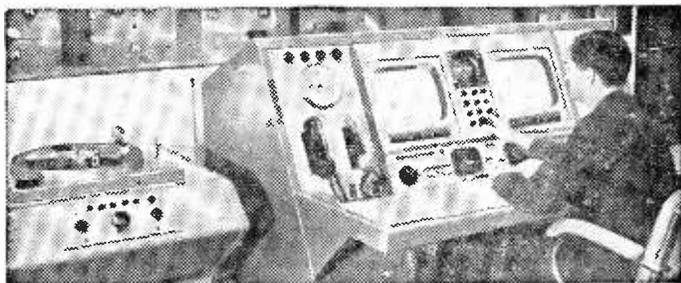Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multimeter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.



THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING. FARMING, GARDENING. ARCHITECTURE & WOODWORKING. SELLING & MANAGEMENT. ART. PHOTOGRAPHY, etc., etc.

PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . .

INTERNATIONAL CORRESPONDENCE SCHOOLS
(DEPT. 170) INTERTEXT HOUSE, PARKGATE RD., LONDON, SW11
PLEASE SEND FREE BOOK ON.....
NAME
ADDRESS
.....
OCCUPATION..... AGE..... 9.62

AWKWARD SPOT?
MINIATURE COMPONENTS?

Soldering is easier with the

NEW 15 WATT
SOLO electric soldering iron

electric soldering iron

- Ideal for transistorised and printed circuitry.
1/4 in. diam. bit in 1/8 in. diam. stem will reach normally inaccessible connections and components.
Just the right amount of heat. Melts resinscored solder within 1/4 minutes from cold.
Spare parts easily replaceable—readily obtainable.
Designed and made by the team responsible for the highly successful 25-watt Solon.
200-220V or 220-240V.

LIST PRICE 23/4d Obtainable from your usual electrical stockist, or electrical counter of your hardware store.

AN AEI PRODUCT

For further details, write to the local AEI Stock Depot, or to:

Associated Electrical Industries Limited
Distribution Equipment Sales Dept
145 Charing Cross Rd.
London WC2



BENTLEY ACOUSTIC CORP. LTD.

33 CHALCOT ROAD, CHALK FARM, LONDON, N.W. 9

Telephone PRImrose 9090

Express postal service. All orders despatched same day as received. Immediate despatch of C.O.D. orders if telephoned before 3.30 pm.

Table listing various electronic components such as resistors, capacitors, and diodes with their part numbers and specifications.

METAL RECTIFIERS, DRMB1 13/-, DRM2B and DRMB 15/6, LW7 21/-, RMO 7/1, RM1 5/3, RM2 7/8, RM3 7/9, RM4 14/-, RM5 19/6, 14A8 17/6, 14A9 25/-, 14A10 27/-, 14A12 28/-, 14A18 33/-, 14B13 35/-, 14B21 11/6, FC101 17/6, 16RCL1 16 1/8, FC31 21/-, 16RD 2.2 11 1/2, 16RE 2.1 8 1/8, 18RA 1.8 1 1/8, 18RA 1.8 1 1/2, FC11 9/6, FC14 15/-, LW15 26/-, ELECTROLYTICS, Can types: 32 x 32/450 v. 5/8, 50 x 50/350 v. 7/-, 64 x 120/350 v. 8/3, 60 x 230/275 v. 9/6, 100 x 400/275 v. 12/6, 100/275 v. 3/-, 200/275 v. 4/-, 100 x 200/275 v. 9/6, Tubular types: 6/450 v. 1/3, 6/450 v. 2/9, 32/450 v. 3/9, 8 x 3/450 v. 3/-, 16 x 16/450 v. 4/-, 32 x 32/350 v. 4/-, 8 x 16/450 v. 3/9, Postpacking charges 6d. per item except where stated. Orders over £3 post free. C.O.D. 2/6 extra. Shop hours 8.30-5.30. Sat. 1 p.m. Any parcels insured against damage in transit for only 6d. extra.


Our full list, with terms of business, includes all types of components, transistors, microphones, condensers, resistors, etc. Price bid. Please note that all goods advertised are brand new, subject to the full manufacturers' guarantees, and actually in stock. We do not sell second-hand goods or manufacturer's rejects.

STERN'S MULLARD DESIGNS

Designed by MULLARD—presented by STERN'S strictly to specification

MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-valve pre-amplifier with which undistorted power output of up to 10 watts is obtained. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES, including PARMEKO MAINS TRANSFORMER and choice of the latest Ultra-Linear PARMEKO or the PARTRIDGE Output Transformer. COMPLETE KIT OF PARTS **£10.00** (PARMEKO Output Trans.). Alternatively we supply ASSEMBLED AND TESTED. **£11.00** INCORPORATING PARTRIDGE OUTPUT TRANSFORMER, **£1.60** EXTRA.

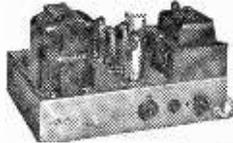

MULLARD'S PREAMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves, and designed to operate with the MULLARD MAIN AMPLIFIERS, but also perfectly suitable for other makes. PRICE COMPLETE **£6.60** ASSEMBLED AND TESTED **£8.00**




Supplied strictly to MULLARD'S SPECIFICATION and incorporating:

- Equalisation for the latest R.I.A.A. characteristics.
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- Sensitive Microphone Channel. ● Wide range BASS and TREBLE Controls.

THE MULLARD "510/RC" AMPLIFIER

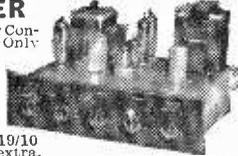
The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 watts high quality reproduction. Only SPECIFIED COMPONENTS and new MULLARD VALVES are supplied including PARMEKO MAINS TRANSFORMERS and choice of the latest PARMEKO or PARTRIDGE ULTRA-Linear Output Transformers.



KIT OF PARTS **£11.00** OR ASSEMBLED AND TESTED **£13.00**
H.P. Dep. **£2.60**, 12 months at 17/0. Dep. **£2.14**, 12 months at 19/10
ABOVE incorporating PARTRIDGE OUTPUT TRANS. **£1.60** extra.


THE MULLARD "33/RC"

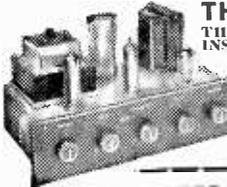THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION PROVIDING EXCELLENT REPRODUCTION OF UP TO 3 WATTS OUTPUT COMPLETE KIT **£7.10.0** OR ASSEMBLED **£8.19.6**
OF PARTS AND TESTED **£2.0.0**
(plus 7/6 carriage and insurance) H.P. Terms: Deposit **£2.0.0**
and 8 months at **£1.0.0**. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMEKO OUTPUT TRANSFORMER.



STERN'S INTER-COMM BABY ALARM

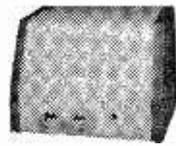A small versatile Unit employing the new MULLARD ECL86 valve and designed to provide two (or three) way conversation up to extreme distances. Operates from A.C. mains 200 to 250 Volts. PRICES . . . MASTER UNIT and ONE EXTENSION



KIT OF PARTS **£6.17.6** ASSEMBLED AND TESTED **£8.8.0**
Consists of a MASTER UNIT, size only 8 1/2 x 5 1/2 x 6 in., and ONE EXTENSION (a second extension may be added to any time). The Master Unit incorporates switching and power supply and with the chassis completely isolated from the mains is operated in absolute safety. Cases covered in quality leatherette.

A BULK PURCHASE OF MARCONIPHONE TAPE RECORDING EQUIPMENT ENABLES US TO OFFER THE MODEL MTR/1 PORTABLE TAPE RECORDER



FOR ONLY **£26.0.0** (Carr. & Ins. 10/- extra)
Deposit **£5.4.0**, 12 months of **£1.18.2**. The list price of the MTR/1 is **£44.2.0**. It is a 3-Speed Twin Track Recorder incorporating the latest Collaro "Studio" Tape Deck and operates at 1 1/2, 3 1/2 and 7 1/2 in./sec. Speeds. It incorporates a "Pause" Control, a safety interlock device which ensures that a recorded tape cannot be accidentally erased and a low level output socket so that the output may be fed into an external high fidelity amplifier for monitoring purposes or for high quality reproduction on playback.

PRICE REDUCTIONS

(a) The KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-valve PRE-AMP CONTROL UNIT H.P. Dep. **£3.7.0** and 12 months at **£12.9.0**..... **£15.15.0**
(b) The "5-10" and the 2-stage PRE-AMP both ASSEMBLED and TESTED H.P. Dep. **£3.16.0** and 12 months at **£17.8.0**..... **£18.18.0**
With Partridge Output Transformer **£1.60** extra.

RECORD PLAYERS

The Latest Models are in stock many at reduced prices.
Send S.A.E. For Illustrated Leaflet.
THE NEW GARRARD "AUTOSLIP" 4-speed Autochanger with Crystal Pick-up **£8.10.0**
COLLARO "JUNIOR" 4-SPEED SINGLE RECORD PLAYER with separate Crystal Pick-up Carriage and Insurance 5/- Above Pick-up separately for **£1.60**.
THE NEW COLLARO C60 4-speed Autochanger unit with Studio "O" Pick-up..... **£7.19.6**
THE E.M.I. 4-speed Single Record Player with Crystal Pick-up **£6.9.6**
B.S.R. MODEL U414. A 4-speed mixer Autochanger with Crystal Pick-up **£7.10.0**
Available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 Records..... **£8.13.10**
GARRARD MODEL TA/MK.II 4 speed Player fitted high output Crystal Pick-up..... **£8.10.0**
GARRARD MODEL RC10A. Autochanger 4-speeds. High output. Crystal Pick-up..... **£9.10.0**
Carriage and Insurance on each above 5/- extra.

SPECIAL CASH OFFER


This very attractive PORTABLE PLYMER CASE



together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER ALL for ONLY **£8.7.6** (Plus 7/6 Carr. & Ins.)
The Amplifier consists of a 2-stage design incorporating modern B.V.A. valves and has separate BASS and TREBLE CONTROLS.
The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexine.
WE ALSO SUPPLY SEPARATELY—
(a) The 2-stage (plus Rectifier) AMPLIFIER **£4.2.6**
(b) The PORTABLE CARRYING CASE **£3.17.6**
(c) 6in. P.M. SPEAKER 18/9. Carriage and Insurance 4/- extra.

MULLARD FOUR CHANNEL MIXER UNIT

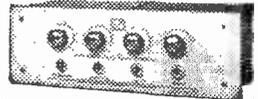Self powered with Cathode follower output. Incorporates Two inputs for MICROPHONES One for CRYSTAL PICK-UP and a fourth for RADIO or TAPE Complete Kit of Parts **£8.8.0**
Assembled and Tested **£10.0.0**
TERMS: Deposit **£2** and 12 months at 15/-
MODEL H.L. one microphone input matched for moving coil or Ribbon Mike. **£1.17.0** extra.



The TOHPHONIC



TRANSISTOR BATTERY OPERATED INTERCOM 89/6 P. & P. 4/-

Including PP3 battery and 55 yards lead with plugs. A completely Portable Intercom with 101 uses being ideally suitable for being battery operated, it is completely safe. Two-way calling system and volume on/off switch, the units are housed in attractive plastic cabinets (black/white) with chrome stands, it is extremely economical operating on one 9-volt battery, replacement price being 2/6

STERN RADIO 109, FLEET ST., LONDON, E.C.4. PREMIER RADIO 23, TOTENHAM COURT RD., LONDON W.1. TELEPHONE FLEET ST. 58123 LONDON, E.C.4. MAIL ORDERS and all POSTAL ENQUIRIES to 7-9 TUDOR PLACE, TOTENHAM COURT RD., LONDON, W.1. MUSEUM 4128/9

Stereophonic Sound by Stern's

THE "STP-1" STEREO TAPE PREAMPLIFIER

DESIGNED TO OPERATE WITH

- BRENNELL Mk. V TAPE DECK incorporating similar 4-TRACK MINI-FLUX TAPE HEADS.
- PUSH-PULL OSCILLATOR CIRCUIT
- 4-SPEED EQUALISATION
- FERROXUBE OSCILLATOR TRANSFORMER
- SENSITIVE METER FOR SIGNAL LEVEL
- SEPARATE GAIN CONTROLS IN EACH CHANNEL
- MULLARD VALVES INCORPORATED



COLLARO "STUDIO" TAPE DECK incorporating the latest 4-TRACK REUTER TAPE HEADS. OVERALL SIZE (Case 13 1/2 x 3 1/2. FRONT PANEL (Choice of Black or White) 14 x 3 1/2 in.

PRICE
£28.0.0

Including separate Power Supply Unit.
Deposit £5.12.0, 12 months at £21.1.0.

COMBINED PRICE SCHEDULE

THE "STP-1" PREAMPLIFIER is offered

- WITH TAPE DECKS AS FOLLOWS:
- BRENNELL Mk. V 4-TRACK MODEL..... **£67.0.0**
Deposit £13.8.0, 12 months at £41.8.5.
- COLLARO "STUDIO" 4-TRACK MODEL..... **£45.0.0**
Deposit £9.0.0, 12 months at £36.0.

STEREOPHONIC RECORD PLAYER UNITS ARE AVAILABLE FROM STOCK

MULLARDS "10 PLUS 10"

STEREO AMPLIFIER

A high fidelity design based on the famous Mullard 10-10". Provides up to 10 watts (per channel) Superb reproduction. Frequency response flat to within 3 db from c/s. to 60 Kc/s at 50 Mw. Total Harmonic Distortion at 10 watts 0.1%.



- (a) ASSEMBLED COMPLETE AMPLIFIER, including CONTROL UNIT (as Illustrated)..... **£21.0.0**
Deposit £4.4.0, 12 months at £11.10.10.
- (b) A complete KIT of PARTS..... **£18.10.0**
Deposit £3.14.0, 12 months at £17.2.

We also supply the assembled MAIN AMPLIFIER only (excludes control unit) for operation with our DUAL CHANNEL PREAMPLIFIER, this provides for a more versatile or elaborate installation and would be essential if a low output Magnetic Pick-up, such as the Deca, is to be used.

- (a) THE ASSEMBLED MAIN AMPLIFIER with the ASSEMBLED DUAL CHANNEL PREAMPLIFIER..... **£30.0.0**
Deposit £5.0.0, 12 months at £24.0.
- (b) A complete KIT of PARTS for both Units..... **£26.0.0**
Deposit £5.4.0, 12 months at £18.2.

Illustrated and Descriptive Brochure available. Please enclose S.A.E.

ARMSTRONG RADIOGRAM CHASSIS

FULL RANGE IN STOCK, please enclose S.A.E. for leaflets.
STEREO 12 Mk. 2 £43.10.0

(ILLUSTRATED)



Deposit £3.14.0, 12 months at £3.3.10.

The most complete chassis ever produced, combines AM and FM Tuners, a Stereo Control Unit and two High Fidelity Amplifiers in one compact unit, provide a total of 16 watts for both mono and stereo. Other features include: inputs for tone recording, playback, pick-ups and stereo radio (should this come about); separate wide range bass and treble control and balance control.

STEREO 55 £32.15.0 Deposit £3.15.0
12 months at £27.8

A junior version of the Stereo 12 Mk. 2 providing ten watts output, five watts from each amplifier and covering the VHF and Medium wavebands.

JUBILEE Mk.2 £30.12.0 Deposit £3.4.0
12 months at £24.9

A Hi-Fi mono chassis giving eight watts push-pull output and covering VHF, medium and long bands. Tape recording and playback inputs.

AF208 £22.18.0 Deposit £4.18.0
12 months at £13.10

An AM/FM chassis providing 5 watts output and covering the full VHF and medium wavebands. Tap: recording and playback inputs.

TVB VHF TUNER £21.18.0 Deposit £4.14.0
12 months at £11.7

A self-powered high-fidelity tuner of outstanding design, incorporating features which are normally found only in the most expensive tuners. The full VHF band (87-108 Mc/s) is covered and a matching output control enables the output to be varied between 0 and 500 mV.


THE MULLARD "10+10" STEREO AMPLIFIER

(described below) with the "STP-1" PREAMPLIFIER and one of the TAPE DECKS provide a COMPLETE STEREOPHONIC INSTALLATION. WE OFFER the "10+10", the "STP-1" and the

- BRENNELL Mk. V 1-DECK..... **£87.0.0**
Deposit £17.8.0, 12 months at £67.8.
 - As above with COLLARO "STUDIO" DECK
Deposit £12.12.0, 12 months at £41.6.0. **£65.0.0**
- Please enclose S.A.E. with all enquiries.

DUAL CHANNEL AMPLIFIER

Incorporates two Mullard 2-valve Preamplifiers combined into a Single unit enabling it to be used for both STEREOPHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 mV/ohms. COMPLETE KIT OF PARTS **£12.10.0** ASSEMBLED AND TESTED **£15.0.0**
H.P. £2.10.0 & 12 mths. at 18/4. H.P. £3.0.0 & 12 mths. at £1.2.0

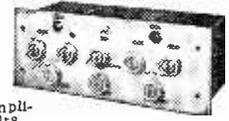

The "TWIN-THREE" STEREO AMPLIFIER

OFFERED ASSEMBLED and TESTED for (Carr. & Ins., 7/6 extra).

Based on a recent design by MULLARD LTD., the "TWIN THREE" is ideally suited for use in PORTABLE RECORD PLAYERS for which purpose we offer a specially designed Portable Case. It incorporates MULLARD ECL86 valves, separate BASS and TREBLE CONTROLS, and produces excellent reproduction of up to 3 watts per channel. Frequency response is 40 c/s to 30 Kc/s. Size is only 1 1/2 x 3 x 5 1/2 in.



To construct a STEREO PORTABLE RECORD PLAYER WE OFFER the assembled AMPLIFIER with two ROLA 3 x 5 in. LOUDSPEAKERS and the PORTABLE CASE for **£14.0.0** (Carr. & Ins., 10/- extra). Deposit £2.16.0-12 months at £1.0.6.

SUITABLE RECORD PLAYERS are AVAILABLE FROM **£8.14.0**

"The TUDOR"

AM/FM TUNING UNIT

A SELF POWERED HIGH FIDELITY TUNER OF OUTSTANDING DESIGN.

PRICE ONLY **£19.19.0** Deposit £4.0.0 and 12 months at £19.4.

Provides full coverage of the VHF/FM band (87-108 Mc/s) and also the LONG and MEDIUM wavebands. Incorporates Multiplex outlet socket for stereophonic purposes (when adopted) and separate controls for tuning the FM and AM bands. Operates perfectly with the STERN-MULLARD AMPLIFIERS and contains matching FRONT PANEL in Black/Gold or White/Black. Also operates equally well with any Amplifier requiring input of 100 to 350 mV/ohms.

"HI-FI" LOUDSPEAKERS WE HAVE IN STOCK A COMPLETE RANGE BY GOODMAN'S-WHARFEDALE-W.B. ILLUSTRATED AND PRICE LEAFLETS ON REQUEST.

STERN RADIO PREMIER RADIO

MAIL ORDERS and all POSTAL ENQUIRIES to

BUILD A HIGH QUALITY TAPE RECORDER LIKE THIS FOR £35.00

FOR THIS WE SUPPLY

- * Complete Kit of Parts to Build the HF/TR3 Tape Amplifier-Loudspeaker.
- * The New Collaro "Studio" Tape Deck.
- * Rola/Celestion 10 x 6in. P.m. Loudspeaker.
- * Portable Carrying Case (as illustrated).
- * ACOS Crystal Microphone and 1,200ft. Spool E.M.I. Tape.

Deposit £7.00 and 12 months at £21.14


ALTERNATIVELY WE SUPPLY THE COMPLETELY ASSEMBLED and GUARANTEED TAPE RECORDER FOR £39.10.0

H.P. Terms: Deposit £7.18.0 and 12 months of £27.11



A very high quality Amplifier incorporating 3-speed treble equalisation by the latest FEROXUCUBE POT CORE INDUCTOR. FOR COLLARO TRUVOX - BRENNEL WEARITE Tape Decks, has GILSEN Output Transformer. Includes separate Power Supply Unit.

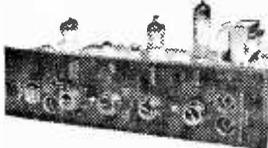HF/TR3MKII TAPE AMPLIFIER (Mullard Type "A" design)



ASSEMBLED and TESTED £17.0.0
 Deposit £3.8.0, 12 months at £14.1.1

SPECIAL "COMBINED ORDER" PRICES

- For Constructors with their own cabinet—WE OFFER—
- (a) COMPLETE KIT to build the HF/TR3 Amplifier together with the COLLARO "STUDIO" DECK **£26.0.0**
 - (b) AS above but with the HF/TR3 supplied ASSEMBLED and TESTED **£29.10.0**
 - (c) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENNEL MK. V TAPE DECK **£42.0.0**
 - (d) AS above but with HF/TR3 supplied ASSEMBLED and TESTED **£45.10.0**
 - (e) THE ASSEMBLED AND TESTED HF/TR3 AMPLIFIER with the WEARITE MODEL 4A DECK, incorporates Wearite Head Lift Transformer etc. Deposit £12.12.0, 12 monthly payments of £4.8.9. (Carriage and Insurance on each above is 10/- extra.) **£60.10.0**


ADD "HI-FI" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION WITH MULLARD TYPE "C" TAPE PRE-AMPLIFIER—ERASE UNIT

The "HI-FI" link to add full tape recording facilities to High Fidelity home installations. Incorporates FEROXUCUBE POT CORE PUSH PULL OSCILLATOR and 3-speed treble equalisation by FEROXUCUBE POT CORE INDUCTOR FOR WEARITE-COLLARO-TRUVOX OR BRENNEL TAPE DECKS. Includes separate power Supply Unit.



ASSEMBLED and TESTED **£17.0.0**
 Deposit £3.8.0, 12 months at £14.1.1
 (Excluding power unit £11.15.0 and £14.10.0 respectively.)

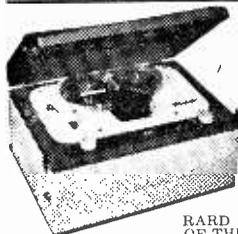- (a) The COLLARO "Studio" Deck with the Model "C" Pre-amplifier and POWER SUPPLY UNIT ASSEMBLED AND TESTED **£29.10.0**
- (b) AS above but the TYPE "C" Unit and POWER UNIT supplied as COMPLETE KIT OF PARTS Deposit £5.6.0, 12 monthly payments of £1.18.10 **£26.10.0**
- (c) The BRENNEL Mk. V Deck with the Model "C" PRE-AMPLIFIER and POWER UNIT. ASSEMBLED AND TESTED **£46.0.0**
- (d) AS above but the Model "C" PRE-AMPLIFIER and POWER UNIT supplied as a COMPLETE KIT OF PARTS **£43.0.0**
- (e) THE WEARITE MODEL "4A" DECK with ASSEMBLED and TESTED Model "C" PRE-AMPLIFIER and POWER UNIT incorporating WEARITE HEAD LIFT TRANSFORMER, Etc. Deposit £12.2.0 and 12 months at £4.8.9 (Carriage and Insurance on above is 10/- extra.) **£60.10.0**



The MODEL HFG/2R PORTABLE TAPE RECORDER (Original Price £33.0.0) FOR ONLY 22 Gns.

Deposit £4.14.0, 12 months £11.3.9
 Crystal Microphone £1.0.0 extra. (Carr. and Ins. 10/- extra). Incorporates THE LATEST GARRARD "MAGAZINE" TAPE DECK and a HIGH QUALITY AMPLIFIER which is entirely based on the very successful MULLARD TYPE "A" DESIGN and specifically developed to operate the GARRARD DECK. Price INCLUDES SUPPLY OF THE GARRARD TAPE MAGAZINE and

4in. SPOOL OF DOUBLE PLAY TAPE. Comprises a Twin Track Recorder operating at 3 1/2 in./sec. speed and providing up to 1 hour 10 mins. playing time. Truly "Portable", weighs only 22 lbs. Outstanding features are excellent performance and simplicity of operation

THE TRUVOX "SERIES 80" TAPE EQUIPMENT

- MODEL D82 Incorporating Twin Track Heads. Deposit £5.5, 12 months of £11.8.7 **£26.5.0**
- TAPE DECK
- MODEL D84 With Four Track Heads and Track Switch for Mono/Stereo operation. Deposit £6, 12 months of £23.11. **£29.8.0**
- TAPE DECK
- MODEL PD82 Complete Twin Track Mono Recorder-Pre-amplifier Unit. Deposit £8.8, 12 months of £31.7. **£42.0.0**
- MODEL PD84 Complete Four Track Mono Recorder-Pre-amplifier Unit incorporating outlets for Stereo reproduction. Deposit £9.4, 12 months of £37.6. **£46.0.0**

The PD82 and 84 comprise two self-contained units to add full tape facilities to existing sound reproducing installations (Hi-Fi equipment, radiograms, record reproducers, or good radio receivers) DESCRIPTIVE LEAFLETS READILY AVAILABLE

THE 'ADD-A-DECK'

Incorporating GARRARD TAPE DECK and MODEL HF/G2P PRE-AMPLIFIER

Supplied on ONE CHASSIS (as illustrated) READY FOR USE **18 Gns.**
 (Carr. & Ins. 10/- extra.)



Price includes Garrard Magazine and a 4 in. Spool Double Play Tape

H.P. Deposit £3.16.0, and 12 months of £17.8. Provides complete tape recording facilities and designed to operate through the pick-up sockets of the standard type of RADIO RECEIVER, or an AMPLIFIER, from which really first class reproduction is obtained. It consists of a Twin Track Deck connected to the Pre-amplifier and operates at 3 1/2 in./sec. speed providing up to 1 hr. 10 mins. playing time.

The JEMCO MODEL MT-955 MULTIMETER



50,000 ohms per volt — D.C.
 5,000 ohms — A.C.
 A truly efficient Meter for the amateur or professional man, having features found normally in more expensive Meters. Ranges:
 D.C. volts 2.5-10-50-250-1K
 A.C. 2.5-10-50-250-1K
 D.C. Current 100µA-10mA-100mA-500mA 10 amp Resistance 4 Ranges up to 20 meg.
 Add D.B. 0-46 Size 7 x 5 1/2 x 3 1/2 in.
 PRICE, including Full Test **£12.19.6** p. & p.
 Lead Kit

SPECIAL OFFER!

WE HAVE A LIMITED QUANTITY OF HMV Model 544 STEREO AMPLIFIERS and OFFER THEM FOR **£18.18.0** Deposit £3.18.0, 12 mths. £17.8. LIST PRICE £27.6.0. Size 11 x 10 x 4 in. high.

A complete Stereo Amplifier incorporating All Controls. Suitable for Crystal or Ceramic Stereo Pick Ups producing 4 watts peak output per channel from input of 200 mV/ohms. Operates with 15 ohm Loudspeakers and has power available for Radio Tuner.

109, FLEET ST., LONDON, E.C.4.
 TELEPHONE FLEET ST. 5812-3
23, TOTTENHAM COURT RD., LONDON W.1
 TELEPHONE MUSEUM 3451
7-9 TUDOR PLACE, TOTTENHAM COURT RD., LONDON, W.1. TELEPHONE MUSEUM 6128/9

MAXI-Q

REGD.

COIL PACKS

CP.3/370 pF and CP.3/500 pF. These 3 waveband Coil Packs are available for use with either 370 pF or 500 pF tuning condensers. The coverages are: Long Wave 800-2,000 metres. Med. Wave 200-250 metres, Short Wave 16-50 metres. Designed for use with "MAXI-Q" glass scale type S2. Retail price of each unit: 32/- plus 9/7 P.T.—total 41/7.

CP.3/G. As above but with Gram. position, suitable for use with 500 pF tuning condenser: 39/- plus 11/8 P.T.—total 50/8.

CP.3/F. This Coil Pack is for use with a 500 pF tuning condenser and covers the standard, Long, Med. and Short wavebands with the addition of the band 50/160 metres. This covers the Trawler band, Aeronautical and the 80 and 160 metre Amateur bands: 49/- plus 14/8 P.T.—total 63/8.

CP.3F/G. As CP.3/F but with Gram. position: 57/- plus 17/1 P.T.—total 74/1.

CP.4/L and CP.4/M. These compact 4-station Coil Packs are available for either 1 Long Wave and 3 Medium Wave Stations (CP.4/L) or 4 Medium Wave Stations (CP.4/M.). They are fully wired and require only four connections for use with any standard frequency changer valve. 25/- plus 7/6 P.T.—total 32/6.


C.P.4L/G and CP.4M/G. As CP.4/L and CP.4/M but with provision for Gram. position. 31/- plus 9/3 P.T.—total 40/3.

See Technical Bulletin DTB.9 for details of all Coil Packs, 1/6.

GENERAL CATALOGUE covering full range of components, send 1/6 in stamps or P.O. PLEASE SEND S.A.E. WITH OTHER ENQUIRIES.

DENCO (Clacton) LTD. (Dept.P.W.) 357/3 Old Road, Clacton-on-Sea, Essex

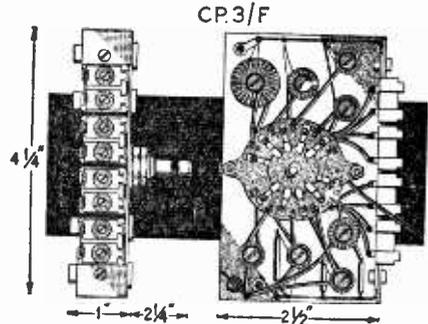STOP PRESS: MULLARD "Twin Three-Three" Stereo Amplifier. Punched Aluminium Chassis and Hammered Gold printed Front Panel, 25/9.



ERSIN MULTICORE SOLDERS

for a first class joint every time

Ersin Multicore contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON
5/-

HANDYMAN'S
CARTON

Suitable for 200 average joints. 6d.

HDME CONSTRUCTORS
2/6 PACK

In addition to the well-known Home Constructors Pack (containing 16ft. of 18 s.w.g. 60/40 alloys) a similar pack is now available containing 35ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SAVIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.

SIZE 1 CARTON 5/-
Available in three specifications.



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruding flex. 3/6 each



MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)

EXPRESS ELECTRONICS

ROSENDENE LABORATORIES
KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/60BA6	6/-	12AU7	8/9	DH77	6/-	EF91	4/-	PL82	7/-	
1C3	8/-	12AX7	8/9	DH142	8/6	EF92	5/6	PL83	7/6		
1F1	8/-	12BH6	8/6	DH150	10/-	EL41	9/6	PY81	6/6		
1F2	7/6	12BH7	10/6	DK91	7/6	EL84	7/-	FX82	7/6		
1FD1	8/-	12BR7	8/9	12K8GT11	10/-	DK95	10/-	FX83	7/6		
1FD9	7/6	12BW5	7/6	12Q7GT	7/6	DL92	7/6	FS41	9/6		
1L4	6/9	12CW7	7/-	12A5	9/-	DL94	8/6	U37	11/6		
1P1	8/-	12D5	4/-	12SA6G	8/6	DL86	8/6	UY81	10/-	U52	7/6
1P10	7/6	12F12	4/-	12L6GT	7/6	EB91	4/-	EZ40	7/6	U76	7/6
1P11	7/6	12HG7	2/-	12Z4G	9/-	EB41	10/-	EZ80	8/-	U78	5/-
1R5	6/-	12J7G	7/6	30C1	7/6	BF80	6/6	EZ81	8/9	U142	7/6
1R5	8/-	12K7G	5/6	30L1	7/6	ECC81	6/-	HVR2	9/6	UBC41	8/6
1T4	7/6	12K8G	8/-	35L6GT	8/-	ECC82	6/7	KT30	11/6	UCH42	8/6
1U5	5/6	12Q7G	5/6	35W4	8/6	ECC83	8/9	KT86	7/6	UY41	8/6
3Q4	8/-	12L7GT	6/-	35Z4GT	8/-	ECC84	7/6	N17	7/6	UY41	8/6
384	7/6	12SN7GT	8/-	35K1	10/6	ECC85	8/6	N18	8/-	UY41	7/6
3V4	8/6	12V6G	7/6	6Y7G3	7/6	ECC82	8/-	N19	7/6	W17	7/6
5U4G	7/6	3X4	8/-	80	8/-	ECH42	9/-	N709	7/-	W76	4/6
5Y3GT	5/-	6X5B	5/-	DAF91	7/6	ECH91	10/-	PC34	7/6	W142	8/6
5Z4G	9/8	8T87	9/8	DAF96	8/-	ECL80	9/6	PC180	7/6	X17	7/6
6AK6	6/6	8C8D3	4/-	DOC90	12/6	ECL82	9/-	PCF82	7/6	X142	9/6
6AL5	4/-	12AD8	11/6	DF91	7/6	EF41	9/-	PCL82	8/-	X150	9/6
6AM6	4/-	12AH8	10/-	DP96	8/-	EF80	8/-	PCL84	9/-	Z77	4/6
6AT6	9/-	12AT7	6/-	DH76	7/6	EF86	9/-	PL81	12/6	ZD17	7/6

High Stability Resistors 1W 5% 50 Ω to 1M, 9D, Midget Ceramics 500 v. 9d. Coils Super quality 1m., 6d., 3d., Pings 9d., Sockets 9d., Silicon H.T. Rects. 250v. 200 MA lin. x 1 1/4. 1/76. Contact Cooled 250v. 50 MA 8/6. 86 MA 8/6.

N3W TRANSISTORS BY MULLARD. OC19, OC26, OC66, 25/-; OC44, OC45, 9/-; OC70, OC71, 8/-; OC72, 7/6; OC72 matched in pra. 16/-; OC74, OC75, OC76, OC81, 7/6; OC82, OC170, 9/6.







VALVES MATCHED IN PAIRS

EL84 17/-, N709 17/-, 6V6G 17/-, 6HW6 18/- per pair. Push Pull P.P. Transformers for above 3-15 Ω 14/6, P. & P. 1/6, 12in. P.M. Speakers 3 Ω 24/6. Baker's "Behnert" 12in. 15 Ω 15/9, 90/-, 12in. Stereo Model, 27/7.0.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94, 19/8 ECH42, EP41, EBC41, DK96, DF96, DAF96, DL96, 27/8 EL41, EZ40, 37/8 1C3, 1F1, 1FD1, 1P1, 27/6 UCH42, UP41, UBC41, 1R5, 1T4, 1R5, 384, or 3V4, 19/8 UL41, UY41, 35/- Postage and packing 6d. Over £1 port free. C.O.D. 2/6.

Just a few of our BARGAINS

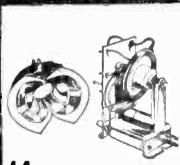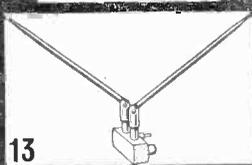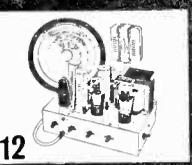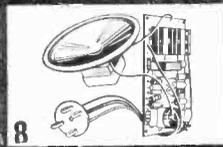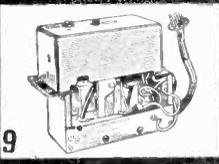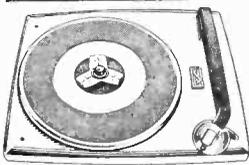

**RADIO & T.V.
COMPONENTS
[ACTON]
LIMITED**

1. **SUPER 5 TRANSISTOR POCKET RADIO INCORPORATING PRINTED CIRCUIT & MINI-EARPIECE.** No Aerial or Earth required. 4 1/2 x 3 1/4 x 1 1/2 in. Output 200 m.w. 5 first quality transistors. High flux moving coil speaker. M/L Internal high gain ferric aerial. £2.19/6. P. & P. 3/6. Circuit diagram 1/6, free with parts. All parts available separately.

2. **TRANSISTORISED POCKET RADIO** with printed circuit, mini-earpiece, high gain ferric slab aerial. No aerial or earth required. To build yourself for completely personal listening. 4 1/2 x 3 1/4 x 1 1/2 in. Luxembourg in favourable areas. Only 21/- P. & P. 2/6. All parts available separately.

3. **A.C./D.C. POCKET MULTI-METER KIT.** 2 in. moving coil meter, scale, calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms ranges 0-10,000, 0-100,000, 24/6. P. & P. 2/-. Wiring diagrams 1/- free with parts.

4. **SIGNAL GENERATORS.** Cash £7.5.0, or 30/- deposit and 6 monthly payments of 21/6. P. & P. 5/6. Coverage 100 kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6 1/2 x 5 1/2 in. Three miniature valves and Metal Rectifier. A.C. mains 200/250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eyes output indicator. Accuracy ± 2 per cent.

5. **SIGNAL GENERATORS.** Cash £5.5.0, P. & P. 5/6. Coverage 120 kc/s to 84 Mc/s. Case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ± 2 per cent.

6. **STAAR 45.** 9 v. BATTERY RECORD PLAYER complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on/off switch governed motor, attractive two tone grey finish. £2.14/6. P. & P. 2/-.

7. **CARRYING CASE FOR STAAR 45 or COMPLETE KIT** beautifully styled in two tone with record compartment. Specially designed to take player and amplifier. Just screw in and connect up. All parts available separately. Case only 22/6. P. & P. 4/-. Complete kit £5.10.0. P. & P. 5/-.

8. **TRANSISTORISED AMPLIFIER,** suitable STAAR 45. Output 1 watt. Size 4 1/2 x 2 1/2 in. Printed circuit, tone/volume controls plus 4 transistors. Push-pull output complete with 5 in. moving coil speaker. Built and tested, 49/6. P. & P. 2/-.

9. **CHANNEL TUNER I.F.** 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCF60 and PC84 (in series). Cover BHC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/-. P. & P. 3/-.

10. **B.S.R. MONARCH UAS WITH FUL-FI HEAD.** 4-speed, plays 10 records, 12 in., 10 in., or 7 in. at 16, 33, 45 or 78 r.p.m. Intermixes 7 in., 10 in. and 12 in. records of the same speed. Has manual play position: colour brown. Dimensions: 12 1/2 x 10 1/2 in. Space required above baseboard 4 1/2 in. below baseboard 2 1/2 in. Fitted with Ful-Fi turnover crystal head, £8.19/6. P. & P. 5/6.

11. **PUSH PULL OUTPUT STAGE** inclusive of transistors with input and output transformers to match 8 ohms speech coil, suitable for use with the POCKET RADIO. Kit of parts, including transistors, 19/6. P. & P. 2/-. Wiring diagram 1/6, free with parts.

12. **8-watt PUSH PULL 4 VALVE AMPLIFIER** plus METAL RECTIFIER. A.C. mains 200-250 v. Size 10 1/2 x 6 1/2 x 2 1/2 in. 5 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls. £3.19/6. P. & P. 5/-. Crystal mike to suit, 15/-. P. & P. 2/-. 8 in. P.M. Speaker to suit, 12/6. P. & P. 2/-.

13. **INDOOR AERIAL** for ITV/BBC/FM. Complete with standard co-axial plug. Heavy chrome extending dipole—7ft. fully extended. Plugs straight into T.V. or VHF Tuner. Fully directional, 10/6. P. & P. 1/6.

14. **LINE E.H.T. TRANSFORMERS.** Built-in line width control. 14 kv. Screen coil 90 in. deflection on ferrite yokes. Frame O.P. transformer pl. 18 kv smoothing condenser, suitable for 14 in., 17 in. or 21 in. tubes. With circuit diagram, 29/6. P. & P. 4/6. Suitable Focus Magnet (state tube), 10/-. P. & P. 3/-.

**21b HIGH STREET
ACTON, LONDON, W.3.**

ALL ENQUIRIES S.A.E.
GOODS NOT DESPATCHED OUTSIDE U.K.

AUDIOTRON HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR


Incorporating the latest Coliario Studio Tape Transcriber. The Audiotron High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best quality Tape and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome finish, size 14 1/2 x 15 x 8 1/2 in. high, and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflet.



HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL34, EL94, 5Y3. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDEPENDENT CONTROLS FOR BASS AND TREBLE** "Lift" and "Cut". Frequency response +3 D.B. 30-30,000 c/s. Six negative feedback loops. Hum level 60 D.B. down. **ONLY 23 millivolts INPUT** required for **FULL OUTPUT**. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For **STANDARD or LONG PLAYING RECORDS**. For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS**, etc. **OUTPUT SOCKET** with plug provides 300 v. 30 mA, and 6.3 v. 1.5 a. For supply of a **RADIO PICK-UP UNIT**. Size approx. 12-9 1/2 in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 16 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. **Only 8 Gns.** 10/- (Or factory built 51/- extra).

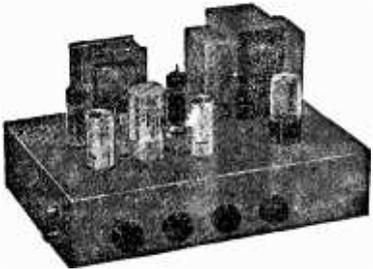

If required louvred metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9, and 9 monthly payments of 24/9.** Send S.A.E. for Illustrated leaflet detailing Ready-to-assemble Cabinets. Speakers, Microphones, etc., with cash and credit terms.

25 1/2

GNS. Carr. 17/6

ONLY 5 PAIRS OF SOLDERED JOINTS PLUS MAINS

H.P. TERMS. Deposit 22-13-9 and 12 monthly payments of 44/- Cash price if settled in 3 months.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereo amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "Lift" and "Cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL94, E281. Outputs for 2-ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. **8 Gns.** Full constructional details and price list 2/6. Carr. 10/-.

Kit can be assembled, ready for use. 55/6 extra.

R.S.C. BATTERY CHARGING EQUIPMENT

HEAVY DUTY CHARGER KIT 6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-250 v. F.W. (Bridge) Selenium Rectifier; Ammeter; Charge Rate Selector; Fuseholder and circuit. 59/9. Carr. 4/6.



Assembled 6/12v. 4-5 amps. Fitted ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with stoved blue hammer finished. Fused 69/9 and ready for use with Carr. 5/- mains and output leads. Terms: Deposit 13/3 and 5 monthly payments 18/3. 6/12 v. 3a., all facilities as above. **Only 59/9, carr. 3/9.**

PARMEKO POTTED COILS
200 mA. 12 H 100 ohms .. 16/9
120 mA. 10 H 200 ohms .. 16/9
120 mA. 6 H 10 ohms .. 13/9

SOLDERING IRONS. 230-250 v. 30 watts. First quality. For Radio work. 19/9. Spare elements and bits available.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened **TOP SHROUDED DROPT THROUGH**
250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a 17/9
350-0-350v. 80mA. 6.3v. 2a. 5v. 2a .. 18/9
250-0-250v. 100mA. 6.3v. 2a. 6.3v. 3a 21/9
250-0-250v. 100mA. 6.3v. 3.5a. C.T. 19/9
300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 25/9
300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. for Mullard 510 Amplifier .. 30/9
300-0-300v. 100mA. 6.3v. 4a. 5v. 3a .. 26/9
350-0-350v. 100mA. 6.3v. 4a. 5v. 3a .. 28/9
350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9
FULLY SHROUDED UPRIGHT
250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a 17/11
Midget type 21-3-11n .. 27/11
250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 27/9
300-0-300v. 100mA. 6.3v. 4a. 5v. 3a 27/11
300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v. 1a. for Mullard Amplifier .. 33/9
350-0-350v. 100mA. 6.3v. 4a. 5v. 3a .. 27/11
350-0-350v. 150mA. 6.3v. 4a. 5v. 3a .. 35/9
425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a 55/-

FULLY SHROUDED (continued)
425-0-425v. 200mA. 6.3v. 4a. C.T. 6.3v. 4a C.T. 5v. 3a .. 59/9
450-0-450v. 250mA. 6.3v. 4a C.T. 5v. 3a .. 69/9
MIDGET TRANSFORMERS
Midget Battery Pentode 66:1 for 351. etc. .. 4/6
Small Pentode. 5000 Ω to 3 Ω .. 4/6
Small Pentode 7/8,000 Ω to 3 Ω .. 4/6
Standard Pentode 5,000 Ω to 3 Ω .. 5/9
Midget Pentode 7,000 Ω to 3 Ω .. 5/9
10,000 Ω to 3 Ω .. 5/9
Push-Pull 8 watts. EL84, or 6V6 to 3 Ω or matched to 15 Ω .. 9/9
Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-8 or 15 Ω .. 19/9
Following types for 3 and 16 Ω speakers:
Push-Pull 10-12 watts 6V6 or EL84 .. 18/9
Push-Pull 15-18 watts. 6L6. KT66 .. 22/9
Push-Pull for Mullard 510 Ultra Linear .. 29/9
Push-Pull 20 watts sectionally wound. 6L6, KT66, EL34. etc. .. 49/9

All for A.C. Mains 200-250v., 50c/s Guaranteed 12 months.

BATTERY CHARGER KITS Consisting of Mains Transformer. F.W. Bridge. Metal Rectifier. well ventilated steel case. Fuses. Fuseholders. Grommets, panels and circuit. Carr. 3/6 extra.
6v. or 12v. 1 amp. 24/9
As above, with Ammeters 32/9
6 v. 2 amps. 25/9
6v. or 12v. 2 amps. 31/6
6 v. or 12 v. 2 amps. inclusive of Ammeter. 42/9
6 v. or 12 v. 4 amps. 49/9
6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 59/9
CHARGER AMMETERS. 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a., 0-60 a. 8/9.

MIDGET MAINS Primaries 200-250 v. 50 c/s. 250 v. 60 mA. 6.3 v. 2a .. 11/9
250-0-250 v. 60 mA. 6.3 v. 2 a. .. 12/11
Both above size 21 x 21 x 2 1/2 in.
FILAMENT TRANSFORMERS
All with 200-250 v. 50 c/s. Primaries 6.3 v. 1.5 a. 5/9; 6.3 v. 2 a. 7/6; 0-4-6.3 v. 2 a. 7/9; 12 v. 1 a. 7/11; 6.3 v. 3 a. 8/11; 6.3 v. 6 a. 17/6
SMOOTHING CIRCUITS
150 mA. 7-10 H 250 ohms. 11/9
100 mA. 10 H 200 ohms. 8/9
80 mA. 10 H 350 ohms. 5/9
80 mA. 10 H 400 ohms. 4/11
CHARGER TRANSFORMERS
All with 200-230-250 v. 50 c/s Primaries:
0-9-15 v. 1a. 12/9; 0-9-15 v. 2a. 14/9; 0-9-15 v. 3 a. 16/9; 0-9-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 23/9; 0-9-15 v. 8 a. 28/9.
AUTO (step up/down) TRANS. 0-110-120-230-250 v. 50-80 watts. 13/9; 250 watts. 39/9; 150 watts. 27/9.
MICROPHONE TRANSFORMERS 120:1 high grade, clamped. 8/9; 120:1 Potted. Mu-metal screened. 9/9.

R.S.C. (Manchester) MAIL ORDERS to 29 Moorfield Rd., Leeds 12. Terms: C.W.O. or C.O.D. No C.O.D. under £1 Ltd. Postage 2/9 extra under £2. 3/9 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

BIRMINGHAM: 6 Gt Western Arcade	SHEFFIELD: 13 Exchange St. Castle Market Bldgs.	HULL: 51 Savile St	LIVERPOOL: 73 Dale St. (8 mins. from Lime St. or Exchange Stations)	BRADFORD: 56 Morley St. (above Alhambra Theatre)	LEEDS: 5-7 County Briggate	MANCHESTER: 8-10 Brown St. (Market St.)
----------------------------------------------	-----------------------------------------------------------------	------------------------------	-------------------------------------------------------------------------------------	------------------------------------------------------------------	-----------------------------------------	------------------------------------------------------

(Half-day Wed.) (Half-day Thurs.) (Half-day Wednesday) (No half day)

SENSATIONAL STEREO OFFER ONLY 4 Gns. carr. 5/-

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v., including pair matched 6in. speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Pre-set balance control. Full instructions and point-to-point wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control. Specially Certified performance figure compare equally with most expensive amplifiers available. Hum level 7 db. down. Frequency response ± 3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF96, ECC83, 807, GZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for DANCE HALLS, CLUBS, THEATRES, etc. For use with Electronic ORGAN, GUITAR, STRING BASS etc. For standard or long-playing records. OUTPUT SOCKET PROVIDED for L.T. and H.T. for an AUDIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram, and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete Kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months guarantee, for 14 gns.

TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9. Suitable microphones and speakers available at competitive prices.

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (especially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, W.Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size approx. 9 x 6 7/16 in. High. Simple wiring diagrams, instructions and priced parts list with illustrations, 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

P.M. SPEAKERS. 10in. W.B. "Stentorian" 3 or 15 ohm. type HP1012 10 watts. hi-fidelity type. Recommended for use with our All Amplifier £4.12.9. 12in. R.A. 3 ohms 10 watts (12,000 lines), 59/6.

TWEETERS. Plessey 30 19/9. 15 0 25/9.

R.S.C. EQUIPMENT CABINET. Size and appearance as Standard Bass Reflex Cabinet. Top hinged Base board adjustable. 6 gns.

Jason FM/IT V.H.F./FM Radio Tuner design. Total costs of parts including valves. Tuning dial, Escutcheon, etc. £6.19.9. Other Jason equipment in stock.

LINEAR L45 MINIATURE 4/5 WATT QUALITY AMPLIFIER. Suitable for use with any record playing unit, and most microphones. Negative feedback 12db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 7-5 1/2in. High. Guaranteed for 12 months. Only £5.19.6. Send S.A.E. for illustrated leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

R.S.C. 4-5 WATT A5 HIGH-GAIN AMPLIFIER


A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down 15 db. of Negative feedback is used. H.T. or 300 v. 25 mA. and L.T. or 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tube-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Blue hammer knish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr.; or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

R.S.C. PORTABLE GUITAR AMPLIFIERS. (For 200-250 v. A.C. Mains) Junior 5 watts High Quality output. Separate Bass and Treble "Cut" and "Boost" controls. Sensitivity 15 m.v. Twin inputs. High Flux 8in. Loudspeaker "built-in". Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in attractive and durable poltrome, and fitted with carrying handle. Terms: **£8.19.6** Deposit £1 and 9 monthly payments of £1. Send S.A.E. for leaflet. Carr. 10/-.

Senior 10 watts High Fidelity output. Separate Bass and Treble "Cut" and "Boost" controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a high Flux 12in. for Bass notes and a 7 x 4 in. elliptical for Treble. Cabinet is well made and finished as Junior model. Size approx. 18 x 18 x 9in. H.P. Terms: Deposit 34/9 and 9 monthly payments of 34/9. Carr. 10/-.

Send S.A.E. for leaflet of this or 15 watt Super Hi-Fi 15 Watt. All facilities as 10 watt. Cabinet size 20 x 15 x 13in. Terms: Deposit £2.11.6. and nine monthly payments of 51/6. Cash 22 gns. Carr. 12/6. Tremolo units on half page ad.

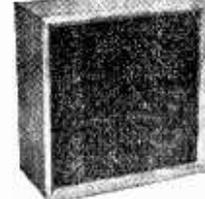12in. 10 WATT HIGH QUALITY LOUD-SPEAKER IN POLISHED WALNUT FINISHED CABINET



Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/- Terms: Deposit 11/3 and 4 monthly payments of 11/3.

12in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS. Size 18 x 18 x 10in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6.

R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL. Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3.19.6.

STANDARD MODEL. As above but for 12in. speakers. Size 20 x 15 x 13in. Especially recommended for Audiotone Loud-speaker systems. £5.19.6. Suitable legs with brass ferrules. 25/- per set of 4.

R.S.C. CORNER CONSOLE CABINETS Polished walnut veneer finish. Pleasing design. Standard Model, size 27 x 18 x 12 in. for 8 or 10 in. speaker. £4.11.9.

SENIOR MODEL. Size 30 x 20 x 12in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.



AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction Standard 10 watt rating £4.19.9. Carr. 5/- Or Senior 15 watt, 7 gns. Carr. 7/6.

AUDIOTRINE EQUIPMENT CABINETS Size 30 x 15 x 16in. Beautifully finished with veneer. Elegant contemporary design. Robust construction. Uncut removable baseboard. Only 12 1/2 gns.



R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. Approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes low consumption types. Complete kit with diagrams, 39/9, or ready to use, 46/6.



VERS normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

TRANSISTOR RADIO CHARGER/ELIMINATOR UNITS. Ready for use, fitted "Snap On" clips. When connected to 200-250v. A.C. mains will charge 9v. battery or replace same. FP3/PP4 Size 19/9. Larger size 29/9.

SENSATIONAL NEW 1962 DESIGNS - BY CONCORD

LOW PRICES ★ PICTORIAL STEP-BY-STEP PLANS ★ EASY AS A.B.C.

THE NEW "LISBON"

TRANSISTOR SET 19/6


This is a pocket 2-stage transistor set not much larger than a matchbox. Excellent clear reception covering all medium waves, works for months off a 6ap 1½ or 3 volt battery costing only 3½d. Easy to build and an excellent introduction to transistor circuitry. Everything can be supplied down to the last nut and bolt incl. **SIMPLE PICTORIAL STEP-BY-STEP PLANS FOR ONLY 19/6**, plus post and packing 1/6. (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.



THE NEW "VOLKSRADIO" ONLY 19/6

TAKE-OVER BID MAKES THIS FANTASTIC OFFER POSSIBLE—the beautifully compact "5-STAR VOLKSRADIO"

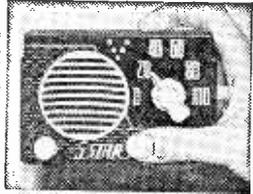measuring 4½ x 2½ x 1½in. receives perfectly—in the Bedroom, Office, Garden—over all medium waves (incl. Luxembourg). Under 1d. hour running cost. ANYONE can assemble it in one or two hours using our simple A.B.C. plan. Complete set of parts ONLY 19/6, plus 2/6 P. & P. (C.O.D. extra). (Parts can be bought separately). Money Back Guarantee.




OUR NEW 4-STAGE "MINUETTE"

Build this newly-re-designed "MINUETTE" 4-STAGE transistor set in very strong ready drilled **ULTRA-MODERN CASE**, size only 8 x 3½ x 1½in. Uses three transistors and diode and **SELF-CONTAINED LOUD SPEAKER**. Very sensitive, ideal for office, bedroom, holidays etc. Months and months of listening off an sd. battery. Can be built **FOR ONLY 39/6**, including **PROPER CASE**, miniature speaker, etc. **SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS** etc. plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.



THE NEW "SAN REMO" 5 STAR 29/6

This All Transistor Speaker Radio—The "San Remo" 5 Star covers all medium waves including "Home", "Light" etc. Reliable and lightweight—Slip easily into the Pocket or Handbag—size only 4½ x 2½ x 1½in. Works for Months off 8d. Battery! Ideal for holidays, Campuz., Bedroom, etc. Anyone can assemble it in an hour or two with our simple **AS-A.B.C. PLAN!** Complete set of parts including miniature speaker—everything—only 29/6, plus 2/6 P. & P. (C.O.D. 2/- extra.) Parts can be bought separately.

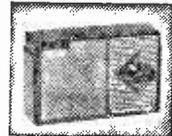

CONCORD ELECTRONICS Dept. 14/6
210, Church Road, Hove, Sussex

Cheques accepted, Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments'k. Complete range of components and values stocked. Regret no C.O.D. abroad. **DEMONSTRATIONS DAILY AT WORKS.**

TRANSISTORS AND DIODES

A set of Transistors comprising 1 OC44, 2 OC45, 1 OC81D, 2 OC81, 37/6 set.

OC73	16/-	OC75	8/-	OC71	25/-	OA71	3/9	Red	
OC77		OC78	12/-	Matched Pcs.	OA81	2/6	Spot	3/6	
OC36	21/6	OC81	8/-	2xOC72	16/-	OA35	3/-		
OC44	6/-	OC84	8/6	Diodes	OA91	3/-	White		
OC45	6/-	OC170	9/6	OA5	OA95	3/6	Spot	5/-	
OC70	6/6	OC171	10/6	OA10	8/-	PXA102	4/-		
OC71	5/-	OC201	31/-	OA70	3/-	GEC S1			
OC72	8/-	OC202	26/-	OA73	3/-	Audio	3/6	XD201	1/-



All components for the Practical Wireless Circuits "Mini-amp", "Regency", "International Short Wave Two", "Mercury Six", "Britannic Two", "Citizen", "Tutor", etc. in stock. Send for detailed price lists.

TRANSISTOR TRANSFORMERS

Osmor Driver Transformer	PW/DT	8/3
Osmor Output Transformer	PW/OT	8/-
Weyrad Driver Transformer	LFDT4	9/6
Repanco TT45	Driver Transformer	5/-
Repanco TT46	Push-pull Output Transformer	45/-
Repanco TT47	Driver Transformer	5/-
Repanco TT49	L.F. Transistor Coupling Transformer	5/-
Ardente DI001 (TI079)	Interstage Transformer	12/-

PRACTICAL WIRELESS POCKET TRANSISTOR SUPERHET. The New Version in a re-designed Cabinet with Carrying Strap. Components Price List: Coil Set (Osc. and 3 I.F.'s), 22/-; Driver Transformer, Type PW/DT, 8/3; Output Transformer, Type PW/OT, 8/-; Ferrite Rod Aerial, Type PW/FR, 8/6; Printed Circuit Board, 7/6; 2 Gang Capacitor, Type "00", 12/6; Volume Control, Type V.C. 1545, 8/-; Switch, 3/6; Hardware (Screws, nuts, washers, spacers, battery clips, cable cradles, cable studs, cable strapping), 4/-; Transistors Type YC (Set of 6), Xtal Diode, Type GD9, 43/-; Speaker: Case, 12/6; Capacitors, 15/-; Resistors, 5/-; Trimmers, Type MT31/4A (3 required), 3/9. Constructional Leaflet and "Blow-up" Circuit Diagram. **PRICE FOR THE COMPLETE KIT £7.19.6.**

AUTOMATIC RECORD CHANGERS

BSR Monarch UA14	£6.19.6
Collaro C60 Studio	£7.19.6
Gerrard Autostim	£8.19.6

RECORD PLAYER CASES
Baseboard cut suitable for a BSR UA14, available in red, turquoise, grey, and black/yellow, 63/- each. Amplifier and Loudspeaker to suit above, 65/-.

RECORDING TAPE

5in. reel, 600ft. Acetate	13/6
5in. reel, 900ft. P.V.C.	21/-
7in. reel, 1200ft. Acetate	23/-
7in. reel, 1800ft. P.V.C.,	37/6

MULTI-RANGE TEST METERS

Pifco All-in-One Radio Meter	32/6
Test Master Model 200H.	20,000 ohms per volt, £6.19.6
Caby Model A10	£4.17.6
Caby Model B20	£6.10.0
Taylor Model 127 A	£10.10.0

MICROPHONES


Acos Mic. 39/1; Stick Type 32/6. Table Stand for above, 7/6. Floor Stand Adaptor, 12/6. TSL Type M1 Dual Impedance Microphone with High (50,000 ohms) or Low (200 ohms), Matching, 84/-; TSL Stick Microphone MX3, 35/-; Acos Mic. 40, 19/6; Acos Mic. 45, 29/6; Microphone Model BM3, 45/-; Table Stand to suit above, 12/6.

Our new 1962/63 48-page catalogue profusely illustrated is now available. Please send 1/- in stamps for your copy. Trade Catalogue also available for which please attach your Business Letter Heading.

ALPHA RADIO SUPPLY CO. 103 LEEDS TERRACE, WINTOUN STREET, LEEDS 7

FREE THIS BOOK WILL
INTEREST YOU!

LEARNING
the
PRACTICAL
WAY

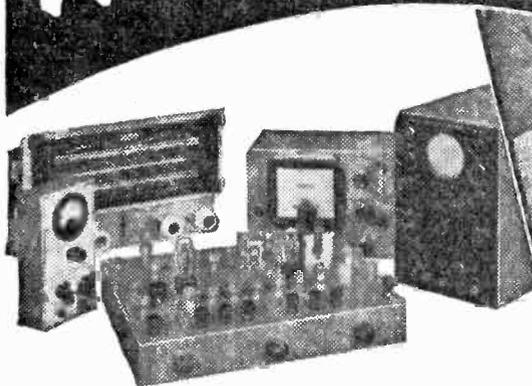

**A NEW-PRACTICAL WAY
of UNDERSTANDING**

Radio • Television • Electronics

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

FOR ... Your Career ... Your Own Business ... An Absorbing Hobby

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details.—

RADIOSTRUCTOR
LEADS THE WORLD
IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G82)
READING, BERKS.

Please send brochure, without obligation, to:

★ Name _____

Address _____

9 62

★ **BLOCK CAPITALS PLEASE**
(We do not employ representatives)

Brand new, individually checked and guaranteed

VALVES

AL60 6/-	EB34 1/6	EYS1 8/-	PL36 10/6	VR150/30	6AK7 6/-	6V6GT 5/-	80 5/6	8020 10/-
ARB 5/-	EB91 3/6	EY86 8/-	PL81 9/-	VT4C 6/-	6AM5 5/-	6X4 5/-	81 9/-	9001 3/-
ARDD5 2/-	EB33 7/6	EY91 3/6	PL82 8/-	VU39 6/-	6AM6 4/-	6X5GT 5/-	82 8/-	9002 5/6
AR3 3/6	EZ41 7/6	EZ40 7/6	PL83 10/-	VU31 7/-	6AQ5 7/-	6Y6G 6/-	83V 9/-	9003 6/-
AR4 3/6	EB30 5/-	EZ41 6/9	PT15 10/-	W31 7/-	6AT6 5/-	6Z4 5/6	84 8/-	9004 2/6
AR12 3/-	EC52 8/-	EZ80 6/9	PT25H 7/6	X66 8/-	6B7 5/6	7B7 7/6	85A1 9/-	9006 2/6
AR21 5/6	EC70 10/-	EZ81 6/9	PT44 19/-	Y63 5/-	6BBG 2/6	7C6 7/6	85A3 15/-	
AR24 3/6	EC90 20/-	FW4/500	PX25 9/-	Y65 4/-	6BA6 5/6	7C7 6/6	89 6/-	Cathode Ray Tubes
AR34 4/-	EC91 3/-		PY32 12/-	Y66 8/-	6C4 2/6	7H7 7/3	210VPT 2/6	ACR1 15/-
ARTH2 7/-	ECC81 5/6	G120/1B 9/-	PY80 6/9	Z31 6/-	6CSGT 6/-	7Q7 7/-	7-pin 2/6	ACR11 15/-
ATP4 2/9	ECC82 6/6	GL450 10/-	PY81 7/-	IA3 3/-	6C6G 3/6	7V7 5/-	250TH 2/6	CV995 15/-
AU7 5/6	ECC83 7/-	GL464A 10/-	PY82 8/-	IA5GT 5/-	6C8B 5/-	7Y4 6/-	350B 8/-	CV1596
AU1 5/-	ECC84 7/6	GU20/21	PY83 7/3	IA5GT 5/-	6D6 4/-	7Z4 4/6	393A 15/-	(09J) 55/-
AU4 5/-	ECC85 8/-		PZ135 9/-	IC5GT 7/6	6F5 5/3	8D2 2/6	705A 15/-	E4103/B4
AW3 4/-	ECC91 4/-	GZ32 9/-	QP21 6/-	ID8GT 6/-	6F6G 4/-	9D2 3/-	715B 6/6	
AZ31 8/-	ECC82 8/6	H63 7/-	QP25 5/3	IE7G 7/6	6F7 5/-	12A6 2/6	717A 8/6	3FP7 25/-
BS4A 5/6	ECH42 7/6	HL23 6/-	QS75/20 6/9	IG6GT 6/-	6F5GT 5/9	12AH7 5/-	801 6/-	5BP1 35/-
BT45 15/-	ECH81 7/9	HL23DD 8/-	OS95/10 6/9	IL4 3/6	6F12 4/6	12AT7 5/6	803 22/6	5CP1 42/6
BT9B 20/-	ECL80 8/-	HVR2 12/6	QV04/7 7/6	IL5 5/-	6F13 5/-	12AU6 6/6	804 55/-	5FP7 45/-
BT83 22/6	ECL82 9/-	KRN2A 19/-	R3 8/-	IR5 5/-	6F17 5/-	12AU7 6/-	805 30/-	5FP7A 25/-
CV54 5/-	EF22 7/6	KT32 8/-	R10 7/6	IS4 5/-	6G5G 2/6	12C8 3/-	807 AMER 8/-	7BP7 40/-
CV264 20/-	EF36 3/6	KT33C 4/-	RL21 25/-	IS5 5/9	6H6M 1/6	12E1 22/6	807BR 6/-	12DP7 60/-
CV4014 8/-	EF39 4/-	KT44 6/3	RK34 2/6	IA4 5/-	6J5 3/6	12H6 2/-	808 8/-	VCRX258
CV4015 7/-	EF50 2/6	KT63 4/-	RL23 10/-	IA5 5/-	6J5G 3/-	12K7GT 4/6	810 80/-	(with scanning coil) 45/-
CV4025 10/-	EF54 3/3	KT76 10/-	RS235 10/-	IA6 6/-	6J6 3/6	12J5GT 3/6	815 40/-	VCR138 30/-
CV4046 40/-	EF55 5/-	KTW62 7/6	SP13 4/6	IA7 5/-	6K7GT 4/9	12Q7GT 4/6	816 30/-	VCR139A 35/-
CY31 7/6	EF70 4/-	KTW63 6/6	SP41 2/6	IA8 5/-	6K8GT 5/9	12S7 4/-	832 15/-	Photo Tubes
D41 3/3	EF73 6/-	KTZ41 6/-	SP61 2/-	IB1 5/-	6K8GT 8/3	12SH7 3/-	843 7/4	CMG8 9/-
D77 4/3	EF80 5/6	MH4 3/6	SU2150A	IB2 5/-	6K8M 8/6	12S17 5/-	866 10/-	CS16 12/6
DA30 12/6	EF85 6/6	MH41 5/-	T41 7/6	IB3 5/-	6L5G 6/-	12SK7 3/6	872 20/-	Special Valves
DAF70 35/-	EF86 7/6	ML4 4/-	TP25 15/-	IB4 5/-	6L6 9/-	12SL7 5/9	930 8/-	
DAF91 6/-	EF89 7/9	ML6 6/-	TT11 3/-	IB5 5/-	6L6G 6/6	12SN7 5/9	954 8/-	2J31 45/-
DAF96 7/6	EF91 3/6	ML6/PEN 6/-	TT15 25/-	IB6 6/-	6L7G 4/6	12SR7 6/-	955 2/6	3A/1481 45/-
DD41 4/-	EF92 3/-	NT2 9/-	TZ20 16/-	IB7 5/-	6L84 4/6	14S7 1/6	956 2/6	3J192/E £35
DE75 15/-	EF95 5/-	OB3 7/-	UI12 14	IB8 6/6	6M7G 5/9	15D2 6/-	957 5/-	£37.10
DET19 3/6	EL92 3/9	OC3 5/-	UI17 5/-	IB8 8/-	6N7GT 6/-	20A2 17/6	958A 5/-	4J31 £35
DET20 2/-	EL33 8/-	OD3 6/-	UI7 5/-	IB9 5/-	6O7G 6/-	21B6 9/-	1616 3/-	4J50 £35
DF39 4/-	EL35 6/-	OZ4 5/-	UI8 8/-	IB10 5/-	6P7 6/-	25L6GT 7/9	1619 5/-	5D21 £3
DF72 7/6	EL41 8/-	PCC84 7/-	UI28 6/6	IB11 5/-	6SC7G 4/6	30L6GT 8/-	1625 6/-	723A/B 50/-
DF91 4/-	EL42 8/-	PCC85 8/-	UI32 5/-	IB12 5/-	6SC7GT 5/-	35L6GT 8/-	1626 4/6	725A 30/-
DF96 8/-	EL84 7/-	PCF80 7/-	UC42 7/6	IB13 5/-	6SG7 5/-	35T 17/6	1629 4/6	726A 27/6
DK96 7/3	EL91 4/6	PCF82 8/-	UB80 8/6	IB14 5/-	6SH7 3/-	35Z4GT 7/-	4043C 13/6	ACT6 160/-
DL92 6/-	EM80 8/-	PCL82 8/6	UB11 5/-	IB15 5/-	6S17GT 5/9	37 4/-	4063 8/-	CV193 30/-
DL94 6/-	EM84 9/-	PCL83 11/-	UB12 5/-	IB16 5/-	6S17 6/6	38 4/-	6064 10/-	CV980 3/-
DL96 8/-	EN31 15/-	PCL84 9/-	UB18 7/6	IB17 5/-	6SK7 5/3	38 4/-	6065 8/-	ESU77 200/-
EA50 1/6	EP37A 7/6	PEN45 4/6	UB24 7/6	IB18 5/-	6SL7GT 6/6	59 5/6	6120 4/-	KR6/3 £4
EABC80 7/3	EP71 6/6	PEN46 5/-	UB29 5/6	IB19 5/-	6SN7GT 4/6	65 7/6	6120 4/-	LS7B 30/-
EAC91 3/6	EP72 5/-	PEN65 6/6	UY41 6/-	IB20 5/-	6SQ7 6/-	76 5/-	7193 1/9	WL47A 15/-
EAC91W7/6	ESU208 6/-	PEN220A 3/-	UY85 6/6	IB21 5/-	6S7 6/-	77 5/-	7475 3/-	
			VP23 3/-	IB22 5/-	6S7GT 4/6	77 5/-	8013A 25/-	
			VP41 5/6	IB23 5/-	6S7 6/-	78 7/-		
			VR99 8/-	IB24 5/-	6V6G 4/6			
			VR105/305/6	IB25 5/-				

AND MANY OTHERS IN STOCK, INCLUDING CATHODE RAY TUBES AND SPECIAL VALVES. All U.K. Orders below 10/-, 1/- P. & P. 2/6 over 10/-. Orders over £3, P. & P. free. C.O.D. 2/6 extra. Overseas Postage extra at costs.

BRAND NEW ORIGINAL SPARE PARTS FOR AR88 RECEIVERS.

Please write your requirements. **MARCONI RECEIVER TYPE CR 100/2** tested and aligned £32.10.0 Carr. £1. **TELEPHONE HANDSET.** Standard G.P.O. type. New 12/- P. & P. 2/-.

CONNECTIONS FOR TCS RECEIVER, TRANSMITTER AND REMOTE CONTROL with original plugs on both ends. New £1.17.6. P. & P. 2/6.

SPECIALLY BUILT POWER PACK for TCS receivers, 230 volts A.C. mains, including 6X5GT valve, £31.10.0 Carr. 5/-.

R.109 RECEIVER. Covering 2-8 Mc/s. 6 v. D.C. with set of spare valves and carrier. Brand new in original packing case. £6.18.0 including delivery in U.K.

R.109A RECEIVER. Covering 2-12 Mc/s. £7.18.0.

"CONNECT AND FORGET—CANNOT OVERCHARGE"—"ESSTRON" AUTOMATIC BATTERY CHARGER. Charging rate 4 amps. The charging rate automatically adjusts itself to the charge in the battery. Automatic current and voltage control. Patented application of magnetic amplification to battery charging. Indicator lights show battery fully charged, receiving charge, incorrectly connected or faulty cells. Mains voltage 200/250 v. Built for 6 or 12 v. batteries. Measurements 7 x 5 x 5 1/2 in. Weight 8 1/2 lbs. Price £6.19.6. P. & P. 3/6.

TANNOY LOUDSPEAKERS, 7.5Ω imp., in wooden case. New 19/-, Carr. 5/-.

HIGH RESISTANCE HEADPHONES (CHR), 12/6. P. & P. 2/-.

LOW RESISTANCE HEADPHONES (D.L.R.) 8/-, P. & P. 2/-.

TELESCOPIC MAST. 34ft. Consisting of 6 sections of steel tubing of such internal and external dia. that the smaller sections may be collapsed with the largest section. Immediate erection. Absolutely complete with brackets, guys, pegs, spikes etc. £12.10.0. Carr. 18/-.

As above but 20ft., £7.10.0. Carr. 18/-.

MULTI-TESTER. 0.6-30-120-600-1,200v. A.C./D.C. 0-120 μA, 0-300 mA, A.C./D.C. 0-30,000 Ω, 0-3 MΩ, 10,000 Ω/v. 3 1/2 x 4 1/2 x 1 in. Very clear, large scale. Price £4.10.0. P. & P. 3/-.

COMPLETE SET OF STRONG AERIAL RODS (American). Screw-in type MP49, 50, 51, 52, 53, total length 15ft. 10in. Top dia. 0.185in. Bottom dia. 0.615in., together with matched aerial base. MP37 with ceramic insulator. Ideal for car or roof insulation £2.10.0. Post free.

53 TRANSMITTER SPARES. Full range. Price list on application.

DYNAMOTORS DM 21 FOR BC 312 RECEIVER. Brand New, £2.10.0. P. & P. 4/-.

P.C. RADIO LTD.
170, GOLDHAWK RD., W.12
Shepherds Bush 946

AERIALS 11ft. long. 2ft. long when folded, 15/-, P. & P. 2/-.

CRYSTAL CALIBRATORS No. 10. Frequency range 1.5 to 10 Mc/s. Together with working instructions, lead and spare valves. £4.10.0. P. & P. 3/-.

COMPLETE V.F.O. UNIT from TX53. Freq. range in 4 switched bands from 1.2-17.5 Mc/s. Two V.T. 501s. as oscillator and buffer, 807 as driver, two 5130s as voltage stabilizers. Output sufficient to drive two 813s in parallel. Slow motion drive directly calibrated in Mc/s. Provision for crystal control, metering of buffer and driver stage. Power requirements 400 v. and 6.3 v. D.C. Can also be used as low power transmitter. In excellent condition with valves and circuit diagram. £5. P. & P. 15/-.


R.209 RECEPTION SET. A 10-valve high-grade Superhet Receiver with facilities for receiving R/T (A.M. or F.M.) and C.W. frequency 1 Mc/s-20 Mc/s. Hermetically sealed. Built on miniature power incorporating its own vibrator power supply unit driven by a 6 v. battery (2 point connector included). The set provides for reception from rod, open-wire or dipole aerial with built-in loudspeaker or phone output. Dimensions: Length 12in., width 8in., depth 9in. Weight 23lb. In as new, tested and guaranteed condition, £23.10.0, including special headphone and supply leads. Carr. £1.

CARBON INSET MICROPHONE, G.P.O. type, 2/6. P. & P. 1/6.

—NOT DODGEY

YOU WILL BE TOP OF YOUR GIRL'S HIT PARADE WHEN YOU PACK A ...

PARISIENNE!

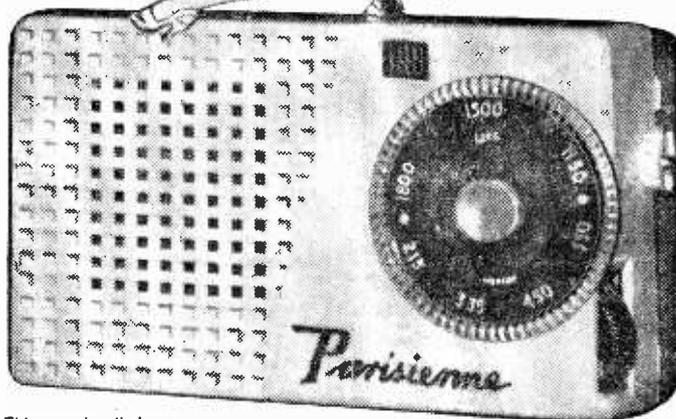

This amazing little set **HAS TO BE HEARD TO BE BELIEVED**
We will supply **ALL** components at a total cost of only

YOU CAN'T GO WRONG!

Free advice bureau, second-to-none service and all your components top quality and fully guaranteed.

Transistors: OC76 4/6, OC71 5/-, Japanese Audio 2/6, G.E.C. 51 Black Audio 3/-, S2, Blue driver 3/-, SB305 9/-, OC170 10/-, OC77 12/6, 2N398 10/-, SB240 7/6, OC42 3/6, XA701 6/-, GET 103 6/-, OA10 6/-, OA2 203 7/6, OA5 diode 5/-, OA2 202 7/6, Latest miniature diode OA90 2/11, XC141 power output as OC16, only 10/-, XA116 6/-, general purpose diodes 1/-, P.P. 4d. on each transistor. All these are new.

OC28 19/6, OC35 19/6, OCP71 19/6, OC200 12/6, P.P. 6d. OC72 5/-, P.P. 3d. OC44 5/6. OA47 V.H.F. or h/speed switching diode 3/6. OA86 4/-, 2N456 19/6, OC28 and OC29 19/6, CG12E diodes 4/-, SB345 6/6, SB346 7/-.

12-way Tag Board, with resistors and condensers as follows, all 1/2in. watt transistor type: two 10 meg., two 0.01, one 3.9 M., 5.6 M, 3.3 M, 1.2 M, 2.2 M, 470 Ω , 470K. All for 2/-, P.P. 3d.

6000 Ω P.O. Relays. Platinum contacts, 3 way normal open, few only at 12/6. P.P. 9d.

£3.19.6 !!!

SWINGIN' !!!

ROPE IN LUXEMBOURG!

WITH THE FANTASTIC

PARISIENNE!!

A SUPERB POCKET TRANSISTOR

Dozens of continentals come rolling in! **LUXEMBOURG ROMPS IN LIKE THE LIGHT!!** Fully tunable over long and medium waves; the complete novice and experienced constructor alike will delight in building it. Already excellent reports have reached us from all over Europe and the U.K.! You will be **ASTOUNDED** by its tremendous volume and truly remarkable performance. Build-up presents **NO PROBLEMS!** **EVEN** to the **COMPLETE NOVICE!**

Components include a built-in ferrite rod aerial, high quality 3in. moving coil speaker, printed circuit, elegant style cabinet, etc.

A fully illustrated booklet, complete with step-by-step assembly instructions and all other data, comes to you for only 2/9 extra; PP4 press-stud type battery 2/3; post and packing on the lot 2/6.

SO GET WITH IT !!

and build yourself this superb little set **NOW!**
PUT THE WORLD IN YOUR POCKET!

4 Transistor Amplifier, printed circuit with circuit 2/-, P.P. 3d. Parts available, but not plans.

Car Aerials. Adjustable angle telescopic. 12in. closed, 36in. extended with Co-ax plug. 17/6. Post paid.

Window Fixing, type for portable, 17/6, post paid.

Miniature Mains Soldering Irons. Designed for transistor kit work, 30 watt, specially light weight, handle unscrews to cover bit so that iron can be carried even when hot, supplied with handsome pocket case in grey leather cloth P.V.C. Spares always available—**ONLY 17/6.** Post paid.

WANTED

Valves, transistors, miniature components, all types of radio equipment, any quantity, but must be new, cash paid by return.


TRADE ENQUIRIES WELCOMED ON ANY LINES



WOLVERHAMPTON RADIO & TV SUPPLIES, 43 Birmingham Rd, Wolverhampton

Terms:—C.W.O. to avoid delay. All orders mailed by return, subject to stocks surviving the onslaught!
All components can, of course, be supplied individually. Fuller details and/or prices by request, write (S.A.E.) or call
Tel.: Wolverhampton 20315

ARMSTRONG AF208 AM/FM RADIOGRAM CHASSIS

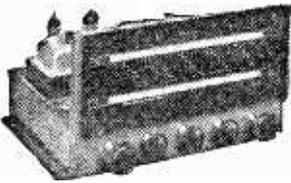

★ Full VHF Band (87-108 Mc/s and Medium Band, 187-570M) ★ 7 Valves ★ 5 Watts Output ★ 15db Negative Feedback ★ Separate wide range Bass and Treble Controls ★ 2 Compensated Pick-up Inputs ★ Frequency Response 30-22,000 c.d.s. ±2db ★ Tape Record and Playback Facilities ★ Continental Reception of Good Programme Value ★ For 3, 7½ and 15 ohm Speakers. Send S.A.E. for leaflet.

PRICE £22.18.0 Carr. Free

LATEST "EMI" 4 SPEED SINGLE RECORD PLAYER

Acos Hi-Fi Pick-up for L.P. and/or 78, 10 and 12-in. records. Silent motor, heavy turntable, auto stop. Complete on Base-plate.

Special offer £6.5.0 post free.

SINGLE-PLAYER BARGAIN

Ready-built, complete with BSR TU9 4-speed gram pick-up unit. Handsome portable case. 3-watt amplifier with 2 valves and speaker. List price £12.12.0. OUR PRICE £8.19.6. Fully guaranteed in manufacturer's sealed cartons.

SUMMER SALE PRICES

New Boxed VALVES 90-day Guarantee

024	5/-	6K7G	5/-	EB9C80	8/-	PCL82	10/-
1R5	6/-	6K8G	5/-	EB91	4/-	PCL84	10/-
185	6/-	6L8G	8/-	EB041	8/-	PL81	10/-
1T4	3/-	6N7M	5/-	EB081	8/-	PL83	8/-
2X3	2/-	6Q7G	6/-	EBF80	6/-	PY80	8/-
384	7/-	6SN7	6/-	ECH42	8/-	PY81	8/-
3V4	7/-	6V8G	6/-	ECH81	8/-	PY82	7/-
3Q5	7/-	6X4	5/-	EP85	6/-	PY83	8/-
5U4	6/-	6X5	6/-	EP89	8/-	QP25	7/-
5Y3	6/-	12AT7	6/-	EL32	5/-	SP11	3/-
5Z4	9/-	12AU7	6/-	EL84	7/-	SP11	8/-
6AC7	4/-	12AX7	7/-	EY51	8/-	U22	7/-
6AM6	5/-	12BH7	7/-	EY86	9/-	UB041	8/-
6A78	6/-	12K7	5/-	EZ40	7/-	UB081	9/-
6BA9	7/-	12K5	14/-	EZ50	7/-	UBF80	9/-
6BP9	5/-	12Q7	5/-	EZ81	7/-	UC181	9/-
6BW8	7/-	25Y5G	9/-	LL148	11/-	UC182	10/-
6C4	5/-	35L6	9/-	HVC8010	10/-	UC183	12/-
6D6	5/-	35Z4	5/-	HVC28A	5/-	UF89	9/-
6G4	4/-	80T	5/-	KT39C	8/-	UL41	9/-
6H6	3/-	85A	2/-	K170	3/-	UY41	7/-
6J5	5/-	DAF96	8/-	MU14	7/-	UY85	7/-
6J6	5/-	DF96	8/-	PCC81	8/-	UU9	7/-
6V7G	6/-	DK36	8/-	PCF80	8/-	VR150	7/-
6K6	5/-	DL96	8/-	PCF82	8/-	W81	6/-

SETS OF VALVES

DK96, DF96, DAF96, DL96 29/6 set.
1R5, 1T4, 185, 384 or 3V4 19/6 set.


NEW ELECTROLYTICS TUBULAR TUBULAR FAMOUS MARKS CAN TYPES

1/350V	2/-	50/350V	5/8	16/450V	5/-
2/350V	2/3	100/25V	3/-	32/350V	4/6
4/450V	2/3	350/25V	3/-	100/270V	5/6
8/450V	2/3	350/25V	3/-	2,000/8V	5/6
16/450V	2/3	500/12V	3/-	5,000/6V	5/6
32/450V	3/8	8+5/450V	3/8	32+32/350V	5/6
25/25V	1/8	8+16/450V	3/8	32+32+32/350V	7/6
50/25V	2/-	16+16/450V	4/8	50+50/350V	7/6
50/50V	2/-	32+32/350V	4/8	64+120/350V	11/6
				100+200/275V	12/6

COMPLETE RADIO £4.19.6 post free



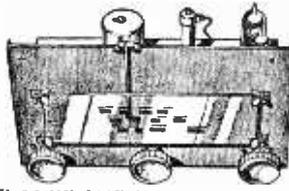4 Mullard valves, 6in. speaker, frame aerial. 4 pre-set stations. 1 long, 3 med. wave. Superhet Circuit. BRAND NEW. Size 9 x 6 x 5.5 in. High. Tested by us ready for use. 200/250 v. A.C.-D.C. Mains.



DE LUXE MODEL as above but with illuminated dial. Fully tunable over Medium and Long Wave. 5 inch speaker. Bargain £5.19.6, post free. Tested by us before despatch. 12-month Guarantee.

MAINS TRANSFORMERS 200/250 v. A.C.

Postage 2/- each transformer.
STANDARD, 250-0-250, 80 mA, 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 3 v. 2 a. or 4 v. 2 a. 22/6, ditto, 350-0-350 .. 29/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 10/6
MIDGET, 220 v. 45 mA, 6.3 v. 2 a. .. 15/6
SMALL, 220-0-220, 50 mA, 6.3 v. 2 a. 17/6
STD., 250-0-250, 65 mA, 6.3 v. 3.5 a. .. 17/6
HEATER TRANS. 6.3 v. 1 1/2 amp. .. 7/6
Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. .. 8/6
Ditto, sec. 6.3 v. 3 amp .. 10/6
GENERAL PURPOSE LOW VOLTAGE, 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. .. 22/6
AUTO TRANSFORMERS, 150 w. .. 22/6
0, 120, 200, 230, 250 v., 500 w. .. 82/6
MULLARD 10" Mains transformer 30/-
PARMEKO MAINS TRANSFORMER. Made for special contract, the ratings can safely be doubled. Guaranteed 2 years. Primary 0-110-210-200-250 v. H.T. 300-0-300 v. 50 mA. L.T. 6.3 v. 1.8 amp. Size 4 x 3 1/2 in. Weight 6lb. Post 2/6. .. 17/6
MAINS POWER PACK. Size 3 1/2 x 4 1/2 x 4 in. with mains transformer, metal rectifier and condensers to provide smoothed H.T. output 220 v. 45 mA. D.C., L.T. 6.3 v. 2 a. Centre tapped. All ready built on a strong metal chassis. Brand New. Bargain. Post 2/6 .. 29/6

O.P. TRANSFORMERS. Heavy Duty 50 mA. 4/6. Multitap, push-pull, 7/6. Ditto, 10 w. 15/8. Minutaire, 384m etc. 5/9. L.F. CHOKES 15/10H, 60/65 mA. 5/-; 10 L. 85 mA. 10/8; 10 H. 150 mA. 14/-
FULL WAVE BRIDGE SELENIUM RECTIFIER. 2, 6 or 12 v. 1 1/2 amp. 8/9; 2 a. 11/3; 3 a. 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps. 15/6. 2 amps. 17/6; 4 amps. 22/6. Circuit included.
4 AMP CAR BATTERY CHARGER with amp meter Leads, Fuse Case, etc., for 6 v. or 12 v., 6/9

BOOKS list S.A.E.

40 Circuits for Germanium Diodes 3/-
"W.W." Radio Valve Data, 6/-
High Fidelity Speaker Enclosure, 5/-
Valve and TV Tube Equivalents, 9/6
TV Fault Finding, 5/-
Quality Amplifiers, 4/8
Radio Valve Guide. Books 1, 2, 3 or 4, 5/- each.
Transistor Superhet Receivers, 7/6
Practical Radio Inside Out, 3/6
Master Colour Code Chart, 1/6
Transistor Controlled Models, 7/6.

C.R.T. BOOSTER TRANSFORMERS

for heater cathode short circuit, C.R. tubes with falling emission. Full instructions supplied.
Type A optional 25% and 50% boost. 2v. or 4v. or 6.3v. or 10.8v. or 13.3v. Mains input. PRICE 10/6.

LOUDSPEAKER P.M. 3 OHM. 24, 3, 4in. 19/6. 5in. Rola, 17/8; 5in. Plessey, 19/8; 7in. x 4in. Rola, 18/1; 6in. Rola, 18/8; 10 x 6in. 27/8; 10in. Rola, 30/-; 4in. Tweeter, 25/-; 12in. R.A. 30/-; 13 1/2 x 5in. Double Cone E.M. 1. 45/-.

STENTORIAN HF1012, 10in. 3 to 15 ohms, 10 w., 85/- 3 ohm, 7 x 4in. 25/-; 3in., 19/6.

BAKER SELHURST LOUSPEAKERS

Details S.A.E.

12in. Baker 15w. Stalwart 3 or 15 ohms, 45-13,000 c.p.s. .. 90/-
12in. Baker Stalwart, Foam Suspension, 15 ohms, 40-13,500 c.p.s. .. 96
12in. Stereo, Foam Suspension, 12w., 35-16,000 c.p.s. .. 86.17.8
12in. Baker Ultra Twelve, 20 c.p.s. to 25 kc/a, £17.10
15in. Auditorium, 35 w., Base: 20 c.p.s. to 12k/cs, £18



TWIN GANG TUNING CONDENSERS. 365 pF miniature lin. x 1 1/2 in. 1 1/2 in., 10/-; 500pF Standard with trimmers, 9/-; midget, 7/8; with trimmers, 9/-; 500 pf slow motion tuning 9/-
SMALL 3 gang 500 pf, 17/-
SINGLE 25 pf, 50 pf, 75 pf, 100 pf, 150 pf, 160 pf, 5/6. Solid dielectric 100, 300, 500 pf, 3/8.

CONDENSERS. New stock. 0.001 mfd. 7 kv: T.C.C., 5/8; Ditto, 20 kv, 9/8; 0.1 mfd., 7 kv, 9/8. Tubular 500 v. 0.001 to 0.05 mfd., 9d., 0.1, 1/-; 0.25, 1/8. 0.5/500 v., 1/8. 0.1/350 v., 9d. 0.1/2,000 v. 0.1/1,000 v., 1/8; 0.1 mid., 2,000 volts, 3/8. CERAMIC CONDS. 500 v. 0.3 pf to 0.01 mfd., 9d. SILVER MICA CONDENSERS. 10% 5 pf to 300 pf, 9d.; 600 pf to 3,000 pf, 1/- Close tolerance (± 1 pf) 2.2 pf to 47 pf, 1/-; Ditto 1% 50 pf to 815 pf, 1/-; 1,000 pf to 3,000 pf, 1/9.

465 kc/s SIGNAL GENERATOR Price 15/- Uses B.F.O. Unit, ZA 30038 Ready made with valve IS5. POCKET METER 2 1/2 x 4 1/2 in. Slight modifications required, full instructions supplied. Battery 8/6 extra 69V 1 1/2V. Details S.A.E.

WAVECHANGE SWITCHES

8 p. 4-way 2 water long spindle .. 8/6
2 p. 2-way, or 2 p. 6-way long spindle or 4 p. 2-way or 4 p. 3-way long spindle .. 3/6
3 p. 4-way, or 1 p. 12-way long spindle .. 3/8
Wavechange "MAKITS", Wafers available: 1 p. 12 way, 2 p. 6 way, 3 p. 4 way, 4 p. 3 way, 6 p. 2 way, 1 water switch 8/6; 2 water switch, 12/6; 3 water switch, 16/-; additional wafers up to 12, 3/6 each extra.
Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.t.d., 4/-; Ex. Govt. s.p.d.t.t., 1/-.

CRYSTAL MIKE INSERT, 6/-

Precision engineered. 1 1/2 in. dia. x 1 in.

ACOS 39-1 DE LUXE STICK MIKE 35/-

QUALITY STICK MIKE.....25/-

Valveholders, Pax. int. oct., 4d. EA50, 6d. B12A, CRT, 1/3, (Engl) and Amer. 4, 5 G and 1 1/2 in. MOULDED Mazda and B.T. oct., 6d.; B7G, B8A, B9C, B9A, 8d. B7G with can, 1/6. B9A with can, 1/9. Ceramic EF50, B7G, B9A, int. oct., 1/-; B7C, B9A cans, 1/- each.

Quality 2-Stage Hi-Fi AMPLIFIER A.C. only, 200-250 v. Valves ECL86 and EZ80, 3 watt quality output. Mullard tone circuits, bass boost, treble and volume control. Separate engraved Perspex front-panel with de-luxe finish. Heavy duty output transformer 3 ohm. Shrouded mains transformer. Stove enamelled chassis size 6in. x 5in. x 3in. Bargain: Price £4.10.0. Circuit supplied.

THE ORIGINAL RADIO COMPONENT

Our written guarantee with every purchase. NEW COMPONENT LIST 1/-

Bus 133 or 68 Pass door S.R. Station Selhurst

Volume Controls 80 OHM COAX
 Linear or Log Tracks. Cable Semi-adj spaced 4in. Long spindles. Midget 6d.yd. 5 K ohms to 2 Meg. L/S, 3/-; D.P., 4/6 stereo L/S 10/6; DP 14/8

TELESCOPIC CHROME AERIALS 13in. extending to 43in. 8/6 ea. Coax Adaptor Plug, 1/6 extra. TRIPLEXERS Bands I, II, III 12/6
COAX PLUG 1/- LEAD SOCKET.. 2/-
PANEL SOCKETS 1/- OUTLET BOXES 4/6
DA..ANCED TWIN FEEDER yd. 8d. 80 or 300 ohms. DITTO SCREENED per yd. 1/6. 80 ohms only. WIRE-WOUND POTS, 3 WATT. Pre-set Min. TV Types. All values 10 ohms to 25 K., 3/- ea. 30 K., 50 K., 4/-; (Carbon 30 K., to 2 meg., 3/-). WIRE-WOUND 4 WATT Pots. Long spindle. Values, 50 ohms to 50 K., 6/6; 100 K., 7/6. PHILIPS TRIMMERS, 0-10 pF, 3-30 pF, 1/-; TRIMMERS, Ceramic, 30, 50, 70 pF 9d.; 100 pF, 150 pF, 1/3; 250 pF, 1/6; 500 pF, 750 pF, 1/6. T.V. etc. TRIMMER, 1000 pF, with knob, 2/-. RESISTORS. Preferred values. 10 ohms to 10 meg., 1 w., 4d.; 1 w., 4d.; 1 w., 8d.; 1 w., 8d.; 2 w., 1/-. HIGH STABILITY. 1 w., 1/6; 2/-; Preferred values. 10 Ω to 10 meg. Ditto 5%, 10 Ω to 22 meg., 9d.
 5 watt { WIRE-WOUND RESISTORS } 1/6
 10 watt { 10 ohms—10,000 ohms } 3/8
 15 watt { } 2/-
 12.5K to 50K 10 w 3/-

AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE
 Double Play 7in. reel, 2,400ft. 60/- Spare Plastic Reels 3in. 1/6
 Long Play 7in. reel, 1,800ft. 35/- 5in. reel, 1,200ft. 23/6 5in. reel, 900ft. 13/6
 Standard 7in. reel, 1,200ft. 25/- 5in. 2/- 5in. reel, 600ft. 16/- 7in. 2/6
 "Instant" Bulk Tape Eraser and Head Defuzzer, 200/250 v. A.C. 27/6. Leadet with full details. S.A.E.

CRYSTAL SET BOOKLET, 1/-
CRYSTAL DIODE G.E.C., 2/-; GEX34, 4/-; OA81, 3/-
HIGH RESISTANCE PHONES, 4,000 ohms, 15/-
SWITCH CLEANER. Fluid squirt spout, 4/6 tin.

HIGH GAIN TV PRE-AMPLIFIERS
BAND I AND I B.B.C.
 Tunable channels 1 to 5. Gain 18db. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCC84 valves if preferred.)
BAND III I.T.A.—Same prices.
 Tunable channels 8 to 13. Gain 17 db.

Paxolin Panels, 10 x 8in., 2/-
Miniature Contact Cooled Rectifiers, 250V 50mA, 7/6; 250V 80mA, 8/6; 250V 85mA, 9/6; 200mA 21/-; 300mA 27/6.
T.V. etc. Silicon Sub-Min. Rectifier, 125V, 300mA, 6/6; 250V, 300mA, 14/6.
Selenium Rect., 300V 65mA, 5/-
Coils Wearing "T" type, 3/- each.
Osmor Midget "Q" type, adj. dust core, from 4/- each. All ranges.
Teletron D.W.R. L. and Med. T.R. with reactions, 4/-
Med wave D.R., 3/6.
Ferrite Aerials, M., 8/6; M. and L., 12/6.
Osmor Ferrite Rod Aerials, L. and M. (or transistor circuits, 10/- each.
Ferrite Rods, 8 x 4in., 3/-; 8 x 5/16in., 3/-
H.F. Chokes, 2/6.
Osmor QCT, 6/6.
T.R.F. Coils, 2/6F 7/- pair; HAX, 3/-
Repanco DRR2, 4/-; DTXL, 2/6.
Radio Screwdriver, 5in., 6d.
Neon Mains Tester Screwdriver, 5/-
Solder Radiograde, 4d. yd., 1lb. 5/-
Black Crackle Paint. Air drying, 3/- tin.

Aluminium Chassis, 18 s.w.g. Plain un drilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in. 4/6; 3 x 7in., 5/6; 11 x 7in., 6/6; 13 x 8in., 8/6; 14 x 11in., 10/6; 15 x 4in., 12/6; 18 x 16 x 3in., 1/6.
Aluminium Panels, 18 s.w.g., 12 x 12in. 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/3; 8 x 6in., 2/-.

6 TRANSISTOR RADIO MED. & LONG WAVE KIT
 First class components to make a 6 transistor 2 wave band superhet chassis. Ideal for portable or table radio. All parts including BVA transistors ferrite aerial, printed circuit, 8 1/2in. x 2 1/2in., but EXCLUDING speaker and cabinet. Simple instructions 1/6 (Free with kit).
 Speakers, 3s ohm. 7 x 1in. 25/- extra or 3 1/2in. round 19/6 extra. **£4.50**

TV Plug-in "V" Aerial 16/6
JACKS. English open circuit, 2/6. Closed circuit, 4/6. Grundig type, 3 pin, 1/6.
JACK PLUGS. English, 3/-; Screened, 4/-; Grundig, 3 pin, 3/6.
Wirewound Ext Speaker Control, 10 Ω 3/-.
ALADDIN FORMERS and cores, 1in., 8d.; 1 1/2in., 10d. 0.3in. FORMERS 5957 or 8 and cans TV1 or 2, 2 1/2in. sq. x 2 1/2in. or 1in. sq. x 1 1/2in., 2/- with core.
SLOW MOTION DRIVES. 6-1, 2/6.
SOLO IRON, 25W, 200V or 230V, 24/-.
ANTEX SUB-MIN IRON 15w. 200 or 240v, 29/6

JASON FM TUNER COIL SET.
 29/-, H.F. coil, aerial coil, oscillator coil, two I.F. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. Complete Jason FMT.1 Kit. Jason chassis with calibrated dial, components and 4 valves, £6.5.0.

MAINS DROPPERS. Midget adjustable sliders. 0.3A, 1,000 ohms, 5/-; 0.2A, 1,200 ohms, 5/-; 0.15A, 1500 ohms, 5/-; 0.1A, 2,000 ohms, 5/-.
LINE CORD. 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 1/- per foot; 3-way 1/- per foot.
MIKE TRANSFORMER. 50-1, 3/6.
P.V.C. Conn. Wire, 8 colours, single or stranded, 2d. yd. Blewing, 1.2mm, 2d.; 4mm, 3d.; 6mm, 6d. yd.
SPEAKER FRET. Gold cloth, 17 x 25in., 5/-; 25 x 35in., 10/-; Tysan, various colours, 9in. wide, from 10/- ft.; 26in. wide, from 5/- ft. Samples, S.A.E. Expanded Metal, gold, 12 x 12in., 6/-.

TELEVISION REPLACEMENTS
Line Output Transformers
 from 45/- each, NEW Stock and other timebase components. Most makes available. S.A.E., with all enquiries

"REGENT" 4 VALVE "96" RANGE VALVES KIT PRICE £6. 6. 0. carr. 4/-



PRINTED CIRCUIT BATTERY PORTABLE KIT
 Medium and long wave. Powerful 7 x 4in. high Flux Speaker. T.C.C. Printed Circuit and condensers. Components of finest quality clearly identified with assembly instructions. Osmor Ferrite Aerial Coils. Rinex covered attache case cabinet. Size 12in. x 8in. x 4in. Batteries used B125 (L5512) and AD35 (L5040), 10/9 extra. Instructions 9d. (free with kit).

MONARCH RECORD PLAYER
 Kit with ready built amplifier, speaker and cabinet. **£12.10.0**
 carr. and ins. 5/-



4 Speed Autochanger, B.S.R., U.A.14 £7.10.0
B.S.R. U.A.12 Stereo/Mono .. £5.5.0
Garrard Model Autostem .. £7.10.0
2 Speed Single Players, FMT .. £6.5.0
Garrard TA Mk.11, GCS Head .. £8.0.0
Garrard Model 4SP GC8 .. £6.17.6
Garrard 4HF Transcription .. £17.10.0
Amplifier flyer cabinets (except 4 H.F.) 70/-
2-wave amplifier and 8in. speaker .. 95/-
3-wave amplifier and 8in. speaker .. 105/-
 Wired and tested ready for use with above.
 All sapphire styli available from 6/-.

I.F. TRANSFORMERS 7/6 pair
 465 kc/s slug tuning miniature can. High Q and good band width. Data sheet supplied.

ARDENTE Transistor Transformers
 Type D3035, 7.3 CT; Push Pull to 3 ohms for OC72, etc., 1 x 1 x 1in. 9/6
 Type D3034, 1.75 : 1CT. Push Pull Driver for OC72, etc., 1 x 1 x 1in. 9/6
 Type D3058, 11.5 : 1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in. 9/6
 Type D187, 18.2 : 1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in. 12/-
 Type D239, 4.5 : 1 Driver Transformer, 10/-
 Type D240, 8.5 : 1 Driver Transformer, 10/-
ARDENTE TRANSISTOR CONTROLS
 Type VC1545, 5K with switch, dia. 0.9in., 10/-
 Type VC1760, 5K with switch, dia. 0.7in., 10/6
 Deaf aid ear piece xtal or magnetic, 7/6.

WEYRAD COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL
 Long and Medium Wave Aerial—RA2W. On 6in. rod, 7/16in. diameter, 236F tuning. 12/6
 Car Aerial Coil. 1/6
 Oscillator Coil P50/1AC. Medium wave. For 176F tuning. 5/4
 1st and 2nd I.F. Transformers—P50/2CC. 4/7
 3rd I.F. Transformers—F50/3CC. to feed diode detector. 6/-
 Spare Cores. 6d. each
 Driver Transformer—LFDT4. 1 5/16 x 1 1/2 x 1 1/2in. 9/6
 Waveshape Switch. 3/6
 Printed Circuit—PCAL. Size 2 1/2 x 8 1/2in. Ready drilled and printed with component positions. 9/6
 Volume Control. 2/6
 7 x 4in., 35 ohm speaker. 2/6
 3 1/2in. round 35 ohm speaker. 1/6
 24 Fixed Resistors. 10/6
 16 Fixed Condensers. 21/-
 Tuning Gang with trimmers. 10/6
 6 Mullard Transistors and diode. 42/-
 Constructor's Booklet. 2/-

NEW MULLARD TRANSISTORS & DIODES
 Audio OC71 8/- R.F. OC44 8/6 OA70 3/-
 OC45 8/6 OC81 7/6
 Sub Miniature Condensers, 0.1 mfd. 30 v. 1/3. 1. 2. 4. 5. 8. 16. 25. 30. 50. 100 mfd. 15 volt. 2/6 each.
B.B.C. Pocket 2 Transistor. M.W. and L.W. Radio Kit, 22/6.
 Miniature earpiece, 7/6. Batt. 2/3.


COMPONENT SHOP SPECIALISTS
 Poqt 1/-, unless otherwise stated. C.O.D. 2/-.

337 WHITEHORSE ROAD WEST CROYDON
 Telephone: THO 1665
 (Export orders. Send remittance and extra postage).

See the whole range at



The Radio Show, Stand 15.

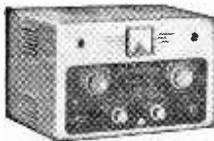

DX-40U

AMATEUR TRANSMITTER. Model DX-40U. Self-contained. 80-10 m. Power input 75 w. C.W., 60 w. peak, C.C. phone. Output 40 w. to aerial. Provision for V.F.O. **£32.10.0**

AMATEUR TRANSMITTER. Model DX-100U Covers all amateur bands, 160-10 m. 150 w. D.C. input. Self contained with power supply. Modulator, V.F.O. **£71.10.0**



DX-100U

AUDIO SIGNAL GENERATOR. Model AG-9U. 10 c/s-100 kc/s. switch selected. Distortion less than 0.1%. 10 v. sine wave output metered in volts and dB's ... **£19.19.6**

VALVE VOLTMETER. Model V-7A. Measures volts to 1,500 (D.C. and R.M.S.) and 4,000 pk to pk. Res. 0.1Ω-1,000 MΩ. D.C. input impeded. 11 MΩ. With test prods, leads and standardising battery. ... **£13.0.0**

R.F. SIGNAL GENERATOR. Model RF-1U. Gives accurate source of R.F. up to 100 Mc/s on fundamentals and 200 Mc/s on harmonics. Up to 100 mV output on all bands. ... **£11.18.0**

SINGLE SIDEBAND ADAPTOR, Model SB-10U May be used with most A.M. transmitters. Less than 3W R.F. input power required for 10W output. Operation on 80, 40, 20, 15 and 10m bands on USB, LSB or DSB **£37.6.0**



SB-10U

HI-FI 18W STEREO AMPLIFIER Model S-99. Ganged controls. Stereo/mono gram, radio and tape recorder inputs. Push-button selection. Printed circuit construction. ... **£26.19.0**

HI-FI AM/FM TUNER. Tuning range: FM: 88-108 Mc/s. AM: 16-50, 200-550, 900-2,000 m. Tuning heart (£5.5.6 incl. P.T.) and I.F. amplifier (£19.8.0) sold separately. Printed circuit board. ... Total **£24.13.6**

SHORTWAVE TRANSISTOR PORTABLE. Model RSW-1. Two short bands, trawler and medium **£21.6.0**

6-TRANSISTOR PORTABLE. Model UXR-1. Preamplified I.F. transformers, printed circuit, 7 x 4in., high flux speaker. Real hide case. ... **£14.3.0**

TAPE RECORDING/PLAYBACK AMPLIFIER Stereo (TA-1S) ... £23.6.0 Monaural (TA-1M) ... **£18.2.6**

STEREO CONTROL UNIT USC-1. Luxury model with press-button inputs to suit any pick-up or tuner and most tapeheads. Output 1.3 v. R.M.S. per channel. Printed circuit construction. **£18.18.6**



MALVERN

HI-FI EQUIPMENT CABINETS. Range available to meet various needs. Details on request. (MALVERN equipment cabinet illustrated on the left) from **£11.12.6 to £18.10.0.**

STEREO HEAD PREAMPLIFIER USP-1. Ideal for boosting tape-head output and low output pick-ups (e.g. Decca ffs) **£6.17.6**



S-99



AM/FM Tuner



TA-1S

VAR. FREQ. OSCILLATOR. Model VF-1U Calibrated 160-10 m. fundamentals 160 and 40 m. Ideal DX-40U and similar transmitters. **£11.2.0**

HI-FI F.M. TUNER. Tuning range 88-108 Mc/s. Tuning Unit (FMT-4U) with 10.7 Mc/s I.F. output (£3.2.0 inc. P.T.) I.F. Amplifier (FMA-4U) complete with cabinet and valves (£11.11.0) ... Total **£14.13.0**

6-W STEREO AMPLIFIER. Model S-33. 3 w/chl. inputs for radio/tape and gram., Stereo or Mono ganged controls. Sensitivity 200 mV. ... **£12.8.6**

SINGLE CHANNEL AMPLIFIER. Model MA-12. 10-12 watt Hi-Fi amplifier. Extremely low distortion and wide frequency range ... **£10.19.6**



GC-1U

Money Saving "PACKAGED DEALS" of Complete Stereo Equipment from **£44.9.0**

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted-port bass reflex cabinet "in white." Twin speakers. Pedestal model **£11.15.0.** Bookcase model. **£10.14.0**

"COTSWOLD" HI-FI SPEAKER SYSTEM. Acoustically designed enclosure "in the white" 26 x 23 x 15 1/2 in. 12in. bass speaker with 2in. speech coil, elliptical middle speaker. Pressure unit covers the full freq. range of 30-20,000 c/s., complete with cross-over unit, level control, etc. **£21.19.0**

AUDIO & DO-IT-YOURSELF accessories also available



COTSWOLD

Assembled models also available—prices on request. Deferred terms available over £10. Free delivery U.K.

Prices will be approximately 5% greater after 20th August

Please send me FREE CATALOGUE (Yes/No) _____

Full details of model(s) _____

NAME _____

ADDRESS _____

PW9

DAYSTROM LTD.

Dept. P.W.9, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

Practical Wireless

Vol. XXXVIII No. 667 SEPTEMBER, 1962

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, W.C.2.

© George Newnes Ltd., 1962

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland	- - -	£1.9.0 per annum
Abroad	- - -	£1.7.6 per annum
Canada	- - -	£1.5.0 per annum

Contents

	Page
Editorial	381
Round the World of Wireless	382
Medium Wave Pocket Superhet	384
Increasing Voltmeter Ranges	388
High-fidelity Main Amplifier	389
On Your Wavelength	392
Power Rectifier Circuits	395
Home-made Hi-fi Output Trans- former	398
Servicing Tape Recorders	403
Servicing the P.W. Pocket Superhet Receiver	405
The Miniscope	408
Compact Converter	413
Short Wave Listeners' Log	418
Noisy Volume Controls	421
Trade News	425
The Consort TRF Receiver	429
The Tudor	433
Letters to the Editor	441
Club News	442

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless".

COMMERCIAL RADIO

THE possibilities of introducing commercial sound broadcasting in this country have long been evident but until the Pilkington Committee reported, no decision could be given. The Committee reported in June and recommended that a service of local sound broadcasting should be introduced by the BBC and that commercial sound broadcasting (broadcasting financed from advertisement revenue) should not be introduced. The reasons for the Committee's decision were similar to those given for their recommendation that there should be a radical overhaul of the commercial television broadcasting services. They were that, when programmes are financed from revenue derived from the sale of advertisement time, then the planners of the programmes always, consciously or unconsciously, arrange the programmes to attract as much advertisement revenue as possible. The programmes, the Committee stated, must necessarily decline in standards and it therefore considered that local sound broadcasting should be provided by the BBC and financed from licence revenue. It had been argued that a commercial network would be able to provide the public with "what it wanted" rather than "what set of programme controllers thought it wanted". However, the Committee pointed out the fallacies in this argument: public taste would gradually be debased—unless the opportunity is available to listen to or view programmes of a high standard, such programmes can never be appreciated or enjoyed by the majority of the general public. The aim should be to improve public taste gradually yet provide programmes which are of high entertainment value.

In the White Paper published by the Government after the Pilkington report, it was stated that there has been little evidence of any general public demand for local sound broadcasting, and the Government would study public reaction before making a decision. We are inclined to think that the lack of demand for a system of local sound broadcasting is due to the lack of public knowledge of the subject; no doubt demand will increase when the public realises the potentialities of such a service. We should be interested to hear readers' views.

MORE BLUEPRINTS

With the next issue, dated October, we are beginning another series of free double-sided blueprints. On one side of the blueprint in next month's issue, will be the first of a series of designs for a comprehensive hi-fi system. This part will consist of the main amplifier and power supply sections of the chain. The main amplifier will have a maximum output in excess of 20W with very low distortion.

On the other side of the October blueprint will be a design for a simple signal generator covering 150 kc/s to 30 Mc/s, modulated or unmodulated. Provision will also be included for use of the internal audio oscillator for test purposes. Although the signal generator uses a simple circuit, is inexpensive, and is easy to build with the large clear diagrams included on the blueprint, all amateur constructors will find it a valuable addition to their range of test equipment.

Our next issue dated October, will be published on September 7th.



of WIRELESS

NEWS AT HOME AND ABROAD

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of May, 1962, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London	642,217
Home Counties	593,774
Midland	429,096
North Eastern	457,568
North Western	395,333
South Western	350,584
Wales and Border Counties	202,893
Total England and Wales	3,071,375
Scotland	325,276
Northern Ireland	107,557
Grand Total	3,508,208

Sound at Wimbledon

FOR over 30 years the sound amplification and distribution for the Wimbledon Lawn Tennis Championships has been the responsibility of the Public Address Department of Standard Telephones and Cables Limited.

STC equipment feeds all sound, except commentaries, from the Centre Courts Nos. 1, 2 and 3 to the BBC and into the Wimbledon distribution system generally. It feeds a ring of monitoring loudspeakers from which the electric scoreboards are operated; it provides facilities for car-park calling, turnstile control, emergency police control, and an over-riding call sys-

tem under the control of Col. A. D. C. Macaulay, the secretary of the All England Lawn Tennis Club.

An elaborate telephone system is also installed by STC to link each umpire with the chief umpire and the referee's room, and also to link the pay boxes and turnstiles.


Fuel cell battery power for GEMINI two-man Spacecraft

THE fuel cell, one of the most promising new ways of making electricity, will be put to operational use for the first time

in the next phase of the United States' manned spaceflight programme.

Under contract to McDonnell Aircraft Corporation, U.S. General Electric will develop a fuel cell battery, the most advanced of its type yet produced, to supply primary power for the two-man Gemini spacecraft.

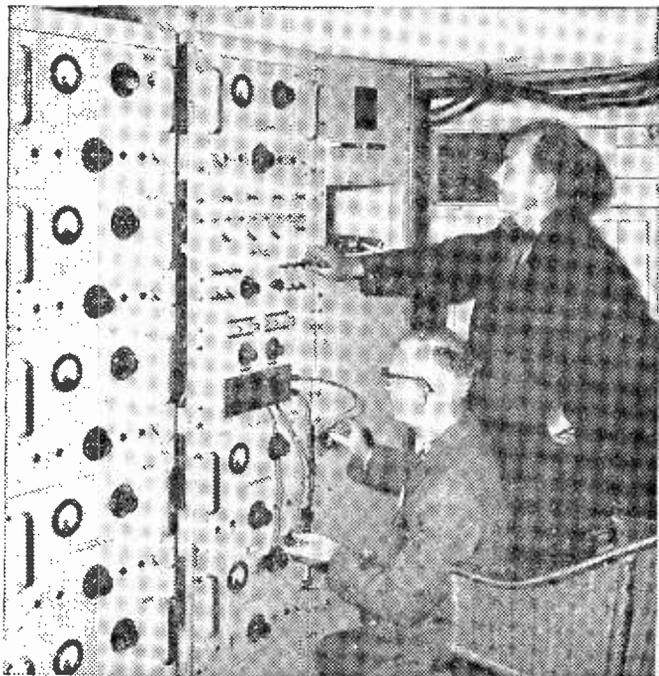In the Gemini vehicle, fuel cells will for the first time take the place of conventional batteries or mechanical power units as the primary electrical power source in space.



Two STC engineers of the Public Address (Hire) Department, making final adjustments to the amplifier equipment before the start of play at the Wimbledon Lawn Tennis Championships.

The fuel cell system was chosen for Gemini because its weight will be significantly less than that of a combination of conventional batteries and solar cells which could also be used in space flight.

The Gemini fuel cell battery will deliver a peak load of almost two kilowatts of D.C., providing primary power for all equipment aboard the spacecraft, including control, artificial environment, communication and instrumentation apparatus.


In addition to its electrical output, it will have a by-product in the form of pure, potable water, accumulating at the rate of one pint per kilowatt-hour of operation. This water can be used, without treatment, to augment the supply stored aboard the spacecraft for drinking, cooling or other life-supporting purposes.

The system is based on General Electric's ion-exchange membrane fuel cell, which produced electricity through the chemical reaction of oxygen and hydrogen. A fuel cell battery is composed of many of the sandwich-like cells connected in series to form building blocks that can in turn be connected in series or parallel to meet specific power requirements. Each cell is separated into two sections by the membrane, a sheet of tough plastic.

In operation, hydrogen gas is fed to one side of the membrane and oxygen to the other. Electrons from the hydrogen atoms are picked up by a thin metallic electrode in contact with the membrane surface, while the remaining hydrogen ions pass through the membrane. The electrons flow into an electrical circuit, providing power, and then return to the other side of the membrane, where they recombine with the ions and join with the oxygen atoms in the formation of water.

Radio tour of the Guildhall

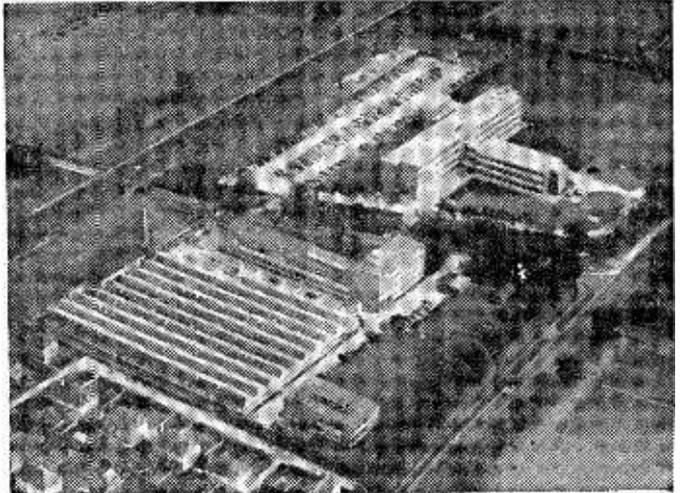THE Lord Mayor of London, Sir Frederick Hoare, inaugurated the Radio tour of the Guildhall in the City of London, on July 5th this year. The radio tour enables visitors to hear a taped commentary of the 15th century Hall and its Crypt, its connections with the Corporation of London, the Freedom of the City and the Livery Companies, by means of a hand-held



The Mullard research laboratories at Salfords, Surrey, was visited recently by representatives of the Press. At these up-to-date laboratories, much experimental work is carried out on colour television, transistors, computers, and many other aspects of the electronics industry.

receiver which picks up the transmissions which are radiated at a fixed frequency.

Radio for Mobil Tanker

THE "Mobil Endurance", a tanker built for the Mobil Shipping Co. Ltd., has been fitted with radio equipment by Associated Electrical Industries Ltd.

The "Mobil Endurance", which has now completed her acceptance trials, is the third of five vessels to be built for Mobil at Gothenburg. All five ships will finally be fitted with AEI marine apparatus. The radio installation on the "Mobil Endurance" will include a 600W W.T./R.T. transmitter, a 28 channel international channel transceiver and an AEI "Escort 601" Chartplan radar.

Satellite Communication System Ground Station

ALMOST all of the equipment at the British Post Office Satellite Communication Ground Station at Goonhilly Downs, Cornwall, planned for the initial experimental projects Relay and Telstar, is of British design and manufacture.

The predominating feature of the facilities which have been provided is an 85ft diameter steerable aerial. The aerial is in the form of a paraboloidal dish with


full automatic steerability over the hemisphere above the horizontal plane on the basis of predicted orbital data, and manual control for resetting purposes.

The steering of the aerial in azimuth and elevation is by means of closed-loop servo type motors. The angular positions of the azimuth and elevation shafts are indicated by digital shaft-angle encoders.

Not the least important of the equipment at Goonhilly, the design authorities for which are the Space Communications Branch and the Research Branch of the Post Office Engineering Department, is the variety of cables which form the vital interconnections between the aerial and the control building, as well as those on the equipment on the aerial itself. The former cable runs in troughs above ground level.

British Insulated Callender's Cables Limited have supplied no less than 20 miles of cable, comprising all of the coaxial cable (31,000yd) which runs from the azimuth and elevation position encoders back to the control building—a distance of about a quarter of a mile—and some 5000yd of the multicore PVC SWA PVC sheathed 250/440 and 660/1100V control cabling between the aerial and the control building.

MEDIUM WAVE POCKET SUPERHET

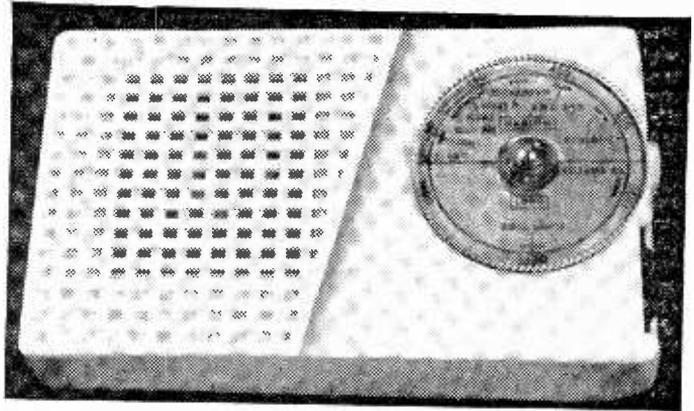

by J. G. THOMPSON

AN ECONOMICAL PORTABLE RECEIVER

THE circuit of this receiver is shown in Fig. 1, and has the advantage that the battery drain is quite small. The full superhet circuit provides very good sensitivity, and the single-ended push-pull output stage is particularly economical. Current consumption, at low volume, is only about 8mA. At average listening volume, this rises to about 12mA to 14mA or so. The usual small type of 9V battery thus has a long working life.

Coverage

The receiver tunes medium waves only, as this simplifies the first stage, but it is possible to add long waves later, without disturbing other parts of the set.

If possible, it is recommended that an OC44 is used for Tr1, with OC45's for Tr2 and Tr3, and an OC71 for Tr4. However, other transistors of similar type were found to work satisfactorily in these stages. For the output stage, a maker's matched pair of OC72 transistors (2 × OC72) should be fitted. Resistors R18, R19, R20 and R21 should also be of 5% tolerance, while all others can be of 10% tolerance. Correct working conditions will then be assured, without any need to experiment, or change resistor values.

Paxolin Panel

This should be made first, all important drilling being finished before mounting any parts. The panel is 5½in. × 3in. × ⅛in. thick, this giving a little clearance all round in the specified cabinet. Drill three holes so that the panel can be secured in the case by short 6B.A. bolts. (A piece of thin card can be used as a template, piercing holes in it in the correct positions.)

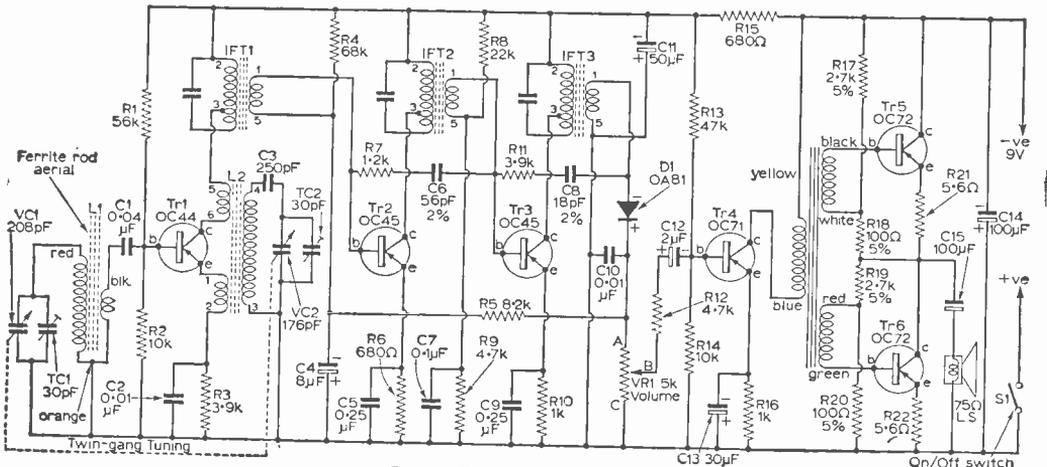


Fig. 1—The circuit diagram.

The gang condenser fits in a fairly large clearance hole. Check that there is space for the battery, with at least $\frac{1}{4}$ in. to spare; then, drill holes for the three short 4B.A. bolts shown in Fig. 3. The pierced card will show exactly where to drill. If the screws project more than the thickness of the condenser plate, washers are needed under their heads.

Volume Control

Mount the volume control as in Fig. 2. One switch tag projects up through a hole, and the other tags are bent flat. Check that the set will fit in the case, and that the battery can be accommodated. The volume control slot in the case will need widening slightly, with a small file. It may also be necessary to enlarge the tuning condenser hole.

These parts are then removed, and the holes are drilled for the four screened coils. If the pins are pressed on the thin card template, this will show where to drill. Check that each coil fits easily, then place it on one side. If any holes are not quite correct they can be enlarged with a small round file.

Loudspeaker Mounting

The loudspeaker hole is about $\frac{1}{2}$ in. larger all round than the loudspeaker magnet. It can be made with a washer cutter, a fretsaw or other very small saw, or by drilling holes, and clearing up with a half-round file. Temporarily position the loudspeaker, mark the two speaker fixing holes (Fig. 3) and drill them.

After drilling holes for the driver transformer,

readily in the case, with battery. Note that the case tapers slightly towards the back; there should be a little clearance all round.

The loudspeaker is now removed until the set is wired. When finally mounted, it is held by two 6B.A. countersunk bolts, inserted from the front. The bolt near the rod mount has two nuts, one locking the loudspeaker, and the other giving

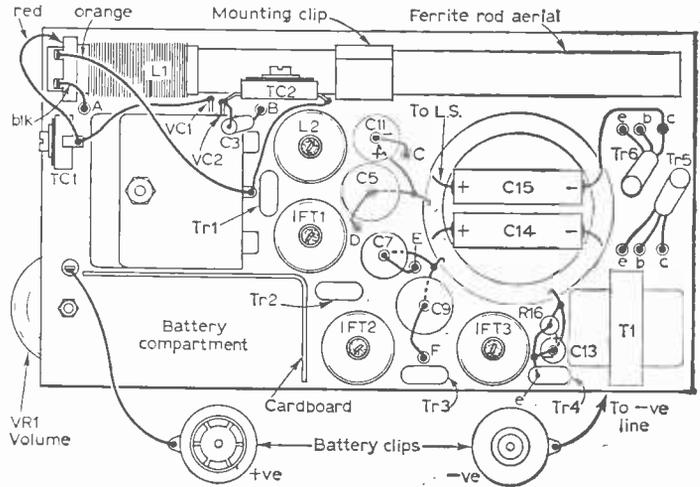



Fig. 2—The layout and wiring diagram of the rear of the receiver panel.

correct clearance between loudspeaker and panel, a third nut then being tightened behind the panel. The remaining loudspeaker mounting hole (Fig. 3) is obscured by the driver transformer. A short countersunk bolt is therefore inserted from behind, and locked with a 6B.A. terminal head. The transformer can then be permanently mounted. Another 6B.A. bolt may then be inserted from the front of the loudspeaker, and run into the terminal head, washers or nuts providing spacing.

Construction

All wiring is of 26s.w.g. tinned copper wire, insulated with 1mm sleeving. It will be helpful to use red sleeving throughout the positive side of the circuit, and black sleeving throughout the negative line, with yellow or some other colour for all other leads. Sleeving is also placed over all transistor leads, and the wire ends of all resistors and condensers. Sleeving on the transistor leads can be of such a length that the

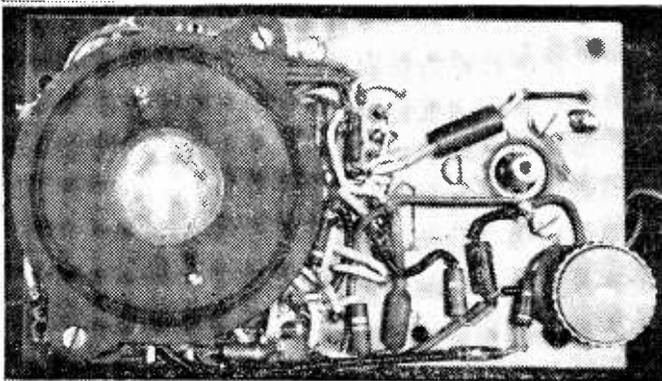tops of the transistors Tr1 to Tr4 come about level with the tops of the screened coils; Tr5 and Tr6 are bent over as in Fig. 2. Be sure that the transistors are in their correct stages, and that the collector base and emitter leads all emerge as



The loudspeaker side of the panel, with the wiring complete.

transistor lead holes can be positioned as in Figs. 2 and 3. A short 4B.A. bolt holds the rod mounting.

Clean up all holes, and mount the rod, gang condenser, speaker, driver transformer and screened coils, and check that the whole can fit

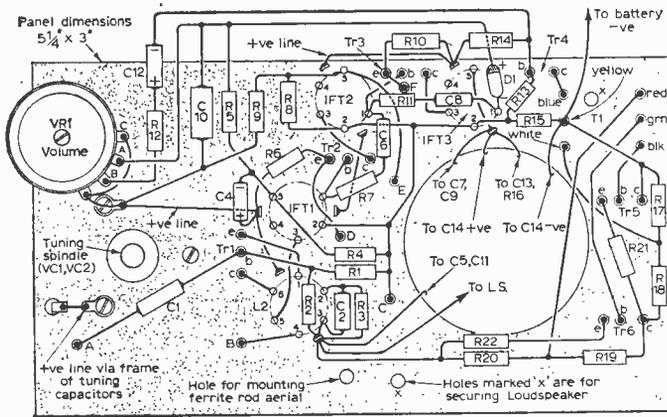



Fig. 3—The wiring on the front of the panel.

shown by the letters c, b and e in Fig. 3.

The various points marked MC form the earth, or positive, side of the circuit, and are all joined. These include the can tags of the oscillator coil and I.F. transformers, and the metal frame of the gang condenser.

Control Wiring

Fig. 4 shows the tag side of the volume control.

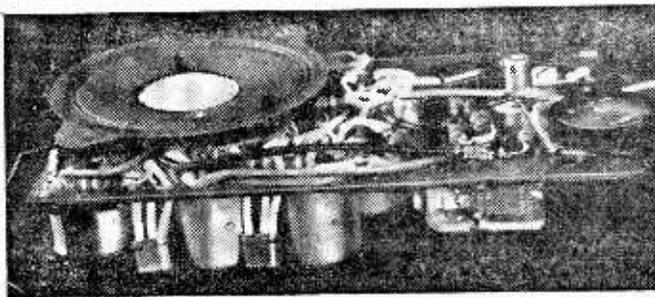

Another view of the completed set, less its case.

In Figs. 1, 3 and 4, A is one end of the element, B the slider, and C is the other end of the element and one switch tag. The remaining switch tag passes through the hole in the panel (see Fig. 2). A short piece of thin red flex is soldered on here and fitted with a positive battery clip.

The trimmer TC1 has one tag inserted in a hole, so that it can be soldered to the tag held by the 4B.A. bolt, in Fig. 3. Trimmer TC2 is soldered directly to the 176pF tag of the gang condenser (VC2), a short lead returning to the condenser frame.

All leads and components are kept close against the panel. Leads and resistors should also be clear of the position which the speaker will occupy. Electrolytic condensers are wired with the polarity shown in Fig. 3. Other condensers, and all resistors, may be wired in either way round. The negative end of the diode must go to pin 1 of the third I.F. transformer.

C13 and R16 are wired in parallel. The wire end of R16 passes through a hole, to the MC tag in Fig. 3. The negative lead of C13 goes to the same hole as the emitter of Tr4, to which it is joined.

The negative end of C15 passes into the same hole as the collector of the one OC72, as in Fig. 2, these leads being joined, and also going to R19, R20 and R22 (Fig. 3).

It is best to leave all the transistor leads reasonably long, but prolonged heating with the soldering iron should be avoided.

The larger fixed condensers are mounted behind the panel, as in Fig. 2; C5, C7, C9 and C11 each have a lead passing directly down through the panel, and all are soldered to the MC or earth line. The top wires of these condensers

COMPONENTS LIST

- Resistors: (10% unless otherwise indicated):**
- | | | |
|---------|----------|-------------|
| R1 56k | R9 4.7k | R17 2.7k 5% |
| R2 10k | R10 1k | R18 100Ω 5% |
| R3 3.9k | R11 3.9k | R19 2.7k 5% |
| R4 68k | R12 4.7k | R20 100Ω 5% |
| R5 8.2k | R13 47k | R21 5.6Ω |
| R6 680Ω | R14 10k | R22 5.6Ω |
| R7 1.2k | R15 680Ω | |
| R8 22k | R16 1k | |
- VR1 5k miniature vol. control with switch
- Condensers (All miniature types):**
- | | | |
|-----------|------------|-----------|
| C1 0.04μF | C6 56pF 2% | C11 50μF |
| C2 0.01μF | C7 0.1μF | C12 2μF |
| C3 250pF | C8 18pF 2% | C13 30μF |
| C4 8μF | C9 0.25μF | C14 100μF |
| C5 0.25μF | C10 0.01μF | C15 100μF |


- | | |
|------------------------------------|------------------|
| TC1 30pF trimmer | TC2 30pF trimmer |
| VC1/VC2 208/176pF gang with screen | |
- Transistors:**
- | | |
|---------------------------------|----------|
| Tr1 OC44 | Tr3 OC45 |
| Tr2 OC45 | Tr4 OC71 |
| Tr5 and Tr6 matched pair OC72's | |
- Diode: OA81**
- Other Parts:**
- Split secondary driver transformer (Fortiphone L442)
 - M.W. Ferrite rod, oscillator coil, 1st, 2nd and 3rd IFT's (Osmor)
 - 75Ω loudspeaker, 2½in., with plastic chassis (W.B.)
 - ¾ x 6½ x 1⅜in. Pocket Superhet case
 - Paxolin, wire, sleeving, etc.

are bent over, and pass down through other small holes, as in Fig. 2, so that they can be connected as in Fig. 3.

C14 and C15 must have insulated sleeves, or be covered with insulated material. They are secured side by side with tape, and rest on the speaker magnet. C14 goes from the positive line to the negative line. C15 is wired from collector to loudspeaker, as in Fig. 2.

In Fig. 1, short pieces of thin coloured flex are soldered to the aerial winding tags, for identification. Both "earth" ends of the windings are joined, for the orange lead. These leads are then connected up as in Fig. 2. That is, orange to condenser frame, red to T1 and VC1, and black to C1, Fig. 3.

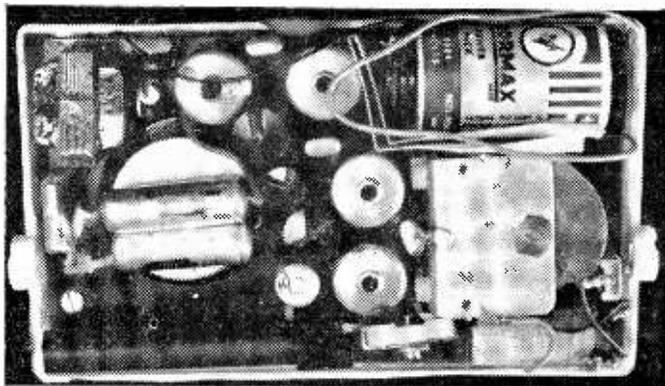After checking the wiring, solder lengths of thin flex to the 75Ω loudspeaker. One lead goes to MC in Fig. 3, and the other passes back to the positive end of C15. Fix the loudspeaker as described, making sure that its tags do not bear upon leads or parts already fitted. The loudspeaker itself is of insulated material. The spacing between loudspeaker and panel should be so adjusted that the



The receiver mounted inside its case.

A strip of paxolin or similar material should now be filed so that it will engage with the coil and transformer cores, to be used as an adjusting tool.

If a signal generator is available, set it for 470kc/s. with modulation, and connect its output to the black lead in Fig. 2, including an isolating condenser in circuit. Put the receiver volume control at maximum, reducing the generator signal,

if volume is too great. The three transformer cores are then adjusted for best results, which will also be the highest reading on the meter included in the battery circuit. All cores should have quite a sharp tuning peak.

Alignment on Stations

If no generator is available, tune in the local station, adding an external aerial a few feet long, if required. Then adjust the three transformer cores for best volume. They should be in a reasonable position, not screwed right in, or very far out.

Aerial and oscillator stage tuning can then be adjusted. TC1 and TC2 must be capable of reaching a low capacity. To begin, unscrew both trimmers, carefully separating the plates, if necessary. If a signal generator is available, adjust it to 550m, close the gang condenser, and rotate the oscillator coil core for best results. Then move the aerial winding on the rod, to obtain maximum volume. The generator is then set to 205m, the gang condenser is opened, and TC1 and TC2 are adjusted for best results.

If coverage is restricted on the low wavelength end of the band, this probably indicates that TC1 and TC2 need opening to a lower capacity. Repeat the trimming and inductance adjustments described a number of times, always adjusting the trimmers at a low wavelength, and the aerial and oscillator coil inductances at a high wavelength. Keep the receiver volume control at maximum, but choose

(Continued on page 417)

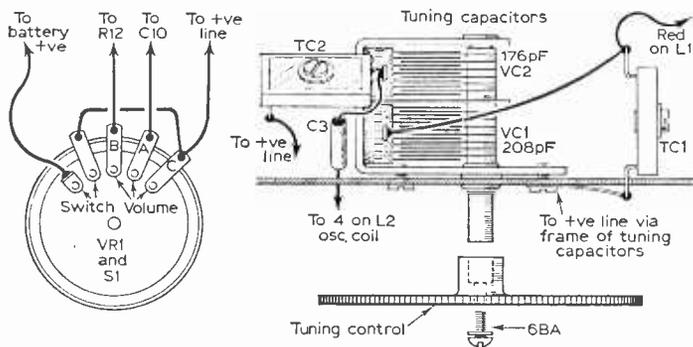


Fig. 4—The details of the volume control and tuning condensers.

loudspeaker rests on the front of the inside of the cabinet. A pad of material, such as thin soft card, is cut to fit inside the speaker opening, and an aperture is cut to match the speaker cone. This avoids buzzing noises due to vibration between case and speaker frame.

Check that the receiver will fit readily in the case. The unwanted tags of the gang condenser are bent down, to leave more space for the battery. A piece of cardboard, bent as in Fig. 2 isolates the battery from other parts, and prevents contact between the battery and second I.F. transformer.

Testing and Adjusting

If possible, a meter should be included in one battery lead. This should read about 7mA when the set is switched on. If the meter shows a high current, switch off at once, disconnect the battery, and check the wiring for shorts or errors.

INCREASING VOLTMETER RANGES

By G. A. W. Partridge

HERE are several types of high reading voltmeters on the market—the multimeter which caters for current and resistance measurement usually reads up to 1000V. But not all instruments have such high ranges. There are, however, quite simple ways of increasing the range of a voltmeter either permanently or temporary.

The most well-known method is to use a resistance type of multiplier connected as shown in Fig. 1. In this case a 0-500V instrument is able to read from 0-1,000V, by connecting a suitable resistance known as a multiplier in series with it.

Multipliers

The following example will show how a multiplier is chosen. The voltmeter reads from say, 0 to 100V and it is desired to increase its range to 1,000V. The sensitivity of the voltmeter is 10,000Ω/V.

The total resistance of the meter and the multiplier must be 1,000V × 10,000Ω/V which is 10,000,000Ω. Now the resistance of the meter alone is 100V × 10,000Ω/V which is 1,000,000Ω.

10,000,000 - 1,000,000 = 9,000,000Ω; the required resistance of the multiplier.

Alternative Calculation

Another way of calculating this resistance is first to find the current taken by the meter on its own, at full scale deflection, which is 100V.

$$I = \frac{V}{R} ; \quad = \frac{100}{1,000,000}$$


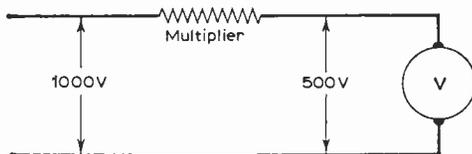


Fig. 1 (above)—The use of a multiplier to increase the range of a voltmeter.

Fig. 2 (below)—A transformer used as a multiplier.

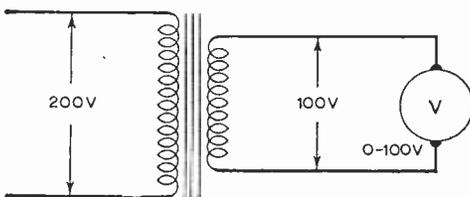

$$I = \frac{1}{10,000} \text{ A (0.1mA)}$$

At full scale deflection with the multiplier in circuit it must still draw 0.1mA. The voltage across the multiplier will be 1000-100=900. Its resistance will be:-

$$R = \frac{E}{I} ; \quad = 900 / \frac{1}{10,000}$$

$$R = 9,000,000\Omega.$$

In this case the instrument reading will have to be multiplied by 10 to give the correct voltage. The wattage of the multiplier is also important. It will be given by I.E, which is 1/10,000 × 900 = 0.09W. A 0.25W resistor will be ample here as it will not overheat.

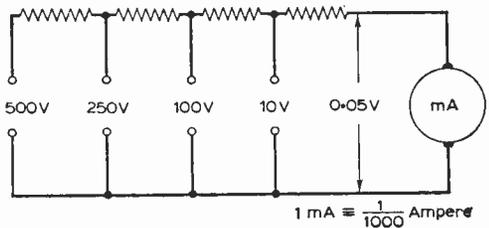


Fig. 3—Converting a millimeter for use as a voltmeter.

If alternating current is to be measured, the calculations must be based on the internal impedance, or ohms-per-volt rating of the instrument as an A.C. meter, not as a D.C. instrument. The multiplier must be non-inductive.

There are special types of instrument resistors on the market which are designed to remain at constant values for many years.

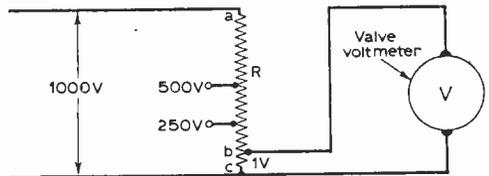


Fig. 4—The voltage divider.

Transformer Multiplier

For temporary and less accurate A.C. work, a transformer can be used as a multiplier (Fig. 2). In this case it has a ratio of 220/110V. The voltmeter reads from 0 to 100 and the transformer doubles this scale. The ratio error has been overlooked, but a reliable transformer should be chosen in order to prevent erroneous readings.

A 0.1 milliammeter can also be used as a voltmeter provided a suitable multiplier is connected in series with it. Fig. 3 shows an instrument of this type arranged to measure up to 500V. The internal resistance of the meter is 50Ω. Therefore the voltage required for full scale deflection is:

$$E = IR ; \quad = 1/1,000 \times 50 ; \quad 0.05V.$$

(Continued on page 400)

helping towards the balance of the output stage.

The output transformer was a Partridge type P3667, which has an 8k primary winding tapped at 6k. The constructor may therefore try both loadings out on the output stage, bearing in mind that resistors R13 and R14 will have to be changed as well (220Ω for normal loading and (390Ω) for low-loading conditions).

Increased Feedback

The degree of negative feedback is about 20dB, and increasing it to 30dB resulted in no instability, giving a good feedback stability margin.

An interesting feature about the driver-section is the resistor R6 and condenser C2 in series from the anode of V1A to earth. This is to prevent parasitic oscillations (rarely present in triode valves) and to provide a time constant giving good stability in the lower registers of the frequency range.

Close tolerance resistors should be used for the anode and cathode loads of the phase inverter, as well as in the grid resistors and stoppers of the output valves. The two coupling condensers, C4, C5 should have no leakage since any D.C. on the output valve grids will result in distortion.

The Power Supply

(Fig. 1). Valve V5, used in the prototype, was a 5Y3, though an EZ81 may also be used. In this case, the rectifier winding will be 6.3V at 1A. If additional current is not required for a radio tuner, 10mA for a pre-amplifier is available. An EZ80 may be used instead of the EZ81, and

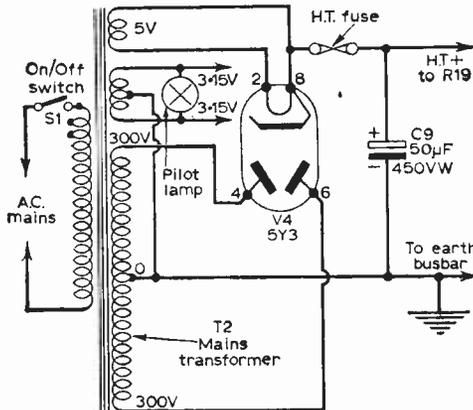


Fig. 2—The circuit of the power supply.

a common heater winding can then be used for all the valves. It should be noted that on no account should more than 90mA be drawn from an EZ80. Two resistors must be included in the anode circuit of the rectifier; the values for the EZ81 are 190Ω per anode, and for the EZ80 216Ω per anode. Under normal loading conditions the amplifier requires about 80mA of H.T. current, and 60mA under low-loading.

Since a smoothing choke was not used, a large smoothing condenser was required to supply the extra voltage on peak drives of the output stage.

COMPONENTS LIST

Resistors (all $\frac{1}{2}$ W unless otherwise stated)

R1	22k	R4	2.2k
R2	220k	R5	180Ω $\pm 5\%$
R3	100k	R6	8.2k
R7	220k (may be increased to 1M for H.F. stability)		
R8	47k $\pm 2\%$	R11	4.7k
R9	2.7k	R12	4.7k
R10	47k $\pm 2\%$		
R13, R14	220Ω (for normal loading) or 390Ω (for low loading)		
	(R13 and R14 are both 5% 3W)		
R15	220k	R18	47Ω
R16	220k	R19	1.2k 1W
R17	47Ω		
VR1	100 w.w. potentiometer		

Capacitors

C1, C9	50μF 450V elec.
C2	680pF
C3	0.05μF 600V
C4	0.05μF 600V
C5	0.05μF
C6	50μF elec.
C7	50μF elec.
C8	220pF $\pm 5\%$ (for 3.75Ω speaker)

Valves:

V1	ECC83	V3	EL84
V2	EL84	V4	5Y3

Mains transformer

Primary: 200-220-240V

Secondaries: 300-0-300V, 60 or 80mA (see text)
3.15-0-3.15V, 2A
Winding to suit heater of V5

Output transformer: Partridge P3667

Chassis:

12in. x 9in. x 2½in. approximately.
Pilot lamp, wire, solder, bolts, sockets, etc.

The possible change in line voltage is only 0.5%. Adequate decoupling of the stage is also assured.

Feedback

The values of R5 and R20 govern the degree of voltage fed back, and the values used in the prototype were 560Ω and 180Ω respectively, giving about 20dB of feedback. Constructors who wish to increase the feedback may do so by decreasing the value of R20 slightly. Resistors R8 and R10 should be good quality components of $\pm 2\%$ tolerance. Lack of balance here or in the output stage itself will result in unnecessarily high second harmonic distortion, owing to incomplete cancellation of the distorted anti-phase wave forms. A condenser in parallel with the feedback loop resistor promotes a phase shift opposite to that of the output transformer at the high frequency resonance of this component, and thus prevents the feedback from becoming positive at this frequency. If the output transformer is different from the one specified, it may be necessary slightly to modify the value of this component. The optimum value is best found by trial and error. Best results

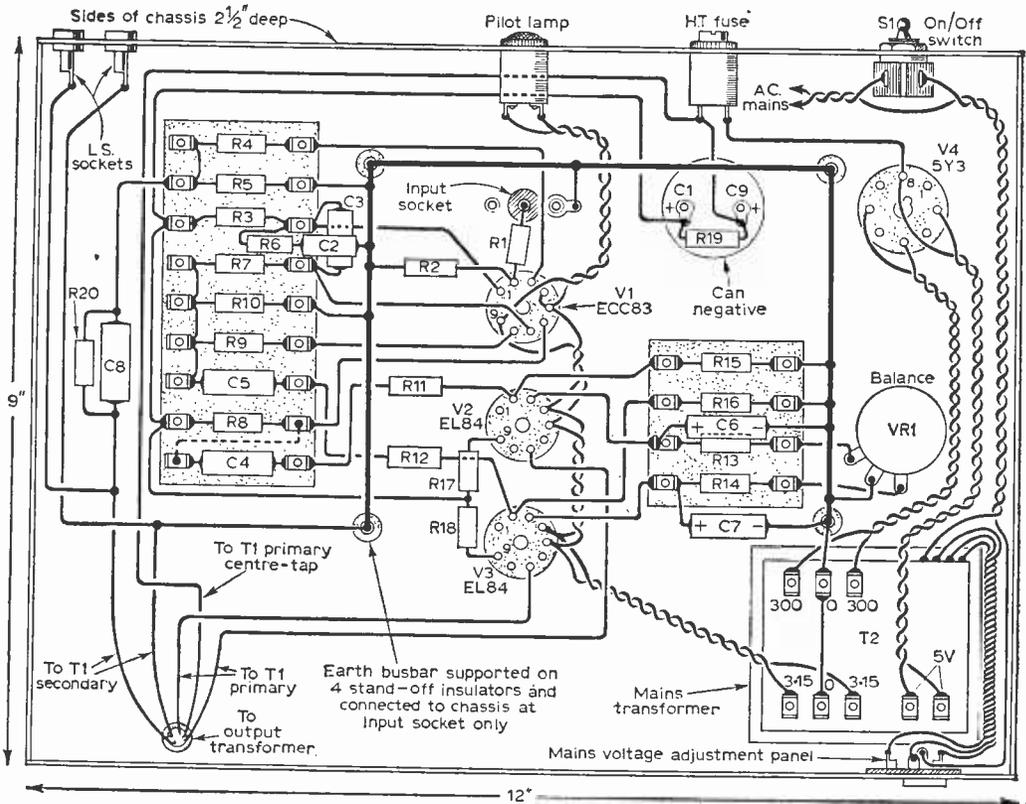


Fig. 3--The complete underchassis wiring diagram.

will be obtained if this amplifier is used in conjunction with the pre-amplifier designed by the author (June issue, 1961), as this was used with the prototype. The basic sensitivity is about 600mV and any high quality pre-amp capable of this output may be used.

Assembly

The components are first mounted on the group boards as shown in Fig. 3. When resistors R8 and R10, R15 and R18 are being soldered, a heat shunt should be used. Only one wire goes beneath the group boards, this is from C3 to R6 and is shown dotted in Fig. 3. When the group boards are assembled, they may be bolted into place with a spacer located between the board and the chassis, to allow for the wiring underneath.

All earth connections are soldered to the busbar, which may be held insulated from the chassis by means of two tagstrips: this busbar should be earthed to chassis at the input socket only.

An output socket may be included if desired, and should be insulated from chassis if possible.

Wiring

The heater and power supply should be wired in first. Tightly twisted wires are used for all A.C. circuits, and this wiring should be kept away from signal circuits and positioned as close to the chassis as possible.


Feedback

For negative feedback to take place, the amplifier output secondary winding must be correctly phased in relation to the input. If in phase with the input, violent oscillations will take place, which may damage a high-grade speaker suspension; hence, it is best to use a low-grade speaker to secure the correct phase relation.

Output Stage Balance

The output stage is next balanced and is a very simple procedure. The balance control VR1 should be slotted with a file for screwdriver adjustment only. Before switching on, check for an H.T. short with the meter. After switching on, if positive feedback occurs, then switch off immediately and reverse the anode connections on the output transformer primary. After about thirty seconds the set should have warmed up and a very slight hum only should be present (the hum level is approximately 80dB below full output).

A D.C. voltmeter is next connected across the anodes of the EL84's and the balance control VR1 is adjusted until no reading is obtained (ignore random fluctuations). The valves are now balanced from the D.C. aspect, which is usually the same for signal input. If a balance cannot be obtained, the valves should be switched over and the procedure carried out again: if a balance is still not obtained, then the valves should be checked for emission. Usually a balance is easily obtained. ■

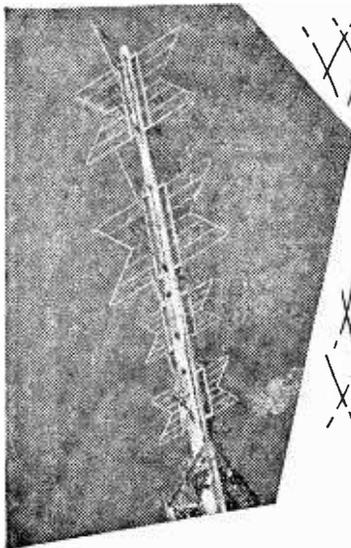

On Your Wavelength

By THERMION

appear to have some useful possibilities. The demonstration consisted of a dance where, if one looked in at the door during the demonstration one would have seen dozens of couples waltzing round the hall in dead silence—yet all in perfect step. The secret was that they were all wearing a form of hearing aid earpiece inserted in the ear, and they carried a small unit which picked up sound from a loop running round the floor of the hall. Fed to this was the output from a record player, and the signal was inductively coupled to their pick-up device. It would seem that there are many very suitable uses for this type of coupling, not only inside buildings, but also out of doors. I will leave my readers to think of some of the most intriguing of these.

Transistor Sets Again

CONSIDERABLE publicity has been given recently in a certain section of the daily press, to a suggestion made in a letter on the "killing" of interference from transistor portables. A reader suggested that the annoyance from these sets could be removed by using a radiating device—which readers will remember was first suggested on this page a long time ago, and I mentioned the fact that it was not known at the time what the reaction of the Post Office authorities would be on the use of such "jamming apparatus". We subsequently published a quotation from the Wireless Telegraphy Act which pointed out that it was an offence to use any apparatus which could cause interference with other apparatus and that therefore such jamming equipment would be considered to be illegal. The references to the interference device quoted in the opening paragraph of these notes has brought apparently shoals of letters in which such terms as "knighthood" and even "canonisation" have been suggested as suitable rewards for the student whose letter first drew attention to the idea. It is, of course, not an "invention", but merely an application of a known device, which is, in fact, being used illegally if its purpose is to jam another receiver, and most readers will know that even a simple super-regenerative set, if it does not have a buffer input stage, can cause interference over a wide area even under the most correct operating conditions. The estimate of £20 for constructing one of these "jammers" seems rather excessive.

Remote Controls

Hard on the heels of my notes about remote controls (August issue) a reader reminds me of a demonstration given many years ago of a magnetic induction form of control which seems to have disappeared with time—although it would

Electronic Games

I have now received a large number of letters on the above subject and some of these make most interesting reading. The one I like best is that describing a "Bingo machine" built by a reader in Kent, and when I have had time to study all of these, I will try and see if the Editor can afford the space to publish details of one or more. Some very ingenious ideas seem to have been applied, and so far expense seems to have been saved by utilising standing equipment which can be obtained very cheaply. I felt sure that our readers would overcome difficulties such as "expense" by making do, and this now does seem to be the case.

One reader suggested the simple plan of having ordinary on-off switches, either toggle or simple bell type, by means of which two people could play against each other, and he pointed out that these switches may be obtained with a bias in some cases so that their operation consists merely of pushing them against the bias, which will operate a desired circuit, and then on releasing them they will return to their original setting. This does offer some scope, but in most cases this arrangement could only be used with what I might call "electrical" circuits, rather than electronic. That is to say, battery and lights with switches in circuit could be employed, and by this means the "game" would be reduced to its most simple form, but this is not the type of device I had in mind in my first remarks on this subject. I was visualising the arrangement where a form of "electronic brain" was employed, whereby after one player operating a button or switch recorded information in the complete equipment analysed the results of his "move" and automatically made an answer to that move and thus enabled one person to "play" the machine. And, of course, such a machine could be so constructed that it could not lose but would always win or draw.

SUPERB COMMUNICATION RECEIVERS

AMERICAN AR8SD RECEIVERS. Fresh release of these renowned sets. 14 valves, 6 wavebands, covering 250 Kc/s-32 Mc/s. Incorporate every possible refinement and have internal A.C. mains pack for nominal 5/230 v. Thoroughly reconditioned, immaculate in appearance and in perfect working order. **ONLY £35** (add carriage 30/- and 50/- deposit on returnable transit case). S.A.E. brings illustrated leaflet.

MARCONI CR. 100/S COMMUNICATIONS RECEIVER. Covers 60 Kc/s to 30 Mc/s. Complete with all valves, makers instruction manual, and internal A.C. Power unit for 200/250 volts. **BRAND NEW IN ORIGINAL TRANSIT CASES.** Aerial tested before despatch. **ONLY £35** (carr. etc. 40/-). S.A.E. for full details.

TEST METERS FOR EVERY PURPOSE & POCKET




2,000 O.P.V. MODEL TP-10. Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 in. x 5 in. x 1 1/2 in.

£3.19.6



20,000 O.P.V. MODEL TP-5S. Reads voltage up to 1,000; D.C. at 20,000 ohms per volt and A.C. at 10,000 o.p.v.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in.

£5.19.6

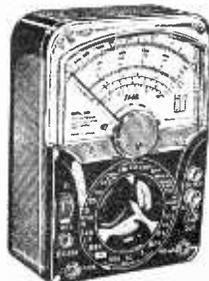

30,000 O.P.V. MODEL 500. Volts to 1,000; D.C. at 30,000 O.P.V.; A.C. at 20,000; 12 Amps D.C. Current; 60 Megs Resistance; -20 to +56 Dbs; Internal buzzer short circuit warning. Size 3 1/2 in. x 6 1/2 in. x 2 1/2 in.

£8.19.6

All New Stock, with leads, prods, and internal batteries. 6 months' guarantee backed by full service facilities. Details S.A.E.

AMPLIFIER TYPE A103. Ex R.A.F. For normal A.C. Mains use. 5Z4 Rectifications with 6V6 output. Input and output jack sockets, gain control, fully fused. 600 ohms output transformer easily changed for 3 ohms type. Standard rack mounting size 19" x 7" x 6". Used, good condition. **ONLY 59/6** (carriage etc. 10/6).

12 VOLTS AMERICAN DYNAMOTORS. Deliver 220 volts at 100 mA. Size 5 1/2 x 3 1/2 in. diameter. Ideal for running Electric Shaver etc. from Car battery. **ONLY 32/6** (post 2/6).

POWER UNITS TYPE 334. Primary 200/250 v. 50 cycles. Outputs of 250 v. 100 mA, and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 19" x 7". Fitted Input and Output Voltmeter, 79/6, or model less meter 59/6. (Carriage ether type 10/6.)


AVOMETER MODEL 7 LEATHER CASES, fitted with carrying handle and long strap, **BRAND NEW.** **ONLY 32/6** (Post 2/6).

PCR COMMUNICATION RECEIVERS

Manufactured by Pye W Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of I.F., using 6 British 10J type valves. Large 180 degrees illuminating and Calibrated Dial. Flywheel Tuning with locking device. Aerial Trimmer. Tone and Vol. Controls. Band switch from panel jacks for speaker or phones. In black metal case, size 17 in. L x 8 in. H x 10 in. D. Model PCR covers 6-18 Mc/s. 200-550 metres and 350-2,000 metres and has internal 5-in. speaker. **£8.19.6.** Model PCR has similar L & M waveband coverage. Short wave 6-22 Mc/s, but no speaker. Used but excellent condition **£5.19.6.** Ev ry receiver aerial tested before des. Add 10/6 carr. all models. Designed to operate from bulky EXTERNAL power supply, but any set can be fitted with **BRAND NEW COMPONENTS INTERNAL PACK** for 200/250 v. A.C. at extra cost of £2.

S.A.E. FOR ILLUSTRATED LEAFLET

"P.W." 6 TRANSISTOR PERSONAL RECEIVER

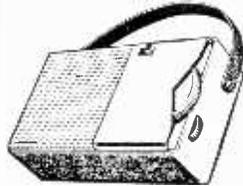

Designed by the technical staff of *Practical Wireless*: easy to build, using printed circuit and 1st Grade Matched Transistors and Diode. Full Medium and Long Wave coverage to internal speakers. All parts sold separately (new components only) enabling you to buy as required and full detailed price list will be sent on request. Constructional details 1/6.

Newly designed OSMOR Cabinet and reduced price. **TOTAL COST INCLUDING BATTERY AND CABINET NOW £8.10.0.** "P.W. TROUBADOUR 7" parts list. S.A.E.

THE "GOOD COMPANION" Mk. II

USING TRANSISTERS, THE LATEST MANUFACTURING TECHNIQUE TO SAVE ALIGNMENT DIFFICULTY THE FINEST COMBINED PORTABLE and CAR RADIO YET DESIGNED FOR THE HOME CONSTRUCTOR

★ 750 mW output.

★ 6 transistors and 2 diodes.

★ Full Medium and Long Wave coverage.

★ Quality speaker.

★ Brilliantly styled 2-tone cabinet, size 11 x 8 x 3 in.

★ Very fine tuning with calibrated dial.

★ Latest printed circuit. ★ Internal high gain aerial with car aerial socket. ★ Easy to follow construction data (available separately 3/6). All parts sold separately and full illustrated details will be sent on request.


£9.19.6.

Total Cost With alternative luxury cabinet using 7 x 4 in. speaker, **£10.19.6.** Either type, plus 5/- post and ins. (Battery 3/6 extra).

"POCKET 4"


TRANSISTOR RECEIVER

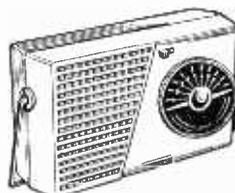Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components and case for only 42/6 (p. & p. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.



HARRIS ELECTRONICS 138 Gray's Inn Road, London, W.C.1
 (LONDON) LTD Phone TERminus 7937

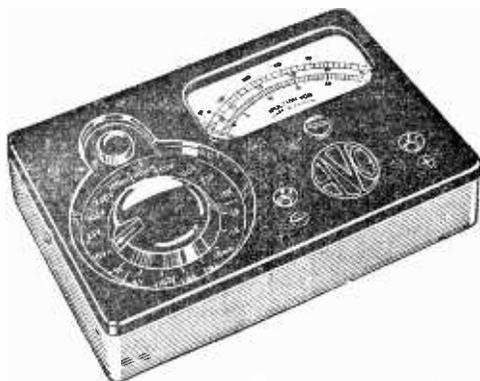Please include carriage costs on all items. (Open until 1 p.m. Saturdays). We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by Bus from King's Cross.



Indispensable

THE

MULTIMINOR

19 Ranges

D.C. Voltage: 0-1,000V in 7 ranges

A.C. Voltage: 0-1,000V in 5 ranges

D.C. Current: 0-1A in 5 ranges

Resistance: 0-20,000 Ω, 0-2M Ω

Pocket Size: 5½ x 3½ x 1½ inches.

Weight: 1 lb. approx.

List Price **£9 : 10s.**

Complete with Test Leads and Clips
Leather Case if required 39/-.

Sensitivity

10,000 ohms per volt on D.C. voltage ranges.
1,000 ohms per volt on A.C. voltage ranges.

Accuracy

On D.C. 3% of full scale value.

On A.C. 4% of full scale value.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.

Whether you're building your own amplifier or servicing a complete installation—for fault finding on anything from pre-amplifier to speaker—you'll find the MULTIMINOR to be "just right". You'll enjoy using this neat pocket instrument giving readings over nineteen ranges on a clear open scale. a.c. and d.c. voltage, d.c. current, and Resistance measurements are made by means of only two sockets. The robust, easy-to-read range selector has a smooth, clean, positive action.

"Can you afford it?" Let's say rather—"Can you really afford to be without it?"

Designed and Manufactured by

AVO LTD AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON - S.W.1
Telephone: VICToria 3404 (12 lines)



SPECIAL FOR THE "HAMS" RADIO STATION

Illustrated


½ inch detachable bit soldering instrument
List No. 70

Combined Protective Unit with Wiper/Abrasion Pad and Solder Reel
List No. 700

Apply **SALES & SERVICE**



ADCOLA HOUSE
GAUDEN ROAD
LONDON, S.W.4

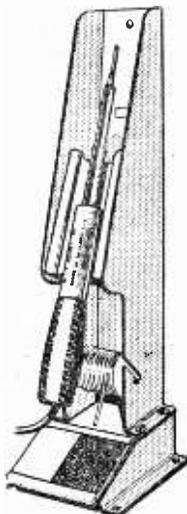

British & Foreign Patents, Registered Designs, etc.

Telephones: **MACaulay 4272-3101**

Telegrams: **"SOLJOINT, LONDON, S.W.4."**

P.W. BEST SETS A-Z 2/6

INSTRUCTIONS

OSMOR PRINTED CIRCUIT VERSIONS

OF

"P.W. POCKET S'HET"

"MERCURY SIX"

"TROUBADOUR"

WE MAKE UP NEARLY ALL P.W. DESIGNS AND ARRANGE SOME FOR PRINTED BOARD

COMPONENT LIST ON REQUEST

OSMOR
418 BRIGHTON ROAD
S. CROYDON



NAME

ADDRESS

POWER Rectifier Circuits

common and uncommon

By L. N. Nash

A SURVEY OF PRINCIPLES OF
PRACTICAL IMPORTANCE, AND
USES OF SUCH CIRCUITS

(Continued from page 308 of the August issue)

LAST month's article finished with an explanation of the advantage of the cascade voltage doubler circuit over the conventional voltage doubler circuit.

Fig. 21 gives an example of a combined H.T./EHT supply on these principles. A further advantage of this circuit is shown in Fig. 22, where the same circuit but of inverse polarity is added to the same transformer winding, in the same method of circuit development as the previous treatment of the other basic circuits. The result here is an output at *four times* the voltage output of a simple half-wave circuit, so that this circuit is called the "Cascade Quadrupler". These types of circuit are called "Cascades" on account of their cumulative method of working. Thus the first rectifier and condenser, MR1 and C1, function as a normal simple half-wave circuit, charging up C1 to the peak. On the half cycle of opposite polarity, where MR1 is now

blocked, polarities are such that the charged C1 and the reversed transformer winding voltage act in series addition as voltage drive for the second rectifier and condenser MR2, C2 also operating in simple half-wave circuit, thus clearly leading to a doubled voltage output. The operation of C3/MR2 and MR4/C4 follows similar lines.

Progressive Cascading

In principle, the charge voltage on C2 and the transformer voltage can be made to act in series across a further rectifier on the next half cycle, and so on up to any number of cascaded stages. Thus a D.C. output voltage of any desired multiple of the output of a simple half-wave circuit is possible with rectifier cascade-multipliers, without the need for any transformers. But such circuits are of little use to the constructor, because rectifiers and condensers of the large voltage ratings required are not commercially available.

It may be mentioned, however, that the rectifiers may be replaced by spark-gaps of graded separation, trimmed so that breakdown just occurs at the half-cycles corresponding to the maximum voltage, exactly where a normal rectifier would be required to conduct in such a circuit. This is an interesting example of the use of spark gaps in substitution for rectifiers, which has actually been used in historical equipment for high-voltage supply for atomic research. Generators with spark-gap cascades have been built with an output of well over a million volts, using a transformer winding input of some thousands of volts.

This completes the survey of those rectifier circuits considered to be of practical use to the experimenter. Many other interesting types, such


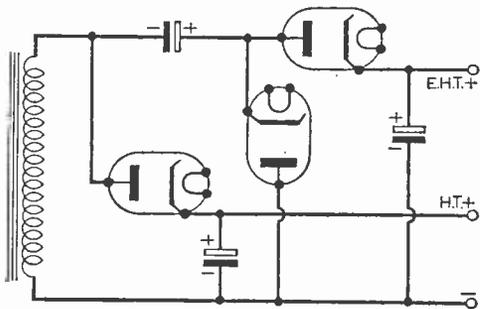


Fig. 21 (above)—Combined H.T./EHT circuit using the cascade voltage doubler principle.

Fig. 22 (right)—The cascade voltage quadrupler circuit. Transformer secondary 250V r.m.s.; rectifiers E250C50 selenium. Do not mount on the same metal chassis, as otherwise flashover inside the casing is likely. Use separate cooling plates of aluminium insulated from each other. (The values given are approximate.)

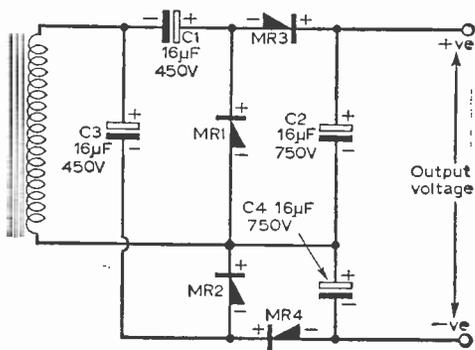

as three-phase and polyphase equipment, grid-controlled rectifiers, etc., are not considered to be of practical importance for the general experimenter.

Peaking and Smoothing

All rectifier circuits work into an output load through which the D.C. output current flows. In basic principle, this output load consists of a resis-

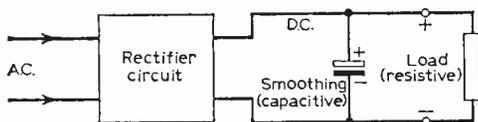


Fig. 23—Resistive and capacitive elements in parallel representing the output load.

tive element (the actual useful load) and a capacitive element (the "smoothing") in parallel, as shown in Fig. 23. Fig. 24 shows the more conventional smoothing, where the capacitive element is split at the "hot" end into two, and a choke or resistor inserted. This enhances the characteristic that the A.C. component of the output (hum ripple) goes preferably through the capacitive element to earth, whilst the true D.C. component goes through the resistive element (real load) to earth, which is the familiar purpose of smoothing—namely to remove as much as possible of the remaining A.C. component of the output.

Now, the capacitive element of the circuit of Fig. 23, as long as it is not charged to the final voltage, represents a short-circuit as soon as the

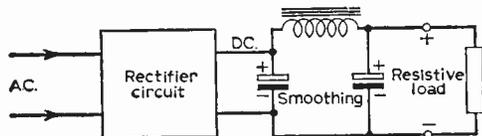


Fig. 24—Conventional smoothing.

transformer winding voltage has reached a part of the half cycle of the conduction-polarity where the voltage has risen above that to which the condenser is at the moment charged and charge current will then flow into the condenser to increase its voltage. It is thus perfectly obvious that this process goes on until the condenser has charged up to the peak voltage of the A.C. wave, which is about 1.5 times the r.m.s. value for the mains sine wave. This property of rectifier circuits is known as (capacitive) peaking, and raises the peak inverse voltage rating required for the rectifier, as explained earlier in this article. Even if no physical condenser is present, the circuit stray capacities, even if very small, are inevitably fully sufficient to give full peaking on open-circuit output, so that no reduction in inverse voltage rating of the rectifiers is permissible even if no physical smoothing condensers are used, as in common accumulator charging circuits.

Load Characteristics

The remarks regarding full peaking made in the previous section apply to open-circuit output, i.e.,

the case when the resistive component of the output load is of infinitely large resistance. As soon as a finite resistive component is connected, i.e. an actual pure D.C. output current is drawn, this will draw charge away from the smoothing condensers.

Thus, in actual practice, the final operating output voltage will be somewhat less than the full peak voltage, according to the balance struck between the load current passing out of the condensers and the rectifier current passing into them on the appropriate portions of the A.C. cycle. Zero output D.C. load results in full peaking, as explained above, and as the output D.C. load current increases the voltage will fall below the peak, the decrease being normally linear with rise of current in most circuits, which means that Ohm's Law is obeyed to the extent that a definite corresponding internal impedance may be ascribed to the circuit. This *internal impedance* lies in the region of about 1k to 2k for normal conventional full-wave H.T. rectifier circuits, so that a decrease of 1V to 2V may be expected in the output voltage for each rise of about 1mA of output current drawn. The actual exact figures in a particular case will depend greatly on the smoothing capacity values, rectifiers, resistances of transformer windings, etc. A good power supply should have as small a change of voltage with load current as possible, i.e. as low an internal impedance as possible.

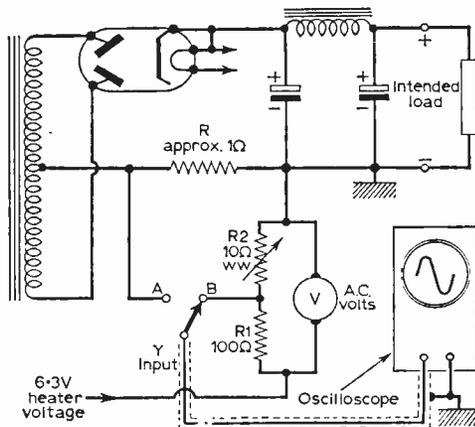


Fig. 25—Measuring peak surge rectifier current.

Condenser Values

Large values of smoothing capacities reduce the internal impedance, in that they keep the output voltage high at greater load currents, but this is at the expense of large surges of current through the rectifier at the A.C. cycle peaks, which exceed the surge-current rating of the rectifier for smoothing capacities larger than a critical value for a given circuit. Thus the use of too large a smoothing capacity can cause overheating and flashover in the rectifier.

Metal rectifiers, and especially the new silicon rectifiers, can tolerate higher peak currents than normal valve rectifiers. This is a great advantage of these devices, and allows the use of much larger

smoothing capacities, which is very useful in half-wave circuits requiring the extra smoothing effect. It is extremely difficult to determine the maximum tolerable smoothing capacity on theoretical lines if one is about to try out a new rectifier circuit of one's own design, but fortunately it is a simple matter to measure the peak rectifier current in an experimental circuit if one possesses an oscilloscope and an A.C. voltmeter. Fig. 25 shows the arrangement for such a measurement, as typically applied to a conventional full-wave H.T. rectifier circuit. The normal load which the circuit is intended to feed is connected, and the small measuring resistor of about 1Ω (the resistance (R) of which must be known accurately) is connected as shown. It does not disturb the function of the circuit appreciably, serving merely to monitor the rectifier current.

The oscilloscope input is now connected to A, and the trace adjusted to suitable height and the timebase to display a convenient number of cycles. The waveform will not be a sine wave, but will display the regular current surges through the rectifiers. Without altering any settings of the oscilloscope controls, the oscilloscope input is now switched to B, and R2 adjusted until the mains sine wave display has exactly the same peak to peak amplitude as the peak to peak amplitude of the rectifier current display. If V is the reading of the A.C. voltmeter, then the peak rectifier current is given by

$$I_{\text{peak}} = \frac{V}{R} \times \frac{3R2}{R1 + R2} \text{ Amps}$$

(Resistances in Ohms)
(V in Volts r.m.s)

The data list should then be consulted to check whether the measured peak current is within the surge-current rating of the rectifier in use. If not, then the smoothing capacity must be reduced, the load current reduced, a different rectifier type used, or a surge limiting resistor or choke inserted (Fig. 26), or any suitable combination of such measures. If one were very careful in the design of circuits, the initial surge currents through the rectifiers as the condensers charge up from zero upon initially switching on would also be studied.

Surge Limiters

If the initial surges are found to exceed the rating of the rectifiers, then the same measures as indicated above can be used, though the best measure in this case would be the use of surge-limiter resistors or chokes. There is in principle a choice of three positions for such components, as illustrated in Figs. 26 a, b, c. Fig. 26a is normally used if resistors are used, whereas Fig. 26b is common if a choke is used, whereas Fig. 26c is seldom found.

There is not a great deal to choose between the three arrangements, the particular preferences being largely a matter of convention. Fig. 26b represents the familiar choke-input smoothing circuit, which has the characteristics of a very rapid initial fall of output voltage away from the full peak at low output currents, but thereafter far slower fall of output voltage with output current in the region of the operating value of output current (assuming proper choice of component values). The result is that such a smoothing

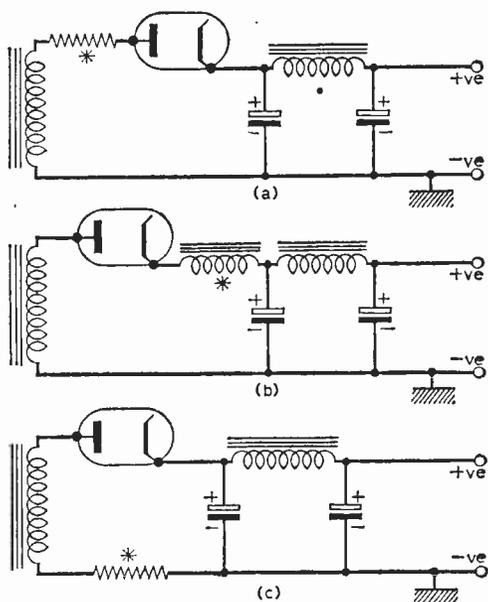


Fig. 26—The three positions for surge limiters.

circuit gives a smaller output voltage at a given load than the conventional smoothing circuit of Fig. 24, but the effective internal impedance is lower, i.e the regulation is better.

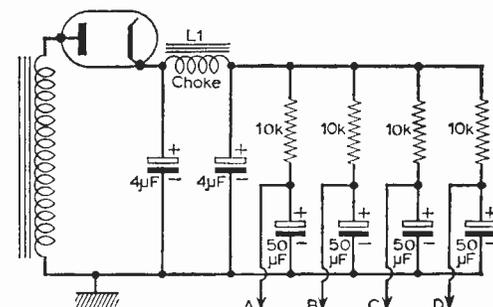


Fig. 27—This circuit provides decoupling and smoothing in one, and avoids unnecessarily large rectifier surge currents.

High Ratings

It should be mentioned that the use of television booster diodes as power rectifiers, in addition to advantages already discussed, has the further advantage of high surge-current rating. This is because these diodes are specially designed for pulse-operation in television line-output circuits, and therefore are fitted with excellent high-emission cathodes. Thus the PY81 is rated at a peak surge current of half an amp. so that with a 400V r.m.s. transformer winding giving a peak voltage of 600V forward, the surge-limiting resistance would only need to be at the very most about 1000Ω . The

(Continued on page 438)

A HOME-MADE HI-FI OUTPUT TRANSFORMER

BY W. GROOME

THE USE OF A TERTIARY FEEDBACK WINDING ARRANGEMENT SIMPLIFIES THE CONSTRUCTION OF THIS TRANSFORMER AND REDUCES THE COST.

PRICES of quality output transformers are still high enough to deter the experimenter who has economy in mind, particularly when the cost has to be doubled for stereo. Substitutes bring distinct risks of trouble with published designs, a fact which emphasises the importance of considering transformer and amplifier circuit side by side. Despite this cautionary remark, the transformer to be described will be found to be stable in several circuits and will provide the basis for some interesting, inexpensive experiments.

Sections

The number of winding sections is small and their arrangement simple enough for home workshop methods and yet the transformer does not

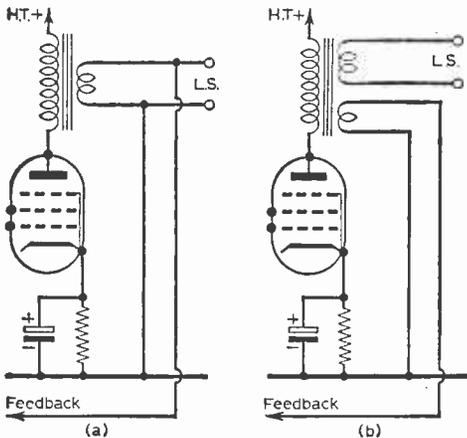


Fig. 1a—Voice-coil feedback circuit; b—tertiary feedback circuit.

lend itself to factory production, possibly because it requires a centre-partitioned bobbin and a "stop-and-start" procedure unsuitable for automatic machinery. Therefore, despite its advantages of small size, simplicity, cheapness and high-quality performance, it is not likely to appear in the shops.

The achievement of stability in an amplifier having overall feedback generally demands a complex sectionalised winding arrangement in the output transformer. A successful alternative for the small amplifiers which, in stereo pairs, can supply a total of about 10W output, is to operate

the output stage safely within class "A" conditions so that small and simple transformers can be used. Another method is to apply heavy negative feedback over the output stage to clean up distortion at its principal source, thereby reducing somewhat the risks of instability with the voice-coil loop.

Separate Feedback Winding

A further arrangement is the provision of a tertiary (third) winding to supply a

Fig. 2 (right)—A push-pull output transformer with tertiary windings (T).


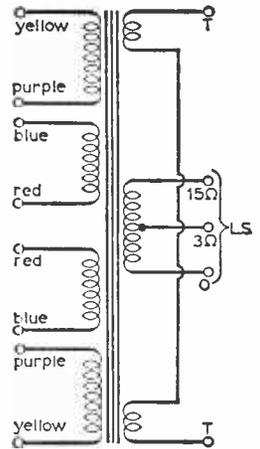


Fig. 3 (below)—Each anode winding is confined to one side of the partition and divided into two sections separated by the secondary. The secondary and tertiary are wound across the full width of the former.

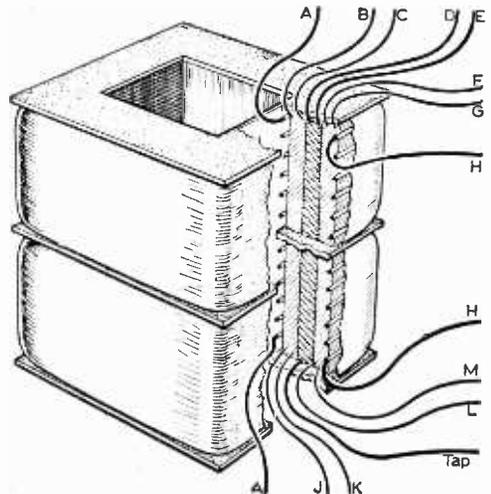- AA Tertiary, one layer, full width;
- BC Primary, inner section, one side of the partition;
- DE Secondary, full width;
- FG Primary, outer section, one side of the partition;
- H Tertiary, one layer, full width;
- JK As BC;
- LM As FG.



feedback voltage that suffers none of the distortions to which voice-coil connections are prone. It becomes possible to apply very heavy feedback without the sectionalising normally required. This is the basis of this transformer. To obtain the greatest versatility, the windings are so arranged and insulated that the leads, which are all brought out instead of being internally connected, provided a choice not only of turns ratio but also of output stage conditions and feedback circuits.

Fig. 1 shows in the simplest forms (a) the conventional feedback circuit and (b) the tertiary arrangement. A very simple tertiary winding would seem to be possible by wrapping the very few necessary turns around the outside of any transformer winding. This can be tried and the transformer may be found to behave reasonably well, but the feedback will be out of balance and some distortion is certain. A virtual replica of the anode signal can be obtained when the tertiary is divided into two single-layer sections in series, one on the inside of the bobbin and the other on the outside. It is also preferable, and easily arranged, to have a balanced primary having the winding for each valve of a push-pull pair kept to its own side of a partitioned bobbin. This not only gives excellent push-pull conditions but balances the D.C. supply and the resistive component of the A.F. load.

Tertiary Sections

The arrangement adopted has both primary windings divided into two sections, each pair on its own side of the partition with the secondary

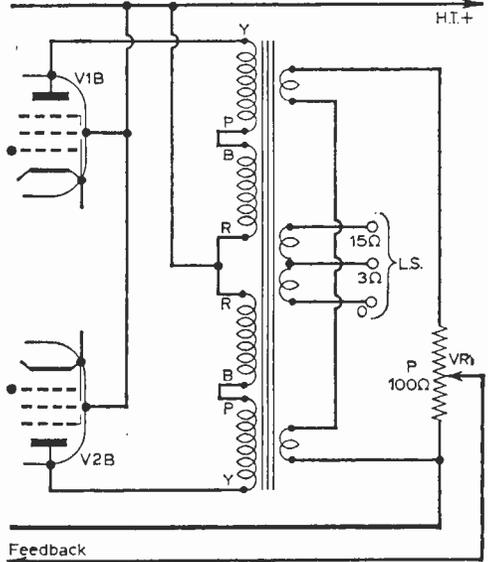


Fig. 5—The method of obtaining variations of gain and feedback by the potentiometer (P) placed across the tertiary windings.

as a single section wound across the full width and tapped for alternative loudspeaker impedances. The tertiary sections comprise only


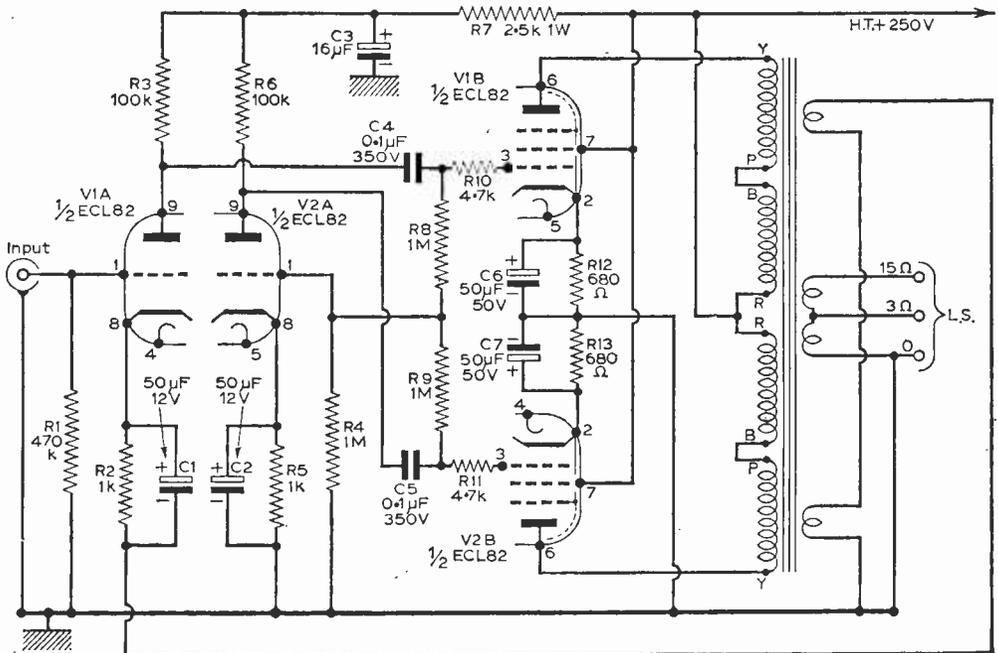


Fig. 4—The circuit of a two-stage push-pull amplifier.

twelve turns each, spaced across the full width. The arrangement of the sections is shown schematically in Fig. 2, with colour identification that will be used throughout this article and the one which follows. Fig. 3 will give some idea of the actual positions of the sections.

No rigid specification for core dimensions and quality will be given because of the difficulty of obtaining laminations of any particular size and

is good and there seems to be little to gain by dividing the windings into the many sections found in the usual high quality job. Nevertheless, for the very finest quality, a generous stack of good quality laminations should be provided. In a 10W amplifier very fine bass down to 30c/s is possible with a 1½in. stack; a ¾in. stack gives excellent results in a stereo amplifier giving about 6W per channel.

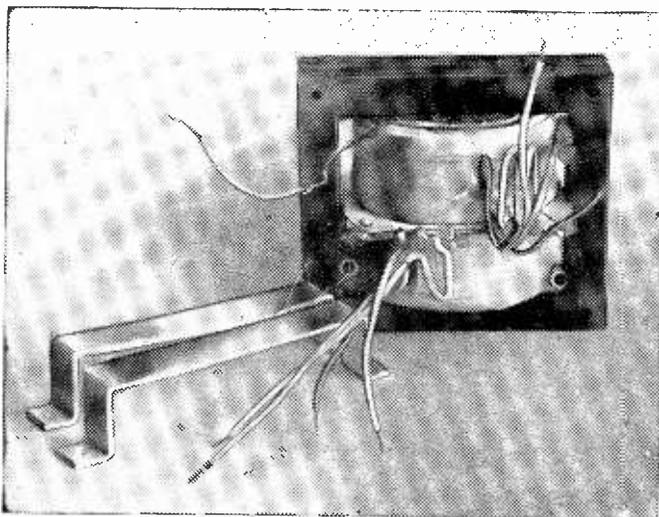

One of the author's experimental transformers.

grad in the shops. Instead, some guidance will be offered to enable the constructor to use the best he has or can obtain and to adjust the windings to suit. A feature of the transformer is that it is tolerant in this respect, and good results can be achieved with cores rather smaller than might be needed with others. High frequency response

simple local loops can be more effective and stable.

In Fig. 4, a triode "see-saw" phase-splitter and amplifier stage feeds the output pentodes. The tertiary winding, earthed one end, supplies feedback to V1 via R1 and provides a path for the cathode current.

(To be continued)

INCREASING VOLTMETER RANGES (Continued from page 388)

The multiplier must take $500-0.05=499.95V$. Its resistance will therefore be:-

$$R = \frac{E}{I} = \frac{499.95}{1/1,000} = 499,950\Omega.$$

Such a multiplier can most conveniently be made by connecting 470,000, 22,000, 7,000, 820, 100 and 30Ω resistors in series. Taps can be arranged for 250, 100 and 10V or other such ranges, calculated in the same way.

The multiplier in circuit at 500V is 499,950Ω, at 250V is 249,950Ω, at 100V is 99,950Ω, and at 10V is 9,950Ω.

The Voltage Divider

Valve voltmeters and oscillographs have a different multiplier system. Fig. 4 illustrates the arrangement. R is known as a divider. The valve voltmeter is connected to a small portion of R and therefore measures only a fraction of the voltage under test. R is usually made up of several high resistances connected in series giving

a total value of about 20M. It is essential to have R as high as possible in order to maintain the sensitivity of the valve voltmeter.

In Fig. 4 the total value of R is 20M. Therefore on 1,000V it will pass:-

$$I = \frac{1,000}{20,000,000} = 1/20,000A = 0.05mA$$

The valve voltmeter reads one volt at full scale deflection. Therefore the resistance between b and c will be:-

$$R = \frac{1}{1/20,000} ; = 20,000\Omega.$$

The resistance between a and b will, of course, be the difference between 20,000,000 and 20,000 = 19,980,000Ω. Tappings can also be arranged between the various components of R to give, say 500, and 250V ranges. In Fig. 4 the resistors are as follows: b to c=20,000Ω, b to 250V tap=4,980,000Ω, 250 to 500V tap=5,000,000Ω, and 500 to 1000V tap=10,000,000Ω. ■

WHAT READERS SAY ABOUT

THE *Common* *Core* SERIES

COMMON-CORE

ILLUSTRATED COURSES OF ELEMENTARY TECHNICIAN TRAINING

"... Wish to congratulate you for publishing one of the best-ever series dealing with this complex subject..."

"... Your books seem to explain things much more easily. I wish they were on sale when I had to learn radio..."

"... Having obtained the two volumes of 'Basic Synchros & Servomechanisms' I find them very interesting and a novel way of learning..."

"... As a lecturer I am finding these of great assistance and congratulate you on publishing such excellent books..."

"... I am writing to tell you how much I enjoyed reading your 'Basic Electricity' and 'Basic Electronics'."

"... I have all the previous sets, namely: 'Basic Electricity', 'Basic Electronics' and 'Basic Synchros & Servomechanisms' and will mention that it's truly one of the best I've studied..."

"... I have found 'Basic Electricity' and 'Basic Electronics' excellent publications..."

"... I have been supplied with some of the above publications, and needless to say I am delighted with them..."

BASIC ELECTRICITY (5 PARTS)

BASIC ELECTRONICS (6 PARTS)

BASIC SYNCHROS & SERVOMECHANISMS (2 PARTS)

ALL THE ABOVE ARE ON SALE NOW

BASIC RADAR (3 PARTS)

PART 1 ON SALE NOW. PARTS 2 and 3 IN PREPARATION

BASIC ELECTRONIC CIRCUITS (3 PARTS)

PART 1 ON SALE NOW. PARTS 2 and 3 IN PREPARATION

COUPON - SEND NOW!

OR ASK YOUR BOOKSELLER

To THE TECHNICAL PRESS LTD.

112 Westbourne Grove, London, W.2.

Please send me your FREE prospectus describing:—

BASIC ELECTRICITY/ELECTRONICS/
SYNCHROS

BASIC RADAR/ELECTRONIC
CIRCUITS

(Please put a X against your requirements).

NAME _____

ADDRESS _____

PW

Home Constructors LOOK!

TRANSISTOR KITS 'JUNIOR MkII'

TRANSISTOR
POCKET
RADIO

OUR IMPROVED
VERSION OF
THE 'JUNIOR 5'

NOW SUPPLIED COMPLETE WITH PRINTED CIRCUIT BOARD AND FREE GIFT OF MINIATURE EAR PHONE. An easy 'first step' set for the young constructor. This miniature marvel with the BIG performance has an internal Ferrite rod aerial—5 transistors and 1 diode—separate medium and long waveband control—200 milliwatt push-pull output—2in. moving coil speaker—unbreakable plastic case with carrying handle. Complete with full instructions. Circuit diagram 1/6, free if all parts bought. All parts sold separately.

£2.19.6

P. & P. 2/-

THE SUPER 'SONIC SIXTY' TRANSISTOR RADIO KIT

6 Mullard transistors, 1 diode, internal ferritised aerial, 7 x 4 high quality speaker, printed circuit, 500 mW push-pull output, 1.5W and LW calibrated direct drive assembly. Highly polished handsome walnut cabinet. Inst. Book 2/6 Complete kit, inc. Battery. All parts sold separately.


£8.19.6

P. & P. 4/6

TRANSISTOR AMPLIFIER

COMPLETE WITH 3in. MOVING COIL SPEAKER

49/6

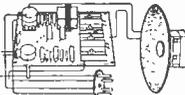

P. & P. 2/-

1 watt full transistorised Amplifier. Incorporates 2 power Transistors and 3 G.E.T. 114 Transistors in push-pull—complete with separate tone and volume controls on 2 1/2 x 4in. printed circuit board. Operates from Ever Ready P.P.11 Battery. Suitable for use with the Star Galaxy Player.

THE PETIT FULMITER


A.C. ELIMINATOR AND 9V. BATTERY CHARGER **18/6** P. & P. 1/6



Converts your Miniature Transistor Set to Mains for the winter and charges your Battery for summer use outdoors; for use with all 9V. Transistor Receivers (approx. same size as P.P.3 battery). Complete with Rex.

Wirecomp's Finest Ever Value Offer— THE 'REALISTIC 7'

FULLY
TRANSISTOR-
ISED PORTABLE
RECEIVER

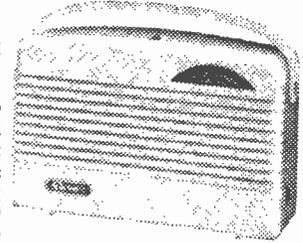

This super set—made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC44, 2 OC45's, OC71, OC81D, and 2 OC81's, plus OA70 Crystal Diode. Delivers 350 milliwatt output to 4in. high flux speaker—1F frequency 470 Kcs.—fully tunable over medium and long wave-bands. All components mounted on single printed circuit board, size 5 1/2 x 5 1/2in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3 1/2in. with easy to read dial and socket for car aerial; choice of Red/Grey, Blue/Grey or all Grey. Complete with full instructions. All parts sold separately.

WIRECOMP'S PRICE **£6.19.6** Including Free P.P.9 Battery — Value 3/9

P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought).

WIRECOMP ELECTRONICS

387 HARROW ROAD, LONDON, W9.

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital. Buses 18B and 36 pass the door.

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS IR5, IS5, 174, 354, 3V4, DAF91, IDP91, DK91, DL92, DL94 ... Set 4 for: 19/6 4 for 27/6

OA2 11/6	6LD20 8/-	30P19 14/6	EBL21 13/6	EZ40 6/9	U25 12/-
1A7GT 11/-	6P1 7/-	30PL13 12/3	ECC40 13/6	EZ41 7/6	U26 9/3
1D5 7/6	6P25 8/-	35A5 15/9	ECC81 5/-	EZ80 6/3	U50 6/-
1N5GT 9/-	6P28 12/-	35L6GT 8/3	ECC82 6/3	EZ81 6/6	U52 4/6
1R5 8/6	6Q7G 8/-	35Z4G 5/6	ECC83 7/7	KT33C 8/6	U78 4/6
1S4 9/-	6Q7GT 8/-	35Z5GT 8/3	ECC84 8/3	KT4 5/9	U191 14/6
1S5 5/3	6SL7GT 5/9	50L6GT 9/-	ECC85 7/9	RT44 5/9	U281 17/-
1T4 5/6	6SN7GT 4/9	85A2 11/6	ECC86 7/6	KT61 6/6	U291 16/6
1U5 5/9	6U4GT 9/9	AZ31 9/6	ECC87 8/6	KT63 6/6	U301 17/-
3A5 9/-	6V6G 4/6	B36 7/6	ECC82 13/6	MU14 6/5	U801 21/-
3Q4 7/-	6V6GT 8/-	L33 12/3	ECH35 7/3	N18 7/-	UABC80 6/6
3S4 6/-	6X4 4/6	DC32 9/-	ECH42 8/9	PC95 10/-	UAF43 8/3
3V4 10/-	6X5GT 5/6	DAC32 9/-	ECH81 7/9	PC97 10/-	UB41 8/6
5U4G 4/6	7B6 9/-	DAF91 5/3	ECH83 8/6	PCC84 7/6	UDC41 7/9
5V4G 8/9	7B7 7/6	DAF96 7/6	ECL80 7/6	PCC89 9/3	URF80 8/3
5Z3GT 6/-	7C5 7/6	DCC90 9/-	ECL82 9/6	PCP80 7/9	URF89 8/-
5Z4G 9/-	7C6 7/6	DF33 9/-	ECL86 15/-	PCP82 8/6	UCC84 13/3
6AL5 3/8	7H7 7/6	DP91 3/6	EF35 4/6	PCP85 14/-	UCF85 7/6
6AN8 3/6	7S7 9/-	DP96 7/6	EF40 11/6	ICL82 9/-	UCF89 14/6
6AQ5 6/-	7Y4 6/-	DH76 4/6	EP41 4/6	PLC83 1/6	UCH21 13/6
6AT6 6/-	10C2 16/6	DH77 6/-	EP42 8/9	PCL84 10/-	UCH42 8/-
6BA6 5/9	12AT6 7/-	DH81 9/-	EP80 4/9	PCL85 10/6	UCH81 8/9
6BE6 5/9	12AT7 5/-	DK32 11/-	EP85 6/6	PENA4 11/-	UCL82 9/9
6BH6 5/9	12AU7 6/3	DK91 6/-	EP88 9/-	PEX39C 8/-	UCL83 13/3
6BJ6 5/9	12AX7 7/-	DK92 7/6	EP89 7/6	PL36 11/6	UF41 7/6
6BR7 9/6	12K7GT 4/9	DK96 7/6	EF91 3/6	PL81 8/6	UF89 7/-
6BW6 8/-	12K9GT 9/6	DL33 8/6	EF92 3/9	PL82 7/6	UL41 8/6
6CD9G 27/3	12N7GT 4/9	DL35 9/6	EL33 9/6	PL83 7/6	UL84 6/6
6F1 10/-	12SN7GT 8/-	DL42 6/-	EL41 9/6	PL84 8/6	URIC 8/-
6F8G 6/6	12Z3 10/6	DL94 7/-	EL42 9/-	PX4 10/-	UY2 11/6
6F13 10/-	20F2 17/-	DL96 7/6	EL41 12/-	PX25 9/-	UY41 8/6
6F14 10/-	20J1 16/-	EABC80 5/6	EL84 6/6	PY32 1/6	UY85 6/6
6F23 10/-	20P3 20/-	EAF42 8/9	EM34 7/3	PY90 7/6	VP4B 9/6
6K7G 1/11	25A6G 8/-	EB91 3/6	EM80 8/9	Y81 7/-	VP41 5/-
6K8G 5/-	25L6GT 7/-	EB93 3/6	EM81 8/9	Y82 6/6	VP1321 16/6
6K8GT 9/-	25Z4G 8/6	EBF80 8/-	EM84 9/6	Y83 7/9	W79 4/9
6L8 10/-	30L15 11/-	EBF89 8/9	EY51 7/6	T41 7/9	W79 4/9
			EY96 7/9	U22 7/3	Z77 3/6

FIRST-CLASS RADIO COURSES ...

GET A CERTIFICATE!
QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 461), 148 HOLBORN LONDON, E.C.1
S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL LONDON, N.16 STA. 4587

SERVICING TAPE RECORDERS

PROGRAMME SOURCES AND SIGNALS

By T. S. Smith

LAST month we dealt with record and replay equalisation and discovered how a reasonably flat overall frequency response can be obtained by applying controlled treble lift on record and bass boost on replay. This month we shall be considering the various programme sources and signals used by the home recordist.

Recording from the Radio

The radio is undoubtedly the most used source of programme material exploited by the amateur but, unfortunately, full advantage is not always taken of this medium and consequently the quality of reproduction may be sadly lacking.

The easiest way of getting a radio recording is to site the microphone in front of the loudspeaker and record in the usual manner. Although the results so obtained are acceptable to some, this is a very poor method of recording technically and far better results are possible by the use of other methods. With the loudspeaker/microphone method, three basic distortions are introduced to the recorder, and these are: (i) the inherent distortion in the output stage of the receiver (even the best sets produce some distortion in the output stage); (ii) the distortion and coloration produced by the loudspeaker itself and by its baffle or enclosure; and (iii) the distortion, reverberation and coloration reflection reflected from the room.

The first kind of distortion is present always and cannot be reduced or eliminated; (ii) is, again, always present and depends much on the loudspeaker and enclosure employed by the receiver; (iii) however, can be varied to some extent by playing with the spacing between the loudspeaker and microphone and by cutting out excessive reverberation by covering the channel between the loudspeaker and microphone with a heavy cloth.

The loudspeaker/microphone channel is virtually an electro-acoustic transducer, in which there are two distortions to contend with: the "electro" distortion and the acoustical distortion, as already described.

Eliminating the Acoustics

It is rather pointless to use the A.F. signal produced by the set to operate a loudspeaker, and for this loudspeaker to cause the diaphragm of a

(Continued from page 315 of the August issue)

microphone to vibrate in sympathy, and then to use the signal produced by the microphone for recording (see Fig. 25). By far the best idea is to utilise the A.F. produced by the set as the recording signal (Fig. 26).

This, then, presents several problems; the best way of extracting the A.F., etc. The obvious arrangement is to disconnect the loudspeaker and apply the two loudspeaker wires to the input of the recorder. This, although obvious, is a bad thing to do for several reasons. One is that as soon as the loudspeaker is disconnected from the set, the output stage is operating without a load. This immediately introduces quite a lot of extra distortion, but not only that, it also causes the A.F. voltage to rise to dangerous peaks at the anode of the output valve and across the primary of the output transformer. Before very long either the valve would flash over or the primary of the transformer would short-circuit or break down.

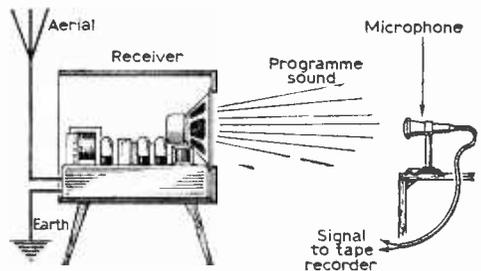


Fig. 25—The simplest way of recording from the radio is to site the microphone in front of the loudspeaker. This is technically poor, however, since there are various distortions introduced to the programme signal as this diagram shows.

If this method of feeding is to be used, then it is essential for either the loudspeaker to remain connected or a resistive load to be used instead. The resistive load should have a value equal to the impedance of the loudspeaker, which, in most ordinary valve-type receivers, is of the order of 3Ω . With transistor receivers, the impedance may be entirely different and in some cases the loudspeaker speech coil may be centre-tapped, in which case special precautions will have to be taken to prevent damage to the output transistors.

Where possible, it is best to operate without the loudspeaker for, apart from the disturbances created by a watt or so of audio during a recording exercise, the varying impedance with frequency of the loudspeaker can detract from the quality of the recording and, in certain cases, upset the equalisation. When a resistor is used instead, it should be able to handle the full output power of the set or amplifier hook-up. As 3Ω resistors are rather difficult to come by, a length of resistance wire (available almost anywhere) wound round the body of a ceramic high-value resistor, and terminated at the lead-out wires, is adequately suitable for this application.

Voltage and Matching

Next things to consider are the signal voltage required at the input of the recorder to give full modulation without overload, and the impedance matching between the output of the set and the input of the recorder.

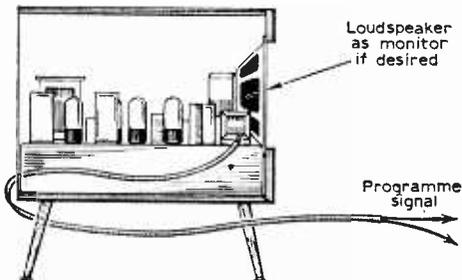


Fig. 26—If the A.F. signal is taken from the loudspeaker circuit, the loudspeaker must be left connected or a load resistor equal to the impedance of the speaker, must be connected instead.

Voltage Considerations

Tape recorders usually have two (or more) inputs, one for microphone and the other for radio. The microphone input is usually more sensitive than the radio input. This is because the voltage at the output of a microphone is much below that available from a radio set. Typical levels for full modulation are: microphone 1mV and radio 100/150mV. Sometimes there is a second radio input suitable for low-level signals direct from the diode detector, but this will be considered later.

The question, then, is what sort of voltage is present at the loudspeaker leads of an average radio set? This depends very much on the impedance of the loudspeaker circuit and the output of the set. The voltage is easily found, however, for any set, by using the simple expression $E = \sqrt{W \times R}$, where E is the r.m.s. output voltage W the watts output and R the impedance of the loudspeaker or load resistor in ohms.

A typical set, for example, might be giving, say 3W across 3Ω . Three times three is nine, and the square-root of nine is three. Thus, it follows that, at full output, 3V r.m.s. exist across the loudspeaker load. This is well above the input signal required on most recorders, so the signal is either turned down at the set (set's volume control) or at the recorder—but this can cause trouble. For

example, say the radio is turned up to nearly full output, using a resistive load instead of a loudspeaker, so that 3V peak are applied to the recorder. This will mean that the record level control will have to be turned well back to avoid overmodulation as indicated on the modulation depth indicator. Indeed, under such conditions the record level control will only be a fraction on.

Now, although the modulation or record level indicator will be showing that overloading is not apparently taking place, the recording will almost certainly be very poor indeed. The main reason for this is not so much a question of matching, but one of overloading in the first stage. The recording level control is usually connected *after* the first valve, so the first valve is receiving a full 3V of A.F.! It cannot handle that, of course, and distortion will occur, the distortion being controlled, in terms of recording level, by the level control after the amplifier.

The Best Settings

The best way of setting up such a combination is, first to turn on the recording level control almost to maximum, then turn up the radio volume control for maximum record level as indicated. In

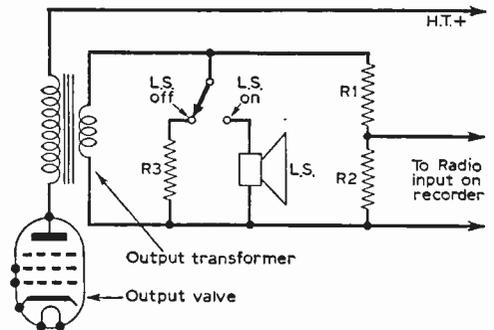


Fig. 27—This circuit shows a "loudspeaker on/off" switch, a dummy load R3 and an attenuator R1 and R2. The attenuator ensures that the first stage of the recorder is not inadvertently overloaded and also gives a theoretically better match between the set and the recorder.

that way the first stage of the recorder will always work well below the distortion level, but difficulty may be had in obtaining a sufficiently low setting of the receiver's volume control—a slight touch being sufficient to push the recording level indicator well over the limit. Also, if the receiver's loudspeaker is to be used as programme monitor, the low volume control setting will not give sufficient output, bearing in mind that only 0.001V or so is required to drive fully the recorder and that this corresponds to very little audio power across 3Ω .

Attenuation


Thus, an attenuator is a good thing to have between the set output and the tape recorder input. This will enable the set to be operated at near normal volume without overloading the first stage

(Continued on page 418)

Servicing the P.W. POCKET SUPERHET RECEIVER

SERVICING DATA FOR
THIS POPULAR PRACTICAL
WIRELESS DESIGN

By F. G. Rayer

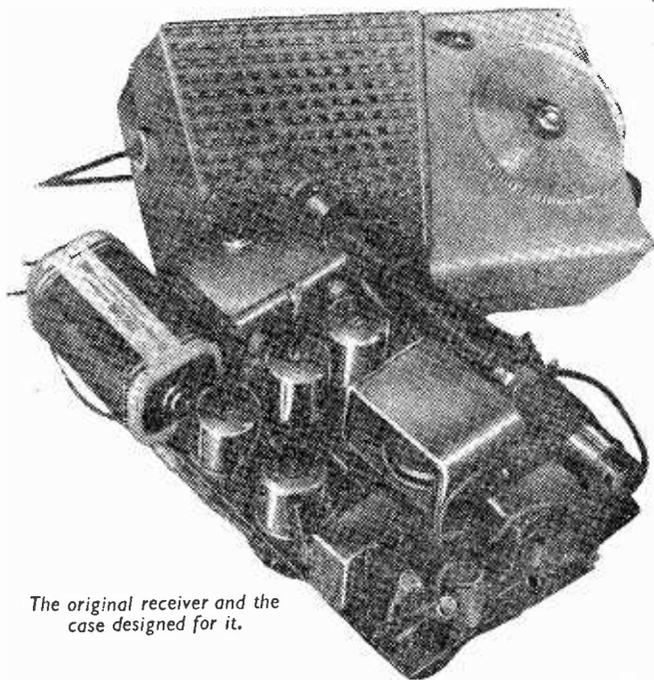

The original receiver and the case designed for it.

THIS receiver, the blueprint of which was presented with the November 1960 issue of PRACTICAL WIRELESS, is capable of very good results indeed, but errors in component values, or in the placing of components or wiring, may introduce difficulty. The use of transistors or other alternative parts, of different type from those specified, can also influence results. Where slight modifications have been made, to use items to hand, or for other reasons, it should still be possible to obtain satisfactory results.

The servicing details given here apply to the circuit and construction given on the blueprint, and the circuit is given again in Fig. 1 for easy reference. There are also a few constructional points.

Results Expected

It is not easy to give an anticipated standard of results, as these depend to some extent on local conditions. If the set is used in average conditions, and not in a screened locality such as a vehicle or metal building, about thirty stations should be heard at sufficient loudspeaker volume, on the M.W. band, during evening. On the L.W. band, about three stations should be received.

Local stations, and a few stations which come in at best strength, should give ample speaker volume with the volume control only advanced

by a quarter revolution, or less.

Speech and music should be of pleasant quality, from low volume right up to ample volume for ordinary listening in an average room.

Battery Space

The unused tags of C1 and C2 should be bent in against the condenser. A round body battery such as the Vidormax T.6004, will fit more easily than a square battery. The IFT2 can safely be positioned a little more to the right, and larger battery clips can then be accommodated. Neither clip must touch the IFT can. To avoid this, a piece of thin card, about 2½ in. x 1 in. may be bent to isolate the battery from the IFT and C1 and C2.

If a trifle more space is needed the tuning condenser can be moved slightly higher by elongating the holes in the paxolin. This can be carried out with a small round file. The T.6004 battery should fit without need for this, unless the holes for the securing screws have been drilled a little inaccurately.

Waveband Coverage

This is about 200-525m on M.W. and 1100-1750m on L.W. A high minimum capacity in the trimmer C3 will prevent 200m from being reached. If so, the spacing between the trimmer plates needs increasing. This can be done by unscrewing the trimmer and bending up the plates with a knife, taking care not to break the insulation.

Stray minimum capacity should be as low as possible, so leads to C7 and C8, and the switch, should be clear of the condenser frame, or earthed wiring.

Trimming can be on 208m (Radio Luxembourg) with the audio gain control at maximum, the set being oriented to keep volume low. Failure to tune to a sufficiently low wavelength indicates that the trimmer is screwed down too much, or that stray capacity is too high.

If signals at about 525m cannot be reached, with the tuning condenser closed, this probably indicates that the oscillator coil core is not screwed into the coil far enough. Even half a turn on this

core will considerably influence band coverage. If C8 is abnormally low in value, this will have the same result.

On the L.W. band, 1500m (Light Programme) should be found near the middle of the L.W. range. If not, C7 may be too low in value, or the oscillator coil core may not be screwed in far enough. If C7 is too low in capacity, wiring a 60pF trimmer in parallel with it will correct this. Adjust C4 near 1200m and the position of the L.W. winding on the rod near 1700m. Poor L.W. reception may be caused by wrong wiring to the L.W. winding tags, switch, or C7.

Complete failure of the oscillator stage to work, with a set just constructed, may arise from wrong oscillator coil positioning. There is electrical continuity between pins 1 and 2, between pins 3 and 4, and between pins 5 and 6. If this is not so, remove the coil, turn it as necessary, and replace it.

Noisy Reception

Receiver background noise should be very low. If high, a transistor may be responsible. Reputable transistors of named make will have passed a low noise test, but cheap or surplus transistors may be noisy.

Noise from defective soldered joints may be found by examination, by moving suspected leads carefully with an insulated tool, or by checking each stage individually. It takes only a moment to "tin" the leads of resistors, etc., by applying the iron and cored solder. If this is always carried out, no joint should be defective.

I.F. Oscillation

Instability in the intermediate frequency amplifier may be heard as a whistle or similar noise. It may arise from wrong values for R7 and R11, or C10 and C13, which should be of 2% tolerance. Very long leads to Tr2 and Tr3 may contribute, and base and emitter wires should not be close together.

If the trouble ceases on tuning in a strong station, it is very slight. If it ceases only on detuning one or more I.F. transformer, check that wiring is short and direct. Increasing the values of C11, C12 and C14 may help. This is most easily done by adding other condensers in parallel to a total of 0.1μF or 0.25μF.

Current Drain

A meter included in one battery lead should read approximately 8mA, with no programme

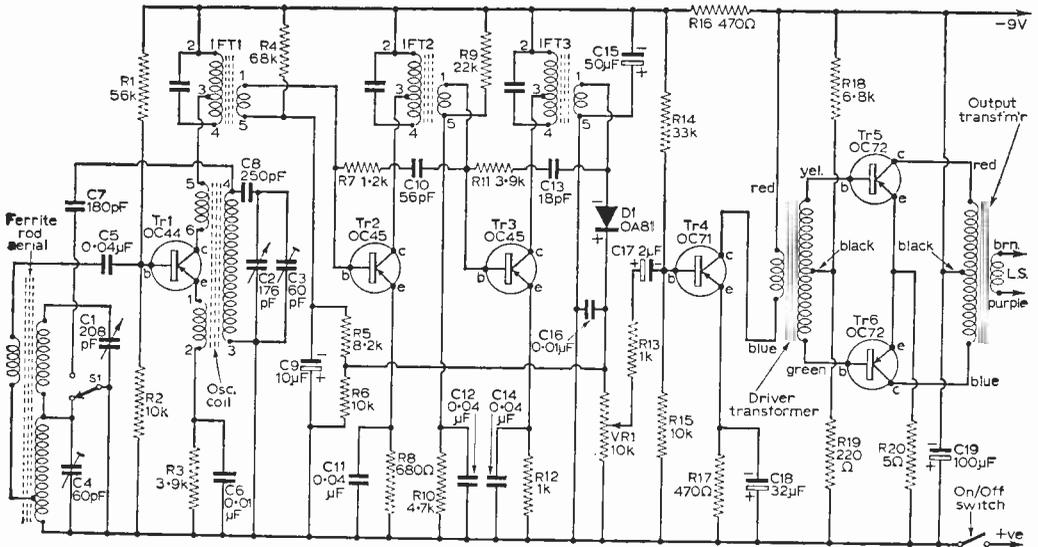


Fig. 1—The original circuit of the pocket superhet.

If R14 is of abnormally low value, or R15 unusually high in value, noise may increase. Noise from this cause will remain if one end of C17 is temporarily disconnected.


A high background noise which ceases abruptly if one or more of the IFT's is detuned, is caused by I.F. instability, described later. This will usually be accompanied by whistles.

Noise generated outside the set, due to ignition systems, light switches etc., cannot be prevented, but the receiver may be placed as far as possible from the source, or from mains wiring.

tuned in, or with volume very low. Current consumption depends directly on volume, rising to about 15mA on peaks with average good volume. Maximum volume from a local station can give peaks of 25mA or higher.

Consumption up to and including Tr4 should be about 6mA. If the no-signal drain of the output stage, Tr5 and Tr6, is much over 2mA, R19 should be slightly reduced in value to correct this. R18, R19 and R20 should be of 5% tolerance, and these values are correct only for OC72's.

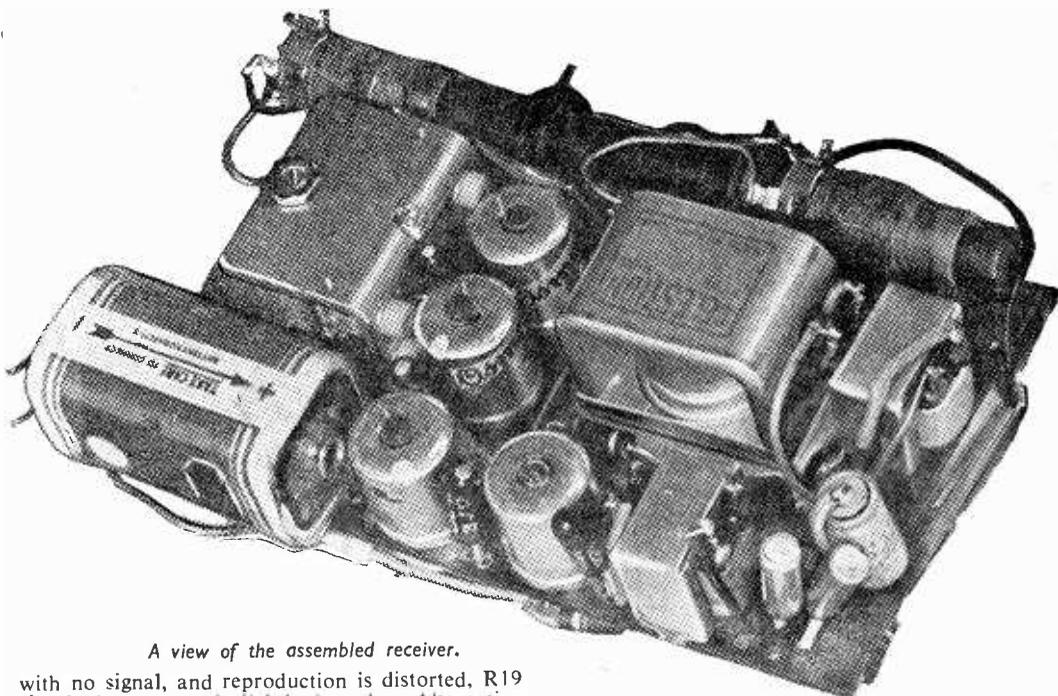If consumption of the output pair is very low,



A view of the assembled receiver.

with no signal, and reproduction is distorted, R19 should be increased slightly in value. Alternative transistors will probably require some change to the value of R18 or R19, to obtain a suitable base voltage. With the OC72's, R20 may be 4.7 Ω .

The driver and output transformers are for OC71 and OC72's and near equivalents. Resistor values shown permit economical working with full output.

Low Temperatures

Very low temperatures, such as may arise in winter in a vehicle or unheated room, may shift transistor characteristics, so that output is reduced and distorted. This is common to many such circuits, and is most likely when R18 and R19 chance to be of such a value as to make the output pair base voltage rather positive. The need for a new battery may be suspected. The trouble should cease when the set is run for some time in a heated room, or is otherwise allowed to reach a more normal temperature.

If this effect is unduly troublesome, R19 should be increased slightly in value to suit the actual output pair fitted. R19 should not be unnecessarily high in value as this will increase current consumption.

Distortion

This is most probably caused by wrong values for R18 or R19, as explained, or for R14, R15 and R17. The first three stages can be most simply checked by wiring phones across R15. Adequate volume with good quality should be obtained.

Transferring the phones to the driver transformer primary should give a very great increase in volume with good quality maintained. If not,

suspect R14, R15 and R17, or Tr4. If quality is good here, but not from the speaker, suspect R18 or R19.

Resistor Coding

Errors in reading values are most likely with low values, such as 4.7 Ω , 47 Ω , and 470 Ω . If values are in doubt, they should be checked with a meter.

The 5% tolerance resistors should have a gold band, and all other resistors should have a silver band to indicate 10% tolerance. Unmarked resistors (20%) should not be used.


Transistors

Leads will be of about the right length if the transistor tops are level with the tops of the I.F. transformers. Alternative transistors will be found to work satisfactorily, if of equivalent or near equivalent type.

If different transistors are incorporated, some changes in component values may be required. With Tr1 (OC44 specified) R2 might require changing, or a low value resistor may need adding between collector and pin 6. With different transistors for Tr2 and Tr3 (OC45's specified) it could occasionally be necessary to modify neutralising values, or base supply resistors.

Warning

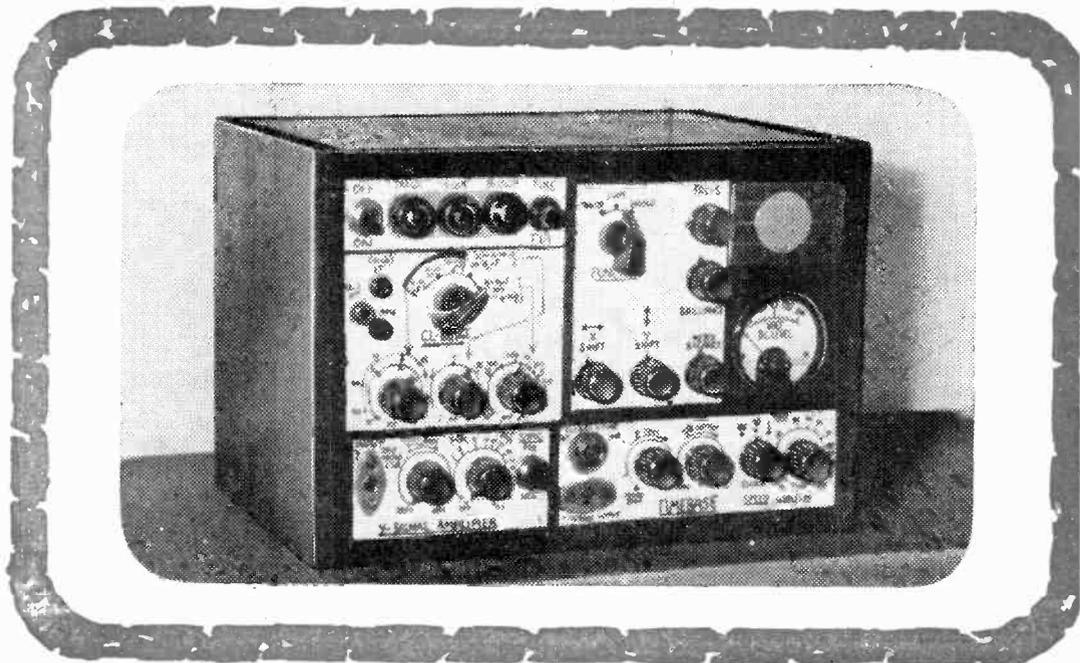This article has been published for the benefit of those readers who built the original P.W. design and the servicing information given here may not apply to later versions of the receiver although it may be found of assistance. ■



By M. L. Michaelis

THIS article describes the construction of a compact test-set combining the functions of several separate units of conventional construction, and enabling a multitude of qualitative and quantitative measurements to be performed on wireless and amplifier circuits.

Introduction

Many keen experimenters must confine their activities to some odd corner of a room used for other purposes too, or possess only a workshop of very limited size. Experimental work, on the other hand, is considerably hampered if essential apparatus has to be stored away in inaccessible places, requiring considerable preliminary setting-up work prior to any working session. This trouble is particularly aggravated if such apparatus is bulky or consists of many separate units. It is thus highly desirable to have the essential measuring and test equipment in as compact and multi-purpose a form as possible, so that it may be left permanently set up ready for immediate use, even under conditions of very limited space.

The "Experimenter's Power Pack" (already published in this magazine in the January 1962 to July 1962 issues inclusive) is aimed to meet experimental power-supply needs under the conditions just mentioned. This article describes a very compact test-set, measuring only 11½ in. x 8 in. x 7½ in. deep, which embodies the full functions of (a) oscilloscope (b) signal tracer (c) audio test-oscillator (d) frequency-meter (e) valve-voltmeter (for A.C. and D.C.) (f) quantitative waveform analyser, and (g) resistance-Inductance measuring bridge. It uses only seven valves and a miniature cathode-ray tube, and has a built-in moving-coil meter and all power-supplies also built-in.

Very considerable experimenting time has been devoted during design to obtaining a really stable and reliable circuit which should function well without any difficulties if the points discussed in the course of this series of articles are carefully observed.

Equipment for the Experimental Workshop

The following question has often been raised: "What basic equipment does the keen experimenter require if he really wants to be able to observe systematically what exactly is going on in his experimental circuits, rather than rely on more hit-and-miss methods?" The "Experimenter's Power Pack" and the "Miniscope" of the present article are the answer which this magazine offers, in a practical way, to this vital question. In addition to these two items (apart from the obvious need for an adequate set of the usual hand-tools such as soldering-iron, screwdrivers, files, pliers, etc.) the following may also be recommended:

(a) A good multimeter which may be home-made, according to information already published in these pages, or any good commercial model from the wide selection of advertiser's offers.

(b) A small handy grid-dip meter covering those ranges of radio frequencies with which the experimenter intends to work. For general-purpose use, an instrument with a set of plug-in coils covering the range 100kc/s to 100Mc/s would be ideal. It is of advantage to see that this instrument is usable as R.F. and I.F. signal generator and absorption-wavemeter too (as most grid-dip meters will already be, or will be after simple modification). Capacities below 1,000pF and inductances in the milli-henry and micro-henry

ranges can then be measured with this instrument, as well as tuning-ranges of tuned circuits, etc., thus augmenting the functions of the Miniscope.

A useful third item here would be a small wobulator for use in conjunction with the "Miniscope" for aligning tuned circuits, bandpass filters, etc. Provision is made on the Miniscope for connection of such a wobulator, in conventional fashion.

A constructor possessing this list of equipment, and having acquired the necessary skill and knowledge in its practical use and possibilities, should be in a position to carry out almost any quantitative or qualitative observation on processes in normal experimental work, giving him a very clear picture of what is going on in his circuits at every stage.

Regarding the Miniscope in particular in this scheme of equipment, the parts-list may appear formidable, with 73 resistors and 43 condensers

The second position of the function switch, entitled "scope", brings the small cathode-ray tube and the sawtooth-sweep timebase circuit into operation in addition. The signal can now be observed in form of its waveform on the CRT in addition to the continued audibility via the earphones, speaker or external amplifier. Of the three pilot lamps the green one labelled "tracer" is still lit and the red one labelled "scope" is switched on too in this setting. A zener-diode calibrator is included in the signal circuits, enabling the vertical-deflection sensitivity to be set accurately to any desired value between 1V/cm and 125V/cm. This enables the A.C. component voltage of any waveform to be read off (A.C. Valve-Voltmeter function), whilst the D.C. component which the waveform may possess in addition is simultaneously indicated, in polarity and magnitude, on the moving-coil meter situated on the panel below the CRT, this representing the D.C. valve-voltmeter function.

THE

MINISCOPE

and a quantity of other material. But, remembering that this instrument combines the functions of about seven instruments which would otherwise have to be built and bought separately, and which are all essential, the price of these components is in fact astoundingly cheap for the benefits reaped.

General Circuit Plan

The Miniscope consists basically of four circuit-positions. The first is the combined H.T./EHT power-supply. The second is the Wide-Band Signal Amplifier (Y-amplifier), including valve-voltmeter functions in the input stage and a signal-tracer output stage. The third is the special time-base circuit, calibrated *quantitatively* for time and frequency measurements in the range from a few microseconds to about 25 milliseconds. The time-base-wave is available externally at a coaxial socket for feeding a wobulator, or for general use as audio test signal. The fourth circuit portion comprises the additional elements and switching for a novel phase-bridge for L and C measurements.

A function-switch selects three operating positions. The first is entitled "tracer". In this position only, the Signal Amplifier (and associated valve-voltmeter) is operating. The amplifier signal may be heard on headphones connected to the output provided or on a miniature loudspeaker which is connected there, or else passed into an external separate power amplifier. Of the three pilot lamps only the green one labelled "tracer" is lit.

If the applied signal is pure A.C., then the waveform appears on the CRT, but the meter needle does not move. If the applied signal is pure D.C., then the meter shows it, but the CRT shows only the undisturbed timebase trace. The advantage of this arrangement over the otherwise more conventional signal-amplifier passing the full D.C. component (D.C. amplifier) and giving D.C. indication by a corresponding bodily shift of the trace on the CRT screen is that *the relative D.C. and A.C. sensitivities may be chosen independently* to suit the relative D.C. and A.C. contents of the waveform being observed. Thus, for example accurate observation of hum-ripple percentage on a power supply is immediately possible which requires two separate measurements with a conventional D.C. oscilloscope.

Furthermore, the arrangement here adopted allows the essential D.C. measurements yet does not require a full D.C. amplifier, which would normally be tricky to construct under amateur conditions. A straightforward, stable and reliable A.C. amplifier is thus used.

The main signal amplifier has a bandwidth, level to within the usual specifications of $\pm 3\text{dB}$, extending from 25c/s to 120kc/s, and will thus give accurate displays of pulsed waveforms even at the highest audio frequencies. A low-pass filter is built in between the CRT-feed stage and the tracer output stage to prevent frequencies higher than 15kc/s reaching the earphones/speaker output (as these could otherwise be rectified at the input

to a subsequent amplifier, causing grid-current blocking or distortion or creating various forms of instability). Thus, even if applied signals are of a frequency well above the highest audible, they are still displayed on the CRT, yet give no tracer output. The amplifier still shows appreciable (though much reduced) gain at 1Mc/s and will just resolve individual cycles of the carrier of medium-wave stations operating around this frequency on the CRT display. These will be seen by connecting a tuned circuit and good aerial to the input or the output of an R.F. signal-generator if local-station signal strength is not sufficient.

The third position of the function switch brings the L-C bridge into operation. The green pilot lamp "tracer" is now extinguished, the red "scope" lamp is still lit, and the third lamp, a green one labelled "bridge", is now also lit. The signal amplifier is operating, as is the CRT, but the sawtooth-sweep timebase is inoperative, the X-deflection now being by the mains 50c/s sine wave. A fixed R-C combination shifts this sine wave so that it is running 45° out of phase with the local mains. If now a sample of the in-phase mains wave is applied to the Y-amplifier (from the 6.3V heater line) the oblique-ellipse trace charac-

teristic of two waves of equal frequency but constant phase-shift relative to each other is obtained on the screen.

But the in-phase wave is taken from the heater line, via an unknown condenser to be measured, on to a calibrated potentiometer, taking the Y-amplifier input from the potentiometer. This gives a phase-shift of an amount dependent upon the relative sizes of condenser and resistance, and a certain definite combination gives 45°, so that X and Y signals are then in phase again, both being 45° off the mains. This condition gives a clean diagonal line on the CRT. As the potentiometer is adjusted, therefore, the ellipse will close up to a narrow diagonal line at balance, and open up again beyond, and the potentiometer may be calibrated in capacity values correspondingly. This arrangement gives very clean, unambiguous balance readings. Ranges giving continuous coverage from 1.000pF to 30μF are incorporated in the Miniscope. Smaller capacities are better measured with a grid-dip meter and larger ones by a method described later in this article.

Inductances give a phase-shift in the opposite direction to condensers with the arrangement here described and thus augment the phase difference between X and Y signals. A good reference

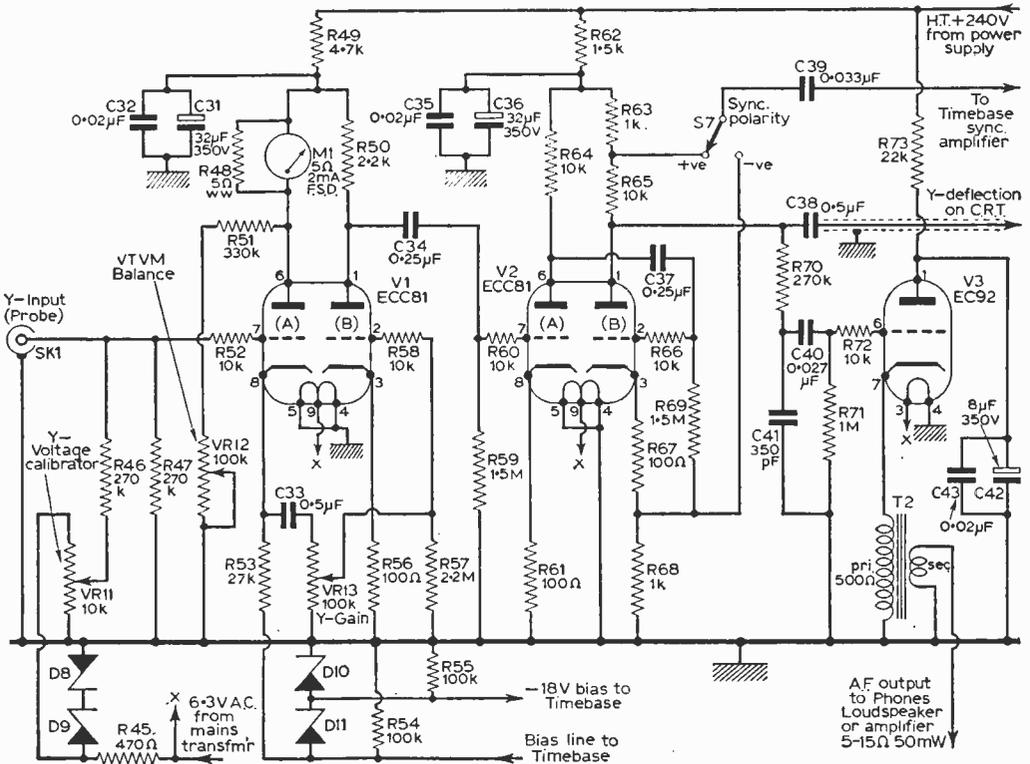


Fig. 1—The Y-amplifier circuit. The input is direct-coupled, and will tolerate a maximum D.C. component of 25V (of either polarity), or an A.C. signal of maximum amplitude 50V peak-to-peak. With the probe to be described at the end of this article, fifteen times these inputs are tolerable, and the calibrations on the D.C. level meter and on the calibrator are made to apply to conditions when using the probe. It is undesirable to use the Miniscope without the probe, unless the extra sensitivity is indispensable. Less waveform distortion of H.F. components of a signal is also obtained when using the probe.

COMPONENTS LIST

Resistors

(All carbon, $\pm 10\%$, 1W unless otherwise stated)

R1 15k	R26 270k	R51 330k
R2 100k	R27 470k	R52 10k
R3 68k	R28 220k	R53 27k 2W
R4 470k	R29 2.2k	R54 100k
R5 47k	R30 100k	R55 100k
R6 500 Ω 2W ww	R31 220k	R56 100 Ω
R7 500 Ω 2W ww	R32 220k	R57 2.2M
R8 680k 2W	R33 47k	R58 10k
R9 22k	R34 100k	R59 1.5M
R10 68k	R35 100k	R60 10k
R11 22k	R36 15k	R61 100 Ω
R12 330k	R37 330k	R62 1.5k
R13 270k	R38 47k	R63 1k
R14 270k	R39 100k	R64 10k 2W
R15 1M	R40 47k	R65 10k 2W
R16 1M	R41 560k	R66 10k
R17 100k	R42 2.7M	R67 100 Ω
R18 47k	R43 10k 2W	R68 1k
R19 270 Ω	R44 47k	R69 1.5M
R20 3.9k	R45 2.7M	R70 270k
R21 39k	R46 270k	R71 1M
R22 470k	R47 270k	R72 10k
R23 47k	R48 5 Ω ww	R73 22k 2W
R24 47k	R49 4.7k 2W	
R25 2.7M	R50 2.2k	

Capacitors

C1 8 μ F 450V elec
C2 16 μ F 350V elec
C3 16 μ F 350V elec
C4 8 μ F 450V elec
C5 16 μ F 350V elec
C6 1 μ F 750V metal-paper
C7 8 μ F 350V elec
C8 100 μ F 50V elec
C9 8 μ F 350V elec
C10 8 μ F 350V elec
C11 8 μ F 450V elec
C12 50 μ F 50V elec
C13 0.01 μ F 1000V paper
C14 0.01 μ F 500V paper
C15 16 μ F 350V elec
C16 8 μ F 350V elec
C17 0.082 μ F 350V elec
C18 8 μ F 350V elec
C19 8 μ F 350V elec
C20 0.25 μ F 500V elec
C21 0.047 μ F 500V paper
C22 300pF 500V paper see text
C23 3000pF 500V paper
C24 0.03 μ F 500V paper
C25 330pF 500V paper
C26 3300pF 500V paper
C27 0.033 μ F 500V paper
C28 0.2 μ F 500V paper
C29 0.1 μ F 500V paper
C30 220pF 500V paper
C31 32 μ F 350V elec
C32 0.02 μ F 500V paper
C33 0.5 μ F 500V paper
C34 0.25 μ F 500V paper
C35 0.02 μ F 500V paper
C36 32 μ F 350V elec
C37 0.25 μ F 500V paper
C38 0.5 μ F 500V paper

C39 0.033 μ F 500V paper
C40 0.027 μ F 500V paper
C41 350pF 500V paper
C42 8 μ F 350V elec
C43 0.02 μ F 500V paper

Potentiometers

VR1 50k lin	VR5 5k log
VR2 250k lin	VR6 50k log
VR3 2M lin	VR7 500k log
VR4 2M lin	
VR8 250k log with D.P. switch (S4)	
VR9 2M log	VR12 100k lin
VR10 100k lin	VR13 100k log
VR11 10k log	

Valves

V1 ECC81	V5 EB91
V2 ECC82	V6 EF86
V3 EC92	V7 EC92
V4 EF80	

V8: DG3-12A cathode ray tube (Telefunken).

These are obtainable from Tellux Ltd., 44 Brunel Road, London, W.3. Orders will take from 2 to 3 weeks to be despatched. (Other $1\frac{1}{2}$ to 2in. electrostatic CRT's may be used if they have 6.3V heaters and require 400-500V on the final anode.)

Larger surplus tubes, such as the YCR135A, may be used, but will require cabinet modifications and possibly slightly different resistor values in the EHT-chain.

Diodes

D1 E250C85 (250V A.C./85mA D.C.)
D2 E250C50 (250V A.C./50mA D.C.)
D3 E250C50 (250V A.C./50mA D.C.)
D4 S36 } 100mA/ W/150 maximum
D5 S36 } 350V peak inverse voltage
D6 S36 } 10pF capacity
D7 S36 } 500kc/s maximum
D8 Z7.5 7.5V 25mA
D9 Z7.5 7.5V 25mA
D10 Z18 18V 20mA
D11 Z18 18V 20mA

Zener Diodes

(Diodes D4 to D11 are available from The Bush Crystal Co. Ltd., Hythe, Southampton.)

Switches

S1 6-pole 3-way ceramic rotary
S2 Single-pole on/off toggle
S3 2-pole 5-way ceramic rotary
S4 2-pole with VR8
S5 2-pole 3-way miniature ceramic rotary
S6 Single-pole 2-way toggle
S7 Single-pole 2-way toggle

Transformers

T1 Mains 250V 60mA/110V 10mA/6.3V 3A: primary to suit mains
T2 Output 9k (R 500 Ω)—5/15 Ω)

Miscellaneous

Thermocouple R.F. Meter


LPI, 2 and 3 Panel pilot lamp holders (2 green, one red); 3 12V 0.15A bulbs; 13 pointer knobs; 3 insulated wander-plug sockets; 2 coaxial sockets; F1 panel fuse holder; 4 Noval and 3 B7G ceramic valveholders with screening cans; 'phones output plug; mains cable and plug; tagstrips; wire, sleeving, etc.

condition is then when the phase difference has been complemented to 90°, giving a vertical or horizontal ellipse instead of an oblique one, which can be adjusted to a **true circle** by suitable adjustment of the Y-amplifier gain. The potentiometer is thus calibrated for coils for the condition for having a trace in the form of a true circle on the CRT screen. A range of 1H to 20H is incorporated for chokes, transformers, etc. Smaller values arising in R.F. coils, etc., are better measured with a grid-dip meter.

A number of other useful measuring operations are possible in the "bridge" setting of the Miniscope, which will be discussed below in conjunction with the circuit details.

The Signal Amplifier (Y-amplifier)

Fig. 1 shows the theoretical circuit of this portion of the Miniscope circuitry. It employs three valves, using high-slope triodes throughout. The input stage, V1 (pins 6, 7 and 8), is a Class-A cathode-follower with unity voltage gain but impedance step-down. The purpose of this arrangement as input stage is to meet several requirements. Firstly, it accepts very high input amplitudes without overloading, so that the input can be run "fully open"—i.e., without a gain control. The input is at high impedance (as it must be, otherwise the signal source would be loaded and its waveform possibly changed in nature) and any volume control connected there would shunt high frequencies considerably on account of its inevitable self-capacity. The wide bandwidth achieved here would then not have been possible. The cathode-follower input stage,

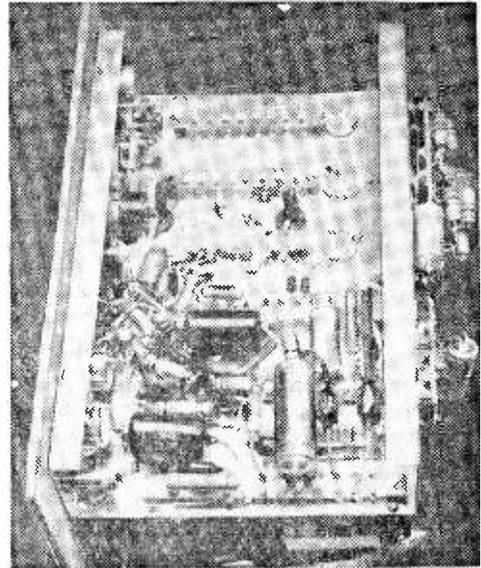

A view of the sub-chassis with the Y-amplifier wiring.

however, transforms the impedance at its output down to a mere one or two hundred ohms and considerable shunt capacity is tolerable there without high-frequency loss—thus the gain-control appears in this position.

(To be continued)

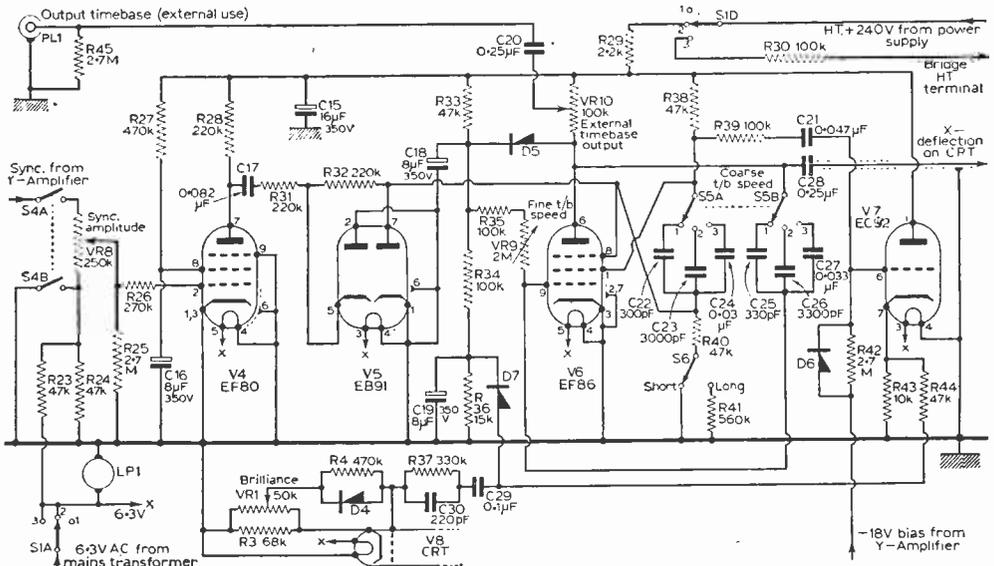


Fig. 2—The timebase circuit. This embodies an extremely linear sweep generator, with speed continuously variable from 12µsec/cm to 25m sec/cm on the CRT screen and also a powerful sync circuit, operating on the Y-signal on either polarity at will, or on the mains frequency. The sync amplifier acts as Buffer, preventing timebase signals entering the Y-circuits, as well as amplifying the sync signals, so that lock is rigid even at tiny Y-amplitudes on the CRT screen. Finally, the timebase screen-grid waveform is shaped in a special circuit, giving effective flyback-blanking, avoiding confusion in displays.

A COMPACT CONVERTER for short waves

A. Sydenham

THIS INSTRUMENT WILL PROVIDE SHORT WAVE LISTENING ON A MEDIUM WAVE RECEIVER

(Continued from page 319 of the August issue)

THE constructor following the instructions given in last month's issue will have fixed the chassis to the front panel and mounted some of the larger components.

When this stage is reached, wiring can be begun using Figs. 4 and 5 for reference. (Avoid overheating the coil spills when soldering.) The small dimensions of the chassis permit short and mostly self-supporting wiring, which is a desirable feature in short-wave equipment. Note the location of the stand-off insulator used as an anchoring and take-off point for the coaxial outlet lead.

All fixed capacitors should be of very high quality and of modern miniature design, since leaky specimens are likely to cause poor operation. Ceramic valve bases were used in the prototype, but are perhaps not entirely essential.

Testing the Converter

If all wiring is correct S1/S2/S3 may be adjusted to position "2", valves inserted and batteries connected at the appropriate points, polarity being carefully observed. Coaxial cable should then be connected to the aerial and earth sockets of the receiver with which the unit is to be used, after first transferring the aerial lead to the converter.

The receiver should then be switched on and tuned to a silent point on its dial around 1.5Mc/s (200m), the volume control being turned well up. The converter sensitivity control, VR1, should next be set to the H.T. end of its travel and VC3 set at approximately half capacity—with its moving vanes half enmeshed in the stationary ones. The converter can now be switched on and aligned.

If no signal generator is to hand the dial of the converter should be rotated until some hiss or a


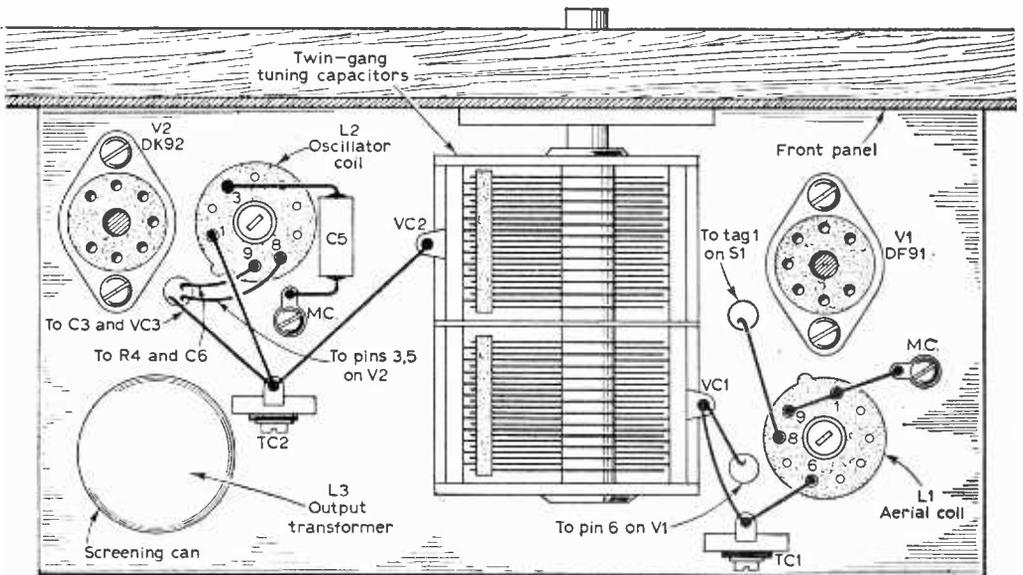


Fig. 4 (above)—Chassis layout of components.

signal is heard when the core of L3 should be manipulated in an attempt to strengthen the signal. The next step lies in trimming and padding the signal and oscillator circuits at the high and low frequency ends of the scale, taking care to allow only the minimum of capacity to be introduced via the trimmers. The oscillator should operate on the high side of the signal frequency, and normally the coil cores will be screwed in reasonably well.

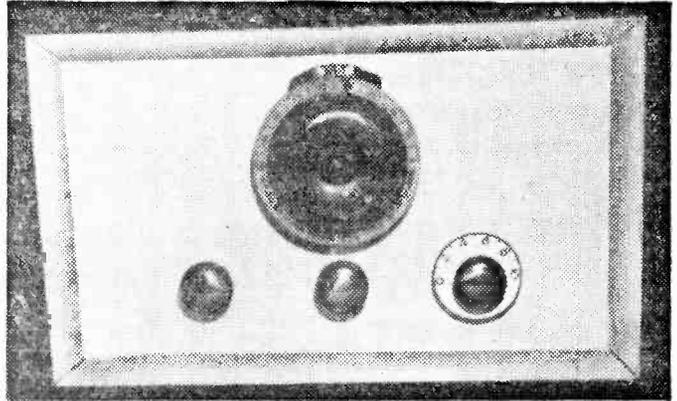No adjustments should be made to VC3 until alignment is complete, which might take a little time in the absence of a signal generator. The sensitivity control might need to be turned



(Above)—The front of the unit.

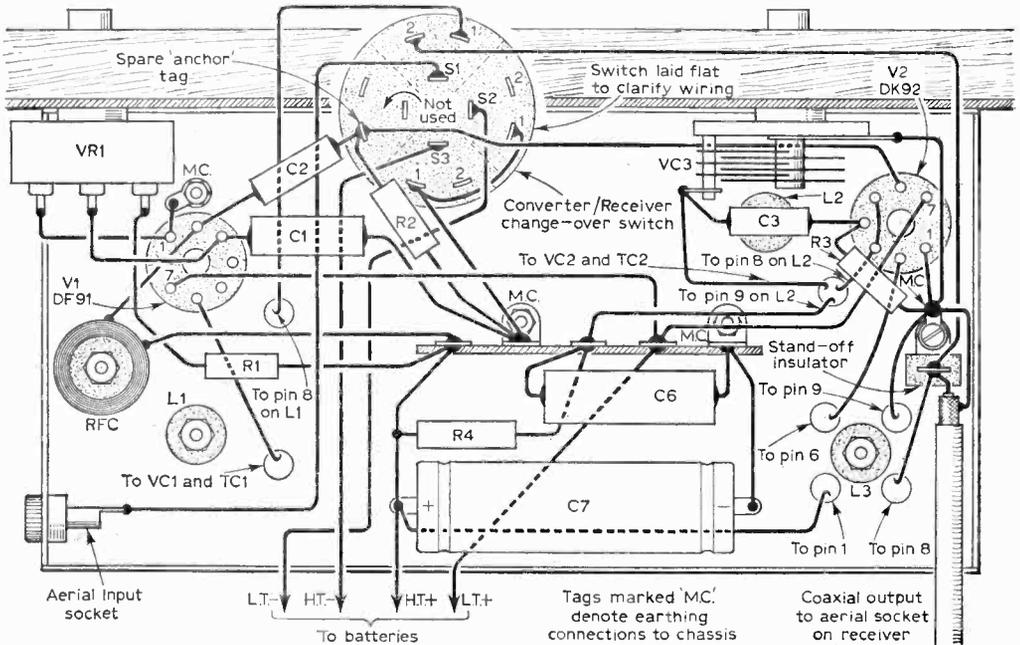



Fig. 5—The underchassis wiring diagram.

down as certain transmissions are received.

Faults

The above supposes "first time working", which in practice might not result. When the converter is first switched on, silence might well result, and if this occurs, and voltage supplies, etc. are in order, as indicated by a suitable testmeter, the oscillator section of V2 should come under suspicion. All-dry frequency changers quite often are more

(Continued on page 417)

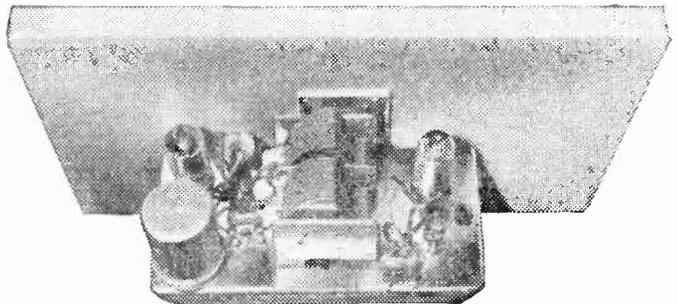

An above-chassis view.

Tel: Mitcham 6202
Open Daily to Callers

R S T

All Valves Brand New
and Fully Guaranteed

211 STREATHAM ROAD, MITCHAM, SURREY

Special 24 Hour Express Mail Order Service

AC2PEN 21/-	ECC88 17/6	EY86 8/6	PCF80 9/6	U12 9/-	UY85 7/-	6A7 9/-	6P25 10/6	12K7GT 5/-
AC2PEN DD 21/-	ECC91 4/-	EZ35 6/-	PCF82 7/-	U14 9/-	VMS4B 12/6	6ABG 8/6	6P28 17/6	12K8GT 10/-
ACTP 32/-	ECF80 8/6	EZ40 7/-	PCF84 16/-	U22 8/-	VP4 15/-	6ABGT 13/6	6Q7 6/6	12Q7GT 6/6
ACVPI 17/6	ECF82 8/6	EZ41 7/-	PCF86 15/-	U24 21/-	VP4A 17/6	6ABR 9/-	6Q7GT 8/6	12SA7 8/6
AZ1 15/-	ECH3 21/-	EZ80 7/-	PCL82 9/6	U25 12/6	VP4B 17/6	6A8 9/6	6SA7 7/-	12SK7 6/-
AZ31 10/-	ECH21 22/-	EZ81 7/-	PCL83 12/6	U26 10/-	VR10530 7/-	6AK5 5/-	6SG7 7/-	12SQ7 8/6
B36 10/-	ECH42 9/6	EZ90 7/-	PCL84 10/6	U27 8/-	VR15030 7/-	6AK8 7/6	6SH7 6/-	12SL7 8/-
C1C 12/6	ECH35 10/-	E1148 2/-	PCL85 16/-	U31 9/-	VU39 9/-	6ALS 5/-	6S17 6/6	12SN7 10/-
CBL31 21/-	ECH81 8/-	FC2 21/-	PEN4A 17/6	U35 17/6	VU111 2/6	6AMS 5/-	6SK7 5/6	13D3 12/6
CCH35 21/-	ECH83 8/6	FC2A 21/-	PEN4A 17/6	U37 17/6	VU120 2/6	6AM6 4/-	6SL7GT 6/6	14H7 10/-
CL33 18/6	ECL80 9/-	FC4 15/-	PEN4D 25/-	U43 8/6	W61 11/-	6AN5 7/6	6SN7GT 5/6	14K7 10/-
CY1 15/-	ECL81 10/-	FC13 21/-	PEN4VA 17/6	U45 10/-	W76 5/-	6AQ5 6/6	6SQ7 8/6	14S7 15/-
CY31 15/9	ECL82 9/6	FC13C 21/-	PEN45 10/-	U47 12/6	W77 4/-	6AQ8 9/6	6U4GT 10/-	19AQ5 8/-
D77 4/-	ECL83 21/-	FW4/500 9/-	PEN45DD 25/-	U50 7/6	W81 6/-	6AT6 6/-	6U5G 7/6	19B6G 21/-
DAF32 9/6	EF9 21/-	GZ30 10/6	PEN45 10/-	U52 4/-	WB1M 6/-	6AU6 9/-	6V6 4/6	20D1 10/-
DAF91 7/6	EF22 14/-	GZ32 10/6	PEN45DD 25/-	U76 7/6	X17 8/6	6BBG 3/-	6V6GT 8/-	20F2 17/6
DAF96 8/9	EF36 4/-	GZ33 19/3	PEN46 5/-	U78 4/6	X18 9/-	6BA6 6/-	6X4 4/6	20L1 17/6
DC90 14/6	EF37 8/-	GZ34 13/6	PEN453DD 27/6	U91 15/-	X41 15/-	6BE6 6/-	6X5 7/6	20P1 25/-
DF33 10/-	EF37A 8/-	GZ37 19/3	PENDD4020 25/-	U281 18/-	X61 12/6	6BG6G 17/6	6X5GT 8/6	20P3 25/-
DF91 4/-	EF39 4/-	HABC8010/-	PL33 15/-	U282 19/6	X65 12/6	6BH6 8/-	6X6 15/-	20P4 22/-
DF92 7/6	EF40 15/-	HL41DD 8/6	PL36 15/-	U301 22/6	X76 12/6	6BR7 12/6	6X6 15/-	20P5 25/-
DF96 8/6	EF42 10/-	HL92 8/6	PL38 21/-	U329 12/6	X76M 12/6	6BR7 12/6	6X6 15/-	20P5 25/-
DF97 9/6	EF42 10/-	HL133DD 10/-	PL81 12/-	U339 15/-	X78 21/-	6BS7 12/6	6X6 15/-	20P5 25/-
DH63 6/-	EF50E 3/6	HN309 22/6	PL82 8/-	U403 10/-	X79 21/-	6BW6 7/6	6X6 15/-	20P5 25/-
DH77 7/-	EF80 5/-	IW4/35010/-	PL82 8/-	U404 10/-	Y61 10/-	6BW7 5/-	6X6 15/-	20P5 25/-
DK32 11/6	EF85 5/-	IW4/50010/-	PL83 10/6	U801 29/-	Y66 9/6	6BX6 5/-	6X6 15/-	20P5 25/-
DK91 8/-	EF86 10/6	KT33C 8/-	PL84 9/-	UABC80 7/6	Z63 7/6	6C4 3/6	6X6 15/-	20P5 25/-
DK92 8/6	EF89 9/-	KT36 17/6	PL84 9/-	UAF42 8/6	Z66 10/-	6C5GT 8/-	6X6 15/-	20P5 25/-
DK96 8/6	EF91 4/-	KT55 17/6	PL84 9/-	UB41 7/6	Z77 4/-	6C6 6/6	6X6 15/-	20P5 25/-
DL33 8/6	EF92 4/-	KT61 9/6	PL820 18/-	UBC41 8/6	Z152 4/-	6C9 12/6	6X6 15/-	20P5 25/-
DL35 10/6	EF95 7/6	KT66 15/-	PM24M 13/6	UBC81 10/-	ZD17 8/-	6CD6G 32/-	6X6 15/-	20P5 25/-
DL92 7/6	EF97 12/6	KT76 10/-	PX4 15/-	UBF80 8/6	ZI52 8/6	6CH6 10/-	6X6 15/-	20P5 25/-
DL93 7/-	EF98 10/-	KT81 15/-	PX25 25/-	UBF89 7/6	OZ4 5/-	6D2 4/-	6X6 15/-	20P5 25/-
DL94 8/6	EF183 18/-	L63 5/-	PY31 15/-	UCL21 21/-	IA7 11/6	6D6 5/6	6X6 15/-	20P5 25/-
DL96 8/6	EF184 14/-	LN152 9/-	PY32 12/6	UCC84 10/6	IC1 8/6	6E5 10/-	6X6 15/-	20P5 25/-
EAS0 2/-	EK32 8/6	LN309 12/6	PY80 7/6	UCC85 7/6	IC2 9/-	6F1 10/6	6X6 15/-	20P5 25/-
EABC80 6/-	EL2 21/-	LZ319 12/6	PY81 7/6	UCF80 13/6	IC3 9/6	6F6 6/9	6X6 15/-	20P5 25/-
EAC91 4/-	EL3 21/-	MKT4 17/6	PY82 7/6	UCH21 21/-	IC5 10/6	6F11 10/-	6X6 15/-	20P5 25/-
EAF42 9/6	EL6 21/-	M54B 17/6	PY83 8/6	UCH42 9/6	ID5 8/6	6F12 4/-	6X6 15/-	20P5 25/-
EB34 2/6	EL32 4/6	MVSPEN 17/6	PZ30 10/6	UCH81 8/-	ID6 10/-	6F13 10/-	6X6 15/-	20P5 25/-
EB41 7/6	EL33 10/-	MVSPENB 17/6	QS9510 18/-	UCL82 10/-	IHS 9/6	6F14 10/-	6X6 15/-	20P5 25/-
EB91 4/-	EL34 10/-	MU14 9/-	QS15015 10/-	UCL83 13/6	IL4 5/-	6F15 12/6	6X6 15/-	20P5 25/-
EBC3 21/-	EL35 10/-	MX40 15/-	R2 10/-	UF41 7/6	ILN5 4/6	6F19 12/6	6X6 15/-	20P5 25/-
EBC33 4/6	EL37 17/6	N18 8/-	R13 8/6	UF42 7/6	IN5 9/6	6F23 10/6	6X6 15/-	20P5 25/-
EBC41 9/-	EL38 21/6	N37 14/-	R12 8/6	UF80 7/-	IR5 8/6	6F33 5/6	6X6 15/-	20P5 25/-
EBC81 10/-	EL41 10/-	N37 14/-	R16 17/6	UF85 7/6	IS4 8/6	6H6 2/-	6X6 15/-	20P5 25/-
EBF80 8/6	EL42 10/-	N78 17/6	R19 19/-	UF86 12/6	IS5 7/6	6J5 4/6	6X6 15/-	20P5 25/-
EBF83 8/6	EL81 12/6	N108 18/-	R20 19/-	UF89 6/6	IT4 4/-	6J5GT 4/6	6X6 15/-	20P5 25/-
EBF89 8/6	EL84 6/6	N308 20/-	S130 7/6	UL41 9/6	IUS 5/9	6J6 3/6	6X6 15/-	20P5 25/-
EBL1 22/6	EL85 10/-	N339 20/-	SP41 3/6	UL44 21/6	3A4 5/-	6J7 5/-	6X6 15/-	20P5 25/-
EBL21 22/6	EL90 8/6	N369 10/6	SU2150 25/-	UL46 14/6	3A5 10/6	6J7GT 7/6	6X6 15/-	20P5 25/-
EBL31 21/6	EL91 4/-	OD3 5/-	SU2150A 25/-	UL84 7/-	3C4 8/-	6K7 2/-	6X6 15/-	20P5 25/-
ECC34 15/-	EL95 10/6	OZ4 5/6	T41 15/-	UL85 7/6	QOS 9/-	6K7GT 8/6	6X6 15/-	20P5 25/-
ECC35 8/-	EM80 8/6	P2 10/-	TDD4 12/6	UM80 10/6	354 7/6	6K8 5/-	6X6 15/-	20P5 25/-
ECC40 21/-	EM81 8/6	PCC80 13/-	TDD13C 17/6	UR1C 15/-	3V4 8/-	6K8GT 9/6	6X6 15/-	20P5 25/-
ECC81 5/9	EM84 9/6	PCC84 9/-	TH41 27/6	U15 19/-	5U4 4/-	6K25 18/-	6X6 15/-	20P5 25/-
ECC82 8/6	EM85 10/6	PCC88 15/-	TY86F 12/6	U16 16/6	5V4 7/9	6L1 13/-	6X6 15/-	20P5 25/-
ECC83 7/6	EY81 8/6	PCC89 9/6	UY1 15/6	U17 16/6	5Y3 8/6	6L6 7/6	6X6 15/-	20P5 25/-
ECC84 8/6	EY81 8/6	PCC89 9/6	UY21 15/6	UY12 12/6	5Y3GT 8/6	6L8 10/-	6X6 15/-	20P5 25/-
ECC85 8/-	EY83 15/-	PCC89 9/6	UY41 7/6	UY41 7/6	5Z4 9/6	6L19 17/6	6X6 15/-	20P5 25/-
					5Z4GT 12/6	6LD20 14/-	6X6 15/-	20P5 25/-

METAL RECTIFIERS

RM1	5/3	14RA 1-2-8-2	17/6 (FC31)	14A97	25/-
RM2	7/6	16RC 1-1-16-1	8/6	14A100	27/-
RM3	7/9	14RA 1-2-8-3	9/6 (FC31)	16RD 2-2-8-1	12/-
RM4	14/-	18RA 1-1-16-1	6/6 (FC116)	16RE 2-1-8-1	8/6
RM5	19/6	18RA 1-2-8-1	11/-	18RA 1-1-8-1	4/6
14A86	17/6	18RD 2-2-8-1	15/- (FC124)		

SPECIAL OFFER

EABC80 6/-, EAC91 4/-, EB91 4/-, EBF89 8/6, ECC81 5/9
ECC85 8/-, ECC91 4/-, ECH81 8/-, EBC33 4/6, EF39 4/-,
EF50 3/6, EF80 5/-, EF85 5/-, EF91 4/-, DF91 4/-, EL84 6/9,
PCC89 9/6, PL84 9/-, UABC80 7/6, UBF89 7/6, UF41 7/6,
UL41 8/6, UF89 6/6, UL84 7/6, UY85 7/-, W81 6/-,
OZ4 5/-, 5U4 4/-, 6A25 6/6, 6A25 6/6, 6BA6 6/-, 6BE6 6/-,
6D2 4/-, 6K7 2/-, 6K8 5/-, 6L6 7/6, 6Q7 6/6, 6SL7 6/6,
6SN7 5/6, 6V6 4/6, 8D3 4/-, 807 5/-, 12AT7 5/-, 12AH8 9/-,
12BA6 7/6, 12BE6 7/6, 12K7 5/-, 12Q7 6/6.

TERMS OF BUSINESS C.W.O. or C.O.D.
3/2 PACKING CHARGE ON ALL C.O.D.
ORDERS. POSTAGE 6d. PER VALVE

OBsolete Valves a Speciality.
Quotations given on any type
not listed

WEYRAD

IMPROVED COMPONENTS FOR THE 6-TRANSISTOR 2-WAVE SUPERHET RECEIVER

NEW ROD AERIAL AND DRIVER TRANSFORMER FOR SIMPLER ASSEMBLY AND HIGHER PERFORMANCE

ROD AERIAL—RA2W
6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208 pF tuning capacity 12/6
Car Aerial coupling Coil 1/-

OSCILLATOR COIL—P50/1AC
M.W. covered with 176 pF tuning capacity.
L.W. by extra padder 5/4

I.F. TRANSFORMERS
1st and 2nd Stage—P50/2CC 5/7
(2 required)

3rd Stage—P50/3CC 6/-

DRIVER TRANSFORMER—LFD4
redesigned to reduce size and improve performance. Six spalls for mounting and connections 9/6



PRINTED CIRCUIT—PCA1
Size 2 3/4 in. x 8 1/4 in. Ready drilled and printed with component positions 9/6
CONSTRUCTOR'S BOOKLET WITH FULL DETAILS AND FREE SCALE 2/-

TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 500 mW OUTPUT.
MATCHING 3 OHM SPEAKER. FULLY ASSEMBLED WITH VOLUME CONTROL 63/6

WEYMOUTH RADIO MANUFACTURING CO., LTD.
REGENT FACTORY, SCHOOL STREET,
WEYMOUTH, DORSET

KITS THAT 'BUILD THEMSELVES'



FOR HIGH QUALITY


TWO & FOUR TRACK TAPE RECORDERS

- AMPLIFIER 'C' for Collaro Studio Deck (illustrated above), 11 gns. Case and Speaker for above. 5 gns.
- AMPLIFIER 'A' (4-TRACK) for BSR Monardeck. 9 gns.
- AMPLIFIER 'B' (TWO TRACK) for BSR Monardeck. 8 gns.
- Two-tone covered wooden case with speaker for above. 4 gns.
- KIT 'A' with Deck, Case and Speaker. 24 gns.
- KIT 'B' with Deck, Case and Speaker. 21 gns.
- KIT 'C' with Case, Speaker and Deck (as illustrated). 28 1/2 gns.

All amplifiers supplied assembled on printed circuit boards with valves.

- HI-FI quality printed-circuit amplifiers, supplied checked and assembled.
- Complete with valves, transformers and everything down to wire cut to length.

Produced by the makers of amplifiers for some of today's best known recorders and backed by years of experience in audio design. The specially designed kits offered here set entirely new standards of performance and finish for the home constructor. Amplifier available separately or with case and speaker and deck. EASY TO FOLLOW INSTRUCTIONS. All equipment complete and guaranteed. From radio dealers, or in cases of difficulty please write direct.

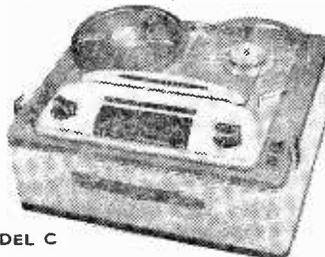

MODEL C

MARTIN RECORDAKITS

Leaflet free on request. Set of full instructions for any one model 2/6d. post free. (Allowable on purchasing kit).

COUPON BRINGS DETAILS

MARTIN ELECTRONICS LIMITED,
155 HIGH ST., BRENTFORD, MIDDX.

Leaflet on Martin Recordakits please

NAME

ADDRESS


(In Block Letters.)

P.V.9

(Right)—The underchassis wiring of the converter.

(Continued from page 414)

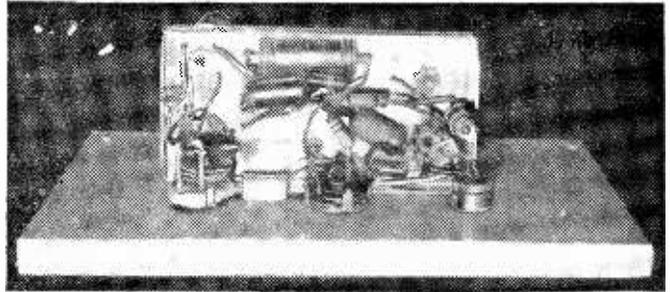temperamental than their mains-powered contemporaries, but oscillator functioning can be checked by disconnecting R4 from the H.T. line and inserting at this point a meter switched to read 0-10mA. The current flow should then be noted, and the value should alter when spills 8 and 9 of L2 are momentarily short circuited. Should no change be detected the oscillator is not operating and no



frequency changing can occur. The remedy lies in checking that part of the circuit very carefully and reducing R4 to 10k or increasing the value of C3 to, say, 100pF.

When the oscillator is working, the above test should be made at several points on the tuning scale, for it is quite possible for it to cease functioning at a particular frequency. Should no signals be heard when oscillator operation is satisfactory, try removing V1 and temporarily connecting a lead from pin 6 on its base to pin 6 on V2 base. If signals now result, V1 or the associated circuitry is at fault and should be investigated.

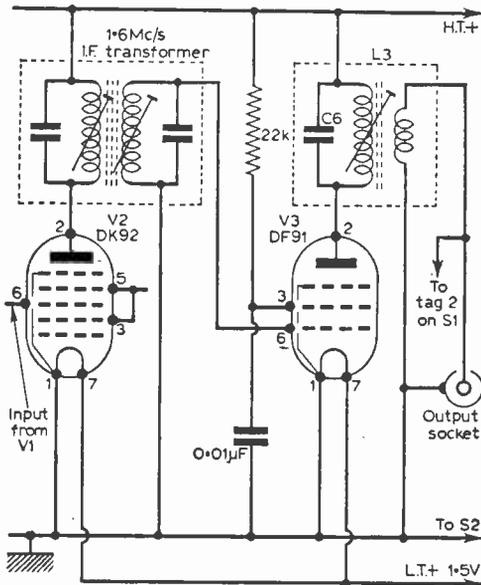


Fig. 6—A circuit modification to increase output.

Modifications

Where the output is considered insufficient, or where the broadcast receiver used with it is of low sensitivity, improved converter efficiency would result from fitting a further valve of the type specified for V1 and using it as an intermediate amplifier. The principle is shown in Fig. 7 where V3 is the added valve. Coil L3 is removed from the frequency changer anode and a miniature 1.6Mc/s I.F. transformer fitted instead. The amplified output is taken from L3, which is transferred to V3 anode. Extra care must be taken in a circuit of this kind to ensure adequate rejection of signals in the 1.5Mc/s band and a wavetrap tuned to the frequency might become necessary at the aerial input.

MEDIUM WAVE POCKET SUPERHET

(Continued from page 387)

weak signals, to keep volume down. Final adjustment should be at frequencies a little from the extreme ends of the bands, once it has been found that band coverage is satisfactory. It may be difficult to keep volume down to a level where the effect of adjustments can be easily heard, when aligning with broadcast stations. If so, rotate the whole receiver, to make use of the directional properties of the rod, to reduce volume. During alignment, volume should not be reduced with the receiver volume control, or an exact setting of trimmers and cores will be difficult to find.

Reproduction should be at adequate volume, and of pleasing quality. Should results sound extremely distorted, it is probable that one secondary of the driver transformer has been wrongly wired, in error. If so, reverse leads to one secondary.

The tuning knob should rotate with a little clearance. If not, a washer may be needed under

it. The set can be used flat, or standing, with the rod horizontal. Only in rare instances need the receiver be rotated for best signal pick up, as volume should easily be sufficient.

The new version of the P.W. Pocket Superhet case can be used for this receiver; the use of this case will facilitate construction since it is larger than the original.

JOIN THE PRACTICAL GROUP			
PRACTICAL TELEVISION	1/9	
Every Month			
PRACTICAL MECHANICS	1/6	
Every Month			
Devoted to Mechanics, Science and Invention			
PRACTICAL MOTORIST	1/6	
Every Month			
PRACTICAL HOUSEHOLDER	1/3	
Every Month			

Short-wave Listeners' Log

FOR the best possible listening results, a general idea of the way in which short-wave signals are propagated will prove to be very helpful. Two types of signals are of interest—those furnished by the ground wave, and those from the sky wave.

On the S.W. bands, the ground wave is soon absorbed and lost, so long distance reception is not possible with its aid. Frequencies in the 20 and 15m bands, or around 14 and 21Mc/s, are most used for long distance reception, and ground waves from stations in these bands may already have become too weak at 20 or 30 miles range. For this reason, local stations may not be heard, even when remote overseas countries are coming in well.

The sky wave travels upwards at an angle, and reaches the ionised layers which surround the earth. When conditions are favourable the wave is bent or reflected by these layers, and returns to earth, often at a considerable distance. The distance from the transmitter to the point where the wave again reaches the earth is the "skip distance". There may be short or long skips, according to time of day, frequency, and other factors. The wave may be reflected from the earth, and again be deflected downwards by the ionised layers, reaching earth again at even greater distances from the transmitter. If conditions or frequencies are unsuitable, the wave may pass through the ionised layers, and be lost in space.

Long Distance Reception

Long distance reception is by waves that have been reflected from the ionised layers, possibly travelling a thousand miles or more at each hop, when skip is long. So best long distance reception will be around those times and frequencies giving long skip conditions.

The 20m or 14Mc/s band is extremely popular for long distance reception, and can give world wide coverage. The ionised layers are not stable, but are influenced by sunspots, magnetic storms, and solar radiation, so results change hour by hour. Usually, most remote stations (Australia, New Zealand) will be audible early in the morning. Somewhat later in the morning, there may be a period when only relatively near stations (European) can be heard. Range may increase after noon, with Near East, Far East, South African, and other distant stations coming in during early afternoon. These are likely to fade out later in the afternoon, when Far East stations are liable to disappear, and many American stations will begin to come up in strength. With evening, very considerable distances can still be covered.

A somewhat similar pattern is repeated daily, except that conditions vary day by day, and month by month, due to seasonal and other changes. With the 15m or 21Mc/s band, rather similar results can be expected, but with even more irregular fluctuation. So this band may be excellent one day, and almost dead the next.

Unless conditions are very bad, listening on these bands will almost certainly furnish some Dx (long distance) stations, and 15m and 20m are often termed the "Dx bands". When conditions are good, signal strength from remote countries may be good enough for satisfactory reception with simple 2-valve and similar receivers.

SERVICING TAPE RECORDERS

(Continued from page 404)

of the recorder, whilst leaving a reasonable margin on the recording level control for low level signals.

Fig. 27 shows a very convenient arrangement, where the attenuator comprises R1 and R2. The single-pole, two-position switch allows the set's loudspeaker to be used as programme monitor when required, while in the "loudspeaker off" position, the output stage is automatically loaded by R3. This resistor, of course, should have a value equal to the impedance of the loudspeaker.

Values for R1 and R2 are well worth considering. From the impedance aspect, there is not too much to worry about by connecting 3Ω across a megohm or so of the radio input socket. On the face of it, there would appear to be a bad case of mismatching, but in practice this has remarkably little adverse effect. Overloading is the chief trouble. However, when an attenuator is employed, the impedance can be stepped up to the tape recorder input so that the match is more theoretically exact.


R1 and R2 simply form a potential-divider. That is, all the signal is applied across the two resistors in series and only a fraction of it is tapped off from across R2. Ignoring the loading effect of the recorder input circuits, then in proportion the voltage across R2 is equal to R2 divided by the sum of R1 and R2. For example, take R1 and 100k and R2 as 50k, then R2 would be 50 divided by 150, which is one-third, meaning that one third of the full voltage from the set's output stage would be fed to the recorder.

In practice, the applied signal would be a little below one-third, since R2 would be shunted by the input impedance of the recorder which, in effect, would reduce the value of R2 in relation to R1, but this should not make a lot of difference in the majority of cases. Thus, the attenuator can be made any required value simply by working out suitable combinations of resistors, as explained above. The value of 100k and 50k may well be used in practice, and this would mean that the input of the recorder would see a resistance almost equal to 50k and 100k in parallel, which is approximately 33k.

The signal should be conveyed via screened cable, the R2 side of which should be connected to the braid and earthed. But beware at this point, since the set may have a "live" chassis; that is, connected to one side of the mains supply to follow the now popular A.C./D.C. technique. This aspect of recording, however, will be discussed in next month's article.

(To be continued)

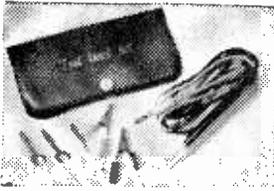BUDGET UNIVERSAL TEST LEAD KIT IN PLASTIC CASE




Consists of 4 1/2 in. long x 3/4 in. dia. red and black plastic handle pin prods with heavy duty 37 in. rubber leads with 5000v. breakdown insulation terminating 3 1/2 in. long x 3/4 in. dia. plastic grip banana plugs. 3 sets of interchangeable terminals are included (spade lugs, phone tips, alligator clips), all slip directly on to banana plugs. 9/6. P. & P. 1/6.

GREATEST TRANSISTOR SET VALUE YET KNOWN

A 5 stage medium waveband radio which can be built in one hour. No aerial or earth required. This set has the appearance of sets worth 7 to 8 pns. and works as well as sets 4 times the price. remember the saving is not in the parts used but by you making it yourself. Complete in case. Size 5 1/2 x 3 1/2 x 1 1/2 in. genuine 2 1/2 in. speaker, tuning condenser, volume control with switch. 37/6 P. & P. etc. All parts sold separately. 2/6



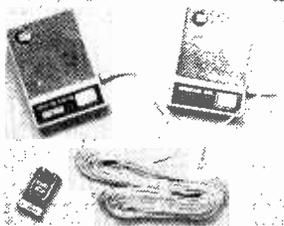HANDY TWO-STATION TRANSISTORISED INTERCOM & BABY ALARM



Fully Guaranteed Fantastic Value Complete with battery and 60ft. of wire. An intercom system for both calling and conversing, operated from a single battery. Ideal Baby Alarm. S.A.E. for further details. 6 gns

TRANSISTOR MEGAPHONE MODEL ER.304

The smallest ever! Incorporates printed circuit amplifier with current limiting device to give effective battery life. Range up to 1000 feet. size 10 1/2 x 8 1/2 in. dia. 12 gns Complete with shoulder strap. S.A.E. for illustrated leaflet.



TAPE SLICER & CUTTER. Model T.635 Cuts 2 rounded indentations in the tape splice leaving the edges of the tape which contact parts of the recorder entirely free of adhesive. As little as 1/2 in. tape need be removed. Complete with instructions. 18/9. P. & P. 1/3.

PORTABLE RADIO-PHONES

Consisting of trans-receiver covering 7.4-9 Mc/s. Range up to 6 miles, depending upon obstruction and elevation. On test the receiver astounded us for we heard 65 short wave stations—one as far away as Russia. Complete with 5 valves, headphones, microphone, function box and 6ft. telescopic aerial. Operates from standard 120 v. and 3 v. dry batteries.

ONLY 60/- EACH P. & P. 1/-. TWO FOR £6 post free (Batteries 20/- per set extra.)



TAPE RECORDER IN KIT FORM


Consisting of three transistor amplifiers, record/play, volume control, miniature speaker, forward-top-rewind-switch, reel of tape and spare reel, motor, attractive coloured case, Mic. and earphone sockets, tick-up coil, mike, earphone and carrying handle supplied. Standard battery operated. Simple to put together in less than one hour. Brand new and guaranteed.

ONLY £6.19.6

A guaranteed saving of at least £4! Results comparable with similar built-up recorders selling at around 12 gns. S.A.E. for further details. Order early.

THE MOST USEFUL AMPLIFIER EVER PRODUCED!

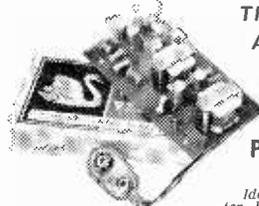4 TRANSISTOR PUSH-PULL AMPLIFIER MODEL PK.543



Ideal for making powerful Transistor Radios, Tape Recorders, Baby Alarms, Record Player, Intercom., etc. must be heard to be appreciated.

NOT A KIT—READY BUILT UNIT

ONLY 52/6 P. & P. 1/6

9V BATTERY CHARGER AND A.C. ELIMINATOR MODEL L.A.6P

A "MUST" for every transistor set owner! Over 20,000 already sold. Rush your order NOW.



Save those batteries by running your transistor set direct from A.C. Mains. Recharge all your old 9V batteries. Unit contains neon indicator and standard battery connections with nearly 2 yards of mains lead and plug. Also snap cord for connection to set.


SLIM RADIO PLUGS

Two-way, black bakelite, solder terminal PLUG. Panel mounting, neat finish. Standard size 2/6 each. (Plug only).

NEW "STEREO-STETHO" HEADPHONES

17 response 40-16000 cps. Impedance 15 ohms. Equipped with two individually transducers and cord sets for true stereo reproduction. Extremely sensitive the sound is carried through plastic tubes tipped with removable earpieces, ingenious hinge device permits adjustment to any desired spacing. Weight less than 2 ozs. May also be used for monaural listening. 27/6.

WIRELESS SET No. 19

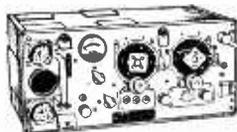

This most famous Army Trans/Receiver covers 2-8 Mc/s. (150-37 metres in two bands and 230-240 Mc/s V.H.F.). Has an intercom. amplifier. Designed for 12 and 24 volt operation. Uses a 6 valve superhet receiver, I.F. being 465 Kc/s, and a 6 valve transmitter designed for voice and C.W. operation. Incorporates tuning and tuning meter for voltages, aerial loading and current tests. Panel Controls: Frequency tuning, P.A. tuning, Gain control, MCW, CW, R/T switch, Het-tone netting, off-on, Quench, aerial—AVC-ILT-HT—Drive tests. Supplied complete with valves and instruction book.

SET ONLY 65/- Carriage 10/-

LIMITED NUMBER ONLY Don't be disappointed—Order Now


MAIL ORDERS TO (DEPT. P.), 32a COPTIC STREET, LONDON, W.C.1



CALLERS WELCOME AT 87 TOTTENHAM COURT ROAD, LONDON, W.1. MUS 9606



Stentorian

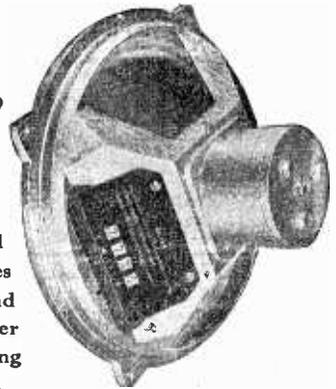

This range of Stentorian loudspeakers, incorporating the patented cambric cone, was developed to provide reproduction that takes full advantage of the television and V.H.F. sound transmissions and high fidelity recordings now available. The cone of the loudspeaker is made from uncured cambric and bonded pulp, the whole being completely cured together and made into one composite cone.

MODEL H.F. 1016

10" Unit H.F. 1016. 16,000 gauss. Instantaneous matching at 3, 7.5 and 15 ohms. Handling capacity 10 watts. Frequency response 30 c.p.s. to 15,000 c.p.s. Bass resonance, 35 c.p.s.

Price £7.16.0 (inc. tax)

* Incorporates a universal impedance speech coil.


Type	Flux Density	Price	Type	Flux Density	Price
8" H.F.816*	16,000 gauss	£6.13.9	T.816	16,000 gauss	£6.6.9
8" H.F.812*	12,000 gauss	£4.1.3	T.12 tweeter	16,000 gauss	£13.4.6
8" H.F.810	10,000 gauss	£3.0.6	T.10 tweeter	14,000 gauss	£4.8.3
6" H.F.610	10,000 gauss	£2.10.3 Steel £2.12.3 diecast	T.359 tweeter	9,000 gauss	£1.14.0

WHITELEY ELECTRICAL RADIO CO. LTD. MANSFIELD, NOTTS
 Telephone: MANSFIELD 1762-5 London Office: 109 Kingsway, London, W.C.2
 WA3

MINISETS LTD. Hatherley Mews London E17

6-STAGE PORTABLE TRANSISTOR RADIO


- ★ All parts including transistors direct from manufacturers
 - ★ Pre-assembled circuit board ensuring ease of construction
 - ★ Full medium-wave coverage
 - ★ After-sales service
 - ★ Attractive two-tone case 9 x 6 x 4in.
 - ★ Push-pull output, 350 milliwatts
 - ★ 5in. high flux speaker
 - ★ Built-in Ferrite Rod aerial
 - ★ No external aerial or earth required.
 - ★ High performance, many stations received on test
- Can be built for **£5.4.0** P.P. 3/-
 Or with long-wave 8/- extra.
 Full instructions 1/6 (Free with order).

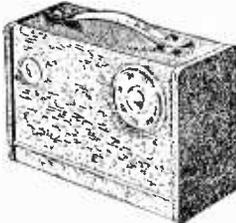

3-TRANSISTOR RADIO (plus 2 diodes)

Total building **70/-** P.P. 2/6

- ★ Pre-assembled circuit board, ensuring easy construction
 - ★ Full medium-wave coverage
 - ★ Attractive case 5½ x 3 x 1½in.
 - ★ All components including transistors are brand new and direct from manufacturers
 - ★ Ferrite Rod aerial coil, no external aerial or earth required
 - ★ 2½in. high flux speaker direct from manufacturer
 - ★ After-sales service
- Send 1/6 for instructions, circuit and price list

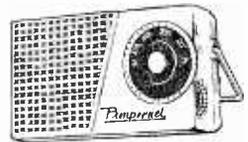


6-STAGE TRANSISTOR POCKET PORTABLE

- Can be built for **£4.19.6** P.P. 2/6
- ★ Completely self contained no aerial or earth required
 - ★ Push-pull output, 250 milliwatts
 - ★ 3in. high flux speaker
 - ★ Pre-assembled circuit board with simple instructions ensuring easy construction
 - ★ High Q Ferrite Rod Aerial
 - ★ After-sales service
- Can be supplied with long-wave 6/- extra.
 Full instructions, price list 1/6 (Free with order)




2-TRANSISTOR RADIO (plus 2 diodes)

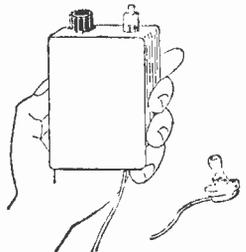- Ideal for personal listening
- ★ Built-in Ferrite aerial
 - ★ Sensitive earpiece.
 - ★ All parts including transistors direct from manufacturers
 - ★ Pre-assembled circuit board and easy-to-follow instructions
 - ★ After-sales service
 - ★ Can be built for **50/-** P.P. 2/-
- Full instructions, etc., 1/6 (Free with order).




Noisy Volume Controls

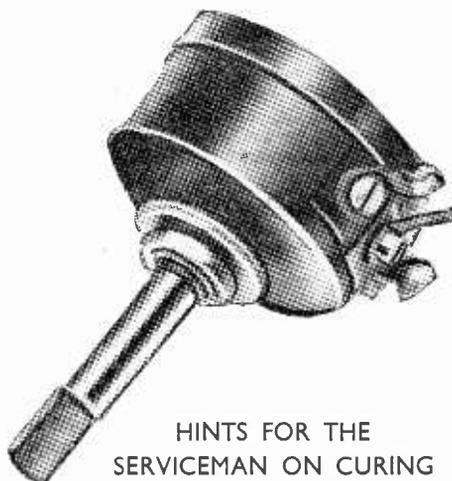

HINTS FOR THE
SERVICEMAN ON CURING
A COMMON FAULT

By E. Dexter

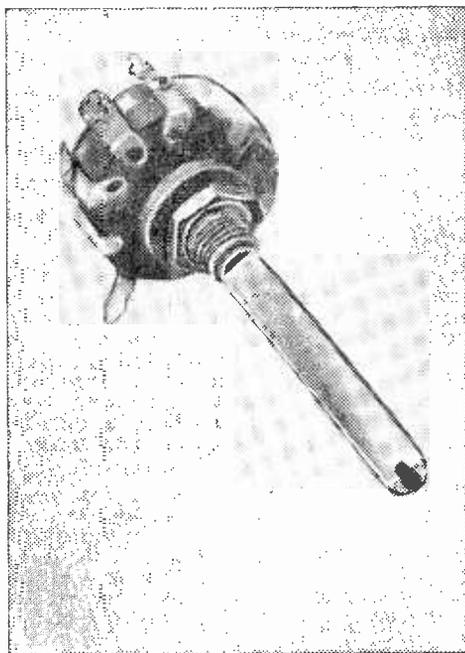(Continued from page 345 of the August issue)



THE reader was introduced to three examples of correct and incorrect circuitry associated with volume controls in last month's article (Figs. 3, 4 and 5, pages 342 and 345).

Fig. 4 shows a volume control used in the same arrangement as Fig. 1, which is basically permissible, but the value is now made *very high*. If the grid leak of a valve is higher than half to one megohm, quite considerable D.C. voltages may be developed across it due to the electron-current reaching the grid of the valve by virtue of the electrons' energy of ejection from the cathode, even though the actual grid voltage may still be quite negative, and thus, theoretically, electron grid-current not to be expected. Thus no volume control track used directly in the grid leak position of a valve should have a total resistance exceeding about 500k. If a greater resistance is, for any reason, desired, then another blocking condenser or separate grid leak, as in Fig. 4b, should be used. Otherwise the volume control is likely to become noisy very quickly.

Fig. 5 gives a typical example from transistor circuitry. It is common practice in modern high-gain transistorised amplifiers to insert the volume control not right at the input to the first stage but between the first and second stages, so that signal-to-noise ratio is improved with reduction of volume (this feature is good practice in all high-gain amplifiers, valve or

transistor, yet carries the danger of running the input unprotected from overload at the first stage).

Now a transistor, in contrast to the grid-circuit of a valve, always draws current at its input, with a D.C. component also in addition to the A.C. signal component. Thus the transistorised version of Fig. 1 is fundamentally incorrect in a transistor amplifier. The subsequent transistor will always draw D.C. through a volume control track if all or part of this were used as the direct-coupled input resistance to the stage. Thus, if a volume control is used between two transistor stages, a

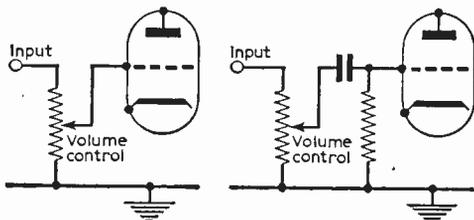


Fig. 6 (left)—A circuit often used for the input stage of audio amplifiers; this is satisfactory provided no D.C. is present with the input signal.

Fig. 7 (right)—Another input circuit for an amplifier—any D.C. present in the input is prevented from reaching the valve.

blocking condenser must be used on both sides of it. For a volume control between two valve stages we saw that a blocking condenser on the input side generally suffices, provided that the resistance of the volume control is not too high. Fig. 5b shows the correct arrangement for a volume control between two transistor stages.

Input Terminals for Amplifiers

The arrangement of Fig. 6 is often used for the input to the first stage of an amplifier. This is quite satisfactory as long as pure A.C. signals are applied as inputs. As soon as the signals contain a D.C. component, noisiness is likely. The arrangement of Fig. 7 would prevent the D.C. component shifting the operating point of the input stage, and thus prevent distortion under such circumstances. But, as the discussion in this article should have made clear, it will not remove noisiness in the presence of a D.C. component in the input signal. The arrangement of Fig. 8 will, however, remove this trouble, too. Thus Fig. 8 is considered to be the ideal arrangement for the input to an amplifier if the volume control is to be situated there. This circuit pattern applies equally to valves and transistors.

Time Constants

Consider Fig. 9. Here we have a transistorised amplifier input circuit, following the scheme of Fig. 8 and with typical component values given. Suppose now we feed this amplifier from a signal source containing a D.C. component and having an internal resistance of 2M—for the purposes of illustrating the following argument with an intentionally severe example. The input electrolytic C3, of 50μF, will now need to charge up to its final resting potential difference through a total resistance of 2M. This represents a time constant of 100 seconds. Charging will not be complete

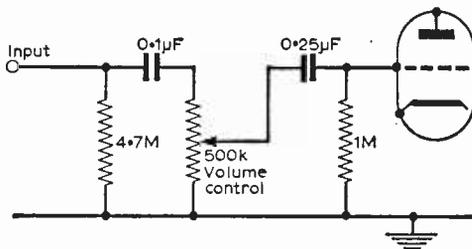


Fig. 8—The ideal input circuit for an amplifier if the volume control is to be situated at the input.

until three to five times this time. Thus it will take about five minutes. All this time D.C. will be flowing in the volume control track. The symptoms are thus that, upon switching on, the volume control will be extremely noisy, becoming gradually less and less so, until after some five minutes it will be quiet. This procedure will repeat itself every time the apparatus is switched on after a rest!

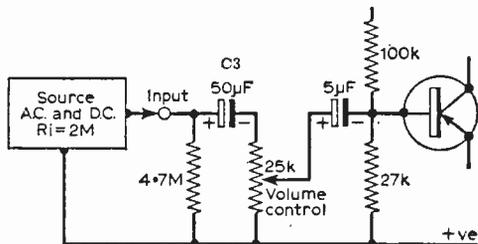


Fig. 9—Transistorised version of Fig. 8—in such a circuit, the large time constants need to be taken into account (see text).


This point is trivial for valve circuits where capacities of coupling condensers are so small that time-constants are normally smaller than the filament-warming-up times of the valves. But for transistors, where large capacities are common, the point must be watched.

However, an arrangement such as Fig. 9 is undesirable anyway on account of its large signal-attenuation (unless this is deliberately wanted). Furthermore, C3 is an electrolytic operating in a low-current, high-impedance circuit—or with a high-impedance-to-capacity ratio. Under such circumstances electrolytics have been known to function as electrolytic rectifiers, giving severe signal distortion. Thus, if a high-impedance source is to feed a low-impedance transistor input circuit, it is desirable to interpose a cathode-follower, an emitter-follower, or a transformer.

Intermittent Faults in Coupling Condensers

The author has had receivers in for repair where intermittent, or permanent, crackling (of low rumbling pitch) appeared alone or in conjunction with volume control crackling of the usual relatively high pitch. This type of fault is indicative of intermittent or randomly-variable leakage in a coupling condenser. The variability of this fault—i.e., its A.C. component, is shunted by the capacity of the coupling-condenser, removing higher harmonics; hence the low pitch.

MULLARD 3-3 HI-FI AMPLIFIER

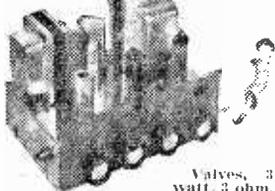

Valves, 3
Vult. 3 ohm.
and 15 ohm. Out-
put. A really first-class Amplifier
giving Hi-Fi quality at a reasonable
cost. Mullard's latest circuit.
Valve line up: EF86, EL84, E281,
Extra HT and EL84 for
Tuner Unit addition. This is the
ideal companion Amplifier for FM
tuner units.

TECHNICAL SPECIFICATION—
Freq. Response: ± 1db. 40 c/s.-25
Kc/s. Tone controls: Max. Treble
Cut 12 db at 10 Kc/s. Max. Bass
Boost 14 db at 60 c/s. Sensitivity:
100 Mv. for 3 w. output. Output
Power (at 400 c/s): 3 w. at 1% total
harmonic distortion. Hum and
Noise Level: At least 70 db. below
3 w.

COMPLETE KIT (incl. Valves, all
components, wiring diagram and
special quality sectional Output
Trans.). **ONLY £6.19.6**. Carr. 3/6.
Complete wired and tested, 8 pins.
Bronze Escutcheon Panel, Printed
Vol. Treble, Bass, On-Off,
supplied with each kit.

Wired O/P socket power and additional
smoothing for Tuner Unit,
10/6 extra. Speakers—WB
HF1012 95/- Goodmans AX10M
110 £6. etc.

SPECIAL BARGAIN OFFER

"6 plus 1" . . . using 3 latest type
surface Barrier
Transistors
RADIO KIT Now only £6.19.6
Complete Kit carr. 2/6.

**MANUFACTURER'S SURPLUS BARGAIN OFFER. PRICE
BARRIER SLASHER**—A further bulk purchase of this popular
Kit enables us to pass on latest price reduction direct to Construct-
or. Kit is a modern, sensitive, quality Receiver with all latest
circuit features and is complete with 7 x 3in. Speaker (3 ohms),
and 11 circuit and assembly instructions, 6 BVA Transistors and
Germ. Diode. Printed Cert. Med. and L.W. Ferrite Aerial and Car
Radio Coupling, 500 MW Output. Attractive Gilt dial and Slow
Motion Drive with "Clear VU" Tuning Knob, etc. Contemp.
two-tone Cabinets 9 x 5 x 3 1/2 in., as illustrated. 25/- extra.

RECORDING TAPE—Reduced Prices

Famous American Columbia (CBS) Premier Quality Tape at
NEW REDUCED PRICES. A genuine recommended Quality
Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted
with leader and stop lolls.

5in. Standard	Long Play	Double Play
5in. 600ft. 13/-	900ft. 17/6	1,200ft. 21/6
5in. 900ft. 16/-	1,200ft. 19/6	1,800ft. 27/6
7in. 1,200ft. 21/-	1,800ft. 28/6	2,400ft. 47/6

P. & P. per reel 1/-, Gd. on each additional reel.

SPECIAL BARGAIN. 3in. mfrs. Tape 225ft. 4/9. P. & P. 6d.
3in. Message Tapes 150ft. . . . 2/9. P. & P. 6d.
Plastic Tape Reels 3in. 1/3, 5in. 2/-, 3in. 2/-, 7in. 2/3
Plastic Spool Containers 5in. 1/6, 5in. 2/-, 7in. 2/3

**ENAMELLED COPPER
WIRE**—1lb. reels, 14s.-20s 2/6;
22s-28s 3/-; 30s-40s 3/6;
Other gauges quoted for.
Ersin Multicoiler Solder 60/40
3d. per yard. 2lb. 2/6, etc.

COAX 80 OHM CABLE
High grade low loss Collular
air spaced Polythene—1/4
diameter. Stranded cond.
Famous mfrs. Now only 6d.
per yard. Bargain Prices—
Special Lengths—
20 yds. 9/-, P. & P. 1/6.
40 yds. 17/6, P. & P. 2/-.
60 yds. 25/-, P. & P. 3/-.
Coax Plugs 1/-, Sockets 1/-,
Couplers 1/3, Outlet Boxes 4/6.

Volume Controls—5K-2 Meg-
ohms, 3in. Spindles Morgan-
ite Midget Type 10in. diam.
Guar. 1 Year. LOC or LIN
ratios less Sw. 3/-, DP. P. Sw.
4/3. Twin Stereo less Sw.
6/6. DP Sw. 8/-.



COLLARO STUDIO TAPE RECORDER KIT

SPECIAL BARGAIN OFFER. Comp. Kit only £25.0.0
Carr. 12/6.

Famous mfrs. surplus offer—Listed 42 mfrs. A quality Tape Recorder
Kit based on Mullard famous design—EF86, ECC83, EL84, EM84
and Rectifier. Specially designed Kit for Collaro latest Studio
Deck. Freq. response ± 3db. 7in. per sec. Amp. and Power Pack
straight, inter. unit wiring only required. Cabinets size: 18 x
16 x 8 1/2 in. finished in contemp. 2 tone blue Rexine with gilt
Speaker Escutcheon. Magic Eye Indicator Circuit and 7c.t.
1/1 Book, supplied free with kit. Send 2/6 now for full details
of our own's outstanding Tape Recorder Bargain.


Cabinet £3.15.0 P. & P. 6/6.
Amplifier Kit £8.19.6, P. & P. 5/-.
Speaker 7 x 1 1/2 in. P. & P. 1/-.
If above items are purchased
together.

£12.19.6 P. & P. 10/-.

**BARGAINS
4-SPEED PLAYER
UNITS**

Single Players Carr. 3/6
Garrard 4 S.P. £6.19.6
Garrard TA Mk.2 £7.19.6
Collaro "Junior" 75/-
B.S.R. Latest TU12 79/6
E.M.I. Junior '955' 89/6

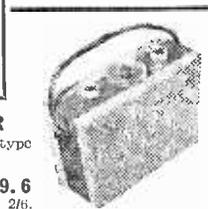Auto-Changeers Carr. 5/-
Collaro "C 60" £7.15.0
B.S.R. (UA14) £7.10.0
Garrard "Auto-slim" £8.12.6
Garrard Model RC289 9/- gns.



**RECORD
PLAYER
CABINETS**

Cabinet
Price

£3.3.0.

Carr. &
Ins. 3/-



Contemporary style, rexine covered
cabinet in two tone maroon
and cream. Size 18 x 13 x 8 1/2
in., fitted with all accessories
including baffle board and anodised
metal fret. Space available for all
modern amplifiers and autochan-
gers, etc. Uncut record player
mounting board 14 x 13in. supplied.

2-VALVE 3-WATT AMPLIFIER
Twin stage ECL82 with vol. and neg.
feedback tone control. A.C. 200
250 v. with knobs, etc., ready wired
to fit above cabinet. £2.17.6.

3in. Spkr. & Trans. 22/-, P. & P. 2/-
Complete Kit, including UA14 Unit
as illustrated, £12.19.6. Carr. 7/6.

SINGLE PLAYER KIT—Similar
spec. to Autochanger Kit except
Player is 4-speed B.S.R. T.U.O.
Single Record Player Unit. At-
tractive Contemporary Styled Cab-
inet. Size: 13 x 13 x 8 ins. with
splendid volume and reproduction.
Bargain Price. £8.19.6 only. Carr.
5/-, All units ready wired. Simple
screwdriver assembly only.

Condens-ers—Silver Mic. All
values, 2P to 1,000Pf. 6c. each.
Ditto. Ceramics 9d. Tub.
450V T.C.C., etc., 0.001 mid. to
0.01 and 0.1/350V. 9d. 0.02-
0.1/500V 1/-, 0.25 Hunts 1/6.
0.5 T.C.C. 1/9, etc., etc. Close
Tol. S/Meeas—10% 5Pf-500Pf
8d. 600-5,000Pf 1/-, 1% 2Pf-
100Pf 9d., 100Pf-500Pf 11d.
575Pf-5,000Pf 1/6. Resistors—
Full Range 10 ohms-10 meg-
ohms 20% j and j W 3c., 1W 5d.
(Midget type modern rating)
1W 6d., 2W 9d. Hi-Strap 10%
1W 5d., 1W 7d. 5% 1W 9d.,
1% 4W 1/6.

JASON FM TUNER UNITS
Designer-approved kits of
parts.
FM11, 5 gns. 1 valves, 20/-
FM12, 27. 5 valves, 37/6.
JTV MERCURY 10 gns.
JTV £13.19.6. 4 valves,
32/6.

**NEW JASON FM HAND-
BOOK**, 2/6. 48 hr. Alignment
Service 7/6, P. & P. 2/6.

TYGAN FRET (contemp. pat.)
12 x 24in. 2/-, 12 x 18in. 3/-,
12 x 12in. 4/-, 18 x 24in. 6/- etc.

Speaker Fret—Expanded
bronze anodised metal fin. x
1in. diamond mesh, now 4/6
sq. ft., Multiples of 6in. cut
max. width. 4ft.

Electrolytics All Types	New Stock	TUBULAR CAN TYPES
25/25V	1/9	8+8/450V 4/6
50/12V	1/9	8+16/450V 5/6
50/50V	2/-	32+32/275V 4/6
100/25V	2/-	50+30/350V 5/6
8/450V	2/3	60+4/250V
16/450V	5/6	275V 12/6
16+16/45V	5/6	100+200/
32+32/450V	6/9	275V 12/6

Transistor Components

Midget I.F.'s—465 Kc/s.
9/16in. dia. 5/6
Osc. Coil—M/W, 9/16in. dia. 5/3
Osc. Coil—M. & L.W.
Midget Driver Trans. 3.5:1 6/9
Midget O/P Trans. P.P. to
3 ohms, 6/9.
Ferrite Aerial M. & L.W. Car
aerial coil, 9/3.

Elect. Condensers—Midget
Type 1 mid-50mf. ea. 1/8.
100mf. 2/-, 12V wkt.
Condensers—0.1 mid. to .04mf
9d.; .05 mid. to .1mf. 1/4; .25mf
1/3; .5 mid. 1/6.

9 Pinning Condensers—"JB" "OO"
208 Pf. + 176 Pf. 8/6, with Trimmer
3/6, Single 365Pf 7/6, Sub
min. fin. J.B. Dile min. .0001.
.0003 or .0005 7/- each.
Midget Vol. Control—with
edge control knob. 5K ohms
with switch, 4/9, less switch 3/6.
Speakers P.M.—2in. Plessey
75 ohms 15/6, 2in. Continental
6 ohms 13/6, 2in. E.M.I. 3
ohms 17/6, 7 x 4in. Plessey
35 ohms 23/6.
Ear Plug Phones—Min. Con-
tinental type. 3it. lead, jack
plug and socket. High Imp. 8/-,
Low Imp. 7/6.

TRANSISTOR BARGAINS

Brand	New—BVA	1st Grade
OC44	10/6	OC114 6/6
OC45	9/6	OC72 7/6
OC81	7/6	OC70 7/6
2C081	15/6	OC71 8/-
XA102	10/-	OC78 7/6
XA101	9/6	OCX34 2/9
XB103	7/6	OA70 7/6
XC101	8/6	OA81 2/9
Special offer: One OC44, two OC45, 2/18. One OC81, two OC81's (matched pair) 19/6.		

Send for detailed bargain lists. 3d. stamp.
We manufacture all types Radio Mains Transi. Chokes, Quality O/P Trans., etc.
Enquiries invited for Specials, Prototypes for small production runs. Quotations
by return.

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m. - 6 p.m., 1 p.m. Wed.
THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1lb. 9d.; 1lb., 1/3; 3lb.
2/3; 5lb., 2/9; 8lb., 3/6.


20,000 o.p.v. Pocket Size Taylormeter 127a

Adopted by the G.P.O.

OUTSTANDING FEATURES

- ★ Sensitivity: 20,000 o.p.v. D.C., 1,000 o.p.v. A.C.
- ★ Very Robust—Shock proof moulding
- ★ Portability
- ★ 20 Ranges
- ★ D.C. current: 50 μ A, 10mA, 100mA, 'S' socket for D.C. shunts
- ★ Volts D.C. 0.3, 2.5, 10, 25, 100, 250, 1,000V (25kV by probe)
- ★ Volts A.C. 10, 25, 100, 250, 1,000V.
- ★ 3 Resistance Ranges: from 0-20 megohms (self-contained)
- ★ 40 μ A Meter 3 $\frac{1}{2}$ in. arc.
- ★ Accuracy: D.C. 3%, A.C. 4%

price £10.10.0

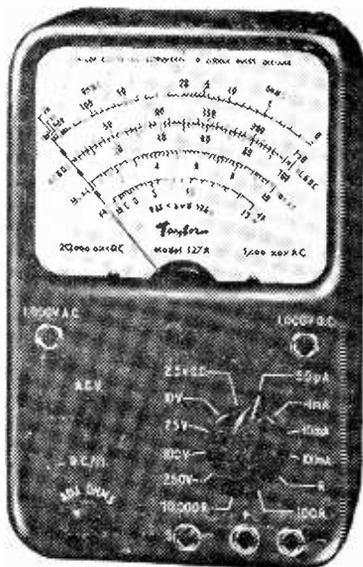

Write for fully illustrated catalogue to:

TAYLOR ELECTRICAL INSTRUMENTS LTD.,

MONTROSE AVENUE, SLOUGH, BUCKS.

Tel.: Slough 21381 Cables: Taylins, Slough



“CODAR CLIPPER” ALL BAND RECEIVERS 10-2000 METRES

LISTEN TO AMATEURS, AIRCRAFT, SHIPPING, SHORT, MEDIUM, LONG WAVE BROADCAST STATIONS THROUGHOUT THE WORLD.

THE MINI-CLIPPER

The ORIGINAL and finest one valve all band receiver. Outstanding performance. New first grade components ensure top efficiency. Low loss air spaced tuners, high gain polystyrene plug in coils. Satin Silver metal panel with engraved dials, grey pointer knobs. Provision for adding 2 transistor amplifier stage. Chassis ready punched. Total building cost, all parts, one coil 20-60 meters, wire solder full plans, 36/6. P. & P. 2/6. Other coils 10-2000 meters and electrical bandspread available. Parts sold separately. Plans and parts list, 2/-.

NEW LOW PRICE 36/6




THE SUPER CLIPPER 88/6

This world-famous hybrid receiver has achieved remarkable success. Tremendous performance with Hi-gain valve detector PLUS two Ediswan transistor amplifiers which are supplied assembled, only 3 wires to connect. Large precision dial, 7 x 4in., with 2 pointers, bandset and bandspread, dual slow-motion drives air spaced variables. Punched chassis 8 x 5 $\frac{1}{2}$ in. Batteries last months. Covers 10-2000 metres (5 coils). Total building cost including chassis, valve, 2 transistor stages, 2 coils 20-60 and 55-190 metres. Step-by-step pictorial plans, nuts, bolts, wire 88/6. P. & P. 2/6. Plans only, 2/6. THE CLIPPER. As above but one transistor stage, 79/6. P. & P. 2/6. Optional Front Panel, Silver Hammer finish, all holes, 6/9.



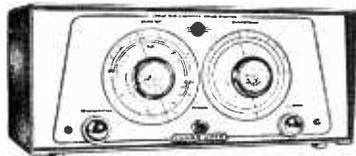THE NEW CR45 ★ NEW STYLING TOP PERFORMANCE



Previously produced exclusively for Export, the de-luxe version of this famous ALL BAND receiver is now also available for the home market. Superb new styling, satin silver front panel, frequency calibrated scales, grey and silver trim knobs, perspex disc cursors. High gain circuit with ECC81 duotriode, EL84 output, EZ80 full wave rectifier. Power output 3 $\frac{1}{2}$ watts for 2/3 ohm speaker. 3 Planetary vernier slow motion drives, separate electrical bandspread. Covers 10-2000 metres (5 Coils). World wide reception. For A.C. supply 200-250 volts (Export version 105-120 volts). Total building cost all parts, valves, front panel, ready punched chassis, 2 coils, 20-60 and 55-190 metres, wire, solder, instruction manual, P. & P. 3/6. Optional extra. CR45 Cabinet 12 x 5 x 7in., slide flap for easy coil changing, Silver grey finish, 27/6.

£6.19.6


No technical knowledge required to build these fine receivers. Send 3d. stamp for illustrated leaflets, testimonials, etc. Now available the NEW 1962 CR 66 A.C. SUPERHET COMMUNICATION RECEIVER.

CODAR RADIO COMPANY, 24 CHAPEL ROAD, FISHERGATE, PORTSLADE, BRIGHTON

G3IRE

Canadian Distributors: JAYCO ELECTRONICS, TWEED, ONTARIO.

G3IPA

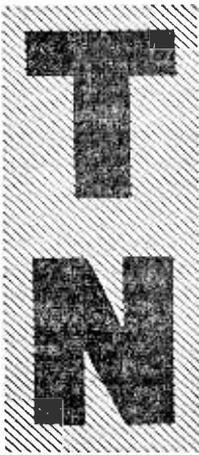


Trade News

TRANSISTOR PORTABLE

A NEW six-transistor pocket portable receiver has been introduced on to the market recently by Pam (Radio and Television) Ltd. The printed circuit gives a maximum output of 45mW through a 2in. loudspeaker. This set will tune over the medium wave band and also provides the Light programme on long waves.

The dimensions of the receiver are 4in. x 2½in. x 1in. and the grey polystyrene cabinet has a fascia of white and gold. A socket is provided in the cabinet for a 10Ω impedance ear-piece.

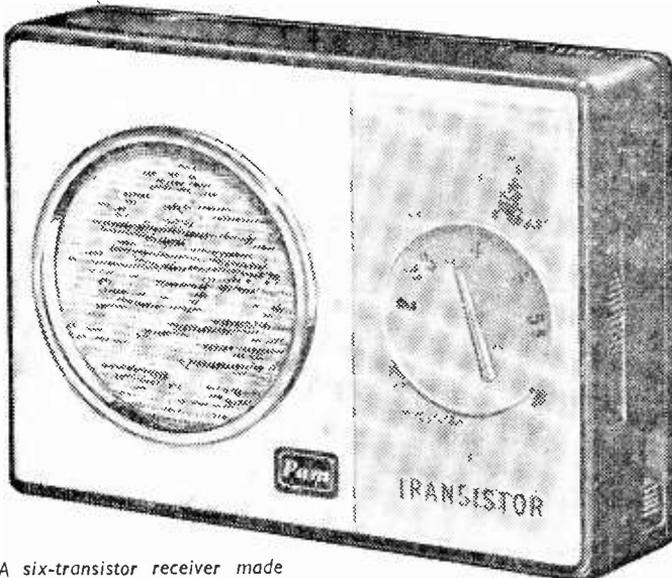The power for the set is supplied by three 1.5V cells, giving a total of 4.5V. The price of the set is 10½ guineas and an optional carrying case is available at 7s. 6d. extra. *Pam Radio and Television Ltd., 295 Regent Street, London, W.1.*



A six-transistor receiver made by Pam Ltd.

POWER DISTRIBUTION UNIT


THE latest addition to the range of distribution boards made by Lexor Electronics Ltd., is the 'Dis-board' portable unit.

This unit is available in 2-, 4- and 6-way groups of 5, 13 or 15A sockets. The finish can be either in brown or ivory and the sockets may be switched or unswitched.

There is a wide variety of extension cables and plugs which can increase the usefulness of any particular unit. The 'Dis-board' is connected to the mains outlet by a length of heavy-duty flexible cable.

List prices range from £3 9s. 6d. to £5 19s. 0d. and all standard combinations (and the available combinations and types now exceed 300) are available from stock.

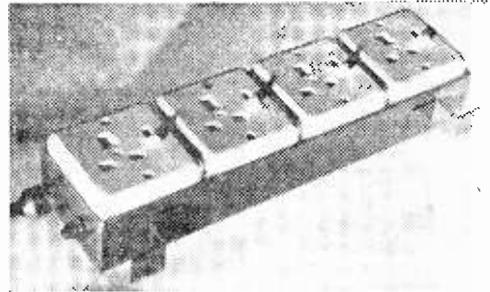The manufacturers are *Lexor Electronics Ltd., 25 Allesley Old Road, Coventry, Warwickshire.*



A 4-way distribution unit from Lexor Electronics Ltd.


STABILISED POWER SUPPLY

THIS Heathkit power supply kit—model MSP-1—has been developed by Daystrom Ltd.

The stabilised D.C. output is variable over a range from 200 to 410V. by a control mounted on the front panel. Separate transformers are used for H.T. and L.T. supplies and Mains H.T. supplies are indicated by two neon lamps. A 3-position off/stand-by/on switch enables the D.C. outputs to be switched off while leaving the heater supplies connected. The unit also features an unswitched 6.3V A.C. centre-tapped output at 4.5A.

Two models are available, one with meters and one without. In the former model, the meters are 3in. moving coil instruments; a voltmeter reading 0-400V, and a milliammeter reading 0-25mA.

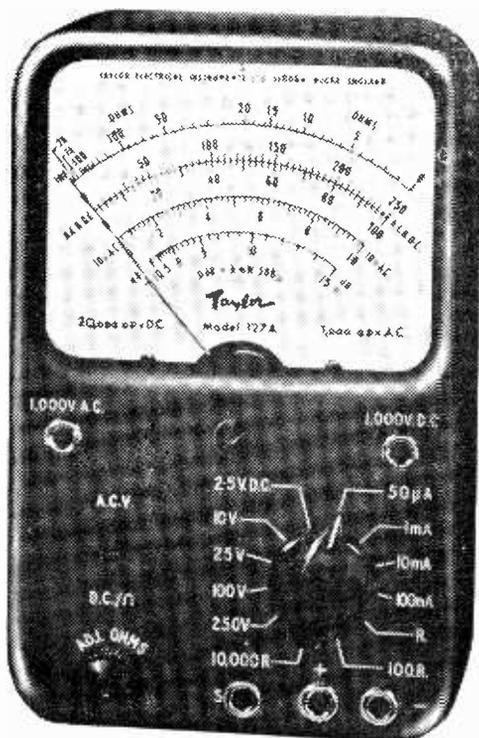The unit is of all steel construction and the cabinet is louvred to ensure adequate ventilation. The dimensions of the cabinet are 13in. x 8½in. x 9½in. The kit is made by *Daystrom Ltd., Gloucester.*




(Above) The model 127A Taylor Multimeter.

TRANSISTOR CLIPS

RECENTLY made available from the Plessey Co. Ltd., are two transistor clips (types A and B), which are intended for 5 or 6mm nominal diameter transistors.

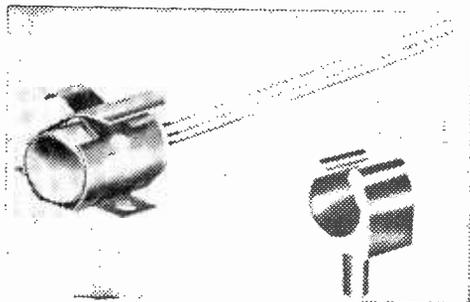The type A clip is moulded in virgin polythene which incorporates a high density pigment to eliminate absorption of ultraviolet radiation. This pigment also serves to identify the two sizes of clip—black for 5mm and brown for 6mm diameter transistors. The poly-



New Plessey transistor clips.

thene used is completely inert and will not affect protective coatings on either metal or glass based components. Tests indicate that these clips do not limit transistor heat dissipation and can be used over a range of ambient temperatures from -55°C to $+70^{\circ}\text{C}$.

Type B is formed from beryllium copper, hardened by heat treatment. One clip covers both 5 and 6mm diameter transistor units.

The Plessey Co. Ltd., Ilford, Essex.

IMPROVED MULTIMETER

AN improved version of the Taylor 20,000Ω/V pocket size multimeter (model 127A) has been recently announced.


A feature of the new model is the facility for measurement of high D.C. The instrument now has a special "millivolt" socket and a range of "plug-in" miniature shunts is now available for readings of 1, 5 and 10A D.C. These shunts are designed to locate directly into the millivolt sockets incorporated in the Model 127A, thus forming a compact unit for measurement of high D.C. current.

A new type of ohms adjust control is now fitted which ensures greater stability and an improved type of A.C./D.C. selector switch is also incorporated.

The instrument is made by *Taylor Electrical Instruments Limited, Montrose Avenue, Slough, Buckinghamshire.*

COMMUNICATIONS RECEIVER

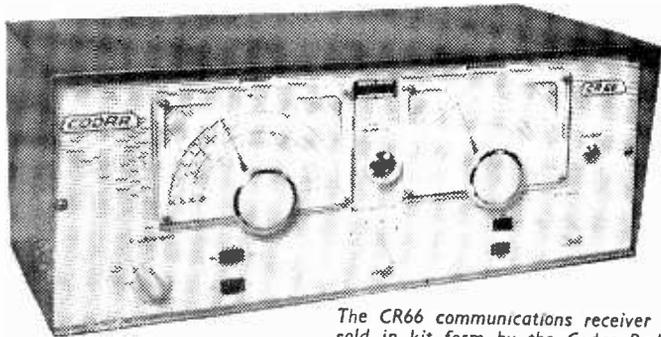THE model CR 66 is a new communications receiver kit from the Codar Radio Company.



The CR66 communications receiver is sold in kit form by the Codar Radio Company.

The CR 66 covers a frequency range from 540kc/s to 30Mc/s in four ranges. The separate main tuning is calibrated in frequencies and the bandsread is calibrated in degrees. The circuit includes a regenerative I.F. stage for maximum gain and BFO for C.W. reception.

The size of the cabinet is 16in. x 6½in. x 8½in. and the front panel is finished in silver and black. An output socket is provided for tape recorders etc. and also one for an external speaker.

The total cost of parts, less the cabinet, is £16 10s. and the cabinet costs £1 15s.

The kit is made by the *Codar Radio Company, Colebrook Road, Southwick, Sussex.*

RADIO CLEARANCE LIMITED

27 TOTTENHAM COURT ROAD, LONDON, W.1.

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE

TRADE ENQUIRIES INVITED

Telephone: MUSEUM 9188

EST. 30 YRS.

**YOU CAN
HOLD EUROPE
IN THE PALM
OF YOUR HAND
WITH THE**



"CAPRI"

A miniature pocket transistor Radio that **REALLY** works, retaining the most attractive features of the famous "Contessa." Six first-grade Mullard transistors plus diode are employed in a highly sensitive superhet MW and pre-set LW circuit embodying the most modern design practices. A special 2½ in. high gauss loudspeaker provides surprising volume and a personal earpiece socket is also available. An attractive two-tone plastic case is supplied in two colours—ivory/red or ivory/blue, the full constructional details being furnished with each set of parts. The total measurements of the "Capri" are 4½ x 2¼ x 1¼ in.

SEE AND HEAR A WORKING MODEL TODAY

Inclusive price for all associated components, case and constructional data, complete in every detail, or our BUY AS YOU BUILD scheme. **£7.10.0** any parts sold separately, (9 volt battery 2/6 extra.) (Plus 2/- P. & Pkg.)

INTRODUCING THE NEW "CONTESSA"


Mk III

The Best is Now Even Better! A brilliant conception of the finest 2-band 6-transistor radio available.

★ Ultra-modern styling with a magnificent twin-tone cabinet fitted with fully expanded metal front and a slide-rule type waveband dial. **GREATHER OUTPUT** using the latest high-efficiency Mullard Transistors and Diodes, incorporating an improved design, featuring different circuit constants.

MORE punch—MORE gain—MORE stations—SUPERB appearance—the NEW "Contessa" scores again!!

SEE it—HEAR it—you will BUY it!

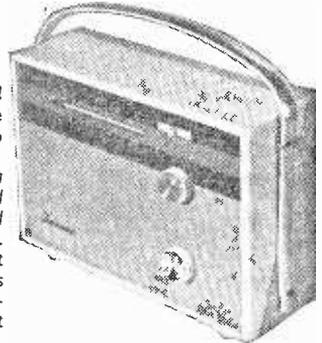

- Waveband coverage of 530 kc/s to 1,620 kc/s and 160 kc/s to 270 kc/s.
- Assured reception of at least a dozen stations in daylight!
- Large clearly-calibrated station-named dial.
- Internal high-gain Ferrite aerial.
- 5:1 ratio slow motion tuning.
- Fitted with the latest £2,000-line high-flux loudspeaker.
- Power of 600 milliwatts from the single-ended push-pull final stage.
- Specially designed aerial matching coil for use in a CAR.
- Only first-grade Mullard fully-guaranteed matched transistors and diodes are used.
- Tape recorder socket provided.
- Double-tuned IF transformers for maximum gain and knife-edged selectivity.
- Fully drilled printed circuit panel marked with component numbers.
- The two-tone case outer measurements are 10½ x 7½ x 3½ in. and weighs approx. 4 lbs. when assembled.
- Battery lasts 4 months with normal usage.
- Book supplied with detailed assembly instructions, diagrams and circuitry.
- Anyone can build this set—everything supplied, just a soldering iron required.
- Cabinets available in two tone beige and two tone blue.
- Adjustable carrying handle.

Inclusive price for all associated components, cabinet and battery complete, in every detail: Or our BUY AS YOU BUILD SCHEME, any part sold separately. **£10.19.6** send for comprehensive descriptive Manual and Parts List, 2/10 post free. (Plus 3/6 P. & Pkg.)

CRASHING the PRICE barrier with SOUND!

This superb MAGNAVOX TM800 "Magitape" outfit ready to switch on for only

- A** The latest world-famous Collaro-Magnavox Studio Tape Transcriber. 3 speeds 11-31-74 l.p.s. 2 tracks (spools not supplied), direct from the Manufacturers at..... **£6.19.6**
- B** Magnavox Amplifier to match above with Valves, interconnecting plugs and sockets, fully wired. Direct from the Manufacturers at..... **£3.10.0**
- C** Power Supply to match above (only sold with A & B) with interconnecting plugs and sockets, rectifier, fully wired. Direct from the Manufacturers at..... **£1.10.0**
- D** Separate components for Power Supply including Mains Transformer, Smoothing, Plugs and Sockets etc. etc. **15/- ONLY**

£11.19.6 Don't miss out on this amazing bargain offer—it cannot last long!

ROCK BOTTOM PRICES QUOTED ABOVE APPLY EVEN TO THE TRADE!

Items A, B and D can be sold separately but we regret CALLERS ONLY owing to suitable packing not being available.

STAMPED and ADDRESSED ENVELOPE with any enquiry please. But regret no lists or catalogues—our stocks move too quickly! PLEASE ALLOW FULL POSTAGE AND PACKING CHARGES

Terms of Business: **CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-.**



RS12/DD

A 12" SPEAKER for the HOME CONSTRUCTOR

A fine 12" Speaker employing a new type of double diaphragm and magnet assembly, the RS12/DD has been designed with the home constructor in mind—it is one of the few 12" models suitable for use in compact enclosures enabling a really high quality system to be assembled at a modest price.

Some important features of the RS12/DD—

Very low bass resonance
Synthetic Centring Device
Ceramic Magnet
Die-cast Chassis
Foam edge Damping
One-piece HF Flare Dome
Airtight impregnated Roll
Surround

£11.00 TAX FREE



Complete the coupon for technical specification of the RS12/DD including Constructional details of suitable cabinets.

Post to Wharfedale Wireless Works Ltd.,
Idle, Bradford, Yorkshire

NAME
ADDRESS

PW

SOLDERING EQUIPMENT

by



PRECISION SOLDERING for the ELECTRONICS INDUSTRY

Comprehensive range—Robust & Reliable
- Light weight - Rapid heating - Bit sizes
3/32in. to 3/8in. - 'Permagit' or Copper
bits - All voltage ranges 6/7v. to 230/
250v. - Prices from 21/-.

Also

- Plastic Cable Strippers
- Miniature Solder Pots
- Heat Guards
- Long Life Bits

Illustrated is the 25w. 3/16in. replaceable
bit model with safety shield.

ADAMIN— new range of pre-
cision micro-soldering instruments—
Have you had details?

Brochure No. S10 sent free on request.

Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, Surrey

Phone: CROYdon 8589 Grams: Litesold Croydon

BENSON'S BETTER BARGAINS TRANSISTORS

The bulk-purchase of a manufacturer's "closing-down" stock
enables us to make the following outstanding offer:—

NEW 16 TRANSISTORS for £1

These are all uncoloured and unbranded but tested by us before
packaging and despatch. Many are equivalents to the following
Ediswan, etc., types:—

NA101; NA102; NB102; NB103; NB104 "Tophats"
NA111; NA112; NB112; NB113; NB114; "Tubulars"
XC101; XC111. Above types BRANDED, at 4/- each.
Although no guarantee is given to this effect, Purchasers can
expect R.F., L.F., F.C., and L.F. types in the parcel.

This offer is made subject to NO correspondence being entered into
regarding types and data appertaining thereto and strictly CASH-
WITH-ORDER.

FURTHER—an equivalent to XC141 is available, at 7/6.
CRYSTAL DIODES 5/- DOZ.

A DISCOUNT OF 25% IS GIVEN ON £20 ORDERS.

SUPER RADIO (W'CHAPEL) LIMITED (W.W.), 116, WHITECHAPEL, LIVERPOOL 1.


Phone: ROYal 1130.

BATTERIES, mercury, TR115, 4.5 v. 30 mA, 6/-. WAVEMETERS
Class "1" No. 1, new condition, 65/-. CONDENSERS, Block paper, 8/600 v.
8/8; 8/400 v. 5/-; 8/250 v. 4/-; 4/2 kw 7/6. MOUSE KEY with buzzer,
XC101, 11/6. 6 v. to 250 v. 100 mA, 11/6. TRANSFORMERS. For
on board, wired for 4 1/2 v. battery, 8/8 (post 4/-). VIBRATORS, Input 10-0-11 v.,
R1132 or R1392 25/- (post 4/-). VIBRATOR TRANS. Input 10-0-11 v.,
output 265-0-265 v. 65 mA, 7/6 (post 1/9). NEW M.C. METERS, 2 1/2 in.
round flush, 200mA centre zero, 50/-; 1 mA, centre zero, 45/-; 1 mA, 55/-;
2 1/2" 100 mA, 8/6; 2 1/2 in. 300 mA, each 8/6; 150 v. A.C. M.I. tin in case,
40/-. VIBRATORS, Maltory 0634C 12 v. 4-pin, 7/6; 12 v. 7 pin 1/8.
10/6; 7 pin rev. 10/6; 6 v. 5-pin reversible, 7/6. DRIVES: Slow-motion
Admiralty 200: 1 ratio scaled 0-100, 5/6. R1155 S.M. "N" type, new,
10/6. VIBRAPAKS 6 v. D.C. to 250 v. 60 mA, smoothed, case, 22/6;
12 v. input, 25/- (p.p. 4/-). DYNAMOTORS (post 4/-), 12 v. to 250 v.
60 mA, 11/6. 6 v. to 250 v. 100 mA, 11/6. CHOKES, L.F. 10 H., 200 mA,
8/6; 100 H., 60 mA, 8/6; 9 H., 100 mA, 5/8; Potted 10 H., 100 mA, 7/6;
"C" 10 H., 250 mA, 12/6; 5 H., 400 mA, 10/8; 30 H., 50 mA, 7/6.
SWITCHES: Wafer, 2 pole, 4 way, 4 bank, 3/6 each.

LINT AND ENQUIRIES S.A.E., please. Terms: C.W.O. Postage extra.
Immediate despatch.

Post: W. A. BENSON (W.W.), 136 Rathbone Road, Liverpool, 15. SEF 6553.
OTHER THAN TRANSISTORS.

THE CONSORT TRF RECEIVER

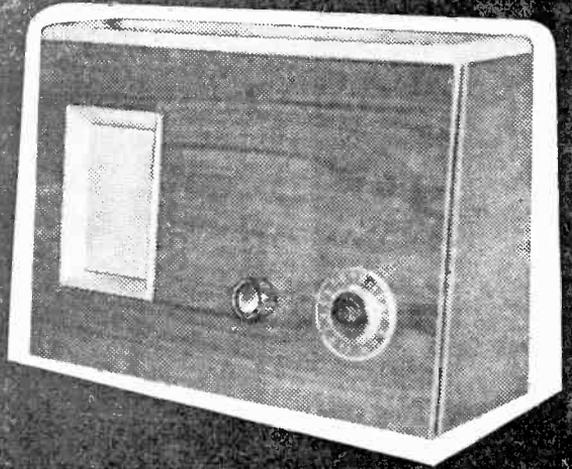

(Continued from page 294 of the August issue)

By B. Lewisham

In last month's article a description of the circuit was followed by details of the construction

of the chassis. Now the constructor may proceed to the next stage, which is wiring.

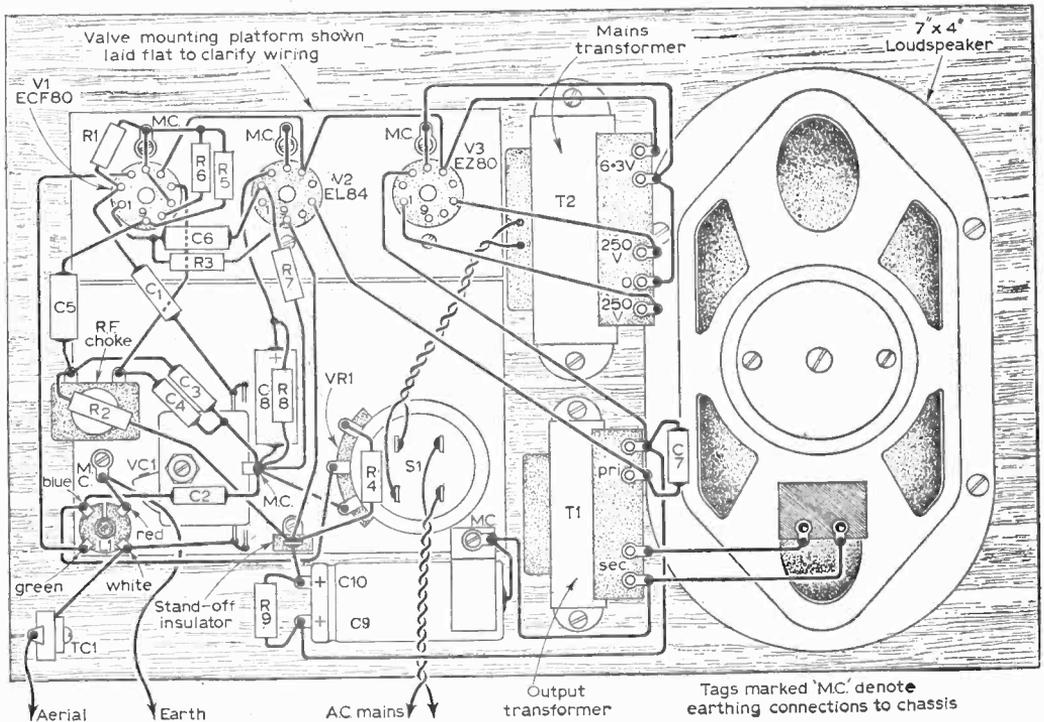


Fig. 4—The complete wiring diagram.

The chassis of the receiver can be wired up independently of the remainder of the circuit. Wiring is simple but the valveholders are best attended to first. In the layout and wiring diagram (Fig. 4), the valve platform is shown pressed out flat so that the underside connections may be seen clearly. Use of modern miniature capacitors and resistors is desirable in order to prevent undue congestion and the electrolytic decoupling capacitor, C8, should be a miniature type.

Testing

The usual tests and checks for faults in the wiring, etc. are made with a testmeter prior to switching on, particular care being taken to ensure that the mains wiring is correct. A three-pin plug should be fitted to the end of the mains lead in the correct sense and a pair of attractive control knobs fitted to the receiver. If all is in order, the receiver may be switched on and an aerial (a few feet of wire will do) connected. It should then be possible to tune in various transmissions by operating VCI and VRI judiciously, care being


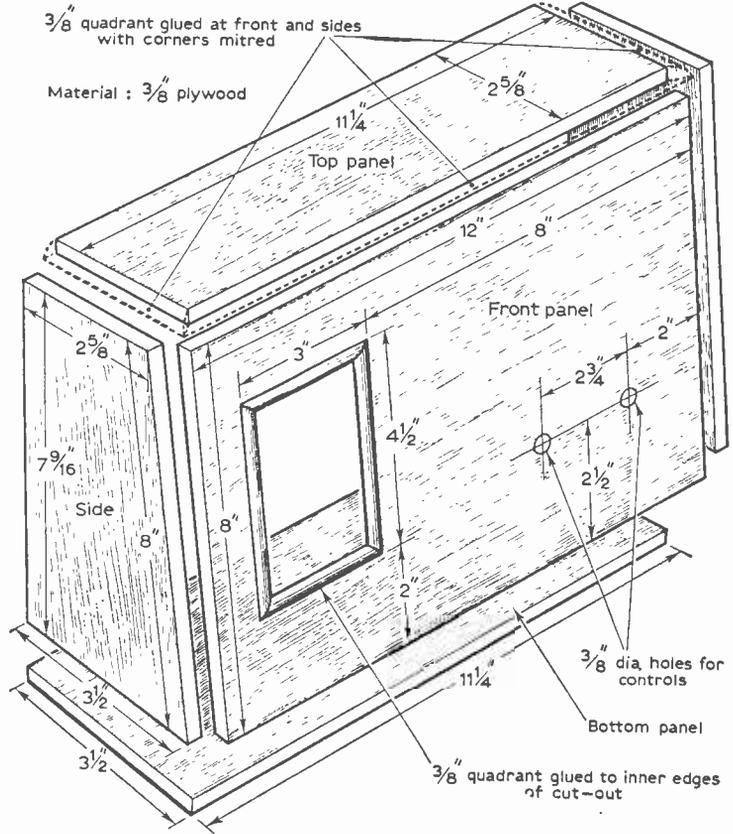


Fig. 5—The method of construction used by the author in making a suitable cabinet for the receiver.

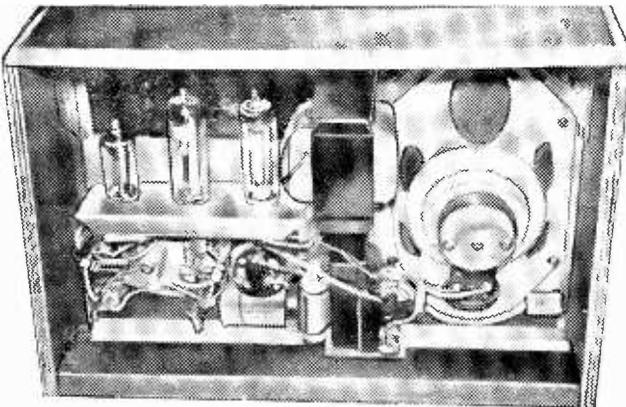

A view of the interior of the completed set.

taken not to let the receiver oscillate. The precise setting of TCI will depend upon the aerial in use, location, etc. but the best position can soon be found by experiment, the smallest capacitance possible probably giving the most satisfactory

results over the band. The value of C7 can also be altered experimentally; for example, if reproduction tends to be shrill, the value may be increased to 5,000pF or more as required.

Housing the Receiver



All the woodwork dimensions required are shown in Fig. 5. The sides are glued to the inside of the panel and are held securely by metal "L" brackets; wooden reinforcement blocks will also serve just as well. Quadrant (3/8 in.) is glued to the top of the panel and sides to form a frame mitted at the front corners. Similarly, quadrant is fitted to the inside edges of the loudspeaker aperture.

REMEMBER TO BUY
OUR COMPANION JOURNAL
PRACTICAL TELEVISION
 1/9 Every Month

UNIVERSAL AVOMETERS

Guaranteed perfect working order. Supplied complete with leads, batteries and instructions.

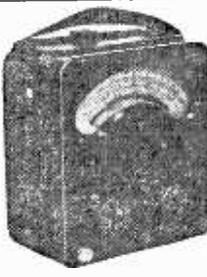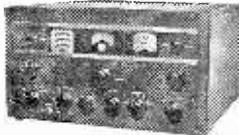Model "D" 34 range £8.19.6 each
 Model "7" 50 range £11.5.0 each
 Model "g" 20,000 ohm/volt model 15/- Gns.
 Registered post 5/- extra.



R.C.A. AR.88 RECEIVERS

Model AR.88 D. Frequency coverage on 6 bands. 550 kc/s to 32 Mc/s, £35 each. Model AR.88 L.F. Frequency coverage on 6 bands. 75 kc/s to 550 kc/s and 1.5 Mc/s to 30 Mc/s, £32.10.3 each. Both models operate on 110/200/250 volt A.C. Supplied fully tested and checked and in excellent condition. Carriage 30/- extra.

AMERICAN C.B.S. TAPES

5in. std.	600ft.....	13/-
5in. L.P.	900ft.....	26/6
5in. D.P.	1200ft.....	32/-
5in. std.	900ft.....	16/-
5in. L.P.	1200ft.....	19/6
5in. D.P.	1800ft.....	37/-
7in. std.	1200ft.....	21/-
7in. L.P.	1800ft.....	29/6
7in. D.P.	2400ft.....	47/-

Brand new and guaranteed. Please add postage. S.A.E. for full list.



24 VOLT D.C. PUMPS

100 gph impeller type. Suitable for water. 15/6 each. P. & P. 2/6.

MINE DETECTORS No. 4A

Will detect all types of metals. Fully portable. Complete equipment supplied tested with instructions, 39/6. Carriage 10/6. Battery 8/6 extra.



PRECISION COMBINATION VOLTMETER/AMMETER FOR A.C. AND D.C.

Two separate instruments housed in polished wood case. 6in. scales with knife edge pointers. Ranges:

Volts A.C. and D.C. 160-300-600v.
 Amps A.C. and D.C. 25-50-150-200A.

Supplied complete with all current shunts, leads and leather carrying case. Manufactured by Elliott Bros. Supplied brand new. £9.19.6 each. Carriage 7/6.

FIELD TELEPHONES TYPE "F"

Ideal for all inter-com systems, house, garage, office, building sites, etc. Generator bell ringing, 2-line connection. Supplied complete with batteries and wooden carrying case, fully tested. £4.19.6 per pair. Carr. 5/-.



BC-221 FREQUENCY METERS

Frequency coverage 125 kc/s to 20 Mc/s. Complete with crystal, valves and calibration charts. First class condition. Price £7.19.6 each. Available only to personal shoppers.

DUMONT K105 IP1 DOUBLE BEAM C.R.T.

Brand New. Boxed. 59/6 each. Carriage 3/6.

1 INCH C.R.T.

Ideal for small scopes. 4v. Heater. Brand New. Boxed. 15/6 each. P. & P. 1/6.

P.C.R. COMMUNICATION RECEIVERS

6 valves. Frequency coverage on 3 bands: 850-2,000 metres, 190-550 metres and 6-13 Mc/s. Super slow motion drive. A.E. trimmer, tone control, built in speaker. AS NEW £6.19.6 each. Carr. 7/6.

P.C.H. 2 KHz T.V. SETS

850-2,000 metres, 190-550 metres, 6-2 Mc/s. Output for phones or 3 ohm speaker. AS NEW £5.19.6. Carr. 7/6. Both above models can be supplied with internal power unit to operate on 200/250 v. A.C. at 39/6 extra or alternatively plug-in external power units are 35/-.




NATIONAL H.R.O. RECEIVERS

BRAND NEW! Senior model, table mounting. Complete with a full set of 9 coils covering 50 kc/s to 30 Mc/s. Supplied in original transit cases. £25. Carr. 20/-.

1kV.A. ISOLATION TRANSFORMERS

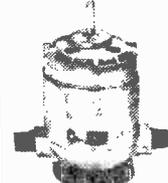230v. pri., 230v. sec. Boxed. £5. Carriage 10/-.




JEMCO 20,000 OHM/VOLT TEST METER

D.C. and A.C. volts up to 1,000v. Current up to 500 mA. Resistance up to 5 megohm. Decibels from -20 to +36 dB. Supplied brand new, guaranteed with instructions, leads and battery. 5 gns. P. & P. 2/6.



230/250 VOLT A.C. MOTORS

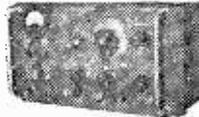Size 4 1/2 in. x 3 in. dia., 90 watt rating, 5,000 r.p.m., 1/4 in. drive spindle. Brand new. 22/6 each. P. & P. 1/6.



CT-53 SIGNAL GENERATORS

Precision instruments covering 8.9 to 15.5 Mc/s and 50 to 300 Mc/s on 6 bands. Variable attenuator from 1 microvolt to 100 millivolts. Operation 110/200/250 volt A.C. Supplied in perfect working order complete with calibration charts. 10 gns. each. Carriage 10/6.

★ PRECISION A.C. & D.C. VOLTMETERS

Two ranges, 160 and 320 volts. 8in. mirror scale with knife edge pointer. Housed in polished wooden case. Ideal for schools, labs., etc. Supplied brand new. £5.19.6 each. P. & P. 3/6.

7.5kV.A. AUTO TRANSFORMERS


0-115-230 volts. Brand new, boxed, £15. Carriage 10/-.

COLLAR STUDIO TAPE TRANSCRIPTORS

Brand new 1962 model. 3 speeds, 3 motors, digital counter, etc. Fitted with latest Bradmatic heads and interlock button. Supplied with spare spool, instructions and fittings. 10 gns. each. Carriage paid.

CLASS "D" WAVEMETERS Mk.II

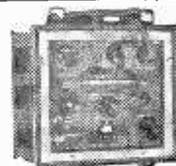Heterodyne crystal controlled frequency meter covering 1.9 to 8 Mc/s. 6 volt D.C. operation. Supplied brand new and complete with crystal, valves, spare vibrator, headset and instruction manual. 59/6 each. P. & P. 3/6.



GW SMITH & CO (RADIO) LIMITED
 Phone: GERRARD 8204/9155
 Cables: SMITHEX LESQUARE
 3-34 LISLE STREET, LONDON, W.C.2

SAVE MONEY!!

BEFORE BUILDING THAT SET SEND FOR OUR LIST OF COMPONENTS AND SAVE 15% OF YOUR BUILDING COSTS!

We can supply any components listed below by RETURN OF POST. TUNING CONDENSERS. .0005 miniature, .0003, .0015 S.W.

COILS. Ferrite rod aerials for all foreign circuits, Potted coils, S.W. coils, 1H Q Crystal coils.

TRANSISTORS. R.F., A.F., matched pairs.

CHOSES. Transistor and S.W. types etc.

TRANSFORMERS. Mini output. Push pull types.

DIODES. Specially selected.


CABINETS. For Pocket portables. Attractive Vinyl covered cabinets.

HEADPHONES. H.R. Lightweight and Ex. Govt.

Ferrite and Slab Rods. Enamel and Litz wires. B.A. nuts and bolts. Solder tags, etc., etc.

SEND S.A.E. FOR PRICE LISTS

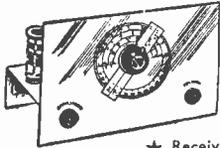EXPLORE THE WORLD ON THIS I-VALVE SHORT-WAVE RADIO



Total Building Costs

35/-

P. & P. 2/-

★ Receives speech and music from all over the world.

Construction price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve. Layout plans etc., 1/6. (Free with order).

All parts for the above circuits are available separately.

Trade Enquiries Welcomed

AMAZING RESULTS from the "OLIVER"

5-Stage Transistor Receiver

A highly sensitive receiver using top grade transistors and components Fully tunable over medium and long waves.

- Can be built in 1 hour.
- High flux moving coil speaker.
- Built in ferrite rod aerial.
- Specially designed coils for maximum signal strength.
- Volume on/off control.
- Eyeletted circuit board.
- Easy to follow building plans.

Send S.A.E. for **FREE** Layout plans and price list.




65/-

P. & P. 2/-

"The REVILO"

5-STAGE POCKET TRANSISTOR PORTABLE

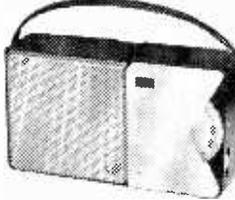

In attractive two tone contemporary case, with gold plated speaker grille and attractive dial. Size only 9 1/2 x 3 1/2 x 1 1/2 ins. No aerial or earth required—completely self contained. Genuine 3in. high flux PM speaker. First grade transistors. Push pull output—250 milli-watts. Volume control with on/off switch. Condenser tuning. Easy assembly on eyeletted circuit board. Total Building Costs **£4.19.6** Socket for personal listening. P. & P. 2/6. Earpiece 7/6 extra if required. Layout plans and price list 1/6. (Free with order).

"PERSONAL TWO" For Private Listening.

An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 1 1/2 x 3 x 4 1/2. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. Two transistors plus diode.

Total Building Costs **35/-**

Plus P. & P. 1/- Earpiece 7/6 extra if reqd. Send S.A.E. for **FREE** Layout plans and price list.

The "BOBETTE" 5-STAGE SUPER SENSITIVE TRANSISTOR PORTABLE

Simple to Build. All First Grade Components. A truly portable transistor radio giving full medium wave reception. Incorporates 5in. High Flux Speaker, push-pull output, first grade transistors. High-Q ferrite aerial, socket for car aerial, pre-tagged circuit board for easy construction. Attractive two-tone case.



Total Building Costs **£5.2.6** P. & P. 2/6. Layout plans and price list 1/6. (Free with order).

ATTENDING COURSE

(A) Full-time One Year Course in Radio and Television. College course in basic principles for prospective servicing engineers. Next course commences 4th September, 1962.

This course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

HOME-STUDY COURSES


(B) Courses in Radio, Telecommunications and Mathematics for the City and Guilds Telecommunication Technicians' Certificates.

To: The Pembridge College of Electronics.
(Dept. P11), 34a Hereford Road, London, W.2.
Please send, without obligation, details of
A. ___ B. ___ (Please tick).

Name _____

Address _____

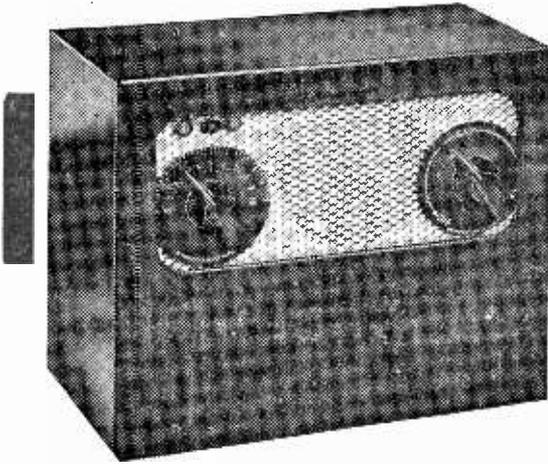THE
PEMBRIDGE
COLLEGE
OF ELECTRONICS
OFFERS TRAINING
IN RADIO
TELEVISION
AND ELECTRONICS



the Tudor

A FOUR-VALVE
BATTERY SUPERHET
FOR MEDIUM AND LONG
WAVES

WHILE transistors have unquestionable advantages for portable equipment, there are many constructors who still prefer the positive and assured results that are obtained with a well-tryed and conventional valve circuit. By taking advantage of the miniature components that are now available a very compact valve set may be constructed with the sure knowledge that it will work first time and give good performance.

Modern low consumption valves are used in this circuit and these, in conjunction with an inexpensive combined H.T. and L.T. battery, provide quite an economical receiver.

All the parts are standard proprietary lines, easily obtainable from any of the suppliers who advertise in this journal and probably many constructors will find quite a few of the parts already in their own store of spares.

Circuit

It will be seen that the circuit (Fig. 1) is a completely conventional 4-valve superhet covering

full medium wave and sufficient of the long wave to tune the Light programme, at good strength, anywhere in the country.

The actual lay-out has been very carefully arranged to achieve a neat and compact design and from the group-board wiring diagrams (Figs. 2 and 3) it will be seen that practically all the small components can be mounted on to two group-boards which can be completely assembled and wired up before fitting to the chassis.

The original prototype had the chassis and front panel made in one from a single piece of aluminium, but this had several disadvantages and it will be found much easier to make these as two separate items as shown in Figs. 4 and 5.

Wiring the Group-boards

Before assembling any components on to the chassis, it will be best to wire and mount the smaller components on the two group-boards; the exact position of these and the method of wiring up at the back of the boards will be seen quite

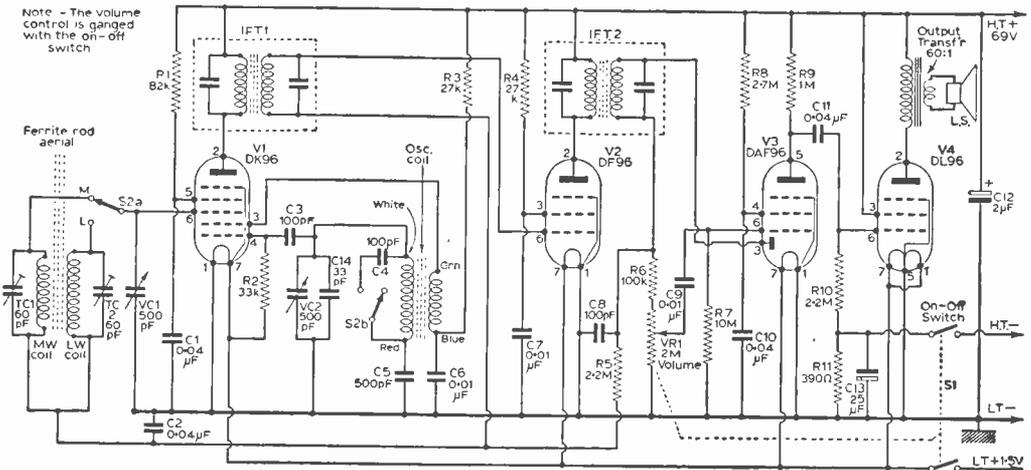


Fig. 1—The circuit.



Fig. 2—Wiring of the main group-board.

clearly in Figs. 2 and 3. It is recommended that one end of the board is marked in some way, as it is quite easy to be confused when constantly turning it round for wiring up.

As these group-boards have to be bolted to the main chassis, remember to leave the two relevant components off until the boards have been mounted, to enable the screws to pass through the holes. It is also important to note that an insulated back-plate is placed between the back of the board and the chassis.

Mounting the Major Components

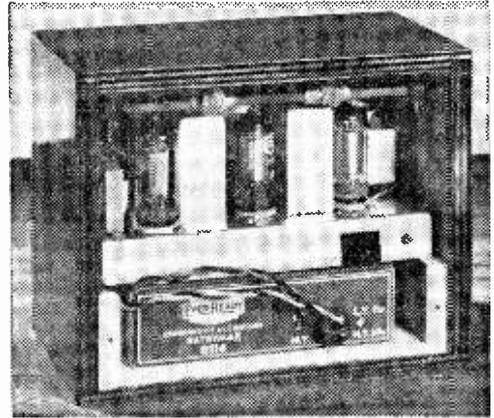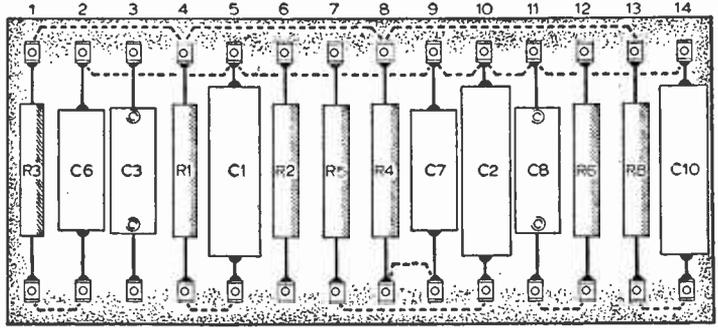Having completed and fitted the tag-boards, the next step is the mounting of all the main components to the chassis taking particular note of the orientation of the valveholders. The I.F. Transformers have similar windings for primary and secondary and it is not important which way round they are fitted. Some constructors may prefer to leave the front panel with its associated controls and



(Above)—The receiver assembled in its case.


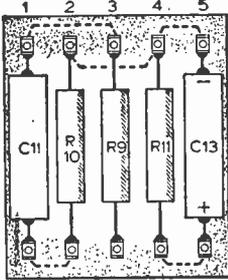


Fig. 3 (left)—Wiring of the auxiliary group board.

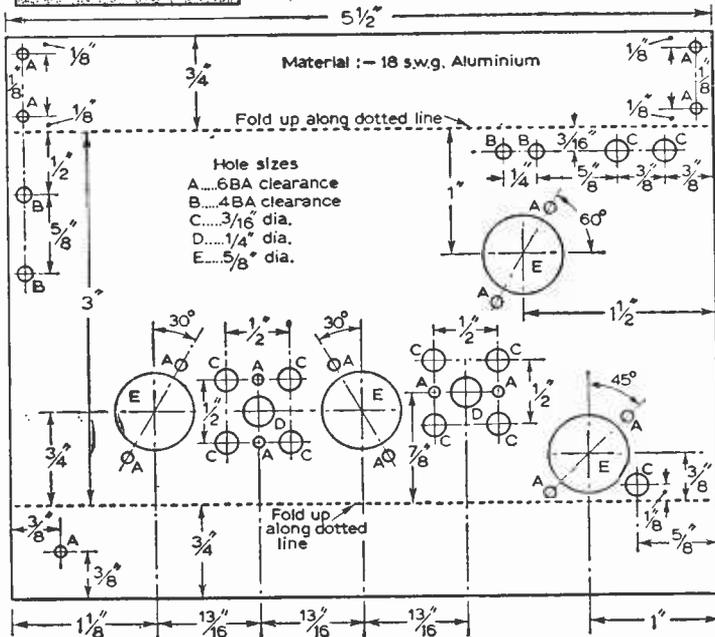

parts separate from the main chassis until later in the assembly, and it is suggested that a strip of insulation tape along the inside lower part of this front panel is a useful precaution as the clearance between it and the group-board tags is rather small.

It is advisable to leave the ferrite rod aerial to last as some alterations to it are necessary before fitting, and also it will eliminate the risk of breaking or damaging it during construction.

The two-gang tuning condenser is mounted from the front of the panel using three countersunk 4B.A. screws. (Ensure that these are cut down short enough to prevent them from projecting through and interfering with the movement of the vanes of the condenser.) The loudspeaker can also be mounted in a similar manner.

(Continued on page 437)

Fig. 4—The chassis drilling dimensions.

MAILPLAN OFFERS

Dept. PW 138 Lewisham Way, New Cross,
London, S.E.14. TIDeway 6667

Immediate Despatch Service! Best Value for Money!

All items advertised have been approved
by our technical team of qualified
engineers.

TWO SENSATIONAL TRANSISTORISED INTERCOMS

HANDY INTERPHONE

For Home, Workshop, Office, two-way calling. Consumes current only when talking or calling. Housed in attractive plastic cabinets with chrome stands. Completely portable. Master and sub-station. Replacement battery only 2/6



MAILPLAN PRICE


89/6

(Today's value 8 gns.)

P. & P. 3/-. Incl. P.P.3 battery, and 25 yds. lead with plugs.

7 Station De Luxe Transistorised Intercom

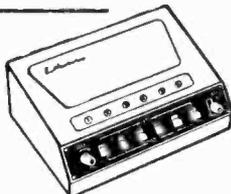The very latest in Office and Factory communication. Calling is audio and visual. Battery operated but consumes current only when calling or talking. Neat compact attractive units, up to 7 extensions supplied separately. Battery life 300 hours.



Master 14 GNS. Post free.
Extensions 2 gns. Post free.

HALF THE PRICE
OF OTHER MAKES

Construct your own Record Player, Intercom,
Tape Recorder, etc., with the

PK.543 SUBMINIATURE 4 TRANSISTOR PUSH-PULL AUDIO AMPLIFIER 52/6



An assembled and wired miniature amplifier incorporating output transformer and 4 transistors, class B200 M watts. All connections for battery, speaker and volume control. The quality is amazing. Complete with instructions and circuit P217A.

3 ohm speaker 2 1/2 flux density, 7,800 gauss. Power, 200 mw. 16/6 P. & P.

MI78 CRYSTAL LAPEL MIKE 17/6

100-9,000 cps. 1 1/2 in. diam., 5ft. lead.

P. & P. 1/-

SLIM CRYSTAL MICROPHONE

— 3 WAY —

Hand held, Stand mounted
or suspended by lavalier
cord.

MODEL 100C 39/6

Post Free



Check the spec. and judge for yourself. Response 60-10,000 cps. Built-in ON-OFF Switch. Output Level -52 dB. Omni-directional. Termination above 500 k ohms. Satin Chrome Finish. Accessory Table Top Stand, 8/6.

PORTABLE SOLDERING IRON Model SPI 30 Watt—230 Volts

(size 10 1/2 in. 6 1/2 in. when not in use). Designed on an entirely new principle for light-weight applications. Highly stable heat characteristics ensures long life. Removable handle permits iron to be carried safely even while hot. Supplied complete with Vynil bag, lead and plug. Spares available. Element 4/6. B & H/6.



18/9 P.&P. 1/-.



TUBULAR BAFFLE EXTENSION SPEAKER

Most adaptable of all speakers. Mounts vertically, horizontally, or sits on desk.

ANOTHER MAILPLAN

Top Value offer . . . 54/6 P. & P. 2/6.

The T.S. 30. Frequency Response: 65-7,000 cps. Impedance 8 ohms. Rated at 1.5 watts. Cabinet, beige leather finish with contemporary gold baffles. Size 9 1/2 x 3 1/2 in. diam.



CALNAD MODEL CR-12AE

12in. coaxial HI-FI loudspeaker. This is the HI-FI Speaker you have been waiting for to fit into your custom-built equipment. Frequency Response: 30-16,000 cps. Resonant Frequency: 45 cps. Capacity: 10 watts, peak 20 watts. Sensitivity: 102 dB/W. Voice Coil Impedance: 16 ohms. Mechanical Cross Over Frequency: 1,800 cps. Total Flux: 85,000 Maxwell. Rigid Glass Voice Coil. Diecast Frame.

MAILPLAN OFFER 8 GNS.


P. & P. 7/6.

Miniature Clear Plastic Panel Meters

FOR YOUR HOME BUILT TEST EQUIPMENT

DC MICROAMMETERS Model MR.25 0 to 50 μ A. . . 39/6
Model MR.250 0 to 500 μ A. . . 32/6
DC MILLIAMMETER Model MR.21 0 to 1 mA. . . 27/6
All models Individually Boxed and Fully Guaranteed.
P. & P. 2/6 each.

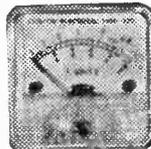"S" METER MODEL SR. 3P. Standard "Ham" Signal strength indicator. Calibrated in "S" units from 0-9 with scale terminating in +10 to +30 dB calibrations. Additional full scale calibrations of 0-5+0-10 in linear scale divisions. 35/-



VU METER MODEL VR. 1P. Calibrated and damped in accordance with standard VU Meter Practice. Upper scale reads -20 to +3VU. Lower scale 0-100% modulation. Uses precision carbon film multiplier resistor and full wave rectifier. 42/6.

SKANTEST—THE L.O.P.T. TESTER

Tests TV Windings for shorting turns by unique pulse method. This compact instrument can save you pounds. It detects a single shorting turn in a line output transformer, deflector coil or other Windings. The pulses provided by the instrument detect intermittent faults. In position one, the continuity of the Windings is checked; in position two, high impedance coils, and in position three, low impedance coils. One you have used the Skantest you will regard it as a must in TV Servicing.

Exclusive Mailplan Offer 99/6 P. & P. 2/8

High resistance Standard type TWIN HEADPHONES 13/6

2,000 ohm Model SF20. Complete with headband. P. & P. 1/-


WATCH FOR MAILPLAN EACH MONTH!

When placing your first order ask for your name to be entered on the MAILPLAN Special Small Quantity Bargain Mailing List

The new NOMBREX

TRANSISTORISED WIDE-RANGE
SIGNAL GENERATOR 27

220 kc/s to 220 Mc/s

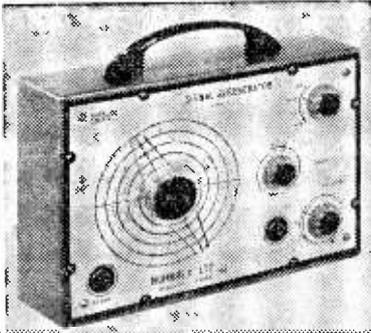

RETAIL £7.10.0 Post and Ins. 3/6
Battery 2/3

Screened Lead and Probe 6/3 extra

CASH WITH ORDER. REGRET NO C.O.D.
NOW IN QUANTITY PRODUCTION
ALL ORDERS IN STRICT ROTATION
Trade and Export Enquiries Invited

CHECK THESE FEATURES!

COMPACT!
Only 6 1/2" x 4 1/2"

PORTABLE!
Weight 2 lbs.

ACCURACY!
Under 2%


ECONOMY!
9v. Battery

DIRECT
Calibration

S.A.E. for full technical leaflet.

H.P. Terms:
Send £2 deposit
pay balance
2 1/2 per month

GIVE YOUR RADIO A PROFESSIONAL FINISH

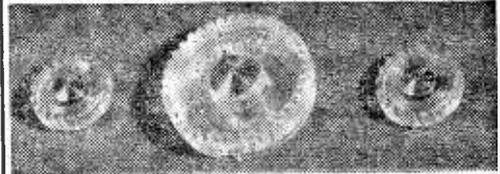

SET OF LUSTRE CRYSTAL PLASTIC KNOBS, PUSH-ON TYPE, SUITABLE FOR ANY RADIO OR RADIOGRAM. Diameters: Large 2 1/2 in., Small 1 1/2 in.

- LIST**
- 47/48 Three knobs, as illustrated, for direct drive tuning, with attractive red centre discs 7/6
 - 46/48 As above, with cursor dial for slow-motion 8/6
 - 49 Tuning scale, diameter 2 1/2 in., lustre gilt finish, printed MW and LW stations and wavelengths in red and black 2/6
 - Above knobs, with smart gold lustre centres, extra per set 1/-
- RADIO CASE TRIMMINGS AND COMPONENTS**
- 51R Case handle brackets, red plastic, to suit 1 in. flexible handle, 4 BA x 1 in. fixing pair 2/3
 - 51G Brackets as above, but brilliant gilt lustre finish pair Speaker escutcheon grille, red plastic, 5 in. x 3 in. ... 3/6
 - 52R Grille as above, but attractive gilt lustre finish ... 4/6
 - 52G Feet for case, black plastic, 1/2 in. x 1/2 in. Set of 4 1/-
 - 55G Personal set escutcheon, 4 in. x 3 in. brilliant gilt finish 3/-
 - 54 Tuning knob for above, edge control, 200-500M and ions 1/6
 - 35/37 Set of 4 Miniature Osc./I.F. Transistor Transformers, High gain, High Q, 9/16 in. diam. 23/-
 - 38/40 Pair of Matched Driver and Output Transformers, Class B output, 500mW, 1 1/2 in. x 1 1/2 in. 18/-
- Six transistor basic components, as previously advertised, still available, 55/-, Circuit diagrams and manual, 2/6. Send S.A.E. for full list of transistor components. Trade and export enquiries invited. Prompt despatch. No C.O.D. under £2 in value. Please include postage.

NOMBREX LTD.

Instruments Division 35

ESTUARY HOUSE, CAMPERDOWN TERRACE, EXMOUTH, DEVON. Phone: 3515.

BBC - ITV - F.M. AERIALS

B.B.C. (BAND 1). Telescopic loft, 19/6. External, 5/3D. 26/8.

I.T.V. (BAND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/6. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H", 28/-, 3 Element loft, 62/6. 5/D loft, 12/6. External 5/D, 26/8. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept.P.W.)
3B, Godstone Road, Kenley, Surrey.

THE AMATEUR RADIO HANDBOOK 1962

- by R. S. G. B., new edition, 34/-, postage 2/6.
- Radio Engineers' Pocket Book, new edition, 10/6, postage 6d.
- Mullard Reference Manual of Transistor Circuits, 12/6, postage 1/-.
- Surplus Radio Conversion Manuals, Vols. 1, 2 and 3, each 24/-, postage 1/- each.
- Beginners' Guide to Radio, by Camm, 7/6, postage 6d.
- World Radio Handbook, by Johansen, 18/8, postage 1/-.
- Radio Amateur Examination Manual by R.S.G.B., 5/-, postage 6d.
- Radio Valve Data, by "Wireless World", 6/-, postage 6d.
- The Radio Handbook by Editors and Engineers, 68/-, postage 2/6.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2 (adjoining Lisle Street)



The PUNCH you need!

HOLE PUNCHES

Instant Type	3/8" diameter	5/6 ea.
Screw-up Type	1/2" diameter	6/8 ea.
	" B7G	7/2 "
	" B8A, B9A	7/8 "
	" "	8/3 "
	" "	8/7 "
	" "	9/6 "
		Postage and packing 1/-.
	1 1/4" diameter Int. Octal	10/11 ea.
	1 1/8" " "	13/3 "
	1 1/4" " "	15/6 "
	1 1/8" " B9G	17/11 "
	1 1/4" " "	20/4 "
	2 3/4" " Meter	27/8 "
		Postage and packing 2/3

Complete set including postage and packing, £7.10.0

Oliver & Randall Ltd

Dept. 7
40 PERRY HILL, LONDON, S.E.6
Tel.: Forest Hill 3415

The SAVOY SUPER-3 3-TRANSISTOR POCKET RADIO

with miniature loudspeaker
No SOLDERING No DRILLING



3 transistors and 2 diodes. Full medium wave coverage. Size 4 1/2" x 2 1/2" x 1 1/2". Full instructions provided.

47/- Battery 1/-
P. & P. 2/- extra

All parts sold separately

or SAVOY-4 with 4 transistors

and 2 diodes, in 5 stage reflex circuit. Size 5 1/2" x 3" x 1 1/2".

75/-

Battery 2/3. P. & P. 2/9 extra.


SAVOY ELECTRONICS LTD

15 Maiden Lane, Strand, London, W.C.2. (Behind the Aelphi Theatre).

SOUTHERN RADIO SUPPLY LTD.

11 LITTLE NEWPORT STREET LONDON, W.C.2. GER 6653

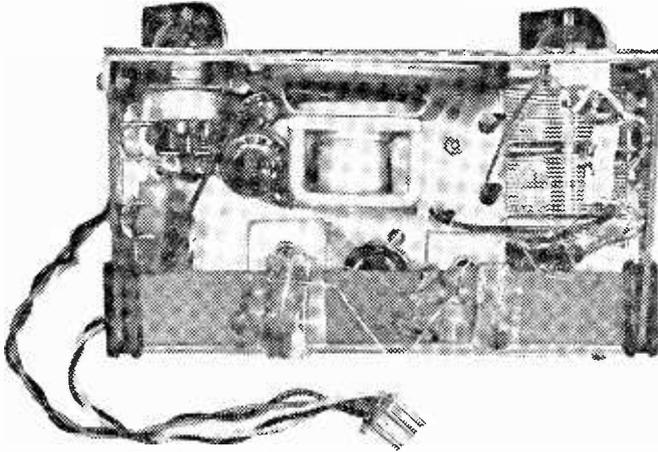All goods still available as previously advertised



The chassis of the receiver viewed from above.

some slight alterations will need to be carried out to the rod aerial before fitting. In the first place it will be found that there are low impedance coupling windings over the top of each of the two coils and these were removed completely. If it is desired to use this set with a car radio aerial in a car these windings may be left on and taken in parallel to a suitable socket for the car aerial. In the prototype it will be seen that the medium wave winding is connected to the upper two tags with a miniature 60pF trimmer soldered in position across it, and the long wave winding is connected to the lower tags and another 60pF trimmer positioned in parallel.

COMPONENTS LIST

Resistors (All $\frac{1}{2}$ W 10%)

R1 82k	R5 2.2M	R9 1M
R2 33k	R6 100k	R10 2.2M
R3 27k	R7 10M	R11 390 Ω
R4 27k	R8 2.7M	

VRI 2M log. with D.P. switch

Capacitors (All miniature components)

C1 0.04 μ F 150V	C8 100pF mica
C2 0.04 μ F 150V	C9 0.01 μ F 150V
C3 100pF mica	C10 0.04 μ F 150V
C4 100pF mica	C11 0.04 μ F 150V
C5 500pF mica	C12 2 μ F 150V elec
C6 0.01 μ F 150V	C13 25 μ F 15V elec
C7 0.01 μ F 150V	C14 33pF mica

VC1, VC2 500/500pF 2 gang tuning (Jackson type L)

TC1, TC2 60pF miniature compression trimmers

Valves

V1 DK96	V3 DAF96
V2 DF96	V4 DL96

Two Denco IFT.11 I.F. transformers (465kc/s)

Miniature output transformer

Oscillator coil (Weymouth radio type H03)

Switches

S1 D.P. switch on VRI
S2 D.P.D.T. slider switch

69V + 1.5V battery

Miniature 14-way and 5-way group-boards

Medium and long wave aerial (Repanco FS2)

2 $\frac{1}{2}$ in 3 Ω loudspeaker


Miscellaneous:

Valveholders; knobs; battery plug; nuts; bolts; etc.

(Continued from page 434)
using 4B.A. countersunk screws with nuts on the inside to make it secure. When all the parts have been fitted to the front panel it can be completed by covering with fine mesh expanded metal, or loud-speaker covering material, leaving a small aperture for the miniature wave-change switch. If it is intended to fit dials one can be mounted under the fixing nut for the volume control and the other one for the tuning indicator is best secured by using contact adhesive.

Most of the wiring is quite straightforward and obvious from a study of the diagrams.

In order to simplify the wiring

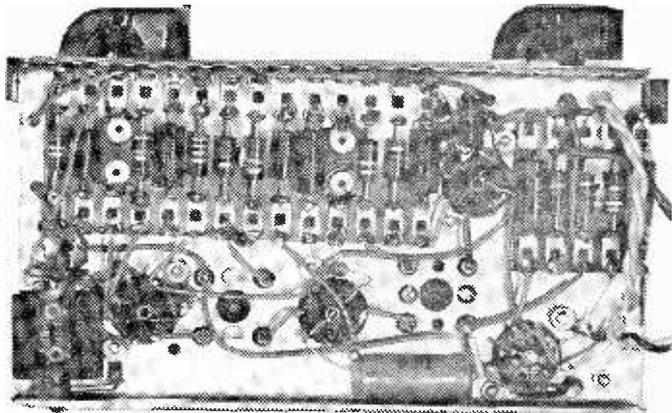

This underchassis view shows the two group-boards clearly.

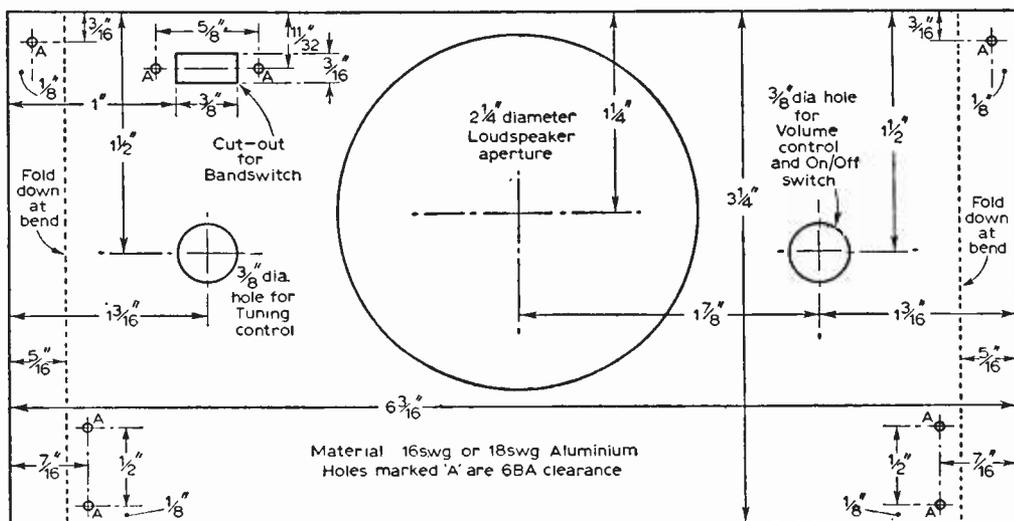


Fig. 5—The front panel drilling details.

Sufficient length of lead should be left to allow both these coils to be moved along the ferrite rod for tuning to the best position. It should be noted that this aerial coil wire is Litz and it is essential when making soldered joints that every single strand is carefully cleaned and tinned otherwise performance may be

affected. The ends can be carefully cleaned by placing on a firm surface and scraping gently with fine emery cloth, or another method is to heat the wire ends in a small flame and while still hot, plunge them into methylated spirit after which the ends can be wiped clean and then soldered.

(To be continued)

Power Rectifier Circuits

(Continued from page 397)

resistance of the transformer winding is often an appreciable fraction of this value, and added to this there is already the internal resistance of the rectifier present. Thus surge limiters of at the most a few hundred ohms will be needed with a PY81, however large the smoothing capacitors may be made. Under the conditions of Fig. 19 where the smoothing capacitors are only $5\mu\text{F}$ each, no limiting resistor was deemed necessary. It is in fact good practice not to make the smoothing condensers too large in the power supply itself, providing the additional smoothing internally in each consumer circuit connected, in the form of a large series resistor and electrolytic condenser, as shown in Fig. 27. This provides decoupling and smoothing in one, and avoids unnecessarily large rectifier surge currents.

Values

Good power supply designs use surprisingly small values for the smoothing capacitors, often only a few microfarads, especially for the first capacitor (the "reservoir" condenser) connected directly to the rectifier. If insufficient smoothing is thereby achieved, then electronic stabilisation is resorted to, which gives far lower internal impedances and far greater smoothing than is achieved by haphazard increases of smoothing capacities, and far lower strain is imposed on the rectifiers. Several such circuit designs have been published in this magazine.

All circuits using large values of smoothing capacitors connected directly to a rectifier are to

be considered basically as compromises in compact or cheap-to-construct apparatus, where it is not deemed desirable to waste too much space or attention on the power supply. Such circuits give very reasonable performance life if capacities not exceeding about $32\mu\text{F}$ are connected direct to the output of normal valve rectifiers, and not exceeding about $64\mu\text{F}$ for metal rectifiers, and not exceeding about $100\mu\text{F}$ for silicon power-rectifiers. However, these figures must be treated as mere, very rough guides. The higher the reservoir capacity, the greater the strain on the rectifier, and the more is its useful life likely to be shortened.

Domestic Equipment

In domestic radio sets and other equipment subject only to intermittent service with long periods of rest, the matter is far less critical than for laboratory apparatus intended for long-period non-stop experiments. Thus the author is at present conducting experiments with Geiger-counter monitors for atomic radiation, for which a large quantity of electronic equipment is in non-stop operation day and night for weeks on end. If insufficient attention would have been given to proper design of power supplies, for example, frequent breakdowns would have been inevitable, which would have caused the loss of valuable measurements, as well as the trouble and expense of such breakdowns. Even for television circuits a higher measure of care is required for power-supplies than for simple radio receivers, because higher voltages and currents are involved, more expensive equipment is in danger in case of breakdown, and the operating hours of television sets in most families are longer than those of radio sets! ■

SETTING A NEW STANDARD FOR DISCRIMINATING CONSTRUCTORS HUNDREDS OF TESTIMONIALS PROVE THE EFFICIENCY OF OUR DESIGNS

THE SUPER SEVEN EASILY THE BEST

(7 Transistors plus 2 Diodes)

- ★ 2 R.F. STAGES.
- ★ Mullard and Surface Barrier Transistors.
- ★ Coverage of Medium, Long Waves, Trawler Band
- ★ Use as domestic radio, car radio or fit with strap for carry-about.
- ★ No aerial required except for use as car radio.
- ★ 3-inch speaker but will drive a larger speaker.
- ★ 400 milliwatts output stage.



May be built for **£6.9.6** SIZE: $7\frac{1}{2} \times 5\frac{1}{2} \times 1\frac{1}{2}$ in.
plus $3\frac{1}{6}$ post, etc.

PARTS PRICE LIST AND EASY BUILD PLANS 2/-

THE EASY-BUILD-7 MED/L.W.


Case as Super Seven.

Simple construction for beginners. 7 transistors plus 2 diodes. Performance will amaze you. May be built for **ONLY £5.19.6**. P.P. 3/6. Parts price list and building plans 2/-.

NEW TRANSONA-6

(6 Transistors, plus 2 Diodes)
M/L & T. BAND

400 Mw Mullard push-pull output Transistors. Powerful magnet 3in. high grade speaker. Push-pull transformers. This is a top performing receiver. Many stations listed in one evening including Luxembourg loud and clear. A pleasure to listen to. **FERRITE ROD AERIAL.** All parts sold separately, including pale blue gleaming polystyrene case with duo-diffusion grilles in red. Uses 9 volt battery. Sockets for car aerial.

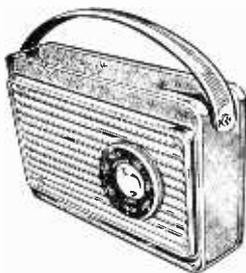

Total building cost **£4.19.6** P.P. 3/-. Size $6\frac{1}{2} \times 4\frac{1}{2} \times 1\frac{1}{2}$ in.

"Agreeably surprised with Trawler Band reception. Luxembourg as loud as local. Your easy build diagram helped a lot... my first attempt."—H. S., Penzance, Cornwall (poor reception area).


PARTS PRICE LIST AND EASY BUILD PLANS 1/6.

BEGINNERS POCKET 5

(MW/LW and TRAWLER BAND)

(5 Transistors, plus 2 Diodes)

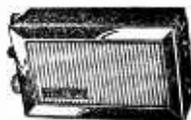Designed round supersensitive **FERRITE ROD AERIAL** and 3in. moving coil speaker. Attractive case in black with speaker grille in red. On test Home, Light, Radio Luxembourg and many Continental stations were received.



Total cost of all parts **£2.19.6** P.P. 3/-

EASY BUILD PLANS AND PARTS PRICE LIST 1/6

THE MELODY SIX

- ★ Ferrite rod aerial.
- ★ 6 new type transistors and top quality components. Attractive case in blue and red and carrying strap with gold trim.
- ★ 3in. Speaker.
- ★ M.W/L.W.



£3.19.6


P.P. 3/-

Components price list and plans, 2/-.

BEGINNERS PUSH-PULL FIVE

(5 Transistors, plus Diode)

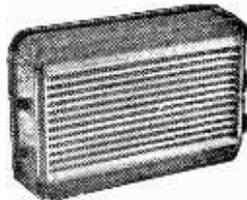- ★ M/C Speaker, 2½in.
- ★ Ferrite rod aerial.
- ★ Tuning condenser.
- ★ Volume/oscillator control.
- ★ Case with speaker grille in red.
- ★ Fully tunable over med/long waves.
- ★ Simple assembly diagrams.
- ★ 250 Milliwatts output stage.



★ Can be built for **59/6** P.P. 3/-. or with 3in. speaker 68/6

★ PARTS PRICE LIST, etc. 2/-.

AFTER SALES SERVICE

NAME AND ADDRESS
CAPITAL LETTERS PLEASE

RADIO EXCHANGE COMPANY

27 HARPUR STREET, BEDFORD

(Opposite Co-op)

PHONE 2367

10 a.m. to 1 p.m. SAT.


LASKY'S RADIO

"BUILD-YOURSELF" TRANSISTOR RADIOS

The "REALISTIC" Seven

STAR FEATURES ★★★★★

- ★ 7 Transistor Superhet. 350 Milliwatt output into 4-inch high flux speaker.
- ★ All components mounted on a single printed circuit board, size 5½ x 5½in. in one complete assembly.
- ★ Plastic cabinet, with carrying handle, size 7 x 10 x 3½in. in choice of colours: Red/Grey, Blue/Grey, all Grey.
- ★ Easy to read Dial.
- ★ External Socket for car aerial.
- ★ I.F. frequency 470 K/c/s.
- ★ Ferrite Rod internal aerial.
- ★ Operates from PP9 or similar battery.
- ★ Full comprehensive data supplied with each Receiver.
- ★ All coils and I.F.'s, etc., fully wound ready for immediate assembly.

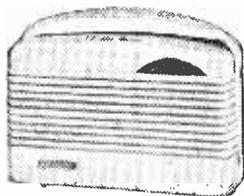

An Outstanding Receiver. Lasky's Price for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data.

£6.19.6 Postage and Packing 4/6
 Battery 3/6 (Included free with complete parcel). Data and instructions separately 2/6, refunded if you purchase the parcel.

The New "ALBERTA 5" Mk. II

Now using printed circuit and supplied with miniature earphones for personal listening at no extra cost.

Push-pull, 200 milliwatts output. Five transistors and one diode. 2½in. moving coil speaker, ferrite rod aerial. Med. and long wave. Plastic Case, 4½ x 3½ x 1½in. overall.



CAN BE BUILT FOR **59/6** Post 3/6
 All components available separately. Full details, circuit diagram, 1/6 post free.

THE BETA TWO

A 2-transistor plus 2-diode personal receiver for home construction. Uses printed circuit and ferrite rod aerial. Personal earphone gives clear reception for private listening. Tunes over full medium waveband. Uses same cabinet as our Alberta 5 receiver. Illustrated above, size 5½ x 3½ x 1½ ins. overall. All components available separately. CAN BE BUILT FOR **21/-** Postage 2s. 6d. extra. Including personal earphone, cabinet, etc. Circuit diagram and step by step instructions 1s. 6d. (Free with parcel).

★ REBUILDING CLEARANCE SALE

at 42 Tottenham Court Rd., W.1.
 LAST SIX WEEKS!
 HUNDREDS OF BARGAINS!!


207 EDGWARE ROAD, LONDON, W.2.
 Near Praed St. PADDINGTON 3271/2

33 TOTTENHAM COURT ROAD, W.1.
 Nearest Stn. Goodge St. MUSEUM 2605

BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W. Edgware Road.

ACKNOWLEDGED TO BE THE BEST COMPONENT CATALOGUE

A MUST for every radio enthusiast

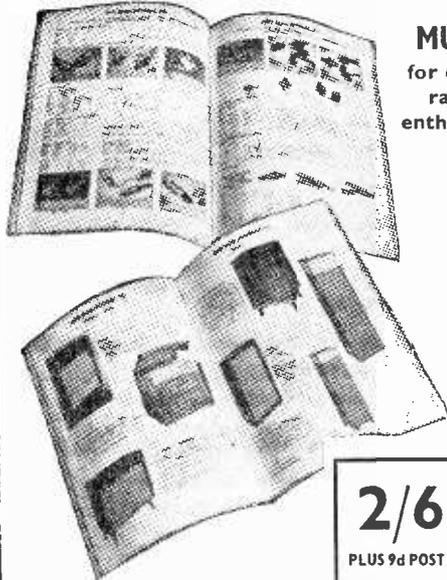

NOW
166 pages
 Over **600**
 Illustrations
 Over **5,000**
 components listed

This is to-day's most up-to-date, most comprehensive component catalogue for the radio constructor, experimenter, engineer and Hi-Fi enthusiast.

POST COUPON TODAY
 Write CATALOGUE on top left of envelope
 Enclose P.O. 3/3

Name.....

Address.....

Home Radio Ltd. (PW) 187 London Rd. Mitcham, Surrey

2/6
 PLUS 9d POST

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

P.C.R. COMMUNICATIONS RECEIVER

SIR,—I wonder if any of your readers could advise me as to what is the correct I.F. of the P.C.R. communications receiver currently available. Also, I would like to know, the make and type of a suitable BFO coil for use with half a 6SN7 in this set.

I would also be very grateful if anyone could sell or loan me a copy of the original circuit for the R.F. unit No. 24.—A. WATT (67 Glenhurst Avenue, Bexley, Kent).

AMERICAN STATION

SIR,—In answer to a query made by Mr. T. Gerrard in the July issue, regarding an American station he heard on the 32m band, the station is one of the American Telephone and Telegraph Co. radio telephone services. These stations are not engaged in broadcasting but are used solely for international communication.

A station which may be of interest to Mr. Gerrard and other readers, is WRUL New York, which broadcasts some excellent programmes and is, in fact, the only commercial S.W. station operating from the U.S.A. The times of transmissions are 15.00-23.00 GMT on week days; 18.30-23.00 GMT at weekends. The frequencies for Europe are 15,380kc/s (19m band) and 17,760kc/s (16m band).—R. PATRICK (Derby).

SIR,—The transmission identified by T. Gerrard (July issue) as coming from an American station, is in fact a single sideband transmission by a German station.

The message in English is as follows: "This is a test transmission by a single sideband system operated by the Overseas Service of the Deutsche-Post Francis Main Terminal. Please give identification signal on channel A for receiver adjustment".

The other message is in German. — R. R. DIAMOND (Stockport, Cheshire).

MEDIUM WAVE FADING

SIR,—I have been having trouble with a 12-year-old McMichael receiver. It has the habit of fading on medium waves after it has been switched on for about 10 minutes.

The only way I have found to rectify this, is by

disconnecting the aerial lead-in and connecting it to earth! Could any reader explain this or suggest another way of curing the fault? — K. CLOUGH (Bolton).

THE P.W. TROUBADOUR

SIR,—I have just completed constructing the P.W. Troubadour, 7-transistor receiver (June and July issues) and am amazed at its performance. This pocket set gives better selectivity, sensitivity and none-fade reproduction than some expensive models owned by friends. Although it does work out expensive if the constructor has not any of the components in stock, this receiver must surely be worth double the complete kit price.—R. W. CRAIG (Bexley, Kent).

TELEVISION BREAK-THROUGH

SIR,—There have been a number of letters in recent issues about the reception of long-distance stations on crystal receivers and I think there is no doubt that in the majority of cases this reception is not direct from the station concerned, but re-radiated from a neighbouring aerial. I experienced a very similar effect some time ago, when I heard music as a background on my simple set, and on trying to resolve it found it was the BBC television programme. I felt that this could not be direct pick-up on account of the frequency used and my distance from the nearest station, and this was confirmed a little later when the station disappeared instantly—that is, it did not fade out. A few nights later I noted that the station returned, again in a sudden manner rather than a gradual signal strength build up, and I knew the people downstairs had a TV and made a few inquiries, as a result of which we carried out some tests, and the programme did, in fact come from their aerial, which was of the indoor type, and their contrast control had to be full up. There was obviously some H.F. instability which resulted in the signal being radiated in this manner. I hope this will be of interest to others.—E. GOWING (Portsmouth).

CORRESPONDENTS WANTED

SIR,—I am 22 years of age, and I am interested in radio servicing as a hobby. I would like to correspond with amateur enthusiasts of my age from any country. — D. L. KIRIWANDALA, P.O. Box 732, Colombo, Ceylon.

SIR,—I am 16 years of age and would like to correspond with amateurs of my age. I have been interested in S.W. for about a year now.—BUTCH BONE, c/o Daw Thein Wa's, Bookland, P.O. Box 294, 385 Bogyoke Street, Rangoon, Burma.

Club News

REPORTS OF CURRENT ACTIVITIES

BRADFORD RADIO SOCIETY

Hon. Sec.: M. T. G. Powell, G3NNO, 28 Gledhow Avenue, Roundhay, Leeds 8.

On June 26th a number of members visited a firm of engineers. The two meetings for July consisted of an informal evening on 10th and a talk by G30GV—"160m SSB"—on 24th.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

G3ERD/P operated from Harborough Rocks, Brassington on July 7th and 8th for the second R.S.G.B. Two-metre Field Day. L. Ball gave a talk on July 11th and the meeting for 18th was taken up by the fourth direction finding league fixture.

A sale of members' surplus equipment was held on August 1st.

Future Events:

August 15th—Direction finding league fixture, No. 5.

August 22nd—Stereophonic demonstration.

MIDLAND AMATEUR RADIO SOCIETY

Hon. Sec.: A. B. Watt, G2DRG, 11 Holly Road, Handsworth, Birmingham 20.

On Tuesday, 17th July, members attended a lecture given by H. C. Smith. The title of his lecture was "Tape Recording", and it was given at the Birmingham and Midland Institute.

Future Event:

August 21st—"G2DAF receiver for SSB" by G3LLN.

MORECAMBE AMATEUR RADIO SOCIETY

Hon. Sec.: K. J. Singleton, G3NLM, 8 Westmoor Grove, Heyham, Morecambe, Lancashire.

Meetings of this society are held on the first Wednesday of each month at the Liberal Club, Balmoral Road, Morecambe, and start at 7.30 p.m. Any new members will be made welcome.

For the July meeting, a number of members visited the automatic telephone exchange in Lancaster. The meeting for August was devoted to a ragchew.

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

Recent club activities have included a display of members' equipment which was held on July 4th.

At the meeting on August 1st, the society played host to members of the Manchester Radio Society, who gave a D.F. demonstration. On August 4th, members operated a demonstration station at the Warley Club and Institute Charity Gala.

PURLEY AND DISTRICT RADIO CLUB

Hon. Sec.: E. R. Honeywood, G3GKF, 105 Whytecliffe Road, Purley, Surrey.

A portable expedition was held on the evening of July 6th, at Walton Heath. Operation was on Two-metres and Top Band.

On July 20th, members heard an R.S.G.B. tape recorded lecture which was illustrated by slides.

Future Event:

August 17th—Film of National Field Day.

RADIO CLUB OF SCOTLAND

Hon. Sec.: A. Barnes, GM3LTB, 7 Southpart Terrace, Glasgow W.2.

This is a new radio club which held its inaugural meeting on June 1st this year. Meetings are held every Friday evening, and commence at 8 p.m. A welcome is extended to anyone who is interested in the hobby of amateur radio. All interests are catered for but suggestions are always welcome for expanding the programme. The first Friday in every month is especially for beginners.

FREE!!

DOUBLE-SIDED

BLUEPRINT

inside
NEXT MONTH'S

Detailed Instructions to build
SIGNAL GENERATOR

Completely self-contained. Portable.
Mains-operated. R.F./A.F., covering
150kc/s—30Mc/s.

AUDIO AMPLIFIER

20W. High quality. For use with most
pre-amplifiers, giving level response
over 30c/s to 20kc/s. Separate power
supply unit to meet H.T. and L.T.
requirements of pre-amplifier or radio
tuner.

COMING!

More FREE Double-Sided BLUEPRINTS
in November and December issues.

Practical WIRELESS

ORDER FROM YOUR NEWSAGENT TODAY!

SURBITON PARK RADIO LTD.

FOR POST HASTE—POST FREE SERVICE

MARTIN RECORDAKITS

The following recorders, available now in four track, are a proprietary range of machines in kit or assembled form. This enables you to take advantage of mass production techniques and prices, should you wish to assemble yourself. The components used are the finest available, with B.V.A. valves, and the decks are the latest having all the improvements B.S.R. and Collaro make from time to time, heads, etc. The amplifier, are packed in special cartons with instructions to enable anyone to build. We are confident you will find these recorders very good value, they have been built up to a standard and not down to a price.

HALF TRACK

B.S.R. TD2 Monardeck, latest model 5 1/2 in. spool	CASH	£99.00
Deposit £1.0, 0 and 9 monthly		£11.10
Tape Amplifier for B.S.R. deck, printed circuit ready wired with ECUC83, ECL82, EM85 and DZ81. Complete with all plugs, sockets, panels, knobs, etc. The whole amplifier mounts onto the deck, making a self contained unit	CASH	£8.50
Deposit £1.0, 0 and 9 monthly		£11.10
Case with 7 in. x 4 in. speaker, in two tone grey	CASH	£4.40
Complete Kit as above	CASH	£22.00
Deposit £2.4, 0 and 12 monthly		£11.65
The above recorder can be supplied assembled, tested and complete with tape and microphone for	CASH	£25.00
Deposit £2.10, 0 and 12 monthly		£21.60
Collaro Studio Deck, Very latest model 3 speeds 7 in. spools	CASH	£12.10.00
Deposit £1.5, 0 and 12 monthly		£11.08
Tape Amplifier for studio deck, with ready wired printed circuit control and input panels, mains and output transformers. Complete with valves, knobs, plans, screws, etc. F186, ECUC83, EM84, EZ81, OA81 and 2 EL84. 3 watta output. Magic eye, radio and mic. inputs, EX L/8 socket, tone and monitor controls. Can be used as an amplifier	CASH	£11.11.00
Deposit £1.4, 0 and 12 monthly		10/-
Case for above including 9 in. x 5 in. speaker		£5.50
Total Kit as above	CASH	£29.00
Deposit £2.18, 0 and 12 monthly		£2.8.2
We can offer the above recorder, complete with tape and microphone, in a De Luxe two tone grey cabinet, assembled for		£35.00
Deposit £3.10, 0 and 12 monthly		£2.18.2

This Machine is listed at 39 gns. by makers and is a very good buy. Building Instructions available at 2/6 each kit (refunded if kit bought).

QUARTER TRACK

B.S.R. TD2	CASH	£111.10
Deposit £1.4, 0 and 12 monthly		19/-
Tape Amplifier as over, but quarter track	CASH	£9.80
Deposit £1.0, 0 and 9 monthly		£11.0
Case, two tone grey, with speaker		£4.40
Complete Kit as above	CASH	£25.00
Deposit £2.10, 0 and 12 monthly		£21.5
Collaro Studio Deck, 4 track		£17.17.0
Deposit £1.18, 6 and 12 monthly		£1.9.5
Tape Amplifier, as over, but 4 track	CASH	£12.12.0
Deposit £1.7, 0 and 12 monthly		£1.0.8
Case with 9 in. x 5 in. speaker		£5.5.0
Complete Kit 4 track Collaro		£24.0
Deposit £3.8, 0 and 12 monthly		£2.16.6
Tape Pre-amplifier for Collaro deck, with power supplies, ECUC83, ECL82, EZ80 and EM83. Radio and Mic. sockets, gives an equalised output of 400 m/Volts		
Half Track	CASH	£8.80
Deposit £1.0, 0 and 8 monthly		£11.0
Quarter Track	CASH	£9.80
Deposit £1.0, 0 and 9 monthly		£11.0
Marriott Tape Heads, 4 track type 1/R/PS/7 and 1/ES/9 Record/Playback and Erase with mounting bracket for Studio deck.		
Pair Complete (Marriott list price is £8.14.0)	CASH	£4.4.0
Marriott 2 track type 1/R/1 Record/Playback only with bracket for Studio deck. Ideal 3rd head		£17.6
Pressure pot for Studio deck only		3/6
M.S.S. 2 track type DRI and DEI Record/Playback and Erase Sets only		£12.6

THE ABOVE SETS ARE BRAND NEW, OBTAINED DIRECT FROM MAKERS

JASON F.M. TUNERS

FMT1, complete with valves	CASH	£6.17.6
Deposit £11.0 and 6 monthly		£12.9
FMT2, complete with valves, Less Power	CASH	£7.17.6
Deposit £11.0 and 7 monthly		£12.6
FMT2, complete with valves, Self powered	CASH	£9.15.0
Deposit £11.0 and 9 monthly		£11.8
FMT3, complete with valves, Less power	CASH	£9.12.6
Deposit £11.0 and 9 monthly		£11.4
FMT3, complete with valves, Self powered	CASH	£12.0.0
Deposit £11.4, 0 and 12 monthly		19/10
Power pack kit ready drilled chassis for FMT1, etc.		£2.12.6
The instruction books are included in all kits but are otherwise 2/6.		
JTV/2, switched F.M. and TV. Sound self powered. All valves.	CASH	£14.15.0
Deposit £11.6 and 12 monthly		£14.4
Mercury 2, as JTV/2 but less power, with all valves	CASH	£10.15.0
Deposit £13.0 and 8 monthly		£1.6.6
The instruction book is again included but is otherwise 3/6 each.		
All the above units are available ready built and aligned. Price on request.		

ARMSTRONG RADIO CHASSIS

T4B V.H.F. Tuner, self powered	CASH	£21.18.0
Deposit £2.6, 6 and 12 monthly		£11.6.1
ST/C Mk. 2 A.M./F.M. Tuner, self powered	CASH	£27.16.0
Deposit £2.16, 6 and 12 monthly		£2.6.1
AF208 A.M./F.M. Radio Chassis, bass and treble controls		
1-U inputs, single ended output stage	CASH	£22.18.0
Deposit £2.8, 6 and 12 monthly		£17.9
Jubilee Mk. 2 A.M./F.M. Radio Chassis with push pull output	CASH	£30.12.0
Deposit £3.3, 0 and 12 monthly		£2.10.8
Stereo 55 A.M./F.M. Radio Chassis, single ended output stage on both channels. Separate tone and volume	CASH	£32.15.0
Deposit £3.8, 6 and 12 monthly		£2.14.5
Stereo 12 Mk. 2 A.M./F.M. Radio Chassis, push pull output, separate controls both channels		£43.10.0
Deposit £4.7, 0 and 12 monthly		£3.12.4
Drum dial escutcheon is available for AF208 and Jubilee. Price 7/6.		
Individual leaflets giving full description and technical details.		

P.W. "POCKET SUPERHET"

OSMOR PRINTED CIRCUIT VERSION

Osmor rod aerial 8/6, L.F.T.s and Osc. coils 22/-, Osmor driver 8/3, Osmor output 3/-. Set transistors and diode 43/-, J.B. gang 12/6, Trimmers 1/8 each, Set condensers 15/-, Set resistors 5/-. Arlene volume control 8/-. W/C switch 3/6, Speaker 17/10, Hardware 4/-. Printed circuit 7/6. New case and dial 12/6. Battery P145/3. Leaded wiring full illustrated details 1/6. All the above components if ordered at one time

Osmore undertake to align this receiver for 10/-.

"WEYRAD"

Weymouth Radio 6 Transistor Superhet, using the P50 coils as they advertise in this journal. P50/LAC Osc. coil 5/4, P50/2CC 1st and 2nd L.F.T. 5/7 each, P50/3CC 3rd L.F.T. 6/-. RA2W rod aerial 12/6, LPDT4 driver 0/6, PACT printed circuit 9/6, Instruction Book 2/-. set resistors 7/6, Vol. control D.P.F. 6/-. set condensers 20/-, J.B. gang 12/3, Beehive trimmers 1/8 each, W/C switch 3/6, dial and knob 5/6, Battery P11 6/6, Battery plug 1/-, OAS1 3/-. Set of Mullard transistors 53/5, Car aerial coupling coil 1/-, 35 ohm 7 in. x 4 in. speaker, ideal for Weyrad circuit

Transistor Cabinet for 7 in. x 4 in. speaker. Ideal for Weyrad circuit, two tone grey

GRAMMOPHONE EQUIPMENT

B.S.R. UA 14 TCS/H cartridge	CASH	£7.15.0
Deposit £1.0, 0 and 7 monthly		£12.3
Garrard Autoslim, new unit	CASH	£8.14.6
Deposit £1.0, 6 and 12 monthly		£12.14.8
Garrard Autoslim De Luxe	CASH	£11.1
Deposit £1.5, 6 and 12 monthly		£11.1
Philips AG1016, new transcription unit (changes on 45 rpm)	CASH	£13.10.0
Deposit £1.7, 0 and 12 monthly		£12.4.

REGENCY

Resistors 2/3, Controls 9/-. Condensers 15/-, Knobs 2/6, Station dial 5/6 J.B. gang 8/-. Mullard OC45 10/- each, OC72 matched pair 18/-, OA81 3/-, Bate's 1/3, W/C switch 3/6, Repanco TT49, TT45, and TT46 all 5/- each, FR: 12/6, R.P.U1 2/6, 7 in. x 4 in. speaker 10/6, Groupboard 1/4. Complete Kit, less cabinet

Transistor Cabinet in two tone grey "Vynal" 10 x 6 x 3 1/2 in. for 7 x 4 speaker, no control holes have been drilled. Ideal Regency, etc.

TRANSISTORS

Mullard has reduced the price of many Transistors to: OC44 11/-, OC45 10/-, OC70 6/6, OC71 6/6, OC72 3/-, OC75 3/-, OC76 8/-, OC81 8/-. These are their new list prices. Why buy surplus, OC72 in matched pairs only at 16/- pair (No other types).

48 SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

Established over 30 Years

Telephone KIN 5549

We pay all postage and insurance.

All orders despatched same day.

Money refund guarantee.

Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday) We do not close for lunch. Open all day Saturday.

SERVICE SHEETS

SERVICE SHEETS: Radio, TV, 5,000 models. List 1/- S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

SERVICE SHEETS for all makes of Radio and TV, 1930-1962. Prices from 1/- with free fault-finding guide. Catalogue of 6,000 models 1/6. 125 Radio/TV sheets covering many popular models 20/-. S.A.E. enquiries: HAMILTON RADIO, Western Road, St. Leonards, Sussex.

WHY TOLERATE DELAY when we can supply your Radio or TV Service Sheet by return of post at 4/- each, plus postage. List 1/-. Also Manuals for sale and hire. List 1/-. S.A.E. with inquiries please. Mail orders only to S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

FAULTFINDER FILES, showing common faults that each receiver is prone to and other useful servicing information, 2/- each. List 9d., plus postage. Mail orders only. S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

SERVICE SHEETS, Radio and TV, 4/- each. List 1/-. All orders dispatched on day received. Also manuals for sale and hire. List 1/-. S.A.E. please, SULTAN RADIO, Pantiles Chambers, Tunbridge Wells, Kent.

SERVICE SHEETS; also Current and Obsolete Valves for sale. — JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London W12. Phone SHE 8441.

CIRCUIT INFORMATION

18 SET TRANSMITTER RECEIVER
Description, Operation, Values, Diagrams.
Tests, etc. P.O. 5/-

38 SET WALKIE TALKIE
Alignment procedure. Faults. Components.
Description, Diagrams, etc. P.O. 5/-

CAMPBELL

Everland Road, Hungerford, Berks.

METAL WORK

METALWORK. All types cabinets, chassis, racks, etc. to your specifications. PHILPOTT'S Metalworks Ltd., Chapman St., Loughborough.

WANTED

WANTED: NEW valves and transistors, any quantity. S. W. WILLETS, 43 Spon Lane, West Bromwich, Staffs. Tel: WES 2392.

NEW VALVES WANTED

Any type, any quantity

CASH PAID

R.S.T. 211 Streatham Road,
Mitcham, Surrey
Telephone: MITCHAM 6202

RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

WANTED

(continued)

WANTED: TEST GEAR, Meters, Valves, Components, Communication Sets, Amplifiers. HUGGETS LTD., 2-4 Pawson's Road, West Croydon, Surrey.

WANTED: New Valves and Transistors, any quantity. Phone Cherrywood 3955. D. & B. TELEVISION, 131-131a Kingston Road, South Wimbledon, SW19.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

NEW VALVES bought, state price. A.D.A. MANUFACTURING CO., 172 Alfreton Road, Nottingham.

A PROMPT CASH OFFER for your Surplus Brand New Valves and Transistors. R.H.S., Beverley House, Manville Terrace, Bradford 7.

VALVES WANTED

IMMEDIATE CASH SETTLEMENT
Must be new.

Phone, write or call

Radio Facilities Ltd.

38 Chalcot Road, London N.W.1
PRImrose 9090

The valve specialists

WANTED: T.C.S. Transmitters, Receivers, Connectors, Loading Coils etc. GILFILLAN, 98 Dominion Road, Worthing, Sussex. Tel.: Worthing 8719.

FOR SALE

100 BAYS of brand new adjustable Steel Shelving, 75in. high by 34in. wide by 12in. deep, stove enamelled dark green. Sent unassembled. Six-shelf bay £3/15/-. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Lancs. Tel.: 69018.

ASK your dealer for American Ferrodynamics. "Brand Five" Recording Tapes—the best tape value!

AMATEUR LICENCE Morse Course. The new Rhythm Method of teaching takes the drudgery out of learning Morse and is the quickest known!!! For full explanatory booklet: S.A.E. GCHS, 45 Green Lane, Purley, Surrey.

FOR SALE

(continued)

WE HAVE a large selection of amplifiers, radios, tape recorders, television sets record players, etc. that have been taken in part exchange ranging from Bush, GEC, Sobell, Philips, Pye, HMV Ferguson and many others. You are invited to call and offer any reasonable sum that you think might tempt us to sell. PORTERS RADIO LTD., Chapel Street, Guildford. Tel: 4766.

AUDIO. America's foremost journal. Year's subscription, 35/-. Specimen copy 4/-. Every American radio journal supplied. Price list free. WILLEN LTD. (Dept. 40), 9 Drapers Gardens, London EC2.

MONITOR 58 triggered oscilloscope. Apply details: MOXON, 19 Deanway, Wilmslow.

E. R. NICHOLLS

47 MIDDLE HILLGATE, STOCKPORT
RETAIL SHOP

BUMPER PARCEL

100 Resistors, 100 Condensers, 100 Cartridge Fuses, 3 Mains Droppers, 2 Rotary Toggle Switches, 6 Paxolin Panels, 2 B.C. Lampholders, 1 Transmitter, Chassis less Valves, 6 Potentiometers. 20/- Post Free.

No. 2 PARCEL. 1 ex Unit Mains Transformer 250-0-250-4+4+5+6.3 volts, 1 Sound Output Transformer, 1 Isolation Transformer, 1 Sin. Speaker P.M., 3 Jack Sockets, 4 Terminal Blocks, 2 Inert Calls, 1 Telephone Fuse Box, 1 12-volt 4-pin Vibrator, 100 Cartridge Fuses, 1 Helmet Spot Lamp, 1 Nylon Parachute for the youngster, 24 asstd. sizes Polythene Bags for the wife, 12 sheet Carbon Paper for the lodger, 1 Thermistor and if you send a local view (post card) I will send 12 High Stub Resistors. All this for 40/-, Post Free. Don't Miss It.

High Stub Resistors 6d. each. S.A.E. List. 20 ft. Telescopic Masts 50/-, via BRS Post free Mail Order to—

33/35 Carrington Field St., Stockport.

EQUIPMENT FOR SALE

WALNUT CABINETS by Pye, bargain £4 each. EMI 4-speed R/player unit with Aco's Pickup, new £3/10/- each. HMV Walnut speaker enclosure Octagonal, bargain £8.

Richard Allan Speaker enclosure Walnut, fitted 8in. speaker, bargain £8. Nurdyk cabinets fitted Dulc Stereo amplifier and control Teppa Stereo player unit Celestion speakers on Nurdyk Bench ready to go, all new, bargain complete £40. Grundig TK35 (the best they ever made), new with guarantee demo only £50. Burn Jones Sonnetta speaker system, high oak, bargain £10.

Famous Audio Empire L08 stereo cartridges few only at £12/10/- each straight from U.S.A.

Grundig T.K.L. Tape Recorders new £20 each. Full range Wharfedale Loudspeakers 20% under list price for one month only. Bargains in all makes of Tape Recorders, Amplifiers, Speakers, Pickups, Turntables, etc Write Your wants for Our price. Sol British Agents for famous German: Eac Pickup cartridges, Miraphone and Miracord Record players and changers.

The Best in the World. Terms cash with order. THE HIGH FIDELITY CENTRE, 61 West Street, Dorking, Surrey.

RECEIVERS & COMPONENTS

NEW  **GUARANTEE.**  **MARKED**
MONEY BACK **TRANSISTORS** **AND TESTED SUCH AS**
 XA101, XA102, XB103, XC101, ETC.
 20/- PER PACKET OF 10.
UNMARKED BUT TESTED MOST RADIO 
Types 20/- PER PACKET OF 16.
UNMARKED UNTESTED 20/-PKT OF 40. **POST**
DUDS MAY BE SUITABLE AS DIODES 20/-PKT OF 80. **FREE**
ANY 2 PACKETS 37/6 CASH WITH ORDER **QUANTITY**
K.R. WHISTON (DEPT PWT), NEW MILLS, STOCKPORT. **DISCOUNT**

SPEAKER REPAIRS. Cones/Fields fitted. Clock coils wound. L. S. REPAIRS, Pluckley, Ashford, Kent.

NEW AND SURPLUS Valves, guaranteed from 3/6. Also reclaimed Valves, perfect, from 1/6. Many bargains. S.A.E. for complete list. LEWIS, 46 Woodford Avenue, Ilford, Essex.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.,** Dept. P.W. 7/8, 138 Lewisham Way, SE14, Tideway 6866.

SPECIAL OFFER. MINIATURE 6-TRANSISTOR SUPERHET chassis (3 1/2in. x 2 1/2in.) All components mounted on printed circuit board. Long and Medium waves; 200mW Push pull output; 2in. moving coil speaker. Earpiece socket fitted. Each set complete with battery and guar. working perfectly. Supplied without case. 25/12/6, p & p and insurance 5/- extra. **SAVOY ELECTRONICS (Sales) LTD.,** 15 Maiden Lane, WC2. Temple Bar 5484.

TRANSISTOR COMPONENTS. 7 x 4in. 35 ohm speakers, 25/-, 7 x 4in. 3 ohm. 10/6. **EARPIECES.** 7 ohm, 150 ohm, 6/6. Xtal with Jack. 7/6, all complete with plugs. 4 pole 2 way switches 1 inch spindle, 2/6 each. Min. Caps, 15 v. wkg.—1, 2, 4, 5, 8, 10, 16, 32, 50 mfd., .04 mfd. 10 v., 100 mfd. 6 v., 100 mfd. 12 v., all at 1/10 each. Resistors mostly 10% small, 10 ohms to 10 meg., 3d. ea. h. Ceramics, most values in stock. 1 pfd. to 5,000 pfd. Slide switches, DP/DT, 3/- ea. h.

TRANSISTORS. OC44, OC45 7/6 each, 1.F. Pack OC81D, 2 OC81, 18/6, set. G.E.C. 7/4, 4/6, S6, S7, good output transistors. 3/6 each. Red spots, 2/3, White spots, 2/6, OC76 3/6, CCP71 12/6. OA81 Diodes 2/6, 3EX 00 9d. Terms C.W.O. or C.O.D.

BROADWAY ELECTRONICS
 92 Mitcham Road, Tooting, S.W.17.

BRIAN E. HAMPSHEIR (R & T) LTD.
 Dept PWA, 23 NORTH CROSS ROAD, S.E.22.

6F13 EF80 EF91 6P25 10F1 Z77 25L6GT
 EB91 6P28 6F1 EF50 L63 6F12

SALVAGED. GUARANTEED 100% ALL AT ONE PRICE
 £1 for 10, p. & p. FREE

KITS BUILT, complete, S.A.E. leaflet. J. KINDER (Dept. 4) 6 Hooker Rd. Heartsease, Norwich, Norfolk.

Speakers, 8/6d., 6in., 8in., and 7 x 4in. Ex-Manufacture salvage. P. & P. 2/9d.
 T.V. Tubes, 15/-, 31/7d., 12d., 121. Ex-rental. Ideal spares, Carr. 10/-. Also 36/2d. Very good condition, 35/-, Carr. 10/-. Set tested. Valves 9d. 6AL5, 6AM6, 6D2, 6F14, 8D3, 9D2, 78, EB91, EF50, EF91, P61, SP61, etc: Post 9d. T.V. Sets. Complete for 25/-.
 Stamp for FREE List. Mail Order Only.

P.P. COMPONENTS LTD.,

623 Romford Rd, Manor Pk, London E.12.

A.1. POST FREE BARGAINS. First grade Transistors. White spots 3/9. Red spots 3/- OC44 9/-, OC45 7/3, OC71 5/-, OC76, OC200 6/-. Matched pairs two OC81 and OC81D 21/-, two OC44 and OC45 23/6. Reclaimed Valves all tested: EB91, EF50, EF91 9d., 10F1 1/-, 6F1 2/-, L63, 20D1 3/-, ECL80, PY81, FZ30, E36 4/-, PCF80, PL82, PL83, PY80, PY82, KT33C 4/6, PL38, N37, KT36 5/-, PCL83 6/-. PY32, 6K25 7/6, 185BT 12/6. 10% reduction on six. 25% on 12. Loud Speakers: 6in. x 4in. 5/6, 7in. x 4in., 8in. 6/6. 10% reduction on 12. 25k, 50k. w.w. Pots., S.P. switch 4/6 each. **A.1. RADIO COMPONENTS,** 14 The Borough, Canterbury, Kent.

SOUND RECORDINGS

TAPE BARGAINS IN ALL SIZES. Example: Top Brand 5 1/2in. 1200ft. 19/6 p & p 1/3. S.A.E. for list. Large choice of new and used recorders. E. C. KINGSLEY & CO., 132 Tottenham Court Road, London W1. EUS 6500.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from the great book "The Principles of TV Receiver Servicing". 10/6 all bookhouses and radio wholesalers. If not in stock, from Secretary, I.P.R.E., 20 Fairfield Road, London N8.

MISCELLANEOUS

YOUR OWN Kits built up or assistance given. Bradford/Leeds area. S.A.E.: TVS, 19 Aberdeen Terrace, Bradford 7, Yorkshire.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings, and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 29 Maude Street, Darlington, Durham. Send 2d. stamp.

EDUCATIONAL

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths practical way. Postal instruction based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. P.W. 12, **RADIOSTRUCTOR,** Reading.

The Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/- Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, 20 Fairfield Road, London N8.



£'s MADE

By repairing Radio and TV sets as a job or as a spare time business. Our practical course will show you the way. No previous experience is required.

SEND FOR FREE BOOK TODAY!

RADIOSTRUCTOR

Dept. G77 READING, BERKS.

(Continued on next page)

SITUATIONS VACANT (continued)

IF YOUR HOBBY IS IN ELECTRONICS AND RADIO

perhaps you would be interested in a position on the clerical staff in the Sales Department of an Electronic Component Manufacturer in London, S.W.18. Someone aged 20/35 years, with previous commercial experience. Hours 9—5.30, five day week. Staff dining room, social club, medical facilities. Please write stating age, experience and salary required to Box 39.

RADIO MECHANIC required for work on transistor kits. Good wages and prospects for capable person. Savoy Electronics Ltd., 15 Maiden Lane, Strand, WC2. Phone: TEM 5484.

TRAINEE ELECTRO-MECHANICAL ENGINEERS

The opportunity occurs for bright young men (age 18-22), looking to the future, to build their careers in the computer field.

DO YOU have a real interest in repairing light electro-mechanical equipment and have you, through your hobbies, work or studies, acquired a basic working knowledge of electrical engineering? Are you keen to learn more and willing to work in order to advance?

If so IBM offers you practical training (on overhaul of punched card machines initially) and theoretical instruction in the engineering school, together with assistance with your college studies. After 18-24 months, according to ability, you can progress via the overhaul of more complex machines to a responsible appointment in the Workshop or to the highly responsible position of field Data Processing Customer Engineer. The starting salary is not less than £520 p.a. with free Life Insurance and Pension plans.

Write now to the
MANAGER OF
PERSONNEL SELECTION,
IBM United Kingdom Limited
101 Wigmore Street
London, W.1.

(or telephone or call on
Mr. W. E. CROSS
(BYRON 7286)
Stanley Road, South Harrow,
Middlesex)

Quoting reference: CE/PW/13

**MINISTRY OF AVIATION
E.I.D.
ELECTRONIC INSPECTORS**

required for

Radio, Radar, Components and Electrical Ancillaries in laboratories at Bromley and Woolwich, and for inspection at firms' works in various part of London and Southern England on a resident or a visting basis. Varied and interesting work with opportunities for gaining valuable experience and further training. Excellent prospects of promotion to grades with pay ranging up to £1,400 a year.

PAY for FULLY SKILLED men:

£13. 6s. 0d.—£14. 1s. 0d. per week

or: £14. 6s. 0d.—£15. 6s. 0d. per week

Rate varies according to ability and class of work available.

For men not fully skilled, but with several years' experience in electronic work, there are vacancies at BROMLEY & WOOLWICH, with the following scales of pay:—

£12. 11s. 2d.—£12. 19s. 2d. per week

£13. 0s. 2d.—£13. 6s. 2d. per week

(with prospects of further progression).

All rates quoted are for the London area and for a 5-day week; in the provinces rates are slightly less.

Post coupon (or telephone IMPERIAL 2600 Extn. 19) for further information:—

To: The Personnel Officer, Inspection Division, Aquila, Golf Road, Bromley, Kent. (P.W.)

Please send me further details of inspectors' posts in _____ (type of work desired) at _____ area.

NAME _____

ADDRESS _____

TV AND RADIO, A.M.Brit.I.R.E. City and Guilds, R.T.E.B. Cert., etc. on "No pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London W8.

A.M.I.Mech.E., A.M.Brit.I.R.E. City and Guilds, G.C.E., etc. brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc. write for 148-page handbook, free. B.I.E.T. (Dept. 242B), London W8.

ENGINEERS REQUIRED, experienced in audio techniques and relay circuitry, for work on public address systems. Also VHF test engineer for television equipment. Write, giving details to CLARKE & SMITH MFG. CO. LTD., Hanworth Air Park, Feltham, Middx.

CITY AND GUILDS (Electrical, etc) on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29 Wright's Lane London W8.



Servicing electronic computer for Comet simulator

Make your hobby your career

In today's R.A.F. you can work on some of the most sensitive electronic equipment ever made

The man in this photograph is an instrument mechanic at work. At least, it's called work, but to him it has the fascination of a hobby—a paid hobby at that. Still, he's an enthusiast; anything to do with electronics and he's not happy until he's ferreted out all the secrets. And there are plenty of secrets in the R.A.F. In fact, you don't really know what advanced equipment is until you've handled some of the R.A.F. stuff.

If you have the flair that makes the born electronics man, the R.A.F. offers you a satisfying career. You will get a skilled training that is yours for life. You get paid well, you live well—and you may travel anywhere in the world. There's no doubt about it, —the R.A.F. gives you a secure career—and an adventurous one.

THE FUTURE IS WITH THE R.A.F.

The Royal Air Force

Fill in this coupon and you will be sent, without obligation, a free copy of "The Man on the Ground", an illustrated booklet giving details of all R.A.F. trades.

NAME _____

ADDRESS _____

DATE OF BIRTH _____

Send the completed coupon to

**R.A.F. Careers Information Centre (PW 116E),
Victory House, Kingsway, London, W.C.2.**

D. & B. TELEVISION

Phone: Cherrywood 3955

**131 & 131A KINGSTON ROAD
SOUTH WIMBLEDON, S.W.19
Dept. A.6**

Open Mon.—Sct. 10 a.m.—7 p.m. (Except Wed. 1 p.m.).

Nearest Tube Station South Wimbledon (Northern Line)

"COMPARE OUR PRICES"

FOR THE FINEST, FASTEST SERVICE IN THE COUNTRY

Your Problems are our Business

LOOK! TRANSISTOR PRICES DOWN AGAIN.

MULLARD. OC44 9/-, OC45 8/-, OC71 5/-, *OC72 6/-, *OC76 7/-, *OC77 12/-, *OC81 7/-, OC81D 6/.

Complete set of 6 Mullard Transistors only 35/-, comprising OC44, two OC45's, OC81D, two OC81's. Matched Pair.

MULLARD DIODES: OA81 2/9, OA90 2/9, OA91 2/9.

G.E.C. Transistors: GET875 11/3, GET874 6/11, GET873 6/10, *GET115 7/6, *GET114 4/8.

Complete Set of 6 G.E.C. Transistors, comprising: GET 874, two GET873's, GET114, Matched Pair GET114. Only 28/6.

COMPLETE SET 6 S.T.C. Transistors. Only 25/6.

(* Available in matched pairs. 1/- extra).

Send 6d. for lists of transistor components Speakers, Transformers, etc.

ALL VALVES ARE SOLD SUBJECT TO FULL GUARANTEE CURRENT VALVE LIST

AZ71	8/6	FF92	4/-	PY89	12/-	16AM6	3/-
B95	5/6	EL33	7/6	PZ30	8/-	6AT6	5/6
D77	3/-	EL28	12/-	U22	6/6	6BW6	7/8
DAF91	5/-	EL41	7/9	U24	10/-	6D2	3/-
DAF96	7/-	EL84	6/9	U25	12/-	6F1	4/6
DF91	3/6	EM80	6/6	U26	9/6	6F2	3/-
DF96	7/6	EM84	6/6	U31	7/-	6F13	6/6
DH73	6/-	FY51	7/9	U37	17/-	6F14	9/-
DH77	4/6	FY86	7/6	U50	5/8	6F15	9/-
DK91	6/-	EZ40	6/3	U52	5/-	6F33	6/3
DK92	2/6	EZ41	6/9	U51	5/6	6L1	12/-
DK96	7/3	EZ46	6/9	U51	9/-	6L6	8/9
DL81	8/3	EZ82	8/9	U282	14/6	6L18	8/-
DL82	6/3	EZ84	12/6	U301	17/6	6L19	12/-
DL84	7/-	KT33C	6/-	U801	22/-	6SN7	4/6
DL86	7/-	KT36	8/6	UABC80	8/6	6V6	5/-
EABC80	7/3	KT61	8/3	UB41	7/9	10F1	4/6
EAF42	7/9	KT63	8/3	UBC41	7/9	10C1	10/-
EB41	6/6	KTW61	5/9	UCF89	7/9	10C2	13/-
EB42	3/-	KTW63	5/9	UCG84	12/6	10P13	8/9
EB33	4/6	PCU84	7/6	UCG88	7/9	10P14	8/9
EB41	7/6	PCU89	8/9	UCF80	14/6	12AT6	7/3
EBF80	7/6	PCF80	7/6	UCH21	12/3	12AT7	4/6
EBF89	8/3	PCF82	7/9	UCH42	7/-	12AU7	5/6
EC81	4/6	PCF89	8/9	UCH31	5/6	12AX7	6/3
EC82	5/6	PCL82	7/-	UCI83	12/6	20D1	8/6
EC83	6/3	PCL83	9/9	UF42	2/6	20F2	8/3
ECC84	7/9	PCL84	7/6	UL41	7/-	20L1	12/6
ECC85	7/6	PCL85	15/-	UL44	10/9	20P1	9/6
ECC80	8/-	PL33	8/4	UL46	7/-	20P3	12/-
ECH31	15/-	PL36	9/9	UL84	7/3	20P4	16/6
ECH35	9/-	PL33	14/6	UO8	14/6	20P5	14/6
ECB42	7/6	PL81	9/-	UO9	6/3	278U	14/6
ECH81	7/6	PL82	6/6	UY41	6/-	30C1	7/6
ECL80	7/3	PL83	6/6	UY85	6/6	30FL1	9/3
ECL82	9/9	PL84	8/9	W77	4/-	30L7	7/6
ECL83	11/9	PY31	7/-	Z77	3/-	30P4	11/3
EF80	4/6	PY32	10/-	5U4	4/9	30P12	8/-
EF85	6/3	PY80	6/-	5V4	8/9	52KU	10/-
EF86	8/9	PY81	6/-	5Y3	6/3	53KU	10/-
EF89	6/6	PY82	6/-	5Z4	10/-	54KU	8/6
EF91	3/-	PY83	8/-	6AL5	8/-	185B7	14/6

We pride ourselves that we can obtain and supply any TV spare. Please ask us for ANY components you may require and we are almost certain to have them.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.s 12/6 inc. Insurance. SATISFACTION ASSURED. RETURN POST SERVICE.

LINEAR TREMOLO/PRE-AMP UNIT
Type TPU1, with 3 controls, volume, amplitude and frequency. Inputs for guitar and microphone. Requires power supply of 250 v, 10 mA and 6.3 v, 1 a, available from any R.S.C. or LINEAR amplifier. The unit is merely connected to normal input socket of hi-fi amplifier or Guitar amplifier. Only 5 kns.

D.C. SUPPLY KIT, 12 v. 1 a. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

SELENIUM RECTIFIERS
F.W. BRIDGE 24 v. 2 a. .. 14/9
6/12 v. 2 a. .. 3/11
6/12 v. 2 a. .. 6/11 H.T. TYPES H.W.
6/12 v. 3 a. .. 9/9 150 v. 40 mA .. 3/9
6/12 v. 4 a. .. 12/3 250 v. 50 mA .. 3/11
6/12 v. 5 a. .. 15/3 250 v. 80 mA .. 4/11
6/12 v. 10 a. .. 25/9 250 v. 80 mA .. 5/11
6/12 v. 15 a. .. 35/9 250 v. 250 mA .. 1/9
CONTACT COOLED, 250 v. 75 mA. F.W. (Bridge) 10/11. 250 v. 50 mA. F.W. (Bridge) 3/11. H.W. 250 v. 60 mA .. 5/11

B.S.R. MONARDECK TAPEDECKS
Speed 3in. per sec. With high quality recording heads, 28.19.6. Carr. 5/-.
Cabinets, to take Deck and amplifier 39/6.

LINEAR TAPE PRE-AMPLIFIER
Type LPL. Switched Negative feedback equalisation. Positions for Record (lin. 3in., 4in. and Playback, EM4 Recorder Level Indicator. Designed primarily as the link between a Colman Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 9 kns. S.A.E. for leaflet.

TELEVISION RECTIFIERS. 250 v.. 200 mA. Small size. Only 5/9.

R.S.C. GRAM. AMPLIFIER KIT. 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit etc., supplied. Only 39/9. Carr. 3/9.

HI-FI 10 WATT AMPLIFIERS
Brand new. Manufacturer's discontinued line. Fitted latest Mullard valves, Dual Inputs for "mike" and gram., etc. Bass and Treble controls. High sensitivity and quality. Output for 3 ohm or 15 ohm speaker. For 230-250 v. A.C. **£7.19.9**
Carriage 4/6.

THE SKYFOUR T.R.F. RECEIVER.
A design of a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, SP81, 6VGG. Selectivity and quality excellent. Simple to construct. Point-to-Point wiring diagrams, instructions and parts list. 1/9, maximum building costs £4.19.6. Inc. attractive Walnut veneered wood cabinet 12" 6 1/2 x 5 1/2 in.

R.S.C. TRANSFORMERISED GRAM AMPLIFIER. Output 1 watt, for 3 ohm speaker. Transistors Mullard OC71, OC81D, OC81, OC81. Fitted Vol. Control with switch. Assembled and tested. Suitable for any normal crystal pick-up. Only 69/6.

MULTI-METERS. BABY MI. Sensitivity 2000 ohms per volt. A.C. and D.C. 54/-.
A.10. Basic Meter sensitivity 155 micro-amps. A.C. and D.C. ranges 24-17.6. B.20. Sensitivity up to 10,000 ohms per volt. A.C. and D.C. £6.10.0.

EX. GOVT. SELENIUM RECTIFIERS. 12v. 15 AMP. F.W. (BRIDGE). Only 18/9

EX. GOVERNMENT ACCUMULATORS. Size 7 1/4 x 4 x 2 1/2 in., 2v. 16 A.H. brand new, 6/9 ea., 3 for 15/6.

EX. GOVT. SMOOTHING CHOKES.
200 mA. 3-5 H. 50 ohms. Farmeko 8/9;
100 mA. 5 H. 100 ohms 3/11; 150 mA.
10 H. 50 ohms 9/9; 80 mA. 20 H. 900 ohms 5/9; 120 mA. 12 H. 100 ohms 8/9; 50 mA.
50 H. 1,000 ohms 6/9; 100 mA. 10 H. 100 ohms 6/9; 60 mA. 5-10 H. 250 ohms 2/11.

EX. GOVT. MAINS TRANSFORMERS
Primaries 200-250 v. 50 c.p.s. A.C.
250v. 60mA 6.3v. 2a. 11/9
250-0-250v. 60mA 6.3v. 2a. 12/9
300-0-300v. 60mA 6.3v. 2a. 12/11
3,500v. 5mA 2v. 2a. 39/9
0-35-40-45-50v.. 300mA 6.3v. 3a. .. 17/9
12v. 20a. (carr. 7/6) 59/9

COMPLETE POWER PACK KIT, 19/11.
Consisting of Mains Trans., Metal Rectifier. Double electrolytic, smoothing choke chassis and circuit. For 200-250v. A.C. mains. Outputs 250v. 60mA. 6.3 v. 2a.

R.S.C. POWER PACK, 39/9. Louvred metal case only 9 x 5 1/2 x 2 1/2 in. Stove enamelled. For 200-250v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA, fully smoothed and 6.3v. 2a. Suitable for power requirements of almost any Pre-amp or Radio Tuner.

R.S.C. BABY ALARM or INTER-COMM. KIT. Complete set of parts with diagrams, etc. Housed in two cabinets of pleasing design. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Controllable at both units. An Intercomm of this class would normally cost £20-£30. Only 79/6, carr. 5/- Or assembled ready for use 85-15.0.

R.S.C. (Manchester) MAIL ORDERS to 29 Moorfield Rd., Leeds 12. Terms: C.W.O. or C.O.D. No C.O.D. under £1 Ltd. Postage 2/9 extra under £2. 3/9 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

BIRMINGHAM: 6 Gt Western Arcade Birmingham	SHEFFIELD: 13 Exchange St. Castle Market Bldgs. Sheffield	HULL: 51 Savile St Hull (Half day Thurs.)	LIVERPOOL: 73 Dale St. Liverpool 2	BRADFORD: 56 Morley St. (above Alhambra Theatre) Bradford	MANCHESTER: 8-10 Brown St. (Market St.) Manchester 2	LEEDS: 5-7 County (Mecca) Arcade Briggate Leeds 1
------------------------------------------------------------	---------------------------------------------------------------------------	-----------------------------------------------------------	-------------------------------------------------	---------------------------------------------------------------------------	----------------------------------------------------------------------	-------------------------------------------------------------------

NEW!

DO-IT-YOURSELF TRAINING TECHNIQUE
in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE... PRACTICAL... FASCINATING... 1st stage receiver

Test equipment supplied

LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!

Basic commercial receivers

Serviceing commercial receivers

Amplifier, oscillator and detector circuits

Power supply circuits

No Mathematics!

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation. **AT LAST**—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory. **YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics! **INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses. **IN FACT** for the 'Do-it-Yourself' enthusiasts, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation.

BUILD YOUR OWN • RADIO EQUIPMENT • TEST GEAR
• HI-FI INSTALLATION—AND LEARN AS YOU DO IT

RADIOSTRUCTOR **FREE-POST TODAY**

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

To: RADIOSTRUCTOR (Dept. G107), Reading, Berks.

Name

Address


BLOCK CAPS PLEASE

(821) We do not employ representatives 9-62

CHANGE PLACES



K/135

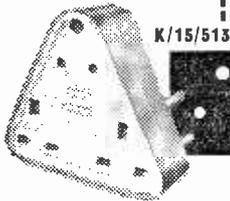

K/15/513

WITHOUT CHANGING PLUG-TOPS



K/135 and K/15/513 ADAPTORS

Essential in homes where 15 amp and 13 amp points exist—ideal when moving from room to room, or home to home, these adaptors provide safe connection for electrical appliances fitted with 13 amp or 5 amp 3-pin plug tops.

Each adaptor provides the following outlets:-
ONE—5 AMP 3 PIN (ROUND) FUSED
TWO—13 AMP 3 PIN (FLAT)

K/15/513 for 15 amp 3-pin sockets
Price: Brown 11/9, White 12/9
 K/135 for 13 amp 3-pin sockets
Price: Brown 10/9, White 12/3

GRELCO LIMITED, MINEHEAD • SOMERSET
 Telephone: MINEHEAD 740

London Office:
 123a Gloucester Rd., S.W.7
 Telephone: FREmantle 3371

DUKE & COMPANY (London) LTD.

TAPE CABINET FOR COLLARO STUDIO DECK 69/6



Beautifully designed covered cabinet in 2-tone colours.
 Size 16 x 15½ x 8½ in.
 Carr. 5/—

TAPE RECORDER AMPLIFIER £9.15.6d.
 By famous manufacturer. Ideal for above. Superb 4-valve amplifier. Two controls and superimposed switch. Sockets for mike and gram. Size 11 x 4 x 6 in. Ins., Carr. 4/6. Drawings FREE with Order.



TUBES

ONE YEARS GUARANTEE

Terms available

FIRST IN LONDON TO DESPATCH DIRECT

21in. 99/6 17in. 90/-
 15in., 14in. 70/-
 Add £1, refundable on receipt of your OLD Tube Ins., Carr. 12/6

COLLARO "STUDIO" DECK £11.19.6

Brand new. Maker's boxed. 3 speed. Press button controls. Insurance & Carriage 5/6.

5 3/4" TAPES Post Free 19/9

SPEAKERS 8/9
 6 and 8in. round and 7 x 4in.

Ex manufacturers salvage. Money back guaranteed. Post 3/3.

Microphones 27/6
 Jack Plugs 1/9

621/3 ROMFORD ROAD MANOR PARK ILF 6001/3

SEE LIST FOR — VALVES - TUBES - T.V. SETS - AERIALS - CHASSIS - TRANSISTORS

18,000 O.P.V. MULTIMETER KIT

Ranges 0-0.25 and 2.5 V DC; 10, 25, 100, 250, 500, 1000 V AC, DC, and output volts; Ohms 100 ohms to 10 Meg. (two ranges); 0.25, 2.5, 25, 250 mA DC (2.5A range 4/- extra). Kit comprises new 3 x 2½ in. Weston 0-50 microamps m.c. meter, all 1% multipliers, 1% ready adjusted shunts, padding resistor adjusted for each meter, 3 other resistors, 1 condenser, meter rec., knobs, switches, sockets, coils, circuit, instructions, wiring diagram, scale (ohms, dB, uF, mA & V. 10V AC scales) i.e. everything except case and battery. Details of 200 pF—0.5uF range. Price 69/-, post free. Circuit, scale, etc. 9d. free with kit. 0-50uA meter as above, with circuit etc. 22/6, post 1/6. Multimeter scale fitted to meter 2/6 extra.

1% High Stability Resistors. S.A.E. list.
PLANET INSTRUMENT CO.
 25 DOMINION AV., LEEDS, 7

What about that 12 w.p.m. Morse Code Test?

You can only reach the goal by keen listening and constant practice with a Morse Key.

The CANDLER System

will help you as it has helped thousands of others over many years, and give you a sound basis.

Send 3d. stamp for details of our Special Course for Amateur Transmitting Licence.

The CANDLER System Co.

Dept. PW. 52b ABINGDON ROAD, LONDON, W.8.

Candler System Co., Denver, Colorado, U.S.A.

2 METRES!

The thrills of 144 Mc/s can now be yours for only 39/6, complete kit! Tunable range 150-100 Mc/s, simplified construction, etc., write today for descriptive literature, also if a newcomer—beginner to Amateur Radio ask for free copy of the world-famous "Globe-King" kits and receivers—stamp to cover postage costs appreciated. Write now to makers:

JOHNSONS (Radio)
 St. Martins Gate, Worcester

The History of Broadcasting in the United Kingdom Volume I:

The Birth of Broadcasting

ASA BRIGGS
 '... an extremely well-balanced and documented account of how broadcasting began in the United Kingdom. The BBC has done well in commissioning an historian of his standing to write this history, and in giving him a completely free hand in the doing of it.'

ENGINEERING Illustrated 42s net
 OXFORD UNIVERSITY PRESS

GRAMOPHONE EQUIPMENT

ALL LATEST MODELS ALL POST FREE Cash Price Deposit Mchly/Pmts. Hire Purchase

	RECORD CHANGERS			
GARRARD AUTOSLIM (GC8 PU)	£7.19.6	£1.12.6	12 of	12/3
GARRARD AUTOSLIM De-luxe (GC8 PU)	£12.14.8	£2.11.8	12 of	18/8
GARRARD AUTOSLIM De-luxe (BV28A PU)	£13.12.9	£2.14.9	12 of	20/-
B.S.R. UA14 (TC8 PU)	£7.17.6	£1.12.6	12 of	12/1
B.S.R. UA14 Monarch (TC8S Stereo/LP78)	£8.17.6	£1.16.6	12 of	13/5
SINGLE RECORD PLAYERS				
GARRARD TA (GC8 PU)	£8.2.6	£1.12.6	12 of	12/6
B.S.R. TU12 (TC8 PU)	£4.5.0	£1.5.0	3 of	£1.3.4

Many of the above can be supplied for stereo working. Send for our Gramophone Equipment List for details.
WATTS RADIO 54 CHURCH ST., Weybridge, Surrey (MAIL ORDER) LTD. (Telephone: Weybridge 4556)
 Please note: Post orders only.
IMPORTANT! Closed for Holidays, AUGUST 11th to 25th

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the *B.I.E.T. School of Electronics*, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee
"NO PASS — NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Oraughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
A.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V. Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME.....

ADDRESS.....

SUBJECT OR EXAM THAT INTERESTS ME.....

(SE/21)

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

H.A.C. SHORT-WAVE EQUIPMENT AND SHORT-WAVE KITS

Famous for over 25 years for V.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Halls, etc.

Improved designs with Denco coils: 5-watt valve Kit, Model "C", Price 25/-; 10-watt Kit, Model "D", Price 50/-; New Addition: Model "K" Receiver, super sensitive "All Dry" Receiver, special inc. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. TH), 44 Old Bond St. ex., London W.1

Please send me FREE and without obligation your 1962 literature.

NAME.....

ADDRESS.....

If you have started or plan to start your own business you need . . .

RADIO AND TELEVISION RETAILER'S HANDBOOK

by F. X. Carus

Company formation, staff selection and training, window display and publicity, servicing facilities, stock selection and control, and management techniques are some of the important topics discussed with a down-to-earth approach.

A business investment for only 35s.

FROM ALL BOOKSELLERS

... or in case of difficulty 37s. by post from GEORGE NEWNES LTD., Tower House, Southampton Street, London, W.C.2.

NEWNES

NEW VALVES!

Guaranteed Set Tested 24-HOUR SERVICE

1R5	1S5	1T4	3S4	3V4	DAF91	DF91	DK91		
DL92	DL94	SET of 4	18/6						
DAF96	DF96	DK96	DL96	SET of 4	26/-				
1D5	7/-	DL35	9/6	PCC89	9/-				
1R5	5/6	DL92	5/12	PCF80	7/-				
1S5	4/6	DL94	6/9	PCF82	7/6				
1T4	3/3	DL96	6/9	PCL82	8/3				
3S4	5/11	EB91	7/-	PCL83	10/-				
5U4C	6/9	EB041	3/6	PCL84	9/9				
5Y3GT	4/6	EB180	7/9	PL36	10/9				
5Z4G	5/9	EB121	12/-	PL81	8/6				
6A4G	8/6	ECC40	13/-	PL82	6/6				
6AK6	2/9	ECC81	4/9	PL83	6/6				
6K7G	1/9	ECC82	5/9	PL84	8/-				
6K8G	4/9	ECC83	6/3	PY32	11/-				
6Q7G	5/6	ECC84	5/-	PY80	7/-				
6V6G	4/-	ECC85	7/6	PY81	6/6				
6V8GT	7/9	ECP80	7/3	PY82	6/-				
6X5GT	5/6	ECP82	8/3	PY83	7/6				
12K7GT	4/3	ECH21	5/9	UC35	11/3				
12K8GT	9/-	ECH42	7/9	UAC80	8/-				
12Q7GT	4/6	ECL80	5/9	UAF42	8/-				
12SN7GT	7/3	EP40	11/-	UBC41	7/-				
35Z4GT	5/-	EP41	7/6	UBF80	8/-				
AZ31	8/0	EP80	4/9	UC35	7/-				
CL33	11/-	EP85	6/6	UCH21	11/6				
DAC32	3/6	EP89	6/9	UCH81	8/9				
DAF91	4/6	EP91	2/9	UCL82	9/3				
DAF96	6/9	EL41	9/-	UCL83	13/-				
DF33	3/6	EL84	6/3	UF41	7/3				
DF91	2/3	EY51	7/3	UF89	6/9				
DH77	6/9	EY88	7/8	UL41	8/-				
DK32	10/6	EZ40	6/-	UL84	6/6				
DK91	5/6	EZ41	7/6	UY21	6/6				
DK92	6/9	EZ80	5/9	UY41	5/6				
DK96	7/3	EZ81	6/-	UY85	6/2				
DL33	7/6	MU14	5/6	VP4B	8/6				
		ECC84	6/9	Z77	2/9				


Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra. Office address, no callers.

GERALD BERNARD
(Note new address—formerly of Leeds)
83 OSBALDESTON ROAD,
STOKE NEWINGTON, LONDON, N.16

JACKSON

the big name in **PRECISION** components

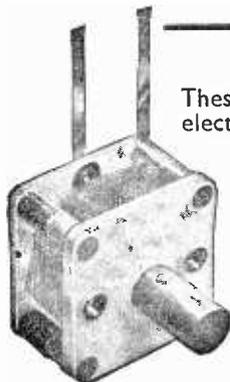Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.



"DILEMIN" CONDENSERS

These miniature solid dielectric condensers are only $\frac{7}{8}$ " square. The $\frac{1}{4}$ " dia. spindle projects $\frac{1}{2}$ " from the Front Plate. Low loss construction provides Power Factor better than .001.

Write for literature

JACKSON BROS. (LONDON) LTD.

(Dept. P.W.) KINGSWAY-WADDON, SURREY

Phone: Croydon 2754-5 Grams: Walfico, Souphone, London

*"There is no Virtue
without Courage—*

*No Reward without
Labour"*

Not simply a school motto but at B.N.R.S. a creed and a way of life. We owe to it all we have and are. If you are prepared to make it your motto and live up to it, we can help you get to the top. It will take time, it will take effort, it will take courage and, as if this were not enough, YOU WILL ACTUALLY BE CHARGED FEES!

If we haven't succeeded in putting you off, write for details, today, to:

Mr. J. SYKES

(M.I.E.E., M.Brit., I.R.E., M.I.N.)

Principal:

BRITISH NATIONAL RADIO SCHOOL
Red Lion Court, Stalbridge, Dorset.

Britain's premier Radio Correspondence School
specialising in City and Guilds examinations.

RADIO ENGINEER'S POCKET BOOK

Facts, figures and formulae indispensable to the service engineer and all concerned in the radio industry.

Trigonometrical logarithmic and arithmetical tables, and algebra formulae have been included.

NEW 13th EDITION

10/6 Postage 6d.

THE AMATEUR RADIO HANDBOOK, an R.S.G.B. Pub. 34/-, Postage 2/-.

WORLD RADIO TV HANDBOOK 1962, Ed. 18/9, Postage 1/-.

ELEMENTS OF ELECTRONIC CIRCUITS, by J. M. Peters. 21/-, Postage 1/-.

THE ORGAN, by W. L. Sumner. 45/-, Postage 1/-.

THE HOME ELECTRICIAN, by F. J. Camm. 12/6, Postage 6d.

MAINTENANCE MANUAL, by Mullard. 16/-, Postage 1/-.

RADIO VALVE DATA, Compiled by "W.W.", 7th Ed., 6/-, Postage 10d.

COMPLETE CATALOGUE 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

LOOK!

TRANSISTORS FROM 1/6 EACH

GREEN SPOT A.F. TRANSISTORS 3 volt type, Only 1/6.

YELLOW SPOT A.F. 6 volt 2/- each.

RED SPOT down to 2/6 each.

WHITE SPOTS down to 2/6 each.

YELLOW/GREEN now only 3/- each.

RED/YELLOW R.F. type 4/6 each.

MINIATURE DIODES 3 for 2/-, 7/- doz.

MULLARD TRANSISTORS

OC44 9/3, OC45 9/-, OC171 10/6, OC170 9/6, AF114 11/-, AF115 10/6, AF116 10/-, AF117 9/6, OC71 6/6, OC78 8/-, OC72 8/-.

Matched pairs OC72 or OC81 16/- pair.

DIODES OA70, OA79, OA81, OA90, OA95 all 3/- each.

TRANSISTOR TRANSFORMERS by REPANCO. Interstage Type TT49 4.5 : 1 5/-. Driver Type TT45, 5/- each. Output Type TT46, 5/- each.

TRANSISTOR HOLDERS 1/- each. J. B. DILECON CONDENSERS. .0001, .0002, .0003 or .0005 all 4/9 each.

REACTION CONDENSERS, .0001 3/-, .0003 3/9, .0005 4/-.

DRX1 Crystal Set Coils 2/6.

Repanco DRR2 Coils 4/-.

ALL SENT POST FREE IN U.K. by

PETHERICK'S RADIO SUPPLIES

22 High Street, Bideford, N. Devon

Tel.: Bideford 1217

S.A.E. WITH ALL INQUIRIES PLEASE

CABINETS & HI-FI EQUIPMENT

We can supply any cabinet to your own specification



The Lowboy
Price 24 gns.

This is only one example of—
THE LARGEST RANGE OF CABINETS
IN THE COUNTRY.

Equipment is also our speciality.
SEND TODAY FOR THE TWO
NEW LEWIS CATALOGUES

Designed to assist your choice of cabinet and equipment.
THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. THE unique 64 page equipment catalogue.

Please send your two new catalogues enclosed is P.O. for 3/6 which will be credited against any purchase I make.

LEWIS radio

100 (P92) Chase Side, Southgate,
London, N.14. Pal 3733/9666

The 'NORPAK'

MAINS POWER PACK KIT FOR TRANSISTOR RADIOS

Saves battery costs, boosts and greatly extends life of old batteries. Miniature Size—4 x 2 x 1 1/2 in. In attractive two-tone plastic case. Assembled in an hour. Normal output 9 v. 100 mA. (Adjustable) Full Mains Transformer. Full wave germanium diodes. Cartridge use. Complete Kit with Plans **35/-** Plus 1/6 P.P. (Ready assembled 45/-).

P.W. 6 OWNERS!!
Convert your set to 7 transistors in **TWO MINUTES!!** with our preassembled extra stage. **COMPLETE** Plus 6d. P.P. **17/6**

FIRST GRADE COMPONENTS FOR
PW TROUBADOUR
PW BRITANNIC 2
And many other PW designs.

ANNOUNCING!

P.W. "MERCURY" 6 PRINTED CIRCUIT VERSION



£9.17.6
Plus 2/6 P.P.

All parts required

This exciting new Transistor Superhet gives superb performance on a 7 x 4 in. speaker housed in attractive two-tone cabinet with ferrite aerial. New extras.

For both of these fine kits every item down to the last nut and bolt is supplied together with detailed building plans. All parts sold separately. Send 1/6 for Building Plan (FREE with Kit).

PAY AS YOU BUILD SCHEME

AT NO EXTRA COST the above sets may be bought in 3 complete stages of 56/8 ("PW" 6) or 65/10 ("Mercury" 6) each plus 1/6 P.P. (state A, B, or C).

ALIGNMENT SERVICE

We Offer a very comprehensive service for both the above versions, including Fault Finding, at reasonable charges (write for details).

LATEST VERSION !!

P.W. 6-TRANSISTOR Medium and Long Wave Pocket Superhet

THE CONTINUED POPULARITY OF THIS FAMOUS SET IS PROOF OF ITS VERY HIGH QUALITY AND FINE PERFORMANCE

- 250 mW Push-Pull Output on 2 1/2 in. P.M. Speaker.
- Printed Circuit.
- Guaranteed first grade Miniature Components.
- High Q Internal Ferrite Rod Aerial.



All parts required **£8.10.0** Plus 2/- P.P.

NORCOL LTD

147 LONDON RD., YORKTOWN, CAMBERLEY, SURREY

Phone: CAMBERLEY 22760

GRAB: This Month's Bargains

★ SHADED POLE MOTORS ★
230v. or 110v. operation. Ideal for fans, blowers or models. One only, 12/6, plus 2/- p. & p. Or pair, £1, plus 2/6 p. & p.

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telecom (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.
COPPER WIRE. 14 G., H/D 140ft. 17/-; 70ft. 8/6. P. & P. 2/-.
Other lengths pro rata.
RIBBED GLASS. 3in. aerial insulators, 1/9 each. Shell ins 2in. 9d. each. P. & P. 1/6. Up to 12.
CERAMIC FEEDER SPREADERS. 6in. type F.S. 10d. each. P. & P. 2/-.
CERAMIC "T" PIECES. Type A.T. for centre of dipoles, 1/6 each. P. & P. 1/-.
2 METRE BEAM 5 ELEMENT W.S. YAGI. Complete in box with 1 - 2 1/2in. mast head bracket. PRICE 49/- P. & P. 3/6.
SUPER AERIAL CABLE. 75 ohm, 300 watts, very low loss, 1/8 per yard. P. & P. 2/-.
50 ohm, 300 watt coax, very low loss, 1/9 yd. P. & P. 2/-.
ABSORPTION WAVEMETERS. 3,000 to 35,000 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham Bands, marked on scale. Complete with indicator bulb. A MUST for any Ham shack. 22/6 post free.
VARIABLE CONDENSERS. All brass with ceramic end plates and ball race bearings. 50 pF. 5/9. 100 pF. 6/6. 160 pF. 7/6. 240 pF. 8/6, and 300 pF. 9/6. All fitted with rear extension for ganging. P. & P. 1/-. Also Flexible Couplers, 1/- each. B.I. 8 MFD. 1,200 v. D.C. Wkg. Capacitors, 12/6 each. P. & P. 2/-.

CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS
Dept. "P", 110 Dale End, Birmingham 4. (CEN 1635)
(No C.O.D. under £1 please). (By return service)

AVO METERS

MODEL 7 £11.10.0. MODEL 7 Mark II £12.10.0.
Guaranteed perfect. Complete with leads and batteries. Registered post and packing 5/- extra.

"ERECON" PANEL METERS. Rectangular 4 1/2 x 4 1/2in. (3in. barrel), 0-500µA. BRAND NEW (Japanese). 52/6.
PANEL METER. 0-500µA. (Surplus). Circular 2in. scale. 0-5. Guaranteed good quality. 15/-.
SILICON RECTIFIERS. A modern marvel. Type 1EA2 (4 x 1/2in. will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier, 8/6.

H.R.O. RECEIVERS—SENIOR MODEL. M.X. Complete with 9 coils from 50 Kc/s—30 Mc/s. A superb communications receiver. Guaranteed in brand new condition, £25. carr. 30/-.
POWER UNIT 59/6. extra carr. 5/6.

R107 RECEIVERS. 1.2 Mc/s—17.5 Mc/s continuously, 3 wave bands. Completely self contained with speaker and power unit for A.C. mains and 12 v. battery operation. Guaranteed perfect. £13.10.0. Carr. 30/-.

PCR COMMUNICATIONS RECEIVER
Type PCR. Has self-contained speaker. Covers 850-2000, 200-550 and 18-50 metres.
AS NEW CONDITION.....£6.19.6
Type PCR-2. Requires external speaker. Covers 850-2000, 200-500 and 18-50 metres.
USED (Good condition).....£5.19.6
Carriage (any type) 10/6. Full details S.A.E. Any model fitted with BRAND NEW INTERNAL POWER SUPPLY, guaranteed ready for use on A.C. mains, £2 extra.

Moving Coil Phones. Finest quality Canadian, with Chamois ear muffs and leather-covered headband. With lead and Jack plug. Noise excluding, supremely comfortable. 19/6, post 1/6.

We now stock The Pocket 4, a neat little job which can be made for 42/6. (Printed Circuit Version 52/6), and The Good Companion (a super job equal to the best). Easily constructed for only £9.19.6. Gladly demonstrated to callers.

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martins Lane, London, W.C.2

TEmpie Bar 0645.

Shop Hours 9-6 p.m. (9-1 p.m. Thursday)
Open all day Saturday.

NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO and ELECTRONICS

EVEN QUALIFY FOR A
CERTIFICATE

It's the most exciting news of the year! Just imagine. You can get 35 large, fact-packed lessons for little more than 1/- per lesson! The lessons are crystal clear, practical, easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert.

Compares favourably with some courses costing ten times as much. You save because you receive all the lessons at one time and are not required to purchase equipment you do not need.

This is a real home-study course that has been bound into one giant 8 x 11 in. 216 page manual. Each page is divided into two columns. A wide column features the text, while a narrow column at the side has the instructor's comments, helpful suggestions and additional pictures to simplify the difficult parts.

Everyone can benefit from this practical course. No old fashioned (or pseudo modern) methods used here, just straight forward, easy to understand explanations to help you make more money in electronics.

As an optional extra, you can pay a further fee if you wish to complete the questions set at the end of each lesson and have an expert check your answers. Students who attain a minimum of 60% correct answers can qualify for a certificate of proficiency in basic radio and electronics. Details sent with each course ordered.

You must be convinced that this is the best value you have ever seen in the electronic training, otherwise you can return the manual (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven days.

The price? Only 38/-, plus postage.

FREE TRIAL OFFER!

To SIM-TECH TECHNICAL BOOKS, Dept. W.A.3, Gater's Mill, West End, Southampton, Hants.

RUSH Radio and Electronics Course for seven days examination. If I keep the course I can either pay 37/6d. cash or 12/6d. deposit after seven days and two payments of 12/6d. monthly. Otherwise I will return the course post-paid and owe nothing.

SAVE! Send only 38/- if paying cash with order. (We pay postage). Same 7-day money-back guarantee.

Name _____

Address _____

City _____

County _____

Lyons Radio Ltd

3 Goldhawk Road,
Shepherds Bush, London W.12

Telephone SHEpherds Bush 1729

HIGH RESISTANCE HEADPHONES. Ex. Govt., extra sensitive, guaranteed with headband and lead. PRICE ONLY 9/6 pair. LOW RESISTANCE ditto, 8/- Postage, either type, 2/-.

RAY 5 RADIO RECEIVERS. Special purpose 11 valve fixed frequency (26.5 Mc/s) 12 x 9 x 8 in. black crackle case, fitted with 24v. D.C. input dynamotor, 7.8 Mc crystal and output level meter. Valve line-up: 2-12S7, 3-6AB7, 6H6, 12J5, 12SR7, 6AC7, 12S37, 12A8. New condition. No data available. "Give away" PRICE only 35/-, carr. 7/6.

BATTERY CHARGERS. 6 or 12 volt for 20/250v. A.C. mains. Charging rate 3 to 4 amps automatically reducing as battery charges. In attractive louvered metal case, 10 x 6 x 5 ins. Fitted ammeter and fuse, complete with instructions, mains and output leads fitted with battery clips. Brand new and guaranteed. PRICE ONLY 52/6, post 3/9.

H.P. MOTORS. 200/250v. A.C. mains, new, unused Crompton Parkinson split phase induction type, spindle 2 x 1/2 in. dia., 1.440 r.p.m. horizontal or vertical mtg. BARGAIN PRICE 75/-, carriage 7/6.

SUPPLY UNITS W/S. No. 19 Mk. 3. 12v. D.C. input fitted with twin rotary transformers with outputs of 250v. D.C. at 125 ma and 500v. D.C. at 65 ma, fuses, switch, pilot light, etc. In metal case 10 x 8 x 6 ins. PRICE ONLY 21/-, carriage 6/6.

AERIAL RODS. Set consists of 3 copper-plated tapering steel sections, each 4 ft., making up a 12 ft. aerial or the ever popular fishing rod. PRICE ONLY 7/6, carriage 2/6.

MOUNTING BASE. Hard rubber with metal fixing plate surround. PRICE 3/-. If supplied separately, post 1/6.

Please mention
"Practical Wireless"
when replying to
Advertisements.

NEW REPANCO TRANSISTOR COMPONENTS

Push Pull Driver Transformer
Type TT45, 5/-

Push Pull Output Transformer
Type TT46, 5/-

Interstage Transformer Type
TT49, 5/-

Dual Range Ferrite Aerial Type
FR2, 12/6

2.5 millihenry Choke Type CH1
2/6

Radio Experimental Products Ltd.

33 MUCH PARK STREET,
COVENTRY

PADGETTS RADIO STORE

OLD TOWN HALL, KNOWLER HILL,
LIVERSEDGE, YORKS.

Phone: CLEckheaton 2866

Type 46. RXTX Walkie Talkie Set, complete with two ARP12, one AR8, one ARTP2, one AP14, one APP7 Valves. Less crystals, plug-in coil and send/receive switch, but otherwise the set is complete. The sets are in new condition. We have 1,500 sets to clear at the special price of 8/6. Post 3/6. No gen on the set at this price.

Complete TV Chassis for Spares. Less valves, 12in., four for 10/-, Carr. B.R.S. 7/6. 14in. Chassis, four for 15/-.

P.31 Speakers all 3 ohms. Removed from TV Sets, perfect condition. Rola 6 x 4in. 5/-, Goodmans 7 x 4in., 6/-; Philips 5in. round, 5/-; Rola, R. and A. Round, 3/6; 8in. Dish, 5/-; 8in. round, 6/-; 10in. round, 10/-. Post extra on any speaker, 2/-. Up to six can be sent for 3/6.

Germanium Diodes, 4/8 doz. Post Free. 6B7 4/8, ex. units. All post free. KT66 6/8, 807 USA 5/-, 6V6 3/-, 6V6GT 4/6, 6C4 2/-, VR150/30 4/-, 12A6M 2/-, EF91 1/8, EB91 1/9, EL81 1/9, 6J6 2/6, 6AQ4 3/-, EF50 1/6, or 6/6 doz., 5U4 4/6, 5Z4 5/6, DH63 4/-, 554 1/6, 5001 9d. or 5/- doz. USA EF50 Red 2/6.

Valves Removed from T.V. Sets. All post free. All tested on a Mullard valve tester and are 100% as new. They carry a three months guarantee. We also have a large stock of old type radio valves and other T.V. valves not listed.

ECL80 4/-, ECC82 5/-, EL38 4/-, EY51 2/6
ECL90 4/6, EB91 9d., EF91 9d., 6F1 1/-, 6FK1
2/-, 6F14 5/-, 6LD20 5/-, 6SN7 2/8, 6SL7 2/9
6Y6 2/6, 6CG6 2/6, 6SS2 2/-, 10C1 2/-, 10C2 2/-
10F1 1/-, 10P13 5/-, 10P14 5/-, 20D1 3/-, 20F1
5/-, 20L1 5/-, 20P4 9d., 185BT 8/6, U35 5/-,
U281 5/-, U282 5/-, U301 8/6, U329 5/-, KT54
5/-, PL81 5/-, PL82 5/-, PY81 4/-, PY82 5/-,
PY80 5/-, PL38 5/-, PZ30 4/-, PCF90 4/-,
PCC84 4/6, PL83 5/-, PL33 4/-, B36 4/-, N37 5/-,
L63 3/-, 6J5 3/-, 275U 5/-, 41 4/-, EF90 1/6
10/- per doz. Grades 2, 6d., 4/- per doz.

Perfect Reclaimed Tubes 6 months guarantee. 12in. 17/-, 14in. 30/- Carr. and ins., 7/6.

Complete TV Sets Untested. 12in. 20/- 14in. 30/-, 14in. 13-channel 50/-, 17in. BB only 50/- Carr. BRS 10/- Sent at owner's risk.

TV Tubes Completely Rebuilt and Refaced. 12 months guarantee. Old glass no required, 12, 14, 15, 16 and 17in., any make. All the same. Special trade price of £3.15.0 Carr. and ins., 7/6.

Special Offer of New Boxed Valves ARP12 1/6, 6 for 5/6, MSPEN 2/6, X41 4/ (KT263, 6J7) 3/-. AC2PEN 4/-. All post free. New Transistors, OCT2 3/6, OC45 4/- Post free.

RES/CAP. BRIDGE 38/-

Checks all types of resistors, condensers
6 RANGES

Built in 1 hour. Direct reading
READY CALIBRATED

Stamp for details of this and other kits.
RADIO MAIL (Dept. PB)

Raleigh Mews, Raleigh Street, Nottingham

RADIO BOOKS

A BRILLIANT NEW
Pictorial approach to understanding
BASIC ELECTRICITY
BASIC ELECTRONICS

In Simple straight-forward words and
Clear Explanatory Pictures, The Reader
is taken Step by Step from Picture to
Picture.

LEARN WHILE YOU PAY
FOR ONLY 2/6 PER WEEK
Write for FREE Illustrated Prospectus
giving details of instalment plan.

**BUMPER BOOK OF TRANSISTOR
CIRCUITS FOR HOBBYS, 6/
ELECTRONIC NOVELTIES, Bradley 5/
ELECTRONIC GADGETS, Bradley 4/
SERVICING TRANSISTOR RECEIVER**
New and enlarged edition. Pettit, 8/-.
All above titles include postage.
SEND STAMP FOR LISTS.

SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLE
KENT. Tel. Hurstway 1818

SUPER 5 TRANSISTOR POCKET RADIO

INCORPORATING

- Printed Circuit —
- Miniature earpiece
- Completely portable
- No Aerial or Earth is required



- ★ Size 4 3/4 x 3 1/2 x 1 1/2 in.
- ★ Output 200mW
- ★ 5 First quality transistors
- ★ Push-pull output
- ★ Fitted 2 1/2 in. high-flux moving coil speaker



ONLY **59/6**

3/6 P. & P.

Complete with internal high-gain ferrox aerial and twin tone case in Red and Black. Med/Long wave. Earpiece has sub-min jack and socket with 3ft. fine cable. Almost invisible in use. All parts available separately. Circuit diagram 1/6—Free with parts.

RADIO & TV LTD. (Dept. 5T)

21B HIGH STREET, ACTON, LONDON, W.3.



UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let I.C.S. tuition develop your talents and help you to success.

STUDY IS EASY with I.C.S. guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

Take the right course now . . .

ADVERTISING Gen. Advertising, Retail & Dept. Store Copywriting.	HORTICULTURE Complete Gardening Flower & Veg. Growing
ART Oil & Water Colour Commercial Illustrating	MANAGEMENT Business Management Hotel Management Office Management Industrial Management Personnel Management Work Study, Foremanship
BUILDING Architecture, Clerk of Wks., Bulldg. Constr. & Allied Trades, Quantity Surveying.	MECHANICAL & MOTOR ENGINEERING Engineering Maths., Weldg. Diesel Engines and Locom. Inspection, Workshop Pract. Refrigeration, Motor Mech. Running and Maintenance (many other subjects)
CIVIL ENGINEERING Highway Eng., Struct. Engrg., Concrete Engineering	PHOTOGRAPHY Practical Photography P.D.A. Examination
COMMERCE Bookkeeping, Accountancy, Office Training, Costing, Secretaryship Storekeeping Shortland & Typewriting	POLICE Police Entrance Exam.
DRAUGHTSMANSHIP Architectural, Mechanical, Math. & Machine Drawing Drawing Office Practice Structural Drawing	RADIO, T.V. & ELECTL. Radio Servicing & Engrg. T.V. Servicing & Engrg. Radio Constr. (with kits)
ELECTRONICS Industrial Electronics Computers & Maintenance	SELLING Commercial Travellers Sales Mangt., Ret. Selling
FARLING Arable & Livestock Farm Machinery Maint. Pig & Poultry Keeping Market Gardening	WRITING FOR PROFIT Short Story Writing Free-Lance Journalism
FIRE ENGINEERING I.F.E. Examinations Fire Service Promotion	And many other subjects
GENERAL EDUCATION Good Eng., Foreign Langs. G.C.E. subjects at ordinary or advanced level	

INTENSIVE COACHING for all principal examinations including C.I.S., A.C.C.A., I.C.W.A., B.I.M., A.M.I. Mech. E. Brit. I.R.E., I.Q.S., City & Guilds of London Institute, R.H.S., P.M.G. Certificates in Radiotelegraphy, etc.

Start today the I.C.S. way!

(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on _____

Name _____

Address _____

Occupation _____

9.62

INTERNATIONAL CORRESPONDENCE SCHOOLS

SERVICE A IN SMALLS

CONDENSERS

Miniature Ceramics. All values, 1—5,000 P.F., 6d.

SMALL PAPERS 150v.

.001, .002, .003, .005, .01, .02, .04, .05, .1, 9d.
.25, .5, 1/3.

SUBMINIATURE ELECTROLYTICS

15V. 1, 2, 4, 5, 8, 10, 16, 32, 50mfd. 2/-.

12V. 100, 250, 500mfd. 3V. 1,000mfd. 2/6.

Miniature Resistors, 10Ω—10M., 3d.

All suitable for transistor circuits and like all our components they are Guaranteed for 12 months.

★ MULLARD TRANSISTORS ★

A.F. pack, 1 OC81D and matched pair, OC81, 18/-.

R.F. pack, 1 OC44, 2 OC45, 24/9. G.E.C. Diodes, 1/- each. 6 for 5/-.

Yellow Plastic Case, 3 x 1 1/4 x 1 3/8 in. Covered metal hinge, sprung snap lid, 1/6. 3 for 3/10. Ideal for small radios.

Why not send stamp for latest component list?


Build a Battery Operated Record Player E.M.I. 9 v. 4 SPEED PLAYER UNIT, £5.9.6. E.M.I. 6—9 v. 4 TRANSISTOR. Printed circuit amplifier. 1 watt output. With Speaker, £4.9.6. The two units, £9.9.0.

STUART SPARES

34 ESSEX RD., RUSHDEN, NORTHANTS

ALL-TRANSISTOR TIME SAVER
OFFICE OR HOME TELEPHONE PICK-UP AMPLIFIER

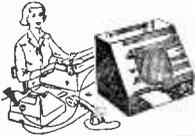★ No more "holding on" wasting time waiting for your call to come through. When it does the amplifier can be switched off if required. No connections, just press the pick-up coil to back of phone as below. Fully Guaranteed. Housed in attractive Gold Finish Cabinet.



BUILT, TESTED, READY TO USE

£5.10.0
P.P. 2/6

4 TRANSISTOR BABY-ALARM
 Very sensitive, £5.10.0 P.P. 2/6.




MODEL TH-L33

2,000 ohms per volt AC/DC. Size 5 x 3½ x 1½ in.

79/6 Fully Guaranteed with test leads, battery and instructions.

0/10/50/250/500/1000 volts D.C., 0/10/50/250/500/1000 volts A.C., 0/500µA/10/250mA., D.C.

3 ranges resistance 0/10K/100K/1 Meg. Capacity and db ranges.

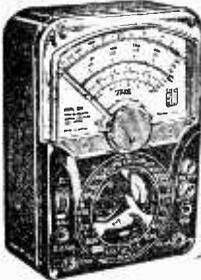

MODEL 500

30,000 ohms per volt multi-meter

£8.19.6

Fully Guaranteed

8 Ranges D.C. volts to 1 kV.
 7 Ranges A.C. volts to 1 kV.
 5 Ranges D.C. current to 12 amps.
 3 Range resistance to 60 meg.
 Short circuit, Buzz test, Output meter dB, etc., etc. Size 6½ x 4½ x 2½ in. With Leads, Batteries and Instructions.



MODEL TP55

A.C./D.C. voltage upto 1,000 in 5 ranges. D.C. current 4 ranges up to 500mA. 4 range resistance to 10 megs. Capacity dB scales, etc. 20,000 ohms/volt Fully Guaranteed

£5.19.6

With Test Leads, Battery and Instructions. Size 5½ x 3½ x 1½ in.

LATEST ILLUSTRATED CATALOGUES NOW AVAILABLE 1/-

- 4-Transistor 2-way Intercomm. 2-way buzzing, 2-speakers, ready to use, 8 gns. P.P. 2/6.
- Miniature 15 watt Solder Iron, ½ bit. Ideal for all printed circuit work, 29/6, P.P. 1/6.
- New Model Control Book with 60 pages of transistor circuits, 7/6, P.P. 6d.
- Complete Set of Meter Leads with Prods. Clips etc. with pouch, 8/6, P.P. 1/-.
- Telephone Recording Coil to record conversations. For all amplifiers and recorders, 14/-, P.P. 9d.
- Printed Circuit Kit, to etch your own circuits. Complete with boards and details, 19/6, P.P. 1/-.
- Miniature 850 ohm Record/Playback Head, with mounting block, 12/6, P.P. 9d.
- 4,000 ohm lightweight Headphones with leads. Very sensitive, 12/6, P.P. 1/-.
- Transistor Pocket RF, IF Generator for Radio, TV etc. Fault finding, 52/6, P.P. 1/-.
- 8-Range All Transistor Signal Generator. 200 kc/s to 220 mc/s: RF, AF, IF, HF, etc., £7.10.0, P.P. 3/6.
- GS12C (Dekatron) Bi-directional 11 way indicator tube. Brand new, 25/-.
- 4½-9 volt Tape Recorder Motor, governed, 12/6, P.P. 1/-.
- 30 watt Pocket Solder Iron, with pocket pouch and mains plug, 18/6, P.P. 1/-.
- 931A Photo Multiplier. Brand new, 60/-.
- 1 Kc/s Transistor Audio Test osc., variable output, 39/6, P.P. 1/6.
- Crystal Contact Microphone. Very sensitive. Ideal for Guitar, 12/6, P.P. 9d.
- Practical Transistor Circuits. 40 circuits to build, 3/6.
- Personal Earphones with leads, Jack plug and socket, 600 ohm, 10/6; 1000 ohm 12/6; Crystal 9/6; 8/10 ohm 9/6.
- W/W Erase Head, FE7, 7/6, P.P. 6d.
- Dynamic Microphone, 49/6, P.P. 1/6.
- Extension Speaker Unit. Plugs into phone socket of most portables. Gives big set volume. Ideal for car use, 57/6, P.P. 1/6.

Miniature Panel Meters	Miniature 250 mW Amplifier.
0/50µA (DC) 39/6	Size 3 x 1½ x 1½ in.
0/500µA (DC) 32/6	Push-Pull output.
0/1mA (DC) 27/6	Built and tested with circuit.
0/5mA (DC) 27/6	52/6, P.P. 1/6
0/300 volts (DC) 27/6	

Brand New Boxed

- 7-Section Telescopic Aerial, 12/6.
- LAI Ferrite Pot Core, 12/6, P.P. 6d.
- Stereo Stethoscope Type Miniature Phones, 27/6, P.P. 1/6.
- Miniature Jack and Socket, 3/6, P.P. 6d
- No. 19 Set Crystal Calibrator with Handbook, 79/6, P.P. 2/-.
- New 2-way Intercomm with 2-way calling. Supplied with cable, battery, etc. Housed in moulded cabinets, 89/6, P.P. 2/-.
- Battery Eliminator and Charger for PP3 9 volt Batts. Ready to use. 29/6, P.P. 1/6 with details
- 9 volt 80 mA battery eliminator kit for larger portables, 35/-, P.P. 1/6.
- Transistor Pocket Radio with speaker output. Complete in moulded cabinet with battery, earphone, carry case telescopic aerial, etc., 99/6, P.P. 1/6.

Henry's Radio Ltd

PADddington 1008/9
5 HARROW ROAD, LONDON W2
 Open Monday to Sat. 9-6, Thurs. 1 o'clock
TRADE SUPPLIED

PLEASE TURN TO BACK PAGE

TRANSISTOR PORTABLE TAPE RECORDER

FOR OFFICE, HOME OR TRAVEL
 ● Play/record up to 30 mins. ● Built-in speaker, volume control, batteries and play/record/rewind. ● Quality reproduction. ● Sturdy case 6 x 8½ x 2½ in.

£10.10.0
P.P. 3/6.



Fully guaranteed

Supplied complete with microphone, tape, batteries and personal phone (for monitoring), and full instructions. Built and tested.

CRYSTAL MICROPHONES

- ACOS 39-1. Stick Microphone with screened cable and stand (list 5 gns.), 32/6, P.P. 1/6.
- ACOS 40. Desk Microphone with screened cable and built-in stand (list 50/-), 15/-, P.P. 1/6.
- ACOS 45. Hand Microphone with screened lead, very sensitive, 25/-, P.P. 1/6.
- 100 C. Stick Microphone with muting switch and screened cable, detachable desk stand, cord and neck, 39/6, P.P. 1/6.
- MC 24. Stick Microphone with muting switch and cable, 25/-, P.P. 1/6.
- LAPL. Miniature Mic. With clip. Ideal for recording, 15/-, P.P. 1/-.

3/4 WATT 4 TRANSISTOR AMPLIFIER



● 1 watt peak output.

± 3db 70cs to 12 kc/s.

Output to 3 ohm speaker

9 volt operated.

Details on request.

Built and Tested Kit of Parts
69/6 OR 59/6
 P.P. 1/6 P.P. 1/6

A printed circuit high gain amplifier size 4 x 2½ x 2½ in. using Mullard OC71/OC81D and 2-OC81 Transistors. Ideal for Intercomm., Record Player, Tuner Amplifier or any application requiring a quality and reliable amplifier.



BATTERY RECORD PLAYER

● 6-7½ volt Garrard turntable with crystal pick-up. Plays 45 r.p.m. ideal for above amplifier.

65/- P.P. 1/6

● Suitable cabinet for amplifier and player 22/6.

TRANSISTORS AND COMPONENTS

We can supply from stock 1st grade transistors, diodes, rectifiers. Silicon or Germanium. Matched sets at special reduced prices. Complete list on request.

QUOTATIONS FOR YOUR CIRCUIT BY RETURN

Practical Wireless

BLUEPRINT

SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for the PW Monophonic Electronic Organ and the PW Roadfarer.

The Index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price	Title	Number	Price
CRYSTAL SETS			A.C. Fury Four	PW20	2/6
Junior Crystal Set	PW94	2/-	Experimenter's Short Wave	PW30a	2/6
Dual-wave Crystal Diode	PW95	2 6	Midget Short Wave Two	PW38a	2/6
STRAIGHT SETS			Band-Spread Three (Battery)	PW68	2/6
Battery Operated			Crystal Receiver	PW71	2/-
Modern One-valver	PW96	2/6	Signet Two (Battery)	PW76	2/6
All-dry Three	PW97	3 6	Simple S.W. One-valver	PW88	2/6
Modern Two-valver	PW98	3/6	Pyramid One-valver	PW93	2/6
SUPERHETS			BBC Special One-valver	AW387	2/6
A.C. Band-pass Three	PW99	4/-	A One-Valver for America	AW429	2/6
A.C. Coronet-4	PW100	4/-	Short-Wave World Beater	AW436	3/6
A.C./D.C. Coronet	PW101	4/-	Standard Four Valve S.W.	WM383	3/6
The PW Pocket Superhet	—	5/-	Enthusiast's Power Amplifier	WM387	3/6
MISCELLANEOUS			Standard Four Valve	WM391	3/6
The PW 3-speed Autogram	—	8/-	Listener's 5-Watt Amplifier	WM392	3/6
The PW Monophonic Electronic Organ	—	8/-			
(No constructional details are available with this blueprint)					
The PW Roadfarer	—	5/-			
(No constructional details are available with this blueprint)					
TELEVISION					
The PT Band III converter	—	1/6			

QUERY COUPON

This coupon is available until 7th September, 1962, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, SEPTEMBER, 1962

Redesigned 'Contessa' Mk. III

★ combined portable and car radio ★

- NOW WITH 600 mW MELLOWTONE OUTPUT ON MEDIUM AND LONG WAVES.
- NOW FITTED HORIZONTAL TUNING SCALE WITH ALL STATIONS CLEARLY MARKED.
- NOW SUPPLIED WITH SIX MULLARD TRANSISTORS AND TWO DIODES.
- NOW FITTED RECORDING SOCKET AND CAR AERIAL SOCKET.
- NOW SUPPLIED WITH TWO-TONE BEIGE OR TWO-TONE BLUE CABINET WITH GOLD FITTINGS.



GUARANTEED THE VERY BEST OBTAINABLE

TOTAL COST
£10.19.6 P.P. 3/6

OVERALL SIZE
10½ x 7½ x 3½ in.

● All parts sold separately ●

● Detailed Leaflet on Request ●

The New "CONTESSA" 6-Transistor Portable Superhet Radio features simple printed circuit construction and fully illustrated building instructions, with all parts clearly marked and identified. Fitted with 8 inch Ferrite Aerial, double IFT's and the latest in components and design. Full tuning of both Medium and Long Wave Bands with unbeatable Selectivity and Sensitivity. Clearly marked station dial and room filling "MELLOWTONE" push-pull output are standard features. Performance is guaranteed to be better than any other design available to the home constructor whether used at home, out and about, or in a car.

FULL AFTER SALES SERVICE AND GUARANTEE

★ ALL THESE EXTRA FEATURES AT NO EXTRA COST ★

"QUINTET" MEDIUM AND LONG WAVE POCKET RADIO

PUSH-PULL SPEAKER OUTPUT

Size
5½ x 3 x 1½ in.
Red or Blue
with Gold
trim.



Total Cost
£5.10.0 P.P. 2/-

A Five-Transistor and Diode medium and long wave printed circuit loudspeaker radio. Features Mullard transistors and plainly marked printed circuit with carded components. Excellent results with full station separation guaranteed. Including Radio Luxembourg. Push-pull output up to 200 mW. Fitted 'Phone/Record socket and Car aerial socket. Full after sales service and guarantee.

"CAPRI" POCKET SIX. 6-TRANSISTOR MEDIUM AND LONG WAVE POCKET SUPERHET RADIO.

● SIZE 4½ x 2½ x 1½ in. REALLY POCKET SIZE ●

The most compact 6-transistor and diode radio with speaker available to the home constructor. Features the latest in miniature components and circuitry. Supplied with Mullard transistors and two-tone moulded cabinets in red/white or Blue/White with gold fittings. All components are supplied in packets and clearly identified. A printed circuit is used with fully illustrated building instructions. Push-pull output coupled with a sensitive and selective circuit make the "CAPRI" hard to beat. Fitted Earphone/Record socket.



- FULL AFTER SALES SERVICE AND GUARANTEE.
- ALL PARTS SOLD SEPARATELY—DETAILED LEAFLET ON REQUEST

★ DESIGNED BY EXPERTS FOR THE HOME CONSTRUCTOR ★

TOTAL COST **£7.10.0** P.P. 2/- (Battery 2/6)

"TRANSIVE" PORTABLE RADIO



Medium and Long Wave Portable
8½ x 6½ x 3½ in.

£6.19.6
P.P. 2/6

A simple to build 5-Transistor and Diode, Printed Circuit, Medium and Long Wave Portable. Features 5in. speaker, Car aerial socket, Mullard transistors and carded components. Building plans free on request. THE IDEAL PORTABLE. Full after sales service and guarantee.

"RANGER 3"

Size 4½ x 3 x 1½ in.



69/6 P.P. 1/6

A Three-Transistor Two-Diode Personal Radio for Medium Waves and Amateur top band and shipping. Quality output on personal phone. Fitted air spaced tuner, vol. control. No aerial or earth. Luxembourg guaranteed.

"CARVERTER"

MOBILE TRANSISTOR SHORT WAVE CONVERTER

As featured in the May Edition of Radio Constructor. Just plugs into the aerial socket of your car radio. Crystal controlled—covers amateur and short wave broadcast bands from 5 to 16 Mc/s.

Total cost with sprayed cabinet, etc.

69/6 P.P. 2/-

Supplied complete with long life battery and 39.40 metre band crystal. Send 1/- stamp for full Booklet. No modifications to car radio at all.

'PW' TROUBADOUR

7-Transistor Superhet

Medium and Long Wave Radio

Size
5½ x 3½ x 2 in.



£8.10.0 P.P. 2/-

('PW' SIX £7.19.6 P.P. 2/-) Modified version of previously advertised "PW" Superhet. Now with new style Two-Tone Cabinet. 1st grade components and transistors. Printed circuit. Features matched set of 7 Transistors, New 2½ inch quality speaker and new illustrated building instructions.

- PW Troubadour
- PW Mercury
- PW Regency
- PW Alpha 3
- PW Mini-amp
- PW Citizen
- P Superhet
- PW Shortwave 2
- PW Feeder Unit

All parts in stock for ALL PW Designs. Parts Lists on Request.

And the latest PW Designs.

Henry's Radio Ltd

PADDINGTON 1008 9
5 HARROW ROAD, LONDON W2
Open Monday to Sat. 9-6 Thurs. 1 o'clock
Send 1/- Stamp for Latest Illustrated Price Lists.

← PLEASE TURN PAGE

418