

DECEMBER
1962

Practical

2/-

WIRELESS

**FREE
INSIDE!**

**DOUBLE-SIDED
BLUEPRINT**

**REFLEX LOUDSPEAKER
ENCLOSURE and
208 metre PRE-SET TUNER**

**LUXEMBOURG
Tuner**




**BERKELEY
Bass Reflex
Enclosure**



Stentorian

NEW MODEL H.F. 1016 'MAJOR'

This new unit makes use of the high flux density available in the magnet system of the previous H.F.1016 unit. A curved diaphragm is used with a rigid centre section coupled to the voice coil. The rigid coupling and the design of the cone termination give a balanced response over the whole audio range. The unit is specially suitable for use in the smaller type of enclosure having a volume of approximately 1½ cubic feet.

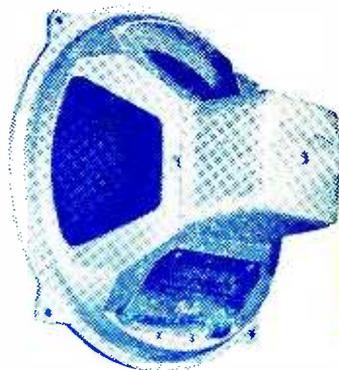

Type	Flux Density	Price	Type	Flux Density	Price
8" H.F.816*	16,000 gauss	£6.13.9	T.816	16,000 gauss	£6.6.9
8" H.F.812*	12,000 gauss	£4.1.3	T.12 tweeter	16,000 gauss	£13.4.6
8" H.F.810	10,000 gauss	£3.0.6	T.10 tweeter	14,000 gauss	£4.8.3
6" H.F.610	10,000 gauss	£2.10.3 Steel £2.12.3 diecast	T.359 tweeter	9,000 gauss	£1.14.0

Specification:

Chassis—die cast aluminium;
Cone—graded pulp cambric surround; Cone dia.—9 ins.; Pole dia.—1 in.; Flux density—16,000 gauss; Total flux—64,000 maxwells; Impedance—15 ohms.

Price: £10.0.0 (inc. tax)

* Incorporates a universal impedance speech coil.

WHITELEY ELECTRICAL RADIO CO. LTD. MANSFIELD, NOTTS
 Telephone: MANSFIELD 1762-5 London Office: 109 Kingsway, London, W.C.2
 WA3

WEYRAD

IMPROVED COMPONENTS FOR THE 6-TRANSISTOR 2-WAVE SUPERHET RECEIVER

NEW ROD AERIAL AND DRIVER TRANSFORMER FOR SIMPLER ASSEMBLY AND HIGHER PERFORMANCE

ROD AERIAL—RA2W

6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208 pF tuning capacity ... 12/6
 Car Aerial coupling Coil ... 1/-

OSCILLATOR COIL—P50/1AC

M.W. covered with 176 pF tuning capacity. L.W. by extra padder ... 5/4

I.F. TRANSFORMERS

1st and 2nd Stage—P50/2CC ... 5/7
 (2 required)
 3rd Stage—P50/3CC ... 6/-

DRIVER TRANSFORMER—LFDT4

redesigned to reduce size and improve performance. Six spills for mounting and connections 9/6

PRINTED CIRCUIT—PCA1

Size 2¾ in. x 8¼ in. Ready drilled and printed with component positions
 CONSTRUCTOR'S BOOKLET WITH FULL DETAILS AND FREE SCALE ... 2/- 9/6

TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 500 mW OUTPUT.
 MATCHING 3 OHM SPEAKER. FULLY ASSEMBLED WITH VOLUME CONTROL ... 63/6



WEYMOUTH RADIO MANUFACTURING CO., LTD.

REGENT FACTORY, SCHOOL STREET,
 WEYMOUTH, DORSET

R.S.T. VALVE MAIL ORDER SERVICES

Tel: MITcham 6202
Open Daily to Callers

All Valves Brand New and Fully Guaranteed
211a STREATHAM ROAD, MITCHAM, SURREY

Special 24 Hour Express Mail Order Service

AC2/PEN 21/-	ECC85 7/6	EY83 12/6	PCC84 8/6	TDD13C	UU9 7/6	6AK5 5/-	6P28 12/6	12SJ7 8/-
AC2/PEN DD 21/-	ECC88 12/6	EY86 7/-	PCC85 9/6	TH41 27/6	UYIN 12/6	6AK8 7/6	6Q7 9/6	12SK7 6/-
AC/TP 32/-	ECC91 3/-	EY91 3/-	PCC88 12/6	TY86F 12/6	UY21 15/6	6AL5 4/-	6Q7G 6/6	12SL7 8/-
AC/VP1-5-7 17/6	ECCF80 7/6	EZ35 6/-	PCC89 9/-	U10 9/-	UY41 7/6	6AM5 5/-	6Q7GT 8/6	12SN7 10/-
AZ1 15/-	ECCF82 8/6	EZ40 7/-	PCF82 7/-	U12 9/-	UY85 7/-	6AM6 4/-	6SA7 7/-	12SQ7 8/6
AZ31 10/-	ECH13 21/-	EZ41 7/-	PCF84 12/6	U14 9/-	VMS4B 12/6	6AO5 6/6	6SC7 8/6	14H7 10/-
B36 9/-	ECH35 10/-	EZ81 6/6	PCF82 12/6	U22 8/-	VP4 15/-	6AQ8 9/6	6SF5 10/-	14L7 10/-
CB131 21/6	ECH81 8/-	EZ90 7/-	PCF84 12/6	U24 21/-	VP4A 15/-	6AT6 6/-	6SG7 7/-	14S7 16/-
CC835 21/6	ECH83 8/6	EZ90 7/-	PCL82 9/-	U25 12/6	VP4B 15/-	6AU6 9/-	6SH7 6/-	19AQ5 8/-
CL33 15/-	ECL80 8/-	FC2 15/-	PCL83 11/6	U26 10/-	VR105/3077-	6BB8 3/-	6SJT 6/6	19BG6G 15/-
CY1 15/-	ECL81 10/-	FC2A 17/6	PCL84 10/6	U31 9/-	W61 11/-	6BA6 6/-	6SK7 5/6	20D1 10/-
CY31 15/-	ECL82 9/6	FC4 15/-	PCL85 10/6	U35 17/6	W76 5/-	6BE6 15/-	6SL7GT 6/-	20D2 21/-
D77 4/-	ECL83 10/6	FC13 17/6	PCL86 12/6	U37 17/6	W77 4/-	6BG6G 15/-	6SN7GT 5/6	20F2 17/6
DAC32 9/6	ECL86 10/6	FW4/800 9/-	PEN44 17/6	U43 8/6	W81 6/-	6BH6 6/-	6SQT 8/6	20L1 24/-
DAF91 6/6	EF6 21/-	GZ30 10/6	PEN45 10/-	U47 12/6	W81M 6/-	6B16 6/-	6U4GT 10/-	20P3 24/-
DAF96 8/-	EF22 14/-	GZ32 10/6	PEN36C 20/-	U50 7/-	X41 15/-	6BR7 12/6	6U5G 7/6	20P4 23/6
DCC90 12/6	EF37 4/-	GZ33 19/3	PEN45D 25/-	U52 4/-	X61M 10/-	6B87 12/6	6V6G 8/6	20P5 24/-
DF33 10/-	EF39 4/-	GZ34 13/6	PEN46 5/-	U54 7/6	X65 12/6	6B97 5/-	6V6GT 12/6	25A6 8/-
DF91 4/-	EF39 4/-	HAB3 19/3	PEN46 5/-	U78 4/6	X76 12/6	6BW7 5/-	6XSGT 8/6	25Y5 8/-
DF92 7/2	EF40 15/-	HAB3C8610 25/-	PEN45DD 20/-	U145 10/6	X76M 12/6	6C4 3/6	6X5GT 8/6	25Y5G 8/-
DF96 8/6	EF41 8/-	HL41 8/-	PEN45DD 20/-	U191 15/6	X78 26/6	6C5GT 8/-	6Y3 12/6	25Z4 7/6
DF97 11/6	EF42 10/-	HL41DD 8/6	PENDD4020 20/-	U251 12/6	X79 26/6	6C9 12/6	6Z6 10/6	25Z5 8/-
DH63 6/6	EF50A 3/6	HL92 8/6	PL33 13/6	U281 15/-	X81 10/-	6CD6G 27/6	6Z6 10/6	25Z6 8/6
DH77 7/6	EF50E 3/-	HL133DD 20/-	PL36 12/6	U301 22/6	Y61 10/-	6CH6 10/-	6D2 4/-	27S5 19/6
DK32 11/6	EF80 5/-	HN309 26/6	PL38 21/6	U329 12/6	Y63 10/6	6D2 4/-	6D6 5/6	30C1 9/6
DK91 7/3	EF85 5/-	IW4/350 10/-	PL81 11/6	U339 15/-	Z63 7/6	6E5 10/6	6D6 5/6	30C15 12/6
DK92 8/6	EF86 9/6	IW4/500 10/-	PL82 8/-	U403 10/-	Z66 10/-	6F1 10/6	6D8 15/6	30F5 10/6
DK96 8/6	EF89 9/6	KT35C 8/-	PL83 10/6	U404 10/-	Z77 4/-	6F1 10/6	6D8 15/6	30FL1 10/6
DL33 8/6	EF91 4/-	KT35 17/6	PL84 8/6	U801 19/9	Z152 5/-	6F6 6/9	6D8 15/6	30L1 8/6
DL35 10/6	EF92 4/-	KT55 17/6	PL83 10/6	UAB80 7/-	OA4 5/-	6F12 4/-	6D8 15/6	30L15 11/6
DL91 8/6	EF95 5/-	KT61 9/6	PL84 8/6	UAF42 8/6	IC5 10/6	6F13 10/-	6D8 15/6	30P4 20/-
DL92 6/6	EF98 10/-	KT66 15/6	PL80 18/-	UB41 7/6	ID5 8/6	6F14 10/-	6D8 15/6	30P12 10/-
DL93 7/6	EF183 10/6	KT76 10/-	PL84 8/6	UBC41 8/6	ID6 10/-	6F15 12/6	6D8 15/6	30P16 21/-
DL94 7/6	EF184 10/6	KT81 15/-	PL80 18/-	UBC81 10/-	IH5 9/6	6F19 12/6	6D8 15/6	30P19 15/-
DL96 8/6	EK32 8/6	KTW61 8/-	PM24M 13/6	UBF80 8/6	IL4 5/-	6F23 10/6	6D8 15/6	30PL3 12/6
EA50 2/-	EL2 25/-	L63 5/-	PM4 15/-	UBF89 7/6	ILN5 4/6	6F25 16/6	6D8 15/6	30PL14 16/6
EABC80 5/-	EL3 21/6	LN152 8/-	PX25 25/-	UBL21 20/-	IN5 9/6	6F26 13/6	6D8 15/6	35A5 17/6
EAC91 4/-	EL6 21/-	LN309 11/6	PY31 15/-	UCC84 10/6	IR5 7/3	6F33 5/-	6D8 15/6	35L6GT 8/6
EAF42 9/6	EL32 4/6	LZ319 12/6	PY32 12/6	UCC85 7/6	IS4 8/-	6H6 5/6	6D8 15/6	35W4 7/6
EB34 2/6	EL33 10/-	MKT4 17/6	PY80 7/6	UCH21 20/-	IS5 6/6	6IS 4/6	6D8 15/6	35Z3 16/-
EB41 5/-	EL34 15/-	MS48 17/6	PY81 7/6	UCH22 20/-	IT4 4/-	6J5G 4/6	6D8 15/6	35Z4 7/6
EB91 4/-	EL35 10/-	MV5/PEN 17/6	PY82 7/6	UCH42 9/6	2P 24/9 9/6	6J5GT 5/6	6D8 15/6	35Z5 8/6
EBC3 21/-	EL37 17/6	MVS/PENB 17/6	PY88 8/-	UCH81 10/-	3A4 5/-	6I7G 5/6	6D8 15/6	40SUA 15/-
EBC33 4/6	EL38 19/6	MU14 9/-	PY88 8/-	UCL82 10/-	3A5 10/6	6I7GT 7/6	6D8 15/6	41STH 21/-
EBC41 8/6	EL41 10/-	MX40 15/-	PY80 10/-	UCL83 13/6	3Q4 8/-	6K7 7/6	6D8 15/6	42 12/6
EBC81 10/-	EL42 10/-	N18 8/-	PZ30 15/-	UF41 7/6	3Q5 9/6	6K7G 2/-	6D8 15/6	50C5 10/-
EBF80 8/6	EL81 12/6	N37 14/-	QS95/10 10/-	UF42 7/6	354 7/6	6K7GT 7/6	6D8 15/6	50CD6G27/6
EBF83 8/6	EL84 6/9	N18 8/-	R2 10/6	UF85 7/6	3V4 7/6	6K8 9/6	6D8 15/6	50L6 8/6
EBL1 8/6	EL85 10/-	N37 14/-	RS150/15 10/-	UF86 12/6	5U4 4/-	6K8G 5/-	6D8 15/6	53KU 12/6
EBL21 21/-	EL90 8/6	N78 17/6	R2 10/6	UF89 6/6	5V4G 7/9	6K8GT 9/6	6D8 15/6	75 8/-
EBL31 21/6	EL91 4/-	N108 15/-	R3 10/6	UL41 8/-	5Y3G 7/-	6K25 18/-	6D8 15/6	78 7/6
ECC35 8/6	EL95 10/6	N308 20/-	R16 17/6	UL44 20/-	5Y3GT 8/6	6L1 10/-	6D8 15/6	80 9/6
ECC83 8/6	EM80 8/6	N339 30/-	R19 16/-	UL46 14/6	5Z4G 9/6	6L6 7/6	6D8 15/6	85 17/6
ECC84 15/-	EM81 8/6	N369 10/6	R20 16/-	UL84 7/-	5Z4GT 12/6	6L7 10/6	6D8 15/6	85A2 12/6
ECC85 5/-	EM84 9/6	OD3 5/6	R20 16/-	UL85 7/6	6A7 9/-	6L19 15/-	6D8 15/6	185BT 30/-
ECC87 5/-	EM85 10/-	OZ4 5/6	SP41 3/6	UM80 10/6	6A8G 8/6	6L34 9/6	6D8 15/6	305 13/-
ECC88 7/6	EY81 8/6	P2 10/6	SP61 3/6	URIC 15/-	6A8GT 13/6	6N7GT 9/6	6D8 15/6	807B 5/-
ECC84 8/6	EY81 8/6	PABC80 13/-	T41 15/-	U06 19/-	6AC7 6/-	6P25 10/6	6D8 15/6	807A 6/-

METAL RECTIFIERS

RM1 5/3	14RA 1-2-8-2	17/6 (FC31)	14A97 25/-
RM2 7/6	16RC 1-1-16-1	8/6	14A100 27/-
RM3 7/9	14RA 1-2-8-3	19/- (FC31)	16RD 2-2-8-1 12/-
RM4 14/-	18RA 1-1-16-1	6/6 (FC116)	16RE 2-1-8-1 8/6
RM5 19/6	18RA 1-2-8-1	11/-	18RA 1-1-8-1 4/6
14A86 17/6	18RD 2-2-8-1	15/- (FC124)	

TRANSISTOR BARGAINS

OC44 6/-	OC45 7/-	OC71 5/-
OC72 6/-	OC74 6/-	OC75 6/-
OC77 6/-	OC81 6/-	OC81D 6/-
OC82 8/-	OC82D 8/-	

SILICON RECTIFIERS

400 volts 350 mA 15/- each

TERMS OF BUSINESS C.W.O. or C.O.D.
3/2 PACKING CHARGE ON ALL C.O.D.
ORDERS. POSTAGE 6d. PER VALVE

OBsolete VALVES A SPECIALITY.
QUOTATIONS GIVEN ON ANY TYPE
NOT LISTED

SURBITON PARK RADIO LTD.

FOR POST HASTE—POST FREE SERVICE

MARTIN RECORDAKITS

The following recorders, available now in four track, are a proprietary range of machines in kit or assembled form. This enables you to take advantage of mass production techniques and prices, should you wish to assemble yourself. The components used are the finest available, with B.V.A. valves, and the decks are the latest having all the improvements B.S.R. and Collaro make from time to time, heads, etc. The amplifiers are packed in special cartons with instructions to enable anyone to build. We are confident you will find these recorders very good value, they have been built up to a standard and not down to a price.

HALF TRACK

B.S.R. TD8 Monardeck, latest model 5 1/2 in. spool	CASH	£9.90
Deposit £1.0.0 and 9 monthly		£11.00
Tape Amplifier for B.S.R. deck, printed circuit ready wired, with ECC83, ECL82, EM85 and EZ81. Complete with all plugs, sockets, panels, knobs, etc. The whole amplifier mounts onto the deck, making a self contained unit	CASH	£8.80
Deposit £1.0.0 and 8 monthly		£11.00
Case with 7 in. x 4 in. speaker, in two tone grey	CASH	£4.40
Complete Kit as above	CASH	£28.00
Deposit £2.4.0 and 12 monthly		£11.68
The above recorder can be supplied assembled, tested and complete with tape and microphone for	CASH	£25.00
Deposit £2.10.0 and 12 monthly		£21.68
Collaro Studio Deck. Very latest model 3 speeds 7 in. spools	CASH	£12.10.0
Deposit £1.5.0 and 12 monthly		£10.88
Tape Amplifier for study deck, with ready wired printed circuit control and input panels, mains and output transformers. Complete with valves, knobs, plugs, screws, etc. EF80, ECC83, EM84, EZ81, OA81 and 2 EL84, 3 watts output. Magic eye, radio and mic. inputs, EX L/S socket, tone and monitor controls. Can be used as an amplifier	CASH	£11.11.0
Deposit £1.4.0 and 12 monthly		10/-
Case for above including 9 in. x 5 in. speaker	CASH	£5.50
Total Kit as above	CASH	£28.00
Deposit £2.18.0 and 12 monthly		£23.82
We can offer the above recorder, complete with tape and microphone, in a De Luxe two tone grey cabinet, assembled for	CASH	£36.00
Deposit £3.10.0 and 12 monthly		£21.82

This Machine is listed at 39 gns. by makers and is a very good buy.
Building Instructions available at 2/6 each kit (retuned if kit bought)

QUARTER TRACK

B.S.R. TD2	CASH	£11.11.0
Deposit £1.4.0 and 12 monthly		18/-
Tape Amplifier as over, but quarter track	CASH	£9.90
Deposit £1.0.0 and 9 monthly		£11.00
Case, two tone grey, with speaker	CASH	£4.40
Complete Kit as above	CASH	£26.00
Deposit £2.10.0 and 12 monthly		£21.68
Collaro Studio Deck, 4 track	CASH	£17.17.0
Deposit £1.18.0 and 12 monthly		£13.95
Tape Amplifier, as over, but 4 track	CASH	£12.12.0
Deposit £1.7.0 and 12 monthly		£11.08
Case with 9 in. x 5 in. speaker	CASH	£5.50
Complete Kit 4 track Collaro	CASH	£34.00
Deposit £3.8.0 and 12 monthly		£21.68
Tape Pre-amplifier for Collaro deck, with power supplies, ECC83, ECL82, EZ80 and EM85. Radio and Mic. sockets, gives an equalized output of 400 m/Volts	CASH	£8.80
Half Track	CASH	£8.80
Deposit £1.0.0 and 8 monthly		£11.00
Quarter Track	CASH	£9.90
Deposit £1.0.0 and 9 monthly		£11.00
Marriott Tape Heads, 4 track type L/RP97 and L/EP9/ Record/ Playback and Erase with mounting bracket for Studio deck	CASH	£4.40
Pair Complete (Marriott list price is £9.14.0)	CASH	£4.40
Marriott 2 track type R/RP1 Record/Playback only with bracket for Studio deck. Ideal 3rd head	CASH	£1.75
Pressure pad (Studio deck only)		8/6
M.S.B. 2 track type DR1 and DR1 Record/Playback and Erase Sets only	CASH	£1.85

THE ABOVE SETS ARE BRAND NEW, OBTAINED DIRECT FROM MAKERS

JASON F.M. TUNERS

FMT1, complete with valves	CASH	£6.17.6
Deposit £1.1.0 and 6 monthly		£12.9
FMT2, complete with valves, Less Power	CASH	£7.17.6
Deposit £1.0.0 and 7 monthly		£12.8
FMT3, complete with valves. Self powered	CASH	£9.15.0
Deposit £1.0.0 and 9 monthly		£11.8
FMT5, complete with valves. Less power	CASH	£9.12.6
Deposit £1.0.0 and 9 monthly		£11.4
FMT5, complete with valves. Self powered	CASH	£12.0.0
Deposit £1.4.0 and 12 monthly		19/10
Power pack kit ready drilled chassis for FMT1, etc.		£2.12.6

The instruction books are included in all kits but are otherwise 2/6.
JTV 8, switched P.M. and TV. Sound self powered. All valves.
Deposit £1.6.0 and 12 monthly. CASH £14.15.0
£11.4.5
Mercury 2, as JTV 2 but less power, with all valves. CASH £10.15.0
Deposit £1.0.0 and 18 monthly. £11.68
The instruction book is again included but is otherwise 3/6 each.
All the above units are available ready built and aligned. Price on request.

GRAMOPHONE EQUIPMENT

B.S.R. UA 14 TCS/H cartridge	CASH	£7.15.0
Deposit £1.0.0 and 7 monthly		£12.3
Garrard Autolinn, new unit	CASH	£8.14.8
Deposit £1.0.0 and 8 monthly		£11.9
Garrard Autolinn De Luxe	CASH	£12.14.8
Deposit £1.0.0 and 12 monthly		£11.1
Philips AG1018, new transcription unit (changes on 45 rpm)	CASH	£13.10.0
Deposit £1.7.0 and 12 monthly		£12.4

REGENCY

Resistors 2/8, Controls 9/-, Condensers 15/-, Knobs 2/8, Station dial 5/8, J.B. gang 8/-, Mullard OC45 10/- each, OC72 matched pair 18/-, OA81 3/-, Battery 1/8, W/C switch 3/6, Repanco TT49, TT45, and TT46 all 5/- each, FR2 12/6, R/FC1 2/6, 7 in. x 4 in. speaker 19/6, Groupboard 1/8.		
Complete Kit, less cabinet	CASH	£6.12.6
Transistor Cabinet in two-tone grey (Vyrnall) 10 x 8 x 3 in. for 7 x 4 speaker, no control holes have been drilled. Ideal Regency, etc.		£1.12.6

TRANSISTORS

Mullard have reduced the price of many Transistors to: OC44 11/-, OC45 10/-, OCT6 8/6, OCT1 8/6, OCT2 8/-, OCT5 7/-, OCT6 7/-, OCT8 8/-, OCT8 8/- These are their new list prices. Why buy surplus. OCT2 in matched pairs only at 16/- pair (No other types.)

ARMSTRONG RADIO CHASSIS

T4B V.H.F. Tuner, self powered	CASH	£21.18.0
Deposit £2.6 and 12 monthly		£11.61
ET/3 Mk. 2 A.M./F.M. Tuner, self powered	CASH	£27.18.0
Deposit £2.10.0 and 12 monthly		£21.61
AF208 A.M./F.M. Radio Chassis, base and treble control	CASH	£22.18.0
P.U. inputs, single ended output stage		£11.79
Deposit £2.8.0 and 12 monthly		£20.12.0
Jubilee Mk. 2 A.M./F.M. Radio Chassis with push pull output	CASH	£20.12.0
Deposit £2.3.0 and 12 monthly		£21.88
Stereo 55 A.M./F.M. Radio Chassis, single ended output stage on both channels. Separate tone and volume	CASH	£32.16.0
Deposit £3.5.6 and 12 monthly		£21.45
Stereo 12 Mk. 2 A.M./F.M. Radio Chassis, push pull output at controls both channels.	CASH	£43.10.0
Deposit £4.7.0 and 12 monthly		£31.8.4

Brass dial scotchcon is available for AF208 and Jubilee. Price 7/6.
Individual leaflets giving full description and technical details.

P.W. "POCKET SUPERHET" OSMOR PRINTED CIRCUIT VERSION

Osmor rod aerial 8/6. I.F.T.s and Osc. coils 22/-, Osmor driver 8/8. Osmor output 8/-, Set transistors and diode 43/-, J.B. gang 12/6, Trimmers 1/8 each, Set condensers 15/-. Set resistors 8/-. Ardent volume control 8/-, W/C switch 3/6. Speaker 17/10. Hardware 4/-. Printed Circuit 7/6. New case and dial 12/6, Battery PP4 2/3. Leaflet giving full illustrated details 1/6. All the above components if ordered at one time. CASH £21.10.0
Osmor undertake to align this receiver for 10/-.

"WEYRAD"

Weyradio Radio 6 Transistor Superhet, using the P50 coils as they advertise in this journal. P50/IAC Osc. coil 5/4, P50/2CC 1st and 2nd I.F.T. 5/7 each, P.50/3CC 3rd I.F.T. 6/-, RA2V Rod aerial 12/6, L.F.D.T.4 driver 9/6, P.A.C.I printed circuit 9/8, Instruction Book 2/-, set resistors 7/6, Vol. control D.P. 6/-, set condensers 20/-, J.B. gang 12/6, Beehive trimmers 1/8 each, W/C switch 3/6, dial and knob 5/6, battery PP1 5/6, Battery plug 1/-, OA81 3/-. Set of Mullard transistors 53/6. Car aerial coupling coil 1/-.

35 ohm 7 in. x 4 in. speaker, Ideal for Weyrad circuit. £1.7.6
Transistor Cabinet for 7 in. x 4 in. speaker. Ideal for Weyrad circuit, two tone grey. £1.12.6

48 SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

Established over 30 Years

Telephone KIN 5549

We pay all postage and insurance.

All orders despatched same day.

Money refund guarantee.


Hours: 9 a.m.—6 p.m. (1 p.m. Wednesday)

We do not close for lunch. Open all day Saturday.

PCR COMMUNICATION RECEIVERS

Manufactured by Pye & Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of I.F. using 6 British I.O. type valves. Large 180 degrees illuminating and Calibrated Dial. Flywheel Tuning with locking device. Aerial Trimmer. Tone and Vol. Controls. Band Switch from panel jacks for speaker or Phones. In black metal case, size 17in. L x 8in. H x 10in. D. Model PCR covers 6-18 Mc/s. 200-550 metres and 850-2,000 metres and has internal 5-in. speaker. **£6.19.6.** Model PCR2 has similar L & M waveband coverage. Short wave 6-22 Mc/s, but no speaker. Used but excellent condition **£5.19.6.** Every receiver aerial tested before des. Add 10/6 carr. all models. Designed to operate from bulky EXTERNAL power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at extra cost of 2/6.

TEST METERS FOR EVERY PURPOSE & POCKET

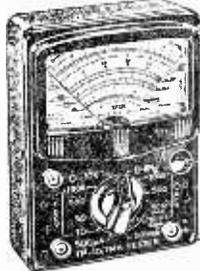

2,000 O.P.V. MODEL TP-10. Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +30; Output jack for Audio Measurements. Size 4in. x 5in. x 1 1/2in.

£3.19.6



20,000 O.P.V. MODEL TP-5S. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 o.p.v.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2in. x 5 1/2in. x 1 1/2in.

£5.19.6



30,000 O.P.V. MODEL 500. Volts to 1,000; D.C. at 30,000 O.P.V.; A.C. at 20,000; 12 Amps D.C. Current; 60 Megs Resistance; -20 to +56 Dbs; Internal buzzer short circuit warning. Size 3 1/2in. x 6 1/2in. x 2 1/2in.

£8.19.6

All New Stock, with leads, prods, and internal batteries. 6 month's guarantee backed by full service facilities. Details S.A.E.

AMERICAN AR88D RECEIVERS. Fresh release of these renowned sets. 14 valves, 6 wavebands, covering 500 Kc/s-32 Mc/s. Incorporate every possible refinement and have internal A.C. mains pack for nominal 5/230v. Thoroughly reconditioned, immaculate in appearance, and in perfect working order. **ONLY £35** (add carriage 30/- and 50/- deposit on returnable transit case).

COMBINED VIBRATOR/MAINS UNIT. The Power Pack of the Army R.107 Receiver. Has vibrator for 12 v. D.C. operation, and mains transformer for 100/250 volts A.C. Output 12.6 volts 3 A. L.T. and 250 v. at 100 mA H.T. Complete with vibrator, 6X5G rectifier, and connecting data. Ideal for driving T.C.S. or Type 52 Receivers, etc., or mobile equipment. **BRAND NEW IN MAKER'S CARTONS ONLY 45/-** (Carr. 5/6).

AMPLIFIER TYPE A1413. Ex-R.A.F. For normal A.C. Mains use. 52A Rectifications with 6V6 output. Input and output jack sockets, gain control, fully fused, 600 ohms output transformer easily changed for 3 ohms type. Standard rack mounting size 19" x 7" x 6". Used, good condition. **ONLY 59/6** (carriage etc. 10/6).


POWER UNITS TYPE 234. Primary 200/250 v. 50 cycles. Outputs of 250 v. 100 mA, and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 19" x 7". Fitted Input and Output Voltmeter, 79/6, or model less meter 59/6. (Carriage either type 10/6.)

AVOMETER MODEL 7 LEATHER CASES, fitted with carrying handle and long strap. **BRAND NEW. ONLY 32/6** (Post 2/6.)

20/- CONSTRUCTORS PARCEL. Assorted colours wiring wire, solder, resistors, condensers, volume controls, tag panel. **ALL NEW.** (Post 2/6.)

RESISTORS. 100 assorted values our choice. **NEW 10/-.** **CONDENSERS.** 100 assorted mica & silvermica. **NEW 12/6.**

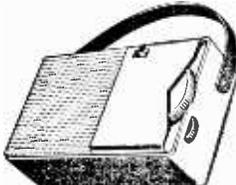"P.W. TROUBADOUR 7" TRANSISTOR PERSONAL RECEIVER




Designed by the technical staff of Practical Wireless' easy to build, using printed circuit and 1st Grade Matched Transistors and Diode. Full Medium and Long Wave coverage to internal speakers. All parts sold separately (new components only) enabling you to buy as required and full detailed price list will be sent on request. Constructional details 1/6.

TOTAL COST INCLUDING BATTERY AND CABINET £8.10.0. "P.W. 6" £7.19.6. Parts List, S.A.E.

THE "GOOD COMPANION" Mk. II
USING TRANSISTERS, THE LATEST MANUFACTURING TECHNIQUE TO SAVE ALIGNMENT DIFFICULTY
THE FINEST COMBINED PORTABLE AND CAR RADIO
YET DESIGNED FOR THE HOME CONSTRUCTOR

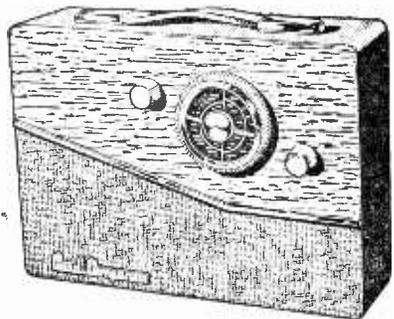- 750 m W output.
- 6 transistors and 2 diodes.
- Full Medium and Long Wave coverage.
- Quality speaker.
- Brilliantly styled 2-tone cabinet, size 11 x 6 x 3in.
- Very fine tuning with calibrated dial.



● Latest printed circuit. ● Internal high gain aerial with car aerial socket. Easy to follow construction data (available separately 3/6). All parts sold separately and full illustrated details will be sent on request.

£9.19.6.

Total Cost
 With alternative luxury cabinet using 7 x 4in. speaker, £10.19.6. Either type, plus 5/- post and ins. (Battery 3/6 extra.)


"POCKET 4" TRANSISTOR RECEIVER

Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components and case for only 42/6 (p. & p. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.



HARRIS ELECTRONICS (LONDON) LTD 138 Gray's Inn Road, London W.C.1
 Phone TERminus 7937

Please include carriage costs on all items. (Open until 1 p.m. Saturdays). We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by Bus from King's Cross.

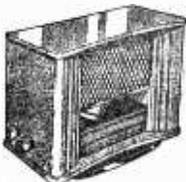

COMPLETE V.H.F./A.M. RADIO FOR £12.10.0

(carr. paid)

Brand new set, in superb walnut cabinet (size 19 x 8 1/2 x 14 1/2 in. high). Covering 80-100 Mc/s. 16-49 M. and 200-600 M. Mains trans. 200-250 v. with 2 tappings. Ferrite rod aerial for A.M. Controls: volume on/off, tone tuning, w/change. Gram and ext. speaker position provided. Valves 12AT7, 12AH8, 6BJ6, 6AB6, 6BW6 and metal rectifier. Fully guaranteed. Today's Value, £20.

TAPE TOP QUALITY BOXED. 5 1/2 in.—850ft., 15/-; 1,200ft., 17/6; 7 in.—1,200ft., 17/6; 1,800ft., 26/8 (all plus 1/6 post, 2/- for 2).

THE "CANTATA" 6-TRANSISTOR AND DIODE PORTABLE COMPLETE KIT FOR ONLY £7.19.6 (post 3/6)



500mW push-pull output. Ferrite rod aerial. Car aerial socket and coil. M.W. and L.W. full coverage. Operates on two 4.5v. cells. Printed circuit board 8 1/2 x 2 1/2 in. All holes drilled and component positions marked. Instructions 2/6 for 16 p. (retuned on purchase of kit). Size 9 x 3 1/2 x 7 1/2 in. P.M. high quality speaker. Attractive Vynair covered cabinet two tone. Two batteries 5/6 the pair (Ever Ready 126). Mullard transistors OC44, 2 x OC45, OC81D, and 2 x OC91. Top grade Weymouth Radio coils and transformers. Alignment service if required 17/6 (inc. post). Write for list of prices. All parts supplied separately. Built in two hours.

BUILD YOUR OWN RECORD PLAYER Price £12 carr. paid

Fully built 2-valve amplifier

B.S.R. 4-sp. autochanger, case 17 x 15 x 6 1/2 in. Similar cabinet for tape recorder with plain base only £8, carr. paid. Attractive colours.



or with 3-valve amplifier 15/- extra

AUTOMATIC RECORD CHANGERS—LATEST MODELS. 4 SPEED CRYSTAL CARTRIDGE. All 5/- extra carr. B.S.R. UA14. £7.10.0. Garrard Slimline, Mono £8. Stereo, £8.5.0. Motor Board for U.A.S. UA20, UA14, Slimline, 5/- (post 1/6) or 3/6 post paid when purchased with Autochanger. Motor Board for Collaro C60, 4/-. Post paid.

TELEFUNKEN STEREO AMPLIFIERS. 2 ECL82—2 x 2 1/2 watts, 12 x 9 x 2 1/2 in. piano keys, £7.0.0, post paid. Complete with power.

SELF-POWERED VHF TUNER CHASSIS
Covering 88-95 Mc/s. Mullard permeability Tuner. Dims. 10 1/2 x 4 1/2 x 5 1/2 in. high. ECC85, EF91, EF91 and 2 diodes. Metal Rectifier. Mains transformer. Fully wired and tested. Only £7.10. (carr. p.l.). Some tarnished chassis otherwise O.K., £8.10.0.

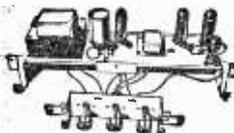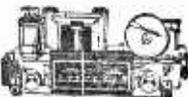Attractive Vynair Cabinet 20/-. Room dipole 12/6. Feeder. 6d. yd.



PUSH-PULL AMPLIFIER £5.5.0

(5/- Carr.)

Brand new 200-240 A.C. mains. Bass, treble and vol. controls. With valves E280, ECC83 and 2-E184 giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel." Stereo version 2 x 4 w. same price.

(Normally screwed to chassis) may be removed and used as "flying panel." Stereo version 2 x 4 w. same price.

TAPE RECORDER AMPLIFIER



Type TR3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 1 1/2 in. Height 5 1/2 in. overall. Front to back 5 1/2 in. Vol. and on/off tone. Mike radio, monitor and ext. speaker jacks. Valves ECC83, E184, E280. Mains trans. Ready to bolt to B.S.R. Deck. Complete with switch water wired. Our Price ONLY £8.2.6. (6/- Packing and Carr.). Similar model without magic eye. Type T.R.I. 3in. instead of 1 1/2 in. £5.16.0. (6/- Carr.).

Also available for Collaro Deck. State which.


Transistor Set Battery Eliminator. Converts your 6 transistor receiver to mains operation. Size 1 1/2 x 1 x 1 1/2 in. With flex lead and battery charging attachment. 15/6.

Star "Galaxy" or Garrard 9v. battery operated single 45 r.p.m. record player deck, with pick-up arm, and stylus etc. Only 50/- P. & P. 4/-.


NEW LOUDSPEAKER BARGAINS. Good Makes.

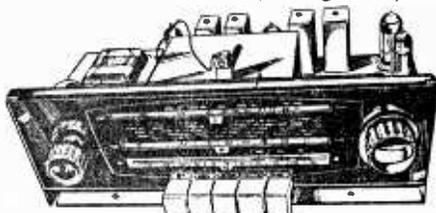2-3 ohms 13 x 8 1/2 in. 35/- (4/-); 7 x 4 in. 14/6 (2/-); 8 1/2 x 4 1/2 in. 12/6 (2/-); 10 x 6 in. 25/- (3/-); 6 in. 12/- (2/-); 4 in. tweeter 7/6 (2/-); 7 x 6 in. 17/6 (2/-); 9 x 6 in. 22/- (2/6); 8 in. circ. 18/6 (2/6); 10 in. circ. 26/- (3/-). Postal charges bracketed.

BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £14.0.0 (Carriage Paid)



A.C. ONLY. Chassis size 15 x 6 1/2 x 3 1/2 in. high. New manufacture. Dia. 1 1/4 x 4 in. in 2 colours predominantly gold. Pick-up. Ext. Speaker. Ae., E., and Dipole Sockets. Five push buttons—OFF L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1800 M.: 200-500 M.: 88-95 Mc/s. Valves E280 rect., ECC83, EF99, 6AB6, E184, ECC85. Speaker and cabinet to fit chassis (table model). 47/6 (post 4/-). 9 x 8 in. ELLIPTICAL SPEAKER, 20/- to purchasers of this chassis. TERMS: (Chassis) £5 down and 5 monthly payments of £2. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. yd. Circuit diagram 2/6.

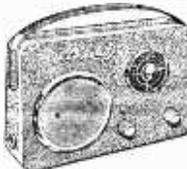

6-TRANSISTOR PORTABLE—Fully Built

The "SCALA" for only £9.17.6, carr. paid. 8 1/2 x 2 x 5 1/2 in. high. Choice of colours. Rexine. M.W. and L.W. Ferrite aerial. Battery included. Printed circuit. Nicely styled. A professional job. 3 1/2 in. speaker. Fully Tunable M.W. and L.W.

THIS SUPERB SET FOR £10

6-transistor radio covered in sponge clean Duracour fabric, in latest two tone shades. M.W. and L.W. ferrite rod, provision for car aerial. 2-colour scale. With PP9 battery giving 300 hours use. Weighs under 4 lbs. With carrying handle. 12 x 7 1/2 in. high x 4 1/2 in. at base tapering to 2 in. at top. Brand new, fully guaranteed, £10. Carr. paid. Worth £16.



SUPERIOR GRAMOPHONE AMPLIFIER

Valves UY85, UF80 and U184. Mains trans. 200-240 a.c. Covered baffle 13 1/2 x 7 1/2 in. (6 1/2 in. speaker) or 11 x 7 1/2 in. (8 x 5 in. speaker). 3 front controls, bass, treble, on-off/vol. 74/- (post 4/-) either type. Rexine cabinet to fit, with carrying handle, and lid (detachable) 14 in. or 12 x 8 1/2 x 6 in., 16/- extra.

GRAMOPHONE AMPLIFIER. With 5in. SPEAKER Baffle 12 1/2 x 6 in. ECL82 and Rectifier. Tone and Volume. On/off switch. Two knobs. Useful for Stereo, 57/- (post 4/-).

SPECIAL OFFER

Brand new tape recorder, two tone beige case, "gold" trimmings. Magic eye, monitor, ext. speaker sockets. With 5 1/2 in. tape and mike. Fully guaranteed. Price usually 19/- gas. Very high gain with low noise. Price £13 carr. paid.

COLLARO STUDIO TAPE TRANSPORTOR, 8 MOTORS, 3 SPEED. 1 1/2, 3 1/2 and 7 1/2 I.P.S. Push buttons, £10.17.8 (10/- carr.) inc. spool.

3-VALVE AMPLIFIER (inc. RECT.)

2 1/2 watts. ECC83, ECL82 and E280. Controls, volume, bass and treble. On/off switch. Mains and O.P. trans. Size as for Push-Pull Amp. Suitable for microphone input and for Guitar. 95/- P. & P. 5/-.

Also acts as telephone amplifier using pick-up coil price 14/-. Chassis 12 x 3 1/2 x 3 1/2 in. Fixed front panel. Price includes handsome walnut finish polished cabinet. 13 x 7 1/2 in. fascia containing high quality 3 ohm P.M. speaker 5 1/2 x 4 1/2 in. (20/- less without cab and speaker).

BATTERY ELIMINATOR

For 4 Low Consumption Valves (86 range). 90v. 15mA and 1.4v. 125mA, 45/- (2/6 post). 200-260v. A.C. Also for 250mA, 1.4v. and 90v. 10mA at same price.

CHASSIS BATTERY RADIO

Valves DK96, DF96, DAF96, DL96. Two Short Wavebands 16 to 49 M. and 25 to 75 M. Size 10 1/2 x 4 1/2 x 5 in. £4.18.0, carr. paid. MW and SW, £5, carr. paid. Or as Kit 75/-.

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH.


Terms Available on Items over £5. Send 6d. (stamps will do) for 20 page illustrated catalogue. Delivered by return. C.O.D. 2/- extra.

ALL ITEMS GUARANTEED 12 MONTHS VALVES 3 MONTHS

G L A D S T O N E R A D I O

"SCALA", CAMP RD., FARNBOROUGH, Hants.

(Farnborough 3871) and at 247 New Road, Copnor, Portsmouth. FARNBOROUGH CLOSED SATS.—PORTSMOUTH WEDS.

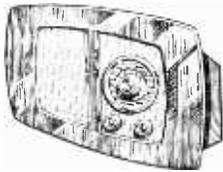


**TABLE MODEL
TRANSISTOR SET**
£9.10.0 (carr. paid)

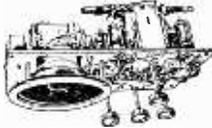6 transistors and diode, 5in. circular speaker, superb circuit. Cabinet 13 x 7½ x 4½in., battery included. Fully tunable LW and MW. Polished walnut front.

**MAINS OPERATED RADIO CHASSIS AND
AMPLIFIER OF FAMOUS MANUFACTURE**

Chassis 10 x 5½ x 4in. front to back. Valves: UBC41, UCH41, UF89, UL54 with metal rectifier. 5in. speaker. Ferrite rod aerial. Tone, vol. and grain. position. Covers L and M. waves. Limited quantity at only £8 (5/- carr.) complete with small dial. Unused and in working order.



TELEFUNKEN

German made P.M. front end, 22/6 (post 2/6), with ECC85 valve. Permeability tuned, 88-99 Mc/s. 4 x 1½ x 2in. high plus valve 2in. Circuit 2/-.

MULLARD

Permeability tuned P.M. front end 22/6 (post 2/6), with ECC85. 4 x 3 x 3½in. 88-96 Mc/s.

TRANSISTOR BABY ALARMS

Two attractive moulded units with connecting lead. Just plug the units together. FULLY BUILT, not a kit. Battery included, lasts months. Is excellent intercom. ONLY £5, carr. paid.

**BRAYHEAD "TRANSTRONIC" TRANSISTOR
CONSTRUCTION KIT**

Two Mullard transistors and diode. Seven circuits can be built inc. transmitter and receiver. 15-page instruction book. Includes all necessary components. Just the gift for a beginner. Originally over £5. Our price 42/6 (post 2/6).

**MINIATURE EARPHONES FOR TRANSISTOR
RADIOS**

3 foot cord. Miniature Jack and Socket. Crystal 8/-, magnetic 7/6.



**4 TRANSISTOR
MINIATURE PUSH-PULL
AUDIO AMPLIFIER**

For 3 ohm speaker. 200mw output suitable for intercoms. Portable radios, etc., with free instruction sheet and diagram. For mike or radio input 4 x 1½ x ¾. Printed circuit 47/6, post paid.

TRANSISTORS POST FREE

Set of 6 Mullard transistors OC44, 2-OC46, OC1D, 2-OC1 (matched) and OA70 diode 30/-; set of G.E.C. transistors 874, 2-873, 3-82 or 83, 17/6.

TEST LEAD KIT

Leads, prods, terminals clips in case, 10/-, post paid.

PANEL OF 7 POTS.

10 x 1½in.—4 x 1M and 3 x 2M. 4/- (post 1/-).



THREE-VALVE AMPLIFIER AND RECTIFIER



4 watts. Valves ECC83, EL84 and EZ80. Controls, volume, bass and treble. On/off switch. (Chassis size 6½ x 3 x 2½in.) 6½in. round or 7 x 4in. elliptical speaker. Not suitable for microphone input. A.C. only. 87/-, P. & P. 3/-.

PERSPEX

12½ x 9½ by 1½in. clear, 5/-, 16 x 14 x 3½in. clear, 7/6. Postage on one sheet 2/-, on two or more 3/-.

TRANSISTOR COMPONENTS

M.W. and L.W. ferrite rod aerial, with car coupling coil. For 203pF condenser, 8/-; One coil; 1st, 2nd and 3rd 1.F.'s, all 5/6 ea.; Driver trans., 7/6; min. 64mF 10v; 10mF 16v; 30mF 6v, all 1/6 ea.; Tuning cond. 208mF + 176pF 8/6; post 8d. on all orders.

NEW 5 WATT AMPLIFIER

By famous manufacturers made to sell at £6.10. Our price ONLY 45/- (post 4/-); a few hundred only; valves EF91 and EL84 with metal rectifier; 6 x 4 x 1½in. high (5in. over EL84). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax input.

100 RESISTORS

100 resistors 6/-; 100 condensers inc. ceramic and silver mica, 9/6.

A FEW EX-RENTAL 4-WATT AMPLIFIERS

With 10P14, U404, and 10F3 valves; used but in fair condition. 8in. speaker; useful for record player, baby alarm, general amplifier, etc., 15 x 12½ x 6½ins. Mains operated, 18/6 (6/- carr.). Some wood and some moulded cabinets.

**SPECIAL OFFER OF
RECORDER CABINET**



Plain boards, polished walnut finish. 38 x 15½ x 23in. high plus 8in. legs. Part delivery charge of £1, as offered elsewhere at over £22, brand new.

Fitted with 3 sliding doors.

PRICE £13

**"READY TO USE"
ITA CONVERTER**

Direct switching ITA to BBC, metal rectifier, co-axial plug. Can be fitted in 5-10 mins., and needs no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months' guarantee (3 months on valves). Separate gain controls. Valves ECF90 and ECU4. Switch positions OFF—ITA—BBC. Bakelite moulded cabinet. 8½ x 4 x 6in. 70/- (3/- P. & P.).



AERIALS

Combined B.B.C. (Single Dipole) and Band 3 I.T.A. (5-Element) Aerial, with chimney lashings and Stand-off Arm. Carriage paid £8.15.0.

I.T.A. (Band 3) Aerials, for clipping to existing mast of diameter 1in. to 2in. Alternatively with wall-fixing plate at same price: 3 element £13.0, 5 element £11.10.0, 8 element £2.10.0, 11 element £3.2.6. Chimney lashings and Stand-off Arm 20/- extra for each of above.

Loft Mounting I.T.A. Aerials. 3 element 20/-, 5 element 26/-. All aerial prices carriage paid. Larger aerials for I.T.A. and B.B.C. can be supplied to special order.

Double 6 Element I.T.A. Plus B.B.C. "H" Aerial with 10ft. pole and double chimney lashings, £8.10.0.

An I.T.A. Table Top Aerial with amazing performance. The Wolsey HI-Q at 19/6 (2/6 post). Good reception up to 20 miles. Cross-over unit in base with socket for B.B.C. aerial. Slightly tarnished at 12/6 (2/6 postage).

PERSPEX. 15 x 12 x 1½in. tinted blue/grey, 6/8; 12½ x 9½ x 1½in., Clear, 5/-; 16 x 14 x 3/16ins., Clear, 7/6. Postage 2/- on 1; 3/- on 2 or more; 6 post paid.

**A FANTASTIC OFFER OF EXTENSION
SPEAKERS**

Made by Goodman. Wood Cabinet 12 x 7 x 10½in. Containing 8in. P.M. 3-ohm speaker; used but good condition. Vol. control fitted. Our price 12/6 (3/6 Post).

**COMPONENTS FOR "P.W." AMPLIFIER,
GENERATOR, ETC.**

Tubular condensers 350v 0.01, 0.02, 0.05mF, 6d. ea.; 0.25 and 0.5mF, 9d. ea.; Resistors 1w 10% 6d. ea, 20% 3d. ea; Contact rectifier 250v, 50mA, 6/8; 16-16mF, 500v, 3/8; D.P.S.T. toggle switch, 3/-; High stab resistors 1/- ea; Valve holders B7G and B9a with skirt and screen, 1/- ea; Co-ax socket 1/-; 1M and 25k pots. with spindle 2/6 ea; RK2, 8K4, and 8K5 sockets 3/- ea; ditto plugs 3/- ea; add postage. Also many other items specified. B.A.E. enquiries.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS 38 CHALCOT ROAD, LONDON, N.W.1

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE

* INDICATES VALVES WITH NEW TYPE CHEMICAL CATHODE FOR EXTRA LIFE AND RELIABILITY


0A3	17/8	6BQ5	7/8	6B87	8/-	25L6GT11/8	AC/PEN/7	EAC91	4/6	EL2	9/-	ELK32	8/8	KT61	12/6	PY88	13/-	U19	48/8	Transistors
0B2	17/8	6BQ15A	15/8	6U4GT	12/6	25U4GT12/2	15/-	EAL2	9/-	EL12	19/8	KT63	7/-	PY80	13/-	PY80	13/-	U21	15/8	and diodes
0Z4	5/-	6BR7*	9/-	6V6	10/6	25Y5	10/6	AC/SO	22/8	EL34	2/6	KT66	15/-	PZ30	19/6	PZ30	19/6	U22	29/1	6D4
1A3	3/-	6BR8	15/2	6V7G	8/8	25Y5	10/6	ACSGVM	EB41	8/6	EL33	12/6	KT84	43/6	QP21	12/6	QP21	12/6	U24	29/1
1A5	3/-	6BR8*	25/-	6V8G	4/8	25Z4G	11/6	AC/PT	15/-	EB91	4/-	EL34	16/-	KT101	32/4	QP22B	12/6	U25*	17/6	G15
1A7	12/-	6BW5*	10/6	6V9GT	8/8	25Z6GT	19/6	AC/PT	32/6	EB33	5/-	EL37	22/11	KTW61	6/6	QP25	14/6	U26*	17/6	G16
1C1	6/-	6BW7*	5/-	6X4	4/8	27B8	19/6	AC/VP	15/-	EB41	8/-	EL38	25/11	KTW62	7/6	QP26	14/6	U27	11/8	G17
1C2	9/-	6BX6	5/-	6X5	5/-	27B9	19/6	AC/VP	22/8	EB41	8/-	EL41	9/-	KTZ41	8/-	RS10	15/8	U28	11/8	G18
1C3	3/8	6C4	5/-	7B6	20/8	28D7	7/-	AC/VP	22/8	EB41	8/-	EL42	10/-	L63	6/6	R10	15/8	U29	11/8	G19
1C5	12/6	6C5	6/8	7B7	8/8	30C1*	7/6	AC/VP	7/6	EB90	6/6	EL42	10/-	L63	6/6	R12	8/6	U37	25/11	G21
1C8	10/8	6C6	6/8	7B8	8/8	30C1B	13/2	AC/VP	5/-	EB90	6/6	EL42	10/-	L63	6/6	R12	8/6	U37	25/11	G21
1D5	18/2	6C8	12/6	7C6	8/8	30F5*	5/-	AC/VP	15/-	EB90	6/6	EL42	10/-	L63	6/6	R12	8/6	U37	25/11	G21
1D6	10/8	6C9	13/8	7C7	8/8	30FL1	10/-	AZ31	10/-	EBP83	13/7	EL84*	8/6	M291	12/6	R18	14/6	U45	13/6	G25
1F1	7/8	6C10	10/8	7B7	8/8	30FL12	18/2	AZ41	13/7	EBP89	9/6	EL85	13/7	MH4	7/-	R19	19/6	U50	5/6	G26
1F2	9/-	6C12	18/7	7Y4	7/8	30L1*	7/6	B36	15/-	EBL1	30/6	EL86	18/10	MHD4	12/6	R22	12/6	U50	5/6	G27
1F3	3/-	6C16G	35/8	8X3	3/8	30L1B*	9/-	CL1	12/8	EBL1	29/8	EL85	10/6	MHLD812/6				U52	4/6	G28
1F7	15/-	6CH8	7/6	8D3	3/8	30P4*	15/-	CL1	12/8	EBL1	29/8	EL85	10/6	MHLD812/6				U52	4/6	G28
1FD9	5/-	6C24W	24/-	9B5W	14/11	30P12	7/6	C1C	12/8	ECM1	13/7	EL360	17/6	M4	3/6	RK34	5/8	U54	4/6	G29
1G8	17/8	6D1	2/-	9D2	4/-	30P16	7/6	CLB1	27/2	EC2	5/6	EL220	18/2	ML6	6/6	S130	23/6	U78	4/8	G30
1H5	10/8	6D3	18/6	9D7	13/7	30P19	19/6	CB15	22/8	EC3	12/6	EL221	19/6	MS4B	22/8	SP4B	23/6	U107	16/2	G31
1H4	4/-	6D8	6/8	9D12	12/6	30FL1	9/6	CB13	22/8	EC4	9/-	EL222	19/6	MS4	20/-	SP13C	12/6	U191	16/2	G32
1LLA6	16/10	6D8	15/-	10C2	25/11	30FL13	10/8	CK50	6/6	EC5	12/6	EM4	17/8	MU12/14/1	8/4	SP42	3/8	U201	10/2	G33
1LD5	5/-	6E5	12/6	10D9	12/6	35A5	20/8	C1A	28/10	EC81	27/8	EM34	9/-	MX40	25/11			U210	16/2	G34
1LN5	5/-	6F1	25/11	10J2	11/8	35L1GT	9/6	CL33	18/8	EC90	7/6	EM5	12/6	N37	22/8	SP81	3/8	U281	19/6	G35
1N5	10/8	6F2	10/8	10J1	25/11	35V4	7/8	CV3	8/8	EC91	10/6	EM7	23/10	N78	22/8	SP82	25/27	U282	25/2	G36
1P1	7/8	6FG6	7/8	10L1	12/6	35V4	7/8	CV3	10/6	EC92	13/-	EM8	9/-	N108	22/8	SP81	8/8	U281	19/6	G35
1P10	6/-	6FG9T	8/8	10F13	12/6	35Z4GT	9/-	CV4	12/6	EC92	5/6	EM84	19/-	N108	22/8	SP2180A		U301	22/8	G37
1P11	7/8	6F8	12/6	10L13	8/8	35Z6GT	9/-	CY1	18/2	EC32	5/6	EM84	19/-	N108	20/1	T41	9/-	U389	16/2	G38
1R5	6/-	6F11	17/8	10LD11	15/7	40H8A	18/2	CY1C	18/2	EC33	8/6	EM85	16/10	N308	20/1	T41	9/-	U389	16/2	G38
1R4	9/-	6F12	3/8	10L14	18/6	41BTE25/11		D1	3/-	EC35	3/6	EN91	15/-	N389	16/10	TDD4	12/6	U404	6/6	G39
1R5	8/-	6F13	3/8	10L14	18/6	41BTE25/11		D1	3/-	EC35	3/6	EN91	15/-	N389	16/10	TDD4	12/6	U404	6/6	G39
1T2	25/11	6F14	25/11	11E1	15/8	43	22/8	D1	3/-	EC35	3/6	EN91	15/-	N389	16/10	TDD4	12/6	U404	6/6	G39
1T4	3/-	6F15	14/11	11E3	15/8	50A5	21/8	D42	10/8	EC81*	5/-	EY51	18/6	P61	9/6	TH23C	20/1	U801	29/1	G40
1U4	12/6	6F16	8/8	12A6	5/6	50C5	20/8	D63	5/-	EC82*	6/6	EY88	16/2	PAB30		TH23	25/11	U801	29/1	G40
1U5	5/8	6F18	12/6	12A8	16/6	50C9D585/7		I77	4/-	EC83*	7/6	EY84	14/6	PC95	13/2	TH33	13/2	U801	29/1	G40
1U7	10/8	6F18	12/6	12A8	16/6	50C9D585/7		I77	4/-	EC83*	7/6	EY84	14/6	PC95	13/2	TH33	13/2	U801	29/1	G40
2C26	4/-	6F19	6/8	12AD0	18/10	52KU	14/6	DAC32	10/6	EC84*	9/-	EY86*	7/6	PC84	7/8	TP25	25/2	VP2	12/6	G41
2D13C	7/8	6F23	10/8	12A6E	18/7	53K10	19/6	DAP96	7/6	EC88	18/6	EY91	7/6	PC85	7/8	TP2630	32/4	VP2B	12/6	G41
2D21	15/-	6F24	12/6	12A7H	8/8	72	4/6	DCU90	10/6	EC91	5/6	EZ40	6/6	PC89*	9/-	UAB	8/6	VP4	15/8	G42
2F	25/11	6F25	10/8	12A8H	12/6	77	8/8	DD4	12/6	EC90*	10/6	EZ41	7/6	PCF80	7/8	UAF42	9/6	VP4R	22/8	G43
2X2	25/11	6F25	10/8	12A7T*	7/8	80	6/6	DD41	13/7	EC92	10/6	EZ80	6/6	PCF82	10/6	UB41	12/6	VP13C	7/8	G44
3A4	6/-	6G6	6/8	12A6C	22/8	83	19/6	DDT4	12/6	EC96	19/6	EZ90	4/6	PCF84	16/2	UB41	12/6	VP23	6/8	G45
3A5	10/8	6H6	3/8	12A6C	22/8	83	19/6	DDT5	7/8	EC98	10/6	EZ90	4/6	PCF86	9/6	UB41	12/6	VP23	6/8	G45
3B7	12/6	6J5G	6/8	12A7U*	6/8	83V	19/6	DF33	10/6	25/11		FC4	25/11	PC12*	10/6	UHF50	9/6	VP33	22/8	G46
3D6	5/-	6J3GT	6/8	12AV6	12/6	85A1	4/6	DF6	15/-	ECH3	25/11	FC3	25/11	PC13*	9/6	UHF59	9/6	VR75	17/8	G47
3Q4	7/8	6K7	7/8	12AX7*	7/8	85A2	18/6	DF72	30/-	ECH21	22/8	FC32	25/11	PC13*	9/6	UHF59	9/6	VR75	17/8	G47
3Q9	9/8	6J7G	4/6	12BA6	6/8	90A3	6/6	DF91	5/6	ECH22	22/8	FC32	25/11	PC13*	9/6	UHF59	9/6	VR75	17/8	G47
3S4	6/-	6J7GT	4/6	12BA6E	9/6	90AV	6/6	DF96	7/6	ECH23	22/8	FC32	25/11	PC13*	9/6	UHF59	9/6	VR75	17/8	G47
3V4	7/8	6J8	12/6	12BH7	20/8	90CV	37/6	DF97	9/6	EC42	9/6	GT1C	25/1	PEN4DD		UCF50	18/2	VT501		G48
4D1	7/8	6K6	8/8	12C1	30/6	90CV	37/6	DF97	9/6	EC42	9/6	GT1C	25/1	PEN4DD		UCF50	18/2	VT501		G48
4G4Y	17/8	6K7G	7/8	12C6	3/6	90C1	16/6	DF97	9/6	EC42	9/6	GT1C	25/1	PEN4DD		UCF50	18/2	VT501		G48
5U4G	4/8	6K7GT	6/8	12C7G	8/8	150B2	12/6	DF97	9/6	EC42	9/6	GT1C	25/1	PEN4DD		UCF50	18/2	VT501		G48
5V40	10/8	6K8G	5/-	12J7GT	8/8	160C2	17/6	DF97	9/6	EC42	9/6	GT1C	25/1	PEN4DD		UCF50	18/2	VT501		G48
5Y3	5/8	6K8GT	10/8	12K5	17/8	161	10/6	DH11	45/3	EC183	13/7	GZ36	9/6	PEN25	4/6	UC42	9/6	VU11	20/8	G49
5Y4	12/6	6K25	19/6	12K7	10/6	185B7	33/4	DH10	17/7	EC186	16/2	GZ37	19/6	PEN45DD		UC41	9/6	VU133	7/6	G49
6A2	12/6	6L1	22/8	12K8CT14	12/6	185B7A22/4		DH107	13/7	EC186	16/2	GZ37	19/6	PEN45DD		UC41	9/6	VU133	7/6	G49
6Z4	9/-	6L6G	7/8	12Q7GT	8/8	191	10/6	DK40	21/10	EC186	16/2	GZ37	19/6	PEN45DD		UC41	9/6	VU133	7/6	G49
6/30L2	10/8	6L6M	10/8	12N47	8/6	302	12/6	DK40	21/10	EC186	16/2	GZ37	19/6	PEN45DD		UC41	9/6	VU133	7/6	G49
6A7	10/8	6L7G	7/8	12N7	8/6	303	10/6	DK91	6/6	EC36	4/-	H12	13/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6A8	3/8	6L18	13/8	12N7G	8/6	304	10/6	DK92	10/6	EC37A	4/-	H12	13/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6A87	8/-	6L19	22/8	12N7H	8/6	305	10/6	DK96	8/6	EC38	4/6	H13	13/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6A07	4/-	6L1D3	8/8	12N7K	8/6	306	10/6	DL33	9/6	EC39	4/6	H13	13/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6AC5	5/8	6L1D3	11/8	12N7K	8/6	307	7/8	DL33	9/6	EC39	4/6	H13	13/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6AC7	7/8	6L1D2	15/7	12N7K	11/8	4633	12/6	DL63	10/6	EC42	10/-	H14	12/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6A13	8/8	6N7GT	8/8	12N7K	8/6	4378	2/8	DL66	17/8	EC42	10/-	H14	12/6	PEN44	22/8	UL41	10/6	W109	18/2	G50
6A15	8/8	6N7G	18/8	12N7K	7/6	4758	7/6	DL68	16/-	BH1	5/-	Annov	12/8	PL38						

STERN'S MULLARD DESIGNS

Designed by MULLARD—presented by STERN'S strictly to specification

MULLARD "5-10" MAIN AMPLIFIER

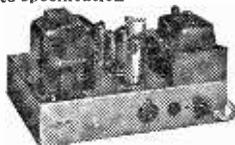For use with the MULLARD 2-valve pre-amplifier with which undistorted power output of up to 10 watts is obtained. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES, including PARMKO MAINS TRANSFORMER and choice of the latest Ultra-Linear PARMKO or the PARTRIDGE Output Transformer. COMPLETE KIT OF PARTS (PARMEKO Output Trans.) **£10.00**



MULLARD'S PREAMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves, and designed to operate with the MULLARD MAIN AMPLIFIERS, but also perfectly suitable for other makes.



KIT OF PARTS **£6.60** ASSEMBLED AND TESTED **£8.00**

- Equalisation for the latest R.I.A.A. characteristics.
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- Sensitive Microphone Channel. ● Wide range BASS and TREBLE Controls.

THE MULLARD "510/RC" AMPLIFIER

The popular complete "5-10" Incorporating Control Unit providing up to 10 watts. Specified Components and new MULLARD VALVES are supplied including PARMKO MAINS TRANSFORMERS and choice of the latest PARMKO or PARTRIDGE ULTRA-Linear Output Transformers.




KIT OF PARTS **£11.10** OR ASSEMBLED AND TESTED **£13.10**

Dep. **£2.60**, 12 months at 17/0, Dep. **£2.14.0**, 12 months at 19/10-ABOVE incorporating PARTRIDGE OUTPUT TRANS. **£1.6.0** extra.

THE MULLARD "33/RC"

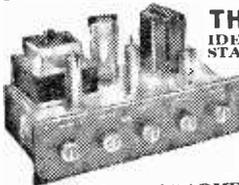IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION PROVIDING EXCELLENT REPRODUCTION OF UP TO 3 WATTS



KIT OF PARTS **£7.10** OR ASSEMBLED AND TESTED **£8.19.6**

(plus 6/6 carr. and ins.) Deposit **£2.0.0** and 8 months **£1.0.0**. Complete to MULLARD'S SPECIFICATION including Mullard valves and PARMKO OUTPUT TRANSFORMER.

valves and PARMKO OUTPUT TRANSFORMER.

with a good quality GRAM AMPLIFIER and P.M. SPEAKER ONLY **£8.7.6** (Plus 7/6 Carr & Ins.)

A 2 stage Amplifier incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS. The Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Rexline.

- WE SUPPLY SEPARATELY—
- (a) The 2-stage (Plus Rectifier) AMPLIFIER **£4.2.6**
 - (b) The PORTABLE CARRYING CASE **£3.17.6**
 - (c) 6in. P.M. SPEAKER 18/9, Carr. and Ins. 4/- extra.




"The TUDOR" AM/FM TUNING UNIT

A SELF POWERED HIGH FIDELITY TUNER OF OUTSTANDING DESIGN.

PRICE ONLY **£19.19.0** Deposit **£4.0.0** and 12 months at **£1.9.4**.

Provides full coverage of the VHF/FM band (87-108 Mc/s) and also the LONG and MEDIUM wavebands. Incorporates Multiplex outlet socket for stereophonic purposes and separate controls for tuning the FM and AM bands. Operates perfectly with the STERN-MULLARD AMPLIFIERS and contains matching FRONT PANEL in Black/Gold or White/Black. Also operates equally well with any Amplifier requiring input of 100 to 350 m/Volts.

THE "TUDOR" STEREO AMPLIFIER

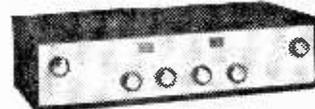

For Only **£18.18.0**

Deposit **£3.18.0**, 12 months **£1.7.8**.

A self contained Amplifier designed to provide high quality

stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts. Separate BASS and TREBLE CONTROLS. DESCRIPTIVE LEAFLET IS AVAILABLE.

MULLARD FOUR CHANNEL MIXER UNIT

Self powered with Cathode follower output. Incorporates Two inputs for MICROPHONES One for CRYSTAL PICK-UP and a fourth for RADIO or TAPE



Kit of Parts **£8.8.0** Assembled and Tested **£10.0.0**

TERMS: Deposit **£2** and 2 months at 15/- Alternatively MODEL I.L. provides for one microphone Input matched for moving coil or Ribbon Mike. **£1.17.0** extra.

STERN'S INTER-COMM BABY ALARM

Employing the new MULLARD ECL86 valve to provide two (or three) way conversation up to extreme distances. A.C. 200 to 250 Volts.



PRICES... MASTER UNIT and ONE EXTENSION

KIT OF PARTS **£6.17.6** ASSEMBLED AND TESTED **£8.8.0** Consists of a MASTER UNIT, size only 8 1/2 x 5 1/2 x 6 in. and ONE EXTENSION (a second extension may be added to any time). WE WELCOME ENQUIRIES and our technical staff will with pleasure assist with choice of suitable equipment.

PRICE REDUCTIONS

- (a) The KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-valve PRE-AMP CONTROL UNIT H.P. Dep. **£3.7.0** and 12 months at **£15.15.0**
 - (b) The "5-10" and the 2-stage PRE-AMP both ASSEMBLED and TESTED H.P. Dep. **£3.16.0** and 12 months at **£18.18.0**
- With Partridge Output Transformer **£1.8.0** extra.

RECORD PLAYERS

THE GARRARD "AUTO-SLIM" 4-speed Autochanger with Crystal Pick-up **£8.10.0**

GARRARD "AUTO-SLIM DELUXE" 4-speed Autochanger incorporates transcription Pick up Arm **£12.14.6**

COLLARO "JUNIOR" 4 SPEED SINGLE RECORD PLAY-ER with separate Crystal Pick-up. Above Pick-up separately for **£1.6.6**.

The COLLARO C60 4-speed Autochanger unit with Studio "O" Pick-up **£7.19.6**

B.S.R. MODEL UA14, A 4-speed mixer Autochanger with Crystal Pick-up **£7.19.6**

GARRARD MODEL TA/Mk.II 4-speed Player fitted high output Crystal Pick-up **£8.10.0**


PHILIPS MODEL AG1016... A 4-speed Player which can be operated both manually and automatically. Suitable for Mono or Stereo operation **£13.13.0** Carr. and Ins. on each 5/- extra.

STERN RADIO 109, FLEET ST., LONDON, E.C.4. **PREMIER RADIO 23, TOTTENHAM COURT RD., LONDON W.1.**
 TELEPHONE FLEET ST., 5913-3 LONDON, E.C.4. TELEPHONE MUSEUM 3451
 MAIL ORDERS and all POSTAL ENQUIRIES to 7-9 TUDOR PLACE, TOTTENHAM COURT RD., LONDON, W.1. MUSEUM 6128/9

Stereophonic Sound by Stern's

THE "STP-1" STEREO TAPE PRE-AMPLIFIER

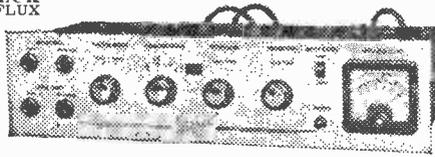- BRENELL Mk. V TAPE DECK Incorporating 1-TRACK MINIFLUX TAPE HEADS.
- PUSH PULL OSCILLATOR CIRCUIT
- 4-SPEED EQUALISATION
- FERROXUBE OSCILLATOR TRANSFORMER
- SENSITIVE METER FOR SIGNAL LEVEL
- SEPARATE GAIN CONTROLS IN EACH CHANNEL
- MULLARD VALVES



DESIGNED TO OPERATE WITH

COLLARO "STUDIO" TAPE DECK Incorporating the latest 1-TRACK TAPE HEADS.

OVERALL SIZE CASE 13 1/2 x 3in. FRONT PANEL (choice of Black or White) 14 x 3in.

PRICES INCLUDE SEPARATE POWER UNITS

Kit of **£22.0.0** Deposit **£4.8.0** 12 months of **£1.12.3**
 Assembled **£28.0.0** Deposit **£5.12.0** 12 months of **£2.1.1**

COMBINED PRICE SCHEDULE

- | | | | |
|--|----------------|---|----------------|
| (a) The BRENELL Mk. V 1-TRACK DECK with the KIT to build the STP-1..... | £61.0.0 | (a) The BRENELL Mk. V 1-TRACK DECK with the Assembled STP-1 and matched to the Deck..... | £67.0.0 |
| Deposit £12.4.0. 12 months of £4.9.6. | | Deposit £13.8.0. 12 months of £4.18.3. | |
| (b) The COLLARO "STUDIO" 1-TRACK DECK with the KIT to build the STP-1..... | £39.0.0 | (b) The COLLARO "STUDIO" 1-TRACK DECK with the STP-1 Assembled and matched to the Deck..... | £45.0.0 |
| Deposit £7.16.0. 12 months of £2.17.3. | | Deposit £2.0.0. 12 months of £2.6.0. | |

STEREOPHONIC RECORD PLAYER UNITS ARE AVAILABLE FROM STOCK

THE MULLARD "10 + 10" AMPLIFIER (described below) with the "STP-1" PRE-AMPLIFIER and one of the TAPE DECKS provide a complete STEREOGRAPHIC INSTALLATION
Details are readily available.

MULLARD'S "10 PLUS 10"

STEREO AMPLIFIER

A high fidelity design provides up to 10 watts (per channel) Superb reproduction. Frequency response flat to within 3 db from c/s. to 60 Kc/s at 50 MV Total Harmonic Distortion at 10 watts 0.1%.



- | | |
|---|-----------------|
| (a) ASSEMBLED AMPLIFIER, including CONTROL UNIT (as illustrated)..... | £21.0.0 |
| Deposit £4.4.0. 12 months at £1.10.10. | |
| (b) A complete KIT OF PARTS..... | £18.10.0 |
| Deposit £3.14.0. 12 months at £1.7.2. | |
- We supply the assembled MAIN AMPLIFIER only for operation with the DUAL CHANNEL PRE-AMPLIFIER, this provides for a more versatile installation and is essential if a low output Magnetic Pick-Up is to be used.
- | | |
|---|----------------|
| (a) THE ASSEMBLED AMPLIFIER and DUAL CHANNEL PRE-AMPLIFIER..... | £30.0.0 |
| Deposit £6.0.0. 12 months at £2.4.0. | |
| (b) A KIT OF PARTS for both Units..... | £26.0.0 |
| Deposit £5.4.0. 12 months at £1.18.2. | |
- Illustrated and Descriptive Brochure available. Please enclose S.A.E.

DUAL CHANNEL PRE-AMPLIFIER

Two Mullard 2-valve Pre-amplifiers combined into a Single unit enabling it to be used for both STEREOGRAPHIC or MONOPHONIC operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of up to 250mV/voits



KIT OF PARTS **£12.10.0** ASSEMBLED AND TESTED **£15.0.0**
 H.P. £2.10.0 & 12 mths. at 18/4. H.P. £3.0.0 & 12 mths. at £1.2.0

STEREO "TWIN THREE" AMPLIFIER

ASSEMBLED and TESTED for (Carr. & Ins., 7/6)



Based on a recent design by MULLARD LTD. Ideally suited for use in PORTABLE RECORD PLAYERS for which purpose we offer a specially designed Portable Case. Incorporates MULLARD ECL86 valves, separate BASS and TREBLE CONTROLS, and produces excellent reproduction of up to 3 watts per channel. Frequency response is 40 c/s to 30 Kc/s. Size 11 1/2 x 3 x 5in. To construct a STEREO PORTABLE RECORD PLAYER Assembled AMPLIFIER with two ROLA 8 x 5in. LOUDSPEAKERS and the PORTABLE CASE for **£14.0.0** (Carr. & Ins. 10/- extra). Deposit **£2.16.0.** 12 months of **£1.0.6.**

SUITABLE RECORD PLAYERS FROM **£8.14.0**

An alternative "TWIN THREE" can be supplied for DUAL CHANNEL MONOPHONIC operation producing output of 6 watts. PRICE AS ABOVE.

ARMSTRONG RADIOGRAM CHASSIS

FULL RANGE IN STOCK. please enclose S.A.E. for leaflets.
STEREO 12 Mk.2 £43.10.0

(ILLUSTRATED)

Deposit **£8.14.0.** 12 months at **£3.3.10.**
 Combines AM and FM Bands, a Stereo Control Unit and two High Fidelity Amplifiers in one compact unit, provides a total of 16 watts output. Other features include: inputs for tape recording, play back, pick-ups and stereo radio; separate bass and treble and balance controls.



STEREO 55 £32.15.0 Deposit **£6.15.0** 12 months at **£2.7.8**
 A junior version of the Stereo 12 Mk. 2. Ten watts output. five watts from each amplifier. Covers the VHF and Medium wavebands.

JUBILEE Mk.2 £30.12.0 Deposit **£6.4.0** 12 months at **£2.4.9**
 A Hi-Fi mono chassis giving eight watts push-pull output and covering VHF, medium and long bands. Tape Record and RC play inputs.

AF208 £22.18.0 Deposit **£4.18.0** 12 months at **£1.13.0**
 An AM/FM chassis providing 5 watts output and covering the VHF and medium wavebands. Tape Record and RC play inputs.

TVB VHF TUNER £21.18.0 Deposit **£4.14.0** 12 months at **£1.11.7**
 A self-powered high-fidelity tuner of outstanding design, incorporating features which are normally found only in the most expensive tuners. The full VHF band (87-108 M/c/s) is covered and an output control enables the output to be varied between 0 and 500 mV.

THE "MONO GRAM" AMPLIFIER



A small Amplifier of genuine high quality performance. It incorporates the new Mullard ECL86 Valve, separate BASS and TREBLE CONTROLS and when driven by the standard Crystal Pick-up a power output of 3 watts is achieved without distortion. PRICE... READY FOR USE **£4.19.6** Carr. & Ins. 5/- extra.

The MONO-GRAM is ideal for portable applications. An attractive case finished in two tone Rexine is available to accommodate the amplifier-speaker and a variety of record changers. Price **£4.0.0.** Constructors (Can Build a Really First-Class Record Player. Complete in all respects, for approx. **£14.** This will compare with known Record Players currently offered at much higher prices.

STERN RADIO PREMIER RADIO
 MAIL ORDERS and all POSTAL ENQUIRIES to

"HI-FI" LOUDSPEAKERS WE HAVE IN STOCK A COMPLETE RANGE BY GOODMANS-WILKINSON-EDWARDS-W.B. ILLUSTRATED AND PRICE LEAFLETS ON REQUEST.



BUILD A HIGH QUALITY TAPE RECORDER LIKE THIS FOR £35.0.0

FOR THIS WE SUPPLY


- ★ Complete Kit of Parts to Build the HF/TR3 Tape Amplifier.
- ★ The Latest Collaro "Studio" Tape Deck.
- ★ Rola/Celestion 10 x 6in. p.m. Loudspeaker.
- ★ Portable Carrying Case (as illustrated).
- ★ ACOS Crystal Microphone and 1,200 ft. Spool E.M.I. Tape.

CARR. and INS. 10/- extra
Deposit £7.0.0 and 12 months of £2.11.4.

ALTERNATIVELY WE SUPPLY THE COMPLETELY ASSEMBLED and GUARANTEED TAPE RECORDER FOR £39.10.0

H.P. Terms: Deposit £7.18.0 and 12 months of £2.17.11.

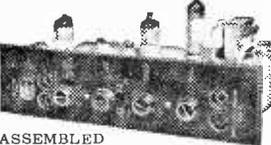HF/TR3MKII TAPE AMPLIFIER (Mullard Type "A" design)



ASSEMBLED and TESTED Deposit £3.8.0, 12 months at £1.4.11. **£17.0.0**

A very high quality Amplifier incorporating 3-speed treble equalisation, by the latest FEROCUBE POT CORE INDUCTOR, FOR COLLARO-TRUVOX-BRENNELL WEARITE Tape Decks, has GILSEN Output Transformer. Includes separate Power Supply Unit. KIT OF PARTS **£13.13.0**
Deposit £2.15.0, 12 months at £1.0.0.

SPECIAL "COMBINED ORDER" PRICES

- For Constructors with their own cabinet—WE OFFER—
- (a) KIT to build the HF/TR3 Amplifier together with the COLLARO "STUDIO" DECK **£26.0.0**
Deposit £5.4.0, 12 monthly payments of £1.18.2
 - (b) As above but with the HF/TR3 supplied ASSEMBLED and TESTED **£29.10.0**
Deposit £5.18.0, 12 monthly payments of £2.3.4
 - (c) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENNELL Mk. V TAPE DECK **£42.0.0**
Deposit £8.8.0, 12 monthly payments of £3.1.7
 - (d) As above but with HF/TR3 supplied ASSEMBLED and TESTED **£45.10.0**
Deposit £9.2.0, 12 monthly payments of £3.6.9
 - (e) THE ASSEMBLED and TESTED HF/TR3 AMPLIFIER with the WEARITE MODEL 4A DECK, incorporates Wearite Head Lift Transformer etc. Deposit £12.12.0, 12 monthly payments of £4.8.9 (Carriage and Insurance on each above is 10/- extra).



The MODEL HFG/2R PORTABLE TAPE RECORDER (Original Price £33.0.0) FOR ONLY 22 gns.

Deposit £4.14.0, 12 months £1.13.9
Crystal Microphone £1.0.0 extra. (Carr. and Ins. 10/- extra). Incorporates THE GARRARD "MAGAZINE" TAPE DECK and a HIGH QUALITY AMPLIFIER based on the very successful MULLARD TYPE "A" DESIGN and specifically developed to operate the GARRARD DECK. Price includes THE GARRARD TAPE MAGAZINE and 4in. SPOOL OF DOUBLE PLAY TAPE.

CLUDES TAPE. Comprises a Twin Track Recorder operating at 3 1/2 in./sec. speed and providing up to 1 hour 10 mins. playing time. Truly "Portable", weighs only 22 lbs.

The TRUVOX "TOUGH" With the New "SERIES 60" Recorders

Two Models are available R62. A Twin Track Recorder with speeds of 1 1/2 and 3 1/2 i.p.s.
R64. A Four Track Recorder with speeds of 3 1/2 and 7 1/2 i.p.s.
PRICE FOR EACH MODEL **£40.19.0**
Deposit £8.4.0, 12 months of £3.0.1.



They offer full MIXING, MONITORING and SUPER-IMPOSING facilities. There is an AUTOMATIC STOP, a REV. COUNTER and a storage compartment for 7 inch spools tape. DESCRIPTIVE LEAFLETS READILY AVAILABLE

109, FLEET ST., LONDON, E.C.4.
TELEPHONE FLEET ST. 5812-3
23, TOTTENHAM COURT RD., LONDON W.1.
TELEPHONE MUSEUM 3451
7-9 TUDOR PLACE, TOTTENHAM COURT RD., LONDON, W.1. TELEPHONE MUSEUM 6128/9

ADD "HI-FI" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION WITH MULLARD TYPE "C" TAPE PRE-AMPLIFIER—ERASE UNIT

The "HI-FI" link to add full tape recording facilities to High Fidelity home installations. Incorporates FEROCUBE POT CORE PUSH-PULL OSCILLATOR and 3-speed treble equalisation by FEROCUBE POT CORE INDUCTOR FOR WEARITE-COLLARO-TRUVOX OR BRENNELL TAPE DECKS. Includes separate power Supply Unit.



KIT OF PARTS **£14.0.0** Deposit £2.16.0, 12 mths. at £1.0.6
OR ASSEMBLED **£17.0.0** Deposit £3.8.0, 12 months at £1.4.11 (Excluding power unit £11.15.0 and £14.10.0 respectively.)

- a) The COLLARO "Studio" Deck with the Model "C" Preamplifier and POWER SUPPLY UNIT ASSEMBLED and TESTED **£29.10.0**
Deposit £5.18.0, 12 monthly payments of £2.3.3
- (b) As above but the Model "C" Unit and POWER UNIT supplied as COMPLETE KIT OF PARTS. Deposit £5.6.0, 12 monthly payments of £1.18.10
- (c) The BRENNELL Mk. V Deck with the Model "C" PREAMPLIFIER and POWER UNIT. ASSEMBLED and TESTED **£46.0.0**
Deposit £9.4.0 and 12 months at £3.7.8
- (d) As above but the Model "C" PREAMPLIFIER and POWER UNIT supplied as a COMPLETE KIT OF PARTS **£43.0.0**
Deposit £8.12.0, 12 monthly payments of £3.3.1
- (e) The WEARITE MODEL "4" DECK with ASSEMBLED and TESTED Model "C" PREAMPLIFIER and POWER UNIT incorporating WEARITE HEAD LIFT TRANSFORMER, Etc. Deposit £12.2.0 and 12 months at £4.8.9 (carriage and insurance on above is 10/- extra.) **£60.10.0**

THE 'ADD-A-DECK' Incorporating GARRARD TAPE DECK and MODEL HFG/2P PRE-AMPLIFIER

Supplied on ONE CHASSIS (as illustrated) READY **18 Gns.** FOR USE (Carr. & Ins. 10/- extra.) Price includes Garrard Magazine and a 4 in. Spool Double Play tape H.P. Deposit £3.16.0, and 12 months of £1.7.8. Provides complete tape recording facilities and designed to operate through the pick-up sockets of the standard type of RADIO RECEIVER, or an AMPLIFIER, from which really first class reproduction is obtained. It consists of a Twin Track Deck connected to the Pre-amplifier and operates at 3 1/2 in./sec. speed providing up to 1 hr. 10 mins. playing time.



The JEMCO MODEL MT-955 MULTIMETER



50,000 ohms per volt—D.C.
5,000 ohms A.C.
A truly efficient Meter for the amateur or professional man, having features found normally in more expensive Meters. Ranges:
D.C. volts 2.5-10-50-250-1K
A.C. 2.5-10-50-250-1K
D.C. Current 100mA-10mA-100mA-500mA. 10 amps Resistance 4 Ranges up to 20 meg.
Add D.B. 0-46 Size 7 x 5 1/2 x 3 1/2 in.
PRICE, including Full Test **£12.19.6** i/f
Lead Kit p. & p.

STEREO-MONO CRYSTAL CARTRIDGES AT GREATLY REDUCED PRICES

- RONETTE Model "OV" Output 110m/Volts **29/6**
 - RONETTE Model "105" Output 250m/Volts. **35/-**
 - RONETTE Model "105" with DIAMOND STYLUS. **39/6**
 - RONETTE Model "106" Output 500m/Volts **32/-**
 - COLLARO "CERAMIC" Output 50m/Volts **25/6**
- All above are "TURNOVER" type Cartridges.

IDEAL CHRISTMAS GIFTS!

TRANSISTOR
POCKET
RADIO

'JUNIOR MkII'

OUR IMPROVED
VERSION OF
THE 'JUNIOR 5'

NOW SUPPLIED COMPLETE WITH PRINTED CIRCUIT BOARD AND FREE GIFT OF MINIATURE EAR PIECE. An easy "first step" set for the young constructor. This miniature marvel with the BIG performance has an internal Ferrite rod aerial—5 transistors and 1 diode—separate medium and long waveband control—200 milliwatt push-pull output—2in. moving coil speaker—unbreakable plastic case with carrying handle. Complete with full instructions. Circuit diagram 1/8, free if all parts bought. All parts sold separately.

£2.19.6

P. & P. 2/-


TRANSISTOR AMPLIFIER

COMPLETE WITH
3in. MOVING
COIL SPEAKER

49/6

P. & P. 2/-

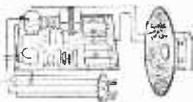1 watt full transistorised amplifier. Incorporates 2 power Transistors and 3 G.E.T. 114 Transistors in push-pull—complete with separate tone and volume controls on 2 1/2 x 4 1/2 in. printed circuit board. Operates from Ever Ready P.P.11 Battery. Suitable for use with the Staar Galaxy Player.



THE 'STAAR GALAXY'

9v. Battery Operated
Single Player

£2.14.6

Complete with P.U. P. & P. 2/6

The ideal deck for your transistorised portable Record Player. Complete with Cartridge and Stylus. Size 7 1/4 x 6 in., depth below motor 2 1/2 in. Attractive two-tone grey finish. Ideally suited for use with the above Transistor Amplifier. Specially offered together with the above Amplifier for £4.19.6. P. & P. 3/-.




SPECIAL PURCHASE!!! HUGE SELECTION OF VARIOUS TYPES OF CHASSIS—SUITABLE FOR RADIOS—RADIOGRAMS—AM/FM TUNERS ETC. ALL BRAND NEW—PRICES FROM £6. PERSONAL SHOPPERS ONLY.

Wirecomp's Finest Ever Value Offer—

THE 'REALISTIC 7'

FULLY
TRANSISTOR-
ISED PORTABLE
RECEIVER

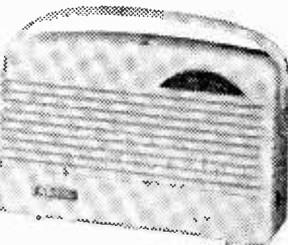

This super set—made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC44, 2 OC35's, OC71, OC81D, and 2 OC81's, plus OA70 Crystal Diode. Delivers 350 milliwatt output to 4in. high flux speaker—10 frequency 470 Kc/s—fully tunable over medium and long wave-bands. All components mounted on single printed circuit board, size 5 1/2 x 5 1/2 in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3 in. with easy to read dial and socket for car aerial; choice of Red/Grey, Blue/Grey or all Grey. Complete with full instructions. All parts sold separately.

WIRECOMP'S PRICE **£6.19.6** Including Free P.P.8 Battery — Value 3/8

P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W9

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day Saturday. Opposite Paddington General Hospital Buses 18B and 36 pass the door.

RECONDITIONED T.V. SETS

ALL MAKES ★ ALL FULLY SERVICED ★ ALL GUARANTEED ★ NOT EARLY CONVERTED MODELS.

14" from £6.0.0 to £9.0.0

3-month Guarantee on Tube and Valves.

17" from £11.10.0 to £20.0.0

12-month Guarantee on Tube, 3-month on Valves.

WE ALSO STOCK SLIM-LINES

from £23.0.0 to £33.0.0

These sets are as new.

PERSONAL COLLECTION ONLY TO ENSURE SATISFACTION.

REBUILT TV TUBES

All our TV Tubes are reprocessed to a high standard and are covered by a 12 MONTHS' GUARANTEE. Each tube is fitted with a new, top-grade electron gun, which is identical with the original, ensuring exact plug-in replacement.

21", £6. 17", £5.10.0. 12", 14" and 15", £4.10.0

* Personal collection advised, carriage by arrangement only.

£1 Refunded from the above price if you return your old tube.

PARK LANE RADIO LTD.

548 ROMFORD ROAD, MANOR PARK, E.12

Phone: ILF 6044

GZAK: This Month's Bargains

★ SHADED POLE MOTORS ★

230v. or 110v. operation. Ideal for fans, blowers or models. One only, 12/6, plus 2/- p. & p. Or pair, £1, plus 2/6 p. & p.

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telecon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

COPPER WIRE, 14 G., H/D 140ft. 17/-; 70ft. 8/6. P. & P. 2/- Other lengths pro rata.

RIBBED GLASS. 3in. aerial insulators, 1/9 each. Shell ins 2in. 9d. each. P. & P. 1/6. Up to 12.

CERAMIC FEEDER SPREADERS. 6in. type F.S. 10d. each. P. & P. 2/-

CERAMIC "T" PIECES, Type A.T. for centre of dipoles, 1/6 each. P. & P. 1/-

2 METRE BEAM 5 ELEMENT W.S. YAGI. Complete in box with 1 - 2 1/2 in. mast head bracket. PRICE 49/- P. & P. 3/6.

SUPER AERIAL CABLE. 75 ohms, 300 watts, very low loss, 1/8 per yard. P. & P. 2/- 50 ohm, 300 watt coax, very low loss, 1/9 yd. P. & P. 2/-

Absorption Wavemeters. 3.00 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham Bands, marked on scale. Complete with indicator bulb. A MUST for any Ham shack, 22/6 post free.

VARIABLE CONDENSERS. All brass with ceramic end plates and ballrace bearings, 50 pF, 5/9. 100 pF, 6/6. 160 pF, 7/6. 240 pF, 8/6, and 300 pF, 9/6. All fitted with rear extension for ganging. P. & P. 1/- Also Flexible Couplers. 1/- each. B.1. 8 MFD. 1,200 v. D.C. Wkg. Capacitors, 12/6 each. P. & P. 2/-

CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS

Dept. "P", 110 Dale End, Birmingham 4. (CEN 1635) (No C.O.D. under £1 please). (By return service)

Luxembourg is guaranteed also A.F.N., plus dozens of other Continental programmes. The Complete novice will build this set in 3 hours and it will work and its volume will astound you. This kit was specially flown to Europe by Boeing 707 jet for testing and it never failed to pick up programmes anywhere.



**ROPE IN LUXEMBOURG!
LIKE THE LIGHT PROGRAMME
WITH THE FANTASTIC TWIN WAVE BAND**

PARISIENNE!!

A SUPERB POCKET TRANSISTOR

Note:—These star items, starred because they are above any other kit available.

- ★ Elegant dial graduated long and M waves.
- ★ Built-in wave change switch not preset.
- ★ Printed circuit for easy assembly.
- ★ 5" ferrite rod aerial.
- ★ Earphone if required, 5/- extra.
- ★ Choice of colour red blue or cream.
- ★ Chrome carrying handle.
- ★ British 3" moving coil speaker.
- ★ Brand new components.
- ★ Best Mullard and Newmarket transistors.

A fully illustrated 30 page booklet, complete with step-by-step assembly instructions and all other data, comes to you for only 2/9 extra: PP4 press-stud type battery 2/3; post and packing on the lot 2/6.

SO GET WITH IT!!

and build yourself this superb little set **NOW**
PUT THE WORLD IN YOUR POCKET!

This amazing little set for home or car
HAS TO BE HEARD TO BE BELIEVED
We will supply **ALL** components at a
total cost of only
YOU CAN'T GO WRONG!

£3.19.6!!!

Second-to-none after sales service and all your components factory new, plainly marked and fully guaranteed.

Transistors: OC76 4/6, OC71 5/-, Japanese Audio 2/6, SB305 7/-, OC170 8/-, OC77 10/6, 2N398 10/-, SB240 7/6, OC42 3/6, XA701 6/-, GET 103 6/-, OA10 6/-, OA2 203 7/6, OA5 diode 5/-, OA2 202 7/6, Latest miniature diode OA90 2/-, XC141 power output as OC16, only 10/-, XA116 6/-, general purpose diodes 1/-, P.P. 4d. on each transistor. All these are new. Special quotes for quantity.

OC28 19/6, OC35 19/6, OCP71 19/6, OC200 12/6, P.P. 6d. OC72 5/-, P.P. 3d. OC44 5/6, OA47 V.H.F. or h/speed switching diode 2/6. OA86 4/-, 2N456 19/6, OC28 and OC29 19/6, CG12E diodes 2/-, SB345 6/6, SB346 7/-.

Co-ax Cable orders above 10 yds., only 6d. per yard over 20 yds. P.P. free. Diodes, set of 12 including OA90 CG84E, OA47, CG12E, only 18/-. P.P. free.

Transistor Solder Irons, 9/6, 17/6, 22/6, 29/6. P.P. on each 1/6. Money back if not satisfied.

ALL COMPONENTS SUPPLIED SEPARATELY IF REQUIRED.

THIS IS THE FINEST BARGAIN EVER OFFERED ON MAIL ORDER

A Seven Transistor. Long, Med. wave superhet, by well known manufacturer. Size only 4 x 3 x 1in. Absolutely complete and tested, less makers case but with leather cloth cover. The most compact set you have seen made like a watch. Money back guarantee. Price £5.12.6. P.P. 2/6. Personal earphones, 7/- extra.

Dynamic Mike Inserts, 2" x 1/2" x 1/2", 7/6. P.P. 6d.

Ferrite Rods, 4" x 1/2" 2/-. 5" x 1/2" 2/6, 6" x 3/4" x 2/6, 5" Slab 2/6. P.P. on all rods 6d.

TRADE ENQUIRIES WELCOMED USUAL DISCOUNT ON ANY LINES

F.T.R. 11. Tape Recorder Kit. Sub-assembled, finished in one hour. Size: 6 x 8 1/2 x 2 1/2in. Fully portable. 20 min. play. Send for illustrated leaflet. S.A.E. Kit cost £6.19.6. P.P. 3/6.



WOLVERHAMPTON RADIO & TV SUPPLIES, 42 Darlington St., Wolverhampton

Terms:—C.W.O. to avoid delay. All orders mailed by return, subject to stocks surviving the onslaught! And see us if you can. Demonstration models always at our showrooms. Fuller details and/or prices by request, write (S.A.E.) or call. Tel.: Wolverhampton 20315.

R.S.C.

Manchester Ltd.

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Suppliers, S.A.E. with all enquiries please.

BIRMINGHAM: 6 Gt. Western Arcade Opp Snow Hill Stn Half-day Wed.

SHEFFIELD: 13 Exchange St. Castle Market Bldgs. Half-day Thurs.

HULL: 51 Savile St. 73 Dale St. 8 mins. from Lime St. or Exchange Stations

LIVERPOOL: 56 Morley St. above Alhambra Theatre Half-day Wednesday

BRADFORD: 5-7 County Mecca Arcade, Briggate

MANCHESTER: 8-10 Brown St. Market St. No half-day

LEEDS: 8-10 Brown St. Market St. No half-day

SENSATIONAL STEREO OFFER (4 Gns.)

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Including pair matched 6in. speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db down. Frequency response ± 3 db, 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT 30 WATTS P.P.S.L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram. and Mike can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete Kit of chassis with fully punched parts and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with 807 output valves and 12 months guarantee, for 14 gns. TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9. Suitable microphones and speakers available at competitive prices.

11 Gns.

Carr. 10/-

WE STOCK ARMSTRONG AND JASON EQUIPMENT GOODMAN'S AND W.B. SPEAKERS

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, W.Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7in. High. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

etc. Substantial cabinet attractively covered in two tone rexine. 39 Gns. Carr. 13/-

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 x 2in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams, 39/9, or ready to use, 48/6.



Type BM2. Size 8 x 5 1/2 x 2in. Supplies 120 v. 90 v. and 60 v. 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed. They completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulators. Complete kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

TRANSISTOR RADIO CHARGER/ELIMINATOR UNITS. Ready for use, fitted "Snap On" clips. When connected to 200-250v. A.C. mains will charge 9 v. battery or replace same. PP3 Size 19/8. Larger size 29/9.

P.M. SPEAKERS. 10in. W.B. "Stentorian" 3 or 15 ohms type HF 10x10 watts, Hi-fidelity type. Recommended for use with our All Amplifier, £4.12.9. 12in. R.A. 3 ohms 10 watts (12,000 lines), 59/6. TWEETERS, Plessey 3 x 10/9, 15 Ω 25/9.

Jason FMT V.H.F./FM Radio Tuner design. Total costs of parts including valves Tuning dial, Escutcheon, etc., £6.19.9. Other Jason equipment in stock.

LINEAR L45 MINIATURE 4/5 WATT QUALITY AMPLIFIER. Suitable for any record playing unit, and most microphones. Negative feedback 12dB. Separate Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E280, ECC83, £1.84. Size only 7-5x5in. Guaranteed 12 months. Only £5.19.6. Send S.A.E. for leaflet. Terms: Deposit £2/6 and 5 monthly payments of 20/6.




230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Bluehammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

R.S.C. PORTABLE GUITAR AMPLIFIERS

(For 200-250 v. A.C. Mains)
Junior 5 watts High quality output. Separate Bass and Treble "Cut" and "Boost" controls. Sensitivity 15 m.v. Twin inputs. High Flux 8in. Loudspeaker "built-in". Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in attractive and durable polioleum, and fitted carrying handle. Terms **£8.19.6** Deposit £1 and 9 monthly payments of £1. Send S.A.E. for leaflet. Carr. 10/-

Senior 10 watts High Fidelity output Separate Bass and Treble "Cut" and "Boost" controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a high Flux 12in. for Bass notes and a 7 x 4 in. elliptical for Treble. Cabinet is well made and finished as Junior model. Size approx. 18 x 18 x 9in. Terms: Deposit £2.11.6 and nine monthly payments of 51/6. Cash £22 gns. 12/6. R.S.A. Bass-major 30 Watt, incorporating massive 12in. high flux speaker and tweeter. Two separately controlled high impedance, high gain inputs for simultaneous connection of two instruments, 39 Gns. Carr. 13/-

12in. 10 WATT HIGH QUALITY LOUD-SPEAKER

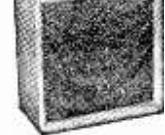

In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/-. Terms: Deposit 11/9 and 8 monthly payments of 11/3.

12in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS. Size 18 x 18 x 10 in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 8/6.

R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER


A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down 15 db. of Negative feedback is used. H.T. or 300 v. 25 mA. and L.T. or 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit or Turn-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Bluehammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

SPECIAL OFFER OF HIGH FIDELITY REPRODUCER. consisting of the very latest Alexette 8 Goodmans speaker (retailing at approx. £55.0) fitted in our Junior Bass Reflex Cabinet. Price complete £7.19.6. **R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL.** Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £5.19.6.

STANDARD MODEL. As above but for 12in. speakers. Size 20 x 15 x 13in. Especially recommended for Audiotone Loudspeaker systems, £5.19.6. Suitable legs with brass ferrules, 19/6 per set of 4.

R.S.C. CORNER CONSOLE CABINETS

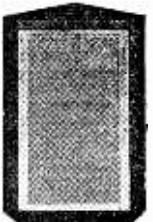Polished walnut veneer finish. Pleasing design. **JUNIOR MODEL.** Size 20 x 11 x 8in. for 8 x 6in. or 10 x 6in. speakers. £2.9.9. **STANDARD MODEL.** Size 27 x 19 x 12in. for 8 or 10in. speakers. £4.11.9. **SENIOR MODEL.** Size 30 x 20 x 13in. for 12in. Speaker. Suitable Speaker systems below Only 7 gns.



AUDIOTONE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction Standard 10 watt rating £4.19.9. Carr. 5/- or Senior 15 watt, 7 gns. Carr. 7/6.

AUDIO EQUIPMENT CABINETS. Size 36 x 15 x 19in. Beautiful walnut veneered finish. Elegant contemporary design. Robust construction. Uncut removable baseboard. Depth above baseboard 5 1/2". Only 121 gns.



AUDIOTRON HI-FI TAPE RECORDER KIT 25¹/₂

GNS. Carr. 17/6


REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR. Incorporating the latest Collaro Studio Tape Transcriber, The Audiotron High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds, High Flux P.M. Speaker, empty Tape Spool, a Reel of Best quality Tape and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome finish, size 14 1/2 x 15 x 9 1/2 in. high, and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £20-£30 class. S.A.E. for leaflets. TERMS: Deposit £2.15.9 and 12 monthly payments of 44/-. Cash price if settled in 3 months.



HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, EZ81, High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE, "LIFT" and "CUT". Frequency response to 3 D.B. 20-30,000 c/s. Six negative feedback loops. Hum. level 60 D.B. down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs. For STAN or DARD or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS, etc.

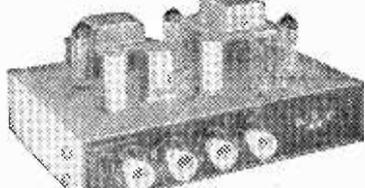

OUTPUT SOCKET with plus provides 300 v. 30 mA, and 6.3 v. 1.5 a. For supply of a RADIO FEEDER UNIT. Size approx. 12-9-7in. For A.C. mains 200-250 v. 50 c.p.s. Output for 3 and 15 ohms speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only 8 Gns. 10/- (Or factory built 51/- extra.) If required louvred metal cover with 2 carrying handles can be supplied for 18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9, and 9 monthly payments of 24/8. Send S.A.E. for illustrated leaflet detailing Ready-to-assemble Cabinets. Speaker. Microphones, etc., with cash and credit terms.

ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS

SPECIAL NOTE. The Tape Decks we supply are latest models. Where customers already have a Deck or wish to use one of those being offered cheaply we can supply Kit less Deck at 18 gns. carr. 10/- Or deposit 2 gns. and 12 monthly payments 23/9. Also if required we can supply in lieu of portable cabinet and 7 x 4in. speaker, the Equipment Cabinet illustrated at foot of opp. page and a high flux 8 1/2 x 5 1/2 in. speaker for 8 gns. extra.

HI-FI CRYSTAL PICK-UP HEADS.

(Cartridges) Acos Standard replaced by Carrard, B.S.R. and Collaro. 18/9. Acos Stereo-Monaural 49/9. Ronette Stereo-Monaural 58/6. DRAMATIC RECORDING HEADS. High Impedance Record/Playback 22/- Low Impedance Erase. 12/6.

PICK-UP ARMS. Complete and with latest Acos/hi-fi Turnover Cartridge 28/11. CRYSTAL MICROPHONES. Hand type NP110 14/9, R.T.C. 19/9, Acos Mic 40 28/9, Acos Mic 45 29/9, Stick type Acos 38-1 39/9, B33 with neck band and heavy table steel 58/9. Label type 35/9.

COLLARO JUNIOR 4-speed Single Player Unit and Crystal Pick-up with hi-fi Turnover head. Only £2.19.9.

COLLARO CONQUEST 4-SPEED AUTO-CHANGERS. Latest model. For 200-250 v. A.C. mains. £6.19.6, Carr. 5/6.

COLLARO RC 457 4-SPEED MIXER AUTO-CHANGERS. Turnover Studio pick-up. Latest model. For 200-250 v. A.C. mains. £7.18.8, Carr. 4/6.

B.S.R. UAS 4-SPEED AUTO-CHANGERS with hi-fi turnover head. £8.19.6, Carr. 4/6.

GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. A.C. mains. Size 1 1/2 x 2 1/2 x 2 1/2 in. Controls: Vol. and Tone with switch. Only 58/6.

R.S.C. TRANSISTORISED GRAM AMPLIFIER. Output 1 watt. for 16 ohm speaker. Transistors Mullard OC71, OC81D, OC81, OC81. Fitted Vol. Control with switch. Assembled and tested. Suitable for any normal crystal pick-up. Only 58/9.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts, suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "Lift" and "Cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, EZ81. Outputs for 2-3ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/-.

Kit can be assembled, ready to use. 58/6 extra.

8 Gns. 10/-

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250v., 50c/s. Guaranteed 12 months.

HEAVY DUTY CHARGER KIT 6/12 v. 6 amps. variable output. Consisting of Mains Transformer (2-200-230-250 v. P.W. (Bridge) Selenium Rectifier, Ammeter, Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit. 58/9, Carr. 4/6.

CHARGER KIT 12v. 4 AMP or 24v. 7 amp. Consisting of mains trans. 200-230-250 v. F.W. (bridge) selenium Rectifier, F. Ammeter, Fuses, Variable Resistor and Circuit. Only 6 gns. Carr. 15/-. Please state if 12v. or 24v. kit required



Assembled 4-5 amps. 6/12v.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with stoved blue hammer finished. Fused and ready for use 69/9 with mains and output leads. Carr. 5/- Terms: Deposit 13/3 and 5 monthly payments 13/3. 6/12 v. 3a., all facilities as above. Only 59/9, carr. 3/9.

69/9 Carr. 3/9

ASSEMBLED 6/12 v. 2 amps.

Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case finished attractive blue hammer blue. Fused, ready for use with mains and output leads. 49/9 Carr. 3/9

6/12v. 1 amp. 27/9 Less meter.

BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6 extra. 6v. or 12v. 1 amp. 22/9 As above, with Ammeters 23/9 6 v. 2 amps. 21/9 6v. or 12v. 2 amps. 27/9 6 v. or 12 v. 2 amps. including v. of Ammeter. 35/9 6 v. or 12 v. 4 amps. 45/9 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 52/9

CHARGER AMMETERS. 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a. a. 3/6.

SOLDERING IRONS. 230-250 v. 30 watts. First quality. For Radio work. 19/9. Spare elements and bits available.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primary 200-230-250 v. 50 c/s. Screened TOP SHROUDED DROP THROUGH 250-0-250v. 70mA, 6.3v. 2a, 0.5-6.3v. 2a 17/9 350-0-350v. 80mA, 6.3v. 2a, 5v. 2a .. 18/9 250-0-250v. 100mA, 6.3v. 2a, 6.3v. 1a .. 21/9 250-0-250v. 100mA, 6.3v. 3.5a, C.T. 19/9 250-0-250v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 25/9 300-0-300v. 130mA, 6.3v. 4a, 6.3v. 1a, for Mullard 510 Amplifier. .. 29/9 300-0-300v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 28/9 350-0-350v. 100mA, 6.3v. 4a, 5v. 3a 28/9 350-0-350v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 29/9 425-0-425v. 200mA, 6.3v. 4a, 5v. 3a .. 40/9 FULLY SHROUDED UPRIGHT 250-0-250v. 60mA, 6.3v. 2a, 0.5-6.3v. 2a .. 17/11 250-0-250v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 27/9 300-0-300v. 100mA, 6.3v. 4a, 5v. 3a 27/11 300-0-300v. 130mA, 6.3v. 4a, C.T. 6.3v. 1a, for Mullard Amplifier. .. 33/9 350-0-350v. 100mA, 6.3v. 4a, 5v. 3a 27/11 350-0-350v. 150mA, 6.3v. 4a, 5v. 3a .. 35/9

ASSEMBLED 12V. 10 Amp with variable charge rate adjustment, ammeter and strong louvred, stove enamelled case. Ready for use. Only 7 gns. Carr. 10/- or in Kit Form 5 gns.

FULLY SHROUDED (continued)- 425-0-425v. 200mA, 6.3v. 4a, C.T. 5v. 3a, 55/- 425-0-425v. 200mA, 6.3v. 4a, C.T. 6.3v. 4a C.T. 5v. 3a .. 59/9 450-0-450v. 250mA, 6.3v. 4a, C.T. 5v. 3a 68/9 (W) TOP SHROUDED MIDREK BATTERY Pentode 66 : 1 for 384, etc. 4/8 Small Pentode, 5000Ω to 3Ω .. 4/8 Small Pentode 78,000Ω to 3Ω .. 4/8 Standard Pentode 5,000Ω to 3Ω .. 5/9 Standard Pentode 7,000Ω to 3Ω, 10,000Ω to 3Ω .. 5/9 Push-Pull 8 watts, EL84, or 6V6 to 3Ω or matched to 15Ω .. 9/9 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-8 or 15Ω .. 19/9 Following types for 3 and 15Ω speakers: Push-Pull 10-12 watts 6V6 or EL84 .. 19/9 Push-Pull 15-18 watts 6V6, KT66 .. 22/9 Push-Pull Mullard 510 Ultra Linear. 25/9 Push-Pull 20 watts, sectionally wound, 6L6, KT66, EL34, etc. 49/9

MIDGET MAINS Primaries 200-250 v 50 c/s. 250 v. 60 mA, 6.3 v. 2a. 11/9 250-0-250 v. 80 mA, 6.3 v. 2a. 12/11 Both above size 2 1/2 x 2 1/2 in.


FILAMENT TRANSFORMERS All with 200-250 v. 50 c/s. primaries 6.3 v. 1.5a, 5/8; 6.3 v. 2a, 7/6; 6.3 v. 3a, 7/11; 6.3 v. 3a, 8/11; 6.3 v. 8 a. 17/6; 12 v. 1.5 a. twice, 17/6.

SMOOTHING CHOKES 150 mA, 7-10 H 250 ohms .. 11/9 100 mA, 10 H 250 ohms .. 8/9 80 mA, 10 H 350 ohms .. 5/9 60 mA, 10 H 400 ohms .. 4/11

CHARGER TRANSFORMERS All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 11 a. 12/9 0-9-15 v. 2a, 14/9 0-9-15 v. 3 a. 18/9 0-9-15 v. 5 a. 19/9 0-9-15 v. 8 a. 23/9 0-9-15 v. 8 a. 28/9.

AUTO (Step up/Step down) TRANS: 250 watts, 39/9 150 watts, 50-80 watts, 39/9

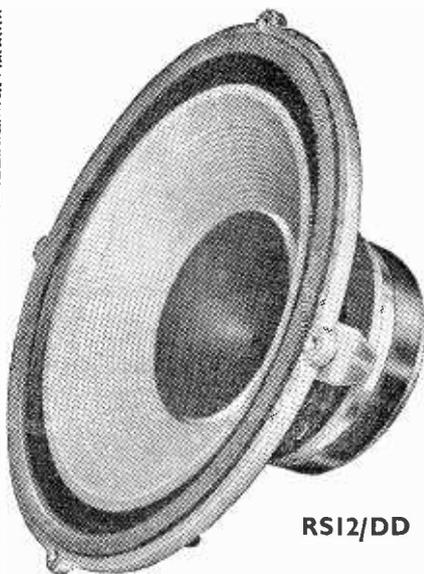MICROPHONE TRANSFORMERS 120 : 1 high grade, clamped. 6/9; 120 : 1 Potted, Mu-metal screened. 9/9.



RS12/DD

A 12" SPEAKER for the HOME CONSTRUCTOR

A fine 12" Speaker employing a new type of double diaphragm and magnet assembly, the RS12/DD has been designed with the home constructor in mind—it is one of the few 12" models suitable for use in compact enclosures enabling a really high quality system to be assembled at a modest price.

Some important features of the RS12/DD—

- Very low bass resonance
- Synthetic Centring Device
- Ceramic Magnet
- Die-cast Chassis
- Foam edge Damping
- One-piece HF Flare Dome
- Airtight impregnated Roll Surround

£11.10.0 TAX FREE

Wharfedale
WIRELESS WORKS LTD

Complete the coupon for technical specification of the RS12/DD including Constructional details of suitable cabinets.

Post to Wharfedale Wireless Works Ltd.,
Idle, Bradford, Yorkshire

NAME

ADDRESS

PW

ASK FOR

OSMOR

Transistor

Coils

TRANSFORMERS

3 IFS & Osc. 22/- set
Driver & Output 16/3 pair

OSMOR 418 Brighton Road,
South Croydon

Amateur or Professional

it pays to have qualifications. Let us tell you what Britain's oldest and most successful radio correspondence school can do for you. We will tell you the facts. No follow-up letters, no high-pressure salesmanship, no callers.

Write for details, today, to:

Mr. J. SYKES

(M.I.E.E., M.Brit.I.R.E., M.I.N.)

Principal:

BRITISH NATIONAL RADIO SCHOOL
Red Lion Court, Stalbridge, Dorset.

Britain's premier Radio Correspondence School
specialising in City and Guilds examinations.

TELESCOPIC AERIAL SNIPS!

Exclusive purchase of entire range. Finest finish—sturdy construction. Three sizes and types available. Limited supply. Ideal for all types of Transistor Radios and Kits, Crystal Sets, Transmitter Receivers, Remote Control Units, Signal Injectors and probes.

T.A.1. Size 31 7/14" Nickel finish 3/6 each
T.A.2. Size 31 7/38" Nickel finish 6/6 each
T.A.3. Size 31 7/31" Chrome finish 9/- each

Plus. P. & P. 9d. each.

MINIATURE COMPONENTS

As previously advertised


P.31 Standard jack plug ..	2/6 ea.
P.5.35 Sub-miniature plug and socket ..	2/6 pr.
CB.25 "Tiny" plug and socket ..	2/6 pr.
CH.305 Chrome miniature plug and socket ..	3/6 pr.
CR.6 Crystal earpiece ..	8/- ea.
MR.4 Magnetic earpiece ..	6/- ea.
LM.179 Crystal lapel microphone ..	14/- ea.
SS.219 Standard slide switch. D.P. D.T. ..	2/6 ea.
T.104 S.P. S.T. Toggle switch ..	2/6 ea.
SS.3271 Miniature slide switch ..	2/6 ea.

Please add P. & P. on above items

SIMPLE TO BUILD FUN TO OWN!!

A 5 STAGE TRANSISTOR RADIO

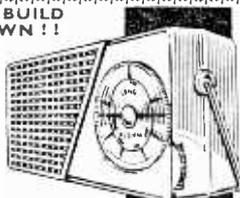which can be built in one hour and will give you endless amount of pleasure. Completely portable has the appearance of sets costing considerably more and works equally well. Attractive case 5 1/4" x 3 1/4" x 1 1/4", genuine 2 1/2in. speaker and G.E.C. transistors, tuning condenser, volume control with switch, etc. All parts sold separately.



ONLY 37/6 P. & P. 2/6.

SPECIAL TWO WAVE BAND HI-FI RADIO OFFER!!

This radio normally sells at anything between 10-15 gns. Offered to our regular customers only at a special price of **ONLY £6.19.6**. P.P. 3/6. High fidelity reproduction in any area due to complete long and medium wave reception. A truly remarkable radio for those who want the best without spending the most. Seven stage superhet circuit with built in ferrite aerial. Complete with earphone, battery, leather case in presentation box. Remember this set has **FULL MEDIUM and LONG WAVE BANDS.**



8" DOUBLE CONE HI-FI SPEAKER

Model 8A7. Frequency range 50-16,000 c/s. Lowest resonance 60 + 15 c/s. Sensitivity 98db. Programme source input 8 watts. Voice coil impedance 16 ohms. Nett weight 970 grammes. **BRAND NEW AND GUARANTEED. 92/6.**

SF-39 RADIO EARPHONES. Hi-impedance 2,000 ohms-general use headset. Black and Ivory plastic cased electro-magnetic units with adjustable headband for comfortable fit. Individual listening for all types of applications. Individually packed, with flexible cord attached, 14/6, post paid.



Signal Injection Probe Model ITI-1. Injects a signal into the circuit at any point given.



Produces a signal rich in harmonics from a built in miniature transistor oscillator.

later. Push button operation, and neon battery strength indicator. Ideal for making rapid checks on radios, amplifiers, T.V. Tuners etc. A must for the amateur, hobbyist and service man. **PRICE 42/6.** Complete with batteries.

VERNIER DIAL Model T.501



A precision vernier dial with approx. 8 to 1 ratio. Surface mounting. Accurately centred metal insert for fin. shaft. Reads counter clockwise 0-100 in 180°. 1 1/2in. diameter dial. 13/16in. front to back 14/-, Post Paid.

A "MUST" for every transistor set owner! Over 25,000 already sold. Rush your order NOW.



9V BATTERY CHARGER AND A.C. ELIMINATOR

MODEL 29/6 P. & P. 1/6. L.A.6P

Save those batteries by running your transistor set direct from A.C. Mains. Reactivate all your old 9V batteries. Unit contains neon indicator and standard battery connections with nearly 2 yards of mains lead and plug. Also snap cord for connection to set.

A MINIATURE TAPE RECORDER IN KIT FORM

Consisting of three transistor amplifiers, recordplay, volume control, miniature speaker, forward-stop-rewind-switch, reel of tape and spare reel, motor, attractive coloured case, Mic. and earphone sockets, pick-up coil, mike, earphone and carrying handle supplied. Standard battery operated. Simple to put together in less than one hour. Brand new and guaranteed.

ONLY £6.19.6

A guaranteed saving of at least 24! Results comparable with similar built-up recorders selling at around 12 gns.



TAPE SPLICER & CUTTER. Model T.635

Cuts 2 rounded indentations in the tape splice leaving the edges of the tape which contact parts of the recorder entirely free of adhesive. As little as 1in. tape need be removed. Complete with instructions. 18/9. Post paid.



THE MOST USEFUL AMPLIFIER EVER PRODUCED!

4 TRANSISTOR PUSH-PULL AMPLIFIER

MODEL PK.548

Ideal for making powerful Transistor Radios, Tape Recorders, Baby Alarms, Record Player, Intercom, etc., must be heard to be appreciated.

NOT A KIT

READY BUILT UNIT

ONLY 52/6 P. & P. 1/6

FINAL OFFER!!! WIRELESS SET No. 19



This most famous Army Trans/Receiver covers 2-8 Mc/s. (150-37 metres in two bands and 230-240 Mc/s V.H.F.). Has an intercom. amplifier. Designed for 12 and 24 volt operation. Uses a 6 valve superhet receiver, I.F. being 465 Kc/s. and a 6 valve transmitter designed for voice and C.W. operation. Incorporates test and tuning meter for voltages, aerial loading and current tests. Panel Controls: Frequency tuning, P.A. tuning, Gain control, MCW, CW, R/T switch, Het-tone netting, Off-on, Quench, aerial AVC LT-HT—Drive tests. Supplied complete with valves and instruction book.


ONLY 65/- Carriage 10/-

FEW ONLY LEFT Don't be disappointed—Order Now

MAIL ORDERS TO (DEPT. P.), 32a COPTIC STREET, LONDON, W.1



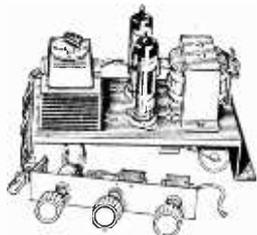CALLERS WELCOME AT 87 TOTTENHAM COURT ROAD, LONDON, W.1. MUS 9606



SPECIAL OFFER!

6 Watt Push-Pull Amplifier

2 ECL82 metal rec., separate bass and treble cont. on aux. panel. Made for one of the largest manufacturers of record players. Used in 30 gn. unit. Size 7 x 4in. panel, 6 x 1 1/2in. 3 ohm output, trans. included.


Our Price **£4.9.6** Post 4/-

TAPE DECKS

B.S.R. Monardeck
(Single speed) 3 1/2in. per sec., simple control, uses 5 1/2in. spools, £6.15.0, plus 5/6 carr. and ins. (Tapes extra.)

COLLARO STUDIO DECK
£10.10.0, plus 5/6 carr. and ins. (Tapes extra.)

10/14 WATT HI-FI AMPLIFIER

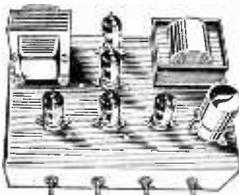

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded ultra output transformer (to match 3-15 speaker) and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6. (Free with parts.)

All parts sold separately.

ONLY **£6.19.6** P. & P. 6/6.

LOUDSPEAKERS

All 3 ohm impedance.

2 1/2in.	12/6
5in.	12/6
6 1/2in.	15/-
12in.	27/6
Goodmans 5in. tweeter	10/6
E.M.I. 2 1/2in. tweeter	10/6
Goodmans 8in. x 5in. middle register speaker	10/6
E.M.I. 13 1/2in. x 8 1/2in. high flux	32/6
Rola Celestion, approx. 9in. x 6in., middle register speaker	10/6

P. & P. 1/6 per Speaker.


TRANSISTORS

All Post Free.

	GET15 (Matched Pair), 15/-		
OC72	6/-	OC71	5/-
OC76	6/-	PXA101	6/6
		XA103	6/6
		V15/10p	12/6

Set of Mullard 6 transistors 25/-; Set of G.E.C. 1,874; 2,873; 3, S1 or GET114 20/-.

AMPLIFIER ON PRINTED CIRCUIT BOARD

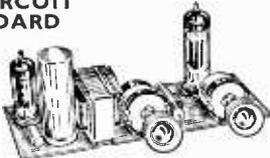

Two valve. UY85, UL84 with O.P. trans., use with 80 volt tap off motor. 39/6.


P.P. 2/6 on above. Dropper res. for filaments if required, 2/6.

B.S.R. AUTO UNITS

160 v. Suitable for use with above. (Slightly soiled.) £5.5.0. P. & P. 5/-.

LARGE CABINET

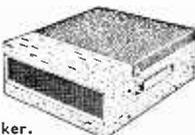Suitable for above two items. Complete with 3 ohm speaker. £3.9.6. Carr. 5/-.



Superior Cabinet. Similar to above to take 8 x 5in. speaker, with motor board, will accommodate B5R UA14 or UA16. £3.9.6. Carr. 5/6. Speaker 15/- extra. P. & P. 1/6 extra.

WODEN TRANSFORMERS

(Ex equip.). 200-240 v. input. Output 12 v. 1 amp., tapped 1, 8 and 10 v. Ideal for model railways and chargers. 8/6, P.P. 2/-.

Colvern Wire Wound Potentiometers. 3in. 10 ohm 1 amp. Suitable for above. 5/-, P. & P. 1/-.

LARGE WODEN MAINS TRANSFORMER

220/240 v. input. Output 40 v. at 3 amps, tapped 30 and 35 v. H.T. voltages 300 v., 100 mA. tapped 10 v., 150 v., 230 v., 260 v., also 90 v., 100 mA., 350 v., tapped at 200 v., 100 mA. Size 4 1/2 x 5 x 5in. Weight approx. 12 lb. 20/- each, P. & P. 5/-.

6 TRANSISTOR AND DIODE SUPERHET

A first class 2 waveband transistor superhet in kit form. ● Printed circuit panel (size 8 1/2 x 2 1/2in.) ● 3 pre-aligned. I.F. transformers. ● High-gain Ferrite rod aerial. ● First-grade G.E.C. transistors. ● Car aerial winding. ● Push-pull output. ● All parts down to the minutest item with simple instructions. All parts sold separately.

ONLY **£4.5.0** P. & P. 2/6

2 1/2in. 35 ohm speaker, 10/6; 3 1/2in. 35 ohms speaker 16/6; 35 ohm 5in. P.M. 18/6; 7 x 4in. 35 ohms speaker 21/-, P. & P. 1/6 per speaker.




PORTABLE CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2in. Suitable for above using 3 1/2in. speaker. 25/-, P. & P. 2/-.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (med., long and aerial coupling), 28/6 complete, post 1/-, 6 transistor printed circuit, board to match, 8/6, post 9d. Circuit diagram 1/6 extra.

HARVERSON'S F.M. TUNER MARK I

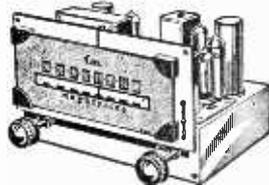

● F.M. tuning head by famous maker. ● Guaranteed non-drift. ● Permeability tuning. ● Frequency coverage 88-100 mc/s. ● OAB1 balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3in. glass). ● Self powered, using a good quality mains transformer and valve rectifier. ● Valves used ECC85, two EF80s, and EZ80 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 5 1/2in. ● All parts sold separately. £5.19.6, plus 8/6 P.P. and ins. Circuit diagram and illustrations 1/6 P. free.

Mark II Version as above but complete with magic eye, front panel and brackets. £6.12.6. P. & P. 8/6.

Mark III Version as Mark I but with output stage (ECL82) and tone control. £7.7.0. P. & P. 8/6.


Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I. 25/- P. & P. 2/6. To fit Mark II. 17/6. P. & P. 2/6.

HARVERSON SURPLUS CO. LTD.

RECORD PLAYER AMPLIFIER

- ★ 2 watt output.
- ★ Ready built with valves and 6 $\frac{1}{2}$ in. speaker, tone and volume controls. Mounted on panel 13 x 7 $\frac{1}{2}$ x 7 $\frac{1}{4}$. P. & P. 2/-.

STEREO AMPLIFIER Bargain Offer

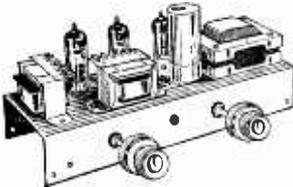

- ★ 4 watts per channel.
 - ★ Full tone and volume controls.
 - ★ Complete with sockets, etc.
- 89/6** P. & P. 2/6.

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. This amplifier (which is used in a 29gn. record player) employs ECC83, EL84, EZ80 valves. Bass, treble and volume. On/off controls.

PRICE **69/6** P. & P. 3/6.

DITTO. Mounted on board with output transformer and 6 $\frac{1}{2}$ in. speaker. Complete at **89/6** P. & P. 4/6.

4-SPEED PLAYER UNIT BARGAINS

SINGLE PLAYERS
B.S.R TU/12, £3.15.0. Carr. 3/6


AUTO CHANGERS
B.S.R. UA14, £6.19.6. Latest B.S.R. UA16, £7.19.6. Latest Garrard "Auto-Slim," £7.15.0. Carr. 5/- on each.

LOUDSPEAKER SILKS 5 $\frac{1}{2}$ in. wide

Heavily woven in ivory and gold. Originally 35/- per yard length. OUR SPECIAL PRICE 13/6 per yard length. P. & P. 1/6. Also Red Rexine, Dark Grey and Oatmeal fabrics for cabinet covering, 5 $\frac{1}{2}$ in. wide, 13/6 per yard length. P. & P. 1/6.

SEND STAMP FOR OUR SURPLUS VALVE LIST.

RADIOGRAM CHASSIS

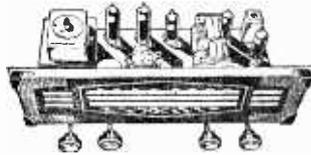


A chassis of distinction, by a famous maker. Covering Long, Med. and Short Waves, plus gram position. (Size 15 $\frac{1}{2}$ x 7 x 6 $\frac{1}{2}$ in. high). Incorporates the latest circuitry, using fully delayed A.V.C., and negative feedback. Controls: Tone, Vol. On/Off, W/Change (L.M.S. and Gram), Tuning. Tapped input 200-250 v. A.C. only. An attractive brown and gold illuminated dial with matching knobs, make this one of the most handsome in addition to being one of the best performing chassis yet offered. Complete with valves (ECH81, EF89, EBC81, EL84, EZ81), knobs, output transformer, leads, etc. OUR PRICE ONLY **£9.19.6**

PLUS 8/6 post and packing.

ALSO AVAILABLE: 6 valve, 3 waveband, F.M. M.W., L.W.; ECC85, ECH31, EF89, EABC80, EL84, EZ80, £11.11.0. P. & P. 8/6. Deluxe version also with F.M., S.W., M.W., L.W. and piano-key wavechange. same line up, £13.13.0. P. & P. 8/6.

6 TRANSISTOR AND TWO DIODES RECEIVER

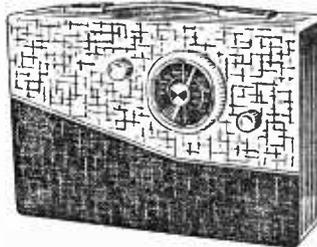Easy to build, using 6 super transistors and 2 diodes 750 M/W output, full medium and long wave coverage, printed circuit, 5in. speaker, prealigned IFTS & OSC. Very fine tuning, ferrite aerial with car aerial socket, attractive 2-colour cabinet. Simple to follow instructions with circuit, everything complete.



£8.19.6 P. & P. 3/6 Battery 3/6 All parts sold separately.

BARGAIN OFFER!

TELEFUNKEN HI-FI STEREO AMPLIFIER
110/250 v. A.C. input. 5 watt undistorted output (10 watts nominal). Size 12 x 9 x 2in. Weight 9 lb. Complete with spec. and instructions.



£5.19.6 Carr. 5/-.

Also Model S32. Similar specification but with balance control. **£6.19.6**. Carr. 5/-.

SPECIAL OFFERS!

GAULER F.M. TUNER HEADS. 10.7 Mc/s. I.F., 15/-, plus 1/9 P. & P. (ECC85 valve 8/6 extra).

ELECTROSTATIC H.F. TWEETERS. Type L.S.H. 75. Size 3 x 3in., 2/6 each, plus 9d. P. & P.

MIDGET 2 GANG CONDENSERS. Capacity 195 and 100 PF. Polystyrene case with built in trimmers. Size $\frac{3}{4}$ x $\frac{3}{4}$ x $\frac{1}{2}$ in. Not used but removed from P/C Boards. 2 for 9/-, Plus 1/- P. & P.

ACOS CRYSTAL MIKES. Hi-imp., 18/6. P. & P. 1/6.


4 MFD MANSBRIDGE PAPER CONDENSERS. Ideal for Crossover Units. 4/6 each. P. & P. 1/-.

TRANSISTOR DRIVER and O/P TRANSFORMERS. (Tapped 3 ohms and 15 ohm o/p), plus 4 suitable Transistors giving approx. 1 watt o/p. 30/-, P. & P. 2/-.

MAINS TRANSFORMERS
Tapped Primary, $\frac{1}{2}$ wave or Bridge Rectifier. Secondary 250 v. at 75 m/a 6.3 volts at 2 amps. 7/6 each. P. & P. 3/-.

3 PUSH-BUTTON TRANSISTOR SWITCH. D.P.—D.T. Each Switch 5/6 and 11/- P. & P.

F.M. TUNER HEAD

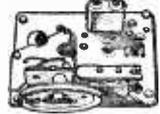

A permeability tuned tuner head by a famous maker, supplied without valve (ECC85) and drum and spindle, 18/6, plus 1/9 P. & P. Valve 8/6 extra. Drum and spindle 3/6 extra.

E.M.I. 4-speed Player and P.U.



Heavy 8 $\frac{1}{2}$ in. metal turntable. Low flutter performance 200/250V shaded motor with tap at 80V for amplifier valve filament if required. Turnover LP/78 head. PRICE 79/6 Plus 4/6 P. & P.

SPECIAL PURCHASE!



E.M.I. 4-speed. 9 v. battery operated Record Player Unit. Mounted on unit plate. Complete with turnover head and sapphire stylus. **69/6** P. & P. 3/6.

WE STOCK GOOD COMPANION AND MARTIN RECORDER KITS.

170, HIGH STREET, MERTON, S.W.19

CHE 3985/6

Open all day Saturday.

Early Closing Wed., 1 p.m.

A few minutes from South Wimbledon Tube Station.


Electronics Ltd

152-153 Fleet St., London, E.C.4. Tel. Flc 2833

Business Hours: Weekdays, 9-6, Saturdays 9-1

Stockists for
**AMPLIFIERS, V.H.F. TUNERS, HI-FI SPEAKERS BY
ALL THE LEADING MANUFACTURERS**

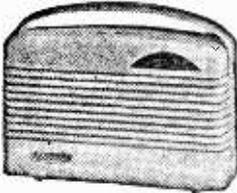SOMETHING TO SHOUT ABOUT THE SET YOU HAVE BEEN WAITING FOR THE REALISTIC SEVEN



The finest receiver at present available for home construction, a set that will give results. Fully tunable long and medium wavebands, using 7 Mullard transistors, OC44, 2-OC45, OC71, OC81D and 2-OC81s, plus OA70 crystal dode. 350 milliwatt output, 4in. high flux speaker, printed circuit board size 5 1/2 x 5 1/2in. Neat plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2in. In choice of colours: red/grey, blue/grey, all

grey. Easy to read dial! External sockets, for car aerial, all coils, IPTs and aerial fully wound ready for immediate assembly. Full comprehensive data and circuit supplied with each receiver. Operates from PP9 or equivalent battery. Price for the complete parcel including transistors, cabinet, speaker, etc. Post and packing 4/6. Battery 3/9. Supplied free with complete parcel. Easy to follow data and instructions 2/6, refunded if parcel is purchased. Parcel supplied on approval. Your money refunded by return post PROVIDING COMPONENTS ARE COMPLETE AND NOT SOLDERED. All parts supplied separately.

£6.19.6



MULTI TEST METER MODEL U1

- Complete with test leads.
- Brand new, fully guaranteed. Sensitivity: 1,000 ohms per volt A.C. and D.C.
- Ranges (A.C. and D.C.): 0-15-50-250-500-1,000 v. D.C. current 0-100-500 mA.

(used at 0-10 v. range).

Resistance: 1-2,000 ohms (centre 24 ohms).
100-200,000 ohms (centre 2.4 k.).
Size: 5in. x 3in. x 2 1/2in.

OUR PRICE **39/6**
Carriage and Packing 5/-.



High Quality Tape Recorder Motor

Polylly shrouded heavy duty. Suitable for capstan or take-up 200/250 v. A.C. only. 50 cycles 1,500 r.p.m. 4 pole single phase with switch.

Complete only **19/11**
P. & P. 3/6.

Special Offer!

TV Remote Control Unit
By well known manufacturer, on/off, brightness and volume controls. In smart grey plastic box with 15 feet of multi 7 way screened cable.
(grey.) Listed at £2/2/-.

Special Price **14/11**
Post 1/6.

HUGE PURCHASE CRYSTAL PICK-UP CARTRIDGES. LOWEST PRICES EVER. Some are less than half list price.

ALL COMPLETE WITH STYL L.P. & STANDARD (AND/OR STEREO WHERE SHOWN). FULLY GUARANTEED STANDARD FITTING. WILL FIT MOST P.U. ARMS AND HEADS. Postage 1/- each extra.

TYPE C.T.1. By well known manufacturer. With 2 sapphire styl. **£2/6**

Garrard GC.2	15/-	Acos GP.65/1	17/-
Ronette Studio O	15/-	Acos GP.67/1	17/-
Acos GP.65/3	15/-	Acos GP.61/1	13/-

STEREO

Acostereo 73/1.	With 2 sapphires 25/-.
Acostereo 73/2.	With Diamond L.P./Stereo and sapphire Std. 29/6.
Collaro type C.	Turnover with 2 sapphires 25/6.
Collell S.C.1	Turnover, with 2 sapphires 24/6.
Collell S.C.1.	Turnover, with Diamond L.P./Stereo and sapphire Std. 28/6.
Ronette Stereo O.V.	Turnover 28/6.
Ronette Stereo type 105	35/6.
Ronette Stereo type 106,	with Diamond L.P./Stereo and sapphire Std. 38/6.
Ronette Stereo type 106	38/-
Ronette Stereo type 106	with Diamond L.P./Stereo and sapphire Std. 37/6.

TECHNICAL TRAINING in radio television and electronics

Whether you plan to have your own business, to become an electronics engineer, to take up a career in industry, or to brush-up your knowledge and study new developments, transistors, etc., an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

EXAMINATION COURSES FOR:-

C. & G. Radio

and

TV Servicing Certificate

(R.T.E.B.)

C. & G. Radio Amateurs' Exam.

(Amateurs' Transmitting Licence)

P.M.G. Certificates in Radiotelegraphy

British Institution of Radio Engineers, etc. C. & G. Telecom. Technician's Cert.

LEARN AS YOU BUILD

Practical Radio Servicing Course

A basic course in radio electronic and electrical theory backed by thorough practical training. You build radio receivers, signal generator and multimeter.



Post this Coupon TODAY! for FREE book on careers in Radio, and full details of other I.C.S. Courses

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171), Intertext House, Parkgate Road, London, S.W.11.

Please send book on _____

Name _____ Age _____
(Block Letters Please)

Address _____

Occupation _____ 12.62

INTERNATIONAL CORRESPONDENCE SCHOOLS

Pullin Thermostat



This is a wall mounting Thermostat intended for the control of room heating up to 3 KW (A.C.) Scale calibrated from 30°-90°F. with neon lamp for on/off indication. Price 27/6, plus 1/6 Post and Ins.

15 Amp Thermostat

You can make yourself a thermostat similar to the above using a "Sunvic" unit which we can offer at 9/6. This is adjustable over the same range as the Pullin and will control the same amount of heating. We can also offer a crackle finished calibrated case which can be used for containing the Sunvic. Price two items together 14/6, plus 1/- Postage.

Ice-Stat

This is a small thermostat which cuts on and off at around freezing point. Has many uses, one of which could be an ice warning device to be fitted under your motor car. Price 7/6, Post 1/-.

Morganite Po tentimeters

Single and 2-gang types available standard size with good length spindle, all new and boxed. Single types, 1/- each, values available: 5K, 10K, 25K, 50K, 100K, 250K, 1 meg., 2 meg. Gauge type 3/- each—values available: 5K±5K, 100K±100K ± meg. ± meg. 2 meg. ± 2 meg.

Component Storage Drawers



Stout board construction, these drawers are ideal for small parts. Supplied complete with simple erection instructions—1/6 each or 12 drawers each 6 x 2 1/2 x 6 1/2 in., 13/6, post 2/-.

Hi Fi Speakers

E.M.I. Ceramic magnet 12,000 lines, size 13 x 8 in. (roughly equivalent to 12 in. round speaker). Handles up to 10 watts. Price 33/6, plus 5/- carriage and insurance. State whether 15 ohm or 8 ohm. Similar model but specially designed and hand made for very low frequencies (40 to 55 cycles). Price £7.10.0.


Miniature Transistor Sets

Cheaper than you can possibly make them, we are able to offer these made up, ready to work, complete with leather carrying case and earphone. Astra 7 uses 7 transistors, covers 535-1065 kc/s, sensitivity 300 micro volts/M, output 150 mW, ferrite slab aerial. Size approximately 4 1/2 x 2 1/2 x 1 1/2 in. Price £6.19.6. Post & Ins. 3/-. Zephyr 6, very similar specification to the above but only 6 transistors. Price £5.19.6 with leather case and earphone plus Post & Ins. 3/-.



The 'Good Companion' Mk. II using Transfilters

In the 'de-luxe' cabinet as illustrated it costs £10.19.6 to build—but What a set! Scan these pages: you will find nothing to compare with its specification. It uses transfilters instead of I.F. transformers, has variable feedback as well as all the usual features. A.V.C., Push-pull output, Ferrite Aerial, Slow Motion Tuning, etc., etc., and is a very powerful Medium & Long Wave set, conservatively rated at 750mW. Every component used is by a famous maker, such as American Philco MADT R.F. transistors—Mullard A.F. transistors—Jackson Brothers' tuning condensers—Rola-Creston loudspeakers—Dubilier—T.C.C.—Morganite resistors and controls. Also full after sales service available. You will definitely be doing the right thing if you buy a Good Companion.

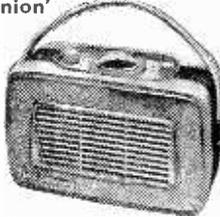

"A jolly fine set but deserving a better case"



This is a comment which many constructors have voiced and therefore we now offer a de-luxe version of the Pocket Companion. This uses a solid hide case of very pleasant red with gold lettering and our Pocket Companion now has the 15 guinea look.

The most up-to-date Superhet portable of its type, it uses a transfilter in conjunction with Philco R.F. transistors and Mullard output transistors. Complete building costs with plastic case £6.15s. or with solid hide cast, £7.15s. If you have already built and want to change your case, then return the plastic case with a postal order for £1 or if you wish to retain the plastic case then send 26/-, plus 1/6 Post and Ins. for the hide case only.

Infra-Red Heaters

Make up one of these latest type heaters ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and instructions 15/6, plus 2/6 post and insurance.



Battery Charger Bargain

Components Would Cost More Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 5 amps, and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250. A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.




LIMITED QUANTITY ONLY!

Waterproof heater wire. 16 yds. length. 70 watts. Self regulating temperature control. 10/-. Post Free.

THIS MONTH'S SNIP !!

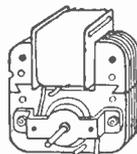Silent running mains motor by very famous maker. Ideal for gramophone, tape recorder, fan, etc., etc. 200-250 volts, A.C., shaded pul start. Size approximately 2 1/2 x 2 1/2 x 1 1/2 in. 2,750 r.p.m. Spindle diameter 5/32 in. Spindle length 1 in. Brand new guarantee. Price 12/6, plus 1/- post.



"Starlux 208"

Solderless '3' TRANSISTOR. Ideal for home and holidays as no Aerial or Earth required. Enjoy assembling and performance. Our solderless Terminals ensure perfect connections using first grade Transistors and all parts incl. Earpiece for private listening. Will receive Luxembourg (the station of the stars) and other stations on both Medium and Long waves. Penlight Battery operated, 37/6. Post and insurance, 2/6.



Building A 'Scope?



3 in. oscilloscope tube. American made type No. 3FP7, 6.3 v. 0.6 amp. heater, electrostatic deflection, brand new and guaranteed with circuit diagram of scope. 15/- each, plus 2/6 post and insurance.

Tape Recorders



One of the easiest ways to learn anything, is to "tape" it and then keep playing it back. The industrious Japanese have really gone to town on tape recorders

this year and many bargains are on offer. It is the writer's opinion that there is bound to be a big demand for them as Christmas presents so there is a good reason why you should buy your tape recorder immediately. Prices range as follows:
Child's Model £4.19.6
Assemble yourself Model £6.19.6
Model No. H11-3 £7.15.0
The "Treasurer" £8.19.6
The "Pocket Secretary" £14.14.0
The first two are not really good enough for music but they are quite good for speech. The last three are reasonable also for music. All have a value out of all proportion to their cost. Try this new learning technique—you will be amazed.


"Dipyt" Automatic Headlamp Dimmer



A transistorised device for automatically dipping headlamps so leaving the driver's hands and feet free for emergency, could easily avoid an accident. We now offer such a device ready made and tested. The unit measures 5 x 2 x 5 in. and fits under the dash, it is very easy to wire into the circuit and can also be used to control side lamps for parking. Price of unit is £10.19.6. Car and Diagram and instructions free with unit or separate 2/6. (Agents wanted.)

Fluorescent Light Bargain

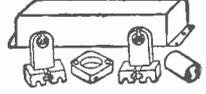
Kit of parts comprising: choke, two lamp holders, starter holder and starter, 40 watt, 19 1/8 x 8 0 watt, 23/6. Plus 2/- post and insurance





Convactor Heater

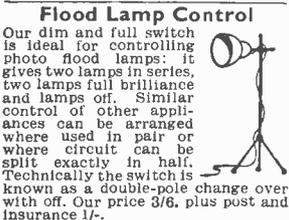Just screw it together. Uses 1250 watt copper clad element which gives off black heat. Will last a lifetime. Ideal for bedroom, it's so safe. Complete in crackle finished case. £3.19.6, easily worth double. Carriage and Insurance, 6/6.




Flood Lamp Control

Our dim and full switch is ideal for controlling photo flood lamps: it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pair or where circuit can be split exactly in half. Technically the switch is known as a double-pole change over with off. Our price 3/6, plus post and insurance 1/-.



Lens System for T.V. Camera

The above illustrated binoculars originally part of the "see in the dark" equipment contain many lenses, and two complete systems suitable for closed circuit TV cameras may be made from each (with the aid of our simple instructions). The binoculars are new and they also contain 2 infra-red cells, but these are sold without guarantee. Offered at a really bargain price of £2.17.6, plus 5/- carr. and ins.

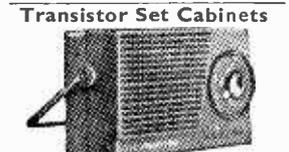


Transistor Set Cabinets

Very modern cream cabinet, size 5 1/2 x 3 x 1 1/2 in. with chrome handle, tuning knob and scale. Price 7/6, plus 1/6 postage and packing. Special quotations for quantities.



Miniature Microphone

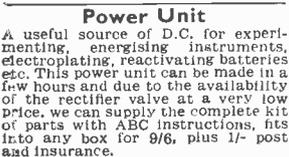American made. Dynamic type, real bargain at 2/6, plus 6d. postage.



Power Unit

A useful source of D.C. for experimenting, energising instruments, electroplating, reactivating batteries etc. This power unit can be made in a few hours and due to the availability of the rectifier valve at a very low price, we can supply the complete kit of parts with ABC instructions, fits into any box for 9/6, plus 1/- post and insurance.



Cabinet & Pick-up

Made for a famous Company intending to make a Battery Record Player but changed their minds. This is an extremely fine looking cabinet, must have cost at least £2 to make. It is complete with handle and fasteners as illustrated. Also included in the parcel is a Cosmo-cord pick-up with crystal cartridge and sapphire stylus. Both items new and perfect. Price 19/6, plus 4/6 Post & Ins.

DO YOU EVER FORGET?



This Pocket Secretary could eliminate the trouble (often embarrassment) your forgetfulness causes you—she will stay in your jacket pocket and as fast as you can think she will capture and store—ideas notes—formulae—appointments—anything you can say or sing! then at your demand she will play them all back to you.

Undoubtedly one of the smallest precision tape recorders made. Entirely controlled by push buttons, you can record at d play back with the instrument in your pocket. It is a full function machine using standard 1/4" tape and easy to replace batteries. Speaking and playing back is from the same (crystal) microphone.

Specifications: Dimensions: 6 1/2 x 2 1/2 x 1 1/2, weight: 14 oz. recording time: 12 mins. rewinding time 4 mins. recording system: D.C. Bias, erasing system: Magnetic erasing, wow and flutter: within 2%, and frequency response: 500-1,200 c/s (within—6db).

Price £14.14.0. Complete ready to work.

Bargain for Service Engineers

You often come up against the old set that won't be parted with. For these we can offer bargain parcel of rectifiers MU12 replacement and 1D5 replacement. Ex-government of course, six of each for £1. post paid.

Parcel of Mica Condensers

50 all very useful values. Total list price over £5. Yours for 5/-, plus 1/6.

Simmerstat Heater Regulator

A device for controlling the quantity of heat delivered from an element, boiling ring, heater, soldering iron (anything up to 2,500 watts). Completely adjustable from zero to max. Normally these are 55/- each. Special snip price 15/- each. Plus 1/6 post and insurance.

Zener Diodes

Latest invention for voltage control and stabilisation. Complete with circuit diagram 7/6.


MULTI-METER BARGAINS!

MODEL IT1/2 (illus. on right). 20,000 ohms per volt, 20 ranges comprising A.C. volts, 5 ranges up to 1,000; D.C. volts, 6 ranges up to 2.5KV; C.C. current, 3 ranges up to 26 ohms; resistance, 2 ranges up to 6 meg.; capacity 2 ranges up to 0.1; decibels—20 to +22. Scale cornerwise to the equivalent of 4 in. movement is a pocket size instrument measuring 4 1/2 x 3 1/2 x 1 in. Complete with test prods, battery and operating instructions, price £5.5.0, post free.

MODEL EPI0K. Similar in size and appearance to IT1/2 except that this is 10,000 ohms per volt and maximum D.C. volts 1,200 instead of 2.5K, also no capacity range. Price £5.19.6. Post free.



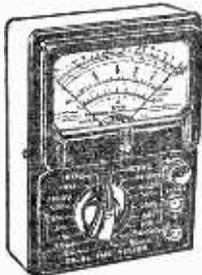ALL METERS BRAND NEW AND FULLY GUARANTEED



MODEL TP55. (illus. on left). 20,000 ohms per volt; D.C. volts, 5 ranges up to 1,000; A.C. volts, 5 ranges up to 1,000; resistance, 2 ranges up to 10 meg.; capacity 2 ranges up to 0.1; decibels—20 to +26. One-switch control, really beautifully made precision instrument, size only 3 1/2 x 5 1/2 x 1 1/2 in., price only £5.19.6. Post free.

MODEL TP10. Similar in size and appearance to TP55, but sensitivity 2,000 ohms per volt, price £3.19.6. Post free.

MODEL U1. A robust instrument of 1,000 ohms per volt sensitivity. A.C./D.C. volts up to 1,000, D.C. current up to 500, resistance up to 200K, size 5 1/2 x 3 1/2 x 2 1/2 ins. complete with test prods, single switch control, large easily-read scale, price only £2.19.6. Post free.

ELECTRONIC PRECISION EQUIPMENT LTD.

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road, Eastbourne, marked Department 7. Callers may use any one of the Companies below.

286 London Road, Croydon. Phone: CRO 6558 Half day Wednesday


29 Stroud Green Rd., Finsbury Park, N. Phone: ARChway 1049 Half day Thursday

520 High Street North Manor Park, E.12. Phone: ILFord 1011 Half day Thursday

42-46 Windmill Hill, Rushlin, Middx. Phone: RUISlip 5780 Half day Wednesday


246 High Street, Harlesden, N.W.10. Phone: ELGar 4444 Half day Thursday

ARMSTRONG AF208AM/PM RADIOGRAM CHASSIS

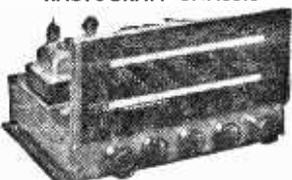

★ Full VHF Band (87-108 Mc/s) and Medium Band, 187-570M ★ 7 Valves ★ 5 Watts Output
★ 15db Negative Feedback ★ Separate wide range Bass and Treble Controls ★ 2 Compensated Pick-up Inputs ★ Frequency Response 30-22,000 c.p.s. ±2db ★ Tape Record and Playback Facilities ★ Continental Reception of Good Programme Value ★ For 3, 7½ and 15 ohm speakers. Send S.A.E. for leaflet.

PRICE £22.18.0 Carr. Free

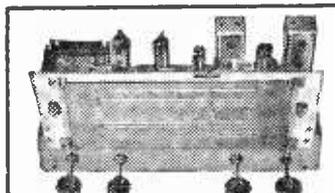

1962 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES
S.W. 16 m.—50. LATEST MULLARD
M.W.200 m.—550 m. ECH18, EP89, EICW1,
L.W. 800 m.—2,000 m.
12-month guarantee.
A.C. 200/250 v. 4-way switch; short-Medium,
Long-gram. A.V.C. and Negative feedback,
3 ohm output, 6 watts. Chassis 13 1/2 x 2 1/2 in.
Glass dial, horizontal or vertical wording, size
10in. x 4 1/2 in. Aligned and calibrated. Isolated
Chassis.

£9.10.0 Carr. & Ins. 4/6.

BARGAIN SALE PRICES

New Boxed VALVES 90-day Guarantee


024	5/-	6K7G	5/-	EAB08	8/-	PCL82	10/-
1R5	6/-	6K8G	5/-	EB91	4/-	PCL84	10/-
1R5	8/-	6L6G	8/-	EB41	8/-	PL181	10/-
1T4	3/-	6N7M	6/-	EB93	8/-	PL85	8/-
6X3	2/-	6X7G	6/-	EBF80	9/-	P130	7/-
3K4	7/-	6SN7	6/-	ECH142	9/-	PY81	5/-
3V4	7/-	6V6G	6/-	ECH81	9/-	PY82	7/-
3Q5	7/-	6X4	5/-	EP85	6/-	PY83	8/-
3Q4	6/-	8X5	6/-	EP89	8/-	QJ25	7/-
6Y3	6/-	12A7T	6/-	EL32	5/-	8F41	3/-
6Z4	9/-	12A7U	6/-	EL34	7/-	8F61	3/-
6AC7	4/-	12AX7	7/-	EY51	9/-	U22	7/-
6AM6	4/-	12BH7	7/-	EY86	9/-	UBC41	8/-
6AT6	6/-	12K7	7/-	EZ40	7/-	UBC81	9/-
6BA6	7/-	12K8	14/-	EZ90	7/-	UBF89	8/-
6BE6	6/-	12Q7	6/-	EZ91	7/-	UC181	9/-
6BW6	7/-	20Y6G	6/-	E1148	1/-	UC182	10/-
6C4	6/-	35L6	9/-	HABC8010	1/-	UC88	12/-
6D9	5/-	35Z4	9/-	HVR2A	5/-	UF89	8/-
6G6	4/-	807	5/-	KT33C	8/-	UL41	8/-
6H6	3/-	85A	2/-	KT78	8/-	UY41	8/-
6J5	5/-	DA P96	8/-	MU14	7/-	UY85	7/-
6J7	6/-	DF99	8/-	PCC84	8/-	UIU9	7/-
6J9	6/-	DK96	8/-	PCP80	8/-	VR150	7/-
6K6	8/-	DL96	8/-	PCF82	8/-	W81	6/-

L.F. TRANSFORMERS 7/6 pair
465 K/s Sigs Tuning Miniature Can, 2 x 1 x 1 in.
High Q and good bandwidth. Data sheets.

NEW ELECTROLYTIC TUBULAR		FAMOUS MARK'S CAN TYPES	
1/350V	2/-	50/350V	5/8
2/350V	2/8	100/25V	3/-
4/450V	2/8	200/25V	3/-
8/450V	2/8	500/6V	3/-
16/450V	3/-	32 + 32/350V	6/-
32/450V	3/8	32 + 32/450V	6/-
26/225V	1/8	32 + 32 + 32/350V	7/-
50/225V	2/-	16 + 16/450V	4/8
50/50V	2/-	100 + 200/350V	11/8
		100 + 200/275V	12/8

COMPLETE RADIO CHASSIS £5.19.6. post free

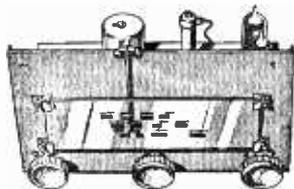4 Mullard valves, 5in. speaker. Superb Circuit. BRAND NEW. Size 9 x 6 x 5 1/2 in. high. Tested by us ready for use. 200/250 v. A.C.-D.C. Mains.



DE LUXE MODEL as illustrated with illuminated dial. Fully tunable over Medium and Long Wave. 12-month Guarantee.

MAINS TRANSFORMERS 200/250 v. A.C.
Postage 2/- each transformer.

STANDARD, 250-0-250, 80 mA, 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. 22/8, ditto, 350-0-350 .. 28/6

MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 15/8

MIDGET, 220 v. 45 mA, 6.3 v. 2 a. .. 15/8

SMALL, 220-0-220, 50 mA, 6.3 v. 2 a. .. 17/6

STD., 250-0-250, 85 mA, 6.3 v. 3.5 a. .. 17/6

HEATER TRANS. 6.3 v. 1 1/2 amp. .. 7/8

Ditto, tapped sec. 4, 4, 6.3 v., 1 1/2 amp. .. 8/8

Ditto, sec. 6.3 v. 3 amp. .. 10/8

GENERAL PURPOSE LOW VOLTAGE, 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/8

AUTO TRANSFORMER, 150 w. .. 22/8

0, 120, 200, 220, 250 v., 500 w. .. 22/8

MULLARD 4510V Mains transformer .. 30/6

PARMEKO MAINS TRANSFORMER. Made for special contract, the ratings can safely be doubled. Guaranteed 2 years. Primary 0-110-210-230-250 v. H.T. 300-0-300 v. 50 mA. L.T. 6.3 v. 1.8 amp. Size 4 x 3 1/4 x 2 1/4 in. Weight 6lb. Post 2/6 .. 17/6

MAINS POWER PACK. Size 3 1/2 x 4 1/2 x 4 in. with mains transformer, metal rectifier and condensers to provide smoothed H.T. output 230 v. 45 mA. D.C., L.T. 6.3 v. 2 a. Centre tapped. All ready built on a strong metal chassis. Brand New. Bargain. Post 2/6 .. 28/6

INTERVALVE TRANSFORMERS 3:1 or 5:1.. 9/6
O.P. TRANSFORMERS. Heavy Duty 50 mA, A.C. Multitap, push-pull, 7/6. Ditto, 10 w. 15/6. Miniature, 384m etc. 5/8. L.F. CHOKES 10/10H. 60/60 mA. 5/-; 10 H. 55 mA. 10/6; 10 H. 150 mA. 14/-

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 6 or 12 v. 1 1/2 amp., 8/8; 2 a., 11/3; 4 a., 17/6

CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps., 15/6. 2 amps., 17/6. 4 amps., 22/6. Circuit included.

4 AMP CAR BATTERY CHARGER with ammeter Leads, Fuse Case, etc. for 6 v. or 12 v. 6/8

BOOKS list S.A.E.

40 Circuits for Germanium Diodes 3/-

"W.W." Radio Valve Data, 6/-

High Fidelity Speaker Enclosure, 5/6

Valve and TV Tube Equivalents, 9/6

TV Fault Finding, 5/-

Quality Amplifiers, 4/6

Radio Valve Guide. Books 1, 2, 3 or 4, 5/- each.

Transistor Superhet Receivers, 7/6

Practical Radio Inside Out, 3/6

Master Colour Code Chart, 1/6

Transistor Controlled Models, 7/6.

4 TRANSISTOR PUSH-PULL AUDIO AMPLIFIER
Size 3 x 1 1/2 x 1.

A ready built miniature push-pull amplifier with input and output transformers, 4 transistors. Ideal for use with record players, intercoms, etc. Complete with full instructions and circuit.

Price 52/6 9v Batt. 2/3, 2 1/2 in. Speaker 15/-

C.R.T. BOOSTER TRANSFORMERS for heater cathode short circuit, or tubes with falling emission. Full instructions supplied, mains input. Type A optional 25% and 50% boost. 2v. or 4v. or 6.3v. or 10.5v. or 12.6v. State voltage reqd. PRICE 10/6.

LOUDSPEAKERS P.M. 3 OHM. 2i, 3, 4in., 19/6. 6in. Rois, 17/8; 8in. Plessey, 19/6; 7in. x 4in. Rois, 18/-; 6in. Rois, 15/8; 10 x 6in. 27/6; 10in. Rois, 30/-; 4in. T.ester, 25/-; 12in. R.A. 30/-; 13 1/2 x 8in. Double Cone E.M.I. 45/-

STENTONIAN EP1012. 10in. 3 to 18 ohms, 10 w. 95/- 35 ohm, 7 x 4in., 25/-; 5in., 22/8; 8in., 19/6.

BAKER SELHURST LOUDSPEAKERS



Details S.A.E.

12in. Baker 15w. Stalwart 3 or 15 ohms, 45-13,000 c.p.s. 90/-

12in. Stereo, Foin Suspension, 12w., 35-16,000 c.p.s. 25.17.9

12in. Baker Ultra Twelve, 20 c.p.s. to 25 kc/s, £17.9

15in. Auditorium, 35 w. Bass, 20 c.p.s. to 12 kc/s, £13

Details and Enclosure plans S.A.E.

TWIN GANG TUNING CONDENSERS. 365 pF. miniature 1in. x 1 1/4 in. x 1 1/2 in. 10/- 500pF Standard with trimmers, 9/-; midget, 7/6; with trimmers, 9/-; 500pF slow motion tuning, standard or midget, 9/-

SMALL 3 GANG 500 pF. 10/-

SINGLE 25 pF, 50 pF, 75 pF, 100 pF, 160 pF, 5/6. Solid dielectric 100, 300, 500 pF, 8/6.

CONDENSERS. New stock. 0.001 mfd., 7 kv. T.U.C.C. 5/6; Ditto, 20 kv, 9/8; 0.1 mfd., 7 kv, 9/8. Tubular 500 v. 0.001 to 0.05 mfd., 9d., 0.1, 1/-; 0.25, 1/6; 0.5/500 v., 1/8; 0.1/500 v., 8d.; 0.1/2,000 v., 0.1/1,000 v., 1/8; 0.1 mfd., 2,000 volts, 3/8.

CERAMIC CONDS. 500 v. 0.3 pF to 0.01 mfd., 9d.

SILVER MICA CONDENSERS. 10% 5 pF to 500 pF 9d.; 600 pF to 3,000 pF, 1/-. Close tolerance (± 1 pF) 2.2 pF to 47 pF, 1/-. Ditto 1% 50 pF to 815 pF, 1/-; 1,000 pF to 5,000 pF, 1/8.

465 kc/s SIGNAL GENERATOR
Price 15/-. Uses B.F.O. Unit, ZA 30038 ready made with valve IS5. **POCKET SIZE** 2 1/2 x 4 1/2 x 1 1/2 in. One resistor to change. Full instructions supplied. Battery 8/6 extra. 69V 1 1/2 V. Details S.A.E.

WAVECHANGE SWITCHES

8 p. 4-way 2 wafers long spindle. 6/6

2 p. 2-way, 0.2 p. 6-way long spindle or 4 p. 2-way or 4 p. 3-way long spindle. 3/6

3 p. 4-way, or 1 p. 12-way long spindle. 3/6

Wavechange "MAKITS". Wafers available: 1 p. 12 way, 2 p. 6 way, 3 p. 4 way, 4 p. 3 way, 6 p. 2 way, 1 wafers switch, 8/6; 2 wafers switch, 12/6; 3 wafers switch, 16/6; additional wafers up to 12. 3/6 each extra.

Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.c.t., 4/-; Rotary Toggles s.p., 3/6; d.p., 4/6.

CRYSTAL MIKE INSERT, 8/6
Precision engineered. Midget size

ACOS 39-1 DE LUXE STICK MIKE 35/-
TSL QUALITY STICK MIKE 25/-

Valveholders. Pax. int. oct., 4d. EA50, 6d. B12A. CRT. 1/3. Engl. and Amer. 4, 5 and 7 pin, 1/-.

MOULDED Mazda and int. oct., 6d.; **BTG, BBA, BBG, B9A, 9d.** BTG with can, 12/6; BBA with can, 18/6. Ceramic EP85, BTG, B9A, int. oct., 12/-; BTG, B9A cans, 1/- each.

Quality 2-Stage HI-FI AMPLIFIER
A.C. only. 200-250 v. Valves ECL86 and EZ80. 3 watt quality output. Mullard tone circuits, bass boost, treble and volume controls. Separate engraved front panel with de-luxe finish. Heavy duty output transformer, 3 ohm. Shrouded mains transformer. Stove enamelled chassis size 6in. x 5in. x 3in. **Bargain Price £4.10.0.** Circuit supplied.

THE ORIGINAL RADIO COMPONENT

Our written guarantee with every purchase. Bus 133 or 68 pass door S.R. Station Selhurst

Volume Controls 80 ohm COAX

Linear of Log Tracks. III
Long spindles. Midget
5 K ohms to 2 Meg. 40 yds. 17/6
L/S, 3/-; D.P. 4/6;
Stereo L/S 10/6; DP 14/6

TELESCOPIC CHROME AERIALS. 13in. extending to 43in. 8/6 ea. Coax Adaptor Plug, 1/6 extra.
TUNERS Ext. Speaker Control, 10/2 3/-.
WIRE-WOUND POTS. 3 WATT. Pre-set Min. TV Types. All values 10 ohms to 25 K, 3/- ea. 30 K, 50 K, 4/- (Carbon 30 K, to 2 meg., 3/-).
WIRE-WOUND 4 WATT Pots. Long spindle. Value 50 ohms to 50 K, 6/8; 100 K, 7/6.
PHILIPS TRIMMERS. 0-10 pF, 3-30 pF, 1/-.
TRIMMERS. Ceramic, 30, 50, 70 pF, 9d., 100 pF, 150 pF, 1/3; 250 pF, 1/8; 500 pF, 750 pF, 1/8. TV etc. TRIMMER, 1000 pF, with knobs, 2/-.
RESISTORS. Preferred values, 10 ohms to 10 meg., 1 w., 4d.; 1 w., 4d.; 1 w., 8d.; 1 w., 8d.; 2 w., 1/6. High Stability, 1 w., 1/2, 2/-. Preferred values 10 Ω to 10 meg. Ditto 5%, 10 Ω to 22 meg., 9d. 5 watt { **WIRE-WOUND RESISTORS** } 1/3
10 watt { 10 ohms-10,000 ohms } 2/-
12.5K to 50K 10 w. 2/3-

AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE

Double Play 7in. reel, 2,400ft. 60/-	Spare Plastic Reels
5in. reel, 1,200ft. 37/6	3in. 1/6
Long Play 7in. reel, 1,800ft. 35/-	5in. 2/-
5in. reel, 1,200ft 23/6	4in. 2/-
5 in. reel, 900ft. 18/6	5in. 2/6
Standard 7in. reel, 1,200ft. 25/-	7in. 2/-
5in. reel, 600ft. 16/-	5in. 2/6

"Instant" Bulk Tape Fraser and Herd Defluxer, 200/250 v. A.C. 27/6. Leaflet with full details. S.A.E.

CRYSTAL SET BOOKLET, 1/-.
CRYSTAL DIODE (G.E.C.), 2/-, GEX34, 4/-, OA81, 3/-.
HIGH RESISTANCE PHONES. 4,000 ohms, 15/- pr.
SWITCH CLEANER. Finkl squirt spout, 4/6 tin.

HIGH GAIN TV PRE-AMPLIFIERS
BAND I B.B.C.
Tunable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCC84 valves if preferred).
BAND III I.T.A.—Same prices.
Tunable channels 8 to 13. Gain 17 dB

1/16in. Paxolin Panels, 10 x 8in., 2/-.
Miniature Contact Cooled Rectifiers, 250V 50mA, 7/6; 250V 60mA, 8/6; 250V 85mA, 9/6; 200 mA, 21/-; 300mA, 27/6.
TV etc., Silicon Sub-Min. Rectifier, 125V, 300mA, 6/6; 250V, 300mA, 14/6.
Selenium Rect., 300V 85mA, 5/-.
Coils Wearite "P" type, 3/- each.
Osrom Midget "Q" type, adj. dust core, from 4/- each. All ranges. List S.A.E.
Teletron D.W.H. L. and Med. T.R.F. with reaction, 4/-. Med. wave D.R., 3/6.
Ferrite Aerials, M., 8/9; M. and L., 12/6.
Osrom Ferrite Rod Aerials, L. and M. for transistor circuits, 10/- each.
Ferrite Rods, 8 x 1in., 3/-; 5 x 3/16in., 3/-.
H.F. Chokes, 2/6. Osrom OC1, 6/9.
T.R.F. Coils, A/H/F, 7/- pair; HAX, 3/-.
Repenco DRR2, 4/-, DRX1, 2/6.
Radio Screwdriver, 5in., 6/1.
Neon Mains Tester Screwdriver, 5/-.
Solder Radiograde, 4d., yd., 4lb, 5/-.
Black Crack Paint. Air drying, 3/- tin.

Aluminium Chassis, 18 s.w.g. Plain undrilled, 4 sides, riveted corners. Lattice fixing holes, 24in. sides, 7 x 4in., 4/6; 9 x 7in., 5/9; 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6.
Aluminium Panels, 18 s.w.g., 12 x 12in., 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/6; 8 x 6in., 2/-.

"6 + 1" TRANSISTOR RADIO MEDIUM AND LONG WAVE KIT
First class components to make a 6 transistor 2 wave band superhet chassis ideal for portable or table radio. All parts including 6V/A transistors, ferrite aerial, printed circuit, 8 1/2in. x 2 1/2in., but EXCLUDING speaker and cabinet. Simple instructions 1/6 (Free with kit).
Speakers, 35 ohm, 7 x 4in. 25/- 5in. 22/6, 3 1/2in. 19/6. **£4.5.0**

BULGIN PLUGS AND SOCKETS. Non-reversible P74, 2-pin, 4/8; P73, 3-pin, 4/6, etc.
JACKS. English open circuit, 2/6. Closed circuit, 4/8. Grundig type, 3 pin, 1/8.
JACK PLUGS. English, 3/-; Screened, 4/-; Grundig, 3 pin, 3/6.
ALADDIN FORMERS and cores, 1in., 8d.; 1 1/2in., 10d.
0.1in. FORMERS 6937 or 8 cans TV1 or 2, 2 1/2in. sq. x 2 1/2in. sq. x 1 1/2in., 2/- with cores.
SLIP MOTOR DRIVES. 6, 1, 2/8.
SOLENO IRON, 25W, 200V or 230V, 24/-.
ANTEX SUB-MIN IRON 15w. 200 or 240 v., 29/6.

JASON FM TUNER COIL SET 29/- H.F. coil, aerial coil, oscillator coil, two i.i. transformers 10.7 Mc/s detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. Complete Jason FMT-1 Kit—Jason chassis with calibrated dial, components and 4 valves, £8.5.0.

MAINS DROPPERS. Midget adjustable sliders, 0.3A, 1,000 ohms, 5/-; 0.2A, 1,200 ohms, 5/-; 0.15A, 1,500 ohms, 5/-; 0.1A, 2,000 ohms, 5/-.
MIKE TRANSFORMER. 60-1, 3/9.
P.V.C. Conn. Wire, single or stranded, 2d. yd. Sleeving, 1 or 2 mm, 2d., 4mm, 3d.; 6 mm, 5d. yd.
SPEAKER FRET. Gold cloth, 17 x 25in., 5/-; 25 x 35in., 10/-. Tycan, various colours, 52in. wide from 19/6. 25in. wide, from 6/- Samples, S.A.E.
Expanded Metal, Gold, 12 x 12in., 6/-.

TELEVISION REPLACEMENTS
Line Output Transformers
from 45/- each, NEW Stock and other timebase components. Most makes available. S.A.E. with all enquiries

WEYRAD
COILS AND TRANSFORMERS FOR 60 WAVE TRANSISTOR SUPERHETS WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL
Long and Medium Wave Aerial—RA2W. On 6in. rod, 208pF tuning. 12/6
Car Aerial Coil 1/-
Osc. Coil P50/1AC, 17pF tuning. 5/4
1st and 2nd I.F. Trans.—P50/2CC, 470kc/s 11/16in. dia. by 1in. 5/7 each.
3rd I.F. Trans.—P50/3CC. 6/-
Spare Cores 1/-
Driver Transformer—LFDT4. 3/6
Wavechange Slide Switch. 9/8
Printed Circuit—PCAL. Size 2 1/2 x 8 1/2in. Ready drilled and printed. 9/8
Volume Control. SK3DP. 4/6
7 x 4in., 35 ohm Speaker. 25/-
3 1/2in. round 35 ohm speaker. 19/6
24 Fixed Resistors. 21/-
16 Fixed Condensers. 10/6
Tuning Gang with Trimmers. 10/6
6 Mullard Transistors and diode. 42/6
Constructor's Booklet. 2/-
Circuit and Details S.A.E.

NEW MULLARD TRANSISTORS
OC1 6/-, OC72 7/6, OC81D, 7/6, OC81, 7/6, OC4 8/9, OC45 8/9, OC171 10/6, AF117 9/6
Sub Miniature Condensers. 0.1 mfd, 30 v. 1/3, 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mfd, 15 volt 2/6 each Transistor Holders 1/3.
B.B.C. Pocket 2 Transistor. M.W. and L.W. Radio Kit, 22/6.
Miniature earpiece, 7/6. Batt. 2/3.

MONARCH RECORD PLAYER

Kit with ready built amplifier, speaker and cabinet. **£12.10.0**
carr. and ins. 5/-



Garrard deluxe auto-player kit

£12.19.6 Carr. and ins. 5/- details S.A.E.

GARRARD QUALITY AUTO-CHANGER, 4-speed, with plug-in xtal head. Ready built 2-valve amplifier, Loudspeaker and contemporary styled Portable Player Case.

All items guaranteed to fit together perfectly, can be assembled in thirty minutes, full instructions supplied.

- 4 Speed Autochanger, B.S.R., U.A.14 **£7.10.0**
 - B.S.R., U.A.12 Stereo/Mono **£8.5.0**
 - Garrard Model Autoslim **£7.19.6**
 - 4 Speed Single Players, EMI **£6.5.0**
 - Garrard TA Mk.II, GC8 Head **£8.0.0**
 - Garrard Model 48P GC2 **£8.17.6**
 - Garrard 4HF Transcription **£17.19.6**
 - Amplifier player cabinets (except 4 H.F.) 70/-
 - 2-valve amplifier and 6jin. speaker **95/-**
 - 3-valve amplifier and 6jin. speaker **105/-**
- Wired and tested ready for use with above.
Replacement sapphire styli available from 6/-.
Replacement Xtals from 21/-; Stereo from 35/-.

SINGLE PLAYER KITS

£8.15.0 post 4/6. **Ready Built**
With 2-stage, 3 watts output amplifier. High flux 5in. speaker. Handsome portable case 13 x 10 1/2 x 7 1/2in. Collaro 4-speed junior motor. LP/Std xtal pick-up for 7, 10, and 12in. records.
FEW ONLY KITS AS ABOVE but with 3-speed B.S.R. Motor complete. **£7.15.0** (Post 4/6)

GABY MULTIMETER

Model M.I. 54/-
2 k ohm per volt, D.C. or A.C. 6 v., 30 v., 120 v., 600 v., 1200 v. D.C. 30 mA, 300 mA. Ohms 0-100k.


ARDENTE Transistor Transformers
Type D3035, 7.3 CT; Push-Pull to 3 ohms for OC72, etc., 1 x 1 x 1in. 9/8
Type D3034, 1.75 : 1CT. Push-Pull Driver for OC72, etc., 1 x 1 x 1in. 9/8
Type D3058, 11.5 : 1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in. 9/8
Type D167, 18.2 : 1 Output to 3 ohms for OC72, etc., 1 x 1 x 1in. 12/-
Type D239, 4.5 : 1 Driver Transformer, 10/-
Type D240, 8.5 : 1 Driver Transformer, 10/-

ARDENTE VOLUME CONTROLS
Type VC1545, 5K with switch, dia. 0.9in., 5/3.
Type VC1760, 5K with switch, dia. 0.7in., 10/6
Deaf aid ear piece xtal or magnetic, 7/6.

COMPONENT SHOP SPECIALISTS

337 WHITEHORSE ROAD WEST CROYDON

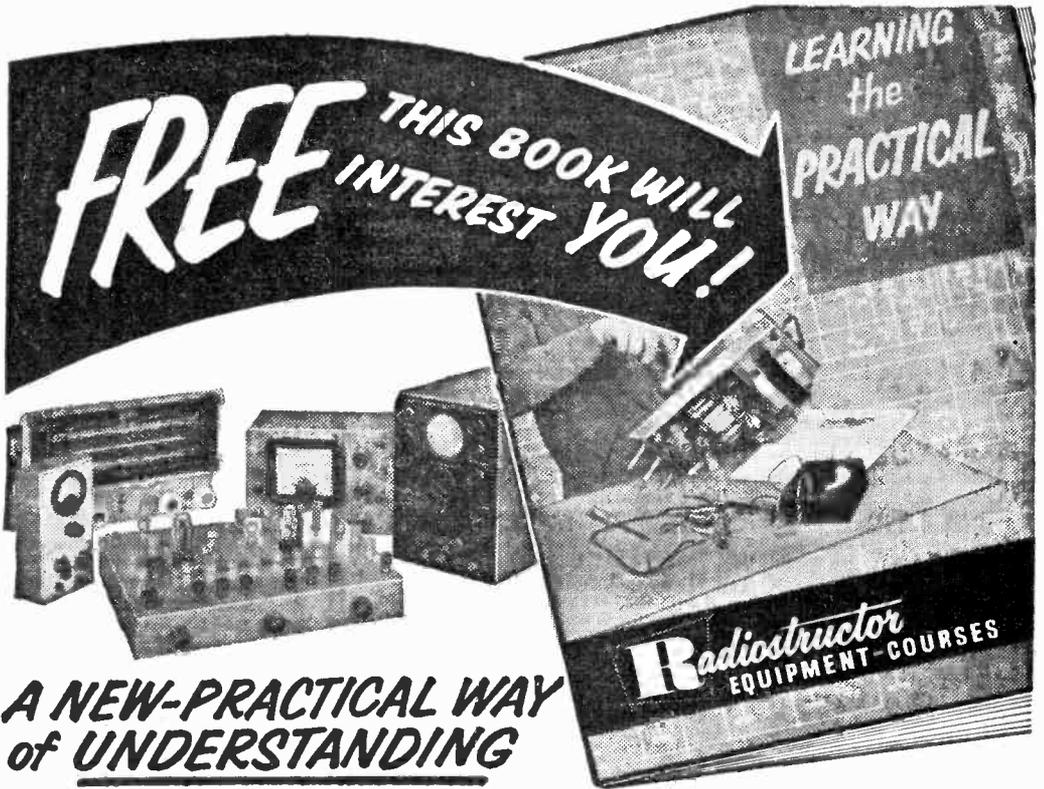Telephone: THO 1665 (Export welcome. Send remittance and extra postage).
Post 1/-, unless otherwise stated. C.O.D. 2/-.



**A NEW-PRACTICAL WAY
of UNDERSTANDING**

Radio • Television • Electronics

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

FOR ... Your Career ... Your Own Business ... An Absorbing Hobby

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis. You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details.—

RADIOSTRUCTOR
LEADS THE WORLD
IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G82)
READING, BERKS.

Please send brochure, without obligation, to:

★ Name _____

Address _____

12/62

★ **BLOCK CAPITALS PLEASE**
(We do not employ representatives)

Practical Wireless

Vol. XXXVIII No. 670 DECEMBER, 1962

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House,
Southampton Street, W.C.2.

© George Newnes Ltd., 1962

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.9.0 per annum
Abroad - - - - £1.7.6 per annum
Canada - - - - £1.5.0 per annum

Contents

	Page
Editorial	689
Round the World of Wireless	690
The Berkeley Loudspeaker Enclosure	692
Transistor Tuner/Receiver ...	696
Central Control Amplifier ...	703
DX on Medium Waves	706
On Your Wavelength	708
The Auditor	711
The Luxembourg Tuner	716
An Audio Absorption Watt- meter	718
Radio Components and their Functions	720
An Advanced Geiger Head ...	725
Trade News	733
A Simple Three Valver	737
Midget Mains Portable	742
Letters to the Editor	750
Club News	753

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

The Final Link

THIS month we present the last in the current series of free, double-sided blueprints and we feel we have produced two designs of widespread appeal and interest.

The first is the Luxembourg Tuner which, as the name implies, has been specifically designed for peak performance on 208m. This tuner incorporates some novel features which will appeal to those wanting to try something a little different, it is easy to build and is strongly recommended to readers who want better-than-normal reception of Radio Luxembourg.

The reverse side of our blueprint also breaks new ground, so far as PRACTICAL WIRELESS is concerned. It is probably true to say that of the thousands of enthusiasts who take the trouble to build good quality receivers and amplifiers, a good many make do with inferior or indifferent arrangements for the final link in the audio chain.

One can, of course, mount a loudspeaker on a solid baffle or insert it into a box of any convenient shape and size and get reasonable (even superb) results. Much depends, naturally, on the predominating acoustics and the degree of audio discernment in the ears of individual listeners.

But this hit-or-miss approach, while capable of relatively good results can lead to disappointment and, in any case, it seems odd to carefully design the electronics and take the acoustics for granted.

In general, then, a well-designed enclosure is the only real housing for a loudspeaker and the only acceptable device for disseminating high quality audio.

We feel it is appropriate, therefore, to conclude this series of blueprints with *The Berkeley*—a specially designed bass reflex speaker enclosure which is suitable for use with P.W. or other high quality amplifiers and which will give added pleasure to your record, radio or tape listening.


Our Query Service

ONCE again we must remind our readers of the rules of our Free Query Service. The following points should be carefully noted:

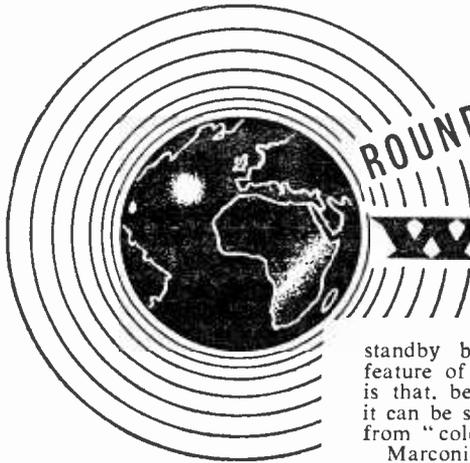- (i) We cannot undertake to answer technical queries over the telephone
- (ii) All queries must be accompanied by the query coupon from the current issue
- (iii) If a postal reply is required a stamped and addressed envelope must be enclosed with the query.

We must also point out that we cannot design circuits to readers' specific requirements. Nevertheless we shall continue to help readers as far as possible but it should be remembered that all information necessary for answering the query should be sent to us.

Our next issue dated January will be published on December 7th.



ROUND THE WORLD of WIRELESS

NEWS AT HOME AND ABROAD

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of August, 1962, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued to blind persons without payment.

Region	Total
London	636,984
Home Counties	592,473
Midland	429,035
North Eastern	450,898
North Western	390,288
South Western	348,923
Wales and Border Counties	198,280
Total England and Wales	3,050,361
Scotland	325,608
Northern Ireland	109,518
Grand Total	3,485,487

High-power Radars for Ministry of Aviation

CONTRACTS by the Ministry of Aviation have been awarded to Marconi's for the provision and setting to work of three dual installations of 500kW, 50cm radars, type S264A. These will be sited at St. Annes (near Blackpool), Ash (near Sandwich, Kent) and Ventnor (Isle of Wight). These are the first radars ordered by the Ministry for the United Kingdom Airways System.

The dual installations consist of the complete transmitting/receiving and ancillary equipment in duplicate, feeding a common aerial head on a main/

standby basis. One particular feature of the S264A equipment is that, being crystal controlled, it can be switched into operation from "cold" if necessary.

Marconi 50cm radars are currently in operation at many British airports. Service establishments and airfields.

Conference on the Design and Use of Microwave Valves

THE Electronics Division of the Institution of Electrical Engineers is organising a three-day national conference in September, 1963, on the design and use of microwave valves. This has been timed to fall between international conferences on microwave valves which are held every other year and the programme will be complementary to these conferences.

The forthcoming conference will review present techniques and developments and will cover fundamental valve design, present performance and the use of valves in systems, including matching system characteristics with achievable valve performance.

It will be of particular interest to engineers in this country who do not attend international conferences and among the subjects to be covered will be "signal amplification and physical measurement", "communications and industrial applications" and "radar".

New Headquarters Installation for R.A.F. Radio Amateurs

THE new headquarters of the R.A.F. Amateur Radio Society was opened recently at No. 1 Radio School, R.A.F. Locking.

The society, which was formed in 1939, includes a large number of professional wireless operators, both R.A.F. and ex-Service, in its membership and most local R.A.F. amateur radio clubs are affiliated.

A grant of £660 from the Nuffield Trust for the Forces has paid for the most expensive of the new installation which is used in conjunction with a beam aerial which can be directed to any part of the globe. A standby transmitter also capable of top band communication has also



A Marconi 50cm surveillance radar of the type recently ordered by the Ministry of Aviation.

been installed in addition to a 2m VHF set which is restricted to United Kingdom use.

Recording Noise

LONDON is the first city in the world to be systematically surveyed for noise. The information obtained will be useful for town planning generally and especially to architects when making provision for insulation in new buildings of all kinds in the central area.

Information about noise levels at selected sites throughout central London is also being recorded for use in particular town planning problems such as assessing the noise effects of elevated motorways and heliports and for siting hospitals and other buildings where noise may be detrimental to their use.

The London Noise Survey is being conducted by the Building Research Station of the Department of Scientific and Industrial Research and the London County Council. Two vans with equipment which includes TR52/2 professional tape recorders supplied by EMI Electronics Ltd. are sampling noise levels for 100 seconds once an hour over a 24-hour period at each of 540 points, distributed at 500yd. intervals on a rectangular grid over central London. The work has continued since early in 1961 and more than 350 sites have already been monitored.

Noises are automatically recorded on magnetic tape every hour on the unattended tape recorders. At the end of the 24-hour period the tape is taken to the Building Research Station at Garston for analysis.

New T.I.M. Recording

THE Post Office is to make new recordings for T.I.M., the Speaking Clock.

The present Speaking Clock, which has been in use since 1936, is to be replaced early next year. While the timekeeping of the present clock is as good as it was a quarter of a century ago some parts of it are obsolete.

The new clock, which has been designed and built by Post Office engineers at the Research Station at Dollis Hill, London, will, with the new techniques employed, be cheaper to instal, maintain and operate. The quality of the recordings will also be improved.



A member of the LCC staff is seen here switching on an EMI tape recorder in a van at an Albert Embankment site, in London, to record sample noise levels (see "Recording Noise").

The Great German Radio Exhibition

OVER 100 firms to date have registered for the Great German Radio Exhibition to be held at the Berlin Funkturm from August 30 to September 8, 1963. Final figures can only be estimated at the commencement of next year. However, it can already be determined that once again all halls and pavilions of the exhibition area occupied in 1961 will also be in demand for the Radio Exhibition of 1963.

The studios of the broadcasting stations will again participate with demonstrations in the exhibition. Formerly only one hall of the exhibition grounds was required to house the Channel 1 television programme; however, in the coming year a further hall is planned for the Channel 2 programme.

Temporary VHF Station on the Isle of Skye

THE BBC's plans for extending and improving reception of

its sound and television broadcasting services in the West of Scotland and the outlying islands provide for several new transmitting stations, including a combined television and VHF sound station for the Isle of Skye. As the completion of this station and of the necessary radio links to connect it with the BBC's Scottish programme networks will take some time a temporary low-power VHF sound relay station has been brought into service at Penifiler to serve the town of Portree. This station is now transmitting the Scottish Home Service on 93.9Mc/s with horizontal polarisation, which means that VHF receiving aerials should be mounted horizontally.

It is hoped to complete the television station for the Isle of Skye and the permanent VHF sound station, which will radiate the Light and Third programmes as well as the Scottish Home Service, early in 1964.


PRESENTED FREE
 WITH
"PRACTICAL WIRELESS"
 DECEMBER 1962

Practical Wireless







BERKELEY BASS REFLEX LOUDSPEAKER ENCLOSURE

PUBLISHED BY GEO. NEWNES LTD., TOWER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.

PRICE
5/-

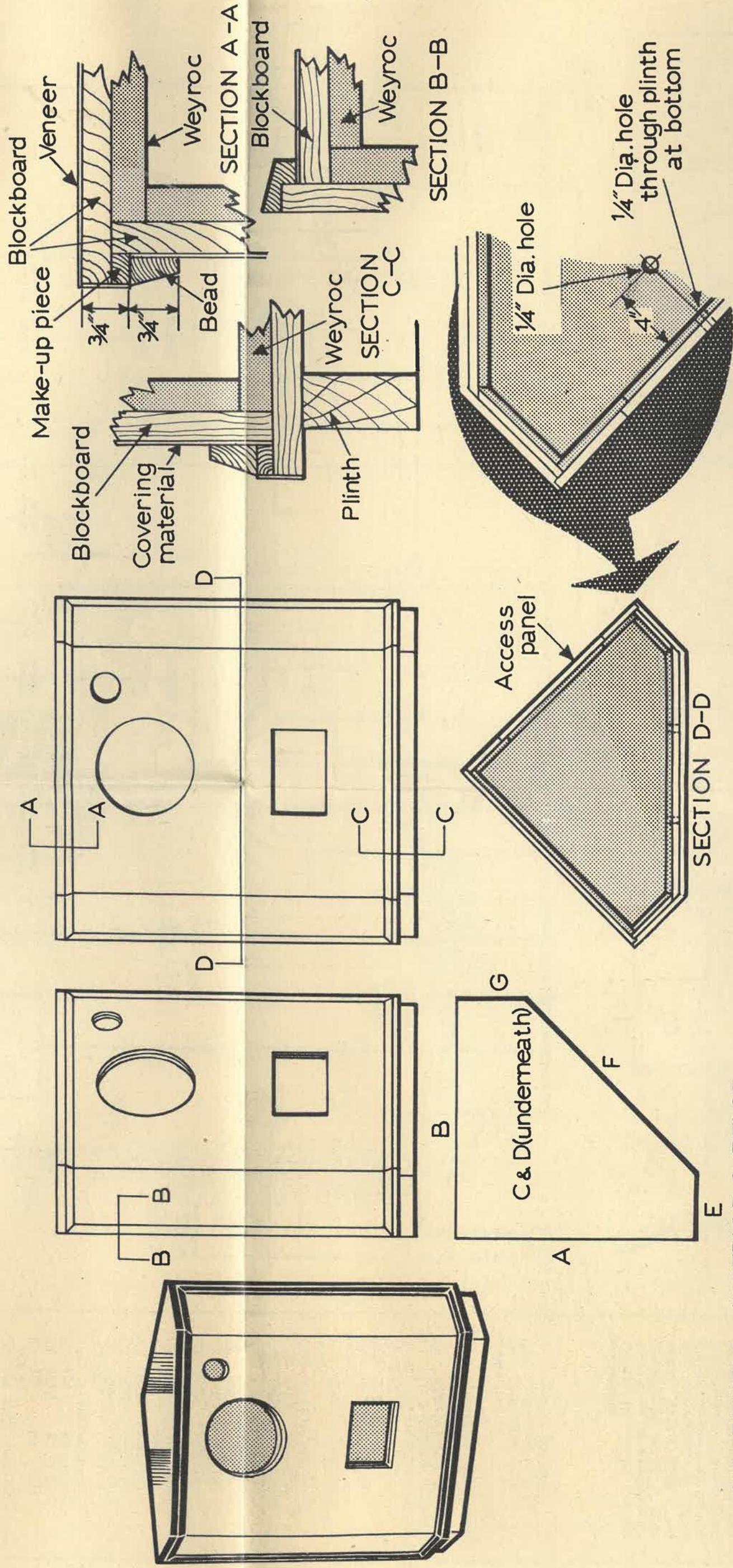


ALL PANELS - INTERIOR SURFACE

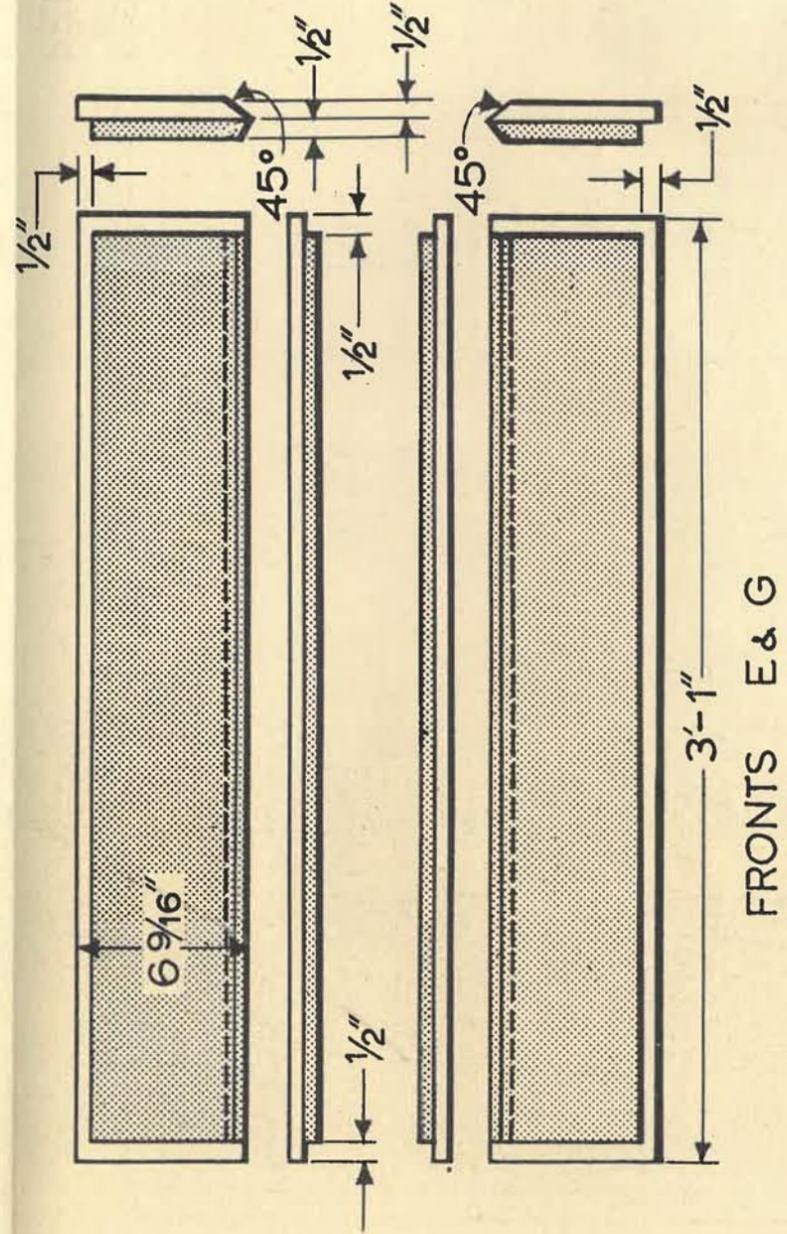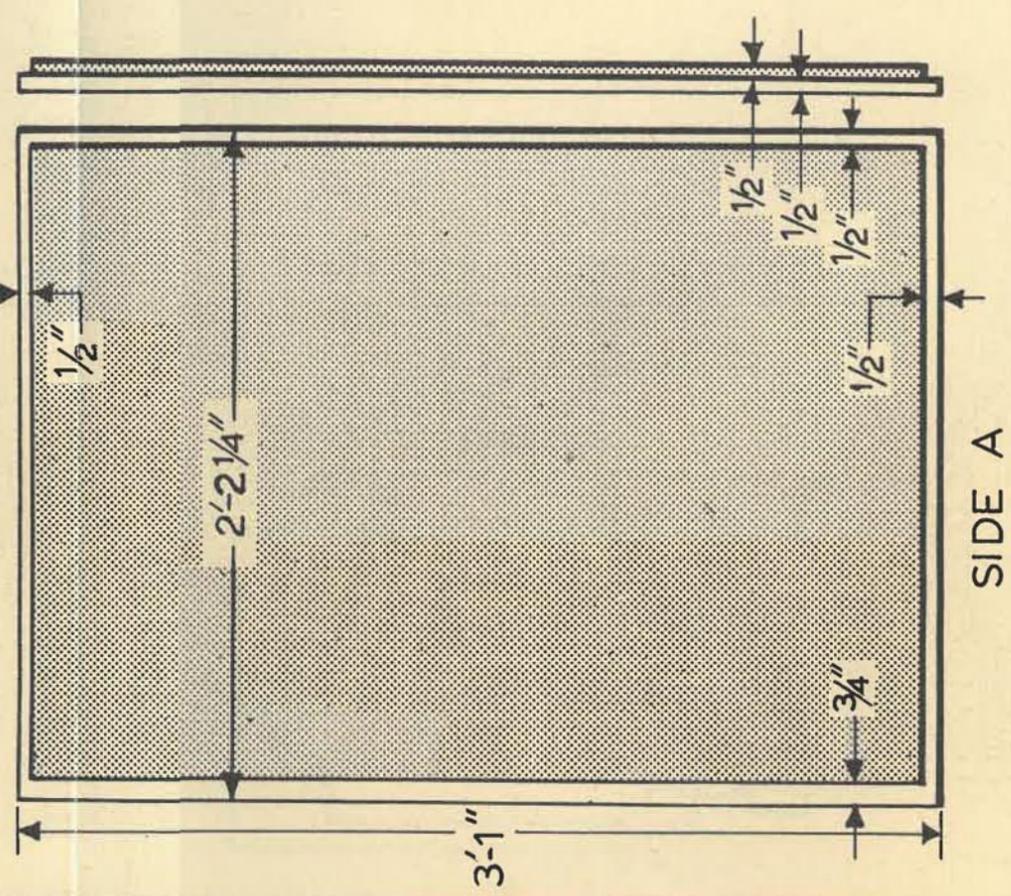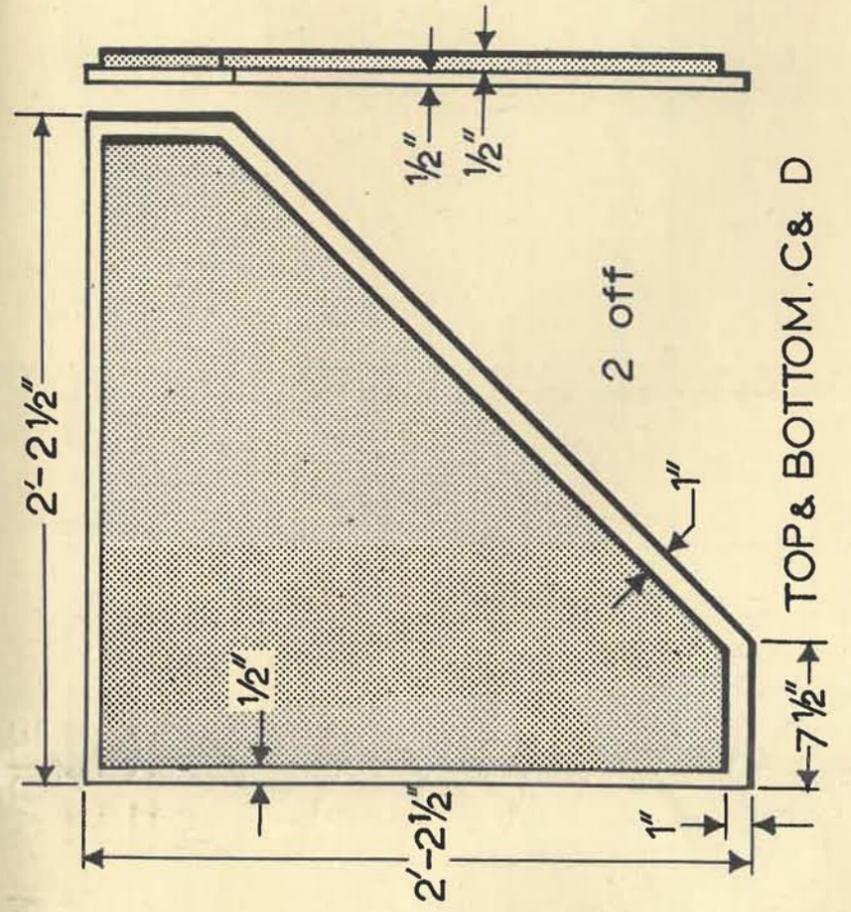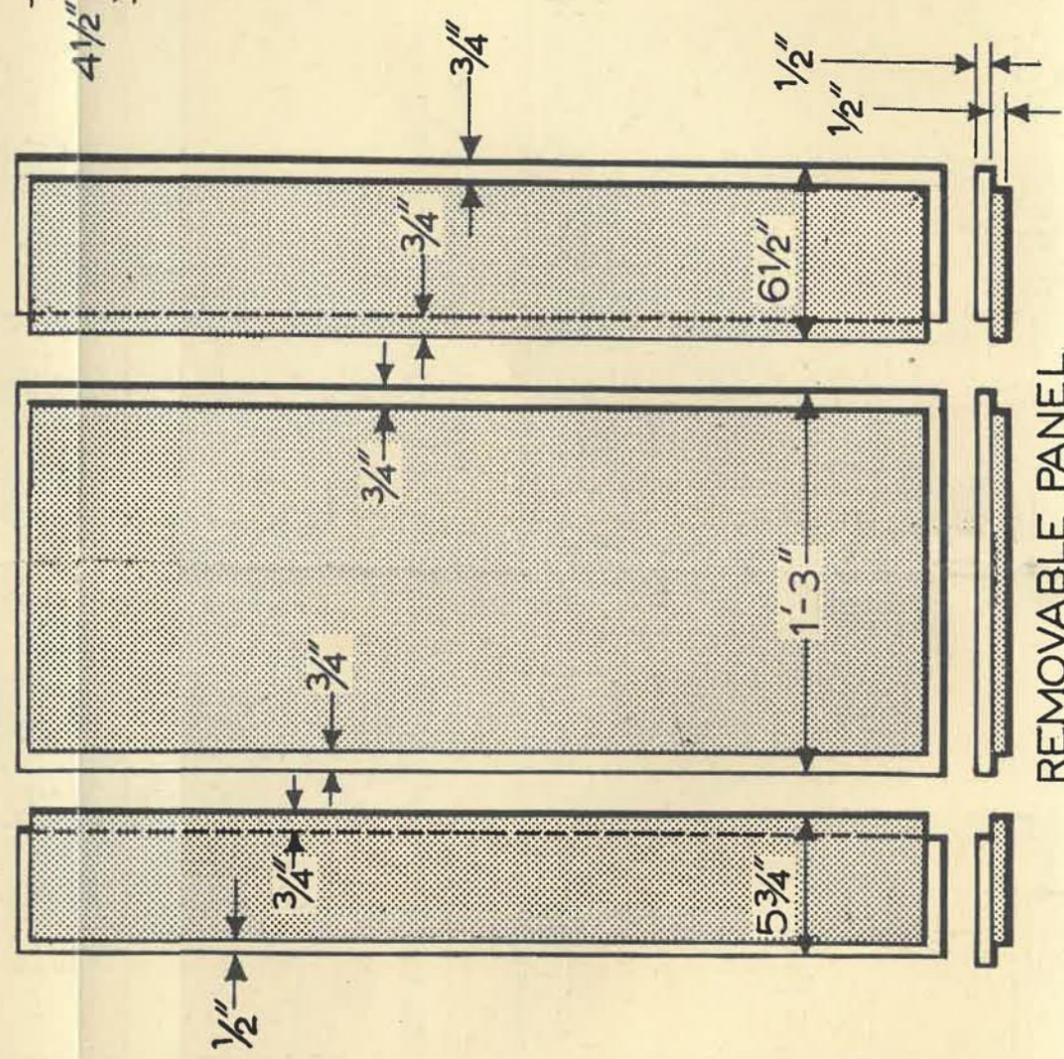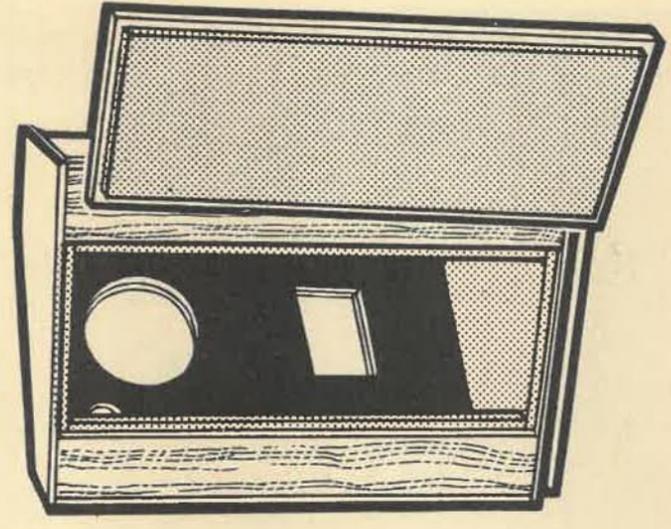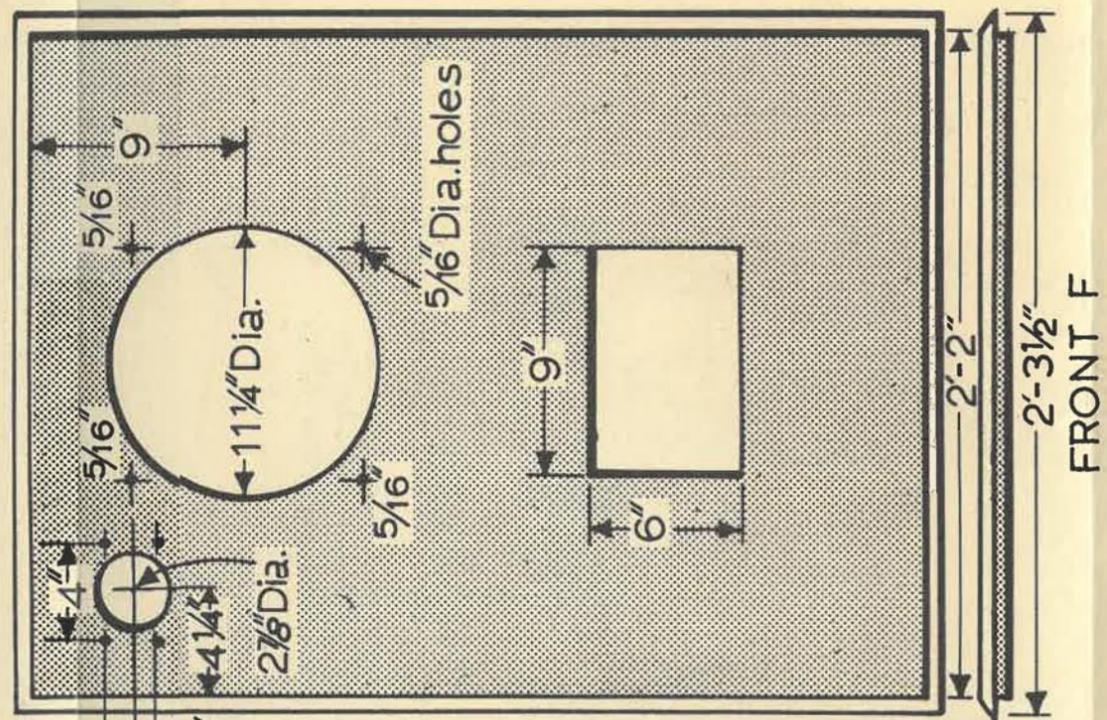

A HIGH QUALITY
BASS REFLEX
CABINET

By R. Edwards

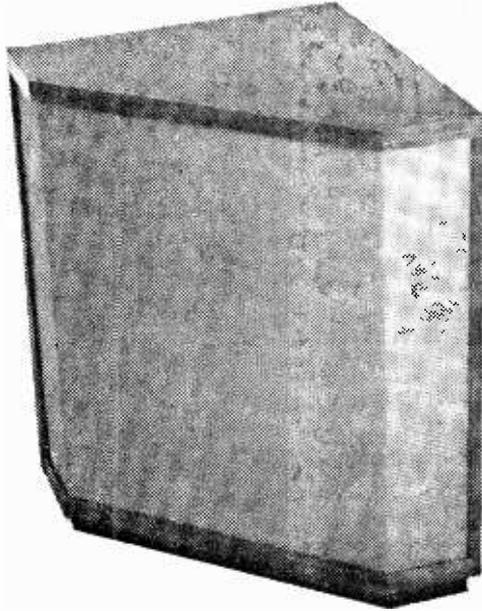

The *BERKELEY* Loudspeaker Enclosure

THE bass reflex type of loudspeaker enclosure has been popular for many years on account of its ability to provide good smooth output down to the lowest frequencies normally reproducible by the particular moving coil unit employed.

In this type of enclosure, which is also known as a "vented enclosure" or "phase inverter cabinet", use is made of the sound waves radiated from the rear of the loudspeaker cone, and these waves are allowed to emerge at the front of the cabinet through an aperture or "vent" close to the loudspeaker opening. The interior of the cabinet forms a resonant cavity and its resonant frequency is determined by the volume of air enclosed and the area of the vent. It is usual practice for the enclosure to be tuned to the bass resonant frequency of the loudspeaker unit.

Due to the loading provided by the enclosure, the characteristic peak in the loudspeaker speech coil impedance curve at bass resonance resolves into a pair of peaks, one just above the enclosure resonant frequency, and the other just below. The amplitude of both peaks is considerably less than that of the original single bass resonant peak, con-

sequently there is less mismatch with the amplifier at this frequency than there would be normally, and so more power is delivered to the speech coil.

Furthermore, in the region of resonance, greater air loading is offered to the cone resulting in improved efficiency of the system together with a reduction of amplitude distortion.

For sound frequencies equal to and just above the enclosure resonant frequency sound waves radiated from the rear of the cone undergo a 180° phase change and appear at the vent in phase with the radiation from the front of the cone, thus the effective sound output is the combined output of these two sources.

When the sound frequency is lowered below resonance the phase of the air in the vent changes abruptly and tends to oppose that from the front of the cone. The response of the system therefore falls off just below the enclosure resonant frequency.

On the other hand, as the frequency is raised above the enclosure resonance the enclosed volume of air becomes increasingly capacitive and the sound waves from the rear of the cone tend to become absorbed within the cavity, until eventually at high frequencies there is practically no output from the vent and the system performs as an infinite baffle.

Design Features

Optimum size for a bass reflex cabinet is governed by the particular loudspeaker to be used, the cone diameter and fundamental resonance being key factors in this respect. The Berkeley bass reflex enclosure is intended for use with a high power amplifier, such as the *Strand Amplifier* (described in the October issue of PRACTICAL WIRELESS), and has been designed around a 12in. dia-

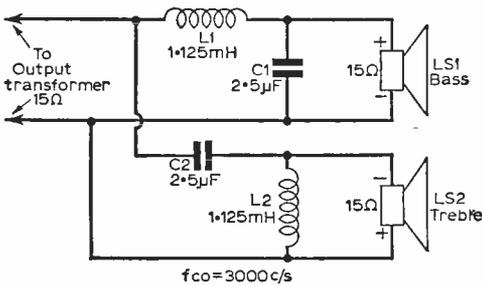


Fig. 1—A half-section, constant-resistance network; parallel connection.

meter moving coil unit having a power handling capacity of 15W. Provision is also made for the fitting of a H.F. tweeter unit.

The loudspeaker specified is WB Model H.F. 1216. This is a full range unit, covering 20c/s to 16,000c/s and has a fundamental resonance of 37c/s. A second choice would be the WB Model H.F. 1214. This is a less expensive unit and has a frequency coverage from 25c/s to 14,000c/s, while the bass resonance is at 39c/s.

A corner style enclosure has been adopted as this allows full advantage to be taken of the walls as reflecting surfaces and these improve the low frequency sound distribution. A triangular cabinet has good acoustical properties and is, of course, likely to prove the most convenient shape for installation in a room.

The dimensions of the *Berkeley* have been chosen to provide a volume of 9 cu. ft. which is about ideal for the type of loudspeakers specified, and it is tuned to just below 40c/s approximately by a plain vent. A smaller cabinet would result in inferior bass response and would also prove more critical in respect of tuning. The effects of standing waves are less serious in a large enclosure and can usually be dispelled by the use of only a small amount of lagging material.

To ensure rigidity and so prevent resonance effects from any of the surfaces, all panels are 1in. thick and are built up from equal thicknesses of blockboard and chipboard and glued together. All joints must be glued and must be air tight since

any air leakage other than through the two apertures in the front panel will impair the proper functioning of the enclosure as a "bass reflex".

The small aperture to the right of the large loudspeaker opening is for an H.F. tweeter unit, but the fitting of such a unit is quite optional. It is certainly advisable to try the enclosure with only the 12in. unit in position before incurring further expenditure which, subsequently, may not perhaps appear fully justified.

The question of what is correct tonal balance is very much a matter for the individual to decide, and it is possible that due to the efficient bass response there may seem to be some deficiency in the upper register. In such a case the incorporation of a tweeter unit should restore the balance satisfactorily by adding the necessary brilliance to the reproduction.

It is considered prudent to carry out this drilling and to fit the four screws during construction, or at any rate before the covering material is fitted to the front panel, since it would obviously be an inconvenient task to perform once the cabinet has been completely finished.

If a tweeter is not to be installed initially this hole must be covered by means of a piece of 1/4in. plywood about 6in. x 4in. This should be drilled to accept the four captive screws, and then clamped tightly against the inside surface of the cabinet with nuts.

The drilling details given on panel F (Blueprint) are for the W.B. Model T.12 Tweeter Unit. Details of this unit and suitable crossover networks are given later.

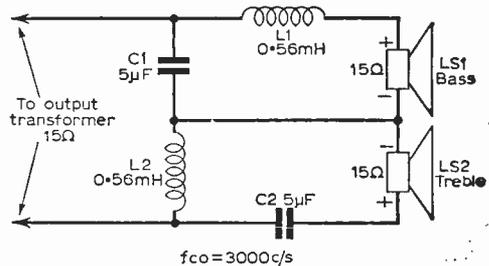


Fig. 2—A half-section, constant-resistance network; series connection.

Lagging the Enclosure


Sound waves from the rear of the loudspeaker cone at middle and upper frequencies produce standing waves in the cavity, and these are sometimes of sufficient severity to disturb the smooth response characteristic of the system and so to "colour" the output. It may be necessary to lag the interior with absorbent material in order to eliminate such effects. The amount of lagging needed can be determined only by experiment.

Critical listening tests should be made with the completed (but unlined) enclosure installed in its final location. Such tests must be of fairly lengthy duration and should involve the reproduction of both music and speech, to permit a proper assess-

ment of the loudspeaker enclosure performance to be made. Dry, unnatural colouration or tendency to boominess or over accentuation of the lower frequencies may be cured by partially lining the inside of the enclosure with felt or fibreglass blanket material $\frac{1}{2}$ in. to 1 in. thick.

It is suggested that only two interior surfaces be lined, preferably the underside of the top panel and one of the side panels. An alternative and possibly better scheme is to suspend a curtain of the same material from the top panel so that it hangs diagonally across the interior of the cabinet.

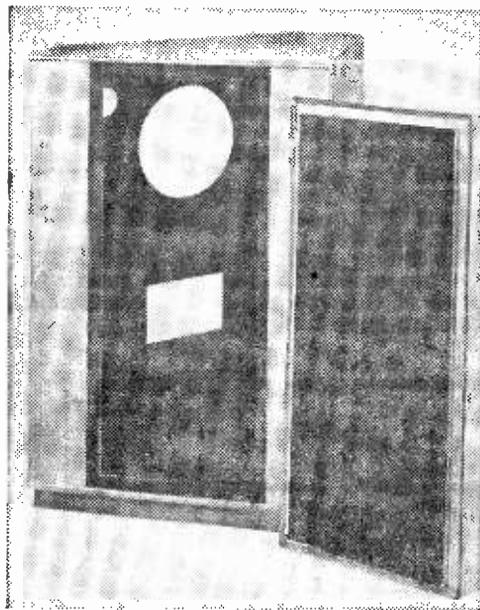The application of absorbent material must be carried out discriminately, since excessive damping of the enclosure can have an adverse effect on the high frequency response. The inspection panel must always be replaced firmly in position before resuming listening tests.




H.F. Tweeter Unit

The H.F. tweeter W.B. Model T.12 is a horn-loaded pressure driven moving coil unit. It has a frequency range of 3,000 to 17,000c/s, an impedance of 15Ω , and a power handling capacity of 15W.

When using the tweeter, a crossover or dividing network is also required in order to restrict the range of frequencies applied to each loudspeaker. The type of crossover network recommended is that known as a half-section constant-resistance network. This particular kind of crossover can take two forms, either "parallel connection" as shown in Fig. 1 or "series connection", Fig. 2. Actually there is very little to choose between these two forms. The series connection is often considered as being somewhat better in performance than the parallel arrangement; however, the latter circuit uses smaller value capacitors and so is cheaper and perhaps easier to make up.

A crossover frequency of 3,000c/s should be used, and the appropriate component values are given in the circuit diagrams. That part of the circuit feeding the L.F. unit forms a low-pass filter, and has an attenuation rate of 12dB per octave above the crossover frequency. The H.F. unit is fed from a high-pass filter, this having a similar rate of attenuation below the crossover frequency.

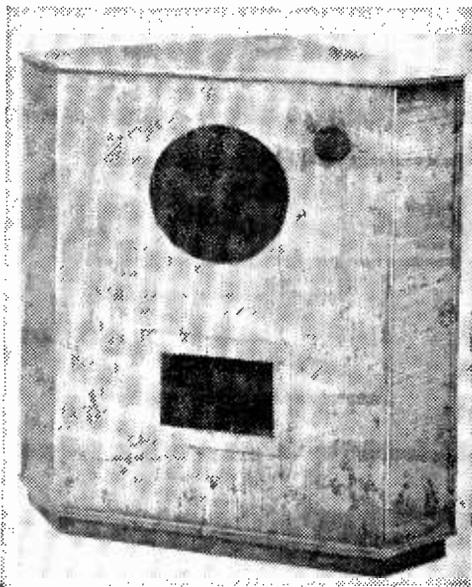The input impedance of the crossover network is 15Ω and the matching to the amplifier is not altered at all by the addition of the tweeter, although a slight loss in the total output does occur in the region of the crossover frequency.



Above—The enclosure ready for the finishing touches.
Left—A view inside the cabinet.

A suitable crossover unit (type CX300—series connection) can be obtained from the manufacturers of the loudspeakers. For those who may wish to construct their own networks details are given below.

Paper, or metallised plastic film type capacitors should be used and these should have a voltage rating of 50-100V. Electrolytic capacitors are not suitable. It will be necessary to use capacitors in parallel in order to obtain the values specified.

The coils can be easily constructed by winding 16s.w.g. enamelled wire on a cardboard or plastic former 1 in. diameter and $1\frac{1}{2}$ in. long. Cheeks about $3\frac{1}{2}$ in. diameter should be fitted at either end of the former. The 1.125mH coil requires 210 turns (about 16 layers) and the 0.56mH coil 145 turns (11 layers). All turns must be close wound and the layers even. Terminate the completed coil by passing each end of the wire through a pair of holes in the end cheeks then bringing out about 1 in. of wire to provide the connection.

For convenience the filter components should be assembled on a small wooden panel and, after the wiring has been completed, this can be

mounted on the floor of the cabinet. In order to avoid inductive coupling it is advisable to arrange the two coils so that their axes are at right angles to one another, and to space them about 3 in. apart.


Since there is a 180° phase shift through the crossover network, the two loudspeakers must be connected in what would be normally anti-phase. Correct phasing can be established by reversing the two leads to one loudspeaker speech coil and observing which arrangement gives best sound output.

The Finish

Regarding the finish to the cabinet, use has been made of applied "Vinyl" or "Fablon" to the sides, and wood or plastic veneer to top and edges. This eliminates the necessity of polishing to great extent. The front is covering with approved loudspeaker fabric. It is suggested that the cabinet should be first made up "dry", then dismantled and finally glued up after any needful adjustments have been made.

Start by cutting all the blockboard panels to drawings on the Blueprint,, plane all edges square,

Fig. 3 (right)—An exploded view of the Berkeley.

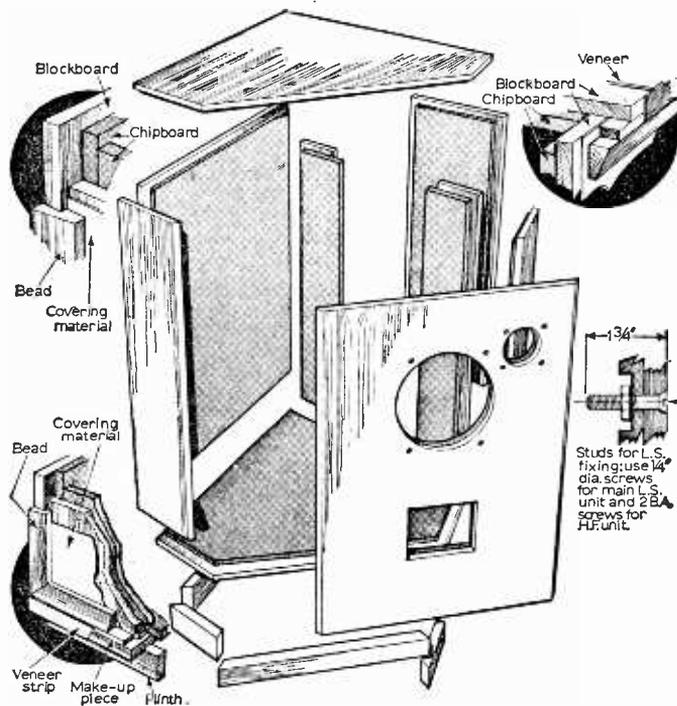

The units undermentioned in this article are manufactured by Whiteley Electrical Radio Company Ltd., Mansfield, Notts., England.

Building the Cabinet

The construction of this corner cabinet is quite simple, complicated joints being eliminated entirely. A little care and attention to planing edges square and true will be well repaid when finally assembling.

Two types of board are used, both of half an inch thickness. The inside is of chipboard (Weyroc) and the outer of blockboard or laminated blockboard. This latter material is a superior board and is well worth the extra expense. Owing to the acoustic requirements regarding cubic volume of the inside of the cabinet it will be found that a 9ft. x 4ft. board of each material will be needed. Stock sized boards are usually 8ft. x 4ft., so enquiries should be made concerning the availability of material of suitable size.

and where required at 45°. Gauge a line to mark the boundary of the chipboard all around the inside face of each panel. Care must be taken to get these marks the right distance in from the edges. They vary, due to the overlapping.

Now cut the chipboard panels to fit the markings and screw each pair together with 3/8 in. x No. 8 csk. screws at 1ft. centres. Having proceeded this far all sections should correspond to details on the Blueprint. Assemble the cabinet by drawing through the edges of the blockboard with 1 in. x No. 6 csk. screws, making any adjustments to the meeting, rabbeted edges, etc.


Glueing

Having checked for squareness and tight joints, dismantle and glue and screw the respective panel sections together. These should be placed one on top of each other on a flat surface and weighted on top. Leave for a day to thoroughly set. This

(Continued on page 749)

transistor tuner- receiver

By A. Sydenham

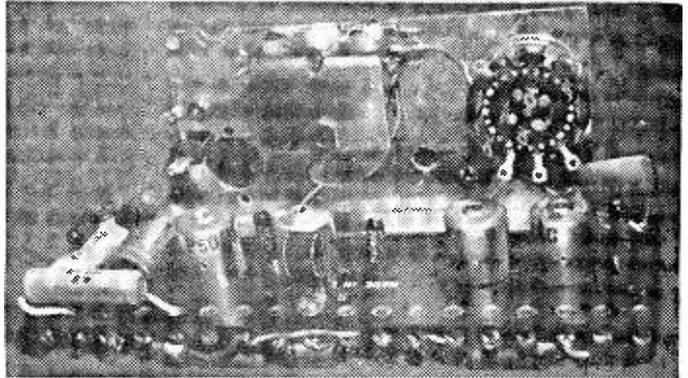

DESPITE many criticisms of transistorised receivers one must acknowledge the high sensitivity of the superhet form—the distinction immediately being drawn between it and the TRF configuration.

A simple TRF receiver employing regeneration might perform well enough in an area of high signal strength but when used under less favourable conditions cause disappointment due to the low reserve of gain and limited tuned circuits.

The superhet holds pride of place for reliability, stability, sensitivity and general performance and no TRF receiver can be made to equal it without becoming equally expensive. Beginners in particular are well advised to realise this for it is easy to become misled.

Criticism of the audio quality emitted by transistor receivers and which is often considered inadequate for home use, is, however, frequently justified and is the price that must be paid for

using small loudspeakers in small cabinets driven by Class B output stages from depreciating batteries.

But listening to a radio programme on a mains powered A.M. receiver—where good quality audio is available—is, in many areas, rather unsatisfactory, due to the characteristic whistle caused by neighbouring TV receivers and/or the sundry bangs and pops due to radiated interference.

It is an interesting project therefore to construct a transistor superhet tuner—which can be kept physically small—and feed its output to a good quality amplifier or, alternatively, to the “Gram” sockets of a suitable receiver. In this way much of the radiated interference is avoided for no external aerial is needed and at the same time an adequate reserve of audio gain becomes available.

Details of a suitable tuner are presented here of a model recently constructed. When fed to the input sockets of a 10W mains powered audio amplifier similar to the “5-10” the unit gave an excellent performance equalling that of the 2-valve superhet tuner it displaced. The quality obtained being considered superior to that of the model using

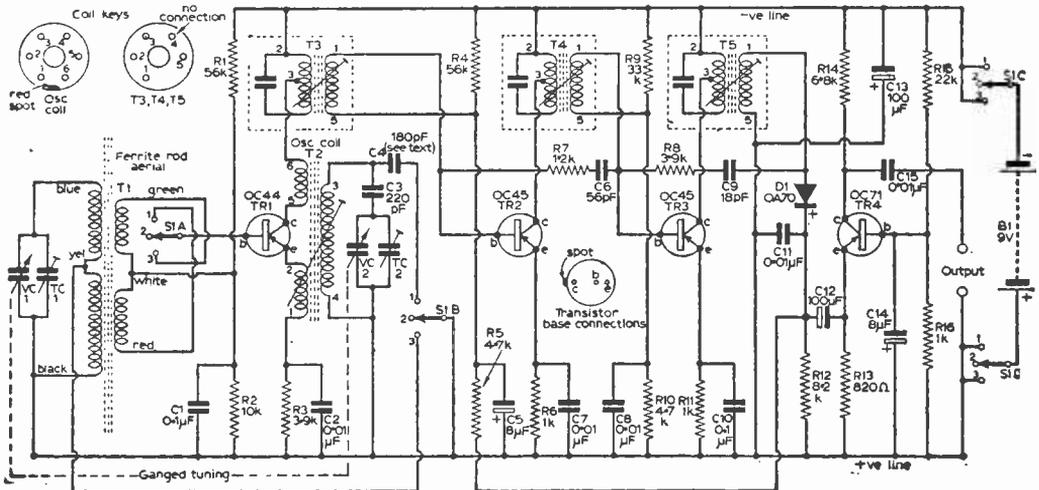


Fig. 1—Circuit diagram of the transistor tuner-receiver.

valves—which also had to have an aerial connected.

The unit has also been tested in connection with the "Gram" sockets of a standard broadcast receiver and it was further proved that the unit could be used as a complete headphone, or personal, receiver if so desired.

The Circuit

This is on conventional lines, reliability being the aim—see Fig. 1. No claims to originality are made; the circuitry is familiar and easily recognised. Practical problems arise, however, in converting a circuit diagram to a working model and a good layout is not always easily obtained. Here the difficulty is resolved.

Both the medium and long wavebands are covered, the switching being arranged so as to minimise the chance of the unit being left switched on accidentally. A standard 3-way, 4-pole rotary switch is employed: S1A and S1B selecting the waveband coverage, and the other two sections performing on/off duties and ensuring that the battery is completely disconnected at position "2". The central switch position is "off"; it is thus impossible to change from one band to the other without going through the "off" position.

TR1 (OC44) functions as the frequency changer with TR2 and TR3 (OC45) as intermediate frequency amplifiers. Following the demodulator diode, D1, is an additional transistor, TR4 (OC71) which is used to drive the subsequent amplifier. The average emitter current of TR4 is 400µA and the whole tuner consumes less than 4mA, thus making battery replacement only a minor problem.

If higher gain is required TR4 may be operated under common emitter conditions but the output impedance will be lowered to approximately 5kΩ. The necessary rearrangement of the stage is shown in Fig. 2 and if the unit is to be used as a headphone receiver this is the best method to adopt.

A minor economy can then also be effected by omitting the 5.6kΩ collector resistor together with the output capacitor connecting instead high impedance phones between the negative rail and TR4 collector. It might also become necessary to experiment slightly with the 100kΩ base feed resistor to obtain optimum results.

If the circuit of Fig. 2 is used to feed a valve amplifier it might also become necessary to vary the value of the upper base feed resistor, 100kΩ, since the collector resistor is, as specified, a little

on the high side. Only a small emitter current is required — about 0.5mA.

Referring again to Fig. 1 it will be noted that all transistors are stabilised by the familiar potentiometer, emitter resistor form, and this together with the neutralising circuitry makes the unit completely stable.

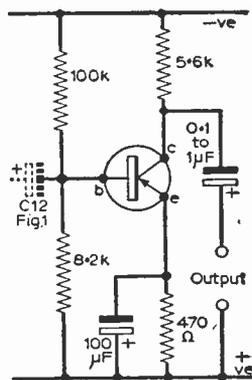


Fig. 2—Alternative circuit for Tr4 in common-emitter mode.

Mechanical Details

The whole tuner is constructed on a standard 18-way tag-board, the tags having been given imaginary numbers to assist correct identification. Although the appropriate figures can be marked on to the board it will usually be sufficient to locate No. 1 and No. 19 and count from there as required.

The oscillator coil and the three I.F. transformers are mounted so that their pins project through the tag side of the board and although a separate hole may be drilled for each pin it is generally simpler to use a single hole—just large enough for all the pins to pass through together—for each component. This also makes the cores available from either end of the can. An array of small holes lies along the centre of the tag-board when it is purchased and it is only necessary to enlarge as required.

Panel

The wavechange switch, twin gang tuning capacitor and outlet insulator are mounted on a metal panel affixed to the tag-board in such a way that the tags come at the bottom as may be seen in the appropriate illustration. For dimensions of metal this panel see Fig. 4. Because it is made of metal the ¼in. fixing holes must be arranged to coincide with tags 3 and 11 on the board as shown and

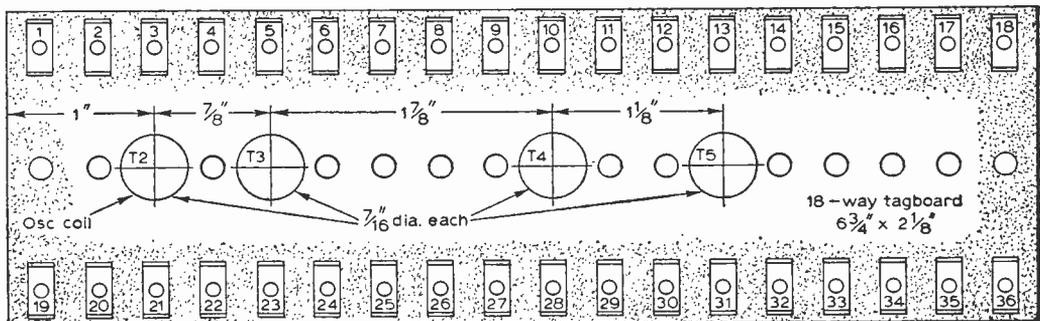


Fig. 3—Drilling details for the component tag board.

prior to bolting it in position $\frac{1}{8}$ in. thick paxolin washers must be placed over the bolts before they are passed through the board to prevent the underside of the "L" from short circuiting all the tag eyelets it hides.

A very simple bracket will also be needed to hold the ferrite aerial (which should be left to one side at this stage) and this will be bolted to tag 28 on the same side as the panel.


Constructional Notes

Actual wiring construction should commence by fixing the canned transformers by letting their fixing lugs pass through small holes drilled for them. Care should be taken to check that the orientation agrees with that shown. These lugs are then pressed out flat and soldered as shown in Fig. 5.

Before proceeding further it is advisable to plug each core hole on the transformers with sleeving or something similar to prevent any blobs of solder accidentally spilling in and locking the cores which are rather fragile.

The remainder of the tag side of the board can then be wired as indicated in Fig. 5. The transistors should be left until last. Check that electrolytic capacitor C12 and diode D1 are connected in the correct sense as shown. The taut layout allows for all component lead-out wires to be snipped off short.

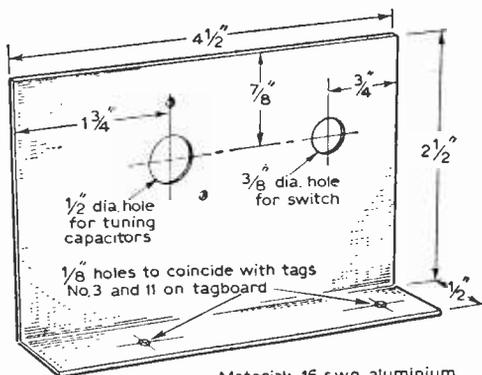When wiring of the tag side of the board is complete (except for the transistors) the other side can be tackled and all wiring is illustrated in Fig. 6 where the panel is shown pressed out flat for



Material: 16 s.w.g. aluminium

Fig. 4—Drilling details of wavechange switch panel.

clarity. C13 actually lies flush with the top of the board and must be slender enough not to foul the aerial (see illustration).

When the capacitors are in position—observe polarities—the transistor wires may be sleeved and passed through existing small holes on the board. Provided thin sleeving has been used the set of leads on each transistor will fit firmly yet not overtightly. The transistor shells thus remain on the top side of the board whilst their wires pass below and are soldered using the normal techniques.

The aerial may now be fixed in position as shown and wired allowing the connecting leads

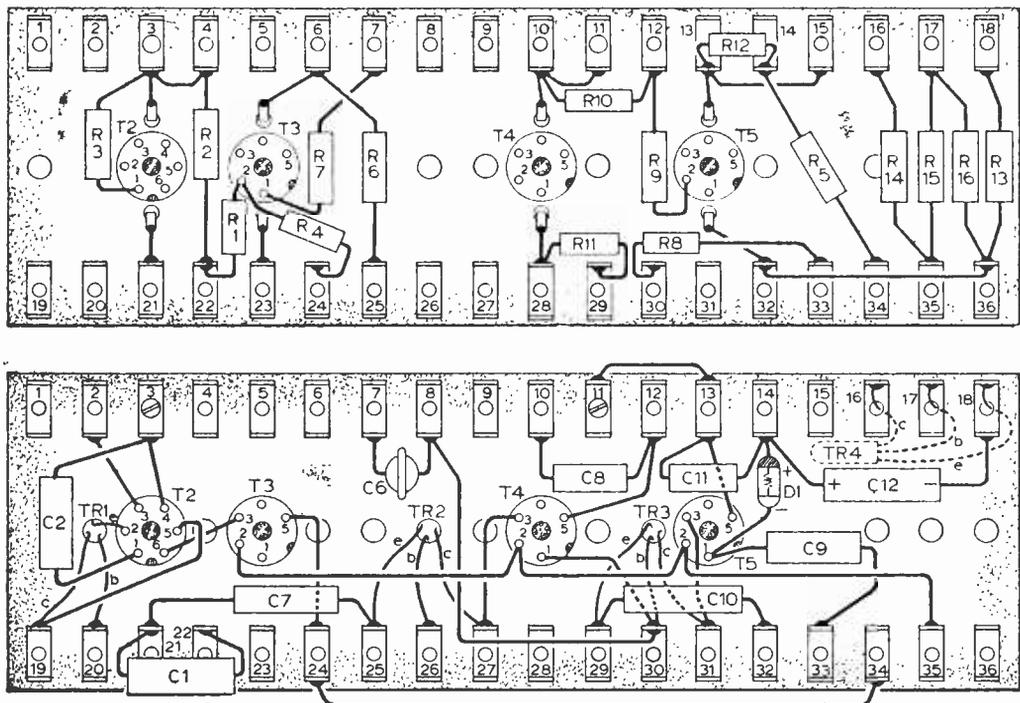


Fig. 5—(a) Details of fixing transformer lugs. (b) Details of tag board wiring.

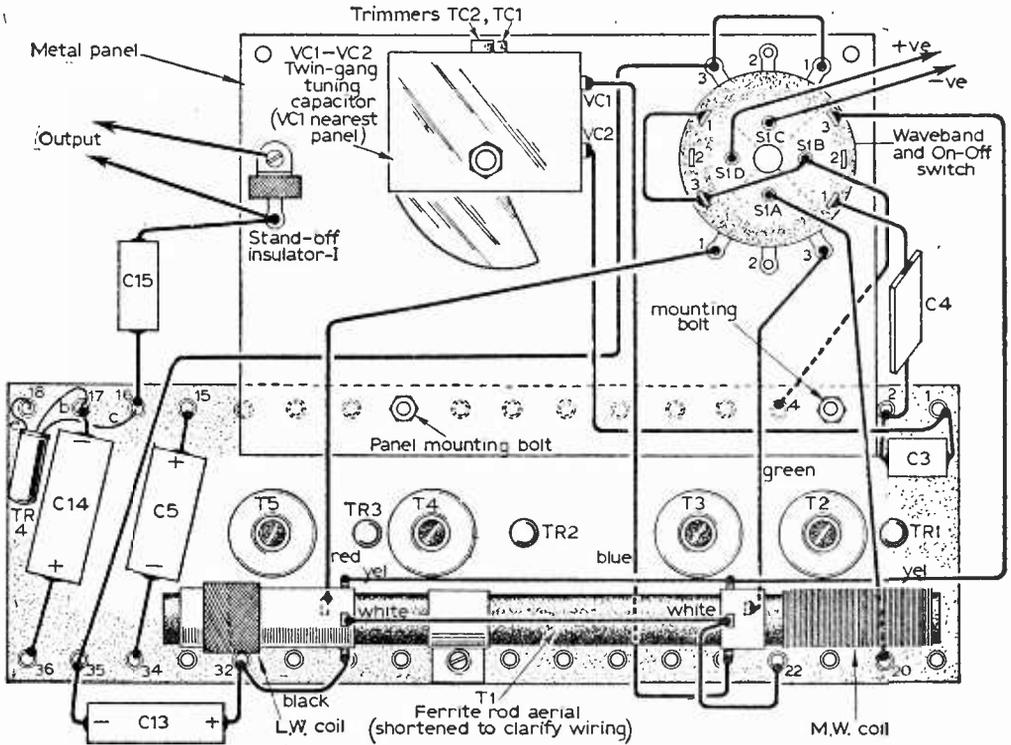


Fig. 6—Wiring diagram for top side of the tag board.

(which should be of stranded conductor) just loose enough to permit free movement of the two coils along the ferrite rod.

The Switch

Each of the four central "pole" tags control three of the "way" tags disposed around the rim of the switch and visual check is initially required to identify them correctly. It is then advisable to press flat alternate "way" sections as shown to obviate incorrect connections being made. If the battery flex leads are left until all the wiring has been checked over chances of damaging the transistors will be minimised.

When satisfied that all is well a black flexible lead approximately 6in. long is soldered to S1C rotor and a similar, but red, lead connected to S1D rotor. The switch should then be set to position "2", the central position, and the appropriate stud connectors affixed to the free ends of the flexible leads which may then be twisted together neatly.

Setting Up

A length of suitable cable (coaxial will do if not very long) should be connected to the stand-off insulator "1" (Fig. 6) the far ends being equipped suitably and connected to an amplifier or to the "Gram" sockets of a suitable broadcast receiver which may then be switched on and adjusted to normal three-quarter volume level setting. Alternatively high impedance phones may be used.

Control knobs are then fitted to the tuner spindles and a battery connected. The rotary switch should then be turned to position "3" (M.W.) and the vanes of the ganged tuning capacitor fully enmeshed.

The modulated output from a signal generator tuned to 470 kc/s is now applied to the fixed vanes connection of VC1. The cores of T5, T4 and T3 should be adjusted for maximum output in that order, the generator output being kept at a low level.

Next the generator is set to 600kc/s and the oscillator coil core adjusted to receive the signal which is then further strengthened by sliding the medium-wave coil along the ferrite rod until best results are obtained.

If the ganged capacitor is now rotated towards the other end of its travel the note should reappear again at 1.200kc/s. before the vanes are fully disengaged, to which frequency the generator may now be set before the aerial and oscillator trimmers TC1 and TC2 respectively, are carefully adjusted for best results.

Should the aerial trimmer need to be set fully home and the signal is still not considered correctly peaked then unscrew the oscillator trimmer slightly until the signal disappears. Now adjust VC1 to slightly fuller capacity when the signal will reappear; it should now be necessary to unscrew the aerial trimmer TC1 slightly to obtain a peaking point. The adjustments should then be made

all over again, viz at 600kc/s and 1,200kc/s, until no improvement is possible.

The Long-wave Band

The rotary switch is next turned to position "1" and an attempt made at receiving the Light programme on 200kc/s with the vanes of VC1 approximately one-half enmeshed. It is quite possible that C4 will need padding a little and is located in such a way as to be easily accessible for this purpose. Values as small as 30pF connected in parallel make a good deal of difference. Experiment by temporarily connecting various small value capacitors (50-150pF) across VC2 in

turn at the same time swinging the vanes over full travel.

Another quick method is to connect a 90pF trimmer across VC2 temporarily. Immediately the signal is received the long-wave coil should be slid gently along the ferrite rod to obtain best results in association with VC1, and an assessment made of the precise value of capacitance needed for C4.

Warning

The unit must not be used under any circumstances in connection with a receiver or amplifier of the A.C./D.C. class nor with a so called A.C. receiver that derives its H.T. from the mains direct. It may be used with a transistorised amplifier, however, if required.

Comparable results are not likely to be obtained if alternative components, or transistors of another make, are utilised; the use of any sub-standard items is almost certain to ensure disappointment.

Cabinet

Dimensions of a suitable easily made cabinet constructed are shown in Fig. 7. It is made from hardboard held together with internally glued reinforcement strips, little weight being involved.

COMPONENT LIST

Resistors

(All 10%, 1/4W carbon unless otherwise stated):

- | | |
|------------|----------|
| R1 56k | R9 33k |
| R2 10k | R10 4.7k |
| R3 3.9k | R11 1k |
| R4 56k | R12 8.2k |
| R5 4.7k | R13 820 |
| R6 1k | R14 6.8k |
| R7 1.2k 5% | R15 22k |
| R8 3.9k 5% | R16 1k |

Capacitors:

- C1 0.1µF paper
- C2 0.01µF ceramic or paper
- C3 220pF mica
- C4 180pF mica (see text)
- C5 8µF electrolytic 6V
- C6 56pF 1% mica
- C7 0.01µF ceramic or paper
- C8 0.01µF ceramic or paper
- C9 18pF 1% mica
- C10 0.1µF paper
- C11 0.01µF ceramic or paper
- C12 100µF electrolytic 12V
- C13 100µF electrolytic 12V
- C14 8µF electrolytic 6V
- C15 0.01µF ceramic or paper
- VC1 } 208 x 176pF twin gang, with trimmers,
- VC2 } Jackson 'OO'.
- TC1 } see VC1, VC2
- TC2 }

Inductors:

- | | | |
|--------------------------|-------|------------------|
| T1 Ferrite aerial, MW/LW | RA2W | } Weymouth Range |
| T2 Oscillator coil | P50/1 | |
| T3 IF coils 470 kc/s | P50/2 | |
| T4 IF coils 470 kc/s | P50/2 | |
| T5 IF coils 470 kc/s | P50/3 | |

Transistors:

- | | | |
|---------|-------------------|--------------------|
| Mullard | TR1 — OC44 White | } RFG3 Pack or Set |
| | TR2 — OC45 Orange | |
| | TR3 — OC45 Blue | |
| | TR4 — OC71 | |
| | DI — OA70 | |

Switch:

S1 Miniature rotary, single wafer, 4-pole, 3-way.

Battery:

B1 PP4, or as suitable, plus stud connectors.

Miscellaneous:

Tagboard: 18-way 6 3/8 x 2 1/4 in. (Radiospares).
Panel material (aluminium), two knobs, hardboard, quadrant beading, stand-off insulator, wire, solder, etc., etc.

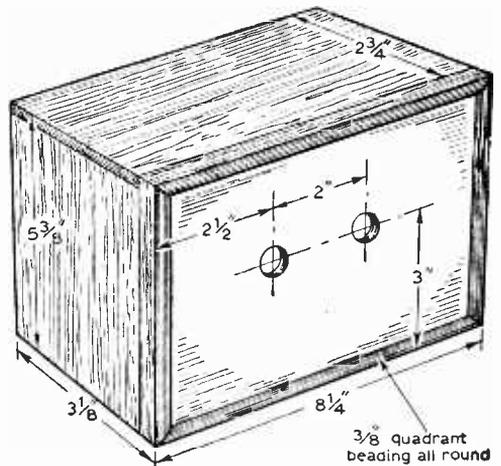


Fig. 7—Dimensions of suggested cabinet.

To avoid defacing the cabinet front the tuner can be locked by creating a sub-panel of hardboard through which four 4B.A. bolts may be passed and countersunk to coincide with holes in the metal tuner panel. This sub-panel can then be glued—with the bolts projecting—to the inside of the cabinet. When dry the tuner is placed in position and the four 4B.A. nuts applied and screwed home.

The actual cabinet front is cut 1/4 in. smaller than the dimensions given in Fig. 7, a frame of 1/4 in. quadrant beading being allowed to overlap by 1/4 in. all round to form a rebate for the sides, top, etc.

As mentioned earlier the unit can be used as a completely self-contained headphone receiver if required and in this case a phone outlet can be provided on the panel.

LASKY'S RADIO

"BUILD-YOURSELF" TRANSISTOR RADIOS

The "REALISTIC" Seven

STAR FEATURES ★★★★★

- ★ 7 Transistor Superhet. 350 Milliwatt output into 4-inch high flux speaker.
- ★ All components mounted on a single printed circuit board, size 5 1/2 x 5 1/2 in. in one complete assembly.
- ★ Plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2 in. in choice of colours:
- ★ Red/Grey, Blue/Grey, all Grey.
- ★ Easy to read Dial.
- ★ External Socket for car aerial.
- ★ I.F. frequency 470 K/c/s.
- ★ Ferrite Rod internal aerial.
- ★ Operates from PP9 or similar battery.
- ★ Full comprehensive data supplied with each Receiver.
- ★ All coils and IF's, etc., fully wound ready for immediate assembly.

The finest receiver at present available for home construction. Fully tunable long and medium wavebands. Uses 7 Mullard Transistors: OC44, 2 OC46's, OC71, OC81D and 2 OC61's, plus Crystal Diode OA70.



An Outstanding Receiver. Lasky's Price for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data. **£6.19.6** Postage and Packing 4/6 Battery 3/9 (included free with complete parcel). Data and instructions separately 2/6, refunded if you purchase the parcel.

The New "ALBERTA 5" Mk. 11 Now using printed circuit and supplied with miniature earphones for personal listening at no extra cost. Push-pull, 200 milliwatts output. Five Transistors and one diode, 2 1/2 in. moving coil speaker, ferrite rod aerial, and long wave. Smart plastic Case, 4 1/2 x 3 1/2 in. overall.



CAN BE BUILT FOR **59/6** Post 3/8 All components available separately. Full details, circuit diagram, 1/6 post free.

TELEFUNKEN STEREO HI-FI AMPLIFIERS £5.19.6

Further Great Purchase Enables us to Offer this Excellent Unit at **£5.19.6**. Post 7/6.

A complete stereo amplifier of unsurpassed quality, with inputs for radio, tape recorder, P.M. tuner or any other hi-fi source, either monaural or stereo. Output power 5 watts total (2 1/2 watts each channel). New and unused, listed at 16 Gns.



REMOTE CONTROL UNITS Comprising ON/OFF switch, BRIGHTNESS and VOLUME Controls. Controls recessed into smart grey plastic case, fitted with 15 feet of 7 way multi cable in grey P.V.C. Listed at £2.2.0. LASKY'S PRICE 9/6, a fraction of list price.

KAPURA Model U1 Multi-Test Meters

- ★ Complete with test leads.
- ★ Brand new, fully guaranteed.
- Sensitivity: 1,000 ohms per volt A.C. and D.C.
- Ranges: (A.C. and D.C.) 0-15-50-250-500-1,000 v. D.C. current 0-100-500 mA, 0-1 mA (used at 0-10 v. range).
- Resistance: 1-2,000 ohms (centre 24 ohms), 100-200,000 ohms (centre 2.4k).
- Size: 5in. x 3 1/2 in. x 2 1/2 in.



LASKY'S PRICE **39/6** Carriage and Packing 5/-

TV TURRET TUNERS

By famous manufacturer, I.F. 33-38 Mc/s., FCC84 and PFC80 valves fitted, also 12 sets of coils. Lasky's Price Complete with Valves and Coils 29/6. Postage 2/6.

Distler Miniature Motors

6 volt battery operated 7/11. P. & P. 2/6.

CRYSTAL PICK-UP CARTRIDGES

Lowest Prices Ever! All complete with Stylus, L.P. and Standard (and Stereo where shown). Fully guaranteed, standard mtng, will fit most P.U. arms and heads. Postage 1/- each extra

MONO	
TYPE C.T.1. By well known manufacturer. With 2 sapphire styli	12/6
Garrard GC.2	15/-
Ronette Studio O	15/-
Acos GP.65/3	15/-
Acos GP.65/1	17/-
Acos GP.67/1	17/-
Acos GP.61/1	18/-
STEREO	
Acostereo 73/1 with 2 sapphires	25/-
Acostereo 73/2 with Diamond, L.P./Stereo and sapphire Std.	29/6
Collaro type C. Turnover, with 2 sapphires	25/6
Collar S.C.I. Turnover with 2 sapphires	24/6
Collar S.C.I. Turnover, with Diamond L.P./Stereo and sapphire Std.	29/6
Ronette Stereo O.V. Turnover, with 2 sapphires	29/6
Ronette Stereo type 105, with 2 sapphires	35/6
Ronette Stereo type 105, with Diamond L.P./Stereo and sapphire Std.	39/6

THE BETA TWO

A 2-transistor plus 2-diode personal receiver for home construction. Uses printed circuits and ferrite rod aerial. Personal earphone gives clear reception for private listening. Tunes over full medium waveband. Uses same cabinet as our Alberta 5 receiver, illustrated above. Size 5 1/2 x 3 1/2 x 4 1/2 in. overall. All components available separately. CAN BE BUILT FOR **21/-** Postage 2s. 6d. extra including personal earphone, cabinet, etc. Circuit diagram and step by step instructions 1s. 6d. (Free with parcel.)

TRANSTRONIC CONSTRUCTION KIT

Make your own transistorised transmitter and receiver. With components supplied, you can build 7 different circuits. Full size wiring diagrams for mounting on peg board 15 x 9 in. supplied. Two transistors OC44 and OC72, 1 XTAL Diode. No soldering necessary. IDEAL GIFT FOR YOUNGSTERS All components marked for absolute simplicity, attractively packed in multi-coloured gift box. 15-page instruction booklet. Originally intended to retail at £5.48. LASKY'S SPECIAL OFFER **49/6** complete P. & P. 4/6 Money refunded if dissatisfied

THE VERY LATEST "PHONOTRIX" TRANSISTOR BATTERY TAPE RECORDER



Supplied in Real Leather Carrying Case, with Shoulder Strap (not illustrated). Capstan drive, push-button controls. Constant speed 3 1/2 r.p.s., uses 3in. spool. High impact plastic case with leather outer case. Size: 9 1/2 x 5 x 3 1/2 in. List 25 gns.

LASKY'S PRICE **18 Gns.** with Mike and Tape. Carr. 7/6.

Electric Motors

Brand New Single-phase motors, suitable for tape recorders, workshops, etc. Many uses. Reversible 200-250v. 5in. oz torque, 1,400 r.p.m. Weight 4 1/2 lb., length 5in. Spindle both ends 1 x 4in.; 2 x 1/2 in. Price, including capacitor, 19/11. P. & P. 3/6 ex.


BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P. W. Edgware Road.

207 EDGWARE ROAD, LONDON, W.2. Near Praed St. PADDINGTON 3271/2.

33 TOTTENHAM COURT ROAD, W.1. Nearest Stn. Goodle St. MUSEUM 2605

A Radio Astronomy Receiver

for the Advanced Constructor

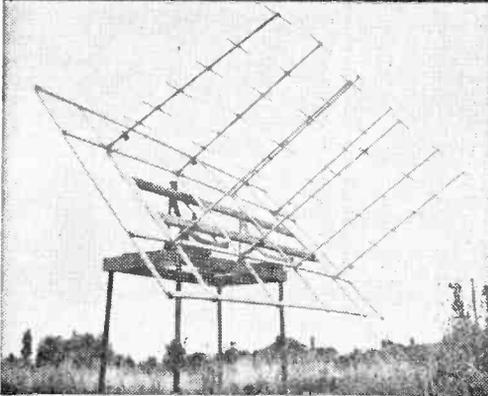

Following upon the great success of the Radio Astronomy series by Frank W. Hyde F.R.S.A., F.R.A.S., we are publishing a further short series by the same author; commencing in December with an article describing a Radio Astronomy Receiver suitable for the advanced constructor.

● In the same issue, for the beginner, we continue "Understanding Radio."

THE **Radio Constructor**

PUBLISHED DECEMBER 1, 1962, PRICE TWO SHILLINGS
DATA PUBLICATIONS LTD., 57 MAIDA VALE,
LONDON W.9.

ADCOLA
PRODUCTS LIMITED
(Incorporated in Great Britain)


SOLDERING INSTRUMENTS

EQUIPMENT FOR THE RADIO AMATEUR

ILLUSTRATED

List 64.
 $\frac{3}{16}$ DETACHABLE BIT
IN
PROTECTIVE SHIELD
List 700

BRIT. & FOR. PATS.

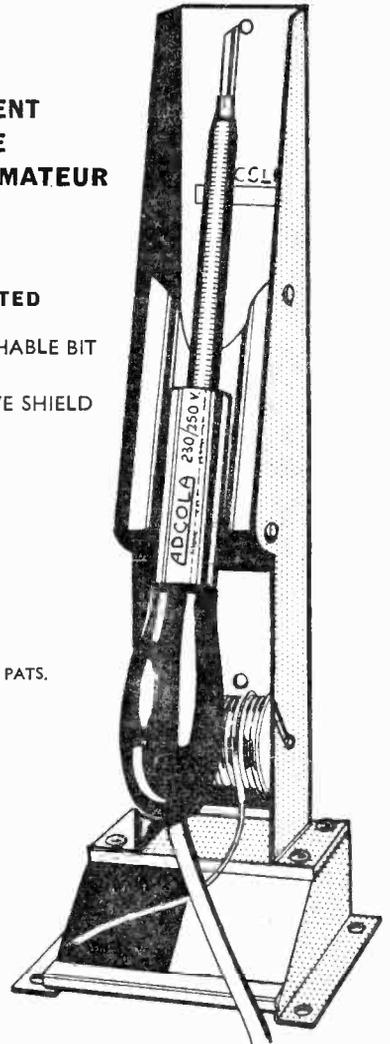

Sales & Service

APPLY DIRECT FOR CATALOGUE
TO

ADCOLA PRODUCTS LTD
ADCOLA HOUSE

GAUDEN ROAD, LONDON, S.W.4

Telephones MACaulay 4272 & 3101 Telegrams SOLJOINT LONDON SW4

Central Control Amplifier

By E. McLoughlin

A MASTER CONTROL UNIT FOR AN AUDIO INSTALLATION

(Continued from page 630 of the November issue)

IT must be stressed that voltages from the power supplies *must* be up to the full specified values. *Slight* deficiencies were found to produce immediate *huge* reductions in power in the prototype in both amplifiers, leading to inferior performance. If the H.T. is down by only 50V below specified value there is almost 40% power loss from the EL84. If the L.T. D.C. supply is down by only 1V at the points shown in the circuits, below the specified values, the available output power can be halved!

But do not use voltages in excess of those specified. Excesses (or deficiencies) can be cured to some extent by changing tappings on the mains transformer primaries (but watch the valve heater voltage!) or by altering the values of reservoir or smoothing capacitors or by using suitable droppers. The power unit *must* be trimmed to the specified voltages, using appropriate measures with the particular power supply components obtained. Rule-of-thumb methods using any old lash-up are here particularly likely to lead to such poor results as to make the whole unit rather disappointingly weak.

Inputs

The amplifier input is switched at will to "Laboratory" or "Line" by means of S4 (Fig. 2). In the position "Line" any signal on the line from apparatus at other stations can be fed into the amplifier and listened to in the laboratory/den on the internal loudspeaker in this unit provided that S3 is set to position "receive". In this position S3 breaks the mains feed to the L.T. power-pack on contacts A, breaks the base-drive on contacts B (so that the transistors are not damaged by receiving base-drive without emitter-collector voltage), breaks the connection of T5 to the line on contacts C (so that other signals are not fully or partially shorted, as explained above) and, finally, on contacts D, switches the incoming signals on the line through to R2 and R7 and hence to the amplifier input.

In the position "Laboratory" on S4 the amplifier input is connected to both of two sources within the laboratory simultaneously via the

decoupling and impedance-transforming resistance network R3, 4, 5, 6. This network assures that both sources transfer virtually all of their signal voltage into the amplifier, but negligible amounts mutually to each other. Which of the sources actually feeds the amplifier then must be decided simply by switching the desired source on and the others off at their own switches. If both are on they will mix in the amplifier without otherwise interfering with each other.

Now, with S4 in the position "Laboratory", S3 may be at either position. The position "Receive" is then used as a "dummy" if the signal is merely to be listened to on the internal loudspeaker, confining it to the laboratory (e.g., when using the oscilloscope/signal tracer source for internal work in the laboratory—see below—and possibly somebody else in the flat or house has other apparatus feeding other signals on to the rest of the line). Such other signals on the line will, of course, not then be actually received until S4 is also switched to "Line".

If the signals from a laboratory source (S4 at position "Laboratory") are now required to be sent on to the whole line—with suppression of any other signals possibly present—then S3 is switched over to "Send". This switches mains on for the L.T. power-pack and connects the transistor amplifier input and output appropriately, also shorting R2 to prevent any possibility of instability.

The combination S3 at "Send" and S4 at "Line" serves no useful purpose, neither does any damage nor causes instability.

The internal loudspeaker can be switched on or off independently. If S3 is at "Send" and all loudspeakers in the system are of the same type the volume on the internal loudspeaker is a true replica of the volume on any other loudspeaker on the line when the series-resistors used as individual local volume controls on the line loudspeakers are cut out of circuit (maximum volume).

Mains/Distribution/Power Supplies

The unit described in this article contains all its own power supplies, which are built in tier fashion on to one side panel of the cabinet body, details of which will be given later.

Fig. 1 (last month) gives details of the mains distribution wiring. This follows the principles and general scheme sketched in the initial general article. Great care is essential in carrying out this wiring, which should be checked, checked, and rechecked before switching on mains power. Wrong connections or insecure, untidy connections could lead to highly dangerous conditions or to destruction of valuable equipment.

Note carefully the arrangements for the mains isolation transformer. This item is generally too heavy and bulky and has too great a stray magnetic field for inclusion within the cabinet of the present unit. It is thus attached via a four-core mains power cable of suitable length and quality and mounted separately at a suitable safe position in a proper and secure manner. The reasons for requiring this transformer were fully discussed in the introductory article. Take great care not to confuse the connections; errors could lead to dangerous conditions.

Cabinet Construction

This unit is to be considered as a fixed item of electrical installation. As such it will most easily satisfy supply company regulations regarding mains wiring.

If the laboratory/workshop wall is of good dry wood at the location where the unit is to be installed, as was the case for the prototype, then the wall itself may be used directly as the rear of the cabinet, of which sides are formed by wooden slats screwed on internally with angle-iron. The distribution tags and cables can then be screwed directly on to the rear wall, according to the drawings, using appropriate regulation fixtures available in the electrical trade. It is advisable to consult an electrician at the start of the whole

for their valves EF86 and EL84. Ample publication has occurred elsewhere, so that only brief comment on essentials is necessary here.

It is essential to mount the two valveholders such that R13 can be mounted as direct and short between the relevant pins as possible (Fig. 3). Furthermore, R10 must have its wire cut off very short and soldered direct on to pin 6 at the valveholder of V1. Failure to observe these conditions will cause treble-performance loss.

High gain is obtained in V1 by means of the unusually large anode load R10. D.C. coupling via the anti-parasitic R13 to V2 grid avoids one source of low-frequency phase-shift and losses. The positive D.C. thereby fed to V2 grid requires the unusually high cathode bias resistor R16 to

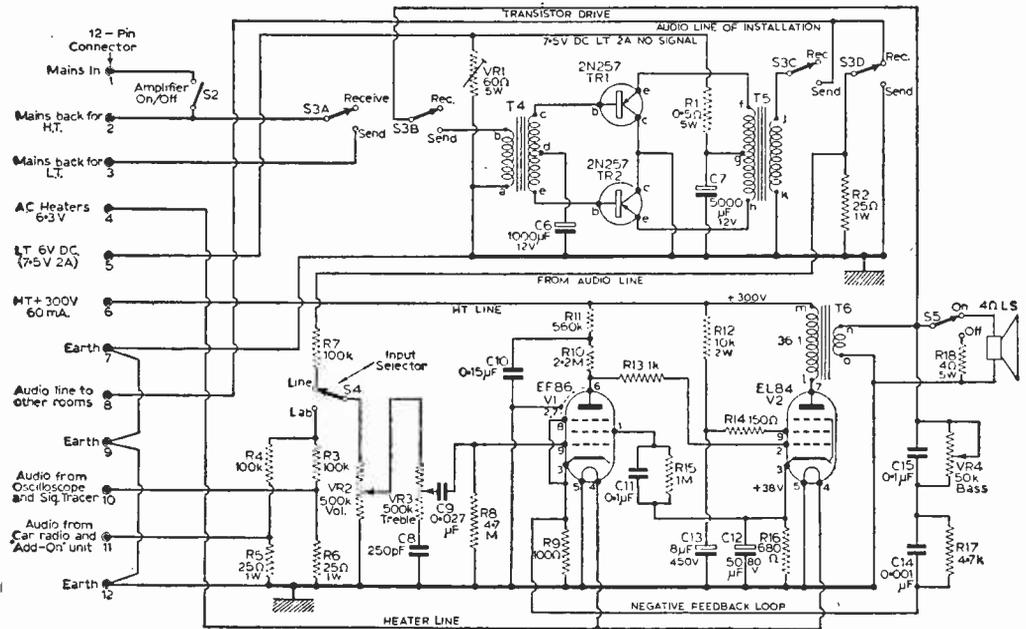


Fig. 2—The circuit of the "lid-unit".

project if one is not conversant with wiring regulations oneself.

The amplifier unit itself is seen, in the drawings and illustrations, to be built in more or less conventional form of construction on to a panel of wood forming the "lid" of the vertical cabinet. A good 12-pin connector, rated at 500V/2A on all pins relative to all other pins, is used to connect the "lid-unit" to the body. This enables rapid removal and replacement for servicing, especially if the take-off hinge and latch type of fixture is adopted.

The Amplifier

This is an excellent "hi-fi" circuit of low expense but fine performance specifically developed by Mullard engineers some time ago

compensate. The value of R16 is critical and a close-tolerance resistor is specified. The cathode voltage resulting for V2 is then sufficient for the screen of V1, which is thus D.C.-coupled to V1 cathode. This also represents D.C.-negative-feedback, which stabilises the operating points of the valves—otherwise such a circuit would drift. C11 is also critical. Too low a capacity causes bass loss, whereas too high a capacity causes pure low-frequency phase-shift oscillation at some or all settings of VR4, especially if inadvertently too high a ratio is used for T6. This oscillation may be of such a pure note and frequency that it can be mistaken for severe mains hum.

If the amplifier howls uncontrollably at full power, whatever settings of the controls are undertaken, reverse connections to the output transformer primary, T6, m and 1.

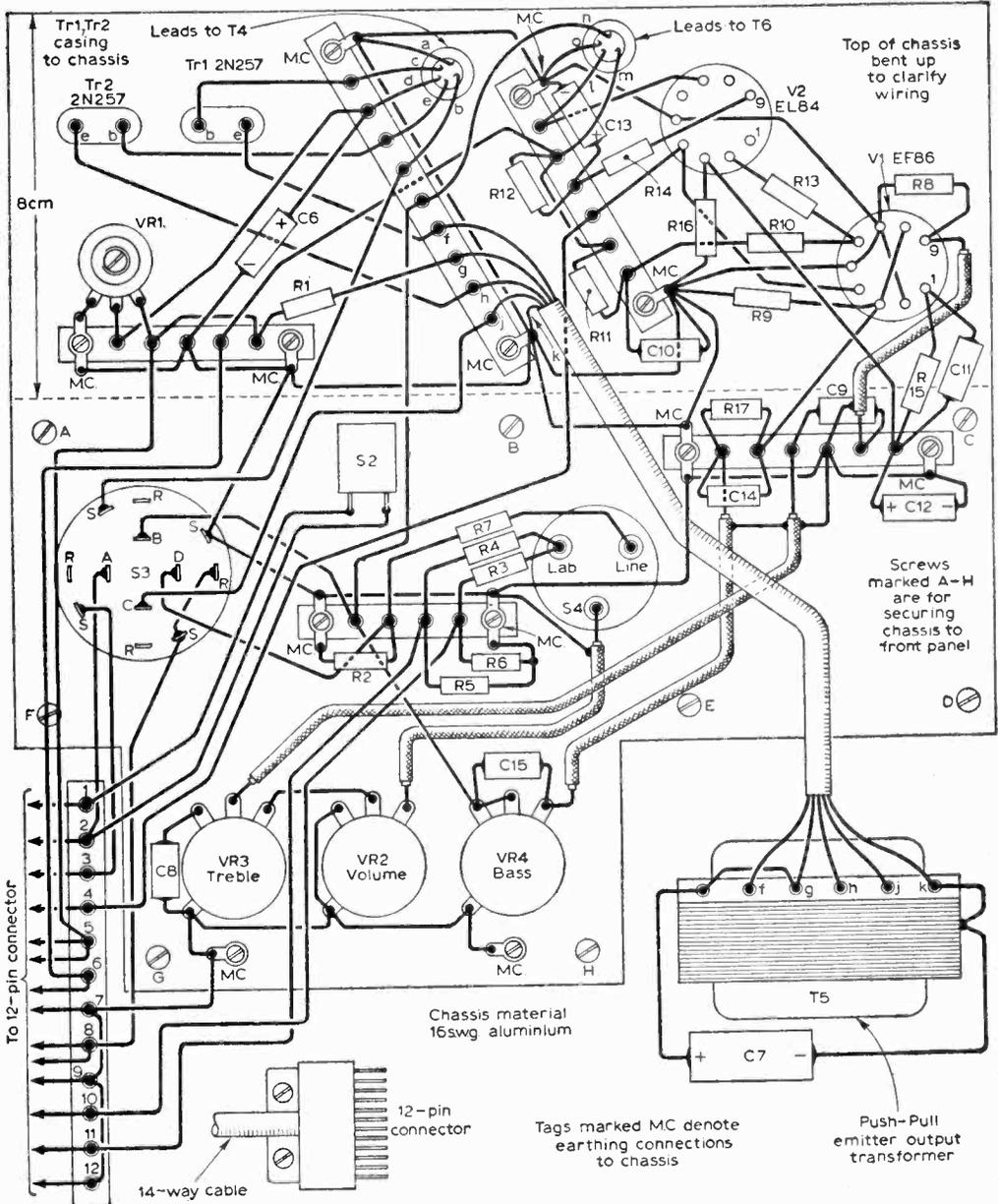


Fig. 3—The "lid-unit" and sub-chassis wiring diagram.

Use low-capacity coaxial cable for the leads shown screened in the wiring diagram, Fig. 3, to avoid treble loss. Note that all screens are bonded together and joined to chassis at only one point. This is highly important as hum is easily introduced if screens are earthed at several points because they can then carry random chassis-currents, which may be partially A.C. Use suitable

sleeving or other measures to prevent the screening from touching the chassis at unwanted points. Note in this connection also the separate earth-busbar for VR2, 3, 4, connected locally to chassis at the earth-feed from the 12-pin plug and *not* connected to the earth-ring-busbar under the amplifier components.

(To be continued)

DX on MEDIUM WAVES

As a change from shortwaves try for some M.W. broadcast band DX this season. This article tells you how.

By S. A. Money

MANY radio enthusiasts will probably be surprised to learn that DX signals from many parts of the world can be heard on the medium wave broadcast band. In the early 1930's many trans-Atlantic stations were heard on quite simple domestic radio sets. With modern receivers it is possible to achieve quite remarkable results despite the great rise in the level of interference since those early days.

During the past two years the writer and a number of other enthusiasts have listened for DX stations on this band. Many stations from both North and South America were regularly heard and others from the more remote parts of Africa and Asia were also logged.

Optimum conditions for long distance reception on the medium waves occur in the winter during the hours of darkness. In the evening reception of DX signals is extremely difficult due to the high level of interference from the very strong European signals. After midnight most of the European stations have closed down and reception of the weaker DX stations is possible. During the summer a high level of "static" noise makes DX reception more difficult and less frequent.

Sunspot activity is well known to have a considerable influence on short wave reception conditions. In the case of medium waves it has been found that the best conditions for DX reception occur during the years around the sunspot minimum. With the next sunspot minimum due to occur around 1963/64 conditions should be excellent for the next few years.

Receivers and Aerials

Under favourable conditions it should be possible to receive the regularly heard North American stations on any good domestic receiver provided that a good aerial system is used.

For serious DX listening a communications type receiver with its high sensitivity and selectivity is almost essential. Ex-Service receivers such as the R1155 have proved to be very good in this respect.

Long wire aerials seem to be the best for DX reception. They should be mounted as high as possible and should be outdoors for the best results. Indoor aerials mounted in the loft or around the picture rail in an upstairs room can give very good results. In order to erect the necessary length of wire it may be necessary to bend it into the form of a square or rectangle. A wire 60 to 90ft long is suitable.

Ferrite rod aerials are not usually sensitive enough for DX reception. A good earth connection is usually needed with domestic radios and will often improve reception on a communications receiver.

North America

Reception from North America usually occurs for a period of from three to five days at a time every two or three weeks, in mid-winter however, the opening may last for as long as two weeks with the exception of one or two poor nights. On many nights there may be heavy "static" interference from thunderstorms over the Atlantic.

Generally reception is possible from just after midnight until about 5 a.m. when interference from local European stations starts to build up, although some trans-Atlantic stations can be heard as late as 7 a.m.

Programmes from North America are for local entertainment and are in English with the exception of a few French-speaking Canadian stations. Identification of stations is fairly easy since they all give their call-signs regularly, often during the breaks for "commercials".

East Coast, U.S.A.

Those stations located in the eastern coastal region of the U.S.A. are the most frequently heard here in Britain. There are no less than 16 radio stations in New York City and of these 14 were known to have been logged in England last winter.

Four of the stations in New York carry the major network programmes. The A.B.C. network broadcasts over station WABC on a frequency of 770kc/s. Further along the band on 880kc/s is WCBS, owned by the Columbia Broadcasting System. Both of these stations are regularly heard at excellent strength. Station WNBC (660kc/s), operated by the N.B.C. network, is not too well received here since its aerial is directed away from Europe. The fourth regularly heard station is WOR on 710kc/s run by R.K.O. and carrying the Mutual Network programme.

Of the independent stations in New York, WHN (1050kc/s), WINS (1010kc/s) and WNEW (1130kc/s) can be heard with very good signals on almost every opening to the U.S.A. These three stations broadcast popular music and newscasts. The New York equivalent to our Third Programme is provided by WQXR on 1560kc/s.

Two stations frequently heard from New York State are WPTR (1540kc/s) at Albany and WKBW (1520kc/s) at Buffalo. Other stations which give good signals from the New England states are WTIC (1080kc/s) Hartford, Conn., WEGP (1390kc/s) Presque Is., Maine, WTOP (1500ks/s) Washington D.C. and WMEX (1510kc/s) at Boston, Mass.

Hill-billy music and songs heard on 1530kc/s will probably be from station WCKY at Cincinnati, Ohio. Pennsylvania state can usually be heard over stations WCAU (1210kc/s) at Philadelphia and KDKA (1020kc/s) at Pittsburgh.

Those stations in the southern states which are near the coast, such as WAVY (1250kc/s) at Portsmouth, Virginia, WBT (1110kc/s) Charlotte, N. Carolina, WCSC (1390kc/s) at Charleston, S. Carolina and WLCY (1380kc/s) at St. Petersburg, Florida, are frequently heard at good strength.

The state of Georgia can sometimes be heard over station WSB in Atlanta which operates on 750kc/s. Some of the other stations which have been logged from time to time are, WHAS at Louisville, Kentucky, on 840kc/s, WSM (650kc/s) at Nashville, Tennessee, and WALA (1410kc/s) at Mobile, Alabama. Most of these stations can be difficult to receive but, with improving band conditions, they should be more frequently logged this coming winter.

Central U.S.A.

What might be considered to be the cream of the DX signals from the United States are those stations located in the central and mid-western states. The nearest and thus most frequently noted stations are WOWO (1190kc/s) Fort Wayne, Ind., WJR (760kc/s) Detroit, Michigan and WCFL (1000kc/s) Chicago, Illinois.

Station KXEL at Waterloo, Iowa can sometimes be heard through WPTR's signal on 1540kc/s and usually peaks up at around 0300 GMT. Another station which is often noted at about this time is KMOX at St. Louis, Missouri operating on 1120kc/s.

Texan stations which have been frequently logged here in Britain are WFAA at Dallas and WOAI at San Antonio using frequencies of 820kc/s and 1200kc/s respectively. Perhaps the most distant U.S. stations noted recently are WCCO (830kc/s) at Minneapolis, Minnesota and KOMA (1520kc/s) at Oklahoma City, Oklahoma.

Reception of these more distant stations does require quite a bit of patience since they are usually weak signals and are often only audible for five to ten minutes at a time.

Canada

The Canadian Broadcasting Corporation, which runs the main network, is a public body similar to the BBC. Station CBA at Sackville, New Brunswick (1070kc/s) is the most consistent of the CBC stations heard in this country. CBA can usually be heard at excellent strength just before midnight whenever the band is open to North America and is useful as an indicator of band conditions.

Other CBC stations which are often heard in England are CBC Montreal (940kc/s), CBI Sydney, N.S. (1140kc/s) and CBE Windsor, Ontario, on 1550kc/s.

Of the independent stations CJON (930kc/s) at St. John's, Newfoundland is usually an excellent signal from midnight and like CBA can be used to indicate the state of the band. Other Canadian stations which usually give good reception are CHNS (960kc/s) Halifax, N.S., CFNB (550kc/s) Fredericton, N.B. and CFCY (630kc/s) Charlottetown, Prince Edward Island.

Generally Canadian signals are not as frequently heard as those from the U.S.A. but reception will normally occur on the same nights as for the U.S.A.

South America

Most of the South American stations broadcast in either Spanish or Portuguese and can usually be heard on any night when the North American stations are not audible. Brazilian stations are the most frequently heard with programmes in the Portuguese language. *Radio Globo* on 1180kc/s, *R. Tupi* on 1280kc/s and *R. Jornal* on 780kc/s are three stations which are usually excellent signals.

Other countries which are frequently logged are Argentina (*Radio Nacional*, 870kc/s), Venezuela (*R. Ondas del Lago* on 1120kc/s) and Uruguay with stations CX6 (650kc/s) and CX14 (810kc/s).

Programmes in English can be heard from *Radio Demarara* (ZFY 760kc/s) in Georgetown British Guiana, which usually gives fair to good reception in the early morning.

Central American stations have been heard from Mexico, Cuba, Jamaica and Trinidad. Generally reception from this area is limited to a short period when the conditions change from the North American area to South America.

For details of these and other South American stations the reader is referred to the *World Radio Handbook* which lists the frequencies, operating times and addresses of nearly every broadcast station in the world.

Asia and Africa

North African stations can usually be heard during the evenings in the winter months and are often stronger signals than the more local European stations.


South Africa has been heard in the early mornings on frequencies of 1268kc/s and 1286kc/s. Other countries logged from Africa have been Kenya, Somalia, Nigeria and Senegal.

Middle East countries such as Syria, Iraq and Iran are best heard during the period of the feast of Ramadan when they operate all night with programmes in Arabic.

Indian, Pakistani and Chinese stations have been heard just after midnight with programmes in their native languages.

The *Voice of America* stations at Okinawa and in the Philippines Islands have been heard in the afternoon on 1140kc/s and 1180kc/s. Reports have been received of the reception in Scotland of stations from the Pacific islands such as Guam and Fiji but so far nothing has been heard from that area by listeners in England.

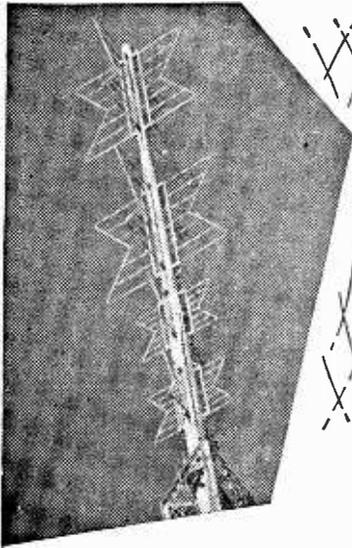The BBC have however, received reports of reception of their Home Service stations in New Zealand so it would seem that reception of Pacific stations in England should be possible if conditions improve as expected. ■



On Your Wavelength

By THERMION

Electronic Organ Keying

SINCE there are now very many different makes of American electronic organs available in this country, a study of some of the techniques involved is very interesting, and although no all-transistor instruments appear to have arrived there are many interesting features to be seen which have hitherto not been used in any English designs.

One of the sections which has always interested me is that concerned with the keying of the instrument, not only from the electrical, but from the actual mechanical point of view. As most of my readers know, the depression of a key actuates some form of electrical contact; in its simplest form two metallic points being brought into contact, or opened, and in its most complicated form, 10 or more contacts being operated, all being opened or closed, or various combinations of them being operated.

Many organs suffer from defects in this part of the instrument, the contacts being very prone to oxidation or the action of dust or fluff, and it is interesting to note the various methods of overcoming these defects.

The use of mixed metals for the contacts, or the introduction of some form of wiping or slight scraping action are well known, but the most interesting is, I think, that employed by the Baldwin Company, where a printed circuit resistance element is so arranged that when a key is operated a spring strip is lowered and travels across the resistance element, thereby gradually cutting it out of circuit.

In addition to getting rid of the difficulties of dirt, corrosion, etc., this also gives a gradual attack effect, and results in the note being sounded in a similar manner to a standard pipe instrument, but I still feel that there are better ways of doing the job.

Any Ideas?

Again, I wonder if any of my readers have spent any time on this aspect and have any ideas of their own they would like to air. Incidentally, the use of the scheme mentioned above does not restrict the instrument to sounding a single note, as the resistance elements can be stacked and practically any number can be operated by a single key.

Of course, the difficulties of suggesting or designing a keying system are restricted, as keys may be of two types, balanced or rear-hung, and thus the contact mechanism must be in the front of the instrument or at the rear, and may present difficulties in accommodating the mechanism.

A Salvage Tip

I know that many of my readers are interested in hints and tips such as are accumulated by the keen serviceman, and I am always anxious to pass on anything which is really worth while. I was recently shown a tip which, although originally used to salvage a valve, is also applicable to transistors. Here it is.

In the case of the valve it relates to the older type with a top cap, which often becomes loose and eventually pulls away leaving the merest piece of wire projecting from the glass. In the case of the transistor, a wire may break and leave a similar short stub of wire projecting. In both cases, the application of a soldering iron being impracticable.

The hint is to obtain a two or three inch length of suitable replacement wire, and to tin one end and then carefully to add solder to this end, holding it end downwards so that a fairly large "blob" of solder is formed.

Now hold the piece of wire at its opposite end in a pair of pliers and lower the "blob" end until it nearly touches the protruding end of the wire you are repairing. Place the soldering iron on the wire being held, at a point midway between the pliers and the solder and as soon as the solder is seen to begin to run, lower it so that it touches the protruding end, and then quickly remove the soldering iron.

Provided that you can keep everything steady the two ends will unite, and the soldering iron will carry off the extra heat so that no damage will arise. You need a very steady hand, however, and will soon see how much solder to leave at the "blob".

MAILPLAN OFFERS

Dept. PW 138 Lewisham Way, New Cross, London, S.E.14. TIDeway 6667


Immediate Despatch Service! Best Value for Money!

All items advertised have been approved by our technical team of qualified engineers.

TWO SENSATIONAL TRANSISTORISED INTERCOMS

HANDY INTERPHONE

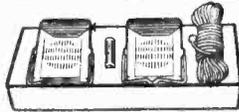For Home, Workshop, Office, two-way calling. Consumes current only when talking or calling. Housed in attractive plastic cabinets with chrome stands. Completely portable. Master and sub-station. Replacement battery only 2/6.




MAILPLAN PRICE 89/6 Incl. PP3 battery, and 25 yds. lead with plugs. P. & P. 3/-.

(Today's value 8 gns.)

7 Station De Luxe Transistorised Intercom

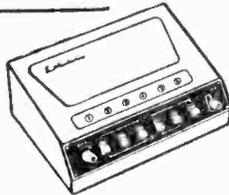The very latest in Office and Factory communication. Calling is audio and visual. Battery operated but consumes current only when calling or talking. Neat compact attractive units, up to 6 extensions supplied separately. Battery life 300 hours.




Master **14 GNS.** Post free. Extension 2 gns. Post free.

HALF THE PRICE OF OTHER MAKES

Construct your own Record Player, Intercom, Tape Recorder etc. with the

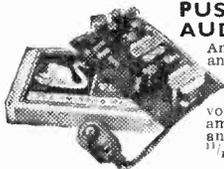PK.543 SUBMINIATURE 4-TRANSISTOR PUSH-PULL AUDIO AMPLIFIER 52/6



An assembled and wired miniature amplifier incorporating output transformer, and 4 transistors, class B, 200 m. watts. All connections for battery, speaker and volume control. The quality is amazing. Complete with instructions and circuit 1217A. Size 3 x 1 1/2 x 1 1/16 in.

8 ohm speaker to suit above. 2 1/2" flux density, 7,800 Gauss. Power. 200 mW. **16/6** P. & P. 1/-

MI78 CRYSTAL LAPEL MIKE 17/6

100-9,000 cps. 1 1/2 in. diam., 5ft. lead. P. & P. 1/-

SLIM CRYSTAL MICROPHONE — 3 WAY —

Hand held, Stand mounted or suspended by lavalier cord.

MODEL 100C 39/6 Post Free

Check the spec. and judge for yourself. Response 60-10,000 cps. Built-in ON-OFF Switch. Output Level -52 dB. Omni-directional. Termination above 500 K ohms. Satin Chrome Finish. Accessory Table Top Stand. 8/6.



PORTABLE SOLDERING IRON Model SPI 30 Watt 230 Volts

(Size 10 1/2 in. 6 1/2 in. when not in use.) Designed on an entirely new principle for light-weight applications. Highly stable heat characteristics ensure long life. Removable handle permits iron to be carried safely even while hot. Supplied complete with Vinyl bag, lead and plug. Spares available. Element 4/6. P. & P. 6d.



18/9 P. & P. 1/-

SERVICE ENGINEERS!

Here's the most useful tool money can buy . . .

the D900 TRANSISTOR TESTER/ POWER SUPPLY

LABOUR SAVING SPEEDY SIMPLE
ONLY £10 Ask for full technical specification.

Checks Alpha gain (Current gain—AC)
Checks Beta gain (Current gain under DC conditions).

Measures Leakage currents between Collector/Base and Collector/Emitter at any voltage between zero and 25 V. **Specially designed for all receivers using PNP Transistors.** Size 5 1/2 x 3 x 2 1/2 in.

NOW you can carry out fast testing of transistors and miniature transistor receivers without removing transistors from circuit. Self-contained signal tracing oscillator, self-contained variable power supply.

Miniature Clear Plastic Panel Meters FOR YOUR HOME BUILT TEST EQUIPMENT

DC MICROAMMETERS Model MR.25 0 to 50 μ A .. **39/6**
Model MR.250 0 to 500 μ A .. **32/6**
DC MILLIAMMETER Model MR.21 0 to 1 mA .. **27/6**
All models individually Boxed and Fully Guaranteed. P. & P. 2/6 each.

"S" METER MODEL SR. 3P. Standard "Ham" Signal strength indicator. Calibrated in "S" units from 0-3 with scale terminating in +10 to +30 dB calibrations. Additional full scale calibrations of 0-5+0-10 in linear scale divisions, 35/-

VU METER MODEL VR. 1P. Calibrated and damped in accordance with standard VU Meter Practice. Upper scale reads -20 to +3VU. Lower scale 0-100% modulation. Uses precision carbon film multiplier resistor and full wave rectifiers. 42/6.



SKANTEST—THE L.O.P.T. TESTER

Tests TV Windings for shorting turns by unique pulse method. This compact instrument can save you pounds. It detects a single shorting turn in a line output transformer, deflector coil or other windings. The pulses provided by the instrument detect intermittent faults. In position one, the continuity of the Windings is checked; in position two, high impedance coils, and in position three, low impedance coils. Once you have used the Skantest you will regard it as a must in TV Service.

Exclusive Mailplan Offer **99/6** P. & P. 2/9


TRANSISTOR MEGAPHONE

MODEL ER304

The smallest ever! Incorporates printed circuit amplifier with current limiting device to give effective battery life. Range up to 1,000 feet. Size 10 1/2 x 6 in. dia.

12 GNS.

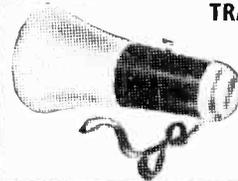Complete with batteries and shoulder strap. Post free.



MULLARD TAPE RECORDER AMPLIFIER

Printed circuit board and set of 27 capacitors **28/-** plus 1/6 ranging from 50 + 50pF at 350 v. to 47 pF. P.P.

MODEL V-7A/F VALVE VOLTMETER

Equal to many higher priced instruments. Gold-plated printed-circuit. High input impedance (11 meg-ohms). The V-7A measures A.C. volts (0-1.5, 5, 15, 50, 150, 500, 1,500) R.M.S. and A.C. volts (0-4, 14, 40, 140, 400, 1,400 and 4,000) pk.-to-pk. D.C. volts (0-1.5, 5, 15, 50, 150, 500, 1,500) Ohms (with 10 ohms centre) X1, X10, X100, X1,000, X10K, X100K and X1 megohm.

£19.18.6


Complete with 32-page handbook.

MODEL V-7A (in kit form).

£13.18.6



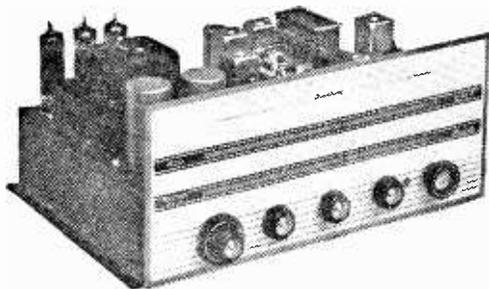an *Armstrong* chassis is more than just a radiogram chassis



It is a carefully designed combination of tuner, control unit and amplifier in one compact unit which can be used as the basis of a complete high fidelity system. A system which can include tape recording and playback as well as radio and record reproduction.

STEREO 12 MK.2 £43.10.0

8 watts push-pull output from each channel, 16 watts total. VHF, with automatic frequency control, medium and long bands. A hi-fi system on one compact chassis.

STEREO 55 (Illustrated) £32.15.0

A junior version of the Stereo 12 Mk. 2. 5 watts per channel. 10 watts total. VHF and medium bands. Inputs for tape, pick-ups and possible future stereo radio.

JUBILEE MK.2 £30.12.0

A mono chassis of 8 watts push-pull output and covering VHF, medium and long bands. Separate tone controls. A.F.C. Pick-up and tape inputs.

AF208 £22.18.0

An AM/FM mono chassis of 5 watts output covering VHF and medium bands. An inexpensive version of the Jubilee Mk. 2

Post this coupon or write for catalogue or call at our showroom for full demonstration and professional advice on your installation. Open 9-5 including Saturdays.

NAME _____ PDC

ADDRESS _____


ARMSTRONG WALTERS ROAD, HOLLOWAY LONDON N.7. NORTH 3213

NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE... PRACTICAL... FASCINATING... 1st stage receiver

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation. **AT LAST**—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory. **YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. **No mathematics!** **INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses. **IN FACT** for the 'Do-it-Yourself' enthusiast, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation.

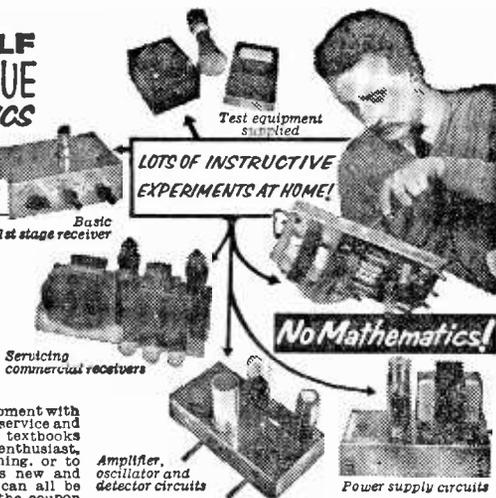

BUILD YOUR OWN • RADIO EQUIPMENT • TEST GEAR • HI-FI INSTALLATION—AND LEARN AS YOU DO IT

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

FREE-POST TODAY

To: RADIOSTRUCTOR (Dept. G107), Reading, Berks.


Name
Address
(821) We do not employ representatives 12-62

BLOCK CAPS PLEASE

THE AUDITRON

(This instrument was previously known as the MINISCOPE—see footnote)

By M. L. Michaelis, M.A.

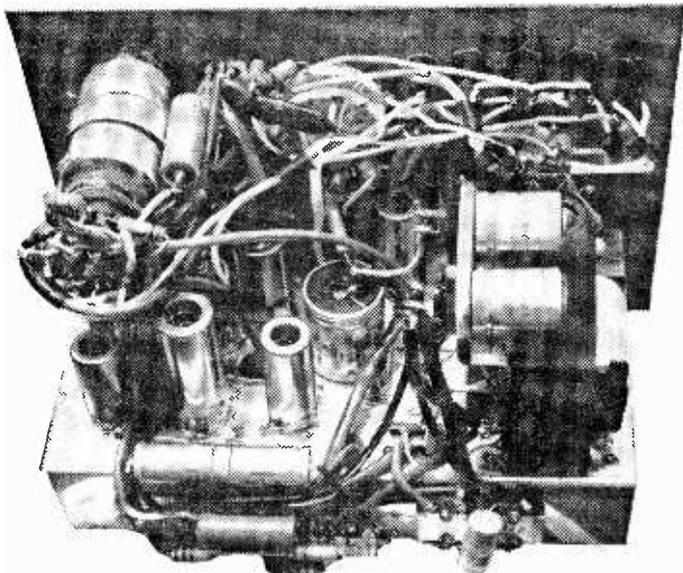

(Continued from page 599 of the November issue)

A MILLER-TRANSITRON oscillator is a special form of multivibrator, in which, loosely speaking, the grid and anode function as one triode and the screen and suppressor as the other triode. The fact that both "triodes" are in one electron-path gives the new characteristics.

The action of one cycle is as follows, starting at the end of a timebase-run. This is reached when the grid voltage has risen to that value for which anode current ceases to show further rise, a condition known as pentode bottoming. (This has nothing to do with anode current saturation.)

All increase of total cathode current then resulting from further rise of the grid voltage (on the charging-curve of the capacitor selected on S5b, via VR9, etc.) is therefore suddenly diverted to the screen-grid at this point, which therefore suffers a sudden rise in current, i.e. fall in voltage. This sudden fall in voltage, at the end of the linear anode run-down, shown in the second lines of waveforms in Figs. 6 and 7 (last month), and shaped in V7 to blank out the flyback as already mentioned, is coupled to the suppressor grid via the capacitor selected on S5a, and thus reduces anode current.

But this reduction of anode current causes a rise of anode voltage, which is fed as a further sharp rise to the grid, via the capacitors on S5b, causing

further cumulative transfer of current from anode to screen. The final result of this very rapid cumulative process is to cut off anode-current completely at the suppressor grid, and send the screen-current to saturation. The anode voltage then returns to H.T. as the capacitor selected on S5b charges via VR10 and grid-current in V6.

Being exponential, however, this process would take, theoretically, infinite time to go to full completion. But in the practical circuit used, it soon reaches the voltage on C18, this being less than H.T., and D5 arrests the process there, the flyback proper being therewith complete.

Conditions then remain stable as long as the negative blocking anode current at the suppressor-grid remains, i.e. as long as the capacitor selected on S5a is still charging through the combination R40, S6, R41. As soon as this charging process has progressed so far that the voltage drop across

R40/R41 has become less than the suppressor-grid-base, a tiny bit of anode current can flow. This causes a few volts drop at the anode, immediately, which are of the order of the normal grid-base of the valve and are fed to the grid via the capacitor selected on S5b.

The result is that all cathode-current is immediately almost cut off, giving a sharp rise of screen voltage, fed as a similar sharp rise to the suppressor, so that the valve is now fully "open" again for any further anode current that wants to flow.

But the anode current at first remains at the very low value giving a drop across VR10 no larger than the grid-base, because any further increase would cause a drop across VR10, fed to the grid via the capacitors on S5b, large enough to cut the valve off, i.e. such increase could not take place. At any rate, it can only take place *slowly* at a rate such that the charge on the capacitors on S5b,

THE "MINISCOPE"

The General Electric Company Ltd. have drawn our attention to the fact that the name "Miniscope" is a registered G.E.C. trade mark. In view of this we have changed the name of our instrument to "The Auditron". We apologise to G.E.C. for the unwitting infringement of their trade mark.

charging through VR9, R35, etc. can follow, thereby avoiding the checking-feedback at the grid.

This gives the relatively slow and very linear rise of anode current, and consequent fall of anode voltage, used for the timebase-sweep of the spot on the CRT. This terminates when the anode current has increased with slowly rising grid voltages up to the point where further rise of grid voltage has no further effect on anode current (bottoming), and we are back where we started.

Current is suddenly diverted to the screen, resulting in total cut-off of anode-current at the suppressor, the flyback takes place, is "caught" by D5, waits until anode current cuts on again at the suppressor, the value is almost cut off at the grid suddenly, a new linear timebase-run takes place, and another cycle is then complete, and so on repeatedly.

Speed-Influencing Elements

It is clear that each cycle consists primarily of two portions, as in any multivibrator, associated with independent CR-time constants, which may be influenced independently.

Thus we have *here* firstly the linear timebase run, determined by the time constant given by VR9 and R35 together with the selected capacitor on S5b, and secondly the anode-current cut-off time, determined by the time constant set by R40/R41/S6 together with the capacitor selected on S5a.

Each time-constant can, in principle, be controlled fully independently from the other, but a *purposeful* ganging is in practice desirable, and has been adopted.

Ganging of Time Controls

S5 constitutes the ganged coarse speed-control for the timebase. This is a three-position switch selecting capacitors of equal values for both time-constants simultaneously, in steps of 10:1 in capacity, and thus 10:1 in speed-ratio. VR9 is the timebase-run fine-speed control.

It has no effect on the anode current cut-off period including the flyback, but as a continuously—variable range of 20:1 for the timebase—run speed, because R35 has one twentieth the resistance of the full track of VR9. This gives sufficient overlap of all ranges for all purposes.

It is *not* the flyback-time, which determines the time from the end of one timebase-run until the circuit commences the next run, but rather the time for which the capacitors on S5a and R40 (and R41, if in circuit) hold the anode blocked at the suppressor. If the latter is shorter than the true flyback, the new run starts before D5 operates, resulting in decreased amplitude of the sawtooth and higher overall frequency. If the suppressor cut-off time is much longer than the true flyback, the anode simply waits resting at C18-potential until the suppressor is ready again (Figs. 6 and 7 respectively).

These two conditions can be selected by means of S6. In the position "short" for S6, only R40 is in circuit for the "recover" time constant, so chosen as to match the flyback proper, i.e. when the flyback has reached the C18/D5 catching-level, the suppressor is then just ready for the next run too.

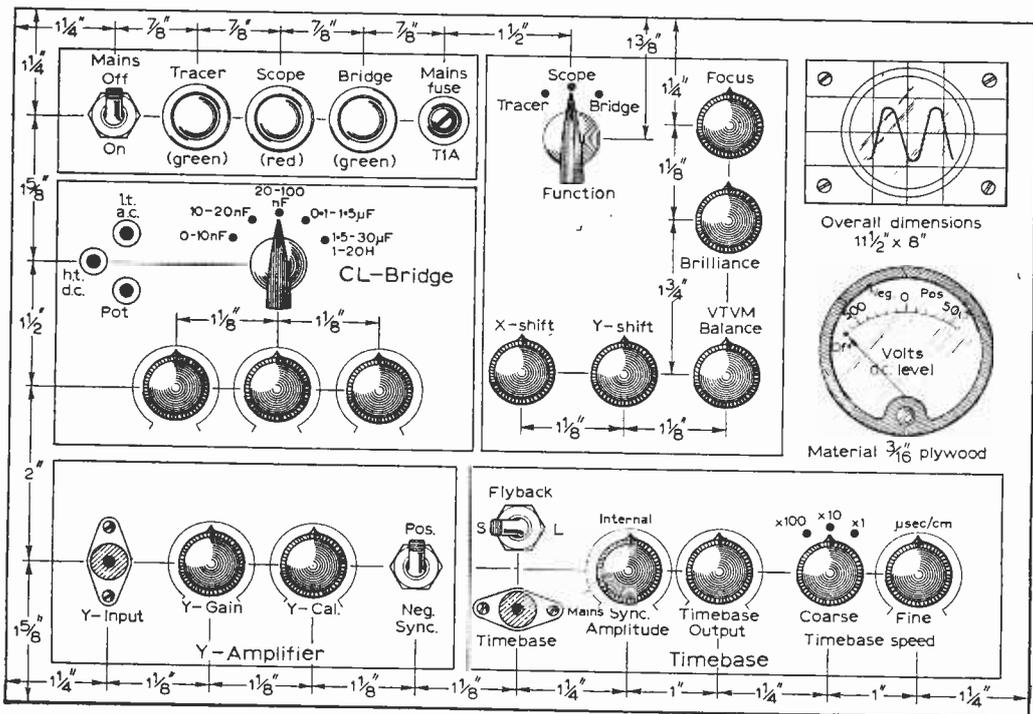


Fig. 8—The layout of the front panel.

Auditron. The sync facilities incorporated, together with the "long/short" function, will satisfy all normal needs of the radio and audio experimenter.

Synchronisation

The Miller-Transitron timebase is synchronised by setting VR9 such that the overall frequency is somewhat lower than the signal frequency, when left to run uncontrolled. The positive pulses, in step with the signal frequency, amplified and shaped by V4 and V5, then jerk the suppressor to cut-on just that little sooner to bring the two frequencies into step.

The gain of V4 and the arrangements for extracting a sync signal from the signal amplifier are such that good strong sync is possible for all signals having at least 10% of the screen-size vertical amplitude, at all frequencies of operation for which the instrument is intended.

VR8 serves as gain-control for the sync signal, to control the strength of the effect with stronger signals, or to remove all sync if desired. VR8 carries a D.P. switch, S4, which switches over to 50c/s mains sync (for frequency-comparisons against the mains) if turned beyond the point of "no sync". The mains-sync signal is obtained from the heater-line via R23 and R24.

Calibrations for the Timebase

A special feature of the Auditron is that the conventional calibration of the timebase controls in terms of basic frequency has been abandoned in favour of a "time per centimeter" of CRT-screen display calibration, which is vastly more useful. A frequency-calibration is relatively useless, as the flyback and wait times are indefinite fractions of a timebase cycle, and thus even if exact number of cycles of the signal appear stationary in the display, the interpretation in terms of signal-frequency is very often rather ambiguous, because it is not clear how much is located on the invisible flyback.

The "time-per-centimeter", in conjunction with a centimeter-grid of lines on the perspex window in front of the CRT, represents a form of calibration removing every ambiguity. S6 has no effect whatsoever on the speed of the timebase run, which is controlled solely by VR9 and S5b. Fully unambiguous calibration of VR9 from 12 to 250micro-seconds per centimeter was thus possible in the prototype, with the three positions of S5 labelled approximately X1, X10, X100. Thus all times from 12 microseconds to 25 milliseconds per centimeter are covered. This enables time measurements to be read off direct, and frequency measurements to be made as follows.

The signal waveform is synchronised stationary, and the length of one cycle read off against the centimeter lines on the perspex window in front of the CRT, which is then multiplied by the time-

per-centimeter readings on the timebase-controls. The result is the time for one cycle of the signal waveform, whose reciprocal gives the frequency.

It might be asked why here a once-and-for-all direct calibration of the timebase controls has been adopted, whereas for the signal voltage calibration an independent Zener-standard calibrator was used instead of direct calibration of the Y-gain control. The reason is that in the timebase our time-determining elements are largely the capacitors C22 to C27, and valve-ageing or voltage fluctuations can act only on the single stage V6, resulting in no drifts greater than tolerable for normal workshop standards of accuracy.

The Flyback-Blanking Circuit

In order to black-out the flyback of the spot on the CRT-screen we need to cut-off the CRT at its grid during all times except the linear timebase-run used for the display. This requires an

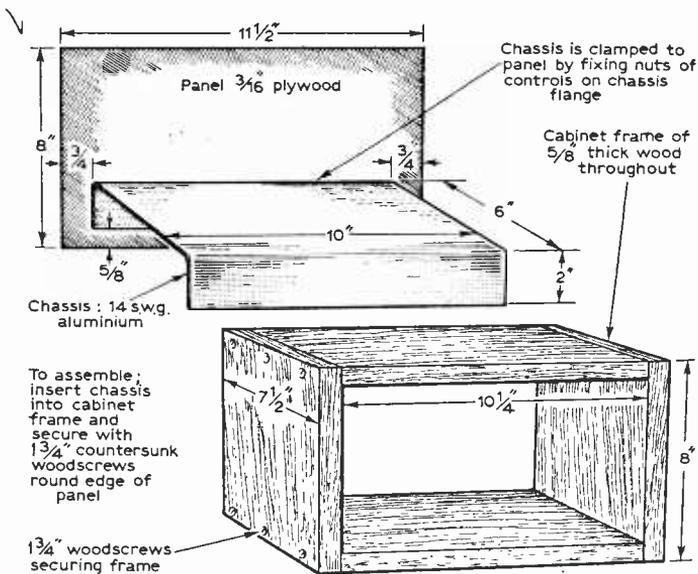


Fig. 10—The cabinet details.

accurately-timed squarewave, whose negative portion coincides with the "flyback and wait" portion of the timebase cycle, and whose positive portion coincides with the linear timebase run.

In order to perform the blanking function properly, this must be as good a squarewave as possible. Furthermore, the D.C. level of this squarewave must be such that the positive part of the wave is coincident with the voltage set on the manual brilliance control, and the negative part goes negative to this level by an amount equal to the amplitude of the wave, the latter needing to be sufficient to cut the CRT off, even for the brightest setting of the manual brilliance control. In other words, the amplitude of the squarewave must be just a little more than the grid-base of the CRT, and 30V was thus found to be satisfactory.

The circuitry round V7, with associated diodes

D6, D7, D4, was devised to meet all these requirements to within sufficient limits of accuracy for all normal amateur purposes.

Shaping of the V6-screen Waveform

Figs. 6 and 7 show that the screen-grid waveform of V6 is already of the required form, very roughly, for the flyback-blanking function. Thus the screen goes negative during the flyback and wait time, because anode-current is then cut-off and heavy current diverted to the screen. During the timebase run, the screen is much more positive, because anode-current is flowing, and thus screen current is low or normal.

Yet the original screen waveform is anything but a good squarewave. At the fastest settings of VR9 the positive-going transition takes about the same time as the timebase run, so that at least half the trace on the CRT would still be dark, and the other half would increase progressively in brightness, were this waveform used directly to bias the CRT grid.

At the slowest settings of VR9 the screen wave rises fairly soon to a maximum positive, and then gradually falls as the anode and screen draw increasing current during progression of the timebase-run. This wave, if applied to the CRT grid, would have the undesirable result of giving a trace which starts dark, rises fairly soon to maximum intensity, and then gradually tails off in intensity towards the end.

However, looking at this screen-grid waveform of V6, it is apparent that both positive and negative transitions commence with steep portions having at least the desired final amplitude of 30V, and pretty accurately coincident, in time, with the start and end of the timebase run. It is thus the purpose of V7, D6, D7, D4 to cut out this portion of the wave, and reject all else.

The D.C.-level of the screen waveform shifts with the setting of VR9, on account of the symmetry - changes thereby involved. It is therefore necessary to clamp the wave to a definite potential prior to introduction of clippers at the desired relative D.C. levels. The combination of C21, D6, R42 performs this function, clamping the wave to $-18V$ (derived from the Y-amplifier bias circuit) as its most negative limit under all circumstances. R31 merely serves the purpose of reducing loading thereby imposed at the screen-grid of V6, which would otherwise react back to distort the timebase action. The function of such a clamp-circuit is identical to a peak-rectifier circuit.

The output waveform at V7 cathode is now clamped at chassis potential and is positive-going from there. All that is needed is to retain the first 30V, and chop off the rest, which is performed by the simple diode-limiter circuit D7, which is returned to the desired potential of plus 30V on R36, C19, D7 and C19 thus short-out all portions of the waveform lying above plus 30V.


We are now left with the desired waveform for flyback blanking. It is merely necessary, as a final step, to give this the desired D.C. level, i.e., to change over from positive-going-to-chassis to negative-going-to-brilliance-control-setting.

This is performed by another clamp-circuit, whose principles of operation are identical to those of the first. A coupling-capacitor C29 first of all removes all D.C., D4 is a negative peak rectifier, and the series-added D.C. is whatever voltage is present at the slider of VR1, the brilliance-control. R37 and C30 were introduced as an equaliser, to make the action of this clamp circuit slightly frequency-selective, speeding it up at the higher frequencies of operation to compensate for slight delays in rise of the original wave there.

The specified value of C30 should be found satisfactory, but if the trace on the CRT is found not to have a clean sharp start at the highest possible timebase-speed setting, slightly larger values should be tried.

Diodes

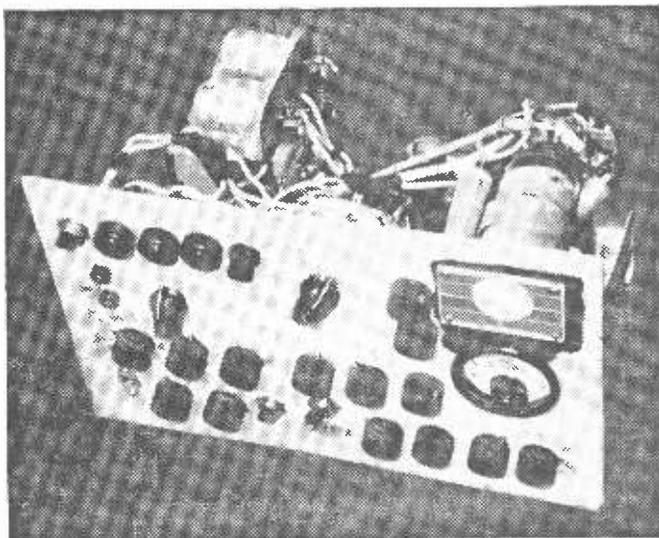Although silicon diodes are less critical than germanium diodes, heat shunts should nevertheless be used when soldering these diodes. If diodes are unwittingly damaged during soldering,



The Miniscope as it appears in an advanced stage of construction.

this circuit can give a variety of forms of erratic performance. Take care, also, to wire all diodes with the correct specified polarity. It is *NOT* permissible to use normal germanium diodes of the RF or low-voltage types *anywhere* in the Auditor, as the voltage ratings of such are far too low, and they would suffer immediate destruction. The peak inverse voltages appearing on the diodes in the Auditor amount to some one or two hundred volts in some cases, and thus the single type number specified throughout is a silicon diode of 350V peak inverse voltage rating.

(To be continued)

PRESENTED FREE
WITH
"PRACTICAL WIRELESS"
DECEMBER 1962

Practical Wireless

LUXEMBOURG TUNER

PUBLISHED BY GEO. NEWNES LTD., TOWER HOUSE, SOUTHAMPTON STREET, LONDON W.C.2.


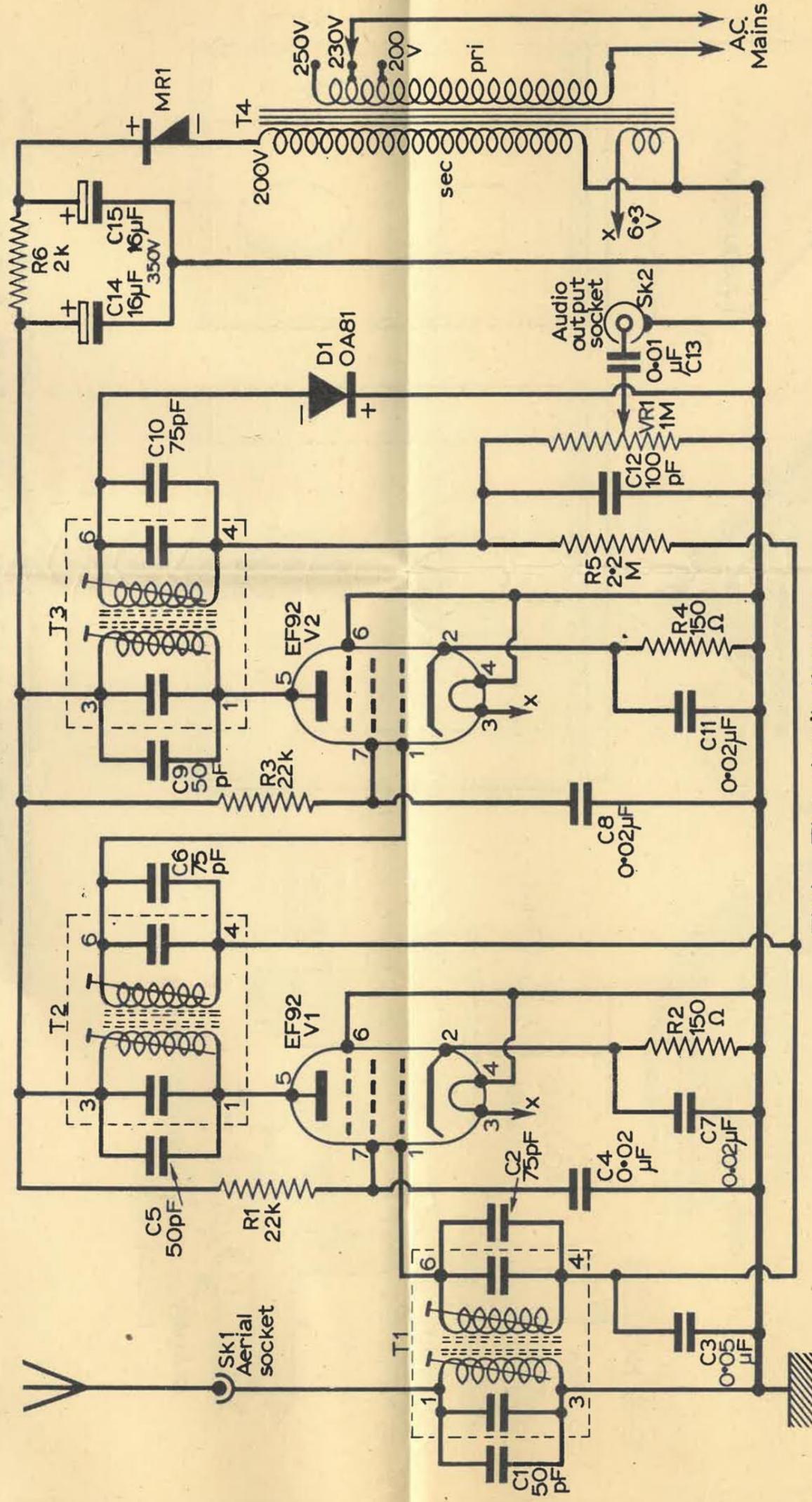


Fig.1—The circuit diagram

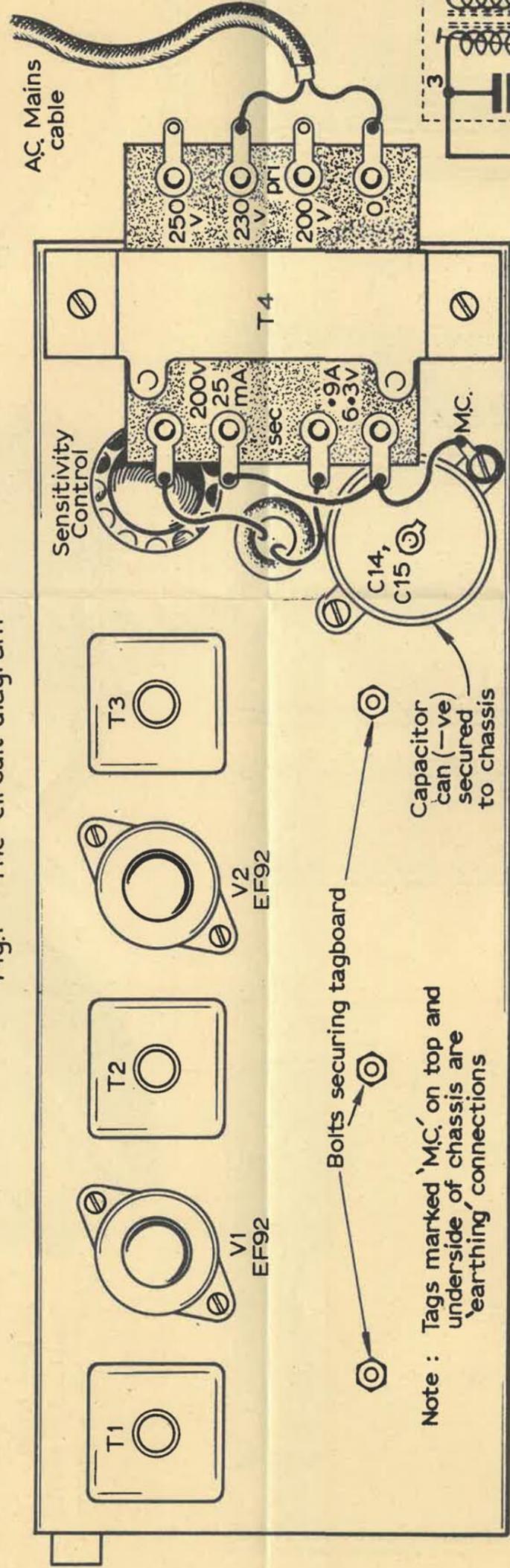

Note: Tags marked 'MC' on top and underside of chassis are earthing connections

Bolts securing tagboard

Capacitor can (-ve) secured to chassis

Fig. 2—The above-chassis wiring

COMPONENTS LIST

Resistors:
(All 1/4W 10% unless otherwise stated)

R1 22k R4 150Ω
R2 150Ω R5 2.2M
R3 22k R6 2k 3W

VR1 1M potentiometer

Capacitors:

C1 50pF 1% silver mica
C2 75pF 1% silver mica
C3 0.05µF paper 350V
C4 0.02µF paper 350V
C5 50pF 1% silver mica
C6 75pF 1% silver mica
C7 0.02µF paper 350V
C8 0.02µF paper 350V
C9 50pF 1% silver mica
C10 75pF 1% silver mica
C11 0.02µF paper 350V
C12 100pF 1% silver mica
C13 0.01µF paper 150V
C14, C15 16 + 16µF elec. 350V

Valves:

V1, EF92 V2 EF92

Sockets:

SK1 Wander-plug socket
SK2 Coaxial socket

Transformers:

T1, T2, T3 Miniature 1.6 Mc/s
I.F. transformer (Denco)
T4 Mains transformer with
tapped primary.
Secondaries; 200V 25mA;
6.3V 1A

Rectifiers:

D1 OA81 signal diode
MR1 Contact-cooled H.T.
rectifier 250V 50mA

Miscellaneous:

Chassis, 8in. × 3in. × 2 1/2in.
Two pieces of aluminium for
screens, 3 1/2in. × 1 1/2in. One in-
sulated backing plate. Two
B7G valveholders with skirts
and screens. One 3-way tag strip
board. One miniature 18-way group
board. One capacitor clip (lin.).
One control knob. One wander
plug and one coaxial plug. Nuts,
bolts, etc.

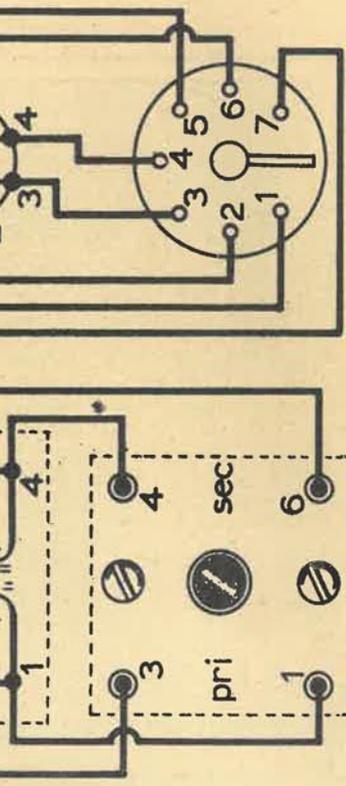


Fig. 5—IF coils and valvebase details

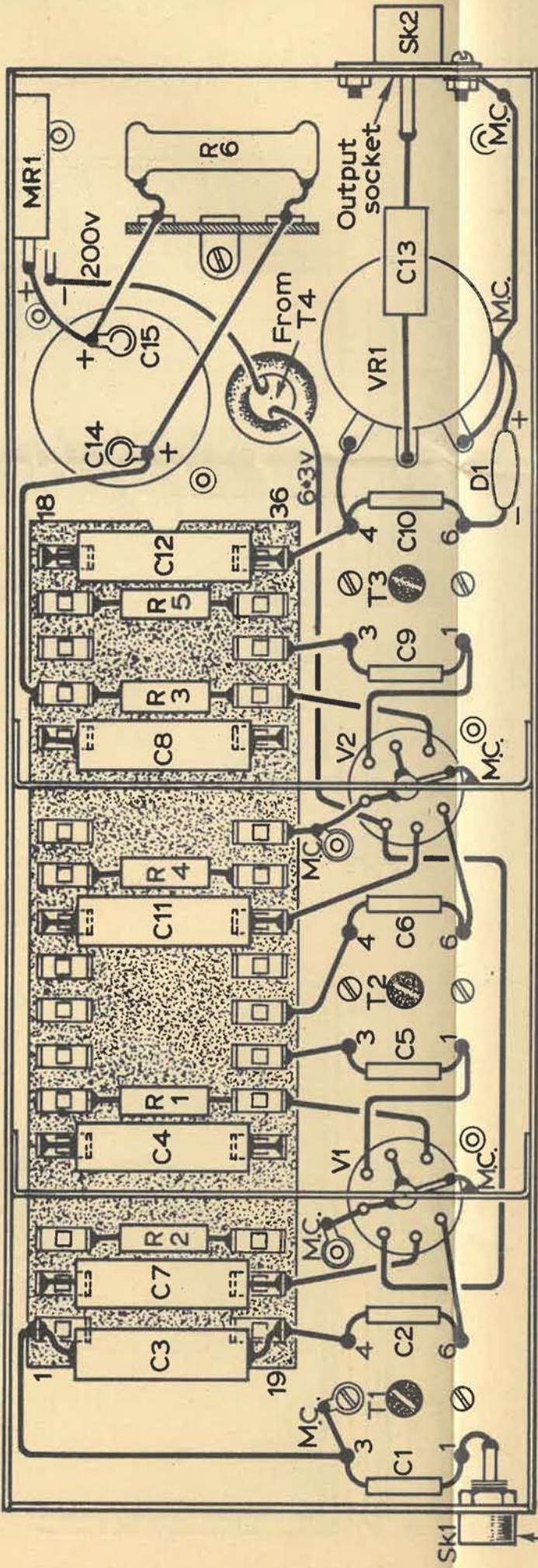


Fig. 3—The under-chassis wiring

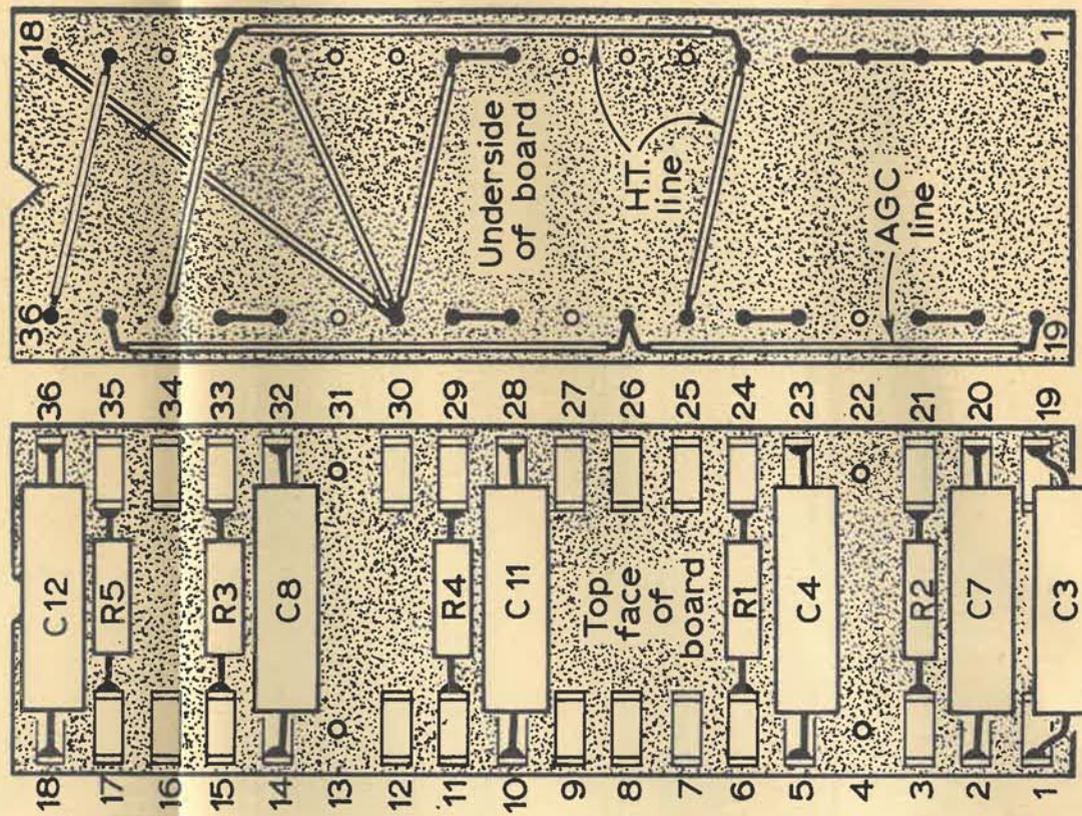


Fig. 6—The tagboard wiring


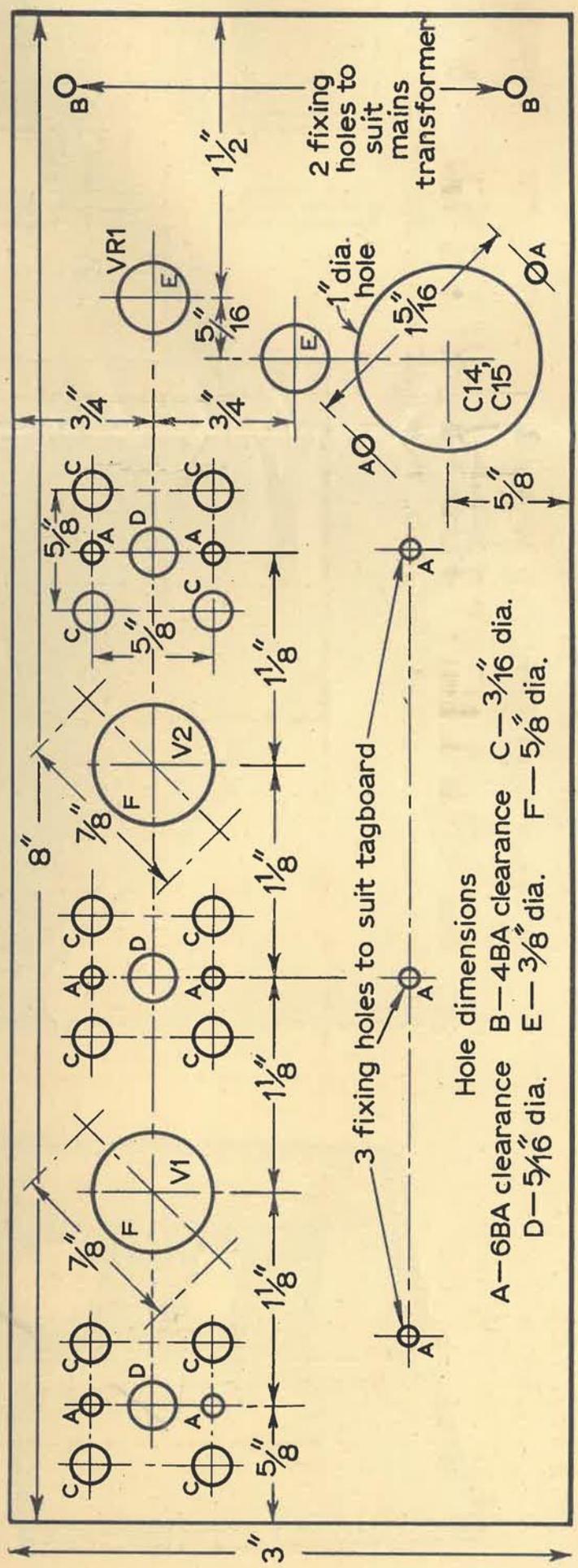
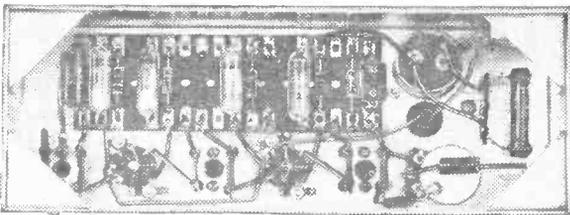


Fig. 4—The chassis drilling diagram

Hole dimensions

- A—6BA clearance
- B—4BA clearance
- C— $3/16$ dia.
- D— $5/16$ dia.
- E— $3/8$ dia.
- F— $5/8$ dia.

THE LUXEMBOURG TUNER

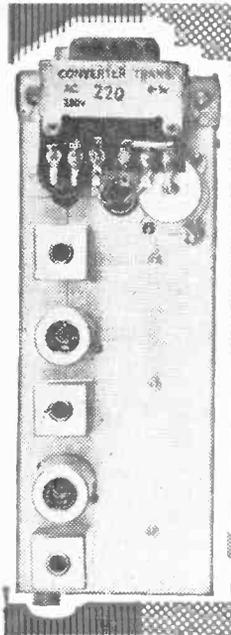

20m
Pre-set

NOWADAYS most people have an F.M. tuner to give them high quality interference-free reception from their local BBC stations but there are numerous occasions when the programmes transmitted are not of the more popular light music type and an alternative is required.

Without doubt the most popular station for light entertainment particularly among the younger generation is Radio Luxembourg on 208m.

In order to receive this station it would normally be necessary to have a complete medium wave tuner but this novel design shows how a high gain and selective tuner pre-set to the Luxembourg frequency can quite easily be constructed.

The Design

The original idea for the circuit came from experiments carried out with a 1.6Mc/s I.F. amplifier strip when it was found that by adding a small fixed capacitor to each winding of the I.F. transformers it was quite simple to bring the tuning point down from 1.6Mc/s to 1.439Mc/s which is the exact frequency for Radio Luxembourg.

As miniature 1.6Mc/s I.F. transformers are available from all the component shops they provide a ready made perfectly screened band-pass coil unit adjusted for optimum coupling which can be easily tuned to 208m.

The circuit which is shown in Fig. 1 on the Blueprint is quite simple but has proved to be very sensitive and yet perfectly stable over long periods. It consists of two straightforward R.F. amplifiers followed by a germanium diode which provides detection and negative bias for non-delayed AVC. In practice the use of a miniature group-board to mount all the small components makes it both very easy to construct and at the same time gives the tuner a neat professional appearance.

It will be noticed that no audio amplifying stage has been included as it was found that feeding

from the detector into a standard Mullard 3W amplifier sufficient signal was always available to overload the input and in fact a preset output control was included, which is normally set at about the halfway position. Good reception has been obtained with this tuner in various locations in and around London and also in parts of South East England using only 4ft of wire as an aerial, however in view of the characteristic fading that does occur from time to time on Luxembourg it is considered that the best aerial possible should always be used.

When the first prototype was completed a considerable amount of experiment was carried out with various different input circuits from the aerial including winding small coupling coils on to the first I.F. transformer to give a step-up ratio but the difference in results was so slight that it was not considered worth the additional time and trouble.

As a precaution against the possibility of some instability due to the high gain with two R.F. stages small screens were fitted across the centre of each valveholder but it would appear that these are not absolutely essential and some constructors may prefer to build on a try-it-and-see basis and only fit them afterwards if needed. The position occupied by the screens is shown dotted in the under chassis wiring diagram Fig. 3 but it should be noted that they were removed for the photograph (at the top of this page) in order to provide a clearer view of the wiring and components.


Construction

The chassis used was an aluminium type with reinforced corners and it measured 8in. x 3in. x 2½in. Actually a chassis having a depth of only 1in. would have been sufficient but the deeper one was chosen as it appeared to be a standard ready made component that was stocked by most of the well-known component shops.

There is comparatively little metal work or drilling to be carried out as will be seen from the chassis drilling diagram Fig. 4. To simplify the

RG R

3 m Tuner

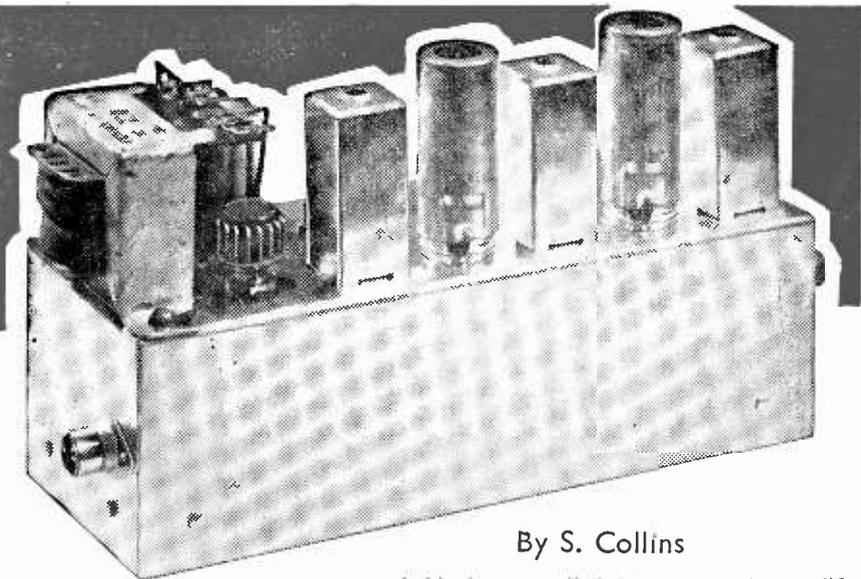

By S. Collins

marking out of the I.F. transformers a small paper template should be used and if desired this can be lightly stuck on to the chassis before drilling.

Having drilled all the holes in the chassis the various components can be fitted into position according to the diagrams Fig. 2 and Fig. 3 but care should be taken to ensure that the valveholders are the correct way round. This also applies to the I.F. transformers and these can be checked quite easily by reference to the small numbers moulded on the base of the formers, 1 and 3 being primary and 4 and 6 the secondary.

Component Group-board

The secret of the clean layout and the easy assembly lies in the 18-way miniature group-board which takes practically all the small components, and by wiring up the various tags on the back first the majority of the work can be done before this item is fitted into the chassis.

The two views of this group-board given provide all the necessary information for carrying out the wiring, but in view of the ease with which it is possible to become confused when constantly turning this component over while working it is strongly advised to positively mark one end with a dab of paint or a small "V" notch as shown. It is recommended that all the wires on the rear of the group-board should either be PVC insulated or covered with 1mm sleeving to avoid the possibility of short circuits.

It is also essential that an insulated backing plate should be fitted between the group-board and the chassis or if preferred it can be mounted just clear of the chassis by two spacing nuts. It will be noted that the two pairs of tags in positions 4 and 13 have been removed and this was done to allow the screens across the valveholders if fitted to be taken close to the chassis.

Power Supply

No mains on/off switch has been included as it was thought that in most cases this unit would

probably be controlled from the main amplifier, but this is a matter of personal requirements.

The mains side consists of a conventional double wound transformer T4 of the type used in most Band III converters giving 200V half-wave H.T. and 6.3V for the heaters; this type of transformer also effectively isolates the chassis from mains to ensure complete safety. The H.T. is rectified by means of the usual contact-cooled rectifier MR1 which must be fixed to the chassis so that the smooth side makes good contact all over for cooling.

One side of the H.T. winding on the transformer goes to chassis together with one side of the 6.3V winding. The other side of the H.T. winding then goes to the tag on the rectifier marked -ve while the +ve tag is taken to the 16 μ F reservoir capacitor and through to the H.T. positive line.

Having completed the actual construction and wiring and carefully checked each part in turn against the diagrams the unit should be connected to the mains and switched on. If a testmeter is available it is a good idea to check at the various valve pins to make sure that there is H.T. on the screens and anodes (pins 5 and 7), and also a small positive on the cathodes (pin 2).

Setting Up

The output socket SK2 should now be connected to an amplifier input and the controls turned to near maximum to start with. If a signal generator is available then the adjustment is very simple and routine.

First of all set the signal generator to about 1440kc/s and feed the modulated signal into pin 1 of V2, then adjust the cores of T3 for maximum sound from the loudspeaker. Now transfer the generator to pin 1 of V1 and adjust both cores of T2 for maximum signal and then connect the signal generator to the aerial socket and finally adjust T1 cores for the best output.

This will bring the tuner fairly close to the Luxembourg programme and if desired a short aerial can be fitted and the final adjustment carried out on the actual transmission. A better way if

(Continued on page 749)

An AUDIO ABSORPTION WATTMETER



By K. BERRY

THIS wattmeter was developed to enable the power output of audio amplifiers to be measured. It is suitable for use with amplifiers having output impedances of 3 or 15Ω, and will measure powers of between 1 and 20 watts. A feature of this design is the fact that the meter has a near-linear scale as opposed to the more usual "square-law" scale associated with instruments of this type.

Theory

The power dissipated in a resistor is given by the expression $P = \frac{V^2}{R}$ watts, where R is the value of the resistor in ohms, and V is the voltage developed across it in volts. Thus if it is desired to measure the output power of an amplifier, a resistor, whose value is the same as the output impedance of the amplifier, should be connected to the output terminals of the amplifier and an A.C. voltmeter connected across it to measure the voltage developed. The power dissipated in the resistor can then be calculated. If, however, the meter was so calibrated, then the power developed could be read off directly thus obviating the need for calculations. This is the basis of the absorption wattmeter.

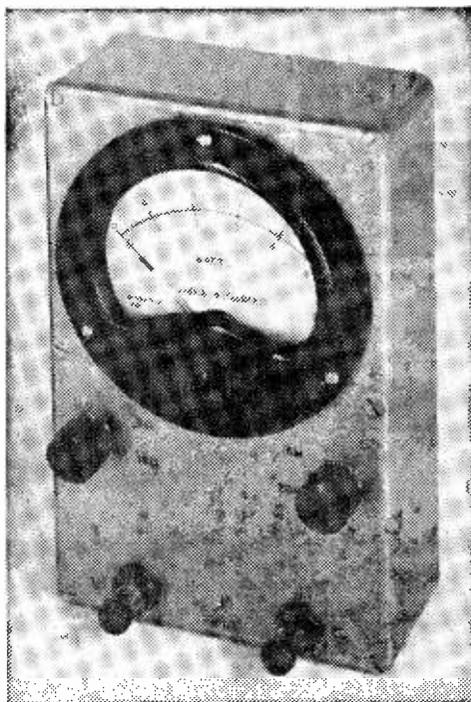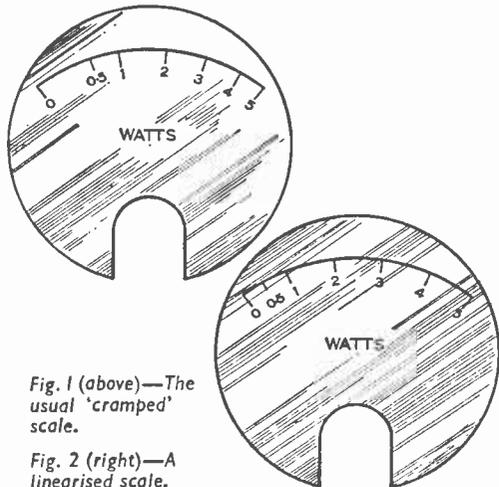If the voltmeter used has a linear scale, the power calibration tends to be cramped at the "top" end of the scale as shown in Fig. 1. In this design, the voltage applied to the rectifier bridge which feeds a moving coil meter has been



The finished instrument.

deliberately kept as small as possible. Consequently the diodes are being worked over the non-linear portion of their characteristics and since this approximates to a "square law" curve this largely cancels the cramping effect normally found at the top end of the scale as can be seen by comparing the scale in Fig. 2 with that in Fig. 1.

Circuit Description

The circuit diagram of the wattmeter is given in Fig. 3. The appropriate load resistor, 3Ω or 15Ω, is chosen by SW1A. The voltage developed across the load resistor is applied to one of four potentiometer networks, the required network being selected when the impedance and power range switches are set. The output from the selected potentiometer network is fed to the bridge rectifier, Mr1-4, and thence to the meter M1. A

Specification

Impedance	3Ω or 15Ω
Power range	5 watts or 20 watts
Frequency response	± 0.5 dB 10 c/s = 100 kc/s

250Ω rheostat VR5 is connected in series with the meter. This has been included to enable an adjustment to be made to the linearity of the scale since this will vary slightly depending on the exact type of diodes used in the rectifier bridge.

The use of four separate potentiometer net-

Table 1

Impedance							
3Ω				15Ω			
Voltage	Power	Voltage	Power	Voltage	Power	Voltage	Power
3.87	5	7.75	20	8.66	5	17.32	20
3.46	4	6.93	16	7.75	4	15.5	16
3	3	6	12	6.7	3	13.42	12
2.45	2	4.9	8	5.5	2	10.95	8
1.73	1	3.46	4	3.87	1	7.75	4
1.23	0.5	2.45	2	2.74	0.5	5.5	2

works instead of the more usual series (multiplier) resistors is explained by the necessity to keep the resistance in series with the bridge, low, and comparable, on all ranges. This results in a common calibration for all ranges.

Components and Construction

The choice of components is quite straightforward. The load resistors, R1 and R2, must, of course, have an ample power rating, but the use of 20W resistors is, perhaps, not essential. Provided the meter is not used to absorb a continuous 20W, there is no reason why, say, 10W resistors should not be used. The 3Ω board is made up of 3.3Ω and 47Ω resistors in parallel (=3.06Ω). The germanium diodes used in the prototype were Mullard type OA70, these are general purpose point-contact diodes and any similar diodes should prove suitable. The meter is a 3½in. 0-1mA movement with a D.C. resistance of 50Ω, but any 0-1mA meter should be equally satisfactory for this purpose.

The prototype wattmeter was housed in an "Eddystone" die-cast case of size 7½ x 4½ x 2 inches (approximately) with four small rubber feet fitted

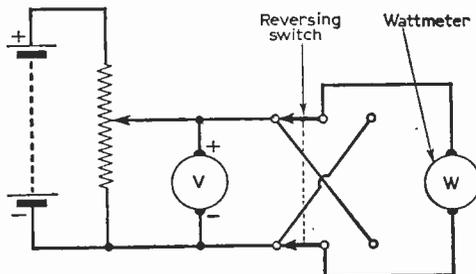


Fig. 4—The calibration arrangement.

to the underside to prevent damage to the paint finish if placed on a rough surface.

Calibration

When the instrument has been assembled and wired, it is necessary to calibrate it by adjusting the potentiometers RV1-5 inclusive. This, fortunately, is quite a simple matter and requires only the use of an accurate D.C. voltmeter. This meter is used to measure the voltage applied to the terminals of the wattmeter. Before commencing calibration, the lead to SW1A should be unsoldered so that the load resistors R1 and R2 are disconnected. A variable D.C. voltage is then applied to the wattmeter as shown in Fig. 4. This can be obtained from a battery and poten-
(Continued on page 754)

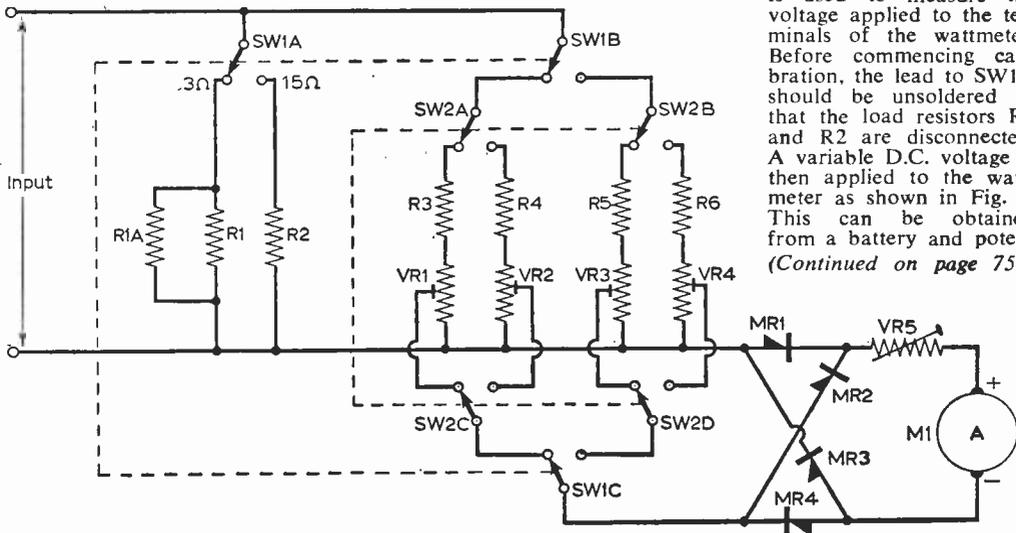


Fig. 3—The circuit of the instrument.

Radio Components and their Functions

(Continued from page 605 of the November issue)

HAVING dealt with both TRF and super-het receivers, we now conclude this short series by analysing audio amplifiers in terms of component functions, voltages and currents. Basically, there are two essential types of audio amplifiers which are the concern of the service technician and experimenter, these being the single-ended output stage type and the push-pull arrangement.

By K. Royal

Single-stage Amplifier

The simplest of audio amplifiers commercially available is shown in Fig. 6. This is designed for use in a record reproducer (Cossor, Model 559), and uses just a single amplifying stage, V1.

This is a high-slope pentode valve, which receives at its control grid the signal direct from the output of a crystal pick-up. The pick-up used has a relatively high output (hence the omission of an audio driver stage or voltage amplifier), and is a Collaro Studio-T type.

The pick-up signal is applied across the resistive element of a 2M volume control, which gives the correct matching. Instead of the slider of this control going straight to control grid, however, it goes to one side of the track of the tone control, R2, which is valued at 1M. As the other side of the resistive element goes via a capacitor to chassis, we get a tone-control, potential-divider arrangement.

Whatever level of pick-up signal is selected by the volume control, this is applied to R2 and C1 in series. Now, at high A.F., the impedance of C1 is relatively low, compared with its impedance at low A.F. At high audio frequencies, therefore, the capacitor end of R2 can be considered as connected to chassis through a low value resistance. Thus, when the slider of R2 is at the capacitor end of the resistive element, there is very little signal between the control grid of V1 and chassis. There is considerably more low-frequency signal, however, since to such signals C1 "looks" like a high impedance. At this setting of the control, then, we obtain an effective "bass lift".

At the other end of the control's range there is virtually no tone correction at all, because signals at all frequencies are applied direct from the slider of the volume control R1 to the control grid of V1, via the slider of R2. The fact that the high series impedance of R2 and C1 is in parallel with the signal at that setting is of little consequence. However, a progressive "top cut" or "bass lift" occurs as the slider of R2 is turned towards the capacitor end of the resistive element. This is a useful tone control circuit for the simple pick-up amplifier, and

one for which the experimenter may well find applications.

The rest of V1 is wired in the usual manner. Grid bias for the valve is obtained from the voltage dropped across the cathode resistor R3, and this is of the order of 6V, as measured between cathode (positive) and chassis on a 1,000 Ω /V meter. The anode is loaded by the loudspeaker transformer T1, whose turns ratio is selected to match the low impedance loudspeaker to the high anode impedance of the valve. C3 across the primary winding gives further tone correction and damps harmonic resonances which may otherwise be set up in the loudspeaker transformer.

The screen grid of the valve is fed through R4 and heavily decoupled (or smoothed) by C4. It is worth noting that the anode of the valve is fed straight from the output of the rectifier V2 without a smoothing choke or resistor. When this is done on a single-stage circuit the screen grid of the valve must have an almost ripple-free voltage, which is accomplished by the decoupling mentioned above. R4, then, can be considered as the smoothing resistor and C4 the smoothing capacitor. C5, at the cathode of the rectifier, is, of course, the ordinary reservoir capacitor. There is no negative feedback in this simple circuit, for even the cathode of the valve is heavily decoupled by C2.

A fully isolated power supply is employed, T2 being the mains transformer with H.T. and L.T. secondaries. The H.T. winding is centre tapped to facilitate full-wave rectification, while the heaters of the two valves are wired in parallel and energised from the 6.3V L.T. winding.

This kind of amplifier runs at about 260V H.T. (from the rectifier). This gives about 240V on the valve anode and 225V on the screen grid with currents of 41mA and 4.8mA respectively. The total H.T. current, therefore, is in the order of 46mA as measured in the cathode of V1. The A.C. voltages either side of the centre tap on the H.T. winding of the mains transformer are 235V.

Push-Pull Stereo Circuit

To illustrate the more complex push-pull circuit we show at Fig. 7 the circuit of the Decca SG188 stereo record reproducer. For any stereo system

two identical amplifier sections are required which are given as Channels A and B on the circuit.

Each channel has a voltage amplifier tone control stage, followed by two more voltage amplifiers, a phase splitter, two pentodes in push-pull and a pair of parallel-connected rectifiers to provide the necessary current for the two channels. For the following discussion Channel A will be considered, bearing in mind that the rectifiers and power circuits only are common to both channels.

The stereo pick-up gives two outputs, one which is fed to Channel A and the other which is fed to Channel B. The pick-up signal is fed direct to triode V1A via the equalising circuit C50 and R50. This gives a rising response to the higher audio

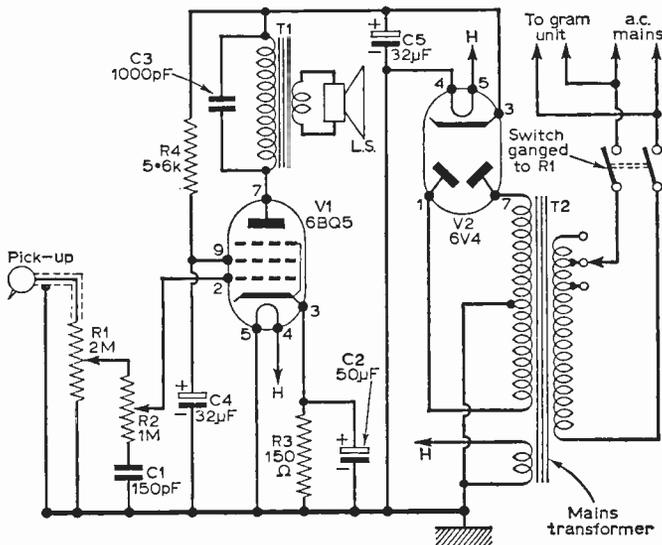


Fig. 6—The circuit diagram of a simple single-stage A.F. amplifier, used in the Cossor, Model 559 Record Reproducer.

signals, since C50 is 100pF (having a high impedance to low A.F.) and R50 is 1M. R52 is simply the grid return for V1A.

The equalised signal is developed across the anode load R51 and fed through C52 to the tone control system. Thus from C52 we have a signal applied to the "treble" circuit (C53, VR1 and C54) and also a signal applied to the "bass" circuit (R56, VR2, C55, C56 and R57). Now when VR1 and VR2 are set to the centre of their ranges a signal of frequency characteristics almost equal to that at the output of C52 is fed to the volume control VR3 and there is no tone correction. There is attenuation, though, which is the reason why the circuit features three voltage amplifiers. At high A.F. C54 "looks" almost like a short-circuit, while C53 has a relatively low value of impedance. Thus, with VR1 slider at C53 end of the control, maximum treble is fed to the volume control and this value of treble diminishes as the control is turned in the opposite direction.

The network comprising R56, VR2, R57, C55 and C56 is, in effect, an adjustable low-pass filter.

The signal goes in at the top of R56 and comes out at the slider of VR2. It thus passes only low-frequency signals to the volume control and the amount of low A.F. relative to high A.F. passed depends upon the setting of VR2.

Two Signals

In that way, then, the volume control receives two signals, one by way of the treble high-pass filter and the other by way of the bass low-pass filter, and as each of these filters are adjustable the required overall frequency response can be accurately established. This type of tone control circuit is also extensively used in hi-fi amplifiers and control units.

The equalised and tone-controlled signal is developed across the volume control and the required level is tapped off at the slider and fed to the control grid of V2A. This is a fairly conventional A.F. amplifier but has facilities in its cathode circuit for the application of negative feedback. The stage is biased by the voltage dropped across R62 and R64 as series in the cathode circuit. R66 is the anode load from whence the amplified signal is fed to the grid of V3A via the coupling capacitor C60.

R65 is the grid leak for V3A and reflects the voltage dropped across R69 in terms of grid bias at its grid. Current negative feedback is applied to this stage, since R69 does not have a bypass capacitor.

V4A is the phase splitter valve. This is direct coupled to the anode of V3A and the splitter is biased because the voltage at its cathode is V2 more positive than the voltage at its grid, thereby making the grid V2 negative with respect to its cathode.

Push-Pull Drive

The phase splitter produces two signals, one at the anode, across R71, and the other at the cathode, across R70. As these resistors are accurately balanced the two signals are of equal amplitude, but owing to the phase inversion effect of the valve the signal at the anode swings positive when the signal at the cathode swings negative and vice versa. These signals represent the drive for the push-pull valves and are fed through C64 to the control grid of V3A and through C63 to the control grid of V4B.

The output pair are biased for class A conditions, meaning that there is no flow of grid current, and the signals are re-established as one complete waveform across the centre-tapped primary of the output transformer T1. They are here coupled to the low-impedance secondary winding, which is tapped to suit a range of loudspeaker impedances.

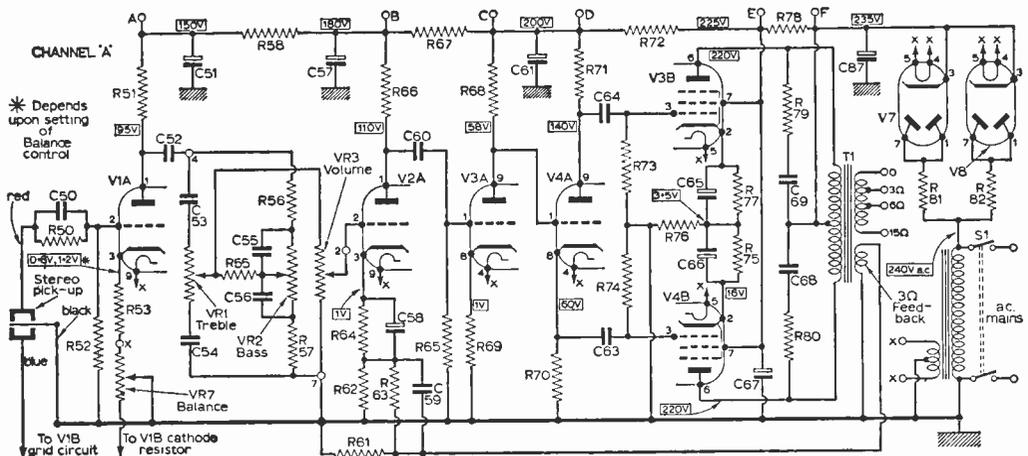


Fig. 7—The functions of all the components employed in this twin-channel, push-pull amplifier (Decca SG188) are given in the text.

Negative Feedback

A further secondary winding on T1 is employed for feeding back a fraction of the output signal to the cathode circuit of V2A as negative feedback. This is done through the frequency-selective network R63 and C59, with R61 as the other arm of a potential divider. In effect the feedback signals are reflected, via the cathode, to the control grid circuit of V2A in counteracting phase to the signals originally applied from V1A. This results in a reduction in total signal applied (hence another reason for the three voltage amplifiers), but its asset, of course, is that it cancels harmonic and other distortions, including hum.

The output valves are biased for class A by R75 and R77 in their cathodes, with the grid return circuit occurring through the balanced grid leaks R73 and R74. R76 is a low-value grid stopper arranged to prevent parasitic oscillations in the output stage. The cathodes of the output valves are decoupled by the electrolytics C65 and C66. This, along with the negative feedback, gives the stage a good damping factor, which is an essential requirement for high-quality reproduction.

Anti-resonant devices comprising R79/C69 and R80/C66 are connected across the primary of the output transformer and the screen grids of the output valves are connected in parallel and fed through R78, with C67 providing decoupling.

Each voltage amplifier stage is individually decoupled on the H.T. line, which is necessary in the interests of low-frequency stability, particularly when two amplifiers are sharing a common power supply. V1A is decoupled by R58/C51, V2A by R67/C57 and V3A by R72/C61.

Power Supply

The power supply used in this model is not isolated from the mains. It will be seen that an auto-transformer is used for feeding the anodes of the rectifiers V7 and V8 and this winding is connected to the mains supply via chassis. There is, however, a separate winding for the parallel-

connected valve heaters and is centre tapped to chassis to reduce the pick-up of hum to the smallest possible level.

The valve anodes are connected by limiting resistors, necessary to avoid overloading of the rectifiers on surges, while the cathodes are connected in parallel, with C87 serving as the reservoir capacitor.

Stereo Balance Control

In twin-channel stereo systems a separate control labelled "balance" is often featured. This simply serves to balance the overall gain of the two channels. In Fig. 7 the balance control is VR7 and it is connected in the cathode circuits of the two first voltage amplifiers and, since the slider is connected to chassis, equal gains should occur with the control set to the centre of its range. When the control is adjusted so that the resistance in one cathode circuit is reduced then that valve increases slightly in gain, while its partner decreases slightly in gain and vice versa.

All the voltages to be expected in the various stages are marked on the circuit and it will be obvious that the circuit of Channel B is identical to that of Channel A.

JOIN THE PRACTICAL GROUP

PRACTICAL TELEVISION 2/-
Every Month

PRACTICAL MECHANICS & SCIENCE 2/-
Every Month
Devoted to Mechanics, Science and Invention

PRACTICAL MOTORIST 1/9
Every Month

PRACTICAL HOUSEHOLDER 1/3
Every Month

RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt.

★ Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

● P.W. STRAND, MAYFAIR & SAVOY UNITS

We stock parts for the P.W. Strand Amplifier, Mayfair Pre-amplifier and Savoy FM Tuner. Detailed price lists are available.

● "P.W. MERCURY"

P.W. Mercury. (Osmor printed circuit version), including Mullard first grade transistors and instruction manual. Complete set of parts £9.19.6. Instruction manual available separately at 2/6 post free. Separate components supplied. Send for list.

● NEW ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● STEREO COMPONENTS

Morkanite ganged potentiometers as specified for the Mullard circuits. ● Log/Anti-Log. 500k, 1 meg., 2 meg. ● Log/Log. 50k, 250k, 1 meg., 2 meg. ● Lin/Lin 250k, 500k, 1 meg. All 10/6 each.

● TRANSISTORS

MULLARD. Reduced prices. Current production types, not rejects. All in makers' boxes. Postage 3d. on each. OC44, 9/3; OC45, 9/-; OC70 and OC71, 6/6; OC72, 8/-; OC72 Matched Pairs 16/-; OC78, 8/-; OC81, 8/-; OC170, 9/6; OC171, 10/6.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer, GEC 912 Plus. Fully detailed list on any of these sent upon request. Instructional Manuals: All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5. GEC912, 4/6. All post free.

● LATEST TEST METERS

	Cash Price	Hire Purchase
	Deposit	Mthly/Pmnts.
AVO Model 8 Mark II	£24. 0/0	£4.16.0 12 of £1.15. 2
AVO Model 8 with leather carrying case	£27.18.0	£5.12.0 12 of £2. 0.11
AVO Model 7 Mark II	£21. 0/0	£4. 4.0 12 of £2.10.10
AVO Multifinor	£9.10.0	£1.19.0 12 of 14/4
AVO Multifinor with leather carrying case	£11. 9/0	£2. 5.0 12 of 17/-
TAYLOR Model 127A	£10.10.0	£2. 2.0 12 of 15/8
CABY A-10	£4.17.6	£1. 7.8 3 of £1. 6.8
CABY B-20	£6.10.0	£2. 0.0 3 of £1.13.4
CABY M-1	£2.14.0	

Full details of any of the above supplied free on request. The AVO Models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

● OUTPUT TRANSFORMERS

GILSON: W0696A, W0696B, 50/6, post 2/6. W0710, 55/6, post 2/6. W0962, 62/3, post free; W0767, 27/-, post 1/6. W0196A, 57/6, post 2/6. W01032, 64/-, Post free.
 PARMKO: P3667, 75/-; P4131, 65/-; P5202, P5203, £5.18.6. All post free.
 PARMKO: P2629, 45/6; P2642, 43/3; P2643, 45/6. All plus post 2/9. P2641, 28/3, post 2/-; P2928, 15/3, post 2/-; P2932, 39/3, post 2/6.
 ELSTONE: OT/ML, 45/-, post 2/9; OT/3, 25/-, post 2/6.

● MAINS TRANSFORMERS

GILSON: W0741AB, 63/-, post free; W0839, 40/9, post 2/9; W01328, 58/6, post 3/6; W01288, 58/-, post 3/6; W01566, 80/-, post free; W01341, Choke, 36/-, post 2/-.
 PARMKO: P2631, 33/9, post 2/9; P2630, 52/6, post 3/3; P2644, 79/6, post free; P2930, 39/3, post 3/-; P2931, 54/6, post 3/3.
 ELSTONE: MT/DU, 45/-, post 3/3; MT/3M, 35/-, post 3/-; MT/510, 42/-, post 3/3.

● LOUDSPEAKERS

GOODMANS: Axiette 8in., £5.17.7; Axiom 10in., £7.0.0; 12in., Axiom 201, £10.7.0; 12in., Axiom 301, £14.10.0; 12in., Axiom 401 Bass, £8.14.0; 12in., Axiom 61 Bass, £13.14.0; Trebax Tweeter £5.4.0; X5000 (crossover unit, £1.19.0)
 WHITLEY: HF1016 10in., £7.15.0; HF1012 10in., £4.17.6; HF816 8in., £6.13.9; TF16 8in., £6.6.8; T10 Tweeter, £4.8.3; T359 Tweeter, £1.14.0; CX3000 Crossover unit, £1.11.6; CX1500 Crossover unit, £2.0.0. H.P. Terms available on all speakers.

● TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £3, minimum of 3/2. Over £3 and under £5, 1/6. Over £5 and under £10, 1/8. Over £10, no charge. Postage extra on CASH orders under £3 except where stated. Postage extra on overseas orders irrespective of price.

● TAPE RECORDING EQUIPMENT

	TAPE DECKS	Hire Purchase
	Cash Price	Deposit Mthly/Pmnts.
ALL CARRIAGE FREE		
B.S.R. TD2	£8.19.6	£1.16.6 12 of 13/7
Latest COLLARO Studio	£10.19.6	£2.3.6 12 of 16/4

We now stock the Martin Recorder Kits. These are partly assembled kits for complete tape recorders. The Amplifier Printed Circuit panels are completely wired, but the assembly of this and external components is left to the constructor. Very complete instructions are supplied. Send for leaflet.

MODEL C for Collaro Studio Deck £11.11.0.
 MODEL B for BSR TD2 Deck, £8.8.0.
 CARRYING CASES. Smart carrying cases are available to take the above amplifiers and decks. Fitted with speaker. For Model C Amplifier and Collaro Deck, £5.5.0. For Model B Amplifier and BSR Deck, £4.4.0.
 H.P. Terms available for amplifiers, cases and decks.

TAPE PRE-AMPLIFIERS
ARMSTRONG PA60-3. This is a ready made version of the Mullard Tape C Pre-amplifier. Price £16.16.0. Hire Purchase Deposit £3.8.0, and 12 monthly payments of £1.4.7.
MULLARD TAPE C PRE-AMPLIFIER. We stock complete kits and all components. Send for list.
MARTIN. Pre-amp kit for Collaro Studio Deck £8.8.0.

● "BRAND FIVE" RECORDING TAPE Post free.
 Long Play: 900ft. (5"). 18/6; 1200ft. (5 1/2"). 23/6; 1800ft. (7"). 35/-.

● JASON F.M. TUNER KITS

Kits supplied complete with every item needed including instruction manuals. Fully detailed list available. Separate items supplied, ask for price list. H.P. Terms available on any kit.
 FMT1, £8.12.6, FMT2 (less power), £7.15.0.
 FMT2 (with power), £9.12.6; FMT3 (less power), £9.9.6.
 FMT3 (with power), £11.7.6, Mercury 2, £10.14.6.
 J1V7, £14.12.6.

● TRANSISTORISE YOUR CRYSTAL SET

We have two new designs for Transistor amplifiers which can be used to greatly improve the signal from any crystal set. RLD4 Kit, one stage 12/-; RLD5 Kit, two stage 21/-; both post free. The kits are easy to build and very detailed instructions are supplied. Leaflet available.

● NEW MULLARD CONDENSERS

We now stock the following range of the new Mullard Miniature Foil and Polyester condensers as used in the latest TV and Transistor sets. Fully detailed list available giving full technical information and dimensions.
 Miniature Foil, 30 volt working for Transistor sets, .01 mfd, 74/-; .022 mfd, 90/-; .047 mfd, 90/-; .1 mfd, 11d.
 Polyester Tubular Capacitors. Moulded outer case designed to withstand accidental contact with the soldering iron. Tolerance 10%. 125v. range: .01mfd, .022mfd, .047mfd, all 9d. each. .1mfd, 1/2; .22mfd, 1/3; .47mfd, 1/6; 1mfd, 3/-.
 400v. range: .001mfd, .0022mfd, .0047mfd, .01mfd, .022mfd, all 9d. each. .047mfd, 1/2; .1mfd, 1/3; .22mfd, 1/6; .47mfd, 2/5. Postage extra.

● GRAMOPHONE EQUIPMENT

	ALL LATEST MODELS	Cash Price	Hire Purchase
	ALL POST FREE	Deposit	Mthly/Pmnts.
	RECORD CHANGERS		
GARRARD AUTOSLIM	£7.19.6	£1.12.6	12 of 12/8
GARRARD AUPOSIM			
De-luxe (GC8 PU)	£12.14.8	£2.11.8	12 of 18/8
GARRARD AUTOSLIM			
De-luxe (EV26A PU)	£13.12.9	£2.14.9	12 of 20/-
B.S.R. UA14 (TC8 PU)	£7.17.6	£1.12.6	12 of 12/1
B.S.R. UA14 Monarch (TC8 Series/LP78)	£8.17.8	£1.16.8	12 of 13/5
	SINGLE RECORD PLAYERS		
B.S.R. TU2 (TC8 PU)	£4.5.0	£1.5.0	3 of £1.8.4
B.S.R. G7 (238 PU)	£5.11.6	£1.13.6	3 of £1.9.4

TRANSCRIPTION UNITS
 GARRARD 4HF (GC8 PU) £7.19.6 £3.11.6 12 of £1.6.5
 PHILIPS AG1016 £13.13.0 £2.15.0 12 of £1.0.0
 Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

● HIRE PURCHASE TERMS

are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 6/- in the £. Service charge 5 per cent but minimum charge of 10/-.
 Six and Twelve months: Deposit 4/- in the £. Service charge 10 per cent, but minimum charge 20/-.


WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 4556

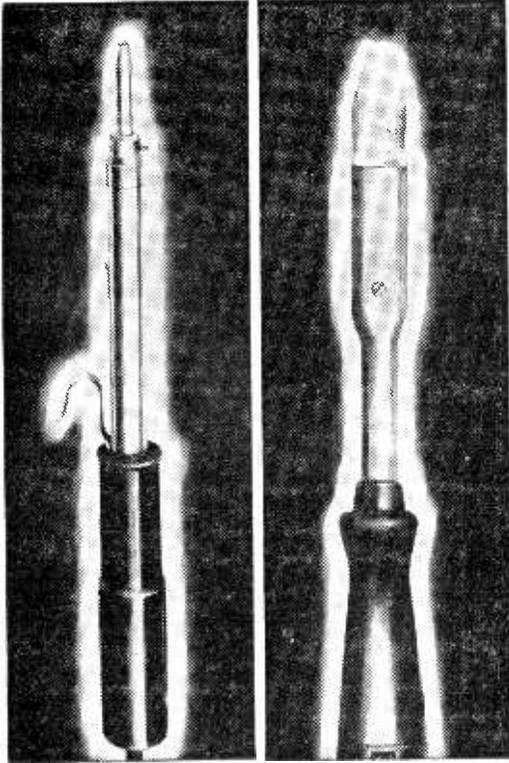Please note: Postal business only from this address



FOR A FIRST CLASS
SOLDERING JOB CHOOSE A

SOLO
TRADE MARK

ELECTRIC SOLDERING IRON

24/- ABOVE LEFT

29/- ABOVE RIGHT

25-watt instrument model For radio, TV, electronics, model making, jewellery and instrument work.

65-watt general purpose model For a wide variety of soldering jobs in home or workshop.

See them at electrical dealers, hardware stores or electrical showrooms.



Associated Electrical Industries Ltd.
Cable Division

DISTRIBUTION EQUIPMENT SALES DEPT
145 CHARING CROSS RD LONDON WC2A

D. & B. TELEVISION (Wimbledon) LIMITED
131 & 131A KINGSTON ROAD
SOUTH WIMBLEDON, S.W.19

Open Mon.—Sat. 10 a.m.—7 p.m. (Except Wed. 1 p.m.).
Nearest Tube Station South Wimbledon (Northern Line).

"COMPARE OUR PRICES"

FOR THE FINEST SERVICE IN THE COUNTRY
Your problems are our Business
LOOK! TRANSISTOR PRICES DOWN AGAIN.
MULLARD OC44 6/-, OC45 6/-, OCT1 5/-, *OC72 6/-, *OC76 7/-,
*OC77 12/-, *OC81 7/-, OC81D 6/-,
Complete set of 6 Mullard Transistors only 30/-. Comprising
OC44, two OC45's, OC81D, two OC81's, Matched Pair.
MULLARD DIODES: OA81 2/6, OA90 2/6, OA91 2/6.
G.E.C. Transistors: GET875 1/3, GET874 6/6, GET873 5/6,
*GET15 7/6, *GET114 4/6.
Complete Set of 6 G.E.C. Transistors comprising: GET874, two
GET873's, GET114, Matched Pair GET114. Only 25/-.
(*Available in matched pairs, 1/- extra).

COMPLETE NEW RANGE OF TRANSISTOR COMPONENTS IN STOCK

THREE BRAND NEW *STAR* BARGAINS

Designed for quality and outstanding value.
NEW R.T.D. 6 Watt Monaural Amplifier,
using heavy duty, double-wound mains Transformer. With separate rectifier winding. Valves: Rectifier, Driver and Output.
5 Controls: Switch, Volume, Bass, Treble
Middle. Heavy duty output Transformer.
METAL CHASSIS. All components brand new. Ready built.....ONLY £5.5.0.
COMPLETE or all parts in kit form. Point to point diagram. ONLY £3.15.0. P. & P. 3/6.



Build your own Portable Radio

Comprising Advance GEC drift-field transistors, high impedance 21in. speaker, powerful reflex circuit and a host of other features rank it as the finest value for the do-it-yourself enthusiast. Built-in Ferrite rod aerial brings you top notch reception both indoors and out, extremely efficient circuit greatly reduces battery drain—provides longer playing time. Uses popular 9V battery available everywhere. Attractive high impact ivory case is virtually unbreakable. Two controls—off/on volume and tuning. Ready drilled circuit board ensures fast, enjoyable assembly and perfect performance. **50/-**
Size 5x3x1 1/2in. All Parts Sold Separately. Price complete
Transistor Radio Ear Pieces, 8/9 P. & P. 3/6

Two Valve Amplifier Kit PY 82/PCL 82

Metal chassis. Point-to-point diagram. 3 watts output. **58/6**
Tone and volume controls. P. & P. 3/6.

ALL TYPES INTERNATIONAL OCTAL VALVES SUPPLIED
ALL VALVES ARE SOLD SUBJECT TO FULL GUARANTEE

CURRENT VALVE LIST

AZ31	8/6	ECF80	8/-	KT61	8/3	8P61	2/3	U9	6/3	787	8/3
B86	5/6	ECH35	9/-	KT63	6/3	C24	6/6	UY41	6/-	7Y4	7/3
CUH35	12/6	ECH42	7/6	KTW61	5/9	U24	10/1	UY95	6/6	10F1	4/6
D77	3/-	ECH81	7/6	KTW63	5/9	P25	12/-	M77	4/-	10C1	10/-
DAF91	5/-	ECL80	7/6	L53	2/9	U26	8/6	Z77	3/-	10C2	18/-
DAF96	7/-	ECL82	9/9	PC84	7/6	U31	7/-	3U4	4/9	10P13	8/9
DF91	3/9	ECL83	11/9	PC89	8/9	U37	17/-	5V4	8/9	10P14	8/9
DF96	7/3	EF39	4/3	PCF80	7/6	U50	5/6	5Y3	3/9	12AT6	7/3
DH63	6/-	EF50	1/3	PCF82	7/9	U52	5/-	5Z4	30/-	12AT7	4/6
DH77	4/6	EF80	4/6	PCF86	14/6	U91	9/6	6AL5	3/-	12AU7	5/6
DK91	8/-	EF83	6/3	PCW82	7/-	U94	9/-	6AM6	3/-	12AX7	6/6
DK92	7/6	EF86	8/9	PCW83	9/9	U202	14/6	6AT6	5/6	12AX7	6/6
DK96	7/3	EF89	6/6	PCW84	7/6	U301	12/6	6BG6	12/-	193B6	14/6
DL61	8/6	EF91	3/-	PCW85	15/-	U801	22/6	6BW6	7/6	201D	8/6
DL92	6/3	EP92	4/-	PL33	8/-	CA650	8/6	6D6	25/6	20F2	8/3
DL94	7/-	EL33	7/6	PL34	9/9	CAF42	8/-	6D6	3/-	20L1	12/6
DL96	7/-	EL38	12/-	PL38	14/6	UB41	7/6	6F1	4/6	20P1	9/6
EAC80	7/3	EL41	7/9	PL81	9/-	UBC41	7/6	6F12	3/-	20P3	12/-
EAF42	7/6	EL84	6/9	PL82	6/6	UCF89	7/6	6F13	6/6	20P4	16/6
EB41	6/6	EM80	8/6	PL83	6/6	UC84	12/6	6F14	9/-	20P5	14/6
EB91	3/-	EM81	8/6	PL84	6/9	UC85	7/6	6F15	9/-	278U	14/6
EB93	4/6	EM84	9/6	PV31	7/-	UCP80	14/6	6F33	6/3	30C1	7/6
EB94	7/6	EY51	7/9	PV32	10/-	UCH42	7/6	6L1	12/-	30FL1	8/3
EBF80	7/6	EY86	7/6	PY80	6/6	UC181	8/3	6L6	9/9	30L1	7/6
EBF89	8/3	EZ40	6/3	PY81	6/-	UC182	12/6	6L8	8/6	30P4	11/3
EBL31	9/6	EZ41	6/9	PY82	6/-	UF42	3/9	6L19	12/-	30P4	11/3
EBW32	6/3	EZ80	6/6	PY83	8/-	UL41	7/6	6SN7	4/6	30P12	8/-
EC84	4/6	EZ82	8/9	PY88	12/-	UL44	10/6	6V6	5/-	32KU	10/6
EC88	5/6	EZ84	12/6	PZ30	8/-	UL46	7/6	6U4	10/-	53KU	10/6
ECX84	7/9	KT33C	6/-	R18	10/-	UL84	7/6	6U5	7/3	34KU	8/6
ECX85	7/6	KT36	8/6	R141	2/3	U8	14/6	7C6	7/6	15KT	14/6

We pride ourselves that we can obtain and supply any TV spare. Please ask us for ANY components you may require we are almost certain to have them.

TERMS: S.A.E. all enquiries, C.O.D. 3/- extra.
C.W.O. Postage on Valves, 6d. each. C.R.Ts, 12/6 inc. insurance.
SATISFACTION ASSURED. RETURN POST SERVICE.
SUBJECT TO STOCK BEING AVAILABLE.

THIS HEAD IS SPECIALLY DESIGNED FOR USE WITH THE DIGITAL COUNTER DESCRIBED IN THE FEBRUARY 1962 ISSUE, THE COMBINATION BEING SPECIALLY SUITED FOR MAKING MEASUREMENTS ON RADIOACTIVITY IN LIQUID SAMPLES (SUCH AS RAINWATER).

THE SENSITIVITY OF THE COMBINATION IS SUCH THAT EVEN SMALL LEVELS OF RADIOACTIVITY PRESENT FROM NATURAL CAUSES (FAR BELOW CONTAMINATION LEVELS) CAN BE EASILY MEASURED.

IT SHOULD BE POSSIBLE TO BUILD THE UNIT DESCRIBED FOR LITTLE MORE THAN £10.

An Advanced GEIGER HEAD

By E. DEXTER

THE theoretical circuit shown in Fig. 1 is very similar to the simple Geiger Head published with the author's Digital Counter in the February issue. The main difference lies in the choice of a completely different type of Geiger-Tube, the Mullard MX124/01. The actual tube is enclosed in a thin-walled glass envelope coaxially within a sealed-on test-tube for containing the liquid to be tested. Thus the liquid intimately surrounds the Geiger-Tube proper, which accounts for the very high sensitivity.

H.T. Voltages

The MX124/01 has an unusually low operating voltage (400 to 500) compared to other tubes of this type. This is a distinct advantage for amateur circuitry. The arrangement of the H.T. feed in the circuit is somewhat unusual, a conventional 300V positive supply in conjunction with an additional 100V negative supply being used.

There are two good reasons why this arrangement has been adopted. Firstly, +300 and -100 are becoming standardised outputs for stabilised power supplies, and are thus also the main outputs of the "Experimenter's Power Pack" published recently in this magazine, which is admirably suited for operation of this unit.


Secondly, the EC92 cathode-follower head-amplifier can be run off the same H.T. supply in this arrangement, as is evident from Fig. 1. The power supply requirements are seen to be identical to those of the Digital Counter, and the two units may be run simultaneously off the "Experimenter's Power Pack".

It is, for reliable and accurately reproducible results, highly desirable to run this equipment off a stabilised power supply, though other ordinary simple power supplies could be tried. It will then probably be necessary to use separate power supplies for this head and for the Digital Counter.

It is *absolutely essential* that the total voltage applied to the tube never exceeds 450V, as otherwise flashover and possible destruction of the tube can take place. Thus the positive H.T. must not exceed 350V.

Threshold Voltage

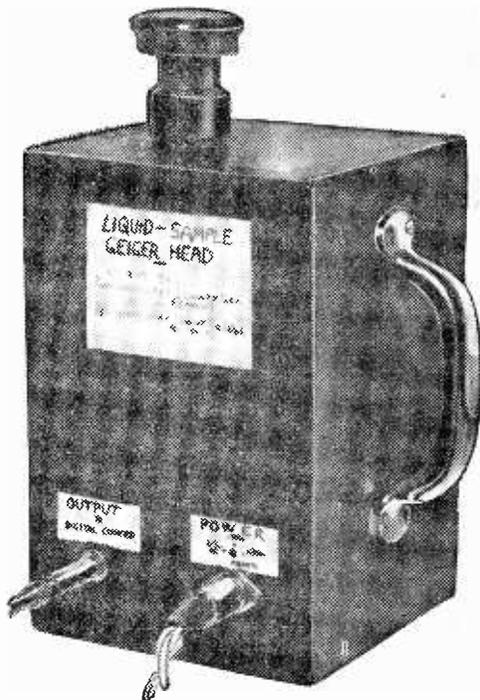Mullard quotation for the Threshold Voltage for the MX124/01 is "maximum 400V". Individual samples vary and the tube in the author's prototype was found to have a threshold at 360V. It is desirable to operate the tube at approx. 50V above threshold which gives 410V for the author's prototype.



The finished instrument.

When the unit is initially put into operation, the output should be connected to an oscilloscope, and the pulses observed as the positive stabilised H.T. is varied on the power pack. As the H.T. voltage is gradually reduced, the pulse amplitude will also decrease, until it vanishes at the threshold voltage.

The voltmeter reading should then be noted, and the H.T. increased by about 40 to 50V. This assures the proper operating point having been set, and it should be checked in the same manner from time to time as the tube ages.

Pulse Amplitude

Fig. 2 is self-explanatory as far as the theoretical details of the generation of the pulses are concerned. The treatment is, of course, simplified, as no account has been taken of chemical effects within the tube also leading to rapid extinction of each discharge.

Nevertheless, the capacity-effects sketched in Fig. 2 generally dominate and are sufficient to give a measure of control over the output pulse amplitude, by means of adjustment of C1. The larger the capacitance of C1 and *Cstray*, the greater is the charge-per-pulse passing through the tube, i.e. the greater the strain on the tube. It is thus desirable to keep both of these capacitances small.

Naturally, any capacitive loading of the tube increases the violence of the discharge on each pulse, and it may thus seem strange that a circuit is proposed which deliberately introduces such loading.

The advantage gained, however, is the production of a substantial pulse giving secure operation of simple counter circuits aimed to avoid all snags and critical effects in the input stages, and this advantage is considerable for amateur purposes.

Tube Life

The price paid for this advantage is a shortening of tube life, to the region of at least 100 million counts, instead of the almost infinite life achievable in more critical specialised circuits. While such a life would be too short for high-counting-rate professional laboratory use, it is still more than ample for the amateur uses intended in this article.

One will be operating at counting rates around 100 per minute for the purposes envisaged, so that even with the minimum life of 100,000,000 counts, at least 15,000 operating hours are certain. Probably much more.

The prototype shows that, after completing more than 2,000 operating hours under these conditions, changes of tube characteristics are at the most a fraction of 1% of those of a brand new tube.

Slow Counting Rates

The adverse effects on dead-time and plateau-slope are of little importance at the slow counting rates intended, though probably seriously limiting the suitability of this circuit for work at normal laboratory counting rates of some hundred or more per second. The plateau-constancy over long periods of usage under the conditions specified has proved itself in practice, and the use of stabilised power supplies adequately removes errors of counting due to plateau-slope for the present purposes.

The actual values of C1 and *Cstray* do not affect the output pulse amplitude as much as the *ratio* of their values. The *total* pulse-voltage generated is necessarily equal to the difference between operating point and threshold, which we deliberately set at about 40 to 50V.

This pulse voltage is seen in Fig. 2 to appear across C1 and *Cstray* in series, the two capacitances thus forming a voltage-divisor. Only the portion appearing across *Cstray* is passed on to the cathode follower V2, and hence to the output. If a reasonably large part of the total pulse voltage is to appear at the output, therefore C1 must at

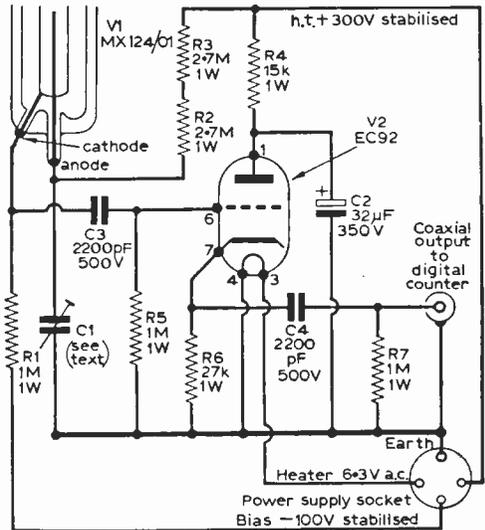


Fig. 1—The circuit of the head.

least be equal to, or somewhat larger than *Cstray*.

This is the reason for including an actual physical component for C1, part of which is made up by the inherent stray anode capacitances of the tube and wiring, and the rest by a physical component in the form of a pair of twisted insulated wires.

It is desirable to set conditions such that, finally, C1 (total) and *Cstray* are approximately equal. This condition is realised when the pulse output voltage from the unit is about half of the threshold-excess, i.e., some 20 to 25V peak. The output pulses should be observed on an oscilloscope in comparison with A.C. sinewave voltages of known amplitude, using the same Y-amplifier gain in all cases.

The length of twist of the insulated wires forming C1 is altered, until the output pulses are observed to have 20 to 25V amplitude. It need hardly be said that the operating point must *previously* have been set 40 to 50V above threshold, as described above.

The Cathode Follower


This stage is fully conventional. C3 blocks the negative 100V D.C., allowing only the positive pulses to pass, and be reproduced accurately at the same amplitude and form at the output. R4

(Continued on page 729)

Easy - to - build kit - sets of



highest quality at lowest cost

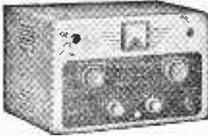


DX-40U

AMATEUR TRANSMITTER. Model DX-40U. Self-contained. 80-10 m. Power input 75 w. C.W., 60 w. peak, C.C. phone. Output 40 w. to aerial. Provision for V.F.O.

£33.19.0

AMATEUR TRANSMITTER. Model DX-100U Covers all amateur bands, 160-10 m. 150 w. D.C. input. self contained with power supply. Modulator, V.F.O.

£74.19.0

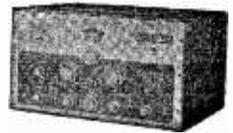

DX-100U

AUDIO SIGNAL GENERATOR. Model AG-9U. 10 c/s-100 kc/s, switch selected. Distortion less than 0.1%. 10 v. sine wave output metered in volts and dB's £21.9.6

VALVE VOLTMETER. Model V-7A. Measures volts to 1,500 (D.C. and R.M.S.) and 4,000 pk to pk. Res. 0.1 Ω-1,000 M Ω, D.C. input impedance, 11 MΩ. With test prods, leads and standardising battery £13.18.6

R.F. SIGNAL GENERATOR. Model RF-1U. Gives accurate source of R.F. up to 100 Mc/s on fundamentals and 200 Mc/s on harmonics. Up to 100 mV output on all bands. £12.15.6

SINGLE SIDEBAND ADAPTOR, Model SB-10U May be used with most A.M. transmitters. Less than 3W R.F. input power required for 10W output. Operation on 80, 40, 20, 15 and 10m bands on USB, LSB or DSB £39.5.0

HI-FI 18W STEREO AMPLIFIER Model S-99. Ganged controls. Stereo/mono gram, radio and tape recorder inputs. Push-button selection. Printed circuit construction £27.19.6

HI-FI AM/FM TUNER. Tuning range: FM: 88-108 Mc/s. AM: 16-50, 200-550, 900-2,000 m. Tuning heart (£5.5.6 incl. P.T.) and I.F. amplifier (£20.13.0) sold separately. Printed circuit board Total £25.18.6

SHORTWAVE TRANSISTOR PORTABLE. Model RSW-1. Two short bands, crawler and medium £22.8.0

6-TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers, printed circuit, 7 x 4in., high flux speaker. Real hide case £14.3.0

TAPE RECORDING/PLAYBACK AMPLIFIER Stereo (TA-IS) ... £24.10.0 Monaural (TA-1M) £19.2.6

STEREO CONTROL UNIT USC-1. Luxury model with press-button inputs to suit any pick-up or tuner and most tapeheads. Output 1.3 v. R.M.S. per channel. Printed circuit construction. £19.10.0

Money Saving "PACKAGED DEALS" of Complete Stereo Equipment from £46.6.0



MALVERN

HI-FI EQUIPMENT CABINETS. Range available to meet various needs. Details on request. (MALVERN equipment cabinet illustrated on the left) from £11.12.6 to £18.10.0. "COTSWOLD" MFS SYSTEM. For the smaller room. Measures 36in. high x 16½in. x 14in. deep. Almost identical performance with standard Cotswold £23.4.0

Assembled models also available—prices on request. Deferred terms available over £10. Free Delivery U.K.



COTSWOLD

"COTSWOLD" HI-FI SPEAKER SYSTEM. Acoustically designed enclosure "in the white" 26 x 23 x 15½in. 12in. bass speaker with 2in. speech coil, elliptical middle speaker. Pressure unit covers the full freq. range of 30-20,000 c/s., complete with cross-over unit, level control, etc. £23.4.0

AUDIO & DO-IT-YOURSELF accessories also available

Please send me FREE CATALOGUE (Yes/No) _____
 Full details of model(s) _____

 NAME _____
 ADDRESS _____

PW12

DAYSTROM LTD.

Dept. P.W.12, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

THE LINEAR L1/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 5 ins. In addition two high impedance input sockets are provided for microphone and gram, etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81, H.T. and L.T. power supply point is included for a radio tuner.

FREQUENCY RESPONSE

± 1 d.b., 30-20,000 c.p.s.

MAXIMUM POWER OUTPUT

in excess of 14 watts.

SENSITIVITY

L.P. 220 m.v. for 10 watts. 78 r.p.m. 220 m.v. for 10 watts. Radio/Microphone 40 m.v. for 10 watts.

TREBLE LIFT CONTROL

+ 10 d.b. to -22 d.b. at 12,000 c.p.s.

BASS CONTROL


+ 14 d.b. to -10 d.b. at 50 c.p.s.

HUM LEVEL

Referred to maximum output and including integral pre-amp.—70 d.b.

NEGATIVE FEEDBACK

21 d.b. in main loop.

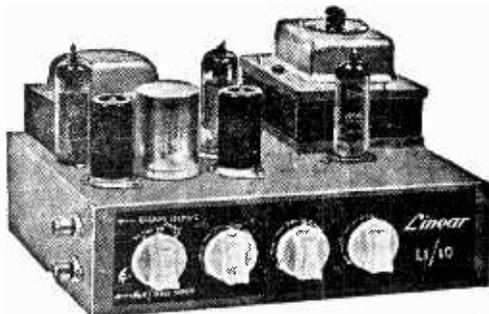

HARMONIC DISTORTION Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3-and-15-ohm speakers. Chassis finish stoved Gold hammer.

HIGHEST QUALITY Retail Price **13 GNS.**
MAXIMUM RELIABILITY
AT A PRICE YOU CAN AFFORD

Send S.A.E. for descriptive literature

TRADE ENQUIRIES to

Also Available—THE L.45.A compact High Quality 4.5 watt amplifier. Size approx. 7.5-5.5 in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner etc. B.V.A. valves used are ECC83 EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5.19.6.

THE LT45 TAPE DECK AMPLIFIER. A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loud-

speaker and practically any make of deck. Negative feedback equalisation adjustment by multi-position switch for 1½, 3½ and 7½ in. per second. Retail price 12 gns.

DIATONIC 10-14 WATT. High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

CONCORD 30 WATT. Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

L50 50 WATT AMPLIFIER. Size approximately 14 x 10 x 8 in. Sensitivity 25 mV. Output for 3 and 15 Ω speakers. Retail price 22 gns.

L5/5 STEREO AMPLIFIER 5 + 5 watt 12 gns.

LINEAR PRODUCTS LTD.

ELECTRON WORKS, ARMLEY LEEDS

EXPLORE THE WORLD ON THIS I-VALVE SHORT-WAVE RADIO



Total Building Cost


35/6

P. & P. 2/-.

★ Receives speech and music from all over the world. Construction price includes valve and one coil. Covering 40-100 metres.

Can be extended to cover 10-100 metres. Suitable headphones 11/8. Can be converted to 2 valve.

THE IMPERIA

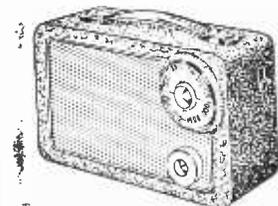

An easy to build 6 Transistor Portable superhet, which can be built by the constructor. Pre-Assembled circuit board for easy construction. All components are new. 5 inch Speaker giving good tone and output.

Attractive case of exclusive design 8½ x 5½ x 2½ with gold plated grille. Specially designed matching coil for use in car. Only first grade fully guaranteed matched transistors and diodes are used. Anyone can build this set for £7.18.6. P. & P. 3/- (Long wave 6/- extra). Everything supplied except soldering iron.

All parts sold separately. Wiring diagrams and parts list supplied free with orders, or separately, 1/6 each item. AFTER SALES SERVICE

The **AIROLO** 6-STAGE POCKET TRANSISTOR PORTABLE




In attractive two-tone contemporary case, with gold plated speaker grille and attractive dial. Size only 5½ x 3½ x 1½ ins. No aerial or earth required—completely self contained. Genuine 3in. high flux PM speaker. First grade transistors. Push pull output—250 milliwatts. Volume control with on/off switch. Condenser tuning. Easy assembly on eyeletted circuit board. Total Building Cost **£4.19.0** P. & P. 2/6. (Long wave 6/- extra).

The RIETI 6-STAGE SUPER SENSITIVE TRANSISTOR PORTABLE


Simple to Build. All First Grade Components. A truly portable transistor radio giving full medium wave reception. Incorporates 6in. High Flux Speaker, pull-push output, first grade transistors.

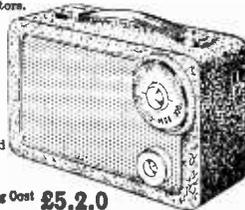High-Q ferrite aerial, socket for car aerial, pre-tagged circuit board for easy construction. Attractive case with gold plated grille. Long wave 8/- extra. Total Building Cost **£52.0** P. & P. 2/6.



CRYSTAL RECEIVER Covering medium wave band. Ideal for the beginner! All components including case for **11/6** P. & P. 1/6. Suitable headphones. 11/8 extra.

THE "TINYMITE"

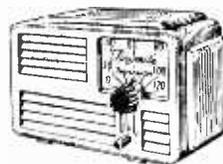

EASY TO BUILD TWO STAGE TRANSISTOR SET

The set that looks like a Radio Set. Attractive Case. Mini .0005 Tuner. High Q Litz Coil. Works for months off No. 3 Battery suitable to construct in 15 min. Medium & Long Wave coverage. Total Building Cost **25/6** P. & P. 1/6.

Suitable headphones 11/8

MINISETS LTD. Hatherley Mews, London E.17.

(Continued from page 726)

and C2 give heavy decoupling for the stage. C4 and R7 remove any D.C. component from the output otherwise resulting from the cathode circuit of V2.

The purpose of V2 is *not* voltage amplification as the output voltage of the geiger tube is ample for the digital counter, etc. The purpose is, rather, to reduce the impedance, allowing transmission of the output signal on reasonably long lengths of coaxial cable without loss. This function certainly amounts to a form of power-amplification, however.

Geiger-Tube Screening

The manufacturers specify operation of the tube in a 2in. thick all round lead container, which can weigh anything up to half a hundredweight! Whilst this is certainly essential for efficient industrial use, it is by no means necessary for amateur use, provided the factors concerned are understood and taken into account. At any rate, it is clear why the bare tube alone must be removable in an industrial arrangement, and mercury-cup connectors used: the whole unit with lead casing would be far too heavy and cumbersome to move about!

The advantages of the heavy lead casing are principally twofold, neither of which is essential for the amateur. Firstly, and most important, the tube is thereby screened from ambient levels of X-rays or other radiation from other experiments and equipment operating on the premises nearby, which have nothing to do with, but would seriously interfere with, the experiment running with the tube in question. This danger of interference is not likely to arise under amateur conditions, provided such sources as luminous watches the clocks are kept away from a running experiment.

Secondly, the lead casing would absorb a large portion of the "Cosmic" background radiation coming from outer space, etc. This reduces the "background-count per minute" to be subtracted from a count made with a liquid sample, i.e. it improves the "signal-to-noise ratio", giving better resolution and shorter required counting times for a given desired accuracy.

This may be important for industrial concerns where time is money, but is unimportant for amateur usage. The saving in expense, and convenience in construction, achieved by omitting a lead screen outweighs all other considerations for the amateur.

Important Points

When operating the tube without a lead screen, the following two points must be watched carefully:—

(a) The unit is vulnerable to interference from external radioactive sources of sufficient intensity. Such sources must be removed to a distance of at least three yards, or kept fixed in position during an experiment, their effects being included in the subsequently subtracted "background count" made without the test-liquid in the tube. In particular, do not move the hands about near the unit during a count whilst wearing a wristwatch with luminous figures.

(b) The background count will be higher with the tube completely empty than when filled with pure non-active distilled water. This is due to the water acting as a weak screen, absorbing some of the low-energy components of the cosmic radiation.

Thus the "background-count" should always be made with the tube filled with pure distilled water, because the water-content of the subsequently counter test liquid will give the same reduction of cosmic background. Failure to observe this procedure can cause quite serious errors.

In the author's prototype, the background-count was found to be 40.4 per minute with the tube completely empty, but only 38.3 per minute with the tube full of distilled water. The count with a certain sample filled into the tube was 47.2 per minute, representing a correct signal of 8.9 per minute due to the sample.

Had the empty-tube background count been used in error, the sample-signal would apparently have been only 6.8 counts per minute, an error of well over 20%!

When using a lead screen the weaker cosmic-radiation components are absorbed anyway, so that then there will be no difference in background counts for an empty tube or one filled with distilled water.

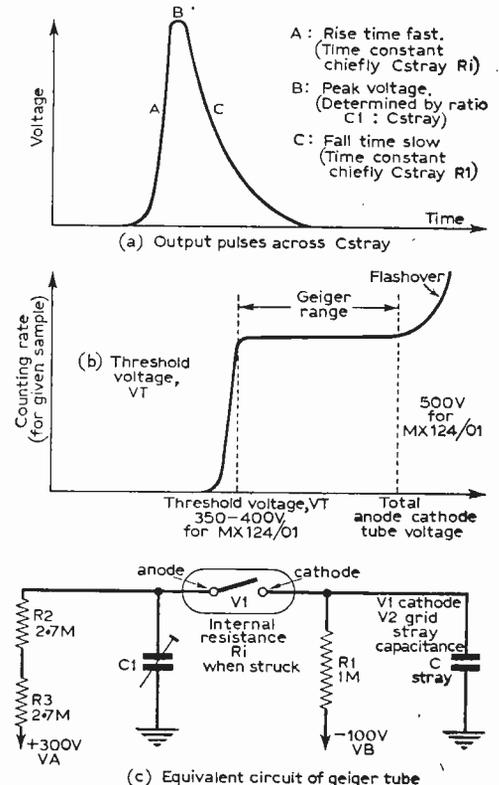


Fig. 2—Production of pulses and effect of C1: (a) output pulses; (b) threshold voltages; (c) equivalent circuit of the geiger tube.

Photoelectric Effect

Geiger-Tubes of the type here specified are often sensitive to light, giving an appreciable counting-rate in response to illumination. This effect was found to be immeasurably small for normal wavelengths of light in the author's prototype. A background-count of 40.4 per minute was obtained with the empty tube, whether completely dark or whether strongly illuminated with a couple of 25W bulbs 5in. away.

The accuracy limits of this experiment were about plus-or-minus one count per minute. Thus error due to normal room illumination, if present at all, is likely to be less than 2%. Nevertheless, it is desirable to keep the tube dark, for safety. The arrangement adopted satisfies this condition, in that most of the tube length is inside the body of the wooden case.

The rest is covered by the black P.V.C.-Tape, to within about $\frac{1}{4}$ in. of the spout, which is covered by a cap, also desirable to reduce evaporation of the sample liquids. Any suitable opaque material of suitable shape and size can be used for the cap, preferably insulating and loosely fitting. *Do not* use a cork of any sort, as this could press down on and break the delicate inner construction of the tube.

Care of the Geiger-Tube

Counting times of more than three hours maximum should seldom if ever be required with the sensitivity achieved by this head. Samples prepared as already discussed in the "Digital Counter" article, and with the further remarks below, normally require counting times of only 30 to 60 minutes for sufficient accuracy. Thus samples need never be left very long in the tube.

Prolonged presence of samples in the tube can cause diffusion through the thin glass of the inner unit, raising the background count permanently.

Thus all samples should be poured out *immediately* after conclusion of a count, and the tube swilled out thoroughly at least three times with clean or distilled water.

Never use tarry, greasy or sticky liquids which could soil the tube permanently or render cleansing extremely difficult. Although dilute acids do no damage avoid using caustic alkalis and do not insert warm or hot liquids into the tube.

Preparation of Samples

Procedure outlined in the "Digital Counter" article should be observed. Whilst it is still necessary to concentrate rainfall and other water samples, lower concentration factors can be used than with the simple Geiger-Head described in the "Digital Counter" article.

The simple Geiger-Head, furthermore, gives really quick definite signals only with those rainfall samples representing the verge of real contamination. With present levels of radioactivity in rainfall, long careful overnight counts are required for reasonable quantitative measurements but with the unit described in this article, definite strong and reliable signals are very easily and very quickly produced even with rainfall of present levels of activity.

Components List

V1 Mullard Geiger Tube MX124/01

V2 EC92

Resistors (All resistors 1W carbon)

R1 1M Ω R5 1M Ω

R2 2.7M Ω R6 27k Ω

R3 2.7M Ω R7 1M Ω

R4 15k Ω

Capacitors

C1 See text C3 2200pF, 500V

C2 32 μ F, 350V electrolytic C4 2200pF, 500V

Miscellaneous

B7G valveholder and screening can

4-pole panel socket

Coaxial panel socket

Tagstrip. Material for cabinet

Quantitative Data

Serious experimenters, and particularly schools and clubs, will be interested in doing quantitative work with this apparatus, to determine not only relative values of radioactivity in liquid samples but also absolute values in terms of equivalent weight of radium per unit volume of the liquid.

The author has had available standard solutions of uranium and thorium, as well as possessing a high-voltage Geiger-Tube of similar type supplied with extensive calibration charts from the manufacturers. Using this apparatus as comparison standard, the prototype MX124/01 has been carefully calibrated. The results of this work, here given in full, may reasonably be supposed to be applicable to any sample of the MX124/01 tube used under the conditions specified in this article.

The Curie

The unit used for measuring absolute values of the radioactivity of substance is the Curie. A quantity of substance having the same effective activity as one gram of radium is said to have an activity of one Curie. This unit is extremely large, so that convenient practical units are the micro-Curie (μ C) and the pico-Curie (pC) representing a millionth part, and a millionth of a millionth part, of a Curie, respectively.

One milligram or ordinary thorium has an activity of about 100pC. This was found to give, when effectively contained in the (exactly) 8 c.c. of liquid needed to fill the MX124/01, an increase of counting rate of about 10 per minute with the head described in this article.

Similarly, one milligram of ordinary uranium has an activity of about 350pC, and was found to give an increase of counting rate of about 35 per minute when present in the 8 c.c. contents of the MX124/01.

The sensitivity to this type of radioactive substance is thus about one count per minute per 10pc present in the contents. These substances, i.e. heavy elements, emit principally alpha-rays (helium nuclei) and gamma-rays (exceedingly short wavelength wireless waves), the tube responding principally to the latter.

(To be continued)

UNIVERSAL AVOMETERS



Guaranteed perfect working order. Supplied complete with leads, batteries and instructions. Model "D" 34 range £8.19.6 Model "M" 50 range £11.0.0 Registered Post 5/- extra.

COSSOR 1035 DOUBLE BEAM OSCILLOSCOPES
Guaranteed perfect working order. £45 each. Carriage £1.

7.5 K.V.A. AUTO TRANSFORMERS
0-115-230 volts. Brand new boxed. £15. Carriage 10/-.

230/250 VOLT A.C. MOTORS
41 x 3 in. dia., 90 watts, 5,000 r.p.m. tin. spindle. £2/6. P.F. 1/6.

1 K.V.A. ISOLATION TRANSFORMERS
230 v. PRI 230 v. Sec. Boxed, £5 each. Carriage 10/-.

VARIAC TRANSFORMERS
24 amp., 230 volt primary, 185 to 250 volt output. £12.10.0. Carriage 10/-.

TELEPHONES TYPE "L"
Generator Bell Ringing, 2 line connection. With batteries, full y tested, 69/6 per pair. Carriage 5/-.

100 AMP A.C. METERS
Nalder Thompsons 6in. scale. Brand new, boxed, 65/-. P.F. 3/6.

AMERICAN C.B.S. TAPES
Highest quality, professional grade. Brand new. Guaranteed.

5in. Std.	600ft.	13/-
5in. L.P.	900ft.	16/6
5in. D.P.	1200ft.	32/-
5 1/2in. Std.	900ft.	18/6
5 1/2in. L.P.	1200ft.	19/6
5 1/2in. D.P.	1800ft.	37/-
7in. Std.	1200ft.	21/-
7in. L.P.	1800ft.	28/6
7in. D.P.	2400ft.	47/-

S.A.E. for full bargain lists. Please add postage.

PANEL METERS

100µA	2 1/2"	F.M.	D.C.	42/6
100µA	3 1/2"	F.M.	D.C.	62/6
1 mA	2 1/2"	F.M.	D.C.	25/-
1 mA	4"	F.M.	D.C.	72/6
300/30 mA	2 1/2"	F.M.	D.C.	9/6
350 mA	2 1/2"	F.M.	D.C.	10/6
2 v.	2 1/2"	F.M.	A.C.	17/6
10 v.	2"	Proj.	A.C.	15/6
300 v.	2 1/2"	Proj.	A.C.	19/6
300 v.	2 1/2"	F.M.	A.C.	25/-
500 v.	2 1/2"	F.M.	A.C.	25/-
120 v.	3 1/2"	F.M.	D.C.	32/6
1500 v.	2 1/2"	Electrostatic	25/-	

FIELD TELEPHONES TYPE "F"
Suitable for many applications. Generator bell ringing. 2 line connection. With batteries and wooden carrying case, fully tested. £4.19.6 per pair. Carr 5/-.

P.C.R. COMMUNICATION RECEIVERS

6 valves. Frequency coverage on 3 bands: 850-2,000 metres, 190-550 metres and 6-18 Mc/s. Super slow motion drive. AE trimmer, tone control, built in speaker. AS NEW £6.19.6 each. Carr. 7/6.

P.C.R.2 RECEIVERS

850-2,000 metres, 190-550 metres 6-22 Mc/s. output for phones or 3Ω speaker. As new £5.19.6. Carr. 7/6. Both above models can be supplied with internal power unit to operate on 200/250 v. A.C. at 39/6 extra or alternatively plug-in external power units are 35/-.



NATIONAL H.R.O. RECEIVERS



BRAND NEW! Senior model, table mounting. Complete with a full set of 9 coils covering 50 kc/s to 30 Mc/s. Supplied complete in original transit cases, £25. Carr. 30/-. Power units to operate direct from 200/250 volt. A.C. 59/6 extra.



PRECISION COMBINATION VOLTMETER/AMMETER FOR A.C. AND D.C.

Two separate instruments housed in polished wood case, 6in. scales with knife edge pointers.
Ranges:
Volts A.C. and D.C. 160-300-600 v. Amps. A.C. and D.C. 25-50-150-200A.
Supplied complete with all current shunts, leads and leather carrying case. Manufactured by Elliott Bros. Supplied brand new. £9.19.6 each. Carriage 7/6.

MINE DETECTOR No. 4A

Will detect all types of metal. Fully portable. Complete equipment supplied tested with instructions, 39/6. Carriage 10/6. Battery 8/6 extra.

COLLARO STUDIO TAPE TRANSCRIBOR


Brand new 1962 model, 3 speeds, 3 motors, digital counter, etc. Fitted with latest bradmatic heads and interlock button. Supplied with spare spool, instructions, fixings. 10 gns. each. Carr. paid.

CLASS "D" WAVEMETERS MK. II

Heterodyne crystal controlled frequency meter covering 1.9 to 8 Mc/s. 6 volt D.C. operation. Supplied brand new. Complete with crystal, valves, spare vibrator, headset and instruction manual. 59/6 each. P.P. 3/6.

CT-53 SIGNAL GENERATORS

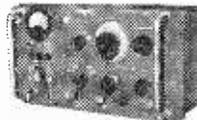Precision instruments covering 8.9 to 15.5 Mc/s. and 20 to 300 Mc/s. on 6 bands. Variable attenuator from 1 microvolt to 100 millivolts. Operation 110/200/250 volts A.C. Supplied in perfect working order. Complete with calibration charts. 19 gns. each. Carriage 10/6.



PRECISION A.C. AND D.C. VOLTMETERS

Two ranges, 150 and 320 volts. 3 inch mirror scale with knife edge pointer. Housed in polished wooden case. Ideal for schools, labs., etc. Supplied brand new. £5.19.6 each. P.P. 3/6.

R.C.A. AR.88 LF RECEIVERS

These world-famous 14-valve receivers are offered in excellent condition. Fully tested and checked before dispatch. Frequency coverage on six bands is 75 to 550 Kc/s and 1.5 to 30 Mc/s. Completely self-contained except phones or speaker. Operation for 100-250 volt A.C. £32.10.0 each, carriage 30/- ex.



Hours of Business: 3 LISLE STREET, 9 a.m.—6 p.m. Half Day Saturday
34 LISLE STREET, 9 a.m.—6 p.m. Half Day Thursday

JEMCO 4,000 OHM/VOLT TESTMETER

1% Precision Resistors throughout. Single control system for all ranges. Highly accurate. Sensitivity 4,000 Ω/volt A.C. and D.C.



Ranges:
D.C. volts: 0-10-50-250-500-1,000V.
A.C. volts: 0-10-50-250-500-1,000V.
D.C. current: 0-250 vA 0-25-500mA
Resistance: 03-0K Ω 0-300K Ω 0-3M Ω
Decibels: -20 to +96 db (2 ranges)

Meter sensitivity: 100 microamp. 62/6 each P.P. 2/6.

JEMCO 20,000 OHM/VOLT TESTMETER

As above but with increased sensitivity and extended resistance range (0-5M Ω). 87/6 P.P. 2/6. Either type brand new. Guaranteed with leads, prods, batteries, instructions.

L.T. METAL RECTIFIERS

All full wave, bridge connected. Brand new, guaranteed.
12/18v. 1.5A. 3/9 24/36v. 4A. 15/6
12/18v. 2.5A. 6/3 24/36v. 5A. 45/-
12/18v. 4A. 8/6 36/48v. 2A. 19/6
12/18v. 6A. 12/3 36/48v. 4A. 29/6
12/18v. 10A. 22/6 36/48v. 6A. 32/6
12/18v. 15A. 37/6 48/60v. 2A. 21/-
24/36v. 1A. 7/3 48/60v. 10A. 22/6
Please add postage

L.T. TRANSFORMERS

All primaries tapped 200/250 volt. 1 Battery Charging, 3.5, 9 or 17 volt, 1 amp., 9/8. Ditto 2 amp., 14/3. Ditto 4 amp., 18/6. 9 or 17 volt, 6 amp., 26/-.
2 Model T, 2 1/2, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 volt, 2 amp., 18/6. Ditto 4 amp., 27/6. Ditto 5 amp., 37/6. Add Postage.

AUTO TRANSFORMERS

Step-up, step-down, tapped 0-115-200-250 volts. 15w., 9/-; 60w., 12/6; 150w., 18/6; 200w., 27/6; 300w., 42/6; 500w. 67/6; 1,000w., 99/6; 1,500w., £6.19.6. P.P. extra.

R.C.A. PLATE TRANSFORMERS

Pri. 200/250 v. sec., 2,000-0-2,000 v. 500 mA. tapped 1,500 v. New, boxed, £6.10.0. Carriage 15/-.

DUMONT KIOSKI DOUBLE BEAM C.R.T.

Twin Gun. Brand new, boxed, 59/6. P.P. 3/6.

12 Ohm 12 Amp RHEOSTAT

Gear'd slider type, new boxed, 15/6 each. P.P. 3/6.

PAINTON 100KΩ 3/4 DIA. INSTRUMENT POTS

Fully screened, precision wirewound, 10/6 each. P.P. 1/3.

CADMIUM SULPHIDE PHOTOCELLS

Very sensitive, full data supplied, 12/6 each. P.P. 6d.

MINIATURE PANEL METERS

For 1 1/2in. dia. panel hole.
0-50 µA 39/6 0-300 v. D.C. 27/6
0-5 mA 32/6 "S" meter 35/-
0-1 mA 27/6 "V" meter 42/6
0-5 mA 27/6

Send S.A.E. for Bargains Lists

G.W. SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C2

LISTEN TO THE WORLD
on "TELSTAR"
OUR EASY TO CONSTRUCT
I-VALVE SHORT-WAVE RADIO



Total Building Cost **35/-**
P. & P. 2/-


★ **Receives speech and music from all over the world.** Construction price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve.

R.C.S. TAPE TUNER

Record your favourite programmes. Variable Medium wave tuning. Triple wound Super HI-Q coil. Chassis and components colour coded. Easily constructed. Size 3 x 1 1/2 x 1 1/2 in. All parts, instructions and layout plans. **30/-** P. & P. 1/6

The **'REVILO'**

5-STAGE POCKET TRANSISTOR PORTABLE

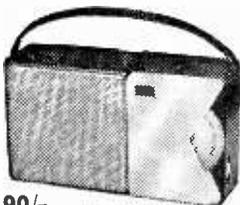

Total Building Cost **90/-**
Including earpiece P. & P. 2/6.

In attractive two-tone contemporary case, with gold plated speaker grille and attractive dial. Size only 5 1/2 x 3 1/4 x 1 1/2 in. No aerial or earth required—completely self contained. Genuine 3in. high flux PM speaker. Socket for personal listening. First grade transistors. Push-pull output—250 milliwatts. Volume control with on/off switch. Counter tuning. Easy assembly on eyeleted circuit board.

All parts available separately. Constructional details on any one of the above sets, 1/6 each. (Supplied free with orders).

OUR SUPERB 5-STAGE SUPER SENSITIVE TRANSISTOR PORTABLE

Simple to Build. All First Grade Components. A truly portable transistor radio giving full medium wave reception. Incorporates 5in. High Flux Speaker, push-pull output, first grade transistors. High-Q ferrite aerial, socket for car aerial, pre-tagged circuit board for easy construction. Attractive two-tone case.

Total Building Cost **95/-** P. & P. 2/6

CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components including case for P. & P. 1/6. Easily converted to 1-transistor or 2-stage transistor receiver. **10/6**

AMAZING RESULTS from OUR LATEST

5-Stage Transistor Receiver
▲ highly sensitive receiver using top grade transistors and components. Fully tunable over medium wave.
★ Can be built in 1 hour.
★ High flux moving coil speaker.
★ Built in ferrite rod aerial.
★ Specially designed coils for maximum signal strength.
★ Volume on/off control.
★ Eyeleted circuit board.
★ Easy to follow building plans.



Total Building Cost **59/6** P. & P. 2/6.

Send S.A.E. for **FREE** Layout Plans and Price Lists for these two wonderful sets.



"PERSONAL TWO"

For Private Listening
An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 1 1/2 x 3 x 4 1/2 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. Two transistors plus diode.

Total Building Cost **32/6** P. & P. 1/-
Earpiece 7/6 extra if required.

R.C.S. PRODUCTS (RADIO) LTD. 11 OLIVER RD., LONDON, E17 (Mail Order Only)

with a **MARTIN RECORDAKIT**

YOU CAN BUILD YOUR OWN



TAPE RECORDER QUICKLY, EASILY, CHEAPLY WITH NO PREVIOUS EXPERIENCE

With a Martin Recordakit everything you need is supplied, ready to assemble—even down to wire cut to length. The easiest and cheapest way to own a Hi-Fi quality Tape Recorder. Fill in the coupon for full details.

Post to: MARTIN ELECTRONICS LTD.
155 HIGH STREET, BRENTFORD, MIDD.
Please send free leaflet on Martin Recordakits

NAME _____
ADDRESS _____
(In block letters).....PW.2....

T N

rade ews

STABILISED POWER UNITS

THE latest versions (Mk. III) of the LEXOR stabilised power units models LT.12-05 and LT.24-05, are now available.


New features of the Mk. III include a much reduced longitudinal noise factor and an improved overload and short-circuit protection. The two models available have output voltage ranges of 5.5-14V or 18-28V. The output voltage of either instrument is continuously variable and may be adjusted either by a panel knob or a pre-set control. Both instruments will deliver output currents up to 0.5A continuously at all voltage settings.

The units are mounted in steel instruments cabinets 8in. x 5in. x 5½in. finished in grey hammer stove enamel with contrasting blue panels. The price of the new Mk. III units is £25 7s. and they are made by *Lexor Electronics Limited, 25-31 Allesley Old Road, Coventry, Warwickshire.*



The new Multicore solder dispenser.

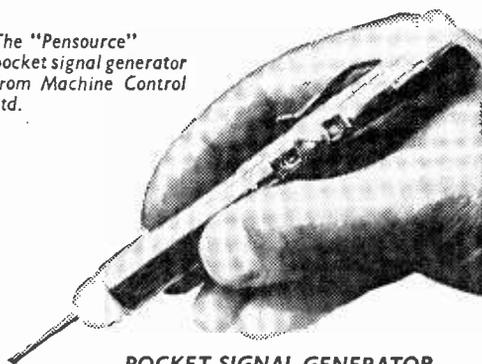The "Pensource" pocket signal generator from Machine Control Ltd.




POCKET SIGNAL GENERATOR

FOR engineers, radio and TV servicemen who require a small and convenient form of input for testing or fault finding, Electronic Machine Control Ltd., have produced the "Pensource" range of pocket signal sources.

These instruments are made available in several ranges and give an output of approximately ¼V.

Basically each "Pensource" is a transistorised oscillator built into a robust chromium plated case. The supply to the oscillator is provided by a 1½V penlight cell and under normal conditions of use, should last approximately four to six months.

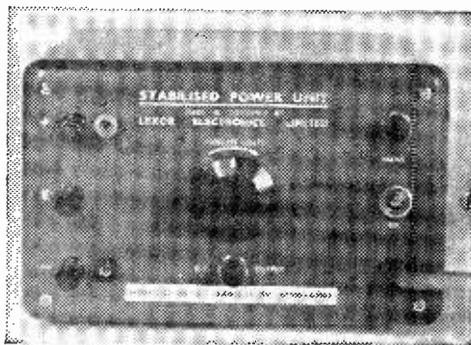The "Pensource" costs £4 10s. and a leatherette case is also available at an extra cost of 10s. 6d. The makers are *Electronic Machine Control Ltd., Mayday Road, Thornton Heath, Surrey.*




One of the new Lexor stabilised power units.

NEW SOLDER PACK

NEW from Multicore Solders Limited is a solder dispenser especially suitable for use by the amateur constructor. It is, in fact, an extruded aluminium tube, the top being tapered to a delivery hole through which the solder is drawn as required. This arrangement prevents the solder tangling and the flat base of the dispenser allows it to be stood firmly on the work bench, leaving the user complete freedom of both hands whilst working.

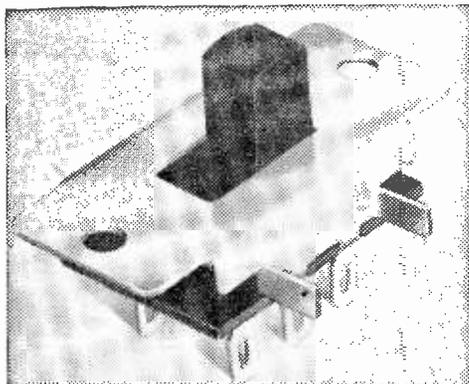The contents of the new pack is a 16ft length of 18s.w.g. Ersin Multicore Savbit alloy and its price is 2s. 6d. complete. The manufacturers are *Multicore Solders Ltd., Maylands Avenue, Hemel Hempstead, Hertfordshire.*




One of the new switches from Carr Fastener Co. Ltd.

NEW SLIDE SWITCHES

JUST incorporated with the range of components produced for the electronics industry by Carr Fastener Co. Ltd., are two new slide switches. These are identical in specification but differ slightly in their mounting facilities. Both switches are of the double-pole, double-throw type, and can be used for radio wavechange, instrument or any relatively low voltage switching application.

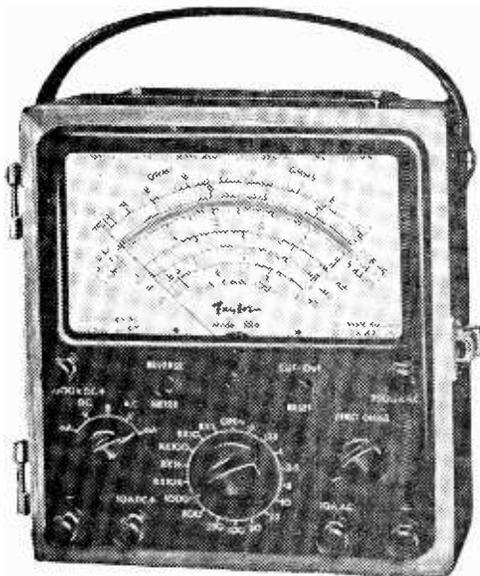Constructionally, the switches differ only in their steel shell, one having vertical fixing lugs and the other having two 0.125in. diameter holes at 1.125in. centres and alternative side-fixing lugs. Carr Fastener Co. Ltd., Stapleford, Nottingham.



This new multimeter is manufactured by Taylor Electrical Instruments Ltd.


MINIATURE SOLDERING IRONS

RECENTLY A.N.T.E.X. Ltd. have added to their range of Precision soldering irons. Amongst the new additions is the model E240, a lightweight instrument operating from 230-240V mains and with a power consumption of 20W.

The novel design of these irons makes them easy to handle and attractive. Interchangeable bits are available to fit this model as well as a wire-stripper attachment. The price of the complete iron is 35s. and the makers are A.N.T.E.X. Ltd., Grosvenor House, Croydon, Surrey.

MULTIRANGE METER

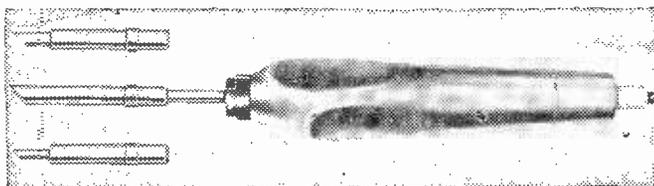THE model 88B multimeter from Taylor Electrical Instruments Ltd., is similar in operation to their popular model 88A, but is somewhat reduced in size. It is available in



The model E.240 soldering iron is made by A.N.T.E.X. Limited.

either a bakelite or wooden case.

The sensitivity of the instrument is 20,000 Ω /V, and other features include a mirror scale, an overload protection device and a reverse polarity facility.

Among the ranges included in the instrument are, resistance ranges up to 50M Ω and decibel ranges. The instrument will also measure capacitance and inductance but a model 388 adapter is required.

Another accessory which is available is a high voltage probe for measurements up to 25kV.

The two batteries used in the meter are located in a separate compartment. The types used are Ever-Ready U.2 and B.121.


The makers of this new multimeter are Taylor Electrical Instruments Ltd., Montrose Avenue, Slough, Buckinghamshire.

THE TRANSISTOR CLOCK

ONE intriguing result of research in radio engineering—the transistor principle—has now been applied to clock-making. The Kundo (Crown Manufacturing Co. Ltd.) transistor clock, on display at the recent Watch and Jewellery Trade Fair, has an operating mechanism of unusual simplicity. A magnet attachment to its pendulum dips into a coil at each oscillation, producing, by induction, a voltage pulse which, fed into the transistor, triggers the flow of current from the battery to the drive coil. A driving impulse is thus imparted to the pendulum.

Needing no maintenance, this extraordinary timepiece runs continuously for no less a period than three years!

MULLARD 3-3 HI-FI AMPLIFIER

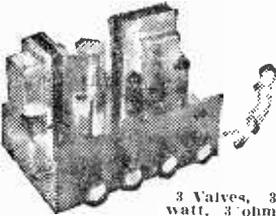

3 Valves, 3 watt, 3 ohm and 15 ohm output. A really first-class Amplifier giving Hi-Fi quality at a reasonable cost. Mullard's latest circuit. Valve line up: EF86, EL84, EZ81. Extra HT unit LP available for Tuner Unit addition. This is the ideal companion Amplifier for FM tuner units.

TECHNICAL SPECIFICATION— Freq. Response: ±1 db, 40 c/s-25 Kc/s. Tone controls: Max. Treble Cut 12 db at 10 Kc/s. Max. Bass Boost 14 db. at 40 c/s. Sensitivity: 100 Mv. for 3 w. output. Output Power (at 100 c/s): 3 w. at 1% total harmonic distortion. Hum and Noise Level: At least 70 db below 3 w.

COMPLETE KIT (incl. Valves, all components, wiring diagram and special quality sectional Output Trans.). ONLY £6.18.6. Carr. 5/-. Complete wired and tested, 3 gns. Bronze Escutcheon Panel, Printed Vol. Knob, Bass, On-off, supplied with each Kit. Wired O/P socket power and additional smoothing for Tuner Unit, 10/6 extra. Recommended Speakers—WB HF102 95/-, Goodmans AXIOM 110 65. etc.

SPECIAL BARGAIN OFFER

A self-contained Portable Unit incorporating latest BSR 4 speed Auto Changer Record Player and famous High Fidelity "Full-Fi" Xtal Pick up with Turnover Cartridge, fitted with LP and 78 Sapphire Styli. Internal 2 valve Amplifier of modern design with variable Tone and Volume Controls. This, together with a quality P.M. Speaker ensures a high standard of reproduction. The whole is housed in a robust wooden Cabinet attractively styled in 2 Tone contemporary leather cloth with contrasting polka dot relet.

Kit consists of 3 sub assemblies already wired. Grub screw connections between Units only necessary—absolutely no soldering. Originally built to be sold at 17 Gns. Recommended Buy!



Standard Mod-I £12.10.0
Carr. & Ins. 7/6
Autochanger Unit—BSR Model UA21. Amplifier—valves UCL82, UY85 and 7 x 4in. Elliptical Speaker. Cabinet size 17 x 14 1/2 x 8 1/2 in.

RECORDING TAPE—Reduced Prices

Famous American Columbia (CBS) Premier Quality Tape at NEW REDUCED PRICES. A genuine recommended Quality Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted with leader and stop coils.

	Standard	Long Play	Double Play
5in.	600ft. 13/-	900ft. 17/6	1,200ft. 31/6
5 1/2in.	900ft. 16/-	1,200ft. 19/6	1,800ft. 37/6
7in.	1,200ft. 21/-	1,800ft. 28/6	2,400ft. 47/6

P. & P. one reel 1/- 6d. on each additional reel

SPECIAL BARGAIN. 3in. Message Tape, 150ft., 3/9 P. & P. 6d. 3in LP, 25ft 4/9, 3in DP, 300ft 6/6

Plastic Tape Reels . . . 3in. 1/3, 5in. 2/-, 5 1/2in. 2/-, 7in. 2/3
Plastic Spool Containers . . . 5in. 1/6, 5 1/2in. 2/-, 7in. 2/3

COAX 80 OHM CABLE
High grade low loss Cellular air spaced Polythene—1in. diameter. Stranded cond. Famous mfrs. Now only 6d. per yard. Bargain Prices—Special Lengths—20 yd. 9/-, P. & P. 1/6. 40 yds. 17/6, P. & P. 2/-, 60 yds. 25/-, P. & P. 3/-.
Coax Plugs 1/-. Sockets 1/- Couplers 1/3. Outlet Boxes 4/6.



COLLARO STUDIO TAPE RECORDER KIT

SPECIAL BARGAIN OFFER. Comp. Kit only £25.0.0 Carr. 12/6.

Famous mfrs. surplus offer—Listed 42 gns. A quality Tape Recorder Kit based on Mullard famous design—EF86, EC83, EL84, EM84 and Rectifier. Specially designed Kit for Collaro latest Studio Deck. Freq. response + 3 db, 60 c/s—10 Kc/s. Amp. and Power Pack already wired, inter unit wiring only required. Cabinets size: 18 x 16 1/2 x 6in. finished in contemp. 2 tone blue Rexine with gilt Speaker Escutcheon, Magic Eye Indicator Circuit and Tech. Hi/Book, supplied free with Kit. Send 2/6 now for full details of to-day's outstanding Tape Recorder Bargain.

Cabinet £3.15. P. & P. 9/6
Amplifier Kit £8.19.6. P. & P. 5/-
Speaker 7 x 4 13/16. P. & P. 2/-
If above items are purchased together.

£12.19.6 P. & P. 10/-

BARGAINS 4-SPEED PLAYER UNITS

Single Players Carr. 3/6
Garrard 4 S.P. £8.19.6
Garrard TA MK.2 £7.19.6
Collaro "Junior" 75/-
B.S.R. Latest TU12 79/6
E.M.I. Junior 885 89/6
Auto-Changers Carr. 3/-
Collaro "C 60" £7.15.0
B.S.R. (UA14) £7.10.0
Garrard "Auto-slim" £8.12.6
Garrard Model RC209 9/1 gns.

Volume Controls— 5k-2 Meg-ohms. 3in. Spindles Morganite Mid-ge Type 1 1/2in. diam. Guar. 1 year. LOG or LIN ratio. 2W Sw. 3/-. DP Sw. 4/6. Twin Stereo less Sw. 6/6. DP Sw. 8/-.

RECORD PLAYER CABINETS

Cabinet Price **£33.0**
Carr. & Ins. 5/-



Contemporary style, rexine covered cabinet in two tone maroon and cream. Size 18 1/2 x 13 1/2 x 8 1/2 in. fitted with all accessories including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, etc. Uncut record player mounting board 14 x 13in. supplied. **2 x VALE 2-WATT AMPLIFIER** Twin stage ECL82 with vol. and neg. feedback. Tone control, P.C. 200 250 v. with knobs, etc., ready wired to fit above cabinet. £2.17.6. P. & P. 1/6.

6in. Spkr. & Trans., 22/-, P. & P. 2/- Complete Kit, including UA14 Unit as illustrated, £12.19.6, Carr. 7/6. **JACK PLUGS.** Standard 2 1/2" Irganic Type, 2/6. Screened Ditto, 3/3. Miniature 1 1/2", 2/3. Screened Ditto, 2/6.

ENAMELLED COPPER WIRE— 1lb. reels 14g-20g, 2/6; 22g-26g, 3/-; 30g-40g, 3/9. Other gauges quoted for.

Ersin Multicore Solder 60/40 3d. per yard. 1lb. 2/6, etc.

Condensers—Silver Mica. All values, 2Pf to 1,000Pf, 6d. each Ditto. Ceramics 9d. Tub. 450V T.C.C., etc., 0.001 mfd. to 0.01 and 0.1/350V. 9d. 0.02-0.1/500V. 1/-, 0.25 Hunts 1/6. 0.5 T.C.C. 1/9, etc. (Close Tol. S/Micas—10% 5Pf-500Pf 8d. 600-5,000Pf 1/-, 1% 2Pf-100Pf 9d. 100Pf-500Pf 11d. 575V sec-5,000Pf 1/6. Rest as above.) Full Range 10 ohm 10 meg-ohms 20% 1 and 1/2 W 3 1/2, 1 W 5 1/2. (Mid-ge Type modern rating) 1W 6d., 2W 9d. 1 1/2 W 11d. 10% 1 W 5d., 1 W 7d. 5% 1 W 9d., 1% 1 W 1/6.

JASON FM TUNER UNITS

Designer-approved kits of parts:
JMT1, 5 gns. 4 valves, 20/-
FMT2, £7. 5 valves, 37/6
JTV MERCURY 10 gns.
JTV2 £13.18.6, 4 valves, 32/6.

NEW JASON FM HANDBOOK, 2/6, 48 hr. Alignment Service 7/6. P. & P. 2/6.

TYGAN FRET (contemp. Pat.)
12 x 22in. 3/-, 12 x 18in. 3/6
12 x 24in. 4/-, 18 x 24in. 6/- etc.

Speaker Fret — Expanded bronze anodised metal 1 1/2 x 1 1/2 in. diamond mesh, now 4/6 sq. ft., Multiples of 6in. cut max. width, 4ft.

Electrolytics All Types New Stock			
TUBULAR		CAN TYPES	
25/25V	1/9	8+8/450V	4/6
50/12V	1/9	8+16/450V	5/6
50/30V	2/-	32+32/275V	4/6
100/25V	2/-	60+60/350V	6/6
8/450V	3/9	80+250/	6/6
16/450V	5/6	275V	18/6
16+16/45V	3/9	100+200/	12/6
32+32/450V	6/6	275V	12/6

Transistor Components

Midget L.F.'s—466 Kc/s. 9/16in. dia. 5/6
Osc. Coil—M/W, 9/16in. dia. 5/3
Osc. Coil—M. & L.W. 3/9
Midget Driver Trans. 3.5:1 8/9
Midget O/Put Trans. P.P. to 3ohms, 6/9.
Ferrite Aerial M. & L.W., Car aerial coil, 9/3.
Elect. Condensers—Midget Type 1 mid-50mfd ea. 1/9. 100 mfd. 2/-; 12V wkg.
Condensers—0.1 mfd. to .04mfd 9d.; .05 mfd. to 1mfd. 1/-; .25mfd 1/3; 5 mfd. 1/3.
Tuning Condensers—"JB" "OO" 208 pF. + 175 pF 8/6, with Trimmers 9/6, Single 365pF 7/6. Sub min. Hn. J.B. Dile min. .0001. 00030r .0005 7/-, each.
Midget Vol. Control—with edge control knob. 5K ohms with switch, 4/9, less switch 3/9.
Speakers P.M.—2in. Plessey 75 ohms 15/6, 2 1/2in. Continental 8 ohms 13/6, 2 1/2in. E.M.I. 3 ohms 17/6, 7 x 4in. Plessey 35 ohms 23/6.
1 1/2 W Plug Phones—Min. Continental Type 3ft. lead, Jack plug and socket, High Imp. 8/- Low Imp. 7/6.

TRANSISTOR BARGAINS

Brand	New	BVA	1st	Grade
	OC45	8/6		GET114 6/6
	OC45	8/6		OC72 7/6
	OC81	7/6		OC70 7/6
	2/OC81	15/6		OC71 6/-
	XA102	10/6		OC78 7/6
	XA101	9/6		GEX34 2/9
	XA103	7/6		OA70 2/9
	XC101	8/6		OAB1 2/9

Special offer: One OC44, two OC45: 21/6. One OC81D, two OC81's (matched pair) 19/6.


Send for detailed bargain lists, 3d. stamp. We manufacture all types Radio Mains Transf. Chokes, Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotations by return.

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m. Wed. THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1lb. 9d.; 1lb., 1/3; 3lb., 2/6; 5lb., 2/9; 8lb., 3/6.

TRANSISTOR AMPLIFIERS

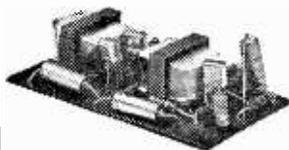1/2 WATT 3 TRANSISTOR AMPLIFIER READY BUILT



45/- Plus 1/6 P. & P.

- 1/2 w. Peak output.
- Output to 3 ohms speaker.
- Push-pull output stage.
- 9 volt operation.

A printed circuit high gain amplifier. Size 3 1/2" x 2" x 1 1/2". Three Newmarket Transistors (two NKT 251 and NKT252). Ideal for intercom or as record player amplifier.

2 WATT 4 TRANSISTOR AMPLIFIER READY BUILT

A 2 watt 4 transistor amplifier with 2 driver and push-pull stage. Size 4 x 2 1/4 x 1 1/2. Plus 1/6 P. & P.

62/6

THE NEW TRANSISTOR 6 PANDORA

Designed By
Mel Electronic

USING NEW HIGH GRADE PARTS

TOTAL BUILDING COST

ONLY £6.19.6



FULL AFTER SALES SERVICE

Obtainable from your local stockist or in case of difficulty DIRECT FROM MEL ELECTRONIC

- MEDIUM WAVE & LIGHT ON LONG WAVE
- 6 TRANSISTORS + DIODE
- SUPERHET CIRCUIT
- AUTOMATIC WAVECHANGE
- 500mW PUSH-PULL OUTPUT
- PRE-TINNED PRINTED BOARD
- EXCELLENT RESULTS

Please send S.E.A. for full details of these and other transistor designs;

MEL ELECTRONIC CO.

REAR OF: 240 HIGH STREET
BECKENHAM, KENT

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.,
- Electrical Eng.,
- Civil Engineering,
- Radio Engineering,
- Automobile Eng.,
- Aeronautical Eng.,
- Production Eng.,
- Building, Plastics,
- Draughtsmanship,
- Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I. Mech.E.
- A.M.I.C.E.
- A.M.I. Prod.E.
- A.M.I.M.I.
- A.I.O.B.
- A.F.R.A.S.
- B.Sc.
- A.M. Brit. I.R.E.
- City & Guilds
- Gen. Cert. of Education
- Etc... etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V. Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing, Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
 (Write if you prefer not to cut page)

NAME _____

ADDRESS _____

SUBJECT OR EXAM THAT INTERESTS ME _____ SE/12



THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

A Simple 3-Valver

By T. M. Bush

THIS unpretentious little receiver can be built very cheaply. Considering the extreme simplicity of the circuit, it has a very good performance and with careful manipulation of the controls, the single tuned circuit will enable all the more powerful transmissions to be received clear of interference.

Circuit

The EF91 is a high slope miniature valve which is available ex-equipment very cheaply indeed. Three of them are used in this receiver. The first is arranged as a pentode R.F. amplifier but it will be noticed from Fig. 1 that there is no tuned circuit associated with it. The high slope of the valve, however, goes a long way towards repairing this omission and quite a worthwhile gain is achieved. Because the EF91 does not have variable-mu characteristics it was necessary to achieve some method of gain control other than by variation of bias, and the problem was solved very satisfactorily and simply by feeding the signal from the aerial to the slider of a 1M potentiometer in the grid circuit.

The second valve, connected as a triode, is used as a conventional leaky grid detector, regeneration

being applied through the variable capacitor VC1 to sharpen the tuning and increase the sensitivity. Because the R.F. stage isolates the aerial from the tuned circuit the tuning is not affected by aerial loading and if by chance, as will sometimes happen, too much reaction is applied, the resultant oscillations will not be radiated to the annoyance of the neighbours. Resistor R5 and capacitors C2 and C3 remove the R.F. component from the output and the audio signal is passed via the capacitor C4 to V3, the output valve. This is another EF91, again triode connected. The optimum load could not be discovered but this is not of much importance with the triode connection and an output transformer having a ratio of 50:1 was found very satisfactory for a 3Ω loudspeaker.

Power Supply

A miniature double-wound mains transformer of the instrument type, having an output of 20mA at 250V and 1A at 6.3V supplies the power in conjunction with a contact-cooled metal rectifier. Smoothing is provided by the resistor R8, and the associated electrolytic capacitors C5 and C6. A

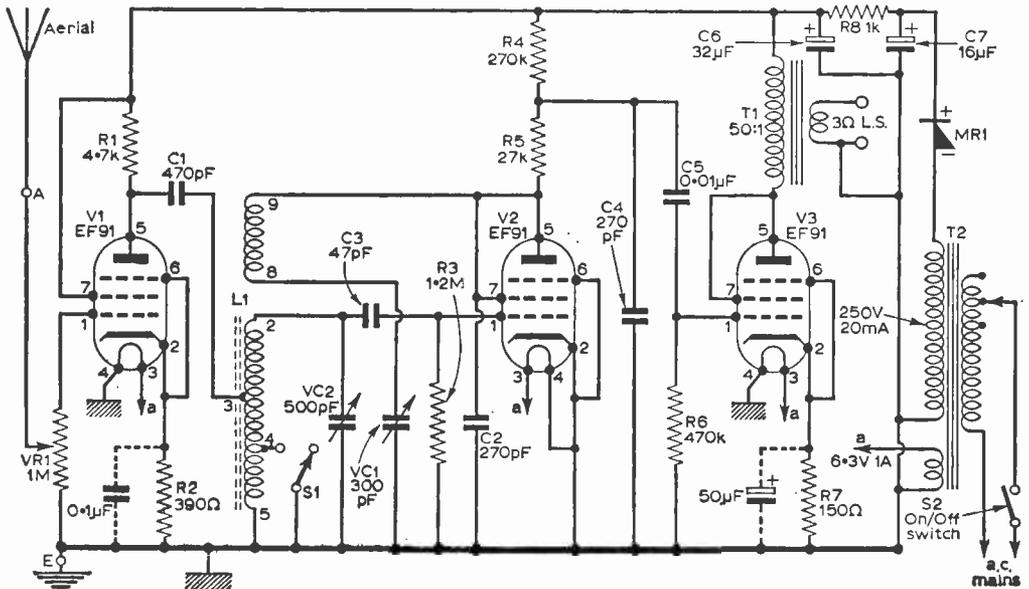


Fig. 1—The circuit.

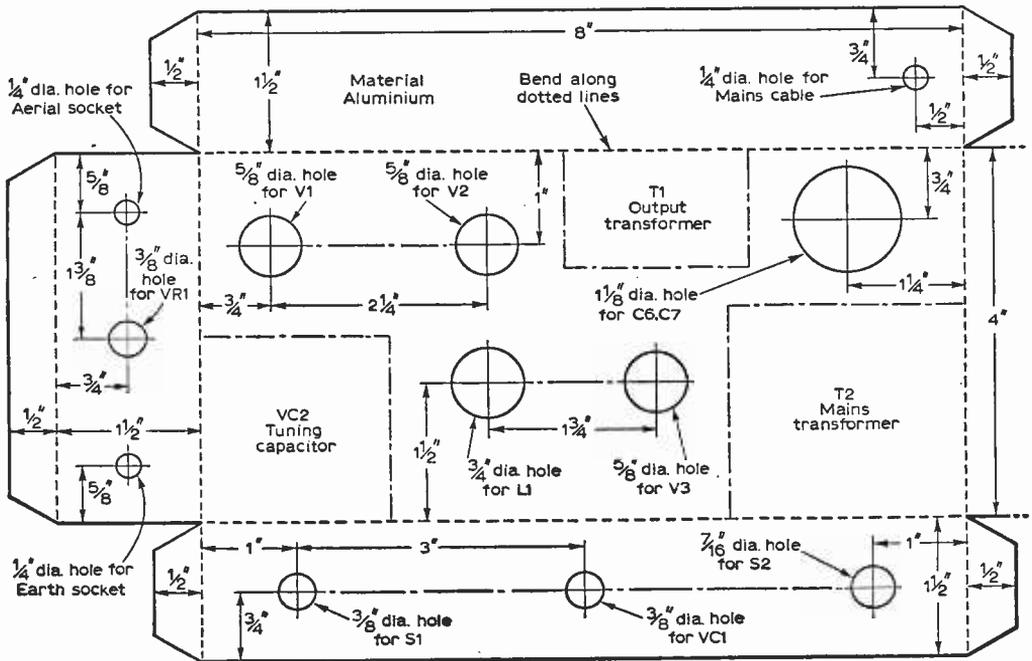


Fig. 2—The drilling dimensions of the chassis.

pilot or dial light, if fitted, should be 6.3V 0.04A, so as not to exceed the rating of the transformer winding. A separate on/off switch was fitted in the prototype but there is no reason why mains switching should not be incorporated with VR1. The power consumption from 240V A.C. mains is less than 20W.


Modifications

It will be noticed that the bias resistors of V1 and V3 are not bypassed. Consequently, if greater gain is required, capacitors may be fitted across them as shown in dotted outline in Fig. 1. A further increase in gain can be obtained by reducing the value of R2 to 150Ω but this will increase the current through the value and is permissible only if the mains transformer can accept the extra load. The total H.T. current in the prototype was exactly 20mA.

Construction

The prototype was constructed on a chassis of 18s.w.g. aluminium sheet measuring 8in. x 4in. x 1 1/2in., details of which are given in Fig. 2. This gives plenty of room for standard size components with the exception of the reaction capacitor, VC1, where a miniature must be used in order that it may be accommodated within the depth of 1 1/2in.; alternatively, the chassis could be made deeper. Construction may proceed in any convenient order. The layout and the arrangement of the wiring and components is not at all critical so long as the

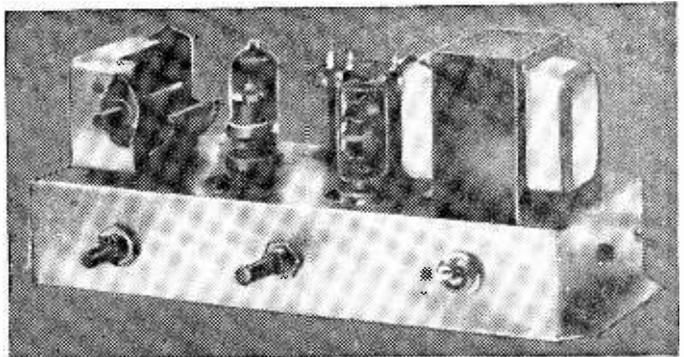connections around V2 and the coil are kept to a reasonable length. Tinned copper wire of 22s.w.g. covered with sleeving is recommended for all the wiring, details of which are given in Fig. 3. The loudspeaker is connected direct to the secondary terminals of the output transformer on top of the chassis. It is good practice to connect one of these



The receiver nearing completion.

terminals to chassis and a solder tag should be fitted for the purpose on one of the transformer holding-down bolts.

Components

Resistors may be 1/4W or 1/2W, except R8 which should be 1W. The capacitors have to withstand
(Continued on page 741)

"THE ROVER" 7 (5 wavebands) PERFORMANCE WILL AMAZE YOU!

★ (7 Transistor plus 2 Diode designs)

- ★ Med/Long Waves, Trawler Band and 2 S.W. to approx. 17 metres.
 - ★ Rich-toned 5in. Speaker.
 - ★ Sockets for car radio use.
 - ★ Telescopic aerial for S. Waves.
 - ★ FERRITE ROD AERIAL FOR M/L.
 - ★ Air spaced gauged Tuning Condenser.
 - ★ Uses latest Mullard Transistors.
- Total cost **£7.9.6** P.P. 5/6.
- ★ Push-Pull output for room filling volume.
 - ★ Two tone Cabinet with gold fittings.
 - ★ Case size 12 x 8½ x 3½in.
 - ★ Parts price list and data 3/-.



THE SUPER SEVEN

★ (7 Transistors plus 2 Diodes)

- ★ 2 R.F. STAGES.
- ★ Mullard and Surface Barrier Transistors.
- ★ Coverage of Medium, Long Waves, Trawler Band
- ★ Use as domestic radio, car radio or fit with strap for carry-about.
- ★ No aerial required except for use as car radio.
- ★ 3-inch speaker but will drive a larger speaker.
- ★ 400 milliwatts output stage.



SIZE: 7½ x 5½ x 1½in.
May be built for **£5.19.6** plus 3/6 post, etc.

PARTS PRICE LIST AND EASY BUILD PLANS 2/-

NEW TRANSONA-6

★ (6 Transistors, plus 2 Diodes)
M/L & T. BAND

400 Mw Mullard push-pull output Transistors. Powerful magnet 3in. high grade speaker. Push-pull transformers. This is a top performing receiver. Many stations listed in one evening including Luxembourg loud and clear. A pleasure to listen to. FERRITE ROD AERIAL. All parts sold separately, including pale blue gleaming polystyrene case with duo-diffusion grilles in red. Uses 9 volt battery. Sockets for car aerial.



Total building cost: **£4.19.6** P.P. 3/-. Size 6½ x 4½ x 1½in.

"Agreeably surprised with Trawler Band reception. Luxembourg as loud as local. Your easy build diagram helped a lot... my first attempt."—H. S., Penzance, Cornwall (poor reception area).

PARTS PRICE LIST AND EASY BUILD PLANS 1/6

AFTER SALES SERVICE

Radio Exchange Co.

27 HARPUR STREET, BEDFORD


Phone: 2367

Closed 1 p.m. Sat. Opp. Co-op.

BEGINNERS POCKET 5

(MW/LW and TRAWLER BAND) (7 Stages)
(5 Transistors, plus 2 Diodes)

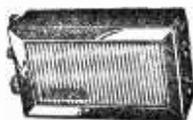Designed round supersensitive FERRITE ROD AERIAL and 3in. moving coil speaker. Attractive case in black with speaker grille in red. On test Home, Light, Radio Luxembourg and many Continental stations were received.



Total cost of all parts **£2.19.6** P.P. 3/-

EASY BUILD PLANS AND PARTS PRICE LIST 1/6

"THE MELODY SIX"

- ★ Ferrite rod aerial.
- ★ 6 new type transistors and top quality components. Attractive case in blue and red and carrying strap with gold trim.
- ★ 3in. Speaker.
- ★ M.W./L.W.
- ★ No aerial required.



£3.19.6


P.P. 3/-

Price list and plans, 2/-.

"BEGINNERS" PUSH-PULL FIVE

(5 Transistors, plus Diode)

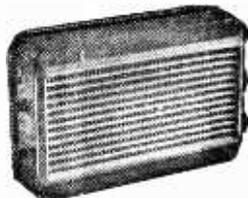- ★ 2½" Super-tone Loudspeaker.
- ★ Ferrite rod aerial.
- ★ Tuning condenser.
- ★ Volume control.
- ★ Case with speaker grille in red.
- ★ Fully tunable over med/long waves and T-band.
- ★ Simple assembly diagrams.
- ★ 250 Milliwatts output stage.
- ★ Min. earpiece free.



Can be built for **59/6** P.P. 3/-, or with 3in. speaker 68/-

★ PARTS PRICE LIST, etc. 2/-.

"Home, Light, AFN, Lux., all at good volume"—G.P., Durham.

HOME RADIO OF MITCHAM

for


EDDYSTONE

SHORT WAVE RECEIVERS and COMPONENTS

MODEL 870A

A very compact high performance All Wave Receiver that is equally at home ashore or afloat.

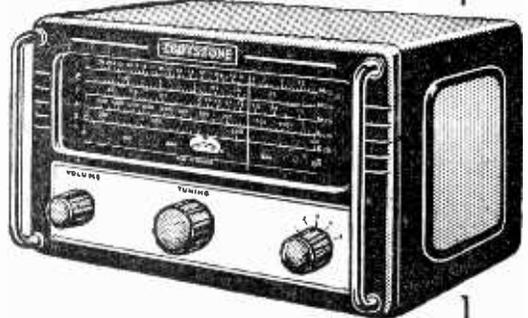- Five wavebands covering 12.5 to 2,000 metres.
- Wide, clear gear-driven horizontal scales.
- Vernier logging device.
- Built-in speaker giving good quality and volume.
- Five valve superhet circuit with high efficiency tuning coils.
- Attractive two-tone metal cabinet with die cast front panel.
- Operates equally well from AC or DC mains, 110 or 200/250 volts.



Price **£34.15.6**

carriage paid U.K.

DIMENSIONS: 11" wide, 8½" deep, 6½" high. Weight: 11½ lbs.

Overseas Customers.
Special Export Price, £26.0.0
plus 30/- carriage.

We also stock the 840C and 940 COMMUNICATIONS RECEIVERS. Details on request.

Our NEW 166 page Comprehensive Components Catalogue is available. Price 2/6, post 9d

(Dept. P) 187 LONDON ROAD, MITCHAM, SURREY

Shop hours: 9 to 6. (Weds. 1 p.m.)

Phone: MIT 3282.

TAPE RECORDER AMPLIFIER

£7.19.6



Well designed 5 valve amplifier. Output 3.5 w. Input for Microphone, Radio and Gram. Size 8½ x 3 x 4½ in. Ins., Carr., 4/6.

T.V. TUBES REGUNNED
2lin. 99/6, 17in. 90/-, 15, 14, 12in. 70/-.

Terms available.
1 Year's Guarantee.
Add 10/- refundable on receipt of your OLD Tube. Ins., Carr., 7/6.

DUKE & CO (London) Ltd
621/3 ROMFORD RD.
MANOR PARK, E.12
Ilford 6001/3
Stamp for FREE list.

TAPE CABINET FOR COLLARO STUDIO DECK



69/6

Beautifully designed covered cabinet in 2-tone colours.
Size 16 x 15½ x 8½ in.
Carr. 5/-.

SPEAKERS 8/9
6 and 8in. round and 7 x 4in.
Ex manufacturer's salvage.
Post 1/3.



COMPLETE TELEVISIONS

14 INCH 17 INCH
£7.10.0 £11.10.0

- ★ 12 months free replacements on Tubes, Valves and Components.
- ★ Ex Rental and repossessed televisions.
- ★ Two channels more, 7/6 extra.
- ★ Demonstrations daily
- ★ Legs—39/6 per set.
- ★ Part exchange allowance on Radios, TV's, etc.
- ★ Personal collection advised, or Insured Carr., 14", 20/-; 17", 30/-.

EXPRESS ELECTRONICS

ROSEDENE LABORATORIES

KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/6	6B4A	6/-	12A07	6/9	DH77	6/-	RF91	4/-	PL82	7/-
1C3	8/-	6B66	7/-	12AX7	6/9	DH142	8/6	EF92	5/6	PL83	7/6
1F1	8/-	6BH6	5/9	12BE6	8/8	DH150	10/-	EL41	9/6	PY81	6/9
1F3	7/6	6BJ6	5/9	12BH7	10/8	DK91	7/6	EL84	7/-	PY82	7/8
1FD1	8/-	6B7R	8/9	12K8GT11/2	7/8	DK96	8/6	EM84	10/-	PY83	7/6
1FD9	7/6	6BW6	7/8	12Q7GT	7/8	DL92	7/6	EM85	10/-	85A1	9/6
1L4	6/9	6BW7	7/-	12S87	7/6	DL94	6/6	EY31	7/6	U37	11/8
1P1	8/-	6D2	4/-	16A5	9/-	DL96	8/-	EY81	10/-	U32	7/6
1P10	7/6	6F12	4/-	25A6G	8/8	EB91	4/-	EZ40	7/6	U78	7/8
1P11	7/6	6H0GT	2/-	25L6GT	7/6	EBC31	10/-	EZ90	6/-	U78	5/-
1R5	8/-	6J7GT	7/6	25Z44	9/-	EBP80	8/6	EZ81	6/9	U143	7/6
1R5	8/-	6K7G	5/6	30C1	7/6	ECC81	6/-	HVR2	6/9	UBC41	8/6
1T4	7/6	6K8G	6/9	30L1	7/6	ECC82	6/9	KT33C	6/9	UBC42	8/6
1U5	5/6	6Q7G	5/6	35L6GT	9/-	ECC83	6/9	KT88	11/6	UF41	8/6
3Q4	8/-	6S17GT	8/-	35W4	8/6	ECC84	7/6	N17	7/6	UL41	8/6
3S4	7/6	6S7GT	6/-	3Z4GT	8/-	ECF80	8/6	N18	8/-	UV41	7/6
3V4	6/6	6V0G	7/6	5763	7/6	ECP82	8/-	N19	7/6	W17	7/6
5U4G	7/6	6X4	5/-	80	6/-	ECH42	9/-	N709	7/-	W76	4/6
5Y3GT	5/-	6X5G	5/-	DAP91	8/-	ECH81	10/-	PCC84	7/6	W142	8/6
5Z4G	9/6	787	9/6	DAP96	8/-	ECL80	8/6	PCF80	7/6	X17	7/6
6AC6	9/6	6B3	4/-	DCX90	12/6	ECL82	9/-	PCF82	7/6	X142	8/-
6AL5	4/-	12AD6	11/6	DF91	7/6	EF41	7/6	PCL82	8/-	X150	9/-
6AM6	4/-	12A8H	10/-	DF96	8/-	EF80	8/-	PCL84	9/-	Z77	4/6
6AT6	6/-	12AT7	6/-	DH76	7/6	EF86	9/-	1L81	12/6	ZD17	7/6

High Stability Resistors 1W 5% 50 Ω to 1M. 9d. Midget Ceramics 500 v. 9d. Coax. Super quality 1in., 6d. yd. Plugs 9d. Sockets 9d. Silicon H.T. Rects. 250v. 300 MA 1in. x 1in. 8/6. Contact Cooled 250v. 50 MA 6/6. 85 MA 8/6.

NEW TRANSISTORS BY MULLARD. OC19, OC28, OC86, 25/-; OC44, OC45, 9/-; OC70, OC71, 8/-; OC73, 7/6; OC72 matched in pair. 18/-; OC74, OC75, OC78, OC81, 7/6; OC82, OC170, 9/6.

VALVES MATCHED IN PAIRS

EL84 17/-, N709 17/-, 8V6G 17/-, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15 Ω 1/4W, P. & P. 1/6. 12in. P.M. Speakers 3 Ω 24/6. Baker's "Selhurst" 12in. 15 Ω 15W, 90/-, 12in. stereo Model, 27.7.0.

SETS OF VALVES

DK91, DF91, DAP91, DL92 or DL84. 1/6/6
ECH42, EF41, EBC41.
DK96, DF96, DAP96, DL98. 2/7/6
EL41, EZ40. 3/7/6
1C3, 1F1, 1FD1, 1P1. 2/7/6
UCH42, UF41, UBC41, 1R5, 1T4, 1R5, 3S4, or 3V4. 2/7/6
UL41, UF41. 35/-
Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

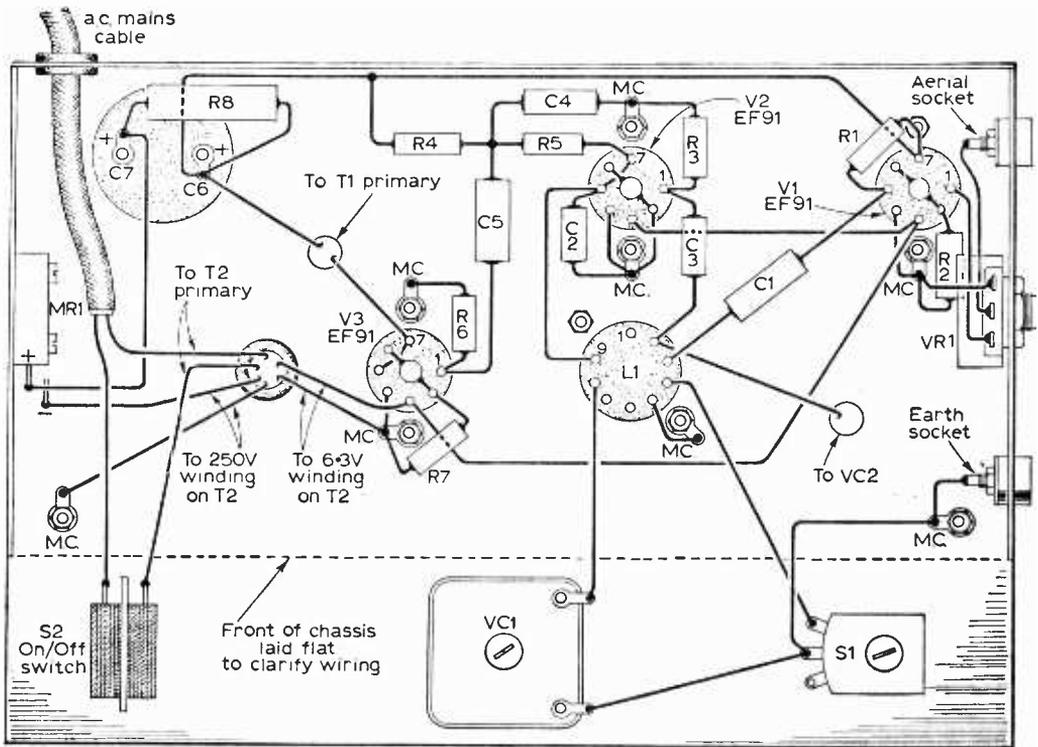


Fig. 3—The complete wiring diagram.

COMPONENTS LIST

Resistors (all ½ W, carbon unless otherwise stated):

- | | |
|---------|----------|
| R1 4.7k | R5 27k |
| R2 390Ω | R6 0.47M |
| R3 1.2M | R7 150Ω |
| R4 270k | R8 1k 1W |

Valves:

- V1
- V2 EF91, B7G base
- V3

Coil:

Iron dust core, dual range, medium and long wave bands, with reaction winding. (Repanco)

Capacitors:

- C1 470pF ceramic or mica
- C2 270pF ceramic or mica
- C3 47pF ceramic or mica
- C4 270pF ceramic or mica
- C5 0.01μF paper 350V
- C6 32μF electrolytic, 350V
- C7 16μF electrolytic, 350V
- VC1 300pF solid dielectric variable
- VC2 500pF air dielectric variable

Transformers:

- T1 Output—about 50 : 1
- T2 Mains—Tapped primary. Secondaries:
H.T.: 250V 20mA half wave.
L.T. 6.3V 1A

Rectifier:

Contact-cooled 250V 20mA

(Continued from page 738)

the full H.T. voltage from the rectifier when first switching on and must therefore be 350V working. Any kind of tuning capacitor, air-spaced or otherwise can be used for VC2 or one-half of a two-gang component can be used as in the prototype. The coil L1, may be any iron-dust-cored dual wave type with a reaction winding but it is convenient if it is designed to plug into a B9A or B7G valve base. For tuning, a 3in. diameter engraved knob is fitted direct to the tuning capacitor but there is no reason why a slow motion drive should not be fitted if desired.

Testing and Operation

When the wiring has been completed, a test should be made with a meter between C6 and chassis to see that there are no short-circuits in the H.T. wiring. If all is well, power can be applied and transmissions should then be received. Two or three feet of wire as a throw-out aerial will usually be enough, though in poor reception conditions, some more efficient arrangement may be necessary. An earth is not essential, but will reduce mains-borne interference.

It will probably be found that with VR1 at maximum, some programmes will be receivable at adequate volume with VC1 set at minimum, but will suffer from interference from adjacent stations. In this case, the procedure is to reduce the volume by means of VR1 and bring it back to the desired level by the application of reaction, at the same time adjusting VC2 for the best results. ■

MIDGET MAINS PORTABLE

By V E HOLLEY

THIS handy little receiver was first built with one R.F. stage followed by a diode detector and in this form it gave good service in the north west London area. When later it was required for use in a less favourable location, a second R.F. stage was added to increase the sensitivity.

R.F. Amplifier

The signal is supplied by a ferrite rod aerial (L1, L2 in Fig. 1) and two R.F. pentodes, EF91, are used to amplify it to a suitable detection level.

The full gain of the two stages is not required and indeed, could not be used with stability, so the gain is reduced by resistance loading in both anode circuits and by omitting by-pass capacitors from the cathodes. If greater gain is required, one or both of these capacitors may be inserted in the manner of C4, which is shown dotted in Fig. 1. Decoupling is provided in both anode circuits.

The inductance of the rod aerial is adjustable within fairly wide limits and the second tuned circuit, which is ganged to it, may therefore incorporate any dual range iron dust cored coil designed to cover the long and medium-wave bands with a 500pF tuning capacitor.

It will be noted that there is no provision against overloading but as both valves operate with negative current feedback no trouble is likely to be encountered under normal conditions.

Selectivity

The selectivity provided by the two tuned circuits is quite good and with the assistance of the directional properties of the aerial, the BBC programmes and some of the continentals can be received clear of interference in daylight and dark-

ness, in any reasonable reception area. Some further improvement might be obtained by applying reaction to L3 and L4; this was not tried.

Demodulation

The signal at the anode of V2 is rectified by a germanium diode D1 (GEX34). After passing through the R.F. filter C10, R8, C11, audio frequencies appear across the volume control, VR1 together with a D.C. voltage negative to chassis, which is used for alignment purposes, as will be described.

A.F. and Output Stages

A triode-pentode valve, ECL82, is used here in a conventional arrangement. Grid leak bias for the triode section avoids the need for a bias resistor and capacitor, but the pentode bias resistor must be bypassed in the normal manner in order to avoid negative current feedback which is, of course, undesirable in an output stage. The optimum load of the valve is 5,600Ω and to match this to a 3Ω loudspeaker, the output transformer must have a ratio of about 45:1.

If the D.C. resistance of the primary is more than about 200Ω, it is advisable to insert a resistor (R12) in the screen supply so that the voltage at the screen will not exceed that at the anode. The network R14, C15 serves to correct the response at the higher audio frequencies where valve and loudspeaker impedances rise considerably.

Power Supply

The receiver requires an H.T. supply of about 60mA at 210V and a heater supply of something (Continued on page 745)

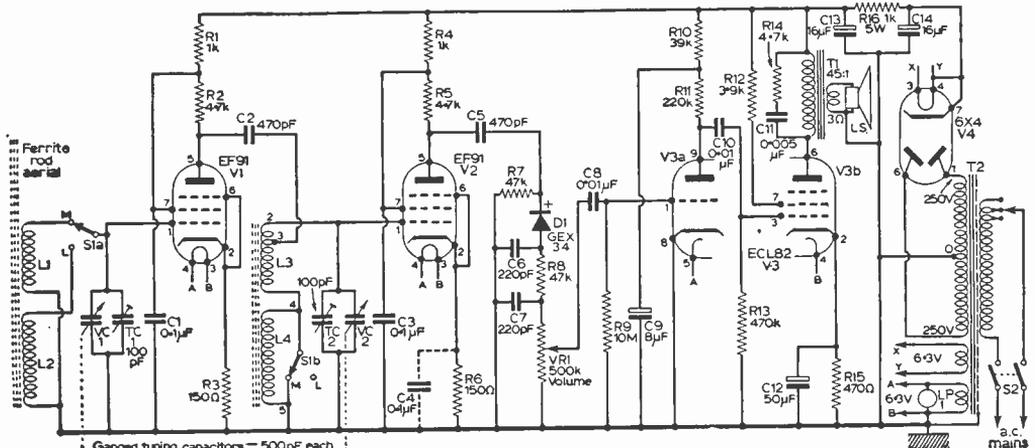


Fig. 1—The circuit.

RADIO CLEARANCE LIMITED

27 TOTTENHAM COURT ROAD, LONDON, W.1.

THE OLDEST COMPONENT SPECIALISTS IN THE TRADE

TRADE ENQUIRIES INVITED

Telephone: MUSEUM 9188

EST. 30 YRS.

**YOU CAN
HOLD EUROPE
IN THE PALM
OF YOUR HAND
WITH THE**



"CAPRI"

A miniature pocket transistor Radio that **REALLY** works, retaining the most attractive features of the famous "Contessa." Six first-grade Mullard transistors plus diode are employed in a highly sensitive superhet MW and pre-set LW circuit embodying the most modern design practices. A special 2½ in. high gauss loudspeaker provides surprising volume and a personal earpiece socket is also available. An attractive two-tone plastic case is supplied in two colours—ivory/red or ivory/blue, the full constructional details being furnished with each set of parts. The total measurements of the "Capri" are 4½ x 2½ x 1½ in.

SEE AND HEAR A WORKING MODEL TODAY


Inclusive price for all associated components, case and constructional data, complete in every detail. **HUGE NEW PURCHASES HAVE ENABLED US TO REDUCE THE PRICE**
TO ONLY £5.19.6
 (Plus 2/- P. & Pkg.)
 (9 volt battery 2/6 extra.) Or our **BUY AS YOU BUILD** Scheme.
 Any parts sold separately.

THE NEW "CONTESSA"

Mk III

The Best is Now Even Better!
 A brilliant conception of the finest 2-band 6-transistor radio available.

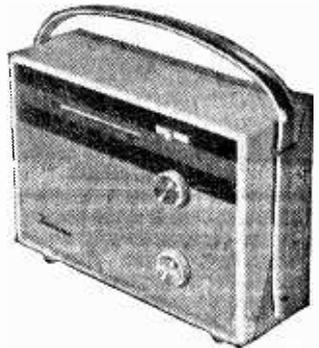★ *Ultra-modern styling with a magnificent two-tone cabinet fitted with fully expanded metal front and a slide-rule type waveband dial. GREATER OUTPUT using the latest high-efficiency Mullard Transistors and Diodes, incorporating an improved design, featuring different circuit constants.*



**MORE punch—MORE gain—MORE stations—SUPERB appearance—the NEW "Contessa" scores again!!
 SEE it—HEAR it—you will BUY it!**

- Waveband coverage of 530 kc/s to 1,620 kc/s and 160 kc/s to 270 kc/s.
- Assured reception of at least half a dozen stations in daylight!
- Large clearly-calibrated station-named dial.
- Internal high-gain Ferrite aerial.
- 5:1 ratio slow motion tuning.
- Fitted with the latest 12,000-line high-flux loudspeaker.
- Power of 600 milliwatts from the single-ended push-pull final stage.
- Specially designed aerial matching coil for use in a CAR.
- Only first-grade Mullard fully-guaranteed matched transistors and diodes are used.
- Tape recorder socket provided.
- Double-tuned IF transformers for maximum gain and knife-edged selectivity.
- Fully drilled printed circuit panel marked with component numbers.
- The two-tone case outer measurements are 10½ x 7½ x 3½ in. and weighs approx. 4 lbs. when assembled.
- Battery lasts 4 months with normal usage.
- Book supplied with detailed assembly instructions, diagrams and circuitry.
- Anyone can build this set—everything supplied, just a soldering iron required.
- Cabinets available in two tone beige and two tone blue.
- Adjustable carrying handle.

Inclusive price for all associated components, cabinet and battery, complete in every detail: Or our **BUY AS YOU BUILD** SCHEME, any parts sold separately.
 Send for comprehensive descriptive Manual and Parts List. 2/10 post free.
£10.19.6
 (Plus 3/6 P. & Pkg.)

STILL AVAILABLE to callers only

SUPERB MAGNAVOX PRINTED CIRCUIT 4-WATT TAPE RECORDER AMPLIFIER

Record, playback and erase facilities. Bass and Treble Tone Controls—40 cys to 12,000 cys. With valves, plugs, leads and full circuit details.

DIRECT FROM THE MANUFACTURERS @ £3.10.0

OR LESS VALVES @ £2.0.0

ALL the Components for the matching POWER SUPPLY including Transformer, Rectifier,

Sub-chassis, smoothing, plugs and sockets. £1.3.6

SPECIAL OFFER! Above amplifier less valves, with suitable power transformer, £2.19.6


Regret Transcriptors SOLD OUT.

STAMPED and ADDRESSED ENVELOPE with any enquiry please. But regret no lists or catalogues—our stocks move too quickly!

PLEASE ALLOW FULL POSTAGE AND PACKING CHARGES

Terms of Business: CASH WITH ORDER OR C.O.D. ON ORDERS OVER 10/-.

Build The Sinclair MICRO-AMPLIFIER

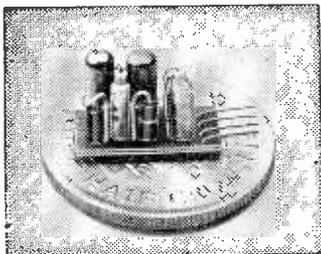

ACTUAL SIZE

This amplifier is made possible by the remarkable micro-alloy transistors it uses. These are available separately at the following prices:—

MAT 100	7/9
MAT 101	8/6
MAT 120	7/9
MAT 121	8/6

This microscopic amplifier, the **smallest of its type in the world**, out-performs amplifiers 20 times as large. The main features of the design are listed below:—

- 1) Power Gain - 60 dB (1,000,000 times).
- 2) Power Consumption - from 0.4 mA at 1.3 V to 1 mA at 9 V. Any battery may be used.
- 3) Output Power - sufficient to drive ANY type of ear-piece or even a **loudspeaker**.
- 4) Frequency Response - 30 c/s to 20 kc/s \pm 1 dB. True **High Fidelity** performance.
- 5) Clear and detailed instructions enable the micro-amplifier to be built in under two hours with ordinary tools.
- 6) Uses brand new microminiature components and micro printed circuit.
- 7) Free applications data supplied with every kit showing how to use the amplifier with high and low impedance pickups and micro-phones and hi-fi stereo headphones. Circuitry is given for using the amp. in **micro-radios** and **transmitters**, and with a micro telephone pick up coil (also available).
- 8) Satisfaction guaranteed. **Overall size:** $\frac{3}{4}$ " \times $\frac{3}{8}$ " \times $\frac{1}{2}$ "

28/6 plus 1/6 Postage and packing from:

SINCLAIR RADIONICS LTD. 69, Histon Rd. Cambridge

TELEPHONE CAMBRIDGE 53965

TRADE ENQUIRES INVITED

SOLDERING EQUIPMENT

by



PRECISION SOLDERING for the ELECTRONICS INDUSTRY

Comprehensive range - Robust & reliable
- Light weight - Rapid heating - Bit sizes 3/32in. to 3/8in. - 'Permabit' or Copper bits - All voltage ranges 6/7v. to 230/250v. - Prices from 21/-.

Also

- Plastic Cable Strippers
- Miniature Solder Pots
- Heat Guards
- Long Life Bits

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.

ADAMIN— new range of precision micro-soldering instruments—
Have you had details?

Brochure No. S10 sent free on request.

Sole proprietors and manufacturers:
LIGHT SOLDERING DEVELOPMENTS LTD.
28 Sydenham Road, Croydon, Surrey

Phone: CROydon 8589 Grams: Litesold Croydon



The new NOMBREX

TRANSISTORISED WIDE-RANGE
SIGNAL GENERATOR 27
220 kc/s to 220 Mc/s



CHECK THESE FEATURES

COMPACT
Only 6 1/4" x 4 1/2"

PORTABLE
Weight 2 lbs.

ACCURACY
Under 2%

ECONOMY
9v. Battery

DIRECT
Calibration

S.A.E. for full technical leaflet.

RETAIL **£7.10.0** Post and Ins. 3/6
Battery 2/3

Screened Lead and Probe 6/3 extra
CASH WITH ORDER. REGRET NO C.O.D.

IMMEDIATE DELIVERY

Trade and Export Enquiries Invited

H.P. Terms:

Send £2 deposit
pay balance
21/- per month

NOMBREX LTD. (Instruments Division 41)

Estuary House, Camperdown Terrace, Exmouth, Devon,
England. Tel. 3515.

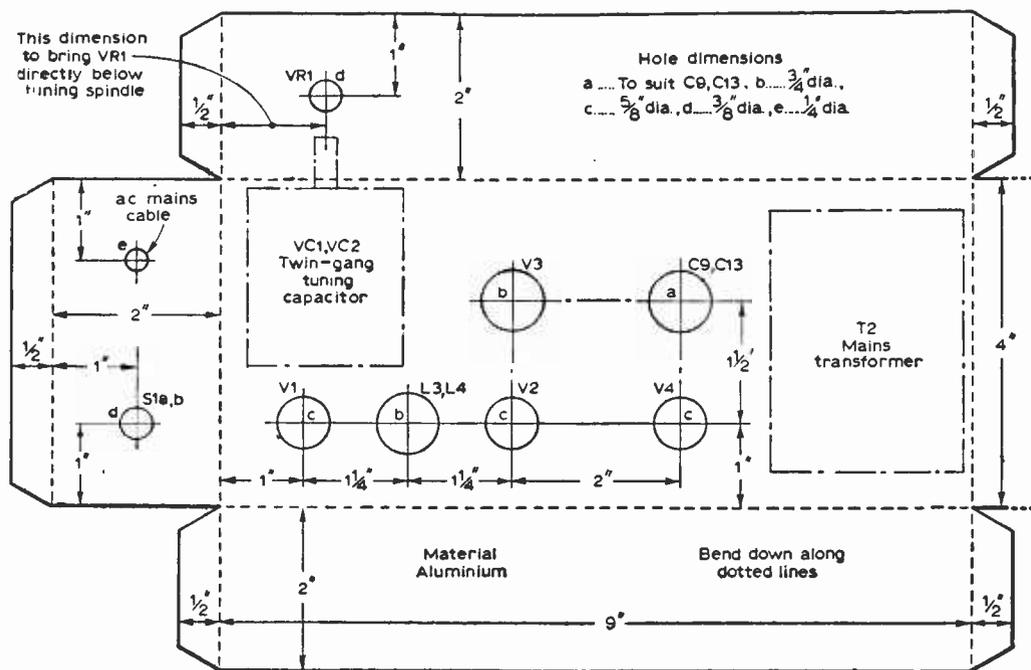


Fig. 2—The chassis drilling details.

(Continued from page 742)

under 2A at 6.3V. The use of a double wound mains transformer to supply this makes the chassis safe to handle at all times and considerably reduces mains-borne interference.

It is convenient to have a separate 6.3V winding to supply the heater of V4 so that there is not a large potential difference between its heater and cathode, but if only one winding is available, it is quite in order to include V4 heater with the others. If this is done, the winding should be rated at not less than 2.5A and it is most important to omit the connection between pins 4 and 7 of the rectifier. (See Fig. 1.)


Smoothing is provided by R16 in conjunction with the electrolytic capacitors C17 and C18, while R10 and C13 provide a little extra for the anode of V3a. The value of R16 may need adjustment in some cases to produce the correct H.T. line voltage. The mains switch is incorporated with VR1.

Construction

The receiver is constructed on a chassis of 18s.w.g. aluminium sheet, 9in. x 4in. x 2in., details of which are given in Fig. 2. The layout is not critical. The grid circuit of V1 which includes the aerial, is the point where in-

stability is most easily introduced and care must be taken that it is not capacitively coupled to any of the later wiring. V1 and V2 must be screened.

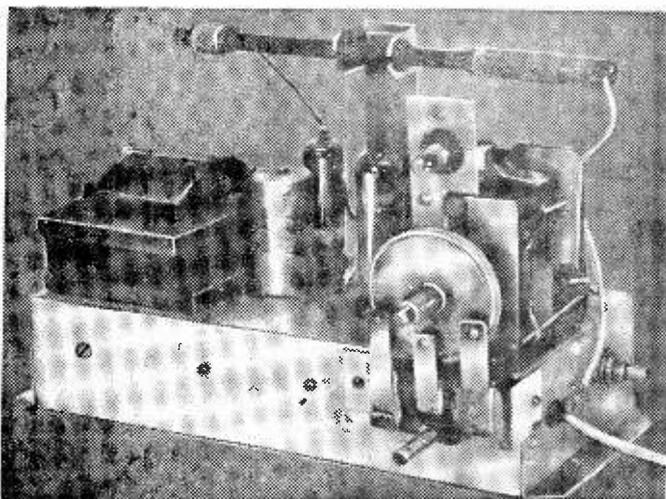The trimmers TC1 and TC2 are mounted on top of the tuning capacitor, and if in this position they can "see" each other, a small screen should be erected between them. The pilot light is also



The complete receiver, less its cabinet

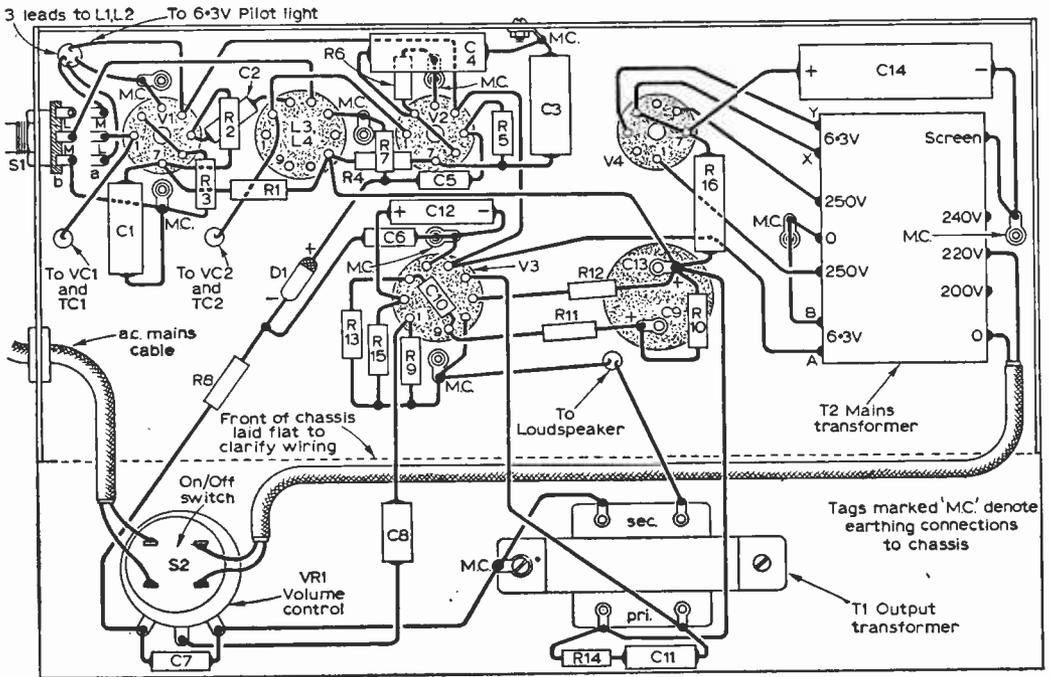


Fig. 3.—The underchassis wiring diagram.

mounted on top of the gang and to achieve a symmetrical appearance in the finished receiver, should be positioned so that its height above the

tuning spindle is equal to the distance between that spindle and the spindle of VR1 below.

(To be continued)

LIST OF COMPONENTS

Resistors

(20%, 1/4W carbon unless otherwise stated):

R1	1k Ω	R9	10M Ω
R2	4.7k Ω	R10	39k Ω
R3	150 Ω	R11	220k Ω
R4	1k Ω	R12	3.9k Ω
R5	4.7k Ω	R13	470k Ω
R6	150 Ω	R14	4.7k Ω
R7	47k Ω	R15	470 Ω , 1W
R8	47k Ω	R16	1k Ω , 1W
VR1	500k Ω carbon potentiometer with switch (S2)		

Capacitors:

C1	0.1 μ F paper 350V
C2	470pF ceramic or mica
C3	0.1 μ F ceramic or mica
C4	0.1 μ F ceramic or mica
C5	470pF ceramic or mica
C6	220pF ceramic or mica
C7	220pF ceramic or mica
C8	0.01 μ F paper 350V
C9	8 μ F electrolytic 350V
C10	0.01 μ F paper 350V
C11	5,000pF paper 350V
C12	50 μ F electrolytic 25V
C13	16 μ F electrolytic 350V
C14	16 μ F electrolytic 350V

VC1	500pF	} twin-gang air variable tuner
VC2	500pF	
TC1	100pF trimmer	
TC2	100pF trimmer	

Valves:

V1	EF91	V3	ECL82
V2	EF91	V4	6X4

Diode:

GEX34 or similar

Pilot lamp:

LPI 6.3V 0.3A

Transformers:

T1	Output	45 : 1
T2	Mains	Tapped Primary. Secondaries: 250.0-250V 60-70mA; 6.3V 2A; 6.3V 1A

Loudspeaker:

LS 3 Ω ; 7 x 4in. elliptical

Switches:

S1	2-pole, 3-way
S2	D.P.S.T. (see VR1)

Coils:

L1, L2	Ferrite rod aerial, type FRA.2
L3, L4	Miniature dual range, iron dust cored

Miscellaneous:


Three B7G valveholders, one B9A valveholder. Screening cans for V1 and V2. Material for chassis.

SENSATIONAL NEW 1962 DESIGNS — BY CONCORD

LOW PRICES ★ PICTORIAL STEP-BY-STEP PLANS ★ EASY AS A.B.C.

THE NEW "VOLKSRADIO" ONLY 19/6

TAKE-OVER BID MAKES THIS FANTASTIC OFFER POSSIBLE—the beautifully compact "6-STAR VOLKSRADIO" measuring 4½ x 2½ x 1½ in. receives perfectly—in the Bedroom, Office, Garden—over all medium waves (Incl. Luxembourg). Under 1d. hour running cost. ANYONE can assemble it in one or two hours using our simple A.B.C. plan. Complete set of parts ONLY 19/6, plus 2/6 P. & P. (C.O.D. extra. (Parts can be bought separately.) Money Back Guarantee.

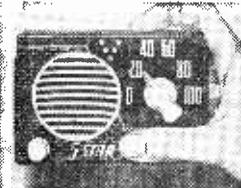

NO EARTH OR AERIAL REQUIRED




Revolutionary INTERNAL FERRITE AERIAL Makes this sensational pocket-size radio the best money-saving bargain of all time. Powerful, superb tone and clarity, ensures perfect reception for all your favourite programmes

Completely portable, only 5½ x 3 x 1½ in. Two-tone case. Anyone can assemble with our simple PRINTED CIRCUIT PLAN. Send 37/6, plus 2/6 P. & P. (C.O.D. 2/- extra.) Satisfaction guaranteed. (All parts available separately).

FREE HIGH SENSITIVITY HIDE-AWAY EAR-PIECE GIVEN WITH EACH SET.

"OUR NEW 4-STAGE MINUETTE"

Build this newly-designed "MINUETTE" 4-STAGE transistor set in very strong ready drilled ULTRA-MODERN CASE, size only 6 x 3½ x 1½ in. Uses three transistors and diode and SELF-CONTAINED LOUDSPEAKER. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening on 1/2 battery. Can be built FOR ONLY 39/6, including PROPER CASE, miniature speaker, etc. SIMPLE AS A.B.C. PICTORIAL STEP-BY-STEP PLANS etc., plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

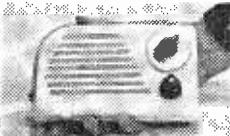


THE MINUTE TRANSISTOR RADIO

MIAMI ONLY 32/6

Unbelievably small—Outrageously cheap You will be amazed at the fine quality of tone and volume of this great little radio. Only a fantastic 3½ x 2½ x 1½ in. the MIAMI will bring you great entertainment for months on a 1/2 battery. Simple assembly plan with each set. ONLY 32/6. YES 32/6!

Plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. Demonstrations given daily. Parts available separately if required.

THE NEW "COSTA BRAVA" 49/6

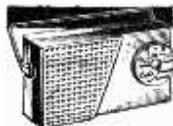

NO EARTH or AERIAL REQUIRED ALL TRANSISTOR RADIO

Revolutionary INTERNAL FERRITE AERIAL and moving coil speaker makes this sensational pocket-size radio the best money-saving bargain of all time. Powerful, superb tone and clarity, ensures perfect reception for all your favourite programmes. Completely portable, only 5½ x 3 x 1½ in. Two-tone case. Anyone can assemble with our simple PRINTED CIRCUIT PLAN. Send 49/6, plus 2/6 P. & P. (C.O.D. 2/- extra). Satisfaction Guaranteed. (All parts available separately). FREE HIGH SENSITIVITY HIDE-AWAY EAR-PIECE GIVEN WITH EACH SET.

THE NEW "LISBON" TRANSISTOR SET

19/6

This is a pocket 2-stage transistor set not much larger than a matchbox. Excellent clear reception covering all medium waves, works for months off a tiny 1½ or 3 volt battery costing only 8d. Easy to build and an excellent introduction to transistor circuitry. Everything can be supplied down to the last nut and bolt incl. SIMPLE PICTORIAL STEP-BY-STEP PLANS FOR ONLY 19/6, plus post and packing 1/6. (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.



THE RINGO BURGALAR ALARM CLEARANCE SALE!




BIG PROFITS FOR YOU IF YOU BUY NOW! Made to retail at 7 gns. you can now buy this famous Twin-gong Alarm for only 37/6—but only if you act now... stocks are strictly limited. Easily installed and operated. Switches on or off at any time. Fantastic FINAL reduction to clear (minimum order of 3) Carr. Free. 37/6 Free literature sent with each alarm.

SELL SAFELY TO THE MOTORIST



Bulk purchase of bankrupt stock ensures this fabulous money-making offer. AUTOMATIC CIGARETTE LIGHTER Instantly provides ready lit cigarette, without the driver taking his eyes from the road. Heavily chromium plated case holds 10. Easily and simply fitted to any car's dashboard. Works off 6 or 12 volts. Retail Price 44/6. Special Clearance offer only 12/6 each. sold in minimum lots of 6. Carriage free.

THE NEW "SAN REMO" 6 STAR 29/6

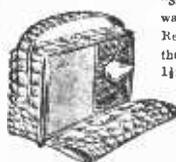

This All Transistor Speaker Radio—The "San Remo" 6 Star covers all medium waves including "Home," "Light," etc. Reliable and lightweight—Slips easily into the Pocket or Handbag—size only 4½ x 2½ x 1½ in. Works for Months on 1/2 Battery! Ideal for holidays, Camping, Bedroom, etc. Anyone can assemble it in an hour or two with our simple-as-ABC PLAN! Complete set of parts including miniature speaker—everything—only 29/6, plus 2/6 P. & P. (C.O.D. 2/- extra.) Parts can be bought separately.

Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and values stocked. Regret no C.O.D. abroad. DEMONSTRATIONS DAILY AT WORKS.

CONCORD ELECTRONICS


(DEPT. 479) 210 CHURCH ROAD, HOVE, SUSSEX

"THOUGH THE WORKING WEEK IS SHORTER WITH WAGES AND MATERIALS EVER MORE COSTLY"

MAXI-Q
REGD.

Thanks to you, our Customers who purchase in ever-increasing numbers, we are still able to offer the finest ever coils without increased prices.

Coverage from 3.8 to 2,000 metres in 7 ranges—Each coil is packed in an aluminium container which may be used as a screening can for the coil itself—Brass threaded, adjustable iron cores—Colour coded moulded polystyrene formers—Chassis/Plug-in Technical Bulletin, DTB.1 1/6—Dual Purpose Technical Bulletin, DTB.4 1/6—Colour Code Identified Coils: BLUE Signal Grid Coil with Aerial Coupling winding—YELLOW Signal Grid Coil with intervalve coupling winding—GREEN Grid Coil with reaction and coupling windings—RED Superhet Oscillator for I.F. of 465 Kc/s—WHITE Superhet Oscillator for 1.6 Mc/s. Prices range from 4/1 to 4/9 each. Five-Colour Glass Scale, Back Plate, Pointer, Pulleys and Cord for use with 315 pF tuning condensers. Coverage (1) 150-400 Kc/s.; (2) 530-1,600 Kc/s.; (3) 1.5-4 Mc/s.; (4) 4-12 Mc/s.; (5) 10-30 Mc/s.; Price 19/-.

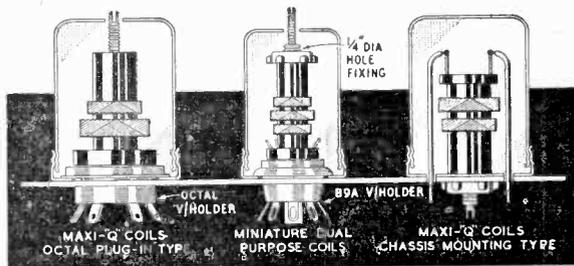

GENERAL CATALOGUE covering full range of components send 1/6d. in stamps or P.O.
PLEASE SEND S.A.E. WITH ALL ENQUIRIES

DENCO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex
"Stop Press: S.B. DECODER TRANSFORMERS — 26/- each"

THE PEMBRIDGE COLLEGE OF ELECTRONICS OFFERS TRAINING IN RADIO TELEVISION AND ELECTRONICS

ATTENDING COURSE

- (A) Full-time One Year Course in Radio and Television. College course in basic principles for prospective servicing engineers. Next course commences 1st January, 1963.

This course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the new Servicing Certificate examinations.

HOME-STUDY COURSES

- (B) Radio and Television Servicing.
1 Introductory course.
2 Basic course covering R.T.E.B. Intermediate Radio and Television Servicing Certificate examination.
- (C) Courses in Radio, Telecommunications and Mathematics up to City and Guilds Telecommunication Technicians' Final Certificate.

To: The Pembridge College of Electronics.
(Dept. P11), 34a Hereford Road, London, W.2.
Please send, without obligation, details of
A ___ B ___ C ___ (Please tick.)

Name _____

Address _____

THE BERKELEY

(Continued from page 695)

method is applicable when using "Croid" joinery glue which does enable a slight adjustment to be made before setting. Impact adhesives are extremely powerful, but a great deal of accuracy is then needed when placing the sections together.

Loudspeaker Apertures

Cut out the two loudspeaker apertures in the front panel and drill the holes for the fixing screws. For the main unit, drill four 5/16in. diameter holes equally spaced on a 13in. diameter. The positions of the H.F. tweeter fixing screws are indicated on the Blueprint and a No. 10 drill (2BA clearance) should be used here. All screw holes should be countersunk on the outer surface of the panel, and enlarged on the inner surface to accommodate a box spanner; the locking nut must be flush with the panel surface, or slightly recessed, when the screw is locked in position as indicated in the inset on Fig. 1.

The removable inspection panel on one side has a ¼in. rabbet all round. The top and bottom of the opening to take this panel will need a wood fillet glued and pinned on to make up a deficiency of ¼in. The panel is held in place by a series of ¼in. x No. 8 csk. screws. Provided the edges of the cover fit the opening closely it should be necessary to insert a layer of felt only on the flat of the rabbet.

The base plinth is quite simply made from 1in. x 2in. batten, screwed and glued to the cabinet as shown (see section C/C on Blueprint), the corners being mitred and pinned. A few glue blocks on the inside can be applied.

Glue a thickening piece to the insides of the top and bottom front edges to give a ¼in. finish, which is afterwards veneering in conjunction with the top.

Clean up all the cabinet edges and fill in screw holes with plastic filler.

The top and bottom edges can now be veneered with the material selected. The edges should be carried right round the cabinet and form a slight projection to mask the edges of the "Vinyl" or "Fablon" covering on the sides. Should this method be adopted a slight adjustment is required to the inspection cover, which will be half an inch less in length.

Paint the whole of the interior and front, which will be covered by loudspeaker fabric, with flat black undercoating. Unless the front is treated in this way the loudspeaker apertures will be discernible through the fabric.

Fit the loudspeaker screws and secure with nuts as indicated in the inset on Fig. 1. The screws should be countersunk type and 1½in. long. Use ¼in. diameter screws for the main unit, and 2BA screws for the tweeter.

Make up the beading as shown in section A/A and B/B on the Blueprint. The vertical lengths are rebated to cover the edges of the side members, but the horizontal length may be left solid.

Now stain and polish, if veneered, the top, edges and beads. The plinth looks well if ebonised.

All that remains now is to cover the sides with "Fablon" or similar material, wrapping this round the front edges, and then to apply the loudspeaker fabric. This material is glued around the edges only, to a depth of 3in. When it is set apply the beads and finish off the wooden surfaces with a final coat of polish.

A suitable loudspeaker covering is the synthetic material sold under the trade name of "Tygan", and is available in many patterns and shades. To obtain a taut surface, the "Tygan" should be shrunk by applying heat for a few seconds. This is most conveniently performed by holding an electric fire in front of the cabinet, about six inches away from the material. Watch carefully for signs of contraction, then immediately remove the fire.

Allow 24 hours for the glue to harden before carrying out this heat treatment. ■

THE LUXEMBOURG TUNER

(Continued from page 717)

another set is available (a transistor portable is ideal) is to tune the second set exactly to Luxembourg and then to beat the signal generator into it until it is precisely the same.

Without altering the signal generator setting go right through the alignment procedure detailed above and the tuner will then be spot on tune to the "Station of the Stars". It is suggested that during the alignment it is advisable to put a shorting link between the junction of C2 and C3 and chassis in order to cut out the AVC, otherwise this can make exact adjustments rather difficult. Do not forget to remove this link afterwards otherwise the AVC will be ineffective.

Alignment without Signal Generator

If you are having to tune up without a generator it will probably take a little longer as there must be a little trial and error adjustment to

start with. If a really good aerial is available then this can be connected first to pin 1 of V2 and T3 adjusted until Luxembourg is heard, do not worry if it is not full strength or if other stations are butting in. Now transfer the aerial to pin 1 of V1 and adjust T2 and the station should emerge at full strength and with careful adjustment the unwanted stations can be eliminated.

Whichever method of alignment is used the final adjustment should always be made on the station itself with the tuner connected up to the actual aerial it is intended to use as this can have quite a marked effect on the tuning position of the two cores in T1.

Although the writer did not carry out experiments with other types of valve as more than enough signal was always available it is interesting to note that the EF91 valve which has considerably more gain has exactly the same base and connections and could possibly be substituted if desired although since this is not variable- μ the AVC circuit would not be effective. ■

Letters to the Editor

HI-FI FANATIC

SIR,—I recently visited a home of an acquaintance of mine who has a fine collection of classical L.P. records and an elaborate hi-fi system, consisting of a separate amplifier, pre-amplifier, record player and loudspeakers. I'm not a great fan of the classics myself, but as he was so enthusiastic in explaining his equipment, I thought it only polite to ask to hear one of his records. This I did and it was obvious that he was delighted. He then told me to choose a record from his collection.

Simple enough, I thought, but it was at this point that I made my big mistake. In my enthusiasm to get the ordeal over with, I had taken both the inner and outer covers of the record off and was turning it over in my hands to choose the side I wanted, before my friend could stop me. The first I knew of my mistake was when my friend grabbed the record from me and started to inspect it closely for any marks or scratches. After a moment or so, it began to dawn on me what I had done. In my innocence I had placed my fingers over the groove!

After many apologies from me and reprimands from my friend, he agreed to go on with the performance. Inside another 20 minutes he had finished making adjustments to the pick-up arm, the tone controls, the loudspeaker positions, cleaning the stylus etc, and then, and only then, could we hear the record.

I have heard about these record fanatics but I never before really believed that anyone could be so concerned about the welfare of something costing only 30s. to £2, and I count myself lucky to be able to listen to my cheap record player without worrying about how much dust is collecting under the stylus. — D. R. DAVENPORT (Doncaster).

ELECTRONIC GAMES

SIR,—You recently asked to hear from readers who have had experience of electronic games. I have designed such a game recently which is played to test a person's ability to recognise aircraft. The unit will be on show at the School-boy's Exhibition at Olympia on the Royal Air Force stand.

It consists of 18 transparencies of different aircraft and parts of aircraft which flash on individually for time periods varying from five to twenty seconds (this was achieved by using a modified P.W. circuit). On the control panel there are 18 buttons with 18 captions by the side of them, and a scoreboard registering the number of aircraft the player has recognised correctly.

The operator gets a visual warning to tell him how long he has before the sequence begins.

The master timing circuit operates a uniselector having 25 circuits, out of which 18 are used for the selection of the transparencies. The other

seven are used to return the score to zero, to operate a warning as to the time left before the sequence starts and also to tell the player whether he is average, good or excellent at recognising aircraft.

In this unit, I used 59 relays, 58 of which were normal GPO type 3.000 and the other was a high-speed, dual coil type. Twenty-eight of the 58 ordinary relays were needed in order that the score could operate automatically. Eighteen were used for the transparencies, and the others used for a bell and several "anti-fiddle" circuits.—CPL. EDWARDS (R.A.F. Hendon).

RECEPTION ON THE CONTINENT

SIR,—Early next year I am taking my holiday in France and I was wondering what success I could expect of receiving British programmes on my car radio. This year, when I stayed at a hotel in France, I greatly missed hearing the Home and Light programmes, as the hotel's radio was always tuned to Continental stations. I wonder if any of your readers could tell me what the quality of reception would be.—A. A. CHILTON (Cardiff).

R.1481 RECEIVER

SIR,—I have recently been given an old R.1481 receiver and would very much like to receive any details on the power supply and circuit of this set, from any reader who owns one.—C. SHINGSLEY (Burgess Hill, Sussex).

CORRECTIONS

THE TUDOR BATTERY SUPERHET. The 2-gang tuning capacitor VC1, VC2, should be Jackson type 02, not "type L" as stated in the Components List on page 437 of the September issue.

THE STRAND AMPLIFIER. There is a wiring error on the Blueprint enclosed in the October issue. The heater wire of V2 (ECC83) as shown in Figs. 1a and 2 must be amended as follows: Connect together pins 4 and 5. Connect the 6.3V supply to pin 4 (or 5) and to pin 9.

Also note that in Fig. 2 pins 2 and 7 of V1 should be shown connected to the valveholder spigot, as described in the article on page 507.

THE TROUBADOUR. Transistor types should read: Tr1 OC44; Tr2 OC45; Tr3 OC45, and not as given in Fig. 1 and in the Components List of the Blueprint (June 1962 issue).

THE P.W. SIGNAL GENERATOR. The following amendment should be made to the Components List on the Blueprint (October 1962 issue): L4 QHF8, L5 QHF9.


TOP QUALITY—LOW COST  **AMATEUR RADIO EQUIPMENT**

CR 66 COMMUNICATIONS RECEIVER ★ **A CODAR KIT TRIUMPH**

NOW ... THE FINEST KIT EVER OFFERED !


This completely new Communications Receiver with its many design features and handsome styling offers more in performance and quality than many higher priced units.

Frequency Range 540 Kc/s to 30 Mc/s in four Band-switched ranges. Separate Main Tuning and Electrical Bandspread. Entirely new design High "Q" ferrite cored Coils. Oscillator Coils fitted temperature compensated trimmers for stability. Coil Unit is wired and assembled, and with the I.F. Transformers is supplied factory aligned and tested. Low loss Trolax glass alkyl switch wafers. Controlled regenerative I.F. amp. for maximum gain and B.F.O. Panel Ant. Trimmer. Delayed A.V.C. Cathode follower output for tape recorder, etc. 3 watts output for external 2/3 ohm speaker. Four panel slider switches, On-Off/Standby-Receive/A.V.C. On-Off/Speaker On-Off. Front Panel Silver and Black, control knobs Grey with Silver trim. Provision for EM 84 Signal strength indicator. Panel phone jack. Heavy gauge steel chassis, cadmium plated. Valve line-up: ECH81/EBF89/ECC81/EL84/EZ80. Instruction Manual, 17 pages. Cabinet size 16 x 6½ x 8½ ins. Silver Grey. For AC 200-250 volts. (Export and Marine Model 115 volts).

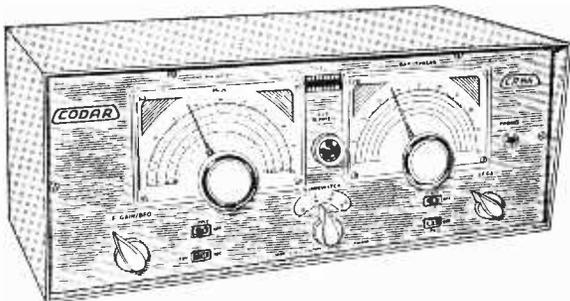

Complete Kit, **£16.10.0** carr. 6/- CR 66 Cabinet **£1.15.0** Signal strength indicator with EM 84 **17/6**
 less Cabinet and Indicator

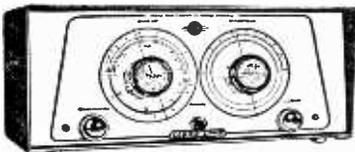THE NEW CR45 ★ **NEW STYLING TOP PERFORMANCE**



- ★ Tunes 10-2000 metres (5 Coils).
- ★ Separate electrical bandspread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb styling, World-wide reception. Total building cost, with 2 Coils, 25-75 and 60-175 metres. **£6.19.6** carr. 3/6.
 Instruction Manual 11 pages, less Cabinet

CR 45 Cabinet Silver Grey, 12 x 5½ x 7in. sliding door for easy coil changing **27/6** Extra coils, all ranges **4/9** each.

ALL PARTS AVAILABLE SEPARATELY

THE MINI-CLIPPER ★

- ★ Tunes 10-2000 metres (5 coils).
- ★ Miniature 1 valve, all band receiver.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Air spaced ball bearing condensers.
- ★ Provision to add two-transistor amplifier.
- ★ Battery lasts months.

36/6



Can be built in one evening, will receive Amateur and Broadcast stations from all parts of the world. Total building cost with one coil 25-75 metres, Instruction Manual 4 pages, 36/6, carr. 2/6. Extra Coils, all ranges, 4/9 each. Electrical bandspread available. All parts available separately.

THE SUPER CLIPPER ★

- ★ Tunes 10-2000 metres (5 coils).
- ★ Large precision dial, dual slow motion drives.
- ★ Bandspeed on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers, pre-assembled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.

88/6



Easy to assemble, this top performing All Band Receiver brings a new world of listening pleasure to your finger-tips at low cost. Total building cost with 2 Coils, 20-60 and 55-190 metres, Instruction Manual 7 pages, 88/6, carr. 2/6. Extra Coils, all ranges, 4/9 each. Front Panel, Silver Grey, 10 x 7½in., 6/9.

CODAR Equipment is famous for Top Quality, Peak Performance and Easy-to-Follow Instructions—no guesswork. All chassis are heavy gauge, pre-punched—all parts fit perfectly into place. All small parts, nuts, bolts, tags, wire, solder, etc., are included. No technical knowledge or equipment is required and Full After Sales Service is available. Hundreds of genuine testimonials from enthusiastic constructors can be inspected at our offices, or ask for copy. CODAR Receivers are supplied to Govt. Depts., Royal Air Force, Royal Navy and Educational Authorities. 6d. in stamps brings full details, illustrated leaflets.

CODAR RADIO COMPANY

24 CHAPEL ROAD, FISHERSGATE, PORTSLADE, SUSSEX
 Canadian Distributors: JAYCO ELECTRONICS, TWED, ONT.

G3IRE.

G3IPA

EXPLORE the WORLD!!

SHORT WAVE

with our exciting new "VENTURE-1" KIT
Covers both 20M and 40M bands (switched). Band spread tuning. Slow motion drive. Aluminium chassis. Three tuning condensers, valve, plugs and sockets. Hardware, etc. Full building plans provided.
COMPLETE FOR ONLY 57/6 P.P. 2/6.
High Imp. Phones 14/6 extra.

The 'NORPAK' MAINS POWER PACK KIT FOR TRANSISTOR RADIOS

Boosts and greatly extends life of old batteries. Miniature Size—4 x 2 x 1 1/4 in. In attractive two-tone plastic case. Assembled in an hour. Normal output 9 v. 100 mA. (Adjustable) Full Mains Transformer. Full wave germanium diodes. Cartridge fuse. Complete Kit with plans
35/- Plus 1/6 P.P. (Ready assembled 45/-).

P.W. 'MERCURY' 6 PRINTED CIRCUIT VERSION



£9.17.6
Plus 2/6 P.P.

All parts required

This fine new Transistor Superhet gives superb performance on a 7 x 4 in. speaker housed in attractive two-tone cabinet with ferrite aerial.

For both of these fine kits every item down to the last nut and bolt is supplied together with detailed building plans. All parts sold separately. Send 1/6 (2/6 Mercury) for Building Plans (Free with Kit).

PAY AS YOU BUILD SCHEME

AT NO EXTRA COST the above sets may be bought in 3 complete stages of 53/2 ("PW" 6) or 65/10 ("Mercury" 6) each plus 1/6 P.P. (state A, B, or C).

ALIGNMENT SERVICE

We Offer a very comprehensive service for both the above versions purchased from us, including Fault Finding, at reasonable charges (write for details).

WE GUARANTEE TO MAKE YOUR SET WORK

NORCOL LTD

147 LONDON RD., YORKTOWN, CAMBERLEY, SURREY
Phone: CAMBERLEY 3743

TERRIFIC VOLUME !! WITH THE P.W. 6-TRANSISTOR

Medium and Long Wave Pocket Superhet
THE CONTINUED POPULARITY OF THIS FAMOUS SET IS PROOF OF ITS VERY HIGH QUALITY AND FINE PERFORMANCE

- 450 mW Push-Pull Output on 2 1/2 in. P.M. Speaker.
- Printed Circuit.
- Guaranteed first grade Miniature Components.
- High Q Internal Ferrite Rod Aerial.



£7.19.6 Plus 2/- P.P.

All parts required

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 .. Set of 4 for 19/-
DAF95, DF95, DK95, DL95 4 for 26/6

OA2 11/8	6P1 7/-	30L15 11/-	ECC40 13/6	EZ40 6/9	U47 12/-
1A7GT 11/-	6P25 8/-	30P19 14/6	ECC81 4/9	EZ80 6/3	U50 6/-
1D5 7/6	6P28 11/6	30P13 12/3	ECC82 4/9	EZ81 6/3	U52 4/6
1H5GT 8/-	6Q7G 6/-	35A5 15/9	ECC83 7/-	CZ32 9/6	U78 4/6
1NSGT 9/-	6Q7GT 6/-	35L4GT 9/3	ECC84 8/3	KT41 11/6	U191 14/6
1R5 6/-	6SL7GT 5/9	35Z4GT 5/6	ECC85 7/9	KT44 5/9	U281 15/-
1S4 8/-	6SN7GT 4/9	50L6GT 9/-	ECP80 7/9	KT61 9/6	U291 16/6
1S5 5/3	6U4GT 9/9	85A2 8/6	ECP82 8/6	KT63 8/6	U301 17/-
1T4 3/6	6V6G 7/6	AZ31 9/6	ECH35 7/3	MU14 6/6	U801 21/-
1U5 5/9	6V6GT 4/3	E85 7/6	ECH42 9/9	N18 7/-	UARC80 6/3
3A5 9/-	6X4 4/6	CL33 12/3	ECH81 7/9	N78 17/-	UAF42 8/6
3Q4 7/-	6X5GT 6/9	CY31 10/-	ECH83 8/6	PC95 10/-	UB41 7/-
3S4 6/-	7B8 9/-	DAC32 9/-	ECL80 7/6	PC97 10/-	UBC41 7/9
3V4 7/-	7B7 8/-	DAF91 5/3	ECL82 9/-	PCC84 7/6	UBP80 8/3
5U4G 4/6	7C8 7/6	DAF96 7/6	ECL86 10/-	PCC89 9/3	UBP89 8/-
5Y3GT 6/-	7H7 7/6	DF33 9/-	EF37A 7/6	PCF80 7/9	UBL21 14/6
5Z4G 6/-	7S7 9/-	DF91 9/-	EF38 4/6	PCF82 8/-	UC92 9/-
6A5 3/9	7Y4 6/-	DF96 7/6	EF40 11/6	PCF86 12/-	UCC84 13/3
6AM6 3/6	10C2 16/6	DH76 4/9	EF41 7/9	PCL82 8/-	UCB2 7/6
6AQ5 6/-	12A8 10/6	DH77 6/-	EF42 8/6	PCL83 10/6	UCP80 14/6
6AT8 9/-	12AT6 10/6	DH81 9/-	EF43 8/9	PCL84 10/6	UCH21 13/6
6BA6 5/9	12AT7 4/9	DK32 11/-	EF48 4/9	PCL85 10/6	UCH42 8/-
6BE6 5/9	12AX7 4/9	DK91 6/-	EF86 5/9	PEN44 11/-	UCH81 9/9
6BH6 8/3	12AU7 4/9	DK92 7/6	EF89 7/-	PEN66C 8/-	UC143 9/6
6BJ8 5/9	12AX7 4/9	DR96 7/6	EF91 3/6	PL36 11/6	UC183 13/3
6BR7 11/-	12K7GT 4/9	DL33 8/-	EF92 3/9	PL82 7/6	UF41 7/6
6BW8 8/-	12K8GT 4/9	DL35 9/6	EL36 8/6	PL83 7/6	UF89 7/-
6CD6G 27/3	12Q7GT 4/9	DL42 6/-	EL41 9/6	PL84 9/6	UL84 6/6
6F1 10/-	12SN7GT 7/6	DL44 7/6	EL42 9/-	PK4 10/-	URIC 8/-
6F6G 6/6	12Z3 8/6	DL96 7/6	EL81 12/-	PK25 9/6	UY21 11/-
6F13 9/6	20F2 17/-	EABC30 4/9	EL84 9/6	PY32 11/6	UY41 6/6
6F14 9/6	20L1 16/-	EAF42 8/6	EM34 7/3	PY80 7/6	UY85 6/6
6K7G 1/11	20P3 18/9	EB91 8/9	EM80 8/-	PY81 7/6	VP43 9/6
6K7GT 8/6	20P4 20/-	EB93 5/-	EM81 8/6	PY82 6/6	VP41 5/-
6R8G 5/6	20P5 15/9	EC41 8/-	EM84 9/6	PY83 7/9	VP1321 16/6
6K8GT 9/-	25A8G 8/-	EFB80 8/-	EY51 7/6	U22 7/3	W76 4/9
6L18 10/-	25L6GT 7/-	EFB89 8/9	EY84 11/6	U25 12/-	W77 3/9
6LD20 8/-	25Z4G 8/6	EBL21 13/6	EY86 7/-	U26 9/3	Z77 3/6

NEW EDITION RADIO SERVICING POCKET BOOK

by J. P. Hawker.

- 12/6 Postage 6d.
- TRANSISTOR RADIOS. Circuitry & Servicing. A Mullard Pub., 5/- Postage 6d.
- BASIC RADIO COURSE, by J. T. Frye, 32/- Postage 1/-.
- ELEMENTS OF ELECTRONIC CIRCUITS, by J. M. Peters, 21/- Postage 1/-.
- THE RADIO AMATEUR'S HANDBOOK, by A.R.R.L., 1962, 36/- Postage 2/-.
- G.E.C. SCR MANUAL, 12/- Postage 1/-.
- G.E.C. TRANSISTOR MANUAL, 16/- Postage 1/2.
- SERVICE VALVE EQUIVALENTS, by R.S.G.B., 3/- New Edition. Postage 6d.
- RADIO VALVE DATA 7th Ed. Compiled by "WW", 6/- Postage 10d.
- COMPLETE CATALOGUE, 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL LONDON N.16 STA. 4587

Post 6d. per valve
Any Parcel Insured Against Damage in Transit 6d. extra.
Any C.O.D. Parcel 3/- extra.

Club News

REPORTS OF CURRENT ACTIVITIES

AMATEUR RADIO SOCIETY OF CHESHAM AND DISTRICT

Hon. Sec.: Capt. C. G. Stephenson, G3CLJ/T, 21 Lynton Road, Chesham, Buckinghamshire.

At the moment, many of the society's members are spending their time improving their headquarters. However, Morse and practical classes continue to be held each Tuesday, and on Fridays, RAE lectures are given.

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: C. Godsmark, G3IWL, 211 Manwood Road, London, S.E.4.

At the society's recent AGM, W. Martin was elected chairman, C. Godsmark secretary and N. Moore treasurer.

On October 5th, G3HWG gave a lecture on "Oscilloscopes" and also demonstrated some of their uses.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

A surplus sale was held on the first meeting in October and on 10th, "Technical Forum" was the topic for the evening.

On October 17th members enjoyed a film show and on November 3rd a number of members visited the R.S.G.B.'s exhibition in London.

DUDLEY AMATEUR RADIO CLUB

Hon. Sec.: D. H. W. Pratt, G3MHS, 23 Kent Street, Upper Gornal, Dudley, Worcestershire.

The Annual General Meeting of this Club was held on October 12th. On 26th of the same month members attended a demonstration and talk by the Wolverhampton Model Radio Control Society.

LOTHIANS RADIO SOCIETY

Hon. Sec.: G. Ritchie, c/o Cormie, 15 Rosslyn Terrace, Edinburgh 6.

"Monkey Glands for the HRO" was the title of the talk given on October 11th by GM3PQU, who also gave a demonstration of TVI proofing. Visitors from the South Lanark, Fife and Falkirk groups who attended the meeting on October 25th, were entertained with a film show.

Future Events:

November 8th—"Some Aspects of Transistors" by Dr. C. Davidson.

November 22nd—A surplus sale.

MITCHAM AND DISTRICT RADIO SOCIETY

Hon. Sec.: M. Pharaoh, G3LCH, 1 Madeira Road, Mitcham.

A talk on R.F. heating and its uses was given by B. Ayrilwood at the meeting on October 5th and at the following meeting on 19th, VQ4EV presented a film show.

Future Event:

November 16th—"Why be Afraid of Transistors?" by G8TB.

MELTON MOWBRAY AMATEUR RADIO SOCIETY

Hon. Sec.: D. W. Lilel, G3FDF, 23 Melton Road, Asfordby Hill, Melton Mowbray, Leicestershire.

At the meeting on October 18th members listened to a recorded lecture on transmitter design and TVI by N. Shires.

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Boninson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

Members operated a station during this year's Scout Jamboree on the Air, under the call-sign G3MVH. On October 23rd, members travelled to Bradford to attend the film show given at St. George's Hall.

For the first meeting in November, G3FQH gave a lecture on single side band.

SHEFFIELD AMATEUR RADIO CLUB

Hon. Sec.: D. R. A. Hill, 16 Tylney Road, Sheffield 2, Yorkshire.

The energy of many members at the moment is being expended on the task of furnishing the club's headquarters. The all-band transmitter and aerials also claim important places in the club's present programme.

In spite of all this work, many members are continuing to attend both the technical and general meetings and the novices classes are carrying on successfully with Morse classes held on alternate Wednesdays.

SLADE RADIO SOCIETY

Hon. Sec.: C. N. Smart, 110 Woolmore Road, Erdington, Birmingham 23.

On October 19th, the club secretary gave a comprehensive lecture on a new transistorised D.F. receiver, and on 31st of that month members attended the Annual Dinner.

SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: L. A. Metcalfe, 1A Moorlands Road, Birkenshaw, Bradford, Yorkshire.

October proved to be a busy month for this society, starting with a talk called "Language of S.S.B." on 4th. A lecture called "Noise Problems" was given on 18th and later in the month members attended a film show.

The first meeting in November was devoted to "Tape Recorders".

STRATFORD-UPON-AVON AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: P. Robinson, G3MGJ, 43 Loxley Road, Stratford-upon-Avon, Warwickshire.

To meet the May 1963 R.A.E., a series of lectures has been started dealing with radio theory.

The lectures for the two last meetings have been given by John Hewitt, G3MDU, and his subjects included alternating current and voltage, alternating current with inductance, etc.

Future Event:

November 9th—Coupled circuits, acceptors and rejector circuits, by M. Webb.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

★ CHRISTMAS GIFT FOR RADIO ENTHUSIASTS ★

★ Send them PRACTICAL WIRELESS, of course. A year's subscription will bring them a reminder of your good wishes every month throughout 1963 . . . and all through the year they'll thank you for the interest and help it contains. ★

★ Either send your friends' names and addresses, together with your own, and remittance* to cover each subscription, to The Subscription Manager (G.2), PRACTICAL WIRELESS, Tower House, Southampton Street, London, W.C.2, or you may place your instructions with one of the leading newsagents or bookstalls, who will be pleased to make the necessary arrangements. ★

★ Whichever way you choose, your friends will receive a Christmas Greetings Card announcing each gift. ★

★ *RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES):—U.K. £1.9.0, OVERSEAS £1.7.6, CANADA £1.5.0. ★

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

ABSORPTION WATTMETER

(Continued from page 719)

tiometer, but a reversing switch *must* be included and a reading obtained with the voltage applied to the wattmeter both "forward and reverse". The average of these is the "correct" meter reading. (This procedure takes account of differences in diode forward resistance.)

The voltage developed across 3 and 15Ω resistors for the 5 and 20W ranges have been calculated and are given in Table 1. The first step in the calibration process is to set the variable resistor controlling linearity (VR5). Having adjusted VR5 for zero resistance, set the D.C. voltage applied to the wattmeter to 8.66 volts. Switch the wattmeter to measure 5W at 15Ω and adjust VR3 until the meter reads full scale. Then reduce the D.C. voltage to 7.75 volts and note wattmeter reading, and so on down column 5 of Table 1. When the linearity control is correctly adjusted, the results obtained should be similar to those given in Table 2. If the readings obtained are lower than these, set RV5 (linearity) to its mid-position and re-adjust RV3. Repeat the comparison of meter readings and applied voltage.

If the readings are still low then RV5 must be further increased, whilst if the readings are high, RV5 must be reduced in value. This procedure may sound complex but in practice it takes but about 10 minutes.

When the linearity control has been set, the table of applied voltage against meter reading should be put to one side as this is required for absolute calibration of the meter. This may be

Table 2

Voltage	Meter Reading
8.66	1
7.75	0.81
6.7	0.61
5.5	0.40
3.87	0.19
2.74	0.09
0	0

done by drawing a calibration curve or alternatively, the scale can be removed from the meter and re-calibrated by hand. This latter method is preferable, but can result in a very "messy" looking job if great care is not taken.

Table 3

7.5Ω			
Voltage	Power	Voltage	Power
6.12	5	12.25	20
5.5	4	10.95	16
4.74	3	9.5	12
3.87	2	7.75	8
2.74	1	5.48	4
1.94	0.5	3.87	2

COMPONENTS LIST

R1	3Ω	} See text for power rating
RIA	47Ω	
R2	15Ω	
R3	150Ω	} 20%, ¼W carbon
R4	330Ω	
R5	330Ω	
R6	820Ω	
VR1-4	100Ω wire-wound potentiometers	
VR5	250Ω wire-wound potentiometer	
MRI-4	OA70 (Mullard)	
M1	Meter, moving coil, 0-1 mA f.s.d.	
SW1	Switch 3-pole, 2-way	
SW2	Switch 4-pole, 2-way	

The only job remaining now is to set the remaining range potentiometers as follows:

- 1 Set the meter to measure 5W at 3Ω, apply a voltage of 3.87 volts and adjust RV1 for full scale deflection.
- 2 Set the meter to measure 20W at 3Ω, apply a voltage of 7.75 volts and adjust RV2 for full scale deflection.
- 3 Set the meter to measure 20W at 15Ω, apply a voltage of 17.32 volts and adjust RV4 for full scale deflection.

The lead to SW1A should now be reconnected and the wattmeter is completed.

Additional Ranges

If additional or alternative ranges are required it is quite simple to add or substitute these. In Table 3 are given voltages appropriate to 5 and 20W ranges for 7.5Ω load. ■

FRIDAY, FEBRUARY 1st, 1963

A FILM SHOW

(In collaboration with Mullard Ltd.)

CAXTON HALL, WESTMINSTER

at 7.30 p.m.

Send for your free tickets now marking your envelope "Caxton Hall" in the top left-hand corner and enclosing a stamped addressed envelope (at least 3½ in. x 6 in.) for the tickets.

The films to be shown will include "Fuel for the Future" and "The Electroneers", and as in previous years, the programme has been arranged to appeal to all who are interested in radio.

The demand for tickets will be great; order yours NOW


Questions and answers for budding engineers

Q. What age should I be for this advertisement to concern me?

A. Around 16 to 19 if you want to join Electricity Supply from school. If you're an engineering graduate, or diploma-holder, you'll probably be in your early twenties. (Older, if you're a parent or teacher!)

Q. Where can I find an engineering career offering me plenty of scope?

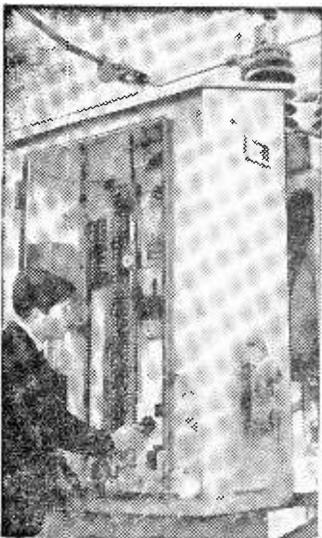A. Electricity Supply offers *dozens* of good jobs. Few individual firms can hope to match the variety you'll find in the Electricity Supply industry.



Q. What is Electricity Supply?

A. It's the national industry responsible for generating electricity, transmitting it, distributing it throughout the country and advising how it can be used.



Q. What qualifications must I have?

A. School-leavers need either a good Ordinary level G.C.E. including Maths, English, and a Science subject; or two Advanced level passes in Maths and Physics. Graduates need a British degree in electrical or mechanical engineering. Or you need an engineering diploma. You can apply in your last year at school or college — preferably in the January-March period before you take your final exams.



Q. What sort of training do I get?

A. For school-leavers, there's a 5-year apprenticeship. It consists of planned practical experience in the various departments, accompanied, for 'O' level entrants, by day release to a technical college and, for 'A' level recruits, by a 'sandwich' course, both leading to engineering qualifications.

Graduate trainees have a 2-year practical training in one of the main sections of the industry. The training of diploma-holders is planned to take into account past practical experience.



Q. Where do I go from here?

A. It's impossible to tell you here all about an industry that has to *double* its output every ten years. But jobs include everything from running a Power Station to bringing power to a new estate. For full details, write (giving age and exams you've passed) to: The Education and Training Officer, The Electricity Council, 155 Winsley Street, London, W.1.

**THE DEMAND FOR ELECTRICITY
DOUBLES EVERY TEN YEARS**

RECEIVERS & COMPONENTS


"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. P.W. 7/9, 138 Lewisham Way, SE14, Tideway 6666.

SPEAKER REPAIRS. Cones/Fields fitted. Clock coils wound. L. S. REPAIRS, Pluckley, Ashford, Kent.

TRANSISTOR KITS built - cheaper than building your own. Choose from free list of latest top quality designs from: M. L. COLTON, 21 Maplewood Drive, Blackpool.

VALVES! VALVES! VALVES! We are the cheapest. Very large stocks. Also Transistor Radio Kits. Trade supplied. S.A.E. for lists. LEWIS, 46 Woodford Avenue, Ilford, Essex.

ULTRA LINEAR AMPLIFIERS

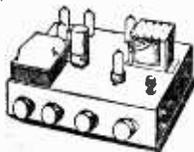

High Fidelity. 15 watts. Valves ECC83. ECC93. EL84. EL94. E281. Two inputs. Sensitivity 10 millivolts. Bass & Treble controls. 3 & 15 ohms outputs. Kit £6.10.0. plus 5/-

carr. Factory built. £9. plus 5/- carr. Sim. Mar 30 watt £12. plus 7/6 carr. Leaflet free. Same day despatch.

STROUD AUDIO

Bath Road, Stroud, Glos.
Tel. Stroud 783.

A1 POST-FREE BARGAINS. First-grade TRANSISTORS: OC44 8/9, OC45 7/3, OC70 OC71 5/3, OC72 OC74 OC78 OC81 7/-, OC170 8/9, OC171 9/3. ALL other Mullard types stocked. VALVES set tested: EB91 EF91 EF50 EP80 9d., 6P1 10P1 1/-, L63 20D1 ECL80 3/-, PY81 PY30 B36 4/-, PCP80 PL82 PL83 PY80 PY82 KT33C 4/3, PL38 N37 KT36 4/9, PCL83 8/-, PY32 GK25 5/9, 185BT 275U U25 9/8, 10% discount on six, 25% on 12, any combination. Ready-made Transistor Set 32/-, A1 RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

TRANSISTORS Marked and Tested Packets of 10. Unmarked but Tested Packets of 16. Unmarked and Untested Packets of 40. Duds suitable as Diodes Packets of 80. All packets 20/- each. Any 2 Packets 37/6. C.W.O. K. R. WHISTON, Dept. TPW, New Mills, Stockport.

CANADIAN MARCONI 52 RECEIVERS

An excellent Communications Receiver covering 1.75 to 16 mc/s in 3 bands. 1 R.F., 2 I.F. stages. 10 valves plus 3 valve crystal calibrator, 10, 100 and 1,000 kc/s. Crash Limiter, Broad/Sharp Selectivity, 500 Mic/amp. valve check/Signal Level meter. 3 in. speaker phone jacks, power required 150 v. H.T. 12 v. a.c. or d.c. I.T. PRICES: Receiver only £5.10, carriage £1. Receiver in steel cabinet with Installation kit comprising power unit ZE12 for a.c. mains 230 or 115 v. or 12 v. D.C., all connecting cables and spares, two pairs padded Headphones and aerial wire. £9.10, carriage £1. Send S.A.E. for detailed leaflet.

G.W.M. RADIO LIMITED
40/42 Portland Road, Worthing, Sussex.

RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS

(continued)

TRANSISTOR COMPONENTS. 7 x 4in. 35 ohm speakers, 25/-, 7 x 4in. 3 ohm. 19/6.

EARPIECES. 7 ohm. 150 ohm. 6/8. Xtal with Jack. 7/8, all complete with plugs. 4 pole 2 way switches 1 inch spindle. 2/6 each. Min. Caps. 15 v. wkg.—1, 2, 4, 5, 8, 10, 18, 35, 50 mfd., 64 mfd., 10 v. 100 mfd., 6 v., 100 mfd., 12 v., all at 1/6 each. Resistors mostly 10% small, 10 ohms to 10 meg., 3d. each. Ceramicons, most values in stock, 1 pd. to 5,000 pd. Slide switches, DP/DT, 3/- each.

TRANSISTORS. OC44, OC45, 7/6 each. A.F. Pack OC81D, 2 OC81, 19/6, set. G.E.C. 874, 4/6, S6, S7, good output transistors. 2/6 each. Red spots, 2/3, White spots, 2/6, OC76, 3/6, OCP71, 12/6, OAB1 Diodes, 2/6, GEX00, 9d. Terms C.W.O. or C.O.D.

BROADWAY ELECTRONICS

92 Mitcham Road, Tooting, S.W. 17.

EXCEPTIONAL VALUE: Picture Tubes, brand new, Mazda 19in., CME1901, Mullard 19in., AW47-90/91, £4/10/-; Mullard 23in., AW59/80, £8/10/-; carriage (insured) paid. 12 months' guarantee. Note, all brand new. We also supply most other sizes completely regunned at £4/17/6. guaranteed 12 months. TOMLINS, 156 Lewisham Way, New Cross, SE14. TID 3857.

DATA TRANSISTOR POCKET KITS

NO SOLDERING OR DRILLING. COMPLETELY SELF CONTAINED

NO AERIAL REQUIRED - MEDIUM & LONG WAVE - ASSEMBLY TOOL PROVIDED - CAN BE BUILT BY ANYONE



DATA 427

5½ x 3 x 1½ in.

75/-

P.P. 2/9 ex. Battery 2/3 ex.

**4 TRANSISTORS - 2 DIODES
7 STAGES - MOVING COIL SPEAKER**



DATA 326

4½ x 2½ x 1½ in.

49/6

P.P. 2/- ex. Battery 1/- ex.

**3 TRANSISTORS - 2 DIODES - 6 STAGES - PERSONAL EAR PIECE
ALL PARTS CAN BE BOUGHT SEPARATELY**

DATA ELECTRONICS LTD.

6 HILLSIDE GDNS., EDGWARE, Middlesex

RECEIVERS & COMPONENTS

(continued)

NEW 10.7 mc/s I.F.Ts. usual square can. 3/- each. S.A.E. for latest lists. Ajax Electronics, 572 Fulham Road, London, S.W.6.

CONDENSERS. Fantastic Bargain! 500,000 miniature condensers, ¼" long, ¼" diameter. Tested 750 volts. Capacity .0001 to .04uf. 7/6 per 100, post free. Ideal for transistor sets. MILWARD, 17 Peel Close, Drayton Bassett, Staffordshire.

Famous R107 Receiver

All Band Amateur, Shipping Broadcast, 9 valves, 1.2 to 17 mc/s (18 to 250 metres.) 100/230V.A.C. or 12V.D.C. operation. Internal Speaker. Absolutely as new. £13.10.0. Carr. 30/-

Many other bargains. S.A.E. enquiries.

A. J. THOMPSON,
"Eiling Lodge", Codicote, Hitchin, Herts
Phone: Codicote 242

FOR SALE

GRUNDIG MA1 Transistor Tape Pre-amplifiers suitable for use as microphone transformer, pick-up and tape head booster. Listed at 4½ gns., offered at £2 17s 6d. Send for full details and free lists. LEE ELECTRONICS, 400 Edgware Road, W2 (PADDDINGTON 5521).

BRAND NEW Adjustable Steel Shelving, 73in. high by 34in. wide by 12in. deep. Stove Enamelled dark green. Sent unassembled. Six-shelf bay £3/15/-. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

ASK your dealer for American Ferro-dynamics. "Brand Five" Recording Tapes—the best tape value!

BUILDING YOUR OWN ORGAN. We have for disposal a few obsolete hire organs. Wealth of parts, including keyboards, consoles, pedal boards, transformers, condensers, and other valuable electronic components. Write for details and prices. Box No. 41.

EXCEPTIONAL Transistor Portable Tape Recorder, value £6/19/6, complete with crystal microphone, earphone, spools, tape, batteries, instructions, presentation box (extra tapes 100 4/6). Ideal gift. £6/19/6. Satisfaction guaranteed. Postage packing 2/6. TOMLINS, 156 Lewisham Way, New Cross, SE14.

TRANSISTORS 100% TESTED

Red Spot Audio, 1/6 each, 14/- doz. A.E.I. Branded Audio XB103 and X.F. XA102, 2/3 each, 25/- doz. RCI41 (11 watt) Audio, 6/6 each, 12/- pair.

All Guaranteed. Post Free.

IDEAL XMAS PRESENTS:

EPIOK Multimeters only £4.10 each. 100 c. Slim Mics, only 32/6 each.

Large Stocks of Ex-Govt. Equipment.

B. W. CURSONS

78 BROAD STREET
CANTERBURY. Phone 5442

MOTORS

B.S.R. MONARCH TAPE RECORDER

and RECORD PLAYER

MOTORS

Price

Monarch Tape-Deck
TD2 Complete
Assembly .. **46/-**

Motor for Monarch
Record Changer
TU8 .. **44/-**

Motor for Monarch
Record Changer
TU9 .. **44/-**

Motor for Monarch
Record Changer
UA12 & UA14 **44/-**

Motor for Monarch
Record Changer UA7,
UA6, UA5,
HF100, GU4A **40/-**

All Motors P. & P. 3/6 extra

ALL SPARES AVAILABLE

Any Motor Supplied

Enquiries S.A.E. P.P. 3/6

WYNSOR TELEVISION

TECHNICAL DIVISION

St. Albans Rd., Barnet
Herts. BAR 1769

FOR SALE (continued)

AMATEUR LICENCE Morse Course. The new Rhythm Method of teaching takes the drudgery out of learning Morse and is the quickest known! For full explanatory booklet: SAE G3CHS, 45 Green Lane, Purley, Surrey.

BARGAIN, EIGHT 45 rev/min Brand New Pop singles (value over 50/-) for £1. S.A.E. for details to: R. FLETCHER (P.W.), 24 Old Hall St., Burnley, Lancs.

PERSONAL EARPHONES

for transistor radios high sensitivity units 25/- complete.

CUNNINGHAM BEATTIE LTD.

49 Wigmore Street, W.1.

SAMPLE PARCEL (and Catalogue). Fantastic value. Sent for only 8/6: Condensers, Knobs, Sleeves, Grommets, Springs, Pots, Droppers, Resistors, Felt Washers, Sockets, Tags, Cond-Clips, Sclaving, etc. ALBATROSS Eng. Co., Gosberton, Spalding, Lincs.

12 VOLTS CONVERTER TO 250 VOLTS Run all your mains a.c.—d.c. equipment from your car battery, shavers, record players, radios, etc. New type vibrator, low battery drain, not to be confused with heavy battery drain Rotary transformers. Spare fuses, Vibrator, battery clips, etc. 12 volts to 250 at 100 m.a. **BRAND NEW** tested, inwaterproofed cartons, ONLY 32/6. carr. 7/6 (few only).

(DEPT. G), J. T. SUPPLY, 309 MEANWOOD ROAD, LEEDS, 7.

TRANSISTOR RADIO KITS built up at reasonable prices. Also complete sets for sale. Send requirements to: NORMAN'S RADIO, Caistor Road, Market Rasen, Lincs. enclosing S.A.E. (Mail order only.)

SPECIAL OFFERS NO INTEREST TERMS DELIVERED FREE

Armstrong AF208 Chassis.	Cash £22.18.0
or 68/- dpt. and 10/- weekly for 29 wks.	Cash £30.12.0
Armstrong Jubilee Mk. 11.	Cash £30.12.0
or 87/- dpt. and 15/- weekly for 33 wks.	Cash £32.15.0
Armstrong Stereo 55.	Cash £32.15.0
or 85/- dpt. and 15/- weekly for 34 wks.	Cash £43.10.0
Armstrong Stereo 12, Mk. 11.	Cash £43.10.0
or 130/- dpt. and 20/- weekly for 37 wks.	Cash £44.2.6
Armstrong A20/PCU25.	Cash £44.2.6
or 132/6 dpt. and 20/- weekly for 38 wks.	Cash £5.5.1
Goodmans Axiette 8.	Cash £5.5.1
or 15/1 dpt. and 5/- weekly for 18 wks.	Cash £5.18.8
Goodmans Axiom 10.	Cash £5.18.8
or 16/8 dpt. and 5/- weekly for 20 wks.	Cash £9.15.0
Goodmans Axiom 201.	Cash £9.15.0
or 30/- dpt. and 5/- weekly for 33 wks.	Cash £7.0.0
Goodmans Tribax 5K/20XL.	Cash £7.0.0
or 20/- dpt. and 5/- weekly for 24 wks.	Cash £13.18.9
Garrard Autoslim GCS.	Cash £7.14.11
or 29/11 dpt. and 5/- weekly for 29 wks.	Cash £19.13.0
Garrard 4H1/GCS10.	Cash £19.13.0
or 63/- dpt. and 10/- weekly for 33 wks.	Cash £13.18.9
Garrard AT6/EV29.	Cash £13.18.9
or 42/3 dpt. and 7/6 weekly for 31 wks.	

Payment accepted monthly by Banker's Draft. These units and other equipment supplied on 18 months' H.P. terms.

A. L. STAMFORD Ltd. (Dept. A29)
98 WEYMOUTH TERRACE, LONDON, E.2

FOR SALE (continued)

SLIDE RULES. Essential to every radio engineer. Send for price list to KENMAR, YOUNG, 137 Westminster Bridge Road, London SE1.

WANTED

A PROMPT CASH OFFER for your surplus Brand New Valves and Transistors. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

WANTED: NEW Valves and Transistors, any quantity. S. N. WILLETS, 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

VALVES WANTED IMMEDIATE CASH SETTLEMENT

Loose or boxed but must be new

Phone, write or call—
RADIO FACILITIES, LTD.
38 Chalcot Road, London, NW1
PRImrose 9090
THE VALVE SPECIALISTS

WANTED: TEST GEAR, Meters Valves, Components, Communication Sets, Amplifiers. HUGGETTS LTD., 2-4, Pawson's Road, West Croydon, Surrey.

TUNABLE OSCILLATOR "JAM-SISTOR" wanted. Blueprint, of same. State price. BOX 42.

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

ABSOLUTE TOP PRICES paid for Valves, Transistors, Components, etc. in quantity. Try us first. Cash by return. Witon Radio & TV Supplies, 42 Darlington St., Wolverhampton. Tel 20315.

NEW VALVES WANTED

Any type, any quantity

CASH PAID

R.S.T. 211 Streatham Road,

Mitcham, Surrey

Telephone: MITCHAM 6202

SOUND RECORDINGS

TAPE BARGAINS in all sizes. Example: Top brand 5in. 1.200ft 19/6 p. and p. 1/3. S.A.E. for list. Large choice of New and Used Recorders. E. C. KINGSLEY AND CO., 132 Tottenham Court Road, London, W1. EUS 6500.

COURSES

CITY AND COUNTY OF BRISTOL EDUCATION COMMITTEE

BRISTOL TECHNICAL COLLEGE

Principal: E. POOLE, B.Sc.(Eng.), M.I.Mech.E., M.I.Prod.E.

SCHOOL OF MARINE RADIO AND RADAR

Lecturer in Charge: F. E. BARLTROP (ex A.S.T. Hamble)

MARINE RADIO OFFICERS

A full-time Course for prospective Radio Officers in the Merchant Navy, leading to the 2nd and 1st Class P.M.G. Certificates, and the M.O.T. Radar Maintenance Certificate, is provided, and entry may be made in January, May or September of each year.

Fees: **P.M.G. Courses:**
 Over 18 years of age £23.10.0 per College year
 Under 18 years of age £2.0.0 per College year
M.O.T. Radar £5.0.0 per term

A six-week Course of Pre-Sea Training is also held, and entry is normally made on completion of the Radar Course.

For further particulars apply to: THE REGISTRAR,
 BRISTOL TECHNICAL COLLEGE, ASHLEY DOWN, BRISTOL 7

SITUATIONS VACANT

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, G.C.E., etc., brings high pay and security. "No pass—no pay" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. B.I.E.T. (Dept. 242B), London, W8.

TV AND RADIO, A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc. on "No pass—no fee" terms. Over 95% successes. For details of exams and courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 148-page handbook, free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London, W8.

CITY AND GUILDS (Electrical, etc.) on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29 Wright's Lane, London, W8.

EDUCATIONAL

The Incorporated Practitioners in Radio and Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, 20 Fairfield Road, London, N8.

**Radio
 Television
 & Electronics**

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; P.M.G.'s certs., etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE** prospectus stating subjects to

I.C.S.

(Dept. 541), Intertext House, Parkgate Road, London, S.W.11

BECOME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam. Home-study Courses in Radio TV, Servicing and Maintenance. R.T.E.B., City and Guilds, etc. Highly informative 132-page Guide—**FREE!** N.I.E. (Dept. 363), 148 Holborn, London, E.C.1.

LEARN RADIO AND ELECTRONICS the new and practical way. Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault-finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11, P.W., RADIO-STRUCTOR, Reading.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period—low fees; scholarships, etc. available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE,** Colwyn Bay.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

DON'T FUMBLE with Formulae. Master Mathematics quickly and easily the Under-standable Way.



The Dryden School of **UNDERSTANDABLE MATHEMATICS**

11F12 Dryden Chambers, Oxford St. London, W.1.

Name: _____
 Address: _____

"**HOW AND WHY**" of Radio and Electronics made easy by a new, non-maths practical way. Postal instruction based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. P.W. 12, RADIO-STRUCTOR, Reading.

METAL WORK

METALWORK. All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS' METALWORKS LTD.,** Chapman St., Loughborough.

UNITED KINGDOM ATOMIC ENERGY AUTHORITY, ATOMIC ENERGY ESTABLISHMENT, WINFRITH

Electronic Instrument Mechanics

A.E.E. Winfrith require experienced men with knowledge of electronic equipment and/or industrial instrumentation for fault diagnosis, repair and calibration of a wide range of instruments used in nuclear reactors and associated experiments.

Men with Services, Industrial or Commercial backgrounds of radar, radio, television, industrial or aircraft instruments are invited to write for further information. Training in Specialised Techniques is provided for successful applicants having suitable background.

Married men living beyond daily travelling distance may be eligible for housing and this will be determined at time of interview. A lodging allowance is payable whilst waiting for housing. Working conditions are good and include sick pay and pension scheme.

Application forms may be obtained by sending a post card quoting your name, address and the reference EL/INST/NAT to the Labour Department, A.E.E. Winfrith, Dorchester, Dorset.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES IN MINUTES from that great book, The Principles of TV Receiver Servicing. 10/6 all book houses and radio wholesalers. If not in stock from Secretary, I.P.R.E., 20 Fairfield Road, London, N8.

MISCELLANEOUS

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 4 valves. With its variable attack you can play Classics and Swin.

Write **NOW** for free leaflet and further details to C. & S., 30 Maule Street, Darlington, Durham. Send 2d. stamp.



By repairing Radio and TV Sets as a job or as a spare time business. Our practical course will show you the way. No previous experience is required

SEND FOR FREE BOOK TODAY!

RADIOSTRUCTOR

Dept. G77

READING, BERKS

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV, 1930-1962. Prices from 1/-, with free fault-finding guide. Catalogue of 6,000 models 1/6. 125 Radio/TV sheets covering many popular models 20/-. S.A.E. inquiries: HAMILTON RADIO, Western Road, St Leonards, Sussex.

WHY TOLERATE DELAY when we can supply your Radio or TV Service Sheet by return of post at 4/- each, plus postage. List 1/-. Also Manuals for sale and hire. List 1/-. S.A.E. with inquiries please. Mail orders only to S.P. DISTRIBUTORS, 44 Old Bond Street, London, W1.

FAULTFINDER FILES, showing common faults that each receiver is prone to and other useful servicing information, 2/- each. List 9d., plus postage. Mail orders only. S.P. DISTRIBUTORS, 44 Old Bond Street, London, W1.

SERVICE SHEETS, Radio and TV, 4/- each. List 1/-. All orders dispatched on day received. Also manuals for sale and hire. List 1/-. S.A.E. please. SULTAN RADIO, Pantiles Chambers, Tunbridge Wells, Kent.

SERVICE SHEETS; also Current and Obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London, W12. Phone: SHE 8441.

SERVICE SHEETS: Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries: TELRAY, 11 Maudland Bk., Preston.

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/-	DAF96, DF96, DK96, DL96, SET of 4, 25/8
1A5 7/-	DL33 7/6
1R5 5/6	DL35 9/6
1R5 4/6	DL92 5/11
1A 5/11	PCL82 8/3
3S4 5/11	DL94 6/9
3V4 6/9	EB91 3/-
5U4G 4/6	EBC41 7/6
5Y3GT 5/9	EBF80 7/9
5Z4G 8/6	EBL21 12/-
6AM8 2/9	ECC40 13/-
6K1G 1/9	ECC81 4/6
6K3G 4/9	ECC82 4/6
6Q7G 5/6	ECC83 6/3
6V6G 4/-	ECC84 7/3
6V8GT 6/9	EY85 7/6
6X5GT 6/6	ECF80 7/9
12K7GT 4/3	ECF82 8/3
12K8GT 9/-	ECH42 7/9
12Q7GT 4/6	ECL80 5/9
12SN7GT 8/-	EB41 7/6
35L8GT 8/-	EF41 6/9
35Z4GT 5/-	EF80 4/3
AZ31 8/9	EF85 5/9
CL33 8/6	EF86 8/6
DAC32 8/9	EF89 8/9
DAF91 4/6	EF91 2/9
DAF96 6/9	EL41 9/-
DC90 8/6	EL84 6/3
DF91 8/9	EY31 7/3
DF93 3/3	EY86 6/9
DF96 6/9	EZ40 8/9
DH77 6/-	EZ80 5/9
DK32 10/6	EZ91 6/9
DK91 5/6	MU14 5/6
DK92 6/9	PCB84 6/9
DK96 7/3	PCB89 9/-
	U41 5/6
	U45 6/3
	VF43 8/6
	Z77 2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra. Office address, no callers.

GERALD BERNARD

(Note new address—formerly of Leeds)
83 OSBALDESTON ROAD,
STOKE NEWINGTON, LONDON, N.16

**NOW ANYONE
CAN AFFORD TO
TRAIN TO BE
AN EXPERT IN
RADIO and
ELECTRONICS**

**EVEN QUALIFY FOR A
CERTIFICATE**

It's the most exciting news of the year! Just imagine. You can get 35 large, fact-packed lessons for little more than 1/- per lesson! The lessons are crystal clear, practical cases to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert.

Compare favourably with some courses costing ten times as much. You save because you receive all the lessons at one time and are not required to purchase equipment you do not need.

This is a real home-study course that has been bound into one giant 5 x 11in. 216 page manual. Each page is divided into two columns. A wide column features the text, while a narrow column at the side has the instructor's comments, helpful suggestions and additional pictures to simplify the difficult parts.

Everyone can benefit from this practical course. No old-fashioned (or pseudo modern) methods used here, just straight forward, easy to understand explanations to help you make more money in electronics.

As an optional extra, you may pay a further fee if you wish to take the Sim-Tech radio and electronics examination. Students who attain a minimum of 50% correct answers can qualify for a certificate of proficiency in basic radio and electronics. Details sent with each course ordered.

You must be convinced that this is the best value you have ever seen in electronic training, otherwise you can return the manual (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven days.

The price? Only 38/-, plus postage.

**FREE
TRIAL
OFFER!**

To SIM-TECH TECHNICAL BOOKS, Dept. WA5, Gater's Mill, West End, Southampton, Hants.

- RUSH Radio and Electronics Course for seven days examination. If I keep the course I can either pay 37/6d. cash or 12/6d. deposit after seven days and two payments of 12/6d. monthly. Otherwise I will return the course post-paid and owe nothing with order.
- SAVE! Send only 36/- if paying cash with order. (We pay postage). Same 7-day money-back guarantee.

Name _____
Address _____
City _____ County _____

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses.

12 volt 36 watt AC/DC SBC 8/6. P. & P. 1/-
12 volt 60 watt AC/DC SBC 8/6. P. & P. 1/-
Transformer to suit the above: Input 200-240 A.C. Output 12 volt A.C. 36 watt, 16/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 30 watt, 22/6. P. & P. 3/6.
Set of 4 colours FLUORESCENT Paint. Red, Yellow, Green and Blue in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs. 9/6. P. & P. 1/6.
BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as if stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.
New! CV2296 STROBOTRON FLASH-TUBE made by Ferranti, brand new, I.O. base. Price 15/- P. & P. 1/6.

MAGNETIC COUNTERS
10 IMPULSES PER SECOND
Very latest High Speed type ex F.O., guaranteed perfect. Type No. 100B, coil 2,300 ohms. For 48 volt D.C. operation will work on 36 volt, overall size 4 x 1 x 1in. Also available, type 10A which can be used as an interesting accessory with our Strobe unit. Either type price 15/- P. & P. 1/6.



Variable Voltage Transformer
Input 230 v. A.C. Output 0-280 v. at 2 1/2 amp. Fully shrouded. New. £5.19.6. inc. carriage. Also available from stock, 5, 8, 10 and 20 amp. Write for details.

ORP 60 MULLARD CADMIUM SULPHIDE PHOTOCELLS

With mounting and leads including circuit for making light sensitive switches, 7/6. Post paid.

SIEMENS H.S. RELAY. Very latest type, sealed. H98E, 1,700 ohms plus 1,700 ohms, single C/O contacts. Price 16/6 each, plus 1/- P. & P.

Miniature ILEX Switch, 24 volt D.C. operation. Two break 1 position plus Homing Contact. A miniature and compact form of unselector. Ex brand new equipment, 32/6. P. & P. 2/-.

7 R.P.M. Geared Motor, 12 volt D.C. Double Gearbox. Consumption 1 amp, size 3 1/2 x 2 1/2 x 2in. Weight 15 oz. Small and extremely powerful, 32/6. P. & P. 2/6.

NEW P.O. RELAYS TYPE 3000
2,000 ohms coil, 4 make 4 break, 12/6 each.
500-500 ohms (1,000) ohms 2 changeovers, 7/6 each.
Price 12/6. 6,500 ohms coil, 2 light c/o., 2 heavy duty c/o. Price 22/6. 16,000 ohms, 2 make 2 break. Price 15/- P. & P. 1/- each item.

100 OHM COIL for 6 v. operation, 4 make, 4 break, 9/6.

CHROMPTON PARKINSON BRAND
NEW 1 lb. MOTORS. 230/250 VOLT A.C. 1.440 R.P.M. Fitted with 2 1/2 x 1in. SPINDLE. Price £3.15.0. Carriage 8/6.

AVO METER MODEL 7. Individually tested on all ranges and guaranteed. Inclusive of Test Leads. £11.5.0 each. P. & P. 5/-. Case 20/-.

SPEAKER
A beautifully made Speaker and Control Unit for the famous Collins TCS communication equipment. Can be used with any top-grade communication setup.

Comprising a super 5in. 3 to 5 ohm speaker, 600 ohm matching transformer, constant impedance type volume control, 3 control switches. Fitted in robust crackle finished case. 29/6. P. & P. 4/-.

SERVICE TRADING CO.

All Mail Orders also callers
47-49 High Street, Kingston on Thames
Tel.: KINGSTON 9450
Personal callers only
9 Little Newport Street, London W.C.2
(off Leicester Square)
Tel.: GERrard 0876

CABINETS & HI-FI EQUIPMENT

We can supply any cabinet to your own specification



The Lowboy
Price 24 gns.

This is only one example of—THE LARGEST RANGE OF CABINETS IN THE COUNTRY. Equipment is also our speciality. SEND TODAY FOR THE TWO NEW LEWIS CATALOGUES. Designed to assist your choice of cabinet and equipment. THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. THE unique 64 page equipment catalogue. Please send your two new catalogues enclosed in P.O. for 3/6 which will be credited against any purchase I make.

LEWIS radio

100 (P112) Chase Side, Southgate, London, N.14. Tel 3733/9666

H.A.C. SHORT-WAVE EQUIPMENT

AND

SHORT-WAVE KITS

Famous for over 25 years for... S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C", Price 25/-. Two-valve Kit, Model "E", Price 50/-. New Addition: Model "K", Super sensitive "All Dry" Receiver. Special Inc. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS
Dept. TH, 44 Old Bond Street, London W.1

Please send me FREE and without obligation your 1962 literature.

NAME.....

ADDRESS.....



The PUNCH you need!

HOLE PUNCHES			
Instant Type	5/6 ea.
3/8" diameter	6/8 ea.
Screw-up Type	7/2 "
1/2" diameter	7/8 "
" B7G	8/3 "
" B8A, B9A	8/7 "
"	9/6 "
"	10/11 ea.
1 1/4" diameter Int. Octal	13/3 "
1 1/2" "	15/6 "
1 3/4" "	17/11 "
1 7/8" "	20/4 "
2 1/4" "	27/8 "
2 3/4" "	Meter

Postage and packing 1/-. Complete set including postage and packing, £7.10.0

We regret all prices will be increased from 1st January 1963

Oliver & Randall Ltd

Dept. 7
40 PERRY HILL, LONDON, S.E.6
Tel.: Forest Hill 3415

SOUTHERN RADIO SUPPLY LTD.

11 LITTLE NEWPORT STREET
LONDON W.C.2. GER 6653

All goods still available as previously advertised



One-valve receiver with electrical band-spread. Attractive blue hammer finish with gold lettering. Amazing performance. Covers 20-60 metres. All parts supplied, no drilling. ONLY 37/8. P. & P. 2/8. Other plug-in coils available 10-2000 metres.

THE CAROUSEL

A 5-stage transistor portable. Attractive two-tone cabinet 9 x 8 x 3in. Covers Long and Med. wavebands. Amazing performance. 5in. loudspeaker, 500 Mw push-pull output. A luxury portable at low cost. £4.19.6 P. & P. 3/6.

THE 208

A pocket portable of contemporary design, printed circuit, push-pull output, high gain ferrite aerial. Tunes over medium waveband—using 6 semiconductor. £4.10.0 P. & P. 2/8.

All kits are fully guaranteed, using only brand new first grade components.

FRADAN RADIO
36 LEIGH RD., LEIGH, LANCs.

Portable Transistor Kit, £5.19.6 (post 3/6). Covers M. & L. Waves, no aerial required, no difficult aligning, simple to follow instructions. Pocket Kits from 52/6 (post 2/-). Pocket Super-het Kit, £6.19.6 (post 3/-). Genuine Red Spot Transistors 2/3, White Spots 2/3, Yell/Green 3/-. Mullard OC71, 6/-; OC72, 7/6; OC44, 9/6; OC45, 7/6. Sets of 6 for Superhets, Mullard 40/-; our selection 30/-. Newmarket V15/10P, 15/-; Silicon Rectifiers 70 piv. 1/2 amp., 3/3; 400 piv. 1/2 amp., 4/9. Sub-min Electrolytics 2, 4, 8, 10, 16, 32, 50uF, 1/9. 100uF 2/9; 250, 500, 1000uF, 3/3. Transistor Holders 1/-; Super Coax. 74 ohms., 6d. yd. Tanny Mike, 3/6 (post 2/-). Crystal Inserts new 7/6. The amazing Gortler 1 watt amplifier (6 volt) ideal for Portable Record Player, £4.12.6. R109A set, brand new, £4 (carriage paid). Driver Transformer P.P. and output P.P. Trans (L744 and LT700) 4/6 each. Headphones H/R., 13/6 and 17/6; L/R., 8/6; Hearing Aid Earphone L/R., 8/6; H/R. (Crystal) 10/-. Twin Gang Var. Capac. 6/6. Battery Charger 6/12v, 32 to 4 amp. 69/11 (post 3/6). 5in. Loudspeaker 18/6, Ardent Trans. D131, D132, 10/- ea. D239, D240, 8/6 ea. Solon Soldering Iron 24/-. Tems: C.W.O. Post extra, excess refunded. Send 10d. stamps for Transistor Notes. MOORES EXPERIMENTAL SUPPLIES (Dept. P) 8 & 10 Graville St., Sheffield 2

RES/CAP. BRIDGE 39/6

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. PF)
Raleigh Mews, Raleigh Street, Nottingham

THE AMATEUR RADIO HANDBOOK 1962

by R.S.G.B., new edition, 34/-, postage 2/6. Radio Servicing Pocket Book, new edition, by Hawker, 12/8, postage 9d. Experimental Recording for Beginners, by Tuchings, 5/-, postage 6d. Handbook of Electronic Tables and Formulas, by Herrington, 15/-, postage 1/-; Beginners Guide to Radio, new impression, 7/6, postage 9d. Magnetic Sound Recording, by Snel, 26/6, postage 1/-. Records and Gramophone Equipment, by Bradley, 8/8, postage 9d. Servicing Transistor Receivers, new enlarged edition, by Pettit, 7/6, postage 6d. Radio Amateurs Examination Manual, 2nd edition, by R.S.G.B., 5/-, postage 6d.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2 (adjoining Lisle Street)

18,000 O.P.V. MULTIMETER KIT

Ranges 0-0.25 and 2.5V D.C.; 10, 25, 100, 250, 500, 1000V A.C.; D.C. and output volts; 100 ohms to 10 Meg. (2 ranges); 0.25, 2.5, 25, 250 mA D.C. (2.5A range 4/- extra). Kit comprises new 3 x 2 1/2in. Weston 0-50uA m.c. meter and all parts except case and battery. Settings ready adjusted to 1%. High stability 1% multipliers (1% stability as stocks permit). Price 68/-, post free. Circuit multimeter scale, instructions 9d. free with kit.

NOUGHTS AND CROSSES MACHINE

This is a fantastic device which will play a game against you, and NEVER LOSE. It is a thinking machine, with a brain, yet is simple, and costs less than 70/- to build. Full circuit, instructions, and details of 250 REWARD to first person to beat the machine, 3/6.

High Stab. 1% Resistors. All popular values 2/-.
1W 1% and 1% Wirewound Resistors. Your value wound to order.

PLANET INSTRUMENT CO.
25 DOMINION AVENUE, LEEDS 7

CLYNE RADIO LTD.



18 TOTTENHAM COURT ROAD, W.1
162 HOLLOWAY ROAD, LONDON N.7
9 CAMBERWELL CHURCH STREET, S.E.5
10 WITTHY GROVE, MANCHESTER, 4

All post orders, etc. to 162 HOLLOWAY ROAD, LONDON, N.7

THE COMPONENT SPECIALISTS

MUSeum 5929/0095
NORth 6295/6/7
RODney 2875
Blackfriars 5379

The "AIR KING"

Our new highly successful Six transistor luxury portable with the "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio with full MEDIUM wave and LONG wave coverage.

Look at these features!



- ★ 500 milliwatt output to high flux 7 x 3 1/2 in. high fidelity loudspeakers.
- ★ Six selected Mullard Transistors in latest super sensitive circuit, plus germanium diode. ★ Compact size—only 3 1/2 x 3 1/2 x 6 1/2 in. (high).
- ★ Attractive three tone cabinet, Black, Dark Grey, and Silver Grey, with gilt control knobs and all gilt fittings.
- ★ Coax socket for car aerial.
- ★ Brand new guaranteed components.
- ★ Push pull output.
- ★ Automatic volume control.
- ★ Long life battery.
- ★ Super sensitive internal ferrite rod aerial.
- ★ Nothing more to buy. Cabinet included.

Special inclusive price for £7.19.6 all required components.

Plus 3/6 P. & P. 4/- Alignment service available. Full assembly details and individually priced parts list, all of which are available separately, price 1/6, post free.

The "HIGHWAYMAN"

At last a quality Car Radio to build yourself, at an economical price. Look at these features—

- ★ Attractive styling.
- ★ Push-pull output.
- ★ 3 latest Mullard transistors plus valves type EBF 83 and ECH 83.
- ★ No Buzz, High Output and sensitivity.
- ★ Printed circuit (newest type).
- ★ 7" x 4" High flux p.m. speaker.
- ★ Medium and Long Waves.
- ★ Push Buttons for fingertip control.
- ★ Extremely low Battery consumption (less than 4 amp).
- ★ Easy to fit any make car (Positive earth only).
- ★ 12 volt operation.
- ★ Compact size measures only 7" x 7" x 2" deep.
- ★ Easy assembly.
- ★ Supplied with dial and drive already mounted.




All parts available separately but if purchased at one time, the whole will be supplied at a special inclusive price of only

£10.19.6

Plus 4/- P. & P.

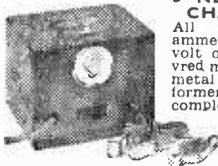Parts list and comprehensive instruction booklet 2/6, post free. (Deduct from cost if complete parcel purchased later.)



2 1/2 amp, 4 1/2 amp, 50/- each plus 2/6 P. & P. Also available 2 amp charger kit complete, no ammeter, fully shrouded mains transformer. Full instructions 30/-, plus 2/- P. & P.

3 NEW BATTERY CHARGER KITS

All complete with ammeter! For 6 and 12 volt operation. Louvred metal case, fuses, metal rectifier, transformer, absolutely complete including heavy duty crocodileclips.

Full instructions provided. 1 1/2 amp, 35/- P. & P. 2 1/2 amp, 50/- P. & P. 50/- each plus 2/6 P. & P. Also available 2 amp charger kit complete, no ammeter, fully shrouded mains transformer. Full instructions 30/-, plus 2/- P. & P.

NEW BRANCH now open in MANCHESTER

at 10 WITTHY GROVE

OPEN ALL DAY SATURDAY

MODEL 500

30,000 ohms per volt Multimeter! 9 ranges D.C. voltage to 1 kV. 7 ranges A.C. voltage to 1 kV. 5 ranges D.C. current to 12 amp. 3 ranges resistance to 60 Meg. Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. Output capacity -20 +5%. Size 3 5/16 x 6.5/16 x 2 1/2 in. Outstanding Value at £8.19.6. H.P. available.



NEW IMPORT! Large quantity shipments enable us to offer keenest meter value yet! 20,000 ohms per volt

MODEL 101-2

Volt-ohm-Milliammeter



Ranges: A.C. Voltage: 10, 50, 100, 500, and 1000 volts (100,000 ohms per volt). D.C. Voltage: 5-25, 50, 250, 500, and 2.5k. (20,000 ohms per volt). D.C. Current: 0-50 microamps, 0-2.5 mA, 0-250 mA. Resistance: 0-6k, 0-6 meg. (300 ohm and 30k at centre scale). Capacity: 10 pF to .001 mfd., .001 mfd. to 1 mfd. Decibels: -20 to +22 dB.

A fully guaranteed pocket size meter (actual size: 4 1/2 x 3 1/2 x 1 1/2) knife edge pointer, top quality supplied complete with test leads and full operating instructions. ONLY £5.5.0 FREE

Also Available! MODEL TE10. Identical in appearance and size with rotary type switch but 10,000 ohms per volt. Voltage: 0-5-30-120-600-1200 volts (10,000 ohms per volt). A.C. voltage: 0-5-30-120-600-1200 volts (10,000 ohms per volt). D.C. Current: 0-120 microamp, 0-3-300 mA. Resistance: 0-30k, 0-3 Meg. (150 ohm and 15k at centre scale.) Capacity: 50 pF to 0.01 mfd., 0.001 mfd., to 0.15 mfd. Decibels: -20 to +63 dB in 5 ranges. ONLY 89/6 POST FREE

Optional Extra. Attractive carrying case suitable for either meter, 13/6 only. (Bona fide trade enquiries invited.) Leaflet available.

THE NEW "CLYMAX"!!



Our new 6-transistor pocket size superhet for Medium and Long Wave at a price you can afford. All required components

NOW ONLY £5.19.6

Nothing more to buy!

Plus 3/6 P. & P. Completely self contained. No external aerial or earth required. ★ Full medium wave coverage, plus switched Light Programme on Long Wave. ★ Push-pull output—250 milliwatts. ★ Matched set of latest type Mullard transistors. ★ Genuine 2 1/2 in. P.M. Speaker. ★ New high-Q Coils. ★ Ferrite rod aerial with high selectivity. ★ Size: 5 1/2 x 3 1/2 x 1 1/2 in. Two-tone cabinet. ★ Precision etched printed circuit with components references clearly marked. Alignment service available. All parts available separately. Full assembly instructions and individually priced parts list. 2/- post free.

MODEL TK.20A



Size 3 1/2 x 2 1/2 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1000 o.p.v. on both A.C. and D.C. volts. 0/15, 0/150, 0/1000 volts. D.C. Current, 0/150 mA. Resistance, 0/100 k. Complete with test probe, battery and full instructions. OUTSTANDING VALUE at 42/- Plus 1/6 P. & P.

The "COURTESAN"

Our New 3 transistor plus 2 diode pocket receiver with full Medium and Long Wave Coverage.



- ★ No external aerial and earth required.
- ★ Latest 2 1/2" - 75 ohm speaker.
- ★ First grade Mullard transistors.
- ★ Condenser tuning.
- ★ Volume control with on/off switch.
- ★ Easy assembly on pre-tagged circuit board.
- ★ Attractive red polystyrene cabinet measures 5 1/2 x 3 1/2 x 1 1/2" chrome handle, attractive gold and black dial.
- ★ Luxemborg, Hilversum, etc., guaranteed in reception areas.

ONLY 63/- plus 2/6 P. & P.





All parts available separately, itemised parts list and full assembly instructions 1/6, post free.

"FAMILY FOUR"

Our supersensitive T.R.F. Receiver for home construction. Covers Long and Medium Wave bands, is housed in very smart plastic table cabinet in Brown or Black, 3 valve plus contact cooled rectifier. For A.C. mains 200/250 v. Comprehensive assembly instructions provided including practical and theoretical diagrams, which are easy to follow and will enable you to complete this receiver which will be the envy of your friends. ALL NECESSARY COMPONENTS ARE BEING OFFERED FOR LIMITED PERIOD ONLY at the REMARKABLE PRICE of ONLY 79/6, plus 2/6 P. & P. Instruction book available separately if you wish to study before purchase at 1/6 post free.



Just a few of our BARGAINS

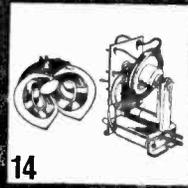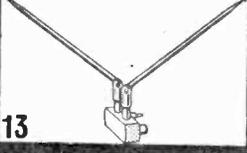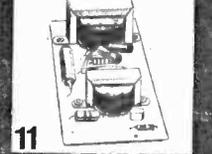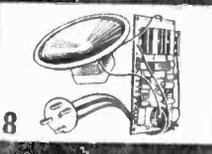

**RADIO & T.V.
COMPONENTS
[ACTON]
LIMITED**

- SUPER 5 TRANSISTOR POCKET RADIO INCORPORATING PRINTED CIRCUIT & MINI-EARPIECE.** No Aerial or Earth required. $4\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ in. Output 200 M.V. 5 first quality transistors. High flux moving coil speaker. M/L Internal high gain ferrox aerial. £2.19.6. P. & P. 3/6. Circuit diagram 1/6, free with parts. All parts available separately.
- TRANSISTORISED POCKET RADIO** with printed circuit, mini-earpiece, high gain ferrox slab aerial. No aerial or earth required. To build yourself for completely personal listening. $4\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ in. Luxembourg in favourable areas. Only 21/- P. & P. 2/6. All parts available separately.
- A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter, scale, calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-30, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms ranges 0-10,000, 0-100,000, 24/6. P. & P. 2/- Wiring diagrams 1/-, free with parts.
- SIGNAL GENERATORS.** Cash £7.5.0, or 30/- deposit and 6 monthly payments of £1/6. P. & P. 5/6. Coverage 100 kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case $10 \times 6\frac{1}{2} \times 5\frac{1}{2}$ in. Three miniature valves and Metal Rectifier. A.C. mains 200/230 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy ± 2 per cent.
- SIGNAL GENERATORS.** Cash £5.5.0. P. & P. 5/6. Coverage 120 kc/s to 34 Mc/s. Case $10 \times 6\frac{1}{2} \times 5\frac{1}{2}$ in. Size of scale $6\frac{1}{2} \times 3\frac{1}{2}$ in. 2 valves and rectifier. A.C. mains 230/250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ± 2 per cent.
- STAAR 45. 9 v. BATTERY RECORD PLAYER** complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on/off switch governed motor, attractive two tone grey finish, £2.14.6. P. & P. 2/-.
- CARRYING CASE FOR STAAR 45 or COMPLETE KIT** beautifully styled in two tone with record compartment. Specially designed to take player and amplifier. Just screw in and connect up. All parts available separately. Case only £2/6. P. & P. 4/- Complete kit £5.10.0. P. & P. 5/6.
- TRANSISTORISED AMPLIFIER,** suitable STAAR 45. Output 1 watt. Size $4\frac{1}{2} \times 2\frac{1}{2}$ in. Printed circuit, tone/volume controls plus 4 transistors. Push-pull output complete with 3in. moving coil speaker. Built and tested, 49/6. P. & P. 2/-.
- CHANNEL TUNER I.F.** 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCP80 and PCC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/- P. & P. 3/-.
- B.S.R. MONARCH UAS WITH PUL-FI HEAD,** 4-speed, plays 10 records, 12in., 10in. or 7in. at 18, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: $12\frac{1}{2} \times 10\frac{1}{2}$ in. Space required above baseboard 4in. below baseboard 2in. Fitted with Pul-FI turnover crystal head, £8.19.6. P. & P. 5/6.
- PUSH-PULL OUTPUT STAGE** inclusive of transistors with input and output transformers to match 3 ohm speech coil, suitable for use with the POCKET RADIO. Kit of parts, including transistors, 19/6. P. & P. 2/- Wiring diagram 1/6, free with parts.
- 8-watt PUSH-PULL 4 VALVE AMPLIFIER plus METAL RECTIFIER.** A.C. mains 200-250 v. Size $10\frac{1}{2} \times 6\frac{1}{2} \times 2\frac{1}{2}$ in. 5 valves. For use with all makes of types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s, 2 db down to 20 kc. Output 8 watts at 5 per cent total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, £3.19.6. P. & P. 6/- Crystal mike to suit, 15/- P. & P. 2/- 8in. P.M. Speaker to suit, 12/6. P. & P. 2/-.
- INDOOR AERIAL for ITV/BBC/FM.** Complete with standard co-axial plug. Heavy chrome extending dipoles—7ft. fully extended. Plugs straight into T.V. or VHF Tuner. Fully directional, 10/6. P. & P. 1/6.
- LINE E.H.T. TRANSFORMERS.** Built-in the width control. 14 kv. Scan coil 90in. Deflection on ferrite yokes. Frame O.P. transformer pl. 15 kv smoothing condenser, suitable for 14in., 17in. or 21in. tubes. With circuit diagram, 29/6. P. & P. 4/6. Suitable Focus Magnet (state tube) 10/- P. & P. 3/-.

**21b HIGH STREET
ACTON, LONDON, W.3.**
ALL ENQUIRIES S.A.E.
GOODS NOT DESPATCHED OUTSIDE U.K.

CABINET HANDBOOK

By G. A. Briggs

Price only **7/6** (8/6 Post free)

112 pages
90 illustrations
Fine art paper
Stiff back



In addition to practical advice on woodworking, veneering, polishing, mesh fittings, etc., this book contains designs for 16 cabinets and baffles, with special attention to compact enclosures, polystyrene diaphragms and also acoustic principles in general.

Other books by G. A. Briggs

- AUDIO BIOGRAPHIES**
With contributions by 64 collaborators.
344 pages, 112 illustrations, 19/6 (20/9 post free).
- A to Z in AUDIO**
224 pages, 160 illustrations, 15/6 (16/6 post free).
- STEREO HANDBOOK**
146 pages, 88 illustrations, 10/6 (11/6 post free).
- LOUDSPEAKERS 5th Ed.**
336 pages, 230 illustrations, 19/6 (20/9 post free).
- SOUND PRODUCTION 3rd Ed.**
368 pages, 315 illustrations, 17/6 (18/9 post free).
- PIANOS, PIANISTS & SONICS**
190 pages, 102 illustrations, 10/6 (11/6 post free).

The above books are sold by many radio dealers and bookshops. In case of difficulty direct from



IDLE, BRADFORD, YORKSHIRE
Tel. Idle 1235/6
Grams 'Wharfedale' Idle, Bradford

MODEL 7 £11.0.0. AVO METERS MODEL 7 Mark II.
Guaranteed perfect. With leads and batteries. Registered P. & P. 5/- extra. Solid leather carrying case £1 extra.

AVO WIDE RANGE SIGNAL GENERATORS. Six turret operated ranges covering 50 Kc/s to 80 Mc/s. For use on standard A.C. mains. In original transit cases with accessories. Post-war type in new condition. £15. Carriage 10/-.
SILICON RECTIFIERS. Type 1E.22 (4 x 1in.) will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier. 7/6.

H.R.O. RECEIVERS—SENIOR MODEL M.X. Complete with 9 coils from 50 Kc/s—30 Mc/s. A superb communications receiver. Guaranteed in brand new condition. £25, cart. 30/-. **POWER UNIT 59/6**, extra cart. 5/6.

AVO L, C & R BRIDGE. Capacity 5 pfd. to 50 mfd. Resistance 5 Ω to 50 M Ω. Inductance can be measured against external standard. Balance is indicated on a meter which can be used as a valve voltmeter from 0.1 to 15 v. Leakage test and Power Factor scale. A.C. mains operation. Tested and guaranteed and in superlative condition. £9.10.0, plus 5/- P. & P.

PCR COMMUNICATIONS RECEIVER
Type PCR. Has self-contained speaker. Covers 850-2000, 200-500 and 16-50 metres. AS NEW CONDITION. £6.19.6
Type PCR-2. Requires external speaker. Covers 850-2000, 200-500 and 13-50 metres. £5.19.6
USED (Good condition) £5.19.6
Carriage (any type) 10/6. Full details S.A.E. Any model fitted with BRAND NEW INTERNAL POWER SUPPLY, guaranteed ready for use on A.C. mains. £2 extra.

Moving Coil Phones. Finest quality Canadian, with Chamois ear muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable. 19/6, post 1/6.

FERRANTI TESTMETER TYPE Q. An extremely compact self-contained multi-meter. Volts 0 to 15, 30, 150, 600 AC/DC, with additional 3 v. DC and 15 v. AC ranges: milliamps 0 to 7.5, 30, 150 and 750 DC; ohms 0-25 K Ω. Accuracy BSS first grade. Knife-edge pointer and clearly calibrated 2 1/2 in. scale. 500 Ω/volt. With leads, prods, battery and instructions. In fitted velvet-lined 4 x 7 x 3 in. case. Brand new condition, tested. 39/6, P.P. 2/6.

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martins Lane
London, W.C.2. TEMPLE BAR 0545
Shop Hours 9-6 p.m. (9-1 p.m. Thursday) Open all day Saturday.

PADGETTS RADIO STORES

OLD TOWN HALL, KNOWLER HILL,
LIVERSEDGE, YORKS.
Phone: Cleckheaton 2866.

Type 46. RX-TX. Complete with two ARP12, one AR8, one ARTP2, one APT4, one APP37, less crystals, coils and send-receive switch, but otherwise complete. These sets are in new condition, 8/6. Post 3/6. Grade two store soiled, 4/6. Post 3/9.

Bomb Computers in new condition. Full of gears, motors etc. 30/-. Carr. B.R.S. 10/-.

P.M. Speakers, all 3 ohms. Removed from TV sets, perfect condition. Rola 6 x 4in., 5/-. Goodmans 7 x 4in., 6/-. Philips 5in. round, 5/-. Rola R and A round, 3/6. 6in. dish, 5/-. 8in. round, 6/-. Post extra on any speaker 2/-. Up to six can be sent for 3/6.

Germanium Diodes. 4/6 per doz. Post free.

New Boxed Valves. Post free. ARP12, 1/6. 6 for 5/6. Box of 50, 20/-, X41, 4/-, 6KT7, 2/-, 6L6 Metal 7/-, 6V6GT 5/-, VR150/30 3/6, 6C4 2/-, 9001 9d., 5/- doz. 6V5 3/-, EL91 1/6. Also new valves ex-units. EF91 1/9, EB91 1/9, 5Z4 5/6, 6X5 4/6, 12A8 Metal 2/6, 5U4 4/6, 6J6 2/6, 307USA 5/-, 6V8 3/-, 6V6GT 4/-, AC/2 per 4/-, 12AT7 2/6, EF50 6/- per doz., 1/9 each. 6F6 2/6.

Valves removed from TV sets. all post free, all tested on a Mullard valve tester and are 100% as new. They carry a three months Guarantee. We also have a large stock of old type radio valves and other TV valves not listed.

ECL80 4/-, ECC82 5/-, EL38 4/-, EY51 2/6, EF89 4/6, EB91 9d., EP91 9d., 6F11, 6F13, 6F13, 6F14 5/-, 7LD2 5/-, 6SN7 2/9, 6Y6 2/6, 6Z6 2/6, 6SS7 2/-, 10C2 5/-, 10F1 1/1-, 10P13 5/-, 10P14 5/-, 20D1 3/-, 20P1 5/-, 20L1 5/-, 18B8T 3/6, U281 5/-, U282 5/-, U801 8/6, C939 5/-, K736 5/-, PL81 5/-, PL92 5/-, PY81 4/-, F782 5/-, F789 5/-, F230 4/-, FCF90 4/6, PCC94 4/6, PL33 5/-, PL33 4/-, B36 4/-, N37 5/-, L63 3/-, 6J5 3/-, 275U 5/-, U12 4/-, EF80 1/6, 10/- per doz. Grade 2 6d., 4/- per doz.

Perfect Reclaimed Tubes. 6 months guarantee, 12in., 17/-, 14in., 30/-, Carr. and Ins., 7/6.

TV Tubes Completely Rebuilt and refaced. 12 months guarantee. Old glass not required. 12, 14, 15, 16, 17in., any make. All the special trade price of £3.15.0. Carr. and Ins., 7/6.

Complete TV Chassis for Spares. Less valves. 12in. four for 10/-, Carr. B.R.S. 7/6. 14in. chassis, four for 15/-, Carr. 8/6. 12in. and 14in. chassis. Your choice with scan coils. Less valves. Untested. 10/- each. Carr. 7/-.

SAVOY TRANSISTOR RADIOS

with Miniature Loudspeaker
No drilling. No soldering. Simple to construct. Can be done by anyone. Full medium wave band coverage.

SAVOY MINI-5
5 transistors. Size: 4 1/2 x 2 1/2 x 1 1/2 in. **57/-**
Battery 1/-.
P. & P. 2/- extra.

SAVOY 3 with 3 transistors and 2 diodes. Size: 4 1/2 x 2 1/2 x 1 1/2 in. Battery 1/- **47/-**
P. & P. 2/- extra.

SAVOY SUPER 4
Moving coil loudspeaker with 4 transistors and 2 diodes. **75/-**
Size: 5 1/2 x 3 x 1 1/2 in.
Battery 2/3. P. & P. 2/9 extra.

SAVOY ELECTRONICS LTD.
15 Maiden Lane, Strand, London, WC2
(TEM 5484)
CALLERS WELCOME

BBC - ITV - F.M. AERIALS

B.C. (BAND 1). Telescope loft, 19/6. External. S/D, 28/3.

I.T.V. (BAND 3). 3 Element loft array. 24/-. 5 Element. 32/6. Wall mounting. 3 Element. 33/9. 5 Element. 41/3.

COMBINED B.R.C. + I.T.V. Loft 1+3 Element. 41/3. 1+5 Element. 48/9. Wall mounting. 1+3 Element. 56/3. 1+5 Element. 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H". 28/-. 3 Element loft. 52/6. S/D loft. 12/6. External S/D. 28/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable. 8d. yd. Coaxial plugs. 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.)
3B, Godstone Road, Kenley, Surrey.



TRANSISTOR SET CASE. 11½ x 8 x 3in. with carrying handle finished in two-tone grey with gold trim, price 22/6. Set of suitable knobs, 5/- extra.
LEATHERCLOTH COVERED RECORD PLAYER CASE, suitable for single player unit, etc. Size 14½ x 13 x 6½in., supplied with uncut motorboard, carrying handle, gold trim, available in red/grey and two-tone grey. Price 44/-.

LEATHER CLOTH CASE, as above but suitable for automatic record player, size 1½ x 14½ x 8½in., available in blue/grey, red/grey, price 56/-.
 Uncut motorboard.

Case as above, base size 15½ x 15 x 8½in., tapered front motorboard cut out for UA14, available lemon/black, price 63/-.

Miniature Jack plug and socket 2/6 set.
 Miniature Slide Switch 2 pole change over 2/6.
 Transformers LT.44/700 Driver and Output 8/- pair.
 Top Quality co-axial Cable semi airspaced 6d. yard.
 All Co-Axial Accessories available from stock.

PERSONAL EARPHONE

A really sensitive dynamic earphone of exceptionally fine quality. Provides clear reproduction of music as well as speech. Fully guaranteed and complete with ear insert, 3 feet cord, sub miniature plug and socket.
Model CR5 Crystal Earpiece high amp. **Model MR-4.** Magnetic earpiece low amp., 6/- each.

"PRACTICAL WIRELESS" POCKET TRANSISTOR SUPERHET



The new version in a redesigned cabinet with carrying strap.

COMPONENTS PRICE LIST

Coil Set, (Osc. and 3 I.F.s)	22/-
Driver Transformer, Type PW/DT	8/3
Output Transformer, Type PW/OT	8/-
Ferrite Rod Aerial, Type PW/FR	8/6
Printed Circuit Board	7/6
2 Gang Capacitor, Type "OO"	12/6
Volume Control, Type V.C.1545	8/-
Switch	3/6
Hardware (Screws, nuts, washers, spacers, battery clips, cable cradles, cable studs, cable strapping)	4/-
Transistors, Type YC (Set of 6)	43/-
Xtal Diode, Type GD9	17/10
Speaker	12/6
Case	15/-
Capacitors	5/-
Resistors	3/9
Trimmers, Type MT31/4A (3 required)	

CONSTRUCTION LEAFLET AND "BLOW-UP" CIRCUIT DIAGRAM. PRICE FOR THE COMPLETE KIT £7.19.6.

LOUDSPEAKER CABINETS

Baffle type, walnut finish:—
 Type suitable for an 8" unit Price 21/-
 Type suitable for a 10" unit Price 25/6
 Type suitable for a 7" x 4" unit Price 17/6

AUTOMATIC RECORD CHANGERS

BSR UA14	£6.19.6
COLLARO C60	£7.19.6
GARRARD AUTOSLIM	£7.19.6

SINGLE PLAYERS

EMT. 4 Speed with pick-up	£3.15.0
BSR EU6	£4.19.6
GARRARD TA MK11	£8.10.0
EMI BATTERY VERSION	£5.9.6

J.B. SD/2 GANG CONDENSER


Sub Min. Solid Dielectric Size 2" square x 7/16" deep. Cap 192pF Aerial 78pF osc. TRIMMERS FITTED 17/6 each.

J.B. DILEMIN CONDENSER

Solid Dielectric available in 300pF or 500pF, 7/6 each.
 Send for our Price Lists on Mini Amp Tutor, etc. etc.

Our new 1962/63 48-page catalogue, profusely illustrated, is now available. Please send 1/- in stamps for your copy. Trade Catalogue also available for which please attach your Business Letter Heading.

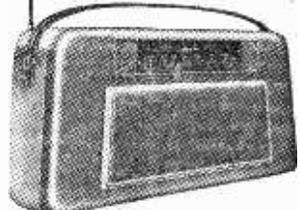"MERCURY SIX" Components Price List for the Printed Circuit Version



COIL SET (OSC. and 3 I.F.s)	22/-
DRIVER TRANSFORMER. Type PW/DT	8/3
OUTPUT TRANSFORMER. Type PW/OT	8/-
FERRITE ROD AERIAL. Type PW/FR	8/6
2-GANG CAPACITOR. Type "OO"	12/6
VOLUME CONTROL, EGEN 10K. S/P SWITCH	6/6
SWITCH	3/6
TRANSISTOR Type Y.C. (set of six)	43/-
XTAL DIODE Type GD9	
SPEAKER	22/5
CASE complete with handle, front grille, studs	25/-
CAPACITORS	17/6
RESISTORS	5/-
TRIMMERS, Type MT.31/4A, 1/3 ea.	3/9
PRINTED CIRCUIT BOARD	14/6
COMPLETE DIAL ASSEMBLY (BOXED)	14/6
HARDWARE (Screws, Nuts, Washers, Spacers, Battery Clips, Aerial Cradle)	5/9
Postage and Packing	2/6
INSTRUCTION HANDBOOK	2/6

TRANSISTORS AND DIODES

Transistors	OC75 8/-	OCP71 25/-	OA73 3/-	GECS1	
OC35 18/-	OC77 12/-	Matched Prs.	OA79 3/9	Audio	3/6
OC36 21/6	OC78 8/-	2xOC72 16/-	OA81 2/6	Red	
OC44 6/-	OC81 8/-	2xOC78 16/-	OA85 3/-	Spot	3/6
OC45 6/-	OC84 8/6	Diodes	OA91 3/-	White	
OC70 6/6	OC170 9/6	OAS 6/-	OA95 3/6	Spot	5/-
OC71 5/-	OC171 10/6	OA10 8/-	PUNdry Types	GEX34 3/-	
OC72 8/-	OC201 31/-	OA70 3/-	XA102 4/-	GEX35 3/-	
OC73 16/-	OC202 26/-			XD201 1/-	

A set of Transistors comprising 1 OC44, 2 OC45, 1 OC81D, 2 OC81, 32/6 set. Set of Audio Transistors, 1 x OC81, 2 x OC81, Driver Matched Pair, 15/6 set.


TERMS: Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d., Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

ALPHA RADIO SUPPLY CO.



103 LEEDS TERRACE
 WINTOUN STREET
 LEEDS 7

TRANSISTOR PORTABLE SIGNAL GENERATOR

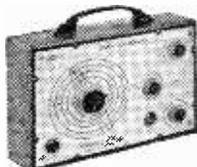

PRICE
£7.10.0
P.P. 2/6

A 1st class Signal Generator covering 200 Kc/s to 200 Mc/s in 8 ranges. Radio broadcasts and I.F., Amateur, VHF, Shipping, TV, etc. R.F., I.F., A.F., modulated R.F. outputs. Easy to read and use with full details. Within 2% accuracy. Size 6½ x 4½ x 2in.

12 MONTHS' GUARANTEE
Leaflet on request

TAPE HEAD

Miniature ½ Track Record/Playback Head with Mounting Block. 850 ohm.

12/6, P.P. 9d.

TAPE RECORDER MOTOR

Miniature Motor designed for Battery Recorders, 4½ to 9 volts. Built in governor, 12/6.

P.P. 1/-.

"TRANSFIVE" PORTABLE RADIO




Medium and Long Wave Portable
8½ x 6½ x 3½in.
£5.19.6
P.P. 2/6

A simple to build 5-Transistor and Diode. Printed Circuit, Medium and Long Wave Portable. Features 5in. speaker, Car aerial socket. 1st grade transistors and ceramic components. Building plans free on request. **THE IDEAL PORTABLE.** Full after sales service and guarantee. (See Back Cover for other types.)

VERNIER DIAL

New Miniature Slow Motion Vernier Dial, 8 to 1 reduction. Marked 0/100 Ideal for all test equipment, 14/-.

3/4 WATT 4 TRANSISTOR AMPLIFIER

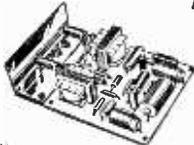

● 1 watt peak output.
± 3db 70c/s to 12 kc/s.
Output to 3 ohm speaker

Built and Tested Kit of Parts
59/6 OR 52/6
P.P. 1/6 P.P. 1/6

9 volt operated.
Details on request.

A printed circuit high gain amplifier size 4 x 2½ x 3in. using Mullard OC71/OC81D and 2-OC81 Transistors. Ideal for Intercomm., Record Player, Tuner Amplifier or any application requiring a quality and reliable amplifier. Suitable large magnet 5-inch speaker, 15/-.

CATALOGUE

New Edition Now Ready. Three times the size, full of components and items. Send 1/- stamp for your copy.

GUITAR CONTACT MICROPHONE. High Impedance Guitar Contact Microphone with screened lead. Plugs into any valve amplifier. Very sensitive. 12/6. P.P. 9d.

TEST LEAD KIT

Complete set of test leads. Suitable for most instruments. Complete with pouch, 8/6. P.P. 1/-.

POCKET RADIO BOOSTER

Tubular unit, size 9½ x 3½in. dia., which plugs into earphone socket of any transistor radio. Performance increase is fantastic. Ideal for home or car. 52/6. P.P. 1/6.

PERSONAL EARPHONES

★ 600 ohm. 10/6 ★ Crystal 9/6
★ 1,000 ohm. 12/6 ★ 8/10 ohm. 9/6
Fitted leads, Jack Plug and Socket.

SOLDERING IRON

Antex miniature 15 watt 220/250 volt iron. Easily removed ¾in. bit. Ideal for all miniature work, 29/6. Spare bits, five sizes to ¼in., 3/- each.

CRYSTAL MIC. INSERTS
ACOS 2in. 10/6
ACOS 1½in. 7/6
2in. sq. 3/6

TYPE 38, TRANSMITTER RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee but are serviceable. 7.4 to 9 Mc/s. P.P. 2/6
Headphones 7/6 pair. Junction Box 2/6.
Throat Mike 4/6. Aerial Rod 2/6.

TELEPHONE ADAPTOR

★ Ideal for recording or amplifying telephone conversations. Supplied with screened cable. Fitted rubber sucker, 14/-.

MARCONI 19 SET CRYSTAL CONTROLLED CALIBRATOR

Crystal controlled oscillators giving either 10 kc/s, 100 kc/s or 1 Mc/s pips. Features neon modulator, supplied with spare valves and full handbook. 79/6 P.P. 2/-

Ideal standard frequency check.

TRANSISTOR PORTABLE TAPE RECORDER

★ New 4-Transistor Version ★

● Play/record up to 30 min.
● Built-in speaker, volume control, batteries and play/record/rewind.
● Quality reproduction.
● Sturdy case 6 x 8½ x 2½in.
£9.19.6
P.P. 3/6




Fully Guaranteed

Supplied complete with microphone, tape, batteries and personal phone (for monitoring), and full instructions. New 4-transistor version with push-pull output, better quality, more attractive case, etc.

The Above are FULLY ASSEMBLED TESTED and GUARANTEED.

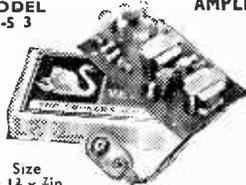4 TRANSISTOR PUSH-PULL AUDIO MODEL PK-5 3 AMPLIFIER



Size
3 x 12 x ½in.

A ready built miniature 250mW push-pull amplifier incorporating input and output transformers, 4 transistors, 9 volt battery snap cord, speaker and column connection leads. Ideal for use with record players, intercoms, hearing aids, tape recorders, etc. Complete with full instructions and circuit diagram.

PRICE **52/6** P.P. 1/6
SUITABLE 2½in. SPEAKER 16/6.

BATTERY RECORD PLAYER



● 6-7½ volt Garrard turntable with crystal pick-up. Plays 45 r.p.m. Ideal for above amplifier.

55/- P.P. 1/6.

● Suitable cabinet for amplifier and player, 17/6. P.P. 2/-.

LIGHTWEIGHT HEADPHONES



★ 2000 OHMS
12/6

★ 4000 OHMS
14/6

HIGH EFFICIENCY.

MINIATURE CLEAR FACED Brand New PANEL METERS

0-50 microamp DC 39/6
0-500 " DC 32/6
0-1 milliamp DC 27/6
0-5 " DC 27/6
0-300 volts DC 27/6
"S" meter 1mA 35/-
"VU" meter 42/6

CRYSTAL MICROPHONES

ACOS 39-1. Stick Microphone with screened cable and stand (list 5 gns.), 32/6. P.P. 1/6.
ACOS 40. Desk Microphone with screened cable and built-in stand (list 50/-), 15/-, P.P. 1/6.
ACOS 45. Hand Microphone with screened lead, very sensitive, 25/-, P.P. 1/6.
100 C. Stick Microphone with muting switch and screened cable, detachable desk stand, cord and neck, 39/6. P.P. 1/6.
MC 24. Stick Microphone with muting switch and cable, 25/-, P.P. 1/6.
LAPEL. Miniature Mic. With clip. Ideal for recording, 15/-, P.P. 1/6.
BM 3. De Luxe Stick Mic., with muting switch cable, neckcord and detachable stand. Complete 52/6. P.P. 2/-.
(Illustrations of all types in our New Catalogue. 1/- post free).

Henry's Radio Ltd

PADDINGTON 1008/9
5 HARROW ROAD, LONDON W2
Open Monday to Sat. 9-6, Thurs. 1 o'clock

PLEASE TURN TO BACK PAGE

★ VALVES ★

by return of post

THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in doses). Post: 1 valve, 6d., 2-11, 1/-.	NEW LOW PRICES GUARANTEED 3 MONTHS	FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-corporation origin. Satisfaction or Money back Guarantee on Goods if returned unused within 14 days.
--	---	---

OZ4	6/-	6J6GT	4/-	12K8GT	9/6	DET19	2/0	EL91	4/-	R19	11/-
1A50T	6/-	6J6	4/-	12Q7GT	5/-	DF39	9/0	EM80	7/9	SP41	2/6
1A70T	11/6	6J7	6/8	12S4T	7/-	DF81	3/6	EM81	8/8	SP61	2/6
1C6GT	9/-	6J7G	4/0	12S7	7/6	DF86	7/6	EM84	8/-	SU25	16/-
1D5	8/-	6J7GT	7/6	12H7	3/6	DF97	8/6	EM85	7/-	SU215	4/6
1D6	9/0	6J8	9/0	12J3T	5/6	DH63	6/-	EN51	16/-	T11	7/6
1N6GT	9/0	6K6GT	9/0	12K7	4/0	DH76	5/-	EY35	7/9	TD4	7/6
1L	6/3	6K7	5/0	12N7GT	7/6	DK32	11/-	EY86	7/8	U14	8/-
1L5	9/0	6K7G	8/0	12P1	4/0	DK92	5/0	EZ35	9/6	U22	8/6
1L6S	4/0	6K7GT	4/0	1487	14/0	DK92	5/0	EZ40	6/0	U24	16/-
1N5GT	9/0	6K8GT	9/0	19A5	7/6	DK96	7/8	EZ41	7/0	U25	11/6
1N5	5/0	6K25	7/8	19B6	19/-	DL33	9/0	EZ80	8/0	U26	9/6
184	8/-	6L1	12/0	20D1	9/6	DL35	9/6	EZ81	6/8	U31	7/-
185	4/0	6L6G	6/0	20F2	9/6	DL38	9/6	EZ82	6/0	U33	12/-
1T4	8/6	6L15	9/0	20L1	16/-	DL52	9/0	EW4/800	9/0	U35	15/6
2A3	9/0	6L19	11/-	20P1	8/0	DL52	9/0	FW4/800	8/0	U35	15/6
2A7	9/0	6L1D5	8/0	20P3	12/6	DL91	8/0	GT10	7/-	U37	26/-
3A4	4/0	6L19	9/0	20P4	13/-	DL92	8/0	GZ32	9/0	U50	5/9
3A3	9/0	6L1D80	2/0	20P5	5/0	DL94	6/8	GZ34	12/6	U52	4/9
3D6	4/0	6N7	7/6	25A6G	8/-	DL94	6/8	HL41DD	8/3	U78	5/6
3Q4	7/-	6P1	7/8	25L8G	9/0	EACB30	6/0	HN309	19/0	U91	12/6
3Q5GT	8/-	6P25	8/0	25L6GT	7/6	EACB1	9/0	HN309	19/0	U91	12/6
3E4	6/-	6E28	12/6	25Y6G	3/-	EAF42	8/-	HW4/350	7/6	U282	15/-
3V4	6/0	6Q7G	6/0	25Z4G	7/-	EB41	5/0	IB31	9/0	U301	16/-
3R4GY	12/6	6Q7GT	6/0	25Z5	2/6	EB31	9/0	IB32	9/0	U301	16/-
5T1	4/-	6R7G	6/0	25Z6G	8/-	EBC33	4/9	ICL32	9/0	U329	6/9
5Q4G	4/0	6S4T	5/0	30C1	3/0	EB41	4/0	KT32	6/9	U329	6/9
5V4G	7/0	6S6T	4/9	30P15	11/6	EBK1	7/0	KT33C	4/6	U339	11/-
5Y3G	5/0	6S7	5/0	30P16	9/6	EBF80	7/9	KT36	12/6	U801	19/-
5Y8GT	5/0	6S8K7	5/0	30F11	9/6	EBF89	6/0	KT45	7/6	UABC80	8/0
5Y4G	11/-	6S17GT	5/0	30L1	6/9	EBF89	6/0	KT45	7/6	UABC80	8/0
5Z4	11/-	6S87GT	4/0	30L15	9/6	EBL21	12/6	KF61	8/6	UB41	7/9
5Z4G	7/6	6S9T	5/0	30P14	9/6	EBL31	17/6	KF63	5/0	UBC41	7/9
6Z4GT	11/-	6S9T	3/6	30P12	6/6	EC91	4/8	KF76	8/6	UBC81	9/6
6J0L3	9/0	6G4GT	9/0	30P16	6/6	ECC31	7/8	KW61	5/0	UBF80	5/6
6A6	4/0	6V6G	5/0	30P19	17/6	ECC32	4/0	KW62	5/0	UBF80	5/6
6A7	10/-	6V6GT	6/0	30P11	9/6	ECC33	4/6	KW63	5/0	UBF81	14/6
6A8G	8/6	6X2	7/0	30P113	13/-	ECC34	9/-	KZ268	5/6	UCC84	14/6
6ASGT	13/6	6X4	6/-	35Z4G	8/6	ECC35	6/-	L83	2/6	UCC85	7/6
6AB9	7/-	6X6G	5/0	35T	25/-	ECC40	14/-	LI82	6/0	UC80	15/-
6AC7	8/6	6X6GT	5/0	35W4	6/0	ECC81	5/6	M114	7/6	UC80	15/-
6AG5	3/-	6Y6G	8/6	35Z4GT	8/6	ECC82	6/-	N37	11/-	UC42	7/3
3A17	7/6	7A7	8/6	35Z6GT	8/6	ECC83	6/6	N78	15/-	UC181	8/0
6AK5	8/-	7B7	8/6	35Z6GT	8/6	ECC84	6/6	N108	16/-	UC192	9/0
6AL5	8/-	7BT	8/6	35Z6GT	8/6	ECC85	7/9	N152	8/6	UC198	13/6
6AM8	3/-	7C5	7/3	30C5	3/0	ECC89	16/-	P41	4/0	UF41	7/6
6AQ5	6/-	7C9	7/6	60C06	19/-	ECC91	4/-	P61	9/0	UF42	6/6
6AT8	6/0	7H7	7/8	60L6GT	10/6	ECCF80	8/0	PAB80	11/6	UF80	7/6
6AU6	7/6	7K7	7/6	7K7	10/6	ECCF81	8/0	PAB80	11/6	UF80	7/6
6B7	6/6	7Q7	8/6	53K	10/6	ECCF82	8/0	PAB80	11/6	UF80	7/6
6B8G	3/-	7R7	10/6	618PT	11/6	ECCF83	8/0	PAB80	11/6	UF80	7/6
6BA6	5/0	7S7	9/0	62B1	13/6	ECCF84	8/0	PAB80	11/6	UF80	7/6
6B8	5/0	7T7	7/9	79	7/6	ECCF85	8/0	PAB80	11/6	UF80	7/6
6S08G	15/-	7Y4	6/9	78	6/6	ECCF86	8/0	PAB80	11/6	UF80	7/6
6S10	6/-	7Z4	7/0	80	5/6	ECCF87	8/0	PAB80	11/6	UF80	7/6
6R3E	6/-	8D3	3/0	83	8/6	ECCF88	8/0	PAB80	11/6	UF80	7/6
6R7	9/6	10C1	11/6	18B7	19/6	ECCF89	8/0	PAB80	11/6	UF80	7/6
6LW6	7/6	10C2	14/6	803	13/6	EF22	7/6	PCL82	7/8	UY1	11/-
6EW7	5/0	10C14	14/6	807(A)	8/6	EF22	7/6	PCL82	7/8	UY1	11/-
6EX6	4/0	10F1	6/0	808	8/6	EF22	7/6	PCL82	7/8	UY1	11/-
6C5	3/0	10P9	10/6	813	55/-	EF39	4/0	PCL34	7/8	UY1	11/-
6C6	5/0	10P18	10/0	832	14/0	EF40	12/-	PCL85	11/8	UY21	11/-
6C8	8/0	10P28	7/0	868A	11/6	EF41	8/-	PCL86	12/6	UY41	6/-
6C9	11/0	10D3	7/0	868A	11/6	EF42	7/6	PCL86	12/6	UY41	6/-
6C0D6	19/6	10L1D11	14/6	958	2/6	EF42	7/6	PCL86	12/6	UY41	6/-
6CH8	7/6	10L1D3	8/-	1265	5/0	EF42	7/6	PCL86	12/6	UY41	6/-
6D9	3/-	10P13	11/0	9001	4/0	EF42	7/6	PCL86	12/6	UY41	6/-
6E1	4/0	10P14	9/0	9002	4/0	EF42	7/6	PCL86	12/6	UY41	6/-
6DE	4/0	10P15	9/0	9003	4/0	EF42	7/6	PCL86	12/6	UY41	6/-
6DF	4/0	12A6	1/0	AZ31	8/0	EF42	7/6	PCL86	12/6	UY41	6/-
6E9G	5/0	12A8	9/0	AZ41	11/0	EF42	7/6	PCL86	12/6	UY41	6/-
6F33	3/-	12A76	7/8	B38	7/6	EF91	8/-	PL84	8/-	X63	8/6
6F15	6/0	12A75	8/0	C13	9/6	EF92	4/6	PL90	8/0	X65	11/-
6F11	9/0	12A76	8/0	C13	9/6	EF92	4/6	PL90	8/0	X66	11/-
6F15	9/0	12A77	6/0	CBL31	8/2	EF93	11/0	PX5	10/6	X73	11/-
6F16	8/-	12AX7	6/0	CC136	14/6	EF94	12/0	PY31	9/-	X78	7/6
6F19	6/0	12BA6	7/8	CL33	9/6	EL32	4/6	PY32	10/-	X79	16/6
6F23	6/0	12BB7	6/0	CY21	9/0	EL33	7/9	PY80	8/0	X81	6/3
6F24	12/-	12BB7	6/0	D77	8/6	EL33	7/9	PY81	6/6	X83	6/3
6F28	18/-	12C8	6/0	D152	8/6	EL41	8/0	PY82	6/0	Z68	8/6
6F28	6/0	12E1	17/6	DA30	12/6	EL42	8/0	PY83	7/0	Z89	8/6
6F33	6/0	12J7GT	9/0	DA32	9/6	EL81	11/-	PY86	9/0	Z152	4/9
6S5	4/8	12K7GT	9/0	DAF81	4/6	EL83	11/-	PZ30	9/0	Z719	4/9
6J5G	3/-	12K85	11/0	DAF86	7/8	EL84	7/-	R18	11/-	ZD132	7/9

Tubes

Carr. & Ins. 12/6

MOST MULLARD MAZDA, COSSOR, EMITRON, EMIS- SCOPE, BRIMAR, PERRIN TYPE, PROCESSED IN OUR OWN FACTORY	HIGHEST QUALITY— COMPARE OUR PRICES		NEW TYPES MW 21/74 £4-0-0 MW 86/24 £5-0-0 CRM 172 MW 43/64 £6-0-0	
	GUARANTEED 6 Months 12 Months			
	12in.	£2. 0.0		£3. 5.0
	14in.	£2.10.0		£3.15.0
	15/17in.	£3. 5.0	£4.10.0	
	21in.	£3.15.0	£5.15.0	

TUBE SNIPS

Due to huge Bulk Special Purchase we are offering MW 81/74 Tubes at the unrepeatable price of 29/-, MW 39/24 ditto, 39/-. P.P. 12/6. The above are guaranteed for 6 months

CO-AX, standard and low loss, 25 yds., 12/6, 50 yds., 22/6; 100 yds., 42/6, Co-ax Plug 1/3. Wall outlet boxes 3/6

4-SPEED RECORD PLAYERS. Latest Turntable, together with lightweight Staal Galaxy dual sapphire crystal turnover pick-up head. Amazing value (pick-up only 18/-). £3.10.0. (arr. 3/-)

P.M. SPEAKERS. 3 ohm, top makes, performance guaranteed. 6in., 8in., 9/-, 5in. 7 x 4in., 11/-.

13 CHANNEL T.V.s.

Table Models, Famous Makes. Absolutely Complete. These sets are unequalled in value due to huge purchase direct from source. They are untested, (our price whilst stocks last, £45/-) order. Carr. etc., 15/-.

12in. £2.19.0 14in. £4.19.0

3 VALVE AMPLIFIERS. Kit of new parts, consisting chassis mains and output transformers, valves (P61, 6X6G, 6XG) and all components. With full instructions for making high gain amplifier with separate base and treble controls, negative feedback, etc. Truly unvalued value at 29/-.

F.M. TUNER KITS. Well known make, comprising F.M. Tuning Head, guaranteed noise drift. Frequency coverage 85-100 Mc/s. OAS1 balanced diode output, Magic Eye Tuning, Two I.F. Stages and discriminator, £28.9.

P.V.C. CONNECTING WIRE. 100 yds. 30 mil. special Price 7/6. 200 yds. 30 mil. special price, 12/6. 25ft. Col. 1/-, 5 Colis different colours, 4/-, Connecting flex. Prices as above.

TRANSISTORS. Red spot 3/6 ea. White Spot 4/6 ea. Yellow Spot 2/8 ea. Germanium diodes 8d. ea., 3/- doz.

TRADE SUPPLIED

CV and industrial valves, receiver valves and components. Quantity quotations for all items advertised plus 10% more. Government depliment 11% and manufacturers supplied.

FRUSTRATED EXPORT ORDER

Amazing Value, Top Quality, Factory Fresh Standard Superhet, plus Magic Eye:-
ECH81 ECH81 All for ONLY 35/- Post Free
EF89 EL44 EM84
Satisfaction Guaranteed. This works out at only 5/10 per valve FM Valve Kits as above plus ECC85 42/- post free.

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/-, etc. No C.O.D. ALL ITEMS LESS 5% and POST FREE IN DOZENS. LIST OF 1000 SNIPS, 6d.
MAIL ORDER only **DEVONIAN COURT,**
PARK CRESCENT PLACE, BRIGHTON 7, SUSSEX

TECHNICAL TRADING CO.
RETAIL SHOP 350-352 FRATTON ROAD, PORTSMOUTH

RUN YOUR RADIO FROM MAINS BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/6, P.P. 1/-.
2. For PP4, PP7, PP9, PP10, 9 volt Portable Radio Batteries up to 300 mA. 45/- P.P., 2/-.
3. De Luxe version of No. 1, also charges PP3 type batteries, 29/6, P.P. 1/-.
4. Rechargeable PP3 battery. Runs as long as 100 batteries. Complete with charger unit. 35/-, P.P. 1/-.



MODEL TH-L33

2,000 ohms per volt AC/DC. Size 5 x 3 1/2 x 1 1/2 in.

75/- Fully Guaranteed with test leads, battery and instructions.

0/10/50/250/500/1000 volts D.C., 0/10/50/250/500/1000 volts A.C., 0/500µA/10/250mA, D.C.

3 ranges resistance 0/10K/100K/1 Meg. Capacity and dB ranges.

MODEL 500

30,000 ohms per volt multi-meter

£8.19.6

Fully Guaranteed



8 Ranges D.C. volts to 1 kV.
7 Ranges A.C. volts to 1 kV.
5 Ranges D.C. current to 12 amps.
3 Range resistance to 60 meg.
Short circuit, Buzz test. Output meter dB, etc., etc. Size 6 1/2 x 4 1/2 x 2 1/2 in. With Leads, Batteries and Instructions.

MODEL TP55

A.C./D.C. voltage up to 1,000 in 5 ranges. D.C. current 4 ranges up to 500mA. 4 range resistance to 10 megs. Capacity dB scales, etc. 20,000 ohms/volt Fully Guaranteed **£5.19.6**

With Test Leads, Battery and Instructions. Size 5 1/2 x 3 1/2 x 1 1/2 in.



AVO-8X PANCLIMATIC

Limited Quantity of these Superb Multi-testers, new conditions and fully guaranteed.

List £30 **£19.10.0** Regd. Post 5/- Inclusive of Batteries, Avo Test Leads and Leather Case. 20,000 ohms per V.

We stock the largest range in the Country of Transistors and Miniature Components for the home constructor. New Catalogue 1/-.

TRANSISTORS

1st GRADE FULLY GUARANTEED

XA101 5/-	XA702 17/6	XC101 6/-
XA102 6/-	XA703 25/-	XC121 6/-
XA103 4/-	Power types	XC131 10/-
XA104 4/-	XC141 10/-	
XB102 4/-	Pairs	(Pairs)
XB112 4/-	12 w 22/6	XC171 10/-
XB113 4/6		XC163 7/-
XB121 8/6	XC156 22/6	XS104 7/6
NPN types	Pairs	XS101 10/-
XA701 9/-	50 w 50/-	

Many Others in Stock.

Complete range of over 400 Transistors and Diodes now available. Latest list on request with equivalents.

SPECIAL—Very Low Prices for Matched Sets from 29/6 to 32/6.

VALVES AND CRYSTALS
NEW CATALOGUE NOW READY
MORE TYPES—LOWER PRICES

GEIGER MULLER TUBES

Mullard Type MX115, 400 volts. Gamma sensitive type. 22/6. P.P. 1/6.

OFFICE, WORKS or HOME USE

COMPLETE INTERCOMM. SYSTEMS

★ 2-transistor transformer coupled, two speakers in moulded cabinets. Features 2-way Buzzer system and talking. Supplied complete with cable **89/6** P.P. 1/6

★ 4-transistor de luxe version, with 2-way calling and talking. Moulded cabinets, long battery life—very sensitive. With cable and **£7.10.0** P.P. 2/-

STEREO PHONES

New stethoscope type stereo earphones with adjustable tubes. Fitted miniature jack plugs and leads. 2 x 8 ohms impedance. 27/6.

STEREO AMPLIFIER

4-Valve Amplifier with 2 watts output per channel to 30 ohms. Ready built, complete with Dials, Sockets and Knobs. Full tone, volume and balance controls. Crystal Input. 220/250 volt mains input. Fully Guaranteed **79/6** P.P. 2/-

PRACTICAL TRANSISTOR CIRCUITS 3/6 (Post Free)

Contains easy to follow plan of 40 all transistor units, including light operated switches, amplifiers, transmitters, receivers, test oscillators, signal tracers, hearing aids, radio control, etc. All parts available separately.

Henry's Radio Ltd

PADDINGTON 1008/9

5 HARROW ROAD, LONDON W2

Open Monday to Sat. 9-6, Thurs. 1 o'clock

PLEASE TURN PAGE—BOTH WAYS!

Send 1/- Stamp for New Triple Size Catalogue



ALL TRANSISTOR BABY OR INVALID ALARM

HOUSED IN ATTRACTIVE GOLD HAMMER FINISH PORTABLE CABINET. Battery operated, push-pull, 400MW output. Low impedance microphone enables unit to be used up to 200 yards. Output on quality speaker. ★ GUARANTEED for 12 MONTHS and 100% SAFE.

★ MICROPHONE is placed within 10ft. of baby; twin flex is taken to amplifier unit and placed in any room required. COMPLETELY BUILT & TESTED. P.P. 2/6. **£5.10.0**

★ Used All Night, Every Night. Battery Life 3 to 4 months.

Also Telephone Amplifier (as previously advertised). **£5.10.0 P.P. 2/6**



MODEL PT34

SIZE: 3 1/2 x 2 1/2 x 1 1/2 in.

1,000 ohms per volt

49/6 Fully Guaranteed

0/10/50/250/500/1000 volts on A.C. and D.C.

0/1/100 mA, 0/500 mA D.C., 0/100K ohm resistance.

Complete with Leads, Battery and Instructions.

MODEL ITI-2 (200H)

20,000 ohms per volt.

£5.5.0

Size 4 1/2 x 3 1/2 x 1 1/2 in. With Test Leads, Battery and Instructions.



6 Ranges D.C. voltage to 2 1/2 kV.
5 Ranges A.C. voltage to 1 kV.
3 Ranges D.C. current to 250 mA. Resistance to 6 meg. Capacity and dB ranges.

AVO-7

Famous Multi-meter, reconditioned and a fully guaranteed. Full A.C./D.C. voltage and current, resistance, dB, power, etc., etc.



Supplied with Batteries, Leads and Instructions. (Normal price £19.10.0)

£11.0.0

Regd. Post 5/-

LEATHER CASES FOR "AVO-7," 25/- extra.

ALL METERS FULLY GUARANTEED for 6 MONTHS

Practical Wireless

—BLUEPRINT—

—SERVICE—

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for the PW Monophonic Electronic Organ and the PW Roadfarer.

The Index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Title	Number	Price	Title	Number	Price
CRYSTAL SETS					
Junior Crystal Set	PW94	2/-	A.C. Fury Four	PW20	2/6
Dual-wave Crystal Diode	PW95	2/6	Experimenter's Short Wave	PW30a	2/6
STRAIGHT SETS					
Battery Operated					
Modern One-valver	PW96	2/6	Midget Short Wave Two	PW38a	2/6
All-dry Three	PW97	3/6	Band-Spread Three (Battery)	PW68	2/6
Modern Two-valver	PW98	3/6	Crystal Receiver	PW71	2/-
SUPERHETS					
A.C. Band-pass Three	PW99	4/-	Signet Two (Battery)	PW76	2/6
A.C. Coronet-4	PW100	4/-	Simple S.W. One-valver	PW88	2/6
A.C. D.C. Coronet	PW101	4/-	Pyramid One-valver	PW93	2/6
The PW Pocket Superhet	—	5/-	<hr/>		
MISCELLANEOUS					
The PW 3-speed Autogram	—	8/-	BBC Special One-valver	AW387	2/6
The PW Monophonic Electronic Organ	—	8/-	A One-Valver for America	AW429	2/6
<i>(No constructional details are available with this blueprint)</i>					
The PW Roadfarer	—	5/-	Short-Wave World Beater	AW436	3/6
<i>(No constructional details are available with this blueprint)</i>					
TELEVISION					
The PT Band III converter	—	1/6	<hr/>		
			Standard Four Valve S.W.	WM383	3/6
			Enthusiast's Power Amplifier	WM387	3/6
			Standard Four Valve	WM391	3/6
			Listener's 5-Watt Amplifier	WM392	3/6

QUERY COUPON

This coupon is available until 7th December, 1962, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, DECEMBER, 1962

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, London, W.C.2 printed in England by WATMOUGHS LIMITED, Idle, Bradford; and London. Sole Agents for Australia and New Zealand: GORD GOTCH (A/asia), Ltd., South Africa and Rhodesia; CENTRAL NEWS AGENCY, LTD. East Africa; EAST AFRICAN STANDARD Subscription rate including postage for one year: Inland £1.9.0. Abroad £1.7.6 (Canada £1.5.0.). Registered at the General Post for the Canadian Magazine Post.

PROVE IT YOURSELF! SEE HOW EASY IT IS TO BUILD ONE OF OUR DESIGNS

● **FULL DETAILS OF ANY MODEL ON REQUEST—WRITE NOW** ●

THE FABULOUS "CONTESSA" Mk. III combined portable and car radio

- WITH 600mW MELLOWTONE OUTPUT ON MEDIUM AND LONG WAVES.
- FITTED HORIZONTAL TUNING SCALE
- WITH ALL STATIONS CLEARLY MARKED
- SUPPLIED WITH SIX MULLARD TRANSISTORS AND TWO DIODES
- FITTED RECORDING SOCKET AND CAR AERIAL SOCKET
- SUPPLIED WITH TWO-TONE BEIGE OR TWO-TONE BLUE CABINET WITH GOLD FITTINGS
- DETAILED LEAFLET ON REQUEST

GUARANTEED THE VERY BEST OBTAINABLE
● All parts sold separately ●

TOTAL COST
£10.19.6 P.P. 3/6



OVERALL SIZE
10½ x 7½ x 3½ in.

The New "CONTESSA" 6-Transistor Portable Superhet Radio features simple printed circuit construction and fully illustrated building instructions, with all parts clearly marked and identified. Fitted with 8 inch Ferrite Aerial, double IFT's and the latest in components and design. Full tuning of both Medium and Long Wave Bands with unbeatable Selectivity and Sensitivity. Clearly marked station dial and room filling "MELLOWTONE" push-pull output are standard features. Performance is guaranteed to be better than any other design available to the home constructor whether used at home, out and about, or in a car.

FULL AFTER SALES SERVICE AND GUARANTEE

NEW HUGE PURCHASE REDUCES TOTAL COST "CAPRI" POCKET-6 6-TRANSISTOR SUPERHET

Size only
4½ x 2½ x 1½ in.

**REALLY
POCKET
SIZE!**



The most compact 6-transistor and diode radio with speaker available to the home constructor. Features the latest in miniature components and circuitry. Supplied with Mullard transistors and two-tone moulded cabinets in red/white or blue/white with gold fittings. All components are supplied in packets and clearly identified. A printed circuit is used with fully illustrated building instructions. Push-pull output coupled with a sensitive and selective circuit make the "CAPRI" hard to beat. Fitted Earphone/Record socket. Full tuning on medium waves with long wave Light.

TOTAL COST **£5.19.6** P.P. 2/-

● Detailed Leaflet on Request ●
● After Sales Service and Guarantee ●

3-TRANSISTOR SUB-MINIATURE AMPLIFIER

New 3-transistor amplifier. 125 mW push-pull output to 35 ohm speaker. PP3 9-volt operated.

★ Size only 1.9 x 1 x 1 inches!
Complete with circuit. **45/-** P.P.
Suitable 2½ in. Speaker, 15/- P.P.

Henry's Radio Ltd

PADDINGTON 1008/9

5 HARROW ROAD, LONDON W2

Open Monday to Sat. 9-6. Thurs. 10'clock
Send 1/- Stamp for new Triple Size
Illustrated Catalogue

← **THREE PAGES** of ITEMS

"QUINTET" MEDIUM AND LONG WAVE POCKET RADIO

PUSH-PULL SPEAKER OUTPUT

Size
5½ x 3 x 1½ in.

Red or Blue
with Gold
trim.

Total Cost
99/6 P.P. 2/-



A Five-Transistor and Diode 7-stage medium and long wave printed circuit loud-speaker radio. Features 1st grade transistors and plainly marked printed circuit with carded components. Excellent results with full station separation guaranteed. Including Radio Luxembourg. Push-pull output up to 200 mW. Fitted 'Phone/Record socket and Car aerial socket. Full after sales service and guarantee.

PW-6

**6-Transistor
Superhet**
Medium
and
Long Wave
Radio

Size
5½ x 3½ x 2 in.

£7.19.6 P.P. 2/-

Modified version of previously advertised "PW" Superhet. Now with new style Two-tone Cabinet. 1st grade components and transistors. Printed circuit. Features matched set of 6 Transistors. New 2½ inch quality speaker and new illustrated building instructions.

ALL PARTS IN STOCK

For "PW"-6, Mercury-6, Weyrad MW/LW and MW/SW, "PW" Regency, Alpha-3, etc.

Price Lists on Request.

NEW! "MINI-RANGER" PERSONAL POCKET RADIO

Size only
3 x 2 x ½ in.

**Three
transistors
Two
diodes**



A new printed circuit 5-stage personal pocket radio fully tunable on medium waves and top band, including Radio Luxembourg. A tiny but powerful radio designed to fit into your jacket top pocket. No external aerial or earth. Full station separation with amazing sensitivity and volume. Fully illustrated instructions with clearly marked pre-tinned printed circuit and 1st grade components make this radio Easy to Build and use. Fitted volume control and calibrated dial.

TOTAL COST **59/6** P.P. 1/6

● Building Instructions Free ●

"RANGER 3" A Three-Transistor Radio for Medium Waves and Amateur top band and shipping. Quality output on personal phone. Fitted air spaced tuner, vol. control. No aerial or earth. Luxembourg guaranteed.



59/6 P.P. 1/6
Easy to follow illustrated building plans Free on request.

We can supply most of the components specified on circuits published in this and other magazines and books. Let us quote for your circuit. Competitive Prices.