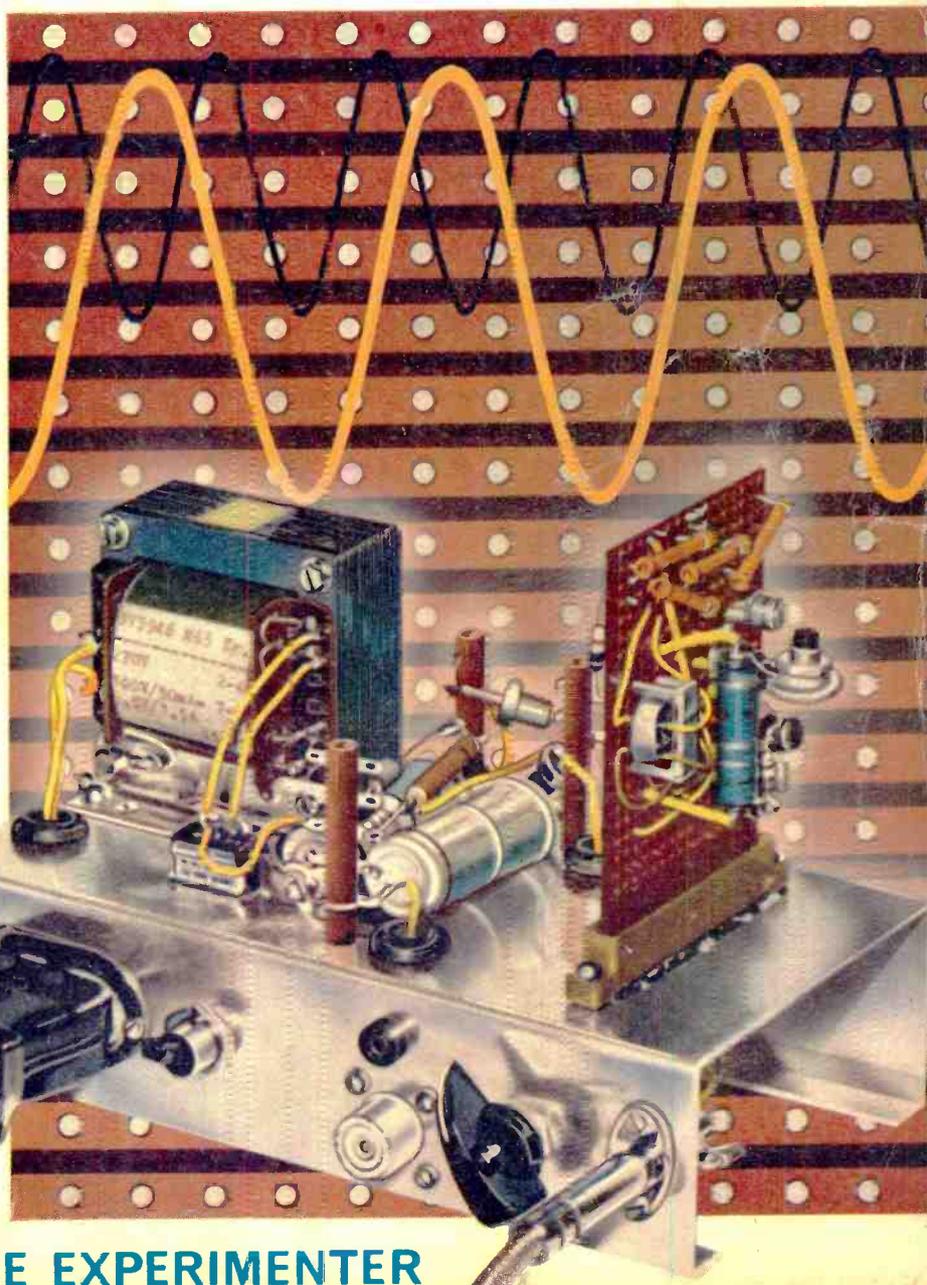


# PRACTICAL WIRELESS

MARCH 1965

2<sup>1</sup>/<sub>2</sub>

KEYED AUDIO  
OSCILLATOR




FOR THE EXPERIMENTER



**SOLDERING EQUIPMENT**

**FOR THE RADIO CONSTRUCTOR**

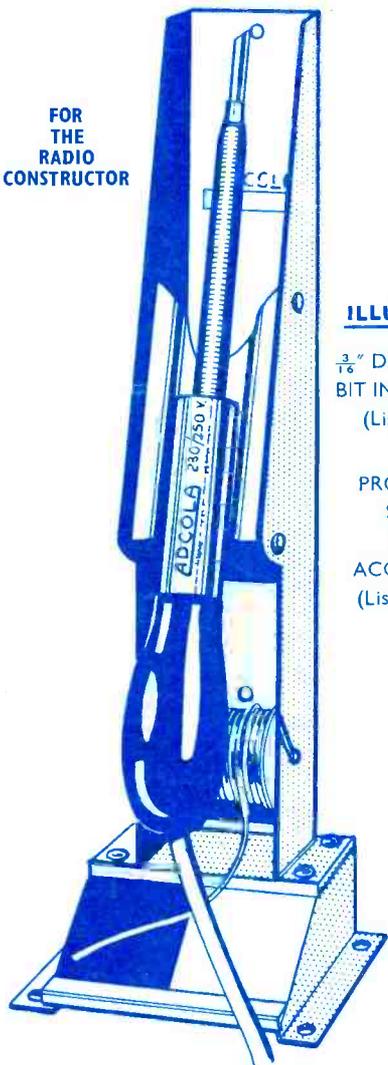

**ILLUSTRATED**

**3/16" DETACHABLE BIT INSTRUMENT**  
(List No. 64)

IN PROTECTIVE SHIELD WITH ACCESSORIES  
(List No. 700)

FOR CATALOGUES APPLY DIRECT  
**ADCOLA PRODUCTS LTD.,**  
**ADCOLA HOUSE,**  
**GAUDEN ROAD,**  
**LONDON, S.W.4**

Telephones:  
MACaulay 3101  
4272

Telegrams: "SOLJOINT" LONDON SW4

*The*  
**SUPER 6**  
**LONG & MEDIUM WAVE**  
**TRANSISTOR RADIO**



A quality radio available as a kit or ready built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.

- ★ All new parts, can be built in 2 hours. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit, Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet, 11 x 7 1/2 x 3 1/2 in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet 2/-. Free with kit. ★ I.F. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list. S.A.E. please. ★ 9v. battery required. VT9 or P.P.9 (3/9 with kit).

**COMPLETE KIT ONLY**  
PLUS 5/- POST **£4.17.6**

OR FULLY BUILT **£6.17.6** Tax & Carr. paid

**TRANSISTORS**

Packet of 3 coded RF transistors (equivalent of OC44/5) 7/6 post paid. Set of 6 transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful for presentation. 15/-, post paid.

**TRADE SUPPLIED**

**ELECTRONICS (Camberley) LTD.**  
15 VICTORIA AVENUE, CAMBERLEY, SURREY  
(Closed Saturdays)



**SAVBIT ALLOY**  
*saves wear on*  
*soldering iron bits*

The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60.40 in 22 s.w.g. for printed circuits, transistors, etc.

**SAVBIT SIZE 1 CARTON**

Contains approximately 30 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.



5/- each

**THE HANDY DISPENSER**



Easy to find in the tool box—Simple to use. Virtually a third hand for tricky soldering jobs. 12 feet 5-core 18 s.w.g. ERSIN MULTICORE SAVBIT alloy in a continuous coil used direct from free-standing dispenser.

2/6 each

**BIB WIRE STRIPPER AND CUTTER**

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex.



3/6 each

**MULTICORE SOLDERS LTD.**

MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS. (BOXMOOR 3636)

# ★ GUARANTEED VALVES ★

by return of post  
**THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY**

All valves are new and unused unless otherwise advised

<b>POST</b> 1 Valve 6d., 2-11 1/- FREE for 12 or more valves.	<b>3 MONTHS GUARANTEE</b> in writing with every valve.	<b>FREE TRANSIT INSURANCE.</b> Satisfaction or Money back Guarantee on Goods if returned within 14 days.
---	---	--

0Z4	4/6 8K3GT	6/- 20L1	18/- DL32	9/- EZ20	5/9 U22	6/9
1A7GT	8/3 8K7	5/9 20P1	9/6 DL20	5/- EZ31	6/- U24	12/6
105GT	7/- 8K7G	2/- 20P3	12/6 DL34	6/6 F04	8/- U25	10/6
1D5	7/- 8K7GT	4/9 20P4	17/- DL36	7/3 FW4/500	7/- U26	8/6
1D9	8/9 8K8G	5/- 20P5	15/- EA30	1/3 G1C	12/6 U31	7/-
1HG7	8/- 8K8GT	11/- 25A0G	8/- EA30B0	6/9 G232	5/9 U33	14/-
1L4	3/- 8K25	3/8 25L0GT	7/9 EA39	4/- G234	11/6 U35	12/6
1LD5	4/3 8L6	9/8 25Y5G	4/- EA42	8/3 HK90	9/8 U37	26/-
1LN5	4/8 8L6G	7/8 25Z4G	7/- EB34	1/3 HL41DD	3/6 U50	4/9
1NSGT	8/9 8L18	7/8 25Z5	8/- EB41	5/- HN309	18/- U52	4/9
1R5	5/8 8L19	11/6 25Z6G	8/- EB81	3/- HV32	9/- U76	5/6
1D5	5/3 8LD20	7/9 27S0	17/6 EB83	4/9 K732	6/9 U73	3/6
184	7/6 8L7	9/9 3C1	6/9 EB811	7/9 K733C	4/- U107	12/6
185	4/6 8P1	9/6 3C15	11/6 EB811	7/9 K736	14/- U131	11/6
1T4	3/- 8P25	8/6 3F5	7/6 EB8F0	7/6 K744	6/- U281	9/6
2D21	5/6 8P28	9/6 3F11	9/6 EB8F3	9/6 K755	17/6 U282	12/-
3A4	4/- 8Q63	6/6 3J11	9/6 EB8F3	7/9 K761	11/- U301	12/-
3A5	8/9 8Q7GT	8/- 3J14	9/6 EB8J21	10/9 K763	4/6 U309	6/6
3D8	4/8 8Q7GT	8/- 3J14	9/6 EB8J21	10/9 K763	4/6 U309	6/6
3Q4	7/- 8Q7G	5/9 3P12	7/6 EC91	4/6 K776	8/9 U331	11/6
3S4	5/- 8G7	4/9 20P19	13/6 EC92	8/6 K783	18/- U403	10/6
3V4	8/6 8G7G	4/9 30P11	9/6 EC93	7/6 K790	5/8 U404	6/6
8R4G	8/- 8H7	3/- 30P13	9/6 EC93	4/9 K792	8/9 U501	17/6
8S4	8/- 8H7	5/8 3C5	8/6 EC93	4/9 K793	5/9 UABC80	7/6
5U4G	5/6 8H7G	5/- 35L0GT	8/- EC94	3/- K726	11/- UAF42	7/6
5V4G	7/6 8SL7GT	5/9 35W4	8/- EC95	5/9 L67	3/- UB41	7/6
5Y3G	4/9 8SN7GT	4/9 35Z4GT	5/6 EC90	8/6 LN82	6/6 UB41	7/6
5Y3GT	8/6 8SQ7	5/9 35Z5GT	7/6 EC92	6/- NU14	7/6 UB51	7/6
5Z4	9/- 8SS7	3/8 42	6/6 EC93	6/- N37	10/8 UB80	7/6
5Z4G	7/6 8G4GT	9/6 50B5	7/6 EC98	6/6 N78	17/- UB89	7/6
5Z4GT	9/6 8V6GT	4/9 50C5	8/6 EC98	7/6 N108	17/- UB121	12/-
6/30L2	8/- 6X4	4/9 50L4GT	7/6 EC98	7/6 N152	8/7 UC82	7/9
6A6	8/9 6X6	5/- 53K0	8/6 EC98	8/6 PA1	2/9 UC85	7/6
6A7	9/- 6X6G	5/- 61BT	17/6 EC92	8/6 PABC80	8/- UC80	10/6
6A8	7/9 6X6GT	6/- 61SPT	11/9 EC91	9/6 PC30	11/6 UC80	9/6
6A8GT	12/6 7B4	10/9 6ZBT	13/6 EC93	11/6 PC97	9/6 UC42	7/6
6C7	3/- 7C5	7/9 75	5/6 EC81	7/6 PC97	9/6 UC42	7/6
6G5	2/9 7C8	7/8 78	5/6 EC81	7/6 PC95	7/9 UCL82	9/6
6G7	6/9 7H7	7/8 83	5/6 EC83	8/6 PC88	11/9 UCL83	12/-
6AK5	5/- 7H7	7/8 83	5/6 EC80	8/6 PC39	9/6 UF41	8/6
6M5	3/3 7Y4	6/- 185BT	19/6 EC82	8/6 PC189	12/- UF42	5/6
6AL6	3/- 8D3	3/- 185BTA	19/6 EC82	8/6 PC189	12/- UF42	5/6
6G5G	6/- 10C1	11/6 807	7/6 EC82	10/6 PC84	12/- UF89	3/6
6G5GT	6/- 10C1	11/6 807	7/6 EC82	10/6 PC84	12/- UF89	3/6
6A8	7/- 10C2	14/6 832	14/- EC22	7/- PCF86	11/- UL41	8/6
6AV6	5/9 10F1	4/9 866A	12/6 EC39	3/3 PCL32	7/3 UL44	14/-
6B7	8/6 10F9	10/9 86A	12/6 EC39	3/3 PCL34	7/3 UL44	14/-
6B8G	5/6 10E18	10/9 865	2/6 EF40	11/- PCL55	10/6 UM80	3/6
6B8	5/6 10D11	14/6 865	2/6 E K 41	8/- PCL36	10/6 URIC	7/9
6B8G	5/6 10P13	8/6 1825	5/6 EF40	6/9 PEN26	3/9 UUT	11/6
6B06G	15/- 10P14	9/6 6080	7/6 EF50	8/1 PEN46	3/8 UUT	9/6
6B16	8/6 10P13	7/- 6057	9/6 EF50	2/6 PEN46	4/6 U19	13/6
6B18	5/9 12A6	2/3 6067	7/6 EF34	3/- PL33	9/6 UY1N	11/6
6B27A	6/6 12A18	11/6 5783	7/6 EF30	4/6 PL36	9/6 UY21	9/6
6B27	8/6 12A76	6/6 9001	3/6 EF85	8/- PL35	15/- UY41	8/6
6B28	9/6 12A77	5/6 9002	4/6 EF88	7/6 PL81	8/3 UY85	6/6
6BW6	7/8 12A0E	9/- 9003	5/9 EF88	6/9 PL82	8/6 VP48	9/6
6BW7	5/- 12A07	6/- ATP4	2/6 EF91	3/- PL83	6/6 VP23	2/6
6C3	2/3 12A76	6/9 AZ31	7/6 EF92	3/- PL84	7/- VP41	5/6
6C4	5/6 12A77	6/9 AZ41	7/6 EF183	9/9 PLS20	8/3 VR105	5/6
6C8	3/6 12BA6	7/- 7C	8/6 EF184	9/6 PLS4	8/- VR150	5/6
6C9	11/- 12BE2	6/6 C1C	8/- EK32	7/6 P7	12/6 W76	4/9
6CDB6	19/6 12BH7	8/9 CBL31	13/6 EL32	3/9 PX25	9/- W81	7/6
6C8E	8/3 12C9	5/6 CCH35	13/6 EL33	11/- YX21	9/- X61M	11/6
6D3	9/6 12H3	1/8 D75	7/6 EL34	11/6 YX32	10/6 X63	8/6
6D6	3/- 12J5GT	3/3 DA30	11/6 EL35	6/- YX33	10/6 X65	11/6
6F1	4/9 12J7GT	8/- DAC32	8/- EL41	8/- YX81	6/3 X76M	11/6
6F6	7/6 12K7GT	4/9 DAF91	4/6 EL42	8/- YX82	5/9 X73	21/-
6F8G	4/6 12K8	8/9 DAF96	7/6 EL81	8/9 YX83	8/9 X79	21/-
6F13	4/9 12K8GT	11/6 F33	8/6 EL54	8/6 YX88	8/9 X91M	8/6
6F14	9/6 12Q7GT	4/9 DF31	3/6 EL55	8/9 YX89	8/9 X91M	8/6
6F15	9/6 12S47	7/- DF86	7/8 EL91	3/9 YF801	7/9 Z63	6/6
6F23	6/- 12S97	4/8 DF97	7/8 EL95	6/- PZ20	9/6 Z63	4/9
6F32	4/9 12SH7	3/6 DH63	5/6 EM30	8/9 R19	9/6 Z66	8/6
LF53	4/- 12SH7	4/6 DH76	4/6 EM80	7/6 RL18	11/-	
6J5	5/6 12K7	4/6 DK92	8/6 EM81	8/9 SP31	8/-	
6J5G	3/- 12S97	8/6 DK92	7/- EM81	16/- S225	16/-	
6J6GT	3/3 13D3	8/6 DK96	7/9 EY51	7/6 SD1250	4/8	
6J6	3/6 19A45	7/8 DL33	7/6 EY86	7/3 T91	6/8	
6J7	8/6 19B6	1/6 DL35	7/6 EY89	9/6 TD4	6/8	
6J7G	4/9 20D1	8/9 DL63	8/- EZ40	7/- U14	7/6	
6J7GT	7/6 20F2	8/9 DL75	8/- EZ41	7/- U18	7/6	

## Tubes

Carry. & Ins. 12/6

MOST MULLARD,	12in.	£2. 0.0	£3. 0.0	NEW MW 31/74
MAZDA, COSSOR,	14in.	£2.10.0	£3.10.0	£3.15.0
EMITRON, EMI-	15-17in.	£3. 5.0	£4. 5.0	MW 36/24
SCOPE, BRIMAR,	19in.	£3. 5.0	£4. 5.0	£4.15.0
FERRANTI TYPES,	21in.	£3.15.0	£5.15.0	CRM 178
PROCESSED IN OUR OWN FACTORY	23in.	£3.15.0	£5.15.0	MW 43/64 £6.0.0

### SATISFACTION GUARANTEED

#### TRANS RECEIVERS

Type STR908. Latest 9 Transistor Loudspeaker type. 1-4 miles range. Few at pre-increase price of **£25**

#### PROFESSIONAL TAPE RECORDER

MAYFAIR FT157. Six Transistor, Cassette Drive, Two Speeds, Dual Track, Push-button Controls, Tape, Ideal Speech and Music, Many Refinements, Only 3.5. Wow Flutter. Beautiful Finish with Mike, 6in. Tape, Telephone adaptor **£17.17.0**

CO-AX, low loss, 6d. yd., 25 yards, 11/6. 50 yds., 22/-, 100 yds., 42/6 Co-ax Plugs, 1/3. Wall outlet boxes 3/6

#### SPECIAL C.R.T. OFFER

Due to huge Bulk Special Purchase we are offering MW 31/74 Tubes at the unrepeatable price of 29/-, MW 36/24 ditto, 39/-. P.P. 12/6. The above are guaranteed for 6 months.

#### LOUDSPEAKERS

8 Ω Top Makes  
6in. **7/6**      5in. **5/6**  
5in. **7/6**      7 x 4in. **8/6**

#### CONNECTING WIRE

P.V.C. Bright Colours. Five 25ft. coils only. **4/-**

#### MAINS TRANSFORMERS

Excellent Quality Guaranteed. 10 bright mounting 250-0-250 V 50 m.A. 6.3 V 3 A (50mA 12/9) **9/6**  
Ditto semi-shrouded 9/6.

#### 13 CHANNEL T.V.s

Table Models. Famous Makes. Absolutely Complete. These sets are unequipped in value due to huge purchase direct from source. They are untested and guaranteed to be in working order. Carry. etc., 16/-  
14in. **£2.19.0**    17in. **£4.19.6**

#### TURRET TUNERS

Most makes. Your choice if available, with valve 16/-, less valves 10/- S.A.E. enquiries.

#### ★ BULK BARGAINS ★

15 POTS, Popular values. 5K to 12 MΩ. Unused, mixed, pre-set, long sp., switch, etc. **4/6**  
CONDENSERS. 26 Mixed Electrolytic. Many popular sizes. List 10/- Value 45. Our price **10/-**

#### 100 RESISTORS 6/6

Excellent. Sizes 1-3 watt.

#### 100 CONDENSERS 9/6

Miniature Ceramic and Silver Mica Condensers, 3 pF to 5,000 pF. LIST VALUE OVER 45.

#### 25 TAG STRIPS 4/-

2, 4, 6, 8 way etc. Unused.

#### 100 HI STABS 9/6

1% to 5% 100 Ω to 5 MΩ.

#### TRANSISTORS

GUARANTEED TOP QUALITY Huge reduction. Red Spot standard L.F. type now only **1/6**  
White Spot R.F. .... **2/-**  
Mullard Matched Output Kit **12/6**  
OC51D and 2-OC51  
R.F. Kits OC44, OC45 (2)- **12/6**  
3 transistors.  
AF114 8/- OC44 5/8  
AF115 7/6 OC45 5/8  
AF116 7/6 OC72 5/8  
AF117 7/- OC81 5/8  
AF127 9/6 OC1D 5/8  
OC76 12/6 OC82 6/-  
OC86 14/- OC170 8/6  
OC171 8/6

#### GERMANIUM DIODES

General Purpose miniature detector, A.V.C. etc. **8d.**  
Gold Bonded highest quality. Individually tested. **1/-**  
9/8 dcz.

#### SILICON RECTIFIERS

Guaranteed performance. Top Makes Tested! 250V working.  
100mA      250mA  
(3 for 9/6) **3/9**      (3 for 19/6) **7/6**

VALVE HOLDERS. B7G, 6d. ea., with Screen 8d. ea., B9A 6d. ea., with Screen 8d. ea. Int. Octal 6d., Mazda Octal 4d. BA 6d. (less 15% in dozens).

#### LINE TRANS

Single quantity, most makes at huge **29/-**  
S.A.E. enquiries.

#### ELECTRIC MOTORS. AC/DC 3-3

1/2 in. Totally enclosed standard mounting, powerful V pulleys. **7/6**  
spare brushes, 2in. x 2in.

#### ELECTROSTATIC SPEAKERS

Type LSH75. Originally 25/-, As fitted to German Hi-Fi Radios. Bargain 5/- ea. **9/8** pair.

#### ACCUMULATORS

Small 2 volt 3 amp/hour, 3/6 each.

#### H.T. TRANSFORMERS

200/250V a.c. 350-350V 150 m.a., 6.3V 5 amp, 5V 3 amp. Gilt 27/8.

#### TUNING CONDENSERS

F.M. 2 gang 15+15 pf. standard with slow motion, 3/9. AM/FM 500 pf. and 15 pf. 2 gang, with slow motion, 4/9. Standard 0005 2 gang, 4/6. Small 0005 2 gang, 4/6.

#### A.C. MOTORS

For 230V a.c. Powerful, self-starting, weight 1 lb., 12/8.

#### SYNCHRONOUS MOTORS

200/250V A.C. 50 Ω top quality 1 rev. per hour. Ideal clocks, timers, etc. 12/6

#### ENQUIRIES WELCOMED

Quantity Prices or Quotes for Items not listed, particularly rare valves. TELEPHONE C.O.D. ORDERS DISPATCHED THE SAME DAY

Post: 2 lbs. 2/-, 4 lbs. 2/8, 7 lbs. 3/6, 15 lbs. 4/-, etc. (C.O.D. extra). ALL VALVES LESS 5% AND POST FREE IN DOZENS.

**TECHNICAL TRADING CO.**  
 250-352 Fraxton Road, Portsmouth Tel: 22034  
 ALL MAIL ORDER, RETAIL SHOP AND HI-FI ROOM  
 DEVONIAN COURT PARK CRESCENT PLACE  
 BRIGHTON. Tel. 608722

**RSC**  
(MANCHESTER) LTD.

MAIL ORDERS  
TO:

54 WELLINGTON STREET, LEEDS 1  
Terms: C.W.O. or C.O.D. No C.O.D.  
under £1. Postage 2/9 extra under £2.  
4/6 extra under £5. Trade Supplied.  
S.A.E. with all enquiries please. Personal  
shoppers welcomed at any of the branches  
below. Open all day Saturday.

**BRADFORD** 54 Morley Street,  
Nr. Alhambra Theatre  
Tel: 25349. (Half-day, Wednesday).  
Opening early February 1965, spacious  
new premises at 10 North Parade.

**BRISTOL** 14 Lower Castle Street  
(Half-day Wednesday)  
Tel: 22904

**BIRMINGHAM** 30/31 Gt. West-  
ern Arcade opp.  
Snow Hill Station  
(No half-day) Larger premises now open.

**DERBY** 26 Osbaston Rd. The Spot  
(Half-day Wednesday)  
Tel: 41361

**DARLINGTON** 13 Post House  
Wynd (Half-day  
Wednesday) Tel: 68043

**EDINBURGH** 133 Leith Street,  
(Half-day Wed.)  
Tel: WAVErley 5766

**GLASGOW** 326 Argyle Street  
(Half-day Tuesday).  
Tel: City 4158

**HULL** 51 Savile Street (Half-day  
Thursday) Tel: 20505

**LEICESTER** 32 High Street (Half-  
day Thurs.) Tel: 56420

**LEEDS** 5-7 County (Macca) Arcade  
(No half-day) Tel.: 28252

**LIVERPOOL** 73 Dale St. (No half-  
day) Tel: CENtral 3573

**LONDON** 238 Edgware Road W2  
(Half-day Thursday)  
Tel: PADdington 1629

## MANCHESTER

60A-60B Oldham St. Tel: CENtral 2778  
(No half-day) New large store.

**MIDDLESBROUGH** 106 New-  
port Rd.  
(Half-day Wednesday) Tel: 47096

**SHEFFIELD** 13 Exchange Street  
Castle Market Bldgs.  
Tel: 20716 (Half-day Thursday)

**EX. GOV. 2V ACCUMULATORS,**  
16 A.H. Size 7 x 4 2in. Brand new,  
4/8 each. Three for 12/6. carr. 5/-.


**MULTI-METERS CABY M1.** Sensitivity  
2,000 ohms per volt. A.C. and D.C. 54/-  
A.10. Basic Meter sensitivity 155 micro-  
amps A.C. and D.C. ranges £4.11.8. B.40I  
Sensitivity up to 10,000 ohms per volt A.C.  
and D.C., £6.2.6. 30,000 ohms per volt. with  
overload buzzer. £8.19.6. Other types in  
stock from 39/8.

**EX GOVT. SELENIUM  
RECTIFIERS 12v 15 AMP  
(BRIDGE) F.W. ONLY** 19/9

**EX. GOVT. SMOOTHING CHOKES.**  
200 mA, 3-5 H, 50 ohms. Parmeko 8/9;  
150mA, 10 H, 50 ohms 9/9; 120mA, 12 H, 100  
ohms, 8/9; 100 mA, 10 H, 100 ohms, 6/9; 60  
mA, 5-10 H, 250 ohms, 2/11.

**HI-FI 10 WATT AMPLIFIER**  
Brand New Complete Units **£7.19.6** Carr.  
5/8  
Manufacturer's discontinued Model. Push-  
pull output. Latest high efficiency valves  
Dual separately controlled inputs for  
'Mike' and gram. Separate Bass and Treble  
Controls. High Sensitivity. Output for 3 or  
15 ohm speaker. Guaranteed tested and in  
perfect working order.
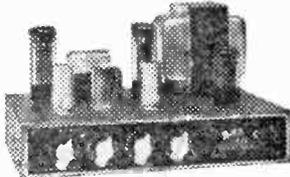
## R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10



A highly sensitive Push-Pull high output unit with self-contained Pre-amp, Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response  $\pm 3$  dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUT-DOOR FUNCTIONS, etc. For use with Electronic ORGAN, BASS, LEAD OR RHYTHM GUITAR, STRING BASS, etc. For standard or long-playing records, OUTPUT SOCKET / PROVIDES L.T. and H.T. for RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike", can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 8 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

### 11 Gns.

Carr. 10/-.  
For 19/9. The amplifier can be supplied, factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

**TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9. (Total £16.17.6).** Suitable microphones and speakers available at competitive prices.

## SPECIAL NOTICE REGARDING GOODS SUPPLIED ON TERMS CASH PRICE FOR 6 MONTHS SETTLEMENT

### R.S.C. 4/5 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity Pick-up heads in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down, 15 dB of Negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. not alive. Chassis is complete in every detail and includes fully punched chassis (with baseplate) with Gold Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0 or assembled ready for use 25/- extra, plus 3/6 carr. Deposit 22/8 and 5 monthly payments of 22/8 (Total £6.15.0), for assembled unit.

**TANNOY RE-ENTRANT LOUDSPEAKERS.** For outdoor or Factory use. 8 ohms, 8 watts. Only 25/9

## ARMSTRONG RADIOGRAM CHASSIS Stereo and Mono Full Range in stock at all Branches Cash or Terms

### TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 inputs, i.e., mic., tape, gram., tuner, etc., into single output. Compact and completely self-contained, uses 8 volt battery. (supplied free) Four standard Jack inputs.  
**PRICE 49/6**

## FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies.  
122/10 20watt, 5 gns. 122/10A 20watt, 6 gns.  
122/12 20watt, 7 gns. 122/12A 20watt, 8 gns.  
122/14 20watt, 9 gns. 122/14A 20watt, 10 gns.  
122/17 20watt, £11.17.6 122/17A 20watt, £12.17.6  
15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies.  
152/12 20watt, 12 gns. 152/12A 20watt, 13 gns.  
152/14 27watt, 14 gns. 152/14A 27watt, 15 gns.  
152/17 33watt, 16 gns. 152/17A 33watt, 17 gns.  
"A" indicates dual cone type. 30-17,000 c.p.s. Send S.A.E. for leaflets and terms.

## GOODMANS QUALITY LOUDSPEAKERS

8in. Axielte 5 gns. 10in. Axiom £6.5.11.  
12in. Audiom 51 (15 watts) £9.2.8  
12in. Audiom 61 (20 watts) £14.7.8.  
12in. Axiom 201 (15 watts) £10.17.4.  
12in. Axiom 301 (20 watts) £15.4.6.  
15in. Audiom 81 (25 watts) £20.0.0.  
18in. Audiom 91 (50 watts) £27.10.0.  
Available cash or terms.

## 12 in. 10 WATT HIGH QUALITY LOUDSPEAKER



In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6. Carr. 5/-. Terms: Deposit 11/3 and 9 monthly payments of 11/3. (Total £5.12.6) 12in. 20 WATT HI-FI LOUDSPEAKERS IN CABINETS. Size 18 x 18 x 10in. Finish as above. Only £7.18.6. Terms: Deposit 17/9 and 9 monthly payments of 17/9 (Total £8.17.6). Carr. 3/6. For larger types see page 2.

**R.S.C. POWER PACK, 39/9.** Louvred metal case only 8 x 5 1/2 x 2 1/2in. Stove enamelled. For 200-250 v. A.C. mains. Output at 4-pin plug and socket 250 v. 60 mA. Fully smoothed at 6.3 v. 2 a. Suitable for power requirements of almost any Pre-amp or Radio Tuner.

**TRANSISTOR SALE** Mullard OC719/9. OC45 4/11, OCC44 4/11, OC72 4/9, OC81 4/11, OC171 8/9, Ediswan XA101 3/9, XB102 3/9, XA112 3/8, XB113 3/9, XB104 3/9, XC101A 3/8. Postage 6d. for up to 3 transistors.

## SPECIAL NOTICE REGARDING GOODS SUPPLIED ON TERMS CASH PRICE FOR 6 MONTHS SETTLEMENT

### R.S.C. 4/5 WATT A5 HIGH-GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity Pick-up heads in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down, 15 dB of Negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. not alive. Chassis is complete in every detail and includes fully punched chassis (with baseplate) with Gold Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0 or assembled ready for use 25/- extra, plus 3/6 carr. Deposit 22/8 and 5 monthly payments of 22/8 (Total £6.15.0), for assembled unit.

**SPEAKERS.** Total Flux 375,000 lines. Extremely high sensitivity. Exceptionally robust 3in. diameter voice coil assemblies. Impedance 15 ohms.

Model 153 15 in 40 watts. Deposit 37/8 and twelve monthly payment of 31/8. (Total £20.15.9).  
Model 183 18 in. (80 watts. Dep-24.9).  
cost 51/- and twelve monthly payments of 42/9. (Total £28.4.0).  
Send S.A.E. for leaflet.

**R.S.C. BAY ALARM or INTER-COMM KIT.** Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An intercom. of this class would normally cost £20-£30. Only 89/6. carr. 5/- or assembled ready for use. 6 gns.





## R.S.C. BASS-MAJOR 30 WATT AMPLIFIER


A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

*Eminently suitable for bass, lead or rhythm guitar and all other musical instruments*

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 3in. diameter speech coils. Designed for efficient handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker Reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 28 x 15 x 13 in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four Jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microph'ns.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut"
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

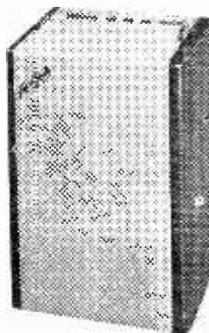**39<sup>1</sup>/<sub>2</sub> Gns.**

Send S.A.E. for leaflet OR DEPOSIT of £4.3.0 and 12 monthly payments of £3.9.11 (Total £46.2.0) Carr. 17/6.



## R.S.C. BASS-REGENT 50 WATT AMPLIFIER


AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT

*For bass, lead or rhythm guitar and all other musical instruments*  
*For vocalist, gram, radio, tape and general P.A.*

- ★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit and a FANE 12in. 20 watt unit with extended frequency response.
- ★ 4 Jack Socket inputs and two independent volume controls for simultaneous use of up to four instruments, pick-ups, or mikes.
- ★ Separate Cabinets fully covered with Rexine and Vynair in contrasting tones for Amplifier and Speakers.
- ★ Separate Bass and Treble controls for "Boost" and "Cut".

Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at more than 3 times the cost.

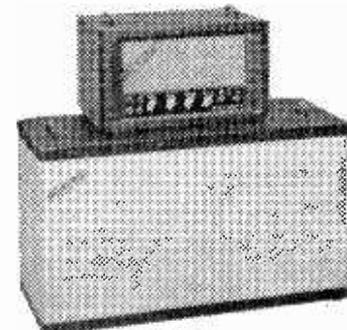**44** Cash Price 19/6 Or Deposit **£4.16.6** and 12 monthly payments of **£3.16.3** (Total **£50.16.6**)




**THE BASS-REGENT AMPLIFIER UNIT ONLY CAN BE SUPPLIED SEPARATELY AT 21 Gns.** Deposit 4/6 and 9 monthly payments of 4/8/6. (Total £24.5.0) Carr. 10/-.

The speaker unit is not separately available.
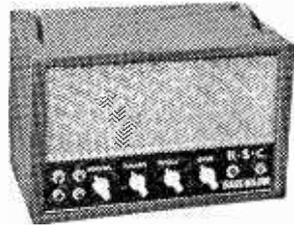
## 30W. HIGH QUALITY AMPLIFIER

A Four Input, two volume control Hi-Fi unit with separate Bass and Treble "Cut" and "Boost" controls. Designed for vocal or instrumental groups. For Bass, Lead or Rhythm Guitar. Six Mullard or Brimar latest type valves housed in strong Rexine covered cabinet with twin chrome carrying handles. Attractive black and gold perspex fascia plate. For 200-250 v. A.C. mains. Output for 3 or 15 ohm speakers. Send S.A.E. for leaflet.

**16<sup>1</sup>/<sub>2</sub>** Carr. or Deposit **£2.1.6** and 12 monthly payments of **£1.8.4** (Total **£19.1.6**)



## HEAVY DUTY LOUSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS

**TYPE BG1** Suitable for Bass Guitar. Speaker Unit 15in. High Flux. 15 ohms. 30 watts. Cabinet size approx. 24 x 21 x 13in. Only **19<sup>1</sup>/<sub>2</sub> Gns.** Or Deposit 4/3- and 12 monthly payments of 34/- (Total £22.11.0).

**TYPE BG3/2** Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vynair **29 Gns.** and Rexine. Rating 50 watts. Only Or Deposit **£3.7.6**. and 12 monthly payments of 50/- (Total **£33.7.6**).



## R.S.C. G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, 'Mike', Gram, Tape or Radio

High-fidelity push-pull output. Separate bass and treble "Cut" and "Boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Sturdy cabinet is covered in pleasing shades of Rexine/Vynair. Model Size approx. 18 x 13 x 8in. Only **19 Gns.** Carr. 10/-

Send S.A.E. for leaflet. Or DEPOSIT 3/11 and twelve monthly payments of 3/4 (Total £21.10.11).



## R.S.C. BASS/20 AMPLIFIER A multi-purpose unit especially suitable for BASS GUITAR

A highly efficient unit incorporating massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "Boost" and "Cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains. Send S.A.E. Or deposit for leaflet **29<sup>1</sup>/<sub>2</sub> Gns.** £3.2.0 and 12 monthly payments of 51/8. (Total **£34.2.0**) Carr. 17/6.

**LINEAR TREMOLO/PREAMP.** UNIT Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch. **ONLY 4 Gns.**


## R.S.C. COLUMN SPEAKERS

Finished in polished veneered walnut. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100 v. line for 35/- extra.

**TYPE C57, 10-15 watts.** Fitted five 6 x 4 elliptical speakers. Overall size approx. **9 Gns.** Carr. 26 x 9 x 4in. **7/6**

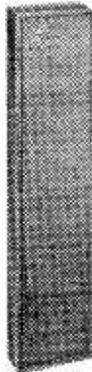**TYPE C58, 15-20 watts.** Fitted five 8in. high flux speakers. Overall size approx. 42 **12 Gns** Carr. x 10 x 5in. **10/-**

Or deposit 2/7.6 and 12 monthly payments 20/10 (Total **£13.17.6**).




## R.S.C. G5 AMPLIFIER

for Guitar, 'Mike', Gram or Radio 5-watt high quality output. Incorporating high flux 12in. 10 watt 12,000 line loudspkr. Sensitivity 30 m.v. High impedance jack input. Handsome strongly made cabinet (size 14 x 14 x 7in. approx.) finished in complementary shades of Rexine/Tygan, 200-250 A.C. mains. Suitable for Lead or Rhythm guitar in home or small club, etc. **£9.19.6** OR DEPOSIT **£2/3** and 9 monthly payments of 2/8 (Total **£11.2.6**) Carr. 7/6.
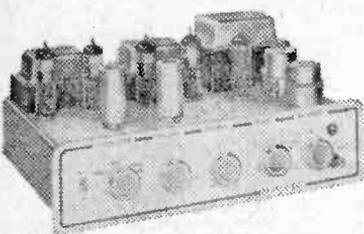
# Introducing the R.S.C. STEREO/20 HIGH FIDELITY AMPLIFIER

PROVIDING 10/14 WATTS ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL



Features include:  
 ★ Three-position tone compensation switch.  
 ★ Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.  
 ★ Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls.  
 ★ Neon panel indicator. **12 Gns.**  
 ★ Handsome Parper Frontplate. Carr. 10/-  
 Send S.A.E. for illustrated leaflet. Complete set of parts with point to point wiring diagrams and Instructions, or Factory assembled, tested and supplied with our usual 12 months guarantee for 16 gns. or DEPOSIT 37/9 and nine monthly payments of 37/9 (Total £18.17.6). Protective wooden cabinet covered in pleasing shade of leathercloth and fitted carrying handles and plastic feet 59/9 extra or DEPOSIT 6/9 and nine monthly payments of 6/9 (Total £3.7.0).

SUITABLE FOR "MIKE" GRAM. RADIO OR TAPE. INTENDED FOR THE HOME OR STUDIO BUT SUITABLE FOR LARGE HALLS OR CLUBS.  
 Based on a current Mullard design and employing valves ECC83, ECC83, ECL86, BCL26, ECL86, ECL86, EZ81. Output transformers are high quality sectionally wound to required specification. Output matching for 3 and 15 ohm speakers on each channel.  
 FREQUENCY RESPONSE ± 2dB. 30-20,000 c.p.s.  
 HUM LEVEL 65dB down.  
 SENSITIVITY: 15 millivolts maximum.  
 HARMONIC DISTORTION (each channel) 0.2%  
 For operation on 200/250v. A.C. Mains.

**R.S.C. STANDARD BASS REFLEX CABINET.** For 12in. loudspeakers, acoustically lined and ported. Size 20 x 14 x 13in. Beautiful walnut veneer finish. Especially recommended for use with Audiotrine Speaker System £5.19.6. Set of four legs can be supplied with brass ferrules for 18/6.

**AUDIOTRINE CORNER CONSOLE CABINETS.** Strongly made. Beautifully polished walnut veneered finish. Pleasing design. **JUNIOR MODEL.** To take up to 8in. speaker. Size approx. 20 x 11 x 8in. Only £2.9.0

**STANDARD MODEL.** To take up to 10in. speaker. Size 27 x 18 x 13in. £4.11.9.  
**SENIOR MODEL.** To take up to 12in. speaker and with Tweeter cut-out. Size approx. 30 x 30 x 15in. (Recommended for use with Audiotrine speaker system). 7 gns. or terms.

**W.B. "STENTORIAN" HIGH FIDELITY P.M. SPEAKERS HF1012.** 10 watts rating. Where really good quality speaker at a low price is required, we highly recommend this unit with an amazing performance. £4.12.0. Please state whether 3 ohm or 15 ohm required.

**R.S.C. JUNIOR BASS REFLEX CABINET.** Designed for above speaker, but suitable for any good quality 8in. or 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10 in. Strongly made. Handsome appearance. Ensures superb reproduction for only £3.19.6.

## AUDIOTRINE 3D/1

A complete three diaphragm high fidelity loudspeaker unit designed to occupy a minimum of space. Depth is only approx. Height 24in. Width 15in. This has been made possible by the latest developments in loudspeaker design. The 12in. cast chassis Bass unit has a resonant frequency which is extraordinarily low. It has a second diaphragm which extends the frequency range to 17,000 c.p.s. A further speaker operates only on the middle frequencies and ensures a smooth response from 40-17,000 c.p.s. Rating 20 watts. Imp. 15 ohms. Cabinet finish in either polished walnut veneer, or leathercloth to match stereo/20 cabinet. Highly recommended for a Stereo or Mono Amplifier. Surely the best value ever at 11 gns. Or Deposit 25/9 and nine monthly payments of 25/9 (Total £12.17.6).

**R.A. 12in. DUAL CONE 3 ohm 8 watt Speakers.** Ideal for Stereo. Only 39/9 ea.

**LOUDSPEAKERS.** 24in. to 18in. at keen prices. 12in. 6-8 watt 3 ohm 29/11. 12in. 10 watt 12,000 lines 3 ohm or 15 ohms, 59/6. **TWEETERS.** 4in. R.A. 3 ohms 25/9. R.A. 15 ohms 25/9. W.B. 15 ohms 32/3. Fane 15 ohms. Pressure type £3.15.0. Eagle CT 10-15 ohms 27/6.

## AUDIOTRINE EQUIPMENT

**REPRODUCTION**  
 Size 30 x 15 x 18 in. Beautiful walnut veneered finish. Elegant contemporary design. Robust construction. Uncut removable baseboard. Depth above baseboard 34in. Only 184 gns. Carr. 15/-  
 Terms: Deposit 29/9 and 9 monthly payments 25/9 (Total £14.17.6). Full range of equipment cabinets available.  
**R.S.C. JUNIOR HI-FI REPRODUCER**  
 The very latest Goodmans Axiote's 8 High Fidelity loudspeaker (retailing at £5.5.7), fitted in a specially designed Bass Reflex cabinet, size 12 x 18 x 10in. Acoustically lined and ported and finished in polished walnut veneer. Matching impedance 15 ohms. Frequency range 40-15,000 c.p.s. Power handling 6 watts nominal. Ideal for Stereo Carr. 4/6. Deposit 21 and nine monthly payments of 21. **£8.19.6** (Total £10.0.0).

**LINEAR L45 MINIATURE 45 WATT QUALITY AMPLIFIER.** Suitable for any record playing unit and most microphones. Negative feedback 12dB. Separates Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E280, ECC83, EL84. Size only 7 x 5 x 6in. high. Guaranteed 12 months. Only 6 gns. Send S.A.E. for leaflet. Terms: Deposit 24/9 and 6 monthly payments of 24/9. (Total £27.8.6).

**JASON FM11 V.H.F./F.M. Radio Tuner** design. Total cost of parts including valves, Tuning dial, Escutcheon, etc. £8.19.6.

**WE STOCK AT ALL BRANCHES ARMSTRONG, TRUVOX, LINEAR ROGERS, LEAK and JASON EQUIPMENT. GOODMANS, W.B. and FANE SPEAKERS, GARRARD and GOLDRING T/ABLES, LUSTRA-PHONE, GRAMPHON, RESLO and SHURE MICROPHONES, CASH OR TERMS.**

**SUPERHET FEEDER UNIT.** Design of a high quality Radio Tuner (especially suitable for use with our Amplifiers). Delayed A.V./C. Controls are Tuning, W/C and Vol. Only 250 v. 15 mA H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total building costs £5.5.0. S.A.E. for leaflet.

**AUDIOTRINE HI-FI SPEAKER SYSTEMS.** Consisting of matched 12in. 12,000 line. 15 ohm high quality speaker; crossover unit consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. £4.19.9. Carr. 5/- Or Stereo 20 watt. £6.19.6. Carr. 7/6.

## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram., as in A10 High sensitivity includes 5 valves. ECC83, ECC83, EL84, EL84, EZ81. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut".** Frequency response ± 3 dB 30-20,000 c/s. Six negative feedback loops. Hum level 60 dB down. **ONLY 23 millivolts INPUT required for FULL OUTPUT.** Suitable for use with all makes and types of pickups and microphones. Comparable with the quality best designs for **STANDARD or LONG PLAYING RECORDS. FOR MUSICAL INSTRUMENTS** such as **STRING BASS, LEAD OR RHYTHM GUITARS, etc.**  
**OUTPUT SOCKET** with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a **RADIO FEEDER UNIT.** Size approx. 12 x 9 x 7in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohm speakers. Kit is complete to last unit. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** Carr. 10/- (Or factory built 51/- extra.)  
 If required louvred metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9 and 9 monthly payments of 24/9 (Total £17.6).** Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

**LINEAR TAPE PRE-AMPLIFIER.** Type LPI. Switched Negative feedback Equalisation. Positions for Record (1in., 3in., 7in. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Colliate Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck, Only 81 gns. S.A.E. for leaflet.

## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Gained Bass and Treble Control give equal variation for "Lift" and "Cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, EZ81. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. **8 Gns.** Carr. 10/- Full construction details and price list 2/6. Carr. 10/-  
 Kit can be supplied assembled and ready to use for 59/6 extra.

# AUDIOTRINE HI-FI TAPE RECORDER KIT 25 1 GNS. 2 Carr. 17/6

**REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR**  
 Incorporating the latest Collaro Studio Tape Transcriber. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet tastefully covered in two contrasting shades of Bendin and Vynair, size 14 x 15 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £80-£30 class. S.A.E. for leaflets. T.R.M.S. Deposit £2.13.9 and 12 monthly payments of 44/- (Total £28.7.9). Cash price if settled in 3 months.



**R.S.C. GRAM AMPLIFIER KIT.** 3 watts output. Negative feedback. Controls Vol., Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/8. Carr. 3/9.

**BRADMATIC RECORDING HEADS.** High Impedance Record/Playback 22/-. Low Impedance Erase. 12/6.  
**MARROTT RECORDING HEADS.** High Impedance. Record/Playback, Low Impedance. Erase. 25/- pair.

**ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS**

## SELENIUM RECTIFIERS

F.W. BRIDGE	6/12 v. 1a.	3/11	H.T. TYPES	H.W.
6/12 v. 2a.	6/11	150 v.	40 mA	3/9
6/12 v. 3a.	9/9	250 v.	50 mA	3/11
6/12 v. 4a.	12/9	250 v.	80 mA	4/11
6/12 v. 6a.	15/3	250 v.	80 mA	5/11
6/12 v. 10a.	26/9	250 v.	250 mA	11/9
6/12 v. 15a.	35/9			

CONTACT COILS. 250 v. 75 mA. F.W. (Bridge). 10/11. 250 v. 50 mA. F.W. (Bridge). 8/11. H.W. 250 v. 60 mA. 5/11.

**THE SKYFOUR T.R.F. RECEIVER.** A design for a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, SP6L, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-Point wiring diagrams, instructions and parts list 1/9. maximum building costs £4.19.6. Inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

**HI-FI CRYSTAL PICK-UP HEADS.** (Cartridges.) Acos Standard replacement for Garrard, B.S.R. and Collaro, 16/9. Acos Stereo-Monaural 29/9. Ronette Stereo-Monaural 39/9. B.S.R. Stereo 39/9.  
**PICK-UP ARMS.** Complete and with latest Acos/hi-fi Turnover Cartridge 29/11.  
**CRYSTAL MICROPHONES.** Hand type NP10 12/9. R.C. 19/9. Acos Mic 40 25/9. Acos Mic 45 29/9. Stick type Acos 39-1 39/9. BM3 with neckband and heavy table stand 59/9. Lapel type 29/9.

## ARMSTRONG High Quality TUNER AMPLIFIER

### 127M MONO

- ★ 5 watts output
- ★ Frequency response 40-20,000 c.p.s.
- ★ Volume, Treble and Bass Controls
- ★ Inputs for Pick-up and Tape Play-back



A.M. Tuner—Medium Wave 180—600 metres  
 F.M. Tuner—87—108 m/c.s.

**£26.10.0**

(Case £3.10.0 extra) or deposit 58/4 and 9 monthly payments of 58/4 (Total £29.3.4)

**ALL OTHER ARMSTRONG MODELS AVAILABLE**

**127 STEREO**  
 Details as Mono unit but 5 watts per channel

**£37.10.0**

(Case £3.10.0 extra) or deposit £3.15.0 and 12 monthly payments of £3.2.0 (Total £41.5.0)

### 222 STEREO AMPLIFIER

10 watts push-pull per channel. Frequency response 30-20,000 c.p.s. ± 1 dB. Volume, Treble, Bass and Balance Controls. Input sensitivity 80 mV.

**£27.10.0**

or deposit £3.0.7 and 9 monthly payments of £3.0.7 (Total £30.5.10)

## SENSATIONAL STEREO OFFER

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Sensitivity 180 mV. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

### COMPLETE POWER PACK KIT

Consisting of Mains Trans., Metal Rectifier, Double electrolytic smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v., 60 mA. 19/11 6.3 v., 2 a.

## R.S.C. BATTERY CHARGING EQUIPMENT



charging. Louvred steel case with stoved grey hammer finish. Fused and ready for use with mains and output leads and battery clips. Carr. 4/6. Terms: Deposit 12 and 5 monthly payments of 12/- (Total £3.12.0).

All for A.C. Mains 200-250v. 50c/s. **ASSEMBLED 6/12 v. 2 amps.** Fitted Ammeter and selector and variable charge rate selector. Also selector plug for 6 v. or 12 v. Fused, ready for use with mains and output leads and output leads Carr. 3/9. **6/12 v. 1 amp 27/9** Less meter.

### Guaranteed 12 months

**BATTERY CHARGER KITS** Consisting of Mains Transformer F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6 extra.  
 6v. or 12v. 1 amp..... 22/9  
 As above with Ammeter .. 25/9  
 6v. or 12v. 2 amps..... 28/9  
 6v. or 12v. 2 amps, including Ammeter .. 35/9  
 6v. or 12v. 4 amps, with Ammeter and variable charge rate selector .. 52/9

### CHARGER AMMETERS

0-1.5 a., 0-4 a., 0-7 a. 8/9 each.  
**CHARGER KIT, 12v. 10 Amp.** with variable charge rate adjustment and ammeter. 24.19.6. Carriage 10/-.

## R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-250-250 v. 50 c/s. Screened  
**TOP SHROUDED DROP THROUGH**  
 250-0-250v. 70mA, 6.3v. 2a, 0.5-6.3v. 2a 17/9  
 350-0-350v. 80mA, 6.3v. 2a, 0.5-6.3v. 2a 19/9  
 250-0-250v. 100mA, 6.3v. 2a, 6.3v. 1a .. 21/9  
 250-0-250v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 19/9  
 300-0-300v. 130mA, 6.3v. 4a, 0.5-6.3v. 1a, for Mullard 510 Amplifier .. 33/9  
 300-0-300v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 27/9  
 350-0-350v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 27/9  
 350-0-350v. 150mA, 6.3v. 4a, 0.5-6.3v. 3a 35/9

### FULLY SHROUDED UPRIGHT

250-0-250v. 80mA, 6.3v. 2a, 0.5-6.3v. 2a .. 17/11  
 Midget type 2 1/2 x 3 x 3 in. .... 17/11  
 250-0-250v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 28/9  
 300-0-300v. 100mA, 6.3v. 4a, 5v. 3a .. 28/9  
 300-0-300v. 130mA, 6.3v. 4a, C.T. 6.3v. .... 35/9  
 A. for Mullard Amplifier .. 28/9  
 350-0-350v. 100mA, 6.3v. 4a, 0.5-6.3v. 3a 28/9  
 350-0-350v. 150mA, 6.3v. 4a, 0.5-6.3v. 3a 37/9

**FULLY SHROUDED (continued)**  
 425-0-425v. 200mA, 6.3v. 4a, C.T. 5v. 3a 57/9  
 425-0-425v. 200mA, 6.3v. 4a, C.T., 6.3v. 4a, C.T., 5v. 3a .. 59/9  
 450-0-450v. 250mA, 6.3v. 4a, C.T., 5v. 3a 69/9  
**OUTPUT TRANSFORMERS**  
 Midget Battery Pentode 66:1 for 6S4, etc. .... 4/6  
 Small Pentode, 5,000Ω to 3Ω .. 4/6  
 Small Pentode, 7/8, 900Ω to 3Ω .. 4/6  
 Standard Pentode 5,000Ω to 3Ω .. 5/9  
 Standard Pentode 7,000Ω to 3Ω .. 5/9  
 10,000Ω to 3Ω .. 5/9  
 Push-Pull 8 watts, EL84, or 6V6 to 3Ω or matched to 15Ω .. 9/9  
 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-3 to 15Ω .. 19/9  
 Following types for 3 and 15Ω speakers  
 Push-Pull 10-12 watts 6V6 or EL84 .. 18/9  
 Push-Pull 15-18 watts, 6L6, KT66 .. 22/9  
 Push-Pull Mullard 510 Ultra Linear .. 28/9  
 Push-Pull 20 watts, sectionally wound 6L, KT66, EL34, etc. .... 49/9

**MIDGET MAINS TRANSFORMERS** 200-250 v. 50 c/s. 250v. 60mA, 6.3v. 2a. .... 11/9  
 250-0-250v. 80mA, 6.3v. 2a. .... 12/11  
 Both above size 2 1/2 x 2 1/2 in.

### FILAMENT TRANSFORMERS

All with 200-250v. 50 c/s primaries  
 0.9-15v. 11a, 12/8; 0.9-15v. 2a, 14/9; 0.9-15v. 3a, 16/9; 0.9-15v. 6a, 17/6; 12v. 1.5a, twice 17/6.  
**SMOOTHING CHOKES**  
 150mA, 7-10 H. 250 ohms .. 11/9  
 100mA, 10 H. 200 ohms .. 8/9  
 80mA, 10 H. 350 ohms .. 5/9  
 60mA, 10 H. 400 ohms .. 4/11

### CHARGER TRANSFORMERS

All with 200-250v. 50 c/s primaries  
 0.9-15v. 11a, 12/8; 0.9-15v. 2a, 14/9; 0.9-15v. 3a, 16/9; 0.9-15v. 6a, 17/6; 12v. 1.5a, twice 17/6.  
**(Step up/Step down) TRANS.**  
 0-110/120-230/250v. 50-80 watts, 13/9; 250 watts, 49/9; 150 watts, 27/9

**MICROPHONE TRANSFORMERS**  
 120:1 high grade, clamped, 8/9.



BRADFORD, BRISTOL, BIRMINGHAM, DERBY, DARLINGTON, EDINBURGH, GLASGOW, HULL, LEICESTER, LEEDS, LIVERPOOL, LONDON, MANCHESTER, MIDDLESBROUGH, SHEFFIELD

SEE PRECEDING PAGES FOR ADDRESSES.


# BENTLEY ACORN RADIO CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9093

**NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE**

0A2	4/6	6R87	25/-	7A7	12/8	25X5	7/9	AC/PCPN	EAS0	1/8	EL35	10/-	KTW92	5/8	QP25	5/-	U47	8/6	AF124	11/-	
0B2	6/-	6RW6	8/0	7B4	12/6	25X5G	7/9	DD	12/6	EAT6	6/9	EL26	8/9	KTW43	5/6	Q87520	10/6	U50	4/0	AF125	10/6
0ZAGT	4/3	6RW7	5/-	7B7	9/6	25Z4G	7/9	AC/PCEN	ELBC80	5/9	EL57	12/3	KTZ41	5/6	Q8150/10/6	1/2	4/0	AF126	10/6		
1A3	2/0	6RX6	4/-	7C5	8/-	25Z7	7/3	DD	23/3	EAT91	3/3	EL11	7/3	L63	3/-	R10	15/0	U70	4/0	AF127	9/6
1A4	12/6	6RX4	2/3	7C6	6/9	25Z6GT	8/-	AC/PCEN	EAF42	7/6	EL42	7/6	LN192	6/9	R12	5/0	U75	3/9	BYZ18	11/6	
1A5	5/-	6C5	4/-	7C7	5/-	25T10	23/3	AC/PCEN	EBS44	1/-	EL81	8/3	LN309	7/9	R16	29/-	U84	10/6	GB101	5/6	
11AGT	7/9	6R9	5/-	7D2	15/-	2817	6/9	AC/PCEN	EBC11	4/9	EL83	8/9	LN819	8/6	R17	17/6	U101	19/6	G16	10/6	
1C1	4/-	6C8	3/-	7D3	14/6	30C1	6/6	AC/PCEN	EBC19	2/3	EL84	4/6	LP2	9/6	R18	9/6	U107	17/6	GD14	10/-	
1C2	8/-	6C9	10/9	7D6	14/6	30C15	9/-	(7)	17/-	EBC23	20/6	EL85	7/6	LZ19	6/9	R19	6/9	U191	9/6	GET103	7/-
1C3	6/0	6C10	8/0	7H7	5/9	30C18	9/6	AC/SG	22/6	EBC33	6/-	EL89	7/3	LZ29	6/9	R25	7/6	U251	9/6	GET104	10/6
1C3	6/0	6C12	8/0	7H7	12/0	30CFS	5/9	AC/SGVM	EBC40	6/9	EL91	2/6	ME41	13/-	RG3/240A	4/0	U261	8/6	GET105	10/6	
1C8	10/6	6PD9G	12/0	7V7	5/-	32PL1	8/3	AC/PCEN	EBC91	6/-	EL93	5/6	MD1	12/6	84/-	U262	12/3	U262	12/3	GET111	12/6
1D5	6/0	6CH6	5/-	7Y4	5/-	30L1	5/9	ACTH1	15/-	EBC30	3/0	EL360	27/-	MH4	3/6	RGK34	7/0	U301	11/6	GET113	6/9
1D6	9/0	6CW4	24/-	8D2	2/6	30L15	9/3	ACTPT	15/-	EBC91	5/9	EL820	18/4	MHD4	7/6	S130	22/6	U329	9/6	GET114	6/9
1PD1	6/0	6D11	1/4	8BWS	9/6	30P4	12/3	ACTV1	12/-	EBCF0	5/6	EL122	18/6	MHL01210	6/6	SP4B	19/6	U339	9/6	GET115	6/9
1PD9	3/6	6D13	3/0	9D2	3/0	30P12	7/8	ACTV2	29/-	EBCF3	7/3	EL180	13/6	ML84	5/9	SP13C	12/6	U403	5/9	GET116	10/6
1G3	6/-	6D6	5/-	9D7	7/6	30P16	5/3	ATP4	2/3	EBCF9	6/3	EM4	17/9	SP41	2/0	U405	6/9	U405	6/9	GET117	10/6
1HG7	7/9	6E5	9/6	10C1	8/0	-0P19	12/3	AZI	1/6	EBC121	10/6	EM84	12/6	MSP1	12/6	SP12	12/6	U501	18/3	GET118	6/9
1L4	2/3	6F1	9/6	10C2	12/3	30P11	8/0	AZI	6/6	EC52	4/3	EM32	15/6	MS212/14/6	8/6	SP61	2/0	U502	6/9	GET119	6/9
1L4A	17/6	6P6G	3/9	10D1	7/-	30P115	9/6	AZ41	6/6	EC53	12/6	EM71	15/6	MX40	3/9	SP25	27/2	VMP4G	11/6	MA120	8/6
1L4B	16/10	6P6GT	7/6	10D2	11/3	30P114	12/6	B36	4/9	EC54	6/6	EM90	6/3	N37	23/3	T41	9/-	W5M4B	12/6	MA121	8/6
1L4S	4/-	6P7G	6/3	10D3	11/6	35P15	12/6	CI	12/6	EC59	6/6	EM91	6/3	ST2	24/2	T42	9/-	W61	2/0	MA122	8/6
1L5A	4/6	6P8	5/-	10P9	9/9	35P15	12/6	CI	12/6	EC59	6/6	EM94	6/9	N108	26/2	T104	7/6	VP18	3/6	MA121	8/6
1NSGT	8/6	6P11	17/0	10P18	9/9	35A5	20/9	CC/HS	12/6	EC91	4/1	EM85	8/9	N399	15/6	T14B	15/6	VP1	14/6	OA5	6/9
1P1	9/-	6P12	3/0	10L13	6/3	35L6GT	6/6	CC/SGM	6/6	EC92	6/6	EM84	7/8	P41	3/6	T121U	10/6	VP1A	14/6	OA10	6/9
1P10	4/6	6P13	3/0	10L11	9/6	35M4	4/9	CL4	19/6	EC93	7/3	EN31	10/6	P61	10/6	T141	10/6	VP1B	29/-	OA70	7/6
1P11	5/6	6P14	2/3	10L13	6/3	35Z3	6/9	CL33	11/6	EC94	3/6	EN31	5/6	PA1C80	9/9	T142	10/6	VP1C	29/-	OA70	7/6
1R5	4/-	6P15	1/6	10P11	4/6	35Z4GT	4/9	CA	2/6	EC95	29/1	EN51	5/9	PC6	10/3	T22	5/6	VP2	2/0	OA79	3/6
1R4	5/-	6P17	12/6	11D4	17/6	35Z6GT	5/2	CV63	10/6	EC93	21/7	EN71	7/3	PC8	9/6	T25	5/6	VP4	5/6	OA81	3/6
1R5	3/6	6P18	13/6	11D4	17/6	35Z6	12/6	CV85	14/6	EC95	5/6	EN93	9/3	PC93	11/3	T2929	7/6	VP13	9/6	OA85	3/6
1T2	29/-	6P21	9/6	11E1	15/-	39	2/6	CV27	12/6	EC94	4/0	EN94	9/6	PC97	7/3	TY96	11/8	V175	21/-	OA86	4/6
1T4	2/3	6P22	6/3	12A3	2/3	39	2/6	CV28	11/6	EC98	11/6	EN91	5/6	PC98	9/6	TY96	11/8	V175	21/-	OA86	4/6
1U4	5/6	6P22	6/3	12A3	2/3	39	2/6	CV28	11/6	EC98	11/6	EN91	5/6	PC98	9/6	TY96	11/8	V175	21/-	OA86	4/6
1U5	5/3	6P23	3/6	12A	16/6	4181U	15/-	CY1C	6/0	EC93	4/6	EN91	3/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
2A7	12/6	6G6	2/6	12ACG	8/6	42	1/6	CY31	5/9	EC94	5/6	EZ35	4/6	PC98	9/6	UB4	10/6	VT01A	7/6	OA96	3/6
2C6	2/0	6H6	1/6	12A16	9/6	43	10/-	DI	1/3	EC95	5/9	EZ40	5/3	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
2D13G	7/-	6H5G	3/6	12A25	8/6	45	17/6	D15	1/3	EC95	5/9	EZ41	6/1	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
2D21	5/6	6H5GT	4/3	12A17	4/6	45Z6GT	17/6	D42	10/6	EC91	11/6	EZ80	8/9	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
2P	23/3	6J6	3/-	12A18	10/9	50A5	21/10	10B3	5/1	EC97	15/6	EZ91	4/1	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
2X2	3/-	6J7G	4/6	12A79	4/6	50B5	6/6	1077	2/3	EC98	6/6	EZ90	3/9	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3A4	3/9	6J7GT	7/6	12A77	3/8	50C5	6/6	10A92	7/9	EC92	6/3	F02	14/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3A5	5/9	6J8	12/6	12A16	9/6	50CDB0	6/6	10A93	4/1	EC96	11/3	F04	8/9	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3B7	6/-	6K6GT	5/6	12A17	4/6	50L6GT	6/3	10A96	23/6	EC94	23/6	F03	14/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3Q6	3/9	6K7G	1/3	12A16	6/6	52KU	14/6	10C90	9/9	EC93	23/3	F03C	17/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3Q4	5/3	6K7GT	4/3	12A17	4/6	53KU	14/6	10E14	12/6	EC91	9/6	FW4500/6	6/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3Q6GT	7/-	6K8G	3/3	12A17	4/6	53KU	14/6	10E14	12/6	EC91	9/6	FW4500/6	6/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
384	4/6	6K8C/TM3G	12/6	12A19	5/9	57	6/6	10D11	10/6	EC93	22/6	FW4500/6	6/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
3Y4	5/3	6K25	2/6	12A17	4/6	57	6/6	10D11	10/6	EC93	22/6	FW4500/6	6/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
4D1	3/9	6L1	10/6	12B17	6/1	59	5/3	DF3A	8/6	EC94	5/9	GZ30	7/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
4R4G	8/6	6L8G	12/6	12E1	16/9	58	22/3	DF66	15/6	EC93	6/6	GZ32	8/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
5T4	7/-	6L6GT	7/6	12H6GT	2/6	58V3	8/6	DF72	30/6	EC94	9/6	GZ33	17/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
5U4G	4/6	6L7GT/3	5/6	12B17	2/6	58V3	8/6	DF91	2/3	EC98	6/6	GZ34	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6V4G	8/6	6L8G	12/6	12D17	7/3	80AG	6/6	DF99	6/6	EC96	11/3	GZ35	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6Y3GT	4/9	6L19	19/6	12K3	10/6	90AC	4/6	DF97	10/6	EC93	9/6	H30	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
5A4	9/6	6L1D3	6/6	12K7GT	3/6	90AV	8/2	DF130	15/6	EC96	8/6	H30	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
5Z3	7/-	6L1D3	7/6	12K4GT	3/6	90CV	4/2	DH64	4/6	EC91	8/6	HL2	7/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
5Z4	7/6	6L1D2G	5/6	12Q3GT	3/6	90E1	18/6	DH75	3/6	EC96	11/3	HL3C	2/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6 3012	6/0	6L25	2/6	12K6	6/6	130B2	6/3	DF9	6/6	EC96	11/3	HL3D	2/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6AGG	3/9	6P1	9/6	12K7	4/6	150C2	4/6	DH14	23/3	EP9	20/6	HL23D5	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6AG1	6/9	6P25	6/9	12K47	3/6	151	18/-	DH10	25/-	EP22	6/6	HL41	3/9	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6A87	4/-	6P26	9/6	12K17	3/6	15A7B	34/11	10P11	16/11	EP96	3/3	HL41D1D1/2	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6A17	3/-	6P25	11/6	12K87	5/6	21-8G	6/6	DK32	7/6	EP75A	8/6	HL42D1D1/2	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6A65	2/6	6P24	10/6	12K87	7/6	220B	6/6	DK41	15/6	EP9	6/6	HL43D1D1/2	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	3/6
6A67	5/9	6P24GT	7/9	12K87	8/6	301	20/6	DK91	4/6	EF40	8/9	HL43D1D1/2	5/6	PC98	10/6	UB4	10/6	VT01A	7/6	OA96	

# INCREASE YOUR KNOWLEDGE

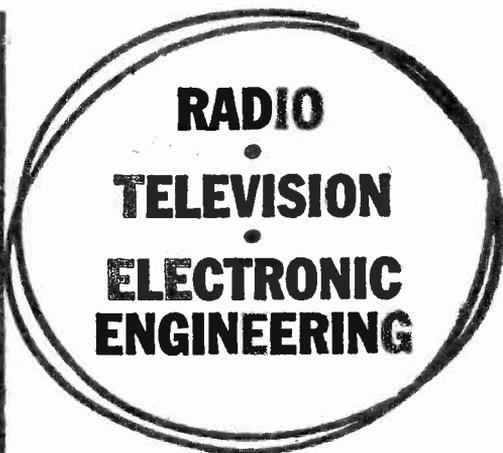

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

### CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING,  
INDUSTRIAL TELEVISION, RADIO AND  
TELEVISION SERVICING, ELECTRONICS,  
COMPUTERS AND PROGRAMMING  
ELECTRONIC TECHNICIANS, SERVOMECH-  
ANISMS, TELEMTRY, COLOUR TV,  
INSTRUMENTATION, AND PRINCIPLES OF  
AUTOMATION.

### ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers  
C. & G. Telecommunication Techns' Cert.  
C. & G. Supplementary Studies  
R.T.E.B. Radio/TV Servicing Cert.  
P.M.G. Cerificates. Radio Amateurs' Exam.

### LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of  
Radio as you build YOUR OWN 5-valve superhet  
Receiver and Transistor, Portable Signal Generator  
and High Quality Multitester. At the end of the course  
you have invaluable practical equipment and a fund of  
personal knowledge and skill. ICS Practical Radio  
Courses open a new world to the keen amateur.

### THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to com-  
plete your technical qualifications, or further special-  
ised knowledge, ICS can help you with a course  
individually adapted to your requirements.

There is a place for you among the fully-trained men.  
They are the highly paid men—the men of the  
future. If you want to get to the top, or to succeed  
in your own business, put your technical training in  
our experienced hands.

ICS Courses are written in clear, simple and direct  
language, fully illustrated and specially edited to  
facilitate individual home study. You will learn in  
the comfort of your own home—at your own speed.  
The unique ICS teaching method embodies the  
teacher in the text; it combines expert practical  
experience with clearly explained theoretical training.  
Let ICS help you to develop your ambitions  
and ensure a successful future. Invest in your own  
capabilities.
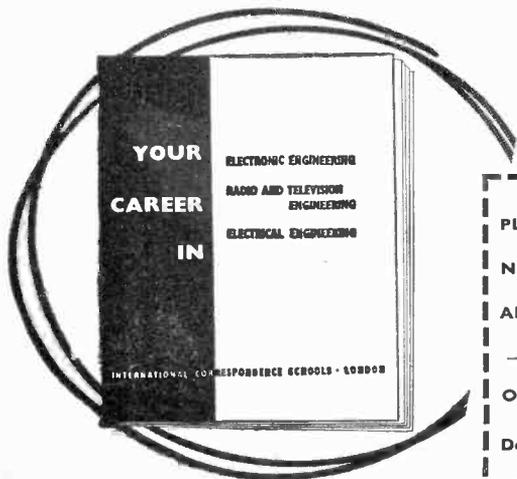
### FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the  
examinations and ICS technical courses in radio, television  
and electronics. PLUS details of over 150 specialised  
subjects.



PLEASE SEND FREE BOOK ON \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

OCCUPATION \_\_\_\_\_ AGE \_\_\_\_\_

INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. 170, INTERTEX HOUSE, PARKGATE RD, London SW11  
3.65

# LASKY'S RADIO

# Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days when the sum paid will be refunded less postage.



**NEW!**

## The SKYROVER Mk II

Now supplied with redesigned cabinet, edgewise controls, new colour tuning scale and cabinet in Sierra Tan. Controls: Waveband Selector, Volume Control with on/off Switch, Tuning Controls. In plastic cabinet, size 10 x 6 1/2 x 3 1/2 in. with metal trim and carrying handle. Can now be **£8.19.6** P. & P. built for 5/- H.P. Terms: 20/- deposit and 11 months at 18/6.

## The "SKYROVER" RANGE

**GENERAL SPECIFICATION:** 7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-64 M. and also 4 separate switched band-spread ranges, 13M, 16M, 18M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.

**SPECIFICATION:** Superhet 470 Kc/s. All Mullard Transistors and Diode Uses 4-U2 batteries, 6in. Ceramic Magnet PM Speaker, Easy to read Dial Scale. Band Spread Tuning, 500 MW Output. Telescopic Aerial & Ferrite Rod Aerial. **WAVEBAND COVERAGE:** 180-576M; 31-94M and Band Spread on 13, 16, 19 and 25 metre Bands.

A simple additional circuit provides coverage of the 1100/1950 M. band (including 1600 M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with detailed construction data. Post **Only 10/- extra** Free. This conversion is suitable for both models that have already been constructed.

## The SKYROVER DE LUXE

Tone Control Circuit is incorporated with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet size 11 1/2 x 6 1/2 x 3 1/2 in. covered with a washable material with plastic trim and carrying handle. Also car aerial socket fitted.

Can now be built for **£10.19.6** P. & P. 5/- H.P. Terms: 25/- deposit and 11 months at 20/-. Data for each Receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All Components Available Separately.



## The "Sixteen" Multirange METER KIT

This outstanding meter was featured by Practical Wireless in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer.

**RANGE SPECIFICATION:** D.C. volts: 0.2-5-25-50-250-500 at 20,000 n/V. A.C. volts: 0.2-5-50-250-500 at 1,000 n/V. D.C. current: 0-50 uA. 0.2-5-50-250 mA. Resistance: 0-2,000 Ohm. 0-200 Ohm. 0-20M Ohm. Basic movement: 40 uA f.s.d. moving coil. With universal shunt full scale deflection current is 50 uA. Size/finish: Black plastic case, 3 1/2 x 5 1/2 x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment rot. meter; meter zero. External connections: Two 4mm. sockets for test lead plugs. Power requirements: One 1.5V. and one 1.5V. batteries. Complete with all parts and full construction details.

Data and circuit available separately 2/6 refunded if all parts bought. Pair of Batteries 2/5 extra.

**LASKY'S PRICE £5.19.6** P. & P. 5/- H.P. Terms: 21/- deposit and 5 months at 21/-.

## THE NEW SINCLAIR SUPER MINIATURES

**THE MICRO-6** Self-contained pocket radio. Size only 1 1/2 x 1 1/2 x 1 1/2 in. A marvel of modern miniaturisation—truly amazing performance. Without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. **59/6** Mercury cell 1/11 extra (2 required). Can be built for only **59/6** All parts sold separately.

## THE SLIMLINE

The new 2-transistor pocket radio. Size only 2 1/2 x 2 1/2 x 1 1/2 in. Micro alloy transistorised and printed circuit. All components available separately. **49/6** Easy to assemble. **CAN BE BUILT FOR 49/6**

## THE X10

10 watt power amplifier fitted with integrated pre-amplifier. Requires only 1 mV. for an output of 10 watts undistorted. Frequency response is flat  $\pm 4$  dB from 5 c/s. to 20 kc/s. Size only 6 x 8 x 3 1/2 in. Weight 5 oz. Built on printed circuit. Operates from 12 v. D.C. at 75 mA. quiescent. Circuit uses **£5.19.6** Free Post. **KIT PRICE £5.19.6** Free Post.

## E.M.I. 4-SPEED RECORD PLAYER

New, unused and individually boxed fitted with lightweight pick-up with ACOS G.P. 73/2 stereo cartridge. Cabinet space required 13 1/2 x 12 1/2 x 4 1/2 in. 1 1/2 in. metal turntable is fitted. For use on 230/250 volt A.C. Mains with Auto-stop. The stereo cartridge will play all types of Mono Records, 7 1/2", 10", 12" etc.

**LASKY'S PRICE 79/6** P. & P. 3/6 extra

## The "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker. ★ All components mounted on a single printed circuit board. ★ Full medium and longwave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue/Grey or all Grey. ★ Easy to read dial. ★ External socket for car aerial. ★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full comprehensive data supplied with each receiver. All coils and I.F.'s etc. fully wound ready for immediate assembly. ★ Outstanding Receiver **LASKY'S PRICE** for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction **£5.19.6** Data. Can be built for P. & P. 5/6



PP9 Batt. 3/9. Data and Instructions separately 2/6. Refunded if you purchase the parcel.

## REALISTIC Seven DE LUXE

With the same specification as standard model—PLUS a superior wood cabinet in contemporary styling. ALSO a full vision circular dial. **FOR ONLY £1 EXTRA** P. & P. as std. model.

## RECORD PLAYERS

45 r.p.m. 6 volt Batt. Operated Complete with pick-up fitted crystal cartridge. Size only 7 1/2 in. x 6 in. Fitted auto. stop and start. New and perfect. **49/6** P. & P. 2/6



2-speed model for 33 and 59/6 P. & P. 45 r.p.m. (as illustrated) 2/6

## TRANSISTORS

**ALL BRAND NEW & GUARANTEED**  
OET 3120; GET S6, 2/6; 873A, 874P 3/6; OC45, OC71, OC81D 4/6; OC44, OC70, OC76, OC81 (match pair 10/6) 5/6; AF17, OC75, OC200 6/6; OC42, OC43, OC73, OC82D 7/6; OC201, OC204 15/-; OC205, OC206 19/6; OC28 24/6.

## TRANSTORISED TELEPHONE AMPLIFIER

Powerfully amplifies the incoming call. The pick-up is suction fixed to phone. Battery-operated at negligible cost. Fitted with on/off switch and vol. control. Size: 4 1/2 x 3 x 1 1/2 in. Complete with PP3 battery. **LASKY'S PRICE 99/6** P. & P. 2/6.

## GUITAR PICK-UPS

**CGM5** Crystal-High Imp. Size only 1 1/2 x 1 1/2 x 1 1/2 in. Clips to finger board—no screws. Complete with cable. **LASKY'S PRICE 15/11** P. & P. 1/-

**CG M35** Fully adjustable pick-up position carrier. Simply fixed. Separate tone and volume control. Heavy chrome finish. Pick-up size 3 1/2 x 1 1/2 in., control size 2 1/2 x 1 1/2 in. Complete with long lead and jack plug. **LASKY'S PRICE 59/6** P. & P. 1/6

# LASKY'S FOR D.C. CONSTRUCTION BARGAINS

# Service in Great Britain to both & HI-FI ENTHUSIASTS

**NOTE! THERE WILL BE NO INCREASE IN OUR PRICES ON IMPORTED GOODS WHILE STOCKS LAST**

## SPEAKER OFFERS !!!

### THE HARROW 12AII

12in. Thin line, two-way speaker. 15 ohms imp. Power Handling 15-20 watts. Rigid die-cast frame. Roll surround. Bulk purchase before import increase enables us to offer this quality speaker at this incredibly low price.

### LASKY'S PRICE

**£4.19.6** P. & P. 5/-



**WHARFEDALE WNA, 12**  
12in.—15Ω impedance. Flux density 14,000 oer/da. Max. input 30 watt peak. Frequency range 25—4,000 c.p.s. Cone fitted with roll surround.

**WHARFEDALE SUPER 5**  
6in.—mid-range and high frequency speaker. 15Ω impedance. Frequency range 300-17,000 c.p.s. Alum-nim voice coil. These two speakers provide an ideal matched pair for a roll range Hi-Fi speaker system. Both brand new and 1/2 dividually boxed.

**LASKY'S PRICE £12.19.6**  
(P. & P. 10/- extra) **THE PAIR**

## THE HARROW CV1 VARIABLE CROSSOVER

Gives variable volume control of Woofer and Tweeter. Strong metal construction. Size 4 x 2 1/2 x 1 1/2in. Screw tax connections.

**LASKY'S PRICE 22/6** P. & P. 1/6.

## NOW IN STOCK THE NEW STUDIO RANGE OF CELESTION HI-FI SPEAKERS

## TRANSISTORISED MICROPHONE MIXER

The Harrow will mix 4 high impedance channels: mikes, tape rec's, tuners, gramms, etc. 9 v. battery operated. Neatly styled, size only 6 x 2 1/2 x 2 1/2in. Standard Jack sockets. Complete with PCB batt., full circuit diagram and operating instructions.

**Model TM4 Mono 59/6** P. & P. 2/6

**Model SM5 Stereo 72/6** P. & P. 2/6

## "HARROW" POWER PACK

Battery eliminator—converts your battery portable to A.C. mains. Replaces 6 v., 4 1/2 v. or 9 v. batteries. Stand voltage required when ordering. Size only 3 x 2 x 2 1/2 in.


**LASKY'S PRICE 29/6** P. & P. 1/6.

## INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

3in. Message tape, 150ft.....	4 11
3in. Message tape, 225ft.....	3 6
3in. Message tape, 300ft.....	7 6
3in. Triple play, 450ft., Mylar base.....	12 6
4in. Triple play, 900ft., Mylar base.....	22 6
5in. Double play, 1,200ft., Mylar base.....	15 0
5in. Long play, 900ft., Acetate base.....	10 0
5in. Standard play, 600ft., P.V.C. base.....	8 6
5in. Triple play, 1,800ft., Mylar base.....	42 6
6 1/2in. Long play, 1,200ft., Mylar base.....	15 0
6 1/2in. Double play, 1,800ft., Mylar base.....	19 6
6 1/2in. Long play, 1,200ft., Acetate base.....	12 6
6 1/2in. Standard play, 850ft., P.V.C. base.....	11 6
6 1/2in. Triple play, 2,400ft., Mylar base.....	55 0
7in. Standard play, 1,200ft., Mylar base.....	12 6
7in. Long play, 1,800ft., Mylar base.....	19 6
7in. Double play, 2,400ft., Mylar base.....	25 0
7in. Long play, 1,800ft., Acetate base.....	15 0
7in. Triple play, 3,600ft., Mylar base.....	75 0

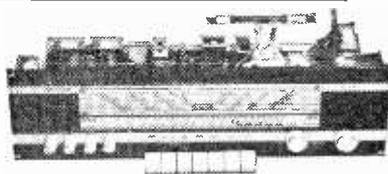P. & P. 1/- extra per reel; 4 reels and over Post Free



eye tuning indicator. Ferrite rod aerial. The very latest printed circuitry. Provision for multiplex-adaptor. 5 valves—line up: ECC85, ECH801, ECH83, EL180, EAF801. Full vision tuning scale, size 2 1/2 x 6in. Over-all dimensions: 21 x 6 1/2 x 8in. Made to the very highest standard.

**LASKY'S PRICE 29 1/2 GNS.**



## THE NEW "KUBA" IMPORTED AM/FM STEREO RADIOGRAM CHASSIS

Long, medium and short waveband coverage plus VHF FM. Piano key wave-change. Separate flywheel tuning on AM and FM. Bass, treble and balance controls. Magic-matrix printed circuitry. Provision for multiplex-adaptor. 5 valves—line up: ECC85, ECH801, ECH83, EL180, EAF801. Full vision tuning scale, size 2 1/2 x 6in. Over-all dimensions: 21 x 6 1/2 x 8in. Made to the very highest standard.

Carriage & Insurance 12/6 extra.

## SUPER TAPE RECORDER OFFER SIEMENS STEREO TAPE RECORDERS

High precision machines offering a maximum of facilities for the enthusiast and composer. Exceptional performance standards ensuring superb reproduction. All models have the following general specification: ● Completely self contained. Record, replay and Audio amplifiers built in. ● All transistorised—no warming up period. ● Three heads—separate record, replay, erase (also provides sound-on-sound recording). ● Three speeds—7 1/2, 3 1/2, 1 1/2 i.p.s. ● 4 tracks. ● Takes 7in. reels. ● Record level indicators on both channels. ● Remote control facilities. Other facilities on these exceptional machines include: push button controls; tape end stop; separate switched bass boost and treble cut; sep. inputs for 2 microphones. 2 radios and 2 pick-ups with provision for mixing 3 inputs. Outputs provided are 2 at 4 ohms; 2 sets headphones; 2 external amplifiers. Power output 2 1/2 watts per channel. All brand new, boxed and fully guaranteed.



**MODEL 12 (illustrated). Self contained portable with 2 built in speakers. Last price 94 gns.**

**LASKY'S PRICE 59 GNS.**

**MODEL 14 built on a contemporary styled wood panel with one built in speaker. Last price 87 gns.**

**LASKY'S PRICE 49 GNS**

Carriage and insurance 15/- extra on each.

## VIKING "TRANSISTOR 50"

50 watt amplifier. Superb amplifier for all music and P.A. work—ideal for guitar, groups etc. Fully transistorised for maximum efficiency. 4 inputs with mixing facilities plus reverb/echo chamber. Bass and treble controls. Fully built and guaranteed. In strong wood cabinet covered in washable material. Size approx. 22 x 10 x 6in. Output imp. 15 ohms. For operation on 200-250v. A.C. mains.




**LASKY'S PRICE 45 GNS.**

Car. & Pack. 10/6
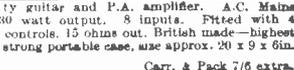
## VIKING "SOUND 30"

High quality guitar and P.A. amplifier. A.C. Mains operated—30 watt output. 8 inputs. Fitted with 4 separate volume controls for mixing also Bass and Treble controls. 15 ohms out. British made—highest quality components used throughout—fully guaranteed. In strong portable case. Size approx. 20 x 9 x 6in.



**LASKY'S PRICE 35 GNS.**

Car. & Pack 7/6 extra.

## MATCHING LOUDSPEAKER SYSTEMS

Will handle up to 50 watts. Suitable for both the "Sound 30" and "Transistor 50". In floor standing enclosure styled to match amplifiers. Fitted with two 12in. special Goodmans Full Range speakers.

**LASKY'S PRICE 33 GNS.**

Car. & Pack 15/-


## THE BH-14 AMPLIFIER

High quality 14 watt power amplifier with bass and treble controls and separate volume controls on each input. Output 3 or 15 ohms. Valve line-up: 2 x EL84, 1 x EF80, ECH83 and EZ81. Frequency res. 15 c/s—20 Kc/s. Ideal for the hi-fi enthusiast or for guitar amplifier. Gold hammer finish with Perspex front panel. Complete kit of parts with detailed construction data. Instruction book avail. sep. 1/6

**LASKY'S KIT PRICE 10 GNS.**

**AVAILABLE READY BUILT AND TESTED**

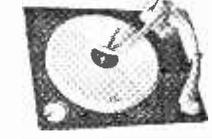**LASKY'S PRICE 12 GNS. Post and Packing 7/6.**



## B.S.R. AUTOCHANGERS—BRAND NEW AT LOWEST EVER PRICES

All brand new and fully guaranteed—complete with cartridge and stylus.

UA16 4 speed, mains.....	\$4.19.6
UA14 4 speed, 9v. battery operated.....	\$5.19.6
UA20 4 speed, mains.....	\$6.19.6

Add 6/- carriage and packing on each.

207 EDGWARE ROAD, LONDON, W.2 | 33 TOTTENHAM COURT ROAD, W.1 | 152/3 FLEET STREET, LONDON, E.C.4  
 Near Praed St. PADDINGTON 3271/2 | Nearest Stn., Gooode St. MUSEUM 2605 | Telephone: Fleet Street 2833  
 BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. X.W., Edgware Rd. | Open all day Thursday. Early closing Sat.

**LASKY'S FOR SPEEDY MAIL ORDER SERVICE**

Brand new individually checked and guaranteed VALVES

Table listing various vacuum tube types and their specifications, including AC/EL, ACPL, AL60, ARS, ARP, etc., with associated numbers and prices.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. All U.K. orders below £1. P. & P. 1/-; over £1, 2/-; over £3, P. & P. 10/-.


MARCONI COMMUNICATION RECEIVERS CR.150. Frequency coverage 2-60 Mc/s in 5 bands. Two lfs 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 dB up to 30 Mc/s and 20-40 dB from 30-60 Mc/s.

CR.150/2. Frequency coverage 1.5-22 Mc/s in 4 bands, all other features as in CR.150. Price £35. Carriage 30/-.

P.C. RADIO S'mains P.S.U. for above, 90/- SEALED HI-SPED SIEMENS RELAYS 1700 x 1700 ohms 15V. P. & P. 1/6.

SIGNAL GENERATOR MARCONI TR 995A-I. Range 1.5-220 Mc/s in 5 bands. Output voltage variable in 1 dB steps from 1uV to 100 mV. Carrier may be unmodulated, frequency modulated, amplitude modulated, or simultaneously frequency and amplitude modulated.

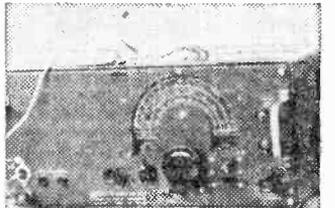WELL PROVEN RELIABLE COMMUNICATION RECEIVER P.C.R.2



(Made by Pye). 12U kc/s-350 kc/s. 525 kc/s-1600 kc/s. 6 Mc/s-22 Mc/s. Overall sensitivity 1-2uV. S/Noise ratio 10 dB at 6uV. Circuit incorporates an RF stage, two i.f. stages, tone control, A.V.C. antenna trimmer, 6V6 output. Set in fully working condition together with headphones and speaker plug, £7.12.6. Carriage 15/-.

Ditto but with built-in power supply for 210-250V. A.C. £9.19.6. Carriage 15/-.

PANEL METERS (round)

Table listing panel meter specifications including microamps ranges (0-100, 0-1000, 0-2000, 0-5000, 0-500 microamps, 0-1 mA, 0-1 mA\*, 0-1 mA, 0-5 mA, 0-100 mA, 150-0.1, 500 mA, 0-15 V, 0-5 V, 0-50 V, 0-150 V, 0-500 V (shunt), 0-10 kV) and their prices.

\*\*"Weston", as usually used in H.R.O. as "S" meter. \*\*Projection type

STABILISED POWER SUPPLY UNIT TYPE 128C (EDISWAN) with 5 independent outputs.

- 1. 0-300v. 150mA m. tered and regulated
2. 0-300v. 75mA metered and regulated
3. 200v. 25mA bias voltage
4. 6.3v. AC CT 4 amps.
5. 6.3v. AC CT 4 amps.
Stability 0.02%. Price £48.


STABILISED POWER SUPPLY UNIT TYPE R.109S (EDISWAN) with 2 independent outputs.

- 1. DC 120-250V. 50mA metered and regulated
2. AC 6.3v. CT 3 amps.
Stability 0.02%. Price £18.


P.C. RADIO LTD
170 GOLDHAWK ROAD, W.12
Shepherd's Bush 946
Open 9-5.30 p.m. Thursday 9-1 p.m.

# Here's vital time-saving data

# to earn money for you!

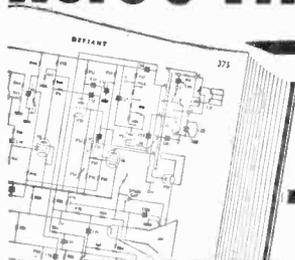


**NEARLY 1,200  
CIRCUITS**

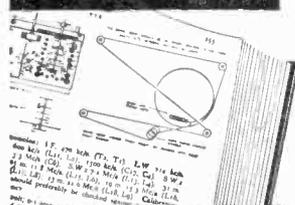

**HUNDREDS OF  
DIAGRAMS**



**PACKED WITH  
REPAIR HINTS**

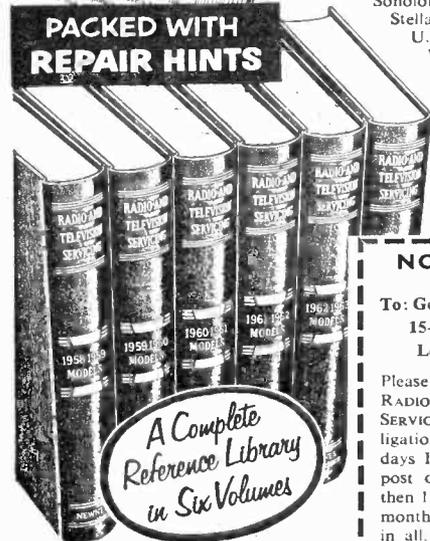

*A Complete  
Reference Library  
in Six Volumes*

## NEW 12th EDITION OF NEWNES RADIO & TV SERVICING

This is the set you **MUST** have to beat the frustration and time loss which fritter away your opportunities to earn more. To-day with the vast number of models needing repair and maintenance, more and more difficult repair jobs will crop up. Yet these complicated jobs become so simple when you have the right information at hand. Here, always ready, is your complete library of data—Newnes famous **RADIO & TV SERVICING**. Nearly 55,000 sets of previous editions have been sold . . . solid proof of its importance to you—the engineer in Radio and TV. You can use this new edition for a week free.

**3,500 PAGES OF REPAIR INFORMATION FOR NEARLY**

# 2,300 Popular Models!

## DATA FOR OVER 90 MAKES 1964 BACK TO 1958

Ace, Aerodyne, Ajax, Alba, Argosy, Baird, Beethoven, Berec, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Doric, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Elpico, E.M.I., Emerson, Emusonic, Eumig, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.B.C., G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, Magnavox, Marconiphone, Masteradio, McMichael, Motorola, Murphy, National, Newmatic, Pageant, Pam, Perdio, Petro Scott, Philco, Philips, Pilot, Playmate, Portadyne, Portogram, Pye, Pye Telecommunications, Radiomobile, Raymond, Recording Devices, Rediffusion, Regentone, Retra, Revelation, R.G.D., Roberts' Radio, Sobell, Sonolor, Sony, Sound, Spencer-West, Standard, Stella, Stereosound, Stuzzi, Thorn, Trans Arena, U.K.W., Ultra, Vidor, Volmar, Walter, Waltham-Standard, Zenith.

- TELEVISION
- RADIO
- RADIOGRAMS
- TAPE RECORDERS
- RECORD REPRODUCERS
- CAR RADIOS

POST COUPON NOW FOR

# 7 days FREE TRIAL

## NO CHARGE FOR CREDIT IF KEPT AFTER FREE TRIAL

*If under 21 your father must fill up coupon.  
If married woman your husband must fill it up.*

To: George Newnes Ltd.,  
15-17 Long Acre,  
London, W.C.2

Full Name \_\_\_\_\_  
(BLOCK LETTERS) (Mr., Mrs., Miss)

Address \_\_\_\_\_

Occupation \_\_\_\_\_

Signature \_\_\_\_\_  
(Mr., Mrs., Miss)

Tick  where applicable

The address on left is —

My Property

Rented unfurnished

Parents' Home


Furnished Accom.

Temporary Address

(RV)41/1095

Please send Newnes RADIO & TELEVISION SERVICING without obligation to buy. In 8 days I will return it or post only 16/- deposit, then 16/- monthly for 20 months, paying £16 16s. in all. Cash in 8 days £16 16s.

**LOUDSPEAKERS**

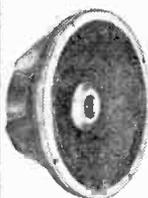

We supply a complete range of Goodmans, Wharfedale, Stentorian, TSL Speaker Units and complete systems. A comprehensive leaflet is available on request this covers technical specifications and prices of

nearly 50 types including:—

- Celestion Model CX1512 (as illustrated) £11.10.0.
- Celestion Model CX2012 £16.10.0.
- Stentorian HF312 5 watts £3.15.0.
- Stentorian HF1012 10 watts £4.12.0.
- Goodmans Axiom 8 6 watts £5.5.7.
- Goodmans Axiom 10, 10 watts £6.5.11.
- Goodmans Axiom 20L, 15 watts £10.17.4.
- Wharfedale Super 5/RS/12/DD 8 watts £6.14.2.
- Wharfedale Golden RS/DD 8 watts £7.17.5.
- Wharfedale RS/12/DD, 15 watts £11.10.0.

Guitar Speakers include:—

- Wharfedale W12EG 15 watts £10.10.0.
- Wharfedale W16EG 20 watts £17.10.0.
- Goodmans Audiom 51B, 15 watts £9.2.8.
- Goodmans Axiom 61B, 20 watts £14.7.8.

Carr. and Ins. extra

**THE TRAVLER MK. II CAR RADIO**

Our ready built transistorised car radio for only

**9½ Gns.**

P. & P. 5/-



including 7 x 4in. speaker fitted to baffle, fixing brackets, filter unit, all nuts and bolts with fitting instructions.

**STAR FEATURES**

★ Handsomely Styled ★ Mullard Valves and Transistors ★ Push Buttons. ★ 1½ watts Output. ★ Long and Medium Wavebands. ★ Quality Speaker (E.M.I.). ★ Easily fitted. ★ Radio Luxembourg (and many other foreign stations). ★ 12-volt Positive Earth only (applies to 99.9% of cars on the road). ★ Dimensions: 7 x 2 x 7in. depth. Optional extras: 3-section chromium plated weatherproof telescopic aerials type 1, 17in./44in. 13/6. Type 2 2in./43in. 29/6, both plus p. & p. 2/6 if purchased separately.

**THE "HIGHWAYMAN" CAR RADIO TO BUILD YOURSELF**

Similar in appearance to above but with on/off push-button switch. Complete set of parts only **£7.19.6** P. & P. 5/-

**MICROPHONES**

Acos Crystal Model MIC 45/1 19/6  
 Acos "Stick" Microphone Crystal.  
 MIC 39/1 32/6. DM.303 Dynamic High Impedance Desk Microphone complete with stand. Metallic Green Finish 5 gns. BM.3 Quality Crystal Microphone with Muting Switch. Complete with Lead, Neck Harness and Removable Stand Adaptor 39/6.  
 Matching Table Stand 12/6 extra.  
 DX.29 Dynamic High Impedance. Black Crackle Finish with Desk Stand 59/6. DM.301 Dynamic High Impedance with On/Off Switch. Omnidirectional. Chrome plated diecast frame 99/6. DM.304 Dynamic Dual High or Low with On/Off Switch. satin chrome finish 89/6. DM.107. Dynamic High Imp. with Switch. Chrome and black enamel finish 69/6.

**MICROPHONE STANDS**

MS.4 3 section floor stand 59/6.  
 MS.8 2 section floor stand 105/6.  
 MS.2 2 section desk stand 22/6.  
 P. & P. 2/6 extra on all above.

**BULK TAPE ERASERS**

DUVIDAL MODEL NT.120. Completely erases old recordings in seconds. Suitable for all sizes up to 7in. 250/250v. A.C. Size 4½ x 3½in. Price 4 Gns. P. & P. 3/6.  
 MODEL NT.178. As above but for all sizes up to 10in. Size 7½ x 4½ x 3½in. Price 5 Gns. P. & P. 4/6.

**TAPE HEAD DEMAGNETIZER**

DUVIDAL MODEL NT.200. Ensures top performance from recorder heads at all times. 250/250v. A.C. Price 29/6. P. & P. 2/6.

**STEREO**

**GREAT BRITAIN'S GREATEST**

**STERN-CLYNE HI-FI EQUIPMENT**  
 Ready built or Kit of Parts

	Complete Kit of parts	Ready built and tested	Carr. and Ins.	Instruction book available separately
Stern Mono-Gram Amplifier 3 watts.....	£4 10 0	£6 0 0	3/6	2/6
Mullard 2 valve Audio Pre-amplifier.....	£6 6 0	£9 10 0	5/-	2/-
Mullard 3 valve Audio Pre-amplifier.....	£10 0 0	£13 13 0	5/-	3/6
Mullard "3-3" Amplifier with Tone Control Unit 33/RC 3 watts	£8 8 0	£11 10 0	6/6	2/-
Mullard "5-10" Main Amplifier Model 51/0/M, 10 watts.....	£10 0 0	£13 10 0	6/6	2/-
Mullard "5-10" Amplifier with Tone Control Unit, 10 watts.....	£12 0 0	£16 0 0	7/6	2/-
Stern Twin Three Stereo Amplifier, 3 watts per Channel.....	—	£9 0 0	5/-	—
Stern Twin Three Stereo Amplifier in Portable Case with Two Speakers and Leads.....	—	£16 10 0	10/-	—
Mullard "10+10" Stereo Amplifier, 10 watts per Channel.....	£16 0 0	£20 0 0	8/6	—
Mullard "10+10" Stereo Amplifier with Passive Control Unit.....	£20 0 0	£24 0 0	10/-	3/-
Mullard Dual Channel Pre-amplifier.....	£12 10 0	£16 0 0	7/6	3/-
The above two items purchased together.....	£27 0 0	£34 0 0	15/-	—
Mullard 4-channel Electronic Mixer Unit Model 2H for 2 Mics. Radio and Gram.....	£8 8 0	—	5/-	2/6
Mullard 4-channel Electronic Mixer Unit Model 1L.....	£10 5 0	—	5/-	2/6
HF/TES Tape Amplifier with Power Unit.....	£13 13 0	£19 0 0	7/6	3/-
Type "C" Tape Pre-amplifier with Power Unit.....	£14 0 0	£19 10 0	7/6	3/6
STP-1 Tape Pre-amplifier with Power Unit, Mono and Stereo.....	£22 0 0	£28 0 0	8/6	5/-
CR3/8 Tape Recorder with Studio Deck.....	£33 8 0	—	15/-	3/-

INDIVIDUAL DESCRIPTIVE LEAFLETS GIVING TECHNICAL SPECIFICATIONS, DIMENSIONS, PRICES, TERMS, ETC. FREE ON REQUEST

**TAPE EQUIPMENT AND ACCESSORIES**

**AMERICAN ACETATE TAPE**  
 5in. 600ft. Standard 8/6  
 5in. 900ft. Long Play 10/-  
 5½in. 1,200ft. Long Play 12/6

**AMERICAN MYLAR TAPE**  
 3½in. 600ft. Double Play 11/6  
 7in. 1,200ft. Standard Play 12/6  
 5in. 1,200ft. Double Play 15/6  
 7in. 1,800ft. Long Play 20/-  
 5½in. 1,800ft. Double Play 22/6  
 7in. 2,400ft. Double Play 25/-

**BEL CLEER ACETATE TAPE**  
 5in. 600ft. Standard 12/6  
 5in. 900ft. Long Play 15/-  
 5½in. 1,200ft. Long Play 18/6  
 7in. 1,200ft. Standard 19/6  
 7in. 1,800ft. Long Play 25/-  
 Postage and Packing 1/- per Reel extra, 4 or more Reels POST FREE.

**FULLY AUTOMATIC TAPE SPLICER**  
 14/6. P. & P. 1/6.

**PLASTIC TAPE SPOOLS** 2½in. 1/-; 3in. 1/8; 4in. 2/-; 5in. 2/-; 6½in. 2/3; 7in. 2/6.

**PLASTIC SPOOL CONTAINERS.** For spool sizes 6in. 1/8; 5½in. 2/-; 7in. 2/8. Any single item plus 6d. P. & P. Orders over £1 post free.

We carry fully comprehensive stocks of Tape Recorders, Decks and Accessories at all Branches or order with confidence by mail.

**RECORD PLAYERS**



Garrard SRP10 Single Player £5.9.1. Carr. and Ins. 4/6. BSR UA15 Auto-changer £5.19.6. Garrard Antoslim Autochanger #8.10.0. Garrard AT6 Autochanger #10.19.6. BSR Super Slim Autochanger #8.19.8. Garrard AT5 LM Autochanger (3000LM) #11.11.11. Philips AG1016 Stereo/Mono Record Player #12.12.0.

Carriage and Ins. 5/- on above.

Garrard 4HF Single Player #16.17.6. Goldring Lenco Model 88 Transcription Turntable #18.18.5. Garrard Laboratory Type "A" Autochanger #19.15.0. Garrard 301 Strobe Transcription Turntable #22.0.1. Goldring Lenco GL58 with 580 Cartridge #21.19.0. Goldring Lenco GL70 less Pick-up Head #27.9.4.

Carr. and Ins. 7/6 on above.

Descriptive leaflet including prices with alternative cartridges, dimensions, terms etc., free on request.

**NEW LOW PRICE COMMUNICATION RECEIVERS**



Model HE 40. Frequency range 550 Kc/s-30 Mc/s in 4 bands. PRICE #19.19.0. Carr. 10/-.

Model HE 30. Frequency range 550 Kc/s-30 Mc/s in 4 bands. PRICE #24.13.0. Carr. Paid.

Model KT 320. Specification as HE-30 but offered as complete kit of parts. PRICE #26.5.0. Carr. Paid.

Model HE ED. Frequency range 540 Kc/s-30 Mc/s and 142-148 Mc/s in 5 bands. PRICE #61.19.0. Carr. Paid.

Model HA #3. Frequency range 550 Kc/s-31 Mc/s in 4 bands. PRICE #25.4.0. Carr. Paid.

Starlite 80 Wa 4 Transmitter  
Band coverage 80 - 40 - 20 - 15 and 10 Metres.  
PRICE #30.9.0. Carr. 15/- (H.P. Terms available).  
Send S.A.E. for fully descriptive brochure.

**TUNER UNITS**



ARMSTRONG Mono/Tuner Amp. Model # 127M #28.10.0.  
Stereo/Tuner Amp. Model 127 #37.10.0.  
AM/FM Tuner Model #23, #28.15.0.  
FM Tuner Model #24 #22.10.0. Carr. and Ins. 7/6.

STERN FIDELITY Mk. II VHF/FM Built and Tested #14.5.0. Carr. and Ins. 5/-.

**JASON**

FMT1 FM Tuner, Kit of Parts #6.15.0.  
FMTE FM Tuner, Kit of Parts #10.12.6.  
FMT3 FM Tuner for Fringe Areas. Kit of Parts #15.5.0.  
FMT4 FM Tuner #20.0.4.  
JTV2/FM/TV Sound, Kit of Parts #15.15.0.  
Carr. and Ins. on above 5/- each.

**TRIPLETONE**

FM Tuner unpowered, #13.19.6.  
FM Tuner Self-powered, #15.14.6.  
Carr. and Ins. 5/- each.  
Descriptive leaflets free on request. Please state model required.

**STERN-GLYNE**

**ELECTRONIC HOBBIES ORGANISATION**

**DOUBLE FEATURE PRE-AMPLIFIER**



Inputs for microphone, crystal or magnetic pick-ups. tuner unit, and in addition offers full facilities for tape recording and high fidelity replay.

This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck. Push-button switching for 3 tape speeds equalised.

KIT OF PARTS 11 GNS. (Carr. & Ins. 5/-)

**JL10 POWER AMPLIFIER**



Incorporates the latest diode/pentode ECL86 valves in push-pull PARTRIDGE ultra linear output transformer, PARTRIDGE mains transformer and smoothing choke. 10 watts

power output, surplus power output, surplus power available for tuner.

KIT OF PARTS 91 GNS. BUILT AND TESTED 12 GNS. (Carr. & Ins. 7/6)

Prices if both units purchased together: KIT OF PARTS 191 GNS. BUILT AND TESTED 26 GNS. (Carr. & Ins. 10/-)

**VISIT YOUR NEAREST STERN-GLYNE ELECTRONICS CENTRE**

**LONDON**

18 Tottenham Court Road, W.1. MUSEUM 5929/0055. Half Day Saturday.  
23 Tottenham Court Road, W.1. MUSEUM 3461/2. Half Day Thursday.  
309 Edgware Road, W.2. PADDDINGTON 6953. Half Day Thursday.  
109 Fleet Street, E.C.4. FLEET STREET 5819/5. Half Day Saturday.  
162 Holloway Road, N.7. NORTH 7941. Half Day Thursday.  
9 Camberwell Church Street, S.E.5. RODNEY 2875. Half Day Thursday.

**CROYDON**

12 Suffolk House, George Street, MUNICIPAL 3250. Half Day Wednesday.

**BRISTOL**

26 Merchant Street, Bristol 1. Bristol 20261. Open 6 days a week.

**LIVERPOOL**

52 Lord Street, Royal 7450. Open 6 days a week.

**MANCHESTER**

20/22 Withy Grove, Manchester 4, BLACKFRIARS 5379/5246. Open 6 days a week.

**SHEFFIELD**


125 The Moor, Sheffield. Sheffield 28993. Half Day Thursday.

**MAIL ORDERS AND ENQUIRIES TO**


Dept. P.W. 3/6 Eden Grove, Holloway, London N.7. NORTH 8161/4.

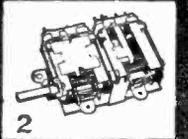**NORTH LONDON CUSTOMERS NOTE!**

Come and see our New Self Service facilities at 162 Holloway Road Branch



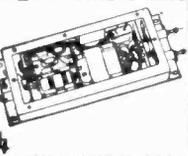3 to 4 watt Amplifier Kit comprising chassis 8½ x 2½ x 1in. Double wound mains transformer, output transformer, volume and tone controls, resistors, condensers etc. Valves 6V6, ECC81 and metal rectifier. Circuit 1/6 free with kit. 29/6 plus 4/- P. & P.



1. \* VALVE 15 WATT PUSH-PULL AMPLIFIER, 15 x 17 x 1½in. A.C. Mains 200-250 volts, 4 inputs with controls for same and bass and treble lift controls. Tapped for 3 and 15 ohm speakers. Extra H.T. and L.T. for F.M. Tuner supplies etc. Built and tested. 7 gm. P. & P. 12/6.

2. GYLDON A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION. Size 2½ x 2½in. approx. By famous manufacturer. A.M. I.F. 470 Kc/s. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-525 Kc/s. F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagrams 2/6. FREE with Tuner, 1st, 2nd, 3rd A.M. I.F.'s, 1st, 2nd, 3rd and 4th F.M. I.F.'s v.H.F. Osc. choke, A.M. I.F. trap, A.F. 114 and A.F. 115. All the above are the R.F. end of an A.M./F.M. receiver car radio etc. The above six items. £2.10.0.

3. AMPLIFIER KIT.

4. TRANSISTOR INVERTOR, 50 v. D.C. Input. Output 240 v. A.C. 40 watts incorporating transformers, choke, condensers and 2 Gel573. In solid 16 gauge aluminum case size 15 x 6 x 2½in., by famous manufacturer. 10/6, plus 6/- P. & P.

5. FLUORESCENT LIGHT FITTING. Twin 40 watt 200/250 v. less tubes 50/6. P. & P. 6/-.

6. SIGNAL GENERATORS: Cash £75.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6½ x 3½in. Three miniature valves and Metal Rectifier. A.C. mains 200/250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 multivolts, C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.

7. A.C. MAINS MOTOR. Can be used for a variety of purposes, silent running satisfactory in every way. 230/250 v. A.C. 9/6. P. & P. 2/-.

8. POCKET MULTI-METER. Size 3¼ x 2¼ x 1¼in. Meter size 2¼ x 1¼in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts, 0-15 0-150, 0-1000. D.C. current 0-150 mA. Resistance 0-100K Ω. Complete with test leads, battery and full instructions. 39/6 P. & P. 2/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

9. CHANNEL TUNER LF. 16-19 Mc/s. Continuously trimable from 174-216 Mc/s. Valves required—PCF80 and PCX84 (in series). Cover RBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker 10/-, P. & P. 3/-.

10. The MOTORISTS' REV. COUNTER. Kit of parts comprising 270 degree 3in. moving coil movement. Manufacturer's present price of this movement would be at least £7. Complete with full instructions and circuit diagram. Scale/calibrated up to 8,000 r.p.m. Can be used with any 4 or 6 cylinder car. 49/6, plus 3/6 P. & P.

11. B.S.R. MONARCH UA14 WITH FULL FI HEAD. 4-speed, plays 10 records, 12in., 10in., 7in. at 16, 33, 45 or 78 r.p.m. Internix 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions: 12¼ x 10½in. Space required above baseboard 4½in., below baseboard 2½in. Fitted with Full FI turnover crystal head, £5.18.6. P. & P. 6/6.

12. 50 MICRO-AMP METER movement by world famous manufacturer. Size 3 x 2½in., 25/-, plus 1/6 P. & P.







13. 8-watt PUSH-PULL 5 VALVE AMPLIFIER, A.C. mains 200-250v. Size 10½ x 9½ x 2½in. 5 valves with all makes and types of pick-ups and mike. Negative feedback. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kc/s. 2 dB down to 20 Kc/s. Output 8 watts at 5 per cent total distortion. Note level 40 dB down all burn. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or I.F. records, musical instruments such as guitars, etc. Suitable for small halls. £3.18.6. P. & P. 7/- Crystal mike to suit, 15/-, P. & P. 2/- 8in. P.M. Speaker to suit, 12/6, P. & P. 2/-.

14. FLUORESCENC LIGHT KIT. Twin 20 choke instant start, complete with 4 bi-pin 200/250 v. holders, 11/8. P. & P. 4/- Twin 40 choke instant start with 4 bi-pin 200/250 v. holders, 17/6. P. & P. 4/-.

15. RINGO BURGLAR ALARM SYSTEM. A.C. mains, 200/240 volt. Fire salvage slightly tarnished. List price 7 gm. Our price, complete with double gong bell five micro switches and full instructions, 48/6. P. & P. 4/-.

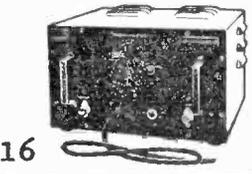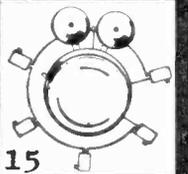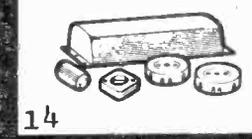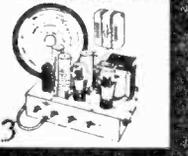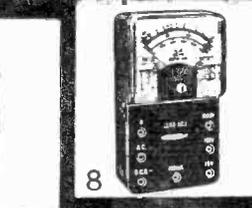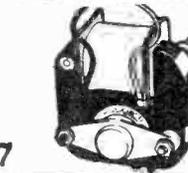16. FIXED FREQUENCY SIGNAL GENERATOR. Crystal control in metal case size 10 x 6 x 6in. Incorporating two PC13 valves, mains transformer, metal rectifier, choke, indicator lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new. 39/6, plus 6/- P. & P. A.C. mains 200-250 volts.

SILICON RECTIFIERS. 250 v. P.I.V. 750 mA. Six for 7/6 post paid.



**RADIO & T.V. COMPONENTS (ACTON) LTD.**  
21b High Street, Acton, London, W.3.

All enquiries S.A.E. Goods not despatched outside U.K.  
Shop hours 9 a.m.—6 p.m. Early closing Wednesday

# SPECIAL OFFER! FROM R. & T.V. LTD.

*Elegant Seven*

## COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features  
4in. SPEAKER


- ★ 7-transistor superhet. Output 350mW.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 11½ x 2⅝ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 K/c/s.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

ONLY  
**£4.19.6**

Plus 5/6 P & P. Parts list & circuit diagram 2/6. FREE with parts


SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts incorporating mains transformer etc. A.C. mains 200-250v. Output 9v 100mA 7/6.

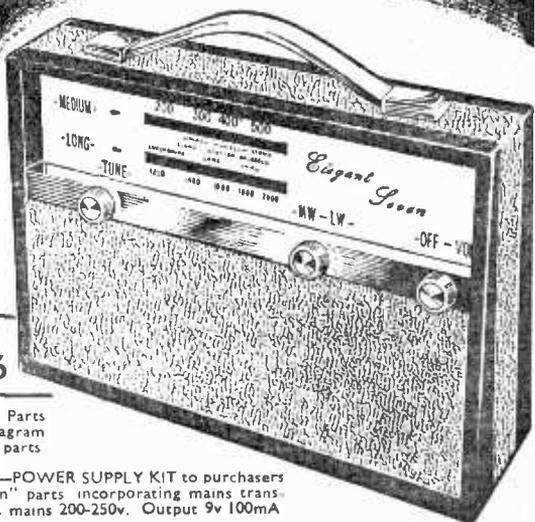Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O


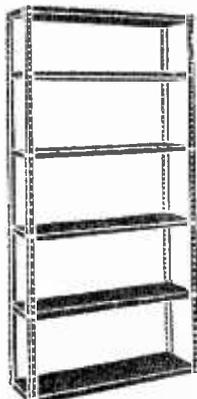
## RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed.



## STEEL SHELVING

BRAND NEW

C.W.O. or C.O.D. FREE DELIVERY within 14 days. N. Scotland, Ireland I.O.M. 10% extra.

**65/-**

71in. high x 34in. wide 12in. deep with 6 shelves as illustrated.

Each shelf will hold over 3 cwt. Shelves adjustable every 2 in. Stove enamelled dark green. White enamel units 50% extra.

Height	Width	Depth	No. of shelves	Price	Price each 3 or more	Extra shelves
71 in.	34 in.	9 in.	6	68/-	61/-	7/-
71 in.	34 in.	12 in.	6	65/-	63/-	8/-
71 in.	34 in.	18 in.	6	74/-	72/-	9/6
71 in.	34 in.	18 in.	6	86/-	84/-	11/8
85 in.	34 in.	12 in.	6	73/-	71/-	8/-
85 in.	42 in.	12 in.	6	91/-	89/-	11/-

Contractors to H.M. Govt. and United Kingdom Atomic Energy Authority. Exporters of Steel Shelving.

Buy direct from the manufacturers

**ROCHDALE METAL PRODUCTS**  
WATERFOOT — LANCS  
Dept. P.W.  
Phone: Rossendale 2450

## BARGAINS FROM BROADWAY ELECTRONICS

GARRARD A.T. 6 Hi-Fi Autochanger G.C.8 mono cartridge—£9.18.6, post free.

GARRARD AUTOSLIM 4 speed changer—£6.10.0, post free.  
12in. ALTHAM SPEAKER with built in tweeter 3 ohm or 15 ohm 7,000 Gauss Magnet. Only 29/6, postage 3/6.

HAYDON CABINET (17 x 15 x 8in.) designed to take a 12in. Heavy Duty Speaker. 50/-, postage 7/6.

The Famous B.M.E. XTAL MICROPHONE with neck lanyard 30/- table stand for above 9/6 extra. Xtal insert 7/3.

GUITAR PICK-UP complete with clip and screened lead—12/6.

3-WAY PUSH BUTTON UNITS Each button operates a 4-pole 2-way switch—4/6.

BARGAINS IN TRANSISTORS Mullard RF Packs OC44 two OC45, 12/6; AF Packs OC81D two OC81, 8/8; OC44, 3/6; OC45, 3/-; OC71, 2/6; OC72, 3/-; OA81 diode 2/3; OC170, 6/6; AF 117, 6/6; ORP12, light cell, 7/6; OC23, 12/6; OC35, 12/6.

TRANSISTOR ELECTROLYTICS 1, 2, 4, 5, 8, 10, 15, 32, 50, 100 Mfd. all at 15 volts—1/3 each.

McMICHAEL TELESCOPIC TV AERIAL 23in. extends to 45in., fitted with coax plug, will suit any set. Only 7/6.

CARTRIDGES Acos 87-1G Low Output, 87-2G Medium Output G.P.59-5 High Output, Garrard GC2 or GC8 all with mounting bracket 15/6.

Ronette Stereo with mounting bracket, 25/-.

EARPIECES with cord and 3.5mm plug. 8 ohm magneto 3/-; 250 ohm, 4/-; 180 ohm magnetic with clip 6/6; Xtal. 4/-; 3.5mm plugs with nice long shank complete with 'jack', 3/-.

3.5mm plugs with nice long shank complete with 'jack' SCREENED, 4/-.

TOGGLE SWITCHES Single pole with on/off plate. 2/6.

NEON PANEL LIGHTS 240v. A.C. Arcoelectric, 2/6.

TERMS: C.V.O. OR C.O.D.

## BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3984  
(four minutes from Tooting Broadway Underground Station)

# SURBITON PARK RADIO LTD.

ALL ORDERS DESPATCHED SAME DAY ● WE PAY POSTAGE AND INSURANCE  
MONEY REFUND GUARANTEE

## LEADING STOCKISTS OF MARTIN RECORDAKITS AND AUDIOKITS

### MARTIN RECORDAKITS

	Dep.	&	Mthly. pmt. of
<b>HALF TRACK</b>			
TAPE AMPLIFIER FOR STUDIO DECK with ready wired printed circuit control and input panels, mains and output transformers, knobs, plans, screws, etc. EF86, ECC83, EZ80, EM85 and 2 EL84. 3 watts output. Magic eye. Radio and Mic. inputs. Ex. speaker socket. Tone and Monitor controls. Can be used as an amplifier. . . . .			
COLLARO STUDIO DECK. Very latest model. 3 speeds. 3 motors and 7-in. spools. . . . .	47/-	8	25/0
CASE for above with 8 x 5in. speaker. two-tone grey . . . . .	44/-	8	24/6
COMPLETE KIT with tape and microphone. . . . .	120/-	12	44/-
<b>QUARTER TRACK</b>			
TAPE AMPLIFIER FOR STUDIO DECK as above . . . . .	52/-	8	27/6
CASE as above with speaker. two-tone grey . . . . .			
COLLARO STUDIO DECK fitted Marriot "X" series heads . . . . .	56/-	12	20/6
COMPLETE KIT with tape and microphone. . . . .	136/-	12	49/10
<b>TAPE PRE-AMPLIFIERS</b>			
HALF TRACK for STUDIO deck. 400 mV out . . . . .	34/-	6	25/8
QUARTER TRACK as above . . . . .	39/-	6	28/4
<b>TAPE HEADS</b>			
BEADMATIC Half track Record/Playback and Erase on plate . . . . .			£1.19.6

### MARTIN AUDIOKITS

	Dep.	&	Mthly. pmt. of
NOW—MARTIN AUDIOKIT F.M. TUNER. Units Nos. 15, 16 and 17 come to . . . . .	51/6	12	18/10
We show only the popular units here. Others are available. Leaflet upon request.			
UNIT 1. FIVE INPUT SELECTOR. Size 3 1/2 x 3in. Mag. P.U., Crystal P.U., Radio, Mic Tape head. 9-15 Volts. Must be used with Unit 4 . . . . .			£2. 7.6
UNIT 4. PRE AMPLIFIER AND CONTROL. Size 6 1/2 x 2 1/2in. Volume on/off, Bass and Treble control 9-15 Volts. Must be used with Unit 1 . . . . .			£3. 2.0
UNIT 7. MAIN AMPLIFIER. 10 watts. 6-transistor Transformerless. Push-pull output. Mounted on Heat sink. 15 ohms output. 40 Volts supply . . . . .			£6. 12.6
UNIT 8. POWER SUPPLY. Gives 9 and 40 Volts. Heavy duty transformer, rectifier and smoothing £2.15.0 CONTROL PANEL (for Units 1 and 4) . . . . .			10.6
ALL FOUR ABOVE UNITS WITH PANEL to make a 10 watt 15 ohms amplifier. . . . .	62/-	12	22/6
UNIT 5. MAIN AMPLIFIER. As Unit 7 but 3 ohms output. 24 Volts . . . . .			£5. 12.6
UNIT 6. POWER SUPPLY. As Unit 8, use with Unit 5 . . . . .			£2. 12.6
ALL FOUR UNITS 1, 4, 5 & 6 WITH PANEL. 3 ohms output. . . . .	57/-	12	20/10
STEREO VERSIONS NOW AVAILABLE, LEAFLET UPON REQUEST.			

## NEW ARMSTRONG TUNERS AND AMPLIFIERS



Model 222	Model 223		
● TUNERS, SELF-POWERED			
224 F.M. . . . .	£92.10.0 90/- 12 33/-		
228 A.M./F.M. . . . .	£28.15.0 115/- 12 42/2		
● TUNER/AMPLIFIERS, MONO			
127 A.M./F.M. with 5 watt amp . . . . .	£26.10.0 106/- 12 38/10		
227 A.M./F.M. with 10 watt amp . . . . .	£36.15.0 147/- 12 53/-		
● TUNER/AMPLIFIERS, STEREO			
127 A.M./F.M. with 5+5 watt amp . . . . .	£37.10.0 150/- 12 55/-		
227 A.M./F.M. with 10+10 watt amp . . . . .	£52.15.0 211/- 12 77/4		
226 A.M./F.M. with 10+10 watt amp . . . . .	£56. 0.0 214/- 12 82/1		
● STEREO AMP 222 10+10 WATT . . . . .	£27.10.0 110/- 12 40/4		
SHIELD MOUNTING TRAK CASE £9.10.0 EXTRA. ALL MODELS. SEND FOR NEW LEAFLET GIVING FULL TECHNICAL DETAILS.			

### F.M. TUNERS

TRIPLETONE F.M. TUNER. Least power . . . . .	46/-	12	20/6
TRIPLETONE F.M. TUNER. With power . . . . .	63/-	12	23/1
JASON JTV2 F.M. and T.V. sound. Switched, self-powered . . . . .	89/-	12	32/7

## GRAMOPHONE UNITS

NEW BSR UA25 with Mono cart. . . . .	£6. 6.0	—	—	—
GARRARD SRP10. Single player. Mono cart. . . . .	£5.10.0	—	—	—
GARRARD AUTOSLIM. 4 speed changer. Mono £6.12.6				
GARRARD AT6 AUTOSLIM DE LUXE. Mono £10.10.0	42/-	8	23/6	
GARRARD AT7/5 Improved Autoclim (Stereo) . . . . .	36/-	6	17/4	
GARRARD AT7/3000 LM as AT 6 with slim arm (Stereo) . . . . .	96/8	8	26/9	
GARRARD "DECCADEK" Single Player with Decca Deram Cartridge . . . . .	£11.12.0			
GARRARD 4FE Transcription Unit. Mono . . . . .	£15.15.0	63/-	12 23/1	
GARRARD LAB "A" Transcription changer . . . . .	£17. 0.0	68/-	12 24/11	
GARRARD 301 STROBE Transcription unit . . . . .	£19.14.9	79/-	12 28/11	
PHILIPS AG106. Stereo cartridge will change 7in. records with adaptor 10/- extra. . . . .	£22. 0.0	88/-	12 32/3	
GOLDRING GL58 with arm but less cartridge. . . . .	£12.12.0	50/6	12 18/6	
GOLDRING GL70 with arm but less cartridge. . . . .	£17. 1.0	69/-	12 24/11	
GOLDRING "88" Transcription. less arm . . . . .	£27. 9.4	111/4	12 40/1	
	£18.18.5	76/5	12 27/8	

## MONO AMPLIFIERS

LINEAR L45A 3 valve. 3 watt . . . . .	£6. 6.0		
DULCI GA5 Integrated. 5 watts. ECL86 valve 1/2 EL84 . . . . .	52/8	12	19/3
TRIPLETONE HI-FI MAJOR 10 watts output. 2 EL84 . . . . .	£15.18.9	64/9	12 23/3
LEAK TL12 10 watt MAIN AMPLIFIER . . . . .	£20. 0.0	80/-	12 29/4
LEAK VARISLOPE Mono Pre-amplifier . . . . .	£15.15.0	63/-	12 23/1
DULCI DPA15 15 watt with 2 valve Pre-amp. . . . .	£26.5.0	105/-	12 38/8

## STEREO AMPLIFIERS

ROGERS GADE Mk II with P.A. . . . .	£26.15.0	107/-	12 39/3
LEAK TRANSISTOR STEREO 30 P.A. . . . .	£20.10.0	198/-	12 72/7
LEAK STEREO 20 P.A. and main amplifier . . . . .	£55. 9.0	229/-	12 80/8

## HI FI LOUDSPEAKERS

GOODMANS AXIETTE 8-inch . . . . .	£5. 5.7		
GOODMANS AXIOM 10 inch . . . . .	£26. 5.11		
GOODMANS 5K 20 XL Tweeter and crossover £7. 7.0			
GOODMANS 50600 £2.0.11. X0650. £5.10.11			
GOODMANS 210 12in. unit. Full range. 15 watt £10.17.8	43/6	8	24/3
GOODMANS 301 12in. unit. Full range. 20 watt 15. 4.6	81/-	12	23/4
GOODMANS "MAXIM" . . . . .	£17.10.0	70/-	12 25/8
W.B.HF1012 10in. unit 3.75, 7.5 & 15 ohms . . . . .	£4.12.0		
WHARFEDALE SUPER 3 Tweeter . . . . .	£5.16.8		
WHARFEDALE SUPER 5 Tweeter . . . . .	£5.19.7		
WHARFEDALE SUPER 8 RS/DD . . . . .	£6.14.2		
WHARFEDALE SUPER 10 RS/DD. Full range £10.18.0	44/-	8	24/3
WHARFEDALE RS12/DD 12in. unit. Full range . . . . .	£11.10.0	46/-	8 25/6
WHARFEDALE SUPER 12 RS/DD . . . . .	£17.10.0	70/-	12 25/8
LEAFLETS BY WHARFEDALE AND GOODMAN ON REQUEST.			

## GUITAR SPEAKERS

FANE L 12in. Heavy duty unit. 20 watt. . . . .	£5. 5.0		
WHARFEDALE W12 EG 12in. 15 watt LEAD £10.10.0	42/-	8	23/6
WHARFEDALE W15 EG 15in. 15 watt BASS £17.10.0	70/-	12	25/8
GOODMANS AUDIOM 51 12in. 15 watt BASS £9. 2.8	36/8	6	27/8
GOODMANS AUDIOM 61 12in. 20 watt LEAD or BASS £14. 7.8	57/8	12	21/1
GOODMANS GUITAR Speaker Audiom 81-15in. £25. 0.0	100/-	12	36/8
GOODMANS AUDIOM 51 15in. 15 watt BASS £27.10.0	110/-	12	40/4
WRITE FOR GOODMAN'S LEAFLET "LOUDSPEAKERS FOR ELECTRIC GUITARS."			

## GUITAR AMPLIFIERS

LINEAR DIATONIC 12 watt 2 inputs . . . . .	£13. 2.6	52/6	12 19/3
LINEAR CONCORD 30 watt with COVER . . . . .	£19. 4.6	77/-	12 25/2
RESLO Heavy with Pre-amp. 25 watt . . . . .	£7. 6.0	160/-	12 41/11
LEAK TL50 with Pre-amp. 50 watt . . . . .	£51. 5.0	205/-	12 75/2

## MICROPHONES AND FLOOR STANDS

RESLO RBH T Ribbon . . . . .	£11. 2.6	44/0	8 24/9
RESLO RBH TS Ribbon with on/off switch . . . . .	£13.10.0	54/-	12 19/9
RESLO Heavy with Duty Floor Stand . . . . .	£7. 6.0	160/-	12 41/11
TEISCO DM304 Dual impedance with switch . . . . .	£4.10.0		
PIEZO BM3 Crystal with switch . . . . .	£2.10.0		
JAP: FLOOR STAND . . . . .	£3. 3.0		

EASILY REACHED BY FREQUENT TRAINS FROM WATERLOO TO SURBITON

# SURBITON PARK RADIO LTD.


48, SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

Phone: KIN 5549

- Order for Cash. C.O.D. or Terms.
- Hours 9 a.m.-6 p.m. (1 p.m. Wed.)
- Open Lunch Time and all day Sat.

FOR PEAK PERFORMANCE AT LOW COST —

PICK **CODAR** AMATEUR RADIO EQUIPMENT

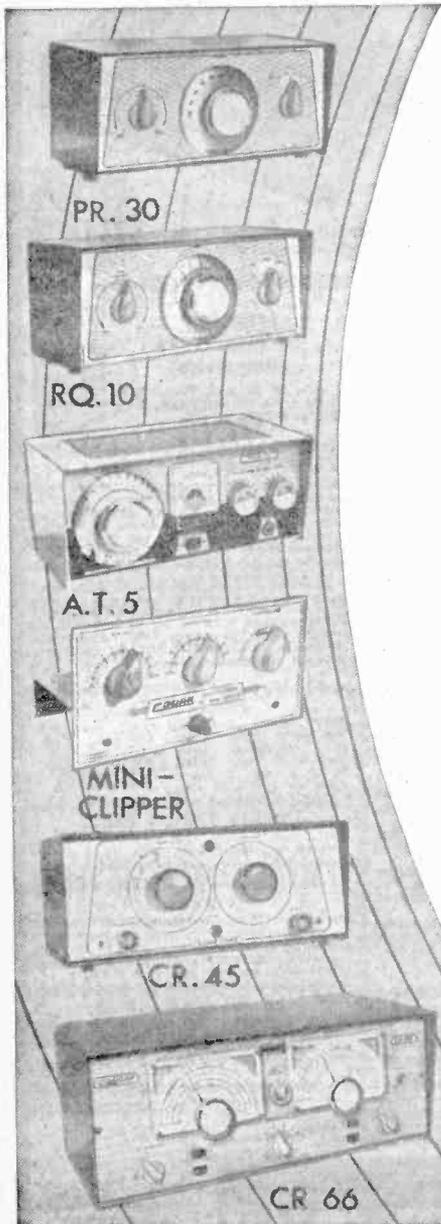

Advanced design and craftsmanship plus an unequalled reputation proved by the many hundreds of testimonials received from CODAR users is your guarantee of complete satisfaction. Only the best is good enough for CODAR—Mullard, Brimar, Jackson, Denco, Electroniques, Thora, A.E.L. are just some of the famous names built into CODAR equipment. CODAR-KITS are supplied with clear pictorial diagrams and easy to follow instructions—no technical knowledge or special tools are required for complete success. Build your Short Wave Station with CODAR-KITS and enjoy peak performance and world wide reception previously possible only from much more expensive equipment.

For illustrated leaflets giving fullest details send 6d. in stamps.

**CODAR R.F. PRE-SELECTOR.** Will considerably improve the performance of any superhet receiver. "Results are amazing." "Well worth the money." **MODEL P.R.30.** Uses EP153 Frame Grid tuned R.F. Amplifier and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity Selector switch for either dipole or single wire antenna. Power requirements 180-230 volts 12 M/A H.T. 6.3 volts, 3 amp L.T. Size 8 1/2 in. x 5 in. x 4 in. Ready built, complete with cables, plugs and instructions. £4.19.6 Carr. 3/- **MODEL P.R.30X.** Self powered version for 200-250V. A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £7.2.0. Carr. 3/-.

**CODAR "Q" MULTIPLIER MODEL R.Q.10.** For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either speaking or rejecting a signal on AM, CW or SSB. Both PEAK and NULL functions tunable over receiver. I.F. passband, B.F.O. facility included. Size 8 1/2 in. x 5 in. x 4 in. Power requirements 180-250V. H.T. at 5 M/A 6.3V. 3 amp L.T. Ready built complete with cables, plugs and instructions. £3.15.0. Carr. 3/- **MODEL R.Q.10X.** Self powered version for 200-250V. A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £3.8.0. Carr. 3/-.

**CODAR A.T.5. 12 WATT 2 BAND TRANSMITTER.** The newest, most compact transmitter for fixed or mobile use on 180/80 metres. "The tiny TX with the BIG voice." Size only 8 1/2 in. x 5 in. x 4 in. (Base area is less than two-thirds of this parcel) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR-QOIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate/screen modulator. AM/DW switch and panel key jack. Plug changerover for 6 or 12 volt heater supply. Ready built £16.10.0. Carr. 4/- **A.T.5 POWER SUPPLY UNITS.** Type 250/S. For 200/250 V. A.C. with Stand by/Net/Transmit and aerial changeover switching, stabilised V.F.O. supply, neon standby/transmit indicator £8.0.0. Carr. 5/- Type 12/MS 12V. Transistor power supply unit now available. (H.P. Terms available).

**CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER**  
 ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4 page instruction manual. PRICE 33/6. Carr. 2/6. Extra Coils 4/9 each. Instruction Manual only 2/- (credited on order). Electrical Bandspread available. Provision to add 2 transistor amplifier.

**CODAR-KIT CR45 MAINS T.R.F. SHORT-WAVE RECEIVER.** World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ80. **CODAR-KIT CR45** complete with valves, 3 coils (10-23, 25-75, 60-176 metres) and 11 page instruction manual (LESS Cabinet) £7.5.0. Carr. 4/6. **CR45 CABINET.** 12 in. x 5 1/2 in. x 4 in. with sliding door for easy coil changing. 35/-. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can now be supplied ready built—price on request). (H.P. terms available).

**CODAR-KIT CR 66 COMMUNICATION RECEIVER.** The finest superhet kit ever offered. ★ Covers 540 Kc/s—30 Mc/s in 4 bands. ★ Separate electrical bandspread. ★ Factory aligned Coil unit and I.F. Transformers. ★ Regenerative I.F. stage for maximum gain and B.F.O. for C.W. reception. ★ Power output 3 watts for 2/3 ohm speaker. ★ Panel controls: Aerial Trimmer, A.V.C.I. Standby, Bandswitch, A.F. Gain, I.F. Gain, B.F.O., etc. ★ Valve line up: ECH81, EBF89, ECC81, EL84, E230, EM84. ★ Size 16 in. x 8 1/2 in. x 8 1/2 in. **CODAR-KIT CR 66.** Complete with 17 page instruction manual. £19.15.0. Ready-built £23.0.0. **CR 66 "S"** Meter Model Kit £22.0.0 (Ready-built £25.0.0). Carr. 7/6 extra on all models (H.P. terms available). Instruction Manual only. 7/6 (credited on order).

**CODAR COILS AIR-SPACED INDUCTORS.** A complete range of low loss air-spaced inductors developed by CODAR. Over 40 different sizes from 1 in. to 3 in. diameter suitable for all types of circuit application including V.F.O. P.A. Tank, Pi-network, A.T.U. aerial loading, etc. Full data and prices on request.

**CODAR RADIO COMPANY**

G3IRE G3HGO

**BANK HOUSE, SOUTHWICK SQUARE, Southwick, Sussex.**

Tel. 3149

Canada: Codar Radio of Canada, Tweed, Ontario.

# The Goldenair



## "THIRTY" HI-FI AMPLIFIER



A high quality 30 watt amplifier developed for use in large halls and clubs etc. Ideal for bass lead or rhythm guitars, schools, dance halls, theatres and public address. Suitable for any type of mike or pick-up.  
 Valve line-up: two EF86; one ECC83; one GZ34; two EL34.  
 Four separate inputs are provided with two volume controls. Bass and Treble controls are incorporated. Amplifier operates on standard 50 c/s mains. 3 ohm and 15 ohm speakers may be used.  
 Perforated cover with carrying handles can be provided if required, price **21/-**

# Go Goldenair

**TWICE THE QUALITY  
HALF THE PRICE**

Send for leaflet of suitable loudspeakers that we can supply.

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade.  
 Send S.A.E. for illustrated leaflet.

or deposit of £1.16.0 and twelve monthly payments of £1.9.2.  
 Carriage 15/- to be sent with order.



### TRANS/RECEIVER No. 46

Compactly built to be carried by one man. This has a range of approx. 10 miles and being crystal controlled, tuning is avoided, and operation is as accurate as a telephone. Frequency 3.6-5.1 Mc/s. Complete stations comprising receiver/transmitter, rod aerial. One set of headphones and mike, in canvas carrying bag. Crystal coil unit available for only 35/- per set. Post Free. Brand new in maker's sealed cartons. For authorised use only. Price per station Sale Price **£3.0.0** P. & P. 10/- each  
 Two stations for **£6.0.0** Post free



### CRYSTAL SET

A wonderful educational kit for all children. Provides hours of amusement while following the easy step by step instructions. It is powered entirely by wireless waves, eliminating the expense of batteries. No soldering required. Receives all main stations. Price 28/6. P. & P. 2/6.



### LEAD ACID ACCUMULATORS (Unspillable)

2 volts at 16 A.H. Brand New. Size 4 x 7 x 2 1/2 in., 4/11 each. 3 for 12/6. P. & P. 3/6 per cell.



### GOLDENAIR SOUND MIXER

This splendid unit enables the mixing of up to 4 inputs, i.e. mic., tape, gram, tuner, etc. Compact and completely self-contained using a standard battery. Four standard jack inputs. Well finished handsome cabinet. Ideal for use with valve or transistor amplifiers. Price 45/- P. & P. 2/6.

### TRANSMITTER/RECEIVER No. 46 and No. 38 SET H.T. POWER PACKS

Power your 46 trans/rec. or 38 trans./rec. set straight from the mains. This valuable unit provides a stabilised D.C. H.T. for these sets. Robustly and compactly made. Sale Price 29/6. P. & P. 5/-.

### MORSE KEYS

Morse key assembly. Key with base cover and terminals. Complete with lead. 6/11. P. & P. 2/-. 2 Morse Keys for 12/6 post free.



### DOUBLE THROAT MIKES

Double throat mikes. Can be adapted for use with musical instruments. 5/11. P. & P. 9d.

### 19 SET TRANS./REC. MAIN POWER PACK

Operate your 19 set receiver straight off the mains. Ready built power unit complete with modification and fitting instructions. Price 59/6. P. & P. 3/6, please state model Bk. II or Mk. III. Suitable headphones for 12 set. Price 15/- P. & P. 2/6.

### 19 SET ACCESSORIES

12 Pin Connectors 12/6 each. P. & P. 2/6. Headphones and Microphone in good condition mostly new 17/6. P. & P. 2/6. Whip Aerials. 8ft. 6in. 7/6. P. & P. 2/6. 5ft. 4ft. P. & P. 2/6.

### No. 19 SET INSTRUCTION

**HANDBOOK 3/6 each** P. & P. 6d.

**1155 INSTRUCTION HANDBOOK**

**3/6 each** P. & P. 6d.

### H.R.O. INSTRUCTION HANDBOOK

**3/6 each** P. & P. 6d.

### TRANSMITTER/RECEIVER No. 46

**HANDBOOK 3/6 each** P. & P. 6d.

### FREQUENCY METER BCC221

**HANDBOOK 3/6 each** P. & P. 6d.

### 2-WAY SOUND POWERED TELEPHONE

As used by the armed forces. These sound powered earpieces will work up to a distance of one mile without the use of batteries. Beautifully made, ideal for use in the house, office or garden. Complete with connecting cable. 17/6. P. & P. 2/6.

**NEW WALK ROUND STORE OPEN IN LAMBERT'S ARCADE, LOWER BRIGGATE, LEEDS 1, NEXT TO HALFORDS CYCLE SHOP. OPEN ALL DAY SATURDAY, S.A.E. WITH ALL ENQUIRIES. ALL MAIL ORDERS TO OUR BRIGGATE HOUSE ADDRESS.**  
 Postage rates apply to U.K. only. Send 1/- for full lists

#### TERMS:

CASH WITH ORDER  
 5/- EXTRA ON C.O.D.  
 ORDERS  
 No C.O.D. under 30/-



TRADE SUPPLIED  
 ORDERS FROM  
 ABROAD WELCOMED

Telephone: 34708

**SONA ELECTRONIC CO. (Dept. PW15) BRIGGATE HOUSE, 13 ALBION PLACE, LEEDS**

FOR - IMMEDIATE - DESPATCH - PHONE - US - TODAY

BUILD YOUR RECORD PLAYER

4 Speed Autochange 2-tone Cabinets 17 x 15 x 8 1/2 in. High flux loudspeaker and 3 watt valve amplifier ready built. Quality output. Volume and tone controls. All items fit together perfectly. Special instructions enable assembly in 30 minutes. Only 5 wires to join. 12 months' written guarantee.



AUTOCHANGE KITS Complete—as above. B.S.R. Monorch \$110.19.6 P.P. 5/- Garrard Automotim £11.19.6 P.P. 6/- OR SEPARATELY Cabinet with board 14 x 13in. \$9.9.6 P.P. 3/6 Amplifier with speaker \$3.17.6 P.P. 3/6 AUTOCHANGERS (Stereo/Mono 16/- extra) B.S.R. U225 Superstim \$25.19.6 P.P. 3/6 Garrard Automotim Mono \$6.10.0 P.P. 3/6 SINGLE PLAYERS Garrard SRP10 auto. stop \$5.5.0 P.P. 3/6

Q MAX CHASSIS CUTTER

Complete: die, punch, Allen screw and key. 1/4 in. 14/6 1 1/2 in. 18/- 2 in. 22/6 2 1/4 in. 14/6 1 1/2 in. 18/- 2 in. 22/6 2 1/4 in. 15/9 1 1/2 in. 20/- 2 in. 22/6 2 1/4 in. 18/- 1 1/2 in. 20/6 1 in. sq. 31/6

CRYSTAL MIKE INSERTS, 6/6

High output. Size 1 1/2 in. dia. x 1 in. ACOS MIC. insert 1 1/2 in. dia. x 1 in. 8/6 ACOS39-1 IDELUXSTICK MIKE 35/- TSL QUALITY STICK MIKE... 25/- TELEPHONE TAPE MIKE... 10/6 GUITAR CONTACT MIKE... 15/6 MOVING COIL MIKE, high or low impedance, 90/- FLOOR STAND, 57/- TANNY Carbon Hand Mike... 5/6

FULL WAVE BRIDGE SELENIUM RECTIFIER: 2, 9 or 12 v., 11 amp., 8/9/-; 2 a., 11 1/2; 4 a., 17/8; CROCKER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps., 16/9; 2 amps., 17/8; 4 amps., 22/6. Circuit included.

MINIATURE PANEL METERS

Size 1 1/2 in. sq. Precision jewelled bearings, 2% accuracy, silvered dials, black numerals and fine pointers, zero adjustment screw on front of meter. 1 mA... 27/6 500 uA... 30/6 5 mA... 27/6 500 uA... 32/6 300V... 27/6 "S" Meter 35/-

VALVE HOLDERS. Int. Oct. or Mazda Oct. 6d; B7G, B8A, B8G, B8A, 9d; B7G with can 1/6; B9A with can 1/8. Ceramic EF50, B7G, B9A, Int. Oct. 1/-. Valve plus B7G, B9A, Int. Oct. 3/3.

1965 RADIOGRAM CHASSIS



Three Wavebands Five Valves: ECH81, Long, Med., Short EF89, EB061, EL84, EZ80 12-month warranty. A.C. 200/250 v. Ferrite Aerial, 5 watts, 6 ohm, 13 1/2 in. x 7 in. high x 5 in. deep. Dial size 1 1/2 x 4 in., horizontal wording. Aligned, calibrated. Chassis isolated from mains. BRAND NEW £9.15.6 Carr. 4/6. Matched speakers 8 in. 17/6; 10 in. 25/-; 12 in. 30/-

NEW ELECTROLYTICS FAMOUS MAKES

Table with columns: TUBULAR, CAN TYPES, and various capacitor specifications like 1/350V, 2/350V, etc.

CONDENSERS. 0.001mfd., 7 kv., 6/6; 20 kv., 10/8; 0.1mfd., 7 kv., 9/8; Tubular 500 v., 0.001 to 0.05. 9d; 0.1, 1/-; 0.25, 1/6; 0.1850 v., 9d; 0.5/350 v., 1/9; 0.01/2000 v., 2/6; 0.04/2000 v., 3/6; CERAMIC. 500 v., 1 pF., 0.01 to 9d. Pulse 100 pF., etc., 12 kv., 6/6. SILVER MICA. Close tolerance (plus or minus 1 pF.). 2.2 to 47 pF., 1/-; ditto 1% 50 to 815 pF., 1/-; 1.000 to 5,000 pF., 1/6. TWIN GANG. -0-0" 208 pF. +176 pF., 19/6; 365 pF., miniature, 10/4; 500 pF. standard with trimmers, 9/-; midset, 7/6; midset with trimmers, 9/-; 500 pF., slow motion, standard, 9/-; small 3-zang 500 pF., 17/8. Single "0" 365 pF., 7/8. SHORT WAVE. Single 10 pF., 25 pF., 50 pF., 75 pF., 100 pF., 100 pF., 5/6 each. Can be knaged to other. COUPLERS 9d. each. TUNING AND REACTION. 100 pF., 300 pF., 500 pF., 3/6 each, solid dielectric. TRIMMERS. Compression ceramic 30, 50, 70 pF., 9d., 100 pF., 150 pF., 1/3; 205 pF., 1/6; 600 pF., 750 pF., 1/9.

MAINS TRANSFORMER 200/250 v. A.C. Postage 2/- each transformer. STANDARD 250-0-250, 50mA, 0.5 v., 3.5 a., tapped 4 v., 4 a. Rectifier £53 v., 1 a., 5 v., 2 a., or 4 v., 2 a., 22/6; 100, 350-0-350 MINUTE 200 v., 20 mA, 6.3 v., 1 a., 10/6 MIDGET, 220 v., 45 mA, 6.3 v., 2 a., 15/6 SMALL 250-0-250, 45 mA, 6.3 v., 2 a., 17/8 STD. 250-0-250, 65 mA, 6.3 v., 3.5 a., 17/8 HEATER TRANS. 6.3 v., 1 a., 3/6 Ditto, tapped 1.4, 2, 3, 4, 5, 6.3 v., 10/6 GENERAL PURPOSE LOW VOLTAGE. 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v., 22/8 AUTO TRANSFORMERS. 150 v., 2/6 MULLARD "5510" Main Transformer 32/6 0, 115, 200, 230, 240 v., 500 v., 2/6

TELESCOPE CHROME AERIALS, 12 to 23 in., 6/8 LEAD SOCKETS, 2/-, PANEL SOCKETS, 1/-, OUTLET BOXES (Surface or flush), 4/- each. BALANCED TWIN FEEDER yd. 6d., 80 or 300 ohms. TWIN SCREENED per yd. 1/-, 80 ohms only.

THE "INSTANT" BULK TAPE ERASER AND RECORD HEAD DEMAGNETIZER. 200/250 v. A.C. 35/-

"THE POWER MITE" 45/- PM9 Mains Unit 9 volt for Transistor Radios. Same size as P.P.9 (200/250 v.)

4 TRANSISTOR AMPLIFIER Ready built. Size 3 x 1 1/2 x 1 1/2 in. with transformers 3 and 8 ohms output. Ideal for use with record players, intercoms, BABY ALARMS. Complete with instructions and circuit. Price 47/6

NEW MULLARD TRANSISTORS OC71, 6/-; OC72, 7/6; OC81D, 7/6; OC81, 7/6; AF115, 10/6; AF114, 11/-; OC84, 8/-; OC85, 8/-; OC171, 9/-; OC170, 8/6; AF117, 9/6; OA1, 3/-; OC28, 12/6; Holders, 1/3. Sub Min. Condensers 0.1 mFd., 30 v., 1/3; 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mFd., 15 volt, 2/6.

Volume Controls 80 ohm Cable Coax Linear or Log Tracks Semi-air spaced 1/4 in. Long optudes. Midset. 40 yds. 17/6 5 K ohms to 2 Meg. 60 yds. 25/- 6d. yd. L.S., 8/-. D.P., 4/8. Ideal 625 lines. U.H.F. stereo L10/8; D.P. 14/7. Im. log + Im. log, 7/8 100ft. 500 Mobs. 1/6 yd.

B.T.H. TAPE MOTORS 115 v. A.C. 28 w. 12/6 pair, for 200/250 v. (in series).

BAKERS

'Selhurst' 25 WATT 5 Gns. 12" GUITAR HEAVY DUTY 15 OHM VOICE COILS Response 20-10,000 cps Bass Resonance 80 cps Genuine Musical Instrument Loudspeaker



BAKERS 12in. STALWAT 15w. 5 gns. 3 or 15 ohms voice coils. Unlimited applications. Response 45-13,000 cps. Magnet 12,000 lines. BAKERS 12in. STANDARD 20w. 7 gns. More powerful magnet 14,000 lines special suspension. 40-14,500 cps. Recommended. BAKERS 12in. BASS 25 w. 12 gns. New 1965 high power model. Aluminium coil former with magnetic dampinx 25-15,000 cps. BAKERS 16in. AUDITORIUM 35w. 18 gns.

LOUDSPEAKERS P.M. 3 OHM FAMOUS MAKES. 2 1/2 in., 3 in., 4 in., 5 in., 7 x 4 in., 15/6 each; 8 in., 17/6; 6 in., 16/6; 10 in., 30/-; 12 in., 30/- (15 ohms 35/-); 10 x 6 in., 22/6; 8 x 5 in., 21/-; 8 x 6 in., 21/- WAVE-CHANGE SWITCHES, 3/6 each. 2 p. 2-way or 2 p. 6-way 3 p. 4-way or 1 p. 12-way? 2 p. 2-way or 4 p. 3-way. Wavechange "MAKITS" available: 1 p. 12-way, 2 p. 6-way, 3 p. 4-way 4 p. 3-way, 8 p. 2-way. Kit prices: 1 water, 8/6; 2 water, 12/6; 3 water, 18/- Extra waters, 3/6 each. TOGGLE SWITCHES, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-

BOOKS Please add postage

Boys' Book of Crystal Sets... 2/6 "W.W." Radio Valve Data... 7/8 High Fidelity Speaker Enclosure... 5/- TV Fault Finding... 8/6 Multivert Amplifier Manual... 8/6 Radio Valve Guide, Books 1, 2, 3, 4 or 5... 5/- each Practical Radio Inside Out... 3/6 Master Colour Code Chart... 1/6 Transistor Controlled Models... 2/6 International Radio Stations... 2/6

JACKS. Standard open-circuit 2/6, closed circuit 4/6 Grundig type 3-pin 1/3; Grundig Lead Type 3/6. Phono Plugs 1/-, Socket 1/-. Banana Plugs 3/6. I.A.C. PLUGS. Screened 3/-. Grundig 3-pin 3/6. BULGIN NON-REV PLUGS and SOCKETS. P74 2-pin 4/3; P73 3-pin 4/6; P184 6-pin 6/6; P466 12/6. RESISTORS. Preferred values, 10 ohms to 10 meg. 1 w., 4 v., 1 w., 20 v., 4 1/2, 1 w., 8d., 2 w., 1/- 1 w., 1 w., 20 v., 1 w., 2/- Preferred values, 10 ohms to 10 meg. Ditto 5%, 10 ohms to 22 meg., 9d. 5 watt... 1/8 10 watt... 1/6 WIRE-WOUND RESISTORS 1/6 15 watt... 1/8 10 ohms-6,000 ohms 2/6 MAINS DROPPERS. Midset. With sliders. 0.3a. 1 K., 0.2 a., 1.2 K., 0.15 a., 1.5 K., 0.1 a., 2 K., 6/- each. Line Cord 100 ohms ft. 3-way, 1/- 1/-. Wirewound Ext. Speaker Control, 10 1/2 3/-; 25 0 8/6. WIRE-WOUND POTS. 3 WATT. Pre-set. Min. 1V Type. All values up to 10 ohms to 25 K., 8/- each. 30K-4/-, Carbon 30K to 2 meg., 3/-.

WIRE-WOUND 4 WATTS POTS. Long spindle. Value, 50 ohms to 50 K., 6/6; 100K., 7/6. SPEAKER PRET. Tylan various outputs. 50in. wide from 10/- to £20n. wide from 5/- to 5.5n. S.A.M. EXPANDED METAL. Gold 12 x 12in., 6/-.

ARBENTEN TRANSISTOR TRANSFORMERS D8035, 7.3 CT.1 Push-pull to 3 ohms output 11/- D8084, 1.5:1 C.T. Push-pull driver 11/- D8088, 11.5:1 Output to 3 ohms, etc. 11/6 D829, 4.5:1 Driver 11/6 D829, 4.5:1 Driver D240, 8.5:1 Driver 5/3 D829 TRANSISTOR POTS 5 K Switched 7/6 SUB-MIN. EARPIECE 2x1 or magnetic 7/6 SUB-MIN. JACK AND PLUG 2.5 or 3.5n. 3/6 9/- BULKY Aluminium Chassis, 18 a.w.g. 4 sides, riveted corners, lattice fixing holes, 2 1/2 in. sides, 7 x 4 in., 4/8; 9 x 7 in. 5/9; 11 x 7 in., 8/9; 13 x 9 in., 8/6; 14 x 11 in. 10/6; 15 x 14 in., 12/6.

RETURN OF POST DESPATCH EXPERTS ANSWER ALL ENQUIRIES NO ORDER TOO SMALL

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD WEST CROYDON Telephone TH 1665

Written guarantee with every purchase Buses 133, 68 pass door. S.R. Stn. Selhurst P.P. Charge 11/-, Full List 1/-, C.O.D. 2/- extra (Export welcome. Send remittance and extra postage, no C.O.D.)

# ELECTRONICS


## LEARN - THE PRACTICAL WAY . . .

your career . . .  
hobby . . .  
own business . . . ?

The demand for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities, then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek high qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises ONLY in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.


A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

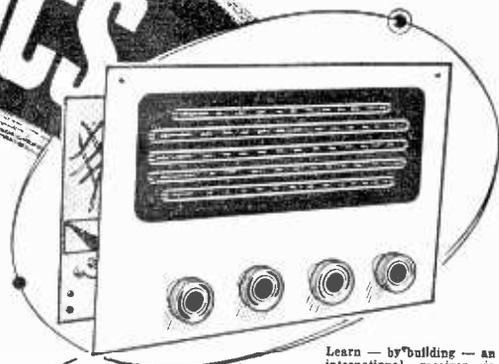


Learn — by building — an international receiver in the top quality class . . . nine transistors . . . L.W. M.W. TWO SHORT WAVE Bands and VHF/FM . . . incorporates every modern receiver design technique.



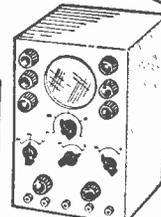20,000 ohm/volt modern multi-range test meter . . .



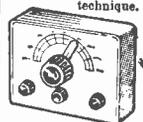Cathode ray oscilloscope to show how circuits work . . .



Transistorized signal generator of new design and wide frequency coverage . . .



Complete picture way library of theory books and practical manuals NO MATHEMATICS'

### EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION
- RADIO AMATEURS LICENCE EXAMINATION
- P.M.G. CERTIFICATES FOR RADIO OPERATORS.
- R.T.E.B. SERVICING CERTIFICATES.

### OTHER COURSES

- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADAR & NAVIGATIONAL AIDS

## BUILD AND EXPERIMENT WITH ALL THE ABOVE—AS—YOU—LEARN . . .

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; etc.—and finally to the design, construction, testing and servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVEBANDS plus VHF/FM reception. It is of real luxury quality throughout—operates from a 9v. battery and can be used anywhere in the world. Every present-day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out during this comprehensive course enabling anyone to gain full mastery of electronics.

# FREE



**POST NOW**  
TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS.  
Please send me your free Brochure, giving details of your Courses, without any obligation to —

NAME.....  
ADDRESS .....

} Block Caps Please

I am interested in.....courses above  
(We do not employ representatives) PW 3/65

# British National Radio School

# Practical Wireless

Vol. XL No. 697 MARCH, 1965

Editorial and Advertisement  
Offices:

**PRACTICAL WIRELESS**

George Newnes Ltd., Tower House  
Southampton Street, W.C.2

© George Newnes Ltd., 1965

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London

**SUBSCRIPTION RATES**

including postage for one year

To any part of the world £19.0

## Contents

Editorial	1037
Round the World of Wireless	1038
Keyed Audio Oscillator	1040
How to Align a Receiver Without Test Equipment...	1044
Cabinet and Chassis Tech- niques	1048
Preventing Accidental Tape Erasure	1053
Practically Wireless	1054
Preselector and B.F.O. Unit	1055
A Voltage Stabilised V.F.O.	1060
The "Cadet" 7 Watt Hybrid Amplifier	1064
Building a Transistor Solo Organ	1069
On the Short Waves	1077
Trade News	1081
Preparing for the R.A.E.	1085
Letters to the Editor	1093
Club News	1094

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS is a Corporation of America.

## Diversified Interests

WE have all, no doubt, at some time or another been subjected to the frustrating boredom of the man with a one-track mind. There are countless versions: he (or she, come to that!) may be a football fanatic, a motor car maniac, a prattling philatelist, a rabid racing addict. His tastes may be low or high, academic, athletic, scientific, active or sedentary. He lives for only his chosen subject to the exclusion of all else. his pet interest has become an obsession.

Such a person suffers from the sad delusion that everyone else is equally interested, or should be, and he succeeds only in being devastatingly boring and infuriating. He is usually magnificently unloved. Even his best friends won't tell him. And among this population of over-zealous enthusiasts there must be, if only on the law of averages, one or two radio bores!

Many hobbies, and ours is no exception, present limitless opportunities for exploration and exploitation. There are so many basic activities, so many possible diversions, so much to do in so short a time, that the really keen enthusiast can easily find himself so inextricably involved that the hobby becomes the master. The dividing line between a Fan and a Fanatic may be extremely thin!

Most of us, of course, keep a reasonable sense of proportion but the line of thought being pursued does suggest some self-interrogation that might be applied at times.

Unless one is engaged professionally, it is probably better not to become too highly specialised—or too narrow minded. Don't get into a rut by building only valve or only transistor equipment, or only receivers, or only amplifiers. Try something different, even if only occasionally.

"Jack of all trades, master of none" may be a justifiable slur in industry, but surely not in amateur radio, where a diversity of interests is the best way to get the most from the hobby and to avoid becoming a radio bore even to other radio enthusiasts!

A sense of proportion is also advisable in our general approach. Since the hobby is a technical one, it is inevitable (and desirable) that equipment is appraised in a technical manner. But the time to take stock is when you listen to recordings and hear not music but only frequency response, harmonic distortion, wow and flutter percentages. Or when you watch a TV programme in misery because the raster is slightly non-linear or there is a fraction too much overshoot. Or when you are impelled to switch off a radio in the middle of a programme to change a coupling capacitor. Or when you mentally read advertisement posters in morse code!

The search for improvement, if not perfection, is highly commendable, but the place to do this is on the work bench when the equipment is being designed, constructed, aligned or serviced.

It should always be remembered that equipment is built to be used and to be enjoyed. And if it is in the living room, no doubt other members of the family will be only too pleased to point this out!

Our next issue dated April will be published on March 4th



# of WIRELESS

## NEWS AT HOME AND ABROAD

### RADIO MASTS FOR ATLANTIC ISLAND

**B**BRITAIN'S Ascension Island in the South Atlantic Ocean is shortly to have nine radio masts erected on it. An order valued at over £90,000 for the masts from the Marconi Company Limited has been received by British Insulated Callender's Construction Company Limited.


Under the contract BICC will supply one 250ft. and eight 325ft. radio masts for use on the island.

### Miniature Resistors Protect Motors

**N**EW protection devices for electric motors recently introduced by Mullard are designed to be incorporated directly in the windings of the motor. The new devices—positive temperature coefficient resistors—will provide cheaper and more effective protection of electric motors than conventional methods.

The miniature resistors (see illustration) are made from doped barium titanate ceramics. In operation they exhibit a high positive temperature coefficient which causes a large and rapid increase in value when an excessive increase in the temperature of the motor windings (above about 110°C) occurs, and this will cut-off the power supply.

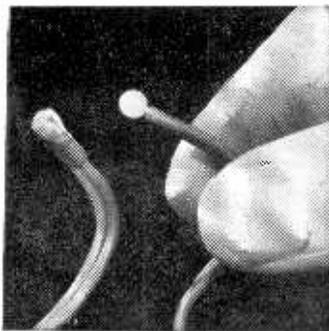A number of special advantages are presented by the introduction of these resistors and applications in transistor circuits are foreseen.




### AIRCRAFT NAVIGATION BEACONS FOR U.S.S.R.

**R**ADIO navigation beacons for aircraft, of the type now covering the Western European air lanes, will shortly be installed in the U.S.S.R. under a contract signed recently in London.

The contract, which is for two high-power long-range VOR beacons (one is shown on the right), is the first ever Soviet order for this type of equipment. Standard Telephone and Cables Limited are to supply the beacons which will be installed on the airway between Moscow and the Baltic coast.

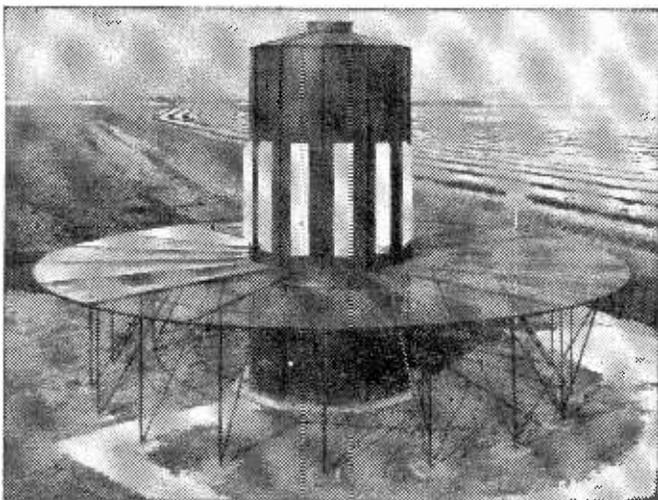During the negotiations for the contract, which also includes STC airborne equipment, Soviet representatives witnessed the operational procedures of the VOR receiver equipment during a demonstration flight in the Company's aircraft.



## RADAR REFLECTORS FOR HIGH-FLYING GLIDERS


AT Ipswich airport, home of the London Gliding Club, the Marconi Company, on behalf of the Ministry of Aviation, are currently carrying out a series of experiments aimed at reducing the danger of collision between gliders and high-speed aircraft.

Because of their very light construction, gliders do not register on the radar screens of air-traffic control centres and as the modern high-performance glider can easily reach the airways of civil and military aircraft, this danger of collision is increasing.

The experiments carried out by the Marconi Company will investigate possible methods of improving the radar reflective properties of gliders by such means as cheap, light-weight radar reflectors that could be easily fitted in a glider to make it visible to radar, without being in any way detrimental to the performance of the glider.


After a series of experiments using scale models at the Marconi Research Laboratories, Great Baddow, a number of radar reflectors have been designed and tested in flight. For these trials a glider with a tug aircraft has been operated by members of the London Gliding Club.

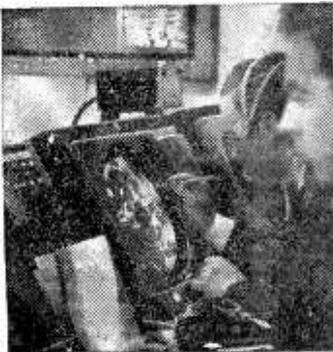At the Marconi Rivenhall Establishment in Essex, Marconi research engineers have observed these flights and recorded the strength of the reflected radar signals received by three separate radar systems.



Marconi engineers recording the radar signals received from a glider fitted with experimental reflectors.

## NEW AERIALS FOR RADIO ASTRONOMY

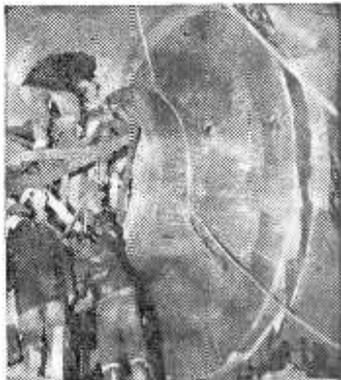

THE contribution of the Commonwealth to the study of radio sources throughout the universe, has advanced on two accounts recently by the installation of a new 15ft. radio telescope at Coxtie Green, near Brentwood, Essex, and the erection at Parkes, New South Wales, Australia of a 60ft. interferometer.

The Coxtie Green telescope (above) has been produced by the Marconi Company Limited for research scientists from Queen Mary College, London University, to examine the brighter planets and radio sources in the sky. The telescope, which operates at wavelengths in the region of one millimetre, has the unusual feature of being moulded in glass fibre reinforced plastic.

The New South Wales interferometer (below) joins a 210ft. radio telescope on the same site. On occasions these two instruments will be used in conjunction for the accurate position fixing of radio sources.



## Ionosphere Sounders for U.S. Navy

EQUIPMENT which will be used by the United States Navy to ascertain the best operational frequency for long range h.f. radio communications, is to be developed under a contract awarded to EMI-Cossor Electronics Ltd. of Canada, subsidiary of EMI.

The equipment—an ionospheric oblique sounder—will be a sophisticated version of the company's Ionosonde 8000, which is currently being evaluated by several NATO nations.

Due to the physical structure of the ionosphere, quality of reception of short wave radio transmissions varies considerably between one frequency and another. The new sounder will enable the U.S. Navy to detect the best possible wavelength for communications without relying on possibly incorrect forecasts or lengthy trial and error methods.

## Telegraph System in North Sea

DURING the intensive search for oil and natural gas under the North Sea, a G.P.O. radio telegraph system will be used to provide communications between the many mobile drilling rigs and one of two shore stations at Humber, on the Lincolnshire coast, and Stonehaven, near Aberdeen.


Both shore stations will be fitted entirely with Marconi multi-channel telegraph transmitting and receiving systems and will provide up to 30 individual communication channels.

This order was placed by the General Post Office. An accompanying order from the Marconi International Marine Company will provide radio equipment on one of the drilling rigs.



# KEYED Audio Oscillator

By M. L. Michaelis

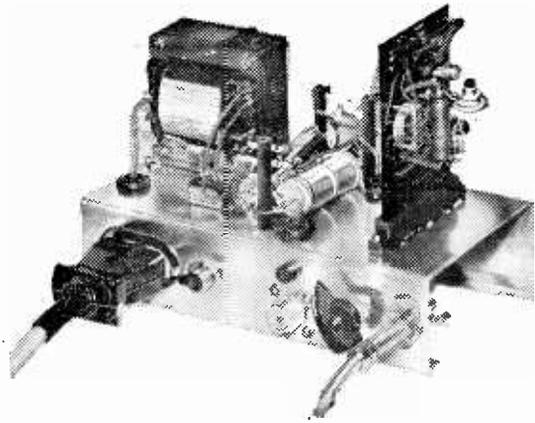

**M**ODERN electronics practice makes increasing use of small circuit bricks comprising circuitry which can be used in virtually the same form for the most diverse applications. Such arrangements are all the more valuable on account of the tendency to miniaturisation on small circuit boards, using transistorised circuitry. The particular "brick" which is the subject of this article comprises a versatile keyed audio oscillator which has been devised and thoroughly tested by the author. It is built-up on a 4in. x 2.5in. Veroboard

(small paxolin sheet with regular rows of holes for affixing components, as described in PRACTICAL WIRELESS, May 1964) and has seven terminals for external connections (Fig. 1).

The basic function of this circuit is to provide an audio output signal, of almost pure sine-waveform, whenever and only as long as the d.c. current or voltage injected at P1 exceeds a certain threshold limit which can be set over a wide range in each case with the help of the sensitivity control VR1 (or VR1a). The three n.p.n. silicon epitaxial

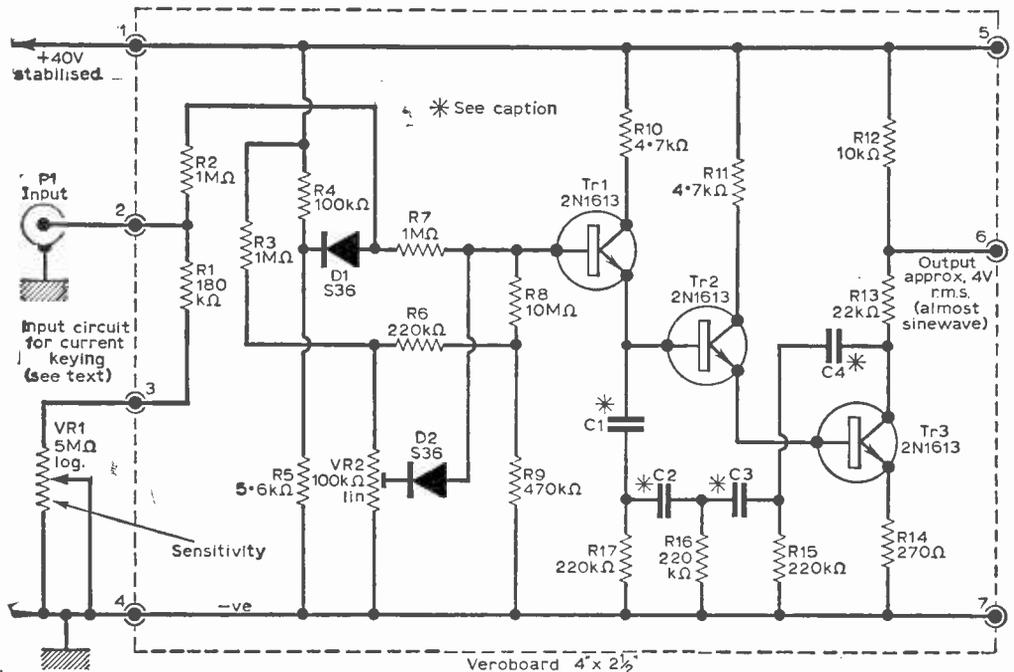


Fig. 1: The oscillator circuit. The output frequency is determined by the capacity of the four (equal) capacitors C1-C4. At 100pF, the frequency is about 5 kc/s, at 250 pF 2 kc/s, at 500pF 1 kc/s, at 1000pF 500 c/s, at 0.01μF 50 c/s, at 0.1μF 5 c/s and at 0.5μF 1 c/s. The relationship is thus strictly linear.

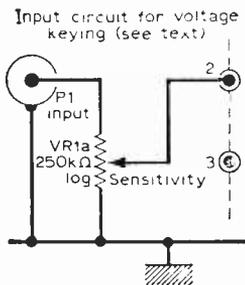


Fig. 2: The P1 input of the circuit of Fig. 1 modified for voltage keying.

transistors are basically in a three-stage emitter follower cascade arrangement and are normally cut-off because the bias applied to the base of Tr1 is just less than the threshold voltage of such an arrangement. A very small current injected via P1 (a fraction of a microamp in the most sensitive setting of VR1) cuts the cascade of three transistors on, whereupon the last two, Tr2 and Tr3, immediately commence to oscillate as a phase-shift oscillator through the feedback network C1—C4/R15—R17.

**Uses**

This circuit can be used for any purpose requiring this function. The input circuit at P1 is, for example, more than adequately sensitive to operate directly from a vacuum photocell of the 90AV type, whose cathode is then connected directly to P1 and anode to the appropriate positive voltage needed to operate the photocell (in fact, the same +40V line as needed to operate the Veroboard circuit will generally do). Whenever the photocell is illuminated, it draws a tiny current in proportion to the intensity of the illumination. With the sensitivity control VR1, the current at which the transistors "switch on" and the audio oscillation thereupon appears at the output socket, can be adjusted between about 0.5 and 12μA, this being the normal current operating range for most photocells. The sensitivity control VR1 will, in such applications, normally be set so that the photocell current due to the ambient illumination just does not "switch" the oscillator on, response then being obtained only to any "wanted" additional light signal.

Regarding the output circuit, this may be connected via a simple blocking capacitor and volume control (Fig. 3) between terminals 6 and 7 to the input of any audio amplifier, transmitter modulator amplifier or to the record-player input sockets on the recording amplifier of any conventional domestic tape recorder. However, if you wish to record the bursts of audio oscillation (in response to the d.c. voltage or current pulses applied at the input) on tape, an additional recording amplifier is

not absolutely essential. Fig. 4 shows how a normal type of recording head can be fed directly from the output terminals 5, 6 and 7. R23 here gives d.c. bias for the head in place of the otherwise (for musical recordings) more usual r.f. bias. This is quite satisfactory here, particularly if erase is performed with a powerful permanent magnet over the pole of which the tape passes, which also has the advantage of completely avoiding the need for any form of electronic bias and erase oscillator for such a technical pulse-recording tapedeck, therewith greatly simplifying circuitry. The erase magnet will saturate the tape: the d.c. bias passed into the recording head via R23 must be of opposite polarity, i.e. such as to move the magnetisation of the tape away from saturation again, to the recording operating point on the hysteresis curve. The playback head will function normally, using a normal playback amplifier.

When deciding to build a special tapedeck from scratch the characteristics of the recording head RH1 chosen should be obtained from the makers. These will normally state an (r.m.s.) r.f. bias current and a signal current required for correct operation. Satisfactory performance is obtained, in most cases, with the value of R23 chosen such that the d.c. current obtained as bias is some two-

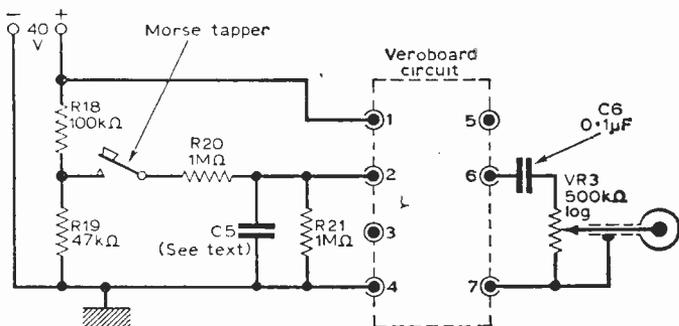


Fig. 3: Input and output connections for m.c.w. telegraphy and model control transmitters, as well as for electronic organs and tremolo insertion on guitar amplifiers.

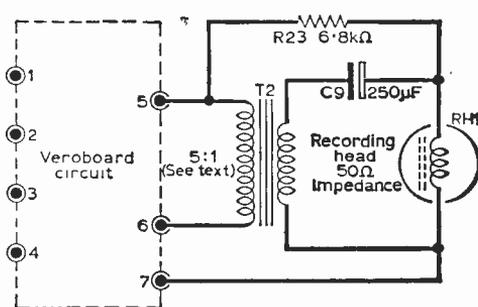


Fig. 4: Output connections for direct tape-recording, without an additional recording amplifier being required.

thirds of the specified r.m.s. value for r.f. bias. The transformer L2 must have a step-down ratio approximately equal to the number of mA signal current specified for the particular recording head. The sub-miniature types sold for interstage coupling in transistorised audio amplifiers will in most cases be found satisfactory; conditions are not very critical.

### Practical Uses Requiring Tape Recording of the Output

Apart from numerous applications in the control of industrial machinery which are beyond the scope of this article there are several interesting amateur applications, particularly in the field of remote control of model ships and aircraft. These involve the prerecording of a sequence of pulses tapped in with a Morse key at the input so that, on playback of the tape into the modulator of the model control transmitter, the model can be made to respond to the particular sequence of commands automatically without further manual attention. If a closed loop of tape is used the sequence of commands can be repeated indefinitely as the tape goes round and round until stopped. There is a wide field here for model control experimenters.

A transmitted signal using modulation of the carrier with various audio frequencies is best used here, the receiver on the model employing audio tuned circuits of resonant reed relays to select the individual frequencies and thereupon cause the appropriate responses in the correct control circuits of the model. All necessary components for building such model control receivers, together with profuse technical information, are stocked by good modelmakers' shops and are made by such firms of world repute as, for example, Messrs. Grundig.

The advantage of this method of model control is that as many different commands can be sent *simultaneously* as different audio frequency "channels" are available. Several of the Veroboard circuits described in this article (Fig. 1) can be made, differing solely in the value chosen for the four capacitors (all *must* be equal) C1 to C4, which determines the frequency of oscillation. Alternatively a two-pole, multi-way wafer switch—or a set of push-buttons—may be used to select various similar networks with different C values between the collector of Tr3 and the base of Tr2 on a single circuit. The different "channels" are then merely no longer available simultaneously but only successively in any order.

It is in fact possible to use this Veroboard circuit as a virtually complete multi-channel model-control transmitter, the output signal at terminal 6 generally being of ample power to grid-modulate a conventional transistorised p.a. stage, which is all that will be required in addition on the r.f. side, no additional modulation amplifier being necessary. If a row of suitable press-buttons are used, each having two contacts selecting and connecting different networks between the collector and base of Tr3 and Tr2 respectively, and a third contact in the function of Morse tapper (Fig. 3), then by **pressing** the appropriate button it will cause the transmitter to send out the associated selective command in each case.

With a tapedeck connected to the output, as shown in Fig. 4, the programme of commands "tapped in" with the buttons can be recorded for subsequent automatic operation of the model according to the predetermined programme on playback into the transmitter modulation input. The great advantage of the d.c. bias shown in Fig. 4 for the recording head and of being able to dispense entirely with an erase oscillator, using a permanent magnet, lies in the extraordinary simplicity of the tapedeck thereby rendered possible. The playback amplifier need only be a perfectly straightforward audio amplifier with an input sensitivity in the region of 1mV, almost any microphone amplifier advertised ready built or as a kit in these pages (e.g. baby alarms) being satisfactory. It is consequently possible to accommodate the sub-miniature tapedeck into the model-control transmitter casing (hand-carried

### COMPONENTS LIST

#### Resistors:

R1	180k $\Omega$	R13	22k $\Omega$
R2	1M $\Omega$	R14	270 $\Omega$
R3	1M $\Omega$	R15	220k $\Omega$
R4	100k $\Omega$	R16	220k $\Omega$
R5	5.6k $\Omega$	R17	220k $\Omega$
R6	220k $\Omega$	R18	100k $\Omega$
R7	1M $\Omega$	R19	47k $\Omega$
R8	10M $\Omega$	R20	1M $\Omega$
R9	470k $\Omega$	R21	1M $\Omega$
R10	4.7k $\Omega$	R22	3.3k $\Omega$ 2W
R11	4.7k $\Omega$	R23	6.8k $\Omega$
R12	10k $\Omega$		

All 10%  $\frac{1}{2}$ W carbon, unless otherwise stated

#### Capacitors:

C1	100pF-0.5 $\mu$ F	} To suit desired frequency See caption Fig. 1
C2	100pF-0.5 $\mu$ F	
C3	100pF-0.5 $\mu$ F	
C4	100pF-0.5 $\mu$ F	
C5	10 times C1/C4 value	
C6	0.1 $\mu$ F paper	
C7	100 $\mu$ F electrolytic 125V	
C8	100 $\mu$ F electrolytic 125V	
C9	250 $\mu$ F electrolytic 9V	

#### Semiconductors:

D1	S36 diode	} Brush Crystal Co., Hythe, Southampton
D2	S36 diode	
D3	ZL39 zener diode	
D4	200/250V silicon h.t. rectifier	} Brush Crystal Co.
D5	200/250V silicon h.t. rectifier	
D6	200/250V silicon h.t. rectifier	
Tr1	2N1613 transistor	
Tr2	2N1613 transistor	
Tr3	2N1613 transistor	

#### Potentiometers:

VR1	5M $\Omega$ log.	VR1a	250k $\Omega$ log.
VR2	100k $\Omega$ lin. preset sub-miniature		
VR3	500k $\Omega$ log.		

#### Miscellaneous:

T1	Mains transformer. Secondaries: 50V 30mA (heater transformer with rewound secondary)
T2	Transistor interstage transformer with 5:1 ratio, or to suit recording head (see text)
S1	Mains toggle on/off switch
F1	250mA mains fuse
	Plugs, sockets, wire, piece of Veroboard 4in. x 2 $\frac{1}{2}$ in., etc.

portable) with a switch on the panel "auto/direct" being included. In the auto setting the transmitter is modulated with a prerecorded sequence of commands from the tape; in the direct setting the transmitter is modulated directly by the commands. Various combinations are possible, e.g. commands can be recorded simultaneously to direct transmission so that if some hand-controlled acrobatic antic of the model proved particularly pleasing it can immediately or at any later time be repeated by playing back the tape.

It is, of course, immaterial whether several Veroboard circuits are used so that commands such as throttle and rudder control can be given simultaneously or whether only one switched-frequency circuit is used for successive commands as far as the tapedeck and receiver function is concerned. The tape can record all frequencies simultaneously if necessary and the receiver audio tuned circuits will sort them out. There is only one important practical condition, namely that the various audio frequencies associated with the different channels should bear no harmonic relationships, i.e. they should not be simple multiples or other simple ratios of each other but rather as "odd" as possible. This is to avoid the harmonics generated upon distortion of the waveform in any one channel causing spurious responses in one or more other channels. The receiver audio tuned circuits will already be staggered appropriately and it is then merely necessary to trim the Veroboard circuit networks to proper resonance (if necessary wire small trimmers in parallel with C1 to C4).

### Geiger Counters

A somewhat more specialised but nevertheless interesting and practical use of the circuit concerns Geiger counters, this also requiring tape recording of the output pulses. In PRACTICAL WIRELESS, December, 1962/January, 1963, an article was published on an advanced Geiger head, followed by a digital register in the April to June, 1963, issues. Finally in the December, 1963, issue, a description was given of the many experiments possible with this equipment which, as readers will remember, involved among other things a study of the natural radium-product activity in rain or snow. This can reach enormous intensities and decay within some three to five hours. The study of these activities in relation to season, location and weather patterns, as explained in the last-named article, can be a most instructive line of experiment for schools and clubs but it is often rather time consuming since the counter must be read off every few minutes after as many rains as possible. More troublesome still is the fact that many of the most interesting rains and thunderstorms occur deep in the night and it is bad enough having to get up and switch the apparatus on then—but having to sit by it for the rest of the night reading off the counter every few minutes is the last straw! A second almost insurmountable problem is involved with the fact that many of the most interesting studies concern quick successions of many showers in a row. A study of the changes of radioactivity with the progress of such weather patterns is particularly interesting but quite

impossible with the design already published unless one duplicates the whole set-up as many times as the number of showers in a row to be studied. However, the problem here is that whilst one shower is still being studied to follow the decay of its activity over three to five hours, the next will maybe many more will arrive and the counter will be "engaged". Having come up against this problem the author hit upon the idea of tape recording the signals from the successive showers so that these can be counted out at any later time by replaying the tape through a suitable circuit into the digital register. The circuit described in this article was first designed for this particular application. It is only necessary to duplicate the Geiger head the necessary number of times and associate each head with a Veroboard circuit giving output pulses of a particular (in each case different) audio frequency. All signals can be fed on to one single continuously running tape track, using a perfectly ordinary domestic tape recorder. The Geiger counters will be "started up" one after the other as the successive showers occur and their samples are ready. It is not absolutely necessary even to keep checks of the clock because the relative timing will automatically be indicated later on the tape counter of the recorder! Upon subsequent playback at any later time a tunable audio resonant circuit (choke-coil and switched parallel capacitors to bring it to resonance at the various channel frequencies) is fed from the extension speaker terminals of the tape recorder and in turn feeds a simple rectifier circuit, much the same as an ordinary diode detector arrangement, for reconstituting the original Geiger counter pulses. Each channel, i.e. each shower, can then be played back and registered in detail in the digital register by tuning to each channel frequency on successive runs. Only a single digital register unit, running correspondingly longer, is thereby required. Furthermore, rains and snows occurring at night, even if only single, can be recorded and analysed on the digital register the next day. It is only necessary to get up in the middle of the night to switch the Geiger counter and the tape recorder on!

A different solution would be to use a digital register with facilities for printing out the count at predetermined regular intervals on an automatic basis. This will solve problems of work at night but still not help in the matter of recording many showers whose radioactive overlap in time. Short of duplicating the whole equipment several times there is no other sensible solution apart from the use of the Veroboard circuits described in this article in conjunction with an ordinary domestic tape recorder.

### Modulated Continuous Wave (MCW) Telegraphy for "Ham" Transmitters

A useful incorporation for the Veroboard circuit is shown in Fig. 3 which itself again has a variety of specific uses. Bursts of the characteristic audio frequency are obtained at an amplitude which is adjustable with VR3 (as volume control) in rhythm with the tapping of the Morse key. R20, C5 and R21 serve as key-click filter in this

—continued on page 1068



# How to Align a Receiver Without Test Equipment

BY GORDON J. KING

IT often happens that the enthusiast finds himself in a spot when it comes to the alignment or realignment of home constructed receivers and receivers in for repair. This is because the service sheet or building instructions stipulate the use of a signal generator for this exercise, such an instrument not always being in the possession of the enthusiast. Indeed, the radio beginner may yet have been able to acquire only the essential multi-range test meter.

Nevertheless, it is possible successfully to align and realign radios, including a.m. and f.m. sets and transistor portables, without any instruments at all, and this article tells how it is done.

## Misalignment Symptoms

The term alignment implies the trimming and tuning of the various radio-frequency (r.f.),

stations and being dead to more distant stations and weak signals. Misalignment can also cause poor reproduction owing to a restricted or distorted response, while the breakthrough of adjacent stations can prove troublesome if the response of the tuned circuits is too wide.

## Trimming

Let us look first at the tuned radio-frequency (t.r.f.) receiver, which is the simplest of all types so far as alignment is concerned. Such a receiver is shown in the form of a block diagram in Fig. 1. From the tuning aspect we have two stages, the tuned r.f. amplifier and the detector. The detector produces the audio signals which are amplified and applied to the loudspeaker.

It is the purpose of the r.f. amplifier to receive the very weak aerial signals, to amplify these and then pass them on to the detector. The aerial is supplying the r.f. stage with hundreds of signals, so it is essential for that stage to select or tune the required signal. Likewise the detector stage must tune to the required signal. Thus, both the r.f. amplifier and the detector must tune to the same frequency simultaneously.

Tuning in most cases is accomplished by tuning capacitors. In the early days of radio separate tuning capacitors were used for the r.f. amplifier and detector, the exercise being first to tune the

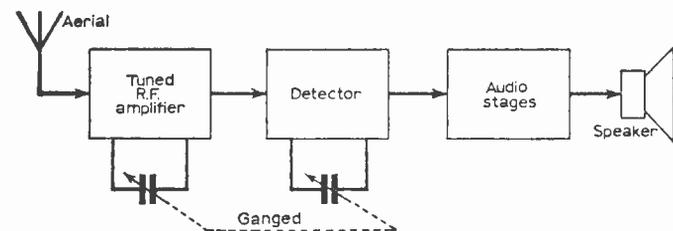


Fig. 1: Block diagram of tuned radio-frequency receiver.

oscillator and intermediate-frequency (i.f.) circuits for optimum tracking, sensitivity and response. A set which is completely out of alignment will not usually function at all, while a set whose alignment is not right will exhibit various symptoms.

One is an inaccuracy of scale calibration. That is, for example the Light Programme may tune on Radio Luxembourg instead of the correct 1,500 metres. Moreover, the "tracking" may be wrong, giving the correct calibration on stations, say, at the high frequency end of the medium wave band and incorrect calibration on stations at the other end of the band.

Another misalignment symptom is poor sensitivity, the set working only on powerful local

detector to pick up the signal and then tune the r.f. amplifier for maximum sensitivity (to get the signal as loud as possible).

Modern receivers, of course, feature ganged tuning capacitors, as Fig. 1 shows, and it is important that each section of the gang tunes to exactly the same frequency over the whole tuning range.

The design of the ganged capacitor and associated tuning coils ensures that this happens reasonably well but final trimming is necessary for correct dial calibration and optimum sensitivity over the bands. It should be noted that with t.r.f. sets the dial calibration is established by the detector tuning and the sensitivity by the r.f. amplifier tuning.

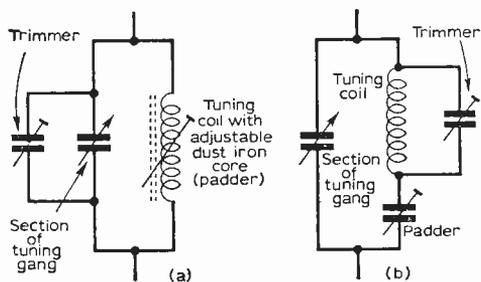


Fig. 2: At (a) trimming is effected by a preset capacitor across the tuning gang and padding by an adjustable dust-iron core in the tuning coil, while at (b) a preset capacitor across the coil serves for trimming and a similar type of capacitor, though larger value, in series with the tuning coil for padding.

**Padding**

While it is relatively easy to arrange for the two circuits to tune to the same frequency (or wavelength) at one point on the dial it is not quite so easy to arrange for the tuning to be accurately maintained over the whole of the dial. The simultaneous and accurate tuning of more than one tuned circuit is called "tracking".

To secure good tracking most t.r.f. sets (and all superhet sets) embody what is called a "padding adjustment". This consists either of a small trimmer-type capacitor or an adjustable dust-iron core in the tuning coil.

In addition there are "trimming capacitors" on each circuit. In inexpensive t.r.f. sets the trimmers consist simply of compression type preset capacitors on each section of the tuning gang, while more expensive versions have separate trimmers (and padders) for each band.

The important points to remember are that the trimmers have the greatest effect on the tuned frequency at the high frequency (low wavelength) end of the band, while the padders have the greatest influence at the low frequency (high wavelength) end of the band. Examples of padders and trimmers are shown at (a) and (b) in Fig. 2.

The idea of trimming and padding then is to adjust the trimmers for correct calibration and optimum sensitivity at a frequency at the high frequency end of the tuning and the padders for like conditions at the low frequency end of the tuning.

**T.R.F. Example**

Now let us suppose that we have a t.r.f. set that is in need of trimming and no instruments at all. The set should be switched on and allowed thoroughly to warm up. A good aerial should be connected and the volume control turned to maximum. The first thing to do is to get the circuits into approximate alignment. This can be done by carefully listening at the speaker while tuning the set over the band. When the local station is heard the r.f. *trimmer* should be adjusted for maximum output.

Next the calibration should be attended to. Say the local station is the long wave Light Programme and that this is coming in at 1,600m instead of the correct 1,500m. This means that more capacitance is required on the *detector* trimmer. A compression type should be screwed in and the station followed by tuning the set as the trimmer is adjusted until the correct calibration is established. The r.f. trimmer should then be readjusted for maximum output at the correct tuning point on the dial.

For final adjustment the set should be tuned to a station (say Radio Luxembourg) at the top end of the medium wave band, *trimmed* first detector and then r.f. wise and then tuned to a station at the bottom end of the band and then *padded* detector and r.f. wise.

It is generally necessary to repeat these adjustments until no further improvement can be obtained at both ends of the band—both for calibration and sensitivity. It will then be found that stations between the two alignment points will tune correctly on the dial and that the sensitivity is maintained over the band.

If the station is tuning too low on the dial, say 1,400m for the Light Programme instead of 1,500m, the detector trimmer should be screwed out. In some cases the trimmer on a completely misaligned set may not give the correct calibration over its range. In that case the trimmer should be set to its approximate mid-setting and the padder adjusted to give the correct tuning point. After this, of course, the process as detailed above should be carried out.

For a delicate setting of sensitivity, when the r.f. adjustments are being made, the aerial should be very loosely coupled to the set by winding a few turns of the aerial wire round the aerial socket or lead of the set. This will ensure that the r.f. circuits are not swamped by aerial capacitance.

It is generally best first to align the medium wave band, followed by the long wave band and then the short wave band if fitted.

**Superhet Principle**

A superhet type receiver is a little more difficult to handle but, once the basic principle is understood, there should be no undue problem. Fig. 3 shows the block diagram of this type of set. Here the signals in the aerial are applied to the mixer along with a signal from the local oscillator. The aerial and oscillator signals are effectively "mixed" in the mixer and the output is either the sum or the difference in terms of frequency of the two signals.

As an example, suppose that the incoming signal is at a frequency of 150kc/s (that is 1,500m—the wavelength of the Light Programme) and the oscillator is producing a signal at 320kc/s. In the mixer these two signals beat together and their sum gives a frequency of 470kc/s, while their difference gives a frequency of 170kc/s.

In practice either the sum or the difference frequency is selected and tuned by the intermediate frequency (i.f.) tuned circuits. The standard a.m. i.f. these days is 470kc/s, so the sum frequency of the example given above would be selected.

If the difference frequency is selected as the i.f. then the oscillator would produce a signal of 620kc/s to beat with the 150kc/s of the Light Programme (i.e. 620 minus 150 equals 470).

Clearly then the mixer and oscillator tuning must always be out of step with each other over the whole tuning range by an amount equal to the i.f. This is one thing that the alignment process has to ensure. It also has to ensure that the i.f. tuning is correct and that each i.f. transformer winding is tuned to the same frequency.

Let us assume that we have a completely misaligned set to deal with. What we want is breakthrough of some sort of signal just to get a start on tuning the i.f.s. for as these come into tune so the sensitivity of the whole set rises and the remaining alignment becomes possible using off-air signals.

### Peaking the I.F.s

One way found by the author that can be adopted to peak the i.f.s somewhere within their tuning range is to connect the screen of the television aerial's downlead, via a 100pF capacitor, to the signal grid of the mixer section of the frequency changer valve (note that the frequency changer is the valve that performs both functions of mixing and producing a local oscillator signal. Communications type sets and certain domestic models employ separate valves for mixer and oscillator).

When this connection is made and the set's volume control turned fully up, slight clicks and a hiss can be heard in the speaker. If the i.f.s are miles off tune the noise output will be very weak, but as the transformers are brought into tune so the output will increase and a Continental station may be heard in the background.

The idea then is carefully to adjust the i.f. cores in turn, starting from that nearest to the detector (see Fig. 3) and working back towards the mixer (frequency changer) until the background disturbances are at their loudest. When this has been achieved one can rest assured that the i.f. windings are all tuned to the same frequency.

This may not be the exact i.f. frequency but it will not be a long way out if the noise peak is arranged to occur when the trimmers are approximately halfway within their range of adjustment.

An adjustment of greater accuracy can be made later if necessary.

Having established a setting for the i.f. tuning the next step is to adjust the local oscillator and mixer tuning on a local station. This time the long wave should be adjusted first and, since the Light Programme puts a strong signal into most areas, this is a good station to work with.

With the television downlead connected still to the mixer signal grid the set should be switched to long wave and the tuning carefully adjusted until the Light Programme is heard. It may be very weak and well off calibration, but if the set is without fault, apart from being misaligned, then it will be found somewhere on the dial.

When it is found the long wave local oscillator trimmer should be adjusted step by step to put the Light Programme nearer and nearer the correct point on the tuning dial until eventually the correct tuning point is established. Tests will have to be made to see which way the oscillator trimmer needs to be turned to move the station tuning in the required direction.

The programme should now be coming in very loud, though interference and whistles may be troublesome. At this stage the television downlead should be disconnected and the correct aerial plugged into the proper aerial socket (if fitted). The signal will now be weakened again but it will soon be brought back to its correct volume by adjusting the mixer trimmer. The interference and whistle should then disappear.

### Snags

The set is now in approximate alignment on the long wave band but to arrive at that condition several snags may be encountered. It may be found, for instance, that the Light Programme cannot be tuned at the correct position on the dial at any setting of the oscillator trimmer. In that event a check should be made to ensure that the dial drive is working properly and that the cursor (or dial) corresponds to the high frequency (low wavelength) end of the scale when the gang is fully open and to the low frequency (high wavelength) end when fully closed. A check should also be made to ensure that the gang spindle or dial drive is tightly secured and not slipping in any way.

If all is well here a badly misadjusted long wave padder may be responsible. Initially this should be set to the centre of its adjustment. If this is correct then the i.f. is too far away from its correct frequency.

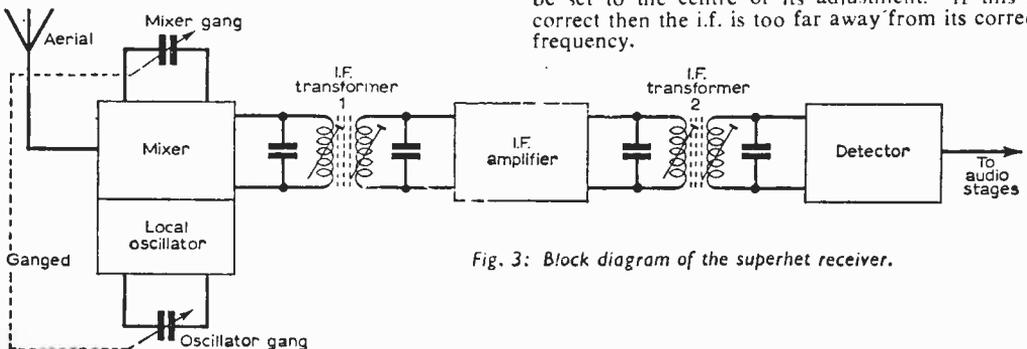


Fig. 3: Block diagram of the superhet receiver.

To correct for this the long wave oscillator trimmer should be adjusted as far as possible to bring the tuning as close as possible to the Light Programme (1,500m) on the dial. It will either be wide open or very tightly compressed. If wide open it should be closed up several turns or if tightly compressed it should be opened a little to give scope for eventual further adjustment. The Light Programme should then be retuned on the dial, the tuning error being a little greater than previously of course.

The idea now is to adjust the i.f. tuning to correct the tuning error. This is not difficult. The core of the winding connected to the detector

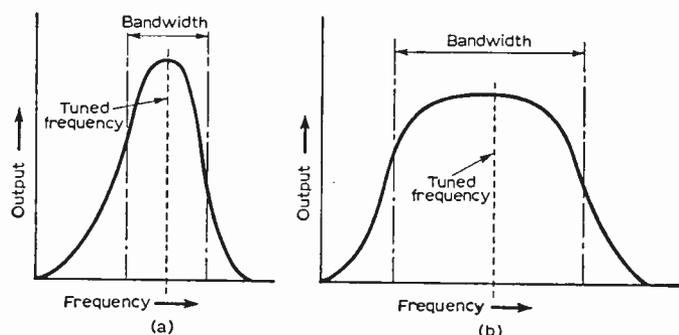


Fig. 4: Response curves. The narrow curve of restricted bandwidth (a) may attenuate the treble response and also aggravate the effects of oscillator drift in f.m. sets, and in f.m. sets the wider response of (b) is often to be preferred. A response of extended bandwidth cannot, however, be used in a.m. sets for fear of adjacent stations breaking into the wanted tuned station.

should first be adjusted—one way and then the other to find out which way the trimmers need to be adjusted to give correction—a little at a time to bring the tuning nearer to the correct point on the dial.

This should be done in stages and after each stage the remaining three i.f. cores should be adjusted for maximum output. Eventually it will be found that the i.f.s will peak when the dial is tuned spot on the Light Programme calibration mark.

One can then be certain that the i.f.s are very closely tuned to their correct frequency, for only if that condition exists will it be possible to establish the correct dial tuning within normal range of the oscillator trimmer.

Once the i.f.s are correctly tuned, alignment of the rest of the set resolves almost to that as explained for t.r.f. sets. Trimmers and padders on all but the most inexpensive receivers exist for each band and these are adjusted respectively on a station marked on the dial at the top of the band and then at the bottom of the band, making repeat adjustments until the best tracking is achieved.

#### Trimmer Location

Some mains sets use a bank of trimmers and a corresponding bank of padders and unless the service sheet is available it may be difficult to

locate the adjustments for specific bands.

The oscillator trimmers and padders, however, can be discovered by touching the "live" side of the component with the blade of a screwdriver while a finger is resting on the blade (*keep the other hand clear of the chassis to avoid shock*). If, for instance, the set is receiving a medium wave signal, contacting the medium wave oscillator component in the manner described will detune the signal.

The adjusting components for the mixer or r.f. stage (note that some superhets also feature an r.f. stage with a *three-gang* tuning capacitor) when contacted in a like manner will give rise to loud clicks from the speaker. The trimmer or padder which is not in circuit at the time will result in zero response.

Sets using ferrite rod aerials need no special attention and the instrument-less alignment procedures outlined in the foregoing can be adopted with them also.

#### F.M. Sets

F.M. sets utilise the superhet principle and basically the alignment information already given applies also to this type of set. There are now plenty of f.m. stations on the air and very strong signals are delivered by local stations via correctly cut f.m. (Band II) aerials.

Frequencies of local stations are given in the *Radio Times*. The Light Programme has the lowest frequency and the Home Service the highest frequency. This is easy to remember taking the L of Light for low and the H of Home for high. The Third Programme has a frequency between the Light and Home.

The ratio detector or discriminator may need special attention after the basic alignment process. This should be adjusted for the best quality reception, ensuring that each tuning point has only a single major peak. Two or three peak tuning means that the i.f. response is faulty.

Magic eye tuning indicators can be of considerable assistance for instrument-less alignment. Such indicators increase in deflection for increase in signal strength. Thus they can be used as an output indicator to reveal when, say, the i.f. transformers are tuned to optimum frequency or when the tuned circuits are peaked.

I.F. transformers peaking in f.m. sets may **not** be desirable, for a sharp response (Fig. 4a) can suppress the higher order sidebands and impair the treble response. After peaking as a preliminary adjustment, slight detuning may be warranted to give a flatter top to the response as shown at Fig. 4b. Insufficient bandwidth can also aggravate oscillator or tuning drift effects on f.m. sets.

## PART TWO

## CABINET AND CHASSIS TECHNIQUES

BY F. L. THURSTON

**C**ABINETS for radio or test gear can be made from a number of different materials and in a range of styles. The principal materials for amateur use are aluminium, wood, and synthetics.

**Aluminium Cabinets**

The general hints given in Part 1 for making aluminium chassis also apply when making aluminium cabinets, i.e. drilling methods.

Sheet aluminium is best cut with the aid of a hacksaw, large holes with a fret saw using metal cutting blades. When marking out prior to bending, if the drawing shows *external* dimensions of chassis of cabinet, the score lines along which the bends are to be made must be marked *short* of the overall dimensions by the thickness of the metal for each bend.

When bending the metal, if a special bending machine is not available, a normal vice can be used. But if a depth of bend greater than about 3in. is required, as it will be for most cabinet making jobs, a carpenter's vice may be used, using a bending technique similar to that already outlined.

If no carpenter's vice is available, use pieces of wood, of suitable size, clamped to the metal with a pair of carpenter's clamps, the wooden blocks

being used in a similar fashion to the jaws of the carpenter's vice. The wood used should be of a fairly hard type if a good sharp bend is to be obtained.

Failing all of these alternatives, the bending operation can be performed at reasonable cost by one of the many firms that specialise in this kind of work, some of whom advertise in this magazine.

Several basic cabinet styles are available, and Fig. 7 shows a type made from a single sheet of metal forming an open-ended box into which a complete chassis and front panel assembly may be fitted. The front panel is bolted to the cabinet by means of "clinch" nuts secured into flanges at the front of the cabinet.

Clinch nuts are similar to normal nuts but have a tubular extension on one side which is drilled out to give clearance of the bolt. When the clinch nut is bolted to a piece of metal a hole is drilled of such a size as to just give clearance to the outside diameter of the tube and the hole is then counter-sunk.

The nut is then pushed into the hole from the blank side of the metal and the tube is peened over into the countersink, securing the nut to the metal panel. The inset of Fig. 7 shows the principle involved. If a suitable peening punch is not available a ball bearing can be used as a substitute.


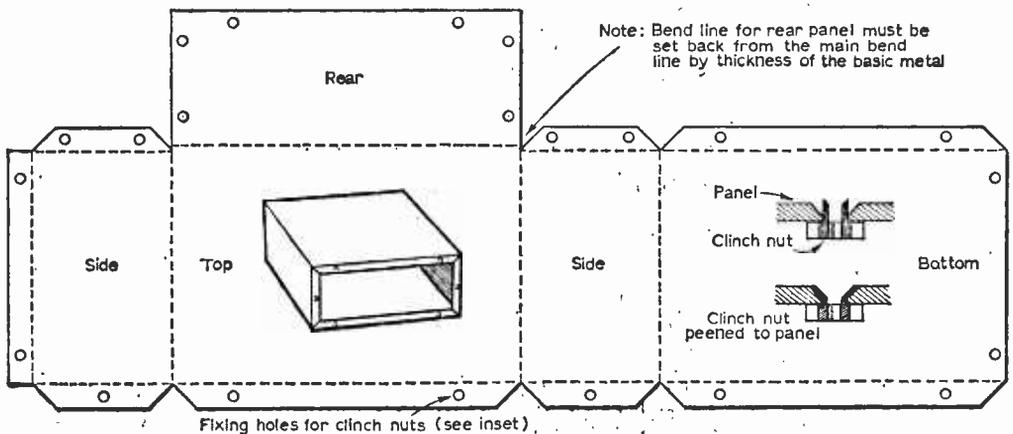


Fig. 7: An open-ended aluminium cabinet, made from a single sheet of metal.

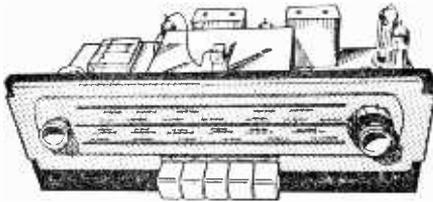**BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)**



Chassis size 15 x 8 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. in 2 colours, predominantly cream, 200-250v. A.C. only. Pick-up, Ext. Speaker, Ac., E., and Dipole Sockets. Five push buttons—OPF L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone control, 1000-1900 M., 200-550 M., 88-96 Mc/s. Valves E280 rect.; ECH81, EP89, EAB700, EL84, EC85. For 3-ohm speaker. 10 x 6in. ELLIPTICAL SPEAKER 25/- to purchasers of this chassis. TERMS: (chassis) £3.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. per yard. ALTERNATIVE DESIGN. L.W. 1000-1900 M., s.w. (9-15 Mc/s): M.W. 100-475 M.; V.H.F. 87-100 Mc/s; Gram position. Otherwise similar to above chassis. Price £15.15.0 (carr. paid). TERMS: £3.10.0 down and 6 monthly payments of £2.4.0. Circuit diagram 2/6.



**PUSH-PULL O.P. AMPLIFIER £5.5.0**

(6/- Carr.) Brand new 200-240 A.C. mains Bass, treble and vol. controls with valves E250, EC85 and 2-EL84's giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "dying panel."

**LAFAYETTE BRAND TAPE**

FULLY GUARANTEED AT RECORD LOW PRICES

MYLAR BASE		MESSAGE TAPES	
7in. Stand. play, 1,200ft. ....	13/9	3in. Stand. play, 150ft. ....	3/9
7in. Long play, 1,800ft. ....	21/6	7in. Stand. play, 1,200ft. ....	5/5
5in. Double play, 1,200ft. ....	16/8	5in. Long play, 900ft. ....	8/3
5 1/2in. Double play, 1,800ft. ....	24/9	5 1/2in. Long play, 1,200ft. ....	15/6
7in. Double play, 2,400ft. ....	27/6		
3in. Triple play, 450ft. (Plain white boxes) ..	13/9		
4in. Triple play, 900ft. (Plain white boxes) ..	24/9		
5in. Triple play, 1,800ft. (Plain white boxes) ..	46/8		
5 1/2in. Triple play, 2,400ft. (Plain white boxes) ..	60/8		
7in. Triple play, 3,000ft. (Unboxed) ..	82/8		

Postage 1/- per reel (4 or more post free)


**SELF-POWERED VHF TUNER CHASSIS.** Covering 88-95 Mc/s. Mullard permeability tuner. Dims. 8 x 6 x 6 in. high. Valves EC85 and 2-EP89's plus 2 diodes with E270 rectifier. Mains transformer. Fully wired and tested ONLY £8.17.6 (carr. paid). Room dipole 12/6. Feeder 6d. per yard.



**6-TRANSISTOR**

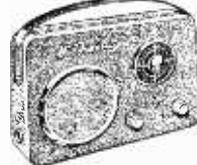**PORTABLE Fully Built**

The "SCALA" for only £7.10.6 carr. paid. 8 1/2 x 2 x 5 1/2 in. high. Choice of colours. Rexine. M.W. and L.W. Ferrite aerial Battery 2/9 extra. Printed circuit. Nicely styled. A professional job 3 1/2 in. speaker. Fully tunable M.W. and L.W. Superhet circuit.



**BATTERY ELIMINATOR**

For 4 Low Consumption Valves (96 grid 90v. 15mA and 1.4v. 125mA 42/8 (4/3). 200-250v. A.C. Also for 250mA. 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries, 4 x 2 1/2 x 2 1/2 in. and 3 x 2 1/2 x 1 1/2 in.

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Delivery by return. Terms available on Items over £5. Send 6d. (stamps will do) for 20 page illustrated catalogue. C.O.D. 2/6 extra.

ALL ITEMS GUARANTEED 12 MONTHS. VALVES 3 MONTHS. Regret overseas orders cannot be executed.

**GLADSTONE RADIO**

NOTE NEW ADDRESS:— (CLOSED WED.) 66 ELMS ROAD, ALDERSHOT, Hants. Aldershot 22240 (2 mins. from Station and Buses).

**"REALISTIC" 'SEVEN'**

7 Transistor Superhet. 350 Milliwatt output 4-inch speaker. All components mounted on a single printed circuit board size 5 1/2 x 5 1/2 in. in one complete assembly. Plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2 in. External socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistors, Cabinet, Speaker, etc. and full Construction Data: **£5.19.6** P. & P. 4/6.



PP9 Battery 3/8. Data and instructions separately 2/6. Refunded if you purchase the parcel. Any parts supplied separately.



**4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE**

PRINTED CIRCUIT. 4in. x 2 1/2in. 1 1/2in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player guitar and intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Two types. 200 mW. 35/-; 500 mW. 41/- (P. & P. 2/6 each.)

**4 to 5 WATT HIGH GAIN AMPLIFIER**

Only £5.15.0. (P. & P. 5/-). Suitable for record player, radio, tape after equalisation. Double wound mains transformer. Fully built. For A.C. mains of 200-250 v. 14 d.b. neg. feedback. Controls are volume (on/off), treble and bass. Contact cooled metal rectifier (bridge); ECH 83 and EL 84 valves. Output for 3 ohm speaker. Chassis size 8 1/2 x 6 in. (including spindles) overall height, including valves, 5 1/2 in. High and low input by Phono sockets.

**E.M.I. 4-SPEED PLAYER & P.U. (separate)**

8 1/2 in. metal turntable. 200-250 v. motor. Turnover head. Our price 59/6 (P. & P. 4/6).

**2 1/2 WATT AMPLIFIER—SPECIAL OFFER TO CLEAR STOCKS**

Our price ONLY 39/6 (post 5/-); a few only: valves EF91 and ECL82 with metal rectifier; 6 x 4 x 1 1/2 in. high (5 in. over ECL82). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax. input.

**GRAMOPHONE AMPLIFIERS AND PLAYERS**

1 1/2 watt type. With 6 x 4 in. speaker. Baffle 1 1/2 x 7 1/2 in. 200-240v. A.C. ECL82 and Rectifier. Tone and Volume On/Off switch. Two knobs. Ready to play. 49/6, post 5/-.  
4 watt type. Valves UY5, UF89 and UL84. 200-240v. A.C. Covered baffle 1 1/2 x 7 1/2 in. (6 in. speaker), 3 front controls; bass, treble, on-off/vol. 60/-, post 5/-. Double wound mains transformer. Cabinet to fit either type with plain motor heard £3 carr. pd. Complete record player in beautifully styled cabinet, fully built (NOT A KIT), £10.17.6. With 1A14 4-speed autochanger, or with Garrard Autostim 4-speed autochanger, £11.5.0. Single Player in Cab. 13 1/2 x 13 1/2 in. B.S.R. Monarch 4-speed deck, £8.9.6.

**ADVANCE INFORMATION ON 30 WATT TRANSISTORISED AMPLIFIER**

Chassis size 7 x 7 x 4 in. Input for 500-ohm (50 mV for full output) and 500K (5mV for full output). 14 d.b. neg. feedback. Controls are volume (on/off), bass, treble. Transistors 2 x NKT 401, 1 x 452, 2 x 262, 1 x 264 Fitted with carrying handle. Input standard Jack sockets. Output and supply on terminal block. Black matt finish. Price £15.15.0 (P. & P. 6/-).

Write for details

**TAPE RECORDER AMPLIFIER**

Fully built. Front panel 12 1/2 x 3 in. Chassis size 10 1/2 x 4 in. Valves EF86, EC83 and 2-EL84's. Controls (1) MIC. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor. (4) Tone. 2 Jack sockets for Tuner/P.U. and MIC-switch for superimpose. Separate power pack containing transformer and rectifier. For Collaro studio deck only. Price £8.14.0. (6/- P. & P.).

**4-SPEED AUTOCHANGERS**

BSR-CA14 .....	£5.19.6
GARRARD AUTOSLIM .....	£8.10.0
STEREO .....	£7. 8.0
AL TOSLIM DE LUXE AT9 .....	£10.19.6
STEREO .....	£11.10.0

Carr. 5/- each

**13 x 8 in. LOUDSPEAKERS 49/6 (post 2/6)**

Three ohm. Ceramic magnet of latest type. BRAND NEW.

**CM21. CRYSTAL MICROPHONE**

With 3.5 mm. jack plug. 12/6 (Post 1/6).

**HEATER TRANSFORMER**

Mains input giving 6.2v. 2 amp. Size 2 1/2 x 2 in. (2 1/2 in. over windings) 5/6 ea. Less 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 6, post free more than six.



**UNLIMITED OPPORTUNITIES** exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to success.

**STUDY IS EASY** with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

**YOUR ROAD TO SUCCESS** can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

**Take the right course now . . .**

**ADVERTISING & ART**

- Copywriting
- Layout & Typography
- Commercial Illustrating
- Oil & Water Colour
- BUILDING & CIVIL ENGR'G**
- Architecture, Bricklaying
- Building Construction
- Builders' Draughtsmen
- Builders' Quantities
- Interior Decoration
- Quantity Surveying
- Heating & Ventilation
- Carpentry & Joinery

**COMMERCE**

- Book-keeping
- Accountancy & Costing
- Business Training
- Office Training
- Purchasing, Storekeeping
- Secretaryship
- Shorthand & Typing
- Computer Programming
- Small Business Owners
- DRAUGHTSMANSHIP**
- Architectural Mechanical
- Drawing Office Practice

**ELECTRONICS**

- Computer (Educ. Subj.)
- Electronic Technicians
- Industrial Electronics

**FARMING**

- Arable & Livestock
- Pig & Poultry Keeping
- Farm Management & Accounts

**GENERAL EDUCATION**

- G.C.E. subjects at Ordinary & Advanced Level
- Good English
- Foreign Languages

**HORTICULTURE**

- Home Gardening
- Park Gardening
- Market Gardening

**MANAGEMENT**

- Business Management
- Hotel Management
- Industrial Management
- Office Management
- Personal Management
- Public Relations (IPR)
- Works Management
- Work Study
- Foremanship

**MECHANICAL & MOTOR ENGR'G**

- Engineering Maths.
- Diesel Engines, Welding
- Industrial Instrumentation
- Workshop Practice
- Refrigeration
- Motor Mechanics, etc.

**POLICE**

- Entrance Examination
- Pulice Promotion

**PHOTOGRAPHY**

- Practical Photography

**RADIO, TV & ELECTRICAL**

- Servicing & Engineering
- Radio (Construction (with Kits)
- P. M. O. Certificates
- Telecommunications
- Electricians\*
- Electrical Contractors

**SELLING**

- Company Reps.
- Sales Management
- Marketing

**WRITING FOR PROFIT**

- Television Scriptwriting
- Short-story Writing
- Free-lance Journalism

**INTENSIVE COACHING** for all principal examinations —G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges



**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....

Address.....

.....

Occupation .....

3.65

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

**VALVES SAME DAY SERVICE**  
**NEW! TESTED! GUARANTEED!**

SETS	1R5	1T4	384	3V4	DAF91	DFD1	DK91	DL92	DL94	Set	
	or 4 for 15/-	DAF99	DF99	DK99	DL99	4 for 22/6					
1A7GT	7/87B7	8/-	DF91	2/6	PC182	7/-	PC95	6/9	U47	8/6	
1D3	0/87C5	7/8	DF96	6/-	ECL96	9/-	PC97	7/-	U49	9/6	
1H3GT	8/37C8	7/8	DF97	3/6	EF99	6/3	PC98A	5/6	U50	5/-	
1N5GT	6/-	7/17	5/0	DI77	4/-	EF41	6/6	PC989	9/8	U52	4/8
1R3	4/97X4	5/-	DH81	12/6	EF42	4/6	PCF90	6/9	U54	8/9	
1R5	3/97ZAT7	3/8	DK92	8/-	EF90	4/3	PCF92	6/9	U78	8/6	
1T4	2/87ZAU7	4/8	DK91	4/8	EF95	5/-	PCF94	7/8	U91	9/3	
2P	19/87ZAX7	4/8	DK92	6/9	EF96	6/3	PCF96	9/8	U281	8/6	
3A5	6/97ZK7GT	4/3	DK96	6/6	EF99	4/3	PCF905	9/6	U291	9/-	
3Q4	4/107ZK8GT	8/0	DL33	7/3	EF91	2/6	PC182	6/0	U301	12/-	
384	4/97ZQ7GT	4/3	DL35	6/9	EF92	2/6	PC183	9/-	U301	12/9	
3V4	5/87ZRB7	8/6	DL92	4/8	EF183	7/6	PC184	7/8	U4020	5/9	
5Y40	4/67ZPL1	12/6	DL94	5/6	EL38	11/6	PC185	6/6	U4030	5/9	
5Y3GT	5/37ZP4	13/6	DL96	6/-	EL41	7/3	PEN44	6/6	U4032	8/-	
5Z4G/UT8-	20P5	11/9	DY86	6/9	EL84	4/6	PEN385	9/6	UBC41	7/6	
6AL5	2/-	25L6GT	4/8	DY7	8/-	EL85	5/6	PEN390	UBC81	7/6	
6AQ5	6/-	30CL18	9/6	EACB80	6/-	EM34	7/11	15/-	UBF80	8/6	
6AT8	4/-	30PL1	9/6	EAF42	8/-	EM14	6/3	PEN4VA	UBF89	6/9	
6BA6	6/-	30L15	9/6	ER141	4/-	EM81	7/3	12/6	UC9	8/6	
6BE6	6/3	30P4	13/6	ER191	2/-	EM84	6/3	PEN36C	UC94	8/-	
6BR6G	12/6	30P19	13/6	ER33	5/-	EM47	7/-	15/-	UC95	8/9	
6B10	6/-	30PL1	9/6	ER41	7/3	EY91	6/-	PL36	UCP80	3/6	
6B7B	5/8	30PL13	10/6	EAF90	6/-	EY66	5/6	PL81	7/-	UC142	7/6
6B8	3/8	35A5	14/-	EF83	7/8	EZ40	5/6	PL82	6/9	UC161	8/6
6F14	9/-	35L6GT	6/3	EFB99	6/-	EZ41	6/6	PL83	5/-	UC182	7/6
6F74	4/6	35Z4GT	6/-	EEL21	10/6	EZ90	4/-	PL84	5/9	UC183	9/8
6K7G	1/8	53K U	8/6	ECU40	4/6	EZ61	4/6	PX25	7/9	U41	7/3
6K7GT	5/8	ACV1P	EC981	3/8	PW4500	6/3	PY32	8/9	UF42	4/9	
6K36	4/3	19/8	EC92	4/8	EL14	14/6	PY28	8/9	UF43	8/9	
6K80T	7/6	AZ31	6/8	EC93	7/-	GZ37	8/9	PY80	5/8	U41	7/6
6P28	9/6	B36	4/6	EC94	6/3	KT76	8/-	PY81	5/9	U44	15/-
6Q7G	4/9	CU135	12/6	EC95	8/8	KT76	8/-	PY82	5/-	U44	6/3
6Q7GT	6/9	CL33	8/6	ECF90	6/3	ME1400	15/-	PY83	5/9	U421	7/-
6S17GT	4/9	CY1	12/6	EC97	5/8	M114	14/6	PY28	7/3	U41	4/9
6S7GT	3/9	DAC32	8/8	ECF86	10/9	MVB/PEN1	PY80	6/8	UY65	5/6	
6V6G	3/0	DAF91	3/9	ECH35	6/-	12/6	TH21C	9/6	V4B	12/6	
6V6GT	6/6	DAF96	6/9	ECH42	8/8	N18	4/10	TH233	7/9	W76	3/6
6X4	3/9	DC930	6/9	ECH51	6/3	N108	16/6	U25	8/6	W77	2/6
6X5GT	6/8	DF93	8/-	ECL80	6/9	OD3	4/6	U39 J*	8/9	W729	16/6

**READERS RADIO**

24 COLBERG PLACE, and at 35 TORQUAY GARDENS, STAMFORD HILL, LONDON, N.16. STA 4587 | REDBRIDGE ILFORD, ESSEX. CRE 7441

Post 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d extra. Any C.O.D. Parcel 4/3 extra.

**EXPRESS ELECTRONICS**

FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS				
TRIPLETONE HI-FI MAJOR	12 watt	...	...	£15.18.6
TRIPLETONE CONVERTIBLE	5 watt	...	...	£6.19.6
LINEAR	3 watt	...	...	£6. 6. 0
LINEAR DIATONIC	12 watt	...	...	£12.12.0
LINEAR CONCHORD	30 watt	...	...	£16.16.0
ADASTR4 3-3	4 watt	...	...	£4.13.6
LEAK TL12	14 watt	...	...	£18.18.0
LEAK VARISLOPE PRE-AMP	15 watt	...	...	£15.15.3
LEAK TL50	50 watt	...	...	£33.12.0
QUAD	15 watt	...	...	£22. 1. 0
QUAD STEREO/MONO PRE-AMP	...	...	...	£25. 0. 0

**LOUDSPEAKERS**

GOODMANS AXIETTE 8in.	6 watt	...	...	£5. 5. 0
GOODMANS AXIOM 10in.	10 watt	...	...	£6. 6. 0
GOODMANS AXIOM 201	15 watt	...	...	£10.15.0

**BAKERS 'SELHURST' 3 or 15 ohm**

JUNIOR 8in.	8 watt foam	...	...	£5. 5. 0
STALWART 12in.	15 watt	...	...	£5. 5. 0
BASS GUITAR 12in.	20 watt	...	...	£5. 5. 0
STANDARD Heavy Duty 12in.	20 watt	...	...	£7. 7. 0
BASS Heavy Duty 12in.	25 watt	...	...	£12.12.0
AUDITORIUM 15in.	35 watt	...	...	£18.18.0

**RECORD PLAYERS**

GARRARD SRP10 4-speed	...	...	...	£4.17.5
GARRARD AUTOSLIM 4-speed	...	...	...	£6. 7. 6
GARRARD AT6 TRANSCRIPTION	...	...	...	£9.17.6
GARRARD 4HF TRANSCRIPTION	...	...	...	£14.17.6
GARRARD A LAB SERIES	...	...	...	£17.10.0
GARRARD 301 LAB SERIES	...	...	...	£19. 5. 0

DELIVERED FREE U.K.  
S.A.E. WITH ALL ENQUIRIES

**EXPRESS ELECTRONICS**

32 SOUTH END, CROYDON, SURREY  
Telephone: Croydon 9186


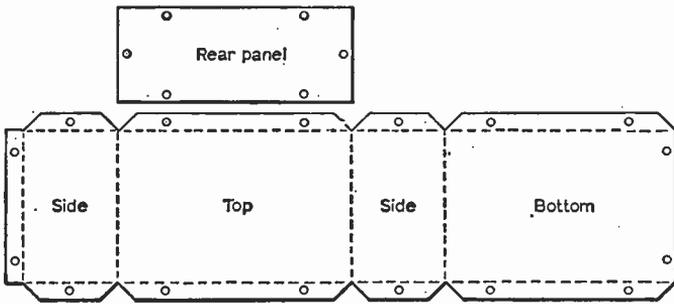


Fig. 8 (above): Another method of constructing a cabinet on the lines of that of Fig. 7, and Fig. 9 (below): an easier method of achieving the same result.

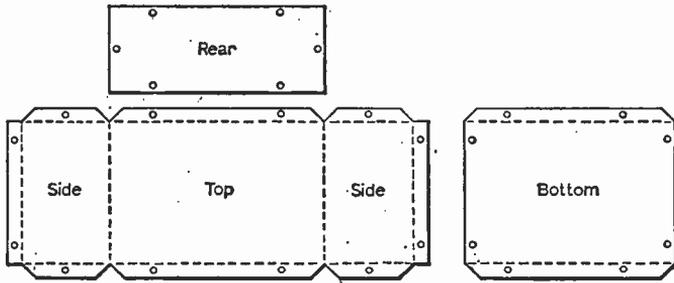

The cabinet of Fig. 7 is very robust but difficult to bend. The same final shape can be obtained by using a number of different methods of construction, as shown in Figs. 8 and 9.

A different style of construction is shown in Fig. 10. The front and rear panels are bolted directly to the chassis and a separate bottom plate and cover unit are used. A pair of clinch nuts are bolted to each side of the chassis and holes drilled in the side of the top cover to line up with them.

Four clamp plates, drilled out and tapped, are secured to the top cover with countersunk screws and line-up holes drilled in the front panel, enabling the whole assembly to be fitted together.

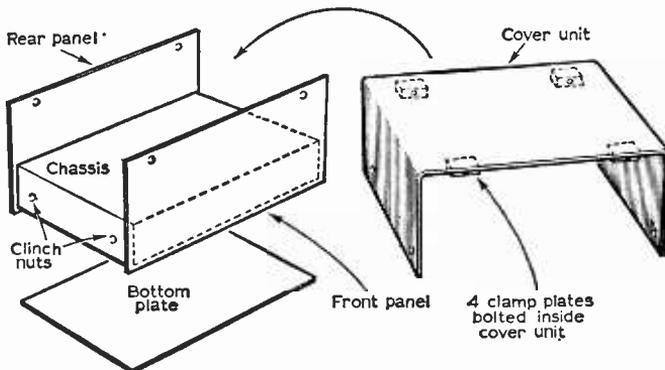


Fig. 10: Another approach to the problem of cabinet construction.

A method of construction which involves no bending of sheet metal at all is shown in Fig. 11. A skeleton frame, made from steel or aluminium angle, is assembled and individual top, bottom, front, rear and side panels bolted to it, using clinch nuts secured to the frame.

An advantage of this method, which is widely used for large commercial equipment, is that the frame can be used as a basic part of the chassis assembly, separate sub-units being bolted to it. Strengthening struts are added where required. When cutting the panels care should be taken to ensure that a good final fit is obtained, i.e., some panels may have to be made larger than the basic frame if unsightly cracks in the finished cabinet are to be avoided.


A variation on this theme is shown in Fig. 12, which shows a close up detail of a frame unit made from a composite assembly of  $\frac{1}{2}$  in. and  $\frac{1}{4}$  in. angle. The complete frame assembled in the same way as that of Fig. 11, but

the finished article now gives a number of recess areas, available between the  $\frac{1}{4}$  in. angle, to take each of the main panels, which may be bolted to the  $\frac{1}{2}$  in. frame.

The advantage of this system is that the panels can be cut to the dimensions of the recesses, without the danger of making expensive mis-calculations when allowing for overlap. Any slight errors will be masked by the recesses, and the complete assembly, when painted, has an attractive appearance, the  $\frac{1}{2}$  in. framework standing proud of the panels.

If ventilation holes are to be provided in the cabinet, the easiest method is to provide a cut out and bolt one of the commercially available grilles over it. Alternatively, a large number of drill holes can be provided as long as great care is taken in positioning them.

Ventilation louvres can be made by two methods. Fig. 13a shows a "handle" type and the "mould" required for making them. To make the mould, cut out a piece of steel plate, the same thickness as the depth of the louvres, the cut-out being "negative", and, after case hardening, bolt down to a hardwood base. Cut a slot in the panel to be formed, and press the metal slightly outward under finger pressure, then locate the

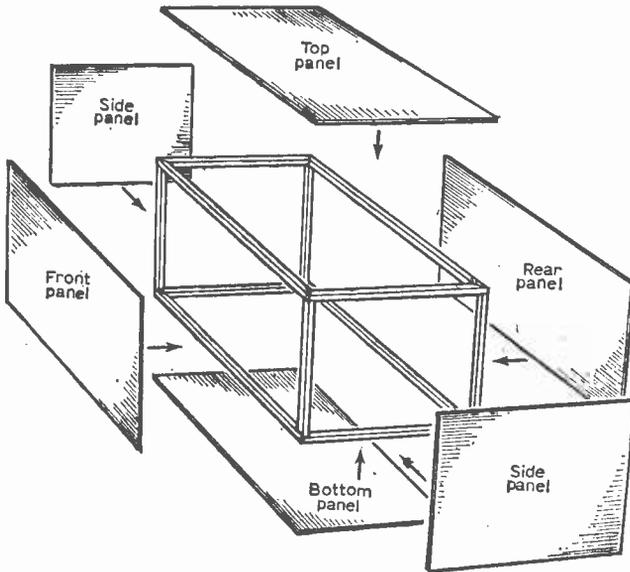

"lip" that results in the lower edge of the recessed mould. A soft mallet is used to force the panel into the shape of the mould.

When making the mould, keep the overall width only slightly greater than that of the louvre, otherwise it will not be possible to space the individual louvres reasonably close together.

The "venetian blind" type of slot (Fig. 13b) required no mould. The positions are marked out and cut, using a metal cutting fret saw after drilling a small pilot hole. Cut only as far as shown, and then, using either finger pressure or a pair of pliers, bend as shown.

Both of the above methods require a certain amount of practice before really good results are

Fig. 11: This method of construction requires no bending of metal.

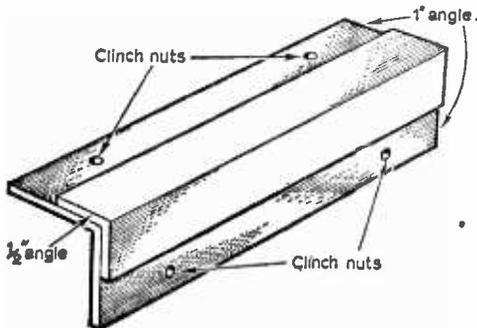


Fig. 12: 1/4 in. and 1 in. angled metal bolted together with countersunk bolts can be used to make a cabinet frame.

obtained, and a few test runs should be made on a piece of scrap aluminium first.

**Plastics and Insulating Materials**

Most plastics materials can be bent under the application of heat and thus may be used for some forms of cabinet construction. If sufficient heat is applied the material can be melted. Fittings such as nuts, bolts, hinges, etc., may therefore be heated and moulded permanently into the plastics if needed.

Most plastics are easily worked, and special glues are available for fitting plastics to plastics or to other materials. If only two-dimensional bends are required, the plastics can be heated locally and bent around a wooden former to obtain the required shape. If three dimensional shapes are required, it will be necessary to make a male or female mould and apply heat over a large area when shaping the material on the mould.

Most non-plastics insulating materials are non-malleable but can be cut and drilled fairly easily. Both of the materials mentioned above are best suited for use in the type of construction shown in Fig. 11, where simple panels are used.

Part Three Next Month

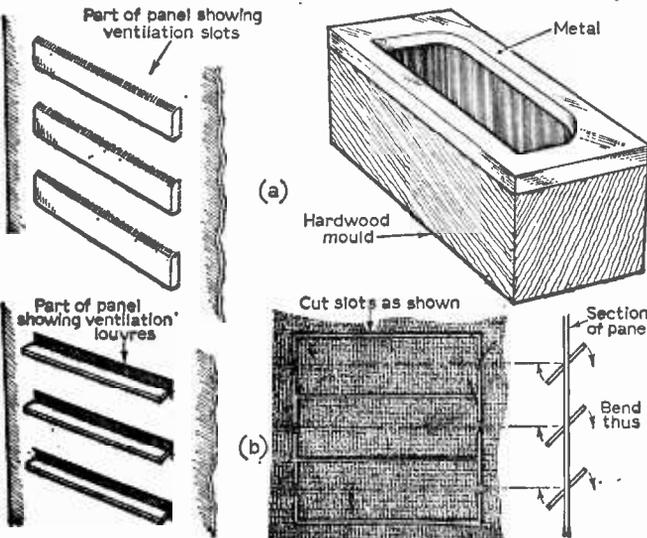


Fig. 13: Methods of forming louvres for ventilation purposes.

# Preventing Accidental Tape Erasure

There is no perfect system of preventing accidental erasure of wanted recordings and many recorders have mechanical or electrical "reminders" that the instrument is switched to "record" and, therefore, will erase any previous recording.

An additional precaution which will prevent erasure, unless a microphone plug or other signal source plug is plugged in the appropriate socket, is described below.

Using sockets of the Bulgín J14 type, the grid of the r.f. erase and bias oscillator valve is earthed until a plug is inserted and, of course, with the grid shorted to chassis erasure is impossible, even though the instrument is switched to "record".

This feature is well worth incorporating because if the instrument is being used for playback only and a microphone is not available for plugging-in, then the recordings are safe.

A single screened and insulated lead is taken from the oscillator valve grid pin to the jack socket (see diagram). The outer screen should be taken to the nearest chassis point at the valve socket.

This system cannot be used with recorder amplifiers which use a common output/oscillator valve, however the erase head feed or winding can be shorted via the jack socket but it will be found that the bias current will partially erase. This is better than losing the recording.

BY J. SCOTT

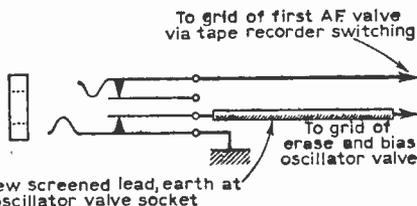


Fig. 1: The input circuit arrangement for the recorder with a single socket.

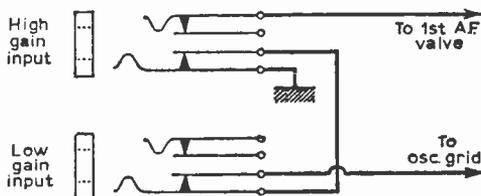


Fig. 2: The arrangement for recorders with two input sockets.

*You can't afford to miss these March issues!*

## "Practical Electronics"

- ELECTRIC CLOCK with digital display. A faceless clock with four Digitron tubes.
  - AUTOMATIC PARKING LIGHT. Dusk to dawn switching.
  - TRANSISTOR TUNER covering M.W. and L.W. bands.
  - VERSATILE OSCILLOSCOPE for servicing electronic equipment.
- Plus: another 8 pages of the Guide to Semiconductor Circuit Design.

on sale February 11th

## "Practical Television"

- IMPROVING THE P.T. CCTV CAMERA. Some further notes on this outstanding design.
- "DO-IT-YOURSELF" GUIDE TO TV SERVICING. Specially written for the lesser-experienced enthusiast.
- G3NOX/T. A description of this well-known amateur TV transmitting station.
- TIMEBASE STABILISATION, ELEMENTS OF CCTV, SERVICING TV RECEIVERS, and all the usual features, including the latest DX-TV news.

on sale February 18th

A COMMENTARY BY HENRY

# PRACTICALLY WIRELESS

## No. 7 The "H" Factor

ANYBODY who watched Prof. Colin Cherry expounding on the telly about Science and Communications, will have been struck by the idea that our boxes of electronic tricks were no more than links between the mysterious forces that direct our existence and the puny grey cells that fill the space between our ears.

The conception of information theory does not concern us here—which is just as well, for my ignorance of the subject is just as remarkable. But the implicit assumption that the means are infallible, given enough time for development, and only the ends matter, is rather alarming.

A recent report from the Equipment Reliability Committee of the Electronic Engineering Association only serves to confirm my view that the boffins are overlooking one vital point in their assessment of the electronic situation.

This report, for example, shows a graph failure rate of electronic equipment against time. As one might have expected, the curve starts high, swoops rapidly, levels out, then creeps up at an ever-increasing rate. Which means that the gear breaks down

more frequently, just after it is thrown together, settles to a comparatively trouble-free level for a while, then begins to break down again as it ages.

To some extent, we go along with that view. Too often, brand new sets conk out and investigations prove that the faults could—nay, should—have been foreseen in production. Things like dry joints, wrong components, early mechanical wear, and so on.

You and I, concerned mainly with our own little box of bombs, tend to give the benefit of the doubt to the manufacturer. Maybe one of the girls on the production line was mooning as our set went by and forgot to apply the solder gun. What we overlook is the fact that her lovesick lapse will have affected half a hundred other prospective owners, too.

So, in this report, the committee advocate the manufacturer delivering his product "only after the constant failure rate period has commenced. . .".

Doesn't that phrase strike a cold chill? The constant failure rate, mate, is the time you and me are going to be proud users of the equipment.

They have even worked out the probable frequency of breakdown, and computed a "Mean Time Between Failure", which they cleverly abbreviate to MTBF. From this, they work out a formula for reliability, saying, the MTBF over  $t$  hours being

$$\frac{t}{T}, \text{ then } P_s = e^{-\frac{t}{T}}$$

This gives the frightening calculation that for a chance of successful operation for various multiples of  $T$ , the MTBF required to give a 90 per cent chance of fulfilling a two hour mission successfully must be 2/0-1, or twenty hours. It makes you wonder how they ever got



A tendency to give off wild puffs of smoke . . .

Telstar up there, let alone working.

My point is that the boffins have overlooked a vital factor. This elusive parameter, the "H" factor—(H for Henry, I'm after a Nobel Prize)—must be inserted in any formula that attempts to assess reliability. It is the tendency of a piece of electronic gear to give off wild puffs of smoke, or horrid noises, or sudden bouts of unbearable silence, at the most embarrassing moments.



Just at the moment when the Director of the Electronological Institute is passing through, or when those political purseholders who haunt the men at R3 pay a visit, or when Aunt Mabel comes to tea, the "H" factor comes into play.

We have laboriously built the hi-fi rig, planned and glued the cabinetry, tackled all the wires out of sight, assembled our friends and neighbours for the preview and—presto—comes a power cut. Small use citing the Reliability Committee or quoting MTBF then. As your wife passes the coffee and makes with the small talk, you can muse on the "H" factor, and write another failure up to experience.



Maybe one of the girls was mooning. . .

# PRESELECTOR & B.F.O. UNIT

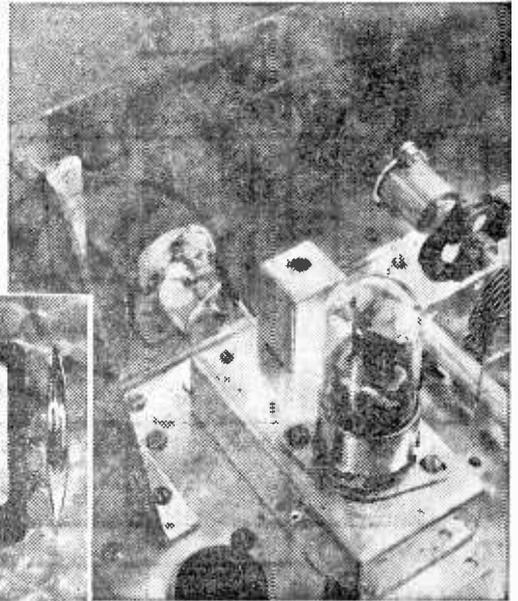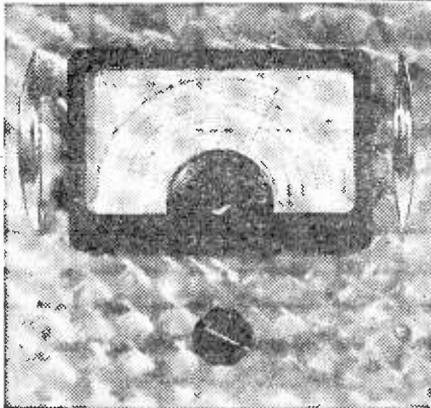

H. WEBSTER

## FOR THE BEGINNER'S S.W. SUPERHET

CONTINUED FROM PAGE 968 OF THE FEBRUARY ISSUE

IN a c.w. frequency transmission the carrier wave is unmodulated and means must therefore be provided to render the signal intelligible at the receiver. In the simplest type of receiver such as the detector and I.f. type this is often accomplished by making the detector oscillate at a frequency slightly removed from the incoming frequency.

The difference in the two frequencies is equal to the frequency of the beat note. This process whereby the detector itself provides the local frequency is known as the autodyne method. Another and more general method employed in the superheterodyne receiver is to use a separate oscillator. This oscillator, known as the beat

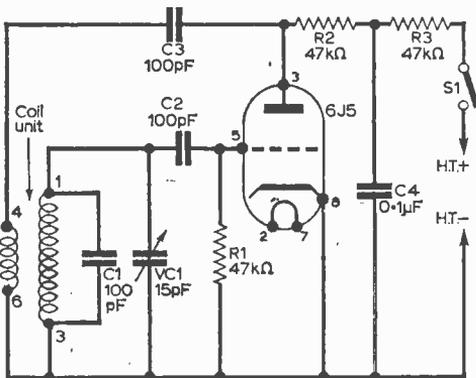


Fig. 7: The one-valve circuit of the b.f.o. unit.

### COMPONENTS LIST

**Resistors:**

- R1 47kΩ 1/2W
- R2 47kΩ 1W
- R3 47kΩ 1W

**Capacitors:**

- C1 100pF silver mica
- C2 100pF silver mica
- C3 100pF silver mica
- C4 0.1μF tubular
- VC1 15pF variable (Jackson C804)

**Miscellaneous:**

- V1 6J5
- S1 S.P.S.T. switch
- L1, L2 1.6Mc/s b.f.o. coil. Denco BF02
- International octal ceramic valveholder. Chassis top plate 4in. x 7in. (Home Radio). Knob, wire, etc.

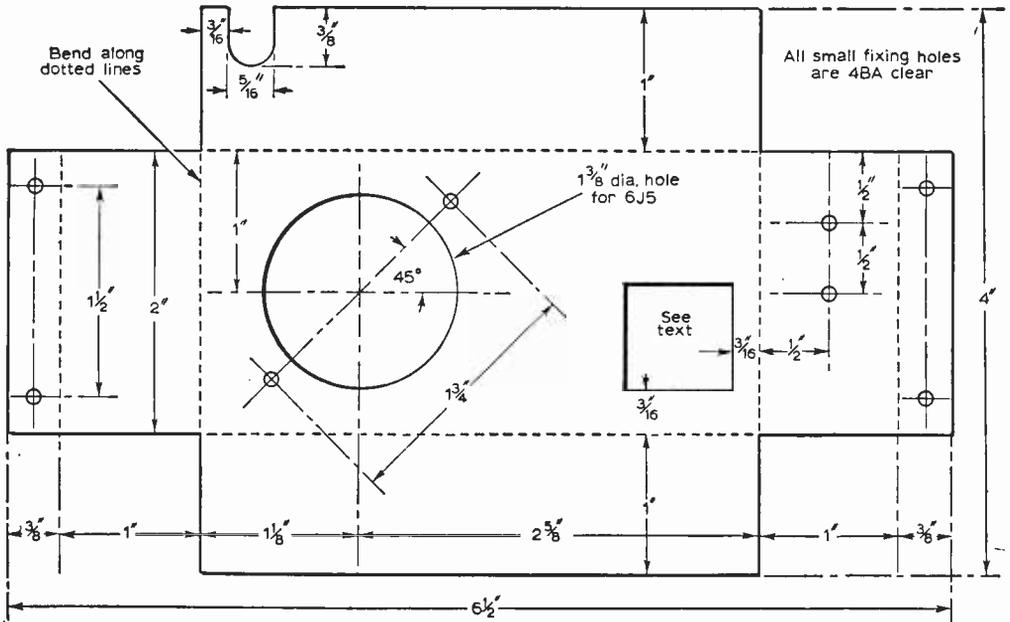


Fig. 8: Details of the b.f.o. chassis which is eventually attached to the main receiver chassis. This arrangement may be seen in one of the heading photographs on page 1055.

frequency oscillator, injects an unmodulated signal into the second detector circuit. The frequency of this oscillation can be varied over several kilocycles each side of the receiver intermediate frequency.

A further and important use for a b.f.o. is in the reception of single side band (s.s.b.) transmissions. Since these signals are generally transmitted with little carrier, means must be provided to insert the carrier at the receiver. A description of this technique will be given later in the article.

#### Circuit

The b.f.o. is built round a 6J5 medium impedance triode. The circuit diagram is shown in Fig. 7. L1, L2 is a Denco 1.6Mc/s beat frequency oscillator coil. The frequency of the oscillator can be varied a few kilocycles each side of the 1.6Mc/s i.f. by means of a panel-operated control VC1. Screening of the unit is of importance since harmonics of the b.f.o. may find their way into the front end of the receiver. Although the author did not find this troublesome it may be necessary to screen the 6J5 to reduce the b.f.o. injection.

#### Constructional Details

The b.f.o. unit is built on a small sub-chassis which is mounted on the main receiver chassis. Sufficient space is available between the output valve (6V6) and the gang capacitor. The sub-chassis is cut from a 7in. x 4in. piece of aluminium

to the dimensions given in Fig. 8. The method for mounting on the receiver chassis is given in Fig. 9.

Since the unit is comparatively small care must be exercised in wiring the components. It will be




A rear view of the completed preselector described in last month's issue.

Pioneers in  
build it yourself  
tuners and test  
equipment

**JASON**  
KITS

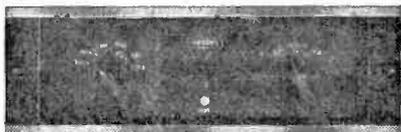Jason were first to produce a stable switched f.m. tuner for reception of BBC transmissions and an outstanding success has been achieved with the introduction of simple-to-operate switched tuners to receive both f.m. and TV sound transmissions. Jason tuners and test equipment offer a wide choice of models designed to meet present-day requirements and are a delight to build.



**JTV2 SWITCHED TUNER** for the reception of all BBC f.m. transmissions and BBC-1 and ITV television sound channels at the turn of a switch. Foster-Seeley discriminator. Built-in power supply. Sensitivity 10 $\mu$ V for 40 dB quieting. Audio output 0.4V approx. All components including turret and coil plate but less four valves **£14.0.4.**



**FMT2 F.M. TUNER** covering 88—108 Mc/s. Built-in power supply. All components, less four valves **£9.9.0**, less power supply components **£7.15.0.**  
**FMT3 TUNER** similar appearance to above, but for fringe area reception. All components, less valves **£10.9.0**, less power supply components **£8.15.0.**



**JTL TAPE PREAMPLIFIER** designed to suit any tape deck or head. Will simultaneously record and playback stereo or mono using two or four track heads. Especially recommended for use with the Lorlin SB26 tape deck. (Send for details). All components including valves **£22.1.0.** Ready built and tested **£30.9.0.**

**OTHER JASON KITS**

- FMT1 F.M. TUNER**, less valves **£5.19.0.**
- MERCURY II** Switched Tuner, less valves, **£9.15.4.**
- ARGUS** Transistor m.w. Tuner, complete, **£7.10.0.**
- OG10** Oscilloscope, less c.r.t., **£18.10.0.**
- W11** Wobbulator, complete, **£14.19.0.**
- EM10** Valve voltmeter, complete **£23.0.0.**
- SB26** Tape Deck (built only)  $\frac{1}{2}$ -track mono **31 gns.**  
4-track stereo **39 gns.**




**AG10 AUDIO GENERATOR.** Excellent stability with constant output over entire range. Tunes from 10 c/s to 100 Kc/s in four switched ranges. Square wave or sine wave outputs. Square wave rise time less than 2 $\mu$ /sec. at all frequencies. Minimum calibrated output 100mV. Self powered. All components, including valves **£15.19.0.**

Write for descriptive leaflets and name of nearest stockist.

**JASON**  
KITS

VISIT OUR  
NEW WEST END  
SHOWROOM

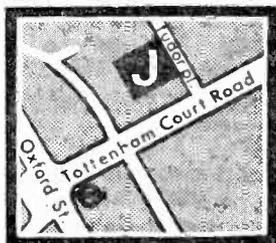18 TUDOR PLACE, TOTTENHAM CT. RD., LONDON W.1.  
Tel: MUSEum 4666/8




# Easy-to-make cabinets to house your hi-fi

- 1 Tape deck/record storage
- 2 & 5 Loudspeaker
- 3 Record storage
- 4 Radio/record player

These easy-to-make sectional units are part of an outstanding new range of designer-styled cabinets for high fidelity sound equipment. They are the direct result of a close collaboration between well-known industrial designer Frank Guille Des RCA FSIA and Percy Wilson MA, technical editor of "The Gramophone" and prominent authority on acoustical engineering.

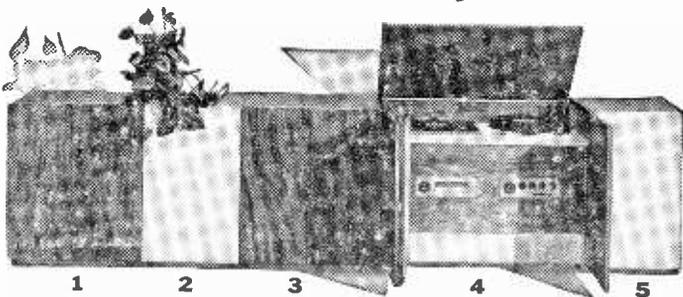The cabinets which will house almost any combination of Hi-Fi equipment have been especially designed for making in Vipboard. Vipboard



is a fine quality board with superior screw-holding qualities; specifically made for easy and economical furniture-making within the home. It comes in 20 standard sizes, fully veneered on all surfaces and ready

to polish. No special skills are required, and you need only basic household tools. Total cost of Vipboard for the cabinets shown above is £27.0.4. The individual cabinets cost from £3.8.11 (units 2 and 5).

## Vipboard fully veneered chipboard with the natural wood finish

Find out how you can choose and build the units best suited to your Hi-Fi requirements—at a fraction of their "shop price". Ask for **Free Instruction Leaflets** and the **Vipboard Furniture Brochure** at your local Vipboard stockist, or write to: Vipboard Division, G.W.E. Boards Limited, 6 John Street, London WC1. Holborn 8421

*- all these and hundreds more*

Mon. Sat. 9 a.m.—5.45 p.m. Wednesday 1 p.m.  
Lunch 1.30 to 2.30

Special 24 Hour Express Mail Order Service

AZ31 12/6	EBF89 7/6	EL89 8/-	EZ41 7/-	PCL85 9/-	U25 10/-	UL84 6/-	5Y30/GT 3/6	6C5GT 3/6	6U50 7/6	12AX7 5/6
DAF91 4/6	ECU81 4/-	EP91 5/-	EZ80 5/6	PCL84 7/-	U26 10/6	UY41 7/6	6C6 6/6	6U6G 4/-	12BA6 7/6	
DAF96 6/6	ECC82 5/-	EP92 4/-	EZ81 5/6	PCL83 7/6	U191 13/6	UY85 5/6	6AT 12/6	6U6GT 7/6	12BE6 7/6	
DF91 3/-	ECC83 5/6	EP98 1.7s	UZ32 12/6	PCL86 10/-	U301 15/6	VP48 12/6	6A4 5/6	6U6 10/-	6X4 4/6	12K7GT 5/-
DF96 6/6	ECC84 6/6	EP183 9/-	RL4DD 12/6	PL36 11/6	G801 19/6	VR150/30 7/-	6AL5 3/6	6U6 5/6	6X5G 5/-	12K8GT10/-
DK91 5/6	ECC85 6/-	EP184 8/-		PL81 7/6	UABC80 5/6		6A36 4/-	6P6 5/6	6X5GT 8/6	12Q7GT 6/-
DK92 7/-	ECH85 12/6	EL33 17/6	KT66 17/6	PL82 7/6	UAF42 8/6	WR1M 6/-	6AQ5 6/6	6H6 2/-	6Y5012 12/6	12SQ7 12/-
DK96 7/6	ECH82 8/6	EL41 9/-	KT81 10/6	PL83 7/6	UB41 8/-	N61M 13/6	6AT6 4/6	6J50/GT 7/6	7B6 21/-	19AQ5 8/-
DL92 5/-	ECH81 7/-	EL42 9/-	KTW61 7/-	PL81 7/-	UB80 7/6	N78 20/-	6B8Q 2/6	6J7G 5/6	7B7 8/6	25Z4 7/6
DL94 7/-	ECH83 5/6	EL84 5/6	MU14 17/6	PY32/3 10/-	UBF89 7/6	N7J 40/-	6BA6 5/6	6J7G 5/6	7C6 10/6	35LGT 8/6
DL96 6/6	ECL80 6/6	EL85 9/6	N78 22/6	PY81 9/-	PCL42 8/6	IR5 7/6	6BE6 5/6	6K7G 5/6	7C6 9/6	35W4 0/6
EAB90 5/6	ECL82 6/6	EM80 8/-	OZ4 5/-	PY82 9/6	UCL81 7/-	L85 4/6	6BJ6 8/-	6K7GT 2/6	7H7 6/-	35Z4 6/6
EAF42 8/6	ECL86 5/6	EM81 8/-	PY84 6/-	PY85 7/6	UCL82 8/6	UPI 7/-	6BR7 10/6	6K8. 3/-	787 13/-	50C5 8/6
EB91 5/6	EP41 7/6	EM84 5/6	PX89 8/6	PY800 8/6	UL83 9/-	3Y4 5/-	6BL8 12/6	6K8GT 9/6	7Y4 2/-	80 7/6
EB41 8/-	EP40 5/-	UV31 7/6	PCF80 7/-	PZ30 1.6s	UF41 7/6	3X4 7/-	6BW6 8/-	6L6GT 7/6	8D3 4/-	90C1 25/-
EBF80 7/6	EP45 5/-	EV86 7/6	PCF86 9/6	S861 3/-	UF89 7/6	5U4G 4/-	6BW7 4/-	6Q7G 6/-	10P1 10/-	98CV 25/-
EBF83 8/-	EP86 7/-	EZ40 7/-	PCL82 7/6	U14 9/-	UL41 7/6	5Y4G 9/-	6C4 3/6	6Q7GT 10/-	12AU7 5/-	807 9/6

COMPLETE VALVE LIST FREE WITH ORDER

OBsolete VALVES A SPECIALITY SEND FOR QUOTATION

TERMS OF BUSINESS C.W.O. or C.O.D. 4/2 PACKING CHARGE ON ALL C.O.D. ORDERS. POSTAGE 6d. per VALVE

Mon.—Sat. 9 a.m.—5.45 p.m. Weds. 1 p.m.  
Lunch 1-30 to 2-30

BRAND NEW TRANSISTORS			
OC35 10/-	OC72 8/-	OC81D 5/-	
OC42 6/-	OC74 8/-	OC81m/pr 12/6	
OC44 5/-	OC75 8/-	OC82 8/-	
OC45 5/-	OC77 8/-	OC82D 6/-	
OC71 5/-	OC81 5/-	OC710 6/-	
SILICON RECTIFIERS			
400 volts 350 mA	...	...	7/6 each

SETS OF VALVES			
IR5, IS5, IT4, 354, 3V4	...	...	Set of 4, 17/-
DAF91, DF91, DK91, DL92, DL94	...	...	Set of 4, 17/-
DAF96, DF96, DK96, DL96	...	...	Set of 4, 25/-

**R.S.T. VALVE MAIL ORDER CO.** Tel: MITcham 6202  
Open Daily to Callers  
211a STREATHAM ROAD MITCHAM SURREY

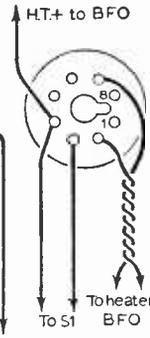
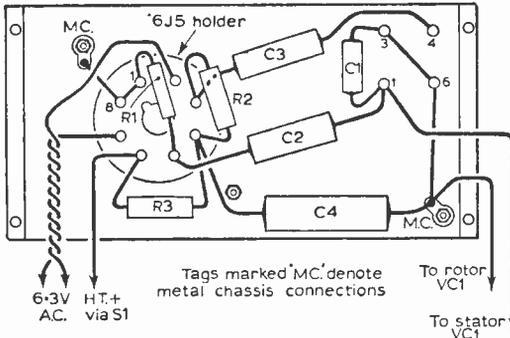
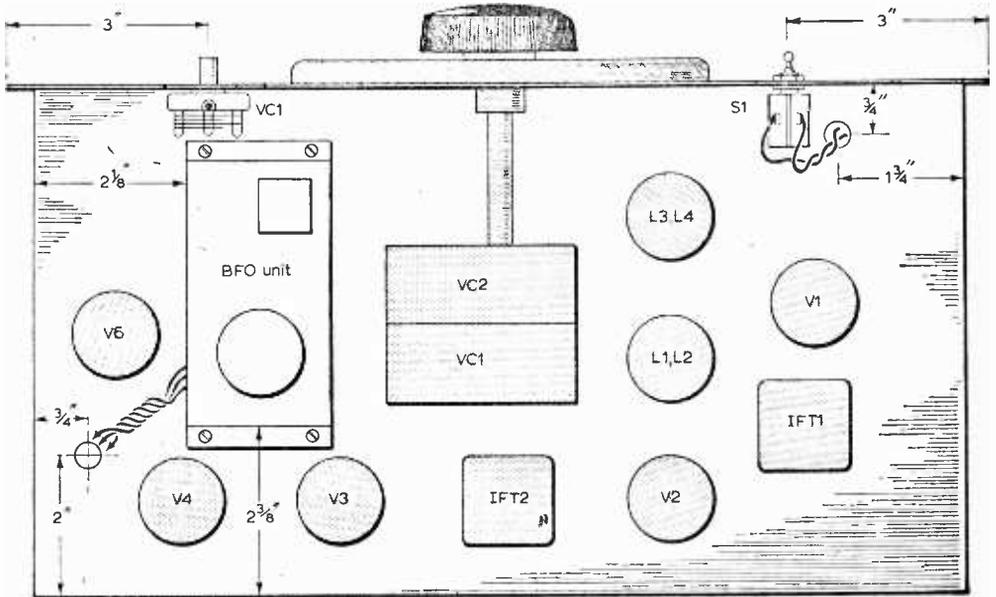


Fig. 9 (above): The position of the b.f.o. unit on the main chassis. The shaded parts indicate components on the original receiver.

Fig. 10 (far left): Under-chassis wiring of the b.f.o. unit.

Fig. 11 (left): Additional wiring from the power input socket of the main receiver, to provide for the b.f.o.

noted that no fixing details are given for the b.f.o. coil unit. Fitting is best done using the unit itself as the template.

A point-to-point wiring diagram is shown in Fig. 10. When wiring is complete the usual routine check is made of the resistance between h.t. positive and chassis. If this is satisfactory the unit may be bolted to the receiver chassis and the heater and h.t. leads taken through the hole in the receiver chassis. The power leads are soldered to the tags of the octal input socket at the rear of the receiver. The relevant details are shown in Fig. 11.

**Adjustment and Operation of B.F.O.**

Adjustment of the b.f.o. is best done with the aid of a signal generator such as was described in the original article. Inject an unmodulated signal of 1.6Mc/s via the top cap of the frequency changer. Set the b.f.o. panel trimmer to mid-capacity and then carefully adjust the dust core of

the b.f.o. coil until zero beat is obtained. The setting is now correct.

If no signal generator is available the coupling between the grid and anode of the i.f. stage pentode can be increased to the point where the stage breaks into oscillation. A gentle hissing noise will be heard at this point. The b.f.o. is adjusted until zero beat is again obtained.

**Single Side Band Reception**

S.S.B. signals can be rendered intelligible by the following procedure. The signal is accurately centred on the main receiver. If the preamplifier is used the gain control is set to minimum and the receiver volume control turned to maximum. VR1 is now adjusted until a weak signal is heard. Switch on the b.f.o. and adjust the pitch control until intelligible speech is obtained. A little practice may be needed before the correct setting is obtained.




# A VOLTAGE STABILISED V.F.O.

**T**HE variable frequency oscillator described here may be used to control the two-band speech transmitter (January, 1965, P.W.) so that no crystals are needed. It enables the transmitter to be tuned to any frequency in the 1.8 or 3.5Mc/s amateur bands.

The v.f.o. may be employed with other transmitters. The fundamental operating frequency is 1.75-2Mc/s but output may be taken at 3.5-3.8Mc/s if a different transmitter requires this.

Fig. 1 shows the circuit and the VR150 regulates the anode and screen supply for the 6AG7. L1, the oscillator coil, is tuned by VC1 from 1.75-2Mc/s. There is good isolation between L1 and the anode circuit and L2 is tuned to about 1.9Mc/s and needs no further adjustment. A coaxial lead takes r.f. to the transmitter.

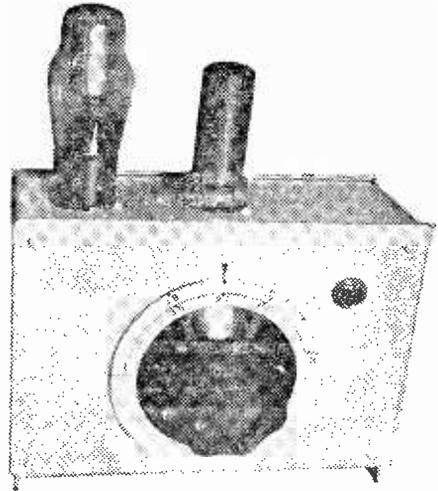Heater and h.t. currents are drawn from the companion transmitter. Heater drain is 0.65A, plus 0.3A for the indicator lamp. For h.t. about 25mA will be needed at 200-500V.



**BY F. G.  
RAYER  
G30GR**

## CONSTRUCTION

As the v.f.o. replaces the crystals, rigid construction is needed. An aluminium box about 7in. x 5in. x 3in. is used, completely enclosed, and with a 7in. x 3in. shelf bolted 2in. from the case top. The panel is screwed to this shelf and the box to increase rigidity. L1, TC1, C1 and VC1 are below the shelf with other components in the top compartment.

The valve and voltage regulator stand clear on top of the v.f.o. so that their heat does not cause unnecessary frequency drift in the circuit L1. All components are securely held, with short leads and tag strips where needed. With these precautions the general stability of the unit was found satisfactory.

Fig. 2 shows all internal wiring, including the underside of the box top, to clarify valveholder connections. Stout wire such as 18s.w.g. is used throughout. Two leads pass through the shelf. These go to B on L1 and to R1 and C2. These wires are in thick insulated sleeving which is a push fit in the holes.

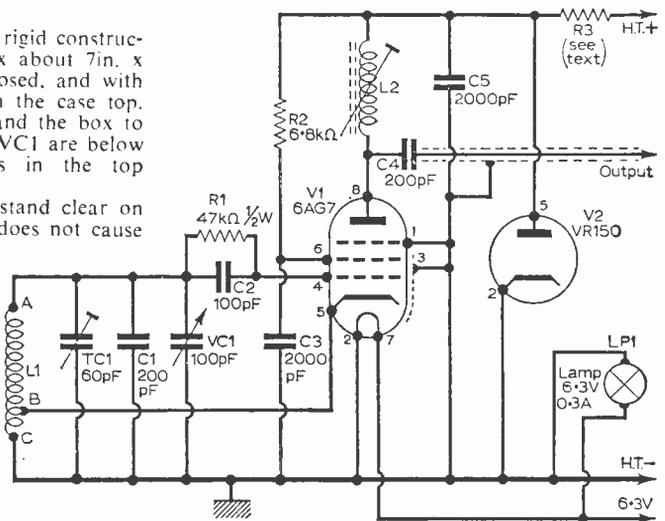


Fig. 1: The v.f.o. circuit. The operation of this simple circuit is described in the text.

It will be seen that L2 is at right-angles to L1. L2 is attached to a bracket on the shelf and is horizontal. All construction must be perfectly solid to avoid random changes in frequency.

**V.F.O. COIL**

L1 is wound on a strong paxolin tube 1in. in diameter and about 2½in. long. Drill two small

holes at A (Fig. 2). About 1in. away drill two further holes for end C.

A length of 26s.w.g. enamelled wire is anchored to some convenient point and threaded through the holes at A. The centre lin. of the tube is smeared thinly with an adhesive cement. The coil can then be wound by rotating the tube, walking slowly forwards and keeping the wire under


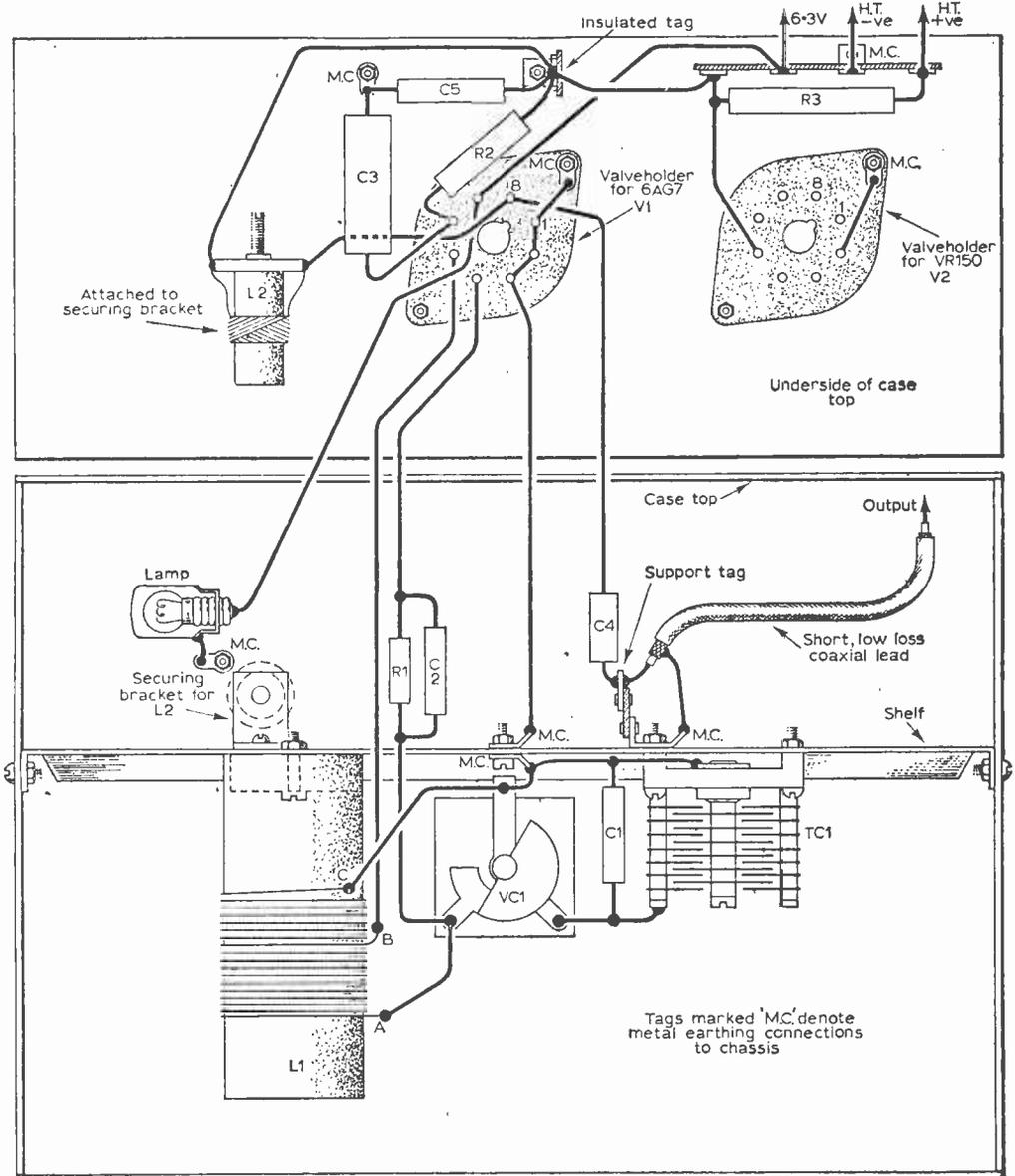


Fig. 2: The complete wiring diagram of the finished unit.

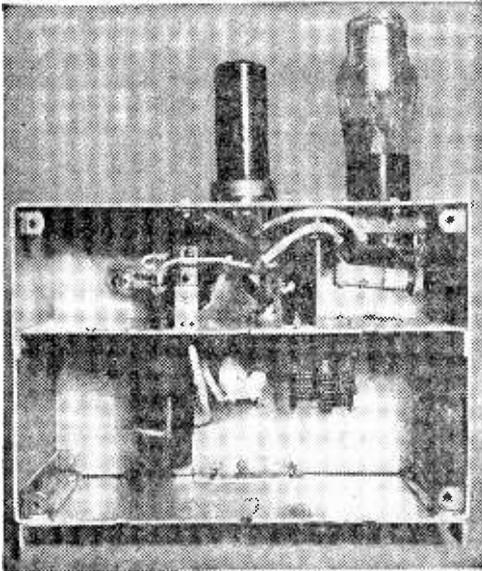



A rear view of the completed prototype v.f.o. unit.

the v.f.o. to roughly 1.8Mc/s and adjust the new coil core for maximum grid current with the switch closed. The switch must be open if crystals are inserted.

**GRID/ANODE SWITCH**

For the above adjustments a fairly accurate indication of small changes in grid current will be necessary. It may thus be felt worth while to change the transmitter meter circuit to show grid and anode currents at will.

A three-way, two-pole rotary switch can be mounted on the transmitter panel near the meter and wired as in Fig. 4. With the switch in the position shown, grid current is read. The 470Ω resistor is only to complete the grid circuit when reading anode currents. The most convenient meter is a 0-5mA model.

With the switch fully turned to its other position the meter reads anode current, the shunt changing the range to 0-100mA. It is necessary to use a three-way switch so that the contacts clear the grid circuit before completing the anode circuit. But if a *break-before-make* two-way switch is to hand this is perfectly suitable.

In use grid current is checked as necessary and the meter is then used to show anode current as previously described.

meter in series with the voltage regulator and adjust R3 until the regulator draws about 25mA.

**TRANSMITTER DOUBLER**

When operating on 160m the original crystal oscillator valve acts as an untuned buffer. No changes at all are needed except to plug the v.f.o. in instead of a crystal.

When working in the 80m band the first transmitter stage must operate as a doubler. This is done by fitting an on/off switch on the chassis and panel near the crystal socket and wiring it to a 3.65Mc/s coil as in Fig. 3. This coil can be 65 turns of 32s.w.g. enamelled wire, side by side, on a 1/2 in. diameter former provided with an adjustable dust core.

For 160m the switch is left open. For 80m set

**V.F.O. CALIBRATION**

VC1 has a large knob with dial, a reduction drive being optional. It is only necessary to calibrate for one band as 80m coverage is obtained by the second harmonic.

A crystal calibrator or marker is ideal for calibration. Open VC1, tune a receiver to 2Mc/s from the marker and adjust TC1 until the v.f.o. is at zero beat. Mark the dial 2Mc/s. The process can then be repeated at 1.95, 1.9, 1.85, 1.8 and 1.75Mc/s.

Divisions are filled in between the calibrated points. The 160m band is indicated from 1.8-2Mc/s on one scale. Each frequency is then multiplied by two and placed on a second scale for 80m. Only frequencies from 3.5-3.8Mc/s (1.75-1.9Mc/s fundamental) should be shown on the 80m range.

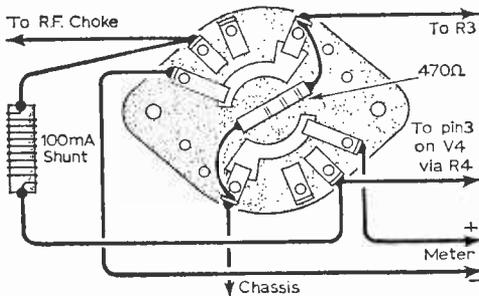


Fig. 4: Connections for a two-pole, three-way switch to be incorporated in the transmitter meter circuit to provide indications of grid and anode currents.

**V.F.O. WORKING**

The method of loading up and tuning the transmitter for crystal operation has already been described. V.F.O. working is similar except that any required frequency can be selected.

If a CQ call is to be made find a vacant channel with the receiver and tune the v.f.o. to this, using the net position of the switch. Then switch to transmit and tune the p.a. as described.

If a CQ is to be answered the v.f.o. is tuned to zero beat with the transmission heard, again using the net position. The p.a. is then quickly tuned with the function switch at transmit. The switch is then returned to receive until the calling station stands by for replies. The switch is then turned to transmit and a reply made.

THE

# Cadet

## 7 WATT HYBRID AMPLIFIER

THE amplifier to be described was built to fulfil the requirements of a medium power amplifier at the lowest possible cost. Although it could not be placed in the hi-fi class by any stretch of the imagination, it gives a good output for a wide range of inputs.

When originally designed, careful consideration was given to parts available from the junk box, and many constructors will probably find that they already have the majority of the parts. There are no critical values in the amplifier at all, and even starting from scratch, with careful buying from the columns of this magazine it should be possible to make the amplifier for about £2 10s. (excluding case).

The original amplifier had two low level inputs (actually for two guitar pick-ups) and a treble cut control but it can easily be modified to give up to ten low level inputs, with or without the treble cut control, and also a socket can be brought out to give a high level input (i.e. from a gramophone or carbon microphone). It can therefore be built for virtually any application which requires a maximum output of approximately 7W.

### CIRCUIT DESCRIPTION (FIG. 1)

The amplifier is a hybrid design: that is, it uses transistors for low level amplification, and valves for the driver and the output stage. Both valves and transistors derive their power from a mains power pack.

This arrangement was decided on because modern transistors are well suited to low level

amplification and are also cheaper than their valve counterparts: a wholly transistorised amplifier could have been designed, but transformers for transistorised amplifiers are still quite expensive items.

Direct coupling is possible, but can be difficult to set up properly without an oscilloscope. A hybrid amplifier offers the best compromise between cost and simplicity compatible with performance.

### TRANSISTOR PREAMPLIFIER

The transistor preamplifier uses two OC71 Mullard transistors (or equivalents) in a conventional R-C coupled circuit. The two inputs are wired so that the operation of one control does not effect the other control. R1 and R2 in series with the inputs ensures that the microphone or pick-up is not completely short circuited when the associated volume control is turned down to its minimum position.

The volume controls are coupled to the base of the first transistor by C1; R3 and R4 determine the base bias for the transistor. R5 and R6 are chosen to give a collector current of approximately 1mA in the first stage, and R9 and R10 give a


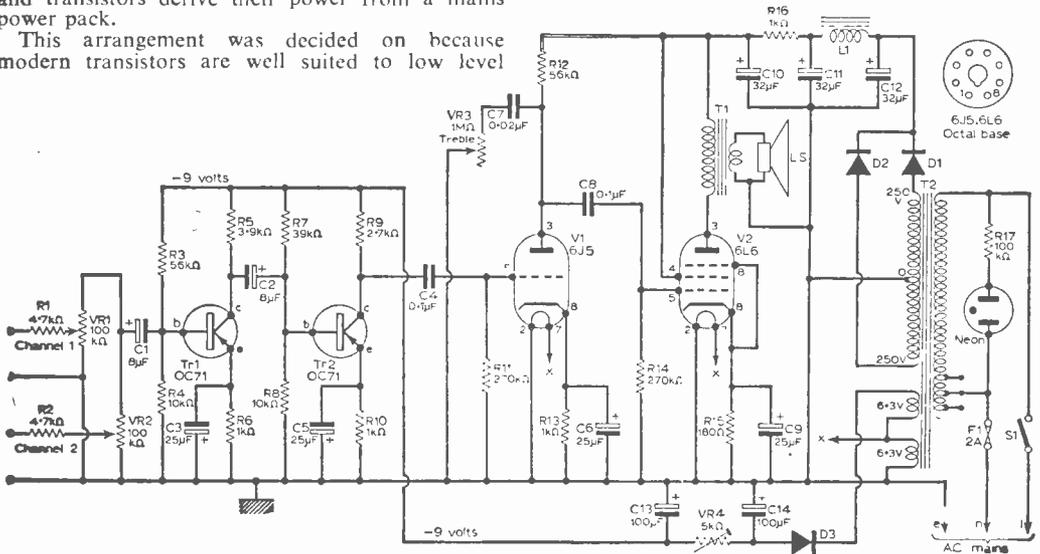


Fig. 1: The basic hybrid circuit of the "Cadet", complete with preamplifier stage and power supply.

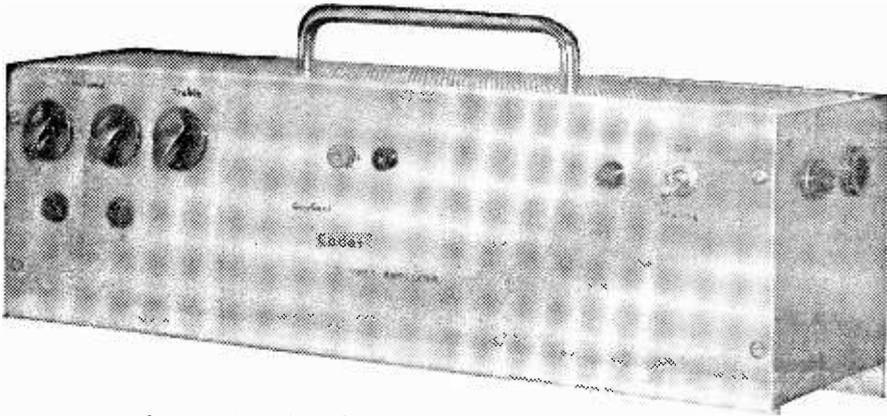

collector current of approximately 1.5mA in the second stage.

The preamplifier will work satisfactorily with a supply voltage between 4.5 and 15V, though a certain amount of gain will be lost at the lower voltages, and the circuit may be rather noisy at the higher supply voltages (depending on the transistors used).

A nominal supply voltage of 9V was chosen, obtained by using two 6.3V windings on the mains transformer, and the voltage is set for optimum performance when the amplifier is tested by means of a 5k $\Omega$  preset potentiometer (VR4) in the power supply.

#### MAIN AMPLIFIER

The output from the preamplifier is taken via C4 to the grid of a 6J5 triode. This feeds a 6L6 beam tetrode operating in class "A". A treble cut circuit is provided between the two valves. The h.t. for the valves is approximately 275V with the values specified.

As with the preamplifier, the main amplifier was tested with voltages between 180—400V, and again, the output was somewhat lower with the lower voltages and a bit noisier at 400V.

One side of the secondary of the output transformer should be earthed, not only from a safety point of view, but also to prevent parasitic oscillations which can occur when a long lead is used to the speaker.

#### THE POWER SUPPLY

The power supply uses a full wave transformer and modern silicon rectifiers which are available at a reasonable price through the columns of this magazine. These are very efficient and have a very low voltage drop across them: but because they have such a low impedance they can be destroyed by switching-on surges.

Some suppliers suggest that a resistance of approximately 50 $\Omega$  is connected in series with the rectifier. However, most, if not all, of the resistance is supplied by the windings of the transformer, so the series resistors have not been included in this design, but 2W 47 $\Omega$  resistors may be wired between the rectifier and the transformer for safety if required. Alternatively, metal rectifiers may be used if they are to hand or more easily obtainable.

The negative 9V supply is obtained by wiring two of the low voltage secondaries of the transformer together, and using a simple half-wave rectifier circuit with a smoothing consisting of 5k $\Omega$  preset potentiometer and two 100 $\mu$ F 25V electrolytics. Most transformers have at least two 6.3V windings,

#### COMPONENTS LIST

##### Resistors:

R1	4.7k $\Omega$	R10	1k $\Omega$
R2	4.7k $\Omega$	R11	270k $\Omega$
R3	56k $\Omega$	R12	56k $\Omega$
R4	10k $\Omega$	R13	1k $\Omega$
R5	3.9k $\Omega$	R14	270k $\Omega$
R6	1k $\Omega$	R15	180 $\Omega$ 1W
R7	39k $\Omega$	R16	1k $\Omega$ 5W
R8	10k $\Omega$	R17	100k $\Omega$ (for neon)
R9	2.7k $\Omega$		

All 10%  $\frac{1}{2}$ W carbon unless otherwise stated

##### Potentiometers:

VR1	100k $\Omega$	VR3	1M $\Omega$
VR2	100k $\Omega$	VR4	5k $\Omega$

##### Capacitors:

C1	8 $\mu$ F electrolytic 25V
C2	8 $\mu$ F electrolytic 25V
C3	25 $\mu$ F electrolytic 25V
C4	0.1 $\mu$ F paper 350V
C5	25 $\mu$ F electrolytic 25V
C6	25 $\mu$ F electrolytic 25V

C7	0.02 $\mu$ F paper 350V
C8	0.1 $\mu$ F paper 350V
C9	25 $\mu$ F electrolytic 25V
C10	32 $\mu$ F electrolytic 450V
C11	32 $\mu$ F electrolytic 450V
C12	32 $\mu$ F electrolytic 450V
C13	100 $\mu$ F electrolytic 25V
C14	100 $\mu$ F electrolytic 25V

##### Valves and Semiconductors:

V1	6J5	V2	6L6
Tr1, Tr2	OC71 or equivalent		
D1, D2	400 p.i.v. 100mA silicon rectifiers (see text)		
D3	30V 5mA surplus diode (see text)		

##### Miscellaneous:

T1	Output transformer: ratio 3.5k $\Omega$ : 3 $\Omega$ 8W
T2	Mains transformer. Secondaries: 250-0-250V, 80mA; 6.3V, 3A; 6.3V, 1A (see text)
L1	10H, 100mA choke (see text)
F1	2A fuse
	70'90V neon, tag strips, aluminium, etc.

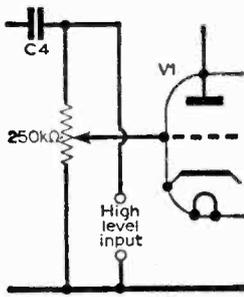


Fig. 2: The modification to the V1 circuitry to provide a high level input. This allows for the use of record player, carbon microphone and similar inputs with the amplifier.

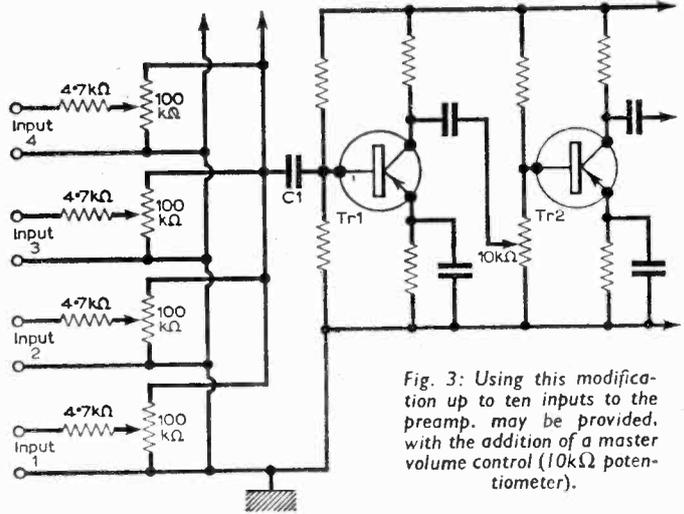


Fig. 3: Using this modification up to ten inputs to the preamp. may be provided, with the addition of a master volume control (10kΩ potentiometer).

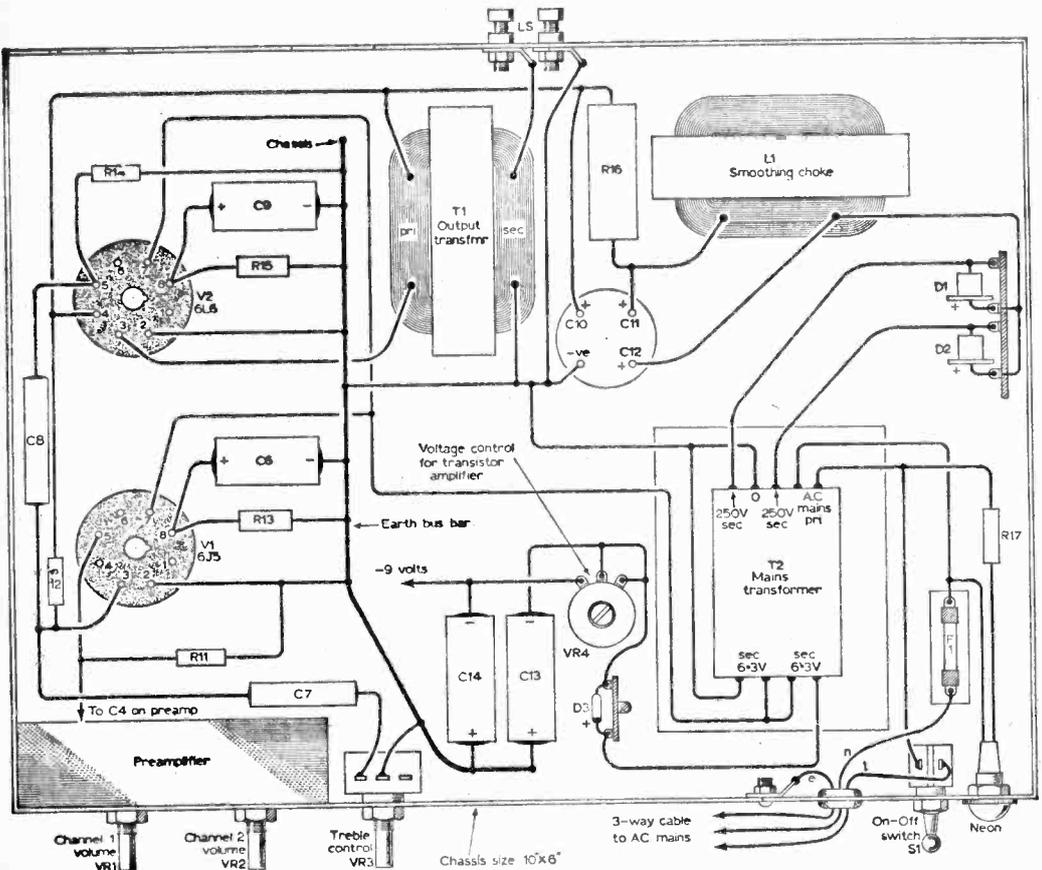


Fig. 4: Complete wiring details of the main amplifier and power pack chassis.

or one 6.3V winding and a 5V winding for the rectifier.

The 6.3V winding (with the larger current capacity if there is more than one winding) has one side connected to the chassis: this also supplies the heaters of the valves. The other winding is connected in series with the first winding.

It must be connected the right way round otherwise the two windings will be 18° out of phase and the total output voltage will be zero. To check the sense of the connections, connect the transformer to the mains, and connect the two low voltage windings together and measure the output voltage.

A 12V bulb can be used for this purpose if no a.c. meter is available. The bulb will glow brightly with the windings connected one way round, and the windings should be connected in this sense when building the amplifier.

Virtually any diode can be used for the 9V supply since it is only required to supply about 2.5mA. One of the diodes obtainable at about 1s. 6d. will be adequate. Note that the black end goes to the smoothing circuit and the red end goes to the transformer.

The 250V supply is smoothed by a choke-resistor-capacitor arrangement: this was found to be more than adequate. If required, the choke could be replaced by a 1,000Ω 10W resistor with consequent economy but slight degradation of performance.

**MODIFICATIONS**

As has been previously stated, a number of modifications can be introduced in to the amplifier to increase its usefulness while it is being built. The treble cut control may be omitted by removing C7 and VR3.

A high level input socket may be added simply by bringing out the grid of V1 via a length of screened cable to a suitable socket. It is not very simple to provide a volume control at this point however, because the output impedance of the transistor amplifier will effect the use of such a control.

However, the circuit of Fig. 2 would work since the volume control has been "turned round". R1 is made a variable component, and the slide is taken to the grid of V1.

The real limit to the number of channels is the layout, since the more channels there are, the greater the problems of hum pick-up and control interaction become. There is no reason why 10 channels should not be possible so long as efficient screening and the shortest possible lead between the input socket and the potentiometer are used. A master volume control may be built in between the two transistors by making R8 a variable component.

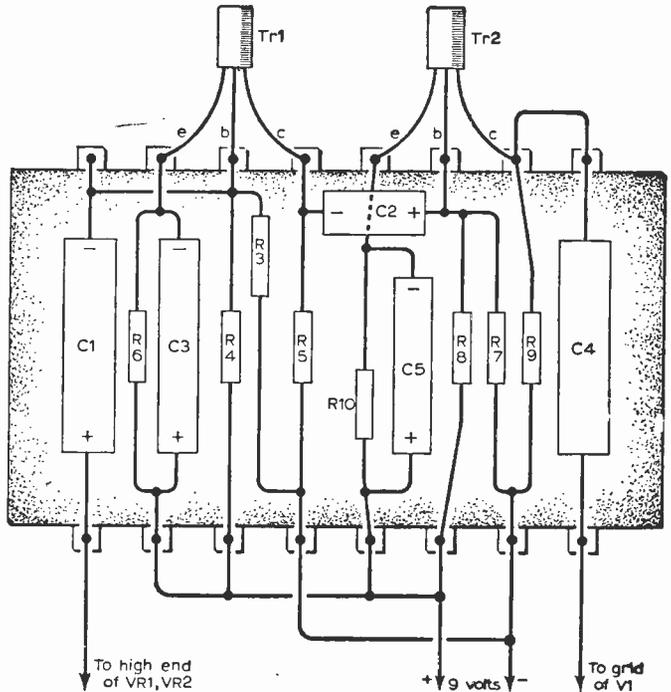


Fig. 5: Construction details of the preamplifier chassis which is built separately and fitted to the underside of the main chassis when complete.

**CONSTRUCTION**

The author's original amplifier was constructed to fit in a case 17in. x 5in. x 5in. This gave plenty of room (except that a 6L6M had to be used instead of 6L6G, since the 6L6G was taller than 5in.!). The layout is by no means critical providing the usual rules are followed such as wiring the heaters first of all and keeping the leads carrying a signal as short as possible.

The output transformer, smoothing choke and mains transformer should have their cores in opposite planes to avoid interaction. No wiring carrying 50c/s (such as mains or heater supplies) should pass anywhere near the preamplifier.

It is suggested that the main amplifier and the power pack are constructed on the same chassis and the preamplifier is constructed on a tag board and fixed under the main amplifier chassis. It is a good idea to use transistor sockets so that different transistors can be tried to select one for good noise characteristics.

The cabinet is left to the constructor's ingenuity (don't forget that the 6L6 gets fairly hot in operation). If required the cabinet can be dispensed with and the amplifier left as a plain chassis with the controls on the front. A neon bulb was used as a pilot light; a low voltage bulb wired across the heater winding would be equally sufficient. A mains fuse of 1A should be included in the live mains lead.

## TESTING

When the amplifier has been completed and the wiring checked the amplifier should be connected to the mains supply. The chassis should always be earthed when the amplifier is in use, not only because this is safer but it also cuts down hum and noise.

The preamplifier should be left disconnected at this stage. When the main amplifier has warmed up and a loudspeaker has been connected a pronounced hum should be heard when the grids of the valves are touched with a screwdriver.

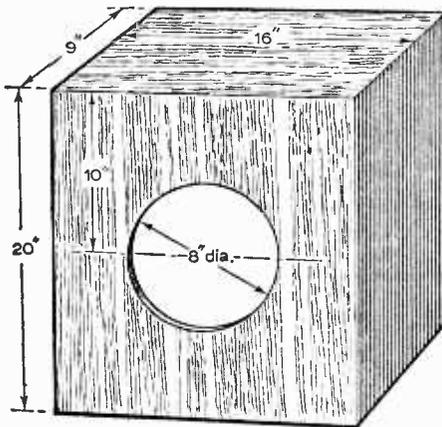


Fig. 61 Basic details of a suggested cabinet for the loudspeaker.

Assuming that the main amplifier works, check that the transistor supply is giving a negative output and turn the preset potentiometer down to its minimum voltage setting. This voltage may be quite high, since there is no load connected across it.

Switch off the mains and connect the preamplifier. Turn on the mains and adjust the preset potentiometer to give approximately 9V. (If no meter is available set it for minimum noise.) An input, such as a low impedance microphone, can now be connected and the whole amplifier tested.

## LOUDSPEAKER AND ENCLOSURE

An 8in. 10W loudspeaker was used with the original amplifier. This was mounted in a shallow box with the dimensions shown in Fig. 6. A single piece of wood (say) 20in. x 16in. would have been just as efficient acoustically but it is well worth the trouble involved in making the baffle board into a shallow box, since it not only makes it more convenient to stand up but it also protects the speaker from accidental damage to the back of the cone.

Finish of the case depends on how much money and time the constructor is prepared to allow. The box itself should be solidly made  $\frac{3}{4}$ in. ply or chip-board to avoid resonances at the lower frequencies to be handled. If the box does resonate it may be necessary to include one or more braces to increase the rigidity.

The dimensions given should serve as a guide: actual measurements can be decided by the individual. If required the main amplifier and power pack chassis could be mounted at the bottom of the box and the preamplifier and controls could be mounted at the top. ■

## KEYED AUDIO OSCILLATOR


—continued from page 1043

arrangement, causing the audio oscillation to rise and fall at the beginning and end of each pulse respectively, smoothly over about one cycle. The capacitor C5 should have ten times the capacity of the capacitors C1 to C4 determining the audio frequency to realise this condition correctly. Since the audio output has an amplitude of some 4V r.m.s. with VR3 turned full up, only simple audio amplifiers are required for even the most powerful transmitters met with in amateur transmitters. The output can alternatively be plugged in in place of the mike of an existing telephony transmitter, giving immediate conversion to m.c.w. operation without any other alterations of any kind.

A few words about the advantages of m.c.w., for which the carrier runs uninterrupted as in telephony, the Morse characters being impressed as corresponding bursts of a.f. modulation as if these were music or speech signals. Apart from the fact that no b.f.o. is required in the receiver and some loss of signal-to-noise ratio the greatest outstanding advantage is the available multiplicity. Several Morse operators at the one transmitter can

each key their own Veroboard circuit with their own particular audio frequency output. All outputs are used to modulate the one transmitter simultaneously. At the receiver each receiving operator interposes a tuned circuit resonant to the audio frequency of his intended signal in front of his phones. Alternatively the entire signal can be tape recorded and a single receiving operator can read each message successively on successive playbacks with his audio resonant circuit tuned to the m.c.w. channels one after the other. Ordinary carrier-keyed c.w. cannot transmit more than one message per r.f. channel. When it is remembered that with the m.c.w. technique single sideband (s.s.b.) modulation techniques can be combined therewith, the upper and lower sidebands containing completely different sets of multiplex m.c.w. signals, it is clear that the total information which can be modulated on to a single r.f. carrier frequency without exceeding the conventional bandwidth is quite enormous. It is little wonder that these types of communications systems are very popular with the GPO nowadays! They provide some measure of solution to the increasing congestion of the communications wavebands.

CONTINUED NEXT MONTH

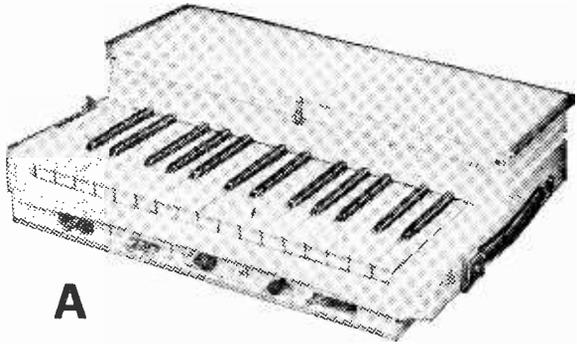

# BUILDING A TRANSISTOR SOLO ORGAN

by  
G. W. Hardy

CONTINUED FROM PAGE 945 OF THE FEBRUARY ISSUE

**T**HE layout of the three panels—the wiring of which was detailed last month—the controls, batteries and sockets viewed from underneath the cabinet, is shown in Fig. 8.

### Keyboard Switches

For ease of manipulation from the keyboard it was decided to adapt the three-way switches so that they are moved by levers instead of knobs.

The levers were made from  $\frac{1}{4}$ in. wide strips of brass about  $\frac{3}{16}$ in. thick and 2in. long. For half the length, width is reduced to  $\frac{1}{4}$ in. At the end of the wide portion a  $\frac{1}{4}$ in. clearance hole is drilled and the surface adjacent to this hole tinned.

We now need bosses (with grub screws) to which the levers can be soldered. A brass  $\frac{1}{4}$ in. spindle coupler sawn in half will provide us with two. The circular ends are tinned and placed on the tinned portion of the levers, with holes correctly aligned, and heat with pressure applied with a large soldering iron, when they should unite.

The case under the keys is recessed back  $\frac{3}{4}$ in. The switches are fixed so that the ends of the levers project out  $1\frac{1}{2}$ in. from centre of spindles and come level with front of keyboard.

Coloured plastic adhesive tape is now bound around the ends of levers to form a neat handle.

### The Keyboard and Case

Assuming the constructor has an accordion keyboard, and the rest of the instrument has been dismantled, we should now have the keyboard with its keys sticking up in the front and at the end of each a spike with leather covered pallets attached.

Care must be taken now as we cannot level the keys until a baseboard has been fitted. This should be of plywood the width of the keyboard plus 1in. and 12in. from back to front and about  $\frac{1}{4}$ in. thick.

Any plastic covering should be removed and the keyboard now placed so as to be level with the front of the baseboard,  $\frac{1}{4}$ in. spacing either side, and fixed to it with countersunk screws.

As the front of the keys are sticking up it can be seen that under them is a shallow compartment containing key guides and springs. It is the bottom of this compartment which is fixed to the baseboard and any screws coming through from baseboard will need to be carefully positioned or kept short. The strongest fixing will be into the key blocks at each end.

Having fixed the keyboard we can attend to the keys. The pallets should be removed and the malleable spike on each key carefully pressed back and downwards to form an extension of the key whilst the front of key is held down firmly.

The spikes should now rest on a felt-covered piece of wood the length of the 29 keys. Height of wood is by experiment (see Fig. 9). The keys can now be levelled and adjusted to give a  $\frac{1}{4}$ in. deep touch at the front.

The idea now is to build up a compartment at the back of the keys and another under the baseboard. The bottom compartment need only be  $1\frac{1}{4}$ in. deep and will accommodate all the panels, batteries and switches (Figs. 8 and 9).

Planed wood  $1\frac{1}{2}$ in. x  $\frac{1}{4}$ in. is cut to length and mitred or butt-jointed in the form of a frame and fixed with countersunk screws level with back and sides of baseboard. The front part of the frame should be fixed  $\frac{3}{4}$ in. from the front of baseboard. A piece of hardboard cut to the size of the frame and fixed with countersunk screws will form a cover.

The top compartment is built up in a similar manner with  $\frac{1}{4}$ in. wood. Depth must be obtained by measuring from top of highest spike and, with the key down, adding  $1\frac{1}{4}$ in. for hopper and another

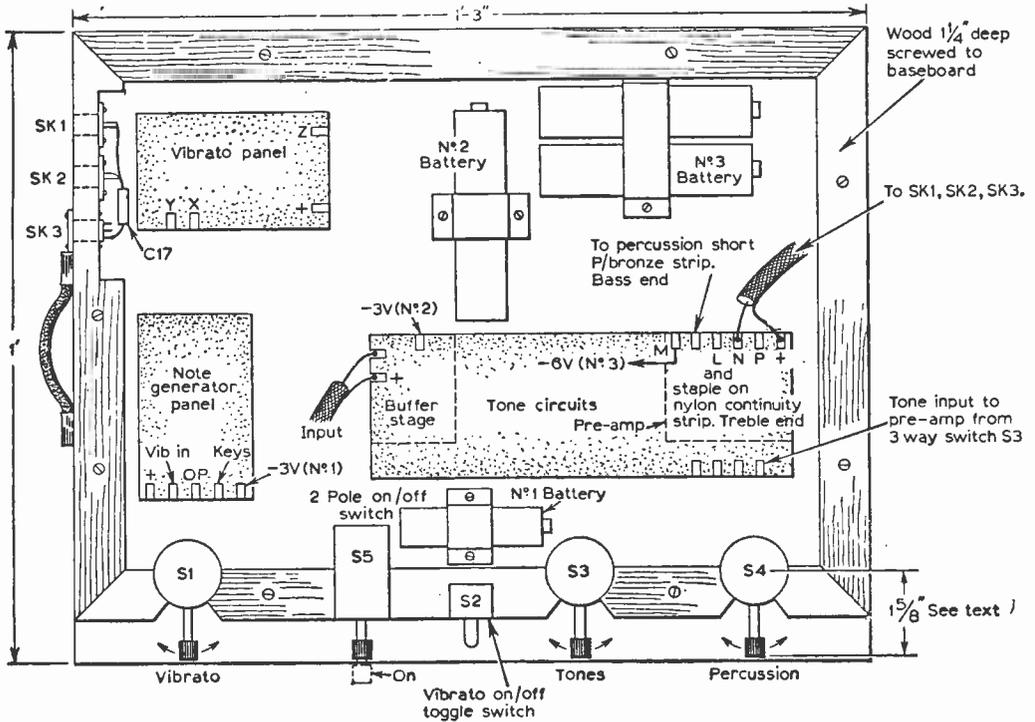


Fig. 8: The layout of the bottom compartment which accommodates the three panels, batteries and controls.

4in. for clearance; this height to the baseboard is the width of wood required.

The planed wood is now fixed on the baseboard level with the back and two sides. The sides, which finish level with the front of the keyboard, are shaped and levelled down to the original key blocks, to which a fixing can be made.

Fig. 10 shows the author's method of fixing the panels to the interior casework. The screws remain captive and wiring always held clear.

**Using Piano Keys**

These can often be obtained from a piano dealer as old instruments taken in part exchange are always being broken up. They are slightly larger than accordion keys and for the same


compass of 29 keys would need another 2 1/2 in. or one could make do with 25 notes (two octaves).

They would need to be shortened from the back and each one fitted with a coil tension spring. The upward thrust of the keys would be taken by a felt-covered wooden bar situated over the keys just at the back of the black notes. From then on they could be adapted as later described for accordion keys.

**Making Action for Key Contacts**

The action to be described uses spring brass sliding contacts which are self-cleaning and found

Fig. 9: This drawing illustrates how keys, hoppers, distribution strips, etc., are arranged within the cabinet.

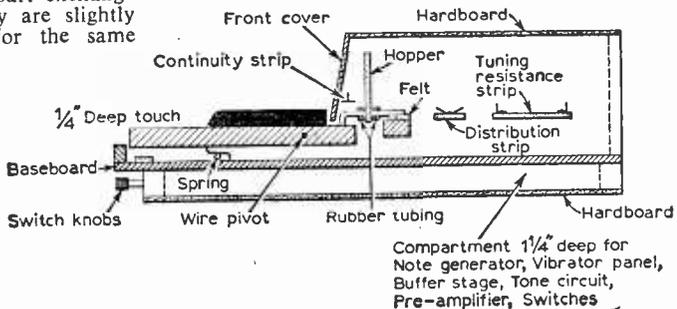

# L.K. ELECTRONICS

## The Cheapest - The Best - The Quickest Service

● **Famous Autochanger or Single Player Units** supplied with brand new, two-tone, de-luxe portable cabinets, 17 x 15 x 8½ in. Strong carrying handle, gilt finish clips and hinges are used by famous make for 22 gn. model. Ready cut out motor board, 14 x 13in. Front baffle 7 x 4in. High flux loudspeaker and 3 watt amplifier. Amplifier ready built on metal chassis with output transformer, volume and tone controls. All items fit together perfectly. Assembly in 30 minutes. Only 5 wires to join. 12 months' written guarantee. Available separately or package deals as below.

Our NEW MK II Superb Kits are now being dispatched.

### L.K. PRICES FOR COMPLETE KITS:

**Autochanger Kits as above**  
 B.S.R. U.A. 14, T.C. 8 Mono ..... £10.17.6 P.P. 5/6  
 Garrard Autoslim, Mono ..... £11.7.6 P.P. 5/6

**Single Player Kits as above**  
 Garrard S.R.P. 10, Mono ..... £10.12.6 P.P. 5/6  
 E.M.I. Autostop, Mono ..... £10.17.6 P.P. 5/6

Individual Prices for those who wish to purchase separately.  
 Record Player Cabinet with Cut-out Board... £3.10.0 P.P. 3/6  
 Amplifier with 7 x 4in. speaker ..... £3.10.0 P.P. 2/6

● **SCOOP! B.S.R. U.A. 25 Autochangers.** T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note OUR price £5.15.0. P.P. 5/-. The very very, latest model.

● **SCOOP! B.S.R. U.A. 14 Autochangers.** T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note OUR price £5.15.0. P.P. 5/-. Latest model.

● **SCOOP! Garrard Autoslim.** Mono P.U. Brand new and boxed. Wired for stereo. Latest model. Note OUR price £6.5.0 only. P.P. 5/-.  
 ● **SCOOP! Garrard A.T.5.** Wired for stereo, inclusive of head and mono cartridge (A.T.5 is an auto transcriber). The finest changer of them all. OUR price, brand new and boxed £7.10.0 only. P.P. 5/-.  
**AUTOCHANGERS**  
 Single Players  
 E.M.I. Autostop, Mono ..... £5.10.0 P.P. 4/6  
 Garrard S.R.P. 10, Mono ..... £5.10.0 P.P. 4/6  
 E.M.I. Separate Pick-up ..... £3.5.0 P.P. 3/6

**Transcription Units** Stereo Head Mono  
 Garrard 4 H.F. Stereo ..... £15.0.0 P.P. 5/-.  
 Philips A.G. 10/16 Stereo ..... £12.10.0 P.P. 5/-.  
 Garrard A.T.6, Stereo ..... £10.10.0 P.P. 5/-.  
 Garrard 301 ..... £16.10.0 P.P. 5/-.  
 ● **SCOOP! Record Player Cabinets.** Two-tone, de-luxe finish with cut-out board. These are brand new and product of very famous national manufacturer. OUR price £3.5.0 only. P.P. 4/6.  
 ● **SCOOP! 3-watt Gramophone Amplifier.** Complete with 5in. Speaker, 49/6. P.P. 5/-.  
 The amplifier is complete, on a fabric-covered baffle board. Output transformer included. Tone and volume controls and on/off switch. Ready to switch on and play. Terrific volume. Size 12½ x 6 x 3½in. back to front. For 200-250v. A.C. Output 3 watts.  
 ● **SCOOP! Diodes**—over 1,000,000 in stock—ideal substitute O.A.81 vision detector.  
 Note OUR price £1.0.0 per 500. P.P. 2/- (in 500 lots only).  
 ● **SCOOP! Transistor Tape Recorder.** The best obtainable by very famous manufacturer. Brand new, boxed, guaranteed. Reduced from 12 gns. OUR price £7.10.0. P.P. 3/6. Complete with microphone, tape, batteries and operational booklet. Features push-pull amplifier, two motors, single switch operation, pause speed, wind, rewind, record, play back. Can be used in any position, indoor or outdoor.  
 ● **SCOOP! For £27.10.0 only.** A fabulous offer, Garrard A.T.5 Transcriber, plus 2 12in. 15 watt Hi-Fidelity speakers, plus the very latest Continental push-button chassis by Brittamer. Stereo 3-wave band, 6 valves 5 watts per channel. The finest chassis of its type in the world. You will be amazed at performance and quality. We unhesitatingly recommend this chassis. P. & P. 2/1-.  
 ● **SCOOP! A Limited Number Only.** Tape Decks by B.S.R. Latest model. A.C./200/240v. Brand new and boxed. OUR price £7.4.0 only. P.P. 4/6.


● **SCOOP! Hi-Fidelity Speakers.** 15-watt. Very famous national manufacturer—we cannot mention name. 45-13,000 c.p.s., 3 or 15 ohm voice coils, response 45-13,000 c.p.s. Magnet 15,000 lines. In carton—unopened and unused. OUR price £4.4.0 only. P & P. 4/6.

● **SCOOP! A Stereophonic Amplifier** with the following features. A twin ganged tone control in a special negative feedback circuit, giving a wide range of tone correction. A balance control enabling the amplifiers to be equalized in output to compensate for pick-up, lead, speakers, recording differences. A speaker switch, M1, single amplifier. M2 dual amplifiers for increased Monaural output. 53, two speakers at 5 watts per channel. Twin ganged volume controls and all four controls placed equidistant along the front of the chassis. Designed, made and guaranteed by Brittamer Ltd. Brand new and at a fraction of original cost. OUR price £7.10.0 only. P & P. 4/6.

● **SCOOP! Cartridges**—Ceramic Diamond Styli—Stereo—by Acos. Limited number only at one quarter of original price—15/- only. P.P. 1/-. While stocks last.

● **SCOOP! 1964 Radiogram Chassis.** Stereo 3-wave bands, long, medium, short. 5 watts per channel. 6 valves Latest Mullard A.C. 200-250v. Ferrite aerial. Glass dial. Horizontal winding. Size 13 x 4in. Aligned and calibrated. Concentric controls. Isolated chassis. Size 13½ x 9in. high x 5in. deep. Product of famous national manufacturer. Brand new and boxed. Maker's guarantee. OUR price £14.0.0. List price £19.8.0. P.P. 5/6. Our Chassis List quotes prices—the keenest in the Trade. We are Main Agents for the complete range of Brittamer Chassis and Amplifiers. "Brittamer"—makers of Radiogram Chassis to the Top Names in Radio.

### THE SIOUX 60 WATT GUITAR AMPLIFIER

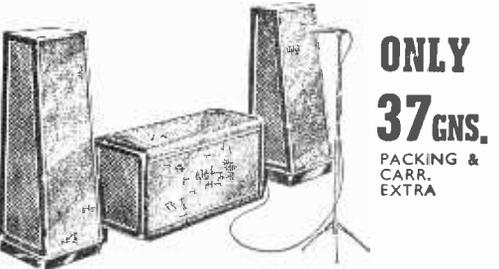

**ONLY 37 GNS.**  
 PACKING & CARR. EXTRA

Incorporating Ten High Duty Speakers in two columns of five designed to handle efficiently the full output of Amplifier at frequencies down to 25 c.p.s. Heavily made Cabinet in two-tone Vynair. For 200-250 v. to 50 c.p.s. A.C. Mains operation. Four jack socket inputs and two independent volume controls for simultaneous connection of up to four instrument pick-ups or microphones. Level frequency response throughout the Audible Range. OUR INCLUSIVE PRICE FOR AMPLIFIER, MIKE, STAND, SPEAKERS, LEADS, ETC. ONLY 37 Gns. (REGRET NO H.P.).

Speakers ex Equipment. 5in. 5/-. 7in. x 4in. 6/-. 6in. 6/6. 8in. 7/- P.P. 1/6 each.

### TRANSISTOR SECTION

● **SCOOP! A first-class 2 wave-band 3 transistor superhet chassis** by world famous manufacturer. Fully built, aligned, tested, guaranteed. Full coverage long and medium waves. Note OUR price only £6.0.0. P. & P. 2/6. Suitable speaker 10/6. P. & P. 1/6. A few cabinets can be supplied at 22/6 each, P. & P. 2/-. OUR price for the package deal £7.4.0 only, plus 3/6 P. & P. Ideal for Caroline.

S.A.E. enquiries please. Our Complete Lists 1/- only—credited against your order.

● IF NOT ADVERTISED IT IS STILL IN STOCK

# L.K. ELECTRONICS (Victoria) LTD.

★ 17 GILLINGHAM ROW, WILTON ROAD, LONDON, S.W.1. ★

# UNUSUAL SINGLE SPEAKER SYSTEM

## A CONCRETE COLUMN

An inexpensive column speaker constructed from a concrete pipe and fitted with a good 8in. or 10in. unit has attracted much interest and admiration because of its clean open sound. Complete kits of wooden fixtures are available including absorbent wadding and diffusing cone.



Price £3.15.0 for 8" model. Recommended 8" unit—Super 8/RS/DD £6.14.2 including purchase tax.

Price £4.18.0 for 10" model. Recommended 10" units—Super 10/RS/DD £10.18.8; Golden 10/RS/DD £7.17.5; 10" Bronze/RS/DD £4.12.9. Prices include purchase tax.

Suitable concrete pipes can be purchased from builders' merchants at about 12/6 and 17/6.

Descriptive leaflet free on request from.




WHARFEDALE WIRELESS WORKS LTD.  
IDLE BRADFORD YORKSHIRE  
Grams: Wharfedel Bradford  
Phone: Idle 1235/6

# HOUSING HI-FI?

The **Lowflex** is the world's most flexible hi-fi unit. Its three compartments are fully adjustable to take a complete hi-fi set up including tape recorder and records. For full details of this and other cabinets in the Record Housing range write for free catalogue and name of local stockists. (U.K. only).

Walnut or  
Mahogany  
29 gns.

Teak  
30 gns.

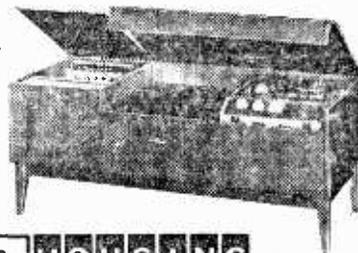

## RECORD HOUSING

(Dept. PW.3), Brook Road, London, N.22

Telephone: BOWes Park 7487/8

## LEARN ELECTRONICS AS YOU BUILD 25 CIRCUITS EXPERIMENTS TEST GEAR

including:

- MINIATURE CATHODE RAY OSCILLOSCOPE
- VALVE EXPERIMENTS
- BASIC AMPLIFIER
- BASIC RECTIFIER
- PHOTO ELECTRIC CIRCUIT
- TIME DELAY CIRCUIT
- SQUARE WAVE GENERATOR
- SIMPLE TRANSMITTER
- TRANSISTOR EXPERIMENTS
- BASIC OSCILLATOR
- ELECTRONIC SWITCH
- SIGNAL TRACER
- BASIC COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- MORSE CODE OSCILLATOR
- ETC., ETC.

This complete practical course will teach you all the basic facts of electronics by making experiments and building apparatus. You learn how to recognise and handle all types of components—their symbols and how to read a circuit diagram. You see how circuits are built and how they work BY USING THE OSCILLOSCOPE PROVIDED. Applications of all the main electronic circuits are demonstrated—radio reception and transmission; photo-electrics; computer basics; timers; control circuits, etc. including servicing techniques. NO MATHS USED OR NEEDED. NO THEORY NEEDED. NO PREVIOUS KNOWLEDGE OR EXPERIENCE NEEDED. Tutor service available. No extras needed—tools provided. Send now, for FREE DETAILS without obligation, to address below.

TO: LERNAKIT, Dept. K 10, RADIO HOUSE, 40 RUSSELL STREET, READING


Please send free details—

POST  
NOW

NAME .....

ADDRESS .....

Fig. 10: The method of fixing the panels to the case-work.

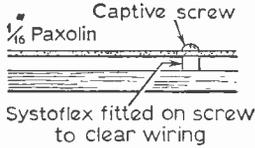

reliable in use. Twenty-nine vertical strips of 1/16 in. paxolin 1/4 in. wide and 1 1/2 in. long will now be required as drawn in Fig. 11.

These will now be referred to as hoppers and each one is drilled with a hole just large enough to go on the key spike. The holes should only have very slight clearance in the direction required in keeping the hoppers upright throughout the movement of the key.

A 1/4 in. length of cycle valve rubber tubing is pushed on to each spike, followed by the hoppers and another piece of rubber tubing. The hoppers can now be lined up level by adjustment of the tubing, which also prevents undue movement of the hoppers. These can now be roughly checked by moving each key while holding the hopper vertically between the fingers.

Paxolin (1/16 in. thick) is used throughout and if two pieces are laid side by side on a flat surface it is possible to feel if one is slightly thicker than the other. A small piece of the thicker should be put aside for guide pieces and will save having to stick on gummed paper to allow hoppers to work freely.

Two strips of paxolin are now required, one 1/8 in. wide and one 1/16 in. wide; length is a clearance fit between the two cheeks of the top compartment and in line with the hoppers.

Place the two strips together with edges level on a flat surface, clamp together with both ends level. Measure 1/4 in. from each end on the narrow strip and mark for drilling a 4BA. hole centrally.

Drill the two holes, turn the assembly so that the level edges are top and overlapping edge bottom back, unclamp and mark each one on the front for identification and right way up.

The action supports should now be made from 1/8 in. aluminium angle (see Fig. 11). Drill with two

holes each so that they can be fixed, one on each key block, after being lined up exactly with the hoppers.

From now on it will be easier to work with the organ case on its back and the hoppers straightened out. The widest long strip is placed under the tops of the hoppers and brought up to the underside of action supports. The other, narrower, long strip is now placed on top of the hoppers and action supports.

Spring paper grips or clothes pegs will be found useful here to temporarily hold things together. The exact spot can now be marked for drilling a hole in each support. One 4BA. bolt and nut each end will be sufficient.

Correct height is ascertained by seeing that none of the hoppers project beyond the top of the two long strips when keys are held down. Drill the 4BA. holes in each support, bolt together and check that everything is in line. Proceeding, with organ still on its back, the guides can now be made—from the thicker paxolin if any.


From now on each note is treated individually. Guides may vary from 1/8 in. to 1/4 in.; the main concern now is that each hopper will be truly vertical when playing.

Each part, including the hoppers, must be numbered on the front. Start by making the first guide against the metal support, filing down where necessary so that adjoining hopper would be truly vertical. Each one is now cut down to 1/4 in., numbered on front and reinserted, and process repeated throughout.

It will facilitate later assembly if the bottom corners of each guide are slightly rounded, also tops of hoppers.

A supporting piece of wood along the wide strip and wedged up from back of case would now help. Check that each guide is in place and level with top edges, mark for drilling on strip dead centre between hoppers and 1/4 in. down from top of strip. Mark bottom of each guide 1/8 in. up.

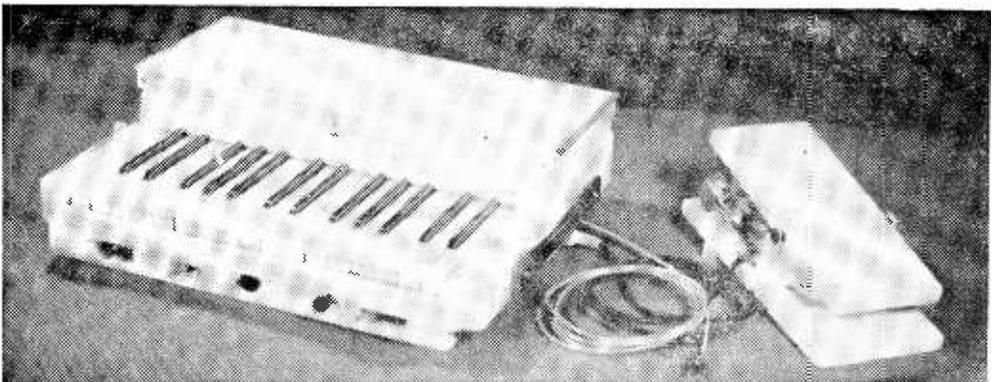While the guides are in place mark off where the short contact strips are to be fixed on the front paxolin strip as in Fig. 11. Take out guides,



The finished instrument complete with the expression pedal.

numbering if not already done, place aside in order. Unbolt and remove long strips and bolt them together.

**Drilling Guides and Strips**

All holes are  $\frac{1}{8}$  in. diameter. Care must be taken with this small drill and all work should be clamped or weighted down to ease withdrawal.

An archimedean drill is best but if a hand machine drill is used it may be necessary to pad out the stem of drill so it can be gripped in the chuck.

A sharp-pointed awl pushed down hard on the work will assist in starting the drill at the correct point. Drill holes through the two long strips while bolted together and clamped down. Drill one hole at bottom of each guide (Fig. 11).

With organ again on its back reassemble as before and with each guide correctly in place mark each through the holes in top strip. Drill these holes and lay guides aside. Remove strips from supports.

Thoroughly clean and cut one strip of phosphor-bronze, as used in draught excluders, 13in. long and  $\frac{1}{16}$  in. wide for rear contact strip. For front strip 15 pieces  $\frac{1}{16}$  in. wide are needed. They are measured off as in Fig. 9, allowing for bending each end at right-angles to fit into saw cuts. Remove and trim ends to just under  $\frac{1}{8}$  in. so as not to project inside. Put aside in order.

Drill holes to take  $\frac{1}{8}$  in. x No. 1 brass countersunk screws where the centre of each short strip will come. Countersink so that the screw head is level with paxolin, cut off threaded end, make a slight countersink at the back, put screws in from

front, place and hold firmly on a piece of flat iron, tap end of screw until it is tight, finally see none project at back. Lightly tin each screw head.

Fit contact strips into saw cuts, hold down near centre with a screwdriver and correct if not laying flat. Still holding down firmly, apply a hot iron just over the screw head and hold down with screwdriver for a moment to cool.

The 13in. long bronze strip can now be fitted to the rear paxolin strip. Scratch a line  $\frac{1}{8}$  in. from the top—this will give position of the bronze strip working edge (see Fig. 11). Fixings can be made as before with a tinned screw positioned over each guide.

**Assembly of Action**

Wire staples are made from copper wire, a good fit in the holes. Bend at right-angles to match length between each pair of holes, commencing with guide against the metal support. Push through the two strips and guide, bend over to fasten.

When completed place assembly on the two supports and gradually push down whilst inserting the hoppers between their guides.

This done check that all work freely and, if necessary, remove any guide by undoing the staple and easing or packing as required.

The bottom holes in guides are drilled through into the wide strip. With care it is possible to do this without removing the assembly. A thinner wire is pushed through each drilling, given one twist and snipped off. It is an advantage that there should be a little sideplay here.

CONCLUDED NEXT MONTH

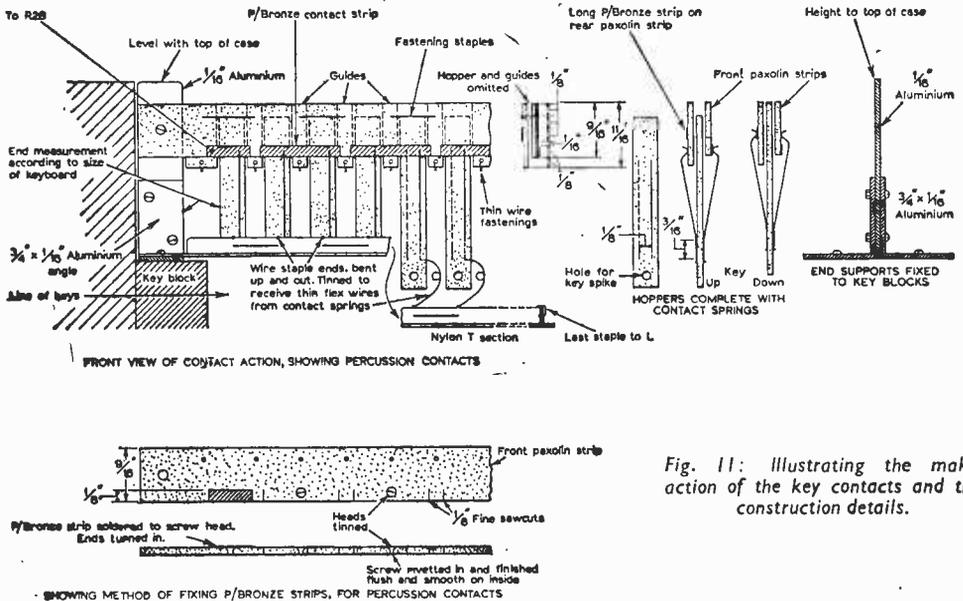


Fig. 11: Illustrating the making action of the key contacts and their construction details.



**LAFAYETTE HA 63 COMMUNICATION RECEIVER**

7 valves + Rectifier. 4 Bands 550 Kc/s-31 Mc/s. 'S' Meter-BFO-ANL-Bandsread Tuning 200/250v A.C. Brand New. 24 Gns. carr. paid.



**TE-22 SINE SQUARE WAVE AUDIO GENERATORS**

Sine: 20 c.p.s. to 200 Kc/s. Square: 20 c.p.s. to 25 Kc/s. 200/240 V. A.C. Brand new Guaranteed. £15. Carr. 5/-.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYZER**


2 pF, 2,000 mFd, 2 ohms, 200 megohms. Also, checks impedance. Turns ratio. Insulation 200/250v. A.C. Brand New £15. carr. 5/-.

**LONDON AGENTS FOR CODAR EQUIPMENT**

**LAFAYETTE HE-40 COMMUNICATION RECEIVER**

4 Bands 550 Kc/s-30 Mc/s. 'S' Meter-BFO-ANL-Bandsread Tuning - Built in speaker. 200/250v A.C. Brand New. 19 Gns. Carriage 10/-.

**S.A.E. FOR DETAILS OF ALL EQUIPMENT**

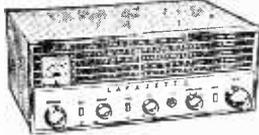

**LAFAYETTE HE-39 HI-FI AMPLIFIER**

9 valves. 550 Kc/s-30 Mc/s. Semi Kit form. 25 Gns. Carr. paid.

**LAFAYETTE TE-20A R.F. SIGNAL GENERATOR**

120 Kc/s-390 Mc/s on 6 ranges. Variable R.F. and A.F. outputs. Large clear scale. Size 7 1/2 x 10 1/2 x 4 1/2. 200/250v. A.C. Operation. Brand New £12.19.6. Carr. 5/-.



**Transistor 4-channel Microphone Mixer 49/6**


**Mullard OC81 Two for 5/-**

**VARIABLE VOLTAGE TRANSFORMERS**  
Brand New Guaranteed. Fully Shrouded. input 230v. 50/60 c/s output 0-230v.  
1 Amp £4.10.0. 8 Amp £4.10.0.  
2.5 Amp £5.17.6. 10 Amp £16.10.0.  
5 Amp £9.10.0. 12 Amp £18.15.0.  
2.5 Amp Portable 20 Amp £32.10.0.  
Metal Case with Meter Fuses etc. £9.17.6.



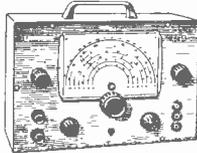**RK140 STEREO TAPE DECKS WITH BUILT-IN PREAMPLIFIER**

4 Transistors, 4 Valves. Will record or playback 1 Track Stereo or Mono at 7 1/2 or 3 1/2 IPS. 7in. spool size. Twin meter MW. 40-18,000 CPS., response. Size 15 x 10 x 6 1/2in. 200/250 volt A.C. operation. Brand New £42 Gns. P. P. 15/-.



**RCA AR.88 RECEIVERS**


L.F. Model 75-550 Kc/s and 1.5-30.5 Mc/s Guaranteed Perfect Order £85. carr. 30/-.  
D. Model 550 Kc/s-32 Mc/s. Guaranteed As New Condition-£85. carr. 30/-.



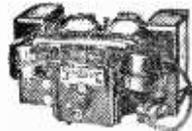**CLEAR PLASTIC PANEL METERS**

First grade quality. Moving Coil panel meters available ex-stock. S.A.E. for illustrated list. Discounts for quantity. Available as follows. Type MRA. 28P. 1 21/32in. square fronts.  
2mA .. .. 22/8 10V. DC .. 22/8  
5mA .. .. 22/8 20V. DC .. 22/8  
1mA .. .. 22/8 50V. DC .. 22/8  
50mA .. .. 22/8 100V. DC .. 22/8  
100mA .. .. 22/8 150V. DC .. 22/8  
150mA .. .. 22/8 300V. DC .. 22/8  
200mA .. .. 22/8 500V. DC .. 22/8  
300mA .. .. 22/8 750V. DC .. 22/8  
500mA .. .. 22/8 15V. AC .. 22/8  
500A .. .. 22/8 50V. AC .. 22/8  
50-0-500A .. 22/8 1-0-1mA .. 22/8  
100-0-100A .. 22/8 1A. DC .. 22/8  
500-0-500A .. 22/8 5A. DC .. 22/8  
1mA .. .. 22/8 5V. DC .. 22/8  
"S" Meter 1mA 29/6

**ARMY FIELD TELEPHONES TYPE F**  
Generator B-11 Ringing. 2 Line Connection. With Wood Carrying Case. Fitted Batteries. Supplied Fully Tested £4.19.6. Pair Carr. 5/-.



**LAFAYETTE HI-FI STEREO HEADPHONES**

16Ω -25-15,000 Cycles. Air Cushioned Headband with cables and overload Junction Box. Brand New Guaranteed. 82/6. P. & P. 2/6.



500A .. ..	32/6
1000A .. ..	29/8
2000A .. ..	27/6
5000A .. ..	25/-
50-0-500A ..	29/8
100-0-100A ..	27/6
500-0-500A ..	22/8
1mA .. ..	22/8

POST EXTRA - Larger sizes available - send for lists.  
**ILLUMINATED "S" METER.** 1 1/2in. square front. Cal. in 4 units. 6V. lamp. 29/6. P.P. 1/-. Ditto 2 1/2in. square 39/6. P.P. 1/-.



**TS-76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER**

Large clear plastic scale, simple operation. D.C. volts up to 1,000v. A.C. volts up to 1,000v. Resistance up to 10 megohm. Current up to 250mA. Decibels. 20 to + 36dB. Size 6in. x 4 1/2in. x 2 1/2in. Complete with leads, batteries and instructions. ONLY £5.5.0. P. & P. 2/-.

**TYPE 13 DOUBLE BEAM OSCILLOSCOPES**


Perfect order. £27.10.0. Carr. 20/-.

**AMERICAN TAPES**  
First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.  
3in. 300ft. L.P. mylar 4/-  
3 1/2in. 600ft. T.P. mylar 10/-  
5in. 600ft. std. plastic 8/6  
5in. 900ft. L.P. acetate 10/-  
5in. 1200ft. D.P. mylar 15/-  
5 1/2in. 1200ft. L.P. acetate 12/6  
3 1/2in. 1800ft. D.P. mylar 22/6  
7in. 1200ft. std. mylar 12/6  
7in. 1800ft. L.P. acetate 15/-  
7in. 1800ft. L.P. mylar 20/-  
7in. 2400ft. D.P. mylar 25/-  
Postage 2/-. Over £3 post paid.

**RECORDING HEADS**  
Reuter 1 track, set of 2, 19/6  
Miniflux 1 track, set of 3, 29/6  
Bradmatic 1 track, set of 2, 99/6  
Post Extra

**HEADSETS**  
D.L.R.A. LOW IMP 10/8  
R.C.A. LOW IMP 15/8  
Chamois padded moving coil with jack plug 22/6  
Ditto with Mic. 25/-  
All New-Post Extra

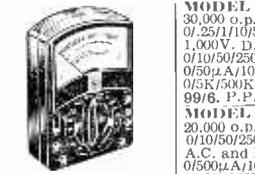**MULTI-METERS**  
Brand New-Fully Guaranteed. Lowest ever prices. Supplied with leads, batteries and instructions.



**MODEL NI-201**  
30,000 o.p.v.  
0/15/30/120/300/1,200/1,000V. D.C.  
0/10/50/250/500V. A.C.  
0/50A/10/250mA  
0/5K/500K/5 MegΩ  
99/6. P. & P. 2/6.

**MODEL AR-620**  
20,000 o.p.v.  
0/10/50/250/500/1,000V. A.C. and D.C.  
0/500A/6/60/600mA  
6/6K/600K/5 MegΩ  
5/6P.-2mFd  
£5.19.6. P.P. 2/6.

**MODEL NI-201**  
30,000 o.p.v.  
0/25/1/10/50/250/500/1,000V. D.C.  
0/10/50/250/500V. A.C.  
0/50A/10/250mA  
0/5K/500K/5 MegΩ  
99/6. P. & P. 2/6.

**MODEL AR-620**  
20,000 o.p.v.  
0/10/50/250/500/1,000V. A.C. and D.C.  
0/500A/6/60/600mA  
6/6K/600K/5 MegΩ  
5/6P.-2mFd  
£5.19.6. P.P. 2/6.

**MODEL PT-34**  
1,000 o.p.v.  
0/10/50/250/1,000V. AC and DC  
0/100/500mA DC.  
0/100KΩ  
39/6. P.P. 1/6.

**MODEL NI-400**  
10,000 o.p.v.  
0/3/30/120/300/600/1,200V. DC  
0/120V. A/30/300mA DC  
0/2K/200K/2 MegΩ  
100P.F.-2mFd  
79/6. P. & P. 2/6.

**MODEL 250J**  
2,000 o.p.v.  
0/10/50/500/2,500V. DC  
0/10/50/500/2,500V. AC  
0/2 MegΩ  
0/250mA  
-20 to +36dB  
49/6. P.P. 2/6.

**MODEL ITI-2**  
20,000 o.p.v.  
0/5/25/50/500/2,500V. DC.  
0/10/50/500/1,000V. AC  
0/50A/1/25/250mA DC  
0/50KΩ MegΩ  
.01-.3mFd  
82/6. P.P. 2/6.

**MARCONI TFI44G/4 STD SIGNAL GENERATORS**  
85 Kc/s-25 Mc/s. Perfect order. £25. Carr. 30/-.

**SILICON RECTIFIERS**  
250 P.I.V. 750mA 3/-  
200 P.I.V. 6 amp 5/6  
1,000 P.I.V. 650mA 7/6  
800 P.I.V. 500mA 5/6  
400 P.I.V. 3 amp 7/6  
400 P.I.V. 500mA 3/6  
150 P.I.V. 165mA 1/-  
70 P.I.V. 1 amp 3/6  
95 P.I.V. 3 amp 5/6  
Post extra


**MINE DETECTOR No. 4A**  
Will detect all types of metals. Fully portable. Complete with instructions. 99/6 each. Carr. 10/- Battery 8/6 extra.

**BEST BUY!**  
Send 1/- P.O. for full catalogue and lists.  
Open 9 a.m. to 6 p.m. Every day. Monday to Saturday. Trade supplied.

**G.W. SMITH & CO (RADIO) LIMITED**  
Phone: GERRARD 8204/9155  
Cables: SMITHEX LESQUARE  
3-34 LISLE STREET, LONDON, W.C.2


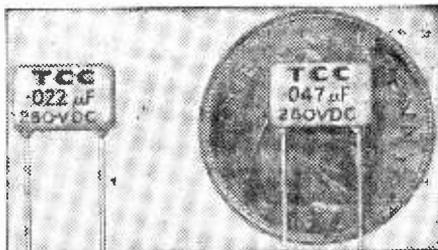
# MINIATURE METALLIZED POLYESTER CAPACITORS



Ideally suitable for printed wiring panels and transistorised circuits.

Incorporating a new dielectric material and of unique construction, they are of small physical size and meet the requirements of H.5 D.E.F. 5011 Specification. The windings are virtually non-inductive and the wire terminations are soldered direct to the metal electrodes eliminating contact resistance and ensuring the minimum possible inductance.

Cap Tolerance

$\pm 20\%$

Voltage Rating:

Ranges available in 250V D.C. and 400V D.C.

Power Factor:

$\leq 0.01$  at 1 Kc/s at  $+20^{\circ}\text{C}$ .

Temperature Rating:

Suitable for working at  $+85^{\circ}\text{C}$ . without degrading.

Details of the full range are given in T.C.C. Bulletin 93, available on request.

Insulation Resistance

10,000 megohms or 2,000 ohm farad whichever is less.


Terminations:

22 s.w.g. solder-coated parallel wires for vertical mounting.

Finish:

Insulated—special non-cracking heat resisting thermosetting compound providing good insulation and good protection against the ingress of moisture.

Cap. $\mu\text{F}$	Dimensions		T.C.C. Type No.
	H.	T.	
0.01	$\frac{1}{4}''$ 9mm	$\frac{1}{8}''$ 5.5mm	PM X1
0.022	$\frac{1}{4}''$ 9mm	$\frac{1}{8}''$ 5.5mm	PM X2
0.047	$\frac{1}{4}''$ 9mm	$\frac{1}{8}''$ 5.5mm	PM X3
0.1	$\frac{1}{4}''$ 11mm	$\frac{1}{8}''$ 7.2mm	PM X4

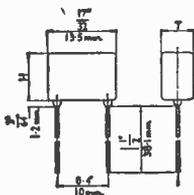


## THE TELEGRAPH CONDENSER CO. LTD.

Electronics Division • NORTH ACTON • LONDON • W.3 • Tel: ACOrn 0061 • Telex: 261383  
also at CHESSINGTON, SURREY and BATHGATE, SCOTLAND
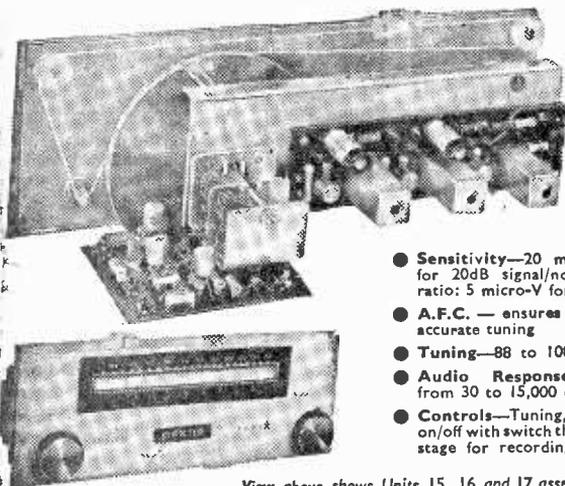
# NOW ADD F.M. RADIO to your MARTIN AUDIOKIT SET-UP

with only 3 easy-to-assemble prefabricated units



- Sensitivity—20 micro-V for 20dB signal/noise ratio; 5 micro-V for 40dB
- A.F.C. — ensures easy accurate tuning
- Tuning—88 to 108 Mc/s
- Audio Response—Flat from 30 to 15,000 c/s
- Controls—Tuning, and on/off with switch through stage for recording, etc.

View above shows Units 15, 16 and 17 assembled. Below, the attractive escutcheon.

UNIT 15  
F.M. Head & tuning condenser  
**£5.12.6**

UNIT 16  
I.F. Amp. **£5.7.6**

UNIT 17  
Mounting drive escutcheon & controls **£1.17.6**

**SUPERB QUALITY FOR VERY MODEST OUTLAY**

From Radio and Hi-Fi Stockists

Trade enquiries invited

**MARTIN ELECTRONICS LTD.** 154/5 High Street, Brentford, Middlesex ISLewth 1161/2

The unique and outstandingly successful system developed by Martin Electronics whereby prefabricated transistorised units can be assembled to make your own choice of hi-fi now brings 3 further Units, No. 15, 16 and 17 to enable you to build a modern F.M. Tuner of exceptionally good design and performance. Intended primarily for those who have chosen an Audiokit hi-fi set-up, the Tuner may also be used with other good amplifiers if desired. With a few simple connections, you will have a tuner of excellent appearance to please the most critical ear, yet it is surprisingly inexpensive.

A whole range of Audiokit Units is available which you can assemble to your own choice with ease and complete success. Ask for the Audiokit leaflet.

**MARTIN ELECTRONICS**

154 High Street, Brentford, Middlesex

Please send F.M. Tuner and Audiokit Leaflets to:

Name .....

Address.....

P.W.3

# on the Short Waves

## MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

### The Broadcast Bands—by John Guttridge

**A**LTHOUGH this feature is called "On the Short Waves", it is interested in DX (long distance) reception news of all sorts. News is given therefore this month of some recent loggings in the medium waveband.

For the beginner to medium wave DX the best station to try for is the Trans World Radio—Radio Nederland transmitter at Bonaire in the Netherlands Antilles. From 2330—0020 it carries the Spanish programme of Radio Nederland followed by the English programme from 0040—0130. From 0130 the programmes of Trans World Radio can be heard. The frequency is 800kc/s. In London a SINPO rating of 34343 was recorded at 0130 recently. Another very reliable one is the Canadian CBA (Maritime) on 1070kc/s.

Two listeners who have been "working" North America on medium waves between 2200 and 0200 are J. Fitzgerald (Great Missenden) and D. Walsh (Ballyllynch, Ireland). Some of those logged were—640 CBN St. John's, Newfoundland; 660 WNBC New York; 710 WOR New York; 860 CJBC Halifax, Nova Scotia; 880 WCBS New York; 930 CJON St. John's, Newfoundland; 940 CBM Montreal; 960 CHNS Halifax, Nova Scotia; 1,010 WINS New York; 1,010 CFRB Toronto; 1,050 WHN New York; 1,090 WBAL Baltimore; 1,130 WNEW New York; WMEX 1,510 Boston; 1,520 WKBW Buffalo; 1,560 WQXR New York.\*

Now let's take a look at changes in the Short Wavebands. First comes news from E. H. Conduit (Wolverhampton) of the introduction of English and Spanish transmissions by *Radio Algeria*. They are aired from 2200—2230 and 2230—2300 respectively on 11,835.

According to R. Coates, of Burton-on-Trent, the schedule of AFRS New York is now 1430—1900 on 15,225; 1430—1800 21,645; 1430—2245 15,280; 1815—2245 11,920; 1900—2245 11,905. The transmitters used are those of the *Voice of America* at Bound Brook (WBOU) and Greenville. Reception in London is usually good on most frequencies. Mailing address of the station is Armed Forces Press, Radio and Television Service, 250 West 57th Street, New York 19, U.S.A.

\* This season, the DX has been extremely good on the M.W. Band. My own log includes over 100 stations from U.S.A. and Canada (including a few from the West Coast). Also many Caribbean and South Americans, Africa, Iran, Iraq, India, Pakistan, Philippines, Okinawa, Formosa, China, Aden, Kuwait, etc. Some East Coast Canadians have been heard as early as 2000 G.M.T!—EDITOR.

News of test transmissions by Saudi Arabia Broadcasting comes from Roy Patrick (Derby) who says reports are wanted and should be sent to the Deputy Minister, Ministry of Information, Jeddah, Saudi Arabia. He has heard the transmissions from 1500—1700 on 9,670. Frequencies of 7,170 and 11,890 are also used according to the International Short Wave Club.

*Radio Nacional de Espana* now has a 50kW transmitter at Tenerife in the Canary Islands, says Roy Patrick. Transmissions are from 1400—1600 on 9,660. This frequency is given as 9,640 by the ISWC which also mentions a transmission from 0000—0300 on 11,800.

This year the Far East Broadcasting Company, Box 2041, Manila, Philippines, hopes to put the first of several new high power transmitters into operation. At present English programmes are aired at the following times. 2200—2330 on 15,300/17,810; 0330—0100 on 11,850/15,380/17,810; 0100—0200 on 15,380; 0230—0300 on 9,710/11,740/15,380/17,810 (also 0300—0830 Sundays plus 15,300); 0830—0900 on 9,710/11,920/15,380/17,810; 0900—1200 on 15,380/17,810; 1200—1430 on 15,300; 1230—1300 on 9,505/15,300; 1330—1400 and 1530—1630 on 9,505. There is also an 0900—1000 transmission on 11,850.

On March 7, 9,520 replaces 15,165 for the 0630—0700 and 0900—1000 transmissions from *Radio Denmark*. At the same time 15,165 replaces 9,520 for the 1600—1630 transmission.

Special English language programmes for the Caribbean are carried by the B.B.C. from 2230—2245 on Mondays to Fridays. The frequencies used are 6,110/9,580/11,750.

English language programmes are now transmitted as follows by *Radio New York Worldwide*, 4 West 58th Street, New York 19, N.Y., U.S.A. From 1200—1615 on 17,760/15,440/15,135/11,940; 1615—1730 17,760/15,440/15,135/11,940/11,840; 1730—1745 17,760/15,440/11,840; 1745—2000 17,760/15,440/11,840/9,640; 2000—2015 15,440/9,640; 2015—2140 15,440/11,940/11,855/9,640; 2140—2200 11,940; 2200—2400 6,015/11,940. The transmissions are beamed to Northern South America, the Caribbean, Africa, Continental Europe, the British Isles and Scandinavia.

Radio Moscow announces that the following frequencies are being used for its English transmission to North America starting at 2300: 9,660/9,620/9,570/7,360/7,310/7,290/7,250/7,200/7,150. Reception in London is good.

At present one of the most frequently heard 19 metre band transmitters is that of the *Voice of America* at Greenville.

From 1300—1400 15,235 can be heard with Spanish for Latin America. At 1400 the beam switches to Europe with a consequent jump in signal strength and a programme in Georgian begins. The signal is good and programmes include Ukrainian at 1530, Armenian at 1600 and Latvian at 1900. The Europe English outlet of 15,205 has

been heard at good strength at 1600 and 1900. CW interference spoils the 15,250 outlet which is beamed to Africa. Swahili is carried at 1830 with Arabic from 1900—1930. One of the last channels to fade out in the evenings is 15,415 which carries French and English to Africa. At close down at 2215 it returns SINPO 35333.

## The Amateur Bands—by David Gibson G3JDG

**S**UCCESS, success!! At last my ageing eardrums have been stimulated by signals heard on 21Mc/s. At 1140 G.M.T. on the 16th December I heard G3TMA, OH1WF, SMSLH, SM5BKY, EL8AF and 6W8BL, all on c.w.

Now an important point: readers sending in reports must make clear whether the stations logged were on 'phone or c.w. In order to avoid confusion 'phone stations can be given a two digit signal report, and c.w. three digits. These digits are, of course, the standard amateur Readability, Signal strength, and Tone. For instance: G3TMA (579)—R5 S7 T9. Therefore, the station was c.w. Or G3TMA (57), i.e. R5 S7, the station was on 'phone. Better still, keep 'phone and c.w. separate.

### Top Band

160 metres is going like a bomb! G-DX is about almost nightly and many Europeans are popping up. December 10th raised VO1FB (Newfoundland) 459, GM3FXM, GW3TOW, GW3HUM, GW3DRV, GW3PMR and GW3SPA, all between 2300—2330 G.M.T. December 16th gave 9LITL (Sierra Leone) 569, VO1BD 459, VO1FB 559, OK100 579.

It may not be generally appreciated, but at the moment the 160 metre Transatlantic and Worldwide DX tests are being held. Accepting a kind invitation from SWL Frank Videan I went along to his QTH to listen in on one of these test dates (December 20). The receiver was an Eddystone 888A, but the antenna was only 30ft of wire running from the bedroom window to the fence. We heard all these:

DJ8GR, DL7AA, PAØPN, 9LITL, OK1AFN, OK1KLX, OK1AGB, VO1BD, GW3CW, GW3SPA, PAØVB, OK1IQO, VO1FB, GM3TMK, OK1KIT, W1BB/1, W2IU, W1WY, DL1FF, W2GGL, W1HGT, VE3DDR, W1BU, VE2UQ, W8HRV, GI3PDN, VE3AGX, W2UWD, W1BHQ, VE2LI.

The next test dates are February 7th and 21st from 0500 to 0730. I would be interested to know what you hear.

### Other Bands

This month ten metres has been very dead, and twenty, usually good for some DX, failed to oblige. At the time of writing, it dies a natural death around 1900. Forty metres, however, is quite lively now and again. On December 13th most of Europe was there on c.w., including DJ9SQ, OK2KHF, LZ1KPG, SP8AJK, UA6CP, ITIAGA, YU1LM, YO5THY.

And at 1845 two real pieces of DX came out of nowhere.—VK2EO (449) and VK7SM (459) in QSO with YO8KAE. Just goes to show that besides sharp ears the magical gifts of patience and persis-

tence are a requirement for DX winking. Two virtues not possessed by your scribe!

Eighty was disappointing. Early evenings produced Europeans only, but later around 2330 the best that came in was W1PKW.

### Readers' Reports

From Renfrewshire, Gillies Wylie sends in the following report:

21Mc/s. SSB:—9M4LX, ZE4JZ, MP4TBJ, ZS7R, XE1FSV.

A.M. — VK6QL, VK3AZY, CR4AJ, CR7GM, 9JZMI, 9L1WN, VE3CQG, CT2AL. C.W.—ZD3TJ, W8AMO, WA1AGO, all between 1005 and 1830 hrs.

14Mc/s. SSB:—ZB2AK, FM7WQ, VK6MK, HC1MX, HK5ACI, VE1AJR/SU, W6MWF, VE6CJ.

3.5Mc/s. SSB:—WA2EVH, W1ONK. A.M.—VE2SX, VO1FX, SM7BSE/MM.

SWL Coull in Littlestone, Kent, has a recently acquired HRO with an end fed 60ft. antenna. This set up is working extremely well as the following list shows:—

3.5Mc/s — VE1IE (57), W1FRR (58), K1KDA (54/5), W2ZDL (56/7) all round 2200 and all SSB.

14Mc/s.—VE8ML (59), VE8RG (48), OX3MN (58), TG9RJ (57), all SSB from 1500—2000.

21Mc/s.—VK2NN (57), VK3AZY (58), ZC4TJ (56), 9J2W (58), 9J2DT (58), ZS1AB (56), WØYDB (58), KØFPZ (56), ZS6U (57).

R Collins writes in to query Z6AP/KC4 heard on 20 metres at 2330 and claiming the QTH as Queen Maud Land, Antarctica. Anyone else heard this one?

Maurice Curtis in Sheffield with an EA12 receiver found the following on 14Mc/s 'phone between 1345 and 1845:—

K5ZVP, W2RNV, W2RAV, UO2GC, W2ONV, W4SHP, UH8BO, H89JO, W2BLF, W4RJO, VO8AF, K8AIR, W4FZE, K1DRE, W5AZI/MM (Marine Mobile) 11FW, W8TF, W4BHU, W1KJ, W9DPI, DJ5JI.

### News in General

People puzzled by the prefix SPØ will be pleased to note that the Ø prefix was issued to SP stations instead of their numeral i.e. 9 and was authorised for the duration of the International Marathon DX scheme which was in operation from May to September last year. VK3TL reported loose on Norfolk Island with s.s.b. and c.w. while CEØAG also s.s.b. and c.w. is keeping Easter Island on the radio map. In case you think its cold at your QTH, spare a thought for KC4USN who is in Antarctica. He runs s.s.b. into a Rhombic antenna pointed at

—continued on page 1093

**New list of Bargains**

Transistor ferric rod aerial with medium and long wave coils with circuit, 7/6.

Oscillator Coil and set of 3 I.F. transformers or transistor set with circuit, 12/6. Tuning Condenser to suit air-spaced with trimmers, 9/- Dito but min. 10mm., 12/6 the set; two gang Condensers to suit, 8/8 (request sub. circuit).

Midget 3m. P.M. Loudspeaker 3 ohm 12/6, 80 ohm 18/6.

Midget 808 pF + 178 pF two-gang Tuning Condenser with trimmers for transistor set Price 9/-.

Push-Pull Transformer. Sub-miniature 8/6. 0005 mid. Sin. Tuning Condenser. Solid dielectric 1in. spindle for transistor or Crystal set, with spindle tapped 6 BA, 2/8 46 Sets (Receiver/Transmitter pack set). Unused sets complete except for crystals. Packed with parts and easily rebuildable into other gear. 19/6 each. Post 3/-.

Mains Transformer. 250-0-250 at 80 mA, 6.3 volts, 5a (normal mains input), 12/6 each. Garage 2/6.

Output Transformer. Standard pentode matching type, 3/6 each. 38/- per doz.

Slide Switch. Sub-miniature but dptd, 2/- each, 18/- per doz.

Other gear. 19/6 each. Post 3/-.

Battery Charger Kit. Comprises 5 amp. transformer, 5 amp. rectifier, metal case and meter to charge 6 or 12 volt batteries up to 5 amps. With variable charge rate, 99/6 each. Post and insurance, 3/6.

T.C.C. or Dubilier Tubular Condensers.

.5 mf 500 v. . . . .	10/- doz.
.25 mf 500 v. . . . .	7/8 doz.
.125 mf 500 v. . . . .	6/- doz.
.05 mf 500 v. . . . .	5/- doz.
.0001 mf 1,000 v. . . . .	5/- doz.
.001 mf 1,000 v. . . . .	6/- doz.
.002 mf 1,000 v. . . . .	7/8 doz.
.005 mf 1,000 v. . . . .	9/- doz.
.02 mf 750 v. . . . .	8/6 doz.
.01 mf 1,000 v. . . . .	10/- doz.

Battery Charger Rectifier—selenium 12.15 v. 5 amp. 9/6.

Metal Chassis—punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled, 12/6 set.

Filament Transformer, 6.3 v. 11 amps, 8/6. Neon Lamp—midget wire ended. Ideal mains tester, etc., 2/- Ex. Govt., 1/6.

Philips Trimmers—0.30pF 1/- ea., 9/- doz. Tag Panels. Ideal for constructors, experimental circuits, etc. 3 of each of 12 different types, 5/-.

Slidek Panel Mounting Fuses with carrier. 5 amp, 2/- each. 15 amp, 2/8 each.

Metal Rectifier. 250 v. 60-90 millamps, ideal for mains set or instrument or to replace that expensive valve, 4/6.

Piano Key Type Switches, 3 key type 3/-, 1 key type 3/8, 5 key type 4/6, post and packing 1/-, regardless of number ordered.

Ozone Ounit, for removing smells and generally improving and oppressive atmosphere. Kit consists of Philips ozone lamps and mains unit, only needs box. 19/6 + 3/6 postage and insurance.

Black Light Unit, 125 watt intensity, comprises quartz lamp, adjustable lamp holder and 123 watt choke. Only 29/8 + 6/6 carriage and insurance.

Packard Bell Pre-Amp. Contains a relay push-pull input and output transformers and many useful spares. Less valves 6/8 each + 2/8 post and insurance.

Fridge Handles, with Yale-type locking mechanism, two keys and locking plate, 2/8 + 2/- post, 8 for 30/-, post free.

0-1mA Meter made by the American Westinghouse Co. 3in. diameter, flush mounting scale calibrated in volts. 25/- + 2/- post and insurance.

Ferrari Fire Bar. 500 watt 10in., 3/8 each + 1/- post. Three or more post free.

B7G Valve Holder. Best make (Amphenol). 8/- dozen, post 1/6. 3 dozen, post free.

Precision Wheatstone Bridges, opportunity occurs to build—100k wire wound 15 watt potentiometer, price 5/- + 1/- postage.


Olydon Turret Tuner. 35 Mc/s, with band 1 and band 3 coils. Brand new, 9/8 each post 2/6.

**Hi-Fi Speakers**

Hi-Fi Speakers—E.M.I. Ceramic magnet 12,000 lines, size: 13 x 1in. (roughly equivalent to 12in. round speaker). Bass frequency 40-30 c/s. Handles up to 10 watts. Price 89/6 plus 5/- carriage and ins. State whether 15 ohm or 3 ohm.

Where postage is not definitely stated add 2/- all orders under £3.

**GOOD COMPANION Mark III**

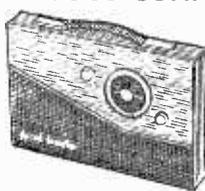

The 6 transistor set with the 8 transistor performance. Incorporating all the latest requirements. Anyone who can solder can make it. Many thousands already in use all over the country. Full coverage of Long and Medium wavebands. Fine locking cabinet, size 11 x 8 x 3in. Q.P.P. Output approx. 750 mW. Excellent reception of difficult stations like 205. Variable feed back gives excellent tone. Complete Kit, £4.19.6 everything for ONLY P. & P. 5/-.

**OUR BARGAIN OF THE YEAR**



A complete kit of parts to build 6 transistor 2 wave superhet receiver at only 45/-. Post and Ins. 3/6. "CORONET" Mk. IV

It fully covers the medium waveband and that part of the long waveband to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and 2 1/2in. P. M. speaker. Overall size approximately 4 1/2 x 2 1/2 x 1 1/2in. Supplied complete with carrying case.

**Infra Red Heater**

Make up one of these latest type heaters, ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—use silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and metal casing as illustrated 19/8 plus 2/6 post and insurance. Full switch, 3/- extra.



**—THIS MONTH'S SNIP—**


**AIRCRAFT RADIO RECEIVER**



Type CW 0460 48 D This is part of the equipment RU19, American made equipment for the Navy. It is a 5-valve receiver with a really beautiful precision tuning mechanism. Brand new and in original packing but less coil units. Limited quantity only, 19/8 plus 3/6 P. & P.

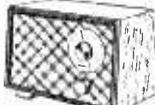**INTERCOM BARGAIN**

Cabinet as illustrated, less knobs, ideal if you are tanking small radio, office intercom, amplifier, etc. Has the modern look; originally sold at 20/6 limited quantity available at 15/-, plus 2/6 postage. All components to make two of the intercoms described in "Practical Electronics," 7/6-.



**£5.10.0 Radio for only 27/6**

Originally sold at £5.10.0, we now offer the "Pimpernel" 3/ Transistor Pocket Radio at only 27/6. The set is complete but are "line rejects" so there will be some small faults to find. Components are all new and unused, and their retail value, even at today's lowered price, is over £4. Parts you will get include:— Jackson "OO" Tuning Condenser, 9/-. Plessey Driver Transformer, 8/6. Goodman's or Plessey 3in. speaker, 12/6. Borganite Volume Control with switch 4/6. Philips RF Transformer, 12/6. S.T.C. matched output transformer and driver 15/-. Plastic case with carrying handle, 7/6. 5 Electrolytic Condensers, 7/6. 10 Resistors, 3/8. Ferrite Aerial, 5/- and printed circuit board, trimmer, battery connectors, r.f. choke, etc., etc. All this fine equipment offered this month at only 27/6 plus 2/6, post and insurance.



**FLUORESCENT LIGHTING BARGAINS**

Complete 40 watt 3in. white enamel-clad fitting, ready for use with choke control gear, radio suppressed starter and tube. Originally intended to sell at £3.15.0, offered at only 39/6, plus 3/- carriage and insurance; two or more carriage free. Ditto fit. 80 watt 49/6, plus 7/6 carriage and insurance. two or more, carriage free.

**MAKING AN FM TUNER**



Available at present is a very nice oad/min. plated P.M. Tuner chassis with holes punched for coils and other components, also a nicely printed perspex front, calibrated using P.M. frequencies. Real bargain 8/6 + 2/- or with two-gang tuning condenser 10/- + 2/- postage.

**Speaker Bargains**

12in. High-fidelity loudspeaker. Eight 1/2in. permanent magnet type with either 3 ohm or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 27/8 + 3/6 post and insuranc.



**Waterproof Heater Wire** 16 yds length. 70 watts, self regulating temperature control. 10/- post free

**TRANSISTOR SET CASE**

Very modern cream cabinet, size 6 1/2 x 3 x 1 1/2in. with chrome handle, tuning knob and scale. Price 4/8 plus 1/6 postage.




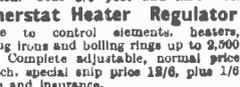**Building a 'Scope**

3in. oscilloscope tube. American made type No. 3P47, 6.3 v. 0.8 amp. heater electrostatic deflection, brand new and guaranteed with circuit diagram of scope, 15/- each. Plus 2/6 post and insurance.



**Simmerstat Heater Regulator** Suitable to control elements heaters, soldering irons and boiling rings up to 2,900 watts. Complete adjustable, normal price 55/- each, special snip price 18/6, plus 1/6 postage and insurance.



**THERMOSTATS**

Type 'A' 15 amp. for controlling room heaters greenhouse, airing cupboard. Has spindle for pointer knob, quickly adjustable from 30-80°F. 9/6 each. Suitable box for wall mounting, 5/- P. & P. 1/-.

Type 'B' 10 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-650°F. Internal screw alters the setting so this could be adjustable

over 30° to 1,000°F. Suitable for controlling furnace, oven, kiln. Immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.

Type 'D' is a small porcelain thermostat as fitted to electric blankets etc. 14 amp. setting adjustable by screw through side, 5/6, P. & P. 6d.

Type 'E'. We call this the Ice-stat as it cuts in and out at around freezing point, 2-8 amps. Has many uses, one of which would be to keep the hot pipes from freezing, if a length of our heater wire (18 yds. 10/-) is wound around the pipes, 7/6, P. & P. 1/-.

Type 'F'. This is a standard refrigerator thermostat. Spindle adjustments over normal refrigerator temperature, 7/6 plus 1/- post.

**Timer Kit**

Special offer of all components except metal box to make using operated interval timer for photography etc. 18/6 plus 3/6 post.

**ELECTRONICS (CROYDON) LTD**

266 LONDON ROAD WEST CROYDON SURREY  
Post orders to: 43 Silverdale Road, Eastbourne, Sussex

# IMPROVED

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions.

Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.

STANDARDS OF



Mk 4

# MULTIMINOR

# ACCURACY AND RELIABILITY

The Mk 4 MULTIMINOR is an entirely new version of this famous Avo instrument and supersedes all previous models. It is styled on modern lines, with new high standards of accuracy, improved internal assemblies, and incorporating panclimatic properties.

The instrument is supplied in an attractive black carrying case, which also houses a pair of leads with interchangeable prods and clips, and an instruction booklet. It is packed in an attractive display carton. Robust real leather cases are available, if required, in two sizes, one to take the instrument with leads, clips and prods, and the other to house these and also a high voltage multiplier and a d.c. shunt.


D.C. Current: 100µA f.s.d. — A f.s.d. in 5 ranges	Resistance: 0.2 MΩ in 2 ranges using 1.5V cell.
A.C. Voltage: 10V f.s.d. — 1,000 f.s.d. in 5 ranges	Sensitivity: 10,000Ω/V on d.c. Voltage ranges.
D.C. Voltage: 2.5V f.s.d. — 1,000 f.s.d. in 6 ranges	1,000Ω/V on a.c. Voltage ranges.
D.C. Millivolt range: 0 — 100mV f.s.d.	

● For full details of this great new pocket-size instrument, write for descriptive leaflet.

**AVO LTD** AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - VICTORIA 3404 (12 lines)



MM17

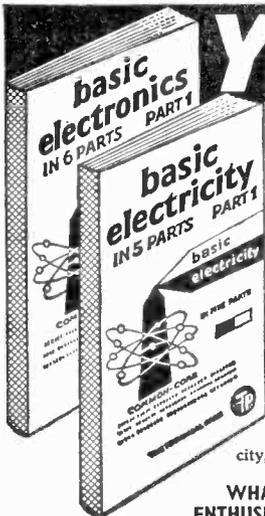

# YOURS FREE FOR 7 DAYS

## The New 'Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the **Pictorial Approach** to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

### WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTBAG. "Clear, concise and really to the point: I agree that your pictorial approach to learning is wholeheartedly appreciated by my trainees," signed Training Officer. "I am very pleased with my purchase, I only wish I had bought a set a few years ago when they first came out. They are a good bargain." P.S.G., Bristol. "Thank you for a wonderful set of manuals." A.G.A., Birmingham.

To Selray Book Co.  
60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY  BASIC ELECTRONICS

Signature \_\_\_\_\_ (If under 21, signature of parent or guardian)

Name \_\_\_\_\_  
BLOCK LETTERS BELOW  
FULL POSTAL  
Address \_\_\_\_\_

**POST NOW FOR THIS OFFER !!**


**TRADE NEWS • TRADE NEWS • TRADE NEWS • TRADE NEWS • TRADE NEWS**

**Transistor Set Inductive Amplifier**

FROM Design Engineering Wokingham Ltd., comes the "Dewtron" Wave Trap, designed to improve reception on medium wave stations when used in conjunction with any transistor or portable radio.

Basically the circuit comprises an r.f. stage, which contains a ferrite tuned circuit capable of receiving m.w. signals. The amplification of this stage is very high, and its output is fed into an inductive element on the end of a length of screened cable. This element is termed the "injector", because when placed near to the ferrite rod in the portable radio, its output is injected into the aerial by direct induction.

On distant stations, the Wave Trap injects a boosted signal in such a way that the mean level of received signal at the set is of sufficient order to ensure that the a.v.c. circuit operates, and will then ensure that any variations in the mean received signal level will not be noticed in the loud-speaker. When used in place of a car aerial on reasonably local stations, the high factor of amplification afforded by the Wave Trap's circuit makes sure that the inherent directional characteristic of the Wave Trap receiving ferrite aerial is cancelled, since the receiver is once again fed with a signal of sufficient strength to make it operate well beyond the a.v.c. threshold, even when the vehicle turns so that the Wave Trap aerial is in the "null" position. Battery voltage is 9V and the current drain is 4mA. Price is 39s. 6d. p. and p. 1s. 6d. Design Engineering (Wokingham) Ltd., "Caledon", Ringwood Road, Ferndown, Dorset.

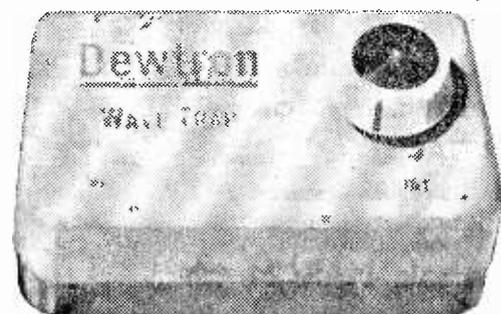

Above: The "Dewtron" Wave Trap inductive amplifier.


Right: The BEO BOX fully transistorised battery, mains table radio.

**SSB Transmitter/Receiver**

THE Hammarlund Manufacturing Company, a Giannini Scientific Company, has announced the CSB-125C s.s.b. transmitter/receiver. The power output of this unit is 125W s.s.b.-p.e.p., and six channels can be provided (two of these supplied and the other four optional), to cover the frequency range 2 to 30Mc/s.

The CSB-125C features sensitivity of less than 0.5µV for s.s.b./c.w. and 1µV for 10dB s.n./n ratio, 30% modulation on a.m. The separately housed power supply is designed for 115/230V, 50/60c/s operation.

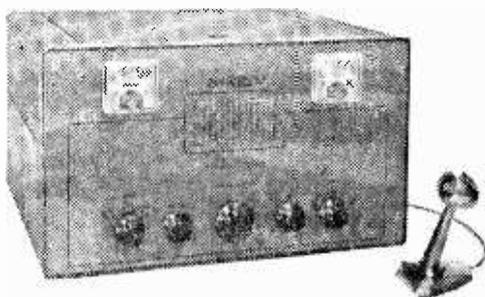
The U.K. agents for this range of equipment are K.W. Electronics Ltd., Vanguard Works, 1 Heath Street, Dartford, Kent.



Hammarlund's CSB-125C s.s.b. transmitter/receiver.

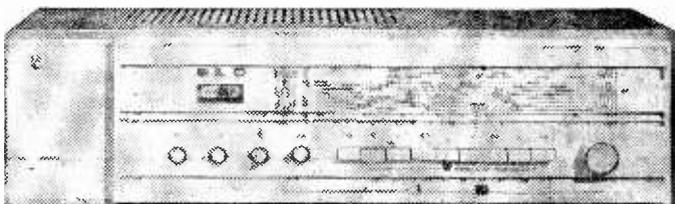**Mains/Battery/Table Radio**

A NEW model in the Bang and Olufsen range is the Beo Box battery operated transistor table radio, having a separate power unit for mains operation. It covers v.h.f., medium, long and two short wave bands (1.45-4Mc/s and 7-16Mc/s), and has 14 transistors and 8 diodes. Weighing 16lb., and measuring 19½in. x 8½in. x 6in., this receiver has the feature of providing a high standard of reproduction without a mains supply. The output is 2W when operating from the mains and 1W when working from batteries. There is an 11in. x 7in. elliptical speaker, and separate treble and bass controls are provided. A 500µA moving coil indicator gives visual indication of accurate tuning, and the aerial is detachable and rotatable and can be used for the improvement of v.h.f. and short wave reception. Finished in teak, the Beo Box retails at 39 guineas. St. Aldate Warehouse Limited, Innsworth Lane, Gloucester.



# FREE INSIDE NEXT MONTH'S ISSUE

## "PRACTICAL WIRELESS"


# 24-PAGE POCKET GUIDE

Packed with invaluable at-a-glance data. You'll use it again and again.

It includes:

- ELECTRICAL QUANTITIES UNITS AND SYMBOLS
- WIRE AND METAL GAUGE DATA AND COMPARISONS
- FREQUENCY AND WAVELENGTH DATA with Conversion Table
- DECIBEL CALCULATIONS

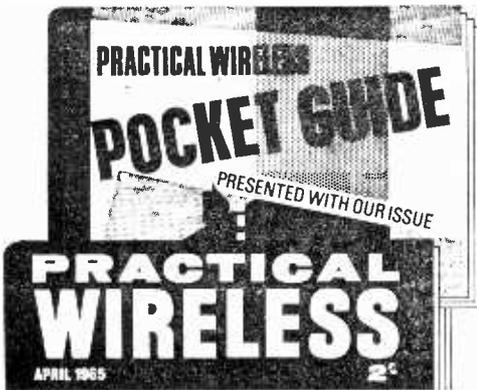Plus Multiples and Sub-Multiples - Greek Alphabet Symbols - Conversion of Units and Constants - Eureka Resistance Wire Data - Copper Wire Data - Transformer Matching - Time Constants



Also in the April issue

- FIDELITY F.M. TUNER WITH PULSE-COUNTER DISCRIMINATOR
- THE IONOPHONE LOUDSPEAKER
- S.S.B. USING A PRODUCT DETECTOR
- COMBATING INSTABILITY
- PLUS other articles and all the regular features

## APRIL ISSUE on sale MARCH 4th

**MAKE SURE OF YOUR COPY!**

Hand this form to your Newsagent

To .....(Name of Newsagent)

Please send/reserve the April issue of "PRACTICAL WIRELESS" (2!-), on sale March 4th, and continue until further notice.

Name.....

Address .....

THE PRACTICAL WAY  
TO ENJOY ELECTRONICS



HIGHEST QUALITY  
AT LOWER COST

## World-famous kit-sets anyone can build

The clearly written instruction manuals, issued with each kit, show you how  
**A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, LABORATORIES**



**HI-FI F.M. TUNER.** Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. output (£215.0 incl. P.T) I.F. Amp. (FMA-4U) complete with cabinet and valves. (£133.0). Total kit £15.18.0. Assembly can be arranged.

**COMMUNICATIONS TYPE RECEIVER.** Model RG-1. Freq. cov: 600 kc/s.-1.5 Mc/s; 1.7 Mc/s.-32 Mc/s. A two-speed tuning drive. R.F. "Front end" supplied assembled and aligned. Kit £39.16.0. Assembled £53.0.0.



**HI-FI A.M./F.M. TUNER.** Covers F.M. 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000m. Tuning heart (£4.13.6 incl. P.T.) and I.F. Amp. £21.16.6. Printed circuit board. Total Kit £26.10.0  
**6W DE LUXE AMPLIFIER.** Model S-33H. An inexpensive Stereo-Mono amplifier with high sensitivity. Suitable for Decca Deram Cartridge. Kit £15.17.6. Assembled £21.7.6  
**6 TRANSISTOR PORTABLE.** Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7 x 4in. high flux speaker. Real hide case. Very easy to build. Kit £12.11.0 incl. P.T. Tax  
**SHORTWAVE TRANSISTOR PORTABLE.** Model RSW-1. Two short bands, trawler and medium wave Kit £19.17.6 incl. P.T. Tax

**5W HI-FI MONO AMPLIFIER.** Model MA-5. A low-priced well designed amplifier. Printed circuit construction makes it easy to build. Kit £10.19.6. Assembled £15.10.0  
**'COTSWOLD' HI-FI SPEAKER SYSTEMS.** MFS or Standard. Range 30-20 000 c/s. Kit £23.4.0. Assembled £30.15.0  
**MONO CONTROL UNIT.** Model UMC-1. Ideal for use with MA-12 or similar amplifier. Kit £8.12.6. Assembled £13.12.6  
**HI-FI EQUIPMENT CABINETS.** Large range, in kit form or assembled and finished, incl. record housing range, available to meet various needs. Details on request. from £7.7.0 to £37.16.0

## SEND FOR FREE BRITISH HEATHKIT CATALOGUE — MANY MODELS TO CHOOSE FROM

All models available assembled.

Deferred terms available over £10.

Free delivery U.K.




**5in. OSCILLOSCOPE.** Model 10-12U. Wide band amplifiers essential for T.V. servicing, F.M. alignment etc. T/B covers 10 c/s-500 kc/s in 5 ranges. Kit £32.12.6. Assembled £41.10.0. The ideal low-priced 'scope.

**'OXFORD' DE-LUXE TWO WAVEBAND TRANSISTOR PORTABLE.** Model UXR-2. The ideal domestic, car, or personal portable receiver. 10 Semi-conductors. Send for full details. £14.18.0 Kit (incl. P.T.). Assembly can be arranged.



**PA AMPLIFIER.** Model PA-1. 50W output. For vocal and instrumental groups, guitars, etc. 4 inputs, 2 speakers, Tremolo. Send for full details. Kit £54.15.0. Legs optional extra 17/6 set. Assembled £74.0.0.

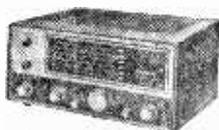**50W POWER AMPLIFIER.** Model MA-50. Ideal for PA work etc. Kit £19.18.0. Assembled £27.18.0.



RA-1


**2½in. PORTABLE SERVICE OSCILLOSCOPE.** Model OS-1. An ideal light, compact 'scope for servicing and general work. Printed circuit construction. Kit £22.18.0. Assembled £30.8.0.  
**'MOHICAN' TRANSISTOR GEN-COVERAGE RECEIVER.** Model GC-1U. An excellent portable for the short wave listener. Kit £37.17.6. Assembled £45.17.6  
**VALVE VOLTMETER.** Model V-7A. Measures up to 1,500 v. (D.C. and r.m.s.) and 4,000 pk-to-pk. Res. 0.1Ω to 1,000 MΩ. Kit £13.18.6. Assembled £19.18.6.

**AMATEUR BANDS RECEIVER.** Model RA-1. Covers the amateur bands from 160 to 10m. Special features incl.: half-lattice filter; 8 valves; Tuning meter; tuned RF amplifier stage. Kit £39.6.6. Assembled £52.10.0.

**Q MULTIPLIER.** Model QPM-1. For 450/470 kc/s. I.F. Kit £8.10.0. Assembled £12.14.0.

**LATEST AMERICAN SINGLE-SIDE-BAND AMATEUR EQUIPMENT.** Now available from Gloucester. Please send for details.

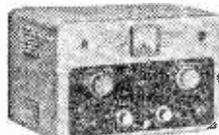**MULTIMETER.** Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C. 0-150µA—15A D.C. 0.2Ω to 20MΩ 4½ in. 50µA meter. Kit £12.18.0. Assembled £18.11.6  
**R.F. SIGNAL GENERATOR.** Model RF-1U. Up to 100 Mc/s. fundamental, 200 Mc/s. on harmonics. Up to 100 mV output all bands. Kit £13.8.0. Assembled £19.18.0



**TELEVISION ALIGNMENT GENERATOR.** Model HFV-1. Accurate alignment of TV receivers achieved in minimum time at low cost. Covers 3.6 to 220 Mc/s. fundamentals. £34.18.0 Kit. £44.10.0 Assembled



DX-100U

**AMATEUR TRANSMITTER.** Model DX-40U. Self-contained. 80-10 m. Power input 75 w. CW., 60 w. peak C.C. phone. Output 40 w. to aerial Prov. for VFO Kit £33.19.0. Assembled £45.8.0

**AMATEUR TRANSMITTER.** Model DX-100U. Covers all amateur bands. 160-10 m. 150 w. D.C. input, self contained with power supply, Modulator, VFO Kit £79.10.0. Assembled £104.15.0

# DAYSTROM LTD.


Dept. P.W.3, GLOUCESTER, ENGLAND

A subsidiary of Weston Instruments Group, manufacturers of the  
**WORLD'S LARGEST-SELLING ELECTRONIC KITS**

Send me **FREE BRITISH CATALOGUE** (Yes/No)  
Full details of model(s) \_\_\_\_\_

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

PW3

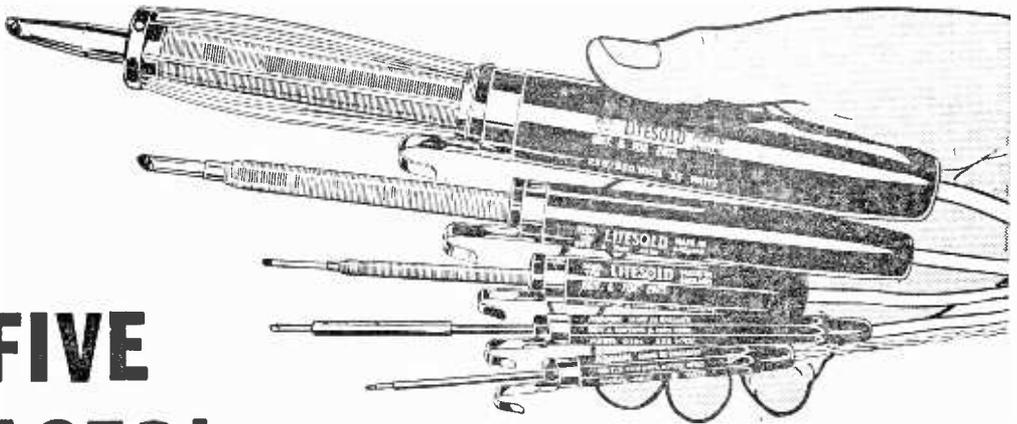

# FIVE ACES!

This is a hand that can't be beaten. Five models from our tremendous range of soldering instruments. Superb performance. Amazingly compact. Developed to simplify YOUR soldering. Copper bits for greatest speed. Permatip bits for long life. May we deal you in?


Brochure P.W.10 post free on request

**LIGHT SOLDERING DEVELOPMENTS LTD.**, 28, Sydenham Road, Croydon, Surrey

Telephone: CROydon 8589

**HOME RADIO LTD.** 187 LONDON RD., MITCHAM, SURREY 'Phone MIT 3282


## WE HAVE IN STOCK ALL THE RANGE OF ARMSTRONG TUNERS AND TUNER AMPLIFIERS

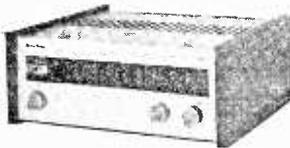

Model 223

Model 223 is an  
**AM/FM TUNER**

PRICE **£28.15.0**

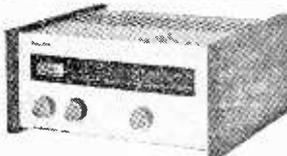

Model 224

Model 224 is an  
**FM TUNER**

PRICE **£22.10.0**

Don't forget that the Home Radio Catalogue is the most comprehensive catalogue offered to the constructor to-day

PRICE **5/-** PLUS 1/- POSTAGE AND PACKING

# PREPARING R.A.E. FOR THE

BRIAN ROBINSON.

## 5: THERMIONIC VALVES

### 5.1 The Emission of Electrons from a Filament

WHEN a hot wire or FILAMENT is enclosed in an evacuated glass bulb it will give off "particles". These particles are called ELECTRONS. If a plate of metal is introduced into the bulb it will be found that electrons from the filament will strike the plate. Many more electrons will be attracted to the plate if a POSITIVE potential is applied to it as this will attract the negatively charged electrons. The higher the positive potential applied to the plate the greater will be the electron flow from the filament to the plate. In the diagrams shown in Fig. 38 the electrons emitted by the filament are represented by arrows.

As we saw when dealing with simple d.c. circuits a current can only flow in a circuit when the circuit is complete. Therefore to show the current flowing from the filament to the plate a milliammeter must be connected between the filament and the plate.

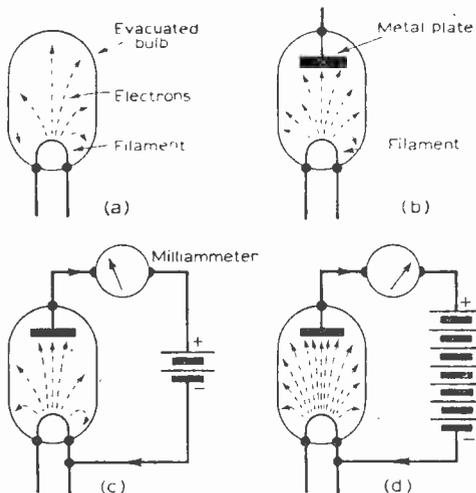


Fig. 38: A heated filament in an evacuated bulb emits electrons (a), some of which strike the metal plate (b). When a positive potential is applied to the plate, more electrons are attracted to it (c) and the greater the potential, the greater the electron flow (d).

The flow of electrons from the filament to the plate or ANODE is the principle on which the operation of the radio valve is based. The valve is so called because it will allow electrons, which enable a current to flow, to travel in one direction only—i.e. towards the plate or anode. If a negative potential were applied to the anode no current would flow as this would only repel the negatively charged electrons.

### 5.2 The Diode

This is the simplest type of valve and it has only two ELECTRODES, the FILAMENT or CATHODE and the PLATE or ANODE. The two electrodes are generally arranged concentrically so as to increase the area of the anode.

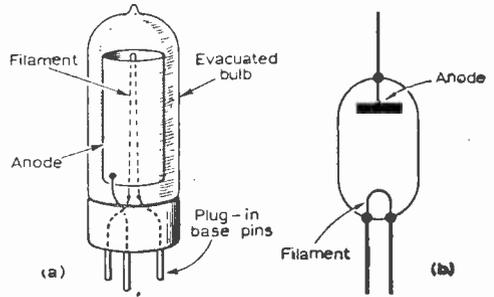


Fig. 39: The diode: (a) practical representation; (b) theoretical representation.

In the diagrams shown in Fig. 39 the type of diode shown is called a *directly heated diode*. This is because the electrons which travel to the anode come directly from the filament. However, the surface area of the filament is very small and the current which could be drawn from it would also be small. The current could be increased by increasing the temperature of the filament but an easier way is to encase it in a sheath of metal which will emit many electrons at a low temperature. In this case the filament now becomes the HEATER (i.e. it heats the sheath) and the sheath is called the CATHODE. This type of valve, which has the heater enclosed by the cathode, is called an *INDIRECTLY HEATED* type as the electrons come from the cathode and not the heater.

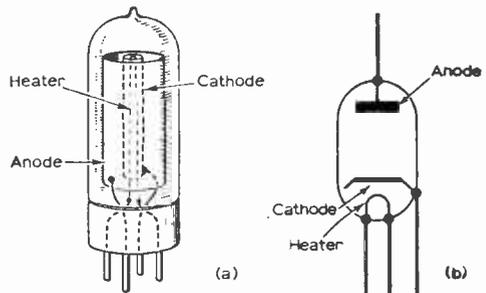


Fig. 40: The indirectly heated diode, practical construction (a) and theoretical representation (b).

Practical and theoretical representations of an indirectly heated diode are given in Fig. 40 (N.B.: The cathode in an indirectly heated valve is generally made of a base metal with a coating of barium oxide, strontium oxide, etc.).

**5.3 Characteristic Curve of the Diode**

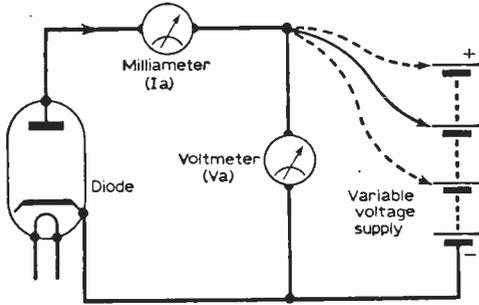


Fig. 41: Circuit to determine the characteristic curve of a diode.

If the circuit shown in Fig. 41 is set up the anode voltage can be varied and for each value of anode voltage the corresponding value of the anode current can be found. It would be suitable to start the anode voltage at 0 and increase this in 10V steps until no further increase in anode current is noted.

Typical results obtained using the circuit shown in Fig. 41 are shown in Fig. 42 and the graph which results when these are plotted is shown in Fig. 43.

It can be seen from the graph that there is a fairly long, STRAIGHT LINE portion and the valve is generally operated within the limits of this portion

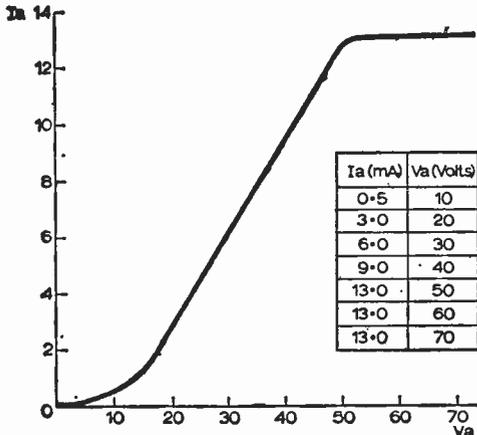


Fig. 42: (inset table): Typical values obtained using the circuit in Fig. 41.

Fig. 43: Graph obtained by plotting Va against Ia.

of the graph—e.g. in this case the valve would be operated with anode voltages between 20 and 50V and anode currents of between 3 and 13mA. It can be seen that on the graph the anode current has been represented by Ia and the anode voltage by Va. This type of graph is therefore usually called an Ia/Va graph and, as its name suggests, it shows the relationship between anode current and anode voltage.

If the graph shown in Fig. 43 is studied it can be seen that after a certain value of anode current is reached any further increase in anode voltage will not cause it to rise any further. When this occurs the value of anode current noted is called the SATURATION CURRENT and the valve is said to be SATURATED. The point on the graph where saturation first occurs is called the SATURATION POINT.

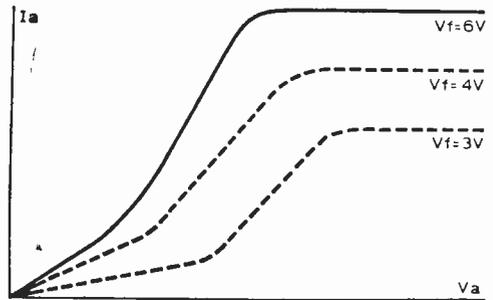


Fig. 44: Characteristic curves using different heater voltages.

If the characteristic curve for a diode were taken with heater voltages less than the recommended value the curve(s) would be of the type shown in Fig. 44.

**5.4 The A.C. Resistance or Impedance of a Diode**

We know from Ohm's Law that  $R = \frac{E}{I}$

therefore if we find the limits of the straight line portion of the characteristic curve of a diode we could express the SLOPE of this portion of the graph as being from, say, 20—50V and from 3—13mA. This is represented on Fig. 45. We can see that the line AB extends over 30V and the line

BC extends over 10mA. Knowing that  $R = \frac{E}{I}$  the a.c. resistance of the valve could be expressed as being

$$\frac{30}{0.01} \text{ ("I" must be in AMPS)}$$

or 3,000Ω.

Therefore the a.c. resistance of this particular diode would be expressed as being 3,000Ω. The a.c. resistance of a valve is sometimes called the IMPEDANCE or DIFFERENTIAL RESISTANCE of the valve. The valve used as an example

# Why

## NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...


BACKED BY OUR SUPER AFTER SALES SERVICE

### ROAMER SEVEN Mk III

5 WAVEBAND PORTABLE OR CAR RADIO  
Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 9 stages—7 transistors and 2 diodes  
Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned heavy duty "Celestion" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Real leather-look case with tilt trim and shoulder and hand straps. Size 9 x 7 x 4 in. approx. The perfect portable and the ideal car radio. (Uses PP7 battery available anywhere)

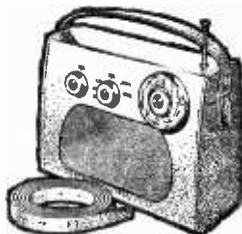Total cost of parts now only **£5.19.6** P. & P 5/6  
Parts Price List and easy build plans 3/-




"... amazed at volume and performance... has really come up to my expectations."  
S. G. Stockton-on-Tees.

### New TRANSONA FIVE

"Home, Light, A.F.N., Lux. all at good volume".  
G. P. Durham.

● 7 stages—5 transistors and 2 diodes

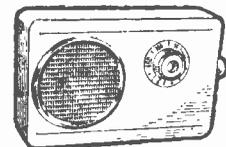Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2 1/2 in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in.



with red speaker grille. (Uses 1289 battery available anywhere.)  
Total cost of all parts now only **42/6** P. & P. 3/6. Parts Price List and easy build plans 2/-.

### TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3 in. speaker makes listening a pleasure. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.)



Total cost of all parts now only **59/6** P. & P. 3/6.  
Parts Price List and easy build plans 2/-.



### SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful

reception. Special circuit incorporating 2 R.F. Stages, push-pull output. 3 in. speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses 9v battery, available anywhere.)  
Total cost of all parts now only **£3.19.6** P. & P. 3/6. Parts Price List and easy build plans 2/-.

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated. Overseas post 10/-.

### MELODY SIX




Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx. with tilt speaker grille and supplied with hand and shoulder straps.

Parts Price List and Total cost of all easy build plans 2/- parts now only **£3.9.6** P. & P. 3/-.
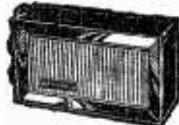
### POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3/4 in. (Uses 1289 battery available anywhere.)



Parts Price List and easy build plans 1/6.  
Total cost of all parts now only **42/6** P. & P. 3/-.

### ROAMER SIX NEW!!

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !!

● 8 stages—6 transistors and 2 diodes



Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long Waves, Trawler Band and 3 Short Waves. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. Top grade transistors, 3-inch speaker, handsome case with tilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. Carrying strap 2/8 extra.

★ EXTRA BAND FOR EASIER TUNING OF LUX, ETC.  
Parts Price List and Total cost of all easy build plans 2/- parts now only **£3.19.6** P. & P. 3/6.

## RADIO EXCHANGE CO.

61, HIGH STREET, BEDFORD. Phone: 2367

Callers side entrance  
Barratts Shoe Shop  
Open 9—5 p.m.  
Sots. 10—12.30 p.m.

# NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO, TV, AND ELECTRONICS

Anyone can afford these amazing courses—anyone can understand this practical training—No complicated mathematics to hold you back—No old fashioned, obscure explanations to frustrate you!

The lessons are **CRYSTAL CLEAR, PRACTICAL EASY TO MASTER AND USE**—Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert! Companies favourably with some courses costing very much more! By creating a mass market through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you!

Each course is printed on extra large quarto size sheets and bound into one manual to simplify handling and distribution.

Please select the course most suitable for your requirements from the following:

**No. 1. RADIO COURSE.** Fundamental facts—Electrons—Conductors and Insulators—Radio Batteries—Circuits—Magnetics—Ohm's Law—Resistor Colour Code—Chart—What resistor to use—Electro-Magnetism—Electro-magnetic Induction—Self Induction—Radio Frequency Inductances—Capacity Coupling—I.F. Transformers—Radio Coils—Radio Capacitors—The Farad—Dielectric—Capacitor Colour Code—Alternating Current Theory & Filters—Resistance and Resistance Charts to calculate Capacity—Frequency and Inductance—Handy Radio Formulae—Practical Aspects of Radio Servicing—Radio Valves—Transistor Theory—N Type Germanium—P Type Germanium—Diode Action—Transistor Action—D.C. Stabilization—Transistor Bias Adjustment—R.F. Amplification—Superheterodyne Principles—A.C.V. Power Supply—Meters—Valve Testers—Point to Point Servicing—Signal Generators and Signal Tracers—Using an Oscilloscope for Servicing—Alignment—Amplifiers and P.A. Equipment—High Fidelity—Advantages of Inverse Feedback—Speakers—Frequency Modulation—How to Obtain Radio Jobs. Price for the complete course. **ONLY 38/-**. Plus postage 1/6.

**No. 2. ELECTRONICS COURSE.** Includes most of the above lessons plus L.C. and B. Combined Circuits and Valve Testers—Behaviour at Resonance—How Meters Work—Making a Voltmeter—Ohm meter Connections—Valves—Electron Behaviour—Triode—Characteristic Curves—Power Supplies—Audio Amplifiers—Microphones—Resistance Coupling—Obtaining Grid Bias—Push, Pull and Parallel—Phase Inverter Circuit—Radio Frequency Voltage Amplifiers—I.F. and Multiband Coils—Detection—Receiver Circuits—Results of Frequency Modulation—A.V.C.—Electronic Oscillators—Quartz Crystals—Radio Transmitter Circuits—Modulation and Tuning—Lines, Antennas and Radiation—Test Equipment Using Meters—Electronic Test Equipment—Thyristors—Photo-cell Equipment—Radio Compass—H.F. Heating—Electronic Shaping Circuits—Electron Microscope—Electric Strain Gauge—Inter-Communicators—Radio Servicing Techniques—Servicing Printed Circuits. Price for the complete course. **ONLY 39/6**. Plus postage 1/6. Graduates of the Electronics Course can qualify for a certificate—details sent with each order.

**No. 3. TELEVISION COURSE.** Effect of Mis-adjusted controls—Pictures of various faults—Service adjustments—Circuit Faults indicated by a Poor Picture—Finding Bias Valves by observing Picture—Separate Channel I.F. System—Inter-carrier I.F. System—Negative Picture—Interference—Antenna Principles and Practices—U.H.F. Transmission Lines—Facts About the T.V. Signal to Help you in Service Work—Synchronizing Separators—T.V. Interference Aids—All about Cathode Ray Tubes—Explanation of T.V. Circuits—Video Detector—Video Amplifier—D.C. Restorer Circuit—Automatic Gain Control Circuits—Oscillators—Deflection Coils—Automatic Frequency Control Circuits—Analysis of Stagger Tuned I.F. Receiver—Analysis of Three Inter-carrier Type Receivers—The Vertical Deflection Circuit—The Horizontal Deflection Circuit—Waveforms—Schematics of various sections of a T.V.—U.H.F. Converters and Tuners—T.V. Test Equipment and Alignment—Analysis of Various Problems. Price for the complete course. **ONLY 36/-**. Plus postage 1/6.

**UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION** You must be convinced that this is the best value you have ever seen in Electronic, Radio or T.V. Training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a full seven days.

**IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE 70-PAGE BOOK.** Tick on the coupon one book for each course ordered with full cash. **RADIO SERVICING FAULT FINDING BOOK.** **TELEVISION FAULT BOOK.** **OSCILLOSCOPE BOOK.**

These free books are authoritative, and loaded with information. Would cost at least 50p. each if bought separately—by sending cash you reduce book-keeping and other costs, which savings we pass back to you.

**FREE TRIAL OFFER**  
Pay only 5/- per week if you wish. Trip coupon right now for this special offer. To: Sim-Teck Book Company, Dept. CW10, Gater's Mill, West End, Southampton, Hants.

Please send the following courses for a full seven days' trial.  
 No. 1. RADIO COURSE.  No. 2. ELECTRONICS COURSE.  
37/6, incl. postage. 41/-, incl. postage.  
 No. 3. TELEVISION COURSE.  
37/6, incl. postage.  
(Free trial customers tick only one please).

If not delighted, I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price OR 5/- weekly until purchase price plus 2/6 service charge has been paid.

Tick here if enclosing full purchase price.  
Please send me  FREE. RADIO FAULT FINDING BOOK.  
 FREE. T.V. FAULT FINDING BOOK.  FREE. OSCILLOSCOPE BOOK.  
Amount enclosed £.....

I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers send full amount (including Ireland).

NAME.....  
ADDRESS.....  
City..... County.....

# RETURN-OF-POST ON CASH OR C.O.D. ORDERS

● **SPECIAL OFFER !! STEREO CARTRIDGES**  
ICONETTE 105 Stereo/Mono Cartridge. Complete with fixing bracket and stylus. List 59/4. OUR PRICE 23/6 Post free.

● **ILLUSTRATED LISTS**  
Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● **AMPLIFIER KITS**  
We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer. Fully detailed list on any of these sent upon request.  
Instruction Manual; All Mullard Audio Circuits in "Circuits for Audio Amplifiers" 9/5 Post Free.

● **LATEST TEST METERS**

	Cash Price	Deposit	Credit Terms
			Mthly/Pmts.
AVO Model 8 Mark III ..	£24. 0.0	£4.16.0	12 of £1.15.2
AVO Model 7 Mark III ..	£22. 5.0	£4. 8.0	12 of £1.12.9
AVO Multimeter Mark 4 ..	£9.10.0	£1.18.0	12 of £1.4.4
T.M.K. TP10 ..	£4. 7.6	£1. 7.6	3 of £1. 3.4
T.M.K. TP58 ..	£6.11.6	£1.11.6	6 of 19/2
T.M.K. Model 500 ..	£9.17.6	£1.17.6	12 of 15/-
FAYLOR MODEL 127A ..	£10.10.0	£2. 2.0	12 of 15/8

Full details of any of the above supplied free on request.

● **MARTIN AUDIO KITS**  
High quality, easy to assemble Hi-Fi Units. Fully transistorised for mono and stereo working. All units are assembled and tested and the constructor has only to link together units chosen for any particular installation. The following mono units available.  
Unit 1 Input selector 47/6  
Unit 2 Pre-amplifier with volume control 37/6  
Unit 3 Mixer Unit 79/6  
Unit 4 Pre-amplifier with tone and volume controls 62/6  
Unit 5 Main Amplifier 10 watt, 3 ohm output **£5.12.6**  
Unit 7 Main Amplifier 10 watt, 15 ohm output **£6.12.6**  
Unit 6 Power unit for unit 5 52/6  
Unit 8 Power Unit for unit 7 55/-  
Unit 9 A special pre-amplifier for low output Pick-ups 55/-  
Units 1, 2, 3 and 4 are available for stereo working at twice the prices shown. Smart plastic escutcheons are available for all combinations of units. Full details in the Martin Illustrated Leaflet, available free. Credit Terms available on any combination of units.

● **GRAMOPHONE EQUIPMENT**  
ALL LATEST MODELS  
ALL POST FREE

	Cash Price	Deposit	Credit Terms
			Mthly/Pmts.
<b>RECORD CHANGERS</b>			
GARRARD AUTOSLIM (Mono PU fixed head) ..	£6.10.0	£1. 5.0	6 of £1
GARRARD AUTOSLIM Duo-Luxe AT6 (Mono PU) ..	£11. 9.0	£2. 6.0	12 of 16/11
GARRARD AUTOSLIM AT6 (Stereo/Mono PU) ..	£12. 5.4	£2. 8.4	12 of 18/-
GARRARD LAB AUTO A (GC8 Mono PU) ..	£16.12.6	£3. 6.8	12 of £1.4.5
GARRARD AT5 LM (3000 LM) Low mass pick-up arm (9TA Stereo/Mono PU) ..	£12.15.0	£2.15.0	12 of 18/4
GARRARD AT5 (Mono PU plug in head) ..	£10. 8.2	£2. 4.2	12 of 15/4
B.S.R. UA15 (TC8 Mono PU) ..	£6.19.6	£1.14.6	6 of £1
B.S.R. UA15 (TC8 Stereo/LP78) ..	£7.19.6	£1.19.6	6 of £1.2.6

See our Gramophone List for details of Single Record Players and Transcription Units.

● **HI-FI LOUDSPEAKERS**  
GOODMANS: Axiette 8in., £5.5.7; Axloom 10in., £6.5.11; 12in. Axloom 201, £10.17.4; 12in. Axloom 301, £15.4.8; 12in. Axloom 51 Bass, £9.2.8; 12in. Axloom 61 Bass, £14.7.8; Trebax Tweeter, £6.10.2; CX5000 Crossover unit, £2.0.11.  
W.H. HEALEY: Hi-Fi 10in., £7.7.0; Hi-Fi 12in., £4.12.0; HF816 8in., £6.6.0; TS16 8in., £5.19.6; T10 Tweeter, £4.12.0; T359 Tweeter, £1.12.3; CX3000 Crossover Unit, £1.13.3; CX1500 Crossover Unit, £2.2.0. Credit Terms available on all speakers.

● **STEREO COMPONENTS**  
Morzante ranged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log, 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 250k, 1 meg., 2 meg. ★ Lin/Lin 250k, 1 meg., 2 meg. All 10/6 each. Postage extra.

● **JASON F.M. TUNERS**  
We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:  
FMT3 (less power), £8.5.0; FMT2 (with power), £10.2.6.  
FMT3 (less power), £9.19.6; FMT3 (with power), £11.17.6.  
FMT1, £6.12.6.  
Credit Terms available. Ask for list.

● **MAINS & OUTPUT TRANSFORMERS**  
GILSON AND PARNIEKO TYPES for many popular circuits stocked. Send for list.

**WATTS RADIO (Mail Order) LTD**  
54 CHURCH STREET, WEYBRIDGE, SURREY  
Telephone Weybridge 47556  
Please note: Postal business only from this address  
Callers welcome by appointment

in the above calculation would normally be operated with anode voltages of 20—50V and anode currents of 3—13mA.

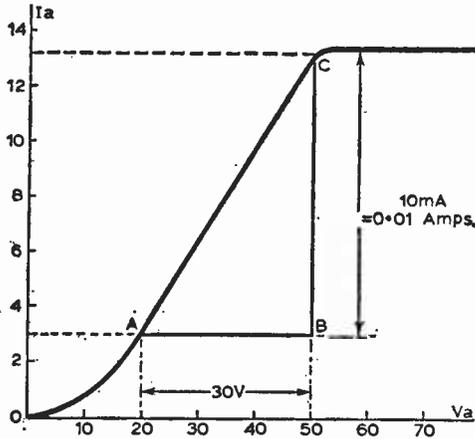


Fig. 45: Determination of the a.c. resistance of the diode.

We already know that a diode will allow a current to pass through it only when a positive voltage is applied to the anode, therefore if an alternating voltage were applied to the anode of a diode a current would only flow on the POSITIVE HALF-CYCLE. The current flowing in the circuit would therefore be no longer a.c. as it would now not have a negative component.

The current could be said to be an UNSMOOTHED DIRECT CURRENT. The diode has then changed the a.c. shown in Fig. 46 into the type of d.c. shown in Fig. 47, i.e. the diode has acted as a RECTIFIER.

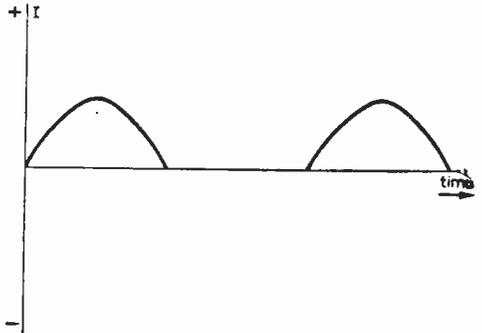


Fig. 47: Current flowing in the anode circuit of a simple diode rectifier.

**5.5 The Diode as a Rectifier**

From the section which dealt with a.c. theory it will be remembered that an alternating current could be represented graphically in the form shown in Fig. 48; this would also, of course, be the same shape as a graph of an alternating voltage (both graphs being drawn with respect to time, of course). However, it can be seen that the current (or voltage) starts at zero, reaches a maximum positive value, returns to zero, reaches a maximum negative value and returns to zero once more. This is a complete CYCLE for an alternating current or voltage.

In the diagram shown in Fig. 48 it will be seen that the alternating current has been supplied by a TRANSFORMER and that the D.C. OUTPUT of the rectifier has been connected to a LOAD which has been represented by "R".

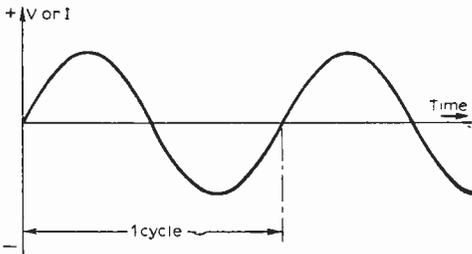


Fig. 46: Typical a.c. waveform.

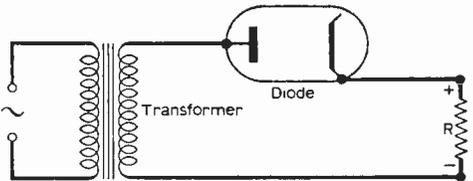


Fig. 48: Typical circuit using a diode as a simple rectifier.

**5-6. Smoothing the Output from a Simple Diode Rectifier**

Where a steady current of the d.c. type is required it is obvious that a current of the type shown in Fig. 47 will be unsuitable. This current has then to be SMOOTHED. We know that a CAPACITANCE is an electrical device which can be used to "store" a current. If we were to connect a large capacitor across the load R in Fig. 48 what would be the effect? Well, between A and B the capacitor would be charging and between B and C

The mains supply in most areas is an alternating supply and if d.c. is required for any particular purpose then this a.c. has to be changed to d.c. or, to use the correct term, it has to be rectified.

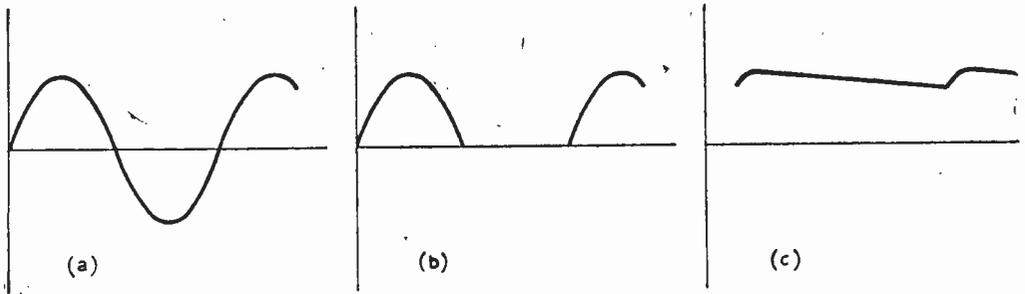


Fig. 49: The a.c. waveform: (a) before rectification; (b) after rectification and (c) with smoothing capacitor.

the capacitor would be discharging. Thus the capacitor would be a current to the circuit where previously no current had been flowing. The capacitor would in fact be acting as a RESERVOIR for the current and is in fact called a RESERVOIR CAPACITOR. The larger the value of the capacitor the greater the smoothing effect. The three stages mentioned in the rectification of a.c. by a simple diode circuit are shown in Fig. 49. (It is often said that a SMOOTHING CAPACITOR "absorbs the peaks and fills in the troughs" of the type of waveform shown in Fig. 47.)

The type of rectifier which only rectifies one half of the a.c. cycle, i.e. a single diode, is called a HALF-WAVE RECTIFIER.

Answer to last month's question

$$\begin{aligned}
 f &= \frac{10^6}{2\pi\sqrt{LC}} \\
 &= \frac{10^6}{6.28\sqrt{10 \times 100}} \\
 &= \frac{10^6}{198.6} \\
 &= 5,035\text{kc/s or } 5.035\text{Mc/s.}
 \end{aligned}$$

Question

Attempt to answer the following questions which relate to the graph given in Fig. 50.

1. Mark with an "X" the point where saturation occurs.
2. Between what values of  $V_a$  and  $I_a$  would the valve be normally operated?
3. Using the graph, calculate the a.c. resistance of the valve.
4. In practice would you expect the graph to pass through the points  $V_a=0, I_a=0$ ?

New frequency is 2,517kc/s.

$$\begin{aligned}
 \therefore 2517 &= \frac{10^6}{6.28\sqrt{10 \times C}} \\
 \sqrt{10C} &= \frac{10^6}{6.28 \times 2517} \\
 &= \frac{10^6}{15810} \\
 \therefore \sqrt{10C} &= 63.25 \\
 \therefore \sqrt{10C} &= 63.25^2 \\
 &= 4000 \\
 C &= \frac{4000}{10} \\
 &= 400\text{pF.}
 \end{aligned}$$

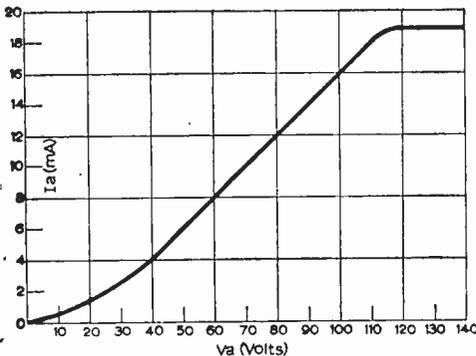


Fig. 50: The graph relating to this month's problems.

Part 6 Next Month

SEE ALSO PAGE 1094 THIS MONTH

### THE KEENNED TAPE RECORDER BARGAIN OF THE YEAR!



A 24 gns. Tape Recorder offered at the bargain price of only 15 Gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A Modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.T. Twin Track Monorack Type TP2. Valve line up—EF86, ECL85, EM84, 1Z80 and Selenium Diode. Send for detailed list—3d. stamp.

**Complete Kit** complaints items below.  
**BARGAIN PRICE 15 Gns.** +10/- Carr.

2-tone Cabinet and 3in. x 5in. Speaker. Size 14in. x 10 1/2in. x 7 1/2in.	£3.10	+ 5/- Carr.
Wired Amplifier complete with 4 Valves, front Panel, Knobs, etc.	£5.10	+ 3/6 Carr.
B.S.R. Monorack Type TD2	£7.70	+ 4/6 Carr.
Accessories: Mike, Tape, empty Reel, screened Lead and Plugs, Instructions, etc.	£1.00	+ 2/- Carr.

### RECORDING TAPE

Famous American Columbia (CBS) Premier quality tape at **NEW REDUCED PRICES.** A genuine recommended Quality Tape—TRY IT BRAND new, boxed and fully guaranteed. Fitted with leader and stop folds.

Standard	Double Play	Long Play	
5" 600 13/1-	1200 3/18	000 1/76	
5 1/2" 900 18/-	1800 3/78	1200 1/96	
7 1/2" 200 21/-	2400 4/76	1800 2/86	

Post & Package per reel, 1/- plus 6d. each for additional reels.

**SPECIAL OFFER.** 3" Message tape 150', 3/8; 3" L.P. 225', 4/8; 3" L.P. 300', 6/6. P. & P. per reel 6d.

**TAPE REELS.** Mufrs. surplus 7". 2/3; 5". 2/-; 3". 2/-; 3". 1/3; Plastic spool containers, 5". 1/8; 7". 2/-; 7". 2/3.

**Condensers—Silver Mica.** All values 2pF to 1,000pF, 6d. each. Ditto, Ceramics 9d. Tub. 450V T.C.C. etc. 0.001 mF to 0.01 and 0.1/250V... 9d. 0.02-0.1/500V... 1/-, 0.25 years 1/8, 0.3 T.C.C. 1/9, etc. Glass, Tol. S/Micas—10% 5pF-500pF 8d. 600-5,000pF, 1/-, 1% 2pF-100pF, 9d. 100pF-500pF, 11d. 575pF, 5,000pF, 1/6. Resistors—Full Range 10 ohms-10 meg. ohms 20p, 1 and 1/4W, 3d. 1/4W, 5d. (Midstap type modern rating) 1W, 6d., 2W, 9d. Hi-Stab. 5% 1/4W, 1/4W 6d., 100 ohms-1 meg. Other values 9d. 1% 1/4W, 1/8, etc., etc.

**JASON FM TUNER UNITS**  
Designer-approved kits of parts.  
FM1, 5 gns. 4 valves, 20/-;  
FM2, 7 gns. 5 valves, 35/-, JTV  
MERCURY 10 gns. 5 valves 28/6,  
JTV2 £13.10. 4 valves, 28/6,  
NEW JASON FM HANDBOOK, 2/6,  
48 hr. Alignment Service 7/6.  
P. & P. 2/6.

**TRIMMERS.** Ceramic (Compression Type)—30pF, 50pF, 70pF, 9d.; 100pF, 150pF 1/3; 250pF, 1/6; 600pF, 1/8, PHILIPS. See Hints Type (conc. air-spaced)—2-2pF, 1/-; 3-30pF, 1/4-  
**KNOBES**—Modern Continental types Brown or Ivory with Gold Ring: 1" dia., 9d. each; 1 1/4", 1/- each; Brown or Ivory with Gold Centre, 1" dia., 10d. each; 1 1/4", 1/3 each.  
**LARGE SELECTION AVAILABLE.**  
**METAL RECTIFIERS, STC Types**—RM1, 4/8; RM2, 5/8; RM3, 7/8; RM4, 16/-; RM5, 21/-; RM4B, 17/6.

**TUB-ELECTROLYTICS-CAN**  
25/25v. 50/15v. 1/8; 8+8/450v. 4/6;  
50/50v. 100/125v. 2/- 32+32/275v. 4/6  
8/450v. 4/350v. 2/3; 50/50/350v. 6/8  
16+16/450v. 5/8; 60/250/275v. 12/6  
32+32/450v. 8/6; 100+200/275v. 12/6

**Volume Controls**—5K-2 Meg. ohms, 3in. Spindles. Morganite Midget Type 1/4in. diam. Guar. 1 year. LOG or L.I.N. ratios less SW. 3/-. DP. SW. 4/8. Twin Steer less SW. 4/6. DP. SW. 3/-. Specials to order.

**WAVECHANGE SWITCHES.** 1 p. 12-way 2 p. 2-way, 2 p. 6-way, 3 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle. 3/6 ea.

### RECORD PLAYER CABINETS 59/6

Carr. & Ins. 5/-. Contemporary style, rexine covered cabinet in two-tone maroon and cream. Size 15 1/2" x 14 1/2" x 8 1/2", fitted with all accessories including baffle board and Vynair fret Space available for all modern amplifiers and auto-changers etc. Uncut record player mounting board 14 1/2" x 12 1/2" supplied.



**2 VALVE 2 WATT AMPLIFIER**  
E2329 and Twin ECL85 with vol. and neg. feedback tone control. A.C. 200/250v with knobs, etc. ready wired to fit above cabinet. £27.16. P. & P. 1/6. 7" x 4" Speaker and trans. 22/-, P. & P. 2/-.  
**COMPLETE R/PLAYER KIT.** As ill. inc. BSR UA14 Unit. New Barkrain Price. Now only £11.10. 7/6 carr. Double wound mains Tr. no live chassis.


**BONDACOUST Speaker Cabinet** Acoustic Wadding (lin. thick approx.) 12in. wide, any length cut, 1/8 1/4, 4/- yd. TINNED COPPER WIRE, 16-23g. 2/6 1/2 lb. ERSIN MULTICOE SOLDER. 60/40 4d. per yard. Cartons 2/6 etc.

**TYGEN PRET**(Contem. pat.), 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/-, etc. etc.  
**EXPANDED ANODISED METAL.** Attractive gilt finish 1/4in. x 1/4in. diamond mesh 4/8 sq. ft. Multiples of 6in. cut. Max. size 4ft. x 3ft. 47/6 plus carr. Don. finer patterned mesh, 4/8 sq. ft., multiples of 12in., max. size 3 ft. x 2 ft., 27/6 sheet.

**ENAMELLED COPPER WIRE**—1lb. reels 14g-20g, 2/6; 22g-28g, 3/-; 30g-34g, 3/8; 36g-38g, 4/3; 39g-40g, 4/6, etc.



Inst. 1949

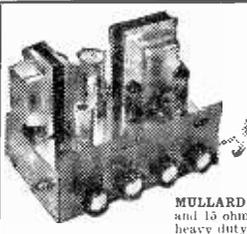

### MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

3 ohm & 15 ohm output  
"3-3" Amp. 3 valve, 3 watt hi-fi quality at reasonable cost. Bass Boost and treble controls, quality sectional output transformer, 40 cf-25 kc/s + 14H. 100mV for 3W, less than 1% distortion. Bronze escutcheon panel. Complete Kit only £8.19.6. Carr. 5/- Wired and tested 8 gns.

**MULLARD "5-10" AMPLIFIER.** 5 valves 10W 3 and 15 ohm output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer Carr. and Ins. 7/6.  
**£9.19.6**

Basic amplifier kit price Ready built 11/- gns.  
**CONTROL PANEL KIT.** Bass, Treble and Volume controls with 4-position selector switch for radio tape and 11in. x 4in. escutcheon panel.  
**AMPLIFIER KIT AND CONTROL PANEL KIT.** £11.19.6. Ditto, ready wired. £14.19.6.

**2-VALVE PRE-AMP. UNIT.** Based on Mullard's famous 2-valve (2xEF86) circuit with full equalisation, with volume, bass, treble and 5-position selector switch. Size 9 1/2 x 2 1/2 in. complete Kit £5.19.6, carr. 3/6. Ready Built £7.19.6.

### 6 VALVE AM-FM TUNER UNIT

Med. and VHF 190 M-550 M, 85Mc/s-103Mc/s 6 valves and metal rectifier. Self contained power unit. AC 200-250v. operation. Magic eye indicator, 3 push-button controls, on/off, Med., VHF diode and high output sockets with gain control. Illuminated 2-col. perspex dial 1 1/2 x 4in. Chassis 1 1/2 x 3 x 5 1/2 in. A recommended Fidelity Unit for use with Mullard 2/3 5-10 amplifiers. Available only at present as built-up units, aligned and tested ready for use. Bargain price £12.10.0 Carr. 5/-. We hope to produce this popular unit in kit form very shortly.

### DE-LUXE RECORD PLAYER KIT



Incorporating 4 Sp. Garrard Auto-8lim unit and Mullard latest 3 watt printed circuit amplifier (ECL 85 and 1Z 80), vol., bass and treble controls, with 5" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue relief. Size 17 1/2" x 16" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit)  
**COMPLETE KIT £13.19.6**  
Carr. and ins. 10/-


Illuminated perspex control panel escutcheon, 7/6 extra. Ready wired 30/- extra. Four contemporary mounting lugs (6 or 13in.) 12/6 per set.

### TRANSISTOR COMPONENTS

Midget I.P.F.—465 Kc/s 9/16in. diam. .... 5/3  
Osc. coil M. & L.W. .... 5/9  
Midget Driver Trans. 3.5:1 .... 6/9  
Midget Output Trans. Push-Pull—3 ohms .... 8/9  
Elect. Condensers—Midget Type 1 mFd.-50 mFd. ea. 1/8, 100 mFd. 2/-, 12V.  
Condensers 150 v. working: .01 mFd., .02 mFd., .03 mFd., .04 mFd., .05 mFd., .1 mFd., 1/- .25 mFd., 1/3; 5 mFd., 1/6, etc.  
Midget Tuning Condensers, J.B. "00" 205 pF and 33 pF, 8/6, ditto with trimmers, 9/6. J.B. "20 pF and 105 pF conc. slow motion 10/6. 365pF single 7/8. Sub. min. 2in. Minitem 100 pF, 200pF, 500pF, 7/- each.  
**FERRITE AERIALS, M. & L.W.** car aerial coil 9/3.  
Midget Vol. Control with edge control knob, 5 K/ohms, with switch 4/9; Ditto less switch 3/9.  
Speakers: P.M.: 2in. Plessey 75 ohms 15/6. 2 1/2in. Continental 8 ohms, 13/6. 7 x 4in. Plessey 35 ohms 23/6.  
Ea. 2 Plus Phones—Min. Continental type 3ft. lead, jack plug and socket. High Imp., 8/-, Low Imp., 7/6.  
Brand New. Mfrs. 1st grade, 1 OC34 & 2 OC45, 15/6. 1 OC81D & 2 OC81, 15/6. All above and 0A81, 32/6. Post Free.
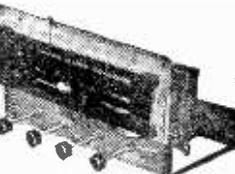
### 7 VALVE AM/FM RADIOGRAM CHASSIS


Valve line-up EOC85, ECH81, EF89, EAC80, EL54, EM81, E230.  
Three Waveband and Switched Gram. positions. Med. 200-550 m. Long 1,000-2,000 m. VHF/FM 88-95 Mc/s. Philips Continental Tuning insert with permeability tuning on FM and combined AM/FM IF transformers. 400 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 x 6 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 x 3 1/2 in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Circuit diagram n/w available. Aligned and tested ready for use £13.10.0. Carr. & Ins. 7/6  
Complete with 4 Knobs—valnut or ivory to choice. Indoor FM aerial 3/8 extra. 3 ohm P.M. speaker only required. Recommended Quality Speakers 10in. R.A. 27/6; 13 1/2 x 8in. E.M.L. "Fidelity" 37/8; 12in. R.A. with conc. Tweeter, 42/6, Carr. 2/6.



We manufacture all types Radio Mains Transf., Chokes, Quality O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain list, 3d. stamp
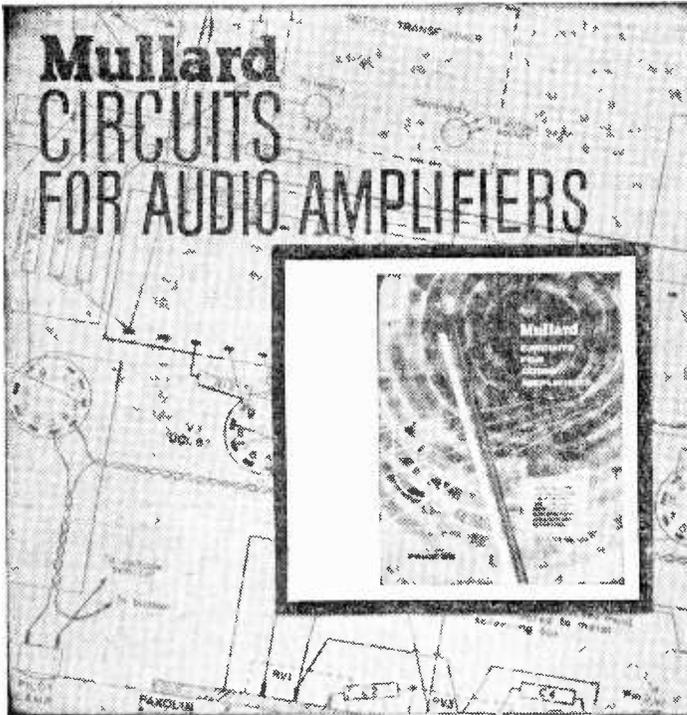
### RADIO COMPONENT SPECIALISTS

70 Bristock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m. Wed. THO 2188. Terms C.V.O. or C.O.D. Post and Packing up to 1 lb. 9d.; 1 lb. 1/8; 3 lb. 2/3; 5 lb. 2/9; 8 lb. 3/6.



## A BOOK EVERY ENTHUSIAST WILL WANT!

This Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction. Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives you just the sort of information you need.


This informative book costs only 86 (U.K. price). The demand for it is high, so get your copy now from your radio dealer, or order direct from Mullard Ltd. (postage and packing 1s. 0d. extra in U.K.).

MULLARD LIMITED · MULLARD HOUSE  
TORRINGTON PLACE · LONDON W.C.1

MVM4005

THE WORD **MAXI-Q** IS THE REGISTERED  
REGD. TRADE MARK  
OF DENCO (CLACTON) LIMITED  
IT IS ALSO A GUARANTEE OF  
WORKMANSHIP AND  
TECHNICAL PERFORMANCE

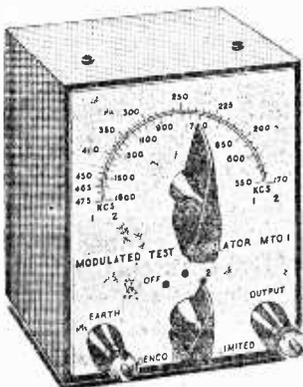OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1s. 6d. FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 1s. 6d. IN STAMPS.



### MODULATED TEST OSCILLATOR MTO.1

- ★ Provides modulated signal suitable I.F. alignment, also trimming and tracking R.F. circuits.
- ★ Frequency is continuously variable from 170-475 kc/s and 550-1,600 kc/s.
- ★ Suitable for the alignment of transistor receivers.
- ★ Operates from a single 9-volt grid-bias battery (not supplied) which is housed within the unit.
- ★ The case is manufactured from steel and is finished in silver hammer. The front panel is gloss black bearing white lettering. Dimensions are  $5\frac{1}{8}$  in. x  $4\frac{1}{16}$  in. x 3 in.
- ★ Supplied with full operating instructions.

**PRICE £3/17/6**

Stop Press 3 Pole 3 Way 3 Bank Switch 7s. 6d. each 1 Pole 8 Way 4s. 3d.

**DENCO (CLACTON) LTD.**

(DEPT. P.W.)

357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

*The Editor does not necessarily agree with the opinions expressed by his correspondents*

### THE PRICE OF GENEROSITY

**SIR.**—I think that you and many readers of *PRACTICAL WIRELESS* and *Practical Television* may be interested in the response to my letter in the October issue of P.W. (page 577) in which I offered free all my past issues of the two magazines.

I had 256 letters requesting copies, and in order to be as fair as possible I selected letters at random; within ten days I had dispatched all my copies to 88 readers by post and the half dozen local ones I delivered personally.

I had (in my simple way), expected about six requests and was staggered, to say the least, by the amount of mail that descended on me. On three days there were as many as 60 letters per day!

The pleasant task of reading so many friendly letters was enjoyable. I am so sorry to have had to disappoint many, many readers, but I could easily have distributed 50 copies of each issue had they been available.

The one unpleasant aspect of my "give-away" scheme was the out-of-pocket expense it caused me, principally by the thoughtlessness of so many people who enclosed crossed P.O.'s, loose cash, stamps, cheques and paper money etc., and in some cases not even a threepenny stamp!

Only twelve readers enclosed an s.a.e.; to them many thanks, they were a great help in what proved to be a gigantic task of replying to everyone.

Incidentally, only ten readers out of nearly 90 to whom I sent copies, bothered to send a word of thanks.

So may I warn any other reader who might be considering the same offer as mine, that my out-of-pocket expenses have been:— 212 threepenny stamps—(£2 13s.), 136 P.O.'s (3d. postage)—(£1 14s.) and 200 envelopes, writing paper, wrappers etc.—(9s. 3d.) totalling £4 16s. 3d. — J. F. HITCHCOCK (Sutton, Surrey).

### UNUSUAL MICROPHONE

**SIR.**—Having built my tape recorder from a kit, I was very dissatisfied with the peaky result from my crystal mike. This led me to thinking that a more expensive one such as a ribbon type may be the answer to my problem but the price of such an instrument stopped my progressive thoughts. It was then that I decided to experiment with a small 2½in. loudspeaker with an 80Ω voice coil, but alas,

my junk box did not reveal a matching output transformer. All that could be found was an old 230V in 230 + 6.3V out mains transformer removed from an old TV converter. Nevertheless, it was all that was available and I subsequently connected my speaker (now to be called microphone) to the 6.3V winding, feeding the 230V winding to my tape recorder input.

The result was most surprising, a very fair all-round response and my "tapespondent" friend feels certain that I am using an expensive ribbon-type mike!

Should any other readers be interested in similar experiments they may care to bear in mind the fact that the actual cone diameter of the speaker should be no less than 2½in., as this would probably result in loss of bass response.—JOHN B. COX (Brighton).

### CORRESPONDENTS WANTED

**SIR.**—I am interested in transistor circuitry and radio in general. I would like to correspond with anyone who is interested in radio and who is about my own age (16). — DONALD GABRIEL (43 Oliver Plunkett Street, Blandon, Co. Cork, Ireland).

### ON THE SHORT WAVES

—continued from page 1078

America, and you never know he may spray a little r.f. in your direction (listen at the high end of 20m band).

Part One of the 1965 ARRL DX contests are scheduled for February and could provide something interesting. There are two sections: 'phone a.m. and s.s.b. and c.w. In February there is one section of each with another in March. The full list of contest dates this month is as follows:—

6th—7th QCWA Party.

13th—14th ARRL DX Contest, 'Phone section.

14th 70 Mc/s Contest.

20th—21st BERU Contest.

20th—21st YL/OM 'Phone Contest.

27th—28th ARRL DX Contest, c.w. section.

27th—28th REF Contest, 'Phone section.

The ARRL contest by the way, starts at 0001 G.M.T. Saturdays and ends 2400 Sundays.

My thanks to listeners who sent in logs. We are hoping to provide report forms to make it easier to send in a log. If you would like to send in a regular report drop me a line with your address (printed please) and I'll forward them if and when they become available.



**ACTON, BRENTFORD AND CHISWICK RADIO CLUB**  
Hon. Sec.: W. G. Dyer, G3GEH, 188 Gunnersbury Avenue, Acton, London, W.3.

At the meeting to be held on 16th February at 8 p.m. at 66 High Road, Chiswick, the Club will be having a show of mixed films, to which all those interested in amateur radio are invited.

**CHESTER AND DISTRICT AMATEUR RADIO SOCIETY**  
Hon. Sec.: P. J. Holland, Field House, 19 Kingsley Road, Great Boughton, Chester.

The only function arranged for January by the outgoing committee was the A.G.M. held in the Y.M.C.A. hall, Chester  
**CLIFTON AMATEUR RADIO SOCIETY**  
Hon. Sec.: J. Rose, G3OGE, 63 Broomfield Road, Beckenham, Kent.

Winner of the 1964 Constructional Contest was SWL Dave Reed, with a 430 Mc/s. transistor converter.

**COVENTRY AMATEUR RADIO SOCIETY**  
Hon. Sec.: E. E. Snow G3TKO, 11 Lupton Avenue, Coventry.

On 11th January there was an evening of construction on the Club top band transmitter, and on the 18th there was a Frequency Measurement symposium. On 25th January there was a lecture aimed at SWLs, entitled H.F. Bands Converter.

**DERBY AND DISTRICT AMATEUR RADIO SOCIETY**  
Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

The R.S.G.B. Affiliated Societies' Contest was held on 23rd and 24th January, and on 3rd February the Annual General Meeting took place.

**DURHAM CITY AMATEUR RADIO SOCIETY**  
Hon. Sec.: M. Allenson, G3TGD, Physics Department, University of Durham, South Road, Durham.

The Society is now one year old and can look back on a prosperous year with average attendances of thirty or more members. Meetings are held every alternate Thursday at 7 p.m. at the Bridge Hotel, North Road, Durham.

**FAREHAM AMATEUR RADIO CLUB**  
Hon. Sec.: C. A. Gledhill, G3LGX, 113 Oak Road, Fareham, Hampshire.

Meetings of this club take place fortnightly at 39 Nicholas Crescent, Fareham, and full details can be obtained by writing or telephoning the Hon. Secretary at the above address.

**HALIFAX AND DISTRICT AMATEUR RADIO SOCIETY**  
Hon. Sec.: J. Ingram, G3RMQ, Lambert House, Greetland, Halifax, Yorkshire.

The speaker on 26th January was J. J. Platt, G2VO, whose topic was "Radio a long time Ago". On the 30th and the 31st January, there was the CQ Worldwide 160 meter Contest.

**MID-WARWICKSHIRE AMATEUR RADIO SOCIETY**  
Hon. Sec.: T. Inkester, 13 Dormer Place, Leamington Spa Warwickshire.

The New Year activities commenced on Monday, 11th January with an Open Meeting. The meeting on 25th January was devoted to a film show, and will be followed on 8th February by the Annual General Meeting.

**NORTHERN HEIGHTS AMATEUR RADIO SOCIETY**  
Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax, Yorkshire.

With the permission of Staw WIBB, a copy of his tape-recorded talk entitled "Top Band DXing", along with slides has been made and any club wishing to borrow it may do so, provided that the club concerned agrees to registered postage both ways. Application should be made to G3MDW.

**READING AMATEUR RADIO SOCIETY**  
Hon. Sec.: R. G. Nash, G3EJA, 'Peacehaven', 9 Holybrook Road, Reading, Berkshire.

The Annual General Meeting was held on 30th January at the Palmer Hall, West Street, Reading, and new officers were appointed to take over from those retiring this year.

**SLADE RADIO SOCIETY**  
Hon. Sec.: D. T. Wilson, 177 Dower Road, Four Oaks, Sutton Coldfield, Warwickshire.

On 8th January there was a General Discussion on d.f. arrangements for 1965 with special reference to Harcourt, rules and technical organisation. A talk entitled "The Early Days" was given by H. Wilson, on 22nd January.

**SPEN VALLEY AMATEUR RADIO SOCIETY**  
Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Near Leeds.

The subject under discussion on 21st January was, "Aerials for

Radio Astronomy". On 4th February, there was an evening for Model Control enthusiasts.

**UNIVERSITY OF SHEFFIELD AMATEUR RADIO SOCIETY**  
Hon. Sec.: J. P. Billingham, G8AAC, 2 St. Andrew's Way, Ardsley, Barnsley, Yorkshire.

On 8th December, Messrs. G. Harris and M. Taylor of Whitley Electrical Radio Co. Ltd., gave a demonstration of High Quality Sound Reproduction. Seven of the Club's members sat the R.A.E. at the University on 10th December.

**WELLINGBOROUGH RADIO CLUB**  
Hon. Sec.: J. Baker, 34 Essex Road, Rushden, Northamptonshire.


At the meeting held on 14th January, P. Elderkin gave a talk on Home Made Gadgets. On 21st January there was a junk sale and on the 28th G. Abrams gave a talk on Transistors. The General Meeting was held on 4th February.

**WEST KENT AMATEUR RADIO SOCIETY**  
Hon. Sec.: H. F. Richards, 17 Reynolds Lane, Tunbridge Wells, Kent.

On 8th January there was a Gossip Group in which the AFS Contest arrangements came under discussion. At the meeting on the 22nd G6SSE/T and friends gave a lecture and demonstration on Colour Television.
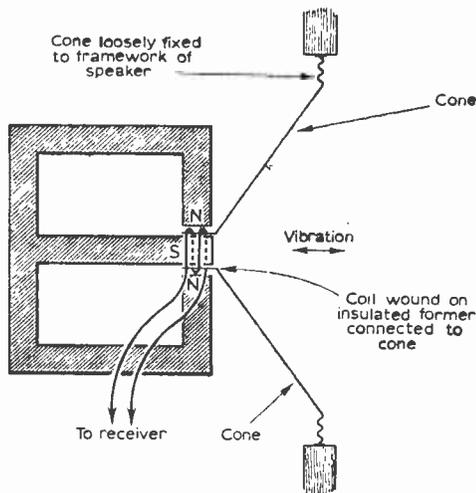
## Preparing for the R.A.E.

The loudspeaker diagram of Fig. 12 (page 740, December '64 issue) was considered, by some readers, over-simplified and ambiguous. Below we reproduce a more explanatory diagram.



Also in this issue, the meter coil of Fig. 14 was shown in the mid-deflection position, and therefore the pointer also should have been set mid-way on a linear scale. Fig. 17 should have shown the two coils wound in opposite directions, so as to produce one North and one South pole uppermost, for maximum attraction.

# WIRECOMP ELECTRONICS BARGAINS FOR THE RADIO ENTHUSIAST

## NEW COMMUNICATION RECEIVERS MODEL HE30



Covers range from 540 Kc/s to 30 Mc/s. Ham Band is provided with a scale for direct reading, and can also be band spread. Facilities: A.N.L., A.V.C. and M.V.C. Q Multiplier also serves as B.F.O. H.F. stage and two

I.F. stages ensure high sensitivity and selectivity. Valve line up: 3x6BA6, 2x6BE6, 2x6AV6, 1x6X5 and 5Y3. 2 Aerial Sockets. Standby position for use with a transmitter. 3 meter fitted. 200-250v. A.C. mains. Brand new and unused. Boxed with full instruction manual, in attractive steel cabinet, grey crackle finish. Cabinet size 15x8x10in. Dial 12x4in.

**WIRECOMP'S PRICE 33 GNS.** Carr. and Pack free

Available in KIT Form, 25 GNS. Carr. and Pack free. H.P. Terms (Ready Built): £6.13.0 deposit and 11 monthly payments of £2.16.0.

**MODEL HE40** Covers medium wave band and 1.6-4.4 Mc/s., 4.5-11.0 Mc/s. 11.0-30.0 Mc/s. In separate switched band spread ranges. Controls include B.F.O. Sensitivity, A.N.L. Receiver—Stand-by-Switch, Tone Switch, S-Meter. For 200/250v. A.C./D.C. Internal loop and telescopic antennae fitted. Valve line-up: 12BE6, 12BA6, 12A6, 6X5, 6C5 and metal rectifier. Size 13 1/2 x 8 1/2 x 5 1/2 in. Instruction manual included. No Kits available.

**WIRECOMP'S PRICE 19 GNS.** Carr. and Pack 10/- H.P. Terms £4. dep. and 11 months at £1.12.0.

**MODEL HE 80** 14-valve super sensitive communication receiver. Freq. range 540 Kc/s-30 Mc/s. and 144-146 Mc/s. Dual conversion on 2 metres with extra R.F. stage. Single R.F. stage, two I.F. stages on all other bands. B.F.O. and Q-multiplier circuits. Improved A.N.L. and voltage regulated power-pack. "S" meter, band spread on amateur bands, large illuminated dial with logging scale. All controls fitted. Outputs for speaker and phones. Valve line-up: 4x6AQ5, 3x6BA6, 2x6BE6, 1x6BL8, 6AL5, 6AQ5, 6CA4 and OA2. Steel case 17 x 7 1/2 x 10 1/2 in. For 200/250v. A.C. mains. Brand new with full instruction manual. No Kits available.

**WIRECOMP'S PRICE 59 GNS.** Carr. and Pack free. H.P. Terms £12.19.0 dep. and 11 months at £4.18.0.

## Ready Built BOY'S TRANSISTOR RADIOS

2-transistor pocket radio. In plastic case. Size only 4in. x 2 1/2 in. x 1 1/2 in. Fitted with 2 1/2 in. speaker. Socket for personal earpiece. Works from PP3 type batt. tunable over full medium wave-band. Supplies comp. with earpiece, carrying purse and 9-volt batt. Ideal present.

**WIRECOMP'S 42/-** Post Price (Ready built model) available only 69/6. Post Free.

## NEW SUPER MINIATURE POCKET RADIOS



**THE SINCLAIR MICRO-6.** Self-contained pocket radio. Size only 1 1/2 x 1 1/2 x 1 1/2 in. A marvel of modern miniaturisation—truly amazing performance. May be built in an evening. Complete with earphone and detailed construction data.

Can be built for only **59/6** Mercury cell 1/11 extra (2 required).

**THE SINCLAIR SLIMLINE.** The new 2-transistor pocket radio size only 2 1/2 in. x 1 1/2 in. x 1 1/2 in. Micro alloy transistorised and printed circuit. All components available separately. Easy to assemble. **Can be built for 49/6**

## SUPER AMERICAN TAPE

INTERNATIONAL BRAND, FULLY GUARANTEED MYLAR BASE	
7in. Triple play, 3,600ft.	75/-
3in. Triple play, 450ft.	12/6
4in. Triple play, 900ft.	22/6
5in. Double play, 1,200ft.	15/-
5in. Triple play, 1,800ft.	42/6
5 1/2 in. Long play, 1,200ft.	15/-
5 1/2 in. Double play, 1,800ft.	22/6
5 1/2 in. Triple play, 2,400ft.	55/-
7in. Stand, play, 1,200ft.	12/6
7in. Long play, 1,800ft.	19/6
7in. Double play, 2,400ft.	25/-
P. & P. 1/- extra per reel. 4 reels and over Post Free.	

ACETATE BASE	
3in.—150ft.	3/6
3in.—225ft.	4/11
3in.—300ft.	7/6
5in.—Long play, 900ft.	10/-
5 1/2 in. Long play, 1,200ft.	12/6
7in. Long play, 1,800ft.	15/-

P.V.C. BASE	
5in. Standard play, 600ft.	8/6
5 1/2 in. Stand, play, 840ft.	11/6

## WIRECOMP'S BARGAIN STORE


48 Tottenham Court Road, London, W.1

Thousands of bargains: Transistor Radios—Record Players—Tape Recorders—Radiograms—Rock Bottom Prices

## SUPER TAPE RECORDER OFFER
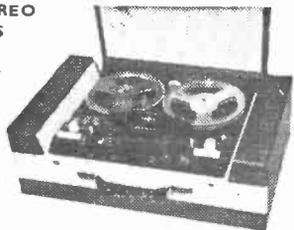
### SIEMENS STEREO TAPE RECORDERS

High precision machines offering a maximum of facilities for the enthusiast and connoisseur. General specification ★ Completely self contained. Record replay and Audio amplifiers built in. ★ All transistorised. ★ Three heads—separate record, replay, erase (also provides sound-on-sound recording). ★ Three speeds—7 1/2, 3 1/2, 1 1/2 i.p.s. ★ 4 tracks. ★ Takes 7in. reels. ★ Record level indicators on both channels. ★ Remote control facilities. Other facilities on these exceptional machines include: push button controls, tape end stop; separate switched bass boost and treble cut; sep. inputs for 2 microphones—2 radios and 2 pick-ups with provision for mixing 3 inputs. Outputs provided are 2 at 4 ohms; 2 sets headphones; 2 external amplifiers. Power output 24 watts per channel. All brand new, boxed and fully guaranteed.



**MODEL 12** (illustrated) self contained portable with 2 built in speakers. List price 94 gns.

**WIRECOMP'S PRICE 59 GNS.** Carr. and Ins. 15/-

**MODEL 11** on a contemporary styled wood plinth with one built in speaker. List price 67 gns.

**WIRECOMP'S PRICE 49 GNS.** Carr. and Ins. 15/-

## THE "REALISTIC" 7

Transistorised Portable Receiver made to the highest professional standard. Comprises 7 Mullard Trans. plus Crystal Diode, 350 milli-watt output to 4in. speaker.—I.F. frequency 470 Kc/s—fully tunable over medium and long wavebands. Two-tone plastic cabinet with handle—size 7 x 10 x 3 1/2 in. fitted socket for car aerial. Complete with full instructions.



**MAY BE BUILT FOR £5.19.6** All parts sold separately. Battery 3/6 extra. P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought. Also De Luxe Model with superior PVC covered wood cabinet and full valve tuning dial. ONLY £11.9.0. All parts sold separately. Battery 3/6 extra. P. & P. 4/6.

## GUITAR AND P.A. AMPLIFIER

### THE VIKING "TRANSISTOR 50"

50 watts output. Superb amplifier for all music and P.A. work—ideal for guitars, groups, etc. Fully transistorised for maximum efficiency. 4 inputs with mixing facilities plus reverb/echo chamber. Bass and treble controls. Fully built and guaranteed. In strong wood cabinet covered in washable material. Size approx. 22 x 10 x 6 in. Output imp. 15 ohms. For operation on 200/250v. A.C. mains.



**WIRECOMP'S PRICE 45 GNS.** Carr. and Pack 10/-

ALSO VIKING "SOUND 30"—30 watt valve model. 8 inputs, 4 sep. vol. controls plus bass and treble. 150 out.

**WIRECOMP'S PRICE 35 GNS.** Carr. and Pack. 7/6

## MATCHING LOUDSPEAKER SYSTEMS FOR THE "TRANSISTOR 50" OR "SOUND 30"

Will handle up to 50 watts. In floor standing enclosures styled to match the above amplifiers. Fitted with two 12in. Goodman Full Range speakers.

**WIRECOMP'S PRICE 33 GNS.** Carr. and Pack. 15/-

323 EDGWARE ROAD, W.2. AMB 7115

Both open all day Saturday. Early closing Thursday


378 HARROW ROAD, W.9. CUN 9530

Mail Orders to the above address.

# TRANSISTOR DESIGNS BY SINCLAIR 1
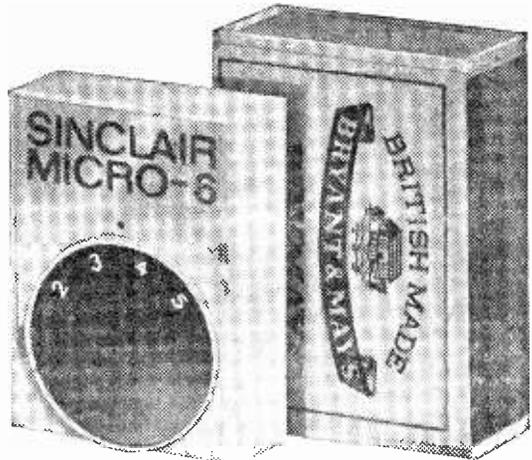
## Have you built the smallest set in the world yet?

It brings in stations from all over Europe. It is completely self-contained, including batteries which give about 70 hours working life and built-in aerial. It works in cars, buses, trains and many places where other sets cannot be heard at all. Yet the Micro-6 measures only  $1\frac{1}{2}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$  and weighs less than 1oz. Wherever you listen with your Micro-6, it will never intrude into other people's privacy, and you can even wear it like a wrist watch. So build yours now—it costs so very little to enjoy radio the Micro-6 way.




ACTUAL SIZE

## IT'S THE SINCLAIR MICRO-6

THOUSANDS ARE IN DAILY USE ALL OVER THE WORLD
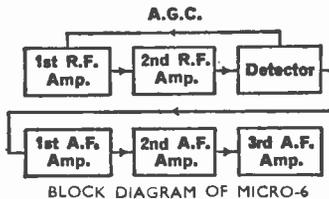
### Amazing circuitry!

Only three special Sinclair Micro-Alloy transistors (MATs) are used to provide two stages of R.F. amplification, followed by an efficient double diode detector which drives a high-gain 3-stage A.F. amplifier. Powerful A.G.C. applied to the first R.F. stage ensures fade-free reception from the most distant stations tuned in. Tuning is by means of a unique vernier control which extends over the medium wave-band and has bandspread for easy Luxembourg reception.



### Easy to build, too!

You can build the Micro-6 in an evening. All parts including transistors, case, lightweight earpiece and instructions come to


# 59/6

- Mallory Mercury Cell
- Type ZM312 (2 required)
- Each 1/11
- Pack of six 10/6
- 'Transista'
- Black nylon wrist strap 7/6

## SINCLAIR TR750 AMPLIFIER

Designed specially for Micro-6 and Slimline Users

SIZE  
2" x 2"

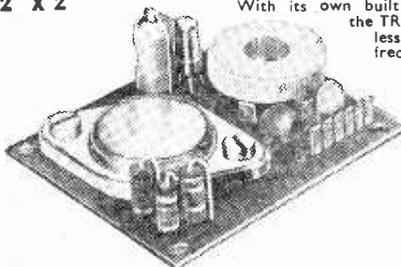

Another highly original Sinclair design which enjoys enormous popularity. The TR750 amplifier makes a powerful car, portable or domestic radio used with the Micro-6 or Slimline receivers and a plug is included for connecting to these sets. With its own built in volume control and on-off switch.


The TR 750 has a full 750 milliwatt transformerless output for 10mV into 10K ohms and a frequency response from 30 to 20,000 c/s  $\pm 1$ dB. It will also make an efficient hi-fi record reproducer used singly or paired for stereo and there are many other uses for the TR 750 which is available for building or ready built.

All parts with instructions come to **39/6**

Ready built and tested **45/-**
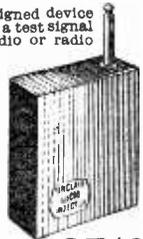
## Trace that fault with a Sinclair MICRO-INJECTOR

This ingeniously designed device generates and injects a test signal into any part of audio or radio equipment at any frequency from 1 kc/s to 30 Mc/s by means of which it becomes easy to locate faults rapidly and accurately. Measures  $1\frac{1}{2}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$  including probe. With full instructions. No constructor should be without a Micro-Injector.



Parts and instructions come to **27/6**

Ready built and tested **32/6**



**SINCLAIR RADIONICS LTD.**  
**COMBERTON Cambridge**

Telephone  
COMBERTON  
682

# TRANSISTOR DESIGNS BY SINCLAIR 2

## SINCLAIR X-10

COMBINED 10 WATT AMPLIFIER AND PRE-AMP

A 100% British Design!



### WITH PULSE WIDTH MODULATION

The most advanced design of its kind in the world

### Build it now!

All parts including 11 transistors, building instructions and X-10 Manual come to

## £5.19.6

Ready built and tested with X-10 Manual

## £6.19.6

X-10 Power Supply Unit (ready built) for Mono or Stereo. A.C. Mains 200-240V. **£2.14.0**

- ★ 11 Transistors and no heat sink
- ★ Unique output stage
- ★ Facilities for adding your own choice of tone control circuit
- ★ Input sensitivity 1mV into 1kΩ
- ★ Can be used with all types of inputs including low-output pick-ups and microphones
- ★ Total harmonic distortion less than 0.1%
- ★ Output power up to 10 watts
- ★ Frequency response 5-20,000 c/s ± 1dB
- ★ Speaker impedance 15Ω
- ★ Damping factor—greater than 100
- ★ Supply voltage 12 volts from batteries or mains supply unit
- ★ Size 6" x 3"

#### SINCLAIR X-10 MANUAL


included with every X-10 it explains how the amplifier functions and how you can add the correct tone and volume control system to suit your precise requirements. A variety of systems is shown, none of which will add more than a few shillings to the original cost of your Sinclair X-10, be it for MONO or STEREO. Obtainable separately, price 1/6.

**UNIQUE GUARANTEE**  
If you are not completely satisfied with your purchase (we are confident you will be delighted) the amount you have paid for it will be refunded in full instantly and without question.

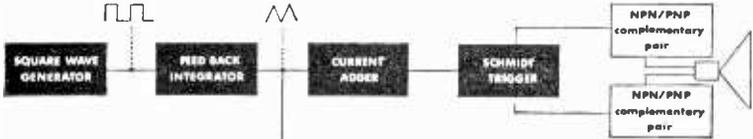**FULL SERVICE FACILITIES ALWAYS AVAILABLE**

*If you do not wish to cut coupon please mention "Practical Wireless" form on ordering.*

This remarkable amplifier which is complete with its own pre-amp stage and unique output stage uses Pulse Width Modulation resulting in an entirely new conception of amplifier design and performance. With P.W.M., when the input signal is at any frequency up to 20 kc/s (which although well above the range of audibility is of vital importance in hi-fi reproduction) the net current is an exact replica of the input signal and is independent of the transfer characteristics of the output transistors. This makes the distortion figures incredibly low. Due to the way in which P.W.M. operates and the special output stage of the X-10, the output transistors actually act as switches and so dissipate negligible power. This advanced technique enables 5 Mc/s transistors to be used with great savings in space, current consumption and costs. It makes having a heat sink unnecessary, and the X-10 may even be satisfactorily operated from two 4½" batteries.



**BLOCK DIAGRAM** shows in simplified form the stages of junction of this remarkable amplifier. Such design with its very much better standards of performance is made possible by use of the very latest transistors and high quality components.

**TO SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE** Phone: COMBERTON 682

Please send items detailed below      £   s.   d.

.....

.....

.....

TOTAL £ \_\_\_\_\_

For which I enclose cash/cheque/money order

NAME .....

ADDRESS .....

.....

.....

BLOCK LETTERS      P.W.3

**SOUND RECORDINGS**

**A UNIQUE BUY** Recording tape top brand, 7in. 2.400ft. D.P. 25/-; 5in. 1.200ft. 19/6d. P. & P. 1/6d. per spool. Bargains in all sizes. S.A.E. for list. We repair, buy and sell recorders. **E. C. KINGSLEY & CO. LTD.**, 132 Tottenham Court Road, London.

**RECEIVERS & COMPONENTS**

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. PW7/9, 126 Hamilton Road, West Norwood, S.E.27. Gipsy Hill 6166.

**19 SETS** for spares from 12/6 each. Sets complete 35/-. Sets complete with Power Pack control unit and aerial tuner £3. Mk II and Mk III, 38 sets, 15/- each. 38 sets for spares 6/- each. Spare valves for all above sets 2/6 each. Vibrator units new & unpacked 25/- each. **MAIN ROAD GARAGE**, South Green, Billericay, Essex

**TRANSISTORS** now half price. unmarked but tested packets of 16; unmarked, untested packets of 40; diodes suitable as diodes, packets of 80. All packets 10/- each, postage 1/-. Four packets post free. **C.W.O. K. R. WHISTON** (Dept. PWT), New Mills, Stockport.

**NEW VALVE TESTERS £12.** Mollnux, Lowfield Heath, Sussex.

**TRANSISTORISED SIGNAL INJECTOR.** Complete kit of components and circuit of injector for testing and amplifier or radio, 7/6 only, post free. **G. F. MILWARD**, 17 Peel Close, Drayton Bassett, Staffs.

**TRANSISTORS!** Give-away price. **NKT124.5** Power Type, 6 for 10/-; **260V1**, 4W, up to 60V, 6/- each, post free. **G. F. MILWARD**, 17 Peel Close, Drayton Bassett, Staffs.

**DIRECT TV REPLACEMENTS LTD.**, largest stockists of TV Components in the UK. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes, Day and Night Telephone Gipsy Hill 6166, 126 Hamilton Road, West Norwood, S.E.27.

**AERIAL MATCHING TUNING UNITS**  
**LATEST AMERICAN RELEASE BULK PURCHASE**  
OF 3,000

These well-made tuning units made for the American 19 T.X.-B.X. are housed in a metal case (Green or Brown) using a large precision calibrated scale, are an essential piece of equipment for the serious T.X. or R.X. operator. This unit will match an untuned wire or whip aerial to almost any short wave receiver or transmitter, exceptionally good for mobile top band use. This American version being well noted as far superior to any other. **GUARANTEED BBAND NEW** only 20/-, post 7/6. Instructions supplied.

**V.H.F. RADIO RECEIVER R10, FX4840 Mc/s.** 4475 Mc/s. (6.2-6.7 Cm/s). These recently made sets are supplied in two units.

(1) Receiver. This is manual or auto-tuned by an internal motor using a total of 18 valves, o.c. mixer CF90 Lt. 45 mc/s. aerial input via ordinary Pyc coaxial plug (supplied).

(2) Power unit and output stage, contains 300 v.h.t. and -50 v. Bias Supplies, also receiver auto-tune supply. Both units housed in matching metal cases, size 1 7/8 x 8 x 10in. Supplied in first-class order complete with circuit and connecting cable from power unit to set. Mains 230 volt input. Offered at a fraction of cost. £41.00 per unit, carr. 10/-.

19in. Rocks, 5ft. and 6ft. high 50/- each, carr. 10/-.

**J. T. SUPPLY (Dept. D)**  
**38 MEADOW LANE, LEEDS 11**

**RATES:** 7/3 per line or part thereof average live words a line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Lower House, Southampton St., London W.C.2.

**RECEIVERS & COMPONENTS**

(continued)




**V.H.F. Receivers P104 (R1392)**, 100 to 150 Mc/s. 13 valves. B.F.O. A.G.C. R.F. and L.F. gains. Tuning Meter. In good condition complete with instructions to convert to tunable; can be used crystal controlled as is. £31.00 carriage 15/-

**Power Unit Type 3** for 230 volts a.c. input suits above R1132 and P104. £25.00 carriage 10/-

**Ceramic Insulated 3 Gang Variables.** 56 x 56 x 35 Pt. 3/8. Post 1/6. Meters 2in. round 500 microamp. Used, tested before despatch 3/6. Post 1/6. Toggle Switches. 5 amp. 230 volts, single pole or double pole on-off 2/-, Post 1/-

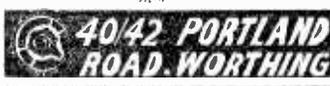(Carriage charges apply to England and Wales only)



"CENTURION All-Wave" Receiver. kit / chassis / phones / diagrams complete, mainly assembled. Cost £11/18/6. Sell 80/- o.n.o. **BUTCHART**, 17 West Cromwell Road, London, SW5.


**FAMOUS TRANS-RECEIVER**

Covers 2-4.5, 4.5-8 mc/s. (150-37 metres) in two bands, 230/250v. A.C. mains. Six valve superhet receiver with I.F.'s of 485 Kc/s. and six valve transmitter designed for voice and C.W. Incorporates test and tuning 500 uA meter for voltages, aerial loadings and current tests. Panel controls. Freq. PA. Tuning Gain MCW. CW. RT. Het Tone, Netting, On/Off Quench, Aerial, AVC, Lt-HT tests. Supplied complete. Fully tested and working

**PRICE £12.10.0.**  
Carr. £1.0.0.



**WAVEMETER CLASS D**

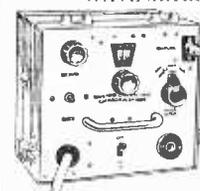

Freq. band 1,900 Kc/s. to 8,000 Kc/s. (158-37.5 metres) in two ranges, 1,900 Kc/s. 4,000 Kc/s. also 4,000 Kc/s. 8,000 Kc/s. Supply 6 v. D.C. input. Complete with twin crystal. As new.

**PRICE 57/6.**  
P. & P. 5/-

**ROTARY TRANSFORMERS.** 12 v. D.C. input, 300 v. D.C., 120mA output, note size only 4 1/2 x 2in. 15/-, Post 2/6

**ROTARY TRANSFORMERS.** 12 or 24 v. D.C. input, 265 v., 120A and 540 v., .026 Amps. American made. Only 25/-, P. & P. 5/-

**R.C.A. ATNSD USED MODEL.** Fully tested and working £45. Carr. 2/6

Many other bargains. S.A.E. all enquiries.

**A. J. THOMPSON**  
"HILTON LODGE"  
**CODICOTE, HITCHIN, HERTS.**  
Phone: CODICOTE 242

**RECEIVERS & COMPONENTS**

(continued)

**COMPONENTS** at give-away prices! Transistors: Valves: Coaxial Cable: Electrolytics: Vol Controls: Pre-sets: Speakers: Test Meters: Recording Tapes: Wiring Cable: Microphones: Pick-up Cartridges: Soldering Irons: Plugs, Sockets, Panels etc. Send a 3/- stamp for full price lists. **DIAMOND** (Mail Order) Products. (P.W.) BMC/DIA, London, W.C.1.

**TELEVISION SETS**, not working, 17in. £2; 21in. £3/10/-; 14in. Portables £2/10/-. Phone: Bournemouth 26849.

**A1 POST FREE BARGAINS:** Guaranteed test tested Valves, EF80, EB9, 9d. each; ECL80, 2/-; ECC82, PY31, P230, 3/- each; PY30, PY32, 3/3 each; PL83, 3/6; PL82, PCF80, 3/9 each; 20P1, 4/-; EB90, N37, 4/3 each; PL33, 4/8; PL81, 4/8; 10P13, 5/3. S.A.E. for list or enquiries **A1 RADIO COMPONENTS**, 14 The Borough, Canterbury, Kent.

**TRANSISTORISED TREMOLO UNIT** - Compact unit with volume, depth and tone controls. Provisions for a foot switch, two inputs and output to the amplifier. The unit complete with the battery is 4 gns, p. & p. included. Orders by post and CWO only please. **D MILLS**, 20 Andrew Close, Calmore, Totton, Hants.

**BARGAIN VALVES**, set tested; money back guarantee. EF90, EF8, EB91, 1/-; ECL80, 2/-, P. and P. 6/- each. **ASTELL**, 1 Rowallan Ct., Colchester, Essex.

**SPEAKER REPAIRS**, cones fitted. Satisfaction guaranteed. **L. S. REPAIRS**, Pluckley, Ashford, Kent.

**R & R RADIO & T V SERVICE**

Dept. P.W.

**MARKET STREET, BACUP, LANCS.**  
Telephone 465

SALVAGE VALVES		Tested before dispatch	
6F13	4/6	10F4	5/-
6L8	4/8	20P5	6/6
EF80	1/6	30P4	7/-
ECC82	3/-	6F15	5/-
ECL8	3/6	10P11	5/-
30P5	5/-	EF85	5/-
PL88	6/-	83012	4/-
PLF80	4/-	30P13	6/-
PL81	5/-	30P11	3/-
P230	5/-	PL82	5/-
U229	5/-	PL82	5/-

Speakers, Ex-TV, 5in. round, 6 x 4in. 3/6; 8in. round, 6/-; post 2/-

Line Output Transformers available. State set model No.

Turret Tuners, 3/-, post 2/-

Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

**FOR SALE**

**5-TON FACTORY CLEARANCE.** Radio, TV Electrical Components, in mixed parcels Example: 28.6 mixed parcel £1 pp 7/6d. Speakers, grilles, valves, bases, i.f.s. covers, condensers etc. Hundred other items. S.A.E. List and Postal Orders to **P. NEWTON**, 16 Shalcross Crescent, Hatfield, Herts.

**HAMMER FINISH PAINT.** The modern finish for electronics. Can be brushed or sprayed. Blue or silver. 2lb. tins 3/6, 1 pint 7/6, 1 pint 15/-. Post 6d. on any order. Trade supplied. **FINNIGAN SPECIALITY PAINTS** (tpw), Mickley Square, Stocksfield, Northumberland.

# NOW READY!

A modern way of instrument case assembly using our "Die Strip" and Stelvetite panels. The strip has been specially made for us at Birmingham on qty. production, for low price to the public. It is made of high strength alloy and will enable anyone to assemble an instrument case or cabinet in minutes. The Stelvetite sheet is cut to size ready for use. Full details of these products will be sent free. Please send large envelope self addressed.

Also available Key Switches. 4 pole 2 throw 3/6 each or 3 position D.P. plus D.P. centre off 5/- or rotary switch 6 pole 3 way 3/-.

Bank of 4 Pye Sockets with plugs and leads 5/- set. Ever Ready Batteries, 90 volts plus 7 1/2 volts 4/6 each.

Plessey 2-4-12-25 way plugs and sockets all 5/- pair.

Jones Plugs and Sockets 4-12-18-24-32 way all 5/- pair.

Special Lightweight 7in. x 4in., 3 ohm P.M. Speaker 6/-.

88 set transmitter receiver Chassis less valves, 20/- each. Post paid.

**19in. RACK FITTING CABINET.** 34in. high by 21in. deep with telescopic drawer slides. Louvred sides, back and top. Brand new Swedish make. £4. only, plus B.R.S. delivery.

ECR Tube with Screen and Base with ECR 35 data, 25/-.

SUP7 Tube with Screen and Base, with data, 30/-.

## COLLARO AUTO CHANGE

3 speed Gramophone Decks  
Tested and Guaranteed  
Post free 50/- each  
Brown or Cream

Copper Laminate Board, single or double sided, 5/- per square foot panels, either type 3ft. by 4ft., 33/-.

High Stab Resistors, 5%, 6d.; 2%, 9d.; 1% 1/-. Every six packed in 7-compartment linen finish component box. Unmarked.

Speakers, 3 ohm P.M. 5in., 5/-, 6in., 6/-, 7 x 4in., 7/-, 8in., 8/-, 10in., 12/6.

U.K. ONLY

# E. R. NICHOLLS

Mail Order and Retail Shop  
46J LOWFIELD ROAD  
off SHAW HEATH, STOCKPORT  
CHESHIRE

## FOR SALE (continued)

**CONDENSER BARGAIN!** Miniature Paper Condensers, 1/2in. x 1/2in. Ideal for transistor sets. .0001, .001, .002, .005, .02, .04µF. Your choice 7/6 per 100 or £3 per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

## MORSE MADE EASY!

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum!

One student, aged 2 1/2, took only 13 DAYS and another, aged 71, took only 6 WEEKS to obtain a G.P.O. pass certificate. If you wish to read Morse easily and naturally, please enclose two 3d. stamps for full explanatory booklet.

To G3CHS, THE MORSE CENTRE, 45 GREEN LANE, PURLEY, SURREY.

**ARMATURE REWINDS** — Hoover Junior Exchange Service Models, 375/119/1224, 32/6 inc. post. Fields 15/-, Rolls washing machine spares, Trade discounts. Send for list. JERVIS & TONGE LTD. (Dept P.W.), Ringwood Road, Brimington, Chesterfield, Derbyshire. Telephone: Chest 75267.

## TESTED TRANSISTORS

All new, few equivalent.  
1/- each, Red or White Spots.

2/- each. XA101, XA102, XB103, OA90, OC430, XA112, XA111.

3/- each, OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16.

4/- each, AF114, AF115, AF117, OC170, OC171, SX658, XU611.

5/- each, OC72, OC139, OC140, OC204, ORP60, BY100, GET8.

10/- each, OC35, OC26, OC28, GET57, 2SO13. All new, few equivalent.

ZENER DIODES 4.7 v. to 33 volt 1/2 watt, 3/6 each. 1.5 watt, 5/- each. 7 watt, 6/- each.

Send 3d stamp for Full Price List and Free Equivalent Chart.

## B. W. CURSONS

78 BROAD STREET  
CANTERBURY, KENT

## YUKAN Get this Air Drying Grey HAMMER FINISH now — IT'S SUPERB . . . THE PUSH-BUTTON WAY!

YUKAN Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Available in Grey Hammer at 14/11 at our counter or 15/11. Carr. paid, per push-button sellspray can. SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11.

Please enclose cheque or P.O. for total amount to:

**YUKAN**  
Dept. P.W.3, 307a EDGWARE RD., LONDON W.2

(Closed Thurs. afternoons, open all day Sats.)

Choice of 13 self-spray plain colours and primer (Motor car quality) also available.




## FOR SALE (continued)

**240 watt ELECTRIC POWER ANYWHERE**  
**ANYTIME from 12 watt CAR BATTERY**  
WITH THE AMERICAN DYNAMOTOR UNIT  
Input 12v. output 200/250v. at 150 to 220 watts.  
Perfect for TELEVISION, POWER TOOLS and all universal AC/DC ELECTRICAL EQUIPMENT, gives wonderful results. Price ONLY £8 + 12/- carriage.  
Send stamped envelope for full illustrated details to SCIENTIFIC PRODUCTS, CLEVELTON, LEEDS.

**MARCONI INSTRUMENTS.** Signal Generator, 10-300Mc/s. Tested £5, carriage £1. 58 King St., Aspatria, Cumberland

## ELECTRIC SOLDERING-IRON

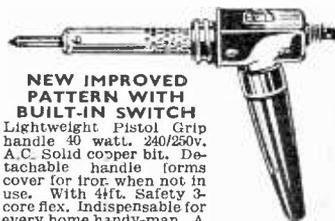

**NEW IMPROVED PATTERN WITH BUILT-IN SWITCH**

Lightweight Pistol Grip handle 40 watt, 240/250v., A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handy-man. A boon to model makers and a necessity for every wireless enthusiast. P. & P. 1/-.

ONLY 12/6

**G. H. SERVICE (Dept. P. W. 3),** Lusted Hall Lane, Tatsfield, Kent

## WANTED

WE BUY new valves for cash, large or small quantities, old types or the latest. Send details, quotations by return. WALTONS WIRELESS STORES, 15 Church Street, Wolverhampton.

## WANTED VALVES ONLY

Must be new and boxed

Payment by return

**WILLIAM CARVIS LTD.**

103 North Street, Leeds 7

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S. Beverley House, Mannville Terrace, Bradford 7.

WE BUY new Valves and transistors. Amplifiers. Short-wave Receivers and Components etc. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

**SITUATIONS VACANT**

**RADIO AND TV Exam**, and Courses by Britain's finest Home-study School, Coaching for Brit.I.R.E., City and Guilds, Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. **FREE** brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

**RADIO TECHNICIAN**

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. stations.)

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19, £722; at 25, £929 (highest pay on entry) rising by four increments to £1,067.

Prospects of promotion to grades in salary range £997—£1,634.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days.

Normal Civil Service sick leave regulations apply.

Apply:

**RECRUITMENT OFFICER (RT 37)**

**Government Communication**

**Headquarters, Oakley Priors Road  
Cheltenham**

**SITUATIONS VACANT**

(continued)

**YOUNG MAN** required, over 18 years, to work in busy Radio Shop and Mail Order Dept. Some previous experience necessary. For appointment telephone Paddington 1008-9. **HENRY'S RADIO LTD.**, 303 Edgware Road, London, W.2.

**A.M.I.Mech.E., A.M.I.E.R.E.**, City and Guilds, G.C.E., etc., brings high pay and security. "No pass—no fee" terms. Over 95% successes. For details of Exams, and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page Handbook—**FREE**. **B.I.E.T.** (Dept. 242B), London, W.8.

**STUDY RADIO, TELEVISION AND ELECTRONICS** with the world's largest home-study organisation. **I.E.R.E.**, City and Guilds, R.T.E.B., etc. Also Practical Courses with equipment. All books supplied. Write for **FREE** Prospectus stating subject to **I.C.S.** (Dept. 542), Intertext House, Parkgate Road, London, S.W.11.

**TV AND RADIO—A.M.I.E.R.E.**, City & Guilds, R.T.E.B. Cert., etc., on "No pass—no fee" terms, over 95% successes. For details of exams and home training courses (including practical apparatus in all branches of radio, TV and electronics) write for 148-page Handbook—**free**. **B.I.E.T.** (Dept. 242G), 29 Wright's Lane, London W.8.

**BOOKS & PUBLICATIONS**

**AUDIO**, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—**list free**. **WILLEN** (Dept. 46), 61a Roadway, London, E.15.

**EDUCATIONAL**

**BECOME "TECHNICALLY QUALIFIED"** in your spare time. Guaranteed Diploma and Exam Home-study Courses in Radio, TV Servicing and Maintenance. **R.T.E.B.**, City and Guilds etc. Highly informative 120 page Guide. — **FREE**. **CHAMBERS COLLEGE** (Dept. 363), 148 Holborn, London, E.C.1.

**THE INCORPORATED PRACTITIONERS IN RADIO AND ELECTRONICS (I.P.R.E.) LTD.**, Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/-. post free. Secretary, Dept B. 32 Kidmore Road, Caversham, Reading, Berks.

**TRAIN FOR SUCCESS  
WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for **I.E.R.E.**, City & Guilds (Telecoms and Radio Amateurs) **R.T.E.B.**, etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE** prospectus and find out how **ICS** can help you in your career  
**ICS DEPT. 541 PARKGATE ROAD,  
LONDON, S.W. 11.**

**INCREASE YOUR INCOME  
WIDEN YOUR KNOWLEDGE  
MAKE NEW FRIENDS**

**JOIN THE**

**ARMY EMERGENCY RESERVE  
R.E.M.E.**

**WIRELESS AND TELECOMMUNICATION MECHANICS** with or without previous military service are required as volunteers to train for 15 days in the summer on modern equipment. Generous pay and bounties. For details write:

**HQ AER, R.E.M.E., BROXHEAD HOUSE, Bordon, Hants.**

**EDUCATIONAL**  
(continued)

**TRAINING**

Full-time courses in RADAR and RADIO-TELEGRAPHY for prospective marine Radio Officers. Govt approved exam. centre. Also courses in basic ELECTRONICS, RADIO, TELEVISION and PRACTICAL SERVICING.

Apply:—Director, British School of Telegraphy, 20 Penywern Road, Earls Court, London, S.W.5.

**RADIO OFFICERS** see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1965/6. Day and Boarding Students. Grants and scholarships available. Stamp for Prospectus, WIRELESS COLLEGE, Colwyn Bay.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**DON'T FUMBLE** with Formulae. Master Mathematics quickly and easily the Understandable Way.

**1st lesson and details FREE**

The Dryden School of **UNDERSTANDABLE MATHEMATICS**

11 J. Dryden Chambers, Oxford Street, London W.1

Name.....  
Address.....

**METAL WORK**

**METAL WORK.** All types cabinets, chassis, racks, etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman St., Loughborough.

**CABINETS • CASES CHASSIS**

Anything in metal. "One-offs" a pleasure. Send your drawing for quote. Stove enamelled in any professional finish.

**MOSS, WATSON**

40 Mount Pleasant Street, Oldham Lancs. MAIN 9400

**SERVICE SHEETS**

**SERVICE SHEETS,** Radio and Television, 3/6 post paid. VEST AND EMERY, 17 Hollgarth St., Durham.

**SERVICE SHEETS:** Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** for all makes of Radio and TV 1925-1964. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models, 1/6. Valves, modern and obsolete Radio/TV Books, S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

**SERVICE SHEETS**  
(continued)

**SERVICE SHEETS,** also current and obsolete Valves for sale. JOHN GILBERT'S TELEVISION, 1b Shepherd's Bush Road, London, W.12. Phone: SHE 8441.

**SERVICE SHEETS** (75,000) 4/- each. Callers Welcome; Always Open. 6 South Street, Oakenshaw, Bradford.

**S.E.S. SERVICE SHEETS** for all TV Radio and Tape Recorders, etc. List 1/6 plus S.A.E. SUN ELECTRICAL SERVICES, 38 St. George's Road, Hastings, Sussex.

**SERVICE SHEETS**

4/- ea., plus postage

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country. Speedy service.

To obtain the Service Sheet you require, please complete the attached coupon.

From:.....  
Name:.....  
Address:.....

To: **S.P. DISTRIBUTORS**  
44 Old Bond St., London, W.1  
Please supply Service Sheets for the following:

Make:.....  
Model No.:..... Radio/TV  
Make:.....  
Model No.:..... Radio/TV  
Make:.....  
Model No.:..... Radio/TV

I also require list of Service Sheets at 1/6.

(please delete items not applicable)  
I enclose remittance of.....

**MAIL ORDERS ONLY** MaPW

**MISCELLANEOUS**

**CONVERT ANY TV SET** into an oscilloscope. Instructions and diagrams 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

**WILL** anyone capable of repairing R1155 receiver please telephone WIMBLEDON 03307

**ELECTRONIC MUSIC?**

Then how about making yourself an electric organ? Constructional data available—Full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

**Write NOW** for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2d. stamp.

**TEST METERS**



**20,000 O.P.V. MODEL TP 55.** Reads voltages up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/4 in. x 6 1/4 in. x 1 1/4 in., £5.19.6.

**2,000 O.P.V. MODEL TP 10.** Reads A.C. and D.C. Volts up to 2,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +35; Output jack for Audio Measurements. Size 8 1/2 x 5 x 1 1/4 in., £3.19.6.

**30,000 OHMS PER VOLT MODEL 500.** Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 O.P.V.; D.C. current to 12 amps. Resistance to 60 Megs.; Decibels from -20 to +35; Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 3/4 in. x 6 1/4 in. x 1 1/4 in., £5.19.6.

**TRANSISTORISED TEST EQUIPMENT.** Fully guaranteed, brand new. By NUMBEX: 150 Kc/s.—350 Mc/s. Signal Generator, £9.10.0. Resistance-Capacitance Bridge, £8.5.0. 1-16 volts D.C. Power Supply, £6.10.0. Audio Generator 10/100,000 c/s., £16.15.0. Inductance Bridge, £18.0.0.

**By T.M.K. INSULATION TESTER.** Measures up to 500 megohms at 3 testing voltages, 100, 250 and 500. Supplied with leather case and leads, £17.10.0. Illustrated details on any of the above sent on request.

**LINEAR AMPLIFIERS** LG34, 4 watts, size 8 1/2 x 4 1/2 x 2 1/4 in. high, £5.5.0. L45A 5 watts, size 7 x 7 x 5 in. high, £5.19.6. Protective cover, 12/9. L5/55 6 watts stereophonic, size 10 1/2 x 8 x 6 in., £12.12.0. cover with carrying handles 25/-. "Distic" 10 watts Hi-Fi Ultra Linear Push-Pull, size 9 x 7 x 9 1/2 in. high, £12.0. Cover with carrying handles, 19/6. 11/10 10 watts Hi-Fi Ultra Linear size 9 x 7 x 6 in. high, £13.13.0. Cover with carrying handles, 19/6. "Conchord" 30 watts Hi-Fi Ultra Linear size 12 1/2 x 9 x 7 1/2 in. high, £18.10.0. Cover with carrying handles, 25/-. L50 50 watts Hi-Fi Ultra Linear, size 14 x 10 x 3 in. high, £25.2.0. Cover with carrying handles, 32/6. All amplifiers for normal A.C. mains, and ex stock. Details on request.

"Tripletone" Convertible Amplifier. Size 10 x 3 x 4 1/2 in. high. 4 watts output matched for 2-3 ohms. OR 2 amplifiers can be coupled together for STEREO, £25.19.6 each.

"Tripletone" F.M. Tuner, size 11 x 6 x 3 in. high. Coverage 86-104 Mc/s. £13.18.6 (unpowered), or £16.14.6 (self powered). Details on request.

**MICROPHONES.** Crystal Types. Guitar 12/6. Desk, with built-in stand 15/-. Acce 39/1 Stick, and Table Stand 32/6. Super Stick, with heavy Desk Stand 49/6. Moving Coil Types. Stick, with heavy Desk Stand 59/6. "stunline" Stick, 50K impedance, with switch 75/-. Omni-directional, chrome plated die-cast frame, 50K. with switch 99/6.

**ADJUSTABLE MIKE STANDS,** with heavy bases and plated stems. Table type 29/6. floor type 55/-.  
Telephone: TERNINUS 7037


**HARRIS ELECTRONICS**  
(London) LTD.  
138 GRAY'S INN ROAD,  
LONDON, W.C.1

Please include carriage cost on ALL items  
Open until 1 P.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross

**Precision 6 minute Delay Action Switch.** Clock-work actuated. Made by Smiths.  
Separate switching actions at 1 1/2 mins., 1 1/4 mins. and 3 mins.  
Each switch action designed for current loading up to 15 amps at 250 volts. Suitable for photographic time, sequence switching operations etc. etc. Brand new and unused units offered at a fraction of their true value. **OUR PRICE ONLY 8/6 each.** Post Free. 2 for 15/-  
Special quotations for quantity.

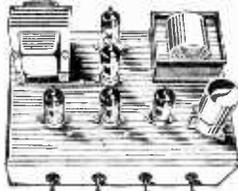**10/14 WATT HI-FI AMPLIFIER KIT**

A stylish finished monaural amplifier with an output of 14 watts from 2 EL84's in push-pull Super reproduction of both music and speech with negligible hum.



Separate inputs for mike and gram. allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84's, EOC83, EF86, and E280 rectifier. Simple instruction booklet 1/6. (Free with parts).

All parts sold separately. **ONLY £6.19.6** P. & P. 6/6  
Also available ready built and tested complete with standard input jack socket. £8.15.0. P. & P. 6/6  
Carrying case for above 28/8 P. & P. 4/-

**HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI**




● Peak output in excess of 1 1/2 watts. ● All standard British components. ● Built on printed circuit board size 6 x 3in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GE114) or 81 Mullard OC81D and matched pair of OC81 o/p. ● 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive, easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately.

**SPECIAL PRICE 45/-** P. & P. 2/6  
Also ready built and tested, 52/8. P. & P. 2/6.  
A pair of TAI's are ideal for stereo.

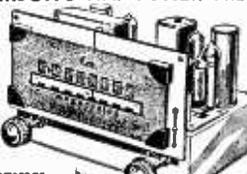**HARVERSON'S F.M. TUNER Mk. I**

● F.M. Tuning head by famous maker. ● Guaranteed non-drift. ● Permanently tuning. ● Frequency coverage 88-100 Mc/s. ● Balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3in. glass). ● Self-powered, using a good quality mains transformer and valve rectifier. ● Valves used EOC85, two EF80's and E280 (rectifier). ● Fully drilled chassis. ● Size of complete tuner 8 x 6 x 5 1/2 in. ● All parts sold separately. Set of parts if purchased at one time £5.19.6. plus 8/6 P. & P. and ins. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and provisions. £6.12.8. P. & P. 8/6.  
Mark III Version as Mark I but with output stage (ECL82) and tone control. £7.7.0. P. & P. 8/6.  
Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/-, P. & P. 2/6. To fit Mark II, 17/8. P. & P. 2/6.



**SPECIAL PURCHASE TURRET TUNERS**

By famous maker. Brand new and unused. Complete with PC84 and PC80 valves. 34-38 Mc/s I.F. Biscuits for Channels 1 to 5 and 8 and 9. Circuit diagram supplied. **ONLY 25/-** each. P. & P. 2/6.

**GORLER F.M. TUNER HEAD**

88-100 Mc/s 10.7 Mc/s I.F. 15/-, plus 1/8 P. & P. (EOC85 valve. 8/6 extra).

**QUALITY RECORD PLAYER AMPLIFIER**

A top-quality record player amplifier. Size 7in. w. x 2 1/2 in. d. x 5 1/2 in. h. This amplifier (which is used in a 29 gm. record player) employs heavy duty double wound mains transformer. EOC83, EL84, E280 valve. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested.

**PRICE 69/6** P. & P. 3/6.  
**ALSO AVAILABLE.** Mounted on board with output transformer and 6in. speaker, ready to fit into cabinet below. **PRICE 89/6** P. & P. 4/6.

**QUALITY PORTABLE R/PLAYER CABINET**

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player. Unit. size 18 x 14 x 8 1/2 in.

**PRICE £39.6.** Carr. 5/-

**EMBASSY PORTABLE RECORD PLAYER CABINET.**

Will accommodate amplifier, up to 7 x 4in. speaker and B.S.R. or GARRARD autochanger or single player unit. Attractive tortoise covered finish. Overall size 17 x 15 x 8 1/2 in. with uncut motor board. **PRICE 69/6** Carr. 5/-.

**4-SPEED PLAYER UNIT BARGAINS**

All Brand New in Maker's Original Packing  
MONO SINGLE PLAYERS (Stereo 12/6 extra)  
GARRARD SERVO 25.9.11. Carr. 4/- B.S.R. GUY with unit mounted pick-up arm £4.18.8. Carr. 4/-  
MONO AUTO CHANGERS (Stereo 12/6 extra)  
LATEST B.S.R. UA25 Super Slim mono £6.2.8 B.S.R. UA15 £6.19.6; B.S.R. UA16 £6.19.6  
Latest Garrard AT5 Mono ..... £8.0.0  
Standard Garrard Autoch. Mono ..... £8.0.0  
Garrard AT6 Mono ..... £10.10.0 Carr. 5/- on each

**SPECIAL OFFER !!**

**BRAND NEW HEAVY DUTY 12in. SPEAKERS**  
Response 45 c/s-15 Kc/s. 1 1/2in. voice coil. Available in 3 or 15 ohm. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. **LIMITED NUMBER ONLY UNREPEATABLE AT 89/6** P. & P. 2/6. Also 25 watt GUITAR Model available at 25.5.0.

**LATEST MODEL B.S.R. TU/12**

**4-SPEED PLAYER AND PICK-UP ONLY 69/6** Carr. 4/-

7in. metal turntable  
Low flutter performance. 200/250 v. shaded pole motor with 90 v. tap for valve filament.  
High gain crystal pick-up with turn-over LP/78 head complete with sapphire stylus.



**THE NEW HARVERSON KIT FOR THE HOME CONSTRUCTOR**

Valves: excellent all purpose: A.C. mains 200/240v.  
**AMPLIFIER KIT TYPE HSL 'FOUR'**  
3 VALVE 4 WATT USING EOC83, EL84 E280 VALVES  
Special features include:

● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages, ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● All this builds onto a chassis size only 7 1/2 in. wide x 4 in. deep. ● Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the unexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder etc. (No extras to buy). **79/6** P. & P. 5/-  
Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with Kits).



**3-VALVE AUDIO AMPLIFIER MODEL HA34**




Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates EOC83 EL84 E280 valves, heavy duty double-wound mains transformer and output transformer matched for 3 ohm u. speaker, separate B. s. Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quality order enables us to offer them complete with knobs, valves, etc., wired and tested for only **£4.5.0** P. & P. 5/-

**NEW CARTRIDGE BARGAINS**

**RONETTE STEREO 105 CARTRIDGE.** Stereo/LP/78. Complete with two sapphires. Original list price. 67/8. **OUR PRICE 24/-** P. & P. 1/-  
**GARRARD G62 Mono complete.** List price 24/11. **OUR PRICE 12/6** P. & P. 1/-  
**B.S.R. TC85 High output compatible Stereo cartridge.** Stereo/LP/78 sapphire stylus and universal mounting bracket. List price 44/11. **OUR PRICE 22/6** P. & P. 1/-

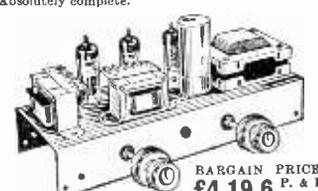**STEREO AMPLIFIERS**

Incorporating 2 ECL82's and 1 E280 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



**BARGAIN PRICE £4.19.6** P. & P. 5/-

**6 TRANSISTOR AND DIODE SUPERHET**

A first-class 2 waveband transistor superhet ● Printed circuit panel size 6 1/2 in. x 3 1/2 in. ● Dual-aligned I.F. transformers. ● High-gain Ferrite Rod Aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time. **ONLY £4.5.0** P. & P. 2/6. Circuit diagram 1/6 (free with set of parts).

**35 OHM SPEAKERS**

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables, 8/6, 3/4in., 12/8; 5in., 17/8; 7 x 4in., 21/-, P. & P. 1/6 per speaker.

**Portable CABINET**

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker. 25/-, P. & P. 2/-.

**COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET**

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (med., long and car aerial coupling). 32/6 complete, post 1/- 6 transistor printed circuit board to match, 8/6. Post 9d. Circuit diagram 1/6 extra.

**SPECIAL BRAND NEW TRANSISTOR BARGAINS**

GET 15 (Matched Pair) 15/-; V13/10p, 10/-; OC7L 5/-; OC76 8/-; AP11 7/8; QP12 10/8. Set of Mullard 6 transistors OC44, 2-OC45, OC81D matched pair, OC8L 25/-.

**EDISWAN MAZDA**

PXA101 6/8; XA105 8/8.  
R.F.I. Pack: 1-PXA102 Mixer; 2-PXA101 I.F. Amp.; (Equip. OC44 and OC45). 10/8  
R.F. Amp. 2 Pack: 2-PXA101 I.F. 1-PXA102 Mixer. 12/8  
L.F.S. Pack: Consisting of PXB113 Driver. Matched pair PX171, mounted complete with heat sinks (Equip. OC81D and OC8L) ..... 12/6  
**ALL TRANSISTORS POST FREE**

**HARVERSON SURPLUS CO. LTD.**

**170 HIGH ST., MERTON, S.W.19** CHerrywood 3985  
Open all day Saturday Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station (Please write clearly)  
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.  
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE RIGHT HAND PAGE FOR MORE ITEMS

## DIGITAL COMPUTER

A simple digital Adder/subtractor using switches and lamps only. A fascinating demonstration of Binary Arithmetic. Full circuit, with notes on the Binary System 3/6, post free.

**MULTIMETERS.** Plus leaflet on request. EP10K, 10,000 o.p.v., 67/6, post 1/6; EP30K 30,000 o.p.v., 105/-, post 2/3; EP50K 50,000 o.p.v., 145/-, post 2/6. Leather case for EP30K. 17/-, EP50K. 25/-, post 1/3.

**1% High Stability Resistors—2/- each, 1W.** Full range 10Ω to 10MΩ. Many special non-standard multimeter values in stock.

**Audio-I.F.-R.F. Oscillator.** Simple transistor square wave circuit, multi-frequency output from audio up to 1.8 Mc/s. Variable amplitude. For 'Signal Injection' rapid receiver and amplifier testing, or for Morse practice. All parts except case and battery 10/-, post 1/-.

**PLANET INSTRUMENT CO.,**  
25(w) DOMINION AVENUE, LEEDS 2

## HARVERSON AMPLIFIER BARGAIN

Special offer of Manufacturers Surplus

### 2 VALVE GRAM AMPLIFIERS

Valves UY85 Rectifier and UCL82 Triode. Pentode giving 3 1/2 watts output. Overall chassis size (inc. valves) 5 in. high x 5 1/2 in. wide x 2 in. deep. Each amplifier new and tested and supplied complete with valves, 3 ohm output transformer and knobs for ton- and volume/on or control.

ONLY 37/6 P. & P. 3/6.

Can be used with 80v. motor tap or 1.5k. mains dropper 2/6 extra if required. Owing to the limited number available and the extremely high value we regret we cannot enter into any correspondence.

## BRAND NEW 3 OHM LOUDSPEAKERS

2 1/2 in., 12/6; 5 in., 12/6; 6 1/2 in. 15/-; 8 in., 21/-; 10 in., 26/-; 12 in., 27/6; (12 in. 15 ohm, 30/-). 10 in. x 6 in. 26/-  
Latest type E.M.L. 1 1/2 x 8 in. with high flux ceramic magnet, 11,000 gauss. Aluminium centre cone. 10 watts. 50 c/s to 10 Kc/s. 42/-.  
P. & P. up to 6 in. 1/6; over 6 in. 2/6 per speaker.

## TAPE DECKS

**COLLARO STUDIO DECK.** 3 motors, 3 speeds, push button control. Up to 7 in. spools. £10.10. P. & P. 5/6.

**B.S.R. MONARDECK.** Single speed, 3 1/2 in. per sec. Simple control uses 5 1/2 in. spools, £6.15.0 plus 3/6 cart. and ins. Tapes extra on both.

## BARGAIN OFFER CORNER

**ROLA CELESTION.** Approx. 9 in. x 6 in. x 3 ohm Middle register speaker. 10/6. P. & P. 2/6.

### MAINS TRANSFORMER

Drop thru type. Tapped primary 110v., 200v., 220v., 240v., 320/320v. at 80mA and 0.3A, at 3 amps. Generous core, stack size 3 1/2 x 2 1/2 x 1 1/2 in. Weight 1 1/2 lbs. ONLY 15/-. P. & P. 3/6.  
**ACC CRISTAL MIKES.** High imp. For desk or hand use. High sensitivity 18/6. P. & P. 1/6.  
**3L CRYSTA. SPICK MIKE.** Listed at 45/-. Our price 18/6. P. & P. 1/6.  
**T.O.C. SUPPRESSOR CONDENSERS.** 250v. 45.005 + .005 x 1. In tubular can 1 1/2 in. long x 3/4 in. dia. 2 for 3/-. Post free.

**TRANSFORMER DRIVER AND Q/P TRANSFORMERS.** (Tapped 3 ohms and 15 ohm output). Plus 4 suitable Transformers giving approx. 1 watt output 25/- P. & P. 2/6.  
**CONDENSERS.** 5,000 mF/d. 12v. wkg. Size 3 x 1 in. 1/4. 2/- each. P. & P. 6d. each.  
**T.V. or AMPLIFIER EDGE CONTROL PANELS.** Two 500K Lin. pots: one 500K Log; one D/P mains switch. Brand new 3/6 panel. P. & P. 1/-.  
**CONTACT COOLED BRIDGE RECTIFIERS.** 250v. at 125 mA. Size 1 1/2 x 1 1/2 x 1 in. 7/6. P. & P. 1/-.  
**MATCHED PAIR 24 VA. TAPED TRANSFORMER DRIVER AND OUTPUT TRANSFORMERS.** Stack size 1 1/2 x 1 1/2 in. Output taps, tapped for 3 ohm and 15 ohm output. 10/- pair. plus 2/- P. & P. Worth double.

**BRAND NEW PLESEY 12v. 4 pin non-sync. vibrators.** Type 12.1.43D. ONLY 8/6. P. & P. 1/6 each.

**TWIN TELESCOPIC AERIAL.** Comprising two 3-section heavily chromed rods. Closed 12 in. each extending to 32 in. each. Completely adjustable from vertical to hor. contal. Supplied complete with universal mounting bracket, approx. 36 in. of coax. and standard coax plug. Suitable for F.M. or T.V. 12/6 plus 2/- P. & P.  
**MALCOLM QUARTZ CRYSTALS** Types ZBB. Still available as previously advertised.

Harverson Surplus Co. Ltd.

## NEW VALVES!

Guaranteed Set Tested  
24-HOUR SERVICE

1R2, 1S, 1T, 3S, V4, DAF91, DF91, DK91, DL92, DL94, SET OF 4, 14/-.

DAF90, DF96, DK96, DL96, SET OF 4, 22/-.


0A2	3/9	DL84	5/-	PCL83	7/8
1D5	4/9	DL86	5/6	PCL84	7/8
1R5	4/3	DY86	6/6	PL36	7/8
1S5	3/3	DY87	7/8	PL81	6/6
1T4	2/3	EABC80	5/9	PL82	5/-
3S4	4/3	EBC41	8/3	PL83	5/-
3V4	5/-	EBF80	5/6	PL84	5/-
5Y3CT	5/3	FCC81	3/6	PY32	8/8
6KT6	1/3	ECC82	4/6	PY33	8/8
6X83	3/3	FC83	4/3	PY80	4/6
6Q7G	4/3	1CC84	6/3	PY81	5/-
6SL7GT	4/6	ECC85	8/-	PY82	4/11
6V6G	3/6	ECP80	5/9	PY83	5/6
6X7GT	6/3	LCF82	5/9	PY800	5/11
12K7GT	3/3	ECH42	7/3	U25	8/-
12X4GT	8/6	ECH81	6/-	U26	8/6
12Q7GT	3/3	ECL80	5/9	U81	8/-
20P4	13/3	ECL82	6/6	U301	11/-
25L6G	4/9	EP41	5/9	U801	15/-
30FL1	7/9	EP80	4/3	UABC80	5/-
35L6GT	6/-	EP85	4/6	UAF32	6/8
85A2	5/9	EP86	5/11	UBC41	8/-
CLC3	8/6	EP89	4/6	UBF80	5/6
DAC32	7/9	EL41	7/-	UCC84	7/11
DAF91	3/3	EL84	4/6	UCC85	6/-
DAF96	5/6	EX51	5/6	UF80	8/3
DF33	7/6	EX83	5/6	UCH42	8/9
DF96	2/3	EZ40	5/-	UCH81	5/9
DF96	5/6	EZ60	7/9	UCL82	7/6
DH77	3/6	EZ81	4/3	UCL83	9/3
DK32	7/6	KT41	6/6	UF41	8/3
DK31	4/3	PC84	5/6	UF89	5/9
DK82	6/9	PC89	8/8	UL81	8/9
DK96	6/-	PCF80	6/8	UL84	5/9
DL33	6/9	PCF82	6/-	URIC	5/-
DL35	6/6	PCF805	9/-	UY11	3/11
DL92	4/3	PCL82	6/3	UY85	4/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra. Office address, no callers.

**GERALD BERNARD**  
83 OSBALDESTON ROAD,  
STOKE NEWINGTON,  
LONDON, N.16.

FAMOUS FOR THIRTY YEARS FOR SHORT-WAVE EQUIPMENT OF QUALITY

## H.A.C. SHORT-WAVE KITS

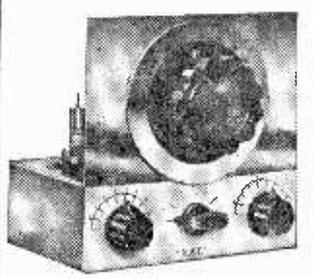

H.A.C. were the original suppliers of Short-Wave Receivers, Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army Bases, etc.

### IMPROVED 1965 RANGE

1-Valve model "CX", complete kit, Price 34/6

Customers say: "Definitely the best one-valve S.W. kit available at any price." This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and of course a all our products, fully guaranteed.

**FULL RANGE** of other kits still available including the famous model "K", price 72/-


Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

**H.A.C. SHORT-WAVE PRODUCTS**  
(Dept. T.H.), 44 Old Bond St., London W.1

# Lewis have the Cabinet for you

We can supply any cabinet to your own specification. These are only two examples of —THE LARGEST RANGE OF CABINETS IN THE COUNTRY

Equipment is also our speciality.

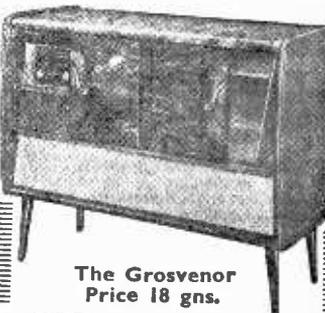

The Grosvenor  
Price 18 gns.



The Lowboy  
Price 27 gns.

## LEWIS radio

100(P365) Chase Side, Southgate London N.14, Tel 3733/9666

### FREE CATALOGUE

Send today for the new Lewis Catalogue

Designed to assist your choice of cabinet. Sent absolutely free. The new Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Choose from 49 different Models.

Please send your new free 2A page colour cabinet catalogue.

Name \_\_\_\_\_  
Address \_\_\_\_\_

BLOCK CAPITALS PLEASE

# TIME TESTED BY THE PIONEERS OF LOW PRICED KITS!

**MAKE 5 DIFFERENT TRANSISTOR RADIOS FOR 35/-**



**NO EXPERIENCE NECESSARY. No Soldering.** Only 3 connections for first radio to work. Just look, you get A.B.C. Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES - EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr. R. (M.D. of Londonberry, writes:— " . . . I received your components and I must say that I am very satisfied with them. I have it already set up! . . ." **COMPLETE HOME RADIO COURSE.** Originally 26 SEND ONLY 35/- plus 2/6 post etc. (C.O.D. 3/- extra).

**NEW RADIO ANYONE CAN BUILD IN 2-3 HOURS 19/6**



**EVEN THE OLDER CHILDREN BUILD THEM!** . . . no soldering—only 16 connections! they hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4" x 2 1/2" x 1 1/4". Many Testimonials: M.H. of Bradford, writes: " . . . I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here, and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them . . ." **Direct from Manufacturers to You. SEND 19/6 plus 1/6 post etc. (C.O.D. 2/6 ex.).** **PARTS AVAILABLE SEPARATELY**

**AMAZING CIGARETTE RADIO! ONLY 18/6**



Yes, a perfectly ordinary packet of cigarettes!—but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bustling testimonial file, Mr. D.H. of Huddersfield writes:— " . . . I have fitted the parts in and it is working wonderfully . . ." **ALL PARTS** including Semi-conductors, A.B.C. Plans, etc. **ONLY 18/6 plus 1/6 post, etc. (C.O.D. 2/6 ex.).** (Parts available separately).

## READ WHAT SATISFIED CUSTOMERS SAY

- |  |  |  |   |
|--|--|--|---|
| <b>R.C. of HARRINGAY</b> writes<br>Received with thanks Skyroma<br>... Very pleased. Working well. | <b>L.S. of LONDON W.8</b> writes<br>... given it a good try out<br>and I am very pleased with the results. | <b>D.R. of GLASGOW</b> writes<br>... it is a lovely little thing<br>and as clear as a bell.        | <b>J.W. of BRIGHTON</b> writes<br>... I have recommended your radio to many of my friends           |
| <b>B.M. of HARROGATE</b> writes<br>... I would like to thank you ... It is a real bargain.         | <b>S.B. of SOMERSET</b> writes<br>... delighted with this radio<br>... glad if you could send one more.    | <b>T.F. of STEVENAGE</b> writes<br>I would just like to say how pleased my son is with this radio. | <b>W.H. of MIDDLESEX</b> writes<br>Thank you for my dear little radio. It is a real treasure to me. |

## CONCORD ELECTRONICS

SEND 1/- FOR FULL LIST OF OTHER KITS AND STOCK RANGE LTD. (Dept. P.W.17) 9 Western Road, Hove, Sussex

# THE PEMBRIDGE COLLEGE OF ELECTRONICS PROVIDES TRAINING IN RADIO AND TELEVISION

## FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 27th April, 1965.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

**To:**  
**The Pembridge College of Electronics (Dept. P11)**  
**34a Hereford Road, London, W.2.**

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 \_\_\_\_\_

# SOUTH SUPPLIES

(ELECTRICAL LTD.)


Post orders to 95 Old Kent Road, London, S.E.1

95 OLD KENT RD., S.E.1  
72 BOROUGH HIGH ST., S.E.1  
90 HIGH ST., EDGWARE  
17 WOODFORD AVE., ILFORD  
291 HIGH ROAD, CHISWICK, W.4

BER 5810  
HOP 2125  
EDG 6751  
GRE 4815  
CHI 0154
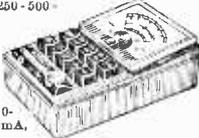
### ECCO Model S.E.37B

Push Button 20,000 O.P.V. Test Meter  
D.C. Volts: 0-1  
10-50-250-500-1000  
A.C. Volts 0  
-10-50-250-500-10000  
D.C. Current 0-50A, 10mA, 50mA  
Resistance 0-5K  $\Omega$ -5000K  $\Omega$ -5M  $\Omega$ .  
Inductance 50H-5000H. Capacitance 150pF-0.02  $\mu$ F. D.B. -20  $\Omega$  +22dB 20  $\Omega$  30dB. The simplest and most efficient meter on the market at **£5.15.0** P. & P. below its true value. **£5.15.0** P. & P.



### TECH. MODEL PV-58 VACUUM TUBE VOLTMETER

Finest design for stable and accurate measurement. 1% tolerance on all resistors. Large design 4in. 2000A meter for accurate readings 11 meg. ohm input.  
Ranges:  
-D.C.V. 0-1 5-5-15-50-150-500-1500V.  
+D.C.V. 0-1.5-5-15-50-150-500-1500V.  
A.C.V. 0-1.5-5-15-50-150-500-1500V. RMS  
0-1.4-1.5-40-140-1400-4000 P.P.  
Resistance: 2 ohms to 1000 megohm.  
Decibels: -10dB to +65dB.  
Operation: 220/240V A.C. Size 7 x 4 1/2 x 4in.  
Each tester is supplied brand new and fully guaranteed complete with probes and operating instructions.  
The finest value in testers available at only **£12.19.6** P. & P. Complete

### SUN ACE

Ready built 4 transistor new push button Superdix tape recorder circuit 4 transistors. Recording D.C. bias & track built in 2 1/2in. P.M. speaker. Recording time 17 mins. approx. on 200ft. tape. Batteries 1 U2-1 P.P.3. Complete with crystal microphone, personal car phone, 200ft. tape and test, spare spool carrying strap and batteries. Wonderful value. At only **£4.15.0** plus 4/9 P. & P. Fully guaranteed.



### ECCO Model S.E.550

100,000 O.P.V. PROFESSIONAL TEST METER  
Highest accuracy  
3% on D.C.V. -amps -ohms.  
4% on A.C.V. D.C. Volts:  
0-0.5-2.5-10-50-250 at 100,000 O.P.V.  
0-500-1000 at 55,000 O.P.V.  
A.C. Volts:  
0-2.5-10-50-250-1000 at 12,500 O.P.V.  
D.C. Amps: 0-100  $\mu$ A at 500mV, 0-250  $\mu$ A-2.5mA-250mA-10 at 150mA.  
Resistance: 0.20-2m-200k-20k. 100k-10k-100  $\Omega$  Centre Scale.  
Decibels: -20 to 62 (0dB-0.775V).  
**£7.19.0** P. & P. 5/-



### ECCO MODEL S.E.100 TRANSISTORISED VARIABLE D.C. POWER SUPPLY

Meter Ranges: Volt 0-20 V.D.C. Current 0-200mA 0-200mA Intermittent, 0-20V, 150mA continuously.  
Impedance Source: Current position, 3.3 ohms. Voltage position 0.2 ohms.  
Power Input: 220/240 V. Size 6 x 3 1/2 x 2 1/2in.  
Fuses: 0.5 amp slow blow in D.C. circuit.  
The extremely wide variable voltage range, low A.C. ripple and source impedance of the S.E.100 makes it a most satisfactory power supply to operate transistor radios, hearing aids, pre-amplifiers, instruments and other electronic devices under repair. The S.E.100 can be used in television and radio servicing, as an A.V.C. or voltage source as a D.C. filament supply operate relays, recharge small batteries and light electro plating as well as dentistry. **£6.10.0** P. & P. 4/6. Fully guaranteed and complete with test lead, croc. clips and operating instructions

### MINIATURE PUSH-PULL AUDIO AMPLIFIER

4 Transistor Output 2W r.m.w. Low and high gain inputs to operate 8  $\Omega$  speaker. Wonderful value **31/6** P. & P. Complete with operating instructions.

### A GENUINE 4 AMP BATTERY CHARGER For Only 49/6 P. & P. 4/6



### ECCO Model U.D.801 UNI-DIRECTIONAL DYNAMIC MICROPHONE

Dual impedance (600  $\Omega$ , 5k  $\Omega$ ). Frequency Characteristics: 100  $\Omega$ , 14,000 c/s. 13dB. Sensitivity: -75dB -3dB at 600  $\Omega$  -55dB  $\pm$  3dB at 50K  $\Omega$  0dB-1V/ $\mu$  bar. Directionality uni-directional (60  $\Omega$ , 7,000 c/s over 15 dB at 180 $^\circ$ ). This is a new and high class dynamic uni-directional microphone, very high in sensitivity and excellent in frequency characteristics, maintains high stability even against poor ambient conditions. Complete with 12ft. twin screened mic. cable. **£9.10.0** P. & P. Fully Guaranteed. **£9.10.0** P. & P.



### ECCO MODEL S.E.200 MINI-LAB TESTER

This remarkable meter has seven test instruments packed into one pocket size case which can be taken and used anywhere.  
Resistance Substitutes 100  $\Omega$  - 1K  $\Omega$  - 10K  $\Omega$  - 110K  $\Omega$  - 1M  $\Omega$ . Capacitance Substitutes .002mfd. - .005mfd. - .01mfd. - .1mfd. and 10mfd.  
R.F. Signal Generator. Frequency fixed at 446 Kc (adjustable to 700 Kc) output 35mV approx.  
Audio Generator Output 400 c/s. Output 35mV approx. D.O. and A.C. Volts. 4 ranges 0-15-50-150-500 volts at 400 O.P.V.  
R.F. Field Strength Indicator Frequency range 1 to 140 Mc. Antenna 5 sections. length 10 1/2in. Size 6 x 2 1/2 x 3 1/2in.  
The Mini-Lab is completely battery operated and suitable for quick checks in the service shop and Home Service calls **£8.19.6** each. Complete With Test Prods. and Battery Fully Guaranteed.




### FANTASTIC OFFER!

(Ready built and working). 4-speed Record Player. Incorporating a 24 watt output amplifier. 6in. 16,000 line speaker and the latest I.S.R. angle player unit. Beautifully designed wood cabinet covered with two-tone fabric in blue and grey. Mains voltage 220/250 volts A.C. only. Wonderful value at **£7.19.6** P. & P. 7/6


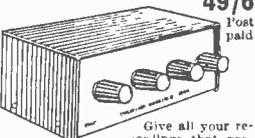
### ECCO 4-Ch. Transistorised MICROPHONE MIXER

49/6 Post paid  
Give all your recordings that professional touch. The Ecco mixer allows you to mix 4 signals such as—Mic-tape, records and tuner into a single output. Wonderful for groups, amateurs, recorders, etc. Guaranteed to give hours of pleasure.



### ECCO Model M54 FLOOR STAND

Height fully opened 55 1/2in Fully closed 33in. Three sections fully telescopic. 1 or 1 1/2 in. mic. adaptor Price **39/6** P. & P. Heavy cast iron base. Wonderful value.



MD 175 DYNAMIC MIC **45/-** P. & P. 2/-  
Sensitivity-55 Impedance dB at 1000 non-directional, latest American design.

### ACOS

Die cast, hand shaped body. Special offer 15/6 plus P. & P. 2/6.  
MULTI METER BARGAIN. ECCO Model 220S 4,000 O.P.V. on both A.C. and D.C. D.C. volts 0-5-25-125-500-2500. A.C. volts 0-10-50-250-1000. D.C. current 0-250  $\mu$ A-0-250mA. Resistance 0-10 K  $\Omega$ -0-1meg.  $\Omega$  Decibels -20 to +22 dB. Meter size 4 1/2 x 3 1/2in. Complete with test prods and battery. Wonderful Value at 63/- plus 3/- P. & P.

### RONETTE BINOFLUID B.F.40 STEREO CARTRIDGE

Free. Rev. 30-12,000 c/s. Sensitivity 40mV/100mV. Load 1m  $\Omega$  100  $\mu$  F Complete with sapphire Stylus. OUR PRICE 12/6 each. P. & P. 1/-.

### RONETTE STEREO O.V.S. TURNOVER CARTRIDGE


with 2 sapphire Stylus. OUR PRICE 19/6 each. P. & P. 1/-.

### NEW!!! NEW!!!

CM8—High Impedance Crystal Mic. with built-in on/off switch. Complete with Table Stand, Plug-in Mic. lead and neck holder, all in a wonderful satin chrome finish. **★ VALUE AT 33/6** Plus 1/9 P. & P.
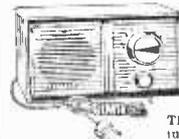
### VANTONE MAINS RADIOS

Ready built 5 valve superhet with built in Ferrite tuning bar. **£3.15.0** plus 3/9 P. & P. Fully Guaranteed.



This wonderful little radio will receive all stations on Med/ware loud and clear inc. Latest country. Ideal for bedrooms, kitchens or as a second mains radio.

### EHRECORDER



4 Transistor Tape Recorder. Ready built. Easy to operate single lever function control. 200mW output complete with microphone—3in. Tape—Spere 800l—Personal earpiece and batteries. Wonderful value **£4.19.6** plus 5/- P. & P.

# WEYRAD

## TRANSISTOR COILS

The P50 series remain the most popular and widely used components for Medium and Long-wave Transistor Superhets:—

P50/1AC Oscillator Coil for 176 pF tuning ... ..	5/4 ea.
P50/2CC 1st & 2nd I.F. Transformers ... ..	5/7 ea.
P50/3CC 3rd I.F. Transformers ... ..	6/- ea.
All mounted in individual cans $\frac{1}{16}$ in. diam. x $\frac{3}{4}$ in. high.	
RA2W Ferrite Rod Aerial 208 pF Tuning ... ..	12/6 ea.
LFDT4 Driver Transformers ... ..	9/6 ea.
OPTIA Output Transformers ... ..	10/6 ea.
PCAI Printed Circuit Panel ... ..	9/6 ea.
Constructor's Booklet ... ..	2/- ea.

## VALVE RECEIVER COILS

Our individual "H" type iron-cored coils are without equal for the construction of a wide range of receivers. For the simplest T.R.F. sets covering one or more wave-bands the Aerial and H.F. Transformer coils are ideal. The standard superhet circuit using the ever-popular triode-hexode frequency change layout would employ the Aerial and Oscillator coils and the coverage can be selected from 7 different bands ranging from 12.5 to 2,000 metres. For a really high-performance receiver an R.F. stage can be added by using the Aerial, H.F. Transformer and Oscillator Coils and a circuit is provided illustrating such a layout.

H Coils 3/9 each.

## WEYMOUTH RADIO MANUFACTURING CO. LTD.

REGENT FACTORY, SCHOOL STREET,

WEYMOUTH, DORSET



### AERIAL EQUIPMENT

**TWIN FEEDER**, 300 ohm twin ribbon feeder similar K25 6d. per yard K35B Telecon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

**COPPER WIRE**, 14G., H/D 140ft. 22/6; 70ft. 11/6, P. & P. 2/6. Other lengths pro rata.

**AERIAL INSULATORS**, Shell type 2in. 9d. Plus Postage. **CERAMIC FEEDER SPREADERS**, 6in type F.S. 10d. each. P. & P. 2/-.

**CERAMIC "T" PIECES**, Type A.T. for centre of dipoles 1/6 each. P. & P. 1/-.

**2 METER BEAM 5 ELEMENT W.S. YAGI**. Complete in box with 1-2 1/2in. mast head bracket. PRICE 49/-. P. & P. 3/6.

**SUPER AERIAL CABLE**, 75 ohms 300 watts very low loss 1/8 per yard. P. & P. 2/-, 50 ohms, 300 watt coax very low loss 1/9 yard. P. & P. 2/-.

**ABSORPTION WAVEMETERS**, 3.00 to 35.00 Mc/s in 3 switched bands. 3.5, 7, 14, 21 and 28 Mc/s. Ham bands marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. 22/6 post free.

**VARIABLE CONDENSERS**. All brass with ceramic end plates and ballrace bearings, 50 pF, 5/9, 100 pF, 6/6, 160 pF, 7/6, 240 pF, 8/6 and 300 pF, 9/6. All fitted with rear extension for ganging. P. & P. 1/-. Also Flexible Couplers 1/- each.

**SETS OF VALVES** for AR88 (14) £3.10.0 post free.

**METERS**. 3 1/2in. with 2 1/2in. scale, 0-10 mA, 15/-; 0-100 mA, 15/-, P. & P. 1/6.

**THERMO**, 2 1/2in. round 0-2.5 amp, 7/6 each. P. & P. 1/6.

170-172 CORPORATION ST.  
BIRMINGHAM 4

Telephone CEN 1635

TELEPHONE  
HANDSETS  
**15/6**  
pair

G. P. O. pattern House to Workshop, garage, inter-office, etc. Works off any small battery. P & P. 4/6.

**DUKE & Co. (LONDON) Ltd.**  
621/3 Romford Road, Manor Park, E.12  
Liverpool St.—Manor Pk.—10 mins.  
Phn: ILFord 6001/2/3 Stamp for Free List


VALVES 9d. each, 1,000's available. Send for List.  
CONDENSERS, 100—10/-, New. Assorted electrolytics and pFs. P. & P. 2/6.  
V/CONTROLS, 20—10/-, A selection of types and sizes. P. & P. 2/6.  
SPEAKERS, 7/8, 6in., 8in., 7 x 4in. and 8 x 3in. Ex. ind. Salvage. P. & P. 2/3.  
NEONS, 25 box 2/-, (R.B.C.D.P. fittings) Mains tester and visual reminders. P. & P. 1/-.

### EX-RENTAL T.V. SETS

Coloured FREE LIST. Demonstrations daily from our large selection

12 months' written guarantee

Channels for all areas

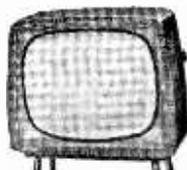

17in. £11.10.0  
14in. £7.10.0

Carr. 14in. 20/-  
17in. 30/-  
Personal Collection advised

AERIALS, BCC/ITA combined Loft and room aerials—from 25/-, BBC2/UHF and colour aerials—from 29/6. SEND FOR FREE LIST.

### EX-MAINTENANCE TESTED TUBES

17in. — 35/- 14in. — 15/-  
Carriage 5/- Satisfaction Guaranteed

### RE-GUNNED TUBES

Guaranteed one year  
Carr. 10/6. Add 10/- refundable on OLD TUBE  
(110° Tubes in stock)



21 in. 99/6  
17 in. 79/6  
15,14  
12 in. 59/6



The PUNCH you need!

**SOLE PUNCHES**

Instant Type	diameter	...	...	6/10 ea.
Screw-up Type	diameter	Toggle switch	...	8/6 "
"	"	B7G	...	8/6 "
"	"	B8A, B9A	...	9/6 "
"	"	"	...	10/2 "
"	"	"	...	10/8 "
"	"	"	...	11/8 "
"	diameter Int.	Octal	...	13/4 "
"	"	"	...	16/2 "
"	"	"	...	18/10 "
"	"	B9G	...	21/8 "
"	"	"	...	24/4 "
"	"	Meter	...	33/2 "

Complete Set £9.3.6.

No extra charge for postage and packing in the U.K.

**Oliver & Randall Ltd**

Dept. 7  
9 KELSEY PARK ROAD  
BECKENHAM, KENT  
Tel.: Beckenham 8262

**TRANSISTOR SPECIFICATIONS AND SUBSTITUTION HANDBOOK**

15/- Postage 9d.

**PRACTICAL TAPE RECORDING** by P. J. Guy, 7/6, Postage 6d.

**SERVICING TRANSISTOR RADIOS & PRINTED CIRCUITS** by L. Lane, 42/-, Postage 1/-.

**THE TRANSISTOR RADIO HANDBOOK** by D. L. Stoner and L. A. Earnshaw, 44/-, Postage 1/-.

**THE AMATEUR RADIO HANDBOOK**. An R.S.G.B. Pub.: 34/-, Postage 2/-.

**RADIO AND TELEVISION TEST INSTRUMENTS** by G. J. King, 25/-, Postage 1/-.

**RADIO, TELEVISION AND ELECTRICAL REPAIRS** by R. C. Norris, 50/-, Postage 2/-.

**RADIO CONTROL MANUAL** by E. L. Safford Jr., 25/-, Postage 1/-.

**COMPLETE CATALOGUE** 1/-.

BRITAIN'S LARGEST STOCKS OF British and American Technical Books

**THE MODERN BOOK CO**

19-21 PRAED STREET  
LONDON, W.2

Phone: PADDington 4185  
Open 6 days 9-6 p.m.

**SENSATIONAL HALF PRICE OFFER!**

THE FAMOUS 'Continental' **RADIOGRAM** AT **HALF PRICE!**

**Only £29-19-6**

- Easily fitted
- No soldering or Technical knowledge necessary
- Fits almost any cabinet with minimum trouble
- Modernises your old radiogram
- 3 wave bands, Medium Long and Short
- Complete with two 10in. elliptical Hi Flux loudspeakers
- And Hi Fi 4-speed stereo/mono automatic record changer
- Built-in ferrite rod aerial
- Piano key switching
- Luxembourg and Caroline received in full strength
- Listen to U.S.A. Russia, Africa, Canada and even Australia in your armchair
- Unique Lewis Radio 365 day guarantee, even on all the valves
- All British make
- Everything brand new and fully guaranteed

**SPECIAL** terms available of £3 deposit followed by 18 monthly payments of £1.14.6, postage and packing 15/- extra.

**INDIVIDUAL CABINETS SUPPLIED ON REQUEST**

**LEWIS radio**

Avoid disappointment send cheque or P.O. immedia tely LEWIS RADIO (P.W.35), 100 CHASE SIDE, SOUTH-GATE, LONDON, N.14. Telephone: PAL 3733/9666

**RADIO CLEARANCE LTD.**

27 TOTTENHAM COURT ROAD, LONDON W.1. Telephone: MUSeum 9188  
Trade enquiries invited. The oldest component specialists in the trade Est. 35 yrs

**LOUDSPEAKER BARGAINS STILL AVAILABLE**

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

**SCHEDULE OF LOUDSPEAKERS AVAILABLE**

Diameter Gauss Imped.				Diameter Gauss Imped.				Diameter Gauss Imped.							
in inches		lines		ohms		Price		in inches		lines		ohms		Price	
2 1/2	7000	80	8/-	3 1/2	7000	35	8/8	5	7000	3	8/8	5	7000	3	9/-
2 1/2	7000	85	8/8	3 1/2	9500	50	10/8	5	7000	25	11/6	5	8500	3	9/8
2 1/2	7000	80	8/-	4	6000	35	10/8	5	9500	3	10/8	5	9500	15	12/8
3	8500	3	10/-	4	7000	35	11/-	5	9500	3	11/8	5	8500	25	10/8
3	6000	5	8/6	4	9500	35	11/6	5	9500	15	12/8	5	8500	25	10/8
3	7000	5	5/-	4	4Wtr.10000	3	11/8	5	8500	25	10/8	5	9500	35	11/8
3	7000	35	9/6	4	9500	15	12/-	5	9500	35	11/8	5	8500	3	11/8
3 1/2	9500	3	10/8	5	6000	3	8/-	6 1/2	6000	3	11/8	6 1/2	6000	3	11/8
3 1/2	9500	8	10/8												

ALLOW 2/- each Speaker for postage and packing and handling charge and please specify the exact requirements—the nearest available will be sent.

**SELECTED BARGAINS**  
Beautifully geared AM/FM 2 gang Condensers, 4/6; AM/FM IFT'S 465 kc/s and 10.7 Mc/s 4/8 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; 3 watt Stereo Amplifiers, complete, ready to switch on, 79/8; Sentercell rectifiers R3/2D-D3-2-1-Y, 2/6 each. DIODES—0A79, 0A90, CG46H, GD10, 2/- each.  
TRANSISTORS: OC45 4/6, PXA101, 3/9, AF115, 4/6. Sub min. Germanium diode 1/3, M1 diode 9d, each. Silicon diodes, 200 p.i.v. 20V mA, 1/- each, 400 p.i.v., 330mA, 2/6 each please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogue—our stocks move too quickly! Kindly make provision for additional postage and packing charge to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.

**A QUALITY RECORD PLAYER FOR 10 GNS !!  
(FULLY AUTOMATIC) ASSEMBLED in 30 MINS.**

**REF: NO. K116 Fully Auto**

Cabinet Size 16 x 15½ x 8. Complete Kit 10 gns. plus P.P. 6/6 includes very latest BSR.UA25 Superlim. Tasteful cabinet in 2-tone Rexine, Vynair and Gold/White Trim. Cut out Motor Board 7 x 4 P.M. Loudspeaker. Printed circuit amplifier. Double wound Mains TX A.C. 240 volts. Entirely safe and reliable. Separate switch, tone and volume controls. Six simple connections to make, FULL instructions supplied. Guaranteed 12 months. Complete down to the last washer !!

**REF: K82 De Luxe Version of above**

Cabinet 17 x 15½ x 8 of pleasing design. Includes 8 x 5 top quality Loudspeaker and Hi-Fi performance Amplifier. 11½ gns. plus P.P. 6/6.



**SIEMENS RECTIFIERS**

B.30 C.400	9/4	B.250 C.100	14/3
B.30 C.600	13/6	B.250 C.125	15/5
B.30 C.1000	22/6	B.250 C.150	17/7
E.250 C.50	8/3	B.250 C.250	22/4
B.250 C.75	13/6	E.250 C.300	25/-
E.250 C.85	11/3	B.300 C.120	24/2

**WESTINGHOUSE RECTIFIERS**

FC.31 (14RD-1-2-8-3)	.. .. .	26/8
FC.116 (18RD-1-1-16-1)	.. .. .	7/8
FC.117 (18A-1-1-8-2)	.. .. .	12/6
FC.118 (18RD-1-1-8-1)	.. .. .	5/-
FC.124 (18RD-2-2-8-1)	.. .. .	16/4
FC.130 (18RD-2-2-10-1)	.. .. .	19/-
FC.141 (16RC-1-1-16-1)	.. .. .	10/8
FC.142 (18RD-2-2-8-1)	.. .. .	12/10
FC.144 (16RD-2-2-10-1)	.. .. .	14/8
FC.146 (18RD-2-2-8-1)	.. .. .	12/-
FC.148 (16RC-1-1-8-1)	.. .. .	4/10
FC.150 (16RE-2-1-8-1)	.. .. .	10/3

**CHARGER RECTIFIERS**

12 volt 1 amp contact cooled..	.. .. .	5/6
12 volt 1 amp fin type	.. .. .	8/9
12 volt 2 amp fin type	.. .. .	7/8
12 volt 4 amp fin type	.. .. .	12/8
12 volt 6 amp fin type	.. .. .	16/-

**TRANSISTORS**

AA120 4/6	AF128 10/-	OA81 1/9
AC113 (OC81D) 5/6	AF127 9/6	OA90 1/9
A154 (OC81) 5/6	AR1 100 PIV 600ma 4/-	QA2207 8/-
AC155 (OC71) 4/-	BY100 7/8	OC26 8/-
AC156 (OC75) 6/6	BY101 6/-	OC35 12/-
AC157 (NKT1713) 7/-	BE114 6/-	OC36 17/6
AD140 25/-	GE113 6/9	OC42 8/-
ADT140 15/-	GE114 6/8	OC44 5/-
AF114 11/-	GE115 9/6	OC70 6/-
AF115 10/6	GET116 17/-	OC71 4/3
AF116 6/-	GET173A 3/-	OC72 5/6
AF117 5/-	MA*201 3/8	2 x OC72 18/-
AF118 20/-	MA*120 7/9	OC74 8/-
AF119 11/-	MA*121 8/6	OC75 5/6
AF120 10/6	NKT171 10/-	OC81 5/6
AF121 2/-	.. .OC44 5/-	OC82 10/-
AF122 10/6	NKT1404 (OC35) 10/-	OC83 4/-
	OA70 2/-	OC139 8/-
	OA79 2/-	OC169 6/6
		OC170 8/8
		OC171 6/-

**REF: K500 Single Record Player  
Only £8.00 + P.P. 6/6**

Cabinet 14 x 13 x 6½. N.B. Plays 12in. record with Lid closed. Complete with T.U./2. Single Record Player. Other details as K.116.


**SETS OF TRANSISTORS**  
Set No. 1: comprising OC44, 2 x OC45, OC81, matched pair OC81, 20/-.  
Set No. 2: comprising OC81, matched pair OC81, 12/6.

**CATALOGUE**  
Our latest 1964/65 Catalogue is now available. Copies have been sent to many of our regular customers. If you have not received your copy please drop us a card. Please send 1/- in stamps. Wholesale terms to Schools, Universities and Business Houses. Trade Catalogue now available. Please apply on business letter heading.

**TERMS:** Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d. Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

**ALPHA RADIO SUPPLY CO., 103 LEEDS TERRACE, WINTOON ST., LEEDS 7**

**GUITAR AMPLIFIERS  
WITH TREMOLO**

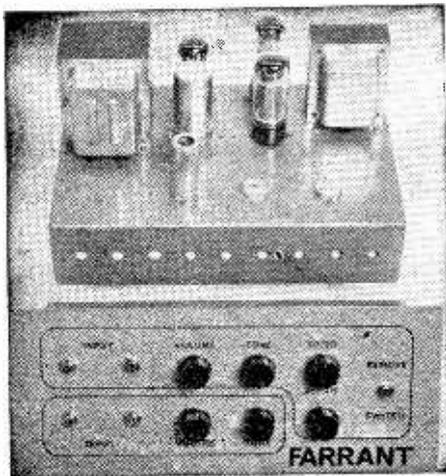

Our latest 30 watt Amplifier. For cabinet fitting 17 GUINEAS plus 15/- carriage Other models still available

Send for details. Credit Terms Arranged

**STROUD AUDIO**  
PAGANHILL LANE, STROUD, GLOS. Stroud 783

**MARCONI TF-643B.** Absorption wavemeters. 20 to 300 Mc/s in 4 ranges. Individual calibration charts. Accuracy 1%. 50µA 2½in. panel meter. No power supply required. New cond. in original transit cases. £5.19.6. Carr. 7/6.

**AERIALS VERTICAL 3ft.** Ten heavy duty (Screw together) rods (3ft. x ¼in.) separate 14ft. wired through whid. base, guy ropes, insulators, hammer etc. In canvas golf-type bag. Unused. 59/6. Carr. 10/6.

**MARCONI TF-588/3.** Portable receiver tester. Combined Sig. Gen. (70 Kcs to 70 Mc/s) and output meter. Crystal checks (500 Kcs and 5 Mc/s). A.C. mains operation. Modern Eqpt. Tested and guaranteed. Inst. Book and Oct. £39.10.0 Carr. 10/-.

**SILICON RECTIFIERS.** Type BY100 (4in. x ¼in.) will handle 250 volts up to 500 mA. Replaces any TV metal rectifier. BRAND NEW—not seconds. 7/-.

**VHF COMMUNICATIONS RECEIVER R-1949.** This is the Air Force version of the well-known Hallicrafters S-27 or S-36. Covers 27 to 145 Mc/s. in three wavebands. It is complete with all valves, stabiliser, "S" meter etc., but requires an external power supply to give 250 volts HT and LT. Picks up police, amateurs etc. and could easily be used for mobile operation. Tested and in good condition. £17.10.0. Carr. 10/-.

**AR 88 VIBRATOR PACKS.** For 8V. operation. Complete with vibrator and OZ4 rectifier. NEW in original cartons. 15/- P. & P. 5/-.  
**AR 88 SPARE VALVES.** Complete Set of BRAND NEW individual boxed original valves (1-4), 50/- Plus 2/6 P. & P.

**MOVING COIL PHONES.** Finest quality Canadian with Chamois ear muffs and leather covered headband. With lead and jack plus. Noise excluding, supremely comfortable. BRAND NEW ..... £2/6, post 1/6.

**MAGNETIC COUNTERS (ex. GPO).** 4 figures to 9.999. Coils 500n for 24V. operation. Tested. (No reset). 5/- each. P. & P. 1/6. SPECIAL OFFER! 10 for 30/- P. & P. 6/-.

**MICRO AMMETER.** 0-500µA. Made by R.C.A., Weston Westinghouse and other famous American manufacturers. Circular 2½in. flush panel mounting. Dials are engraved 0-15 0-600 volts. As used in the American version of the "19 SET". TESTED AND GUARANTEED 15/-.

**HEAVY DUTY TRANSFORMER.** Input 220 to 250 volts A.C. mains (tapped every 5 volts). Output 50V. at 15 amps. A really rugged job, very conservatively rated. Size 7½ x 5½ x 7in. Weight 28 lbs. ONLY £5.19.6. Carr. 7/6.

**CHARLES BRITAIN RADIO LTD.**  
11 UPPER SAINT MARTINS LANE, LONDON W.C.2  
TEMPle Bar G545  
Shop hours 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday

# NEW not just 1 but 2 NEW TUNER-AMPLIFIERS

model 127 Stereo £37.10.0

model 127 Mono £26.10.0




Armstrong

Optional case (both models)  
TEAK & VINYL HIDE £3. 10. 0  
For full details, technical specifications and  
list of over 300 stockists, post coupon or  
write mentioning PW. 3.65.

Name .....

Address .....

PW. 3.65

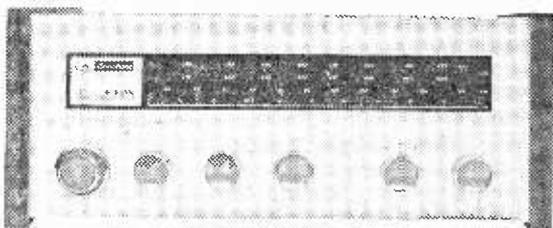

ARMSTRONG AUDIO LTD. WALTERS ROAD, LONDON N7

Wright + Connor

## NEW CONSTRUCTORS' PARADISE — FAST POSTAL SERVICE

### ADASTRA 3 WATT AMPLIFIER



Recently introduced highest quality ready built British Made Amplifier. Separate Bass, Treble and Volume Controls. Separate high quality finished front panel. Output 3 watts into 3 ohms. Excellent mains transformer 200/250 volts AC input Enamelled chassis. Size 9 x 7 x 4in. Price 99/6. Post and packing 3/6.

### LOUDSPEAKERS

Fatons make 10 x 6in., 3 ohms brand new. Our price whilst stocks last, only 29/6. Post and packing 2/6. Heavy duty 15 watts, 12in. Loudspeakers. Heavy die-cast chassis. 8 or 15 ohms. Speech coil. Frequency response 30 to 14,000 Cycles. Price 25/10.0.

### FAMOUS LINEAR AMPLIFIERS

Stereophonic Amplifier. Two channel high impedance input. Sensitivity is high enough to load fully the output when connected to practically any make of stereo head. Can also be used for normal heads. Output as stereo in excess of 3 watts, and as monaural over 6 watts. Separate volume tone and balance controls for 3 ohm speaker. Size 9 x 7 x 5in. Price 27.19.6. Post and packing 3/6. Attractive matching protective cover 25/-.

### LINEAR DIATONIC 10 WATT HI-FI including pre-amplifier

Ultra linear push-pull. Two separate controlled input sockets for gram-needle etc. Two different inputs can be simultaneously applied. Maximum output exceeds over 14 watts. Separate control for Bass, Treble and Volume. Output 3 or 15 ohms. Reserve power supply for tuner etc. Price 213.2.6. Post and packing 4/6. Chrome handled protective cover available at 25/-.

### SENSITIVE CRYSTAL SET



Ready built and complete with personal earphone etc. Size 3 1/2 x 2 1/2 in. in beautiful plastic case. Price 15/- . Post and packing 1/6. (Ideal Christmas Present).

### MAINS RADIOS 5 Valve Superhet Circuits


Attractive quality plastic cases. 200/250 volts. Medium waves coverage. Price 97/6. Post and packing 2/6. Makes ideal Christmas present (All waves models 7 kms).

### QUALITY MULTI- METER



Pocket size 4 x 2 1/2 x 1 1/2 in. High sensitivity of 1,000 ohms per volt on AC as well as DC ranges: 0 to 15 volts, 0 to 150 volts, 0 to 1,000 volts. Same range when switched to AC. Current range 0 to 150 mA. Resistance 0 to 100 K ohms. Weight only 8 oz. Sturdy instrument complete with test probes, battery, instructions etc. Price 35/- . Post and packing 2/6.

### TRANSISTORIZED SIGNAL INJECTOR

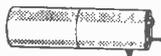

Complete with batteries, extra long probe and full instructions for fault tracing on radios or television sets (shows alternate black and white bars which inserted into a television). Will pay for itself over and over again in fault finding. Price 37/6. Post and packing 2/6.


### PP3 BATTERY CHARGER

Same size as PP3 battery it either replaces it by plugging into the mains or charges your PP3 Battery. Boxed with full details etc. Price 17/6. Post and packing 1/6.

### SLIMLINE CRYSTAL MICROPHONE

With aluminium die cast casing with satin chrome finish. Incorporates On/Off locking switch. Complete with cable, chrome stand holder etc. etc. Sensitivity —32 dB. Frequency Response 50 to 10,000 Cycles. Termination of over 500,000 ohms. Price 47/6. Post and packing 3/-.

### FOUR TRANSISTOR AMPLIFIER

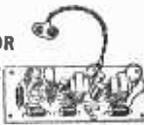

(Ready built) only 4 x 1 1/2 x 1 1/2 in. Includes own output transformer with standard 3 ohm output, and four transistors giving nearly 1 watt output from standard 9 volt PP3 type battery. Complete with full instructions. Price 37/6. Post and packing 2/-.

### TRANSISTOR RADIOS

6 Transistor covering Medium waves beautifully boxed and complete with all extras. Price 69/6. Post and packing 2/6. (Two wave models 98/6).

CONCORD ELECTRONICS LTD.

(Dept. P.W.J. 3) 9 WESTERN ROAD, HOVE, SUSSEX.  
C.O.D. 3/- ex. Catalogue of every item in stock 1/- post free MAIL ORDER ONLY.

**We are stockists for VEROBORD**  
The perforated Copper Board for Modern Circuitry

- .15 x .15 pitch. .. 3/-
- 2.5 x 3.75 .. 3/8
- 2.5 x 5 .. 3/8
- 3.75 x 5 .. 5/-
- Special Verobords, Pkts. 200 .. 14/-

P. & P. on all items 1/- S.A.E. for price list.

**TRANSISTORISED MORSE OSCILLATOR**

Fitted 2 1/2in. Moving Coil Speaker. Uses type PP3 or equiv. 9 v. battery. Complete with latest design Morse Key, 22/6, plus 1/6 P. & P.

**TRANSISTORS—1st Grade only, no seconds, no rejects, no surplus.**

OC23	17/-	OC77	9/-	GET105	10/-
OC29*	18/-	OC81*	8/-	GET573	12/6
OC41	7/-	OC83*	8/-	ZNT06A	17/6
OC43*	6/8	OC39	12/-	2N458	20/-
OC45*	5/-	OC140	19/-	SB345	7/6
OC71	5/-	OC171	10/6	AC107	14/6
OC72*	7/-	OC200	10/6	AF114	11/-
OC73	6/-	OC201	21/-	AF115	10/6
OC75	7/-	OC203	14/-	AF116	10/6
OC78	8/-	GET104	8/-	AF117	9/6

\* Available in matched pairs.

**SIEMENS SEALED H/S RELAYS**

H96A	2.2 ohm P2.2 ohm, new	12/6
H96B	50 ohm f50 ohm, new	12/6
H96C	145 ohm P145 ohm, new	12/6
H96D	500 ohm f500 ohm, new	12/6
H96E	1700 ohm P1700 ohm, ex-equip.	16/6

**BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.**

The ideal instrument for workshop, lab, or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.



**VARIABLE VOLTAGE TRANSFORMER £4.10.0**

Output 230 v. A.C. Output 0-250 v. at 1 amp., fully included, new. Also available 2.5, 4, 5, 8, 10, 12, 20, 37.5 and 50 amp. Write for details.

**LIGHT SENSITIVE SWITCH**  
Kit of parts, including ORP 12 Cadmium Sulphide, Photocell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP 12 including circuit, 10/6 each, plus 1/- P. & P.

**D.C. AMMETERS**  
0-15 amp. D.C. M-Coil 2 1/2in. round .. 12/6  
0-5 amp. D.C. M.I. 2 1/2in. round .. 11/6  
0-30 Microamp. sub-min. 1 1/2in. dia. Scaled 0-1 milliamp. .... 21/-  
Postage extra.

**ULTRA VIOLET BULBS**

Easy to use source of UV for dozens of practical and experimental uses. 12 volt 36 watt AC/DC SBC 6/8. P. & P. 17-. 12 volt 60 watt AC/DC SBC 8/6. P. & P. 17-. Transformer to suit the above: Input 230-240 A.C. Output 12 Volt A.C. 36 watt, 16/6. P. & P. 2/6. Input 200-240 A.C. Output 12 volt A.C. 60 watt, 22/6. P. & P. 3/6.

Set of four colours **FLUORESCENT PAINT**. Orange, Yellow, Green and Red, in 1oz. tins. Ideal for use with the above Ultra Violet Bulbs. 9/6. P. & P. 1/6

**VAN DE GRAAFF ELECTRO-STATIC GENERATOR**

fitted with Motor drive for 230 v. A.C. giving a potential of approx. 50 000 volts. Supplied absolutely complete, including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £6.6.0, plus 4/- P. & P.

**A.C. VOLTMETERS**  
0-15 v. A.C. M.I. 2 1/2in. F.L. .... 12/6  
0-200 v. A.C. Rect. M-Coil 3 1/2in. Type W23 45/-  
0-300 v. A.C. M.I. 2 1/2in. F.L. .... 22/6  
0-300 v. A.C. Rect. M-Coil 2 1/2in. .... 29/-  
0-300 v. A.C. Rect. M-Coil 3 1/2in. Type W23 55/-  
**A.C. AMMETERS**  
0-1, 0-5, 0-10, 0-15, 0-20 amp. F.R. 2 1/2in. dia. All at 21/- each.

**SERVICE TRADING CO**

All Mail Orders. Also Callers at:  
47-49 High St., Kingston-on-Thames  
Telephone: Kingston 9450 Closed Saturday

Personal Callers only: 9 Little New-  
port St., London, W.C.2. Tel. Ger 0578  
(off Leicester Square)

**PADGETTS RADIO STORES**  
OLD TOWN HALL  
LIVERSEDGE, YORKS  
Telephone: Cleckheaton 2888

**USA Bomb Computers** in original transit case, full of gears, motors, vidior counter, gyro, etc., 37/-, carriage 10/-.  
**PCR**, 12 volt Vibrator Pack, in original packing case, 25/-, carriage 8/-.  
**RAF Sighting Heads**, Complete with lamp, lens, etc. No details. Packed in original metal case, 15/-, carriage 10/-.  
**Single Phase 240 volt, 1400 r.p.m., 1/2 h.p. motor with pulley, 28/-, less pulley 24/-, fully guaranteed, ex washing machine. Carriage 8/6.**  
**One sixth h.p. motor, 240 volts, 15/-, post 6/6.**  
**New Indicator Unit, CRT 106**, complete with two tubes, type VCRX393 and VCRX298 plus 21 small valves, relays removed, 57/-, or less valves 32/-, carriage 10/-, Sorry no details on the unit.  
**New 12in. Speakers with built-in Tweeter**, 15 or 3 ohms, 28/6, post paid.

**P.M. Speakers**, all 3 ohms ex TV sets. 6in. round 6 x 4/25 and 5in. 3/-, post 2/6 for 20/-, Post paid. 8in. round 6/-, post 2/-, 7 x 4in. 5/-, post 2/-.

**VALVE LIST**

Ex equipment.	3 months guarantee		
EL91	1/6	U801	8/6
ELC180	2/-	U231	5/-
ECC82	3/-	U282	5/-
EY51	2/6	U283	5/-
EY86	5/-	KT36	5/-
EBF80	4/6	5U4	4/-
EB91	9d.	6V6GT	4/-
EL38	5/-	8X5	4/-
EF91	8d.	6C325	5/-
6F1	1/-	6P25	3/6
6F14	5/-	6U4	4/-
6F15	5/-	PY33	6/-
10C2	5/-	Y80	3/-
10F1	1/-	PY41	3/-
10F13	5/-	PL81	4/-
10P14	5/-	PL82	3/-
20D1	2/-	PL83	3/-
20L1	5/-	PL33	3/-
20P3	4/-	PY82	3/-
20P4	8/6	PCF80	4/-
		PCC84	4/-
		PCL82	5/-
		PCL84	5/-
		PL36	5/-
		V25	5/-
		VR150/30	3/-
		1T4	1/9
		12AT7	3/6
		6C46	1/6
		6X4	3/6
		AR12	1/6
		807	5/-
		EF50	1/-
		Doz. 8/-	
		113	1/3
		6K7	10/-
		Doz. 10/-	
		6V8	1/9
		Doz. 18/-	
		6KB	1/9
		Doz. 18/-	

**Breaking Up Mark III Type 19 Sets**, Meter 500 micro-amp., 5/-, post 1/9. Jack Socket, 1/-, post 6d., doz. 10/-, post paid. Jack, 1/6, post 6d. Toggle Switch, metal, 6d., post 6d. Doz. 10/-, post paid. Relay type 300, 1/9, post 1/9. Doz. 20/-, post paid. Any other spare send 2/- plus post to cover.  
**Reclaimed Tubes**, 6 months guarantee. 14in. Mullard and Mazda 17/-, carriage 10/-, 17in. 30/-, carriage 10/-.

**2 METRES 4**

The thrills of VHF Amateur Radio can now be yours for as low as 42/6 complete kit (by post, carriage and packing 2/6 extra). Tuning range 70-150 Mc/s. Stamped addressed envelope for free copy of literature and full details. Newcomers to Short-Wave Radio ask for details of the famous "Globe-King" kits and receivers. Home and Overseas Sales.

**JOHNSONS (Radio)**  
St. Martins Gate, Worcester

**COMMON CORE SERIES**

The following is one of the many letters of appreciation that we have received in connection with this series.

'Some time ago I was fortunate in ordering a set of "Basic Electronics" and now that I have had time to read and digest their contents I should like to record the pleasure and gratification I derived from their simple and unique presentation of what has hitherto been regarded as a difficult subject to grasp. Indeed I have no hesitation whatsoever in wholeheartedly recommending them to my friends, the only regret being that they were not available years ago. I should now like to order "Basic Synchros & Servo-mechanisms" and enclose a cheque to the value of 34/- for that purpose and eagerly look forward to their delivery. May I add that I have no objection to your using this testimonial should you so desire since they are truly "value for money", indeed they would be cheap at twice the price.'

J. Penington, Connah's Quay, Chester

Take advantage of our **SEVEN DAYS FREE TRIAL** to inspect a set of these highly successful training manuals by signing your name on the coupon provided on page 1080

**SELWAY BOOK CO.**  
68, Hayes Hill, Hayes, Bromley, Kent.

**RES/CAP. BRIDGE 39/6**  
p. & p. 2/6.

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading

**READY CALIBRATED**

Stamp for details of this and other kits.

**RADIO MAIL (Dept. K)**  
Raleigh Mews, Raleigh Street, Nottingham

**BBC2 (625 LINE) TV AERIALS**

Most Spaced Arrays, 9 element 45/-; wide spaced high gain, 11 element 55/-; 13 element 62/6. Wall Mounting with Cranked Arm, 9 element 60/-; wide spaced high gain, 11 element 67/6; 14 element 75/-; Chimney Arrays Complete, 9 element 72/-; wide spaced high gain, 11 element 80/-; 14 element 87/6. 10Tf Arrays, 7 element 38/6; wide spaced high gain, 11 element with Tilting Arm, 62/6; 14 element 70/-; All high gain units have special Multi-rod Reflector. Low loss co-axial cable 1/8 per yard.

**BBC - ITV - F.M. AERIALS**

**B.B.C. (Band 1)**, Telescopic loft 21/-, External S/D 30/-.

**I.T.V. (Band 3)**, 3 Element loft array 25/-, 5 element 35/-, Wall mounting, 3 element 35/-, 5 element 45/-.

**Combined B.B.C./I.T.V.** Loft 1+3. 41/3; 1+5. 48/9; Wall mounting 1+3. 56/3; 1+5. 63/9; Chimney 1+3. 63/9; 1+5. 71/3.

**F.M. (Band 2)**, Loft S/D 12/6, "H", 30/-, 3 element, 52/6, External units available Co-ax cable 8d., yd., Co-ax plugs, 1/3, Outlet boxes 4/6, Diplexer Crossover Boxes, 12/6, C.W.O. or C.O.D. P. & P. 3/-. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept. P.W.)**  
3b Godstone Road, Kenley, Surrey  
CRO 2527

Head Office and Warehouse:  
44A WESTBOURNE GROVE  
LONDON W2  
Tel.: PARK 8641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail Orders to the Head Office  
When sending cash with order, please include 2/6 in 2 for postage and handling  
MINIMUM CHARGE 1/6. No C.O.D. orders accepted

Retail Shop:  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel.: LANHAM 8403

0A2	6/-6AK4	7/-6L14	8/-20L1	14/-956	2/-DY86	3/-EP40	9/-KT88	20/-TT15	35/-TRANSISTORS			
0B2	6/-6AM0	4/-6Q74	6/-20P1	14/-957	5/-E88C2	14/-EF41	7/8-N78	15/-TT21	32/-AF114	9/-OC42	8/-OC77	8/-
0B3	6/-6AN6	10/-68L7GT	6/-20P3	14/-958	4/-EAB80	7/-EF42	6/-NFS1	25/-TT29	32/-AF116	8/-OC44	6/-OC81	5/-
0C3	6/-6AQ5	6/-68N7GT	4/-20P4	14/-959	3/-EAF42	8/-EF54	9/-NSP2	22/-U25	11/-AF116	7/8-OC70	5/-OC18D	5/-
OD8	5/-6AQ6	8/-6C4GT	10/-20P5	14/-959	6/-EB41	5/-EF55	8/-OCPT7	24/-U26	11/-AF117	7/8-OC71	5/-OC139	12/-
1A5GT	5/-6AR5	6/-6U8	7/-25A8G	5/-5783	10/-EBC33	7/-EF40	5/-JHP12	12/-U191	11/-OC26	8/-OC72	8/-OC171	9/-
1A7GT	6/-6AR7G	25/-6V6	9/-25L6GT	8/-5080	25/-EBC41	7/-EF93	10/-OLP50	10/-U251	12/-OC28	17/8-OC75	6/-OC204	10/8
1L6GT	7/-6AT8	4/-6V6GT	7/-25Z4G	7/-6146	27/-EBC81	5/-EF85	6/-PC86	12/-U281	13/-OC35	15/-OC76	6/-	
1H6GT	7/-6AU6	9/-6X4	4/-26Z5	7/8-9002	5/8-EBF90	6/8-EB86	7/-PC88	12/-U282	14/-OC35	15/-OC76	6/-	
1L6	17/-6AV8	9/-6X5GT	5/8-26Z6GT	8/6-A21	9/-EBF83	7/8-EB89	4/8-PC87	9/-U301	12/-R.C.A.	2N110 (OC45);	2N419 (OC44)	7/3/8 each.
1N3GT	8/-6H7	6/-6X9G	6/-30C15	10/-AZ41	6/8-EBF89	8/8-EB94	4/9-PC85	7/-U401	18/-GET114	5/8; GET115	7/-; GET573	80/-.
1Q5GT	8/-6H8	6/-7B7	6/-30C17	12/-C1C	8/-EBC38	12/8-EB94	10/-PC89	11/-U402	7/8-SEMICONDUCTOR RECTIFIERS			
1R4	6/-6RA8	4/8-7C8	7/-30F5	8/-CBL1	15/-EC80	8/8-EB95	5/-PC88	12/-U402	7/8-BY190	800 p.l.v.,	450mA, 7/-.	
1R5	5/-6BR6	5/-7D8	7/-30F11	11/-CL38	9/-EC88	12/8-EB98	10/-PC89	11/-U403	7/8-DI058	800 p.l.v.,	500 mA, 12/8.	
1R4	5/-6BH6	7/-7R7	12/-30L17	13/-CY31	8/8-EC90	2/8-EB95	5/-PCF80	7/-U404	7/8-OA210	400 p.l.v.,	500 mA, 6/8.	
1R5	4/8-6B16	5/-7E7	18/-30P12	10/-DAC32	7/-EC81	5/8-EB183	8/-PCF80	7/-U404	6/8-OA211	800 p.l.v.,	400 mA, 7/8.	
1T3GT	6/-6BK4	20/-6BW6	7/-30P19	14/-DAF7	4/8-EC82	4/8-EB184	8/-PCF82	7/8-U404	11/-22Z3W	4.25V, 4.75V, 5.25V, 5.75V, 7.0V, 8.0V—all at 6/8.		
1U4	5/-6BK7A	8/-9D7	7/-S0PL1	11/8-DAF92	6/-EAC40	9/-EBP80	10/-PCF84	8/-U404	9/8-280mW	OAZ202 (6.8V);	OAZ203 (6.2V)	9/8—all at 6/-.
1U5	6/-6BN6	7/-10C1	10/-						9/8-OAZ204 (6.8V)—6/8.			
1X2A	7/-6BQ7A	8/-10C2	10/-						7/8-300mW	RK448, 12.0V—6/-.		
1X2B	7/-6BRT	11/8-10D1	10/-						7/8-SEMICONDUCTOR DIODES			
2XW4	12/-6BR3	8/-10P1	14/-						10/-IN32	4/-IN81	4/-OA90	2/-.
2D1	6/-6B7	10/-10F3	8/-						7/8-IN32B	4/8-GEX23	1/8-SX641	8/-.
3A4	4/-6BW6	9/-10F0	10/-						6/8-IN35	6/-OA79	2/8-SX642	3/8.
3A5	7/-6BW7	9/-10F18	9/-						6/8-IN28	20/-OA81	2/-SX645	15/-.
3D6	4/-6C4	2/8-10L1	7/8-						7/8-IN34A	4/-OA86	8/-SX761	4/8.
3Q4	6/8-6C21	12/-10L11	10/-						10/-IN32	4/-OA86	3/8-	
3Q5GT	6/8-6C16	6/-							6/8-MAIN POWERED (230V a.c.) 19in. Rack			
3B4	5/-6C8D6	17/-10P14	18/8-						6/8-mounted fully fused power supply unit			
3V4	5/8-6C8E	6/-12AH7	5/-						7/-providing fully smoothed H.T. of 180 to			
4F4A	10/-6C16	9/-12AH8	11/-						8/-270V at 80 mA and L.T. of 6.3V a.c. at			
4B4G	9/-6CW4	12/-12AQ5	7/-						4/8-4 amps. Fitted with panel lamp, on-off			
5T4	8/-6D8A	15/-12A78	6/-						switch, socket for connection of an			
5U4C	5/-6F8	9/-12AT7	4/-						external powered iron meter for reading			
5U4GB	6/8-6P7	5/-12AU6	6/-						6/-input and output volts depending on			
5V4G	8/8-6F8G	5/-12AU7	5/-						8/8-the position of a key switch.			
5Y3GT	5/-6F11	8/-12AX7	6/-						8/-Record hand, in perfect order, £8.10.0.			
5Z3	6/-6F13	6/8-12BA6	6/-						22/-£8.18.6. P. & P. 15/-.			
6Z4GT	6/-6F17	8/-12BE6	5/-									
6S0L2	10/-6F23	9/8-12BH7	8/-									
6A8	8/-6F24	11/-12E1	2/8-									
6A8B	6/8-6F28	10/-12J7GT	7/8-									
6AG5	8/8-6F33	6/-12K7GT	7/-									
6AU7	6/-6J4	9/-12K8	10/-									
6AH6	10/-6J7GT	7/8-12Q7GT	5/-									
6AJ5	9/-6K7	5/-19AQ6	5/-									
6AK5	8/8-6L6GT	7/8-20F2	18/-									



# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy? ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee  
"NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building Plans,  
Draftsmanship,  
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.Prod.E.  
A.M.I.M.I.  
A.I.O.E.

B.Sc.  
A.M.I.E.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

## PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E., City & Guilds  
Radio Amateur's Exam. R.T.E.B. Certificate  
P.M.G. Certificate  
Practical Radio  
Radio & Television Servicing  
Fresnel Electronics  
Electronics Engineering  
Automation

## INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T.  
NOW offers you a real laboratory training at home with practical equipment. Ask for details.

## B.I.E.T. SCHOOL OF ELECTRONICS



### POST COUPON NOW!

■ Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"  
 ■ (Write if you prefer not to out page)  
 ■ NAME \_\_\_\_\_  
 ■ ADDRESS \_\_\_\_\_  
 ■ SUBJECT OR EXAM THAT INTERESTS ME \_\_\_\_\_

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
 (Dept. SE/21), 29 Wright's Lane, London, W.8  
**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

We supply from stock most of the components and items specified or circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

PW 6 Superhet  
PWS.W Converter  
PW Beginners SW2.  
PW Transistor Inverter  
PW Mains Power Pack  
PW Build and Learn Series  
PW, Transistor SW Converter.

All parts in stock for practically all "PW" circuits and designs. Send stamp with list of parts required for Quotations.

**CATALOGUE**

90 pages fully detailed and illustrated with hundreds of new items and price reductions. PRICE 2/6 Post Paid.

● OUR STOCKS ARE TOO VAST TO ADVERTISE—A CATALOGUE IS THEREFORE, A MUST ●



**MAINS AND BATTERY RECORD AND TAPE DECKS**  
(p.p. 3/6 any type)

- ★ All Decks Complete with Cartridges
- ★ BSR UA14 4-speed Auto ... £5 16 6
- ★ BSR UA15 4-speed Auto ... £6 19 6
- ★ Garrard Autoslim Auto ... £6 10 0
- ★ Unpluggable Hd. Vern. Auto ... £6 19 6
- ★ Battery Autoslim ... .. £8 19 6
- ★ Stereo Version Auto ... .. £7 19 6
- ★ SRP10 4-speed Single Player ... £5 0 0
- ★ SRP10 Battery Version ... .. £5 19 6
- ★ BSR GU7 4-speed Single Player ... .. £5 0 0
- ★ Garrard AT6 with Stereo Cartridge Autochanger ... £10 19 6
- ★ AT6 Mono ... .. £10 10 0
- ★ Collaro 2-track Studio Deck £10 10 0
- ★ Collaro Studio 4-track Deck £13 19 6
- ★ BSR TD2 2-track Deck ... .. £7 19 6
- ★ P. & P. 3/6 any type above.
- ★ 9 volt Starr 45 r.p.m. .... 89/6
- ★ 45 or 33 r.p.m. Starr 9V ... 39/6
- ★ 45 r.p.m. Garrard 6V. .... 35/-
- ★ 4-speed B.S.R. 9V ... .. 5 gns
- ★ Garrard 9V, 2-speed, 2-track Tape Deck with cassette ... £10 10 0
- ★ Fully guaranteed. P. & P. 3/-

**NEW LOW PRICES**



**MULTI-METERS**  
Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateurs, designers repair shops, all domestic uses. Full details and specification in our catalogue.

- PT34 1 K ohm/volt. .... £1 19 6
- MI 2 " " " " " " £2 9 6
- THL33 2 " " " " " " £3 15 0
- ★ EPIOK 10 " " " " " " 79/6
- ★ ITL2 20 " " " " " " 89/6
- ★ TP55 20 " " " " " " £5 19 6
- ★ EP30K 30 " " " " " " £5 10 0
- ★ 500 30 " " " " " " £8 10 0
- ★ EP50K 50 " " " " " " £8 10 0
- ★ EPIOOK 100 " " " " " " £9 19 6

★ Leather Cases available.

**RECORD/REPLAY/ERASE TAPE HEADS**



Marriot Type R/RP/3 1/2 track record/replay head and Mullard type TS erase head with mounting post. Bargain offer 15/- pair P.P. 9d.

**TRANSISTOR POCKET RADIOS**

Ready to use complete with Battery. Leather Case. Earphone. P.P. 2/- any type. Fully Guaranteed.

- 6-Transistor De Luxe ... .. 69/6
- 7-Transistor Zephyr ... .. 79/6
- 6-Transistor MW/LW ... .. £5.19.6

**TRANSISTOR PORTABLE TRANSCIEVERS**  
9-transistor Portable Transcievers. Supplied complete with leather cases, batteries, aerials, etc. in presentation case. Range up to 5 miles in favourable conditions. Sizes 6 1/2 x 3 x 1 1/2 inches. Superhet crystal controlled on transmit and receive. Price £21 Per Pair. P.P. 3/6

**TRANSISTOR TRANSCIEVER**  
3-transistor crystal controlled version of above. Range up to 1/2 mile. Price £8.19.6 Per Pair. P.P. 2/6.

**A SELECTION FROM OUR STOCKS—NEW PRICES**  
See Catalogue for full details.

- Sinclair Micro-6 (to build) ..... 59/6
- Sinclair TR 750 amps. (to build) ... 39/6
- Sinclair Micro Injector (to build) ... 27/6
- PP3 9 volt Battery Eliminator ..... 18/6
- Tap Jack Tuner..... 29/6
- 10-Watt Horn Tweeter..... 27/6
- 20-Watt Super Tweeter..... 69/6
- Two-channel Mixer..... 15/-
- 1 to 200 Mc/s F/str. Meter ..... 59/6
- 1/2-Watt 4-transistor 9 v. 3 ohm..... 49/6
- 5-hole Chassis Punch Kit ..... 49/6
- Headphones 2 K ohm 12/6; 4K ohm 14/6
- Stereo Headphones 8 x 8 ohm..... 3 gns.
- Stereo Stethoscope Headset 8 x 8 ohm ..... 25/-
- Resistor Substitution Box..... 32/6
- Crystal Mono Stethoscope Headset ..... 10/6
- Magnetic Mono Stethoscope Headset ..... 12/6
- Transistor Signal Injector ..... 35/6
- Fully Disappearing Car Aerial ..... 39/6
- Test Lead Kit with Pouch..... 8/6
- Capacitor Substitution Box ..... 22/6
- De Luxe Stereo Headsets with junction box ..... £6
- 4-channel transistor mixer ..... 49/6
- ★ 3-Transistor MW Superhet Tuner ..... 67/6
- ★ 4-Transistor Superhet MW/SW Tuner ..... £7.9.6
- Transistor Telephone Amplifier 59/6

**FM VHF TUNING HEART**  
Printed circuit-construction. RF stage and osc./mixer stage. fully tunable 85 to 105 Mc/s. Completely screened. Requires UCC85 (8/6). Brand new in maker's cartons 15/- P.P. 1/-.  
Supplied with circuit.

**MULLARD PORT CORES**

LA1 12/6	LA5 17/6	LA45 15/-
LA2 15/-	LA6 22/6	LA2503 15/-
LA3 19/6	LA9 17/6	LA2504 15/-
LA4 12/6	LA10 17/6	LA2505 17/6


- 30 watt Soldering Iron 14/6 P.P. 1/-
- Tape Demagnetiser ..... 29/6
- 2 K ohm 1 in. diam. mag. mic..... 15/-
- Antex 15 watt min. soldering iron 29/6
- Earphones Mag. or Crystal ..... 5/-
- Telephone Recording attachment... 9/6
- Crystal Guitar contact mic..... 12/6
- ★ 7-transistor Record Player or tuner amplifier with treble/bass and vol. controls, £5.19.6.
- ★ 4-transistor 1/2 watt amplifiers. Kit, 39/6. P.P. 1/6. Built 49/6. P.P. 1/6.

**RECORDING TAPE**  
5in. 600ft., 12/6; 5in. 900ft., 15/-; 7in. 1,200ft., 18/6; 7in. 1,800ft., 25/6; 7in. 2,400ft., 27/6. Excellent quality.

● SCOTCH BOY TAPE. 3 1/2in., 300ft. L.P. complete with spare spool. 5/6 P.P. 9d.

● SINCLAIR X10 AMPLIFIERS in stock. Kit £5.19.6. Built £6.19.6. Also Mains Unit 54/-.

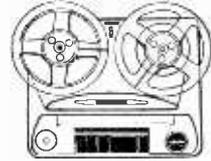**BUILD A QUALITY TAPE RECORDER**  
Leaflet on request



- ★ 6 Valve Printed Circuit designs. 2-track or 4-track units. 11 gns. 2-track, 12 gns. 4 track.
- ★ Collaro Studio Decks. 2-track 10 gns. P.P. 3/6. 4-track £14. P.P. 3/6.
- ★ Portable cabinets with Speakers, 5 gns. P.P. 3/6.
- Complete Systems
- 2-track £26. P.P. 8/6. 4-track £30. P.P. 8/6.
- Complete in Every Detail ●

**NOMBREX TEST EQUIPMENT**



All transistor-portable units supplied with full instructions.

Leaflets on Request.

- ★ 150 Kc/s to 350 Mc/s generator. RF Mod. AF, 8 ranges. Leads, batteries, instructions, £9.10.0.
- ★ Resistance/Capacitance Bridge, £8.5.0.
- ★ Antistatronic Power Supply, £6.10.0.
- ★ Audio Generator, £16.15.0.
- ★ Inductance Bridge, £18.
- Fully Guaranteed.



**CRYSTAL MICROPHONES**

(See Catalogue for Full Range)

- Acos 39-1 Stick Microphone 32/6
- Acos 60-1 Stick Microphone 19/6
- Acos 40 Deck Microphone 15/-
- Acos 45 Hand Microphone 19/6
- Lapel/Hand Microphone... 12/6
- 100C Stick with Stand ... 32/6
- BM3 Stick with Stand..... 49/6
- Lapel/Hand Magnetic..... 8/6

● MINIGRAM PORTABLE TRANSCIEVER RECORD PLAYER KIT, as previously advertised. 79/6 P.P. 3/6 (Battery) 3/9.

**QUARTZ CRYSTALS**  
100 kc/s 15/-; 500 kc/s 15/-; 455 kc/s 12/6; 456 kc/s 15/-; 27.255 Mc/s 15/-; 1 Mc/s B76 25/-.  
Twin Crystal, 1 Mc/s, and 100 kc/s 22/6. Over 800 frequencies in stock.

**Henry's Radio Ltd.**  
PADdington 1008/9

303 EDGWARE RD., LONDON W.2  
Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

# PRACTICAL WIRELESS

# blueprints

**M**OST of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (\*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

## DOUBLE-SIDED BLUEPRINTS

The Strand Amplifier ... ..	}	*	5/-
The PW Signal Generator ... ..			
The Savoy VHF Tuner ... ..	}	*	5/-
The Mayfair Pre-amplifier ... ..			
The Berkeley Loudspeaker Enclosure	}	*	5/-
The Luxembourg Tuner ... ..			
The PW Troubadour ... ..	}		7/6
The PW Everest Tuner ... ..			
The PW Britannic Two ... ..	}	*	6/-
The PW Mercury Six ... ..			
The PW Regency ... ..	}	*	5/-
The PW International Short Wave Two			
Beginner's Short Wave Two ... ..	}	*	5/-
S.W. Listener's Guide ... ..			
Beginner's 10-watt Transmitter	}	*	5/-
Transmitting and Aerial Data...			
P.W. "Sixteen" Multirange Meter ... ..	}	*	5/-
Test Meter Applications Chart ... ..			
The Celeste 7-transistor Portable Radio	}	*	5/-
The Spinette Record Player ... ..			
The P.W. 35-watt Guitar Amplifier ... ..	}	*	5/-
Transistor Radio Mains Unit ... ..			
7 Mc/s Transceiver ... ..	}	*	5/-

## RECEIVERS

The Tutor * ... ..	3/-
The Citizen * ... ..	5/-
Dual-Wave Crystal Diode ... ..	PW95 2/6
Modern One-valver ... ..	PW96 2/6
All-dry Three ... ..	PW97 3/6
Modern Two-valver ... ..	PW98 3/6
A.C. Band-pass Three ... ..	PW99 4/-
A.C. Coronet-4 ... ..	PW100 4/-
A.C./D.C. Coronet ... ..	PW101 4/-
The PW Pocket Superhet ... ..	5/-

## MISCELLANEOUS

The PW 3-speed Autogram ... ..	8/-
The PW Monophonic Electric Organ ... ..	8/-
The PT Band III TV converter ... ..	1/6
The Mini-amp * ... ..	5/-
The PT Olympic * ... ..	7/6
The PT Multimeter * ... ..	5/-

**PLEASE NOTE** that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

## QUERY SERVICE

The P.W. Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot supply detailed information for converting war surplus equipment, or supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

**(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

### QUERY COUPON

This coupon is available until 4th MARCH, 1965 and must accompany all queries in accordance with the rules of our Query Service.


PRACTICAL WIRELESS, MARCH, 1965

## First Class Designs — Proven Unbeatable Performance

★ CIRCUITS AND DETAILS ON REQUEST — FULL AFTER SALES SERVICE AND GUARANTEE ★

### CALL IN FOR DEMONSTRATION
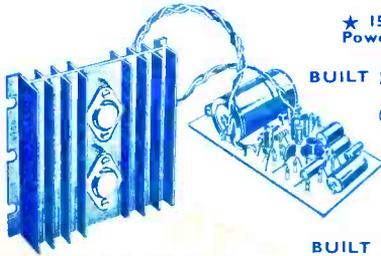
#### ● TRANSISTOR HIGH FIDELITY EQUIPMENT MONO or STEREO 10 WATTS and 20 WATTS



★ 15 ohm 10 watt  
Power Amplifier

BUILT £5.19.6 P.P. 2/6

(OR KIT £5.10.0  
P.P. 2/6)

★ 3 ohm 10  
watt power  
amplifier

BUILT £5.10.0 P.P. 2/6

(OR KIT 99/6 P.P. 2/6)

★ MAINS UNITS 59/6 for one  
amplifier, or 69/6 to power  
two amplifiers

#### PREAMPLIFIERS

● Mono full function  
pre-amplifier with 8 in-  
put positions. Low  
noise, high quality and  
sensitivity. Gives 10  
watts with one power amplifier  
or 20 watts with two ampli-  
fiers. Size 9 × 2½ × 2in.



BUILT £5.10.0 P.P. 2/-  
(KIT 99/6 P.P. 2/-)

★ Brown and Gold detailed front  
panel plate 8/6

#### ● STEREO PREAMPLIFIER

For use with two power  
amplifiers

Size: 9 × 3½ × 1½in.

PRICE BUILT £10.19.6

P.P. 3/6

★ Dark Brown with  
Gold front panel 12/6



#### ● MULTI-INPUT PREAMPLIFIER

Simplified preamplifier for use with one  
or two power amplifiers, 8 inputs.

PRICE BUILT 65/- P.P. 1/6

★ Front Panel Plate 6/6.



All the above preamplifiers can be used with any valve or transistor power amplifier requiring 250mV plate for full output. They can be operated with two 9 volt batteries in series or from the power amplifiers.

● 10 Watts R.M.S. music power or 20 watts peak power per amplifier.

#### TWO NEW PACKAGED TRANSISTOR QUALITY AMPLIFIERS



4 WATT and  
1½ WATT

● 6-Transistor printed circuit designs. Push-pull output for 3 to 5 ohm speakers. Can be battery operated. 6mV into 1 Kohm sensitivity. Response 30 cis to 15 kc/s. Input suitable for mics., pick-ups, tuners, etc. Can be used with above preamplifiers for mono or stereo in any application requiring a low distortion low cost amplifier.

OVERALL SIZE: 2½ × 2 × 1½ inches.

● 4-watt version  
operates from  
12 to 18 volts.

● 1½ watt version  
operates  
from 9 to 12v.

PRICE BUILT  
79/6 P.P. 1/6

PRICE BUILT  
65/- P.P. 1/6

#### “REGENT-6”

New!

● MEDIUM and LONG WAVE  
POCKET SUPERHET RADIO  
A New 6-transistor printed circuit  
designed with full coverage on both  
wavebands. Features “Cleartone”  
push-pull speaker output, geared  
tuning and complete set of 1st grade  
components. Moulded two tone  
cabinet size 5 3/8 × 1½”. Easy to  
follow building details. All parts sold separately.

● Total cost of all parts 85/- P & P 2/-  
(Battery 2/6 extra)  
Available mid-February



#### ‘CONVAIR’ PUSH-BUTTON PORTABLE/ CAR RADIO

##### ● UNBEATABLE FOR PERFORMANCE AND DESIGN

Printed circuit 6-Transistor 2-  
Diode superhet radio with  
full tuning on medium and  
long wavebands. Quality  
push-pull output up to 1  
watt. Attractive portable  
cabinet, size 10 × 7 × 3½”,  
with horizontal slow motion  
turning dial and push button  
wave change. Easy to build with superb performance. All parts  
sold separately. After sales service and guarantee.



● Total cost of all parts. £7.19.6 P.P. 3/6.  
(Batteries 6/- extra) ★ The finest portable available.

#### ALL TRANSISTOR CAR RADIO

##### ● 1 HOUR TO BUILD WITH PRE-ASSEMBLED CHASSIS AND PANELS

6-Transistor 3 diode med.  
and long wave superhet  
design. Features double  
tuned IFTS, AVC, perm-  
ability tuning with geared drive. Push-pull car filling volume.  
Full tuning on both wavebands. A high sensitivity printed  
circuit professional design to fit any type of vehicle. Case size  
7 × 4 × 2”. For 12 volt positive earth or dry battery. All parts  
available separately.

● THE “ROADSTER” £8.19.6 P.P. 3/6  
Total cost to build  
7 × 4” Hi-Flux speaker with baffle and car fixing kit 20/- extra.



#### VHF TRANSISTOR FM TUNER

##### ● HIGH STABILITY— HIGH SENSITIVITY ●

Features 5-Mullard transistors  
with 4-diodes, compact  
printed circuit, high gain,  
low distortion, superhet  
design. Full tuning from 87  
105 Mc/s with geared tuning,  
AVC and AFC. 9 volt 9 mA  
operation. 50 dB S/N. Out-  
put up to 1 volt audio. Easy  
to build and align. Overall size in cabinet 3½ × 2½ × 4in.  
All parts sold separately.

● Total cost with front panel.— £6.19.6 P.P. 2/6  
(Cabinet Assembly 20/- extra)



#### HENRY'S RADIO LTD.

PADDington 1008 9.

303 EDGWARE ROAD, LONDON, W.2.

(Open Monday to Saturday all day 9 a.m. to  
6 p.m. Half-day Thursday 1 p.m.)

● Trade and export enquiries invited ●  
PLEASE TURN TO INSIDE PAGE