

31. LEOP

# PRACTICAL WIRELESS

NOVEMBER 1965

2<sup>1</sup>/<sub>2</sub>

**FREE INSIDE**


**24-PAGE POCKET GUIDE**

BASIC RADIO FORMULAE & DATA

OHMS LAW CALCULATIONS

TRANSISTOR BASE CONNECTIONS

WORKSHOP DATA & TABLES

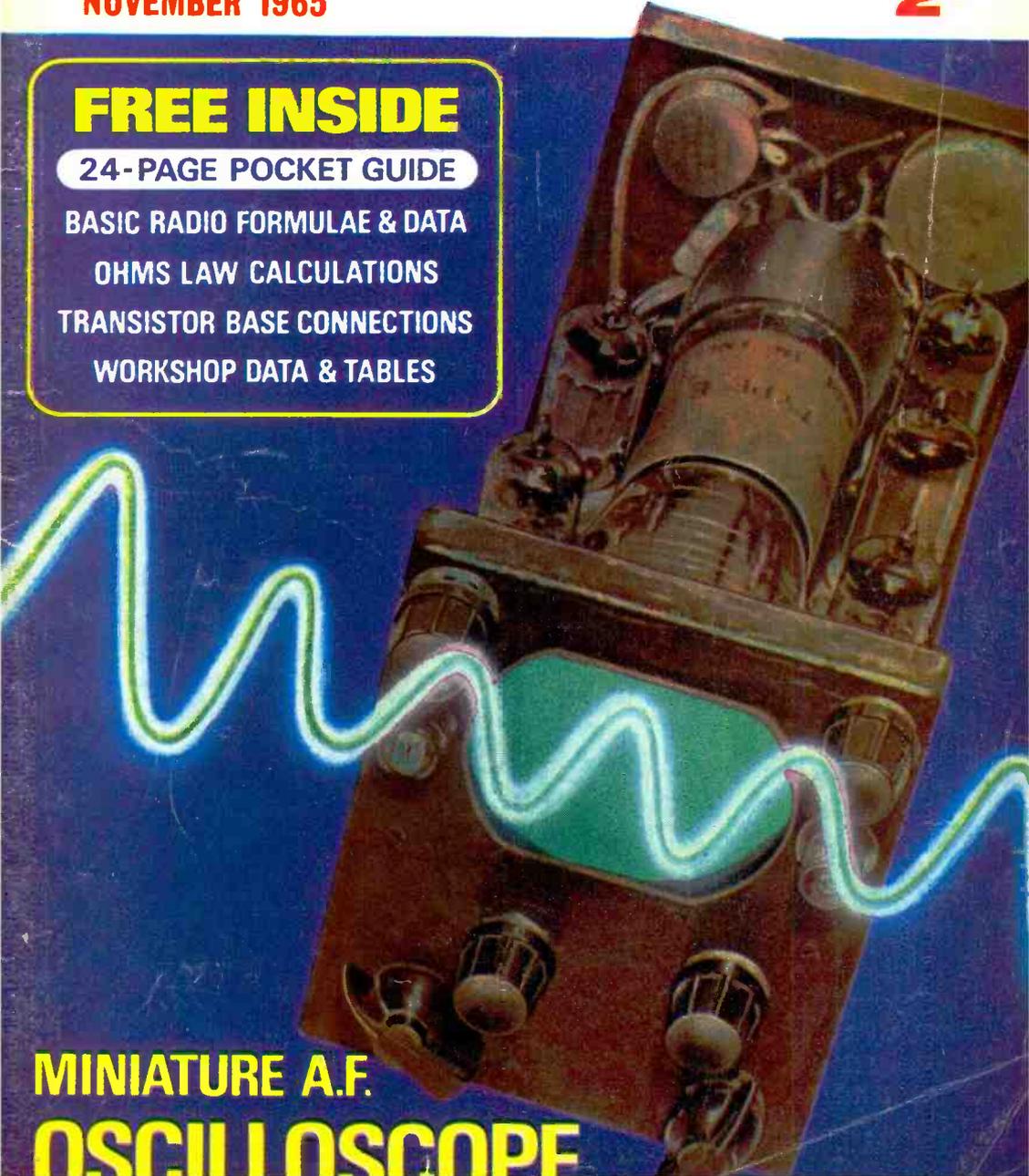


**MINIATURE A.F.  
OSCILLOSCOPE**



**SOLDERING EQUIPMENT**

FOR THE RADIO CONSTRUCTOR

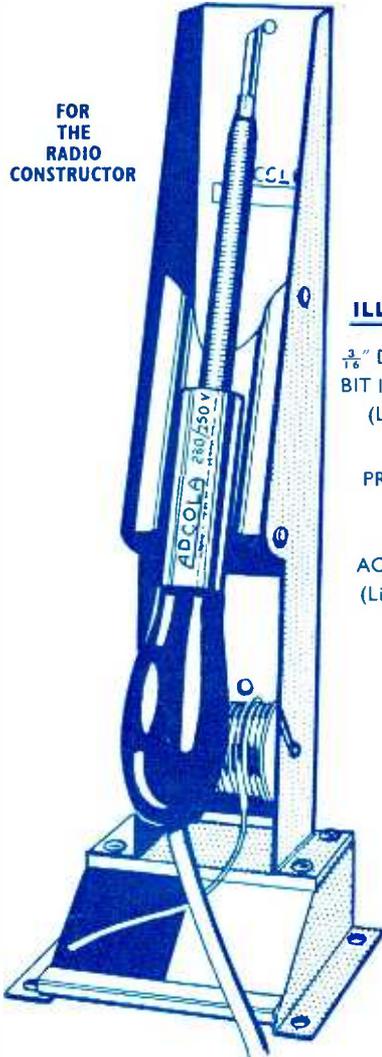

**ILLUSTRATED**

**3/16" DETACHABLE BIT INSTRUMENT**

(List No. 64)

IN PROTECTIVE SHIELD WITH ACCESSORIES (List No. 700)

FOR CATALOGUES APPLY DIRECT  
**ADCOLA PRODUCTS LTD.,**  
**ADCOLA HOUSE,**  
**GAUDEN ROAD,**  
**LONDON, S.W.4**

Telephones:  
 MACaulay 3101  
 4272  
 LONDON SW4

Telegrams: "SOLJOINT"

The **SUPER 6**  
 LONG & MEDIUM WAVE  
 TRANSISTOR RADIO



A quality radio available in parts or ready built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12. 12. 0 commercial model.

- ★ All new parts. ★ 6 transistors and diode. ★ 350m W output.
- ★ Superhet circuit. Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet, 11 x 7 1/2 x 3 1/2 in.
- ★ Vynil covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet 274. Free with kit. ★ I.F. Frequency 470 kc/s.
- ★ Lining up service if required. ★ All parts supplied separately. Write for list. S.A.E. please. ★ 9v. battery required. VT9 or P.P.9 (3.9 with kit).

Complete Set of Parts ONLY

**£4.17.6**

PLUS 5/- POST  
 OR FULLY BUILT **£6.17.6** Tax & Carr. Paid

V.H.F. Pre-amplifier with high signal-noise ratio and gain of at least 3:1 under average fringe area conditions. Metal container 3 1/2 x 3 1/2 x 1 1/2 in. high, with strap for eaves, loft or skirting fixing. 9 volt battery operated, using transistor AF114. 88 to 108 Mc/s. Order with confidence of improved reception. ONLY 30/- (post 2.9).


Transistors Packet of 3 coded RF transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful for presentation. 15/- post paid.

**GLADSTONE RADIO**

66 ELMS ROAD, Aldershot, Hants  
 Tel. 22240

Post orders only please  
 Please also see our advertisement on page 577

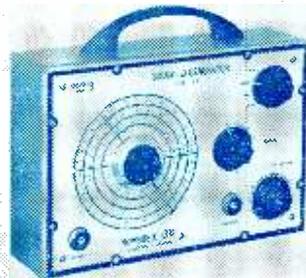**NOMBREX INSTRUMENTATION**  
 TRANSISTORISED SIGNAL GENERATOR  
 Model 27 £9.16.9



Also available:

- ★ INDUCTANCE BRIDGE 66 ... **£18.6.9**
- ★ POWER SUPPLY UNIT 61 ... **£6.14.6**
- ★ C.R. BRIDGE 62 ... **£8.11.9**
- ★ AUDIO GENERATOR 63 ... **£17.1.9**

All Prices include Battery, Post and Packing.  
 Prompt delivery

S.A.E. for Technical Leaflets

Trade and Export enquiries invited

**NOMBREX LTD.**

Phone: 3515

Estuary House, Camperdown Ter., Exmouth, Devon

# Tubes

HIGHEST QUALITY  
COMPARE OUR PRICES

	GUARANTEE		NEW TYPES
	8 Months	12 Months	
MOST MULLARD	12in. £2. 0.0	£3. 0.0	MW 31/74
MAZDA, COSSOR.	14in. £2.10.0	£3.10.0	£3.15.0
EMITRON, EMISCOPE, BRIMAR.	15-17in. £3. 5.0	£4. 5.0	MW 36/24
FERRANTITYPES	19in. £3. 5.0	£4. 5.0	£4.15.0
PROCESSED IN OUR OWN FACTORY	21in. £3.15.0	£5.15.0	CRM 172 MW 43/64
	23in. £3.15.0	£5.15.0	£6.0.0

## SATISFACTION GUARANTEED

### Autochangers, etc.

**LATEST GARRARD**  
All Factory Fresh with cartridge.  
**SRP10 Mono (Single) Player, £4.19.0.**  
**SP25 Semi-Transcription (Single) £11.19.0.**  
**AUTOSLIM Standard Auto, £5.19.0.**  
**AT8 Auto (Limited Number), £2.19.0.**  
**ATS Slimline similar to AT8, £7.15.0.**  
**Model 1.000-1.000-Compact low-priced record changer, automatically playing up to 10 records, £6.19.0.**  
**Model 2.000-Automatic record changer with large turntable, playing up to 8 records, £7.19.0.**  
**Model 3.000-Designed for use with high-compliance cartridges; low-mass arm gives exceptionally low record wear, £10.10.0.**  
**AT66-Automatic or manual operation, hand operation arm, bias compensator and heavy turntable, £11.19.0.**  
**AT70-For the critical user-offers automatic playing, with pusher-platform, and many other features, £19.19.0.**  
**LAB88-An outstanding automatic transcription turntable for professional reproduction, £25. 8.0.**  
**301-Transcription Heavy Table, £22. 8.0.**  
**AT66-Automatic or manual operation, hand operation arm and plug-in pick-up head, £9.10.0.**  
**H.S.R.**  
**GUT-Single Deck Complete, £4.5.0.**  
**UW14 or U25-Auto Changer, £5.15.0.**

**AULTY-METERS, 7K.20.A. 8 Range AC/DC/Current/Resistance 0-100K, moving coil, EP.10.K. 10.000 OPV, High Quality, 15 Ranges AC/DC/Current/Resistance, Accuracy ±3%. £19.19.6**  
**EP.20.K. 20.000 OPV, more sensitive version of EP.10.K. £4.19.6**  
**EP.30.K. 30.000 OPV, 18 Ranges, including Resistance to 10 Meg. £6.19.6**  
**EP.50.K. Professional Quality, 22 Ranges, AC/DC/Volts/Current/Resistance/Decibels/Capacitance. £9.19.6**  
**TEST EQUIPMENT. ITI-19.6**  
**Stencored Signal Injector, complete with Transistor Oscillator with Indicator Lamp. Detachable Test Probe and instructions. £35/-**

**IDEAL FOR ANY RECORDER. PRICES SLASHED. GUARANTEED APPROX. 1/3 PRICE. WORLD WIDE MAKE BY ENORMOUS PURCHASE.**

### ★ TAPE ★

We offer you fully tenalised polyester/nylon and P.V.C. tapes of identical quality hi-fi, wide range rectorial characteristics as top grade tapes. Quality control manufacture. Not standard in any way. Try one for yourself. They are truly worth a few more pence than acetate, substandard, jointed or cheap imports! Try one and prove it for yourself!

	Standard Play	Double Play
3" 225ft. 19/8	3" 300ft. 4/-	3" 600ft. 8/-
5" 900ft. 10/6	5" 1200ft. 15/6	5" 2400ft. 27/-
3" 225ft. 2/9	4" 900ft. 13/-	4" 1800ft. 25/-
5" 900ft. 10/6	5" 2400ft. 27/-	5" 3000ft. 34/-
5" 1200ft. 13/6	7" 2400ft. 27/-	7" 3000ft. 34/-
5" 1800ft. 18/6	4" 900ft. 13/-	4" 1800ft. 25/-

Postage 1/- or Post Free less 5% on three reels. Quantity and Trade enquiries invited.

### AM/FM RADIOS

Latest wonderfully styled, guaranteed top make, 10-transistor with full long and medium waves. Size 9 1/2 x 6 1/2 x 1 1/2 in. Magnificent reproduction. A pleasure to look at. "An aristocrat in its class". 12 months guarantee against faulty manufacture. Genuine retail price £25.75. Unrepeatable. **17 Gns.**

### QUALITY PORTABLE TAPE RECORDER

Fabulous quality and reproduction of music. 6 transistor, 1 1/2 in. and 3 1/2 in. speeds. Output 500mW into high quality speaker. Ingenious stack control knob. Fast forward and rewind. Battery level and record level meter. Fast load. Precision capstan drive with dynamic carcepe monitor recording. Radio recording leads. Outside speaker facilities. The most outstanding portable in the country. Size 8 1/2 x 3 1/2 x 6 1/2 in. Genuine normal price of 35 Gns. Unrepeatable. 12 month guarantee. All spares available. With 19Gns. tape, tape reel, mike, etc.

## VALUE IN VALVES

GUARANTEED 3 MONTHS BY RETURN OF POST

Satisfaction of Money Back Guarantee on goods if returned unused within 30 days. ALL VALVES ARE NEW UNLISHED OTHERS UNLISHED UNFORMED FREE TRANSIT INSURANCE. POSTAGE 1 valve 6d., 2-11 1/4-. Free over 12.

024	4/8	6K8GT	8/3	1457	14/6	EB34	6/3	EZ41	5/9	R19	9/8
1A7GT	9/9	10C25	3/1	14Q5	7/9	EB31	5/6	EZ80	5/9	SP41	2/3
10G5T	7/6	8L	6/9	20D1	8/9	EBF80	7/6	EZ81	6/-	SP81	2/-
145GT	8/9	6L6	7/8	20F2	9/6	EBF89	7/9	FC4	8/-	T41	6/9
15N5GT	8/9	6L6	6/8	20L1	16/-	EBL21	9/9	GZ32	7/8	TDD4	7/-
154	7/6	6L18	7/8	20P1	9/6	EBL31	19/6	HV22	9/-	U14	7/8
22E1	5/8	6L19	12/8	20P3	11/-	EC2	4/9	KT30C	3/9	U18	7/8
3A4	4/-	6LD20	7/8	20A4	17/-	EC32	4/-	KT36	14/-	U22	6/9
3A5	6/-	6P25	8/9	25A6	8/6	EC34	9/-	KT44	6/-	U24	12/8
3D8	4/-	6P28	9/8	25L6GT	7/9	EC40	6/8	KT45	8/6	U25	8/3
3Q4	5/-	6Q7G	4/-	25Z4G	7/-	ECB1	4/9	KT61	8/6	U26	7/-
5B4GY	8/-	6Q7GT	8/-	30F5	6/-	EC32	4/9	KT73	5/9	U35	12/8
6U6G	5/6	6G7	5/8	30FL1	9/8	EC38	5/8	KT75	12/-	U50	4/8
5Y3G	4/6	6G7	4/8	30L15	9/8	EC54	7/6	KT76	8/6	U107	12/8
5Y3GT	4/-	6SK7	5/-	30P4	9/6	EC55	6/-	KT78	17/8	U191	9/-
5Z4	9/-	68L7GT	5/6	30P12	7/-	EC58	9/6	KT61	5/9	U281	3/6
5Z4G	7/-	68N7GT	4/6	30P11	9/6	ECF80	6/-	KTW53	5/-	U282	15/-
6Z4GT	9/6	6G7	5/8	35L15	8/8	ECF82	8/-	KTZ63	7/-	U301	12/8
630L2	9/-	6U4GT	8/-	35L6GT	8/-	ECB21	11/6	MU14	7/-	U326	8/6
6A8G	7/9	6V8G	6/8	35W4	6/-	ECB35	7/6	N7	10/6	U801	10/-
6A7G	7/6	6V8GT	8/-	35Z4G	5/8	ECB28	8/6	N78	13/-	UABC80	7/-
6A5K5	4/3	6X4	4/8	50L6GT	8/6	ECB31	10/3	P38	11/8	UBF59	7/8
6A5K5G	4/1	6X6G	5/-	50	5/-	ECB32	8/6	PC86	10/-	UB41	6/8
6A7S	5/-	6X5GT	5/8	15B5T	19/6	ECB10	6/6	PC97	7/6	UCB41	7/8
6A6U6	7/-	7B8	9/-	18B7A19	6/6	ECB2	8/6	PC84	6/8	UCB81	6/-
6A6V6	8/-	7B7	5/8	80TA	19/6	ECB38	10/6	PC85	6/8	UBF70	7/8
6B4A	5/6	7C5	7/8	80T6	4/9	ECB36	10/3	PC83	11/8	UBF59	7/8
6B4B	5/6	7C6	8/8	80T8	4/9	ECB37	6/6	PC88	8/6	UC85	7/8
6B6G	15/-	7H7	5/-	866A	12/6	EF39	4/6	PC89	13/6	UC85	7/8
6B6E	5/-	7B7	8/9	954	3/8	EF40	11/-	PCF80	6/9	UCF80	8/8
6B6J	5/-	7Y4	4/8	955	2/3	EF41	8/-	PCF82	6/-	UCH21	9/8
6B7	8/10	10E1	9/8	958	2/6	EF54	3/6	PCF83	12/-	UCB42	4/3
6B7E	11/-	10A7	7/8	958	4/6	EF52	3/6	PCF86	10/6	UB41	7/8
6B7W	5/-	10F1	4/9	9002	4/9	EF85	6/-	PCF82	7/6	UCH82	8/-
6C4	2/3	10D11	14/8	9003	5/8	EF86	7/6	PCF83	8/-	UCH38	10/-
6C5	5/6	10P13	3/8	AT4	6/6	EF89	6/8	PCF84	7/3	UF41	6/8
6C8	5/6	10P14	9/8	AT61	6/6	EF91	3/6	PCF85	7/6	UF42	4/3
6C9	11/-	10A7	7/8	AT62	4/6	EF92	3/6	PCF86	10/6	UF42	4/3
6CD6G	17/-	12A88	9/-	CB131	19/6	EF188	9/9	PE26	5/9	UF85	7/8
6D6	3/-	12A78	6/8	CL33	9/-	EF184	3/6	PE45	8/6	UF89	5/3
6F1	4/9	12A77	4/8	CY31	7/8	EL32	9/6	PE46	4/8	UL41	7/8
6F6G	3/8	12A76	9/-	DAF91	4/8	EL33	9/6	PL33	8/6	UL44	14/-
6F13	4/3	12A77	4/8	DAF96	7/3	EL34	11/6	PL36	8/6	UL46	8/3
6F14	9/6	12A78	6/8	DF31	3/6	EL35	6/-	PL38	17/6	UL84	7/8
6F15	9/6	12A77	4/8	DF92	3/6	EL38	12/6	PL51	7/8	URIC	7/8
6F23	6/6	12BA6	7/-	DF96	7/3	EL41	8/-	PL82	6/8	UM80	9/8
6F5G	3/-	12BE6	6/8	DK91	5/8	EL42	7/8	PL53	6/8	U08	8/9
6F5GT	4/3	12B17	8/9	DK92	1/6	EL43	6/6	PL54	7/6	U08	8/9
6G6	2/6	12E1	17/8	DK96	7/3	EM34	6/6	PY31	8/-	U18	11/-
6G7G	4/9	12Q7GT	5/-	DL92	5/-	EM80	7/9	PY32	10/-	UY21	9/8
6G7GT	7/8	12K7GT	4/-	DL84	6/8	EM81	6/8	PY80	8/6	UY41	6/-
6K8GT	6/8	12K58	9/8	EL78	7/8	EM84	8/8	PY81	5/9	UY85	5/-
6K7	9/9	12KSGT	9/8	EBAC80	6/6	EM85	8/6	PY82	5/9	VR105	5/-
6K7GT	1/-	12Q7GT	5/-	EAF42	3/3	EV71	7/6	PY83	5/9	VR150	7/8
6K7GT	4/8	12A7	6/3	EB41	5/-	EV68	7/3	PY88	9/-	VR150	7/8
6K8	8/8	12K57	2/8	EB81	2/-	EV88	8/8	PY80	6/3	X68	7/8
6K8G	5/-	12SG7	7/6	EB33	4/8	EZ40	6/6	PZ30	9/8	Z86	3/8

### CONNECTING WIRE

P.V.C. Bright Colours. Five 4/-  
25ft. coils only.

### MAINS TRANSFORMERS

Excellent Quality. Guaranteed Up-rating. 250-0-250V.  
30mA, 6.3V., 3A (NOMA 12/6)  
Ditto semi-shrouded **7/6**

### SPECIAL C.R.T. OFFER

Due to huge Bulk Special Purchase we are offering C1M141 and MW 36/24 Tubes at the unrepeatable price of 39/-. P.P. 12/6. The above are guaranteed for 6 months.

### ★ BULK BARGAINS ★

- 12 POTS. Popular values. 5K, to 2 Meg. Unused, mixed pre-set. **4/6**
- CONDENSERS. 25 mixed Electrolytics. Many popular sizes. List Value 65. Our price **10/-**
- 100 RESISTORS 6/6  
Excellent. Sizes 1/2-2 watt.
- 100 CONDENSERS 9/6  
Miniature Ceramic and Silver Mica Condensers, 3pF to 5000pF. LIST VALUE OVER 65.
- 25 TAG STRIPS 4/-  
2, 4, 6 8-way etc. Unused.
- 100 HI STASS 9/6  
1% to 5% 100Ω to 5 Ω m.

### TRANSISTORS

GUARANTEED TOP QUALITY  
Huge reduction. Red Spot standard LF type now only  
White Spot R.P. .... **1/6**

Mulard Matched Output  
Kits OC81D and OC81E  
R.P. Kits OC44, OC45 (2)  
3 transistors. **12/6**

AF114 8/- OC44 5/8  
AF115 7/8 OC45 5/8  
AF116 7/8 OC72 5/8  
AF117 8/8 OC82 5/8  
AF127 9/8 OC81D 5/8  
OC26 12/8 OC82 6/-  
OC38 14/- OC170 8/8  
OC171 8/8

### GERMANIUM DIODES

General Purpose miniature detector A.V.C. etc. **8d.**  
9/6 Individually highest quality Individually tested. **1/-**  
9/6 doz.

### SILICON RECTIFIERS

Guaranteed performance. Top Makes. Tested 250V. working.  
100mA **3/9** 250mA **7/6**  
(3 for 9/6) (3 for 19/6)

LOUDSPEAKERS. 3Ω Top Makes. 5in. **7/6**  
7 x 4in. **8/6**

# TECHNICAL TRADING CO.

Post: 2lbs. 2/-, 4lbs., 2/6, 7 lbs., 3/6, 12 lbs., 4/-, etc. (C.O.D. extra). ALL VALVES LESS 5% AND POST FREE IN DOZENS.  
Retail Only. Hi-Fi Demonstrations, 72 East Street, Southampton  
Tel. 25851 11/12 North Road, Brighton, Tel. 67999  
ALL MAIL ORDER AND RETAIL SHOP  
350/352 FRATTON RD., PORTSMOUTH TEL. 22034

# LASKY'S RADIO

## Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days when the sum paid will be refunded less postage.

### THE "SKYROVER" RANGE

#### GENERAL SPECIFICATION

7 transistor plus 2 diode superhet. 6 waveband portable receiver. Operating from four 1.5 v torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 M and also 4 separate switched band-spread ranges, 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed 'n under three hours from our easy to follow stage by stage instructions.

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500 M. Light programme). All components and detailed construction data. **Only 10/-extra** Post Free

This conversion is suitable for both models that have already been constructed. Data for Receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All components available separately.

### NEW—The SKYROVER Mk III

Now supplied with redesigned cabinet, edgewise controls, black and chrome plastic cabinet. Size 10 x 6 1/2 x 3 1/2 in. with carrying handle. **£8.19.6** Post 5/- Can now be built for H.P. Terms: 27/- dep. and 11 months at 15/8. Total H.P. Price £10.0.3.

### The SKYROVER DE LUXE

Tone Control Circuit is incorporated with separate Control. In a wood cabinet size 1 1/2 x 6 1/2 x 3 1/2 in. covered with a washable material with plastic trim and carrying handle. Car aerial socket fitted. Can now be built for **£10.19.6** Post 5/-



H.P. Terms: 33/- dep. and 11 mths at 19/2. Total H.P.P. £12.3.10

### The "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker. ★ All components mounted on a single printed circuit board. ★ Full medium and longwave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue/Grey or all Grey. ★ Socket for car aerial. ★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operate from PP9 or similar battery. ★ Full data supplied. All coils and I.F.'s etc. fully wound ready for immediate assembly. Any outstanding receiver. **Can be built for £5.19.6** Post 4/6



PP9 Batt. 3/9. Data and instructions: separate 2/6. Refunded if you purchase the parcel. All parts sold separately.

### REALISTIC Seven DE LUXE

With the same specification as standard model—PLUS a superior wood cabinet in contemporary styling with full vision circular dial. **ONLY £1 EXTRA**

### SINCLAIR MINIATURES

**THE MICRO-6** Self-contained pocket radio. Size only 1 1/2 x 1 1/4 x 1 in. Amazing performance. Complete with earphone and detailed construction data. **Can be built for only 59/6** Mercury cell 1/11 extra. All parts sold separately.

**THE SHIMLINE** 2-transistor pocket radio. Size only 2 1/2 x 1 1/2 x 1 1/2 in. Micro alloy transistors on printed circuit. **CAN BE BUILT FOR 49/6**

**THE NEW X-20 AMPLIFIER** 20 watts P.W.M. amplifier and pre-amplifier built on single printed circuit size 3 1/2 x 3 1/2 in.—weight only 4 1/2 ozs. built input sens. 1mV for 20 watts out. Output Imp. 7.5 and 15 ohms. **£7.19.6** Post Free **AVAILABLE READY BUILT AND TESTED £8.19.6.** Post Free. 1 no.s. for vol. base and treble, 7/6 the extra mains power pack. If required £4.19.6.

**THE X-10 AMPLIFIER** 10 watt power amplifier fitted with integrated pre-amplifier. Requires only 1mV. for an output of 10 watts. Only 3 x 3 x 4 in. **KIT PRICE £5.19.6** Post Free **AVAILABLE READY BUILT, TESTED AND GUARANTEED, £6.19.6.** Post Free. 3 pots for Volume, Base and Treble. 7/6 the extra. Mains power pack. If required 54/-.

### U.H.F. TUNERS

Only a few available. Complete with PC86 and PC88 valves. We regret no circuit or data is available. Knobs included.

Lasky's Price **79/6** Post 2/6.

### GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 106 Mc/s. For use with one EC085 valve in metal case, size 7 x 2 1/2 x 1 1/2 in. Circuit supplied. **Lasky's Price 19/11** Post 2/-

### COLLARO STUDIO TAPE DECKS

3 speed model—1 1/2, 3 1/2 and 7 1/2 i.p.s., available with either 1 track or 2 track heads. Fitted with 3 motors; pause control and tape position indicator. Fast forward and rewind. Deck size: 12 1/2 x 10 1/2 x 4". For use on 110-125V, 50 or 60 c.p.s. mains but by the simple addition of a step-down auto transformer these decks can be operated direct from normal 200-250v. A.C. mains. State whether 50 or 60 c.p.s. model required when ordering (note: U.K. mains are normally 50 c.p.s.). Brand new and unused.

**LASKY'S PRICE** 1 track Model **£6.19.6**

**LASKY'S PRICE** 2 track Model **£10.10.0**

Carriage and Packing 7/6 extra.

Standard Model for 200/250v. mains operation available at **£10.10.0**; 1 track **£13.19.6.** Post 7/6.



Suitable Mains auto transformer 15/6 if ordered with the deck. (List price 19/6).

### ELIZABETHAN LZ 27 PORTABLE TAPE RECORDER

Special Bargain Offer—brand new, unused and fully guaranteed. Brief specification: 2 speeds—7 1/2 and 3 1/2 i.p.s.; 2 track; 3 1/2 watt output; inputs for mic. and radio; outputs for ext. speaker and additional amp. or monitor; built in 7 x 4 in. speaker; tape position and record level indicators; fast forward and rewind. Volume and tone controls also superimpose facilities. Takes 7 in. spools. For 200/250V. A.C. mains. Attractively styled cabinet with carrying handle and detachable lid, size: 16 x 13 x 7 in. Complete with crystal mic., tape and empty spool. **Makers List Price 27 Gns.**



**LASKY'S PRICE 18 Gns.** Carriage and Packing 10/-

### B.S.R. AUTOCHANGERS—BRAND NEW AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.

- UA14 4 speed mains model .....£4.9.6
- UA16 4 speed mains model .....£4.19.6
- UA16 9 v. battery model .....£5.19.6
- UA20 4 speed mains model .....£5.19.6

Add 5/- carriage and packing on each.

### INTERNATIONAL TAPE

3in. Message tape, 150ft. ....	3 6
3in. Message tape, 225ft. ....	4 11
3in. Message tape, 300ft. ....	7 6
3 1/2 in. Triple play, 600ft., Mylar base ....	15 0
4in. Triple play, 900ft., Mylar base ....	17 6
5in. Double play, 1,200ft., Mylar base ....	15 0
5in. Long play, 900ft., Acetate base ....	10 0
5in. Standard play, 600ft., PVC base ....	8 6
5in. Triple play, 1,800ft., Mylar base ....	35 0
5in. Double play, 1,800ft., Mylar base ....	25 6

Famous American Brand—Fully Guaranteed

5 1/2 in. Long play, 1,200ft., Acetate base ....	12 6
5 1/2 in. Standard play, 850ft., PVC base ....	11 6
5 1/2 in. Triple play 2,400ft., Mylar base ....	45 0
7 in. Standard play, 1,200ft., Acetate base ....	10 0
7 in. Standard play, 1,200ft., Mylar base ....	12 6
7 in. Long play, 1,800ft., Mylar base ....	19 6
7 in. Double play, 2,400ft., Mylar base ....	25 0
7 in. Long play, 1,800ft., Acetate base ....	15 0
7 in. Triple play, 3,600ft., Mylar base ....	58 6
P. & P. 1/- extra per reel: 4 reels and over Post Free	

## LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

# Service in Great Britain to both & HI-FI ENTHUSIASTS

TAPE RECORDERS . RECORD PLAYERS . AMPLIFIERS ETC. COMPLETE MONO/STEREO SYSTEMS TO YOUR SPEC.



## NEW COMMUNICATION RECEIVERS MODEL KT 320 KIT



Supplied in sub-assemblies for easy building. Covers range from 540 Kcs to 30 Mc/s. Ham Band is provided with a scale for direct reading and can also be band spread, 9 valves. Facilities: A.N.L., A.V.C. and M.V.C. Q Multiplier also serves as B.F.O. H.P. stage and two I.F. stages ensure high sensitivity and selectivity (all coils and I.F.s are supplied pre-aligned). 2 Aerial sockets. Stand-by position for use with a transmitter 8 meter fitted. 200-250V. A.C. mains. Steel cabinet, grey crackle finish. Size 15 x 8 x 10 1/2 in. Dial 12 x 4 in. All parts new and fully guaranteed. Complete with full construction data and operating manual.

**LASKY'S PRICE 25 GNS.** POST FREE  
Also available ready built and tested 2s. 6ns. H.P. Terms Available.

**MODEL HE30** Still a few available—as advertised June '65  
**LASKY'S PRICE 30 GNS.**  
H.P. Terms available.

## MODEL HE40



Covers medium wave band and 1.6-4.4 Mc/s. 4.5-11.0 Mc/s., 11.5-30.0 Mc/s. in separate switched band spread ranges. Controls include B.F.O. sensitivity, A.N.L. Receiver—stand-by switch. Tone switch. S-Meter. For 200-250V. A.C./D.C. Internal loop and telescopic antennae fitted. Valve line-up: 12BE6, 12BA6, 12AV6, 50C5, and metal rectifier. Size 13 1/2 x 8 1/2 x 5 1/2 in. Instruction manual included. No Kits available.

**LASKY'S PRICE 19 GNS.** POST 10/-  
H.P. Terms £4.0.0. dep. and 11 monthly payments of £1.12.0. Total H.P.P. £21.12.0

**MODEL HE80** 14-valve super sensitive communication receiver. Freq. range 540 Kcs—30 Mc/s. and 144-116 Mc/s. Dual conversion to 2 metres, with extra R.F. stage. Single R.F. stage, two I.F. stages on all other bands. B.F.O. and Q-multiplier circuits. Improved A.N.L. and voltage regulated powerpack. "S" meter band spread on amateur bands, large illuminated dial with logging scale. All controls fitted. Output for speaker and phones. Valve line-up: 4 x 6AQ5, 3 x 6BA6, 2 x 6BE6, 1 x 6BL6, 6AL5, 6AQ5, 6CA3 and OA2. Steel case 17 x 7 1/2 x 10 in. For 200/250V. A.C. mains. Brand new with full instruction manual. No Kits available.


**LASKY'S PRICE 59 GNS.** POST FREE  
H.P. Terms £12.0.0 dep. and 11 monthly payments of £4.18.0 Total H.P.P. £68.17.0.

207 EDGWARE ROAD, LONDON, W.2 Tel: PAD 3271/2  
33 TOTTENHAM CT. RD., LONDON, W.1 Tel: MUS 2605  
Both open all day Saturday. Early closing Thursday.  
Please address all Mail Orders to Dept.

## The "Sixteen" Multirange METER KIT

This outstanding meter was featured by Practical Wireless in the Jan. '64 issue. Lasky's are able to offer the complete kit of parts as specified by the designer.  
**RANGE SPECIFICATION:** D.C. volts: 0-2.5-25-50-250-500 at 20,000 Ohm A.C. volts: 0-2.5-50-250-500 at 1,000 Ohm. D.C. current: 0-50uA, 0-2.5-50-250 mA. Resistance: 0-2,000 Ohm, 0-200 Ohm, 0-20M Ohm. Basic movement: 40uA i.s.d. moving coil. Black plastic case, 3 1/2 x 5 1/2 x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot. meter; meter zero. Complete with all parts and full construction details. Data and circuit available separately. 2/6 refunded if all parts bought. Pair of Batteries. 2/5 extra. H.P. terms available.

**LASKY'S PRICE £5.19.6** P. & P. 5/-

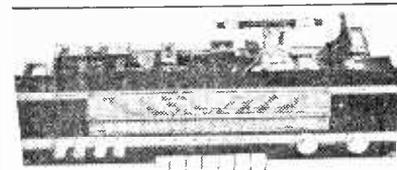

## THE LATEST "KUBA" IMPORTED AM/FM STEREO RADIOGRAM CHASSIS

Long, medium and short waveband coverage plus VHF/FM. Piano key wave-change—separate flywheel tuning on AM and FM Bass, treble and balance controls. Magic-eye tuning indicator. Ferrite rod aerial. The very latest printed circuitry. Provision for multiplex-adaptor. 5 valve line-up: ECC85, ECH801, ECC83, ELL80, EAF801. Full vision tuning scale, size 2 1/2 x 6 in. Overall dimensions: 21 x 6 1/2 x 8 in. Made to the very highest standards.

**LASKY'S PRICE 29 1/2 GNS.** Carriage & Insurance 12/6 extra.

## TEST METER ADAPTOR

Type P.E. 290. Transistorised device which enables any 50 microamp D.C. Multimeter to be used in place of a valve volt meter. On the 1v. range an impedance of 1 megohm is offered which increases on the 100v. range to 100 megohms. 7 ranges immediate connection to AvO X but suitable for use with any other 50 microamp meter. Size 6 x 6 x 5 in. New and boxed. List Price 7 Gns.



**LASKY'S PRICE 39/6** Post 2/6. Set of batteries 7/5 extra.

## DOMESTIC PROCESS TIMERS BY SMITHS

Finest quality Smith's Clocks originally intended for use in the most expensive electric cookers. 3 types available—brand new and unused—at well below production cost.  
Type 1. Clockwork Interval Timer. Gives loud and prolonged ringing to indicate the end of any set time from 1/2 minute to 1 hour. 3in. dia. dial x 2in. deep.


**LASKY'S PRICE 9/11** Post 2/-

Type 2. An electric clock with combined sequence switching to give automatic switching of an electric appliance to switch on at any pre-set time up to 12 hours ahead and to switch off at any pre-set time up to 9 1/2 hours later. Switch contacts are rated at 25 amps, 200/250 V., 50 c.p.s. and are therefore suitable for cookers and heating appliances as well as tape recorders, radios, lights, etc. Easy to set. 3in. dial. Fully enclosed mechanism—overall size 5 x 3 1/2 x 2 1/2 in.

**LASKY'S PRICE 25/-** Post 2/6.

Type 3. De Luxe version of Type 2 with fully calibrated, easy to read, dial (as illustrated). Note this model does not have a back cover.

**LASKY'S PRICE 35/-** Post 2/6.

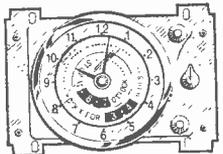

## GREENCOAT RECORD PLAYERS

45 r.p.m. 6 volt Battery operated. Complete with pick-up fitted crystal cartridge. Size only 7 1/2 in. x 6 in. Fitted auto. stop and start. New and perfect. **49/6** P. & P. 2/6



2-speed model for 33 and 45 r.p.m. (as illustrated) **59/6** P. & P. 2/6

**TRANSISTORS Brand new & guaranteed**  
GET S1, GET S5, GET S6, 2/6; 873A, 874P, 3/6; OC43, OCT1, OC21D, 4/6; OC44, OCT9, OC75, OC81 (match pair 10/6) 5/6; AF117, OC75, OC200 6/6; OC42, OC43, OC73, OC82D 7/6; OC201, OC204 15/-; OC205, OC206 19/6; OC28 24/6.

**TRANSFILTERS BY BRUSH CRYSTA. CO.**  
TV-O1B 465 kc/s. ± 2 kc/s.  
TO-O1D 470 kc/s. ± 2 kc/s.  
TO-O2B 465 kc/s. ± 1 kc/s.  
TO-O2D 470 kc/s. ± 1 kc/s.  
TP-O1B 465 kc/s. ± 2 kc/s.  
TP-O1D 470 kc/s. ± 2 kc/s.  
**7/6 EACH** Post 6d.

42 TOTTENHAM CT. RD., LONDON, W.1 Tel: LAN 2573  
152/3 FLEET STREET, LONDON, E.C.4 Tel: FLE 2833  
Both open all day Thursday. Early closing Saturday.  
X.W 207 Edgware Road, London, W.2.

**LASKY'S FOR SPEEDY MAIL ORDER SERVICE**

# INCREASE YOUR KNOWLEDGE



## RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

### CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING,  
INDUSTRIAL TELEVISION, RADIO AND  
TELEVISION SERVICING, ELECTRONICS,  
COMPUTERS AND PROGRAMMING,  
ELECTRONIC TECHNICIANS, SERVOMECH-  
ANISMS, TELEMETRY, COLOUR TV,  
INSTRUMENTATION, AND PRINCIPLES OF  
AUTOMATION.

### ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers  
C. & G. Telecommunication Techns' Cert.  
C. & G. Supplementary Studies  
R.T.E.B. Radio/TV Servicing Cert.  
P.M.G. Certificates. Radio Amateurs' Exam.

### LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of  
Radio as you build YOUR OWN 5-valve superhet  
Receiver and Transistor, Portable Signal Generator  
and High Quality Multitester. At the end of the course  
you have invaluable practical equipment and a fund of  
personal knowledge and skill. ICS Practical Radio  
Courses open a new world to the keen amateur.

### THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to com-  
plete your technical qualifications, or further special-  
ised knowledge, ICS can help you with a course  
individually adapted to your requirements.

There is a place for you among the fully-trained men.  
They are the highly paid men—the men of the  
future. If you want to get to the top, or to succeed  
in your own business, put your technical training in  
our experienced hands.

ICS Courses are written in clear, simple and direct  
language, fully illustrated and specially edited to  
facilitate individual home study. You will learn in  
the comfort of your own home—at your own speed.  
The unique ICS teaching method embodies the  
teacher in the text; it combines expert practical  
experience with clearly explained theoretical training.  
Let ICS help you to develop your ambitions  
and ensure a successful future. Invest in your own  
capabilities.
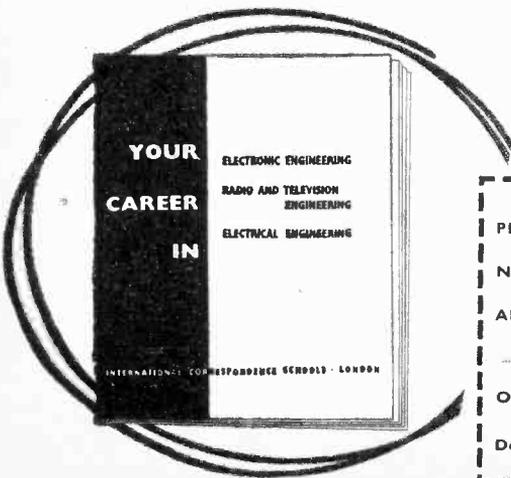
### FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the  
examinations and ICS technical courses in radio, television  
and electronics. PLUS details of over 150 specialised  
subjects.



PLEASE SEND FREE BOOK ON \_\_\_\_\_

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

OCCUPATION \_\_\_\_\_ AGE \_\_\_\_\_

INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. 170, INTERTEXT HOUSE, PARKGATE RD, London SW11  
11.65

Another step forward . . .

# AN IMPROVED AVOMETER Model 8 Mk. III

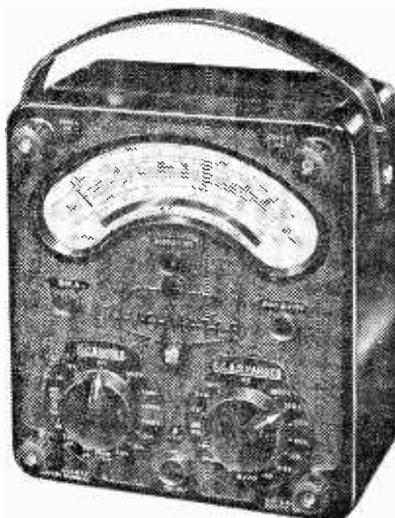

- Fused ohms circuit provides increased protection against inadvertent overload.
- Improved temperature coefficient over whole range. With the aid of a range of d.c. shunts, measurements can be made up to 400 amps d.c.

This new model incorporates increased sensitivity, the lower a.c. ranges and wide frequency characteristics, with the traditional Avometer features including the AVO automatic cut-out mechanism and interlocking rotary switches for quick range selection.

Write for fully descriptive Folder or for complete Catalogue of AVO Instruments.



AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - VICtoria 3404



## SURBITON PARK RADIO

### MARTIN AUDIOKITS & RECORDAKITS

- F.M. TUNER UNITS Nos. 15, 16 and 17. . . . . Cash £12.17.6  
 Or Dep. 51/6 and 12 m. pymts. of 18/10. . . . . (H.P. Price £13.17.6)  
**TRANSISTORISED AMPLIFIER** with 5 position input selector, pre-amp and controls. 10 watt amplifier and Power Pack. . . . .  
 For 3 Ohm Speaker. Cash £14.5.0  
 Or Dep. 57/1- and 12 m. pymts. 20/10. . . . . (H.P. Price £15.7/0)  
 For 15 Ohm Speaker. Cash £15.8.0  
 Or Dep. 62/- and 12 m. pymts. 22/6 . . . . . (H.P. Price £16.12/0)  
 All above include Front Panels, Knobs and Instructions.  
**TWO TRACK RECORDAKIT AMP.** (Valve) **FOR STUDIO DECK**, 6 valves, controls, self powered . . . . . Cash £11.11.0  
 Or Dep. 47/- and 8 m. pymts. 25/6 . . . . . (H.P. Price £12.11.0)  
**COLLAR KIT STUDIO DECK** 3 speed latest Two Track Cash £10.19.6  
 Or Dep. 44/- and 8 m. pymts. 24/6 . . . . . (H.P. Price £12.0.0)  
**COMPLETE KIT** with case, spkr., tape and mic. . . . . Cash £28.19.6  
 Or Dep. 120/- and 12 m. pymts. 44/- . . . . . (H.P. Price £32.6.0)  
**FOUR TRACK AMP.** as above. . . . . Cash £12.12.0  
 Or Dep. 52/- and 8 m. pymts. 27/6 . . . . . (H.P. Price £13.12.0)  
**FOUR TRACK COLLARO DECK** Marriott "X" Series heads . . . . .  
 Cash £13.19.6  
 Or Dep. 58/- and 12 m. pymts. 20/6 . . . . . (H.P. Price £15.2.0)  
**COMPLETE KIT** with case, spkr., tape, and mic. . . . .  
 Four Track Cash £33.19.6  
 Or Dep. 138/- and 12 m. pymts. 49/10. . . . . (H.P. Price £36.14.0)  
**TAPE PRE-AMP** for Studio Deck, self powered . . . . .  
 Two Track Cash £8.8.0  
 Or Dep. 34/- and 6 m. pymts. 25/8 . . . . . (H.P. Price £9/9/0)  
**TAPE PRE-AMP** as above . . . . . Four Track Cash £9.9.0  
 Or Dep. 39/- and 6 m. pymts. of 28/4 . . . . . (H.P. Price £10.9.0)  
 We are leading stockists for all Martin Constructional Kits

### AMPLIFIERS-TUNERS Selection

- ARMSTRONG 222 10-10 watts Stereo Amplifier. . . . . Cash £27.10.0  
 Or Dep. 110/- and 12 m. pymts. 40/4 . . . . . (H.P. Price £28.14.0)  
 ARMSTRONG 224 F.M. TUNER Powered . . . . . Cash £22.10.0  
 Or Dep. 90/- and 12 m. pymts. 33/- . . . . . (H.P. Price £24.6.0)  
 ARMSTRONG 223 AM/FM TUNER Powered. . . . . Cash £28.15.0  
 Or Dep. 115/- and 12 m. pymts. 42/2 . . . . . (H.P. Price £31.1.0)  
 ARMSTRONG 127 MONO 5W with AM/FM. . . . . Cash £26.10.0  
 Or Dep. 106/- and 12 m. pymts. 38/10 . . . . . (H.P. Price £28.12.0)

## SURBITON PARK RADIO LTD.

- ARMSTRONG 127 STEREO as above Stereo amp. . . . . Cash £37.10.0  
 Or Dep. 150/- and 12 m. pymts. 55/- . . . . . (H.P. Price £40.10.0)  
 ARMSTRONG 227 MONO 10W amp. with AM/FM. . . . . Cash £36.15.0  
 Or Dep. 147/- and 12 m. pymts. 53/10 . . . . . (H.P. Price £38.13.0)  
 ARMSTRONG 227 STEREO as above with Stereo Amp. . . . .  
 Cash £52.15.0  
 Or Dep. 211/- and 12 m. pymts. 77/4 . . . . . (H.P. Price £56.19.0)  
 ARMSTRONG 226 STEREO as above, but Mag. P.U. Filter . . . . .  
 Cash £61.0.0  
 Or Dep. 260/- and 12 m. pymts. of 88/- . . . . . (H.P. Price £65.16.0)  
 Teak Cases for all Armstrong Units . . . . . £3.10.0  
 ROGERS CADET MK. 3 10-10 watt Stereo Amp. Mag. P.U. . . . .  
 Cash £29.10.0  
 Or Dep. 118/- and 12 m. pymts. of 43/3 . . . . . (H.P. Price £31.17.0)  
**CASE MODEL ROGERS CADET MK 3** . . . . . £3.0.0 extra  
**LEAK STEREO 30 TRANSISTOR AMPLIFIER** . . . . . Cash £49.10.0  
 Or Dep. 198/- and 12 m. pymts. of 72/7 . . . . . (H.P. Price £53.9.1)

### LOUDSPEAKERS Selection

- FANE 122/10 heavy DUVY 12in. 20 watt. . . . . Cash £5.5.0  
 WHARFEDALE SUPER 8/RS/DD . . . . . Cash £6.14.8  
 WHARFEDALE SUPER 10/RS/DD . . . . . Cash £10.18.0  
 Or Dep. 44/- and 8 m. pymts. of 24/3 . . . . . (H.P. Price £11.18.0)  
**GOODMANS MAXIM** . . . . . Cash £17.10.8  
 Or Dep. 70/6 and 12 m. pymts. 25/8 . . . . . (H.P. Price £18.16.8)

### MOTORS-PICK-UPS Selection

- GARRARD SRP10 Mono . . . . . Cash £5.10.0  
 GARRARD Model 1000 Mono . . . . . Cash £7.10.0  
 GARRARD Model 2000 Mono Large Table . . . . . Cash £8.10.0  
 Or Dep. 34/- and 6 m. pymts. 25/- . . . . . (H.P. Price £9.10.0)  
 GARRARD Model 3000 Stereo Lightweight arm. . . . . Cash £11.11.0  
 Or Dep. 47/- and 8 m. pymts. 25/6 . . . . . (H.P. Price £12.11.0)  
 GARRARD S.P. 35 Less cart. Single player. . . . . Cash £12.10.0  
 Or Dep. 50/- and 8 m. pymts. of 27/6 . . . . . (H.P. Price £13.10.0)  
 GARRARD AT 60 Less cart. Heavy table. . . . . Cash £13.0.0  
 Or Dep. 52/- and 12 m. pymts. 19/- . . . . . (H.P. Price £14.0.0)  
 GARRARD A 70 De Luxe changer. less cart. . . . . Cash £22.10.0  
 Or Dep. 90/- and 12 m. pymts. 33/- . . . . . (H.P. Price £24.6.0)  
 GARRARD LAB 80 Push button oper. less cart. . . . . Cash £27.10.0  
 Or Dep. 110/- and 12 m. pymts. of 40/4 . . . . . (H.P. Price £28.14.0)  
 GARRARD 401 Transcription Table. No arm. . . . . Cash £32.10.0  
 Or Dep. 130/- and 12 m. pymts. 47/8 . . . . . (H.P. Price £35.2.0)  
**GOLDRING G66** Mono Single Player. . . . . Cash £11.11.0  
 Or Dep. 47/- and 8 m. pymts. 25/6 . . . . . (H.P. Price £12.11.0)  
**GOLDRING GL26** less cart. Heavy table. single play. Cash £17.1.0  
 Or Dep. 69/- and 12 m. pymts. 24/11 . . . . . (H.P. Price £18.6.0)  
**GOLDRING GL70** trans. Unit with arm. less cart. . . . . Cash £22.18.8  
 Or Dep. 120/6 and 12 m. pymts. 42/9 . . . . . (H.P. Price £25.5.6)  
 Leaflets available upon receipt of 6d. stamp.

48-50, Surbiton Road, Kingston-on-Thames, Surrey  
 Phone KIN. 5549:: Hours 9 a.m. to 6 p.m. daily (1 p.m. Weds.).

# BENTLEY ELECTRIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK, ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

0A2	5/8	8BX	4/3	7.57	9/8	2525	7/3	(5)	17/8	EB41	4/8	EL35	7/6	LG299	6/8	RG1/240A	LC91	11/-	GD14	10/-	
0B2	6/-	8/4	2/3	7/5	6/9	2526/27	8/-	AC/PCPN	EB91	2/3	EL86	7/3	MHD4	54/-	LC39	9/8	LC39	9/8	GET104	10/-	
0ZAGT	4/3	6C5	4/-	7/6	6/9	2789	23/3	(7)	17/-	EB37	2/6	EL91	2/6	MHL16	12/8	RC34	7/8	LC39	9/8	GET104	10/-
1A3	2/8	8/4	3/-	7/57	5/-	2807	6/9	AC/SG 26/2	EB33	6/-	EL93	5/-	ML6	5/8	R130	25/8	LC40	9/8	GET106	17/8	
1A4	12/6	6C8	3/-	7/13	15/-	3001	6/-	AC/SG 6/5 V	EB44	6/6	EL360	27/-	MR4B	20/8	SP4B	19/8	LC40	6/8	GET111	8/8	
1A5	5/-	6/9	10/8	7/15	14/6	3005	10/-	(12)	EB31	6/3	EL920	16/4	MP94	12/-	SP13C	12/8	LC01	15/-	GET113	6/8	
1ATGT	7/6	8C10	8/-	7/16	14/8	3007	11/9	AO/TP110/10	EB30	3/6	EL922	22/6	MC1214	4/8	SP41	8/-	LC420	9/8	GET114	8/8	
1B5	4/-	6C19	5/8	7/17	15/8	30018	9/3	AC/CP	EB30	5/6	EL330	13/6	MX40	8/8	SP42	12/8	VC16G	11/8	GET115	8/8	
1C2	8/-	6C06G	13/4	7/7	12/8	30053	7/3	AC/VP112/7	EBF80	5/8	EM80	5/8	N87	10/8	SP81	8/-	VM44B	8/8	GET163	17/8	
1C3	6/6	6C06	6/6	7/7	5/-	3001L	9/3	AC/VP212/7	LBFB3	7/3	EM34	11/8	N78	20/-	SP95	27/2	VP2	3/6	GET174	6/8	
1C5	5/-	6C24	24/-	7/4	5/-	3001L	5/8	ATP4	2/3	EBF89	5/8	EM35	12/-	N108	26/2	T41	9/-	VP2B	9/8	GET13	3/6
1C6	10/6	8D1	1/6	8D2	2/8	30015	10/8	AZ1	6/8	EBL21	10/3	EM71	15/6	N388	20/-	TPD2	12/8	VP4	14/8	GETX3	8/6
1D3	6/6	8D3	9/8	9B3/8	3/8	30017	11/8	JZ31	9/6	EB32	9/8	EM74	8/8	P41	8/6	TPD1	7/6	VP4A	24/8	GETX4	10/8
1D5	9/6	8D6	3/-	8D2	3/-	30014	12/-	A41	6/6	EC55	12/6	EM81	7/-	P61	2/6	TH4B	10/8	VP4B	12/8	GETX4	6/8
1FD1	6/-	8E5	9/6	9D7	7/6	30012	7/6	B36	4/9	EC34	6/-	EM84	6/-	PABCO	6/8	TR21C	10/8	VP13C	7/6	GEN64	11/6
1FD9	3/3	8F1	9/6	10C1	9/8	30016	5/3	B349	10/3	EC70	4/9	EM85	3/8	PC26	9/8	TR21C	10/8	VP23	2/6	GEN66	16/6
1G6	8/-	8F8/3	3/8	10C2	12/-	30019	12/-	B719	5/9	EC90	2/3	EM87	7/6	PC98	9/-	TR41	10/-	VP41	5/-	MAT100	7/8
1HG8T	7/8	8F6T	7/8	10C1	10/8	30011	10/8	DK63	10/8	EC34	4/-	EM82	10/8	PC83	6/8	TR233	6/8	VP23	9/8	MAT10	8/8
1H4	2/8	8F7G	5/-	10P2	11/8	30013	10/8	CL1	12/6	EC92	6/6	EM81	5/6	PC97	5/8	TR22	5/-	VP75	21/-	MAT120	7/8
1L4A	17/6	8F8	5/-	10P1	10/-	30014	11/3	CK306	6/6	EC31	7/3	EM81	5/6	PC85	5/8	TR25	6/-	VP85	5/8	MAT121	8/8
1L6A	16/10	8F11	17/8	10P9	9/8	30015	9/8	CL4	19/8	EC32	4/6	EM81	7/3	PC80A	8/8	TR290	7/8	VP85	5/8	OA5	6/8
1L6S	4/-	8F12	3/-	10P18	9/8	35614	12/8	CL38	11/6	EC33	29/1	EM85	9/8	PC88	10/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1L6S	4/-	8F13	6/8	10L03	6/8	35615	12/8	CL39	11/6	EC34	21/7	EM84	9/8	PC89	11/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1NSGT	8/6	8F14	23/3	10L11	9/8	35616	6/8	CV63	10/8	EC35	4/8	EM86	5/8	PC818	10/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1P1	6/-	8F16	6/8	10P13	12/-	35W4	4/6	CV271	12/8	EC40	7/-	EM88	8/8	PC8P8	6/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1P10	4/8	8F16	6/8	10P14	11/8	35Z3	18/2	CV428	19/-	EC41	3/8	EM91	3/8	PCF82	6/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1P11	5/-	8F17	12/8	1103	17/8	35Z47	6/8	CV1	18/4	EC42	8/8	EM93	5/8	PCF84	8/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1P12	5/-	8F18	11/8	1104	17/8	35Z57	6/8	CV2	18/4	EC43	8/8	EM93	5/8	PCF84	8/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1P4	5/-	8F23	9/8	11E8	17/-	40A	8/8	CV81	5/8	EM84	5/8	EZ41	6/8	PCF801	9/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1S2	3/3	8F24	10/6	12A6	2/3	41M71	8/-	D1	13/8	EC85	5/8	EZ80	3/8	PCF802	10/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1T2	29/-	8F32	3/3	12A6T	10/8	41H8	10/8	D15	13/8	EC88	8/8	EZ81	4/3	PCF805	9/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1T4	2/3	8F38	3/6	12A6S	3/6	42	5/-	D42	10/6	EC818	11/8	EZ90	3/8	PCF809	12/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1U4	5/8	8F45	3/6	12A6G	3/6	44	5/8	D43	10/6	EC819	11/8	EZ90	3/8	PCF809	12/8	TR90F	11/8	VP81A	7/-	OA10	6/8
1U3	5/3	8F46	1/6	12A6E	8/4	45	17/8	D77	2/3	EC807	16/-	FC4	3/8	EC138	5/8	UCF80	8/8	VM18	6/8	OA21	13/6
2A7	12/6	8J50	3/3	12A6T	5/-	45Z66T	15/-	DAFC2	7/6	ECF80	7/8	FC13	14/8	PC154	7/8	UCF81	8/8	VM18	6/8	OA21	13/6
2C26	2/8	8J50T	4/3	12A6H	10/8	50A5	21/10	DAF91	8/8	ECF82	6/8	FC13C	17/8	PC145	8/8	UCF82	8/8	VM18	6/8	OA21	13/6
2D13C	7/-	8J6	3/-	12A70	4/8	50B5	6/8	DAF96	6/8	ECF83	10/-	FC13C	17/8	PC145	8/8	UCF82	8/8	VM18	6/8	OA21	13/6
2D11	5/-	8J7G	4/8	12A77	6/8	50C3	6/8	DCX90	6/8	ECF84	10/-	FC13C	17/8	PC145	8/8	UCF82	8/8	VM18	6/8	OA21	13/6
2X2	3/-	8J7GT	7/-	12A76	5/8	50CDDG40/8	8/8	DD4	12/6	ECF84	23/3	GTIC	9/8	PCN40DD	8/8	UCF83	8/8	VM18	6/8	OA21	13/6
3A4	3/8	8K6GT	6/8	12A7	4/8	50L66T	6/8	DD41	10/6	ECB21	9/-	GU50	55/-	84/-	84/-	UP41	6/8	X24	16/8	OC19	25/-
3A5	6/8	8K7G	1/3	12A76	5/8	52K1	14/6	DDT4	7/6	ECB28	22/8	GU50	7/6	PCN45	7/6	UP42	4/8	X41	10/8	OC22	23/8
3B7	5/-	8K7GT	4/8	12A77	4/8	53K1	14/6	DEF25	7/6	ECB33	6/8	GU52	8/8	PCN45DD	8/8	UP43	4/8	X41	10/8	OC22	23/8
3B8	3/8	8K8	3/8	12A77	6/8	53C3	6/8	DF38	8/6	ECB42	2/6	GU54	12/8	PCN46	12/8	UP46	6/8	X43	5/8	OC23	12/8
3Q4	5/3	8K8GT	8/6	12A78	4/8	53D6	6/8	DF38	8/6	ECB41	6/8	GU54	12/8	PCN46	12/8	UP46	6/8	X43	5/8	OC23	12/8
3Q5GT	6/8	8K26	24/-	12B6	4/9	78	4/9	DF72	30/-	ECB83	6/8	GU57	14/8	PCN8510/3	8/8	UP49	6/8	X68	6/8	OC28	23/8
384	4/9	8L1	10/-	12B7	6/-	80	5/8	DF91	2/3	ECB84	9/8	H80	3/6	PCN45DD1	8/8	UP47	6/8	X66	7/8	OC28	16/8
5V14	5/8	8L15	12/8	12E1	6/8	81CV	6/8	DF91	2/3	ECB84	9/8	H80	3/6	PCN45DD1	8/8	UP47	6/8	X66	7/8	OC28	16/8
4D1	8/8	8L6GT	12/8	12E2	6/8	85A2	6/8	DF97	10/-	EC192	8/8	HABC90	9/8	PCN44	10/8	UP48	6/8	X78	8/8	OC28	16/8
8A4GY	8/6	8L7GT	6/8	12E5GT	2/6	90A6	6/8	DF130	15/8	EC183	8/8	HL18C	4/8	PCN44	7/8	UP48	6/8	X78	8/8	OC28	16/8
5T4	7/-	8L18	10/-	12E7GT	7/3	90CA	6/8	DF63	4/8	EC186	8/8	HL23	12/8	4020	17/8	UP48	6/8	X78	8/8	OC28	16/8
5V46	4/8	8L19	18/-	12E6	10/-	90G47	4/8	DF76	3/6	EC186	20/6	HL23DD	5/8	PFL200	30/5	UP48	6/8	X78	8/8	OC28	16/8
5V43	8/8	8L23	6/8	12E7	3/6	90G48	4/8	DF76	3/6	EC186	20/6	HL23DD	5/8	PFL200	30/5	UP48	6/8	X78	8/8	OC28	16/8
5V3GT	8/8	8L13	6/8	12K8GT	6/8	90C1	16/-	DH18	23/8	EE2	2/6	HL41DD12/8	12/8	PL38	8/8	UP48	6/8	X78	8/8	OC28	16/8
5Z3	6/6	8L20	6/8	12Q7GT	3/6	130B2	16/8	DH101	25/8	EE26	3/6	HL42DD12/8	12/8	PL38	18/-	UP48	6/8	X78	8/8	OC28	16/8
5Z4	7/6	8N7GT	7/6	12A76T	10/8	150C2	5/8	DH107/18/11	17/8	EE37A	7/-	HL133DD/9/6	9/6	UP48	6/8	UP48	6/8	X78	8/8	OC28	16/8
6 30L3	8/8	8P1	9/3	12B8	4/-	161	13/-	DK32	7/6	EE39	5/-	HL309DD/9/6	9/6	UP48	6/8	UP48	6/8	X78	8/8	OC28	16/8
6A6G	3/8	8P25	6/8	12B7	6/8	182B1	34/8	DM37	15/8	EE40	5/8	HL309DD/9/6	9/6	UP48	6/8	UP48	6/8	X78	8/8	OC28	16/8
6A8	5/8	8P26	6/8	12B7	3/6	215MG	6/8	DK91	4/-	EE41	6/8	HV2K4	8/8	PL84	6/3	UP48	6/8	X78	8/8	OC28	16/8
6A8T	4/-	8P28	11/8	12B7	5/-	220B	10/8	DK92	8/8	EE42	3/8	W3	5/6	PL500	15/8	UP48	6/8	X78	8/8	OC28	16/8
6A7	3/-	8P7G	4/-	12K7	3/8	301	20/-	DK96	6/8	EE50	2/6	W4/350	5/6	PM84	9/8	UP48	6/8	X78	8/8	OC28	16/8
6A5	2/6	8P7GT	7/8	12K7	9/-	302	15/-	DL3	9/8	EE54	3/8	W4/350	5/6	PT15	10/8	UP48	6/8	X78	8/8	OC28	16/8
6A6	5/8	8P7G	5/3	12K7	5/8	303	15/-	DL3	9/8	EE54	3/8	W4/350	5/6	PT15	10/8	UP48	6/8	X78	8/8	OC28	16/8
6A7	8/8	8H7GT	12/8	12L5G	7/-	304	15/-	DL38	5/3	EE50	4/3	KP33	12/8	PM25	8/8	UP48	6/8	X78	8/8	OC28	16/8
6AK5	4/8	8H7	7/-	12Y4	2/-	305	16/8	DL65	15/-	EE58	9/8	KL33	11/8	PY31	6/8	UP48	6/8	X78	8/8	OC28</	



MAIL ORDERS TO:  
54 WELLINGTON STREET, LEEDS 1

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4.6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

**PERSONAL SHOPPERS WELCOME AT ANY OF THE BRANCHES BELOW. OPEN ALL DAY SATURDAY.**

**BRADFORD** 10 North Parade (Half-day Wed.) Tel: 25349

**BRISTOL** 14 Lower Castle Street (Half-day Wednesday) Tel: 22904.

**BIRMINGHAM** 30/31 Gt. Western Arcade, opp. Snow Hill Station. CENTRAL 1279. No half-day

**DERBY** 26 Osmonston Rd., The Spot (Half-day Wed.) Tel: 41361

**DARLINGTON** 13 Post House Wynd (Half-day Wednesday) Tel: 68043

**EDINBURGH** 133 Leith Street, (Half-day Wed.)

**GLASGOW** 326 Argyle Street, (No half-day).

**HULL** 51 Savile Street (Half-day Thursday) Tel: 20505

**LEICESTER** 32 High Street (Half-day Thurs.) Tel: 56420

**LEEDS** 5-7 County (Mecca) Arcade (No half-day) Tel: 28252

**LIVERPOOL** 73 Dale St. (No half-day) Tel: CENTRAL 3573

**LONDON** 238 Edgware Road W2 (Half-day Thursday) Tel: PADdington 1629

**MANCHESTER** 60A-60B Oldham St. Tel: CENTRAL 2778 (No half-day) New large store.

**MIDDLESBROUGH** (Half-day Wednesday) 106 Newport Road. Tel: 47096

**SHEFFIELD** 13 Exchange Street Castle Market Bldgs. (Half-day Thursday) Tel: 20716

**JASON FMTI** V.H.F. F.M. Radio Tuner design. Total cost of parts including valves, tuning dial, esutcheon, etc. **£6.19.6**

**SUPERMET FEEDER UNIT** Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, V.I.C. and Vol. Only 250v. 15mA H.T. and L.T. of 6.3v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7in. high. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total building costs £5.5.0. S.A.E. for leaflet.

**TRANSISTOR SALE** Mullard OC71 2/11. OC15 3/11. OC4 3/11. OC72 2/11. OC81 2/11. OC11 3/9. A.T. 6/1. Biswan XA 101 3/9. XA112 3/9. XC101A 3/9. Postage 6d. for up to 3 transistors.

**EX GOVT. SELENIUM RECTIFIERS** 12v. 15 AMP (BRIDGE) F.W. ONLY **19/9**

**EX. GOVT. SMOOTHING CHOKES.** 200mA, 3-5 H. 50 ohms 2/6; 100mA, 10H, 50 ohms 9/8; 120mA, 12H, 100 ohms 8/9; 100mA, 10H, 100 ohms 6/9; 60mA 5-10H, 250 ohms, 2/11.

**TANNOY RE-ENTRANT LOUD-SPEAKERS.** For outdoor or Factory use, 8 ohms, 8 watts. **27/6** Plus 4/6 carriage

**HI-FI 10 WATT AMPLIFIERS** BRAND NEW **8Gns.** Carr. 6/6  
**EX-GUITAR AMPLIFIERS** 6/6  
Manufacturers' discontinued Model. Push-pull output. Latest high efficiency valves Dual separately controlled inputs for 'Mikes' and gram. Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohms speaker. Guaranteed tested and in perfect working order.

**R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)**

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened.  
**TOP SHROUDED DROPT THROUGH**  
250-0-250v. 70mA, 6.3v. 2a. 0-5-6.3v. 2a 17/8  
350-0-350v. 80mA, 6.3v. 2a. 0-5-6.3v. 2a 21/8  
250-0-250v. 100mA, 6.3v. 2a. 6.3v. 1a. 21/8  
250-0-250v. 100mA, 6.3v. 3.5a. C.T. 19/9  
250-0-250v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a 28/9  
300-0-300v. 130mA, 6.3v. 4a. 6.3v. 1a. (or Mullard 510 Amplifier) 35/9  
300-0-300v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a 28/9  
350-0-350v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a 28/9  
350-0-350v. 150mA, 6.3v. 4a. 0-5-6.3v. 3a 37/9  
**FULLY SHROUDED UPRIGHT**  
250-0-250v. 60mA, 6.3v. 2a. 0-5-6.3v. 2a 18/9  
Midget type 2 1/2 x 3 1/8in. 18/9  
250-0-250v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a 29/9  
300-0-300v. 100mA, 6.3v. 4a. 5v. 3a 29/9  
300-0-300v. 130mA, 6.3v. 4a. C.T. 6.3v. 1a. (or Mullard Amplifier) 36/9  
350-0-350v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a 29/9  
350-0-350v. 150mA, 6.3v. 4a. 0-5-6.3v. 3a 38/9  
425-0-425v. 200mA, 6.3v. 4a. C.T. 5v. 3a 57/9  
425-0-425v. 200mA. (6.3v. 4a Twice). 5v. 3a 58/9  
450-0-450v. 250mA, 6.3v. 4a. C.T. 5v. 3a 69/9

**MIDGET MAINS TRANS** 2 1/2 x 2 1/2 x 2 1/2in. 250v. 60mA 6.3v. 2a 13/9  
250-0-250v. 60mA, 6.3v. 2a 14/9  
**OUTPUT TRANSFORMERS**  
Standard Pentode 5,000Ω to 3Ω .. 5/9  
Standard Pentode 7,000Ω to 3Ω .. 5/9  
Push-Pull 8 watts, EL84, or 6V6 to 3Ω or matched to 15Ω .. 9/9  
Push-Pull 10-12 watts to match 6V6 or EL84 to 15Ω .. 10/9  
Following types for 3 and 15Ω speakers  
Push-Pull 10-12 watts. 6V6 or EL84 .. 18/9  
Push-Pull 15-18 watts. 6L6, K706 .. 22/9  
Push-Pull Mullard 510 Ultra Linear .. 28/9  
Push-Pull 20 watts, sectionally wound 6L, KT66, EL84 etc. .. 49/9  
**SMOOTHING CHOKES**  
60mA, 10H 400 4/11, 100mA, 10H, 200Ω 8/9  
60mA, 10H 350Ω 5/9, 150mA, 10H, 250Ω 11/8  
**CHARGER TRANSFORMERS**  
All with 200-230-250v. 50 c/s Primaries:  
0-9-15v. 11a, 12/9; 0-9-15v. 2a, 14/9; 0-9-15v. 3a, 18/9; 0-9-15v. 5a, 19/9; 0-9-15v. 6a, 23/9  
0-9-15v. 8a, 28/9.  
**AUTO (Step up/Step down) TRANS.**  
0-110/120-230/250v. 50-80 watts, 13/9; 150 watts 27/9; 250 watts, 49/9; 500 watts 99/9  
**MIKE TRANSFORMERS** 12B1 8/9.

**TWEETERS** R.A. 3 ohm 25/9 15 ohm 25/9  
12" R.A. DUAL CONE SPEAKERS 39/9  
12" watt 3 ohm Ideal for Stereo each

**FANE HEAVY DUTY HI FI SPEAKERS**  
12" 20 watt Type 122/10 Only 5 Gns.

**R.S.C. POWER PACK.** 39/9. Louvred metal case only 8 x 5 1/2 x 2 1/2in. Silver plated. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA. fully smoothed at 6.3 v. 2a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

**ARMSTRONG, TRUVOX, LEAK, QUAD, ROGERS, LINEAR, W.B., FANE, WHARFEDALE, GOODMAN'S GARRARD, GOLDRING, GRAMPIAN, LUSTRAPHONE, SHURE, RESLO, TANDBERG, FERROGRAPH Products stocked. Usual credit terms available.**

**SPECIAL PURCHASE OF TRUVOX D84 4-TRACK TAPE DECKS** Carr. 7/8  
3 speeds 7; 3; 1 1/2 p.s.  
Brand New and Boxed Only (Normal price over £30) **21 Gns.**

**LINEAR TREMOLO/PRE-AMP UNIT**  
Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interruptions), Depth (of heavy or light effect), Volume and Switch. **4 Gns.**

**SCOOP PURCHASE OF HIGH QUALITY RECORD CHANGERS** Carr 5/6  
Brand new Garrard 3000LM. Very latest model. Normal Retail price approx. £12.15.3  
Heavy Turntable and light weight pick-up arm. High fidelity Stereo/Mono cartridge. Fully guaranteed. **11 Gns.**

**R.S.C. 4/5 WATT AS HIGH-GAIN AMPLIFIER**

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high-fidelity pick-up heads in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down 14 dB of Negative Feedback is used. H.T. of 300v. 20mA and L.T. of 6.3v. 1.5a is available for the supply of a Radio Feeder Unit or Tape-Deck pre-amplifier. For A.C. mains 200-230-250v. 50 c/s. Output for 2-3 ohms speaker  
Chassis is not alive. Kit is complete in every detail with fully punched Gold Hammer finished chassis, point-to-point wiring diagrams and instructions. Exceptional value for use as extra or assembled ready for use. Deposit 22/6 and 5 monthly payments of 22/6 (Total £6.15.0) for assembled unit. **£4-15-0**

**R.S.C. GRAM AMPLIFIER KIT.** 3 watts output. Negative feedback. Controls Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr 3/9.

**4 1/2A MINIATURE 2-3 WATT GRAM AMPLIFIER.** For use with any single or auto-change unit. Output for 2/3 ohm speaker. For 200-250v. A.C. mains. Size 1 1/2 x 2 1/2 x 2 1/2in Volume and Tone Controls with Switch. **59/6**

**COMMUNICATION RECEIVERS**


**RX60 DELUXE 4 BAND** 220/240v 50/60 c.p.s. A.C. mains operation. Frequencies covered 1600 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial 1 1/2 meter. Internal ferrite aerial for medium wave. Telescopic whip aerial 58in. 10 section for short waves. Fitted sockets for optional outdoor aerial. Headphones, external speaker socket. Other features are electrical handspread tuning. Noise limiter. A.V.C., B.F.O., stand by switch. Size approx. 12 1/2 x 5 1/2 x 8 1/2in. Crackle finished metal with full instructions manual and guarantee **19 Gns.** Carr. & 10/6

**VACANCIES FOR PERMANENT STAFF AT VARIOUS BRANCHES**

**R.S.C. 4 WATT GRAM AMPLIFIER KIT.** Complete set of parts to build a good quality compact unit suitable for use with any record playing unit. Mains isolated chassis. Separate Bass and Treble controls. Output for 2-3 ohm speaker. For 200-250v. A.C. **59/9**

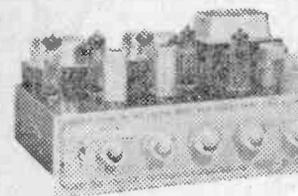**R.S.C. BABY ALARM or INTER-COMM KIT.** Complete set of parts with diagrams etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 270-250v. A.C. mains. Fully isolated. Controllable at both units. An intercom of this class would normally cost £20-£30. Only 89/6 carr. 5/- Ready for use. **6 Gns.**

**R.S.C. BATTERY TO MAINS CONVERSION UNITS.** Type BML. An all-dry battery eliminator. Size 9 1/2 x 4 1/2 x 2 1/2in. approx. Completely replaces batteries supply 1.4v and 90v where A.C. mains 200-250v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4v. and 90v. Complete kit with diagram 38/9 or ready for use 48/9



## R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

PROVIDING 10/14 WATTS ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL

SUITABLE FOR "MIKE" GRAM, RADIO OR TAPE. INTENDED FOR THE HOME OR STUDIO BUT SUITABLE FOR LARGE HALLS OR CLUBS

- ★ Four-position tone compensation and Input Selector switch.
- ★ Will amplify direct from Tape Heads.
- ★ Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.
- ★ Separate Bass "Lift" and "Cut" and Treble "Lift" and "Cut" controls.
- ★ Neon panel indicator.
- ★ Handsome Perapex Frontplate.

Based on a current Mullard design and employing valves ECC83, ECC85, ECL86, ECL84, ECL86, E2B1. Output transformers are high-quality sectionally wound to required specification. Output matchings for 3 and 15 ohm speakers on each channel. (Carr. 10/-) Complete set of parts with point-to-point wiring diagrams and instructions, or Factory assembled, tested and supplied with our usual 12 months guarantee for 18gns. or DEPOSIT 57/- and 9 monthly payments of 39/10 (total £20.15.6).

FREQUENCY RESPONSE  $\pm 2$ dB. 30-20,000 c.p.s.  
HUM LEVEL 65dB down.  
SENSITIVITY: 5 millivolts maximum.  
HARMONIC DISTORTION (each channel) 0.2%.

**13 Gns.**

## AUDIOTRINE HI-FI TAPE RECORDER KIT 25<sup>1</sup> Carr. 17/6. 2<sup>2</sup> Gns.

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR. Incorporating the latest Collaro Studio Tape Transcriber. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty 12" Cassette Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet tastefully covered in two contrasting shades of Rexine and Vynair Size 14 $\frac{1}{2}$  x 15 x 8 $\frac{1}{2}$ in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. **TERMS: Deposit 4gns. and 12 monthly payments of 42/- (Total 26 Gns.)**



ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS

## R.S.C. A10 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response  $\pm 3$  dB 30-20,000 c.p.s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, BASS, LEAD or RHYTHM GUITAR, STRING BASS etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES 2, 2, and 4, 7, for**

RADIO FEEDER UNIT, An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50 cts. A.C. Mains output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and (Carr. 10/-) instructions. Supplied factory built with EL34 output valves and 12 months' guarantee for 14 Gns. If required perforated cover with carrying handles can be supplied for 19/9. Send S.A.E. for leaflet, also speaker. **TERMS: DEPOSIT 45/- and 9 monthly payments of 32/4 (Total 16 gns.)**

## INTEREST CHARGES REFUNDED

on H.P. and CREDIT SALE Accounts settled in 6 months.

LINEAR TAPE PRE-AMPLIFIER, Type LP/1. Switched Equalisation. Positions for Recording at 15in., 3in., 7in. per sec. and PlayBack. EMed Resonance Level Indicator. Designed primarily as the link between a Collaro Tape Deck 9 $\frac{1}{2}$  Gns. and Hi-Fi amplifier, suitable almost any Tape Deck. S.V.E. for leaflet. **9 $\frac{1}{2}$  Gns.**


## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, E2B1. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut"** Frequency response  $\pm 3$  dB 30-20,000 c.p.s. Six negative feedback loops. Hum level 60 dB down. **OUTPUT** 23 millivolts input required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for **STANDARD or LONG PLAYING RECORDS, FOR MUSICAL INSTRUMENTS such as STRING BASS, LEAD or RHYTHM GUITARS, etc.** **OUTPUT SOCKET** with plus provides 300v. 30mA. and 6.3v 1.5a. for supply of a **RADIO FEEDER UNIT**. Size approx. 12 x 9 x 7in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohms speaker. Kit is complete to last unit. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. **Only 8 Gns.** Carr. 10/- (Or factory built 51/6 extra).

If required louvred metal covers with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS. DEPOSIT 33/3 and 9 monthly payments of 24/1 (Total £12.10.0).** Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Mikses, etc.
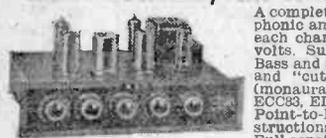
## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereo-ophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation for "Lift" and "Cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E2B1. Outputs for 2-3 ohm speakers **Point-to-Point wiring diagrams and instructions supplied.** Send S.A.E. for leaflet. Full constructional details and price list 2/6. **8 Gns.** Carr. 10/-

Or supplied factory assembled with 12 months' guarantee for £11.7.6. **8 Gns.** Carr. 10/- **TERMS: Deposit 2 gns. and 9 monthly payments of 24/2 (Total £12.10.0).**

### S4/4 STEREO AMPLIFIER

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 8 watts. For A.C. mains input of 200-250 v. Sensitivity 150 m.v. Ganged Volume and Tone Controls. Preset balance control. Full instructions and wiring diagram supplied. **5 Gns.**

Always in Stock at keen prices **SINGLE and AUTO RECORD PLAYING UNITS, PICK-UPS, CARTRIDGES, MICROPHONES, CABINETS VALVES and COMPONENTS TOO NUMEROUS TO LIST**

## 12in. 10 WATT HIGH QUALITY LOUDSPEAKER

In walnut veneered cabinet. Gauge 12,000 lines. Speech coil 3 ohms or 15 ohms. Only **£4.19.6** Carr. 5/6 **TERMS: Deposit 11/3 and 9 monthly payments of 11/3 (Total £5.12.6).**

**12in. 20 WATT HI-FI LOUDSPEAKERS IN CABINETS**, Size 18 x 18 x 10in. Finish as above. **£7.19.6** Carr. 8/6 **TERMS: Deposit 17/9 and 9 monthly payments of 17/9 (Total £8.17.6).**

**W.B. "STENTORIAN" HIGH FIDELITY P.M. SPEAKERS HF1012**, 10 watts rating. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. Please state 2, 4 or 8 ohms or 3 or 15 ohm required. **£4.19.6**

**R.S.C. JUNIOR BASS REFLEX CABINET**. Designed for above speaker, but suitable for a good quality 8in. or 10in. speaker. Accoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Strongly made. Handsome appearance. Superb reproduction. **£4.7.6**

**R.S.C. STANDARD BASS REFLEX CABINET**. For 12in. loudspeaker acoustically lined and ported. Size 20 x 14 x 12in. Beautifully finished. **£5.19.6** Carr. 7/6

**SENIOR MODEL**. To take up to 12in. speaker and 18" Tweeter cut-out. Size approx. 30 x 30 x 15in. (Recommended for use with Audiotrine speaker system). Carr. 8/6. **8 Gns.**


**AUDIOTRINE HI-FI SPEAKER SYSTEMS**. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit consisting of choice, condenser, etc.) and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. **£4.19.9** Carr. 5/7

Or Senior 20 watt, **£6.10.8**. Carr. 7/6.


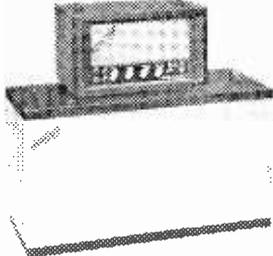
# R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT  
For lead, rhythm, bass guitar and all other musical instruments  
For vocalists, gram, radio, tape and general public address



- \* UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 20 watt unit with extended frequency response. 4 Jack Socket Inputs and two independent Volume Controls for simultaneous use of up to 4 pick-ups or 'mikes'.
  - \* Separate cabinets fully covered in contrasting tones of Rexine/Vynair with gold trimming for speakers and amplifiers.
  - \* Separate Bass and Treble Controls giving 'Boost' and 'Cut'.
- Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at more than three times the cost.  
**49 Gns.** Or deposit £7.16.0 and 12 monthly payments of 81/6 (Total 54 Gns.)

**49 Gns.** Or deposit £7.16.0 and 12 monthly payments of 81/6 (Total 54 Gns.)

## TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 standard jack inputs, i.e. mic., tape, gram, tuner, etc., into single output. Compact and completely self-contained uses standard 9 volt battery.  
**49/9** Post 3/6

Full range of FANE and GOODMAN Speakers in Stock and all type 'Mikes'. Credit terms if required.

## R.S.C. B20 MULTI-PURPOSE AMPLIFIER

especially suitable for Bass Guitar  
A highly efficient unit incorporating massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample 'Boost' and 'Cut'. Two jack socket inputs separately controlled. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13ins. Send S.A.E. **29 1/2 Gns.** Carr. 17/6  
Or deposit £4.14.6 and 12 monthly payments of 49/- (Total 32 1/2 gns.)



## R.S.C. G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, 'Mike', Gram or Radio

High-fidelity push-pull output. Separate bass and treble 'Cut' and 'Boost' controls. Twin separately controlled inputs so that two instruments or 'mike' and pick-ups can be used at the same time. Loudspeaker is a heavy duty flux 12in. 20 watt model with cast chassis. Cabinet is covered in contrasting shades of Rexine/Vynair. Size approx. 18 x 18 x 8in. **19 Gns.** Carr. 10/-  
Or deposit £2.12.6 and 12 monthly payments of 31/6 (Total 21 gns.) Send S.A.E. for leaflet.

## R.S.C. G5 AMPLIFIER

4 watt high quality output. Incorporating high flux 12in. 10 watt loudspeaker. Sensitivity 40 mV. High impedance jack input. Handsome cabinet (size 14x14x7in. approx.) finished in Rexine/Vynair. 200-250V. A.C. mains. Suitable for Lead or Rhythm Guitar in home or small club etc.  
**£9.19.6** Or Deposit 30/9 and 9 monthly payments of 22/3 (Total 11 Gns.) Carr. 7/6.

## R.S.C. BATTERY CHARGING EQUIPMENT

Guaranteed 12 month All for A.C. Mains 200-250 v., 50cs.  
Assembled 4amps/6/12v. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case finished attractive hammer blue. Fused, ready for use with mains and output leads.  
**39/9** Carr. 3/6  
6/12v. 1 amp 27/9 Less meter.  
Also selector plug for 6 v. or 12 v. Louvred metal case finished attractive hammer blue. Fused, ready for use with mains and output leads.  
**59/9** Carr. 4/6  
Terms: Deposit 12/- and 5 monthly payments of 12/- Total £3.12.0



## BULK PURCHASE OF FAMOUS MAKE

Heavy Duty 12" 25 watt 1700 Line Loudspeakers List Price approx. £12 Limited Stocks at  
carr. 10/- **£6.19.6**

## MAGNAVOX STUDIO TAPE DECKS

3 speed Twin Track Model. Few only at  
carr. 8/6 **£12.19.6**

## PRINTED CIRCUIT KIT Only 16/9


Etch your own circuits. Kit includes 72sq. in. Laminate. Fluids, Brush and instructions.

## SPECIAL PURCHASE OF RECORD PLAYING UNITS

- B.S.R. AC25 4-SPEED AUTO-CHANGERS with hi-fi turnover head, £5.19.6. Carr. 5/6.
- GARRARD AUTO-SLIM 4-SPEED AUTO-CHANGER with high fidelity pick-up. Latest model. For 200-250 v. A.C. mains, £6.19.6. Carr. 5/6.
- GARRARD AT6 AUTO-SLIM DELUXE 4-SPEED AUTO-CHANGERS. Turnover CCB head. For 200-250 v. A.C. mains, 11 Gns. Carr. 5/6.
- COLLARO JUNIOR. 4-speed Single Player Unit and Crystal Pick-up with hi-fi Turnover head. Only 65/-.
- HI-FI CRYSTAL PICK-UP HEADS (Cartridges) Acos Standard replacement for Garrard, B.S.R. and Collaro, 16/9. Acos Stereo-Monaural, 29/9. Konette. Stereo-Monaural 39/9. B.S.R. Stereo 39/9.
- BRADMATIC RECORDING HEADS. High Impedance Record/Playback 22/-, Low Impedance Erase, 12/6.
- PICK-UP ARMS. Complete and with latest Acos/hi-fi Turnover Cartridge 29/11.
- CRYSTAL MICROPHONES. Hand type NP110 14/9. R.T.C. 19/9. Acos Mic 40 25/9. Acos Mic 45 29/9. Stick type Acos 39-1 39/9. BM3 with neck band 39/9. Lapel type 29/9.
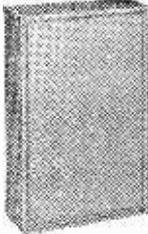
## AUDIOTRINE 3D-1 SPEAKER SYSTEM

A complete three diaphragm high fidelity loudspeaker unit designed to occupy a minimum of space. Depth is only approx. 6in. Height, 24in. Width 15in. This has been made possible by the latest developments in loudspeaker design. The 12in. cast chassis bass unit has a resonant frequency which is extraordinarily low. It has a second diaphragm which extends the frequency range to 17,000 c.p.s. A further speaker operates only on the middle frequencies and ensures a smooth response from 49-17,000 c.p.s. Rating 20 watts. Imp. 15 ohms. Cabinet finish is either polished walnut veneer, or leathercloth to match stereo/20 cabinet. Highly recommended for a Stereo or Mono amplifier. Surely the best value ever at  
**11 gns.** carr. 8/6  
Terms: Deposit 2gns. and 9 monthly payments 24/6 (Total £13.2.6.)



INTEREST CHARGES REFUNDED ON H.P. ACCOUNTS SETTLED IN 6 MONTHS



Addresses Page 551

## R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100v. line for 35/- extra.  
Type C58, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5in.  
**12 1/2 Gns.** Carr. 10/- £2 and 9 monthly payments of 27/9 (Total £14.9.0).  
Type C412, 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 56 x 14 x 9in. approx. **19 1/2 Gns.** Carr. 15/- £7  
Or deposit of 43/2 (Total 211 gns.)

## 30 WATT HIGH QUALITY AMPLIFIER FOR LEAD, RHYTHM and BASS GUITAR and VOCAL or INSTRUMENTAL GROUPS.

A Four Input, two volume control Hi-Fi unit with separate Bass and Treble 'Cut' and 'Boost' controls. Designed for vocal or instrumental groups. For Bass, Lead or Rhythm Guitar, Muffled or Brimar latest type valves. Housed in strong Rexine covered cabinet with twin carrying handles. Attractive black and gold perspex fascia plate. For 200-250V. A.C. mains. Output for 15 ohm speakers. Send S.A.E. for leaflet.  
Or deposit £3 and 9 monthly payments of 37/- (Total £19.13).  
**17 Gns.** Carr. 12/6.

## HEAVY DUTY CHARGER KIT

6/12 v. 6 amps, variable output. Consisting of Mains Transformer 0-200-230-250 v.; F.W. (Bridge) Selenium Rectifier; Ammeter, Variable Charge Rate Selector Panel; Plugs, Fuses, Fuseholder and Circuit. Carr. 3/6  
**59/9**  
F.W. (BRIDGED) TYPES  
6/12v. 1a. 3/11 6/12v. 3a. 9/9 6/12v. 5a. 15/3  
6/12v. 2a. 6/11 6/12v. 4a. 12/3 6/12v. 10a. 26/9  
6/12v. 15a. 35/9

## SELENIUM RECTIFIERS

Consisting of Mains Trans. Metal Rectifier and circuit. For 200/250 v. A.C. mains. Output 250 v., 60 mA. 6.3 v., 2a.  
**19/11**

## COMPLETE POWER PACK KIT


Consisting of Mains Trans., Metal Rectifier, Double electrolytic smoothing choke, chassis and circuit. For 200/250 v. A.C. mains. Output 250 v., 60 mA. 6.3 v., 2a.  
**19/11**

## BRUSH HAMMER PAINT 3/9

Silver, Grey or Blue (9d. Post) **TIN**

## MAINS NEON INDICATORS 3/11

Red, Amber, White post 6d

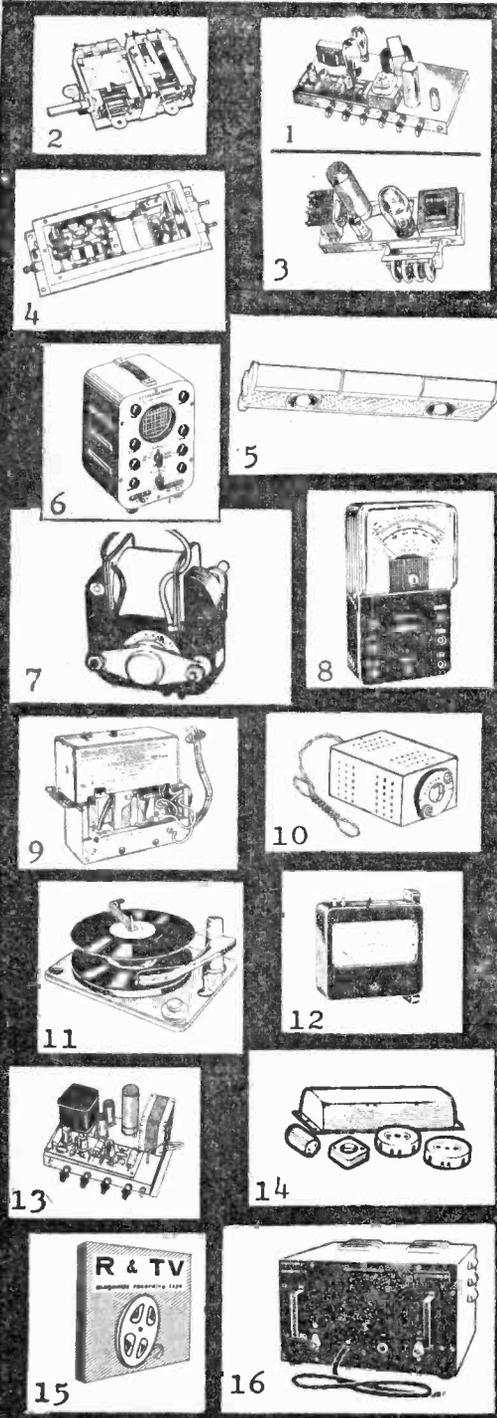

1. **6 VALVE 15 WATT PUSH-PULL AMPLIFIER.** 15 x 7 x 1 1/2in. A.C. Mains 200-250 volts. 4 inputs with controls for same and bass and treble hit controls. Tapped for 3 and 15 ohm speakers. Extra H.T. and L.T. for F.M. Tuner supplies etc. Built and tested. 7 gns. P. & P. 18/8.
2. **CYLDON A.M.F.M. PERMEABILITY TUNERS FOR ALL TRANSISTOR OPERATION.** Size 2 1/2 x 2 1/2in. approx. By famous manufacturer. A.M. I.F. 470 Kcs. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1620 Kcs/-525 Kc/s. F.M. coverage 108 Mc/s-88Mc/s. Circuit diagrams 9/6. FREE with Tuner, 1st, 2nd and 3rd A.M. I.F.'s, 1st, 2nd, 3rd and 4th F.M. I.F.'s V.H.F. Osc. chucks, A.M. I.F. trap. All the above are the R.P. end of an A.M.-F.M. receiver car radio etc. The above items, £2.10.0.
3. **AMPLIFIER KIT.** 3 to 4 watt Amplifier Kit. Comprising chassis 8 1/2 x 2 1/2 x 1 1/2in. Double wound mains transformer, output transformer, volume and tone controls, resistors, condensers etc. Valves 6X5, ECC81 and uctal rectifier. Circuit 1/6. free with kit. 29/6 plus 4/6 P.&P.
4. **TRANSISTOR INVERTOR.** 50 v. D.C. Input. Output 240 v. A.C. 40 watts incorporating transformers, choke, condensers and 2 GET573. In solid 16 gauge aluminum case, size 15 x 6 x 2 1/2in. by famous manufacturer, 19/6, plus 7/- P. & P.
5. **FLUORESCENT LIGHT FITTING.** Twin 40 watt 200/250 v. less tubes. 39/6. P. & P. 7/-.
6. **OSCILLOSCOPE FOR D.C. and A.C. APPLICATIONS.** Push-pull X amplifier. Fly-back suppression. Internal Time-base Scan Wave form available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external—L.P. and R.T. Brightness Modulation. A.C. mains 200-250 v., £18 13.0. P. & P. 10/- FULL 12 MONTHS' GUARANTEE INCLUDING VALVES and TUBE.
7. **A.C. MAINS MOTOR.** Can be used for a variety of purposes, silent running, satisfactory in every way. 230/250v. A.C., 9/6. P. & P. 3/-.
8. **POCKET MULTI-METER.** Size 3 1/2 x 2 1/2 x 1 1/2. Meter size 2 1/2 x 1 1/2in. sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts: 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100k Ohm. Complete with test probes, battery and full instructions. 42/6. 1. & P. 3/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.
9. **CHANNEL TUNER I.F.** 16-19 Mc/s. Continuously tunable from 174-218 Mc/s. Valves required—PCF40 and PCU24 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/-, P. & P. 3/-.
10. **POWER SUPPLY KIT** in metal case, size 3 1/2 x 2 1/2 x 2in. Incorporating mains transformer, rectifier and condensers. 230/250 A.C. mains. Output: 9v., 100mA. 10/6 plus 3/- P. & P.
11. **B.S.R. MONARCH UA14 WITH FULL FI HEAD.** 4-speed, plays 10 records 12in. 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Internals 7in., 10in. and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12 1/2 x 10 1/2in. Space required above baseboard 4 1/2in. below baseboard 2 1/2in. Fitted with Full FI turnover crystal head. £5.19.6. P. & P. 7/6.
12. **50 MICRO-AMP METER** movement by world famous manufacturer. Size 3 x 2 1/2in. 25/-, plus 2/- P. & P.
13. **8-WATT 5-VALVE PUSH-PULL AMPLIFIER & METAL RECTIFIER.** Size: 9 x 6 x 1 1/2in. A.C. Mains, 200-250v. 6 valves. For use with 8rd. or L.P. record reproducing instruments, also makes of pick-ups and solen. Output 8 watts at 3 percent total distortion. Separate bass and treble hit controls. Two inputs, with controls for gain, and noise. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. £8.19.6. P. & P. 2/-.
14. **40W. FLUORESCENT LIGHT KIT** incorporating GEC Choke size 8 1/2 x 1 1/2 x 1 1/2in. 2 bi-pin holders, starter and starter holder, 11/6. P. & P. 4/6. Similar to above: 80W Fluorescent Light Kit incorporating GEC choke size 11 1/2 x 1 1/2 x 1 1/2in. 2 bi-pin holders, starter and starter holder 17/6. P. & P. 5/6.
15. **FIRST QUALITY PVC TAPE**

5 1/2in. Std. 850ft.	.. 9/-	6in. L.P. 850ft.	.. 10/6
7in. Std. 1200ft.	.. 11/8	6in. T.P. 600ft.	.. 8/-
6in. L.P. 240ft.	.. 4/-	6in. T.P. 1800ft.	.. 20/8
5 1/2in. L.P. 1200ft.	.. 11/8	5 1/2in. T.P. 2400ft.	.. 27/6
7in. L.P. 1800ft.	.. 18/6	7in. T.P. 2800ft.	.. 37/6

P. & P. on each 1/6. 4 or more Post Free.
16. **FIXED FREQUENCY SIGNAL GENERATOR.** Crystal control in metal case, size 10 x 6 x 4in. Incorporating two PC13 valves, mains transformer, metal rectifier, choke, indicator, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new. 39/6, plus 7/- P. & P. A.C. mains 200-250 volts.

SILICON RECTIFIERS. 250v. P.I.V. 750 mA. Six for 7/6 post paid.

**RADIO & T.V. COMPONENTS (ACTON) LTD.**  
 21b High Street, Acton, London, W.3.  
 All enquiries S.A.E. Goods not despatched outside U.K.  
 Shop hours 9 a.m.—6 p.m. Early closing Wednesday

# SPECIAL OFFER! FROM R. & T.V. LTD.



## COMBINED PORTABLE & CAR RADIO

**4in. SPEAKER** The Radio with the STAR features


- ★ 7-transistor superhet. Output 350mV.
- ★ Grey wooden cabinet, fitted handle with silver coloured fittings. Size 12¼ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 11¼ x 2⅝ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial
- ★ I.F. neutralisation on each stage 460 kc/s.
- ★ D.C. coupled output stage with separate A.C. negative feed back.
- ★ All components, ferrite rod and tuning assembly mounted on printed board.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.

ONLY **£4.4.0**

Plus 6/6 P & P. Parts list & circuit diagram 2/6. FREE with parts.

SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer, etc. A.C. mains 200-250v. Output 9v. 50mA. 7/6.

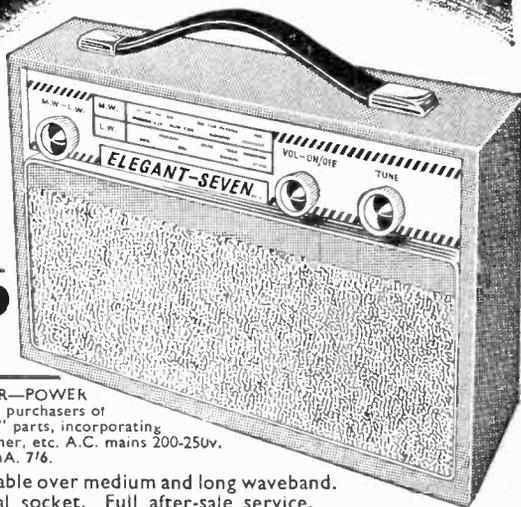- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket. Full after-sale service.



## RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed. Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O.

**THE  
PEMBRIDGE  
COLLEGE  
OF ELECTRONICS  
PROVIDES TRAINING  
IN RADIO  
AND TELEVISION**

### FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 5th January, 1966

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.


Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:  
**The Pembridge College of Electronics (Dept. P11)  
34a Hereford Road, London, W.2.**

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
\_\_\_\_\_
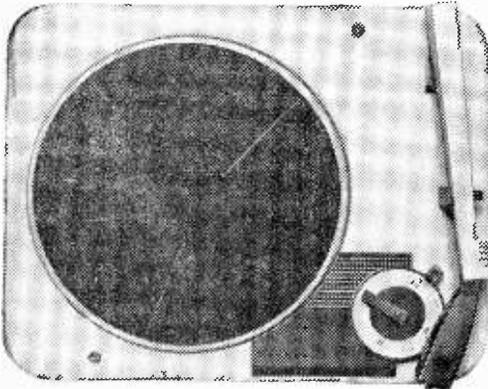
## An integrated hi-fi turntable unit from only 11 gns?



### YES!

Only Goldring's 60 years of experience of making gramophone turntables and pick-ups could lead to a unit like this... the ideal integrated turntable, arm and pick-up for do-it-yourself hi-fi aspirants... at such a modest price. Just look at the features of this remarkable G.66 unit:

Silent, specially made Swiss mains motor. Pressed steel turntable on precision bearings evens out mains current fluctuations. Die-cast light alloy arm with full stylus pressure adjustment. Plug-in head shell, wired for mono and stereo, takes alternative pick-up cartridges. Eddy-current speed control (as fitted on some professional units) varies the four standard speeds by  $\pm 10\%$ . Pick-up raising/lowering device coupled to on/off switch and idler-wheel disengagement mechanism. Deck size  $12\frac{1}{2} \times 10$ ".

See the Goldring G.66 at your dealers—or write for descriptive leaflet.

### THE GOLDRING G.66

G.66/MX.2 £9.18. 8 + £1.12.4 P.T. £11.11.0

G.66/CS.80 £10.10. 0 + £1.14.2 P.T. £12. 4.2

G.66/CS.90 £12.12.10 + £2. 1.2 P.T. £14.14.0



Goldring Manufacturing Co. (GB) Ltd.,  
486-488 High Road, Leytonstone, London E.11  
Telephone: Leytonstone 8343

## SHORT WAVE MAGAZINE

- Covers the whole field of Amateur Radio
- Is now in its 28th Year and 23rd Volume
- Runs 64 pages every Month
- Circulates in more than 75 Countries
- Is Independent and Unsubsidised
- Prints Constructional, Practical and Theoretical Articles on Amateur Transmission
- Includes Regular Activity Features
- Is Entirely Devoted to Amateur Radio
- Stocks most American Radio Books and Manuals
- Costs 42s. a Year (\$6.00 U.S.) by Subscription
- Is obtainable to order through any Retail Newsagent (3s. 6d.)

(Specimen Copy 3s. 6d.)

55 Victoria Street,  
London, S.W.1.



### For quick, easy faultless soldering

Ersin Multicore 5-core solder is easy to use and economical. It contains 5 cores of non-corrosive flux, cleaning instantly, heavily oxidised surfaces.

No extra flux is required.



#### HANDY SOLDER DISPENSER

12 ft. of 18 s.w.g. SAVBIT alloy in a continuous coil, used direct from free-standing dispenser.  
2/6 each



#### LOW TEMPERATURE SOLDER

Size 9 pack contains 24 ft. of 60/40 high tin quality 22 s.w.g.  
2/6 each  
Size 10 pack 212 ft. 15/- each.



#### SAVBIT SIZE 1 CARTON

Contains approx. 30 ft. of 18 s.w.g. SAVBIT alloy. Also available in 14 and 16 s.w.g.  
5/- each



#### BIB WIRE STRIPPER AND CUTTER

Strips insulation, cuts wire cleanly. Adjusts to any size.  
3/6 each

Available from all Electrical and Hardware shops.  
If unobtainable write to:

**MULTICORE SOLDERS LTD.**

Multicore Works, Hemel Hempstead, Herts. Hemel Hempstead 3636 M.4



# Why anyone can build a Heathkit model—and save money

The success of a **HEATHKIT MODEL**

is assured by the world-famous **HEATHKIT MANUAL**

- 1—Clear, step-by-step instructions enable assembly of models without difficulty.
- 2—Components are pictured with full size drawings enabling easy identification.
- 3—Extra large Pictorials illustrate clearly, each step given in text.
- 4—All manuals give operation and adjustment instructions.

**A KIT FOR EVERY INTEREST . . . HOME, SERVICE WORKSHOP, LABORATORY**

## AUDIO HI-FI



FM Tuner

**F.M. TUNER** (in two parts)  
Total price Kit £16.8.0, incl. P.T.  
**AM/FM TUNER** (in two parts)  
Total price Kit £27.5.0, incl. P.T.

- 6W STEREO AMPLIFIER, S-33H.**  
Kit £15.17.6 Assembled £21.7.6
- 18W STEREO AMPLIFIER, S-99.**  
Kit £28.9.6 Assembled £38.9.6
- 6W STEREO AMPLIFIER, S-33**  
Kit £13.7.6 Assembled £18.18.0
- 40W ALL TRANSISTOR STEREO AMPLIFIER, AA-22U**  
Kit £43.18.0 Assembled £68.16.0
- 5W MONO AMPLIFIER, MA-5**  
Kit £10.19.6 Assembled £15.10.0
- 10W POWER AMPLIFIER, MA-12**  
Kit £11.18.0 Assembled £15.18.0
- 50W POWER AMPLIFIER, MA-50**  
Kit £19.18.0 Assembled £27.18.0
- MONO TAPE PRE-AMPLIFIER, TA-1M**  
Kit £19.18.0 Assembled £28.18.0
- NEW "STUDIOMATIC" TAPE DECK (MONO)**  
£14.19.6
- LOW PRICED SPEAKER SYSTEM, SSU-1**  
Legs 14/6 extra. Kit £11.17.6, incl. P.T.

A range of Record Players, Cabinets, Mics, etc.

## TEST & SERVICE INSTRUMENTS



10-12U

- 5" OSCILLOSCOPE, 10-12U (TB 10c/s-500kc/s)**  
Kit £35.17.6 Assembled £45.15.0
- 2 1/2" PORTABLE "SCOPE OS-1**  
Kit £22.18.0 Assembled £30.8.0
- 4 1/2" VALVE VOLTMETER, V-7**  
Kit £13.10.6 Assembled £19.18.6
- 6" VALVE VOLTMETER, 1M-13U**  
Kit £18.18.0 Assembled £26.18.0
- REGULATED POWER SUPPLY, IP-20U (Transistorised)**  
0.5-50v d.c. to 1.5A Kit £35.8.0 Assembled £47.8.0
- TV ALIGNMENT GENERATOR, HFV-1 (3.6-220M cs)**  
Kit £37.18.0 Assembled £47.10.0
- RF SIGNAL GENERATOR, RF-1U (Up to 100Mc/s fund)**  
Kit £13.8.0 Assembled £19.18.0
- MULTIMETER, MM-1U (wide V. A. res, dB ranges)**  
Kit £12.18.0 Assembled £18.11.6

## HARMONIC DISTORTION METER, 1M-12U



Enables, fast, accurate noise and distortion measurements to be made in amplifiers, etc.

Send for Full Details.

Kit £24.15.0 Assembled £34.0.0

Other instrument kits include: R/C Bridge, C-3U, £10.10.0. Wattmeter, AW-1U, £17.5.0. Cap. Meter, CM-1U, £15.15.0. Transistor Tester, 1M-30U, £24.18.0.

Power Supplies, Decade R and C Boxes, etc.

Many other instruments in the American range. Full details and catalogue, 1/-, post paid.



## TRANSISTOR MIXER TM-1

A must for the tape enthusiast! 9v. battery. Beautiful walnut cabinet, 4 channels.  
Kit £11.16.6 Assembled £16.17.6

## 'AMATEUR' EQUIPMENT

A wide range of models including:

- AMATEUR BANDS RECEIVER, RA-1 (160-10 m).**  
Kit £39.6.6 Assembled £52.10.0
  - COMMUNICATION TYPE RECEIVER, RG-1 (600kc/s-1.5Mc/s 32Mc/s-1.7 Mc/s)**  
Kit £39.16.0 Assembled £53.0.0
  - AMATEUR TRANSMITTER, DX-100U (160-10 m)**  
Kit £79.10.0 Assembled £104.15.0
  - AMATEUR TRANSMITTER, DX-40U (80-10 m).**  
Kit £33.19.0 Assembled £45.8.0
- Other kits in range include: SSB Adaptor, SB-10U £39.5.0.  
Variable Freq. Oscillator, VF-1U, £10.17.6. Balun Coil Unit, B-1U, £4.15.6. Grid-Dip Meter, GD-1U, £10.19.6. Multiplier, QPM-1 £8.10.0 Reflected Power Meter, HM-11U, £8.5.0.  
Also wide range of American models. Please send for details.

## TRANSISTOR RADIOS



- "OXFORD" LW/MW RECEIVER, UXR-2**  
Kit £14.18.0, incl. P.T.
  - 6 TRANSISTOR PORTABLE, UXR-1, LW/MW.** Kit £12.11.0, incl. P.T.
  - "MOHICAN" GENERAL COVERAGE RECEIVER, GC-1U**  
Kit £37.17.6 Assembled £45.17.6
  - ELECTRONIC WORKSHOP, EW-1 (Experimental Kit)**  
Kit £7.13.6, incl. P.T.
  - JUNIOR RADIO, UJR-1**  
Kit £2.7.6, incl. P.T.
- Headphones 30/- extra. Additional amplifier stage (will work speaker), 16/6 extra.

**A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS AND PRICES.**

**FREE CATALOGUE** of the **BRITISH HEATHKIT RANGE**

Gladly send on request . . .

To **DAYSTROM LTD. Dept. P.W.-11, GLOUCESTER, ENG.**

Please send me **FREE BRITISH CATALOGUE (Yes/No)**

Full details of model(s).....

American Catalogue, 1/- Post Paid (Yes/No)

NAME .....

ADDRESS .....

# STERN-CLYNE

## HIGH FIDELITY EQUIPMENT



**(1) Mullard "10 Plus 10" Stereo Amplifier**  
A High Fidelity design providing up to 10 watts (per channel).  
**KIT OF PARTS £20.0.0.**  
Built and tested £24.0.0 (C. & I. 7/6). We can also supply the Main Amplifier for operation with our Dual Channel Pre-amplifier.  
**KIT OF PARTS £27.0.0.**  
Built and tested £34.0.0 (C. & I. 10/6).



**(2) Mullard Dual Channel Pre-Amplifier**  
A four-valve design for both Stereophonic and Monophonic operation.  
**KIT OF PARTS £12.10.0.**  
Built and tested £15.0.0 (C. & I. 5/-).



**(3) The "Twin Three" Stereo Amplifier**  
Based on a recent design by Mullard Ltd. it is ideally suited for use in Portable Record Players.  
Built and tested £9.0.0 (C. & I. 7/6). To construct a Stereo Portable Record Player, we offer:  
Assembled Amplifier with two 8 x 5in. Loudspeakers and Portable Case for £15.10.0 (C. & I. 10/-).

Fully descriptive leaflets available on any of the above items.

Instruction Books and Detailed Price Lists are supplied Free with Kits of Parts but may be purchased separately if required.


Items 1, 2 and 14, 3/- each; 6 and 13, 3/6 each; 7, 8, 9, 10, 2/- each; 11, 2/6 each; 12, 5/-. All Post Free.



**(5) Tudor AM/FM Tuner**  
Self powered VHF/FM long and medium waves. FM 87.5-108.5 Mc/s AM MW 522-1,630 Kc/s. LW 145-270 Kc/s. Multiplex output.  
Built and tested 24 Gns. (P. & P. 7/6).



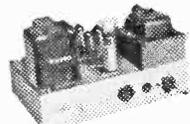**(6) Mullard 3-Valve Pre-Amplifier Tone Control**  
Designed mainly for the Stern Mullard range of Monophonic Power Amplifiers.  
**KIT OF PARTS £10.0.0**  
Built and tested £13.13.0 (C. & I. 5/-).




**(8) Mullard "5-10" Main Amplifier**  
For use with Mullard 2- or 3-valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained.  
**KIT OF PARTS £10.0.0.**  
Built and tested £13.10.0 (C. & I. 6/6). Above incorporating Partridge Output Transformer £1.8.0 extra.



**VERITONE 30 AMPLIFIER**  
A general purpose amplifier of outstanding quality ideally suitable for Dance Bands, Clubs, Hotels, Factories, Indoor and outdoor Public Address requiring a powerful robust portable Amplifier which will provide high quality reproduction, distortion free. The Amplifier has two standard Jack Socket inputs, high gain and low gain with individual volume controls and the master volume control the inputs may be mixed and balanced as required. Housed in a really robust steel case finished in smooth grey hammer finish with chrome handles and silver grey front panel with contrasting letters and knobs. Built-in Pre-amplifier and Control Unit. 30 watt Undistorted Output. Switched Output for 3 or 15 ohms Loudspeakers. Fully assembled and tested  
**Price 18 Gns.**  
Cover with chrome handles as illustrated, 35/- extra.



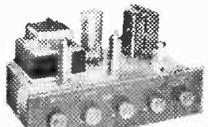
**(9) Mullard "5-10RC" Amplifier**  
The popular "5-10" complete incorporating Passive Control Unit providing up to 10 watts high quality reproduction with an input of 600mV.  
**KIT OF PARTS £12.0.0.**  
Built and tested £16.0.0 (C. & I. 7/6). With Partridge Output Transformer £1.6.0 extra.




**(10) Mullard "3-3RC" Amplifier**  
A high quality Amplifier developed from the very popular 3-watt Mullard "3-3" design.  
**KIT OF PARTS £8.8.0.**  
Built and tested £11.10.0 (C. & I. 6/6).



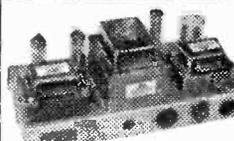**(11) The "Mono-Gram" Amplifier**  
A small Amplifier of genuine high quality performance producing up to 3 watts undistorted output.  
**KIT OF PARTS £4.10.0.**  
Built and tested £6.0.0 (C. & I. 3/6).




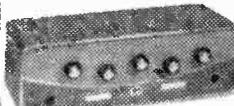**(16) JL10 Power Amplifier**  
Incorporates the latest diode/pentode ECL86 valves in push-pull. Partridge ultra linear output transformer. Partridge mains transformer and smoothing choke. 10 watts power output, surplus.  
Built and tested £12.12.0 (C. & I. 7/6).



**(17) Double Feature Pre-Amplifier**  
Inputs for microphone, crystal or magnetic pick-ups, tuner unit, and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck.  
Built and tested £18.18.0 (C. & I. 5/-). Prices if both units purchased together:  
Built and tested £30.9.0 (C. & I. 10/-)

### VERITONE 30

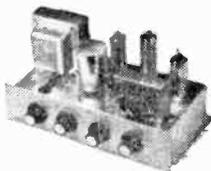

A small versatile 3-4 watts Gram Amplifier suitable for Crystal Pick-up or Radio Tuner, ideally suited for a small domestic installation. Output imp. 3 ohms, volume control, treble control, bass control and middle control. Valve line-up: EL84, EF86, E289.  
Chassis size 8½ x 4 x 1½in. Silver anodised finish. Attractive front panel silver grey finish with contrasting lettering and knobs. Size 8½ x 2½in.  
Fully assembled and tested 6 Gns. (C. & I. 5/-).



**(7) MULLARD 2-VALVE PRE-AMPLIFIER**  
Employing two EF86 valves and designed to operate with the Mullard MAIN AMPLIFIERS but also perfectly suitable for other makes. Now with new design front panel.  
**KIT OF PARTS £6.6.0.**  
Built and tested £9.10.0 (C. & I. 5/-).



**(12) Stereo Tape Pre-Amplifier Model STP-1**  
For use with current Truvox, Brenell or Collaro "Studio" 1- and 4-track Stereo Decks. Now with new design front panel.  
**KIT OF PARTS £22.0.0.**  
Built and tested £28.0.0 (C. & I. 8/6).



**(13) Mullard Type "C" Tape Pre-Amplifier**  
Suitable for most 4-track Mono Tape Decks. Now with new design front panel.  
**KIT OF PARTS £14.0.0.**  
Built and tested £19.10.0 (C. & I. 7/6).



**(14) Mullard Tape Amplifier Model HF/TR3**  
Based on Mullard's type "A" design and suitable for most 4-track Mono Tape Decks. Now with new design front panel.  
**KIT OF PARTS £13.13.0.**  
Built and tested £19.10.0 (C. & I. 7/6).

# STERN-CLYNE Appointed stockists for the New Veritone range of hi-fi equipment



## TWO ENTIRELY NEW DESIGNS FOR THE MODERN-MINDED HI-FI ENTHUSIAST

### THE VERITONE SATURN TRANSISTORISED FM TUNER

**SPECIFICATION:** Transistors: 1 x AF125, 1 x AF121, 4 x AF116. Diodes: 4 x OA79, 1 Variable Capacity Diode, 1 1B10J05 Solid State Full Wave Bridge Rectifier, 1 OAZ212 Zener Diode. 4 I.F. Stages. Switchable A.F.C. Tuning Meter. Facility for plug-in Multiplex Stereo Adaptor (available at a later date). Tuning Range: 87.5-108.5 Mc/s. Stabilized Power Supply. Din Outlet Socket. Fully Variable Audio Output Attenuator. Supplied with or without Plastic Laminated Case (Teak). High Sensitivity. Attractive Black and Silver Grey front panel with mirror strip top and bottom.

**PRICE 25 GNS. Carriage & Insurance 7/6**

Teak case optional extra.

### THE VERITONE VEGA TRANSISTORISED STEREO AMPLIFIER

**SPECIFICATION:** Power response, with channels used simultaneously, 13 watt R.M.S. per channel, at 50 c/s and 10 Kc/s the above features are reduced by approximately 2 watts. Loudspeaker impedance 15 ohm. Frequency response on unequalised input, flat  $\pm 1$ dB from 40 c/s to 20 Kc/s.—3dB at 20 c/s. Total harmonic distortion at 10 watts approximately 0.5%. Cross talk, —50dB at 1 Kc  $\pm 5$ dB. Hum and noise—50/60dBs on Radio, Aux, Tape and Magnetic P.U.—50dBs on Ceramic P.U.  $\pm 3$ dB. Controls: Bass, Treble and Balance, Inputs for Radio, Tape, Aux, Magnetic P.U. and Ceramic P.U. Tape Output and Tape Monitor. Mains input 200-220-240 volts. Transistors per channel 5 x OC45, 2 x OC35 or OC29, 2 x ACY17, 1 x 2N696, 6 x Diodes per amp. Dimensions: 11 x 4 1/2 x 6 1/2 in. Front Panel: Silver Grey with contrasting Black markings and knobs. Operation: 200/250 v. A.C. 50 c/s.

**PRICE 39 GNS. Carriage & Insurance 10/-**

Teak case optional extra.

**NOW ON DEMONSTRATION AT ALL BRANCHES**

# STERN-CLYNE

SEE FOLLOWING PAGE FOR ADDRESSES

# STERN-CLYNE

ELECTRONIC CENTRES THROUGHOUT GREAT BRITAIN

### RECORD PLAYER BARGAINS



**B.S.R. UA.25** 4-speed Autochanger with mono cartridge .. £5.19.6  
**B.S.R. UA.15** "Super Slim" 318 4-speed Autochanger with mono cartridge. . . . . £9.19.6

### SPECIAL GARRARD OFFERS!

3000 4-speed Autochanger with Sonotone PFA Stereo Cartridge **£9.19.6**. LAB "A" GC8 Mono **£15.15.0**. LAB "A" on plinth **£17.17.0**.

### OTHER GARRARD MODELS

BRP.10 Single Player .. £5.9.11  
 A.1090 with cartridge .. £8.10.0  
 SP.25 Single Player .. £13.10.8  
 AT.60 with cartridge .. £14.1.1  
 4HF with GC8 cartridge .. £16.17.6  
 A70 less cartridge .. £27.11.1  
 LAB 80 less cartridge .. £27.10.0  
 201 Transcription Unit .. £25.5.4  
 401 Transcription Unit .. £32.10.0  
 (C. & I. 5/- extra all models)

### HIGHWAYMAN DE LUXE CAR RADIO KIT



Look at these features:—  
 ● Push-pull output. ● Three latest Mullard transistors plus valve types 6BF63 and ECH83.  
 ● No buzz, high output and sensitivity. ● Prated circuit (latest type). ● 7 x 4in. high flux p.m. speaker and baffle.  
 ● Medium and Long Waves. ● Extremely low battery consumption (less than 3 amp.). ● Easy to fit any make car (positive earth only). ● 12-volt operation. ● Compact size, measures only 7 x 7 x 2in. deep. ● Easy assembly, supplied with dial and drive already mounted. ● Push button for finger-tip control includes wavechange, pre-set tone control and provision for switching in an Extension Speaker. ● Attractive new style tuning scale and chrome switchgear. Price **£7.19.6**. 5/- carriage and insurance.

### AMERICAN RECORDING TAPE

5in.	600ft. Std. Acetate	.. 8/6
5in.	1000ft. LP Acetate	.. 10/-
5 1/2in.	1200ft. LP Acetate	.. 12/6
5 1/2in.	600ft. LP Polyester	.. 11/6
7in.	1200ft. Std. Polyester	.. 12/6
5in.	1200ft. DP Polyester	.. 15/-
7in.	1800ft. LP Polyester	.. 20/-
5 1/2in.	1800ft. DP Polyester	.. 22/6
7in.	2400ft. DP Polyester	.. 25/-

P. and P. 1/- per reel. 4 or more Reels **POST FREE.**

### FULLY AUTOMATIC TAPE SPLICER

34/6. P. & P. 1/6.  
**PLASTIC TAPE SPOOLS**  
 5in.. 1/8; 4in.. 2/-; 5in.. 2/-; 5 1/2in.. 2/3; 7in.. 2/6.


**PLASTIC SPOOL CONTAINERS.** For spool sizes 5in.. 1/6; 5 1/2in.. 2/-; 7in.. 2/3; Any single item plus 6d. P. & P. Orders over £1 post free.

We carry fully comprehensive stocks of Tape Recorders, Decks and Accessories at all Branches or order with confidence by mail.

## TWO SPECIAL TAPE RECORDER BARGAINS



FAMOUS MANUFACTURER

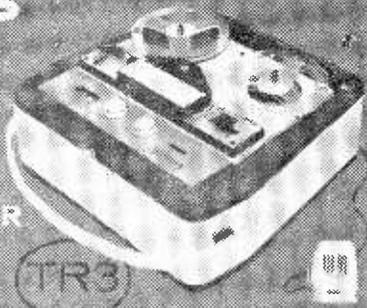

**TR2 PORTABLE TAPE RECORDER.** A truly first-class portable machine by famous manufacturer incorporating the renowned BSR single speed 2-track Tape Deck.

**SPECIFICATIONS:** Single speed 3 1/2 i.p.s. Tape Counter. Record Level Indicator. Volume and On/Off Tone Control. 3 watts output. Inputs for recording from Microphone and Radio. Tape Monitor Socket. Extension Loudspeaker Socket. Attractive two-tone greycream resin covered Portable Cabinet. Supplied complete with Microphone. Reel of Tape and Spare Spool. Carriage and insurance 15/- extra. Credit Terms: £2.18.0 deposit and 12 monthly payments of £1.8.4. Total credit price **£20.10.0.**

**Price 18 Gns.**

**TR3 PORTABLE TAPE RECORDER.** A high quality Portable Tape Recorder to the discerning enthusiast incorporating the latest BSR TD10 3-speed Tape Deck.

**SPECIFICATIONS:** 3-speed, 1 1/2, 3 1/2 and 7 1/2 i.p.s. 2-Track. Record interlock to prevent accidental erasure. Tape Counter. Record Level Indicator. 3-4 watts output. Volume and On/Off Tone Control. Inputs for recording from Microphone and Radio. Tape Monitor Socket. Extension Loudspeaker Socket. Attractive two-tone blue resin covered Portable Cabinet with silver trimmings. Supplied complete with Microphone. Reel of recording from Radio or Record Player. Full Reel of Tape and spare stool. Carriage and insurance 15/- extra. Credit Terms: **£3.3.0** deposit and 12 monthly payments of **£1.12.3.** Total credit price **£22.10.0.**

**Price 20 Gns.**

### LONDON

18 Tottenham Court Road, W.1. MUSEUM 5929/0095. Half Day Saturday  
 23 Tottenham Court Road, W.1. MUSEUM 3451/2. Half Day Thursday.  
 309 Edgware Road, W.2. PADDINGTON 6983. Half Day Thursday.  
 109 Fleet Street, E.C.4. FLEET Street 5812/3. Half Day Saturday.  
 162 Holloway Road, N.7. NORTH 7941. Half Day Thursday.  
 9 Camberwell Church Street, S.E.5. RODNEY 2875. Half Day Thursday.

### CROYDON

12 Suffolk House, George Street, MUNICIPAL 3250. Half Day Wednesday.

### BRISTOL

26 Merchant Street, Bristol 1. BRISTOL 20261. Open 6 days a week.

### LIVERPOOL

5 Lord Street, ROYAL 7450. Open 6 days a week.

### MANCHESTER

20/22 Withy Grove, Manchester 4. BLACKFRIARS 5370/3246. Open 6 days a week.

### SHEFFIELD


125 The Moor, Sheffield. SHEFFIELD 98983. Half Day Thursday.

### MAIL ORDERS AND ENQUIRIES TO:

Dept. P.W., 20, Eden Grove, HOLLOWAY, LONDON, N.7. NORTH 8161/5.

**Vacancies for Expt. & Trainee Sales Staff in all Branches**

Apply **Head Office NORTH 8161**

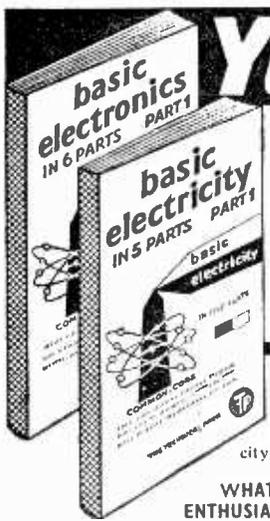

# YOURS FREE FOR 7 DAYS

## The New 'Picture-Book' way of learning BASIC ELECTRICITY (5 vols.) ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

### WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTAGE.  
 "I am delighted with the way in which they lay down the straightforward uncomplicated facts." A. P. Weston.  
 "I must agree with the previous testimonials, the subject is admirably presented; by far the best I have ever seen."  
 J. A. Plymouth: "These books are everything you claim for them, it took me only five minutes to make up my mind to purchase them." R. D., Welling.

**POST NOW FOR THIS OFFER!!**

To Selray Book Co.  
 60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/- (Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/- (Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only. Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY  BASIC ELECTRONICS

Signature .....  
 (If under 21, signature of parent or guardian)

NAME .....  
 BLOCK LETTERS BELOW  
 FULL POSTAL ADDRESS .....

## VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R3, 1R5, 1T4 3R4, 3V4, DA F91 DF91, DK91, DL92, DL94.  
 Set of 4 for 15/-; DA F96, DF96, DL96, DL98, 4 for 24/6.

1A7GT	7/6-7B7	7/8-CL38	9/6-ECF92	6/-	ME140015/-	7Y86F	10/6	
1H3GT	7/3-7C3	7/8-CY1	12/6-ECF98	10/6	MT44	4/-	U95	8/6
1N6GT	7/8-7C6	5/8-DAC32	7/8-ECR85	6/-	N18	5/6	U98	8/6
1R5	4/9-7B9	4/8-DA F91	3/9-ECH42	8/3	PC85	6/3	U47	8/6
1R4	4/9-7Y4	5/-DA F96	6/-ECH81	6/-	PE97	7/-	U52	4/6
1R6	3/9-9B W6	6/8-DCC90	6/9-ECL80	6/3	PC94	5/6	U54	8/6
1T4	1/9-10P1	9/8-DF33	7/8-ECL82	6/9	PC99	9/6	U74	3/6
2P	1/9-10L D12	7/8-DP91	1/9-ECL86	8/6	PCF80	8/6	U191	9/6
2A5	8/9-12A17	3/9-DP98	6/-EP99	3/9	PF82	6/9	U281	8/6
3Q4	5/6-12A U7	4/9-DU75	3/6-EP91	6/3	PP84	7/9	U301	10/9
3R4	4/9-12A X7	4/9-DH77	4/-EP90	4/9	PP88	8/3	U801	15/-
3V4	5/9-12K7GT	4/8-DH81	12/6-EP93	5/-	PP802	9/8	UAB30	5/9
3U4G	4/8-12K8GT	8/8-DK32	7/9-EP86	6/9	PP802	9/8	UAF42	7/9
4Y3GT	4/11-12Q7GT	4/8-DK91	4/9-EP89	4/3	PCF805	8/-	UBC41	6/6
5Z4G/GT/8/9	1/9BGG6	6/9-DK92	8/-EP92	2/6	PCL82	6/3	UBC91	7/3
6/30L2	8/8-26L1	12/3-DK96	6/6-EP91	1/9	PCL83	9/-	URF80	6/6
6AL5	3/-30P3	10/8-DL33	6/9-EP97	7/6	PCL84	8/6	URF90	5/9
6AM6	2/8-30P4	13/8-DL35	5/-EP183	6/9	PL25	5/6	UC684	8/-
6AQ5	5/6-20P5	11/8-DL92	4/9-EL34	6/6	PEN44	6/6	UC685	6/6
6AT5	4/-25L8GT	4/8-DL94	5/6-EL38	11/9	PEN883	9/8	UC850	8/3
6BA6	4/8-30C18	8/-DL96	6/-EL41	6/9	PEK36C15/-	UCH42	7/6	
6BB6	4/8-30F5	8/6-DY86	6/9-EL84	4/8	PL20017/6	UCH81	6/6	
6BH6	5/-30P14	9/6-DY87	8/-EL86	6/6	PL86	8/9	UCL82	7/3
6BJ6	5/6-30L15	10/8-PAB C80	6/-EM34	8/6	PL81	6/9	UC83	8/9
6RW6	7/8-30L17	12/-EAF42	7/6-EM50	6/3	PL82	5/6	UF41	6/6
6F13	3/8-30P4	13/8-EB41	4/-EM81	7/3	PL83	8/-	UF42	4/6
6F14	3/8-30P12	7/8-EB91	2/-EM84	6/9	PL84	6/3	UR85	6/9
6K7G	4/8-30P19	13/8-EB C33	6/-EM87	6/6	PL500	14/-	UP89	5/9
6RS0	4/3-30P11	9/6-EB C41	6/6-EV31	6/3	PL901	7/6	UL41	7/3
6K8C F	7/8-30PL13	10/8-EB F90	6/-EV86	6/-	PN25	7/9	UL44	15/-
6P28	9/8-30PL14	11/8-EB F83	7/6-EZ40	6/9	PV32	8/9	UL46	8/6
6K7G	5/8-35L5GT	6/3-EB F89	5/8-EZ41	6/6	PV33	8/9	UL84	5/-
6K7G	7/8-35W4	4/6-EB C40	6/9-EZ80	4/-	PY80	5/3	UV41	4/9
6SL7GT	4/9-35Z4GT	4/6-ECC51	3/9-EZ81	4/8	PY81	5/3	UY85	4/9
6V6G	3/8-35K U	8/6-ECC82	4/9-FV4/5006/3	PY82	5/-	VP4B	11/-	
6V6GT	6/8-80	4/8-ECR83	7/8-GZ33	14/6	PY83	5/9	W76	3/6
6X4	3/8-9063	1/6-ECR84	6/8-GZ37	3/9	PY809	6/6	W77	2/-
6X3GT	6/3-AZ31	9/6-ECR85	5/6-KT61	6/6	TH-10	9/6	Y19	26/-
7B8	10/6-836	4/6-ECF80	7/8-KT76	7/3	TH238	8/6	Z77	2/6


## READERS RADIO

24 COLBERG PLACE, and at 85 TORQUAY GARDENS STAMFORD HILL REDBRIDGE, ILFORD LONDON N.16. STA 4587 ESSEX. CRÉ 7441

Postage on 1 valve 9d. extra. On 2 valves or more postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

## GUITAR AMPLIFIERS with TREMOLO

12 months' guarantee (valves 3 months)

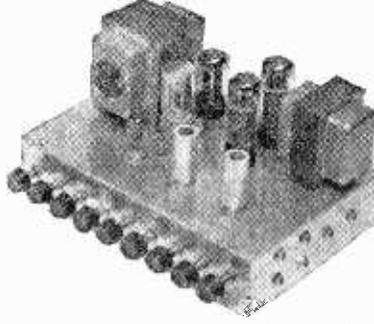

Five jack socket inputs, with four separate mixing volume controls. High gain of 10 millivolts makes it suitable for all types of guitars and microphones. Separate Bass and Treble controls. Master gain control. Tremolo speed and depth controls. Remote tremolo switch socket. 7.5 and 15 ohms outputs. 30 and 50 watt valves.

EC683, EC683, EL34, EL34, GZ34. 15 watt valves EC683, EC683, EL84, EL84, EZ81. Two extra valves EC683 used in the tremolo circuit. Tremolo operates on one input only. Black and gold trim panel (fitted tremolo type only at present) chassis finished silver grey hammer. Cover with chrome handles 35/- extra.

50 watt with tremolo	.....	£21.76
50 watt less tremolo	.....	£19.10
30 watt with tremolo	.....	£16.76
30 watt less tremolo	.....	£14.10
15 watt with tremolo	.....	£13.78
15 watt less tremolo	.....	£11.10

All carriage 10 - any amplifier. No Trade or Export. Descriptive leaflet free, stamp appreciated. Suitable speakers, Bakers 12" Guitar L.B. 5 zns. Bakers 12" Comby 50 L.S. 18 zns. Carriage Inc.

## STROUD AUDIO

CASHES GREEN ROAD, STROUD, GLOS. STROUD 783.

THE WORD **MAXI-Q** IS THE REGISTERED  
 TRADE MARK  
 OF DENCO (CLACTON) LIMITED  
 IT IS ALSO A GUARANTEE OF  
 WORKMANSHIP AND  
 TECHNICAL PERFORMANCE

OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 2s. 0d. FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 2s. 0d. IN STAMPS.

IN RESPONSE TO CONTINUOUS DEMAND WE HAVE COMMENCED PRODUCTION of self Contained Multiplex Decoder Unit, aligned ready for immediate use, that will convert your two receivers—tuner and two amplifiers—tuner and stereo amplifier or stereo receiver without Multiplex provision to a complete B.B.C. Stereo Broadcast Reception Unit. Price £8.0.0. post paid. Technical Publication MD.1. 4s. 0d. post paid.

**IFT.11/465** kc/s centre tapped transformer for use in crystal filter circuits, 1-7/8" x 13/16" square. 10s. 6d. plus 8d. post.

**IFT.18/465** kc/s and 1.6 Mc/s Double Tuned transistor IF transformer, 1 1/2" x 1 1/2" square. 10s. 6d. plus 8d. post.


General Catalogue 2s. 0d. post paid. S.A.E. all enquiries please.

## DENCO (CLACTON) LTD.

(DEPT. P.W.)

357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX

# BUY AND BUILD STAGE BY STAGE

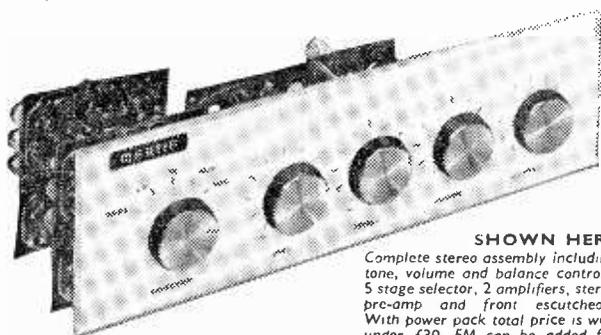

### SHOWN HERE

Complete stereo assembly including tone, volume and balance controls, 5 stage selector, 2 amplifiers, stereo pre-amp and front escutcheon. With power pack total price is well under £30. FM can be added for another £12.17.6.

### LOOK HOW YOU SAVE

- 5 stage Input Selector £2.7.6
- Pre-amp. and vol. control £1.17.6
- Pre-amp. with tone controls £3.2.6

- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0

WITH THE MOST SUCCESSFUL  
 CONCEPT OF HI-FI EVER OFFERED  
 TO CONSTRUCTORS

MARTIN AUDIOKITS comprise a range of well made prefabricated units designed to be assembled and used in the way best suited to your personal requirements. They enable you to start with a modest installation and to enlarge it stage by stage till it becomes a high fidelity stereo assembly complete with F.M. tuner, suitable for use with 3 ohm or 15 ohm loudspeakers. Power packs are available, and new units introduced will be standardised to enable you, where appropriate, to add them to existing Audiokit systems. No previous knowledge is needed to build with complete success.

## HI-FI • F.M. RADIO



Martin Audiokits and Recordakits are obtainable from good stockists everywhere. In cases of difficulty please write direct.

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD M'SEX

Phone: ISLeworth 1161/2

MARTIN ELECTRONIC LTD. 154-155 High Street  
 Brentford Middlesex

Full details of Martin Audiokits please

NAME .....

ADDRESS .....

(Block letters) PW11



**LAFAYETTE HA 63 COMMUNICATION RECEIVER**

7 valves + Rectifier. 4 Bands 550 Kc/s-31 Mc/s. 'S' Meter-BFO-ANL-Bandspread Tuning. 200/250v. A.C. Brand New. 24 Gns. carr. paid.



**STAR SR 40 COMMUNICATION RECEIVER**


4 Bands 550 Kc/s-30 Mc/s. 'S' Meter-BFO - ANL - Bandsread Tuning-Built in speaker, 200/250v. A.C. Brand New. 18! Gns. Carriage 10/-.



**NEW MODEL! LAFAYETTE HA-230 AMATEUR COMMUNICATIONS RECEIVER**

Supersedes model HE-30. 8 valves + rectifier. Continuous coverage on 4 bands. 550 Kc/s-30 Mc/s. Incorporates 1 RF and 2 IF stages. Q Multiplier, BFO, ANL, 'S' meter, electrical bandsread, Aerial trimmer, etc. Supplied brand new and guaranteed. 33 Gns. SAE for full details.

Also available in Semi Kit form 25 Gns.

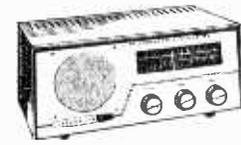

**NEW MODEL! LAFAYETTE HA-55 Aircraft Receiver**

108-138 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 6CW4 Nuvistor. 8 tubes for 11 tube performance. Solid state power supply, adjustable squelch control, slide rule dial, built in 4in. speaker and front panel phone jack. 220/240v. A.C. Supplied brand new and guaranteed. 19 Gns. Carr. 10/-.

**OS/8B/U OSCILLOSCOPES**

High quality Portable American Oscilloscope. 3in. c.r.t. T/B 3c/s-50 kc/s X Amp; 0-500 kc/s Y Amp; 0-2 Mc/s. Power requirements 105-125v. A.C. Supplied in "as new" condition, fully tested. £25. Carr. 10/-, Suitable 230/115v. Transformer. 15/8.



**TE-21 SINE SQUARE WAVE AUDIO GENERATORS**

Sine: 20 c.p.s. to 200 Kc/s on 4 bands. Square: 20 c.p.s. to 25 Kc/s. Output imp. 500 ohms. 200/240 v. A.C. Brand new Guaranteed. £15. Carr. 7/6.



**LEADER LSG-10 R.F. SIGNAL GENERATOR**

120 Kc/s-280 Mc/s on 6 ranges. Variable R.F. and A.F. outputs. Large clear scale. Size 7 1/2 x 10 1/2 x 4 1/2. 200/250v. A.C. operation. Brand New. £12. Carr. 7/6.

**CLEAR PLASTIC PANEL METERS**

First grade quality. Moving coil panel meters, available ex-stock. M.A.E. for illustrated leaflet. Discounts for quantity. Available as follows. Type MR 3SP. 1 1/2" square fronts.

2mA .. .. .	22/6	3V. DC .. .. .	22/6
3mA .. .. .	22/6	10V. DC .. .. .	22/6
10mA .. .. .	22/6	20V. DC .. .. .	22/6
20mA .. .. .	22/6	50V. DC .. .. .	22/6
30mA .. .. .	22/6	100V. DC .. .. .	22/6
100mA .. .. .	22/6	150V. DC .. .. .	22/6
150mA .. .. .	22/6	300V. DC .. .. .	22/6
200mA .. .. .	22/6	500V. DC .. .. .	22/6
300mA .. .. .	22/6	750V. DC .. .. .	22/6
500mA .. .. .	22/6	15V. AC .. .. .	22/6
1000mA .. .. .	22/6	50V. AC .. .. .	22/6
50/2 A .. .. .	32/6	750V. AC .. .. .	22/6
100/2A .. .. .	28/6	300V. AC .. .. .	22/6
200/2A .. .. .	27/6	500V. AC .. .. .	22/6
500/2A .. .. .	25/6	750V. AC .. .. .	22/6
30-0-300/2A .. .. .	29/6	1000V. AC .. .. .	22/6
100-0-100/2A .. .. .	27/6	1A. DC .. .. .	22/6
500-0-500/2A .. .. .	22/6	2A. DC .. .. .	22/6
1mA .. .. .	22/6	5A. DC .. .. .	22/6

ILLUMINATED "S" METER 1 1/2" square front. Cal. in S units. 6v. lamp. 28/8. P.P. 1/-. Ditto 2 1/2" square 39/8. P.P. 1/-.

**AVOMETERS**



Supplied reconditioned, guaranteed perfect. Model D. £5.18.6. Post & Ins 5/-.

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**

Operative over amazingly long distances. Separate call and press to talk buttons, 2-way connection. 1000' of application. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. 7 gns. pair. P. & P 5/-.

**SILICON RECTIFIER**

200 P.I.V. .. .. .	200mA	2/6
1,000 P.I.V. .. .. .	650mA	7/6
600 P.I.V. .. .. .	500mA	5/6
400 P.I.V. .. .. .	3 amp	7/6
400 P.I.V. .. .. .	500mA	3/6
150 P.I.V. .. .. .	165mA	1/-
70 P.I.V. .. .. .	1 amp	3/6
95 P.I.V. .. .. .	3 amp	5/6

Post extra.

**AMERICAN TAPE**

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.

3in. 225ft. L.P.	4/-
3 1/2in. 600ft. T.P. mylar	8/6
3 1/2in. 600ft. std. plastic	10/6
5in. 300ft. L.P. acetate	10/6
5in. 1200ft. T.P. mylar	15/-
5in. 1800ft. D.P. mylar	15/-
5 1/2in. 1200ft. L.P. acetate	12/6
5 1/2in. 1800ft. D.P. mylar	22/6
7 1/2in. 2400ft. T.P. mylar	45/-
7in. 1200ft. std. mylar	12/6
7in. 1800ft. L.P. acetate	15/-
7in. 1800ft. L.P. mylar	20/-
7in. 2400ft. D.P. mylar	25/-
7in. 3600ft. T.P. mylar	55/6

Postage 2/- Over £3 post paid.

**ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPES**



Timebase 2 c/s-750 kc/s. Separate Y1 and Y2 amplifiers. Up to 5.5 Mc/s. calib. at 100 kc/s. and 1 Mc/s. 100/230 v. A.C. Guaranteed perfect. £27.10.0. Carr. 20/-.

**MINE DETECTOR No. 4A**

Will detect all types of metals. Fully portable. Complete with instructions. 39/8 each. Carr. 10/- Battery 8/6 extra.

**BEST BUY!**

Send 1/- P.O. for full catalogue and lists. Trade supplied. Open 9 a.m. to 8 p.m. Every day, Monday to Saturday.

**TWO-WAY RADIOS**

Superb quality. Complete with all accessories and fully g'v'd. 3 Transistor

4 Transistor £9.17.8 pr.

9 Transistor £25 pr.

10 Transistor 28 gns pr.

Post extra. (S.A.E. for full details).

**VOLTAGE STABILIZER TRANSFORMERS**

Will stabilize your mains voltage. Ideal for TV Receivers and Industrial equipment. Input 80-120 v. and 160-240 v. Constant output 110 v. or 240 v. 250 watts. Brand new guaranteed. £10.10.0 Carr. 7/6.

**VARIABLE VOLTAGE TRANSFORMERS**


Brand New Guaranteed. Fully Shrouded. Input 230v. 50/60 c/s. Output 0-23v.

0 Amp	£4.10.0.
2.5 Amp	£5.17.6.
5 Amp	£9.0.0.
8 Amp	£13.10.0.
10 Amp	£17.10.0.
12 Amp	£19.15.0.
20 Amp	£29.10.0.

2.5 Amp Portable Metal Case with Meter Fuses etc. £9.17.6.

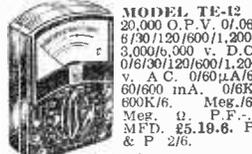**LAFAYETTE NUVIATOR GRID DIP METER**

Compact true one hand operation. Frequency range 1.7-180Mc/s. 230v. A.C. operation. Supplied complete with all coils and instructions. £12.10.0. carr. 6/-.



**MODEL TE-12**

20,000 G.P.V. 0/0.05/0.1/0.2/0.5/1/2/5/10/25/50/100/200/3,000/6,000 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/60/1A/6/60/600 mA. 0/6K/600K/6. Meg. 160 Meg. 0 P.F. -2 MFD. £5.19.6. P. & P 2/6.



Stockists of Nombrex, Codar, Sinclair, and all Electronic Equipment and Components.

**C.W. SMITH & CO (RADIO) LIMITED**

Phone: GERRARD 8204/9155  
Cables: SMITHEX LESQUARE  
3-34 LISLE STREET, LONDON, W.C.2

# looking to the future in electronics?

**YOUR CAREER · YOUR HOBBY · YOUR OWN BUSINESS**

We can train you, in the comfort of your own home, for any subject in ELECTRONICS—including tuition for any of the principal professional examinations such as: Institution of Electronic and Radio Engineers; the City and Guilds Telecommunications Certificates; the R.T.E.B. Radio & T/V Servicing Certificate; the RADIO AMATEURS' LICENCE Examination; the P.M.G. Certificate; etc. We also conduct general training courses in radio and television; radar; transistors; computers; etc.

For those who require a practical type course, we provide a complete 'build as you learn' servicing course based on a full set of practical equipment covering transistorised radio apparatus; test meter; signal generator and oscilloscope.

No previous experience or knowledge is necessary in order to take any of the above courses nor do you take on any obligation when starting any course of study. **POST COUPON BELOW TO-DAY for FREE BROCHURE**

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.**

*Please send details of your courses, without any obligation, to:*

NAME .....

**BLOCK  
CAPS  
PLEASE**

ADDRESS .....

I am interested in .....

exam or course.

(We do not employ representatives)

P.W.11 65

## British National Radio School



# PRACTICAL WIRELESS

NOVEMBER 1965

VOL 41 NO 705

## RESOURCEFULNESS

"I wonder if the average radio enthusiast is so resourceful and ingenious as he used to be?" This chance remark, thrown up after a reference to the "hints and tips" columns without which no self-respecting radio magazine would once have been complete, sparked off a lively discussion. It proved inconclusive.

One line was that the *apparent* ingenuity increases as one rolls back the years, for the earlier you made a start the more resourceful you *had* to be. Right back in the early 1920's, the average enthusiast even had to make many of his own components before thinking of wiring them up. Would he have gone to all this trouble if commercial products had been readily and inexpensively available? Is it a case of necessity being the mother of invention?

And what of that fine field of gimmicks? The little self-designed gadgets, the odd uses for conventional bits and pieces, the salvaging of otherwise discarded items for further use, the novel ways to overcome constructional snags—all these used to flourish in an unending stream.

Are constructors no longer interested in such gadgetry or in this affluent society is the saving of the odd pence no longer a driving force? Perhaps the seeming absence of those Hints and Tips is due to the fact that most of them are now common currency and that people *are* still using them, like family heirlooms passed on from previous generations.

On the other hand, it could be that the average constructor is no longer so resourceful since everything is made so very easy for him and he has no need to puzzle over such things. In order to attempt some sort of assessment on this problem we are inviting readers to send along any original ideas they may have. The best of those received will be published.

## CONTENTS

	<i>page</i>
News and Comment	566, 596
Miniature Oscilloscope	568
Reducing Transmitter BCI/TVI	572
Self-Regulating Transistor Circuits	574
The Morse Bogey	579
Showtime—a look at the new models	580
Practical Substitutes—Part 4	583
Tape Terminology—Part 4	589
Bandswitching the "Ten-Five"	592
MW DX	598
Practically Wireless	606
On the Short Waves	610
Thumbnail History of Radio	614
Club Spot—Derby and District	621

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 29s. per year to any part of the world. © George Newnes Ltd., 1965. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproduction or imitations of any of these are therefore expressly forbidden. **The DECEMBER ISSUE WILL BE PUBLISHED ON NOVEMBER 4th**

## PCR Mods

AFTER having read W. V. Wood's article "PCR Mods" in the June issue of PRACTICAL WIRELESS, I have added a noise limiter, a.v.c. switch to my PCR and I am now working on the b.f.o. unit. I have also added another audio stage which was not described in the article.

I do not intend replacing the r.f. or frequency changer valves, but I would like to modify the set to cover the 80 and 160 metre bands so that my receiver will tune 18m to 2,000m.

If possible, I would like to have these extra coils inside the set rather than an external converter. Can anyone help please? I am aged 15.

Terence Wright,

The Bungalow,  
Glenbana, Ballyaughlis,  
Lisburn, Co. Down,  
N. Ireland.

## Tagboard Warning

IN the article for beginners in the July issue of PRACTICAL WIRELESS, the use of either paxolin or Formica for a tagboard is specified. May I give a word of warning about Formica being used for this purpose? As it is heat-resistant it has a thin metal foil sandwiched in it, and this foil can cause short-circuits. To be safe, use paxolin and ignore any form of decorative plastic sheet.

Some years ago I hit on what I thought was a bright idea to use Formica for tagboards, but soon found to my cost the damage that the metal foil could do when the power supplies were switched on!

W. E. Thompson, G3MQT,  
St. Leonards-on-Sea,  
Sussex.

## Correspondent


I WOULD like to correspond with someone of my own age (14).

G. Jackson.

50 Bury Street,  
Coff Sandy Lane,  
Stockport, Cheshire.

# NEWS AND..

## MINIATURE JACK SOCKETS

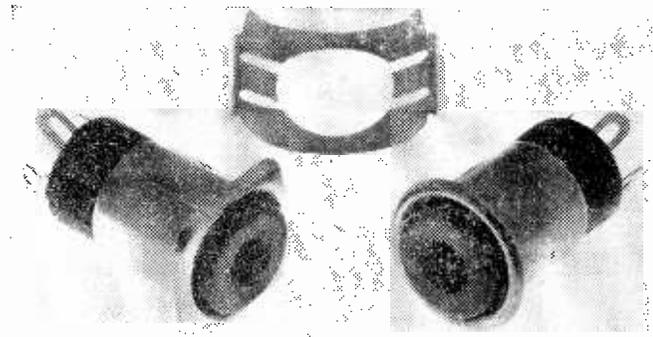

A new moulded miniature jack socket from Carr Fastener Co. Ltd., is designed to accept all miniature jack plugs including Carr's jack plug type 83/263. The contacts have a tinned finish for ease of soldering and are fully enclosed within the moulding thus protecting them from damage in handling or transit.

## THE HAMS OF EUROPE

According to the IARU (International Amateur Radio Union), the number of licensed radio amateurs in Europe has now risen to over 54,000 including over 11,000 in the UK. The country which boasts the most amateur radio stations is Germany, with 11,465.

## FIVE MEN PROBE SPACE SIGNALS

Five experts—two from the Soviet Union, two from the United States and one from Czechoslovakia, have been assigned to the job of making a thorough probe into radio signals received on earth from all over the universe. They will study the signals for six months then report their findings back to the International Astronautical Academy.

Scientists in many countries have received extremely powerful radio signals from outer space, and the signals from one source, called CTA-102 appear to follow a definite pattern which changes every fortnight. One of the Russian scientists in the team says that he cannot rule out the possibility that these signals may emanate from intelligent beings.

## BALL BEARINGS IN SPACE

Four foot diameter aluminium "ball bearings" are being placed in orbit round the earth for radar calibrations and signal strength tests and also for experiments to measure the influence of atmospheric conditions on satellite relay communications.

The first "ball bearing", made by the Rohr Corporation of USA was launched last May. A second in the series of five was launched with the experimental communications satellite LES-2.

A useful life of about five years is expected before surface deterioration through micrometeorite bombardment renders the spheres useless.

# .. COMMENT

## TEN THOUSAND USERS OF RADIO CONTROLLED MODELS

The ten thousandth licence for radio controlled model vehicles, ships and aircraft has recently been issued by the Post Office.

Costing £1 these licences remain in force for five years and were first introduced in 1954, under the Wireless Telegraphy Act of 1949.

## WIN A RECEIVER AT THE R.S.G.B. EXHIBITION


At the Radio Communications Exhibition (see News and Comment, P.W., October issue) every visitor has an opportunity to win an Eddy-stone communication receiver worth £182 if he obtains a free ballot card at the door.

The Exhibition opens daily from 10 a.m. to 9 p.m. and admission is 3s.
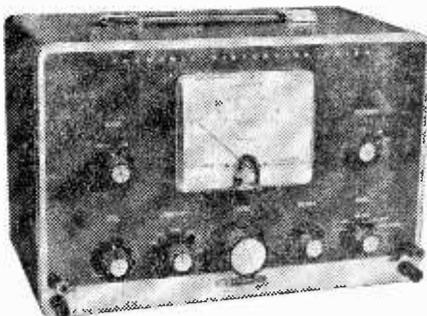
## HEATHKIT HARMONIC DISTORTION METER

From Daystrom Ltd., of Gloucester, comes model 1M-12U Harmonic Distortion Meter. The instrument measures total harmonic distortion, volts, and dBm., has five distortion ranges covering 1% to 100% full scale and covers the complete audio frequency spectrum.

There are four volt-meter ranges covering 1V to 30V full scale and oscilloscope monitoring facilities. The unit, assembled, costs £34 and in kit form £24 15s.



## RADIO GOES TO YOUR HEAD

Hats with a pocket for a transistor radio so that the wearer can listen-in while walking down the street or hear a boxing commentary while watching a football match, are being marketed by the Hat Corporation of America. The hat is made of imitation black Persian lamb in "Cossack" style. A pocket in the side carries the small radio and a thin wire leads to a miniature earpiece.

## MERCURY SPACE CAPSULE AT SCIENCE MUSEUM

The Science Museum, South Kensington, is exhibiting for several months the Mercury Space Capsule, Freedom 7, in which Commander Alan B. Shepard made the first manned Mercury flight on 5th May, 1961.

The capsule incorporates many features which have been found essential for manned space flight, such as capsule altitude controls, environment requirements for the astronaut and communication between capsule and ground.

A set of panels giving details of the United States lunar and manned space flight programmes with emphasis on the Mercury programme is also exhibited.

The exhibition has been made possible by the courtesy of the Smithsonian Institution in Washington, who have kindly lent the capsule.

more News and Comment

## Hawaiian Guitar

I HAVE successfully built the Hawaiian Guitar from your June issue. However, instead of just making the frets on the guitar body, I have constructed a fret-board which I have stuck on to the guitar. The board was made from a piece of black formica 2in. wide. The frets were cut with a saw and gold paint was rubbed into the cuts to make a really professional finish.

M. Edwards.

Herne Bay,  
Kent.

## Correspondent

I AM interested in transistor circuitry and in radio in general. I would like to correspond with anyone who shares my interests and who is about my own age (16).

Donal Gabriel.

43 Oliver Plunkett St.,  
Bandon,  
Co. Cork, Ireland.

## Offer of Components

I HAVE in my possession certain components that I would like to offer to *Practical Wireless* readers. They are valves: EF80, 6Q7G, HL133/DD, 6A8G, DAF96, EF39, ECL80, MHD4, 6F6G, DH63, DL96, D77, PY81, W42, ECH35, 25A6G, DF96, PCC84, 20F2, 10F1.

Also I have most values of resistors, all 20%, and electrolytic capacitors: 8 $\mu$ F 500V, 12/4 $\mu$ F 450V, 100 $\mu$ F 6V, 32/32 $\mu$ F, 8 $\mu$ F 350V, 100/200 $\mu$ F 275V, 16/32 $\mu$ F 350V, 16 $\mu$ F 350V, 200 $\mu$ F 12V, 40/30/20 $\mu$ F 275V.

In addition I also have a selection of pre-cut chassis.

D. J. Geer.

The Caldecott Community,  
Mersham-le-Hatch,  
Ashford,  
Kent.

We must stress that ample postage and a stamped addressed envelope must accompany all requests for components sent to Mr. Geer. First come will be first served.—Editor.

on page 596



oscilloscope proper, occupies a bench space of 9 x 4 x 5 in. (high) and contains the c.r.t., Y-amp and timebase. The power supply was built on a chassis 8 x 4 x 2 in.

### COMPONENTS LIST

#### Resistors:

R1 10M $\Omega$	R21 47k $\Omega$
R2 1M $\Omega$	R22 47k $\Omega$
R3 1M $\Omega$	R23 1k $\Omega$
R4 1k $\Omega$	R24 68k $\Omega$
R5 2.2M $\Omega$	R25 1M $\Omega$
R6 10k $\Omega$	R26 2.2k $\Omega$
R7 39k $\Omega$	R27 3.3k $\Omega$
R8 1k $\Omega$	R28 47k $\Omega$ Hi Stab. 5%
R9 33k $\Omega$	R29 47k $\Omega$ Hi Stab. 5%
R10 1M $\Omega$	R30 22k $\Omega$
R11 22k $\Omega$ 5% Hi Stab.	R31 10k $\Omega$
R12 22k $\Omega$ 5% Hi Stab.	R32 330k $\Omega$ 5% Hi Stab.
R13 2.2k $\Omega$	R33 27k $\Omega$ 5% Hi Stab.
R14 3.3k $\Omega$	R34 470k $\Omega$
R15 10k $\Omega$	R35 1M $\Omega$
R16 470k $\Omega$	R36 1M $\Omega$
R17 10k $\Omega$	R37 1 $\Omega$ 1W (See text)
R18 1M $\Omega$	R38 1.5k $\Omega$ 3W
R19 100k $\Omega$	R39 1.5k $\Omega$ 3W
R20 68k $\Omega$	R40 100k $\Omega$

All 20%  $\frac{1}{2}$ W except where stated

#### Potentiometers:

VR1 25k $\Omega$	VR5 2M $\Omega$
VR2 25k $\Omega$	VR6 1M $\Omega$
VR3 100k $\Omega$	VR7 100k $\Omega$
VR4 100k $\Omega$	

All linear

#### Capacitors:

TC1 3-30pF trimmer
C1 0.1 $\mu$ F 350V paper
C2 25 $\mu$ F 25V electrolytic
C3 1000pF silver mica
C4 0.25 $\mu$ F 350V paper
C5 0.05 $\mu$ F 350V paper
C6 2 $\mu$ F 150V electrolytic
C7 1000pF silver mica
C8 0.01 $\mu$ F paper
C9 100pF silver mica
C10 500pF silver mica
C11 2500pF silver mica
C12 0.01 $\mu$ F 350V paper
C13 0.05 $\mu$ F 350V paper
C14 0.25 $\mu$ F 350V paper
C15 0.1 $\mu$ F 350V paper
C16 32 $\mu$ F 350V electrolytic
C17 32 $\mu$ F 350V electrolytic
C18 32 $\mu$ F 350V electrolytic
C19 32 $\mu$ F 350V electrolytic
C20 16 $\mu$ F 350V electrolytic
C21 0.1 $\mu$ F 750V paper
C22 0.1 $\mu$ F 750V paper
C23 0.1 $\mu$ F 1000V paper
C24 32 $\mu$ F 350V electrolytic

#### Valves:

V1 12AT7	V2 EF86	V3; V5 12AU7
V4 EF86	V6 6X4	V7 E4205-B-7 or VCR139

#### Miscellaneous:

S1, 1p 5W or 2p 5W (see text). D1, OA81, D2 D3 K3/40. L1, Repanco 2.5mH, L2 10H 60mA. Mains transformers 200-240V Primary, 250-0-250V at 60mA, 6.3V at 2.5A, 5V or 4V at 1A.

### SPECIFICATION

#### Y Amplifier:

Sensitivity	150mV/cm adjustable
Frequency response	25c/s-50Kc/s $\pm$ 1dB
	15c/s-200Kc/s $\pm$ 3dB

#### Timebase:

Timebase	10c/s-100Kc/s
X-Amplifier	15c/s-50Kc/s $\pm$ 3dB

### The Y Amplifier

The circuit of this is shown in Fig. 1, from which it will be seen to be quite conventional and straightforward. The input valve V1a is a 12AT7 double triode the other half of which is used as the sync amplifier. V1a is arranged as a cathode follower input stage with the fine gain control VR2 forming the cathode load. This is connected "back to back" with the sync amplitude control. Of the two attributes of a cathode follower, namely high input and low output impedances, use is made of the low output impedance only by connecting, as already described, the gain control across it. The high input impedance has been sacrificed in order to provide a coarse input attenuator in the grid circuit. This is necessary because a high-amplitude signal would overload the stage, and, although VR2 would reduce the signal sufficiently to fill the c.r.t., the waveform would contain distortion that was introduced by the oscilloscope itself due to V1a overloading. Since panel space was at a premium the input attenuator was made in the form of a probe which could be plugged in as and when required. This probe consists of a high-value resistor R1 and low-capacity trimmer TC1 in parallel. At low frequencies R1 and R2 form the potential dividing elements but, as the frequency is increased, the stray capacities to earth play an ever-increasing part so that the attenuation factor is increased. The attenuator can in fact be said to be frequency conscious. The inclusion of TC1 alters this considerably and allows an attenuator to be constructed that is for practical purposes, not frequency conscious. The optimum value for TC1 is when the time-constant of C1 R1 is equal to the time constant of R2 x strays and, since the strays cannot be calculated, TC1 is made a trimmer with a maximum capacity of 30pF. An incidental though important advantage of using such a probe is the reduction in the input capacity of connecting cable plus strays imposed upon the circuit under test.

V2 provides the bulk of the Y amplifier gain and comprises a triode connected EF86. Two minor modifications to this stage can increase the input sensitivity but at the expense of a much-curtailed h.f. response. These are increasing the value of the anode load and connecting the valve as a pentode. The h.f. response is further extended by the frequency conscious characteristics of L1

and C5. The impedance of L1 increases with increasing frequency and, since it is in series with R7, the o/p tends to increase. Similarly the impedance of C5 decreases, so shunting or bypassing R8 more and more, their combined result being to increase the o/p from V2, thus compensating for the h.f. losses incurred elsewhere in the circuit.

The E4205-B-7 in common with many other c.r.t.'s benefits from the use of symmetrical deflection. V3 is accordingly connected as a push-pull o/p stage, the anodes being directly coupled to the c.r.t.'s Y1 and Y2 plates. Vertical movement of the trace is accomplished by altering the grid bias on V3b by means of VR3, which causes the d.c. potential of V3b anode to alter with respect to V3a anode. Since these anodes are directly coupled to the Y1 and Y2 plates the change in the d.c. potential causes the trace to move up or down. It must be noted that too much vertical movement is very undesirable, requiring as it does an excessive change in the valves' grid bias with the attendant danger of waveform deformation.

**The Sync Amplifier**

Although some sync signals could have been introduced from the Y-amp to the t.b. by means of a simple capacitive coupling the inclusion of an amplifying and limiting stage was considered to be well worth the slight increase in cost and complexity. The sync take-off point is by means of VR1, which as the sync amplitude control allows just the right amount of sync to be selected. V1b operates with zero grid bias and so tends to amplify only positive-going signals which emerge from the anode in an amplified and phase-reversed form, i.e. negative going. These are then fed to

the suppressor grid of V4 via C7, thus synchronising it to the waveform under examination. Since D1 clamps any positive-going signals which may have escaped the limiting action of V1b, V4 is synchronised by negative-going signals only, obviating the jitter caused by double synchronising by positive and negative peaks.

**The Timebase**

This is a comparatively simple circuit but still provides an adequately linear sawtooth waveform. The five coarse speeds are selected by S1, which switches the appropriate integrator capacitor into circuit. Fine speed is controlled by VR5, which provides a small overlap from range to range. In the interests of simplicity and space economy the flyback capacitor consists of just C8 instead of being switched in step with C9 to C13. This has the disadvantage that the flyback speed varies from range to range, though the value finally selected for C8 was a reasonable compromise. Constructors wishing to switch in different flyback capacitors could use a two-pole switch and arrange it to select capacitors having values of 1/3 to 1/5 of those integrators they are in step with. Flyback suppression was not included in the prototype but can be added quite easily if desired and is shown dotted in the t.b. circuit. The values shown may require adjustment, particularly the 0.001µF capacitor to the c.r.t. grid, the value of which should be no higher than is necessary for adequate blanking.

The timebase output is taken from the slider of VR4, which is the X gain or width control and is fed via C14 to V5, the t.b. amplifier stage, which is similar in design to the Y o/p stage. Since an extended h.f. response is unnecessary here the anode loads have been increased in value to

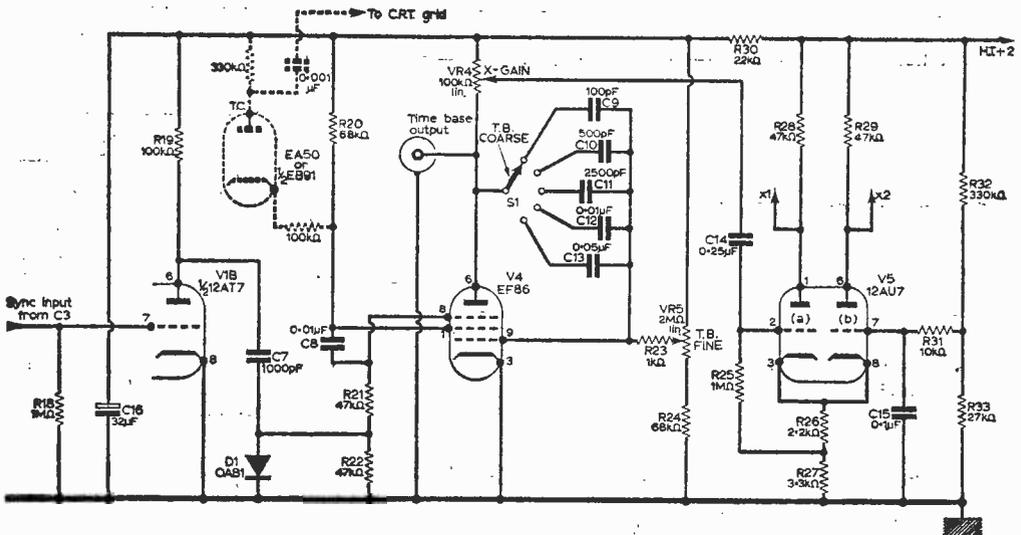


Fig. 2: The timebase and symmetrical deflection amplifier (X-amp). The dotted components comprise the flyback blanking circuitry.

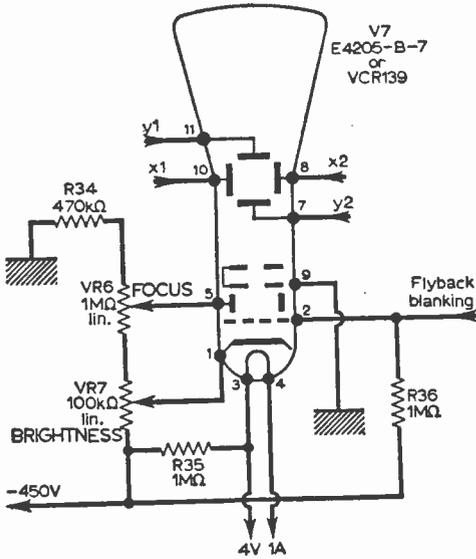


Fig. 3: The c.r.t. network including brilliance and focusing controls.

require adjustment in individual cases to bring the trace to a central position on the screen.

**The C.R.T. Circuit**

This does not call for any particular comment except for saying that the capacitor used for coupling the flyback pulses to the grid must be of impeccable character. The tube will almost certainly be damaged if this should break down and allow a comparatively large positive voltage to be impressed upon the grid for any length of time.

**Power Supply**

The power supply circuit is quite conventional. Two separate, well filtered and decoupled (from each other) h.t. supplies are provided for the Y amplifier and t.b. circuits. By using a 6X4 or U78 rectifier and running its heater from the common 6.3V line the 5V winding is left available for the c.r.t. and, since its heater requires 4V at 1A, a 1Ω 1W resistor (R37) is used to drop the surplus volt. This expedient will not, of course, be necessary where the transformer already has a suitable 4V winding. The normal rectifier heater windings are well insulated and are eminently suited to feeding the c.r.t., the heater of which is at a quite high potential with respect to chassis. A voltage doubler comprising C23 and D2. D3 provides some -450V e.h.t. and although the trace is not as bright as it would be with 1,000V e.h.t. it is still adequate in all but the brightest light. The current demands are very modest and so a simple filter comprising R40 and C21. C22 is all that is necessary for adequate e.h.t. smoothing.

**PART 2 NEXT MONTH**

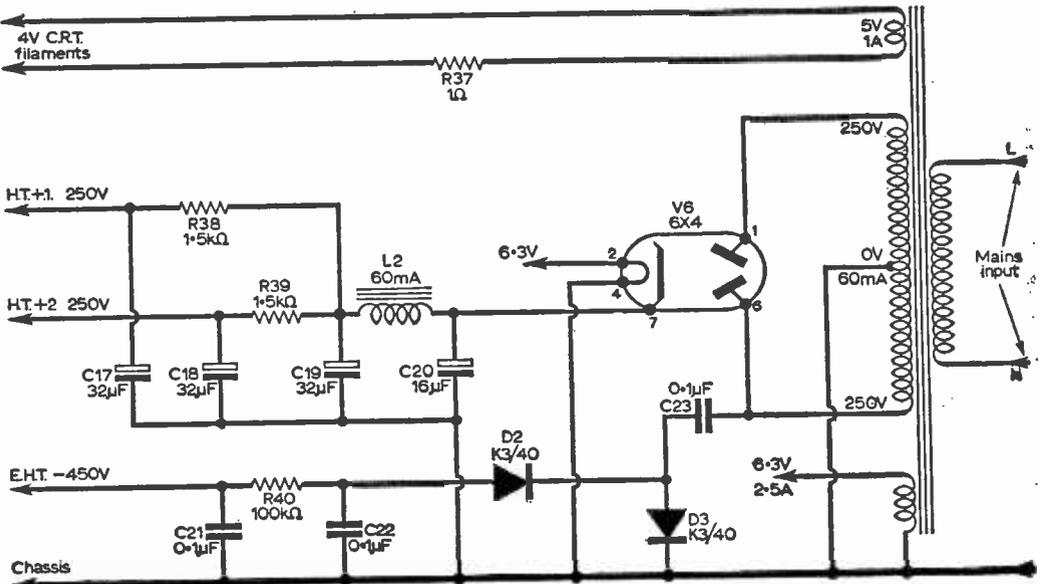


Fig. 4: The oscilloscope power supply unit.



# REDUCING TRANSMITTER BCI/TVI

BY F. G. RAYER G30GR

IT is a great inconvenience to everyone when television or broadcast band interference is caused by one's own transmitting equipment as this imposes limits on operating. However, after some experiment the writer found it possible to operate a 150W transmitter, with full high-level modulation on all bands from 1.8Mc/s to 14Mc/s, with no interference to the radio or television receivers in the same house.

The complete removal of all broadcast band or TV interference seems often to be extremely difficult. But it is hoped that some of the causes and possible cures given here will be helpful.

### Broadcast Images

Very many domestic broadcast band receivers are superhets with a frequency changer as first stage and an i.f. of about 470kc/s. These receivers are susceptible to second channel or image frequency interference. Points at which this will arise are easily calculated.

As an example suppose the wanted broadcast station uses 1,000kc/s (300m). If the receiver i.f. is 470kc/s the receiver oscillator is tuned to 1,470kc/s. The second channel is 470kc/s above 1,470kc/s or 1,940kc/s. This is in the 1.8-2.0Mc/s amateur band. So if the transmitter is operating around 1,940kc/s it will probably be heard on the receiver.

This interference is tunable on the receiver. It may easily be possible to use a transmitter frequency which does not result in the unwanted signal falling on or near a wanted broadcast station.

Receiver oscillator harmonics cause similar trouble. Suppose the broadcast band receiver is tuned to 1,100kc/s. The receiver oscillator is then on 1,570kc/s if the receiver i.f. is 470kc/s. The second harmonic of 1,570kc/s is 3,140kc/s. This

will beat with an amateur signal on 3,610kc/s to produce a 470kc/s output. So the amateur signals in the 3.5-3.8Mc/s band can also be tuned in on the receiver.

Again this trouble can be avoided by using frequencies which do not result in such spurious receiver responses falling on or near wanted stations. With troubles of this nature any steps which reduce the power of the amateur signal at the receiver will help alleviate the interference.

If the transmitter radiates harmonics these will probably cause television interference. Multiples of frequencies in the h.f. band easily fall near TV channel frequencies. A harmonic detector such as that in Fig. 1 will help check for unwanted output at multiples of the transmitter frequency. Many crystal and other oscillators produce strong harmonics and may in fact be designed to do so for multi-band work. So it is wise to have several tuned circuits after the oscillator.

In the home-built transmitter mentioned a 7Mc/s v.f.o. was followed by a 7Mc/s buffer, working into a 14Mc/s doubler-amplifier, which in turn was followed by the 14Mc/s p.a. Each stage was tuned and with this line-up no harmonic output could be detected. When using an end-fed aerial an aerial tuner was also added to provide one further tuned circuit.

### Little Suppression

If the transmitter has much harmonic output this may well be due to some of the broad-banded or untuned types of coupling which are often used to simplify band changing. Some of these circuits offer little suppression of unwanted harmonics.

Harmonics may be reduced by adding a harmonic filter in the transmitter. One simple circuit is shown in Fig. 2. It is a series tuned acceptor and can be adjusted with a grid-dip oscillator or by reference to the offended TV receiver or a harmonic detector.

An aerial which is a good harmonic radiator will naturally increase troubles from this cause. An end-fed aerial will often work effectively as a harmonic radiator. A coaxial or twin-lead-fed dipole may also be fairly effective at odd multiples (3, 5, etc.) of the transmitter frequency.

In some tests changing from an end-fed aerial to a 14Mc/s dipole very greatly reduced TVI. In these tests TVI was less when using the end-fed aerial with a tuner. With a popular commercially made transmitter TVI was bad with an end-fed

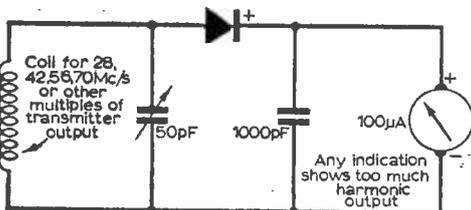


Fig. 1: Harmonic Detection.

aerial but slight with a dipole. This also seemed to be bound up with the presence of stray radio frequency currents in house wiring, etc.

**Stray RF**

With an end-fed aerial the return r.f. path must be through earth, the earth connection, mains wiring to the transmitter, etc. With a system such as a balanced dipole this return r.f. path is not employed as the r.f. power is applied to the two halves of the dipole, not to an aerial and earth.

In tests balanced dipoles were always found much less likely to cause interference than end-fed aerials. End-fed aerials were at their worst when in part near house mains wiring, etc. That is, when causing strong r.f. currents in other circuits.

A separate good r.f. earth for the transmitter was also found helpful in reducing TVI. In some tests TVI was extremely bad when earthing of the transmitter was via the mains earth. Here no other change than providing a good r.f. earth almost wholly removed TVI. The actual length of the earth connection can be important and, if long or near resonant frequency on transmitter frequency or harmonics, then two or three alternative earths of different length can be provided.

**Blanketing**

The amateur signal may be so strong in the immediate vicinity that it breaks through on broadcast band or TV receivers, even if no spurious or harmonic responses arise. This was experienced on 80m when an end-fed aerial download ran within a few feet of a room in which a broadcast band receiver was used. The transmitter signal completely blanketed reception and was not tunable.

This was completely cured by changing to a dipole, though the dipole feeder ran over exactly the same path as the original download.

Blanketing will be reduced by steps which reduce the strength at the receiver of the offending signals. Single-wire downloads which radiate may cause the trouble. Or it may help to remove the transmitter aerial from near the receiver or its aerial. When this fails filters or wavetraps are often added at the receiver.

For a TV receiver a high-pass filter is probably most suitable. But no such filter was found necessary when taking the other precautions so far described here.

**Mains Suppressors**

Where r.f. is passing from the transmitter to the receiver through the mains a suppressor such as that in Fig. 3 may be helpful. Something of this kind is often present in commercially made equipment. The chokes are probably best placed inside the transmitter but immediately adjoining the point where the mains power lead enters.

A suppressor may be added at the receiver if this is found helpful. But it is probably better to keep r.f. out of the mains by measures at the transmitter itself or by using some balanced aerial system.

If a driver or power amplifier stage is operated at an unnecessarily high level of grid drive this is supposed to increase the chances of harmonic

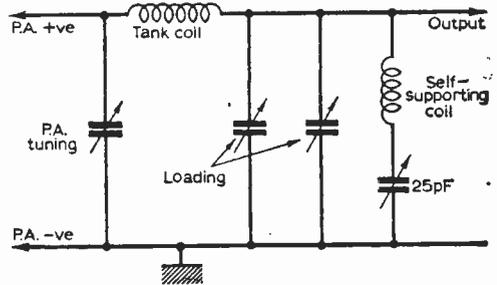


Fig. 2: Tunable Harmonic Trap.

output. In the home-built transmitter mentioned the grid drive on each stage was kept just about at the level needed for efficient working.

Later it was found that no interference troubles arose even if drive was increased to twice that normal. But with other transmitters it may be worth running each stage with the minimum drive which does not cause a loss of efficiency.

If interference is bad it may be worth running the transmitter into an artificial aerial for a first test. For a.m. equipment this can be a 100W or other suitable domestic-type lamp. It may be screened with an old cabinet, metal box or other means if required.


If interference ceases or is much reduced with the a.a. then the transmitter aerial or aerial/earth system, including the aerial feeder, are suspected. But if interference remains very bad, then the offending signals are probably travelling on the mains or reaching the receiver by direct radiation from the transmitter.

Radiation from the transmitter can be much reduced by good screening. But it was found that totally unscreened transmitters could quite often be operated with no broadcast band or TV interference to receivers only a few feet away.

When testing the effect of various aerials it was generally found that a tuned doublet with an open-wire feeder had the same advantages as a dipole with low-impedance feeder. As the tuned doublet can be used for several bands it may be preferred.

A watch should be kept for individual, unnecessary forms of coupling between transmitter and receiver. One set of equipment, used for many months, always caused TVI. This transmitter was placed near a wall and the TV receiver aerial

—continued on page 576

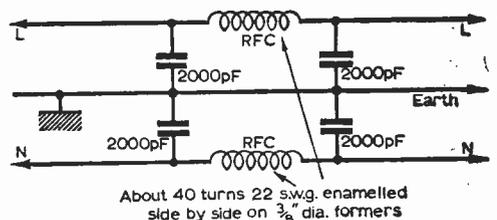

About 40 turns 22 sw.g. enamelled side by side on 3/8" dia. formers

Fig. 3: Mains Suppressor.

FOR  
THE BEGINNER

# SELF REGULATING TRANSISTOR CIRCUITS

BY G. R. WILDING

**P**ARALLEL with the dramatic improvements in transistor performance over the past few years has been the improvements in transistor circuitry with especial emphasis on self regulating and stabilising arrangements to protect and enhance portable design.

Thus current designs now incorporate circuitry to stabilise the output transistors bias, compensate for cabinet temperature rises, protect against overloads, extend a.g.c. characteristics, stabilise power supplies in battery/mains versions, and stabilise the v.h.f. oscillator voltage in f.m. models.

To this end small diodes and transistors connec-

ted as diodes are mainly used, but miniature thermistors and voltage-dependent resistors (v.d.r.'s) are also utilised.

Probably the most important self-regulating device is that which controls the base bias of the output transistors within quite wide battery voltage variations and also increases battery economy.

As is well known, particularly with push-pull output stages, it is very important to obtain correct base biasing. Insufficient bias causes cross-over distortion due to the extremes of the half-cycles not being fully amplified, while excess biasing causes an unnecessarily high no-signal standing current.

Thus if biasing is just right when a new battery is fitted it tends to fall off with falling battery voltage.

To avoid this, a transistor connected as a diode, is wired from the lower end of the base biasing resistor to chassis thus forming the bottom end of a potential divider. (Fig. 1).

However, the internal resistance of a transistor so connected, increases as the applied voltage decreases, so that as the terminal battery voltage falls, a relatively larger proportion of it is developed across transistor Tr1.

This voltage is also the biasing voltage to the two power transistors so that over a longer period of time than usual, the battery can correctly work the output transistors.

Furthermore, should the temperature rise excessively so that the output transistors reduce their normal internal resistance and pass excessive collector current, the control transistor Tr1 will similarly be affected, its volts-drop will reduce and thus bias back the output stage.

Other makers use somewhat similar schemes to provide bias stabilisation but all generally operate on the same principle, the variation of a diode or diode-connected transistors internal resistance with applied voltage.

However, one or two models made by Berec and Ever Ready, and quite a few Car Radios made by Radiomobile, Ekco and Motorola etc. which are of course especially liable to extremes of temperature, employ miniature thermistors to keep the output transistors correctly biased in spite of excessive cabinet temperature.

The basic circuit is very simple and merely comprises the shunting of the thermistor across the bottom section of the resistor potential divider that biases the output transistors.

Thermistors type KS2Y, VA1040 and VA1039 are usually used and in Fig. 2 can be seen the typical arrangement as used in some Ever Ready "Sky Prince" and "Brigand" receivers where the thermistor is paralleled across the bottom 33Ω resistor of the 1 2K/33Ω voltage divider combination.

As temperature increases, the ohmage of the thermistor

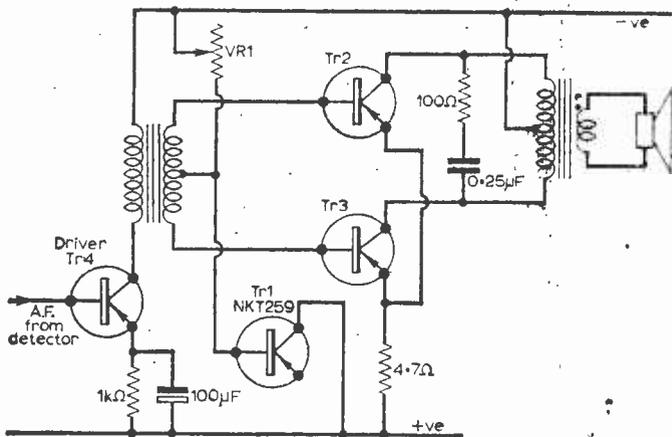


Fig. 1: Typical bias stabilisation circuit (Ferranti). As battery voltage falls it increases internal resistance developing a higher proportion of the available e.m.f. and thus maintaining output transistor bias constant over a wide battery voltage range.

decreases and reduces the potential developed across it, thus biasing back the output transistor pair.

A really effective a.g.c. system is probably the most difficult section of a small transistor portable to design, since transistors are essentially current and not voltage operated devices, while a.g.c. bias can only usually be applied to an r.f. or i.f. stage since application of the bias to the frequency-changer would result in mis-tuning with variations of voltage.

It is often the practice to augment the normal a.g.c. control with a transformer damping arrangement so that on these high inputs the "Q" of an i.f. transformer can be cut down.

In practice it is usually the primary of the first i.f. that is selected and Fig. 3 shows a very typical arrangement.

The series combination of the OA79 diode and 680Ω resistor links the live end of the i.f.t. 1 primary to the junction of the decoupling resistor and capacitor of the i.f. amplifier's collector.

Under normal no-signal conditions the anode connection to the rectifier is slightly more negative than the cathode so no conduction occurs, the combination is virtually open circuit and no loading is imposed of the i.f.t. primary.

However, should a very strong signal be received so that the i.f. transistor is fed with a heavy a.g.c. bias, its collector current will reduce and its collector voltage rise to approaching that of the frequency-changer. Partial conduction through the rectifier and resistor occurs, loading i.f.t. 1 primary, and reducing gain.

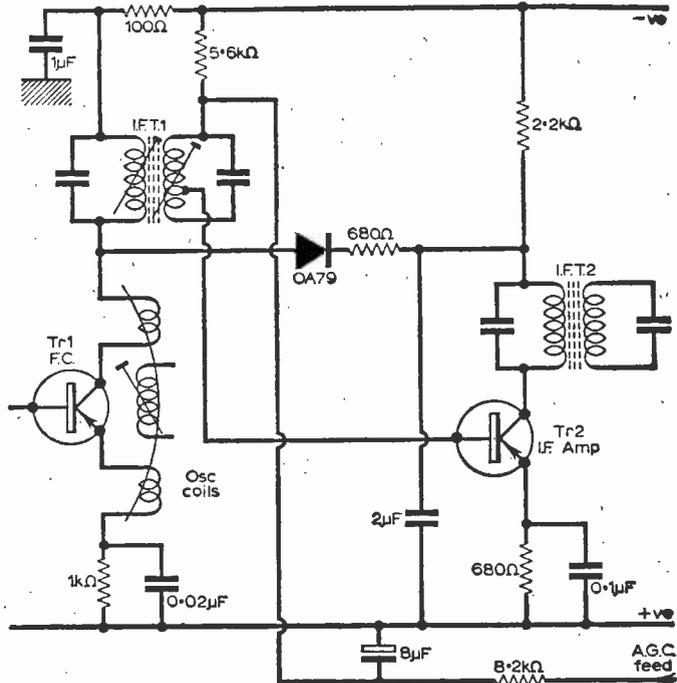


Fig. 3: Typical a.g.c. circuit incorporating transformer loading (Sobell). Normally anode connection to OA79 is more negative than cathode connection and no conduction occurs. However as a.g.c. voltage on strong signal reduces T2 collector current, T2 collector voltage increases above that of T1, conduction occurs through the rectifier and the combination of rectifier and 680Ω resistor loads the I.F.T.1 primary via 2μF capacitor.

Particularly strong inputs will raise the Tr2 collector voltage above that of Tr1 and so bias the rectifier that it acts almost like a short circuit in series with the limiting 680Ω resistor heavily curtailing "Q" and gain. Naturally, this transformer damping results in some slight loss of selectivity, but the freedom from over-loading more than compensates.

Other makers vary the design by tapping the rectifier across a section of the i.f. winding or by completely eliminating the series resistor, while one or two designers shunt the rectifier across the aerial coils and control it from the emitter resistor of the i.f. amplifier.

Most all-transistor Car Radios employ an r.f. stage, not merely to provide extra gain, and maintain volume over widely varying reception conditions, but also to help maintain the signal input voltage to the frequency-changer within fairly close limits as big changes in input strength can cause mistuning in a transistor mixer stage.

To this end, the r.f. stage is

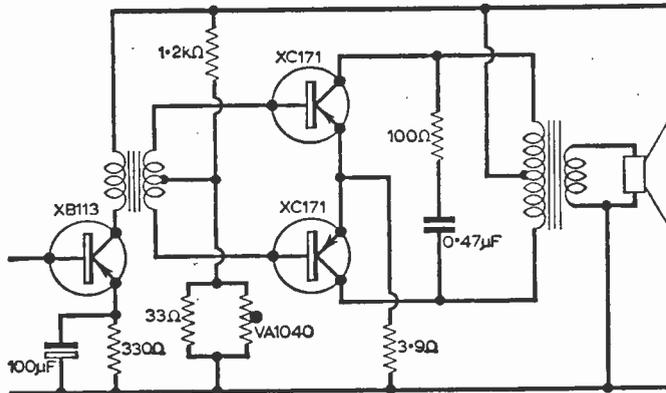


Fig. 2: Bias stabilisation circuit using thermistor. (Ever Ready Berec) thermistor VA1040 decreases the p.d. developed across the 33Ω resistor as temperature rises thus biasing back the twin output transistors.

a.g.c. controlled by a separate diode from the detector, and is fed by a small capacitor from the collector of the i.f. transistor.

Fig. 4 shows a typical a.g.c. circuit to the r.f. stage and it will be noted that the diode is shunted across the a.g.c. line to provide the rectifying action.

Also present in the circuit is a voltage dependent resistor paralleled across the aerial tuned circuit but in no way connected with the a.g.c. action.

Car radios invariably operate on a low signal/noise ratio and on many occasions can be subject to very heavy brief bursts of interference, which apart from its aural objections can momentarily over-run the transistors. The v.d.r. prevents this for while acting as a very high value load on low value signals, performs as a much lower one on high value signals and thus effectively cuts down their strength.

Quite a number of table-size transistor receivers are available in mains/battery versions, and while the power supply circuits in these is always orthodox, the associated voltage stabilising system is often a new development.

In the eight transistor Ferranti MBT1089 receivers for instance, a conventional quadruple rectifier bridge circuit provides the rectified d.c. power for the receiver, but it is fed to the circuit via a NKT251 power transistor.

The smoothed output from the rectifiers is fed

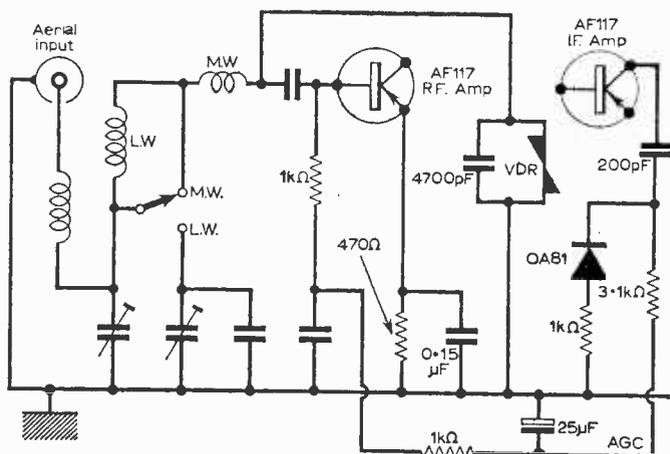


Fig. 4: Skeleton r.f. amp and a.g.c. circuit all-transistor car radio (Motorola). Separate a.g.c. circuit controls r.f. stage only while v.d.r. shunted across aerial coils clamps down on heavy interference peaks.

to the transistors collector and taken off at the emitter, so that it is virtually in series with the d.c. supply.

However a separate small rectifier produces a separate reference voltage from another secondary winding which is used to bias the base of the transistor, so that increases or decreases of mains voltage increase or decrease this base bias and vary its internal resistance to provide a very constant output indeed.

Adjustment of the 5kΩ potentiometer selects the optimum output voltage which is then automatically maintained by this simple circuitry.

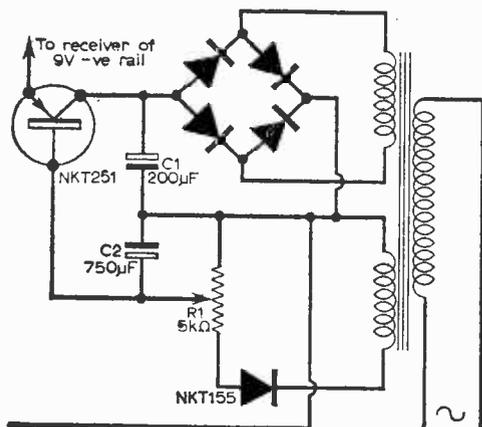


Fig. 5: Stabilised power supply circuit for battery/mains transistor sets (Ferranti). The entire d.c. output passes through the NKT251 power transistor to the receiver's negative rail. Variations in mains voltage produce similar variations across R1 which are applied to the base of the transistor so that its internal resistance is varied accordingly. When mains voltage rises its internal resistance increases, taking up a larger volts drop, and maintaining output within very close limits.

## REDUCING BCI/TVI

(continued from page 573)

feeder ran on the outside of this wall only a few feet from the transmitter. With this set of equipment merely moving the transmitter to the other side of the room reduced TVI very much.

It will be noted that licence conditions stress that "every precaution shall be taken to avoid over-modulation". When making tests it was found that any over-modulation often immediately caused bad interference.

In the circumstances described it was found possible to operate on the 14Mc/s and lower frequency bands with no TVI on a receiver a few feet away in another room. As these bands were those most wanted only a little attention was given to possible TVI from working on 21Mc/s and 28Mc/s bands.

The home-built transmitter covered the 21Mc/s band and gave no broadcast band interference but bad TV interference on this band. As the third harmonic of 21Mc/s (63Mc/s) was not very far removed from the particular BBC-TV frequency it was felt this problem would have to be examined separately.

A commercially made transmitter also gave bad TVI on 21Mc/s and 28Mc/s but not on 14Mc/s. When using the latter band TVI was not experienced on either BBC or ITA channels. ■

**THE "VICEROY" 30 watt amplifier**

Valves 2 x EL34, GZ34, EP86, ECUC82, ECUC83. Size 14 x 8 x 7 1/2 in. high over cover. Complete with protective cover with carrying handles. High and low gain inputs. Front control are: Vol. (low gain), Vol. (high gain), Treble Step, Bass, Treble Slope and Mains Switch. For 3 and 15 ohm Speakers. Price £19.19.0 (carr. pd.).

**4-SPEED AUTOCHANGERS**

BSR-UA14 .....	£5.19.6
GARRARD AUTOSLIM .....	£6.7.6
GARRARD STEREO .....	£8.15.0
AT9 .....	£10.7.6
AT6 STEREO .....	£19.17.6
TYPE 3000 .....	£9.10.0

Carr. 5/- each

ATTRACTIVE CABINET TO FIT ABOVE CHANGERS (and to take our 3 valve Gram. Amp. at 60/-) 57/6 (carr. 6/6).

**13 x 8in. LOUDSPEAKERS 49/6**


Three ohm. Ceramic magnet of latest type. BRAND NEW. (post 3/6).

**HEATER TRANSFORMER**

Mains input giving 6.3v. 2 amp. Size 2 1/2 x 2 x 1in. (2 1/2in. over winding). 6/6 ea. Less 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 6, post free more than six.

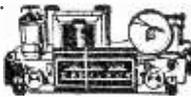**SELF-POWERED V.H.F. TUNER CHASSIS.**

Covering 88-95 Mc/s. Mollard permeability tuner. Dims. 8 x 6 x 6in. high. Valves ECUC85 and EABC80 with metal rect. Mains transformer. Fully wired and tested ONLY £8.17.6 (carr. paid). Room dipole 12/6. Feeder 6d. per yard.



**AMERICAN BRAND RECORDING TAPE**

FULLY GUARANTEED AT RECORD LOW PRICES

**MYLAR BASE**

7in. Stand. play, 1,200ft. ....	12/6
7in. Long play, 1,800ft. ....	19/6
5in. Double play, 1,200ft. ....	15/-
5in. Double play, 1,800ft. ....	23/6
7in. Double play, 2,400ft. ....	25/-
5in. Triple play, 450ft. (Plain white boxes) .....	12/6
3 1/2in. Triple play, 600ft. (Plain white boxes) .....	14/-
5in. Triple play, 900ft. (Plain white boxes) .....	22/6
5in. Triple play, 1,300ft. (Plain white boxes) .....	42/6
7in. Triple play, 3,600ft. (Unboxed) .....	75/-

**ACETATE BASE**

5in. Stand. play, 600ft. ....	8/-	MESSAGE TAPES	
7in. Stand. play, 1,200ft. ....	11/-	3in. Stand. play, 150ft. ....	3/6
5in. Long play, 900ft. ....	10/-	5in. Long play, 225ft. ....	4/11
5in. Long play, 1,300ft. ....	12/6	3in. Stand. play, 300ft. ....	7/6
7in. Long play, 1,800ft. ....	15/-		

Postage 1/- per reel (4 or more post free)

**4 to 5 WATT HIGH GAIN AMPLIFIER**

Suitable for record player, radio, tape after equalisation. Double wound mains transformer. Fully built. For A.C. mains of 200/250 v. 14 dB eq. feedback. Controls are volume (on/off), treble and bass. Contact coil-metal rectifier (bridge). ECUC82 and EL84 valves. Output for 2-ohm speaker. Chassis size 6 1/2 x 8in. (over spindle); overall height, including valves, 5 1/2in. Phono sockets for high and low input.

PRICE only £4.19.6 (P. & P. 6/-).

STEREO VERSION of this Amplifier, £5.2.8 (P. & P. 6/-). Using 2 x UCUS9 giving 2 x 3 watts. Outputs for 3-ohm speakers. Switch for mono/stereo giving mono at 5 watts. Suitable for Record Players, etc. For mains 200-250 v.

**SINCLAIR MINIATURES**

The MICRO-3. Self contained pocket radio, size only 1 1/4 x 1 3/16 x 3/16 in. Truly amazing performance. All parts complete with carbon and detailed construction data. Mercury cell 1/11 extra (2 required). Can be built for 59/6.

The SLIMLINE. 2-transistor pocket radio size only 2 1/2 x 1 1/2 x 1 1/2 in. Micro alloy transistorised and printed circuit. All components available separately easy to assemble. Can be built for 49/6.

The X10. 10 watt power amplifier with integrated pre-amplifier. Requires only 1mV. for an output of 10 watts undistorted. Size only 6 x 3 x 3 in. Weight 5 oz. Circuit uses 7 M.A.T.s and 4 RF power transistors. Kit price £6.19.6.


Available ready built, tested and guaranteed, £6.19.6 post free. 3 pots. for vol., Bass and Treble, 7/6 the 3 extra. Mains power pack. if required 54/-.

**6-TRANSISTOR PORTABLE—Fully Built**

The "SCALA" for only £4.19.6 carr. paid. 8 1/2 x 2 x 6 1/2 in. high. Choice of colours. Rexine. M.W. and L.W. Ferrite aerial. Battery 2/9 extra. Printed circuit. Nicely styled. A professional job 3 1/2 in. speaker. Fully tunable M.W. and L.W. Superbet circuit.



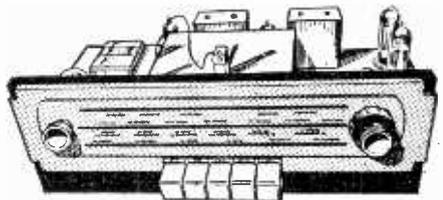**BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.13.0 (Carriage Paid)**



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dia. 1 1/4 x 4 in. in 2 colours, predominantly cream. 200-250v. A.C. only. Pick-up. Ext. Speaker. Ac., E., and Dipole sockets. Five pushbuttons—OFF, L.W., M.W., P.M. and Gram. Aligned and tested. O.P. Transformer. Tone control. 1090-1900 Mc.; 200-550 Hz.; 88-98 Mc/s. Valves EZ80 rect.; 12H61, EP59, EABC80, EL84, ECUC85. 3-ohm speaker required. 10 x 6in. ELLIPTICAL SPEAKER 25/- to purchasers of this chassis. TERMS: £3.10.0 down and 5 monthly payments of £2.4.0, total £14.10.0. Room Dipole for V.H.F., 12/6. Feeder 6d. per yard. ALTERNATIVE DESIGN. L.W. 1000-1900 M.; S.W. (9-15 Mc/s); M.W. 190-475 M.; V.H.F. 87-100 Mc/s.; Gram position. Otherwise similar to above chassis. Price £15.15.0 (carr. paid). TERMS: £3.10.0 down and 6 monthly payments of £2.4.0. Total H.P. price £16.14.6. Circuit diagram 2/6.

**2-VALVE GRAMOPHONE AMPLIFIER**

Price 37/6 (P. & P. 2/6)

Overall size 4in. wide x 5in. high x 2 1/2 in. Volume and tone controls. (Mains lead. Screened lead input. With output transformer for 3-ohm. For series connection to Garrard and B.S.R. Autochangers and Players. having 90v. tapping.

Can also be supplied on fabric covered board with mains transformer and 6 x 4in. speaker at 55/-. (P. & P. 5/-).

3-Valve Gram. Amp. on board 14 x 7 1/2 in. (2 1/2 in. overall). UY85, UC086 and UL84. Speaker 7 x 4in. Price 60/- (P. & P. 6/-).

**BATTERY ELIMINATOR**

For 4 low consumption valves (96 range) 90v. 15mA and 1.4v. 125mA. 42/6. (4/- post), 200-250v. A.C. Also for 250mA, 1.4v. and 90v. 15mA at same price. Two units 4 x 2 1/2 x 2 1/2 in. high and 3 x 2 1/2 x 1 1/2 in. high.

**PUSH-PULL O.P. AMPLIFIER**

£5.5.0 (6/- Carr.)



Brand new 200-240 A.C. mains Bass, treble and vol. controls, with valves EZ80, ECUC83 and 2-EL84 giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans for 2-ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "bying panel".

**4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE**

PRINTED CIRCUIT. 4 x 2 1/2 x 1 1/2 in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player and intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Three types, 200mW. 85/-; 600mW 41/-; 1.2W. 57/6. (P. & P. 2/6 each).

**CM21 CRYSTAL MICROPHONE**

With 3.5 mm. Jack plug 12/6 (Post 1/6.)

4 TRANSISTOR BABY ALARM. Attractive walnut veneer speaker cabinet 13 1/2 x 8in. front. Barpiece as mike sensitive at 20ft. 60ft. Ext. Lead. (P.P.G. battery required—will last for hundreds of hours). Volume Control and On/Off. Price £3.19.6. (P. & P. 5/-).

**TAPE RECORDER AMPLIFIER**

Fully built. Front panel 12 1/2 x 3in. Chassis size 10 1/2 x 5 x 4in. Valves EP86, ECUC83 and 2-EL84. Controls (1) Mic. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor, (4) Tone. 2 jack sockets for Tuner/P.U. and Mic-switch for superimpose. Separate power pack containing trans. and rectifier. For Collaro studio deck only. Price £32.14.0. (6/- P. & P.)


**GLADSTONE RADIO**

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses.) Aldershot 22240  
CLOSED WEDNESDAY AFTERNOON  
CATALOGUE 6d.

Regret overseas orders cannot be executed

Please also see our advertisement on page 11.

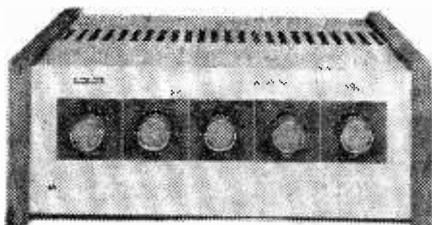

model 222



# IS AUDIO

To amplify this statement, or your music, choose model 222 Integrated Stereo Amplifier. Designed with the new high quality ceramic pickups such as the Decca Deram in mind, and having stereo and mono inputs for ceramic and crystal pickups, tape playback and radio, tape recording outputs suitable for virtually any tape recorder, 20 watts push-pull power output, frequency response 30-20,000cps  $\pm$  1db, distortion less than 0.5%, this unit is an opportunity to acquire the basis of a genuine high fidelity system at relatively economic price. Matching this or any other good quality amplifier are two Armstrong tuners, and all three units have been selected for The Design Centre, London where model 222 is on display. For full details and technical specifications of complete range, plus list of over 300 stockists, post coupon or write, mentioning

- 222 Integrated Stereo Amplifier £27-10-0
- 223 AM-FM Tuner £28-15-0
- 224 FM Tuner £22-10-0
- Optional cases. Teak and vinyl hide £3-10-0

ARMSTRONG AUDIO LTD - WALTERS RD - N.7  
Telephone: NORth 3213

Name \_\_\_\_\_

Address \_\_\_\_\_

11PW65

## BARGAINS FROM BROADWAY ELECTRONICS

**TRANSISTORS:** AF115, AF116, AF117, OC170 all at 4/6 ea. OC26 7/6, Mullard RF Packs OC44 two OC45 12/6; AF Packs OC81D two OC81 8/6; OC44 3/6; OC45 3/-; OC71 2/6; OC72 3/-; OA81 Diode 2/3; ORP12 Light Cell 7/6

**TRANSISTOR ELECTROLYTICS:** 1, 2, 4, 5, 8, 10, 16, 32, 50, 100 mfd. all at 15 volts, 1/3 each.

**EARPIECES** with cord and 3.5 mm plug 8 ohm magnetic 3/-; 250 ohm 4/-; 180 ohm magnetic with clip 6/6; Xtal 4/-.

**GUITAR PICK-UP** complete with clip and screened lead, 12/6.

**B.M.3. XTAL MIKE** 30/-; table stand for same 9/6.

**GARRARD A.T.6.** Mono £8.19.6. Stereo £9.5.0. A.T.5. Stereo £8.10.0. New 1000 £6.15.0; Autoslim pick-up arm fitted with Ronette Stereo only 25/-; A.T.6 shells 6/6; GC8, GC2 cart. with brackets 15/- ea. Motor Board 15 x 14in. 12 mm ply cut out for Garrard or B.S.R. changer 7/6 ea.

Cabinets suitable for tape deck, A.T.6 etc., 18 x 14 1/2 x 8 1/2in. covered in red and black Rexine with carrying handle. 67/6. Speaker cabinets to match with sloping front to take 12in. speaker. 42/6; to take 10in. speaker. 37/6.

The "BLAKE" 12in. Heavy Duty Cabinet. Size 24 1/2 x 18 x 8in. The Baffle is 1in. thick. Plain white wood £3; covered in Rexine and Vynair 55/-; De Luxe model veneered with wood grain Formica and standing on smart 6in. legs £5. Please add 10/- for carriage.

"HAYDON" Cabinet. 16 1/2 x 15 x 7 1/2in. Fabric covered, suitable 12in. speaker 45/-. Postage 7/6.

Vynair speaker cloth 50in. wide 14/- yard.  
Rexine leather cloth 50in. wide 10/6 yard (S.A.E. for samples).

NEON PANEL LIGHTS. 240V A.C. Arcoelectric, 2/6 ea.  
TERMS: C.W.O. or C.O.D.

Plus post and packing charge. Garrard changers etc., 6/-.  
Small parcels 6d.

## BROADWAY ELECTRONICS 92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3934  
(four minutes from Tooting Broadway Underground Station)

## BUILD OVER 40 CIRCUITS/EXPERIMENTS and learn Electronics the LERNAKIT way

INCLUDING

- CATHODE RAY OSCILLOSCOPE
- VALVE EXPERIMENTS
- BASIC AMPLIFIER
- BASIC RECTIFIER
- PHOTO ELECTRIC CIRCUIT
- TIME DELAY CIRCUIT
- SQUARE WAVE GENERATOR
- SIMPLE TRANSMITTER
- TRANSISTOR EXPERIMENTS
- BASIC OSCILLATOR
- ELECTRONIC SWITCH
- SIGNAL TRACER
- BASIC COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- MORSE CODE OSCILLATOR ETC. ETC.

This complete practical course will teach you all the basic facts of electronics by making experiments and building apparatus. You learn how to recognise and handle all types of components — their symbols and how to read a circuit diagram. You see how circuits are built and how they work BY USING THE OSCILLOSCOPE PROVIDED. Applications of all the main electronic circuits are demonstrated—radio reception and transmission; photo-electrics; computer basics; timers; control circuits, etc; including servicing techniques. NO MATHS USED OR NEEDED. NO THEORY NEEDED. NO PREVIOUS KNOWLEDGE OR EXPERIENCE NEEDED. Tutor service included. No extras needed. Send now, for FREE DETAILS without obligation, to address below.

TO: LERNAKIT, RADIO HOUSE,  
40 RUSSELL STREET, READING

Please send free Brochure without obligation—

**POST  
NOW**

NAME .....

ADDRESS .....

(No representatives employed) P.W. 11/66



# SHOWTIME

\*\*\*\*\*

## A SUMMARY OF THE NEW MODELS

**I**N the absence of a Radio Show this year, many manufacturers booked hotel suites to display their new season's models to the trade. There were hundreds of new radio receivers, record players, tape recorders and radiograms, many of them extremely attractively presented. There was little, however, to excite us technically and the main trend noticeable was the obvious one of the spread of transistors to more and more record players, radiograms and tape recorders. There was a good deal more stereo equipment and more bandspreading (not only the h.f. end of the m.w.), more multiband sets and more sets with more than one speaker.

It would be impossible to cover all the new sets in the space available, but the following are a few notes on some of the more interesting models we noticed, intended to show the overall picture rather than be a detailed summary. The new TV sets are described in the October issue of PRACTICAL TELEVISION.

## RADIO RECEIVERS

Where to begin? Perhaps to give an unqualified bouquet to practically every manufacturer for a dazzling display of first-rate styling. The latest transistor radios look good and, generally, are very good. We must admit, however, to being very disappointed at the almost complete lack of main-

operated transistor sets although there were many models intended primarily for home use only.

Full marks, then, to **PYE** for their *Trans-Continental*, Model 1110, an elegant table model incorporating 15 semiconductors and covering long, medium, short and v.h.f./f.m. bands. Output is 3W to a 7 x 5in. speaker. Three internal aerials are fitted and there are sockets for external aerials, tape recorder, gram pickup. The set operates from standard a.c. mains supplies and sells at 32 gns.

Novel feature of the **MURPHY** *Magna* B818 is a pre-tuned position which gives Luxembourg reception at the push of a button. It has 8 semiconductors, a 6 x 4in. speaker, 1W output and sells at 15 gns. Another attractive new one from Murphy is the *Magna* B837, intended as a "home portable", covering l.w., m.w. and v.h.f./f.m. bands, plus the now customary bandspread for pop station coverage. This set retails at 23 gns.


Another example of really good value is the new **McMICHAEL** M126 which has push button selection of l.w., m.w., s.w. and bandspread, and features a dust-proofed speaker and telescopic aerial. Housed in an unbreakable cyclas case it sells at 14½ gns.

From **PHILIPS** comes the new *Le Mans*, which incorporates a "power boost" switch—at maximum the output is 1W (for group listening) and on minimum the output is reduced to 400mW, thus reducing battery drain. It costs 15½ gns. Also new from Philips is the *Cadiz*, an interesting two band portable featuring microtechnique. It has a battery check button. Price 11 gns.

**HMV** have added several to their range, including the Model 2124. This features a "car" button which switches in permeability tuned front end for use in a car, and an illuminated scale for night driving. Price, 18½ gns. An innovation is the 2130, which also incorporates the 2124 features but has v.h.f./f.m. coverage and is housed in fashionable teak cabinet. It incorporates a dual speaker system and retails at 26 gns.

**STELLA** showed their new ST7228T, described as a 3-band, a.m./f.m. sports portable. It features a special biasing circuit to reduce distortion as the battery voltage falls and has automatic frequency control for f.m. Incorporating 16 semiconductors it sells at 25½ gns.

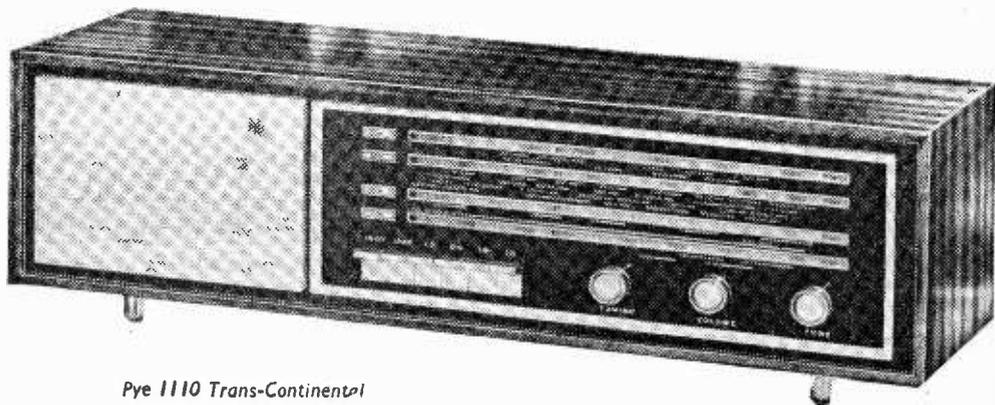**DECCA** introduced several high quality radio



Pye 1110 Trans-Continental

sets, most unusual being the *Diadem*, a 15-semiconductor set with 7 x 3½ in. speaker, covering m.w., l.w. and v.h.f./f.m. bands. It is fitted into a teak or rosewood cabinet of novel design, styled like a music box. It costs 30 gns. The four new portables, TP85, TP86, TP89 and TP90 cover m.w., l.w. and v.h.f./f.m. bands. The TP90 (20 gns.), has 10 semiconductors. The TP85 and TP86 (both 25 gns.) have 15 semiconductors and feature a "mute" control for low volume level listening. The TP89 at 30 gns., incorporates 17 semiconductors and also has short wave coverage. It has mechanical bandspread on *all* bands. It is interesting to note that all Decca receivers now carry a two-years' guarantee for all components, including transistors.

The new GEC models G826 and G828 (both 14½ gns.), cover l.w., m.w., Luxembourg bandspread and s.w. (though this coverage is only over the 31, 41 and 49m bands). There were also two new ones in the ALBA range—the *Trans-Continental* 838, covering m.w., l.w. and s.w. (16–50m), bandspread on *all* bands and telescopic aerial. Price 16 gns. The Alba *Scout* 737 sells at 14 gns., and covers l.w., m.w. and Luxembourg bandspread, housed in a wooden cabinet.

Another one with short wave coverage is the BUSH TR116, which has a two-transistor mixer for efficient s.w. operation. It also covers m.w. and l.w. bands and incorporates pre-tuned Luxembourg. Output 500mW via a 6 x 4 in. speaker. Price, 17 gns. The new TR130 at 15 gns. has a 1W output, 6 x 4 in. speaker, and covers m.w. and l.w.


GRUNDIG introduced two new luxury radio sets. The *Ocean Boy* incorporates 23 semiconductors, two speakers, a tuning meter, a.f.c., fine tuning on s.w., bass and treble tone controls, and covers v.h.f., l.w., m.w. and four s.w. bands (10–185m). The set measures only 15 x 8½ x 4½ in. and weighs 10½ lb. The cost is 87 gns. Even more luxurious is the *Satellit* which operates from batteries or from a.c. mains. It has 28 semiconductors, and covers no less than 13 wavebands (six of them bandspread s.w. bands). It has fine tuning for s.w., a.f.c. on v.h.f., two speakers, a tuning and battery power meter, sockets for almost everything! Price? 119 gns.

Another new one with s.w. coverage is the ULTRA 6120—9 semiconductors, l.w. and m.w. reception also, plus bandspread Luxembourg, retailing at 13½ gns. V.H.F., plus m.w. and l.w. is covered by the 6122 (17 gns.) and the 6128 (at 23 gns.) has a wooden cabinet, v.h.f., m.w., l.w. and Luxembourg bandspread, 15 semiconductors.

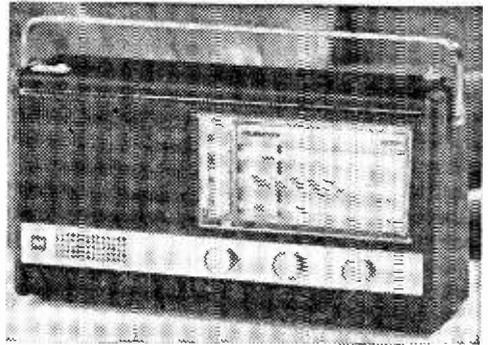
## RECORD PLAYERS AND GRAMS

Everyone seemed to have a good range of attractive record players and radiograms. Here is a quick selection of some of them.


ALBA showed a smart new 5-transistor record player with 3W output via an 8 x 5 in. speaker and separate bass and treble controls. The 328 has a BSR UA15 autochanger and sockets for microphone and tape recorder, the mic' can be used in conjunction with the amplifier as a baby alarm. Price is 24 gns. Also new is a range of *Gold Star*



Murphy Magna B837.

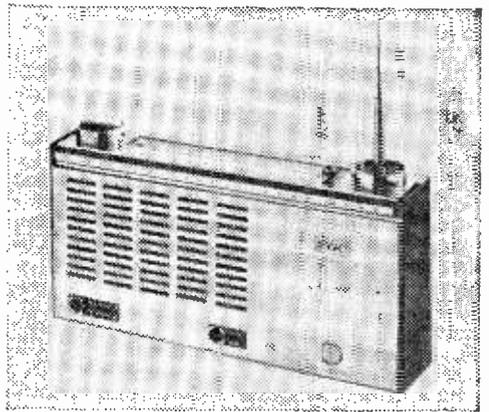

G.E.C. G819.

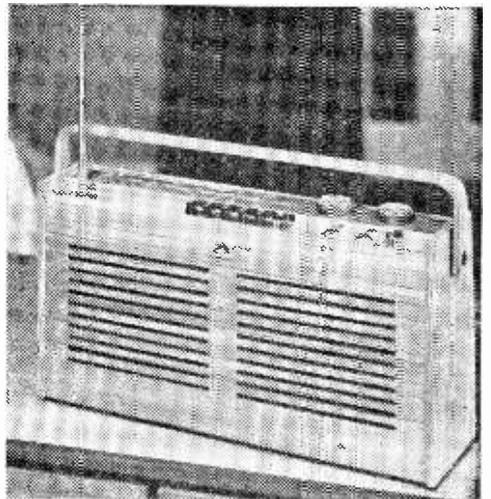

H.M.V. 2130

stereograms, ranging in price from 69½—134 gns. The *Viscount* (134 gns.) and *Viking* (129 gns.) have 8W per channel, four speakers (two in tuned enclosures), l.w., m.w., v.h.f./f.m. and two short wave bands.

At the other end of the (price) scale is the radiogram described by **PHILIPS** as "Britain's Smallest" and which could be carried inside most ladies' handbags. Based on the AG4000 *Disc Jockey* player it incorporates a two-band radio within the space of the original lid, which also houses the 4in. round speaker. It measures 11 x 7½ x 4½in., and sells at 21 gns.

"Upright" model from **RGD** is the RP233 stereo record player, housed in a suitcase-type cabinet with top carrying handle. Transistor amplifiers feed 8 x 5in. speakers at 3W each channel. The changer is a BSR UA15. Price 36 gns. **FALCON** now introduce "solid state" radiograms, ranging from the mono FT65 at 31 gns. to the *Galaxy*, *Concerto* and *Fiesta* stereograms (from 47-62 gns.). **BUSH** add the SRG107 luxury stereogram to their range; the speaker system has six units in an acoustically balanced network with 5W per channel. Twelve semiconductors are incorporated and the radio covers l.w., m.w. and v.h.f. Price is 125 gns., but other Bush stereograms range down to 65 gns.


**GEC** have two new stereograms, G980 and G981. Both have a Garrard changer and 5-band a.m./f.m. radio sections feeding 14W twin channel amplifiers into 10 x 6in. and 4in. speakers. The v.h.f. tuner has a.f.c. Price 110 gns.

**ULTRA** also have an "upright" record player in Model 6010, a completely self-contained 20-semiconductor stereo system. Separate bass and treble, indicator lamp, tape and radio sockets, both speaker units detachable. Price 36 gns. Also new are 6008 (15½ gns.) and 6006 (29 gns.) record players and 6316 (61 gns.) and 6320 (86 gns.) stereograms.

Novel design from **K-B** is the KP033 stereo record player with 3W transistor amplifiers. The wooden cabinet has a rear hinged lid and has a compartment for the extension speaker unit when not in use. Price 34 gns. **SOBELL** showed their



R.G.D. RP233

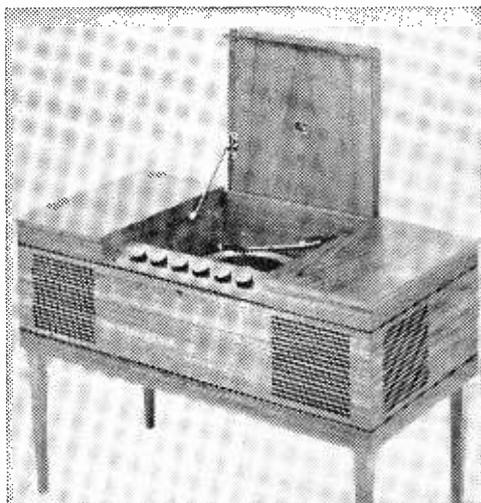

H.M.V. 2018 "Stereomaster"

new S680 stereogram, with all-transistor circuitry and 7W per channel (85 gns.).

Two new record players for **MARCONI-PHONE**. The *Mirabelle* has a BSR *Super Slim* deck and gives 2½W output (15 gns.). The *Major* has separate bass and treble controls and gives 2½W via an 8 x 5in. speaker (19 gns.). Also new were the 4314 a.m./f.m. stereogram (56 gns.), and the Model 4310—a m.w., l.w. and v.h.f. "solid state" stereogram at 83 gns.

**GRUNDIG** came up with two luxury stereograms. The KS680 has ten speakers in an infinite baffle enclosure and incorporates the Grundig HF10 tuner, NF10 stereo amplifier and a transcription autochanger. The tuner has a.f.c. on v.h.f. and the set is fitted with a stereo decoder for possible future stereo radio broadcasts. Space is provided for incorporating a TM45 tape recorder chassis and there is provision for a reverberation unit. The KS740 incorporates a four-band a.m./f.m. radio chassis and feeds 3W per channel to large *Superphon* speakers. Prices for both models not available at time of going to press.

Highlighted by **HMV** was their new 2018 *Stereomaster*, a compact unit (33in. wide) incorporating four soft-suspension speakers, Garrard 300 autochanger, low mass arm-high compliance pickup, 7 watts per channel, treble and bass controls; price 59 gns. Also seen was a new solid state portable record player with Garrard 2000 autochanger, 8 x 5in. speaker (Model 2012, 25 gns.) and a range of radiograms from the popular priced a.m./f.m. stereogram 2320 (56 gns.) to the 22-

—continued on page 588

# Practical Substitutes

by M. L. Michaelis, M.A.

## PART FOUR

### Zener Diodes and Neon Stabiliser Tubes

Zener diodes are now marketed with graded zener voltages ( $V_z$  in Fig. 13) from one or two volts up to 180V or more at current ratings from a fraction of a milliamp up to 1A or more.

The circuit of a zener diode connected as voltage stabiliser (Fig. 14a) is essentially the same as that of the familiar neon tube stabiliser circuit (Fig. 14b). The input voltage is applied to the zener diode through a suitable series resistor such that the anode is negative and the cathode positive wherewith inverse current flows through  $D_i$  and  $V_z$  and  $R_z$  of Fig. 13.

Since  $R_z$  is small for a good zener diode it may be neglected to a first approximation, so that the output voltage across the zener diode is then largely independent of the current through the diode and is equal to  $V_z$ .

Provided that the maximum current rating and the zener voltage of a given zener diode are the same as the current rating and operating voltage of a particular neon tube the zener diode may always be substituted for that neon tube in a voltage stabiliser circuit.

This leads to further advantages, since zener diodes do not manifest a striking voltage higher than their running voltage and there is no lower limit to the stable range of zener currents. Thus zener diodes can be connected in series without any need for auxiliary starter resistors as in the case of series-connected neon tubes and they can operate down to zero zener current.

THE lists of parts for constructional articles are those found satisfactory in the prototypes. Queries which the Editor receives show that many beginners regard these lists as strictly binding down to the last detail.

It is the aim of these articles to help beginners make on-the-spot substitute decisions when their dealers do not have specific components on stock. The information should also help when replacing obsolete components and making use of junkbox parts.

Neon tubes tend to oscillate when starved of current. It is for this reason not always possible to substitute a neon tube of the same operating voltage for a specified zener diode. If the operating current is too low the neon tube may oscillate and if the input voltage is not sufficiently high the neon tube may refuse to strike. Apart from these limitations zener diodes and neon tubes of similar ratings may be interchanged.

Zener diodes at present have somewhat greater differential resistances  $R_z$  (Fig. 13) than neon tubes of the same voltage ratings and the temperature coefficients of zener diodes are somewhat greater.

Neither neon tubes nor zener diodes may be connected in parallel to achieve increased current ratings, since in both cases even the slightest differences of characteristics will lead to grossly unequal current sharing.

### Relays, Meters, Switches

Relays and meters may be shunted in the same manner to achieve higher current values for energising or for full-scale deflection respectively. Thus if a relay or a meter of a certain sensitivity is specified for a piece of equipment it is always possible to use more sensitive components with suitable shunts as substitutes.

If a definite internal resistance is also specified for the relay or meter then any other component of lower resistance may be used if the difference is added as an external series resistor. Both adjustments may be used simultaneously.

A simple example will suffice to make this clear. Suppose a relay of 100mA sensitivity and 150 $\Omega$  resistance is specified for a piece of equipment. A relay of 25mA sensitivity and 120 $\Omega$  resistance is available as a substitute.

The shunt must be such that 75mA of the total 100mA flow through it, leaving the required 25mA for the relay coil. Since 75 is three times 25 the shunt must have one-third as great a resistance as the relay coil, i.e. 40 $\Omega$ . The shunted relay then has an effective resistance of 40 $\Omega$  in parallel with 120 $\Omega$ , which is equal to 30 $\Omega$ .

Thus an external series resistor of 120 $\Omega$  must be added to reach the specified total figure of 150 $\Omega$ . Note that the relay must first be shunted before any required external series resistor is subsequently determined. Exactly the same procedure is used to shunt a meter for a higher current range.

If a relay is fitted with insufficient contacts for a particular purpose any required number of

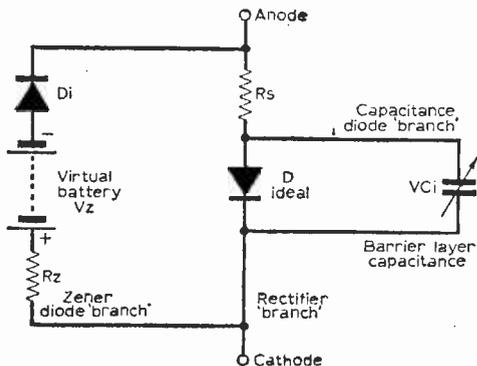


Fig. 13: Equivalent circuit of any semiconductor diode.

similar relays may be energised in series or in parallel or a master relay can energise various slave relays via its own contacts. The latter procedure is useful if a very sensitive relay cannot be obtained with contacts of sufficient voltage or current rating; it is then merely used to energise a larger, more robust relay which in turn has the required rugged contacts.

If a specified multi-contact wafer switch is unobtainable it is possible to use a simpler switch energising suitably disposed multi-contact relays. Such measures are often useful for other reasons too, e.g. to perform switching operations at each stage of a piece of equipment without the need for long signal current leads of intolerable stray capacity and stray couplings to a central manual switch.

**Loudspeakers and Output Transformers**

It is always possible to substitute N smaller loudspeakers for a single larger one. In such cases it is convenient to make N a perfect square, e.g. 4, 9, 16 or more, so that  $\sqrt{N}$  groups or  $\sqrt{N}$  series-connected speakers (Fig. 15) may be wired in parallel. The power rating is then N times that of a single speaker but the matching impedance is quite unchanged.

If N speakers of smaller size are disposed on a large baffle in a well-designed cabinet the quality of reproduction is at least as good as that of a single, much larger speaker. Make sure that all speakers are identical in such a case and that connection polarities are the same for all speakers so that all speech cones move in sympathy. If the speakers are in separate rooms the polarity of connection of each speaker is immaterial.

If an amplifier or receiver design is published with an output transformer for a specified speaker impedance then an output transformer for any other speaker impedance may be substituted provided it matches the specified output valves or the latter are substituted with ones matching the available output transformer.

The only other point to watch when substituting other output transformers is to correct any negative feedback circuit taken from the output transformer secondary to the amplifier input. Such a negative feedback circuit should be examined to determine the attenuation ratio of the signal through the connection from the output

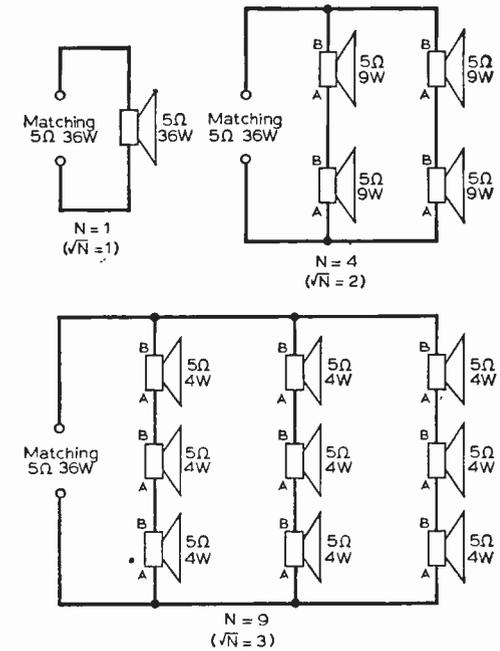


Fig. 15: Loudspeaker groupings

transformer secondary to the amplifier input.

This attenuation factor must be changed by the square root of the factor by which the output impedance (speaker matching impedance) is changed and in the same sense. For example, in Fig. 16 the negative feedback attenuation factor is given by  $R1/R2=50$  for the depicted output impedance of 3-4Ω. If the output transformer is changed to match a 15Ω speaker, i.e. the output impedance is now about four times as great, the negative feedback attenuation must be doubled, i.e. a 10kΩ resistor must be substituted for R1. There is generally no need to be over-critical in this kind of correction.

If the output impedance of an amplifier or receiver is arranged to match a 15Ω speaker three 5Ω speakers may be connected in series to the same output without any need for modifications. The three speakers should be identical, at least electrically, and each must be capable of handling one-third of the total output power of the amplifier.

If the output impedance of the amplifier is 5Ω three mutually identical 15Ω speakers may be connected to it in parallel and each must again be able to handle one-third of the total power output of the amplifier. Any similar matching combinations of identical speakers may

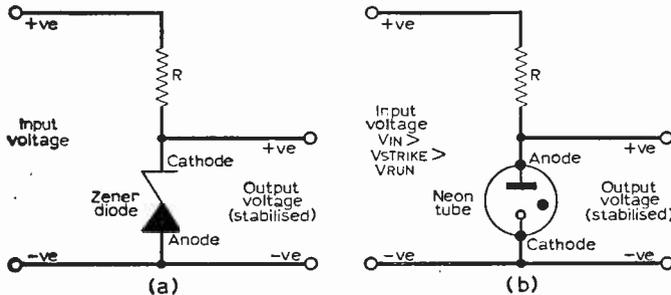


Fig. 14: Simple voltage stabiliser circuits (a) Zener diode stabiliser circuit; (b) Neon tube stabiliser circuit.



# R.S.T. VALVE MAIL ORDER CO.

211a STREATHAM ROAD, MITCHAM, SURREY

Mon-Sat. 9 a.m. - 5.45 p.m.  
 Wednesday 1 p.m. - 5.45 p.m.  
 Open Daily to Callers  
 Tel. MITcham 6202

0A2	5/3	6BR7	10/6	6L1	9/6	10LD11	10/-	30C1	6/6	7475	2/6	EB41	4/6	EF92	2/6	N37	10/-	PY82	5/6	UCL83	8/9
OC3	5/-	6BR8	7/6	6L6G	7/-	10P13	12/6	30C17	12/-	ATP4	1/9	EB91	3/-	EF98	10/-	N78	15/-	PY83	6/-	UF41	7/-
1A7	7/9	6BR7	15/-	6L18	7/6	12A7H	10/6	30F5	9/-	ATP5	7/-	EB23	6/-	EF183	6/6	N108	15/-	PY90	5/9	UF99	6/1
1D5	7/6	6BW6	8/6	6Q7G	5/6	12A7E	4/6	30P11	10/-	ATP7	4/6	EB31	4/6	EP184	6/6	NGT1	3/1	PY80L	6/3	UL41	6/9
1H5	7/6	6BW7	8/6	6Q7T	9/-	12A7F	9/-	30L15	12/-	AU2	20/-	EB30	3/6	EL32	3/6	NGT1	25/-	R2	4/-	UL84	5/6
1LD5	5/-	6C4	1/9	68A7	7/-	12A6U	5/9	30L17	12/6	AU5	6/-	EBF80	5/-	EL33	17/6	OZ4	4/-	R19	7/-	UM80	7/6
1NSGT	8/-	6C5G	4/-	68C7	6/6	12A7U	10/-	30P12	10/-	AZ1	8/9	EBF83	7/8	EL34	9/6	PC86	10/-	RG6/500		U06	13/6
1R5	5/-	6C6	3/9	68G7	4/-	12A7V	4/6	30P19	14/-	AZ31	7/9	EBF89	5/9	EL41	7/3	PC88	9/3	S130	10/-	U09	7/6
1R4	5/-	6C8G	6/-	68H7	2/6	12B4E	6/-	30P11	11/-	CB11	12/6	EBL1	17/6	EL42	7/8	PC87	7/-	SP4	9/-	UY21	7/6
1S5	3/3	6CDD6G	22/6	68J7	5/-	12B2E	4/9	30P15	12/6	CK502	5/-	EBL21	10/6	EL84	4/6	PC84	5/6	SP41	1/8	UY41	4/6
1T4	2/6	6CH6	8/-	68K7GT	4/9	12B7H	6/9	30P14	12/6	CL33	12/6	ECC40	7/-	EL90	6/-	PC89	9/6	SP61	1/8	UY85	4/9
1A4	3/6	6CW4	14/-	68L7GT	4/6	12B8T	7/6	35A5	17/-	CV31	10/6	ECC41	3/8	EL95	6/-	PC8189	10/-	SP61	1/8	UY85	4/9
3Q4	6/6	6D6	2/9	68N7GT	4/6	12P1	19/6	35L6	6/9	DA332	7/6	ECC82	5/-	EM34	3/6	PC82	6/6	T41	9/-	VCR517B	
3Q5	6/6	6E5	5/9	68Q7	6/-	12B8T	2/3	35W4	4/9	DAF91	3/3	ECC83	4/6	EM80	6/-	PC82	6/6	TD4	9/-	VCR517C	
3S4	4/9	6F1	9/-	6U4GT	10/-	12TGT	7/3	35Z3	10/6	DAF96	6/-	ECC84	5/6	EM81	7/-	PC82	6/6	TD4	9/-	VCR517C	
3V4	6/-	6F3G	5/-	6U5G	7/6	12K7GT	3/-	35Z4GT	3/9	DCX90	7/-	ECC85	5/9	EM84	6/-	PC82	6/6	TD4	9/-	VCR517C	
5R40	8/-	6P6G	4/-	6V6G	8/-	13K8GT	8/3	36Z5	5/6	DF38	8/-	ECC88	8/9	EM150	27/6	PC801	9/9	U10	7/6	VCR517C	
5U4G	4/-	6R8G	4/6	6V6G	8/6	12Q7GT	3/-	37	5/-	DF70	5/-	ECC90	6/6	EY31	6/6	PC802	9/9	U14	7/6	VCR517C	
5V40	8/-	6P11	12/6	6V6GT	4/6	12A7	6/6	42	4/6	DF91	2/6	ECC92	6/-	EY86	6/3	PC803	10/6	U19	30/-	VCR517C	
5Y3GT	4/6	6F13	5/-	6X4	3/6	12S6GT	3/6	50B5	6/6	DF92	2/6	ECH21	13/-	EZ35	4/6	PC806	12/-	U23	10/6	VCR517C	
5Z4GT	8/-	6P14	12/6	6X5G	4/9	12M7	2/9	50C5	6/3	DF96	6/-	ECH35	13/-	EZ40	5/6	PC808	12/6	U26	10/6	VCR517C	
6J30L2	10/-	6P23	9/6	6X5GT	7/6	12S47	3/9	50C6	6/3	DF96	6/-	ECH42	8/-	EZ41	6/-	PC82	6/6	U26	10/6	VCR517C	
6A7	15/-	6G6	2/6	7B5	11/-	12S87	2/9	50L6GT	6/-	DK32	7/9	ECH43	8/-	EZ41	6/-	PC82	6/6	U26	10/6	VCR517C	
6A7	6/6	6H6	1/3	7B7	7/-	12S87	5/-	73	4/6	DK91	5/-	ECH83	6/6	EZ81	8/6	PC184	7/7	U301	12/6	VCR517C	
6A7	3/-	6J5M	6/6	7C5	10/-	1487	20/-	78	4/6	DK92	7/9	ECH80	6/6	EZ80	5/6	PC185	7/3	U403	6/6	VCR517C	
6A7	4/6	6J5G	2/6	7C6	6/-	19A2G5	7/6	80	5/-	DK96	6/6	ECL82	6/6	EZ82	9/-	PC186	8/9	U801	18/6	VCR517C	
6A15	3/-	6J5GT	4/3	7D5	8/-	20D1	10/-	813	80/-	DL70	7/-	ECL83	8/-	EZ84	9/9	PEN44	20/-	U801	18/6	VCR517C	
6A15	2/6	6J6	3/-	7H7	5/-	20P2	11/-	85A2	8/6	DL82	4/9	ECL86	8/6	EZ86	22/6	PEN84	20/-	U801	18/6	VCR517C	
6A15	2/6	6J7M	8/6	7R7	12/6	20L1	12/6	150B2	11/6	DL82	3/6	EF9	20/-	KT61	17/6	PEN45	6/-	U801	18/6	VCR517C	
6A15	2/6	6J7G	4/6	787	18/6	20P4	14/-	150C4	12/6	DL94	6/-	EF38	3/-	KT66	12/-	PEN46	2/9	U801	18/6	VCR517C	
6A15	2/6	6J7G	7/-	7Y4	5/-	20P5	12/-	801	5/-	DL95	6/6	EP37A	9/6	KT81	10/-	PL36	9/6	U801	18/6	VCR517C	
6A15	2/6	6K6GT	5/-	8B7	5/-	25A6	6/6	807	7/9	DL96	6/6	EP39	5/6	KT88	20/-	PL81	7/-	U801	18/6	VCR517C	
6A15	2/6	6K7M	5/-	10C1	9/-	25B6GT	4/6	837	5/6	DM70	5/-	EP41	6/6	KTW61	4/3	PL82	5/6	U801	18/6	VCR517C	
6B9G	2/-	6K7G	1/3	10C2	12/-	25Y5	6/-	864	6/6	DM78	7/-	EP50	2/6	KTZ41	8/-	PL83	6/6	U801	18/6	VCR517C	
6B4A	4/6	6K7GT	4/6	10P1	12/6	25Z4	6/6	954	4/-	DY87	7/9	EP80	4/6	ML4	17/6	PL84	6/3	U801	18/6	VCR517C	
6B6E	4/6	6K8M	8/6	10P9	9/9	25Z5	7/-	1625	5/-	EA8CC	14/-	EP85	4/6	ML6	12/6	PL80	5/6	U801	18/6	VCR517C	
6B6H	7/-	6K9G	3/-	10L1	10/9	25Z6	8/6	4022AR	15/-	EA8D	2/-	EP86	6/6	MS84	12/6	PX4	8/6	U801	18/6	VCR517C	
6B7E	6/6	6K8GT	8/3	10F3	12/-	28D7	5/-	5763	10/6	EAR30	5/6	EP89	4/6	MU14	4/6	PY33	8/6	U801	18/6	VCR517C	
6B7E	7/6	6K25	20/-	10F18	9/-	30C15	9/6	7183	1/6	EAF42	7/6	EP91	2/9			PY81	5/6	U801	18/6	VCR517C	

**SPECIAL 24 HOUR SERVICE**

OBsolete TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Postage 6d. per Valve. C.W.O. No C.O.D.

**Special 24 Hour**

Express Mail

Order Service

DAF91, DF91	DK91, DL92, DL94	Set of 4, 19/-
DAF96, DF96	DK96, DL96	Set of 4, 25/-

**BRAND NEW TRANSISTORS**

OC35	9/6	OC72	6/-	OC81D	4/-
OC44	4/6	OC81	4/-	OC82	6/-
OC45	3/6	OC81m/pr	12/6	OC82D	6/-
OC71	4/6				

## More BARGAIN PACKS of RESISTORS and CONDENSERS HOME RADIO (MITCHAM)

**FIRST** The ever popular pack of sixty ½ watt Erie type Resistors (at least thirty different preferred values between 10 ohms and 10 megohms). Value approx. 25/- . Going at 10/6d. post free.

**SECOND** The less popular but equally useful pack containing thirty different Erie type T2 Resistors, 2 watt rating, all preferred values between 22 ohms and 3.3 megohms. Value approx. 20/- . Going at 7/6d. post free.

**THIRD** A new pack consisting of Silver Mica, Moulded Mica and Paper Condensers. Silver Mica values: 15, 25, 65, 71, 80, 160, 200, 240, 330, 470, 1000, 1500, 1670, 4000 pF. (The 470 pF are 750 volts). Twelve out of these fourteen values are included in this pack. Moulded Mica values: 68, 820, 1000 pF and .002, .005, .01µF. (The .002µF are 2250 volts test). Five out of these six values are included in this pack, plus one .02µF paper 750 volts, and one .1µF plastisec T.C.C. 750 volts. Value approx. 15/- . Going at 5/6d. post free.

Anyone ordering all three packs will get them at the special price of 21/-, plus a free Colour Code Calculator, value 1/6d.

**A NEW LINE!** Hammer finish paint in Black, Blue or Silver. Give your work a professional finish. Price for 2½ oz. tin, only 3/6d. plus 2/- post & packing.


Don't forget our famous Components Catalogue. 210 interesting pages, plus 21 page Supplement, listing 5,800 items, 900 of them illustrated. Price 7/6d. plus 1/6d. post & packing. The catalogue contains 5 coupons, each value 1/- when used as directed. Send the Coupon off today with your cheque or P.O. for 9/-.

Please write your name and address in block capitals

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

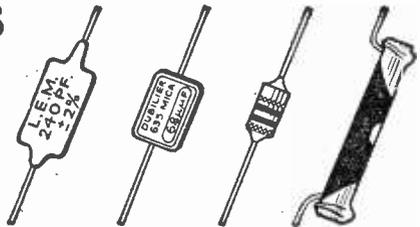HOME RADIO LTD, Dept. PW, 187 LONDON RD., MITCHAM, SURREY



be used as required.

In all such cases, where the correct matching impedance is preserved, it is never necessary to modify any negative feedback circuit connected to the secondary of the existing output transformer.

Whilst reasonably good matching should be aimed at in audio output stages it is not necessary to be over-critical. Thus if an output transformer of  $8k\Omega$  anode matching impedance is specified any other available item with a value between  $7-9k\Omega$  will usually be quite satisfactory. Simple equipment may well tolerate even greater departures, especially if the low-impedance secondary of the output transformer has several tapings for obtaining optimum results by trial and error selection.

### Interchangeable Stages

It would be useful to discuss one final problem—the interchangeability of entire stages from various independent published designs to constitute a new design meeting the particular requirements of the constructor.

There exists a very large scope for such measures and it is the aim of the magazine to provide readers with ideas for "circuit bricks" as much as to provide complete designs for copying as they stand. Many published constructional articles implicitly cater for both these requirements, even if a design happens to be for a piece of equipment complete in itself.

If a reader wishes to use individual stages from one design with ones from another or even with others of his own devising he must be able to discern the input and output positions of each stage. In general an amplifier stage commences with the input coupling capacitor from the

previous stage (which thus belongs to it) and ends with the output load component (e.g. the collector or anode load resistor in the conventional type of RC-coupled amplifier stage).

The coupling capacitor from the output load to the next stage *belongs to the next stage*. This is because it determines the frequency response of the next stage in conjunction with the input load resistor (e.g. a gridleak) of the next stage, which has nothing to do with the function of the stage from which the output is being taken through this coupling capacitor.

If a piece of electronic equipment uses some stage to drive a relay, and the next stage consists of some device actuated by the relay contacts, then any other actuated stage may be substituted, even if of a completely different function.

### Simple Matching Measures

Any sound radio tuner may be connected to any audio amplifier of sufficient quality in relation to the tuner output. Normally only simple matching measures are required which are in many cases completely non-critical. If an amplifier is published with a microphone preamplifier stage this can always be omitted if only a radio or pick-up is to be used as input signal source. Or some quite different preamplifier circuit may be substituted. Auxiliaries such as a magic eye may be added or dispensed with according to individual desires.

- ★ UHF TEST OSCILLATOR—  
full constructional details
- ★ DOES THE AERIAL  
MATCH?
- ★ SPOT WOBBLE
- ★ REPETITIVE FAULTS
- ★ TV SERVICING
- ★ YOUR PROBLEMS SOLVED

*These and many other interesting  
articles appear in the November  
issue of PRACTICAL TELEVISION  
ON SALE OCTOBER 21, price 2/-*

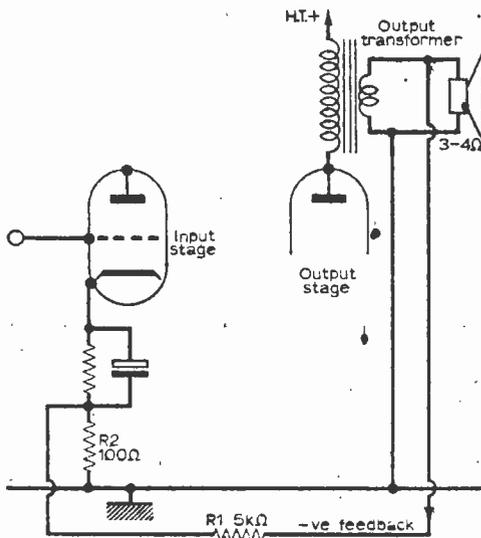


Fig. 16: Correcting a negative-feedback loop when changing an output transformer to a different loudspeaker matching impedance (see text).

## SHOWTIME

—continued from page 582

semiconductor 4-band 2318 (86 gns.).

**DECCA** has three new grams. MRG525 is a mono radiogram at 45 gns. SRG545 is a three-band a.m./f.m. stereogram with 25 semiconductors, 8 x 5in. speakers, 3W per channel (57 gns.). Model SRG565 is similar electrically (66 gns.). These grams carry a year's guarantee on components plus a 5-year guarantee on the Decca auto-changer.

## TAPE RECORDERS

**FIDELITY** introduce their new *Playmatic*, a 3-speed, 7in. recorder in a teak, metal and plastics housing. It has separate bass and treble controls, monitor and external speaker sockets, separate inputs (which can be mixed) for mic and radio/gram, magic eye level indicator, and optional automatic or manual recording level. It is available for 2-track at 28 gns. or 4-track at 31 gns.

Teak styling is also used on the new **PHILIPS** EL3556, a 4-track, 4-speed recorder with separate bass and treble controls (62 gns.). **GRUNDIG** showed their TK27L, designed to fit into the recorder compartment of a Grundig stereogram. It is similar to the TK23L and has optional automatic/manual facilities for recording. Price is 69 gns.

New from **ELIZABETHAN** is the LZ012, 4-track, 3 speed solid state recorder. Maker's spec. claims wow and flutter not greater than 0.15% at 7.5 i/S, frequency response 60—15,000c/s  $\pm 4$ dB at 7.5 i/S, signal-to-noise ratio 40dB. The machine features VU meter, mic' and gram inputs, hi-fi and external LS/headphone outputs, bass and treble controls, 4W output, two speakers. Price is 49 gns. Also new is the LZ711—a stereo recorder with 3W per channel to two 8 x 5in. speakers, VU recording




Philips AG4000

level meters, four inputs, four speaker outputs, 5% distortion at full gain, separate channel selector switches, monitoring facilities, sound on sound and dub-in system. Price 75 gns.

**DENHAM & MORLEY** displayed the new *Standard* SR-F21T, a 6-transistor miniature tape recorder measuring 7 x 6 x 3in., giving 500mW output. It has a 2-track system at 1 1/2 i/S and incorporates a recording level and battery life meter. Price is 15 gns.

**PERDIO** enter the tape recorder field with their T26 (2-track) and T46 (4-track) models. Maximum spool size, 5 1/2in. 3-speed Deck. Model T46 incorporates a parallel track switch. Prices, 29 and 33 gns. **ULTRA** exhibited their new Model 6204, a 2-speed 4-track recorder with two-way tape inching, straight-through amplifier facilities, various auxiliary sockets (34 gns.).

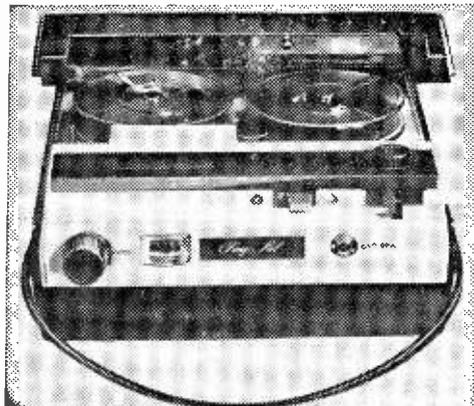**STELLA** showed their smallest-ever tape recorder, weighing only 3 lb., and battery operated. (Five U11's.) About 20 hours' playing time is claimed. This camera-styled recorder uses Philips tape cassettes, Fast Rewind, Playback and (linked with a safety interlock button) Record. There is a combined modulation level meter and battery condition indicator. Price of the ST472 is 26 gns.



Standard SR-F21T.

## A GIFT ON THE RIGHT WAVELENGTH

You'll be sending your Christmas message loud and clear if you give friends who are fellow radio enthusiasts a year's subscription to PRACTICAL WIRELESS.

It's a gift you know they'll appreciate.

Simply send your friends' names and addresses, together with your own and remittance\* to cover each subscription to The Subscription Manager (G-1), Practical Wireless, Tower House, Southampton Street, London, W.C.2. We will despatch first copies to arrive in time for Christmas, and send an attractive Christmas Greetings Card in your name to announce each gift.

\* Rates (including postage) for one year (12 issues): UK and Overseas £1 9s; U.S.A. \$4.25.

# TAPE TAPE TAPE TERMINOLOGY TAPE

## PART FOUR

### PRE-RECORDED

**T**HIS term is used indiscriminately to mean a tape record or a tape being replayed on which a recording has been made (e.g. for test). The tape record made by reputable engineers should conform to international specifications (see Standards).

### PRESSURE PADS

Felts pads mounted on sprung arms, making contact with the back (polished) surface of the tape, pressing the tape into intimate contact with the head facing during recording or replay.

Alternative methods are the *pressure sling*, a strip of material sprung to engage tape and heads in the same way; *tape pins*, which press the tape inward at intermediate points, forming a "wrap-around" contact with the heads.

A method of screening, making use of the pressure pad system, is the provision of a mumetal shield on the pad spring, completely closing off the face of the playback head.

### PRESSURE ROLLER

Free-running roller wheel of rubber or composition which engages the tape and holds it against the revolving capstan spindle to obtain drive. The pressure roller (or pinch wheel) is mounted on a sprung bracket or arm to ensure correct pressure and obviate tape slip (see also Pinch Wheel).

### PRINT THROUGH

When tape is tightly spooled, magnetism from one spot on the tape can affect the field at a corresponding spot of the adjacent layers. This produces spurious effects which at their extreme cause *pre- and post-echo*; i.e. a replica of the original at a short interval before or after the correct signal is replayed. Modern tapes of good quality are not so prone to this effect as some older types.

### PUSH-PULL OSCILLATOR

For good-quality recording it is necessary that the bias waveform be free from distortion. If one side of the wave, for example, has greater amplitude than the other, second harmonic distortion results and the tape becomes partially magnetised.

To reduce second harmonic distortion a push-pull bias oscillator is used in place of the tuned

by H. W. Hellyer

anode or tuned grid Class C oscillator generally employed (see Fig. 15).

### QUARTER TRACK

Loosely used as a synonym for four-track. Correctly used to denote the type of head, i.e. quarter-track head designed for standard ( $\frac{1}{4}$  in.) tapes has two windings and two gaps and records the first and third tracks (top to bottom) of a four-track system. (E.g. a quarter-track head is used to make a four-track recording.) (See also Tracks.)

### REPLAY

Playing back recordings; strictly those made on the same machine. Loosely used to denote playback.

### RESONANCE

Particularly regarding loudspeaker cones: resonance occurs when the natural frequency of a

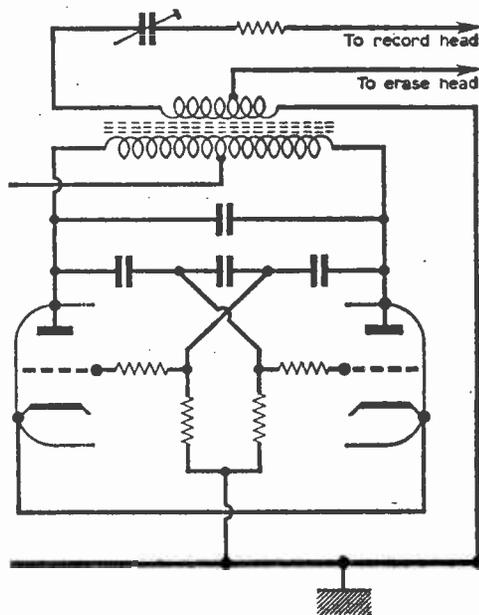


Fig. 15: Push-pull r.f. oscillator to minimise second harmonic distortion.

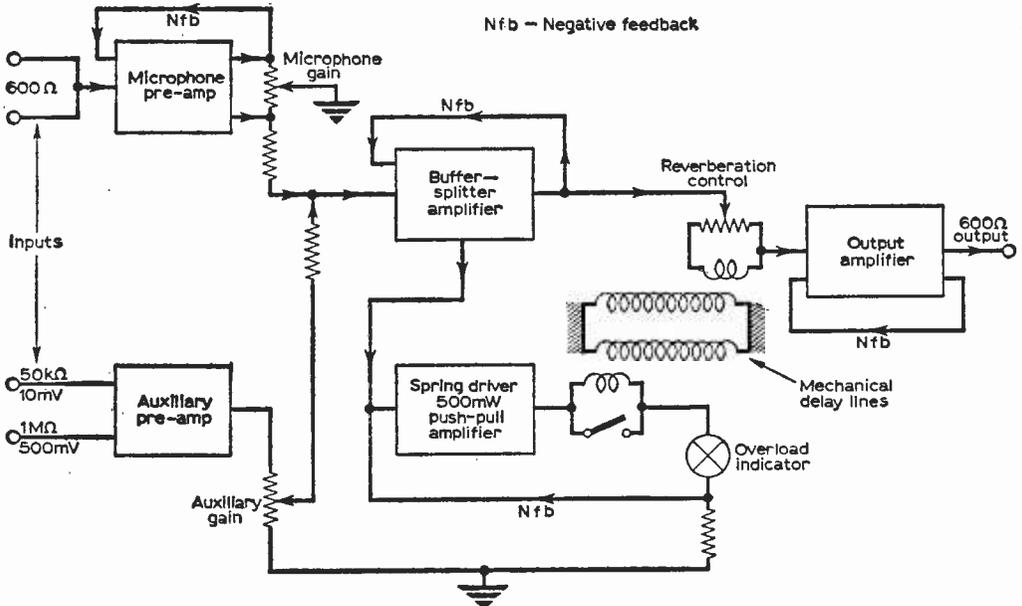


Fig. 16: Schematic diagram of commercial reverberation unit (Grampian 636).

system such as the vibrating cone coincides with the frequency of the stimulus such as the signal source. The output at this frequency is greater. Distortion is thus produced.

Enclosure design concentrates on balancing out the resonances of loudspeaker, "box" and enclosed air and keeping any resonance that may introduce distortion to a frequency below that usefully employed.

A resonant peak below 50c/s is not unusual with bookcase-type enclosures or larger columns with acoustic damping.

#### REMOTE CONTROL

Method of switching the functions of a tape recorder when at a distance from the apparatus. May consist of electrical switching to actuate solenoids or of mechanical devices such as Bowden cables or torque connectors. Widely used with dictating and transcribing machines where the operator has a foot control to select "stop", "start" and "backspace".

Type of remote control used on many machines is a simple on/off switch in the microphone housing.

#### REVERBERATION

To recapture the ambience of the concert hall or other site of recording, various methods of delaying the reproduced sound slightly have been developed. Reverberation units, so called, can consist of simple delay spring devices or complicated tape loop methods with circuitry that also allows variable characteristics.

The schematic diagram of a portable reverberation unit (Grampian 636) is given in Fig. 16. This is a transistorised device using spring delay lines

driven from a split signal derived from the input via a push-pull Class B amplifier and a direct signal from the splitter, making the unit also useful as a mixer.

#### REVERBERATION TIME

A measure of the acoustic properties of a room or hall. The time it takes for a sound to die away to one-millionth of its original strength. Typical figure for a hall may be three to five seconds when empty, less than a second with a full audience.

#### REWIND

The action of winding tape back to the feed spool.

#### REWIND TIME

The time taken to respool a complete reel of tape.

#### SAFETY SWITCH

A method of preventing accidental selection of the recording function by fitting an interlocking switch or by requiring a double switch action to select "record".

#### SENSITIVITY

The voltage of input signal required to produce a fully modulated tape (or other specified output, where stated) Correctly, should be qualified by the distortion figure at this level.

#### SERVO BRAKE

Method of braking where the rotation of the brake drum is used as variable force, aiding or opposing the wrap of the brake according to direction of rotation. Very effective for smooth,

rapid halting of fast-winding function.

**SIGNAL-TO-NOISE RATIO**

The ratio between the output level of a fully modulated recording (1kc/s signal, undistorted) and the inherent noise in the system with no signal played back. Stated in decibels. Should be greater than 45dB unweighted (see also Weighted). Professional standards demand better than 70dB.

**SINGLE TRACK**

Recording full width of the tape. Used for certain professional applications.

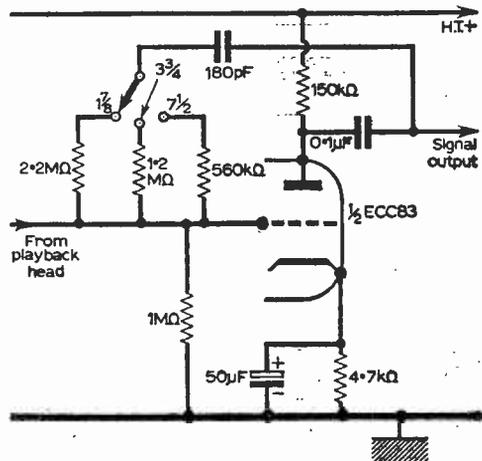


Fig. 18: Playback equalizing circuitry for three speeds.

**SLEEP-LEARNING**

Method of replaying instructional matter via a pillow loudspeaker, using either a time switch or loop-cassette system. With correct preparatory study this method of learning is effective by its impression on the subconscious mind.

**SOUND-ON-SOUND**

Trade term for cross-track or multiplay recording. Output from one track is applied to input of another and mixed with existing signal. The process is more effective and easier to control than super-imposition and can be used to build up quite complicated recordings from simple sources.

**SPEED**

Tape speeds have evolved arbitrarily. After the successful development of the German AEG Magnetophone during the Second World War, which had a tape speed of 76 cms/sec., it was necessary to adapt machines with compatible systems to replay pre-recorded tapes. The nearest whole number was then 30in./sec., which became the original standard.

Improvement in tapes and recording and playback heads, and reduction of gap widths made reduction of speed possible with no loss of quality. The reductions were made by halving speeds successively. Speeds are 15, 7½, 3¾, 1¾ and ¾in. per second. The highest speed is generally used for high-quality work, the lowest mainly for dictation or other speech-only work.

In general the higher the speed the better the high-frequency response. Doubling the speed of a pre-recorded tape raises the tone one octave, halving the speed lowers the tone an octave. The standard speed for domestic use is ¾in./sec. at present.

(To be concluded)

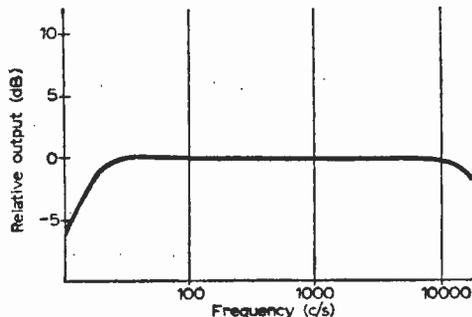
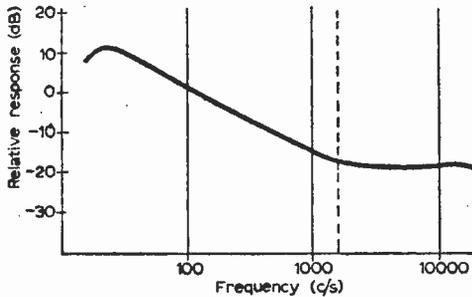
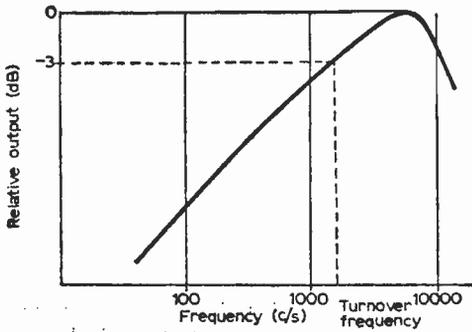


Fig. 17 (a): Playback head curve showing response for signal of constant recording level.

Fig. 17 (b): Playback amplifier response.

Fig. 17 (c) Final response curve.

# BANDSWITCHING

1-67

5-0

Details of a unit that will enable you to dispense with the plug-in method of band changing.

**B**ECAUSE the "Ten-Five" receiver was the first complete double-conversion transistorised communications type model to be described in this magazine it aroused considerable interest. Correspondence shows that the receiver has already been built by a great many PRACTICAL WIRELESS readers and it is pleasing to note that models other than the prototype are giving good results. Full details relating to the "Ten-Five" appeared in the October and November, 1964, issues of the magazine, whilst a further short article suggesting some minor changes to certain sections appeared in the April, 1965, issue.

The "Ten-Five" may be run either from the domestic mains supply of 220-240V a.c. or from a battery; in the latter case this can be the car battery, thereby facilitating /P or /M working. Bearing this last point in mind it is noted that some readers have enquired whether a switched "front end" is feasible, since in the original scheme a plug-in band changing method was adopted.

In the original "Ten-Five" a total of nine transformers (coils)—three per band—have to be moved around to obtain complete gap-free coverage of the frequency range 1.67-31.5Mc/s

and, whilst the system used is a simple one to set up and operate, losses via the pins can degrade performance. The loose coils are also apt to become mislaid or their core settings may become disranged.

Trimmer adjustments are also likely to become a compromise, although this is overcome somewhat by the inclusion of panel-fitted TC4. Although some improvement would result from adopting a "unit-built", three-coil, plug-in assembly for optimum results a switched front end is to be preferred.

## Physical Considerations

Assembling a suitable switched front end, however, is tricky, since to cover the range of frequencies quoted a total of nine individual transformers must be used, whilst the switch itself must have not less than nine "pole" tags and 27 "way" tags. These "poles" and "ways" should be available via a three-way rotary switch carrying three wafers each having identical three-pole, three-way characteristics.

Incorporating the switched circuitry into a

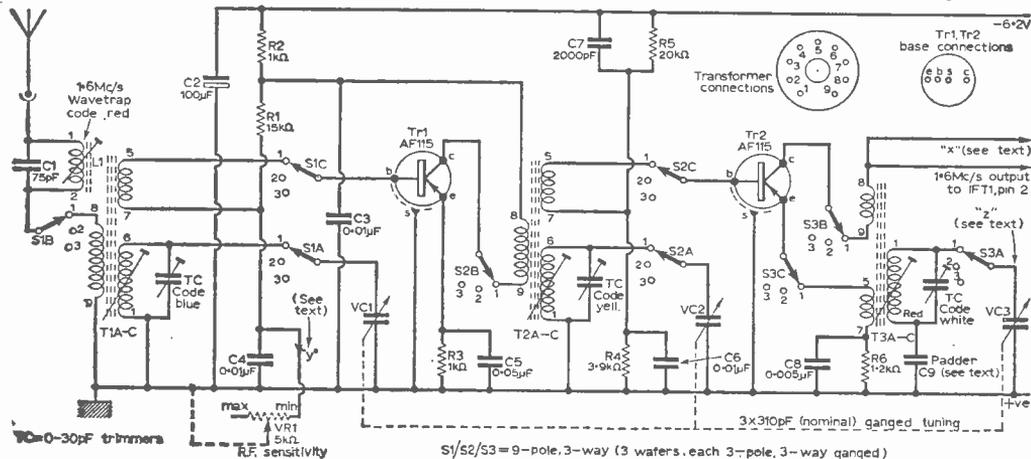


Fig. 1. Complete theoretical circuit diagram of the bandswitched front end. In the interests of clarity only one transformer for each range is shown.

# the 'TEN-FIVE'

A.S. CARPENTER, G3TYJ

"Ten-Five" already built also requires consideration, for it is inadvisable to disturb the receiver wiring unduly. At first sight it would seem a simple matter to remove the existing front end wiring, etc., and mount the nine coils in the vacated space, but in practice this is not easily accomplished.

An alternative is to construct a separate unit as a sub-assembly carrying the minimum number of outlets and although this scheme is also open to criticism it does seem to be the best of the two. Such a unit can be wired separately and on completion be fitted to the receiver with the minimum of trouble.

It should be noted, however, that considerable effort is required to construct a suitable unit, for the work needs concentration and thus tends to become tedious. Patience, a miniature bit soldering iron, and a pair of strong tweezers are essentials. Each joint, too, must first be made mechanically firm before solder is applied.

## Circuitry

The circuit of the complete switched front end is shown in Fig. 1 and closely follows that portrayed earlier. Component designations are also kept identical. Only one transformer is shown for each range in the interests of clarity but the locations of the necessary switching positions are clearly indicated.

The slightly amended (external) r.f. sensitivity

control wiring necessitates but one lead-out and this is taken from point "y"; the original panel fitted "oscillator trimmer" control, if used, may finally be connected at point "z".

Output at 1.6Mc/s i.f. appears at pins 8, T3A-C, and is then fed to pin 2 of the original i.f. transformer, IFT1 (see Fig. 2a, P.W., October, 1964), whilst the original damping diode, D1, is also connected there via R14 (see Fig. 2b as above).

In passing it may be noted that this particular switched unit may be used as a front end for other receiving apparatus capable of accepting 1.6Mc/s signals provided VR1 (5kΩ) is incorporated; in such cases the connections marked "x" and "z" can be ignored. For essential details regarding the frequency ranges available refer to Table I.

## Construction

The unit is most conveniently built on a small L-shaped piece of 16s.w.g. aluminium suitably drilled and cut to size. It is not recommended that a thinner gauge be used since a high degree of rigidity is desirable in the interests of stability.

In Fig. 3a the switch and its associated transformers are shown mounted. At first sight it would seem impossible to reach contacts of switch wafers "b" and "c" (see Fig. 3b) with the soldering iron, but the transformer stems are less thick than the pin ends and so no such difficulty arises. Tagstrips "A" and "B" are not wired until the remainder of the unit is completed, nor are any trimmers mounted.

An attempt has been made to secure minimum transformer interaction and although some degree of absorption might be present the compact wiring enables the majority of the leads to be no longer

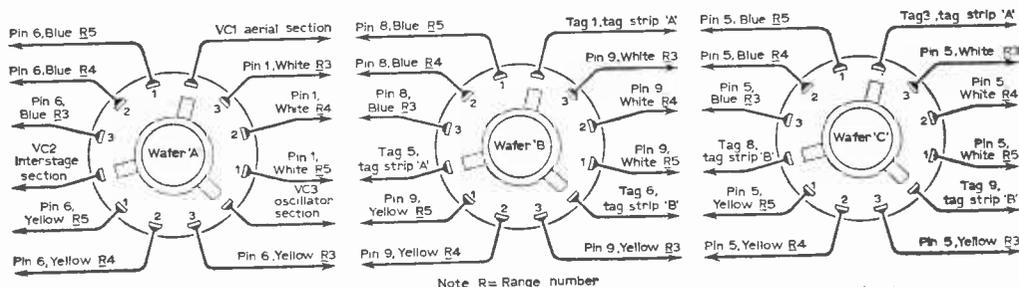


Fig. 2: (a) Connections made to wafer "a". (b) Wafer "b" connections, (c) Connections required at wafer "c".

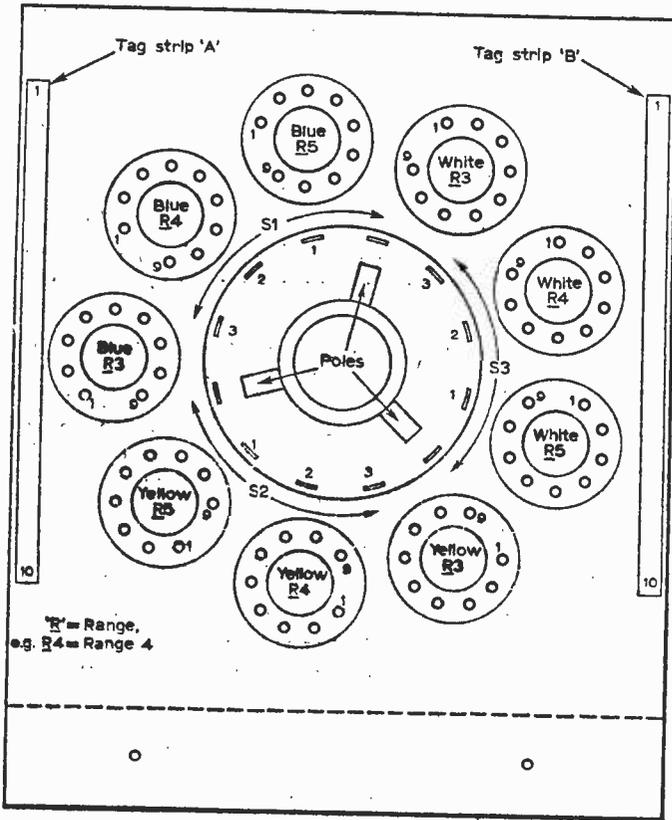


Fig. 3: The way in which the transformers and switch should be orientated.

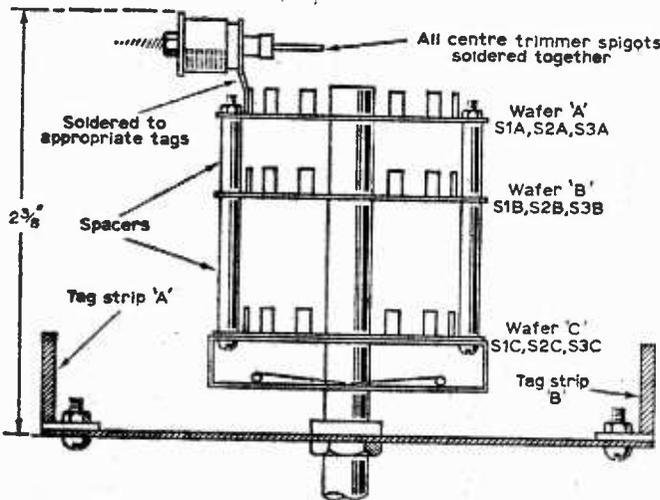


Fig. 4: Switch wafer arrangement and trimmer location.

than  $\frac{1}{16}$  in. This point is further favoured by the transformer orientation.

Commence wiring with wafer "c", proceed to wafer "b" and finish on wafer "a". Owing to confusion which may arise, constructors are strongly advised to wire in this order and for each wafer use wire with a different shade of insulation, since this will considerably assist final checking. Do not overheat the transformer pins whilst soldering but should the polystyrene soften due to this cause leave the particular pin for a few minutes to enable the material to reset.

When most of the wiring associated with the various switch wafers has been completed the tagstrips may be mounted and then wired to agree with Fig 5. Most of the associated items are already available from the existing "Ten-Five".

To find the required values of the padder capacitors (C9) and the pins to which they should be connected refer to Table 1. For the external connections that will be required use flying leads with distinctive insulations; these leads may be shortened later but the lead carrying the 1.6Mc/s i.f. signal should be screened or spurious signals may be received later.

**Mounting of Trimmers**

Trimmers are afterwards mounted as is indicated in Fig. 6, the centre spigots being brought together sufficiently close to enable a copper wire ring to be soldered to them. The other trimmer connections are soldered to the appropriate tags of wafer "a" on the lines shown in Fig. 4.

The finalised unit should feel physically rigid and before it is bolted to the receiver a thorough check should be made.

First remove all the original front end material except the wavetrap and first i.f. transformer, together with the three valveholders which previously held the transformers, and if necessary reinforce the base board. Bolt the switched unit in so that its control shaft will project through the cabinet side—looking at the receiver from the front.

Check that the moving vanes

of VC1 cannot foul the trimmers, then solder the eight flying leads in position, shortening them as required. The eight leads are: (1) +ve line, (2) negative line at point "C" (original Fig. 2a), (3) "Y" to VR1, (4) to pin 2 of IFT1 (screened), (5) to pin 2 of wavetrap, (6) to VC1, (7) to VC2, (8) to VC3.

Remove any trimmers associated with VC1-3 and if the original trimmer, TC4 is to be used connect this to VC3.

**Alignment**

This is carried out on the basis of core adjustments at the low frequency end of the bands, followed by trimmer adjustments at the high frequency ends. Commence with the lowest switched range, i.e. range 3, and if TC4 is being used set this to about 25% capacity.

Use of a signal generator is necessary and, although results can be achieved without one, these are likely to be sub-optimum. When using a generator always attenuate its output sufficiently to give but the smallest detectable indication on the "S" meter or other indicator in use. Core locking is achieved by means of a 6BA nut fitted to each transformer stem.

(1) Connect the generator via a standard dummy load (or 400Ω resistor) to the aerial socket and, using Table II as a guide, inject a 1.67Mc/s signal with the tuning capacitor vanes fully enmeshed.

(2) Adjust the core of White R3 to resolve the signal (see note on "Second Channel" later).

(3) Set generator to 5.3Mc/s and fully disengage tuning capacitor vanes. Set White R3 trimmer for maximum output.

(4) Repeat (2) and (3) above.

(5) Set generator to low frequency (LF) tracking point (see Table II) and tune in signal using VC1-2-3. Adjust Blue R3 and Yellow R3 cores for maximum output. (See note on "pulling" later).

(Continued on page 624)

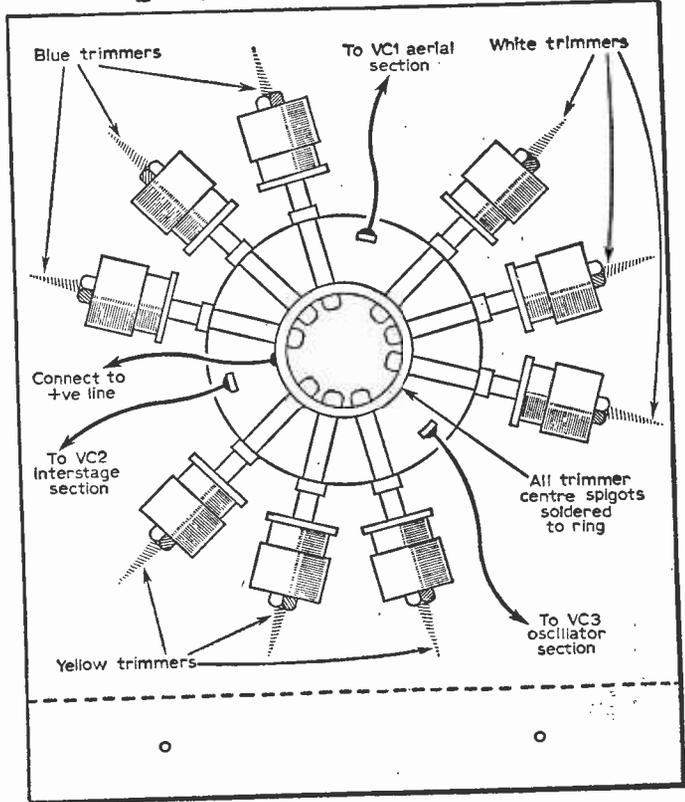
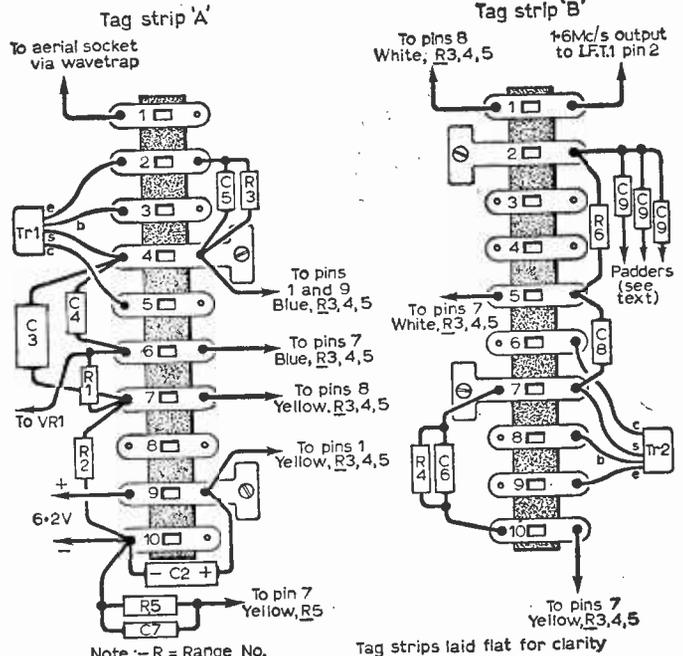


Fig. 5 (top): Type of tagstrip required and wiring details. Fig. 6: The trimmers in position. Note the central ring made from copper wire.

## C.W. Standards

I WOULD like to reply to F. Taylor's letter in the August issue as I am such a person to which he refers, i.e. an old ex-Service operator keen to do a spot of operating.

Over the years I have followed the arguments in PRACTICAL WIRELESS for and against the R.A.E. and have kept an open mind.

Last year I took a six-month course for the R.A.E. at the local Technical College and sat the examination last May. I am pleased to say I passed this and in addition have since passed the G.P.O. Morse Test.

Perhaps this proves that if you are keen enough, you are not too old at 40 to pass the R.A.E. and do a spot of operating.

Conway Parker,

Bath,  
Somerset.

## Tape Terminology

I WOULD like to congratulate Mr. H. W. Hellyer on his series of articles, Tape Terminology. So often one sees references in books to Modulation, Noise Levels, Monitoring etc., and to the uninitiated, like me, these terms conjure up all sorts of weird ideas.

Mr. Hellyer's articles do help a great deal by explaining exactly what things are and what they do. I think it would be a good idea to publish them as a separate booklet which would really help beginners like myself understand some of those many "Mysteries" of radio.

A. Read,

Walthamstow,  
London, E.17.

## Correspondents

I WOULD like to correspond with anyone who is interested in making crystal sets.

Nanubhai Patel.

33 Princeville St.,  
Bradford 7,  
Yorkshire.


I AM interested in radio and electronics and would like to correspond with other P.W. readers of any age and country.

Omar bin Abdullah.

203 Arab Street,  
Singapore 7.

# NEWS AND.

## THE RADIO SHOW SPECIAL

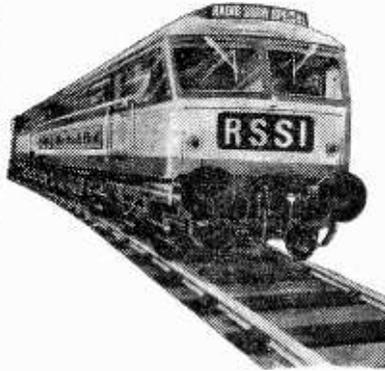

This year's Radio Show is over 200 yards long, runs on wheels and comes direct to the public in their own towns and cities.

The Radio Show Special, a thirteen coach train, is touring Britain for three weeks and spending two days each at Southampton, Cardiff, Bristol, Birmingham, Manchester, Glasgow, Newcastle, Nottingham and Norwich.

In one coach, a complete local broadcasting station is showing just how local radio works and the form it will take when it comes to this country. Another coach will

supply pictures on both 405 and 625-lines to television sets all over the train. A third coach will show working demonstrations of radio-telephones and other communications equipment. The remaining coaches will display the full range of Pye/Ekco domestic products.

## SEMICONDUCTOR DIODE CIRCUITS

Mullard Educational Service announce a new 27-frame filmstrip entitled "Semiconductor Diode Circuits". Intended for use in universities, technical colleges, training establishments and industry, this film forms part of a series covering advanced electronic circuitry.

"Semiconductor Diode Circuits" describes the theory and construction of semiconductor diodes and their use in power supply circuits, computers, and radio and television.

Copies of the film cost 25s. per strip including fully comprehensive teaching notes and may be ordered from Unicorn Head Visual Aids Ltd., 42 Westminster Palace Gardens, Artillery Row, London, S.W.1.

## LARGEST COMPUTER FOR BRITISH INSURANCE

English Electric-Leo-Marconi announces that the largest computer system ordered by a British insurance company has been installed at the Sun Life Assurance Society's head office in London.

The computer, a KDF 9, will be used to maintain the records of more than half a million insurance policies. This large file will be interrogated and brought up to date each day by the computer in under two and a half hours.

The machine was built and tested at English Electric-Leo-Marconi's factory at Kidsgrove, near Stoke-on-Trent. It brings the total value of computers delivered by the company to insurance offices to nearly £2 million.

Sun Life's KDF 9 is a multi-programming machine (able to carry out more than one job at a time). It has nine magnetic tape deck units each capable of transferring 80,000 characters per second, a magnetic drum store, two 1,000 lines per minute on-line printers and paper tape and punched card equipment.


## CATALOGUE RECEIVED

Lind-Air (Supplies) Ltd., 53 Tottenham Court Road, have produced a new catalogue of transistors, motors and servo equipment and separate lists are included on pen recorders, transducers and accelerometers, industrial plugs and panel meters.

# .. COMMENT

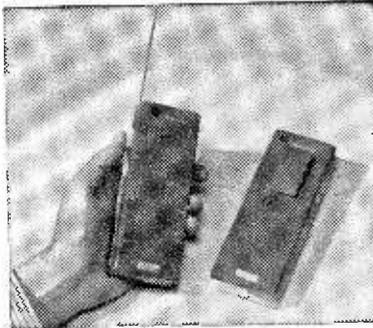
## PYE MINIATURE RADIOTELEPHONE EQUIPMENT

Pye Telecommunications of Cambridge announce their new u.h.f. radiotelephone, the Pye Pocketfone. Coming in two separate units, the receiver unit fits into the breast pocket, has its own power supply and loudspeaker and contains a built-in concealed aerial. The transmitter, a similar small unit, is normally carried in the side pocket. To make a call, the transmitter is held in front of the mouth and when the transmit button is pressed, a small rod aerial, about 6in. long, springs out. Very high quality two-way communication may then take place over ranges up to a distance of two to five miles depending on the kind of installation provided.



An outstanding feature of the Pocketfone is the long battery life that has been achieved. A new and patented battery economy circuit enables a battery life of several times that of a more conventional receiver to be realised. The tiny receiver battery, which measures only 1.8 x 1 x 0.55in. and weighs only 1.6oz has been made to give continuous receiver operation of thirty hours. Either chargeable or replaceable batteries may be used.

## LARGS NEW COMPARATOR

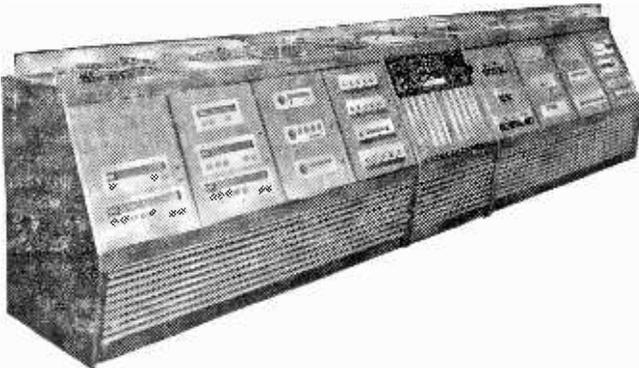

Largs of Holborn have installed a new Comparator which enables customers to hear and compare different types of hi-fi equipment. It was designed by Arthur Burrows, the company's chief engineer, and constructed by the company's engineers and cabinet workshop team.

Expressly intended for stereo equipment, the Comparator permits a virtually uncountable number of permutations of equipment under demonstration. There are facilities for combining 16 pickup arms, 16 tuners, 16 amplifiers, 12 tape recorders and 16 auxiliary inputs, playing through 50 loudspeakers. 4,750 yards of wire are used and the whole unit is built on 20 different chassis.

BECAUSE OF THE LARGE NUMBER OF OUTSTANDING "SELL OR LOAN" REQUESTS NOW HELD BY US, WE REGRET THAT FOR THE NEXT FEW MONTHS WE WILL NOT BE ABLE TO ACCEPT ANY LETTERS FOR THIS COLUMN.

Sir, I would be grateful if any reader could sell or loan me . . .

... service sheet, circuit diagram for Kolster Brandes Model No. BR30T table radio.—G. Missen, 8 Russell Drive, Amptill, Beds.

... any information on Clavinolines Concert Model.—D. E. Jones, 31 Heath Road, Timperley, Altrincham, Cheshire.

... circuit diagrams and details of headset and battery connections of the type 38 transceiver.—P. C. Bateman, 42 Buckingham Road, Port Elizabeth, South Africa.

... any information at all about the "McMichael moving coil mains Receiver" especially the coil pack. Set is about 30 years old, 3 valve, regenerative. V1=12A2 V2=3 x 23 V3=?—N. D. Benyon, "Westleigh", 3 Elmfield Road, Audenshaw, Lancashire.

... information of any kind on v.h.f. receiver type 62H, Ref. No. AP61357, Ser. No. 2216, Modification No. 7085 A/10.—K. J. Martin, Belmont Hall, Dundee, Angus.

... any information on indicator type 62 Ref. No. 10Q/13000—A.M., Ser. No. GO61219.—Tony H. Yassa, Abbassin Street No. 8, Heliopolis, Cairo, United Arab Republic.

... details of conversion of V.H.F. RXR.1132 from 100-125mc/s to 65-86mc/s.—W. Stockburn, 40 Netherburn Road, Sunderland, Co. Durham.

... information on assembly of National HRO tuning dial.—N. H. Punford, 93 Sunny Gardens Road, Hendon, London, N.W.4.

... circuit diagram and details of P.C.R. communications receiver.—T. Wright, The Bungalow, Glenbana, Ballyaughlis, Lisburn, Co. Down, N. Ireland.

... the plans for a battery tremolo unit.—I. H. Wesley, 16 Emperors Gate, London, S.W.1.

... details of the Synchrodyne Receiver, produced in brochure form about 1946.—L. A. Wilkinson, Radio Designer, Field Aircraft Services Ltd., Wymeswold Aerodrome, Burton-on-the-Wolds, Nr. Loughborough, Leicestershire.

... the circuit of the transmitter type 5AH, No. 162, made in 1949.—S. Powell, 7 Commercial Road, Hereford.

... any information on comparison of performance between HE-30 Lafayette and Eddystone 840C.—F. W. Brown, 79 Glebe Road, Stoneferry, Hull.

... any data on the P.104 (R1392) Receiver Model No. 62H, Navy version 1.F.972mc/s. I would particularly like to know the aerial input impedance and the phone output impedance.—N. A. Courroy, 7 Nab Lane, Shipley, Yorkshire.

... any information or circuit of Globe King I valve plus add-on amplifier.—S. L. Holding, Roselea, Tideford, Saltash, Cornwall.

... BC312M manual circuit modifications or correspondence on the receiver.—R. Wilson, 11 Sulgrave Close, Liverpool 16, Lancashire.

... circuit of the "Regency" transistor radio.—J. Owens, 26 Ardd Fawr, Dolgelly, North Wales.

... a circuit diagram and information on Govt. Surplus Power Unit Type 633 Ref. No. 10KB/6205 using valve nos. CV45 and CV572.—P. I. C. Payne, 33 Strawberry Vale, Twickenham, Middlesex.

# MW DX

W. N. STEVENS  
Editor, Practical Wireless

## ★ SOME NOTES FOR BEGINNERS

**M**ANY of us become involved in the business of radio in the oddest ways. My introduction was accidentally listening to KDA in Pittsburgh on the medium waves. It was one in the morning and the set was the family radio.

This phenomena fired my schoolboy enthusiasm. The die was cast. Like an addict needing a "fix", I wanted American stations and since late night listening was restricted, the family was persuaded to buy a short wave converter and I was thus exposed to the infinite fascination of DX.

Since then, there have been many exciting moments—receiving the first QSL cards . . . obtaining an amateur licence . . . working DX myself. There have been moments of triumph—being first to report reception of low power broadcast stations . . . acquiring coveted DX certificates . . . making two-way with America using a 1-valve receiver and 1-valve transmitter . . . working exotic DX stations.

Yet, even so, some of the best moments have been in pulling through a difficult medium wave DX station. For despite the perennial pleasures of the short waves, there is a special something about m.w. DX which cannot be explained, as might be imagined in the writer's case, as nostalgia.

Most of the older hands at the game are well familiarised with the world of m.w. DX, but the newcomers (and potential newcomers) may find some basic notes of interest. And as the "season" is now with us, this is the time to get organised.

### When to Listen

By virtue of the range of frequencies involved, optimum results are obtained with paths of maximum darkness. Thus, the winter months are the best for all-round reception; the atmospheric noise level is lower, too, during the colder months. You can still hear some DX through the summer but this means very late night (or more precisely, early morning!) sessions. Conditions will also vary from season to season and, quite naturally, the best years for m.w. DX are those with low sunspot activity. We are in such a trough now, and conditions can be expected to be quite good for at least several years.

In many ways, m.w. DX listening is much less predictable than s.w. listening. Conditions can be really good for several days, then really bad. Some days North Americans will be good and South Americans poor. Some years may be good for North America, others good for South America. Skip distance effects are very pronounced; peak times for different areas may be short lived. There are numerous permutations of possible conditions. Life is exciting, if at times frustrating!

Here is a, necessarily, brief outline of what to expect from different parts of the world.

### North America

**USA:** The East Coast stations of the USA are there, to some extent, all through the year. In the summer, the openings may be in the period around 0430. As the hours of nightly darkness increase, so will the openings start early, and last longer. In the actual winter months, some of the stations will be heard from midnight or earlier but QRM from European stations may be troublesome. They will "stay" until dawn or later. Last year there was one fantastic opening when many of the East Coasters were still coming through at 1000 in the morning—though this was unprecedented.

There are a few regular stations from the central States, but the best chances are around 0300. The West Coast represents really first rate DX and the openings are quite rare; when they do occur they are usually around dawn (0300—0600).

There are three major networks—NBC, ABC, CBS, but many stations are independently owned, though they may carry network programmes at times. Most US stations have a callsign beginning W, some have K. The callsign is invariably used as identification. Many of the East Coast stations are received very regularly during the best months and often reach quite surprising strengths.

**Canada:** Similar remarks apply. They tend, however, to break through much earlier and a few of them are often heard as early as 2100 hours in the winter, and reception as early as 1900 is not unknown. There is a national State-owned network, rather BBC-ish—the Canadian Broadcasting Corporation. There are also numerous privately owned and operated stations. Most CBC stations have a three-letter callsign (such as CBA, CBF, etc), all the others have four-letter callsigns (CJCX, etc). The callsigns are invariably used for identification.

Important note for newcomers: Many of the Canadian stations broadcast *only* in French!

Normally, Canadians will be heard when the U.S.A. is good but this is not an invariable rule. Many occasions will occur when the USA is poor and Canada good—and vice versa.

**Latin America:** Harder to identify, but experienced short wave listeners should not have too much trouble. Call signs are usually used, together with other means of identification. Best times for the Latin Americans is usually an hour or two after the North Americans are well established. This again depends on conditions and last season many of them were heard at reasonable strength before midnight. Central American, how-

**MAINS POWER PACK**

Designed to operate transistor sets and amplifiers. Adjustable output 6v-9 to 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1-PP3-PP4-PP6-PP7-PP9 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor 5000 and 500 mfd condensers, zener diode and instructions. Real snip at only 14/6 plus 3/- post.

**List of Bargains**

Transistor ferrite rod aerial with medium and long wave coils with circuit, 7/6.  
Oscillator Coil and set of 3 I.F. transformers for transistor set with circuit, 12/6. Tuning Midget 3in. P.M. Loudspeaker 3 ohm 12/6. 80 ohm 12/6.  
Midget 208 pF + 176 pF two-gang Tuning Condenser with trimmers for transistor set. Price 9/-.  
Push-Pull Transformer. Sub-minature 8/6. .005 mfd. Single Tuning Condenser. Solid dielectric 3in. spindle for transistor or Crystal set, with spindle tapped 6 BA. 2/6.  
46 Sets (Receiver/Transmitter pack set). Unused sets complete except for crystals. Packed with parts easily rebuildable into other rear 19/6 plus 6/6 carr. and ins.

**Waterproof Heater Wire**  
16 yds. length 70 watts, self regulating temperature control, 10/- post free.

Mains Transformer. 250-0-250 at 80 mA. 6.3 volts, 5a (normal mains input), 12/6 each. Carriage 2/6.  
Output Transformer. Standard pentode matching type, 3/8 each. 38/- per doz. Slide Switch. Sub-miniature but dotted, 2/- each. 18/- per doz.  
Other gear, 19/6 each. Post 5/-.

Best of Charger Kit. Comprises 4 amp. transformer, 5 amp. rectifier, metal case and meter to charge 6 or 12 volt batteries up to 5 amps. With variable charge rate, 39/6 each. Post and insurance.  
Battery Charger Rectifier—selenium 12.15 v. 5 amp. 9/6.  
Metal Chassis—punched for Mullard 510 Amplifier. complete with inner screening sections and stove enamelled, 5/6 set, p. & p. 2/9.  
Filament Transformer, 6.3 v. 1 1/2 amps., 4/6.  
Neon Lamp—midgit wire ended. Ideal mains tester, etc. 1/8. Ex. Govt. 1/3.  
Phillips Trimmers—0.30pF 1/- ea., 9/- doz.  
Tar Panels. Ideal for constructors, experimental circuits, etc. 3 of each of 12 different types, 5/-.

Slydlok Panel Mounting Fuses with carrier, 6 amp., 2/- each, 15 amp., 2/6 each.  
Potentiometer. Sealed type by Morganite, among the best ever made. Standard 1/2 spindle lin. long, 8/- dozen. 2 mek. 1/2 mek. 1 mek. 100K. 3/6.

MU Metal Screen for American 5 CFI etc. 10/6 pair for VCR97 and other 6in. tubes, 7/- complete. Ditto for 2.3in. tube, 5/6 complete.  
Electric Lock. 24v. coil but rewindable to other voltages, 4/6; 48/- dozen.  
Low Resistance Headphones. Ideal crystal sets, etc. 7/6, plus 2/6.

Unbreakable Mains Lead. Type of lead fitted to electric fuses, makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream P.V.C. covered. Normally costs 2/- per yard. Three fit, leads for 2/-.

24 Volt Motor with blower attached 12/6 plus 2/9.  
115 Volt American magislops (selsyns) 50/- each transmitter or receiver, post 2/9. Pair post free.

Music Practice outfit. Comprises valve oscillator with controls in wooden box, battery operated 12/6 plus 2/9.  
Mains from Car Battery. Rotary generators 12v. input, 240v. output, 110 mA, 40/-; 300 mA, 45. Plus 5/- post.

H.R.O. Power Pack. Suitable 240 or 115 volt mains give 250v. H.T. and 6.3v. l.t. new and unused but less rectifier valve. 19/6 plus 6/6 carr. and ins.

A.C./D.C. Ammeter. 2 1/2in. flush mounting, 0.9 amps. but external shunt easily removed offered at silly price, 8/6. 25 doz.  
D.L.R.S. Headphones. 8/6 pair. Post 2/-.  
Sound Powered Inserta. Make excellent microphones or speakers. 5/6 each. 28 doz.

Where postage is not definitely stated add 2/- all orders under £2 (also add 2/6 if you would like our new 100 page list of bargains).

See in the Dark

**INFRA-RED BINOCULARS**

These If fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lens for TV camera—light cell etc. (details supplied). The binocular form part of the army night driving (Tabby) equipment. They are unused and believed to be in good working order, but sold without a guarantee. Price £2.17.6 plus 10/- carriage and insurance. Handbook 2/6.



**750 mW TRANSISTOR AMPLIFIER**



4 transistors including two in push-pull input for crystal or magnetic microphone pickup—fed back loops—sensitivity 5 m/v.

**Price 19/6**

Post and insurance 2/6.  
Speakers 3"-12/6, 5"-18/6  
6" x 4" 14/6.

**OUR BARGAIN OF THE YEAR**



A complete kit of parts to build 6 transistor 2 we ve superhet receiver at only 39/6. Post and Ins. 3/6.

**"CORONET" Mk. IV**

It fully covers the medium waveband and that part of the long waveband to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and 2 1/2in. P.M. speaker. Over all size approximately 4 1/2 x 2 1/2 x 1 1/2in. Supplied complete with carrying case and instructions.


**THIS MONTH'S SNIP**



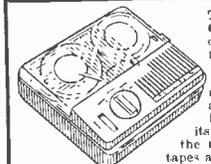**Garrard Auto-Record Player Model A.T.5**

This is undoubtedly the finest AT changer made in fact its large heavy, non-magnetic, die cast turntable and bias compensated constant pressure stylus together with its laboratory series motor with balanced rotor make it almost a transcription unit. Other special AT.5 features are:— Will take 8 records which may be mixed size—stylus pressure adjustable—may be stopped whilst playing a record without rejecting same record—fitted with latest pick-up for playing stereo or mono records.

OFFERED AT THE AMAZING PRICE OF £6.15.0 plus 6/6 carriage and insurance.



**THE "MINIV" TAPE RECORDER.**

Of the many tape recorders to offer, at £12 or less we have at last found one we can recommend. Equally suitable for music or speech this instrument uses two motors, is completely portable and is beautifully styled and looks like a good tape recorder. Among its many good features is a switch on the microphone to stop and start the tapes a very useful feature for you when recording, and for your typist for note taking, recording, and for your lyrics for note taking, stock taking, etc. Other points are twin track recording—Although 40 mins. with normal tapes, standard batteries. Although originally sold at £16.10.0 we are able this month to offer for only £7.19.6 plus 5/- post and insurance. Brand new and complete with microphone, batteries, tape and spools, nothing else to buy. DON'T MISS THIS AMAZING OFFER.


**INFRA RED HEATER**

Make up one of these latest type heaters, ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—use silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and metal casing as illustrated, 19/6 plus 2/6 post and insurance. Pull switch 3/- extra.



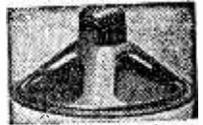**MAKING AN FM TUNER**

Available at present is a very nice cadmium-plated F.M. Tuner chassis with holes punched for coils and other components, also a nicely printed perspex front calibrated usual F.M. frequencies. Real bargain 8/6 + 2/- or with two-gang tuning condenser 10/- + 2/- postage.



**Speaker Bargain**

12in. High-fidelity loudspeaker with 8 ohm speaker coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 + 3/6 post and insurance.

**Simmerstat Heater Regulator**

Suitable to control elements, heaters, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 65/- each, special snip price 13/6, plus 2/-.

**This month's new bargains**

Noughts & Crosses machine—an opportunity to make this very amusing item—described in Practical Electronica. Kit of 19 switches only 40/- post paid.

Neons for Panel Game Switch etc.—not the midgit type but possibly more suitable, 12 for 10/6 post paid.

Midget wire ended type 1/8 (Ex equip.) or 1/9 new.

Paxolin Panels Size 5 x 8 Ideal for most transistor projects 6/6 doz post paid.

Tubular Heater New & unused by G.E.C.—60 watt per foot loading—ideal in home office or store—curtains, papers etc. can drop on them without catching fire—connect these for off peak rates and a warehouse may be supplied complete with fixing brackets—all lengths from 5ft to 12ft—only 39/6 per foot (less than half price) carriage extra at cost.

Transistor Set Cabinet—red and grey zinc covered size 10 x 8 x 3 with handle—ideal for boxing a pocket radio. You'll be amazed how good these sound with a 6" Speaker—15/- plus 3/6 post and ins.

**THERMOSTATS**

Type 'A' 15 amp for controlling room heaters, greenhouse, airing cupboard. Has spindle for knob quickly adjustable from 30/-80° F. 9/6 plus 1/- post. Suitable box for wall mounting, 5/- P. & P. 1/-.

Type 'B' 15 amp. This is a 17in. long rod type made by the famous Surviv 550° F. Internal screw alters the setting so this could be adjustable



over 30° to 1,000° F. Suitable for immersion heater or to make flammable or fire alarm. 8/6 plus 2/6 post and insurance.

**Three Unusual Items**

**OZONE OUTFIT**—for removing smells and generally improving any oppressive atmosphere. Kit consists of Phillips Ozone Lamp and mains unit, only needs box. 19/6 plus 3/6 postage and insurance.

**BLACK LIGHT UNIT.** 40 watt intensity, comprises lamp, lamp holder and 40 watt choke. Only 29/6 plus 6/6 carr. & ins.

**TIMER KIT.** Special offer of all components except metal box to make mains operated interval timer for photography etc. 12/8 plus 2/6 post.

**ELECTRONICS (CROYDON) LTD**

Dept. P.W. 266 LONDON ROAD, WEST CROYDON, SURREY

Post orders to: 43 Silverdale Road, Eastbourne, Sussex

# Hi-Fi

## EQUIPMENT CABINETS OF DISTINCTION



Imperial

- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These Cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

### FREE THE NEW LEWIS RADIO CATALOGUE

Designed to assist your choice of Cabinet.

The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE! Please send your FREE 24 page cabinet catalogue.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(Dept. 115)

Capitals please

# LEWIS radio

100 Chase Side, Southgate, London N.14. Tel: Palmers Green 3733/9666

## 4-STATION INTERCOM



£7/19/0

Solve your communication problems with this latest 4-station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9v. battery. On/off switch. Volume control. Ideally suitable to modernize Office, Factory Workshop Warehouse, Hospital, Shop etc. for instant inter-departmental contacts. Complete with long connecting wires and other accessories. Nothing else to buy. P. & P. 5/-.



Intercom/Baby Alarm

Usually £6.95

Our Price ONLY 59/6

Modernize your Office, Shop, Warehouse, Workshop, Surgery, Nursery and Home with this latest two-way Transistor Intercom, consisting of two units, Master and Sub, in strong plastic cabinets with chromium stands. Elegantly designed or use as two-way instant communication system—call/talk/listen—between two persons anywhere, indoors or outdoors. Both units operate on one 9v. battery. Fully transistorized. Complete with accessories. Ready to operate. P. & P. 2/9. Outstanding value.

**BATTERY ELIMINATOR & CHARGER, 27/6**  
Use your Transistor Radio or Intercom from domestic A.C. mains and charge dry battery PP3 9v. thus boost battery's life many times. Unbeatable value. Save you pounds on batteries. P. & P. 1/6. Complete with Plug, Lead and Snap cord.

Full price refunded if not satisfied in seven days.  
WEST LONDON DIRECT SUPPLIES (PW/11)  
6 Chignell Place, West Ealing, London, W.13

## THE HANDBOOK OF ELECTRONIC TABLES

### AUDIO - RADIO - TV - DC - AF - RF UHF - VHF

by M. Clifford

21/- Postage 1/-

**TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR**, by A. Douglas & S. Astley. 18/-. Postage 1/-.

**VALVE & CATHODE RAY TUBE MANUAL No. 10**. Brimar 7/6. Postage 1/-.

**CLOSED-CIRCUIT TELEVISION HANDBOOK**, by L. A. Wortman. 42/-. Postage 1/6.

**ELECTRONIC ORGAN HANDBOOK**, by H. E. Anderson. 35/-. Postage 1/-.

**BASIC THEORY & APPLICATION OF TRANSISTORS**, by U.S. Army. 10/-. Postage 1/-.

**RADIO & LINE TRANSMISSION**, by G. L. Danielson & R. S. Walker. Vol. 1. 21/-. Vol. 2. 22/6d. Postage 1/- each.

**TROUBLESHOOTING WITH THE OSCILLOSCOPE**, by R. G. Middleton. 20/-. Postage 1/-.

**THE RADIO AMATEUR'S HANDBOOK**, by A.R.R.L. 1965 ed. 40/-. Postage 3/-.

**COMPLETE CATALOGUE 1/-.**

## THE MODERN BOOK CO.

19-21 PRAED STREET LONDON, W.2

Phone: PADDington 4185  
Open 6 days 9-6 p.m.

## TEST METERS



**20,000 O.P.V. MODEL TP 55**. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2in. x 5 1/2in. x 1 1/2in. £5.1.6.

**20,000 O.P.V. MODEL TP 10**. Reads A.C. and D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 x 3 x 1 1/2in. £3.19.6.

**30,000 OHMS PER VOLT MODEL 500**. Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 O.P.V.; D.C. current to 12 amps. Resistance to 20 Megs.; Decibels from -20 to +58; incorporates internal buzzer for audible warning of direct shorts & blocking condenser for A.F. output measurements. Size 3 1/2 x 5 1/2 x 2 1/2in. £8.19.6.

**TRANSISTORISED TEST EQUIPMENT**. Fully guaranteed, brand new. By NOMBREX: 150 K.C./s.—550 Mc/s. Signal Generator. 29.10.0. Resistance-Capacitance Bridge. 28.5.0. 1-1.6 Mc/s. D.C. Power Supply. 26.10.0. Audio Generator 10/100.00 o/s. 216.15.0. Inductance Bridge. 118.0.0.

**SPECIAL OFFER OF AMERICAN VALVE VOLTMETERS**. 11 Megs., Input. 6 D.C. Voltage ranges to 1,000. 5 A.C. voltage ranges to 1,000. Resistance range to 20 Megs. Decibels 4in. 200 microamp. meter. For 110/250 volts A.C. operation. With test prods and operating instructions. Manufactured by RCA and Electronic Designs. ONLY 27.19.6 (Post etc. 3/6).

**LINEAR AMPLIFIERS**. LG34, 4 watts, size 8 1/2 x 4 1/2 x 3 1/2in. high. £5.0.0. L45A 5 watts, size 7 x 7 x 5in. high. £4.9.6. PZ2 2.5 watts. 12/8. L5/55 5 watts stereophonic, size 10 1/2 x 8 1/2 x 2 1/2in. cover with carrying handles. 25/- "Diatonic" 10 watts Hi-Fi Ultra Linear Push-pull size 9 x 7 x 5 1/2in. high. £12.12.0. Cover with carrying handles. 19/6. L1/10 10 watts Hi-Fi Ultra Linear size 9 x 7 x 5in. high. £13.13.0. Cover with carrying handles. 19/6. "Conchord" 30 watts Hi-Fi Ultra Linear size 12 1/2 x 5 x 7 1/2in. high. £16.16.0. Cover with carrying handles. 25/- L50 50 watts Hi-Fi Ultra Linear, size 14 x 10 x 5in. high. £23.2.0. Cover with carrying handles. 32/6. All amplifiers for normal A.C. mains and ex stock. Details on request.

"Tripletone" Convertible Amplifier. Size 10 x 3 x 4 1/2in. high. 4 watts output matched for 2-3 ohms OR 2 amplifiers can be coupled together for STEREO. 26.19.6 each.

"Tripletone" F.M. Tuner, size 11 x 6 x 3in. high. Coverage 56-104 Mc/s. £13.19.8 (unpowered), or £15.14.8 (self-powered). Details on request.

**MICROPHONES**. Crystal Types. Gunitar, 12/6. Desk, with built-in stand, 15/-. Acos 39/1. Stick and Table stand 32/6. Super Stick, with heavy Desk stand 49/6. Hearing Aid Types. Stick with heavy Desk Stand. 59/6. "Slimline" Stick 30K impedance, with switch. 75/-. Omni-directional chrome plated die-cast frame. 50K with switch 89/6.

## HARRIS ELECTRONICS (London) LTD.

138 GRAY'S INN ROAD, LONDON, W.C.1

Telephone: 1E Rmington 7961  
Please include carriage cost on ALL items.  
Trading hours 9 a.m.—6 p.m., Monday—Friday.  
Closed Saturday. Wire 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.

ever, is usually best later on (around 0230—0330 for example). Again not a general rule, they will often be heard at their best when North America is below average. Regular s.w. DX'ers will find a familiar scene with Venezuela and Colombian Republic well to the fore.

**Africa:** Winter evenings can produce a large number of North Africans, plus things like Kaduna (Nigeria) and Dakar (Senegal). They often reach superb strength. Liberia is another possible, later in the evenings. Kenya has been heard signing on around 0300 and one or two South African stations have been logged at around 0130—but these are not easy by any means.

**Asia:** A surprising number of Asian stations can be heard, with patience and perseverance. Middle East stations are fairly plentiful, some being quite regular—last season for instance Kuwait was heard night after night (small hours). Although they can be heard in the late evening, some have been logged in the afternoons in winter. A good time is during the Feast of Ramadan when they operate all through the night!

Further afield, India and Pakistan are worth searching for. Best times for All India Radio and Radio Pakistan stations last season were around 0000—0100, 0100—0200 and similar hour-long peaks. On good days, they can sometimes be heard during the afternoons. English announcements and news bulletins are helpful in identification, but are not of long duration. Some, particularly Indians often have strong signals.

China is more difficult but some stations are quite well received. Best times are from 2200 and at various times from early afternoon onwards, according to time of year. Japan is very rare but several were heard last season, mostly during afternoon Far East openings. Other stations in this area have been heard, mainly during the afternoon/early evening.

**General:** Having acquired a general idea of what to expect, from actual listening sessions, and having located a few key stations, the band is yours to search. Expectation of conditions can often be fairly well assessed by the signals of a few star performers. Judging from last season, these are worth checking as a guide to conditions on a particular day:

CBA, Sackville, N.B., Canada on 1.070kc/s. Probably the most consistent North American, heard night after night, sometimes even before Paris on the same frequency has closed down. If CBA is not coming in, not much else will be heard from North America; at least Canada. Another good check is CJON, St. John's, Newfoundland, on 930kc/s, usually earlier even than CBA—sometimes from 2000 or so in peak conditions. By midnight, in winter, these (and others) should be very strong in good conditions.

South Americans are difficult to judge since skip seems to vary through the season. I.R.I., Buenos Aires, for instance, is on the same frequency as CBA and whereas it was hardly heard (by the writer at least) early in the season, it was often dominant over CBA later in the season. The sub-continent is a vast area and you can expect good periods of, say, Argentinians and others of, say, Brazilians, etc.

For the Caribbean areas, however, there is no

better than the Spanish-speaking propaganda station *Radio Americas* on Swan Island (1,160kc/s) which is very consistent and very strong. Another pointer is Bonaire, Netherlands Antilles, which has been putting out phenomenal signals on 800kc/s.

A key station for Far Eastern prospects is the *Voice of America* station in Okinawa on 1,178kc/s. This is often surprisingly strong and is heard during the winter from early afternoon onwards, closing around 1630. Programmes are in Eastern tongues, but there are English announcements.

Of the Indians, the best last year were Rajkot (910kc/s) and Sangli (1,250kc/s). From China, the most consistent were Kiangsi (840kc/s) and Anwei (940kc/s).

### Equipment

A standard transistor portable is virtually useless and a communications receiver is ideal. Between the two extremes there is a good deal of scope. Main requirements are high sensitivity and high selectivity; remember that many European stations are on the air till 0200 and many start up again around 0400. Most Americans (South and North) operate on even 10kc/s channels (i.e. 770, 780, 790kc/s) whereas Europeans, Africans and Middle East stations are on 9kc/s channels (i.e. 764, 773, 782kc/s). Even so, selectivity is a major requirement for serious DX work.

Fortunately there are still a number of very good war surplus communications receivers on the market at bargain prices. The more experienced may also find that some of the vintage domestic valve radio sets have good possibilities, especially if they can be hotted up.

Calibration is another aspect. A set without reasonably accurate calibration (in kc/s) can be supplemented with a simple frequency meter, but this is inconvenient except where specially precise measurements are wanted.

Really good slow motion tuning is essential. Variable selectivity in some form (and/or crystal filters) and noise limiters are useful features.

These features are all desirable to some extent, depending on how serious one takes his m.w. DX.

Aerials need thought. Simplest is a random long wire, erected as long and as high as possible. And clear from obstructions such as trees, roofs, etc. Various systems should be tried, and results evaluated. Indoor aerials are not completely useless and, in fact, can give quite good results if sufficient wire is used (routed around picture rails, etc). Vertical aerials have some advantages. A good earth is worth while, too.

Many serious DX enthusiasts use tuned loops and aerial tuning units, useful in view of their variable direction properties. If sufficient readers are interested we hope to publish some fuller data on aerials, tuner units and loops.

### Practical Experiment

Should the desirable features of the receiving equipment scare off potential m.w. DX'ers, let them take heart from the following! Last season (from September 1964 to March 1965) the writer undertook a fairly intensive survey of m.w. DX using only a home built tuner (r.f. amp, f.c., two i.f. amps, variable selectivity) into an audio

amplifier and feeding the tuner from the downlead of the chimney-mounted TV aerial!

The list which follows shows the large number of DX stations from all over the world which were received on this less-than-ideal set up. We hope it will encourage others to give the neglected medium wave band a good search during the coming months. It leaves out semi-DX such as Egypt, Morocco, Algeria, etc.

#### Reference Material

(1) World Radio TV Handbook. This contains, by country, details of all the broadcasting stations

of the world. A wealth of invaluable information. Cost is 26s.

(2) World Medium Wave Guide. Essential for all m.w. DX fans. Gives complete listings of all m.w. stations by frequency as well as North America stations by location.

These two books are published in Denmark (written in English throughout) and obtainable through specialist book shops.

(3) Medium Wave News. A privately distributed newsletter published during the main DX season containing all the latest news. Details from the Editor—Ken Brownless, 7 The Avenue, Clifton, York.

### LOG FOR SEPTEMBER 1964—MARCH 1965

Kc/s	Call	Location	Kc/s	Call	Location
560	LVI	Mendoza, Argentina	760	ZFY	Georgetown, British Guiana
	CKCN	Seven Sisters, P.Q.			Lucknow, India
570		Godthab, Greenland		WJR	Detroit, Michigan
580	CJFX	Antigonish, N.S.	764		Dakar, Senegal
	CFRA	Ottawa, P.Q.			Baghdad, Iraq
	LWI	Tiruchi, India	770	WABC	New York
	VOCM	Cordoba, Argentina			Hupei, China
590		St. Johns, Newfoundland	775	PJA8	Aruba, Netherlands Antilles
		Peking, China	777		Zaheden, Iran
600		Ajmer, India	785		Damascus, Syria
	CFCF	Montreal, P.Q.	790	CFDR	Dartmouth, N.S.
610	CHNC	New Carlisle, P.Q.	800	PJB	Bonaire, Netherlands Antilles
620	CKCM	Grand Falls, Newfoundland		CHRC	Quebec City, P.Q.
		Peking, China			Amman, Jordan
		Santa Cruz, Canary Is.	810	WGY	Schenectady, N.Y.
630		Lahore I, Pakistan		WKVM	San Juan, Puerto Rico
	CFCY	Charlottetown, P.E.I.			Delhi, India
	WKYN	Rio Pedras, Puerto Rico	820	HJED	Cali, Columbian Rep.
638		BBC Relay, Cyprus		WBAP	Fort Worth, Texas
640	CBN	St. Johns, Newfoundland	830	CMCA	Havana, Cuba
	CMQ	Havana, Cuba		JOBB	Osaka, Japan
		Peking, China	835		Belize, British Honduras
		Point-a-Pitre, Guadeloupe	840		Kiangsi, China
650	YVQO	Puerto la Cruz, Venezuela		WHAS	Radio Caribbean, St. Lucia
	ELBC	Indore, India		CKVL	Louisville, Kentucky
		Monrovia, Liberia	850	CX16	Verdum, P.Q.
	WSM	Godhavn, Greenland			Montevideo, Uruguay
656		Nashville, Tennessee			Ahmedabad, India
660	WNBC	Tel Aviv, Israel		PRA3	Pyongyang, North Korea
	CE660	New York	860	CBH	Rio de Janeiro, Brazil
	YVLH	Santiago, Chile		CJBC	Halifax, N.S.
668		Caracas, Venezuela			Toronto, Ontario
677		Damascus, Syria			Lanchow, China
680	CJCM	Jerusalem, Jordan	870	WWL	Sambalpur, India
	WNAC	Grand Bank, Newfoundland	880	WCBS	New Orleans, La.
	WAPA	Boston, Mass.	890	WLS	New York
690	CMBC	San Juan, Puerto Rico		YVLW	Chicago, Ill.
	CBF	Havana, Cuba	900	XEW	Valencia, Venezuela
		Montreal, P.Q.		CJBR	Mexico City, Mexico
692		Dacca I, Pakistan	908		Rimouski, P.Q.
701		Nicosia, Cyprus	910		Baghdad, Iraq
700	WLW	BBC Relay, Perrim Is.		WABI	Rajkot, India
710	WOR	Cincinnati, Ohio		YVPF	Bangor, Maine
	CJOX	New York	920	CJCH	Marquetia, Venezuela
		Grand Falls, Newfoundland	930	CJON	Halifax, N.S.
746		Jullunder, India	940	CBM	St. Johns, Newfoundland
749	CBL	Aleppo, Syria		WINZ	Montreal, P.Q.
	PRA4	Toronto, Ontario			Miami, Florida
750	WSB	Salvador, Brazil			Anwei, China
	YVK5	Atlanta, Georgia	950	CKNB	Kaduna, Nigeria
		Caracas, Venezuela		WPEN	Campbellton, N.B.
					Philadelphia, Penn.

# FOR PEAK PERFORMANCE AT LOW COST — PICK CODAR AMATEUR RADIO EQUIPMENT



Advanced design and craftsmanship plus an unequalled reputation proved by the many hundreds of testimonials received from CODAR users is your guarantee of complete satisfaction. Only the best is good enough for CODAR—Mullard, Brimar, Jackson, Denco, Electronique, Thorn, A.E.I., are just some of the famous names built into CODAR equipment. CODAR-KITS are supplied with clear pictorial diagrams and easy to follow instructions—no technical knowledge or special tools are required for complete success. Build your Short Wave Station with CODAR-KITS and enjoy peak performance and world wide reception previously possible only from much more expensive equipment. For illustrated leaflets giving fullest details send 6d. in stamps.

**CODAR R.F. PRE-SELECTOR.** Will considerably improve the performance of any superhet receiver. "Results are amazing". "Well worth the money". **MODEL P.R.30.** Uses EF183 Frame Grid tuned R.F. Amplifier and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12 M/A H.T. 6.3 volts, 3 amp L.T. Size 8 1/2 x 5 x 4in. Ready built, complete with cables, plugs and instructions, £4.19.6. Carr. 3/6. **MODEL P.R.30X.** Self powered version for 200-250v. A.C. and also provides 25 M/A at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories, £7.4.0. Carr. 3/6.

**CODAR "Q" MULTIPLIER MODEL R.Q.10.** For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB. Both PEAK and NULL functions tunable over receiver I.F. passband, BFO, facility included. Size 8 1/2 x 5 x 4in. Power requirements 180-250v. H.T. at 5 M/A 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions, £6.15.0. Carr. 3/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25 M/A at 200v. H.T. and 6.3v. 1 amp. L.T. for other accessories £8.8.0. Carriage 3/6.

**CODAR A.T.5. 12 WATT 2 BAND TRANSMITTER.** The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice". Size only 8 1/2 x 5 x 4in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL P1-net output, P. A. Plate current meter plus neon indicator. Plate/Screen modulator. AM/CW switch and Panel key jack. Plug changeover for 6 or 12 volts heater supply. Ready built £16.10.0. Carr. 4/- **A.T.5 POWER SUPPLY UNITS.** Type 250/S. For 200/250v. A.C. with Stand-by/Net/Transmit and aerial changeover switching, stabilised VFO supply, neon stand-by/transmit indicator £8.8.0. Carr. 6/6. Type 12/MS 12 volt cold state power supply unit £11.5.0. Carr. 5/-. Type 12/SC Remote Control and Aerial Switching unit, £2.7.8. Carr. 3/-. (H.P. Terms available).

**CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER** Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/-. Extra Coils 4/9 each. Instruction Manual only 2/- (credited on order). Electrical Bandspread available. Provision to add 2 transistor amplifier.

**CODAR-KIT CR.45 MAINS T.R.F. SHORT-WAVE RECEIVER.** World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★Separate electrical bandspread. ★3 slow motion vernier drives. ★Low loss polystyrene plug-in coils, factory aligned. ★Dials calibrated in frequencies and degrees. ★Power output 3 watts for 2/3 ohm speaker. ★Valve line-up: ECC81, EL84, E280. **CODAR-KIT CR.45** complete with valves, 3 coils (10-23, 25-75, 80-176 metres) and 11 page instruction manual (LESS Cabinet), £7.5.0. Carr. 5/6. **CR.45 CABINET,** 12in. x 6 1/2in. x 7 1/2in. with sliding door for easy coil changing, 35/-. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can now be supplied ready built—price on request). (H.P. terms available).

**CODAR-KIT CR.66 COMMUNICATION RECEIVER.** The finest superhet kit ever offered. ★Covers 640 Kc/s-30 Mc/s in 4 bands. ★Separate electrical bandspread. ★Factory aligned Coil unit and I.F. Transformers. ★Regenerative I.F. stage for maximum gain and BFO for C.W. reception. ★Power output 3 watts for 2/3 ohm speaker. ★Panel controls: Aerial Trimmer, A.V.C., Standby Bandswitch, AF Gain, IF Gain, BFO, etc. ★Valve Line up: ECH81, EBF89, ECC81, EL84, E280, EM84. ★Size up: 16in. x 6 1/2in. x 8 1/2in. **CODAR-KIT CR.66** Complete with 11 page instruction manual, £19.15.0 (Ready-built £23.0.0). **CR.66 "S" Meter Model Kit** £22.0.0 (Ready-built £25.0.0). Carr. 7/6 extra on all models (H.P. terms available). Instruction Manual only 7/6 (credited on order).

We shall be pleased to see you

ON STAND 20A AT THE  
INTERNATIONAL RADIO COMMUNICATIONS  
EXHIBITION  
SEYMOUR HALL, OCTOBER 27th-30th

## CODAR RADIO COMPANY

G3IRE G3HGQ

BANK HOUSE, SOUTHWICK SQUARE,  
Southwick, Sussex. Tel. 3149

Canada: Codar Radio of Canada, Tweed, Ontario

# WEYRAD

## TRANSISTOR COILS

The P50 series remain the most popular and widely used components for Medium and Long-wave Transistors Superhets:—

P50/1AC Oscillator Coil for 176 pF tuning ... ..	5/4 ea.
P50/2CC 1st & 2nd I.F. Transformers ... ..	5/7 ea.
P50/3CC 3rd I.F. Transformers ... ..	6/- ea.
All mounted in individual cans $\frac{1}{16}$ in. diam. x 3in. high.	
RA2W Ferrite Rod Aerial 208 pF Tuning ... ..	12/6 ea.
LFDT4 Driver Transformers ... ..	9/6 ea.
OPTIA Output Transformers ... ..	10/6 ea.
PCAI Printed Circuit Panel ... ..	9/6 ea.
Constructor's Booklet ... ..	2/- ea.

## VALVE RECEIVER COILS

Our individual "H" type iron-cored coils are without equal for the construction of a wide range of receivers. For the simplest T.R.F. sets covering one or more wave-bands the Aerial and H.F. Transformer coils are ideal. The standard superhet circuit using the ever-popular triode-hexode frequency change layout would employ the Aerial and Oscillator coils and the coverage can be selected from 7 different bands ranging from 12.5 to 2,000 metres. For a really high-performance receiver an R.F. stage can be added by using the Aerial, H.F. Transformer and Oscillator Coils and a circuit is provided illustrating such a layout.

H Coils 3/9 each.

PLEASE NOTE OUR CHANGE OF NAME  
**WEYRAD (ELECTRONICS) LIMITED**  
 REGENT FACTORY, SCHOOL STREET,  
 WEYMOUTH, DORSET

# WIRECOMP ELECTRONICS

## WIRECOMP'S BARGAIN STORE

48 Tottenham Court Road, London, W.1

Thousands of bargains: Transistor Radios—Record Players—Tape Recorders—Radiograms—Rock Bottom Prices!

### TRANSISTOR POCKET RADIOS

Ideal Gifts—all supplied complete with personal earpiece, battery and carrying case. Fully guaranteed. Post free.

#### BOY'S 2 TRANSISTOR

In attractive plastic case. Size only 4 x 2½ x 1½ in. 2Hn. speaker. Uses PP3 battery. Tunable over full medium waveband. 39/6

#### BOY'S 4 TRANSISTOR MODEL 45/-

In plastic case, 4 x 2½ x 1½ in. with 2Hn. speaker. Uses PP3 type battery Tunable over full medium waveband. 59/6

2 Waveband (Long and Medium) Model size 5 x 3½ x 1½ in. cream/black plastic case. 89/6

### NEW SUPER MINIATURE POCKET RADIOS

THE SINCLAIR MICRO-4. Self-contained pocket radio. Size only 1½ x 1½ x ¾ in. Complete with earphone and detailed construction data. Can be built for only Mercury cell 1/11 extra (2 required). 59/6

THE SINCLAIR SLIMLINE. The new 2-transistor pocket radio size only 2½ x 1½ x 1½ in. Micro alloy transistorised and printed circuit. All components available separately. Easy to assemble. Can be built for 49/6

### INTERNATIONAL BRAND TAPE—Fully Guaranteed

MYLAR BASE	ACETATE BASE	
3½ in. Triple play, 600ft. 15/-	3in.—160ft. ....	3/6
4in. Triple play, 900ft. 17/6	3in.—225ft. ....	4/11
5in. Double play, 1,200ft. 15/-	3in.—300ft. ....	7/6
5in. Triple play, 1,800ft. 35/6	5in. Long play, 1,200ft. 12/6	
5½ in. Double play, 1,800ft. 22/6	5in. Long play, 1,200ft. 12/6	
5½ in. Triple play, 2,400ft. 45/-	7in. Stand. play, 1,200ft. 10/-	
7in. Stand. play, 1,200ft. 12/6	7in. Long play, 1,800ft. 15/-	
7in. Long play, 1,800ft. 19/6	P.V.C. BASE	
7in. Double play, 2,400ft. 25/-	5in. Stand. play, 900ft. 8/6	
7in. Triple play, 3,600ft. 55/6	5in. Stand. play, 800ft. 11/6	

P. & P. 1/- extra per reel, 4 reels and over Post Free.

### THE "SKYROVER" RANGE

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. Cover the full Medium Waveband and Short Waveband 31-94 M and also 4 separate switched band-spread ranges. 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station selection.



**NEW—THE "SKYROVER" Mk III**  
 Now supplied with redesigned cabinet, edgewise controls, black and chrome plastic cabinet. Size 10 x 6½ x 3½ in.  
 Can now be **£8.19.6** Post 5/-  
 built for H.P. Terms: 27/- dep. and 11 months at 15/8. Total H.P.P. Price £10.0.3.

**THE "SKYROVER" DE LUXE**  
 Tone Control Circuit is incorporated with separate Control. In a wood cabinet, size 11½ x 6½ x 3½ in., covered in a washable material, fitted carrying handle.  
 Can now be **£10.19.6** Post 5/-. H.P. Terms: 33/- dep. and 11 months at 19/2. Total H.P.P. £12.3.10.

A simple additional circuit provides coverage of the ONLY 1100/1950M. band. This conversion is suitable for 10/- Post both models that have already been constructed. EXTRA Free

Data for Receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All components available separately

### PAMPHONIC HI-FI EQUIPMENT

ONLY A FEW OF EACH STILL AVAILABLE

TYPE 3001 Integrated Stereo Amp. List Price £88.10.0.  
 WIRECOMP'S PRICE £8 Gns. Post 10/6  
 TYPE 1002A Control Unit. WIRECOMP'S PRICE £4.19.6. Post 2/6.  
 TYPE 2001A Pre-Amplifier. WIRECOMP'S PRICE £4.19.6. Post 3/6.  
 TYPE 782A Switched Radio Tuner. WIRECOMP'S PRICE £5.19.6. Post 7/6.  
 All fully described in our advertisement in "P.W." April 1965

323 EDGWARE RD., LONDON, W.2. AMBassador 7115

All Branches open all day Saturday Early closing Thursday

378 HARROW RD., LONDON, W.9. CUNningham 9530

Mail Orders to the above address for prompt service

Kc/s	Call	Location	Kc/s	Call	Location
950	LR3	Buenos Aires, Argentina	1250	WKBR	Manchester, N.H.
953		Aleppo, Syria		CKBL	Matane, P.Q.
955	XZK	Rangoon, Burma		WRYT	Sangli, India
960	CHNS	Halifax, N.S.	1260	WEZE	Pittsburg, Penn.
	WEAV	Plattsburg, N.Y.		LT9	Boston, Mass.
970	WCSH	Portland, Maine		WAME	Santa Fe, Argentina
	HLGA	Suwon, Korea	1270	CJCB	Miami, Florida
990	CBY	Corner Brook, Newfoundland		LS11	Sydney, N.S.
1000	XEOY	Mexico City, Mexico	1280	CJMS	Buenos Aires, Argentina
	CKBW	Bridgewater, N.S.		WADO	Montreal, P.Q.
	WCFL	Chicago, Ill.		PRG3	New York
	KOMO	Seattle, Washington	1290	WKNE	Rio de Janeiro, Brazil
1010	WINS	New York		WERE	Keene, N.H.
	CFRB	Toronto, Ontario	1300	CBAF	Cleveland, Ohio
		Hyderabad, Pakistan		CHGB	Monkton, N.B.
1020	KDKA	Pittsburg, Penn.	1310	WLOB	St. Anne, P.Q.
	YVQT	Cumana, Venezuela		WORC	Portland, Maine
1030	WBZ	Boston, Mass.		CKOY	Worcester, Mass.
1040	VUB	Bombay, India			Ottawa, P.Q.
1050	CHUM	Toronto, Ontario	1315	HJAK	Radio Martinique, Martinique
	WHN	New York	1320	CKEC	Barranquilla, Colombian Rep.
1060	CJLR	Quebec City (F)		CJSO	New Glasgow, N.S.
	CB106	Santiago, Chile		WZOK	Sorel, P.Q.
1070	CBA	Sackville, N.B.		LU6	Jacksonville, Florida
	LRI	Buenos Aires, Argentina	1325	4VW	Mar del Plata, Argentina
	VUD	Delhi B, India			Port-au-Prince, Haiti
	WMIA	Arecibo, Puerto Rico	1330	WPOW	Teheran, Iran
1080	WTIC	Hartford, Conn.		WCRB	New York
1090	WBAL	Baltimore, Maryland			Waltham, Mass.
	CX28	Montevideo, Uruguay	1340		Bikaner, India
	KING	Seattle, Washington		PRH6	Belo Horizonte, Brazil
1100	PRG9	Sao Paulo, Brazil	1345		Kuwait
	KYW	Cleveland, Ohio	1350	WAVY	Portsmouth, Va.
	YVKE	Caracas, Venezuela		WEZY	Cocoa, Florida
1110	CBD	St. John, N.B.	1360	CKBC	Bathurst, N.S.
	WBT	Charlotte, N.C.		WDRC	Hartford, Conn.
1120	KMOX	St. Louis, Missouri	1370	CFLV	Valleyfield, P.Q.
1130	WNEW	New York		WSAY	Rochester, N.Y.
	WDGY	Minneapolis, Minnesota	1375		REF, St. Pierre
	YVMF	Maracaibo, Venezuela	1380	CFDA	Victoriaville, P.Q.
1140	CBI	Sydney, N.S.		WLCY	St. Peterburgh, Florida
		V.O.A., Philippines	1385	4VS	Port-au-Prince, Haiti
1150	CHSJ	St. John, N.B.	1390	WCSG	Charleston, S.C.
	XEJP	Rawalpindi, Pakistan		WEGP	Presque Is., Maine
	CKTR	Mexico City, Mexico			Arwaz, Iran
		Three Rivers, P.Q.			Imphal, India
1160	WJJD	Chicago, Ill.	1400	WOND	Pleasantville, N.J.
	HJCK	Bogota, Colombian Rep.	1410	WPOP	Hartford, Conn.
1165		Radio Americas, Swan Island	1420	WOC	Davenport, Iowa
1170	WWVA	Wheeling, West Virginia		WCOJ	Coatsville, Pa.
1178		V.O.A., Okinawa	1430	WENE	Endicott, N.Y.
1180	WHAM	Rochester, N.Y.	1440	CKPM	Ottawa, P.Q.
1190	WOWO	Fort Wayne, Indiana		WHHH	Warren, Ohio
	HJCT	Barranquilla, Colombian Rep.	1460	CKRB	Ville de St. Georges, P.Q.
1200	WOAI	San Antonio, Texas		WHEC	Rochester, N.Y.
	YVOZ	Caracas, Venezuela		WOKO	Albany, N.Y.
	BED88	Taiwan, Formosa	1470	WLAM	Lewiston, Maine
1210	WCAU	Philadelphia, Penn.		CFOX	Pte. Claire, P.Q.
1230	VUB	Bombay, India	1480	CBZ	Fredericton, N.B.
1235	ZBMI	Hamilton, Bermuda	1490	WLDB	Atlantic City, N.Y.
1240		Aden, Forces Broadcasting Service	1500	WTOP	Washington, D.C.
			1510	WMEX	Boston, Mass.
			1520	WKBW	Buffalo, N.Y.

## A COMMENTARY BY HENRY

# PRACTICALLY WIRELESS

## No. 14

### The Import Gap

**THIS** month, dear reader, I beg your leave to indulge in what an editorial colleague has called a "typical Henry Carp".

There are several subjects that rouse Henry's spleen. Among them, as hinted in September during a dissertation on the Metric System, is the imported radio receiver or other associated equipment.

Not that imports are wrong in themselves. Not even that the price-cutting techniques of some makers allow batches of cheap rubbish to be spawned upon the supermarket shelves. To be realistic about this, we can hardly expect a healthy export business unless we accept some sort of reciprocal trade.

My objection is to the indifference, almost contempt, of British distributors who unload foreign gear on us and, having made their profit from its sale, want nothing more to do with the product. Lip service is paid to "specialised service facilities", or "distribution backed by one of the largest manufacturers . . . etc". But just try, as a private individual, as a purchaser, obtaining spares or service information and see what happens.

This is no sour grape contention. Henry is in the trade, and has had the bitter experience of having to return goods to customers because repair was impossible—or at least, economically unsound. And why?



"Fancy buying that rubbish"

Because the importers could do no more than forward the equipment to its source of origin when repairs were needed.

In the case of tiny radios this may have seemed sound policy; but a half-hour with some service information and the appropriate spare parts would in many cases have solved the problem. And would have suited the customer far better than the protracted wait while his precious unit sailed half across the world.

If the bona fide members of the radio service fraternity cannot get as much as a polite acknowledgement from some distributors, what hope is there for the man in the street? Hardly surprising that some radio dealers turn such service work away with the implied comment: "Fancy buying that rubbish."

The annoying fact is that so much imported equipment is by no means rubbish. And the foregoing remarks certainly do not apply to the better foreign manufacturers who take great trouble to ensure service facilities and information to back their sales. Although even they cannot always keep the spares rolling.

It should be the absolute rule that imported goods must always be backed with service information—and this information should be available on request to any accredited service agency. Not just to the so-called service agents of the importers, who are anybody willing to accept the franchise at the terms these astute gentry are prepared to offer.

They need have no special training in dealing with the equipment, and very often their facilities are unquestioned. Bill Jones in the next street is as likely to be accepted as Messrs Mendit with branches in every major city. The customer is not to know. Not, that is, until his equipment goes wrong and it is too late for tears.



"Succumb to rough treatment . . ."

Needless to say, there are notable exceptions. The larger companies have admirable service facilities. To the extent that we regard a couple of them as British as anything on the market. There is seldom any difficulty with Grundig spares, nor lack of information; and it is interesting to note that the recent Philips' challenge to the Hong Kong portables is a fist-sized Popmaster designed and produced at Croydon.

We do not ask for massive tomes of data pinned to every set. No need for a Guide Littéraire with every model. Not even for the sort of instruction book, complete with thirty-six full-page illustrations, that accompanies the Beocord 2000 tape recorder. (Yet it is worth noting that this quality manufacturer has always insisted on inserting a service diagram in the bowels of even the least of their portables.)

All we want is the common courtesy of our money's worth. After all, what's cheap about a set that has to be thrown away when it goes wrong, merely because nobody in town has the facilities to repair it?

# TIME-TESTED KITS BY THE PIONEERS OF KITS!

## MAKE 5 DIFFERENT TRANSISTOR RADIOS

FOR **35/-**



**NO EXPERIENCE NECESSARY.**  
No Soldering. Only 8 connections for first radio to work. Just look, you get A.B.C. Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES - EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr. R. O'D. of London writes: "... I received your components and I must say that I am very satisfied with them. I have already set up 1... **COMPLETE HOME/RADIO COURSE, Originally 26 SHILLING ONLY 35/- plus 3/6 post. etc.**

## FABULOUS ST. TROPEZ MK. 6

The Sensational Pocket Radio



This fantastic offer will amaze you—the beautifully compact ST. TROPEZ, measuring 4 1/2 x 3 1/2 in. receives perfectly in bedroom, office or garden—over all medium waves including Luxembourg. Under 1d. per hour running cost. ANYONE can assemble it in one or two hours using our simple A.B.C. plan. 25/- (P. & P. 2/6 extra). Case extra. Parts can be bought separately.

## AMAZING CIGARETTE RADIO

ONLY **18/6**



Yes, a perfectly ordinary packet of cigarettes!—but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our glowing testimonial file, Mr. D.B. of Huddersfield writes: "... I have fitted the parts in and it is working wonderfully..." **ALL PARTS including Semi-Conductors, A.B.C. Plans, etc. ONLY 18/6 plus 2/6 post etc.**

**PARTS AVAILABLE SEPARATELY**

## DON'T WALK—JUST TALK!!




**INTERCOM OUTFIT & BABY ALARM**

LIMITED QUANTITY SAVE £3.13.1

Robustly made, brand new current models. You get 2 separate, fully transistorised intercommunicating sets—each can speak or listen to the other—complete with 60 ft. connecting wire. Fixed in a flash. Ends baby-crying worries. Ideal for Workshop 10 House, Sickroom, hundreds of uses! Hangs on wall or stands up. Our absurd price 52/11, battery 2/6 extra. Post, etc. 3/7. Money refunded if not 8 gns. value!

## CAR CIGARETTE LIGHTER DISPENSER

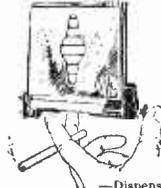

High Class Stores sell at 3 gns.—save **£2.4.6** Top quality chromium. Car cigarette—Lighter Dispenser. Fixed in a jiffy—Pressing Button delivers ready-lit Cigarette into your hand! Takes 10 cigarettes—King size or any size! As fitted to luxury cars, state, foot-prot. 4 1/2 x 4 x 1 1/2 in. Lifetime tested, ready to use. Refund if not worth 8 gns. 75/0 only. 18/6 plus 1/6 P. & P. (state 6 or 12v.).

## TRANSISTOR RADIO KITS

SOLD IN DEPARTMENT STORES AT £5.8.0.

OUR PRICE **37/6**

P. & P. 3/6 Extra




Well-known brand Transistor Radio Kits—YOU SAVE £3.10.6. Covers all medium/long wave with parts including Mullard Set-Up Conductors, 48 page instruction manual, Entertaining and educational. No soldering, just plug in making many different Radios in a few mins. Money back if not delighted.

## NEW RADIO VOLKSRADIO

ANYONE CAN BUILD IN 2-3 HOURS

**19/6**

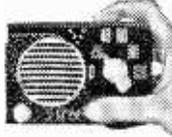

EVEN THE OLDER CHILDREN BUILD THEM!—no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2 in. Many Testimonials! M.H. of Bradford, writes: "... I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them..." **Direct from Manufacturers to You. Send 19/6 plus 2/6 post, etc.**

**PARTS AVAILABLE SEPARATELY**

## TRANSISTOR POCKET RADIOS



**BULK PURCHASE ENABLES US TO MAKE THIS FANTASTIC OFFER—AND WITH MONEY BACK GUARANTEE!!!**


The "SAN REMO" ... so tuned that it brings the voices of star entertainers and vocalists dramatically to life—in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months on 1 1/2 battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker, carrying case—everything only 28/6, 2/6 P. & P. (Parts can be bought separately.) Limited period—no rush your order before it's too late. **DEMONSTRATIONS DAILY.**

ONLY **28/6**

NO MORE TO PAY
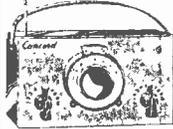
## IT HAD TO COME EVENTUALLY! THE "SKYSCRAPER" PERSONAL COMMUNICATIONS RECEIVER.

Highly sensitive. World-wide short-wave reception including news in English and countless other broadcasts from RUSSIA, AMERICA, etc. etc. Take it anywhere—it's featherweight! 6 in. x 3 1/2 in. x 1 1/2 in. Band spread Tuning Vernier Dial, Miniature Valve Circuits, Plug-in Coils, Own Rod Aerial, etc. 30% of production to be exported. Any one can assemble it within 2 hours—only a few connections to make—experience unnecessary. Parts incl. Case, Personal phone. Easy-to-follow plan—45/6 plus 2/6 Post, etc. Ref. C/tee.



Read what just a few of our satisfied customers say

**R.C. of Harringay writes** Received with thanks Skyrroma ... Very pleased. Working well.

**B.M. of Harrogate writes** ... I would like to thank you ... It was a real bargain.

**L.S. of London W.8 writes** ... given it a good try out and I am very pleased with the results.

**S.B. of Somerset writes** ... delighted with this radio ... glad if you could send one more.

**T.F. of Stevenage writes** ... I would just like to say how pleased my son is with this radio.

## 10 TRANSISTOR CAMERA HI-FI RADIO



ONLY **55/-**

POST 3/6

**LIQUIDATION PURCHASE 500 ONLY** Made to sell at 54 gns.—Save £3.0.6. Latest camera style radio. Big-Set tone from tone-chamber moving coil speaker. new device plugs in Station after Station including Luxembourg, Carols, etc. Fantastic coverage—187-577 metres! Expensive looking finish, simulated leather, black and chromium. Size 4 1/2 x 2 1/2 x 1 1/2. 7 semi-conductors. 55/6+2/6 batt. + 3/6 P. & P. Refund if not delighted.

# RADIONIC

## RADIO & ELECTRONIC CONSTRUCTION SYSTEM

**YOU** NEED RADIONIC


**IF** YOU ARE A BEGINNER  
YOU WISH TO EXPERIMENT  
YOU TEACH RADIO OR ELECTRONICS

Unique and brilliantly simple. Hundreds of educational establishments—Universities, Technical Colleges, Schools, the Armed Forces—are already using Radionic for electronic instruction. Enthusiastic owners range from 9 to 83 years of age. Selected by the Council of Industrial Design for all British Design Centres. Featured in Sound and Television broadcasts.


The system is beautifully engineered from top quality British components. No soldering. No mains. No prior knowledge needed. Simply arrange components on perforated transparent panel, position brass connecting strip underneath, fix with 6BA nuts and circuit works with full efficiency. You can then dismantle and build another circuit. Your results are guaranteed by our Technical Departments and News Letter Service. All parts available separately for conversion or expansion of sets.

- No. 1 Set **£5.18.6.** 14 Circuits (Earphone)
- No. 2 Set **£6.19.6.** 20 Circuits (Earphone)
- No. 3 Set **£10.19.6.** 22 Circuits (7 x 4in. Loudspeaker output)
- No. 4 Set **£14.19.6.** 26 Circuits (include 6 Transistor and reflex superbets)

Prices (Post Free)

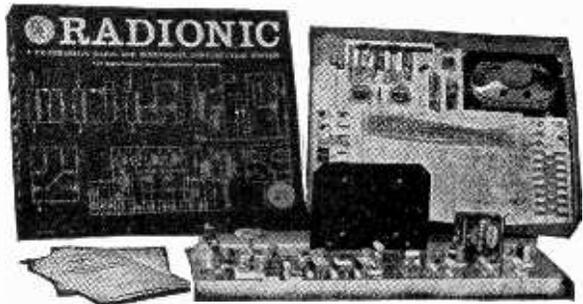

A No. 4 SET and 6-TRANSISTOR SUPERHET

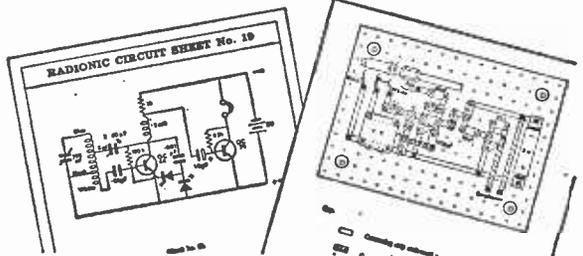

Theoretical Circuit

Practical Layout

Our new 'E' Series of basic electronic circuits is also available separately

Full details from:


**RADIONIC PRODUCTS LIMITED**  
STEPHENSON WAY, THREE BRIDGES  
CRAWLEY, SUSSEX

Tel.: CRAWLEY 26700

Trade Enquiries Invited



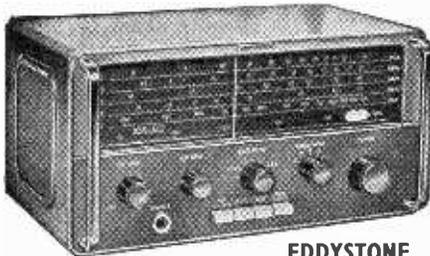The Sensational  
**ALL-TRANSISTOR!**  
Communications Receiver



**EDDYSTONE  
EC10**

for use in the home, caravan, car or boat,  
H.P. facilities. **Only £48** Part exchanges.

Write for brochure

170-172 CORPORATION STREET  
BIRMINGHAM 4  
Telephone CEN 1635

## EXPRESS ELECTRONICS

32 SOUTH END, CROYDON, SURREY

Telephone: Croydon 9186

FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS			
TRIPLETONE HI-FI MAJOR	12 watt	...	£15.18.6
TRIPLETONE CONVERTIBLE	5 watt	...	£6.19.6
TRIPLETONE GEMINI STEREO	5 watt	...	£15.15.0
LINEAR	3 watt	...	£6. 6.0
LINEAR DIATONIC	12 watt	...	£12.12.0
LINEAR CONCHORD	30 watt	...	£16.16.0
ADASTRA 3-3	4 watt	...	£4.19.6
LEAK TL12	14 watt	...	£18.18.0
LEAK VARISLOPE PRE-AMP	...	...	£15.15.0
LEAK TL50	50 watt	...	£33.12.0
QUAD	15 watt	...	£22. 1.0
QUAD STEREO/MONO PRE-AMP	...	...	£25. 0.0
LOUDSPEAKERS			
GOODMANS AXIETTE 8in.	6 watt	...	£5. 5.0
GOODMANS AXIOM 10in.	10 watt	...	£6. 6.0
GOODMANS AXIOM 20I	15 watt	...	£10.15.0
BAKERS 'SELHURST' 3 or 15 ohm			
JUNIOR 8in.	8 watt foam	...	£5. 5.0
STALWART 12in.	15 watt	...	£5. 5.0
BASS GUITAR 12in.	25 watt	...	£5. 5.0
STANDARD Heavy Duty 12in.	20 watt	...	£7. 7.0
BASS Heavy Duty 12in.	25 watt	...	£12.12.0
AUDITORIUM 15in.	35 watt	...	£18.18.0
RECORD PLAYERS			
GARRARD SRP10 4-speed	...	...	£4.17.6
GARRARD MODEL 1000 4-speed	...	...	£6.19.6
GARRARD AT6 TRANSCRIPTION	...	...	£9.17.6
GARRARD 4HF TRANSCRIPTION	...	...	£14.17.6
GARRARD A LAB SERIES	...	...	£17.10.0
GARRARD 301 LAB SERIES	...	...	£19. 5.0
DECCADEC WITH DERAM HEAD	...	...	£14.15.0
BSR TAPE-DECKS TD2 Twin Track	...	...	£7. 9.6

De-Luxe record players with excellent sound reproduction incorporating the latest BSR 4-speed autochanger, independent tone and volume controls, high quality speaker. Not in kit form but factory made and tested. Finished in most attractive two-tone cabinets in blue/grey, red/grey or charcoal/grey with gilt trim. 200-250v, AC. £12.12.0.

Delivered free U.K. S.A.E. enquiries

**FREE** *INSIDE NEXT MONTH'S ISSUE*

ANOTHER "PRACTICAL WIRELESS"

24-page pocket guide to

## AERIAL DATA

*Packed with at-a-glance reference you'll use again and again, including:-*

**FORMULAE • CALCULATIONS  
DESIGN • OTHER DATA**

Sections on aerial designs for receiving and transmitting . . . half-wave, vertical, multiband and long wire aerials . . . folded dipoles . . . Yagi arrays . . . aerials for TV and u.h.f. . . . attenuator design . . . transmission line data . . . matching of aerials.



*Also in the December issue*

**BUILDING AN LCR BRIDGE  
TWO-BAND PHONE TRANSMITTER  
CORRECT EARTH SYSTEM  
SHORT WAVE CONVERTER**

**DECEMBER ISSUE on sale NOV 4th**

**MAKE SURE  
OF YOUR  
COPY!**

*Hand this  
Form to Your  
Newsagent*

TO \_\_\_\_\_ (Name of Newsagent)

Please reserve/deliver the December Issue of PRACTICAL WIRELESS (2/-) on sale Nov. 4th and continue until further notice.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

# on the Short Waves

## MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

### The Broadcast Bands—by John Guttridge

**Tunisia:** *Radiodiffusion Television Tunisienne* (139 Avenue de Paris, Tunis), gives full QSL details. English from 2200—2300 is often audible on 962.

**Cyprus:** BBC—East Mediterranean Relay has an English transmission from 1845—1900 on 9,580. After 1900 this channel carries a relay of the BBC World Service in parallel with 9,625 until close down at 2115.

**Iran:** *Radio Iran* (Ministry of Information, Meydan Ark, Tehran), keeps drifting around the 19 and 25 m.b. with its foreign service from 1730—2130 (English 2000—2030). Most reported outlets are 11,760/15,110, although 11,750, 15,135, 15,145 and 15,150 have also been reported. The clandestine station *Radio Peyk-e Iran* (Radio Free Iran), has been heard from 1500—1600 on 11,410/11,695.

**Iraq:** *Broadcasting Station of the Republic of Iraq* (Salihya, Baghdad), now has Arabic on 6,905 until 1930 when its foreign service starts with an English transmission. The latter is also on 6,030.

**Israel:** *Kol Israel*, now uses 9,725 to Europe and 9,009 to South Africa during its 2045—2115 English transmission. 9,625 has been dropped. Full QSL.

**Japan:** N.H.K., Tokyo, has replaced 11,940 by 6,140 for General Service transmissions from 2100—0030. Other frequencies used are 2100 and 2200 transmissions 9,605/15,195; 2300 and 0000 transmissions 15,105/15,425. The European service from 0615—0845 (English 0800) is on 15,135/17,875. Frequencies for the South Asian transmission at 1500—1630 (English 1525) are 7,195/9,525/9,765. Several new QSL's have been issued by this station.

**Korea (North):** *Radio Pyongyang*, has French from 2000—2100 on 6,540/7,580/9,875/11,750.

**Pakistan:** *Radio Pakistan* (71 Garden Road, Karachi 3), now uses 11,672/9,615 in English to Europe from 1945—2030.

**Taiwan:** *Voice of Free China* (New Park, Taipei), now uses 15,125 in its transmissions from 1530—1800. The English broadcast at 1530—1610 has been heard in the U.K. on this outlet.

**New Zealand:** New Zealand Broadcasting Corporation (P.O. Box 98, Wellington), gives full QSL.

**Canada:** Canadian Broadcasting Corporation (P.D. Box 6000, Montreal), has been using 17,820/15,320/11,720 for the English and French transmission to Europe from 2000—2150 during the summer but is expected to replace 17,820 by

9,630 during the winter. CHNS (Halifax) has been heard on 960 at 0330—0400.

**U.S.A.:** Armed Forces Radio and TV Service (250 West 57th Street, New York, New York 10019), uses 15,430/15,350/15,330 from 1330—2245. From 1800—2245 17,855 is used also.

Radio New York Worldwide (4 West 58th Street, New York City 19, N.Y.). English frequency utilization is 15,155 1200—1515; 15,310 1500 (1200 Saturday and Sunday)—2200; 15,440 1200—2400; 17,755 1800—2145; 17,880 1245 (1200 Saturday and Sunday)—1745; 11,790 1200—1515 Saturdays and Sundays. From 2200—2400 11,970 is also believed to be in use. Has formed a SWL Club, membership of which costs \$1 a year. Members will be offered QSL report forms in Spanish, German, French, Arabic and English; the use of a station identification bureau; a station address bureau and a monthly DX bulletin.

*Voice of America* (U.S. Information Agency, 330 Independence Avenue, S.W. Washington 25, D.C.), is transmitting to Europe as follows during the autumn: On 1,196 Munich 0400—0430, 0500—0700, 1600—1830, 2200—2330; 3,980 Munich 0300—0700, 1400—2330; 5,965 Tangier, 5,995 Greenville, 7,200 BBC and 7,270 0300—0700; 5,995 Tangier 1630—2330; 9,540 and 9,740 BBC 0430—0730; 9,760 1830—2245; 11,790 Tangier 0600—0730; 15,205 Greenville. 1400—2215; 15,290 Tangier 1400—2000; 15,295 Tangier 0600—0730; 17,780 Greenville 1400—1745.

**Windward Islands:** Windward Islands Broadcasting Service (St. George's, Grenada, W.I.), now uses 15,130 for its evening transmission to Europe.

**Argentina:** *Radio Belgrano* (Cerrito 941, Buenos Aires), has been heard over LR3 on 950 at 0330—0400 with a fairly good signal.

**Ecuador:** *La Voz de los Andes* (HCJB, Casilla 691, Quito), has been trying different frequencies for its evening European transmission. English 1845—2030, and Swedish 2030—2100 are on 17,890/15,105 and German 2100 and Spanish 2130—2200 are on 17,850/15,105.

**Austria:** *Osterreichischer Rundfunk* (Wien IV, Argentinierstrasse 30a) has a music programme for 2300—2400 on 9,770. There is an English transmission on Tuesdays and Thursdays at 1705 and every other Sunday at 1830 on 6,155/7,245. Also October 18 at 1230 on 6,155/7,245/9,770; October 22 at 1300 on 6,155/9,770; October 28 at 0920 on 6,155/7,245/9,770/11,785 and October 23 at 1700 on 6,155/7,245. Full QSL.

# Why

**NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS**

**BACKED BY OUR SUPER AFTER SALES SERVICE**

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans available separately at fixed prices stated. Overseas post 10/-



"Transona Five" size 6½ x 4½ x 1½ in. approx.


Covers M. and L. Waves and Trawler Bands, a feature usually found in only the most expensive radios. On test Home Light, 200, and many Continental stations were received loud and clear. Designed round super-sensitive Ferrite Rod Aerial and new type fine tone super dynamic 2½ in. speaker. Attractive plastic cases with red grille.

Total cost of all parts now only **42/6** P. & P. 3/6 (State type req.)
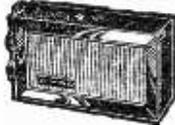
## TRANSONA 5 or POCKET 5

● 7 stages—5 transistors and 2 diodes

Covers M. and L. Waves and Trawler Bands, a feature usually found in only the most expensive



"Pocket Five" size 3½ x 1½ x 3½ in. Parts Price List and easy build plans 2/-

radios. On test Home Light, 200, and many Continental stations were received loud and clear. Designed round super-sensitive Ferrite Rod Aerial and new type fine tone super dynamic 2½ in. speaker. Attractive plastic cases with red grille.

Total cost of all parts now only **42/6** P. & P. 3/6 (State type req.)

## TRANSONA 6

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Ferrite rod aerial. Many stations listed in one evening, including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6½ x 4½ x 1½ in. (Uses PP4 battery, available anywhere.) Carrying strap 1/- extra.



Total cost of all parts now only **59/6** P. & P. 3/6

Parts Price List and easy build plans 2/-

## SUPER SEVEN

● 9 stages—7 transistors and 2 diodes



Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/-

Covers Medium and Long Waves and Trawler Band. The ideal radio for home car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 R.F. Stages push-pull output. 3in. speaker (will drive large speaker). Size 7½ x 5½ x 1½ in. (Uses 9v battery available anywhere.)

## NEW! ROAMER 7 MK IV

7 WAVEBAND PORTABLE OR CAR RADIO  
Amazing performance and specification

★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS  
● 9 stages—7 transistors and 2 diodes  
FULLY TUNABLE ON ALL WAVEBANDS

Covers Medium and Long Waves, Trawler Band and two short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned heavy "Crestion" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for 8 Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4 in. approx.



The perfect portable and the ideal car radio. (Uses PP7 batteries, available anywhere. Extra band for easier tuning of pirate stations, etc.)


Total cost of **£5.19.6** P. & P. 3/6 Parts Price List and easy build plans 3/-

## MELODY SIX

... amazed at volume and performance ... has really come up to my expectations."

S. G. Stockton-on-Tees.

● 8 stages—6 transistors and 2 diodes

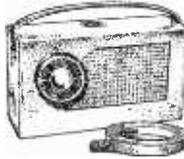

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board. 3in. heavy duty speaker, top grade transistor volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light. 200 and many Continental stations. Handsome speaker grille and supplied with hand and shoulder straps.

Leather-look pocket size case, only 6½ x 3½ x 1½ in. approx. with gilt Total cost of all **£3.9.6** P. & P. 3/6 Parts Price List and easy build plans 2/-

## NEW ROAMER SIX

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !! ● 8 stages—6 transistors and 2 diodes




Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long waves, Trawler Band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7½ x 5½ x 1½ in. Carrying strap 1/6 extra.

★ EXTRA BAND FOR EASIER TUNING OF LUX., ETC.

Total cost of all parts now only **£3.19.6** P. & P. 3/6 Parts Price List and easy build plans 2/-

## SPECIAL RADIO EXCHANGE BARGAINS

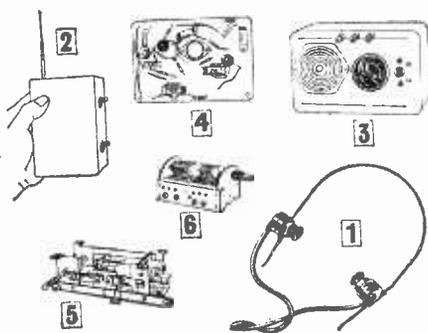

1. HEADPHONES. Sonotone H.S.30 High Fidelity Headphones. Made by famous American manufacturer. Approx. 150 ohms impedance for direct matching into most transistor circuits. BRAND NEW in original sealed cartons. 15/-, p. & p. 1/6. Matching transformers for higher impedance 2/6 extra.
2. THE SIG-GEN. A versatile Signal Injector. Something no constructor should be without. The ingenious device generates an audible signal through the Audio and R.F. ranges. With variable output. Telescopic Probe. Pocket size slim line case measures 4½ x 3½ x 1 in. Complete set of parts with full instructions. 19/6, p. & p. 1/6.
3. QUICK CHECK TRANSISTOR TESTER. Checks gain of R.F. and Audio Transistors. Also checks for noise level and diodes. All parts ready through the Audio and R.F. ranges. With variable output. Telescopic Probe. Pocket size slim line case measures 4½ x 3½ x 1 in. Complete set of parts with full instructions. 19/6, p. & p. 1/6.
4. 1200mW TRANSISTOR AUDIO AMPLIFIER. Designed to give high quality at low cost. This superb amplifier uses 4 transistors including a special power type operating from a 12-volt battery. Variable input impedance. Matches directly into 25-35 ohms loudspeaker. Special gain control circuit can also reduce noise to a minimum. All parts including transistors, printed circuit board, etc. 42/6, p. & p. 2/6. Easy build plans free with set of parts. 6 x 4 in. 35 ohm Speaker 12/6, p. & p. 1/6.
5. CYLON PERMEABILITY TUNERS. By famous manufacturer. Full M.W. coverage. Fitted coupling coil oscillator coil, ferrite slugs and slow motion tuning with cursor etc. GIVE AWAY PRICE 10/-, p. & p. 1/6. Switched type 2/6 extra.
6. TUNING CONDENSERS. Air spaced fine quality German manufacture with slow motion drive. 0.0005. With oscillator section. BRAND NEW! Only 6/8, p. & p. 1/6.

# RADIO EXCHANGE CO.

61 HIGH STREET, BEDFORD. Phone: 2367

Callers side entrance  
Barratts Shoe Shop  
Open 9—5 p.m.  
Sats. 10—12.30 p.m.




If you're thinking in terms of tape recording then the Brenell deck and complete recorders should be uppermost in your mind. The reliability, the versatility and the quality of manufacture are seldom equalled in other tape recorders (even in those costing much more).

**How many can equal or better this specification?**

- 4 record/playback speeds 1 7/8, 3 3/4, 7 1/2 and 15 ips
- 3 motors
- low 'wow and flutter' content
- double-gapped ferrite erase head to minimise erase noise
- narrow-gapped record/playback head to give extended frequency response
- pause control
- superimpose control
- 8 1/4" dia. reels
- fast rewind
- digital rev. counter.

**MARK 5  
Series 3  
Deck**

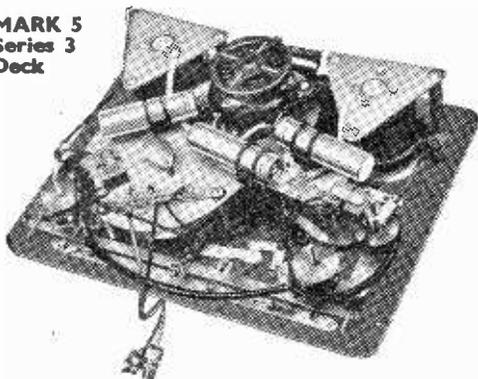

For details of the specially designed amplifier for use with the above deck and the range of mono and stereo recorders, write or telephone the sole manufacturers!



**BRENELL ENGINEERING CO. LTD.**  
231/5 Liverpool Road, London, N.1  
Telephone: NORTH 8271 (5 lines)

G.D.840

## RETURN-OF-POST

ON CASH OR C.O.D. ORDERS

### ● MARTIN AUDIO KITS

Complete transistorised Hi-Fi Pre-Amplifier and Main Amplifier comprising Unit 1. (Pre-Amp input selector). Unit 4 (Pre-Amp. with volume, bass and treble controls). Unit 7 10 watt Main Amplifier. 15 ohm output) Unit 8 (Power Unit) and smart plastic Escutcheon. All units are assembled and tested and the constructor has only to link the various units together. Full instructions supplied. Cash Price £15.8.0. Credit Terms. Deposit £2.2.0 and 12 monthly payments of £1.3.0. Total Credit Price £16.18.0. Stereo and other Mono Units available. Full list free on request.

### ● MARTIN FM TUNER KIT

Transistorised FM Tuner Kit for use with the above Martin Audio Kit and most other Amplifiers. Supplied ready assembled in unit form and tested. The constructor has only to link together and mount the units. Full instructions supplied. Cash Price £12.7.8. Credit terms Deposit £2.11.6 and 12 monthly payments of 19/4. Total Credit Price £14.3.6.

### ● LOUDSPEAKERS

	Cash Price	Credit Terms	Total Credit	
		Deposit	Payments	
GOODMANS Axiom 201. 15" 16 watts.	£11. 8.9	£2. 5.9	12 of 17/4	£12.13.9
GOODMANS Axiom 10. 10" 10 watts.	£6.12.4	£1.12.4	6 of 9/0-	£7.12.4
GOODMANS Axiotele 5. 8" 6 watts.	£5.10.11	£1. 7.11	6 of 17/8	£6.10.11
WB HF1012. 10" 10 watts.	£4.12.0 (Postage 4/-)	—	—	—

### ● LATEST TEST METERS

All the latest models from current production. Illustrated list available.

	Cash Price	Deposit	12 monthly payments	Total Credit
AVO 8, Mk. 3	£24. 0.0	£4.16.0	£1.16. 0	£26. 8.0
AVO Multimeter Mk. 4	£9.10.0	£1.18.0	14. 9	£10.15.0
Taylor Model 88B	£24.10.0	£4.18.0	£1.16.10	£27. 0.0
Taylor Model 187A	£10.10.0	£2. 8.0	16. 0	£11.15.0
TRC Model 500	£5.16.6	£1.16.6	14. 0	£10. 4.6

All Cash and COD orders are dealt with on day of receipt. Credit orders are subject to only the minimum of delay.

## WATTS RADIO (Mail Order) LTD

**54 CHURCH STREET, WEYBRIDGE, SURREY**

Telephone: Weybridge 47566

Please note: Postal business only from this address

## NEW ENLARGED EDITION

### of the popular GUIDE TO AMATEUR RADIO



An invaluable guide for those new to Amateur Radio. The book, which contains a wealth of interesting and helpful information, is great assistance in obtaining a transmitting licence.

Several new constructional projects have been added to this Eleventh Edition. The Guide has 88 pages, well illustrated with photographs, circuit diagrams etc.

Price 5/- (by post 5/6) and 80 cents post paid in U.S.A. and Canada.

Further details of other R S G B publications, information about membership of the Society, including a free copy of the monthly R S G B BULLETIN, and the book itself may be obtained from the publishers:

**RADIO SOCIETY of GREAT BRITAIN**  
Dept. PW, 28 Little Russell St, London, W.C.1.

## The Amateur Bands—by David Gibson G3JDG

**W**HAT a month. A colossal mailbag from just about everywhere on all frequencies. The 160 metre specialists are out in force and reports on all bands all modes have arrived from topband transatlantics to the v.h.f. n.f.d. which finished today. (I was on at 0300 hrs—no justice anywhere these days). **A. Botley** writes to say that ZB4 call signs are illegal, certainly up till 29.7.65. Alan's just returned from Cyprus where he was active under ZC4GT. Congratulations to **Alan Dailey** (Leeds) who got his ticket, call to listen for on 160 and 80 is G3UMH. L.F. DX news from **E. Rawlands** (Liverpool) 9M20V (Malaya) on 7Mc/s s.s.b. between 2130—2300. ZL2BCG (New Zealand) has skeds with G's on 3800kc/s 0530—0600 hrs. If they can hear him perhaps you can. OX3JV on 7Mc/s most nights, his QTH 600 miles from the N. Pole and running 600W.

### One Hundred and Sixty

If you've heard only G's on this band have another listen. **Alan Baker** (Welwyn) R107+PR30 60ft. long wire: times given for would-be topband DX hounds—GM3—EGW 2235, HUN 2125, KDT 2300, GW, 3NMZ 2200, 5BI 2330, OK—1KR1.2300, 3BU2230, OL3—ABD 2300, ABO 0300, PAØPN 2315 and 0950, VO1FB 0330, W1BB 0330.

A very interesting letter from **I. Ross** GM3TMK. Ian says that the 4U1—4U6ITU stations are on the band and have worked VO1FB in Newfoundland. Also on is K1LMO, VE3DM, and of course, W1BB. He says "Stew's" new antenna is a "big un". Inverted V 265ft. high at the apex. (Wonder what he uses on 28Mc/s?) 3TMK has worked W1BB, the Scilly Isles expedition, and VO1FBB, the latter on 18 occasions since last November. Ian's antenna is 260ft. long and 39ft. high and he's about 60 miles s.s.w. of John O'Groats. **Robert Nelson** (Nr. Blackpool) B34, 60ft. longwire, says he hears many mobiles up there. From further afield on phone GM3RYO, and GW3—HUM/M, MDK, NNF, TFN

### Eighty and Forty

Fared better this month and just shows what's about if you are prepared to search for it as opposed to 20 where "it" finds you.

**E. Rawlands** (Liverpool) 52 set 71ft. longwire, says "Good for W/VE after 2300 hrs", his best on s.s.b. K1NAC, K4LDR/M, VE1—MA, WH, VO1EL, W41NL, while on 40 the same set up raised MP4BAA, OX3JV, PY7AOT, YV5BPJ, at 58 too. ZS1JA, ZS1KJ, 4X1DK, 5A2TR. **G. Watson** (Sheffield) reports hearing over 200 G, GC, GI, GW stations on 80 since April, with only ½ in. bandspread on his transistor portable, while **Chris Woodrow** (Norwich) tells of almost a worldwide net on 7015kc/s with GW3AX and many DJ's, DL's, ON's, OH's and a Zs. Chris also logged a fine signal from VK2KM and 4X1DK. **P. Edwards** (Birmingham), Hammerlund comet, pre-selector, 33ft. longwire, started quietly on 80 with DL1FI, F2WS, GD3RFK, and SM5ABO when

who should come in but EA9AZ, K1GXU/P/7, W9JLH, YV5BPJ, ZP5—KT, OG.

Expensive gear isn't necessary for DX. A three valve t.r.f., 132ft. longwire, and **Steve Wilson** (Nr. Wakefield) between the headphones August 1st—4th. CP5EZ, CX3JV, KØBAT, K4NET, K7PDZ, OA4SE, OY7X. (Faroes), PY5UL, TF2BR, VE3BLU, WA—1NOJ, 2SHK, 4PUB, 8FFO, W5—MCO, JXC, XE1DD, YV5—BK, CET, ZP5CF all c.w. on 40, Vy fb OM.

"40 opens up around 0030 hrs", so states **M. Jolley** (Stafford). 19 Set, 66ft. longwire, numbers are standard r.s.t. to show just how they're coming in. HR1FD 569, K1LPL 579, K3JIG 579, PY1CJL 569, VE3FTM 449, VK8KA 559, VO1HS 569, VP6AK 559, 4X4NVE 449, 4X5VB (Israel?), 5X5UD 569. **R. Hall** (Worksop). SX28, PR30, 80ft. of 14s.w.g. HK—4EB, 41X, 7X1, LU3BLK, VE—2NI, 7AC, WA5KAI.

### Royal Twenty

Yes royal, because it's hard not to hear the distant ones. Almost misery to try local working because the Europeans are blotted out by the DX. Well, not quite, but take **Bob Garvey** with his trusty S640 and 90ft. longwire, the result is CN8BW, CO2JB, CP5EZ, CR3AD (Portuguese Guinea), CR—4BC, 6CH, FG7XS, FM7WP, HK3RQ, HP1PV, K5AEU, KG4AN, KH6DQ, KZ—5AY, 5BC, LU4AA, LX1AN, OH2AM/OHØ, TF3EA, UB5ARTEK, VE3AR, VK6WT, VP3AC, VS9OG, VU2CO, WA5IZT, W6CYV, YAØH (Gus Browning), ZB2AM, ZC4TX, ZS5UP, 7X2AP, 9J2W, 9M2BM, 9M4ML, B. Wilde (Wirral) 52 Set, ground plane CT1NL, EP2TF, HZ1AB, K2CAP, PY7ABW, VE2BL, VK6XXX, W2MM, 4X4HJ, 5A1TK, 7Q7PBD, 7X2MD, 9M4MX.

**Stephen Beal** (N.10) t.r.f. 66ft. indoor antenna as per P.W., May 1964, HB9, K—1, 2, MP4, W—2, 3, 4, 6, YA4, 4U1, **Martin Davies** (Alnwick) 52 Set, dipole, all a.m. or s.s.b. HC, HK, HV, JA, KA3, LU, OHØ, OX4, PJ2, PZ1, VE3/P, VK9, VO1, VP2, VP7, W5, XE1, YV1, 3A8, 5R4, 9Q5. **Jim Dunnett** (Royston) Raca1 RA17, 60ft. longwire, c.w.—CO2, CP5, CR6, KH6, KL7, KP4, KZ5, MP4, PJ3, SL6, UH8, VS9, 6Y5/P, 7X3, 9M4, 9M6, 9Q5, s.s.b.—EA6, EPZ, FG7, HB9/P, KZØ, KZ5, 9H3, 9Q5. **I. Black** (Gillingham) HE30, window frame (I wondered how long it would be). CN8, EL8, ET3, FG7 (Guadaloupe), FM7 (Martinique) HS1 (Thailand), KA6, KG4, LA8 (Jan Mayen Is.), PJ1 and 2, VP2, VS6, ZB2, 4X4, 5A4, 5Z4, 6Y5, 7Q7, 7X2, 9M2, 9M4, 9Q5.

### Fifteen and Ten

Poor old 15, so popular a few months back, isn't getting much attention these days. Exceptions to the rule—**G. Wood** (Grimsby) AR88D, PR30, 2-ele. beam or quad, all phone—CE3QB, CR—5SP, 6EP, 7FM, EA3HL, EL8D, HB9FU, HC1DM, IT1DJ, KV4CX, KZ5AY, OA5C.

—continued on page 618

by *R. F. Farley, G3SSJ*

# A Thumbnail History of Radio

## PART 2: FROM SPUTTERING SPARK TO SPOKEN WORD

**I**N 1901 the Marconi Company began installing spark stations in ships. The detector was still the coherer but many experiments were being made to improve its efficiency. Particularly notable were those of Chunder Bose, of Calcutta, who found that potassium would decohere without tapping. Unfortunately the potassium proved vulnerable to oxidation and had to be used in a vacuum or under paraffin oil.

During the same year P. Castelli, of the Italian Navy, invented a greatly improved detector of the coherer type. It consisted of a glass tube containing a globe of mercury between two electrodes of polished copper. The spacing between the electrodes could be adjusted by a micrometer screw. This coherer decohered automatically in the absence of signals and this eliminated the cumbersome tapping mechanism.

### Trans-Atlantic Tests of 1901

For the transatlantic tests of 1901 between Poldhu and Newfoundland a power of 20kW was used. Dr. Ambrose Fleming (later Sir Ambrose Fleming) was in charge of engineering design. Fleming is perhaps best known for the invention of the thermionic diode but he was without question one of the first great wireless engineers.

The transmitter at Poldhu was an a.c.-operated set, using an alternator in conjunction with a transformer to power the spark. It is claimed that this was the first time that this method was used but De Forrest also used it in America during the same year and American historians claim that he was the first to use a.c. power.

The great advantage of this method was that the troublesome primary circuit interrupter of the d.c.-powered spark coil was eliminated. The Poldhu transmitting aerial consisted of a large inverted cone, 200ft high, supported between four towers. The receiver in Newfoundland consisted of a Castelli mercury detector used in conjunction with a telephone receiver, together with an aerial tuning inductance and an aerial and earth system. The aerial was carried aloft by a kite à la Loomis. Tuning had been introduced by Sir Oliver Lodge in the 1890's and was now becoming universally adopted.

Although the world was astounded by the results of these tests they were only of experimental value; the received message consisting of the single letter "S" in Morse code, i.e. three dots. Even these were hardly distinguishable from the high background of static; in fact some sceptics suggested that Marconi and his assistant, Kemp, had imagined they heard it. Marconi's

prestige was, however, high and among those who believed his claim was the inventor, Edison.

Shortly after these tests signals were picked up on the American liner "Philadelphia" from a source 2,000 miles away. The world was awakening to the possibility of world-wide wireless communication, but it was not until the development of continuous wave transmission that reliable transatlantic communication was realised.

### Spark Stations Open

The next few years were to witness the opening of a number of high-powered long-distance spark stations. Notable among these were the German stations at Nauen and Nordeich. The French station on the Eiffel Tower was transmitting regular time signals and was heard throughout Europe.

Perhaps the most famous of the great spark stations was that built by the Marconi Company at Clifden in Ireland, although the site is now better known as the place where Alcock and Brown crash-landed in 1919. Clifden was powered by a 15,000V bank of accumulators which were kept charged by three generators connected in series and powered by a steam engine. The cells were used to charge a huge condenser through series resistor. The condenser discharged through a rotary spark gap via the primary winding of the aerial transformer or "jigger" as it was then called. The power drawn from the cells was 300kW and the sparking rate was 500 per second.

### "An Exciting Rescue at Sea"

In 1908 the newspapers carried accounts of an exciting rescue at sea in which wireless had played an important part. On a foggy January night the steamship "Florida" collided with the "Republic". The "Republic's" hull was badly damaged and she began to sink. Her Marconi operator was an Englishman, John R. Binns. He began calling CQD, which was then the distress call. The ship's lighting system had failed but fortunately the transmitter continued to operate (probably from batteries).

The call was received by a station in Massachusetts, the land operator there then notified several other ships in the area and all aboard were rescued. When Binns landed he was astonished to find the dockside crowded with cheering people; he had become a hero overnight.

It is almost certain that the CQD of Binns was

—continued on page 617

**Brand new individually checked and guaranteed VALVES**

AC/BL 4/6	DL84 5/9	EF80 5/7
AC74 6/1	EF81 6/1	EF81 6/1
AC/CPEN 9/7	DL810 8/7	EF85 4/6
AL60 5/1	DL819 15/7	FR86 6/6
ARA 5/7	EB80 23/7	FR89 3/9
ARP3 3/7	EB8CC 12/7	FR91 2/9
ARP12 2/6	E90CC 10/7	FR92 2/7
ARP24 2/6	EF148 3/6	FR95 5/7
ARP34 2/6	EL1265 50/7	EF183 8/7
ARTP1 6/7	EL1415 30/7	EF184 8/7
ATP1 2/3	EL1524 12/6	EBF11 300/7
AV77 5/6	EL17 4/7	EL32 3/9
AU7 55/1	EL171 7/7	EL34 10/7
B9H 15/6	EACB80 5/7	EL36 5/7
BD78 4/0	EA91 3/6	EL38 17/6
BL63 10/7	EAF42 8/7	EL41 3/7
B81 8/7	EB84 1/6	EL42 5/6
B85 20/7	EB91 3/7	EL50 8/7
B884 37/6	EB83 6/7	EL41 8/7
B2134 1/6	EB041 7/7	EL83 6/3
BT19 25/7	EB081 5/7	EL84 3/7
BT83 25/7	EB780 5/7	EL85 8/7
BT43 150/7	EB883 6/7	EL84 4/6
BT83 35/7	EB889 6/9	EL85 5/7
CC3L 2/7	EC52 4/7	EL350 20/7
CL33 9/7	EC68 12/6	EM80 5/7
CV71 3/7	EC70 4/7	EM81 6/7
CV77 9/7	EC90 4/7	EM82 6/7
OV102 1/7	EC91 3/7	EM85 9/7
CV108 4/7	EC081 4/7	ENR1 10/7
CV4004 7/7	EC082 5/7	ESR174 80/7
CV4014 7/7	EC083 3/7	ESR1908 6/7
CV4015 7/7	EC084 5/6	EY51 5/6
CV4025 10/7	EC085 6/6	EY86 6/6
CV4044 4/7	EC088 9/7	EY91 3/7
CV4049 6/7	EC091 4/7	EZ40 9/7
CV81 6/6	EC81 6/7	EZ80 6/7
D1 1/6	EC842 8/7	EZ80 6/7
D41 6/7	EC851 8/7	EZ81 3/6
D61 6/7	EC888 7/6	FV0057 5/7
D77 3/8	EC180 6/7	FV0061 5/7
DA30 12/6	EC192 7/6	FV020 6/7
DAF96 6/7	EC188 10/7	FW4600/6
DD41 4/7	EC186 10/7	FW4808/6
DE75 6/7	EF36 3/4	GI1230/6
DE720 2/7	EF37 7/7	GI571K19/7
DE725 15/7	EF39 6/7	GM20 6/7
DF78 5/7	EF90 2/6	GM02/M15/7
DF91 3/7	EF82 6/6	G14 65/7
DF92 8/7	EF83 4/6	GZ82 10/7
DF96 6/7	EF85 3/7	GZ83 10/7
DL92 9/7	EF71 6/7	GR8 10/7
DL96 5/6	EF72 6/7	HK54 22/6
DL97 5/6	EF73 5/7	HLK2 8/6
DL98 8/7	EF74 4/7	HLR2 6/7

HL23DD 5/7	QP21 6/7	VU33A 4/7
HL41 4/7	QP25 5/7	V139 6/7
HYR2 9/7	QP230 5/7	VX3256 4/7
KNA 30/7	QG160 10/7	VX4122 5/7
KTC8 22/7	QR80 10/7	WX1234 5/7
K732 8/7	QR85/10 5/6	W145 5/7
K734 6/7	QR1202 8/7	W118 8/7
KT44 5/9	QV047 8/2	W119 8/7
KT78 2/7	RS 8/7	X66 7/6
KT85 12/9	RG4/1250	X113 8/7
KT87 6/7	SP41 1/6	Z800 20/7
KV76 8/6	RK72 6/7	Y68 5/7
KT88 8/6	SL30 15/7	Y69 4/7
KTW61 4/6	SL30 12/6	Y66 8/7
KTW63 2/7	SP2 8/7	YF 1/7
KTW64 6/7	SP4 1/6	Z800 20/7
KTZ63 5/7	SP61 1/6	Z801 10/7
MR100 9/7	SP210 3/6	IAS 3/6
MR142 12/7	STV280/40	1A5GT 5/6
MR161 7/7	1B22 30/7	1A6GT 2/6
MR41 5/7	SU150/4	1K5GT 7/6
MHLD810/7	10/7	1D8GT 6/7
ML6 6/7	T41 6/6	1D7G 7/6
N78 15/7	TP22 5/7	1P2 3/6
NE17 7/7	TP25 15/7	1P6GT 8/7
OB3 3/7	TP11 6/6	1L4 6/6
OD3 7/7	TT15 35/7	1A4 6/6
OD5 5/7	TRR31 45/7	1L6C 7/6
OZ4A 5/7	TZ0520 4/7	1N14 4/7
PC84 5/7	TZ20 18/7	1N2B 4/7
PC85 5/7	U81 30/7	1R43 4/7
PC89 10/7	U12/4	1R44 4/7
PC89 6/6	U17 5/7	1R4 5/7
PCF82 6/6	U18 6/7	1R5 3/6
PCF84 6/7	U25 11/7	1R4 5/7
PC85 6/7	U27 8/7	1R5 4/6
PC86 6/7	U28 4/6	1T4 2/7
PC87 8/3	UAC080 5/6	2A8 5/7
PC88 7/7	UBC41 6/7	2A5 6/7
PC85 8/7	UBF80 5/6	2B26 3/6
PC86 6/6	UBF89 6/6	2C26 7/6
PC87 6/6	UL21 11/7	2C26A 3/6
PEN25 4/7	UCC45 6/6	2C34 2/6
PEN46 3/7	UCC42 6/6	2C43 12/6
PLN200A/3/7	UCH81 6/7	2C45 22/6
PLN36 7/7	UCL82 9/7	2C46 30/7
PL81 7/7	UCS3 10/7	2C51 12/6
PL82 6/7	UF41 7/7	2D21 5/6
PL83 6/7	UF89 6/7	3A2 3/6
PL84 6/7	UL41 6/7	3A3 4/6
PL85 6/7	UL84 5/6	3A105A/6
PL86 6/7	UL85 7/6	3A463 38/7
PT15 10/7	U09 8/6	3A167/3/6
PT25H 7/6	UY21 7/6	3B7 25/7
PT25M 7/6	UY25 5/7	3B7 25/7
PX4 14/7	W1120 4/7	3B24 5/6
PX25 6/7	W1607 5/7	3B28 15/6
PY38 5/7	W1924 80/7	3D6 4/6
PY80 5/6	WMP45 12/7	3E29 50/7
PY81 5/6	VP22 3/7	3Q4 6/6
PY82 5/6	VP153 9/7	3R7 7/6
PY83 5/6	VR99 8/7	384 4/7
PY800 6/7	VR105/305/7	3V4 5/9
PZ1-35 9/7	VR150/305/7	4C27 35/7

4D1 4/7	6F14 6/7	9D6 3 8 57	6/7	8066 6/7
5A173G 5/7	6F22 4/7	1A26 2 6 58	6/7	6080 22/7
5A174G 5/7	6F38 3/7	1A26 5 9 59	6/7	7193 1 9
3B231M 25/7	6G66 2/6	12A8H 11 7 73	5/6	7475 9/7
3B234M 40/7	6H83 6/7	12A77 4 6 78	4/6	8013 25/6
3B235M 55/7	6H4W 10/7	12A17 5 7 77	7/6	8030 3 6
6R4Y 9/7	6J5 6/7	12A7 6 7 78	5/6	9001 3 7
6T4 7/7	6F5G 2/7	12A17 10 8 80	5/6	9902 4 6
5U4G 4/6	6J8 3/6	12B4G 5 7 81	9/7	9003 6/7
5V4G 3/6	6J9 3/6	12B5E 7 7 82	3/6	9004 2 6
6B34M 40/7	6I7G 5/7	12B87 6 7 84	8/7	9008 2 6
6V8G 4/7	6J7M 8/7	12D8 3 7 85A2	8/7	
5V8GT 5/6	6K6GT 5/6	12B6 2 7 210VPT	2/6	
5V3WGTB 6K7G	6K7G 2/6	12B6GT 2 6 7-pio	2/6	
6Z4G 6/6	6K7GT 4/6	12K7GT 6 6 80P A	4/7	C.R. Tubes
6K8G 3/7	6K8GT 3/7	12K7GT 5 7 220T A	7/7	CV180 6/7
6K8GT 3/6	6K8GT 3/6	12K9M 10 7 225DU	9/7	(OR1) 55/7
6B6 6/6	6K8M 6/6	12Q7GT 3 3 307A	5/6	E4504/B16
6A7 6/7	6L5G 6/7	12M47 7 7 310C	26/7	VCR97 26/7
6A9G 2/6	6I8G 6/7	12B87 4 7 350B	6/7	VCR138 6/7
6A7 6/7	6L6GA 7/6	12B87 3 7 357A	7/7	VCR139 4/6
6A6H 10/7	6L8M 11/7	12B87 3 7 386A	5/6	VCR139A 30/7
6A17 3/7	6L7G 4/6	12B87 5 7 399A	10/7	VCR139B 30/7
6A5 6/7	6L34 4/6	12B87GT/7 446A	3/6	VCR139C 40/7
6A67 6/7	6L2D0 5/6	12B87GT/7 468A	3/6	VCR139D 40/7
6A7 6/7	6L7G 5/6	12B87GT/7 478A	3/6	VCR139E 40/7
6A7G 6/7	6N7G 6/7	12B87GT/7 515B	6/6	VCR139F 40/7
6A65 2/6	6Q7G 6/7	12Y4 2 7 717A	3/6	
6A65 4/7	6R7 6/7	12L7 7 7 724A	15/6	3BP1 30/7
6A7 6/7	6R7 6/7	12D2 8 6 801	6/7	3FP37 40/7
6A7G 6/7	6A7GT 6/7	19E2 12 6 802	8/6	3P37 40/7
6A8G 4/7	6K8GT 4/7	19G3 10 6 807	8/6	5PC1 30/7
6A88W 9/6	6K8GT 7/7	19G8 9 6 808	8/6	5FP7A 12/6
6A87G 2/6	6K8GT 6/7	19G7 5 6 811 17/6	6/7	
6A7G 3/6	6K8GT 6/7	19H1 6 6 813	6/6	Photo Tubes
6A7 6/7	6A7GT 6/7	19M16 7 6 814	6/6	CMG8 5/6
6A7 6/7	6A7 6/7	5 20P 14 8 829A	30/7	OR16 12/6
6A7 6/7	6B7 6/6	6B7GT 6 6 218A	9/7	829B 5/6
6A7G 6/6	6B7GT 6/6	515L6GT 6/7	8/6	829C 5/6
6A7 6/7	6B7GT 6/6	521G 6 6 829A	46/6	829D 5/6
6A7GT 6/6	6B7GT 6/6	525G 7 6 833A	21/6	Valves
6A7GT 6/6	6B7GT 6/6	526GT 6 6 838A	8/6	ACT6 88
6A7GT 6/6	6B7GT 6/6	2 25D 7 6 864	14/6	E301 84
6A7GT 6/6	6B7GT 6/6	8 80 6 6 864	10/6	1KN2A 24
6A7GT 6/6	6B7GT 6/6	30C15 6 6 864	10/6	86 10.0
6A7GT 6/6	6B7GT 6/6	30F5 6 6 955	2/6	1B24 25/6
6A7GT 6/6	6B7GT 6/6	30F6 6 6 955	2/6	2J22 12.10.9
6A7GT 6/6	6B7GT 6/6	30F7 6 6 955	2/6	2J24 23
6A7GT 6/6	6B7GT 6/6	30F8 6 6 955A	4/7	411A 20/6
6A7GT 6/6	6B7GT 6/6	30F9 6 6 955A	4/7	3792A 6/6
6A7GT 6/6	6B7GT 6/6	30F10 6 6 955A	4/7	437.10.6
6A7GT 6/6	6B7GT 6/6	30F11 12 6 955A	4/7	714Y 4/6
6A7GT 6/6	6B7GT 6/6	30F12 12 6 955A	4/7	728A 30/6
6A7GT 6/6	6B7GT 6/6	30F13 12 6 955A	4/7	789A 10/6
6A7GT 6/6	6B7GT 6/6	30F14 12 6 955A	4/7	2051 5/6
6A7GT 6/6	6B7GT 6/6	30F15 12 6 955A	4/7	4048C 13/6
6A7GT 6/6	6B7GT 6/6	30F16 12 6 955A	4/7	4093 3/6
6A7GT 6/6	6B7GT 6/6	30F17 12 6 955A	4/7	4313C 8/6
6A7GT 6/6	6B7GT 6/6	30F18 12 6 955A	4/7	5704 9/6
6A7GT 6/6	6B7GT 6/6	30F19 12 6 955A	4/7	5726 8/6
6A7GT 6/6	6B7GT 6/6	30F20 12 6 955A	4/7	6060 8/6
6A7GT 6/6	6B7GT 6/6	30F21 12 6 955A	4/7	6064 7/6

MANY OTHERS IN STOCK include *Guinde Ray Tubes and Special Valves*. All U.K. orders below £1. P. & P. 1/- over £1. 2/- over £3. P. & P. free. C.O.D. 2/6 extra. Overseas Postage extra at cost.

**MARCONI COMMUNICATION RECEIVERS CR. 150.** Frequency coverage 2-60 Mc/s in 5 bands. Two lfs 1st 1,600 kc/s. 2nd 463 kc/s. Image signal protecting over 40 dB up to 30 Mc/s and 20-40 dB from 30-60 Mc/s. Self-checking calibration (built-in calibrator) Stabilisation of supply and temperature compensation. Electrical and mechanical indicator Bandpass from 100 c/s to 10 kc/s bandspread. Metering and visual tuning in 5 stages. Acoustic filter associated with 100 c/s. Bandpass position for CW reception. Facilities for diversity reception. Excellent checked condition. £39. Mains P.S.U. by P.C. Radio £4.10.0 Carriage 30/- CR.150/2. Frequency coverage 1.5-22 Mc/s in 4 bands, all other features as in CR.150. Price £31. Carriage 30/-.

**P.C. RADIO'S mains P.S.U.** for above. 90/-.

**H.R.O. SENIOR TABLE MODEL** in excellent, fully checked and tested condition together with set of 9 general coverage coils and mains P.S.U. £28. Carriage and Packing 30/-.

**ORIGINAL MAINS POWER SUPPLY UNIT FOR H.R.O. RECEIVER** 260/115v. Brand New 65/- P. & P. 5/-.

**VERY HIGH CLASS COMMUNICATION RECEIVER TYPE BR 402E.** 150 kc/s-385 kc/s., 515 kc/s-30 mc/s. Fully tested £60. Carriage 30/-.

**EVERSHED MEGGER CIRCUIT TESTER.** 2 ranges 0 to 1,000Ω, 100Ω to 200,000Ω. With test leads, leather carrying case. Tested £4.19.6. P. & P. 3/6.

**PANEL METERS (round)**

500mV	3 3/4	DC	32/6
500mA	2 3/4	DC	25/6
500 microamp	2 3/4	DC	19/6
0-500 microamp	2 3/4	D.C.	15/6
0-500 microamp.	2 3/4	D.C.	12/6
0-1 mA	2 3/4	D.C.	12/6
25-0-25 mA	2 3/4	D.C.	45/6
150-0-150 mA	2 3/4	D.C.	29/6
0-500 mv	3 3/4	D.C.	32/6
0-5 v	3 3/4	A.C.	22/6
0-15 v	2 3/4	A.C.	17/6
0-50 v	2 3/4	D.C.	28/6
0-150 v	2 3/4	A.C.	24/6
0-10 kv	2 1/4	D.C.	63/6

\*Protection type.

**2 KW ULTRASONIC GENERATOR** together with power supply unit for 200-250v. A.C. Complete two chassis with interconnecting cables. Frequency 37 to 43 kc/s adjusted by fine control. Peak output 2kw, average output 500w. Completely new with valves and manual £65. Carriage paid U.K.

**ARR88 METER** for No. 19 set. 17/6. P. & P. 3/-.

**ARR88 RECEIVERS.** Fully reconditioned. £55. rebuilt models £85. Carriage paid U.K.

**THERMAL PLUS MECHANICAL CIRCUIT BREAKER FOR A.C. & D.C.** Current 1 amp. Protects against shorts (instantaneous cut-out at approximately 8 amps) and against overloads: 1-8 amp 30 seconds, 2-amp 15 seconds, 2-5 amp 6 seconds. Delayed cut-off may be adjusted to different currents and times. Separate pair of contacts to indicating device. Dimensions 3 1/2 x 1 1/2 x 1/2 in. Price 12/6. P. & P. 2/6.

**WELL PROVEN RELIABLE COMMUNICATION RECEIVER P.C.R. (Made by Pye).** 120 kc/s-350 kc/s. 525 kc/s-1600 kc/s. 6 Mc/s-22 Mc/s. Overall sensitivity 1-2µV. S/Noise ratio 10 db at 6µV. Circuit incorporates an RF stage - two I.F. stages, lone control. A.V.C. antenna trimmer. 6V6 output. Set in as new condition together with headphones built in speaker, enough chassis space to build in internal power supply. £8.15.0. Carriage 15/-.

**A.R. 88 INSTRUCTION MANUALS.** 20/- P. & P. 2/6.

**TELEPHONE HANDESET.** Standard G.P.O. type, new 12/- P. & P. 2/-.

**WIRELESS SET NO. 52 (CANADIAN)** Complete station consisting of Transmitter. Receiver. supply unit for 12 v. All contained in special carrier. 1-75-16 mc/s in 3 bands. 813 as output valve. 45-75 w. phone and MCW, 70-100 watt CW. M.O. or crystal. Receiver includes crystal calibrator. Tx can be exactly tuned to Rx frequency. Noise limiter Sidetone. Loudspeaker on receiver with on/off switch. All brand new with accessories. Export. Price on application.


**P.C. RADIO LTD**

170 GOLDHAWK ROAD W.12.

Shepherd's Bush 4946

Open 9-9.30 p.m. Thursday 9-1 p.m.
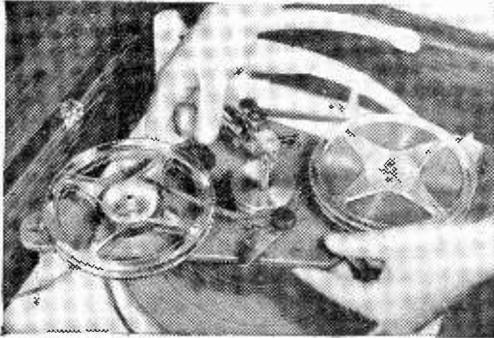
# STOP PRESS NEWS! A FABULOUS OFFER FROM GRAMDECK!



**1** The famous Gramdeck, complete with accessories and the Gramdeck Transistorised Pre-amplifier/Control Unit, delivered to your home

FOR ONLY **£6.10.0.**

**2** The famous high-quality, moving-coil Lustraphone microphone (value £3.7.6.)

## FREE WITH EVERY ORDER

- ★ Uses standard tapes.
- ★ Plays at 7½" per sec. or three other speeds.
- ★ Records direct from radio or microphone.
- ★ Erase and fast rewind.

The Gramdeck will turn any record player, radiogram or hi-fi system into a first-class tape recorder. And it's as easy as putting on a record. Brilliantly designed, beautifully engineered, the Gramdeck's performance will astonish you, giving you a quality of reproduction determined only by your existing equipment.

Gramdeck is a 'must' for the man who likes to experiment—for anyone who wants full recording and playback facilities at a fraction of the normal cost. And it's now offered to you at a sensationally low price—together with a FREE high-quality moving-coil microphone (List price £3.7.6.). Limited numbers available—cash orders only. Send only £6.10.0. and the outfit, together with your free Lustraphone microphone, will be sent direct to your home. Money gladly refunded if you are not delighted.

Rush your order now to . . .

# GRAMDECK

ANDREW MERRYFIELD LTD.

(Dept. PA/822) 29 Wrights Lane, London W.8.

FOR VALVES - SEMI CONDUCTORS - METAL RECTIFIERS



NEW 1965/6 CATALOGUE  
NOW AVAILABLE

56 PAGES SEND 1/- in stamps  
FOR YOUR COPY

### SEMI CONDUCTORS


AC154	5/6	MAT120	7/9	OA202	4/-	OC71	4/3
AC155	4/-	MAT121	8/6	OA2203	7/6	OC72	5/6
AC156	5/6	NKT404		OA2204	7/6	OC75	5/6
AC157	7/-	(OC35)	10/-	OA2207	7/6	OC81	5/6
ADT140	15/-	OA5	6/-	OA2208	5/6	OC83	4/-
ASY28	6/8	OA10	6/6	OC42	6/-	OC139	8/-
BY100	7/6	OA70	2/-	OC43	9/-	OC170	6/-
BY114	5/-	OA79	2/-	OC44	5/-	OC170	6/-
MAT100	7/9	OA81	2/-	OC45	5/-	OC200	7/6
MAT101	8/6	OA200	3/6	OC70	4/6	OCP71	25/-

### VALVES

DK96	8/6	EF80	5/9	PCL83	10/-
DF96	7/3	EF86	8/-	PL81	8/6
DAF96	7/6	EY51	8/-	U25	10/-
DL96	8/-	EY86	8/6	U26	12/6
ECC81	5/-	PCC84	7/9	UCL82	9/6
ECC82	5/6	PCF80	7/9	UCL83	11/6
ECC83	6/-	PCL82	9/3		

**ALPHA RADIO SUPPLY CO.**  
103 LEEDS TERRACE, WINTOUN ST,  
LEEDS 7.

### EX-RENTAL TELEVISIONS

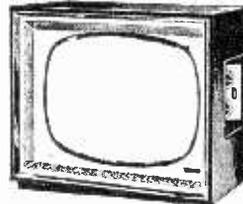

14 in. £7.10.0  
17 in. £11.10.0  
12 months 3 star Guarantee  
★ Tube ★ Valves  
★ Components  
Coloured FREE LIST  
Channels for all areas  
Demonstrations daily  
from our  
large selection  
Personal collection or  
Insured Carr.,  
14in. 20/-; 17in. 30/-

### ONE YEAR GUARANTEED TUBES

100% REGUNDED  
Add 10% or old tube. 21 in. 99/6  
All 110°-99/6 + 30% refundable on 17 in. 79/6  
OLD TUBE. Carr. 15,14  
10/6.  
14in., Slimline 17 and 19 inch. 59/6  
Export Postage 30/- 12 in.



### EX-MAINTENANCE TESTED TUBES

17in.—35/- Most makes and types available. 14in.—15/-  
Guaranteed good picture. Carriage 5/- extra.

TELEPHONE  
HANDSET  
15/6

pair  
G.P.O. pattern, Home to  
Workshop, Garage, Inter-  
Office, etc. Works off any  
small battery. P. & P. 4/6

VALVES £1 per 100. Assorted T.V. and Radio.  
Supplies ex-rental dismantled receivers. Post  
4/6. Send for list.

CONDENSERS 10/- per 100. New Assorted  
Electrolytics and P.F.s. P. & P. 2/6.

RESISTORS 5/- per 100. New. Mostly High  
Stabs. Assorted. P. & P. 2/-. Overseas 3/6.

SPEAKERS 7/8. 6in., 8in., 7 x 4in., 8 x 3in.  
Ex-mtd. salvage. P. & P. 2/3 Overseas 4/-.

Phone  
Il.Ford  
6001/2/3

**DUKE & CO. (LONDON) LTD.**  
621/3 Romford Road, Manor Park, E.12  
Liverpool St.—Manor Pk.—10 mins.

Stamp  
For Free  
List

### Thumbnail History of Radio

—continued from page 614

not heard directly by the ships in the vicinity due to skip effects. Heaviside had already published his theory about the reflecting layers above the earth but it was treated with scepticism. In 1912 the theory was expanded by Dr. Eccles, of the Marconi Company, and this time caused a storm of controversy.

The value of wireless was probably emphasised most strongly by the part it played in the "Titanic" disaster of 1912. There followed a sharp increase in the number of licensed stations and it became necessary to establish the first International Radio Telegraphic Conference. As a result it became international law that all vessels of a certain size should carry wireless installations and trained operators.

Meanwhile much had been done to improve the efficiency of the spark transmitters. Ionisation was a frequent source of trouble with the early spark gaps. When this occurred damped oscillations from the primary circuit of the spark coil were fed into the aerial circuit.

The contacts of the primary interrupter also tended to become pitted so that the general tone (which in any case was low pitched) was wavery. This was overcome by the introduction of the synchronous rotary gap in which a number of interrupter and discharger electrodes were evenly spaced circumferentially on two insulating discs. These were rotated on a common shaft.

In marine installations the equipment was required to operate from the ship's d.c. main supply. A.C. power for the spark was usually derived from a motor generator set used in conjunction with a transformer having a synchronous gap mounted on the generator shaft. An input frequency of 500c/s would give a steady sparking rate of 1kc/s which was easily identified through the high static on marine frequencies.

### Marconi's Chief Competitors

The German Telefunken Company were Marconi's chief competitors and produced the ultimate in spark transmitters. A German physicist, Max Wien, invented the quenched spark gap, which was highly efficient because of its superb heat dissipation.

In 1906 Colonel Donwoody invented the carborundum crystal detector. Other crystal detectors soon followed and were commercially produced. The Fleming diode was patented in 1904 but was little used.

The Marconi magnetic detector was very popular in ship installations on account of its reliability, although its efficiency was lower than that of the crystal detector. It consisted of an endless band of soft iron wire which passed through a coil carrying the received current. A secondary coil was wound over the primary coil and connected to a pair of telephone receivers.

A magnetic field was provided by two powerful horseshoe magnets and the iron band was kept moving by an arrangement of two wooden pulleys and a clockwork motor which the operator had to rewind every half-hour or so. Due to hysteresis

effects in the iron wire a rectifying action took place.

It was first devised by Rutherford in 1895 but the popular version was greatly improved and patented by Marconi in 1903. It was finally ousted by the thermionic valve during the First World War.

Experimental work with wireless telephony had been going on since the turn of the century. The spark transmitters generated damped waves at a recurrence frequency of about 1kc/s at the most and were, of course, useless as carriers for speech frequencies, having a spectrum of from 300 to 3,000c/s.

A Danish engineer, Valdemar Poulsen, developed a d.c. arc for use as a continuous wave generator. It was with this device that R. A. Fessenden transmitted speech over a distance of one mile in 1902.

### Musical Headphones

On Christmas Eve, 1906, marine operators were astonished to hear music in their headphones. It was followed by a short speech inviting everyone to write to R. A. Fessenden at Brank Rock, Mass., several hundred miles away from many of his listeners. Again Fessenden was using a d.c. arc to excite the aerial circuit. Modulation was by a carbon button directly connected to the aerial circuit. By this time most detectors consisted of rectifiers of one form or another which, unlike the coherer, would demodulate.

In 1907, in America, De Forrest added a third electrode, now known as the grid, to the Fleming diode and soon discovered that it would amplify besides detecting. At first De Forrest believed that his valve (or "audion", as it was called) amplified by controlling ionisation caused by wireless waves within the bulb and it was several years before its action was understood.

Meanwhile a fierce battle developed between the Marconi Company and De Forrest over patent rights, since the Marconi Company held the patents of the Fleming diode. The final outcome was that neither could use the "triode" without the consent of the other party.

Much controversy still exists as to who discovered the triode's potentiality as regenerative detector and oscillator. Mr. K. W. Alford, then a student at the London School of Telegraphy, observed that signals were accidentally heterodyned by a De Forrest audion he was experimenting with in 1913 (he was later known for his pioneer work on superhets and is still well known as G2DX in the field of amateur radio) but he did not know why. Meisner developed a triode oscillator in the same year in Germany.

Edward Armstrong announced his first claims around this time. Armstrong's subsequent inventions included the superhet. In 1914 he filed a patent for a regenerative audion circuit. It was soon followed by another patent from De Forrest, claiming that his circuit could be used for regeneration and oscillation. After prolonged legal proceedings the Supreme Court upheld De Forrest's claim. During this year the Marconi Company in England marketed a combined telephony transmitter and receiver using valves. ■

# BOOKS REVIEWED

**CLOSED CIRCUIT TELEVISION HANDBOOK.**  
Leon Wortman. W. Foulsham & Co. Ltd., Slough, Bucks.  
273 pages. Size 8½in. x 5½in. Price 42/-.

**T**HE title of this book raised my hopes of some interesting reading, together with some practical circuitry, as the name handbook usually implies.

At 42s. I thought I was at least entitled to one or the other. As it happens this book, in my opinion, provides neither. It is a long-drawn-out account of the hundreds of different ways to use CC-TV. Chapters such as cameras, video recording techniques are entirely commercial and there is very little of interest to the amateur or practically minded enthusiast.

The professional engaged in this field might find it interesting but for me it was one long, hard 273-page slog.—*D.L.G.*

**BASIC ELECTRONIC CIRCUITS.**  
Published by The Technical Press Ltd.  
112 Westbourne Grove, London, W.2. Price 42/-.

**H**AVE you ever opened a text book and found the type so small you almost had to use a magnifying glass to read it? And circuit diagrams tyrannically reduced until they looked more like a street map of Hong Kong? Those who like such miniaturisation will be disappointed in this book!

The type is large and easily readable, the circuit diagrams and illustrations are bold and clear. Add careful thought and planning, as has obviously gone into this book.

Clearly intended for the would-be technician, it offers a near-ideal work for the purpose. Each circuit has a group of waveforms and has a step-by-step explanation showing clearly what is happening at various stages. Nearly all circuitry is shown with valves, followed by the equivalent using transistors, and again the circuit action and waveforms are shown step by step at each instant of time.

Commencing with the response of CR circuits to pulses it proceeds to diodes and thence to multi-vibrators. The clear way in which the latter are dealt with make the book worth having on the shelf.

## SOLID-STATE PHOTOFLASH

With regard to the Photoflash unit which should have appeared in the October issue, we regret that just before publication we learnt that the photoflash tube had been discontinued by the manufacturers.

We are investigating the possibility of re-designing this equipment to use a tube which is in current supply, and should this be possible the article will appear without delay. In the meantime we trust that our readers will accept our apologies.

Part 2 covers timebase circuitry, again with the same thorough treatment, with separate consideration for both electrostatic and electromagnetic deflection. The later sections of the volume tend towards radar circuitry and give the same meticulous treatment to strobe pulse markers.

All good basic reading and offering a very sound basis on which to build later knowledge. For technicians, engineers or indeed anyone wanting a good basic primer in electronics this book is a good buy. The price may be high but, compared with some others, it becomes a decided bargain.—*D.L.G.*

## ON THE SHORT WAVES

—continued from page 613

PX1JS, PY5ACB, SV1DL, TR2DE, VO1BD, W7HH/MM, ZD8TV, ZS6BRG, 4X1DK, 5A1TK, 5N2SMV, 5Z4AA, 9L1MJ, 9Q5DL, 9U5BB. On 28Mc/s P. Baker (Pontypool) HE30, 14ft. whip CM3TDS, CT1GE, DJ—2UC, 8XQ, 9EV, DM3WEK, EA7BD, EL2JT, F9IE, IILCE, LA—4AX, 5WU, W4ZZZ (Florida) 9Q5WB all a.m. Note the W's starting to appear.

## News

9M8KS is reported low end of 20 seeking G's, VKØ on Macquarie Is. around 14,200, a PYØ is rumoured active on Fernando de Noronha and/or Trinidad Is. same prefix, ZS2MI for the vigilant on Marion Is., and ZD9 on Gough Is.

If you're contest minded, then the following happenings are forecast for October 2/3rd VK/ZL contest (phone section); 2/3rd WADM (c.w.); 9/10th Raynet Rally 1·8, 3·5, 70 and 144Mc/s. Times for this one—9th 1800—2200 and 10th 0800—1200, 1500—1900. 9/10th VK/ZL (c.w.); 10th Northern Radio Society's Convention at Belle Vue; 16/17th 7Mc/s DX contest (phone). 16/17th Eighth Jamboree-on-the-Air; 23/24th CQ World Wide contest (phone); 30/31st VU2/4S7 contest (c.w.). Nov 6/7th VU2/4S7 (phone); Nov. 6/7th 7Mc/s DX (c.w.) 73 good DX and deadline for this month is 28th.

IF YOU KEEP UP WITH PRESENT-DAY  
TRENDS YOU MUST TAKE

**PRACTICAL ELECTRONICS**  
NOVEMBER ISSUE ON SALE  
OCTOBER 14


★ PE DOORPHONE ★  
★ WATER LEVEL ALARM ★  
★ CLASSIC COMMUNICATIONS ★  
★ RECEIVERS PART ONE (BC 348) ★  
AND SEE FOR YOURSELF!

## 26 $\frac{1}{2}$ gn TAPE RECORDER for ONLY £19.10.

carr. 10/-

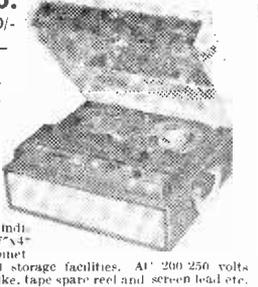**Bargain of the Year Offer—Cancelled Export Contract**

Famous manufacturer's brand new unused and factory tested 2 speed, 37 and 71 l.p.s. twin track tape recorder. 3 Watt output. Tape position Rew-counter, fast forward and rewind, takes 7" reels, mike and gram input. Straight through amplifier facilities. Output sockets for ext. speaker, monitor or external amplifier. Super-imposed switching magic are recording level and means neon indicator. Volume and tone controls 7+3 speaker. Attractively styled cabinet with detachable lid mike and reel storage facilities. At 200/250 volts operation. Complete with crystal mike, tape spare reel and screen lead etc.



## L.P. RECORDING TAPE BARGAIN OFFER

By leading British Manufacturers Professional Grade Double Sided (each side coated) 5 $\frac{1}{2}$ -in. reels only. Special Price Offer 1.450 test (2 reels) 20/- post free. (ideal for the experimenter who wants to record both sides, and a good L.P. tape for the enthusiast who wishes to record single side only).

**Jack Plugs.** Standard 2 $\frac{1}{2}$ " Igranic Type, 2/6. Screened Ditto, 3/3. Miniature scr. 1 $\frac{1}{2}$ " 2/3. Sub-min. 1/3. **Jack Sockets.** Open Igranic Moulded Type, 3/6. Closed Ditto, 4/- Miniature Closed Type, 1/6. Sub-min. (deaf aid) ditto, 1/6. Stereo Jack Sockets, 3/6. Stereo Jack Plugs, 3/6. **Phono Plugs, 9d.** Phono Sockets (open), 9d. Ditto (closed), 1/- Twin Phono Sockets (open), 1/3.

**Grundig Continental.** 3 p. or 5 p. plug, 3/6. Sockets, 1/6. **Soldering Irons.** Mains 200/220V or 230/250V. Solon 25W Inst., 2/4s. Spare Elements, 5/6. Bits, 1/3. 65W, 29/6, etc. **Alumin. Chassis.** 18g. Plain Undrilled, folded 4 sides, 2" deep, 6" x 4", 4/6, 8" x 6", 5/9, 10" x 7", 6/9, 12" x 6", 7/6, 12" x 8", 8/-, etc. **Alumin. Sheet.** 18g. 6" x 6", 1/-, 6" x 9", 1/6, 6" x 12", 2/-, 12" x 12", 4/6, etc.

## 6 VALVE AM-FM TUNER UNIT



Med. and VHF 180m-550m, 46 Mc/s-103 Mc/s, 6 valves and metal rectifier, self-contained power unit. A.C. 200/250V operation. Magic-eye indicator, 3 push-button controls, on/off. Med., VHF. Diodes and high output sockets with gain control. Illuminated 2-colour perspex dial 11 $\frac{1}{2}$ "x4", chassis size 11 $\frac{1}{2}$ "x4"x5 $\frac{1}{2}$ ".

A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers. Available only at present as built-up units, aligned and tested ready for use.

This popular unit will be available in kit form within the next few weeks. Circuit and constructor's details, 4/6. Free with kit. **£12.10** BARGAIN PRICE Carr. & Ins. 7/6.

**Condensers—Silver Mica.** All values 2p to 1,000pF, 6d. each. Ditto Ceramics 9d. Twp. 450V T.C.C. etc. 0.001 mFd. to 0.01 and 0.1/350V. 6d. 0.02-0.1/300V. 1/-, 0.25 Hints 1/6, 0.5 T.C.C. 1/6, etc. etc. Close Tol. 8/Micas—10% 5pF-500 pF 8d. 600-5,000pF 1/-. 1% 2pF-100pF, 9d. 100pF-500pF 11d. 575pF, 5,000pF, 1/8. Resistors—Fwd Range: 10 ohms-1 meg. ohms 20%, 1 and 1/4 3d. 1W. 6d. (Mid-range type modern rating) 1W. 6d., 2W. 9d. Hi-Stab. 5% 1W. 6d. 10W. ohms-1 meg. Other values 9d. 1% 1/4 1/6, etc., etc.

**Volume Controls—5K-2 Meg. ohms.** 3in. spindle, Morganite Midget Type 1in. diam. Gun. 1 year, LOG or LN. rttos less Sw. 3/-, D/P. sw. 4/6. Twin Stereo less Sw. 7/6 100k to 2M ohms with DP Sw. 9/6.

**WAVELENGTH SWITCHES.** 1 p. 12-way 2p. 2-way, 2 p. 6-way, 3 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6 ea.


**EXPANDED ANODISED METAL.** Attractive gilt finish. In. x 1in. diamond mesh 4/6 sq. ft. Multiple or bin cut. Max. size 4ft. x 3ft., 47/6 per cart. Do., finer patterned mesh, 4/8 sq. ft., multiple of 12in., max. size 3 ft. x 2 ft., 27/6 sheet.

**JASON FM TUNER UNITS** (Designer-approved kit of parts). FMT1, 5 gn., 1 valve, 20/- FMT2, 5 gn., 5 valves, 35/- JTV MERCURY 10 gn., 3 valves, 22/6. JTV £13.18/6. 4 valves, 23/6. NEW JASON FM HANDBOOK 2/6. 48 hr. Alignment Service 7/6. P. & P. 2/6.

**TRIMMERS.** Ceramic (Compression Type)—30pF, 50pF, 70pF, 9d.; 100pF/150pF 1/3; 250pF, 1/6; 600pF 1/9. PHILLIPS. See Hire Type (conc. in spec.)—2p, 1/-; 3-30pF, 1/-. **KNOBBS—Modern Continental type.** Brown or Ivory with Gold Centre: 1" dia., 9d. each; 1 $\frac{1}{2}$ " 1/- each; Conc. knobs Ivory with Gold Centre: 1 $\frac{1}{2}$ " dia. 2/9 per pair. Matching ditto 2/6 ea.

**LARGE SELECTION AVAILABLE.** METAL RECTIFIERS, S.T.C. Types—RM1, 4/9. RM2, 5/6. RM3, 7/6; RM4, 10/-; RM5, 21/-; RM4B, 12/6.

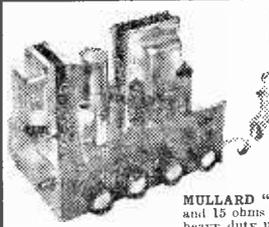**TUB-ELECTROLYTICS—CAN** 25/25v, 50/12v, 1/3; 3-8/450v, 4/6; 50/50-100/125v, 2/-; 32-2/275v, 4/6; 8/450v, 4/550v, 2/3; 50/50/350v, 6/6; 16-16/450v, 5/6; 60/250/275v, 12/6; 32-32/450v, 6/6; 100-200/275v, 12/6



## MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

3 ohm & 15 ohm output

"3-3" Amp, 3 valve, 3 watt hi-fidelity at reasonable cost. Bass Boost and treble controls quality sectional output transformer, 30 c/s-25 kc/s + 1 dB, 100mV in 3W, less than 1% distortion. Bronze escutcheon panel. Complete Kit only £6.19.6. Carr. 5/- Wired and tested £8.10.0.

**MULLARD "5-10" AMPLIFIER.** 5 valves 10W 3 and 15 ohm output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer Carr. and Ins. 7/6. **£9.19.6**

Basic amplifier kit price. Ready built 11s. 6ms. **CONTROL PANEL KIT.** Bass, Treble and Volume controls with 4-position selector switch or radio tape and 11in. x 4in. escutcheon panel. **AMPLIFIER KIT AND CONTROL PANEL KIT.** £11.19.6. Ditto, really wired, £14.19.6. **2-VALVE PRE-AMP UNIT.** Based on Mullard's famous 2-valve (2xEF80) circuit with full equalisation, with volume, bass, treble and 5-position selector switch. Size 10x6 $\frac{1}{2}$ in. Complete Kit £5.19.6. carr. 3/6. Ready Built £7.19.6.

## DE-LUXE RECORD PLAYER KIT



Incorporating 4 Sp. Garrard Auto-Slim unit and Mullard latest 3 watt printed circuit amplifier (ECL 86 and E2, 80), vpt. bass and treble controls, with 8" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue-reelief. Size 17 $\frac{1}{2}$ " x 15" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit)

**COMPLETE KIT £13.19.6** Carr. and ins. 12/6 Illuminated perspex control panel escutcheon, 7/6 extra. Ready wired 30/- extra. Four contemporary mounting legs 6in. 10/6; 9 in. 11/6. 12in. 12/6 extra

## TRANSISTOR COMPONENTS

Midget I.P.s.—465 Kcs/9.10in. diam. first, second or third. 5/6 Osc. Coupl. M. & W. 9.16 in. dia. 5/6 Midget Driver Trans. 9.1. 6/- Midget Output Trans. Push-Pull—3 ohms + ..... 6/-

**Elect. Condensers—Midget type** 1 mFd.-50 mFd. ea. 1/9, 100 mFd. 2/-, 12V. Condensers 150 v. working: .01 mFd., .02 mFd., .03 mFd., .04 mFd., .05 mFd., .1 mFd., 1/- .25 mFd., 1/3; .5 mFd., 1/6, etc. Midget Tuning Condensers, J.B. 100-200 pF and 170 pF. 9/6. ditto with trimmers, 6/6. J.B. 220 pF and 105 pF conc. slow motion 10/6. 365pF single 7/6. Sub. min. 3in. Dialexin 100 pF, 300pF, 500pF, 7/- each.

**FERRITE AERIALS, M. & L.W.** car aerial coil 9/3. Midget Vol. Control with edge control knob, 5 K/ohms, with switch 4/9; Ditto less switch 3/9. Swakers, P.M., 2in. Plessey 5 ohms 15/6. 2 $\frac{1}{2}$ in. Continental 8 ohms, 13/6; 7 x 4in. Plessey 35 ohms, 23/6.


**Ear Plug Phones—Min. Continental type 3rt. lead, jack plug and socket, High Imp., 8/- Low Imp., 7/6.**

**Brand New. Mfrs. 1st grade:** 1 OC44 & 2 OC45, 15/6; 1 OC81D & 2 OC81, 15/6. All above and OAS1, 32/6. Post Free.
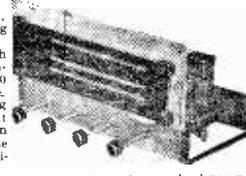
## 7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up EC085, EC151, EF99 EABCSO. EL84, EM81 EZ280. New 1965 Model now available

Three Waveband and Switched Gram. positions. Med. 200-550 Mc. Long 1.00-2,000 M. VHF/FM 88-95 Mc/s. Philips Continental Tuning Insert with adjustable tuning on FM and combined AM-FM IF transformers. 400 Kcs/s. and 10.7 Mc/s. Dust core tuning coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 $\frac{1}{2}$  x 6 $\frac{1}{2}$ in. Height 7 $\frac{1}{2}$ in. Edge illuminated glass dial 11x3 $\frac{1}{2}$ in.



Vertical pointers, Horizontal station names. Good on brown background A.C. 200-250V. operation. Magic-eye tuning. Circuit diagram now available.

Aligned and tested ready for use £13.19.6. Carr. & Ins. 7/6. Comp. with 4 tube O/P socket, ext. spkr. & P/U sockets and indoor FM aerial and 4 knobs—w/out or ivory to choice. 30 P.M. Speaker only required. Recommended Quality Speakers 10" Rola, 27/6. 13 $\frac{1}{2}$ " x 8" E.M.I. Fidelity, 37/6. 12" B.A. with conc. Tweeter, 42/6. Carr. 2/6.

**BONDAOUST Speaker Cabinet.** Acoustic Wadding (1 in. thick approx.) 18in wide, 4in. length cut, 2.3 per ft., 8/- per yard. **TINNED COPPER WIRE.** 16-22g. 2/6 lb. ERSIN MULTICORE SOLDER, 60/40 4d. per yard. Cartons 2/8, etc.

**TYGAN FRET** (Contem. par.), 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/-, etc.

We manufacture all types Radio Mains Trans., Chokes, Quality O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain list, 2d. stamp.

## RADIO COMPONENT SPECIALISTS


70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m. Wed. THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1 lb. 1/-; 1 lb. 19s; 3 lb 2/-, 5 lb, 3/6; 8 lb, 4/6.



Est. 1949


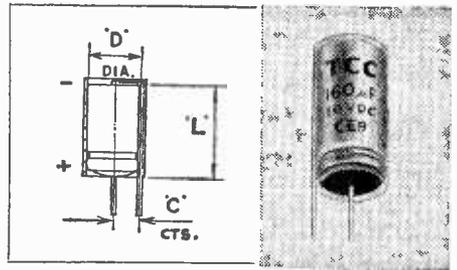
# Sub-miniature Electrolytics for Transistor Circuits



**Operating Temperature Range.** —20°C. to +60°C.

Connection wires are welded for low resistance contact, and solder-coated for ease of assembly, the standard length being 1½" for the horizontal range, cropped to ¾" long for the vertical range.

The capacitors are in insulated seamless aluminium cases, and sealed with a synthetic rubber bung.

**Cap. Tolerance.** The standard tolerance of all capacitors is —20% + 100% of the rated capacitance.

**Leakage Current.** CE.2-7 may be determined from the following: 1 (µA) = .01 C.V. + 10 at applied working voltage and at 20°C. CE.8-9 may be determined from : .02 C.V. + 20 at applied working voltage and at 20°C.

T.C.C. TYPE No.	Case Size in inches			Maximum D.C. Wkg. Voltages and Cap. (µF)					
	D	L	C	3V.	6V.	9V.	12V.	15V.	25V.
CE.2 'V' or 'H'	½	½	0.07	8	6	4	3	2	—
CE.3 ..	⅞	⅞	0.1	25	20	15	10	6	4
CE.4 ..	⅞	½	0.1	40	30	20	15	8	6
CE.5 ..	½	⅞	0.14	50	40	25	20	10	8
CE.6 ..	½	½	0.14	80	60	40	30	15	12
CE.7 ..	⅞	½	0.18	100	75	50	40	20	15
	D	L	C	3V.	6V.	10V.	15V.	25V.	50V.
CE.8 ..	½	¾	0.14	100	80	60	40	25	8
CE.9 ..	¾	¾	0.2	250	200	160	100	60	20

V=Vertical Mounting H=Horizontal Mounting

## THE TELEGRAPH CONDENSER CO. LTD.

Electronics Division · NORTH ACTON · LONDON · W.3 · Tel. ACOrn 0061 · Telex: 261383  
also at CHESSINGTON, SURREY and BATHGATE, SCOTLAND

### Super 8/RS/DD

Frequency range 40 c/s—20,000 c/s  
Impedance 10/15 ohms  
Power handling capacity 6 watts  
(12 watts peak) £7 0 0 (Tax Paid)

### Super 10/RS/DD

Frequency range 30 c/s—20,000 c/s  
Impedance 10/15 ohms  
Power handling capacity 10 watts  
(20 watts peak) £11 13 3 (Tax Paid)

### Super 12/RS/DD

Frequency range 25 c/s—20,000 c/s  
Impedance 12/15 ohms  
Power handling capacity 20 watts  
(40 watts peak) £17 10 0 (No Tax)

### POST THIS COUPON TODAY

For fully illustrated 8 page booklet on Wharfedale Speaker Units (Dept. P.)



NAME .....

ADDRESS .....

TOWN ..... COUNTY .....

WHARFEDALE WIRELESS WORKS LIMITED Idle Bradford Yorkshire  
Telephone Bradford 612552/3 Telegrams 'Wharfdel' Bradford



## No. 1 DERBY AND DISTRICT AMATEUR RADIO SOCIETY

IT is an established fact that the first wireless club in the country was formed in Derby during 1911. In the spring of that year, Professor G. P. Bailey gave a lecture in the Guildhall, entitled "Scientific Progress In Our Time" and demonstrated the ringing of bells and lighting of lamps by means of wireless waves. This prompted local experimenters to form a group and with the guidance of S. Grimwood-Taylor and A. T. Lee (whose sudden death was reported on 10th June, 1965), the Derby Wireless Club (QIX) was formed.

In the following year, books were purchased and a lending library started, and in 1913, the Club moved to new rooms. An exhibition was presented which received full-page coverage in the 6th February issue of the "Daily Sketch". On 7th May, in the "Daily News and Leader", there was a column devoted to the Club and in the 9th July issue of the same paper, under the heading "Aerial Music", reference was made to the Club and to a cigar-box crystal receiver made by A. T. Lee.

The February 1913 issue of "Model Engineer" carried a letter with a plea for other towns to start radio clubs and correspondence ensued in which the Club helped in the formation of several others.

The Club continued during the next few years, although the 1914-18 war reduced its activities. In 1921 there were transatlantic tests on the short waves and several members co-operated in these.

In 1922, on 12th May, the local newspaper featured a paragraph on the Club with an illustration showing A. T. Lee's sister broadcasting the result of the Carpentier-Lewis fight, which had taken place the previous night.

### Wireless for Hospital


The main project in 1926 was the provision of wireless for the patients in Derbyshire Royal Infirmary. This was carried out in co-operation with several other local organisations and the

installation was officially presented on 15th November. It included 300 pairs of headphones and several loudspeakers.


The Club celebrated its coming-of-age with a dinner on 8th February, 1932, and many of the founder and early members were present. In 1936, the Silver Jubilee was celebrated with a dinner on 28th October, and a presentation was made to the founder members S. Grimwood-Taylor and A. T. Lee.

In 1937, 10th April saw the erection of an aerial on the Police Headquarters Building, for experiments in communication on the 5m band.

With the outbreak of the Second World War, transmitting activity ceased, all apparatus being confiscated by the authorities. After the war, in 1947, it was decided to form the Derby and District Amateur Radio Society to cater for all aspects of radio and electronics, both technically and socially. Membership was to be open to all, on payment of a 5s. annual subscription (the same incidentally as today and when the Derby Wireless Club started in 1911).

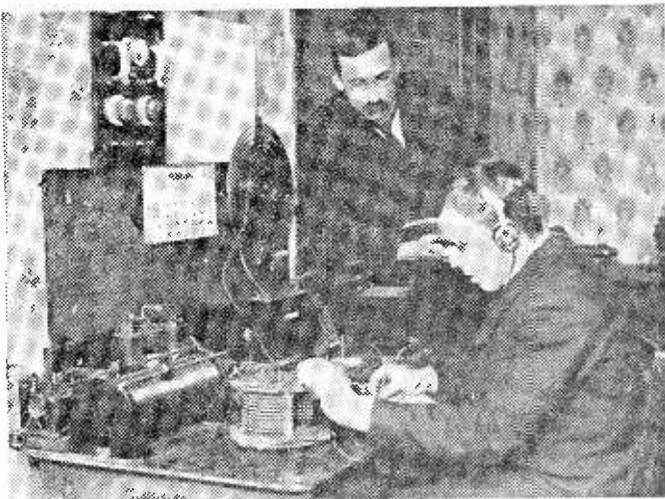

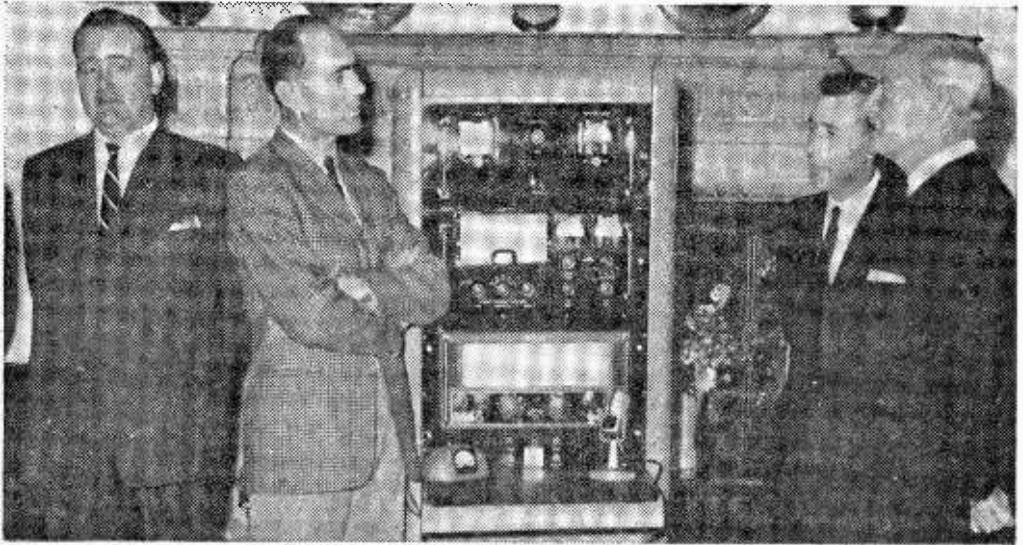A. T. Lee (seated) operating the Derby Wireless Club transmitter in the Full Street, Derby, Club Room in 1913. Looking on is another founder member S. Grimwood-Taylor.



Near Derby, at Staunton Harold, is one of the Group Captain Cheshire Homes, and a project undertaken by the Society in 1960 was the provision of a complete amateur station at the Home. The prime mover in this project was J. Ballinger, G3NAJ, who constructed an all-band transmitter in a console cabinet. The parts for the transmitter were given by local and national firms and members of the Society. A sale of donated items organised by the Society realised £60 which was used to provide a receiver for the station.

The picture shows (left to right) J. Ballinger; Group Captain Cheshire, V.C., D.S.O., D.F.C.; F. C. Ward (Secretary); and Sir Denning Pearson, who presented the equipment to the Home on behalf of the Society.

At the Annual Dinner, held in 1949, A. G. G. Melville, F.R.C.S.(E.), Consultant Radiologist at Derbyshire Royal Infirmary, accepted office as the Society's President, a post which he continues to hold.

Interest in the society continued to grow, and in 1954, at a meeting between the Committee and the founder members of Derby Wireless Club, it was agreed that the Society should incorporate in its title "Derby Wireless Club 1911".

#### Mobile Rally

It was in 1958 that the first of the Society's Annual Mobile Rallies was held at Rykneld School, Derby. This proved to be a very popular event. In the next year, the second rally was held and was an even greater success than the first had been, with over 1,000 visitors. (Recent rallies have often attracted as many as 4,000 visitors.)

Near Derby, at Staunton Harold, is one of the Homes founded by Group Captain Leonard Cheshire, V.C., D.S.O., D.F.C., and a project undertaken by the Society in 1960 was the installation of a complete amateur station at the Home.

#### History

As may be seen from the foregoing, the members of the Society are keen on keeping track of its history and many of the items constructed by Club members in the first days of amateur radio are preserved together with original documents and photographs, and items of correspondence.

#### Club Room

The present Club room is in the sub-basement of Derby College of Art, and the limited accommodation restricts the activities of the Club, at least so far as transmitting from the premises is concerned. However, it is hoped that the Club will be provided with better accommodation in the not too distant future.

The Society's call-sign was originally G3ERD (Experimental Radio Derby) and this is still in use. However, the Society has recently been fortunate enough to acquire another call-sign—G2DJ— which it is hoped will shortly be as well known on the air as G3ERD.

#### Meetings

Meetings are held once per week, at 7.30 p.m., on Wednesdays, at 119 Green Lane, Derby (near the College of Art) and visitors are always welcomed. Details of meetings are issued four times per year with full information on the next quarter's events.

A popular annual function is the Dinner and Dance. This year the attendance was 186, the members travelling from as far afield as Stamford, Bristol and Marlow.

The Derby and District Amateur Radio Society has now flourished for many years, due to a very keen membership and the continuing existence of an enthusiastic Management Committee. Present members and committee are as keen as the earlier ones were and see no reason why the Society should not continue to expand and preserve its position in the forefront of amateur radio.

# SEE THE WORLD'S FINEST COMMUNICATION RECEIVERS

AND RADIO EQUIPMENT OF LEADING  
MANUFACTURERS ALSO AMATEUR TV

AT THE  
RADIO SOCIETY OF GREAT BRITAIN

## RADIO COMMUNICATIONS EXHIBITION

SEYMOUR HALL : SEYMOUR PLACE  
MARBLE ARCH : LONDON W

WEDNESDAY, OCTOBER 27th to  
SATURDAY, 30th

Open 10 a.m. to 9 p.m.

Admission 3/-

DISPLAYS by ROYAL NAVY AND POST OFFICE ENGINEERS  
HOME CONSTRUCTION AND DESIGN DISPLAY  
COMPLETE TRANSMITTING STATION WORKING  
EDUCATION AND TRAINING INFORMATION

WIN £182 EDDYSTONE EA12 COMMUNICATION RECEIVER  
by exchanging this advert for free raffle entry

**COMPONENTS LIST**

**Note:** The majority of the following items are already present in the "Ten-Five".

**Resistors**

- R1 15kΩ
- R2 1kΩ
- R3 1kΩ
- VR1 5kΩ pot.
- R4 3.9kΩ
- R5 20kΩ
- R6 1.2kΩ

**Capacitors**

- C1 75pF mica
- C2 100μF electrolytic
- C3 0.01μF ceramic or paper
- C4 0.01μF ceramic or paper
- C5 0.05μF paper
- C6 0.01μF ceramic or paper
- C7 2000pF mica or ceramic
- C8 5000pF mica or ceramic
- C9 See Table I
- TC 0.30pF Beehive trimmers (9)

**Semiconductors**

- TR1/2 AFI15

**Switch**

- 3-wafer, 3-pole, 3-way rotary (Radiospares, etc.)

**Coils and Transformers**

- T1A Miniature Dual purpose transistor coil—Blue. Range 3

- T1B Miniature Dual purpose transistor coil—Blue. Range 4
- T1C Miniature Dual purpose transistor coil—Blue. Range 5
- T2A Miniature Dual purpose transistor coil—Yellow. Range 3
- T2B Miniature Dual purpose transistor coil—Yellow. Range 4
- T2C Miniature Dual purpose transistor coil—Yellow. Range 5
- T3A Miniature Dual purpose transistor coil—White. Range 3
- T3B Miniature Dual purpose transistor coil—White. Range 4.
- T3C Miniature Dual purpose transistor coil—White. Range 5
- L1 Miniature Dual purpose valve type coil—Red. Range 2

**Note:** All the above coils and transformers are by Denco (Clacton) Ltd.

**Oddments**

- Piece aluminium 4 x 3½ in., Control knob, 6BA nuts (15), 6BA bolts (6), Tagstrips (2), Connecting wire, insulated and assorted colours.

*Continued from page 595*

(6) Set generator to HF tracking point and tune in signal using VC1-2-3. Adjust trimmers of Blue R3 and Yellow R3 for maximum output.

Exactly the same procedure as outlined above is used for aligning the other two ranges, always taking care not to upset the adjustments already made. Final locking of the cores and trimmers is not recommended until each range has been rechecked in case interaction has introduced changes.

**Second Channel**

Two responses can usually be found on short wave ranges and the one requiring minimum core or trimmer in circuit is the correct one. To check move the generator pointer on completion above and below its setting (3Mc/s), when a second response will be noted. This should be higher in frequency than the one used for initial adjustment.

Detuning of the oscillator can occur when aligning the signal circuits (pulling) but may be overcome by slightly rocking the tuning capacitor when making adjustments.

**TABLE I**  
Blue/Yellow transformers      White transformers

Maker's Range Number	Coverage		C9	Padder Pin Number
	Mc/s	Metres		
3	1.67—5.3	57—180	340pF	3
4	5.0—15.0	20—60	960pF	4
5	10.5—31.5	9.5—28	2000pF	6*

\* Harmonic mixing used on this range, the 2nd harmonic being automatically present.

**TABLE II**  
Tracking Points


Range	LF Band End	LF Tracking Point	HF Band End	HF Tracking Point
3	1.67 Mc/s	1.83 Mc/s	5.3 Mc/s	4.5 Mc/s
4	5.0 Mc/s	5.50 Mc/s	15.0 Mc/s	13.5 Mc/s
5	10.5 Mc/s	11.50 Mc/s	31.5 Mc/s	28.5 Mc/s

**Conclusion**

It is now merely necessary to retrim the wavetraps against 1.6Mc/s signals if necessary and to cut out a hole in the receiver casing to accommodate the switch shafting. The casing now requires no hinged or removable lid, of course, but screening against self pick-up is necessary. This means that if the casing is not metal its interior must be lined with metallised foil that is grounded.

Proof of adequate screening is easily found by adjusting the switched section to the highest frequency range and noting if any signals are received when the aerial is left disconnected.

# ADAMIN THERMAL STRIPPERS

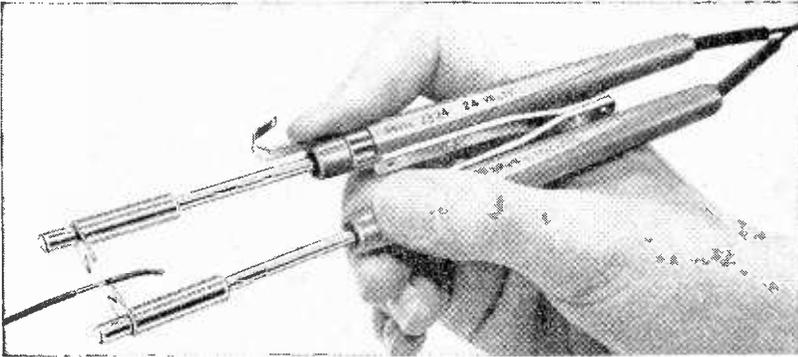

The new ADAMIN thermal wire strippers allow one-handed operation, using a simple tweezer action.


They strip coverings of up to about 5/32 inch diameter with absolutely no risk of damaging the conductors.

FOR **PTFE** INSULATION  
FOR **PVC** INSULATION

use Model 2B24, (illustrated), available for 24 volts only.  
and similar low temperature materials, use Model 2B6, available for 12 or 24 volts.

**LITESOLD TRANSFORMERS** permit safe operation from any mains power point. Free details of the whole wide range of ADAMIN and LITESOLD soldering equipment in brochure SPI0.

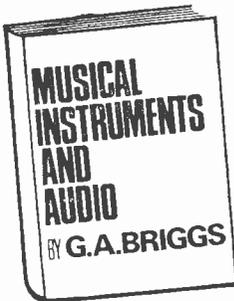**LIGHT SOLDERING DEVELOPMENTS LTD.**, 28 Sydenham Road, Croydon, Surrey. Telephone: CRO 8589



## A NEW BOOK

By **G. A. BRIGGS**  
Publishing date  
October 22nd 1965

240 pages 212 illustrations  
Fine art paper cloth bound  
32/6 (34/- post free)

In this book, the sixteenth to be produced by the Briggs-Wharfedale set-up, attention has been turned to musical instruments as the basis of audio.

The performance and frequency range of more than 60 instruments is examined, with a large number of photographs and diagrams. In fact, the book is intended to appeal to both the concert-goer and the audiophile. The usual touches of humour enliven some of the pages, with 16 cartoons to relieve the monotony of reading. Chapters include:

GENERAL PRINCIPLES · VARIOUS SOUNDS—CAUSE AND EFFECT · CHARACTERISTICS OF INSTRUMENTS · FORMANTS · DISTORTION IN SOUNDS · DISTORTION IN REPRODUCTION · ORGANS · ELECTRONIC ORGANS · PIANOS · TUNING · MUSIC IN SCHOOLS ·



**Wharfedale Wireless Works Ltd.**  
**IDLE · BRADFORD · YORKSHIRE**  
Tel. 612552/3 Grams. 'Wharfedel' Bradford

## SOUDOGAZ

### The all round BLOWLAMP

**SOLDERING  
PAINT STRIPPING  
BRAZING**

The finest blowlamp available on the market! Quick, easy and clean to use. No PREHEATING REQUIRED. All you do is turn the tap and light. Fuelled by a 200 gramme butane cartridge, which by virtue of its design is able to use all the gas in the cartridge. Burns for 2½ hours at full pressure. Ideal for all ordinary brazing, paint stripping, soldering, defrosting pipes, gutter repairs etc.

Complete with normal jet  
Cartridge 3/9

**45/-**

- |                         |     |
|-------------------------|-----|
| 1. Paint Stripper ..... | 9/- |
| 2. Fine Jet .....       | 9/- |
| 3. Soldering Iron ..... | 9/- |



## SOUDOGAZ 200 BLOWLAMP

Available from all branches of HALFORDS, Departmentals, Hardware Stores, Ironmongers, Garages. Cartridges available from 5,000 stockists throughout the country.

PTC (P.W.) South St., Dorking, Surrey



# ANOTHER SINCLAIR



## The world's first pocket-size FM Tuner / Receiver


Sinclair's latest design, the SINCLAIR MICRO FM is a high quality FM tuner designed to be used with hi-fi amplifier or tape recorder. It can also be used independently as a self-contained pocket F.M. receiver for personal listening anywhere. This exciting Sinclair triumph, barely half the size of a packet of 20 cigarettes, is a fully fledged 7 transistor-2 diode superhet circuit incorporating many unique and original design features to achieve fantastically good standards of performance. Pulse counting detection ensures better linearity than conventional detection methods, and therefore better audio quality. Powerful A.F.C. which locks on to the station tuned in, together with unusually good sensitivity make tuning easy and the set's own telescopic aerial suffices almost everywhere. Separate output stages allow the unit to be used both as a tuner and as a self-contained receiver. *In styling, this is the most elegant, most professional looking design in miniaturised equipment ever made available to constructors, and is one you will be very proud to possess.* **YET WITH ALL THESE WONDERFUL FEATURES, THE SINCLAIR MICRO F.M. COSTS POUNDS LESS AND MEANS THAT ANYONE CAN AFFORD AND ENJOY THE ADVANTAGES OF F.M. RADIO TODAY.**

*Does all you expect from a high quality FM unit, yet measures only  $2\frac{15}{16} \times 1\frac{11}{16} \times \frac{3}{4}$  ins. in its case.*

- COMPLETE WITH TELESCOPIC AERIAL
- POLISHED AND BRUSHED TWO-TONE ALUMINIUM FRONT PANEL
- SPUN ALUMINIUM TUNING CONTROL
- ONE OUTPUT FOR TAPE AND HI-FI
- ONE OUTPUT FOR PERSONAL LISTENING
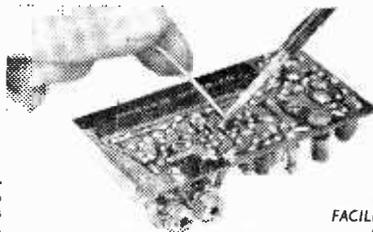
### ANYONE CAN BUILD THE SINCLAIR MICRO FM

All you need is a small electric soldering iron (preferably with  $\frac{1}{4}$  in. bit), tweezers and something to cut wire with such as nail clippers. The instructions take you step by step through every stage and are a delight to follow.



FULL SERVICE  
FACILITIES ALWAYS  
AVAILABLE TO  
SINCLAIR CUSTOMERS


# sinclair

**SINCLAIR RADIONICS LTD.**  
COMBERTON, CAMBRIDGE

Telephone  
COMBERTON  
682
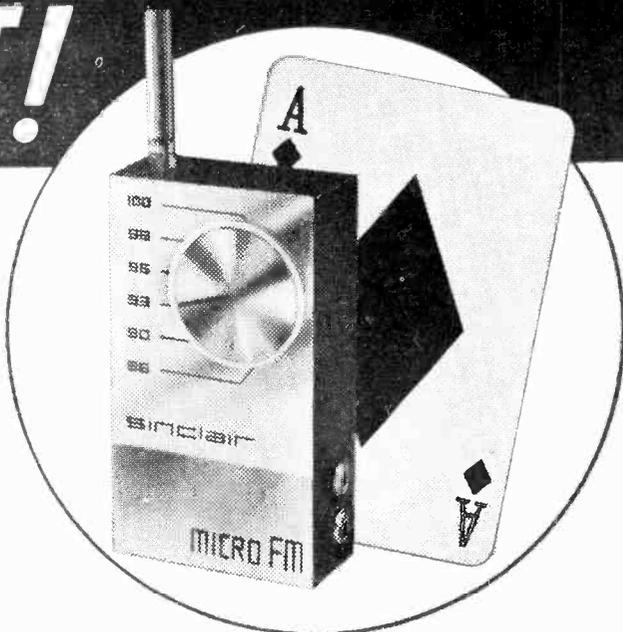
# FIRST!

- A.F.C.
- TUNES FROM 88-108 Mc/s
- NO ALIGNMENT NECESSARY
- A JOY TO BUILD
- THE ONLY SET OF ITS KIND IN THE WORLD



## SINCLAIR MICRO FM

### TECHNICAL DESCRIPTION

THE SINCLAIR MICRO FM is a seven transistor, two diode F.M. superhet for use both as a tuner for amplifier or tape recorder and as a self-contained pocket portable receiver. The telescopic aerial is coupled to an R.F. amplifier followed by a self oscillating mixer. Use of a low I.F. dispenses with the need for alignment. A three stage I.F. amplifier amplifies and limits the signal to produce a square wave of constant voltage which is fed into the pulse counting discriminator. This converts the square wave formation into uniform pulses, the average output from which is directly proportional to the signal frequency, so that the original modulation is reproduced exactly. After equalisation, the signal is fed to the audio output socket for use as a tuner and also to the receiver's own audio amplifying stage which enables the Micro FM to be used as an independent self-contained receiver. A.F.C. "locks" on each station automatically. THE SINCLAIR MICRO FM is completely self-contained within a neat black plastic case faced by an elegantly designed front panel of brushed and polished solid aluminium with spun aluminium tuning dial to match. The tuning scale is marked in Mc/s. When built, the Micro FM performs as well as any other good tuner.

- SUPPLY VOLTAGE 9V from self-contained standard battery.
- CONSUMPTION—5mA
- SENSITIVITY—Typically 3 microvolts
- AUDIO OUTPUT—300mV approx. from 25K ohms
- HIGH LEVEL AUDIO OUTPUT—9V peak to peak
- TUNING RANGE—87.5 to 108 Mc/s
- SIGNAL TO NOISE RATIO—30dB at 30 microvolts
- AUDIO FREQUENCY RESPONSE—10 to 20,000 c/s  $\pm$  1dB

### THE GREATEST VALUE IN QUALITY FM EVER

THE COMPLETE KIT OF PARTS for building the SINCLAIR MICRO FM including extending aerial. 7 transistors, case, tuning dial, aluminium front panel, lightweight earpiece, plugs and sockets and instructions costs only

## £5.19.6

### GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without questions.

ORDER FORM AND MORE SINCLAIR DESIGNS ON PAGES FOLLOWING

### 7 TRANSISTOR 2 DIODE SUPERHET FM TUNER/RECEIVER

Use it as—

AN F.M. TUNER FOR YOUR TAPE RECORDER



AS A SELF-CONTAINED POCKET F.M. RECEIVER.

(The only one in the World!)



# MORE UNIQUE DESIGNS FROM

## BRILLIANT PERFORMANCE • ADVANCED CIRCUITRY • EASY

# SINCLAIR X-20

INTERGATED 20 WATT PULSE WIDTH  
MODULATED AMPLIFIER AND PRE-AMP

*A new type of amplifier that  
gives you 20 watts output RMS*

By the use of Pulse Width Modulation in circuitry developed exclusively by Sinclair Radionics, the unique X-20 achieves standards never before reached by any audio amplifier in the world. From the input of the integrated pre-amp through to the power output stage, this amazing amplifier gives quality and power far ahead of anything in its class to make it the most original and interesting design in years. You use your X-20 like any conventional quality amplifier, but it occupies far less space, costs less, behaves perfectly and brings a refreshingly new approach to audio that is setting the standard for the whole industry. Build it for yourself—you will be delighted with the results, whilst its extremely compact size enables you to build equipment in the slimmest and most modern styling without heating or ventilating problems.

- ★ 12 transistors
- ★ Output stage — silicon epitaxial planars
- ★ Constant square wave amplitude
- ★ 95% conversion efficiency at output
- ★ Superb quality and reliability
- ★ 20 to 20,000 c/s  $\pm$  1dB
- ★ Total harmonic distortion — 0.1% at 10 watts R.M.S.
- ★ Input sensitivity — 1mV into 5k $\Omega$
- ★ Signal to noise ratio — better than 70dB
- ★ Power requirements — 36V d.c. at 700mA
- ★ Output into 7.5 ohms — 20 watts R.M.S. music power
- ★ 15 watts R.M.S. continuous
- ★ Output into 15 ohms — 15 watts R.M.S. music value
- ★ 10 watts R.M.S. continuous
- ★ Makes ideal guitar or P.A. amplifier
- ★ Built-in low-pass filter ensures wide tolerance of load at output
- ★ Add tone and volume control, mono or stereo, system to choice
- ★ Easily built in an evening

**QUALITY AND POWER FOR  
SUCH VERY SMALL OUTLAY**

Complete kit of parts including transistors and X-20 manual in sealed carton

**£7.19.6**

Built and tested with X-20 manual in sealed carton

**£9-19-6**

X-20 Power Pack sufficient to drive two X-20's

**£4-19-6**

**SIZE**  
8  $\frac{1}{4}$ " x 3  $\frac{1}{4}$ "  
x 1"

**weight  
only**  
4  $\frac{1}{2}$  ozs.

### X-20 MANUAL

Details various tone and volume control systems, stereo operation, input switching stage, etc. Supplied FREE with every X-20. Available separately, 2/- post free.

### A UNIQUE TUNER FOR A UNIQUE AMPLIFIER

See previous pages for details of the amazing Sinclair Micro FM Tuner/Receiver. Ideal for use with the X-20.

Full service facilities available to all Sinclair customers

**sinclair**

**SINCLAIR RADIONICS LTD.**  
**COMBERTON, CAMBRIDGE**

Telephone  
COMBERTON 682


# SINCLAIR

TO BUILD • GUARANTEED

## SINCLAIR MICRO-6

*The smallest radio of its kind in the world*

PHOTO SHOWS ACTUAL SIZE

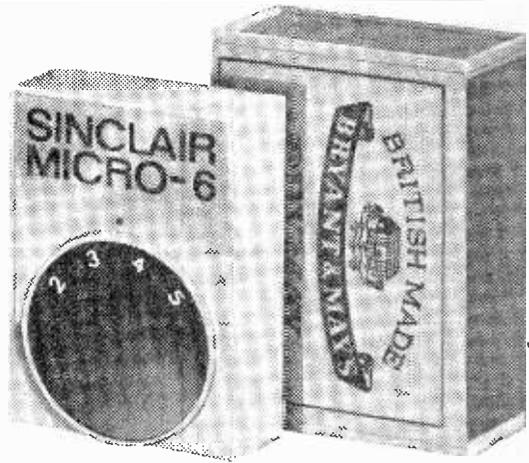

*Everybody's building it!*

**SIZE**  
1 4/5" x 1 3/10" x 1/2"

**SIX-STAGE  
CIRCUIT**

**LUXEMBOURG  
COMES IN LIKE  
A LOCAL**

**FANTASTIC RANGE  
AND POWER**

**EASILY BUILT IN  
AN EVENING**

**PLAYS ANYWHERE**

No transistor set has ever yet compared in its class with the Micro-6 for size, power, performance and design. Enthusiasts from electronic engineers to beginners in transistor construction go on building the Micro-6 until thousands are now in use all over the world. Everything except the lightweight earpiece is contained within the smart minute white, gold and black case. With pill-size batteries and self-contained aerial, the Micro-6 weighs under one ounce! Unique features which make such wonderful performance possible include bandspread over the higher frequency end of the

medium waveband for easy reception of Luxembourg, powerful A.G.C. to counteract fading of distant stations, and vernier type tuning. Quality of reproduction is outstandingly good, so that you derive real pleasure from using this fantastic set. Order your Micro-6 now and you will quickly see why it cannot be too highly recommended as an intriguing design to build and a most practical radio to use. You can build it in an evening and when you have built your first, be certain others are going to want one too, when they see and hear the Micro-6.


All parts including transistors, case, lightweight earpiece and instruction manual.

Mallory mercury cell ZM312 (2 required) each 1/11  
Pack of 6 cells—10/6

**59/6**

- A POWERFUL AMPLIFIER
- FOR YOUR
- MICRO-6
- 
- 

**TR  
750**

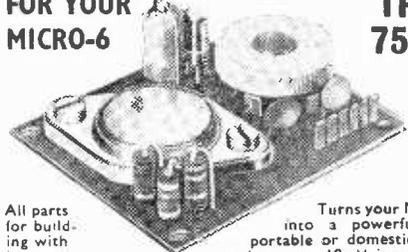

All parts for building with instructions.  
**39/6**

Ready Built  
**45/-**

Turns your Micro-6 into a powerful car, portable or domestic loud-speaker set. 10mV input gives 750 milliwatt output into a standard 25-30Ω speaker. Frequency response 30-20,000 c/s ± 1dB. Also makes a good record player, intercom, baby alarm, etc. Complete with built-in volume control and switch. 9v. operation.

## SINCLAIR X-10

Integrated P.W.M. Amplifier


Recommended for use where a less powerful amplifier than the X-20 is required. The X-10 also offers wonderful advantage of quality, compactness and price, and it can be battery operated if desired. Tone control system added to choice. For 12-15 volt operation.

Complete kit and instructions  
Ready built and tested  
X-10 power supply unit

**£5.19.6**

**£6.19.6**

**£2.14.0**

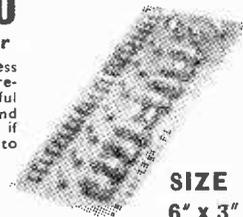

**SIZE**  
6" x 3"

Manual free with all X-10's

SINCLAIR MICRO FM—SEE PREVIOUS PAGES

## GUARANTEE ORDER FORM

### Guarantee

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question. Please quote PW.11 should you prefer to write your order instead of cutting out this coupon.

Please send me

.....  
.....  
.....

NAME .....

ADDRESS .....

for which I enclose Cash/Cheque/Money Order  
value £.....s.....d.

**TAPE RECORDERS, TAPES ETC.**

**TAPE TO DISC** — New High-level Cutters, 45 r.p.m., 21/-. S.A.E. leaflet. DEROY, 52 Hest Bank Lane, Lancaster.

**SOUND RECORDINGS**

**A UNIQUE BUY:** Recording Tape, top brand, 7in., 2,400 ft., D.P., 25/-; 5 1/2in., 1,200 ft., 10/6. P. and p. 1/6 per spool. Bargains in all sizes. S.A.E. for list. We repair, buy and sell Recorders. E. C. KINGSLEY & CO. LTD., 132 Tottenham Court Road, London.

**SERVICE SHEETS**

**SERVICE SHEETS** for all makes of Radio and TV, 1925-1965. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models 1/6. Valves, modern and obsolete. Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

**SERVICE SHEETS, Radio and Television, 4/- post paid. VEST AND EMERY, 17 Hallgarth St., Durham.**

**SERVICE SHEETS, Radio, TV, 5,000 models, List 1/-. S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.**

**RADIO AND TV SERVICE SHEETS.** All makes and models from 1924, 4/- each, plus s.a.e. If we haven't got it you won't get it. GRIMSDYKE RADIO, 77 Merriam Ave., Stanmore, Middlesex.

**SERVICE SHEETS**

4/- ea., plus postage

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon.

From: .....

Name: .....

Address: .....

.....

.....

To: S.P. DISTRIBUTORS  
44 Old Bond St., London, W.1  
Please supply Service Sheets for the following:

Make: .....

Model No..... Radio/TV

Make: .....

Model No..... Radio/TV

Make: .....

Model No..... Radio/TV

I also require list of Service Sheets at 1/6.

(please delete items not applicable)

I enclose remittance of .....


MAIL ORDERS ONLY. No. P W

**RATES:** 7/3 per line or part thereof average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., London W.C.2.

**RECEIVERS & COMPONENTS**

**CHASSIS ARE OLD HAT!** Get with it! Radiomatics Printed Circuit Kits. Approx 50 sq. ins. of top quality P.C. Board, plus all chemicals to process it and many more. Complete with comprehensive instructions. All parts available separately. 8/6 plus 2/6 post and packing. From — RADIO-MATICS, 140 Oak St., Norwich, Nrk.

**MARCONI CANADIAN RECEIVER NO.52**

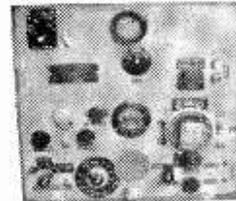

Shipping Amateur & Broadcast. Magnificent 10-valve receiver in three switched wavebands covering 1.75-16 Mc/s. (19-170 metres). p u s 3 valve crystal-stabilised

brator employing dual crystal to provide marker click at 10-100-1000 kc/s. One RF and two IF stages. Other refinements: valve, HT, and signal check meter. Internal 3in. speaker and two H/Phone outputs with switched control. RF-AF Gain Noise Limiter, Filter, BFO Heterodyne pitch control. Wide and Narrow Bandwidth Man or AVC on CW & RT Fast and Slow tuning with lock. Additional OSC Tuning (plus & minus). Power requirements HT 190v. 60mA; LT 12v. 1 1/2 amps. size 15 x 14 x 12in. Fully tested and working. ONLY £219.8. Carr. 15/8 or complete with Power supply unit suitable for 115/230v. AC mains £12.19.6. Carr. 20/-.

No. 52 GROUND-STATION comprising Receiver, Transmitter and 12v. D.C. Power Unit. £27.10.0. Carr. £2.10.0. (Mainland only).


**4 VALVE 4 WATT AMPLIFIER**

"C" Core transformers A.C. Mains 110/230 volts 600 ohms of high impedance input. Output 3 or 600 ohms (state choice) Controls: On/Off switch Gain control, Indicator light. Valve inspection panel. 19 x 7 x 7in. Brand New in maker's carton, 79/6. Carr. 10/-.



TELESCOPIC AERIAL MASTS. Tubular steel coppered spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixing and base locations. Bottom section 1 1/2in. diameter, 20ft. (4 section) Closed 5ft. 9in. Weight 16lb., 55/-, Carr. 5/-, 34ft. (6 section) Closed 6ft. 6in. Weight 20lb., 75/-, Carr. 5/-.

**WAVEMETER CLASS D**

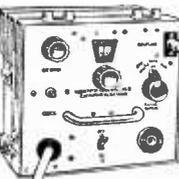

Freq. band 1,900 Kc/s to 8,000 Kc/s. (158-37.5 metres) in two ranges. 1,900 Kc/s. 4,000 Kc/s. also 4,000 Kc/s. 8,000 Kc/s. Supply 0 volt D.C. input. Complete with twin Crystal. As new. PRICE 62/6. P. & P. 5/-.

**TELEPRINTERS**  
CREED 7B used condition Price from £15; Teletype Corp. Type 14B, £17.10.0. Carr. 30/- each.  
**MOVING COIL HEADPHONES (BRAND NEW).** Chamos padded complete with jack plug, 15/6. Microphone, 10/6, post 2/- quantities.  
All No. 19 set parts available.

Many other bargains! S.A.E. all enquiries.

**A. J. THOMPSON (Dept P.W.)**  
"EILING LODGE"  
CODICOTE, HITCHIN, HERTS  
Phone: CODICOTE 243

**RECEIVERS & COMPONENTS (continued)**

**50 TRANSISTORS**, all tested, marked and guaranteed. AF, PF, Silicon and PNP. Unobtainable elsewhere at this low price of 35/-, plus p. and p. 1/-. D. & W. LTD., 224 West Road, Westcliff-on-Sea, Essex.

**TRANSISTORS**, new. Red Spot and White Spot, 28/- per 100 (minimum quantity either type). Post paid. G3LMR 112 Groby Road, Glenfield, Leicester.

**DIRECT TV REPLACEMENTS LTD.**, direct stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone GIPSY Hill 6166, 126 Hamilton Road, West Norwood, S.E.27.

**R & R RADIO & T V SERVICE**

Dept. P.W.  
MARKET STREET, BACUP, LANCs.  
Telephone 465

**SALVAGE VALVES** Tested before de patch

6F13	4/6	U239	5/-	PL36	6/-	20P4	6/6
6L18	4/6	10P14	5/-	10F12	3/6	60P16	5/-
EF80	1/6	20P5	6/6	U801	7/6	PC84	4/-
EC82	3/-	30P	7/-	10F1	1/6	PY81	8/6
ECL30	3/6	6P15	5/-	20P2	5/3	U301	8/-
30P5	6/-	EH91	1/-	30P11	5/-	10P13	5/6
1P38	6/-	EF85	6/-	PY32	6/-	20P1	2/-
PC80	4/-	6/3012	4/-	6U4GT	5/-	30P12	5/-
1P81	5/-	20P3	6/-	6P1	2/6	PY83	5/-
PZ30	5/-	30P11	4/-	EY86	4/-		

Speakers. Ex-TV. 5in. round 6 x 4in., 3/6; 8in. round, 8/-; post 2/-.  
Line Output Transformers available. State set model No.  
Turret Tuners. 8/-, post 2/-.  
Scan Coils etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

**TRANSISTORS, UNMARKED, UNTESTED**, 40 for 10/-, p. and p. 1/-. 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc., 5,000 items free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

**VALVES REACTIVATED** to as-new condition. Receiving 3/- each, transmitting 4/-. Post 6d. per valve. Restore performance of your equipment at minimum cost. Send stamp for leaflet. G. ELLIOTT, 3 Sandgate Ave., Tilkehurst, Reading, Berks.



**CANADIAN MARCONI 52 RECEIVERS** Superhet Receiver covering 1.75 to 16 Mc/s in 3 bands. 13 valves, crystal calibrator, meter, etc. Requires 150 volts D.C. 60 mA and 12.6 volts D.C. or A.C. Complete with steel outer case. In new condition, packed in original Ministry crates £10.10.0 Carriage Paid. Reprinted handbook with Circuits, etc. 5/-. Send S.A.E. for leaflet.  
**MARCONI CR 100/125 RECEIVERS**, 60Kc/s to 30Mc/s. Crystal filter, B.P.O. 2 R, P. 3 I.F. stages. Good working order £18.10 carriage £1.  
**10 WATT MODULATION TRANSFORMERS**, pair 6V6 to match 2500 ohms. 12/6. Post Paid.  
(Carriage charges apply to England and Wales only)

Telephone: Worthing 9097  
**40/42 PORTLAND ROAD, WORTHING**

**V.H.F. Panoramic Adaptor ALA-2**

This is a 30 Mc/s I/P Pan Adaptor that will display signals 2 Mc/s either side of 30 Mc/s. Valves 6H46 (2), 6RE6, 6AL5, 6AU7, 6AQ5, 8K4, 6SL7 (2), 6XN2, D100, 6X4, 1B3 and C.R.T. 3BP1. Power I/P is 115 v, 400 c/s if an external P.U. is to be used the power requirements are +300 at 70 mA, —1 kV at 2 mA and 0.5 v. twice. Controls: Focus, Brilliance, X and Y Shift, Gain, Centre Frequency and Width. These units are useful for scanning the V.H.F. Bands and will work with a Rx or Converter with an I.F. of 30 Mc/s. These are of recent American manufacture and in good condition. Price £5.15.0 plus 7/6 post.

**Selsyns 115 v.**

Tx and Rx selsyn. Rx selsyn is fitted with dial reading 0 to 10 plus and minus, also 24 v. D.C. brake. These will transmit position of aeriels etc. with a high degree of accuracy. Supplied with 230 to 110 v. Auto Transformer and connections. Brand new £2.10.0 per pair plus 3/6 post.

**Selenium Rectifiers**

H.W. type 1/P 300 v. A.C. O/P current 100 mA. with mounting brackets. Made by Fed-Two Phone Co., U.S.A. Brand new and boxed. Price 2/6 each plus 1/- post, or 4 for 10/- plus 1/- post.

**Marconi Canadian No. 52 Rx**

10 valve Rx covering 1.75 to 16 Mc/s in 3 Bands also as 3 valve crystal calibrator with check at 10-100-1000 Kc/s. Has one R.F. and two I.F. stages Control: R.F.-A.F. Gain, Noise limiter, C.W. filter, B.F.O., Wide and Narrow Bandwidth, Mod. or A.V.C. Built-in Sin. Speaker and Valve check and Tuning Meter. Two Headphone wks. Power requirements 160 v. at 60 mA, 12 v. A.C. at 2 amps. Brand new with outer case and circuit. Price £9.17.6 plus 12/6 carriage.

**Meters 5Q/171**

500 ΩA scaled 0 to 5. Marconi single hole fitting type 22 O.S.D. 90 Ωt. Res. New Tx equipment. Price 15/- plus 1/6 post.

**Power Unit Type 311**

1/P 200/250 v. 50 c/s O/Ps + 300 v. at 200 mA — 300 v. at 40 mA and 12 v. D.C. Smoothed at 4 amps. The O/Ps are all fused and can be switched by relays in P.U. Complete in case with circuit. New condition and crated. Price £6.10.0 plus 2/- carriage.

**Auto L.T. Transformer**

1/P 230 v. 50 c/s O/Ps 6 v. 3 amp. or 12 v. 1.5 amp. or using the 110 v. Pri. tap as a 40 watt auto trans. Totally enclosed, with terminal block on 1/P and O/P. Brand new and boxed. Price 10/- plus 3/6 post.

**Monitor Unit AN/GRD**

This comprises a Scope, Bearing Ind. and A.F. Monitor. The scope uses C.R.T. 2BP1 and valves 6AU6 (2), 6AL5, 12AU7 (2), 6AQ5 (2), OA2, 2D21, 12AX7, 5Y3 (2), also 3In. speaker, 360° Bearing Ind. etc. Tube shield and Vibe Controls Form, B.H. X and Y shift, sync. train, X amp power 1/P at 115 v. 50 c/s. 19In. rack unit with outer cover. Recent American manufacture in good condition (Good base) 1/2 general station monitor. Price £20.10.0 plus 12/6 carriage.

**Loudspeaker Units**

Heavy duty portable extension speaker in case size 17 x 17 x 8In. Speaker is a 10In. 3 ohm unit with 15 vds. of cable and plug. Brand new in sealed boxes, made by Pye Ltd. Price £8.10.0 plus 7/6 carriage.

**American HS33 Headphones**

These are a lightweight head set of 600 ohms and are fitted with soft rubber ear pads. supplied in good condition but less cord and plug. Price £2/6 plus 2/6 post. G.P.O. cord with plug 5/- post paid.

**Chassis with cover**

Comprises chassis with cover size 11 x 6 x 14In. deep with 4 Ind. lamps 6. Blue, Orange, Green and White each with polaroid filter. 3 relay 24 v. sealed 4P c/o. dimmer, Tog. switch etc. Finished in black crackle with 2 handles. Brand new. Price £2/6 plus 5/6 post.

**Power Transformers**

Westinghouse ZA29200 Pri. tapped 200/250 50 c/s — sec. 60 v. at 50 amp or 120 v. at 25 amp. Open construction size 15 x 12 x 9In. Weight approx. 1 cwt. Good condition. Price £8.10.0 plus 30/- carriage.

**B. SLATER,**  
34 Lifford Street,  
Tinsley, Sheffield

**RECEIVERS & COMPONENTS**  
*(continued)*

**SPEAKER REPAIRS,** cones fitted Satisfaction guaranteed. L. S. REPAIRS. Pluckley. Ashford, Kent.

**Guaranteed Brand New in original carton CANADIAN MARCONI 52 RECEIVERS**  
Few only at £9.10.0 Carr. 20.-  
**MAINS POWER UNIT £2.10.0**  
Supplied with Outer Case, Handbook and Circuit. Range 1.75-16 Mc/s.

Set has Crystal Calibrator, Speaker, etc.  
**V.H.F. RECEIVER, PYE P.T.C. 114**  
65-100 Mc/s 12 Volt D.C. Supply  
This is an 11 valve double superhet receiver, operating on one fixed frequency between 65-100 Mc/s., crystal controlled, speaker output using midget valves throughout. Supplied in 1st class condition with tuning data, circuit diagram and complete crystal formula. Ideal for the four-metre band (70.2 Mc/s.) offered at only 70/-, post 5/-.

These well made tuning units, made for the American 19 Tx-Rx, are housed in a metal case, colour green or brown, using a large precision calibrated scale, are an essential piece of equipment for the serious Tx or Rx operator. This unit will match an untuned wire or Whip Aerial to almost any Short Wave Receiver or Transmitter, exceptionally good for Mobile Top Band use. This American version being well noted as far superior to any other. **GUARAN. TEED BRAND NEW, only 20/-, Post 7/6.**  
Instructions supplied.

**JOHN'S RADIO**  
OLD CO-OP WHITEHALL ROAD  
DRIGHLINGTON, BRADFORD.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. PW7/9, 126 Humilton Road, West Norwood, S.E.27 GIPsy Hill 6166

**SPECIAL CLEARANCE OFFER**  
UNUSED TOP-QUALITY COMPONENTS

- I.F.T.S 465 Kc/s. ... .. Pair 4/6
- DP Switch on off 2 toggle ... each 2/-
- 1 Mid. 350V Capacitors ... .. 6 for 3/-
- 2 Mid. 250V Capacitors: ... each 1/6
- Variable 4 gang Capacitors ... each 4/6
- Fuseholder, Panel Mtg. ... .. each 2/6
- Lampholder " " Red. ... .. each 2/-
- Potentiometer 1 Meg. 2W ... .. each 2/-
- Hi-flux speakers 15 ohm 10x6 ... each 21/-
- WS.19 Connrs. 6-12 Pt. ... .. each 4/6
- ..... 12-12 Pt. ... .. each 5/6
- Roty. Tfr. 12V. o/p 350V 30mA ... each 12/6
- Work Carriers, Aerial Rod 4' 6" ... each 2/6

also used, but guaranteed  
Hand telephones, self-powered. 10/6 each  
Minimum Order Value 15/- plus 2/- p. & p.

**R. GILFILLAN & Co. Ltd**  
98 Dominion Road,  
Worthing, SUSSEX  
Tel: Worthing 8719

**SURPLUS AIRCRAFT NAVIGATIONAL EQUIPMENT**

Originally part of an aircraft direction finding equipment and containing A.R.B. approved components.

**POWER UNITS**

12 volt D.C. input, 25 watts

Outputs 2 at 350v. D.C. smoothed, and 1 at 6.3v. Contains 3—OC36, 2—OC72, 9—Diodes, transformer relay, etc. In mottle grey aluminium case 5 1/2 x 5 x 6In. Could be adapted for shaver operation. With circuit diagram 45/- plus P. & P. 6/6  
Diagram only 2/6 plus P. & P. 9d.

**POWER UNITS** as above but 24v. input ... 40/- plus P. & P. 6/6

**INDICATOR UNIT**

Contains 2 1/2 in. C.R.T. Type DG7-5 (CV. 2175), 2—ECC83, 1—ECC81, E.H.T. rectifiers and numerous condensers and resistors. In mottle grey aluminium case 9 x 6 x 3 1/2In. and would form the basis of a miniature Oscilloscope  
With circuit diagram 55/- plus P. & P. 6/6  
Diagram only 2/6 plus P. & P. 9d.  
The above items are brand new and complete but have not been tested and cannot therefore be guaranteed.  
A small number of incomplete units of each version are available at 15/- each plus P. & P. 4/6.

**COMPONENTS**

—all first grade

- Transistors OC36—Matched pair ... 25/-
- Transistors OC36—Single ... .. 10/-
- Transistors OC170 ... .. 7/-
- Transistors OC45 ... .. 4/-
- Transistors AFZ12 ... .. 12/6
- Valves 12AT7 (ECC81) ... .. 4/-
- Valves 12AX7 (ECC83) ... .. 5/-
- P. & P. 9d.
- E.H.T. Rectifiers K3.45 ... .. 7/-
- Vinkors LA2409 ... .. 15/-
- Vinkors LA2108 ... .. 15/-
- Crystals 10.7 mc/s. ... .. 15/-
- P. & P. 1/-.
- C.R. Tubes DG7-5 ... .. 25/-
- P. & P. 3/6.

Also many other items including capacitors, resistors, relays, diodes, slow motion drives, transformers, group wiring boards. Please send S.A.E. for list.

Enquiries and orders by post only to:—  
**N.J. GAWLER**  
40 Medina Road, COWES  
Isle of Wight

## RECEIVERS &amp; COMPONENTS

(continued)

TV CHASSIS, 110 with v.h.f., store soiled, £5 including carriage. NEW 19in. TUBES with small spot burnas £4 including carriage. C.W.O. TRURO VALVE SUPPLY LTD., Carclew St., Truro, Cornwall.

## FOR SALE

**240WATT ELECTRIC POWER ANYWHERE**  
**ANYTIME!** from 12V CAR BATTERY  
 WITH THE AMERICAN DYNAMOTOR UNIT  
 (Input 12v. output 200/250v. at 150 to 220 watts.  
 Perfect for TELEVISION, POWER TOOLS and all  
 universal AC/DC ELECTRICAL EQUIPMENT, gives  
 wonderful results. Price ONLY £8 + no carriage  
 5-4 stamped envelope for full illustrated details  
 W. SCIENTIFIC PRODUCTS, CHEVELEY, LANC.



EDDYSTONE 940 Receiver, new and guaranteed, one only. Usual Price £133, Special Price £109. DERHAMS, Radio and TV, Kent St., Kendal, Westmorland.

## TRANSISTORS

1/- each. Red or White Spots.

2/- each. XA101, XA102, XB103, OA90, XA111, XA112, OC430, 10/15.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, XA151, XB104, XC101, XC101A, OC169, OC200.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171, XA103, XA116, XB102, XB105, XC121, XU611.

5/- each. OC139, OC140, OC204, ORP60, XA701, XA703, GET7, GET8, GET9, XC141, BY100, OA211.

10/- each. OC19, OC22, OC25, OC26, OC28, OC35, 25013.

## ZENNER DIODES

4.7v. to 30v., 1/4w. 3/6, 1.5w. 5/-, 7w. 6/- each.

Plus many more. Send 6d. in stamps for full list and eq. chart

## B. W. CURSONS

78 BROAD STREET  
CANTERBURY, KENTYUKAN  
SELF-SPRAY

YUKAN Aerosol spray kit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Available in Grey Hammer at 14/11 at our counter or 15/11. Carr. paid per-push-button selfspray can.

SPECIAL OFFER: 1 can plus optional transferable map-on trigger handle (value 5/-) for 18/11.

## FOR SALE

(continued)

## MORSE MADE !

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 71, took only 6 WEEKS to obtain a G.P.O. pass certificate. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two international reply coupons for full explanatory booklet.

To G3CHS,  
45 GREEN LANE, PURLEY, SURREY.

**HAMMER FINISH PAINT.** The modern finish for electronics. Can be brushed or sprayed. Blue or Silver. 2oz. tins 3/6, post 8d.; 1-pint 7/6, post 1/9; 1 pint 15/6, post 2/9. Orders over 30/- post free. Retailers supplied. Write for details. Amazing results! Return of post service. FINNANG SPECIALITY PAINTS (PW), Mickley Square, Stocksfield, Northumberland.

## ELECTRIC SOLDERING-IRON

FANTASTIC  
BARGAIN OFFER

Lightweight Pistol Grip handle 40 watt, 240/250v. A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft Safety 3-core flex. Indispensable for every home handy-man. A boon to model makers and a necessity for every wireless enthusiast. Offered to P & P you at this new amazing price.

C. H. SERVICE, (Dept. P.W.)  
Lusted Hall Lane, Tatsfield, Kent.

## WANTED

WE BUY New Valves Second-hand Cameras. Binoculars. Projectors. Amplifiers, Records, Car & Transistor Radios, Components, etc. Send s.a.e. to EDDY'S (Nottm.) Ltd., 116 Alfreton Road, Nottingham.

WANTED: Information on converting W.S.38 set to top band and all other modifications. D. WOODHALL, 67 Belvere Ave., Blackpool, Lancs.

WE BUY New Valves for cash, large or small quantities, old types or the latest. Send details. Quotations by return. WALTONS WIRELESS STORES, 15 Church Street, Wolverhampton.

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S. Beverley House, Mannville Terrace, Bradford 7.

Get this Air Drying Grey, HAMMER FINISH now—IT'S SUPERB... THE PUSH-BUTTON WAY

Please enclose cheque or P.O. for total amount to:

YUKAN  
Dept. P.W.11  
307A EDGWARE RD.  
LONDON W.2

(Closed Thurs. afternoons, open all day Sat.)  
Choice of 13 self-spray paint colours and primer (Motor car quality) also available.



## WANTED

(continued)

URGENTLY WANTED: New modern Valves, Transistors, Radios, Cameras, Tape Recorders and Tapes, Watches, Tools, any quantity. S. N. WILLETTS, 16 New Street, West Bromwich, Staffs. Tel 2392.

## NEW VALVES WANTED

Any type or quality

CASH PAID

R.S.T. Valve Mail Order Co.

211A Streatham Road  
Mitcham, Surrey

Telephone: MITCHAM-6202

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. HUGGETT'S LTD., 2-4 Pawnsons Road, West Croydon.

WANTED  
VALVES ONLYMust be new and boxed  
Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

## MISCELLANEOUS

## ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & N., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

## BOOKS &amp; PUBLICATIONS

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied — list free. WILLEN (Dept. 401, 61a Broadway London, E.15.

## SURPLUS HANDBOOKS

19 set Instruction Handbook 3/6, p/p 6d.  
1155 Instruction Handbook 3/6, p/p 6d.  
H.R.O. Instruction Handbook 3/6, p/p 6d.  
38 set Instruction Handbook 3/6, p/p 6d.  
46 set walkie talkie Circuit & Notes 3/6, p/p 6d.  
88 set walkie talkie Instruction Handbook 4/6, p/p 6d.  
Frequency Meter BC221 Instruction Handbook, 3/6, p/p 6d.  
Wavemeter Class D Handbook Mk.1. 1/- & 111 3/6, p/p 6d.  
18 set Circuit Details & Notes 3/6, p/p 6d.  
52 set Instruction Handbook 4/6, p/p 6d.  
R.107 Instruction Handbook 4/6, p/p 6d.  
R1116/A Circuit Diagram & Details 1/9, p/p 6d.  
R1224/A Circuit Diagram & Details 1/6, p/p 6d.  
RF Unit 24 Circuit Diagram & Details 1/6, p/p 6d.  
RF Unit 25 Circuit Diagram & Details 1/6, p/p 6d.  
RF Unit 26 Circuit Diagram & Details 1/6, p/p 6d.  
Amplifier A1184 Circuit Diagram & Details 1/9, p/p 6d.  
Resistor Colour Code Indicators, Indicates the value of a resistor at a glance. Price 1/8, p/p 6d.  
All mail orders to:

Instructional Handbook Supplies,  
Talbot House, 28 Talbot Gardens,  
Roundhay, Leeds, 8.

## SITUATIONS VACANT

**TV AND RADIO**—A.M.I.E.R.E., City and Guilds, R.T.E.B. Cert., etc., on "Satisfaction or refund of fee" terms. Thousands of passes. For details of Exams, and Home-training Courses (including practical apparatus) in all branches of Radio, TV and Electronics write for 156-page handbook—FREE—B.I.E.T. (Dept. 242G), 29 Wright's Lane, London, W.8.

**MINISTRY OF DEFENCE (Army Department), Woolwich, S.E. 18,** requires Technician to be responsible for supervision of industrial staff engaged on proof and trials of ammunition stores. To control operation of electronic recording instruments and electrical firing circuits. **Qualifications:** Recognised electrical engineering apprenticeship or equivalent training. Experience in operation or maintenance of electrical instruments and interpretation of circuit diagrams essential. A knowledge of environmental testing procedure would be an advantage. **O.N.C. C. & G. Finals or equivalent. Salary:** £2990 (age 26)—£1,179 p.a. (Outer London). Application Forms from Manager (PE.4705), Ministry of Labour, Professional & Executive Register, Atlantic House, Farningdon Street, London, E.C.4.

**A FULL-TIME TECHNICAL EXPERIENCED SALESMAN,** required for Retail Sales. Write, giving full details of age, previous experience and salary required, to the Manager, HENRY'S RADIO LTD., 303 Edgware Road, London, W.2.

**MINISTRY OF DEFENCE (ARMY DEPOT.)  
ROYAL ARMAMENT RESEARCH AND  
DEVELOPMENT ESTABLISHMENT  
POTTON ISLAND, GREAT WAKERING, ESSEX**

**HAS INDUSTRIAL VACANCIES FOR**

**Electronic Mechanics** — Who have served an apprenticeship or equivalent training, or 5 years experience as a skilled man.

**Electronic Wiremen (Semi-skilled)** — Who are over 21 years, have had experience in Wiring Techniques and can identify electronic components.

**Rates of Pay**

Only basic theoretical knowledge is required.  
— Skilled—£15.6.0 to £16.19.0 per week  
— Semi-skilled—£12.13.0 per week.

- 42 hour 5-day week
- Paid Sick Leave
- Paid annual leave in addition to public holiday
- Prospects after a period of qualifying service at establishment in Government Service, with Superannuation benefits
- Free Transport from Shoeburyness.

Applicants should write or telephone for particulars to:

**Administrative Officer, Ministry of Defence (AD),  
R.A.R.D.E., Potton Island, Great Wakering, Essex.**

Telephone: Great Wakering 491. Extension 102.

## SITUATIONS VACANT

(continued)

Ideal opportunity to further your experience and be associated with Aeronautical Research and Development

AS AN  
ELECTRONIC CRAFTSMAN  
AT THE  
ROYAL AIRCRAFT ESTABLISHMENT  
BEDFORD

Electronic Craftsmen are required to work in a wide range of new and interesting fields in electronic engineering, covering instrumentation associated with model aircraft, digital data measurement and recording, digital computer techniques, radio telemetry systems coupled to research flying, aircraft simulation involving servo systems, aircraft radar systems with particular reference to automatic blind landing of aircraft, and also ground radio/radar systems associated with Air Traffic Control.

In all these fields Craftsmen work very closely with research scientists and engineers, and are given every opportunity to expand their experience. Craftsmen are mainly employed in the construction, testing and maintenance of equipments. Encouragement is given to craftsmen to further their technical education. R.A.E. can offer excellent working conditions with good prospects for promotion, and housing may be available within a short time to married candidates from outside the area. Radio/T.V. service experience would be an advantage, but men who have an approved apprenticeship or training in electronics, telecommunications, light current electrical engineering, or H.M. Forces training in radio or radar, and who wish to further their experience, should apply to:—

Labour Manager.

Royal Aircraft Establishment,  
Bedford.

Tel. Bedford 67411 Ex. 7.519

**RADIO AND TV Exam. and Courses** by Britain's finest Home-study School. Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL, Russell Street, Reading.

**A.M.I.Mech.E., A.M.I.E.R.E., City and Guilds, G.C.E., etc.** Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams, and Courses in all branches of Engineering, Building, Electronics etc., write for 156-page handbook—FREE—B.I.E.T. (Dept. 242B), London, W.8.

## EDUCATIONAL

**THE INCORPORATED PRACTITIONERS IN RADIO AND ELECTRONICS (I.P.R.E.) LTD.** Membership conditions booklet: 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, Dept. B., 32 Kidmore Road, Caversham, Reading, Berks

**RADIO OFFICERS** see the world Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1965-66. Grants available. Day and boarding students. Stamp for prospectus. **WIRELESS COLLEGE,** Co.wyn Bay

**TRAIN FOR SUCCESS  
WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses inc. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career

ICS DEPT. 541 PARKGATE ROAD  
LONDON S.W. 11.

**EDUCATIONAL**  
(continued)

**CITY AND GUILDS** (Electrical, etc.) on "Satisfaction or refund of fee" terms. Thousands of passes. For details of modern courses in all branches of Electrical Engineering, Electronics, Radio, TV, Automation, etc., send for 156-page handbook—FREE. B.I.E.T. (Dept. 242A), 29 Wright's Lane, London, W.8.

**RADIO OFFICERS'** training courses. Write Principal, Newport and Monmouthshire College of Technology.

**METAL WORK**

**METAL WORK.** All types cabinets, chassis racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman St., Loughborough.

**CHASSIS ALUMINIUM AND TIN PLATE, e.g.**

- 6 x 4 x 2" 5/3d.
- 12 x 3 x 2" 9/-.
- 8 x 6 x 2" 7/-.

Special sizes made to order.  
**LOUDSPEAKERS** All sizes, e.g.:  
2 1/2" x 8 ohms round 9/8d.  
Reconditioned elliptical 3 ohms 7/8d.  
**SINCLAIR** X10 assembled and in kit form; X20 assembled.

**TAPES AND EMPTY SPOOLS**

All sizes, e.g.:  
Message tape 150' or only 3/-.

**TAPE SLICERS AND CUTTERS**

12/6d.  
**CAPACITORS** all sizes, e.g.:  
2 MFD TCC 15 volt 1/8d.  
100 MFD TCC 12 volt 2/-.

**SOLDER MULTICORE** Boxes 6d. to 15/-.

**SOLDERING IRONS** Solon, Lightoid Rifco, Ross e.g.:  
Ross straight and pistol grip 9/-.

**LARGE RANGE OF EAR PIECES, TEST METERS, STOCKS OF VERO-BOARD, etc.**

Give yourself the treat you deserve—call at our shop, see our qualified staff and discuss your electronic problems, no matter how simple or complex—we'll do our best to help.  
Also you can use our postal services or telephone 80uth 2904

**TRADE ENQUIRIES WELCOMED**

**ROTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.**  
54 EGLINTON STREET,  
GLASGOW, C.S.  
Member of the Lander Group

**PADGETTS RADIO STORE**  
**OLD TOWN HALL**  
**LIVERSEDEGE, YORKS.**

Telephone: Cleckheaton 2866  
Special Offer. Brand New Boxed TV Tubes. MW43/69. 65/-, AW43-88. 75/-, MW36/24. 37/6. 90 Dekree Tubes with slight glass fault 37/- each. Carriage on any tube in G.B. 10/- Fully Guaranteed for 12 months.  
Re-claimed Tubes. Six months guarantee. AW43/80. 30/-, MW43/80. 30/-, MW43/69. 30/-, CRM172. 30/-, CRM142. 17/-, 12 inch tubes. 10/-, 17 inch tubes perfect but without guarantee. 17/- each. Carriage on any tube in G.B. 10/-.  
Scope tube removed from units. DG7-S. 2.5in., perfect condition. 30/-, Post 4/6. New JAP earpieces complete with lead and plug. 3 or 5mm. 1/11. Post paid or 20/- per dozen.  
New Transistors, OC72. 2/-; CV425. 10d.; CV448. 10d.; CV442. 10d.  
New Diodes, top grade, no duds. 3/- doz.

New 12in. Speakers with built-in tweeter 3 or 15 ohms. 28/6. Post paid.  
Perfect Speakers ex. equipment. 10in. round. 10/-, Post 3/-, 8in. round. 6/-, Post 3/-, 7 x 4in., 5/-, Post 2/-, 6 x 4in., 3/-, Post 2/-, Six for 20/-, post paid, 6in. round, 3/-, Post 2/-, 20/-, Philips 5in. Round. 5/-, Post 2/-.  
Motors Single Phase 240v. quarter H.P., 28/-; 1400 Revs. Fully guaranteed. ex. washing machines, carriage 8/6.  
Small Switch Motor 24v. will run from 12 or 6 volts. 10/-, Post paid.  
Bush 12in. TV 24 C13 channel TV. Complete and tested with good tube, only wants cleaning. 75/-, carriage 10/-, G.B.

**VALVE LIST**  
Ex equipment. 3 months' guarantee

EL91	1/6	20P1	4/-	PCC84	4/-
EL80	2/-	20P4	8/6	PCL82	5/-
EL84	3/-	U801	8/6	PCL85	5/-
ECC81	3/-	U281	5/-	PL36	5/-
ECC82	3/-	U282	5/-	12AT7	3/-
EY1	2/6	U329	5/-	6CH6	1/6
EY86	5/-	KT36	5/-	R18	3/6
EBP80	4/6	8V8GT	4/-	ARP12	1/6
EB91	9d.	6B3	1/6	Box 50 for 51	8/
ECC83	4/-	6K25	5/-	807	5/-
EL38	5/-	6P25	3/6	EP50	1/-
EF91	9d.	6U4	5/-	Doz. 6/-	1/6
6P1	1/-	PY33	6/-	EF80	1/6
6P15	5/-	PY80	3/-	Doz. 10/-	1/3
10C2	5/-	PL38	8/6	6K7	Doz. 10/-
10F1	1/-	PL81	4/-	6V6	Doz. 11/9
10P13	5/-	PL82	3/-	Doz. 18/-	1/9
10P14	5/-	PL83	3/-	6K8	Doz. 18/-
20D1	2/-	PY82	3/-	U25	5/-
20L1	5/-	PCF80	4/-		
20P3	4/-	PZ30	5/-		

All valve posts paid

**NEW DEAL FOR AMATEURS**

Every component is brand new. Accurate, tested resistors, condensers, components to give you first time working. Instruction books written by Radio Instructors—anyone can build without any knowledge of Radio or Maths. Superb after sales service facilities. Our designs are to the highest specifications top quality is put first.




All kits include valve, nuts, screws, hardware etc. Money back guarantee; should you feel on receipt of the kit that you are unable to build it, return it within 7 days and we'll refund you money! As supplied to schools, universities, H.M. Forces etc. The President 4 is a pocket size medium wave radio—only 3 1/2" x 2 1/2" x 1". Specially designed case, ferrite rod, 4 new Mullard semiconductor, proper tuning condenser proper plug-in battery. Special reflex plus regeneration circuit give performance equal to 6 transistor Radio (even operates a speaker). Amazing power, superb tone—tune into station after station, home and abroad. No aerial or earth needed—works beautifully anywhere at all!

Only 39/6 plus 2/6 p. & p. Everything—including 4 Mullard semiconductors. OC44, OA70, OC71 & OA70, personal earpiece etc. The Vice-President 3 is smaller still—in fact there is no smaller! Size only 1 1/2" x 1 1/2" x 1 1/2". Specially designed case, ferrite rod, covers all medium waves, works anywhere indoors or outdoors. Uses 3 new Mullard semiconductors—OA90/91, OC44 and OA90/91 in new reflex circuit—pulls in Luxembourg. "Pirates". Foreigners etc., and even this size uses Proper Tuning Condenser ONLY 29/6 plus 2/6 p. & p. Everything—including 3 Mullard semiconductors, personal earpiece etc. No more to pay. All parts available separately.  
**EDUCATIONAL ELECTRONICS CO. (EEPW2)**  
77 New Bond Street, Mayfair, London W.1.

**FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT OF QUALITY**

**H.A.C. SHORT-WAVE KITS**

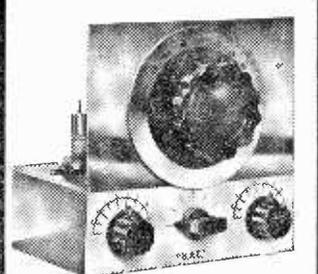

H.A.C. were the original suppliers of Short-Wave Receiver Kits to the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F. Army, Hams. etc.

**IMPROVED 1965 RANGE**  
1-Valve model "CX", complete kit. Price 34/6  
Customers say: "Definitely the best one-valve S.W. kit available at any price". This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and of course, as all our products, fully guaranteed.  
**FULL RANGE** of other kits still available including the famous model K, price 77/-. Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to—

**"H.A.C." SHORT-WAVE PRODUCTS**  
(Dept. T.H.), 44 Old Bond St., London W.1

when  
replying  
to  
advertisements  
please  
mention  
**Practical**  
**Wireless**

**GO AROUND THE WORLD**  
GO A.F.N. PARIS TELEGRAPH WIRELESS MOSCOW

**39/6**  
£2 POST FREE

Pat. App. For

On your OWN TRANSISTOR PORTABLE!  
★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio! Boosts 'Pirate' and distant stations, reduces 'fading'.  
★ Extends Battery Life!  
★ Use in car or caravan Without Aerial!  
British-made. Supplied with PP3 batt. (life several months) and instructions. Money refund guarantee.  
**D.E.W. LTD., Dept. P.W. Rinswood Road, FERNDOWN, Dorset**

# NEW VALVES !

Guaranteed Set Tested  
24-HOUR SERVICE

IRS. 1S5, 1T4, 3S4, 3V4, DA91, DF91, DK91, DL92, DL94, SP1, SP 4, 14/ DF96, DF96, DK96, DL96, SET OF 4, 23/6.

QA2	3/9	EB91	1/9	PL36	3/6
1R5	4/-	EB41	6/3	PL81	6/6
1S5	3/3	EBF80	5/9	PL82	5/-
1T4	1/9	EBF89	5/9	PL83	5/11
2S4	4/3	ECB81	3/3	PL81	6/-
3V4	5/-	ECB82	4/6	PY32	3/6
6K7G	1/3	ECB83	4/6	PY33	3/6
6K8G	3/3	ECB85	5/3	PY80	4/9
6Q7G	5/6	ECB82	5/9	PY81	5/-
6V6G	3/-	ECB85	5/9	PY82	4/9
20P3	10/6	ECH42	7/9	PY93	5/3
20P4	13/-	ECH81	5/6	PY800	5/11
20P5	11/6	ECL80	5/11	U25	5/3
30FL1	9/3	ECL82	6/6	U26	6/6
30L15	9/9	EC186	3/6	U181	3/6
30PL13	10/-	EF36	3/3	U301	10/6
35L6GT	5/6	EF41	5/9	U801	14/9
85A2	5/9	EF80	4/3	UABC80	5/-
CL33	8/6	EF85	4/6	UAB42	6/11
DAC32	6/9	EF86	4/6	UBC41	6/-
DAF81	3/3	EF89	4/3	UBF80	5/6
DF96	5/11	EL31	2/3	UBF89	5/9
DF33	7/6	EL41	6/9	UCB84	7/11
DF91	1/9	EL84	4/8	UCC85	6/6
DF96	5/11	EY51	5/11	UCF80	8/3
DK32	7/-	EY86	5/6	UCB42	7/-
DK91	4/-	EY89	5/6	UCH81	6/-
DK92	7/9	EZ90	3/3	UCL82	7/9
DK96	6/3	EZ81	4/3	UCL83	6/6
DL33	6/8	PCC84	5/6	UF41	6/6
DL35	4/9	PCF36	9/6	UL41	5/6
DL92	4/3	PCF80	6/3	UL41	7/9
DL94	5/-	PCF82	6/-	UL84	4/9
DL96	5/11	PCF805	8/-	UY41	3/11
DY86	6/3	PCL82	6/3	UY86	4/9
DY87	7/3	PCL83	9/-	W77	1/9
EACB80	5/6	PCL84	7/3	Z77	2/6

Postage on 1 valve 9d. extra. On 2 valves or more, postage 9d. per valve extra. Any parcel insured against damage in transit 6d. extra.

Office address, no callers.

## GERALD BERNARD

83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON N.16.

# RADIO CLEARANCE LTD.

27 TOTTENHAM COURT ROAD, LONDON W.1. Telephone: MUSEum 9188  
Bulk enquiries invited. The oldest component specialists in the trade. Est. 35 yrs.

## LOUDSPEAKER BARGAINS STILL AVAILABLE

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

Size in. inches	Watts	Imped. ohms	Price	Size in. inches	Watts	Imped. ohms	Price	Size in. inches	Watts	Imped. ohms	Price
2	7000	80	8/-	3 1/2	6000	3	10/8	4	9500	25	11/6
2 1/2	7000	80	8/6	3 1/2	9500	8	10/8	5	7000	3	8/6
3	7000	30	8/6	3 1/2	7000	25	8/6	5	7500	3	9/-
3 1/2	7000	30	8/-	3 1/2	9500	30	10/8	5	9500	3	10/8
3	5000	3	10/-	4	7000	25	11/8	5	9500	15	12/6
3	6000	5	8/8	4	6000	25	10/8	5	9500	15	12/6
3	7000	5	9/-	4	7000	33	11/-	5	8500	25	10/8
3	7000	25	9/-	4	7500	5	9/8	6 1/2	7000	3	11/-
3	6500	29	9/8	4	9000	50	11/8	8	6000	15	13/6
3 1/2	6000	15	10/-	4	8500	33	11/8	8	6000	3	13/6
3 1/2	7000	15	9/6	4	9500	15	12/-	8	6000	3	13/6
5 x 3	9000	33	12/-	7 x 3 1/2	9500	5	10/8	8 x 2 1/2	9500	3	10/-
5 x 3	7000	3	8/-	7 x 3 1/2	9500	4	11/8	8 x 5	9500	3	11/-
5 x 3	9000	3	8/8	7 x 4	9500	3	12/8	8 x 6	11000	3	13/6
5 x 3	9500	3	9/-	7 x 4	9500	30	12/8	10 x 6	11000	3	22/6
6 x 4	8500	3	9/6	7 x 4	10000	3	12/8	10 x 6	11000	3	22/6
6 x 4	9500	3	10/-	7 x 4	12000	3	15/6	10 x 6	11000	3	22/6
6 x 4	9500	33	12/-	8 x 2 1/2	6000	3	8/6	10 x 6	11000	25	13/6
7 x 3 1/2	7000	1	9/6	8 x 2 1/2	7000	3	9/-	10 x 6	11000	25	13/6

ALLOW 2/6 each speaker for postage and packing and handling charge and please specify the exact requirements—the nearest available will be sent.

### SELECTED BARGAINS

Beautifully geared AM/FM 2-gang Condensers, 4/6; AM/FM IFT'S 465 kc/s and 10.7 Mc/s 4/6 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; 3 watt Stereo Amplifiers complete, ready to switch on, 7/6; Sentercel rectifiers R3/2D-D3-2-1-Y, 2/6 each. DIODES—0A79, OA90, CG46H, GD10, 2/- each. TRANSISTORS: OC45 4/6, PXA101, 3/9, AF115, 4/6. Sub min. Germanium diode 1/3. Ni diode 6d. each. Silicon diodes, 400 p.i.v., 330mA, 2/6 each, please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogue—our stocks move too quickly! Kindly make provision for additional postage and packing charge to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.

# FREE TO AMBITIOUS ENGINEERS

THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy? ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

## SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

(Dept. SE/21), 29 Wright's Lane, London, W.8

### WHICH IS YOUR PET SUBJECT?

- Mechanical Eng..
- Electrical Eng..
- Civil Engineering.
- Radio Engineering.
- Automobile Eng..
- Aeronautical Eng..
- Production Eng..
- Building, Plastics.
- Draughtsmanship.
- Television, etc.

### GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.Prod.E.  
A.L.I.M.I.  
A.I.O.B.

B.Sc.  
A.M.I.E.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.I.E.R.E., City & Guilds  
Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate  
Practical Radio  
Radio & Television Services  
Practical Electronics  
Electronics Engineering  
Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T.  
NOW offers you a real laboratory training at home with practical equipment. Ask for details.

### B.I.E.T. SCHOOL OF ELECTRONICS

### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_


SUBJECT OR EXAM THAT INTERESTS ME

SE/21



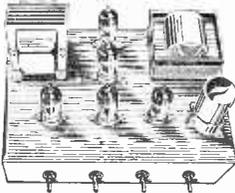**10/14 WATT HI-FI AMPLIFIER KIT**

A stylish finished monaural amplifier with an output of 14 watts from 2 EL54s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram, allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 ELS4s, EC083, 6F8s and E250 rectifier. Simple instruction booklet 1/6. (Free with parts).



All parts sold separately. **ONLY £6.19.6** P. & P. 8/6. Also available ready built and tested complete with standard input sockets. £8.15.0. P. & P. 8/6. Carrying Case for above £5/6. P. & P. 7/6.

**SPECIAL HARVERSON OFFER!** 11 BRAND NEW HEAVY DUTY 12in. SPEAKERS Response 45 to 15 Kc/s. 14in. voice coil. Available in 3 to 15 ohms. (guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered will below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE AT 8/9.6. P. & P. 5/- Also 25 watt Guitar Model available at £5.5.0 And 35 watt Guitar Model £8.8.0.


**HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1**



● Peak output in excess of 14 watts. ● All standard British components. ● Built on printed circuit panel size 6 x 3in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (3ET114) or 23 Mullard OC81D and matched pair of OC81 0/ps ● 9 volt operation. ● Everything supplied, wire battery clips, solder etc. ● Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-** P. & P. 2/- Also ready built and tested 52/6. P. & P. 3/- A pair of TA1's are ideal for stereo.

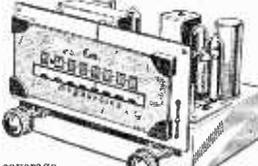**HARVERSON'S F.M. TUNER Mk. 1**

● F.M. tuning head by famous maker. ● Guaranteed non-drift. ● Set of measurable tuning. ● Frequency coverage 88-100 Mc/s ● Balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3in. glass). ● Self-powered using a good quality mains transformer and valve rectifier. ● Values used: EC085, two E250's and E280 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 3 1/2 in. ● All parts sold separately. Set of parts if purchased at one time. £5.19.6. plus 8/6 P. & P. and Inc. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye front panel and brackets £8.12.6. P. & P. 8/6.



Mark III Version as Mark I but with output stage. (ECL82) and tone control £7.7.0. P. & P. 8/6. Handsome Metal Cabinets. Choice of Black or Green. To fit Mark I, 25/-, P. & P. 3/-. To fit Mark II, 17/6. P. & P. 3/-. **SPECIAL PURCHASE TURRET TUNERS** By famous maker. Brand new and unused. Complete with PC034 and PC030 valves 34-38 Mc/s 1.F. Biscuits for Channels 1 to 3 and 8 and 9. Circuit diagram supplied. **ONLY 25/-** each. P. & P. 3/9.


**GORLER F.M. TUNER HEAD** 88-100 Mc/s 1.F. Mc/s 1.F. 15/-, plus 2/- P. & P. (EC085 valve, 8/6 extra).

**4-SPEED PLAYER UNIT BARGAINS**

All Brand New in Maker's Original Packing SINGLE PLAYERS  
GARRARD SP25 De Luxe...£12.10.8. Carr. 5/6  
B.S.R. GU7 with unit mounted pick-up arm. £4.18.8. Carr. 5/6  
E.M.I. with unit mounted pick-up arm. £4.9.6. Carr. 5/6  
AUTO CHANGERS  
LATEST B.S.R. UA25 Super Slim mono. £6.2.6  
B.S.R. UA16, £6.19.6. B.S.R. UA16. £6.19.6  
LATEST GARRARD AT6...£8.0.0  
Standard GARRARD Autoslim...£8.10.0  
GARRARD AT6...£10.10.0. Carr. 6/6 on each.  
All the above units are complete with 1/6 mono head and sapphire styli or can be supplied with compatible stereo head for 12/6 extra.

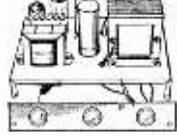**THE NEW HARVERSON KIT FOR THE HOME CONSTRUCTOR**

A really excellent all purpose A.C. mains 200/240V AMPLIFIER KIT TYPE HSL 'FOUR' 3 VALVE, 4 WATT USING EC083 EL84, E250 VALVES  
Special features include:



● Heavy duty double wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● All this builds onto a chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder etc. (No extras to buy). **PRICE 79/6** P. & P. 6/- Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with kits).

**QUALITY RECORD PLAYER AMPLIFIER**

A top-quality record player amplifier. Size 7in. w. x 2 1/2 in. d. x 3 1/2 in. h. This amplifier (was used in a 29 zn. record player) employs heavy duty double-wound mains transformer, EC083, EL84, E250 valves, separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested **PRICE 69/6** P. & P. 4/9  
ALSO AVAILABLE. Mounted on board with output transformer and 6in. speaker ready to fit into cabinet below. **PRICE 89/6** P. & P. 5/9.

**QUALITY PORTABLE R/PLAYER CABINET**

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player Unit. Size 18 x 14 x 8 1/2 in. **PRICE £3.9.6.** Carr. 7/6

**6 TRANSISTOR AND DIODE SUPERHET**

A first-class 2 waveband transistor superhet ● Printed circuit panel (size 8 1/2 x 2 1/2 in.). ● 3 pre-aligned transformers. ● High-gain Ferrite Rod Aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time. O.V. £4.5.0. P. & P. 2/6. (Circuit diagram 2/- free with set of parts).

**35 OHM SPEAKERS**

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables 8/6, 3 1/2in. 12/6, 5in. 17/6; 7 x 4in. 21/-, P. & P. 2/- per spkr.

**Portable CABINET**

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker. 25/-, P. & P. 2/6.

**COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET**

3 1P transformers one oscillator coil one driver transformer and wound Ferrite aerial (used, long and car aerial coupling) 32/6 complete post 2/- 6 transistor printed circuit board to match 8/6. Post 1/-. Circuit diagram 1/6 extra.


**LATEST MODEL B.S.R. TU/12 4-SPEED PLAYER AND PICK-UP**

**ONLY 69/6** Carr. 5/6  
7in. metal turntable. Low flutter performance. 200/250 v. shaded pole motor with 90 v. tap for valve heaters. High gain crystal pick-up with turnover 12/178 head complete with sapphire styli.



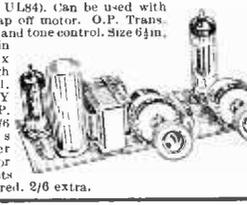**TWO VALVE GRAM AMPLIFIER ON PRINTED CIRCUIT BOARD**

(UY85, UL84). Can be used with 80 v. tap off motor. O.P. Trans. volume and tone control. Size 6 1/2 in. wide x 2 1/2 in. deep x 3 1/2 in. high overall. **ONLY 39/6** P. & P. 2/6 Mains dropper res. for filaments if required. 2/6 extra.



**SPECIAL PURCHASE!**

**FROM LEADING HI FI MANUFACTURERS**


7-10 watt OUTPUT TRANSFORMERS to match pair of ECL85's in push-pull to 3 ohm output. **ONLY 11/-** P. & P. 2/6. 7-10 watt ULTRA LINEAR OUTPUT TRANSFORMERS to match pair of ECL82's in push-pull to 3 ohm output. **ONLY 15/-** P. & P. 2/6. **SPECIAL MAINS TRANSFORMERS** to match either of the above. Tapped primary. Secondary 250v. 80mA half wave and 6.3v. 2 amps. **ONLY 12/6** P. & P. 3/6.

**NEW CARTRIDGE BARGAINS**

**RONETTE STEREO 105 CARTRIDGE.** Stereo/LP/78. Complete with two sapphires. Original list price 67/9. **OUR PRICE 24/-** P. & P. 1/- **GARRARD GC2 Mono complete.** List price 24/11. **OUR PRICE 12/6** P. & P. 1/-

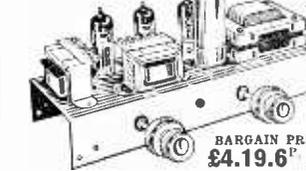**STEREO AMPLIFIERS**

Incorporating 2 ECL82's and 1 E250 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



**BARGAIN PRICE £4.19.6** P. & P. 6/6  
**SUPER DE LUXE** version of above incorporating ECL85 valves separate bass and treble controls and full negative feedback. 8 zns. P. & P. 6/6.

**SPECIAL BRAND NEW TRANSISTOR BARGAINS**

GET 15 (Matched Pair) 15/-; V15/100, 10/-; OCT1 5/-; OCT6 6/-; AP17 7/6; ORP12 10/8. Set of Mullard 6 transistors OC4, 2-OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6.

**EDISWAN MAZDA**

PXA101 6/8; XA103 6/6. R.F.1. Pack: 1-PXA102 Mixer: 2-PXA 101 I.F. Amp. (Pair) OC4 and OC45. R.F. 2. Pack: 2-PXA101 I.F. 1-PXA102 (osc. 1-PXA102 Mixer. L.F.1 Pack: Consisting of PXB113 Driver Matched pair PX171 mounted complete with heat sinks (Equip. OC81D and OC81). **ALL TRANSISTORS POST FREE.**

**HARVERSON SURPLUS CO. LTD.**

170 HIGH ST, MERTON, S.W.19 CHERRYWOOD 3985  
Open all day Saturday Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station (Please write clearly)  
PLEASE NOTE: P's & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. OVERSEAS ORDERS CHARGED EXTRA.  
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE RIGHT HAND PAGE FOR MORE ITEMS

**3-VALVE AUDIO AMPLIFIER  
MODEL HA34**



Designed for Hi-Fi reproduction of records A.V. Mains operation. Ready built on plate-d heavy gauge metal chassis size 4 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates Ect 83 E1.84, E280 valves, heavy duty double-wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, P. & P. etc. wired and tested for only **£4.50** 6/-

**BRAND NEW 3 OHM SPEAKERS**

5in., 12/8; 6 1/2in., 15/-; 8in., 21/-; 10in., 25/-; 12in., 27/6; (12in., 15 ohm, 30/-; 10in., 8in., 28/-; E.M.L. 134 x 5in. with high d.c. ceramic magnet 42/-; 15 ohm 45/-; 4in. HIGH FLUX TWEETER 3 ohm or 15 ohm imp. Famous British one 12" P. & P. 4 and 5in. 2/-; 6 1/2 and 8in. 2/6; 10 and 12in. 3/6 per speaker.

**TAPE DECKS**

**COLLARO STUDIO DECK** 4 operators, 3 speed push button control. Up to 7in. spools £10.10.0 P. & P. 7.6.  
**B.S.R. MONARDECK**. Single speed. 3 1/2in. per sec. simple control uses 3 1/2in. spools—£6.15.0 plus 7/6 cart. and ins. Taxes extra on both.

**BARGAIN OFFER CORNER  
MAINS TRANSFORMERS**

Fully shrouded, can be mounted upright or drop through. Tapped pri. 110, 200, 240v. Sec. 250v., 1 wave at 50mA and 6.3v., 2 amps. 1/71 Stack size 3 1/2 x 1 1/2 in. PRICE **12/6** P. & P. 3/6

ALSO semi-shrouded drop thro' type. Pri. 200, 220, 240v. Sec. 250v., 1 wave at 70mA and 6.3v. at 2 amp. ckt. Stack size 3 1/2 x 1 1/2 in. PRICE **11/-** P. & P. 3/-

**PRECISION 6-MINUTE DELAY ACTION SWITCH** (Clockwork actuated. Made by Smiths. Separate switching action at intervals up to 6 minutes. Each switch action set against current loading up to 15 amps at 250 volts. Suitable for photographic timer, sequence switching operations, etc. etc.). Brand new and unused units offered at a fraction of their true value. OUR PRICE ONLY 10/- each. P. & P. 1/6 (3 or more post free). Special quotations for quantity.

**HEAVY DUTY NON INDUCTIVE D/C MICRO SWITCH**. Conservatively rated 10 amps at 250v. standard one-hole fitting. Body size 1 1/2 x 1 1/2 in. Deep inc. terminals 3/8" each. P. & P. 1/- (6 or more post free).

**NEON A.C. MAINS INDICATOR**. For panel mounting, cut out size 1 1/2 x 3/4 in. 3/4 in. deep inc. terminal. White case with 280 acvms. bright light. For mains 200-250v. 2 pin. cirm. P.P. 6d. (6 or more post free).

**VYNAIR AND BEXINE SPEAKER AND CABINET FABRICS**. Approx. 54in. wide (Usually 35/- yard. OUR PRICE 13/6 per yard length. P. & P. 2/6 (min. one yd.) S.A.E. for samples.

**ACOS CRYSTAL MIKES**. High imp. For desk or hand use. High sensitivity 18/6. P. & P. 1/6.  
**TLB CRYSTAL STICK MIKE**. Listed at 48/- OUR PRICE 13/6. P. & P. 1/6.

**T.C.C. SUPPRESSOR CONDENSERS**. 250v. A.C. .005 + .005 x 1 1/2 in. tubular can 2 1/2 in. dia. 2 for 3/- post free.

**TRANSISTOR DRIVER AND O/P TRANSFORMERS**. (Tapped 3 ohm and 15 ohms output). Plus 4 suitable Transformers giving approx. 1 watt output 25/-, P. & P. 2/6.

**2-GANG .0005 TUNING CONDENSERS**. 2 1/2 in. h. x 2 1/2 in. d. x 1 1/2 in. w. with built-in trimmer. 4/6. P. & P. 2/-.


**MATCHED PAIR OF 21 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS**. Stack size 1 1/2 x 1 1/2 in. Output traus. tapped for 3 and 15 ohm output 10/- (each). P. & P. 2/-

**BRAND NEW PLESSEY**. 12v. 4-pin. non-synch. vibrators. Type 12 1.481. ONLY 9/8. P. & P. 1/6 each.

**TWIN TELESCOPIC AERIAL**. Comprising two 3-section heavily chromed aerial. Closed 12in. each extending to 32in. each. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for P.M. or T.V. 12/6. P. & P. 2/-  
**4-WAY NON-TANGLE TELEPHONE CABLE**. Latest spring back coil type. extends 12ft. to 5ft. Complete with rubber bushes. 4/6 each P. & P. 1/6.

Harverson Surplus Co. Ltd.

**PRICE SPECIAL RADIO CHASSIS OFFERS**

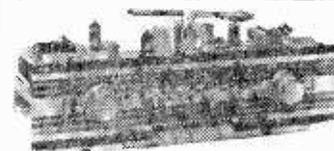

Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Complete with two 10" elliptical loudspeakers plus a mono/stereo 4-speed autochanger. Complete £29.19.6. Chassis only 19/- gns. Special terms available of £4.10.0 deposit followed by 18 monthly payments of £1.13.0 (total H.P. of £34.4.0) + 15/- P. & P. Send £5.5.0 now.

**IMPERIAL HI-FI STEREOGRAPHIC RADIOGRAM CHASSIS**



The Imperial stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons. Long-Medium-Short and VHF bands with two 10" loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete 39 1/2 Gns. Chassis only 29 1/2 gns. Special terms available of £6.4.6 deposit followed by 24 monthly payments of £1.15.10 (total H.P. £44.4.6) + 17/6 P. & P. Send £7.2.0 now.

**HI-FI EMPRESS RADIOGRAM CHASSIS**



This fabulous 'Empress' Hi-Fi radiogram chassis is offered complete with 10" loudspeaker plus 4 speed autochanger. At only 23 gns this is the bargain of the year. Chassis only 15 1/2 gns. Special terms available of £3.12.6 deposit followed by 18 monthly payments of £1.6.7 (total H.P. £27.11.0) + 15/- P. & P. Send £4.7.6 now.

All Lewis Radio equipment (including valves) are fully guaranteed for one year. Send your cheque or P.O. today while stocks last to Dept. P.115.

**LEWIS radio**  
LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE  
LONDON, N. 14. Telephone: PAL 3733 / 9666

**NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO and ELECTRONICS**

It's the most exciting news of the year! Just imagine. You can get 35 large, fact-packed lessons for little more than 1/- per lesson! The lessons are crystal clear, practical, easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert.

Compares favourably with some courses costing ten times as much. You save because you receive all the lessons at one time and are not required to purchase equipment you do not need. This is a real home-study course that has been bound into one giant 8 x 11in. 216 page manual. Each page is divided into two columns. A wide column features the text, while a narrow column at the side has the instructor's comments, helpful suggestions and additional pictures to simplify the difficult parts. Everyone can benefit from this practical course. No old-fashioned (or pseudo modern) methods used here, just straight forward, easy to understand explanations to help you make more money in electronics.

The price! Only 39/6 plus postage 1/6.  
Terms! Why of course! See Coupon.

**OTHER COURSES AVAILABLE**  
**RADIO COURSE** (23 lessons, price 36/-)  
**TELEVISION COURSE** (price 38/-)

**UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION**

You must be convinced that this is the best value you have ever seen in Electronics, Radio or T.V. Training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a full seven days. IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE BOOK VALUED 5/-. Tick on the coupon one book for each course ordered with full cash. These free books are authoritative, and loaded with information. Would cost at least 5/- each if bought separately—by sending cash you reduce book-keeping and other costs which savings we pass back to you.

**— FREE TRIAL OFFER —**

Pay only 5/- per week if you wish. Clip coupon right now for this special offer.

To: Sim-Tech Technical Books, Dept. ETV10, Gater's Mill, West End, Southampton, Hants.

Please send the following courses for a full seven days' trial.

- No. 1. RADIO COURSE. 37/6, incl. postage.
- No. 2. RADIO & ELECTRONICS COURSE, 41/6, incl. postage.
- No. 3. TELEVISION COURSE. 37/6, incl. postage.

(Free trial customers tick one only please).

If not delighted, I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price of 5/- weekly until paid.

Tick here if enclosing full purchase price.

Please send me

FREE TRANSISTOR CIRCUITS BOOK.

FREE OSCILLOSCOPE BOOK.

Amount enclosed £.....

I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers please send full amount (including Ireland).

Name.....  
Address.....  
City..... County.....



The **PUNCH** you need!

**HOLE PUNCHES**

Instant Type 3/4" diameter ... ..	6/10 ea.
Screw-up Type 3/4" diameter Toggle switch ...	8/6 "
" " " " " " " " " " " "	8/6 "
" " B7G " " " " " " " "	9/- "
" " B8A, B9A... " " " " " "	9/6 "
" " " " " " " " " " " "	10/2 "
" " " " " " " " " " " "	10/8 "
" " " " " " " " " " " "	11/8 "
1 1/4" diameter Int. Octal... ..	13/4 "
" " " " " " " " " " " "	16/2 "
" " " " " " " " " " " "	18/10 "
" " B9G " " " " " " " "	21/8 "
" " " " " " " " " " " "	24/4 "
2 1/2" " " Meter " " " " " "	33/2 "

Complete Set £9.3.6.

No extra charge for postage and packing in the U.K.

Now supplied by:

**TOMPKINS & LONGMAN LTD.**  
237 GIPSY ROAD  
WEST NORWOOD, S.E.27  
Tel. Gipsy Hill 5000

ONLY 7' 6" LONG!

## LISTEN

AND ENJOY THE  
WORLD'S RADIO AMATEUR  
AND BROADCAST STATIONS WITH  
THE GREATEST OF EASE !!!

ONLY 7' 8" LONG!

WE HAVE SOLVED your aerial problem for WORLD-WIDE RECEPTION—NO MATTER WHERE YOU LIVE !!!  
World Expert Radio Amateur W1BB (U.S.A.) claims the "JOYSTICK" aerial—easier to read stations than with his massive 520' VEE aerial 70' high. ZL4GA, who is probably NEW ZEALAND'S best known Radio Amateur, has scrapped his outstanding 300' 45' high aerial and has WORKED ALL CONTINENTS on the JOYSTICK in under 12 hours !!!

"CQ" the Radio Amateur's journal claims JOYSTICK better for reception than the world popular DIPOLE (four different receivers used to confirm this decision).


YOU CAN BE THE PROUD OWNER OF THE WORLD'S MOST VERSATILE & COMPACT "JOYSTICK" COMPLETE RECEIVING SYSTEM FOR AS LITTLE AS  
£5.5.0 (DX-MAGNET system), £6.6.0 (Standard system), £7.7.6 (De-luxe system) including carriage and packing.

Money Back if not Delighted

Not convinced? Then send for brochure and showers of testimonials to:—

**PARTRIDGE ELECTRONICS LTD**  
(Dept. P.W.)  
CAISTER HOUSE, PROSPECT ROAD,  
BROADSTAIRS, KENT  
I.R.C. Exhibition Stand No. 26

## BBC2 (625 LINE) TV AERIALS

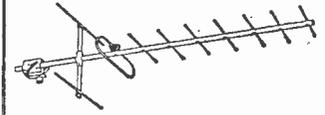

Mast Mounting Arrays, 9 element 45/-; wide spaced high gain, 11 element 55/-; 14 element 62/6. Wall Mounting with (Cranked Arm) 9 element 60/-; wide spaced high gain, 11 element 67/6; 14 element 75/-; Chimney Arrays Complete, 9 element 72/-; wide spaced high gain, 11 element 80/-; 14 element 87/6. Loft Arrays, 7 element 32/6; wide spaced high gain, 11 element with Tilting Arm, 62/6; 14 element 70/-; All high gain units have special Multi-rod Reflector. Low loss Co-axial cable 1/6 per yard. VHF transistor pre-amps from 75/-.

## BBC · ITV · F.M. AERIALS



B.B.C. (Band D). Tele-scope loft 21/-; External S/D 30/-.  
I.T.V. (Band 3), 3 Element loft array 25/-, 5 element 35/-; Wall-mounting, 3 element 35/-, 5 element 45/-.  
Combined B.B.C./I.T.V. Lofts 1+3, 41/3; 1+5 48/9; Wall mounting 1+3 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.  
VHF transistor pre-amps from 75/-.

F.M. (Band 2). Loft S/D 12/6. "H", 30/-; 3 element, 52/6. External units available Co-ax cable 8d. Yd., Co-ax plugs, 1/3. Outlet boxes 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 3/6. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept P.W.)**  
3b Godstone Road, Kenley, Surrey  
CRO 2527

## 2 METRES 4

The thrills of VHF Amateur Radio! Complete kit, 70-150 Mc/s. costs only 42/6 (by post, UK, 3/6 extra) also now available. Short-Wave kit, model TR2, 10-180 metres. Ideal for beginners to Ham radio via simplified "Easy-Build" step-by-step instruction from 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Regd.) precision standard products tried and trusted by Amateurs everywhere.

**JOHNSONS (Radio)**  
St. Martins Gate, Worcester

## DIGITAL COMPUTER

A simple digital Adder/Subtractor using switches and lamps only. A fascinating demonstration of Binary Arithmetic. Full circuit, with notes on the Binary System, 3/6, post free.

**MULTIMETERS.** Illus. leaflet on request. EP10K, 10,000 o.p.v., 67/6, post 2/-. EP20K, 30,000 o.p.v., 105/-, post 2/6. EP50K, 50,000 o.p.v., 145/-, post 2/6. Leather case for EP30K, 17/-; EP50K, 25/-, post 1/6.

1% High Stability Resistors—2/- each. 1/2 W. Full range 10 Ω to 10M Ω. Many special non-standard multimeter values in stock.  
**Audio-I.F.-R.F. Oscillator.** Simple transistor square wave circuit, multi-frequency output from audio up to 1.8 Mc/s. Variable amplitude. For "Signal Injection" rapid receiver and amplifier testing, or for Morse practise. All parts except case and battery 10/-, post 1/-.

**PLANET INSTRUMENT CO.,**  
25(w) DOMINION AVENUE, LEEDS 7

## SERVICING ELECTRONIC ORGANS

by Pittman & Oliver. 30/-, P. & P. 1/3  
101 Ways to use your Oscilloscope by Middleton. 21/-, P. & P. 1/-.  
101 Ways to use your Signal Generator by Middleton. 18/-, P. & P. 1/-.  
Principles of Transistor Circuits new ed. by Amos. 25/-, P. & P. 1/-.  
Transistor Specifications Manual by Sams. American, Jap. etc. 24/-, P. & P. 1/-.  
Radio Amateur Mobile Handbook by Caringham. 24/-, P. & P. 1/-.  
A Guide to Amateur Radio new ed. by R.S.G.B. 5/-, P. & P. 6d.  
Radio Amateur Examination Manual new ed. by R.S.G.B. 5/-, P. & P. 8d.  
Where possible 24 hours service guaranteed


**UNIVERSAL BOOK CO.**  
12 Little Newport Street, London, W.C.2  
(adjoining Lisle Street)

## A Depth Micrometer —

This Depth Micrometer (with extra spindle for 1" — 2" conversion), usual price 21/3, is given FREE as part of the SPECIAL OFFER of a 3-instrument set comprising:  
1" Micrometer usual price 13/6  
2" Micrometer usual price 16/6  
1" — 2" Depth Micrometer FREE (save 21/3!)  
Total 30/- plus p. & p. 2/6,  
Each Micrometer can be bought separately for the individual prices shown (plus 1/6 p. & p.)  
Ideal Micrometers for Hobbyists, Students and General Industrial use. Correct to .0009 of an inch.  
Put TOOLMAKER precision into Your project  
SEND NOW ONLY 32/6 POST PAID TO:  
DEPT. J, A.G.M. INDUSTRIES LTD.,  
Holloways Lane, Welham Green, Nr. HATFIELD, Herts.



**FREE!**

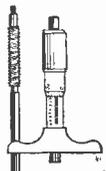

1" — 2" Depth Micrometer

## 96 pages of factual tabulated data . . . "PRACTICAL WIRELESS" RADIO AND TELEVISION REFERENCE DATA

Compiled by J. P. Hawker

Contains full details of colour codes; everyday formulae for calculating the values of biasing components, potential dividers, resonance, gain, etc.; aerial dimensions; a quick frequency-wavelength conversion table; stations and frequencies; common symbols and abbreviations; notes on amateur radio and a list of call-sign prefixes; communication receiver I.P.s.; mathematical data including logarithm tables; wire and cable data; battery equivalents; valve, transistor and picture tube pin connections, bases, ratings and equivalents, including selected CV types. 96 pages, illustrated, over 62 pages of tables.

10s. 6d. FROM ALL BOOKSELLERS  
... or, in case of difficulty 11s. 6d. by post from  
GEORGE NEWNES LTD., Tower House, NEWNES  
Southampton Street, London, W.C.2.

# TRANSISTOR BARGAINS!

OC 71 equivalent	...	1/- each, £1 for 25, £3 for 100
NKT 124/5 switching type	...	2/- each, 10/- for 6
2G 371	...	2/6
OC 25	...	10/-
OC 35	...	10/-
NKT 405	...	10/-

Packet containing:—  
 3 2G417: 2 2G371: 1 2G381: 1 2G339: 1 diode ... £1 complete  
 (For making superhet with complementary symmetry transformerless output stage)  
 Diodes ... .. 1/-  
 Zener Diodes, ZÉ 12, ZB 4.3 ... .. 5/-  
 BY 100 Rectifiers ... .. 7/6  
 Colvern 10 ohm pre-sets ... .. 2/6  
 50K ohm pre-sets ... .. 1/6  
 1K ohm Skeleton pre-sets ... .. 1/-  
 Resistors 1/4th and 1/10th watt. Your choice of value.  
 Minimum 10 of any value ... .. 10/- per 100  
 Mixed values and wattages ... .. 50/- per 1,000  
 Condensers. 2.2uf., 500uf., .0001, .001, .002, .005, .02, .04uf. ... .. 7/6 per 100, £3 per 1,000

## RELAYS

700 ohm or 2,500 ohm coil. Transparent dust cover.  
 2 pairs of change-over contacts. PLUG-IN TYPE.  
 Base included in price ... .. 25/- each

## ELECTROLYTIC CONDENSERS, Tubular

2uf. 4uf. 8uf. 16uf. 32uf. 64uf. 15V special price	...	1/2 each
2uf ... 30 volt	200uf ... 30 volt	All at 2/- each
25uf ... 30 volt	250uf ... 6 volt	
50uf ... 15 volt	250uf ... 15 volt	All at 2/- each
64uf ... 25 volt	320uf ... 2.5 volt	
100uf ... 3 volt	400uf ... 6.4 volt	All at 2/- each
100uf ... 6 volt	500uf ... 15 volt	
100uf ... 18 volt	500uf ... 50 volt	All at 2/- each
100uf ... 30 volt	500uf ... 50 volt	
1,000uf ... 6 volt		All at 2 1/2 each
1,000uf ... 12 volt		
1,000uf ... 15 volt		
1,000uf ... 25 volt		
1,000uf, 50 volt Can-type	...	3/-

### Special offer:—

Television smoothing condensers, 200/100uf or 200/200uf, 275 volt. Whilst stocks last ... .. 6/6 each  
 Special circuit and components to make transistorised:—  
 HIGH FIDELITY LOW-NOISE PRE-AMPLIFIER ... .. 30/-  
 RUMBLE AND SCRATCH FILTER ... .. 30/-  
 REV. COUNTER FOR CAR (excluding meter) ... .. 10/-  
 SIGNAL INJECTOR ... .. 10/-  
 VERY HIGH IMPEDANCE (1 MEG. OHM/VOLT) MULTIRANGE VOLTMETER (excluding meter) ... .. 30/-  
 20 MEG. OHM. OHM-METER (excluding meter) ... .. 15/-  
 Brand-new meters suitable for above application ... .. 30/- each  
 New 4in. LOUDSPEAKERS ... .. 10/- each  
 Midget earphones with plug and lead ... .. 5/-  
 Magnetic Lapel Microphone with plug and lead ... .. 10/-  
**VERNIER DIALS**  
 1 in., 8:1 ratio, 180° Calibration ... .. 14/-  
 2 in., 8:1 ratio, 180° Calibration ... .. 15/6  
 3 in., 8:1 ratio, 180° Calibration ... .. 17/-  
 Very useful pocket size 1,000 o.p.v. Multimeter ... .. £3

### Extra Special Bargain!

ACOS PICK-UP HEADS. Complete with needles.

Monaural	...	14/-
Stereo	...	21/-
Stereo with Diamond Needles	...	28/9

For orders of 10/- or less please add 6d. toward postage. Regret that no orders can be accepted under 5/-. Orders over £5 deduct 5% Cash Discount.

## G. F. MILWARD

17 Peel Close, Drayton Bassett  
 Near Tamworth, Staffordshire

Tamworth 2321

Post only



**UNLIMITED OPPORTUNITIES** exist today for "getting on" ... but only for the fully trained man. Let ICS' tuition develop your talents and help you to succeed.

**STUDY IS EASY** with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

**YOUR ROAD TO SUCCESS** can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

## Take the right course now . . .

- ADVERTISING & ART  
Copywriting Cartooning  
Layout & Typography  
Commercial Illustrating  
Oil & Water Colour
- BUILDING & CIVIL ENGINE  
Architecture, Bricklaying  
Building Construction  
Builders' Draughtsmen  
Builders' Quantities  
Interior Decorator  
Quantity Surveying  
Heating & Ventilation  
Carpentry & Joinery
- COMMERCE  
Book-keeping  
Accountancy & Costing  
Business Training  
Office Training  
Purchasing Storekeeping  
secretaryship  
Shorthand & Typing  
Computer Programs  
Small Business Owners
- DRAUGHTSMANSHIP  
Architectural Mechanical  
Drawing Office Practice
- ELECTRONICS  
Computers  
Electronic Technicians  
Industrial Electronics
- FARMING  
Arabi & Livestock  
Pig & Poultry Keeping  
Farm Management & Accounts
- GENERAL EDUCATION  
G.C.E. subjects at Ordinary & Advanced Level  
Good English  
Foreign Languages
- HORTICULTURE  
Home Gardening  
Park Gardening  
Market Gardening
- MANAGEMENT  
Business Management  
Hotel Management  
Industrial Management  
Office Management  
Personnel Management  
Public Relations (I.P.R.)  
Transport Management  
Works Management  
Work Study  
Foremanship
- MECHANICAL & MOTOR ENGINE  
Engineering Maths  
Diesel Engines Welding  
Industrial Instrumentation  
Workshop Practice  
Refrigeration  
Motor Mechanics, etc.
- POLICE  
Entrance Examination  
Police Promotion (Educ. Subj.)
- PHOTOGRAPHY  
Practical Photography  
RADIO, TV & ELECTRICAL  
Servicing & Engineering  
Radio Construction (with Kit)  
P.M.G. Certificates  
Telecommunications  
Electricians  
Electrical Contracts
- SELLING  
Company Reps.  
Sales Management  
Marketing
- WRITING FOR PROFIT  
Television Scriptwriting  
Short-story Writing  
Free-lance Journalism

**INTENSIVE COACHING** for all principal examinations —G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

*Start today the I.C.S. way!*

### INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....

Address.....

Occupation .....

11.65

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Head Office and Warehouse:
44A WESTBOURNE GROVE
LONDON W2
Tel.: PARK 5641/2/3

Z & F AERO SERVICES LTD.

Please send all correspondence and Mail Orders to the Head Office
When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 1/6. No C.O.D. orders accepted

Retail Shop:
36 TOTTENHAM COURT ROAD
LONDON W1
Tel.: LAMHAM 8403
Open all day Saturday



Table listing various electronic valves with columns for part numbers, descriptions, and prices. Includes sections for 'First Quality Fully Guaranteed' and 'Aerov Brand Electronic Valves'.

TRANSISTORS

Table listing transistor models and prices, including OC29, OC24, OC25, etc.

GERMANIUM DIODES

Table listing germanium diode models and prices, including OA6, OA7, OA73, etc.

ZENER DIODES

Table listing zener diode models and prices, including OA2200, OA2201, etc.

WIRELESS SETS No. 38A.F.V.

Small battery operated Transmitter-Receiver covering frequency range of 7.3-9mc/s. Transmits over a distance of at least 2 miles. Requires external batteries of 180 v. and 12 v. in perfect condition, complete with all valves, but not tested. Supplied complete with circuit diagram-12/6 each. Packing and postage 5/-.

Two transistor receivers £1.75 post paid. Also available: 12 point connections 4/6 each. 3-section aerial with base 12/6.

NUVISTORS

2CW4 (2V. heaters) or 6CW4 (6.3V. heaters)- for VHF tuners and F.M. Applications 12/- GD84-similar to 6CW4 but with remote cut-off for use in weak signal areas 15/- 7886 General Purpose Industrial Triode, high X 22/6 7896 General Purpose Industrial Triode, high X 22/6

Sets of 2-2N410 and one 2N12 9/-
Bases for the above 2/9 each.

# PRACTICAL WIRELESS

## blueprints

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

### DOUBLE-FEATURE BLUEPRINTS

The Strand Amplifier ... .. } The PW Signal Generator ... .. }	5/-
The Savoy VHF Tuner ... .. } The Mayfair Pre-amplifier ... .. }	5/-
The Berkeley Loudspeaker Enclosure } The Luxembourg Tuner ... .. }	5/-
The PW Troubadour ... .. } The PW Everest Tuner ... .. }	7/6
The PW Britannic Two ... .. } The PW Mercury Six ... .. }	6/-
Beginner's Short Wave Two ... .. } S.W. Listener's Guide ... .. }	5/-
Beginner's 10-watt Transmitter Transmitting and Aerial Data... .. }	5/-
PW "Sixteen" Multirange Meter ... .. } Test Meter Applications Chart ... .. }	5/-
The Celeste 7-transistor Portable Radio } The Spinette Record Player ... .. }	5/-
Transistor Radio Mains Unit ... .. } 7 Mc/s Transceiver ... .. }	5/-

### SINGLE-FEATURE BLUEPRINTS

The Tutor ... .. }	3/-
The Citizen ... .. }	5/-
The PW Pocket Superhet ... .. }	5/-
The PW 35-watt Guitar Amplifier ... .. }	5/-
The Mini-amp ... .. }	5/-
The PT Multimeter ... .. }	5/-
The Autocrat Car Radio ... .. }	5/-
The Beginner's Short Wave Superhet ... .. }	5/-
The Empire 7 Three-band Receiver ... .. }	5/-
Electronic Hawaiian Guitar ... .. }	5/-

**PLEASE NOTE** that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

## QUERY SERVICE

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

**(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

### QUERY COUPON

This coupon is available until 4th November, 1965 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, NOVEMBER, 1965

### 1 MW/LW POCKET SUPERHET RADIO TO BUILD



- ★ 6-transistor plus diode.
- ★ Push-pull speaker output.
- ★ Easy printed circuit.
- ★ Slow geared tuning.
- ★ Full MED and long waves.
- ★ Moulded cabinet 5 x 3 x 1 1/4 in.

**TOTAL COST TO BUILD 85/-**

P.P. 2/- (Battery 2/6, Phone 5/-)  
Amazing sensitivity and selectivity.

### 2 TWO WAVEBAND ALL TRANSISTOR CAR RADIO TO ASSEMBLE



**TOTAL COST TO BUILD £8.19.6**

P.P. 3/6.

- ★ Supplied as factory built assemblies—just interconnect.
- ★ 6-transistor push-pull design.
- ★ Push-button wavechange—full tuning range.
- ★ Size 7 x 4 x 2 in.—fits any car—chromed front dial.
- ★ Full superhet circuit.
- ★ Units available separately.
- ★ Guaranteed high performance and quality.

### 3 TWO AND FOUR TRACK PORTABLE TAPE RECORDERS TO ASSEMBLE

Prebuilt equipment—6 valves—Collaro studio decks—portable cabinets—8" x 5 in. speakers. Complete recording and playback.




- ★ Two track deck 10 gns. P.P. 5/-.
- ★ Amplifier 11 gns. P.P. 3/6.
- ★ Cabinet with speaker, 5 gns. P.P. 3/6.

or **SPECIAL PRICE £26**

- ★ **Four Track deck £13.19.6.** P.P. 5/-.
- ★ Amplifier 12 gns. P.P. 3/6.
- ★ Cabinet and speaker 5 gns. P.P. 3/6.

or **SPECIAL PRICE £30** P.P. 8/6 **FOUR TRACK**

### 4 VHF FM TUNER TO BUILD

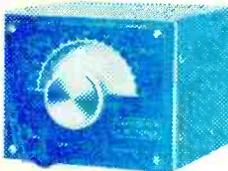

- ★ 5-transistors, 4-diodes.
- ★ Printed circuit superhet.
- ★ Tuning range 87 to 105 Mc/s.
- ★ RF stage and double tuned IFT's—9 volt 9 mA operated.

- ★ All parts sold separately.
- ★ Output up to 1 volt.
- ★ Size 4 x 3 1/2 x 2 1/4 in.

P.P. 2/6 (complete with front panel)  
★ Cabinet Assembly 20/- extra.

**TOTAL COST TO BUILD £6.19.6**

### 5 5 WATT AND 1 1/2 WATT PACKAGE AMPLIFIERS NEW DESIGN 5 watt Unit



- ★ 6-transistor push-pull printed circuit designs.
- ★ Peak output 10 watt and 3 watt.
- ★ Size only 2 1/2 x 2 x 1 1/4 in.
- ★ 5 watt, 18 volt; 1 1/2 watt, 9/12 volt.
- ★ Output for 3 to 2 ohm speakers.
- ★ 7 mV into 1 Kohm, 30 c/s to 16 kc/s.

**PRICES 1 1/2 WATT BUILT 65/-** P.P. 1/6 **5 WATT 79/6** P.P. 1/6

**NEW FM POCKET RECEIVER KIT £5. 19. 6.**  
**SINCLAIR.** Micro-6, 59/6; X10 Kit, £5.19.6; X10 built, £6.19.6; X20 Kit, £7.19.6; X20 built, £9.19.6.

**HENRY'S RADIO LTD.**  
303 EDGWARE RD., LONDON W2

Open Mon. to Sat. 9-6  
Thurs. 1 p.m.

PADdington 1008/9 Open all day Saturday  
Let us quote for Parts for your circuit.  
Send a list for quick reply.

## PROVED and TESTED DESIGNS

FULL AFTER SALES SERVICE AND GUARANTEE  
UNBEATABLE FOR PERFORMANCE AND VALUE  
★ DETAILED LEAFLETS FREE ON REQUEST ★

### NEW! "GLOBEMASTER"

- ★ SHORT WAVES
- ★ MEDIUM AND LONG WAVES

The only FULLY tunable 3-Waveband Radio available to the Home Constructor. Printed circuit. 1 watt output. Geared tuner. Car aerial socket with special circuits. Push-button unit. 6-transistor high gain superhet design. Size 11 x 7 1/2 x 3 1/2 in. Case fabric covered with chromed front and fittings. All parts sold separately and fully guaranteed



**TOTAL COST TO BUILD £8.19.6** P.P. 3/6.

★ "CONVAIR" as previously advertised. Two Waveband Portable to Build, still available. **Total Cost £7.19.6.** P.P. 2/6.

### 10 WATT AND 20 WATT AMPLIFIERS

#### 1 ALL TRANSISTOR PRE-BUILT AND TESTED UNITS

Units 1 and 2

#### ★ POWER AMPLIFIERS

10 watts RMS music power output. 20 watts peak. 6-transistor designs. Response 40 c/s to 20 kc/s. 100 mV sensitivity.

Unit 1. For 12/15 ohm speakers. 40 volt supply. **PRICE BUILT £5.19.6** P.P. 2/6

Unit 2. For 3 to 5 ohms. 24 volt. **PRICE BUILT £5.10.0** P.P. 2/6

(Mains units Mono 59/6 Stereo 69/6)

#### ★ PREAMPLIFIERS—MONO AND STEREO VERSIONS.

8 inputs, 1 1/2 mV to 300 mV at 1K to 500 Kohm. Response 30 c/s to 20 kc/s. Complete range of controls.

Unit 3. Mono full function preamplifier.

Size 9 1/2 x 2 1/2 x 2 in.  
(Brown/Gold front panel, 8/6).

Unit 4. Simplified version of Unit 3. Price built 65/-. P.P. 1/6.

Unit 5. Stereo preamplifier for use with two power amplifiers. Size 9 x 3 1/2 x 1 1/8 in. **PRICE BUILT £10.19.6** P.P. 3/6. (Brown/Gold panel 12/6).



★ **LOW NOISE—LOW DISTORTION QUALITY DESIGNS**—Enables complete Mono or Stereo equipment to be assembled at a fraction of the cost of a commercial comparable design. Simple to interconnect, outstanding quality.

#### 6 VHF FM TUNER TO ASSEMBLE

- ★ Supplied as prebuilt and aligned units plus metal work just interconnect.
- ★ 88 to 108 Mc/s. FM tuning.
- ★ 100 mV to 100 Kohm output.
- ★ 6-transistor printed circuit. Superhet design.
- ★ Size 9 1/2 x 3 1/2 x 4 in.



**TOTAL COST TO BUILD £12.17.6** P.P. 2/6

#### CATALOGUE

Fully detailed and illustrated catalogue. Now 96 pages. All types of components and equipment at competitive prices. Price 2/6 post paid.

**FREE! New 8 page book with details of over 80 projects, available from stock. Uses transistors, light cells, scrs, etc., etc. Ask for your FREE copy.**