

PRACTICAL WIRELESS

MARCH
1969

310

PROGRESSIVE
ALL-WAVE
SUPERHET




ALSO: HOME WORKSHOP PRACTICE

ADCOLA

SOLDERING
EQUIPMENT

THE PEAK OF EFFICIENCY!

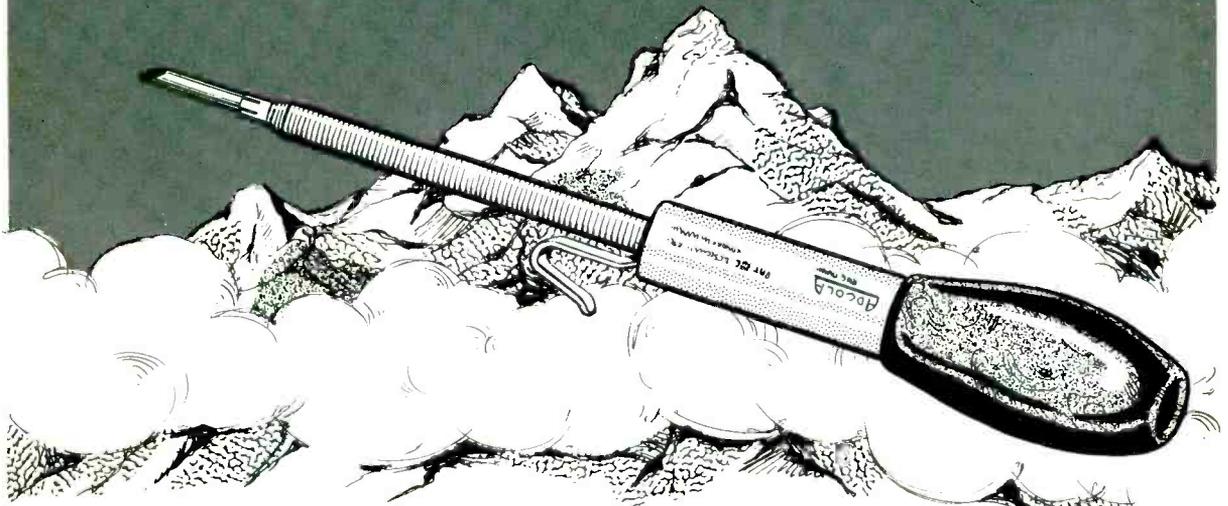

ILLUSTRATED

Model 64. $\frac{3}{16}$ " Bit
25 WATTS PRICE 36/-

**WIDELY USED BY INDUSTRY &
THE DISCERNING ENTHUSIAST FOR RADIO,
T.V. & PRINTED CIRCUIT WORK**

FROM YOUR LOCAL DEALER
OR SEND DIRECT TO:-

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON. S.W.4.
TELEPHONE 01-622-0291**

Send coupon for latest leaflet

Name	_____
Address	_____

Lasky's Radio

AUDIO-TRONICS PICTORIAL 1969 FREE!



This year we celebrate our 36th anniversary by bringing to you this great new issue of our "AUDIO TRONICS PICTORIAL" now 16 colour pages in large 16 x 11 in. format, simply packed with 1000's of items from our vast stocks of EVERYTHING for the Radio and Electronics Hobbyist, Hi-Fi Enthusiast, Serviceman and Radio Ham. Plus 100's of Lasky's exclusive STAR PRICE Bargains.

All items are available by Mail Order or from any of our branches.

FREE Just send your name, address and 1/- FOR POST ONLY, and inclusion on our regular Mailing List.

Branches

- 207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271
Open all day Saturday early closing 1 p.m. Thursday
- 33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605
Open all day, 9 a.m. — 6 p.m. Monday to Saturday
- 152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833
Open all day Thursday early closing 1 p.m. Saturday

High Fidelity Audio Centres

- 42 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573
Open all day Thursday, early closing 1 p.m. Saturday
- 118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789
Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE, YORKSHIRE.

Telephone: Cleekeheaton 2866

Indicator Unit type 26

Size 12x9x9in. with outer case. Fitted with 2½in. tube C.R.T. type CV1526. Nine B7G valves. Clean condition, but not tested. 32/6, p. & p. 10/-.

Lumator and Secant Gear Unit. Delight for the model maker. 12/6, p. & p. 8/6.

Silicon Rectifier 500mA, 800 P.I.V. No duds. 2/6, post paid. 24/- per dozen, post paid.

Jap Ear Piece, Magnetic 8 ohm. Small and large plug. 1/11, post paid.

Reclaimed TV tubes with six months guarantee. 17in. type AW43/88, AW43/80, 40/-; MW43/69, 30/-; 14in. types, 17/-; All tubes, 12/- carriage.

Speakers removed from TV sets. All PM and 3 ohms. 8in. round and 8x5in., 6/6, p. & p. 3/6.

6in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

6x4in., 3/-, p. & p. 3/-; 6 for 24/-, post paid. 7x4in., 5/-, p. & p. 3/-; 6 for 34/-, post paid. 5in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

Slot Speakers, 8x2½in., 5/-, p. & p. 3/-; 6 for 30/-, post paid.

Untested 12-channel 14in. TV sets, 20/-, carriage 15/-. Passenger train, double rate. **Untested Pye, KB, RDG, Ekco 17in. TV sets, Bush 17in. TV sets, 50/- each, carriage 15/-.** Passenger train double rate.

VALVE LIST

Ex. Equipment. 3 months' guarantee

Single Valves Post 7d., over 3 Valves p. & p. paid. 10F1, EF80, EB91, ECL80, EF50, PY82, PZ30, 20P3. All at 10/- per dozen, post paid.

ARP12	1/6	EF91	9d.	PL81	4/-	U329	5/-	185BT	8/6
EB91	9d.	EY51	2/6	PY33	5/-	U251	5/-	20D1	3/-
EF85	3/-	EY86	5/-	PY81	1/6	6B8	1/8	20P1	5/-
EBF80	3/-	PCC84	2/-	PY82	1/6	6BW7	2/6	20P3	2/6
ECC81	3/-	PCF80	2/-	PZ30	5/-	6K7	1/9	30PL1	5/-
ECC82	3/-	PCL82	4/-	U191	5/-	6U4	5/-	30P12	5/-
ECC83	4/-	PCL83	5/-	U281	5/-	6V6	1/9	30F5	2/6
ECL80	1/6	PL36	5/-	U282	5/-	6P28	5/-	30FL1	5/-
EF50	1/-	PL38	6/-	U301	5/-	10P13	2/6	6/30L2	5/-

17in.—£11.10.0

19in. SLIMLINE

SOBELL—24 Gns.

**TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS**

FREE ILLUSTRATED
LIST OF TELEVISIONS

17"–19"–21"–23"

WIDE RANGE OF MODELS

SIZES AND PRICES

DEMONSTRATIONS DAILY

**TWO-YEAR GUARANTEE
TUBES 100% REGUNNED**


14in.—69/6 17in.—89/6

21in. and ALL SLIMLINE TUBES 99/6

EXCHANGE BOWLS. Carr. 10/6


EX MAINTENANCE TESTED TUBES

17in.—35/-, Carr. 5/- (not slimline)

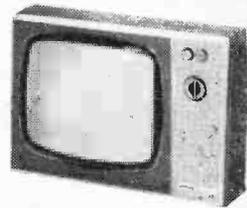

COCKTAIL/STEREOGRAM CABINET £25

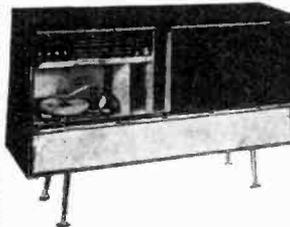Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35½in., width 52½in., depth 14½in. Legs 1gn. extra.



Speakers 6/6: 2"–75Ω. 2½"–35Ω. P. & P. 2/6. Acos Mics. 35/- Standard: Stick Mic. 2gns. P. & P. 3/6. Asstd. Condensers: 10/- for 50. P. & P. 7/6. Asstd. Resistors: 10/- for 50. P. & P. 4/6. Asstd. Controls: 10/- for 25. P. & P. 7/6. Transistors: Mullard matched output kit 9/OC81D—2OC81's. P. & P. FREE.

Ferrite Rods 3/6: 6" x 3/8" complete with LW/MW Coils. P. & P. FREE.

TRANSISTOR CASES 19/6. Cloth covered, many colours. Size 9½"x6½"x3½" P. & P. 4/6. Similar cases in plastic 7/6.

TRANSISTOR RECORD PLAYER CABINETS 19/6. Dim. 11" x 14½" x 5½" P. & P. 7/6.

SINGLE PLAYER CABINETS 19/6. P. & P. 7/6.

STRIP LIGHT TUBES 3/9 each. 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1. P. & P. free.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

HOME RADIO (Mitcam) LTD., Dept. PW, 187 London Road, Mitcham, Surrey, CR4 2YQ Phone : 01-648 3282

THE ELECTRONIC COMPONENTS CATALOGUE THAT SETS THE STANDARD



Used and
acclaimed by:—

**SCIENTISTS
ENGINEERS
TECHNICIANS
TEACHERS &
STUDENTS**

This edition of the Home Radio Catalogue is the result of eleven years of careful selecting, compiling and indexing. It is the most comprehensive we have ever produced—it has 300 pages, over 8,000 items and over 1,500 illustrations. With each catalogue we supply a Book Mark giving Electronic Abbreviations, an Order Form, an addressed envelope, and 6 Vouchers each worth 1/- when used as directed. All this for only 8/6 plus 3/6 post, packing and insurance. Send the coupon today, with your cheque or P.O. for 12/-.

Of course no catalogue is ever really finalised. As soon as we have one edition off the press, our researchers get busy finding out what is the latest in the world of Radio and Electronics—ready for the next printing.

Please write Name & Address in block capitals

NAME

ADDRESS

Home Radio (Mitcam) Ltd., Dept PW, 187 London Road,
Mitcham, CR4 2YQ

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or
REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS
YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications—Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng.
— Refrigeration — Elem.
Electrical Science — Electrical
Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng.
— Hydraulics — Mining —
Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng. —
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work—Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance —
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT.
OF EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT
CAREER - GUIDANCE

PRACTICAL
EQUIPMENT

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc
A.M.I.E.R.E. City & Guilds
Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING
TOOLS

The specialist Elec-
tronics Division of
B.I.E.T.
NOW offers you a
real laboratory train-
ing at home with
practical equipment.
Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and if you are earning less than £30 a week you should send for your copy now—FREE and without obligation.



POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME


ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Here's a Selection of Models from the FREE HEATHKIT CATALOGUE

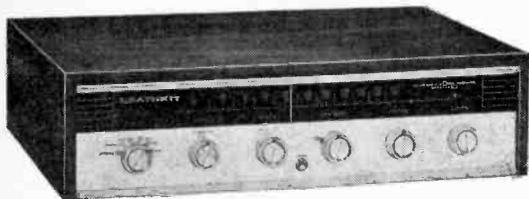
AVAILABLE AS EASY TO BUILD KITS OR READY-TO-USE MODELS




Kit K/AR-14 P.P. 13/6 **£54.0.0**
 Ready to use A/AR-14 P.P. 13/6 **£76.11.7**
 Cabinet £4.10.0. extra



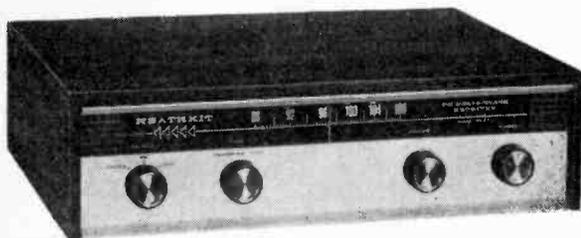Kit K/AR-17 P.P. 10/6 **£39.0.0**
 Ready to use A/AR-17 P.P. 10/6 **£60.4.10**
 Cabinet £3.10.0. extra



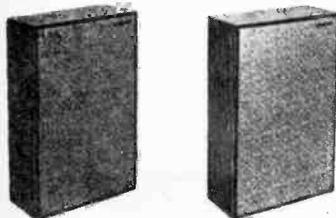Kit K/AR-27 P.P. 10/6 **£22.10.0**
 Ready to use A/AR-27 P.P. 10/6 **£32.13.6**
 Cabinet £3.10.0 extra



BERKELEY LOUDSPEAKER SYSTEM

Use two for stereo. Best performance from a slim-line cabinet. Uses less than 1 sq. ft. of floor space. Available in Teak or Walnut finish.

Kit P.P. 13/6 **£21.4.0**
 Ready to use P.P. 13/6 **£24.0.0**

CHOOSE A QUALITY
HEATHKIT LOUD-
SPEAKER SYSTEM
TO GET THE BEST
FROM YOUR AUDIO
SET-UP.

Top Value in a 30 Watt FM Stereo Receiver, AR-14

- 31 transistor, 10 diode circuit for cool, instant operation with the transparent, natural sound only transistors can deliver ● ± 1 dB, 15 to 50,000 Hz at 10 watts per channel continuous (20 watts total). 15 watts per channel IHF music power (30 watts total) ● Wide-band AM/FM stereo tuner plus two preamplifiers and two power amplifiers. ● Front panel stereo headphone jack. ● Compact—just 3 $\frac{3}{8}$ " H x 15 $\frac{1}{2}$ " W x 12" D. ● Custom install it in wall, your own cabinet, or use as a free standing unit. ● Build it in 20 hours.

Kit K/AR-14 (less cab.) . . . kit **£54.0.0** P.P. 13/6
 A/AR-14 (less cab.) . . . **£76.11.7** P.P. 13/6
 Cabinet extra: Teak or Walnut finish **£4.10.0**

Unbeatable Value in a 14 Watt FM Stereo Receiver, AR-17

- 28 transistor, 7 diode circuit for natural transparent sound, instant operation, long trouble-free life. ● 14 watts music power, 10 watts RMS from 25-35,000 Hz at ± 1 dB. ● Automatic stereo indicator light. ● Adjustable phase control for maximum separation. ● Complete front panel controls. ● Flywheel tuning. ● All critical circuits including FM "front-end" factory assembled and aligned. ● Circuit board assembly. ● Compact 10 $\frac{3}{8}$ " D x 3" H x 12" W. ● Front panel stereo headphone jack.

Kit K/AR-17 (less cab.) . . . kit **£39.0.0** P.P. 10/6
 A/AR-17 (less cab.) . . . **£60.4.10** P.P. 10/6
 Cabinet extra: Teak or Walnut finish **£3.10.0**

A Quality Table Radio FM Mono Receiver, AR-27

- 13 transistor, 6 diode circuit for high-fidelity sound reproduction, long life, low heat, freedom from hum, and service-free operation. ● 7 watts music power. ● ± 1 dB, 25 to 60,000 Hz at 5 watts. ● Input connectors for phonograph and auxiliary signals. ● Complete front panel controls. ● Flywheel tuning. ● Preassembled and prealigned FM tuner, all other critical parts factory aligned. ● Easy, circuit board assembly. ● Compact bookshelf size. ● 3-way installation . . . wall, free standing or in a suitable cabinet. ● 117 v. A.C. or 210/240 v. A.C., 50 Hz operation.

Kit K/AR-27 (less cab.) . . . kit **£22.10.0** P.P. 10/6
 A/AR-27 (less cab.) . . . **£32.13.6** P.P. 10/6
 Cabinet extra: Teak or Walnut finish **£3.10.0**



Showrooms: LONDON, Tottenham Ct. Rd. BIRMINGHAM, St. Martins Hse. GLOUCESTER, Bristol Rd.

There's Something for Everyone in the HEATHKIT Electronic Range . . .



STEREO TAPE RECORDER, STR-1

A complete stereo system including speakers in one compact Transportable. Versatile recording facilities. Powerful output, 4 watts rms per channel.
Kit K/STR-1 £58.0.0 P.P. 10/6




STEREO AMPLIFIER, TSA-12

Fully transistorised. Fantastic performance at lowest cost. Many exceptional features.
Kit K/TSA-12 £32.16.0 P.P. 10/6
Cabinet £3.16.0 extra



PORTABLE VOM, IM-17

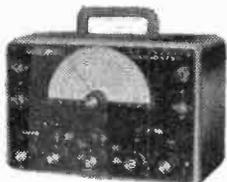The latest solid-state circuit, plus rugged polypropylene case. For homeowners, hobbyists, service.
Kit K/IM-17 £13.12.0 P.P. 6/-



RF SIGNAL GENERATOR, RF-1U

100kHz to 200MHz in six bands. The specification is outstanding for price. A dependable service instrument.
Kit K/RF-1U £13.18.0 P.P. 6/-




VALVE VOLTMETER, V-7A

Popular size, 7 AC, DC, ohms range. Popular price.
Kit K/V-7A
£14.16.0 P.P. 4/6




HIGH PERFORMANCE CAR RADIO CR-1

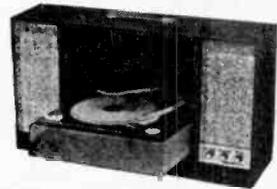Latest transistor circuit gives powerful output, 4 watts. For 12v pos or 12v neg earth systems.
Kit K/CR-1 (incl. speaker)
£14.12.0 P.P. 4/6



STEREO RECORD PLAYER, SRP-1

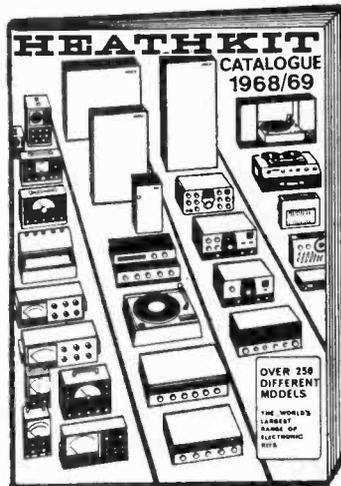A complete stereo system including speakers in one compact portable. Plays mono or stereo records. Cool, crisp, bold sound.
Kit K/SRP-1 £28.6.0 P.P. 10/6



Send for the
FREE
Catalogue
and see for
yourself,
Today!



4 BAND RECEIVER, GR-64

Offers you the exciting world of shortwave at low-cost. Modern styling.
Kit K/GR-64 £22.8.0 P.P. 9/-



UXR-1



UXR-2

TRANSISTOR PORTABLES

UXR-1. The popular choice. Many de-luxe features.

Kit K/UXR-1 leather £13.8.0 P.P. 4/6

Kit K/UXR-1 colour case £12.8.0 P.P. 4/6

UXR-2. For clean, bold sound. Rugged leather case in black or brown.

Kit K/UXR-2 £15.10.0 P.P. 6/-



To
DAYSTROM LTD., Dept. PW-3, GLOUCESTER, GL2-6EE.

Please send me FREE CATALOGUE tick

NAME

ADDRESS

Prices and specifications subject to change without notice

BOOKS BY G. A. BRIGGS

A QUARTER OF A MILLION COPIES SOLD SINCE 1948

AERIAL HANDBOOK (second edition)

176 pages, 144 illustrations.
Price (semi-stiff cover) 15/- (16/6 post free).
Cloth bound 22/6 (24/- post free).



CABINET HANDBOOK

112 pages, 90 illustrations.
Price 7/6 (8/6 post free). Semi-stiff cover.



AUDIO BIOGRAPHIES

344 pages, 64 contributions from pioneers and leaders in Audio. Cloth bound.
Price 25/- (27/- post free).



MUSICAL INSTRUMENTS AND AUDIO

240 pages, 212 illustrations. Cloth bound.
Price 32/6 (34/6 post free).



LOUDSPEAKERS

Fifth edition—336 pages, 230 illustrations.
Cloth bound.
Price 25/- (27/- post free).



A to Z in AUDIO

224 pages, 160 illustrations. Cloth bound.
Price 15/6 (17/- post free).



MORE ABOUT LOUDSPEAKERS

136 pages, 112 illustrations.
Price 8/6 (9/6 post free). Semi-stiff cover.



PIANOS, PIANISTS AND SONICS

190 pages, 102 illustrations. Cloth bound.
Price 18/6 (20/- post free).



AUDIO AND ACOUSTICS

168 pages, 140 illustrations.
Price 12/6 (13/6 post free). Semi-stiff cover.



ABOUT YOUR HEARING

132 pages, 112 illustrations.
Price (semi-stiff cover) 15/6 (16/6 post free).
Cloth bound 22/6 (24/- post free).



LETTERS FROM U.S.A.

May, 1968

Dear Sir:

Would you please forward me a list of your books and leaflets presently available. I have had several of your books but friends have failed to return them over the years. I think your books are the finest works on high fidelity available and I would like to add them to my library again.

Thank you very much, VERNON T. RANDLE, Dallas, Texas.

Extract of letter from Mr. Wendell C. Ward of Texas, U.S.A. September 1968.

I have recently read through Mr. Briggs's book "A to Z in Audio" and found it most interesting. It's refreshing to find a man who can write about what could be a dry subject with enthusiasm and humor."

● PLEASE SEND BOOK ORDERS
DIRECT TO OUR ILKLEY BRANCH—
BWS 13 WELLS ROAD, ILKLEY, YORKS.

Leaflets giving a general outline of the above books are also available post free from the above address.

Sold by Radio Dealers and Book Shops. Published by
RANK WHARFEDALE LTD., IDLE, BRADFORD, YORKS.
Telephone: Bradford 612552

BI-PRE-PAK LTD

222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0702) 46844

SPECIAL OFFER

Stock Clearance of Manufacturers
Rejects. Limited Number

UHF/VHF Tuner Units. Consisting of:
2 AF186 Transistors, Tuning Condensers, Coils and Comps etc.:

Price 5/- each

Post and Packing U.K. 2/6.

Transistors	Price
AC107	3/-
AC126	2/4
AC127	2/4
AF117	3/6
AC176	4/-
AD149	10/-
BC107-8-9	4/6
OC271	10/-
BSY96A	3/-
OC22	6/-
OC23	6/-
OC25	7/6
OC26	5/-
OC28	10/-
OC35	5/-
OC36	7/6
OC41	2/6
OC42	3/-
OC44	1/11
OC45	1/9
OC71	2/6
OC72	2/6
OC73	3/6
OC81	2/6
OC81D	2/6
OC83	2/6
OC139	4/-
OC140	3/6
OC200	5/-
OC201	8/-
2N1302 or 3	4/-
2N1304 or 5	5/-
2N1306 or 7	6/-
2N1308 or 9	8/-

BRAND NEW PRE-PAKS

No.	Description	Price
B1	50 Unmarked Trans. Untested	10/-
B2	4 Solar Cells Inc. Book of Instructions	10/-
B6	17 Red Spot AF Transistors	10/-
B6A	17 White Spot EF Transistors	10/-
B9	1 ORP12 Light Sensitive Cell	9/-
B53	25 Silicon Transistors 400 M/c	10/-
B54	40 Silicon Transistors NPN To5	10/-
B56	40 Silicon Transistors NPN To18	10/-
B56	40 Silicon Transistors NPN/PNP unmarked	10/-
B61	25 BSY26/7 Transistors new, untested	10/-
B62	25 BSY96a Transistors new, untested	10/-
B64	25 BFY50/1/2 Transistors new, untested	10/-
B68	25 BC107/8/9 Transistors new, untested	10/-
B56	150 Germ. Min. Diodes, untested	10/-
C2	1 Unijunction Transistor 2N2160	15/-
A3	25 Mixed Marked and Tested Transistors	20/-
A21	5 Power Transistors, one AD149, one OC26 and three more	20/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

Send for our FREE lists and catalogue of all our products. Check your own equivalent with our free substitution chart.

Matched Set, NPN/PNP AD181-AD182
Comp. pair Pak **10/- PR.**
Complementary Set, NPN/PNP Germ. trans., Pak F.3 **2/6 PR.**

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/-
CASH WITH ORDER PLEASE, add 1/- post and packing.
OVERSEAS ADD EXTRA FOR AIRMAIL

ENGINEERS TEST EQUIPMENT AND ACCESSORIES

MULTIMETERS

Complete range of high precision instruments.

TRANSISTOR CHECKERS

For use with PNP, NPN Transistors IF and RF Resistors, Diodes, Rectifiers.

RESISTOR SUBSTITUTION BOX

CAPACITANCE SUBSTITUTION BOX

ADJUSTABLE AC DC CONVERTER

TEST LEAD KITS, etc.

We also stock large range of Microphones, Audio Units, Recording Tapes, Intercoms, Telephone Amplifiers, Car Radios, TV Spares etc.

Send S.A.E. for illustrated brochures and price list.

D. WEBB


WHOLESALE

61-63 Clifton Street, Hull, E. Yorkshire

Telephone 36016

THE CLASSIC

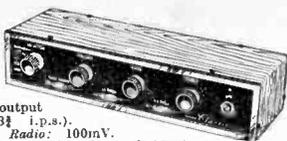Controls: Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.



Specification: Sensitivities for 10 watt output at 1KHz. Tape head: 3mV (at 3½ i.p.s.). Mag. P.U.: 2mV. Ger. P.U.: 80mV. Radio: 100mV. Aux.: 100mV. Tape/Rec. output: 100mV. Equalisation for each input is correct to within ± 2dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ± 13dB at 60 Hz. Treble ± 14dB at 15KHz. Total distortion: (for 10 watt output) < 1.5%. Signal noise: < -60dB. A.C. mains 200-250v. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case. Price 8 gns. + 7/6 p. & p.

THE DORSET (600mW output)



7-transistor fully tunable M.W.-L.W. superhet portable —with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

MAINS POWER PACK KIT: 9/6 extra.

PRICE £5.5.0 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.

THE ELEGANT SEVEN MK. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.

Circuit 2/6 FREE WITH PARTS.



X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: RMS Power Output (into 8 ohms speaker): 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0-33 microamp). Total Distortion at 1KHz. at 5 watts 0-35%, at rated output 1-5%. Frequency Response: Minus 3dB points 20Hz and 40KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24V d.c. at 800mA (6-24V may be used).

Control assembly: including resistors and capacitors.

1. Volume: PRICE 5/-.

2. Treble: PRICE 5/-.


3. Comprehensive bass and treble: PRICE 10/-.

The above 3 items can be purchased for use with the X101.

Power Supplies for the X101:

P101 M (for mono) 35/- plus 4/6 p. & p.

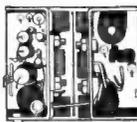P101 R (for stereo) 42/8 plus 4/6 p. & p.



Price 49/6 plus 2/6 p. & p.



THE RELIANT 10W SOLID-STATE HIGH QUALITY AMPLIFIER

SPECIFICATIONS

Output—10 watts

Inputs—1. xtal mic 10mV

Output Impedance—3 to 4 ohms

2. gram/radio 250mV

3. Comprehensive bass and treble: PRICE 10/-.

Frequency Response—with tone controls central) Minus 3dB points are 20Hz and 40KHz.

Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220-250V. A.C. Size of chassis—10" x 3½" x 2".

A.C. Mains 200-250V. For use with Stel. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control for gram. and mike. Built and tested. X" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P. PRICE £5.5.0 plus 5/- P. & P.

Price 13½ Gns. Postage & Packing 7/6 extra.

THE VISCOUNT

Integrated High Fidelity Transistor Stereo Amplifier

SPECIFICATIONS: Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monoral). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U., Tuner. Tape and Tape Rec. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency response: 40Hz-20KHz+2dB. Tone controls: (Baxandall type), separate bass and treble controls. Treble 13dB lift and out at 15KHz. Bass 15dB lift and 25dB cut at 60Hz. Volume controls: Separate for each channel. A.C. Mains input: 200-240v. 50-60Hz. Size 12½ x 6 x 2½in. in teak-finished case. Built and tested.

Price 13½ Gns. Postage & Packing 7/6 extra.

Goods not despatched outside U.K. Terms C.W.O. All enquiries Stamped Addressed Envelope

RADIO & TV COMPONENTS (Acton) LTD
21c High Street, Acton, London, W.3.

All orders by post to our Acton address
323 Edgware Road, London, W.2.

Personal callers only at our Edgware address



POCKET MULTI-METER

Size 3¼ x 2½ x 1¼in. Meter size 2½ x 1¼in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test leads, battery and full instructions, 42/8. P. & P. 3/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

CYLDON U.H.F. TUNER

Complete with PC88 and PC86 Valves. Full variable tuning. New and unused. Size 4¼ x 5¼ x 1¼in. Complete with circuits diagram. 35/- p. & p. 3/6



THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross over network. Peak handling power 10 watts. Impedance 15 ohms. Flux (density) 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20kc/s. Size 13½ x 8½ x 4½ inches. By famous manufacturer. List Price £7. Our price 89/8 plus 5/- P. & P. Similar speaker to the above without tweeters in 3 and 15 ohm 89/8 plus 5/- P. & P.

600 mW FOUR TRANSISTOR AMPLIFIER

Features N.P.N. and P.N.P. complementary symmetrical output stage, 2¼" x ¾" x ¾" Speaker. Output impedance 12 ohms frequency response 3dB points 90 c/s and 12 Kc/s. Price 19/6 plus 1/- P. & P. 7" x 4" Speaker to suit, 13/6 plus 2/- P. & P.

2½ watt ALL TRANSISTOR AMPLIFIER

AC mains 240V. Size 7" x 4½" x 1½". Frequency response 100 c/s—10 Kc/s Semi conductors, two OC 75's two AC 128's and two stabilizers AA129. Tone and volume controls on flying leads. £2.10.0 plus P. & P. 3/6. Suitable 8" x 5" 10,000 line high flux speaker, 18/6 plus 2/- P. & P.




FIRST QUALITY P.V.C. TAPE

5½"	Std.	850ft.	9/-	5"	L.P.	850ft.	10/6
7"	Std.	1200ft.	11/6	3"	T.P.	600ft.	10/6
3"	L.P.	240ft.	4/-	5"	T.P.	1800ft.	25/6
5½"	L.P.	1200ft.	11/6	5½"	T.P.	2400ft.	32/6
7"	L.P.	1800ft.	18/6	7"	T.P.	3600ft.	42/6
5½"	D.P.	1800ft.	18/6	4"	T.P.	900ft.	15/-

P. & P. on each 1/6, 4 or more post free.

50 WATT AMPLIFIER A.C. MAINS 200-250V

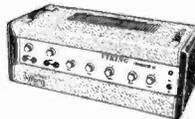


An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls.

Price 27 gns. Plus 20/- p. & p.

RECORD PLAYER SNIP A.C. MAINS 240V

The "Princess" 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent styli brush clean styli after each playing and at shut off. The pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.18.6 complete with cartridge and ready to play. Post and insurance 7/6 extra.

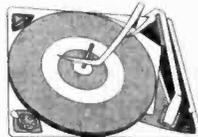


CAR TRANSISTOR IGNITION SYSTEM

(by famous manufacturer)

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers etc.).

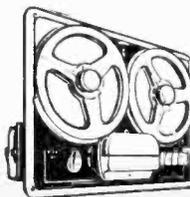PRICE £4.19.6. (post and packing 5/- extra).



MOTEK

3 Speed 2 track Tape Deck complete with heads, takes 7in. spool.

Incorporating 3 motors.

A.C. mains, 240 volts, listed at £21.0.0.

Our Price £9.19.6, plus 10/- P. & P.

AERIAL WIRE: Coils of 25 yds. solid core 2/8, 1/- P. & P.

BATTERY ELIMINATORS for Transistor Supplies. 9v., 7½v., 6v. 29/8, plus 2/6 P. & P.

CONDENSERS. Large range available from 6d. each.

COAX SOCKETS. Flush 6d. plus 6d. P. & P.

CARTRIDGES. Acos, BSR, Sonatone.

EAR PIECES. 2-5µ/m or 3-5µ/m Mag. 2/8 plus 1/- P. & P. 2-5µ/m or 3-5µ/m Crystal. 5/8 plus 1/- P. & P.

HIGH IMPEDANCE HORNS. 1½ to 4½ volt, ideal for alarms. 3/6 plus 1/- P. & P.

LOUDSPEAKERS. Large range from 2in. 8 ohm 7/6 plus 1/- P. & P.

TRANSISTORS. Full range, i.e. OC44, OC45, OC71, OC82, 2/6; OC35 9/-; Fet. MPF103, 9/6.

TRANSFORMERS. 12-volt battery charger £1.2.6. 250-0-250 volt 60mA. 18/8; 0-250 with 6-3 volt, 18/6, plus 3/8 P. & P.

RELAYS. 12 volt, suitable for car alarm, 21/-, plus 1/6 P. & P.

Send S.A.E. for Free Price List.

Many other items, please send stamp for free price list.



BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.
54 EGLINTON STREET,
GLASGOW, C.S. Tel. 041 80Uth 2904

Member of the Lander Group



**IT'S A MUST
OUR
CATALOGUE
JOIN THE
THOUSANDS
OF SATISFIED CUSTOMERS
SEND NOW FOR**

**OUR NEW 1968/69
illustrated catalogue
NOW AVAILABLE**

(send 2/- in stamps for your copy)

Catalogue contains prices and details of Amplifiers — Hi-Fi Tuners — Loudspeakers — Pick-ups — Playing Decks — Microphones — Test Meters — Hand Tools — Valves — Soldering Irons — Tape Recording Accessories, etc.

ALPHA RADIOSUPPLY CO

103 Leeds Terrace, Leeds 7. Tel: 25187

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

The ideal, economical and safe way of running Transistor Radios, Record Players, Tape Recorders, Amplifiers etc. from A.C. Mains. All units are completely isolated from mains by double wound transformer ensuring 100% safety.

PLUS-3

MAINS UNIT

Provides three separate switched output voltages 6v., 7½v. and 9v. DC. Attractive case with indicator light, mains lead output socket, plug and lead. Size 4½ x 3½ x 2½ in.



57/6 P. & P. 2/6
(Extra lead with DIN plug for Cassette Recorders 7/6)



45/- P. & P. 2/6

POWER PLUS MAINS UNIT

for Cassette Tape Recorders using 7½v. Complete with DIN plug for recorder power socket. Can also be supplied for a 6-volt output complete with suitable plug. (Please state make, model and voltage required.)

**MAINS UNIT for FI-CORD 202A
TAPE RECORDER P. & P. 5/-**

£4.15.0

MAJOR POWER PLUS MAINS UNITS

For single outputs, 9v, 6v, 39/6. P. & P. 2/6.
For two separate outputs, 9v + 9v,
6v + 6v, 42/6. P. & P. 2/6.
(Please state outputs required.)



R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.), 31 Oliver Road, London, E.17

EVER TRIED TV

CONSTRUCTION?

After working on radio it's the next logical step. You'll find all you want to know to get cracking in our companion magazine, PRACTICAL TELEVISION. It's packed with know-how on this fascinating subject... expert guidance on set and equipment construction, repair, maintenance, detailed analyses of latest TV developments... the lot. Why not follow through now? Ask your newsagent for a copy today.

MONTHLY 2/6

Practical TELEVISION

Practical TELEVISION

FEBRUARY 1969

2/6

EXPERIMENTS IN COLOUR TV



ALSO INSIDE: POWER SUPPLY
TESTING

EXCLUSIVE PURCHASE!

PORTABLE AMPLIFIER UNIT

BY WELL-KNOWN BRITISH MAKER



A luxury unit at a bargain price. Only 35/- P. & P. 4/6
Designed as a Telephone Amplifier but can be used in many different ways—a booster amplifier for transistor radios, a baby alarm, intercom, paging system, etc., etc. High gain four transistor amplifier unit housed in attractive leathercloth covered wooden cabinet with upward facing 3in. high flux P.M. speaker covered by neat plastic grille. Fitted 3.5mm jack socket and volume/on/off control. Size 7 x 4 1/2 x 3 1/2in. high. Operates on standard PP6 or VT6 battery. Supplied complete with telephone pick-up induction coil fitted suction pad, lead and 3.5mm jack plug.

OUR SPECIAL PRICE ... 35/- P. & P. 4/6.

Or as above with 3.5mm plug and DLR5 unit for use as sensitive microphone for baby alarms, communication systems etc. Will operate over distances of up to 200ft. or more when connected with twin flex or bell wire.

PRICE 40/- P. & P. 4/6
(Batteries and flex not included.)

BRAND NEW 3 OHM LOUDSPEAKERS

5in. 14/-; 6in. 18/6; 8in. 27/-; 7 x 4in. 18/6; 10 x 6in. 27/6. E.M.I. 8 x 5in. with high flux magnet 21/-; E.M.I. 13 1/2 x 8in. with high flux ceramic magnet 42/- (15 ohm 45/-). E.M.I. 13 x 8in. with two built-in tweeters and crossover network. 3 or 15 ohms 4 gns. P. & P. 5in. 2/-; 6 1/2 x 8in. 2/6; 10 x 12in. 3/6 per speaker.

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hi-Fi ceramic ferrobar magnet assembly 25.10.0. P. & P. 5/-; Guitars models: 25w. 25.0.0 35w. 28.0.0. E.M.I. 8in. **HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.

12in. **"RA" TWIN CONE LOUDSPEAKER.** 10 watts peak handling. 3 or 15 ohms. 35/- P. & P. 3/6.

35 OHM SPEAKERS

3 1/2in. 12/6; 7 x 4in. 21/- P. & P. 2/- per speaker.

VYNAIR AND REXINE SPEAKERS AND CABINET FABRICS app. 5 1/2in. wide. Usually 35/- yd., our price 13/6 yd. length. P. & P. 2/6 (min. 1 yd.). S.A.E. for samples.

LATEST COLLARO MAGNAVOX 363 STEREO TAPE DECK. Three speeds 4 track, takes up to 7in. spools. 116.10.0. Carr. 10/-.

QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6. Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser 35/- P. & P. 3/-.

ACOS CRYSTAL MIKES. High Imp. for desk or hand use. High sensitivity. 18/6. P. & P. 1/6.

ACOS HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/- P. & P. 1/6.

NEW S.T.C. TYPE 25 MINIATURE RELAYS— 12 volt. 4 s/p, c/o contacts. 1 amp rating. Coil resistance 185 ohms. Size approx. 1 1/4 x 1 1/4 in. high. 10/- each. P. & P. 1/6.

Also some similar to above but coil resistance 3,500 ohms 48 volt operation. 8/- each. P. & P. 1/6.

SPECIAL OFFER! PLESNEY TYPE 29 TWIN TUNING GANG 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Size approx. 2 x 1 1/4 in. Only 8/6. P. & P. 2/6.

TRANSFORMER BARGAINS

MAINS TRANSFORMER. Primary 200-240V two separate 1/2 wave secondaries giving approx. 18V at 1 amp and 20V at 1.2 amp; secs. can be connected in series for 36V at 1.5 amp. Ideal for transistor power supplies. Drop through mounting. Stack size 2 1/4 x 3 1/4 in. 15/- P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. 11/- P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6.

MATCHED PAIR OF 2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/4 x 1 1/4 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

7-10 watt output TRANSFORMERS to match pair of ECL86's in push-pull to 3 ohm output. ONLY 11/- P. & P. 2/6.

BRAND NEW MAINS TRANSFORMERS for Bridge Rectifier. Pri. 240v. AC. Sec. 240v. at 50mA and 6.3v. at 1.5 amp. Stack size 2 1/4 x 3 1/4 in. 10/6. P. & P. 3/6. (Special quotations for quantities).

HIGH GRADE COPPER LAMINATE BOARDS 8 x 6 x 1/16in. FIVE for 10/- P. & P. 2/-.

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design. All parts supplied including drilled metal work. Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3dB. 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 6 amp.

PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0. All Post Free.

Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).



SPECIAL PURCHASE!

E.M.I. 4-SPEED PLAYER
Heavy 8 1/2in. metal turntable. Low flutter performance 200/250 v. shaded motor (90 v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. LIMITED NUMBER ONLY 63/- P. & P. 6/6.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. E.M.I. MODEL 999 Single Player with unit mounted pick-up arm and mono cartridge ... 25.5.0 B.S.R. UA25 with latest mono compatible cart. ... 26.19.6

All plus Carriage and Packing 5/6.
LATEST GARRARD MODELS. All types available 1000 SP25, 3000, AT60 etc. Send S.A.E. for latest Bargain Prices!
PLINTH UNITS cut out for Garrard Models 1000, 1026, 2000, 3000, AT60, SP25. With rigid perspex cover. OUR PRICE 5 gns. complete. P. & P. 5/6.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. Only 32/6. P. & P. 2/-.
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on SOMONE STAEIC compatible Stereo Cartridge with diamond stylus 50/- P. & P. 2/-.
FEW ONLY! ACOS GP69/1. For EP and LP 10/- P. & P. 2/-.


QUALITY RECORD PLAYER AMPLIFIER MKII
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7" w. x 3" d. x 6" h. Ready built and tested. PRICE 75/- P. & P. 8/6.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MKII
Unit motor board size 1 1/4 x 1 1/2in. clearance 2in. below 8 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD autochanger or Single Player Unit (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6 P. & P. 9/6.

FM/AM TUNER HEAD

Beautifully designed and precision engineered by Dormer & Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. Prealigned FM section covers 86-102 Mc/s. I.F. output 10-7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-.
GORLER F.M. TUNER HEAD. 98-100 Mc/s. P. & P. 2/6 I.F. 15/- plus 2/6 P. & P. (ECC85 valves. 8/6 extra)

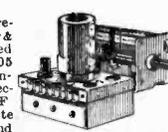

3-VALVE AUDIO AMPLIFIER MODEL H84 B

D signed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.5.0. P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to H434 above but employs entirely different and advanced circuitry. Complete with matched pair. PRICE 79/6. P. & P. 6/-.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V18/10p, 10/-; OC71 5/-; AF117 7/6.

Set of Mullard 6 transistors OC44, 2—OC45, AC128D, matched pair AC128 25/-; Mullard LPH3 Audio Transistor Pack AC128D also matched pair AC128 12/6; OR P12 Cadmium Sulphide Cells 10/6. All post free.

SPECIAL OFFER!


A great opportunity to purchase a first class GENERAL PURPOSE HIGH GAIN HIGH SENSITIVITY PORTABLE AMPLIFIER. Completely self contained and can be used for a variety of purposes, i.e. Intercom, Baby Alarm, Booster unit for transistor radios etc., also ideal for classroom unit etc. Works perfectly with our special offer ACOS stick Microphone (21/-). Output 1000mW. Uses standard 9 volt battery. Smart tone carrying case size 12 x 4 x 3in. fitted standard input jack socket, volume controls, 7 4in. speaker. Completely built and tested, brand new with full maker's guarantee.



Only 79/6 P. & P. 5/8

STEREO AMPLIFIER

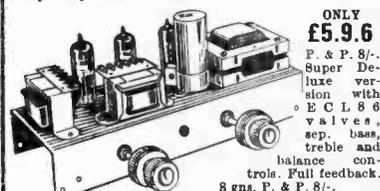Incorporating 2 ECL86s and 1 EZ80, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete. Output impedance 3 ohms.



HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI

● Peak output in excess of 14 watts.
● All standard British components.
● Built on printed circuit panel size 6 x 3in.
● Generous size Driver and Output Transformers.
● Output transformer tapped for 3 ohm and 15 ohm speakers.
● Transistors (GET114 or 81 Mullard AC128D and matched pair of AC128 o/p). ● 9 volt operation.
● Everything supplied, wire, battery clips, solder, etc.
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/- P. & P. 3/- Also ready built and tested, 52/6. P. & P. 3/-.


HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7" wide x 3" deep x 6" high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. LIMITED NUMBER ONLY.

OUR ROCK BOTTOM BARGAIN PRICE 49/6 P. & P. 6/-

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished extra amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Well shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with etc. input sockets. 28.5.0. P. & P. 8/6.

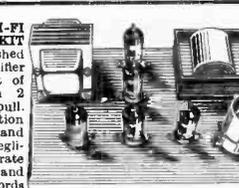

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Please write clearly
PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY.
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit
★ Response 30-20,000 c.p.s. Impedance 15 ohms. **18 Gns.**
★ Performance comparable with units costing Carr. 12/6 considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3 way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Measured weight of woolen acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions.

DEMONSTRATIONS AT ALL BRANCHES.

R.S.C. STEREO/20 HI-FI AMPLIFIER

10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE. (7) valves ECC83, (2) ECL86, (4) EZ81. Frequency Response: ±2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 30 millivolts max. Harmonic Distortion: 0.2%. ★ Four-position tone compensation and Input Selector Switch. ★ Front/Mono switch. ★ Neon panel indicator. ★ Handsome Perspex Frontplate. ★ Separate Bass and Treble controls. Output transformers are high quality sectionally wound. Outputs for 3 and 15 ohms speakers. Complete set of parts, point-to-point wiring diagrams and instructions. Or factory assembled with our usual 12 mths' guarantee 19 Gns. Or Dep. £4.10 and Carr. 12/6 9 monthly payments £2 (Total £22.10.0). Send S.A.E. for leaflet.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Performance figures. Hum level -70dB. Frequency response ±3dB 30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **14 Gns.**

Twin-handled perforated cover 27/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 17 Gns. TERMS: Deposit £5.14.0 and 9 monthly payments of 31/3 (Total £19.5.3). Send S.A.E. for leaflet.

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of "mike" and gram, etc. etc. High sensitivity. 5 valves—ECC83 (2), EL84 (2), EZ81. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response ±3dB 30-20,000 c/s. Hum level -60dB. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic PUs, all types

"mikes". For Musical Instruments such as String Bass, Electronic Guitars etc. Size approx. 12 x 9 x 7in. For A.C. mains 250-250v. 50c/s Output for 3 and 15 ohm spkrs. SAE for leaflet. Complete kit. **9 Gns.** Full instructions and point-to-point wiring diagrams. Carr 11/6 (Or factory built 12 Gns.) Twin handled metal cover 27/6. TERMS ON ASSEMBLED UNITS. Deposit 87/6 and 9 monthly payments of 22/- (Total £14.5.6).

R.S.C. A11 TRANSISTORISED VERSION OF ABOVE COMPLETE KIT 9 Gns (Assembled 13 Gns)

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

An exceptionally powerful hi-fi quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, etc. Peak O/P rating.

★ Two extra heavy duty 12in. Loudspeakers.

★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

52 Gns. Carr. 30/- or dep. £10.1.0 and 9 monthly payments of 25.11.0 (Total 57 Gns.). Send S.A.E. for leaflet.

Also B20 Bass Inc. 15in. 25w Spkr. 29 Gns. G15 Inc. 12in. 20w Spkr. 19 Gns.

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BMI An all-dry battery eliminator. Size 5 1/4 x 4 1/2 in. approx.

Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 49/11 or assembled 59/11.

SELENIUM F.W. RECTIFIERS (Bridged)

A116/12v. D.C. output. Max. A.C. input 18v. 1a. 3/11. 2a. 6/11. 3a. 9/9. 4a. 12/8. 6a. 15/8.

SMOOTHING CHOSES 150mA, 7-10H, 250 0 12/9; 100mA, 10H, 200 0 10/9; 80mA, 10H, 350 0 8/9; 60mA, 10H, 400 0 4/11.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.

250v., 60mA, 6-3v. 2a. 15/11
250-0-250v. 60mA, 6-3v. 2a. 16/11

FULLY SHEROUD UPRIGHT MOUNTING 250-0-250v. 80mA, 6-3v. 2a. 0-5-6-3v. 2a. 21/9
250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
300-0-300v. 130mA, 6-3v. 4a., c.t., 6-3v. 1a.

For Mullard 510 Amplifier 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
425-0-425v. 200mA, 6-3v. 4a., c.t., 5v. 3a. 69/9
425-0-425v. 200mA, 6-3v. 4a., 6-3v. 4a., 5v. 3a. 75/9
450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 3a. 85/9

TOP SHEROUD DROP-THROUGH TYPE 250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a. 21/9
250-0-250v. 100mA, 6-3v. 3-5a. 25/9
250-0-250v. 100mA, 6-3v. 2a., 6-3v. 1a. 24/9
350-0-350v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a. 25/9
250-0-250v. 100mA, 6-3v. 1a., 0-5-6-3v. 3a. 35/9
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
300-0-300v. 130mA, 6-3v. 4a., 0-5-6-3v. 1a. 35/9

Suitable for Mullard 510 Amplifier 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9
425-0-425v. 200mA, 6-3v. 4a., 0-5-6-3v. 3a. 35/9

FILAMENT or TRANSISTOR POWER PACK Types 6-3v. 1.5a. 7/9; 6-3v. 2a. 8/9; 6-3v. 3a. 10/9; 6-3v. 6a. 21/9; 12v. 1a. 8/9; 12v. 3a. or 24v. 1.5a. 21/9; 0-9-18v. 1a. 17/9; 0-12-25-42v. 2a. 29/9.

CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 14/11; 2 1/2a. 17/9; 3a. 19/11; 5a. 23/9; 6a. 27/9; 8a. 33/9.

AUTO (Step Up/step DOWN) TRANSFORMERS 0-110/120v. 200-230-250v. 50-80 watts 16/9
150 watts 29/11; 250 watts 49/9; 500 watts 99/9

OUTPUT TRANSFORMERS Standard Pentode 5,000 0 or 7,000 0 to 3 0. 8/9
Push-Pull 8 watts EL84 to 3 0 or 15 0 12/9
Push-Pull 10 watts 6V6 ECL86 to 3, 5, 8 or 15 0 22/9
Push-Pull EL84 to 3 or 15 0 10-12 watts 21/9
Push-Pull Ultra Linear for Mullard 510, etc. 35/9
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 0 33/9
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 0 59/9

SMOOTHING CHOSES 150mA, 7-10H, 250 0 12/9; 100mA, 10H, 200 0 10/9; 80mA, 10H, 350 0 8/9; 60mA, 10H, 400 0 4/11.

BLACKPOOL AGENT APPOINTED O. & C. ELECTRONICS 27 CHURCH ST.



R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address, 15 ohm matching. C57 15 watts inc. five 7 x 4in. speakers £7.19.11. Type C48S, 30 watts. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 65/- **16 Gns.** and 9 mthly pmts 34/9 (Total £18.17.9) Carr. 10/-
Type C412S, 50 watts. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/-
Or Deposit £4.13.6 and 9 monthly payments of 52/6 (Total £28.5.0).

30 WATT HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group A 2 or 4 Input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold perspex fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm **18 Gns.** Carr. 12/6
Deposit 3 Gns. and 9 mthly payments of 39/8 (Total £21).

12in. HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered covered Cabinets 15 Watt 11,000 lines £5.15.0 20 Watt 10,000 lines £8.19.9
3or15ohms.Carr7/6 3or15ohms.Carr9/9

LOUDSPEAKERS

Limited number of heavy duty units at well below list prices. Brand new, guaranteed. Terms available over £8. Carr. 10/- extra.
12in. 30 watt 6-8 ohms 15 ohm impedance 15in. 30 watt DUAL CONE Normally £6.19.9 Normally £6.19.9 Normally 9 Gns. approx £12 £10.0.0 over £14

FANE 'POP' 100 LOUDSPEAKER

18" 100 Watt Fantastic power handling. Guaranteed anteed 2 years. **19 Gns** POST FREE

R.S.C. GRAM AMPLIFIER KIT, 4 watts output. Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. **49/11** Circuit etc. supplied. ONLY

POWER PACK KIT Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250v. A.C. mains. Output 250v. 60mA 6-3v. 2a. Supplied with case **24/11** in lieu of chassis 28/11. Or assembled 39/11.

CLEARANCE LINES

HIGH QUALITY 8" x 3" LOUDSPEAKERS 10000 Gauss 3 ohm only **11/9**

14 WATT HI-FI AMPLIFIERS

High sensitivity. Two separate Jack inputs. Two vol. controls for mixing purposes. Separate Bass and Treble Controls. Valves ECC83, ECL86, ECL86, E280. Output for 15 ohm Loudspeaker. 200-250v 50 c.p.s. A.C. mains operation. Size approx. 8 x 8 x 6in. Factory built and fully guaranteed. Limited number to clear at **£6-19-11** 10/-

EXTENSION 'SPEAKERS 29/9 Cabinet size 12 x 8 x 5in. attractive grey lizard skin finish. Fitted high flux 6in. 5w. 3 ohm speaker. **59/9** Mono Stereo

EMI PLAYER TURNTABLES with P.U. 4 speed. Turnover cart-ridge. Limited number. **69/9**

PHONE AMPLIFIERS

Speak and listen with both hands free. Standard dry battery operated. Attractive black moulded case. **59/9**

1 WATT TRANSISTOR AMPLIFIERS

For 3-5 ohm loudspeakers. Miniature size. Brand new boxed. **37/9**

PRINTED CIRCUIT KITS

for making printed circuits. Complete with 72 square ins. laminated board and necessary fluids. **12/9**

J.B. VHF/FM DIAL & DRIVE ASSEMBLIES

Complete with escutcheon. Size 7" x 4 1/2". Escutcheon 7 1/2" x 2 1/2". **ONLY 9/9**

TAPE RECORD/PLAYBACK AMPLIFIERS

4 watts output. Magic Eye Recording level indicator. For 3 ohm L/S. All normal facilities. Less Facia plate. For 200/250 A.C. mains. Carr 8/6. **£7.19.11**

HEAVY DUTY 15in. 40 WATT LOUDSPEAKERS

in substantial Rexine/Vynair covered cabinet. Carr. 15/- **14 Gns.** ONLY

MINI-8 HI-FI LOUDSPEAKER UNITS

Teak veneered cabinet, size 9 1/2 x 6 1/2 x 7 1/2 in. Peak power handling 8 watts 3 ohms or 15 ohms. Clearance Price **59/11**

JASON VHF/FM TUNER DESIGNS

All parts FMT1 5 Gns. FMT2 £6.19.11. JTV2 9 1/2 Gns. Please state channel

STEREO/TEN HIGH QUALITY AMPLIFIER

5 watts high quality output on each channel. Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo cartridges. Ganged Bass and Treble Controls. Valves ECC83 (2), EL84 (2), EZ81. For 2-3 ohm speakers. Assembled with 12 months' guarantee Carr. 11/6 **£11.19.6**

R.S.C. 6/12V CAR BATTERY CHARGERS

Complete kit of parts incl. Ammeter and Circuit. **49/9**

6 amp heavy duty with variable charge rate selector **69/9**

All types 200-250v. A.C. mains. Ready built 10/- extra.

SENSATIONAL R.S.C. HIGH FIDELITY STEREO PACKAGE OFFERS

"PACKAGE 3" 30 WATT SYSTEM
 ★ Goldring Transcription Turntable on Plinth
 ★ Shure Magnetic Pick-up Cartridge
 ★ Super 30 Amplifier in cabinet
 ★ Pair of Stanton Loudspeaker Units
 Special inclusive price. Fully wired units ready to "plug-in". Carr. 25/-
85 Gns.
TERMS AVAILABLE ALL PACKAGE OFFERS

Matched for optimum performance. Send for coloured brochure showing other money saving offers.



"PACKAGE 2" 30 WATT SYSTEM
 ★ Garrard SP25 Mk II Turntable on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ Super 30 Amplifier in cabinet
 ★ Pair of Stanton Loudspeaker Units
 Special inclusive price. Fully wired units ready to "plug-in". Carr. 25/-
75 Gns.

AUDIOTRINE HIGH FIDELITY LOUSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround giving low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range 40-15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.

Prices include carriage. HF100D 12" 15W £5.15.0
 HF50H 5" 10W 57/9 HF120 12" 15W 69/9
 HF80D 8" 8W 57/9 HF120D 12" 15W 79/9
 HF81D 8" 10W 4 Gns. HF126 12" 15W 89/9
 HF102D 10" 8W 59/9 HF126D 12" 15W 5 Gns.

HIGH FIDELITY LOUSPEAKER UNITS
 Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled woolen damping. Ported where appropriate. Credit terms available.



DORSET Size 16 x 11 x 9in. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 8in. Dual Cone £8.19.9 speaker. Imp. 3 or 15 ohms. Inc. Carr.

STANTON III Size 18x11x10in. Rating 10 watts. Incorporating Fane 803B speaker with roll rubber cone surround and 15,000 line magnet. High flux tweeter or Handsome Scandinavian design cabinet. Range 30-20,000 c.p.s. Im-16 Gns. realistic sound output. Inc. Carr.

GLOUCESTER Size 25 x 16 x 10in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Frequency range 12 1/2 Gns. 40-20,000 c.p.s. Impedance 15 ohms.

E2 EQUIPMENT CABINET
 Size 17" wide 14" deep 11" high. Cut for TA12, Super 15, Super 30 and other amplifiers. "Hinged" perspex cover. Satin Teak or Afrormosia veneer 8 Gns. finish. Price inc. carr.

MOTOR BOARDS cut for Garrard Turntables and many other units. Price 12/9

RECORD PLAYING UNITS

Money saving units. Ready to RP2 plus into Amplifier or Tape Recorder. Consisting of Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Mounted on Plinth. Inc. Perspex cover. Carr. 22 Gns. 15/- Plus 8/7 P.T. surcharge.

RP3 As above but with Goldring Lenco GL68 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. Carr. 21/- surcharge.

£28 Inc. P.T. surcharge

R.S.C. PLINTHS



For Record Playing units. Teak finish cut for Garrard 3000, AT6, AT60, SP25 or Goldring GL68. Available with clear Perspex cover as ill. Inc. Carr. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/9

59/9 1000. 2000.

BLACK POOL R-S-C-TA12 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ 20-250V A.C. mains ★ Frequency Response 30-20,000 c.p.s.—2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise—70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV ★ Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 months warranty 15 Gns 0/12 1/2 Car. Deposit £4.16 and 9 monthly pymts 29/- (Total 17 GNS.) Or in Teak or Afrormosia veneer housing 19 Gns. Dep. £4.19.0 and 9 monthly payments 39/- (Total £22.10.0)



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 12,000 line 10 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. 5 Gns. Or Senior 15 watt inc. HF 126 15,000 line Speaker 6 Gns. Carr. 6/6

HI-FI SPEAKER ENCLOSURES Teak or Afrormosia veneer finish. Modern design. Acoustically lined and ported. Inc. carr. 4 Gns.

JES Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. 5 Gns.

SE10 For outstanding results with 10in Hi-Fi speaker. Size 24 x 15 x 10in. £5.10.0

SE12 For excellent performance with 12in Hi-Fi speaker and Twt. Size 26 x 16 x 10in. Pressurised. £6 Gns.

R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250V. A.C. mains operated Frequency Response 30-20,000 c.p.s.—2dB Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm speakers. Max. sensitivity 5mV. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 5 1/2in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Carr. 7/6 Or factory built with 12 months guarantee. 8 Gns.

INTEREST CHARGES REFUNDED ON Credit Sales settled in 3 months.

Total cost of parts with detailed wiring diagrams & instructions. 14 Gns.

Or factory built 16 1/2 Gns. Or in Teak finished cabinet as illustrated 19 1/2 Gns. Terms: Deposit £5 and 9 monthly payments £2. Total £23.

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ High-sensitivity ★ 200-250V. A.C. Mains operation ★ Sharp A.M. Rejection. ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Simple alignment instructions. ★ Output available for feeding tuning meter. ★ Tuner head using silicone Planar Transistors. ★ Designed for standard 8 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry. Only high grade transistors and components used. A quality product at considerably less than the cost of comparable units. Stereo version, all parts 18 Gns. Inc. Carr. Assembled £22 Gns. inc. carr.

R.S.C. SUPER 15 HI-FI AMPLIFIER SOLID STATE CONSTRUCTION R.S.C. SUPER 30 STEREO AMPLIFIER

FULLY TRANSISTORISED 200/250V. A.C. Mains. OUTPUT 10 WATTS R.M.S. cont. into 15 ohms. 15 WATTS R.M.S. cont. into 9-4 ohms. TRANSISTORS, 9 current types of high quality by leading manufacturers. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10Kc/s. NEG FEEDBACK: 52dB. BASS CONTROL: +17dB to -15dB at 50 c/s. HUM LEVEL: -75dB. HARMONIC DISTORTION at 10 Watts 1,000 c.p.s. 0.2%. Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6 11 1/2 Gns. Supplied factory built 15 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.0). Or in Teak or Afrormosia veneer housing as illustrated. 19 Gns. ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING MANUFACTURERS.

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. High quality Ganged Pots. Matched Components. CROSS TALK: -52dB at 1,000 c.p.s. CONTROL: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Right 18 s.w.s. Chassis. Size approx. 12in. wide, 8in. high and 8in. deep. Neon Panel indicator. Attractive Facia Plate and Spun Silver Matching Knobs. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15. THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon). CURRIBLY AVAILABLE SUPER SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. Carr. 15/- Unit factory built 28 Gns. or deposit £7.5.0 and 9 monthly payments 58/3. (Total £32.13.3). Or in veneered housing 31 Gns. Carr. 15/- or deposit £7.3.6 and 9 monthly payments 64/- (Total £35.18.6). Send S.A.E. for leaflet.

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
BRISTOL 14 Lower Castle St. (Half-day Wed.) Tel. 22904
BIRMINGHAM 30/31 Gt. Western Arcade opp. Snow Hill Station 021-236-1279 (Half-day Wed.)
DERBY 26 Osaston Rd. The Spot (Half-day Wed.) Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
 403 Sauchiehall St. (Opp. Locarno) (Half-day Tues.) Tel. 332-1572
HULL 91 Paragon Street. (Half-day Thursday) Tel. 20505

R.S.C. HI-FI CENTRES LTD.

MAIL ORDERS TO: 102 Hunconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 1/6 extra under £2. 5/6 extra under £5. Trade supplied S.A.E. with enquiries please. HI-FI Catalogue 4/6. Open all day Sats. except High Holborn

32 High Street. (Half-day Thurs.) Tel. 56420 **LEICESTER**
 5-7 County (Mecca) Arcade, Briggate (Half-day Wed) Tel 28252 **LEEDS**
 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**
 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1829 **LONDON**
 96 High Holborn, WC1. Tel. HOL 9874 (Half-day Sat.)
 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 **MANCHESTER**
 106 Newport Rd (Half-day Wed) Tel. 47096 **MIDDLESBROUGH**
 41 Blackett Street (Opp. Fanlocks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 769-0199/1649

1A7 7/9	6BH6 7/8	6K6GT 5/-	787 48/-	20L1 17/-	78 5/-	DF96 6/9	ECC88 7/-	EM80 7/8	PCX94 11/3	8130 35/-	UL84 7/-
1CP31 3/8	6B7G 9/-	6K7M 5/9	7Y4 8/8	20P4 19/-	80 8/0	DE391 2/6	ECF80 6/8	EM81 7/8	PCF89 8/8	8F4 3/-	UM80 6/-
1D5 7/-	6HQA 7/-	6K7G 2/-	9BW8 7/-	20P5 13/-	85A2 7/3	DH77 4/8	ECF82 7/-	EM84 7/8	PCX189 11/8	8P41 3/8	UL6 13/8
1H5 7/-	6BR7 12/-	6K7GT 4/8	9C1 12/-	25A5 5/9	150B2 9/8	DK22 7/9	ECH21 12/8	PCCH21 12/8	ESL15020/3	8P61 3/8	UU7 13/8
1LD5 5/-	6FR3 12/8	6K8M 6/8	10C2 12/8	25LGT 5/8	150C4 7/8	DK91 5/8	ECH35 11/-	EY81 7/8	PCF84 8/-	8T25 8/8	UV9 8/-
1N5GT 8/-	6B87 16/9	6K8G 3/-	10F1 9/-	25Y5 6/-	801 6/-	DK92 8/-	ECH42 11/-	EY86 7/8	PCF84 8/-	8U25 19/8	UV21 9/-
1R5 5/8	6BW6 14/-	6K8GT 7/-	10F3 8/-	25Z4 6/3	807 7/-	DK96 7/8	ECH81 5/8	EY88 7/8	PCF84 8/-	8U25 19/8	UV21 9/-
841 5/-	6BW7 14/-	6K25 20/-	10F9 9/9	25Z5 7/-	81USA 8/-	D166 15/-	ECH88 8/8	EZ40 8/-	PCF80 10/-	8U2150 12/8	UV41 7/-
185 4/-	611 9/8	10F18 9/-	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
1T4 3/-	6C4 2/9	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
3A4 3/8	6C5G 4/8	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
3Q4 6/8	6C6 3/8	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
3Q5 6/8	6C6 3/8	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
384 4/8	6C6 3/8	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
3V4 5/8	6C6 3/8	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
6R4G 9/8	6C6 3/8	611 9/8	10F18 9/9	25Z6 8/8	81USA 8/-	D166 15/-	ECH88 8/8	EZ41 10/-	PCF80 10/-	8U2150 12/8	UV41 7/-
6U4G 4/-	6E5 7/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
5Y4G 3/-	6F1 9/-	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
5Y3GT 5/8	6F5G 5/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
5Z4G 6/8	6F6G 6/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6/30L2 13/-	6F8G 4/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6A7 15/8	6F9G 4/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6A8G 12/8	6F13 5/-	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6A7 3/8	6F14 12/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6AK5 4/8	6F23 13/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6AL5 3/8	6F24 12/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6AM5 2/8	6F25 12/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6AM6 3/8	6F28 11/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6AQ5 6/-	6G6 2/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6A87G 15/-	6H6 2/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6A76 4/8	6J5G 2/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6A76 6/8	6J5G 2/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6B4G 15/-	6J5GT 4/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6B8G 2/-	6J7M 7/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6BA6 5/-	6J7G 4/9	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-
6B6 5/-	6J7GT 6/8	68H7 3/3	12A7 7/8	30P5 14/-	5763 10/-	DY86 6/-	EF9 20/-	KT36 17/8	PCU84 9/8	U26 13/8	VT25 5/-

SPECIAL 24 HOUR SERVICE

OBsolete TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Express postage 9d. per valve.

Ordinary postage 6d. per valve. C.W.O. No C.O.D.

Complete range of T.V. Tubes available from £4.5.0.

Manufacturers and Export Inquiries Welcome

**Special 24 Hour
Express Mail
Order Service**

SETS OF VALVES

DAF91, DF91, DK91, DL92 or DL94 19/- the set
DAF96, DF96, DK96, DL96 27/6 the set

BRAND NEW TRANSISTORS

AC127 7/8	OC25 11/-	OC71 4/8	OC81 4/-	OC82D 6/-
AF114 7/-	OC29 16/-	OC72 6/-	OC81D 4/-	OC83 6/-
AF115 7/-	OC33 11/8	OC73 6/-	OC81DB 6/-	OC10 7/-
AF116 7/-	OC44 4/8	OC76 6/-	OC82 6/-	OC171 8/-
AF117 6/8	OC45 4/-	OC77 8/-	OC82 6/-	OC200 7/8

SEND S.A.E. FOR LIST OF 2,000 TYPES

Bargain—Car Radios. Our Price 9 gns. Negative or positive earth (switched) fully transistorised (12v) medium and long waves. Speaker and fitting kit supplied at no extra cost. P/P 5/-.

Sonotone 9TA and 9TA/H.C. Diamond Cartridge brand new, boxed in manufacturers' carton 49/6 + 2/6 p/p. Acos GP 91-1 and GP 91-3 stereo compatible cartridges, new in sealed manufacturers' cartons 22/6 + 2/6 p/p.

BAS TAPe 25% OFF

5"	600ft.	14/-	900ft.	19/-	1200ft.	30/-
5 1/2"	900ft.	19/-	1200ft.	24/-	1800ft.	39/-
7"	1200ft.	24/-	1800ft.	35/-	2400ft.	57/-

P. & P. 2/- per reel.—over £5 FREE

KELETRON HI-FI SPEAKER K12TC—12in. 12 watt

Offers an exceptionally smooth and extended response, with very low level of distortion from the specially designed twin diaphragms.

Frequency Response: 30-16,000Hz.
Impedance: 15-160Hm.

OUR SPECIAL PRICE 97/6 PLUS P. & P. 6/6

BARGAIN — Speakers, Hi-Fi — The Baker Selhurst Stalwart. 12in. round, 15 watt rating, 12,000 lines gauss, 15 ohms, response 45-13,000c/s. Bass resonance 40-50c/s. solid aluminium chassis. Our price £5.9.6.

Brand new, p/p 6/6

DULCI HI-FI UNITS

The Dulci range of tuners and amplifiers offer exceptional quality at a sensible price.
Amplifiers: 207 and 207M. Tuners: FMT and FMT7s. SEND NOW FOR FULL DETAILS

TRIO Stereo Moving Magnet Cartridge Model AD76K. Diamond Stereo LP Stylus. Frequency response 20-20,000 c/s output. 7mv tracking pressure 2 grammes ± 0.5 gm. Fully guaranteed. Price 85/- p/p free.

Bargain—Changer decks at lowest prices ever

Beautiful teak	1025	£8.0.0.
plinth and perspex	2025	£8.10.6.
cover to suit	AT60 Mk. II	£12.19.6.
these units	SP25 Mk. II	£12.0.0.
5 Gns. P. & P. Free	3500 with Son	
	9TA.HC diam. cart.	£10.19.6.

Add 10/- p/p for each Garrard unit


KELETRON SPEAKER ENCLOSURES

Type: INFINITE BAFFLE
Model 8: 8" plus 3" tweeter
Model 13B: 13" x 8" EMI
Both £4.19.6 each
Model 1012: 10" or 12" plus 4" tweeter
£7.19.6

All enclosures are in oiled teak, fully built. Please add 8/- p. & p. on each enclosure

BARGAIN — Speakers, Hi-Fi — The Baker Selhurst Guitur Group. 25, 12in. round, 25 watt rating, 12,000 gauss, 15 ohms, response 30-10,000c/s, solid aluminium chassis, heavy duty cone. Our price £5.9.6.

Brand new, p/p 6/6

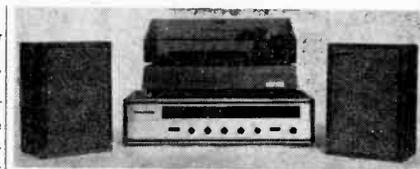

The greatest HI-FI Budget system to-day—can't be beaten—price or quality anywhere—look at these great features—then compare.

Teleton F2000 tuner amp. AM-FM with multiplex decoder and A.F.C.—2 x 5w channels R.M.S. Bass Volume Treble Balance controls, a truly outstanding unit £ 39 12 1
Garrard SP 25 Mk II Transcription deck 15 6 4
Teleton SA 1003 matching speaker enclosures 9 5 0
Sonotone 9 TA Diamond Cartridge 3 16 7
Plinth and Perspex cover 7 0 0
£75 0 0

Exclusively offered by WALDON at the remarkably low price of 63 gns.

E.M.I. HI-FI SPEAKERS


SET 450: 13 x 8 with two built-in tweeters and cross-over unit. Our Price 89/6. 3 or 15 ohm, 10w, 40-13,000 Hz.
SET 850: 6 1/2" bass plus 3 1/2" tweeter and cross-over unit. 8 ohm. 10w, 65-20,000 Hz. 79/6.
SET 250: 5 1/2" heavy duty bass plus 3 1/2" tweeter and cross-over unit. 8 ohm, 6w, 80-20,000 Hz. 85/-.
Add 5/6 p/p for each speaker set

Build yourself a quality transistor radio

backed by our
after sales service!

roamer seven mk IV SEVEN WAVEBAND PORTABLE

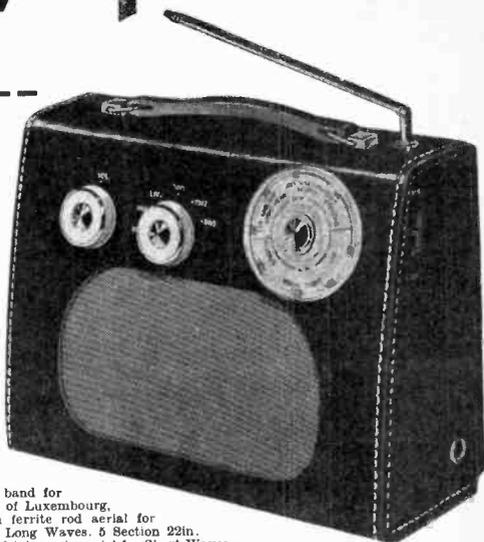SEVEN TUNABLE WAVEBANDS—
MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.



pocket five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 6½ x 1¼ x 3¼in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
44'6 P. & P.
3/6

Extra M.W. band for easier tuning of Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push pull output. 7 transistors and 2 diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 3in. P.M. speaker for rich-tone volume. Air spaced ganged tuning condenser. Separate on/off switch, volume control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build.

Total building costs
£5.19.6 P. & P.
7/6 Personal Earpiece with switched socket for private listening 5/- extra.

Parts price list and easy build plans 3/- (Free with parts).

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½in. x 1½in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).




Total building costs
47'6 P. & P.
3/9

NEW LOOK melody six

TWO WAVEBAND PORTABLE

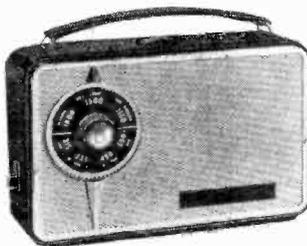8 stages—6 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. stages for extra boost. High "Q" Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 4 x 2in. Easy build plans and parts price list 2/- (FREE with parts).



Total building costs
69'6 P. & P.
4/3

super seven

THREE WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings. The ideal radio for home or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts price list 2/- (FREE with parts) (Personal Earpiece with switched socket for private listening 5/- extra.)



Total building costs
69'6 P. & P.
4/6

roamer six

SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build Plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra.)



Total building costs
79'6 P. & P.
4/6

* Callers side entrance Stylo Shoe Shop
* Open 10-1, 2.30-4.30 Mon-Fri. 9-12.30 Sat

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. Bedford 52367

I enclose £..... please send items marked

ROAMER SEVEN	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	SUPER SEVEN	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	MELODY SIX	<input type="checkbox"/>

Parts price list and plans for

Name

Address

PW3

MULTIMETERS for EVERY purpose!

LAFAYETTE DE-LUXE 100K Ω/VOLT "LAB TESTER" Giant 6 1/2 in. scale Built-in meter protection 0/5/2-5/10/50/250/600/1,000V D.C. 0/3/10/50/250/500/1,000V A.C. 0/10/100/1k/10/100/500mA 2/5/10A. 0/1K/10K/100K/10M/10M Ω. -10 to 49-4dB £18.18.0. P. & P. 5/-



TE-900 20,000 Ω/VOLT GIANT MULTIMETER mirror scale and overload protection. 6 1/2 in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V A.C. 0/25/12.5/10/50/250/1,000/5,000V D.C. 0/50/100/100/500 mA/10 amp. D.C. 0.2K/200K/20 MEG. OHM. £15. P. & P. 5/-




LAFAYETTE 57 Range Super 50k Ω/volt Multi-meter. D.C. volts 12 mV -1000V. A.C. volts 1.5V -1000V. D.C. current 25 μA -10 amp. Ohms 0/10meg Ω dB -20 to +81 dB. Overload protection. £12.10.0. Carr. 3/6.



NEW MODEL 500 30,000 O.P.V. with overload protection. mirror scale 0/-5/2.5/10/25/50/250/500/1,000V. D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50/100/500/500mA. 12 amp. D.C. 0/60K/6 Meg. /60 Meg. Ω. £8.17.6. Post paid.

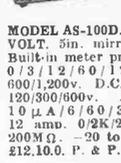MODEL AS-100D. 100K Ω/VOLT. 5 in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V. D.C. 0/6/30/120/300/600V. A.C. 0/10 μA/6/60/300 mA/12 amp. 0/2K/200K/2M/200M Ω. -20 to +17dB. £12.10.0. P. & P. 3/6.



PROFESSIONAL 20,000 ohm LAB. TYPE Multimeter. Automatic overload protection, mirror scale. Ranges: 1/10/50/250/500/1,000 volts. D.C. and A.C. 0-500 μA, 10mA, 250mA. Current 0/20K/200K Ω megohm. Decibels: -20 to +22dB. £5.18.6. P. & P. 2/6.




MODEL TE-90 50,000 O.P.V. mirror scale overload protection. 0/3/12/60/300/600/1,200V. D.C. 0/6/30/120/300/600V. D.C. -03/6/60/600mA. D.C. 16K/160K/1.6/16meg Ω. -20 to +63dB. £7.10.0. P. & P. 3/-




MODEL TE-12 20,000 O.P.V. 0-0.6/6/30/120/600/1,200/3,000/6,000V. 1 C. 0/6/30/120/600/1,200V. A.C. 0/6/60/1k/6/60/600mA. 0/6K/60K/6Meg. /60 Meg. Ω. 50pF. 0-2mFd. £5.18.6. P. & P. 3/6.



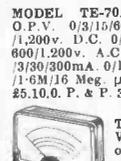MODEL TE-70 30,000 O.P.V. 0/2/15/60/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30 μA/3/30/300mA. 0/16K/160K/1.6M/16 Meg. Ω. £5.10.0. P. & P. 3/-



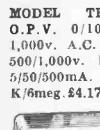MODEL TE-80. 20,000 O.P.V. 0/10/50/100/500/1,000V. A.C. 0/5/25/50/250/500/1,000V. D.C. 0-50 μA. 5/50/500mA. 0/5K/60K/600 K/6meg. £4.17.6. P. & P. 3/-



TE-51. NEW 90,000 Ω/VOLT MULTIMETER with overload protection and mirror scale. 0/6/60/120/1,200V. A.C. 0/3/30/60/300/600/3,000V. D.C. 0-60 μA/12/300mA. D.C. 0/60K/6 meg. ohm. 92/6. P. & P. 2/6.



MODEL TE-10A. 200k Ω/VOLT 5/25/50/250/500/2,500V. D.C. 0/50/100/500/1,000 v. A.C. 0/50 μA/2.5 mA/250 mA. D.C. 0/5K/6 meg. ohm. -20 to +22dB. 10-0, 100mFd. 0-100-0-1mFd. 69/6. P. & P. 2/6.



MODEL PT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100K Ω. 39/6. P. & P. 1/6.



NEW STAR SR-200 SSB AMATEUR RECEIVER

An exciting new receiver covering 6 amateur bands 160/80/40/20/15/10 metres. Illuminated slide rule dial ● 8 meter ● Crystal calibrator ● Product detector ● Automatic noise limiter ● HF tuning and gain controls ● Speaker or phone outputs ● 8 valves, 2 transistors, 2 diodes 220/240V. A.C. Supplied brand new and guaranteed. £40.0.0. Carr. 10/-



T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1/003/1/3/1/3/10/30/100/300V. R.M.S. 4cps. -2Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.10.0. Carr. 5/-



TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for every day use. Y amp. Bandwidth 2 CFS-1 MHz. Input imp. 2 meg Ω 25 pF. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240V a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/-



AVOMETERS

Supplied in excellent condition, fully tested and checked. Complete with prods, leads and instructions. Model 7 £13.10.0. P. and P. 7/6.



TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-111Ω. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0-1dB x 10) + (1dB x 10) + 10 + 20 -30 + 40dB. Frequency: d.c. to 200kHz (-3dB). Accuracy: 0-0.5dB. +Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-



NEW CATALOGUE

Nearly 200 pages giving full details of a comprehensive range of COMPONENTS, TEST EQUIPMENT, COMMUNICATION EQUIPMENT AND HI-FI EQUIPMENT. Each section greatly enlarged and fully illustrated. Thousands of items many at bargain prices.

Free Discount Coupons Value 10/-

SEND NOW-ONLY 7/6 PEPI-



UNR-30 4-BAND COMMUNICATION RECEIVER


Covering 550 Kc/s-30 Mc/s. Incorporates variable BFO for CW/SSB reception. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instruct-13 gns. Carr. 7/6

LAFAYETTE SOLID STATE HA600 RECEIVER 5 BAND AM/CW/SSB AMATEUR AND SHOR WAVE 150 Kc/s-400 Kc/s and 550 Kc/s-30 Mc/s FET front end ● 2 mechanical filters ● Huge dial ● Product detector ● Crystal calibrator ● Variable BFO ● Noise limited ● S meter ● 24in. Bandspread ● 230V. A.C./12V. D.C. neg. earth operation ● RF gain control. Size 15in. x 9 1/2in. x 8 1/2in. Weight 18 lbs. EXCEPTIONAL VALUE. £25. Carr. 10/- S.A.E. for full details.



TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kc/s to 30 Mc/s. continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW ● ANL ● Variable BFO ● 8 meter ● SSB. bandspread dial ● IF 485 Kc/s ● Audio output 1.5 W. ● Variable RF and AF gain controls. 115/250V A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £39.15.0. carriage paid. TRIO COMMUNICATION TYPE HEADPHONES. Normally £5.19.6. OUR PRICE £5.15.0 if purchased with above receiver.

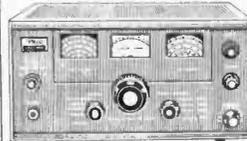

LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £37.10.0. Carr. 10/-




LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER

19 transistors, 8 diodes, 1HF music power, 30W at 8 Ω. Response 30-20,000 +2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16 Ω. Separate L and R. Volume control. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary meta. case. Size 10 1/2 x 3 9/16 x 7 13/16in. Operation 115/230V. A.C. £28. Carriage 7/6.



GARRARD

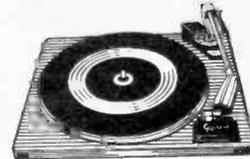FULL CURRENT RANGE OFFERED BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS



SRP22 Mono	£6.10.0
SRP22 Stereo	£6.18.6
*1025 Mono	£7.10.0
*1025 Stereo	£7.18.6
*2025 Stereo	£8. 8.0
*3025 T/C Mono/Stereo	£8.17.6
*3000 Stereo	£9.18.6
*SP25 MKII	£11.18.6
*SL55	£11.18.6
A70 MK II	£12.10.0
*AT60 MKII	£13.10.0
*SL65	£14.14.0
AP75	£19. 0.0
401	£28. 7.6
SL75	£28. 0.0
SL95	£35. 0.0

Carriage/insurance 7/6 extra any model. *Special offer base and cover available for these models at £4.15.0. Carr. 5/- Full range of Garrard accessories available.

E.M.I. SINGLE PLAYERS

4 speed with separate arm and cartridge. 52/6. Carr. 3/6.

FIELD TELEPHONES TYPE L

Generator ringing, metal cases. Operates from two 1.5V. batteries (not supplied). Excellent condition. £24.10.0 per pair. Carr. 10/-

GW SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2


OPEN
9 a.m. to 6 p.m.
every day Monday to Saturday.
Trucks supplied.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

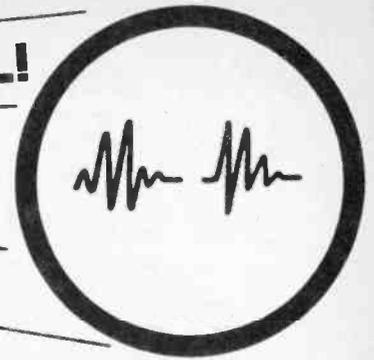


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing ...


1 ▶ OWN and HANDLE a

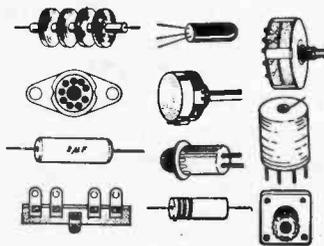complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

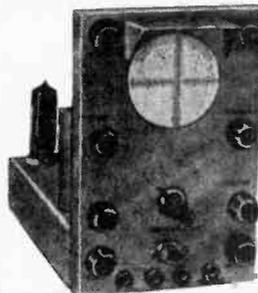a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND **CIRCUIT DIAGRAMS**

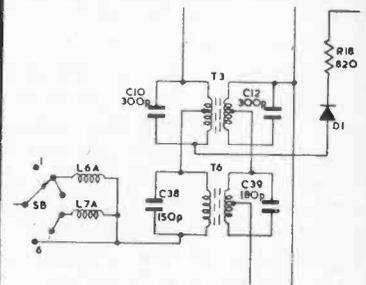

4 ▶ CARRY OUT OVER **40** EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK ... INCLUDING ...

- VALVE EXPERIMENTS
 - TRANSISTOR EXPERIMENTS
 - AMPLIFIERS
 - OSCILLATORS
 - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
 - COMPUTER CIRCUIT
 - BASIC RADIO RECEIVER
 - ELECTRONIC SWITCH
 - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
 - D.C. EXPERIMENTS
 - SIMPLE COUNTER
 - TIME DELAY CIRCUIT
 - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS PLEASE PW 3

PRACTICAL WIRELESS

VOL 44 No 11

Issue 745

MARCH 1969

TOPIC OF THE MONTH

Ancient and Modern

WE would dearly like to meet the character who coined the phrase "*the customer is always right*". Many organisations are either blissfully unaware of this sentiment or feel that such consideration is below their dignity. As readers of *Practical Wireless*, you who are (we hope) eagerly scanning these lines are in a sense customers of the Editor. And before you all rush for pens and typewriters, let it be said that all of us on the editorial staff are anxious to please our customers—at least to the extent that as we have so many customers it is impossible to please everyone all the time!

In recent months it has been our policy to lay a greater emphasis on semiconductor devices. Most of the industry, including the domestic equipment field, is using semiconductors; not only that but as the months go by more and more sophisticated devices become available. It is obvious that the home constructor generally wants to be as up to date as possible and we hope that the articles we publish give him the raw material to achieve this end.

However, the postbag during this period has contained a large number of letters from readers deploring the fact that we appear to be debarring the humble valve from our pages. The readers who write thus have perfectly valid arguments for their case. The valve champions say that they have plenty of valves in their spares boxes which are still capable of giving good results; they say that they *prefer* using valves to semiconductors; they point out that in some applications, valves can still give as good a service, or better, than transistors.

There is no doubt that the valve is far from obsolete to the home constructor or to those who repair equipment either as a hobby or professionally. People are still buying valves in some quantity and they are cheap and plentiful; as an exercise take a look through the advertisement pages and see how many valves are being offered for sale!

As the customer is (nearly) always right, we will therefore make a point of incorporating information on valve projects (and the main article this month describes a valve receiver) but must bear in mind advancing technology and place the main emphasis on more modern circuitry. We might then please *all* readers—though we doubt if this is strictly possible!

W. N. STEVENS—*Editor*.

NEWS AND COMMENT

Leader	825
News and Comment	826, 827
MW Column <i>by C. Molloy</i>	833
On the Short Waves <i>by Christopher Danpure and David Gibson, G3JDG</i>	840
Your Questions Answered	847
Practically Wireless <i>by Henry</i>	857
Letters to the Editor	862, 865

CONSTRUCTIONAL

Progressive Superhet <i>by F. G. Rayer, G3OGR</i>	828
One-Sixty Superverter <i>by A. S. Carpenter, G3TYJ</i>	844
Six Transistor FM Tuner, Part 2 <i>by W. Cameron</i>	852
Microphone Preamplifier <i>by J. A. Jebb</i>	858

OTHER FEATURES

Repairing Radio Sets, Part 3 <i>by H. W. Hellyer</i>	834
Home Workshop Practice, Part 1 <i>by P. Hamley</i>	848
Magnetic Sound Recording, Part 2 <i>by W. S. Fowler</i>	866
P.W. Guide to Components, Part 4, Modern Electronic Components, <i>by M. K. Titman, B.Sc.</i>	870

APRIL ISSUE WILL BE PUBLISHED
ON MARCH 7th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2. Phone: 01 836 4363. Subscription rates, including postage: 42s. per year to any part of the world. © IPC Magazines Ltd., 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

NEWS AND COMMENT...

FILMSHOW 1969

The annual filmshow, organised jointly by Mullard Ltd., *Practical Wireless* and *Practical Television* magazines is to be held once again at Caxton Hall, Caxton Street, Westminster, London, S.W.1. The date this year is 28 March and the show will start at 7.30 p.m. prompt.

The programme will include a lecture on Colour Television, covering the setting-up procedure and dealing in detail with degaussing, purity, convergence and grey-scale tracking.

The film is entitled *It's the Tube that makes the Colour* and describes the manufacture of Mullard Colour Screen TV picture tubes.

Refreshments, free of charge folks, will be served at half-time.

Application for tickets—which are also FREE—should be made to "Filmshow", *Practical Wireless*, Tower House, Southampton Street, London, W.C.2. A stamped, addressed envelope enclosed with all applications please.

MOBILE RALLIES SO FAR

APRIL 20—North Midlands at Drayton Manor Park, near Tamworth, Staffordshire.

MAY 18—Northern Mobile Rally.

JUNE 1—Amateur Radio Mobile Society.

JUNE 29—Longleat at Longleat Park, near Warminster, Wiltshire.

JULY 6—South Shields Mobile Rally.

AUGUST 10—RSGB Mobile Rally at Woburn Abbey.

AUGUST 17—Derby and District.

AUGUST 24—Torbay Amateur Radio Society.

Club Secretaries: if you want us to publish details of your Mobile Rally, drop us a line and we'll try and put information in the next issue.

AH, THAT'S BETTER!




There is a persistent, boring, increasing pain about a burn that won't let you forget it and it can turn into a nasty sore, if neglected.

The beginner dealing with tools with which he isn't familiar is apt to have a burning accident, and the professional, with all his know-how, sometimes gets a trifle careless.

All sorts of domestic remedies can be tried and fail—butter, baking powder, iodine. The answer now is a quite new product—"Burneze", price 7s 3d.

Burneze is neither sticky, messy nor glutinous and to spray for 8 to 10 seconds, which thoroughly chills the area, is sufficient. It is a scientifically developed product which takes the heat out of the burn immediately so that tissue damage is reduced. A topical anaesthetic is included to soothe pain. It also reduces the over-release of histamine which causes blisters, and inhibits the spread of toxic molecules.

MULLARD AT BRISTOL SCIENCE EXHIBITION

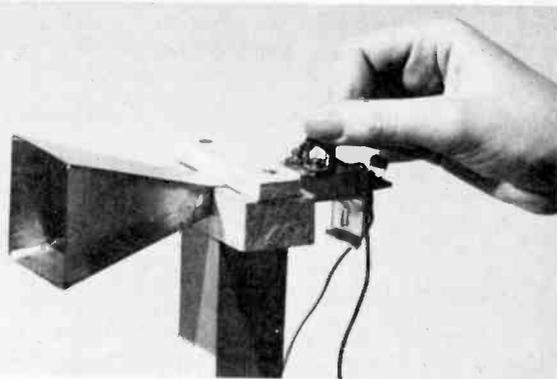

At the exhibition arranged by the Association for Science Education in the School of Chemistry, Bristol University, from 1st to 3rd January 1969, Mullard Educational Service demonstrated a simple high-impedance d.c. voltmeter and microwave system, both primarily intended for construction by schools and technical college pupils or staff.

The voltmeter can measure up to 500V d.c. in eight ranges. It incorporates a d.c. amplifier using a field effect transistor type BFW64, so that on every range the input impedance exceeds 10M Ω . It requires a supply voltage of 9V and takes a current of approximately 6mA.

The Gunn effect device greatly facilitates the construction of a simple, compact microwave system for demonstrating the properties of radio waves. The transmitter consists of a transmitting horn attached to a short length of waveguide containing a Gunn effect device. An adjustable screw in the cavity behind the device provides a means of tuning the transmitter by matching the waveguide to the device. Power is supplied by a 9V battery and the current drain is approximately 100mA. With a Gunn effect device type CXY11A the output is about 6mW at 10Gc/s.

The receiver has a horn and a waveguide similar to those of the transmitter. The signal is detected by a microwave diode and is indicated on a 50 μ A meter.

The microwave transmitter being tuned in the photograph consists simply of a Gunn effect device inside a short length of waveguide attached to the transmitting horn. A resistor in series with the Gunn device and a zener diode in parallel with it ensures that the applied voltage is of the correct value.

NEW WELLER CATALOGUE

Weller Electric Ltd., the manufacturers of soldering tools, have just published a new catalogue which deals with their range of temperature controlled soldering tools.

This four page, coloured catalogue deals with many aspects of soldering with temperature-controlled soldering pencils and their inherent advantages over more conventional tools. Details are given on the curie point principle—the control factor behind these soldering pencils, with information concerning cost saving Wellertips, safety aspects, and temperature and tip size choices for the TCP range. A price list for the complete range of Weller soldering tools and accessories is included with the catalogue.

This catalogue is available on request to Weller Electric Ltd., Redkirk Way, Horsham, Sussex.

NEWS AND COMMENT...

GET IT BOXED

The complete range of Electroniques die-cast boxes now extends from 4 x 3 x 1 in. to 11 x 7 x 6 in.

The new larger sizes incorporate the slot guide system unique to Electroniques boxes used on the original range.

The four larger sizes, which are not available elsewhere, will prove useful in housing equipment for which fabricated steel cases are currently used.

The greater depth offered by the new boxes also permits the inclusion of larger components such as wafer switch assemblies and multi-ganged potentiometers.

Further inquiries to: Electroniques, Edinburgh Way, Harlow, Essex. (Manufacturing industry inquiries to Electronic Services, same address).

RADIO, TV AND ELECTRONICS BOOKS

The Modern Book Co., 19-21 Praed Street, London, N.W.2 announce their new catalogue of technical books. Price of this invaluable booklet is 2s.

COMPONENT SHOW IN MAY

Space for the 21st London Electronic Component Show in May which celebrates its majority in 1969 by going fully international is now completely booked up.

The organisers, Industrial Exhibitions Limited, report that a substantial influx of foreign exhibitors, added to the fact that many of the UK firms taking part have increased their stand space, means that the show is 25% bigger than before.

NORTHERN POLYTECHNIC AND MULLARD LTD. RUN JOINT COURSE ON I.C. LOGIC SYSTEM DESIGN



This picture shows members of the first one-week course in the theory and practice of integrated circuit logic system design at Northern Polytechnic, London. The courses are organised jointly by Mullard Ltd. and the Northern Polytechnic. The picture was taken on the last day when members took part in individual projects involving the use of integrated circuits. Typical examples included a traffic light control system, vending machine sequence logic and adder circuits. One course a month is planned until May of next year. December and January courses had their full complement of members and bookings for the remainder of the courses are coming in.

A YEAR OF ACHIEVEMENT



During 1969, BSR Ltd., the makers of record changers, confidently expect to achieve over 50% of the world's market following 1968's 47% share. In Great Britain nine out of ten record changers are made by BSR, yet this accounts for only a fifth of the output, the remainder are exported to over eighty countries throughout the world.

The photograph shows record changers of the MA 65, MA 70 and MA 75 range being manufactured at Old Hill, one of their three British factories.

LATEST HEATHKIT CATALOGUE

Heathkit will be pleased to forward a free catalogue to readers who care to write to them at their factory at Gloucester.

MORE GEN FROM MULLARDS

Pamphlet No. 21 in the series Educational Electronic Experiments issued by Mullard Educational Service describes a simple motor speed controller using a thyristor.

The circuit described is intended for the speed control of fractional horse power, a.c. series motors of the type normally used in electric hand drills and food mixers ($\frac{1}{2}$ h.p. maximum). The controller not only enables the speed of the motor to be varied but also maintains a reasonably constant speed under varying load conditions.

Also available from Mullard Educational Service is a pamphlet entitled *Introducing silicon planar transistors*. Its description of how silicon planar transistors are manufactured will be of use to teachers and students of electronics, and of interest to engineers using semiconductor devices.

Copies of these two pamphlets can be obtained from Mullard Educational Service, Mullard Limited, Mullard House, Torrington Place, London, W.C.1.

WITH the larger type of receiver, progressive stage-by-stage construction has several advantages. A simple but efficient working receiver is first obtained without very complicated construction, reducing chances of wiring errors and also initial expense. Extra valves and other circuitry can be added later, each being tested when fitted.

This receiver is built initially as a 4-valve (plus rectifier) superhet, having frequency changer, intermediate frequency amplifier, detection and output stages. In this form, it gives excellent results, covering one chosen waveband, without the complication of band-switching, a straightforward project of this kind should not present any difficulty even for a beginner.



F. G. RAYER G30GR

progressive SUPERHET

Band-switching is then added, so that the receiver has five switched ranges, as follows: (1) 150-400kc/s, (2) 525-1500kc/s, (3) 1.7-4.6Mc/s, (4) 4.1-12Mc/s, and (5) 11.5-31Mc/s. These cover long, medium and short waves. The receiver can be used on any of these bands as the coils are added and by testing it on each band as the coils are wired, difficulty or confusion in switching is eliminated.

A radio frequency amplifier is then added, without disturbing existing work. This r.f. stage increases sensitivity, and greatly reduces second channel interference on the h.f. bands; again the receiver can be tested as each r.f. coil is added. As the complete circuit has fifteen coils to cover the five bands, with associated switching, padders, etc., this method of proceeding step-by-step is very helpful in avoiding errors in wiring.

The complete coil and switch section is built into a screening box easily made from "universal chassis" flanged members, giving complete screening and a rigid assembly. The oscillator and mixer coils have small trimmers incorporated, and this saves space and work. The aerial coils have no pre-set trimmers, but a panel variable aerial trimmer, which is almost essential for best results with any aerial. All unused coils are shorted to avoid absorption losses.

To increase sensitivity and selectivity, a further i.f. amplifier can then be added. The other additions described can be added later. They include a signal-strength or S-meter with panel zero control, manual control for r.f. and i.f. gain, heterodyne oscillator for c.w. and for s.s.b. carrier insertion, and headphone jack. The dial allows direct calibration for all frequencies and also has a 0-500 logging scale. A ready-made, sprayed aluminium cabinet and panel are used resulting in a finished receiver of quite professional appearance and performance.

Basic Circuit

This is shown in Fig. 1, and it can be wired in this form before adding the band-switching. Assuming that the r.f. stage will in any case be added later, VC1 and VC2 are two sections of a 3-gang tuning capacitor. V1 is the frequency changer, and the grid coils are temporarily used as aerial coils by taking blue to aerial, and red to chassis. When

the r.f. stage is present, blue goes to r.f. valve anode and red to h.t. positive supply.

Each oscillator coil has its own particular padder capacitor value, as listed, and these are added with each coil, as the coils are wired in later. The grid and oscillator coils each have a small trimmer (TC) incorporated. The layout allows trimmers to be adjusted from below the chassis, and coil cores from above.

The aerial coils for the r.f. stage, when added, have no pre-set trimmers, and their cores are adjusted from under the chassis. V2 is the usual i.f. amplifier, V3 provides automatic volume control bias from one diode (pin 6), this being applied to V2. In the completed receiver, a.v.c. is applied to the r.f. stage and both i.f. stages. V3 also gives audio amplification, and finally the output stage V4 drives a speaker (or phones when required). V5 is an indirectly heated rectifier, and this avoids high initial surge voltages, a fuse protects this valve and the transformer. The final receiver requires a 100mA h.t. supply, this is easily provided by the transformer recommended. With this transformer, R15 and R16 (150Ω) are fitted to reduce the h.t. voltage a little, especially when fewer valves impose a lighter load, and to limit peak rectifier anode current.

When the r.f. stage is added, it does, of course, come in before the existing stages V1, the extra i.f. amplifier is placed between V1 and V2 in Fig. 1, the S-meter is operated by V2 cathode circuit, so could, if wished, be added to Fig. 1.

Chassis Dimensions

The chassis measures 13 × 8in. by 2½in. deep, the depth being needed to clear the coil box. Figure 2 shows the most important dimensions. The easiest method is to fix a piece of paper 13 × 8in. to the chassis with tape or a few spots of adhesive, and mark out on this in pencil then pierce through all drilling positions with a centre-punch or pointed tool, the paper is then removed and the chassis is drilled.

The 9-pin holders require ¼in. diameter holes (ECH81, 6BW6 and EZ81), and other holders need ⅜in. holes, these sizes are easily made with a screw-up chassis punch. It is wise to make the holes for the r.f. stage, extra i.f. stage, and b.f.o. at the

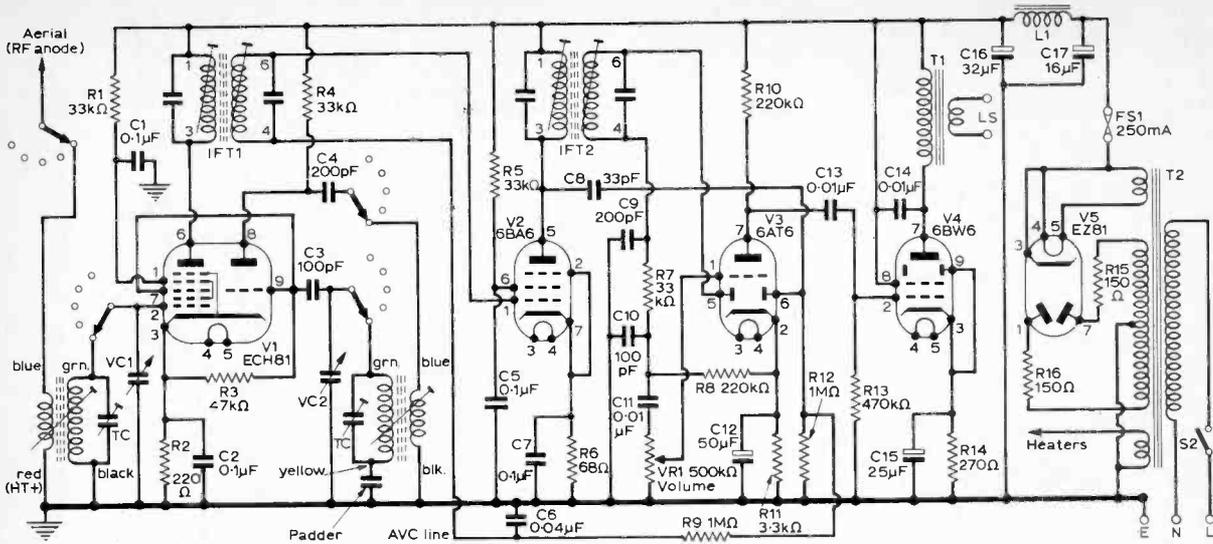


Fig. 1: The basic circuit of the Progressive Superhet; only one set of coils are shown.

same time. All coils occupy $\frac{1}{4}$ in. diameter holes, aerial coil 1 is under the ganged capacitor, but does not have to be adjusted from above. Mixer grid and oscillator coils for band 3 have to be reached from above with a core tool, with the ganged capacitor nearly closed.

Seven holes are necessary for each of the i.f. transformers, those to clear the four tags should be $\frac{1}{8}$ in. while two $\frac{1}{4}$ in. holes take fixing screws. A central $\frac{1}{8}$ in. hole allows one core to be reached from below. The mains transformer is bolted over a hole which will clear all tags and a piece $3 \times 1\frac{1}{2}$ in. is cut from the front of the chassis to take the

tuning drive mechanism. A paper template is provided with the drive, this is placed on the panel so that holes etc. can be marked and the large aperture is made by sawing between corner holes. Fixing holes should be cleared of burr with a countersink bit or a few turns with a larger drill, and all fragments and filings, etc., should be cleared away before fitting the switch, ganged capacitor, and other items. The ganged capacitor is raised by threaded spacers, long bolts with extra nuts, or some similar means, so that capacitor shaft and drive shaft are in line. Before fitting the capacitor, solder a lead to the bottom tags of each section (Fig. 2) and

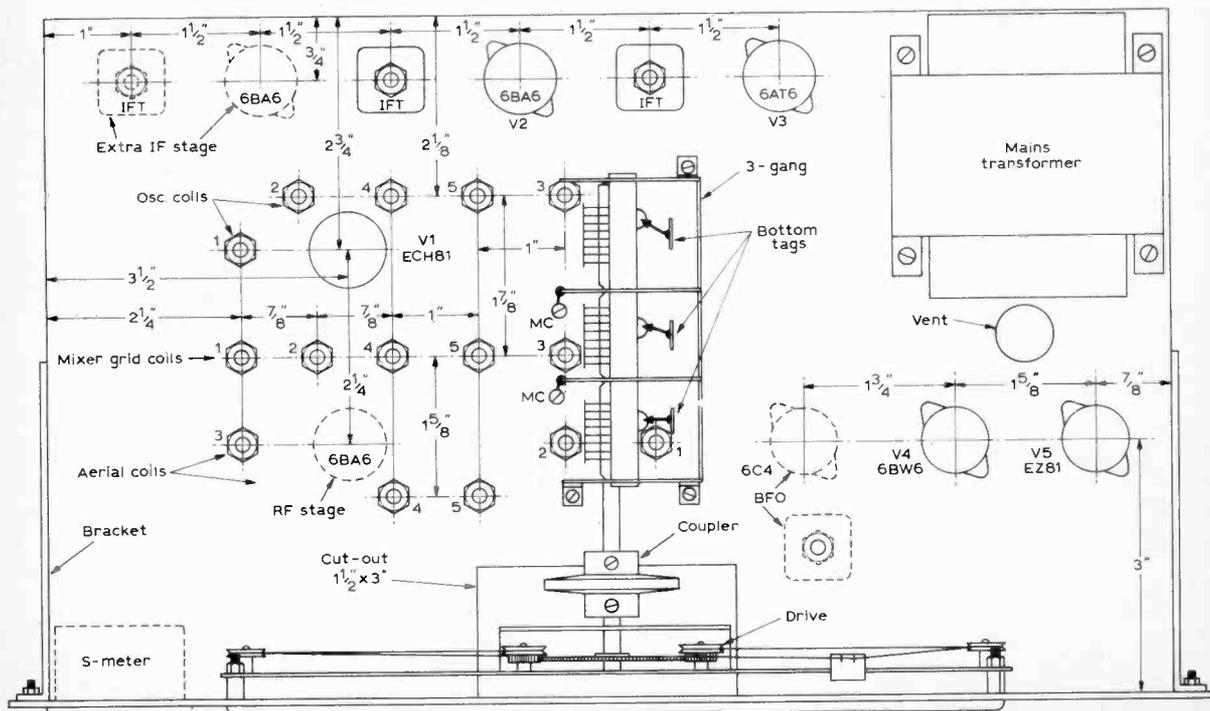


Fig. 2: The layout and details of the chassis viewed from the top.

★ components list

Take care that the i.f.t.s are bolted so that their tags are arranged as shown in Fig. 3, short pieces of insulated sleeving on the tags will prevent possible shorts to the chassis due to fragments of solder etc. Figure 3 shows the position occupied by the coil box, but the holder for V1 (Fig. 1) is wired before making and fitting this box. When the box is fitted later, run V1 anode lead out through a hole as shown, as this will later be taken to the adjacent extra i.f.t. The 6.3V heater lead then passes through the rear of the box to V2, while the h.t. positive lead will go through the box to the strip holding R10.

When the wiring of the basic circuit is completed, as in Fig. 3, it is wise to test the circuit. Figure 3 shows the positions of the b.f.o. pitch control, c.w./a.m./s.s.b. switch, band switch, aerial trimmer, and r.f./i.f. gain controls, but these will not yet be present; the coil box is also absent.

Take range 2 (medium wave) oscillator coil and the 270pF padder, the tags are identified by colours. Connect green to C3, using the lead marked "switch" in Fig. 3, similarly take blue to C4, yellow to the padder, and black to chassis. Assuming that the r.f. stage will be added later, connect the m.w. mixer grid coil blue to aerial, green to V1 pin 2, and red and black to chassis. The receiver can now be aligned and tested, and should give good results on this waveband.

If any wiring errors are made, these are most likely to be in the band-switching, so when the coil box and switch have been assembled and fitted, it is recommended that the set is tested again with only the same m.w. mixer and oscillator coils, but this time selected by the appropriate switch position, results should be the same as before. This is better than making a mistake which perhaps would result in a whole series of other coil connections being made incorrectly.

Coil Box

The coil box is made from a 6 × 5 × 2in. "universal chassis" with the addition of two extra 6 × 2in. runners. The chassis has two 6 × 2in. runners, two 5 × 2in. runners, and a 6 × 5in. flat plate. The two extra 6 × 2in. runners have about 3/4in. removed from the flanges at each end, so that they will fit inside the flanges of the 5 × 2in. runners. They can then be bolted together to form a box with three sections as shown in Fig. 3.

Drill 6BA clearance holes and punch a 1/2in. hole so that the switch mechanism can fit against the front runner. Similar holes are made in each 6 × 2in. runner, including the back one, this allows the switch shaft to pass through all runners and also two 6BA screwed rods, to hold the switch wafers. To avoid any inaccuracy, the box is taken apart and the front runner used as a template to mark drilling holes on the other runners, if this is done all holes will be exactly in line when the box is assembled.

Drill the flanges so that the box can be bolted to the chassis, position it with the switch shaft in the panel hole, mark through the flange holes on to the chassis and drill. Also drill or punch holes in the box sides for the heater, h.t. and other leads. One flange is cut to clear the r.f. valveholder.

The box, with switch, is assembled complete before bolting it to the chassis. The mixer stage

Resistors:

R1	33kΩ 1W	R9	1 MΩ 1/2W	} See text
R2	220Ω 1/2W	R10	220kΩ 1/2W	
R3	47kΩ 1/2W	R11	3.3kΩ 1/2W	
R4	33kΩ 1W	R12	1 MΩ 1/2W	
R5	33kΩ 1W	R13	470kΩ 1/2W	
R6	68Ω 1/2W	R14	270Ω 1W	
R7	33kΩ 1/2W	R15	150Ω 1W	
R8	220kΩ 1/2W	R16	150Ω 1W	
	VR1	500kΩ log pot with switch		

Capacitors:

C1	0.1μF 350V	} Padders: Band Value	
C2	0.1μF 150V		
C3	100pF silver mica		
C4	200pF silver mica		
C5	0.1μF 350V		
C6	0.04μF 150V		1 110pF
C7	0.1μF 150V		2 270pF
C8	33pF silver mica		3 1000pF
C9	200pF silver mica		4 3000pF
C10	100pF silver mica		5 3900pF
C11	0.01μF 150V		silver mica
C12	50μF 25V		
C13	0.01μF 350V or mica		
C14	0.01μF 350V		Trimmers TC: Built on coils
C15	25μF 25V		VC1/VC2 2 sections of 3-gang Jackson JB/4507 /10/320, 320pF
C16	32μF 450V		
C17	16μF 450V		

Coils:

Band	Aerial circuit	Mixer grid	Oscillator
	Coilmax:	Stabcoil:	Stabcoil:
1	MZ8	MX8	OS8
2	MZ9	MX9	OS9
3	MZ10	MX10	OS10
4	MZ11	MX11	OS11
5	MZ12	MX12	OS12

(Electroniques)

1FT1 S3D/6/460

1FT2 S3D/1/460 (Electroniques)

Switch (to include R.F.)

Four TSW6/2/S six-way all unused shorting wafers
TSW/SH/5/2 mechanism

Studding (6BA rod) (Electroniques)

Eddystone No. 898 drive. Flexible coupler

Aluminium case 15 x 9 x 8in. Type W (H. L. Smith & Co. Ltd.)

L1 P3141 120mA 5H smoothing choke (Electroniques)

T1 45:1 60mA speaker transformer

T2 P2931 250/0/250V 150mA, 6.3V 1A, 6.3V 4A (Electroniques)

Chassis 8 x 13 x 2 1/2in. Pair 4 x 4 in. Type C brackets (H. L. Smith & Co. Ltd.) Coil box, "Universal Chassis" 6 x 5 x 2in. with two extra 6 x 2in. sides (Home Radio, Mitcham)

V1 ECH81 V4 6BW6

V2 6BA6 V5 EZ81

V3 6AT6

Two B7G holders with cans

Three B9A holders, one 2 1/2in. can

PLH2 bracket bulbholder and 6-8V 0.15A bulb (Home Radio, Mitcham)

E895 7/8 x 7/8in. black round knobs (Home Radio, Mitcham)

KN38 black pointer knobs (Home Radio, Mitcham)
250mA fuse and holder, tagstrips, etc.

valveholder is wired before the box is fitted, as described, flying leads being left for heater and anode circuits.

Later, when all wiring is finished in the box, take a scrap piece of transparent sheet about 6 × 5in. and place it on the box. Put a dot with paint or ink directly over the centre of each coil core and trimmer, place the sheet on the 6 × 5in. aluminium plate, mark through at the dots, and punch or drill fifteen 1/16in. holes. The plate is fixed to the box flanges with self-tapping screws. Drill these holes in the plate first, mark through on to the runner flanges, then drill these to take the screws.

The 50pF trimmer occupies a 1/8in. diameter hole, with a washer each side, this allows a little freedom to line up the shaft with the panel bush.

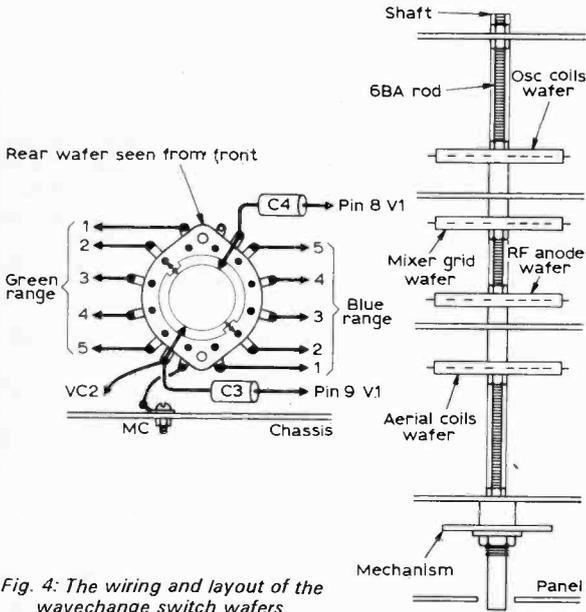


Fig. 4: The wiring and layout of the wavechange switch wafers.

Switch Assembly

The switch mechanism has a stop plate which can be loosened and this is set so that there are five positions; each wafer has two poles, six ways, one way being unused. Each wafer has shorting contacts included, so that all coils not in circuit are shorted to chassis, the sixth tag of each set is earthed to the chassis for this purpose. Since the shorting contacts are common to both poles of a wafer, two separate wafers are necessary to isolate h.t. positive and earthed circuits in the mixer grid position, the h.t. positive wafer is *not* earthed to chassis.

Place the wafers so that contacts come as in Fig. 4, for each wafer, when viewed from the front. If there is any doubt about working, check for continuity with a meter for each position. Errors should in any case be avoided if the receiver is tested with coils for one band only, other coils afterwards being added systematically.

The switch mechanism, 6 × 2in. runners, and switch wafers are all secured together by two lengths of 6BA screwed rod, with extra nuts, washers or spacers, as required. A fibre or spring washer is placed against the wafers, and nuts holding them should not be overtightened. Those switch contacts which will lie near the underside of the chassis cannot be reached when the box is fixed, so solder on leads which can join those to pass through chassis holes to the ganged tuning capacitor. Also solder on leads for the three wavebands where the contacts will be near the chassis, and for the tags which short all unused coils to the chassis.

The box is then arranged on the chassis, with leads passing through and is bolted. The ganged capacitor, mixer, oscillator and aerial circuits can then be wired. When this has been done, replace the oscillator and mixer grid coils for one band. Place the switch in the correct position, and check that proper results are obtained.

Coil and switch connections can be more readily checked if a different coloured wire, or sleeving, is employed for each band. For example, blue for

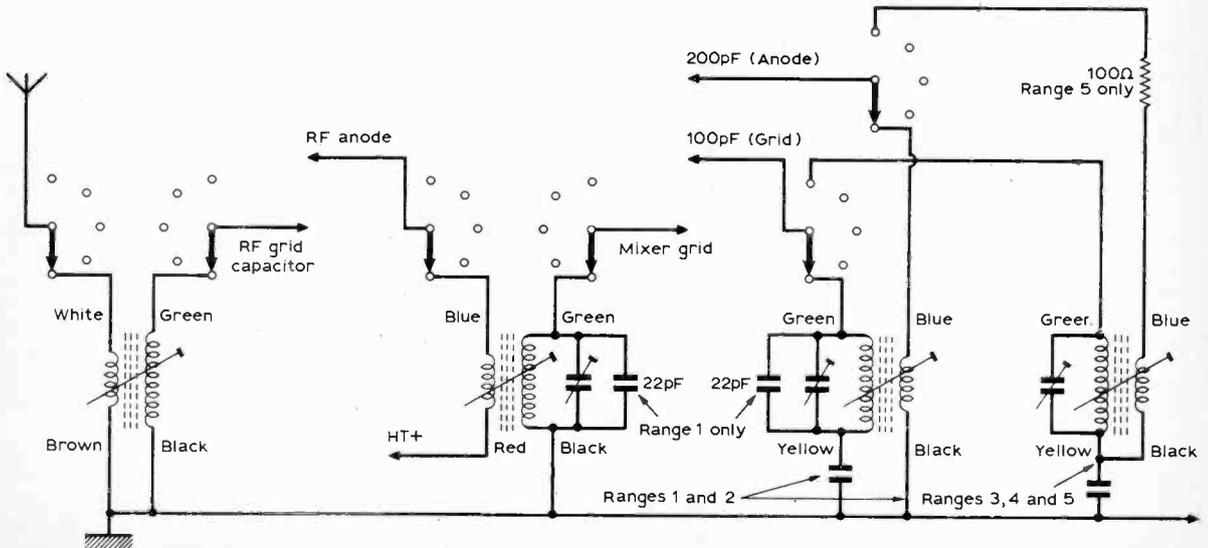


Fig. 5: The skeleton circuit of the r.f. and oscillator coils. Note the wiring differences in the oscillator section between ranges 1 and 2 and 3, 4 and 5.

all long wave coil leads from switch to coils, yellow for all medium wave leads, and so on.

Coil Wiring

Note that for long and medium bands (ranges 1 and 2) the oscillator feedback windings go to the chassis, but with ranges 3, 4 and 5, these are joined to the tuned windings and padders. Mixer grid and oscillator coils are placed so that the cores can be reached from above with the correct tool. These coils have small trimmers already fixed and these are reached through the holes in the 6×5 in. plate, as described. (The aerial coils have no trimmers, the cores are reached through the cover plate holes.)

It is best to wire m.w. coils (range 2) first, followed by l.w. (range 1), then ranges 3, 4 and 5, in that order. Range 4 and 5 coils are immediately adjacent to the switch wafers, so if wired first the switch tags are not easily reached for other bands.

Leads from the ganged capacitor rotor contact tags are connected directly to two tags bolted to the chassis. These bolts also secure tags under the chassis which are used as earth return connecting points for the h.f. coils. These leads need to be short and those in the switch and grid circuits are also short and away from earthed items, if not, the upper frequency limit may not be reached on band 5.



The completed receiver with the loudspeaker mounted on top.

The specified l.w. padder is 110pF, but correct alignment was found possible with either 100pF or 120pF. Note that the oscillator and mixer l.w. coils each have a 22pF or similar fixed capacitor in parallel with the trimmer. These are necessary, for the h.f. end of this band falls near the receiver i.f. of 460kc/s.

The band 5 oscillator coil has a 100Ω resistor in series with the feedback winding. It is wise to mark the range numbers on the coil box plate for later identification when aligning. Test the receiver on each waveband, when the coils for it have been connected to the switch, Fig. 5 shows the coil circuitry.

Next Month: Aligning the receiver and adding the R.F. Stage, the extra I.F., the S-Meter and the B.F.O.

THE MW COLUMN

THE North American path opened up late in November after a period of unsettled reception during the autumn. Conditions were outstanding during the early hours of 1st December. WOAI (1200) San Antonio, Texas, was clear and steady at 0240hrs GMT, WLS (890) Chicago was weak while KMOX (1120) St. Louis was fair at 0300hrs. Tentative loggings were made of WLW (700) amid strong QRM and of KOMA (1520) Oklahoma City behind WKBW. Conditions were still good in mid-December (the time of writing). Among the better loggings during this period were WGN (720) Chicago; tentative; WSB (750) Atlanta, Georgia; WJR (760) Detroit, "The Great Voice of the Great Lakes"; WGY (810) Schenectady, N.Y.; WCFL (1000) Chicago; CFRB (1010) Toronto; KDKA (1020) Pittsburgh; CKBL (1250) Matane, Quebec. Stations heard consistently at good strength were CBN (640); WNBC (660); WABC (770); WCBS (880); WINS (1010); CBA (1070); WBAL (1090); WKBW (1520); WQXR (1560). Two US stations have changed their call-signs recently. WAVY (1350) is now WCVU while WZOK (1320) has changed to WVOJ.

Other North American and Caribbean loggings were Godhavn, Greenland (650); CMGN (720) *Radio Rebelde*, Cuba; *Radio Belize* (830) British Honduras; ZBM-1 (1235) Bermuda; WBMJ (1190) San Juan, Puerto Rico, in English; WMDD (1480) also in San Juan, in Spanish. Little of note was heard from South America, probably because of the predominance of signals from the north. The only loggings were SRS (725) Surinam and HJDK(750) Medellin, Colombia, relaying the Caracol programme.

Local radio is well established in Spain, every main town possesses at least one low power commercial station. There are four major networks operating groups of stations under the callsign prefixes EFE, EFJ, EAJ, ECS, CES. There are also a number of high power regional stations run by the Government (RNE). The commercial stations—there are about 150 of them scattered across the country—can be a source of interesting DX to the newcomer to the MW band. Stations to look for are: EA17 (800) *Radio Madrid*; EAJ5 (809) *R. Seville*; EAJ1 (827) *R. Barcelona*; EAJ101 (872) *R. Zaragoza*; EAJ8 (1025) *R. San Sebastian*; EFE14 (1097) *La Voz de Madrid*; EAJ3 (1259) *R. Valencia*; ECS1 (1385) *R. Centro*; EAJ28 (1412) *R. Bilbao*. The shared channels—1133, 1394, 1412, 1475 are interesting after midnight when stations close down in succession, generally with full identification. Some rare catches can sometimes be made under these conditions.

Youthful reader Alan Mercer of Wigan, Lancashire sends in a log of recent DX which includes WINS, WBAL, CBA and KMOX. Well done, Alan, welcome to MW DXing. Alan, aged 12, is probably our youngest medium wave enthusiast. Can anyone claim to be the oldest? It would be interesting to hear from someone with experience of MW DXing in the early days of radio. **CHARLES MOLLOY**

repairing radio sets

PART 3 (Third Series)

REPAIRING THE UNKNOWN SET

WE are faced with the unknown set and a damaged transformer. The next question is: 'What do we use to replace it?' And it is no use quoting matching formulae to us, for the shop down the road sells us a multi-ratio job designed to match anything to anything else. Which ratio to use?


First, we need to know the loudspeaker impedance. This will normally be about one-third to a half more than the measured d.c. resistance. Remember that impedance is an arbitrary figure, varying with frequency, and normally taken at 800 to 1,000 Cs. Our task is made considerably easier by the habit of manufacturers to keep within the brackets of 3, 7.5 and 15 ohms. Next, we need to know the output impedance of the valve. Recourse to valve tables is the correct way, but, of course, we have left the valve tables behind, so we need to remember a few popular values and relate our experiments to these. The table below gives anode impedances, anode currents and voltages of some common valves, with the transformer load impedances and ratios for 3 and 15 ohm loudspeaker speech coil matching. Remember that the higher the anode impedance, the more exact the match should be, but to make this less critical, and improve matters all round, some negative feedback can always be added.

Valve type	Va.	Ia.	Ra. Load	Turns Ratio	
				3Ω	15Ω
ECL80	200	17.5mA	11k	60:1	28:1
ECL82	250	28	9k	55:1	25:1
ECL83	200	27	7.5k	50:1	22:1
ECL86	250	36	7k	48:1	22:1
EL34	250	100	2k	22:1	10:1
EL84	250	48	4.5k	38:1	18:1
EL95	250	24	8k	62:1	22:1
ELL80	250	24	10k	58:1	25:1
UCL82	200	35	5.6k	42:1	20:1
UCL83	170	30	5.5k	42:1	20:1
UL41	200	45	4.3k	38:1	18:1
UL84	200	60	2.4k	30:1	15:1

Turns ratio = $\sqrt{Z_1/Z_2}$ where Z_1 = anode impedance and Z_2 = loudspeaker impedance

Commonly used output valves giving typical working conditions and output transformer ratios.

Two small practical points: the output transformer is an electro-magnetic device and can contribute greatly to your hum problems unless you (a) mount it in the same plane and with the same axis as the old one, and (b) make sure the clamp has a good earth contact and is tight. Second point: in accordance with Henry's First Law, as I once heard it described, "the fixing holes of the new component will never line up". Do not be tempted to mount it precariously with a single screw; neither, I implore you, drill holes in the loudspeaker casting for a new fit. (In accordance with the Second Law, "the swarf will always descend to the least accessible place".)

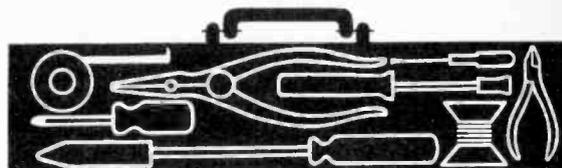

H. W. Hellyer

The correct method is to cut a piece of metal long enough to encompass the transformer base or mounting bracket, whichever is the greater, then drill this so that it can be mounted on the speaker, with the new transformer screwed to it and thus taking up approximately the same position as the old. This is to assume that the transformer is mounted, as so often, on the speaker casting. If it is on the main chassis, all that is needed is a new fixing hole.

TRANSISTORISED OUTPUTS

Test procedures around the output stages, and throughout the audio section of the set, have been adequately covered in previous articles. But before leaving the subject, it is perhaps wise to insert a warning again about transistorised output stages. Except on the higher quality audio amplifiers, protection circuits will not be fitted—they are too expensive. The loudspeaker then, if it fails, needs replacing with one of exactly similar impedance unless one is prepared to alter the circuit to suit the new one. Quite a few of the earlier "little-uns" had transformer output stages, and speakers will usually be 3-8 ohms and matching is not quite so critical. But with many transformerless output stages, the impedance of the transformer is a vital part of the current balance of the stage, and reducing it from the 25 ohms or more that was often used will result in transistors over-running.

For the same reason, the adding of an extension loudspeaker by paralleling with the old one is not a feasible proposition. As we have already seen, it is fairly common practice to fit an earphone socket which will usually isolate the internal speaker. If we know the impedance, or can work it out, then an external loudspeaker will almost invariably improve matters.


On the subject of protection, some readers have asked about the simple matter of fusing the common line of the output stage, especially of the transformer type of circuit, usually Class B. This is in order as long as it is remembered that even a fuse has resistance and signal currents cause a varying current to flow through it, which can upset the bias if we are not careful. The answer is to tap off the bias equalising resistor from the "inner" end of the fuse, that is the negative voltage end. This resistor, which limits the base-emitter current, is vital for prevention of crossover distortion—a prevalent fault with these circuits.

Output transistors, especially in these push-pull circuits of older design, tend to run hot. They should

be adequately heat-sinked (if that term may be excused), but there may still be some doubt about the ambient temperature. One particular car radio had a high incidence of output transistor failure simply because it was a convenient size to mount under dashboards and in glove compartments where there was not adequate ventilation or where the airstream from the heater did an unnecessarily good job in warming up the back of the set.

For added heat dissipation in unavoidable locations, a coin taped to the collector casing can sometimes make all the difference. Before halfpennies get out of date completely, you might consider this additional use for them—they won't buy much, so may as well earn their keep.

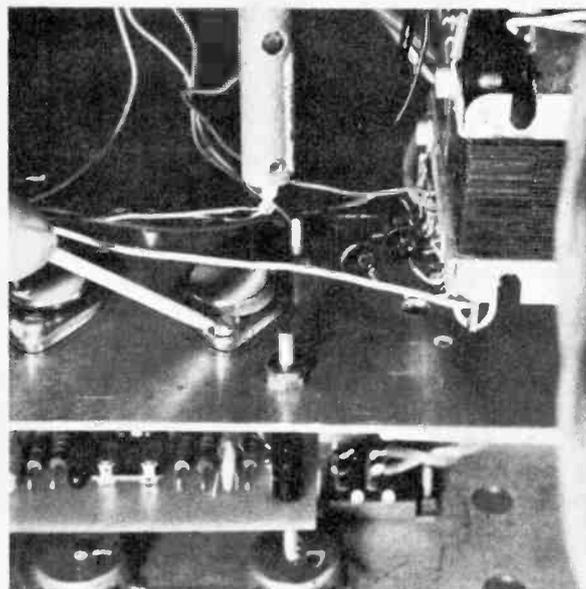
Again, the insulator between collector (i.e. transistor casing), and chassis has to be a good heat conductor; this is imperative. Mica is often used, or some form of plastic that is fine enough to



Good heat conductivity is essential for power output transistors. Check that fixing screws are correctly insulated from chassis by sleeves and washers when remounting. Outer case is the collector.

afford good heat conduction yet still able to act as an insulator. It is rather easy to damage—or even lose when the transistor is removed from its mounting. If no mica is available—and this material has a habit of being generously abundant when not needed—then a piece of thin varnished cambric, such as is used for transformer protection, may do the job quite well, and is easily cut to shape. When fitting this, and also when fitting the mica after handling, make sure the surfaces are clean, and smear a thin layer of silicon grease over the heat-sink, this helps heat conduction enormously.

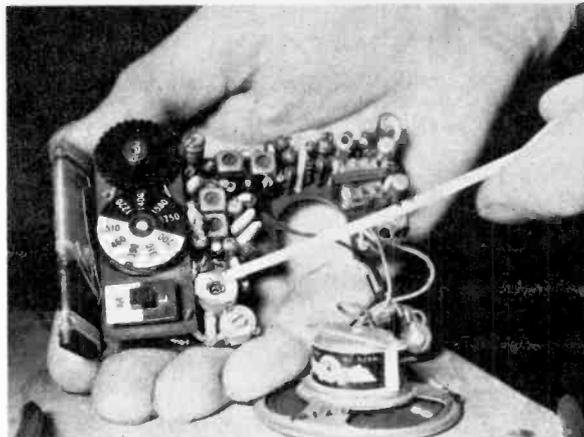Of the i.f. and frequency-changer sections of the receiver, little remains to be said. The problem when tackling an unknown set is to identify which is which! Layout of a transistor radio seldom follows any given pattern, being a matter of production convenience, and valved sets are more and more turning to unit panel designs. So the best bet is to trace



Oscillator coils can usually be identified by different construction, mounting or colour coding. Note in this picture the use of a simple slide switch of the type described in the text.

from the tuning capacitor, remembering that the oscillator coil is likely to be identified by a colour spot and will have a switch connection, whereas the i.f. transformers will be interstage units whose connections can generally be traced directly to the succeeding transistor.

Aerial circuits and the practical aspects of both rod and external aerials have been treated pretty fully and should need no further remarks from me. From the practical point of view, one has only to identify the coils of the rod aerial, remembering that the more turns the higher the wavelength (lower frequency), then patiently trace through the switch circuits, there are no real short-cuts. But on the contrary, much time can be lost if one omits to make a rough sketch of connections, colour codes, layout, and so on when removing multi-connection components. I speak with feeling, having had to rebuild many pieces of equipment thus butchered.

TRANSISTOR SUBSTITUTES

Unlike valves, whose equivalences are well documented, transistors fall into less neatly defined categories. There are several substitute lists, hedged about with provisos, but as is the way of life, the particular transistor we wish to replace will never be mentioned (Third Law?). Our correspondence shows that readers get a bit worried about the Japanese and American types with strings of apparently meaningless numbers as their only identification.

First thing to determine is what the function of the transistor may be, and whether it is an n-p-n or p-n-p device. The stage of the receiver gives us the first clue and voltages will tell us the second fact. All the popular bases have been given in previous articles and wall charts, and the collector and base connections will be identifiable. If the collector is negative to the base, the transistor is p-n-p, and if positive to the base, n-p-n.

Next, we need to know something about ratings. Maximum collector-base voltage is one of the limiting factors, and the circuit voltages will give us a clue. Most designers keep well within this rating, and our replacement needs to have a V_{CB} greater than the measured voltage. Collector current must also be great enough to be safe, and this is not so easy to determine if—taking the gloomiest view—

the transistor we wish to replace is not conducting at all to give us a clue. The collector voltage will then, of course, be equal to the rail voltage. The collector load is our next clue. If we work out what current through this load would drop the collector volts to about two-thirds of the rail voltage, this again should give us a clue.

TRANSISTOR RATINGS

Total dissipation is the next factor, and here we are limited to common sense. Obviously, we are not going to try an a.f. driver with a P_{tot} of 50mW in place of a silicon planar device with a 300mW rating, or an output type of 6 watts power dissipation. Again, intelligent assessment of the stage of the receiver will be needed.

For radio frequency types, the f_T rating will also be important, and again we need to know what the circuit is expected to do. Luckily for us, most of the germanium alloy-diffused types are quite generously rated, and mixer-oscillators for a.m. receivers with an f_T figure of 75Mc/s are well within specification for our substitution. Even those designed for i.f. amplification will have an f_T of 30Mc/s or more. But for f.m. oscillators, we need to be more careful. The important thing to remember is that lead length at these higher frequencies plays its part and our replacement may tend to be unstable. If so, reduce the value of the emitter bias. Often, this will be derived from a pair across the voltage line, and in this case, the upper resistor should be changed. The emitter feedback capacitor may also need changing to suit our new transistor. This is a matter for trial.

Likewise, the i.f. transistors are substituted in f.m. receivers, the upper resistor of the emitter bias network may be increased to reduce bias, but this reduction should not be to less than half of the value first noted. If instability persists, check the neutralising capacitor (not always fitted on later receivers), and experiment with values near the original. As a final expedient, damp the i.f. coil with a resistor across it; value again a subject for experiment.

FAILURE TO OSCILLATE

With a.m. mixer stages, the usual trouble is a reluctance to oscillate. This may indicate we need a little more emitter current, and a compromise between no oscillation and squegging will have to be reached. If there is no leeway, and squegging persists, reduce the emitter decoupling capacitor or even, in desperation, damp the oscillator tuned circuit with a resistor.


It may seem a retrograde step to fit a neutralising capacitor where a designer has managed to do without it, but we are plunging into the unknown and are forced to "suck it and see". Gordon King has dealt with these components, and there is no need for me to draw out details of the circuitry. A value of between 1 to 10pF should do the trick. More than this will indicate we need try another transistor. But before admitting defeat, try the transformer damping trick also, especially with i.f. stages.

CORD DRIVE SYSTEMS

Finally, a purely practical point. In the fourth article of the original series, way back in April 1967,



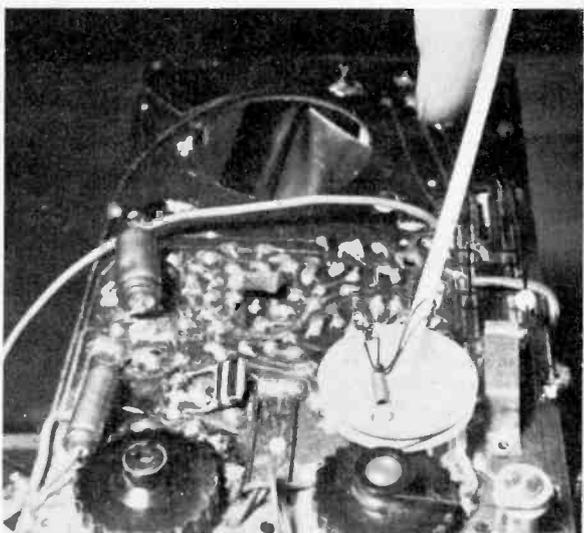A quick test for noisy components is a squirt of freezer from an aerosol.




Even the simplest of drive cords can be troublesome if spring tension is lost or the wrong relationship of drum to spindle prevents sufficient cord 'wrap' to turn the drum at the end of its travel. Note that in this view, the slide switch has been removed to show printed circuit connections (right of P.C. board).

I gave as much advice as I could muster about the fitting and adjustment of drive cords, and included a few typical diagrams. Correspondence shows that readers are often faced with the problem of restringing a drive cord with no clue at all as to its run or the desired number of turns around spindles and drums. To help matters somewhat, I include a few typical drive cord systems, drawn in the flat dimension to show cord run and spindle and drum turns. From these, it should be possible to work out a clue, even if the exact type is not depicted.

Indeed, that has been the purpose of this whole series of articles, and I am sure my colleague Gordon King will join with me in expressing the hope that they have proved helpful in solving some of the ticklish problems of radio repair, both theoretical and practical. ■

SOLDER ON WITH

A N T E X

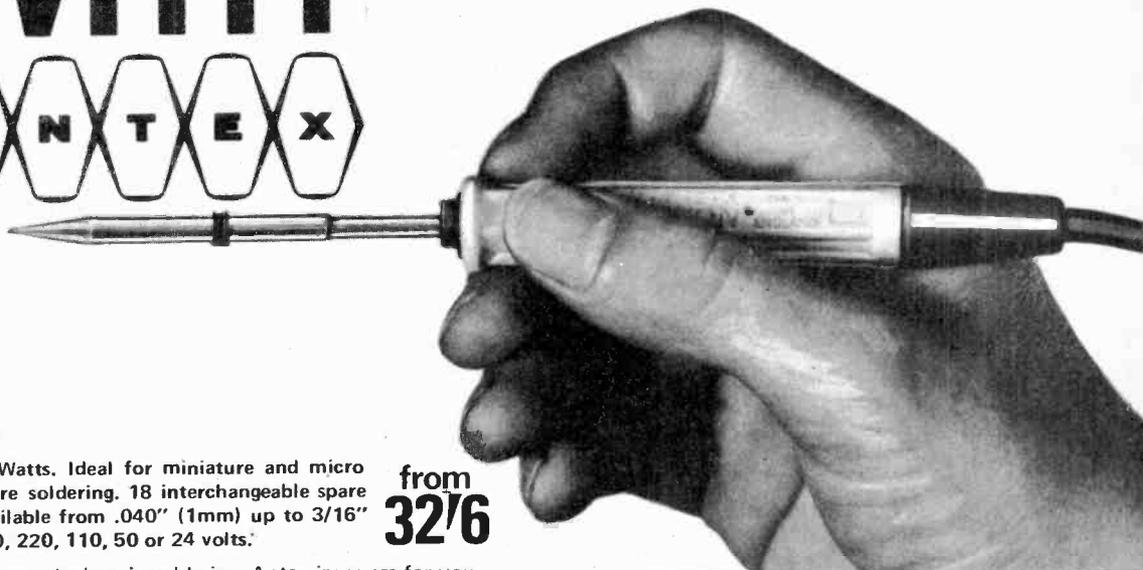

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 32/6**

If you want the best in soldering, Antex irons are for you. Pin point precision, fingertip control, interchangeable bits that slide over the elements and do not stick, sharp heat at the tip, reliable elements and full availability of spares. World-wide users, both enthusiasts and professionals solder with Antex. It's time you joined them.

Antex soldering irons are stocked by quality electrical dealers, or order direct from Antex by sending Cash. A free colour catalogue will be supplied on request.

A N T E X

PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon
Telephone : Plymouth 67377/8. Telex 45296. Giro No.258 1000



Model CN 240/2
15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

31/-

Complete precision soldering kit



This kit—in a rigid plastic "tool-box" — contains everything you need for precision soldering.

- Model CN 15 watts miniature iron, fitted 3/32" bit.
- Interchangeable spare bits: 3/32", 1/8", 3/16", 1/4".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron
- Space for storage of lead and plug

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

From Electrical and Radio Shops or send cash to Antex. **49/6**



G 18 watts. Ideal for miniature work on production lines. Interchangeable spare bits, 3/32", 1/8", 3/16", and 1/4". For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits: 3/32", 1/8", 3/16". For 240, 220, 110 or 24 volts. from 35/-



ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4". Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. from 35/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" Very high temperature iron. Available for 240, 220, 110, 24 or 20 volts. from 42/6. Spare bits and elements for all models and voltages immediately available from stock.

- Please send me the Antex colour catalogue
 Please send me the following irons

Quantity	Model	Bit Size	Volts	Price
.....
.....
.....

To: Antex, Mayflower House, Plymouth, Devon

I enclose cheque/P.O./cash value
NAME
ADDRESS
PW 3 Telephone:

BENTLEY ACoustIC CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT ROAD, LONDON, N.W.1

Telephone Primrose 9090

ALL GOODS LISTED BELOW, ACTUALLY IN STOCK, ALL GOODS ARE NEW, BEST QUALITY MANUFACTURE ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS AND REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

OBA2 5/9	6CL6 8/6	12A6 3/6	58KU 14/6	DL75 30/-	EF86 6/-	LZ319 6/6	R11 19/6	VT301 3/-	ASy28 10/-	OA70 3/-
OB2 6/9	6CW4 12/6	12AC6 7/6	72 6/6	DL92 4/9	EF89 4/9	R12 6/9	VU11 7/6	VU11 7/6	BA116 2/6	OA79 1/8
OZ4 4/3	6D3 7/6	12AD6 6/6	77 4/6	DL94 5/6	EF91 3/3	MHD4 8/3	R16 34/11	VU120 12/-	BA129 2/6	OA81 1/8
IA3 4/6	6D6 3/6	12AE6 7/6	78 6/6	DL96 7/6	EF92 2/6	MHL4 12/6	R17 17/6	VU120A12/-	BA130 2/6	OA85 1/8
IA5 5/6	6E5 7/6	12AT6 4/6	85A2 6/6	DL810 6/6	GF94 5/6	MHL16 7/6	R18 9/6	VU133 7/6	BA130 2/6	OA85 1/8
IA7GT 7/6	6F1 8/9	12AT7 3/9	90AG 67/6	DM70 6/6	GF95 4/6	MU12/14 4/6	R19 8/6	W42 10/6	BCY10 5/6	OA86 4/6
IC1 7/9	6F6G 4/6	12AU6 4/9	90AV 67/6	DM71 7/6	GF96 4/6	N12/14 4/6	R20 8/6	W61M 24/6	BCY12 5/6	OA90 2/6
IC2 7/9	6F6M 12/6	12AU7 4/9	90CC 34/-	DW4/350 8/6	GF97 10/6	N78 38/4	R21 9/6	W65 10/6	BCY33 5/6	OA91 1/8
IC3 7/9	6F12 3/6	12AV6 5/6	90CV 33/6	DW4/500 8/6	GF98 10/6	N108 26/7	SP13C 12/6	W76 5/6	BCY34 4/6	OA92 1/8
IC5 4/9	6F13 3/6	12AV7 4/6	90C1 16/-	DY86 8/6	GF99 10/6	N152 7/3	SP42 12/6	W77 2/6	BCY38 5/6	OA200 1/8
LD5 6/6	6F14 15/-	12AX7 4/6	150B2 14/6	DY87 7/6	GF99 10/6	N339 25/-	SP61 3/6	W81M 6/6	BCY39 4/6	OA202 2/6
LD6 9/6	6F15 9/6	12AY7 9/9	150C2 5/9	DY87 7/6	GF99 10/6	N359 7/3	TD14 8/3	W101 26/2	BCZ11 3/6	OA210 9/6
LD9 3/9	6F17 12/6	12BA6 6/6	161 15/-	DY87 7/6	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI07 4/6	OA211 12/6
LD10 3/9	6F18 7/6	12BE6 5/9	185BT 35/-	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI08 3/6	OA22012/-
LD11 3/9	6F19 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI09 4/3	OA2201 7/6
LD12 3/9	6F20 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI10 3/6	OA2201 7/6
LD13 3/9	6F21 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI11 3/6	OA2201 7/6
LD14 3/9	6F22 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI12 3/6	OA2201 7/6
LD15 3/9	6F23 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI13 3/6	OA2201 7/6
LD16 3/9	6F24 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI14 3/6	OA2201 7/6
LD17 3/9	6F25 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI15 3/6	OA2201 7/6
LD18 3/9	6F26 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI16 3/6	OA2201 7/6
LD19 3/9	6F27 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI17 3/6	OA2201 7/6
LD20 3/9	6F28 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI18 3/6	OA2201 7/6
LD21 3/9	6F29 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI19 3/6	OA2201 7/6
LD22 3/9	6F30 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI20 3/6	OA2201 7/6
LD23 3/9	6F31 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI21 3/6	OA2201 7/6
LD24 3/9	6F32 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI22 3/6	OA2201 7/6
LD25 3/9	6F33 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI23 3/6	OA2201 7/6
LD26 3/9	6F34 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI24 3/6	OA2201 7/6
LD27 3/9	6F35 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI25 3/6	OA2201 7/6
LD28 3/9	6F36 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI26 3/6	OA2201 7/6
LD29 3/9	6F37 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI27 3/6	OA2201 7/6
LD30 3/9	6F38 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI28 3/6	OA2201 7/6
LD31 3/9	6F39 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI29 3/6	OA2201 7/6
LD32 3/9	6F40 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI30 3/6	OA2201 7/6
LD33 3/9	6F41 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI31 3/6	OA2201 7/6
LD34 3/9	6F42 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI32 3/6	OA2201 7/6
LD35 3/9	6F43 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI33 3/6	OA2201 7/6
LD36 3/9	6F44 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI34 3/6	OA2201 7/6
LD37 3/9	6F45 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI35 3/6	OA2201 7/6
LD38 3/9	6F46 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI36 3/6	OA2201 7/6
LD39 3/9	6F47 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI37 3/6	OA2201 7/6
LD40 3/9	6F48 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI38 3/6	OA2201 7/6
LD41 3/9	6F49 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI39 3/6	OA2201 7/6
LD42 3/9	6F50 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI40 3/6	OA2201 7/6
LD43 3/9	6F51 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI41 3/6	OA2201 7/6
LD44 3/9	6F52 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI42 3/6	OA2201 7/6
LD45 3/9	6F53 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI43 3/6	OA2201 7/6
LD46 3/9	6F54 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI44 3/6	OA2201 7/6
LD47 3/9	6F55 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI45 3/6	OA2201 7/6
LD48 3/9	6F56 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI46 3/6	OA2201 7/6
LD49 3/9	6F57 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI47 3/6	OA2201 7/6
LD50 3/9	6F58 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI48 3/6	OA2201 7/6
LD51 3/9	6F59 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI49 3/6	OA2201 7/6
LD52 3/9	6F60 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI50 3/6	OA2201 7/6
LD53 3/9	6F61 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI51 3/6	OA2201 7/6
LD54 3/9	6F62 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI52 3/6	OA2201 7/6
LD55 3/9	6F63 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI53 3/6	OA2201 7/6
LD56 3/9	6F64 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI54 3/6	OA2201 7/6
LD57 3/9	6F65 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI55 3/6	OA2201 7/6
LD58 3/9	6F66 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI56 3/6	OA2201 7/6
LD59 3/9	6F67 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI57 3/6	OA2201 7/6
LD60 3/9	6F68 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI58 3/6	OA2201 7/6
LD61 3/9	6F69 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI59 3/6	OA2201 7/6
LD62 3/9	6F70 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI60 3/6	OA2201 7/6
LD63 3/9	6F71 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI61 3/6	OA2201 7/6
LD64 3/9	6F72 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI62 3/6	OA2201 7/6
LD65 3/9	6F73 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI63 3/6	OA2201 7/6
LD66 3/9	6F74 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI64 3/6	OA2201 7/6
LD67 3/9	6F75 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI65 3/6	OA2201 7/6
LD68 3/9	6F76 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI66 3/6	OA2201 7/6
LD69 3/9	6F77 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI67 3/6	OA2201 7/6
LD70 3/9	6F78 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI68 3/6	OA2201 7/6
LD71 3/9	6F79 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI69 3/6	OA2201 7/6
LD72 3/9	6F80 12/6	12BH7 6/6	301 20/6	E80F 24/-	GF99 10/6	N359 7/3	TD14 8/3	W107 7/6	BCI70 3/6	OA2201 7/6
LD73 3/9										

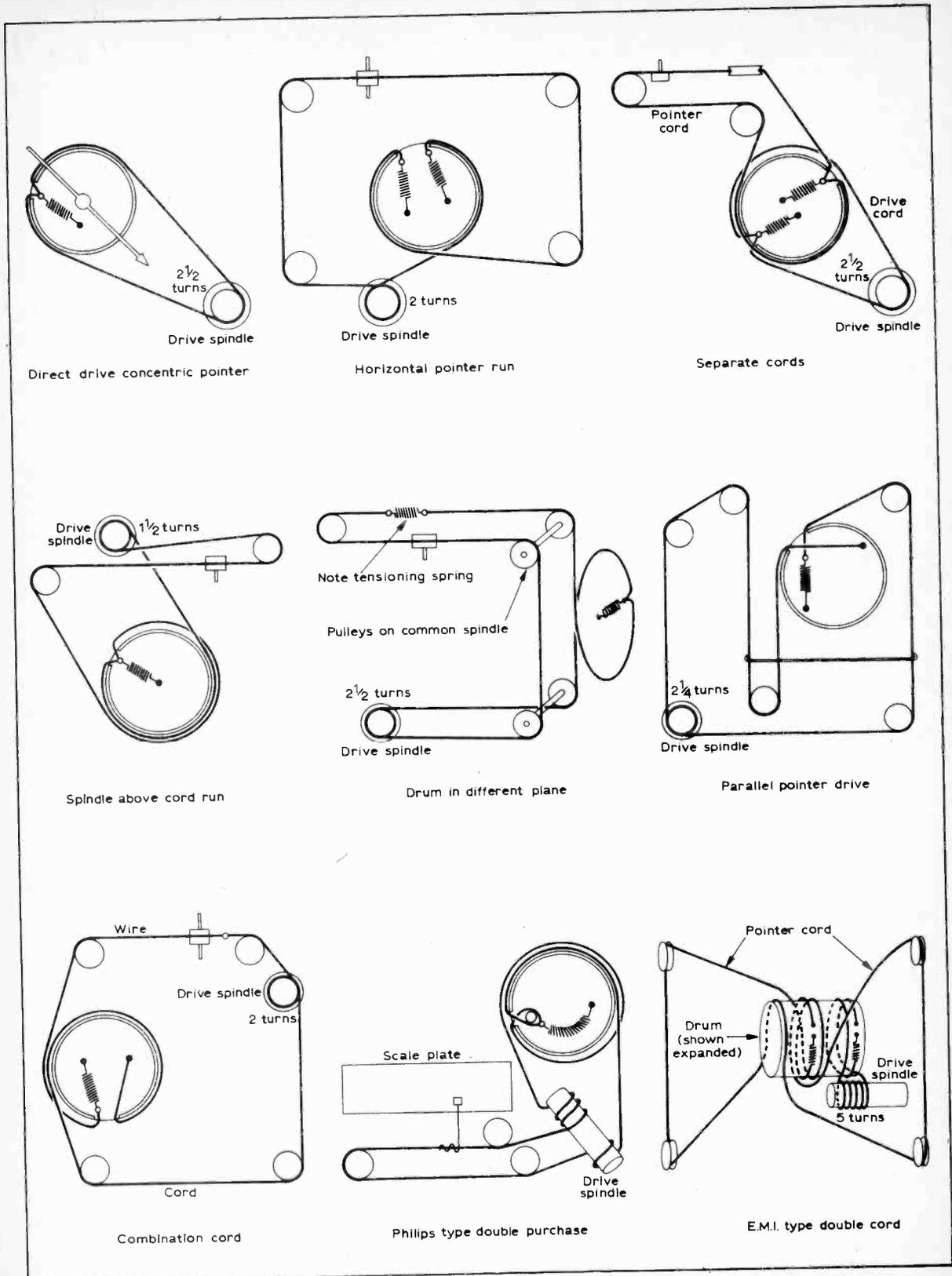


Fig. 11: Collection of cord drive systems from popular receivers, old and new. Note the importance of correct number of turns around spindles, drums, etc., and relative direction of cord run to main gang.

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times GMT
Frequencies in kc/s

THE BROADCAST BANDS by CHRISTOPHER DANPURE

WITH the winter now coming to an end and spring around the corner this is the time of the year to hear stations in the Pacific area and Far East in the mornings and afternoons. But now here are this month's propagation conditions.

West Africa: 0800-1400 25, 21, 17 and 15Mc/s; 1400-1600 25, 21, 17, 15 and 11Mc/s; 1600-1800 25, 21, 17, 15, 11 and 9Mc/s; 1800-2000 21, 17, 15, 11, 9, 7, 6 and 5Mc/s; 2000-2200 17, 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 2200-2400 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 2400-0400 11, 9, 7, 6, 5, 4 and 3Mc/s; 0400-0600 9, 7, 6, 5, 4 and 3Mc/s; 0600-0800 15, 11, 9 and 7Mc/s.

South Africa: 0800-1400 25, 21 and 17Mc/s; 1400-1600 25, 21, 17 and 15Mc/s; 1600-1800 25, 21, 17, 15 and 11Mc/s; 1800-2000 17, 15, 11, 9, 7 and 6Mc/s; 2000-2200 15, 11, 9, 7, 6, 5 and 4Mc/s; 2200-0200 11, 9, 7, 6, 5 and 4Mc/s; 0200-0400 11, 9, 7, 6 and 5Mc/s; 0400-0600 11, 9 and 7Mc/s; 0600-0800 17 and 15Mc/s.

East Africa: 0800-1200 25, 21, 17 and 15Mc/s; 1200-1400 25, 21, 17, 15 and 11Mc/s; 1400-1600 25, 21, 17, 15, 11 and 9Mc/s; 1600-1800 21, 17, 15, 11, 9, 7 and 6Mc/s; 1800-2000 17, 15, 11, 9, 7 and 6Mc/s; 2000-2200 11, 9, 7, 6, 5 and 4Mc/s; 2200-0200 11, 9, 7, 6, 5 and 4Mc/s; 0200-0400 9, 7, 6 and 5Mc/s; 0400-0600 11 and 9Mc/s; 0600-0800 17, 15 and 11Mc/s.

South Asia: 0800-1200 25, 21, 17 and 15Mc/s; 1200-1300 25, 21, 17, 15, 11 and 9Mc/s; 1300-1400 21, 17, 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 1400-1600 17, 15, 11, 9, 7, 6, 5, 4, and 3Mc/s; 1600-1800 11, 9, 7, 6, 5, 4 and 3Mc/s; 1800-2000 11, 9, 7, 6, 5, 4 and 3Mc/s; 2000-2200 9, 7, 6, 5, 4 and 3Mc/s; 2200-2400 7, 6, 5, 4 and 3Mc/s; 2400-0200 7, 6, 5, 4 and 3Mc/s; 0200-0400 7 and 6Mc/s; 0400-0600 9Mc/s only; 0600-0800 17, 15 and 11Mc/s.

South East Asia: 0800-1000 25, 21 and 17Mc/s; 1000-1200 25, 21, 17 and 15Mc/s; 1200-1400 25, 21, 17, 15, 11 and 9Mc/s; 1400-1600 21, 17, 15, 11, 9, 7, 6, 5 and 4Mc/s; 1600-1800 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 1800-2000 11, 9, 7, 6, 5, 4 and 3Mc/s; 2000-2200 9, 7, 6, 5 and 4Mc/s; 2200-2400 9 and 7Mc/s; 2400-0600 circuit closed; 0600-0800 17 and 15Mc/s.

North East Asia: 0700-1000 21, 17 and 15Mc/s; 1000-1200 15 and 11Mc/s; 1200-1400 11 and 9Mc/s; 1400-2000 9Mc/s only; 2000-0600 circuit closed; 0600-0700 15Mc/s only.

Australia via Asia: 0700-1000 21Mc/s only; 1000-1200 17Mc/s only; 1200-1400 17, 15, 11Mc/s; 1400-1600 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 1600-1800 11, 9, 7, 6, 5, 4 and 3Mc/s; 1800-2000 9, 7 and 6Mc/s; 2000-0700 circuit closed.

West Coast South America (North of Chile): 1200-1800 25 and 21Mc/s; 1800-2000 21 and 17Mc/s; 2000-2400 15Mc/s only; 2400-0400 11 and 9Mc/s; 0400-1000 9Mc/s only.

Now on to this month's DX-tips, but first please note that on Sunday, 2nd March, most international stations will change over to spring/autumn schedules and information in this column will be liable to alteration on that date.

AUSTRALASIA

New Zealand: *Radio New Zealand* is now operating to the Pacific Isles from 1700-1945 on 11,780 and 9,520; 2000-0545 on 15,110; 0600-0800 daily on 11,780 and 9,540; 0800-0845 weekdays on 11,780 and 9,540; 0800-0845 Sundays on 11,780 only. To Australia from 2000-0545 on 17,770; 0900-1145 on 11,705 and 9,520. To the Antarctic on Sundays only from 0815-0845 on 9,520.

AFRICA

Ruanda: *R. Deutsche Welle* relay at Kingali is now operating as follows. To East Africa and Central Africa from 0300-0530 on 9,565; 1015-1045 Sundays only on 11,785; 1045-1145 daily on 11,785; 1415-1445 on 15,435; 1500-1730 on 9,735. To West Africa from 0545-0745 on 11,905; 1200-1400 and 1745-2015 on 17,765; 2030-2325 on 15,380.

EUROPE

Denmark: *Voice of Denmark*, Copenhagen, is now on the following schedule. 0730-0845 on 15,165; 1015-1030 Saturdays only on 9,520; 1030-1100 Saturdays and Sundays on 9,520; 1100-1145 Sundays only on 9,520; 1130-1315 on 15,165; 1330-1345 on 15,165; 1400-1515 on 15,165; 1730-1815 on 15,165; 1830-1945 on 15,165; 2100-2215 on 15,165; 0100-0215 on 9,520. English is broadcast for last 30 minutes on weekdays only 0730, 1200, 1400, 1830 and 0100. The 1015 and 1030 transmissions at weekends are all in English. On weekdays the last 30 minutes of the 2100 transmission is in Spanish.

MIDDLE EAST

Israel: *Kol Israel*, Jerusalem, is now operating as follows: 1530-1600 Russian, 1600-1630 in Yiddish, 1630-1700 in Persian, 1700-1730 Russian, 1730-1745 Hungarian, 1745-1800 Rumanian, 1800-1815 Ladino, 1815-1830 Mograbit, 1830-1900 Yiddish, 1900-1930 Hebrew, 1930-2000 in Russian, all on 9,725 and 9,009. 2015-2030 on 9,725 and 9,009; 2030-2045 on 9,725; and 2045-2100 on 9,725 and 9,009 in English; 2100-2130 in French; and 2145-2200 in Russian on 9,725 and 9,009.

Well that's about it for this time. Deadline this month is 10th February, so good DX-ing and 73s.

DRY JOINT TESTER

The most reliable way of testing for a dry joint is to measure the resistance between the component lead and the printed circuit board. Our kit for doing this comprises a large scale (3in.) moving coil meter, a variable resistance for adjusting zero setting, and a wiring diagram with instructions. The only additional items you will need are a battery, some wire, a pair of test rods. Price 19/6, postage and insurance 2/6.

MINIATURE WAFER SWITCHES

4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each, 38/- dozen, your assortment.

WATERPROOF HEATING ELEMENT
26 yards length 70W. Self-regulating temperature control. 10/- post free.

BLANKET SWITCH

Double pole with neon light on side so luminous in dark, ideal for dark room light or for use with waterproof element—new plastic case. 5/6 each. 3 heat model 7/6.


PHOTO-ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit. Laminated boards and chemicals. Latching relay. Infra-red sensitive Photocell and Hood, 2 transistors, cond., terminal block. Plastic case. Essential data, circuits and P.C. chassis plans of 10 photo-electric devices including auto. car parking light, modulated light alarm. Simple invisible ray switch—counter—stray light alarm—warning light, electronic alarm—project lamp stabiliser, etc. etc. Only 39/6, plus 2/- post and insurance.

PPS ELIMINATOR. Play your pocket radio from the mains! save 5s. Complete component kit comprises 4 resistors—main dropper resistances, smoothing condenser and instructions, only 6/6 plus 1/- post.


BECKASTAT

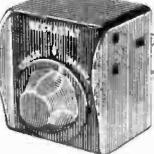This is an instant thermostat, simply plug your appliance into it and its lead into wall plug. Adjustable setting for normal air temperatures. 13A loading. Will save its cost in a season 19/6. Post and ins. 2/9.



KETTLE ELEMENT

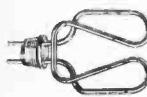230/240V 1500 watt. Made by Best for kettles with 7/16 in. dia. hole including: Best, Besco, Chalfont, Davidson, Dimplex, Grafton, Hawkins, Jurynaid, Mirroware, Monogram, Picco, Revvo, Town, Swan. Normally 32/6. Our price 15/- plus 2/6 post.



QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Best! Full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. 19/6, post and insurance 1/6. 12v. car model also available.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 35°-80° F. 8/6 plus 1/- Post. Suitable box for wall mounting. 5/-, P. & P. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-350°F. Internals screw alters the setting so this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven kiln immersion heaters or to make flame-start or fire alarm, 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point, 2/3 amps. Has many uses one of which would be to keep the 10ft. pipes from freezing, if a length of our blanket wire (16 yds. 10/-) is wound round the pipes. 7/6, P. & P. 1/-.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vials or tubes—thermostat is held (ball submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/-, plus 2/- post and insurance.


ELECTRIC CLOCK WITH 25 AMP. SWITCH

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



INFRA-RED HEATERS

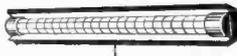Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instruction—uses silica enclosed elements (designed for the correct infra-red wavelength (3 microns). Price for 750 watts element, all parts, metal casing, as illustrated, 19/6, plus 4/- post and insurance. Pull switch 3/- extra.




DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything that and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 29/6, plus 2/6 post.



REPAIRABLE RADIOS

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in.—complete with soft leather zippered bag. Specification:—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kcs. Sensitivity: 5 mv/m. Intermediate frequency: 465 Kcs, or 455 Kcs. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. These radios are complete but require attention. Circuit diagram is not available. 17/6 each plus 2/9 post and insurance. 4 radios 63 post free.

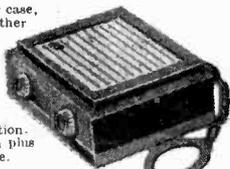

THIS MONTH'S SNIP


5A, 3 pin switch sockets

An excellent opportunity to make that bench board you have needed or to stock up for future jobs. This month we offer 6 British made (Hicraft) bakelite flush mounting shuttered 5A switch sockets for only 10/- plus 3/6 post and insurance. (20 boxes post free).



THERMOSTAT WITH PROBE

This has a sensor attached to a 15A switch by a 14in. length of flexible capillary tubing—control range is 20°F to 150°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddlington Co., we offer these at 12/6 each. Postage and insurance 2/9.

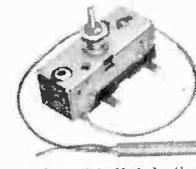

ELECTRIC CLOCK WITH 3A SWITCH

Electric Clock with 3 amp switch made by Smith's for Dreamland. These are mains driven and frequency controlled so are extremely accurate. The dial enables "switch-on" time to be accurately set. Switch off is 3 hours later. Also suitable for controlling switching electric blankets this needs only one setting for the season. Suitable also to control tape recorder, radio and lamp etc. up to 600W. In neat plastic case with mains lead and two outlet plugs. New and unused. 39/6, post and insurance 3/6.



FLUORESCENT LIGHTING SNIP THE TWENTYLITE



A 2ft. 20 watt lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. If left on all the time costs only one penny per day (uses 1 unit). Measures 2ft. long. Is ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer: 39/6 with tube. Assembled ready to install. Postage and Insurance 6/6 extra. Other "Atlas" fluorescent fittings with tubes 4ft. 40W 49/6 4ft. twin 40W 59/6 5ft. 80W 59/6 5ft. twin 80W 89/6 4ft. and 5ft fittings carriage 10/- on each sent at purchasers risk.

INDICATOR LAMP

Panel mounting, consists of neon lamp in red Plastic lens with resistor in leads for mains operation 2/8 each 24/- dozen.



12V BLOWER


Heavy duty motor with centrifugal blower coupled to one end. Ideal for car heater. 12/6, plus 4/6 post.

2 1/2 kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/4 kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit 23.15.0. Post and ins. 7/6.




SNIPSCOPE

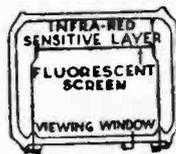

Famous war-time "cat's eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. A golden opportunity for some interesting experiments. 7/6 each, post 2/6. Data will be supplied with cells, if requested.

AC FAN

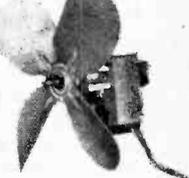Small but very powerful mains motor with 4 1/2in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips with wiring instructions. Suitable for normal fluorescent tubes or the new "Gloxux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—80 w. 19/6. Kit E—65 w. 19/6. Kit MF1 is for 6in., 9in., and 12in. miniature tubes, 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6.



Be first this year! SEED AND PLANT RAISING

Soil heating wire and transformer. Suitable for standard size garden fence. 19/6 Post and ins. 3/6.

BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching the blanket on for varying time periods thus giving a complete control from off to full heat. Also suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/6 each, we offer these while our stocks last at only 12/6 each.

16 RPM GEARED MOTOR

Made by Smith's Electrics, these are almost silent running, but are very powerful. They operate from normal to 240V. mains and the final shaft speed is 16 r.p.m. 15/-, Post & ins. 2/9.

REED SWITCH

Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass in coated switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- a dozen. Suitable magnets are 1/- each.

MINIATURE RELAY

American make—630 ohm coil 20-30 v. operation—2 pole change over 4/6 each, 48/- doz.



SPRING COIL LEADS

as fitted to telephones, 4 core 2/6 each, 3 core 2/- each.

ELECTRONICS (CROYDON) LTD
Dept PW 266 London Road, Croydon CR0-2TH
Also 102/3 Tamworth Road, Croydon

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

3/69

INTERNATIONAL CORRESPONDENCE SCHOOLS

Field-effect Transistors at Realistic Prices

2N 3819 N-channel. RF Amplifier. Low Noise.	10/- each (5 or more)	9/6 each
2N 3820 P-channel. Complement to 2N 3819.	17/6 each (5 or more)	16/3 each
2N 3823 N-channel. V.H.F. Amplifier.	33/6 each (5 or more)	28/6 each
BFW 10 N-channel. V.H.F. Amplifier.	45/- each (5 or more)	39/- each
MPF 102 N-channel. V.H.F. Amplifier.	8/- each (5 or more)	7/6 each
MPF 103 N-channel. AF Amplifier.	7/9 each (5 or more)	7/3 each
MPF 104 N-channel. AF Amplifier.	7/9 each (5 or more)	7/3 each
MPF 105 N-channel. AF Amplifier/Switch.	7/9 each (5 or more)	7/3 each
MFE 2094 N-channel. AF Amplifier/Switch.	31/6 each	

All of the above items are Ex-stock delivery at 31/8/68.

All components offered for sale are guaranteed to be brand new first grade items only. All items are subject to the guarantee terms of their individual manufacturer, where applicable.

M. R. CLIFFORD & COMPANY (PW) Component Stockholding Services 66, Old Oscott Lane, Great Barr, Birmingham, 22A.

Terms: C.W.O. MAIL ORDER ONLY. (Nett monthly a/c to approved accounts).
Suppliers to: Government and Educational Establishments, H.M. Forces, etc.
Please add 2/- postage and packing per order.


SILICON TRANSISTORS. EX-STOCK—many others available.

BC 107	3/6	BC 172	3/2	2N 697	5/-	2N 3704	3/8
BC 108	3/-	BC 173	3/9	2N 706	2/6	2N 3705	3/2
BC 109	3/6	BC 182L	4/-	2N 706A	3/2	2N 3706	3/7
BC 115	10/-	BC 183L	3/3	2N 2926	2/6	2N 3707	3/10
BC 116	12/-	BC 184L	4/9	2N 3053	6/-	2N 3708	2/6
BC 167	3/-	BFY 50	5/3	2N 3054	15/6	2N 3709	2/4
BC 168	2/6	BFY 51	4/4	2N 3055	21/-	2N 3710	2/7
BC 169	2/9	BFY 52	5/3	2N 3391A	7/-	2N 3711	3/-
BC 170	3/-	BFY 53	4/4	2N 3702	3/2	2N 3793	3/3
BC 171	3/8	BSY 95A	3/9	2N 3703	3/6	2N 4292	3/3

We are also an Electroniques Agency (960 page Catalogue 16/6 post free)

STRONGHOLD steel shelving that adjusts every inch of its height!

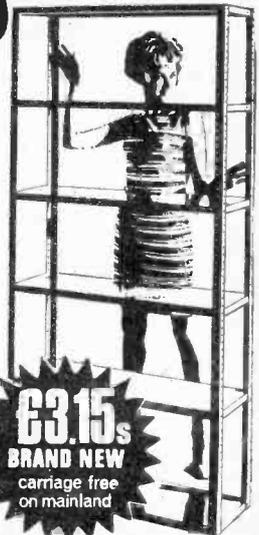Immensely strong—completely adjustable, every inch. Delivered free, mainland, with spanner provided for erection in minutes. Buy it by the bay! Cash with order
73" high x 34" wide x 12" deep unit with six shelves in heavy-gauge steel, stove enamelled grey or green!
£3.15s.—Brand New! See the rest of the N.C. Brown range!



£3.15s
BRAND NEW
carriage free
on mainland



N.C. BROWN LTD.

pacesetters in storage equipment

Send your FREE BROCHURE or Send (how many) bays of steel shelving @ £3.15s. in green grey (tick which)

Name.....

Address.....

Dept. PW Eagle Steelworks, Heywood, Lancs.
Tel: 69018. London: 25-27 Newton St., W.C.2.
Tel: 01-405 7931

MY thanks this month to the eighteen thousand s.w.l.s, ironmongers, watercress pickers and everyone who has written in to inform me that LG5LG is legit. Please fellas, I'm convinced.

Each year a new flock of people arrive at the s.w.l. door armed with various types of receivers and antennas. Judging by the many queries raised in the mail this month, the invasion is already in full swing. In answer to the commonest inquiries—you can obtain a list of countries and their prefixes from the RSGB at 35 Doughty Street, London W.C.1. There is no such thing as "the best aerial". The "best" receiver is a matter of opinion, although there are some very nice solid state marine receivers going these days—for around £800.

If you want the latest news on the Amateur scene with the accent entirely on Ham Radio, then you should listen out every Sunday morning when the RSGB transmit a bulletin especially for this purpose. These transmissions are on 80 metres and 2 metres. Exact frequencies and times are as follows: South-East England, listen at 0930 hrs. on 3.6 Mc/s or for the station in the S.E. beaming North on 145.1Mc/s at the same time; at 1000 hrs., a station in the Severn area on 3.6Mc/s and also on 145.1Mc/s beaming West. Also at 1000 hrs., there is a 2 metre station at Aberdeen beaming West on 145.8Mc/s; at 1030 hrs., on 3.6Mc/s the Midlands is covered while at the same hour, two stations on 2 metres are—Aberdeen, beaming South-West and Birmingham on 145.3Mc/s beaming North-West; for North-West England listen at 1100 hrs., on 3.6Mc/s or on 145.3Mc/s for a signal from the Birmingham area beaming South-West; at 1130 hrs. (they get up later up North), there is a 145.5Mc/s Leeds signal beaming North and a 3.6Mc/s transmission for South-West Scotland; finally, at 1200 hrs., a transmission for North-East Scotland on 3.6Mc/s and a 145.5Mc/s transmission from Leeds beaming East. Thus the whole of England is covered and you should be able to hear one of these signals. The call sign to listen for is GB2RS.

For those who haven't heard, they're mucking about with the call signs again. The PJ prefixes have been given a shuffle (Netherlands Antilles) so they now read: special stations—PJ1; Curaçao—PJ2; Aruba—PJ3; Bonaire—PJ4; St. Eustacius—PJ5; Saba—PJ16; Sint Maarten—PJ17. Visitors to islands with a PJ5, 6 or 7 prefix will use PJ8, while visitors to PJs 2, 3 and 4 will use PJ9. Wonder what prefixes will be given to those "novice licences" which the GPO were rumoured to be giving a ruling on last year? I suggest the prefix TV1 or BCI might be a sensible choice (even my transistor grid-dipper can flatten channel one right down the road if I'm not careful).

A very good month for all six bands although, as usual, some periods were better than others. Twenty metres dies the death at around 2100hrs., while 10 metres has been very good but with its now established temperamental nature. My two best on this band were ZD9BE and VQ9DH both between 0900 and 1100 using phased verticals in the loft.

What about all these DXpeditions these days. Amsterdam Island, Chatham Island, Kerguelen and

Tromelin were all rumoured to be waving antennas around but it seems that no one has heard an r.f. dickie bird from any of them, although a couple of PYØ stations were at it from Santa Barbara Island.

G. Taylor writes from S.W.6 and confesses envy at some of the logs printed. Some months I'm green too but that's just how it goes. Being able to read c.w. helps as often there's quite a bit of DX readable on key, while the phone signals are virtually impossible to interpret.

Messrs. **Littlefield** and **Sams** (Essex), query the call ZX3HX. Wonder if that might not be ZS misread?

John Moore (Leicester), tells of 80 metres opening up and 75 metres loaded with W and VE stations. John's log is a good illustration of persistence and keenness. You have to listen often and diligently and not just a quick QRX now and again expecting the DX to be there just waiting for the privilege of adorning your lugs.

John's log reads: 160 metres—E17AF, G16TK, GM3BQA, GW3SRG, OH5SM: 80 metres—K2AAS, K2MPK, LG5LG (I know, I know), OY2Z, PAØDX/M, W1EBC, W1SZJ/KP4, W3BMS, W4BUV, VE1AAW, VO1FG, ZB2A; 40 metres—EA8EC, IS1DMN/P, PX1BW (Andorra), ZC4MO, 9Y4TA; 20 metres—CE6EZ, ET3USA, HI3MPW, HP1HXG, K4PHY/YV5, LG5LG (nuff sed), OD5BU, OX5BA, PY7ACQ, TF3BV, VE3CBG, VO1HH, YV5AG, 5A3TE, 5Z4LG, 9K2AM, 9K2CF: 15 metres—EA6AR 9 (Majorca), JA2GES, KA2NY, MP4BGY, PY8YZ, TF2WLM, U1A (?), VE2AFC, VE3GHL, VK2FA, VK2XT, WØVXO/KV4, YA5RG, YN1URI, YV1WX, ZF1EP (Grand Cayman Is.); 10 metres—ET3USA, HV3SJ, KR6NR, KV4AD, OD5FA, PJØMM, PZ1BI, VE2DJR, VE3CVX, W1—WØ, YA1HD, YV1LA, YV5CPA, 9K2BJ, 9Q5DS. All the log on s.s.b. and with a CR100/2 plus 60ft. end fed.

L. Boucher (Near Swansea), has a virgin 1155 and 75ft. of wire. Twenty s.s.b. produced audibilities from—CE8CP, CN8CS, CR6LF, CT2AA, EA6AR, EA7ID, EA8FM, EP2DA, KL7EBK, MP4TCE, OD5FM, PY1TX, PY5AJ, PJØCC, PZ1DF, SVØDD, TA3AR, VE5BF, VK2AZ, VK4PX, VK6XW, W6HYG, W7KQ, YV5BFBK, ZB2A, ZB2BC, ZE6JM, ZL3LE, ZS1NU, ZS6OY, 3A2EE, 4X4HT, 5A3TX, 5A4TE, 7P8AR, 8P6CC, 9J2VX, 9K2AV, 9Y4VT.

R. Dinning (Ayrshire), HA350 and PR3OX, 380ft. long wire logged these on 10 metres s.s.b.—CR7FM, EP2JP, HR1JMS, HV3SJ, IS1GS, KP4AQX/KG6, KV4AD, LU6DRB, MP4BVX, VK6XX, YN1HSM, YN1GLB, 5A5TH, 9J2DT, 9K2CC, 9N1MM plus "... millions of JAs". Fifteen metres with the same set up raised—CT2AM, EL2BD, HR1JS, KG4AM, KG6ALY, KP4BCL, KR6JT, KV4FQ, KZ5WL, MP4MBB, OX3LP, TA3AR, VK2ADV, VK3SM, ZL1AJU.

Activities and happenings in February include: 15th—16th, topband contest; 16th, 4 metre fixed station contest: 22nd—23rd, YL/OM phone contest (see how many YLs you can log); March 1st—2nd, 2 metre contest.

DESIGNED for "Top Band" mobile working in conjunction with a 12V transistorised car radio receiver, this rugged solid-state Superverter has proved to be completely satisfactory. Consuming but 3.5mA of current the prototype is so quiet in operation that under no-signal conditions one wonders if in fact it is operating. Doubt on this point is rapidly eliminated, however, on receipt of a signal!

The Superverter is designed to accept signals in the 160m. Amateur Band (1800-2000kc/s), converting them to a new frequency—1.6Mc/s or thereabouts—so that they may be heard on the car radio, the tuning of which is adjusted to the high frequency end of the Medium waveband. The car radio then performs as a second amplifier. The output from the unit could alternatively be fed to other types of receiver capable of being tuned around 1.6Mc/s subject to a point being located on the scale where no spurious unwanted signals break through.

Power can be in the form of a small dry battery—and adequate space exists in which to incorporate



one—or the car battery may be used. Switchery for various operating modes will be included later.

Physical size is of importance in connection with items used for "mobile" usage and although dimensions associated with the prototype Superverter will be given these can be modified considerably to suit the needs of the individual.

The Superverter is not a "general coverage" design for the simplified tuning system adopted restricts frequency coverage to a few hundred kilocycles to provide a "one band" affair. Two bands could perhaps be catered for by introducing switching; an alternative method is to use plug-in coils. Plug-in coils—but rigidly located—are in fact embodied in the prototype Superverter and suggestions regarding other frequency bands will be given in a later article.

Although no 3-gang tuning capacitor is used the Superverter does employ an r.f. amplifier stage ahead of its mixer/oscillator stages. This is possible because the frequency bands available to radio amateurs are but 200kc/s or so wide overall and the phone section is considerably less. Top Band covers 1800-2000kc/s but few QSOs take place near the band edges.

The prototype Superverter cannot resolve single-sideband (s.s.b.) transmissions nor can c.w. be made intelligible since a b.f.o. is not fitted. The inclusion of a b.f.o. is not entirely a practical proposition, for

"on the move" operators usually find it difficult to adjust the control to the correct point. Fortunately, on "Top Band", a.m. is used mostly for daytime QSOs.

Since the required i.f. output is approximately 1600kc/s, local oscillations generated by the Superverter in the range 3400-3600kc/s will supply the necessary product. The purist may prefer to fully tune the three circuits simultaneously (this entails use of a 3-gang variable capacitor) but the practical-minded find it more convenient to preset tune the r.f. and mixer stages around mid-band position—say 1900kc/s—and to tune only the oscillator over the necessary 200kc/s segment. This is the method adopted, the oscillator being tuned from the panel by means of a reduction drive legended "Tune".

Circuitry

The complete circuit of the Superverter is shown in Fig. 1 where TR1 is the r.f. amplifier with TR2 the combination mixer/oscillator. The emitter-follower,

ONE-SIXTY A.S. CARPENTER G3TYJ SUPERVERTER

TR3, is included to isolate the i.f.t. secondary tuned winding from the associated receiver which is connected to socket SK2. Panel controls are associated with T1 (R.F. Trim), VCJ (Tune) and VR1 (R.F. Gain).

In order to strengthen signals receivable higher or lower in frequency than the 1900kc/s mid-band position the core of T1 is made adjustable from the panel. The safety diode D1 is only needed when a transmitter is being used nearby.

Plenty of decoupling is included and all values specified are as used in the prototype unit. The value of R11 is governed by the power supply to be used; a negative potential of 9V d.c. at TR3 collector is suitable and remembering that the unit requires about 3.5mA the value of R11 is easily calculated.

If improved selectivity and higher gain are desired TR3 can be used as an additional amplifier by adopting the final circuitry of Fig. 2 when an additional i.f. transformer (a Denco type IFT17) is required plus the other items as legended in the diagram.

Constructional

The prototype Superverter is made to stand on top of the car radio receiver with which it is used and is secured thereto firmly. All metalwork is of 18 s.w.g.

—continued on page 846

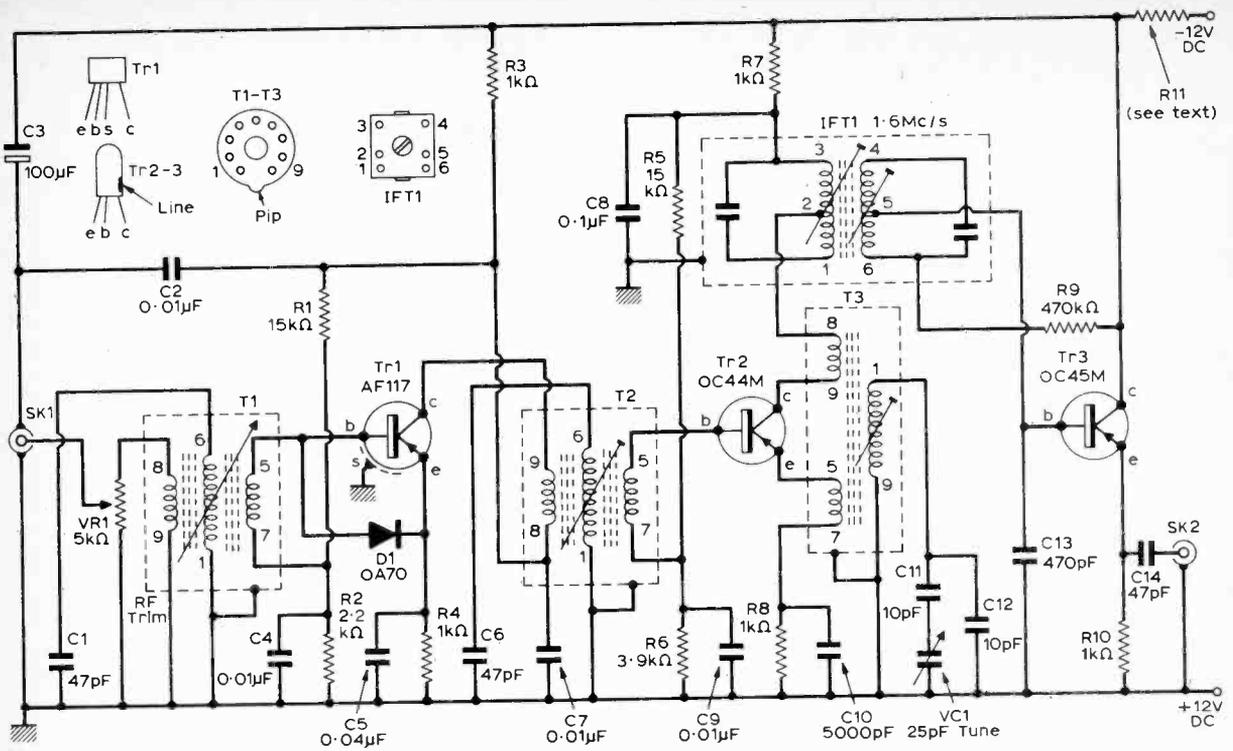


Fig. 1: The circuit of the Superverter.

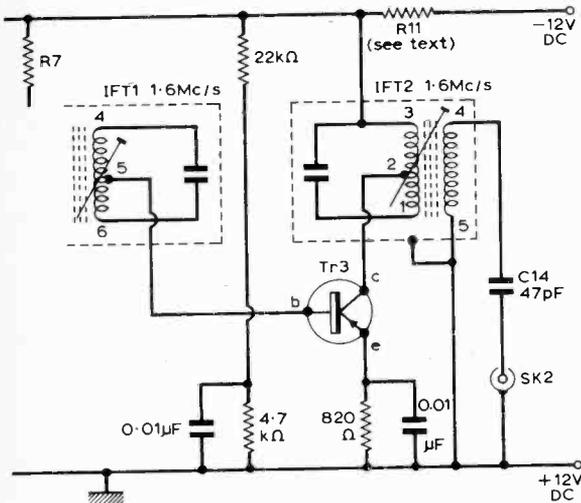


Fig. 2: An alternative output stage.

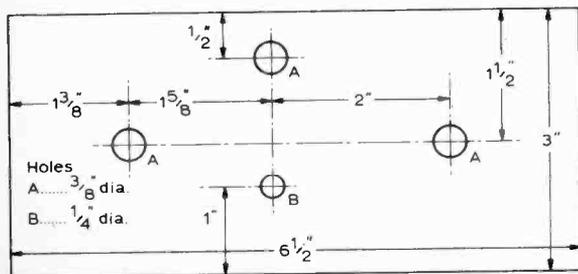


Fig. 3: Front panel dimensions.

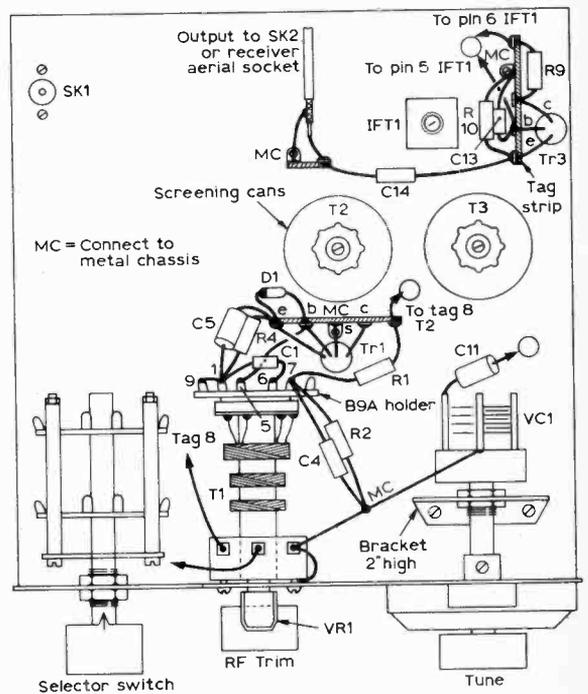


Fig. 4: Above-chassis layout and wiring details.

—continued from page 844

aluminium and front panel dimensions are given as a guide in Fig. 3. The top of chassis layout can be seen in Fig. 4 where the location of T1 should be noted, the coil being locked to the front panel with its brass core adjusting stem projecting and fitted with a brass bush to accommodate a small control knob. A Noval valve holder is then "push-on" fitted to the spills at its other end. All three coils are so designed that they may be plugged in to Noval valve holders and one holder is required for each. The selector switch shown will be mentioned later.

Essential dimensions of the main chassis are given in Fig. 5 which also shows the orientation of the two coil holders associated with T2 and T3. The screening cans associated with these two coils (these are the containers the coils come in) are not fitted initially. It should be noted that the chassis dimensions shown allow of no bends and front and back flanges should thus be added. The rear flange need be no more than $\frac{3}{8}$ in. deep. A simple L-shaped bracket is also made to carry VC1.

The i.f. transformer is simply fitted by cutting a square in the chassis to afford a firm fit for the screening can without distorting it. The i.f.t. can is then pushed through the chassis a short distance and its mounting lugs bent *outwards* to be soldered to tags suitably positioned. Three small tagstrips are located as shown and wiring up carried out along the lines indicated.

All items used must be of modern design and miniature in type. Coil T1 can also be mounted vertically if preferred when a small variable capacitor may be panel fitted for peaking purposes and connected across its tuned winding.

The Coils

Ready-made coils are used and for the oscillator coil T3 a Range 2 "White" specimen is selected from the Denco range of transistor types. The induc-

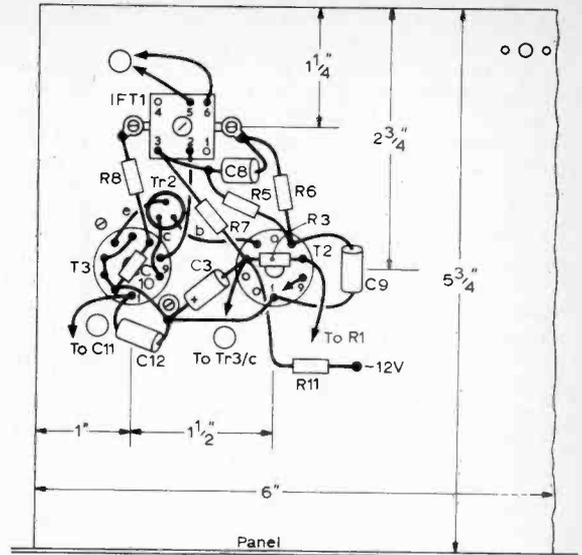


Fig. 5: Below chassis layout and wiring with dimensions.

tance of this coil is approximately $66\mu\text{H}$. At the mid-band position for an input r.f. signal of 1900kc/s the oscillator must be tuned to 3500kc/s for 1600kc/s output and a tuning capacitance of about 30pF is thus called for; components C11, C12 and VC1 are appropriate in value.

Denco Range 2 Aerial and Interstage coils (Blue and Yellow respectively) are also used for T1 and T2 but have to be modified since their inductance is too great. The coils are easily modified. A side view of the signal frequency coils is shown in Fig. 6, the aerial coupling winding being "A" plus a 2-pie tuned winding at "B" and "C". A transistor base coupling

★ components list

Resistors:

R1	15k Ω	R7	1k Ω
R2	2.2k Ω	R8	1k Ω
R3	1k Ω	R9	470k Ω
R4	1k Ω	R10	1k Ω
R5	15k Ω	R11	See text
R6	3.9k Ω	VR1	5k Ω pot.

All $\frac{1}{4}$ watt, 10%.

Capacitors:

C1	47pF ceramic	C9	10,000pF ceramic
C2	10,000pF ceramic	C10	5,000pF ceramic
C3	100 μF , 15V	C11	10pF ceramic
C4	10,000pF ceramic	C12	10pF ceramic
C5	0.04 μF paper	C13	470pF ceramic
C6	47pF ceramic	C14	47pF ceramic
C7	10,000pF ceramic	VC1	25pF trimmer
C8	0.1 μF		type Jackson
			Bros. C804

Semi-conductors:

TR1	AF117	TR3	OC45M
TR2	OC44M	D1	OA70

Coils:

- T1 Miniature Blue Transistor type Denco range 2
 - T2 Miniature Yellow Transistor type Denco range 2
 - T3 Miniature White Transistor type Denco range 2
- See text for above three coils.
- IFT1 Miniature transformer Denco type IFT18/1.6Mc/s.

Switch:

See text

Tuning Unit:

Vernier Drive, 2in.—Eagle T502

Miscellaneous:

Chassis and panel material 18 s.w.g. aluminium, Tagstrips (3), Noval valve holders (3), Control knobs (3), Coaxial sockets, etc.

Note: In cases of difficulty all items can be obtained from: Alpha Radio Supply Co., 103 Leeds Terrace, Wintoun Street, Leeds.

winding associated with spills 5 and 7 is not shown: this is wound on top of winding "B".

To modify the Blue and Yellow coils for 160m. band working the wire is cut free from spill No. 6 tag and turns are carefully removed from winding "C" without causing damage to connections running from winding "A" to spills No. 8 and 9. Turns are slowly removed until only one-quarter or slightly less of the winding remains when compared to winding "B". The loose end of the winding is then soldered to spill tag No. 6 after cutting off the wire freed. The precise number of turns left on the winding need not be known since the core is adjustable and affords compensation. It may be thought that the next coil "down" in the maker's range could be used unmodified and although this is true—using Range 3 Blue and Yellow coils—a large shunt capacitor is required across each tuned winding; the approximate capacitance value is 270pF. It should be noted that the Range 2 White oscillator coil specified for T3 must not be modified in any way!

The Yellow and White coils are each screened by means of the metal containers they are supplied in. These containers are cut off to a length of 1½ in. as is shown in Fig. 7a; a ¼ in. diameter hole is also cut as shown. The two coils are plugged in to their appropriate holders, the lock nuts removed and the containers inverted over them. The lock nuts are then screwed on thumb tight and a 6BA brass lock nut is screwed lightly on to each core stem. A length of

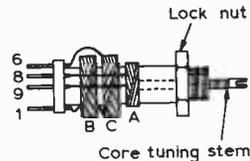


Fig. 6: Aerial and inter-stage coils.

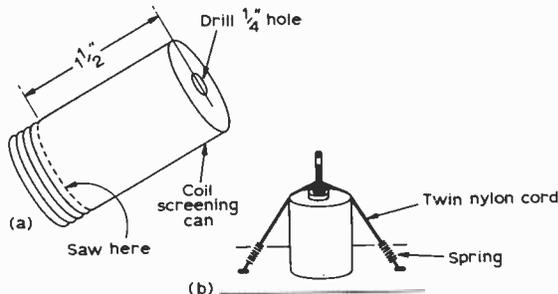


Fig. 7a: Screening can modifications; 7b: Mounting method

twin nylon cord attached to a pair of small springs of the type used for cord drives is used to hold each container firm under all mobile conditions. The coils can, however, be easily removed very quickly if this is required. The mounting method is shown in Fig 7b.

TO BE CONTINUED

YOUR QUESTIONS ANSWERED

Ripple Current

With reference to the higher voltage types of electrolytic capacitors and some obscurities that seem to exist. There seems to be no indication on the majority of them to indicate permissible ripple current. Is there any way by which this can be determined?—J. Wackett (Devon).

Details of the ripple-current rating of electrolytic capacitors can normally be obtained from the manufacturer concerned. A useful rule of thumb for determining whether or not the leakage current of a capacitor is excessive is: $\text{mA} = \text{V} \times \mu\text{F} / 2000$, in other words, the permissible leakage current in mA is taken as the product of the working voltage and the capacity in μF divided by 2000.

Speaker Damage

I have an all-transistor tuner/amplifier. Would any damage be done if it were switched on with all speakers disconnected? Also, would any damage occur if too many speakers were switched in?—H. Smith (Perth).

Loading of transistor amplifiers can be regarded as "roughly" the opposite of valved amplifiers in that they will usually suffer no damage by discon-

necting the loudspeaker/s, but short-circuiting of the output increases the current in the output stage dangerously. An inadvertent short-circuit of loudspeaker wiring has ruined many an output transistor, and there is generally no leeway—thus the utmost care is necessary. From this it follows that the addition of extra loudspeakers reducing the load impedance, also increases the output current. In fact, this is sometimes used to boost, artificially, the output from an amplifier. For example, where an amplifier is rated to deliver ten watts to a fifteen ohm speaker and actually delivers more like four watts (!) the device of connecting a well-rated 4Ω speaker gets more output with comparative distortion figures. But it is not to be recommended—for the reasons I have stated. If more speakers are needed, it is advisable to equalise the load. For example, a single speaker of nominal X ohms impedance can be replaced by four similar impedances in series parallel.

Volume Control

I should be grateful if you could give me some advice regarding the fitting of a tone control to my transistor set. The output is class B push-pull with one OC81D and two OC81s, transformerless with a 30Ω speaker.—G. Lawton (Herts).

You can probably alter the tone of your transistor radio by connecting an 8μF 6V or a 4μF 6V capacitor in series with a variable resistor, say, 5kΩ, and connecting this combination across the volume control. It might also be wired from the base of the driver transistor to the positive line. However, this must be a matter for your personal experiment.



PART 1 HOME WORKSH

IN order to construct radio and electronic apparatus, hand tools are required. The problem confronting the beginner to radio construction is to know which tools to buy initially and which tools may be left until more ambitious projects are undertaken. The purpose of this article is to outline a kit of tools which the author considers to be the minimum necessary for starting serious construction work; with these tools, additional tools can be made at home and details of these will be given in subsequent articles. Finally, more sophisticated tools will be mentioned.

In the main the raw materials are copper, aluminium and their alloys, and it is to cut, join, shape, pierce, measure and smooth these materials that tools will be required. The basic tools required by the beginner are: **Vice, clamps, hacksaw, chisel, tinsnips or shears, scissors, rule, punches, try-square, hammers, hand-drill complete with twist drills, spanners, screwdrivers, pliers and soldering iron.**

Unfortunately for the beginner, many of these tools can be obtained in a variety of forms and sizes, and the author will attempt, in the brief discussion of each item which follows, to indicate the type of tool most suited to the beginner in terms of value and versatility. Before leaving the subject of value, a word of warning here. No matter how limited the budget, on no account should *quantity* of tools be allowed to take precedence over *quality* of tools.

Good quality tools are actually easier to use than inferior tools, and have an immeasurably longer useful working life. The British market is flooded with inferior tools imported from Europe and the Far East, as experience is gained, these cheap tools can be made to work within their limitations but the beginner is strongly advised to start with good, branded British products.

Returning now to our list, we start with the vice. This is one of the most useful tools in the workshop and an engineer's vice with 3in. or 4in. interchangeable jaws is preferred. A possible drawback with this type is that it has to be bolted down through the workbench and where it is intended to use the

kitchen table as a makeshift workbench, a clamp-on portable vice makes a good substitute. A range of excellent aluminium alloy vices is currently available, and the constructor can make his own jaws to suit from scraps of wood, etc.

To augment the vice, a pair of "G" clamps are invaluable, although one will do for a start. In normal use, "G" clamps are subjected to severe tensional stresses, and cast-iron clamps should be avoided because these are very weak in tension. Good clamps are made of forged steel, and will withstand considerable abuse indefinitely. A 5in. clamp is a good size to start with.

The **hacksaw** should be of the adjustable type, ranging between 8in. and 12in. Imported hacksaws often have fixed adjustments corresponding to metric sizes and will not accept English blades unless modified.

A range of cold chisels is useful in the workshop but where it is intended to purchase only one, a 6in. chisel of about $\frac{1}{4}$ in. diameter will serve. More will be said about chisels later.

Metal-cutting **shears** or **tinsnips** are available in a range of sizes, with either flat jaws, straight or curved, or with plump jaws, invariably straight. This latter type is known as a *Goosebill* shear because of its shape. Both types have their uses, but the *Goosebill* is recommended for its ability to cut a straight line through sheet metal. A 10in. shear will cut 20 gauge aluminium without undue effort, and if it is necessary occasionally to cut heavier gauges, one handle of the shear can be gripped in the vice, whilst the other handle is *pumped* to obtain the required leverage.

A pair of **scissors** is included in the list to cover those occasions when aluminium foil, cardboard, fabric, fuse-wire, etc., need to be cut.

A six-foot extending **rule** is a useful accessory in the workshop and a cheaper type with printed graduations will be accurate enough for most marking out.

A steel **try-square** is included in the list, but if a combination square is obtained it will have a number

of additional features such as a removable rule with engraved graduation with which more accurate measurements can be made. Most squares of this type also incorporate a useful little scriber and a spirit level.

Punches for use in the workshop include centre punches, pin punches and piercing punches. One of the uses of the centre punch is to make a small conical indentation in a surface that is to be drilled, the small *pop* mark guides the drill accurately into the desired position. Centre punches do not vary much in size, but a punch of square section, or with an enlarged square head, is less likely to roll off the workbench. Pin punches are used to drive cotter pins and retaining pins and could probably be left out of the basic kit without too much inconvenience. On the other hand, the piercing punch is one of the most useful, but neglected, tools in the constructor's kit. Proprietary punches are quite expensive to buy, but fortunately satisfactory substitutes are not at all difficult to make, as will be described later. The

piercing punch is a round piece of tool-steel with a concave relief in the cutting end which is driven through the panel by a firm blow from the hammer, taking a small slug of metal with it, the panel is supported on a piece of softwood to prevent damage to the punch as it breaks through.

Holes can be produced more accurately and quickly with a punch than with a drill and, with careful planning and marking out, a complete radio chassis can be punched in the flat before the sides are raised into the box shape. Large holes are difficult to punch by this method, however, and for this reason a set of screw-up type chassis punches is specified. These are available as a set of the most popular sizes and full instructions are included.

Many workshops have a large selection of **hammers**, but for our purpose only two are considered to be essential. These are a perfectly standard one pound ball-pein, and a fibre, plastic or rubber hammer for sheet metalwork. The resilience of the latter hammers helps to prevent damage when soft metals are being worked.

The **hand-drill** should have well-fitted bearings, preferably including a proper thrust race, and an idler pinion to balance the crown wheel. A $\frac{1}{2}$ in. capacity chuck is usual, although a larger drill with a $\frac{3}{8}$ in. chuck has much to commend it.

A set of **twist drills** with the diameters increasing by increments of $\frac{1}{16}$ in. from say $\frac{3}{16}$ in. to $\frac{1}{2}$ in. should be obtained. Beware the very cheap imported sets often labelled "Hi-carbon" or similar, which are in fact made of iron wire and will not drill even hard wood satisfactorily. A good British set is indicated here, the extra cost is easily justified.

A set of **BA extension socket spanners** will be required right from the beginning, and is especially useful when dismantling scrap equipment to reclaim parts. Look for neatly broached sockets when purchasing, and a long clearance hole inside the shaft is useful when running nuts on to long screws. The type with an interchangeable plastic handle is convenient to use and takes up little space.

Screwdrivers are obtainable in sets especially pre-

pared for the radio worker. Make sure your set includes at least one of the Phillips type blade.

Of the many types of **pliers** available, three are preferred for a start, these are combination, side-cutting, and long-nosed. Insulated handles can be obtained if desired, although the author has a strict rule that metal tools will not be used in the vicinity of live power circuits. Cheap side-cutters rapidly become blunt and cannot be sharpened.

The last of the basic tools is the **soldering iron**, these are obtainable at prices ranging from 10s upwards, and wattages from about 25 upwards. The writer prefers a big, powerful, soldering iron, but the choice is rather a matter for the individual. The beginner might be well advised to start with a 30 watt iron and to consider others as dexterity is acquired. A solder gun should be the ultimate goal, of course. The elements of the cheaper irons usually burn out after a couple of hours, and are often irreplaceable. Other cheap irons have recently been found to be lethal owing to faulty insulation. A well-known

brand name is the best safeguard.

As the projects undertaken become more complex, the need for more tools will be felt, and these can be bought when necessary. Other tools might already be knocking around the house or garage such as files and oilcans.

SOURCES OF COMPONENTS

Armed with the kit of tools described the would-be constructor now requires components and materials with which to work. It is possible, of course, to purchase all that one requires, brand new, from the radio supplies shop, but the expense involved often imposes a serious limitation on the number of projects which can be undertaken. Often the necessary materials and components can be obtained free of charge or at a purely nominal cost.

The most prolific source of components is the scrap TV or radio chassis, any number of which can usually be obtained from the local radio and TV repair shop simply for the asking. More than once the writer has had the boot of his car filled with scrap chassis by the grateful proprietor of the local repair shop, who would otherwise have had to pay to have these removed. Old radios and radiograms can often be picked up for a couple of shillings at second-hand furniture stores or jumble sales.


Those fortunate enough to live near a war surplus shop will find that a few shillings will buy a complicated piece of apparatus which undoubtedly cost the Government hundreds of pounds when new. The writer particularly remembers buying an ex-W.D. valve-tester and having a large box of valves "thrown in to practice on".

Most electronic projects are built on a chassis of some sort or other. It is often found possible to utilise a chassis salvaged from an old set, but where this is not possible, a new chassis can either be purchased ready made up or fabricated by the constructor from sheet material. A cheap substitute used by the author is the oven meat tin obtainable from all chain stores. Unlike aluminium, components can be soldered directly on to the tin-plate chassis and

TOP PRACTICE BY P. HAMLEY

wiring, is greatly facilitated since earth leads can be kept short and direct by soldering to the chassis at the nearest point.

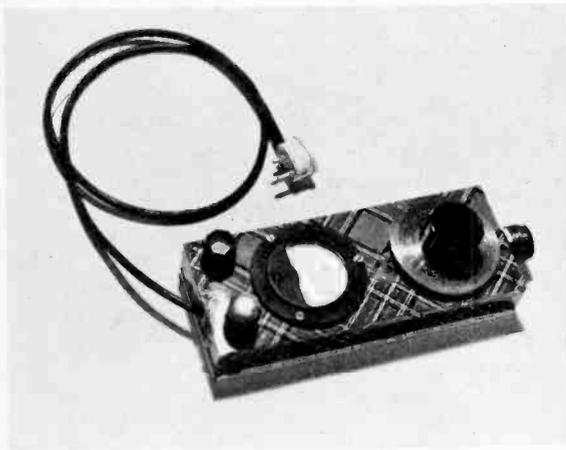Biscuit tins can sometimes be pressed into service, as the photo of the G.D.O. shows. Larger biscuit tins can be cut into panels which in turn are formed into small chassis as required. A slight disadvantage with ordinary tin-plate is that it lacks rigidity and special attention must be given to stiffening up tin-plate chassis.



The Authors' Grid Dip Oscillator built in a biscuit tin.

Inevitably the constructor will come across a design where a definite shape and size of chassis is called for. Here, a sheet of aluminium will be required for making up and most good radio shops will stock this. However, anyone living near a coach-builder or caravan building works should first try a visit to the works manager with a view to buying offcuts of aluminium at the scrap rate. The writer was able to buy 7lb. of 20 gauge aluminium in useful size sheets for a shilling from such a source. Before leaving the subject of chassis and chassis materials, consideration should be given to sandwich tins, tobacco and mustard tins and similar containers, the choice is limited only by the imagination of the constructor.


Having found the necessary components and built a chassis, the constructor will require wire to wire up the project. Single- and multi-stranded copper wire, PVC covered, can be purchased on small drums for a few shillings, but owing to political troubles in the copper producing areas of the world, copper is today rather an expensive commodity and economies can be made by using wire stripped from scrap sets. When insulation is needed, the wire can be threaded into rubber or plastic tubing, obtainable in bundles for a few pence; another very good sheath goes under the trade name of "Systaflex" and is a varnished cambric and it is somewhat easier to thread than rubber or plastic. For insulating fairly straight lengths of wire, an ordinary plastic drinking straw can be tried and will be found to possess a resistance of 500M Ω at quite high potentials. In the absence of heat or physical abrasion it will last for ever.

FINISHING IT OFF

Summarising our discussion so far, we have considered some methods by which components can be

obtained; assembled to a chassis; wired up; and tested under power. All that remains is to fit the project into a housing of some description. A wooden or plastic cabinet can be made or purchased, but the author's preference is to make a metal cover, the main reason being that the equipment is then screened to r.f. both ways. In the vast majority of cases, the equipment will consist of a chassis with components above and below deck, and a vertical front panel to which tuning and volume controls, inputs and outputs, meters and lamps etc. are attached, depending on the type of equipment.

An attractive cover for the remaining three sides and top of the equipment can be fabricated from expanded metal available in many anodised finishes from trade advertisers in this journal. However, the really dedicated improviser will find that perforated zinc, sold in rolls by most hardware shops, makes an excellent substitute for expanded metal at rather less than half the price. The zinc is extremely easy to cut and form into any shape, and is joined merely by pressing adjacent pieces together with a hot soldering iron. The accompanying photo of a home-made preamplifier shows one application of this material.

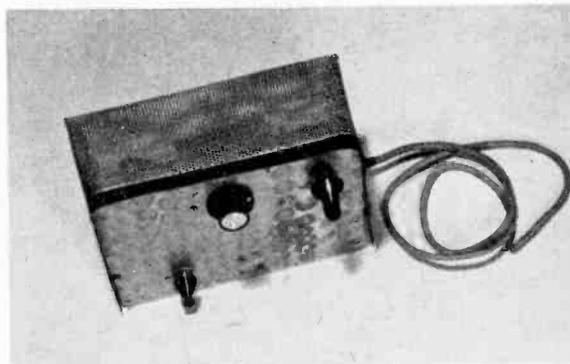

The cover of this pre-amp is made from perforated zinc. Note the finish on the front panel, made by rubbing with steel wool.


The edges of aluminium and similar sheets and panels can be bound quite attractively with plastic tape. Other possibilities include gilded plastic strip such as is sold for edging hardboard, etc., and possibly the simplest way is to file and smooth the edge and spray the panel. Decorative finishes can be applied to the natural metal in various ways—for instance a pad of steel wool rubbed firmly round and round in small adjacent circles on the surface produces an attractive finish. Another method of achieving a similar result is to attach a small piece of medium emery cloth to the end of a $\frac{1}{4}$ in. diameter wooden dowel and revolve the dowel between the hands, pressing the emery cloth lightly against the surface.

So much then for the ways and means of gathering together the raw materials for the constructional project. Next month special techniques for dismantling, reclaiming and rebuilding components and equipment will be described, and finally a list of more advanced hand and power tools for the guidance of those fortunate enough to have the space to provide themselves with a fully-equipped home workshop.

TO BE CONTINUED

FREE!

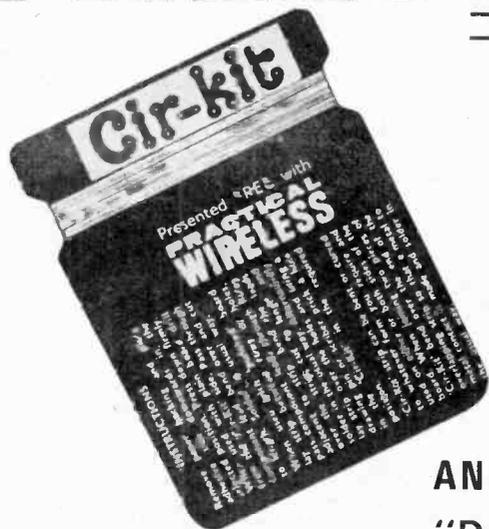CIR-KIT sample in next month's Practical Wireless



AND THESE SPECIAL FEATURES

"Double-12" Stereo Amplifier


A superb new hi-fi project for the home constructor. Impressive specification, with 12W r.m.s. per channel at below 0.1% distortion at 10W. To be described in three instalments, the Double-12 can be built as an integrated unit or as a preamp/control unit to drive an existing amplifier.

Relays

Although relays are nowadays often replaced by semiconductor devices, they still have plenty of useful applications, as this article will explain.


The "Mite"

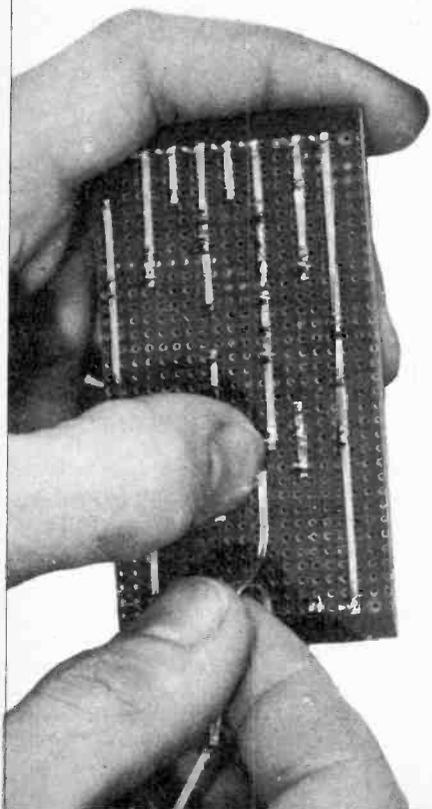Another P.W. design—a 3-transistor pocket radio receiver. Full constructional details of this useful little set which can operate a loudspeaker.



PRACTICAL WIRELESS

3/- ORDER YOUR COPY NOW!

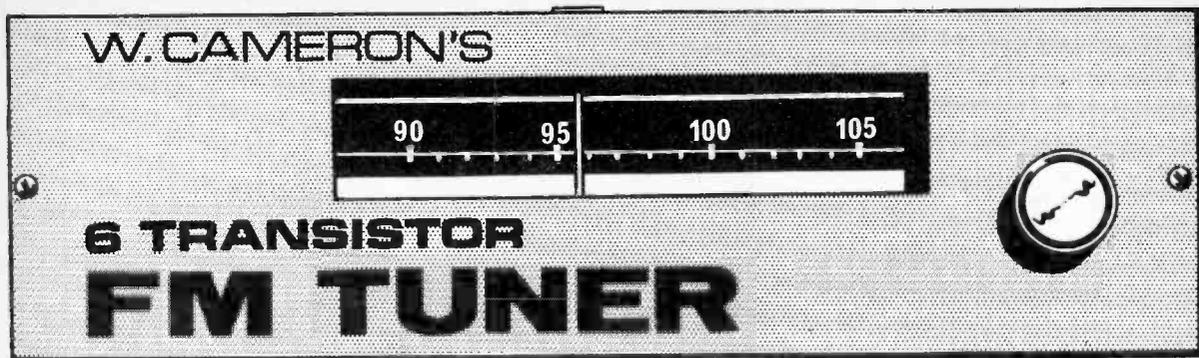

PART 2 — continued from February

Work may now proceed on the wiring and soldering of the small components (see underchassis layout details, Fig. 7). It is as well to start at the output end, TR6, working forward to the first i.f. TR3, up to the dotted line on the circuit diagram Fig. 1. The i.f. amplifier must now be checked and given the rough alignment described below, after which the front end can be completed.

Initial I.F. Alignment

The i.f. amplifier is now ready for testing and rough alignment. Plug the output into an amplifier and connect the supply leads to a 9 volt battery. Check all voltages with Table 1. Clicks should be heard during these tests, perhaps becoming progressively louder as the tests proceed towards the first i.f., particularly when collector and base voltages are measured. Any fault that may be apparent at this stage must obviously first be located and corrected before proceeding to the actual alignment. Disconnect the battery, disconnect capacitor C15 and connect a length of 3 or 4 yards of wire to the emitter of TR3. Re-connect the battery. The i.f. amplifier can now be considered as a rather wideband t.r.f. receiver, the length of wire connected to TR3 emitter being the aerial, and provided no fault exists short wave signals, mainly Morse, on a frequency somewhere between 10 and 11Mc/s will be clearly heard.

The nominal frequency to which the i.f. transformers should be tuned is 10.7Mc/s, but any frequency within the tuning range of the transformers (approx. 10-11-Mc/s) will do just as well. With a trimming tool and starting with the core of L11, adjust for maximum

output, progressively working forward adjusting each of the cores in turn for maximum, finishing with L6. Precise tuning does not matter at this stage, but it will help if one signal can be singled out and the adjustments made to bring out this one at maximum, disregarding others. The final adjustments to the i.f. come later, when the front end is completed and operating. Now re-connect C15.

For those with access to a signal generator, a 10.7-Mc/s signal is injected into the emitter of TR3 via a capacitor of 0.01 μ F, and the i.f.'s adjusted for maximum as above, the output from the signal generator being reduced to prevent overloading as the i.f.'s come into alignment. The discriminator can also be adjusted at this stage in the manner described next under "Tuning and Alignment". Use an unmodulated signal and meter the output as described in this method.

No mention will be made of wobblulator alignment as it is assumed that the limited number of constructors who might have access to one of these instruments will know how to use it.

The front end wiring should now be completed and voltages checked with Table 1.

Tuning and Alignment

Connect a shorting link of wire across C12 to cut the a.f.c. Connect a d.c. voltmeter, 2.5 volt scale to start with, across C27 and in the same polarity. Connect the aerial. The type of aerial will depend on location and distance from the transmitter, but a simple dipole mounted in the correct direction will be suitable in most cases. The author, who lives 20 miles from a transmitter, found a 2ft. 6in. length of wire to be sufficient, but this is not recommended. Adjust the tuning gang until a signal is received, when a reading will be seen on the voltmeter. Adjust all the i.f.t. cores in the order L11 to L6 for maximum reading on the meter, switching the meter to the next highest range if necessary. As a guide, the reading should finally be about 4V if the received signal is of reasonable strength.

With a signal being received, the discriminator is correctly tuned when the d.c. voltage from each diode of the ratio detector is equal and opposite with respect to chassis, or in other words, when the voltage across C27 is maximum and the voltage between the test point (junction of C26 and R22) and chassis is zero.

To tune the discriminator, transfer the meter (2.5V scale) to between T.P. and chassis. The reading will be

TABLE 1 — Transistor Voltages

Transistor	E	B	C
TR1	8	7.25	0
TR2	7.8	7.2	0
TR3	2.2	2.4	8.4
TR4	1.6	1.8	8.4
TR5	1	1.2	8.6
TR6	0.4	0.58	6.2

The total current is 11 mA. All voltages were measured with a 20k Ω /V meter.

either positive or negative depending on whether L11 is detuned higher or lower than the i.f. Adjust the core of L11 until the reading is zero, at the point where further adjustment of the core will swing the reading positive or negative depending on which way the core is turned. The i.f. alignment is now complete.

The r.f. and oscillator stages will now require some adjustment. The oscillator coil L4 is adjusted by squeezing the turns closer together, or by widening the spacing between the turns as required, to get the tuning gang and hence the scale pointer in the correct position. Squeezing the turns together will result in less tuning capacitance being required, and vice versa. The calibration will be approximately correct when Radio 2 (Light Programme) is received with the gang at about seven-eighths full capacity (plates almost fully in).

The r.f. coil is also adjusted by squeezing or widening, and is adjusted to give maximum on the meter connected across C27. A plastic trimming tool is useful for making these coil adjustments as it will have little self-effect on the tuning when touching the coils.

The coil L2 on the aerial coupling T1 may be tuned if necessary, by optimising the value of C1. Capacitors of between 12pF and 20pF should be tried, choosing the value which gives greatest reading on the meter.

Remove the shorting link from C12 to restore a.f.c.

The diode will be at its nominal capacitance when the d.c. voltage from the discriminator is zero. Any frequency drift would result in this voltage becoming either negative or positive depending on whether the drift was to the high or low frequency side of the received signal. The diode capacitance would then be either increased or reduced, maintaining the oscillator on a set frequency.

In this receiver where the oscillator is highly stable and frequency drift is unlikely, the main advantage of the a.f.c. is the easy and positive tuning it provides. When tuning, it will be noted that this is quite broad. Tuning through a signal will produce a "plop" when the a.f.c. locks onto the signal, and again when tuning through the signal and beyond the range of the a.f.c.

Scale and Drive

Two pulleys are fitted to the front panel with 4BA screws, and two nuts, one on each side of the panel, lock the screws while allowing the pulleys to run free. Approximately 30 inches of nylon drive cord are required for the drive, details of which were shown in Fig. 4.

The scale may simply be a strip of good quality paper marked appropriately where the BBC stations appear,

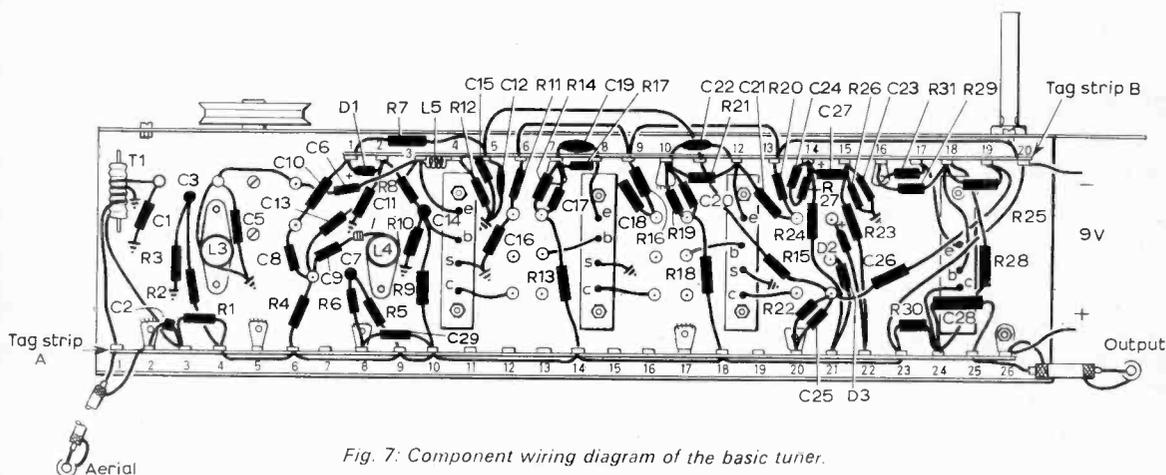


Fig. 7: Component wiring diagram of the basic tuner.

Automatic Frequency Control

The diode D1 is a special variable capacitance diode, type BA102. Other silicon diodes have been tried but without much success, except for the type BA100 which gave reasonable results.

The diode is biased by the fixed voltage provided by the potential divider R9-R10. The fact that this divider also supplies bias to TR3 is of no consequence as the junction is at chassis potential to r.f. via capacitor C14.

The a.f.c. control voltage is taken from the centre point of the discriminator via R7 and R15. The junction of these resistors is by-passed to a.f. by C12. Improved linearity at the expense of gain can be obtained by leaving out C12, when the audio component will swing the oscillator in opposition to the received f.m. signal, giving in effect negative feedback, but more correctly volume compression.

The diode, in series with C10 and C11, is across L4 and in parallel with the tuning capacitor C4b.

or else calibrated in frequency. On the model, the scale is a strip of black plastic tape, lettered with Radiospares white marking transfers.

A second front panel of 1/4 in. Perspex is fitted over the scale, using countersunk 4BA screws and distance pieces to clear the pointer drive and drum. The back of the Perspex is painted, or preferably, sprayed, using a flat paint or aerosol primer. A 1 in. wide strip of masking tape or Sellotape is placed in the scale position before painting, and when removed provides the scale window. If a case is to be fitted over the unit, the Perspex should be the same size as the aluminium front panel, but if the tuner is to be installed in a cabinet, the Perspex should be made larger than the cabinet aperture to facilitate fixing.

Power Supplies

A 9 volt dry battery is very suitable for supplying

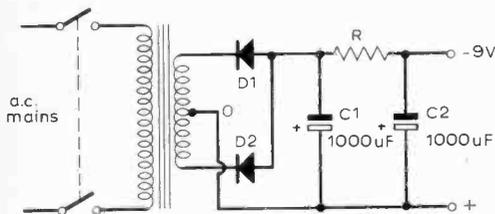
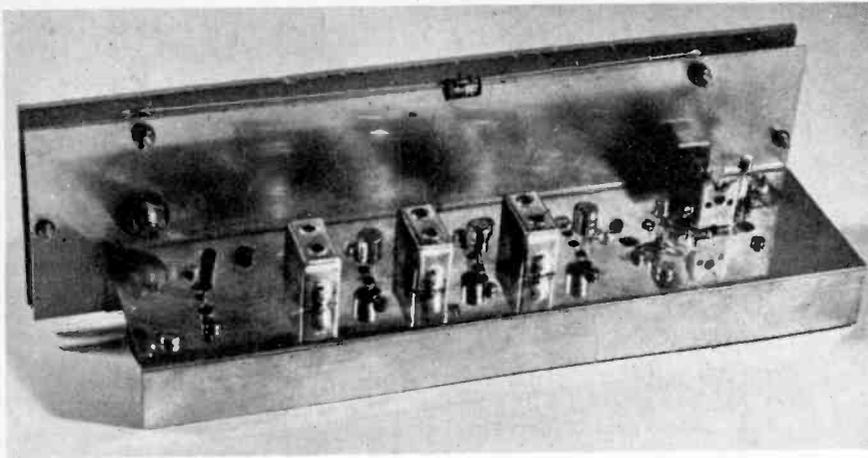


Fig. 8: An a.c. mains power supply. C1, C2—1000µF. D1, D2—BA100, OA202 etc. R—180Ω–390Ω, ½W, to give 9V output.

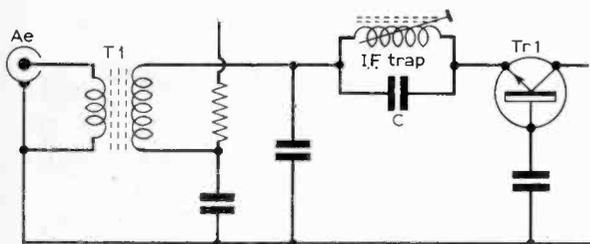


Fig. 9: If signals on 10.7Mc/s are being received this i.f. trap can be included. Details are provided in the text.

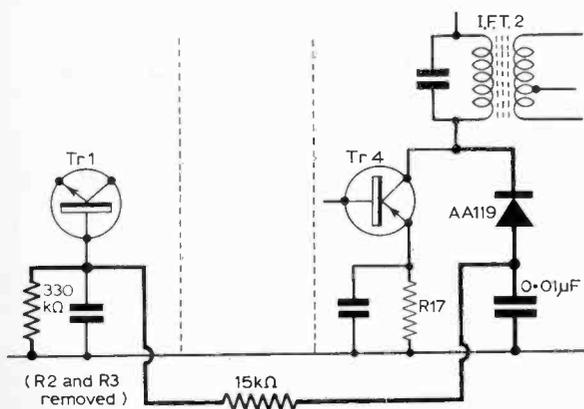


Fig. 10: An a.g.c. system which is a useful addition in high signal strength areas.

power to the tuner, and will have a long life as the current requirement is modest. It does, however, have the disadvantage that it must be replaced occasionally, and the performance of the tuner will fall off as the battery voltage falls. Even so, the tuner will perform satisfactorily until the voltage falls to 6 volts.

The tuner can be conveniently powered from the mains supply using the circuit Fig. 8. The mains transformer can be a small type with a centre tapped secondary supplying any voltage between 8–0–8 volts and 12–0–

12 volts. The resistor R is chosen to give 9 volts at the output of the supply with the tuner connected, and will be approximately 180 Ω with an 8 volt transformer and 390 Ω with a 12 volt transformer. The capacitors C1 and C2 will both be 12 volt working with an 8 volt transformer, but should be 15 v.w.g. with a 12 volt transformer. Almost any general purpose type of diode will serve for the rectifiers.

With either of these supplies, it will be desirable to fit an on-off switch.

If the tuner is to be used with a transistor amplifier, the supply can be taken from this provided it is either regulated or very adequately decoupled. For example, with an amplifier such as the PW Low Cost Hi-Fi, power can be taken from the 12 volt negative line via a 270 ohm ½ watt resistor, and decoupled with a capacitor of not less than 5000µF. The large decoupling capacitor is necessary to remove all trace of a.f. from the amplifier supply.

I.F. Rejection

In fringe reception areas where a particularly good aerial is a necessity, trouble may be experienced with i.f. breakthrough, as in the unit described no i.f. trap is incorporated.

An i.f. trap is shown in Fig. 9. L consists of 25 turns of 26s.w.g. enamelled wire close wound on a Radiospares former with core. C is a 30pF capacitor. The trap should be mounted on the chassis top adjacent to Tr1 and connected between the emitter and feed-through insulator.

The core of L is adjusted to the point where i.f. breakthrough is completely eliminated.

Automatic Gain Control

A.g.c. was not found necessary as the maximum output is set by the limiting action of TR5.

In areas of very high signal strength where overloading might occur, a.g.c. may be desirable and a suitable arrangement is suggested in Fig. 10.

Acknowledgements

The author wishes to thank: C & D Electronics Ltd for their assistance and for supplying all of the components for the prototype.

Jackson Bros Ltd and Weyrad Ltd for their very willing and helpful co-operation. ■

P.W. F.M. TUNER

Complete kits of specified parts

- Resistor Kit (31 pieces) 10/6
- Capacitor Kit (28 pieces) 32/6
- Semiconductor Kit (9 pieces) 49/6
- Coil Kit. Comprising set of 3 Weyrad IF Transformers, Formers and wire etc for L1, 2 and 3 28/6
- Tuning gang Kit. Comprising Jackson C21 with 1/2" shaft, Drive, Drum, Pulleys, Pointer and cord 22/6
- Drilled chassis 7/6
- Aluminium front panel, undrilled 2/6
- Hardware Kit. Comprising 2 x 28 tagged strip, Paxolin 4" x 2" for transistor mounts, all screws and nuts 9/0
- P.T.F.E. feed through insulators, set of 3 5/6
- Scale, printed card, frequency calibrated 1/0

Complete Kit All of above
 Post paid: £8.00
 Post and Packing per order 2/6
 Kits of parts for P.W. Low Cost Hi Fi Amplifier (P.W. Jan.-Feb. 1968) S.A.E. for list

G. & D. ELECTRONICS
 17 St. Lukes Road,
 SUNDERLAND

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

WIRE-LESS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 9/6 extra.

INTERCOM/BABY ALARM



OUR PRICE ONLY 65/-

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

Transistor TELEPHONE AMPLIFIER



59/6

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (P/W) 189 KENSINGTON HIGH STREET, LONDON, W.8.

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets and Manufacturers' Manuals for most makes and types of Radios, Tape Recorders and Televisions.

Please complete order form below for your Service Sheet to be sent by return. To:

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND
 LONDON WC2

Make	Model	Radio/TV

1968 List available at 2/- plus postage

If list is required indicate with X

From _____
 Address _____

enclose remittance of _____
 (and a stamped addressed envelope)
 s.a.e. with enquiries please
MAIL ORDER ONLY (March PW)


YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

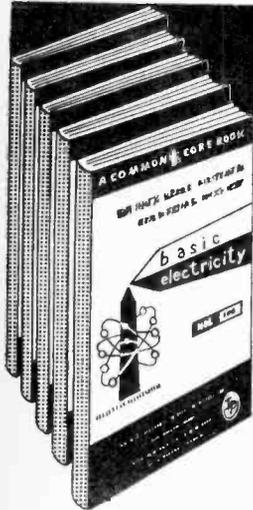

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"May I take this opportunity to thank you for such enlightening works and may I add, in terms, easily understood by the novice." L. W. M., Birmingham.

"I find that the new pictorial method is so easy to understand, and I will undoubtedly enjoy reading the following five volumes: thank you for a wonderful set of books." C. B., London.

"Please accept my admiration for producing a long felt want in the field of understanding Electronics." S. B. J., London.

"The easiest set of manuals it has been my pleasure to study." J.P.P., Taunton.

A TECH-PRESS PUBLICATION

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 15/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY BASIC ELECTRONICS
 Prices include Postage and Packing.

Signature _____
 (If under 21 signature required of parent or guardian)

NAME _____
 BLOCK LETTERS
 FULL POSTAL ADDRESS _____

POST NOW FOR THIS OFFER !!

**Fully guaranteed
Individually packed
VALVES**

PERSONAL CALLERS WELCOME
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-, 10/- to £1. 2/-; over £1. 2/- per £1; over £3 post free. C.O.D. 4/- extra

COOMOR ALL valves guaranteed brand

A2134 8/-	ECF82 6/6	KT66 18/6
ARR 5/-	ECH35 11/-	KT67 45/-
ARRP 3/-	ECH48 10/-	KT71 7/6
AR12 3/6	ECH81 5/6	KT76 2/-
ARTP1 5/6	ECH83 5/6	KT88 27/-
ATP4 2/3	ECL90 7/6	KT263 7/-
AZ31 9/6	ECL82 6/6	LK3 6/-
BD78 10/-	ECL83 10/6	MH4 5/6
BL48 40/-	ECL86 8/6	MH41 8/6
BT35 15/-	EF36 3/6	MHL106 7/6
BT45 15/0	EF37A 8/-	M16 6/-
B783 35/-	EF39 6/-	N34 8/6
CV102 3/-	EF40 9/6	N76 15/-
CV103 4/-	EF41 9/6	OA2 6/-
CV316 (unatched pair) 120/-	EF42 13/6	OB2 6/-
CV315 (single) 50/-	EF50 4/6	OC3 7/-
CV316 (single) 50/-	EF85 6/6	OD3 6/-
CV317 7/6	EF86 6/6	OZ4A 5/-
D41 3/3	EF89 5/-	P41 7/-
D77 3/3	EP91 3/-	PABC80 7/6
DA100 2/3	EP92 2/6	PC86 10/3
DA90 7/6	EP93 5/-	PC87 9/6
D141 4/-	EP95 5/6	PC90 9/3
DET20 2/-	EP183 6/6	PC90 9/3
DET25 10/-	EP184 7/-	PC84 6/6
DF91 3/-	EP189 7/6	PC89 9/6
DF92 2/6	EL31 15/-	PC189 10/6
DF96 7/6	EL32 10/3	PC189 10/6
DK92 9/-	EL34 18/6	PC182 6/3
DK96 8/-	EL35 5/-	PC184 9/3
DL63 8/6	EL38 24/-	PC186 9/3
DL92 4/-	EL41 10/3	PCF80 9/6
DL94 6/6	EL42 11/-	PCF80 9/6
DL96 8/-	EL43 9/6	PCF80 9/6
DL810 12/-	EL44 9/6	PCF80 9/6
DY86 6/6	EL45 5/6	PCF80 9/6
DY87 6/6	EL46 5/3	PCF80 9/6
EM0F 18/-	EL50 9/6	PCF80 9/6
EM0C 8/-	EM31 5/-	PCF80 9/6
EM0D 8/-	EM32 7/-	PCF80 9/6
EM0E 8/-	EM33 7/-	PCF80 9/6
EM0F 8/-	EM34 7/-	PCF80 9/6
EM0G 8/-	EM35 7/-	PCF80 9/6
EM0H 8/-	EM36 7/-	PCF80 9/6
EM0I 8/-	EM37 7/-	PCF80 9/6
EM0J 8/-	EM38 7/-	PCF80 9/6
EM0K 8/-	EM39 7/-	PCF80 9/6
EM0L 8/-	EM40 7/-	PCF80 9/6
EM0M 8/-	EM41 7/-	PCF80 9/6
EM0N 8/-	EM42 7/-	PCF80 9/6
EM0O 8/-	EM43 7/-	PCF80 9/6
EM0P 8/-	EM44 7/-	PCF80 9/6
EM0Q 8/-	EM45 7/-	PCF80 9/6
EM0R 8/-	EM46 7/-	PCF80 9/6
EM0S 8/-	EM47 7/-	PCF80 9/6
EM0T 8/-	EM48 7/-	PCF80 9/6
EM0U 8/-	EM49 7/-	PCF80 9/6
EM0V 8/-	EM50 7/-	PCF80 9/6
EM0W 8/-	EM51 7/-	PCF80 9/6
EM0X 8/-	EM52 7/-	PCF80 9/6
EM0Y 8/-	EM53 7/-	PCF80 9/6
EM0Z 8/-	EM54 7/-	PCF80 9/6
EM0A 8/-	EM55 7/-	PCF80 9/6
EM0B 8/-	EM56 7/-	PCF80 9/6
EM0C 8/-	EM57 7/-	PCF80 9/6
EM0D 8/-	EM58 7/-	PCF80 9/6
EM0E 8/-	EM59 7/-	PCF80 9/6
EM0F 8/-	EM60 7/-	PCF80 9/6
EM0G 8/-	EM61 7/-	PCF80 9/6
EM0H 8/-	EM62 7/-	PCF80 9/6
EM0I 8/-	EM63 7/-	PCF80 9/6
EM0J 8/-	EM64 7/-	PCF80 9/6
EM0K 8/-	EM65 7/-	PCF80 9/6
EM0L 8/-	EM66 7/-	PCF80 9/6
EM0M 8/-	EM67 7/-	PCF80 9/6
EM0N 8/-	EM68 7/-	PCF80 9/6
EM0O 8/-	EM69 7/-	PCF80 9/6
EM0P 8/-	EM70 7/-	PCF80 9/6
EM0Q 8/-	EM71 7/-	PCF80 9/6
EM0R 8/-	EM72 7/-	PCF80 9/6
EM0S 8/-	EM73 7/-	PCF80 9/6
EM0T 8/-	EM74 7/-	PCF80 9/6
EM0U 8/-	EM75 7/-	PCF80 9/6
EM0V 8/-	EM76 7/-	PCF80 9/6
EM0W 8/-	EM77 7/-	PCF80 9/6
EM0X 8/-	EM78 7/-	PCF80 9/6
EM0Y 8/-	EM79 7/-	PCF80 9/6
EM0Z 8/-	EM80 7/-	PCF80 9/6
EM0A 8/-	EM81 7/-	PCF80 9/6
EM0B 8/-	EM82 7/-	PCF80 9/6
EM0C 8/-	EM83 7/-	PCF80 9/6
EM0D 8/-	EM84 7/-	PCF80 9/6
EM0E 8/-	EM85 7/-	PCF80 9/6
EM0F 8/-	EM86 7/-	PCF80 9/6
EM0G 8/-	EM87 7/-	PCF80 9/6
EM0H 8/-	EM88 7/-	PCF80 9/6
EM0I 8/-	EM89 7/-	PCF80 9/6
EM0J 8/-	EM90 7/-	PCF80 9/6
EM0K 8/-	EM91 7/-	PCF80 9/6
EM0L 8/-	EM92 7/-	PCF80 9/6
EM0M 8/-	EM93 7/-	PCF80 9/6
EM0N 8/-	EM94 7/-	PCF80 9/6
EM0O 8/-	EM95 7/-	PCF80 9/6
EM0P 8/-	EM96 7/-	PCF80 9/6
EM0Q 8/-	EM97 7/-	PCF80 9/6
EM0R 8/-	EM98 7/-	PCF80 9/6
EM0S 8/-	EM99 7/-	PCF80 9/6
EM0T 8/-	EM100 7/-	PCF80 9/6

RG1-240A	U5 7/-	X66 7/8	184 5/-	5A1740 5/-	6AC7 3/-	6CW4 13/-	12AT6 4/6	77 6/8
	U21 10/6	X76M 7/-	185 4/6	5B251M40/-	6AG5 2/6	6D6 3/-	12AT7 4/6	78 5/8
	U41 7/6	X118 8/6	174 3/-	5B252M35/-	6AG7 6/6	6E5 8/6	12AT7WA 4/6	80 5/8
	U85 5/8	X145 8/6	2A3 5/-	5B254M40/-	6AH6 11/6	6EA8 6/6	12A7 4/3	81 1/6
	V246A 1K	Y63 6/6	2D21 4/9	5B265M	6AT7 3/-	6E17 7/6	12AV6 5/6	84 5/8
		Y65 4/-	3A4 4/-		6B7 3/-	6F23 13/6	12AX7 6/6	85A2 7/6
		Z80U 29/-	5R4WG4		6BK6 12/6	6F50T 8/-	12AX7WA 282A	25/6
	VLS631 35/-	Z80U 25/-		5R4WG4	6BK6 12/6	6F6G 8/-	12AX7WA 282A	25/6
	V22 3/6	Z80U 12/-	3B7 5/-	5U4G 4/6	6BK6 12/6	6F7 6/-	12AY7 10/6	307A 5/6
	VP133 9/6	Z80U 12/-	3B24 14/-	5V4G 7/6	6BK6 12/6	6F8G 5/6	12BA6 6/6	357A 70/-
	VR99 7/6	Z80U 12/-	3D6 3/-	5X4G 8/6	6BK6 12/6	6F12 4/-	12B6E 3/6	368A 30/-
	VR105/30	Z80U 12/-	3E29 50/-	5Y3GT 5/6	6BK6 12/6	6F17 5/6	12JH7 3/6	393A 27/6
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F22 3/6	12C8 3/6	446 8/-
	VU150/30	Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F23 20/-	12E1 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F24 20/-	12E2 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F25 20/-	12E3 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F26 20/-	12E4 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F27 20/-	12E5 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F28 20/-	12E6 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F29 20/-	12E7 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F30 20/-	12E8 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F31 20/-	12E9 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F32 20/-	12E10 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F33 20/-	12E11 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F34 20/-	12E12 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F35 20/-	12E13 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F36 20/-	12E14 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F37 20/-	12E15 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F38 20/-	12E16 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F39 20/-	12E17 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F40 20/-	12E18 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F41 20/-	12E19 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F42 20/-	12E20 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F43 20/-	12E21 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F44 20/-	12E22 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F45 20/-	12E23 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F46 20/-	12E24 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F47 20/-	12E25 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F48 20/-	12E26 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F49 20/-	12E27 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F50 20/-	12E28 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F51 20/-	12E29 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F52 20/-	12E30 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F53 20/-	12E31 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F54 20/-	12E32 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F55 20/-	12E33 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F56 20/-	12E34 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F57 20/-	12E35 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F58 20/-	12E36 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F59 20/-	12E37 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F60 20/-	12E38 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F61 20/-	12E39 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F62 20/-	12E40 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F63 20/-	12E41 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F64 20/-	12E42 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F65 20/-	12E43 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F66 20/-	12E44 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F67 20/-	12E45 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F68 20/-	12E46 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F69 20/-	12E47 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F70 20/-	12E48 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F71 20/-	12E49 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F72 20/-	12E50 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F73 20/-	12E51 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F74 20/-	12E52 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F75 20/-	12E53 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F76 20/-	12E54 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F77 20/-	12E55 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F78 20/-	12E56 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F79 20/-	12E57 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F80 20/-	12E58 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F81 20/-	12E59 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F82 20/-	12E60 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F83 20/-	12E61 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F84 20/-	12E62 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F85 20/-	12E63 17/-	703A 30/-
		Z80U 12/-	3Q4 8/-	5Y3WGB	6BK6 12/6	6F86 20/-		

practically wireless

commentary by HENRY

No. 54
Anti-Fubble Device

SORTING through some papers to learned societies. Came across a blatant case of ideas piracy. Shocking: Henry is hurt.

You know how it is. Some guy blazons a scheme for making millions out of rubberised magnets or reversible diodes, just after you had the whole invention perfected, produced and packaged. All you wanted was the time to actually *invent* it. Henry's bright notion was an anti-fubble device.

Fubble, I should mention, is not a patentable description. If Revox can coin the term "Wobble" to describe Wow and Flutter, surely Henry can get away with Fubble as a portmanteau word for flutter and rumble?

An anti-fubble device is essentially simple. Anything electronically impelled can be electrically controlled. So we receive the output from a non-linear source, process it, use the result to control that source and the output should be linear within the acceptance time of the detecting system.

The principle is applied to gramophone and tape deck motors. In these cases, current consumed by the d.c. motor depends partly on any mechanical resistance. Torque varies—current varies. The variation is sampled, controlling a transistorised circuit which effectively damps the

supply line. So the motor attempts to turn always at the same speed.

I say "attempts" for in practice the device has fairly narrow limits. When the retarding force causes the drive mechanism to vary beyond those limits, the effect can be wild, man, wild. Not all servo systems are as effective as the Sony 3000 turntable, whose control circuit is more comprehensive than the average gramophone amplifier, and whose "black box" (well, silver, actually) is larger than the motor it controls. But when one has a turntable so finely engineered that one has to take a walk around the block after fitting the turntable, to allow the air bearing to settle, who is arguing about a few extra refinements? Not this green-eyed critic.

Logically, in audio engineering, the next step is to control whatever is outside the feedback loops. Perfectionists tell us that the ultimate is a signal injected directly into the brain. But I do not fancy calling in the surgeon every time I want the slope filter adjusted. We shall have to settle for a perfectly controlled system feeding some sort of transducer. Which, with loudspeaker output, is what we have.

There are various methods of damping an amplifier-loudspeaker combination to reduce resonances, maintain a constant drive, keep some sort of equilibrium. But the mechanics of the system always add some kind of coloration. As long as we are aware of the cone former puffing in and out of that gap, we shall feel uneasy.

For those who say the electrostatic speaker is the answer, I can only point mutely to the little woman, who refuses to take any more furniture out of the lounge. The room is not big enough for the siting of a stereo pair at least four feet from *any* wall. Henry wants to *sit* and listen, not prop himself in the doorway.

So let's be inventive and defeat fubble with a method of including the loudspeaker in the feedback loop.

We shall float a transducer at the focal point of the loudspeaker cone, read off pressure variations, convert them to an electrical signal and combine it with the audio output. Brilliant! Why didn't someone think of that before?



The little woman who refuses.

Trouble is, someone has. Cutting right across Henry's bows, Messrs. Philips describe what they call motional feedback with loudspeakers in *Technical Review* Vol. 29, 1968, No. 5. The paper is by J. A. Klaasen and S. H. de Koning and is far too long and detailed for my exposition here. Briefly, however . . .


An acceleration transducer consisting of a piezo-electric device is fixed to the moving coil. At low audio frequencies it produces a feedback signal which is integrated and added to the main feedback, giving a flat amplitude characteristic, to below the mechanical resonant frequency of the loudspeaker. Substantial improvement in bass is reported. They have beaten fubble—or have they simply made it possible to hear it with greater clarity?

Ah well, back to the drawing-board.



A walk around the block.

MICROPHONE PREAMPLIFIER

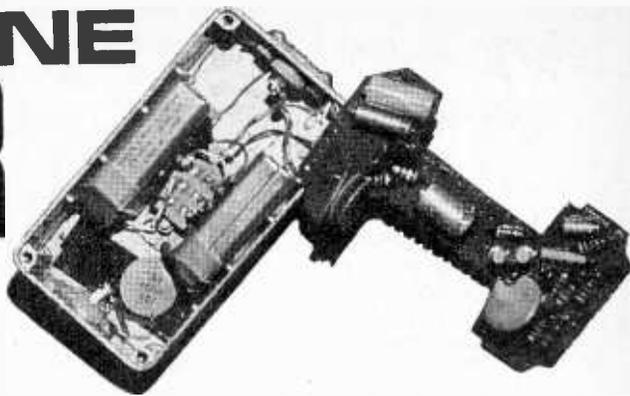

J. A. JEBB

A HIGH-GAIN RUGGED UNIT FOR BOOSTING LOW-LEVEL AUDIO SIGNALS

THIS unit was designed to meet the needs of general amateur tape-recording systems, both indoor and outdoor, for insertion in a signal line carrying insufficient signal for the purpose for which it is intended. Such a unit must have a very high gain, high stability, be small in size, and have good frequency response. Several two-transistor designs were tried, and it was found that these had low noise levels, but rather insufficient gain. Moreover, loading of the output resulted in alteration of the a.c. negative feedback level in one case, and this produced severe distortion.

A three-transistor circuit was then tried, and it was found that an increase in gain resulted. This circuit was originally designed by A. R. Bailey and described in *Wireless World*, Dec. 1966, and the author claims no credit for the exact details. The characteristics of this circuit were found to fit the needs of the unit, having an input impedance of about 200k Ω with an output impedance of 200 Ω and that the feedback point was at low impedance, so no loading effects caused by any feedback network used were apparent.

Silicon transistors are used throughout, giving a gain of 30dB. The type of transistor is not of critical importance, but if others than the types specified are used, then care must be taken to ensure that the d.c. operating point of the amplifier is satisfactory. The voltage supply is quite high (18V), this is to ensure that the amplifier does not easily bottom and square off the wave-form. This high voltage presents difficulties as far as size of battery is concerned, but this can be overcome by careful layout. The current drawn is between 2.1 and 2.5mA.

Frequency response will be the least of the constructor's problems; the unit has been used by the author at 200kc/s while still providing useful gain. The lower limit is about 20c/s.

Circuit description

Tr1 is a simple amplifier operating in common emitter mode, coupled by an R.C. parallel network to the d.c. connected pair, Tr2 and Tr3. This network allows the d.c. operating point to be stabilised over the whole amplifier, rather than independently over Tr1 then over Tr2 and Tr3. The output is at low

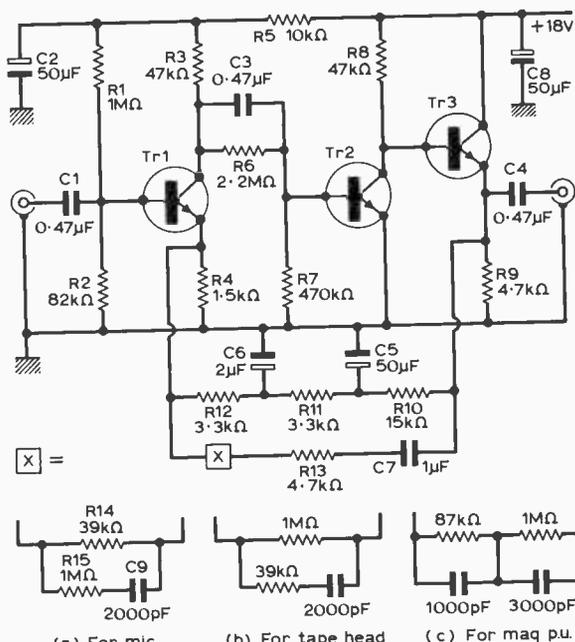


Fig. 1: The circuit of the preamp. Networks a, b and c are inserted at x for correct equalisation.

impedance, being of the emitter-follower configuration as the connection of long leads could load a high impedance output to an intolerable level. Feedback is applied between Tr1 emitter and Tr3 emitter at both d.c. and a.c. It is possible to modify the response curve of the unit by alteration of the a.c. part of the feedback loop, as will be explained later.

Construction

The unit was built in an Eddystone die-cast steel box, type 896. These boxes are a little expensive, but are ideal for this purpose as the close-fitting lid and the rigid construction are necessary features.

Veroboard was used, the components being arranged on the circuit-board corresponding to their relative positions in the circuit as far as possible. The input capacitor and several of the inter-circuit capacitors were ceramic types of only 10V working, for reasons of size limitation. It is therefore essential that the input does not contain any d.c. component.

The input and output plugs were of the flush-


Everything You need to know about

RADIO, TELEVISION & ELECTRICAL REPAIRS

AMAZING 'KNOW HOW' BOOK
Brings You RIGHT UP TO DATE!

576
PAGES
OVER
470
ILLUSTRATIONS

REVISED AND ENLARGED—this essential handbook for the enthusiast, handyman or professional repairer, is packed with detailed information and easy-to-follow instructions on how to service radio and TV sets (including all-transistor and U.H.F. circuits), audio equipment and domestic appliances of every kind. Shows every step in fault tracing and the use of modern test gear, from simple meters to complex oscilloscopes. Also provides practical guidance on household electrical installation work. 576 pages. Over 470 illustrations. Mammoth value—Special Library Edition, superbly bound in Leather, 10th, 50/-, or on easy terms: 13/- down and 3 monthly instalments of 14/- (total credit price 55/-). But first accept 7 Days' Home Trial Offer—without obligation!

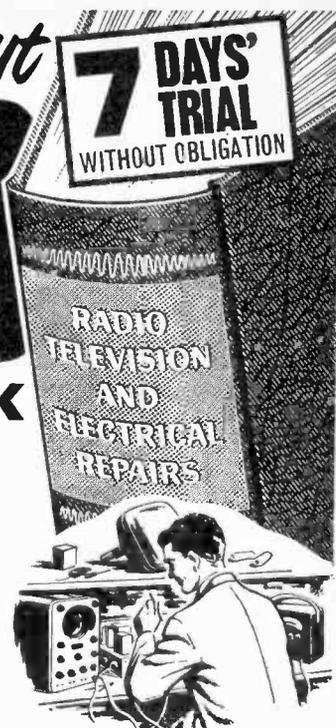

COVERS ALL THE LATEST TECHNICAL ADVANCES!


U.H.F. TELEVISION

Here are basic circuits and full instructions to enable you to service modern sets—get perfect 625-line reception.

Getting the best from RADIO AND TELEVISION SETS

How to make adjustments and repairs in order to get the best possible performance from any set.

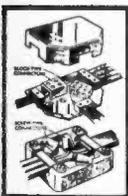All you need to know about DOMESTIC INSTALLATIONS




Learn from these helpful pages how to carry out modifications and extensions—with efficiency and safety! Complete guidance on lighting and power circuits, practical wiring work, safety regulations, cables, earthing, fuses, etc. Also Fluorescent Lighting, Time Switches and Thermostats.

Junction Boxes for Lead-covered Cables

WATER HEATING

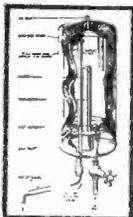All you should know about water heaters and how to install them and keep them in perfect working order. How to service FIRES and SPACE HEATERS.



HOW TO MAINTAIN AND REPAIR DOMESTIC APPLIANCES

From irons, toasters, hair dryers, etc. to cookers, washing machines and refrigerators. Also covers the repair and rewinding of small motors.

SPECIAL SECTION ON COLOUR TELEVISION

Explains clearly and concisely the principles of all the main colour systems.

FAULT FINDING

This grand book is invaluable for tracing faults in radio and TV sets (both valve and transistor circuits). Deals fully with tools and bench work—shows how to make the best use of test instruments. Tells everything you want to know—from how to carry out preliminary tests to how to align tuned circuits.

Servicing DOMESTIC AUDIO EQUIPMENT

How to locate and rectify faults in hi-fi equipment (mono or stereo), record players, tape recorders, etc.

ACT NOW!

Simply complete form, indicating method of payment preferred, and post without delay. Offer applies in U.K. only. Hurry, make sure of your copy NOW!

ONE GREAT VOLUME covers:

Current, Voltage and Resistance, Coils, Capacitors and Tuning, Valves, Tubes and Transistors, Radio Components, Receiver Design Principles, Transistor-Radio Circuits, Valve-Radio Circuits, Valve-Television Circuits, Transistor-Television Circuits, Colour-Television Systems, Audio Amplifier Circuits, Audio Equipment and Gramophones, Tape Recorders, Radio and Television Aerials, Tools and Bench Work, Test Instruments and Their Use, Fault Tracing and Circuit Testing, Alignment of Tuned Circuits, Television Fault Tracing, Interference Suppression, Domestic Power Supply Circuits, Electrical Wiring Work, Fluorescent Lighting, Thermostats and Time Switches, Motor Repair and Rewinding, Small Appliances, Space and Water Heaters, Electric Cookers, Washing, Drying and Ironing Machines, Electric Refrigerators, Suction Cleaners and Floor Polishers.

SEND NO MONEY NOW!

To: Dept. AFZ, Odhams Books, Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION please send me, on 7 Days' Home Trial, Radio, Television and Electrical Repairs. Within 8 days I will either (a) send the Cash Price of 50/- (plus charge for postage and packing), or (b) send a down payment of 13/- (plus postage charge), followed by a 3 monthly payments of 14/- (Total Credit Price 55 -). Alternatively, I will return volume in good condition, postage paid, within 8 days.

Cross out words NOT applicable below:

I wish to pay by CASH TERMS. I am (a) houseowner; (b) tenant in house or flat; (c) temporary resident; (d) single; (e) married; (f) over 21; (g) under 21.

PLEASE SIGN HERE

Your Signature

(Or, if you are under 21, signature of parent or guardian)

BLOCK LETTERS BELOW

NAME (Mr./Mrs./Miss)

Full Postal

ADDRESS

AFZ/EB/CC7

AIRCRAFT- PLUS GENERAL TELECOMMUNICATIONS BAND REC.

Listen to the thrills of aircraft, pilots and airports at work. Also Civil Depts., Fire and Ambulance services. Also taxis, Gas and Electricity services. Ideal for receiving 2 metre amateurs. Gives super reception within the range of all transmissions. A VHF broadcasts. Robust attractively finished metal cabinet size approx. 7 x 7 x 4in. Operates from a 9 volt internal battery. Internal speaker or headphone output. Price only £8.19.6, carr. and insurance 10/6.

MINIATURE TRANSISTORISED B.F.O. UNIT

This is a miniature transistorised B.F.O. unit, (tunable) that will enable your set to receive C.W. or B.S.B. reception. Compact. Single hole fixing. This small unit will fit anywhere. Ideal for all Ex-Govt. Communication Receivers and most Commercial Types. Complete with fitting instructions. 49/6, post free.

SCOOP PURCHASE TRANSFORMER SALE




Bulk purchase enables us to offer the following transformers at these ridiculously low prices. Made by a famous manufacturer and fully tested and guaranteed. Charger Transformers, 0-9-15V. 2A. 8/6 each, p. & p. 2/6. Two for 17/6, post free. Transistor Power Pack Type 6.3V at 2A. 7/6 each, p. & p. 2/6. 12V at 2A. 12/6 each, p. & p. 2/6.

ONE WATT TRANSISTOR AMPS

For 3-6 ohm speakers. Miniature Brand new and British inside. 9 volt operation. Only 37/6, p. & p. 2/6. Suitable 7 x 5in. Moving Coil Loudspeaker in cabinet. Only 17/6, p. & p. 2/6. If purchased together deduct 10/- from total.

PLUG-IN TX/RX

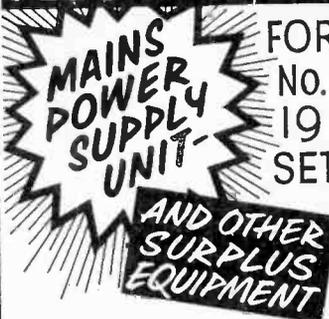

Run your 19 Set Transmitter and Receiver direct from your AC mains supply. We make a special unit brand new and ready to plug in, complete with full leads and connectors. Contained in a handsome louvered steel cabinet of robust and pleasurable finish. Price only £6.10.0, carriage 10/-.

Also manufactured by us are AC mains input Power Supply units handsomely appointed as above with full connecting leads and instructions for operating the following RECEIVERS.

No. 19 Set Receiver, £3.10.0, carriage 10/-, R. 1132 Receiver £3.10.0, carriage 10/-, H.R.O. Receiver £4.0.0, carriage 10/-, R. 1155 Receiver £3.15.0, carriage 10/-, 1475 Receiver £3.15.0, carriage 10/-, P.C.R. Receiver £3.10.0, carriage 10/-.

S.A.E. for details of other mains supply units for your equipment.

19 SET CONTROL UNITS. Brand new and boxed. Only 10/-, p. & p. 2/6.

19 SET HEADPHONES AND MIKE. Not new but working. 7/6 per pair, p. & p. 4/6.

TRAN-SISTORS

All tested and guaranteed

OC44
three for 5/-
post free.

OC72
three for 5/-
post free.

OC71
three for 4/6
post free.

OC45
three for 3/6
post free.

OC81
three for 5/-
post free.

AC128
three for 5/-
post free.


BSY 95A
three for 10/-
post free.

2N706
three for 6/6
post free.

BSY27
300Mc/s silicon
3 for £1 post free.

AIR/SEA TRANS/REC. RESCUE

Compact V.H.F. Trans./Rec. Fits in the pocket. Consists of Mike/Speaker, amplifier, aerial, transmitter and receiver. Were made to operate up to 100 miles depending on terrain. Operates from dry batteries. Completely self-contained. Cost Govt. over £50 each. Regulations state must not be operated in UK so please mention "For Dismantling purposes only" when ordering. Price £2.10.0 each, p. & p. 10/- Two sets for £5.0.0, post free. Four sets £8, carriage free. Bulk sale of 10 sets £15, carriage £1. Export enquiries invited.

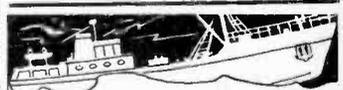

SHIPPING/S.O.S/BAND RECEIVER

Hear shipping from all over the world. Covers the complete maritime, trawler and amateur bands. A neat little superhet. Attractive black crackle finish case approx. 7 x 5 x 5in. Fully transistorised. 9 volt battery fits inside. Speaker or headphone output. Brand new direct from makers. Comparable with sets being sold at 30gu. Our Price only £9. Carr. and ins. 10/-.

HANDY POWER PACK KIT

Consists of Mains, Transformer, Silicon Rectifier, Electrolytics, and choke etc. Also robust chassis and full circuit and instructions. Input 200/250v. AC. Output 250v. 75mA. 6.3v. at 2 amps. Price assembled 32/6, p. & p. 7/6.

GLOBE SCIENTIFIC LTD
DEPT. P.W.24 CAWOODS YARD,
MILL STREET, LEEDS 9

FULLY BUILT STEREO AMPLIFIER. 2x3 watts, mains trans., metal rect., 2 x UCL82, 2 o.p. trans. for 3 ohm, vol/on-off, tone, balance, chassis type with 3 controls on front. 11 x 3 1/4 x 4in. high. 88 (8/- p. & p.).

Write for details of our F.M. (V.H.F.) tuner, self powered, mains, valves ECC85, EF89, 6BW7, ECC82. Fully built £7.10.0 or as kit £5. Book of instructions 2/6 (free with kit).

DULCI SOLID STATE TRANSISTOR AMPLIFIER. 2 x 7 watts, radio, tape and gram. inputs. For outputs of 4 to 15 ohms. £19.19.0 or with input for magnetic cartridges £23. S.A.E. for colour leaflet.

Full range of Garrard auto and single record decks usually in stock.

TRANSISTORISED F.M. TUNER A1005. Size 6 x 4 x 2 1/2in. 3 I.F. stages, double tuned discriminator, cap. tuned. £8.17.6 post paid, corresponding stereo decoder A1005M £5 post paid or £11 the two items if purchased together. 88-108 mc/s.

The "IMMEDIATE" bulk tape eraser and recording head demagnetiser, only 34/- post paid.

BUILT PRINTED CIRCUIT BOARD. 8 1/2 x 3in. with sec., 3 i.f. stages, driver trans. ready for output transformers (can be provided at 6/6 extra the 3). Includes OC44, two OC45. A bargain at 30/- post paid.

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS — 2 or 4 TRACK



Chassis 12 1/2 x 5 1/2 x 4 1/2in. high. Front panel aluminium and black—12 1/2 x 4 1/2in. 200-250 A.C. Record/Playback amp. switch On/Off-Tone; Vol./Mic.; Vol./Gram; Mic. Input; Gram. Input; Monitor; Speaker Socket Valves 6BR7; ECC83; EM84; EL84 & Rect.; Power pack, 2 Track £10.10.0; 4 Track £15 (12/6 p. & p.). Rexine covered cabinet (tan) 15 1/2 x 17 x 9 1/2in. high with sloping front for amp; complete with two tweeter speakers, and special adapting brackets for Magnavox Deck 85/- (8/- carr.) 3 speed Magnavox 4 track tape deck, Type 363. £16.10.0, carr. paid. 2 x 2 Stereo deck £20.

"SUPER SIX" L.W. and M.W. TRANSISTOR RADIO KIT, Mark 2. Complete set parts £4.2.6 (5/- post), PP6 batt. 2/9 extra. Instructions and list 2/- (free with kit). Superhet; ferrite rod; wooden cab. 9 1/2 x 7 1/2 x 3in. Celestion 4in. speaker, 6 transistors, diode, etc.

SPEAKERS IN CABINETS. 20 x 15 x 6 1/2in. Finished Vynal and Rexine, various colours. With E.M.I. 13 x 8in. 3 or 15 ohm speaker 90/-; with 12in. Elac 15-ohm 16W speaker. £8.10.0 (post 10/- on either). Top quality speakers 6 x 4in. (3 or 15 ohm), 14/6; 6in. (3-ohm), 12/6; 4in. (3 or 10 ohm), 12/6d.; 7 x 3 1/2in. (3 ohm), 16/6; 13 x 8in. (3 or 15 ohm) 4 1/2 (post 3/6) all others post 1/6 each. 12in. heavy duty Elac Loudspeaker 15 ohm, 20 watt, £6.6.0 (10/- post).


8 W. PEAK PUSH-PULL OUTPUT AMPLIFIER. 200-250 Volts A.C. EZ80, ECC83. 2—EL84, Bass, treble, vol/on-off, £7.17.6 (post paid). Size 12 x 3 1/4 x 5in. high. For Record Player, Radio Tuner, etc. **MAINS TRANS.** o.p. trans. for 3 ohm.



RADIOGRAM CHASSIS unused but very slightly tarnished. Size 13 1/2 x 5 1/2 x 7in. Dial 18 x 4in. gold and brown. Controls beneath dial. Tone, Volume/on/off, MW/LW/Gram Tuning. Ferrite rod aerial. Valves UY85 rect., UCL82, UB789, UCH81. Limited quantity. £7.7.0, carr. paid.

1 1/2 W MAINS GRAMOPHONE AMPLIFIERS. EZ80, ECL82, O.P. Transformer (3 ohm). Vol./On-off and Tone Control. Double wound mains transformer. 2 1/2 x 2 1/2in. x 2 1/2in. separate but wired to chassis, 4in. x 2 1/2in. x 4 1/2in. over valves, 65/- post paid including 6 1/2in. Speaker. (52/6 less speaker.)

6 PUSH-BUTTON STEREOGRAM CHASSIS

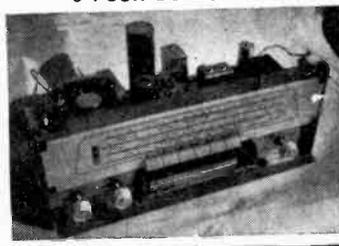

M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Gram; Vol; Tone; Mains Trans; 200-250 Volts; 2 o.p. for 3 ohm. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2in. high. Dial silver and black 15 x 3in. 190-550M; 18-51M; 60-187M; VHF 86-100 Mc/s. Valves: ECC85, ECH81, EF89, 2x ECL86, EM84 and Rect. Price £19.19.0, carr. paid. With Stereo Decoder fitted £7.10.0 extra.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.
(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
CLOSED TUESDAY AND WEDNESDAY.

mounted Belling-Lee type, these are quite strong, and the plugs will not pull out very easily. The base-bias resistors of Tr1 are very important, as they determine the current that flows through the system. Consequently, resistors of good thermal and long-term stability are essential here, though the others in the circuit are not critical.

Because of the low impedances used in the circuit, no problems with feedback oscillations should occur, but a low-impedance earth path is essential as the circuit may oscillate under certain conditions, e.g. input shorted. The components used are all available from *Radiospares*, with the exception of the die-cast box and transistors, which the author obtained from *Electroniques*, (STC) Ltd. and Mullard Ltd. respectively.

Operation

Care must be taken when switching-on for the first time, for if a mistake has been made, transistors may start to illuminate the workbench! A multimeter and a few resistors or a resistance box are of great assistance here, since then the battery voltage may be increased gradually, and watch be kept on the total current, which should be around 2mA. The circuit will not operate at about 12V, so do not be discouraged if nothing happens below this level. With the input open-circuit, the noise may seem excessive, but on connection of a 50K Ω or less input load, the noise should disappear.

The unit should find use among tape enthusiasts, as it is suitable for use with a microphone at the distant end of a long coax cable, thus feeding the cable at volt rather than millivolt level, and also alleviating the treble-loss due to cable capacitance by reduction of the impedance of the signal.

The author's own unit has proved reliable over a period of about 18 months, and has withstood several hard landings on various floors, and even immersion in water. ■

★ components list

Resistors:

R1	1M Ω †	R9	4.7k Ω
R2	82k Ω †	R10	15k Ω
R3	47k Ω	R11	3.3k Ω
R4	1.5k Ω	R12	3.3k Ω
R5	10k Ω	R13	4.7k Ω
R6	2.2M Ω †	R14	39k Ω
R7	470k Ω	R15	1M Ω
R8	47k Ω		

All $\frac{1}{2}$ watt miniature; all 10% except, †, Carbon film 5%

Capacitors:

C1	0.47 μ F 10V	C6	2 μ F 15V
C2	50 μ F 40V	C7	1 μ F (2 x 0.47) 10V
C3	0.47 μ F 10V	C8	50 μ F 25V
C4	0.47 μ F 10V	C9	2000pF
C5	50 μ F 16V		

Semiconductors:

BC 107/108/109 or BC 167/168/169
2N 2926
2N705—may need 500k Ω at R1 instead of 1M Ω .

Miscellaneous:

Eddystone die-cast box type 896, Veroboard, two PP9 batteries, connectors, on/off switch, etc.

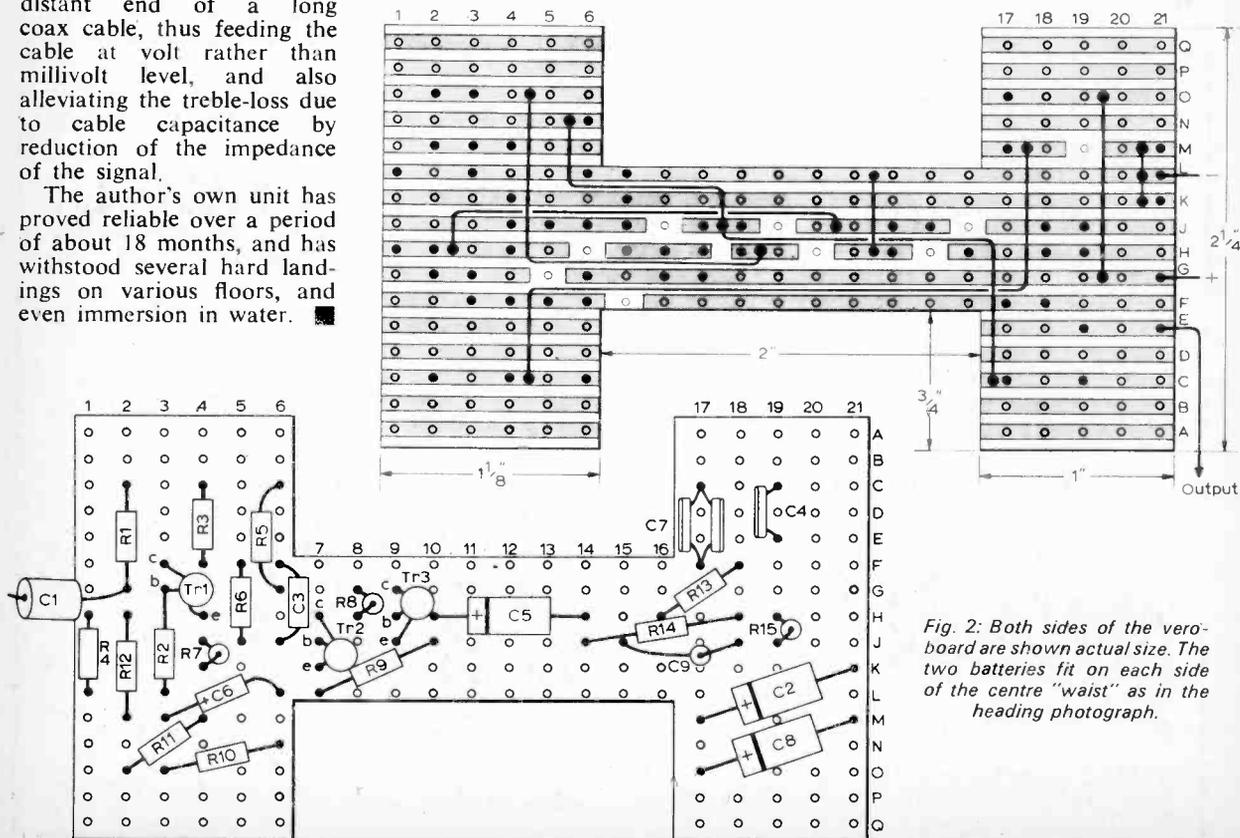


Fig. 2: Both sides of the veroboard are shown actual size. The two batteries fit on each side of the centre "waist" as in the heading photograph.

LETTERS

The Editor does not necessarily endorse the views expressed by correspondents.

What an un-holy business

I was delighted to note in Mr. Sinclair's article on Transistors, (Part one, January 1968), that "hole" theory is a fiction. Working in semi-isolation as I do, with contact mainly with students, I was under the impression that I was quite alone in believing this was so.

When I was called upon to take an RAE Course for the first time some years ago, transistor theory was a hole in my knowledge which needed filling.

I found it quite impossible to believe what I read in various text-books, many of which varied in their statements anyway, and I was forced to think for myself. I found it extremely simple to explain p-n-p by electron flow only and developed a theory to explain all the observable facts.

No text-book that I have seen "explains" in any other way than by "holes" so I sent my effort to a National Radio Society which is supposed to encourage the work of its amateur members with a view to publication and consequent controversy. What other scientific process is there in the constant search for truth?

The "acknowledged experts"—their description of themselves, not mine—seemed to shy away in horror for they sent it back with neither reason nor counter-argument. A subsequent challenge from me to meet either of them in a public debate brought no reply at all. But as I told them later, anyone who actually believes—and publishes diagrams to make that belief very plain—that current in a high vacuum valve flows in at the anode and screen grid and out through the cathode, can hardly expect to be taken seriously as experts on anything.

One could laugh at their behaviour if it wasn't for the harm they do. Every batch of students I get each year confess that they have become stuck on this very point. I tell them to ignore it and ask themselves always "What are the electrons doing?"

People seek to justify "hole theory" as an aid to understanding the transistor. Such people cannot be teachers, for nothing is further from the truth. My own belief is

that comparatively few people actually make any real effort to understand them. They follow the circuit directions and, since they usually work, that's all they bother about. This, in my experience, is because they find "hole" theory incomprehensible. I would also say here in this connection that young people becoming interested in radio for the first time invariably turn to PRACTICAL WIRELESS.

Unlike people who just write text-books, I have to stand and justify every statement I make, not only to mature students, but also to myself. Twenty-five years ago I had to write about another fiction in order to obtain my City & Guilds Certificates in "Radio Communication". This fiction was called AETHER. I've hardly heard of it for the past quarter of a century.

Now, so that my students can satisfy City & Guilds examiners in RAE, I have to teach them another fiction—"hole" theory.

Does any "expert" deny that large quantities of electrons enter a p-n-p transistor at the COLLECTOR terminal and leave at the EMITTER? If they do not deny this, how do these electrons get through?

As far as I am aware, I am the only person who has gone to the trouble to try to explain this and I have yet to discover anyone who can "shoot it down". You will certainly not find any mention of electron flow in p-n-p in any text-book or periodical. For one great moment I thought Mr. Francis (The Semiconductor Diode, P.W. May 1968), was on his way to it but it was not to be.

So, sir, if you are interested, may I say that I do not believe in "holes" which carry a positive charge—nothings which are current carriers. I regard "hole" theory as a disease. May I suggest the name HIATITIS PUNGENS for this distressing clinical condition?—**B. R. Meredith, G2CYV (London, S.W.16).**

Switch off and make room

I note in the December issue that letters are still appearing as a result of Mr. Meachim's comments last September.

I agree and would go even further:

Why have an RAE which re-

quires such a high standard of radio knowledge, when many of the successful candidates immediately purchase commercially built equipment (including aerial systems) sit down at their rigs and rabbit on for hours about their warts etc?

Admittedly a certain amount of humour is to be welcomed but to say that a radio amateur can advance his knowledge very little, and that it is a hobby not to be taken too seriously, amazes me!

Amateurs who have this outlook will quickly lose interest and we will soon see their gear offered for sale in these columns.

To those genuinely interested, radio is a wonderful and rewarding pastime, one learns something new every day, and can never learn enough.

To the chatterboxes I say, "Switch off and make room!"—**D. M. Seager (Wales).**

I'm for it too

I think a lot of people's views on the Beginners' Licence are completely wrong, as I and I am sure many others, would love to have the chance to become licensed to transmit. As there is not a s.w.l. club in the district, all I can do is go on listening and hoping too that I can become licensed.—**A. Bradley (Huddersfield).**

★ ★ ★

The RAE is not beyond anyone who is really keen and the sort of examination the "aspiring GW3" suggests is such a short step from the present RAE that it will make little difference in the amount of study required.

I also fail to see how a Beginner's Licence would raise the standard of the RAE and I too would like to know when Mr. Williams would possibly find time to transmit (I say nothing of even building his rig) if he did have a Beginners' Licence since he is so tied up with "O" level studies.

I am studying for "A" levels and still find time to prepare for the RAE. I therefore believe that people are only trying to find an easy way out in seeking a Beginners' Licence.

Do we really want to transmit with "L plates"? I think not.—**J. Kojminihni (Bournemouth).**

INCREASE YOUR KNOWLEDGE



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

MANY COURSES TO CHOOSE FROM incl.
RADIO & TV ENGINEERING & SERVICING,
TRANSISTOR & PRINTED CIRCUIT SERVICING,
CLOSED CIRCUIT TV, ELECTRONICS,
NUMERICAL CONTROL ELECTRONICS,
TELEMETRY TECHNIQUES, SERVOMECHANISMS
PRINCIPLES OF AUTOMATION,
COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

C. & G. Telecommunication Technicians' Certs
C. & G. Electronic Servicing
R.T.E.B. Radio/TV Servicing Certificate
P.M.G. Certificates in Radiotelegraphy
Radio Amateurs' Examination
General Certificate of Education, etc

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments, incl. professional-type valve volt meter (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.

THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

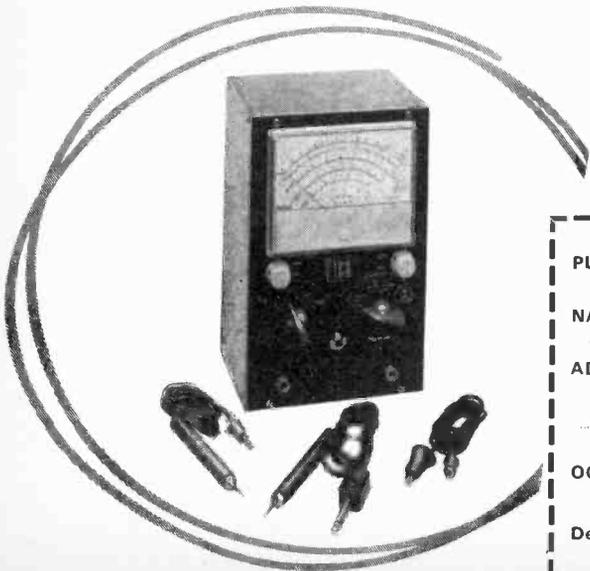You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialized subjects.



PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170. INTERTEXT HOUSE, PARKGATE ROAD, London, SW11
3/69

BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE,
150 REGENT ST., LONDON, W.1.

KING OF THE PAKS SUPER PAKS

Unequaled Value & Quality
BI-PAK NEW—UNTESTED
SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak, or money back.

PAK NO.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N708	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 Watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY128/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-Amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-Amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1 Amp SCR's TO-5 can up to 600 PIV CRS1/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise 2N3707	10/-
U32	25 Zener diodes 400mW DO-7 case mixed Vlt. 3-18	10/-
U33	15 Plastic case 1 Amp silicon rectifiers W4000 series	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

FULLY TESTED

AC107	3/6
AC126-7-8	2/6
AF118-117	3/6
AF139	10/-
AL102	15/-
BC107-8-9	5/6
BFY50-51-52	7/6
BSY26-7	3/6
BSY28-9	4/6
BSY95-95A	4/6
OC22-25	5/-
OC26-35	5/6
OC28-29	7/6
OC44-45	1/9
OC71-81	1/6
OC72-75	2/6
OC81D-82D	2/3
OC82	2/6
OC140	5/6
OC170	2/6
OC171	3/6
OC201	7/6
ORP12-60	8/6
OC271	9/6
OA45-10	1/9
OA47	2/-
OA70	1/3
OA79	1/9
OA81-85	1/8
OA81	1/9
OA85	1/9
OA200	3/-
OA202	3/6
2N696-7	5/-
2N706	3/8
2N708	5/-
2N2100	15/-
2N2646	15/-
2N2712	5/6
2N2926	2/6
MAT100-101	3/-
MAT120-121	3/6
BT140	3/8
BT141	4/-

SIL. RECTS TESTED

PIV 760mA 3A	10A 30A
50 1/- 2/9	4/3 9/6
100 1/3 3/3	4/6 15/-
200 1/9 4/-	4/6 20/-
300 2/3 4/6	6/6 22/-
400 2/6 5/6	7/6 25/-
500 3/- 6/-	8/6 30/-
600 3/3 6/9	9/- 37/-
800 3/6 7/6	11/- 40/-
1000 5/- 9/3	12/6 50/-
1200 6/6 11/6	15/-

PRINTED CIRCUITS

EX-COMPUTER
Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/- . Plus 2/- P. & P.

UNIJUNCTION

UT46 Eqt. 2N2646, 7/6
Eqt. TI843

FET's

2N3819	10/-
2N3820	25/-
MPP105	8/-

AD161-162 NPN-PNP
Comp. Pair 12/6 pr.
28034 15/- ea.

TRANSISTOR EQUIVALENT BOOK

52 pages of Cross References for transistors and diodes, types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each.

TESTED SCR'S

PIV 1 AMP 7A 16A 30A	25 50 7/6 8/6 10/6 35/-
25 50 7/6 8/6 10/6 35/-	100 8/6 10/- 15/- 45/-
200 12/6 15/- 20/- 55/-	300 15/- 20/- 25/-
400 17/6 25/- 35/- 80/-	500 30/- 40/- 45/- 95/-
600	— 40/- 50/-

INTEGRATED CIRCUITS

I.C. Operational Amplifier with zener output.

Type 701C. Ideal for P.E. Projects. 8 Lead TO-5 case. Full Data. Our Price 12/6 each. 5 off 11/- each. Large qty prices quoted for.

Fairchild Epoxy TO-5 8 Lead. I.C.

uL900 Buffer	10/6
uL914 Dual Gate	10/6
uL923 J.K. Flip-Flop 14/-	I.C. Data Circuits etc. 1/6
Mullard I.C. Amplifiers	TAA243 ORP.A.M.P. 70/-
TAA263 Min AF Amp 18/6	TAA293 G.P. Amp 26/-
RCA CA3020	Audio Amp 30/-

PLEASE NOTE.—To Avoid any further Increased Postal Charges to our Customers and enable us to keep our "By

Return Postal Service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, Direct to our Warehouse and Despatch Department, postal address:—BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and Packing 8/11/- per order. Minimum Order 10/-.

ERSIN



for quick,
easy, reliable
soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER

Contains 10 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy. 2/6 each.



SIZE 15 SOLDER DISPENSER

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



SIZE 12

Ideal for home constructors. Contains 90 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



BIB MODEL 8 WIRE STRIPPER AND CUTTER

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.

From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

FABULOUS VALUE
TRANSISTORISED STEREO HI-FI RECORD PLAYER
Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 5" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.
Advanced solid state amplifier plus 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.
EASY TO INSTALL
NO TECHNICAL KNOWLEDGE REQUIRED
Only **28** Gns. + P&P 17/6
H. P. terms available. Dep. £9.16.0 & 12 monthly payments of 36/9 (Total H.P. £31.17.0).
Send £10.13.6 today.
Amplifier available separately at only 16 Gns.

FANTASTIC BARGAIN OFFER!
"TRANSCONTINENTAL"
FULLY TRANSISTORISED STEREPHONIC RADIOGRAM CHASSIS
Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY** 34 1/2 GNS. 17/6
17 Transistors & 10 diodes
EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
H.P. available £12.16 dep. plus 18 monthly payments of 32/- (Total H.P. £40.17.6).
Send £12.19.0 today.

Callers Welcome

PLEASE SEND ME FREE DETAILS OF YOUR RANGE
Name: _____
Address: _____
LEWIS radio 100 CHASE SIDE, SOUTHGATE, DEP. P369 LONDON, N.14. TELEPHONE PAL 3733/9665

LETTERS

The Editor does not necessarily endorse the views expressed by correspondents.

No excuses please!

Recently several correspondents, particularly some of the younger enthusiasts, have written to you advocating a Beginners' Licence so that they can operate a transmitter without having to sit for the Radio Amateurs' Examination. There seems to be a general complaint that forthcoming "O" levels, or other commitments, leave no time to study for the RAE.

One can appreciate the difficulty in this respect, but I would like to put just one question—if these poor unfortunates have no time to study for the RAE, how could they find time to operate the transmitters they have such a burning desire to put on the air?—W. E. Thompson, G3MQT (*Sussex*).

★ ★ ★

I am becoming appalled by young readers who are sending in correspondence in greater and greater amounts, all grumbling and bemoaning either the terrible "work" for GCE and other exams, or the absence of easy or beginners' transmitting licences. (As if Amateur Radio has not survived for quite a long time without.) I want to assume that J. Waters and C. Williams are not using the reasons given as excuses for not aiming at the requirements (international I might add) for a full transmitting licence. I want to concentrate on the signs of inhibition and strait-jacketing that is the only other answer to their attitude.

I have had a great deal of experience with youth Amateur Radio schemes, and radio/electronic club work, as some of your readers might know. Always, those boys with fears, and excuses, and cramming tendencies about exams and school work make by far the worst club members. So often they are inhibited by this pressure; coming, I'm afraid, from unenlightened parents, and from a competitive school situation. Teachers too, use this pressure as an offshoot of the Authoritarian system we still have in the schools. I have waged war against this kind of thing as a teacher inside the system, and will continue to do so outside it. The social development and creativity of youths with the attitude I have mentioned, particularly suffers. To see a conflict between Amateur

Radio/Electronic hobbies for boys and this pressure for "progress" is, well frankly, very depressing, and all of us who know how releasing and worthwhile our activities are should attack the creeping paralysis of the freedom and fun and personal exploration which is a right for youth. I have even had a case where a Headmaster more or less demanded that a boy leave his Scout Troop, for the sake of some school requirement. There was a case of school trying this kind of thing on with a member of the Roding Boy's Society, and we were ready for a real battle . . . a few well-aimed mental kicks up the appropriate region of these pompous teachers, but they climbed down.

What is the usual excuse given? "You won't get a good job", or "The school must keep up its record", or perhaps "What will the neighbours think, if he isn't suffering with his work; good heavens he shouldn't enjoy it!" For an answer, read the first few paragraphs of *A Career in Physics* published by the Institute of Physics. (About boys building amplifiers, and its preferability to academic swots.) Also, I have known young possessors of an Amateur Licence gain great advantage in employment with industry. Personnel officers being quite impressed, at the least RAE being equal to a GCE (Although all this is not the reason for the RAE!) And finally, I assure you, the attitude of many a college department head, or professor is, "Yes, yes, OK on the GCEs, you have a few, I'm not interested in them; now what projects have you carried out, what clubs have you been in? Can you take responsibility—have you been an officer in a club or society?" I think Amateur Radio with its social-scientific experience, its national, no international, friendship forming powers and other advantages, is uniquely placed regarding this. So let's not have this inhibited grumbling from young people who should have the opposite view.—Ken Smith, G3JIX (*Kent*).

I disagree

I disagree with C. Williams (January issue) on having a beginners' licence. I too have "O" levels coming up this year, but I foresaw

the amount of studying coming up and so took the RAE last year.

If C. Williams is really keen he will be able to wait until next December and anyway, if he cannot find the time to study, how is he going to find the time to go on the air? I'll be removing my PA bottle!—J. O. Parkinson, G3XJB (*Manchester 23*).

Not telegraph ops

It would appear that Mr. Dixon ("P.W." January 1969) would like to see the G.P.O. issue an Amateur licence to cover all bands with a special licence for the morse key. He implies that Amateurs only use morse because it is a skill they have been forced to acquire in the process of obtaining a licence. He goes on to say that if the morse test is abolished, Amateur morse will be killed and radio Amateurs will be struck down with some sort of malady leaving them unable to send morse at more than two words per minute.

I fear I cannot agree with Mr. Dixon's views. I still feel that the morse test is unnecessary. If it were abolished I don't think that morse would disappear or that the standard would be lowered. Amateurs realise that if they are to work DX under difficult conditions then obviously AI is the best form of emission. If they want to operate under bad conditions then they will learn morse. If they are motivated in this way they will learn the code very quickly and enjoy doing so.

At present a radio Amateur has the option of using either phone or c.w. Under the new system where there is no longer a morse test, there would be the same choice of modes of operation. Mr. Dixon feels that only phone would be used under the new system. I hold that if the morse test were abolished morse would still continue to be used as the most effective mode under difficult conditions. R.T.T.Y. operators are not required to obtain an 80 w.p.m. certificate before they are allowed on the air. Why then should radio Amateurs be required to obtain a certificate in morse? We must continue to bear in mind that radio Amateurs are supposed to be experimenters and not telegraph operators.—T. Wright (*Northern Ireland*).

PART 2

MAGNETIC SOUND RECORDING

W.S.FOWLER

THE chief difficulty with the type of tape recorder described last month lies in the fact that the tape speed is constantly varying, because the spool drive diameter gradually increases during the recording process, thus pulling the tape off the supply spool at a gradually increasing rate. A typical machine of the type described may commence recording at a speed of about 3 i.p.s., and towards the end of the spool the speed may have increased to over 7 i.p.s. This is wasteful of tape and furthermore as the quality of the recording is dependent upon the speed of the tape travel, the recording will be uneven in quality.

Furthermore, as this simple "spool drive" system does not employ any kind of governor or regulator to stabilise the actual motor speed, any variations or irregularities in the load will produce variations in tape speed which give rise to "wobbles" in reproduction known as *wow* and *flutter*. For this reason such machines are not suitable for the recording and reproduction of music, etc.

For serious recording work, especially of music, it is necessary to use a drive system which will allow the tape to traverse past the record/play head at a constant speed (usually $3\frac{1}{2}$ i.p.s., with alternatives of $7\frac{1}{2}$ in. for high quality work and $1\frac{1}{2}$ in. for speech etc.) This constant speed is achieved by the use of a small capstan in conjunction with a pinch wheel, revolving at a constant speed (see Fig. 9).

As with the spool-driven recorder, the tape is fed from the left hand tape spool, which usually "free-wheels" for this function. (With quality decks, a slight reverse pull is applied in order to maintain an even tape tension). The tape leaves the feed spool and passes around the left hand guide pillar and along to the erase head, followed by the record/play head. Before continuing to the take-up spool via the right hand tape guide it is pressed against the constantly revolving capstan (see diagram) by the pinch wheel.

This arrangement ensures that, regardless of the increasing size of the take-up spool as the tape "builds up" on it during recording, the actual speed of tape traverse past the heads remains constant. It follows that some kind of "clutch" system of power drive to the take-up spool is necessary, in order to avoid a constantly increasing tension, since the take-up spool is increasingly working against the constant drive of the capstan.

THREE MOTOR DECKS

Some commercial decks employ three separate electric motors for the tape drive system; motor 1 is connected directly to the left hand feed spool and is used to provide rapid rewinding of the tape

before replay, see Fig. 9. It may also be used in conjunction with a dropper resistance to provide a slight "reverse drag" during normal operation.

Motor 2 drives the capstan at a constant speed, to produce tape speeds of $1\frac{1}{2}$; $3\frac{1}{2}$; or $7\frac{1}{2}$ i.p.s. The drive from the motor spindle is generally via a stepped pulley and a rubber idler wheel which drives against the flywheel rim of the capstan itself. The manner of construction closely resembles that of the motor drive of a gramophone turntable providing for various speeds.

The drive motor is usually mounted on rubber bushes to minimise vibration etc., and on high quality tape decks the flywheel is dynamically and statically balanced, as is the motor armature, in order to minimise the irregularities which produce wow and flutter, noticeable as a "whine" on playback, especially with piano music. The wow and flutter specification for a satisfactory tape recorder for music use should not be in excess of 0.15% at a tape speed of $7\frac{1}{2}$ i.p.s., and 0.2% at a tape speed of $3\frac{1}{2}$ i.p.s.

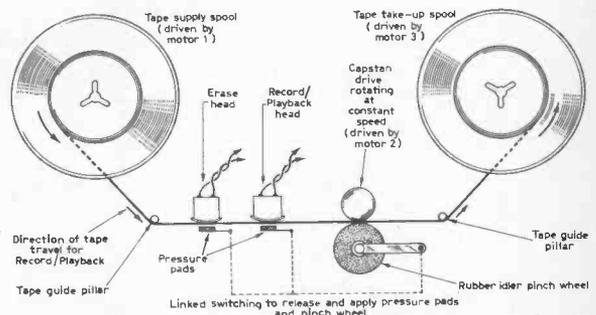


Fig. 9: The arrangement of the feed and takeup spools, the heads and the pinch wheel on a three motor tape deck.

Motor 3 is the "take-up" motor which spools the tape after it has passed the capstan. The motor spindle is usually directly coupled to the spool platform. This motor is also brought into function to provide a "fast forward" facility when it is desired to reach a certain point which may be, for example, half-way through the tape length.

Many satisfactory tape recorders, while using the capstan principle, have dispensed with the "three motor" principle described. The alternative system uses a single motor which drives the capstan by means of a rubber pulley. On its return journey the pulley is taken back to the motor via a flanged wheel; this wheel is coupled to the take-up spool by means of a felt clutch, which allows for the varying

Wharfedale High Fidelity single unit speaker - Super 8



£7.10.0.

The Super 8 is a single, wide spectrum loudspeaker unit. The massive magnet gives it very high sensitivity and it will give a much louder and purer sound volume than ordinary speakers.

It is simplicity itself to install in a home-built cabinet, needing no special skills.

The Super 8 will transform the results from your radio or radiogram. The sound of your television set can be greatly enhanced by using the Super 8 with a Wharfedale transformer.

Installed in your car, you will achieve a wonderful depth of sound from a normal car radio.

The Super 8 is a real high fidelity loudspeaker and gives a response from 20 Hz to 20,000 Hz in a good enclosure.



RANK WHARFEDALE LTD.,
IDLE, BRADFORD, YORKS.



Radio Technicians

enjoy exciting new scope now in
Air Traffic Control

There are opportunities in the National Air Traffic Control Service, a Department of the Board of Trade, for you to play a vital part in the safety of Civil Aviation. You'll work on the latest equipment including Computers, Radar and Data Extraction, Automatic Landing Systems and Closed-Circuit Television, at Civil Airports, Air Traffic Control Centres, Radar Stations and other engineering establishments including Heathrow, Gatwick and Stansted.

If you are 19 or over, with practical experience in at least one of the main branches of telecommunications, fill in the coupon now. Your starting salary would be £869 (at 19) to £1,130 (at 25 or over); scale maximum £1,304 (rates are higher at Heathrow). Non-contributory pensions for established staff.

Career prospects. Your prospects are excellent, with opportunities to study for higher qualifications in this expanding field.

Apply today, for full details and application form.

Write for details to: Mr. T. H. Mallett, B.Sc.(Eng.), C. Eng., M.I.E.E., Room 705, The Adelphi, John Adam Street, London, W.C.2 marking your envelope 'Recruitment'.

Name _____

Address _____

Not applicable to residents outside the United Kingdom.

RPW7

NATCS National Air Traffic Control Service



YOUR GUIDE TO A BETTER HOME IN 1969

PRACTICAL 1969 HOUSEHOLDER ANNUAL



FIVE FOR A DRIVE
Gutter and Flat Roof Renewal

A LOFT TO LIVE IN
Decorating made easy
FENCES and HOW TO FIX THEM

GET DOWN TO FLOORS



Packed with ideas and step-by-step instructions for a wide range of attractive home improvements indoors and out

- DECORATING MADE EASY CENTRAL HEATING
- KEEPING OUT THE RAIN LAYING A DRIVE
- GET DOWN TO FLOORS KITCHEN FITMENTS
- KNOW-HOW ON DRAINS A LOFT TO LIVE IN
- FIXING FENCES POWER TOOLS

GET YOURS AT YOUR NEWSAGENTS TODAY 2/6

speed of take-up during the recording and playback processes. In order to provide a "fast rewind" facility, a second pulley (or rubber idler wheel) is brought into action to connect to the rewind spool.

SPOOL SIZES

The smallest size of spool in common use is the "message" size of 3in. diameter. 5½in. is a size often used on popular tape recorders, while the 7in. spool is the standard for serious recording work. Semi-professional tape recorders will usually accommodate reels up to 10½in. in diameter. The size of the spool of course determines the length of play which can be achieved at one "run" of the machine. Another factor affecting total playing time is the number of "tracks" used by the recorder.

Professional machines usually employ full-width heads but the standard for domestic use has become half-track. Here the tape heads cover a little less than half the available tape width (see Fig. 10). When the recorder is being used for normal monaural work, it can therefore be reversed at the end of the run, so that the previously blank half of the tape is brought into use. The same side of the tape (the dull, coated side) must of course always be in contact with the record/play head.

For *stereophonic* use both tracks are used simultaneously, and a stereo record/play head is necessary. This type of head consists of an "upper" track and a "lower" track head stacked vertically and connected to the left and right channels of the input signal. It is of course possible to use a stereo recorder for "mono" work and if desired, music can be recorded on the upper track and speech on the lower track. On replay, the two channels can be mixed, to give the effect of a commentary with background music.

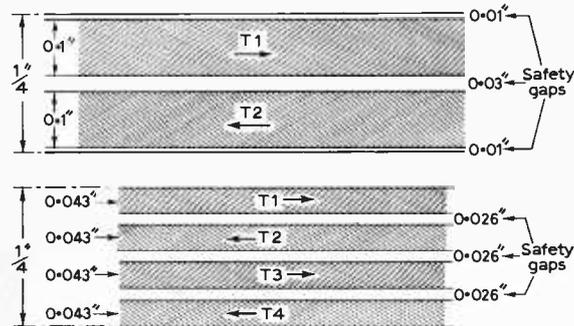


Fig. 10: The recorded track widths showing directions and safety gaps for both two and four track standards.

A further development of the normal "two track" system has been the division of each of the two tracks into two further tracks, making a total of four tracks in all (see Fig. 10). The disadvantages of the four track system are (a) the signal to noise ratio is poorer; (b) there is more likelihood of cross-interference between channels; (c) extra care is necessary over tape quality and condition because the recording area comes to the edges of the tape; (d) editing of recordings is more difficult because, wherever a cut is made, four separate recordings will be involved.

RECORDING TAPE

As has already been remarked, the standard tape

width is ¼in., and the magnetic oxide is generally backed on to clear plastic. In the earlier days of tape recording, paper tape was commonly used, and this was referred to as "craft based" tape; this had a low breaking point, and also a high noise factor due to the comparatively brittle nature of the backing. It is interesting to note that the very earliest experiments in magnetic recording employed, among other media, waxed paper impregnated with iron filings!

The cheaper variety of tape on sale today may be acetate based, and although this is generally satisfactory, the breaking point is again fairly low, and it tends to become brittle, especially in cold weather. Better quality tape has a plastic backing known as polyester, and high quality tape will also have been pre-stretched before spooling; this is known as *tensilised polyester* tape. Different varieties of tape also have their own characteristic and can vary considerably in background noise and in high frequency response. An interesting experiment is to splice together several short pieces of different brands of tape and use it to make a sample recording. The most acceptable tape can usually be spotted upon replay as the quality and sound level vary between each joined piece.

An important factor in assessing the playing time of a spool of tape is the actual tape thickness. A 7in. spool will hold 1,200ft. of standard thickness tape giving about half an hour of playing time at 7½ i.p.s. (a further half-hour is obtained when the tape is reversed). With the introduction of thinner tape backings, "long play" tape is now common, giving 45 minutes playing time. Double play tape is also available, giving one hour's playing time at the same speed, and triple and even *quadruple* play tapes are now on the market.

A SOLID STATE RECORDER

From what has already been discussed, it will be obvious that the drive and capstan mechanism constitute a piece of precision engineering which is out of the range of most constructors. Battery tape decks using capstan drive are available for around £4 however, and as the amplifier etc., can be taken from the previously mentioned spool driven machine, this constitutes virtually the only expense.

Apart from the battery connection, the only other connections which have to be made between amplifier and the tape deck consist of two leads from the record/play head on the tape deck. These are connected to the piano key switches, and in the record position the signal take-off lead (from C6) should be connected to the head via the record switch.

On replay, the record/play leads go via the play piano key to the input section of the transistor amplifier. This will have a microphone jack socket in circuit, M1, and the flying lead from the piano key is connected to the jack socket so that it connects the base circuit of TR1 via C1 when the microphone jack is removed. If it is desired to leave the microphone in the jack socket during replay, then the contacts on the play and dictate keys should be used to provide the requisite "switchover" from microphone input (on record) to head input (on replay). Erasure is automatically achieved by permanent magnet when the dictate key is depressed, and d.c. bias is provided on record via R13.

TO BE CONTINUED

P.W. GUIDE TO COMPONENTS

PART 4

M. K. TITMAN, B.Sc. (Eng)

Microphone transformers have special requirements due to the high sensitivity and impedance associated with the circuit. Great care is taken in design, and very large high inductance windings are used. The coil is usually resin potted in a cylindrical aluminium or in a quality transformer mumetal can. Lead-out wires usually protrude as flying leads. The transformers are thus fully screened both magnetically and electrically from surrounding fields. Prices are relatively high, from 15s. to £10.

Pulse and inverter transformers often use iron cored coils and for these types special methods are required. In general, thin laminations and low resistivity windings are used. Occasionally air gaps are deliberately introduced to prevent saturation, and thus extend the limits of usefulness, although this reduces the inductance.

As coils of a given power requirement reduce drastically in size as the frequency is increased, high frequency transistor inverters are used increasingly in miniature circuits. Often the inverter transformer is designed to saturate and provide the transistor switching action.

Swinging chokes are also used increasingly to cut down circuit size. These inductors decrease in inductance as the standing d.c. current through them increases. This effect is achieved by using two different core materials one of which saturates at low current, or by using an air gap in part of the core. The inductance is therefore high until saturation at which point it reduces to the portion of material which has not saturated.

Former Wound Coils

These coils are extremely common and find their greatest use in radio circuitry. The formers are made of various plastic materials such as polystyrene and generally have provision for a dust core to be inserted. The core material is of fairly low relative permeability, from 2 to 100, and therefore the inductance is low, from 0.1 μ H to 10mH. Figure 1 shows a typical former wound coil with an iron dust core. Both iron dust

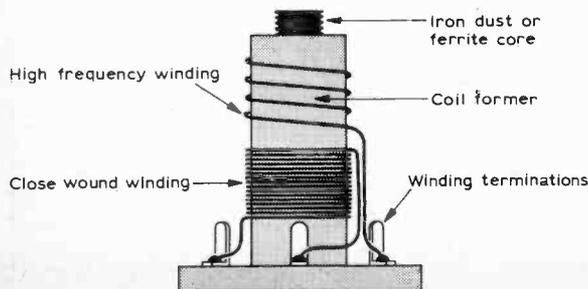


Fig. 1: Former wound coil.

and ferrite cores are used and because of the inherent air gaps they are non-saturable. The winding terminations are soldered to the pins on the base of the former, which usually provides the screw mounting holes.

These inductors and transformers are used for radio frequency chokes, aerial tuning coils and transmitter tank circuits, and are often wound by the home constructor. Because of the rather hit-and-miss methods of winding that are employed many newcomers are dismayed by coil winding. This is further aggravated by the lack of information displayed on circuit diagrams. Much information is published on coil winding and various charts and abacs can be used. One useful formula for an air-cored coil is due to J. H. Reyner:

$$L = \frac{0.2 N^2 d^2}{3.5d + 8l} \times \left(\frac{d - 2.25 D}{d} \right) \mu H \quad (1)$$

where L is the inductance, N the number of turns, d the external diameter in inches, l the winding length and D the depth of winding.

For a single layer coil the bracketed term is unity. As a very rough guide however 20-36 s.w.g. can be used from 100kc/s to 10Mc/s and 16-20 s.w.g. for coils up to 100Mc/s.

On a $\frac{1}{2}$ in. diameter former approximately 4 turns of 18 s.w.g. will give tuning with a 100pF capacitor at 30Mc/s whilst 10 turns gives 15Mc/s, 20 turns 8Mc/s and 40 turns of 30 s.w.g. gives 4Mc/s. Hence trial and error and common sense readily result in the desired coil. Cores and formers cost from 6d. to 2s. 6d.

Ranges of r.f. and oscillator coils are available from 4s. to 10s., and many people prefer to purchase coils ready wound. I.F. transformers are also wound on formers, and can be purchased between 10s. and £2 in matched pairs. These particularly require careful design since a very important factor is the Q or quality of the coils. I.F. transformers require a high Q to give good rejection of unwanted signals and to define the bandwidth. The value of Q depends on the formula:

$$Q = \frac{2\pi f L}{R} \quad (2)$$

where f is the frequency in c/s, L the coil inductance in henrys and R the dynamic (r.f. + d.c.) resistance in ohms.

The formula shows that to obtain high Q factors the ratio of inductive reactance to resistance must be high, and coils with Q factors of 100-1,000 are readily available. I.F. coils are usually screened with aluminium alloy cases and have ferrite or iron dust cores to give tuning adjustment.

The resistive portion of the formula for Q consists of both the d.c. and r.f. resistances and this is due to the skin effect. At radio frequencies the current path is

DE LUXE PLAYERS

PORTABLE CABINET AS illustrated. To fit standard 69/6 player or autochanger.

RCS AMPLIFIER 3 WATT. Ready made and tested. This is a 2-stage unit using a triode pentode circuit consisting of coupled valve circuit 3 watts output into a 3 ohm loudspeaker. Tone and volume controls mounted on chassis with knobs. Supplied with loudspeaker and valve UCL82. Frequency response 50-12,000 cps. 59/6 Sensitivity 200mV.



Post 5/8 each item

SINGLE PLAYERS MONO

BSR GU7 6v. £4.9.6
Garrard AT70 Mk I £12.9.6
EMI Junior Mats £2.9.6
Garrard BRP22 £6.9.6

AUTOCHANGERS MONO

BSR Supramil £6.9.6
Garrard AT70 Mk I £12.9.6
BSR Transcription £12.9.6
UA70 Stereo/Mono £12.9.6

All fitted LP/78 stylus and mono pickup crystal complete. Stereo/mono pickups 20/- extra except UA70

GARRARD TEAKWOOD BASE WB.1. Ready cut-out for motor 1000, 2000, 3000, EP25, AT70. GARRARD PERSPEX COVER SPC.1 for WB.1

DE LUXE STEREO GRAM CHASSIS V.H.F. M.W. SW 10-50m. SW 60-180m. Magic eye, push buttons. 6 valve plus rect. Size 16 x 7 1/2 x 6in. high. £19.19

PICK-UP ARM Complete with ACOS LP-78 GP67 and Stylus 20/6; Xial GP67 17/6; Stereo Ceramic 35/-

CRYSTAL MIKE INSERTS

1 1/4 x 1in. 6/6; ACOS 1 1/4 x 1in. 8/8; BM3, 1" dia. 9/8 MOVING COIL MIKE with Remote Control Switch 18/6

PORTABLE TRANSISTOR AMPLIFIER

PLUS DYNAMIC MICROPHONE

A self-contained fully portable mini p.a. system. Many uses—ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player, Amplifier, etc. Attractive rezine covered cabinet size 12 x 9 x 4in. with powerful 7 x 4in. speaker and four transistor one watt power amplifier plus ultra sensitive microphones. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make.



ONLY 90/- POST FREE

WEYRAD P50—TRANSISTOR COILS

RA2W 6in. Ferrite Aerial Spare Cores 9/6
with ear aerial coil. 12/8 Driver Trans. LFDT4 6/6
Ord. P50/1AC 5/4 Printed Circuit, PCA1 9/6
1.F. P50/2CC 47cfs. 5/7 J.B. Tuning Gang 10/6
3rd I.F. P50/3CC 6/6 Weyrad Booklet 2/-
Telescopio Chrome Aerials 6in. extends to 23in. 5/-
Ferrite Rods 8 x 1/2 in. 4/4; 6 x 1/2 in. 5/4

VOLUME CONTROLS

Long spindles. Midget Size 5K, ohms to 2 Meg. LOG or LIN. L/8 3/-. D.P. 5/-
STEREO L/8 10/6, D.P. 14/6.
5K. S.P. Edge type 5/4.

80 Ohm Coax 8 D yd.

SEMI-AIR SPACED 1/4 in. 20/-; 60 yd. 30/-
FRINGE LOW LOSS 1/6
Ideal 625 lines yd.

VEROBOARD 0-15 MATRIX

2 1/2 x 5in. 3/8. 2 1/2 x 3in. 3/2. 3 1/2 x 3in. 3/8. 3 1/2 x 5in. 5/2.

EDGE CONNECTORS 16 way 5/-; 24 way 7/6.

PINS 36 per packet 3/4. FACE CUTTERS 7/6.

S.R.B.Y. Board 0-15 MATRIX 2 1/2 in. wide 6d. per 3in. 3/4in.

wide 9d. per 1in.; 5in. wide 1/- per 1in. (up to 1 1/2 in.).

S.R.B.Y. undrilled 1 1/2 in. 3/4. 10 x 1in. 3/4.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides 7 x 4in. 5/6; 9 x 7in. 6/6; 11 x 3in. 6/6; 11 x 7in. 7/6; 13 x 9in. 9/6; 14 x 11in. 12/6; 15 x 14in. 15/-.

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. 6/6; 14 x 9in. 5/6; 12 x 8in. 4/6; 10 x 7in. 3/6; 8 x 6in. 2/6; 6 x 4in. 1/6.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key

1in. 10/-; 1 1/2 in. 17/8; 1 3/4 in. 19/8; 1 1/2 in. 24/-; 2 1/4 in. 44/3

1in. 18/-; 1 1/2 in. 29/6; 1 3/4 in. 29/-; 2 1/4 in. 57/3

1in. 16/9; 1 1/2 in. 19/6; 1 3/4 in. 21/6; 2in. 39/-; 1 in. sq. 36/8

Tape Spools 2/8. Tape Splicer 5/-. Leader Tape 4/8. Reuter Tape Heads for Collaro models 2 track 21/- pair.

"THE INSTANT"

BULK TAPE ERASER AND RECORDING HEAD

35/-

Post 2/6.

DEMAGNETISER

200/250 v. A.C. Leaflet S.A.E.



Minimum Post and Packing 2/6. RETURN OF POST DESPATCH. CALLERS WELCOME—CUSTOMERS FREE CAR PARK

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON

Full list 1/- Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.) Buses 133, 68 pass door. S.R. Stn. Selhurst Tel. 01-684-1665

BARGAIN STEREO/MONO SYSTEM

Attractive Slimline PLAYER CABINET with B.S.R. UA25 Deck, 4 x 4 AMPLIFIER and TWO matched LOUDSPEAKERS Carr. 10/6 £19.19.6. (Only 4 pairs of wires to join)

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V	2/3	100/25V	2/8
4/350V	2/3	250/25V	2/8
8/450V	2/3	500/25V	4/-
16/450V	3/-	8+8/450V	3/6
32/450V	3/6	8+16/450V	3/9
25/25V	1/9	16+16/450V	4/3
50/50V	2/2	32+32/550V	4/6
SUB.MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 2/-; 500, 1000mF 12V 3/8; 2000mF 25V 7/-		CERAMIC. 500V 1pF to 0.01mF, 9d. Discs 1/-	
PAPER. 350V-0-1 9d; 0-5 2/6; 1mF 3/-; 2mF 150V 3/-		500V-0-001 to 0-05 9d; 0-1 1/-; 0-25 1/8; 0-5 3/-	
1.000V-0-01, 0-0025, 0-0047, 0-01, 0-02, 1/8; 0-047, 0-1, 2/8.		SILVER MICA. Close tolerance 1%, 5-500pF 1/-; 500-2,200pF 2/-; 2,700-5,600pF 3/8; 6,800pF-0-01, mfd 6/- each.	
TWIN GANG. "0-0" 208pF+176pF, 10/8; 365pF, miniature 10/-; 500pF standard with trimmers, 9/6; 500pF		small 8-grammers, 7/6; 500pF slow motion, standard 9/-; midge 3-gram 500pF 18/9. Single "0-0" 865pF 7/8, Twin 10/-	
SHOR T WAVE. 25pF, 10pF, 50pF, 75pF, 100pF, 160pF, 200pF, 10 6c. can be ganged, Couplers 9d. each.		TUNING. Solid dielectric. 100pF, 300pF, 500pF, 7/- each.	
TRIMMERS. Compression ceramic 30, 50, 70pF, 1/-; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF, 7/6; 1000pF, 2/6.		250V RECTIFIERS. Selenium 1 wave 100mA 5/-; BY10010/-	
CONTACT COOLED 1/2 wave 80mA 7/6; 85mA 9/6.		Full Wave Bridge 75mA 10/-; 150mA 19/8; TV rect. 10/-	
NEON PANEL INDICATORS. 250V. AC/DC. 3/8.		RESISTORS. Preferred values, 10 ohms to 10 meg.	
1w. 1/4, 1w. 20/-; 3d. 1/8; 5d. 2/8; 1/2w. 10/-; 1w. 10/-; 2w. 10/-		HIGH STABILITY. 1w. 1/2, 10 ohms to 10 meg. 2/-	
Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.		5 watt 0-5 to 8-2 ohm 3w. 2/-	
10 watt 10 watt 2/-		WIRE-WOUND RESISTORS 2/-	
15 watt 10K, 15K, 20K, 25K, 30K, 10W 3/-		FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 amp. 8/9; 2a., 11/8; 4a., 17/6.	
CHARGER TRANSFORMERS. P. & F. 5/-; Input 200/250v. for 6 or 12v., 1/4 amps., 17/6; 2 amps., 21/-; 4 amps., 30/-		WIRE-WOUND 3-WATT WIRE-WOUND 4-WATT	
T.V. Type. Values 10 ohms to 30K. 4/6		STANDARD SIZE POTS. LONG SPINDLE. 50 OHMS to 100K. 7/6	
Carbon 20K to 2 meg. 2/6		VALVE HOLDERS. 9d. CERAMIC 1/-; CANS 1/-	

NEW MULLARD TRANSISTORS 6/- each

OC71, OC72, OC81, OC44, OC45, OC171, OC170, AF117

REPNACO TRANSISTOR TRANSFORMERS

TT45. Push Pull Drive, 9 CT, 6/-, TT46 Output, CT8, 1, 6/-

TT49. Interstage 20, 4, 6/-; TT52 Output 3 ohms, 4, 5, 1, 6/-

TT53/4 PAIR. 10W amp. Transformers and circuit 45/-

TRANSISTOR MAINS POWER PACKS. FULL WAVE

9 volt 500mA Size 4; 2 x 2.2uF Output terminals. 49/6

Switched. Metal case, crackle finish. On/off switch.

Half Wave 9 volt 50mA Size 2 x 1in. Snap terminals 32/6

9 volt 500mA TRANSFORMER ONLY. 2 x 1 1/2 x 1 1/2 in. 10/6.

MAINS TRANSFORMERS

250-0-250 50 mA. 8.3v. 2a. Centre tapped. 19/6

250-0-250 80mA. 6.3v. 3.5a. 8.3v. 1a. or 5v. 2a. 30/-

350-0-350 80mA. 6.3v. 5.5a. 6.3v. 1a. or 5v. 2a. 35/-

300-0-300 120mA. 6.3v. 3.5a. C.T. 8.3v. 2a. 45/-

MINIATURE 200v. 20mA. 6.3v. 1a. 2 1/2 x 1 1/2 in. 12/6

MIDGET 220v. 40mA. 6.3v. 2a. 2 1/2 x 2 1/2 in. 17/6

HEATER TRANS. 6.3v. 1a., 8/6; 6.3v. 4a. 12/6

Ditto tapped sec. 1.4v., 2.3, 4, 5, 6.3v. 1 amp. 12/6

GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 8, 9, 10, 12, 15, 18, 24, 30, 40, 48, 60 35/-

1 amp. 6, 8, 10, 12, 16, 18, 24, 30, 36, at 2a. 60 35/-

3 amp. 0-12v. and 0-18v. 19/6

AUTO TRANSFORMERS 0-115-230v. Input/Output, 30w. 18/6; 150w. 30/-; 500w. 92/6; 1000w. 175/-

COAXIAL PLUG 1/8. PANEL SOCKETS 1/8. LINE 2/-

OUTLET BOXES. SURFACE OR FLUSH 4/6.

BALANCED TWIN FEEDERS 1/8 yard 80 or 300 ohms.

JACK SOCKETS 3d. open circuit 2/6, closed circuit 4/6.

Chrome Lead Socket 7/6. Phono Plugs 1/4. Phono Socket 1/4.

JACK PLUGS Std. Chrome 3/-; 3.5mm Chrome 2/8.

DIN SOCKETS Chassis 3-pin 1/8; 5-pin 2/-.

DIN SOCKETS Lead 3-pin 3/6; 5-pin 5/-.

WAVE-CHANGE SWITCHES WITH LONG SPINDLES.

1 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/8 each.

1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 4/8 each.

Wavechange "M.A.R." 12-way 12/-; 2 p. 6-way 3 p. 4-way.

4 p. 3-way, 6 p. 2-way, 1 waf. 12/-; 2 waf. 17/-; 3 waf. 22/-.

Additional wafers 5/- each water up to 12 max.

TOGGLE SWITCHES, sp. 2/8; sp. dt. 3/8; dp. 3/6; dp. dt. 4/6.

MINI-MODULE LOUDSPEAKER KIT


10 WATT 55/- Carr. 8/-

Triple speaker system combining on ready cut baffle. 1in. chip-board

15 x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover

condenser. The heavy duty 5in. Bass Woofer unit has a low bass resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm

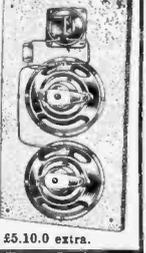Teak Veneered Bookshelf Enclosure £5.10.0 extra.



BAKER 12in. DE-LUXE MKII LOUDSPEAKER

Suitable for any Hi-Fi System. Provides truly rich sound recreating the musical spectrum virtually flat from 25-16,000cps. Latest double cone with special "Feroba" ceramic magnet. Flux density 14,000 gauss. Bass resonance 32.38cps. 15W British rating. Voice coils available 3 or 8 or 15 £9 Post ohms. Free 48 page Enclosure Manual 5/9 post paid



BAKER "GROUP SOUND" SPEAKERS—POST FREE

"Group 25" "Group 35" "Group 50"

12in. 6 gns. 12in. 8 1/2 gns. 15in. 18 gns. 25w. 35w. 50w.

ALL MODELS "BAKER SPEAKERS" IN STOCK

Super Cone Tweeter 2 1/2 in. square, 3-17kcs. 10W 17/6.

Quality Horn Tweeters 2-18kcs. 10W 23/6. Crossover 16/6.

LOUDSPEAKERS P.M. 3 OHMS 2 1/2 in. 3in. 4in. 5in. 7 x 4in.

15/8 each; 8in 27/8; 6in 22/8; 10in 37/8; 8 x 3in. 21/-; 12in.

Double cone 3 or 15 ohm 35/-; 10 x 6in. 30/-.

E.M.I. Double Cone 13 1/2 x 8in., 3 or 15 ohm models, 45/-, or with twin tweeters, crossover and H/D magnet, 79/6.

SPECIAL OFFER! 8 ohm 2 1/2 in. 6 x 4in.; 8 ohm 2 1/2 in. 2 1/2 in. 25 ohm 6 x 4in. 35 ohm 8in. 15/6 EACH 15 ohm, 10 x 2 1/2 in. 7 x 4in.

5/6 TYPE 15 ohm, 10 x 2 1/2 in. 8 or 15 ohm 8in. 8/6.

15in. WOOFER. 8 watts max. 30-10,000 cps. 8 or 15 ohm 39/6.

OUTPUT TRANS. EL84 etc. 4/6; MIKE TRANS. 50.1, 3/6.

SPEAKER FRET Various Tyan samples. Send S.A.E.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms General Purpose... 19/6

H.R. HEADPHONES 2000 ohms Super Sensitive... 35/-

LOW RESISTANCE HEADPHONES 8-5 ohm... 35/-

DE LUXE PADDED STEREO PHONES 8 ohms... 79/6

MINETTE AMPLIFIER

A.C. Mains Transformer. Chassis size 7 x 8 1/2 x 4in. High. Valves ECL82, E280. Quality output 3 ohm. With entranced fascia, valves, knobs, volume and tone controls, wired and tested. 12 month guarantee. Post 5/8



69/6

ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES

BARGAIN AM TUNER. Medium Wave. 79/6

Transistor Superhet. Ferrite aerial, 9 volt.

BARGAIN DE LUXE TAPE SPLICER Cuts, trims, joins for editing and repairs. With 3 blades. 17/6

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with special tone controls into single output, 9 volt. 59/6

BARGAIN FM TUNER 89-108 Mc/s Six Transistor. Ready built. Printed Circuit. Cuttered slide dial. tuning. Size 6 x 4 x 2 1/2 in. 9 volt. £6.19.6.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. 69/6

45-PAE EAGLE CATALOGUE 5/- Post Free

★ RADIO BOOKS ★ (Postage 9d.)

Practical Transistor Receivers 5/-

Practical Stereo Handbook 3/8

Supersensitive Transistor Pocket Radio 3/8

High Fidelity Speaker Enclosures and Plans 5/6

Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- No. 5 ea. 6/8

Practical Radio Inside Out 4/8

Shortwave Transistor Receivers 5/-

Transistor Communication Sets 6/8

Modern Transistor Circuits for Beginners 7/8

Sub-Miniature Transistor Receivers 5/8

Wireless World Radio Valve Data 9/8

At a glance valve equivalents 5/8

Valves, Transistors, Diodes equivalents manual 10/6

How to receive Foreign T.V. programmes on your set by simple modifications 5/-

SANGAMO 3 inch SCALE METERS

Various calibrations/movements, 500 Microamp; 1 Milliamper; 50-500 Microamp, etc. S.A.E. for list. 45/-

POCKET MOVING COIL MULTIMETER

0-1,000 AC/DC. ohms 0 to 100k, etc. 49/6

SUPERIOR MOVING COIL MULTIMETER 0-2-500V D.C. 20,000 ohms per volt, 0-1,000V A.C. Ohms 0 to

PEAK SOUND


Aids to economical high fidelity

ES/10-15 BAXANDALL SPEAKER

"A
thoroughbred"

SAYS
RALPH WEST
HI-FI NEWS
OCTOBER, '68

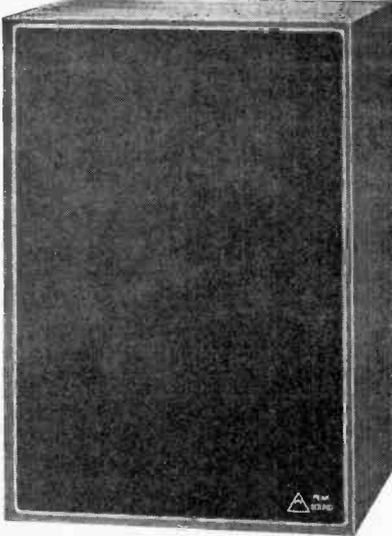"The immediate impression was of a thoroughbred speaker, smooth and effortless... voices were uncannily real. Once again we see the possibility of Rolls Royce standards... when you know how."




A revolutionary advance in design logic

We can only quote briefly from the report in *Hi-Fi News* which goes thoroughly into the merits of this remarkable loudspeaker. We supply the kit exactly to the specifications described by the designer, P. J. Baxandall in *Wireless World* (Aug. and Sept.). These designer-approved Peak Sound Kits come ready for instant assembly. Frequency range—60 to 14,000 Hz (100–10,000 Hz ± 3 dB); impedance—15 ohms; loading up to 10 watts R.M.S.; size 18" x 12" x 10". Here indeed is quality performance of a very high order for a very modest outlay. Equaliser assembly 36/- (p/p 1/6); Speaker unit 38/- + 8/11 P/T (p/p 5/-); Teak finished cabinet assembly £6.3.6 + 12/8 P/T (Carr. 8/6). Cross-over choke for additional woofer. £1.2.6 (p/p 2/6).

£9.17.6

+ 21/7d. P/Tax.
(Carr. in U.K. 11/6)

A new Peak Sound Power Amplifier

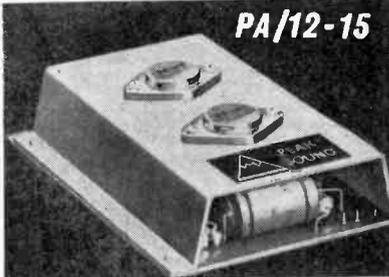

THE PEAK SOUND PA/12-15 (12 watts R.M.S. out into 15 Ω) is for the constructor who appreciates both sensible design and genuine power and hi-fi performance. Available built or in kit form. Response 10 Hz – 45 KHz ± 0.5 dB. Distortion at max. output –0.1%. 43 dB neg. feed back. Size 5" x 3 $\frac{3}{8}$ " x 1 $\frac{3}{8}$ ". With full instructions. Pre-amp. details available.

BUILT AND TESTED **£5.19.6** Kit less heat sink and board **£3.19.6** Heat sink 6/- (p/p built or kit, 2/6) (p/p 1/6)

From your dealer or direct in case of difficulty.
PEAK SOUND (HARROW) LTD., 32 St. Judes Road,
Englefield Green, Egham, Surrey Telephone: EGHAM 5316

TO PEAK SOUND

Please send (post free)

for which I enclose £.....s.....d

NAME

ADDRESS

Block letters please PW369

The professional touch

A really professional training—that's what you get in the Army. 15 months course in electronics with the Royal Signals (for instance) with the most modern equipment and the best instructors soon makes the whole business second nature to you. And quite apart from setting you up for life, it'd give you a good deal of pleasure. Because Army life's varied enough to make every day full of interest. Look into it. If you're between 17 and 30 it's wide open to you.



For all the facts send off this coupon

TO: ARMY CAREERS MP6(A),
LANSDOWNE HOUSE, BERKELEY
SQUARE, LONDON W1X 6AA
PLEASE SEND ME THE
LATEST FREE ARMY LEAFLET.

M70994401

NAME

ADDRESS

TOWN

COUNTY

DATE OF BIRTH

(You must be a resident in the U.K.)



confined to the surface layers of the conductor and hence the resistance tends to increase. In order to limit this effect in high Q circuits the conductor is often silver plated, or with multi-turn coils Litz wire is used. Litz wire consists of a number of thin conductors bundled together. This has the result of increasing the surface area and thus giving lower r.f. resistance values.

Many radio circuit coils are now made in ultra miniature form for mounting directly on printed circuits. As these versions are only slightly larger than the average transistor they have great application in miniature receivers. They are available in sets consisting of r.f., oscillator and two i.f. coils from 15s. to £3.

Self-supporting Coils

Commonly v.h.f. and transmitter power coils are self-supporting. As the frequencies are high the number of turns is small, and in order to reduce skin effect large diameter conductors of 12-18 s.w.g. are used. The better quality coils are silver plated to further reduce the r.f. resistance.

The home constructor usually winds these coils around a tube and experiments to obtain the correct inductance. Most f.m. circuits give details of any coils to be wound. Lack of information should not deter the novice, for experiment is simple and 20 turns of 16 s.w.g. wound on a pencil and then chopped gradually to give the required inductance is usually successful.

For transmitter coils $\frac{1}{2}$ in. copper tubing is often used, and many varieties are available on the market. Variable types with sliding contacts are available and silver plating is common. These coils are fairly large, 6 x 2in. in diameter or more, and reasonably expensive, from £1 to £10. When building these coils it is as well to remember that porcelain supporting members should be used as sparingly as possible since high r.f. power results in great stress in the material.

Ferrite Pot Cores

A very wide range of core types and mountings is produced. An average form of core is shown in Fig. 2. The coils are wound on a small plastic bobbin, and end wires left protruding 5-6 inches out of the bobbin. This is slipped over the centre spindle of the half-core and the other core located on the top. The end connections are located in grooves in the cores. The core is rigidly held by a metal clamping assembly which usually incorporates the terminals for end connections. The coils are mounted on the circuit by one or more bolt connections.

Ferrite cores are designed for use in the general range 1kc/s to 15Mc/s for both inductors or trans-

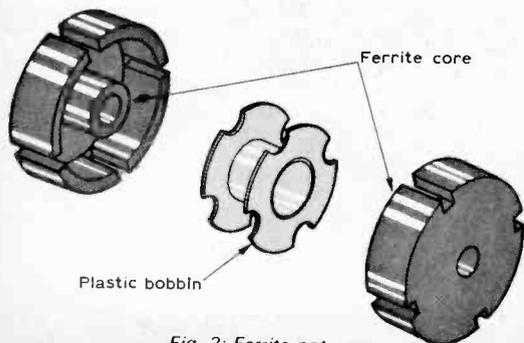


Fig. 2: Ferrite pot core.

formers and the number of turns for 1mH inductance varies from 20 to 250. As the permeability varies from 20 to 400 they are not as effective as iron cores at low frequencies but due to the inherent air gaps in the material they tend to be non-saturating. They have no eddy current losses whilst hysteresis losses are kept to a minimum.

Ferrite core inductors and transformers are used from audio frequencies to r.f. as low power transformers, filtering inductors, tuned loads, oscillator transformers, thyristor trigger transformers, etc. Most circuits give details of the winding of transformers and the type of core to be used. However, the design is readily modified to suit existing cores by adjusting the winding to give the correct frequency, inductance and turns ratio. The costs vary from 10s. to £4, depending on the fittings used.

Ferrite Rods

Ferrite rod cores are used extensively in modern transistor receivers as the aerial coil circuit up to 20Mc/s. They consist of ferrite material in rod form of approximately $\frac{1}{8}$ in. diameter and from 4 to 10in. long. The rods are available at 1s. to 5s. each. In common with the alternative former wound coils the number of turns is dependent on the frequency range (waveband) to be covered. The rods have a permeability of between 10 and 25, which increases with length up to approximately 10in.; the resulting Q factors are from 100 to 500. Figure 3 shows the construction of a ferrite rod aerial with coils wound for medium and long waves.

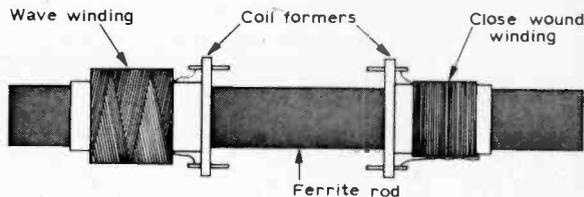


Fig. 3: Ferrite rod aerial.

Table 1: Ferrite Rod Aerial Windings

Waveband	Frequency	Turns	Wire type	Winding form
Long	250kc/s	175	Litz 9-strand	Wave
Medium	1Mc/s	54	Litz 22-strand	Close
Short	10Mc/s	6	22 s.w.g.	1in.
Short	20Mc/s	4 $\frac{1}{2}$	22 s.w.g.	1in.

The coils are wound on card formers with terminals for the coil termination. Using a tuning capacitor of 500pF the winding details are as given in Table 1. The long wave coil is wave wound in which the turns cover the entire length of the coil many times. Close wound coils are wound with each turn in close proximity to the last. Short wave windings are open, and cover the full 1in. with 4 $\frac{1}{2}$ to 6 turns.

When the coils are wound the receiver is lined up and tuned by adjusting the coil positions relative to the ends of the rod. The card formers are then fixed in position with drops of wax.

Toroids

Ferrites, iron dust and iron cores are available in toroidal form. The advantage of this construction is that stray magnetic fields are held to a minimum.

Mechanical winding of toroids is more difficult than bobbin coils and therefore they tend to be slightly more expensive.

Toroids are used for filters, magnetic stores, magnetic amplifiers, saturating inverter coils, pulse transformers, etc. A typical toroid is shown in Fig. 4.

Ferrite and iron dust cores are usually pre-moulded and ceramic covered whilst iron cores are made of iron alloy tape wound in a reel and surrounded by a plastic cover to protect the windings. Windings are usually of enamel covered wire covered with tape. The coils are either mounted directly with the coil terminations as flying leads, or the whole is resin encapsulated in a metal container and connections made to terminals or printed circuit pins projecting through the casing.

Ferrite and dust toroidal cores can be obtained readily at 1s. to 5s. each, and inductance information is usually supplied. They are very suitable for differentiating and trigger transformers for switching thyristors and power circuits. Trial and error will produce the required transformer, whilst the inductance required can be calculated from the pulse width, voltage and current using the formula:

$$V = -L \times \frac{di}{dt}$$

$$\text{or } L = -\frac{V\tau}{\Delta I} \quad (3)$$

where L is the coil inductance, V the voltage across the winding (volts), τ the pulse width (secs) and ΔI the change of current (A).

Recapitulation and Future Trends

We have seen that the range of coils manufactured is wide and the construction and materials are dictated largely by circuit requirements. Standard coils are

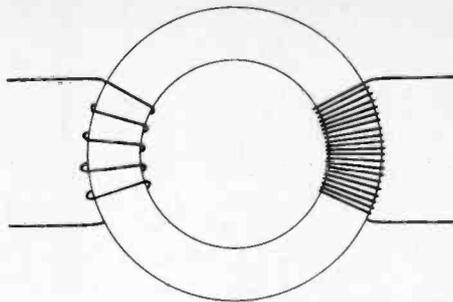


Fig. 4. Toroidal transformer.

available for most applications but are difficult to obtain for unorthodox or new requirements. Prototype coils are built as a service by most manufacturers but these are expensive and take between 2 and 6 months to make. Therefore the only solution for the home constructor is to wind and build his own coils using available materials.

In general, satisfactory coils can be reconstructed with a very limited knowledge of coil design. The main requirement is common sense and trial and error. The novice to coil design, once he takes the plunge, is often surprised at the simplicity of obtaining the desired results. They may not always be ideal in design but will fill the bill, which is all that matters.

Future trends will be towards even greater diversity of coil type, especially in the field of switching, inverter and pulse circuits. Power supplies, which at present are limited in size by the large mains transformer, will reduce in size as high frequency switching supplies take over. Most coils will reduce in size as better materials become available.

TO BE CONTINUED

In the March issue of

PRACTICAL TELEVISION

★ PRACTICAL AERIAL DESIGN

Start of a new series explaining aerial design and characteristics. Construction is dealt with in a practical way indicating the dimensions that are critical and those that are not, with simple formulae for calculating the dimensions for particular channels. Both v.h.f. and u.h.f. designs will be featured.

★ VIDEO AMPLIFIER

Details of a simple video amplifier for use with a photo-multiplier tube in our flying-spot scanner. Also details of the receiver modifications required for scanning and display.

★ WORKSHOP HINTS

Start of a new series providing useful hints and guidance on workshop techniques. The opening part deals with the practical problems of faulty transistor diagnosis and replacement, how to remove excess solder from printed panels and techniques for temporarily bridging components.

★ VALVE AND COMPONENT OVERHEATING

Many TV faults cause valve or component over-heating. Do you know exactly what can be deduced and what remedial action to take? This article provides a systematic guide to fault diagnosis when confronted with the symptom of overheating.

★ DISCOVERY OF CATHODE RAYS

The cathode-ray tube was one of the first thermionic devices and played an important part in the development of electronic theory. This account of early experiments provides a lively introduction to electronic phenomena.

★ POWER SUPPLY TESTING

Gordon J. King continues his treatment of this subject by telling how to test the h.t., boost h.t. and e.h.t. supplies in television receivers. He also takes a look at the use of silicon rectifiers for voltage dropping and colour receiver supplies.

ON SALE FEBRUARY 21st.

SINCLAIR Z.12

12 WATT INTEGRATED HI-FI AMPLIFIER & PRE AMP



12 watts R.M.S. continuous sine wave output.

This is the recommended amplifier for those requiring great power versatility and reliability. This eight transistor amplifier is the most successful of its kind ever designed. It has an excellent power to size ratio and is easily adapted to a wide variety of applications. The Z.12 performs satisfactorily from a wide range of voltages and it can easily be run from car batteries. This true 12 watt amplifier comes to you ready built, tested and guaranteed together with useful manual of circuits and instructions for matching the Z.12 to your precise requirements. Two may be used for stereo, when the Sinclair Stereo 25 will be found the ideal control unit for use with it.

Size—3in x 1½in x 1½in. Class B Ultralinear Output: Frequency response from 15 to 15,000Hz ±1dB: Output suitable for loudspeakers from 3 to 15 ohms impedance. Two 3 ohm speakers may be used in parallel: Input 2 mV into 2K ohms: Output 12 watts R.M.S. continuous sine wave (24 watts peak); 15 watts music power (30 watts peak) Power requirements 6—20V d.c. from battery or PZ.4 Mains Supply Unit. Ready built, tested and guaranteed.

89/6

SINCLAIR STEREO 25

De Luxe Pre-amp and Control Unit for use with Z.12 Stereo assemblies. Switched inputs for P.U. (equalised to R.I.A.A. curve from 50 to 20,000 Hz ±1dB), Radio and auxiliary. Supplied ready built with very attractive solid brushed and polished aluminium front panel. Control knobs for Bass/Treble/Volume/Balance/Input are solid aluminium. Size—6½ x 2½ x 2½in plus knobs. Built, tested and guaranteed.

£9.19.6




SINCLAIR PZ4

STABILISED MAINS POWER SUPPLY UNIT

Heavy duty transistorised power supply unit to deliver 18V d.c. at 1.5A. Designed specially for use with two Z.12 Amplifiers together with Stereo 25. Built, tested and guaranteed.

99/6

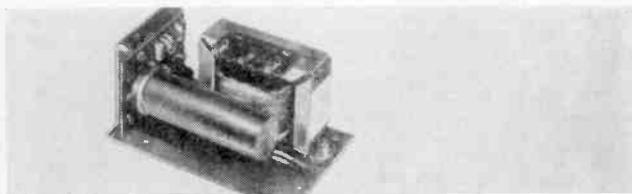

sinclair

SINCLAIR RADIONICS LTD, 22 Newmarket Road, Cambridge. OCA-3 52731

SINCLAIR MICROMATIC



The world's smallest radio

This fantastic little British pocket receiver is available in kit form to build for yourself or ready built, tested and guaranteed. Its range and selectivity must be experienced to be believed; its power and quality everything you could want. The Micromatic tunes over the medium wave-band and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier; in fact, you will find your Micromatic performing where other sets cannot be heard at all. The neat black case with aluminium front panel and tuning control give the Micromatic elegantly modern appearance.

- High quality magnetic earpiece
- Choice of many stations
- Plays anywhere

Kit in fitted pack with earpiece, solder and instructions. **49/6**

Built, tested and guaranteed. **59/6**

Mallory Mercury Cells RM.675 (2 reqrd) each 2/9



SINCLAIR Q.14

the most challenging loudspeaker design in years

It is more than a matter of saving money when you choose the Q.14. This is the loudspeaker that delights experts and critics alike for its fine forward quality, its clarity and exceptional adaptability. Designed on original lines and from unusual materials, the Q.14 will easily carry up to 14 watts and has very smooth response from 60 to 16,000 Hz. Size—9½ in square x 4½ in deep, with matt black finish and solid aluminium bar embellishment. Input impedance—8 ohms.

The Q.14 costs about a quarter of what you might expect to pay for a good stereo speaker system. A pair used with two Z.12s and the Stereo 25 will give you superb high fidelity to stand comparison with far costlier equipment.

Try the Q.14 in your own home without delay. If it does not delight you, send it back and your money including cost of postage will be refunded in full.

£7.19.6

THE SINCLAIR Q.14 LOUDSPEAKER has a seamless sealed acoustic pressure chamber contoured to ensure forward sounding presence and wide dispersal of sound. The driver unit employs a massive ceramic magnet, special cone suspension and aluminium speech coil resulting in brilliant transient response. The input impedance of 8 ohms makes the Q.14 particularly suitable for use with transistor amplifiers. It can be used as a bookshelf speaker, a corner reflect or flush mounted on any appropriate flat surface, etc.

GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question. Full service facilities available to all purchasers.

ORDER FORM BRINGS PROMPT DELIVERY SENT TO YOU POST PAID

To: SINCLAIR RADIONICS LIMITED 22 NEWMARKET ROAD, CAMBRIDGE.

Please send POST FREE

NAME

ADDRESS

For which I enclose cash/cheque/money order.

PW.369

sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET ROAD,
CAMBRIDGE OCA-3 52731

TRANSISTORS etc.

AC107	3/-	OC28	8/6
AC126	2/-	OC35	7/6
AC145	3/-	OC44	2/0
AC147	4/-	OC45	2/0
ACY19	3/9	OC70	2/3
ACY21	3/9	OC71	2/3
AF115	3/-	OC72	2/3
AF116	3/-	OC73	2/3
AF117	2/9	OC75	2/2
BFY18	4/6	OC81	2/-
BFY51	4/-	OC81D	2/-
BBY26	3/-	OC82D	2/3
BBY28	3/9	OC140	5/-
BBY65	3/-	OC169	3/6
BSY85A	2/6	OC170	2/2
GRT113	2/6	OC171	2/2
OA5	1/8	OC200	4/6
OA9	1/8	OC202	4/6
OA81	1/8	OC203	4/6
OA85	1/8	OC204	5/6
OA91	1/9	OC204	5/6
OC23	6/6	TK22C	1/6
OC25	5/-	2N743	4/6
OC26	5/-	2N753	2/9

SILICON DIODE

RECTIFIERS	
BY100 800 piv	2/10
New 500 mA	
250 piv	1/9
Avalanche 11A	3/6
1200 piv	1/9
Six Amp Series	4/8
BYZ1 300 piv	3/6
BYZ12 600 piv	4/6
BYZ11 900 piv	5/6
BYZ10 1200 piv	5/6
Mullard Stack FW	
Bridge	
12A 100 piv	39/6 (3/-)
OC140	5/-
OC169	3/6
OC170	2/2
OC171	2/2
OC200	4/6
OC202	4/6
OC203	4/6
OC204	5/6
TK22C	1/6
2N743	4/6
2N753	2/9

Midget Electrolytic

Conds. Wire Ends	
At 6d. each	
0.8µF	25 volt
1µF	275 volt
2µF	150 volt
4µF	150 volt
640µF	2.5 volt
At 9d. each	
2µF	300 volt
4µF	12 volt
8µF	12 volt
10µF	25 volt
15µF	18 volt
30µF	10 volt
30µF	6.4 volt
100µF	6 volt
125µF	4 volt
At 1/- each	
16µF	250 volt
50µF	10 volt
100µF	12 volt
320µF	10 volt

Crystal Diodes—6 for 2/6 (7d.).

Also 8µF 350V 1/2, 25µF 25V 1/3 and 50µF 50V 1/9. Other electrolytics in current list.

Postage, Packing and Insurance all above 7d. up to 3/- from 4-11; 12/- and over paid.

2 GANG VAR. CONDENSER: Mod., small, air-spaced, .0005 ea. sec. 5/- (12/- and over paid).

TRANSFORMERS: Sub-min. Output (3Ω for OC72 etc.) and Driver 2/6 (each 6d.).

MULTIMETER: 20,000 Ω/v. D.C., 10,000 Ω/v. A.C. 0-5/250/500/1K volts (D.C. 0-10/50/100/500/1K volts A.C. 0-50/142/500/2500mA D.C. 0-0.6K/0.6 meg Ω 10µA/100µA/1mA).

TEST LEADS and INSTRUCTIONS. Over-load protected 1969 model with every refinement. £4.76 (2/6). JUNIOR MODEL at 35/- (1/6) 1000Ω/v. described in free list.

SOLDERING IRON. 80W Mod. British High speed. 8 1/2". All parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use. 19/6 post free. GUN TYPE. Built in transformer for instant power, 45/- (4/6).

DIAMOND STYL: Replacements for TC8LP, FC8/Stereo, TC8LP/Stereo, Studio 'O', BP401/P, Ronette, GC2, GC3, GP47, all at 7/6 each. Also GP91-LP/8 at 13/6. SAPPHIRE STYL. All these types, also GP37 at 3/3. GP91 at 6/9 (6d. each all types). No 78 rpm available in diamond or sapphire.

PICK-UP CARTRIDGES. All fitted Styl and Standard fittings. Mono GP67/2, 13/6. Mono de Luxe GP91/2, 17/-.

Stereo—Compatible—Mono which also plays Stereo records monaurally with min. wear. GP91/SC, 19/6. Latest Stereo GP93, 23/-.

Ceramic Stereo, top quality for expensive outfits. GP94, 35/6 (all 1/-).

PP3 ELIMINATOR (A.C.) 17/6. (1/8) TWO STATION TRANS. INTER-COM. Excellent baby alarm. Instant. easy fitting. All you require 32/6 (3/-).

FOUR TRANSISTOR 3 WATT AMPLIFIER 2 1/2 x 2 1/2 x 1 1/2: 9v. 8Ω and 16Ω, excellent on 3Ω speakers. 45/6 (1/6).

HIGH POWER AMPLIFIER, transistorised, batt. op. Fitted in seconds—leaves both hands free when phoning 52/6 (1/6).

Extra High Torque MINI-MOTOR, 4 1/2 to 12v, 1 1/2 x 1/2 in 5/- (9d.). 9,000 r.p.m.

Mech. REV. COUNTER to 999, long spindle, reset wheel, for T/recorders etc. 4/6 (1/-).

BATTERY CHARGERS: Small, sturdy, neat; 2 amp. 12v. 35/-; 6v/12v 39/- (4/6 either type). Larger British 6v and 12v with meter, fuse, etc. 42/6 (6/-). All absolutely complete (4/6 either type).

RECORDING TAPE: Finest quality British Mylar. STANDARD: 5in. 600ft. 7/3. 5 1/2in. 800ft. 8/9. 7in. 1200ft. 11/3. LONG PLAY 5in. 900ft. 10/-. 5 1/2in. 1200ft. 11/3. 7in. 1800ft. 18/- (1/3 rest). Other types in our list.

MICROPHONES—CRYSTAL. MIC91, Cream, 16/3; MIC45, curved hand grip 17/3; Stick "60" 20/3; Stick "39" 26/6 (1/6 each type). Desk plastic hand type 7/6, or with "strut" stand, switch and 2 leads with 2.5 and 3.5 plugs 11/-, or with single lead, no plugs. 8/9 (1/3 each type). Lapel (or hand) with clip 6/6 (1/-). Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands. 25/- (1/6). DYNAMIC: Cream hand/table neck cord and adaptor to fit standard floor stands. 25/- (1/6). PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).


PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

PIEZO 20K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).

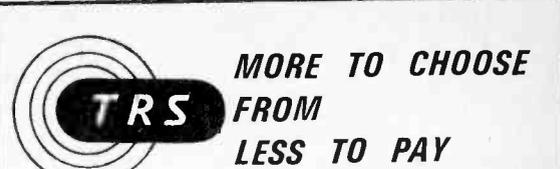PIEZO 50K Ω, similar, but fixed on flexible Swan neck to switch-fitted base. 42/6 (2/6).



A NEW DE-LUXE FM MONO/STEREO TUNER FROM TRS

- A.F.C. & A.G.C.
- Noise Limiter
- Chassis Ready Built
- pre-tuned

Kit to make MONO tuner inc. chassis and tuning assembly (p.p. 3/6) 15 gns.
Add-in Stereo Unit (p.p. 2/6) 10 gns.
Power Unit (p.p. 2/6) £2.50
Simplex Cabinet (p.p. 2/6) £1.17.6

This advanced design commutable Hi Fi mono/ stereo FM tuner comes in easy-to-assemble pre-fabricated units engineered to the highest standards of efficiency and performance. Valuable refinements include switchable A.F.C., automatic noise suppression, flywheel tuning, stereo indication light, excellent audio response. Sensitivity better than 5 microvolts. Stereo can be added later if so requested. Inclusion of a world famous Gorler I.F. amplifier ensures superb performance. Excellent chassis design made specially to fit the standard TRS Simplex cabinet system. Styled to match the TRS Stereo 4-4.

S.A.E. brings full details.

Total Price (for mains operation) £29.10.0 (Carriage 10/-).

TRS STEREO 4-4 INTEGRATED AMPLIFIER

A T.R.S. design based on newly developed Mullard 4 watt modules with BC108 pre-amp. Suitable for speakers from 3 to 15 ohms. Bass and treble cut/boost. Response—60 to 14kHz ±3dB. This excellently engineered layout requires only wiring between controls and modules. Complete with metal chassis and T.R.S. 4 pins. DIN plugs and simplex lead-ended cabinet for instant assembly. Stereo/Mono and Radio/PU switches. Amplifier Kit £7.10.8 Complete kit inc. cabinet/ power pack/ DIN plugs and sockets £12.10.0
T.R.S. Power Unit £2.5.0 (p.p. 2/6)
T.R.S. Simplex Cabinet, £1.17.6 (p.p. 2/6)
4 pins. DIN plugs and sockets if purchased separately. 15/-

PLAYING UNITS BY GARRARD AND E.M.I.

LM3000 Record Player with 9T.A. Stereo Cartridge. £10.15.0.
AT.60 Mk. II De-Luxe Auto-changer, die-cast turntable. Less cartridge. £13.17.6.
SP.26 De-Luxe single record player, die-cast turntable. Less cartridge. £12.10.6.
Brand new in makers' cartons. Packing and carriage on any of above 7/6.
GARRARD PLINTH W.B.I. In the 7in. Feak for above units. (Packing and carriage 5/-) 67/6.
Clear-view rigid perspex cover (carriage 4/6). 65/-.
CARTRIDGES FOR ABOVE STEREO: Sonotone 9T.A./HC Ceramic with diamond 52/6; Decca Deram with diamond 95/-; MONO Accos GP91-1 22/6; Goldring MX2M 27/6.
EMI 4-sp. single player. 10 1/2in. T/table, separate arm and T/O cart. 72/6 (p.p. 5/-).

MAKE A BOOKSHELF SPEAKER

With a set of matched speakers and cross-over from TRS. Comprises modern style high efficiency 5in. bass unit with special cone assembly, X-over and 2 1/2in. tweeter for mounting into your own cabinet or built-in system. Smooth response from 80 to 20,000Hz. Loading up to 6 watts. Made by a world-famous manufacturer. A genuine bargain for only 79/6 (arr. 5/-).

SKELETON PRESETS for P/circuit use. 100 ohms—2.5 Meg. 2/0-2/6.
STANDARD W/OUND W/OUND POTS. Long Spindle. 100 ohms—5000 ohms. each 6/-.
100,000 ohms each 6/9.
VOLUME CONTROLS 1 1/2in. dia. Long Spindles. Famous make. All values 5000 ohms—2 Megohms. Guaranteed 12 months. Log or Linear tracks. Less Sw. 3/6. DP Sw. 5/-.
Centre Tapped 4 Megohm Log, 1 Megohm less Sw. 5/-.
TWIN GANGED STEREO 1 1/2in. dia., Long Spindles. All values 5000 ohms to 2 Megohms less Sw. ea. 8/6. All values 100k to 2 Megohms with DP Sw. ea. 10/6.
STEREO BALANCE CONTROLS Log/Anti-Log 5K, 10K, 1/2 Meg. 1 Meg., 2 Meg. ea. 3/6.
VEERBOARD—All standard sizes including 2 1/2 x 5in., 3/8; 2 1/2 x 3 1/2in., 3/4; 3 1/2 x 5in., 5/2; 3 1/2 x 3 1/2in., 3/8; 2 1/2 x 1 1/2in., 12/8. All accessories and tools in stock.
"CIR-KIT" Adhesive copper strip for circuit building (60in. spool, 1/4in., 2/-).
RESISTORS—Modern ratings, full range 10 ohms to 10 megohms, 10%, 1-1 w., 4d. ea.; .5% Hi-Stab. 1/4 w., 6d. ea. (below 100 ohms—2.5 Meg. 2/0-2/6. ea. (below 100 ohms, 2/- ea.).
CONDENSERS, Silver Mica. All value 2 pF to 1,000 pF, 6d. ea. Dkts ceramic 9d. Tub. 450v. T.C.C. etc. .001 mF to 0.1 mF/350 v. 10d. .02 mF to 0.1 mF. 500 v. 1/-; .25 T.C.C. 1/9. 5 T.C.C. 2/-.
CLOSE TOL. S/MICs. 10% 5 pF—500 pF. 9d. 600—5,000 pF 1/-, 1% 2 pF—100 pF. 11d. 100—250 pF 1/2. 270—800 pF 1/4. 800—5,000 pF 2/-.
ALWAYS IN STOCK AT KEENE'S PRICES. Transistors. Coils. Switches. Valves. Speakers. Materials. See latest TRS lists.

ORDERING—Send cash with order. Post and packing where not stated add 1/- per lb.; 1/9 1 lb.; 3/6 2lb.; 5/- 6lb.; 9/6 10lb.; 8/- 14lb.; over 10/- S.A.E. with enquiries please.
LISTS—Eight large printed pages, packed with bargain offers including difficult to find items. Send 6d. for latest copy.

FELSTEAD ELECTRONICS

(PW16)

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted. Charges, which apply to G.B. and Eire only, are paid by us on orders value 25 and over. Overseas air or surface mail extra at cost.

TRS RADIO COMPONENT SPECIALISTS

EST. 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY



Telephone: 9 a.m.—6 p.m. daily
01-6842188 1 p.m. Weds. Health Stn. (S.R. Victoria Station)

FREE! handyman's putty knife

BLADE EXTENDABLE
ADHESIVE SPREADER
ATTACHMENT
MADE IN DURABLE
PLASTIC

Plus
special feature

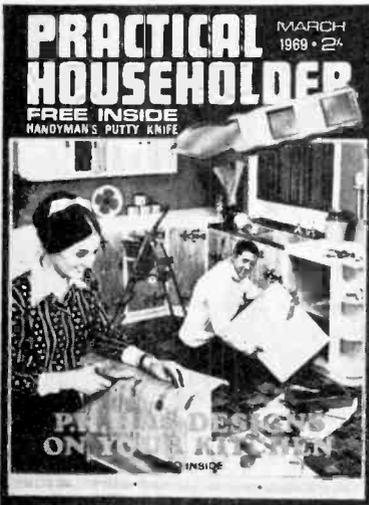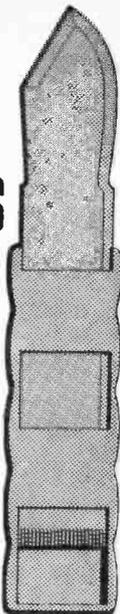Practical Householder has
designs on your kitchen
—and other rooms in your house too.
Packed with ideas for unusually attractive
wall and floor treatments, and
simple furniture fittings you'll find
easy to build.



Also

Wall-to-Wall Cupboard for Your
Bedroom
How to do Ornamental Ironwork
Wiring for Light and Power
How to Get the best from Furniture—
Kits and Whitewood Units

MARCH ISSUE OUT NOW 2/-

PRACTICAL HOUSEHOLDER

ADD NEW EXCITING STEREO EFFECTS TO YOUR LISTENING



with a Dewtron "NEW DIMENSIONS" 3-Dimensional effects amplifier. Gives Big Hall Stereo effect to most radios, tapes, etc. PLUS fully adjustable echo, vibrato and tone. 9 volt model, 8 kws. Speaker, 25/- extra. 6/12V car model, 10 kws. incl. speaker. Post and ins. 5/- either model. Write now—right now.

D.E.W. LTD.,
P.W., RINGWOOD ROAD, FERNDOWN, DORSET

Est. 1943 **JOHNSONS** Tel: 24864

VHF and Short-Wave kits for the Amateur enthusiast and constructor. For 2 and 4 metres, the unique two transistor model SR2/P, 70-150Mc/s, 75/6, p.p. 4s. New super 5V all-wave, all-band kit, also "Mini-Amp" self-contained, cabinet, size a mere 4½ x 3½ x 2½. Write today, enclosing a stamped addressed envelope for interesting free literature, and details, direct to

JOHNSON'S (RADIO)
St. Martin's Gate, Worcester

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

IR5 4/9	DY86 5/6	EZ80 3/8	PL500 12/-
186 4/3	DY87 5/6	EZ81 4/6	PL504 12/6
1T4 2/9	EAB00 5/9	KT81 8/3	PY32 10/-
384 5/9	EBC41 8/-	KT66 15/9	PY33 10/-
3V4 5/6	EBF80 5/9	N78 14/6	PY81 5/-
6AQ5 4/6	EBF89 5/9	PAB00 6/9	PY82 4/9
6L18 6/-	ECX81 3/9	PC86 9/3	PY83 5/3
30C18 8/9	ECC82 4/3	PC88 9/3	PY88 6/-
30FL12/3	ECC83 4/9	PC97 7/9	PY800 6/6
30FL12/14/3	ECC85 4/9	PC900 8/-	PY801 6/6
30FL14/10/3	ECH35 5/6	PCC84 5/9	R19 6/3
30P4 11/6	ECH42 9/9	PC89 9/9	U25 12/9
30P19 11/6	ECH81 5/3	PCG189 9/6	U26 11/6
30PL12/3	ECL80 6/3	PCF80 6/3	U191 12/6
OCH35 9/9	ECL82 6/3	PCF82 5/9	UABC80 5/9
CL33 18/6	ECL83 8/9	PCF801 6/9	UBC41 7/6
DAC32 6/9	ECL86 7/6	PCF805 8/9	UBF89 6/3
DAF91 4/3	EF39 3/6	PCF808 10/3	UCC84 7/9
DAF96 5/11	EF80 4/9	PCL82 6/8	UC85 6/-
DF33 7/6	EF86 5/-	PCL83 8/9	UCF80 8/-
DF91 2/9	EF86 6/3	PCL84 7/-	UCH42 6/8
DF96 5/11	EF89 4/9	PCL85 8/-	UCH81 6/-
DK32 6/9	EF183 5/9	PCL86 8/-	UCL82 6/9
DK91 4/9	EF184 5/6	PFL20012/-	UF41 9/6
DK96 6/6	EL33 8/3	PL36 9/3	UF89 6/11
DL35 4/9	EL41 9/3	PL81 7/-	UL41 8/9
DL92 5/9	EL84 4/6	PL82 5/9	UL84 5/9
DL94 5/6	EY51 6/9	PL83 6/-	UY41 6/6
DL96 6/8	EY86 6/-	PL84 6/-	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

JASON KITS

FANTASTICALLY POPULAR

★ TAPE ★

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/8	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/8
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	7in. 3,600ft.	44/-
		Quadruple Play	
		3in. 600ft.	8/6

Postages 1/- reel.

Post Free less 5% on three reels.

Quantity and Trade enquiries invited.

NOTE: Large tape stocks at all branches.

TUBES

Highest Quality—
Compare Our Prices

Carr. & Ins.	GUARANTEED	
12/6	6 Months	12 Months
14in.	22.10.0	28.10.0
17in. & 19in.	23.5.0	24.5.0
21in. & 23in.	23.15.0	25.15.0

SATISFACTION GUARANTEED
Most Mullard, Mazda, Cossor, Emitron, Emiscope, Brimar, Ferranti types processed in our own factory.
NOTE: ALL tube orders only to Portsmouth branch please.

*NEW and SPECIAL Lines at
the keenest prices*

AM/FM STEREO MULTIPLEX RECEIVERS
18 transistors, 9 diodes, 1 variable diode, 2 Silicon Rectifiers. Push-pull Stereo Amplifiers. FM Stereo Separation 15dB. AM Medium Wave 180-550 Meters. Power output 10W R.M.S., 220/240V A/C Mains. Beautiful wooden plinth case—approximately 15"(w) x 6"(h) x 8"(d). Controls: Function Switch, Balance, Base/Treble Control, Volume, Tuning, Fine finish. Special purchase enables us to offer these superb machines of famous make at a ridiculously low price. Unrepeatable offer at a fraction of list price... only 28 GNS. POST FREE.

SHARP	RD504 Mains Battery Tape Recorder. List 36 gns	28 gns
HITACHI	SW/MAR/MW/LW Marine D/F Receivers	27 gns
GARRARD	1025 Changers with Stereo Cartridge	£8 10s
JASON	12in. Diecast full range twin cone Speakers	£4 10s
AJAX	Mains/Battery, AM/FM larger Radio	12 gns
WELESMERE	AM/FM High Sensitivity Black Leather	7 gns
HITACHI	WH937E All-Wave, full size. Excellent Short Wave	13 gns
HI-FI	By Leak, Wharfedale, Goodmans, WB, Dulci, Arona, Teleton, etc., etc.	

All items previously advertised available. Huge Hi-Fi and Component stocks at all branches. Please call and view without obligation.

TECHNICAL TRADING

RETAIL BRANCHES:

LONDON, 10 Tottenham Court Road (MUS 2639)
PORTSMOUTH, 350-352 Fratton Road (Tel. 22034)
SOUTHAMPTON, 72 East Street (Tel. 25851)
BRIGHTON, 6 Queen's Road (Tel. 23975)

MAIL ORDER WAREHOUSE:

Devonian Court, Park Crescent Place, Brighton.
(Tel. 680722)

BARGAIN PARCELS


Including variable condensers, i.f. coils, loudspeaker plug/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors at a small fraction of list value. Due to heavy demand we now pack them in several sizes—be amazed—try one now.

3 lbs. (post 3/-)	9/-
7 lbs. (post 5/-)	17/8
14 lbs. (post 6/-)	29/-

PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX.

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Echant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

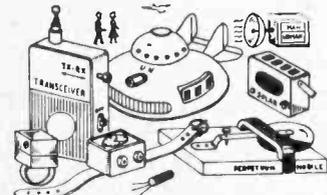

EXPERIMENTER'S PRINTED CIRCUIT KIT

8/6


Postage & Pack. 1/6 (UK)

Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand
South Africa, Canada.

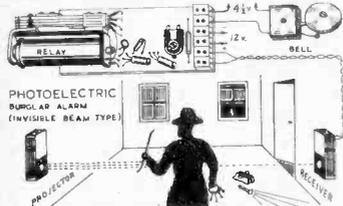(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio 70" x 70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal-Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT

39/6

Postage and Pack. 2/6 (UK)

Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (UK). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

PHOTOELECTRIC PARKING LAMP SWITCH

Automatically turns parking lamp on at dusk, off at dawn. Protects your car. Saves the battery. Miniature construction. Simply insert in parking lamp lead. Price: 27/6. Post & Packing 2/6 (U.K.)

THYRISTOR LIGHT DIMMER

Add a touch of luxury to your home. Adjust the light at parties, while watching TV, etc. Ideal for Children's bedroom. (100 watts max.) Replaces on-off switch. Price: 59/6. Post & Packing 2/6 (U.K.)

YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 82 Radio, Electronic and Photoelectric Projects Assembled.

PUBLICATIONS FOR RADIO AMATEURS AND ENTHUSIASTS

Amateur Radio Call Book (1968 ed. RSGB)	7/3
Amateur Radio Circuits Book (RSGB)	11/6
Antenna Book (10th ed. ARRL)	18/6
Amateur Radio Techniques (RSGB)	13/3
Basic Theory and Application of Transistors (Dover)	11/6
Course in Radio Fundamentals (ARRL)	10/-
Cubical Quad Antennas (Radio Pubs.)	22/-
Foundations of Wireless (Iliffe)	22/6
Guide to Amateur Radio (12th ed. RSGB)	6/9
How to Listen to the World	26/-
Mobile Handbook (CQ)	23/-
Mobile Manual for Radio Amateurs (ARRL)	23/6
Radio Amateur Operator's Handbook (Data)	5/6
Radio Amateur's Operating Manual (ARRL)	7/9
Radio Amateur's Vocabulary (German/English)	9/3
Radio Communication Handbook (RSGB)	69/-
RTTY Handbook (CQ)	30/-
Service Valve and Semiconductor Equivalents	5/6
Single Sideband for the Amateur (4th ed. ARRL)	23/6
S-9 Signals (Radio Pubs.)	8/6

Further details of other publications, information about membership, and a sample copy of the Radio Communication (4s.) (the RSGB monthly journal), may be obtained by writing to:

RADIO SOCIETY of GREAT BRITAIN, Dept. PW.
35 DOUGHTY STREET, LONDON, WC1

MARTIN IS HIGH FIDELITY plus

ADD-ON-ABILITY

THRILLING POWER

DEPENDABILITY

GENUINE ECONOMY

How would you like to start with a simple amplifier, say, and add to it until it became a fully stereo twenty watt amplifier with FM tuner and facilities to take the most sensitive low output pickups ever made? With Martin Audiokits it's easy, for with these superbly engineered all-transistor prefabricated units, success is built in from the start and you build to your own preferred plan. IT'S A MONEY SAVING SCHEME, TOO.

Details from:

● Trade enquiries invited.

MARTIN ELECTRONICS LTD., 155 High St., Brentford, Middlesex. ISLeworth 1161

To MARTIN ELECTRONICS, 155, High Street, Brentford, Middlesex.

I have not had your leaflets before. Please send them on
AMPLIFIERS FM TUNER RECORDAKITS
(Tick as required)

NAME
ADDRESS
PW3

SILICON N.P.N. TRANSISTORS. Similar to 2N2926. All individually tested. Gold plated leads for easy soldering. Unbeatable value at 1/6 each or £5 per 100.

12 VOLT TRANSISTORISED FLUORESCENT LIGHT. * 8 WATT 12in TUBE. Current drain only 700mA! Complete and tested £2/19/6 only! Or in kit form:

*Case	10/-
Transistor	10/-
Lamp holders—	pair 5/-
Condensers, etc.	3/-
Transformer	13/6
Tube	8/-

*Post and Packing 3/-

TRANSISTORS

OC200, OC203, OC204, all at 2/- each.
ASY22, 2N753, BSY28, BSY65, 2G344A, 2G345A, 2G345B, 2G371A, 2G378A, all at 1/6 each.

Transistors similar to OC44, OC71 and OC72, all 1/- each. Unmarked, untested transistors, 7/6 for 50.

LIGHT SENSITIVE TRANSISTORS (similar OCP 71), 2/- each. 30 watt transistors (ASZ17), 10/- each.

ORP 12 Cadmium sulphide light-sensitive resistors, 9/-.

RECTIFIERS

BY100, 800 p.i.v., 2/6 each, 24/- per doz., £7/10/- per 100, £50 per 1,000. BYZ13, 6-amp, 400 p.i.v., available on same terms.

MULLARD POLYESTER CAPACITORS FAR BELOW COST PRICE!

0-001µF 400 volts	3d	0-15µF 160 volts	6d
0-0015µF 400 volts	3d	0-22µF 160 volts	6d
0-0018µF 400 volts	3d	0-27µF 160 volts	6d
0-0022µF 400 volts	3d	1µF 125 volts	1/-
0-01µF 400 volts	3d		

VERY SPECIAL VALUE! Small Silver-mica, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values. 10/- per 100. **PAPER CONDENSERS, MIXED BAGS,** 0-0001 to 0-5µF. 12/6 per 100.

RESISTORS! Give-away offer! Mixed types and values, 1/4 to 1/2 watt 6/6 per 100, 55/- per 1,000. Individual resistors 3d each. Also 1/2 to 3 watt close tolerance. Mixed values. 7/6 100, 55/- 1,000.

WIRE-WOUND RESISTORS. 1 watt to 10 watts. Mixed bags only. 16 for 10/-.

RECORD PLAYER CARTRIDGES

ACOS

GP 67/2 Mono.	15/- complete with needles.
GP 91/3 Stereo Compatible	£1/-
GP 93/1 Stereo Ceramic	£1/5/-
GP 94/1 Stereo Ceramic	£1/5/-

Small pick-up arms complete with cartridge and needle, 10/- only.

**UNREPEATABLE OFFER!
GIANT SELENIUM PHOTO-CELLS
PRODUCE UP TO 6ma. FROM
DAYLIGHT!**

67mm. Diameter (29.2sq.cm.) 10/- each.
50mm. x 37mm. (16.5sq.cm.) 2 for 10/- each.

TRANSISTORISED SIGNAL INJECTOR KIT R.F./I.F./A.F. 10/- only

TRANSISTORISED SIGNAL TRACER KIT 10/- only

TRANSISTORISED REV. COUNTER KIT 10/-

VEROBOARD

2 1/2in x 1in 0-15in matrix	1/6	17in x 2 1/2in 0-15in matrix	11/-
3 1/2in x 2 1/2in 0-15in matrix	3/3	17in x 3 1/2in 0-15in matrix	14/8
3 1/2in x 3 1/2in 0-15in matrix	3/11	3 1/2in x 2 1/2in 0-1in matrix	4/2
5in x 2 1/2in 0-15in matrix	3/11	3 1/2in x 3 1/2in 0-1in matrix	4/9
5in x 3 1/2in 0-15in matrix	5/6	5in x 2 1/2in 0-1in matrix	4/7
		5in x 3 1/2in 0-1in matrix	5/6

Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins 3/6-36.

MULTIMETERS. 20,000 ohms per volt.

Ranges: a.c. 1,000V, 500V, 100V, 50V, 10V.

d.c. 250mA, 2.5mA, 50µA.

d.c. 2,500V, 500V, 250V, 50V, 25V, 5V.

Resistance: 0/60kΩ and 0/6MΩ.

Special price £4 only.

ELECTROLYTIC CONDENSERS

0-25µF 3 volt	4µF 4 volt	10µF 25 volt	64µF 9 volt
1µF 6 volt	4µF 12 volt	20µF 6 volt	100µF 9 volt
1µF 20 volt	4µF 25 volt	25µF 6 volt	320µF 4 volt
1-25µF 16 volt	5µF 6 volt	25µF 12 volt	320µF 10 volt
2µF 3 volt	6µF 6 volt	25µF 25 volt	400µF 6.4 volt
2µF 350 volt	8µF 3 volt	30µF 6 volt	All at 1/- each.
2-5µF 16 volt	8µF 12 volt	30µF 10 volt	20 assorted
3µF 25 volt	8µF 50 volt	50µF 6 volt	(our selection)
3-2µF 64 volt	10µF 6 volt	64µF 2.5 volt	10/-

SMALL TRANSISTOR OUTPUT TRANSFORMERS 2/6 each.


SMALL TRANSISTOR DRIVER TRANSFORMERS 2/6 each.

Orders by post to:

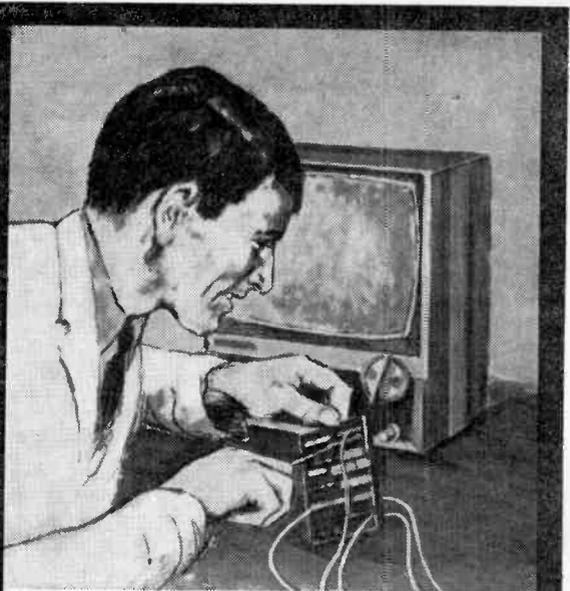G. F. MILWARD, DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/- Stamped addressed envelope must accompany any enquiries.

For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.



Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full time 16 month College Diploma Course which gives a thorough fundamental training for radio and television engineers, starts on 16th April 1969.

The Course includes theoretical and practical instruction in Colour Television receivers and is recognised by the Radio Trades Examination Board for the Radio and Television Servicing Certificate examinations. College Diplomas are awarded to successful students.

The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now with the world famous Pembridge College. Minimum entrance requirements: 'O' Level, Senior Cambridge or equivalent in Mathematics and English.

To: The Pembridge College of Electronics
(Dept. PW7), 34a Hereford Road, London, W.2

Please send, without obligation, details of the Full-time Course in Radio and Television.

NAME

ADDRESS

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman Street, Loughborough.

BOOKS & PUBLICATIONS

AUDIO. America's foremost journal. Year's subscription 50/-. Specimen copy 4/6. All American radio journals supplied—list free. Willen (Dept. 40), 61a Broadway, London E.15.

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/6 p/p 6d.
1155 set Circuit and Notes	6/6 p/p 6d.
H.R.O. Technical Instructions	5/6 p/p 6d.
38 set Technical Instructions	5/6 p/p 6d.
46 set Working Instructions	5/6 p/p 6d.
88 set Technical Instructions	7/- p/p 6d.
BC.221 Circuit and Notes	5/6 p/p 6d.
Wavemeter Class D Tech. Instr.	5/6 p/p 6d.
18 set Circuit and Notes	5/6 p/p 6d.
BC.1000 (31 set) Circuit and Notes	5/6 p/p 6d.
CR.100/B.28 Circuit and Notes	10/- p/p 9d.
R.107 Circuit and Notes	7/- p/p 6d.
AR.88D Instruction Manual	18/- p/p 6d.
62 set Circuit and Notes	6/6 p/p 6d.

Circuit Diagram 5/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.134, T.1154, CR.300, BC.312, BC.342, BC.346J, BC.348 (E.M.P.), BC.624, 22 set.

52 set Sender and Receiver circuits 7/6 post free

Resistor colour code indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8



This useful handbook gives detailed information and circuits for British and American Government Surplus Receivers, Transmitters, and Test Equipment etc., plus suggested modification details and improvements for the equipment. Also a Surplus/commercial cross reference valve guide and Government component codings and references. Invaluable to Radio enthusiasts, Universities and Laboratories.

Available only from us at:

GUILTEX

24 Stansfield Chambers, Great George Street, Leeds 1, Yorkshire.

at 30/- per volume, post paid. Extra postage for Foreign Orders.

SITUATIONS VACANT

TESTERS AND TROUBLE-SHOOTERS required by manufacturers of car radios, tape recorders, record players, etc. Good rates of pay. Apply to Elizabethan Electronics Ltd., Ref. PW2, Crow Lane, Romford, Essex. Telephone: Romford 64101.

SITUATIONS VACANT

(continued)

DESIGN DEVELOPMENT ENGINEER for laboratory work in the design of audio amplifiers, V.H.F. tuners and quality tape recorders. Only persons holding a similar position need apply. Salary according to experience. Apply to Elizabethan Electronics Ltd., Ref. PW1, Crow Lane, Romford, Essex. Telephone: Romford 64101.

RADIO and tape recorder testers and trouble shooters required. Canteen, excellent rates of pay. 8.00 a.m. to 5.00 p.m. 5-day week. Elizabethan Electronics Limited, Crow Lane, Romford, Essex. Phone: Romford 64101.

ENGINEERS. A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C. Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts, Building, etc. For full details write for **FREE 132 page guide: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TRAINEE RADIO TECHNICIANS

A PROGRESSIVE CAREER IN THE FIELD OF RADIO AND ELECTRONICS

Applications are now invited for an intensive training course of 3 years, leading to appointment as a fully qualified **RADIO TECHNICIAN**, with further prospects of progression to the Telecommunication Technical Officer Class.

Generous Pay and Conditions while under training.

Candidates must be over 16 and under 21 years of age as at September 8th, 1969, on which date training commences.

Minimum educational qualifications required are passes at G.C.E. 'O' Level in English Language, Mathematics and Physics (already held or expected to be obtained in the Summer 1969). Equivalent passes in Scottish or Northern Ireland Certificates and C.S.E. Grade 1 passes are also acceptable.

Closing date for applications 31st March, 1969. Interviews will be commenced about end of April.

Apply for full details and application form to:

**THE RECRUITMENT OFFICER (TRT/37),
GOVERNMENT COMMUNICATIONS
HEADQUARTERS, OAKLEY, PRIORS RD,
CHELTENHAM, GLOS. GL52 5AJ**

SITUATIONS VACANT

(continued)

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page Handbook—**FREE**. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

TRAIN TODAY FOR TOMORROW

Start training **TODAY** for one of the many first-class posts open to technically qualified men in the Radio and Electronics industry. ICS provide specialized training courses in all branches of Radio, Television and Electronics—one of these courses will help **YOU** to get a higher paid job. Why not fill in the coupon below and find out how?

Courses include:

- RADIO/TV ENG. & SERVICING
- AUDIO FREQUENCY
- CLOSED CIRCUIT TV
- ELECTRONICS—many new courses
- ELECTRONIC MAINTENANCE
- INSTRUMENTATION AND SERVOMECHANISMS
- COMPUTERS
- PRACTICAL RADIO (with kits)
- PROGRAMMED COURSE ON ELECTRONIC FUNDAMENTALS

Guaranteed Coaching for:

- C. & G. Telecom. Techns' Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Cert.
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education

Start today—The ICS Way

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 173, Parkgate Rd., London, S.W.11.

Please send **FREE** book on

Name

Address

3.69

EDUCATIONAL

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam-home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1969. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

MISCELLANEOUS

RHYTHM MODULES. Build your own rhythm box—simply, cheaply. Realistic sound guaranteed. S.A.E. for details. D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset.

BUILD IT in a DEWBOX quality cabinet. 2in. x 24in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

CONVERT ANY TV into an Oscilloscope. Instructions \$2. REDMOND, P.O. Box 38397, Los Angeles, California 90038.

GEARED MOTORS

Rectifiers, Potentiometers

6d Stamp for Catalogue

F. HOLFORD & CO.

6 Imperial Square, Cheltenham

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

ELECTRICAL

**240 VOLT
ELECTRICITY
ANYWHERE**



MOST BRILLIANT PERFORMANCE EVER from 12 volt Car Battery

BRILLIANT HEAVY DUTY 240 volt AMERICAN DYNAMOTOR with BIG 220 WATT OUTPUT. Marvellous for TELEVISION, ELECTRIC DRILLS, MAINS LIGHTING and ALL UNIVERSAL AC/DC MAINS EQUIPMENT. Marvellous for Fluorescent lighting. Thousands of uses. Tremendous purchase of this model makes fantastically low price possible.

ONLY £5.19.6 each plus 10/6 delivery. C.O.D. with pleasure. MONEY BACK if not DELIGHTED. Please send s.a.e. for full illustrated details.

(Dept. PW) **STANFORD ELECTRONICS**, Rear Derby Road, North Promenade, BLACKPOOL, Lancs.

Open 7 days a week

SERVICE SHEETS

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. TELRAY, 11 Maudland Bank, Preston, Lancs.

SERVICE SHEETS (1925-1969) for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. **HAMILTON RADIO**, 54 London Road, Bexhill, Sussex.

RADIO, TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. **THOMAS BOWER**, 5 South Street, Oakenshaw, Bradford.

C. & A. SUPPLIERS

SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS)

Only 5/- each, plus S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

**71 BEAUFORT PARK
LONDON, N.W.11**

We have the largest supplies of Service Sheets (strictly by return of post) Please state make and model number alternative.

Mail order only.

WANTED

DAMAGED AVO METERS, Models 7 & 8, any quantity. Send for packing instructions. **HUGGETT'S LTD.**, 2/4 Pawsons Road, West Croydon.

NEW VALVES WANTED. Popular TV and Radio types. Best cash price by return. **DURHAM SUPPLIES**, 367c Kensington Street, Bradford, 8, Yorkshire.

WANTED FOR CASH. Car radios, Transistor radios. All surplus Radio, T.V. and electrical equipment. Complete parcels bought. Write details, M. ALEXANDER, 20 Pauline House, Hanbury St., London E.1.

WANTED NEW VALVES, televisions, radio-grams, transistors, etc. **STAN WILLETT'S**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WE BUY New Valves and Transistors. State price. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

WANTED

(continued)

WANTED: New valves, transistors etc.; state prices. **E.A.V. Factors**, 202 Mansfield Road, Nottingham.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

WANTED: Popular Brand New Valves. **R.H.S.**, Stamford House, 538 Great Horton Road, Bradford 7.

FOR SALE

MINIFLUX HEADS

Special offer SKN4 1/2-track stereo record/play-back head (list 8 gns.). Special offer 55/-. Miniflux LF6-0 self oscillating half-track mono erase head, list £3.10.0. Offered at 22/6. VLF4 1/2-track ferrite erase head, list £4.5.0. Offered at 32/6. S.A.E. for full lists.

LEE ELECTRONICS

400 EDGWARE ROAD. PADdington 5521

HIGH GLOSS METALLIC

**HAMMERED ENAMEL
MAKES FANTASTIC**

DIFFERENCE TO PANELS

—say hundreds of enthusiastic users 'Crackle' pattern appears like magic on wood and metal. No undercoat. Air dries 15 min. to hard glossy finish. Heat, liquid and scratch-proof. Bronze, Silver, Green, Black, Lt. and Dk. Blue. Send NOW for free list, or 8/- (+ 1/9 post and packing) for trial 1/2 pt. tin, colour samples and instructions.



FINNIGAN SPECIALITY PAINTS, Dept. P.W. STOCKSFIELD (Tel. 2280), Northumberland.

TOP TRADE DISCOUNTS FOR ALL

COMPONENTS

VALVES

TUBES

TRANSISTORS

Free Trade Catalogue

Engineers & Service Dealers Only

WILLOW VALE

THE SERVICE DEPT.

WHOLESALEERS,

4 The Broadway, Hanwell,

London, W.7

01-567 5400/2971

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY—

Get these air drying **GREY HAMMER** **OR BLACK WRINKLE** (CRACKLE) finishes

Now!

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Finishes available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 13/6 at our counter or 16/11 carriage paid. per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept: **M/2 YUKAN**, 307A, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organizations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

FOR SALE
(continued)

£6,000 IN VOUCHERS GIVEN AWAY. See free Catalogue for details. Tools, materials, mechanical, electrical, thousands of interesting items. WHITSON, Dept. VW, New Mills, Stockport SK12 4HL.

THE IDEAL Panel Mounting Meter Movement for any Sensitive Test Meter etc. 200 Micro Amp F.S.D. 4 1/2 in. x 4 1/2 in. In clear plastic case. Our special price only 39/6d. P. & P. free. Limited number only. WALTON'S WIRELESS STORES, 35A Worcester Street, Wolverhampton, Staffs.

MORSE MADE !!
EASY

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)
Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without transcribing. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.
For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to:
G3CHS/P, 45 GREEN LANE, PURLEY, SURREY

RECEIVERS & COMPONENTS

McMURDO Silver, 6 band, chassis and speaker. Offers. SUFF, 48 East Street, Hereford.

WHAT OFFERS for 5-10 Amplifier (Gilson transformers), F.M. Tuner and 1 valve tone unit, all as book. F. H. REEVES, c/o Sun Inn, St. Nicholas at Wade, Birchington.

COMPONENTS AT GIVE AWAY PRICES. Digital Counters, Rev Counters, Thyristors, Transistors, Valves, Tool Bags, Track Heads, Recording Tape, Aerials, Intercoms, Microphones, Micro Switches etc. 6d. stamp only to DIAMOND MAIL ORDER PRODUCTS, PROSPECT HOUSE, CANAL HEAD, POCKLINGTON, YORK. NO4 2NW.

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS 2" x 4" packed with semiconductors and top quality resistors, capacitors, diodes etc. Our price: 10 boards 10/-, P. & P. 2/-, with a guaranteed minimum of 35 transistors.

Special Bargain Pack. 25 boards for £1. P. & P. 3/6, with a guaranteed minimum of 85 transistors. 100 boards, 65/-, P. & P. 6/6, with a guaranteed minimum of 350 transistors.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-, P. & P. 2/-.

NPN GERMANIUM TO5 1 WATT POWER TRANSISTORS on small heat sink, on 2" x 4" panel. 5 for 10/-, P. & P. 2/-.

POWER TRANSISTORS sim. to 2N174 ex-eqpt., 4 for 10/-, P. & P. 2/-.

POWER TRANSISTORS sim. to 2N174 ON Finned Heat Sink (10D) 4 for £1, P. & P. 3/-.

LONG ARM TOGGLE SWITCHES ex eqpt. SPST 13/6 doz., DPDT 22/6 doz., DPST 17/- doz. P. & P. all types 2/- doz.

ORGAN BUILDERS special 500 T018 transistors on panels £4, P. & P. 6/-.

OVERLOAD CUT outs. Panel mounting in the following values... 5/- each. 1, 1 1/2, 2, 3, 4, 5, 7, 8 amp. P. & P. 1/6.

MINIATURE GLASS NEONS, 12/6 doz. P. & P. 1/6. NEW MIXED DISC CERAMICS. 150 for 10/-, P. & P. 2/-.

LARGE CAPACITY ELECTROLYTICS 4 1/2 in., 2 in. diam. Screw terminals. All at 6/- each + 1/6 each P. & P.
4,000mF 72V d.c. wkg.
10,000mF 25V d.c. wkg.
6,300mF 72V d.c. wkg.
1,500mF 150V d.c. wkg.
16,000mF 25V d.c. wkg.
25,000mF 12V d.c. wkg.

Send 1/- stamps for list.
KEYTRONICS, 52 Earls Court Road London, W.8. Mail order only

RECEIVERS & COMPONENTS (continued)

ELECTROVALUE

RAPID MAIL-ORDER SERVICE

PROMPT DELIVERY

VERY LARGE STOCKS

EVERYTHING BRAND NEW AND TO SPECIFICATION

★ **Unbeatable Value in SEMICONDUCTORS**

30W BAILEY AMPLIFIER MJ481 and MJ491 matched pair output, 59/-; 40361 and 40362 matched pair driver, 30/5; 40361 12/8; 40362 15/9; BC125 12/-; BC125 12/-; BC107 2/9; BC109 2/9. Main amp. PC board 12/6 each but FREE with each complete transistor set.
Total for one channel £7.8.0 list with 10% discount; only £6.13.3. Total for two channels £14.16.0 list. with 15% discount only £12.11.8. Complete power supply kit £4.5.0 list. Circuit reprints 1/- each.

G.E. 2N2926 PLASTIC RANGE Price reductions
Red spot = 55 to 110 2/3; Orange spot = 90 to 180 2/3; Yellow spot = 150 to 300 2/6; Green spot = 235 to 470 2/8.
All the above brand new stock.

TEXAS SILECT RANGE PRICES REDUCED
30V 800mA npn: BC108 20V = 125 to 900 2/8
2N3704 = 90 to 230 3/9 BC109 20V = 125 to 900 2/9
2N3705 = 45 to 185 3/5 BC167 series (180mW) = 125 to 900 2/9
25V 200mA pnp: BC169 20V = 240 to 900 2/3
2N3702 = 60 to 300 3/6 BC167 45V = 125 to 500 2/3
2N3703 = 30 to 150 3/3 300MHz (T. T092):
small signal npn: BC167 45V = 125 to 500 2/3
2N3707 low noise 4/1- BC168 20V = 125 to 900 2/-
2N3711 = 180 to 660 3/11 BC169 20V = 240 to 900 2/3
small signal pnp: BC109 and BC169 are 300MHz FT T018: BC167, BC168 and BC169 are plastic.
2N4058 low noise 4/9
2N4062 = 180 to 660 4/3
BC107 series 300mW
BC107 45V = 125 to 500 2/8
Beta values for above immediately quoted after type No.

FETs - Prices reduced
MPF105 25V max., gm = 2 to 6mA/V, low noise 7/8;
2N3819 25V max., gm = 2 to 6mA/V, low noise 8/-.

MINI TRANSISTORS - Prices reduced
2N4285 pnp hFE 35 to 150 at 10mA (T 7MHz min., Veb 35V max., 2N4286 npn 30V hFE over 100 at 10µA to 1mA (T 280MHz typ. 2N4289 pnp 60V hFE over 100 at 10µA to 1mA (T 170MHz typ. 2N4291 pnp 40V hFE over 100 at 100mA, 2N3794 npn 40V hFE over 100 at 100mA, complementary driver output 2N4292 npn 30V UHF N.P. 6dB max at 100MHz. FT 570MHz typ. B5041 Power 14-3W at 100°C base temp. 35V, hFE over 100 at 0.5A. Insulated TO66 size mounting surface.
Prices: 2N4285 to 2N4292 and 2N3794 2/11; B5041 13/6.

1,000V 1.5A GENERAL PURPOSE RECTIFIER type 1N5054 3/6 only.
1,000 0.75A miniature rectifier type T81 1/9; 400V type T84 2/3.

ZENER DIODES 3V to 27V 5% 400mW all preferred voltages. 4/6 each.

NEW TRANSISTOR BARGAINS
2N696 5/6 2N1711 7/4 2N4060 4/3 BC148 3/6
2N697 6/- 2N2147 16/9 40250 15/- BC149 4/3
2N706 3/5 2N2369A 40408 16/3 BD123 24/3
2N1132 13/- 6/9 40408 14/6 BF194 7/-
2N1302 4/- 2N2646 9/6 AC126 6/8 BFX29 12/3
2N1303 4/- 2N2924 5/- AF128 6/- BFX84 7/5
2N1304 4/- 2N2925 5/9 AC176 11/- BFX85 8/3
2N1305 4/- 2N3053 5/6 ACV17 8/- BFX88 7/9
2N1306 6/9 2N3054 15/8 AD161 7/- BFY51 4/3
2N1307 6/9 2N3055 16/8 AD162 7/- B8X20 4/6
2N1308 8/9 2N3391A AF114 7/- NKT403 -
2N1309 8/9 5/6 AF124 7/8 14/10
2N1613 6/6 2N3706 3/3 BC147 4/3

All power types supplied with FREE Mica Washers.

★ **RESISTORS**

METAL OXIDE type TR5 0.5W 5%, tolerance. Very low noise, low temperature coefficient, low drift. A Professional resistor. All E24 preferred values 10 Ω to 1M Ω. Price: 1 to 11 10d; 12 to 25 9d; 25 up 8d.
CARBON FILM high stab low noise.
1 W 10% 1 Ω to 3 Ω and 1 W 5% 3-9 Ω to 1 M Ω 1/10 doz., 14/8 100.
1 W 10% 4-7 Ω to 10 M Ω, 1/9 doz., 13/6 100.
1 W 5% 4-7 Ω to 10 M Ω 2/2 doz., 37/- 100.
1 W 10% 4-7 Ω to 10 M Ω, 3/3 doz., 25/10 100.
1/6 less per 100 if ordered in complete 100s of one ohmic value.
Please state resistance values required.
Carbon Skeleton pre-sets: 100 Ω, 250 Ω, 500 Ω, 1k Ω, 2k Ω, 2.5k Ω, 5k Ω, 10k Ω, 20k Ω, 25k Ω, 50k Ω, 100k Ω, 200k Ω, 250k Ω, 500k Ω, 1M Ω, 2M Ω, 2.5M Ω, 5M Ω, 10M Ω. Vertical or horizontal mounting.
Small high quality, 1/- each; Sub-min, type 11d each.

★ **PEAK SOUND PRODUCTS**

Peak Sound PA.12-5 Power Amplifier has a maximum distortion level of only 0.1% at 11-5W, into 15 Ω. In kit form £3.19.8, plus 12/- for ready prepared heat sink and mounting board. Power supply P8.45 Kit £4.11.0.
Pre-amp kit 27/- plus controls mono: 6/3; stereo 20/-.
Active tone filter kit 19/- plus controls: mono 5/-; stereo 16/-.
No discounts allowable on basic kits only.

★ **ELECTROLYTICS**

SUB-MIN.
C426 range (µF/V): 0.64/64, 1/40, 1.6/25, 2.5/16, 2.5/64, 4/10, 4.4/40, 5/64, 6.4/64, 6.4/25, 8/4, 10/2.5, 10/16, 10/64, 12.5/25, 16/10, 16/40, 20/16, 20/64, 25/6.4, 25/25, 32/4, 32/10, 32/40, 32/64, 40/2.5, 40/16, 50/6.4, 50/25, 50/40, 64/4, 64/10, 80/2.5, 80/16, 80/25, 100/6.4, 125/4, 125/10, 125/16, 160/2.5, 200/6.4, 200/10, 250/4, 320/2.5, 320/6.4, 400/4, 500/2.5. **Price reduction 1/3 each.

MINIATURE (µF/V):
5/10, 10/10, 25/10, 50/10, 9d each, 25/25, 50/25, 100/10, 200/10, 1/- each; 50/50, 100/25, 1/8; 100/50, 25/25, 2/-.

LARGE ELECTROLYTICS (µF/V):
1000/50 7/-; 2000/50 8/3; 5000/50 17/6; 5000/25 10/3; 2500/64 15/-. Vertical clips for above types 9d each.

★ **CAPACITORS**

Ceramic disc 20% 500V: 1,000pF, 2,000pF, 5,000pF. 50V: 0.01µF, 0.02µF, 0.05µF. Mylar film 10%. 100V: 1,000pF, 2,000pF, 5,000pF, 0.01µF, 0.02µF, 0.05µF. Polystyrene 5% 100V: 22pF preferred values to 820pF. ALL at 5d each. Polyester 250V 20%: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068µF 7d each. 0.1µF 8d. 250V 10%: 0.15, 0.22 9d; 0.33 1/2; 0.47 1/8; 1µF 2/3; 2.2µF 4/-.

★ **POTENTIOMETERS**

Prices reduced
Short spindle 100 Ω to 10M Ω lin. 5K Ω to 5M Ω log., std. values. Only 2/- each.
Long spindle 4-7k Ω, 10k Ω, 22k Ω, 47k Ω, 100k Ω, 270k Ω, 470k Ω, 1M Ω, 2-2M Ω, lin. or log. Only 2/8 each.
Long spindle dual stereo: 10k Ω, 22k Ω, 47k Ω, 100k Ω, 220k Ω lin. or log. Only 8/6 each.

ALL GOODS BRAND NEW—NO SURPLUS

1968 CATALOGUE now ready, full of most up to date information essential to every serious user. Send 1/6 for your copy.
COMPONENT DISCOUNTS
10% on total order over £3.0.0. 15% on total order over £10.0.0. unless stated otherwise.
POSTAGE AND PACKING on orders up to £1, add 1/-; over, post free in U.K.
OVERSEAS ORDERS WELCOMED. Carriage charged at cost.

ELECTROVALUE Dept. P.W.3

32A ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Telephone: EGHAM 5533 (STD 0784-3)

RECEIVERS & COMPONENTS

(continued)

SUB-MINIATURE ELECTROLYTICS, 15 Volt, 2, 6, 8, 10, 15, 20, 30, 40, 50, 100 mfd. 8/6 per doz. 30 for £1. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield 8.

COMPLETE RANGE of Amateur, Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 4-20 watt, 12/6 Post Free. WHITSAM ELECTRICAL, 33 Drayton Green Road, West Ealing, W.13.

PLEASE MENTION

PRACTICAL WIRELESS

WHEN REPLYING TO

ADVERTISEMENTS

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 37/8, 11 element, 45/-, 14 element, 52/8, 18 element, 60/-, **Wall Mounting with Cranked Arm**, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. **Must Mounting with 2in. clamp**, 7 element, 42/8, 11 element, 55/-, 14 element, 62/-, 18 element, 70/-, **Chimney Mounting Arrays**, Complete, 7 element, 72/8, 11 element, 80/-, 14 element, 87/8, 18 element, 95/-, Complete assembly instructions with every unit. **Low Loss Cable**, 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

BBC · ITV AERIALS



BBC (Band 1), Telescopic loft, 25/-, External S/D, 30/-, "H", 22, 15.0.
ITV (Band 3), 3 element loft array, 30/-, 5 element, 40/-, 7 element 50/-, Wall mounting, 3 element, 47/8, 5 element 52/8. **Combined BBC/ITV**, Loft 1+3, 40/-, 1+5, 50/-, 1+7, 60/-, Wall mounting 1+3, 57/8; 1+5, 67/8; Chimney 1+3, 67/8; 1+5, 75/-.
VHF transistor preamps, 75/-.


COMBINED BBC1 — ITV — BBC2 AERIALS, 1+3+9, 70/-, 1+5+9, 80/-, 1+5+14, 90/-, 1+7+14, 100/-. Loft mounting only. Special leaflet available.
F.M. (Band 2), Loft S/D, 15/-, "H", 32/6, 3 element, 55/-, External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/4. Outlet boxes, 5/-, Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D. P. & P. 5/-, Send 6d. stamps for illustrated lists.

Callers welcomed — open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)
 27 Central Parade, New Addington
 Surrey (CRO-OJB)
 LODGE HILL 2266

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

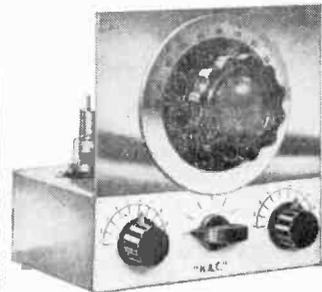

Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hains, etc.

IMPROVED 1969 RANGE

One-valve model "DX", complete kit—price 56/8 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS
 29 Old Bond Street, London W.1

Fabulous Value

Fantastic Bargain Offer

STEREOPHONIC KUBA "ROYAL" RADIOGRAM
 This radiogram chassis is offered complete with carefully matched loudspeaker system, two 10in. speakers, two 4in. Cone Tweeter and latest BSR UA70 Mono/Stereo record changer—a complete quality stereophonic radiogram at half normal price.

4 wavebands—AM/FM—8 pickups control, 8 watt push-pull output per channel—frequency response 30-20,000 cycles. EASY TO INSTALL, NO TECHNICAL KNOWLEDGE REQUIRED. ONLY **£79.19.6.**

11 P. terms available. Deposit £26.13.2 and 24 monthly payments of 55/7 (total H.P. £93.7.2). Send £27.10.8 today or write for free leaflet.

KUBA "IMPERIAL 666" STEREOPHONIC HI-FI RADIOGRAM CHASSIS—complete with two 10in. x 5in. speakers and the latest BSR Mono/Stereo record changer—a complete radiogram at half normal price. 4 Waveband AM/FM chassis with the very latest printed circuitry—7 push button control, 12 watts total output. Provision for stereo decoder. Only 47 1/2 Gms. plus P. & P. 17/8. EASILY FITTED. TECHNICAL KNOWLEDGE NECESSARY. H.P. available £17.6.6 deposit plus 24 monthly payments 36/2 (total H.P. £60.14.4). Send £18.4.0 today.

CALLERS WELCOME

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name
 Address

LEWIS radio 100 CHASE SIDE, SOUTHGATE. Dept. P189. LONDON, N.14. TELEPHONE 01-886 3733/9666

POST THIS COUPON NOW!

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME Block

ADDRESS Caps.

..... Please 3/69

BRITISH NATIONAL RADIO SCHOOL

PARTRIDGE APOLOGISE TO DEALER AND CUSTOMER

FOR delivery delays due to heavy demand
... We are doing our best

SEE YOUR JOYSTICK V.F.A. STOCKIST

All branches of R.S.C. Hi-Fi Centre Ltd.

All branches of Lasky's Radio

ASHFORD Middx. Echelford Communications
BATH Ryland Huntley
BIRKENHEAD R.S. Radio & Electrical Stores
BIRMINGHAM. Amateur Electronics
Chas. H. Young
BOURNEMOUTH. Forresters Nation Radio Supplies
BRADFORD. Radio Ham Shack
BRIGHTON. Arthur Sallis
BURNLEY. Trafalgar Supplies
CARDIFF. Weak Radio
CHELMSFORD. Radio Service
CHELTENHAM. Spa Radio
CHESTERFIELD. J. & A. Tweedy Ltd.
COVENTRY. Swanco Products Ltd.
CROYDON. Huggetts
DOWCASTER. B. Page
EDINBURGH. F. Brow & Co.
EXETER. Electrosure Ltd.
FOLKSTONE. John Guilding
GILLINGHAM Kent. B. J. Kayes
GLASGOW. R. M. E. Surplus Supplies
GOODMAYES. Unique Radio Ltd.
HALIFAX. Albert Hind Ltd.

HARTLEPOOLS. The Specialist Radio Shop
HERNE BAY. Purrys
HUDDERSFIELD. Radio Craft Ltd.
HULL. Short Wave
ILFORD. Radio Development Ltd.
LEEDS. George Blakey
Henry Electric Ltd.
LEICESTER. S. May Ltd.
LIVERPOL. Stephens-James Ltd.
LONDON. Alfred Innhoff Ltd.
112-116 New Oxford Street, W.1.
City Radio, 37 Bond Street, Ealing, W.5.
Daystrom, 233 Tottenham Court Road, W.1.
Harversons, 170 High Street, Merton, S.W.19.
Newbury Radio Ltd., 272 Romford Road, Forest Gate, E.7.
R. T. & I. Electronics Ltd., Ashville Road, E.11.
G. W. Smith, 3-34 Lisle Street, W.C.2.
LOUGHBOROUGH. Taurus Electronic Supplies
LUTON. Coventry Radio Ltd.

NEWARK. George Francis Electronic Supplies
NEWCASTLE UNDER LYNE. Sidney T. Chadwick
NEWCASTLE UPON TYNE. Richley & Freeman Ltd.
NEWPORT Mon. K. F. Paul Ltd.
NORWICH. Radiomatics
NOTTINGHAM. Petes Electronics Ltd.
OLDHAM. The Electronic Centre
PLYMOUTH. Radioparts
PURLEY. GHSFC, 45 Green Lane
READING. M. J. Milne & Sons Ltd.
ROMFORD. Newbury Radio Ltd.
SCARBOROUGH. Derwent Radio
SOUTHAMPTON. Frank Victor
SOUTH SHIELDS. J. R. Gough Electronics
ST. HELENS. Harold Stott Ltd.
SUNDERLAND. The Red Radio Shop
SWANSEA. W. J. Holt
WESTCLIFF ON SEA. Radio Constructors Co.
WORCESTER. Jack Porter Ltd.
WOLVERHAMPTON. Lings Radio & Electronics
WORTHING. G. W. M. Radio Ltd.

All direct from:

PARTRIDGE ELECTRONICS LTD. (PWC)

PROSPECT ROAD,

BROADSTAIRS, KENT

Phone: 0843-62535 (C.O.D. Orders)



RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only

high grade components and transistors.



LT55 6 WATT AMPLIFIER

A HIGH FIDELITY UNIT PROVIDING EXCELLENT RESULTS AT MODEST OUTPUT LEVELS.

Sensitivity 5 mv (max).
Frequency Response 30-20,000 cps—2dB
Harmonic Distortion 0.5% at 1,000 cps
Output for 3-8-15 ohm Loudspeakers.
Input Sockets for "Mike," Gram and Radio Tuner/Tape Recorder.

Recommended **9 gns**
Retail price
Size 9½ x 2½ x 5½in.
Controls (5) Volume, Bass, Treble, Mains Switch, Input Selector Switch.

LT66 12 WATT STEREO AMPLIFIER

A TWIN CHANNEL VERSION OF THE LT55 PROVIDING UP TO 6 WATTS HIGH FIDELITY OUTPUT ON EACH CHANNEL.



Recommended **16 gns**
Retail price
Size 12 x 3½ x 6in.

Switched Input Facilities
Socket (1) Tape or crystal PU
(2) Radio Tuner (3) Ceramic PU
Microphone.

Controls (8) Volume, Bass, Treble, Balance, Mains Switch, Input Selector Switch. Stereo/Mono Switch.

Facia Plate Rigid Perspex with black/silver background and matching black edged knobs with spun silver centres.

If required an attractive wood cabinet with satin Teak veneer finish can be supplied for any model. **70s.**
Prices from

Please send a stamped addressed envelope for full details of above units, also TUNER/AMPLIFIERS STEREO and MONO
AVAILABLE FROM YOUR LOCAL HI-FI DEALER

Wholesale and Retail enquiries to:

LINEAR PRODUCTS LTD, Electron Works, Armley, Leeds

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS

1R5, 1R5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 17/6. DAF96, DF96, DK96, DL96, 4 for 28/-.

024	4/6	12K8GT 7/-	DK96	7/-	EL41	9/6	PCL86	8/6	UC284	7/9
1A7GT	7/6	19B66G17/6	DL36	5/-	EL84	4/0	PEN44	12/6	UC285	6/6
1H5GT	7/3	20F2 13/6	DL92	5/9	EL90	5/-	PEN36C15/-		UCF80	8/3
1N5GT	7/9	20L1 16/9	DL94	5/9	EL96	5/-	PF120012/-		UC42	9/9
1R5	5/6	20P3 11/9	DL96	7/-	EM80	5/6	PL36	9/6	UCB1	6/6
1R5	4/3	20P4 18/6	DM86	5/9	EM81	6/9	PL81	7/3	UCL82	7/-
1T4	2/9	25U4GT11/6	DY87	5/9	EM84	6/3	PL82	6/6	UCL83	11/6
3B4	5/9	30C1 6/9	EABC80	6/6	EM87	7/6	PL84	6/6	UF41	9/9
3V4	5/9	30C15 13/-	EAF42	8/9	EY51	7/-	PL84	6/3	UF80	7/-
5U4G	4/6	30C18 9/-	EB91	2/3	EY86	6/3	PL500	12/-	UF85	6/9
5Y3GT	5/9	30F5 13/6	EB333	7/6	EZ40	7/6	PL504	12/6	UF89	6/3
8Z4G	7/6	30FL1 12/6	EB341	8/3	EZ41	7/6	PL508	15/-	UL41	9/6
6J00L2	12/6	30PL12 14/6	EBF80	6/-	EZ80	4/6	PL802	14/6	UL44	20/-
6AL5	2/3	30PL14 10/6	EBF89	6/3	EZ81	4/9	PM84	7/9	UL84	6/6
6AM6	3/6	30L1 6/-	ECC81	3/9	GZ32	5/9	PX25	10/6	UM94	7/6
6AQ5	4/9	30L15 14/-	ECC82	4/9	KT61	8/9	PY32	10/-	UY41	7/-
6AT6	4/-	30L17 13/-	ECC83	7/-	KT66	16/-	PY81	6/3	VP4B	10/6
6AU6	4/6	30P4 12/-	ECC84	5/6	ME140015/-		PY82	5/-	VP121	21/-
6HA6	4/6	30P12 11/6	ECC85	5/-	N78	14/9	PY83	5/9	Z77	3/6
6BE6	4/3	30P19 12/-	ECC80412/8		PABC80	7/9	PY88	5/9	Transistors	
6BJ6	7/-	30PL1 12/6	ECP80	7/-	PC86	9/6	PY88	6/3	AC107	3/6
6BW6	13/-	30PL13 14/6	ECP82	6/9	PC88	9/6	PY800	6/9	AC127	2/-
6C4	2/9	30PL14 15/-	ECH35	6/6	PC86	8/6	PY801	6/9	AD120	7/6
6F13	3/6	35L6GT 8/-	ECH42	10/6	PC97	8/6	R19	6/6	AD140	7/6
6F14	9/-	3W4 4/6	ECH81	5/9	PC900	8/3	R20	12/6	AF102	13/-
6P23	13/6	35Z4GT 5/-	ECH84	6/9	PC884	6/6	TH21C	9/9	AF115	3/6
6K7G	2/6	6063 12/6	ECL80	6/9	PC885	6/6	U25	13/-	AF116	3/6
6K8G	4/3	AZ31 9/-	ECL82	6/9	PC888	9/9	U26	12/-	AF117	3/6
6L18	6/-	B729 12/6	ECL83	9/6	PC898	10/6	U47	13/6	AF124	7/6
6V8G	3/6	CH35 10/-	ECL86	8/3	PCF89	9/9	U49	13/6	AF125	3/6
6V6GT	6/6	CL33 18/6	EF39	3/9	PCF80	9/9	U52	4/6	AF126	7/-
6X4	3/6	Y31 6/9	EF41	6/9	PCF82	6/6	U78	3/6	AF127	3/6
6X5GT	5/9	DAC32 7/3	EF90	4/9	PCF86	9/3	U191	12/6	OC26	5/9
7B6	10/9	DAF91 4/3	EF85	5/6	PCF80013/6		U301	13/6	OC44	2/3
7B7	7/-	DAF96 6/-	EF86	6/3	PCF801 7/-		U801	18/-	OC45	2/3
7C6	6/6	DF33 7/9	EF89	5/3	PCF802 6/6		UABC80	6/3	OC71	2/6
7Y4	6/6	DF91 2/9	EF91	3/6	PCF805 9/-		UAF42	9/6	OC72	2/6
10F1	15/-	DF96 6/-	EF94	4/9	PCF80611/6		UB41	6/9	OC75	2/6
10P13	15/6	DH77 4/-	EF183	6/-	PCF80810/6		UB41	7/9	OC81	2/3
12A17	3/9	DI81 10/9	EF184	5/9	PC182 7/-		UBC81	7/-	OC81D	2/3
12A06	4/9	DK32 7/6	EF190	6/6	PC183 9/-		UBF80	6/-	OC82	2/3
12A07	4/9	DK41 5/6	EL33	8/9	PC184 7/6		UBF89	6/9	OC82D	2/6
12A07	4/9	DK92 8/3	EL34	9/6	PC185 8/3		UC92	5/-	OC170	2/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

DUXFORD ELECTRONICS (PW)

97/97a MILL ROAD, CAMBRIDGE

Tel: 0223-63687

(Visit us—at our new Mail Order, Wholesale and Retail Premises)

MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/-

DISCOUNT 10% over £2
15% over £5

CERAMIC DISC CAPACITORS (Hunts). 500V ±20%: 100, 220, 330pF. -20%, +80%: 470, 680, 1,000pF. 5d each.

ELECTROLYTIC CAPACITORS (Mullard). -10% to +50%.

Subminiature (all values in µF)

4V	8	32	64	125	250	400
6.4V	6.4	25	50	100	200	320
10V	4	16	32	64	125	200
16V	2.5	10	20	40	80	125
25V	1.6	6.4	12.5	25	50	80
40V	1	4	8	16	32	50
64V	0.64	2.5	5	10	20	32
Price	1/6	1/3	1/2	1/-	1/1	1/2

Small (all values in µF)

4V	800	1,250	2,000	3,200
6.4V	640	1,000	1,600	2,500
10V	400	640	1,000	1,600
16V	250	400	640	1,000
25V	160	250	400	640
40V	100	160	250	400
64V	64	100	160	250
Price	1/6	2/-	2/6	3/-

POLYESTER CAPACITORS (Mullard)

Tubular, 10%, 160V: 0.01, 0.015, 0.022µF, 7d, 0.033, 0.047µF, 8d, 0.068, 0.1µF, 9d, 0.15µF, 11d, 0.22µF, 1/-, 0.33µF, 1/3, 0.47µF, 1/6, 0.68µF, 2/3, 1µF, 2/8.

400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d, 6,800pF, 0.01, 0.015, 0.022µF, 7d, 0.033µF, 8d, 0.047µF, 9d, 0.068, 0.1µF, 11d, 0.15µF, 1/2, 0.22µF, 1/6, 0.33µF, 2/3, 0.47µF, 2/8.

Modular, metallised, P.C. mounting, 20%, 250V: 0.01, 0.015, 0.022µF, 7d, 0.033, 0.047µF, 8d, 0.068, 0.1µF, 9d, 0.15µF, 11d, 0.22µF, 1/-, 0.33µF, 1/5, 0.47µF, 1/8, 0.68µF, 2/3, 1µF, 2/9.

POLYSTYRENE CAPACITORS: 5%, 160V (unencapsulated): 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 5d, 1,000, 1,500, 2,200pF, 6d, 3,300, 4,700, 5,600pF, 7d, 6,800, 8,200, 10,000pF, 8d, 15,000, 22,000pF, 9d.

1%, 100V (encapsulated): 100, 120, 150, 180, 220, 270, 330, 390, 470, 500, 560, 680, 820pF, 1/-, 1,000, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900pF, 1/3, 4,700, 5,000, 5,600, 6,800, 8,200, 10,000, 12,000, 15,000pF, 1/6, 18,000, 22,000, 27,000, 33,000, 39,000pF, 1/9, 0.047, 5,000, 0.056µF, 2/-, 0.068, 0.082, 0.1µF, 2/3, 0.12µF, 2/9, 0.15, 0.18µF, 3/-, 0.22µF, 4/-, 0.27, 0.33µF, 5/-, 0.39µF, 5/9, 0.47, 0.5µF, 6/3.

JACK PLUGS (Screened): Heavily chromed, 1/4in Standard, 2/9 each. Side-entry, 3/3 each.

Standard (Unscreened): 2/3 each.

JACK SOCKETS (1/4in Plug): With chrome insert, 2/9 each. Available with: Break/Break, Make/Break, Break/Make, Make/Make contacts.

POTENTIOMETERS (Carbon): Long life, low noise, 1W at 70°C. ±20% ≤ 1M, ±30% < 1M. Body dia. 1/2in. Spindle, 1in × 1/4in, 2/3 each. Linear: 100, 250, 500 ohms, etc., per decade to 10M. Logarithmic: 5k, 10k, 25k, etc., per decade to 5M.

SKELETON PRE-SET POTENTIOMETERS (Carbon): Linear: 100, 250, 500 ohms, etc., per decade to 5M.

Miniature: 0.3W at 70°C, ±20% ≤ 1M, ±30% > 1M. Horizontal (0.7in × 0.4in P.C.M.) or Vertical (0.4in × 0.2in P.C.M.) mounting, 1/- each.

Submin. 0.1W at 70°C, ±20% ≤ 1M, ±30% > 1M. Horizontal (0.4in × 0.2in P.C.M.) or Vertical (0.2in × 0.1in P.C.M.) mounting, 10d each.

RESISTORS (Carbon film), very low noise. Range: 5%, 4.7Ω to 1MΩ (E24 Series); 10%, 10Ω to 10MΩ (E12 Series).

1W (10%), 11d (over 99, 11d), 100 off per value 12/-, 1W (5%), 2d (over 99, 11d), 100 off per value 13/9, 1W (10%), 2d (over 99, 11d), 100 off per value 13/9, 1W (5%), 2d (over 99, 2d), 100 off per value 15/6.

SEMICONDUCTORS: OAS, OA81, 1/9, OC44, OC45, OC71, OC81, OC81D, OC82D, 2/-, OC70, OC72, 3/4, AC107, OC75, OC170, OC171, 2/6, AF115, AF116, AF117, ACY19, ACY21, 3/3, OC140, 4/3, OC200, 5/-, OC139, 5/3, OC25, 7/-, OC35, 8/-, OC23, OC28, 8/3.

SILICON RECTIFIERS: (0.5A), 170 P.I.V., 2/9, 400 P.I.V., 3/-, 800 P.I.V., 3/3, 1250 P.I.V., 3/9, 1500 P.I.V., 4/-, (0.75A), 200 P.I.V., 1/6, 400 P.I.V., 2/-, 800 P.I.V., 3/3, (6A), 200 P.I.V., 3/-, 400 P.I.V., 4/-, 600 P.I.V., 5/-, 800 P.I.V., 6/-.

THYRISTORS (5A): 100 P.I.V., 8/-, 200 P.I.V., 10/-, 400 P.I.V., 15/-.

SWITCHES (Chrome finish, Silver contacts): 3A 250V, 6A 125V, Push Buttons: Push-on or Push-off 5/-. Toggle Switches: SP/ST, 3/6, SP/DT, 3/9, SP/DT (with centre position) 4/-, DP/ST, 4/6, DP/DT, 5/-.

PRINTED CIRCUIT BOARD (Vero).

0.15in Matrix: 3 1/2in × 2 1/2in, 3/3, 5 1/2in × 2 1/2in, 3/11, 3 1/2in × 3 1/2in, 3/11, 5in × 3 1/2in, 5/6.

0.1in Matrix: 3 1/2in × 2 1/2in, 4/-, 5in × 2 1/2in, 4/6, 3 1/2in × 3 1/2in, 4/6, 5in × 3 1/2in, 5/3.

RECORDING TAPE (Finest quality MYLAR—almost unbreakable).

Standard Play: 5in, 600ft, 7/6, 5 1/2in, 850ft, 10/6, 7in, 1,200ft, 12/6.

Long Play: 3in, 225ft, 4/-, 5in, 900ft, 10/6, 5 1/2in, 1,200ft, 13/-, 7in, 1,800ft, 18/-.


SEND S.A.E. for JANUARY, 1969 CATALOGUE

SPEAKER SYSTEMS




THE CAXTON COLUMN This is a column cabinet. Size 22 1/2 x 3 x 6 1/2in., fitted with 3 speakers. This will handle 10 watts and will improve the quality of any tape recorder, or record player. Finished in wood grain cloth and sandstone Vynair. A real bargain at 59/6. P. & P. 10/6.

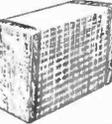THE MILTON. A Hi-Fi Bookcase Cabinet. Size 9 x 5 x 6in., with 5in. speaker. Finished in Teak cloth with bold silk front 30/-. P. & P. 4/6.



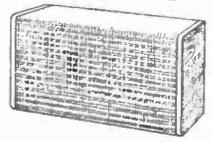THE IMP. Extension Speaker Cabinet. Wedge shaped, size 7 1/2 x 6 1/2in., fitted 7 x 4in. speaker. Covered with attractive walnut with fawn Vynair front. Keyhole slot in back. Only 25/8. P. & P. 4/6




THE STEREO. A superior extension speaker cabinet fitted with two 7 x 4in. speakers. Size 16 x 9 x 8 1/2in. Finished in fawn Vynair with natural/teak ends. 23. P. & P. 5/-.



DUO. Wedge shaped Speaker Cabinet. Size 7 1/2 x 7 1/2in., fitted 7 x 4in. speaker. Covered in attractive two tone Vynair. Price 32/6. P. & P. 4/6.



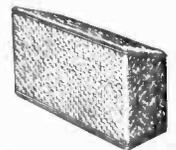CLARENCE. Extension Speaker Cabinet fitted 8 x 5in. speaker. (3 ohms imp.) and volume control. Size 10 1/2 x 8 1/2 x 4 1/2in. Finished in black and grey Vynair. 45/-. P. & P. 4/9.



THE SCOTT. Table top or wall mounting speaker. Size 10 1/2 x 5 1/2in., tapered as illustrated. Fitted 1 1/2 x 8in. Speaker with volume control. Finished in teak cloth and contrasting Vynair. (Please state 3 or 15 ohm imp.) 24.5.0. P. & P. 7/8.

All cabinets are new and speakers are mounted on jin. chipboard baffles. All speakers ex TV reconditioned hi flux magnet. All carefully tested before despatch.


SPEAKER ENCLOSURES



The Baker. Size 8 x 15 1/2 x 2 1/2in. Teak veneered top and sides. Fawn Vynair covered front. Cut out for 12in. speaker and 3in. tweeter with port and internal bass reflex board. Fitted rubberfeet. 26.15.0. P. & P. 10/6.



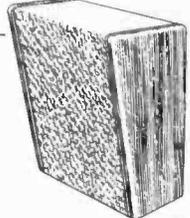The Cowdrey. Corner Cabinet in natural teak finish for 13 1/2 x 8in. speaker also cut out for tweeter. 23.15.0. P. & P. 8/6.



The Tennyson. Wedge shape for table or wall mounting 13 1/2 x 16 x 8 1/2in. Cut out for 13 1/2 x 8in. speaker with port. Finished wood grain cloth and matching Vynair. 22.2.6 P. & P. 7/6.

The Vernon. Table top or wall mounting enclosure for 13 1/2 x 8in. speaker (similar to The Scott illus. above).

27/8. P. & P. 6/-.

The Haydon. 16 1/2 x 15 x 7 1/2in., wood grain cloth and contra-tin Vynair covered suitable for 12in. speaker, 22/6. P. & P. 9/-.

SPEAKERS: Elac Heavy duty Ceramic Magnets 11,000 line, 10in. round, 10 x 6in. 3 ohm, or 15 ohm, 48/6. P. & P. 6/6, 8in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 13 1/2 x 8in. 15 or 3 ohm 45/-, P. & P. 3/6. E.M.I. 2in. tweeter, 15/-, P. & P. 1/6. E.M.I. 13 1/2 x 8in. fitted two 2 1/2in. tweeters, 15 ohms, 77/8. P. & P. 4/6. R.M.I., 13 1/2 x 8in. (15 ohm) Hi Fi Quality, 25.19.6. P. & P. 4/6. E.M.I., Woofers, 6 1/2 x 6 1/2in. square, 3 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/-. EAGLE Crossover units, 3 or 16 ohms, 14/6. P. & P. 1/-. Bakers 12in., 25 watt, 15 ohm, 28.6.0. P. & P. 3/6. All other speakers supplied—Goshuans, Bakers, W.B., Wharfedale, Eagle, Tripletton.

VYNAIR Widths from 40 to 54in., 17/8 yd. off roll. P. & P. 1/9, 4 yard, 9/-.

P. & P. 1/9. Send 1/- stamps for samples.

SPEAKER MATCHING TRANSFORMERS. 3, 7, 15 ohms, 8 watt, 11/6. P. & P. 1/6.

CARTRIDGE: Reuter STD/2, 17/6. (C1911), 20/-, Mono Sonotone, 275S, 15/-, Acou-Sound 6167/2 high output, 18/6. P. & P. 1/-.

MICROPHONES: Xtal Hand Mikes. B1201 with stand, 54/8. P. & P. 3/6. ACOS Mike 45, 21/-, ACOS Mike 40, 18/6. Dyn. Mike 13M-891, 30/-, CM2 Xtal, 12/8. Telephone Pick-up, 10/6. P. & P. 1/-. Xtal lapel Mike, 7/8. Guitar Mike, 12/6. P. & P. 1/-.

TRANSISTOR ELECTROLYTICS: 1, 2, 4, 5, 8, 10, 16, 26, 32, 50, 100 mfd 15 volt working, 1/3. P. & P. 1/-. 250 mfd DC, 3 1/2-500 mfd 12v, 3/-, 500 mfd 25v DC, 3/6. P. & P. 1/-.

VACUUM CLEANER LEAD. 5 1/2yds. twin cable with moulded 5 amp. two pin plug. 4/8. P. & P. 1/6.

EX- "PAM" TRANSISTOR RADIO CABINETS. Fitted 36in. telescopic aerial, car aerial socket, two 3-pin sockets, perspex dial 12 1/2 x 3 1/2in. Cabinet size 13 1/2 x 4 1/2 x 8in. finished brown and grey. 25/-, P. & P. 4/6.

EARPIECES WITH COIL and 3-5 mm. plug, 8 ohm magnetic, 3/-, 250 ohm, 47/-, 150 ohm with coil, 6/6. P. & P. 1/-.

TRANSISTOR SPEAKERS 8 ohm 2in., 8/8, 3in., 10/8, 3 1/2in., 12/8, P. & P. 1/-.

FERROX RODS: 6 x 3/4in., 2/6; 4 x 1 1/2in., 2/-; 6 x 1in., 2/6; 8 x 1in., 3/-, P. & P. 1/-.

FERROX RODS WITH COILS, 4 1/2 x 1 1/2in., 3/6; 8 x 1 1/2in., 5/6. P. & P. 1/-.

ROTARY SWITCHES: 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/-.

FLYMO KEY PUSH BUTTON SWITCHES. 7 button inc. mains on off. 6 banks of 6 P.C.C.O., 3/6. P. & P. 1/-.

SIEMENS CONTROL COOLED RECTIFIERS. 250v 350mA., 4/8. P. & P. 1/-.

BROADWAY Electronics
92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON, S.W.17 Telephone 01-672 3984 (Closed all day Wednesday)
(Few minutes from Tooting Broadway Underground Station)

The following blueprints are available from stock. **Descriptive text is not available but the date of issue is shown for each blueprint.** Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to *Blueprint Department, Practical Wireless, I.P.C. Magazines, Tower House, Southampton Street, London, W.C.2.*

The Strand Amplifier }	(Oct. 1962) 5/-	Transistor Radio Mains Unit }	(June 1964) 5/-
The PW Signal Generator }		7 Mc/s Transceiver }	
The Berkeley Loudspeaker Enclosure }	(Dec. 1962) 5/-	The Citizen (December 1961) }	5/-
The Luxembourg Tuner }		The Mini-amp (November 1961) }	5/-
The PW Britannic Two }	(May 1962) 6/-	The Beginner's Short Wave Superhet (Dec. 1964)	5/-
The PW Mercury Six }		The Empire 7 Three-band Receiver (May 1965) ..	5/-
Beginner's Short Wave Two S.W. Listener's Guide }	(Nov. 1963) 5/-	Electronic Hawaiian Guitar (June 1965) }	5/-
The Celeste 7-transistor Portable Radio }	(June 1963) 5/-	Progressive SW Superhet (February 1966) }	5/-
The Spinette Record Player }		Beginner's 5-Band Receiver }	(Dec. 1966) 5/-
		Home Intercom Unit }	

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 7th March, 1969 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, MARCH 1969

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT

Mono or Stereo Audio. Equipment developed from Dinsdale Mk.II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM £15.5.0

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately

SEND FOR FREE BROCHURE (No. 21) TODAY!
DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD




Acclaimed by everyone MAYFAIR ELECTRONIC ORGAN

A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 165 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle. A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service.

Once built the 'MAYFAIR' will then provide years of enjoyable entertainment. **ONLY 99 Gns.**
Call in. See it and play it yourself.

ORGAN COMPONENTS	Deferred terms available.	BUILT AND TESTED
We carry a comprehensive stock	COMPLETE KIT	Deposit £36.8.0
of organ components for	Deposit £29.19.0	12 monthly payments of
TRANSISTOR AND VALVE FREE	12 monthly payments of £7.	£9. Total £144.8.0.
PHASE designs	TOTAL £113.19.0	RHYTHM UNIT
Ask for BROCHURE 9	EXPORT ENQUIRIES INVITED	£59.10.0 pp. 10/-

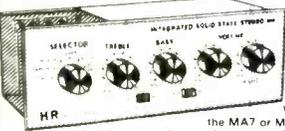

INTEGRATED SOLID STATE TRANSISTOR POWER AMPLIFIERS

Complete with full Bass Treble, Volume and Selector Controls
MA66 12 WATTS STEREO
We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways, being suitable for use with all types of PICK-UPS, TUNERS, DECKS and MICROPHONES—with fantastic power and quality with far greater adaptability with freedom for battery or mains operation. Output is from 3 1/2 OWMS. Whether you require a home or portable Hi-Fi installation, electronic guitar, P.A. System, Intercomm the MA7 or MA66 will FILL THE BILL.
for complete listening satisfaction choose either the
£8.10.0 OR THE STEREO **MA66 £16.10.0**
OPTIONAL MAINS UNIT P520 82 8d p.p.4 Suitable for either model.
Illustrated leaflets 12 and 14 FREE on request. Demonstrations Daily at our 309 Edgware Rd. Branch.

SINCLAIR EQUIPMENT

IC10 Integrated Circuit Amplifier	56/8
Z12 Amplifier	89/8
Micromatic (Kit)	49/8
Micromatic (Built)	59/8
P24 Power Unit	99/8
Stereo 25	£9.19.0
Q14 Speaker System	£7.19.0

All POST PAID. Delivery from stock.

DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 transistors plus diode, push pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.
TOTAL COST £6.19.6. P.P. 4/6
TO BUILD Send for Brochure 1

NEW MODELS NOMBEX TRANSISTORISED Test Equipment

MODEL	PRICE	Leaflet
£ s. d.	No.	
22 Power Supply	14 0 0	22
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	25
32 C.R. Bridge	10 10 0	26
33 Inductance Bridge	20 0 0	29

Send for descriptive illustrated Brochure.

QUALITY CAR RADIOS

A precision engineered car radio that's perfect company for long hours on the road. Has quick push button operation for immediate station selection and choice of Medium or Long wave frequency. Output of 31 watts ensures crisp top quality sound even at high motoring speeds. Includes full accessories and instructions.
POSITIVE/NEGATIVE EARTH PRICE: £12.12.0 pp. 4/6
MANUAL as above £8.19.6 but with single MW/LW Push Button.
Ask for Leaflet 2

MULLARD 1 WATT AMPLIFIER

PORTABLE TRANSISTOR UNIT with volume control. Many uses: Intercom, Baby Alarms, Circuit Practice, Telephone or Record Player Amplifier.
Optional Resine covered Wood cabinet 12 x 9 x 4 1/2. 7 x 4 in. speaker. 17/6.
Uses P9B battery.
45/- 3/6d
Ask for Leaflet 2

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK you need a MARTIN RECORDAKIT. This comprises a special high quality 8 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER which when built will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.

2 Track 36 gns. 4 Track 39 gns.
P.P. 22/6 either model.
Kit comprises: Deck Amplifier, Cabinet and speaker, with MICROPHONE 7 in 1 200 ft. tape, spare spool!
ALL UNITS AVAILABLE SEPARATELY. Today's Value £60.
ASK FOR BROCHURE 6

VHF FM SUPERHET TUNER MKII

5 MULLARD TRANSISTORS & 4 DIODES - 300 Kc/s BANDWIDTH - PRINTED CIRCUIT CONSTRUCTION - HIGH FIDELITY REPRODUCTION MONO AND STEREO.
A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and with the decoder atmospheric broadcast. There is no doubt about it—VHF FM gives the 'real' sound! Excellent stability, economically priced.
TOTAL COST £6.19.6
DECODER £5.19.6 (CABINET 20/- EXTRA) ASK FOR LEAFLET 3

NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES
*RM12 1.35 volts 3600 mAh OUR PRICE 10/- each Size 2 1/4 x 1 1/2
*RM25 10.35 volts 350 mAh Pack of 8 Size 2 1/4 x 1 1/2
OUR PRICE 10/- each
Easily split into eight 1.35v cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required.
QUANTITIES AVAILABLE.

GARRARD RECORD DECKS

MANUFACTURERS—DISTRIBUTORS

We publish a QUANTITY, SEMI-CONDUCTOR BULLETIN listing over 500 different devices available FROM STOCK in medium to large quantities at KEEN PRICES coupled with PROMPT DELIVERIES.
TO OBTAIN YOUR COPY WRITE TO US (on Company headed Notepaper, please) requesting our SEMI-CONDUCTOR BULLETIN FOR TELEPHONE QUOTATIONS. PHONE (01) 723 1008/9 Extn 4 (01) 723 0401 Extn 4.

We purchase medium to large quantities of Transistors and Devices excess to Manufacturers and Distributors requirements.

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 types. Send for your FREE COPY TODAY. (list 36)

S.C.R.'s from 5/-
Field Effect Transistors from 9/6
Power Transistors from 5/-
Diodes and Rectifiers from 1/6

BRAND NEW All below list price

2025 Mono/Stereo	£ 9 9 0
3500 LW with ST4HC	10 10 0
SP25 Mk II	12 19 6
LAB80 Mk II	26 0 0
AT60 Mk II	14 10 0
3500 Mono/Stereo	12 19 6
401	28 10 0
4A75	21 10 0
5L55	12 10 0
5L65	16 10 0
5L75	32 10 0
5L95	41 10 0
470 Mk II	12 12 0

Send for illustrated brochures 16, 17 Complete range of accessories available

Hi-Fi equipment to suit EVERY POCKET

VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE RD.

for all leading makes AMPLIFIERS TUNERS DECKS SPEAKERS MICROPHONES TEST EQUIPMENT SYSTEMS
ALL WITH DISCOUNTS
Ask for Hi-Fi Stock List Leaflet 16.17
IT WILL PAY YOU TO PAY US A VISIT!

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)
The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE
Complete with 10/- worth discount vouchers
FREE WITH EVERY COPY
* 32 pages of transistors and semi-conductor devices, valves and crystals.
* 210 pages of components and equipment.
* 70 pages of microphones, decks and Hi-Fi equipment.

6,500 ITEMS
320 BIG PAGES
Send today 7'6 Post etc 2/

HENRY'S RADIO LTD

OPEN MON.—SAT. 9 a.m.—6 p.m. THURS. 9 a.m.—1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723 6963