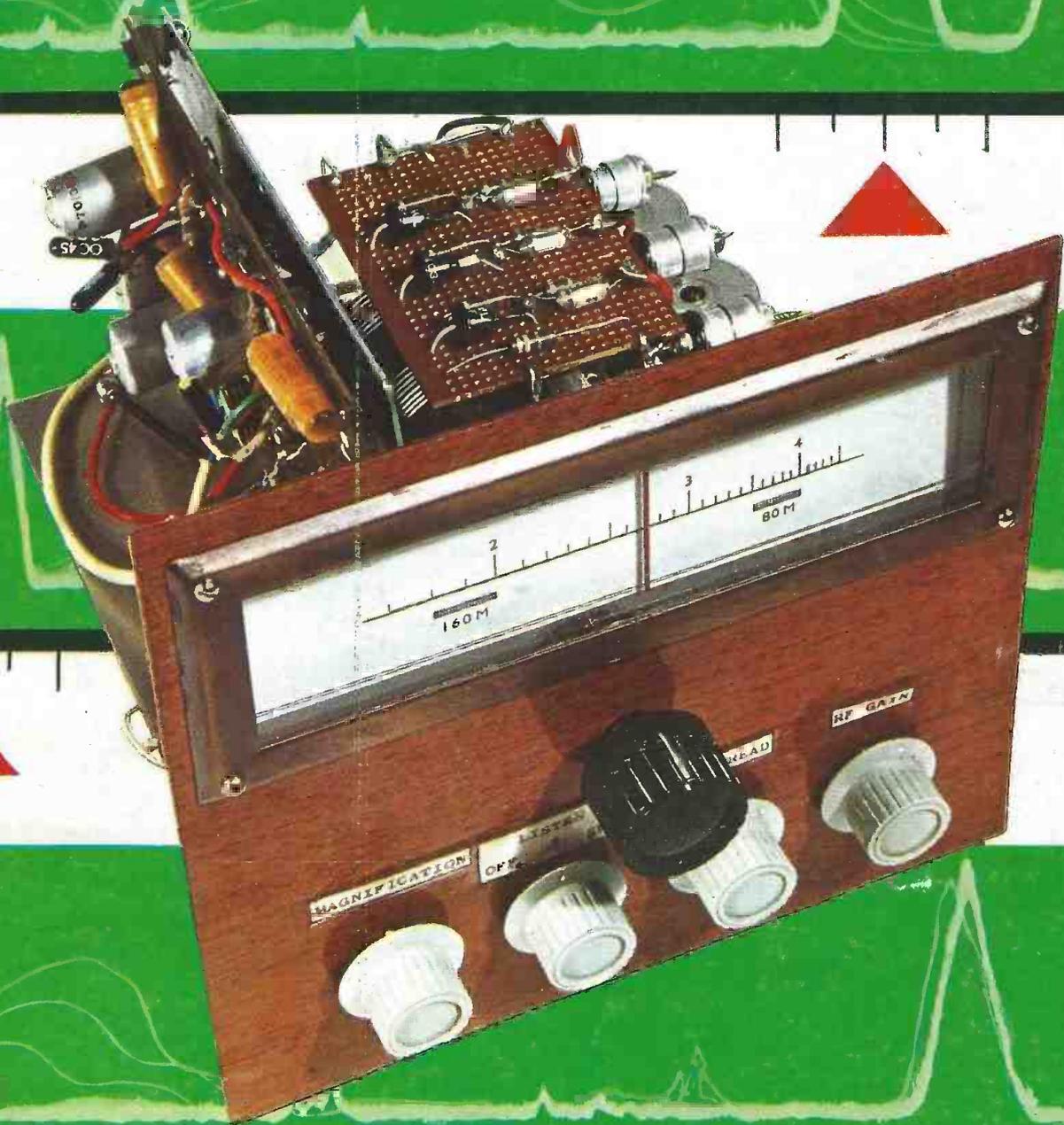


# PRACTICAL WIRELESS

JANUARY  
1970

3'0

## PANORAMIC RECEIVER



**Also: LOW NOISE MICROPHONE MIXER**

# VALUABLE NEW HANDBOOK

# FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

**On 'SATISFACTION or REFUND of FEE' terms**

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

**WHICH OF THESE IS YOUR PET SUBJECT?**

**RADIO ENGINEERING**  
Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

**ELECTRONIC ENG.**  
Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Prac. Electronics — Radar Tech. — Frequency Modulation — Transistors.

**ELECTRICAL ENG.**  
Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Elec. Engineering.

**MECHANICAL ENG.**  
Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work—Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

**CIVIL ENGINEERING**  
Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

**AUTOMOBILE ENG.**  
Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Elec. Equipment — Garage Management.

**WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.**

Which qualification would increase your earning power? B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

**British Institute of Engineering Technology**  
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER - GUIDANCE

**PRACTICAL EQUIPMENT**

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

**INCLUDING TOOLS**

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.**

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy now—FREE and without obligation.



**POST NOW!**

TO B.I.E.T., 453A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**

**FLOG LIST No. 4**

**FANTASTIC BARGAIN**

**sale**

**discount**

**H.I.F.I. systems.**

**WIEN. It's Unequaled**

1. Model FMX-1917 AM/FM Stereo Tuner with Decoder. Value £61.19s. Complete with 2 Jason high compliance speaker enclosures (8 ohm) in matching "rosewood" finish. For Only **38 gns.**

2. As 1 above but complete with Garrard 2025 T/C latest deck. Plinth & perspex super cover. Sonotone 9TAHC Diamond cart. **55 gns.**

3. As 2 above but with famous SP25 semi-transcription deck. **58 gns.**

**TELETON. It's Elegant**

4. Famous F-2000 AM/FM Stereo Tuner with Decoder. Complete with 2 Jason high compliance speaker enclosures (8 ohm) in matching "rosewood" finish. Greatly reduced. **49 gns.**

5. As 4 above but complete with Garrard 2025 T/C latest deck. Plinth & perspex super cover. Sonotone 9TAHC Diamond cart. **66 gns.**

6. As 5 above but with famous SP25 semi-transcription deck. **69 gns.**

NOTE: All Prices are subject to alteration without prior notice as present stocks run out.

**Jason** Garrard SP25 MKII TAPE PRICE £11.19.6

**TELETON F-2000 AM-FM STEREO TUNER AMPLIFIER** 38 gns

**I N D E X**

SECTION.	PAGE-COLOUR
H.I.F.I. SYSTEMS	Front Page
AMPLIFIERS	2 Buff/Brown
AMPLIFIERS	3. Black/Gold
Pre-amplifiers	
BATTERIES	Chargers 4. Black/Gold
Eliminators	
CABINETS	Chassis... 5. Red/Blue
CABLES & WIRES	6. Green/Blue
CONDENSERS	6
ELECTRICAL EQUIP.	7. Brown/Blue
EX-GOVERNMENT EQUIP.	8. Brown/Green
KNOBBS	8
LOUDSPEAKERS	
Cabinet & Chassis	
MICROPHONES	9. Green/Gold
PLUGS & SOCKETS	10. Green/Buff
RECEIVERS	10
RECORD DECKS	11. Black/green
RECORD PLAYERS	11
SCIENTIFIC INSTRUMENTS	12. Brown/green
SWITCHES	12
TAPE RECORDERS	12
TAPE REPRODUCERS	13. Green/Pink
TEST EQUIPMENT	13
TRANSFORMERS	4. Black/ellow
RECTIFIERS	4. Black/Green
TUNERS	
MISCELLANEOUS	Black/Buff
BARGAIN PARCELS	Black/Pink
T.V. TUBES	17
TRANSISTORS	17
VALVES	Green/Yellow
VALVES	19

**NEW! WIEN FMX-1917 AM-FM STEREO TUNER AMPLIFIER**

R. R. Price £11.19.6

**TECHNICAL TRADING**

★ LONDON

★ BRIGHTON

★ PORTSMOUTH

★ SOUTHAMPTON

**XMAS GIFTS?**

Your enquiries welcomed at all Branches or by Mail Order

**★ BUMPER ENLARGED 19 PAGE FLOG LIST 100's OF OFFERS.**

FILL IN COUPON NOW AND SEND TOGETHER WITH ONE SHILLING IN STAMPS TO ENSURE YOUR COPY

**POST NOW FOR "FLOG LIST"**  
To TECHNICAL TRADING CO., PARK CRESCENT PLACE, BRIGHTON. Please send "Flog List", without obligation, to

NAME .....  
BLOCK CAPITALS PLEASE

ADDRESS .....

..... PW 1.70

OR CALL AT YOUR NEAREST BRANCH

- ★ A FEW EXAMPLES!
- ★ QUANTITY DISCOUNTS!
- ★ GUARANTEED GOODS!
- ★ MANY NEW OFFERS
- ★ ARRIVING FOR XMAS

**GARRARD 3000 LM Autochange Deck**, complete with diamond 9TA HC Cartridge. Huge saving at only... **10gns.**

**MODULES with instructions**  
ADASTRA Electric E1315 organ, 22/6; E1316 Code oscillator, 22/6; E1317 Wireless code oscillator, 22/6; E1318 Dual lamp flasher, 22/6.

**Jason KITS**

**FANTASTICALLY POPULAR TAPE**

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-f, wide range recording characteristics as top grade tapes. Quality control manufacturer. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. **TRY ONE AND PROVE IT YOURSELF.**

Standard Play		Long Play	
3in. 150ft.	2/8	3in. 225ft.	2/8
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,500ft.	25/-
5in. 1,200ft.	15/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	3in. 600ft.	8/6

Postages 1/- reel.  
Post Free less 5% on three reels.  
Quantity and Trade enquiries invited.  
NOTE: Large tape stocks at all branches

**TAPE RECORDERS—including**

- ★ NOVAC (Belgian Philips) Super-Stereo T/R black/teak wood finish, 2 mikes. Deib. spkrs. Normal value approx. £85—in makers' boxes... **49 gns.**
- ★ SEARF ED504 Super mains/batt. portable 5in. spool. castan drive m/c mike. 5 yr. guar. approx. £10 under retail list... **28 gns.**
- ★ SEARF ED706 professional style, vert. op. 7in. spool. 5 yr. guar., superb value, large savings... **49 gns.**

**RECEIVERS—including**

- TOKYO Pocket Radio** with amazing loudspeaker reproduction complete with E.R.C. headphone, battery. Really superb value present at only... **55/-**
- WIEN PILOT II. Aircraft/MW receiver**... **11 gns.**
- ERRES. 4-band L/M/B/FM large type wooden cases, 5in heavy speaker, car socket—bargain offer**... **12 gns.** (normal value approx. 25 gns.!!)
- FMT940 F.M. TUNER** High sensitivity, 21V, high fidelity, response 20-20,000 cps. tuning meter, AF3 built-in power pack, attractive plinth, provisioned for multi-plex (RRF over £30) Super snip... **23 gns.**

**LOUDSPEAKER CHASSIS—including**

- 10 x 5in EMI ceramic 8 ohms... **25/-**
- Elae 7 x 4in. 25 ohms (car radio)... **15/-**
- Plessey 5 x 3in. 30 ohms... **12/-**
- Goodmans 6 x 4in. 8/10 ohms... **15/-**
- EMI 8 x 5in. heavy ceramic, 8 ohms... **25/-**
- Elae 9 x 6in. ceramic, 8 ohms, super... **39/-**
- EMI 10 x 6in. 8 ohms, ceramic... **35/-**
- Rolls Standard silver 10 x 6in. 8 ohms... **29/-**
- 1 1/2 x 2in Westwell 8 ohms midjet speakers... **8/6**
- 3in. round 15 ohm speakers... **9/6**
- 3in. round 8 ohm speakers... **9/6**
- 4in. round 125 ohm speakers... **9/6**
- 4 1/2in. round HI-Flex 8 ohm... **12/6**
- Lichtgewicht HI-Flex 8 ohm... **13/6**
- 12in. B & A with tweeter... **35/-**
- EMI 8 x 13in. 3 ohms... **45/-**
- EMI 8 x 13in 15 ohms... **45/-**
- Celestion 3 1/2in. round 125 ohms... **8/6**

**MIXED BARGAIN PARCELS ★★★**

Selected from variable condensers, I.F. coils, loudspeakers, plugs, sockets, knobs, potentiometers, condensers, resistors, nuts, bolts, cabinet fittings, switches, valves, transformers, lamps, complete p.c. boards, chokes, rectifiers, transistors, etc., etc. OFFERED at a small fraction of list value. DUE TO HEAVY DEMAND, we now pack them in several sizes—BE AMAZED!—TRY ONE NOW: 3in. parcel (post 3/-), 9/-, 7in. parcel (post 5/-), 17/6; 14in. parcel (post 6/8), 29/-.

**FANTASTIC BARGAIN OFFER**

**PARCELS OF POTENTIOMETERS**  
Twenty-five mixed types, our selection, from ganged, presets, switched, un-switched, tandems, 10g. and 1in., at approx. 4d. each!... **9/6.**

**AMPLIFIERS—including**

- SINCLAIR PACKAGE DEAL** 2 x Z12 amps, P24 power supply, Stereo 85 pre-amps... **231**
- MINET. 3-4W AC amplifier chassis—sacrificed price**, £3.10.0
- VALVE RECORD PLAYER AMPLIFIERS. 4W output with 2 valves UY85, UL84.**... **39/-**
- DITTO high gain UCL82 valve**... **45/-**
- ADASTRA 3-3 ditto de luxe model with base and treble controls**... **5 gns.**
- ADASTRA 5W+5W stereo transistor amplifier**... **10 gns.**
- ADASTRA NT100 super, compact, high-powered 12V 10W (car, etc.) amp.**... **11 gns.**
- ARENA F210 superb Danish stereo amp., complete in wooden plinth, magnetic/crystal inputs**... **29 gns.**
- DJ PUBLIC ADDRESS AMPLIFIERS**
- DJ 100 transistor amp 35W multi-input black portable case**... **39 gns.**
- DJ 106 ditto, 70W, ideal super power guitar use**... **55 gns.**
- EAGLE Transistorised Stereo TSA20 20W per channel RMS magnetic crystal Fantastic performance**... **22 gns.**

**TECHNICAL TRADING**

Stockists of Leak, Quad, Goodman, Armstrong, Tripletone Linear, Rogers, Truvox, Ferrograph, Warfedale, etc., etc

- ★ **LONDON** 10 Tottenham Court Rd., W1 Tel. MUSeum 2639
- ★ **BRIGHTON** 6 Queens Road Tel. 28975
- ★ **PORTSMOUTH** 350-352 Fratton Rd. Tel. 22034
- ★ **SOUTHAMPTON** 72 East Street Tel. 26851

★ ALL MAIL ORDER TO  
★ **BRIGHTON** Devonian Court, Park Crescent Place. Tel. 680723

24-hour telephone C.O.D. Order Recording Service.

POSTAGE: ADD 1 lb. 1/-; 1 1/2 lb. 2/6; 6 lb. 4/6; 10 lb. 6/-; 14 lb. 7/6.

Wide range of audio equipment and electronic components in all branches at keenest prices. Complete installation quotations a speciality.

# Lasky's

## EXCLUSIVE HI-FI STEREO TUNER AMP. OFFER THE MT-65 CHASSIS

Solid state AM/FM multiplex tuner with FET front-end/17+17 watts stereo amplifier by world famous manufacturer. Frequency response 20-45KHz. Inputs—2.3mV mag p/u and 140mV tape play. Tape record output. Controls: Left/right volume, bass, treble, loudness, monitor. Tuning meter and stereo beacon. Stereo 'phone jack. Machined stainless steel front panel. Overall size 20 x 3 3/8 x 16in.

**LASKY'S PRICE £78.0.0** CARRIAGE 12/6

### DE-LUXE "COMPACT" PACKAGE OFFER LASKY'S PACKAGE

MT-65 Chassis	£78	0	0
GARRARD AP-75 3-speed Single Player	£23	18	7
AUDIO DEVELOPMENT AD-96K Magnetic Cartridge	£5	18	6
2 WHARFEDALE DENTON Speaker Systems	£36	0	0
"Compact" Teak Cabinet (as shown)	£7	10	0

**PRICE**

**£132.0.0**

U.K. carriage 40/-  
All units avail. separately



## TMK METER KITS

These two meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position; the Model 200 also has the range selector in position. The highest quality components and 1% tolerance resistors are used throughout. Both offer professional standards of accuracy. Supplied complete with full constructional, circuit and operating instructions.

### MODEL 200

**20,000 O.P.V. MULTIMETER.** Features 24 measurement ranges with mirror scale. Large 3 x 2in. meter. Full scale accuracy: DCV and current: ±2%, ACV: ±3%, resistance ±3%. Special 10-6V DC range for transistor circuit measurements.

- DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV.
- ACV: 0-6-30-120-600-1,200V at 10K/OPV.
- DC Current: 0-0.6-6-60-600mA.
- Resistance: 0-10K-100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale).
- Capacitance: 0-002-0-2µF (AC 6V range).
- Decibels -20 to +63dB.
- Output: 0-0.05µF blocking capacitor. Uses two 1.5V (U.7 type) batteries. Black bakelite cabinet—Size 5 1/4 x 3 1/2 x 1 1/2in. Complete with test leads.



**LASKY'S PRICE 85/-** Post 3/6

### MODEL 5025

**50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES**

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is clearly indicated on the actual meter face. High speed rotary range selection knob; also features polarity reversal switch, shielded meter movement with overload protection circuit; Special uA and mA measurement ranges.



- DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0.25-125-500V at 50K/OPV.
- ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV.
- DCuA: 0-25uA at 125mA; 0-50uA at 250mA.
- DCmA: 0-2.5-25-250mA at 125mV; 0-5-50-500mA at 250mV.
- DC Amps: 0-5A at 125mV; 0-10A at 250mV.
- Resistance: 0-10M/ohms (13, 65, 650, 6.5K and 65K/ohms at centre scale).
- Output: Capacitor (0.1uF, 400VW) in series with ACV ranges.
- Decibels: -20 to +81.5dB in 10 ranges.
- Operates on two 1.5V (U.7 type) batteries. Black bakelite cabinet, size 5 1/4 x 6 1/2 x 2 1/2in. Strong, resilient plastic handle. Complete with test leads.

**LASKY'S PRICE £10.10.0** Post 5/-

ALSO AVAILABLE READY BUILT AND TESTED £12.10.0. Post 5/-.

## Garrard

**SL55 with J2006 stereo cartridge**

**£11.19.6** Post 5/-




<b>AUTOCHANGERS</b>	
1025 less cartridge	£6.9.6
1025 with GCM21 mono cartridge. Stereo compat.	£6.19.6
2025TC with 9TA stereo diamond cartridge	£8.17.6
AT60 Mk II less cartridge	£13.5.0
SL65B less cartridge	£15.19.6
SL75 less cartridge	£28.10.0
SL95 less cartridge	£35.0.0
A70 Mk II less cartridge	£13.19.6
BSR UA47 less cartridge	£5.9.6
<b>SINGLE PLAYERS</b>	
AP75 with AD.76K magnetic cartridge	£21.10.0

AP75 less cartridge	£18.10.0
SP25 Mk II less cartridge	£11.19.6
SRP22 Mains model less cartridge	£16.12.10
SRP22 Battery model less cartridge	£7.15.3
<b>TRANSCRIPTION DECKS</b>	
401	£28.10.0
<b>GARRARD BASES</b>	
WB1 £3.6.11; WB4 Mk II £5.8.11; WB5 £5.8.11.	
<b>CLEARVIEW PERSPEX COVERS:</b>	
SPC1 £3.5.0; SPC4 Mk II £4.6.6.	
Postage on all above 5/-	

## DENSHI BOARD KITS
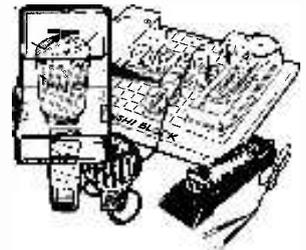
### EXPERIMENTAL AND EDUCATIONAL CIRCUIT SYSTEM

The DENSHI BOARD system enables the young experimenter and electronics hobbyist to produce a wide range of transistor circuits of increasing sophistication—without soldering or the use of any tools at all! Basically the system comprises a slotted circuit board into which plug-in components and bridge pieces are set to produce up to 30 different circuits. The components are encapsulated in transparent plastic blocks bearing the appropriate circuit symbol and value thus enabling even the complete novice to visually grasp the fundamentals of circuitry after only a few moments study. In addition each DENSHI BOARD KIT comes complete with an 80 page manual of circuits and data.



**THESE ARE JUST A FEW OF THE CIRCUITS YOU CAN BUILD IN MINUTES:**

VARIOUS RADIO RECEIVERS, AMPLIFIERS, MORSE CODE PRACTICE DEVICE, CONTINUITY TESTER, SIGNAL INJECTOR, SIGNAL TRACER, WIRELESS MICROPHONE ETC., ETC.

#### DENSHI BOARD KIT SR-1A comprises:

Base board; tuner block; 4 resistors; choke coil; transformer; 2SA transistor for RF; 2 diodes; 3 capacitors; battery block; morse key; antenna lead; crystal earphone; various bridge and connecting pieces. This kit permits the building of 16 basic circuits.

**LASKY'S PRICE 99/6** Post 3/6


**DENSHI BOARD KIT SR-2A** as SR-1A but with the following additional parts; 2SB transistor for AF; 2 resistors; 1 capacitor; crystal microphone; test probes; electrode additional connecting pieces; 9V battery. This kit permits the building of 30 basic circuits

**LASKY'S PRICE £7.2.6** Post 2/6

DENSHI KIT MANUALS are available separately at 4/6\* Post 6d.  
\*Refundable if you purchase kit.
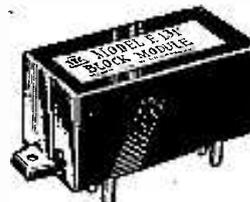
## LASKY'S ENCAPSULATED SOLID STATE MODULES

Size of each module only 1 1/4 x 1 1/4 x 3/8in. Ready for immediate use—just connect to power source (usually 9V battery), input and output. Encapsulated modules are shockproof and almost indestructible. Complete with full ins. Post 1/6 each.




<b>E-1311 Phono Pre-amp Module</b> —max. output 3V, RMS, input 50mV, input imp. 100kΩ, gain 28dB, RIAA compensation.	29/6
<b>F-1312 Tape Head Pre-amp Module</b> —max. output 4V, RMS, input 50mV, input imp. 100kΩ, gain 25dB, NARTE compensation.	29/6
<b>E-1313 Microphone Pre-amp Module</b> —max. output 4V, RMS, input 50mV, input imp. 100kΩ, gain 28dB, response 10-50kc/s.	29/6
<b>E-1314 Power Amplifier Module</b> —max. output 300mW, input imp. 1kΩ, gain 20dB, response 50-10kc/s, distortion 3% at 20mW.	29/6
<b>E-1315 Electronic Organ (tone oscillator) Module</b> —frequency 200-1,000c/s, output 80mW. For use with keyboard, variable resistors and 8Ω speaker.	25/-
<b>E-1316 Morse Code Practice Oscillator Module</b> —frequency 400c/s, output 80mW. For use with morse key and speaker.	25/-
<b>E-1317 Modulated Wireless Signal Transmitter</b> for use in test bench fault finding—frequency 400c/s-30Mc/s, tone freq. 400c/s. For use with any AM receiver.	25/-
<b>E-1318 Lamp Flasher Module</b> —flashes two miniature lamps alternately. For use with 6V, 100/200mA bulbs and 6V power supply.	25/-

# Lasky's

## NEW! FOSTER "Criterion" Mk II

2 SPEAKER TWO WAY BOOK-SHELF SPEAKER SYSTEM

Another high quality sub-miniature bookshelf system from Foster. The "Criterion" Mk. II is a sealed infinite baffle type enclosure using 5 1/2 in. bass/mid-range woofer with rolled cloth edge and a 2 1/2 in. HF cone type tweeter. The compact cabinet is constructed of 3/4 in. laminate with handsome oiled walnut veneer finish and black woven plastic gauze front panel with satin chrome edge insert. SPEC: Frequency range 90-20,000Hz. Power handling 10 watts. Impedance 8 ohms. HF crossover. Screw tag connections at rear. Size 12 1/2 x 7 1/2 x 6 1/2 in. The performance of the "Criterion" is superior to many larger and more expensive units and at Lasky's exclusive price offers absolutely unbeatable value.

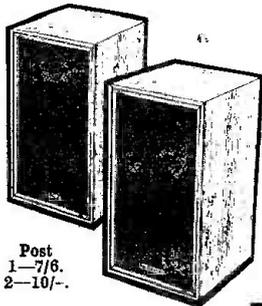


Post 1-7/6. 2-10/-.

LASKY'S PRICE £9.10.0 or 2 for £17.10.0
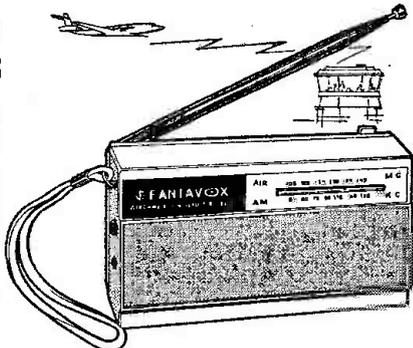
## FANTAVOX TV-1008

VHF AIRCRAFT BAND AND AM RECEIVER

The first pocket size Receiver of its type allowing you to "tune-in" anywhere to the entire air-to-ground, ground-to-air communications band covered by 108-137Mc/s in addition to full AM medium wave band cover of 535-1605Kc/s. An extremely sensitive 10 transistor and 2 diode, superhet circuit plus 1 variable capacitor and 1 thermistor. Intermediate frequencies: AM-455 Kc/s; VHF-10.7Mc/s. Output power: 200mW. 2 1/2 in. Permanent Dynamic 8 ohm speaker, earphone also provided for "silent" listening. A built-in ferrite rod aerial is provided for AM reception and a fully directional telescopic antenna for VHF reception—the latter when collapsed neatly clips across the top of the set. Power is from 4-1.5v penlight cells and a jack socket for connection to a suitable AC converter is also provided. The Model TV-1008 is extremely well made and finished in grey plastic with metallic blue speaker grille, chrome telescopic antenna; attached wrist strap is also provided. Size 6 1/2 x 3 1/2 x 1 1/2 in. Complete with batteries, magnetic earphone, instructions etc.



LASKY'S PRICE £8.7.6 Post 2/6

## MIDLAND Model 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1605Kc/s, 88 to 108Mc/s respectively—with no electrical conversion or connection required. The Model 10-502 self powered by one 9V (PP3 type) battery is merely placed close to the receiving set and then tuned over 110 to 135Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 18in. chrome telescopic antenna, size only 4 x 2 1/2 x 2 1/2 in. (inc. knobs). Complete with battery and full instructions.



LASKY'S PRICE 79/6 Post free

### GET YOUR LASKY'S AUDIO-TRONICS PICTORIAL

16 colour page catalogue in large 16 x 11in. format packed with 1,000's of items from our vast stocks. Hi-Fi, Radio, Electronics, Test Equipment, Components etc., etc.  
Send 1/- for post only and inclusion on our regular mailing list (5/- overseas)

## SCOOP! THE WORLD'S SMALLEST 6 TRANSISTOR

TWO WAVEBAND RADIO RECEIVER Over 10,000 sold

The Astrad ORION



Made to the highest space-age standards—this remarkable micro-set measures only 1 1/2 in x 1 3/4 in x 5 1/2 in. yet it contains 6 transistors and other components combined in a photo etched circuit, only 1/2 x 1/2 in.; tuning capacitor, ferrite rod aerial, battery, wave band selection switch, etc. Output to a high impedance crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec.: Waveband coverage—Medium wave 525 to 160 kc/s, Long wave 150 kc/s to 408 kc/s. Sensitivity: 35mV max. Selectivity—10dB (at 30 kc/s de-tuning). Power source: 1 x 1.4V Mercury battery.

The Orion is supplied fully built and tested complete with battery, left and right fitting earphone supports and attractive black and ivory plastic carrying case—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others.

LASKY'S PRICE ONLY 39/6 Post 2/6 Extra rechargeable battery 3/6


\*NOTE: The battery we supply with the Orion is a rechargeable type. Charger units are available enabling you to recharge the battery from AC Mains 220/240V supply.

PRICE 19/6 extra Post Free with radio—otherwise 2/-.
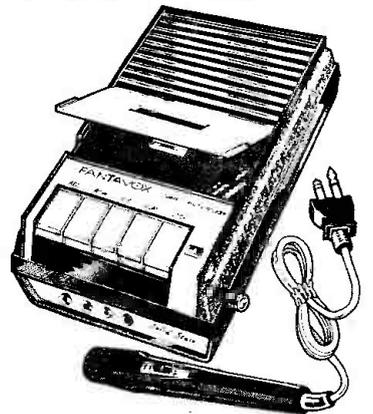
## FANTAVOX TPC-2

SOLID STATE COMPACT CASSETTE RECORDER

A new Lasky's STAR BARGAIN this beautifully made compact cassette recorder and play back machine offers tremendous performance and value. BRIEF SPEC: 6 transistor and 1 thermistor circuit. Constant speed capstan drive system. AC bias recording. FM magnet erase. 2 1/2 in. FM Dynamic speaker. Economical operation on 4 x 1.5V (U2 type) batteries. SPECIAL FEATURES: Absolutely fool proof operation. Piano key controls. Powerful volume with recessed control. Handsome impact resistant cabinet finished in black with satin aluminium and Ivory trim. Size 9 1/2 x 5 1/2 x 2 1/2 in. Jack sockets for remote control microphone, earpiece and external 6V battery pack (or AC adaptor). COMPLETE WITH Remote control Dynamic microphone, earpiece, removable carrying strap, batteries, full instructions and three C-60SX cassettes.



LASKY'S PRICE £16.10 POST 5/- Leather carrying case 30/- extra

### NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE at RECORD LOW PRICES

3in. Message tape, 150ft. ....	2 6	5 1/2in. Standard play, 850ft. PVC ..	11 6
3in. Message tape, 225ft. ....	3 9	5 1/2in. Long play, 1200ft. Mylar ..	15 0
3in. Message tape, 300ft. ....	7 6	5 1/2in. Triple play, 2400ft. Mylar ..	45 0
3 1/2in. Triple play, 900ft. Mylar ..	10 0	7in. Standard play, 1200ft. Acetate ..	12 6
4in. Triple play, 900ft. Mylar ..	17 6	7in. Standard play, 1200ft. Mylar ..	12 6
5in. Double play, 1200ft. Mylar ..	15 0	7in. Long play, 1800ft. Mylar ..	19 6
5in. Long play, 900ft. Acetate ..	10 0	7in. Double play, 2400ft. Mylar ..	25 0
5in. Standard play, 800ft. PVC ..	8 6	7in. Long play, 1800ft. Acetate ..	15 0
5in. Triple play, 1800ft. Mylar ..	25 0	7in. Triple play, 3600ft. Mylar ..	50 0
5 1/2in. Double play, 1800ft. Mylar ..	22 6		
5 1/2in. Long play, 1200ft. Acetate ..	12 6		

P. & P. 1/- extra per reel. 4 reels and over Post Free. Special quotes for quantities.

PRICED CASSETTES from U.S.A.

C.60-7/6 (6 for 42/6), C.90-12/6 (6 for 70/-), C.120-17/6.

Post 1/- each. 4 and over Post Free. Special quotes for quantities.

## Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel. 01 723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel. 01 631 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel. 01 353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel. 01 580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday


118 EDGWARE ROAD, LONDON, W.2 Tel. 01 723 9789

Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1

Tel.: 01-790 4821



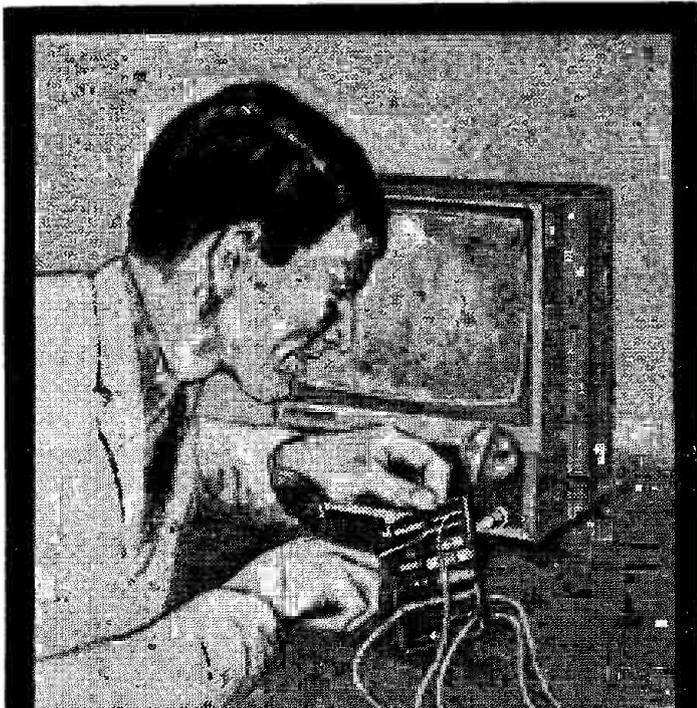

## Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full time 16 month College Diploma Course which gives a thorough fundamental training for radio and television engineers, starts on 1st January 1970.

The Course includes theoretical and practical instruction on Colour Television receivers and is recognised by the Radio Trades Examination Board for the Radio and Television Servicing Certificate examinations. College Diplomas are awarded to successful students.

The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now with the world famous Pembridge College. Minimum entrance requirements: 'O' Level, Senior Cambridge or equivalent in Mathematics and English.

To: The Pembridge College of Electronics  
(Dept. PW11), 34a Hereford Road, London, W.2

Please send, without obligation, details of the Full-time Course in Radio and Television.

NAME .....

ADDRESS .....



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 90 ft. 18 gauge on plastic reel. Recommended retail price 15/-



### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 202 ft. 22 gauge on plastic reel. Recommended retail price 15/-



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF.	ALLOY	SWG		
4A	60/40	18	2/6*	
Size 5 (ill-ustrated)	Savbit	18	2/6*	
15	60/40	22	3/-*	

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



From Electrical and Hardware shops. If unobtainable, write to:  
Multicore Solders Ltd., Hemel Hempstead, Herts.

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

### SETS

1R5, 1R5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 13/6. DAF96, DF96, DK96, DL96, 4 for 28/6.

OZ4	4/6	12K8GT	7/3	DK91	5/9	EH90	6/3	PCL83	9/-	UBF80	5/9
1A7GT	7/6	12SN7GT	6/6	DK92	8/3	EL33	8/9	PCL84	7/6	UBF89	6/9
1B5GT	7/3	19B6G	17/6	DK96	7/-	EL34	9/6	PCL85	9/-	UC92	5/-
1N5GT	7/9	20F2	13/6	DL35	5/-	EL41	10/6	PCL86	8/3	UCC84	7/-
1R5	5/9	20P3	11/9	DL92	5/9	EL84	4/9	PENA4	12/6	UCC85	6/9
1R5	4/3	20P4	18/6	DL94	6/-	EL90	4/6	PFL200119		UCF80	7/3
1T4	2/9	25L6GT	5/-	DL96	7/-	EL500	12/6	PL86	9/9	UCH42	11/6
3B4	5/9	25U4GT	11/6	DY86	5/9	EM80	7/6	PL81	7/3	UCH81	6/3
3V4	4/-	30C1	6/6	DY87	5/9	EM81	7/6	PL82	6/6	UCL82	6/6
5U4G	4/6	30C15	13/-	EABC80	6/6	EM84	6/6	PL83	6/6	UCL83	11/6
5Y3GT	5/9	30C17	16/-	EAF42	10/-	EM87	7/6	PL84	6/6	UF41	10/6
5Z4G	7/6	30C18	11/6	EB91	2/3	EY51	7/6	PL600	13/-	UF80	7/-
6/30L2	12/-	30F5	18/-	EBC33	8/6	EY86	6/6	PL504	13/6	UF85	6/9
6AL5	2/3	30FL1	13/9	EBC41	9/6	EZ40	8/-	PL508	23/6	UF89	6/9
6AM6	2/9	30FL12	14/6	EBF80	6/9	EZ41	8/-	PL802	14/6	UL41	10/9
6AQ5	4/6	30FL14	12/-	EBF89	6/3	EZ80	4/6	PM84	7/6	UL44	20/-
6AT6	4/-	30LI	6/6	ECC81	3/9	EZ81	4/9	PX25	10/6	UL84	7/-
6AU6	4/6	30L15	14/-	ECC82	4/9	GZ32	8/9	PY32	10/6	UM84	6/6
6BA6	4/6	30L17	15/6	ECC83	7/-	GZ34	9/9	PY33	10/6	UY41	7/6
6BE6	4/9	30P4	12/-	ECC85	7/-	KT61	8/9	PY81	5/3	UY85	5/9
6BJ6	8/6	30P12	13/9	ECC91	3/-	KT66	16/-	PY82	5/3	VP4B	10/-
6BW6	13/-	30P19	12/-	RCC804	12/-	N78	17/6	PY83	5/9	W119	7/-
6F13	3/6	30PL1	13/9	ECF80	6/6	PABC80	7/-	PY88	6/9	Z77	2/9
6F14	9/-	30PL13	15/6	ECF82	5/9	PC86	10/3	PY800	7/6	Transistors	
6F23	14/3	30PL14	15/6	ECH85	6/-	PC86	10/3	PY801	6/9	AC107	3/6
6F25	13/-	35L6GT	8/6	ECH42	12/6	PC86	8/6	R19	6/6	AC127	2/6
6J6	3/-	35W4	4/6	ECH81	5/3	PC97	8/6	R20	12/6	AD140	7/6
6K7G	2/6	35Z4GT	5/-	ECH84	7/6	PC900	7/6	U25	13/-	AF115	3/6
6K8G	2/9	6063	12/6	ECL80	6/9	PCC84	6/6	U26	12/-	AF116	3/6
6L18	6/-	AC/VP210		ECL82	6/9	PCF85	6/-	U47	13/6	AF117	3/3
6V6G	3/6	AZ31	9/6	ECL83	8/6	PCC88	9/-	U49	13/6	AF125	3/6
6V6GT	6/6	B729	12/6	ECL86	8/6	PCC89	10/6	U52	4/6	AF127	3/6
6X4	4/3	CCH35	13/6	EF37A	4/6	PCC189	11/6	U78	4/3	OC26	5/9
6X5GT	5/9	CL33	18/6	EF39	8/9	PCF80	6/6	U191	12/6	OC44	2/3
7B7	7/-	CY31	6/9	EF41	10/9	PCF82	6/6	U193	8/6	OC45	2/3
7C6	6/9	DAC92	7/3	EF80	4/6	PCF86	11/6	U251	14/6	OC71	2/6
10F1	14/-	DAF91	4/3	EF85	5/3	PCF20013/6		U301	10/6	OC72	2/6
10F18	7/-	DAF96	6/6	EF86	6/3	PCF80013/6		U329	14/6	OC75	2/6
10P13	15/6	DF33	7/9	EF89	5/3	PCF801	6/9	U801	19/6	OC81	2/3
12AT7	3/9	DF91	2/9	EF91	2/9	PCF802	9/-	UABC80	6/6	OC81D	2/3
12AU6	4/9	DF96	6/6	EF94	4/6	PCF805	11/6	UAF42	10/3	OC82	2/3
12AU7	4/9	DH77	4/-	EF183	5/9	PCF808	12/-	UB41	6/6	OC82D	2/6
12AX7	4/9	DK32	7/6	EF184	5/6	PCL82	7/-	UBC41	9/-	OC170	2/6

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD,  
ESSEX. Tel. 01-550 7441

Postage on 1 valve 3d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

## NEW! roamer eight mk1 WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

**£6.19.6**

Parts Price List and Easy Build Plans 5/- (FREE with parts).

P & P 7/6.

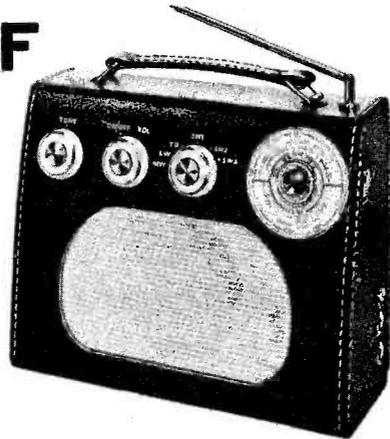


## roamer seven mk1V

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy B.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

Total building costs

**£5.19.6**

P & P. 7/6

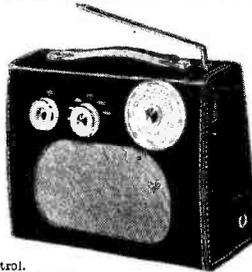

## NEW! trans eight


SIX WAVEBAND  
PORTABLE WITH  
3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5 1/2 x 2 3/4in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

Total building costs

**89/6**


P & P 5/6

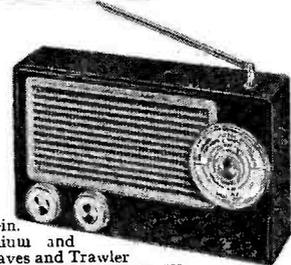
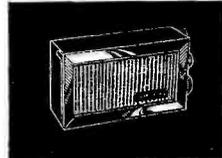
## pocket five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/4in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs


**44/6**

P. & P.  
3/6
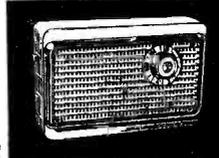
## transona five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**47/6**

P. & P.  
3/9

## roamer six

SIX WAVEBAND PORTABLE  
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7 1/4 x 5 1/4 x 1 1/2in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 8 stages—5 transistors and 2 diodes including Micro-Alloy B.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts).



Total building costs

**79/6**

P. & P.  
4/6

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

PW13

\* Callers side entrance Stylo Shoe Shop

\* Open 10-1, 2.30-4.30 Mon-Fri. 9-12 Sat

# Complete stereo system – 28 gns.

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

**Type 1 SPECIFICATION:-**

Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" speaker and 2½" tweeter. Teak finish 12" x 6½" x 5½". 4 guineas each. 7/6d. p. & p.

**Type 2 as type 1.** Size 17½" x 10½" x 6½". Incorporating 10½" x 6½" bass unit and 2½" tweeter. 3 ohms impedance 5½ guineas plus 7/6 p. & p.

Garrard Changers from £7.19.6d. p. & p. 7/6d.

Cover and Teak finish Plinth £4.15.0d. 7/6d. p. & p.

The items illustrated can be purchased together for 28 gns.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

**SPECIFICATION:-**

R.M.S. power output: 3 watts per channel into 10 ohms speakers.

**INPUT SENSITIVITY:** Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1 Kc/s.

**CONTROLS:** 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

**TONE CONTROL:** Treble lift and cut. Separate on/off switch. A preset balance control.

*Duetto* Integrated Transistor Stereo Amplifier

**9GNS.**  
plus 7/6d.  
p. & p.



The above 5 items can be purchased together for £29.10 + £1.10.0 p. & p.

## The Classic

**£9** plus 7/6 p. & p.

**Controls:** Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.



**Specification:** Sensitivities for 10 watt output at 1KHz into 3 ohms. *Tape head:* 3mV (at 3½ i.p.s.). *Mag. P.U.:* 2mV. *Cer. P.U.:* 80 mV. *Tuner:* 100mV. *Aux.:* 100mV. *Tape/Rec. output:* Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20Hz to 20KHz. *Tone control range:* Bass ±13dB at 60Hz. Treble ±14dB at 15KHz. *Total distortion:* (for 10 watt output) <1.5%. *Signal noise:* <-60dB. A.C. mains 200-250v. Built and tested. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case.

## The Viscount

**£14.5** plus 7/6 p. & p.

**Integrated High Fidelity Transistor Stereo Amplifier.** Specification—Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo), P.U., Tuner, Tape and Tape Rec. out. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency Response: 40Hz-20KHz ±2dB. Tone Controls: Separate bass and treble controls; treble, 13dB lift and cut (at 15KHz); Bass, 15dB lift and 25dB cut (at 60Hz). Volume Controls: Separate for each channel. A.C. Mains Input: 200-240V. 50-60Hz. Size, 12½" x 6" x 2½" in teak finished case. Built and tested.

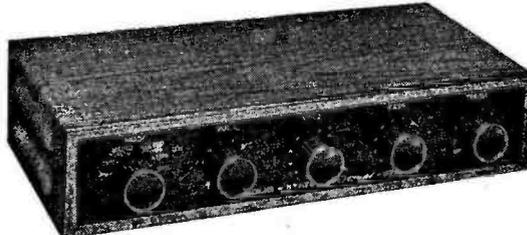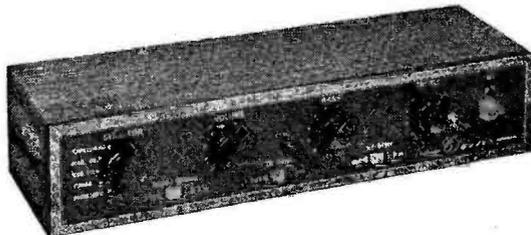**VISCOUNT MARK II** for use with magnetic pick-ups specification as above. Fully equalised for magnetic pick-ups. Suitable for cartridges with minimum output of 4mV/cm/sec. at 1kc. Input impedance 47k. £15.15 plus 7/6 p. & p.




## SPECIAL OFFER!

Complete stereo system comprising BALFOUR 4-speed autoplayer with stereo head, 2 Duo speaker systems, size 12in. x 6½in. x 5½in. Plinth (less cover) and the DUETTO stereo amplifier. All above items

**£20** plus 20/- p. & p.

Also see opposite page

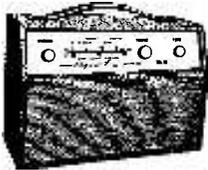

### The ELEGANT SEVEN Mk. III (350mW Output)

7 transistor fully tunable M.W.-L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. MAINS POWER PACK KIT: 9/6 extra.

Circuit 2/6  
FREE WITH PARTS.

Price £4.9.6 plus 7/6 P. & P.

### The DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

Price £5.5.0 plus 7/6 P. & P.

MAINS POWER PACK KIT: 9/6 extra



Circuit 2/6  
FREE WITH PARTS.



### EXTRACTOR FAN


A.C. mains 230/250v. complete with pull switch. Size 6 x 6 x 4in.

Price 27/6 plus 7/6 P. & P.

### X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0.33 microamp). Total Distortion at 1KHz at 5 watts, 0.35%, at rated output 1.5%. Frequency Response: Minus 3dB points 20Hz and 40KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24V. D.C. at 800mA (6-24V. may be used).

Price 69/6 plus 2/6 P. & P.

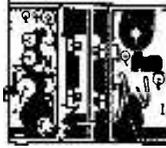

Control assembly: including resistors and capacitors. 1. Volume: PRICE 5/- . 2. Treble: PRICE 5/- . 3. Comprehensive bass and treble: PRICE 10/- . The above 3 items can be purchased for use with the X101.

Power Supplies for the X101:  
P101 M (for mono) 35/- plus 4/6 p. & p.  
P101 S (for stereo) 42/6 plus 4/6 p. & p.


### CAR TRANSISTOR IGNITION SYSTEM

by famous manufacturer

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers etc.).

Price £4.19.6 plus 5/- P. & P.
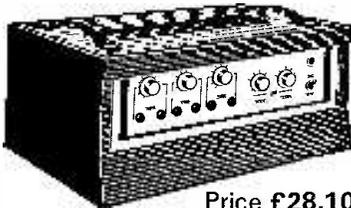
### 50 WATT AMPLIFIER A.C. Mains 200-250V



Price £28.10 plus 20/- p. & p.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

TECHNICAL SPECIFICATIONS  
3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. SENSITIVITIES AND INPUT IMPEDANCES. Channels 1 & 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars.

Channels 3 & 4 300mV at 1m. Suitable for most high output instruments (gram, tuner, organ etc.). Input sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +12dB at 60 Hz. Bass Cut -13dB at 60 Hz. Treble Boost +11dB at 15 KHz. Treble Cut -12dB at 15 KHz. With bass and treble controls central -3dB points are 30 Hz and 20 KHz. POWER OUTPUT: For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output to match into 8 or 15 ohms speaker system. NEGATIVE FEEDBACK 20dB at 1 KHz. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES adjustable from 200-250V. A.C. 50-60 Hz. A protective fuse is located at the rear of unit. Output impedance 3, 8 and 15 ohms.


### B.S.R. TD-2 TAPE DECK

Takes 5 1/2 in. spools, fitted with B.S.R. 1/2 Track Heads. Size 13 1/2 in. long by 8 1/2 in. wide. Price £8.19.6 plus 7/6 P. & P.

TERMS C.W.O.  
All enquiries S.A.E.
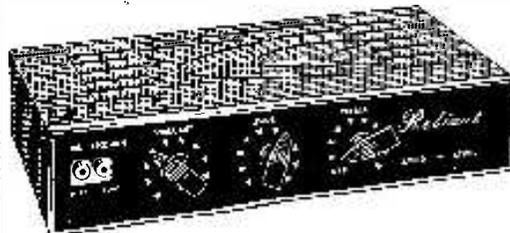
### The RELIANT

SOLID STATE  
GENERAL  
PURPOSE  
AMPLIFIER



#### SPECIFICATIONS

Output—10 watts  
Inputs—1. xtal mic 10mV 2. -gram/radio 250mV  
Tone Controls—Treble control range ±12dB at 10 KHz  
Bass control range ±13dB at 100Hz  
Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz.  
Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10 1/2" x 4 1/2" x 2 1/2". For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram. and mike. Built and tested. 8" x 5" speaker to suit price 14/6 plus 1/6 p. & p. Crystal mike to suit 12/6 plus 1/6 p. & p.

#### RELIANT Mk. I

As above less teak case

£5.15 plus 7/6 P. & P.

#### RELIANT Mk. II

In teak finished case.

£6.16 plus 7/6 P. & P.

### RECORD PLAYER SNIP A.C. Mains 240V

The "Princess", 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and ins. 7/6 extra.

ONLY £5.19.6 plus 7/6 P. & P.



### POCKET MULTI-METER

Size 3 1/2 x 2 1/4 x 1 1/2 in. Meter size 2 1/2 x 1 1/2 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1,000 D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods, battery and full instructions.

42/6 plus 3/6 P. & P.

FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

### STEREO PRE-AMPLIFIER

Inputs—6 position rotary switch (3 position mono, 3 position stereo). Tuner 150mV into 680k. Magnetic pick-up fully equalised and suitable for magnetic cartridges with minimising output of 4mV/cm/sec. Load 47k. Ceramic pickup 150mV into 680k. Sensitivities taken for 200mV output. Controls—separate volume controls for each channel. Twin ganged bass, 12dB lift and 15dB cut at 60c/s. Twin ganged treble, 10dB lift and 15dB cut at 10kc/s. Voltage required 23-30V DC at 5mA. Size 12 1/2 x 3 1/2 x 2 1/2 in. In teak finished case, complete with front panel and knobs. Built and tested.

£7.7.0 plus 5/- P. & P.

### CYLDON 2 TRANSISTOR U.H.F. TUNER

Brand new. Complete with circuit diagram.

Price £2.10.0 plus 1/- P. & P.

### THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss crossover network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 Gauss. Resonance 40 60 c/s. Frequency range 50c/s to 20Kc/s. Size 13 1/2 x 8 1/2 x 4 1/2 in. By famous manufacturer.

List price £7 OUR PRICE 74/6 plus 5/- P. & P.

Similar speaker to the above without tweeters in 3 and 15 ohms 44/6 plus 5/- p. & p.

### PYE CAR RADIO

Push Button Tuning Heart

This PRESTOLOK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6 1/2" x 4" x 2".

25/- plus 3/- P. & P.



### QUALITY MAINS TRANSFORMER

Input 250 volts. OUTPUT (All RMS values) 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used.

1. 23-0-23 volts. 2. 46 volts.

Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- plus 7/6 P. & P.



Goods not despatched outside UK

RADIO & T.V. COMPONENTS (ACTON) LTD  
21c High Street, Acton, London W.3.

Also at 323 Edgware Road, London W.2.


ALL ORDERS BY POST TO OUR ACTON ADDRESS

RADIO & TV COMPONENTS  
**R TV**  
(ACTON) LIMITED

# MAINS Keynector

A REVOLUTIONARY PRODUCT

## cuts out plugs

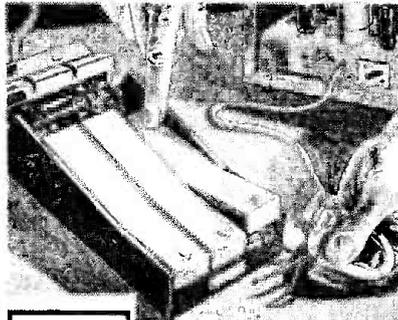

**SAFEST & QUICKEST WAY TO CONNECT ELECTRICAL EQUIPMENT TO THE MAINS**

No plugs—no sockets—no risk of bare wires. To connect anything electrical, from an oscilloscope to an electric drill, simply open the fuse housing, depress the keys, insert the wires and close the housing. A neon light on the front of the Keynector glows to indicate proper connection. Multi-parallel connections can be made up to 13 amps. Keys are colour coded and lettered LEN for quick identification. The Keynector casing is in two-tone plastic and measures 5 x 3 x 1 1/2 in. Price 39/6, plus 5/- p. & p.

### E. B. INSTRUMENTS

DIVISION OF ELECTRONIC BROKERS LTD.  
49-53 PANCRAS ROAD, LONDON, N.W.1.  
Telephone: 01-837 7781

## AUDIO EFFECTS

5 SHAW LANE HALIFAX YORKS.

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

**REVERBERATION AMPLIFIER.** Self-contained transistorised battery operated. An entirely different approach to sound reproduction. Normally sound reproduction from a single source has a flat, one-dimensional effect. With this unit proper sound delay through reverberation, tones are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc. in and the output into your amplifier. Supplied in a beautiful walnut cabinet. 7 1/2 x 3 x 4 1/2 in. £10.4.0. P.P. & Ins. 6/-.



**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete

with box, power socket, cables, etc. In kit form with easy to follow instructions 26.9.6. Ready built 29.4.6 plus 6/6 P.P. & Ins.

**VOX SWITCH.** This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions, 42/6. Ready built, tested and guaranteed, 62/6 plus 2/6 P.P.


**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6 post paid. Ready built in an attractive black and white polythene case 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speakers. In kit form 17/6 post paid. Ready built in similar case as above, 25/- post paid.

**JUST ARRIVED IN STOCK.** Texas transistors. Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid.

Free lists with every order. For lists only send 1/6 (deductable from first order).

## 4-STATION INTERCOM

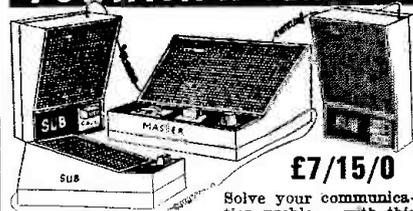

£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 8/6 extra.

## INTERCOM/BABY ALARM



OUR PRICE ONLY 3 gns.

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.


### Transistor TELEPHONE AMPLIFIER



59/6

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (PW1) 169 KENSINGTON HIGH STREET, LONDON, W.8.

# YOURS FREE FOR 7 DAYS

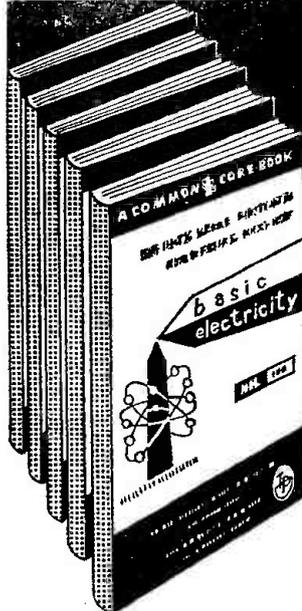

## The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 vols.)** **BASIC ELECTRONICS (6 vols.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

### WHAT READERS SAY

'Everything is clearly set out ...'

... I am very pleased with this pictorial system. Everything is clearly set out in diagrams, . . . L.P., Co. Armagh.

'... very pleased with the set ...'

... I was very pleased with the set of Basic Electronics. Please send Basic Electricity . . . D.W., Margate.

'... how understandable your books are ...'

... Pleased to say how understandable your books are, I now have a sound knowledge of the subject . . . A.A., Hull.

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER!!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.

Signature \_\_\_\_\_ (If under 21 signature required of parent or guardian)

NAME BLOCK LETTERS \_\_\_\_\_

FULL POSTAL ADDRESS \_\_\_\_\_

# ELECTROVALUE

Everything brand new and to specification • Large stocks • Good service

## RESISTORS:

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	100Ω-220KΩ	E12	16	14	13
C	1/8W	5%	4.7Ω-1MΩ	E24	2.5	2	1.75
C	1/4W	10%	4.7Ω-10MΩ	E12	2.5	1.75	1.5
C	1/2W	5%	4.7Ω-10MΩ	E24	3	2.25	2
MO	1/2W	2%	10Ω-1MΩ	E24	9	8	7
C	1W	10%	4.2Ω-10MΩ	E12	4	3.25	3
WW	1W	10% + 1/20Ω	0.22Ω-3.3Ω	E12	15d all quantities		
WW	3W	5%	12Ω-10KΩ	E12	15d all quantities		
WW	7W	5%	12Ω-10KΩ	E12	15d all quantities		

Codes: C = carbon film, high stability, low noise.  
MO = metal oxide, ElectroSil TR5, ultra low noise.  
WW = wire wound, Plessey.

Values: E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades.  
E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2, 2.4, 3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.

Prices are in pence each for each ohmic value and power rating. (Ignore fractions of one penny on total resistor order)

## COLVERS 3 WATT WIRE-WOUND POTENTIOMETERS:

10Ω, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1KΩ, 1.5KΩ, 2.5KΩ, 5KΩ, 10KΩ, 15KΩ, 25KΩ, 50KΩ.  
Price only 5/6 each.

## CARBON TRACK POTENTIOMETERS: Double wiper ensures minimum noise level. Long plastic spindles.

Single gang linear: 220Ω, 470Ω, 1K etc. to 2.2MΩ	each 2/6	Log/Anti-log: 10K, 47K, 1MΩ only	each 3/6
Single gang log: 4K7, 10K, 22K, etc. to 2.2MΩ	2/6	Dual anti-log: 10K only	3/6
Dual gang linear: 4K7, 10K, 22K etc. to 1MΩ	8/6	Any type with 1/2 amp. double pole mains switch:	extra 2/3
Dual gang log: 4K7, 10K, 22K etc. to 2M2Ω	8/6		

FETS n-channel low cost general purpose  
2N5163, 25 volt, only 5/- each. Audio/  
r.f. Texas 2N3819 9/-, Motorola 2N5459  
(MPF105) 9/6 each.

NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER TYPE  
SL403A. Only 57/- each. Operates with 18V power supply. Sensitivity  
20mV into 20MΩ, 3 watts into 7.5Ω. PE Nov. 69 Stereo Amplifier kit  
less metal work. £11/13/- NET complete.

## WATT BAILEY AMPLIFIER COMPONENTS:

Transistors for one channel £7/9/8 list, with 10% discount only £6/14/6  
Transistors for two channels £14/19/- list, with 15% discount only £12/14/-  
Capacitors and resistors for one channel list £2.  
Printed circuit board free with each transistor set.  
Complete unregulated power supply kit £4/14/6 mono or stereo, subject to discount.  
Complete regulated power supply kit £9/5/- subject to discount. Further details on application.

SINGLAIR IC.10 Integrated Circuit Amplifier and Pre-amplifier  
This remarkable monolithic integrated circuit amplifier and pre-amp  
now available from stock. The equivalent of 13 transistor/  
18 resistor circuit plus 3 diodes and the first of its kind ever.  
It is d.c. coupled and applicable to an unusually wide range of  
uses as detailed in the manual provided with it. As advertised,  
post free 59/6 NET.

CARBON SKELETON PRE-SETS. Small, high  
quality, type PR. Linear only, 100Ω, 220Ω, 470Ω,  
1KΩ, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K,  
470K, 1MΩ, 2M2, 5M, 10MΩ vertical or horizontal  
mounting, 1/- each.

S-DeCs put an end to "birdsneating". Components just plug in. Saves valuable time. Use components again and  
again. S-DeC only 30/6 post free. Compact T-DeC, increased capacity, may be temperature-cycled T-DeC only 51/-  
post free.

## CAPACITORS: All new stock

High ripple current types:	Medium elec.	Small elec.
2000µF 25V 7/4; 2000µF 50V 11/4; 5000µF 25V 12/6; 5000µF 50V 21/11; 1000µF 100V 18/3; 2000µF 100V 28/9; 5000µF 70V 36/-; 5000µF 100V 58/3; 1000µF 50V 8/2; 2500µF 64V 15/5; 2500µF 70V 19/6.	Axial leads: Values (µF/V): 50/50 1/9; 100/25 1/9; 100/50 2/8; 250/25 2/6; 250/50 3/9; 500/25 3/8; 1000/10 3/-; 500/50 4/6; 1000/25 4/6; 1000/50 7/-; 2000/25 6/-.	Axial leads: 5/10, 10/10, 25/10, 50/10 1/- each, 25/25, 47/25, 100/10, 220/10 1/8 each.

## PEAK SOUND ENGLEFIELD KITS

Brilliant new styling and  
available in two forms:  
Stereo 15 watts per channel  
In kit form with complete  
amplifier and pre-amplifier  
modules and power supply. Build it 12 + 12 or 25 + 25  
Output per channel into 15Ω, 12 watts R.M.S. Price £38/4/- net

25 WATTS PER CHANNEL As above but Output per channel into  
15Ω 25 watts R.M.S. Price £53/15/- Net  
Brief specification: Total harmonic distortion 0.1%.  
Inputs: Magnetic, Ceramic, Tape, Radio Signal to noise ratios:  
Better than 60dB all inputs. 0/load factor 2dB all channels.

ENGLEFIELD CABINET to house either above assemblies (as  
illustrated) £6 Net OTHER PEAK SOUND PRODUCTS AS  
ADVERTISED.

MULLARD Sub-min electrolytic C426 range-  
Price 1/3 each. Axial leads, Values (µF/V):  
0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10;  
4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5;  
10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64;  
25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16;  
40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10;  
80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10;  
125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/  
2.5; 320/6.4; 400/4; 500/2.5.

Wavechange switches: 1P 12W; 2P 6W; 3P 4W;  
4P 3W long spindles, 4/9 each.

Slider switches, double pole double throw,  
3/- each.

## BARGAINS IN NEW TRANSISTORS

All power types supplied with  
free insulating sets

2N696	5/6	2N5192	25/-
2N697	6/-	2N5195	29/3
2N706	3/-	40406	16/3
2N1132	14/3	40408	14/6
2N1302	4/-	AC126	6/6
2N1303	4/-	AC127	6/-
2N1304	4/6	AC128	6/-
2N1305	4/6	AC176	11/-
2N1306	6/9	ACY22	3/9
2N1307	6/9	ACY40	4/-
2N1308	8/9	AD140	19/-
2N1309	8/9	AD149	17/6
2N1613	6/6	AD161	} 16/- pr.
2N1711	7/4	AD162	
2N2218	10/6	AF118	16/6
2N2147	18/9	AF124	7/6
2N2369A	6/9	AF127	7/-
2N2646	10/9	BA102	9/-
2N2924	4/3	BC107	3/6
2N2925	5/3	BC108	3/-
2N2926R	2/6	BC109	3/6
2N2926O	2/6	BC147	4/3
2N2926Y	2/3	BC148	3/3
2N2926G	2/6	BC149	4/3
2N3053	5/6	BC153	10/-
2N3054	14/3	BC154	11/-
2N3055	16/6	BC157	3/9
2N3391A	5/6	BC158	3/6
2N3702	3/6	BC159	3/9
2N3703	3/3	BC167	2/6
2N3704	3/9	BC168	2/3
2N3705	3/5	BC169	2/6
2N3706	3/3	BC177	6/3
2N3703	4/-	BC178	5/6
2N3708	2/9	BC179	6/-
2N3709	3/-	BD121	18/-
2N3710	3/3	BD123	24/3
2N3711	3/11	BF178	10/6
2N3904	7/6	BFX29	10/9
2N3906	7/6	BFX85	8/3
2N3731	23/-	BFX88	7/9
2N3820	25/6	BFY50	4/6
2N3925	10/6	BFY51	4/3
2N3794	3/3	BSX20	3/9
2N4286	3/3	MJ480	21/-
2N4289	3/3	MJ481	27/-
2N4291	3/3	MJ491	30/-
2N4292	3/3	P346A	5/9
2N4410	4/9	V405A	7/9

MAIN LINE AMPLIFIER KITS as advertised. Prices Net.  
Authorised dealer.

## COMPONENT DISCOUNTS:

10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on net items).

## POSTAGE AND PACKING:

Free on orders over £1.  
Please add 1/- if order is under £1.  
Overseas orders welcome: carriage charged at cost.

# ELECTROVALUE

(Dept. PW.1) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM,  
SURREY.

Telephone: Egham 5533 (STD 0784-3)  
Open 9-5.30 Sats. 1 p.m.

# R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

## 30 WATT OUTPUT

★ Goldring Transcription Turntable on Plinth  
★ Shure or Goldring Magnetic Pick-up Cartridge  
★ Super 30 Amplifier in veneered housing  
★ Pair of Stanway II Loudspeaker Units  
Special total price. Four fully wired units ready to "plug-in". Carr. 30/-  
**86 Gns.**  
**TERMS AVAILABLE ALL PACKAGE OFFERS**

Matching as recommended for optimum performance. Send for coloured brochure showing other money saving offers.

## 30 WATT OUTPUT

★ Garrard SP25 Mk II Turntable on Plinth  
★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus  
★ Super 30 amplifier in veneered housing  
★ Pair Stanway II Speaker Units  
Four fully wired units ready to "plug-in" Special total price **76 Gns.** Carr. 30/-

## 13 WATT OUTPUT

★ Garrard SP25 Mk II 4 sp. player unit on plinth  
★ Goldring CS90 Ceramic P.U. Cartridge  
★ TA12 Amplifier in veneered housing  
★ Pair of Dorchester Loudspeaker Units. Special total price. **51 Gns.**  
Or Dep. £10 and 9 mthly payments **£5.11.0** (Total **£59.19.0**). Transparent plastic cover 3 gns. extra

## AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround for low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost. Prices include carriage.

HF510L 5" 10W	57/9	HF120 12" 15W	79/9
HF801D 8" 8W	59/9	HF120D 12" 15W	89/9
HF111D 8" 10W 4 gns.		HF126 12" 15W	£5.0
HF121D 10" 10W	65/-	HF126D 12" 15W	£5.15.0

**HIGH FIDELITY LOUDSPEAKER UNITS**  
Cabinets latest style Satin Teak or Afrormosia veneer. A acoustically lined or filled woollen damping. Ported where appropriate, credit terms available

**DORCHESTER** Size 16 x 11 x 9in. Appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. Dual Cone spkr. Imp. 3 or 15 ohms **£8.19.9**


**STANWAY II** Size 20x10x9in. Rating 10 watts. Incorporating Pane 13x8in. speaker with rubber cone surround and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

**GLOUCESTER** Size 25 x 16 x 10in. 12in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Frequency range 40-20,000 c.p.s. Impedance 15 ohms. **12 1/2 Gns.**

**E2 CABINET** Size 17" wide 14" deep, 11 1/2" high. Cut for TA12, Super 15, Super 30 and other amplifiers. "Roll over" transp. plastic cover. Satin Teak or Afrormosia veneer finish **8 Gns.**

**MOTOR BOARDS** cut for Garrard Turntables and many other units. Price **12/9**
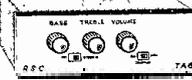
## R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER



200-250v. A.C. mains operated Frequency Response 30-20,000 c.p.s. -3dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble "lift" and "cut" controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output rating 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Carr. 7/6  
Or factory built with 12 months' guarantee. **£8.19.9**



Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

## RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

**RP2C** Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. **22 Gns.**

**RP3C** Goldring Lenco GL68 Transcription unit and CS90 cartridge. **28 Gns.**

Other types available with Magnetic cartridges and with alternative design plinths.

**R.S.C. PLINTHS** for Record Playing units. cut for Garrard 1025, 2025, 3000, AT90, SP25 etc. **59/9**


Available with trans. plastic cover. Inc. Carr **6 Gns.**

**INTEREST CHARGES REFUNDED** On Credit Sales settled in 3 months.
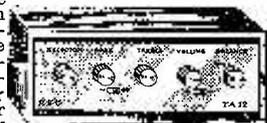
## R.S.C. TA12 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, "Mike" etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV. Output rating I.H.F.M. ★ Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 mthly pmtts **12 1/2 Gns.** Or in Teak or Afrormosia veneer housing **19 1/2 Gns.** Dep. **£5.10.6** and 9 mthly pmtts **39/-**. (Total **£23.1.6**)



## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.15.0**  
Or Senior 15 watt inc. HF 126 15,000 line Speaker **£6.15.0** Carr. 6/6 Carr. 5/9

**LINEAR L10 HIGH FIDELITY 10W AMPLIFIER** with separate Pre-amp. Magnet P.U. matching. To clear **10 Gns.**

**HI-FI SPEAKER ENCLOSURES** Teak or Afrormosia veneer finish. Modern design. Acoustically lined. Prices Inc. carr.

**JES** Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£4.10.0**

**SE8** For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. **£5.10.0**

**SE10** For outstanding results SE12 For excellent performance with 12in. Hi-Fi speaker and Tweeter. **£6.15.0**

## R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER



Total cost of parts with detailed wiring diagrams & instructions. **14 Gns.**

Or factory built **16 Gns.** Or in Teak finished cabinet as illustrated **19 gns.** Terms: Deposit **£5** and 9 monthly payments **£2**. Total **£23**.

★ High-sensitivity ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Rejection. ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Simple alignment instructions. ★ Output available for feeding tuning meter. ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed and of the same high standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry. Only high grade transistors and components used. A quality product at considerably less than the cost of comparable units. Stereo version. all parts **20 gns.** Inc. carr. Assembled **23 1/2 gns.** inc. carr.

## R.S.C. SUPER 30 MK II HIGH FIDELITY STEREO AMPLIFIER

High Grade Components. Specifications comparable with units costing considerably more.

**TRANSISTORS** 9 high quality types in each channel.

**OUTPUT** 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.

**INPUT SENSITIVITIES** Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.

**FREQUENCY RESPONSE** ±2 dB. 10-20,000 c.p.s.

**TREBLE CONTROL** +17 dB to -14 dB at 10 Kc/s.

**BASS CONTROL** +17 dB to -15 dB at 50 c/s.

**HUM LEVEL** -80 dB.



Employing Twin Printed Circuits. 200/250v. A.C. mains operation. **HARMONIC DISTORTION** 0.1% at 10 watts 1,000 c.p.s. **CROSS TALK** 52 dB at 1,000 c.p.s. **CONTROLS** 5 Position Input Selector, Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. **INPUT SOCKETS** (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).

**CHASSIS** Strong Steel construction Approx. 12 x 3 x 8in.

**FACIA PLATE** Attractive design in rigid Perspex. Spun silver matching control knobs as available.

**COMPLETE KIT OF PARTS** Carr. 15/-

Point to point wiring diagrams and detailed instructions.

Eminently suitable for use with any make of Pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first-rate ancillary equipment. Unit factory built **28 Gns.**

or Deposit **£7.5.0** and 9 monthly payments **£6/3** (Total **£32.11.3**) or in Teak or Afrormosia veneer housing **31 Gns.** Carr. 15/- Terms: Deposit **£7.3.6** and 9 monthly payments of **64/-** (Total **£35.19.6**). Send S.A.E. for leaflet.

## R.S.C. SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams.

Carr. **12 1/2 Gns.**

or factory built **15 1/2 Gns.** Carr. 12/6. Terms: Deposit **4 Gns.** and 9 monthly payments **31/1** (Total **£18.3.9**) or in Teak or Afrormosia veneered housing. **19 Gns.**



- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) D. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade 021-236-1279 (Half-day Wed.)
- DERBY** 25 Osmaston Rd. The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street. (Half-day Thursday) Tel. 20505

- 32 High Street. (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed) Tel 28252 **LEEDS**
- 73 Dale St. (Half-day Wed.) Tel. CENTral 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
- 60A Oldham Street (Half-day Wed.) Tel. CENTral 2778 **MANCHESTER**
- 106 Newport Rd (Half-day Wed) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp. Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half day Thursday) Tel. 20716 **SHEFFIELD**

Mail Orders must not be sent to shops

## THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit **20 Gns.**  
 ★ Response 30-20,000 c.d.s. Impedance 15 ohms. Carr. 12/6  
 ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-watt quarter section series cross-over system. (3) 3 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Woolen acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.6 and 9 monthly payments 39/- (Total £23.1.0).  
**DEMONSTRATIONS AT ALL BRANCHES**



## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp./Tone Control Stages. Performance figures of factory built units: Hum level -70dB. Frequency response +3dB 30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 mV. Suitable for high impedance microphones, Crystal or Ceramic P.U's. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **15 Gns.** Carr. 12/6

Twin-handled perforated cover 27/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 13 gns. TERMS: Deposit £6.3.0 and 9 monthly payments of 34/- (Total £21.9.0). Send S.A.E. for leaflet.

## R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of "mike" and gram, etc. etc. High sensitivity. 5 valves—ECC83 (2), EL84 (2), EZ81. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response +3dB 30-20,000 c/s. Hum level -60dB. SENSITIVITY 40 millivolts. For Crystal or Ceramic P.U's. High Impedance "mikes". For Musical Instruments such as String Bass, Electronic Guitars etc. Size approx. 12 x 9 x 7in. For AC mains 200-250v. 50 cps **9 1/2 Gns.** Output for 3 and 15 ohm spkrs. SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr 11/6 (or factory built 12 1/2 gns.) Twin handled metal cover 27/6. TERMS ON ASSEMBLED UNITS. Deposit 99/6 and 9 monthly payments of 23/- (Total £15.6.6)

RSC A11 TRANSISTORIZED VERSION of above complete kit **9 Gns** (Assembled 13 Gns)

## R.S.C. BASS-REGENT 50 WATT AMPLIFIER

An exceptionally powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak O/P rating. ★ Two extra heavy duty 12in. Loudspeakers. ★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. **55 Gns.** Carr. 30/- or dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60 gns.). Send S.A.E. for leaflet. **1100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Spkrs). 99 gns**

★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. **55 Gns.** Carr. 30/- or dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60 gns.). Send S.A.E. for leaflet. **1100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Spkrs). 99 gns**

★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. **55 Gns.** Carr. 30/- or dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60 gns.). Send S.A.E. for leaflet. **1100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Spkrs). 99 gns**

★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. **55 Gns.** Carr. 30/- or dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60 gns.). Send S.A.E. for leaflet. **1100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Spkrs). 99 gns**

## R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5x4x2in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram **52/6 or assembled 3 Gns.**

SELENIUM RECTIFIERS F.W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 4/3. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.

SELENIUM RECTIFIERS F.W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 4/3. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.

## 6/12V CAR BATTERY CHARGERS

Complete kit of parts with Ammeter and Circuit. Both models with variable charge rate selector. **4 amp 49/9 6 amp 69/9** All types 200-250v. A.C. Mains. Built 10/- extra.

**14 WATT HI-FI AMPLIFIERS** High sensitivity. Two separate inputs. Two vol. controls for mixing purposes. Separate Bass and Treble Controls. Valves ECC83, ECL86, ECL86, EZ30. Output for 15 ohm Loudspeaker. 200-250v 50 c.p.s. A.C. mains operation. Size approx. 8 x 8 x 6in. Factory built and fully guaranteed. Limited number to clear at **£7-19-11** Carr. 10/-

## FANE POP 30c LOUDSPEAKERS

12in. 8-15Ω 25 watts R.M.S. continuous. Dual cone. Carr. free **£5.19.9**



## R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair, ideal for vocalists and Public Address, 15 ohm matching. **C57 15 watts inc. five 7 x 4in. speakers £7.19.11.** TYPE C48S 30 WATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 67/- and 9 mthly pmts 34/9 (Total £18.19.9) Carr. 10/-  
**TYPE C412S, 50 WATTS.** Fitted four 12in 11,000 line 15 watt 26 Gns. speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/-  
 Or Deposit £5.17.6 and 9 monthly payments of 54/6 (Total £30.7.0).

## 30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group A 2 or 4 input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold perspex fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 5 gns. and 9 mthly payments of 39/8 (Total 22 gns). **19 Gns.** Carr. 12/6




## F.A.L. 'Phase Fifty' PUBLIC ADDRESS AMPLIFIER

Solid State Circuitry. 50 Watts Peak Output. 3 separately controlled inputs for mixing purposes. Separate Bass and Treble Controls. Output for loudspeakers 3-30 ohms. Suitable for Dynamic, Ribbon or Crystal Mikes. For Clubs, Theatres, Restaurants, Hotels, Schools, etc. For Vocal or Instrumental Groups. Send S.A.E. for leaflet. **only 29 Gns.** Carr. free
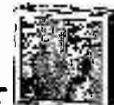
## HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered Cabinets  
 L13 13" x 8" 10 Watt L12 12" 20 Watt 10,000 lines **£4.19.9** 15 ohms. Carr 8/9  
 3or 15 ohms. Carr 7/6



## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High Flux 14,000 line ceramic magnets. Heavy cast chassis.

<b>'POP' 100</b> 18" 100 Watt <b>21 GNS.</b> Carr. free	<b>'POP' 60</b> 15" 60 Watt <b>12 GNS.</b> Carr. free	<b>'POP' 50</b> 12" 50 Watt <b>10 GNS.</b> Carr. free
---	---	---

**POWER PACK KIT** Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250v. A.C. mains. Output 250v. 60mA 6-3v. 2a. Supplied with case in lieu of chassis **28/11.** Or assembled 42/-.

**MINI-8 HI-FI Loudspeaker Units Special Offer**  
 Teak or Afrormosia veneered cabinet, size approx. 10 1/2 x 6 1/2 x 7 1/2 in. Peak power handling 8 watts 3-5 ohms. **69/11** Inc. Carr.

RADIO COMMUNICATION HANDBOOK

over **16,000** copies sold

Now in its second printing

**Radio Communication Handbook**  
 832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. The standard work in its field. **69s post paid**

**THE VHF-UHF MANUAL**  
 By George Jessop, G6JP  
 A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA. **23s post paid**

**THE RSGB AMATEUR RADIO CALL BOOK**  
 1970 edition containing 120 pages  
 Complete up to date listing of all amateur stations in the U.K. and Eire together with much operating information including beam headings and list of prefixes. **7s 3d post paid**

Obtainable from:  
**RADIO SOCIETY of GREAT BRITAIN**  
 35 DOUGHTY STREET, LONDON, WC1

# TECHNICAL TRAINING

*in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

**Examination Students coached until successful**

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Dept. 171, Intertext House, Stewarts Road, London, S.W.8

Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam.) .....

NAME .....

ADDRESS .....

1/70

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

SEND NOW for your

# FREE

**CALENDAR  
DIARY SECTION  
DECIMAL COIN TABLE  
DATA SHEETS**

These are all included in our  
**1970 ENLARGED CATALOGUE**

*RESERVE your copy now for  
despatch early in January*


Write to

**W.E.C. LTD. (W)**

74 THE STREET, ASHTEAD, SURREY

*A new catalogue will be sent to readers in possession  
of our 1969 catalogue.*

## Listen to the world with Eddystone

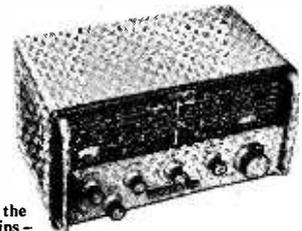

When you own an Eddystone communications receiver, you have the broadcasting world at your finger tips—wherever you happen to be—on land or at sea. The reputation these sets have attained is proof of their excellence and reliability and at Imhofs, there is a special Eddystone department, where you can see, hear and compare all models listed here. Same day despatch to any part of the world; free delivery in the U.K.; plus after sales service for which Imhofs and Eddystone are world famous.

**EDDYSTONE EB35** Mark II broadcast receiver AM/FM transistorised. A high performance all-band receiver, can also be used as a 'Hi-Fi' tuner. Powered by 6 SP2 torch cells, or, with Type 924 power supply unit, from AC mains. £82.4.9d.

**EDDYSTONE 940** (13 valve) communications receiver. A connoisseur's instrument combining 'Professional' appearance with performance: has a world-wide reputation, two RF stages ensure high-sensitivity. £153.0.0d.

**EDDYSTONE EC10** transistorised communications receiver. An enthusiast's receiver at a modest price. Embodies features usually only found in much more expensive designs. Powered by 6 SP2 torch cells or Type 924 power unit (AC). £59.10.0d.

**EDDYSTONE EC10** Mark II transistorised communications receiver. A de-luxe version of this famous design now incorporating 'S' meter and limited fine tuner. £69.10.0d.

**EDDYSTONE EA12** 'Ham Band' receiver. Built to professional standards but specifically for the amateur enthusiast. High sensitivity for all reception modes CW, MCW, AM and SSB. FSK adaptor available as ancillary £195.0.0d.

**EDDYSTONE EY11** a variant of the EC10 tailored to the requirements of the small off-shore boat owner. Available shortly.

*There is an Eddystone Communications receiver for any frequency between 10kHz and 1000 MHz, full details from Imhofs or your local Eddystone agent.*


**IMHOFS** MAIN EDDYSTONE DISTRIBUTORS

Dept: PW1  
112-116 New Oxford Street, London, WC1 Tel: 01-636 7878




R35B

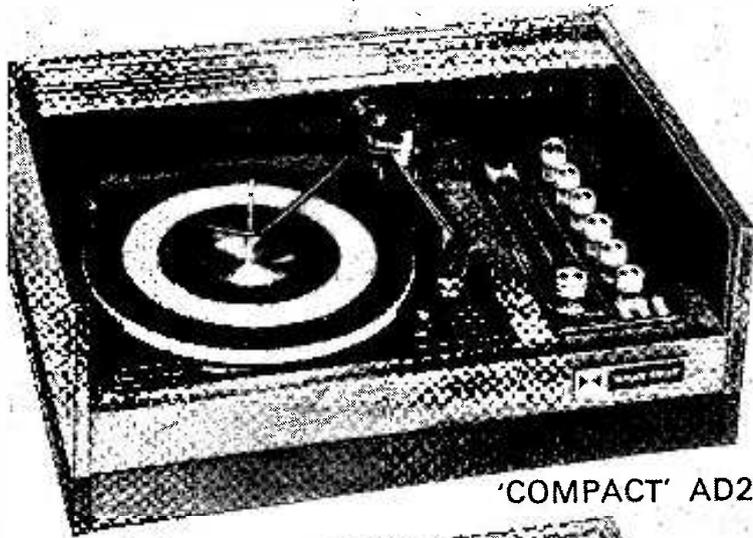
# Heathkit for the new "Compact" Sound of the 70's



'COMPACT' AD27

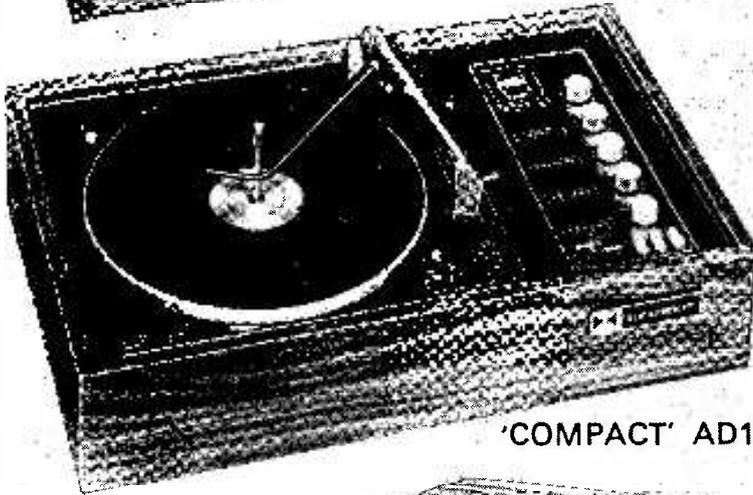

'COMPACT' AD17

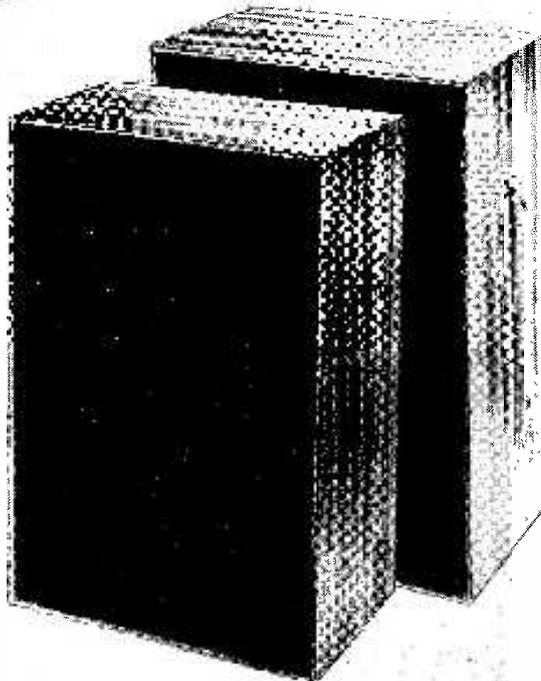

AMBASSADOR SPEAKERS



DAYSTROM LTD  
GLOUCESTER  
GL2-6EE

The fabulous stereo "Compacts" Models AD-17 and AD-27 are setting the pace in hi-fi for the 1970's. They offer outstanding value and performance. The AD-17 comprises a BSR MA-65 turntable/Shure M44-MB magnetic cartridge and a 10 watt (RMS) per channel stereo amplifier all mounted on a Teak or Walnut plinth.  
**Total Kit Price £54. Carr. 13/-**

The AD-27 is similar but uses the MA-70 turntable and includes an FM stereo tuner. In this case the "plinth" is better described as a small cabinet. It has the additional features of a "Roller Shutter" lid and is available in Teak or Walnut.  
**Total Kit Price £82. Carr 13/-**

Heathkit offer many excellent loudspeaker systems the new "Ambassador" HF loudspeaker is winning many friends. Its cabinet is supplied ready assembled and finished in selected Teak or Walnut veneers to harmonise with other current Heathkit hi-fi equipment. It uses three loudspeaker units a 12in. bass, 5in. mid range and a 1in. Dome Pressure Tweeter.  
**Excellent value at £29.16.0 Carr 15/-**

The complete Heathkit hi-fi range of stereo amplifiers, tuner/amplifiers, FM tuners, Stereo "Compacts", loudspeaker systems and ancilliary hi-fi equipment are all described and illustrated, many in full colour. In a wonderful free catalogue.

**Send for the  
FREE Catalogue  
and see for  
yourself . . .  
Today !**

TO DAYSTROM LTD., GLOUCESTER, GL2-6EE


Please rush me details of the latest Heathkit Hi-Fi Models

NAME . . . . .

ADDRESS . . . . .

PW-1B


**CAR LIGHT FLASHERS**

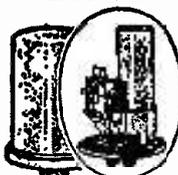

Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset). Housed in strong plastic case. Flashing rate between 60-120 per minute. 12V DC operation. Maximum load 6 amps. Size 2-11/16in. dia. x 4in. Supplied brand new at a fraction of original cost. 6/8 each P. P. 2/6. (3 for 17/6 P. P. 4/8).

**HAMMARLUND SP600JX COMMUNICATION RECEIVER**  
540 Kc/s-54 Mc/s in 6 bands. Few only. \$100 each.

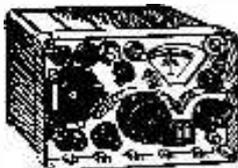**R209 MK II COMMUNICATION RECEIVER**  
11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 12V D.C. internal power supply. Supplied in excellent condition, fully tested and checked \$15.0.0. Carr. 20/-



**TYPE 13A DOUBLE BEAM OSCILLOSCOPES**



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5 Mc/s. Sensitivity 39mV/CM. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. \$22.10.0. Or complete with all accessories, probe, leads, lid, etc. \$25. Carriage 30/-.




**MARCONI T/44/TF956 AF Absorption Wattmeter**  
1 μwatt to 6 watts. \$20. Carr. 10/-.

**SOLARTRON CD-1016 OSCILLOSCOPE**

Double beam. D.C. To 5 Mc/s. Excellent condition. \$55 each. Carr. 20/-.

**GEARED MAINS MOTORS**

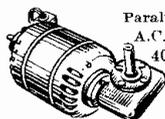

Paralux type SD19 230/250V. A.C. Reversible. 30 r.p.m. 40 lb./ins. Complete with capacitor. Excellent condition. 99/6. Carr. 10/-.

**SOLARTRON CD.711S.2 OSCILLOSCOPES**


Double beam. D.C. to 9Mc/s. Perfect order. \$85. Carr. 50/-.

**TO-3 PORTABLE OSCILLOSCOPE**



3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity 0.9v p-p/CM. Bandwidth 1.5 cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £35.0.0. Carr. 10/-.

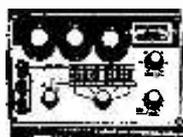**TRANSISTORISED L.R. A.C. MEASURING BRIDGE**




A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 meg Ω 6 Ranges ±1%. L1 L H - 111 HENRYS 6 Ranges -2%. C. 10pF ±1110mFd. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 3/4 x 5 x 2in. \$20. P. & P. 5/-.

**UNR-30 4-BAND COMMUNICATION RECEIVER**


Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6 **13 gns.**



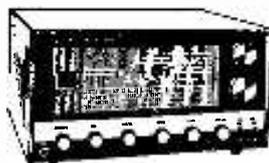**TRIO JR.310 New Amateur Band 10-80 Metre Receiver in stock. \$77.10.0.**



**LAFAYETTE SOLID STATE HA600 RECEIVER**  
5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 150 Kc/s-400 Kc/s and 550 Kc/s-80 Mc/s F E T front end ● 2 mechanical filters ● Huge dial ● Product detector ● Variable BFO ● Noise limiter ● 8 meter ● 24in Bandsread ● 230V. A.C./12V. D.C. neg. earth operation ● RF gain control. Size 15in. x 9 1/2in. x 8 1/2in. Weight 18 lbs. EXCEPTIONAL VALUE. \$45. Carr. 10/- S.A.E. for full details.

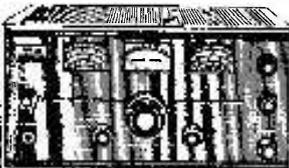


**TRIO COMMUNICATION RECEIVER MODEL 9R-59DE**  
4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical bandsread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW ● ANL ● Variable BFO ● 8 meter ● Sep. bandsread dial ● IF 455 Kc/s ● Audio output 1.5 W. ● Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. \$42, carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES.** Normally \$5.19.6. OUR PRICE \$3.15.0 if purchased with above receiver.

**TRIO JR. 500SE 10-80 Metre Receiver £69.10.0**

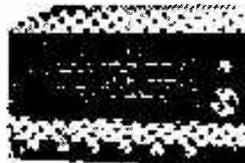**TRIO TS 510 AMATEUR TRANSCEIVER with speaker and mains P.S.U. \$212. IN STOCK!**

**LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER**  
Six bands 3-5-4, 7-7-3, 14-14-35, 21-21-45, 28-29-7, 50-54Mc/s. Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. FET front end, product detector, variable BFO, 100Kc/s crystal calibrator. 'S' Meter. Huge slide rule dial. Operation 230V AC or 12V DC. Size 15 x 9 1/2 x 8 1/2in. Complete with instruction manual. \$57.10.0 Carr. Paid. 100Kc/s crystal 39/6 extra.



**RCA COMMUNICATIONS RECEIVERS AR88D**

Latest release by ministry BRAND NEW in original cases. 110-250V. A.C. operation. Frequency in 6 Bands. 535 Kc/s-32 Mc/s continuous. Output impedance 2.5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price \$37.10.0. Carr. £2.

**LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER**

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. \$37.10.0. Carr. 10/-.




**CLASS D WAVEMETERS**



A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. \$5.19.6. Carr. 7/6 Or brand new with accessories. \$7.19.6. Carr. 7/6.

**CRYSTAL CALIBRATORS NO. 10**

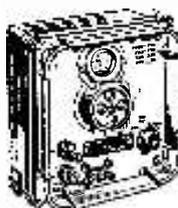

Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V. D.C. 0.3A. Excellent condition. \$89/6. Carr. 7/6.

**CLASS D WAVEMETERS No. 2**

Crystal controlled. 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. \$12.10.0. Carr. 30/-.

**CLEAR PLASTIC PANEL METERS**


First grade quality Moving Coil panel meters. Type MR 38P. 1 1/2 x 1 1/2 in. square fronts.



500-0-500 μA	27/6	150V. D.C.	27/6
1mA	27/6	300V. D.C.	27/6
1-0-1mA	27/6	500V. D.C.	27/6
2mA	27/6	750V. D.C.	27/6
5mA	27/6	15V. A.C.	27/6
10mA	27/6	50V. A.C.	27/6
50-0-50 μA	37/6	150V. A.C.	27/6
100 μA	37/6	300V. A.C.	27/6
100-0-100 μA	35/-	500V. A.C.	27/6
200 μA	35/-	8 meter 1mA	32/-
500 μA	40/-	VU meter	42/-

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

**AVOMETER MOVEMENTS**

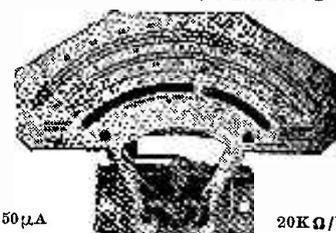

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multi-meter. Brand New & Boxed. 69/6. P. & P. 3/6. AVO 48A. Perfect order with set of shunts and resistances. \$12.10.0. P. & P. 7/6.

**TE-40 HIGH SENSITIVITY A.C. VOLTMETER**



10 meg. input 10 ranges: .01/.003/.1/.3/1/3/10/30/100/300V. R.N.S. 4cps. 1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17.10.0. Carr. 5/-.

**LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS**

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. \$12.10.0. Carr. 10/-.

**TE-65 VALVE VOLTMETER**



High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17.10.0. P. & P. 6/- Additional probes available: R.F.35/-, H.V.42/6.

**COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES**

D.C. coupled. Band width 1Kc/s. Perfect order. \$25. Carr. 30/-.

**AM/FM SIGNAL GENERATORS**



Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmec. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. \$45. Carr. 20/-.

**EDDYSTONE VHF RECEIVERS**

Model 770R. 19-165 Mc/s. Excellent condition. \$150.



**TE-16A Transistorised Signal Generator.** 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. \$7.19.6. P. & P. 4/-.

**FIELD TELEPHONES TYPE L**

Generator ringing, metal cases. Operates from two 1.5V batteries (not supplied). Excellent condition. \$4.10.0 per pair. Carr. 10/-.

**AUTO TRANSFORMERS**

0/115/230V. Step up or step down. Fully shrouded.  
150 W. \$2.2.6. P. & P. 3/6.  
300 W. \$2.19.6. P. & P. 4/6.  
500 W. \$4.10.0. P. & P. 6/6.  
1,000 W. \$6.10.0. P. & P. 7/6.  
1,500 W. \$7.19.6. P. & P. 8/6.  
7,500 W. \$15.10.0. P. & P. 20/-.

**Variable Voltage TRANSFORMERS**



Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output full variable from 0-260 volts. Bulk quantities available. 1 amp. - \$5.10.0; 2.5 amp. - \$6.15.0; 5 amp. - \$9.15.0; 8 amp. - \$14.10.0; 10 amp. - \$18.10.0; 12 amp. - \$21.0.0; 20 amp. - \$37.0.0.

**G. W. SMITH & CO (RADIO) LTD.**  
Also see oppo. page

**ARF-100 COMBINED AF-RD SIGNAL GENERATOR**



A.F. SINE WAVE 20-200,000 c/s. Square wave 20-30,000 c/s. O.P. HIGH IMP. 21V. P/P600Ω 3-8V. P/P. TF 100 Kc/s-300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £80.0.0. Carr. 7/6.

**TE-20D RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140x215x170 mm.

**PEAK-SOUND PRODUCTS.** Full range of Amplifiers, Kits, Speakers in stock.

**TY75 AUDIO SIGNAL GENERATOR**

Sine Wave 20c/s to 200 kc/s. Square Wave 20c/s to 30kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts A.C. Size 210 x 150 x 120 mm. Brand new with instructions. £16. Carr. 7/6.



**MARCONI TF142E DISTORTION FACTOR METERS.** Excellent condition. Fully tested. £20. Carr. 15/-.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**

2 pF-2000 mFd 2 ohms 200 megohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New £17.10.0 Carr. 7/6.



**MODEL ZQM TRANSISTOR CHECKER**

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9987. B: 5-200. Ico: 0-50 microamps 0-5mA. Resistance for diode 200Ω-1MΩ. Supplied complete with instructions, battery and lead. £5.19.6. P. & P. 2/6



**ADVANCE TEST EQUIPMENT**

Brand new and boxed in original sealed cartons **VM.76 VALVE VOLTMETER.** R.F. measurements in excess of 100 Mc/s and D.C. measurements up to 100V with accuracy of +2% D.C. range-300 MV to 1 KV. A.C. range 300 MV to 300 V RMS. Resistance 0.2-500 MΩ. Price £72.

**VM.79 UHF MILLIVOLT METER.** Transistorised. A.C. range 10 MV-3 V. D.C. current range -0.1μA-3 MA. Resistance 1 ohm-10 megohms. Price £125.

**H1B AUDIO SIGNAL GENERATOR.** 15 c/s-50 Kc/s. sine or square wave. Price £80.

**J1B AUDIO SIGNAL GENERATOR.** 15 c/s-50 Kc/s. Price £80.

**TT15 TRANSISTOR TESTER.** £37.10.0. Carriage 10/- per item.

**SOLARTRON MONITOR OSCILLOSCOPE TYPE 101**

An extremely high quality oscilloscope with time base of 10μs/sec to 20m/sec. Internal Y amplifier. Separate mains power supply 200/250V. Supplied in excellent condition with cables, probe, etc., as received from Ministry. £8.19.6, carriage 30/-.


**HOSIDEN DHO4S 2-WAY STEREO HEADSETS**



Each headphone contains a 2 1/2in. woofer and a 3/4in. tweeter. Built in individual level controls. 8Ω imp. 25-18,000c/s with cable and stereo plug. £5.19.6. P. & P. 2/6.

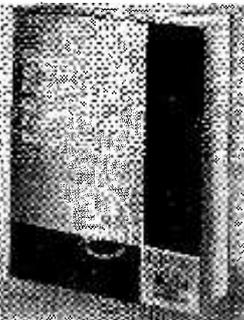**Latest Catalogue**

The latest edition giving full details of a comprehensive range of Hi Fi EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. . . . Nearly 200 pages, fully illustrated and detailing thousands of items—many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-



SEND NOW—ONLY 7/6

**GARRARD**

FULL CURRENT RANGE OFFERED BRAND NEW AND GUARANTEED AT FANTASTIC SAVINGS

- SRP22 Stereo £5.19.6
- \*1025 Mono £7.10.0
- \*1025 Stereo £7.15.0
- \*2025 Stereo £7.19.6
- \*2025T/C Mono/Stereo £8.17.6
- \*3000 Stereo £9.19.6
- \*SP25 MK II £11.19.6
- \*SL55 £11.19.6
- A70 MK II £12.10.0
- \*SL65 £14.14.0
- AP75 £17.17.0
- 401 £23. 7.6
- SL75 £23.10.0



Carriage/insurance 7/6 extra any model. WB4 Bases £3.19.6. Perspex covers £3.10.0. \*Special offer base and cover available for these models at £4.15.0. Carr. 5/- . Full range of Garrard accessories available.

**LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER**



19 transistors, 8 diodes, IHF music power, 30W at 8Ω. Response 30-20,000 ± 2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16Ω. Separate L and R. volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 1/2 x 3 9/16 x 7 13/16in. Operation 115/230V. A.C. £28. Carriage 7/6.

**MULTIMETERS for EVERY purpose!**

**TE-51. NEW 20,000Ω/VOLT MULTIMETER** with overload protection and mirror scale. 0/6/60/120/1,200v. A.C. 0/3/30/60/300/600/3,000v. D.C. 0/60/120/300mA. D.C. 0/60K/6 meg. ohm. £2/6. P. & P. 2/6.

**TE-900 20,000Ω/VOLT GIANT MULTIMETER** mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2-5/10/250/1,000/5,000 v. A.C. 0/25/12-5/10/50/250/1,000/5,000v. D.C.0/50 μA/110/100/500 mA/10 amp. D.C. 0.2K/200K/20 MEG. OHM. £15. P. & P. 5/-.

**MODEL AS-100D. 100K Ω/VOLT.** 5in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200v DC 0/5/30/120/300/600v AC. 0/10 μA/6/60/300 mA/12 amp. 0/2K/200K/2M/200MΩ. -20 to +17dB. £12.10.0. P. & P. 3/6.

**MODEL TE-10A.** 20kΩ/Volt 5/25/50/250/500/2,500v. D.C. 10/50/100/500/1,000 v. A.C. 0/50 μA/2-5mA/250mA D.C. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100mFd. 0-100-0-1mFd. 69/6. P. & P. 2/6.

**MODEL TE-80 50,000 OPV** mirror scale overload Protection 0/3/12/60/300/600/1200 v. DC. 0/6/30/120/300/1200v. DC. 0/6/60/600mA. DC. 16K/160K/1-6/10meg Ω. -20 to +63dB. £7.10.0. P. & P. 3/-.

**LAFAYETTE 57 Range Super 50kΩ/volt Multi-meter.** D.C. volts 12 mV -1000V. A.C. volts 1.5V -1000V. D.C. current 25μA-10 amp. Ohms 0-10 meg Ω dB -20 to +81 dB. Overload protection. £12.10.0. Carr. 3/6.

**MODEL TE-70.** 30,000 OPV. 0/3/15/60/300/600/1200v DC. 0/6/30/120/600/1200v AC. 0/30 μA/3/30/300mA. 0/16K/160 K/1-6M/16 Meg. Ω. £5.10.0. P. & P. 3/-.

**MODEL TE-80.** 20,000 O.P.V. 0/10/50/100/500/1,000v AC 0/5/25/50/250/500/1,000v DC. 0-50 μA/5/50/500mA. 0/6K/60K/600 K/6meg. £4.17.6. P. & P. 3/-.

**MODEL FT-34.** 1,000 OPV. 0/10/50/1250/500/1,000v AC and DC. 0/1/100/500mA DC. 0/100K Ω. 39/6. P. & P. 1/6.

**MODEL TE-12** 20,000 O.P.V. 0/0-6/6/30/120/600/1,200/3,000/6,000v. D.C. 0/6/30/120/600/1,200v. A.C. 0/60 μA/6/60/600mA. 0/6K/600K/6Meg. 50 Meg. Ω 50pF. 0-2mFd. £5.19.6. P. & P. 3/6.

**★ TRANSISTORISED FM TUNER ★**



6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**



Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.

**SINCLAIR EQUIPMENT**

Z12 12 watt amplifier, 89/6  
PZ4 Power Supply Unit 89/6  
Stereo 25 Preamp. £9.19.6  
Q14 Speakers £7.19.6  
Micromatic Radio Kit. 49/6. Built 59/6.

Now in Stock  
IC10 59/6. All post paid.  
**SPECIAL OFFER**  
Two Z12 Amps., PZ4 Power Supply, Stereo 25 Preamplifier, £22, or with two Q14 speakers, £37.

**NEW SINCLAIR 2000 SYSTEM**

35 watt Integrated Amplifier, £29. Carr. 5/-.  
Self-powered FM Tuner, £25. Carr. 5/-.

**ECHO HS-606 STEREO HEADPHONES**



Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

**RACAL MA.168 TRANSISTORISED DIVERSITY SWITCH**

Brand New Condition. £15. Carr. 10/-

**TE111. DECADE RESISTANCE ATTENUATOR**



Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600Ω range (0-1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0-0.5dB. + Indication. 3B x 0-0.1. Maximum input less than 4W (50V). Built-in 600Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.

**RECORDING HEADS**

**COSEMOCORD** 1-track heads. High imp. record/playback 65/- . Low imp. erase 20/- .  
**MARRIOTT** 1-track heads. High imp. record/playback 65/- . Low imp. erase 20/- . Post extra.

**AMERICAN TAPE**

First grade quality American tapes. Brand new. Discount on quantities.

- 3in. 225ft. L.P. acetate ..... 3/6
- 3 1/2in. 600ft. T.P. mylar ..... 10/-
- 5in. 600ft. std. plastic ..... 8/6
- 5in. 900ft. L.P. acetate ..... 10/-
- 5in. 1,200ft. D.P. mylar ..... 15/-
- 5 1/2in. 1,200ft. L.P. acetate ..... 12/6
- 5 1/2in. 1,200ft. L.P. mylar ..... 16/-
- 5 1/2in. 1,800ft. D.P. mylar ..... 22/6
- 5 1/2in. 2,400ft. T.P. mylar ..... 39/6
- 7in. 1,200ft. std. acetate ..... 12/6
- 7in. 1,800ft. L.P. acetate ..... 15/-
- 7in. 1,800ft. L.P. mylar ..... 20/-
- 7in. 2,400ft. D.P. mylar ..... 25/-
- 7in. 3,600ft. T.P. mylar ..... 45/-

Postage 2/- . Over £3 post paid.

**MAXELL TAPE CASSETTES**

C60, 10/8; C90, 14/8; C120, 19/6. Post extra

**G.W.SMITH & CO. (RADIO) LTD**

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 6562  
(Trade supplied)

**Sonotone 9TA and 9TA/H.C.** Diamond Cartridge brand new, boxed in manufacturers' carton 49/6 plus 2/6 p/p. **Acos GP 91-1 and GP 91-3** stereo compatible cartridges, new in sealed manufacturers' cartons 22/6 plus 2/6 p/p.

### BASF TAPE 25% OFF

5in. 600ft. 14/- 900ft. 19/- 1200ft. 30/-  
 5½in. 900ft. 19/- 1200ft. 24/- 1800ft. 39/-  
 7in. 1200ft. 24/- 1800ft. 35/- 2400ft. 57/-  
 P/P 2/- per reel—over £5 FREE

### SPECIAL PURCHASE 12in. 15 watt HI-FI LOUDSPEAKERS

Made by famous British manufacturer to very high standards, heavy duty cast chassis, twin cone construction, smooth extended range, with very low level of distortion.—Response 35-17,500Hz.—impedance 15 ohms—flux, 11,000 gauss.

**WALDON PRICE 97/6** each plus 6/6 P. & P.

### E.M.I. HI-FI SPEAKERS

**SET 450:** 13 x 8 with two built-in tweeters and cross-over unit. Our Price 69/6 3 or 15 ohm, 10W, 40-13,000Hz.

**SET 850:** 6½in. bass plus 3½in. tweeter and cross-over unit. 8 ohm, 10W, 65-20,000Hz. 79/6

**SET 250:** 5in. heavy duty bass plus 3in. tweeter and cross-over unit. 8 ohm, 6W, 80-20,000Hz. 65/-

Add 5/6 p/p for each speaker set.

**TRIO Stereo Moving Magnet Cartridge Model AD76K.** Diamond Stereo LP Stylus. Frequency response 20-20,000c/s output. 7mV tracking pressure 2 grammes ± 0.5 grm. Fully guaranteed. Price 85/- p/p free.

### GARRARD UNITS

	£	s	d
SP25 Mk. II ..	11	9	6
AP75 .. .. .	17	19	6
SL65 .. .. .	14	9	6
*3500 .. .. .	11	9	6

\*Denotes including Sonotone 9TA-Stereo/Diamond Cartridge. Elegantly styled plinth and cover to suit the above units. From 5 gns. Please add 10/- p/p each on all above items.

### SPEAKER ENCLOSURES


Designed to accept the full range of E.M.I. loudspeakers. Beautifully styled in teak.

Prices from **89/6** each.

### 25 WATT GROUP SPEAKERS

**Guitar group 25.** 12in. round, heavy duty cone, with solid aluminium chassis, 15 ohms imp. 12,000 gauss. Response 30-10,000c/s. OUR SPECIAL PRICE

**£5.9.6** plus 6/6 P. & P.

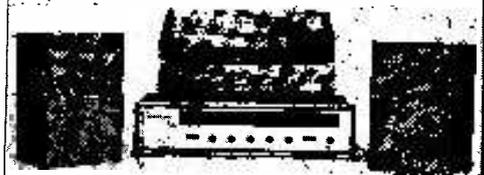

The greatest budget system available today—can't be beaten—price or quality anywhere—look at these great features—then compare:

**Teleton FZ000 Mk. II.** Tuner amp. Latest version with all the new features. Tuning indicator—fused circuit protection, AM—FM fitted multiplex, A.F.C. 2 x 5 watts per channel. A truly outstanding unit.

£ s d  
43 1 8

**Garrard 3500 (Auto/single).** Latest in the great new Garrard range, provides facilities and controls that are usually found only on much more expensive units

13 11 0

**Teleton SA1003** matching speaker systems

10 0 0

**Sonotone 9TA** stereo cartridge with diamond styli—a perfect match

4 2 0

**Plinth/Cover** elegantly styled

7 0 0

**Plugs and Leads** all supplied

1 5 0

Normal Retail Price

£78 19 8

Exclusively offered by **WALDON 63 gns** + 25/- at the remarkably low price of **63 gns** Carr.

All items may be purchased separately.

## WALDON ELECTRONICS, 707 Blackburn Road, Bolton, Lancs. Bolton 54280

PLEASE ENCLOSE 2/- IN STAMPS WITH ENQUIRIES

17in.—£11.10.0

19in. BBC 2  
**FERGUSON 39 Gns.**

**TWO-YEAR GUARANTEE  
 EX-RENTAL TELEVISIONS**


### FREE ILLUSTRATED LIST OF TELEVISIONS

17" - 19" - 21" - 23"


Wide range of models, sizes and prices  
 Carr. ins. on all sets 30/-  
**DEMONSTRATIONS DAILY**
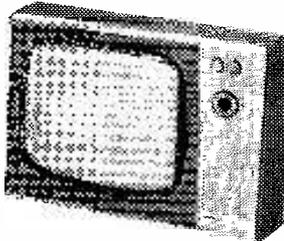
### TWO-YEAR GUARANTEED REGUNNED TUBES

70° and 90° 14in.—69/6, 17in.—89/6, 21in.—99/6, 110° 17in., 19in. and 21in.—99/6.  
 23° (not bonded)—119/6. Exchanged bowls.  
 Carr. 10/6.



### COCKTAIL/STEREOGRAM CABINET 15 gns.

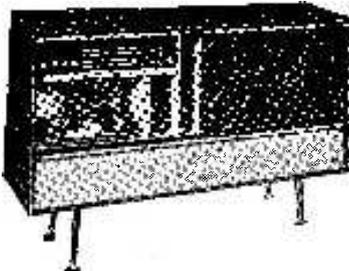

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35½in., width 52½in., depth 14½in. Legs 1 gn. extra.

**Speakers 10/-:** 3½"—25Ω. 4"—10Ω. 7" x 4"—3Ω. Brand new. P. & P. 2/6  
**Asstd. Condensers:** 10/- for 50. P. & P. 7/6. **Asstd. Resistors:** 10/- for 50. P. & P. 4/6. **Asstd. Controls:** 10/- for 25. P. & P. 7/6. **Transistors:** Mullard matched output kit 9/- OC81D—2 OC81's. P. & P. FREE.

**Ferrite Rods 3/6:** 6", complete with LW/MW Coils. P. & P. FREE.

**TRANSISTOR CASES 19/6.** Cloth covered, many colours. Size 9½" x 6½" x 3½" P. & P. 4/6. Similar cases in plastic 7/6.

**RECORD PLAYER CABINETS 49/6.** Cloth covered, size 16½" x 14½" x 8". Takes any modern autochanger. P. & P. 7/6.

**SINGLE PLAYER CABINETS 19/6.** P. & P. 7/6.

**STRIP LIGHT TUBES 3/9** each. 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1. P. & P. free.

### DUKE & CO. (LONDON) LTD.


621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3
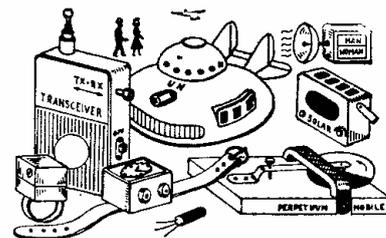
## PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4½" x 2½". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



**EXPERIMENTER'S  
 PRINTED CIRCUIT KIT  
 8/6**

Postage & Pack. 1/6 (UK)

Commonwealth:  
 SURFACE MAIL 2/-  
 AIR MAIL 8/-

Australia, New Zealand  
 South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62" x .95" x .25". (11) Wristwatch Radio 1.15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

### YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.



### 2 1/2 kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2 1/2 kW), switch down for half heat (1 1/2 kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £8.15.0. Post and ins. 7/6 or made up model £4.15.0. Post & ins. 7/6.

### FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15—20 w. 19/6. Kit B—30—40 w. 19/6. Kit C—80 w. 19/6. Kit E—65 w. 19/6. Kit MF1 is for 6in., 9in. and 12in. miniature tubes, 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 for first kit then 3/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

### BECKASTAT

This is an instant thermostat, simply plug your appliance into it and its lead into wall plug. Adjustable setting for normal air temperatures. 13A loading. Will save its cost in a season. 19/6. Post and insurance 2/9.



### REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types.

**Miniature.** lin. long x approximately 1/4 in. diameter. Will make and break up to 1/2 amp up to 300 volts. Price 2/6 each. 24/- dozen.

**Standard.** 2in. long x 3/16 in. diameter. This will break currents of up to 1 amp, voltages up to 250 volts. Price 2/- each. 13/- per dozen.

**Flat.** Flat type, 2in. long, just over 1/16 in. thick, approximately 1/4 in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp. 200 volts. Price 6/- each, £3 per dozen.

Small ceramic magnets to operate these reed switches 1/3 each. 12/- dozen.

### 15 Amp FOOT SWITCH

Suitable for Sewing Machine Motor, Drilling Machine or in fact to switch any job where both hands are to be left free. Rated at 13 amps. 250 volts. Price 22/6.

### 3 DIGIT COUNTER

For Tape Recorder or other application, re-settable by depressing button. Price 8/6.



### TRANSDUCER

Made by Acos, reference No. 1.D.1001. For measuring vibration, etc., to be used in conjunction with "G" Meter. Regular price £5. Our price 49/6. Brand new and unused.

### ISOLATION SWITCH

20 Amp D.P. 250 volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on. 4/6. 43/- per dozen.



### LIGHT CELL

Almost zero resistant in sunlight increases to 10 K. Ohms in dark or dull light, epoxy resin sealed. Size approx. 1 in. dia. by 1/2 in. thick. Rated at 500 MW, wire ended. 8/6 with circuit.

### FLEX BARGAINS

**Screened 3 Core Flex.** Each core 14/0076 Copper PVC insulated and coloured, the 3 cores laid together and metal braided overall. Price £3.15. per 100 yds. coil.

**15 Amp 3 Core Non-kink Flex.** 70/0076 insulated coloured cores, protected by tough rubber sheath, then black cotton braided with white tracer. A normal domestic flex as fitted to 3 Kw. fires. Regular price 3/6 per yd. 50 yd. coil £4.10.0. or cut to your length 2/6 per yard.

**10 Amp 3 Core Non-kink Flex.** As above but cores are 28/0076 Copper. Normal price 2/6 per yd. 100 yd. coil £7.10.0. or cut to your length 1/9 yd.

**6 Amp 2 Core Flex.** As above, but 2 Cores each 23/0076 as used for Vacuum Cleaners, Electric Blankets, etc. 39/6 100 yd. coil.

**28/0076 Triple Core P.V.C. covered,** circular, normally sold at 1/6 yd. Our price 100 yd. coil £3.19.6. Post and Insurance 6/6.

### 6, 12 or 24 VOLT SOLENOID

For energising Reed Switches, etc., size approx. 1 1/2 in. long by 1 in. diameter. Hole through Solenoid approx. 1/2 in. 8/6 each.



### 'GLADIATOR' 2 WAVE BAND TRANSISTOR RADIO

7 transistor, 2 wave band (medium and long) pocket radio with carrying handle and ear-plug. These radios use a ferrite slab aerial and a conventional superhet circuit with built in moving coil speaker. Completely built up, ready to play. Offers less than importers price due to bankrupt purchase. A remarkable bargain. 39/6 plus 3/6 post and insurance.



### MINIATURE EXTRACTOR FAN

Beautifully made by famous German Company. PAPST System, 230/240 A.C. Mains operated, size 3 1/2 in. x 3 1/2 in. x 2 in. Made for instrument cooling but ideal to incorporate in a cooker hood, etc. 65/-.

### BUY TIME SLOT METERS

If you hire out equipment such as TV sets by the hour then these slot meters are what you require. We have 3 types, 8d. an hour, 1/- an hour and 1/6 an hour. Brand new. Made by the famous Weston Company. Price £3.19.6, postage and insurance 6/6.




### DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs. Supplied complete with 6 feet of heavy cable and 13 amp plug. Similar advertised at £5. Our price 39/6, + 4/6 P & I.
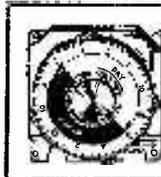
### THIS MONTH'S SNIP 24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 2 on, offs per 24 hours. Contacts rated 15 amps, repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 with Perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.



### DOUBLE ENDED MAINS MOTOR

On foot with holes for screw-down fixing. To drive models, oven, blower heater, etc. 10/- each, plus 3/6 post and insurance. 6 or more post free.




### INSTRUMENT MOTOR WITH GEAR BOX

Made by the famous Smiths Company. This motor has an 8-gear train in perspex gear box. Approximate dimensions, motor 1 1/2 in. x 1 1/2 in. diameter, gear box 3/4 in. x 2 1/2 in. diameter. Although only 2 watt motor this is really powerful and impossible to stop by hand. Mains operated and available with the following final speeds 1 rpm, 4 rpm, 30 rpm, 60 rpm, and 1 rev per hour, 35/-.


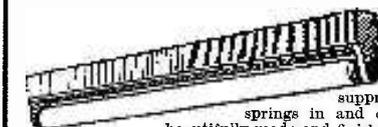
### ATLAS SLIMLINE FLUORESCENTS THE TWENTYLITE & THE FORTYTWIN

A Fluorescent lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. If left on all the time costs only one penny per day (uses 1/2 unit). Measures 2ft. long. Is ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembled ready to install. 4ft. twin model 59/6. Postage and insurance 6/6 extra.



### 1 WATT AMPLIFIER & PREAMP

5 transistors—highly efficient, made for use with tapehead G4 but equally suitable for microphone or pick up—limited quantity 29/6. Full circuit diag. also shows tape controls 5/-.



### VARYLITE

Will dim incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob £3.19.6.



### 15, 30 & 100 WATT HI FI SPEAKERS

**FULL F1 12 INCH LOUDSPEAKER.** This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in.—12 1/2 in. over mounting lugs—Baffle hole 1 1/2 in. Diam.—Mounting holes 4, holes 1 1/2 in. diam. on pitch circle 1 1/2 in. diam.—Overall height 5 1/2 in. A 26 speaker offered for only £3.9.6 plus 7/6 p. & p. Don't miss this offer. 15in. 30 watt £17.9.6. 18in. 100 watt £24.10.0.



### 5 kW PORTABLE HEATER

For workshop—stores—greenhouse, etc. Uses twin balanced motors for silent operation and reliability. three position switch gives "max. heat", "half heat", and "blow cold". A really fine heater. Price £9.19.6, plus 10/6 post and insurance.



### MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment



### WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.


### AC FAN

Small but very powerful mains motor with 5 1/2 in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



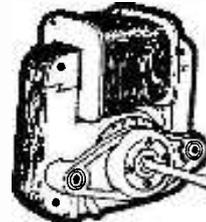
### MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.


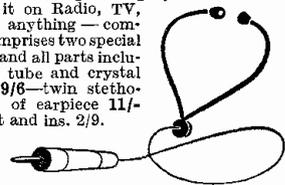
### RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal set piece. 29/6—twin stethoscope instead of earpiece 11/- extra—post and ins. 2/9.




### MAINS TRANSISTOR POWER PACK

Designed to operated transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (Class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.
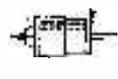
### PHILIPS TRIMMER

0-30pf an old design but one which has never been bettered. 1/- each. 10/- doz. £4.0.0 per 100.



### MOTOR WITH GEAR BOX

Very powerful 7 r.p.m., operates from standard A.C. mains. 29/6, plus 3/6 P. & P.



### INSTRUMENT BUZZER

6-12 volts adjustable tone. Very neat metal cased U.S.A.-made unit approx. 1 1/2 in. x 1 in. x 1/2 in. thick, 6/6 each



### 230 VOLT SOLENOID

1/2 in. stroke. Size 2 1/2 in. x 2 in. x 1 1/2 in. 14/6, postage 2/9.



### PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.



### SPRING COIL LEADS

as fitted to telephones, 4 core 2/6 each, 3 core 2/- each.



### PANEL LAMPS

In neat plastic cases, available in several voltages as follows: 4v., 6v., 12v., 24v., 36v., 48v., 60v., 110v., 220v., 350v. Note all below 110v. are fitted with lamps. 110v. and above are neons. Price 3/- each. 30/- dozen.



### APPLIANCE THERMOSTAT

This is a skeleton type control intended for building into oven, for baking, curing, pottery, etc. Two models, one preset for screwdriver control. The other has a shaft for knob control. Approximate operating temperature. Note only high temperature insulation used in these stats. Price 12/6 each.


## ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH  
Also 102/3 Tamworth Road, Croydon


Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please
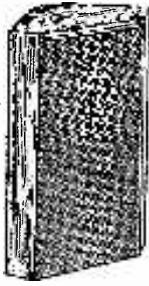
# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 3/4 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.




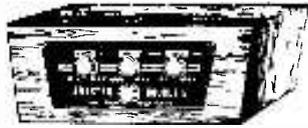**COWDREY FIVE.** Specially designed Corner Cabinet; Fitted rubber feet. 20 1/2 x 13 x 7 1/2 in. deep. Finished in natural teak veneers with Vynair front. Fitted 8 x 3 in., 7 x 4 in. and three 5 in. round speakers wired in series to match. 15 ohm impedance (handles 15 watts). £6.6.0. P. & P. 8/6 each.




**ADAstra DOUBLE 5** stereo solid state amplifier housed in handsome cabinet veneered in natural teak. Size 11 1/2 x 6 x 5 1/2 in. 10 Transistors—power output 5 watts peak per channel. 220-240v AC. Output impedance 12 to 15 ohms (our Cowdrey speaker system eminently suitable). Smart blue escutcheon. £14.14.0. P. & P. 10/6.

**SCOTT.** The elegant tapered cabinet, for table or wall mounting measuring 10 1/2 x 16 x 5 1/2 in. deep, is attractively finished in black cloth with a striped grey Vynair front fitted with 1 3/4 x 8 in. speaker with volume control. Please state impedance required—3 or 15 ohm. £4.5.0. P. & P. 7/6 each. Fitted with E.M.I. 13 x 8 in. speaker and twin tweeters. 15 ohm impedance capacity 10 watts 30/- extra.

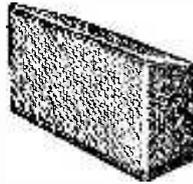

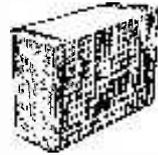**ELF.** An extension speaker of quality. 9 x 5 1/2 x 3 1/2 in. veneered in natural teak, with smart gold and brown Vynair front trimmed with white. Fitted re-conned 5 in. 3 ohm speaker. The baffle is half inch thick. A real bargain at 37/6. P. & P. 3/6.



**IMP.** Wedge shaped extension speaker cabinet is fitted with 7 x 4 in. speaker. Covered in walnut wood grain cloth with fawn Vynair front, keyhole slot in back. 7 1/2 x 6 1/2 in. Only 25/6. P. & P. 4/6 each.

**SPEAKERS:** Elac Heavy duty Ceramic Magnets 11,000 line, 10 in. round, 10 x 6 in. 3 ohm or 15 ohm. 48/6, P. & P. 3/6. 8 in. round 15 or 3 ohm, 42/6, P. & P. 3/6. E.M.I. 13 1/2 x 8 in. 3 ohm, 45/-, 15 ohm 48/6, P. & P. 1/6. E.M.I. 3 in. tweeter 17/6, P. & P. 1/6. E.M.I. 1 3/4 x 8 in. fitted two 2 1/2 in. tweeters. 15 ohm 77/6, P. & P. 4/6. E.M.I. 1 3/4 x 8 in.

(15 ohm) Hi-Fi quality £5.19.6, P. & P. 4/6. E.M.I. Woofers, 6 1/2 x 6 1/2 in. square, 8 ohm, 59/6, P. & P. 4/6. E.M.I. Crossover, 16/6, P. & P. 1/- EAGLE Crossover units 3 or 16 ohms. 16/-, P. & P. 1/- Bakers 12 in., 25 watt 15 ohm £6.6.0, P. & P. 3/6.

**TEAK PLINTH AND PERSPEX DUST COVER** for SP25 etc. £5.5.0. P. & P. 5/-

**VYNAIR.** Widths from 40 to 54 in., 17/6 yd. off roll. P. & P. 1/9. 1/2 yard, 9/-, P. & P. 1/9. Send 1/- stamps for samples.

**SPEAKER MATCHING TRANSFORMERS.** 3, 7, 15 ohms, 8 watt, 11/6. P. & P. 1/6.

**MICROPHONES:** Xtal Hand Mikes. B1201 with stand, 54/8. P. & P. 3/6. ACOS Mike 45, 21/- ACOS Mike 40, 18/6. Dyn. Mkr. DM-391, 30/- CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/- Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-

**FERROX RODS:** 6 x 5/16 in., 2/6; 4 1/2 x 3/8 in., 2/-; 6 x 3/16 in., 2/6; 8 x 3/16 in., 3/-, P. & P. 1/- each.

**FERROX RODS WITH COILS.** 4 1/2 x 3/16 in., 3/6; 8 x 5/16 in., 5/6. P. & P. 1/- each.

**ROTARY SWITCHES:** 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/-

**TRANSISTOR SPEAKERS** 8 ohm 2 in., 8/6. 3 in., 10/6. P. & P. 1/-

**CARTRIDGES.** Stereo: Sonotone 9TA H/C Diamond, 47/6. 9TA Sapphire, 37/6. 8TA Sapphire, 30/- Ronette S105 Medium Output, 28/6. S106 High Output, 28/6. DC284 Stereo Compatible, 22/6. Acos GP93/1 Sapphire, 37/6. GP94/1 Sapphire, 39/6. GP81 Diamond, 42/- GP91 Stereo Compatible (High, Medium or Low Output), 25/- TA500 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 60/- TA700 equivalent to B.S.R. SX1M, 35/- Japanese equivalent to B.S.R. TC8, 35/-

**Mono:** Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/- B.S.R. TCSH Jap. equivalent, 26/- Sonotone 2TSS, 15/- P. & P. 1/6.

**EARPIECES WITH CORD** and 3-5 mm. plug. 3 ohm magnetic, 3/- 250 ohm, 4/- 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

**PIANO KEY PUSH BUTTON SWITCHES.** 7 button inc. mains on off. 6 banks of 6 P.C.O., 3/6. P. & P. 1/-

**BROADWAY Electronics** (Few minutes from Tooting Broadway Underground Stn)  
92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01-672 3984 (Closed all day Wednesday)

# R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m. —5.30 p.m.  
Closed Sat. 1.30—2.30 p.m.  
Open Daily to Callers

Tel. 769-0199/1649

1A7 7/9	6BQ7A 7/-	6K7M 6/6	7Y4 8/6	20P5 20/-	80 7/6	DF96 7/6	ECF82 6/6	EM80 7/6	PC97 8/9	RG5/50080 4/-	UF89 7/6
1D5 7/6	6BR7 17/-	6K7G 2/-	9BW6 7/-	25A6 5/9	85A2 7/3	DH77 4/9	ECH21 12/6	EM81 8/3	PCC84 6/6	S130 40/-	UL41 12/-
1H5 7/-	6BR8 12/6	6K7GT 4/6	10C1 12/6	25L6GT 7/-	1502B 11/6	DK32 7/9	ECH35 11/6	EM84 7/6	PCC89 10/6	SP4 8/-	UL84 7/-
1LD5 6/-	6BS7 25/-	6K8 2/9	10C2 12/6	25Y5 6/-	150C4 9/6	DK91 6/-	ECH42 12/6	ESU15020/-	PCC189 10/6	SP41 5/6	UM80 5/6
1N5GT 8/-	6BW6 14/6	6K8M 11/6	10F1 14/9	25Z4 6/3	801 9/6	DK92 9/9	ECH51 5/9	EY51 8/-	PCF80 6/9	SP61 5/-	UC6 21/-
1R5 6/-	6BW7 13/-	6K8G 3/-	10F3 18/-	25Z5 8/-	807 9/6	DK96 7/9	ECH53 8/6	EY86 7/-	PCF82 6/6	STV280/80	UU7 21/-
1S4 5/6	6C5G 5/-	6K8T 7/-	10F8 10/6	25Z6 8/6	813USA	DL66 25/-	ECL50 5/9	EZ35 6/-	PCF84 8/-	STV280/80	UU8 21/-
1S5 4/6	6C6 3/9	6K25 15/-	10F18 8/-	28D7 9/3	813	DL82 6/3	ECL52 7/-	EZ40 8/9	PCF86 9/-	SU25 95/6	UU9 8/3
1T4 4/-	6C8G 8/-	6L1 8/-	10L1 8/-	30C1 6/9	813 75/-	DL93 4/-	ECL53 10/3	EZ41 9/6	PCF801 9/9	SU2150 12/6	UY21 9/6
3A4 4/-	6CD8G 24/-	6L18 6/-	10L11 10/6	30C15 15/-	866A 15/-	DL94 6/9	ECL58 9/6	EZ80 5/6	PCF802 9/9	T41 17/6	UY41 8/6
3Q4 7/9	6CH6 7/6	6Q7G 6/-	11E3 70/-	30C17 16/-	954 5/3	DL95 7/9	ECL86 9/-	EZ81 5/6	PCF805 15/-	TDD4 8/6	UY85 8/5
3Q5 7/-	6CW4 12/-	6Q7GT 8/6	12AT6 4/9	30C18 15/-	1625 6/6	DL96 7/9	ECL800	GZ30 10/-	PCF806 13/-	U10 7/6	VMP4G 17/-
3S4 6/3	6D6 3/9	6SA7M 7/-	12AT7 6/3	30F1 17/-	4022AR 67/-	DM70 6/-	EF9 20/-	GZ32 10/-	PCF808 15/6	U14 7/6	VP4B 25/-
3V4 6/9	6E5 7/6	6SAC7 7/-	12A06 5/9	30F5 17/-	5763 12/-	DY86 5/-	EF37A 7/-	GZ34 11/-	PCL82 7/9	U19 35/-	VR105/30
5R4GY 10/6	6F1 12/6	6SG7 6/-	12A07 5/9	30F11 18/-	5763 12/-	DY87 5/-	EF39 8/-	HN309 22/6	PCL83 10/3	U25 15/6	VR150/30
5U4G 5/6	6F5G 4/6	6SH7 3/3	12AX7 6/3	30L15 17/-	7475 14/-	E88CC 12/-	EF41 12/-	KT36 18/-	PCL84 8/6	U26 15/6	VT25 15/-
5V4G 3/-	6F6G 5/-	6SJ7 6/-	12BA6 6/3	30L17 17/-	ATP4 2/3	EA50 3/6	EF50 5/-	KT61 17/6	PCL85 9/3	U78 4/6	VT31 80/-
5Y3GT 6/-	6F8G 5/6	6SK7GT 4/9	12BE6 6/3	30L17 17/-	ATP5 15/-	EABC80 6/6	EF50 4/3	KT66 21/-	PCF86 9/3	U119 13/9	VT31 80/-
5Z4G 7/-	6F11 6/6	6SL7GT 6/-	12C8GT 5/-	30P12 16/-	ATP7 8/6	EA42 10/-	EF56 7/-	KT81 35/-	PEN44 20/-	U251 16/3	VR111 8/9
6J30L2 15/-	6F13 6/6	6SN7GT 5/6	12E1 20/-	30P19 15/-	AU2 80/-	EB41 10/-	EF86 6/6	KT81 (7C5)	PEN44 20/-	U301 12/6	VU120 12/6
6A7 15/-	6F14 12/6	6SUG7 7/6	12J5GT 2/6	30P18 18/-	AU5 8/9	EB91 3/-	EF89 5/6	KT88 22/6	PEN45 7/-	U403 6/6	VU508 35/-
6ASG 12/6	6F23 16/-	6U4GT 12/-	12J7GT 6/6	30P113 18/6	AZ1 8/-	EB93 8/6	EF89 5/6	KTW61 3/6	PEN46 4/-	U404 7/6	VR150/30
6AC7 4/-	6F24 14/-	6U5G 7/6	12K7GT 7/-	30P114 15/-	ABZ1 16/-	EB99 4/9	EF92 2/6	KTZ41 6/-	PL36 10/9	U801 23/6	VR150/30
6AK5 5/-	6F25 15/-	6V6M 12/-	12K8GT 8/-	35A5 11/6	CBL131 10/-	EBF80 7/6	EF98 15/-	ML4 17/6	PL81 8/-	UABC80 6/6	VR150/30
6AM5 4/6	6F28 14/-	6V6G 4/6	12Q7GT 6/-	35L6 9/-	CBL35 15/-	EBF83 9/6	EF183 6/6	ML6 7/6	PL82 8/6	UAF42 10/6	VR150/30
6AM6 3/6	6F32 2/9	6V6GT 6/6	12SA7 8/-	35W4 4/6	CL33 20/-	EBF89 6/6	EF184 7/-	MSP4 10/-	PL83 7/6	UBC41 9/6	VR150/30
6AQ5 6/3	6G6 2/6	6X4 4/6	12SG7 6/-	35Z3 10/-	CV450 25/-	EBL1 14/-	EL32 3/6	MU14 7/6	PL84 7/-	UBC81 9/3	VR150/30
6AS7G 16/-	6H6 3/-	6X5G 4/6	12SH7 3/9	35Z4GT 8/6	CV30 12/6	EBL21 12/-	EL33 12/6	N78 19/-	PL500 14/6	UBF80 7/6	VR150/30
6AT6 4/9	6J5M 9/-	6X5GT 6/-	12SJ7 4/9	35Z5 6/-	CV31 8/6	EBL31 27/6	EL34 12/6	NT8 25/-	PL84 7/-	UBF89 7/6	VR150/30
6AU6 5/-	6J5G 4/-	7B6 11/6	12SK7 4/9	37 6/6	DAC32 7/-	EC90 5/-	EL38 22/6	NGT1 3/6	PL85 7/6	UCF80 7/6	VR150/30
6BAG 2/6	6J5GT 5/6	7B7 7/6	12SR7 5/-	42 6/-	DAP91 4/6	ECC81 5/6	EL41 10/6	NGT2 5/6	PL87 7/6	UCF85 7/6	VR150/30
6BA6 5/-	6J7G 6/6	7C5 22/6	12SH7 3/9	50B5 6/6	DAP96 7/6	ECC82 5/9	EL42 10/6	OA2 8/-	PL88 7/6	UCF89 8/6	VR150/30
6BE6 5/-	6J7GT 7/6	7C6 15/-	19AQ5 5/-	50C5 6/3	DOC90 10/6	ECC83 6/6	EL42 10/6	OC3 5/-	PL89 7/6	UCH42 10/6	VR150/30
6BH6 9/-	6K6GT 7/6	7D5 8/-	20L1 20/-	50CD6G31/-	DF33 8/-	ECC84 5/6	EL84 4/9	OC3 5/-	PL89 7/6	UCH82 6/9	VR150/30
6BJ6 9/-	6K7 1/9	7H7 6/6	20F2 14/-	50L6GT 8/-	DF70 9/-	ECC85 7/6	EL95 6/6	OC4 4/6	PL89 7/6	UCL83 10/-	VR150/30
		7H7 13/-	20L1 20/-	75 9/6	DF91 4/-	ECC88 5/6	EL95 6/6	OC36 11/6	PL89 7/6	UCL83 10/-	VR150/30
		7S7 45/-	20P4 20/-	78 5/-	DF92 3/6	ECC88 5/6	EM34 21/-	PC88 11/6	PL89 7/6	UF41 10/6	VR150/30

Manufacturers and Export Inquiries Welcome  
OBSOLETE TYPES A SPECIALITY  
QUOTATIONS FOR ANY VALVE NOT LISTED  
Express postage 9d. per valve.  
Ordinary postage 6d. per valve. C.W.O. No C.O.D.  
Tube postage 7/6 each  
**Special Express Mail Order Service**

<b>TUBES</b>	14 inch .. £4 0 0	<b>SETS OF VALVES</b>	DAF91, DF91, DK91, DL92 or DL94 .. 19/- plus postage
	17 inch .. £4 5 0		DAF96, DF96, DK96, DL96 .. 27/6 plus postage
	19 inch .. £6 0 0	<b>TRANSISTORS</b>	
	21 inch .. £6 10 0	AC127 5/-	OC25 8/-
	23 inch .. £12 0 0	AF114 5/-	OC28 8/-
	27 inch .. £8 0 0	AF115 5/-	OC35 6/-
		AF116 5/-	OC44 4/6
		AF117 5/-	OC45 2/6
		OC71 2/6	OC81 4/-
		OC72 6/-	OC81D 4/-
		OC75 6/-	OC81DM 4/-
		OC76 6/-	OC170 7/-
		OC77 8/-	OC171 8/-
			OC82 6/-
			OC200 7/6

SEND S.A.E. FOR LIST OF 2,000 TYPES

# COMPLETE STEREO SYSTEM

FOR ONLY

# 39 GNS

CARRIAGE 35/-

The Premier Stereo System consists of an all transistor stereo amplifier, Garrard Model 2025 auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of two watts per channel with inputs for pick up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

### SPECIAL OFFER CARTRIDGES

	SHURE	Premier Price
M3D	£8.10.6	£6.19.6
M44-5	£14.9.1.	£10.10.0
M44C	£12.19.6	£9.9.0
M44E	£17.8.4	£13.19.6
M55E	£20.15.1	£15.15.0
M75-6	£17.8.4	£13.19.6
M75E	£25.18.10	£21.0.0

### AUDIO TECHNICA

A.T.7S stereo	£22.0.0	£15.0.0
A.T.7X elliptical	£25.0.0	£18.0.0

Post and Packing 1/6 each

### "NOVA" TRANSISTOR STEREO AMPLIFIER

A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 10 watts per channel. Frequency response 40-20,000 Hz ± 3dB. Inputs for radio, P.U. Ceramic, P.U. Magnetic Tape, Separate bass and treble controls, Volume and Balance controls Mono/Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14 1/2 x 9 1/2 x 3 1/2 in. A.C. 200/250V.



WONDERFUL VALUE  
AT ONLY 25 Gns. Carr. 10/-

### PICK-UP CARTRIDGES


AT MONEY SAVING PRICES!

GOLDRING G800 (Stereo)	£8.19.6
SONOTONE 9TAHC/D (Stereo)	£2.15.0
ACOS GP91/18C (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 8.7
ACOS GP94 (Stereo)	£2.14.8
B S R X3M (Mono compatible)	£1.16.5
B S R X3H (Mono compatible)	£1.16.5
RONETTE 105 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.
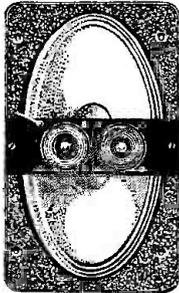
### WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dulci, Wharfedale, Goodmans, Goldring, Shure, etc. etc.



### E.M.I. 13 x 8 in. HI-FI SPEAKERS

Fitted two 2 1/2 in. tweeters and crossover network. Impedance 3 and 15 ohms. Handling capacity 10 watts. Brand new. 99/6, p. & p. 7/6.

Also available without tweeters 49/6, p. & p. 7/6.

**TEAK FINISHED CABINET**  
Size 17 1/2 x 10 x 7 1/2 in. Ideal for above speakers £5.10.0, p. & p. 10/-.



### HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2" speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

59/6 P. & P. 5/-

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.  
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-.  
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-.

### "NOVA" 5 WATT PER CHANNEL STEREO AMPLIFIER.

Specification as above. £18 18 0, Carr. 10/-.

### SAVE NEARLY £5!

Premier Stereo System with "Nova" 10 watt Stereo Amplifier as above. 45 Gns. Carr. 35/-.

### VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phonoplug output. Attractive teak wood grain finish case.



MONO MODEL 59/6 STEREO MODEL 69/6 P. & P. 2/6.

### VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use; this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.



34/6 P. & P. 1/6.

### SPECIAL BARGAIN OFFER

B.S.R. MA75 RECORD PLAYER UNIT. 4 speeds. Automatic or Manual operation. Low mass arm with cue and pause lever, bias compensator, stylus pressure adjuster, etc. Complete with Stereo/Mono Cartridge. Original Price £17.17.8.



Our Price 12 Gns. Carr. 10/6

### "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped - attractively boxed

LP3 3"	250'	P.V.C.	5/6	LP6 5 1/2"	1200'	P.V.C.	12/6
TT3 3"	450'	POLYESTER	7/6	DT6 5 1/2"	1800'	POLYESTER	22/6
DT3 3 1/2"	600'	POLYESTER	11/6	TT6 5 1/2"	2400'	POLYESTER	37/6
SP5 5"	600'	P.V.C.	8/6	SP7 7"	1200'	P.V.C.	12/6
LP5 5"	900'	P.V.C.	10/-	DT7 7"	2400'	POLYESTER	25/-
DT5 5"	1200'	POLYESTER	15/-	TT7 7"	3600'	POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5", 5 1/2", 7" 1/9, TAPE CASES 5", 7" 2/6.  
Post and Packing 3" 1/-, 5", 5 1/2" 1/6, 7" 2/- (3 reels and over Post Free).




**WELLER "EXPERT" SOLDER GUN.** Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. 67/6 P. & P. 2/-.



**POCKET SIZE MULTI-TESTER** With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C. 19 Ranges: 0-5-25-50-250-500-2500 volts DC. 0-10-50-100-500-1000 volts AC. 0-50µA-2.5 mA-250 mA DC. 0-6000 ohms-6 megohms, 10µ µf-0.001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. £4.19.6 P. & P. 3/6.
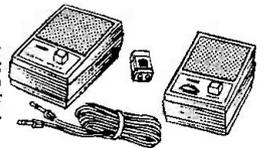
### TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc. 65/- P. & P. 4/-.



**FOUR STATION INTERCOM.** Master unit and 3 slaves. Ideal for office and home. Complete with battery and connecting wire £7.19.6 P. & P. 5/6.

### "PREMIER" TAPE CASSETTES



C60 (60 min.) 7/6

THREE FOR 21/-

C90 (90 min.) 12/6

THREE FOR 36/-

C120 (120 min.) 17/6

THREE FOR 51/- P. & P. 1/-.



### CASSETTE HEAD CLEANER

Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. 11/6 P. & P. 1/-.

# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1

Tel: 01-636 3451

OXFORD ST.



# LIND-AIR OPTRONICS LTD

## TTC.C1001 MULTITESTER in leather case.




Overload protection.  
20,000 opv. AC volts  
10, 50, 250, 1,000v.  
DC volts 5-25, 125,  
500, 2500v. D.C. Cur-  
rent 0-50µA, 0-250mA  
Resistance 0-60K, 0-6  
Megohm. Decibels -20  
to +22dB. Size of  
meter 4 1/2 x 3 1/2 in.  
85/- P. & P. 3/6.

## SEIRA 68D MULTI-TESTER 20,000 o.p.v.

DC voltage: 5-25-50-250-500-2.5K (20,000 ohms per volt). AC Voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50µA, 0-2.5mA, 0-250mA. Resistance: 0-6K, 0-6Mg (300 ohm and 30K at centre scale). Capacitance: 10pf. to 0.01 mfd., 0.01µf to 1µf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 in. 71/- P. & P. 3/6



## S-DeC BREAD BOARD

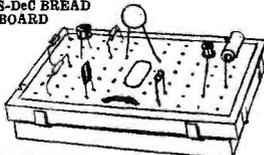

### British Made

Solderless breadboard panels, for fast reliable component connections.  
Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.

4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £5.17.6. P. & P. 3/6.

## GARRARD DECKS



- SRP22 less cartridge..... £5. 9.6
- 1025 Stereo/Mono with cart. .... £6.19.6
- 2026 Stereo/Mono with cart. .... £7.19.6
- 3006S Stereo/Mono with cart. .... £9.19.6
- 3000D Stereo/Mono with cart. .... £10.19.6
- SP25 less cartridge..... £11.19.6
- SP25 with Decca Deram cart. .... £17. 4.6
- SL55 less cartridge..... £11.19.6
- SL55 with Decca Deram cart. .... £17.4.6
- SL66 less cartridge..... £14.9.6
- Covers for above..... £8.19.6
- Bases for above..... £2.10.0
- AP75 less cartridge..... £18.18.0
- SL75 less cartridge..... £28.7.0
- SL95 less cartridge..... £38.19.6
- Bases for above..... £4.19.6


**SPECIAL OFFER!**  
SP25 less cart., with base..... £13. 2.6  
P. & P. Decks 12/6, Cover 4/6, Base 4/6.  
P. & P. Deck/Cover/Base 17/-.

## SPECIAL OFFER!

**SONOTONE STAHO Stereo Cartridge** with diamond stylus. Normal retail price 4 gns.  
**OUR PRICE 55/-, P. & P. 1/6**  
Suitable for use with all Garrard decks.
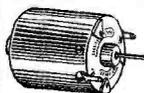
## MODEL MAKER'S MOTOR

No. 16RN. Voltage 11.5v.  
Current 400mA. Torque.  
12g-cm. Body size  
1 1/2" long x 1 1/2" dia.  
Shaft 3/16" long x  
1/16" dia. Ideal for  
small models and  
toys. 5/6 each.  
P. & P. 1/3. 3 for 15/- P. & P. 2/6.



9V d.c. Gram deck replacement motor.  
2in x 1 1/2in dia.  
Shaft with long x  
3/32in. 17/6. P. & P. 2/6.

## Special Lind-air Offer!




**Teleton  
SAQ203**  
Transistor  
Stereo  
Amplifier

List Price £28.7.0.

**OUR PRICE 22 Gns**

One of the most popular models from the fabulous Teleton range. Incorporates 16 transistors and diodes producing superb quality hi-fi. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble. Housed in attractive oiled walnut cabinet with brushed aluminium front panel.

## MAINS KEYNECTOR SAVES TIME—SAFELY!

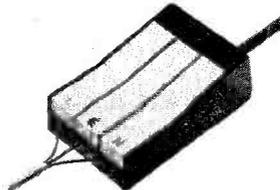

One mains "Keyconnector" instantly and safely connects electrical appliances to mains supply without the use of a plug. A number of appliances may be used simultaneously up to the full 13 amp rating of this device. A red light glows when "live". The "Keyconnector" is fused and has its own robust switch which is interlocked to prevent connections when "live". *Unvaluable to handymen, servicemen, demonstrators etc.*

39/6 P. & P. 3/-.

## VHF AIRCRAFT BAND CONVERTOR.



When placed within line of a MW band radio full coverage of VHF Aircraft Band 108-135 Mc/s. can be obtained. All transistor. 9v battery operation. Fully tunable 18in. x 7 section telescope aerial. Size 4 x 2 1/2 x 1 1/2in. 79/6. P. & P. 3/6.

## SINCLAIR IC-10 INTEGRATED CIRCUIT



10 watt Amplifier. Size only 1.0 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. ONLY 59/6. P. & P. 1/6.


**SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10** from A.C. mains 230/250V. Output 13v. at 0.5 amp. 12/6. P. & P. 2/6.

## SINCLAIR PROJECT 60

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly.  
Z.30 24 watt Power Amplifier 59/6 (2 required).  
Stereo Sixty Control/Pre-amplifier 29.19.6  
P.Z.5 Power Supply Unit £4.19.6.  
Project 60 is supplied complete with instruction manual and templates for plinth mounting.
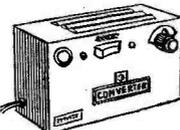
## "HI-TEN" LOUSPEAKER

British made full range 10in. unit handles up to 10 watts. Ceramic magnet. Freq. response: 40 to 10,000 cps. Imp: 15 ohms Flux density: 10,000 lines. 49/6. P. & P. 4/6.



**Battery Eliminator.** Enables transistor equipment to be operated from A.C. mains. 6/9 12v. output.

Selector switch and on/off switch, 100mA. Case size 4 x 2 1/2 x 2in. complete with mains lead, connecting leads and instructions. 59/6. P. & P. 3/6.



## DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000cps. With lead and stereo plug. ONLY 59/6. P. & P. 3/6.

# TRANSFORMERS

## AUTO WOUND TRANSFORMERS

All Winding Voltage Ratings and Tapping 0-115-200-220-240v except MT118-0-115-210-240v.

Model	Watts	Size	Wgt	11oz	Price	P&P
MT118	20W	2 1/2 x 1 1/2 x 2 1/2 in.	Wgt	1 1b	12oz	Price 12/6 P&P 2/6
MT64	75W	2 1/2 x 2 1/2 x 2 1/2 in.	Wgt	3 1b	14oz	Price 21/9 P&P 4/6
MT4	150W	3 1/2 x 2 1/2 x 3 in.	Wgt	3 1b	Price 38/-	P&P 6/-
MT65	200W	3 1/2 x 4 1/2 x 4 in.	Wgt	4 1b	Price 39/6	P&P 6/-
MT66	300W	4 x 4 x 3 1/2 in.	Wgt	6 1b	7oz	Price 59/4 P&P 9/-
MT110	400W	4 1/2 x 4 1/2 x 4 in.	Wgt	11 1b	Price 85/-	P&P 10/6
MT67	500W	5 1/2 x 4 x 4 1/2 in.	Wgt	12 1b	8oz	Price 89/- P&P 10/6
MT88	750W	5 1/2 x 5 1/2 x 5 1/2 in.	Wgt	13 1b	4oz	Price 95/7 P&P 10/6
MT84	1000W	5 1/2 x 5 1/2 x 5 1/2 in.	Wgt	16 1b	Price 142/2	Carr. ex.
MT93	1500W	5 1/2 x 5 1/2 x 6 1/2 in.	Wgt	28 1b	9oz	Price 170/8 Carr. ex.
MT94	1750W	5 1/2 x 5 1/2 x 6 1/2 in.	Wgt	31 1b	Price 195/-	Carr. ex.
MT95	2000W	5 1/2 x 5 1/2 x 6 1/2 in.	Wgt	40 1b	Price 211/2	Carr. ex.
MT73	3000W	6 1/2 x 7 x 8 1/2 in.	Wgt	45 1b	8oz	Price 300/- Carr. ex.

## LOW VOLTAGE 12 VOLT RANGE

Primary	Secondary	Wgt	12oz	Price	P&P	
200-250v	12v	Wgt	1 1b	12oz	Price 15/8 P&P 2/6	
MT11	0.5 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt	1 1b	Price 19/- P&P 3/9	
MT71	2 Amp	Size 2 1/2 x 3 1/2 x 2 1/2 in.	Wgt	2 1b	4oz	Price 28/- P&P 6/-
MT69	4 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt	3 1b	12oz	Price 39/- P&P 6/-
MT70	6 Amp	Size 4 x 3 x 3 1/2 in.	Wgt	6 1b	3oz	Price 51/- P&P 9/-
MT72	10 Amp	Size 3 1/2 x 4 1/2 x 4 in.	Wgt	11 1b	13oz	Price 85/- P&P 9/-
MT115	20 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt	16 1b	12oz	Price 180/- P&P 13/6
MT187	30 Amp	Size 5 1/2 x 4 1/2 x 4 1/2 in.				

## LOW VOLTAGE 24 VOLT RANGE

Primary	Secondary	Wgt	11b	7oz	Price	P&P
200/250v	24v	Wgt	1 1b	7oz	Price 23/9	P&P 4/6
MT98	1 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt	3 1b	6oz	Price 38/- P&P 6/-
MT114	3 Amp	Size 2 1/2 x 3 x 3 in.	Wgt	5 1b	12oz	Price 53/10 P&P 9/-
MT72	5 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt	7 1b	8oz	Price 75/7 P&P 9/-
MT17	8 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt	11 1b	13oz	Price 95/- P&P 11/-
MT115	10 Amp	Size 4 1/2 x 4 1/2 x 4 in.	Wgt	11 1b	13oz	Price 95/- P&P 11/-

## LOW VOLTAGE 30 VOLT RANGE

Primary 200/250v Secondary Tapped 12-15-20-24-30

MT112	0.5 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt	1 1b	4oz	Price	17/4	P&P	3/9
MT79	1 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt	2 1b	Price	23/-	P&P	6/-	
MT20	3 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt	4 1b	8oz	Price	46/2	P&P	9/-
MT51	5 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt	6 1b	8oz	Price	60/9	P&P	9/-
MT98	8 Amp	Size 5 1/2 x 3 1/2 x 4 1/2 in.	Wgt	9 1b	6oz	Price	92/4	P&P	11/-
MT89	10 Amp	Size 5 1/2 x 4 1/2 x 4 1/2 in.	Wgt	12 1b	2oz	Price	103/6	P&P	11/-

## LOW VOLTAGE 50 VOLT RANGE

Primary	Secondary	Wgt	11b	11oz	Price	P&P
200-250v	50v	Wgt	1 1b	11oz	Price 21/3	P&P 6/-
MT102	0.5 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt	5 1b	Price	45/8 P&P 6/-
MT104	2 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt	6 1b	Price	77/- P&P 9/-
MT106	4 Amp	Size 4 1/2 x 3 1/2 x 4 in.	Wgt	18 1b	9oz	Price 135/- P&P 13/6
MT118	8 Amp	Size 5 1/2 x 3 1/2 x 4 1/2 in.	Wgt	19 1b	12oz	Price 165/- P&P 15/6
MT119	10 Amp	Size 6 1/2 x 4 1/2 x 6 1/2 in.	Wgt	19 1b	12oz	Price 165/- P&P 15/6

## LOW VOLTAGE 60 VOLT RANGE

Primary	Secondary	Wgt	2 1b	4oz	Price	P&P
200/250v	60v	Wgt	2 1b	4oz	Price 94/-	P&P 6/-
MT124	0.5 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt	5 1b	8oz	Price 52/10 P&P 9/-
MT127	2 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt	10 1b	6oz	Price 99/- P&P 11/-
MT123	4 Amp	Size 4 1/2 x 3 1/2 x 4 1/2 in.	Wgt	23 1b	2oz	Price 152/- Carr. ex.
MT122	10 Amp	Size 6 1/2 x 5 1/2 x 6 1/2 in.				

## MAINS H.T. RANGE

Model	Primary	Secondary	Wgt	Price	P&P
MT1AT	250-0-250v	80MA 6-3v 3-5A 5/6-3v 1A	3 1/2 x 3 x 3 in.	33/-	6/-
MT2AT	250-0-250v	100MA 6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in.	35/6	6/-
MT110	250-0-250v	120MA 6-3v 3-5A 5/6-3v 1A	4 x 4 x 3 1/2 in.	44/9	6/-
MT11AT	300-0-300v	100MA 6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in.	37/9	6/-
MT12AT	300-0-300v	120MA 6-3v 4A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in.	46/2	9/-
MT3AT	300-0-300v	150MA 6-3v 4A 5/6-3v 1A	4 x 4 x 3 1/2 in.	59/4	9/-
MT2AT	350-0-350v	80MA 6-3v 3-5A 5/6v 1A	4 x 3 1/2 x 3 1/2 in.	38/6	6/-
MT7	350-0-350v	100MA 6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in.	42/4	6/-
MT8	350-0-350v	120MA 6-3v 3-5A 5/6-3v 1A	4 x 3 1/2 x 3 1/2 in.	50/-	6/-

## BATTERY CHARGER TYPES


Primary	Secondary	Wgt	11b	6oz <th>Price</th> <th>P&amp;P</th>	Price	P&P
200-250v	6-12v.	Wgt	1 1b	6oz	Price 21/9	P&P 4/6
M77	1 Amp	Size 2 1/2 x 2 1/2 x 2 1/2 in.	Wgt	3 1/2	Price	25/4 P&P 6/-
MT45	1.5 Amp	Size 3 1/2 x 2 1/2 x 2 1/2 in.	Wgt	3 1b	11oz	Price 33/- P&P 6/-
MT46	2 Amp	Size 4 x 2 1/2 x 2 1/2 in.	Wgt	5 1b	4oz	Price 42/- P&P 6/-
MT47	3 Amp	Size 4 x 3 x 3 1/2 in.	Wgt	6 1b	4oz	Price 48/- P&P 6/-
MT5	4 Amp	Size 4 x 2 1/2 x 3 1/2 in.	Wgt	6 1b	4oz	Price 42/- P&P 6/-
MT78	5 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt	7 1b	8oz	Price 56/7 P&P 9/-
MT86	6 Amp	Size 4 x 3 1/2 x 3 1/2 in.	Wgt	7 1b	8oz	Price 75/- P&P 9/-
MT48	7 Amp	Size 4 x 4 x 3 1/2 in.	Wgt	8 1b	3oz	Price 105/- P&P 9/-
MT146	8 Amp	Size 4 1/2 x 3 1/2 x 3 1/2 in.	Wgt	11 1b	14oz	Price 125/- P&P 11/-
MT49	9 Amp	Size 4 1/2 x 3 1/2 x 3 1/2 in.				
MT147	10 Amp	Size 4 1/2 x 4 x 4 in.				
MT50	12.5 Amp	Size 5 1/2 x 4 1/2 x 4 1/2 in.				

Amperages are D.C. with nominal selenium bridge rectifiers  
MAINS ISOLATING RANGE ALSO AVAILABLE

# LIND-AIR OPTRONICS LTD

See our vast range of Electronic Components and Accessories at our enlarged Component Centre 25 Tottenham Court Road

## TRANSISTOR MODULES

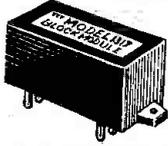

**E.1311. PHONO PRE-AMPLIFIER.** Size 2x1x1/2 in. Built-in R.I.A.A. characteristics enabling low output magnetic pick-up cartridges to be amplified up to 1 volt. Input 100Kohm. Gain 28dB. Max. output 3v. Max. input 50mV. Distortion 0.15% (at 1v level). Power supply 9-12v. 29/6. P. & P. 2/-.

**E.1313. MICROPHONE PRE-AMPLIFIER.** Enables a low output microphone to be used with an amplifier or radio. Input imp. 100Kohms. Gain 28dB. Max. output 3v. Max. input 50mV. Distortion 0.15% (at 1v level). Freq. response 10Hz-50KHz. Power supply 9-12v. 29/6. P. & P. 2/-.

**E.1318. DUAL LAMP FLASHER.** A switch module for electronically alternating two miniature bulbs, 6V, 100-200mA. Ideal for models, toy boats and planes, displays, warning and security devices, communication signals, etc. Flasher time 1/2 sec. Power supply 6v DC. Current 150mA. Lamp 6v 150mA. 25/- P. & P. 2/-.

**E.1315. ELECTRONIC ORGAN TONE OSCILLATOR.** Used in conjunction with an organ keyboard, variable resistances and a 9 volt power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz. Output 80mW. Current 15mA. 25/- P. & P. 2/-.

**E.1314. POWER AMPLIFIER.** When used in conjunction with E.1311, E.1312 and E.1313 units this amplifier module produces about 300mW output for speaker connection (8-16 ohms), without necessity for an output transformer. Input imp. 1,000 ohms. Gain 20dB. Output 300mW. Distortion 3% (at 200mW output level). Freq. res. 50Hz-10KHz. Power supply 9v. Current 20mA at no signal, 30mA at max. output. 29/6. P. & P. 2/-.

**E.1317. MINIATURE MORSE TRANSMITTER.** Will transmit to any adjacent AM Receiver, also makes a useful oscillator for trouble shooting. Audio tone 400c/s. Radio frequency range 400c/s to 30Mc/s. Power supply 9v DC. Current 35mA. 25/- P. & P. 2/-.

**E.1312. TAPE PRE-AMPLIFIER.** Incorporating N.A.R.T.B. curve characteristics, this amplifies tape head signals up to 1 volt within the frequency range of 30Hz-15KHz. Input imp. 100Kohm. Gain 25dB. Max. output 3v. Max. input 50mV. Distortion 0.15% (at 1v level). Power supply 9-12 volts. 29/6. P. & P. 2/-.

**E.1316. MORSE CODE OSCILLATOR.** A transistorised morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone freq. 400Hz. Power output 80mV. Power supply 3-9v. Current 45mA. 25/- P. & P. 2/-.

## MINIATURE SOLDERING IRON

British made and designed for use with transistor circuitry but ideal for many other uses. AC 240v. 18 watt. Length 7 3/16 in., 1/2 in. slide on bit. Price 32/6 P. & P. 2/-.

Visit our Brand New enlarged Hi-Fi Demonstration Room, Tape, Record Bar and Scientific Show of Microscopes, Binoculars, Telescopes and Watches at 18/19 Tottenham Court Road

# FANTASTIC XMAS OFFER!

## Lind Air Audio 'COMPACT' Hi-Fi Stereo System

NEVER BEFORE SUCH VALUE!

IT'S OUT OF THIS WORLD



ONLY **39 1/2** LNS

Carr. & Ins. 25/- LIMITED PERIOD ONLY!  
£5. 9. 6 DEPOSIT plus 25/- Carr. & Ins. and 9 monthly payments of £4. 9. 7. Total Credit Sale Price £45. 15. 9.


### BIG SOUND AT LOW COST!

6 watts r.m.s. per channel. Controls: Bass, Treble, Volume, Balance, Function selector. Mono/Stereo switch. Tape record outlet. Inputs for Tape replay/Tuner. Headphone facility. Beautiful teak case with matched loudspeakers. Garrard Autochanger unit fitted Stereo Cartridge. Sizes: Plinth 16 1/2" x 14" x 3 1/2" Speakers 12 1/2" x 6" x 8"

EXCLUSIVE TO LIND-AIR

See and hear the Lind-Air Audio "Compact" now at London's Newest Hi Fi Store - All leading names in stock plus Expert Advice, Hi Fi and T.V. Demonstrations, Part Exchanges, Mail Order and Export Sales.

## COMPACT 2-WAY INTERCOMS

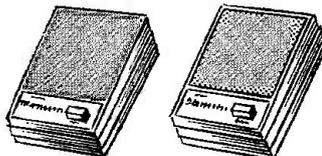

For table of wall mounting. Smart two tone grey cases size 3 1/2 x 1 1/2 x 2 1/2 in. Complete with lead, staples and 9v battery. 55/- P. & P. 3/6.

## HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY			
J1001	3"	Long Play PVC	225ft. 5/6
J1002	3"	Triple Play Poly	600ft. 10/8
J1003	5"	Long Play PVC	900ft. 10/-
J1004	5"	Double Play Poly	1200ft. 15/-
J1005	5 1/2"	Long Play PVC	1200ft. 12/6
J1006	5 1/2"	Double Play Poly	1800ft. 22/8
J1007	7"	Standard Play PVC	1200ft. 12/8
J1008	7"	Long Play PVC	1800ft. 17/8
J1009	7"	Double Play Poly	2400ft. 25/-
J1010	7"	Triple Play Poly	3600ft. 50/-

P. & P. 1/2.  
P. & P. 1/2.  
P. & P. 1/8.  
P. & P. 1/8.  
P. & P. 2/-.  
P. & P. 2/-.  
P. & P. 2/6.  
P. & P. 2/6.  
P. & P. 2/6.  
P. & P. 2/6.



# LIND-AIR OPTRONICS LTD

18, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm

ALL MAIL ORDERS  
To Dept. PW170,  
54a Tottenham  
Court Road,  
London, W1.



... or any day you please (Sundays included)—any time of day or night. Your message will be received loud and clear. Even if we are not there "live" at the other end of the line, our telephone recording machine will take your message for us to deal with as soon as we are back on the job. If your message is a fat order we'll be delighted. If it's just a teeny-weeny order we'll still be delighted.

This "order-by-phone" facility is just one of the many advantages offered by our new **CREDIT ACCOUNT SERVICE**. Here are a few more advantages:

Order forms and prepaid envelopes are provided, so if you want to order by post, you don't even have to find a stamp. To settle your account you need only *one* cheque, postal order or money order per month. Normally on credit accounts there is a minimum invoice charge of 30/-, but *we* stipulate *no* minimum.

Of course, this Credit Account Service is available only if you are already using our catalogue for ordering components, but after you have been in the service for 12 months we regularly send you an up-to-date catalogue FREE of charge.

Like to know more about this trouble-saving, money-saving service? Then drop us a line or give us a ring, 01-648 8422.

You should certainly have an up-to-date copy of the Home Radio Catalogue even if you do not intend to use our Credit Account Service. It's a *must* for every Radio and Electronics enthusiast. It has 350 pages and lists 8,000 components, over 1,500 of them illustrated. Moreover it contains 6 vouchers, each worth 1/- when used as indicated. Give *yourself* a Christmas present this year. Post the coupon with 12/- (8/6 plus 3/6 post and packing) and we'll send your catalogue by return of post.

## A Merry Christmas to all our readers!

Please write your Name and Address in block capitals

Name .....

Address .....

HOME RADIO (COMPONENTS) LTD.,  
Dept. PW. 234-240 London Road, Mitcham, CR4 3HD



# PRACTICAL WIRELESS

VOL 45 NO 9

Issue 755

JANUARY 1970

## TOPIC OF THE MONTH

THE optimists will soon be ringing out 1969 and hopefully heralding what they imagine will be a brighter new year. The pessimists will just groan and say things can't be worse. It's all a matter of viewpoint and temperament, but whatever these are one must first assess the retiring year before speculating on the one to come. We have done this with P.W.

Circulation figures and readers' letters remained at a high level, so we assume that most readers got what they wanted. During 1969 we published 194 articles and features, an average of 16-plus per issue. Of these there were 7 on building amplifiers, 11 on receivers and front ends and 10 on test equipment. This apart from the projects under the Take 20 and IC of the Month banners, and constructional items in other categories.

On the semi-constructional and theoretical front there were series on repairing radio sets, pulse circuits, aerials, magnetic sound recording, semiconductor theory and 12 instalments of P.W. Guide to Components. Other articles ranged a varied field and took in home workshop practice, relays, power supply units, a stereo decoder, printed circuit design, a pedal steel guitar, etc.—and, of course, the regular news and comment features.

If we left anyone out during the year he must surely be a weird misfit! Having modestly patted our own editorial backs it is only just to convey our appreciation for the support from readers in the way of comments, criticisms, suggestions and letters of encouragement. And, of course, for sending along manuscripts for consideration; a high proportion of published material is the work of ordinary readers of P.W. So, to every one of you, from the regular subscribers to those who cadge a copy from a mate at the local club. . . .

## Merry Christmas and a Happy New Year

from

W. N. STEVENS

L. E. Howes, G3AYA

C. Riches

H. Moorshead

T. R. Preece, G3TRP

## NEWS AND COMMENT

Leader	663
News and Comment	664
MW Column by C. Molloy	668
P.W. at the Exhibitions <i>Richard Collins Reports</i>	669
On the Short Waves by Malcolm Connah and David Gibson, G3JDG	688
Practically Wireless by Henry	696
Letters to the Editor	698

## CONSTRUCTIONAL

Microphone Mixer by V. Capel	666
Pedal Steel Guitar, Part 3 by F. C. Judd	677
Panoramic Receiver for 160 to 80 Metres, Part 1 by D. Bollen	684
I.C. of the Month, Power Control Circuits by L. A. J. Ireland	690
Beginner's Portable Receiver by C. R. Bradley	692
Take 20, 3-transistor Radio by Julian Anderson	709


## OTHER FEATURES

Basic Semiconductor Technology, Part 8 by M. F. Docker, M.Sc.	670
Experimenters' Corner, Designing Class A Amplifiers by C. R. Boggis, M.A.P.A.E.	682
P.W. Guide to Components, Part 13 by M. K. Titman, B.Sc.	701

February issue will be published on  
January 9th.


©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Tower House, Southampton Street, London, W.C.2. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.
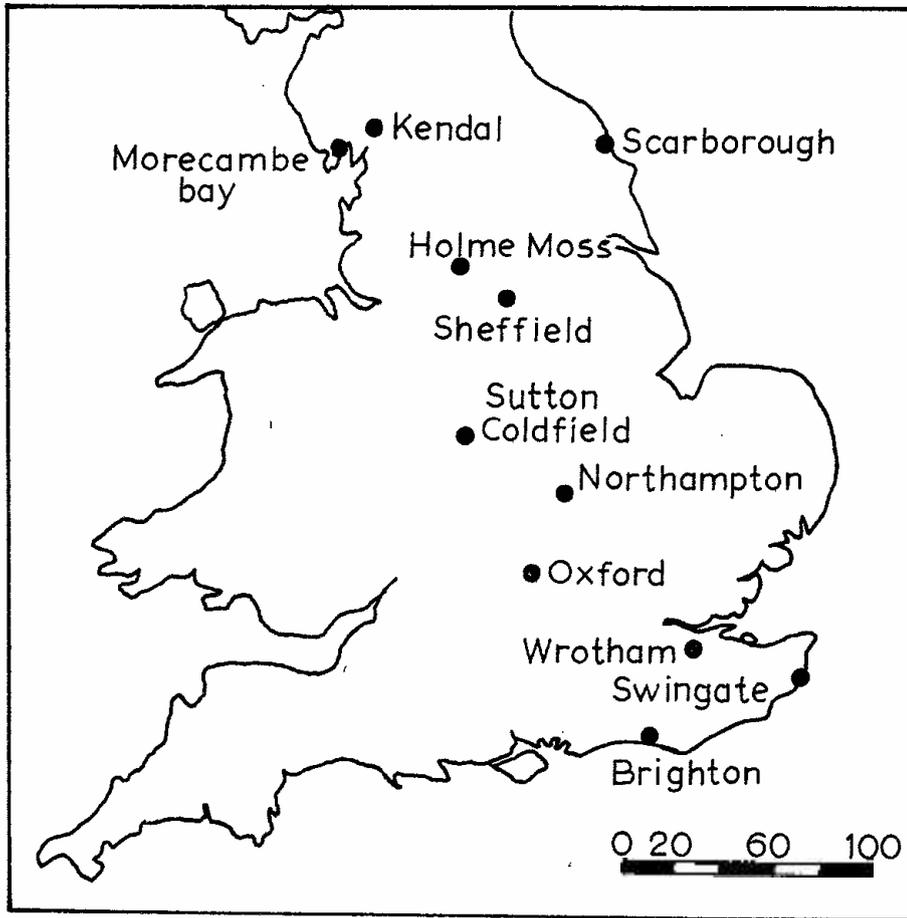
## VHF STEREO RADIO TRANSMITTING STATIONS ON RADIO 3



	Frequency		Maximum ERP
Brighton	92.3MHz	South & West	150W (directional aerial)
Holme Moss	91.5MHz	North	120kW
Kendal	90.9MHz	North	25W (directional aerial)
Morecambe Bay	90.9MHz	North	4kW (directional aerial)
Northampton	91.1MHz	Midland	60W (directional aerial)
Oxford	91.7MHz	Midland	22kW (directional aerial)
Scarborough	92.1MHz	North	25W (directional aerial)
Sheffield	92.1MHz	North	60W
Sutton Coldfield	90.5MHz	Midland	120kW
Swingate	92.4MHz	London	7kW (directional aerial)
Wrotham	91.3MHz	London	120kW

## THE "ENGLEFIELD" CABINET

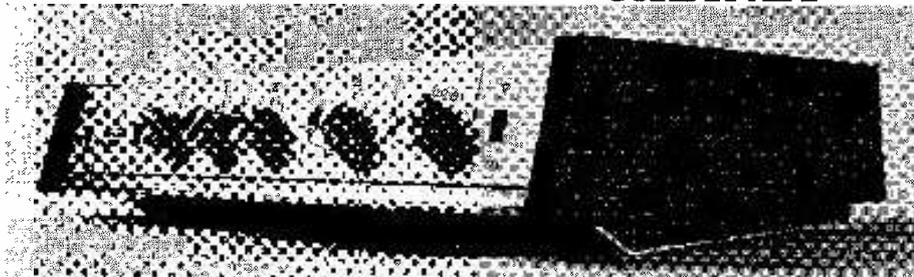

Peak Sound, the CirKit people have announced the "Englefield" cabinet for their amplifier modules. It is in kit form and includes components to complete a stereo amplifier based on the PA.12-15 Power Amp Module, the SCU/400 Stereo Preamp Module and the PS/45K Power Supply Kit. Cost of this kit is £38 4s. for 12W per channel system. Peak Sound, 32 St. Judes Road, Englefield Green, Egham, Surrey.

## SWANSEA COLLEGE SOCIETY

The University College of Swansea Amateur Radio Society is once again fully active with activities such as Morse code and R.A.E. tuition for students. Amateurs and listeners are also welcomed to the meetings and details may be obtained from: Rob Wilcox, Room 520, Neuadd Gilbertson, University College of Swansea, Singleton Park, Swansea, SA2 8PS.

## North Leeds Radio Club

The North Leeds Radio Club has recently been formed. Will anyone wishing to join or visit this club please contact the Secretary, G. Brown, 2 Fearnville Close, Dib Lane, Leeds 8, Yorkshire.

## Desoldering the dry way




Southern Watch & Clock Supplies Ltd. are UK selling agents for "Soder Wick"—a dry wick method of desoldering. As can be seen in the illustration, it is supplied in reel form and is used by direct contact with the joint together with a soldering iron for heating purposes.

Soder Wick draws the solder up into itself quickly and no excessive heat is required and the desoldered joint is left solder-free, pure and non-corrosive. Prices range from 18 to 20s. but for readers who would like to try it out there is a special offer, open until 31st December whereby they can get a sample for 16s. Further particulars may be obtained from: Southern Watch & Clock Supplies Ltd., Industrial Tools Division, 48/56 High Street, Orpington, Kent, BR6 0JH

# NEWS... NEWS... NEWS...

## SCOPE FOR SCHOOLS

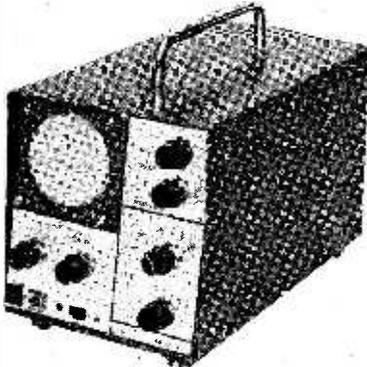

A new oscilloscope, type EA 0699-1 has been announced by Mitre Electronic Products. It is intended mainly for use as a basic class oscilloscope in schools, and features a 2½in. diameter tube with green medium persistence trace and the Y bandwidth is d.c. to 100kHz. There is less than 100mV/cm Y sensitivity at maximum gain with full Y shift and automatically synchronised time-base range is 100mS/cm to 10µS/cm (approx.). X input with full X shift when timebase is off is 1V/cm.

The oscilloscope is housed in an all-metal case measuring 6¼ × 6¼ × 10¼in. Weight is 8 lb., supply voltage, 200-250V 50-60Hz and power consumption 25W. It is fully guaranteed and price is £24 10s. (1 off) with a discount for schools. A data sheet is available. *Mitre Electronic Products, 22 Powis Terrace, London, W11.*

## LOW VOLTAGE AND ISOLATING TRANSFORMERS

Gardners Transformers Ltd., have introduced a range of open-style (Avon series) and enclosed style (Twynham series) Low Voltage and Isolating Transformers for input voltages of 100-125V and 200-250V. This applies for sizes from 24V/A to 1kV/A with a wide variation of output voltages. Further details in brochure GT.17 obtainable from: *Gardners Transformers Limited, Christchurch, Hampshire.*

## Better Things are Electric

A new 16-page illustrated booklet in full colour designed to help people choose the right electrical fitting—plug, switch or socket—for every room in their home, is now available. Called "Better Things are Electric—with MK", it has been produced by MK Electric Ltd. It is available free on request from most electrical retailers or electricity showrooms, or direct from *MK Electric Ltd., Edmonton, London, N9.*

## SPLICER FOR CASSETTE TAPES

Bib Division of Multicore Solders Ltd., announce the introduction of the Bib Model 24 ¼in. cassette tape splicing and editing kit. It comes in a plastic wallet together with a plastic handled razor blade, Tape marker, reel of splicing tape on dispenser and a device for withdrawing tape from the cassette. The price is 29s.

The kit has been specially designed for use in jointing tape from C60, C90 or C120 cassettes and is particularly useful as it enables music from pre-recorded cassettes to be joined so that the playing time of a single cassette is extended.


## It's 5 new pence




Multicore Ltd. announce an adjustment to their well-known 6d. solder pack. It now costs twice the price but you get double the amount of solder (enough for 100 average joints). It has been given the reference "2D" and packages are marked 1s. or 5p. *Multicore Solders Ltd., Hemel Hempstead, Herts.*

## Don't forget the Practical Wireless filmshow

## 100 WATTS FROM ADASTRA

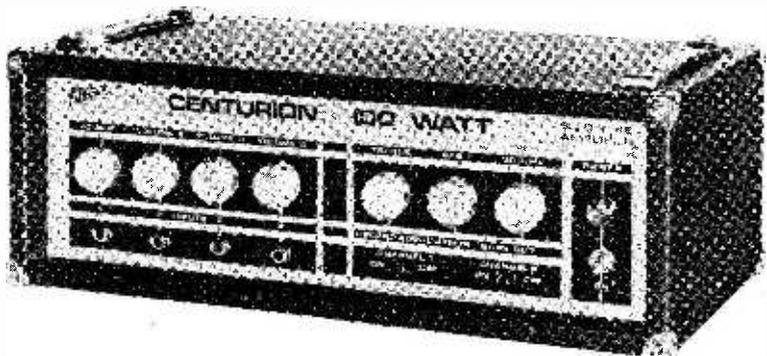

Adastra Electronics Ltd. announce their "Centurion" 100W amplifier which has a suggested list price of £99 and features a hand-assembled 25-transistor 6-diode printed circuit construction. The four individually gain controlled inputs have a sensitivity range from 1mV to 20V. A feature of this amplifier is that its design allows its output (100W at 4Ω; 140W peak) to be open- or short-circuited without ill effect. The amplifier is housed in a black leathercloth cabinet with carrying handles and matching silver/black control panel. *Adastra Electronics Ltd., 167 Finchley Road, London, N.W.3. Tel. 01-624 8164/5.*

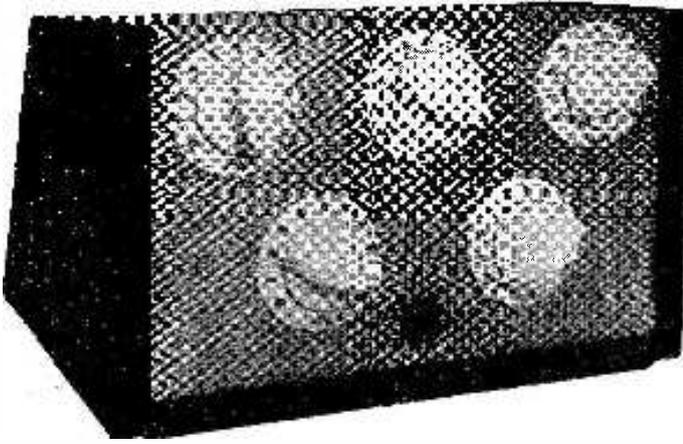

# A MICROPHONE MIXER UNIT

V. CAPEL

ONE of the main requirements for a microphone mixer is that of low noise level. Many of the cheaper commercial mixers fall down on this feature; although passable when used with low-output power amplifiers, noise levels become noticeable and disturbing at higher powers such as with large p.a. amplifiers. It is true that the ratio between the signal and the noise level will be the same irrespective of the power of the amplifier, but there are moments of silence especially with speech reproduction when there is no signal to mask the noise and it is then that high level noise is especially unpleasant.

Inexpensive commercial mixers were found unacceptable on this score whereas the better ones were unacceptable because of price. Hence the unit here described was designed and built. Other features required were a degree of amplification as well as mixing, a self-contained arrangement that could be operated at some distance from the main amplifier, and an input for tape or gram which

could not be overloaded by too high an input signal resulting from use and operation by unskilled hands.

## Circuit

One of the reasons why the cheaper commercial mixers fail to achieve a good signal-to-noise ratio is because the input sockets are connected directly to the gain controls. The output from these is combined and fed to the base circuit of the first stage. An advantage of this arrangement is that only one transistor is needed for all inputs which saves cost. However it also means that the noise generated in it is fed uncontrolled into the following stages. Turning down a control only reduces the input signal thereby decreasing the signal-to-noise ratio.

In the circuit adopted for the mixer, each input has its own transistor which is followed by the gain control. When this control is turned down therefore, the noise from the input transistor decreases as well as the signal. The input stage is always the most significant as respects noise, because it is amplified

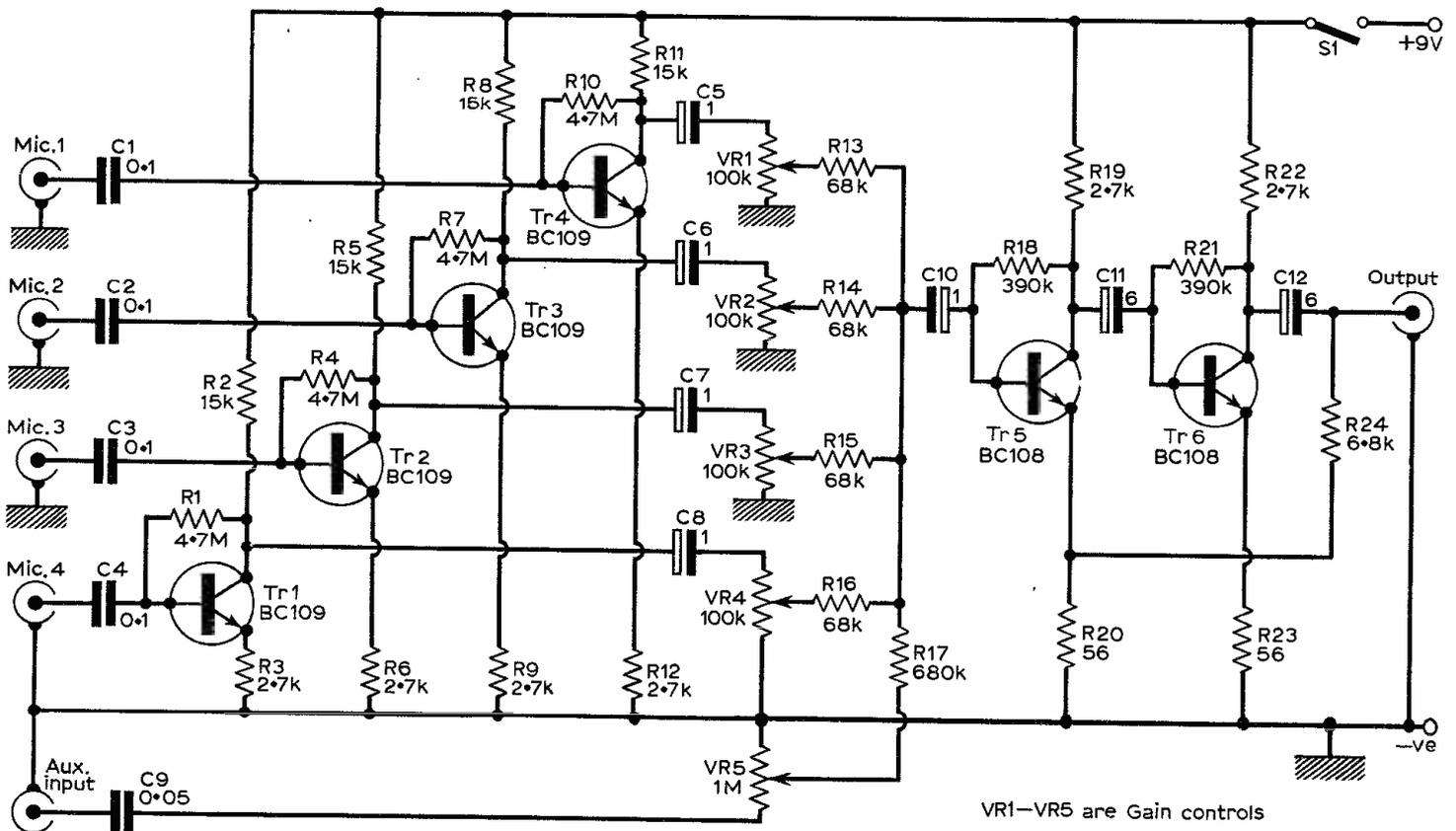


Fig. 1: The circuit of the five channel mixer. Four inputs are provided for microphones with an additional one for high level.

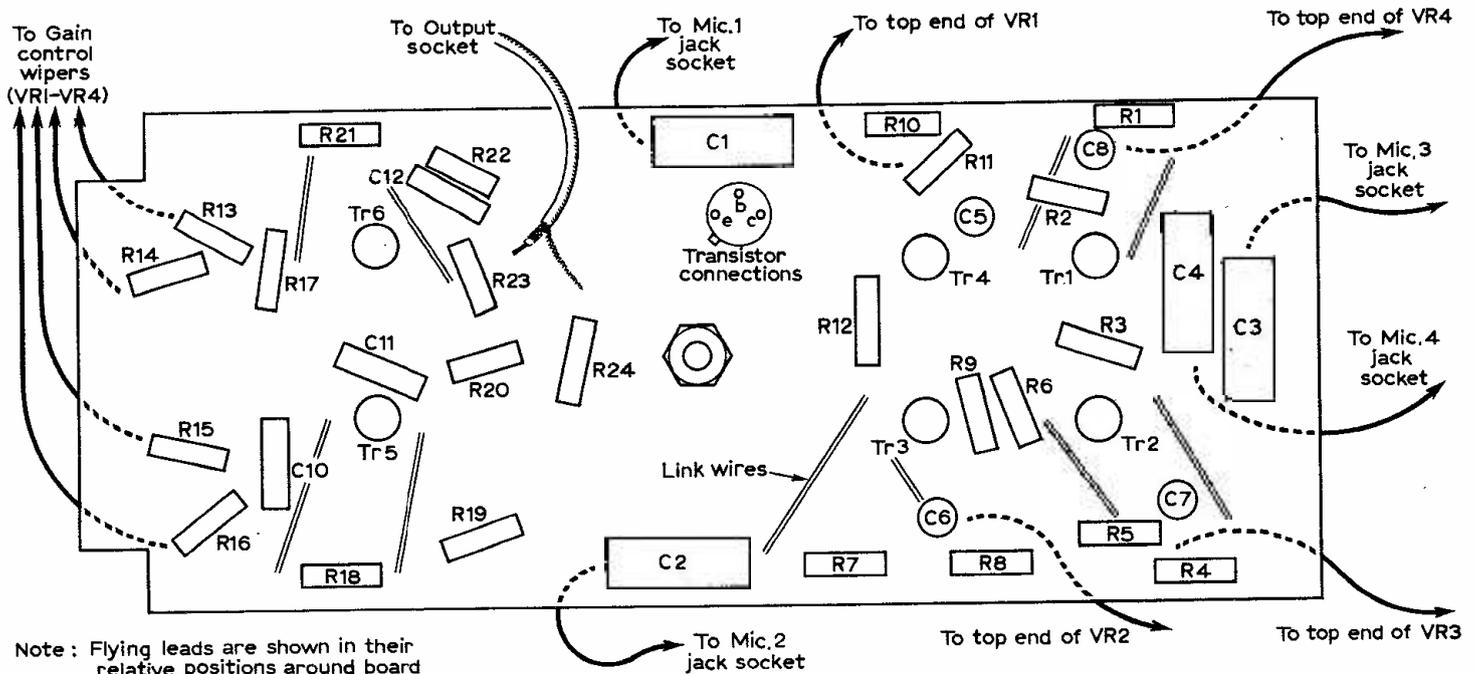


Fig. 2: The components are arranged as shown above on a Radiospares standard printed circuit.

## ★ components list

### Resistors:

R1	4.7M $\Omega$	R13	68k $\Omega$
R2	15k $\Omega$	R14	68k $\Omega$
R3	2.7k $\Omega$	R15	68k $\Omega$
R4	4.7M $\Omega$	R16	68k $\Omega$
R5	15k $\Omega$	R17	680k $\Omega$
R6	2.7k $\Omega$	R18	390k $\Omega$
R7	4.7M $\Omega$	R19	2.7k $\Omega$
R8	15k $\Omega$	R20	56 $\Omega$
R9	2.7k $\Omega$	R21	390k $\Omega$
R10	4.7M $\Omega$	R22	2.7k $\Omega$
R11	15k $\Omega$	R23	56 $\Omega$
R12	2.7k $\Omega$	R24	6.8k $\Omega$

All 10%,  $\frac{1}{8}$  or  $\frac{1}{4}$  watt miniature types.

VR1, VR2, VR3 and VR4 100k $\Omega$  log. potentiometers

VR5 1M $\Omega$  log. pot.

### Capacitors:

C1	0.1 $\mu$ F	C7	1 $\mu$ F 12V
C2	0.1 $\mu$ F	C8	1 $\mu$ F 12V
C3	0.1 $\mu$ F	C9	0.05 $\mu$ F
C4	0.1 $\mu$ F	C10	1 $\mu$ F 12V
C5	1 $\mu$ F 12V	C11	6 $\mu$ F 12V
C6	1 $\mu$ F 12V	C12	6 $\mu$ F 12V

### Semiconductors:

Tr1	BC109	Tr4	BC109
Tr2	BC109	Tr5	BC108
Tr3	BC109	Tr6	BC108

(Plastic encapsulated versions of the BC108 and BC109 are now very common, have identical characteristics and are cheaper. Their numbers are BC168 for the BC108 and BC169 for the BC109.)

### Miscellaneous:

Six jack sockets; pointer knobs; Radiospares printed panel; SW1 toggle on-off switch; battery; battery clips; screened lead etc.

by all the stages that follow, whereas the succeeding stages have less amplification following them.

Obviously, low-noise transistors should be used, so the Mullard silicon planar epitaxial transistors BC109 and BC108 were chosen. These are n-p-n types so battery polarity will be negative to earth. Constructors used to working with the more familiar p-n-p varieties will need to check polarity of the electrolytic capacitors.

Current biasing of the first stages is employed by returning the single high-value base resistor to the collector. A measure of negative feedback results, and further feedback is achieved by leaving the emitter resistor unbypassed. If desired, a greater or lesser number of inputs can be provided as required. Three were really all that were necessary, but an extra one was fitted in case it should be required in the future. It is easier to add one when first constructing, than later! Extra inputs will not add to the noise level providing the controls of those not being used are turned back to zero.

Although all controls are taken to a common input of the next stage each one will have only marginal effect on the settings of the others due to the isolating resistor in series with the wiper of each control.

The auxiliary input is fed into the same point. In this case it is best to feed the input directly to its gain control, because if applied first to an amplifying stage as is the case with the microphone inputs, this stage could be overloaded by a high level signal such as the output of a tape recorder. Here, the control will reduce the signal to an acceptable level. Impedance of this input is kept as high as possible so that crystal or ceramic pick-ups can be used, hence the higher value of the control and isolating resistor.

At first, direct coupling was considered between the second and third stages as this would avoid reactance in the coupling and provide d.c. stabilisation by a d.c. feedback loop. However, as the second stage must be "above" the first as regards d.c. voltage in directly coupled stages, this in effect halves the battery voltage to each. Where a line voltage

of around 20 volts is available as is common with most mains-powered transistor equipment, this is quite satisfactory, but things are different when the supply is only 9 volts and reducing as the battery voltage falls. Silicon transistors are less prone to thermal and other vagaries of germanium transistors, so it was deemed best to dispense with the d.c. stabilisation.

To further reduce noise levels, a negative feedback loop was included right from the output socket back to the emitter of the second stage.

## Construction

With any construction, one of the first things to consider is the case, as this will determine the way the components are assembled. The case chosen for the prototype started life as a Channel TV tuner unit. There are probably many of these around in dealers' junk rooms, but if one cannot be obtained, a similar construction can easily be made.

A Radiospares transistor printed panel was used for the building of the circuit. These are not obtainable direct from the firm as they deal only with the trade, but almost any dealer could get one within a few days even if he did not have one in stock. There are positions for eight transistors on these boards, and the base, emitter and collector connections are all marked. A centre strip of print running down the middle of the board can be used for earth, and two conductors on either side, for the battery positive rail. Along both edges of the board are triangular multiple connections.

The most straightforward way of wiring is to connect a wire link from the transistor print connection to the nearest multiple, and then wire the associated components from there. It may be necessary to link two adjacent multiples where several connections are needed to the one point. Flying leads were fitted so that connections could be made to the controls and jack sockets.

## Performance

The gain of the microphone channels is 35dB, which enables the mixer to be used with power amplifiers having low input sensitivity. High impedance microphones should be used, either crystals or moving-coil and ribbon instruments with built-in transformers. Medium impedance microphones of 600 or 200 ohms will work satisfactorily, there being sufficient gain for these, although the signal-to-noise ratio is decreased. When used with high impedance instruments, the noise level, even with a large p.a. in a hall, is unobtrusive at normal levels.

The gain of the auxiliary input is unity, there being no amplification required here, only the facility of mixing. A fairly high input impedance is presented so that crystal or ceramic pick-ups can be used with no loss of bass.

Overall frequency response is flat between 20Hz and 10kHz, and there is a gradual drop at the upper end to -3dB at 25kHz. Battery consumption is about 6mA so a PP6 battery should give long service.

When using this or any other mixer, always keep the controls that are not in use to the minimum position. Those that are being used should be set at an advanced level and the control on the power amplifier kept to a low position, as this will give a better signal-to-noise ratio than the reverse. ■

# THE MW COLUMN

**S**OUTH AMERICAN medium wave stations are often audible after midnight during the winter. Propagation is good over the long sea path from UK enabling the DXer to hear stations quite considerable distances away. Even when conditions are poor the Argentinian stations LR3 (950) *Radio Belgrano* and LR1 (1070) *Radio el Mundo*, can often be heard, sometimes they are the only DX on the band. South Americans are usually at their best when the North American path is poor. Brazilians most frequently logged are PRA3 (860) with the slogan *Radio Mundial*, PRF4 (940) *Radio Jornal*, PRE8 (980) *Radio Nacional*, PRE3 (1180) *Radio Globo*; all are situated in Rio de Janeiro. Brazilian stations are easy to recognise as the language is Portuguese instead of the more usual Spanish from that continent. A number of Venezuelan stations can be heard, the more prominent being YVRS (1020) *Radio Margarita* and YVQJ (1080) in Barcelona. Further to the west are the Colombian stations HJDK (750) *La Voz de Antioquia* and HJBI (840) *Ondas del Caribe* in Santa Marta. The Surinam station PZX7 (725) in Paramaribo is frequently a strong signal though interference from the German station on 728 can be troublesome. PZX7 identifies itself as "SRS" which are the initials of the Dutch organisation which owns the station. Announcements are in Dutch, English and Hindi and the station will QSL. More difficult South American countries are Peru with OAX4A (854) *Radio Nacional* and OAX4U (1010) *Radio America*, both stations in Lima; Uruguay with CX16 (850) *Radio Carve* in Montevideo; Chile with CB106 (1060) *Radio Minería* and CB118 (1180) *Radio Portales*, both in Santiago.

During the late evening while waiting for the DX paths to open, readers may care to try some semi-DX from Europe. The *Portuguese National Radio* operates a number of high power MW transmitters and two of these—on 755 and 1161—have programmes in English at 2245 hrs GMT. Commercial stations to look for include *Radio Coub Portugues* with CSB9 (782) in Miramar and CSB2 (1034) in Lisbon; *Radio Renascena* CSB3 (1286) in Lisbon; *Emissora Norte Reunidas* CSB5 (1578) Oporto; *Emissora Associados de Lisboa* CSB4 (1594) Lisbon. The commercial stations run on well into the night and all will QSL. *Sud Radio* in nearby Andorra on 818 has been heard recently with programmes in English at 2130 hrs and this station too will QSL. Three stations from the far north of Europe that often appear in the late evening are Murmansk (656) in Arctic USSR; Godhavn (650) in Greenland and Hofn (665) in Iceland.

Ramadan ends on 11th December, so have a look for some of the rare Middle East countries mentioned last month while there is still time. Saudi Arabia has been heard on 705 recently at 2100 hrs GMT with a programme in English. The new *All India Radio* megawatt station in Calcutta is reported to be on 1130kHz though it has not been heard yet by the writer.

CHARLES MOLLOY

# P.W. at the EXHIBITIONS

## RICHARD COLLINS reports...

This year PRACTICAL WIRELESS was represented at two exhibitions. The first one was the 1969 International Radio Engineering and Communications Exhibition (the RSGB Exhibition) held at the Royal Horticultural New Hall, Westminster, S.W.1 from 1st to 4th October.

The second exhibition was the 1969 International Audio Fair held at Olympia from 17th to 23rd October. Below are photographs taken during the two exhibitions.



The opening address was made by Mr. R. J. Halsey, C.M.G., F.C.G.I., D.I.C., B.Sc.(Eng.), F.I.L., Director of Cable & Wireless Ltd. He is seen here welcoming visitors to the Exhibition.



Mr. J. W. Swinnerton, T.D., B.Sc.(Econ.), G2YS, President of the Radio Society of Great Britain presents the Exhibition Organisers' Plaque to George Jessop, G6JP, for his 2m Transistorised Transmitter/Receiver.



A group of enthusiasts gathered round the PRACTICAL WIRELESS stand, while staff member, Trevor Preece, G3TRP, explained the workings of the P.W. Pedal Steel Guitar.




The Exhibition transmitting stations which were operating on all Amateur Bands between 1.8 and 144MHz. The equipment was provided and manned by the Crawley group of the RSGB.



Diana and Audrey looking after the magazine sales section of the P.W. and P.E. stand at the Audio Fair.

# BASIC SEMICONDUCTOR TECHNOLOGY

## PART EIGHT

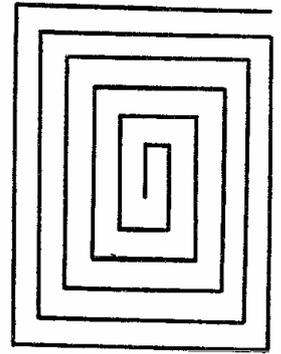

by M.F. DOCKER, M.Sc.

**I**N this article several new devices will be discussed and the final two articles in the series will deal with the techniques of producing integrated circuits, both monolithic and hybrid thick and thin film types.

### Thyristors

The first device, the thyristor, could well have been described in the section dealing with diodes as it is often found in two lead form. However its construction is radically different from that of a diode and the same device can be easily converted during manufacture to form a triode or tetrode thyristor. The thyristor can be defined as a four layer p-n-p-n device as seen in Fig. 1(a) and relies on regeneration in the structure to produce a switching action.

With the polarities shown in this Fig. 1(a) junctions A and C are both forward biased whilst junction B is reverse biased. Consequently only a very small current, the saturation current of the material, will be able to flow across junction B. However, when the potential difference between the input terminals is increased sufficiently it is found that the current through the device suddenly increases as shown in the voltage-current curve of Fig. 2. This behaviour can be explained by considering the device as composed of a pair of complementary transistors, Tr1 and Tr2, in Fig. 1(c). From Fig. 1 (b) Tr1 is seen to be a p-n-p transistor and Tr2 a complementary n-p-n transistor. If the alphas of the two transistors are  $\alpha_1$  and  $\alpha_2$  respectively and if the saturation collector current of each device is  $I_{sat1}$  and  $I_{sat2}$  respectively then it is readily seen that:

$$I_1 = \alpha_2 I + I_{sat2}$$

and  $I_2 = \alpha_1 I_1 + I_{sat1}$  also, since the current across junction B must be equal to I:

$$I = I_1 + I_2$$

$$\text{or } I = \alpha_1 I_1 + \alpha_2 I + I_{sat}$$

$$\text{where } I_{sat} = I_{sat1} + I_{sat2}.$$

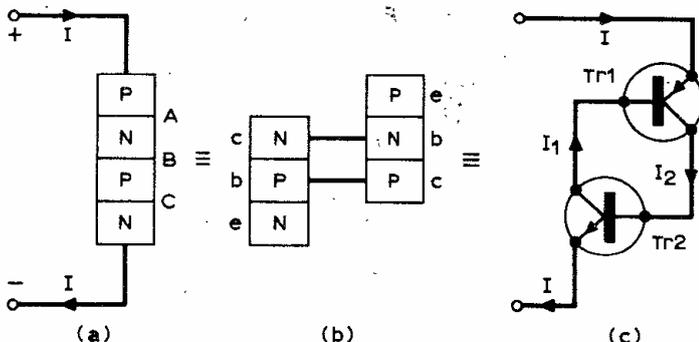


Fig. 1: Basic thyristor representation (a) together with two derived equivalents (b) and (c).

This equation can be reduced to the form:

$$I = I_{sat} / (1 - (\alpha_1 + \alpha_2))$$

and this relates the current through the thyristor to the leakage current and the current gains of the equivalent transistors. Now in a previous article it was shown that the alpha of a transistor depends on the amount of recombination which occurs in the base region, so that for a high alpha the base has to be narrow.\* But the thyristor is intended for high voltage applications, so to avoid punch through the individual regions all have to be wide. This gives the device a low alpha.

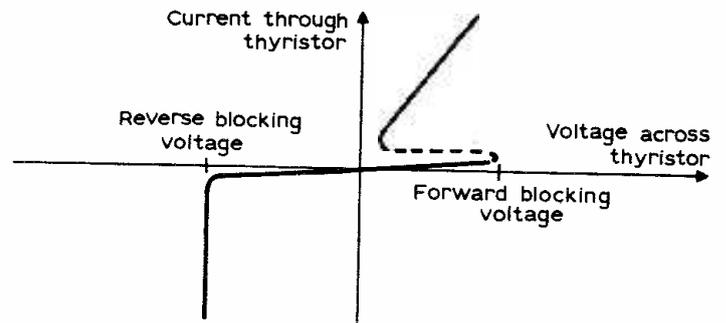


Fig. 2: Characteristic curve of the voltage across a thyristor and the current through it.

Because of this the term  $(1 - (\alpha_1 + \alpha_2))$  above is fairly large and I is not much larger than the leakage current. If in some way recombination can be reduced the alphas will grow and I becomes large. This is done by temporarily filling the impurity centres in the base so that a larger current will flow, carriers then becoming available to diffuse across to the collector junction B, normal transistor action then taking place. After this regenerative feedback holds the device on until the voltage across the terminals is reduced to zero.

There are various ways of filling the trapping centres and one of these, used in this diode form, is to increase the voltage across the device until the leakage current across junction B goes into an avalanche condition. This results in a large current flowing across the junction into the two base regions. The carriers constituting this current fill the impurity centres and enable the transistor alphas to become larger, this in turn resulting in an increase in the current through the device so that the thyristor is then turned on. When this happens all the junctions are in effect forward biased and the voltage across the thyristor falls to a fraction of a volt. The voltage at which the avalanche starts to take place is called the forward breakover voltage  $V_{bo}$  and is quoted in manufacturers' literature.


When a reverse voltage is applied to the thyristor junctions A and C are reverse biased and junction B is forward biased. However the previously described

# Merry Christmas from Antex



A choice of Practical Christmas gifts for amateur or professional

### Complete precision soldering kit

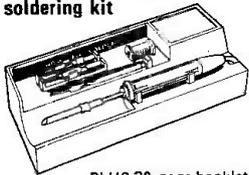

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits. 3/32", 1/8", 3/16"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**

Attractively gift wrapped.




Model CN 240/2  
15 watts - 240 volts


Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

Attractively gift wrapped.

**31/.**

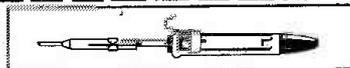

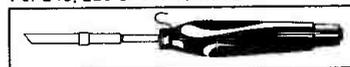
G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 35/-



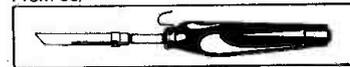ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From 35/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6 Spare bits and elements for all models and voltages immediately available from stock.



### PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

PW1

# BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT PLACE, LONDON, N.W.1

Telephone 01-722-9090

EXPRESS POSTAL SERVICE. SAME DAY DESPATCH BY FIRST CLASS MAIL.  
All goods are offered subject to the standard three month guarantee.

OA2 5/9	6F1 8/9	12AV6 5/8	150C2 5/9	EA42 8/9	EL91 2/8	PCF82 8/8	UCC84 8/-	X41 10/-	B1181 10/-	OA47 2/-
OB2 6/-	6F6G 4/-	12AV7 3/-	301 20/-	EB34 7/8	EL95 5/8	PCF84 8/-	UCC85 6/9	X61 5/9	B1182 9/-	OA70 3/-
OZ4 4/6	6F6M 12/6	12AX7 4/6	302 16/8	EB41 4/6	EM71 14/-	PCF86 9/-	UCF80 8/8	X63 5/9	B1183 2/8	OA73 3/-
LA9 4/6	6F12 3/8	12AX7 9/9	303 15/-	EB91 2/8	EM80 7/-	PCF80013/-	UCF91 9/-	X64 12/6	B1184 2/8	OA79 1/9
LA5 5/-	6F13 3/8	12BA6 6/-	305 16/8	EB41 9/8	EM81 7/8	PCF801 7/-	UCF81 13/-	X65 5/9	B1185 2/8	OA81 1/9
LA7GT 7/3	6F15 10/-	12BB6 5/9	306 13/-	EB81 9/8	EM84 6/8	PCF802 9/-	UCF82 6/8	X66 7/6	B1186 2/8	OA85 1/8
IC1 5/6	6F18 7/8	12BB7 5/9	307 11/9	EB90 4/8	EM85 11/-	PCF805 11/8	UCF83 7/-	X101 30/6	BCY10 5/-	OA86 4/8
IC2 6/6	6F22 12/9	12B7 4/-	308 9/8	EB91 5/8	EM87 7/8	PCF806 11/8	UCF84 10/-	X102 26/-	BCY12 5/-	OA90 2/8
IC3 7/-	6F24 11/9	12J5GT 2/6	1821 10/6	EBF80 9/-	EY71 7/-	PCF808 12/8	UF41 10/-	X119 6/9	BCY33 5/-	OA91 1/9
IC5 4/9	6F25 12/9	12J7GT 6/8	6763 10/6	EBF83 8/-	EY81 7/-	PCF81 7/-	UF42 9/-	X179 5/9	BCY34 5/-	OA182 2/9
ID6 6/9	6F28 10/8	12K5 10/-	6060 5/6	EBF89 6/8	EY83 8/8	PCF82 9/-	UF80 6/9	Z63 4/9	BCY35 5/-	OA200 1/-
ID6 9/6	6F32 3/8	12K7GT 5/9	7193 10/6	EEL21 11/-	EY84 7/8	PCF84 7/8	UF85 6/9	Z67 3/8	BCY39 4/8	OA202 2/9
IFD1 6/8	6G6G 2/6	12Q7GT 4/6	7476 4/-	EC33 12/8	EY86 6/8	PCF85 9/-	UF86 9/-	Z152 4/6	BCZ11 3/8	OA210 9/8
IFD9 4/3	6H6GT 3/8	12SA7GT/9/8	A1334 20/-	EC34 6/8	EY87 6/8	PCF86 8/8	UF89 9/9	Z339 10/-	BCZ12 3/8	OA211 18/8
IG6 6/6	6H6 8/8	12SB7 4/-	A3134 10/8	EC70 4/8	EY88 7/8	PCF86 11/8	UL10 10/6	Z719 4/8	BCZ18 5/-	OA2200 12/-
IH6GT 7/-	6J5GT 4/6	12SG7 3/-	A3042 15/-	EC86 12/8	EY91 3/8	PCL80015/-	UL46 12/6	Z739 6/8	BCZ19 5/-	OA2201 10/8
IL4 2/6	6J6 8/8	12SH7 3/-	AC2PEN	EC88 12/8	EZ36 5/8	PCL80115/-	UL84 6/6	Z749 13/8	BCZ19 5/-	OA2202 9/8
ILD5 5/-	6J7G 7/8	12SH7 4/6	AC2PEN	EC92 6/8	EZ40 7/8	PEN45 7/-	UM80 6/8	Z759 45/-	BCZ19 5/-	OA2203 9/8
ILN5 8/-	6J7GT 6/8	12SK7 4/9	AC2PEN	ECC31 15/8	EZ41 8/8	PEN45DD	UR1C 10/6	Transistors and diodes	BD119 9/-	OA2304 9/8
IN5GT 7/9	6K7G 9/-	12SQGT/6/8	AC2PEN	ECC32 4/6	EZ81 4/9	PEN46 4/-	UU5 7/-	IN1124 10/6	BFY50 10/-	OA2305 9/8
IP1 7/-	6K7GT 4/6	13D1 19/8	AC2PEN	ECC33 30/11	EZ81 4/9	PEN46 4/-	UU5 7/-	2G225 10/6	BFY61 4/-	OA2307 10/8
IP10 5/9	6K8GT 7/8	13D3 9/8	AC2PEN	ECC34 25/8	EZ90 4/8	PEN45SDD	UU9 7/8	2M404 6/8	BFY62 4/-	OA2310 9/8
IP11 5/9	6L1 19/6	14H7 9/8	AC2PEN	ECC40 9/8	FC4 12/8	PEN45 19/6	UY12 4/9	2N968 10/6	BFY62 4/-	OA2311 9/8
IR5 5/6	6L6GT 7/9	1487 15/-	AC2PEN	ECC41 3/8	FW4/500 6/8	PEN44 19/6	UY19 9/6	2N968 10/6	BFY62 4/-	OA2313 7/-
IR4 4/9	6L7 12/6	18 18/8	AC/TH110/-	ECC42 4/8	FW4/500 6/8	PEN44 19/6	UY21 9/6	2N1756 10/6	BFY62 4/-	OA2314 16/8
IR5 4/3	6L18 6/-	19A95 6/-	AC/TH110/-	ECC43 4/8	GZ30 7/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
IR4 2/9	6L19 12/6	19C39 40/8	AC/TH110/-	ECC44 9/8	GZ30 7/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
IR4 5/9	6L20 8/6	20D1 13/6	AC/TH110/-	ECC45 9/8	GZ32 9/8	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
IR5 6/9	6N7GT 6/8	20D4 20/6	AC/TH110/-	ECC46 7/8	GZ33 12/6	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
2A7 12/6	6P1 12/-	20F2 14/-	AC/TH110/-	ECC47 9/8	GZ34 10/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
2D13C 7/-	6P25 12/6	20L1 13/-	AC/TH110/-	ECC48 9/8	GZ37 14/6	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
2D21 5/6	6P26 12/6	20P1 17/8	AC/TH110/-	ECC49 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
2X3 4/9	6P28 25/8	20P2 17/8	AC/TH110/-	ECC50 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3A4 3/8	6G7G 8/8	20P4 18/6	AC/TH110/-	ECC51 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3A5 10/-	6Q7GT 8/6	20P5 15/6	AC/TH110/-	ECC52 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3B7 5/-	6R7G 7/8	25L6GT 8/8	AC/TH110/-	ECC53 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3D6 3/9	6I7 11/-	25Y6 8/8	AC/TH110/-	ECC54 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3D4 6/6	6A7GT 7/8	25Y6G 8/8	AC/TH110/-	ECC55 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3G5GT 6/6	6S4 7/8	25Z4G 6/-	AC/TH110/-	ECC56 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
384 5/9	6S4GT 6/8	25Z4G 6/-	AC/TH110/-	ECC57 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
3V4 8/9	6S7GT 6/8	25Z4G 6/-	AC/TH110/-	ECC58 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
4D1 3/9	6S7 6/8	30C1 6/6	AC/TH110/-	ECC59 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
5R4GY 8/9	6S7GT 6/8	30C15 13/-	AC/TH110/-	ECC60 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
5U4G 4/9	6S7GT 6/8	30C17 11/6	AC/TH110/-	ECC61 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
5V4G 7/6	6S7GT 6/8	30C18 11/6	AC/TH110/-	ECC62 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
5Y3GT 5/6	6S7GT 6/8	30C17 11/6	AC/TH110/-	ECC63 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
5Z3 5/6	6S8 8/8	30C17 11/6	AC/TH110/-	ECC64 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
5Z4G 7/-	6U4GT 12/-	30FL12 15/-	AC/TH110/-	ECC65 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6/30L2 12/6	6U7G 7/8	30FL13 8/-	AC/TH110/-	ECC66 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6A8G 5/6	6V6G 3/6	30FL14 12/6	AC/TH110/-	ECC67 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6A7 3/6	6V6GT 6/8	30L1 6/8	AC/TH110/-	ECC68 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AG5 8/6	6X4 4/8	30L15 15/8	AC/TH110/-	ECC69 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AJ5 9/6	6X5GT 6/8	30L17 15/8	AC/TH110/-	ECC70 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AK5 5/6	6X6G 8/8	30P4 12/-	AC/TH110/-	ECC71 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AK6 6/6	6X7G 12/6	30P4MR	AC/TH110/-	ECC72 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AK8 6/6	7A7 12/6	30P12 13/8	AC/TH110/-	ECC73 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AL5 2/8	7AN7 6/8	30P19 12/8	AC/TH110/-	ECC74 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AM5 2/6	7B6 10/9	30P19 12/8	AC/TH110/-	ECC75 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AM6 3/8	7B7 10/9	30P19 12/8	AC/TH110/-	ECC76 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AN5 5/6	7C6 6/8	30P15 15/8	AC/TH110/-	ECC77 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AB5 20/-	7D6 15/-	30P14 15/-	AC/TH110/-	ECC78 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AT4 4/6	7F8 12/6	30P15 15/8	AC/TH110/-	ECC79 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AU6 5/6	7H7 12/6	35A3 9/-	AC/TH110/-	ECC80 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6AV9 5/6	7H7 12/6	35B5 12/6	AC/TH110/-	ECC81 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6B8G 2/6	7T7 7/8	35D5 12/6	AC/TH110/-	ECC82 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BA6 4/6	7X4 6/6	35L6GT 8/8	AC/TH110/-	ECC83 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BR6 6/9	7Z4 4/6	35W4 4/6	AC/TH110/-	ECC84 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BO6G 20/6	9B7W6 7/8	35Z9 10/8	AC/TH110/-	ECC85 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BR6 7/6	9D 9/8	35Z4GT 4/8	AC/TH110/-	ECC86 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6B76 8/6	10C1 12/6	35Z6GT 4/8	AC/TH110/-	ECC87 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BQ5 4/9	10C2 10/-	42 5/-	AC/TH110/-	ECC88 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BQ7A 7/9	10D1 8/8	43 10/-	AC/TH110/-	ECC89 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BR7 8/6	10D2 14/7	50B5 6/8	AC/TH110/-	ECC90 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BR8 8/6	10F1 15/6	50C5 6/8	AC/TH110/-	ECC91 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BR7 18/6	10F9 9/8	50L6G45/2	AC/TH110/-	ECC92 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BVG 12/9	10F8 9/8	50L6GT 9/8	AC/TH110/-	ECC93 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BWT 11/-	10LD3 8/8	52KU 14/8	AC/TH110/-	ECC94 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-
6BX6 4/6	10LD11 10/-	53KU 14/8	AC/TH110/-	ECC95 12/8	HE0 5/-	UY41 7/8	UY41 7/8	2N2147 17/-	BFY63 4/8	OC19 25/-

action does not occur in this case as the circuit is non-regenerative being in fact simply two diodes in series. The result is that when the reverse voltage does become sufficient to cause avalanching to take place the voltage across the device is maintained and a high power dissipation takes place in the thyristor. The variation of current with voltage across a thyristor is shown in Fig. 2. In most devices the peak reverse capability is made somewhat greater than the forward breakover voltage so that the device can be used as triggerable switch.

The rate of change of voltage across the thyristor can also be used to produce switching. This relies on the injection of charge into the depletion layer as its width changes. In this way it is possible to switch the thyristor by putting a pulse on to the terminals, of amplitude less than the breakover voltage.

### Silicon controlled rectifier

A third method of triggering involves the injection of a pulse of current directly into one of the base regions. This produces an increase in the alpha of the equivalent transistor and the regenerative feedback of the circuit causes the current through the thyristor to rise quickly. Devices using this method are called silicon controlled rectifiers (s.c.r.s.). The size of the pulse required to trigger the thyristor depends on which of the two bases the pulse is injected into. The lower p-type base is the more sensitive and devices in which this base is connected as trigger are called conventional s.c.r.s. Connection to the upper n-type layer of Fig. 1(a) results in a so-called complementary s.c.r.

### Silicon controlled switch and light activated s.c.r.

The silicon controlled switch is a thyristor with connections to both the base regions so that in consequence it is a four terminal device. Current pulses can be injected into either one or both of the bases to produce switching. Another method commonly used to trigger the thyristor is the use of light induced carriers in the base regions. This is used in the light activated silicon controlled rectifier (l.a.s.c.r.) and in the phototran. These are used in many optoelectrical control systems.

### Switch off

A point to be noticed in the operation of the thyristor is that once it is switched on it cannot easily be switched off until the voltage across its terminals has been reduced to a very low value. Even then sufficient time has to be given for the charge carriers which are stored in the base region during the forward conducting state of the thyristor. This time is typically several microseconds: if the voltage is reapplied before expiration of this time the thyristor will switch on again immediately.

### Types and uses

The construction of a typical alloy-diffused thyristor is shown in Fig. 3(a). The p-type regions are produced by diffusion of acceptor atoms from the gaseous state and the cathode region is produced by alloying suitable impurities into one surface. Leads are then attached as shown. Planar thyristors are also produced as shown in Fig. 3(b), usually several

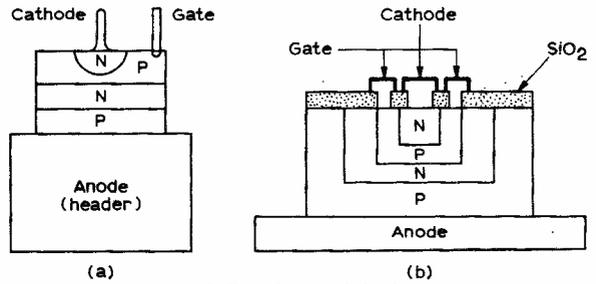


Fig. 3: Two forms of thyristor.

devices being made on one wafer which is then cut up into dices to give the individual thyristors.

The thyristor is often used to control a.c. supplies. However in this application they have the disadvantage that they only switch into their forward conducting state in one direction. In order to permit full wave control of power supplies it is possible either to use two thyristors or to use a device called a triac. This is a multiple layer device which is equivalent to two s.c.r.s so arranged that they switch on alterna-

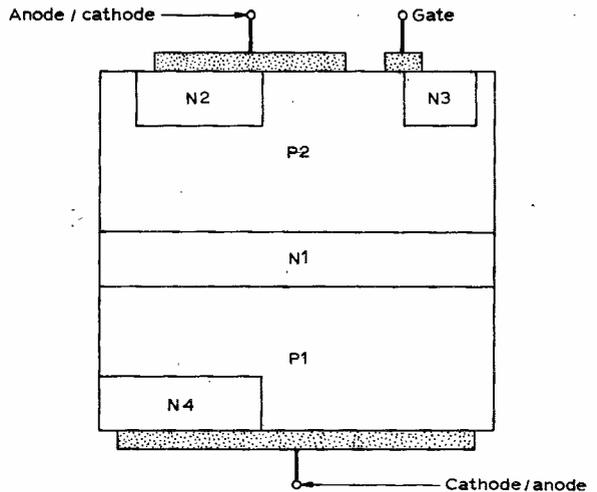


Fig. 4: Triac thyristor construction.

tive half-cycles of the mains. The structure of this device is shown in Fig. 4 and its voltage against current characteristic is given in Fig. 5.

A small s.c.r. with an avalanche diode between the anode and gate electrodes is also available. This can be used as a low current switch and is given the name silicon unilateral switch, or s.u.s. A bilateral version of this device is also available and is used to trigger high power triacs as it provides the alter-

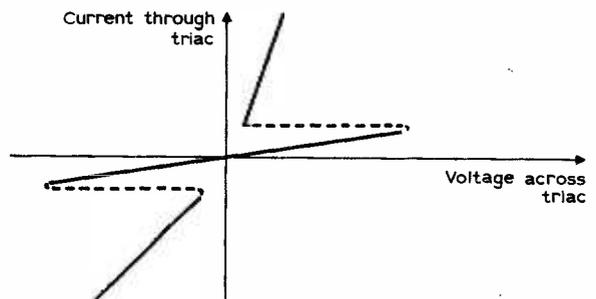


Fig. 5: Characteristic curve showing the variation in current flowing through a triac as the voltage across it is changed.

nately positive and negative pulses required for biphasic operation of the triac.

There are numerous other thyristors available including the diac which is similar to the s.b.s. and is also used to switch the triac. The quadrac, which is a three terminal device containing both a diac and triac and can be used in phase control of biphasic power supplies, is another thyristor which has only recently become available.

### Unijunction transistor

Another device exhibiting a negative resistance effect is the unijunction transistor. This is similar in construction to the f.e.t. but its gate electrode is called the emitter and is much smaller than that of the f.e.t. It is normally operated in forward bias and the structure of a typical bar type u.j.t. is shown in Fig. 6 together with its circuit representation. It con-

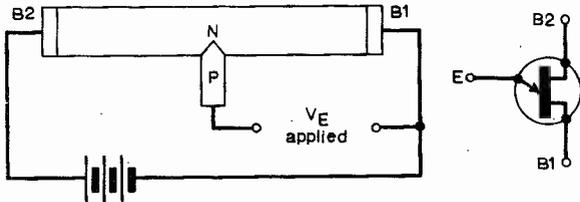


Fig. 6: Unijunction transistor construction and circuit symbol.

sists of a silicon bar with two ohmic connections made to each end, called the base terminals, and an aluminium emitter which is alloyed to the base to form a p-n junction. If a current is made to flow through the base the potential at the emitter will be  $V_e$ . As long as the voltage applied to the emitter is less than this the junction will be reverse biased and no current will flow. However if the applied voltage is increased beyond  $V_e$  the junction will go into a forward conducting state and holes will be injected into the base region. In order to maintain neutrality electrons will be released in the base region between the emitter and base one, which results in the resistance of the region falling. This then causes the potential drop across the bar in this region to fall with a consequent increase in the forward bias applied to the junction and the number of injected holes rises yet again. Obviously this is a regenerative effect and causes the emitter current to rise sharply.

A curve showing the variation of emitter voltage as the emitter current changes is shown in Fig. 7, where the curves for different voltages between bases are indicated. The most significant point of this is that when the emitter voltage reaches  $V_e$  the

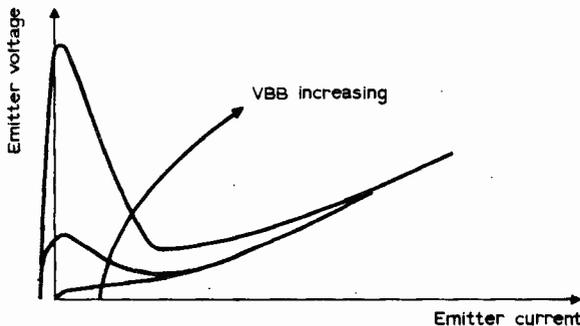


Fig. 7: Variation of emitter voltage with current as the base-to-base voltage in a unijunction transistor is changed.

emitter current suddenly increases and whilst this is happening the voltage across the emitter falls. This is the opposite behaviour to that shown by a resistor and is consequently called a negative resistance effect. This enables the unijunction transistor to be used in many oscillators, staircase waveform generators and dividers and circuits where a negative resistance effect is required.

### Spacistor

Two other devices which are occasionally met but which do not yet seem to have reached the world of the amateur are the spacistor and the tetrode transistor. A brief explanation of these devices is worthwhile.

The spacistor is a single junction amplifier. Basically it is a p-n junction with a large reverse bias so that it has a wide depletion region. Current carriers are injected into this depletion region from a metal contact and are swept across the depletion region by the electric field. Because of the high field it is possible to have quite short transit times and thus to have a high cut off frequency. Another

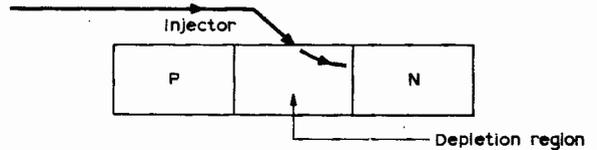


Fig. 8: Basic spacistor construction.

type of spacistor employs a fourth electrode called a modulator which affects the gain of the device. It also increases the input and output impedances of the spacistor by increasing the isolation of the injector from the output current. A diagram of the simple spacistor is shown in Fig. 8.

### Tetrode transistor

The tetrode transistor is similar to the ordinary transistor except that it has two base contacts. Because of this it is possible to produce a field across the base so that effectively only a small portion of the emitter-base contact is forward biased. This reduces the active width of the base so that its resistance is reduced and also the transition capacitance is reduced. These assets make the tetrode especially useful in high frequency applications including high speed switching circuits. Figure 9

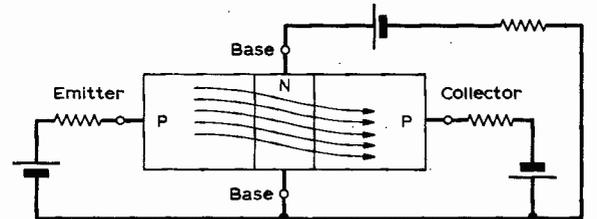


Fig. 9: Construction of a tetrode transistor and its circuit connections.

shows the schematic cross-section of a tetrode transistor including a representation of the current flow pattern. The reduction in the base width is clearly seen from this figure and results in a decreased base resistance because of the lessened distance the base current has to travel before recombination.

**TO BE CONTINUED**

# This book will send you mad with desire!



Don't read on unless you're feeling really strong. This book will start you on a mad, crazy spending spree. It's got everything, but everything for the do-it-yourself radio and hi-fi man.

Everything from a vast range of electronic components available to the home electronics constructor, to a complete range of equipment for the radio "ham". What's the book?

The Electronics Constructors Catalogue.

Only the most exciting, mouth-watering items are there. Carefully placed in 6 sections for easy reference. And backed by truly efficient sales service.

So if you order any of the vast selection of goods, you're sure to get it pretty soon.

All you have to pay for this great big hunk of temptation is 13/- (including packaging and postage).

**So fill in the coupon now. If you dare.**

Enclose PO cheque for 13.- made out to:  
Electroniques (proprietors Standard Telephones  
and Cables Limited), Edinburgh Way, Harlow,  
Essex. Telephone: Harlow 26811.

Name .....

Address .....

PW-1



electroniques

**Fully guaranteed  
Individually packed  
VALVES**

**PERSONAL CALLERS WELCOME**

**Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.**

**MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders  
up to 10/-, 1/-; 10/- to £1, 2/-; over £1, 2/- per £1; over £3 post free. U.O.D. 4/- extra**



**ALL valves  
guaranteed**

CY31	7/6	ECL80	9/-	KT66	26/-
DAF96	7/9	ECL82	12/6	KT88	32/-
DF96	7/9	ECL83	6/8	N78	25/-
DF92	9/-	ECL86	3/6	OAB	2/6
DK96	7/6	EF82	3/6	OAB	2/6
DL92	6/8	EF87A	8/-	PABC80	7/6
DL94	6/8	EF89	6/-	PC97	9/-
DL96	6/8	EF40	10/-	PC90	7/6
DM70	7/6	EF41	12/6	PC84	6/9
DM71	7/6	EF42	14/6	PC202	2/6
DY86	6/8	EF80	6/-	PC189	11/6
DY87	6/8	EF83	9/6	PC82	17/-
DY89	6/8	EF85	6/6	PC80	15/-
EAB30	6/6	EF86	5/8	PC82	6/8
EAF42	10/-	EF89	5/8	PCF84	9/8
EB91	2/-	EF91	3/6	PCF86	10/-
EB93	8/6	EF92	2/6	PCF201	15/6
EB94	10/6	EF96	5/6	PCF201	15/6
EB95	9/6	EF133	6/6	PCF801	9/9
EB96	7/6	EF184	7/6	PCF802	9/9
EBF83	8/6	EF800	21/-	PCF805	14/6
EBF89	6/6	EF812	15/6	PCF806	13/-
EC81	6/6	EF1200	15/6	PCF808	14/6
EC82	5/9	EH90	7/6	PL36	10/9
EC83	6/6	EL34	10/6	PL81	9/3
EC84	6/6	EL42	11/6	PL82	8/3
EC85	5/6	EL42	11/6	PL83	8/6
EC86	9/6	EL84	4/9	PL84	8/6
EC88	7/6	EL85	8/9	PL85	8/6
EC89	7/6	EL86	9/6	PL86	8/6
EC189	9/9	EL95	7/6	PL87	8/6
EC804	12/6	EL800	17/-	PL88	8/6
ECF89	6/8	EL808	17/-	PL89	8/6
ECF82	6/6	EM31	5/6	PL89	8/6
ECF83	12/6	EM30	7/6	PL89	8/6
ECF801	12/6	EM34	7/6	PL89	8/6
ECF802	12/6	EM37	11/6	PL89	8/6
ECF803	12/6	EY31	3/6	PL89	8/6
ECI84	7/6	EY36	7/6	PL89	8/6
ECI85	11/6	EY38	8/6	PL500	14/9
ECI84	13/6	EZ40	3/8	PX4	14/6
ECI81	5/9	EZ41	3/6	PX25	12/6
ECI83	10/9	EZ80	5/6	PY33	12/6
ECI80	12/6	EZ81	5/6	PY80	6/6
		EZ84	10/6	PY81	6/6

**TRANSISTORS, ZENER DIODES etc.**

0A5	2/6	OC16	15/-	OC83	5/-	AC176	7/8	CRS120	9/6	MPP102	11/-
0A10	3/-	OC22	10/-	OC83B	4/6	ACY28	4/-	CRS130	10/-	MPP103	9/6
0A70	2/6	OC25	7/6	OC139	7/6	AD140	13/-	CRS135	10/-	MPP104	10/-
0A71	2/6	OC26	5/-	OC140	9/6	AF17	5/-	CRS140	11/6		
0A79	1/9	OC29	15/-	OC145	4/-	AF18	10/-				
0A81	1/8	OC35	10/-	OC171	6/-	AF124	7/6				
0A200	1/9	OC38	8/6	OC172	7/6	AF127	5/-				
0A202	2/6	OC44	4/-	OC200	7/6	AF139	10/-				
0A210	7/6	OC45	2/6	IN21	3/6	AF178	12/6				
0A211	9/6	OC71	2/6	IN21B	5/-	AFY19	22/6				
0A220	15/-	OC72	4/6	IN25	12/-	ASV28	5/6				
0A220110/-		OC73	11/6	IX45	4/-	ASV28	5/6				
0A220110/-		OC75	6/-	IN70	4/-	BC107	3/6				
0A2206	8/6	OC76	5/-	2N1306	6/6	BFY51	5/-				
0A2208	6/6	OC81	4/-	2N1307	6/6	BFY52	4/6				
0A2213	6/6	OC81D	3/-	2S830	10/-	BEY27	5/-				
0A2223	6/6	OC81DM	3/6	AC126	6/6	BYZ18	15/-				
0A222510/-		OC82	5/6	AC127	7/6	BYZ16	15/-				
		OC82DM	3/6	AC128	6/6	CRS110	5/6				

12BA6	6/-	813	75/-
12BE6	6/8	832A	45/-
12BH7	3/6	866A	15/-
12C6	3/-	954	4/6
12E1	17/-	355	2/6
12K5	10/-	956	5/6
12K6GT	7/6	957	5/6
12RGT	5/6	991	6/6
12RGT	5/6	1622	17/-
12RGT	5/6	1903	6/6
12RGT	5/6	1962	5/9
12RGT	5/6	1963	6/6
12RGT	5/6	1964	20/-
12RGT	5/6	1965	10/-
12RGT	5/6	1966	10/-
12RGT	5/6	1967	10/-
12RGT	5/6	1968	10/-
12RGT	5/6	1969	10/-
12RGT	5/6	1970	10/-
12RGT	5/6	1971	10/-
12RGT	5/6	1972	10/-
12RGT	5/6	1973	10/-
12RGT	5/6	1974	10/-
12RGT	5/6	1975	10/-
12RGT	5/6	1976	10/-
12RGT	5/6	1977	10/-
12RGT	5/6	1978	10/-
12RGT	5/6	1979	10/-
12RGT	5/6	1980	10/-
12RGT	5/6	1981	10/-
12RGT	5/6	1982	10/-
12RGT	5/6	1983	10/-
12RGT	5/6	1984	10/-
12RGT	5/6	1985	10/-
12RGT	5/6	1986	10/-
12RGT	5/6	1987	10/-
12RGT	5/6	1988	10/-
12RGT	5/6	1989	10/-
12RGT	5/6	1990	10/-
12RGT	5/6	1991	10/-
12RGT	5/6	1992	10/-
12RGT	5/6	1993	10/-
12RGT	5/6	1994	10/-
12RGT	5/6	1995	10/-
12RGT	5/6	1996	10/-
12RGT	5/6	1997	10/-
12RGT	5/6	1998	10/-
12RGT	5/6	1999	10/-
12RGT	5/6	2000	10/-

**P. C. RADIO LTD.**  
170 GOLDHAWK RD., W.12  
(01) 743 4946

**METERS**  
Full List of our very large stock of meters on request.

**ALL OVERSEAS ENQUIRIES AND ORDERS**  
Please address to  
**Colomor (Electronics) Ltd.**  
170 GOLDHAWK ROAD, LONDON W12.  
Tel.: 01-743 0899

**RADIO AND ELECTRONIC HOBBIES**

**F. C. Judd** 21s net  
Here's a comprehensive guide for the amateur constructor covering Radio Receivers, Audio-amplifiers, Transistor Circuits, High Fidelity and Stereo, Tape Recording, Electronic Music and Musical Instruments, Amateur Radio Transmitting, Radio Control, Short-wave Listening and Amateur Radio, the Cathode Ray Tube, Aerials, Test Equipment, etc.  
"Highly recommended as a mine of information for the experimenter wishing to leave audio at a tangent."—*Tape Recorder*

**RADIO-CONTROLLED MODELS**

**R. H. Warring** Second Edition 18s net  
This is a complete book on Radio Control as applied to model aircraft, boats and land vehicles. It describes radio-control principles and the various methods of relating radio signals to mechanically controlled surface movements via actuators and servos. Simple single-channel systems, proportional control systems and multi-channel operations are all fully described, including installation and operation details in various models. Other chapters explain the various types of receivers and transmitters as well as building simple transmitters from components or kits and the selection of equipment.  
"Just what the modeller wants and needs to know".—*Air Pictorial*—

**COMPUTERS FOR THE AMATEUR CONSTRUCTOR**

**R. H. Warring** 20s net  
This book sets out to provide a background knowledge of computers as a whole and their working principles. It gives an overall picture of modern computers and their capabilities. The bulk of the book however, is devoted to practical descriptions of computer circuits and circuit elements well within the capabilities of anyone to build. In particular, detailed circuits are given of two designs intended for amateur construction. Both are easy to build, yet they are quite advanced computer designs.



**MUSEUM PRESS**

PITMAN PUBLISHING, 39 PARKER STREET, LONDON WC2

**CITY & COUNTY OF BRISTOL  
BRISTOL POLYTECHNIC**

Director: R. W. Bolland, B.Sc., Ph.D., F.R.I.C.

Applications invited for the following technicians in the Science Department, duties to commence as soon as possible

**SENIOR TECHNICIAN (Grade T.3) in PHYSICS**  
Ref. T698/66/1

**ASSISTANT TECHNICIAN (Grade T.1) in PHYSICS**  
Ref. T698/67/1

**Salary Scales:**  
Senior Technician £930—£1,095  
Assistant Technician £355—£800

Starting salary dependent upon age, qualifications and experience. An additional £50 or £30 per annum will be paid to candidates with appropriate National Certificate and C. & G. qualifications.

Applicants for Senior Technician post should be over 21 and have qualifications to at least O.N.C. or C. & G. Ordinary Technician standard and previous laboratory experience. Applicants for Assistant Technician post should have appropriate G.C.E. 'O' level or C.S.E. qualifications.

38-hour 5-day week with generous holiday and sick pay schemes. Opportunities for evening work with additional pay. Permanent posts with superannuation under Local Government conditions of service. All appointments subject to satisfactory medical report.

Further particulars and application forms (to be returned within fourteen days of this advertisement) from Chief Administrative Officer, Bristol Polytechnic, Ashley Down, Bristol BS7 9BU

Please quote appropriate reference number in all communications.

# PEDAL STEEL GUITAR

Part 3

F.C. JUDD


THE conclusion of Part 2 dealt with the last stage of assembly which was the linkage of the pedals to the roller levers by means of the "connecting" rods. The photograph on this page shows the actual connection of the horizontal rods to the roller levers. Adjustment of the pedal movement and linkage depends on the tuning adopted for the instrument but for the example given in Part 1 (an E6th tuning), string 2 will be tuned sharp and string 4 will be tuned flat when their respective pedals are depressed. The accuracy of the raising or lowering of pitch depends entirely on the accuracy of adjustment to the roller lever stop screws and the downward movement of the pedals. Adjustment should be such that when the pedal is depressed the string is re-tuned just as the pedal touches the stop rail beneath it and as the roller lever comes into contact with its own stop screw. The actual downward movement of the pedal for a semitone change of pitch should not be more than half an inch i.e., the pedals should normally rest about  $\frac{1}{2}$  inch or even less above the stop rail as shown in the photograph.

When preliminary adjustment of the pedal mechanism has been completed the engraved fretboard can be fitted. This may be glued to the guitar body with Evostik or Bostik. The strings can now be tuned to pitch and the accuracy of tuning checked over the full length of the fretboard i.e., at all fret positions. Providing the distance between the "nut" and the 12th fret and between the 12th fret and the centre line of the roller bridge are exactly equal (see diagrams in Part 1) the tuning should be accurate at all fret positions.

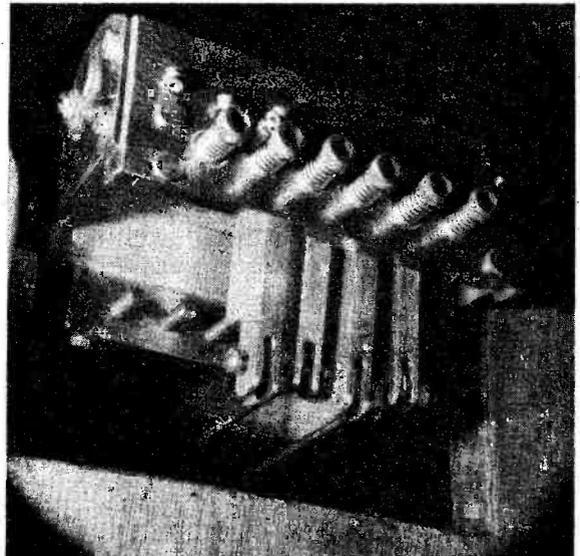
## The Preampifier

The final stages of construction are concerned with the preampifier, its power supply and the optional foot pedal volume control (swell pedal). The preampifier might also be considered as optional for there is no reason why the guitar pick-up should not be directly connected to a suitable amplifier already equipped with tone controls and volume control and having an input sensitivity of 50 to 100mV.

However, there is a purpose for the built-in preampifier in that it makes up for gain loss incurred by the foot-operated volume control and more important, it has a treble lift and cut control that will enable the player to obtain that very sharp brilliant tone favoured by players of the pedal steel guitar. In



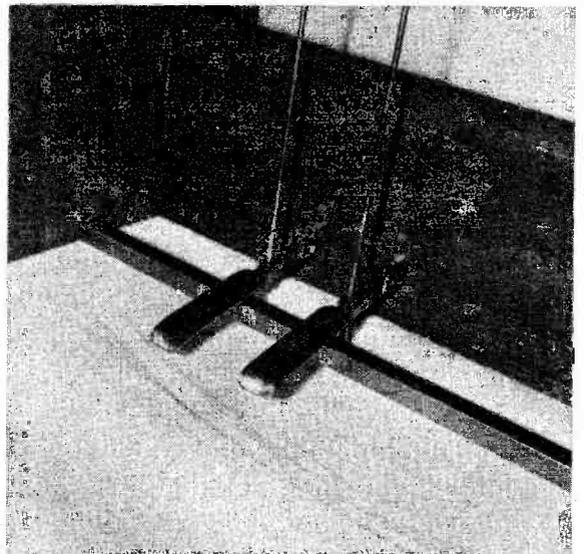*How the flat ends of the connecting rods are secured by 4BA screws to the roller levers.*



*Linkage to foot pedals. Adjustment is made by the 2BA nuts beneath the pedals, i.e., the pedals can be raised or lowered on the ends of the vertical connecting rods.*

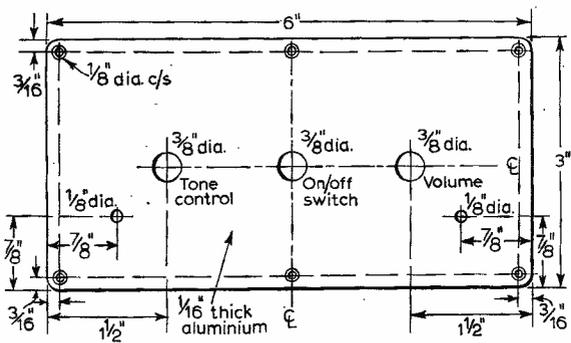


Fig. 20: The preamplifier panel. Details for drilling, etc.

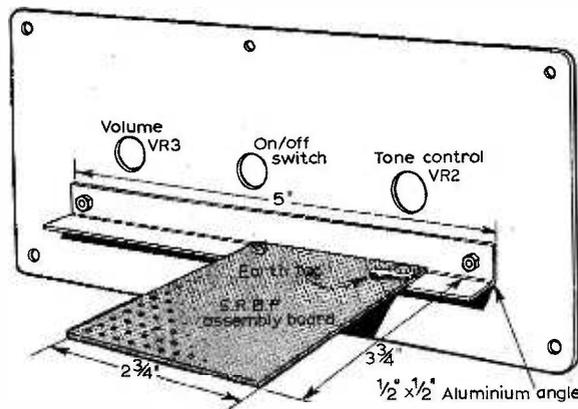


Fig. 21: Assembly of the preamplifier panel and circuit board.

fact the preamplifier may be of interest to plectrum guitarists.

The whole preamplifier is assembled on its own panel and if constructed to the dimensions given in Figs. 20 and 21 will fit into the slot provided on the top of the guitar console (see Part 1). The circuit is shown in Fig. 22 and employs two Mullard BC109 transistors with a negative feedback tone control system that provides approximately 15dB treble lift

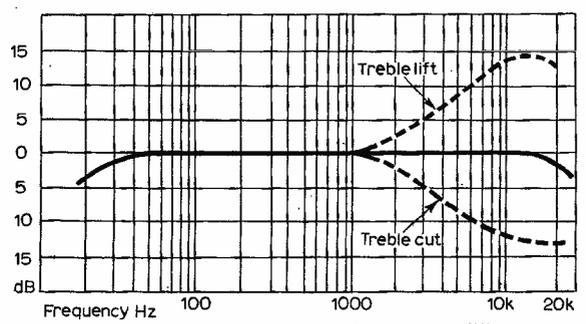


Fig. 23: Frequency response of the preamplifier.

and 12dB treble cut as shown by the response curves in Fig. 23.

The overall gain of the preamplifier can be varied a little by means of the pre-set control VR1 (4.7kΩ). For normal operation this control should be set to about midway position. At its maximum resistance the overall gain of the amplifier will be decreased. At its minimum resistance the gain of the amplifier will be increased but the amount of treble lift will

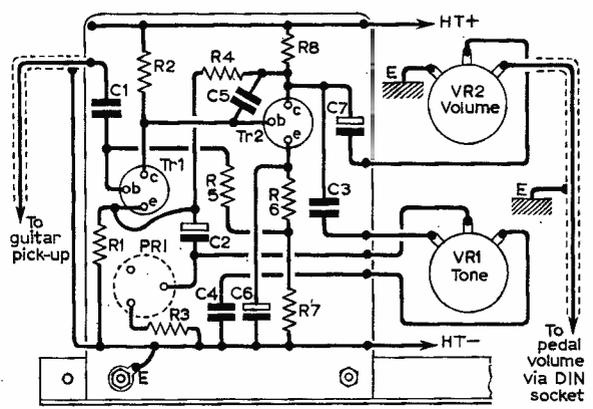


Fig. 24: Pictorial wiring diagram and layout for the preamplifier.

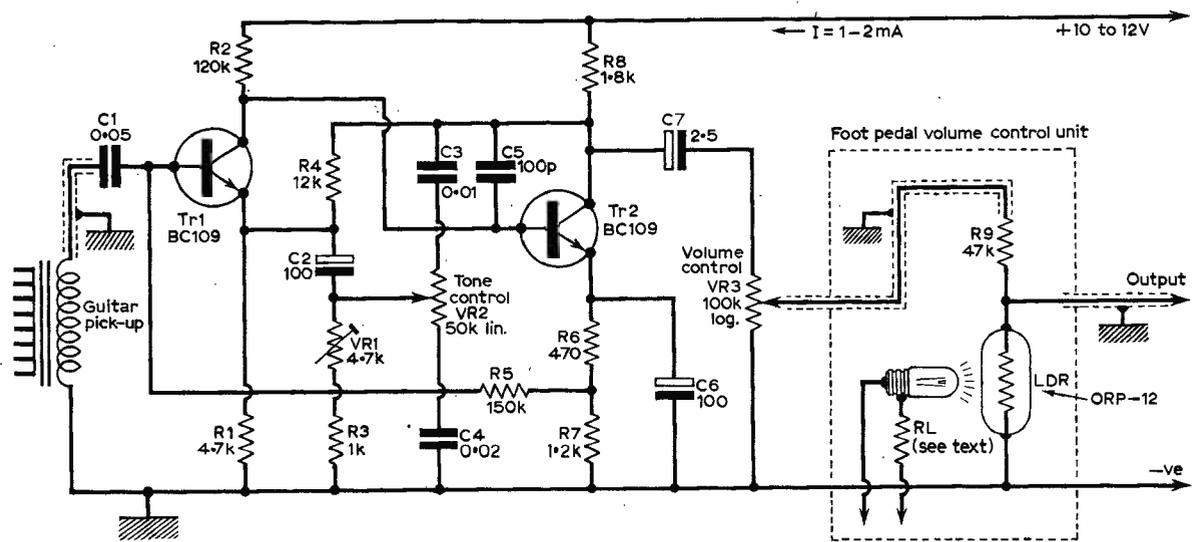


Fig. 22: Circuit diagram of the preamplifier.


be reduced. The average signal output from the pre-amplifier is about 200mV with VR1 set midway. With the foot pedal volume control in circuit the output is reduced to about 100 to 150mV. If the pedal volume control is not used, the output can be taken from the slider of VR3 and will be around 200mV. The preamplifier, with or without the pedal volume control, can be connected to any amplifier having an input impedance of 10kΩ or greater and an input sensitivity of 100 to 200mV. As already mentioned a higher or lower signal output can be obtained by adjusting the pre-set VR1. A pictorial wiring diagram for the preamplifier is given in Fig. 24.

Details for the power supply are given in Figs. 25A and B. If constructed as shown it can be mounted up inside the console as can be seen in the photograph. It may be necessary to orientate or reposition either the whole assembly or the mains transformer itself to prevent hum being induced into the guitar pick-up.
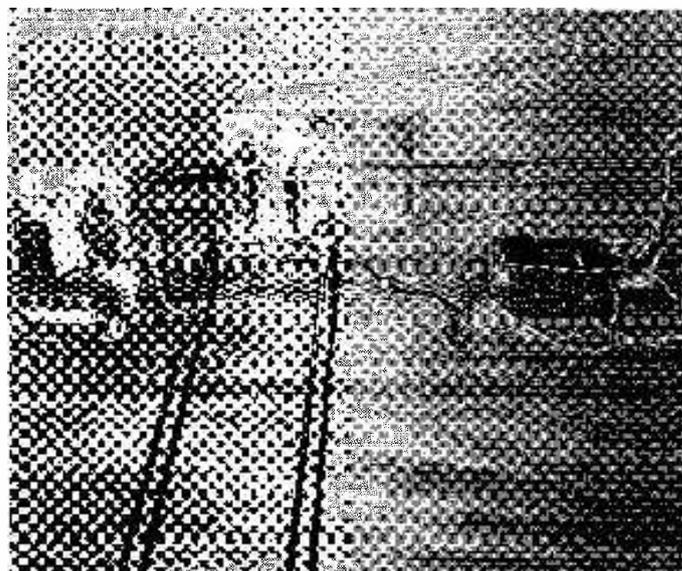
## The Foot Pedal Volume Control

Assuming the pedal volume control is to be used, then the pre-amplifier output can be fed to it via a 3-pin DIN socket mounted at the side of the console (see Part 1). This socket also carries the 12V d.c. (from the power supply) to light the control lamp in the pedal volume control. Wiring connections for the socket are shown in Fig. 26. The signal lead must be screened and the overall length of the cables between the two DIN plugs (A and B) should be at least 2 feet.

The pedal volume control employs a light discriminating resistor (ORP12) which becomes part of



The position of the power supply (left) and the pre-amp (right). Note also the relative position of the pedal rod linkage mechanism (centre) and the pre-tension spring just to the left of it.

an attenuating network formed by itself and R9. When the pedal is depressed in the backward direction, light from the control lamp decreases the resistance of the LDR and reduces the signal level. The light must not be too bright hence the need for some series resistance (RL). The author used a 6.3V 0.15A bulb with a series resistor of approximately 60 ohms. Lamps up to 12V at 60 to 100mA

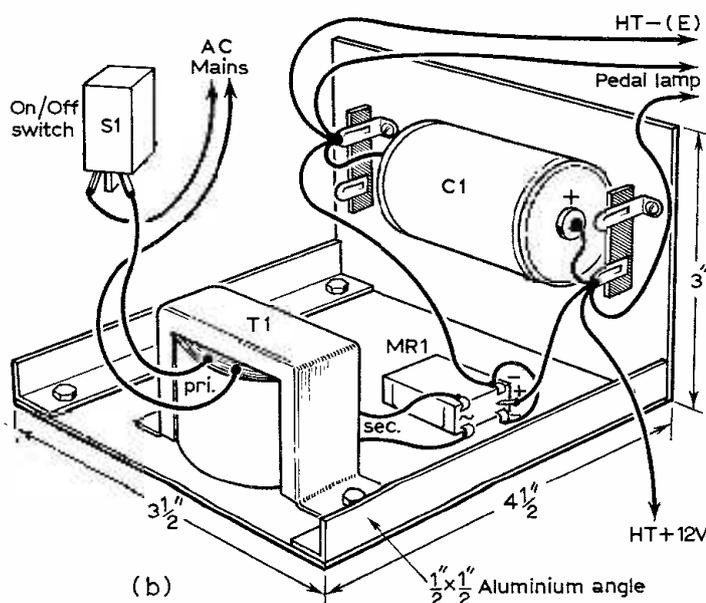
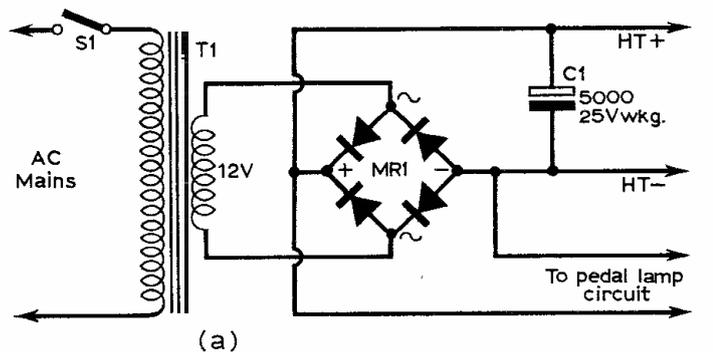


Fig. 25: (a) Power supply circuit. (b) Power supply assembly.

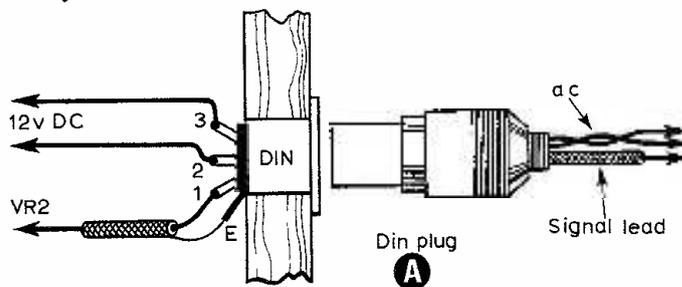


Fig. 26: Connections to the 3-pin DIN socket at the side of the console.



The completed foot pedal volume control.

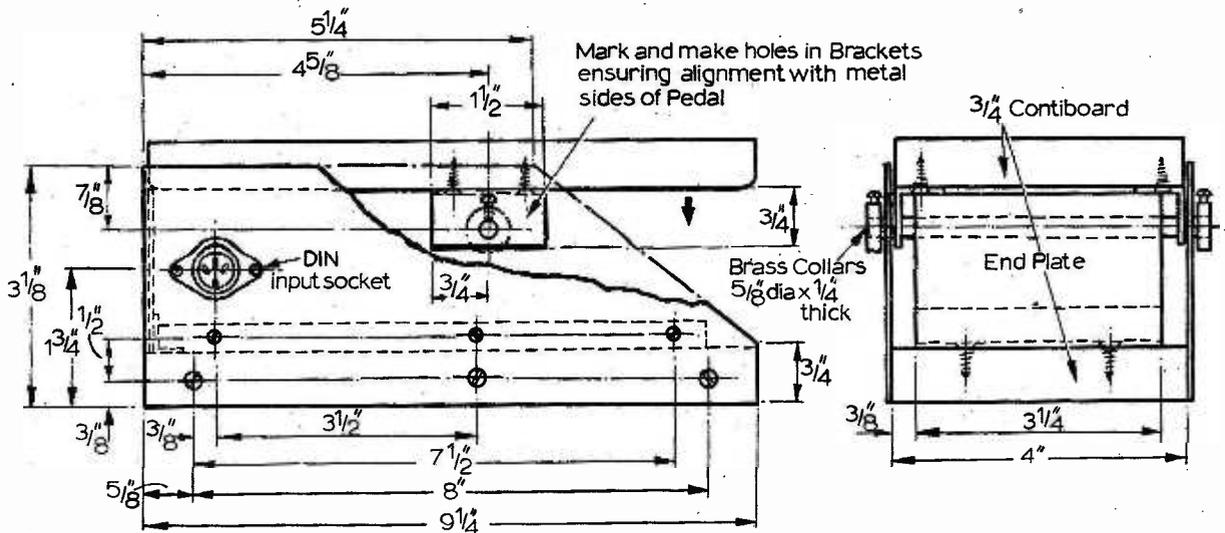


Fig. 27: Details of the foot pedal volume control.

can be used but should be dimmed a little with series resistance of appropriate wattage. A pre-set wire-wound resistor of about 50 ohms and 2W rating would be suitable.

An ordinary geared potentiometer pedal volume control could of course be used. The only real advantage of the LDR system is noiseless operation and the fact that it does not wear out as would a carbon track potentiometer. The photograph shows the completed pedal volume control and the diagrams in Figs. 27, 28, 29, and 30 give details for construction. The base of the control and the foot pedal were cut from  $\frac{3}{8}$  in. Contiboard left over from making the console. The two sides were made from  $\frac{1}{8}$  in. thick Dural. The pedal itself is hinged to the body on a  $\frac{1}{4}$  in. diameter spindle held fast by collars at each end and has an overall movement from level to a backward slant, of about 30°.

The control lamp and the LDR are both mounted in small wood blocks as shown in Figs. 30 and 31. It is best to solder the leads for the lamp directly to it and secure the lamp in the block with a spot of adhesive. The two blocks must be only just far enough apart to allow the aperture plate to move freely between them. The wiring for the 3-pin DIN socket, the output jack socket and the LDR and lamp are shown in Fig. 31. Providing the LDR is recessed in its mounting as shown in the diagrams it will not be affected by light coming from outside. Note that the end plate as shown in Fig. 29 serves as a forward stop for the pedal.

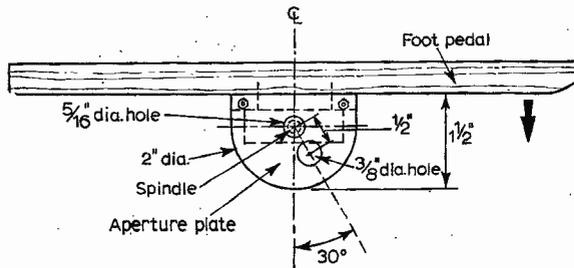


Fig. 28. The foot pedal of the volume control and the LDR aperture plate.

The complete and finished instrument, exactly as described in this series of articles, gave a very pleasant but brilliant tone quality with a good *sostenuto* (sustaining of sound) typical of the pedal steel guitar and its forerunner the Hawaiian guitar. As pointed out previously the number of pedals need not be confined at two only—some commercial single-neck instruments have four.

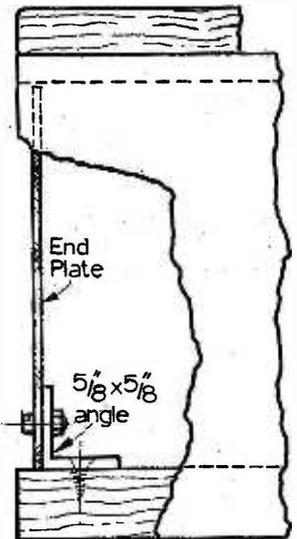


Fig. 29: The end plate acts as a stop for the forward-downward movements of the pedal volume control.

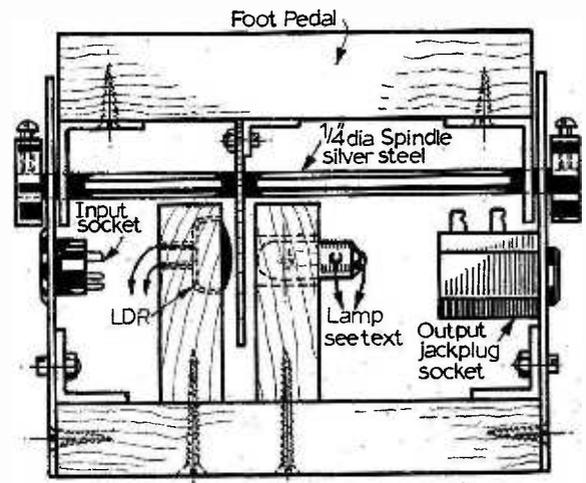


Fig. 30: The LDR and its lamp are mounted so as to be in line with the  $\frac{1}{4}$  in. diam. spindle and the centre line of the aperture plate.

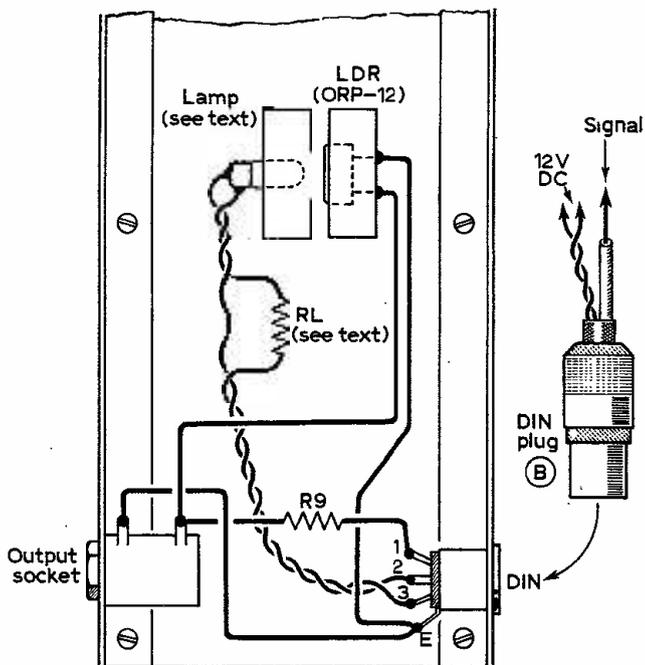


Fig. 31: Wiring for the pedal volume control, its input and output sockets and the 3-pin DIN connecting plug.

However, by making and fitting four roller levers as suggested, the two pedals can be changed over to other strings should alternative tuning combinations be required.

On reading through the first two articles again the writer has discovered one or two points that might not have been clear. First the unused roller levers. These should be locked at midway position (hanging vertically) by means of the locking screws. The strings can be anchored to them directly or to the holes in the tailpiece.

Before adjusting the movement of the pedals and linkage, set the roller levers concerned by means of their stop screws, so that they too hang vertically. The roller that is used to tension its string should now have its forward stop screw adjusted so that the lever can move forward i.e., toward the pick-up. The roller lever that is used to de-tension its string should have the rear (tailpiece) stop screw adjusted so that the lever can move toward the tailpiece. The basic tuning should of course be done with the pedals in their off or neutral position.

Finally a note on suitable strings. Those used for the tuning prescribed in Part 1 which is based on the chord of E6 were selected from the wide range of "Rotosound" strings for guitars of all kinds. These were as follows:

8	7	6	5	4	3	2	1
A $\flat$	B	D	E	A $\flat$	B	C $\sharp$	E
0.038"	0.028"	0.020"	0.016"				
Covered	Covered	Plain	Plain				
	0.036"	0.024"	0.018"	0.014"			
	Covered	Plain	Plain	Plain			

Heavy gauge covered strings could be used for 8, 7 and 6 with a resultant rounder and stronger tone. Some experiment with string gauges is well worthwhile and a list giving all the different gauges of strings and a chart showing the different types recommended for guitars i.e., pedal steel, Hawaiian and plectrum can be obtained by writing to Rotosound—James How Industries Limited (Music Division), 20 Upland Road, Bexley Heath, Kent.

## NEXT MONTH IN

# PRACTICAL WIRELESS

### THE MICROTEST

Few people build multi-range testmeters nowadays because Japanese ready-built meters are freely available at very competitive prices. There does, however, remain one distinct advantage in "rolling one's own", and this is the high degree of accuracy to which a meter can be calibrated. It is quite easy to do, and is fully described in this article on the Microtest 24-range a.c./d.c. multimeter using a 50 $\mu$ A movement.

### THE TWO-FIFTY TRANSMITTER


Radio Amateurs who are keen on turning their attention to 2-metres will find G3TYJ's Two-Fifty transmitter very appropriate. It is a relatively simple crystal controlled 4-valve 40watt input design which can be used as it stands for c.w., or connected to any normal modulator for phone. A circuit is also provided to assist those who prefer to use the simpler clamp-tube modulation. Full coil-winding details are given, along with sufficient constructional information to enable anyone who has a transmitting licence to build this transmitter without difficulty.

### REPAIRING LOUDSPEAKERS

Loudspeaker cones are very fragile, and the slightest tear can seriously impair reproduction quality. Having a speaker reconed professionally can be very expensive, however, and so this article explains how to carry out this task oneself, replacing the original paper cone with a combination of paper, expanded polystyrene, polyurethane foam and aluminium foil, the mixtures depending on which frequency range the loudspeaker is intended to cover. The complete cost of repairing one of the author's 12in. loudspeakers came to about 14s.
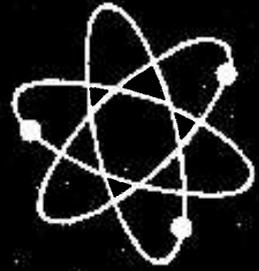
### PLUS OTHER CONSTRUCTIONAL PROJECTS AND REGULAR FEATURES

Do not miss your copy of the February issue of Practical Wireless—on sale 9th January price 3/-



## DESIGNING CLASS "A" TRANSISTOR AMPLIFIERS

C. R. BOGGIS, M.A.P.A.E.

**D**ESIGNING basic transistor amplifier stages can be made very simple by following a few "rules of thumb", so enabling the experimenter with but a modicum of theoretical knowledge to tailor established circuits to his own needs. This article, which can be read in conjunction with last month's "Experimenters Corner", describes how to work out the component values for germanium or silicon amplifiers and couple them to other stages without upsetting their operation.

### Germanium Amplifiers

If a single amplifier stage as shown in Fig. 1 is designed as follows it will be able to function over the temperature range of 20 to 50° Centigrade. In the worked example, a general-purpose small signal transistor is used (Mullard type OC71, or similar).

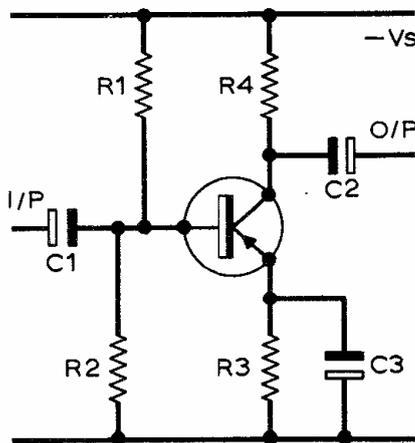


Fig. 1: A straightforward amplifier stage suitable for a germanium transistor.

First the supply voltage is chosen. Here we select 9 volts, this being readily available from standard batteries. We then decide on a value of collector current. For a very small input and low noise this should be around 100-200 microamperes, but for large inputs the current could be anything up to about 100 milliamps. As a general rule a current of 1mA is desirable, and it is around this figure that the stage designed here is evolved.

Having decided on the collector current, the first rule may be applied. This states that the emitter resistor should drop approximately 1 volt. Therefore in our example, R3 will be equal to  $\frac{1 \text{ volt}}{1\text{mA}}$ , since the emitter current can be considered equal to the collector current for this purpose, which suggests a resistor value of 1000 ohms.

The next rule states that for good stability, the collector voltage should be equal to half of the result of subtracting the emitter voltage from the supply voltage.

Here the collector voltage should be  $\frac{9-1 \text{ volts}}{2}$  or 4 volts.

With a collector current of 1mA, R4 should be  $\frac{4 \text{ volts}}{1\text{mA}} = 4000 \text{ ohms}$ , the nearest preferred value being 3.9kΩ.

Using yet another rule of thumb, R2 should be 10 times R3, which yields a value of  $10 \times 1\text{k}\Omega$ , or 10kΩ in this case.

The base voltage is determined by the  $V_{be}$  for the transistor plus the emitter voltage. For a germanium transistor,  $V_{be} = 0.2 \text{ volts}$  approx., so the base voltage required is 1.2 volts. The current through R1 is the same as the current through R2, since the base current, being very small, can be ignored. This current equals  $\frac{1.2 \text{ volts}}{10\text{k}\Omega}$ , which is 120 microamps. Thus R1 should drop 9-1.2 or 7.8 volts at 120 microamps. R1 therefore equals  $\frac{7.8 \text{ volts}}{120\mu\text{A}}$ , which is 65kΩ (use a 62kΩ preferred value).

The values of C1 and C2 hardly need calculating. Suffice to say that their reactance should be negligible at the lowest frequency to be amplified. An ideal value for each is 10μF. The working voltage is determined by the collector voltage of the stage and the base voltage in the following stage—usually a 6 volt capacitor will be suitable. Note the polarity of these two capacitors.

C3 should also be chosen such that its reactance is small at the lowest frequency. Here a value of 50μF will be ample, but again, note the polarity.

### Silicon Amplifiers

Using silicon transistors it is possible to obtain adequate temperature stability with a simplified circuit as shown in Fig. 2. The design procedure is even simpler


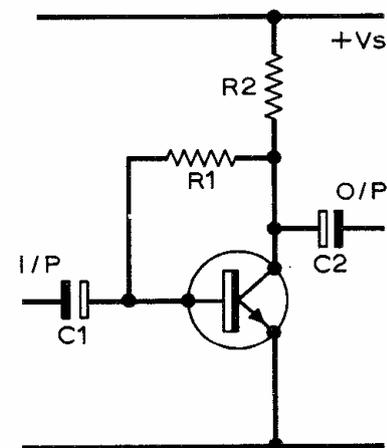


Fig. 2: A simple amplifier particularly suitable for a silicon transistor.

Fig. 3: A simple but effective passive four-input mixer with a high input impedance to each channel. As this circuit incurs considerable resistive loss, the circuit of Fig. 1 is used as a post amplifier.

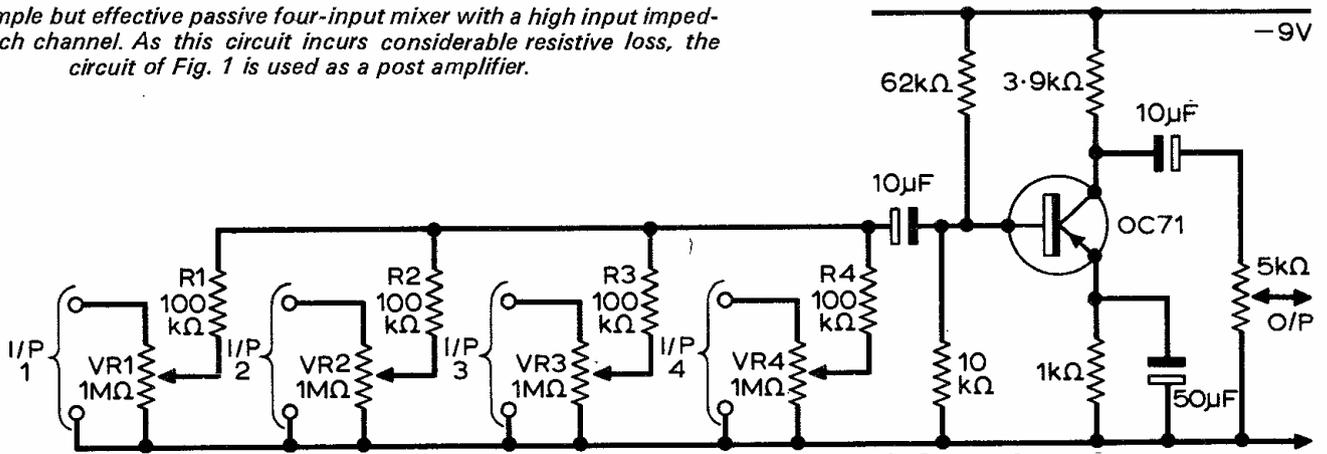

with this circuit, the number of components being so few.

First, choose the supply voltage; say 6 volts. The collector current is picked next. Here a value of  $200\mu\text{A}$  is used, as we are designing an input stage to be fed from a microphone, and low noise is most important. The transistor chosen is a Mullard BC109 (or similar).

As in the previous example using a germanium transistor, the collector voltage should be approximately half the supply voltage minus the emitter voltage. As the emitter voltage is zero, the collector voltage should be 3V. R2 will therefore be equal to  $\frac{3 \text{ volts}}{200\mu\text{A}} = 15\text{k}\Omega$ .

R1 is arranged to drop the collector voltage down to the level required for the base of the transistor. The base voltage needed here is equal to the  $V_{be}$  for the transistor, which is about 0.4 volts for silicon.

The base current required is calculated from the collector current divided by  $h_{fe}$  or beta for the transistor at that collector current. For the BC109,  $h_{fe}$  at  $I_c = 200\mu\text{A}$  is typically 300, so the required base current is  $\frac{200\mu\text{A}}{300}$ , which is  $0.6\mu\text{A}$ . R1 is therefore equal to  $\frac{3 - 0.4 \text{ volts}}{0.6\mu\text{A}}$ , which is  $4\text{M}\Omega$ . Allowing for somewhat lower  $h_{fe}$  values that may occur in production spreads R1 should be chosen as  $2.7\text{--}3.3\text{M}\Omega$ .

## Using the Circuitry

The circuit designed in Fig. 1 could be utilised in many ways. It could be used to amplify the signal from the detector of a tuner up to sufficient level to drive an earphone, in which case R4 should be replaced by a headset with a d.c. resistance of 4000 ohms. Alternatively, R4 may be left in circuit and driver and output stages added to drive a loudspeaker.

Another application could be as an audio mixer for several inputs, and the circuit in Fig. 3 shows such an arrangement. Resistors R1-R4 are included to reduce interaction between each of the mixer volume controls. The volume control at the output is the master volume control, and is effective over all inputs. By inverting the supply rail polarity, the circuit in Fig. 2 could be substituted for the OC71 amplifier stage.

## High Input Impedance

Where a high input impedance is required such as for amplification of a gramophone pick-up output, an emitter follower can be used in front of the circuit in Fig. 2. This additional amplifier is shown in Fig. 4, and this will give an input impedance of approximately  $2\text{M}\Omega$ . This is because the input impedance of the

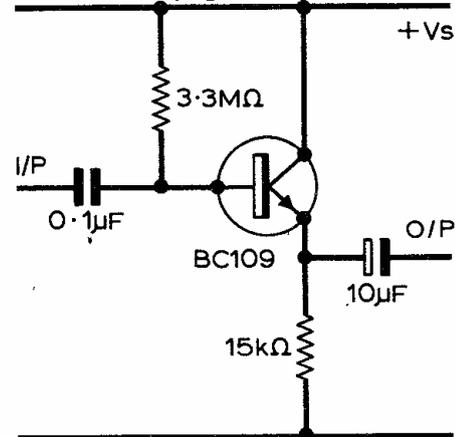


Fig. 4: An emitter-follower which exhibits a very high input impedance and a low output impedance. Its voltage gain is fractionally less than 1.

transistor is almost equal to the beta or  $h_{fe}$  times  $R_e$ .  
 $\text{Input } Z = 300 \times 15\text{k}\Omega = 4.5\text{M}\Omega$ .  
 This is shunted by R1, which is  $3.3\text{M}\Omega$ , so the input impedance =  $\frac{3.3 \times 4.5}{3.3 + 4.5} \text{M}\Omega = 2\text{M}\Omega$ . ■

### PRACTICAL GIFT FOR A PRACTICAL MAN

A full year series of PRACTICAL WIRELESS issues delivered by post each month would be an ideal Christmas present. Why not give a subscription to a friend. He would certainly find the magazine just as interesting as you do, and each issue would remind him of your good wishes.

But don't think too long—Christmas is very close. Just fill in both parts of the form below, and post it with your remittance (£2 20 United Kingdom and overseas) to:  
 Subscription Manager, Practical Wireless, Dept. X  
 Tower House, Southampton Street, LONDON W.C.2.

We will despatch first copies to arrive in time for Christmas, and send an attractive Christmas greeting card in your name, to announce your gift.

To: Subscription Manager (Practical Wireless) Dept. X.  
 Tower House, Southampton Street, W.C.2.

MY NAME .....  
 ADDRESS .....



I enclose PO/MO/Cheque (made payable to IPC Magazines Ltd.) for the sum of (.....) for a Christmas Gift subscription of 12 issues of PRACTICAL WIRELESS.

It should be sent to:


NAME .....  
 ADDRESS .....

To avoid disappointment, make sure of your own copy by placing a regular order NOW with your newsagent.

# A PANORAMIC RE

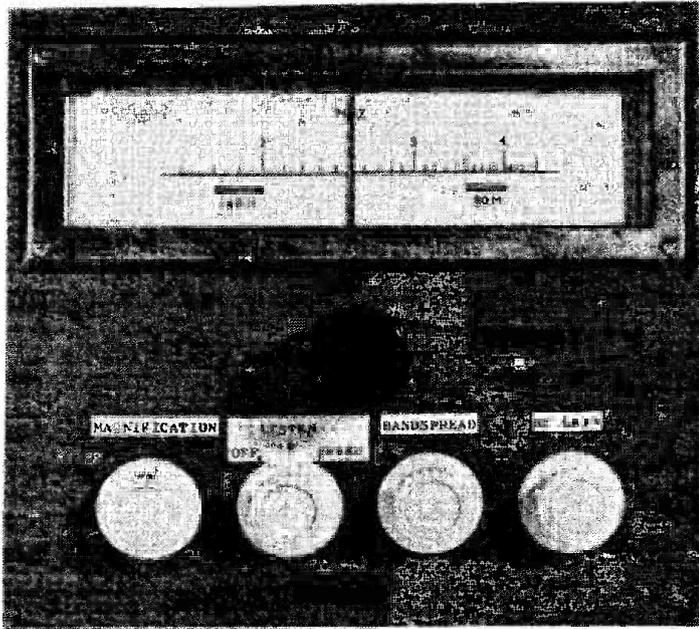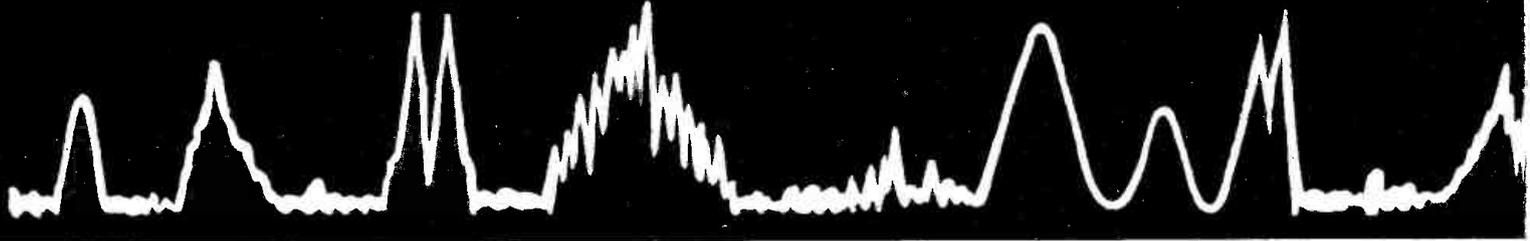

## D. BOLLEN PART 1

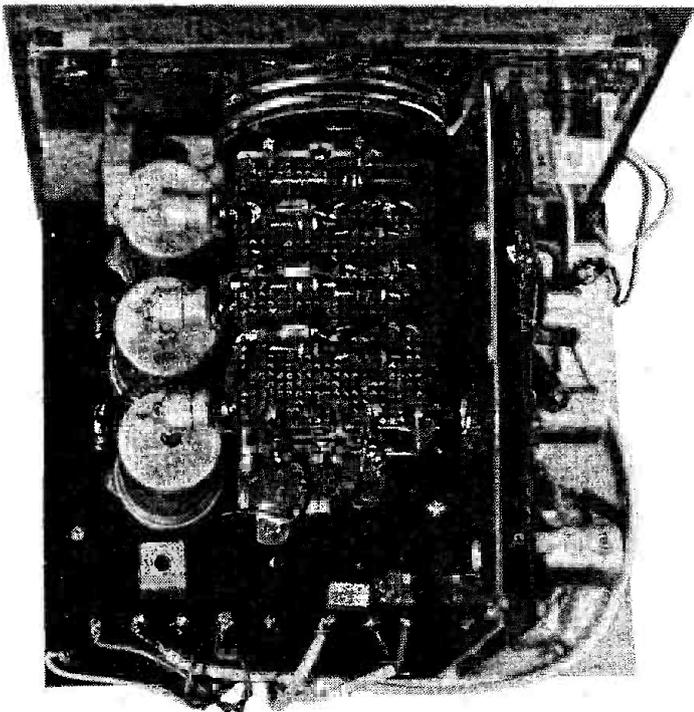

A PANORAMIC receiver provides a visual display of a band of frequencies when coupled to an oscilloscope, and this can be a useful aid to the serious short-wave listener or radio amateur. Signals appear on the oscilloscope screen as a series of resonance curves, of differing amplitude and character, spaced along the X-axis as though on a tuning scale. All signals are resolved visually without switching, whether they be a.m., c.w., s.s.b. or f.m., and the operator soon learns to distinguish between them. A quick assessment of general conditions on the band can be made without having to break off an existing contact on the main "shack" receiver. Thus, the need for searching by means of frequent manual retuning is largely eliminated.

Before semiconductors came on the scene, automatic "sweep" tuning of a receiver could only be accomplished by complicated arrangements of motor-driven tuning capacitors or reactance valve circuits, but now simple circuits based on the capacitance variation of semiconductor diodes when reversed biased are used.

The equipment described here employs ordinary, readily available components, and is designed for simple construction and low cost, to cover bands of frequencies up to 500kHz wide lying between 1.7MHz and 4.5MHz, which includes 160 and 80m.

### HOW IT WORKS

Figure 1 gives the block diagram of the panoramic receiver. A conventional two transistor converter, involving three "gang" tuned circuits, is coupled to a 1.6MHz i.f. strip. An alternative arrangement is with the converter feeding a medium wave receiver which is tuned to 1.6MHz, thus achieving a double-superhet configuration. A voltage taken from the oscilloscope timebase simultaneously varies the capacitance of three diodes, each placed across one of the tuned circuits in the converter. At the same time, an output voltage is derived from the final i.f. detector diode for display on the oscilloscope Y-axis. If a continuous unmodulated carrier is received, the oscilloscope will show the overall response curve of the panoramic receiver, in the form of a single peak situated somewhere along the X-axis. Two plain carriers at different frequencies will appear side by side. The effects of modulation will be discussed later.

In practical terms, the small change of diode capacitance, compared with the main tuner capacitance swing, is quite sufficient to offer a useful "sweep". If an attempt is made to get a really wide panoramic bandwidth then signals will be too cramped on the display for easy recognition, and

# RECEIVER for 160 to 80 METRES

“tracking” problems will arise. Under typical operating conditions, “sweep” bandwidths of less than 50kHz will offer an informative display, but the bandwidth obtained with the prototype receiver is continuously variable between zero and 500kHz on 80 metres, and zero to 100kHz on Top Band, which is sufficient for most requirements.

Although intended primarily as an accompaniment to an existing communications receiver, the panoramic receiver can be used on its own. Switching is included to stop the “sweep” and allow normal reception of an a.m. signal, either with headphones or via an amplifier and loudspeaker, as shown in Fig. 1.

The prototype receiver made use of a mixer and 465kHz i.f. strip taken from an old transistor portable radio. After careful peaking of the 465kHz i.f. transformers—made easy by the panoramic receiver display of its own response curve—excellent reception of signals was obtained, including s.s.b. when a b.f.o. was added.

Although, at first sight, the panoramic receiver would seem to involve quite a lot of constructional work, it will only be necessary to build a straightforward two transistor converter, plus a “sweep” tuner circuit panel consisting of a small collection of components, if a medium wave receiver and an inexpensive oscilloscope are already to hand. Even greater simplification results when the “sweep” tuner is fitted to an existing receiver.

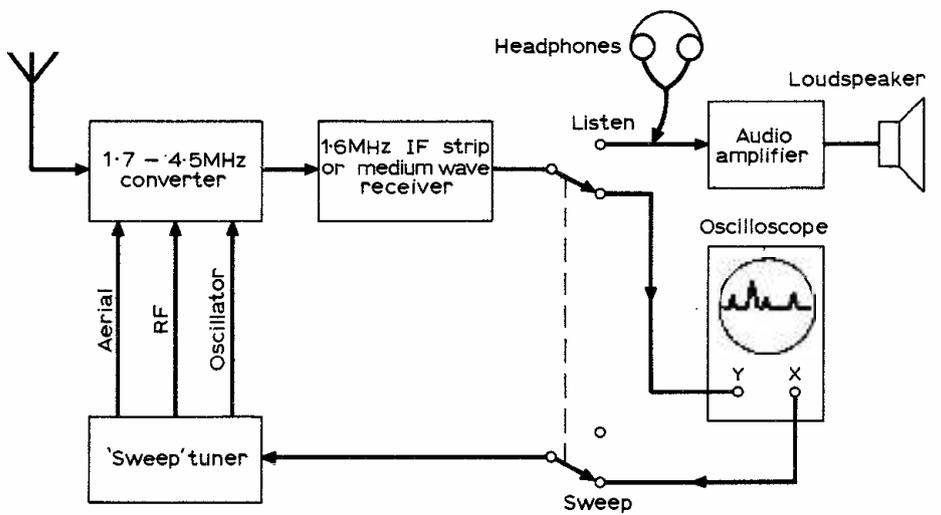


Fig. 1: Block diagram of the panoramic receiver.

capacitance is obtained when a reverse voltage of 10V is applied.

A single diode “sweep” tuner circuit serves to demonstrate how a rectifier diode can be linked to the tuned stage in a radio receiver (see Fig. 3). The tuned circuit, consisting of an r.f. inductor L1, a trimmer capacitor TC1 and a variable capacitor VC1, is coupled in parallel with the variable capacitance diode D1 via d.c. blocking capacitor C1. A re-

## DIODE CAPACITANCE

Virtually all semiconductor rectifier diodes exhibit junction capacitance, due to the depletion layer when reversed biased, and this capacitance varies with reverse voltage. Varactor diodes are specially manufactured to exploit depletion layer capacitance and to offer a good performance at very high frequencies. It is not generally realised, however, that ordinary silicon power rectifiers, as used for h.t. supplies, can also be employed as voltage controlled capacitors in circuits working at several MHz. The graph given in Fig. 2 shows the capacitance characteristics of four types of silicon rectifier. It can be seen that the characteristic of each diode is non-linear, and that maximum capacitance depends on the particular diode type. In nearly all cases, a capacitance variation amounting to some 50% of maximum junction

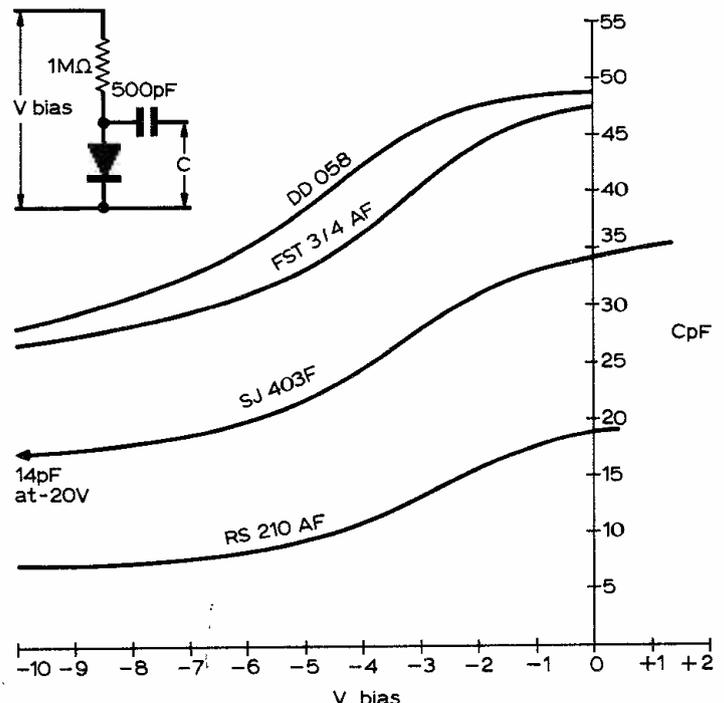


Fig. 2: The capacitance characteristics of four types of silicon diode.

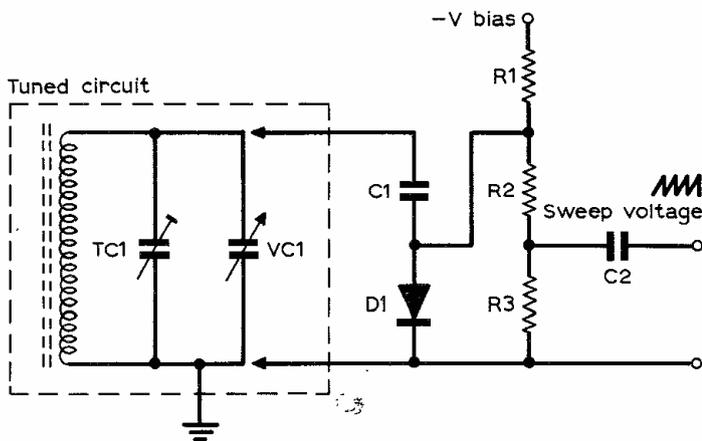


Fig. 3: A single diode "sweep" tuner.

verse voltage is applied to the diode by the potential divider formed by R1, R2 and R3. R1 and R2 have values of more than 1M ohm, to minimise loading of the tuned circuit. Approximately half the bias voltage will appear at the junction of R1 and R2, and the sawtooth timebase voltage, which is fed to R3 via C2, will cause the reverse voltage across the diode to "sweep" in sympathy with the oscilloscope X deflection, between zero and full bias conditions. It is important to avoid driving the diode into conduction by the application of too large a timebase voltage. Although no damage will result, a forward bias across the diode will lower the "Q" of the tuned circuit, and cause loss of gain. An interesting feature of the Fig. 3 circuit is that a small alteration of d.c. bias across the diode will change its capacitance, therefore, bandsread tuning can be accomplished easily merely by placing a variable resistor in series with R1.

The governing factor in the choice of a diode for receiver tuning is its zero bias capacitance. If the diode has a large capacitance it will seriously restrict the high frequency coverage of the receiver. On the other hand, if the diode has a small capacitance, the "sweep" bandwidth of the panoramic receiver will be correspondingly narrow. As a general rule, a zero

bias capacitance of about 10% of the maximum tuned circuit capacitance will be about right.

In the case of the 1.7MHz-4.5MHz converter used for the panoramic receiver, maximum tuned circuit capacitance is in the region of 330pF, calling for a diode capacitance of 33pF. Varactor diodes listed by well-known suppliers fall outside the required capacitance value, being either too large or too small, but a wide choice of rectifier diodes exists. The A.E.I. type SJ 403F was found to be ideal, having a zero bias capacitance typically of 34pF, falling to some 14pF with a reverse voltage of 20V, see Fig. 2. If difficulty is experienced in obtaining the SJ 403F, there is no reason why other types should not be tried. A diode can be checked for zero bias capacitance value by connecting it, in series with a fixed mica capacitor of about 500pF, across the terminals of a capacitance bridge. The aim should be to find three diodes, preferably of the same type, which have a nearly identical capacitance value falling close to 33pF. In practice, anything from, say, 25pF to 40pF can be deemed usable in the panoramic receiver.

The converter circuit of Fig. 4 is designed around Denco transistor tuning coils and n-p-n silicon transistors. Coils T1, T2, and T3 are intended for use with a 310pF+310pF+310pF tuning capacitor and 30pF trimmers. Padder capacitor C7 in Fig. 4 serves to give correct tracking between oscillator and other stages.

Denco 3T coils normally cover the range 1.7MHz to 5MHz, but the addition of extra diode tuner capacitance to the tuned circuits in the converter will lower the upper frequency limit to 4.5MHz, without otherwise affecting performance.

In Fig. 4, the aerial coil T1 is tuned by VC1. A signal is amplified by r.f. stage Tr1 and is then passed to the secondary winding of T2. T2 is tuned by VC2. Self-mixing oscillator Tr2 converts the signal to 1.6MHz, and the oscillator coil T3 is tuned by VC3. I.f. transformer IFT1 provides the correct matching impedance to the base of a following tran-

## ★ components list

### Resistors:

R1 18kΩ  
 R2 6.8kΩ  
 R3 2.7kΩ  
 R4 18kΩ  
 R5 6.8kΩ  
 R6 2.7kΩ  
 R7 1kΩ  
 R8 470Ω  
 R9  
 R10  
 R11 } 2.2MΩ  
 R12 }  
 R13 }  
 R14 }  
 R15 560kΩ  
 VR1 1kΩ carbon linear pot.  
 VR2 25kΩ carbon linear pot.  
 VR3 100kΩ carbon linear pot.  
 VR4 1MΩ miniature skeleton pre-set.  
 All fixed resistors ½W, 10%.

### Transistors:

TR1 } 2N2926 (orange  
 TR2 } spot)

### Diodes:

D1 }  
 D2 } SJ403F (see text)  
 D3 }

### Switch:

S1 Four-pole three-way rotary

### Coils and transformers:

T1 Blue }  
 T2 Yellow } Denco 3T  
 T3 White }  
 IFT1 Denco IFT 16/1.6

### Capacitors:

C1 0.05μF }  
 C2 0.01μF } polyester 250V  
 C3 0.05μF }  
 C4 0.033μF }  
 C5 0.01μF }  
 C6 0.01μF }  
 C7 340pF polystyrene 125V ±2½%  
 C8 0.1μF polyester 250V  
 C9 470pF }  
 C10 470pF } polystyrene 125V ±2½%  
 C11 470pF }  
 C12 0.1μF polyester 500V  
 VC1/VC2/VC3 Jackson type E3 310pF + 310pF + 310pF  
 TC1 }  
 TC2 } 30pF Philips concentric airspaced.  
 TC3 }

### Miscellaneous:

Jackson SL16 scale drive assembly. Bias battery type B122. S.r.b.p. sheet 7in. × 5½in., turret tags, 0.1in. matrix Veroboard or plain drilled s.r.b.p. 21 × 30 holes, matrix pins, 18s.w.g. aluminium plate 7in. × 2½in.

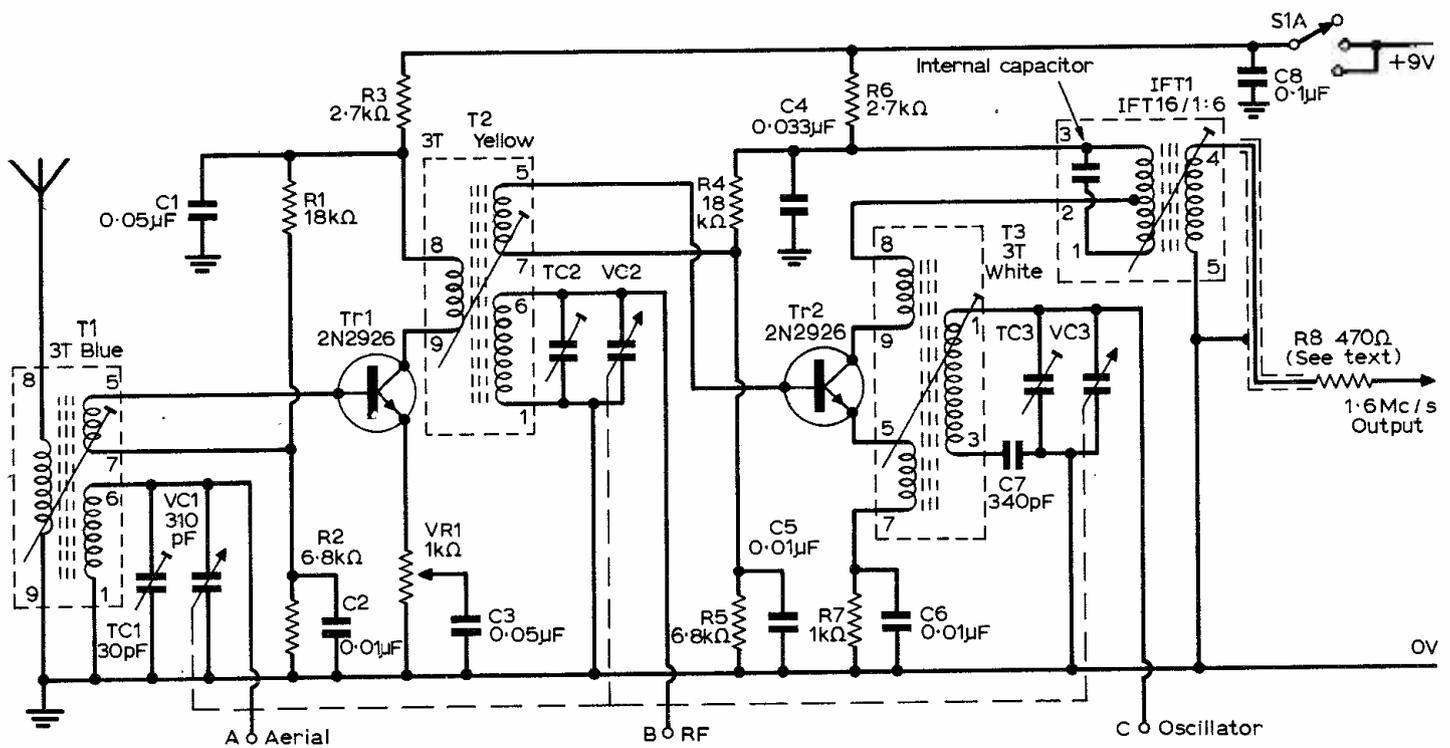


Fig. 4: The 1.7 to 4.5MHz front-end. This is a simple tuner designed around Denco coils.

sistor stage in a 1.6MHz i.f. strip, or a mixer in a medium wave receiver. Methods of coupling the converter to following stages will be outlined later.

To prevent instability, the r.f. stage in Fig. 4 is decoupled by R3 and C1, and the mixer by R6 and C4. C8 decouples the +9V supply line. VR1 is included to allow adjustment of r.f. gain, so that an optimum signal-to-noise performance may be achieved. The purpose of resistor R8 will be explained later.

### THREE-GANG diode tuner

In the diode tuner circuit of Fig. 5, d.c. bias for the diodes is conveniently supplied by a small, long-life 22.5V battery. Diode and bias polarities are so arranged that a left to right timebase sweep will give high frequency signals on the right-hand side of the

display. VR2 and R15 form a potential divider, and VR2 acts as a bandspread control, giving deviations of the order of  $\pm 15\text{kHz}$  at 3.4MHz, and just a few kHz at 1.9MHz. Short-term frequency stability of the diode tuner, when switched to "listen" is sufficiently good to allow s.s.b. signals to be easily resolved with the aid of a b.f.o.

Each diode in Fig. 5 has its own potential divider, formed by the 2.2M ohm bias resistors R9-R14, but the dividers are connected to earth via a common resistor, formed by the track of potentiometer VR3. Thus, while each diode is individually d.c. biased, and is isolated from other diodes by the high value of divider resistors, a sweep voltage injected into VR3 will swing all three diodes simultaneously. Capacitors C9-C11 couple the diodes to the tuned circuits in the converter.

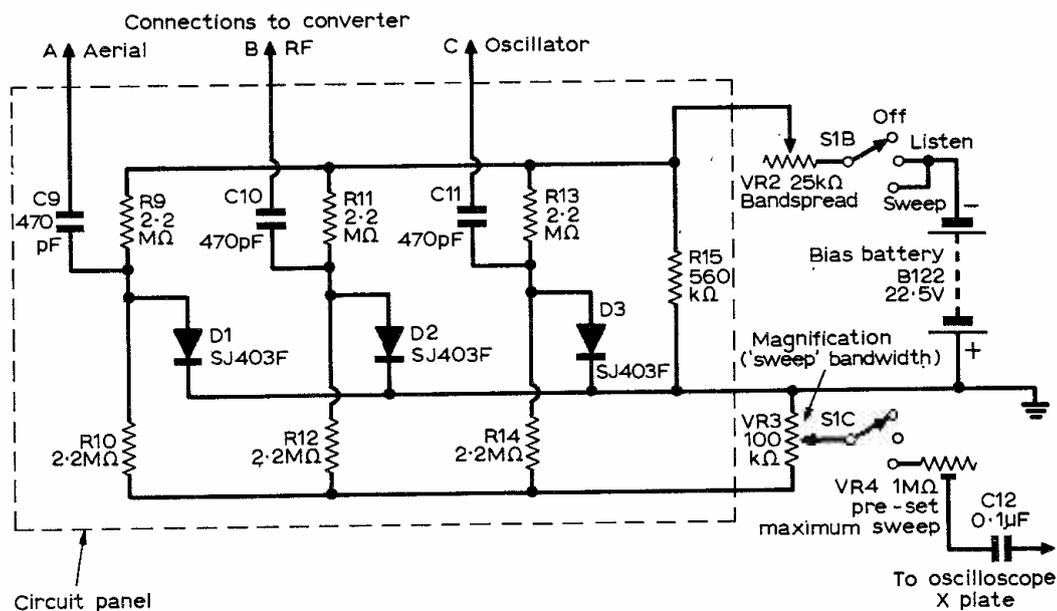


Fig. 5: The "three gang" diode sweep tuner, Sections A and B swing the r.f. tuned circuits T1 and T2 in Fig. 4, and section C sweeps the oscillator T3.

The oscilloscope time-base sweep voltage is fed to the diode tuner via C12 and VR4. VR4 serves to pre-set the maximum sawtooth peak voltage when VR3 is set for minimum magnification (maximum sweep bandwidth), and will cater for typical oscilloscope X-plate voltages of 100V-400V. As the slider of VR3 is moved towards the earth rail, a signal peak at the centre of the display will be expanded, i.e., magnified, until it fills the screen; this facility is useful for a close examination of adjacent signal heterodyne interference, as well as various transmitter modulation defects.

**Part 2 next month:**  
**Construction, alignment and use.**

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

IT is my intention to devote as much space as possible to news and logs sent in by readers of this column. Several logs were received this month and they have been included in this article.

If you have any news or loggings which you think would be of interest to your fellow-readers you should send them to PRACTICAL WIRELESS by the 14th of each month or to my home address: 58 Kensington Gardens, Ilford, Essex, by the 17th. It would be helpful if you could enclose a list of the equipment you use as this helps people to make a comparison between your logs and their own results.

### Readers' Logs

**John W. Smith**, of Anstruther, in Fife, sent in the following items from his log:

11,770: *Radio Nigeria* in English from 1900 to 1930.

15,080: *Radio Euzkadi*, clandestine, in the late evening.

15,155: *Radio Dif. de Sao Paulo* at 2320.

He also reports that *Radio Denmark* transmits its European Service from 1030 to 1115 (Saturday-Sunday) instead of 1015-1100. The frequency is still 9,520 and the "DX Window" programme will be broadcast at 1045 on Sundays.

**Mr. H. Wood**, of Manchester, sent in these news items:

**Canada:** The new autumn schedule of the CBC is 0715-0745 on 9,625 and 5,990, 1217-1313 on 15,325 and 2115-2152 on 11,720, 15,325 and 17,820. All times and frequencies refer to the European Service.

**Netherlands Antilles:** The *Radio Nederland* transmitter at Bonaire is now using the frequency of 9,715 from 0800 to 0920 and from 0500 to 0620.

**Roy Patrick**, of Derby, sent in these interesting items:

**Andorra:** The English Service of *Radio Andorra* is from 0100 to 0200 on Saturday mornings (according to my information, Roy, it is from 0000-0100 GMT). Roy also lists the shortwave outlet as being inactive.

**Canada:** CHNX has been logged by Roy on 6,130 around 0100 with a fair signal.

According to *Radio Canada* the plan to replace the 50kW transmitters with ones of 250kW has been dropped. (This is due to the Government's recent austerity economy measures.—MC.)

**Luxembourg:** The shortwave outlet of *Radio Luxembourg* on 6,090 will increase its power to 500kW early next year.

**S. Arabia:** Roy has heard an English newscast from this country at 1700 on 11,855 but has not been able to hear it since.

### Africa

**Biafra:** *The Voice of Biafra* continues to broadcast on 6,144 from 0455 to 0200 whilst *Radio Biafra*

Times in GMT • Frequencies in kHz

## THE BROADCAST BANDS

Malcolm Connah

uses 7,307 from 0430 to 2230. The two stations do not use parallel programming.

### Asia

**Cyprus:** The Cyprus Broadcasting Corporation has resumed its shortwave transmissions. The station broadcasts at 1900-2105 Monday to Saturday on 15,260 and at 0900-1600 on Sundays on 17,875. The Corporation is very interested in receiving reports from listeners.

**Korea:** *Radio Pyongyang* has a new frequency of 9,613 for its English transmissions at 1900-2000 which are beamed to Europe, Africa, the Near and Middle East.

### Europe

**Andorra:** The English Service of *Radio Andorra* on 701 and 5,995 is now scheduled for 0000-0100 on Saturday mornings but there is no sign as yet of the shortwave outlet.

**Austria:** *Radio Austria's* DX programme is broadcast every second Sunday at 1915 on 6,135, 9,610, 11,925 and 15,210.

**Belgium:** The English programme "Belgium Speaking" is broadcast at 2205-2215 on 9,550, 9,660 and 11,715 and at 0050-0100 on 6,125, 9,660 and 11,715; 9,660 is a new frequency for this broadcast.

**Germany:** One of my German colleagues informs me that Europe's most powerful shortwave transmitter will be built at Mindelheim, West Germany. The transmitter will beam programmes to all parts of the world during the Olympic Games at Munich. Six hundred announcers will inform sports fans all over the world about the Games in twenty-eight languages.

**Great Britain:** The Sunday broadcast of the BBC's "World Radio Club" programme is now broadcast at 0815 instead of 0930.

**Sweden:** Due to interference problems *Radio Sweden* is altering the frequency of its broadcasts to Eastern North America from 9,710 to 5,990. This change concerns the English, Swedish and Spanish programmes broadcast between 0000 and 0230.

### South America

**Colombia:** *Emisora Atlantico, Barranquilla* (HJAG) which is listed as inactive in the *World Radio-TV Handbook* is now operating on 4,905 until sign-off at 0500 with a power of 10kW.

**Ecuador:** HCJB, *The Voice of the Andes*, uses two new frequencies of 15,415 and 17,780 for its programmes from 1845 to 2030.

**Nicaragua:** *Radio Nacional de Nicaragua* can be heard in Europe after 0100 on the new frequency of 11,875.

73's and good DX until next time.

# THE AMATEUR BANDS

## David Gibson, G3JDG

**A** VERY good month for the DX hounds, but not too satisfying for those who only listened on 20 metres. This band, although, perhaps, the main DX band for many, has put on its winter overcoat of fading and is usually rather dead in the evenings.

The i.f. bands are beginning to come into their own and there has had been a noticeable improvement, especially on 40 and 80.

Topband has helped to inspire its followers by allowing a few American c.w. signals across the pond and this is very heartening for topband transatlantic enthusiasts. Listen early mornings down the l.f. end for these sigs.

Honours this month go to 10 metres which played host to a very large number of signals throughout the month. Twice when your scribe's ears flapped over the 28-29.7MHz segment, four of the continents could be heard during the same session. It's quite surprising how many a.m. signals are loose on this band as compared to, say, 14MHz where sideband mostly dominates. The majority of the 10 metre signals were romping through at S9 too, so don't forget to keep an eye on this band whenever you switch on.

Two sharp-eyed correspondents have drawn my attention to the G3RPE/P F2FO/P contact made on 10,000MHz. Alas, my "red spot" transistors don't function up that far, but congrats to both operators on a very fine achievement! Who knows, now that the amateurs have shown that it's possible, the professionals may decide to have a go.

Just to be different, let's take a look at the happenings for the month when all good Christmas pud's are stirred. Four main events down in my diary are: 6th-7th December, 80 metre c.w. contests; 6-7th, CHC International c.w. contest; 7th, 4 metre c.w. contest; 13th-14th, CHC international s.s.b. contest.

Don't forget that on Christmas morning there will be a large number of "local" club nets on the go. Topband is a favourite for these and some are quite witty. Certainly they all provide good festive r.f. entertainment. G3JDG promises to erect a reasonable antenna for topband on that morning and rude remarks concerning signal strength and mod. from over 25 miles would be appreciated.

So, where's it all been happening? Well, **Charles Morgan** (Northumberland), had great success on topband. Between 0430 and 0630 he logged K1PBW (599), KV4FZ (579), VP9GJ (459), W1BB/1 (599), W2EQS (359), W2IU (499). Figures in brackets are standard RST reports and all signals were c.w. Frequencies to listen from band edge to 1,805kHz.

If you are still unconvinced that the l.f. end of the spectrum is worth a listen, how about the log from **R. Bagwell** (Surrey). He runs a Trio 9R59DE with a PR30 pre-selector, an RQ10 and a switched attenuator fed by an a.t.u. which in turn squints down a 70ft. long wire. Eighty metres revealed—CN8AW, HV3SJ, JW1CI, JW3KJ, VE1IE, PY7ASQ, PY7GV, TF5TP, VO1CW, VU1AX, 3V8NC, 3Z3BLG (new prefix for Poland) 5A2TR, all on s.s.b.

**Philip Lawson** (Derby), has an Ekco domestic receiver and sends in a long log bearing evidence of high Eu activity on 80 with the majority of stations at S8-9, so there's plenty of stations on the band.

**John Moore** (Leicester), hasn't done too well on topband mainly due to high noise level with similar remarks for 80, although he did log XE1KB at 0615 and says that W's are beginning to show on 75 metres around this time.

Higher up on good old 20 the stalwarts managed to pull in some good DX sigs even with the band closing in the evenings.

**Trevor Rumble** (Wilts.), has an HA700 plus PR30X and a 100ft. long wire. Twenty s.s.b. between 0720 and 0755 produced some good openings to Australia and stations logged included—VK2ID, VK3MO, VK3RZ, VK3UJ, VK5AX, VK6FB, VK7PR and ZL4BX at 5 and 9 plus 10dB.

Fifteen metres was the band for **Stephen Randall** (London), whose 9R59DE and 110ft. long wire produced r.f. music from s.s.b. types like—CR6LVC, CT1BF, CX2SA, EA3RF, EP2CB, JA2JAW, JA9AGP, JH1ODO, KP4AST, KZ5IT, LA7XM, TZ5CJT, VE3OSC, VU1FA, VK2ZQ, VK7AZ, VP2ME, WA9NSR/P1, YV4UA, 4X4FQ, 4Z4HF, 5A2AAF.

**Glyn Richards** (Isle of Wight), is still the only 2-metre fan who writes in. What about it, all you v.h.f. types? Glyn runs a JXK converter into a Mohican receiver used as an i.f. strip. Although his antenna is only 6ft. of wire, still the signals come in on 2. Examples include—G3CLW (Paignton) and G3MCS (Aylesbury), F5NS (near Normandy) and G3GZJ (Redruth), the latter station being some 120 miles away.


On to the top of the pops for this month, the one and only—10 metres. **John Moore** (see earlier) logged these on s.s.b.—CR6AG, CR6GM, CR6LF, CR7LX, DUIFH, ET3USA, HK4DF, K8YBU, KØSFU, KP4DGX, LU3DD, LU4BH, MP4BHC, MP4BHR, OD5BA, OD5BZ, PY2DVH, UA9TT, VE2DHF/P/YV1, VE3CI/W4, VE3ABS, VP5AA (Caicos Is.), VP8KD, VP8KL, VQ8CV (Mauritius), VS6DR, VU2DK, VU2XX, VU2BEO, W2CRW, W4IQS, WA5SDT, WA8SWV, WØIMC, XW8AL, YV4UA, YV5CIL, ZC4AK, ZE1BP, ZE1JE, ZE3JJ, ZE6JN, ZS2GP, ZS4AA, 4X4UF, 4X4YP, 5H3KJ, 5H3LV, 5N2AAF, 8P6CX, 9J2DT, 9J2VX.

**Nicholas Richardson** (Bucks), has a CR70A and PR30. Together with a 40ft. long wire at 18ft. they produced—CT1OF, K8ASM, KV4AD, OD5RZ, PY1MT, PY3GS, UA3NUE, VE2AIH, VE3WY, YV5BX, ZE1CE, 5B4EZ all on s.s.b.

On a.m., Nicholas managed—CE2JA, CR7FM, LU5XE, SV1CX, UA3AFA, UA6OJ, UA6ARA, UB5FAQ, WB4KJF, ZE1BR, 9H1BG which is pretty good going.

**Ian Wadman** (Berks) reckons that the JGD ear-holes should be alert on 10 metres on Sunday afternoons. Ian sends news of great activity around this part of the day. Ian logged CR7EZ, K4BG, OD5BZ, UW4II, ZE1JE, 4X4GB, 5N2AAF. All these with a CR70A and 70ft. long wire.

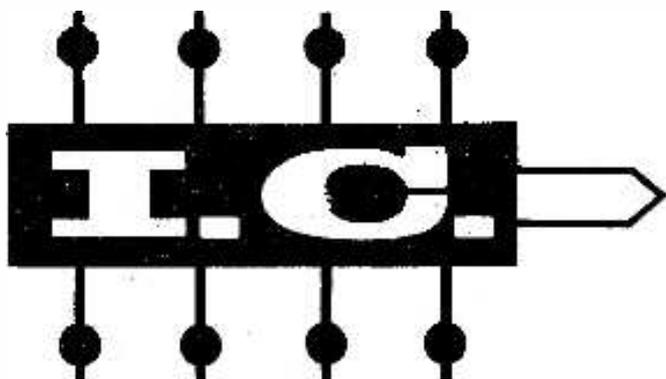That's it for this year! Vy Mx OM's es bcnu in 1970. Address for logs is 5 Edward Close, St. Albans, Herts, and the deadline is that they must reach me by the 18th of the month.



# OF THE MONTH

L.A.J. IRELAND

Number 3

The PA424 and PA436, power control circuits

ANY definition of electronics today would have to include among its applications not only computation and communications, but also control circuits. More and more mechanical and even electromechanical control systems are being replaced by all-electronic methods, and this month we shall see the initial contribution of integrated circuits to this process. The key device in the development of electronic control circuits is, of course, the silicon controlled rectifier (S.C.R.) in which the device operates as a diode only when a pulse is applied to a gate electrode. Following this event, the device conducts only as long as the voltage applied to it retains its proper polarity. In a.c. circuits, therefore, a separate pulse is required to initiate conduction in each cycle.

For full wave operation, two S.C.R.s are required, though these may take the form of a single bidirectional silicon controlled switch or TRIAC. To maintain conduction in a TRIAC 100 pulses per second are required, one to initiate conduction in each positive and negative-going half-cycle of the waveform. If these pulses are applied simultaneously with the beginning of each half-cycle of an a.c. waveform, the device behaves as a short-circuit, and current flows in exactly the same way as if the device were absent from the circuit.

If, however, the pulse is delayed relative to the start of the half-cycle, no current will flow in the interval, and the total power delivered to the load will be reduced by an amount dependent on the extent of the delay. Obviously, then, if a control system delays or eliminates pulses from the gate circuit of an S.C.R. or TRIAC, the output power is dependent on the control system. And this is where our I.C.s come in.

Many situations requiring power control can be sensed or measured electronically, for example temperature by a thermistor, illumination by a photoconductor, or even pressure by a strain gauge. Control is then exercised by relating transducer output to timing pulses in a TRIAC gate, limiting the power supplied to a heater, lamp, or pump. Two suitable I.C.s for the job are the General Electric types PA424 and PA436.

First the PA424. This unit is described as a zero voltage switch, and acts as a combined threshold detector and pulse generator. The signal from the transducer is compared with a preset internal voltage using the differential amplifier Tr1 and Tr2. If the threshold is not exceeded, pulses are generated and applied to the TRIAC; otherwise pulses are inhi-

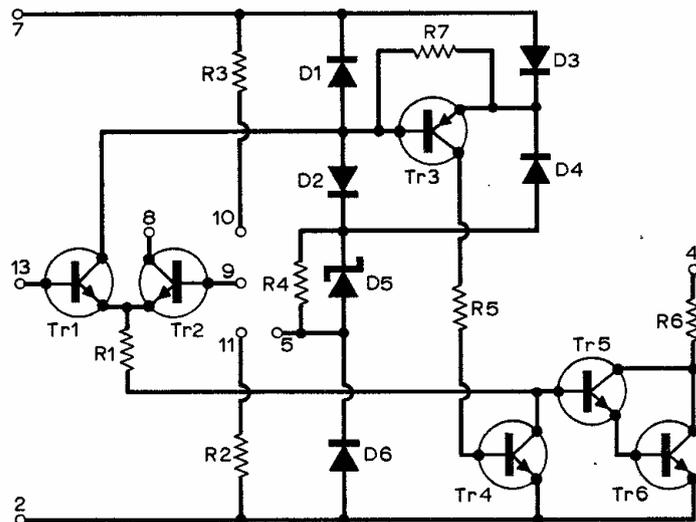


Fig. 1: Circuit of the PA424 'zero voltage switch'. The device is supplied in a 14-lead dual in-line plastic package.

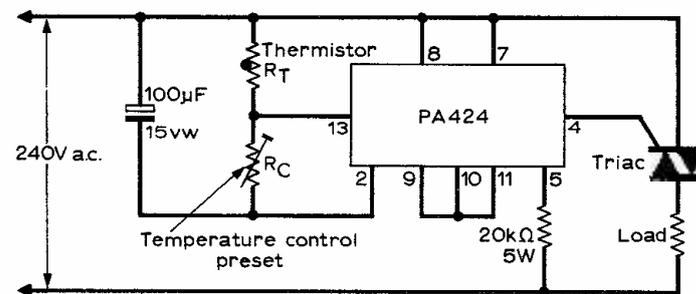


Fig. 2: Application circuit for the PA424.  $R_T$  is the thermistor and  $R_C$  the temperature control preset.

bited and the TRIAC will not conduct. This circuit, then, acts as a go/no go control; to some extent this is a limitation, in that the circuit controlled is either fully on or shut off.

In practice this is only a slight problem, since in heating systems, for example, the sensitivity of a thermistor/PA424 combination is such that the temperature is held to within a fraction of a degree of the chosen value by the automatic succession of periods off and at full power. Further, as all the pulses occur at the instant of crossover between positive and negative-going half-cycle of the waveform. (hence the name "zero voltage switch") there is no question of repetitive switching of appreciable currents, a factor which can produce r.f. interference in some power control circuits.

One obvious advantage of the PA424 is that it serves as its own d.c. power supply; the application

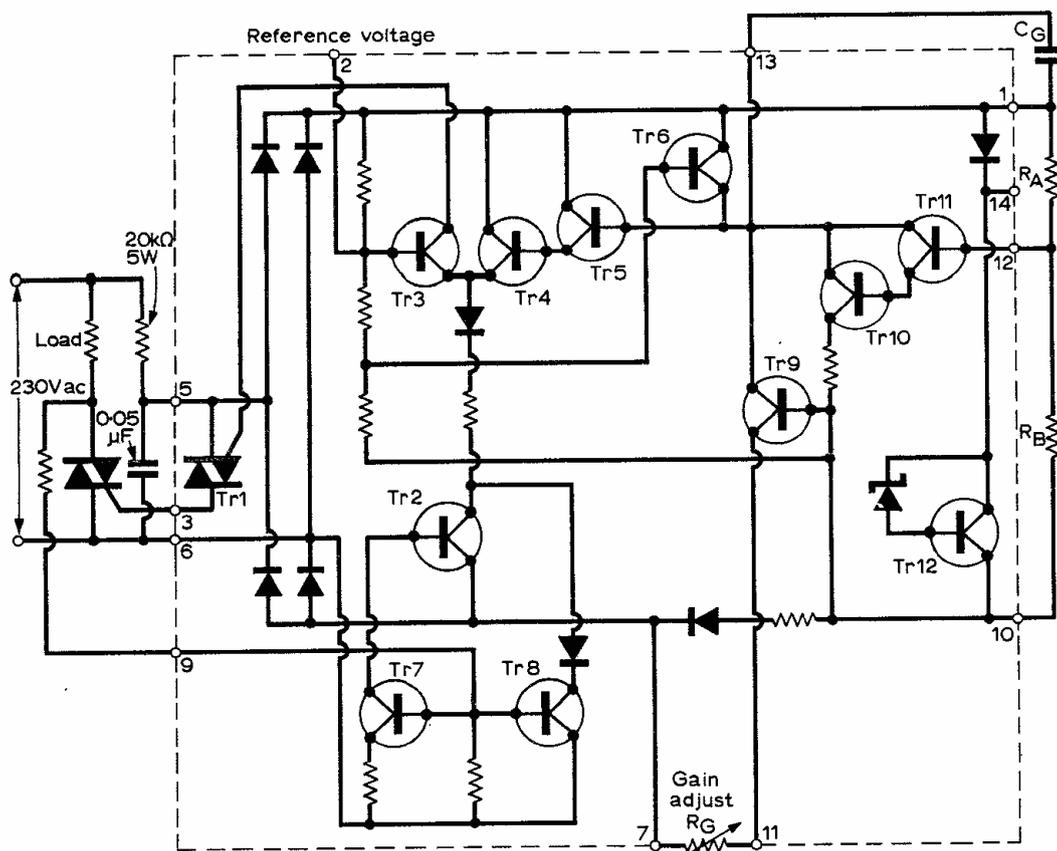


Fig. 3: Application circuit for the PA436, phase control trigger circuit.

diagram shows it in operation directly off the power line without a separate transformer. This is an obvious contribution to economy. In a negative-going half-cycle D1 conducts, charging C1, which supplies d.c. for the remainder of the cycle. As pin 5 approaches zero volts, the output Darlington pair, Tr5 and Tr6 begin to conduct, thereby applying a pulse to the TRIAC gate, unless Tr1 happens to be conducting. In this case, Tr3 is also conducting, and Tr4 saturates, shunting the base input to Tr5 and inhibiting the pulse. The internal resistors R2 and R3 are available as one arm of a bridge circuit, the other being the thermistor (in heating applications) and a preset potentiometer. The ingenuity of the reader will indicate analogous transducer circuits for the control of other systems, such as those already mentioned.

The other device for our consideration this month is an actual phase controlling trigger circuit. It actually delays the triggering pulses required by the TRIAC to the extent determined by the transducers employed, and in some cases this feature is well worth the slightly higher price. Again, the power for the operation of the circuit comes directly from the mains, and a minimum of external components leads to further convenience and economy. The d.c. from the internal bridge rectifier is regulated by a zener diode and a reference voltage produced at pin 2. As in the PA424 there is a differential amplifier (here Tr3 and Tr4) to compare reference and transducer levels and hence control the pulse output.

One of these is modulated with a time-dependent voltage built-up across the external timing capacitor, and hence the variable delay in pulse generation. The rate of variation of this time-dependent modulation depends on Rg, which therefore acts as a sensitivity control for the system. The actual output pulse is obtained by discharge of the external capacitor C1 through a low current, low voltage TRIAC, Tr1, integrated into the PA436.

Choice of which I.C. to use in any particular situation requires some consideration. In heating circuits, for example, it will not be immediately obvious whether the element is conducting at any instant, provided overall thermal regulation is satisfactory. With lighting, we are all aware that the action of the a.c. mains in incandescent lamps provides quite a satisfactory light, and there is no objectionable flickering; however, this can occur under certain conditions with a PA424 controlled lamp, as the I.C. causes "off" periods much longer than the normal a.c. cycle. Similar considerations lead to the selection of the PA436 true proportional controller in a few other specialised situations, but in general the PA424 is advised, for its greater

#### APPLICATION DATA, TYPE PA436

	Minimum	Maximum
External gain controls R <sub>G</sub>	7.5kΩ	100kΩ
C <sub>G</sub>	0.01 μF	0.1 μF
R <sub>A</sub> +R <sub>B</sub>	10kΩ	200kΩ

R<sub>A</sub> and R<sub>B</sub>: external control resistors (one may be a transducer, e.g. thermistor, photocell, resistive vacuum gauge etc.).

For temperature control systems R<sub>A</sub> is a thermistor of resistance about 5kΩ at the controlled temperature; R<sub>B</sub> is a preset of 20kΩ.

The integrated circuits PA424 and PA436 are available from:

Jermyn Industries, Vestry Estate, Sevenoaks, Kent; or Neltronic Ltd., 14 Wellington Park, Belfast BT9 6DJ.

simplicity and economy, not to mention its "cleaner" r.f.i.-free operation. At any rate, control systems will become much more elegant with the elimination of slow bulky relays, with the associated difficulties of burnt contacts and general unreliability.

**N.B.** Just before going to press we have learnt from the suppliers of the PA436 that problems in manufacture have led to a temporary withdrawal of stocks. Newer versions using the same type number will be available in a few months but these are only capable of handling 150mA instead of 2A. Constructors should take careful note of the instructions supplied with this device which may modify certain parts of the above article. ■

#### BLUEPRINT SERVICE

We would like to draw readers' attention to the fact that the BLUEPRINT SERVICE has been discontinued and therefore no further BLUEPRINTS are available.

# beginner's

## PORTABLE RECEIVER

C. R. BRADLEY

ALMOST all radio constructors have memories of unsuccessful first attempts. Beginners are faced with a wide selection of designs and often make the mistake of choosing one that is too advanced for their nascent capabilities, or alternatively, one whose extreme simplicity leads to a disappointing performance. This portable radio design is intended for the beginner and aims to fulfil the following requirements:

1. The circuit must be straightforward and trouble

free. The radio is a six transistor superhet on conventional lines.

2. Performance must be good enough to repay the builder's efforts. In fact, performance of the radio is comparable with commercial portables. Alloy diffused transistors provide high gain in the mixer and i.f. stages, and the audio quality from the transformerless complementary output stage is especially good. No external aerial or earth is required.

3. All components must be immediately obtainable so that there will be no necessity to choose substitutes. To this end a matched kit of miniature coils and tuning capacitor is specified in the parts list. A packaged set of matched semiconductors is used for the audio stage. The remaining components are easily found, everything is available from advertisers in PRACTICAL WIRELESS.

4. Construction must be simple. The circuit is wired on a small piece of Veroboard using a suitable miniature soldering iron. There is a good prospect of the radio working "first try" provided normal precautions are taken in construction, i.e., insulated sleeving used where required to avoid shorts between closely mounted components, and correct identification of transistor, diode and electrolytic capacitor leads.

### The Circuit

The circuit is shown in Fig. 1. The ferrite bar aerial L1 is tuned to the desired station by VC1 and

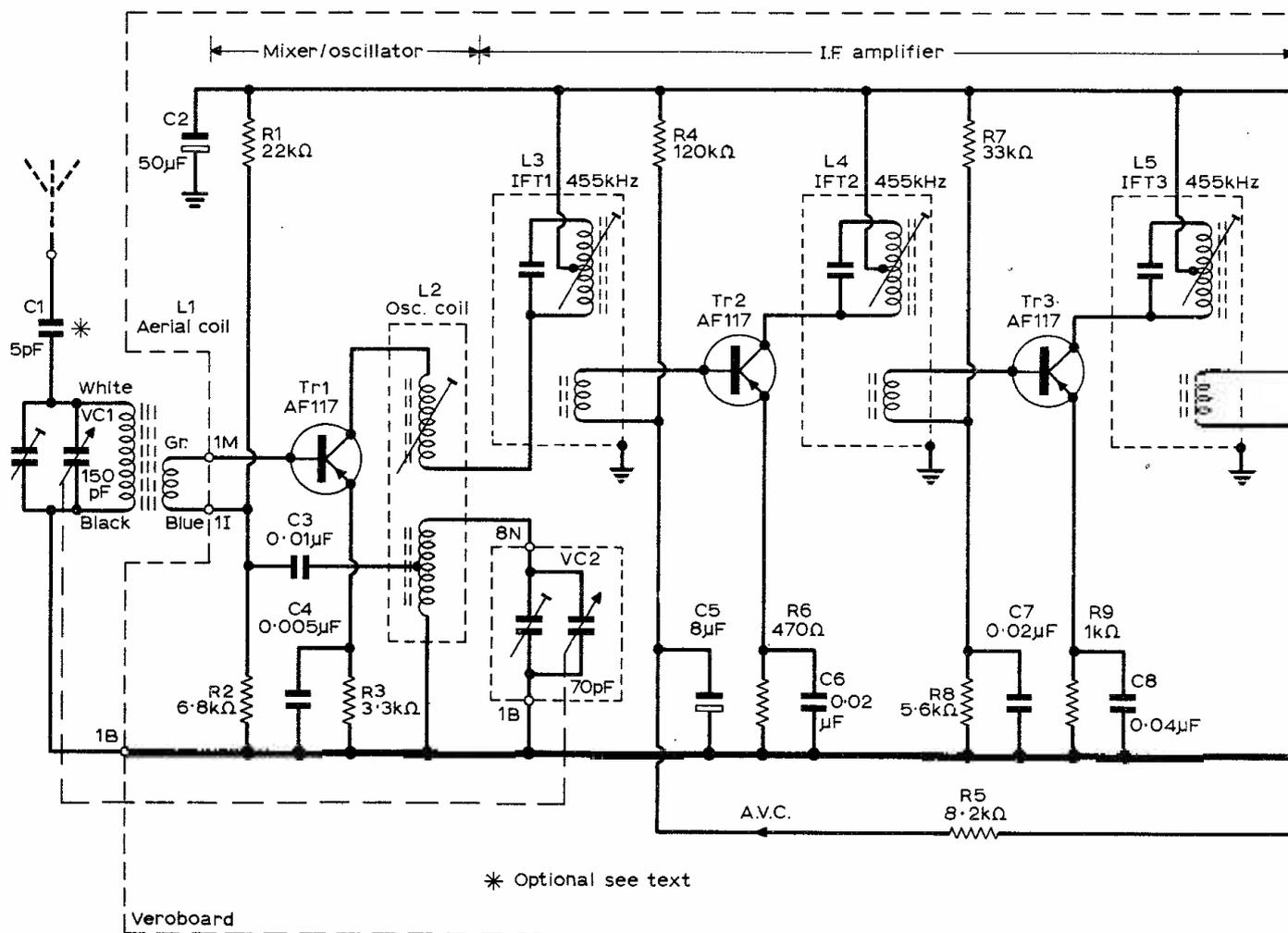


Fig. 1: The mixer/oscillator and i.f. stages, followed by the detector and audio stages. Note that the value of C6 should

# ★ components list

## Resistors:

R1	22kΩ	R10	2.2kΩ
R2	6.8kΩ	R11	1.2kΩ
R3	3.3kΩ	R12	100Ω
R4	120kΩ	R13	560Ω
R5	8.2kΩ	R14	2.2Ω 5% ¼W
R6	470Ω	R15	2.2Ω 5% ¼W
R7	33kΩ	R16	1kΩ
R8	5.6kΩ	R17	2.2kΩ
R9	1kΩ	R18	220Ω

VR1 5kΩ volume control with switch  
 VR2 10kΩ miniature skeleton potentiometer  
 All resistors ¼W 10% unless indicated

## Capacitors:

C1	5pF ceramic (optional)
C2	50μF 10V electrolytic
C3	0.01μF (10,000pF) ceramic
C4	0.005μF (5,000pF) ceramic
C5	8μF 6V electrolytic
C6	0.05μF (50,000pF) ceramic or paper
C7	0.02μF (20,000pF) ceramic
C8	0.04μF (40,000pF) ceramic or paper
C9	0.01μF (10,000pF) ceramic
C10	50μF 6V electrolytic
C11	100μF 6V electrolytic

C12	25μF 6V electrolytic
C13	500μF 6V electrolytic
C14	200μF 10V electrolytic


## Semiconductors:

Tr1–Tr3	AF117	
Tr4	AC113	} Thorn LP15 package
Tr5	AC154	
Tr6	AC157	
D2	AA120	
D1	Germanium detector diode, e.g.: OA70, OA79, OA81, OA90, OA91, IN60 etc.	

## Miscellaneous:

S1	Single pole on/off switch (on VR1)
VC1/VC2	Miniature 150/70pF ganged tuning capacitor with trimmers and dial
L1	MW ferrite aerial coil
L2	Oscillator coil "O"
L3	I.F.T.1 "A"
L4	I.F.T.2 "B"
L5	I.F.T.3 "C"
L/S	3Ω 7 x 4in. loudspeaker; B1 PP7 or PP9 9V battery; Veroboard 3½ x 2½in. 0.15in. matrix; knob for volume control; cabinet; battery clips; loudspeaker grille cloth; wire; solder, etc.

Eagle  
H.402  
coil kit

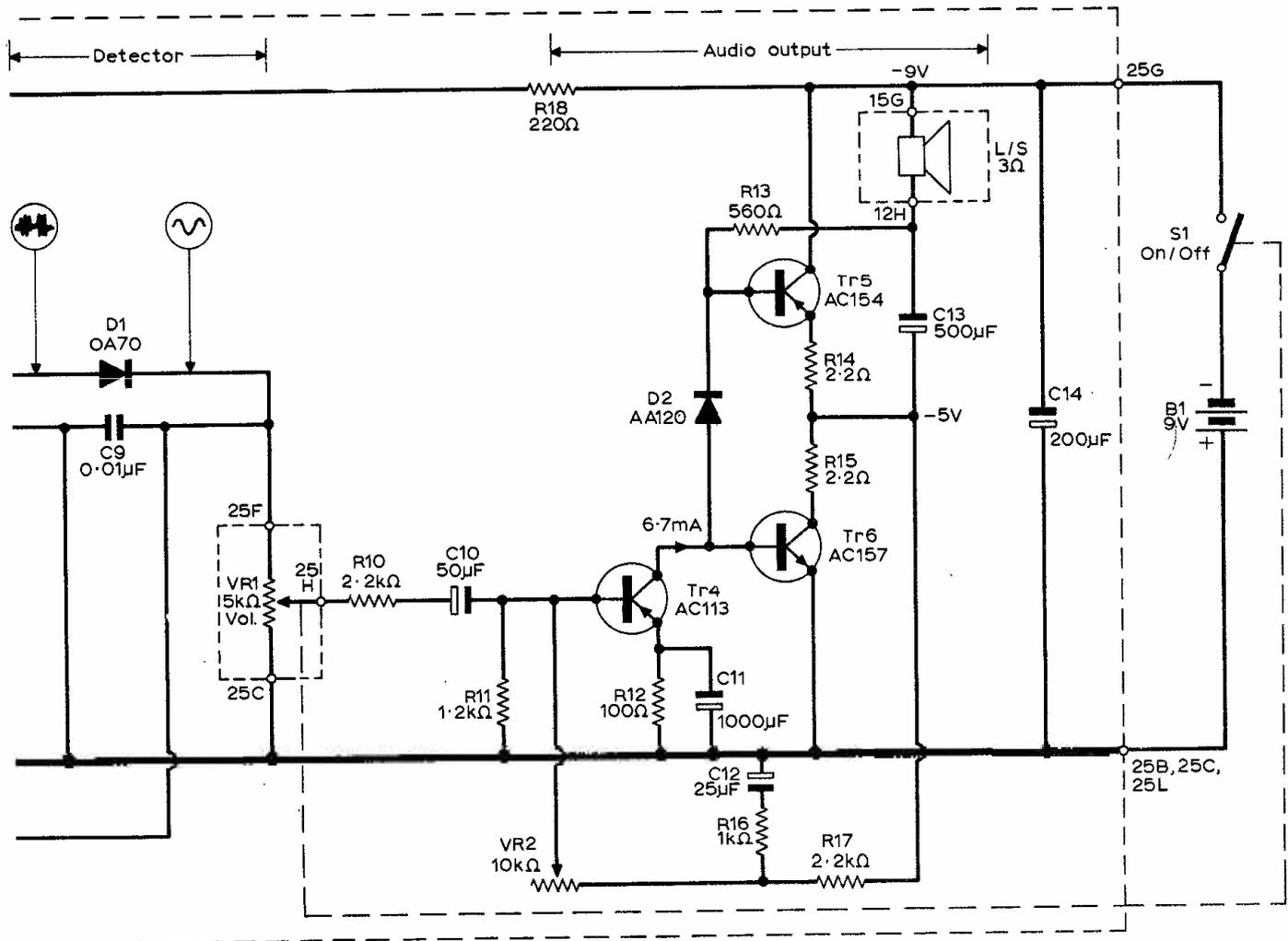

have been shown as 0.05μF and C11 as 100μF. The Veroboard circuitry is indicated by the dotted enclosure.

the radio frequency signals induced in it are fed to the base of Tr1. Base bias current for Tr1 is provided by R1 and R2. C3 couples Tr1 base to a tapping on the oscillator coil L2, and Tr1 therefore oscillates at a frequency tuned by VC2. The radio frequency is mixed with the oscillation frequency in Tr1 to produce a difference frequency known as the intermediate frequency. VC1 and VC2 are ganged together to maintain a constant i.f. (about 455kHz) as VC1 is tuned over the whole tuning range (medium waveband). The importance of this is that subsequent stages can be tuned by their coupling transformers for maximum gain at one frequency only. Tr2 and Tr3 amplify the i.f. signal and are coupled by single tuned i.f. transformers i.f.t.1, i.f.t.2 and i.f.t.3. The AF117 transistor used for Tr1, Tr2 and Tr3 is an alloy diffused type with a low feedback capacitance (2-3pF). We can therefore dispense with the neutralisation components normally needed to maintain stability with the OC44/OC45 junction type transistors which have a higher internal capacitance, and have a higher i.f. gain.

The amplified i.f. signal appears at i.f.t.3 secondary. It is rectified and smoothed by D1 and C9 to isolate (detect) the audio envelope—see waveforms in Fig. 1. A portion of the audio signal is picked off by R5 and fully smoothed by C5 to provide automatic volume control to Tr2 base. If a strong signal is tuned in, the resulting positive a.v.c. voltage returned to Tr2 base reduces the transistor's gain and overloading of subsequent stages is avoided. The a.v.c. compensates to some extent for fading signals and the signal variation caused by moving the radio from place to place. When a weak station is received, there is no a.v.c. feedback and all stages work at full gain.

The audio signal is applied across volume control VR1 whose slider feeds audio driver transistor Tr4. The amplified signal at Tr4 is direct coupled to the base of complementary symmetry output pair Tr5/Tr6. The voltage drop across D2 is fairly independent of battery voltage and maintains the small no-

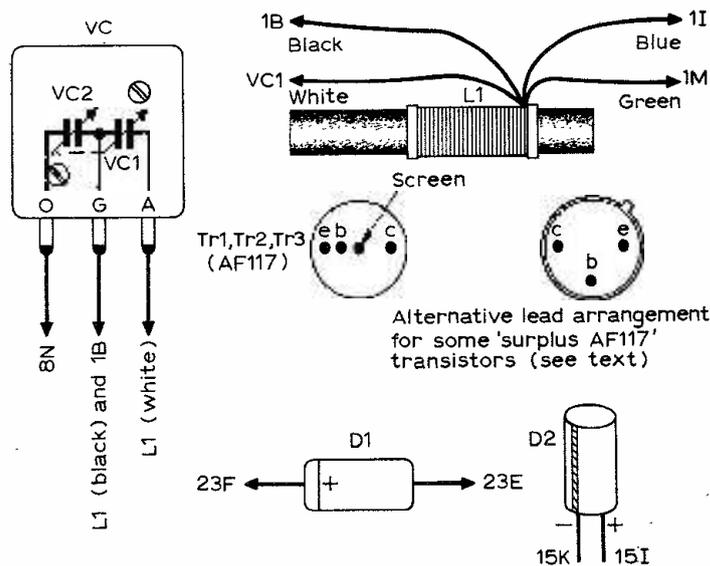


Fig. 3: Lead identification of various components.

signal bias current to Tr5/Tr6 needed for minimum distortion. Tr6 (n-p-n) and Tr5 (p-n-p) are turned on by positive and negative voltage swings respectively. The transistors drive the loudspeaker in push-pull; each supplies current alternately through C13. This arrangement provides a very low output impedance which permits the circuit to drive the speaker directly without an output transformer. D.C. feedback for stability and a.c. feedback for improved audio quality are provided by R17 and VR2. VR2 is preset to give a no-signal voltage of  $-5V$  at the junction of R14 and R15.

The audio output power is about  $\frac{1}{2}$  watt. With a  $7 \times 4$  in. or larger loudspeaker, volume and clarity are more than ample. The radio is best built in a non-miniature cabinet for best audio quality. But the circuit board is small enough to be incorporated in a pocket size radio in which case a 2 in. loudspeaker could be used.


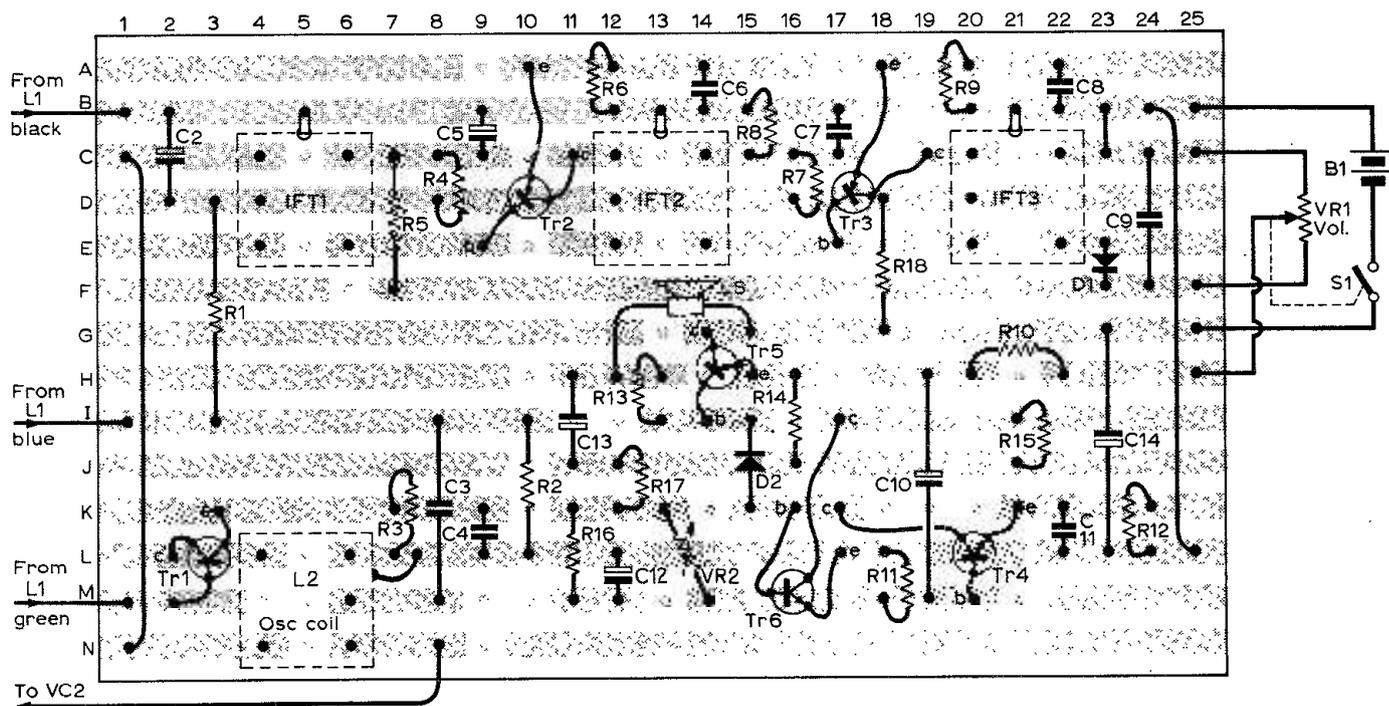


Fig. 2: Veroboard layout viewed from the copper side.
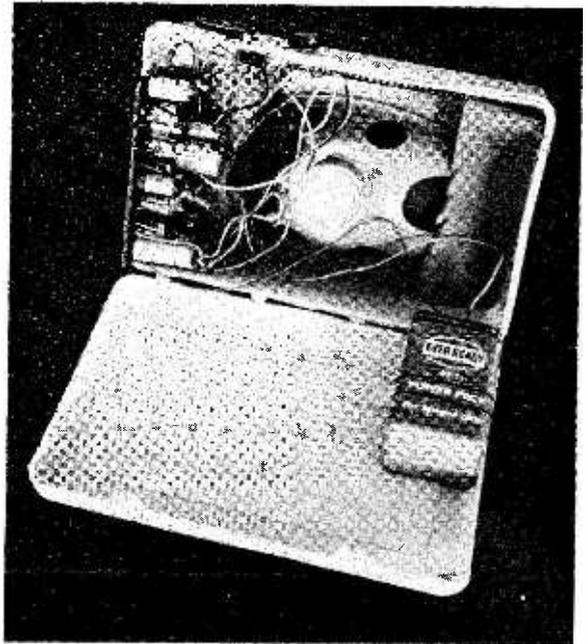
## Construction

The components are wired on a standard piece of Veroboard and the layout is given in Fig. 2. The numbers and letters provide a cross-reference for each hole. The top and bottom copper strips (unlettered) are left unused for possible use in mounting the Veroboard in the cabinet.

First cut the Veroboard strips as shown, preferably with the Vero cutting tool. There are 36 breaks in all. It is advisable to mark (say) the top left-hand corner of the board before starting for identification. Wiring is easier if the positions of the components are sketched on the top of the board with a fibre-tip pen. Identify the three i.f.t.s ("A", "B", "C") and oscillator coil L2 ("O") in the coil kit. Bend up the screening can lugs. With slight persuasion the coil pins will make a neat fit in the Veroboard holes in the positions shown in Fig. 2. Solder them in place. It may be noticed that the left-hand pair of pins on the oscillator coil L2 in Fig. 2 are connected oppositely to the manufacturer's data with the coil kit. The author has decided the data is incorrect as the stage will only oscillate with this way of connection, with the coils sampled at least. However, if the mixer subsequently refuses to oscillate, it is easy to try swapping the connections at 2L and 1N to agree with the manufacturer's data. Short pieces of wire are used to earth the screening cans of L2, i.f.t.1, i.f.t.2 and i.f.t.3 to holes 8L, 5B, 13B and 21B respectively. Resistors and capacitors are next mounted with the shortest possible lead lengths, mostly upright. Put a piece of plastic sleeving on the lead from the top of each component wherever there is any danger of it touching any adjacent metal. This is particularly likely if bare metal-cased electrolytic capacitors are used. Electrolytic capacitors must be wired the right way round, i.e., positive lead to earth (except C10 and C13). Finally, solder the diodes and transistors to the board, making sure the leads are identified correctly from Fig. 3. Note that the lead identification of D2 can be misleading. Some surplus transistors marked AF117 were tried by the author and worked satisfactorily; however the lead arrangement was non-standard for AF117 (see Fig. 3) and they



Internal view of the completed receiver.

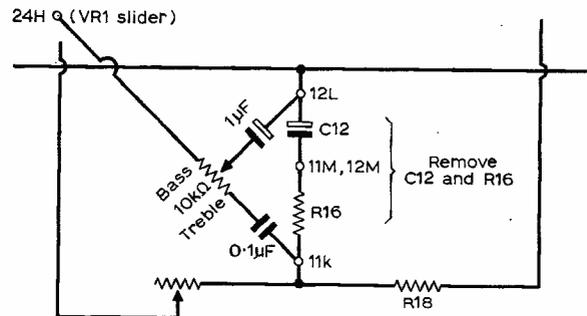


Fig. 5: Adding a bass/treble tone control.

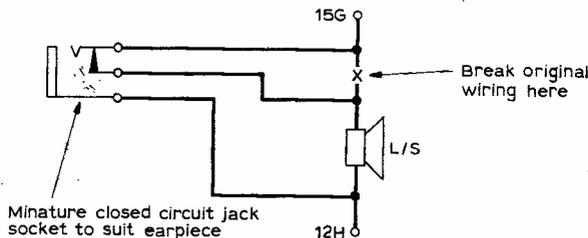


Fig. 4: Adding a socket for a low impedance magnetic earpiece.

had no screen lead. The screen lead of the AF117 has little use at the frequencies used here and can be cut short or connected to the nearest earth point as preferred. Leave about  $\frac{1}{2}$  inch of sleeved lead on all transistors and diodes and solder as quickly as possible to avoid heat damage.

The cabinet for the author's prototype was a Woolworth's plastic lunch box. The top of the box carries the tuning capacitor, volume control VR1 and

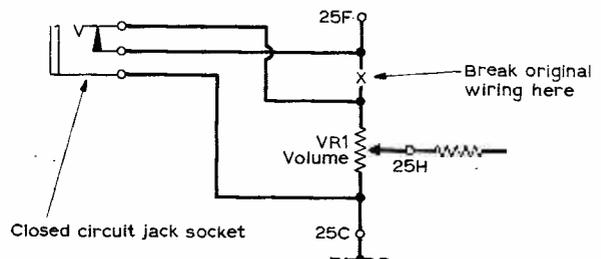


Fig. 6: Adding a socket for microphone, guitar, record player etc.

the ferrite aerial is taped underneath. The calibrated knob supplied with VC is rather small and a larger disc of plastic glued to it would make tuning easier. The  $7 \times 4$  in. loudspeaker is mounted in the side of the box and the aperture is covered with Tygan speaker fret. The largest 9 volt battery the cabinet

—continued on page 706

# practically wireless

commentary by **HENRY**

Spin-off

SIX hundred million people, we are told, watched Neil Armstrong plant his foot in the moondust on 20th July, 1969—the day that President Nixon, begging a few questions, described as ‘... the greatest since Creation’.

You have had time to simmer down since then; to consider the equally stupendous achievement of discovering that Mars has no little green men paddling along its canals. And perhaps join a disgruntled chorus who were muttering, even as the Eagle took flight, that the 24,000,000,000 dollars might have been better spent on child welfare, cures for cancer or ear-muffs for under-privileged ocelots.



“... ear-muffs for under-privileged ocelots.”

In answer to these mutterings the science-bent will usually say something about the spin-off. Non-stick aluminium frying pans often find their way into the conversation.

“And it took 300,000 technicians eight years to produce a non-stick pan?” someone is bound to ask.

Well, there is more to it than that. Many of the technical innovations creeping into our lives had their origins in space research.

You need look no farther than

the flip-chips that are occupying our editorial wizards at present. How do you think contributors could continue to dream up ten different ways of constructing an electronic shoehorn\* † without integrated circuits to save them from repetitions? Only recently I sat in a high-level quorum who wanted to know how the advent of IC designs would affect serviceability. And had to admit that my own opinion was for a shift in emphasis, no more. I cannot see the spin-off as a threat—yet.

There is, however, a much more human type of spin-off problem. Inspiration was drawn from a very readable book, *Don't Launch him, he's mine!* by Mary Jane Chambers, who is the wife (or space-widow) of one of the boffins behind the Apollo project.

Randall Chambers is an experimental psychologist whose work on the centrifuge which gave the astronauts their moon-legs has earned him world scientific recognition. Mary Jane describes life with him very amusingly and touches Henry on several risible trigger-points.

First, his “study”, which seems as typical as the den of any wireless ham I've met. Looking like “a library recently wrecked by an explosion”, it houses “piles of graphs, notes, charts of atmospheric measures and weights and measures and maps of many places, including outer space. There are railway timetables, old telephone books, a sterilizer with an assortment of old surgical instruments... an assortment of synthetic hearts, brains, ears, skulls. Overlooking all, a huge model of the human eye, staring balefully at the casual visitors”.

More than ever am I reminded of life with the Henrys by Mrs. Chambers' account of the day the children knocked the extractor fan out of the window. There were present: an aeronautical engineer, a project engineer, a mechanical engineer and a



“... Staring balefully at the casual visitors.”

human factors engineer. “Prodded by several doctors and psychologists, the engineers hesitantly studied the fan, but they made no promises. Each one kept saying: ‘I'm not that kind of engineer’”.

They finally mended it with the help of a flight-surgeon and a research psychologist. That gives you and me, Joe, a fine excuse for the day the ‘fridge breaks down or the washing machine develops a “kerplunk”. We are chips specialists, not *that* kind of engineer.

If only Mrs. Henry, confronted with a scattered square-wave generator on the draining-board—because that is just the right height and the soldering iron lead will reach, and there is a half-drawn “project” on the only flat surface of the den—would realise, as Mary Jane has done, that a male brain runs anti-clockwise...

I hope Mrs. Chambers gets her book serialised in the women's magazines. That would be the best possible spin-off from the space-race. Henry wants to construct a few of these chip-flavoured projects, and the ironing-board seems ideal for the purpose. We boffins need encouragement.


\* *Bootstrapped, of course.*  
† *Ouch!! Ed.*

# LOOK!

## PRACTICAL!

## VISUAL!

## EXCITING!

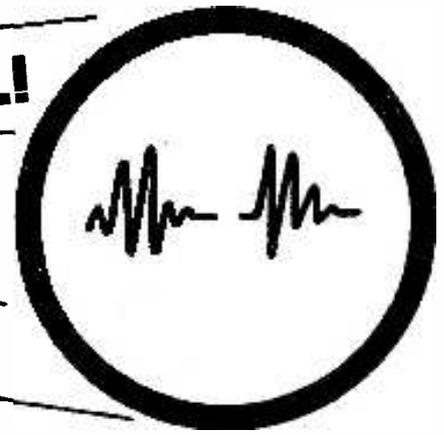

a new 4-way method of mastering


# ELECTRONICS

by doing — and — seeing . . .

### 1
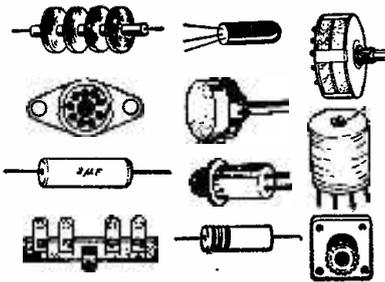
#### OWN and HANDLE a


complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



### 2
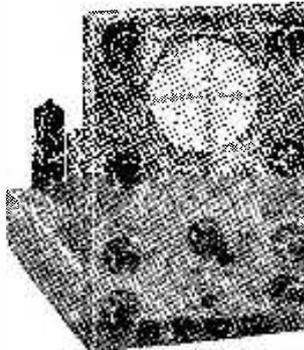
#### BUILD and USE


a modern and professional **CATHODE RAY OSCILLOSCOPE**



### 3

#### READ and DRAW and

#### UNDERSTAND CIRCUIT DIAGRAMS

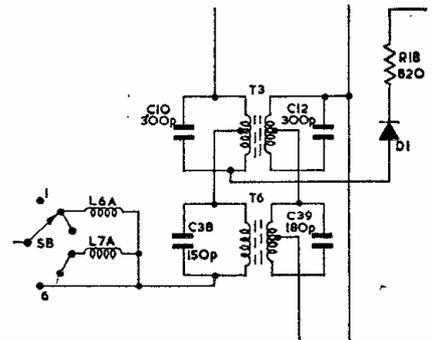

### 4

#### CARRY OUT OVER **40** EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
  - TRANSISTOR EXPERIMENTS
  - AMPLIFIERS
  - OSCILLATORS
  - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
  - COMPUTER CIRCUIT
  - BASIC RADIO RECEIVER
  - ELECTRONIC SWITCH
  - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
  - D.C. EXPERIMENTS
  - SIMPLE COUNTER
  - TIME DELAY CIRCUIT
  - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

## FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW1

# LETTERS

The Editor does not necessarily endorse the views expressed by correspondents

## Martians Again!

Whilst not having heard that Marconi claimed to have received signals from Mars as A. Trowbridge of Middlesex says, I was told many years ago that some person who believed in the existence of men on Mars paid the GPO a sum of money to transmit a certain regular pattern of Morse code signals each day either from Daventry or Rugby, on long waves.

I was told that this went on for quite a time but with no response from the Red Planet.

I would imagine that we shall not hear anything from other planets until we are able to probe frequencies such as those involved in thought-transference and in which extra-sensory perception is only on the extreme outer fringe.

When the thought-transference frequencies are discovered, all will be plain sailing.

In answer to the letter from Mr. Richard Ross of Worcester, I think perhaps he is using a plumber's soldering iron and no heatsink!—**R. Hall** (*Penzance, Cornwall*).

## The Early Days

I would like to comment on two of the letters in the November issue.

As another "oldie" I also remember the early days of wireless. Around 1917 I made an 8in. dia. coil, tapped every turn to a stud switch for tuning, and a coherer as detector, with which I could hear Morse from ships. As I could not read Morse a recorder was made to mark it on paper tape.

The gift of a box camera, loaded in the dark with 12 glass plates, took my interest for some years, but when broadcasting started interest in wireless was revived, and a crystal set was made using the large coil.

The purchase of a valve was a big step, there was not much money to spare in those days. Two tins sliding inside each other made an experimental condenser. A real 0.005 $\mu$ F tuning condenser was the next purchase, and with a few more home-made items mounted on a base-board, and a 3ft. long wooden rod fitted to the

condenser shaft, it was a thrill to hear Sydney, Australia, for the first time.

A fortunate find at a surplus shop in Strutton Ground was a number of fixed condensers made of copper foil and mica sheets clamped between ebonite plates. These could easily be altered to give other capacities. I still have some of the mica.

Then with the arrival in shops of more components, remember Igranic and Telsen etc? a multi-valve receiver was built with elaborate dials and panel of ebonite on an oak case. The loud-speaker was a 6ft. papier-maché exponential horn which was pretty good. Next, to save the space this took up, I made a stretched doped linen cone 2ft. square which hung up like a picture. It was some time before an 8in. permanent-magnet speaker could be bought and mounted in a 3ft. square board as a "fire-screen". That gave beautiful music.

The h.t. battery was made from a lot of little glass pots, copper, zinc and chemicals obtained from a chemist in Charing Cross Road. I was just married then and my wife and I sat for hours packing manganese dioxide in linen bags. The finished battery giving 120 volts was packed in a wooden crate. L.T. was from an accumulator, one in the set and one at the shop being charged. The local electricity station also charged them for you.

Licences at that time were in my father's name as the householder, but I still have one for 1927. On the back are regulations such as "the combined height and length of the aerial shall not exceed 100 feet", "interference is taking place if a...whistle is heard, if this...changes when the wavelength of the receiver is altered the cause is inside the receiver and the reaction must be reduced".

At an early Radio Exhibition I bought "Commander Someone's" aerial device for which marvellous results were claimed. It made no difference in my case so I opened it to find no wonderful new invention, only a coil of wire and a small condenser in a

card tube filled with pitch.

A trick to mystify friends was to wind a certain number of turns of wire around the hand, twist one end to a needle resting on a piece of coal and with headphones hear 2LO. For this you still required a licence!

I have some sub-min diodes in a small tin labelled the "Mighty Atom Crystal", one of the first I bought and mounted in Wood's metal in a brass cup.

No doubt youngsters nowadays get some satisfaction when they put supplied components into holes in a printed-circuit board and it works, but I bet it is not the kind of thrill we got in those early days, and now with cheap i.c.'s. even less is left to the constructor.

The second item I would refer to is the Hertz, a term which I refuse to use, and no one can make me! The good old "cycle per second" is clear and self-sufficient, whether for electrical or mechanical purposes. Imagine, my watch ticks 5Hz. And Hz itself could mean Henry  $\times$  Impedance.

As to the new mains-lead colours, can anyone explain the reasoning behind the decision to use brown for live. Is it not natural to us to connect the colour red with danger, green with safety and black or grey with neutral? Brown has usually been used for things like valve heater supplies. Anything red made one think before touching. Do "they" contemplate changing all the traffic warning signs to brown? Shall we soon hear it referred to as the "Brown Button"?

I could not agree more with Mr. Harold's last paragraph. Trouble is, except in things like using Hz, we do have to acquiesce. Of course, behind the decimal currency there is a well-laid scheme to put prices up and get even more of our money out of us, as well as using our money to effect the change. I feel that in major decisions such as this, and any others which profoundly affect our way of life, there should be a nation-wide referendum. After all, in most of the things being altered, we WERE first.—**E. W. Baigent** (*High Wycombe, Bucks.*).

# CODAR CR.70A

## Communications Receiver 540-10 metres



The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £21 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres, where the rapidly improving conditions that now prevail allow the regular reception of world-wide call-signs!

The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5½" x 7½" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months! New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.


# 20 gns.

Carriage 7/6 extra


- \*Ideal for SWLs \*5 valves (inc. two twin triodes) giving 7 valve line-up
- \*Excellent on amateur and shipping frequencies
- \*Calibrated signal strength meter (illuminated)
- \*Automatic volume control
- \*Separate B.F. oscillator for morse and S.S.B. signals
- \*Two speed vernier tuning
- \*Separate output for recording etc.



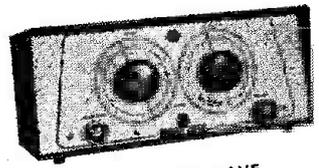**T28 RECEIVER FOR 160 & 80 METRES AMATEUR BANDS**  
9 transistors, bandspread 1.8-2Mc/s and 3.5-4Mc/s 12 volts, only 8" x 4" x 3½", ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £15.17.6. Carr. 4/6.



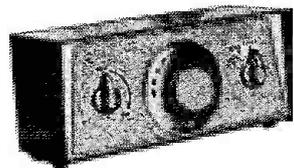**CR45 MAINS T.R.F. SHORT-WAVE RECEIVER**  
World wide reception. \*Separate electrical band-spread. \*3 slow motion drives. \*Output 3 watts for 2/3 ohm speaker. \*Valves ECC81, EL84, EZ80. Size 12" x 5½" x 7". CODAR-KIT CR.45K with 3 coils (10-28, 25-75, 60-176 metres). £9.15.0. Carr. 6/-, or ready built CR.45 £11.19.6. Carr. 6/- Extra coils 5/4 each.



**R.F. PRE-SELECTOR MODEL P.R.30**  
1.5-20Mc/s Provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Power requirements 180-250 volts 12mA H.T. 6.3 volts, 3 amp L.T. Size 8½" x 5" x 4". Ready built complete with cables, plugs and instructions. £5.19.6. Carr. 4/6. Self-powered P.R.30x £7.19.6. Carr. 4/6.



**MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER**  
\*Can be built in one evening. \*Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price £2.4.6. Carr. 3/- Extra coils 5/4.

# CRC

**CODAR RADIO COMPANY**  
UNIT 1, MEADOW ROAD, INDUSTRIAL ESTATE,  
EAST WORTHING, SUSSEX. WORTHING 37315  
World-wide Mail Order Service

Please supply (tick as required)

I enclose cheque/M.O./P.O. value of £.....

8d stamp enclosed for leaflets

NAME .....

ADDRESS .....

**POST ORDER FORM TODAY**

# There's Something for Everyone in the NEW HEATHKIT CATALOGUE!



- GUITAR PRACTICE AMPLIFIER
- ELECTRONIC METRONOME
- AMBASSADOR SPEAKERS
- AUTO-TUNE-UP METER
- AIRCRAFT MONITOR RECEIVER
- CAR RADIO
- TECHNICIANS LOW-COST 'VVM'
- SEVERN AM/FM RADIO
- FABULOUS STEREO HI-FI COMPACTS
- STEREO RECORD PLAYER
- D.I.Y. SPEAKER SETS
- GENERATORS
- POWER SUPPLIES
- D.I.Y. RADIOGRAM PACKS
- MANY OTHER MODELS TOO NUMEROUS TO MENTION

Send for this  
**FREE Catalogue**  
and see for yourself, Today!



DAYSTROM LTD  
GLOUCESTER  
GL2-6EE

TO DAYSTROM LTD, GLOUCESTER GL2-6EE

Please send me my free copy of the 1970 HEATHKIT CATALOGUE

NAME .....

ADDRESS .....

PW-1A

# P.W. GUIDE TO COMPONENTS

## PART 13

M. K. TITMAN, B.Sc. (Eng)

THE number of devices using semiconductor materials to meet specific requirements in electronic circuits is increasing rapidly as research and development continues on an unprecedented scale. The devices examined in this part of the series are the most common and easily obtainable of such devices, but because of the diversity and number of items to be discussed only general practical information has been included. Further detailed information can usually be obtained from manufacturers. Let us now examine the usage, construction, limitations, cost and operation of each type.

### Variable Capacitance Diode or Varactor

The variable capacitance diode, varactor or voltage variable capacitor is a device which behaves essentially as a capacitor and circuit symbols are shown in Fig. 1. The capacitance is however capable of variation by means of a d.c. bias voltage. It is therefore particularly useful for automatic frequency control (a.f.c.), frequency modulation, fine tuning and bandwidth regulation. Varactors are also used for frequency multiplication purposes at microwave frequencies.

Varactors are constructed from single p-n junction semiconductor material and are operated in the reverse—non-conducting—direction, the capacitance being the normal diode junction capacitance. They are thus diodes which utilise normal diode construction—such as the alloy, diffusion or planar processes described in a previous part in this series. The junction size and impurity levels are modified to give the required capacitance values and characteristic. A typical capacitance against reverse voltage characteristic is shown in Fig. 2.

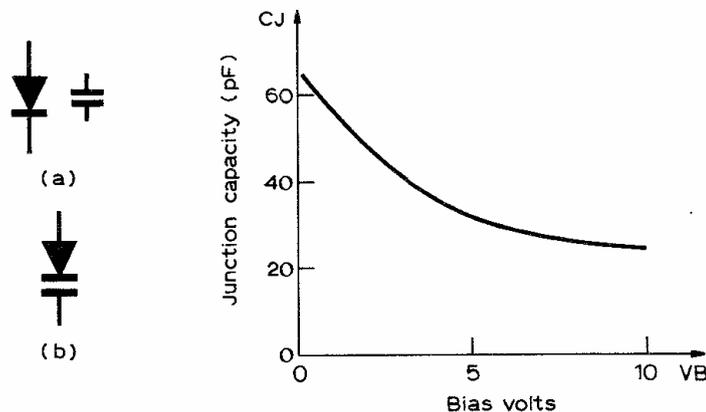


Fig. 1a, b (left): Circuit symbols for a diode used as a variable capacitor or varactor.

Fig. 2 (right): Reverse biased diode capacitance characteristic.

It is worth noting that all semiconductor diodes exhibit a similar characteristic and can therefore be used by the home constructor for applications where variable capacitance diodes are required. However the actual capacitance level differs from diode to diode and for most signal diodes is reduced to a minimum since it is parasitic and determines the upper frequency limit of the diode. Improvisation can nevertheless save time and expense and the home constructor is well advised to try a selection of available diodes for a.f.c. and oscillator tuning applications.

The ideal varactor should have all the characteristics of a capacitor: low leakage, low capacitance tolerance, stability and reliability. The real device closely approaches this ideal except for leakage current which is generally  $0.1\mu\text{A}$ – $10\mu\text{A}$  and is generally higher than all but electrolytic capacitors. Capacitance tolerance varies and is usually  $\pm 10\%$  or  $\pm 20\%$ . Stability and reliability are both good as it is a semiconductor device. The main disadvantage is the requirement for a d.c. bias since they are polarised devices; also the Q factors, which are generally 30–40 for the v.h.f. range low cost units, although Q factors up to 500 can be obtained.

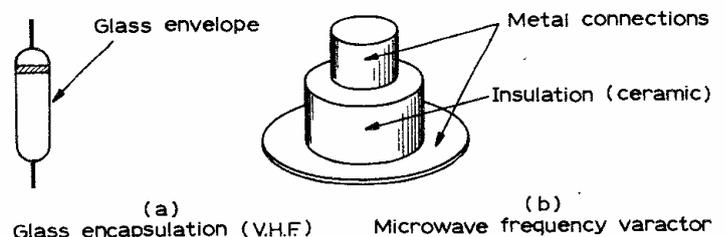


Fig. 3: Varactor encapsulations.


As varactors employ the basic diode structure the encapsulations follow the same pattern. Oscillator trimming and a.f.c. diodes at v.h.f. frequencies, with capacitances of approximately 30pF at 1V reverse, usually employ standard glass encapsulations as shown in Fig. 3(a). Microwave varactors which operate at extremely low capacitance values from 0.1pF to 10pF, with reverse voltages in excess of 50V, utilise special low capacitance encapsulations such as that illustrated in Fig. 3(b). Microwave varactors—which operate in various bands up to 250GHz—frequently operate at higher power levels and consequently have metal encapsulations which directly connect to heatsinks to give increased dissipation.

With all semiconductor devices costs are largely determined by the level of demand and the tolerance ratings and yield of the device. Varactors are no exception and glass encapsulated v.h.f. devices with high


demand levels and low Q factors (10-40) are available from 7s. to 30s. whilst devices with higher Q factors and tuning ranges can cost from £2 to £5. Microwave varactors, particularly power devices, are correspondingly more expensive and cost from £3 to £20 for low power and from £15 upwards for high power types.
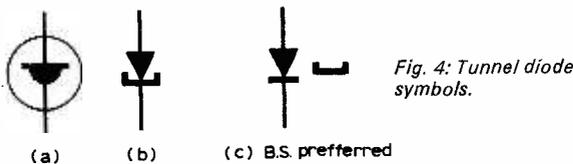
### Tunnel Diode and Backward Diode

Tunnel diodes, like varactors, are two-terminal single-junction devices, but unlike the varactor their action is active in that they are capable of producing power gains despite the two-terminal configuration. They are used as oscillators, amplifiers and switching devices and can be used up to very high frequencies. Indeed tunnel diodes are used in amplifiers operating at 6GHz. They are extremely stable components and crystal controlled transmitters and chronometers use tunnel diodes particularly in frequency division circuits—where three tunnel diodes can give an accurate frequency division of 2,000 to 1. At present the circuit symbol for the tunnel diode has not been standardised and consequently a selection of symbols is shown in Fig. 4, with the B.S. preferred symbol indicated.



A typical tunnel diode characteristic is illustrated in Fig. 5 and this clearly indicates its essentially active mode of operation. The characteristic shows a peak and a valley, and a region between in which the current falls with increase in voltage, indicating a negative resistance and therefore unstable region. Switching action from point A to point B can occur and is used to aid tuned circuits to give gain or oscillations. Following this region the characteristic follows a normal diode characteristic as would be expected from its single p-n junction structure. This curve is shown for comparison.

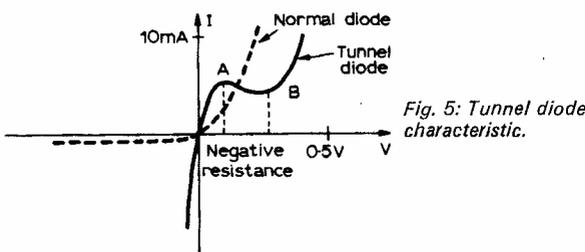

The mechanism which produces the negative resistance region in the characteristic is called the quantum-mechanical tunnelling effect, from which the device takes its name. This rather awe-inspiring terminology

tends to overwhelm the potential user but—although the mechanism is mathematically complicated to prove—this should not be a deterrent to the practical engineer. Suffice it to say that the tunnelling effect causes an increase of current at a definite point in the characteristic by sweeping or tunnelling the electrons across the junction, thus producing the characteristic of Fig. 5. The parameters quoted by manufacturers confine themselves to the characteristic and when considered with the characteristic are relatively self-explanatory. Table 1 shows the parameters with a range of values for typical general-purpose tunnel diodes. Microwave diodes up to 40GHz have negative conductance values of 65-75 mhos  $\times 10^{-3}$  and capacitance values of 0.35-5pF.

Backward diodes are tunnel diodes with current values below 0.5 to 1mA and a consequent negative resistance greater than 1k $\Omega$ . The characteristic is consequently modified and a typical backward diode characteristic is illustrated in Fig. 6. The peak point

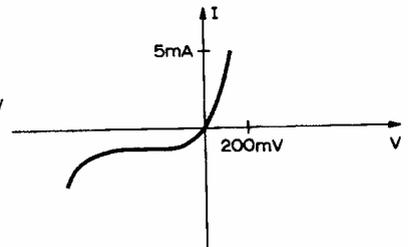


Fig. 6: Backward diode characteristic.

current varies from 0.01 to 1mA with capacitance values of 1-20pF. The characteristic allows the backward diode to be particularly useful as mixer and detector diodes at extremely high frequencies.

Both tunnel and backward diodes, being single p-n junction structures, use normal diode manufacturing techniques. They are manufactured from germanium material with extremely heavily doped, small area junctions. The heavy doping produces the tunnelling effect whilst the small junction area minimises junction capacitance. Due to the extremely high operating frequencies lead inductance is a problem and is reduced to a minimum (0.5nH to 5nH) in diodes operating below 2GHz which use axial or TO-18 packages. Epoxy resin plastic packages are used and have lead inductances of 1-2nH whilst microminiature pill packages having lead inductances of 0.1nH are used for microwave diodes. Some typical encapsulations are illustrated in Fig. 7.

Tunnel diode costs vary considerably but increase

Fig. 7: Tunnel diode encapsulations.

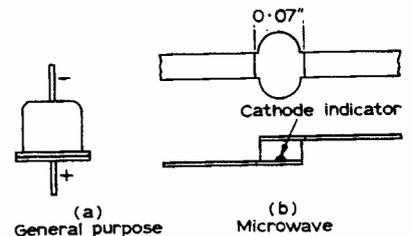


Table 1: General purpose tunnel diode parameters with typical values

Peak point current $I_p$	Max. valley point current $I_v$	Peak voltage $V_p$	Max. series resistance $R_s$	Capacitance $C$	Negative conductance $G$	Cut off frequency from
1-25mA	0.5-5mA	50-60mV	1-10 $\Omega$	5-150pF	4-200mhos $\times 10^{-3}$	1-4GHz

# INCREASE YOUR KNOWLEDGE



## RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES


**MANY COURSES TO CHOOSE FROM incl.**  
RADIO & TV ENGINEERING & SERVICING,  
TRANSISTOR & PRINTED CIRCUIT SERVICING,  
CLOSED CIRCUIT TV, ELECTRONICS,  
NUMERICAL CONTROL ELECTRONICS,  
TELEMETRY TECHNIQUES, SERVOMECHANISMS  
PRINCIPLES OF AUTOMATION,  
COMPUTERS, ETC.

### ALSO EXAMINATION COURSES FOR

C. & G. Telecommunication Technicians' Certs  
C. & G. Electronic Servicing  
R.T.E.B. Radio/TV Servicing Certificate  
P.M.G. Certificates in Radiotelegraphy  
Radio Amateurs' Examination  
General Certificate of Education, etc
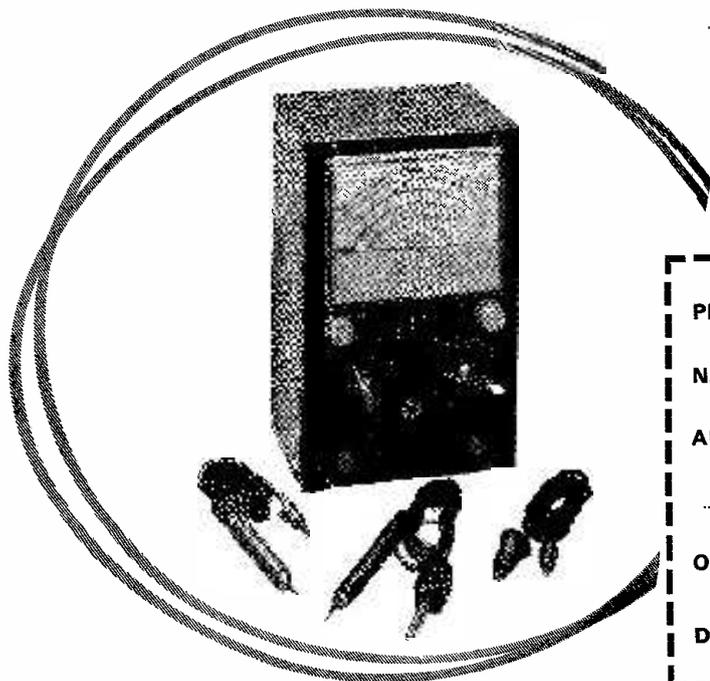
### BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments, incl. professional-type valve volt meter (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



## THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

### FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME .....

ADDRESS .....

.....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. 170, INTERTEXT HOUSE, PARKGATE ROAD, London, SW11  
1/70

# 4! brings you a mountain of components at manufacturers' prices

The serious amateur should never be without this comprehensive price list and guide to semiconductors and electronic components from RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold and others (together with manufacturers' application data) which you can buy direct from us at manufacturers' prices e.g. IN914 1/3d.

- IN916 1/11d. □ 2N697 4/5d. □ 2N706 2/3d. □ 2N706A 2/9d. □ 2N929 5/8d.
- 2N1613 4/8d. □ 2N3011 9/1d. □ 2N3053 6/2d. □ 2N3055 15/9d. □ 3N140 15/3d. □ BFY50 4/8d. □ BFY51 3/9d. □ BSY27 18/-
- BSY95A 3/3d. □ C407 4/6d. □ CA3012 18/3d. □ CA3014 25/6d. □ CA3020 25/9d. □ OA200 1/9d. □ OA202 1/11d.



## Build the NEW Mainline Audio Amplifier kits - UP TO 70 WATTS

The result of the combined resources of SGS and RCA, these quasi circuits set new standards in quality and performance. Each kit is complete with circuit diagram, all semiconductors, resistors, capacitors and printed circuit board.

<b>12A</b> .....	<b>£7. 0. 0.</b>
<b>25A</b> .....	<b>£8. 5. 0.</b>
<b>40A</b> .....	<b>£9. 0. 0.</b>
<b>70A</b> .....	<b>£10.10. 0.</b>

Any two will make an outstanding stereo equipment.



To: Mainline Electronics Limited, Thames Avenue, Windsor, Berkshire

I enclose 4/-. Please send me your price list and guide

I am interested in ..... Amp Mainline Audio Amplifier Kits. Please send me full data

I am interested in receiving data on preamplifier & power supply kits

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_

(A member of the ECS Group of Companies) PW170

rapidly in the regions beyond 1GHz. Average axial and plastic package diodes for use below 1GHz are available from 15s. to £4, with metal encapsulations ranging from 30s. to £7. Microwave devices are available from £10 upwards.

## Unijunction Transistor

As its name implies the unijunction transistor is a three-terminal, single-junction device and its symbol is shown in Fig. 8. The circuit operation is however unlike either a transistor or diode, as indeed is the construction.

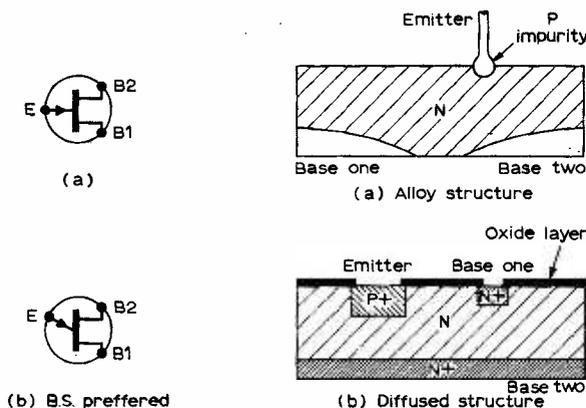


Fig. 8a, b (left): Unijunction transistor symbols.  
Fig. 9a, b (right): Unijunction transistor constructions.

The structure consists of a block of resistive semiconductor material with a junction formed at a definite position along the length of the bar. Leads are connected to the ends of the bar and are denoted base 1 and base 2 whilst the connection to the junction is referred to as the emitter. Hence the designation double base diode which was the original term for this device. At present only n-type silicon is used for the bar and the junction is formed by alloying or diffusing a p-type impurity at the required point along the bar. Typical alloy and diffused junction constructions are shown in Fig. 9 and although alloy junction types are the cheapest as well as the most widely used the diffused construction is increasingly popular due to the low leakage currents and faster switching times. Encapsulation is usually in the familiar TO-18 and TO-5 transistor casing although plastic is used increasingly for the cheaper devices. At present terminations are not completely standardised and the manufacturers' data should be consulted.

The circuit operation of the unijunction transistor can be understood by referring to Fig. 10 which shows the essential diagrammatic structure and its equivalent

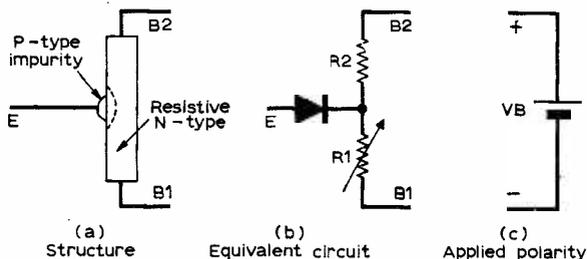


Fig. 10: Basic unijunction structure.

circuit. If the battery is connected as indicated, a voltage gradient is set up in the high resistivity n-type bar. As a result the position of the junction along the bar determines the positive potential required at the emitter terminal to enable the p-n junction diode to conduct. Thus if the battery is 12V and the junction is midway between base 1 and base 2—the potential required to make the diode conduct is  $(6V + \text{diode drop}) \approx 6.7V$ . This parameter is sometimes quoted in specifying unijunction transistors and is known as the peak point emitter voltage ( $V_p$ ). The resistance ratio which determines this potential on the equivalent circuit is  $\left(\frac{R_1}{R_1+R_2}\right)$  and this is known as the intrinsic standoff ratio ( $\eta$ ). Hence to turn on the unijunction transistor the emitter voltage must satisfy the following equation:

$$V_{\text{emitter}} = V_p = \left(\frac{R_1}{R_1+R_2}\right) V_B + V_d = \eta V_B + V_d \quad (1)$$

Since the intrinsic standoff ratio  $\eta$  determines  $V_p$  for any supply voltage this is always quoted as a parameter and for any given device has a stated tolerance.

When the diode is made to conduct by this potential  $V_p$  then the base 1 resistance  $R_1$  reduces rapidly to a low value—thus causing a rapid increase in emitter current and a drop in emitter voltage towards zero volts. This effect is achieved by the electron input through the emitter causing the reduction in resistivity of the base 1 region of the bar structure.

In order to reduce the base 1 region to low resistivity a minimum current into the emitter is required. This parameter is called the peak point current ( $I_p$ ) and is clearly shown in the unijunction characteristic Fig. 11.

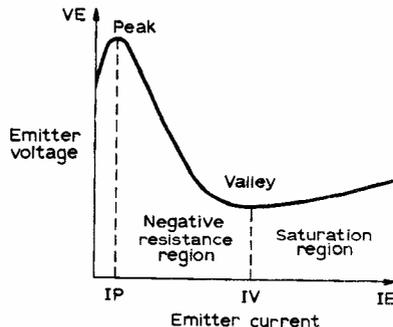


Fig. 11: Unijunction transistor characteristic.

The characteristic also shows the negative resistance region which causes the switching action and the stable saturation region which is achieved after  $I_p$  is exceeded.  $I_p$  is usually of the order of 0.5 to 100  $\mu A$  and  $\eta$  of the order of 0.5 to 0.85. The total resistance known as the interbase resistance  $R_{BB1}$  varies between 4k $\Omega$  and 12k $\Omega$ . Other parameters supplied by the manufacturer are peak emitter current ( $\sim 2A$ ), power ( $P_D$ ), maximum base to base voltage ( $V_{B2} - V_{B1}$ ,  $\sim 30-50V$ ) and frequency—which can be in the megacycle region.

It can be seen from the characteristics that until the diode conducts the impedance is very high (1-10M $\Omega$ ) whilst at switch on it drops rapidly towards zero. When coupled to a charging capacitor it is off until  $V_p$  is reached, then rapidly conducts and discharges the capacitor. When the discharge current falls below  $I_p$  it switches off and the capacitor can recharge to  $V_p$ . Thus it is useful as a relaxation oscillator but can also be used for thyristor triggering, voltage sampling and in protection circuits.

The disadvantages of unijunction transistors are that the ratio  $\eta$  varies considerably as it depends on the

positioning of the junction—as a result the turn-on emitter voltage (peak point voltage  $V_p$ ) also varies considerably. In addition these parameters are affected by temperature.

Unijunction transistors are available at varying price levels depending on the demand, range of tolerance of  $\eta$  and hence  $V_p$ , and frequency response. Cheapest types are plastic encapsulated at 5s. with high frequency, low leakage devices available at 9s. to 35s. At present only p-type emitter devices are available as shown by the symbol which indicates—in the emitter arrow—the direction of current flow. If n-type emitter devices become available they will be expensive initially and as with transistors the reversal of current flow will be indicated on the symbol by a reversal of the emitter arrow.

TO BE CONTINUED

## **PRACTICAL TELEVISION**

*in the JANUARY issue*

### ★ DEVELOPMENTS IN TV RECEIVERS

A detailed account of the changes that have been taking place in TV receivers in recent years, including the introduction of i.c.s and single-standard operation.

### ★ A CONSTRUCTOR'S 625-LINE RECEIVER

Details of a 17in. 625-line receiver built up by a constructor to provide superior performance, including black-level stabilisation.

★ **TRANSISTOR LINE DRIVER STAGES**  
Line output driver stages are unique to fully transistorised receivers and present some tricky design problems. A detailed look is taken at these problems and the methods of successfully overcoming them.

### ★ SIMPLE GADGETS FOR THE REPAIR SHOP

A number of simple gadgets that can save much time and effort are described in *Workshop Hints*.

**PLUS ALL THE REGULAR FEATURES**  
on sale

**DECEMBER 19th**

**PRACTICAL WIRELESS and  
PRACTICAL TELEVISION**

## **FILM SHOW**

**Caxton Hall, Caxton Street  
London S.W.1  
Friday, March 6th, 1970  
at 7.30 p.m.**

Come and spend an interesting evening (free tea and sandwiches), which will include a colour film entitled **SOMETHING BIG IN MICRO-CIRCUITS**. Ian Nicholson of Mullard Ltd., will be the principal speaker. W. N. Stevens, Editor, Practical Wireless and Practical Television will be in the chair.

## **BEGINNERS PORTABLE RECEIVER**

—continued from page 695

will accommodate should be used. The wires between L1, VC and the board must be short and not liable to flexing or the alignment will be affected. If possible, L1 and VC should be fixed rigidly to the Veroboard to ensure this. The wires connecting the volume control to the board are not so critical.

## **Operation**

The receiver should work fairly well without any alignment at this stage and the coil cores must not be adjusted indiscriminately if it does not. If there is no sound, the stages can be checked individually as follows. Connect one end of a capacitor (about  $0.1\mu\text{F}$ ) to battery negative and touch the other end to successive transistor bases, working from the loudspeaker to the aerial. Clicks should be heard in the loudspeaker until the faulty stage is located.

The radio works well without an external aerial but this can be used by adding C1 to the circuit (see Fig. 1). A car aerial can be connected in this way. If the connection of the external aerial upsets the radio tuning unduly or causes overloading, use a smaller value for C1.

## **Alignment**

If the radio is receiving signals, it can be aligned without other equipment if proper care is taken. Tune in a *weak* station at the centre of the range. Use a plastic screwdriver blade (e.g., a filed down plastic knitting needle or toothbrush handle) to adjust i.f.t.1, i.f.t.2, i.f.t. 3 for the strongest signal. Repeat this adjustment several times, keeping the signal tuned in as well as possible with VC. Find a weak station at the l.f. end of the range. Adjust L2 oscillator core in one direction somewhat and retune the station with VC. If the reception is better, continue adjusting the dust core in the same direction until the best signal is obtained; if the reception is worse, adjust in the opposite direction. After each core adjustment, the same station must be retuned with VC. Retune VC to a weak station at the h.f. end of the range and adjust VC2 trimmer for correct station position. Finally adjust VC1 trimmer for maximum signal strength. The process must be repeated until best results are obtained. Alignment is now complete.


A socket for a magnetic earpiece can be connected as shown in Fig. 4. The same socket can be used to operate extension speakers. If the socket is wired as shown, the radio speaker is muted when anything is plugged in.

Figure 5 shows a treble/bass tone control that can be added to the circuit. R16 and C12 are no longer used and should be removed from the board. The tone control reduces the audio gain slightly but provides a useful range of adjustment.

The audio stages can be used as a useful loudspeaker amplifier for microphone, guitar, signal tracing, record playing, etc. by adding a socket as shown in Fig 6. ■



**THE RELIABLE  
SOLDERING INSTRUMENT!**

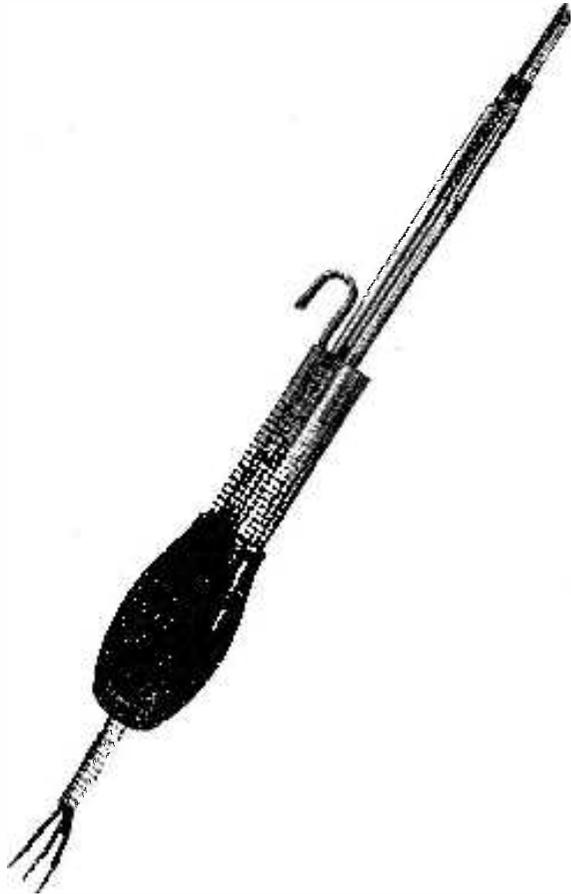

SEND COUPON FOR LATEST LEAFLET

**ADCOLA PRODUCTS LTD  
ADCOLA HOUSE  
GAUDEN ROAD  
LONDON SW4  
Telephone 01-622 0291/3**

NAME .....

ADDRESS .....

.....

.....

.....

PW177

**SEMICONDUCTORS  
BRAND NEW AND FULLY GUARANTEED**

1N914	1/6	2N2905A	8/-	ACY22	4/-	BD123	21/6	MJ490	22/6
1N916	1/6	2N2906	6/-	ACY28	4/-	BD124	12/-	MJ491	25/6
18021	4/-	2N2906A	8/-	AD140	8/-	BF115	5/-	MPP102	8/6
18025	5/-	2N2923	4/-	AD149	11/6	BF117	10/6	MPP103	7/6
18113	3/-	2N2924	4/-	AD161	7/6	BF167	5/6	MPP104	7/6
18120	2/6	2N2925	3/6	AD162	7/6	BF173	7/6	MPP105	8/-
18121	2/6	2N2926		AF114	5/-	BF180	7/-	NK70013	8/8
18130	2/6	„ Green	3/-	AF116	5/-	BF181	6/6	NKT216	7/6
18131	2/6	„ Yellow	2/9	AF117	5/-	BF184	7/6	NKT217	8/8
18132	2/6	„ Orange	2/9	AF118	12/6	BF194	5/-	NKT261	4/-
1844	2/-	2N3011	12/6	AF124	4/6	BFX12	4/6	NKT262	4/-
2G301	4/-	2N3053	6/6	AF125	4/6	BFX13	4/6	NKT264	4/-
2G302	4/-	2N3054	12/6	AF126	4/-	BFX29	12/6	NKT271	4/-
2G303	4/-	2N3055	15/-	AF127	3/6	BFX30	9/-	NKT272	4/-
2G371	3/-	2N3702	3/6	AF139	7/6	BFX35	19/6	NKT274	4/-
2N696	4/6	2N3703	4/6	AF181	8/6	BFX43	8/6	NKT275	4/-
2N697	5/-	2N3704	4/6	AF186	11/-	BFX44	8/6	NKT281	5/8
2N698	4/6	2N3705	4/-	AF239	7/6	BFX84	7/6	NKT403	15/-
2N706	2/6	2N3706	4/6	AFZ12	8/6	BFX85	9/-	NKT404	12/6
2N706A	2/6	2N3707	4/-	ASY26	5/6	BFX86	6/6	NKT405	15/-
2N708	4/-	2N3708	3/6	ASY27	8/6	BFX87	6/6	NKT613	6/6
2N929	5/6	2N3709	3/6	ASY28	5/6	BFX88	5/-	NKT674	5/-
2N930	7/-	2N3710	4/-	ASY29	5/6	BFY10	4/6	NKT677	5/-
2N1090	6/6	2N3711	4/-	ASZ20	7/6	BFY17	4/6	NKT713	5/-
2N1091	6/6	2N3819	9/-	ASZ21	7/6	BFY18	4/6	NKT773	5/-
2N1131	6/6	2N3820	23/6	BAX13	2/6	BFY19	4/6	NKT781	6/-
2N1132	6/6	2N4058	5/6	BAX16	2/9	BFY20	12/6	NKT20329	8/6
2N1302	3/6	2N4059	5/-	BAY31	1/6	BFY41	10/-	NKT8011	
2N1303	3/6	2N4060	5/-	BAY38	3/6	BFY43	12/6	NKTS0112	15/6
2N1304	4/6	2N4061	4/6	BC107	3/6	BFY50	4/6	NKTS0113	19/6
2N1305	4/6	2N4062	4/6	BC108	3/6	BFY51	4/6		
2N1306	5/-	2N4254	8/6	BC109	3/6	BFY52	4/6		
2N1307	5/-	2N4255	8/6	BC113	6/6	BFY76	8/6		
2N1308	6/-	2N4284	3/6	BC116	12/6	BFY77	11/6	OA5	2/8
2N1309	6/-	2N4285	3/6	BC118	6/6	BFY90	12/6	OA9	2/-
2N1507	5/6	2N4286	3/6	BC125	11/-	BSX19	3/6	OA70	1/8
2N1613	5/6	2N4287	3/6	BC125	11/-	BSX20	3/6	OA73	2/-
2N1711	6/6	2N4288	3/6	BC126	11/-	BSX21	7/6	OA79	1/9
2N1589	6/6	2N4289	4/6	BC147	3/6	BSX26	10/6	OA81	1/6
2N1893	8/6	2N4291	3/6	BC148	3/6	BSX27	10/6	OA85	1/6
2N2102	15/-	2N4292	3/6	BC149	3/6	BSX28	6/-	OA90	1/6
2N2147	14/6	40361	12/6	BC167	3/6	BSX29	13/6	OA91	1/6
2N2148	12/6	40362	14/6	BC168B	3/6	BSY26	4/-	OA95	1/8
2N2160	14/6	3N128	18/6	BC168C	3/9	BSY27	4/-	OA200	2/-
2N2193	5/6	3N140	19/6	BC169B	3/6	BSY28	4/-	OA202	2/-
2N2193A	5/6	3N141	21/6	BC169C	3/9	BSY29	4/-	OC26	6/6
2N2194A	5/6	3N142	16/6	BC212L	5/-	BSY38	4/6	OC28	8/6
2N2217	6/6	AAZ13	2/-	BCY30	5/6	BSY39	4/6	OC35	6/8
2N2218	6/6	AAZ15	2/6	BCY31	5/6	BSY40	6/6	OC36	6/6
2N2219	6/6	AAZ17	2/6	BCY32	7/6	BSY51	8/6	OC44	4/-
2N2220	5/-	AC107	6/-	BCY33	4/-	BSY52	9/-	OC45	2/6
2N2221	5/-	AC126	4/-	BCY34	4/6	BSY53	8/6	OC71	2/6
2N2222	6/6	AC127	5/-	BCY38	4/6	BSY54	10/6	OC72	2/6
2N2368	5/-	AC128	4/-	BCY39	7/6	BSY95A	3/6	OC75	4/6
2N2369	5/-	AC176	5/-	BCY40	6/6	BY100	4/6	OC81	4/-
2N2369A	5/6	AC187	12/-	BCY42	3/-	BYX10	5/6	OC83	4/6
2N2539	4/6	AC188	12/-	BCY43	3/-	BYZ10	9/6	OC84	5/-
2N2540	4/6	ACY17	5/-	BCY44	7/6	BYZ11	7/6	OC139	6/6
2N2646	11/6	ACY18	5/-	BCY54	4/6	BYZ12	6/-	OC140	6/6
2N2904	8/-	ACY19	5/-	BCY70	4/6	BYZ13	5/-	OC200	6/6
2N2904A	8/-	ACY20	5/-	BCY71	8/6	BD116	35/-	OC201	7/6
2N2905	8/-	ACY21	5/-	BCY72	4/-	BD121	17/6	OC202	10/6

**MULLARD  
INTEGRATED  
CIRCUITS**

FCH211 Hextuple DTL Inverter Gate	23/6
FCH221 Triple 3 Input DTL Line	23/6
FCJ101 3 Input JK Flip Flop	35/-
TAA241 Operational Amplifier	47/6
TAA243 Operational Amplifier	47/6
TAA 263 Linear AF Amplifier	18/6
TAA320 Most LF Preamplifier	15/6

**SPEAKERS (3 ohm)**

10" x 6" 37/8,	
9" x 4" 23/8,	
8" x 5" 19/8,	
7" x 4" 15/8,	
5" x 3" 12/8,	
3" 9/8, 5" 14/8,	
8" 27/8, 12" 39/8.	

Post and Packing 2/9

SEND 6d. STAMP FOR CATALOGUE  
P.P. for Components 1/6 per order

**THYRISTORS**

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.  
3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/6.  
ZENERS. 1 1/2 WATT 2.7-33V 4/6,  
400m/w 3.0-33V 5/-.

**INTEGRATED CIRCUITS—R.C.A.**

CA3005 30/-, CA3011 20/-, CA3012 25/-,  
CA3013 30/-, CA3014 30/-, CA3018 25/-,  
CA3019 25/-, CA3020 27/6, CA3021 42/6,  
CA3022 35/-, CA3023 32/6, CA3026 27/6,  
CA3028A 25/-, CA3028B 35/-, CA3035 35/-,  
CA3036 20/-.  
FAIRCHILD  
L900, 914 11/-, L923 14/-.  
DATA SHEETS FOR RCA DEVICES 2/- per type.

Presets std., horiz. or vert. 1/6  
Potentiometers, Log/Lin 3/3 each

MFD	V	Price	MFD	V	Price	MFD	V	Price
1	15	1/6	25	10	1/8	200	6.4	1/9
1	40	1/9	25	25	1/6	200	16	2/-
2	15	1/6	25	50	1/8	250	25	3/9
2	350	2/-	32	15	1/6	250	50	3/8
2.5	16	1/9	32	450	1/8	320	10	1/6
4	15	1/6	40	6.4	1/8	400	16	2/9
4	40	4/9	40	16	1/8	500	6	2/6
4	350	2/3	50	12	1/6	500	25	3/9
5	15	1/6	50	25	1/6	500	50	4/9
6.4	6.4	1/9	50	50	2/-	640	16	3/6
8	15	1/6	64	25	1/6	1000	12	3/9
8	40	1/8	80	6.4	1/6	1000	16	4/-
8	450	3/-	80	16	1/8	1000	25	5/-
10	15	1/8	100	6.4	1/8	1000	50	7/6
10	25	1/8	100	12	1/8	2000	25	8/6
12-b	25	1/9	100	25	1/6	2000	50	12/6
16	18	1/8	100	50	2/6	2500	25	9/8
25	6.4	1/6	125	4	1/6	5000	25	12/6

VEROBOARD	RESISTORS	
15 Matrix	1 Matrix	
2 1/2" x 3 1/2"	3/6	1/2 watt 10%, 4d.
2 1/2" x 5"	4/3	1/2 watt 5%, 5d.
3 1/2" x 3 1/2"	4/3	1/2 and 1 watt, 6d.
3 1/2" x 5"	5/8	3 watt, 5%, 1/8
2 1/2" x 17"	12/6	5 watt 2/-
3 1/2" x 17"	16/-	1 watt Metal Oxide, 1/6
Cutter	9/-	


**A. MARSHALL & SON**  
28 CRICKLEWOOD BROADWAY, LONDON N.W.2  
01-452 0161/2/3 CALLERS WELCOME  
Post & Packing U.K. only, 1/6. Europe 10/-, Commonwealth (Air) 13/-.

# Kinver for Components

## LINEAR INTEGRATED CIRCUITS FOR ALL YOUR REQUIREMENTS

Plessey SL403A 3 Watt Audio Amplifier	30/6
G.E. type PA230 Low Level Amplifier	31/
G.E. type PA234 1 Watt Audio Amplifier	23/
G.E. type PA237 2 Watt Audio Amplifier	24/
G.E. type PA246 5 Watt Audio Amplifier	54/
RCA type CA3000 D.C. Amplifier	54/9
RCA type CA3011 Wide Band Amplifier	30/-
RCA type CA3020 1/2 Watt Wide Band Amplifier	30/-
RCA type CA3028A Differential/Cascode Amp (120 MHz)	30/-
RCA type CA3029 Operational Amplifier	55/2
RCA type CA3035 Ultra High Gain Amplifier	30/-
Mullard type TAA263 A.F. Amplifier	15/9
Mullard type TAA293 General Purpose Amplifier	21/8
Mullard type TAA310 Record/Playback Pre-Amplifier	32/-
Mullard type TAA320 MOS L.F. Amplifier	13/5
G.E. type 2N5306 Darlington Pair	11/6
G.E. type DI3T1 Programmable Unijunction Transistor	10/8

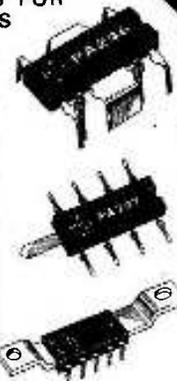ADD 1/- each to the above i.e. for data sheets if required. Data sheets may be purchased separately at 1/6d. each post free. Issued free with SL403A only



### TRANSISTORS

BCY17	8/8	BC212L	3/9	OC26	2/-	2N1308	9/6
BCY18	4/3	BC213L	3/9	OC28	2/-	2N1309	9/6
BCY19	5/8	BC214L	4/-	OC33	2/-	2N2006	13/-
BCY20	4/6	BCY70	5/4	OC36	2/-	2N2024	4/4
BCY21	4/11	BCY71	10/4	OC71	2/-	2N2025	5/3
BCY22	2/10	BCY72	4/6	OC72	2/9	2N2926	3/-
BCY23	18/-	BD121	18/-	OC76	2/9	2N2928	6/8
BCY40	3/5	BF184	7/6	OC81D	2/-	2N3033	2/5
BCY41	4/4	BF194	7/-	OC10	3/9	2N3702	3/6
BCY44	8/-	BFY50	5/4	OC11	3/9	2N3703	3/3
BCY26	6/2	BFY51	4/6	2N606	4/9	2N3704	3/4
BCY27	8/1	BFY52	5/-	2N607	5/-	2N3705	3/4
BCY28	6/2	BSY95A	3/11	2N706	3/8	2N3707	4/-
BCY29	8/1	MJ481	27/3	2N1132	10/9	2N3708	2/5
BC107	3/3	MJ491	32/11	2N1302	3/11	2N3849	9/-
BC108	3/-	TIP31A	17/-	2N1303	3/11	2N3899	18/9
BC109	3/3	TIP32A	23/-	2N1304	5/-	2N3922	5/11
BC152L	3/2	TIS44	1/9	2N1305	5/-	2N4058	4/6
BC158L	2/5	TIS49	2/6	2N1306	6/5	2N4059	3/5
BC184L	3/2	TIS50	3/9	2N1307	6/5	40408	14/11
2N240 Unijunction	14/11						

### DIODES

AA119	3/-	OA91	1/8	1N82A	9/8	1S134	5/3
AA211	2/6	OA202	2/-	1N87A	4/6	1S940	1/-
AA215	3/3	1N34A	4/-	1N914	2/-		
BAY38	3/9	1N60	4/-	1S44	1/8		
OA47	2/-	1N64	4/-	1S131	3/-		

### VEROBOARD

	0-1	0-15
2 1/2in x 5in	4/9	4/2
2 1/2in x 3 1/2in	4/2	3/5
3 1/2in x 5in	5/6	5/6
3 1/2in x 3 1/2in	4/9	3/11
17in x 2 1/2in		10/6
17in x 3 1/2in		14/8

### PLAIN VEROBOARD

(Uncoopered)  
(0.15in Matrix only)

2 1/2in x 5in	3/8
2 1/2in x 3 1/2in	3/-
17in x 2 1/2in	7/6
17in x 3 1/2in	9/8
17in x 5in	14/8
Cutter	7/3
Pin Insertion Tool (0-1)	9/6
Pin Insertion Tool (0-15)	9/6
Packet of 36 pins (0-1)	3/11
Packet of 36 pins (0-15)	3/11

### INTERNATIONAL RECTIFIER HANDBOOKS

HB10 Rectifier Engineering Handbook	16/9
HB20 Zener Diode Handbook	16/9
HB30 Solar Cell and Photocell Handbook	16/9
HB40 SCR Handbook	20/-

### PHOTOCELLS

IR CS-120	19/8
Mullard Type ORP12	9/-

### ZENER DIODES

1S2030 Series (400mW, 3-3V to 15V)	4/8
Z1100-C Series (1 Watt, 3-9V to 27V)	7/11

### COMPONENTS CATALOGUE 2/- Post Free (Inland) P. & P. 1/6 inland, overseas at cost (min. 10/-)

Cash with order please, discounts may be deducted as follows:—order over £5—10%; order over £10—15%. Trade orders—net 30 days. Please send SAE with enquiries. CALLERS WELCOME. Open 9.00 a.m.—12.50 p.m., 2.00 p.m.—5.00 p.m. Weekdays and Saturday Mornings 9.00 a.m.—12.50 p.m.

### TRANSISTORS etc.

AC107	3/-	OC35	7/6
AC126	2/-	OC44	2/-
AF115	3/-	OC45	2/-
AF116	3/-	OC70	2/3
AF117	2/9	OC71	2/-
BFY18	4/6	OC72	2/2
BFY51	4/-	OC73	2/3
GET113	2/6	OC75	2/2
OA5	1/6	OC75	2/2
OA9	1/8	OC81	2/-
OA47	1/9	OC81D	2/-
OA81	1/6	OC82D	2/3
OA85	1/6	OC140	5/-
OC23	6/8	OC169	3/6
OC25	5/-	OC170	2/2
OC26	5/-	OC171	2/2
OC28	6/8	OC202	4/6
		TK22C	1/6

### SILICON DIODE RECTIFIERS

BY100 800 pIV	2/10
500 mA 250 pIV	1/9
Avalanche 1 1/2 A	4/8
1200 pIV	1/9
Six Amp Series	
BY213 300 pIV	3/6
BY212 600 pIV	4/6
BY211 900 pIV	5/-
BY210 1200 pIV	5/6

### Mullard Stack FW Bridge

12A 100 pIV	30/6 (3/-)
-------------	------------

### THYRISTORS

5 amp series	
100 pIV	7/6
200 pIV	9/-
300 pIV	10/6
400 pIV	12/-
800 pIV	25/-
10 amp series	
50 pIV	10/-
100 pIV	12/-
100 amp series prices available on request.	

### Midget Electrolytic Conds. Wire Ends

At 6d. each	
0-8 uF	25 volt
4 uF	150 volt
640 uF	2-5 volt
At 9d. each	
2 uF	350 volt
4 uF	12 volt
8 uF	12 volt
16 uF	16 volt
30 uF	10 volt
100 uF	6 volt
125 uF	4 volt
At 1/- each	
16 uF	250 volt
50 uF	10 volt
100 uF	12 volt
100 uF	25 volt
200 uF	10 volt
320 uF	10 volt
2000 MFD 30V	4/6
1500 MFD 30V	4/6

Crystal Diodes—6 for 2/6. (7d.)

Additional Transistors—AF147 and AF150, 24V. Larger envelope, 4 leads, collective current 10mA, gain 70—4/- each. AF149—gain 225—4/6 each. Also 8 uF 50V 1/2, 25 uF 25V 1/3 and 50 uF 50V 1/9. Other electrolytics in current list. Postage, Packing and Insurance all above 1/- up to 11, 12 and over charges paid.

2 GANG VAR. CONDENSER: Mod., air-spaced, -0005 ea. sec. 5/- (1/-). 3 GANG, 7/6 (1/-). SUB-MIN TRANSFORMERS: Output (3 Ohm for OC72 etc.) 2/6. Driver 2/9 (up to six, 1/-). MULTIMETER: 20,000 Ohm/V D.C., 10,000 Ohm/V A.C. 0-5/25/50/250/500/1K volts D.C. 0-10/50/100/500/1K volts A.C. 0-50 uA/2-5mA/250mA D.C. 0-6K Ohm meg Ohm 10 uA/0-100 mV/1mA. -20 to +22dB. Complete with test leads and instructions.

Over-load protected 1970 model with every refinement. 24.7.6 (2/6). JUNIOR MODEL at 47/6 (2/6) 1000 Ohm/V described in free list.

SOLDERING IRON, Slim Mod. British High speed. 8 1/2in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use. 19/6 (1/6).

DIAMOND STYL. Replacements for BSR TC8L/P, TC8/S and TC8L/P/STEREO. COLLAR "O". RONETTE BF40LP; GARRARD GC2LP and GC8LP; ACOS GP65/67; all at 7/6 each (1/-). ACOS GP91 ST/PL; BSR ST4 and ST9; SONOTONE 9TA and 9TAHC, PHILLIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304) state whether 1/2in. or 1/4in. all at 13/6 (1/-).

SAPPHIRE all the above 7/6 types only, also ACOS GP37 at 2/3 each (1/-). ACOS GP91 at 6/9 (1/-). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES. All fitted Styl and Standard fittings. Mono GP37/2, 13/6. Stereo Compatible—Mono which also plays Stereo records monaurally with min. wear. GP91/SG, 19/6. Latest Stereo GP93, 24/6. Ceramic Stereo, top quality for expensive outfits. GP94, 28/6 (all 1/-).

PP3 ELIMINATOR (A.C.) 17/8. (1/6) TWO STATION TRANS. INTER-COM. Excellent baby alarm. Instant, easy fitting with leads, plugs and battery. All you require 52/8 (3/-). TRANSISTORISED AMPLIFIERS. 3 watt, 9V operation, 45/6 (1/6); 7 1/2 watt, 6 trans. 24V operation, 67/6 (2/6).

Extra High Torque MINI-MOTOR, 4 1/2 to 12V, 1 1/2 x 1/2in. 5/- (1/-), 9.000 r.p.m.

SUBSTITUTION BOXES, Capacitance 25/6 (1/6). Resistance 32/6 (1/6). Both full range and complete. Full details in list.

TEST PRODS: Flexible, unbreakable 24in. Red and Black leads, thin 4 1/2in. prods, 1 1/2in. plugs 4/9 (1/-). Croc. Clips: Plated with screw, or with red/black handles, 6d. each. 5/- doz. (1/-).

RECORDING TAPE: Finest quality British Mylar. STANDARD: 5in. 600ft. 7/3. 5 1/2in. 550ft. 8/9. 7in. 1200ft. 11/3. LONG PLAY 5in. 900ft. 10/-, 5 1/2in. 1200ft. 11/3, 7in. 1800ft. 18/- (1/3 each). Still the finest quality and value obtainable.

MICROPHONES—CRYSTAL MIC91, Desk, 16/3; MIC45, curved hand grip 17/6; Stick "60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand type 7/6, or with "strut" stand, switch and 2 leads with 2-5 and 3-5 plugs 12/6 (1/3). Lapel (or hand) with clip 6/8 (1/-). Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands, 25/- (1/6). DYNAMIC: Cream hand/table 15/6 (1/6). MS10 50K Ohm, 3 1/2 x 1/2in. with Base, Adaptor 37/6 (2/6). MS11, similar, but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6). DM125 Uni-directional, 50K/600 ohms imp, stand adaptor, very high quality 6 1/2 x 2 x 1 1/2in., 25.9.6 (5/-).

CARDIOM DYNAMIC OMNI-DIRECTIONAL: Two highly successful mikes "SQUARE" 208, 25.10.0. "BALL" type, 209, with built-in vol. control, switch 50K/600 ohms imp., 25.17.6 (either type 5/-). Full details in list.

MICROPHONE INSERTS: Diameter 1.75in. or 0.9in. either size 5/6 (1/-). SPEAKERS: 12in. round, fitted Tweeter, 6W, 3 or 15 Ohm (state which), 37/6 (5/6); or for stereo, 50/- per pair (charges paid); 2 1/2in. 3 Ohm (1/-); 6 x 4 heavy duty 3 Ohm 14/6 (3/6) or for Stereo 34/6 pair (charges paid); (1/-). Limited quantity powerful 2 1/2in. FM transistor replacement speaker, high ohms, excellent 5/9 (1/-). HEADPHONES: High Res. 2000 Ohm ea. earpiece 18/6 (1/6); Stereo Dyn 8-16 Ohm 63/- (3/-). EARPIECES with lead and min. jack plug, magnetic 1/9, Crystal 4/9 (up to 3 for 1/- on either). State if 2-5mm. or 3-5mm. plug required. (Crystal 3-5mm. only.)

AERIALS, Car Types: Telescopic, vandal proof, locks retracted, 2 keys and all fittings, 22/6 (2/6) Motor driven, 12V, 5 section, complete 27.10.0 (5/-).

FOR ALL PORTABLES and F.M. SETS. 7-Section 5 1/2-3 1/2in., no swivel, screw hole in base, 6/6. 10-section 6 1/2-4 1/2in., no swivel, screw hole in base, 12/6. DISAPPEARING 8 section, swivel fixing assembly, 6 1/2-3 1/2in. 10/-, New 6 section 5 1/2-2 1/2in., screw hole in base, no swivel 4/- (1/- all sizes).

SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 2/3, SPDT 2/9, DPST 3/-, DPDT 3/3. Slide type, Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre "off" 1/9. Reed magnetic on/off 1/9 (up to three, 1/-; 1d. each all additional). Rotary Switches etc. in list.

VIBRATORS: Famous makes only. 12 volt 4 pin non-synch 2/6, 12 volt 7 pin synch 10/-, 6 volt 7 pin synch 10/- (1/- each, all types). No other types available.

MAINS NEON TESTER: Fly leads 2/-. Pocket screwdriver type 3/6. PLUGS: Std. Jack, plastic body 2/3. Screened 3/-. VALVE HOLDERS: B7G or B9A, Moulded 6d. (all above, 1/- up to three). CONNECTING WIRE: 5 coils asstd. coils, each 5 yds. Solid Core 2/6. Flexible 3/-. Super thin for transistor wiring etc. 3/- (1/- all types per 5 coils). PICK-UP WIRE: Twin Super thin Flex, Screened, Sheathed, 1/3 yd. (6d. up to 6 yds., over 6 yds. post free). TWIN MIKE CABLE: 1/3 yd. SINGLE MIKE CABLE: 7d. yd. Both flexible, screened and sheathed. (Up to 3 yds 8d., each additional yard, 1d. extra.)

R.F. INDICATOR, 5-Band, with meter antenna, monitoring crystal earpiece etc., 48/6 (1/6). Details in list.

RETRACTABLE FLEXIBLE LEADS. Space saving "Curly", many uses in car and home: with phono plug each end, 6ft., 4/6; 12ft., 7/8. With phono plug one end, phono socket at other, 6ft., 5/-, 12ft., 8/6 (1/- each all types).

CAR RADIO: Splendid new All-British dash-mounting radio using Mullard transistors and circuit. M. and L. wave. Separate speaker and baffle. Absolutely complete, for + or - chassis. 21.11.0 (6/6). A huge success since introduction.

CURRENT LIST: Sent with all orders or free for s.a.e. details of cable, croc. clips and leads, Continental din plugs for Grundig, Telefunken equipment, etc., dials, plugs and sockets, panel meters, record player and tape recording accessories. BATTERY CHARGERS: test equipment, terminals, tape recorder, special transistors, portable sets, more switches and other components, tools, Veroboard etc., etc. This advertisement cancels all previous ones and lists supplied prior to November 30th.

## FELSTEAD ELECTRONICS

(PW26) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire only. Overseas air or surface mail extra at cost, plus 3/2 registration or insurance fee. S.A.E. please for all enquiries, otherwise reply cannot be repited to

# TAKE 20

JULIAN ANDERSON

No. 9

## THREE TRANSISTOR RADIO

This month's special Christmas project describes a three transistor radio which is highly selective together with a good output level. By careful 'shopping around' among the advertisers the complete radio may be built for under 20s; as usual less than twenty components are used

A FEW months ago our project was a one transistor radio which did not require an external aerial and operated a loudspeaker; however this design did have limitations—especially volume which was mentioned in the text. With Christmas just around the corner there must be many readers who would like to take advantage of their interest in electronics and knock up something for the children, and it was with this specifically in mind that this month's project was planned.

First, the radio had to have decent selectivity and volume, and as it is intended primarily for children it had to be able to get Radio Luxembourg well. The circuit had to be reliable and quickly built. (To this end three prototypes were built to ensure the circuit was reliable.) Building of the prototype shown in the photographs took under three hours including the cabinet. Also the radio had to have a presentable but cheap case.


### The Circuit

There is nothing particularly unusual about the circuit. The first transistor acts as an r.f. amplifier with VR1 as its collector load. Positive r.f. feedback (regeneration) is taken from the slider of VR1 and connected via VC2 to the top of the aerial coil.

The r.f. signal is fed to the base of Tr2 which is biased in such a way as to detect the r.f. signal, the output is smoothed by C3. The audio output is d.c. connected to Tr3, the output transistor. The emitter resistor is bypassed by C4, the base bias for Tr2 being taken from this circuit via R3, 100k $\Omega$ . The 200 $\mu$ F capacitor, C5, decouples r.f. and a.f. from the positive rail.
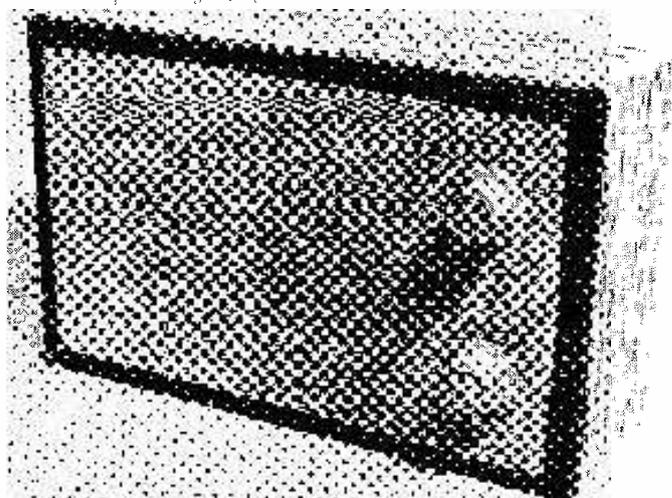
### Components

Care will have to be taken in the purchase of components to come within our 20s. maximum. Whereas aerial coils can be bought, it is far cheaper and very



The Take 20 three transistor radio.

simple to wind your own. For this L1 should consist of about 70 turns and L2 of 5 turns on a four to six inch length of  $\frac{3}{8}$  in. or  $\frac{1}{4}$  in. ferrite rod. VC1 may be any type of tuning capacitor between 200pF and 350pF. For economy the loudspeaker should be a 6 x 4 in. size removed from old TV sets.

### Construction

All components apart from the speaker, VR1, VC1 and the battery are mounted on an eleven-way minia-

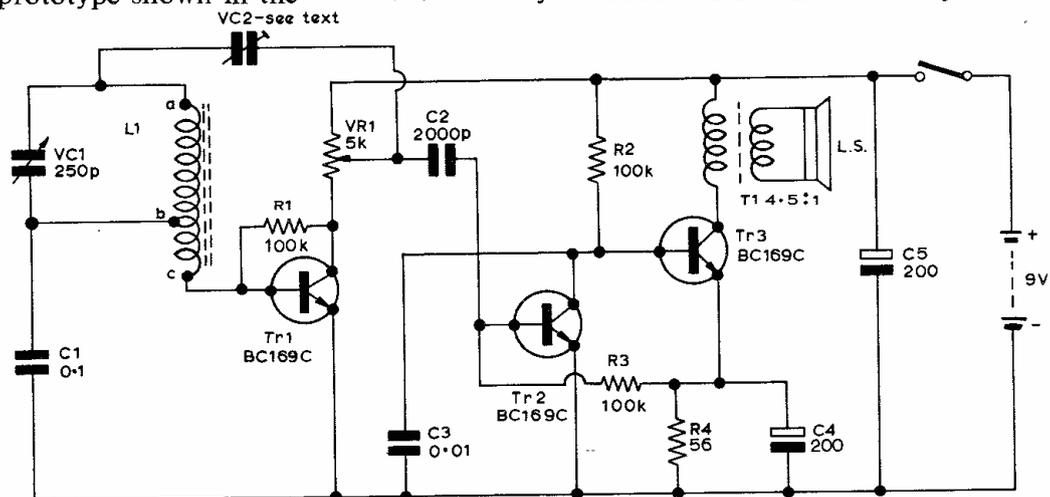


Fig. 1: The circuit of the three transistor radio.

A vacancy exists on the editorial staff of  
**PRACTICAL WIRELESS**

Required to prepare articles from authors copy through to final printing. Knowledge of modern electronics and editorial procedure essential. Applicants are invited to write to the Managing Editor, Practical Wireless, Tower House, Southampton St., London W.C.2 giving full details.

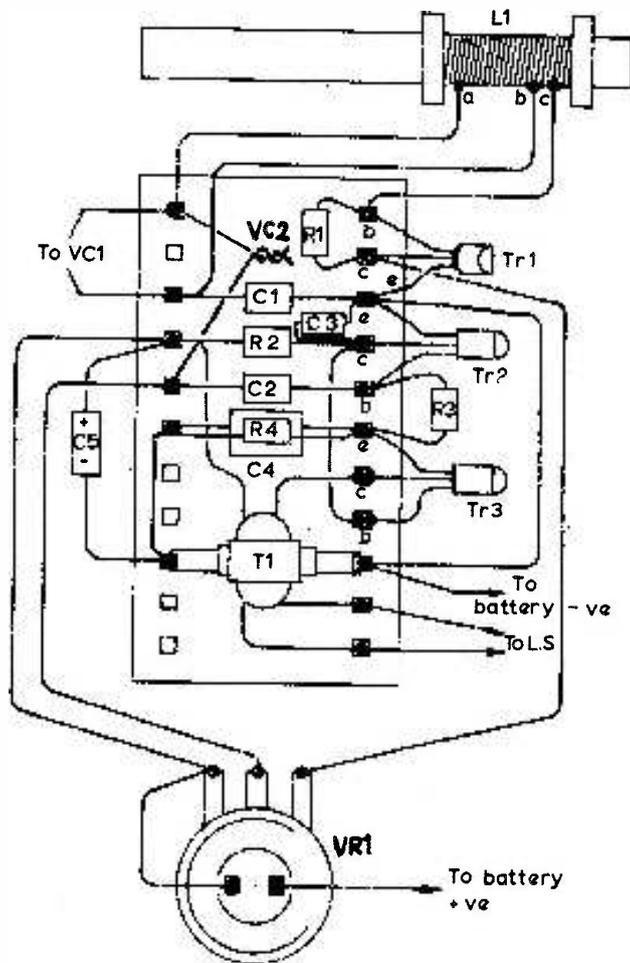


Fig. 2: The components are mounted on an eleven way tag-board. Compare this with the photograph.

ture tag board as shown in Fig. 2. The ferrite rod is secured to this board by tying one end to the top of the tag board as shown in the photograph.

The cabinet front is made from a piece of hardboard  $9 \times 5$  in. to which are fixed the sides made from  $2\frac{1}{2} \times \frac{1}{2}$  in. planed softwood. These sides should be glued and nailed together and nailed with hardboard pins to the side framework. Holes must of course be drilled for the speaker and the two controls. The tag board is held inside the case by making a small bracket, one end of which is bolted to one of the holes in the tag board and the other screwed to the inside of the case ensuring that the ferrite rod is not too close to the speaker magnet.

The cabinet front can be covered with speaker fabric or any reasonably strong material. This should be cut exactly to size and glued. The sides and the back of the cabinet are covered in self-adhesive plastic covering such as Fablon. The junction of the speaker fabric and plastic covering may be hidden by using black plastic tape.

### QUERY COUPON

This coupon is available until 7th January, 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, JANUARY 1970

## ★ components list

### Resistors:


R1 100k $\Omega$                       R3 100k $\Omega$   
 R2 100k $\Omega$                       R4 56 $\Omega$   
 All  $\frac{1}{8}$  or  $\frac{1}{4}$  watt, 10% miniature types  
 VR1 5k $\Omega$  log pot. with switch

### Capacitors:

C1 0.1 $\mu$ F                      C4 200 $\mu$ F 9V  
 C2 2,000pF                    C5 200 $\mu$ F 12V  
 C3 0.01 $\mu$ F  
 VC1 250pF variable—see text  
 VC2 see text
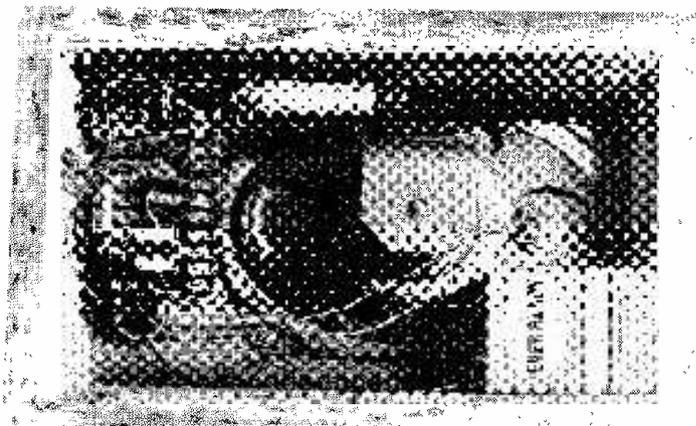
### Miscellaneous:

Tr1, Tr2, T3r BC169C; Ferrite rod with windings—see text; T1, transistor output transformer, approx. 4.5:1; Loudspeaker 3 $\Omega$ ; Battery PP7 or equivalent; Eleven-way tag board; Hardboard and softwood for case—see text; Speaker fabric; Self-adhesive plastic covering.



An interior view of the prototype.


## Conclusion

Assuming everything has been wired up correctly the only adjustment is that of VC2 and this, being frequency selective, should be peaked so that the set just fails to break into oscillation on Radio Luxembourg. VC2 consists of two 1in. lengths of wire twisted together. Incidentally the gain of the first stage is so high that unless the general layout is carefully followed there is a danger of the set continually oscillating. Because of the fairly high capacitance of Veroboard it is not to be recommended for this particular project. ■


Next month's *Take 20* article describes a small, cheap, transformerless amplifier. It provides between 750mW and 1W into a 3 $\Omega$  loudspeaker.

Published approximately on the 7th of each month by IPC Magazines Limited, Tower House, Southampton Street, London, W.C.2. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia, Malawi and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2 2s 0d.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given be lent, resold, hired out or otherwise disposed of in any way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

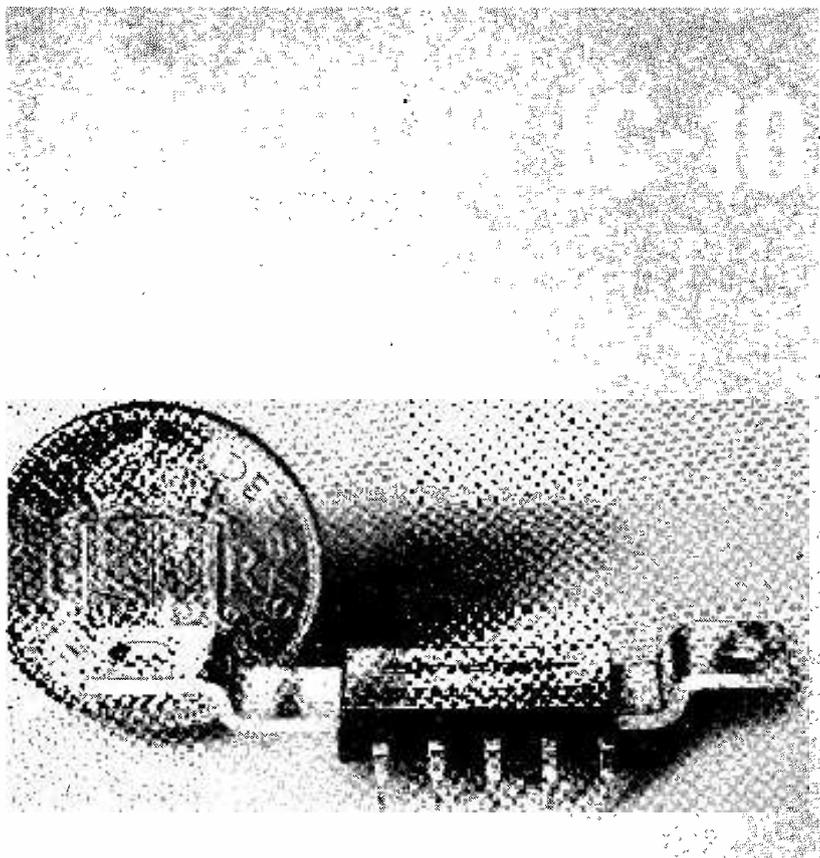
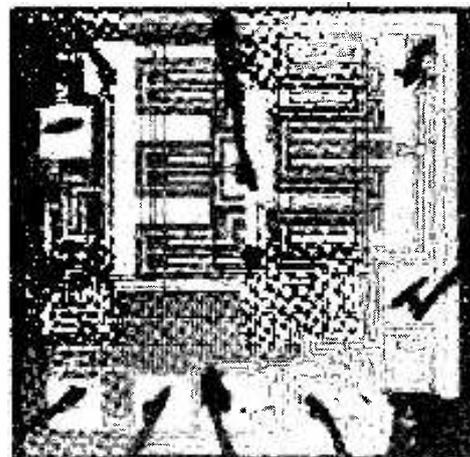
## MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



### the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of the usual tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required for producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. It also enables us to give a 5 year guarantee on each IC-10 knowing that every unit will work as perfectly as the original and do so for a lifetime.

#### ■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm$ 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000.000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

#### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

#### ■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.


SINCLAIR

**IC.10** with IC.10 manual and 5 year guarantee **59/6**

POST FREE

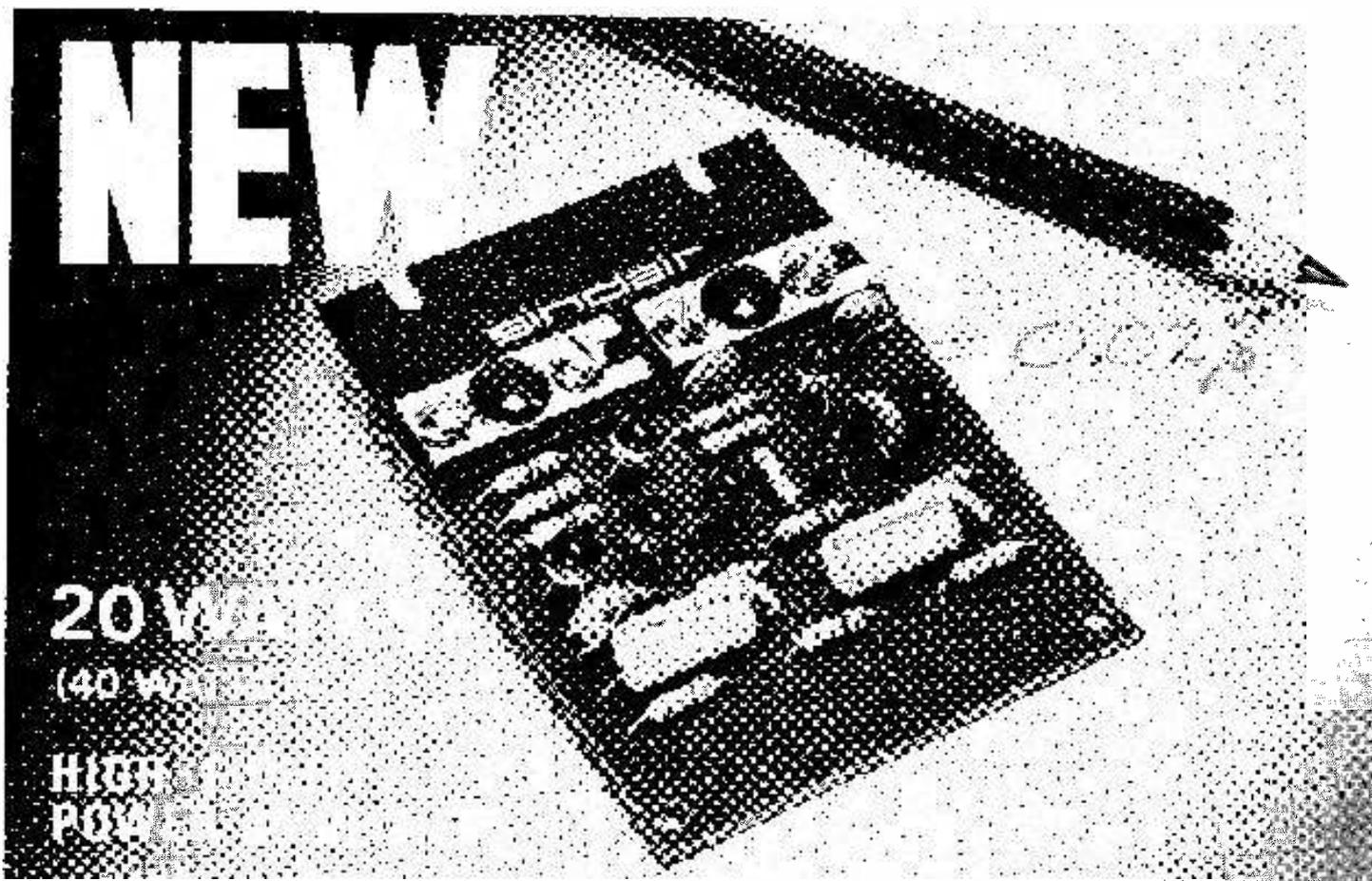**sinclair**

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD · CAMBRIDGE  
Tel. 0233-52731



# Z.30


## THE WORLD'S LOWEST DISTORTION HIGH FIDELITY AMPLIFIER.

For four years, the Sinclair Z.12 dominated the constructor world, being the best selling unit of its kind this side of the Atlantic. Excellent as it was, the new Sinclair Z.30 is still better. Half the size of the Z.12, it has more than twice the power, very much greater gain and a level of distortion 50 times lower. This incredible figure results from using over 60dB of negative feed back with a constant current load to the driver stage obtained by incorporating a two transistor circuit in place of the more usual boot-strapping. 9 silicon epitaxial planar transistors are used to provide enormous power (up to 20 watts RMS continuous sine wave, 40 watts peak). The circuitry of this marvellous amplifier allows it to be operated from any voltage from 8 to 35 to perfection.

At all output levels, distortion is only 0.02%. This puts true laboratory standards into the hands of every user of a Z.30. Two Z.30s and a new Stereo Sixty will make a stereo assembly of such perfection that it could not be bettered in its class no matter how much you spent. But the Z.30 has an enormous variety of applications, particularly where quality, precision and reliability are essential. Yet this brilliant new Sinclair design costs not a penny more than its famous predecessor.
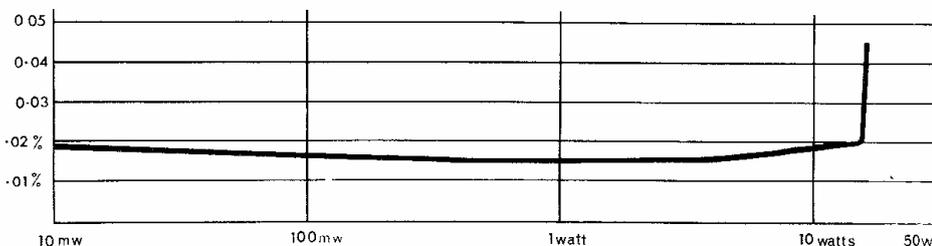
### APPLICATIONS

Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; intercom; electronic music and instruments; P.A.; laboratory work, etc. Full details for these and many other applications are given in the manual supplied with the Z.30.



### SPECIFICATIONS

**Power output:** 15 watts R.M.S. into 8 ohms using a 35 volt supply; 20 watts R.M.S. into 3 ohms using a 30 volt supply.

**Output:** Class AB.

**Frequency response:** 30 to 300,000Hz  $\pm 1$ dB.

**Distortion:** 0.02% total harmonic distortion at full output into 8 ohms and at all lower output levels.

**Signal-to-noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100 Kohms.

**Damping factor:** > 500.

**Loudspeaker impedances:** 3 to 15 ohms.

**Power requirements:** From 8 to 35V. d.c. (The Z.30 will operate ideally from batteries if required).

**Size:**  $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$  inches.

*Built, tested and guaranteed, with circuits and instructions manual*

# 89/6

# sinclair

## SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD, CAMBRIDGE Tel: 0223 52731





# WIRECOMP ELECTRONICS

LONDON'S LEADING  
BARGAIN SPECIALISTS

FOR THE RADIO • HI-FI  
& ELECTRONICS ENTHUSIAST

Special displays of radios, recorders, record decks, tuners, amps., meters, speakers, etc., etc. ALL faulty or damaged needing repair—

**AT GIVE AWAY PRICES!**

100's of component bargains from our easy to see and choose from self service racks.

100's OF OLD TYPE VALVES — from 2/- each

ASSORTED TRANSISTORS 9d each. 7/6 per doz

Huge stocks of shop soiled and reconditioned second hand radios, record players, tape recorders, etc.

**SPOT CASH PART EXCHANGES**  
WE OFFER THE HIGHEST RATES IN LONDON

There's something for everyone

COME AND LOOK TODAY (Open 6 days a week!)

ALL THESE ITEMS ARE AVAILABLE TO CALLERS ONLY

PERSONAL CALLERS TO:

48 TOTTENHAM CT. RD., W.1

Tel. 01-636 0647

## YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME ..... Block


ADDRESS ..... Caps.

..... Please 1/70

**BRITISH NATIONAL RADIO SCHOOL**
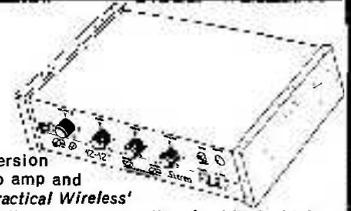
## BETTER Bargains Service FROM TRS

BUILD THIS FINE  
VERSION OF THE  
PW.12-12 WITH A  
TRS KIT



T.R.S. have produced their own kit version of this outstanding combined stereo amp and pre-amp. It conforms precisely to *Practical Wireless'* excellent circuit but is styled for a flatter, more conventional cabinet which will be available shortly. Kit includes two-tone front panel and control knobs, components and transistors.

Inputs—Mag. P.U. (R.I.A.A.) 2.5mV into 68 Kohms; Ceramic P.U. and Radio; Response 20Hz to 30KHz  $\pm 1$ dB. Output—12 watts per channel. R.M.S. into 15 ohms.

Kit complete, less cabinet **£24.10.0** (Carr. 7/6) *Power Amplifier & Pre-amp Kits available separately. S.A.E. brings list.*

### AMPLIFIERS

Styled and kitted by T.R.S., using quality components, including valves or transistors as necessary and excellent instructions. Backed by T.R.S. service.

**MULLARD 5-10.** Basic kit (requires pre-amp). Input Sensitivity—40mV; Response 20Hz–15KHz  $\pm 1$ dB; Output 10 watts R.M.S. at 3 or 15 ohms. KIT **£10.10.0**. BUILT **£13.0.0** (Carr. either, 7/6).

**MULLARD 2 VALVE PRE-AMP.** Switching for 5 inputs; bass/treble/volume controls, etc. Sensitivity at input—4mV max. into 80K–1 Megohm; Response 20–25,000Hz  $\pm 1$ dB. KIT **£8.19.6**. BUILT **£9.10.0** (Carr. either 5/6).

**MULLARD 10-10 STEREO AMPLIFIER.** Input sensitivity—210mV per channel; Response 12Hz–35KHz  $\pm 3$ dB; 10 watts R.M.S. output per channel into 3 or 15 ohms. KIT **£18.10.0**. BUILT **£22.10.0** (Carr. either 12/6).

Basic Kit (no panel or controls) **£17.0.0**. Built **£21.0.0**. Pre-amp must be used here.

**MULLARD 2+2 STEREO PRE-AMP** with same characteristics per channel as mono pre-amp (+ balance). BUILT **£13.19.6** (Carr. 7/6).

**T.R.S. 4x4 ECONOMY STEREO.** Modular assembly. With cabinet power supply and Din plugs **£12.10.0** (Carr. 7/6).

SINCLAIR PRODUCTS AS ADVERTISED

### TUNERS

**T.R.S. 6 VALVE AM/FM.** Self-powered, large scale; push-buttons. Magic eye. Med. Wave and F.M. Diode output per tape. COMPLETE KIT **£12.10.0** (Carr. 7/6).

**T.R.S. FM TUNER.** Transistors, Inter-station suppression, A.F.C. etc. Modular assembly. Modules, chassis, drive etc. come to **£15.15.0** (Carr. 7/6) Cabinet to match T.R.S. 4+4 **£1.17.6** (Carr. 2/6) Power supply **£2.5.0** (Carr. 3/-) Decoder for Stereo **£10.10.0** (Carr. 2/6)

### GRAMO UNITS & PLINTHS

**GARRARD SP.25 MK. II.** Manual: Arm and 10½in. die-cast t/table, cueing device, etc. less cartridge. Brand new in maker's carton **£12.7.6**.

**GARRARD LM.2025.** With Sonotone 9TA/MC Stereo Cartridge and lift control **£10.19.6** (Carr. 7/6)  
Garrard WB.1 Plinth **£3.7.6** (Carr. 5/-)  
Garrard CLEARVIEW Cover SCP.1 **£3.5.0** (Carr. 4/6)  
Garrard Scandinavian Type Plinth **£5.5.0** (Carr. 5/-)

### ALWAYS IN STOCK

Resistors in all values; wire-wound resistors; volume controls log or linear, 10K–2meg. Mono 3/6 (with switch 5/-). Stereo 8/6 (with switch, certain values 10/6). Log/antilog balance controls, capacitors and electrolytics; Vinaire speaker covering 48in.—22/6 yd; Bondacoust 48in. x 1in. thick 7/- yd.; Veroboard; Cir-Kit; valves; transistors. S.A.E. with enquiries please.

**TRS** RADIO COMPONENTS  
70 BRIGSTOCK ROAD,  
THORNTON HEATH,  
SURREY

Open Sats.  
Close early Weds.

• ½ min. Thornton Heath  
Sin. (Southern)

• Phone:  
01-684 2188

### FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/8	OC171	4/-
AC127	2/8	OC200	3/6
AC128	2/8	OC201	7/-
AC176	5/-	2C301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N1302-3	4/-
AF115	3/6	2N1304-5	5/-
AF116	3/6	2N1306-7	6/-
AF117	3/6	2N1308-9	8/-
AF239	12/6	2N3819 FET.	9/-
AF186	10/-	2N3844A	5/-
AF139	10/-	<b>Power Transistors</b>	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC26	5/-
BSY28	3/-	OC28	7/6
BSY29	3/-	OC35	5/-
BSY95A	3/-	OC36	7/6
OC41	2/6	AD149	10/-
OC44	2/6	AU Y10	30/-
OC45	2/6	2N3055	15/-
OC71	2/6	<b>Diodes</b>	
OC72	2/6	AAV42	2/-
OC73	3/6	OA95	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
OC83	4/-	OA81	1/9
OC139	2/6	IN914	1/6
OC140	3/6		

### NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data and Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
B82	10	OC45, OC810 and OC81 Trans. Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and term.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B86	150	High quality Germ. Diodes. Min glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B80	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes. 50-1,000 Volts.	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type.	10/-

### NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries -3 to +5 volt, +5 to 2ma.	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output. Pair	10/-
B79	4	IN4007 sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Miniature.	10/-
B81	10	Reed Switches, mixed types, large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92	4	NPN. Sil Trans. A06=B8X20, 2N2369 500 MHz. 360mW.	10/-
B93	5	GET118 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96	5	2N3136 PNP sil. Trans. TO-18, HFE 100-300 I.C. 600mA. 200 MHz.	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
B99	200	Capacitors, Electrolytics, paper silver mica, etc. Post and packing, this Pak 2/6.	10/-
H4	250	Mixed Resistors. Post and packing 2/-.	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-

**FREE!** Packs of your own choice up to the value of 10/- with orders over £4.

### RETURN OF THE UNBEATABLE P.1, PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

**P1** PLEASE ASK FOR PAK P.1. ONLY 10/- 2.- P & P on this Pak.

Complementary Set.  
NPN/PNP Germ.  
trans., Pak F.3

**2/6**  
PAIR

MULLARD DATA BOOK  
Semiconductor & Valve  
Data & equivalents.

**3/6**  
EACH  
Postage 6d.

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVER SEAS ADD EXTRA FOR AIRMAIL.

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT

The ideal, economical and safe way of running Transistor Radios, Record Players, Tape Recorders, Amplifiers etc. from A.C. Mains. All units are completely isolated from mains by double wound transformer ensuring 100% safety.

### PLUS-3

#### MAINS UNIT

Provides three separate switched output voltages 6v., 7½v. and 9v. DC. attractive case with indicator light, mains lead output socket, plug and lead. Size 4½ x 3½ x 2½ in.




**57/6** P. & P. 2/6

(Extra lead with DIN plug for Cassette Recorders 7/6)

### POWER PLUS
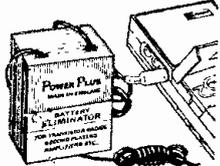
#### MAINS UNIT

for Cassette Tape Recorders using 7½v. Complete with DIN plug for recorder power socket. Can also be supplied for a 6-volt output complete with suitable plug. (Please state make, model and voltage required.)



**45/-** P. & P. 2/6

Also available—Unit to run your Cassette Recorder from 12v. Car Battery 32/6. P. & P. 2/6.

**MAINS UNIT for FI-CORD 202A TAPE RECORDER** P. & P. 5/-.

**£4.15.0**


### MAJOR POWER PLUS MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 39/6. For two separate outputs, 4½v + 4½v, 6v + 6v., 9v + 9v. 42/6. P. & P. 2/6 per unit. (Please state outputs reqd).



**R.C.S. PRODUCTS (RADIO) LTD.**  
(Dept. P.W.), 31 Oliver Road, London, E.17

## SURPLUS EX GOVT. BARGAINS

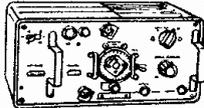

**AMPLIFIER RF NO. 2 MK III.** Increases output of 19 set to 25 watts. Brand New. 12v operation. 75/-, Carr. 15/-.

No. 19 Sets and Auxiliary Equipment available, 12v D.C. Power Units 50/-, Carr. 10/-.

**12024 WILL VIBRATOR MK II No. 2.** 70/-, Carr. 10/- H/MIC SETS. Used 15/-. New 22/6. P. & P. 5/-. Mains P.S.U.'s for 19 TM/RC £6.15.0, Carr. 10/-. R.P. Antenna Tuner (AT) 25/-, P. & P. 5/-.




**COLLINS TCS RECEIVER** 7 valve Int. Octal Covers 1-5-12 Mc/s Tuneable RF, AF, BFO. Power required 240v D.C. 80 MA 12v 1-25A. £8.10.0, Carr 15/-.

**CR100 RECEIVERS.** Amateur Shipping Broadcast. 60Kc/s-30Mc/s AC or DC. Mains operation. Fully tested. £23.10.0, Carr. 50/-.

**B.41 RECEIVER.** LF Version of B.40. Coverage 15Kc/s-700Kc/s. Mains Operation. As new £8.10.0, Carr. 30/-.



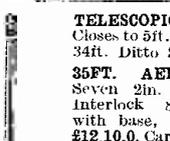**R.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20Mc/s. 4 bands. AM/FM. C.W. BFO. 12v DC. Internal Power Supply. Tested. £13.10.0, Carr. 15/-.



**TELESCOPIC MASTS.** 20ft. Closes to 5ft. 9in. 70/- Carr. 15/- 34ft. Ditto 80/-, Carr. 15/-.

**35FT. AERIAL MASTS.** Seven 2in. dia. sections. Interlock 8in. Complete with base, Nylon Guys. £12.10.0, Carr. 50/-.

**TELEPHONE FIELD TELEPHONES.** Communication up to 10 miles. Tested with batteries. £5.15.0, Carr. 20/-.

**LIVINGSTONE LAB TRANSISTOR AMPLIFIER.** 50 watts R.M.S. Size 14" x 9" 4in. With mains p.s.u. Size 16" x 9" 6in. 22 Gns. Carr. 20/-

**A.J. THOMPSON (Dept. P.W.)**

"Eiling Lodge", Codicote, Hitchin, Herts.  
Phone: Codicote 242

C.W.O. Carriage charges apply to mainland only.

## NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
**Loft Mounting Arrays, 7 element.** 37/6. 11 element, 45/-, 14 element, 52/6. 18 element, 60/-.  
**Wall Mounting with Cranked Arm, 7 element.** 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6.  
**Mast Mounting with 2in. clamp, 7 element.** 42/6. 11 element, 55/-, 14 element, 62/-, 18 element, 70/-.  
**Chimney Mounting Arrays, Complete, 7 element.** 72/6. 11 element, 80/-, 14 element, 87/6. 18 element, 95/-. Complete assembly instructions with every unit. **Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-.** State clearly channel number required on all orders.

### BBC - ITV AERIALS



**BBC (Band D).** Telescopic loft, 25/-, External S/D, 30/-, "H", £2.15.0.  
**ITV (Band 3).** 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 47/6, 5 element, 52/6.  
**Combined BBC/ITV.** Loft 1+3, 40/-; 1+5, 50/-; 1+7, 60/-; Wall mounting 1+3, 57/6; 1+5, 67/6; Chimney 1+3, 67/6; 1+5, 75/-.  
**VHF transistor preamps, 75/-.**

**COMBINED BBC1 - ITV - BBC2 AERIALS** 1+3+9, 70/-, 1+5+9, 80/-, 1+5+14, 90/-, 1+7+14, 100/-, Loft mounting only. Special leaflet available.  
**F.M. (Band 2).** Loft S/D, 15/-, "H", 32/6. 3 element, 55/-, External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/4. Outlet boxes, 5/-, Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D. P. & P. 6/- Send 6d. stamps for illustrated lists.

Callers welcomed - open all day Saturday

**K.V.A. ELECTRONICS (Dept. P.W.)**  
40-41 MONARCH PARADE  
LONDON ROAD, MITCHAM,  
SURREY 01-648 4884

# COMET Hi-Fi DISCOUNT WAREHOUSE

- ALL ITEMS OFFERED ARE FULLY GUARANTEED AND BACKED BY COMET.
- OPEN TO THE PUBLIC 9 to 5.30 p.m. daily (8 p.m. Thursday and Friday evenings) and 5 p.m. Saturdays.
- COMPLETE FREE PRICE LIST CONTAINING OVER 800 ITEMS ON REQUEST.

	Rec. Retail Price	Comet Price
<b>AMPLIFIERS</b>		
ARENA 210 Amplifier ..	£34 13 0	£28 0 0
ARMSTRONG 521 25 watts per channel ..	£52 0 0	£44 0 0
DULCI 207 Stereo Amplifier	£25 0 0	£17 0 0
DULCI 207M Stereo Amplifier takes magnetic P/U ..	£30 0 0	£20 19 0
GOODMANS Maxamp ..	£54 0 0	£41 19 6
New LEAK Stereo 30 Plus ..	£53 0 0	£43 19 6
New LEAK Stereo 30 Plus in teak case ..	£59 10 0	£47 19 6
New LEAK Stereo 70 ..	£63 0 0	£49 19 6
New LEAK Stereo 70 Plus in teak case ..	£69 10 0	£54 19 6
LEAK Stereo 70 in Teak case	£69 10 0	£54 49 6
LINEAR LT.66 Stereo Amplifier ..	£18 18 0	£13 19 6
QUAD 33 Pre-amplifier ..	£43 0 0	£35 19 6
QUAD 303 Stereo Main Amplifier ..	£55 0 0	£46 19 6
ROGERS Ravensbourne 50 watt Stereo ..	£59 10 0	£48 19 6
ROGERS Ravensbourne in Teak case ..	£64 0 0	£52 13 6
ROGERS Ravensbrook ..	£44 0 0	£36 19 6
ROGERS Ravensbrook in Teak case ..	£49 0 0	£38 19 6
TELETON 203E ..	£28 7 6	£20 15 6
TRUVOX TSA.200 ..	£54 12 0	£39 19 6

	Rec. Retail Price	Comet Price
<b>TUNERS</b>		
ARENA 211 Stereo with decoder ..	£39 10 0	£33 19 6
ARMSTRONG 523 FM ..	£52 9 0	£44 19 6
ARMSTRONG 524 FM ..	£40 4 6	£34 19 6
ARMSTRONG M8 Stereo decoder ..	£9 10 0	£7 19 6
DULCI FMT.7 FM Tuner ..	£22 1 0	£17 19 6
DULCI FMT.7S FM Stereo Tuner ..	£31 0 0	£25 5 0
GOODMANS Stereomax AM/FM Stereo Tuner ..	£82 10 5	£71 19 6
LEAK Troughline Tuner with multiplex ..	£51 10 6	£39 19 6
LEAK Stereofetic Chassis form ..	£56 11 0	£45 19 0
LEAK Stereofetic in-Teak case	£64 14 4	£52 19 6
QUAD Stereo FM ..	£51 0 0	£44 19 6
ROGERS Cadet Mark III Tuner ..	£20 12 6	£17 13 0
ROGERS Ravensbourne Tuner with Decoder ..	£61 17 9	£52 12 6
TRUVOX FM 200/IC with decoder ..	£60 11 10	£45 19 0

	Rec. Retail Price	Comet Price
<b>TUNER-AMPLIFIERS</b>		
ARENA 2400 with Decoder ..	£90 6 0	£69 19 6
ARENA 2500 complete with Decoder ..	£97 0 0	£79 0 0
(NEW) GOODMANS Model 3000 with stereo decoder ..	£77 14 7	£66 19 6
ARMSTRONG 525 25 watts per channel. FM ..	£87 16 9	£74 19 6
ARMSTRONG 526 25 watts per channel. AM/FM ..	£98 15 6	£85 19 6

	Rec. Retail Price	Comet Price
ARMSTRONG 127 ..	£43 19 9	£37 19 6
(Teak Case for 127) ..	£3 17 0	£3 10 0
TANDBERG Solv Super 10/71 Tuner/Amplifier AM/FM and 2 short wavebands ..	£75 18 0	£65 18 0
TELETON MX.990 Stereo Tuner/Amplifier with AM/FM Multiplex Stereo Radio c/w two Speakers, each Speaker containing 8in. bass, 2in. tweeter	£64 13 2	£48 19 6
TELETON F.2000 AM/FM Stereo Tuner/Amplifier 2 x 5 watts RMS with silicon transistors ..	£51 0 0	£37 19 6
TELETON R.8000 AM/FM Stereo Tuner/Amplifier 2 x 6 watts RMS, complete with 2 speaker boxes ..	£60 19 6	£49 19 6
TELETON CMS.400 AM/FM Multiplex Tuner/Amplifier with 2 speaker boxes and turntable ..	£126 0 0	£99 0 0
TELETON 7ATI Stereo Tuner/Amplifier AM/FM 50 watts RMS, Stereo Decoder and F.E.T. ..	£133 0 0	£95 0 0

**THE GOODMAN 3000 MUSIC AUDIO SUITE**  
A complete Audio Suite with Stereo Radio complete with Speakers, Turntable and magnetic cartridge. All wired and ready to go. Beautifully finished in Teak.  
£140 9 0 £115 9 4

## CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
BOWERS & WILKINS DM3 A and W ..	£63 0 0	£53 6 0
BOWERS & WILKINS DM3 M ..	£69 10 0	£58 16 0
BOWERS & WILKINS P2H ..	£94 10 0	£81 5 0
CELESTION Ditton 10 ..	£21 3 2	£17 5 0
CELESTION Ditton 15 ..	£31 3 7	£25 19 6
DULCI AS3 Speaker ..	£8 8 0	£6 19 6
GOODMANS Maxim ..	£20 7 9	£15 19 6
GOODMANS Mezzo II ..	£30 18 0	£24 19 6
GOODMANS Magnum-K ..	£40 2 0	£32 19 6
GOODMANS Mirimba ..	£24 0 1	£19 19 6
GOODMANS Mambo ..	£22 5 6	£18 11 9
GOODMANS Loudspeaker System Model 2005 (per pair) ..	£25 0 0	£21 0 0
KEF Celeste ..	£29 0 0	£23 19 6
KEF Concord ..	£43 10 0	£34 19 6
LEAK Sandwich ..	£43 10 0	£34 19 6
LEAK Mini-Sandwich ..	£29 15 0	£23 19 6
QUAD Electrostatic ..	£66 0 0	£57 19 6
TRUVOX LS 200 ..	£22 7 3	£17 19 6
WHARFEDAILE New Airedale ..	£69 10 0	£57 14 0
WHARFEDAILE Denton ..	£18 0 0	£13 19 6
WHARFEDAILE Super Linton ..	£21 10 0	£17 19 6
WHARFEDAILE Melton ..	£29 10 0	£23 19 6
WHARFEDAILE New Dove-dale 3 ..	£39 10 0	£31 19 6
WHARFEDAILE Rosedale ..	£55 0 0	£43 19 6
WHARFEDAILE UNIT 3 Speaker Kit ..	£10 19 6	£8 19 6

Most types of chassis, speakers, cross-over networks, etc., available ex stock.

	Rec. Retail Price	Comet Price
<b>TURNABLES</b>		
GARRARD SP.25, Mark II ..	£15 11 4	£11 19 6
GARRARD AP.75 ..	£23 16 0	£16 19 6
GARRARD SL.55 ..	£13 17 9	£11 12 6
GARRARD SL.65 ..	£19 6 5	£14 9 6
GARRARD SL.75 ..	£35 12 5	£25 19 6
GARRARD SL.95 ..	£45 9 1	£33 19 6
GARRARD 401 ..	£31 14 2	£26 10 0
GARRARD 3000 fitted with GKS 25/Cartridge ..	£13 18 3	£9 19 6
GARRARD 3500 fitted with GKS 25/Cartridge ..	£15 15 0	£10 19 6
GOLDRING GL69 ..	£25 1 6	£21 5 0
GOLDRING 69P ..	£33 11 9	£28 19 6
GOLDRING Lenco GL.75 ..	£36 8 2	£27 19 6
GOLDRING 75P inc. cover ..	£46 18 8	£30 0 0
GOODMANS Model 3025 Complete with magnetic Cartridge ..	£37 14 9	£32 19 6
THORENS TD.125 ..	£69 11 2	£53 19 6
THORENS TD.150A Mark II ..	£41 14 9	£32 19 6
THORENS TD.150AB Mark II ..	£45 10 7	£34 19 6
THORENS TD.124/11 ..	£46 15 10	£42 0 0

Bases, plinths and covers stocked to suit all the above turntables.

## HI-FI STEREO TAPE DECKS AND TAPE RECORDERS

AKAI X-360 4-track ..	£339 0 0	£284 0 0
AKAI X-360D deck 4-track ..	£290 0 0	£243 0 0
AKAI 1710 4-track without accessories ..	£109 0 0	£89 19 6
AKAI 1800 4-track ..	£158 0 0	£133 0 0
AKAI 1800SD 4-track ..	£199 0 0	£167 0 0
AKAI 4000D deck 4-track ..	£87 10 0	£75 10 0
FERGUSON 3324 Twin Track ..	£33 14 0	£24 19 6
FERGUSON 3226 Four Track ..	£46 6 0	£29 19 6
GRUNDIG TK 124 ..	£41 18 6	£36 19 6
GRUNDIG TK 144 ..	£47 13 1	£39 19 6
GRUNDIG TK 149 ..	£55 18 10	£47 19 6
MARCONI 4218 Stereo Tape Recorder ..	£89 11 2	£69 19 6
MARCONI 4238 4-track Tape Recorder ..	£58 11 0	£49 19 6
PHILIPS battery operated tape recorder Model 4200 ..	£35 6 0	£21 19 6
TELETON 7D 70 Stereo Tape Deck ..	£85 10 3	£62 0 0
TELETON FXB501D Stereo Tape Deck and preamplifier ..	£65 0 0	£49 0 0
TELETON 401X FM Multiplex stereo tuner/amplifier 20 watts RMS ..	£67 2 6	£49 0 0
TRUVOX R52 & R54 3-speed 2-track ..	£77 5 1	£52 2 0
TRUVOX PD Stereo Tape Deck ..	£114 15 3	£79 0 0

## PICKUP ARMS

GOLDRING Lenco L75 ..	£12 6 6	£10 10 0
GOLDRING Lenco G65 ..	£7 13 6	£6 10 0
SME 3009 with S2 shell ..	£31 6 3	£24 19 6
SME 3012 with S2 shell ..	£33 7 3	£26 19 6

# COMET DISCOUNT WAREHOUSE

Reservoir Road, Clough Road, Hull. Tel 407906  
68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally  
Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 9/- for post and packing on all orders. Make cheques, Money Orders payable to "COMET".

### 15/20 AMP CONNECTORS

Polythene insulated 12-way strip. 2/6 each, 24/- per doz.

### 13 AMP FUSED SWITCH

Made by G.E.C. For connecting water heater, etc., into 13 amp ring mains. Flush type 3/6 each, 30/- per doz.

### MICRO SWITCH

5 amp changeover contacts 1/9 each, 18/- per doz.

### 0-0005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.

### ELLIOT SEALED

### CONTACT REED RELAY

Three circuits closed by 3V or 100MA. 9/6 each.

### SLIM TUBULAR MICROPHONE

For hand holding or frontal suspension—lever switch—high impedance with lead and plugs for cassette tape recorder but suitable for most amplifiers. 19/6.

### 750 MICRO AMP MOVING COIL METER

2 1/2 in. ex W.D. but brand new and unused 19/6.

### HIGH CAPACITY ELECTROLYTICS

Brand new, not ex equipment.  
100 mfd 25v, 1/3 each, 12/- doz.  
200 mfd 25v, 1/6 each, 15/- doz.  
500 mfd 12v, 2/- each, £11.0 doz.  
1,000 mfd 12v, 3/- each, £11.0 doz.  
5,000 mfd 12v, 4/9 each, £2.8 doz.  
10,000 mfd 6v, 5/9 each, £3.0 doz.  
10,000 mfd 15v, 8/6 each, £4.10 doz.  
15,000 mfd 10v, 10/6 each, £5.0 doz.  
60,000 mfd 8v, 22/- each, £10.0 doz.  
70,000 mfd 13v, 40/- each, £20.0 doz.

### TOGGLE SWITCH

3 amp 250v with fixing ring, 1/6 each, 15/- doz.

### 3-CORE WATERPROOF FLEX

6A, 23/0076 circular PVC covered as fitted to electric drills and most portable appliances, ideal extension lead. Regular price 1/6 per yard, our price 79/6 for 100 yard coil. Post 6/6.

### 5A, 3 PIN SWITCH SOCKETS

An excellent opportunity to make that bench dis board you have needed or to stock up for future jobs. This month we offer 6 British made (Hircraft) bakelite flush mounting shuttered 5A switch sockets for only 10/- plus 3/6 post and insurance. (20 boxes post free).



### DREAMLAND CLOCK SWITCH

The wonderful DREAMLAND mains operated clock switch will automatically switch your blanket on and off each evening and you will always have a warm bed. It's luminous; you can always see the time and it's a really beautiful unit. An ideal gift. Can also control tape recorder, radio, lamp, etc., up to 500 watts. 39/6 plus 3/6 post & ins.

### PROTECT VALUABLE DEVICES

FROM THERMAL RUNAWAY OR OVER-HEATING: Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removed range setting is between 80 to 800deg. F. Price 10/-.



### Horstmann "Time and Set" Switch

(A 15 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6, p. & ins. 4/6.



### BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in. deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4 1/2 volts. Supplied complete with 2 spools ready to install. Record, Replayhead is the sensitive M4 type intended for use with transistor, amplifier. Price 79/6. Post and insurance 4/6.

### INSTRUMENT MOTORS WITH GEARBOX

Made by famous Smiths Company. Very powerful, although only quite small. Overall dimensions approx. 1 1/2 in. deep by 2in. dia. Available with the following speeds: Revs per day, 2-8-12. Revs per hour, 1,2,4,6,12,20,30. Revs per minute, 1,2,3,4,6, 8,15,30,60. 17/6 each.

### BLANKET SWITCH

Double pole with neon let into side so luminous in dark, ideal for dark room light or for use with waterproof element—new plastic case. 5/6 each. 3 heat model 7/6.



### PHOTO-ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit. Laminated Boards and chemicals. Latching relay. Infra-red sensitive Photocells and Hood, 2 transistors, cond., terminal block. Plastic case. Essential data, circuits and P.C. chassis plans of 10 photo-electric devices including auto. car parking light, modulated light alarm. Simple invisible ray switch—counter—stray light alarm—warbling tone electronic alarm—project lamp stabiliser, etc., etc. Only 39/6, plus 2/- post and insurance.

### TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 7/6. KNUCKLED MODEL FOR P.M. 9/6.

### M.W. SIGNAL GENERATOR KIT

Complete kit as described in November issue 12/6 ea.

### 80 OHM BALANCED ARMATURE EAR PIECE

Usable as microphone or loudspeaker, 4/6 each.

### MINIATURE EAR PIECE

As used with imported pocket radios 1/6 ea. 15/- doz.

### BLACK LIGHT

G.E.C. Tube for experiments and special lighting effects—40 watt 2ft. tubes only. 18/6 each; holders and control gear 19/6, postage on single item 4/6 inc. insurance or both items ordered together postage 6/6 inc. insurance.

## ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH

Also 102/3 Tamworth Road, Croydon

**MARCONI CR 150/2** double Superhet receiver 1.5-22Mc/s AM/CW/SSB operation Xtal Filter, BFO fast/slow motion tuning 'S' Meter, etc. Good condition. Tested and working. **£22.10.0. P.P. 30/-**

**R209 RECEIVER**, AM/CW/FM, 1-20Mc/s, Four bands, Vernier tuning, 12 volt DC input. Tested and working. **£13.10.0. P.P. £1.**

**COMPUTER BOARDS**. Min 30 transistors and diodes and res. etc. 10 boards, 10/- and P.P. 2/6; 25 boards 22/6 and P.P. 4/6.

**HEADPHONES**. Chamois padded, low impedance. Moving coil, magnetic microphone, new ex W.D., rare type, limited stock. 25/- per pair and 3/6 P.P.

**AERIALS**, new condition, extending to 11ft fully open; whip type; 12/6 and P.P. 3/6. Whip aerials, 12ft collapsible type; used condition. 10/- and P.P. 3/6 Bases for above 5/- and 2/6 P.P.

**BARGAIN PARCELS**. 14 lb. 29/- and 6/6 P.P.; 28 lb. 55/- and 12/6 P.P.; 56 lb. 90/- and 25/- P.P. Contain Pots., Res., Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value saves £££s. **LUCKY DIP SERVICE.**

**FURZHILL BEAT FREQUENCY OSCILLATOR**. 0-10Kc/s, 110/250 volt. Good condition; complete with spares. **£5.10.0 and 25/- P.P.**

**VHF RECEIVER TYPE 715**, less crystal 60-100Mc/s, can be operated on 2 or 4 meters or made tunable 12 volt input; not tested, complete with valves and speaker. **£3.0.0 and £1 P.P.**

**VIBRATOR POWER SUPPLY TYPE 69** by BCC for 69 T/R. Small compact 12V input gives 250V DC at 80mA and 12V output. Good condition. **25/- and 7/6 P.P.**

**MOBILE POWER UNITS** by **PYE** for the C12 T/R. Power output is 400V DC at 140mA and 300V DC at 100mA. Good condition. **£3.10.0 and £1 P.P.**

**INSULATION TESTERS**. Bench or fieldwork; speed clutch; new condition, complete with leather case; 500V, 500 megohms. **£20 and 12/6 P.P.** Also 1000V 1000 megohms with case. **£23 and 12/6 P.P.**

**CRYSTALS AS NEW**. Hc6U 5,345; 5,055; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s and 10 x J 465 Kc/s. All at 10/- and 1/6 P.P.

**METERS/MOVING COIL EX EQUIPMENT**. Good condition; all from 0-10mA, 30mA, 50mA, 100mA, 500mA. All 2 1/2 in. round 10/- ea and 5/- P.P. from 0-1mA, 5mA, 15 amp D.C., 20 amp D.C., 40 amp D.C. All 2in. round. 10/- ea and 5/- P.P.

# A. H. THACKER

Radio Dept.  
HIGH ST., CHESLYN HAY, Nr. WALSALL,  
STAFFS.



## AMAZING MINI-DRILL

FOR PRECISION MODEL WORK



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6, p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money ref. g'tee.

## MERLIN SUPPLY CO.

Dept. PW1D, Nailsea, Bristol BS19 2LP

## SENSATIONAL BRITISH MADE RADIO CONSTRUCTION OUTFIT—MAKES 5 DIFFERENT TRANSISTOR RADIOS

No soldering—no experience needed—simple lavishly illustrated step-by-step plans enables anyone 9 to 90 to build radios easily with terrific results. Educational—almost a complete Home Radio Course—you start with a simple semi-conductor radio which takes under 1 hour to build, you then progress to multi-transistor internal loudspeaker radio complete in attractive case. All operate off tiny self contained battery costing pennies and lasting months. True to life sound reproduction. Fully tuneable. Receives standard medium wave broadcasts. All parts down to last screw—including 3 Transistors, 1 Semiconductor, 1 Moving Coil Loudspeaker (this alone must be worth 19/6). Personal phone for smaller radios, all resistors, condensers, coil, wire, knobs, Radio Case, A.B.C. Plans etc., etc., **ONLY 47/6** plus 4/6 P. & P. (Parts available separately.) New and boxed direct from Manufacturers to you saving ££s in middlemen's profits. **MAKES FANTASTIC XMAS PRESENT** (Check prices of less comprehensive educational toys in the shops!) **SOLD EVERY YEAR FOR THE LAST 9 YEARS—MANY TESTIMONIALS.**

total building costs—everything

**47/6**

PHOENIX ELECTRONICS (PW7) 18 Little Preston St., Brighton 1, Sussex.

## DE LUXE PLAYERS

PORTABLE CABINET As illustrated To fit standard 75/- player or autochanger  
**RCS AMPLIFIER 3 WATT.**  
 Ready made and tested  
 This is a 2-stage unit using a triode pentode condenser coupled valve, giving 3 watts output into a 3 ohm loudspeaker.  
 Tone and volume controls mounted on panel. Supplied with knobs, loudspeaker and valves UCL82, UY85. Frequency response 50-12,000 cps. Sensitivity 200mV. **59/6**



Post 5/6 each item

**AUTOCHANGERS MONO.**  
 Balfour Princess \$5.58  
 BSR Supermin UA25 \$8.19.8  
 BSR Mini Changer \$8.19.8  
**AUTOCHANGERS STEREO**  
 BSR Supermin \$7.19.8  
 Garrard 1025 \$7.19.8  
 Garrard 3000 \$12.19.8

**SINGLE PLAYERS MONO**  
 EMI Junior Mains \$2.19.6  
 Garrard SERP22 \$6.19.8  
**SINGLE PLAYERS STEREO**  
 Garrard SP25 MHT \$12.19.8

**GARRARD TEAKWOOD BASE W.B.I.** Ready cut out for mounting 1025, 3000, SP25, AT60, etc.  
**GARRARD PLASTIC COVER SPC.1** for W.B.I. BASE. Durable tinted attractive appearance. **65/-**


**E.M.I. PICK-UP ARM.** Complete with mono cartridge 29/8. XTAL GP67 17/6; Stereo Ceramic 35/-; ACOS LP only 10/6.

### CRYSTAL MIKE INSERTS

1 1/2" dia. 6/6; ACOS 1 1/2" dia. 12/6. BMS. 1 1/2" dia. 9/6.  
**QUALITY RIBBON MIKE WITH GOOSENECK** \$11.11.0  
**CRYSTAL HAND MIKE, High Output** ..... 12/6
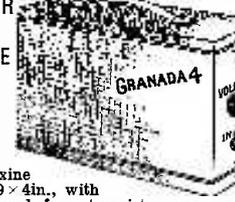
## PORTAL TRANSISTOR AMPLIFIER PLUS DYNAMIC MICROPHONE

A self-contained fully portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 x 4 1/2 in., with powerful 7 x 4 in. speaker and four transistor one watt power amplifier plus ultra sensitive microphone. Uses PP9 battery. Brand new in makers' carton with full makers' guarantee. World famous make. **Only 90/-** Post Free



**WEYRAD P50—TRANSISTOR COILS**  
 RA2W 6in. Ferrite Aerial Spare Cores ..... 6d.  
 Osc. P50/1A/C ..... 12/6  
 3rd I.F. P50/3CC ..... 5/7  
 Telescopic Chrome Aerials 6in. extends to 23in. 5/-  
 Ferrite Rods Only 8 x 3in. 4/-; 6 x 3in. 5/-

**VOLUME CONTROLS** **80 Ohm Coax 8D** yd.  
 Long spindles. Midget Size 5 K. ohms to 2 MeG. LOG or LIN. L/S 3/-; D.P. 5/-  
**STEREO L/S 10/6, D.P. 14/6**  
 Edse 5K. S.P. Transistor, 5/-

**WIRE-WOUND 3-WATT POTS.** T.V. Type. Knurled Knob. Values 10Ω to 30 K. **4/6**  
**WIRE-WOUND 3-WATT STANDARD SIZE POTS.** LONG SPINDLE **10 OHMS to 100 K. 7/6**

**VEROBOARD 0-15 MATRIX** 2 1/2 x 5in. 3/8. 2 1/2 x 3 1/2in. 3/2. 3 1/2 x 3 1/2in. 3/8. 3 1/2 x 5in. 5/2.  
**EDGE CONNECTORS** 16 way 5/-; 24 way 7/6.  
**PINS** 36 per packet 3/4. **FACE CUTTERS** 7/6.  
 S.R.E.P. Board 0-15 MATRIX 2 1/2in. wide 6d. per lin., 3 1/2in. wide 9d. per lin.; 5in. wide 1/- per lin. (up to 17in.).  
 S.R.E.P. undrilled 1 1/2in. Board 10 x 8in. 3/-

**BLANK ALUMINIUM CHASSIS** 18 s.w.g. 2 1/2in. sides. 7 x 4in., 5/6; 9 x 7in., 6/6; 11 x 3in., 6/8; 11 x 7in., 7/6; 13 x 9in., 9/6; 14 x 11in., 12/6; 15 x 14in., 15/-  
**ALUMINIUM PANELS** 18 s.w.g. 12 x 12in., 6/6; 14 x 9in., 5/6; 12 x 8in., 4/6; 10 x 7in., 3/6; 8 x 6in., 2/6; 6 x 4in. 1/6

## Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key  
 1in. 16/-; 1 1/2in. 17/6; 1 3/4in. 19/6; 1 1/2in. 24/-; 2 1/2in. 44/3  
 1in. 16/-; 1 1/2in. 19/6; 1 3/4in. 20/6; 1 1/2in. 29/-; 2 1/2in. 57/3  
 1in. 16/9; 1 1/2in. 19/6; 1 3/4in. 21/6; 2in. 39/-; 1in. sq. 36/6


**WAVE-CHANGE SWITCHES** 1 1/2in. Diameter.  
 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each.  
 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 4/6 each.  
 1 inch Diameter Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/-, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-  
**TOGGLE SWITCHES**, sp. 2/6; sp. dt. 3/6; dp. 3/6; dp. dt. 4/6

## ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms Super Sensitive ... 35/-  
 LOW RESISTANCE HEADPHONES 8-5 ohms ..... 39/6  
 DE LUXE PADDED STEREO PHONES 8 ohms ... 79/6
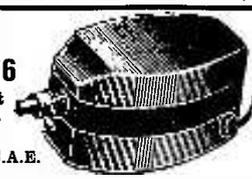
## "THE INSTANT"

**BULK TAPE ERASER AND RECORDING HEAD** **42/6** Post 2/6.  
**DEMAGNETISER** 200/250 v. A.C. Leadet S.A.E.



## RADIO COMPONENT SPECIALISTS

Minimum Post and Packing 2/6. RETURN OF POST DESPATCH. HI-FI STOCKISTS CUSTOMERS FREE CAR PARK CALLERS WELCOME  
**337 WHITEHORSE ROAD, WEST CROYDON**  
 Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)  
 Full List 1/- Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

## BARGAIN STEREO/MONO SYSTEM

Attractive Slim **PLAYER CABINET** with B.S.R. Stereo Autochanger, 3 valve Stereo Amplifier, two 6in. LOUD-SPEAKERS. (Only 4 pairs of wires to join.) **£19.19.6** Carr. 10/6. S.A.E. for details

### NEW TUBULAR ELECTROLYTICS

2/350V ... 2/3	100/25V ... 2/6	8/600V ... 9/6
4/350V ... 2/3	250/25V ... 2/6	16/800V ... 12/6
8/450V ... 2/3	500/25V ... 4/6	16+16/500V ... 7/6
16/450V ... 3/-	8+8/450V ... 3/6	50+50/850V ... 7/-
32/450V ... 3/9	8+16/450V 3/9	60+100/350V ... 11/6
25/25V ... 1/9	16+16/450V 4/3	32+32+32/350V 8/-
50/50V ... 2/-	32+32/350V 4/6	100+50+50/350V 9/6

### SUB-MIN. ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-  
 CERAMIC 500V 1pF to 0.01mF, 9d.  
 PAPER 350V-0.1 9d, 0.5 2/6; 1mF 3/-; 2mF 150V 3/-  
 500V-0.001 to 0.002, 0.1 1/-; 0.25 1/6; 0.5 3/-  
 1,000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1, 2/6.  
 SILVER MICA. Close tolerance 1%, 5-5000pF 1/-; 550-2,200pF 2/-; 2,700-5,500pF 3/6; 6,800pF 0.01, mid 6/- each.  
 TWIN GANG. (4.0") 208pF+176pF, 10/8; 365pF, miniature 10/6; 500pF standard, with trimmers, 12/6; 500pF midget less trimmers, 7/6; 500pF slow motion, standard 9/-; small 8-gang 500pF 19/6. Single "0" 365pF 7/6. Twin 10/6.  
 SHORT WAVE. Single 10pF, 25pF, 50pF, 75pF, 100pF 18pF, 200pF, 10/6 each.

### TUNING

Solid dielectric 100pF, 300pF, 500pF, 7/- each.  
 TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/3; 250pF, 1/6; 60pF, 75pF, 1/8; 1000pF, 2/6.  
 RECTIFIERS. CONTACT COOLED 1/2 wave 60mA, 7/6; 85mA, 9/6. SILICON. BYZ13, 6/-; BY100, 10/-  
 Full wave Bridge 75mA 10/-, 150mA 19/6; TV rect. 10/-  
 NEON PANEL INDICATORS 250v. AC/DC 3/6, Red, Green.

### RESISTORS.

Preferred values, 10 ohms to 10 meg.  
 1/2 w., 1 w., 20% 3d.; 1 1/2 w. 8d.; 2 w. 1/-; 3 w. 10% 6d.  
 HIGH STABILITY. 1/2 w. 1% 10 ohms to 10 meg., 2/-  
 Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.  
 WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 2/- each; 3 watt, 0.5 ohm to 8.2 ohms, 2/-  
 BRAND NEW TRANSISTORS 6/- each  
 OC71, OC72, OC81, OC44, OC45, AF117, MAT100, 7/9; MAT101, 8/6; MAT120, 7/6; MAT121, 8/6.  
 REPANCO TRANSISTOR TRANSFORMERS  
 TT45. Push Pull Drive. 9:1 CT. 6/-; TT46 Output, CT8:1 6/-  
 TT49. Interstage, 4:5:1, 6/-; TT52 Output 3 ohms, 20:1 6/-  
 TT23/4 PAIR 10 watt Amp. Transformer and circuit 35/-

## TRANSISTOR MAINS POWER PACKS, FULL WAVE

9 volt 500mA. Size 4 1/2 x 2 1/2 x 2in. Metal case. **49/6**  
 Crackle finish. Output terminals. On/off switch.  
 Half Wave 9 volt 50mA. Size 2 1/2 x 1 1/2 in. Snap terminals 32/6  
 9 volt 50mA. TRANSFORMER ONLY. 2 1/2 x 1 1/2 x 1 1/2 in. 10/6

## MAINS TRANSFORMERS

Post 5/- each

250-0-250 50 mA. 6.3 v. 2 amps, centre tapped 19/6  
 250-0-250 80 mA. 6.3 v. 3.5 a. 6.3v. 1 a. or 5 v. 2 a 30/-  
 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 35/-  
 300-0-300 120 mA. 6.3 v. 6.3 a. CT.; 6.3 v. 2 a. 45/-  
 MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 1 1/2 in. 12/6  
 MIDGET 220 v. 45 mA., 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 17/6  
 HEATER TRANS. 6.3 v. 1 1/2 a. 3/6; 6.3 v. 4 a. 12/6  
 Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp. 12/6  
 GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. 30/-  
 1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60 35/-  
 AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60w. 18/6; 150w. 30/-; 500w. 92/6; 1000w. 185/-  
 CHARGER TRANSFORMERS. P. & P. 5/-; Input 200/250v. for 6 or 12v. 1 1/2 amp. 17/6; 2 amp. 21/-; 4 amp. 30/-  
 FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12v. outputs. 1 1/2 amp. 8/9; 2 amp. 11/3; 4 amp. 17/6.

**COAXIAL PLUG 1/8. PANEL SOCKETS 1/8. LINE 2/-.**  
**OUTLET BOXES. SURFACE OR FLUSH 4/6.**  
**BALANCED TWIN FEEDERS 1/-.** 90 ohms or 300 ohms.  
**JACK SOCKET Std.** open-circuit 2/6, closed circuit 4/6;  
 Chrome Lead Socket 7/6. Phono Plugs 1/-; Phono Socket 1/-;  
**JACK PLUGS Std.** Chrome 3/-; 3-5mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 5-pin 2/-; DIN SOCKETS Lead 3-pin 3/6; 5-pin 5/-; DIN PLUGS 3-pin 3/6; 5-pin 5/-;  
 VALVE HOLDERS, 9d.; CERAMIC 1/-; CANS 1/-.

## T.S.L. LOUDSPEAKER CROSSOVER HLP2

2-way crossover for 8 or 15 ohm speakers and tweeters. 3 phono input/output sockets.  
 Made to sell. **OUR PRICE 22/6**  
 at 42/- Post 2/6.



## MINI-MODULE LOUDSPEAKER KIT

10 WATT 55/- CARRIAGE 5/-

Triple speaker system combining on ready cut baffle. 1in. chipboard 15in. x 8in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm.

**TEAK VENERED BOOKSHELF ENCLOSURE.** 16 x 10 x 9in. Modern Scandinavian fluted front design for Mini-Module **94/6** Post 5/-


Tape Spools 2/6. Tape Splicer 5/-; Leader Tape 4/6.  
 Reuter Tape Heads for Collaro models 2 track 21/- pair.  
**PHOTO-ELECTRIC RELAY SYSTEM.** 240v. A.C. Exciter and relay unit with infra red filter. For counting, door signals, alarms, etc. **£12 POST FREE.**

## MANUFACTURERS SURPLUS!

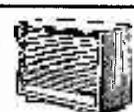**TAPE RECORDER CABINET.** Grey/Red or Grey 2-Tone. Resin covered. Size 15 x 12 in. **POST FREE**

3 inch MOVING COIL METERS  
 Various calibrations/movements, 500 Microamp; 1 Milliamper; 50-0-50 Microamp, etc. S.A.E. for list. **45/-**

**BRAND NEW QUALITY EXTENSION LOUDSPEAKER**  
 Handsome plastic cabinet, 20ft. lead and adaptors. For any radio, intercom, tape recorder, etc. 3 to 15 ohms. **30/-**  
 Size: 7 1/2 x 5 1/2 x 3in. **POST 2/6**



## BAKER MAJOR £8

30-14,500 c.p.s., Hi-Fi double cone, woofer and tweeter cone together with a ceramic BAKER magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module kit, £8-17.000 c.p.s. with tweeter, crossover, baffle and instructions. £10.19.6



**LOUDSPEAKER CABINET WADDING** 18in. wide, 2/6ft.

Goodmans Tweeter 3in 3 ohm 35/-, EMI 2in 8 ohm 17/6.  
 Horn Tweeters 2-18kc/s, 10W 15 ohm 29/6. Crossover 16/6.  
**LOUDSPEAKERS P.M. 3 OHMS.** 2 1/2in 8in, 4in, 5in. 5 x 2 1/2in. 7 x 4in. 17/6 each; 6in 22/6; 8 x 5in. 21/-; 8 x 2 1/2in. 21/-; 10 x 6in. 30/-; 10in. or 12in. Double cone 3 or 15 ohm, 39/6.  
 E.M.I. Double Cone 13 1/2 x 8in, 3 or 15 ohm 10 watt. 45/-  
 DITTO twin tweeters and X/over, 3 or 8 or 15 ohm 10w. 79/6.  
**TEAK HI-FI SPEAKER ENCLOSURES.** Fluted front; For 10in. or 12in. dia. Loudspeaker £8.10.0.  
 For 13in. x 8in. or 8in. dia. Loudspeaker £4.14.6.  
 For 10in. x 6in. or 6in. dia. Loudspeaker £3.16.6.  
**SPECIAL OFFER!** 8 ohm, 2 1/2in; 6 x 4in; 80 ohm, 2 1/2in; **15/6 EACH** 25 ohm, 6 x 4in; 35 ohm, 3in; **TYPE** 15 ohm, 7 x 4in.; 8 x 5in.  
 Sin. LOUDSPEAKER UNITS 3 ohm 27/6; 15 ohm 30/-; ELAC 8in. De Luxe Ceramic 3 ohm 45/-; 15 ohm 50/-  
 Sin. LOUDSPEAKER. TWIN CONE 3 ohm 35/-  
 Sin. WOOFER. 8 watts max. 20-10,000 cps. 8 or 15 ohm. 39/6.  
 OUTPUT TRANS. EL84 etc. 4/6; MIKE TRANS. 50:1 3/9.  
 SPEAKER COVERING MATERIALS. Samples Large S.A.E.

## THE FAMOUS MULLARD 510

£16.19.6 Post 10/6



Main power amplifier and 2 valve pre-amplifier. Silver grey fascia panel. Volume, treble and bass controls. Function switch: Radio, Tape 1, Tape 2, Gram LF, Gram 78. Tape output socket. Valves: 2 x EL84, 3 x EF86, 1 x EC083, 1 x EZ81. Ultra linear Farnako output transformer. 20dB negative feedback. 10 watts r.m.s. mono. 3 or 15 ohm output. Brand New. Guaranteed.

## ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES  
 45-page Eagle catalogue 5/- Post free.

**BARGAIN AM TUNER.** Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **79/6**

**BARGAIN DE LUXE TAPE SPLICER.** Cuts, trims, joins for editing and repairs. With 3 blades **17/6**

**BARGAIN 4 CHANNEL TRANSISTOR MIXER.** Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **59/6**

**BARGAIN FM TUNER 88-108 Mc/s Six Transistor.** Ready built. Printed circuit. Calibrated slide dial tuning. Size 6 x 4 x 2 1/2in. 9 volt. **£6.19.6**

**BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready built, with volume control. 9v. **69/6**


★ RADIO BOOKS ★ (Postage 9d.)

Practical Transistor Receivers ..... 5/-  
 Practical Radio Inside out ..... 4/8  
 Supersensitive Transistor Pocket Radio ..... 3/8  
 Radio Valve Guide, Books 1, 2, 3 or 4 ea. 5/- No.5 ea. 6/-  
 T.V. Fault Finding 405/625 lines ..... 8/8  
 Shortwave Transistor Receivers ..... 5/-  
 Transistor Communication Sets ..... 6/-  
 Modern Transistor Circuits for Beginners ..... 7/6  
 Sub-Miniature Transistor Receivers ..... 5/-  
 Wireless World Radio Valve Data ..... 9/6  
 International Radio Stations Guide ..... 2/6  
 Receive foreign TV programmes by simple modifications 5/-  
 Valves, Transistors and Diodes equivalents Manual ... 10/6

**MANUFACTURERS SURPLUS!** **25/-**  
**TAPE RECORDER CABINET.** Grey/Red or Grey 2-Tone. Resin covered. Size 15 x 12 in. **POST FREE**

3 inch MOVING COIL METERS  
 Various calibrations/movements, 500 Microamp; 1 Milliamper; 50-0-50 Microamp, etc. S.A.E. for list. **45/-**

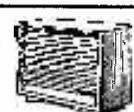**BRAND NEW QUALITY EXTENSION LOUDSPEAKER**  
 Handsome plastic cabinet, 20ft. lead and adaptors. For any radio, intercom, tape recorder, etc. 3 to 15 ohms. **30/-**  
 Size: 7 1/2 x 5 1/2 x 3in. **POST 2/6**



# Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast*, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You **LEARN**—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book—'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court, Aldermaston, Berkshire.

To: B.I.E.T., Dept. 372B, ALDERMASTON COURT, ALDERMASTON, BERKS.


I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name.....  
address.....  
age.....

**POST THIS COUPON NOW!**

# F.A.L. 'PHASE 50'

## Public Address Amplifier

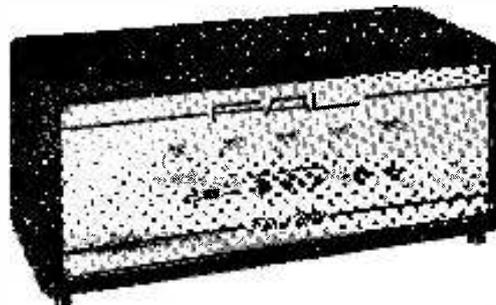

A superb solid state A.C. Mains unit for vocal and Instrumental groups and General Public Address use.

**29 Gns**

Recommended Retail price

- ★ 50 Watts Output (Peak Rating)
- ★ Output matching for speakers from 3-30 ohms
- ★ 3 separately controlled inputs
- ★ Separate Bass and Treble Controls
- ★ Frequency Response 22c.p.s. to 30Kcs.
- ★ High Sensitivity

SEND S.A.E. FOR FULLY DESCRIPTIVE LEAFLET

Available from your local Dealer

Wholesale and Retail enquiries to Manufacturers

**FUTURISTIC AIDS LTD, 103 Henconner Lane, Leeds 13**



**FABULOUS VALUE**

### TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer. Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED

Only **28 Gns.** + P&P 17/6

Credit terms available, first monthly payment £3.6.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

### FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL"

### FULLY TRANSISTORISED STEREOPHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY**

10 Watts Total output **£36.10.0** P&P 17/6

17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY

Credit Terms available. First monthly payment

£4.2.2 followed by 9 monthly payments of £4.1.8.

(Total "Credit Sale" Price £41.1.8.)

Send £4.19.8 today.



Callers Welcome

**POST THIS COUPON NOW!**

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name.....

Address.....

**LEWIS radio** 100 CHASE SIDE, SOUTHGATE, Dep. P170 LONDON, N.14, TELEPHONE PAL 3733/9668



# BI-PAK SEMICONDUCTORS

## KING OF THE PAKS SUPER PAKS

Unequalled Value & Quality  
BI-PAK NEW—UNTESTED  
SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 28104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1-5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Series & OC71	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 800 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1-amp SCR's TO-5 can up to 600PIV CRS1/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	10/-
U33	15 Plastic case 1-amp Silicon Rectifiers IN-4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY50/51/52	10/-
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2S322	10/-
U38	20 Fast Switching Sil. trans. NPN 400Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	30 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

### FULLY TESTED

AC107	3/6
AC126-7-8	2/6
AF116-117	3/6
AF139	10/-
AL102	15/-
BC107-8-9	2/-
BFY50-51-52	4/6
BSY26-7	3/6
BSY28-9	4/6
BSY95-95A	4/6
OC22-25	5/-
OC26-35	5/-
OC28-29	7/6
OC44-45	1/9
OC71-81	1/6
OC72-75	2/6
OC81D-82D	2/3
OC82	2/6
OC140	5/-
OC170	2/6
OC171	3/6
OC201	7/6
ORP12-50	8/6
OC271	8/6
OA5-10	1/9
OA47	2/-
OA70	1/3
OA79	1/9
OA81-85	1/6
OA91	1/3
OA95	1/9
OA200	3/-
OA202	3/6
2N696-7	3/6
2N706	3/6
2N708	5/-
2N2160	15/-
2N2646	15/-
2N2712	5/6
2N2926	2/6
MAT100-101	3/-
MAT120-121	3/6
ST140	3/-
ST141	4/-
2N3819	10/-
2N3820	25/-
2N3055	12/6

### TESTED SCR's

PIV	1 Amp	3A	7A	16A
50	4/6	5/-	6/6	9/6
100	5/-	6/6	7/6	10/6
200	7/-	7/6	9/-	11/6
400	8/6	9/6	11/-	13/6
600	10/6	11/6	13/6	15/6
800	12/6	14/-	15/-	18/-

### SIL. RECTS. TESTED

PIV	750mA	3A	10A	30A
50	1/-	2/9	4/3	9/6
100	1/3	3/3	4/6	15/-
200	1/9	4/-	4/9	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/3	6/9	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/6	11/6	15/-	—

### INTEGRATED CIRCUIT AMPLIFIER

Sim. to the SL402-3 as used in the "P.E. projects" Each circuit incorporates a Pre-Amp and a class A-B Power Amplifier stage, capable of delivering up to 3 watts (RMS). Fully tested and guaranteed, supplied with circuit details for simple audio amplifier, amplifier with tone controls and stereo amplifier, plus all technical data.

Lowest of Low Price 25/- ea. 10 up 21/- ea. Absolutely unbeatable value only obtainable from BI-PAK.

We request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMI-CONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

### BRAND NEW TEXAS GERM. TRANSISTORS

Pak No.	Eqvt.	Price
T1	8 2G371 OC71	10/-
T2	8 2G374 OC75	10/-
T3	8 2G374A OC81D	10/-
T4	8 2G381A OC81	10/-
T5	8 2G382T OC82	10/-
T6	8 2G344A OC44	10/-
T7	8 2G345A OC45	10/-
T8	8 2G378 OC78	10/-
T9	8 2G399A 2N1302/10	10/-
T10	8 2G417 AF117	10/-

FULL RANGE OF ZENER DIODES  
VOLTAGE RANGE 2-16V.  
400mW ..... 2/6 each  
1-5W ..... 3/6 each  
10W ..... 5/- each  
All fully tested. State voltage required.

120 VCB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407. 2N1593 FULLY TESTED AND CODED ND120. 1-24 3/6 each. TO-5 NPN 25 up to 3/- each.

### UNIUNCTION

UT46 Eqvt. 2N2646, 7/6  
Eqvt. TIS43 BEN3000  
25-99 5/-, 100 up 4/- each

F.E.T.'s To-18 case.  
FEL9 Eqvt.  
2N3819, MPF105, etc.  
7/6 each Data supplied.


100 mixed 1/4W and 1/2W RESISTORS, 10/-; 10 $\mu$  SILVERED MICA CAPACITORS, 10/-; 100 CERAMIC CAPACITORS, 20/-.

PRINTED CIRCUIT BOARD (for 6 Transistor Radio) 8 1/2 x 2 1/2 in. with Osc., 1st, 2nd and 3rd I.F.S. M.W. and L.W. FERRITE AERIAL, 2 gang tuner, circuit diagram giving values of components. (Limited quantity). 30/- (2/6 post).

MAKE YOUR OWN RECORD PLAYER. "Soft-Top" Cabinet 17 x 15 x 7 in; motor board (for BSR UA15 or UA25 Autochanger); 1 Tygan for front covering; Amplifier with UY85 and UCL82 valves; Tone & volume, with knobs; 3 ohm loudspeaker to fit; full assembly instructions. All for £6.10.0 (part carr. 10/-).
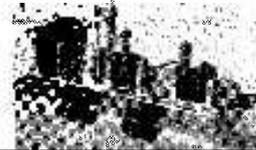
### STEREO AMPLIFIER type HV— 2 x 3 Watts

Fully built. On off, sep. vol. and tone each channel 12 x 4 1/2 x 6 in. high. EZ30. 2 x ECL86; for 3 ohm speakers, double wound main trans: fixing flanges and base plate; suitable for crystal cart., tuner etc. £6.10.0 (8/- p. & p).




### STEREO AMPLIFIER type RC— 2 x 3 Watts

Fully built. 2 x UCL82, metal rect: ganged vol. and tone cont: on-off, balance. 11 x 3 1/2 x 4 in. high. Double wound mains trans. with supporting brackets. For 3-ohm speaker. £6 (8/- p. & p).


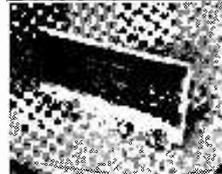
### MONO GRAM CHASSIS

3 Wave band long-med-short. Gram., 200-250v AC Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81 EF89, EBC81, EL84, EZ80. Price £10.12.6. (7/6 p. & p).



AUDIO ACCESS, min. order 10/-. Std. jack plug moulded 2/6; metal 3/6; sockets 2/6; 3-5 and 2-5mm jack plugs and sockets 1/- each; phono plugs 1/-, metal 2/-; sockets: single 10d., double 1/3, triple 2/-; phono line couplers 2/-; 3-pin DIN plug 2/9, 4-pin 3/-, 5-pin 3/4; sockets: 3-pin 1/6, 5-pin 1/9; DIN speaker plug 2/6; one-yr screened lead with phono plug attached, 7 for 10/-; 1-yr with 2.5mm jack plug 10 for 10/-.

BAKERS' Selhurst Speakers, 12in., cast frame, 3, 8 or 15 ohm (state which). Group 25 (25 watt) for guitars, etc. £6.6.0; Stalwart 45-13,000cps, 15W £6.6.0; de Luxe Mk2 dual cone 25-16,000cps. 15W £9 (all carr. paid) less 10% for 2 speakers.

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240  
CLOSED WEDNESDAY. S.A.E. for enquiries please.

## M. & B. RADIO

15a HUNSLET ROAD, LEEDS LS10 1JQ

Telephone: 0532-35649

STEREO CABINETS. A beautifully finished polished wood cabinet supplied in original carton. Size approx. 22 x 16 x 8 in. New 47/6 plus 6/6 carriage.



TELEMETERS. A well finished cabinet containing lots of useful items for the constructor. Endless tape unit and tape head, 2 motors, auto and mains transformers, miniature valve I.F. strip etc. Ideal for modifying or stripping. 77/6 plus 7/6 carr.



STETHOSCOPE HEADSETS. Brand New. Ideal for stereo or mono. Low impedance. 27/6 plus 3/6 pp.

MICROPHONES. Radiotelephone type, used. 5/- plus 2/- pp.

SPRING LOADED aerial base sections. New 6/6 plus 1/6 pp.

TRANSISTORISED 2 METER CONVERTERS. Please state preference of I.F. frequency when ordering. £7.15.0 plus 5/- pp. 4 metre models available at the same price. VHF Marine band model £8.5.0 plus 5/- pp.

VHF MOBILE TX/RX. Miniature valve xtal controlled transmitter with 12 volt transistorised power unit. Internal speaker. Double conversion receiver easily modified to tuneable. Ideal for 4 metres. £9.10.0 plus 27/6 carriage.

MODULATION TRANSFORMERS. scr522 type. 7/6 plus 2/- pp.

AERIAL CHANGE OVER RELAYS 12 volt. Used 4/- plus 1/6 pp.


60 UNTESTED DIODES 2/6 plus 1/- pp.

60 UNTESTED TRANSISTORS 5/- plus 1/- pp.

2-3W. INTEGRATED CIRCUIT AMPLIFIERS.

Tested £1, plus 1/- pp.

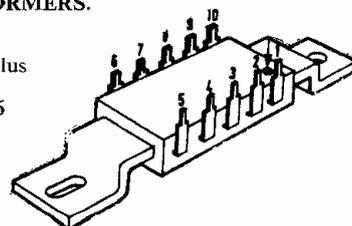USED TESTED VALVES. QQV03/10 6/-, 6AQ5 3/-, 6BJ6 1/6, ECC83 2/6, 5U4 6/-, all plus 1/6 pp.



LOTS OF OTHER EQUIPMENT

PLEASE SEND 6d. PLUS S.A.E. FOR LIST

# DUXFORD ELECTRONICS

## ELECTROLYTIC CAPACITORS (Mullard). -10% to +50%.

Working Voltage (V)		Capacitance (μF)		Price each		Pack Prices				
4V	6.4V	10V	16V	25V	40V	64V	10 off	25 off	100 off	
8	6.4	4	2.5	1.6	1	0.64	1/4	12/4	25/6	89/6
32	25	16	10	6.4	4	2.5	1/2	10/6	23/-	80/3
64	50	32	20	12.5	8	5	1/2	10/4	22/6	77/9
125	100	64	40	25	16	10	1/-	8/9	18/9	63/6
250	200	125	80	50	32	20	1/1	9/6	20/9	70/9
400	320	200	125	80	50	32	1/2	10/4	22/6	77/9
800	640	400	250	160	100	64	1/6	13/4	29/6	102/9
1250	1000	640	400	250	160	100	2/-	18/10	37/9	134/4
2000	1600	1000	640	400	250	160	2/6	22/3	44/3	165/6
3200	2500	1600	1000	640	400	250	3/-	26/9	59/-	204/3
				800	500	320	5/3	46/6	101/-	343/9
				1250	800	500	6/6	57/6	125/4	427/-
				2000	1250	800	8/-	71/4	157/-	541/8
				4000	2500	1600	12/6	91/6	194/9	843/9
				6400	4000	2500	15/-	133/4	291/8	1000/-

## POLYESTER CAPACITORS (Mullard)

Tubular, 10%, 160V:  
Prices per Capacitance value (μF)

each	10 off	25 off	100 off	
0-01, 0-015, 0-022, 0-033, 0-047, 0-068	7d.	5/1	10/11	36/5
0-1	7d.	5/8	11/10	37/6
0-15	8d.	6/6	13/6	43/9
0-22	9d.	6/8	14/3	47/7
0-33	11d.	7/6	16/6	57/3
0-47	1/-	8/2	17/9	61/5
0-68	1/3	10/11	23/3	77/1
1-0	1/6	13/2	28/1	93/9
	2/3	19/7	42/3	140/7
	2/8	23/4	48/9	165/7

Tubular, 10%, 400V:  
Prices per Capacitance value (μF)

each	10 off	25 off	100 off	
0-001, 0-0015, 0-0022	6d.	4/5	9/9	33/4
0-0033, 0-0047	6d.	4/6	9/10	33/6
0-0068, 0-01	7d.	5/1	10/11	36/5
0-015	7d.	5/2	11/10	37/6
0-022	7d.	5/3	12/-	37/9
0-033	8d.	5/8	12/7	42/7
0-047	9d.	6/7	14/5	49/-
0-068	11d.	7/8	16/7	51/-
0-1	11d.	8/-	17/2	57/4
0-15	1/2	10/3	22/-	74/-
0-22	1/6	14/3	28/5	95/10
0-33	2/3	19/7	42/3	140/7
0-47	2/8	23/4	48/9	165/7

Modular, metallised, P.C. mounting, 250V:  
Prices per Capacitance value (μF)

each	10 off	25 off	100 off	
0-01, 0-015	7d.	5/2	11/3	38/7
0-022	7d.	5/4	11/9	41/8
0-033, 0-047	8d.	5/11	12/10	43/9
0-068	9d.	6/7	14/1	47/1
0-1	9d.	6/9	14/9	51/-
0-15	11d.	8/2	18/-	62/6
0-22	1/-	8/9	18/11	63/6
0-33	1/5	12/6	27/-	91/8
0-47	1/8	14/8	31/9	107/10
0-68	2/3	19/10	43/2	146/9
1-0	2/9	23/8	49/8	160/4

## CAPACITORS

Subminiature Polyester film, Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads. ±10% tolerance. 100 Volt Working.  
Prices—per Capacitance value (μF)

each	10 off	25 off	100 off	
0-001, 0-002, 0-005, 0-01, 0-02	6d.	4/3	8/4	30/-
0-05	8d.	6/-	12/6	41/8
0-1	10d.	7/1	15/6	51/-
0-2	1/2	10/-	20/10	68/6

Polystyrene film, Tubular, Axial leads. Unencapsulated. ±5% or ±1pF tolerance. 160 Volt Working.  
Prices—per Capacitance value (μF)

each	10 off	25 off	100 off	
10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 180, 220, 270, 330, 390	5d.	3/7	7/9	24/-
470, 560, 680, 820, 1,000, 1,500	6d.	4/-	8/8	26/8
2,200, 3,300, 4,700, 5,600	7d.	5/-	10/10	33/4
6,800, 8,200, 10,000, 15,000	8d.	6/-	13/-	40/-
22,000	9d.	6/9	18/-	45/4

## POTENTIOMETERS (Carbon)

Miniature, fully enclosed, rear tags, carbon brush wiper. Long life, low noise. Body dia. 1/2 in. Spindle, 1 in. × 1/4 in. 1/2 W at 70°C. ±20% below 1/2 M, ±30% over 1/2 M. Lin. 100 ohms to 10 Megohms. Log. 5 Kohms to 5 Megohms.  
Prices—per ohmic value

each	10 off	25 off	100 off	
	2/-	18/4	41/8	150/-

## GANGED STEREO POTENTIOMETERS (Carbon)

1/2 W at 70°C. Long Spindle. Logarithmic and Linear: 5k+5k to 1M+1M.  
Prices—per ohmic value

each	10 off	25 off	100 off	
	8/-	70/-	162/6	575/-

## SKELETON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1 in. P.C.M. 100 ohms to 5 Megohms (Linear only). Miniature: 0.3W at 70°C. ±20% below 1/2 M, ±30% above 1/2 M. Horizontal (0.7 in. × 0.4 in. P.C.M.) or Vertical (0.4 in. × 0.2 in. P.C.M.). Subminiature: 0.1W at 70°C. ±20% below 2.5M, ±30% above.

Prices—per ohmic value

each	10 off	25 off	100 off	
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

## RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm.): Body: 1/4 W; 8 × 2.8  
1/2 W; 10 × 4.3  
Leads: 35

10% ranges: 10 Ohms to 10 Megohms (E12 Renard Series).

5% ranges: 4.7 Ohms to 1 Megohm (E24 Renard Series).

Prices—per Ohmic value.

each	10 off	25 off	100 off	
1/4 W 10%	2d.	1/6	3/3	10/4
1/4 W 5%	2 1/2 d.	1/9	3/8	11/8
1/4 W 10%	2 1/2 d.	1/9	3/8	11/7
1/4 W 5%	3d.	2/-	4/-	12/10

## SEMICONDUCTORS

Type	1 off	10 off	25 off	100 off	Type	1 off	10 off	25 off	100 off
AC107	3/6	26/3	63/-	232/9	OA5	2/-	15/-	36/-	133/4
AC127	2/6	18/9	45/-	166/3	OA81	2/-	15/-	36/-	133/4
AC128	2/6	18/9	45/-	166/3	OA202	2/-	15/-	36/-	133/4
AD140	8/-	60/-	144/-	533/4	OC23	7/4	58/8	132/-	497/8
AD149	9/-	67/6	162/-	600/-	OC25	6/-	45/-	108/-	399/-
AF115	2/6	18/9	45/-	166/3	OC28	9/-	67/6	162/-	598/6
AF116	2/6	18/9	45/-	166/3	OC35	6/-	45/-	108/-	399/-
AF117	2/6	18/9	45/-	166/3	OC44	3/-	22/6	54/-	199/6
BC107	3/6	26/3	63/-	232/9	OC45	2/6	18/9	45/-	166/3
BC108	3/-	22/6	54/-	199/6	OC71	2/-	15/-	36/-	133/4
BC109	3/6	26/3	63/-	232/9	OC72	2/6	18/9	45/-	166/3
BY234	2/9	24/3	52/4	177/-	OC75	2/4	17/6	42/-	155/4
BY235	3/-	26/3	56/3	187/6	OC81	2/-	15/-	36/-	133/4
BY236	3/3	28/8	61/9	208/4	OC81D	2/4	17/6	42/-	155/4
BY237	3/6	30/8	65/6	218/9	OC82D	2/4	17/6	42/-	155/4
BY238	3/9	34/4	71/6	227/6	OC139	3/4	25/-	60/-	221/8
BYZ10	6/-	45/-	108/-	399/-	OC170	2/6	18/9	45/-	166/3
BYZ11	5/4	40/-	96/-	354/8	OC171	2/6	18/9	45/-	166/3
BYZ12	4/8	35/-	84/-	310/4	2N2926	2/8	20/-	48/-	177/4
BYZ13	4/-	30/-	72/-	266/-	(Green)				

## Thyristors (5 amp)—Stud mounting.

P.I.V.

1 off	10 off	25 off	100 off
100	8/-	60/-	532/-
200	10/-	75/-	665/-
400	15/-	112/6	997/-

## VEROBOARD & ACCESSORIES

0.15 in. Matrix	1 off	10 off	25 off	0.1 in. Matrix	1 off	10 off	25 off
2 1/2 × 3 1/2 in.	3/3	30/-	67/9	2 1/2 × 3 1/2 in.	4/-	37/8	86/-
2 1/2 × 5 in.	3/11	35/10	80/9	2 1/2 × 5 in.	4/6	42/6	96/3
3 1/2 × 3 1/2 in.	3/11	35/10	80/9	3 1/2 × 3 1/2 in.	4/6	43/4	100/-
3 1/2 × 5 in.	5/6	50/-	114/7	3 1/2 × 5 in.	5/6	48/4	111/5

Spot Face Cutter 7/3  
Pin Fitting Tool 9/6  
Terminal Pins 2/- (per 25 off); 6/9 (per 100 off)

SEND S.A.E. FOR 1969 CATALOGUE

## DUXFORD ELECTRONICS (PW) 97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us—at our new Mail Order, Wholesale and Retail Premises)

MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/6

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

## MISCELLANEOUS

**ETCHED PRINTED CIRCUIT BOARD KITS.** Full instructions 19/6 C.W.O. 'Circuit-etch', 12 Cambridge Road, St. Albans, Herts.

**BUILD IT IN a DEWBOX** quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**UFO DETECTOR CIRCUITS,** data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

## THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 29 Maude Street, Darlington, Durham. Send 4d. stamp.

**MUSICAL MIRACLES.** Send S.A.E. for details of Rhythm Modules, versatile bass-pedal unit, self-contained with unique effects, kits for waa-waa pedals. Also new 50uA meters, 25/- post paid. HURRY. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**A CORNUCOPIA OF COMPONENTS!** Scarce valves, selected TV components, Educational and Projects Kits, speakers and cabinets, transistors. Resistors all values 1 watt 3d. each. State your requirements. S.A.E. for details. MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

## 6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent, etc. Fully transistorised, low battery drain. Unbeatable at £2.19.6 post paid.

or in kit form 50/-

## 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed 65/- POST PAID

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop, Shrewsbury, Shropshire S.A.E. for lists

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

**SELL** or exchange for stereo amplifier or W.H.Y. Little used Heathkit Ra-1. Moffett, 11 Riccarton Avenue, Paisley.

**EXPRESS ROTARY SWITCHES.** Switches for Mullard audio circuits, also switches made to customers own specifications. For details and price list, write or phone to 189 Edgware Rd., London W.2. Tel. 01-723 4455.

**BARGAIN PACKS.** 200 assorted springs, nuts, washers, screws. Popular sizes, 7/6 including postage. Cohaven Industrial Estate, Ripley, Derbyshire.

## MISCELLANEOUS (continued)

## SPEAKER CABINET BARGAIN



Beautifully finished in Teak veneer. Size 16 x 8 x 6 in.

Great value at ONLY 72/6 each, p.p. 7/6 or two at 67/6 each, p.p. 10/6. Send SAE for Hi-Fi lists.

ASR-FLETCHER (Audio Equipment)

16 ALBION ROAD, BIRCHINGTON, Kent

**PRINTED CIRCUITS** Prototype, Medium and Batch Production of all types of circuits. Design and layout facilities available. Brooklands Plating Co., Spices Yard, South End, Croydon. Tel. 01-688-2128.

## WANTED

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.

**WE BUY** New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

**WANTED NEW VALVES,** televisions, radiograms, transistors, etc. STAN WILLETTS, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

**AVO METERS, MODELS 8 & 9, ANY QUANTITY, ANY CONDITION, ALSO WEE MEGGERS. SEND FOR PACKING INSTRUCTIONS. HUGGETT'S LTD., 2/4 PAWSONS ROAD, W. CROYDON.**

## WANTED NEW VALVES ONLY

Must be new and boxed  
Payment by return

**WILLIAM CARVIS LTD**  
103 North Street, Leeds 7

**GEC RELAYS, SEALED,** 12v, 180 ohms, four make-before-break contacts. Also tantalum Capacitors 750uF, 3v. Any quantity. 021-454-8305.

## SHORT-WAVE LISTENERS

**INTERESTED IN SHORTWAVE RADIO?** Then you'll be interested in the Radio World-wide Listeners Club! Thousands of members throughout the world now receive a magazine filled with special features dealing with almost every aspect of communications (including SWL) and electronics. Discover the Club. Write for your free sample issue of the Radio World wide magazine or join now, dues are just 8/4 for your first year. **RADIO WORLD-WIDE LISTENERS CLUB, WNYW International, Dept. 188, 485 Madison Avenue, New York 10022 USA.**

## SERVICE SHEETS

**SERVICE SHEETS, RADIO, TV, 5,000 Models.** List 1/6. S.A.E. Enquiries. TELRAY, 11 Maudland Bank, Preston, Lancs.

**SERVICE SHEETS (75,000) 5/-** each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

**SERVICE SHEETS (1925-1969)** for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/- Over 8,000 models available. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

**RADIO, TELEVISION** over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

## FOR SALE

## MORSE MADE !!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 8-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to: 680HS (BOX 11), 45 GREEN LANE, PURLEY, SURREY

**FANTASTIC SALE.** 1,000 of the following Amplifier Kits to clear:

	List price	SALE price	P.8
5 watts	£3.15.0	£1.17.6	9V
7 watts	£6.19.0	£2.7.6	9V
10 watts	£8.19.0	£2.17.6	9V

**M. GLEAVES & BROTHER,** 28 Wenny Estate, Chatteris, Cambs.

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

## ELECTRICAL

**240 volt ELECTRICITY ANYWHERE** 

**BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scope Purchase. The fabulous **M.L. 2D American Heavy Duty Dynamotor Unit** with a massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere.

Brand New and Fully Tested, only £419.6, plus 10/6 postage, C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. PW STANFORD ELECTRONICS, Rear Derby Road, North Promenade, Blackpool, Lancashire.

**BOOKS & PUBLICATIONS**

**SURPLUS HANDBOOKS**

- 19 set Circuit and Notes .. 6/6 p/p 6d.
- 1155 set Circuit and Notes .. 6/6 p/p 6d.
- H.R.O. Technical Instructions .. 5/6 p/p 6d.
- 38 set Technical Instructions .. 5/6 p/p 6d.
- 46 set Working Instructions .. 5/6 p/p 6d.
- 88 set Technical Instructions .. 7/- p/p 6d.
- BC.221 Circuit and Notes .. 5/6 p/p 6d.
- Wavemeter Class D Tech. Instr. .. 5/6 p/p 6d.
- 18 set Circuit and Notes .. 5/6 p/p 6d.
- BC.1000 (31 set) Circuit and Notes .. 5/6 p/p 6d.
- CR.100/B.28 Circuit and Notes .. 10/- p/p 9d.
- R.107 Circuit and Notes .. 7/- p/p 6d.
- AR.88D Instruction Manual .. 18/- p/p 6d.
- 62 set Circuit and Notes .. 6/6 p/p 6d.
- Circuit Diagram 5/-** each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.
- 52 set Sender and Receiver circuits 7/6 post free

Colour code Indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

**INSTRUCTIONAL HANDBOOK SUPPLIES**

DEPT. PW, TALBOT HOUSE,  
28 TALBOT GARDENS, LEEDS 8

**EDUCATIONAL**

**RADIO OFFICERS** see the world! Sea-going and shore appointments. Trainee vacancies during 1970. Grants available. Day and Boarding students. Stamp for prospectus, Wireless College, Colwyn Bay.

**BECOME** "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

**CITY & GUILDS** (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. **B.I.E.T.** (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

**RADIO OFFICER** training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

**TRAIN FOR SUCCESS WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE** prospectus and find out how ICS can help you in your career.

**ICS, DEPT. 541, INTERTEXT HOUSE, STEWARTS ROAD, LONDON, SW8**

**METAL WORK**

**METAL WORK:** All types cabinets, chassis, racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough

**SITUATIONS VACANT**

**TAPE RECORDER ENGINEER** required for workshop repair of **DICTATING MACHINES** in Central London. Write to **PAX-DICTATOR (SOUTHERN) LTD.**, Lysons Ave., Ash Vale, Aldershot.

**SERVICE ENGINEERS**—we are an old established electronics company, but headed by a young management team and we need you to help us. Age is no barrier to a high salary as you will find out when you join us. If you have experience in T.V., Radio or Hi-Fi Service and want a job that looks ahead phone Michael Adler at 01-636 9606.

**SERVICE ENGINEER.** We specialise in the repair and maintenance of 16 mm. Sound Projectors, Tape Recorders and similar Visual Aids Equipment. We need another engineer with some knowledge of Audio Amplifiers. Must be able to drive. Write: Burgess Lane & Co. Ltd., Thornton Works, Thornton Avenue, Chiswick, London W.4.

**TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc.** on "Satisfaction or Refund of Fee" terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

**ENGINEERS. A TECHNICAL CERTIFICATE** or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for **FREE** 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

**HENRY'S RADIO LTD.**

303 EDGWARE ROAD, LONDON, W.2

HAVE THE FOLLOWING VACANCIES IN THEIR ORGANISATION.

**Sales Assistants**

Young man with good general knowledge of electronic components required for our retail sales dept. Please Phone 723-1008/9 Extn. 1.

**Sales Assistants Hi-Fi Dept.**

Young man with a good general knowledge of **HIGH FIDELITY EQUIPMENT** required for our retail **HI-FI SALES DEPT.** Please contact Mr. STEVENS Telephone 723-6963.

**RECEIVERS & COMPONENTS**

**BARGAIN PARCELS**

Any 5, 9/-; 10, 14/-; 100, £5.10.0 from the following:

- ECC82, ECL80, EF80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PCF80, PCL82, PCL83, PCL84, PL36, PL81, PY33, PY81, PY82, U191, 6-30L2, 30FL1, 30F5.

**U.H.F. AERIAL BOOSTER**

Transistorised, cavity tuned, high-gain. All uhf channels. Complete with battery and lead, 69/-, p. & p. 1/-. **VELCO ELECTRONICS**, 62 Bridge Street, Ramsbottom, Bury, Lancs.

**FOR TOP DISCOUNT ON**

Changers, Amplifiers, Speakers

visit the

**HI-FI CENTER**

15 Market Shops, Victoria Road  
**CHELMSFORD, Essex**

**RECEIVERS & COMPONENTS**

(continued)

**WE ARE BREAKING UP COMPUTERS**

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in. packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/-. P. & P. 2/-. With a guaranteed minimum of 35 transistors.

**SPECIAL BARGAIN PACK.** 25 boards for £1, P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 55/-. P. & P. 7/6. With a guaranteed minimum of 350 transistors.

**GIANT PANELS.** 5 1/2in. x 4in., min. 20 transistors, 9 x 56 µH inductors, resistors, diodes, etc. 3 for £1. P. & P. 2/-.  
As above, only 21 transistors, 70 diodes, 62 min. 1/10th W resistors. 3 for 25/-. P. & P. 2/-.  
**PANELS** with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-. P. & P. 2/-.  
**TRIM POTS.** On 2in x 4in boards + Ta caps and other components. Ideal for organ keyboard tuning etc. 100Ω, 500Ω, 15K., 20K. State requirements. 5 boards 10/-. P. & P. 2/-.  
**NPN GERMANIUM TO5 1 WATT POWER TRANSISTORS.** On small heat sink, on 2in. x 4in. panel. 5 for 10/-. P. & P. 2/-.  
**POWER TRANSISTORS.** Sim. to 2N174 ex-eqt. On Finned Heat Sink (10D). 4 for £1. P. & P. 5/-.  
**DIODES.** Ex eqpt., Silicon, 150 PIV, 10 amp. 4 for 10/-. 150 PIV, 20 amp. 4 for £1. Post free.  
**MINIATURE GLASS NEONS,** 13/6 doz.  
**PAPST FANS.** Powerful Extractor/Blower fans. 4 1/2in. x 4 1/2in. x 2in. 230/250V. 100 c.f.m., 2,800 r.p.m. 50/- post free.  
**SPRAGUE POLYESTER.** 0.22µF 250V small capacitors. 5/- doz. P. & P. 1/-.  
**SPRAGUE ELECTROLYTICS.** 4µF 150V. 5/- doz. P. & P. 1/-.  
**NON-POLAR TANTALUM CAPS.** 2.2µF 50V. 10/- doz. P. & P. 1/-.  
**NEW MIXED COMPONENTS**  
150 High stab. resistors 5% and better. 12/6. P. & P. 1/-.  
250 mixed resistors 1/2W + 1/4W. 12/6. P. & P. 1/-.  
Large handful of mixed capacitors. 12/6. P. & P. 1/-.  
**LARGE CAPACITY ELECTROLYTICS**  
4 1/2in., 2in. diam. Screw terminals.  
7/6 each post free.  
4,000µF 72V d.c. wkg.  
10,000µF 25V d.c. wkg.  
25,000µF 12V d.c. wkg.  
4 1/2in. x 1 1/2in. Plessey 5,000µF 55V d.c. wkg.  
8/- each. 3in. x 1in. Plessey 2,000µF 25V d.c. wkg.  
6/- each. 4 1/2in. x 1 1/2in. screw terminals 2,500µF 55V d.c. wkg. 6/- each.

**KEYTRONICS,** 52 Earls Court Road  
London, W.8. Mail order only

Tel. 01-478 8499

**NEW VHF KIT**

Receives Television Sound, Ambulances, Aircraft, Radio 2, 3 and 4 on VHF etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. The Kit comes with easy to follow instructions and circuit. Powered by 9v Battery. Complete with built in Jack Plug Socket for use with Earphones or Amplifier.

ONLY 57/-, P. & P. FREE U.K. ONLY

Postal Orders, Cheques to

Dept. P.W.6

Galleon Trading Co., 298A Lodge Lane, Romford, Essex.

**NEW DEVICES AT LOWEST PRICES**  
GE PA230 Audio Preamplifier 18/6 each.  
GE PA234 IW Audio Amplifier 17/6 each.  
GE PA237 2W Audio Amplifier 32/6 each.  
GE 2N5172 NPN 200mW Transistor 1/9 each.  
All with data. C.W.O. P. & P. 1/- per order.  
**JEF ELECTRONICS,** York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order only.

**ATTENTION,** Radio Constructors, Amateurs, Hi-Fi and Electronic addicts, we can supply all your needs at competitive prices. Send 9d. for lists to **INVENTRONICS**, 14 Elizabeth Drive, Ferrybridge, Yorkshire.

**RECEIVERS & COMPONENTS**  
(continued)

**VHF RADIO TELEPHONE UNITS**

These work in the freq range 80 to 100Mc/s, boot mounting type, the Rx is a crystal controlled double conversion type, the Tx and Rx sections use 16 valves and 14 transistors. Valves Rx section 8B8C, EF95x3 6BH6x6 108C Stab. Tx section QQV03-10, 5763, EL85x2, 12A7T the Modulator, A.F. Amp and O/P stage are all Transistorised. HT to the Tx and Rx sections is provided by 2 separate transistor invertors, also 4 control and Ae c/o relays are fitted. These units are for use on 12V + Ea systems, supplied with outer cover size 11x6x18in., these units are supplied less crystals in good internal condition, slightly soiled over cases through normal use.

Price £15 plus 10/- carr.

**12 VOLT TRANSISTOR INVERTORS**

For use on 12V + or - Ea systems O/P, +250V DC at 100mA and -25V bias fully smoothed, two 12V control relays are also fitted. Well made unit fully enclosed in box, size 8 1/2 x 3 1/2 x 3in. in good condition.

Price £3 plus 4/6 post.

**SPEAKER CONTROL UNITS**

These contain: speaker 3in. 3 ohm, volume control swt type, Tx/Rx sel swt, 12V lamp and jack socket, these are a neat, well made unit, size 6x4x3in. In good condition.

Price 15/- plus 5/- post.

**SMALL BOXES**

These are a plain All box with hinged lid, overall size 3 1/2 x 2 1/2 x 1 1/2" supplied new.

Price 10 for 10/- post paid.

**12 or 24V DC SUPPLY UNIT**

1/P 200/250V O/P 12V D.C. at 3 amps twice, can be connected to give 12V 6a or 24V 3a fitted mains fuses and swt. These units are of robust construction and will supply 5a, with circ. Supplied in good used condition.

Price £3/5/- plus 12/6 carr.

**MINIATURE PLUGS & SOCKETS**

These are a very good quality plug and socket with cover and cable clamp available in the following ways:

26 way 4/-, 18 way 3/-, 14 way 2/6, 7 way 2/- price per pair. Post paid.  
Ex modern equipment in good condition.

**TWIN RELAYS**

These are two relays mounted on a common base, each relay as two coils of 50 and 500 ohm and will work on 6 or 12V D.C. contacts on one relay 3 N.C., 1 N.C. 1 C/O other relay 2 C/O and 2 N.C., these are new ex equipment. Can be cut to make two relays.

Price 7/6 each, post paid.

**METERS**

Edgewise reading type 1mA movement scaled 0 to 2000 yds. linear scale, 10 divisions black face, white letters, size overall 2 1/2 by 1 1/2 by 3 1/2in. deep, good quality, ex equipment.

Price 17/6 plus 2/6 post.

**MAINS TRANSFORMERS**

Primary 230V 50 c/s. Secondary 350-310-0-310-350 at 220mA, 5V at 6a, 6.7V at 5a, 6.3V at 3a twice, 6.3V at 1a twice. Potted type, ex equipment.

Price 35/- plus 7/6 carr.

Matching choke 10H, 250mA, 17/6 Primary 240V, 50c/s. Secondary, 0-1-22-23-24V at 2a, 20V at 2a, 6.5V at 5a, 6.5V at 1a, 20V at 250mA. Ex equipment.

Price 22/6 plus 6/- post.

**CONTROL PANEL**

Contains 15 miniature pots as follows: 1 meg X6, 100K X8, and 1K. All have 1/4-dia. shafts with single nut fixing min. shaft size 3/16in., body size 2 x 1/2in. ex equipment, good condition.

Price 12/6 plus 3/- post.

**A. H. SUPPLIES**  
57 Main Road  
Sheffield S9 5HL

Shop open Mon., Wed., Fri. and Sat. only

**RECEIVERS & COMPONENTS**  
(continued)

**BARGAIN LIST**

Transistors OC44, OC71, OC72, OC45, at 2/- each. OC140, BSY26, BYZ12, BYZ16 at 8/- each. Metal Rectifiers, 12V lamp contact cooled toc, 3/9 each. Metal Rectifiers, 12V 2amp at 3/9 each. Metal Rectifiers, 12V 4amp at 7/6 each. TV Metal Rectifiers, 250v 200mA at 4/6. Edgewise Volume Controls 5k Jap Replacements, 3/6 each. Panel Meters, new square Clear Plastic, 1.65 x 1.65 0-1ma Front at £1.00 each. Panel Meters 500 micro amp at £1.40 each. Toggle Switches 8PST, 2/6, DPDT at 8/- each. New Resistances small 1/2 watt, at 3d. each. Transformers-Subminiature output 3 ohms for OC72 etc. at 2/8 each. Transformers-Subminiature Driver for above at 2/6 each. Jack Plugs Standard at 2/-, Jack Sockets at 1/9. Fax Panels 6in. x 4in. x 1/16in. at 10d. 8in. x 6in. at 1/8 each. Condensers 25mf 25v at 1/-, 4in. Iron dust cores at 6d. per doz. Miniature slide switches DPDT at 1/8 each. Aluminum Panels 6in. x 4in. at 1/8. 8in. x 6in. at 2/- each. Earpieces with lead and 3-5 mm Plug 1/9. Mail Order Only. Post & Packing 1/- S.A.E. for List.

**HALSE SERVICES**

36 GLOUCESTER ROAD, FELTHAM, MIDDLESEX

**Stella Nine Range Cases**

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

**LIST OF PRICES AND SIZES**

which are made to fit Standard Alloy Chassis

Width	Depth	4" Height		6" Height		7 1/2" Height	
		£ s. d.	£ s. d.	£ s. d.	£ s. d.	£ s. d.	£ s. d.
6 1/2"	3 1/2"	12	6	15	0	18	0
6 1/2"	4 1/2"	13	6	16	0	19	0
8 1/2"	3 1/2"	15	0	1	0	1	0
8 1/2"	4 1/2"	1	1	1	6	1	11
10 1/2"	3 1/2"	1	8	1	15	1	18
10 1/2"	4 1/2"	1	1	1	6	1	11
12 1/2"	3 1/2"	1	8	0	14	0	17
12 1/2"	4 1/2"	1	16	0	2	3	2
14 1/2"	3 1/2"	1	5	0	11	6	14
14 1/2"	4 1/2"	2	2	0	25	9	28
16 1/2"	6 1/2"	1	18	6	2	6	3
16 1/2"	10 1/2"	2	10	0	3	5	0

Cases—Post 4s. 6d. per order.  
Discounts available on quantities.

**CHASSIS in Aluminium, Standard Sizes, with Gusset Plates**

Sizes to fit Cases. All 2 1/2" Walls

6" x 3"	5" 6"	10" x 7"	8" 6"	14" x 8"	7" 3"
6" x 3"	5" 6"	10" x 7"	8" 6"	14" x 8"	7" 3"
8" x 3"	6" 6"	12" x 8"	7" 6"	16" x 8"	10" 9"
8" x 6"	7" 9"	12" x 8"	10" 9"	16" x 10"	16" 0"

Chassis—Post 3s. 0d. per order.  
Discounts available on quantities.

**E. R. NICHOLLS**

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

**HI-FI loudspeaker systems** for the home constructor, cabinet kits, the new range of Peerless speakers, speaker kit systems and cross-over networks. BAF wadding, speaker fabric (samples on request) and all other necessary components. Send 5d in stamps to: AUDIOSCAN, Dept. PW, 4 Princes Square, Harrogate, Yorks.

**COMPLETE RANGE of Amateur, Aircraft, Communications receivers.** Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

**EMSAC FOR ANTENNA SYSTEMS AND CONVERTERS.** Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD., Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

**RECEIVERS & COMPONENTS**  
(continued)

**COMPONENTS**

EVERYTHING you need—capacitors, trimmers, resistors, pots, VDR's, thermistors, meters, Veroboard, switches, solder, wires and cables, tagboards and strips, screws, nuts, knobs, panel lamps and bulbs, plugs and sockets, etc. etc., not to mention VALVES AND SEMICONDUCTORS.

Full price lists free on request

J. R. HARTLEY  
78B High Street Bridgnorth Shropshire

**BRAND NEW ELECTROLYTICS, 15/16 volt, 0.5, 1, 2, 5, 6, 8, 10, 15, 20, 30, 40, 50, 100, 200 mfd. 8/- per dozen postage 1/-.** The C. R. Supply Co. 127 Chesterfield Road, Sheffield 8.

**TO HELP THE HOME CONSTRUCTOR,** Heathkit now make available our surplus Resistors, Capacitors, etc. at Bargain prices. Send for lists. E. Moyle, Daystrom Ltd., Gloucester.

**150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 1-20 watt, 15/- Post Free. WHITAM ELECTRIC, 33 Drayton Green Road, West Ealing, W.13.**

**AERIALS**

**S.W.Ls & M.W. DXers**

Whatever your receiver or aerial, you'll be AMAZED at the improvement our JOY-MATCH tuners will make:

Type 3A (Full Short Wave coverage);

£4.4.0

Type 2A (Full Medium Wave coverage);

£4.6.0

Type SM (Short and Medium Wave) NEW;

£5.10.6

plus 4/6 p.p.

FULL MONEY BACK GUARANTEE

**Partridge Electronics**

LTD. (PW)

CAISTER HOUSE, PROSPECT ROAD  
BROADSTAIRS, Kent. Tel: 0843 62535

**BAKER AND BAINES**

All aerials available—Engineered to a high standard. Specials and DX made to order. BBC dipole 30/-, H 42/-, 3 ele 89/-, 4 ele 120/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/5, 11 ele 57/6, 13 ele 71/-, ITA double 8 112/-, 11 ele 140/-, 13 ele 159/-, Combined BBC/ITA D + 5.45/-, D + 8 52/-, H + 5 69/-, X + 5 75/-, BBC2—ITV2 8 ele 29/-, 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, double 22 ele 142/-, FM dipole 21/-, H 38/-, 3 ele 65/-, All aerials suitable loft mounting where space permits. Special high-gain loft BBC1/ITA for confined space with pole, joist bracket and swivel joint 37/-, Co-ax low loss 1/3 per yard—Ultra low loss 2/3 per yard. Co-ax plugs 1/4. Band I/III diplexers 8/3, I/II/III triplexers 13/6. Feed BBC1—ITA—BBC2 all down the same co-ax using pair matched UHF/VHF diplexers, 21/3 pair. Chimney lashings 15/-, 19/-, 5ft. cranked arm pole 10/4, 3ft. arm 6/3, 16ft. x 2in. poles 59/-, Clamps, couplers, etc. Signal boosters BBC2 97/6. Combined BBC1/ITA 75/6.

All cathode Ray Tubes Brand New not rejuvenated (full 2 years guarantee) at sensible prices 14in. £6, 17in £6, 19in. £7.15.0, 21in. £7.15.0, 23in. £9, Twin Panel 19in. £12, 23in. £15.7.6, Ringuard 19in. £10.9.0, 23in. £13.14.0. SAE for full details please.

Most Television Valves available Brand New for extra performance 3 months guarantee, 15% off standard price. SAE will bring full lists.

Carriage: Aerials paid. Accessories—according to weight. TV Tubes 12/6. Insurance 5/- extra. Valves 9d.

11 Dale Crescent, Tupton, Chesterfield.

**TRANSCEIVER.** New and unused Hallicrafter SR 2000 with P/S console and matching aerial all with maker's Warranty, £470 o.n.o. WARE, Sumach, Mill Hill, Edenbridge 3305.

PLEASE MENTION  
"PRACTICAL WIRELESS"  
WHEN REPLYING TO  
ADVERTISEMENTS

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

**JOHNSON'S (RADIO)**  
St. Martin's Gate, Worcester

**ELECTRAMA**  
FANTASTIC  
SPEAKER BARGAIN  
Famous English, 12" high flux, heavy cone, 10 watts speaker with built-in tweeter. 3 or 15 ohms. **39/6** (P. & I. 4/9)  
2 for 70/- (P. & I. 6/9)  
NEW RELEASE  
HI-FI COLUMN  
SPEAKER CABINET  
Beautifully made. Suitable for 7-12" speakers. Rosewood finish. Screwed and glued. Attractive grey cloth front measures 24" x 13" x 10" with tweeter hole above. Mark 11 **95/-** Carr. de luxe model 10/-  
With 12" speaker as advertised above £65.0. (carr. 10/-)  
Dept. PW1, 15 High St, Hailsham, Sussex



## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE


IR5 5/6	DL94 5/9	EY51 6/9	PL84 6/6
IS5 4/3	DL96 6/9	EY96 5/9	PL900 12/9
LT4 2/9	DY86 2/9	EZ99 2/9	PL504 12/8
384 5/9	DY87 4/9	EZ81 4/6	PY29 10/-
3V4 5/9	EABC80 5/9	KT61 8/3	PY33 10/-
6AQ5 4/3	EBCA1 9/3	KT66 15/9	PY81 5/-
6V6G 3/-	EBF80 6/-	N78 17/-	PY82 5/-
25L6GT 4/6	EBF89 5/9	PABC80 6/9	PY83 5/3
30C18 11/3	ECC82 4/9	PC86 10/3	PY88 6/6
30FL1 13/6	ECC83 4/9	PC88 10/3	PY860 6/3
30FL2 12/4	ECC85 5/-	PC97 8/3	PY801 6/3
30FL14 11/9	ECH35 5/6	PC900 7/-	R19 6/3
30P4 11/6	ECH81 5/-	PC884 6/3	U26 12/9
30P19 11/6	ECL80 6/3	PCC89 8/11	U26 11/6
30FL1 13/6	ECL82 6/3	PCF89 5/11	U191 12/-
30FL13 14/9	ECL86 7/6	PCF801 6/6	U193 9/6
CCH35 13/-	EF37A 6/-	PCF802 8/6	UABC80 6/-
CL35 17/6	EF39 4/6	PCF805 11/3	UBO41 8/3
DAC32 6/9	EF80 4/6	PCF808 11/9	UBF89 6/3
DAP91 4/3	EF85 4/9	PCL82 6/9	UCC86 6/6
DAF96 6/3	EF86 6/3	PCL83 8/9	UCH42 10/6
DF33 7/6	EF89 4/3	PCL84 7/-	UCH81 6/-
DF91 2/9	EF183 5/6	PCL85 8/-	UCL82 6/9
DF96 6/3	EF184 5/3	PCL96 8/-	UF41 10/6
DK32 6/9	EH90 6/-	PFL20011/-	UF89 6/3
DK91 5/6	EL33 8/3	PL36 9/3	UL41 10/3
DK96 6/6	EL94 9/3	PL31 7/-	UL84 8/3
DL55 4/9	EL41 10/3	PL82 5/9	UY41 7/-
DL92 5/9	EL84 4/9	PL83 6/3	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

**GERALD BERNARD**  
83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON, N.16

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

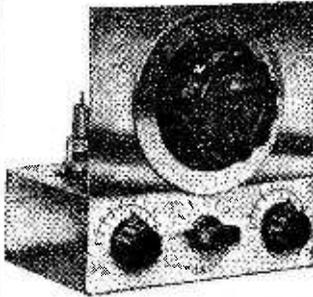

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

#### IMPROVED 1970 RANGE

One-valve model "DX", complete kit—price 56/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, so all our products—fully guaranteed. Full range of other S.W. kits including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

## TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND  
LONDON WC2

Make	Model	Radio/TV

1969 List available at 2/- plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....  
(and a stamped addressed envelope)  
s.a.e. with enquiries please

MAIL ORDER ONLY (January PW)

## PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE,  
YORKS. Tel. Heckmondwike 4285

Indicator Unit Type 26. Size 12 x 9 x 9in. With Outer Case fitted with 2 1/2in. CRT Type CV1526 9 B7C Valves. Fair condition but not tested. 32/6, p. & p. 10/-.

Aircraft Sighting Head with Gyro Unit. Condition fair. 18/6, carriage B.R.S. 12/-.  
Small 12-way Plug and Socket, 1/6 each. p.p. 1/-.  
15/- per doz. p.p. 3/6. Ex unit.

Panel of 19 mixed pots. 5/- post paid. Ex unit.  
Panels of Resistors and Condensers. 8/- per doz. post paid. Ex unit.

N.S.F. Toggle Switches. Ex Units. Single pole 9d. each, post 1/-; 12 for 8/- post paid. Also with centre off at same price.

Complete untested 17 inch T.V. Sets 12 channel 50/-, 15/- carriage.

Model Makers Motor with Train of Gears. 24 volts. Will run off 12 or 6 volts at slower speeds. 5/-, post and packing 3/6.

Speakers removed from T.V. Sets. All PM and 3 ohm. 6in. round 3/-, p. & p. 3/-; 6 for 24/-, post paid. 6 x 4in. 3/-, p. & p. 3/-; 6 for 24/-, post paid. 5in. round 3/-, p. & p. 3/-; 6 for 24/-, post paid. 7 x 4in. 5/-, p. & p. 3/-; 6 for 34/-, post paid. Slot Speakers 8 x 2 1/2in. 5/-, p. & p. 3/-; 6 for 30/- post paid.

Reclaimed T.V. Tubes, with 6 months' guarantee 17in. Type AW43/80, AW43/88 40/-, MW43/69 30/-, 14in. Type 17/-, All Tubes 12/- carriage.

Silicon Rectifier 500mA 800 PIV, 2/6 post paid. 24/- per dozen, post paid.

Jap Earpiece. Magnetic 8 ohm. Small and Large Plug 1/11 post paid.

G.P. Diodes 3/6 per dozen, post paid.

Top Grade Mylar Tapes, 7in. Standard 11/6, 7in. Long Play 14/-, 7in. Double Play 19/6, 5in. Standard 7/9, 5in. Long Play 10/-, plus post on any tape 1/9.

VALVE LIST—Ex Equipment, 3 months' guarantee Single Valves Post 7d., over 3 Valves p. & p. paid

ARP12 1/6	PCL82 4/-	6B8 1/8
EB91 9d.	PCL83 5/-	6BW7 2/6
EF85 3/-	PL35 5/-	6K7 1/9
EBF80 3/-	PL38 6/-	6U4 5/-
ECC81 3/-	PL81 4/-	6P28 5/-
ECC82 3/-	PY33 5/-	10P18 2/6
ECC83 4/-	PY61 1/6	188BT 8/6
ECL80 1/6	PY82 1/6	20D1 3/-
EF50 1/-	U191 5/-	30P1 5/-
EF80 1/6	U981 5/-	30PL1 5/-
EF91 9d.	U282 5/-	30P12 5/-
EY86 5/-	U801 5/-	30P5 2/6
PC84 2/-	U329 5/-	30FL1 5/-
PCF80 2/-	U251 5/-	6/30L2 5/-

## P.W. PARTS KITS

P.W. LOW COST HI-FI

January-February, 1968

Basic Plus Pre-Amp Kit	£ 3 1 0
Basic Plus Pre-Amp Kit—Stereo	6 15 6
Power Amplifier Kit (2 required for stereo)	2 10 0
Power supply kit	4 4 6

## P.W. F.M. TUNER

P.W. February-March, 1969

Complete Kit	8 0 0
Stereo Decoder for this tuner available soon. Parts available separately.	

S.A.E. for list.

**C & D ELECTRONICS,**  
17 St. Luke's Road,  
Pallion,  
Sunderland

Head Office and Warehouse  
 44A WESTBOURNE GROVE  
 LONDON W2  
 Tel. PARK 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office  
 When sending cash with order, please include 2/6 in £ for postage and handling  
 MINIMUM CHARGE 2/6. No C.O.D. orders accepted.

Retail Shop  
 85 TOTTENHAM COURT ROAD  
 LONDON W1  
 Tel. LAngham 8403  
 Open all day Saturday

0A2 8/6	6AU4GTA	6DS4 15/-	9RW6 8/6
0A3 9/-	6AU5GT	6E12 11/-	10C2 10/-
0B2 8/6	6E12 11/-	6E17 8/6	10D1 8/-
0B3 10/-	22/6	6EJ7 7/6	10D2 8/-
0C3 7/-	6AU6 5/-	6EW6 12/-	10F1 13/-
0D3 6/6	6AV5GTA	6F1 14/-	10F9 10/-
1B3GT 7/6	6F1 14/-	6F6G 5/-	10F18 8/-
1I4 3/6	6AY6 9/6	6F11 6/6	10L1 8/-
1N3GT 8/6	6AWSA11/-	6F12 4/6	10LD11 11/-
1Q5GT 10/-	6AX5GT	6F13 7/6	10P13 11/-
1R4 6/6	6F14 12/-	6F14 12/-	10P14 20/-
1R5 7/6	6BA6 4/6	6F15 11/-	12A5 10/6
1S4 5/6	6EB25 5/6	6F18 8/6	12AC6 7/6
1S5 5/6	6EB75 16/-	6F22 8/6	12AD6 7/6
1T4 4/6	6EB76 9/6	6F23 15/6	12A7GT 5/-
1U4 6/6	6BC6G 12/-	6F24 13/6	12A7GT 5/-
1U5 9/6	6B16 8/6	6F25 15/-	12A5 8/6
1V2 9/6	6B76 8/6	6F26 7/6	12AQ5 8/6
1X2B 7/6	6BK4 21/-	6F28 14/-	12AT6 5/6
2CW4 12/-	6BK7A 10/-	6F29 8/6	12AT7 6/6
2D21 6/6	6BL7GTA	6F30 7/6	12A06 9/6
3A4 4/6	6C4 12/-	6F4 9/6	12A07 6/6
3A5 10/6	6BL8 7/6	6G7 8/6	12AV6 6/6
3A8GT 10/6	6C4 12/-	6G7 8/6	12AV7 7/6
3Q4 8/6	6BN4 12/-	6K6GT 10/6	12AX4GTB
3Q5GT 8/6	6BN6 8/6	6K7 6/6	12AX4GTB
3S4 7/6	6BQ5 5/6	6K8G 6/6	12AX7 6/6
3V4 8/6	6BQ6 5/6	6K8S 10/6	12AX7 13/6
5R4GY 11/-	6BQ6GT 6/6	6K26 15/6	12B7 13/6
5U4G 6/6	6C1 13/-	6L6GT 9/6	12BA6 6/6
5U4GB 7/6	6BQ7A 7/6	6L7 6/6	12BA7 6/6
5V4 8/6	6BR8 13/-	6L18 6/6	12BE6 6/6
5Y3GT 6/6	6BS7 20/-	6LD20 6/6	12BH7 6/6
5Z3 9/6	6BWW 16/6	6M7GT 7/6	12BY7 10/6
5Z4G 7/6	6C1 13/-	6M7 8/6	12C3 6/6
5Z4GT 6/6	6BW7 13/6	6P28 12/6	12CU6 15/6
6A8G 15/6	6BX6 5/6	6Q7 7/6	12J5GT 4/6
6A8G 6/6	6C26 6/6	6B7G 7/6	12K5 10/6
6A8G 6/6	6C5GT 7/6	6B82 8/6	12K7GT 7/6
6A8G 4/6	6C9 17/6	6B84 11/-	12K8 10/6
6A8G 4/6	6C14 5/6	6B87 7/6	12L7 5/6
6A8G 10/6	6CA7 10/6	6B87 7/6	12M7 5/6
6A8G 5/6	6CB6 5/6	6BK7 6/6	12NH7 5/6
6AK5 6/6	6CD6GA	6BL7GT 6/6	12S7 5/6
6AK6 11/6	6C6 23/-	6BN7GT 6/6	12S7 5/6
6AL3 8/6	6C6 23/-	12S7GT 8/6	12S7GT 8/6
6AL5 8/6	6C6H 11/-	6B7 7/6	12S7GT 8/6
6AM5 5/6	6CL6 10/6	6B8 6/6	12S7GT 8/6
6AM6 4/6	6CU6 13/-	6U4GT 12/6	12S7GT 8/6
6AQ5 6/6	6CW4 12/6	6U8 7/6	12S7GT 8/6
6AQ6 10/6	6CY5 8/6	6V6GT 6/6	12S7GT 8/6
6AR5 6/6	6D7 12/6	6X4 5/6	14S7 6/6
6AR6 6/6	6D8 8/6	6D1 8/6	20D1 10/6
6AS5 7/6	6DC6 13/6	6X8 11/-	20L1 20/6
6AS7G 16/6	6DK6 8/6	6Y6G 12/6	20P1 10/6
6AT6 5/6	6DQ6B 12/6	6Z4 5/6	20P3 12/6

## First Quality Fully Guaranteed




## ELECTRONIC VALVES

20P4 20/-	85A2 7/6	DY87 7/6	ECL81 8/6
20P5 20/-	90A3 48/-	DY82 10/6	ECL82 8/6
25C5 9/6	90AV 48/-	E557 5/6	ECL83 12/6
25L6GT 7/6	90C1 25/-	E130L 90/-	ECL84 11/-
25Z4G 6/6	90CV 25/-	E180F 19/-	ECL85 10/6
25Z6GT 13/-	90CV 25/-	E280F 48/-	ECL86 8/6
30A5 8/6	307 8/6	EABC80 6/6	EF37A 9/6
30A5 8/6	307 8/6	EAF42 10/-	EF39 9/6
30A5 8/6	307 8/6	EAF801 9/6	EF40 10/6
30C1 6/6	308A 14/-	EB3 9/6	EF41 12/6
30C15 15/6	6080 27/6	EB3 9/6	EF42 14/6
30C17 16/6	6146 30/6	EB3 9/6	EF43 13/6
30C18 15/6	6146 30/6	EB3 9/6	EF44 13/6
30P5 17/6	6287 8/6	EB3 9/6	EF45 13/6
30PL1 15/6	6380 25/6	EB3 9/6	EF46 13/6
30PL12 18/6	6380 25/6	EB3 9/6	EF47 13/6
30PL13 10/6	6380 25/6	EB3 9/6	EF48 13/6
30PL14 15/6	7199 15/6	EB3 9/6	EF49 13/6
30L1 7/6	7586 25/6	EB3 9/6	EF50 13/6
30L1 7/6	7586 25/6	EB3 9/6	EF51 13/6
30L1 7/6	7586 25/6	EB3 9/6	EF52 13/6
30L1 7/6	7586 25/6	EB3 9/6	EF165 13/6
30L1 7/6			



**THE RELIABLE  
SOLDERING INSTRUMENT!**

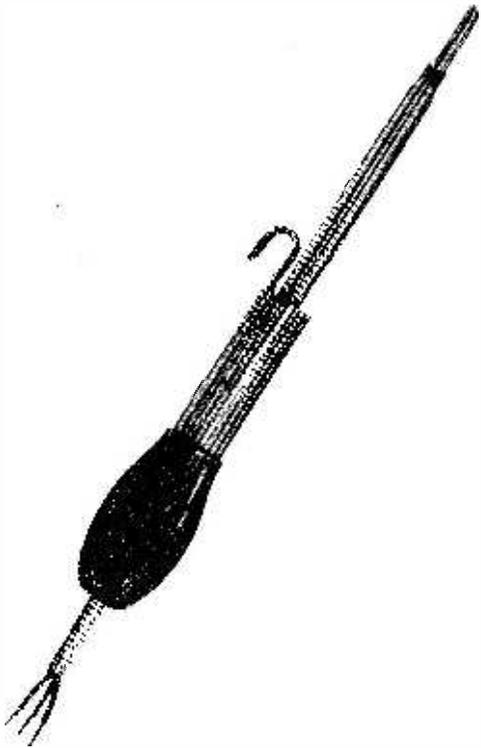

SEND COUPON FOR LATEST LEAFLET

**ADCOLA PRODUCTS LTD  
ADCOLA HOUSE  
GAUDEN ROAD  
LONDON SW4  
Telephone 01-622 0291/3**

NAME .....

ADDRESS .....

PW177

**SEMICONDUCTORS  
BRAND NEW AND FULLY GUARANTEED**

1N914	1/8	2N2905A	8/-	ACV22	4/-	BD123	21/6	MJ490	22/6
1N916	1/8	2N2905	8/-	ACV22	4/-	BD124	12/-	MJ491	23/6
18021	4/-	2N2906A	8/-	AD140	8/-	BF115	5/-	MPF102	7/6
18025	5/-	2N2923	4/-	AD149	11/6	BF117	10/6	MPF103	7/6
18113	3/-	2N2924	4/-	AD161	7/6	BF167	5/6	MPF104	7/6
18120	2/6	2N2925	3/6	AD162	7/6	BF173	7/6	MPF105	8/-
18121	2/6	2N2926	3/6	AF114	5/-	BF180	7/-	NKT0013	8/6
18130	2/6	Green	2/9	AF116	5/-	BF181	6/6	NKT216	7/6
18131	2/6	Yellow	3/9	AF117	5/-	BF184	7/6	NKT217	8/6
18132	2/6	Orange	2/9	AF118	12/6	BF194	5/-	NKT261	4/-
1844	2/-	2N2911	12/6	AF124	4/6	BFX12	4/6	NKT262	4/-
2G301	4/-	2N3053	6/6	AF125	4/6	BFX13	4/6	NKT264	4/-
2G302	4/-	2N3054	12/6	AF126	4/6	BFX29	12/6	NKT271	4/-
2G303	4/-	2N3055	15/-	AF127	3/6	BFX30	8/6	NKT272	4/-
2G371	3/-	2N3702	3/6	AF139	7/6	BFX35	19/6	NKT274	4/-
2N695	4/6	2N3703	4/6	AF181	8/6	BFX43	8/6	NKT275	5/6
2N697	5/-	2N3704	4/6	AF186	11/-	BFX44	8/6	NKT281	5/6
2N698	4/6	2N3705	4/6	AF239	7/6	BFX84	7/6	NKT403	15/-
2N706	2/6	2N3706	4/6	AF272	8/6	BFX85	9/-	NKT404	12/6
2N706A	2/6	2N3707	4/-	ASX23	5/6	BFX86	6/6	NKT405	15/6
2N708	4/-	2N3708	3/6	ASX27	8/6	BFX87	6/6	NKT613	6/6
2N829	5/6	2N3709	3/6	ASX28	5/6	BFX88	5/-	NKT674	5/-
2N830	7/-	2N3710	4/-	ASX29	5/6	BFY10	4/6	NKT677	5/-
2N1090	6/6	2N3711	4/-	ASX20	7/6	BFY17	4/6	NKT713	5/-
2N1091	6/6	2N3819	9/-	ASZ21	7/6	BFY18	4/6	NKT773	5/-
2N1131	6/6	2N3820	22/6	BAX13	2/6	BFY19	4/6	NKT781	5/-
2N1132	6/6	2N4058	5/6	BAX16	2/6	BFY20	12/6	NKT20329	5/6
2N1302	3/6	2N4059	5/-	BAY31	1/6	BFY41	10/-	NKT8011	15/6
2N1303	3/6	2N4060	5/-	BAY38	3/6	BFY43	12/6	NKT8012	19/6
2N1304	4/6	2N4061	4/6	BC107	3/6	BFY50	4/6	NKT8013	29/6
2N1305	4/6	2N4062	4/6	BC108	3/6	BFY51	4/6	OA5	2/6
2N1306	5/-	2N4255	8/6	BC109	3/6	BFY52	4/6	OA9	2/6
2N1307	5/-	2N4254	3/6	BC113	6/6	BFY77	11/6	OA70	1/6
2N1308	6/-	2N4255	3/6	BC116	12/6	BFY90	12/6	OA73	2/-
2N1309	6/-	2N4256	6/6	BC125	11/-	B8X19	3/6	OA79	1/6
2N1507	5/6	2N4286	3/6	BC126	11/-	B8X20	3/6	OA85	1/6
2N1613	5/6	2N4287	3/6	BC129	11/-	B8X21	7/6	OA90	1/6
2N1711	6/6	2N4288	4/6	BC147	3/6	B8X22	10/6	OA91	1/6
2N1889	6/6	2N4291	3/6	BC148	3/6	B8X27	11/6	OA95	1/6
2N1893	8/6	2N4292	3/6	BC149	3/6	B8X28	6/-	OA99	1/6
2N2102	15/-	40361	12/6	BC167	3/6	B8X29	13/6	OA99	1/6
2N2147	14/6	40362	14/6	BC168B	3/6	B8Y26	4/-	OA290	2/-
2N2148	12/6	3N128	18/6	BC169B	3/6	B8Y27	4/-	OA292	2/-
2N2160	14/6	3N140	19/6	BC169C	3/6	B8Y28	4/-	OC26	8/6
2N2193	5/6	3N141	21/6	BC212L	5/-	B8Y29	4/-	OC28	8/6
2N2193A	5/6	3N142	16/6	BCY30	5/6	B8Y38	8/6	OC35	6/6
2N2217	6/6	AAZ13	2/6	BCY31	5/6	B8Y39	4/6	OC36	6/6
2N2218	6/6	AAZ15	2/6	BCY32	7/6	B8Y40	6/6	OC44	4/-
2N2219	6/6	AAZ17	2/6	BCY33	4/-	B8Y51	8/6	OC45	2/6
2N2220	5/-	AC107	6/-	BCY34	4/6	B8Y52	9/-	OC71	2/6
2N2221	5/-	AC126	4/-	BCY38	4/6	B8Y53	8/6	OC72	2/6
2N2222	6/6	AC127	5/-	BCY39	7/6	B8Y54	19/6	OC75	4/6
2N2263	5/-	AC128	4/-	BCY40	6/6	BY100	4/6	OC83	4/6
2N2369	5/-	AC176	5/-	BCY42	8/-	BYX10	5/6	OC83D	4/6
2N2369A	5/6	AC187	12/-	BCY43	8/-	BYZ10	9/-	OC159	5/6
2N2339	4/6	AC188	12/-	BCY54	7/6	BYZ11	7/6	OC140	6/6
2N2340	4/6	ACV17	5/-	BCY70	4/6	BYZ12	6/-	OC200	6/6
2N2646	11/6	ACV18	5/-	BCY71	8/6	BYZ13	5/-	OC201	7/6
2N2604	8/-	ACV19	5/-	BD116	35/-	MJ480	29/6	OC202	10/6
2N2904A	8/-	ACV20	5/-	BD121	17/6	MJ481	27/6		
2N2905	3/-	ACV21	5/-						

**MULLARD  
INTEGRATED  
CIRCUITS**

FCH211 Hextuple DTL Inverter Gate	28/6
FCH221 Triple 3 Input DTL Line	28/6
FCV101 3 Input JK Flip Flop	35/-
TAA241 Operational Amplifier	47/6
TAA243 Operational Amplifier	47/6
TAA 263 Linear AF Amplifier	18/6
TAA320 Most LF Preampifier	15/6

**SPEAKERS (3 ohm)**

10" x 6" 87/6	8	15	1/8	1/8	200	6.4	1/9
9" x 4" 28/6	8	15	1/8	1/8	200	16	2/-
8" x 5" 19/6	8	40	1/8	1/8	250	25	2/9
7" x 4" 15/6	4	40	4/9	4/9	320	10	1/8
5" x 3" 12/6	4	40	2/3	2/3	400	16	2/9
3" 9/8, 5" 14/6, 8" 27/6, 12" 39/6	5	15	1/8	1/8	500	50	3/9
	6.4	6.4	1/8	1/8	500	50	4/9
	8	15	1/8	1/8	640	16	3/6
	8	40	1/8	1/8	1000	12	3/9
	8	40	3/8	3/8	1000	25	4/9
	10	15	1/8	1/8	1000	50	7/8
	10	25	1/8	1/8	2000	25	5/6
	12.5	25	1/8	1/8	2000	50	12/6
	18	18	1/8	1/8	2500	25	9/6
	25	6.4	1/8	1/8	3000	25	12/6

Post and Packing 2/9

2 1/2" x 3 1/2" -15 Matrix	3/8	4/1	1 watt 10%, 4d.
2 1/2" x 5"	4/3	4/9	1 watt 5%, 5d.
3 1/2" x 3 1/2"	4/3	4/9	1 and 1 watt, 6d.
3 1/2" x 5"	5/6	5/6	3 watt, 5%, 1/6
2 1/2" x 1 7/8"	12/6	12/6	5 watt 2/-
3 1/2" x 1 7/8"	16/-	21/6	1 watt Metal Oxide, 1/6
Cutter 9/-			

**THYRISTORS**

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.  
3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/6.  
ZENERS. 1 1/2 WATT 2-7-33V 4/6,  
400m/w 3-0-33V 5/-.

**INTEGRATED CIRCUITS—R.C.A.**


CA3005 30/-, CA3011 20/-, CA3012 25/-,  
CA3013 30/-, CA3014 30/-, CA3018 25/-,  
CA3019 25/-, CA3020 27/6, CA3021 42/6,  
CA3022 35/-, CA3023 32/6, CA3026 37/6,  
CA3025A 25/-, CA3028B 35/-, CA3035 35/-,  
CA3036 20/-.  
FAIRCHILD  
L900, 914 11/-, L923 14/-.  
DATA SHEETS FOR RCA DEVICES 2/- per type.

Presets std., horiz. or vert.								
Potentiometers, Log/Lin						8/3 each		
MFD	V	Price	MFD	V	Price	MFD	V	Price
1	15	1/6	25	10	1/8	200	6.4	1/9
1	40	1/9	25	25	1/8	200	16	2/-
2	15	1/6	25	50	1/6	250	25	2/9
2	350	2/-	32	15	1/8	250	50	3/9
2.5	18	1/9	32	450	1/8	320	10	1/8
4	15	1/8	40	6.4	1/8	400	16	2/9
4	40	4/9	40	16	1/8	500	6	2/8
4	350	2/3	50	12	1/8	500	25	3/9
5	15	1/6	50	25	1/6	500	50	4/9
6.4	6.4	1/8	50	50	2/-	640	16	3/6
8	15	1/8	64	25	1/6	1000	12	3/9
8	40	1/6	80	6.4	1/8	1000	4	4/9
8	40	3/8	80	16	1/8	1000	25	5/9
10	15	1/8	100	6.4	1/8	1000	50	7/8
10	25	1/8	100	12	1/8	2000	25	5/6
12.5	25	1/8	100	25	1/6	2000	50	12/6
18	18	1/8	100	50	2/6	2500	25	9/6
25	6.4	1/8	125	4	1/6	3000	25	12/6

**A. MARSHALL & SON**  
28 CRICKLEWOOD BROADWAY, LONDON N.W.2  
01-452 0161/2/3 CALLERS WELCOME  
Post & Packing U.K. only, 1/6. Europe 10/-, Commonwealth (Air) 13/-.

# HENRY'S RADIO LTD.
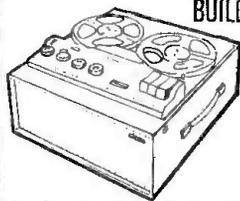
# ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES




## BUILD A QUALITY 4 TRACK TAPE RECORDER

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board - in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises: Deck, Amplifier, Cabinet and speaker, with microphone, 7" 1200 ft. tape, and spare spool. ASK FOR BROCHURE 6. TODAY'S VALUE £60. PRICE 39 gns. p.p. 22/6. NOTHING ELSE TO BUY
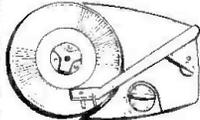
## SCOOP! STAAR RECORD PLAYER

Deck plays 33, 45, 78, R.P.M. records 9 volt operated, with mono cartridge. BRAND NEW as illustrated.



PRICE 59/6.  
p.p. 3/6.  
Send for leaflet No. 2.




## MULLARD 1WATT AMPLIFIER

Portable Transistor Unit-ideal for Intercoms, Baby Alarms, Tele phone, Record Players or Guitar Practice. 9 Volt B+ transistors with volume control, output 3 ohms. Ideal for use with STAAR RECORD DECK. PRICE 45/- p.p. 2/6.

OTHER ITEMS. Suitable 7 x 4 inch. 3 ohm speaker 1/6 p.p. 1/6. Revine covered cabinet 12 x 9 x 4 12/6 p.p. 2/6. P.P.9 9 volt battery 3/9. Write for leaflet No. 2.

## GARRARD RECORD DECKS

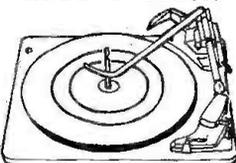


All the latest models BRAND NEW and guaranteed - TERRIFIC SAVINGS!

*2025 STEREO	£ 7.19.6
*2025TC DIAMOND, 9TAH.C.	£ 9.19.6
*3000 STEREO 9TAH.C.	£ 9.19.6
*SP 25 Mk II	£11.19.6
*SL 55	£11.19.6
A70 Mk II	£12.10.0
*AT 60 K.I.I.	£13.10.0
*SL 65	£14.14.0
AP 75	£19.0.0
*401	£28.7.6
SL 75	£29.0.0
SL 95	£35.0.0
CL 75 GOLDRING	£33.0.0
GL 75 P	£46.15.0

ALSO IN STOCK - THORENS - Lenco - B.S.R. Carriage/insurance 7/6 extra on any model. WB4 BASES £3.19.6. PERSPEX COVERS £3.10.0. \*Special offer base and cover available for these models at £4.15.0. Carriage 5/-. Complete range of Cartridges/Plinths/Covers. SEND FOR 8 PAGE BROCHURE 16/17 TODAY.

## BUILD YOURSELF A QUALITY RADIO

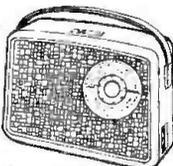

New printed circuit design with full power output. Fully tuneable on both mw/lw bands. 7 Mullard transistors. Fitted 5" speaker, Room Filling Power. Easy to build with terrific results. All local and continental stations. Complete detailed instructions. TOTAL COST £6.19.6. p.p. 4/6. Ask for Leaflet No. 1.

## TRANSISTORS DIODES RECTIFIERS

WE HAVE THE MOST COMPREHENSIVE STOCK IN GREAT BRITAIN. NEW 1969 LIST OF 1000 TYPES. SEND FOR FREE COPY TODAY (LIST 36) Whether you require one or 1000, devices we can fulfil your order from stock! For quantity quotations telephone: (01) 723 0401 Ex. 4, or (01) 402 8823.

## HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks, Mike, Tuners. 16 transistor means operated. Output 5x5 watts for 8-15 ohm speakers. Black, silver and wood finish, size 13" x 3" x 6". PRICE £13.10.0. p.p. 7/6. (Leaflet on request). Complete Stereo System 5-5. Garrard 2025 stereo, 5-5 Amplifier, Plinth/Cover, Two 10 watt speakers with tweeters in polished cabinets. Usual price £47.0.0. OUR PRICE £39.10.0. p.p. 20/-. ASK FOR BROCHURE 13



## SINCLAIR EQUIPMENT


The SINCLAIR IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself has an output power of 10 watts, yet with an overall-size of 1 x 0.4 x 0.2 in.



IC-10 Integrated Circuit Amplifier	59/6	OTHER TYPES OF INTEGRATED CIRCUITS	
Z30	89/6	RCA, CA3014	29/6
Stereo 60	£9.19.6	RCA, CA3018	22/6
P25 Power Supply	£4.19.6	RCA, CA3020	29/6
Q16 Loud Speaker	£8.19.6	RCA, CA3036	18/6
Z12 Amplifier	89/6	Sinclair I.C.7.0	59/6
P2 4 Power unit	99/6	C.E. PA230*	22/6
Stereo 25	£9.19.6	G.E. PA234*	20/0
Q14 Speaker system	£7.19.6	G.E. PA237*	37/6
All post paid, delivery from stock.			
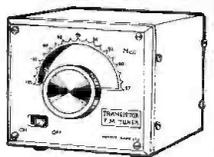
## BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound.



PARTS TOTAL COST £6.19.6. DECODER £5.19.6. ASK FOR LEAFLET No. 3. (FOR STEREO)

## HENRY'S RADIO Fully Illustrated CATALOGUES

ALL TYPES OF ELECTRONIC COMPONENTS TEST EQUIPMENT KITS BUILT UNITS



HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

COMPREHENSIVE · CLEAR · CONCISE · CATALOGUES  
A Over 300 pages fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers, 10/- value, for use with purchases.

ORDER AS CATALOGUE A PRICE 7/6. p.p. 2/-



B New audio and high fidelity catalogue, 120 pages containing ideas and equipment for every application. Special low prices for all leading makes Plus 12/6 extra discount voucher.

ORDER AS CATALOGUE B PRICE 5/- p.p. 1/-

WHY NOT SEND AWAY TODAY!
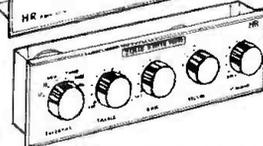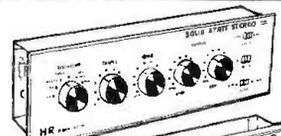
## AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dindale Mk.II - each unit or system will compare favourably with other professional equipment selling at much higher prices. COMPLETE SYSTEMS AND MIXERS from £11.12.6. to £38.17.6. (all units available separately).



THE FINEST VALUE IN LOW COST HIGH FIDELITY - CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS.

SEND FOR BROCHURES No. 12/14 and 21 TODAY!

## Hi-Fi equipment to suit EVERY POCKET

HIGH FIDELITY AUDIO EQUIPMENT CATALOGUE 5/- p.p. 1/-



VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of - AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS - IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40 - £300 TO SUIT EVERY POCKET. DEFERRED TERMS AVAILABLE. SEND FOR ILLUSTRATED BROCHURE 16/17. TWO DEMONSTRATION ROOMS

Electronic Musical Instruments

## ELECTRONIC ORGANS


COMPLETE KITS FOR THE HOME CONSTRUCTOR

START BUILDING FOR AS LITTLE AS £10. MODELS FROM £98 - £350.

STAR FEATURES:  
\*ALL TRANSISTOR PRINTED CIRCUIT DESIGNS.  
\*BRITISH DESIGN. \*STEP BY STEP DETAILED INSTRUCTIONS. \*GIVES UP TO 50% ON COMMERCIAL EQUIVALENT. \*EVERYTHING SUPPLIED DOWN TO THE LAST ITEM. \*FULL AFTER-SALES SERVICE & ADVICE. \*CREDIT SALE & H.P. TERMS AVAILABLE.

We are pleased to offer the choice of FOUR British designs from a single manual portable at £99 THE MAYFAIR for light or classical music - to a two manual five octave de-luxe model with OAK CONSOLE from £285 for the serious musician.

These kits are the result of years of research and design and offer the best that is essential to good organ designs, coupled with excellent value are within the reach of most pockets. No technical skill or knowledge is required in construction, with the aid of the STEP BY STEP illustrated manuals will produce an instrument that will be a delight to own and use and will give years of trouble free entertainment for the whole family.

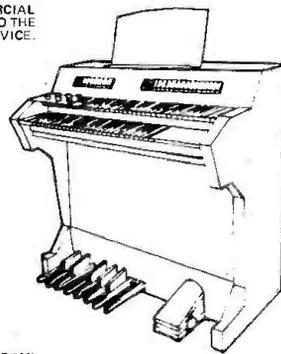

SEND FOR ILLUSTRATED BROCHURES 9/10/11 TODAY! When in LONDON... CALL IN SEE, HEAR, PLAY FOR YOURSELF. Organ Demonstration Room 1st Floor. PRACTICAL ELECTRONICS ORGAN - ORGAN COMPONENTS

We are able to supply all items for this series, details on request.

ILLUSTRATION OF GROSVENOR ELECTRONIC ORGAN

Built models available from £124.

# HENRY'S RADIO LTD.

Mail Order Dept., Components, Organ Dept.  
303 EDGWARE ROAD, LONDON W.2.  
Telephone: 01-723 1008/9

High Fidelity and Equipment Centre  
309 EDGWARE ROAD, LONDON W.2.  
Telephone: 01-723 6963

OPEN MON-SAT 9am-6pm THURS. 9am-1pm