

PRACTICAL WIRELESS

OCTOBER
1970

3/6

TRANSISTOR & DIODE TESTER



ALSO..

TRANSISTOR VFO

SIMPLE MINI-ORGAN

ELECTRONIC DIGITAL
COMBINATION LOCK

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{3}{8}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{1}{4}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE


LONG LIFE

B 42 LL $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{1}{4}$ " — 2.4 mm CHISEL FACE

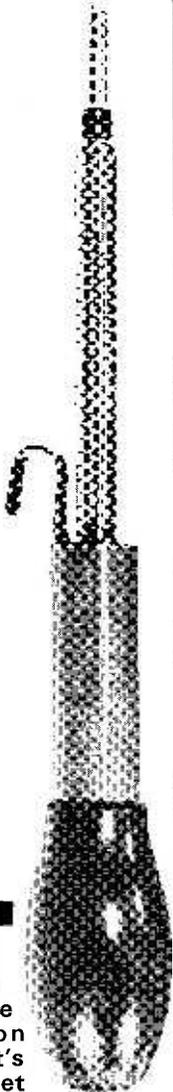B 44 LL $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.




* Write for price list and catalogue

ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-822 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

JACKSONS

Radio and Electronic Components
(Made in England)

SL 16 DRIVE

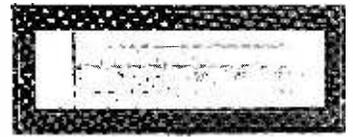

General Purpose Slide Rule Drive. Calibrated 0—100. Aluminium Scale. With provision for individual calibration. Scale Length 4 3/8". Black Escutcheon 7 1/4" x 2 5/8" overall. Fitted with Glass. Smooth 10:1 reduction. Price 26/-



It's reliable if it's made by JACKSON!

MADE IN ENGLAND

JACKSON BROS. (LONDON) LTD.


Dept. RCM, Kingsway-Waddon Croydon, CR9 4DG
Telephone 01-688 2754

Telegrams Walfilco, Croydon

U.S. Office: M. Swedgal, 258 Broadway, New York, N.Y. 10007

PHOTOELECTRIC KIT

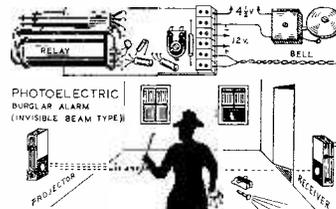CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
39/6

Postage and Pack. 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit. Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth. Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS

CARRIAGE 35/-



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

PREMIER STEREO SYSTEM "TWO"
As system "ONE" above but with Garrard SP25.
PREMIER PRICE 45 Gns. 35/- Carr.


AURIGA 8 WAVEBAND TRANSISTOR PORTABLE

Covers Medium, Long and 6 Short Waves and includes many features not normally found in this price range. 10 transistors and 2 diodes. Push Pull output. Press button dial illumination. Volume, tone, tuning and wave-change controls. Telescopic aerial. Uses 6 x 1 1/2 v. batteries. Sockets for external batteries, tape recorder and aerial. Elegant black and chrome cabinet. Size 11" x 2 1/2" x 7 1/2".



Price **16 Gns.**
P. & P. 7/6

TELETON SAQ203E STEREO AMPLIFIER

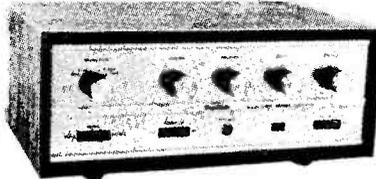

A small but powerful amplifier designed for stereo hi. reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0

PREMIER PRICE 22 Gns. 10/- P. & P.

PREMIER SPEAKER CABINET



Teak finish with black front. Size 16" x 10" x 7 1/2". Cut out for 13 x 8 speaker.

ONLY 49/6 P. & P. 7/6.



E.M.I. 13 x 8 in. HI-FI SPEAKERS

Fitted two 2 1/2 in tweeters and crossover network. Impedance 8 ohms. Handling capacity 10W. Brand new.

79/6 P. & P. 7/6



HI-FI STEREO HEADPHONES
Designed to the highest possible standard. Fitted 2 1/2 in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.
49/6 P. & P. 3/-

MONO HEADPHONES 2000 ohm 14/6 P. & P. 2/6.
STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-.
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-.

PREMIER STEREO SYSTEM "FOUR"

Teleton SAQ203E Amplifier (as above) **£23.2.0**
Garrard SP25 **£11.19.6**
Shure M3D **£6.19.6**
Teak base and cover **£5.10.0**
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers **£26.5.0**
Total cost if purchased separately **£73.16.0**

PREMIER PRICE 65 Gns. 35/- Carr.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. **67/6** P. & P. 2/-
240 volt A.C.
"Marksmen" Soldering Iron. Lightweight, pencil bit. Ideal for regular bench use and around the home. 25 watts. 240 volt A.C. **31/6** P. & P. 2/-.



POCKET SIZE MULTI-TESTER With wide angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohm/volt A.C.
19 Ranges: 0-5-25-50-250-500-2500 volts DC. 0-10-50-100-500-1000 volts AC. 0-50µ-2.5 mA-250 mA. DC. 0-6000 ohms-6 megohms. 10µ µf-0.01 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions. **£4.19.6** P. & P. 3/6.

SPECIAL OFFER!



GARRARD SP25 MK II SINGLE RECORD PLAYER FITTED AUDIO TECHNICA AT66 STEREO CARTRIDGE COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.
Total list price over £24.
PREMIER PRICE 18 Gns.
P. & P. 10/-.

VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 1/2 in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phonoplug output. Attractive teak wood grain finish case.



MONO MODEL **59/6** STEREO MODEL **69/6** P. & P. 2/6.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped attractively boxed.

LP8 3" 350' P.V.C.	5/6	LP6 5 1/2" 1200' P.V.C.	12/6
TT8 3" 450' POLYESTER	7/6	DT6 5 1/2" 1800' POLYESTER	22/6
DT8 3 1/2" 600' POLYESTER	11/6	TT6 5 1/2" 2400' POLYESTER	37/6
SP5 5" 600' P.V.C.	3/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	LP7 7" 1800' P.V.C.	15/-
DT5 5" 1200' POLYESTER	15/-	DT7 7" 2400' POLYESTER	25/-

TAPE SPOOLS 3" 1/2", 5", 5 1/2", 7", 1 1/8", TT7 7" 3600' POLYESTER 50/-
Post and Packing 3" 1/2", 5", 5 1/2", 1/8, 7" 2/- (3 reels and over Post Free).

PREMIER EXCLUSIVE MIDLAND CASSETTE TAPE RECORDER 12-115



Solid state incorporating piano key controls for trouble-free 2-track recording. Inputs for mike and aux. Earphone socket. Complete with batteries **£16.10.0** and earpiece. Size 10 1/2" x 5 1/2" x 2 1/2". P. & P. 7/6.



TAPE CASSETTES
C60 (60 min.) **7/6** 3 for 21/-
C90 (90 min.) **12/6** 3 for 36/-
C120 (120 min.) **17/6** 3 for 51/-
P. & P. 1/-.

All cassettes can be supplied with library cases at 6d. extra each



PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W1 Tel: 01-636 3451



Laskys

TMK METER KITS

EXCLUSIVE

These two meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions.

MODEL 200

20,000 O.P.V. Multimeter. Features 24 measurement ranges with mirror scale. Large 3 x 2in. meter. Full scale accuracy: DCV and current: $\pm 2\%$, ACV: $\pm 3\%$, resistance $\pm 3\%$. Special 0-6V DC range for transistor circuit measurements.



SPECIFICATION

● DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV.
 ● ACV: 0-0.30-120-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-5-600mA. ● Resistance: 0-10-K 100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale).
 ● Capacitance: 0-002-0.2 μ F (ACV range). ● Decibels -20 to +63dB. ● Output: 0.05 μ F blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet. Size 5½ x 3½ x 1½in. Complete with test leads.



TM-5 5 K ohms/V POCKET MULTIMETER

Another new look pocket multi-meter from Lasky's providing top quality and value. The "slimline" impact resistant case—size 4½in. x 2½in. x 1½in., fitted with extra large 2½in. square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorized equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC/V: 3-15-150-300-1,200 at 5K OPV.
- AC/V: 6-30-300-600 at 2.5K OPV.
- DC Current 0-300 μ A, 0-300mA.
- Resistance: 0-10K ohms, 0-1M ohms.
- Decibels: -10dB to +16dB.
- Complete with test leads, battery and instructions.

KIT PRICE ONLY 92/- Post 3/6

MODEL 5025 50,000 O.P.V. FEATURING 57 MEASUREMENT RANGES

Uses an entirely new range selection mechanism which permits the use of a really large meter in a more compact cabinet. The range selected is indicated on the meter face. High speed rotary range selection knob; polarity reversal switch shielded meter movement with overload protection circuit; Special μ A and mA measurement ranges.

SPECIFICATION DCV: 0-0.25-2.5-10-50-250-1,000V at 25K/OPV. 0-0.125-1.25-5-0.25-125-500V at 50K/OPV. ACV: 0-3-10-50-250-1,000V at 2.5K/OPV. 0-1.5-5-25-125-500V at 5K/OPV. DCmA: 0-25 μ A at 125mA; 0-50 μ A at 250mA. DCmA: 0-2.5-25-250mA at 125mV; 0-5-50 500mA at 250mV. DC Amps: 0-5A at 125mV 0-10A at 250mV. Resistance: 0-10M/ohms. Output: Capacitor (0.1 μ F, 400V) in series with ACV ranges. Decibels: -20 to +31.5dB. Operates on two 1.5V batts. Black bakelite cabinet, size 5½ x 6½ x 2½in. Complete with test leads.



KIT £10.10 Post 5/-

MODEL 5025 ALSO AVAILABLE READY BUILT AND TESTED £13.10 Post 5/-

LASKY'S PRICE

49/6 P & P 2/6

TM-1 MINI-TESTER

1 K ohms/volt

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to ± 3 of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case—with white and metallic red/green floures. Ohms zero adjustment.

- Size Only**
3½in x 2½in. x 1½in.
- DC/V: 0-10-50-250-1000 at 1K OPV
 - AC/V: 0-10-50-250-1000 at 1K OPV
 - DC CURRENT: 0-1mA, 100mA.
 - Resistance: 0-150K ohms.
 - Decibels: -10 to +22dB.
 - Complete with test leads, battery and instructions.




LASKY'S PRICE

39/6 P & P 2/6

TMK 100,000 OPV

"LAB" MODEL

A highly accurate yet rugged Multitester using a 10 μ A meter hand calibrated to a D.C. accuracy of $\pm 3\%$ of full scale. Special features—ultra large meter scale 6½ x 3½in incorporating an entirely new type of range selection panel which gives instant range identification without taking your eyes from the meter. An audible buzzer is provided for easy short testing. SPEC: D.C./V ranges: 0-5, 2-5, 10, 50, 250, 500, 1,000V at 100K/O.P.V. A.C./V ranges: 3, 10, 50, 250, 500, 1,000V at 5K/O.P.V. D.C. current: 0-10, 100 μ A, 0-10, 100mA, 0-2.5, 10A. Resistance: 0-1K, 10K, 100K, 1M, 100M/ohms. Decibels: -10 to 49.4dB. Continuity test: Audible buzzer. Operates on 11-5V U2 and 1 x 15V B, 154 type batteries. Cabinet size 7½ x 6½ x 3½in. Weight 4lb.

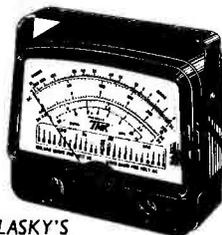

**LASKY'S
PRICE
£19.0.0** Post 5/-

Audio Development

AD-309K

PRECISION PICK-UP ARM
COMPLETE WITH AD-76K
MAGNETIC
CARTRIDGE

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic cartridge is constructed of brass throughout, heavily chrome plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard ¼in. mounting centres and is finished in black enamel with chrome fitting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in dia. mounting hole.



LASKY'S PRICE £9.19.6 POST 3/6

AUDIO DEVELOPMENT AD-76K

Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV, Stylus: Diamond LP. Tracking force: 2 gms ± 0.5 gm. **90/-** Post Free

REPLACEMENT STYLUS TYPE J.S.P1 41/- POST FREE

AUDIO DEVELOPMENT AD-96K
Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV, Stylus: Diamond LP. Tracking force: 2 gms. **£5.18.6** Post Free
Replacement stylus type Y.960S 51/6, post free.

SONICS AS-57

ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS


The AS-57 is a real space saver. This fine miniature high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated listening area. The special high efficiency 5 x 7in. full range speaker has a frequency range of 70-18,000 Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size: 5½ x 15½ x 8½in.

**LASKY'S
PRICE
£15 per PAIR** Post 10/-

AudioTronics 70 THE AMAZING

The 1970 edition of Lasky's Audio-Tronics catalogue is available FREE on request. Packed with 1000's of items for the Radio and Hi-Fi enthusiast, lectronics, Hobbyist, Servicemen and Communications Ham. Covers every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals) Tape recording and Audio accessories plus Lasky's amazing money saving vouchers worth over £25. **SEND TODAY.** Send your name, address and 2/- for post and inclusion of your name on our regular mailing list
This month's vouchers worth 50/-

EXCLUSIVE DIGITAL CLOCK SCOOP!

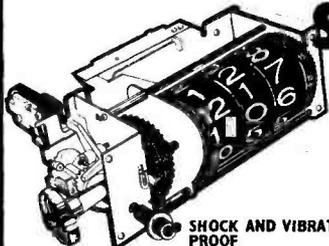

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light etc. at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4 1/2" x 1 1/2" x 3 1/2" (overall from front of drum to back of switch) SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. **HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS. SPECIAL QUOTATIONS FOR QUANTITIES**

LASKY'S PRICE £6.19.6 Post 3/6
KNOBS AVAILABLE SEPARATELY—12/6 per set. Post 1/6

Garrard SPECIAL OFFER

SL 55

One of the famous Garrard Synchro-Lab Series. Takes 8 Lps. 4-speed auto-changer; incorporating a tubular pickup arm and adjustable stylus force.

Wired for Mono and Stereo. Size 14 in wide, 11 1/2 in front to rear. 4 1/2 in above and 3 in below lower edge of unit plate. **NOW AT LASKY'S SUPER SPECIAL OFFER PRICE.**

Complete with SONTONE 9TA STEREO CARTRIDGE

OTHER GARRARD UNITS FROM STOCK AUTOCHANGERS

SL72B.....	£25 0 0	SL65B.....	£15 10 0
2025TC with stereo cartridge	£8 17 6	SL95B.....	£25 0 0
3000 complete with 9TAHC stereo cartridge.....	£9 19 6	SL75B.....	£28 0 0

SINGLE PLAYERS

SP-25 MK II £11.19.6, AP 75, £18.10.0, AP75 with AD76K mag. cart., £21.10.0, 401 Transcription Unit £28.0.0.

BASES AND COVERS FOR GARRARD UNITS

Type WB1 and WB5 for models 2025TC, 3000, SL65B 1025, SP25 Mk II Price £3.18.6, WB3 £5.12.6, Type WB4 for model SL72B, SL75B, SL95B Price £5.12.6. Parapex covers SP C1 for WB1, £3.14.1, SP C4 for WB4 and WB5 allows unit to be played with the cover in place)—£4.5.0.

GARRARD PACKAGE DEALS

SP 25 Mk II complete with AD 76K magnetic cartridge teak plinth and perspex cover **£19.0.0** Post 7/6



SPECIAL OFFER PRICE £10.19.6

Astrad ORION

THE WORLD'S SMALLEST 6 TRANSISTOR TWO WAVEBAND RADIO THOUSANDS SOLD



Made to the highest space-age standards—this remarkable micro-size set measures only 1 1/4 x 1 1/8 x 1 1/2 in. yet it contains 6 transistors and other components combined in a photo etched circuit, only 3/4 x 3/4 in. tuning capacitor, ferrite rod aerial, battery, wave band selection switch etc. Output to a high impedance crystal earpiece, giving ample volume (automatically adjusted) and clear tone. Brief tech. spec.: Waveband coverage—Medium wave 525 to 160kHz, Long wave 150kHz to 480kHz. Sensitivity: 35mV max. Selectivity—10dB (at 30kHz de-tuning). Power source: 1 x 1.4V Mercury battery. The Orion is supplied fully built and tested complete with battery, left and right fitting earphone supports and attractive black and ivory plastic presentation/carrying case (matching the Orion). Never miss your favourite music, sport, news—the Orion is an ideal gift for all, providing a constant source of enjoyment without disturbing others.

AUTUMN PACKAGE PRICE


AVAILABLE SEP: RADIO 39/6, Post 2/6. Spare batt. 3/6. Charger* 19/6, Post 2/6 (*enables Orion to be used non stop).

ONLY 57/-

Post 2/6

TRIO 9R-59DE

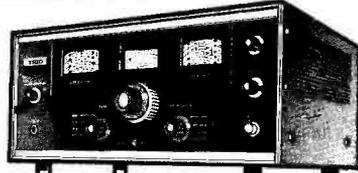● 8 valve plus 7 diode circuit continuous coverage from 550kHz to 30MHz with Calibrated Bandsread on 10, 15, 20, 40 and 80 metre bands ● Clear SSB reception is achieved through the use of a product detector. ● Finished in light grey with dark grey case. Fully guaranteed, complete with instruction - manual and service data.



SPECIFICATION: Frequency Ranges: 550-1600kHz; 1.6-4.8MHz; 4.8-14.5MHz; 10.5-30MHz. Bandsread: (Direct Reading on Ham Bands) 3.5MHz 80m; 7MHz 40m; 14MHz 20m; 21MHz 15m; 28MHz 10m. Sensitivity: A, B, C, Bands—Less than 6dB (for 10dB S/N ratio); D Band—13MHz; Less than 18dB (for 10dB S/N ratio); 28MHz; Less than 10dB (for 10dB S/N ratio). Selectivity: ± 5kHz at -50dB. Audio Output: 1.5w. Power Requirements: AC 115/230V, 50/60Hz. Recommended Speaker Type: 4 or 8 ohm. Built-in Circuits: Bandsread; Automatic Noise Limiter (ANL); Automatic Volume Control (AVC); Headphone Jack. Dimensions: 7in. H 15in. W, 10in. D.

LASKY'S PRICE £42.0.0 Carriage free

TRIO SP-5D —matching all the TRIO receivers in both style and size. Contains 5 x 3 in. elliptical 8 ohms speaker specially designed to give extremely crisp reproduction of voice frequencies. Dark grey metal cabinet—size 7 x 3 1/4 x 5 1/2 in.

LASKY'S PRICE 87/6 post 5/-

TRIO HS-4 HEADPHONES

Rugged construction plus comfort makes these a must for the Ham. Dynamic headset. Impedance 8 ohms, matching 4-16 ohms. Max. power 3w. Frequency range 300-3000Hz.

LASKY'S PRICE £5.19.6 post 3/6



JUST ARRIVED

New Laskys C60, C90, C120. Exclusively made for us in U.S.A. Great savings!

	EACH	FIVE FOR	TEN FOR
C 60—	7/6	33/-	62/-
C 90—	12/6	58/-	109/-
C 120—	17/6	75/-	135/-

U.S.A. Cassette head cleaner 10/6. Post 1/-

Post 1/- each, five for 2/-, ten for 3/-.



Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271

33 TOTTENHAM CT. RD, LONDON, W1P 9RB. Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRES

42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD. Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789

Open all day Saturday early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET LONDON, E1 2BN Tel: 01-790 4821





who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

In only **4 weeks** you're in – and only the incredible **Eduputer** can make it possible.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

Who created Eduputer? The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

Jobs galore! The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

Telephone: (01) 437 9906 NOW!

Or post the coupon today for full details FREE and without obligation.

London Computer Operators Training Centre,
 B7 Oxford House, 9/15 Oxford Street, London W.1.
 Telephone: (01) 437 9906.
 127/131 The Piazza, Dept. B7, Piccadilly Plaza, Manchester 1.
 Telephone: (061) 236 2935.
 Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name _____

Address _____



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price **15/-**



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price **15/-**



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF.	ALLOY	SWG		
4A	60/40	18	3/-*	
Size 5 (illustrated)	Savbit	18	3/-*	
15	60/40	22	4/-*	

*Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,

easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price **8/6**



From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**

FANE 'POP' RANGE OF LOUDSPEAKERS



- ★ Designed for General Purpose Public Address Systems
- ★ Ideal for Vocal and Instrumental Groups
- ★ Heavy Cast Chassis
- ★ Latest High Efficiency Ceramic Magnets

POP '15' 99/9 Rec Retail Price
 Fitted Tweeter Cone
12" FULL FREQUENCY RANGE
 Rating 15 Watts R.M.S. Imp. 15 ohms.

POP '30C' Fitted Tweeter Cone **£5-19-9** Rec Retail Price
12" FULL FREQUENCY RANGE
 Rating 25 Watts R.M.S. Impedance 15 ohms.

Above types not intended for use with Electronic Organ or Bass Guitar

ULTRA HIGH POWER TYPES

Impedance 8-15 ohms for general use inc. Bass Guitar and Electronic Organ Recommended Price

POP '50' 12in 50 Watts R.M.S. Gauss 14,000 lines **10 Gns.**

POP '60' 15in 60 Watts " " " " **12 Gns.**

POP '100' 18in 100 Watts " " 14,500 " **21 Gns.**

Sole Distributors to Wholesale and Retail Trades

LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS 12

COMET

Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Complete Free price list of over 800 items on request.



Customers Welcome
Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday & Friday.

	Rec. Retail Price	Comet Price
STEREO AMPLIFIERS		
ARMSTRONG 521 ..	£52 0 0	£43 10 0
DULCI 207 ..	£25 0 0	£17 0 0
DULCI 207M ..	£30 0 0	£20 19 6
GOODMANS Maxamp ..	£54 0 0	£39 19 6
LEAK Stereo 30 Plus ..	£53 0 0	£43 19 6
LEAK Stereo 30 Plus In teak case ..	£59 10 0	£47 19 6
LEAK Stereo 70 ..	£65 0 0	£52 0 0
LEAK Stereo 70 in teak case ..	£71 10 0	£56 19 6
LINEAR LT.66 ..	£18 18 0	£15 19 6
LL Stereo Amp. ..	£23 10 0	£16 19 6
METRDSOUND ST 20 ..	£32 0 0	£25 19 6
PHILIPS RH 591 ..	£73 0 0	£55 19 6
PHILIPS RH 590 ..	£49 0 0	£37 12 6
PHILIPS RH 580 ..	£28 0 0	£19 19 6
PIONEER SA500 ..	£62 11 4	£45 0 0
PIONEER SA700 ..	£98 0 0	£74 19 6
PIONEER SA900 ..	£134 2 0	£99 19 6
PIONEER Reverberation ..	£45 9 11	£35 19 6
QUAD 33 Pre-amplifier ..	£43 0 0	£38 19 6
QUAD 303 Main Amplifier ..	£55 0 0	£45 19 6
ROGERS Ravensbourne ..	£59 10 0	£46 19 6
(cased) ..	£64 0 0	£49 19 6
ROGERS Ravensbrook ..	£44 0 0	£36 19 6
ROGERS Ravensbrook (cased) ..	£49 0 0	£39 19 6
SINCLAIR 2000 ..	£30 9 0	£24 19 6
TELETON 203E ..	£28 15 0	£19 19 6
TELETON TSA, 200 ..	£54 12 0	£34 19 6
VOLTEX 100 watt stereo discotheque 8 electronic- ally mixed inputs ..	£185 0 0	£139 0 0

	Rec. Retail Price	Comet Price
TUNERS		
ARMSTRONG 523 AM/FM ..	£52 9 0	£44 19 6
ARMSTRONG 524 FM ..	£40 4 6	£34 19 6
ARMSTRONG M8 decoder ..	£9 10 0	£7 19 6
DULCI FMT.7FM ..	£22 1 0	£17 19 6
DULCI FMT.7S Stereo ..	£31 0 0	£25 5 0
GOODMANS Stereomax ..	£82 10 5	£71 19 6
LEAK Stereotic Chassis ..	£59 18 0	£53 19 6
LEAK Stereotic in teak case ..	£67 3 6	£59 19 6
PHILIPS RH 690 ..	£39 0 0	£31 19 6
PIONEER TX900 A/M/FM ..	£17 16 9	£14 19 6
QUAD Stereo FM ..	£51 0 0	£39 19 6
ROGERS Ravensbourne ..	£61 17 9	£49 19 6
ROGERS Ravensbrook ..	£45 0 2	£39 19 6
ROGERS Ravensbrook (cased) ..	£51 5 3	£42 19 6
SINCLAIR 2000 ..	£26 14 6	£19 4 6
TELETON 201X FM ..	£36 0 0	£29 19 6
TRUVOX FM 200/1C ..	£60 11 10	£39 19 6
All above tuners are complete with MPX stereo decoder		

	Rec. Retail Price	Comet Price
TUNER/AMPLIFIERS		
ARENA 2400 ..	£90 6 0	£71 19 6
ARENA 2600 Stereo AM/FM ..	£111 6 0	£94 0 0
ARENA 2700 Stereo ..	£105 0 0	£85 0 0
ARENA T1500F ..	£72 9 0	£59 19 6
ARENA T9000 ..	£303 9 0	£258 0 0
ARMSTRONG 525 ..	£87 16 9	£74 10 0
ARMSTRONG 528 ..	£98 15 6	£82 10 0
ARMSTRONG M8 decoder ..	£9 10 0	£7 19 6
GOODMANS 3000 ..	£77 14 7	£55 19 6
PHILIPS RH781 ..	£17 19 6	£14 19 6
PHILIPS RH791 ..	£125 0 0	£101 19 6
PHILIPS RH691 ..	£83 0 0	£70 10 0
PIONEER KX330 AM/FM/SW ..	£78 12 4	£62 19 6
PIONEER SX770 AM/FM ..	£160 8 6	£129 19 6
PIONEER SX990 AM/FM ..	£194 14 8	£155 0 0
TELETON F.2000 ..	£51 0 0	£37 19 6
TELETON 7ATI ..	£103 19 0	£85 0 0
TELETON R4200 ..	£51 15 0	£39 19 6
TELETON CR10T ..	£39 0 0	£29 19 6
TELETON TFS90 ..	£74 0 0	£59 19 6
WHARFEDALE 1001 ..	£131 5 0	£105 0 0
All above Tuner Amplifiers are complete with MPX decoder		

CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES

	Rec. Retail Price	Comet Price
PICKUP ARMS		
GOLDRING Lenco L75 ..	£12 6 6	£10 10 0
GOLDRING Lenco L69 ..	£9 5 9	£7 0 0
SME 3009 with S2 shell ..	£31 6 3	£25 19 6
SME 3012 with S2 shell ..	£33 7 3	£28 19 6



SECURICOR
SPECIAL DELIVERY SERVICE

All in-stock items value over £50 delivered by **SECURICOR** WITHIN 72 HOURS
(Add 12/- only for Securicor delivery)

ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

	Rec. Retail Price	Comet Price
TURNTABLES		
ARENA SP25 with base, cover ..	£22 1 0	£17 19 6
B.S.R. McDONALD MP60 ..	£15 0 0	£10 19 6
B.S.R. McDONALD 670 ..	£19 19 6	£14 19 6
GARRARD SP25, fully wired with Goldring G800 magnetic cartridge, complete with base, plinth and cover ..	Special price £20 19 6	
GARRARD SP.25 Mk II ..	£15 11 4	£10 10 0
GARRARD AP.75 ..	£23 1 0	£17 19 6
GARRARD SL.55 ..	£13 1 9	£11 12 6
GARRARD SL.65B ..	£19 1 5	£14 9 6
GARRARD SL.75B ..	£35 12 0	£28 19 6
GARRARD SL.95B ..	£45 9 0	£37 19 6
GARRARD 401 ..	£37 1 2	£26 10 0
GARRARD SL.72B ..	£30 2 0	£24 19 6
GARRARD 3500 with GKS Cartridge ..	£15 15 0	£11 19 6
GOLDRING GL.69 Mk. II ..	£26 12 6	£21 19 6
GOLDRING GL.9P Mk. II ..	£32 1 0	£27 19 6
GOLDRING GL.75 ..	£36 8 2	£29 19 6
GOLDRING 75P ..	£46 18 8	£39 19 6
GOLDRING Covers for 69P and 75P ..	£4 4 3	£3 8 0
GOODMANS 3025 complete with G800 cartridge ..	£37 14 0	£25 19 6
PHILIPS 228 ..	£19 19 6	£16 19 6
PHILIPS GA146 ..	£29 19 6	£24 19 6
PHILIPS 217 ..	£32 0 9	£27 4 0
PHILIPS 202 Electronic ..	£64 0 0	£54 0 0
THORENS TD.125 ..	£75 17 8	£61 19 6
THORENS 125AS ..	£120 3 11	£99 19 6
THORENS 150A Mk II ..	£43 12 7	£32 19 6
THORENS 150AB Mk II ..	£47 8 7	£40 19 6
THORENS TD.124/11 ..	£46 15 10	£39 19 6
Bases, plinths, and covers stocked.		

	Rec. Retail Price	Comet Price
SPEAKERS		
ARENA HT 27 ..	£18 18 0	£13 19 6
ARENA HT 28 ..	£17 17 0	£12 19 6
ARENA HT 21 ..	£10 10 0	£9 5 0
ARENA HT 7 ..	£19 19 0	£17 0 0
ARENA HT 10 ..	£22 1 0	£18 19 6
ARENA HT 26 ..	£32 11 0	£26 19 6
B & W DM3 ..	£63 0 0	£53 6 0
B & W P2H ..	£94 10 0	£79 0 0
B & W DM1 ..	£32 0 0	£25 19 6
CELESTION Ditton 10 ..	£21 3 2	£17 5 0
CELESTION Ditton 15 ..	£29 0 0	£22 19 6
CELESTION Ditton 25 ..	£59 17 0	£49 0 0
DULCI AS 3 ..	£8 8 0	£6 19 6
GOODMANS Majesta ..	£57 0 0	£48 19 6
GOODMANS Maxima ..	£20 7 9	£16 19 6
GOODMANS Mezzo II ..	£30 18 0	£23 0 0
GOODMANS Magna-Mk ..	£42 2 0	£29 19 6
GOODMANS Marimba ..	£24 0 1	£19 19 6
GOODMANS Mambo ..	£22 5 6	£17 19 6
GOODMANS 3005 (pair) ..	£25 0 0	£18 19 6
KEF Celeste ..	£29 0 0	£21 10 0
KEF Concord ..	£43 10 0	£32 19 6
KEF Concerto ..	£53 10 0	£41 19 6
KEF Cresta ..	£22 3 4	£18 5 6
LEAK Sandwich ..	£45 10 0	£34 19 6
LEAK Mini-Sandwich ..	£29 15 0	£22 19 6
LOWTHER Acoustica (with PM6) ..	£45 10 0	£38 7 6
LOWTHER Ideal Baffle ..	£35 10 0	£29 17 6

	Rec. Retail Price	Comet Price
LDWOTHER Acoustica (with PM7) ..		
QUAD Electrostatic ..	£66 0 0	£52 19 6
PHILIPS RH 481 ..	£11 0 0	£9 2 6
PHILIPS RH 482 ..	£18 0 0	£14 19 6
WHARFEDALE Speakers		
Alfredale ..	£69 10 0	£57 14 0
Denton ..	£19 0 0	£14 19 6
Super Linton ..	£22 10 0	£18 10 0
Melton ..	£29 10 0	£22 19 6
Dovedale 3 ..	£39 10 0	£29 19 6
Rosedale ..	£59 10 0	£48 19 6
WHARFEDALE UNIT		
3 Speaker Kit ..	£11 19 6	£9 19 6
WHARFEDALE UNIT		
4 Speaker Kit ..	£16 0 0	£13 10 0
WHARFEDALE UNIT		
5 Speaker Kit ..	£23 10 0	£19 19 6
CHASSIS SPEAKERS		
GOODMANS Axiletta 8 ..	£7 9 6	£5 10 6
GOODMANS Twinaxiletta 8 ..	£27 8 8	£21 8 6
GOODMANS Axiom 10 ..	£8 16 8	£6 19 6
GOODMANS Axiom 80 ..	£26 1 4	£21 12 6
GOODMANS Twinaxiom 10 ..	£9 8 5	£7 15 0
GOODMANS Axiom 201 ..	£13 9 0	£9 19 6
GOODMANS Axiom 301 ..	£19 5 0	£14 10 0
GOODMANS Audiom 51 ..	£12 3 0	£9 10 0
GOODMANS Audiom 61 ..	£17 12 0	£12 19 6
GOODMANS Audiom 81 ..	£29 13 0	£22 10 0
GOODMANS Audiom 91 ..	£33 12 0	£25 19 6
GOODMANS Audiom 91/100 ..	£34 17 0	£26 2 0
GOODMANS ARU 180 ..	£37 17 8	£28 19 6
GOODMANS ARU 280 ..	£37 17 8	£28 19 6
GOODMANS ARU 480 ..	£5 8 5	£4 1 3
GOODMANS ARU 172 ..	£37 17 8	£28 19 6
GOODMANS Trebar 100 ..	£25 11 0	£15 6 0
GOODMANS Trebar 5K/20K ..	£11 4 0	£8 8 0
GOODMANS Attenuator ..	£3 1 4	£2 6 0
GOODMANS Crossover		
Networks XO/950/5000 ..	£8 8 7	£6 6 0
GOODMANS Crossover ..	£6 7 9	£4 15 8
Networks XO/950 ..	£2 6 0	£1 14 6
Networks XO/5000 ..	£2 6 0	£1 14 6
WHARFEDALE 8 inch Bronze/RS/DD ..		
WHARFEDALE Super 8/RS/DD ..	£7 12 0	£6 6 0
WHARFEDALE Super 10/RS/DD ..	£12 14 0	£10 10 0
WHARFEDALE WMT 1 Matching Transformer ..		
	16 9	13 6

HI-FI STEREO TAPE DECKS AND TAPE RECORDERS

	Rec. Retail Price	Comet Price
AKAI X-360 ..	£339 0 0	£284 0 0
AKAI X-360D deck ..	£280 0 0	£243 0 0
AKAI 1710 ..	£109 0 0	£85 19 6
AKAI 1710L ..	£99 17 0	£89 19 6
AKAI 1800 ..	£156 0 0	£133 0 0
AKAI 1800SD ..	£199 0 0	£167 0 0
AKAI 4000 ..	£124 18 0	£99 19 6
AKAI 4000 D deck ..	£89 19 1	£69 19 6
ALBA R22 Battery/Mains ..	£50 5 0	£29 19 6
BUSH TP 80 Cassette Tape		
BUSH TP 80 ..	£27 15 8	£24 19 6
FERGUSON 3224 Twin Track ..	£33 14 0	£24 19 6
FERGUSON 3246 ..	£41 14 0	£32 19 6
FERGUSON 3247 4-track ..	£47 1 0	£37 19 6
FERGUSON 3244 Stereo 4-track ..	£97 18 0	£79 19 6
GRUNDIG C200 Cassette ..	£37 19 0	£29 19 6
GRUNDIG TK 120 Continental ..	£39 5 0	£29 19 6
GRUNDIG TK 124 ..	£44 18 0	£34 19 6
GRUNDIG TK 144 ..	£49 19 6	£39 19 6
GRUNDIG 149 ..	£57 12 8	£47 19 6
MARCONI 4218 Stereo tape Recorder		
MARCONI 4218 ..	£28 11 2	£19 19 6
PHILIPS 3302 Cassette Tape Recorder		
PHILIPS 3302 ..	£28 7 0	£21 19 6
PHILIPS 4302 Twin Track Auto.		
PHILIPS 4302 ..	£35 17 6	£25 19 6
PHILIPS 4307 4-track ..	£49 10 0	£38 19 6
PHILIPS N4404 (4 track stereo)		
PHILIPS N4407 Stereo ..	£83 0 0	£69 19 6
PHILIPS N4308 ..	£105 0 0	£89 19 6
PHILIPS N4308 ..	£60 10 0	£49 19 6
TELETON FXB 510D Stereo ..	£52 10 0	£43 19 6
TOSHIBA Battery/Mains ..	£45 3 0	£29 19 6
TRUVOX PD 102 Stereo Tape Recorder ..	£114 15 3	£79 0 0

COMET Hi-Fi DISCOUNT WAREHOUSES

Reservoir Road, Clough Road, Hull HU6 7QD. Tel 407906
also at 68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally.
Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Comprehensive Hi-Fi Catalogue available 9/- Add 9/- for post and packing on all orders under £50 (cartridges 4/-). Orders over £50 add 12/- for Securicor delivery. Make cheques. Money Orders payable to "COMET"

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM



★ Moderate size only 95 x 14 x 10in. COMPLETE KIT 20 Gns
★ Response 30-20,000 c.p.s. Impedance 15 ohms
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. 3 Gns. and 9 monthly payments 45/6 (Total 22! Gns.). DEMONSTRATIONS AT ALL BRANCHES

AUDIOTRINE HIGH FIDELITY SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. £5.15.0



OR SENIOR 15 WATT INC. HF128 15,000 LINE SPEAKER £6.15.0. CARR 6/6

AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. "E" indicates Roll Rubber cone surround. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.



HF801D 8" 8W 54/3 HF120D 12" 15W 79/9
HF120D 10" 10W 67/11 HF120D 12" 15W 89/9
HF100D 10" 15W 24.19.0 HF128 12" 15W 25.5.0
HF105DL 10" 10W 6Gns. HF128D 12" 15W 25.15.0

HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 5/- per enclosure
JES Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any Hi-Fi speaker. £4.14.6
SES For optimum performance with any Hi-Fi speaker. £5.15.0
SE10 For outstanding results SE12 For exact prtnece with 12in with 10in. Hi-Fi spkr £6.19.9
Size 24x15x10in. P.t'd. Size 25 x 16 x 10in.



RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

RP2C Garrard SP25 Mk II (with heavy turntable) fitted Goldring C890 high compliance ceramic Stereo/Mono cartridge with diamond tip. £24.12.6 Carr. 9/6

RP5C Garrard 2025 Auto Unit fitted Garrard GCS 23 Stereo Cartridge with diamond tip. Plinth & Cover as RP2C. £15 Gns.

Other types available with Magnetic cartridges and with alternative design plinths.

R.S.C. PLINTHS

for Record Playing units, Carr. 10/25, 20/25, 30/25, AT/60, SP25 etc.



AVAILABLE WITH TRANSPARENT PLASTIC COVER 3 Gns. 6 Gns. Carr. Free

LEADING MAKES HI-FI EQUIPMENT at CLEARANCE PRICES Available at branches only

LINEAR L10 HIGH FIDELITY 10W AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. 12! Gns. Carr. 12/6

OR FACTORY BUILT 15! Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 81/1 (Total £13.3.9) Available in Teak or Afrormosia veneered housing. 10Gns.



R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'hit' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9! x 23 x 5 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit or parts with full wiring diagrams and instructions. 7 Gns Carr. 7/6

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE £21.9.0

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL. PRE-AMP. Two input sockets with mixing facilities High sensitivity. 5 valves. Independent Bass and treble controls. Frequency response $\pm 3dB$ 30-20,000 c.p.s. Hum level -60dB. Sensitivity 40 millivolts. For Crystals or Ceramic P.U.s. High Impedance "Mike". 9! Gns.

For Musical Instruments etc. 8in. Chassis. For 3 x 15 ohm spkrs. SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover 27/6. Price Factory built 13! Gns. or Deposit 3 and 9 monthly payments of 30/5 (Total £16.13.9) RSC A11 TRANSISTORIZED VERSION of above complete kit 9 Gns. (Assembled 13 Gns.)

R.S.C. COLUMN SPEAKERS

COVERED IN REXINE/VYNAIR, IDEAL FOR VOCALISTS AND PUBLIC ADDRESS. 15 ohm matching. TYPE C48S 26/30 WATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx 48 x 10 x 5in. Or deposit 23 and 9 monthly payments 35/6 (Total £18.19.6). Carr. 10/- TYPE C412S, 50 WATTS. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 8 x 9in. approx. Carr. 15/- Or Deposit 24 and 9 monthly payments of 58/8 (Total £30.8.0). 16 Gns. 26 Gns.

30 WATT HI-FI AMPLIFIER

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP. A 2 or 4 input. 2 vol control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.A. fascia. Neonid l.e.c.o. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 23.14.0 and 9 monthly payments of 42/- (Total £22.12.0) 19 Gns. Carr. 12/6



HIGH QUALITY LOUSPEAKERS

IN TEAK OR AFRORMOSIA VENEERED CABINETS L12 12" x 8" 10 Watt 10,000 lines £4-19-9 12 12" 20 Watt 10,000 lines £8-19-9 3 or 15 ohms. Carr. 7/6 State impedance required

R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, radio radio, tape, Peak Output rating. Loudspeaker unit horizontal or vertical mounting. ★ Two extra heavy duty 12in. Loudspeakers. ★ Four Jack inputs and two Volume Controls for simultaneous use of four pick-ups or "mikes". Bass and Treble controls. Deposit 23.4.9 and 9 monthly payments of 25.1.9. (Total 60! gns.) Send S.A.E. for leaflet 55 Gns. Carr. 30/-



FAL PHASE 50 AMPLIFIER

Solid state 3 Separately controlled inputs Ind. Bass and Treble Controls. Output for Speaker's 3-30 ohms. Size 17 1/2 x 10 1/2 x 10 1/2 200-250 A.C. mains. Peak Output rating. For fuller details of Phase 29 Gns. Carr. Free

FAL PHASE 100 AMPLIFIER

100 Watt Solid State 4 Separately controlled inputs Plus master volume Control. Ind. Bass and Treble Controls. Output for speaker's 3-30 ohms. Includes circuit to guard against damage from accidental shorts I.H.F.M. Output rating 59 Gns.

RSC 50 Watt L/SPEAKER UNITS

Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Two tone Rexine and vinyl finish. 28 Gns.

RSC G100 100 Watt

peak output. Complete with pair of speaker columns and a Bass Unit (Six 12" and Two 15" speakers) 99 1/2 Gns.

FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous, 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis.

'POP' 100 12" 100Watt 14,500 gauss 8/15Ω 21 Gns. Dep. 26 and 9 monthly payments 22 (Total £24). FOR BASS GUITAR DR ELECT. ORGAN ETC.

'POP' 60 15" 60 Watt 14,000 gauss 8/15Ω 12 Gns. Dep. 3 gns. and 9 monthly payments 25/8 (Total £14.12.6)

'POP' 50 12" 50 Watt 14,000 gauss 10 Gns. 15Ω Dep 22 and 9 monthly payments 22/6 (Total £12.2.6) Pair suitable all purposes

F A N E LOUSPEAKERS

'POP' 30C 12in. 25 WATT Dual Cone 15Ω £5-19-9 (For uses other than Bass Guitar Carr. free on deposit or Elect. Organ. Deposit 21 and 9 monthly payments 13/- (Total £8.17.0))

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull High output, with Pre-amp/Tone Control Stages. Hum level -70dB. Frequency response $\pm 3dB$ 30-20,000 c.p.s. All high grade components. Valves EP86, EP86, ECC83, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 30 millivolts. Suitable for High Impedance microphones. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250 v., 50 c/s of parts with point to point wiring diagram and A.C. mains. For 3 or 15 ohm speakers. Complete Kit instructions. Twin-handled perforated cover 35/- Or factory built with EL34 output valves and 12 months' guarantee for 18 Gns. Carr. 12/6

RSC TRANSFORMERS and L.F. CHOKES

FULLY GUARANTEED. Impregnated and Interleaved where necessary

Primaries 200-250v. 50c/s. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.

250v., 60mA, 6.3v. 2a.	17/11
250-0-250v., 60mA, 6.3v. 2a.	18/11

FULLY SHROUDED UPRIGHT MOUNTING

250-0-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 2a.	24/9
250-0-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	24/9
300-0-300v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	28/9
300-0-300v., 180mA, 6.3v. 4a., c.t., 6.3v. 1a.	37/11
For Mullard 510 Amplifier	47/11
350-0-350v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	37/9
350-0-350v., 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	47/9
425-0-425v., 200mA, 6.3v. 4a., c.t., 5v. 2a.	38/9
425-0-425v., 200mA, 6.3v. 4a., c.t., 6.3v. 3a., 0v. 2a.	38/9
450-0-450v., 250mA, 6.3v. 4a., c.t., 5v. 2a.	39/9
450-0-450v., 250mA, 6.3v. 4a., c.t., 5v. 3a.	39/9

TOP SHROUDED DROP-THERO TYPE

250-0-250v., 70mA, 6.3v. 2a., 0-5-6.3v. 2a.	23/9
250-0-250v., 100mA, 6.3v. 3a.	27/9
250-0-250v., 100mA, 6.3v. 2a., 6.3v. 1a.	28/9
350-0-350v., 80mA, 6.3v. 2a., 0-5-6.3v. 2a.	29/11
250-0-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9
300-0-300v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	39/9
300-0-300v., 180mA, 6.3v. 4a., 0-5-6.3v. 3a.	46/9
Suitable for Mullard 510 Amplifier	46/9
350-0-350v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	46/9
350-0-350v., 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	46/11

FILAMENT or TRANSISTOR POWER PACK

Types 6.3v. 1.5a. 8/9; 6.3v. 2a. 9/9; 6.3v. 3a. 13/9; 6.3v. 6a. 22/9; 12v. 1a. 0/11; 12v. 3a. or 24v. 1.5a 23/9; 0-9-18v. 11a. 19/11; 0-12-25-42v. 2a. 21/9; 0-12-19/11; 3a. 21/11; 5a. 25/11; 6a. 29/9; 3a. 36/9	
---	--

CHARGE TRANSFORMERS 0-9-15, 14, 19/9; 0-12-19/11; 3a. 21/11; 5a. 25/11; 6a. 29/9; 3a. 36/9

AUTO (Step up/step down) TRANSFORMERS

0-110/120v., 200-230-250v., 50-80 watts 10/9;	
150 watts, 33/8 250 watts 40/8; 500 watts 105/-	

OUTPUT TRANSFORMERS

Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω	8/9
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω	14/9
Push-Pull 10 watts 6V6, ECL86 to 3 Ω, 5 Ω or 15 Ω	24/9
Push-Pull Ultra Linear for Mullard 510, etc.	39/9
Push-Pull 15-18 watts, sectionally wound 61A, KT66, etc. for 3 or 15 Ω	35/9
Push-Pull 20 watt high quality sectionally wound EL34, 616, KT66 etc. for 3 or 15 Ω	59/9

SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 12/9; 100mA, 10H, 200 Ω 10/9; 80mA, 10H, 350 Ω 8/9; 60mA, 10H, 400 Ω 4/11.

SELENIUM RECTIFIERS F. W. (Brigded)

All 6/12v. D.C. output. Max. A.C. input 18v.	
1a. 4/3. 2a. 6/11; 3a. 9/9. 4a. 12/9. 6a. 15/9.	

R.S.C. HIGH FIDELITY STEREO 'PACKAGE' OFFERS

Four fully wired units ready to 'plug in'!

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Garrard SP25 mk II Turntable on Plinth with cover
- ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ Pair of Stanway II 'Speaker Units'

76 Gns. Carr. 30/-
Special Total Price

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Goldring Transcription Turntable on Plinth as illustr.
- ★ Shure or Goldring Magnetic P.U. Cartridge.
- ★ Pair of Stanway II Loudspeaker units

86 Gns. Carr. 30/-
Special Total Price

Matching as recommended for optimum performance. Send S.A.E. for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



ATTRACTIVE TEAK or AFORMOSIA VENEERED CABINETS and PLINTHS
TERMS AVAILABLE ALL PACKAGE OFFERS

- ★ TA12 Amplifier 6 + 5 watt in veneered housing
- ★ Garrard SP25 mk II Player unit on Plinth
- ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ Pair of Dorchester Loudspeaker Units

53 Gns. Carr. 25/-
Total Price

Or Deposit £7 and 9 monthly payments £6.28 (Total 59 gns.). Transparent Plastic Cover 3 gns. extra.

AS ABOVE BUT WITH GARRARD 3000 AUTOCHANGER AND SONOTONE 9TA Ceramic Cartridge **47½ Gns.** Carr. 25/-
in lieu of SP25 and CS90

Or Deposit £6 and 9 monthly payments £5.11.5 (Total £56.2.9) Trans. Plastic cover 3 gns. extra.

LOW DEPOSIT CREDIT TERMS

Available on purchases over £8
KITS of parts excepted

INTEREST CHARGES REFUNDED
On Credit Sales settled in 3 months

AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

5 + 5 WATT OUTPUT
GARRARD 5200 Changer

with low mass pick-up arm and GCS38 Cartridge.
CONTROLS: TREBLE, BASS, VOLUME STEREO BALANCE. Operation on standard 200-250v. A.C. mains. Output rating I.H.F.M.



Luxurious Teak Veneer Finished Cabinets. Transparent plastic (tinted) cover included for main unit. Silver finished fascia plate and matching control knobs.

PAIR OF LOUDSPEAKER UNITS

incorporating high flux 8" x 3" speaker. Size approx. 13 x 7½ x 8½ ins.

Price complete **39 Gns.** Carr. ONLY 25/-
Deposit £5 and 9 monthly payments 4 gns (Total 44.18.0)

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINABLE FROM THIS COMPACT LOW PRICED SYSTEM

RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing Transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups etc., and for loudspeaker watt. output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive silver finished metal fascia plate and matching control knobs.

Complete KIT of PARTS INCLUDING FULL WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£9.19.9**



Or FACTORY BUILT in Teak veneered cabinet as illustrated **£12.10.0** carr. 7/9 Or deposit 37/6 and 9 monthly payments 29/2 (Total £15).

PACKAGE OFFER SAVE £3 Above G66 assembled in cabinet.
plus pair DORCHESTER LOUDSPEAKER UNITS **£27.9.6** Carr. 4/1
Or Deposit £5 and 9 monthly payments 57/8 (Total £30.17.6).

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER



★ High-sensitivity. ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Selection ★ Drift-free reception ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at a considerably less than the cost of comparable units. FACTORY BUILT 18 gns. Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit £6.1.0 and 9 monthly payments. 2 gns. Total £24.19.0. Stereo version. 23½ gns. Carr. 10/6 extra

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate, credit terms available.

DORCHESTER Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. Dual Cone speaker. Imp. 3 or 15 ohms.

£8.19.9 Carr. 7/6



STANWAY II Size 20 x 10½ x 9in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

R.S.C. TA12 MKIII 6+5 + 6+5 WATT STEREO AMPLIFIER FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for Mono use ★ Speaker Output 3-16 ohms ★ For 200-250v. A.C. mains ★ Pre-quey Response 20-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.2% at 1,000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Fascia plate and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 mth gntee 17 Gns Or Deposit £3.0.0 and 9 mthly pmt 38/10 (Total 19½ Gns.) Or in Teak or Afrormosia veneer. Louding 20½ Gns. Dep. 3 Gns. and 9 monthly payments 46 8. Total 23 Gns.



13½ Gns. Carr. 7/9


R.S.C. SUPER 30 Mk II HIGH FIDELITY STEREO AMPLIFIER

High Grade Components Specifications comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.
OUTPUT 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.
INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5mV.

FREQUENCY RESPONSE ± 2 dB. 10-20,000 c.p.s.
TREBLE CONTROL +17 dB to -14 dB at 10 Kcs.
BASS CONTROL +17 dB to -15 dB at 50 c/s.
HUM LEVEL -80 dB.

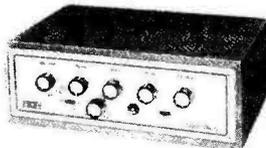HARMONIC DISTORTION 0.1% at 10 watts/1,000 c.p.s. Employing Twin Printed Circuits. 200/250v. A.C. mains operation.
CROSS TALK 52 dB at 1,000 c.p.s.



CONTROLS 5 Position Input Selector. Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.
INPUT SOCKETS (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).
CHASSIS Strong Steel construction. Approx. 12 x 3 x 8in.

FACIA PLATE Attractive design in rigid plastic silver background black lettering. Silver finish matching control knobs as available.

Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

COMPLETE KIT OF PARTS Point to point wiring diagrams and detailed instructions. **22 Gns.** Carr. 15/-

UNIT FACTORY BUILT 29 Gns.

With 12 months guarantee.
or Deposit £4 and 9 monthly payments 66/8 (Total £38.16.3) or in Teak or Afrormosia veneer housing Carr. 15/- Terms: Deposit 4/4 and 9 monthly payments of 74/2 (Total £37.7.6). Send S.A.E. for leaflet.

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279
DERBY 26 Osbaston Rd., The Spot (Half-day Wed.) Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
HULL 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Hencroft Lane, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries.
Branches open all day Sats. **MAIL ORDERS MUST NOT BE SENT TO SHOPS**

32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) **LEEDS** Tel. 28252
73 Dale St. (Half-day Wed.) Tel. CENTral 3573 **LIVERPOOL**
238 Edgware Road, W2 (Half-day Thurs.) Tel. **LONDON** PAD 1629
60A Oldham Street (Half-day Wed.) Tel. CENTral 2778 **MANCHESTER**
106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
41 Blackett Street (Opp Fenwick's Store) **NEWCASTLE UPON TYNE** (Half-day Wed.) Tel. 21469
13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

SOLDERING IRONS?

Whatever your particular application we are almost certain to have just the tool for the job.

ADAMIN—featherweight instruments with the slip-on bits and the big performance.

LITESOLD—the best-selling seven-model range of top-quality 'conventional' irons.

THERMOSTATIC CONTROL? The new LITESTAT instruments are surely the most advanced available — at not so advanced prices.

You ought to get the whole story. Ask for catalogues L10. Free.

LIGHT SOLDERING DEVELOPMENTS LTD
28 Sydenham Road, Croydon, CR9 2LL
Telephone: 01-688-8589 & 4559



GARRARD PRICES SLASHED!!!

SP25 MkII £10-15-0 p.p. 10/-



PLINTHS & COVERS

Teak finish, slenderly designed, ready for use. For Models SP25, 2025, 3000, SL65B. Spindle can be left in position whilst cover on. Cover tinted smokey.

FANTASTIC VALUE 79/6 p. p. 7/6

GARRARD TURNTABLES

- 2025TC Son. 9tahc dia. £9 10 0
- SP25 Mk. II less cart. £10 15 0
- 3000 Son. 9tahc dia. £9 12 6
- SL65B less cart. £13 19 6
- AP75 less cart. £15 19 6
- SL72B less cart. £24 0 0
- SL75B less cart. £25 0 0
- A70 Mk. II less cart. £11 15 0

p.p. 10/- on each of the above

GARRARD SP25 AND OTHERS ON PLINTHS WITH COVERS

Complete, not wired. SP25. £14.12.6 p.p. 15/- . Ready wired with 5 pin DIN or Phono 10/6 extra. For any other deck, 3000, 2025TC, SL65B, add price of deck to plinth and cover and 15/- p.p. and 10/6 for wiring.

MISC

L.L. Nova 505 Amp. Mag. & Cer. Cart. Input 5 watts per Chan. £15.10.0 p.p. 10/-.

"Master" Magnetic Cartridge, Diamond Stylus. 65/- p.p. 5/-.

3 Way Speaker System. Teak cabinet size 14 1/2 x 8 x 6. 10 watts peak. £5.19.6 p.p. 7/6

Best Stereo Headphone 8Ω good quality. 52/6 p.p. 5/-.

AUDIO SUPPLIES (QUOTE PW)

Callers—50A STAMFORD HILL, LONDON, N.16

Mail orders—103A DALSTON LANE, LONDON, E.8

(Quote PW)

TELEPHONE E : 01-806-3611 or 01-254-4957

Open Mon.—Sat. 9 a.m.—6 p.m. Thur. half day. Open Sunday 10 a.m.—2 p.m.

multi-drawer storage units

NEW! HANDY! TIDY! I-N-T-E-R-L-O-C-K-I-N-G

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots—removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (5ins x 2 1/2ins x 2 1/2ins)

Usually 2/6 each. Our Price 24/- dozen

DOUBLE UNITS (5ins x 4 1/2ins x 2 1/2ins)

Usually 4/6 each. Our Price 40/- dozen

PLUS QUANTITY DISCOUNTS!

Orders £5 and over Deduct 1/- in the £


Orders £10 and over Deduct 1/6 in the £

Orders £20 and over Deduct 2/- in the £

Packing/Postage/Carriage: Add 6/- to all orders under £3. Orders £3 and over,

packing/postage/carriage free

Quotations for Larger Quantities

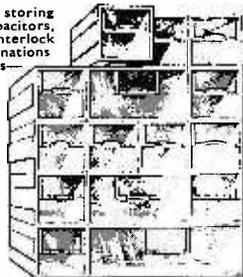

(Dpt. PW10) 31 ALBERT RD
 HENDON - LONDON NW4

A place for everything
 Everything in its place!

JET KING PRECISION BLOW TORCH—SOLDERING IRON

A FABULOUS MULTI-PURPOSE TOOL — **Now Reduced from 35/- to 19/11 p.p. 1/6**
 AMAZINGLY COMPACT YET VERY POWERFUL. Small enough to fit in your pocket and get into tight working areas. Ideal for precise working and intricate soldering.

The pocket size tool that is completely portable and self contained — operates from small instantly-replaceable gas cylinders — each giving 45 minutes continuous burning.

A boon to Do-It-Yourself enthusiasts, Motorists, Caravanners, Boating enthusiasts and Modelmakers.

Develops a pinpoint flame of 3,500°F yet under finger-tip control. Replacement cylinders readily available.

Complete Kit with torch and soldering attachments and spare cylinder. Send 19/11 plus p & p 1/6 to:

Kidde Merchandising, Div. WK, Belvue Road, Northolt, Middx. Only available at this price whilst present stock lasts.



The 'KIT IDEA' by HEATHKIT

kit building is so easy the
Heathkit way.



TRY IT FOR YOURSELF

**START WITH A SMALL
BUT VERY USEFUL KIT**

**THE NEW HEATHKIT
BATTERY CHARGER**

PRICE ONLY

£2.18.0. plus carr. 6/-

- POWERFUL OUTPUT UP TO 4 AMPS
- SOLID KNOCKABOUT CASE
- FOR 6V OR 12V CARS
- FULLY FUSED
- SAFE DOUBLE WOUND TRANSFORMER
- ROBUST AMMETER

Here's the easy to build, inexpensive kit to introduce you to kit building. As well as the fun and fascination of building it yourself you get do-it-yourself savings. The clear, simple, fully illustrated instructions make assembly foolproof. This is the battery charger to keep your car battery in top working condition.

Hurry, and make sure of your order today.

P.S. This also makes an excellent seasonal present . . .



A Schlumberger Company

HEATH (Gloucester) LTD GLOUCESTER GL2 6EE

(Block capitals please)

Name.....

Address.....

Post Code.....

Please send me a battery charger kit for
which I enclose £3.4.0, including carriage.

51/11A

**BELCO AF-5A
SOLID STATE SINE SQUARE
WAVE C.R. OSCILLATOR**

Line 18-200,000 Hz; Square 18-50,000 Hz
Output max + 10 dB (10 K ohms)
Operation internal batteries
Attractive 2-tone case 7 1/2" x 5 1/2" x 4"
Price **£17.10.0**.
Carr. 3/6.

CLASS D WAVEMETERS

A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. **£5.18.6**. Carr. 7/6. Or brand new with accessories. **£7.19.8**. Carr. 7/6.

SPECIAL OFFERS!

Garrard SP25 MK II fitted Goldring B800 cartridge and wooden plinth and plastic cover. Total list price **£35**.
OUR PRICE **£19.15.0** Carr. 10/-
Plastic cover 25/- extra.

GOLDRING GL69/2 fitted Goldring B800 cartridge complete with diamond base and cover. Total list price **£50.16.0**.
OUR PRICE **£39** Carr. 10/-

*** TRANSISTORISED FM TUNER ***

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 8x4x2 1/2in. 3 I. F. stages. Double tuner, discriminator. Ample output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108Mc/s Ready built ready for use. Fantastic value for money. **£6.7.6**. P. & P. 2/6. Stereo multiplex adaptor 89/6.

**TYPE 13A DOUBLE BEAM
OSCILLOSCOPES**

An excellent general purpose D/B oscilloscope. T.B. 2 cps-760 Kc/s. Bandwidth 3.5 Mc/s. Sensitivity 33mV/cm. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. **£22.10.0**. Carriage 30/-.

B.C. 221 FREQUENCY METERS
latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **£27.10.0** each. Carr. 10/-

**MARCONI
T/44/TF956
AF Absorption
Wattmeter**
1 μwatt to 6 watts.
£20. Carr. 10/-

**SOLARTRON CD 71152
Double Beam Oscilloscopes**

D.C. to 9 Mc/s. Perfect order **£65**. Carr. 50/-

TO-3 PORTABLE OSCILLOSCOPE
3in. tube. 2 amp. Sensitivity 0.1 μV p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5 cps-800KHz. Input Imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. **£37.10.0**. Carr. 10/-

**TRANSISTORISED L.C.R. A.C.
MEASURING BRIDGE**

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω-11 Ω meg Ω 0. Range ± 1% 0.1 μH-11 H HENRYS 6 Ranges -2% C. 10pF ± 110mFd. 6 Ranges ± 0%. TURNS RATIO 1:1/1000-1:11000. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. **£20**. P. & P. 5/-.

HALF PRICE OFFER! SINGLAR STEREO 25




Original price **£9.19.6**.
OUR PRICE **99/6** P. & P.
PRICE 3/-

Hi-Fi solid state pre-amplifier and control unit incorporating treble, bass, volume and balance controls. Switched input for p.u. (magnetic and ceramic), mike and radio. Will also accept tape head. Operates from 9V-12V battery (20V max. 7-0mA). Frequency response 25Hz-30KHz ± 1dB. Noise level better than -50dB on all inputs. Principally designed for use with Z12 Amplifier but full instructions are supplied to enable it to be used with any amplifier. Size 6 1/2" x 2 1/2" overall plus knobs. Brushed and polished aluminium front panel with matching knobs. Supplied brand new and guaranteed, with full instructions.

UNR-30 4-BAND COMMUNICATION RECEIVER


Covering 550 Kcs-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**

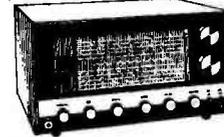**TRIO JR.310 New Amateur Band 10-80
Metre Receiver in Atack. £77.10.0.**



**LAFAYETTE HA-800 SOLID STATE
AMATEUR COMMUNICATION RECEIVER**

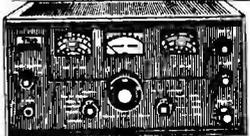Six bands 3-5.4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54Mc/s. Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. FET front end, product detector, variable BFO, 100Kc/s crystal calibrator, '8' Meter. Huge slide rule dial. Operation 230V AC or 12V D.C. Size 15 x 8 1/2 x 8 1/2in. Complete with instruction manual. **£57.10.0** Carr. Paid. 100Kc/s crystal 89/8 extra.



**TRIO JR. 500SE 10-80 Metre
Receiver £69.10.0**

10in. With instruction manual and service data. **£42** carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES**. Normally **£5.19.6**. OUR PRICE **£3.15.0** if purchased with above receiver.



**RCA COMMUNICATIONS
RECEIVERS AR88D**

Latest release by ministry BRAND NEW in original cases. 110-250v. A.C. operation. Frequency in 6 Bands. 535 Kc/s-32 Mc/s continuous. Output impedance 2-3,500 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price **£65.0.0**. Carr. **£2**.

LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. **£37.10.0**. Carr. 10/-

TELETON CR-10T AM/FM STEREO TUNER AMPLIFIER

A new model from Teleton. 31 solid state devices. 4 + 4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFU switch. Stereo headphone socket. Size 13 1/2" x 3 1/2" x 9 1/2" approx. PRICE **£29.19.6**. Carr. 7/6.

CLEAR PLASTIC PANEL METERS

First grade quality Moving Coil panel meters. Type MR 38P. 1 1/2in. square fronts.

500-0-500μA	27/6	50mA	27/6	150V. D.C.	27/6
1mA	27/6	100mA	27/6	300V. D.C.	27/6
10-10mA	27/6	150mA	27/6	500V. D.C.	27/6
2mA	27/6	300mA	27/6	750V. D.C.	27/6
5mA	27/6	300mA	27/6	15V. A.C.	27/6
10mA	27/6	500mA	27/6	30V. A.C.	27/6
750mA	27/6	3V. D.C.	27/6	150V. A.C.	27/6
1 amp	27/6	10V. D.C.	27/6	300V. A.C.	27/6
2 amp	27/6	15V. D.C.	27/6	500V. A.C.	27/6
5 amp	27/6	20V. D.C.	27/6	S meter 1mA 32/6	
20mA	27/6	100V. D.C.	27/6	VU meter 1	42/-

FULL RANGE OF OTHER SIZES IN STOCK SEND S.A.E. FOR LEAFLET

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 3in. dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 14/6. P. & P. 1/6.
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, 21/6. P. & P. 1/6.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms, 27/6 P. & P. 1/6.

CRYSTAL CALIBRATORS NO. 10



Small portable crystal controlled wavemeter. Size 7 x 7 1/4 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA at 12V D.C. 0.3A.

Excellent condition. **£9/8**. Carr. 7/6.

**TE-40 HIGH SENSITIVITY
A.C. VOLTMETER**

10 meg. input 10 ranges: -01/-003/-1/-3/1/3/10/30/100/300V. R.N.S. 400-1.2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. **£17.10.0** Carr. 5/-.

**LELAND MODEL 27 BEAT
FREQUENCY OSCILLATORS**

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. **£12.10.0** Carr. 10/-

TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. **£17.10.0**. P. & P. 6/-.
Additional probes available: R.F. 42/6. H.V. 50/-

**COSSOR 1049 DOUBLE
BEAM OSCILLOSCOPES**

D.C. coupled. Band width 1Kc/s. Perfect order. **£25**. Carr. 30/-.

AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmec. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. **£45**. Carr. 20/-.

ADDYSTONE VHF RECEIVERS Model 770H. 19-165 Mc/s. Excellent condition. **£160**.

**RUSSIAN C1-16 DOUBLE
BEAM OSCILLOSCOPES**

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions **£87**. Carr. paid.

**TE-16A Transistorised
Signal Generator. 5 ranges
400KHz-30MHz. An
inexpensive instrument for
the hamster. Operates
on 9v battery. Wide
easy to read scale.
800kHz modulation.
5 1/2 x 5 1/2 x 3 1/2in.
Complete with instructions
and leads. £7.19.6.
P. & P. 4/-**



**HOSIDEN DH-085
DE-LUXE STEREO
HEADPHONES**

Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug **£7.19.6**. P. & P. 2/6.

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.
150 watt. **£2**. 2.5 P. & P. 3/6.
300 watt. **£3**. 5 P. & P. 4/6.
500 watt. **£4.10.0**. P. & P. 6/6.
1,000 watt. **£6.10.0**. P. & P. 7/6.
1,500 watt. **£8.19.6**. P. & P. 8/6.
7,500 watt. **£15.10.0**. P. & P. 20/-

**G. W. SMITH
& CO (RADIO) LTD.
Also see oppo. page**

VARIABLE TRANSFORMERS

Input 230v. A.C. 50/60cs.
Output variable 0-250v.

BENCH MOUNTING
1 amp \$5.10. 8 amp \$14.10.0.
24 amp \$8.15.0. 10 amp \$18.10.0.
5 amp \$9.15.0. 20 amp \$27.0.0.

PANEL MOUNTING
1 amp \$5.10.0. 2 1/2 amp \$8.12.6.

TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instruction. \$15.0.0. P. & P. 7/6. S.A.E. for details.



PEAK-SOUND PRODUCTS. Full range of Amplifiers, Kits, Speakers, in stock.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Size: 20cs to 200 Kc/s on 4 bands. Square: 20cs to 30 Kc/s. Output Impedance 5,000 ohms, 200/250V. A.C. Supplied brand new and guaranteed with instruction manual and leads. \$16.10.0. Carr. 7/6.



MARCONI TF148E DISTORTION FACTOR METERS. Excellent condition. Fully tested. \$20. Carr. 15/-

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFd
2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New \$17.10.0 Carr. 7/6.



TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2CF8-1 MHz. Input Imp. 2 meg Ω 2P. P.F. Illuminated scale. 2in. tube, 115 x 180 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. \$22.10.0. Carr. 10/-



ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons

J1B. AUDIO SIGNAL GENERATOR. 15 c/s to 30 Kc/s. Sine wave. Output 600 ohms or 5 ohms \$30.0.0.

YM79. UHF MILLIVOLT METER. 100 Kc/s to 1,000 Mc/s. A.C. 10mV to 3v. D.C. 10 mV to 3v. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. \$125.0.0.

TT15. TRANSISTOR TESTER. Full range of facilities for testing PNP or NPN transistors in or out of circuit. \$37.10.0. Carriage 10/- per item.

TE-108S STEREO HEADPHONES

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY 39/6. P. & P. 2/6.



BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price \$27.10.0. Carr. 5/-



Latest Catalogue

The latest edition giving full details of a comprehensive range of HI FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. ... Over 230 pages, fully illustrated and detailing thousands of items—many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-.



SEND NOW—ONLY 7/6 P&P/16

GARRARD

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

1025 stereo	\$7.19.6	SL72B	\$24.19.6
40 Mk II stereo	\$8.8.0	AP75	\$16.19.6
2025T/C stereo	\$8.17.6	SL75	\$25.19.6
3030 stereo	\$9.19.6	SL75R	\$27.19.6
SP25 Mk II	\$10.19.6	SL95B	\$27.19.0
SL55	\$11.12.6	470/11	\$11.19.6
SL65B	\$14.19.6	401	\$25.0.0

Carriage 7/6 extra each item.
TEAK PLINTHS & PERSPEX COVERS
1. For SP25, SL65, SL55, 3000, 2025 T/C 2025, 1000. \$4.10.0
2. For AP75, SL75, SL95 \$5.19.6.
3. For SP25 etc. to operate with lid in place \$5.19.6.
Carriage 7/6 extra each type. Full range of Garrard accessories available.



LAFAYETTE LA-324 STEREO AMPLIFIER

A fine new HI-FI Amplifier at low cost. 12.5 watts R.M.S. per channel. 20-20,000 Hz \pm db. Inputs for Mag or Cer Cartridge, Tuner and Auxiliary. Output 4-16 Ω . Features Head-Phone Socket, Tape output. Protected output stage. Finish simulated walnut vinyl clad metal case with black and brushed anodised aluminium front panel. 10 1/2" x 3 1/2" x 8 1/2".

\$24

Carr. 7/6.


MULTIMETERS for EVERY purpose!



TE-51. NEW 20,000 Ω VOLT MULTIMETER with overload protection and mirror scale. 0/6/60/120/1200V. A.C. 0/3/30/60/300/600/3,000V. D.C. 0.60uA/12/300mA. D.C. 0/60K Ω meg. ohm. 92/6. P. & P. 2/6.



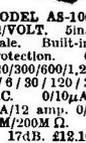TE-900 20,000 Ω /VOLT GIANT MULTIMETER mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 v. A.C. 0/25/12.5/150/50/250/1,000/5,000V. D.C. 0/50uA/110/100/300mA/10 amp. D.C. 02K/200K/20 MEG. OHM. \$15. P. & P. 5/-.




MODEL AS-100D. 100K Ω /VOLT. 5in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V D.C. 0/5/30/120/300/600v A.C. 0/10uA/60/300mA/12mA 12 amp. 0/2K/200K/2M/200M Ω . -20 to +17dB. \$12.10.0. P. & P. 3/6.




LAFAYETTE 57 Range Super 50k Ω /volt Multimeter D.C. volts 12 mV - 1000V. A.C. volts 1.5V - 1000V. D.C. current 25uA-10 amp. Ohms 0-10 meg Ω R - 20 to +81 dB. Overload protection. \$12.10.0. Carr. 3/6.



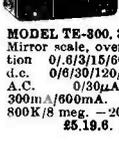
MODEL TE-800 20,000 O.P.V. Mirror scale, overload protection. 0/5/20/125/1,000 V.D.C. 0/10/50/250/1,000 V.A.C. 0/50 uA/250 MA. 0/60K Ω meg. -20 to +32 db. 75/- P. & P. 2/6.



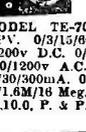MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection. 0/8/15/60/300/1,200V d.c. 0/8/30/120/600/1,200 V. A.C. 0/30uA/6mA/60mA/300mA/600mA. 0/6K/80K/800K Ω meg. -20 to +63 db. 25.19.6. P. & P. 3/-



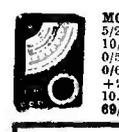MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V D.C. 0/6/30/120/600/1,200V A.C. 0/30uA/3/30/300mA. 0/10K/150 K/1.6M/16 Meg. Ω . \$5.10.0. P. & P. 3/-.



MODEL TE-10A. 90K Ω /Volt 10/50/250/500/1,500V. D.C. 10/50/100/500/1,000 v. A.C. 0/50uA/2.5mA/250mA D.C. 0/6K/6 meg. ohm. -20 to +25dB. 10.0, 100mFd. 0.100-0.1mFd. 69/6. P. & P. 2/6.



MODEL PT-34. 1,000 OPV. 0/10/50/250/500/1,000V AC and D.C. 0/1/100/500mA D.C. 0/100K Ω . 39/6. P. & P. 1/6.

SAVE UP TO 33% OF HI-FI EQUIPMENT Send for discount price list

AVO CT471A MULTIMETER

Battery operated, fully transistorised. Sensitivity 100m Ω /v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 m Ω HF, VHF, UHF Voltage with multiplier 4v to 400v up to 50 Mc/s, 40mV to 4v up to 1,000 Mc/s. Offered in perfect condition. \$55 each. Carr. 10/-

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 100% of application. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. \$6.19.6. P. & P. 3/6.



SINCLAIR EQUIPMENT

Project 60. Package offers. 2 x Z50 anodiser, stereo 60 pre-amp, PZ5 power supply. \$19.0.0 Carr. 7/6. Or with PZ6 power supply \$21. Carr. 7/6. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. \$21.10.0. Carr. 7/6. Transformer for PZ8. 59/6 extra. Add to any of the above \$4.17.6 for active filter unit and £16 for a pair of Q16 speakers. All other Sinclair products in stock. 2,000 amplifier \$23. Carr. 7/6. Neoteric amplifier \$46. Carr. 7/6.



SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20v-250v. Model MR 2305 5 amp 68 x 46 x 43mm \$8.76 Model MR 2310 10 amp 90 x 68 x 60mm \$11.19.8 Postage 2/6



TE111 DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections. Unbalanced P and Bridge T. Impedances 600 Ω range (0.14B x 10) + (14B x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.05dB. +Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new \$27.10.0. P. & P. 6/-



RECORDING HEADS

COSMOCORD 4-track heads. High imp. record/playback 65/- Low imp. erase 20/- MARRIOTT 4-track heads. High imp. record/playback 65/- Low imp. erase 20/- Post extra.

AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities.

3in. 225ft. L.P. acetate	8/6
3in. 600ft. T.P. mylar	10/-
5in. 600ft. std. plastic	8/6
5in. 900ft. L.P. acetate	10/-
5in. 1,200ft. D.P. mylar	15/-
5in. 1,200ft. L.P. acetate	12/6
5in. 1,200ft. L.P. mylar	16/-
5in. 1,800ft. D.P. mylar	22/-
5in. 2,400ft. T.P. mylar	39/6
7in. 1,200ft. std. acetate	12/6
7in. 1,800ft. L.P. acetate	15/-
7in. 1,800ft. L.P. mylar	20/-
7in. 2,400ft. D.P. mylar	25/-
7in. 3,600ft. T.P. mylar	45/-

Postage 2/- Over £3 post paid.

TAPE CASSETTES

Top quality in plastic library boxes. C60 60 min 8/6, 3 for 24/6 C90 90 min 12/6, 3 for 38/- C120 120 min 15/-, 3 for 43/6 Cassette Head Cleaner 11/3. Post Extra.

G.W.SMITH & CO. (RADIO) LTD

All Mail Orders to—
147, Church Street, London, W.2
Tel: 01-262 6562 (Trade supplied)

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	3/6	OC171	4/6
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2C301	2/6
ACY17	3/-	2C303	2/6
AF239	7/6	2N1302-3	4/-
AF196	10/-	2N1304-5	5/-
AF139	10/-	2N1306-7	6/-
BC154	5/-	2N1308-9	9/-
BC171 = BC107	2/6	2N3819 P.E.T.	9/-
BC172 = BC108	2/6	2N3844A	5/-
BF194	3/-	Power	
BF274	3/-	Transistors	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC26	5/-
BSY28	3/-	OC28	7/6
BSY29	3/-	OC35	5/-
BSY95A	3/-	OC36	7/6
OC41	2/6	AD149	10/-
OC44	2/6	AUY 10	30/-
OC45	2/6	2N3053	15/-
OC71	2/6	28034	10/-
OC72	2/6	Diodes	
OC73	3/6	AAV42	2/-
OC81	2/6	OA91	2/-
OC81D	2/6	OA79	1/6
OC139	2/6	OA31	1/6
OC140	3/6	1N914	1/6

FREE! Packs of your own choice up to the value of 10/- with orders over £4.

NEW UNMARKED UNTESTED PAKS

H10	25	Mixed volts 1½ watt Zeners Top Hat type.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
H11	30	Mat series "Alloy" PNP Transistors.	10/-
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
H15	30	Top Hat Silicon Rectifiers 750 mA. Mixed volts.	10/-
B86	50	Sil. Diodes sub. min. 1N914 and 1N918 types.	10/-
H16	8	Experimenters' Pak of Integrated circuits. Data supplied.	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H20	20	BY126/7 type Silicon Rectifiers 1 amp plastic. Up to 1,000 volts.	10/-
H6	40	250mW. Zener Diode DO-7 min. Glass Type. AV. 40% Good.	10/-

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt. .5 to 2 ma.	10/-
H8	4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100	10/-
B79	4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	10/-
B81	10	Reed Switches, mixed types, large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400 Ω Dark 1M Ω	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92	4	NPN. Sil. Trans. AO6 BSX20 2N2369 500 MHz, 360mW.	10/-
B93	5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96	5	2N3136 PNP Sil Trans. TO-18, HFE 100-300 I.C. 600mA. 200MHz.	10/-
B98	10	XB112 and XH1102 equiv. to AC126, AC156, OC81/2, OC71/2, NK271, etc.	10/-
H4	250	Mixed Resistors, Post and packing 2/-	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-
H9	2	OCF71 Light Sensitive Photo Transistors.	10/-

RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

PI PLEASE ASK FOR PAK P.I. ONLY 10/-
2/- P. & P. on this Pak

Complimentary Set.
NPN/PNP Germ.
Trans., Pak F.3.

2/6
PAIR

P.O. RELAYS **8 FOR**
Various Contacts and Coil Resistances.
Post & Packaging 5/- **20/-**

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS and CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVER-SEAS AND EXTRA FOR AIR MAIL.

BUY DIRECT FOR LOWEST PRICE!!
SAVE £'s£'s!!
DESPITE RECENT PRICE INCREASES

LATEST NEW & IMPROVED "JULIETTE"
NA5018A COMMUNICATIONS RECEIVER
(with AFC)
5 BAND MAINS/BATTERY SOLID STATE PORTABLE RECEIVER



OUR PRICE **36 gns.**
(cash only) + 9/- p/p
BFO—OPTIONAL
EXTRA—ADD 35/-

- AM Band: 540-1600 Kc/s Full Medium wave cover.
- Marine Band: 1.6-4.6 Mc/s Shipping, Hams, SW, etc.
- FM/VHF: 88-108 Mc/s Radios 2, 3, 4; TV Sound, Public Services, etc.
- Aircraft 108-134 Mc/s (improved sensitivity); Air-lines and Ground Control
- PB (High VHF Band): 148-174 Mc/s TV Sound, Race Ambulance, etc., Taxis, Shipping, Fuel Boards, Oil

Rigs, Gas and Electric Boilers, Local Hams, Industrial and Commercial Mobiles, Military aircraft etc. (DEPENDENT ON LOCALITY).

FEATURES—4" Dynamic PM Speaker. Directional telescopic VHF aerial. Internal Ferrite rod aerial. Illuminated Dial, size 9" x 5" x 4". Weight 5 1/2 lbs. Impressive and sturdy design in Chrome and Black Leatherette. Ultra sensitive 19 Transistor/Diodes circuit. Earpiece and Socket. Leather carrying and shoulder straps. Batteries incl. (STANDARDS EVER READY TYPE).

RETAIL TRADERS SUPPLIED
Enquiries to wholesale dept.
STOCKTON PARTNERS (DEPT. PW)
BRIGHOWGATE, GRIMSBY, LINCS.
Tel: 0472 64196/58815
Importers & Distributors of Electronic Equipment

4-STATION INTERCOM



£7.5.0.

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £11.19.6. P. & P. 8/6 extra.

INTERCOM/BABY ALARM



OUR PRICE ONLY **3 gns.**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.


Transistor TELEPHONE AMPLIFIER



59/6

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (P/W4)
189 KENSINGTON HIGH STREET, LONDON, W.8.

The Unique MULTI-MINI TWIN-VICE

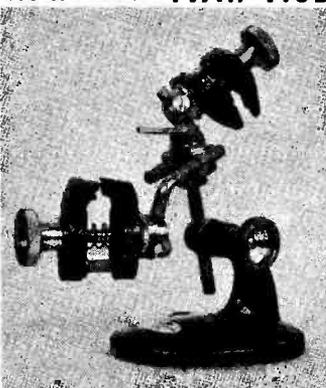

An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5-18-0 (4/6 P & P)


ALSO AVAILABLE

SINGLE VICE: £3-7-6 (3/- P & P)

COVENTRY MOVEMENT CO LTD.
BURNSALL ROAD, COVENTRY
CV5 6BU STD 0203-74363



LIND-AIR AUDIO

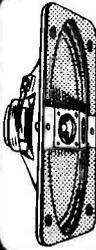

E.M.I. LOUDSPEAKERS
MODEL 450 13 $\frac{1}{2}$ " x 8"
 elliptical with twin tweeters, 8 ohm impedance, 10 watts. Brand New, guaranteed. Lind-Air Price **£9/6 P. & P. 4/6.**
MODEL 150 13 $\frac{1}{2}$ " x 8" elliptical, 3 and 15 ohm impedance, 10 watts. Lind-Air Price **£9/6 P. & P. 4/6.**
TEAK FINISH SPEAKER CABINETS
 Size 16" x 10" x 9". Ideal for above unit. **£5.19.6**

HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001	3"	L.P. PVC 2250ft.	5/6	P & P 1/2
J1002	3"	T.P. Poly 600ft.	10/6	P & P 1/2
J1003	5"	L.P. PVC 900ft.	10/-	P & P 1/8
J1004	5"	D.P. Poly 1200ft.	15/-	P & P 1/8
J1005	5 $\frac{1}{2}$ "	L.P. PVC 1200ft.	12/6	P & P 2/-
J1006	5 $\frac{1}{2}$ "	D.P. Poly 1800ft.	22/6	P & P 2/-
J1007	7"	S.P. PVC 1200ft.	12/6	P & P 2/6
J1008	7"	L.P. PVC 1800ft.	17/6	P & P 2/6
J1009	7"	D.P. Poly 2400ft.	25/-	P & P 2/6
J1010	7"	T.P. Poly 3600ft.	50/-	P & P 2/6
060 Cassette (Library cased)				8/6
090 Cassette (Library cased)				13/-
120 Cassette (Library cased)				18/-



DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug.
59/6 P. & P.

C1001 MULTI-TESTER



Overload protection, 20,000 opv. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-6 Meg ohm. Decibels -20 to +22dB. Size of meter 4 $\frac{1}{2}$ x 3 $\frac{1}{2}$ x 1 $\frac{1}{2}$. Complete with leather case **£5 - P. & P. 3/6**

NEW! STP.800 8-TRACK STEREO CARTRIDGE HOME PLAYER

TELETON STP. 800 8-TRACK STEREO CARTRIDGE HOME PLAYER
 A complete solid state unit ready to plug in and play. Hi Fi reproduction at 3 $\frac{1}{2}$ l.p.s. Player unit incorporates Volume, tone and balance controls and push button track selector. Size 14 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ ". Matched speakers size 11" x 8" x 3 $\frac{1}{2}$ " each.



LIND-AIR PRICE
49 GNS. Carr.

62D MULTI-TESTER

20,000 p.p.v. DC voltage 5-25-50-250-500-2.5 K (20,000 ohms per volt), AC voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance: 0-6k, 0-6 M Ω (300 ohm and 30K at centre scale). Capacitance: 10 to 1000 p.f., 0.01 uF to 1 uF. Decibels: -20 to +22dB. Size 4 $\frac{1}{2}$ x 3 $\frac{1}{2}$ x 1 $\frac{1}{2}$. **71/- P. & P.**




SOLDERING GUN



Comfortable grip with trigger control. "U" shaped 3 $\frac{1}{2}$ " bit to minimize wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use 230-250 volts. 85 watt element **49/6 P. & P. 3/6.**

S-DEC BREADBOARD

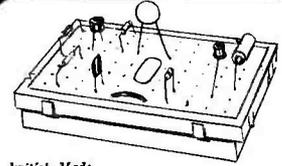

British Made
 Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-Dec with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-Dec" giving construction details for a variety of circuits. **29/6 P. & P. 2/6.**
 4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-Dec" all contained in a strong attractive plastic case. Ideal for the professional user. **£5.17.6 P. & P. 3/6.**
 T-DeC KIT **£5.17.6 P. & P. 3/6.**

NEW from Mullard! UNILEX Audio Modules

Now you can build your own stereo units exactly as you want them, and entirely in your own home. A good quality stereo amplifier can be built with no electrical knowledge. All solid state—Baxendale tone control circuit—no soldering—terminal block connections throughout. Everything you need to know about UNILEX SYSTEMS is in the Mullard book "Do it yourself stereo". Superb designs, detailed plans, simple instructions in non-technical language covering 4 systems in 4 price ranges. Send for your copy now 5/- Post Free.




- UNILEX AUDIO MODULES**
 Amplifier Module **£2.18.0** each EP9000
 Pre-Amplifier Module EP9001 **£3.2.0**
 Power Supply Module EP9002 **£4.12.0**
 Control Panel Assembly and Escutcheon Plate **£3.5.0**



BUILD A STEREO AMPLIFIER FOR ONLY £16.15.0 P. & P. 7/6

LIND-AIR LA.20

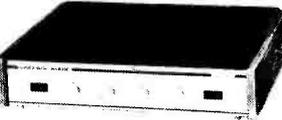

A fantastic stereo amplifier made exclusively for Lind-Air and represents considerable advance in solid state stereo amplifiers. Inputs for gram and radio tuner and provision for direct tape recording. Attractive and modern panel with bass, treble balance and volume controls also on/off and stereo/mono switch. Output 5W per channel music power. Frequency response 40-20,000Hz 8-16 ohm speaker matching. Size 16 $\frac{1}{2}$ " x 14" x 4".

LIND-AIR **22gns.** P. & P. PRICE 10/-

SINCLAIR IC-10 INTEGRATED CIRCUIT

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.
ONLY 59/6 P. & P. 1/6.
SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5 amp. **16/6 P. & P. 2/6.**

Garrard HI-FI TURNTABLES



- 2025 T/G with stereo cartridge **£8.19.6**
 3000 with Sonotone
 9TAHCD stereo cartridge **£10.19.6**
 SP25 Mk II **£10.19.6**
 SL65B **£15.19.6**
 Base and cover for above **£5.19.6**
 AP76 **£18.10.0**
 SL72B **£24.19.6**
 SL78 **£28.7.0**
 SL95B **£30.9.0**
 401 **£38.10.0**
 Base and cover for above **£8.19.6**
 P. & P. Decks 12/6. Base & Cover 10/-
 Deck/Case/Cover 17/6.
SPECIAL OFFERS
 SP25 MkII with base **£14.10.0 P. & P. 15/-.**
 SP25 Mk II with Sonotone 9TAHCD cartridge and base **£15.15.0 P. & P. 15/-.**
 Sonotone 9TAHCD cartridge **£2.15.0 P. & P. 1/6.**

18/19,25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.
 Telephone: 01-580 2255/4532/7679
 Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.


All Mail Orders and correspondence to Dept L5/10, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041

R+TV

RADIO & TV COMPONENTS (Acton) Ltd.
 21c High Street, Acton, London W.3.
 Also at 323 Edgware Road, London, W.2.
ALL ORDERS BY POST TO OUR ACTON BRANCH
 Terms C.W.O. All enquiries S.A.E.

Complete Stereo System £41

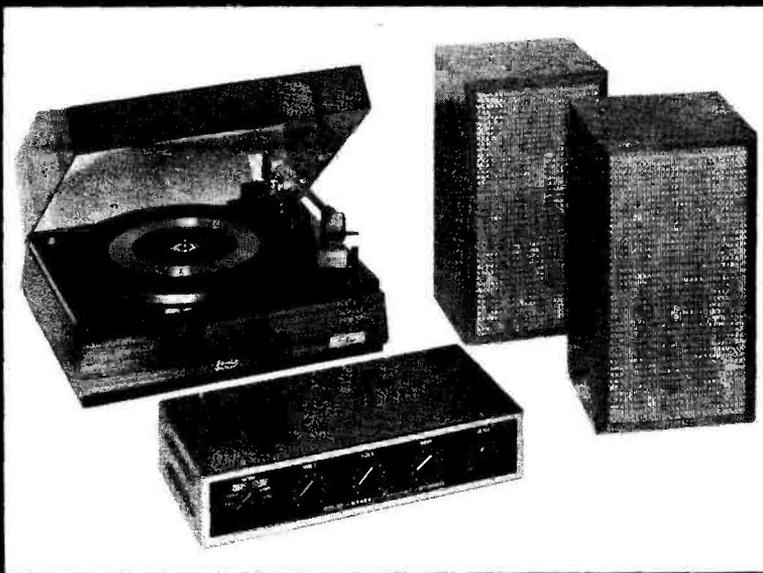WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 Mk II (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½ in x 10½ in x 6½ in, the Duo type 2 speakers are beautifully finished in teak veneer with matching vynair grills. They incorporate a 10½ in x 6½ in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at £6.6.0 each, plus 15/- p. & p.

Complete stereo system £41 plus £2.10. p. & p.

The Viscount F.E.T. Mk I £14.5 plus 7/6 p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Specification—Output per channel 10 watts r.m.s. Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½ in. 6 in. 2½ in. in teak-

finished case. **BUILT & TESTED.** MkII (MAG P.U.) £15.15 plus 10/- p. & p. Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1 kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).

The £29-10-0 Stereo system

The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION—R.M.S. power output 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY. Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.



TONE CONTROL Treble lift and cut Separate on off switch. A preset balance control.

Duetto integrated transistor stereo Amp. Garrard Changer from Cover and teak finish plinth Duo Type 1 speakers (see opp. page) The above items purchased together


£9.10.0 + 7/6 p&p.
 £7.10.0 + 7/6 p&p.
 £4.15.0 + 7/6 p&p.
 ea. £4. 4.0 + 7/6 p&p.
£29.10.0 + £1.10 p&p.

CAR TRANSISTOR IGNITION SYSTEM

by famous manufacturer

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers, etc.).

Price £4.19.6 plus 5/- P. & P.

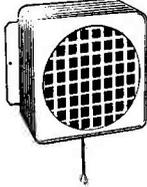


EXTRACTOR FAN

A.C. mains 230/250v. complete with pull switch. Size: 6 x 6 x 4in.

Price 27/6 plus 7/6 P. & P.

PYE CAR RADIO

Push Button Tuning Heart

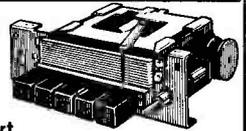

This PRESTOLOCK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6½" x 4" x 2". As illustrated but without knobs.

25/- plus 3/- P. & P.


THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION:—

Impedance 3, 8 or 10 ohms (please state requirement). It incorporates Goodmans high flux 6in x 4in speaker and 2½in speaker. Teak finish 12in x 6½in x 5½in. 4 guineas each. 7/6 p. & p.

50 WATT AMPLIFIER

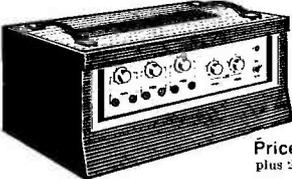

A.C. Mains 200-250V


Price £28.10 plus 20/- p. & p.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

TECHNICAL SPECIFICATIONS

3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. SENSITIVITIES AND INPUT IMPEDANCES. Channels 1 and 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 and 4 300mV at 1m. Suitable for most high output instruments (gram, tuner, organ, etc). Input

THE RELIANT

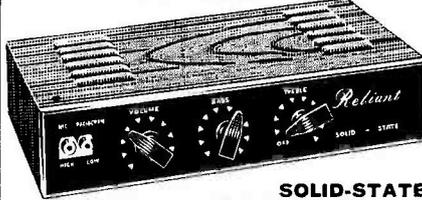

SOLID-STATE GENERAL PURPOSE AMPLIFIER

SPECIFICATIONS
Output—10 watts. Output impedance—3 to 4 ohms
Inputs—1. -xtal mic 10mV Tone Controls—Treble control range ±12dB at 10KHz.
±. -gram/radio 250mV. Bass control range ±13dB at 100Hz.
Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—230/250V. A.C. Size of chassis—10½ x 4½ in x 2½ in. For use with Stel. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram, and mike. Built and tested.


RELIANT Mk. I
As above less teak case
£6.10 plus 7/6 P. & P.

RELIANT Mk. II
In teak finished case
£7.5 plus 7/6 P. & P.

SENSITIVITY relative to 10w output. **TONE CONTROLS ARE COMMON TO ALL INPUTS.** Bass Boost +12dB at 60Hz. Bass Cut -13dB at 60Hz. Treble Boost +11dB at 15 KHz. Treble Cut -12dB at 15 KHz. With bass and treble controls central—3dB points are 30 Hz and 20 KHz. **POWER OUTPUT:** For speech and music 60 watts rms. 100 watts peak. For sustained music 40 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output to match into 8 or 15 ohms speaker system. **NEGATIVE FEEDBACK** 20dB at 1KHz. **SIGNAL TO NOISE RATIO** 60dB. **MAINS VOLTAGES** adjustable from 200-250V A.C. 50-60Hz. A protective fuse is located at the rear of the unit. Output-impedance 3, 8 and 15 ohms.

The ELEGANT SEVEN Mk. III (350m W Output)

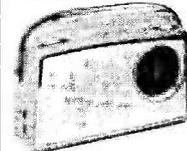7 transistor fully-tunable M.W.—L.W. superb, portable Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. **MAINS POWER PACK KIT: 9/6 extra.**
Price £5.5.0 plus 7/6 P. & P.
Circuit 2/6 FREE WITH PARTS



The DORSET (600m W Output)
Price £5.5.0 plus 7/6 P. & P.
Circuit 2/6 FREE WITH PARTS

7-transistor fully tunable M.W.—L.W. superb portable—with baby alarm facility. Set of parts. The latest modified and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in. **MAINS POWER PACK KIT: 9/6 extra**

QUALITY MAINS TRANSFORMER

Input 250 volts. **OUTPUT** (All RMS values) 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used. 1.25-0-25 volts 2.4A watts.

Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- plus 7/6 P. & P.



LIQUIDATED STOCK

DANSETTE

TOURISTE MK3 CAR RADIO

ALL TRANSISTOR


Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold complete for £15.4.6.

SET OF PARTS **£6.6.0**

Circuit diagram 2/6. Free with parts

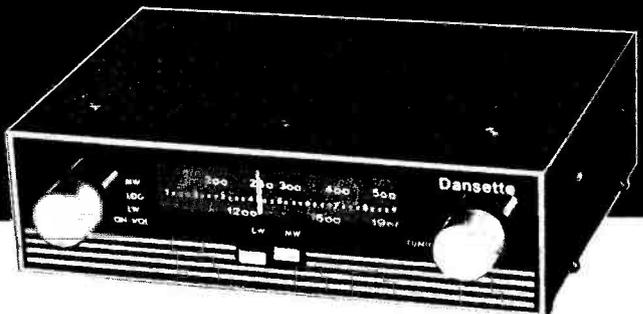Speaker, baffle and fixing kit 25/- extra plus 4/- P. & P. Postage free when ordered with parts.




Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

plus 7/6 P. & P.

See top of previous page for address

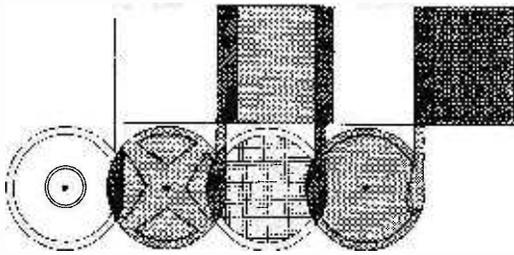RADIO & TV COMPONENTS
R+TV
(ACTON) LIMITED



16th

INTERNATIONAL

AUDIO FAIR

OCTOBER 20-24

Hear and compare the world's finest sound reproducing equipment for the home. The top loudspeakers, amplifiers, tape recorders, pick-ups, tapes, and accessories have been brought together under one roof to give you a superb Festival of Sound.

Famous manufacturers from all over the world will be demonstrating their products in specially constructed studios which will enable you to hear the Sound at its best.

Each day a programme of special live presentations and lectures will be held in the Hi-Fi Theatre . . . and there will be two cinemas continuously showing films of instruction and interest. Entrance to both theatre and cinemas is FREE.

Everyone who takes pleasure in using and listening to Hi-Fi equipment of the highest standard must visit this International Audio Fair.

ADMISSION 5/-

OLYMPIA

10am-9pm LONDON W14

BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:


VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

FAL

**AMPLIFIERS OF QUALITY
AND RELIABILITY**
at the right price


'PHASE 12'

An extremely attractive all silicon stereo amplifier ideal for unit audio use. Facilities include MAGNETIC and CERAMIC P.U. RADIO, TAPE etc. Output 6 watts per channel. Freq. Response 40-40,000 c.p.s.—3 dB. Hum level—74 dB. Controls include Input Selector, Volume, Balance, Bass, Treble and Stereo/Mono Switch. Black and silver facia panel with satin silver control knobs. Slimline finish enhanced by good quality Teak cabinet housing

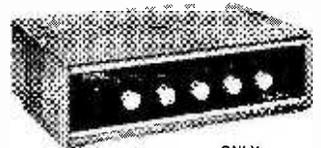

ONLY
24 Gns.

*Recommended
Retail Price*

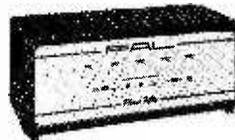

'PHASE 50' P.A. AMPLIFIER

A solid state A.C. mains unit for Vocal and Instrumental Groups and General Public Address use.

29 Gns.

*Recommended
Retail Price*

- ★ 50 watts output (Peak)
- ★ High sensitivity
- ★ 3-30 ohms matching
- ★ 3 separately controlled inputs
- ★ Freq. Response 22 c.p.s.—30 Kcs

For leaflets on the above and other models in the FAL range please send SAE to:—

FUTURISTIC AIDS LTD, 104 Henconner Lane, Leeds 13

When in LUTON, BEDS. you must visit the . . .

SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.

Closed all day Wednesday.

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, BEDS

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPECIFICATION • LARGE STOCKS

BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets

1N014	1/3	2N3706	3/3	40512	45/6	BC147	3/3	BFY51	4/3
1N3754	4/-	2N3707	4/-	40602	9/6	BC148	3/6	B8X20	3/9
1N4148	1/9	2N3708	3/-	AC107	14/6	BC149	3/6	BY164	10/-
1N5054	4/-	2N3709	3/-	AC128	6/6	BC153	10/-	BY238	3/6
1B940	1/-	2N3710	3/6	AC127	6/-	BC154	11/-	C108B1	14/6
2N686	9/6	2N3711	3/11	AC128	6/-	BC157	3/9	MC140	5/-
2N697	5/6	2N3731	24/-	AC176	11/-	BC158	3/6	MJ480	21/-
2N706	2/9	2N3704	3/3	ACY22	3/9	BC169	3/9	MJ481	27/-
2N1302	4/-	2N3819	8/6	ACY40	4/-	BC167	2/6	MJ491	30/-
2N1303	4/-	2N3820	25/6	ACY41	5/-	BC168	2/6	MPI102	7/6
2N1304	4/6	2N3904	7/6	AD142	14/8	BC169	2/3	NKT403	15/6
2N1305	4/6	2N3906	7/6	AD149	17/6	BC177	6/3	NKT406	15/-
2N1306	9/9	2N4058	5/8	AD181/AD182	4/-	BC178	5/8	OA47	1/9
2N1307	9/9	2N4059	4/-	(matched) 18/- pr		BC179	6/-	OA90	1/3
2N1308	2/9	2N4060	4/3	AF114	7/-	BC182L	4/3	OA91	1/3
2N1309	3/9	2N4061	4/3	AF115	7/-	BC183L	2/3	OA95	1/3
2N1613	6/-	2N4062	4/3	AF116	6/6	BC184L	2/6	OA99	3/3
2N1711	7/-	2N4294	3/3	AF117	6/6	BC186	8/6	OA300	1/11
2N2147	18/9	2N4286	3/3	AF124	7/6	BC212L	5/-	OA202	2/-
2N2218	9/3	2N4289	3/3	AF127	7/-	BC213L	5/-	OC71	5/6
2N2270	12/3	2N4291	3/3	AF139	9/9	BC214L	5/3	TIP31A	17/6
2N2484	13/6	2N4292	3/3	AF180	18/6	BCY70	5/6	TIP32A	23/9
2N2646	10/9	2N4410	9/9	AF239	9/9	BD121	18/-	TI943	10/6
2N2904	11/-	2N5062	12/3	ASY26	6/6	BD123	24/3	ZTX300	3/6
2N2924	4/-	2N5163	5/-	ASY27	8/6	BD124	18/-	ZTX301	3/6
2N2926	4/6	2N5192	25/-	ASY28	6/6	BF167	3/3	ZTX302	4/6
2N2926	2/3	2N5195	28/3	B6041	9/9	BF178	10/6	ZTX303	4/6
2N3052	4/3	2N5457	9/9	BA102	9/9	BF180	12/-	ZTX304	4/6
2N3054	14/3	2N5458	9/9	BA156	4/6	BF194	7/6	ZTX500	5/-
2N3055	16/-	2N5469	9/9	BA130	4/8	BF195	7/-	ZTX501	5/-
2N3225	10/9	40250	14/3	BA145	5/6	BFX29	10/9	ZTX502	6/-
2N3663	11/6	40361	12/6	BC107	2/9	BFX34	7/6	ZTX503	5/-
2N3702	3/6	40362	16/-	BC108	2/3	BFX35	3/3	ZTX504	5/-
2N3703	3/3	40406	16/3	BC109	2/9	BFX37	6/6	ZTX530	5/5
2N3704	3/9	40408	14/6	BC125	12/6	BFX88	8/9	ZTX531	6/9
2N3706	3/5	40430	37/-	BC126	12/-	BFY50	4/6		

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	18	16	15
C	1/8W	5%	4.7 Ω-330K Ω	E24	2-5	2	1-75
C	1/4W	10%	4.7 Ω-10M Ω	E12	2-5	2	1-75
C	1/2W	5%	4.7 Ω-10M Ω	E24	3	2-5	3-25
C	1W	10%	4.7 Ω-10M Ω	E12	6	5	4-5
MO	1/2W	2%	10 Ω-1M Ω	E24	9	8	7
WW	1W	10% ± 1/20 Ω	0-22 Ω-3-9 Ω	E12		15d all quantities	
WW	3W	5%	12 Ω-10K Ω	E12		15d all quantities	
WW	7W	5%	12 Ω-10K Ω	E12		15d all quantities	

Codes: C = carbon film high stability low noise
MO = metal oxide ElectroSil TR5 ultra low noise
WW = wire wound Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 50/6 nett.

PLESSEY SL408A Now only 42/8 nett 3W into 7.5Ω for 18V supply. Application data sent with two more.

WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 4/9 each
SLIDER SWITCHES D.P.D.T. 3/- each

NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only 3/9
Round chrome bezel red, amber, clear 4/9 each

Toggle switches, 250V a.c. 1.5A. chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/6; D.P.D.T. 5/9; S.P.D.T. centre off 5/-.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/- Compact T-DeC's increased capacity, may be temperature-cycled. T-DeC only 50/- post free. Full range stocked.

MULLARD polyester C280 series

250V 20%: 0.01; 0.022; 0.033; 0.047 8d ea. 0.068; 0.1 9d ea. 0.15 11d., 0.22 11/-, 10%; 0.33 1/5, 0.47 1/8, 0.68 2/3, 1.1 2/9, 1.5 1/2 4/2, 2.2 1/2 4/9.

MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 1/3 each
Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.3/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 10/25; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/8; 4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/25; 50/64; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/8; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 260/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25 5/5; 1000/50 8/2; 1000/100 16/3; 2000/25 7/4; 2000/50 11/4; 2000/50 11/4; 2000/100 22/8; 2500/64 15/5; 2500/70 19/6; 5000/25 12/6; 5000/50 21/11; 5000/100 53/3; 10000/15 17/-; 10000/25 24/8; 10000/50 44/-; 10000/70 61/-.

MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 1000/100 16/3; 250/50 3/8; 500/25 3/8; 500/50 4/6; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

SMALL ELECTROLYTICS

Axial leads: 4.7/10; 4.7/25; 8/50 1/- ea. 10/10; 10/25; 10/50; 33/10; 50/10 1/- ea. 22/25; 25/50; 47/25; 100/10; 220/10 1/3 ea.

THE NEW 1970 ELECTROVALUE CATALOGUE

48 pages—thousands of items—packed with information 2/- post free. Add 4/- if sent overseas by air mail.

PEAK SOUND PRODUCTS

ENGLEFIELD CABINET KITS

Build it 12 + 12 or 25 + 25



Stereo amplifier in modular kit form 12 watts per channel 258/9/-, 25 watts 288/15/- Cabinet kit only 26. These prices nett.
As recently reviewed in Hi Fi Sound.

BAXANDALL SPEAKER SYSTEM

Designed by Peter Paxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 16 Ω 58RM109 speaker Unit. Kit 218/12/- nett; built 218/8/- nett.

STEREO AMPLIFIER S.A. 10-10.

Developed from the very successful SA.8 amplifier giving first class stereo amplification featuring separate volume controls for each channel, bass and treble controls. 10 watts per channel into 8 Ω. Kit 219/7/6 nett; built 224/16/8 nett. Suitable 8 Ω wide range speakers with woofer, tweeter & c-over in cabinet available 218/15/- nett.

MAINLINE AMPLIFIER KITS

RCA/6188 designed main amplifier kits. Input sensitivity 500-700mV for full output into 8 Ω.
Power Kit price including components Suitable unreg. power supply
12W 168/- nett 92/-
15W 190/- nett N/A
40W 210/- nett 118/1
70W 252/- nett 138/10

30 WATT BAILEY AMP. PARTS

Special summer reduction (to Sept. 30th 1970 only)
Sensitivity 1.2V for full output into 8 Ω
Transistors for one channel 27/5/8 list, 26 only nett.
Transistors for two channels 214/11/- list 211 only nett.
Capacitors and resistors (metal oxide) 30/- per channel nett.
Complete unregulated power supply kit 87/6 nett

ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 4/6 each
1W: 6.8V to 82V 9/- each 1.5W: 4.7V to 75V 12/- each
Clip to increase 1.5W rating to 3 watts (type 268F) 9d.

CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.
Single gang linear 220 Ω to 2.2M Ω 2/6
Single gang log 4.7K Ω to 2.2M Ω 2/6
Dual gang linear 4.7K Ω to 2.2M Ω 8/6
Dual gang log 4.7K Ω to 2.2M Ω 8/6
Log/antilog 10K, 47K, 1M Ω only 8/6
Any type with 1/4 D.P. mains switch, extra 2/3
Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K, 4K, 7K, 10K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω vertical or horizontal mounting 1/- each.

COMPONENT DISCOUNTS

10% on orders for components for 25 or more. 15% on orders for components for 125 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over 22. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

ELECTROVALUE


(Dept. PW.10) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9-5.30: Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3) Telex 264475



Sign here..!

for your
miniature
soldering
iron.

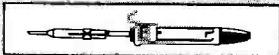CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 34/-**



G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts 36/-



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8" 3/16" available. For 240, 220, 110 volts, 36/-




ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 15 volts, 36/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. 47/6. Spare bits and elements for all models and voltages immediately available from stock.

Complete precision soldering kit

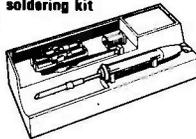

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits 1/8", 3/16", 1/4"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **55/-**



Model CN 240/2
15 watts - 240 volts
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **34/-**



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 67377/8.
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| | | | | |
| | | | | |

I enclose cheque/P.O./cash value

NAME

ADDRESS

PW10

PRACTICAL WIRELESS

VOL 46 NO 6

Issue 764

OCTOBER 1970

TOPIC OF THE MONTH

Women, arise!

WHAT with the establishment of the principles of equal pay and equal rights for women, the unisex concept and other such manifestations of emancipation, perhaps it is about time we did something about this parity of the genders in this hobby of ours.

For long years, women have been favoured by management to perform those delicate tasks in assembly and inspection etc., so admirably suited to their special temperament and this is increasingly evident in the radio and electronics industries. But after leaving the factory or laboratory they seem to lose interest. They want to wash their hair, go to the pictures or watch the telly, when what they *really* ought to be doing is getting to grips with F. G. Rayer's latest creation in Practical Wireless!

With their gentle touch and infinite patience, the wiring up of the modern generation of miniature components ought to trouble them not the slightest. And think of the fruitful field for gossip that can be extracted from the tales of constructional triumphs "she said Radio Australia came booming out the first time she switched on. She hadn't even got the dial on straight. And the colour scheme of the cabinet!"

We admit that many ladies are involved in amateur radio but most of them take a fairly passive (or resigned!) part in the proceedings, eyeing with varying degrees of distaste the activities of their eccentric menfolk. Before the last war there were just *two* licensed lady radio amateurs among the ranks of several thousand in this country. The Services, however, took advantage of their usefulness as wireless operators and mechanics and this was the launching pad for many who decided to take up radio as a hobby—and as a hobby, for most of them seem to have been snapped up by male radio enthusiasts who realised they were on to a good thing!

Today the number of licensed ladies is well over 50 strong and still growing. But we could do with more support on the constructional side. We ought to persuade our betters to join us and let them share our pleasures (and agonies). Apart from brightening things up and allowing us more time with the hobby, we'd have another pair of hands to do some of the donkey work. But that is quite beside the point!

W. N. STEVENS—*Editor*.

**NOVEMBER ISSUE WILL BE PUBLISHED
ON OCTOBER 9**

NEWS AND COMMENT

Leader	427
News . . . News . . . News . . .	428
On the Short Waves by <i>Malcolm Connah and David Gibson, G3JDG</i>	445
MW Column by <i>Charles Molloy</i>	447
Practically Wireless by <i>Henry</i>	473

CONSTRUCTIONAL

Transistor & Diode Tester by <i>J. Thornton Lawrence, GW3JGA</i>	430
Mini Organ by <i>P. M. Delaney</i>	434
Electronic Digital Combination Lock by <i>John Stuart</i>	438
I.C. of the Month, Motorola MFC 4010P/Mullard TAA263 Utility Amplifier by <i>L. A. J. Ireland</i>	450
Transistor V.F.O. by <i>P. Cairns, G3/SP</i>	452
Organ Pedal Bass Unit, Part 2 by <i>A. Lester-Rands</i>	455
Vibrasonic 25-50 Guitar Amplifier, Part 2 by <i>F. C. Judd, G2BCX</i>	462
Notes on the General Coverage Receiver by <i>F. G. Rayer, G3OGR</i>	474
Take 20, Add-on Tone Control by <i>Julian Anderson</i>	478

OTHER FEATURES

Audio Fair Competition	447
Going Back by <i>Colin Riches and Arthur Dow</i>	448

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

NEWS... NEWS... NEWS...


Bench vice for the radio shack

The Lockjaw is a bench vice announced by the Vice & Workholding Co. Ltd. The jaws give a remarkable capacity to grip difficult shapes and delicate objects. With its suction clamp and 'G' clamp, the Lockjaw is a very portable device. It can also be bolted down to a bench, and makes a very useful addition to the wireless 'shack'.

Grooves in the jaws enable a positive hold to be obtained when gripping washers, rods, printed circuits and components. Jaw-grips are available with a rubber face for delicate work or silicon metal for harder usage. The silicon metal ones are supplied as standard. One jaw provides a rocking motion so that the face adjusts to work which tapers. If this jawgrip is turned round it is locked into a straight position.

The vice weighs under 4lb and the body is constructed of fine grain silicon alloy metal. It is claimed to hold as strongly as a typical cast-iron type eight times heavier. Jaw width is 4in. and overall length closed 8in.

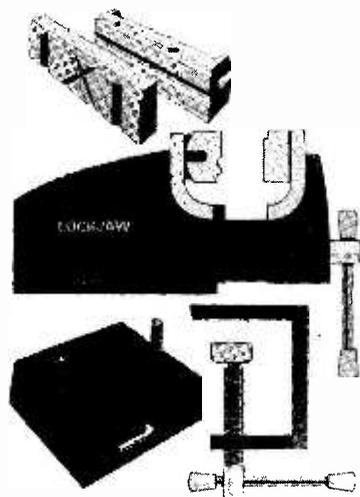Price of the Lockjaw including silicon metal jaws is 86s. The 'G' clamp base is 30s and the rubber-faced jaws for delicate work 14s a pair. Manufacturers are: *Vice and Workholding Co. Ltd., 149a Crayford Road, Crayford, Kent.*



Mobile Conference

One of the first large scale conferences on the subject of mobile radio was held at Brunel University from June 30 to July 2. Organised by the Society of Electronic and Radio Technicians, it comprised eleven contributions from both industry and users. In his concluding address, Mr. J. W. Grandey (Gresham Lion) Chairman of the Conference Organising Committee, said that during his discussions with delegates he had been struck by the interest aroused by the contributions. He felt safe in saying that this Conference had been highly successful from every point of view; not least in bringing together over 120 representatives of all branches of this increasingly important field of electronics. The manufacturing industry was well represented as were the Home Office, Electricity and Gas Boards, Police and British Rail.

Most of the material presented at this Conference was new and had not previously received a public hearing. Many of the delegates were unaware of the work being carried out by various organisations, such as the Home Office, in looking to the future of mobile radio. Mr. E. W. Crompton proposed the adoption of a new system of modulation, double side band suppressed carrier, which appeared to provide two advantages, higher range and narrower bandwidth. Some of the recent work carried out by industry in providing new or better applications of mobile radio were also described. Mr. Welsh and Mr. Carey of Cossor proposed a system of vehicle location using phase measurement which had not previously been publicly described and Mr. N. C. Croft of Storno presented a paper on Automatic Extension Ringing from Vehicles.

One of the pressing problems in this rapidly expanding field is frequency availability. This kept cropping up in discussion and was dealt with at length by Mr. D. B. Balchin of the Ministry of Posts and Telecommunications.

Gravesend. . .

The above Club has now moved from King's Farm Community Centre, Gravesend, to new premises at the Northfleet Recreation Centre, Springhead Road, Northfleet, Kent, and meetings are held on Thursdays from 7.30 p.m. to 10.30 p.m.

They have taken larger premises as they are anxious to extend their membership and any person interested in Radio will be most welcome; there is no age limit.

Anyone interested in joining, should contact Allen J. Moules, after 7 p.m. weekdays at home—tel. no. Gravesend 2965.

I.S.W.C.

The International Short Wave Club will be pleased to send readers a copy of their bulletin International Short Wave Radio, if they would care to make application to them enclosing return postage. The address is: *Mr. Arthur E. Bear, 100 Adams Gardens Estate, London, S.E.16.*


Audio 70

The date of the New Northern International High Fidelity Festival, at the Cairn Hotel, Harrogate, is September 18th-20th. Many well-known companies will be exhibiting.

TRANSISTOR & DIODE TESTER

J THORNTON LAWRENCE

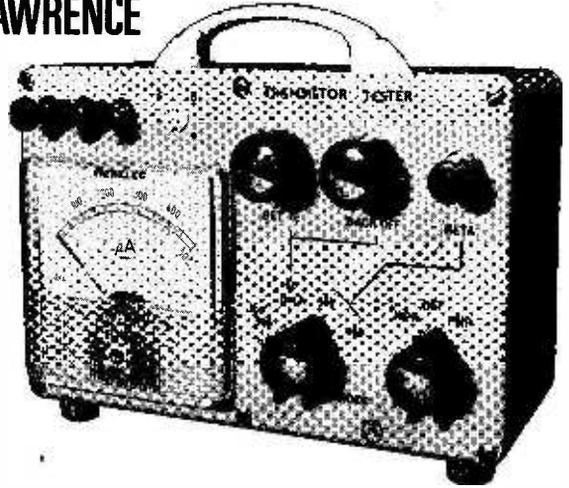
THIS TRANSISTOR AND DIODE TESTER IS THE FIRST OF A SERIES OF ARTICLES DESCRIBING A NEW LINE OF TEST EQUIPMENT. THE VARIOUS INSTRUMENTS, ALL IN MATCHING CASES, WILL PROVE WORTHY ADDITIONS TO ANY WORKSHOP.



THE Transistor and Diode Tester to be described will rapidly check transistor leakage current and measure current gain (beta), over a range of collector currents, up to 5mA, for both n.p.n. and p.n.p. transistors. It is also suitable for checking semiconductor diode forward conduction and reverse leakage current. The tester is simple to build and contains only passive components.


Circuit

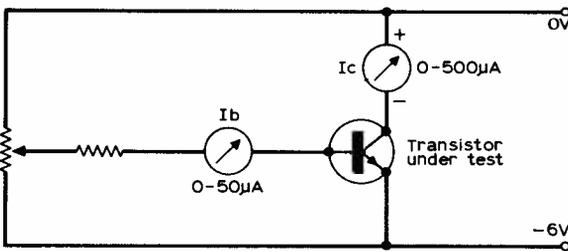The d.c. beta, or h_{FE} , of a transistor is the ratio of the collector current to the base current, $\text{beta} = \frac{I_c}{I_b}$. A simple set-up for measuring beta is shown in Fig. 1. The base bias is adjusted to give a convenient value of I_c and the base current I_b is read off and the calculation made.



▲ Fig. 1.


Fig. 2. ▼

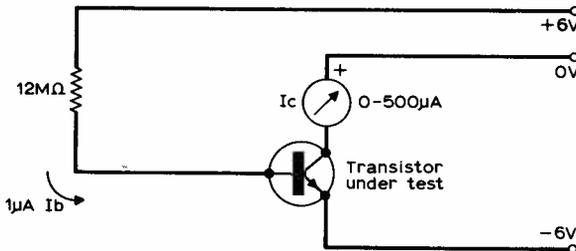

To avoid the necessity of reading I_b from a meter, the base could be fed with a known value of current, say $1\mu\text{A}$, from a known fixed supply voltage through a known value resistor, as shown in Fig. 2. The I_c , in μA , would then be a measure of the beta, e.g. $60\mu\text{A}$ I_c would indicate a beta of 60.


It is often useful to measure beta at different values of I_c , and a basic circuit for doing this is shown in Fig. 3.

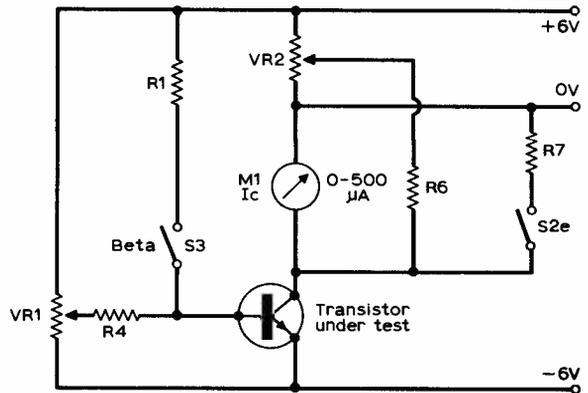In this circuit, R_7 is a 5mA shunt for the $500\mu\text{A}$ meter and with S_{2e} closed, the meter reads 5mA full scale deflection. If, for example, it is desired



▲ Fig. 3.

Fig. 4. ▼

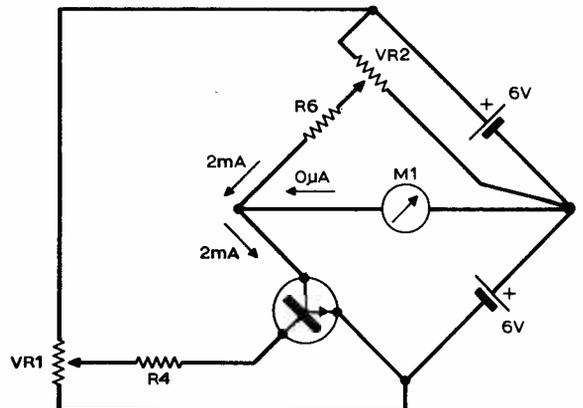

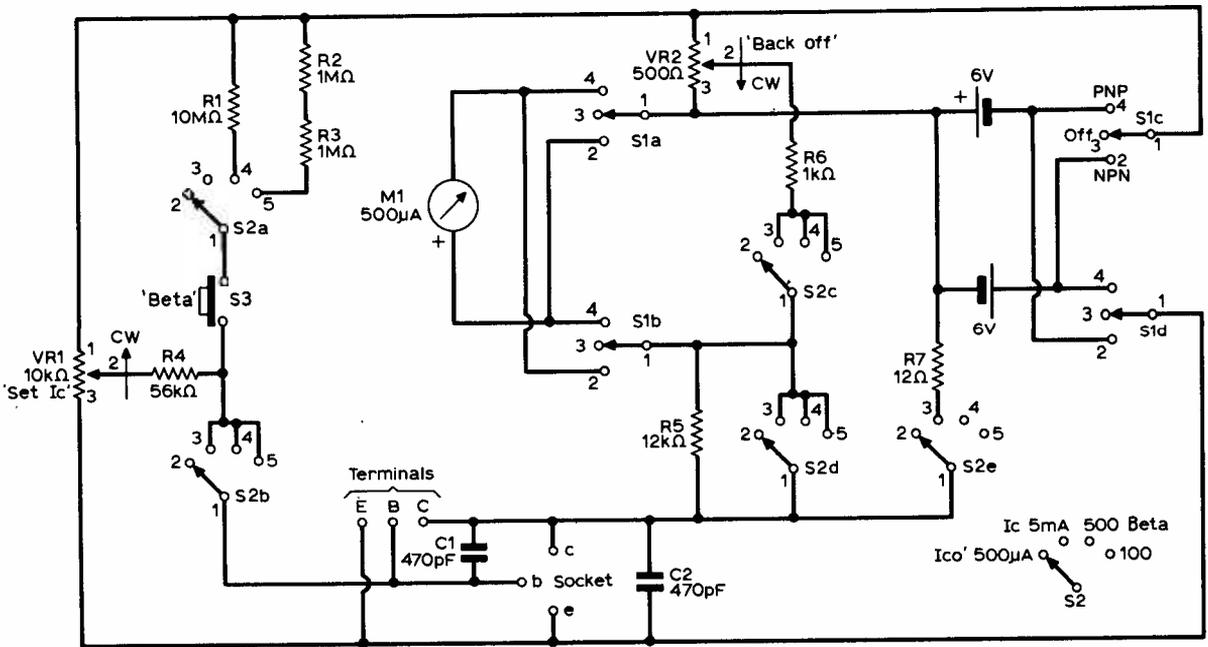


Fig. 5 : Complete circuit of the transistor and diode tester.

to test the transistor at 2mA I_c , VR1 is adjusted to provide sufficient I_b to give an I_c of 2mA, as indicated by M1 (accepting that VR2 and R6 have negligible effect on the accuracy of M1).

The current through M1 is then 'backed-off' by an equal and opposite current, provided by VR2 and R6, until M1 indicates zero. This action may be more easily seen if the circuit is redrawn in the form of a Wheatstone bridge as shown in Fig. 4.

With zero reading on M1, S2e is now opened,

thus disconnecting the 5mA shunt and returning M1 to 500 μ A f.s.d.

To read beta, S3 is closed and the known current, I_b , provided by R1, causes an increase in I_c which is indicated by M1. As previously mentioned, the value of I_b is chosen so that M1 gives a direct reading of beta.

The backing-off current feed resistor R6, has a slight shunting effect on M1, making the meter read about 550 μ A f.s.d. The value of R1 is therefore chosen accordingly and the facility of reading beta directly is retained.

The method of testing applies equally to p.n.p. and n.p.n transistors, although provision must be made to reverse the polarity of the supplies, and of course the connections to M1.

The complete circuit of the transistor tester is shown in Fig. 5, and here S1 is the 'PNP-NPN' switch which also has a centre 'off' position.

The function switch, S2, switches the meter shunt, R7, the backing-off feed R6, and allows for two ranges of beta 0-500 and 0-100 to be provided by switching two values of I_b through R1 and R2+R3 to the base of the transistor.

Diodes may be checked by connecting between the emitter and collector terminals, when forward and reverse current is indicated. The forward current is limited to 500 μ A by R5.

Construction

The transistor tester is built in a 7 $\frac{1}{4}$ x 4 $\frac{1}{2}$ x 3in. deep Eddystone die-cast box, type 6357P. The lid of the box forms the front panel and the drillings for this are shown in Fig. 6.

The meter M1, is a Henrys 'Henelec' MRA-65A 500 μ A moving coil instrument. It should be noted that this meter is a later type to the 65 series illustrated in Henry's catalogue and has slightly different drilling requirements.

★ components list

Resistors :

R1 10M Ω	R5 12k Ω
R2 1M Ω	R6 1k Ω
R3 1M Ω	R7 12 Ω
R4 56k Ω	

All $\frac{1}{2}$ W 5% carbon

VR1 10k Ω potentiometer, wire-wound

VR2 500 Ω potentiometer, wire-wound

Capacitors :

C1/2 470pF disc ceramic

Switches :

S1 2 wafers, each 3 pole 4 way, on Maka-Switch shafting unit (Henry's Radio)

S2 1 wafer, 4 pole 3 way, on Maka-Switch shafting unit (Henry's Radio)

S3 Push button (Micro Omron VAQ-40-45 (Henry's Radio))

Miscellaneous :


M1, Meter, 500 μ A f.s.d. (Henelec MRA-65B Henry's Radio)

Die-cast box (Eddystone 6357P, Home Radio)

Knobs (2-PK, 2-WK, Radiospares)


Terminals (3-Paignton PK 12K Home Radio)

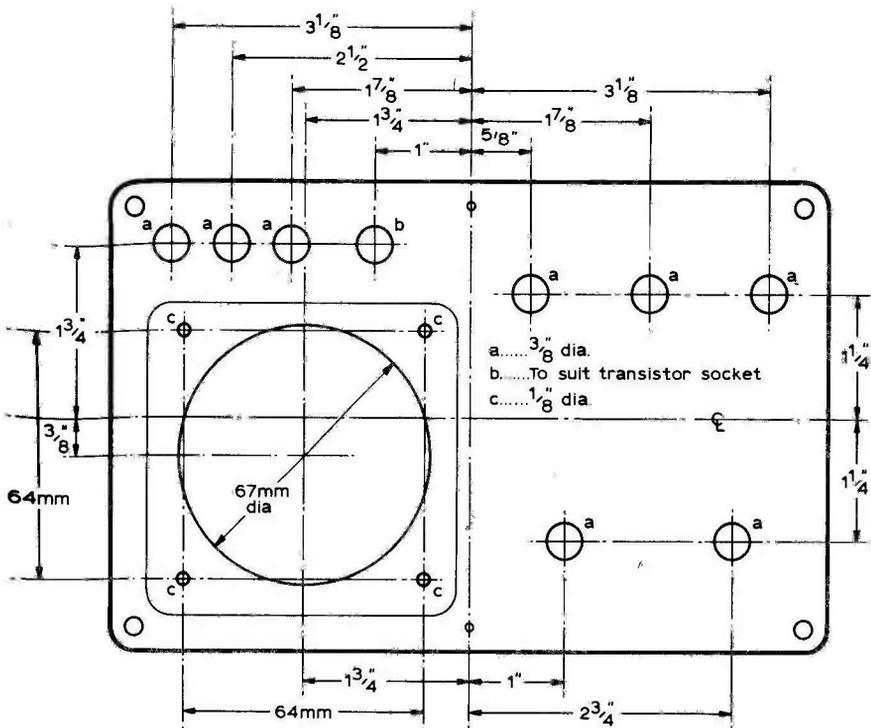Transistor socket. Handle. Plastic feet. Battery connectors



▲ Fig. 6: Drilling details of front panel.

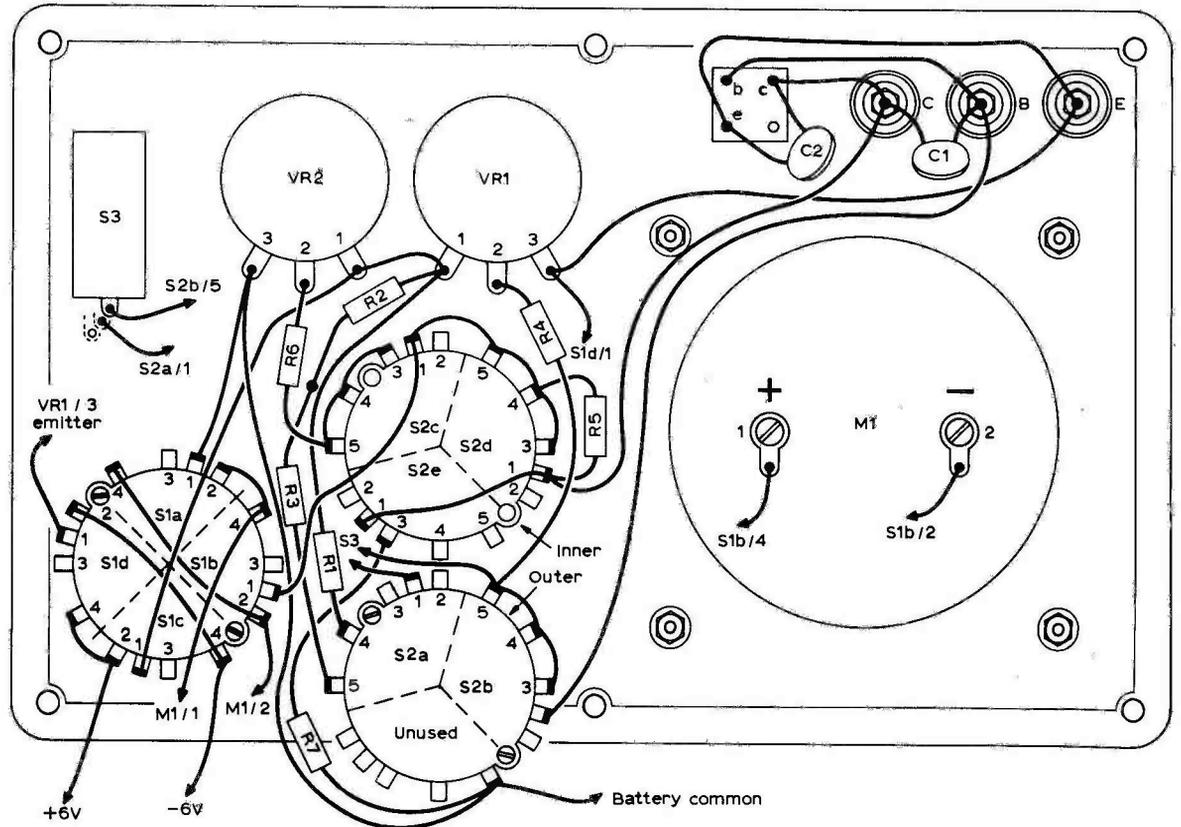▼ Fig. 7: Wiring diagram of tester. The wafers of switch S2 have been separated for clarity.



The switches are Radiospares Maka-Switch types and it is important for these to be assembled with the markings on the switch wafer facing the switch mechanism. No spacers are used between the wafers but a 6BA washer is fitted between the front wafer and the switch mechanism. The connections to the switch wafers are shown in Fig. 7.

The tester is powered by two PP1 batteries and these fit into the die-cast box as shown in Fig. 8. A strip of polythene or similar material is required between the batteries to prevent an accidental short circuit between the battery connectors. Two 470pF disc ceramic capacitors, C1 and C2, are connected across the transistor socket and terminals to prevent parasitic oscillation of the transistor under test.

To give a good external appearance, the box is sprayed with one of the popular car enamel aerosols and lettered with Letraset lettering, sheet 209.

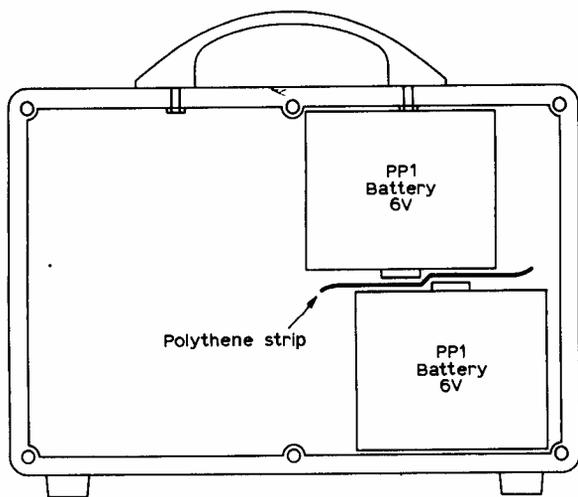



Fig. 8 : Positioning of the two batteries inside the case.

Operation

1. Before connecting the transistor or diode, check the settings of the controls,

Set Ic	fully anti-clockwise
Back off	fully clockwise
Function Switch	to 'Ico'
Polarity Switch	to 'OFF'

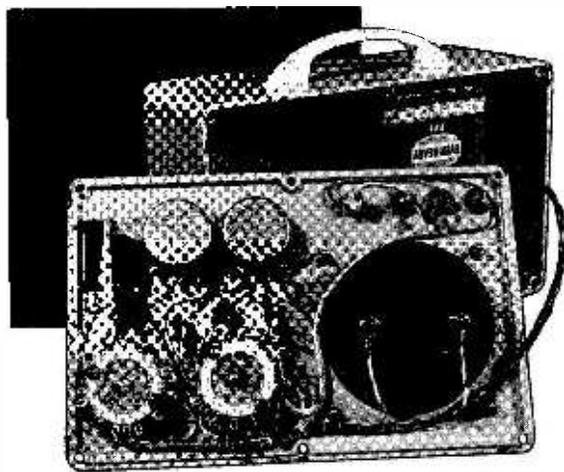2. Connect the transistor to the terminals or socket and switch to 'PNP' or 'NPN' as appropriate. The meter now reads 0-500 μ A of collector leakage current with the base open circuit ('Ico'), at a collector voltage of 6 volts. If the meter reads full scale, the transistor is probably faulty and no further tests should be made. (Some very large germanium power transistors may have leakage currents of this order and may not necessarily be faulty. These are outside the capabilities of this tester.)
3. Set the function switch to 'Ic.'



Completed tester. Compare with the wiring diagram, Fig. 7.

4. Set the 'Set Ic' control for a suitable value of Ic. The meter reads 5mA f.s.d. For small a.f. and r.f. types 1-2mA is suitable, higher currents may be used for higher power types.
5. Adjust the back-off control for zero reading of Ic.
6. Set the function switch to 'Beta 500' or '100' and if necessary re-zero the meter with the back-off control.
7. Press the Beta button for a direct reading of beta.
8. Photo-transistors may be checked as normal transistors providing that they are not exposed to light. The sensitivity to light may be checked by setting the tester to Step 3 and alternately exposing and shielding the photo-transistor to and from light. The 'Set Ic' control should be set to minimum (anti-clockwise).
9. In the testing of semiconductor diodes, the cathode should be connected to terminal C and the anode to terminal E.
10. Set the function switch to Diode.
11. Set the polarity switch to 'FOR' for the forward conduction test. The forward current is limited to 500 μ A.
12. Set the polarity switch to 'REV' for the reverse leakage test. The reverse current, 0-500 μ A, is measured at 6 volts.
13. Switch OFF before returning the controls to the positions given in Step 1.

Identification

A simple method of identifying p.n.p. or n.p.n. transistors is to insert the unknown type in the socket and temporarily short circuit the E and B terminals with a piece of wire. With the function switch at 'Ico', turn the polarity switch to 'PNP' and then 'NPN,' the position which produces little or no current reading indicates the transistor type. The short circuit may then be removed and testing carried out in the usual way. ■

P.W. BINDERS

Preserve your copies of Practical Wireless. Don't let them become torn and dirty—buy a hard-cover binder for 15s. 0d. from:


**Binding Department,
IPC Magazines Limited,
Tower House,
Southampton Street,
London, W.C.2.**

Price includes post and packing.

**COME AND VISIT US AT THE
1970
INTERNATIONAL AUDIO
FESTIVAL & FAIR
OLYMPIA, LONDON W.14**

OCTOBER 20th—24th (10 a.m.—9 p.m. each day)

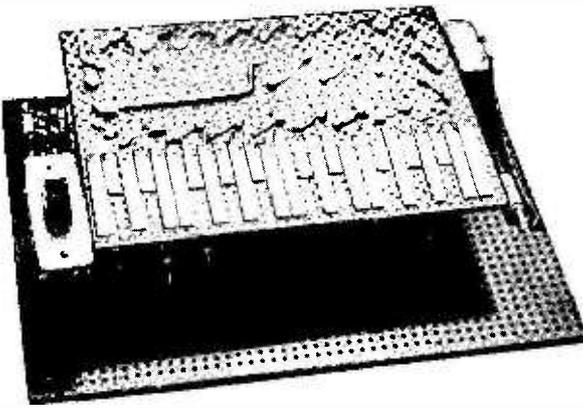The PRACTICAL WIRELESS stand will feature many constructional items.



signal is switched in by S1. The variable resistors VR1-VR25 are used to obtain the different notes.

If a simpler organ is required (without a tremolo), then R1-R7, C1-C4, Tr1 and S1 can be omitted. Similarly a one octave instrument can be built requiring only 13 variable resistors.

Construction

The organ is built on two pieces of Veroboard—one with copper strips and one without. Before assembling any parts, the holes 'Y' should be drilled to clear 8BA. Beginning with the plain board, a

P. M. DELANEY

mini organ

THE small organ to be described in this article can be built in an evening. If it is built as described, then it will give two octaves, one above and one below 'Middle C'. Full constructional details are given, so that even a relative newcomer to electronics should find no difficulty in building this organ.

Circuit

The organ consists of three sections, the circuit diagram being given in Fig. 1. Tr2 and Tr3 together form an astable multivibrator, tuned by VR1-VR25, R9, C5 and C6. It is sometimes difficult to make a transistorised multivibrator begin to oscillate. However, by the omission of the emitter bias resistor to Tr2, the necessary imbalance is produced.

The output transistor, Tr4, uses a transformer T1 for its load to match the speaker. A tremolo is provided by the low frequency oscillator Tr1, and this

keyboard can be made. Using $\frac{1}{8}$ th inch 'Cir-kit' strip, a series of copper strips are laid out as shown in Fig. 2. Note that the corners of strips 2 and 24 are cut off slightly.

Next the variable resistors are fitted around the edge of the board, and VR23-25 are placed in the centre. To ease the task of tuning, these are angled back, so that the tags come through the holes indicated. Wires are now connected along the top as shown, and underneath from the wipers to the copper strips.

The wiper of VR1 goes by the wire numbered 1 to the note 1, etc. The notes 18 and 19 are connected on the top of the board. All the wires should be kept short and as close to the board as possible. A length of wire (about $1\frac{1}{2}$ inches) is attached to the point Z.

The main part of the circuit can then be assembled. Firstly, the copper strips should be broken as indicated in Fig. 4. On the plain side of this board (Fig. 3), the connecting wires to the speaker, switch

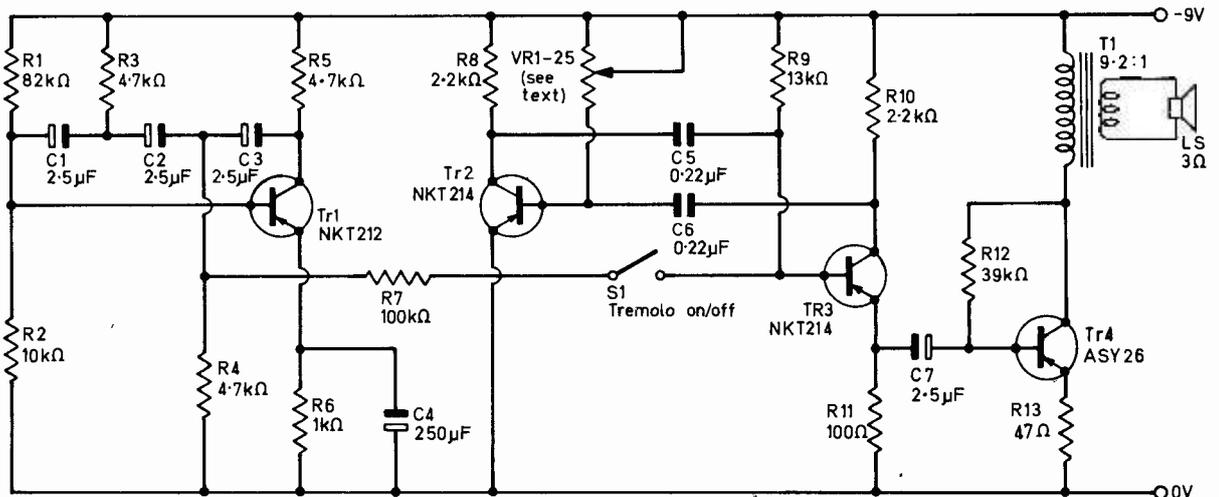


Fig. 1: Circuit of the mini organ. Tr1 provides the tremolo effect, Tr2-3 form the multi-vibrator oscillator and Tr4 the audio amplifier.

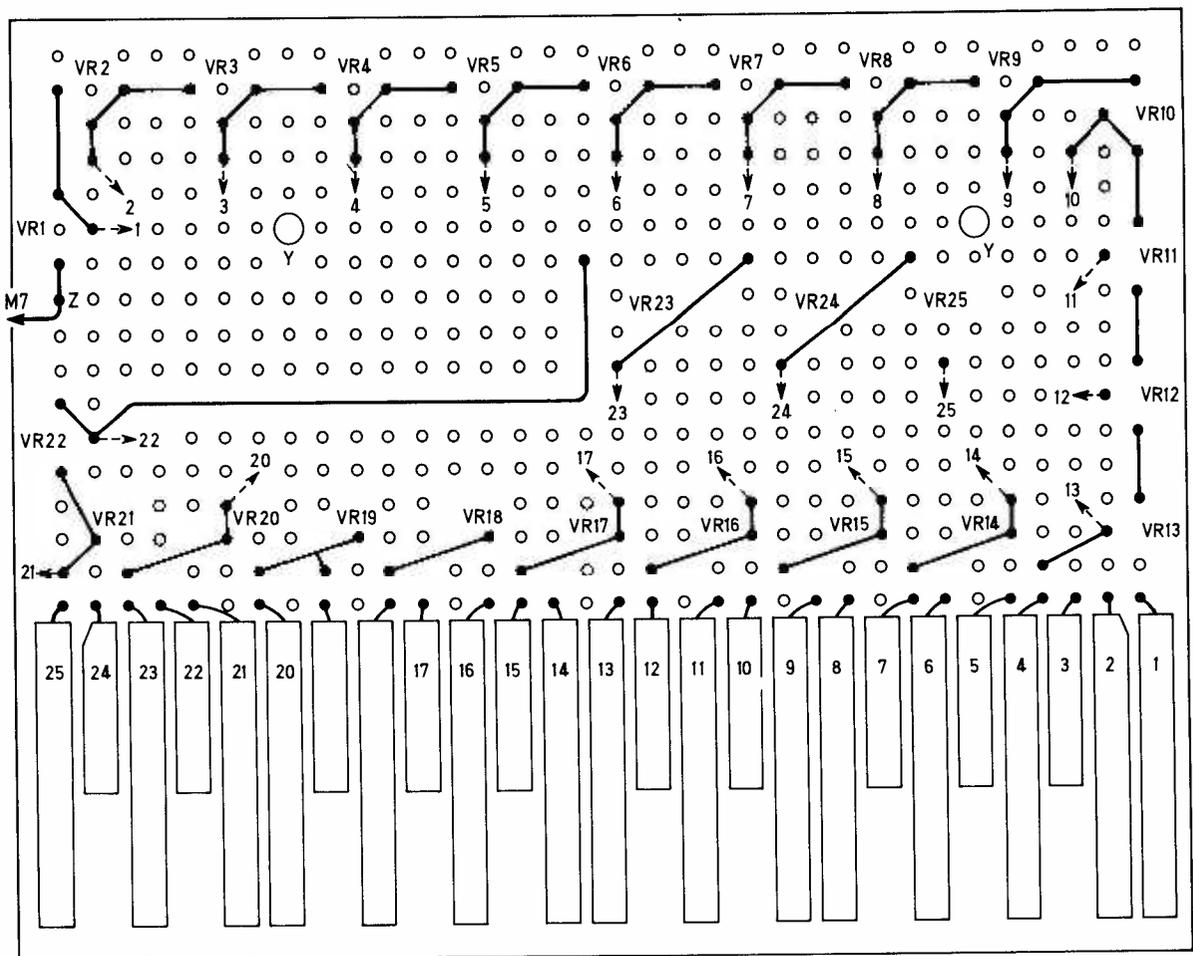


Fig. 2: Layout of the 'keyboard'. Compare with heading photograph.

and battery should be connected, and the wire from the point Z added.

The resistors should be added next, followed by the capacitors (except C4). The switch and the output transformer can then be fixed in place, along with the shorting links. If the transformer specified is used, then the fixing tags should be removed, and the transformer glued to the board, using Araldite (or a similar adhesive).

The four pins to the windings will fit directly onto Veroboard of 0.1 inch matrix—the secondary winding being nearest the edge of the board. Next the transistors can be soldered in. The base diagrams are given in Fig. 5. It is important to get the wires the right way round, and to use a heat shunt between the soldering iron and the transistor can. A pair of pliers held firmly on the wire being soldered will make an excellent heat shunt.

If C4 is not provided with an insulating sleeve



Close-up of some of the pre-set potentiometers which enable the organ to be tuned

around it, then one must be put on the emitter lead of Tr2, which passes underneath. C4 can then be fixed in place. The capacitors C5, C6, and Tr1, Tr2 and Tr3 should be laid against the board.

The stylus can be easily made from an old ball-point pen. The ball tip is removed, and the end soldered over—this removes the possibility of any ink coming onto the keys (see Fig. 6). The cut down body (about 4 inches) has a slot cut in one side at the end, and a wire passed through here, and soldered to the back of the metal part of the pen. This is then glued back in the plastic body, the wire pulled out through the slot, and the end cap replaced.


About a foot of wire is then left from the end cap to the point A49 on the Veroboard, to which the free end is fixed. The speaker is connected to the wires provided for it, and the battery leads connected to a suitable battery connector.

Tuning

Each note is sounded by touching the stylus tip against the corresponding copper strip. The prototype was tuned using the services of a musician and a tuning fork. From the A of the fork, the top C was tuned (using VR1), then the notes 2, 3 and 4 tuned to be of equal intervals in pitch, until note 4 ('A') corresponds exactly to the tuning fork.

The rest of the tuning is completed in a similar

Fig. 3: Lower circuit board which forms the base of the organ. This board may be deeper, as shown in the photographs.

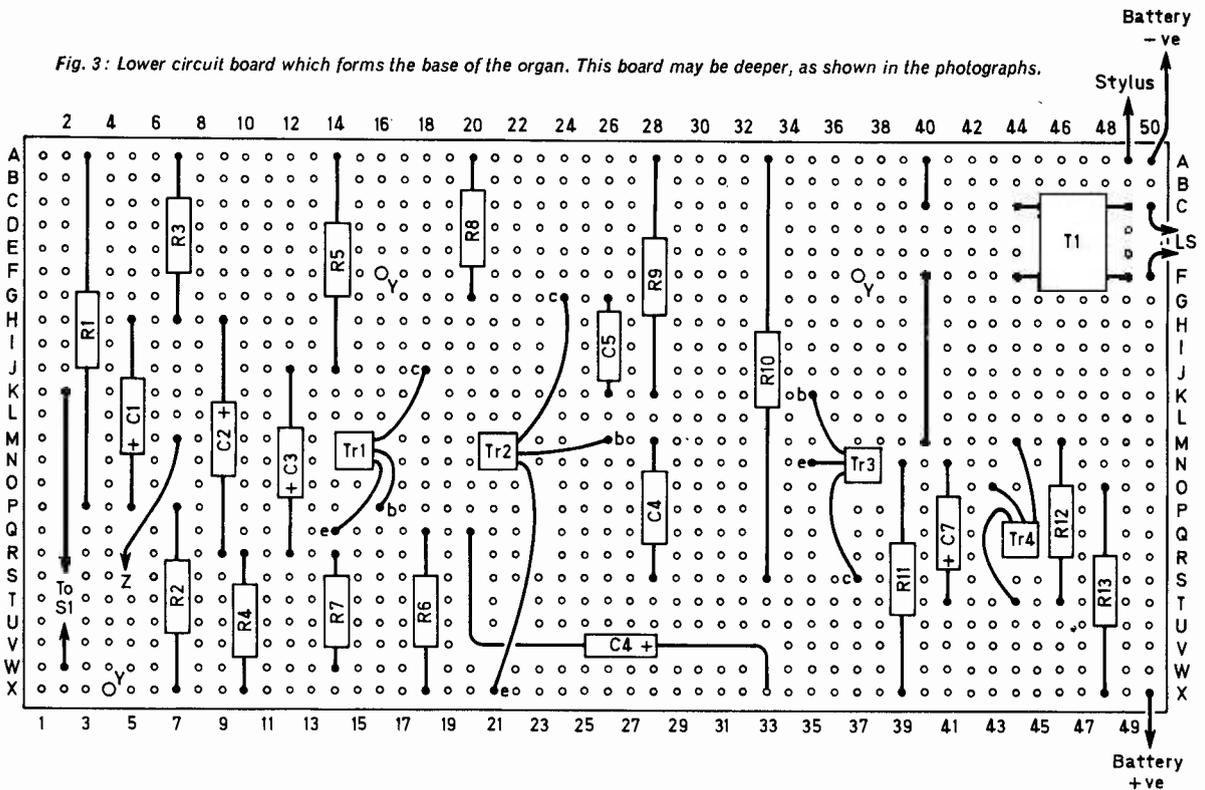

manner—getting equal intervals between successive notes. When completed, notes 1, 13 and 25 should be at octave intervals apart. If an alternative method is required, then the notes can be tuned to be of the same pitch as the corresponding note on a piano. The long strips of copper on the keyboard are equivalent to the white notes on a piano—the short strips to the black notes.

Whichever method is used, once a note has been

set it should be left—the tuning is incremental, so altering one note will affect all the notes below it in the chain. The values of the variable resistors used in the prototype should be used for the range suggested (VR1 and VR14-VR25 are 5kΩ, VR2-VR13 are 1kΩ). Higher values would work of course, but tuning would become difficult. Once tuning is complete, the keyboard and switch should be bolted to the circuit board using 1-inch 8BA bolts.

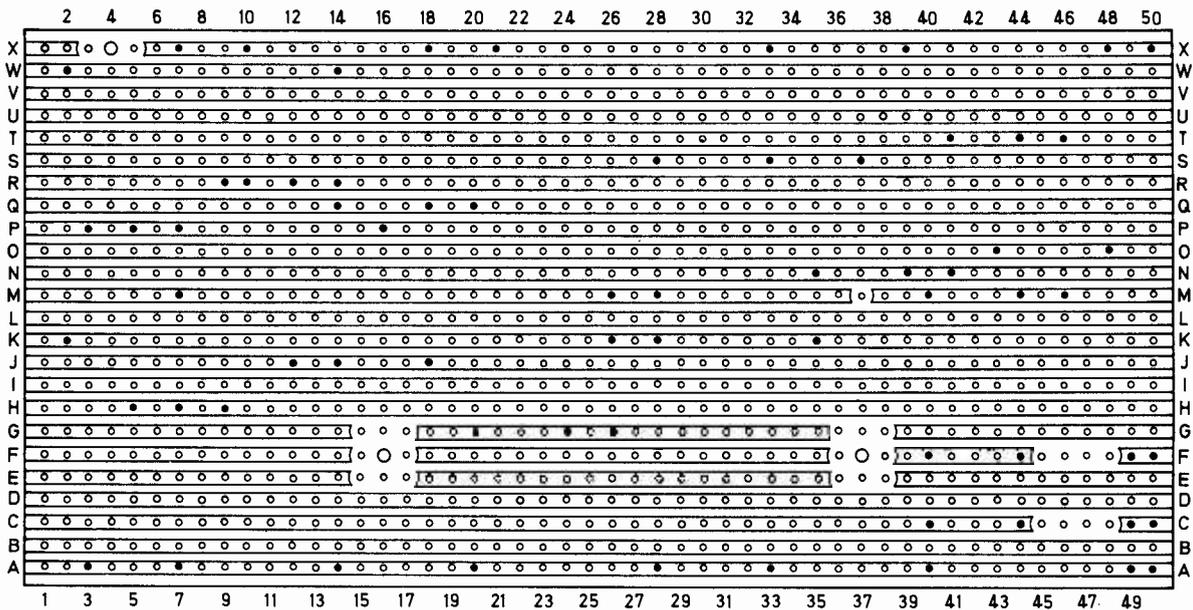


Fig. 4: The copper strips should be cut away as shown above before components are mounted on the lower circuit board.

★ components list

Resistors :

R1 82k Ω	R8 2.2k Ω
R2 10k Ω	R9 13k Ω
R3 4.7k Ω	R10 2.2k Ω
R4 4.7k Ω	R11 100 Ω
R5 4.7k Ω	R12 39k Ω
R6 1k Ω	R13 47 Ω $\frac{1}{2}$ W 5%
R7 100k Ω	

All resistors $\frac{1}{2}$ W 5% unless otherwise noted.

VR1, VR14 to VR25 (13 off) 5k Ω

VR2 to VR13 (12 off) 1k Ω

All subminiature vertical skeleton preset potentiometers

Capacitors :

C1 2.5 μ F 6V elec.	C5 0.22 μ F polyester
C2 2.5 μ F 6V elec.	C6 0.22 μ F polyester
C3 2.5 μ F 6V elec.	C7 2.5 μ F 6V elec.
C4 250 μ F 6V elec.	

Semi-conductors :

Tr1 NKT212	Tr3 NKT214
Tr2 NKT214	Tr4 ASY26

Miscellaneous :

Veroboard, 5 x 2 $\frac{1}{2}$ in, 0.1in matrix, copper clad.
Veroboard, 3 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in, 0.1in matrix, plain board.
Cir-kit strip, $\frac{1}{8}$ in, 5ft. card. Small slide switch.
Output transformer, ratio 9:2:1 (Radio spares T/T4)
Speaker, 3 ohm. Ball point pen. 8 BA nuts and bolts.

Components

Although it is possible to use fixed value resistors in place of VR1-VR25, the tolerances of other parts (C5 and C6 in particular) make variables more satisfactory. The required values of resistance do not equal the standard preferred values anyway, and the extra cost is minimal. Suitable variable resistors are the series PN sold by Messrs Electrovalue.

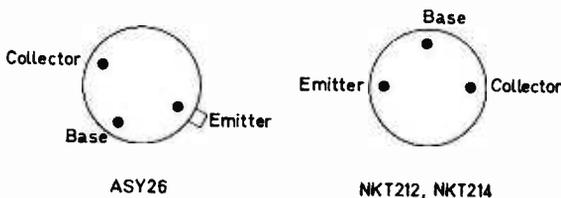


Fig. 5: Base diagrams of transistor connections.

The capacitors may, of course, be substituted by components of higher voltage rating. C1, C2, C3 and C7 could well be from the Mullard C426 series for instance. The speaker is specified only in its impedance (3 ohm), the size being unimportant. Because


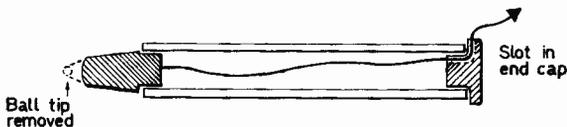


Fig. 6: Stylus made from a ball-pen.

of this no details for a case are given. 0.1 inch Veroboard is specified for ease of assembly, as VR1-VR25 and T1 have tags at multiples of this dimension.

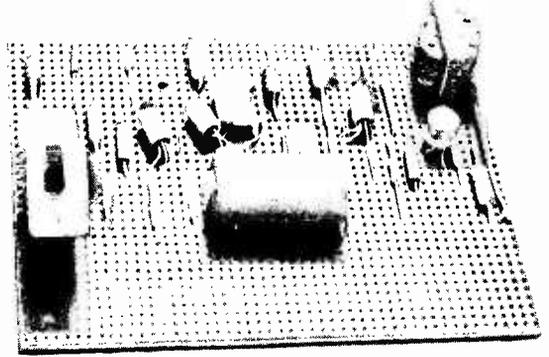It will be noted from the photographs that the piece of Veroboard used for the circuit board is larger than that specified—however the size specified is sufficient to accommodate all the parts. The total cost for a complete instrument should be under £5, a single octave instrument without tremolo would come to about £3.10.0.



Photograph of lower circuit board. Compare with Fig. 3.

Alternative Circuits

As stated earlier, the tremolo can be omitted without affecting the rest of the circuit. The pitch of the instrument can be raised by decreasing R9 or C5 and C6. If C5 and C6 are made 0.1 μ F, the instrument will play an octave higher than that described. The setting of VR1-VR25 will however be different, so a composite device is not really practicable. It is possible to use a higher impedance speaker (about 80 ohm) without a matching transformer. It will then be necessary to reduce, or possibly even omit R13. If required, a switch can be inserted in the negative battery lead. In use the organ will remain in tune even when the battery voltage falls from 9 volts to 6 volts, and having two octaves will play many simple tunes.

"Project Autumn" ENTRY FORM

Full Name

Address

Title of Article

If my article does not win a prize I should like it

(a) to be considered for publication in the usual way.*

(b) to be returned to me.*

Signature..... Date.....


*Delete as required.

Rules on page 451

PA-PW-10



ELECTRONIC DIGITAL COMBINATION LOCK

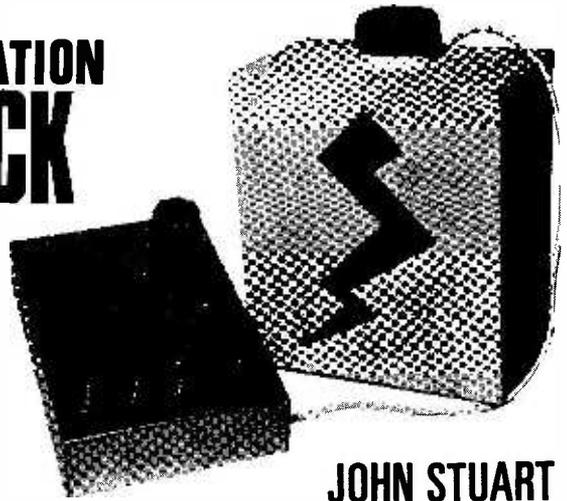

JOHN STUART

THE need for a money-making game, for a Scout Coffee Morning, which was a little more sophisticated than the well tried 'Screw-eye along the bent wire', resulted in this digitally switched combination lock.

PRINCIPLE

The principle of operation is that a code number, 0 to 7, is set up on a 3 pole 8 way rotary switch. The switch is connected in 1-2-4 binary form to a set of three toggle switches, each toggle switch corresponding to one pole of the rotary switch.

For the combination lock to be 'opened', it is necessary to set the three toggle switches (binary 1-2-4) to equal the code number set up on the rotary switch. A correct setting completes the circuit through the switches thus opening the lock. A table of binary—decimal equivalents is shown in Table 1.

If the code number is unknown, the chances of setting the toggle switches to the correct number,

in one try, are 8:1 against. To improve these odds, for the player, it was decided to allow three attempts at any particular combination. The chances of winning are now 8:3 against, but having three attempts psychologically encourages the would-be safe-cracker to feel that the odds could possibly be in his favour.

Two indicator lights, red and green, are connected so as to indicate the failure or success of the attempt. However, this display on its own seemed a little tame for the effort involved and it was decided that a more dramatic 'failure' indication and an attractive reward for a successful attempt was required.

To satisfy these requirements, a mock 'safe' was built which had an electrically opening door and a suitably loud bell mounted on top. The general arrangement of the combination lock and safe can be seen in the photograph.

For the commercially minded, small chocolate bars were used as bait and we charged 3d. for three goes. About 35s. profit was made during one Coffee Morning.

S2	S3 (1)	S4 (2)	S5 (4)
0	0	0	0
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	1	1	1

TABLE 1

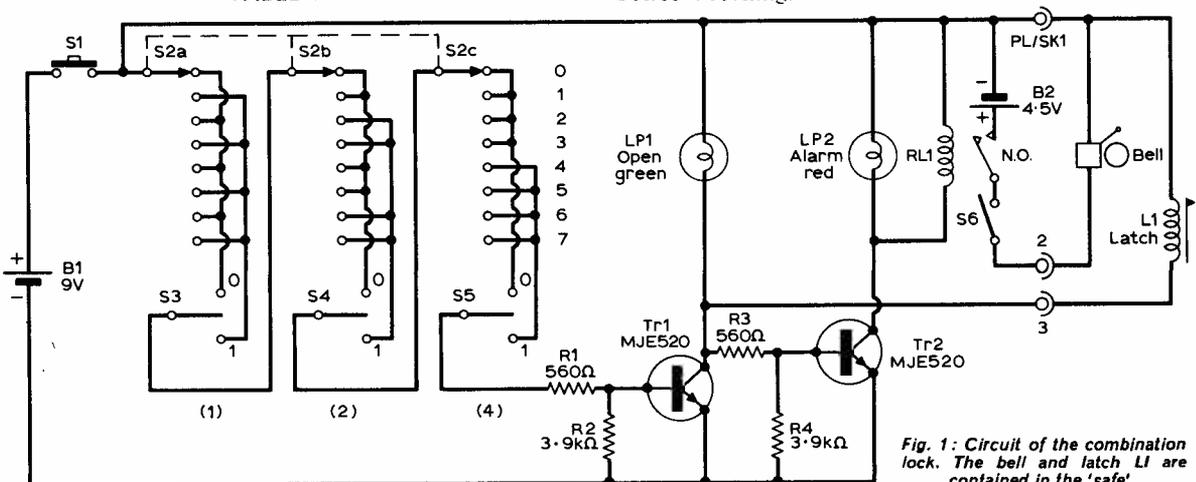


Fig. 1: Circuit of the combination lock. The bell and latch L1 are contained in the 'safe'.

Ever had karnt afindapartitis?



At some time or another most constructors of radio and electronic projects get hit by this complaint! The symptoms? Depression . . . exasperation . . . headaches . . . weariness . . . sore feet, etc. The causes? Frustrating hours spent in thumbing through inadequate out-of-date catalogues, making numerous fruitless phone calls, tramping or touring from shop to shop—all in a vain attempt to locate some vital components.

Here is the answer to the problem—the **Home Radio Components Catalogue** a world renowned medicine for preventing the complaint or for quickly clearing up the trouble if symptoms have already begun to appear! Just send the coupon with 8/6d plus 4/- postage & packing, and your copy will be despatched immediately. In its 350 pages over 8,000 components are clearly listed, over 1,500 of them illustrated. A cross-reference Index and a 30-page Price List enable you to locate your components without any trouble.



Once you have your Home Radio Catalogue you can, if you wish, make life even easier for yourself by joining our **Credit Account Service**. Then you can order by telephone any time of day or night, Sundays included! No need to bother with postal orders, cheques registering envelopes every time you order. We send prepaid envelopes and only one payment is required each month. So simple!
Write for details or telephone : 01-648 8422.



POST THIS COUPON NOW
with your cheque or P.O. for 12/6

Please write your Name and Address in block capitals

NAME



ADDRESS

HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey, CR4 3HD

The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone 01-722-9090

EXPRESS POSTAL SERVICE, SAME DAY DESPATCH BY FIRST CLASS MAIL
ALL GOODS ARE NEW, BEST QUALITY MANUFACTURE ONLY, AND SUBJECT TO MAKER'S GUARANTEE

0A2	5/9	818	3/-	12A8	18/6	85A2	8/6	B880C	18/-	EL42	10/8	F0900	7/8	SP61	8/8	V1501	8/-	AS277	8/8	EA10	8/8
0B2	6/-	825	7/6	12AC6	7/6	85A3	8/-	E180CC	8/-	EL81	10/-	PC08A	6/8	TH48	10/-	VU111	7/8	AS282	8/8	EA11	8/8
0E2	4/6	8F1	12/6	12AD6	7/6	90AG	87/6	E180F	18/-	EL83	7/6	PC08B	6/8	TP233	7/-	VU120	12/6	EA12	8/8	EA12	8/8
1A8	4/6	8F6G	5/6	12AE6	12/6	90AV	87/6	E182CC	22/6	EL84	4/9	PC08C	9/8	TP22	11/-	VU120A18	12/6	EA13	8/8	EA13	8/8
1A5	5/-	8F6M	12/6	12AT6	12/6	90CG	84/-	EA60	12/6	EL85	8/6	PC08D	9/8	TP220	9/8	W63	10/6	BA109	9/8	EA14	8/8
1A7GT	7/8	8F12	3/8	12AT7	3/9	90CV	88/6	EA76	13/6	EL86	8/6	PC08E	12/8	UAF080	6/6	W76	6/9	BA115	9/8	EA15	8/8
101	5/8	8F13	3/8	12AU6	4/9	90C1	14/6	EA80	12/6	EL87	4/6	PC08F	12/8	UAF42	10/8	W77	6/9	BA119	9/8	EA16	8/8
102	9/-	8F18	10/8	12AU7	4/8	150B2	14/6	EAC91	3/6	EL88	5/8	PC08G	12/8	UB41	6/6	W818	12/6	BA120	9/8	EA17	8/8
103	7/8	8F19	7/8	12AV8	4/8	150C2	5/9	EAF42	10/6	EM80	7/6	PC08H	12/8	UB41	6/6	W101	22/6	BA130	9/8	EA18	8/8
105	4/9	8F23	14/8	12AX7	2/6	301	20/6	EB34	3/-	EM81	7/6	PCF80	6/8	UBC41	9/6	W107	8/6	BCY10	5/6	EA19	8/8
106	7/6	8F25	14/8	12AX7	4/8	302	16/6	EB41	4/6	EM84	6/6	PCF82	6/8	UBC41	9/6	W107	8/6	BCY12	5/6	EA20	8/8
106	7/6	8F25	14/8	12AX7	4/8	303	15/6	EB41	2/8	EM87	7/6	PCF84	8/8	UBC41	9/6	W107	8/6	BCY13	5/6	EA21	8/8
106	7/6	8F25	14/8	12AX7	4/8	304	15/6	EB41	2/8	EM87	7/6	PCF86	10/8	UBC41	9/6	W107	8/6	BCY14	5/6	EA22	8/8
106	7/6	8F25	14/8	12AX7	4/8	305	16/6	EB41	2/8	EM87	7/6	PCF88	10/8	UBC41	9/6	W107	8/6	BCY15	5/6	EA23	8/8
106	7/6	8F25	14/8	12AX7	4/8	306	16/6	EB41	2/8	EM87	7/6	PCF90	12/8	UBC41	9/6	W107	8/6	BCY16	5/6	EA24	8/8
106	7/6	8F25	14/8	12AX7	4/8	307	16/6	EB41	2/8	EM87	7/6	PCF92	12/8	UBC41	9/6	W107	8/6	BCY17	5/6	EA25	8/8
106	7/6	8F25	14/8	12AX7	4/8	308	16/6	EB41	2/8	EM87	7/6	PCF94	12/8	UBC41	9/6	W107	8/6	BCY18	5/6	EA26	8/8
106	7/6	8F25	14/8	12AX7	4/8	309	16/6	EB41	2/8	EM87	7/6	PCF96	12/8	UBC41	9/6	W107	8/6	BCY19	5/6	EA27	8/8
106	7/6	8F25	14/8	12AX7	4/8	310	16/6	EB41	2/8	EM87	7/6	PCF98	12/8	UBC41	9/6	W107	8/6	BCY20	5/6	EA28	8/8
106	7/6	8F25	14/8	12AX7	4/8	311	16/6	EB41	2/8	EM87	7/6	PCF100	12/8	UBC41	9/6	W107	8/6	BCY21	5/6	EA29	8/8
106	7/6	8F25	14/8	12AX7	4/8	312	16/6	EB41	2/8	EM87	7/6	PCF102	12/8	UBC41	9/6	W107	8/6	BCY22	5/6	EA30	8/8
106	7/6	8F25	14/8	12AX7	4/8	313	16/6	EB41	2/8	EM87	7/6	PCF104	12/8	UBC41	9/6	W107	8/6	BCY23	5/6	EA31	8/8
106	7/6	8F25	14/8	12AX7	4/8	314	16/6	EB41	2/8	EM87	7/6	PCF106	12/8	UBC41	9/6	W107	8/6	BCY24	5/6	EA32	8/8
106	7/6	8F25	14/8	12AX7	4/8	315	16/6	EB41	2/8	EM87	7/6	PCF108	12/8	UBC41	9/6	W107	8/6	BCY25	5/6	EA33	8/8
106	7/6	8F25	14/8	12AX7	4/8	316	16/6	EB41	2/8	EM87	7/6	PCF110	12/8	UBC41	9/6	W107	8/6	BCY26	5/6	EA34	8/8
106	7/6	8F25	14/8	12AX7	4/8	317	16/6	EB41	2/8	EM87	7/6	PCF112	12/8	UBC41	9/6	W107	8/6	BCY27	5/6	EA35	8/8
106	7/6	8F25	14/8	12AX7	4/8	318	16/6	EB41	2/8	EM87	7/6	PCF114	12/8	UBC41	9/6	W107	8/6	BCY28	5/6	EA36	8/8
106	7/6	8F25	14/8	12AX7	4/8	319	16/6	EB41	2/8	EM87	7/6	PCF116	12/8	UBC41	9/6	W107	8/6	BCY29	5/6	EA37	8/8
106	7/6	8F25	14/8	12AX7	4/8	320	16/6	EB41	2/8	EM87	7/6	PCF118	12/8	UBC41	9/6	W107	8/6	BCY30	5/6	EA38	8/8
106	7/6	8F25	14/8	12AX7	4/8	321	16/6	EB41	2/8	EM87	7/6	PCF120	12/8	UBC41	9/6	W107	8/6	BCY31	5/6	EA39	8/8
106	7/6	8F25	14/8	12AX7	4/8	322	16/6	EB41	2/8	EM87	7/6	PCF122	12/8	UBC41	9/6	W107	8/6	BCY32	5/6	EA40	8/8
106	7/6	8F25	14/8	12AX7	4/8	323	16/6	EB41	2/8	EM87	7/6	PCF124	12/8	UBC41	9/6	W107	8/6	BCY33	5/6	EA41	8/8
106	7/6	8F25	14/8	12AX7	4/8	324	16/6	EB41	2/8	EM87	7/6	PCF126	12/8	UBC41	9/6	W107	8/6	BCY34	5/6	EA42	8/8
106	7/6	8F25	14/8	12AX7	4/8	325	16/6	EB41	2/8	EM87	7/6	PCF128	12/8	UBC41	9/6	W107	8/6	BCY35	5/6	EA43	8/8
106	7/6	8F25	14/8	12AX7	4/8	326	16/6	EB41	2/8	EM87	7/6	PCF130	12/8	UBC41	9/6	W107	8/6	BCY36	5/6	EA44	8/8
106	7/6	8F25	14/8	12AX7	4/8	327	16/6	EB41	2/8	EM87	7/6	PCF132	12/8	UBC41	9/6	W107	8/6	BCY37	5/6	EA45	8/8
106	7/6	8F25	14/8	12AX7	4/8	328	16/6	EB41	2/8	EM87	7/6	PCF134	12/8	UBC41	9/6	W107	8/6	BCY38	5/6	EA46	8/8
106	7/6	8F25	14/8	12AX7	4/8	329	16/6	EB41	2/8	EM87	7/6	PCF136	12/8	UBC41	9/6	W107	8/6	BCY39	5/6	EA47	8/8
106	7/6	8F25	14/8	12AX7	4/8	330	16/6	EB41	2/8	EM87	7/6	PCF138	12/8	UBC41	9/6	W107	8/6	BCY40	5/6	EA48	8/8
106	7/6	8F25	14/8	12AX7	4/8	331	16/6	EB41	2/8	EM87	7/6	PCF140	12/8	UBC41	9/6	W107	8/6	BCY41	5/6	EA49	8/8
106	7/6	8F25	14/8	12AX7	4/8	332	16/6	EB41	2/8	EM87	7/6	PCF142	12/8	UBC41	9/6	W107	8/6	BCY42	5/6	EA50	8/8
106	7/6	8F25	14/8	12AX7	4/8	333	16/6	EB41	2/8	EM87	7/6	PCF144	12/8	UBC41	9/6	W107	8/6	BCY43	5/6	EA51	8/8
106	7/6	8F25	14/8	12AX7	4/8	334	16/6	EB41	2/8	EM87	7/6	PCF146	12/8	UBC41	9/6	W107	8/6	BCY44	5/6	EA52	8/8
106	7/6	8F25	14/8	12AX7	4/8	335	16/6	EB41	2/8	EM87	7/6	PCF148	12/8	UBC41	9/6	W107	8/6	BCY45	5/6	EA53	8/8
106	7/6	8F25	14/8	12AX7	4/8	336	16/6	EB41	2/8	EM87	7/6	PCF150	12/8	UBC41	9/6	W107	8/6	BCY46	5/6	EA54	8/8
106	7/6	8F25	14/8	12AX7	4/8	337	16/6	EB41	2/8	EM87	7/6	PCF152	12/8	UBC41	9/6	W107	8/6	BCY47	5/6	EA55	8/8
106	7/6	8F25	14/8	12AX7	4/8	338	16/6	EB41	2/8	EM87	7/6	PCF154	12/8	UBC41	9/6	W107	8/6	BCY48	5/6	EA56	8/8
106	7/6	8F25	14/8	12AX7	4/8	339	16/6	EB41	2/8	EM87	7/6	PCF156	12/8	UBC41	9/6	W107	8/6	BCY49	5/6	EA57	8/8
106	7/6	8F25	14/8	12AX7	4/8	340	16/6	EB41	2/8	EM87	7/6	PCF158	12/8	UBC41	9/6	W107	8/6	BCY50	5/6	EA58	8/8
106	7/6	8F25	14/8	12AX7	4/8	341	16/6	EB41	2/8	EM87	7/6	PCF160	12/8	UBC41	9/6	W107	8/6	BCY51	5/6	EA59	8/8
106	7/6	8F25	14/8	12AX7	4/8	342	16/6	EB41	2/8	EM87	7/6	PCF162	12/8	UBC41	9/6	W107	8/6	BCY52	5/6	EA60	8/8
106	7/6	8F25	14/8	12AX7	4/8	343	16/6	EB41	2/8	EM87	7/6	PCF164	12/8	UBC41	9/6	W107	8/6	BCY53	5/6	EA61	8/8
106	7/6	8F25	14/8	12AX7	4/8	344	16/6	EB41	2/8	EM87	7/6	PCF166	12/8	UBC41	9/6	W107	8/6	BCY54	5/6	EA62	8/8
106	7/6	8F25	14/8	12AX7	4/8	345	16/6	EB41	2/8	EM87	7/6	PCF168	12/8	UBC41	9/6	W107	8/6	BCY55	5/6	EA63	8/8
106	7/6	8F25	14/8	12AX7	4/8	346	16/6	EB41	2/8	EM87	7/6	PCF170	12/8	UBC41	9/6	W107	8/6	BCY56	5/6	EA64	8/8
106	7/6	8F25	14/8	12AX7	4/8	347	16/6	EB41	2/8	EM87	7/6	PCF172	12/8	UBC41	9/6	W107	8/6	BCY57	5/6	EA65	8/8
106	7/6	8F25	14/8	12AX7	4/8	348	16/6	EB41	2/8	EM87	7/6	PCF174	12/8	UBC41	9/6	W107	8/6	BCY58	5/6	EA66	8/8
106	7/6	8F25	14/8	12AX7	4/8	349	16/6	EB41	2/8	EM87	7/6	PCF176	12/8	UBC41	9/6	W107	8/6	BCY59	5/6	EA67	8/8
106	7/6	8F25	14/8	12AX7	4/8	350	16/6	EB41	2/8	EM87	7/6	PCF178	12/8	UBC41	9/6	W107	8/6	BCY60	5/6	EA68	8/8
106	7/6	8F25	14/8	12AX7	4/8	351	16/6	EB41	2/8	EM87	7/6	PCF180	12/8	UBC41	9/6	W107	8/6	BCY61	5/6	EA69	8/8
106	7/6	8F25	14/8	12AX7	4/8	352	16/6	EB41	2/8	EM87	7/6	PCF182	12/8	UBC41	9/6	W107	8/6	BCY62	5/6	EA70	8/8
106	7/6	8F25	14/8	12AX7	4/8	353	16/6	EB41	2/8	EM87	7/6	PCF184	12/8	UBC41	9/6	W107	8/6	BCY63	5/6	EA71	8/8
106	7/6	8F25	14/8	12AX7	4/8	354	16/6	EB41	2/8	EM87	7/6	PCF186	12/8	UBC41	9/6	W107	8/6				

★ components list

Resistors:

R1	560Ω	R3	560Ω
R2	3.9kΩ	R4	3.9Ω

All ½W 5%

Semi-conductors:

Tr1/2 MJE520 Motorola (L.S.T. Components)

Switches:

- S1 Single pole, push-to-make push switch
- S2 3 wafers, each 1 pole 8 way, rotary
- S3 Single pole, change over, toggle
- S4 Single pole, change over, toggle
- S5 Single pole, change over, toggle
- S6 Single pole, on-off toggle

Miscellaneous:

LP1/2, Lamps 8V 0.2A m.e.s. RL1, Reed operating coil Type 1 with dry reed switch Type 10RSR (Radiospares). L1, Modified P.O. Type 3000 relay, 200 ohm coil. Bell, AC/DC 4.5V. Batteries, 9V PP9, 4.5V 1289 (Ever Ready).

CIRCUIT OPERATION

The complete circuit is shown in Fig. 1. When the settings of S3, S4 and S5 are such as to equal the setting of S2, (correct combination), continuity exists between the rotor of S2a and the common connection of S5.

In this condition, the closing of S1 (push button) will cause +9 volts to be applied to the collector circuits of Tr1 and Tr2 and to R1.

This results in Tr1 conducting, causing the 'OPEN' lamp, LP1, to light and the latch solenoid, L1, to be energised, thus opening the safe door.

In the event of the setting of S3, S4 and S5 not equalling the setting of S2, (incorrect combination), there will be no continuity through the switch system.

In this condition, the closing of S1 will cause +9 volts to be applied to the collector circuits of Tr1 and Tr2, as before, but Tr1 will now be non-conducting.

This results in Tr1 collector being at approximately +9 volts, LP1 remaining unlit and L1 de-energised.

The positive voltage at Tr1 end of R3 causes Tr2 to conduct, lighting the 'ALARM' lamp, LP2, energising the reed relay RL1 and thus ringing the alarm bell.

A separate 4.5V battery, is used to drive the alarm bell, as 9V is rather excessive for the type of bell used. Switch S6 is included in the bell circuit so that the bell may be muted if the lamp indication only is required.



The layout of the components is not at all critical. The two transistors are bolted to the chassis to the right of the reed solenoid.

CONSTRUCTION

The switch system, lamp batteries and other components are housed in a conventional aluminium chassis, size 10×6½×2in. The layout of components is not critical and the general arrangement can be seen in the photographs.

The rotary switch, S2, does not have any positional markings on the knob, so as not to indicate the combination setting to the contestant and thus increase his chances of opening the safe.

The safe is built from ¾in. blockboard and could be scaled up or down to suit individual requirements.

The method of construction is shown in Fig. 2.


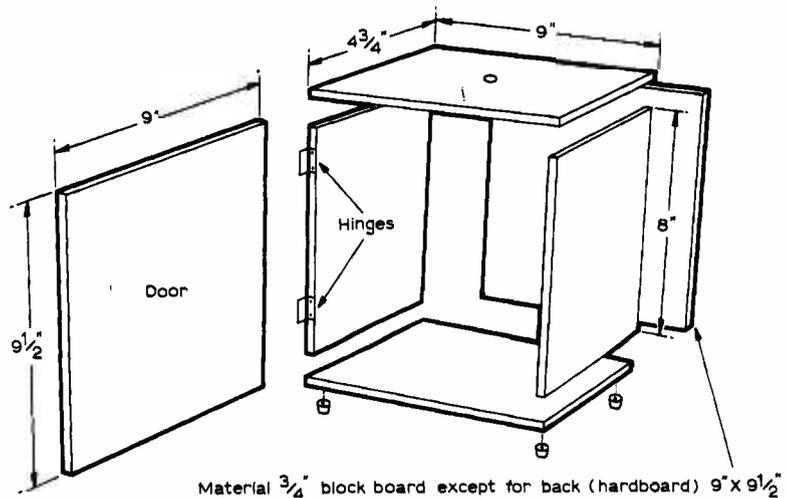


Fig. 2: Constructional details of the 'safe'.

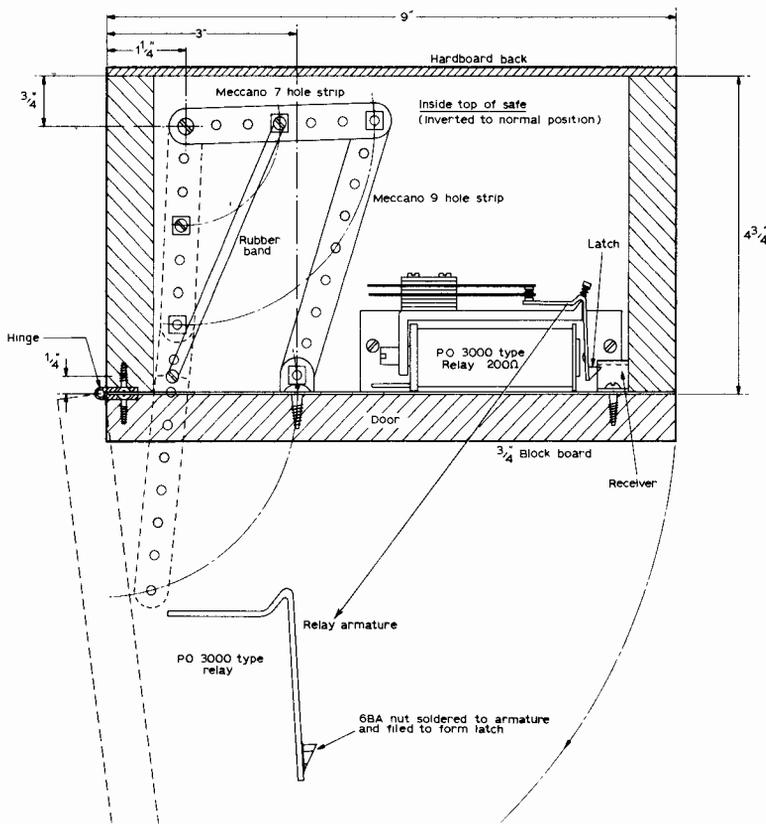


The electrical latch is made from a Post Office type 3000 relay. The relay is modified by soldering a brass latch to the toe of the relay armature as shown in Fig. 3.

The relay is mounted on its side by either soldering the metal bobbin cheek to a brass backing plate or by using a suitable curved clip fitting over the relay bobbin.

The moving part of the latch is formed by a small angle bracket fixed on the side of the door.

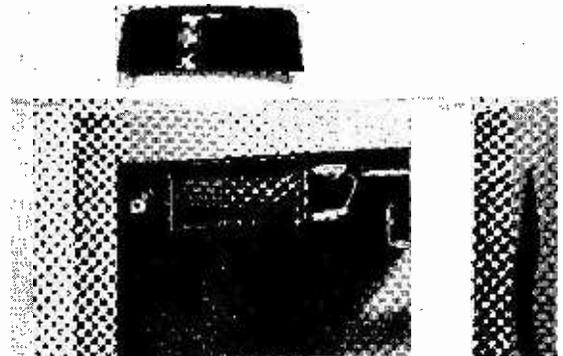The automatic opening mechanism is a crude but effective arrangement using two Meccano strips and a rubber band. The arrangement is shown in Fig. 3. It should be noted that the mechanism is on the underside of the top of the safe and that the drawing and photograph show how it appears when the safe is inverted.



Close-up view of latch mechanism and door catch.

Fig. 3: (top) Details of the latch mechanism and relay modification. (below) photograph of completed control unit.

OPERATION

1. Set Combination Switch S2 to any position.
2. Set bell switch S6 to 'ON' if bell is required.
3. Contestant sets S3, S4 and S5 to his choice.
4. Contestant presses S1, (OPEN or ALARM operates).

Note: S2 must be changed to a new combination after each attempt or set of attempts, to obtain the desired odds.

COMMENTS

Although the Electronic Digital Combination Lock is used as a game, an extension of the number of digits could form the basis of a commercial combination lock having an easy and rapid change of combination. ■

Metrosound Audio Products



ST.20 Stereo Amplifier

Good looks apart the ST.20 offers outstanding performance equal to amplifiers selling at two or three times the price which makes it one of the best buys on the High Fidelity market. All silicon solid state circuitry using 20 transistors and 2 diodes provides a full 20 watts r.m.s. output (10 watts r.m.s. per channel). Conservatively rated components are used throughout to ensure long term reliability and stability. Press button selector switches are a feature of the ST.20 for magnetic phono, crystal phono, radio tuner, tape, mono/stereo and on/off facilities. The slimline cabinet in teak veneers and the front panel fascia of

brushed anodised aluminium finish with gleaming silver trims combine to give a look of expensive and stylish elegance.

Size 15½" x 3½" x 10".

Price £36.0.0.

"Its performance is not just on the fringe of the specification - as happens with many low-priced amplifiers - it is well within it and well within the requirements for hi-fi"

F. C. Judd "Hi-Fi Sound" August 1970




ACCEPTED BY THE
COUNCIL OF INDUSTRIAL
DESIGN FOR INCLUSION
IN DESIGN INDEX



Stereo 10-10 Compact System

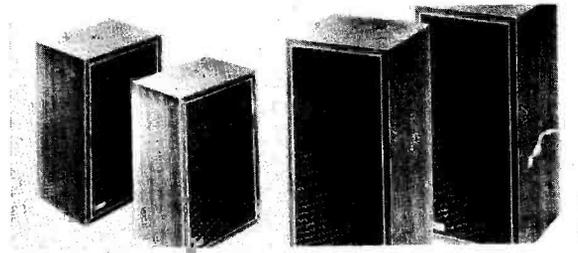Expertly designed and providing outstanding quality reproduction. Not just another compact system but a true "sound centre" incorporating an all silicon transistor amplifier, Garrard 3000 autochanger and two Metrosound HFS.10 speaker systems. Output 20 watts rms. (10 watts rms. per channel) Bass, Treble, Volume and Balance controls. Input for tuner. Tape record outlet. Price £77.6.4.



Metrosound Speaker Systems

MODEL HFS.10 10 watts handling capacity. 8 ohm impedance. Teak finish. Size 14" x 9" x 7". As used in the Stereo 10-10 Compact System and available in matched pairs at £26.3.8.

MODEL HFS.20 20 watts handling capacity. 8 ohm impedance. Teak finish. Size 23" x 11½" x 10½". Price £18.10.0. each.

Please send full details of

ST.20 Amplifier 10-10 Compact Speakers

NAME

ADDRESS

Available from all leading high fidelity dealers
Designed and Manufactured in England by

metrosound

Metrosound Manufacturing Co. Ltd., Audio Works,
Cartersfield Road, Waltham Abbey, Essex.
Telephone: Waltham Cross 31933

This MONTH'S Best Buy . . .



AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £10/8/0d.) Our Price **£5.18.** p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

- * High-fidelity reproduction due to broad frequency response (20-20,000Hz)
- * Substantially increased stereo effect
- * Headphones fit the head gently and do not shift
- * Earpieces fit ears snugly (Cardanic suspension)
- * Tone quality superior to conventional loudspeakers.
- * Only expensive studio loudspeakers can match the reproduction quality of the K50.
- * Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.

GARRARD SP25

mk II **£10.19.6** Plus 10/- carriage
Normal price £15.11.4

Single record playing unit. Features include cue and pause and automatic pick-up return and switch off.
Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug, 10/6 extra
AP75 Complete with base and cover **£25** plus 15/- carriage.

PLUGS?



- Pack 107 5 Pin Din 4/-d.
 - Pack 108 3 Pin Din 3/6d.
 - Pack 135 1/2 Jack 5/-d.
 - Pack 130 1/2 Jack Stereo 9/6d.
 - Pack 103 Loudspeaker Plug 3/-d.
 - Pack 100 Phono Plug 1/3d.
 - Pack 230 3 pin Socket 4/6d.
 - Pack 236 5 pin Socket 6/-d.
 - Pack 234 Loudspeaker Socket 6/-d.
- Express delivery 6d. per unit postage.
Ready-made Leads
3 pin to 3 pin Din 12/6
3 pin to open end 10/6
5 pin to 5 pin Din 16/-
5 pin to open end 13/6
5 pin to 4 phono plugs 18/6
- All leads approx. 6ft. in length. Post free, by return.

PLINTH & COVER £5.50

Unbeatable Value plus 10/- p. & p.
Suitable for: AT60; SP25; 3000; 2500; 3500. Superb finish. Spindle can be left in position with cover on. Cover of neutral smoke tint perspex.
Also available for AP75; SL99; SL75 **£6.17.6** plus 10/- carr.

Replacement Stereo DIAMOND STYL

8TA 9TA 9TAHC GP91 ST4 ST9 EV26 GC8 **15/-** each
others on request p. & p. 1/6

Countdown SPEAKER

Teak Cabinet
£12 insurance & carr. 7/6

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.

EMI 10w matched loudspeaker set 450

Our price **75/-** inc. 5/- p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13000 Hz. The design of the base unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies.

Also 350 KIT 20W
Frequency range: 20 to 20,000 Hz.
£7.10.6 plus 8/- p. & p.

Also 150 KIT 10W
3, 8 or 15 ohms 50/- plus 8/- p. & p.

SINCLAIR Project 60

SAVE nearly £5 Normal price £23.18.0d.



Designed for building into plinths etc., complete with two Z30 Output stages **£19** plus 10/- carr.

(20 watt) and power supply unit. Send S.A.E. for full technical brochure.
SINCLAIR 2000 AMPLIFIER SAVE 6gns. Our price 23gns.

Magnetic cartridges

Diamond **95/-** plus 2/6 p. & p.
Today's value **£6.**

Stylus replacement can be carried out without removing cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) **25/-** 2/6 p. & p.

SONOTONE Cartridges

(Fitted Diamond Styl) (Ceramic) list price 82/-

Sensitivity: 9TA 80mV 47/6
9TAHC 55mV/cm/sec rms minimum at 45° at plus 1000Hz measured on Decca SX12057 p. & p.

J. J. FRANCIS

(WOOD GREEN) LTD
123 ALEXANDRA ROAD, HORNSEY, LONDON, N.8. Tel: 01-888 1662

M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649



VHF FM/MW/LW TRANSISTOR RADIO BRAND NEW 10 transistor plus 4 diode table model of well known British manufacture. The highly polished wood cabinet, speaker and pre-assembled chassis are supplied separate and only require fitting together and the 2 speaker connections making. CHASSIS & CABINET **£9.10.0.** SPEAKER 25/- carr. paid.

STC STEREO/MONO HEADPHONES. Brand new lightweight high quality comfortable padded headphones for stereo or mono use. Weight 10 oz. 20 c/s to 20 Kc/s 300 ohms per earpiece. Supplied with details of matching circuit for 15 ohms using only 3 resistors. 54/- plus 4/- pp. 12 VOLT TRANSISTOR INVERTERS. 12vdc input. 270vdc at 150mA approx output. Transformer 2 1/2 x 2 1/4 in 1 1/4 in mounted on aluminium case 1 1/4 in x 2 1/4 in x 4 in. Weight 15oz. 65/- plus 4/- pp.

TRANSISTOR MODULATOR PRE-AMP PANEL. BRAND NEW 4 transistors plus 1 diode. 4 1/4 in x 2 1/4 in. Fitted with pre-set microphone gain control and mod filter. Originally used to drive an NKT404 which drove a pair of NKT404s. Supplied brand new c/w circuit of complete modulator. 22/6d plus 1/6 pp.

TRANSISTOR AUDIO AND MUTING PANELS. Brand new set of 3 panels. Audio panel with transistor gate originally used to drive an NKT404 output transistor. 2 muting panels with Schmitt trigger circuit to operate the gate on the audio panel. 8 transistors in all. Supplied with full circuit 22/6d plus 2/6 pp.

455Kc/s FM I.F. PANEL. Brand new but faulty 6 transistor panel usually low in gain. 12/6 plus 1/6 pp.

HAND TELEPHONES. Brand new radiotelephone type press to talk handsets. 12/6 plus 1/6 pp.

VHF AERIAL C/O RELAYS. Used but OK. 6 or 12v. 4/- plus 1/6 pp
60 UNTESTED MIXED TRANSISTORS 5/- plus 1/- pp.
60 UNTESTED MIXED DIODES 2/6 plus 1/- pp.

USED TESTED VALVES. 12AX7/EC83 2/6. 6BJ6 1/6. 6AQ5/EL90 2/6. ECF80 2/- . 6AT6 1/6.

ALSO VARIOUS VHF EQUIPMENT IN STOCK
S.A.E. AND 6d. STAMP FOR LISTS

VALVES SAME DAY SERVICE

SETS 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.

Set of 4 for 18/6, DAF96, DF 96, DK96, DL96, 4 FOR 29/-.

1A7GT 7/6	25LGT 5/-	DL92 5/9	EL500 12/6	PCL84 7/6	UBF80 6/9
1H5GT 7/3	25UAGT11/6	DL94 6/9	EM34 14/6	PCL85 9/-	UBF89 6/9
1NGGT 7/9	30C1 6/6	DL96 7/3	EM80 8/3	PCL86 8/3	UC84 7/-
1R6 5/9	30C15 13/-	DY86 5/9	EM81 8/3	FC188 14/6	UC85 7/3
1R5 4/3	30C17 16/-	DY87 5/9	EM84 8/9	PCL80015/6	UCF80 7/3
1T4 2/9	30C18 13/6	EAB30 6/6	EM87 7/6	PEN4A 8/6	UCH42 12/6
3B4 5/9	30F5 16/-	EAF42 10/-	EY51 7/3	PFL20011/9	UCH81 6/6
3V4 6/9	30FL1 12/6	EB91 2/3	EY86 6/6	PL36 9/9	UCL82 7/6
5Y3GT 5/9	30FL12 14/6	EB33 9/-	EZ40 8/-	PL31 9/3	UCL83 11/9
5Z4G 7/6	30FL14 14/6	EB41 10/6	EZ41 8/-	PL82 6/-	UP41 10/6
6AL5 2/9	30L1 6/6	EBF60 6/9	EZ80 4/6	PL83 6/6	UP85 6/9
6AM6 2/3	30L15 13/-	EBF89 3/3	EZ81 4/9	PL84 6/6	UP89 6/9
6AQ5 5/3	30L17 15/6	EC081 3/9	EZ82 9/9	PL500 13/6	UL41 12/-
6A8E 6/3	30P4 9/9	EC082 4/9	EZ34 9/9	PL504 13/6	UL44 20/-
6A8E 6/3	30P12 13/9	EC083 7/-	KT41 16/6	PL608 23/6	UL84 7/-
6AT6 4/6	30P19 12/-	EC085 5/-	KT61 9/9	P84 7/6	UM50 6/-
6BA6 4/6	30P11 12/9	EC084 12/-	KT66 18/9	PX25 23/6	UM84 4/6
6BE6 4/9	30P13 14/6	ECF80 6/6	LN359 14/6	PY32 10/-	UY41 7/6
6BE6 4/9	30P14 14/-	ECF82 6/6	N78 17/6	PY38 10/-	UY86 5/9
6BJ6 8/6	35LGT 8/9	ECH35 6/-	P61 10/-	PY81 5/3	VP4B 15/6
6C5G 4/9	35W4 4/6	ECH42 12/9	PABC80 7/-	PY82 5/3	W77 3/6
6F14 9/-	35ZAGT 6/-	ECH81 5/3	PC86 10/6	PY83 5/9	W119 7/-
6F23 14/3	60E3 13/6	ECH83 5/3	PC88 10/3	PY88 6/6	Z77 4/6
6F2F 12/6	807 9/9	ECH84 7/6	PC89 8/6	PY800 7/6	Transistors
6G5G 4/9	ACV/P215/6	ECL80 7/6	PC97 8/-	PY801 7/6	AC107 3/6
6K7G 2/6	A341 9/6	ECL82 9/9	PC900 7/6	R19 6/6	AC127 2/6
6K8G 2/9	BZ99 13/-	ECL86 3/-	PC84 6/6	R20 12/-	AD140 7/6
6N7GT 4/3	BZ29 12/6	EP37A 6/6	PC85 6/6	SU2150A	AF116 3/-
6P23 14/3	60E3 13/6	ECH83 5/3	PC88 10/3	PY88 6/6	Z77 4/6
6P2F 12/6	807 9/9	ECH84 7/6	PC89 8/6	PY800 7/6	Transistors
6G5G 4/9	ACV/P215/6	ECL80 7/6	PC97 8/-	PY801 7/6	AC107 3/6
6K7G 2/6	A341 9/6	ECL82 9/9	PC900 7/6	R19 6/6	AC127 2/6
6K8G 2/9	BZ99 13/-	ECL86 3/-	PC84 6/6	R20 12/-	AD140 7/6
6N7GT 4/3	BZ29 12/6	EP37A 6/6	PC85 6/6	SU2150A	AF116 3/-
6P23 14/3	60E3 13/6	ECH83 5/3	PC88 10/3	PY88 6/6	Z77 4/6
6P2F 12/6	807 9/9	ECH84 7/6	PC89 8/6	PY800 7/6	Transistors
6G5G 4/9	ACV/P215/6	ECL80 7/6	PC97 8/-	PY801 7/6	AC107 3/6
6K7G 2/6	A341 9/6	ECL82 9/9	PC900 7/6	R19 6/6	AC127 2/6
6K8G 2/9	BZ99 13/-	ECL86 3/-	PC84 6/6	R20 12/-	AD140 7/6
6N7GT 4/3	BZ29 12/6	EP37A 6/6	PC85 6/6	SU2150A	AF116 3/-
6P23 14/3	60E3 13/6	ECH83 5/3	PC88 10/3	PY88 6/6	Z77 4/6
6P2F 12/6	807 9/9	ECH84 7/6	PC89 8/6	PY800 7/6	Transistors
6G5G 4/9	ACV/P215/6	ECL80 7/6	PC97 8/-	PY801 7/6	AC107 3/6
6K7G 2/6	A341 9/6	ECL82 9/9	PC900 7/6	R19 6/6	AC127 2/6
6K8G 2/9	BZ99 13/-	ECL86 3/-	PC84 6/6	R20 12/-	AD140 7/6
6N7GT 4/3	BZ29 12/6	EP37A 6/6	PC85 6/6	SU2150A	AF116 3/-
6P23 14/3	60E3 13/6	ECH83 5/3	PC88 10/3	PY88 6/6	Z77 4/6
6P2F 12/6	807 9/9	ECH84 7/6	PC89 8/6	PY800 7/6	Transistors
6G5G 4/9	ACV/P215/6	ECL80 7/6	PC97 8/-	PY801 7/6	AC107 3/6
6K7G 2/6	A341 9/6	ECL82 9/9	PC900 7/6	R19 6/6	AC127 2/6
6K8G 2/9	BZ99 13/-	ECL86 3/-	PC84 6/6	R20 12/-</	

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

IN the past it has always been thought that the summer months were a time when most enthusiasts had very little time for listening on the bands. The amount of mail that I have received in the last few months has convinced me that this is not so. I sincerely hope that this trend will continue and reports will continue to pour in.

Because of the large number of reports that I now receive every month I have been forced to be more selective in choosing the material that I use. In the future I would be obliged if all reports gave accurate details of the station heard, such as frequency, time and programme details. Reports which conform to this requirement will stand a much better chance of being published.

When I started writing this column a year ago I said that it would be my policy to try and include as much material as possible from the more exotic stations. This is still my policy and with the large number of reports coming in I can select these more interesting stations. I will, however, continue to mention the more common stations, as I have found that among the beginners to the hobby who read this page there is a real demand for these easier stations.

Members Logging and News

Des Walsh of Little Baddow feels that all civilised countries should operate a short-wave service. He is particularly interested in the fact that the Republic of Ireland has no such service. He has tried to get them to start such a service but with no success. He would like all readers who are interested in this problem to write to *Radio Telefis Eireann* to ask them to start a short-wave service.

Malcolm Cheeseman of Llanberis in Caernarvonshire is using a 20-year-old Pye domestic receiver and a 24 foot vertical aerial and he logged the following stations:

- 7065 *Radio Tirana*, Albania at 1840
- 9625 *Radio Israel* at 2045 GMT.
- 11672 *Radio Pakistan* at 2005
- 11815 *Trans World Radio*, Bonaire at 0035
- 15160 *Radio Ankara*, Turkey at 2205
- 15345 *Radio Kuwait* at 1645
- 17890 *HCJB*, Ecuador at 2330

J. Treweek of London Colney has heard some very interesting stations in the last month:

- 11955 *BBC Far Eastern Relay station* with ident. at 1658 and at close down at 1815
- 15165 *Radio Damascus*, Syria at 1930 in English
- 15240 *ABC Australia* with news in Eng. at 2145
- 15320 *ABC Australia* at 2155.

R. F. Bruce of Angus in Scotland has an Eddy-stone 940 receiver and an indoor Joystick which

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

enabled him to hear:

- 5050 *Radio Tanzania* until sign-off at 2000
- 11735 *Radio Morocco*, English news at 1715
- 11955 *BBC Far East Relay*, ident. at 1815
- 15020 *The Voice of Vietnam* in English at 2000
- 15165 *Radio Damascus*, Syria, English news at 1930
- 21690 *WIBS*, Grenada heard at 2100.

Stephen Wainwright of St. Helens has again used his Skyrover Mark II receiver and 100 foot long-wire to good effect:

- 9625 *Radio Trans Europe* with test transmissions for the U.K. from 1345 to 1415.

15345 *Radio Kuwait* in English with news at 1830
 Stephen also reports that HCJB are issuing QSL cards without requiring the information stated in this column in the June issue.

Roy Patrick of Derby sent in the following interesting information:

South Africa: Radio RSA broadcasts to the U.K. at 1800-1850 on 21480 and 15250, the former frequency gives the better reception.

Kenya The Voice of Kenya on 4915 is audible with a fairly good signal with a programme in Swahili at 1900.

Terry Gibbs of Swindon heard the following stations:

- 11800 Italian Broadcasting at 1930 to 2000
- 17860 *ABC Australia* at 2130 to 2230
- 21495 *Radio Portugal* at 2030 to 2100.

Regular reporter **Geoffrey Gilham** of London S.E.12 has been on holiday but still managed to send in the following log:

- 4865 *Azores* with talk in Portuguese at 2157
- 4870 *Dahomey*, vernaculars and music at 2137
- 4915 *Ghana*, talk in English at 2156
- 4940 *Kiev*, classical music at 1935
- 5058 *Tirana*, classical music at 2145.

Mervyn Winters of Co. Antrim used his AR88 and 12 foot whip aerial to hear:

- 9009 *Israel* heard at 2115
- 9560 *Amman, Jordan*, heard at 1600
- 11960 *All India Radio*, Delhi at 2015
- 15265 *Radio Afghanistan* at 1800
- 17855 *NHK, Japan* heard at 0700.

With apologies to all those reporters whose contributions I have not used I will end with a log from **Glen Morgan** of Tredegar:

- 3204 *Ibadan* in English at 2205
- 3380 *Malawi*, dance band music at 2025
- 4774 *Libreville*, African music at 2205
- 6540 *Pyongyang* in English at 1935.

Please note that by the time this article is published I will have changed my address and all reports should be sent to me at 5 *Ranelagh Gardens*, Cranbrook, Ilford, Essex, by the 17th of the month.

SHORT WAVES

It just isn't fair. Every month the contest types come last, so, just to show there's no hidden meaning in it, let's start off by seeing what's happening contest-wise. September 12-13th, WAE DX phone contest; 13th, 3.5MHz field day (go on, have a listen all you h.f. types); October 3-4th, u.h.f./s.h.f. contest. The 10 metre phone contest on October 10-11th, should prove an interesting one, while for those not too far from London there is a lecture at the Institution of Electrical Engineers on the Trans-Arctic Expedition. You get a cup of tea, too!

P. Newman (Bucks.) reckons we ought to have a page of logs from home-brew equipment only. Start dusting the cobwebs off that old t.r.f. you built and get listening! I agree that there is a greater sense of achievement in bagging some good DX on a homebrew. (You wait until my 600 transistor receiver is finished—Cor, think of the gain.)

M. Bernstein (Lancs.) finds that the mornings are the best time for a listen on 14MHz. **S. Ireland**, down in Kent, is giving serious thought to building a 144MHz converter "to give Glyn Richards some competition." Steve also claims that the 5B4NZ heard on topband (Amateur Bands, August issue) was flying the Jolly Roger because the only recent licence in that area was 5B4ES. (Well shiver me dipoles.)

In spite of a patchy period, **Steve Ireland** (Kent), **HR0 MX**, 67ft. end fed, bagged these on 3.5MHz: **CR6IV**, **CT1MC**, **CT2AK**, **OJØDX** (Market Reef), **PY3BAD**, **PY5XQ**, **PY7AF**, **UW9AF**, **VEØNEF/G5**, **VP8FL**, **VP8KF**, **ZB2BY**, **ZS5XA**, **6W8DY**, **9V1PP**. Tuning h.f., a listen on 21MHz brought sigs from: **AX9AC**, **AX9SS**, **AX9XI** (Christmas Island), **CR6CA**, **CT2AK**, **CX5BV**, **EA8BQ**, **EP2SW**, **FHØVP**, **HM5PF**, **HS1ACW**, **IS1DFO**, **KG6AAY**, **KL7FBK**, **KP4CH**, **KR6HB**, **KR8BY**, **KV4FZ**, **KX6HW** (Marshall Island), **KZ5AM**, **LU2DAW**, **LX1SD**, **MP4BFO**, **MP4MBB**, **OA8V**, **OD5BA**, **OX3LP**, **OJØDX**, **PJ9JR**, **PZ5RK**, **TA1TR**, **TU2CW**, **VP2VI**, **VP5HZ**, **VS6DO**, **ZB2BY**, **ZC4CB**, **ZE5JU**, **ZS6DH**, **3V8AL**, **5A5TH**, **5B4ES**, **5H3JL**, **5N2AAE**, **5V4JS**, **5Z4MO**, **6W8AL**, **7Q7BC**, **8P6BQ**, **9F3USA**, **9G1GD**. Perhaps I didn't connect that antenna after all.

N. Sanderson (Edinburgh), **CR45**, 200ft. long wire went s.s.b. spotting on 14MHz. Stations observed: **AP5HQ**, **AX2ARZ**, **AX3XJ**, **AX4HA**, **AX7GK**, **AXØLD**, **CE3BE**, **CR6MT**, **CR7GJ**, **CT3SC**, **DUIFH**, **EA8FS**, **ET3DS**, **GB3GWC**, **GC3VJX/OH5**, **HC2SO**, **HK3BCA**, **HR2HHP**, **JA10WT**, **K5ARJ**, **K6ZDP**, **K7TGF**, **KAIKSO**, **KH6OR**, **KL7EBK**, **KP4DHV**, **LU2HC**, **LX1RC**, **OJØDX**, **OX5BL**, **PJ9HH**, **PY7ACQ**, **PZ1BW**, **SU1MA**, **TA2AE**, **VE2BEO**, **VO1CA**, **VP7NA**, **VR6TC**, **W6TSC**, **W7IM**, **XE1YM**, **YA1EXZ**, **YB2AO**, **YK1AA**, **ZD8DB**, **ZE1DG**, **ZF1GC**, **ZL4CX**, **ZS2OF**, **ZS6IK**, **4U1ITU**, **4X4QA**, **5Z4UK**, **7Q7JO**, **7X2SMA**, **9M2PR**, **9Q5MP**, **9U5DP**, **9Y4US**.

R. Dinning (Ayrshire), **HA350**, **PR3OX**, **RQ10**,

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz ● Times in GMT

380ft. wire at 50ft., has spent a ten-week spell in hospital. It doesn't seem to have affected his skill with a receiver as his 21MHz log shows: **CR7GJ**, **EL1CA**, **EL2DU**, **EP2SW**, **HR1SR/P/HR2**, **HS1ACW**, **IRØIJ**, **KR6KB**, **KS6DH**, **OHØNJ**, **OJØDX**, **TU2CS**, **VU2IXP**, **W5YSL/P/DUI**, **XW8DM**, **XW8DS**, **YBØBD**, **ZD9BM**, **3V8AL**, **4U1ITU**, **5A5TH**, **5H3JR**, **5N2ABG**, **5Z4GK**, **6W8GE**, **6Y5GB**, **7P8AB**, **9F3USA**, **9L1GQ**, **9M2VI**, **9Q5WF**, **9V1PP**, **9X5AA**.

A. Crooks (Leicester), **RA1**, **PR30**, 45ft. end fed, heard **CR6IE**, on 14MHz, **CR6MX** and **9G1GT** on 28MHz while 21MHz s.s.b. brought: **EL2L**, **HØLL**, **PY2HY**, **PY7GAH**, **VU2KV**, **ZD8JK**, **ZS6AD**, **4Z4BG**, **5N2AAE**, **5U4JS**, **9J2PV**, **9U5DP**.

J. Moore (Leicester) claims that topband, eighty and forty were a dead loss this month and bemoans time-base QRM on 160 from local tele's. I reckon that's the transmission of spurious signals, report them to the GPO!

John's bets on 14MHz s.s.b. were: **CR6EV**, **OX5AP**, **PY2ELT**, **UL7JG**, **VR6TC**, **ZP5CF**. Fifteen metres produced: **CE3OE**, **CR6LG**, **JA1TRL**, **VE3GJU**, **4Z4DX**, **8P6BQ**. The gear is a **CR100/2**, a.t.u. and 130ft. end fed. Putting a home-brew f.e.t. converter in front and tuning 24.9—26.9MHz gave a.m.-type squeaks on 144MHz from: **G2JF**, **G2BKC**, **G3DAH**, **G3TDR**, **G3TXB**, **G3VCV**, **G3WRD**, **G8VZ**, **G8CKT/P** (Surrey), **G8AXZ**, **G8BJK**, **G8BPO**, **G8BYB**, **G8CIW**, **G8CQX**, **G8CRN**, **G8CUW**, **G8DAS**, **GC2FZC**. The same band but s.s.b. raised: **G2CIW**, **G3LQR**, **G3SOA**, **G6UW**, **PAØCML** (near The Hague).

A Garex converter feeding a **PR30** and **CR70A** from an 8-element Yagi is located at Wendover and the controls titivated by **N. Richardson**. A peep at 144MHz revealed the following stations: **G3AOS/P**, **G3LHO**, **G3LXP/P**, **G3PNA**, **G3PRM/P**, **G3TQF/P**, **G3UES/P**, **G3VPE/P**, **G6GN**, **G8BCQA**, **G8BDJ/P**, **G8CGX/P**, **GW3ITZ**, **GW3UCB**, **GW8ACG/P**, **GW8BEB/P**, **GW8BHY/P**.

V. Koopman (Lancs. but on holiday at Windsor), **RA1**, Joystick at 15ft., had some success on 7MHz (more success than I did I might warble). Dragged from the dreaded forty (still screaming) were: **AX9XI**, **CR9AK**, **FP8CS**, **HS1ABO**, **JW8MI**, **KJ6CF**, **SVØWO**, **UK3ABA**, **VQ8CZ**, **VR6TC** (Pitcairn Island), **VS6DO**, **W2HCW**, **YA1SG**, **7P8AB**, **9N1MM**—all on c.w. (splendid, splendid) except **W**, **7P8** and **9N1**.

The same gear on 21MHz raised: **CE6DP**, **FO8BW**, **GM3MNM/MM** near Capetown, **IRØXPS**, **JX8IL** (Jan Meyen Island), **KM6DQ**, **LU3AQ**, **TR8DG**, **VR2EK** (Fiji), **VR4EE**, **VU2BEO**, **ZD9BN**, **9G1GD**—all s.s.b.

Please note that the deadline for the month's logs is the 15th of each month, that is, they should reach me by the 15th. If they arrive later, they are too late for the current issue and "out of date" for the following one. So please slaves, letters to 5 Edward Close, St. Albans, Herts., before the 15th—Ta!

THE MW COLUMN

AS the evenings start to draw in, medium wave stations in North America can be logged as early as midnight. Among the first to be heard are an interesting group in Newfoundland right at the low frequency end of the band. There are three networks. The Canadian Broadcasting Corporation (CBC) operates CBT 540kHz in Grand Falls and CBN 640 St John's with satellites CBNA 600 St Anthony and CBNM 740 Marystown. There are two commercial networks. The Colonial Broadcasting System has key station VOXM 590 in St John's plus CHCM 560 Marystown and CKCM 620 Grand Falls. The Newfoundland Broadcasting Company can be heard on CJCN 680 Grand Falls, CJOX 710 Grand Bank and CION 930 St John's. All these stations are logged regularly in the UK. Others from the same area include CFCY 630 Charlottetown Prince Edward Island; CFDR 790 Dartmouth Nova Scotia; CJCH 920 Halifax N.S.; CHER 950 Sydney N.S.; CHNS 960 Halifax; CKBW 1000 Bridgewater N.S.; CBA 1070 Moncton New Brunswick; CBD 1110 Saint John N.B.; CKCW 1220 Moncton; CKEC 1320 New Glasgow N.S.; CKBC 1360 Bathurst N.B. Newfoundland Standard Time is 3½ hours behind G.M.T., the odd half hour being a help to station identification. The remaining Mari-

time Provinces are on Atlantic Standard Time which is 4 hours back. An unusual catch from this area which counts as a separate DX country, is Radio St Pierre 1375kHz in the French islands of St Pierre et Miquelon which lie to the south of Newfoundland. This station can often be heard when Lille 1376kHz signs off for the night at 2300 hrs G.M.T. The programmes from Radio St Pierre are in French and local time is 3 hours behind G.M.T.

Chris Stacey of Tunbridge Wells asks what sort of aerial is suitable for DXing on the Long Waves. At this QTH there is a 90ft long-wire at about 20ft above ground level and it performs very well when used with a CR100. Although a long outdoor aerial is an advantage on this band it is not essential. Dick Clark, a lw DXer in Florida USA has converted a standard m.w. loop for long wave use by increasing the number of turns from 7 to 20 and he regularly logs Europeans with it. Buzz from TV receivers may be troublesome with indoor aerials in some QTHs though this will disappear around midnight when the TV closes down. The long waves extend from 151kHz to 433kHz though only the section below 272kHz is in general use in Europe. There are some 50 Asiatics on this band situated in China, Mongolia, Turkey and asiatic USSR, and many can be logged in this country. Look for Ulan Bator 209kHz Mongolia; Tselinograd 227 Khazakistan; Dushanbe 254 Tadjakistan; Harbin 272 China; Ashkhabad 375 Turmenistan. Among semi-DX there is Tiflis 191 Georgia; Azilal 209 Morocco; Orenburg 300 USSR; Oulu 433 Finland.

Charles Molloy

DON'T MISS THIS!

WIN A **DECCA** (3000 SERIES)
SUITE OF HI-FI SEPARATES

**AUDIO FAIR COMPETITION
SPECIAL ENTRY FORM**


ONLY

IN THE **NOVEMBER** ISSUE
OF


PRACTICAL WIRELESS

ON SALE · OCTOBER 9TH.

GOING BACK...

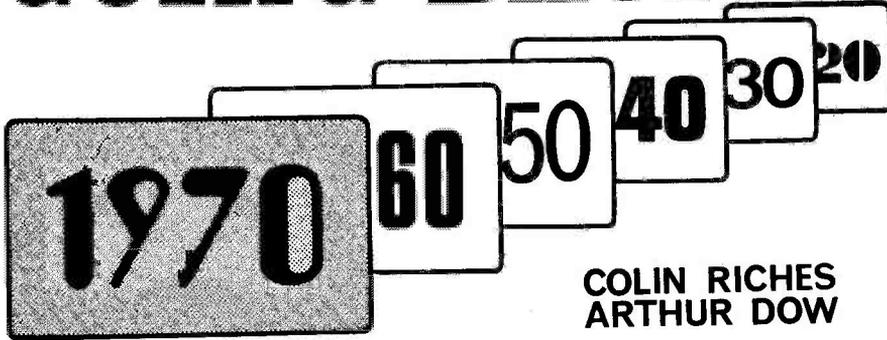

COLIN RICHES
ARTHUR DOW

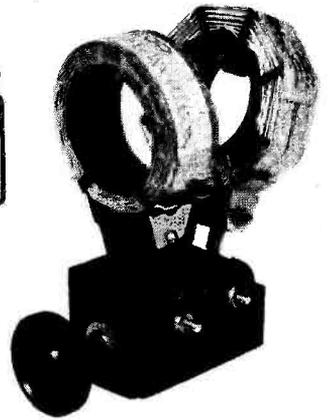


THE first type of spark transmitting equipment used a simple aerial circuit which included the spark gap. The best type of radiator was found to be an elevated aerial but the spark gap in series with it provided a high resistance and naturally a damping action. Therefore, the discharge began at a high initial voltage which soon died away to zero. After some time, another spark discharge would take place but in the meantime, there was no radiation from the aerial.



In the circuitry employing aerial coupling, the spark gap was included in a primary circuit; a separate tuned aerial circuit forming the secondary circuit. This latter was low resistance so that any oscillations induced could persist for a relatively long time before they finally died out. Thus for equivalent radiation compared with the plain aerial, the initial voltage would be lower, causing less strain on insulation but the increased radiation performance demanded less initial power. An added advantage was that the radiation covered a narrower waveband.

Marconi's first tuned transmitter (see photograph) was built in the year 1899. It comprised an oscillation transformer in the primary of which was a spark gap and capacitor. The secondary was connected to an adjustable inductor in the aerial circuit. The Marconi patent No. 7777 of the year 1900

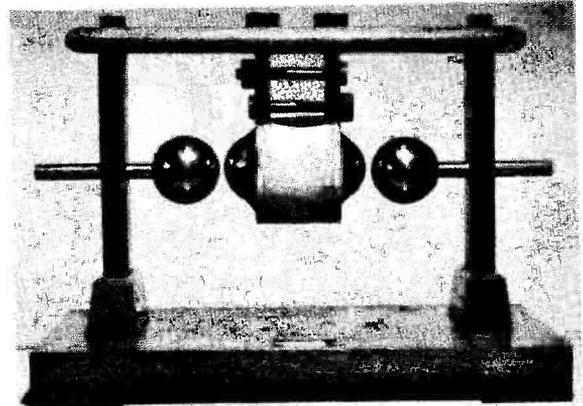was based on this design. It covered the later forms of tuned apparatus without which the famous "Atlantic transmission" of 1901 would have been impossible. This patent clearly specifies the tuning of four circuits, i.e. spark gap circuit, transmitter aerial and primary and secondary of the receiving transformer.



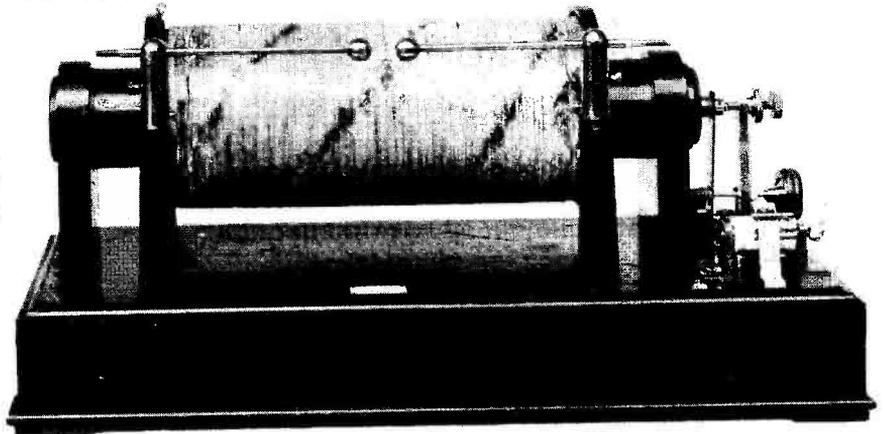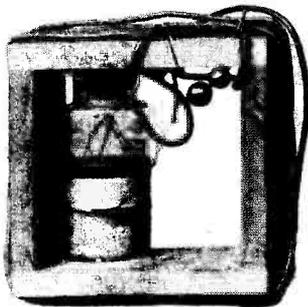Spark gap used by Marconi in his early experiments in the year 1895. Lent to the Science Museum, London, by Marconi Wireless Telegraph Co. Ltd.



Lent to the Science Museum, London, by Marconi Wireless Telegraph Co. Ltd.

Induction coil and tuning inductance of Marconi's first tuned transmitter (1899)

"A wireless penny-in-the-slot machine has been invented in America. The invention consists of an automatic apparatus surmounted by a revolving loop aerial, and takes its power from the lighting circuit supply. When the coin is inserted in the slot two valves are switched on, and the music is heard through a large horn at the bottom of the instrument." . . .

"A racehorse in America has been equipped with a receiver and trained to race by commands from the trainer." . . .

"Suggestions are made in the non-technical Press that by means of piezo-electric crystals London could be lighted by means of its noise. Piezo-electricity is the property possessed by certain crystals whereby they generate electricity when subjected to vibration." . . .

"Experiments in the flying of a pilotless wireless-controlled aeroplane will shortly take place in France." . . .

"There are now 350 broadcasting stations in the United States." . . .

"Experiments to determine the feasibility of reception of wireless signals by the sense of taste have recently been carried out. Silver electrodes were used, one of which made contact with the inner part of the upper lip of the operator and the other with the tip of his tongue. Using four-stage amplification, it was found possible to detect signals and to tune in a station by noting when the intensity of the taste sensation was maximum. For messages to be read, the speed must not be greater than ten words a minute." . . .

"A wireless receiving set has been installed in Buckingham Palace." . . .

"Among the many thousands of people who listened-in to the Prince of Wales's broadcast speech to the Boy Scouts of the nation were the blind soldiers of St. Dunstons. Captain Ian Fraser, the blind chairman of St. Dunstons, has been an ardent wireless experimenter for two years past, and in the course of a short address following the transmission, he stated that wireless telephony was opening a new world for the blind. A blind man's hobbies were limited, but wireless was one of those which he could pursue just as well as anyone else. In listening-in, he was at no disadvantage to those who could see." . . .

"Direct wireless communication between France and New York was established the week before last from the great wireless station at Saint-Assise." . . . August 19, 1922.

"It is rumoured that some enterprising firm has brought out a clothes line which has a stranded copper centre for use in cases where landlords object to aerials." . . .

"Is the doom of the gramophone in sight? A firm is now advertising: 'Why not have your gramophone converted into a high-grade wireless receiving set?' . . ."

During my early youth I had access to current numbers of the old "Model Engineer" and was fired by the rather brief articles on radio then in its infancy; I was born in 1893. V. W. Delves Broughton had described his own installation which featured all the primitive means available at the time, and when I began work on the railway in 1909 most of my spare time was occupied with my own version of the bits and pieces, improvised from materials to hand; I had not then seen any "real" radio apparatus.

In 1910 I joined the Cadet Unit of the K.R.R.'s, and was soon learning Army Signalling; by extraordinary good fortune I was picked in 1913; to attend a Radio Course at Marconi House (evenings) and so became acquainted with the real thing. I saw the Fleming valve, its De Forest improvement, and listened on the Marconi Multiple Tuner and Magnetic Detector, which I soon duplicated in my own way at home. The big rotary generators and 10in. spark coils were rather out of my sphere, and the noise and space required were all too obvious. I do wonder if P.W. can come across any others who attended these Cadet Courses?

1914 found me in uniform seriously, putting my earlier signal training to practical use. As Signal Sergeant of my unit we dabbled on the fringe of radio but few infantry units had the opportunity to use it in action. I heard my first Radio speech when visiting Div. H.Q. just after the Armistice.


I obtained my first Radio Receiving licence in November 1919 in the form of a letter from the G.P.O., and have been a listener ever since.

In North London we formed the North Middlesex Radio Club, which had as the "motto" on the badge: "Listen before sending and so avoid jamming" and our Secretary, Mr. Savage of Winchmore Hill, was a fine enthusiastic character who did great work for us. I moved away to Stevenage in 1922 and found only one radio aerial in the locality, at the hamlet of Todds Green. My own soon went up—I had sold my 30 foot London mast to Arthur Burrows who later became a notable figure in Radio on the organising side; he was the Secretary of the International Organisation.

I had bought No. 1 of *The Wireless World*, and in due course followed with No. 1 of *Practical Wireless* and every other radio paper which appeared and disappeared; I am still faithful to *PW* which has given me much food for thought and had set a fine pattern, if not always "snooty" enough for some.

I am now approaching my 77th birthday, and still dabble, listening over most of the bands, broadcast and otherwise. I was able to do a bit in the Home Guard, and shared the consternation when on official orders we were not able to try out the C.52 sets issued and withdrawn almost at once. Of course I still read Morse, am a sort of unofficial honorary member of the Stevenage Radio Society, who keep the flag flying in this part of the country. But you can imagine I look back and think how very fortunate I was to get that Course of Instruction during 1913/14 at Marconi House when things were still in their infancy.

B. G. ASHMAN,
(Stevenage, Herts.).

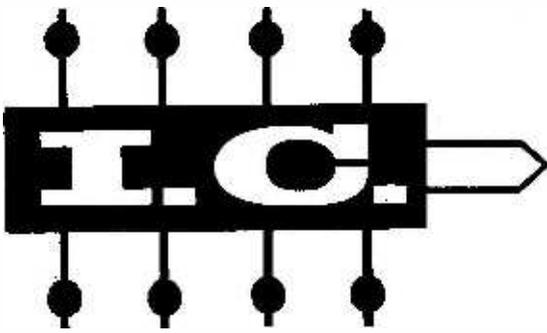

OF THE MONTH

L.A.J. IRELAND

Number 12 Motorola MFC 4010P/Mullard TAA263 Utility Amplifier

WHEN two separate manufacturers in two continents introduce very similar products within a short time, clearly a definite demand has been identified; and even a cursory examination of the circuit diagrams will establish the basic identity of the Motorola MFC4010P (and the Mullard TAA263) mentioned last month.

Application

The application is also clear, as a small signal utility amplifier or "gain block" for industrial or consumer electronic systems. This function is frequently required, so that an integrated unit which eliminates the chore of designing and assembling discrete transistor units will be very welcome.

Performance

The performance of the units extends from d.c. to greater than 1 MHz, a limit which is established by the stray capacitances in the circuit, which degrade gain and introduce phase shifts. However, this still permits the circuit to be described as a wide band unit, i.e., not limited to industrial applications in servomechanisms handling switching or d.c. levels, or to consumer applications in the audio field. It can function, for example, as a fairly effective video amplifier, and indeed, with suitable tuned circuits as an a.m. i.f. amplifier or even as a t.r.f. radio receiver.

One objection may be raised to the circuits as illustrated, Fig. 1. It may be claimed that the base-emitter junction of Tr2 effectively short-circuits

the collector of Tr1, and similarly with Tr2 shunting the output of Tr3. However, it should be remembered that the integrated circuit manufacturing process pre-supposes the use of silicon, and whereas in germanium transistors the 0.2 volts, typical of a base-emitter junction, would indeed bottom the preceding stage, in silicon this junction establishes a potential of approximately 0.7 volts while the bottoming collector voltage is lower. The designers are quick to exploit this feature of the physics of silicon.

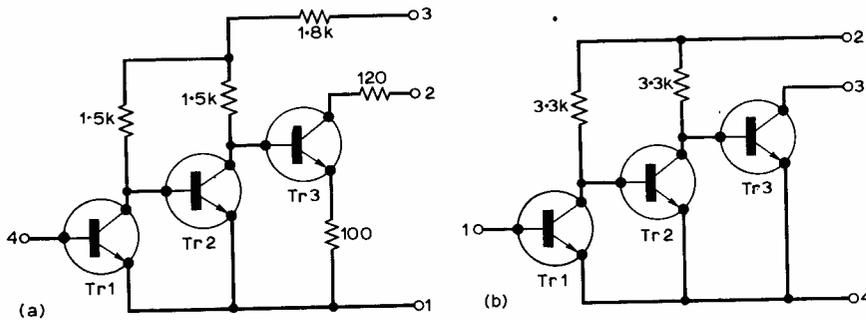


Fig 1 : (a) Circuit of MFC4010P and (b) of the TAA263.

On this point of ubiquity, in the July 1970 *Practical Wireless*, page 195, C. F. Fletcher describes a hybrid transmitter modulator incorporating a "ring of three" direct coupled audio gain stage identical to the integrated units we deal with this month; the same issue features a reverberation unit with an acoustic delay system requiring small amplifiers in conjunction with the input and output transducers; finally there is an account of a light-operated switch indicating the application of a d.c. amplifier, a function for which this month's circuits are ideal. No doubt other issues of this magazine would contain a similar series of projects in which a small signal gain function is required.


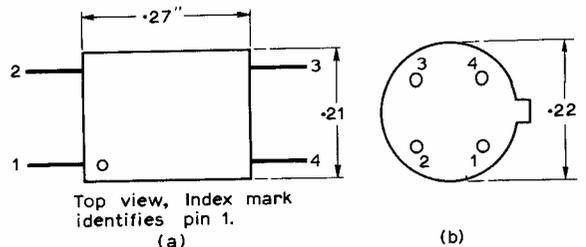



Fig 2 : (a) Connections of MFC4010P and (b) of TAA263.

In a practical application of a "ring of three" direct-coupled transistor amplifier subsystem, the operating conditions are set and stabilised by d.c. feedback, i.e. the base bias of Tr1 is drawn through a suitable resistor network from the output of the block.

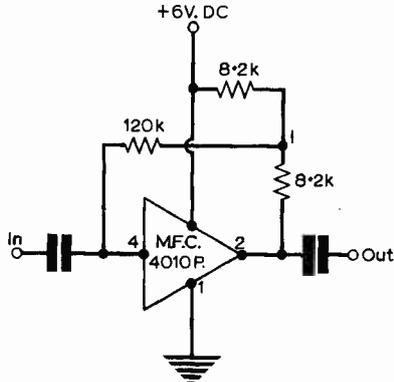Open loop voltage gain for both units is some 70 dB; it is usual to incorporate in the d.c. feedback loop some reactive elements (inductors or capacitors) to determine the amplifier passband and the actual gain realised.



(a) A.F. Low level amp.

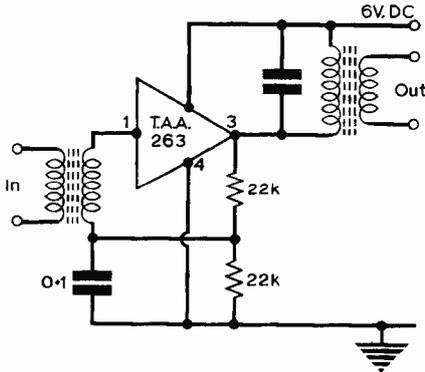

(b) Tuned amplifier (R.F. or I.F.)

Fig. 3 : (a) Circuit as A.F. amplifier.
(b) Circuit as R.F. or I.F. amplifier.

The cost of fabrication of a simple i.c. chip is only slightly greater than that of a good discrete transistor, and the yield, or fraction of satisfactory devices, is not much lower. Packaging is a different matter, though, since the typical i.c. requires more manual attention at this stage. Hence the advantage of this month's i.c.'s, in that both are supplied in simplified four terminal packages, requiring only signal input and output, and power leads.

Connection identification is possible by reference to Fig. 2, and the test circuits, Fig. 3, indicate the approach to the incorporation of one of these units in an actual project.

Constructors may obtain the Mullard units from advertisers in this magazine, while the Motorola i.c. is in stock at the U.K. distributors: Celdis Ltd., 43-45 Milford Road, Reading, Berks.; or Semicomps Ltd., 5 Industrial Estate, Beresford Avenue, Wembley, Middx. ■





Readers of
Practical Wireless are
invited to submit articles for
publication and to compete
for the
Practical Wireless
"Designer's Trophy"

RULES.

1. Articles submitted for the competition should conform to the general style of material published in *Practical Wireless* and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
2. Articles should, preferably, be typed using double spacing, leaving wide margins, and on one side only of each sheet. Circuit diagrams and any other drawings should be on separate sheets and numbered to agree with the text. Author's roughs must be clear enough to permit re-drawing. Component lists must also be separate and laid out to the standard PW format.
3. Photographs of the equipment are desirable and should be in black and white, sharp and clear. Each photograph should be identified by sticking a piece of paper on the back rather than by writing on the photograph itself.
4. Components used in the design must be readily available from retail sources.
5. An entry form, properly completed, must accompany each article submitted. There is no limit to the number of articles submitted by any one author.
6. Articles must reach the Editor, *Practical Wireless*, Old Fleetway House, Farringdon Street, London, E.C.4. by the first post on Monday, November 2nd 1970 with the envelope and title sheet clearly marked "Project Autumn". A stamped, self-addressed envelope must accompany each entry.
7. All entries submitted will be considered by a panel of judges and the Editor's decision on all matters arising will be final. The Editor will require authors of winning entries to submit the equipment to him immediately on request for final assessment by the panel.
8. Employees and staff of *Practical Wireless* are not eligible for entry to this competition.
9. The winner of the competition will receive and retain outright the *Practical Wireless* "Designer's Trophy 1970". Other prizes will be awarded to the best runners-up. Any article published will be paid for at normal rates.

ENTRY FORM
PAGE 437

TRANSISTOR

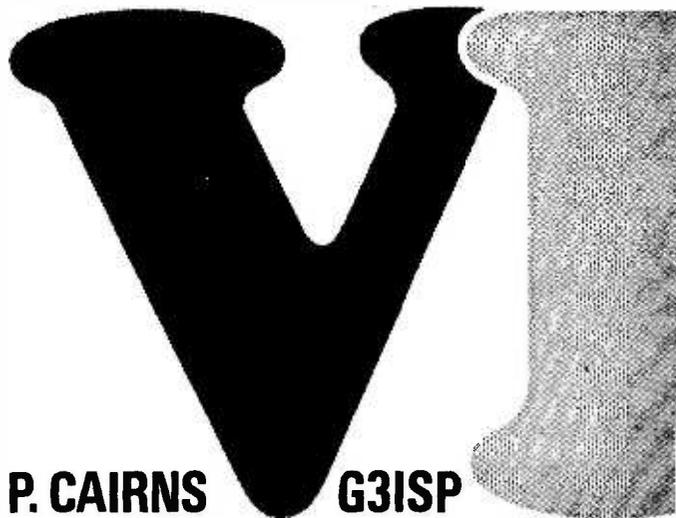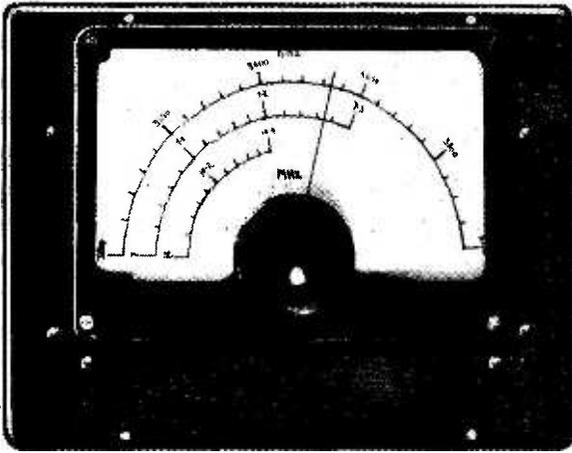

P. CAIRNS G3ISP

THIS article describes a relatively simple transistor v.f.o. unit, suitable for use with most amateur transmitters. Its basic merits are an extremely stable, low drift characteristic for large changes in temperature, supply volts, and over long periods of time and almost constant amplitude output over the frequency range together with a cheap and simple construction.

Specification

The v.f.o., whose complete specification is given in Table 1, was given most stringent tests, particularly with regard to frequency drift and stability, all frequency measurements being made on a digital frequency meter with a discrimination of ± 1 Hz. The results of these tests are shown graphically in Table 2. From these curves it can be seen that even under extreme changes in parameters, the frequency drift was always well under 100Hz or better than 0.003%. As the tuning capacitor represents only a small part of the total capacitance, the oscillator only covers the required frequency range, that is 3.5 to 3.8MHz. This means a large open scale and

almost linear divisions in calibration. With a scale radius of 2½in. (scale length of about 7in.) each 10kHz occupies approximately ¼in. Amplitude stability is maintained by an effective control circuit which does not employ a thermister with its attendant time lag. Supply is 24V d.c., though this is not at all critical, while the current drain is less than 50mA.

The complete unit is housed in an 8in×6in×6in case, co-axial output being taken from the rear. The output impedance is extremely low, thus allowing the unit to drive transmitters having a wide range of input impedance.

The Circuit

The complete circuit diagram, together with component list is given in Fig. 1. Basically the circuit comprises a modified Butler oscillator with emitter follower output. Tr1 and Tr2 form the oscillator circuit with Tr3 as an emitter follower output. L1, VC1, VC2 and C1 determine the frequency of oscillation, the output from Tr2 being d.c. coupled to Tr3. This stage provides isolation between the oscil-


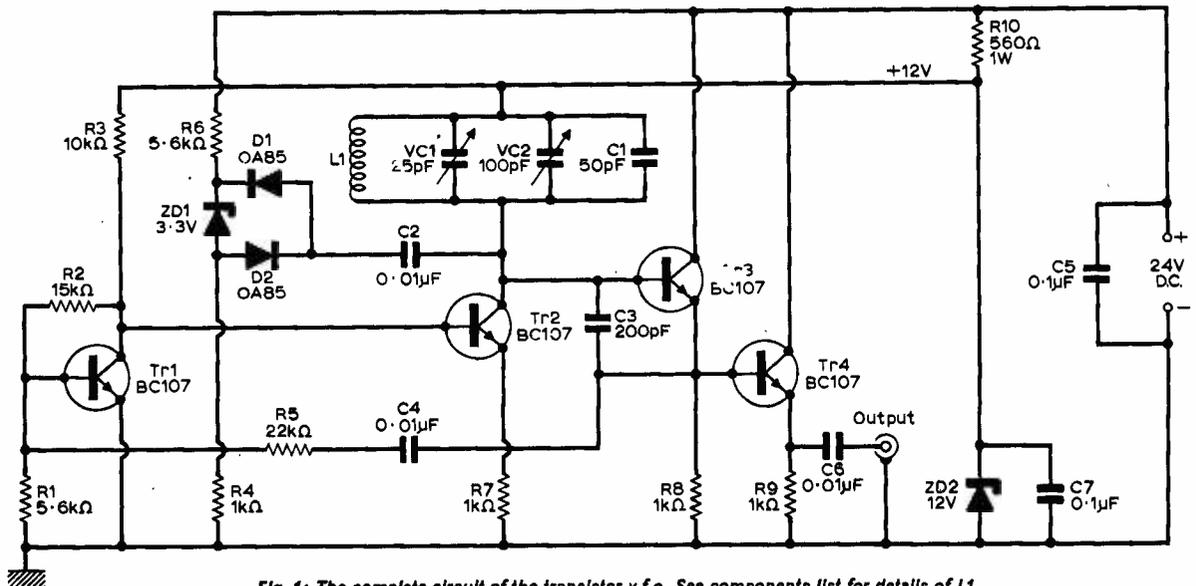


Fig. 1: The complete circuit of the transistor v.f.o. See components list for details of L1.

SPECIFICATION

Frequency Range	3.5MHz to 3.8MHz fundamental (approx.)
Frequency Stability	After 10 mins warmup Temperature 15°C to 60°C: less than 100Hz or 0.003% Supply volts 15V to 30V: less than 30Hz or 0.0009% Over a six hour period: less than 10Hz or 0.0003%
Output	Minimum 5V peak to peak. Amplitude stability over frequency range better than 1dB. Output impedance less than 200Ω
Supply	Nominal 24V d.c. Current drain less than 50mA
Dimensions	8in. x 6in. x 6in.

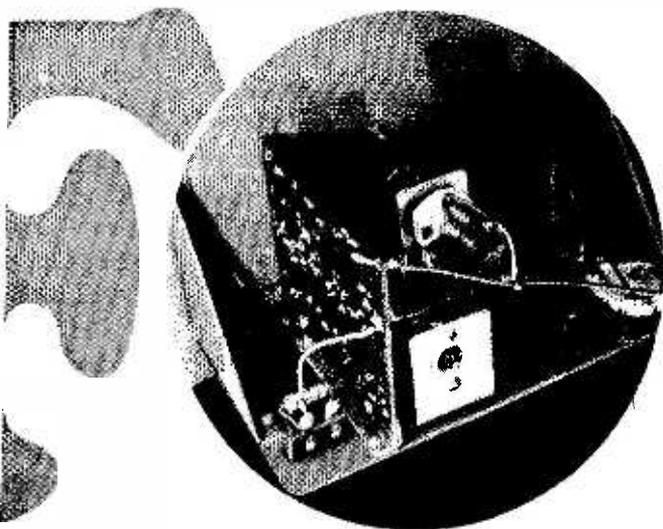

lator and feedback amplifier Tr1. The output developed across emitter load R8 is applied via the feedback components C4 and R5 to the base of Tr1. The output from this transistor is d.c. coupled back to the base of Tr2. Negative feedback is applied to Tr1 via R2 which, in conjunction with R1, determines the effective level of oscillator feedback.

The output stage, Tr4, is also an emitter follower, d.c. coupled from the emitter of Tr3. This stage ensures isolation between the output and oscillator circuit and also provides a low output impedance, C6 providing d.c. blocking to the output terminal. Two levels of supply line are used, 24V and 12V, the 12V being obtained via R10 and ZD2. The output emitter followers are supplied from the higher voltage line, thus ensuring adequate signal swing without clipping and allowing d.c. coupling to be easily achieved.

The amplitude stabilization circuit is formed by components ZD1, D1 and D2. The oscillator output is coupled via blocking capacitor C2 to the diodes D1 and D2. The voltage across the zener diode ZD1 is maintained via the resistor dividers R4 and R6, these being connected across the main d.c. supply. The rectified signal output from diodes D1 and D2 is therefore constantly compared against the fixed zener voltage. Changes in oscillator level are converted to d.c. and simply registering as variations in zener current, the voltage across which is always constant and therefore provides a constant reference for the signal source. Decoupling of the supply lines is provided by C5 and C7.

Construction

The construction of the v.f.o. is quite straightforward and can best be followed from the photographs shown. All components except the tuning and trimming capacitors, coil and C5, are mounted on a piece of Veroboard 4in. x 3in. The complete Veroboard layout is shown in Fig. 2. This is completed first and then fixed vertically on the chassis by means of a small aluminium bracket.

The chassis is simply an aluminium plate with a small right-angle lip bent along the front edge for fixing to the front panel. Side brackets, with lips bent in for fixing the front panel to chassis are


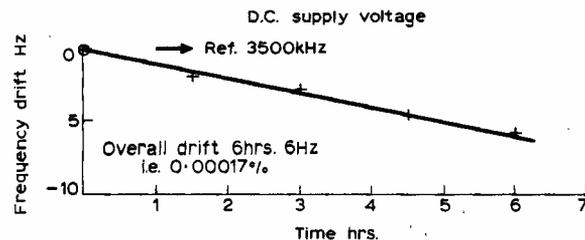
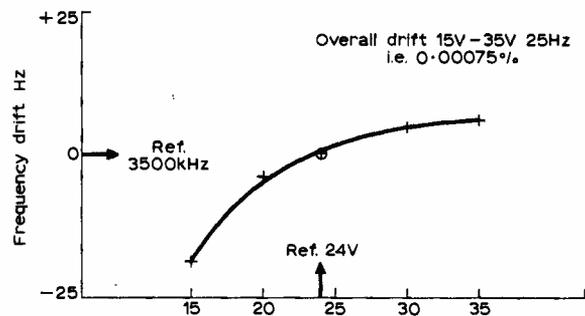
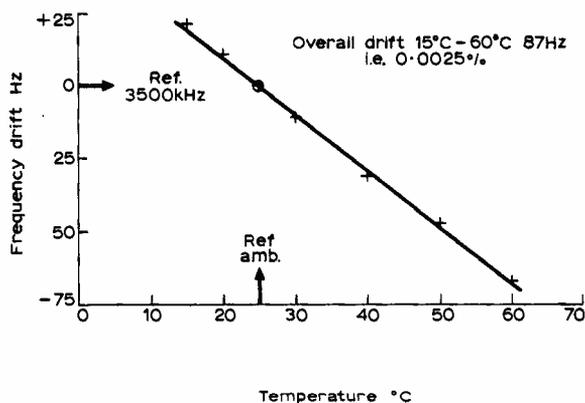


Table 1 (top): gives the specification of the v.f.o. while the graphs in Table 2 demonstrate the stability of the unit with regard to temperature supply voltage and time.

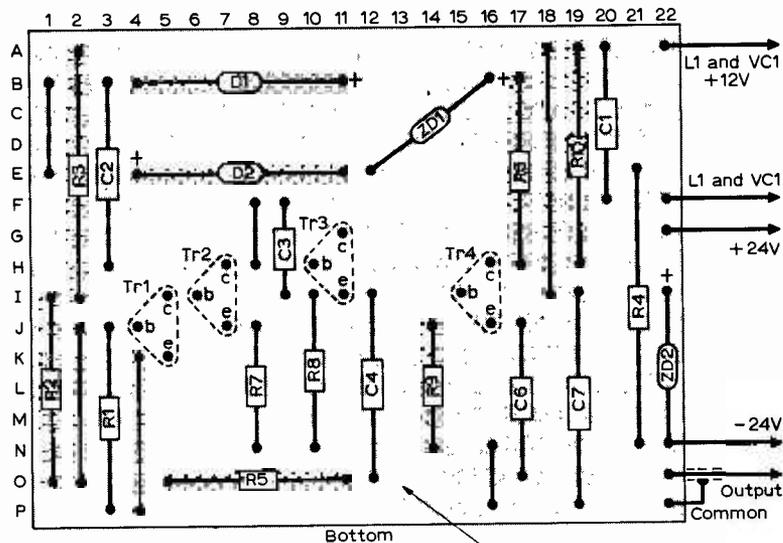

Looking at copper side of board, matrix 0.15" Break in conductor

also used as mechanical rigidity is of major importance for optimum frequency stability. Layout is clearly indicated in the photographs.

Also mounted on the chassis are the tuning capacitor, trimming capacitor and coil. The wiring between these components and the Veroboard is all of 18s.w.g. tinned copper and should be as short and direct as possible, mechanical rigidity again being of first importance. The output co-axial socket is mounted on a small bracket on the rear of the chassis and close to the Veroboard, thus ensuring

★ components list

Resistors:

R1	5.6k Ω	R6	5.6k Ω
R2	15k Ω	R7	1k Ω
R3	10k Ω	R8	1k Ω
R4	1k Ω	R9	1k Ω
R5	22k Ω	R10	560 Ω 1 watt 10%
All resistors $\frac{1}{2}$ watt, 5% except R10			

Capacitors:

VC1	25pF air-spaced variable, ceramic mounting (Jackson Code JB/804/3-3/25)
VC2	100pF ceramic trimmer
C1	50pF silver mica
C2	0.01 μ F polyester
C3	200pF silver mica
C4	0.01 μ F polyester
C5	0.1 μ F polyester
C6	0.01 μ F polyester
C7	0.1 μ F polyester

Semiconductors:

Tr1	BC107	ZD1	3.3V zener, BZY88-C3V3 Mullard
Tr2	BC107	ZD2	12V zener, BZX61-C12 Mullard
Tr3	BC107	D1	OA85 Mullard
Tr4	BC107	D2	OA85 Mullard

Coil:


25 turns, close wound on 1 $\frac{1}{2}$ in. diameter former, 18 s.w.g. enamelled copper wire

Miscellaneous:

Veroboard, 0.15in. matrix, 22 x 16 holes; Transistor heat sinks; Co-ax. socket; Two-way tag strip; Slow motion drive assembly; Chassis 8in. x 6in. x 6in. from H. L. Smith & Co, type W.

Fig. 2: (left) The component layout on Veroboard.

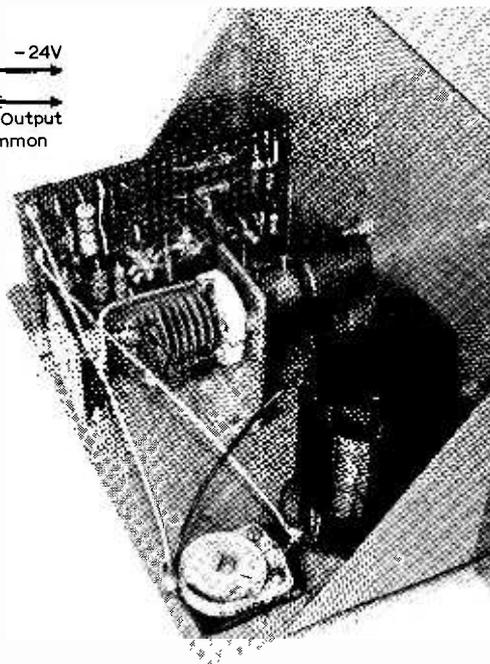(Below) The layout of the v.f.o. can be clearly seen from this photograph and the heading illustration.



short output leads. On the outer side of the Veroboard is the two-way tag strip for the incoming d.c. supply, C5 is connected across these tags, thus decoupling the main supply at its entry point. The negative side of the supply is taken to chassis via the common fixing contact on the tag strip.

The front panel should be drilled to take the particular type of slow motion drive and dial assembly before being fixed to the chassis and side brackets. The tuning capacitor VC1 is mounted on a bracket of suitable height so as to engage with the slow motion drive shaft. This capacitor should be of the ceramic mounting type as with this circuit both sets of vanes must be isolated from chassis.

Holes should be drilled in the rear of the cabinet to allow for the entry of the co-axial plug and supply leads, these being taken through a grommet. While the size of the cabinet used by the writer is specified, being readily available, any similar type of case or cabinet which is already to hand may be used.

Calibration

The ideal instrument for calibrating the v.f.o. is of course a digital frequency meter. As such instruments are seldom available to the average amateur,

—continued on page 477

Organ pedal bass unit

PART 2

A. LESTER-RANDS

THE main note generator is a simple multi-vibrator, Tr1 and Tr2, Fig. 11, with the base of Tr2 taken to the negative rail via the tuning pre-set potentiometers PR1 to PR13 and VR1/R17 and R18. The pre-sets, PR1 to PR13, are used to tune the multi-vibrator to cover one complete octave in tempered scale from C (65Hz approx) to C (130Hz approx).

The potentiometer VR1 will shift the overall pitch up or down by a full interval (one whole note) so that the unit can be tuned instantly to instruments not tuned exactly to concert pitch. The output from the multi-vibrator provides the fundamental notes for the 8ft. pitch and is taken directly to the tone forming network C23, L1 and C24 which provides the 'flute' voicing. The capacitors C25 and C26, together with the resistors R40 and R43 provide the 'clarinet' voicing.

The output from the multi-vibrator simultaneously drives the divider circuit Tr3 and Tr4 which provides the fundamental notes for the 16 ft. pitch. The output from the divider is taken via the flute voicing

network R14, C10, R15 and C11 and then via S1 and R16 to the buffer amplifier Tr9. The voiced outputs from the 8ft. pitch voicing network are switched via S3 and R45 to Tr9 base. The switches S1 and S3 allow a choice of 8ft. flute (or clarinet with S4 closed) or 16ft. flute (or clarinet with S4) or both i.e., the 8 and 16ft. pitches combined.

The signal output from the buffer amplifier is approximately 1V r.m.s. with the output gain control VR2 at maximum.

Drum Brush Circuit

The drum brush sound is generated when any pedal is depressed either momentarily or continuously. The brush sound begins with a medium degree of attack and decays away in approximately 1 second depending on the setting of the pre-set potentiometer PR14. A four notes per bar pedal bass will therefore produce a four beats per bar brush rhythm. The brush rhythm can be switched on or off as desired.

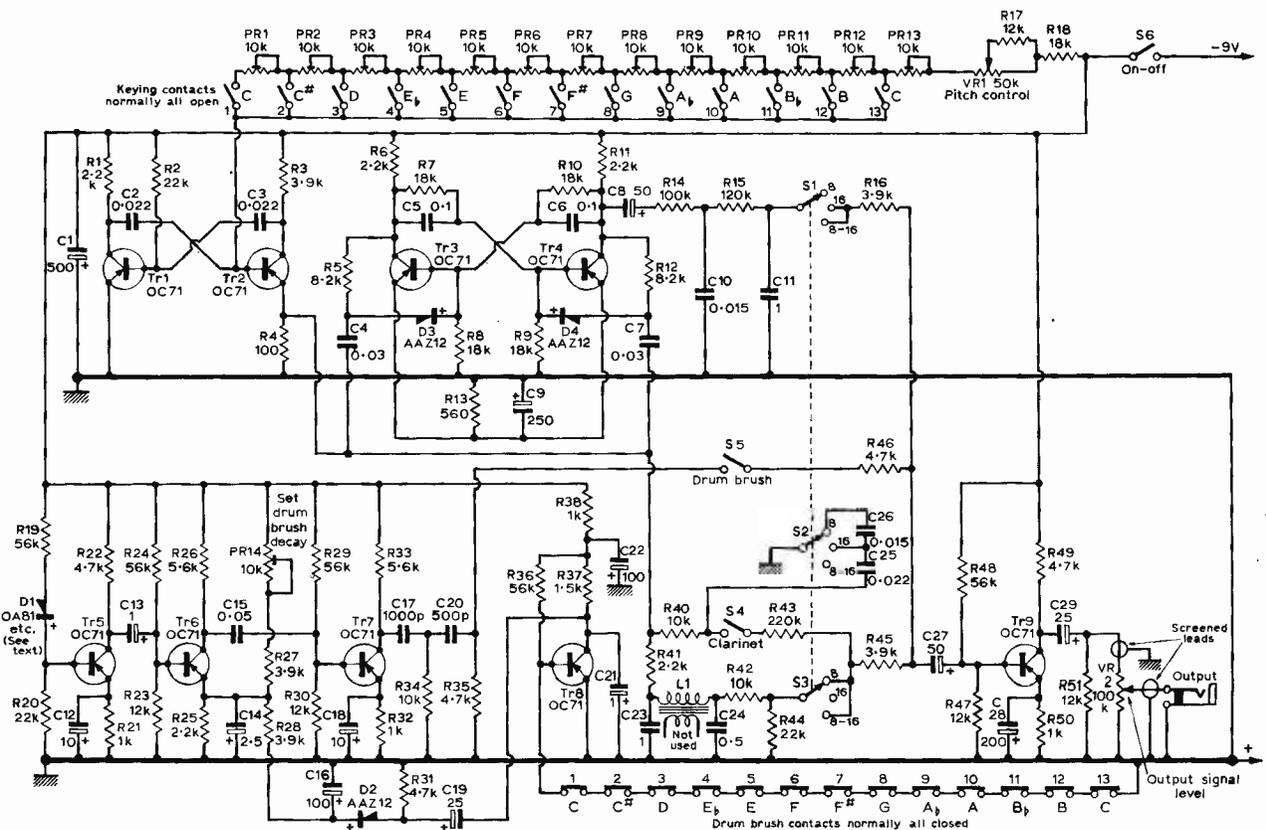



Fig. 11: Complete circuit of the Organ Pedal Bass Unit.

The circuit for the drum brush sound consists of a noise generator (D1, Tr5, Tr6, Tr7) and the attack/decay control circuit (Tr8). The choice of a diode for D1 may require some trial and error as a 'noisy' diode is required i.e., one that generates most noise when current is passed through it.

There should be at least 500mV of white noise from the collector of Tr7 (junction C17 and C20) with Tr6 conducting i.e., with PR14 at maximum resistance. An oscilloscope should display a typical spiky noise signal of about 1V peak to peak.

The function of the attack/delay control is as follows:— With PR14 set to maximum resistance constant noise should appear at the output of the unit. Adjust PR14 until Tr6 is just cut off in which case the continuous noise signal will cease. The function of Tr8 is to provide a positive pulse to the emitter of Tr6 when any of the contacts 1 to 13 (drum brush contacts in Fig. 10 Part 1) are opened.

The control transistor Tr8 is normally cut off but conducts rapidly when any of the contacts 1 to 13 are opened. The result is a fairly large pulse at the collector of Tr8 which is rectified by the diode D2 and charges C16. The charge on C16 allows Tr6 to conduct instantly, thus initiating the 'attack' but the charge then dies away slowly via R28 and R25 thus providing the 'decay' of the brush noise. The decay time will be about 1 second with PR14 adjusted so that Tr6 is only just cut off. Decreasing PR14 resistance so that Tr6 is beyond cut off will produce a much shorter decay time to the brush sound.

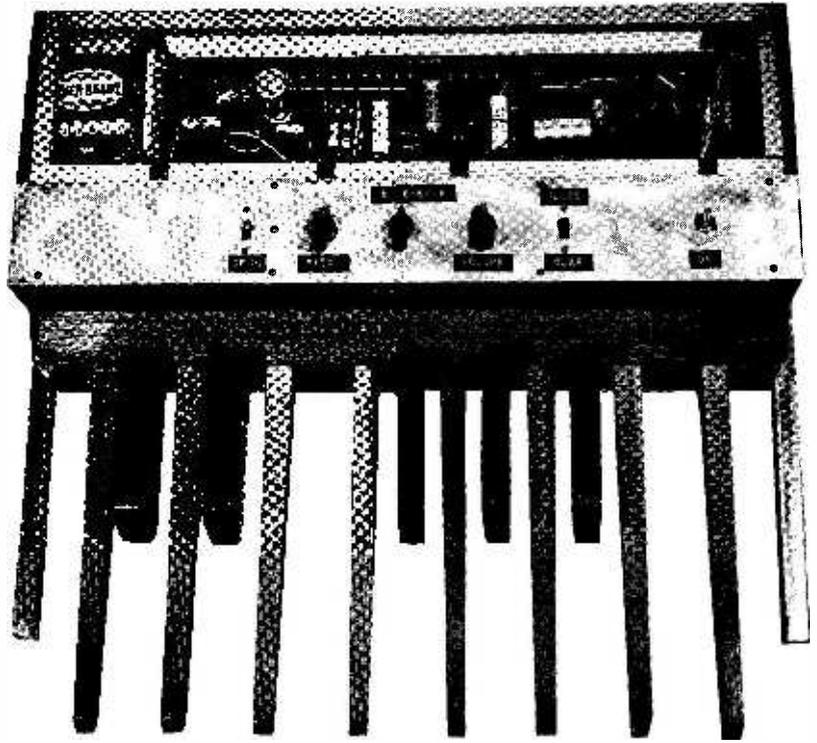

Top view of the completed unit.

The total current consumption of the whole unit with any pedal depressed and the drum brush circuit switched on should not exceed 25mA. It is therefore quite economical to run the unit from a 9V (PP9) battery. There is no reason why a small mains unit should not be used but the smoothing capacitor should be at least 5000 μ F. to keep hum level to an absolute minimum.

Circuit Boards and Panel Controls

The tone generator, divider and voicing networks are assembled on Board A as in Fig. 12. The pre-set tuning potentiometers PR1 to PR13 should be

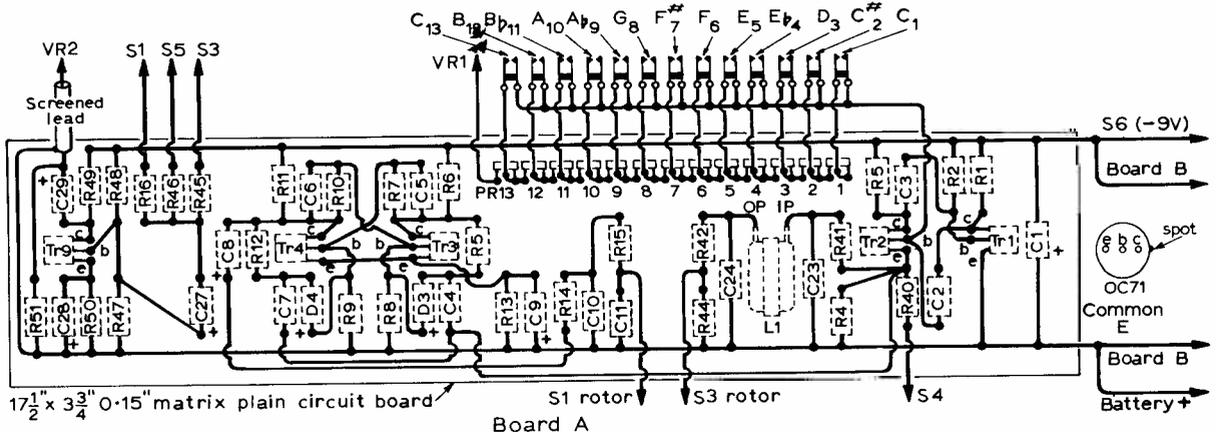



Fig. 12: Layout of circuit Board A for the tone generator, divider and voicing networks.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

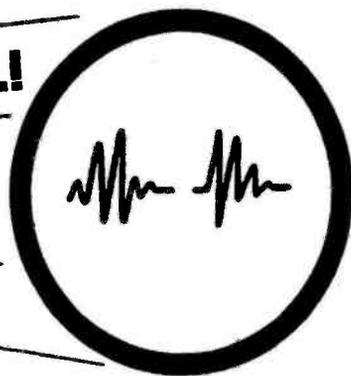


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

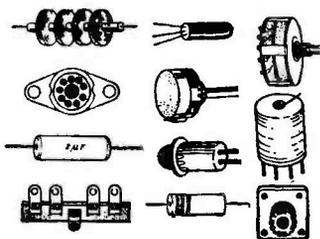complete range of present-day **ELECTRONIC PARTS and COMPONENTS**




2 ▶ BUILD and USE

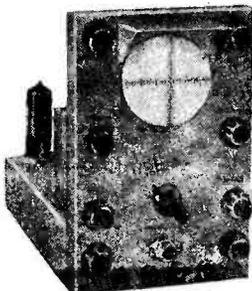a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND CIRCUIT DIAGRAMS

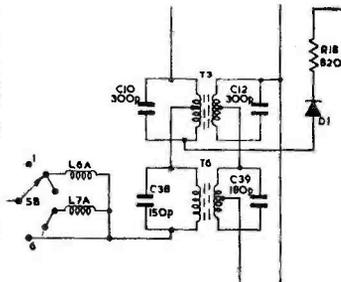

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE


or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.W. 10

DISCOSOUND

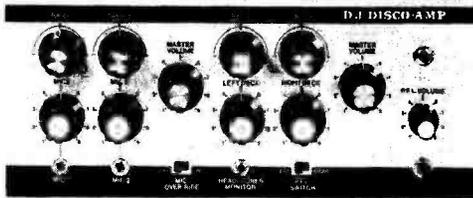

D.J. DISCO-AMP

Designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

A complete Pre-fade listen (P.F.L.) cueing monitor section is featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half.

Specification: Output power 70 watts R.M.S. \pm 1db at 8 ohms. Frequency response: 30-20,000 Hz \pm 3db. Harmonic distortion: Less than 1% at full output. Signal/noise ratio: Better than -65db. Inputs: Mic 1 & 2.5 mV at 50 K ohms. Turntable 1 & 2 100mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost. Size: Front Panel 16 $\frac{1}{2}$ in \times 7in. Cut out 15 $\frac{1}{2}$ in \times 6in. Fuses A.C. 1.5 amp (B.S.) mounted on back panel.

PRICE £85.0.0 inc. P & P.




D.J. 102 DISCOTHEQUE MIXER PRE-AMPLIFIER

Consists of a 4 channel mixer each with its own volume control and a complete P.F.L. monitoring system. Also features a mike cut down switch. For use with amplifiers having tone controls but not having the above facilities. Frequency response 20-20,000 Hz \pm 2db. Distortion less than 1%. Signal to noise ratio better than -65db. Size 10 $\frac{1}{2}$ in \times 4in \times 4in. Self powered.


PRICE £25.0.0 inc. P & P.

DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

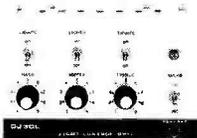3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested



PRICE £37.10.0 inc. P & P.

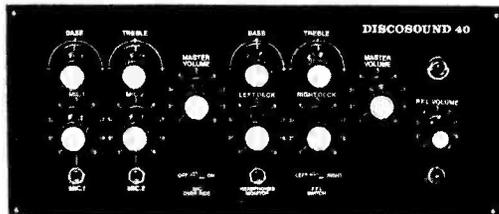

DISCOSOUND 40 PRE-AMP

The Discosound 40 offers the same specification as the D.J. Disco Amp without the power output stage. Size 16in \times 7in \times 7in. Self powered and ideal for use with the Discosound 100 Power Amplifier below and one of the outstanding features is that it is capable of running ten of these Power Amplifiers (Total 1,000 watts)


PRICE £40.10.0 inc. P & P.

DISCOSOUND 100 POWER AMPLIFIER

A 100 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000 Hz \pm 2db. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound 40, or can be used with any other high quality pre-amp control unit. Completely built and tested on steel Chassis.

PRICE £49.10.0 inc. P & P.

DJ 70S INTEGRATED MIXER-AMPLIFIER

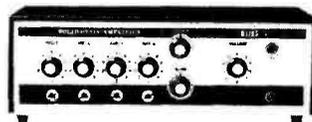

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70 watts R.M.S.) a frequency response (30-20,000 Hz \pm 3db) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs etc., or anywhere that high quality high output is required. Size: 15 $\frac{1}{2}$ in \times 5in \times 6in.

PRICE £55.0.0 inc. P & P.

Also available DJ105S 30 watt P.A. Amplifier. Similar specification to above.

PRICE £35.0.0 inc. P & P.

For full details of these and all Discosound Products write direct to:—

DISCOSOUND, 122 BALLS POND ROAD, LONDON, N.1. Tel: 01-254 5779

Full money back guarantee if returned within 10 days.

All Discosound Products are guaranteed for 12 months.

Demonstrations given at any time.

Control panel - 18 s.w.g. aluminium $21\frac{1}{2}'' \times 2\frac{7}{8}''$

As viewed from front

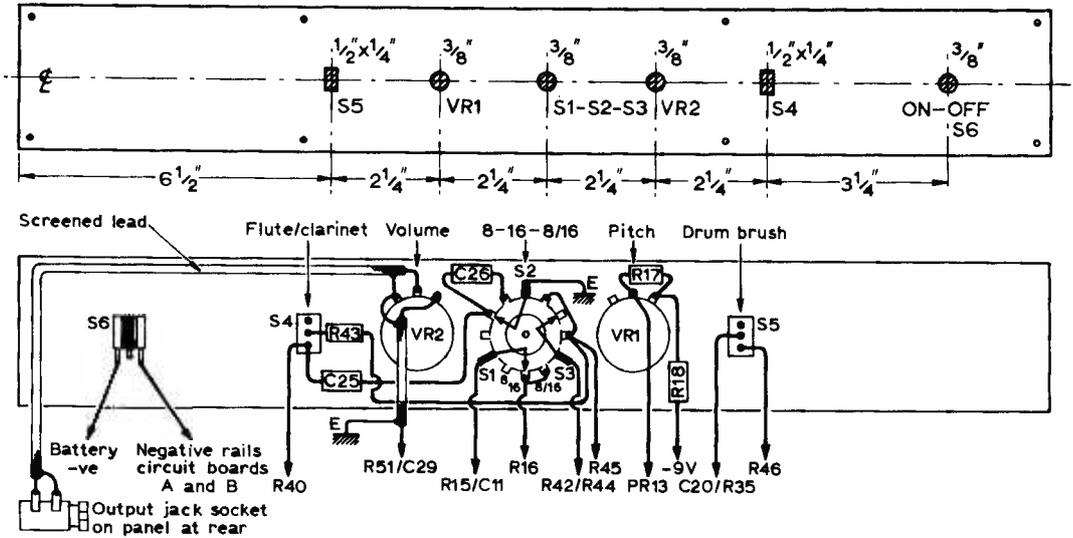


Fig. 13: Details of the layout and wiring of the control panel.

★ components list

Resistors :

R1 2.2k Ω	R14 100k Ω	R27 3.9k Ω	R40 10k Ω
R2 22k Ω	R15 120k Ω	R28 3.9k Ω	R41 2.2k Ω
R3 3.9k Ω	R16 3.9k Ω	R29 56k Ω	R42 10k Ω
R4 100 Ω	R17 12k Ω	R30 12k Ω	R43 220k Ω
R5 8.2k Ω	R18 18k Ω	R31 4.7k Ω	R44 22k Ω
R6 2.2k Ω	R19 56k Ω	R32 1k Ω	R45 3.9k Ω
R7 18k Ω	R20 22k Ω	R33 5.6k Ω	R46 4.7k Ω
R8 18k Ω	R21 1k Ω	R34 10k Ω	R47 12k Ω
R9 18k Ω	R22 4.7k Ω	R35 4.7k Ω	R48 56k Ω
R10 18k Ω	R23 12k Ω	R36 56k Ω	R49 4.7k Ω
R11 2.2k Ω	R24 56k Ω	R37 1.5k Ω	R50 1k Ω
R12 8.2k Ω	R25 2.2k Ω	R38 1k Ω	R51 12k Ω
R13 560 Ω	R26 5.6k Ω	R39 Not required	

All resistors $\frac{1}{4}$ W 10%

PR1-14 10k Ω pre-set potentiometer. (Sub-miniature carbon skeleton type.)

VR1 50k Ω carbon potentiometer, linear.

VR2 100k Ω carbon potentiometer, log.

Capacitors :

C1 500 μ F (elec)	C11 1 μ F (paper)	C21 1 μ F (elec)
C2 0.022 μ F	C12 10 μ F (elec)	C22 100 μ F (elec)
C3 0.022 μ F	C13 1 μ F (elec)	C23 1 μ F (paper)
C4 0.03 μ F	C14 2.5 μ F (elec)	C24 0.5 μ F
C5 0.1 μ F	C15 0.05 μ F	C25 0.022 μ F
C6 0.1 μ F	C16 100 μ F (elec)	C26 0.015 μ F
C7 0.03 μ F	C17 1000pF (cer)	C27 50 μ F (elec)
C8 50 μ F (elec)	C18 10 μ F (elec)	C28 200 μ F (elec)
C9 250 μ F (elec)	C19 25 μ F (elec)	C29 25 μ F (elec)
C10 0.015 μ F	C20 500pF (mica)	

All capacitors at least 12VW

Semi-conductors :

Diodes D1 (see text). D2, 3, 4 AAZ12 (Mullard)
Tr1—Tr9 OC71 (Mullard)

Switches :

S1, 2, 3 3 pole, 3 way, ganged wafer type.
S4, 5 Single pole, on-off, slide type.
S6 Single pole, on-off, toggle or slide type.

Miscellaneous :

Aluminium panel $21\frac{1}{2}'' \times 2\frac{7}{8}''$ in. 18 s.w.g. Inductor L1 (Type CP6713/2, Henrys Radio Ltd). Output Socket.
Control knobs (3). Veroboard (2) $1\frac{7}{8}'' \times 3\frac{3}{4}''$ in. and $7\frac{1}{2}'' \times 3''$ in. both plain, 0.15 in. matrix.

mounted at an angle or side by side so that the adjustment slots can be reached with a small screwdriver from the back of the case.

Connection from the tuning pre-sets PR1 to PR14 to their respective contacts are also shown in Fig. 12 together with connections to the panel controls VR1, VR2, S1, S3, S4, S5 etc.

The control panel assembly and wiring is shown in Fig. 13. Note that some components such as R43, C25, C26, R17 and R18 are wired between controls.

Mention has already been made regarding the drum brush circuit and adjustment for long or short decay. The choice is for the user but should the sound level appear too high, then the resistor R46 (4.7K) should be increased until the required balance between drum brush and bass notes is achieved.

Before tuning set the wipers on the pre-sets PR1 to PR13 to midway, set the 'pitch' control VR1 also to midway position and then begin tuning with PR13 which will tune the highest C note. If possible the

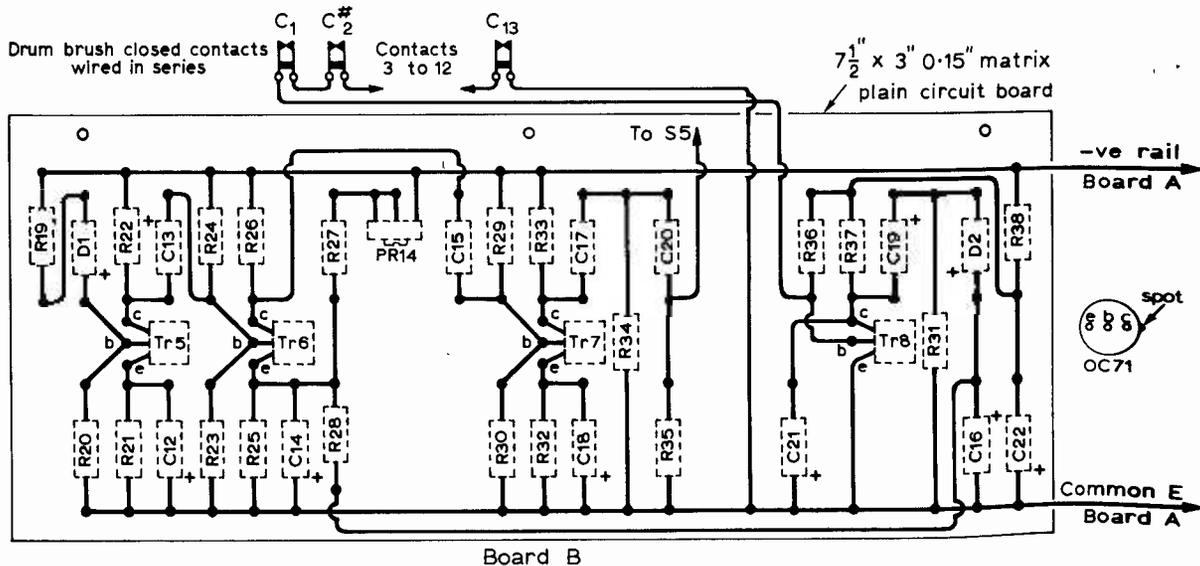


Fig. 14: Circuit Board B containing the noise generator and control amplifier.

The control panel is mounted on the top of the case framework at the front (see Fig. 8 and Fig. 9 Part 1).

The drum brush noise generator and control amplifier is assembled on Board B as shown in Fig. 14. Connections to S5 and the drum brush contacts are also shown.

Board B is mounted toward the rear of the unit on the lower cross members of the case in the position shown in Fig. 8 Part 1. Board A is mounted toward the front of the case as in Fig. 8 Part 1. Board B should be situated to the left of the case (looking from the rear) so as to leave enough space for the battery. The output jack can be mounted on a small aluminium panel as shown in the photograph in Part 1.

Checking and Tuning

If an oscilloscope is available the waveform from the multi-vibrator Tr1-Tr2 can be checked at the junction of R4 and the collector of Tr2 and from the divider at C8-R14. The function of the drum brush circuit can be checked at C20-R35. The voiced waveforms can of course be checked at the output socket and those for flute should appear nearly sinusoidal. With the 'clarinet' switched on a small pulse will be superimposed on the flute waveform and the audible tone will be slightly 'reeby'.

With 8 + 16 pitch the respective waveforms will combine and the 8ft. waveform will appear to sit on top of the 16ft. waveform. Audibly, the 8ft. and/or 16ft. pitch with flute voicing should have a round deep tone.

tuning should be done with the aid of an electronic organ with bass by tuning each note on the pedal unit to zero beat. Failing this, tune with a piano and use the zero beat method for each note. Start with the highest C (PR13) and tune each note going down using 8ft. pitch and flute voicing. The tuning will maintain itself for a long time but should be checked occasionally to ensure perfect pitch.

Final Assembly

The covers for the top, back and base can be made from hardboard cut to fit over the framework. Make a cut-out where the battery goes in and a small separate panel to secure the battery in place, Fig. 15. The covers should be screwed on so as to allow quick access to the pedal contacts and circuit

—continued on page 477


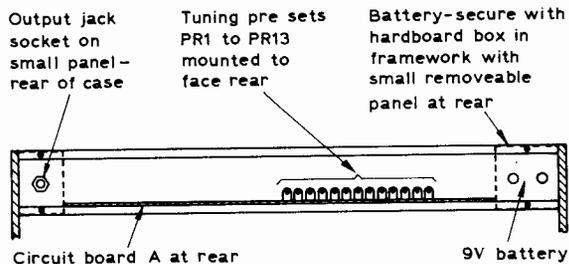


Fig. 15: Arrangement at rear of unit.

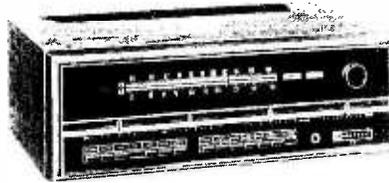
Many New Models! in the FREE HEATHKIT 1971 Catalogue..



CONSUMER



HI-FI & AUDIO

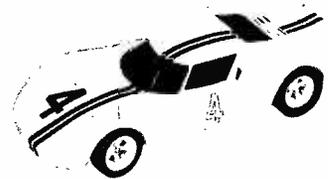


MODEL R/C CARS

Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi . . . Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.
- ★ Save up to 50 % over factory built equipment.
- ★ Money saving direct from factory prices.
- ★ They make excellent Christmas gifts.



MARINE

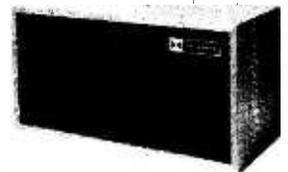

'TRENT' SPEAKER



A Schlumberger Company

Many other models in wide range . . .

**FILL IN THE COUPON FOR YOUR
FREE CATALOGUE TODAY.**

HEATH (Gloucester) LTD, GLOUCESTER GL2 6EE

(In block capitals)

Name

Address

Post Code

VIBRASONIC

25-50

GUITAR AMPLIFIER

Part 2

The previous article (Part 1) dealt with the cabinet and main chassis assembly and with the function of the pre-amplifier and tremulant circuitry. The full circuit for the pre-amplifier was included (Fig. 5 Part 1) which should be used in conjunction with the various assembly details given in this article.

The pre-amplifier and tremulant control circuit is divided into three sections each having its own circuit board as in Figs. 6, 7 and 8. Before dealing with these however, it is advisable to construct the small separate assemblies such as the panel tremulant indicator lamp, the l.d.r. mounting, its control lamp and cover, and the mains input socket panel which is fitted at the rear of the cabinet.

The l.d.r. is mounted on a small piece of s.r.b.p. attached to a chassis fixing bracket as in Fig. 10. Its control lamp B2 is mounted in a dial light holder (m.e.s.) as shown in the same diagram. The two assemblies are secured to the chassis with self tapping screws so that the lamp is level with the l.d.r. and approximately $\frac{1}{4}$ in. in front.

The l.d.r. cover is shown in Fig. 11 and this is simply fitted over the l.d.r. and its lamp and secured to the chassis with self tapping screws. This cover keeps any external light off the l.d.r. and is useful when the amplifier is being tested out of the cabinet,

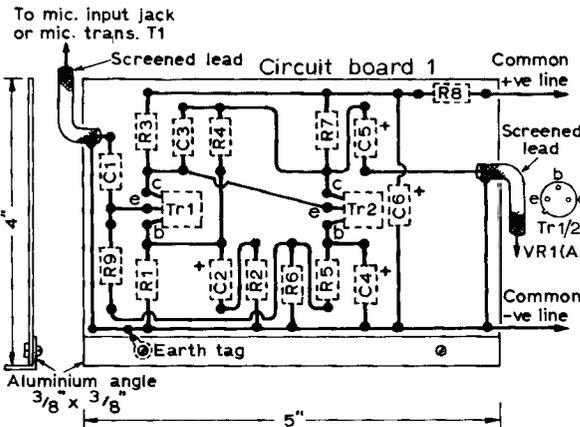


Fig. 6: Microphone pre-amplifier on Circuit Board 1.

With these done and the front panel drilled ready for the controls etc. the circuit boards can be made and wired and the whole amplifier finished off ready for testing.

The panel tremulant lamp unit is simple to make and requires only an m.e.s. batten lampholder mounted on a bracket as in Fig. 9. This is fitted to the chassis with self tapping screws in the position shown Fig. 13, so that the lamp 'looks' through the hole provided as in the front panel layout diagram. A piece of coloured celluloid is glued over the hole, inside the panel, to enhance the appearance.

When the tremulant circuit is operating, this lamp flickers at the tremulant speed and its brilliance varies according to the setting of the tremulant depth control.

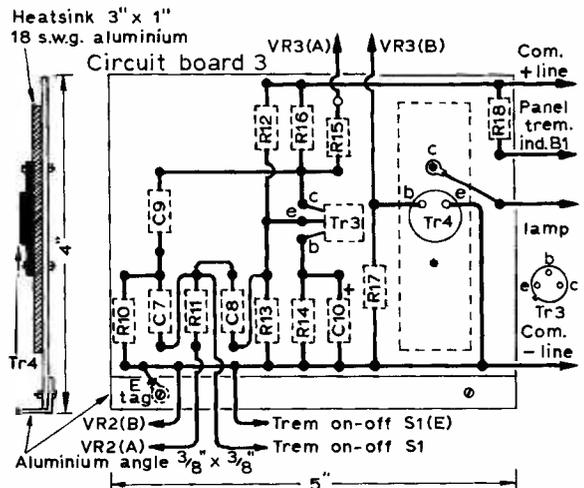


Fig. 8: Phase shift oscillator and LDR control amplifier, Circuit Board 3.

where light could reach the l.d.r. and alter its operating range.

The remaining small assembly is the 3-pin mains input socket which requires only a panel as in Fig. 12. This assembly is fitted at the back of the cabinet as can be seen in the photographs.

Pre-amplifier Circuit Boards

These are numbered 1, 2 and 3 and are located on the main chassis as in Fig. 13. Boards 1 and 3 are 5 x 4 in. plain s.r.b.p. with 0.1 in. matrix and Board 2 is 5 x 7 in. of the same material. Each board is mounted on $\frac{3}{8}$ x $\frac{3}{8}$ in. aluminium angle which secures the board to the chassis (self tapping screws).

LST

ELECTRONIC COMPONENTS LTD

= BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

AA930 1/7	ASV26 4/5	BCY71 7/8	BSY95 3/2	NKT151 6/-	NKT279A 2/6	OC36 12/6	40250 10/9	2N918 8/5	2N3414 5/6	2N5027 10/6
AAZ13 3/2	ASV27 6/-	BCY72 3/2	BSY95A 2/11	NKT153 6/-	NKT281 5/-	OC41 5/-	40309 6/6	2N928 5/3	2N3415 6/-	2N5028 11/6
AA107 1/4	ASV28 6/6	BCY73 6/6	BSY95B 1/4	NKT154 1/6	NKT282 1/6	OC42 1/6	40310 6/6	2N930 6/6	2N3416 7/6	2N5030 9/6
AC126 5/-	ASV29 7/6	BC11 7/6	BY215 33/3	NKT161 6/-	NKT302 12/5	OC43 4/6	40311 6/6	2N1131 6/-	2N3436 15/-	2N5030 8/6
AC127 4/-	ASZ21 7/6	BD119 15/-	C111 18/-	NKT162 6/-	NKT303 17/6	OC44 4/6	40312 9/6	2N1132 6/-	2N3525 21/9	2N5172 3/6
AC127Z 9/6	AUJ10 30/-	BD121 13/-	C111E 12/-	NKT163 6/-	NKT304 10/0	OC45 3/-	40314 7/3	2N1302 3/7	2N3528 19/-	2N5174 10/6
AC128 4/-	BI181 10/-	BD123 16/6	C265 8/3	NKT164 6/8	NKT351 19/0	OC70 2/6	40315 7/3	2N1303 4/6	2N3606 5/6	2N5175 10/6
AC176 5/-	B2M 12/6	BD124 12/6	CR1-051C 8/-	NKT165 6/-	NKT352 17/6	OC71 3/-	40316 9/3	2N1304 4/11	2N3607 4/6	2N5176 9/-
AC187 6/-	B3M 10/6	BDY20 20/8	CR1-401C10/-	NKT201 6/-	NKT361 20/0	OC72 4/6	40317 7/3	2N1305 4/7	2N3702 2/6	2N5232 5/6
AC188 6/-	BA102 9/-	BF115 5/-	D13T1 10/-	NKT202 6/-	NKT362 20/0	OC74 8/-	40319 10/9	2N1306 6/-	2N3703 2/5	2N5249 13/6
ACY17 5/9	B103 7/6	BF122 13/6	FS138AF 5/-	NKT204 6/-	NKT401 14/8	OC75 4/6	40320 7/3	2N1307 6/-	2N3704 3/2	2N5248 13/6
ACY18 6/-	BA111 6/6	BF154 9/-	GET16 12/6	NKT205 6/-	NKT402 15/-	OC76 5/-	40323 6/6	2N1308 6/-	2N3705 2/8	2N5305 7/6
ACY19 4/-	BA114 3/6	BF159 15/-	GET102 6/-	NKT206 6/-	NKT403 14/9	OC77 8/-	40324 9/3	2N1309 6/3	2N3706 2/3	2N5306 8/-
ACY20 3/10	BAX13 1/6	BF163 9/-	GET103 5/-	NKT208 6/-	NKT404 11/0	OC81 4/6	40326 7/3	2N1613 4/6	2N3707 2/10	2N5309 12/6
ACY21 3/10	BC113 5/-	BF167 5/-	GET111 5/-	NKT210 4/2	NKT405 11/0	OC81D 1/6	40329 4/9	2N1711 5/-	2N3708 1/10	2N5354 5/6
ACY22 3/9	BC115 6/6	BF173 6/6	GET113 4/6	NKT211 3/9	NKT406 9/11	OC81Z 11/-	40344 5/3	2N1747 16/3	2N3709 2/-	2N5355 5/6
ACY27 3/6	BC116 8/6	BF176 10/6	ME103 3/3	NKT212 3/6	NKT420 28/11	OC82 5/-	40347 7/6	2N2148 12/6	2N3710 2/3	2N5356 10/6
ACY28 3/6	BC117 7/6	BF177 12/6	ME1480 20/8	NKT213 4/7	NKT451 9/11	OC82D 3/-	40348 10/3	2N2160 12/6	2N3711 2/6	2S001 10/-
ACY29 7/6	BC118 7/6	BF180 7/6	MJ481 27/-	NKT214 3/5	NKT452 9/6	OC83 4/6	40360 8/6	2N2217 5/5	2N3789 5/19	2S002 12/6
ACY30 7/6	BC125 11/-	BF181 7/6	MJ490 22/6	NKT215 3/7	NKT453 6/8	OC84 5/-	40361 9/6	2N2217A 11/4	2N3819 7/-	2S003 12/6
ACY31 4/7	BC126 11/-	BF184 5/-	MJ491 29/6	NKT216 7/6	NKT603F 4/8	OC123 7/-	40362 11/6	2N2218 6/5	2N3820 18/9	2S004 15/-
ACY34 3/5	BC134 5/-	BF185 5/-	MPF102 8/6	NKT217 9/-	NKT613F 5/2	OC139 5/-	40370 6/-	2N2218A 8/2	2N3826 6/-	2S005 15/-
ACY35 3/6	BC135 6/6	BF194 3/6	MPF103 7/6	NKT218 6/-	NKT654F 4/2	OC140 7/-	40406 11/3	2N2219 7/4	2N3854 5/6	2S006 15/-
ACY36 3/9	BC136 9/-	BF195 3/6	MPF104 7/6	NKT219 4/7	NKT655 6/8	OC141 12/6	40408 10/6	2N2219A 10/1	2N3854A 5/6	2S017 8/6
ACY39 11/6	BC137 8/6	BF197 10/6	MPF105 8/6	NKT220 6/-	NKT745 9/11	OC142 7/6	40411 11/3	2N2220 9/6	2N3859 5/6	2S018 10/6
ACY40 3/9	BC138 12/-	BF198 5/-	NKT11 7/6	NKT222 6/-	NKT677 3/10	OC171 6/-	40467 16/6	2N2269A 3/11	2N3855A 6/-	2S019 19/6
ACY41 3/9	BC140 13/3	BF229 6/2	NKT12 5/5	NKT223 5/-	NKT703 8/-	OC200 7/6	40468A 7/-	2N2613 7/6	2N3856 6/-	2S020 20/-
ACY44 8/-	BC142 15/-	BF244 8/-	NKT32 6/-	NKT224 3/7	NKT713 3/10	OC201 9/6	40602 8/-	2N2614 4/-	2N3856A 6/-	2S104 12/6
AD140 11/-	BC143 15/-	BF248 5/2	NKT42 6/-	NKT225 3/6	NKT717 5/10	OC202 12/6	1N3713 30/-	2N2646 10/0	2N3858 5/-	2S301 8/6
AD149 11/6	BC145 15/-	BF285 6/9	NKT43 6/-	NKT226 11/-	NKT734 4/10	OC203 7/6	1N3717 30/-	2N2904 8/10	2N3858A 6/-	2S302 7/6
AD161 7/6	BC147 2/9	BF286 4/11	NKT103 3/9	NKT227 6/-	NKT735 4/12	OC204 8/-	15100 3/3	2N2904A 9/8	2N3859 5/6	2S303 10/6
AD162 7/6	BC148 3/3	BF287 5/11	NKT173 3/7	NKT228 6/6	NKT773 3/7	OC205 9/-	15107 6/6	2N2905 12/11	2N3859A 6/3	2S304 12/6
AD170 12/6	BC149 3/3	BF288 5/3	NKT101 6/-	NKT229 3/11	NKT774 6/-	OC206 15/-	15410 5/1	2N2905A 15/1	2N3860 6/3	2S306 15/6
ADZ11 32/-	BC154 12/6	BFY18 15/-	NKT102 6/-	NKT231 6/-	NKT0013 6/6	OC207 15/-	15410R 5/1	2N2906 8/10	2N3866 25/-	2S320 9/-
ADZ12 39/-	BC167 3/6	BFY50 4/6	NKT103 6/-	NKT232 6/-	NKT104193/10	OC271 19/6	2G302 3/9	2N2906A10/10	2N3877 9/6	2S321 6/6
AF102 12/6	BC168 3/9	BFY51 3/9	NKT104 6/-	NKT237 5/9	NKT10519 4/5	ORP12 10/-	2G339 3/1	2N2923 4/-	2N3877A 9/6	2S322 8/6
AF106 12/6	BC169 3/9	BFY52 3/9	NKT105 6/-	NKT238 4/-	NKT10339 4/7	ORP20 8/-	2G371 3/1	2N2924 4/-	2N3900 10/6	2S323 10/6
AF114 5/-	BC171 2/-	BFY53 3/2	NKT106 6/-	NKT239 4/-	NKT10439 5/5	ORP61 8/-	2G371B 3/1	2N2925 3/6	2N3900A 11/6	2S701 8/6
AF115 5/-	BC182L 2/3	BFY90 13/6	NKT107 6/-	NKT240 3/10	NKT12329 8/5	ORP63 9/-	2G374 5/1	2N3011 12/6	2N3903 7/7	2S702 11/6
AF116 5/-	BC183L 1/10	BFW57 6/1	NKT108 6/-	NKT241 3/9	NKT1242910/6	P346A 3/9	2G381 5/-	2N3036 30/-	2N3904 7/7	2S703 12/6
AF117 5/-	BC184L 3/3	BFW58 5/6	NKT109 6/-	NKT242 2/11	NKT13293/11	RAS310AF 9/-	2N174 18/-	2N3053 5/-	2N3905 7/6	2S711 24/6
AF118 8/10	BC212L 3/4	BFW59 5/6	NKT121 10/6	NKT243 12/-	NKT134293/11	SIM508AF 6/-	2N388A 15/-	2N3054 12/6	2N3906 7/6	2S712 34/6
AF121 6/-	BCY10 10/-	BFY60 4/6	NKT122 10/-	NKT244 3/1	NKT16229 8/5	2N404 4/-	2N404 4/-	2N3055 15/-	2N4037 15/-	2S720 25/-
AF124 5/-	BCY12 12/-	BLV17 3/3	NKT123 8/6	NKT245 3/8	NKT2033 6/8	15/-	2N698 3/6	2N3133 6/-	2N4058 3/4	2S732 8/6
AF125 4/2	BCY30 5/-	BSX19 3/3	NKT124 6/5	NKT261 4/3	NKT20339 6/4	SAM 33/6	2N698 6/6	2N3135 6/-	2N4059 5/-	2S733 5/6
AF126 3/6	BCY31 5/6	BSX20 3/3	NKT125 4/6	NKT262 4/3	NKT319219/9	ST2 9/9	2N698 7/6	2N3136 6/-	2N4060 5/-	3N128 13/6
AF127 3/6	BCY32 10/-	BSX21 7/7	NKT126 4/6	NKT263 4/8	OC19 5/-	ST2 9/9	2N706 2/4	2N3235 28/6	2N4061 4/5	3N140 15/6
AF129 15/-	BCY33 4/-	BSX60 12/17	NKT127 10/6	NKT264 4/3	OC20 19/6	TD716 2/6	2N706A 2/6	2N3234 27/6	2N4062 4/6	3N141 14/6
AF178 9/6	BCY34 5/-	BSX61 7/11	NKT128 10/6	NKT265 5/6	OC22 8/-	T1407 9/8	2N708 3/3	2N3242 7/9	2N4284 3/3	3N142 18/6
AF179 11/6	BCY35 6/-	BSX62 4/6	NKT129 8/6	NKT270 6/-	OC23 10/6	TIC45 8/-	2N709 9/6	2N3251 6/-	2N4287 3/3	3N143 13/6
AF180 12/6	BCY39 9/6	BSX77 6/-	NKT135 6/1	NKT271 2/10	OC24 10/-	TIS34 17/6	2N711 7/6	2N3392 5/-	2N4288 3/3	3N152 17/6
AF186W 8/-	BCY40 10/-	BSX78 6/6	NKT137 6/1	NKT272 2/10	OC25 7/6	TIS44 19/6	2N711A 7/6	2N3393 5/-	2N4289 3/3	SD6 5/6
AF186G 8/-	BCY42 4/-	BSY27 4/-	NKT141 10/6	NKT273 3/8	OC26 6/6	TIP31A 12/4	2N743 4/6	2N3394 4/9	2N4290 3/3	AA119 2/-
AF239 7/6	BCY43 4/-	BSY29 5/-	NKT142 10/6	NKT274 2/10	OC28 12/-	TIP32A 14/10	2N744 6/-	2N3403 5/6	2N4291 3/3	AA111 2/-
AFY19 22/6	BCY54 7/6	BSY32 5/-	NKT143 9/6	NKT275 3/4	OC29 15/-	V205 2/9	2N911 10/-	2N3403 5/6	2N4292 3/3	AA112 2/-
AFZ11 8/-	BCY70 3/10	BSY36 5/-	NKT144 8/3	NKT276 3/6	OC35 10/-	V405A 2/9	2N914 3/11	2N3404 7/6	2N4293 3/3	AA113 2/6

BC107/8/9 2/6
NPN Planar transistors
25+ 2/3 100+ 2/-

2N3819 7/-
Texas FET
25+ 6/- 100+ 5/3

SILICON RECTIFIERS
1 Amp Miniature Moulded Junction Rectifiers.
P.I.V. -124 25+ 100+ 500+
IN4001 50 1/6 1/4 1/2 1/-
IN4002 100 1/6 1/4 1/2 1/-
IN4003 200 1/6 1/4 1/2 1/-
IN4004 400 2/- 1/9 1/6 1/3
IN4005 600 2/6 2/- 1/9 1/6
IN4006 800 3/- 2/10 2/6 2/3
IN4007 1000 4/- 3/3 2/9 2/6
In the event of any IN4000 series going temporarily out of stock we reserve the right to send higher voltage types at no extra charge. 1000+ and over prices on application.

NEWS NEWS NEWS...
L.S.T. Electronic Components Limited are proud to announce their official appointment by Newmarket Transistors Ltd., All Newmarket products now available at Industrial User prices. All R.C.A. Semiconductor standard circuits now also available from L.S.T. at Industrial User prices. Many Mullard, General Electric, Texas types also stock at LST at Industrial User prices and better. Inkra resistors, Mullard Capacitors, Veroboard, Repanco colla and other misc. components stocked in large quantities. Official International Rectifier Semiconductor Centre stockists.

2N4871 6/9
Motorola unijunction
25+ 5/9 100+ 4/9

CRI/051-C 8/-
CRI/401-C 10/-
AE1 400 piv. 50 piv 1 amp SCR's/Thyristors

DISCOUNT: Quantities of different IN4000 series may be combined to qualify for the quantity discount prices quoted example: 10/IN4001 1/5, 10/IN4002 1/10, 5/IN4007 3/4 (25 total pieces).
In the event of any IN4000 series going temporarily out of stock we reserve the right to send higher voltage types at no extra charge.

INTEGRATED CIRCUITS
Some R.C.A. Linear types

CA3005	23/6	CA3022	26/-	CA3041	21/9
CA3011	14/9	CA3023	25/3	CA3042	21/9
CA3012	17/9	CA3025	26/-	CA3043	27/9
CA3013	21/-	CA3028A	14/9	CA3044	24/-
CA3014	24/9	CA3028B	21/-	CA3045	24/6
CA3018	16/9	CA3035	24/6	CA3046	15/2
CA3020	25/3	CA3036	14/6	CA3048	40/9
CA3021	31/3	CA3039	18/9	CA3051	28/9

Application Notes for each individual 2/6d. per copy.

2N3055 15/-
115 watt silicon power transistor
25+ 13/- 100+ 11/-

OCF 71 19/6
Mullard Phototransistor
25+ 17/3 100+ 14/9

ZENER DIODES
400mW 10+ GLASS CASE. TEXAS Mir.
1S2036 3.6 volt 1S2082 8.2 volt
1S2039 3.9 volt 1S2101 10 volt
1S2043 4.3 volt 1S2110 11 volt
1S2047 4.7 volt 1S2120 12 volt
1S2056 5.6 volt 1S2160 16 volt
1S2062 6.2 volt 1S2180 18 volt
1S2068 6.8 volt 1S2270 27 volt
1S2071 7.5 volt 1S2300 30 volt
PRICES: 1-24 3/6, 25-99 100+ 2/3

IC10	Sinclair Audio Amplifier	55/-
PA234	GE IC 1 Watt Amplifier	17/6
PA237	GE IC 2 Watt Amplifier	37/8
PA246	GE IC 5 Watt Amplifier	52/6
PA424	GE IC Zero Voltage Switch	49/6
SL403A	Plessey 3 Watt Amplifier	25/6
SL7025C	Plessey Linear	42/6
TAA283	Mullard General Purpose Amplifier	15/-
TAA293	Mullard General Purpose Amplifier	20/-
TAA310	Record/Playback Amplifier	30/-
TAA320	MOS LF Amplifier	13/-
TAD100	Mullard IC Receiver	39/6
TAD110	Mullard IC Receiver	39/6
3N84	GE Silicon Controlled Switch	..			

**Fully guaranteed
Individually packed
VALVES**

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.
MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves, U.K. Orders
 up to 10/-, 1/-; 10/- to 21 9/-; over 21, 2/- per 21; over 25 post free. C.O.D. 4/- extra



**ALL valves
guaranteed**

TRANSISTORS, ZENER DIODES etc.

<p> CY31 7/- ECL86 8/6 PC97 9/- DAF96 7/9 EF36 8/6 PC900 9/- DF66 7/6 EF37A 7/- PC84 8/6 DK96 7/6 EF39 8/- PC88 9/6 DL92 6/6 EF40 10/- PC189 11/6 DL94 8/6 EF41 12/6 PC880 15/- DL96 7/9 EF83 9/6 PCF80 16/- DM70 6/6 EF85 9/6 PCF84 9/3 DY86 6/6 EF89 8/3 PCF86 10/- DY87 6/6 EF91 8/- PCF201 16/- EY802 9/9 EF95 5/- PCF801 9/9 E88CC/01 EF95 5/- PCF801 9/9 EABC80 27/- EF183 6/6 PCF805 14/6 EAF42 10/- EF184 7/- PCF806 13/- EBC33 8/- EF184 10/6 PCF808 14/6 EBC41 10/6 EL14 11/6 PCL81 18/- EBC81 6/6 EL42 11/6 PCL82 7/6 EBF80 7/6 EL84 4/9 PCL83 18/- EBF83 8/6 EL86 8/- PCL84 8/6 EBF89 6/6 EL90 6/- PCL86 9/3 EOC81 4/- EL95 7/- PFL200 14/- EOC82 5/- EL900 17/- PL36 10/9 EOC83 8/- EM81 5/- PL81 8/9 EOC84 6/- EM80 7/8 PL82 8/6 EOC86 7/6 EM84 7/- PL83 7/8 EOC88 7/- EM87 11/- PL84 6/6 EOC189 9/9 EY81 8/- PL600 14/9 ECF80 6/6 EY81 7/- PL604 8/6 ECF82 6/6 EY86 8/- PL609 8/6 ECF83 15/6 EY86 8/- PL609 8/6 ECF801 18/6 EY81 7/8 PL26 30/- ECF802 12/6 EY80 8/- PY33 12/- ECF85 11/- EY81 8/- PY90 6/6 ECH42 18/- GZ34 10/6 PY81 5/6 ECH81 8/9 KT66 27/6 PY82 5/6 ECH84 7/6 KT88 33/- PY83 7/6 ECH200 12/6 N76 25/- PY83 7/6 ECL80 6/6 OA2 6/- PY88 7/8 ECL82 6/6 OB2 6/- PY800 9/6 ECL83 10/6 PAB380 7/8 PY801 9/6 </p>	<p> OA5 2/6 OC29 15/- OC172 7/6 3PR5 6/6 AF118 10/- CR83/20 10/- OA10 6/6 OC36 8/6 3N128 17/6 AF139 10/- CR83/30 11/6 OA70 9/6 OC38 8/6 3N139 35/- AF178 12/6 CR826/025 OA71 9/- OC44 4/- OC206 10/- 3N140 19/6 AFY19 22/6 OC45 2/6 OC49 1/6 3N154 19/- 3N154 19/- 3N154 19/- OC70 3/6 3N159 33/- 3N159 33/- 3N159 33/- OC71 2/6 3N25 12/- 3PR5 6/6 BAW19 5/6 GET115 9/- OC72 2/- OC72 2/- IN48 4/- 12FR60 14/9 BC107 3/6 GET116 9/- OC73 11/- IN70 4/- 10D1 3/- BC110 9/- 3N159 33/- OC75 4/6 IN702-7257/8 28/6 BC107 3/6 3N159 33/- OC76 8/- IN748A 40/94 27/6 BCY72 7/9 SD948 6/6 OC81 4/- series 5/3 40595 27/6 BFW51 4/6 SD968 7/8 OC81D 3/- IN821A 21/- 40636 28/- BFW52 4/6 SD988 7/9 OC82 3/- IN823A 28/- 40688 27/6 B805 3/6 V405A 7/8 OC82D 3/- IN825 7/9 40689 29/- B81 9/- Z Range OC83 4/6 IZT5 13/6 AC127 4/6 B82 9/3 Zener diodes OC83B 3/- IZT10 12/6 AC128 4/6 BU100 86/- 3/6 ea. OC84 5/- 2N1306 6/6 AC176 7/8 BY213 5/- Z2A range OC122 10/- 2N1307 6/6 ADY28 4/- CR81/10 5/- Z3B range OC139 6/6 2N1308 6/6 ADY40 11/- CR81/20 5/- 5/- ea. OC140 8/- 2N3054 12/6 AD161 7/- CR81/30 10/- 5/- ea. OC170 5/- 2N3055 15/- AD162 7/- CR81/38 11/6 5/- ea. OC171 6/- F100 18/6 AF117 4/9 CR81/40 12/6 ZB range CR83/05 8/- </p>	<p> 6P25 11/- 19AQ5 7/9 2051 10/- 6A7 7/- 19G3 70/- 5933 22/6 6BA7GT 6/6 19G6 80/- 6057 10/- 68C7 13/- 19H4 85/- 6080 7/6 68CTGT 5/6 20P4 17/- 6084 7/- 68G7 6/6 28LGT 7/8 6085 18/- 68J7 7/6 30C15 15/- 6080 27/6 68J7GT 6/6 30C17 18/- 6146 28/- 68K7 7/6 30C18 15/- 6020 28/- 68LGT 6/6 30F15 16/6 9001 3/- 68N7GT 6/6 30F16 6/- 9009 4/6 68P7 7/6 30FL12 18/6 9003 10/- 68Q7GT 7/6 30FL13 9/6 9004 2/6 68V6 3/6 30FL14 15/6 9006 9/6 68V6GT 6/6 30L16 17/- 6X4 4/9 30L17 17/- G.R. Tubes 6X6G 5/6 30P12 18/- VCB97 22/6 6X6GT 8/6 30P19 14/- VCR517 50/- 6Y6G 11/- 30PL1 18/- VCR517B55/- 6Z0L2 14/- 30PL13 18/- VCR517C45/- 6Z4 5/6 30PL14 17/- 5FP7 22/6 7B7 7/6 35L6GT 9/6 8RD 180/- 7C5 14/6 35W4 6/- 8S3 80/- 7C6 9/- 35Z4T 9/- 8SL 90/- 7H7 6/6 42 7/- 7Y4 7/6 50C5 22/6 Photo Tubes 7D6 7/6 50CD6G 80/- CMG26 25/- 11E2 30/- 50E8 18/- 931A 59/- 12AT6 4/6 75 5/6 6097C 85/- 12AT7 4/- 76 6/6 Special Vva. 12AU7 5/6 78 6/- CV1081 100/- 12AV6 5/6 80 6/- CV399 230 12B6 7/- 803 6/6 JP9/7D 750/- 12BA6 6/- 805 180/- K901 44 12BE6 6/- 807 9/- K805 212 12BH7 3/6 813 75/- K808 211 12C8 5/6 832A 58/- K837 212 12E1 17/- 856A 18/- KR39A 70/- 12E5 10/- 864 6/6 W1417A 30/- 12KT6 6/9 955 4/- 3J/9E2 12KR8GT 6/9 956 2/- 287/10/- 12LQ7GT 5/6 957 6/- 5C22 215 12MG7 7/- 991 6/- 714AY 24 14B7 18/- 1292 17/- 725A 210 </p>
--	--	---

P. G. RADIO LTD.
170 GOLDHAWK RD., W.12
 01-743 4946

METERS
 28/44ft. ARRIALS each consisting of ten 3ft. 1in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect in canvas bag 23.9.9. P. & F. 10/6.
 Full List of our very large stock of meters on request.

ALL OVERSEAS ENQUIRIES AND ORDERS
 Please address to
Colomor (Electronics) Ltd.
 170 GOLDHAWK ROAD, LONDON W12.
 Tel: 01-743 0899

**YOUR CAREER in
RADIO &
ELECTRONICS?**

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME Block

ADDRESS Caps.

..... Please 1/70

BRITISH NATIONAL RADIO SCHOOL

BAKER 12in. MAJOR £9

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cones together with a special BAKER CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffles. £11.10.0
 19 x 12in. and instructions.

Baker Reproducers Ltd
 Send 4d Stamp for Further Details
 Bensham Manor Road Passage, Thornton Heath, Surrey.
 Telephone 01-684-1665

FREE LIST! SEND S.A.E. FOR BUMPER FLOG LIST

TECHNICAL TRADING

FANTASTICALLY POPULAR
 ★ **JASON TAPE** ★

We offer you fully tensile polyester mylar and P.V.C. tapes of identical quality but wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more pence than acetate, sub-standard, jointed or cheap imports TRY ONE AND PROVE IT YOURSELF.

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 500ft.	13/-
4in. 600ft.	8/-	5in. 1,000ft.	25/-
5in. 1,200ft.	12/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,100ft.	27/-	7in. 4,200ft.	51/6

★ **ARUNDEL (Tel. 23975)**
 15-17 Queen Street

★ **LONDON (MUS 2636)**
 10 Tottenham Court Road
 PORTSMOUTH (Tel. 22034)
 306-322 Fratton Road

★ **SOUTHAMPTON**
 72 East Street (Tel. 25851)

★ **BRIGHTON (Tel. 23975)**
 8 Queen's Road

Postages 1/- reel.
 Post Free less 5% on three reels.
 Quantity and Trade enquiries invited.

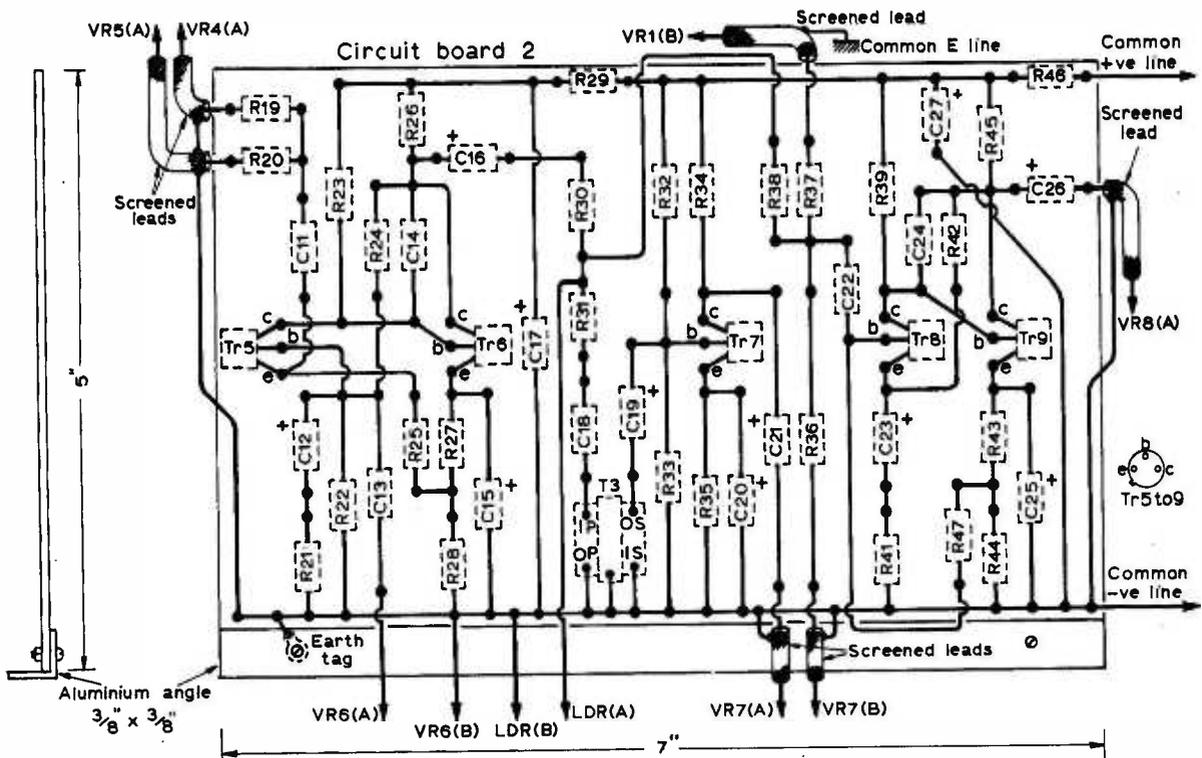


Fig. 7: Guitar and tremulant amplifier on Circuit Board 2.

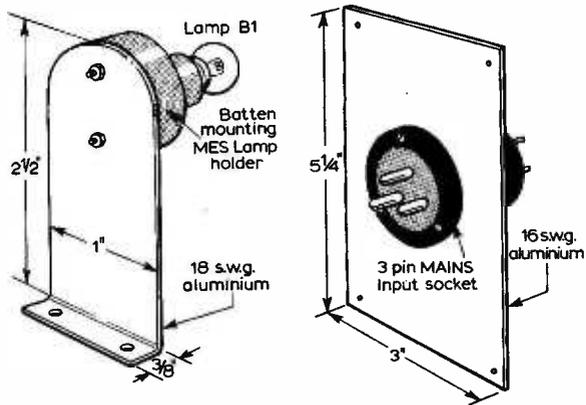


Fig. 9: (far left) Mounting bracket for tremulant indicator lamp.

Fig. 12: (left) Mains input socket mounting.

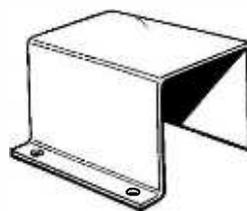


Fig. 10: (left) Mounting details of LDR and lamp.


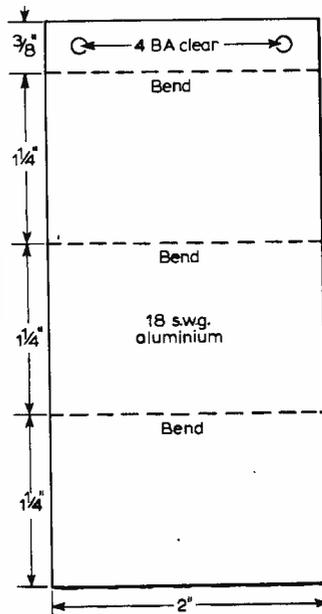


Fig. 11: (right) construction of LDR cover.

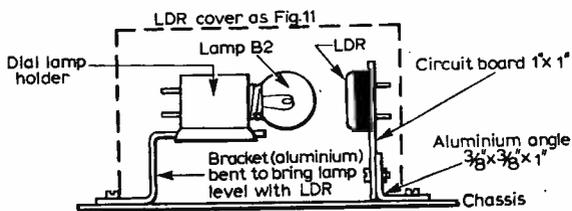

Board 1 contains the microphone pre-amplifier Tr1 and Tr2 and it is most important that the screened leads are earthed to the common earth line as shown.

Board 3 contains the tremulant phase shift oscillator Tr3 and the l.d.r. control amplifier Tr4. Note that the earth returns from VR2 and the tremulant

on-off switch must be made as shown, to the common earth line on the circuit board, and to nowhere else. The l.d.r. control amplifier Tr4 must be fitted with a small heatsink as shown in Fig. 8.

The guitar and tremulant amplifier board (Board 2) has several screened lead connections and again it is important that these are earthed, as shown, to the common earth line on the board, as must the earth return from the l.d.r. (l.d.r-B).

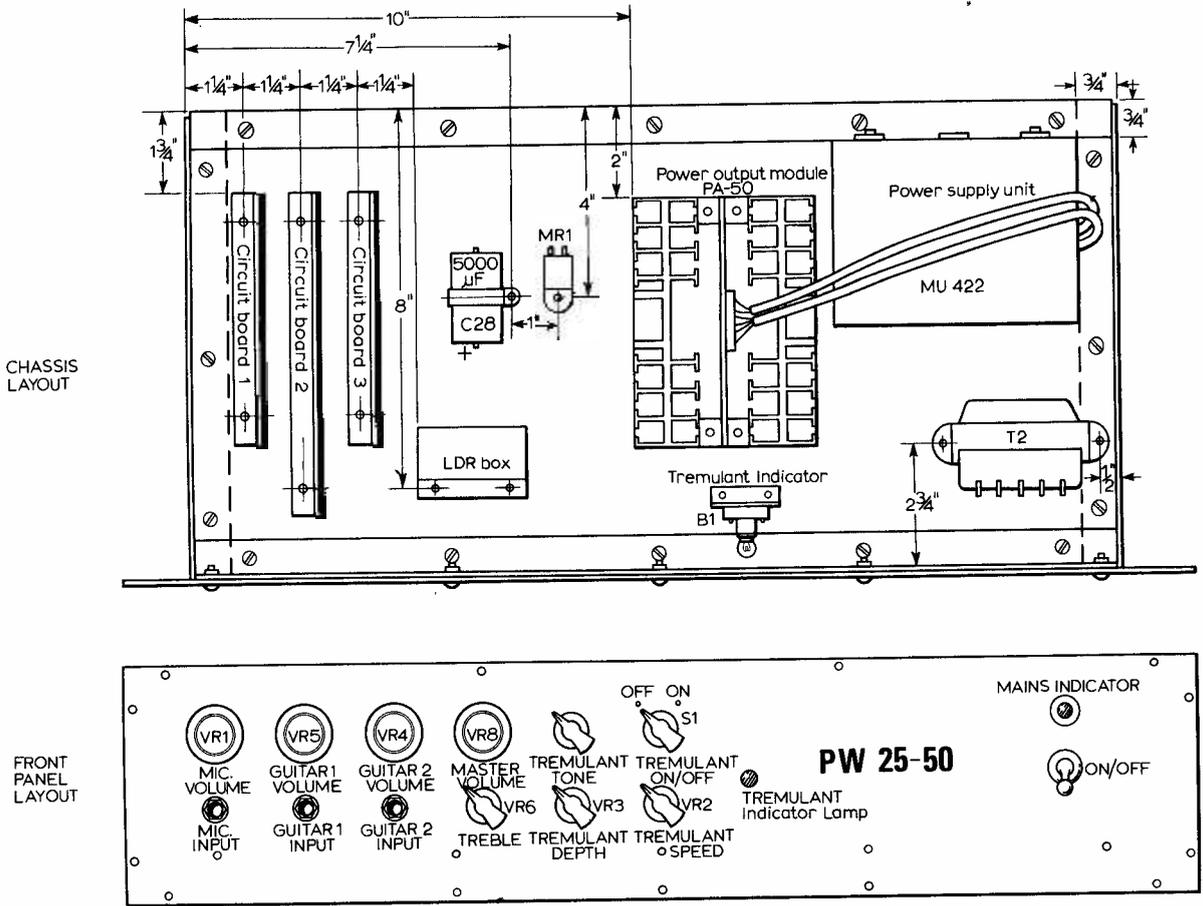


Fig. 13: Layout of panel controls and main components on top of chassis.

The coupling transformer T3 is bolted directly to the circuit board and is a type CP6713/2. It has the IP-OP and IS-OS connections clearly marked on it and these must be connected as in the diagram.

Pre-amplifier Power Supply

It is not convenient to take the supply voltage for the pre-amplifiers from the output module power supply as this is a sealed unit. Transformer T2, the rectifier MR1 and smoothing capacitor C28 form the pre-amplifier power supply and are wired as shown in Fig. 14.


The reason for locating T2 at the far end of the chassis is to prevent the tremulant amplifier transformer T3 from picking up mains hum by mutual coupling. The mains transformer T2 has three secondary windings but only the 17V tap is used.

Chassis and Panel Layout

The positions of the circuit boards, the pre-amplifier power supply components, the power module and the module power supply are given in Fig. 13. It is most important to adhere to this layout to prevent hum loops around the chassis.

Points for the fixing holes of the power output module and its power supply have not been included as prototype units were used by the writer for the original amplifier. Fixing holes are however, provided

Rear view of completed amplifier and speakers.

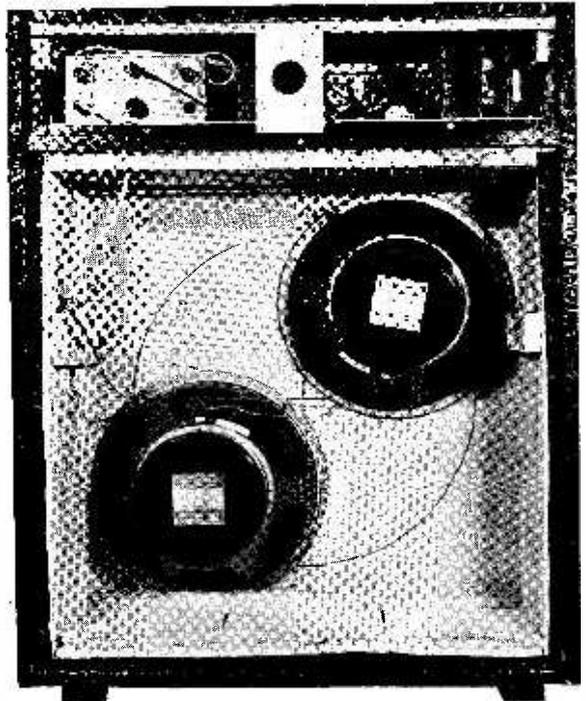

BSR 4-SPEED SUPERSLIM AUTO RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. Size 13 1/2" x 11in. Above motor board 8in. Below 8 1/2in. AC 200/250V.



with STEREO/MONO XTAL £7 Post 5/-
 BSR U70 Stereo/Mono Transcription Auto Changer. Calibrated Stylus Pressure. £14
 BSR Minichanger U450 Stereo/Mono. Plays 12", 10" or 7" records. £8
 Size 18 x 8 1/2in. AC 200/250V. Post 5/-.

GARRARD PLAYERS with Sonotone STA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II 215 AT70 Mk II 215 Model 3000 213 Post 5/-.

RECORD PLAYER PORTABLE CABINET Space for amplifier and autochanger. Post 5/-.
 ROS DE-LUXE 3 WATT AMPLIFIER. Ready made with 9-15k triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker with EULIS, EZ20. Response 50 c.p.s. Sensitivity 80mV. Post 5/-.
 RSC 2 WATT AMPLIFIER with loudspeaker and valve UOLSE. Post 5/- £3

R.G. TEAKWOOD BASE. Ready cut out for mounting (State player make and model) 77/6

R.G. PLASTIC COVERS FOR ABOVE BASES. Durable tinted plastic, attractive appearance. 77/6

EMI PICK-UP ARM. Complete with mono cartridge 29/6
 EMI JUNIOR 4 SPEED RECORD PLAYER. Post Mains operated motor, turntable and pick up. £3 5/-
 HI-FI PICK UP CARTRIDGES
 GP4 55/-; GP28 45/-; GP31 30/-; GP27 19/6, ACOS 15/- only 10/6. All standard fixing complete with stylus.

CRYSTAL MIKE INSERTS

1 1/2" dia. 6/6. ACOS 1 1/2" dia 19/6. BMS, 1" dia. 9/6.

PORTABLE AMPLIFIER

Portable mini p.a. system. Many uses—ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 x 4in., with powerful 7 x 4in. speaker and four transistor one watt power amplifier. Uses 5E5 battery and new with famous guarantee. Only 75/- Post 5/-.



WEYRAD P50—TRANSISTOR COILS

BAW Ferrite Aerial 13/-	Spare Cores 8d.
One P40/AG 10/-	Driver Trans. LEP4 10/-
L.F. P50/200 470 coils 6/-	Printed Circuit, PCAL 10/-
Std L.F. P50/300 6/7	F.F. Tuning Gang 10/6
P61/1 or P61/2 6/7	Weyrad Booklet 2/-
P61/3 6/7	OPT 11/-
Ferrite Rod 8 x 1/4in. 6 x 1/4in. 5/-	

VOLUME CONTROLS

800ohm Coax 9d. rd.
 BRITISH AERIALITY AERIAL-AIR SPACED 40 yd. 28/-; 60 yd. 40/-
 FRINGE LOW LOSS 2 1/2 yd. Ideal 625 Ohms.
 WIRE-WOUND 3-WATT POTS. 5/-
 WIRE-WOUND 3-WATT STANDARD SIZE POTS. LONG SPINDLE 10 OHMS to 100 K.
 VERBOBOARD 0.15 MATRIX 24 x 5in. 3/8; 24 x 3in. 3/8; 24 x 3 1/2in. 3/8; 24 x 5in. 5/8. EDGE CONNECTORS 16 WAY 5/-; 24 WAY 7/6. PINS 36 per packet 3/4. FACE CUTTERS 7/6.
 S.B.F.P. Board 0.15 MATRIX 2 1/2in. wide 6d. per 1in., 3 1/2in. wide 9d. per 1 in.; 5in. wide 1/- per 1in. (up to 17in.). S.B.F.P. drilled 1/4in. Board 10 x 8in. 3/-.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides, 7 x 4in., 6/-; 11 x 5in., 7/6; 11 x 7in. 9/6; 18 x 9in., 10/6; 18 x 14in., 15/6; 18 x 9in., 9/6; 14 x 11 x 5in., 14/6.
 ALUMINIUM PANELS 18 s.w.g. 18 x 12in. 6/6; 14 x 9in. 5/6; 18 x 8in. 4/6; 10 x 7in. 3/6; 6 x 4in. 2/6; 6 x 4in. 1/6.
 1-inch DIAMETER WAVE-CHANGING SWITCHES. 2 p. 2-way, or 2 p. 6-way, or 2 p. 4-way 4/6 each. 1 p. 12-way, or 2 p. 4-way, or 2 p. 4-way 3/6 each. 1/4 inch CHASSIS Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 2 p. 4-way, 4 p. 3-way, 6 p. 3-way, 1 water 12/-, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-, 6 water 42/-.
 TOGGLE SWITCHES, sp. 2/6; sp. 3/6; sp. 4/6; sp. 5/6; sp. 6/6; sp. 7/6; sp. 8/6; sp. 9/6; sp. 10/6; sp. 11/6; sp. 12/6.

ALL PURPOSE HEADPHONES
 H.R. HEADPHONES 2000 ohms Super Sensitive 35/-
 LOW RESISTANCE HEADPHONES 8.5 ohms 39/6
 DE LUXE STEREO HEADPHONES 8 ohms 65/-

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 47/6
 200/250 v. A.G. Leadset S.A.E. Post 2/6
 Minimum Post and Packing 2/6 RETURN OF POST DESPATCH.



RADIO COMPONENT SPECIALISTS

List 1/-. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-604-1665

★ GENERAL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE ★

for Mike, Tape, P.U., Guitar
 Battery 9-15v or H.T. line 200-300v D.C. operation.
 Size 1 1/2" x 1 1/2" x 1". Response 25 c.p.s. to 25 Kc/s. 26db gain.
 For use with valve or transistor equipment.
 Full instructions supplied. 17/6 Post 2/6
 Brand new. Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS CAN TYPES
 2/850V 2/8 100/25V 2/8 16-16/850V 11/-
 4/350V 2/8 250/25V 2/8 50-50/350V 7/-
 8/450V 2/8 500/25V 2/8 80-100/350V 11/6
 16/450V 2/8 8-8/450V 4/8 38-38/250V 3/6
 32/450V 2/8 16-16/450V 4/8 38-38/450V 6/6
 25/25V 2/8 16-16/450V 5/- 32-32+32/250V 9/6
 50/25V 2/8 32+32/250V 5/- 100+50+50/250V 9/6
 SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 50, 100, 200mF 15V 2/-; 500, 1000mF 1.2V 4/8; 2000mF 25V 7/-
 CERAMIC 1pF to 0.01 mF. 2d. Silver Mica 2 to 5000pF, 9d. PAPER 350V-0.1 2d, 0.5 2/6; 1mF 3/-; 2mF 150V 3/-
 500V-0.001 to 0.05 9d; 0.1 1/-; 0.25 1/6; 0.47 5/-
 1.00V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 2/8. SILVER MICA. Close tolerance 1/2, 2.2-200pF 1/8; 500-2.200 pF 2/-; 2.700-12.500pF 4/-; 5000pF 0.01 mF 2/- each
 TWIN GANG. "0-0" 200pF+175pF 11/-; Slow motion drive 365+365 with 25+25pF, 11/-; 500V/F slow motion, standard 9/-; (small 3-gang 500pF 22/-; SHORT WAVE. Single 25pF 11/-; CHROME TELECOPI AERIAL 23in. 5/-
 TUNING. Solid dielectric. 100pF, 300pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/6; 250pF, 1/2; 500pF, 7/6; 1000pF, 0.01 mF 2/- each
 RECTIFIERS. GERTZ. COOLED. Wave. 50ma 7/6; 85ma 9/6. SILICON BYZIS 6/-; BT100 10/-
 Full wave Bridge Rectifiers 75ma 10/-; 150ma 19/6. NEON PANEL RECTIFIERS 250V, 200mA. 6/-
 XI-ON FANET INDICATORS 250V AC/DC Red, Amber 4/-
 RESISTORS. Preferred values, 10 ohms to 10 meg. 1/6 to 2/6. 1/2, 1/4, 1/8, 1/16, 1/32, 1/64, 1/128, 1/256, 1/512, 1/1024, 1/2048, 1/4096, 1/8192, 1/16384, 1/32768, 1/65536, 1/131072, 1/262144, 1/524288, 1/1048576, 1/2097152, 1/4194304, 1/8388608, 1/16777216, 1/33554432, 1/67108864, 1/134217728, 1/268435456, 1/536870912, 1/1073741824, 1/2147483648, 1/4294967296, 1/8589934592, 1/17179869184, 1/34359738368, 1/68719476736, 1/137438953472, 1/274877907344, 1/549755814688, 1/1099511629376, 1/2199023258752, 1/4398046517504, 1/8796093035008, 1/17592186070016, 1/35184372140032, 1/70368744280064, 1/140737488560128, 1/281474977120256, 1/562949954240512, 1/1125899908481024, 1/2251799816962048, 1/4503599633924096, 1/9007199267848192, 1/18014398535696384, 1/36028797071392768, 1/72057594142785536, 1/144115188285571072, 1/288230376571142144, 1/576460753142284288, 1/1152921506284568576, 1/2305843012569137152, 1/4611686025138274304, 1/9223372050276548608, 1/18446744100553097216, 1/36893488201106194432, 1/73786976402212388864, 1/14757395280444477728, 1/29514790560888955456, 1/59029581121777910912, 1/118059162243555821824, 1/236118324487111643648, 1/47223664897422328736, 1/94447329794844657472, 1/188894659589689314944, 1/377789319179378629888, 1/755578638358757259776, 1/1511157276717514519552, 1/3022314553435029039104, 1/6044629106870058078208, 1/12089258213740116156416, 1/24178516427480232312832, 1/48357032854960464625664, 1/96714065709920929251328, 1/193428131419841854522656, 1/386856262839683709045312, 1/773712525679367418090624, 1/1547425051358734836181248, 1/3094850102717469672362496, 1/6189700205434939344724992, 1/1237940041086987868944984, 1/2475880082173975737889968, 1/4951760164347951475779936, 1/9903520328695902951559872, 1/19807040657391805903119552, 1/39614081314783611806639104, 1/79228162629567223613278208, 1/158456325251134447226564032, 1/316912650502268894453128064, 1/63382530100453778890656128, 1/126765060200907557781312256, 1/253530120401815115562624512, 1/507060240803630231125249024, 1/1014120481607260462250498048, 1/2028240963214520924500996096, 1/4056481926429041849001992192, 1/8112963852858083698003984384, 1/16225927705716167396007968768, 1/32451855411432334792015937536, 1/64903710822864669584031875072, 1/129807421645729339168063750144, 1/259614843291458678336127500288, 1/519229686582917356672255000576, 1/1038459373165834713344510001152, 1/2076918746331669426688020002304, 1/4153837492663338853376040004608, 1/8307674985326677706752080009216, 1/16615349970653355413504160018432, 1/33230699941306710827008320036864, 1/66461399882613421654016640073728, 1/132922799765226843308033280147456, 1/265845599530453686616066560294912, 1/531691199060907373232133120589824, 1/1063382398121814744464266241179648, 1/2126764796243629488928532482358976, 1/4253529592487258977857064964717952, 1/8507059184974517955714129929435904, 1/170141183699490351114282598588704, 1/340282367398980702228565197177408, 1/680564734797961404457130394354816, 1/1361129469595922808914607887109632, 1/2722258939191845617829213774212664, 1/5444517878383691235658427548425328, 1/1088903576776738247131169509695056, 1/2177807153553476484262339019390112, 1/4355614307106952968524678038780224, 1/8711228614213905937049356077560448, 1/17422457228427811874098712155120896, 1/34844914456855623748197424310241792, 1/69689828913711247496394848620483584, 1/13937965782742494499269797240967168, 1/27875931565484989998539594481934336, 1/55751863130969979997079188963868672, 1/11150372626193995999415837793737344, 1/22300745252387991999883675587474688, 1/4460149050477598399976751117494976, 1/8920298100955196799953502234989952, 1/1784059620191039359990700446997904, 1/3568119240382078719981400893995808, 1/7136238480764157439962801787991616, 1/142724769615283148799356035759232, 1/285449539230566297598712071514624, 1/570899078461132595197424143029248, 1/114179815692225190039484828605856, 1/228359631384450380078969657211712, 1/456719262768900760157939314423424, 1/913438525537801520315878628846848, 1/182687705107560304063175725773696, 1/365375410215120608126351451547392, 1/730750820430241216252702903094784, 1/1461501640860482432505405806189568, 1/2923003281720964865010816012351136, 1/5846006563441929730021632024702272, 1/1169201312688385946004326404944544, 1/2338402625376771892008652809889088, 1/4676805250753543784017305619778176, 1/9353610501507087568034611239556352, 1/18707221003014175136069224791112704, 1/37414442006028350272138449582225408, 1/7482888401205670054427689916445096, 1/14965776802411340108853779832890192, 1/29931553604822680217707559665780384, 1/59863107209645360435415119331560768, 1/119726214419290720700830238663213136, 1/239452428838581441401660477326426272, 1/47890485767716288280332095465252544, 1/95780971535432576560664190930505088, 1/1915619430708651512013283818601011776, 1/383123886141730302402656763720202352, 1/766247772283460604805313527440404704, 1/1532495544566921209610666654890809408, 1/3064991089133842419221333309781618176, 1/6129982178267684838442666619572236352, 1/122599643565353696768853333391444506704, 1/245199287130707393537706666782891113408, 1/4903985742614147870754133335657822267216, 1/9807971485228295741508286661115545454544, 1/1961594297045659148301717333227090909088, 1/39231885940913182966034346664540181818176, 1/784637718818263659320686933290363636352, 1/1569275437636527318641373866580727272704, 1/3138550875273054637282747733161454545408, 1/6277101750546109274565495466623229090916, 1/125542035010922185491109109332445454544, 1/251084070021844370982218218664890909088, 1/50216814004368874196443643732981818176, 1/10043362808733774392888728745963636352, 1/20086725617467548785777457491927272704, 1/40173451234935097571554914983854545408, 1/8034690246987019514310982996770909088, 1/160693804939740390286219659935401818176, 1/32138760987948078057243139987081818176, 1/64277521975896156114486279974163636352, 1/128555043951792312228932559548327272704, 1/257110087903584624457865119096654545408, 1/51422017580716924891573182193310909088, 1/102844035161433697823146264386621818176, 1/205688070322867395646292527773243636352, 1/411376140645734791292585055548487272704, 1/82275228129146958258517011090909088, 1/164550456258293916517102221821818176, 1/329100912516587833034204443643636352, 1/658201825033175666068488887287272704, 1/13164036500663513321376977757554545408, 1/2632807300132702664275395551510909088, 1/52656146002654053285507911021818176, 1/1053122920531081065710158222363636352, 1/2106245841062162131420216444727272704, 1/4212491682124324262840428894454545408, 1/842498336424864852568085778890909088, 1/168499673284929770513761737781818176, 1/33699934656985954102753547557363636352, 1/6739986931397190820550709511510909088, 1/134799738627943816411101510223221818176, 1/2695994772558876328222020444447272704, 1/539198954511775265644404088894454545408, 1/10783979090235505312888881779090909088, 1/21567958180471010625777735581818176, 1/4313591636094202125155557116363636352, 1/862718327218840425031111142727272704, 1/1725436654377680850062222284454545408, 1/345087330875536170012444446890909088, 1/690174661751072340024888894454545408, 1/13803493235021446804977778890909088, 1/27606986470042893609955557781818176, 1/5521397294008578721991111156363636352, 1/11042794588017157443982222228727272704, 1/22085589176034314887964444467554545408, 1/4417117835206862977592888894454545408, 1/883423567041372595518577778890909088, 1/17668471340827451910375155557781818176, 1/353369426816549038207511111427272704, 1/70673885363309807641502222284454545408, 1/1413477707266196152822444446890909088, 1/282695541453239230544888894454545408, 1/56539108290647846108977778890909088, 1/113078216581296922217795557781818176, 1/22615643316259384435511111427272704, 1/4523128663251876887102222284454545408, 1/904625732650375377420444446890909088, 1/1809251465300750754840888894454545408, 1/361850293060150150968177778890909088, 1/72370058612030030193635557781818176, 1/14474011722406006038727111114272704, 1/2894802344481201207745444446890909088, 1/5789604688962402415490888894454545408, 1/115792093773248048309177778890909088, 1/23158418754649609661835557781818176, 1/46316837509299219323671111

We'll make you a £2,000 a year technician.

We're going to give 175 men just about the finest apprenticeship in the world.

If you're 15½ to 17½ (and bright at Science or Maths) you could be one of them.

We'll train you to be a top Navy technician, in electronic, air or marine engineering.

And that means you'll take equipment like radar, missiles, helicopters, diesels, computers and automation in your stride.

Our training will make you a £2,000 a year man. With more to come.

And some of the best firms in the country will be keen to sign you on, when you leave us.

Send the coupon for your free booklet. With 175 top technicians to train, you're in with a chance.

RN
ROYAL NAVY

Royal Naval Careers Service (Apprenticeships)
(830 XS1), Old Admiralty Building, Whitehall,
London, S.W.1.

Please send me, without obligation, the free booklet
on Artificer Apprenticeships.


Name _____

Address _____

Date of birth _____
(Enquiries from U.K. residents only)



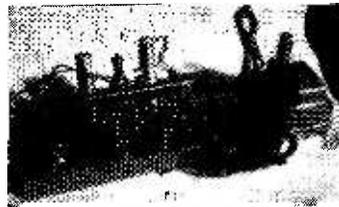AMPLIFIER FOR MAGNAVOX TAPE DECKS — 4 TRACK CAN BE USED FOR 2-TRACK



Chassis 12½ x 5½ x 4½ in. high. Plastic front panel finished in Black and "Silver". 200-250 A.C. Record/Playback amp. switch; Off/On-Tone. Vol./Me.; Vol./Gram; Mic. Input; Gram. Input; Valves 6BR7; 12AX7; 6EM84; EL84 and EZ80. Separate Output Transformer (Already wired to amp). **PRICE £12** (10/- P. & P.). 3-ohm speaker 7" x 4" 16/- extra.


STEREO AMPLIFIER type HV—2 x 3 Watts

Fully built. On off sep. vol. and tone each channel 12 x 4½ x 6 in. high. EZ80. 2 x ECL86; for 3 ohm speakers, double wound main trans: fixing flanges and base plate, suitable for crystal cart, tuner etc **£6.10.0** (8/- p. & p., 200-250V. A.C. Superior version — separate base, treble & vol. each channel with mono/stereo switch 15/- extra.




STEREO AMPLIFIER type RC— 2 x 3 Watts for 200-250V. A.C.

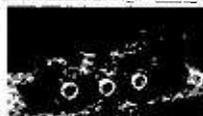Fully built. 2 x UCL82, metal rect: ganged vol. and tone cont: on-off balance. 11 x 3½ x 4 in. high. Double wound mains trans. with supporting brackets. For 3-ohm speakers. **£6** (6/- p. & p.)



MONO GRAM CHASSIS 3 WATT

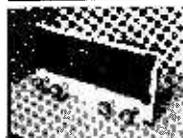3 Wave band long-med-short. Gram., 200-250V A.C. Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH61, EP89 EBC81, EL84, EZ80. Price **£10.12.6.** (7/6 p. & p.) Output trans. for 3-ohm speaker




NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans. 10" x 6" x 4" overall. Rect: ECC83, EL84, Mike and Gram Inputs. **£7.5.0.** (10/- p. & p.) For 3-ohm speaker. (For 200-250V. A.C.)

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
CLOSED WEDNESDAY. S.A.B. for enquiries please.

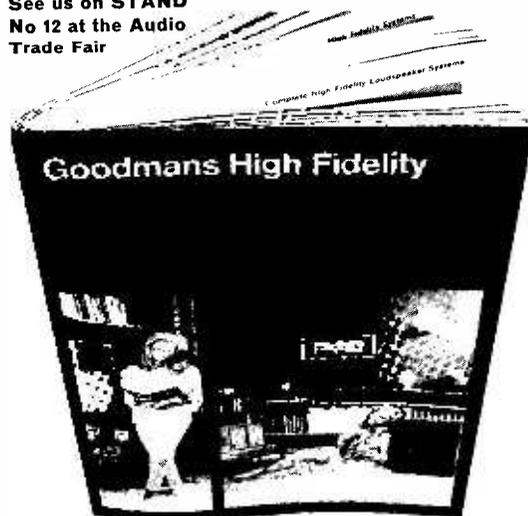See us on STAND
No 12 at the Audio
Trade Fair



Let us give you the facts

From cover to cover Goodmans Manual is packed with fascinating articles on Stereo; a beginners guide to High Fidelity; Stage-built Systems: complete details of Goodmans High Fidelity Audio products. 28 pages you can't afford to miss... and it's yours FREE!

Please send me a free copy

Name _____

Address _____

9/70



Goodmans Loudspeakers Limited

Axiom Works, Wembley, Middlesex, Tel: 01-902 1200


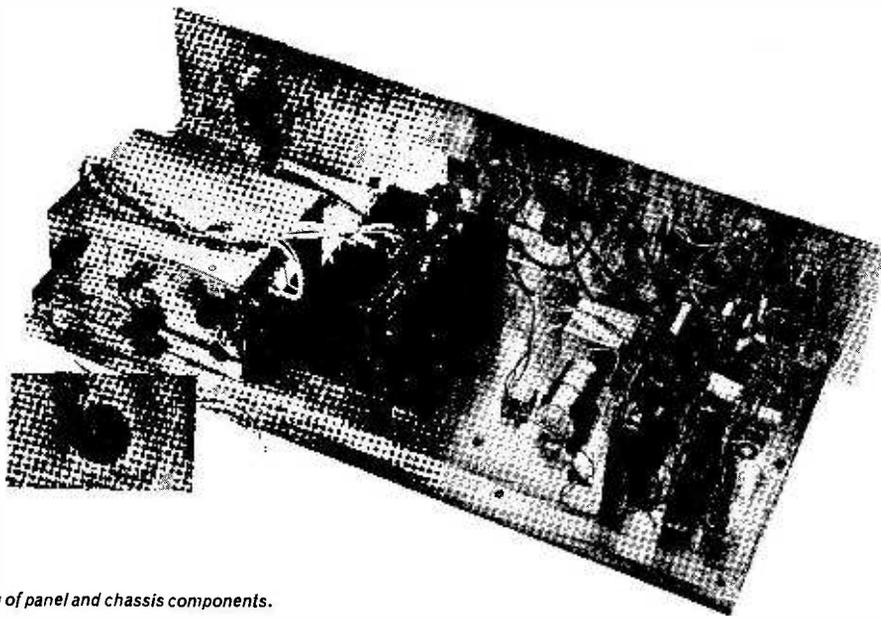


Fig. 14 : (below) Wiring of panel and chassis components.

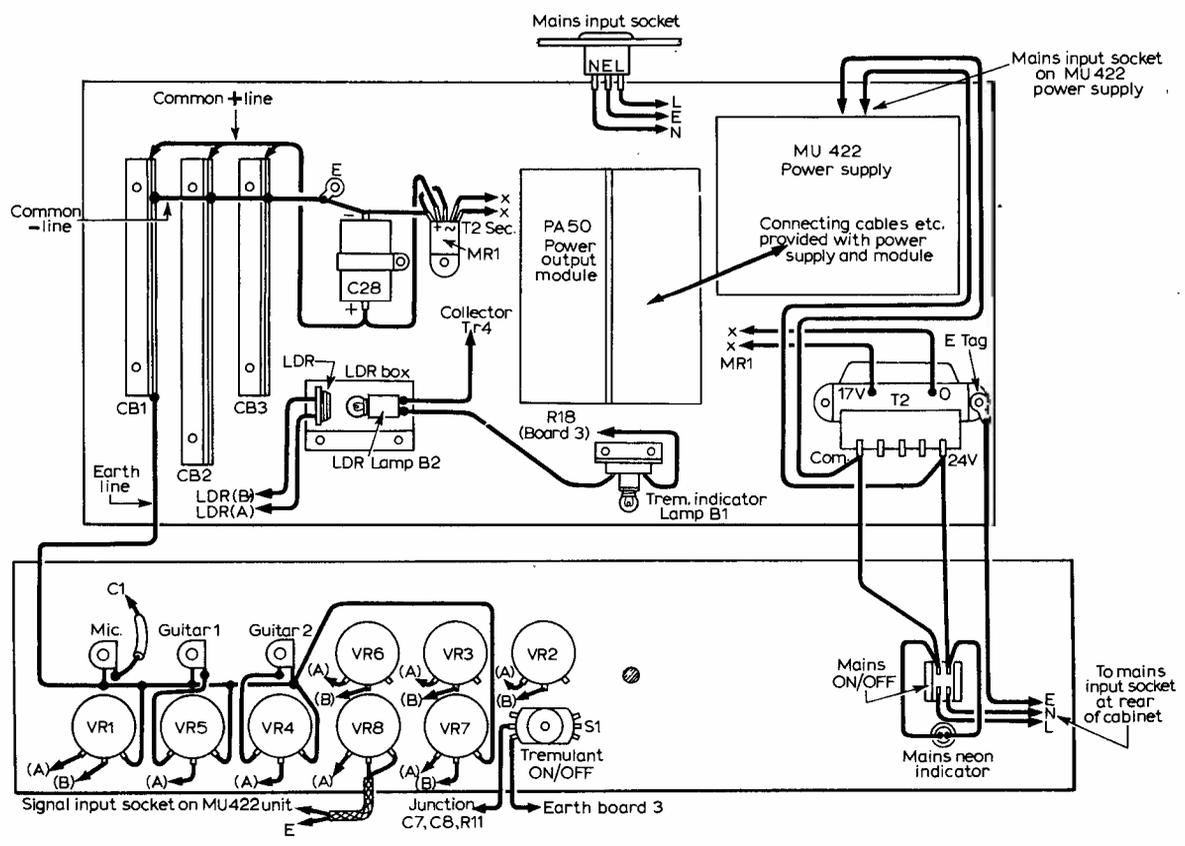

on both and the two units have only to be mounted in the position shown.

Make sure they are firmly bolted to the chassis using all the fixing holes provided.

These units complete with interconnecting cables and plugs and the only external connections necessary are those of the mains input, the loudspeaker(s) and signal lead from the master volume control VR8.

It is most important that the earthed side of VR8 is taken to earth *only* via the screening braid to the earth pin of the power unit input signal DIN socket as shown in Fig. 15B. It should be explained that although the signal input socket for the power module is located on the MU422 power supply unit it is carried through to the power module by the screened interconnecting cables.

Point to point wiring of the various controls, the pre-amplifier power supply and the mains input connections are given in Fig. 14. Note the earth connections for the signal input jacks and controls VR1, VR4, VR5 and VR7 which finally go to the common earth line on circuit Board 1. The mains supply circuits are shown separately in Fig. 16.

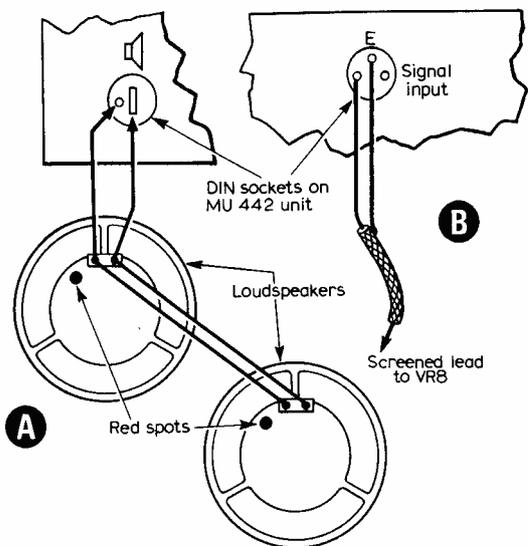


Fig. 15: Connections for speakers and signal input lead.

Loudspeakers

The terminals of the Goodmans type 12P loudspeakers specified for the PW25-50 amplifier are marked with regard to phasing. Connect them in parallel as shown with the 'red spot' terminals on the same line. Do not under any circumstances earth either of the loudspeaker connections or the loudspeaker frames. Connect only to the DIN loudspeaker socket on the left hand side of the MU422 unit as shown in Fig. 15A.

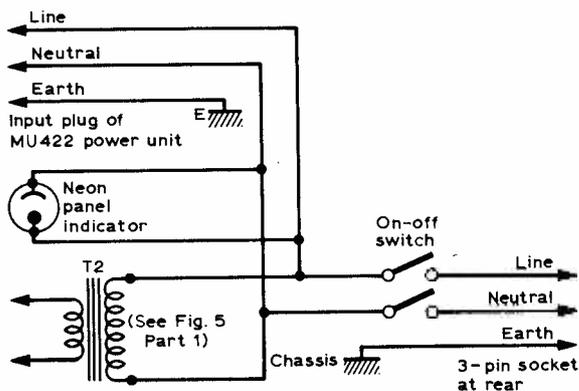


Fig. 16: Mains input wiring details.

The third and final article will deal with optional extras—the foot control tremulant, the wah-wah control and with testing the amplifier for correct performance.

TO BE CONTINUED

NEXT MONTH IN

PRACTICAL WIRELESS

P.W. 25/25 HI-FI STEREO AMPLIFIER

Especially designed for PRACTICAL WIRELESS readers, this 25 watts per channel stereo amplifier will be featured on our stand at the INTERNATIONAL AUDIO FAIR, OLYMPIA, 20th-24th October 1970.

With an impressive specification and extensive facilities including: rumble and scratch filters, inputs for magnetic and ceramic pickups, tape head, tuner etc. Inputs are switch selected and pre-amplifier stages have high overload margins on all inputs.

A ready built cabinet to contain the complete amplifier will be available to constructors.

RESISTANCE—CAPACITANCE BRIDGE

How many times have you been stumped when you tried to decipher the value on that old component from the junk box? Colour codes and markings on resistors and capacitors which have become illegible due to occasional handling often meant that they would have to be thrown out. This simple design for a fully portable checker is a must for the constructor and experimenter.

SHORT-WAVE TRANSISTOR PREAMPLIFIER

This article describes the construction of a unit which can be used in conjunction with almost all types of short wave receivers to improve their performance. It will prove of particular value, with many of the older models or "ex govt" receivers whose sensitivity is not always what one would wish.

Basically the unit is a two stage r.f. transistor amplifier with switched broad-band pre-tuned circuits to give a good measure of r.f. signal gain.

CODAR CR.70A

Communications Receiver 540-10 metres




The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £22.10.0 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the way up to and including the short wave and international amateur bands up to and including 10 metres.

The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5 1/2" x 7 1/2" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months! New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.


£22-10-0

Carriage 13/- extra

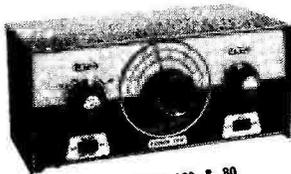
*Ideal for SWLs *5 valves (inc. two twin triodes) giving 7 valve line-up *Excellent on amateur and shipping frequencies *Calibrated signal strength meter (illuminated) *Automatic volume control *Separate B.F. oscillator for morse and S.S.B. signals *Two speed vernier tuning *Separate output for recording etc.



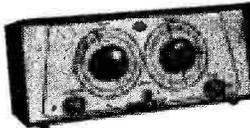
T28 RECEIVER FOR 160 & 80 METRES AMATEUR BANDS
9 transistors, bandspread 1.8-2Mc/s and 3.5-4Mc/s 12 volts, only 9" x 4" x 3 1/2", ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £16.10.0, Carr. 5/-.



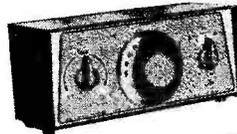CR45 MAINS T.R.F. SHORT-WAVE RECEIVER
World wide reception. *Separate electrical band-spread. *3 slow motion drives. *Output 3 watts for 2/3 ohm speaker. *Valves ECC81, FL84, EZ80. Size 12" x 5 1/2" x 7". CODAR-KIT CR.45K with 3 coils (10-28, 25-75, 60-176 metres). £10.10.0, Carr. 10/- Extra coils 6/3 each.



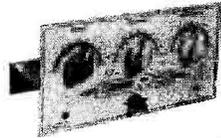R.F. PRE-SELECTOR MODEL P.R.30
1.5-30Mc/s
Provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Power requirements 180-250 volts 12mA H.T. 6.3 volts. .3 amp L.T. Size 8 1/2" x 5" x 4". Ready built complete with cables, plugs and instructions. £6.10.0, Carr. 5/-.
Self-powered P.R.30x £8.10.0, Carr. 5/-.



MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER
* Can be built in one evening. * Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price 55/-, Carr. 3/-, Extra coils 6/3.

CRC

CODAR RADIO COMPANY
UNIT 1, MEADOW ROAD, INDUSTRIAL ESTATE,
EAST WORTHING, SUSSEX, WORTHING 37315

World-wide Mail Order Service

Please supply
(tick as required)
 I enclose cheque/M.O./P.O. value of £.....
 8d stamp enclosed for leaflets

NAME

ADDRESS

POST ORDER FORM TODAY

MONO TRANSISTOR AMPLIFIER HSL.700

A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener.

6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for P.U1, P.U2, Tape, Radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 x 4 1/2 in. high.

Sensitivity: P.U1-50mV/v. 56K input impedance. P.U2-110mV/v. 1 meg input impedance. Page-110mV/v. 1 meg input impedance. Radio-110mV/v. 1 meg input impedance. Output power measured at 1Kc-6.2 watts RMS into 3 ohms. 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kcs. Continuously variable tone controls: Bass, +8db to -12db at 100c/s. Treble, +10db to -10db at 30Kc. The HSL.700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

Our Special Price **£7.19.6**

P & P. 7/6

LOUDSPEAKER BARGAINS

3" 4 ohm 10/- P. & P. 1/6. 5in. 3 ohm 16/- P. & P. 3/7. 7" 4in. 3 ohm 21/- P. & P. 4/-. 10" 6in. 3 or 15 ohm 25/- P. & P. 6/-. E.M.I. 8" 5in. 3 ohm with high flux magnet 28/- P. & P. 4/-. E.M.I. 13 1/2" 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-). P. & P. 6/-. E.M.I. 13" 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network 4 gns. P. & P. 6/-. BRAND NEW, 19in. Hi/D Speaker, 3 or 15 ohms. Current production by well-known British maker. Now with HiDux ceramic ferrobar magnet assembly 25.10.0. P. & P. 7/6 Heavy duty models: 25w. 28.10.0, 35w. 28.10.0. E.M.I. 8 1/2in. HI-FLUX DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 18/6 each. P. & P. 2/6. 12in. "E.A." TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm 37/6. P. & P. 6/-. 35 OHM SPEAKERS 3 1/2in. 14/- P. & P. 2/6.

VYNAIR AND BEXINE SPEAKER AND CABINET FABRICS. Approx. 54in. wide (usually 36" yard). OUR PRICE 15/- per yard length. P & P. 2/6 (min. one yd.). S.A.E. for samples.

MAGNAVOX DESK TYPE MOVING COIL MICROPHONE. Medium imp. Brand New. Special Price 42/- p. & p. 2/-. BALANCED ARMATURE EARPHONE. Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. ONLY 3/6. P. & P. 1/6. CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity 18/6. P. & P. 1/6. HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/- P. & P. 1/6. HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity, 39/6. P. & P. 2/6.

HONEYWELL MICROSWITCHES. S/P. C/O. Push button action. Rating 250V. AC at 15 amps. Size approx. 1 1/2 x 1/2 x 1/2 in. 5/- each. P. & P. 1/6 (6 or more post free).

SPECIAL OFFER! PLESSEY TV 20 TWIN TUNING GANG. 400pF + 146pF. Fitted with trimmers and 5:1 Integral slow motion. Suitable for nominal 470 k/c I.F. Size approx. 2 x 1 x 1 1/2. Only 8/6. P. & P. 2/6.

TELESCOPE AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7in. to approx. 56in. Maximum diameter 1/2 in. 10/- each. P. & P. 1/6. 6 section Lightweight Brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 1/2 in. 6/- each. P. & P. 1/6.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price 35/- P. & P. 6/-. MAINS TRANSFORMER. For transistor power supplies. Pri 200/240V. Sec. 9-0-9 at 500mA. 14/6. P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 17/6. P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240V. Sec. 21.5v. at 500mA. 28/6. P. & P. 2/6.

BATTERY CHARGER TRANSFORMERS. 200/240v. imp. Nominal output for 6 or 12v. batteries 3 amps. Size approx. 3" x 2 1/4" x 2 1/4". Brand New. Price 21/- P. & P. 5/-. HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4 in. FIVE for 10/- P. & P. 2/6.

STOCKISTS OF SINGULAR EQUIPMENT
Z.30 Amplifier 59/6 p. & p. 2/6. Stereo 60 Pre. Amplifier 59/6 p. & p. 6/-. PZ5 Power Supply 44 19 6 p. & p. 3/6. PZ6 Power Supply 47 19 6 p. & p. 3/6. IC.10 Integrated Circuit 59/6 p. & p. 2/6.

SPECIAL OFFER !! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Urvals front. Size 16 1/2" high x 10 1/2" wide x 6 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. 8 Gns. Carr Available 3 or 15 ohm impedance. **8 Gns. 10/-**


TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, Cir-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3dB. 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 5 amp.

PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0. All Post Free. Also available STEREO 10 + 10. As above but 10 watts per channel. PRICES: AMPLIFIER KIT £12; POWER PACK KIT £3.10.0 Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

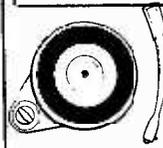For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 25dB. Solid encapsulation on size 18 x 12 x 2 1/2. Brand new complete with instructions. Price 17/6 P. & P. 2/6.



SPECIAL PURCHASE!

E.M.I. 4-SPEED TURNTABLE. Heavy 8in. metal turntable. Low flutter performance 200/250v. shaded motor (90v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. ONLY 63/- P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, EC083, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE 72/- P. & P. 6/6. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MK II. Excite motor board 14 1/2 x 2 1/2 in. clearance 2in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE 79/6. P. & P. 9/6.

10/14 WATT HI-FI AMPLIFIER KIT


A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC083, E280 and EZ90 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 27.19.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 28.19.6. P. & P. 8/6.

BRAND NEW TRANSISTOR BARGAINS. GET 15/- (Matched pair) 15/- V15/100 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NFN) 3/-. Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

VERY POWERFUL COMPACT MOTOR

For 12v. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" L x 1 1/2" dia. Free shaft 3/8" dia. x 1/4" L. Ideal for Model Makers, etc. ONLY 7/6 each. P. & P. 1/6. 3 or more post free (A few 6v. versions also available)

DE LUXE STEREO AMPLIFIER

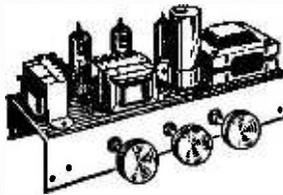

Valve line up:—2 x ECL86 Triode Pentodes. 1 x EZ80 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5 1/2". Ready built and tested to a high standard. PRICE 28.18.6 P. & P. 8/-

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. SPECIAL OFFER! Famous GARRARD 5500 fitted Sonotone STAIUC Diamond Groove Cartridge. List price over £16. Limited Number at £10. Carr. 8/6. LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER. With latest mono compatible cartridge 28.19.6. Carr. 6/6. With stereo cartridge 27.19.6. Carr. 6/6. LATEST GARRARD MODELS. All types available 1025, 1025S, 2025, 3000, AT60 etc. Send S.A.E. for latest Prices! PLINITE UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, 5500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUB PRICE 25.15.0 complete. P. & P. 8/6.

LATEST ACOS GP61/18C mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. 30/- P. & P. 1/6.

SONOTONE STAIUC compatible Stereo Cartridge with diamond stylus 60/- P. & P. 1/6.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78/RS. 38/6. P. & P. 2/-. LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/- P. & P. 2/-. Also ready built and tested. 55/- P. & P. 3/6.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TAI Peak output in excess of 15 watts. All standard British components. Built on printed circuit size 6 x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or 51 Mullard AC128D and tested pair of AC128 c/p). 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 49/6. P. & P. 3/-. Also ready built and tested. 55/- P. & P. 3/6.

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d x 4 1/2" h. Incorporates EC083, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/6.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-. HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier with a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with valves and good quality output transformer. FIVE ONLY. P. & P. 55/- 6/6.

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d x 4 1/2" h. Incorporates EC083, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/6.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-. HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier with a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with valves and good quality output transformer. FIVE ONLY. P. & P. 55/- 6/6.

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d x 4 1/2" h. Incorporates EC083, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/6.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-. HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier with a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with valves and good quality output transformer. FIVE ONLY. P. & P. 55/- 6/6.

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d x 4 1/2" h. Incorporates EC083, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/6.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-. HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier with a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with valves and good quality output transformer. FIVE ONLY. P. & P. 55/- 6/6.

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d x 4 1/2" h. Incorporates EC083, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/6.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-. HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier with a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with valves and good quality output transformer. FIVE ONLY. P. & P. 55/- 6/6.

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" d x 4 1/2" h. Incorporates EC083, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 24.15.0. P. & P. 6/6.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-. HARVERSON'S SUPER MONO AMPLIFIER

Open 9-30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

practically wireless

commentary by HENRY

The "Ah-Ha" Syndrome

ONCE I could rattle away quite happily at these monthly pieces, secure in the knowledge that the boys at the P.W. Office would do no more than rip the sense from context with their surgical blue pencils. At least, I consoled myself, they hadn't to correct the spelling.

Now, I am not so sure. What you see here, Joe, may be the polished version of what my palsied typewriter has stuttered onto the page. All because those indefatigable watchdogs of the public weal, the Consumers' Association, once told me it was not "Good Value for Money."

According to *Which*—and not even a current one, but an oldie Mrs. Henry recovered from a wardrobe drawer—this honest old machine, now stuttering out its resentment after years of faithful service, is far from being a Best Buy.

Lately, shame on them, the watchdogs of *Which* have cast their blight on things hi-fi. Their prime choice of loudspeakers, for example, completely shunned my precious DMIs and my gramophone deck, the result of many hours overtime (not only earning but choosing), gained nary the breath of a mention.



One in forty explodes

Knowing the fierce independence cherished by some reviewers, and guessing at a similar trait in others, Henry is inclined to regard the Consumers' Association as well-meaning but misguided. Unfortunately, the sort of public who write letters of sympathy to Annie Walker or believe that Waggoner's Walk exists, are inclined to take the *Which* verdict as the word of the Law.

The C.A. may say that drafts of reports are subject to verification and revision, and that it is often these drafts that receive instant publicity, but how often, we may ask, is refutation made? Recently, for example, *Which* came out quite strongly about the high breakdown rate of colour television receivers. According to their survey, one in 17 sets gives off smoke and one in 40 explodes!

Explodes, mind you, not merely dissolves into an indeterminate mix of dun and indigo, or curses visual blue streaks at its user, but . . . expands violently with loud report under influence of suddenly developed internal energy.*

Along with the technical secretary of the British Radio Equipment Manufacturers' Association, this cynical onlooker is inclined to think that the *Which* findings were unrepresentative and 'out of line with makers' reports on breakdowns'.

This gent, the appropriately named Mr. Donald Doo, claimed that when the first draft of the *Which* report was submitted to him the paragraph on smoking and exploding colour television sets was conspicuous by its absence.

'We would have challenged it straight away,' he claimed. 'We have had no reports from any of our members of problems like this.'

I'll bet they haven't. Not since the early days of colour television at least. Those of us who have



The permutations from knob-twiddling. . .

slogged at a bench are well aware that teething troubles were experienced; are even ready to admit that, despite the brochures and advertisements, modern television receivers can and do break down.

Stop and think—the average colour television receiver has four times as much in it as the monochrome equivalent. There are between twice and three times as many controls for the installer to set up. The permutations of error from quite simple knob-twiddling are disproportionately large. Signal variations at the site—ghosting, changes in level, interference, etc.—which would be tolerated in black and white become very pronounced when a chromatic scene is being viewed.

Yet how many of the 400,000 colour TV installations are totally unsatisfactory? A higher proportion than black and white—of course. But do we really believe, as *Which* implies, that 10,000 sets have 'exploded' since installation?

After all, if you read this article and feel the same way about the pontifical pronouncements of *Which* as I do, you don't say: 'Ah-Ha, I agree with the writer.'

Oh no, you say: 'Ah-Ha, Henry agrees with me.'

I hope.

*My dictionary definition.

NOTES ON THE PW UNIT-BUILT GENERAL COVERAGE RECEIVER

DETAILS of this 12-transistor 4-waveband receiver were published in the March and April 1970 issues of "Practical Wireless." These brief notes should be of assistance to anyone considering constructing the receiver.

The completed circuit shows 4 diodes and 12 transistors, with 4-band coverage, and it is apparent that quite a number of constructors feel that the wiring of the whole receiver is rather complicated. The whole circuit is not unusually complex for this type of equipment. However, it should not be overlooked that the receiver can be constructed in simpler form, and added to from time to time, and is, in fact, the manner in which the original receiver was made.

This is an important point, because it does mean that a relatively simple, straightforward superhet is initially built and wired which can be tested and used in this way. When this is found to perform correctly, other features can be added the receiver being tested each time an addition is made. Should a wiring error or other fault be present, this greatly reduces the number of circuits to be investigated.

A few further details on this stage by stage method of building the receiver should prove useful.

STAGE BY STAGE ASSEMBLY

The initial circuit is wired for one waveband only which will avoid errors in wiring the many switch contacts, and sets of coils. The SW1 range coils, for 30-11MHz, are very near the switch wafers, and tend to hinder the wiring of coils, so it is probably best to wire the SW2 range coils first, for 14-5MHz.

By omitting the r.f. stage, there are only two coils, those for the mixer and oscillator circuits. The bandswitch is set to its second position, and these two coils are wired in. Should the receiver fail to operate because of a switch or coil wiring error, only these few connections need be checked.

When the receiver is working correctly on the SW2 range, add the pair of coils for the SW3 range, and test to see that proper results are obtained. Then add the m.w. range, and test again. Finally, the SW1 range coils are wired in.

When the r.f. stage has been added, wire in the SW2 aerial coil, and test the receiver. Should a fault be present, only the few new items introduced need be checked. Then add the other aerial coils, one at a time, testing the receiver after each addition.

This is much better than wiring in the twelve coils, for four bands with r.f. stage, then finding some obscure fault exists in coil or bandswitch connections.

As described, the receiver is easily wired as a 6-transistor superhet, for one band. It will then have Tr2 (mixer), Tr3 and Tr4 (i.f. amplifiers), Tr10 (driver) and the output stage Tr11/Tr12. Only the a.m. diode and a.g.c. rectifier D2 need be connected. This means that Tr1 (r.f. amplifier), Tr5 (meter amplifier), Tr6 and Tr7 (product detector) with b.f.o. Tr8, and a.f. amplifier Tr9, are not needed, neither is the multi-way function switch, nor diodes D1, D3 and D4. The circuit, in this simplified form, is capable of excellent reception and volume.

The additional features can be added in any order preferred. Probably the r.f. amplifier, Tr1, will be found most useful. After this, Tr9, for additional audio gain, may be included.

Adding Tr6, Tr7 and Tr8, will then allow c.w. and s.s.b. to be resolved, as the use of the diode D2 allows reception only of a.m. signals.

Remember to test the receiver after each addition. Then if a fault or error has been introduced, it must be in the part of the circuit last added. By proceeding in this way there will be no need to check the whole receiver, but only some relatively small part of it.

AUDIO TRANSFORMERS

The driver and output transformers listed are no longer made. Fortunately many transformers suitable exist for OC81D driver and 2xOC81 and similar output transistors. The Weyrad LFDT4 driver and OPT1 output transformers will be found suitable. Connecting data for the LFDT4 appear in Fig. 1, connections for the OPT1 remaining unchanged.

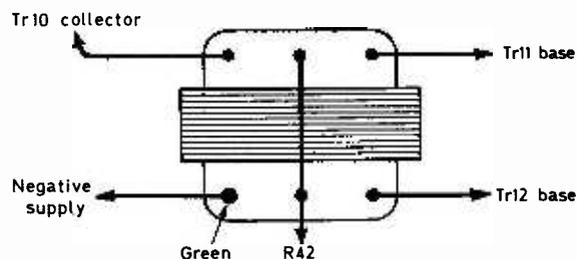


Fig. 1: Connections to alternative audio driver transformer

As is usual with this type of circuit, operation of the output pair is critically dependent upon the relative values of R42 and R40/R41. If there is distortion, R42 should be increased slightly to about 100 ohms.

Any ordinary 2 or 3ohm speaker is suitable, preferably a reasonably large unit, in a cabinet.

AERIALS

Long-range reception is possible with the telescopic aerial, especially on the h.f. ranges. However, for the best possible results with weak signals, some form of external aerial should be added. This can be of any type normally employed with a communications receiver such as a random length external wire, or an end-connected wire with tuner, or a dipole or tuned doublet, etc. Any of these aerials can be expected to give an improvement in the signal strength of several S-points. ■

INCREASE YOUR KNOWLEDGE



Established 1891


MANY COURSES TO CHOOSE FROM incl.
 RADIO & TV ENGINEERING & SERVICING,
 TRANSISTOR & PRINTED CIRCUIT SERVICING,
 COLOUR TV SERVICING, ELECTRONICS,
 NUMERICAL CONTROL, ELECTRONICS,
 TELEMTRY TECHNIQUES, CONTROL SYSTEMS,
 ELECTRONICS FOR AUTOMATION,
 COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

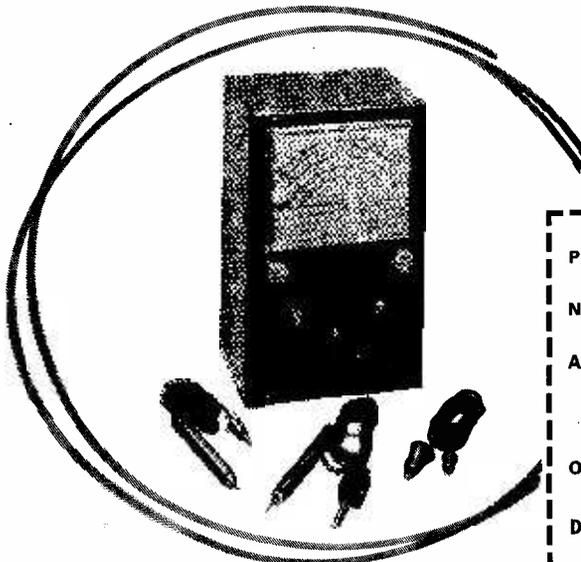C. & G. Telecommunication Technicians' Certs
 C. & G. Electronic Servicing
 R.T.E.B. Radio/TV Servicing Certificate
 P.M.G. Certificates in Radiotelegraphy
 Radio Amateurs' Examination
 General Certificate of Education, etc

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments, incl. professional-type valve volt meter (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
 Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8

10/70

MICRO SWITCH

5 amp. changover contacts, 1/8 each, 18/- doz. 15 amp Model 8/- each or 81/- doz.



TOGGLE SWITCH

3 amp 250v. with fixing ring. 1/6 each, 18/- doz.

CONSTRUCTORS PARCEL

1. Plessey miniature 2 gang tuning condenser with built in trimmers and wave gang switch. 2. Ferrite slab aerial with coils to suit the above tuning condenser. 3. Circuit diagram giving all component values for 6 transistor circuit covering full medium wave and the long wave band around Radio 2. The three items for only 7/6d which is half of the price of the tuning condenser alone.

SLOW MOTION DRIVES

For coupling to tuning condensers etc. One end 4in. shaft, the other end fits to a 3in. shaft with grub screws. Price 4/6 each 48/- dozen.

LARGE PANEL MOUNTING MOVING-COIL METERS

Size 5in. x 4in. Centre zero 200-0-200 micro amp made by Sangamo Weston. Regular price probably 28. Our price 55/6. ditto but 100-0-100 78/6.

A.C. AMMETER

0-5 amps, flush mounting—moving iron. Ex equipment but guaranteed perfect 29/6.

CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet ideal for making power packs etc. as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in. x 5in. 1/6 each. 15in. x 5in. 4/6d each.

6KV AUTO-TRANSFORMER

in ventilated sheet steel case—tapped 110v-140v-170v-200v-230v. Ex equipment but guaranteed perfect 119.10. carriage at cost.

PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.



REED SWITCHES

Glass encased, switches operated by external magnet—no cold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 200 volts. Price 2/6 each. 24/- doz. Standard. 2in long x 3/4in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each, 18/- per dozen. Flat. Flat type, 2in. long, just over 1/16in. thick, approximately 1/4in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each. 28 per dozen. Small ceramic magnets to operate these reed switches 1/8 each. 18/- dozen.

0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.



SUB-MINIATURE MOVING COIL MICROPHONE

as used in behind the ear deaf aids Acts also as phone size only 1/4in. x 1/4in. x 1/4in. Regular price probably 23 or more. Our price 19/6. Note these are ex-equipment but if not in perfect working order they will be exchanged.

CHART RECORDER MOTOR

Small 2" diameter (approx) instrument motor with fixing flange and spindle (1" long, 1/8 diameter) integral gear box gives 1 rev per 24 hours. 19/6

IGNITION (E.H.T.) TRANSFORMER

made by Farneko Ltd., Primary 240V 50 cps. Secondary 5kV at 23 mA. Size approx. 4 1/2" x 3 1/2" x 2 1/2" thick. 29/6 plus 4/6 p. & p.

12V EXTRACTOR FAN BY DELCO

Ideal for ventilation in Caravan, Car or Boat. 6 Bladed 5" diameter fan inside heavy duty cylinder with 3 point fixing lugs. 5 1/2" diameter fixing hole. Length approx. 8 1/2". Exceptional bargain 27/6 plus 5/6 post and insurance.

NEED A SPECIAL SWITCH


Double Leaf Contact. Very slight pressure closes both contacts. 1/3 each, 12/- doz. Plastic push-rod suitable for operating. 1/6 each, 9/- doz.

COMPUTER MULTI-CORE CABLES

12, 14/0076 copper cores, each one insulated by coloured P.V.C. then separately screened, the 12 metal braided cores laid together and P.V.C. covered overall making cable just under 1/2 in. dia. but quite pliable. Price 7/6 per ft. Any length cut. Other sizes available 7 core 5/- ft., 6 core 4/- ft. 4 core 3/6 ft.

RECHARGEABLE TORCH

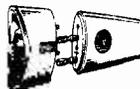Neat flat torch, fits unobtrusively in your pocket, contains 2 Nicad cells and built-in charger. Plugs into shaver adaptor and charges from our standard 200/240 volt mains. American made, sold originally at over 4 dollars. Our price only 19/6 each.



INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of which is well over 21 each. Full circuit details of the ICs are included and in addition you will receive a list of 60 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only 21 post paid; or List and all data 10/- post free. Credited when you order IC's value of 30/- and upwards.

HI-FI SPEAKERS (15, 30, 40 & 100V)

FULL FI 18 INCH LOUSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-coat metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone diameter three—Freq. response 30-10,000 c.p.s.—Speifer 3 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. on pitch circle 1 1/4in. diam.—Overall height 5 1/2in. A 26 speaker offered for only 28.19.6 plus 7/6 p. & p. 12in. 40watt 28.19.6 carr. 8/8. 15in. 25 watt 27.19.6 carr. 10/6. 18in. 100 watt 219.10.0 carr. 30/-.



THIS MONTH'S SNIP

25 Amp Electrical Programmer

Learn in your sleep! Have Radio playing and kettle boiling as you awake—switch-on-lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp switch, the switch continuously variable not off time of which can be delayed up to 12 hours (controllable by a remote control). Similarly the switch-on time can be delayed. This is a beautiful unit, size 8 1/2" x 8 1/2" x 2 1/2" deep. Metal encased, glass fronted with chrome surround. Offered at 47/6 plus 3/6 postage and insurance.



MOTORISED SWITCH

For Animated signs etc.

This is motorised programmer switch, mains operated, with six 15 amp changover contacts operated by triggers on a rotating drum. Six triggers will put switches up and another six triggers will put switches down. Also simple on/off operation or changovers are possible. The triggers are exactly set to any position around the drum which is rotated by a one rev. per hour motor. (Motors with other speeds available). A beautifully made precision switch which probably costs in excess of 20. Limited quantity only 29.15. each post free.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with neon warning light (in metal box). Takes standard 13 amp fused plugs. Supplied complete with 7 feet of heavy cable. 39/6 wired up, ready to work plus 4/6 post & insurance. 5 amp 3 pin model 35/-, 15 amp 3 pin model 45/-

BARGAIN OF THE YEAR

MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/2 x 2 1/4 x 1 1/4in.—complete with soft leather zipped bag. Specification—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kcs. Sensitivity: 5 mV/m. Intermediate frequency: 465 Kcs or 465 Kcs. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only 24/6 less batteries plus 2/6 post 6 for 27 post free.



THE 5-5 WATT STEREO AMPLIFIER

Made by one of our most famous makers for a de-luxe player. This amplifier has a quality of reproduction much better than average. Using a total 16 transistor and a generous sized mains power pack. Controls include bass, treble, balance and volume. Suitable for 8-16 ohms impedance speakers with crossovers for tweeter mid-range and bass thus giving option of 1, 2 or 3 speakers per channel. Offered at about one third of its original price only 29.19.6d. plus 6/8d post and insurance.

OUT OF SEASON BARGAIN

3kW TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and lower heaters costing 215 and more. We have a few only. Comprises motor, impeller, 2kW. element and kW. element allowing switching 1, 2 and 2kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 59/6. Model as above except 2 kilowatts 29/6. Postage and insurance 6/6. Don't miss this.



Where postage is not stated then orders over 25 are post free. Below 25 add 2/9 Semi-conductors add 1/- post. Over 21 post free. S.A.E. with enquiries please.

MAINS TRANSFORMERS

Note all these are first grade Transformers and all have normal 200/240 volt 50 cycle primary. Mains Transformer Type No. 56796 Upright mounting, size 3 x 2 1/2 in. approximately. 2 secondaries one 28 volt 1 amp and the other 5.5 volt 1.5 amp. Earth screen between primary and secondaries—this transformer will power a 5.5 watt stereo amplifier (circuit diagram available, price 8/6). Suitable output transformer is type 56787 described below. Our price 17/6. Plus 4/6 post. Mains Transformer Type No. 56788 Chassis mounting type, size approximately 3 x 2 1/2 x 3in., 2 secondaries one 30 volt at 80 mA and other 6.3 volts 1.5 amp. Earth screen between primary and secondaries. This will power a 5 watt amplifier (circuit available 8/6). Matching OPT. 56784 described below. Price 18/6 plus 4/6 post. Mains Transformer Type No. 56695 Upright mounting, size approximately 4 x 3 x 3 1/2in. 2 secondaries 275-0-275 at 80 mA and 6.4 volts at 3.1 mA. There is a screen between primary and secondaries. This is a partner to output transformer 56684 described below. Price 19/6 plus 4/6 post.

OUTPUT TRANSFORMERS

OPT. ref. 56684 Chassis mounting—size 2 x 2 x 2in. approximately 7 watts. A push pull transformer matching 2/EL54 or similar valves to 15 ohm Loud Speaker 14/- no extra for post if ordered with Transformer 56695. Circuit diagram of amplifier available, price 8/6. OPT. r. l. 56787 Upright mounting, size approximately 3 1/2 x 2 x 2in. Matching impedance 60 ohm to 15 ohms. 5 watts output using transformer type AD40 (Circuit diagram available price 2/6). Price 8/6 each, no extra for postage if ordered with mains transformer type 56788. OPT. ref. 566004 Upright mounting, size approximately 2 x 2 1/2 x 2in. Primary impedance 60 ohm, secondary impedance 3 ohm, otherwise this is as 56787. Price 8/6. OPT. ref. 56784 Chassis mounting, size approximately 2 1/2 x 2 x 1 1/4in. Primary 500 ohm centre tapped. Ratio 27/1.5 watts output using twin EL50 or similar. Price 12/6. No extra for postage if ordered with 56735.

HEAVY DUTY MAINS TRANSFORMER

30V. 37V. Primary tapped 200/240 in 10v. steps. A really beautiful core transformer. Made by Farneko, impregnated and varnished. Weight approx. 50 lb., size approx. 8in. wide 6 1/2in. deep and 8 1/2in. high. Metal framed for free standing and fitted with E.S. screen. Probably priced 240-260 from Farneko. Ex equipment, but perfect. 217.10 each, plus carriage at cost.

50 CYCLE TO 60 CYCLE INVERTERS

For operating electronic instruments and other equipment suitable for 60 cycles 115 v. from 230/240 50 cycle mains. These units have an output of 115 volts A.C. and will handle a load of up to 100 watts. These are precision made and have a reed type frequency meter which vibrates when the frequency is exactly 60 c.p.s. Adjustment of the frequency is by a knob on control panel. Input by 3 core output from 3 pin socket. Original cost of this in excess of 260. A limited quantity available 117.10 each.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 8/6 each. 26/- dozen, your assortment.

WATERPROOF HEATING ELEMENT

28 yards length 70W. Self-regulating temperature control. 10/- post free.

MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. 19/6 each.

AUTO ELECTRIC CAR AERIAL

With dash board control switch—fully extendable to 40" or fully retracted. Suitable for 12V positive or Neg. earth supplied complete with fitting instructions and ready wired dash board switch 25.18.6 plus 5/- p & p

PRECISION MOTOR

Manufactured — as used in record decks and tape recorders—ideal also for extractor fan, blowers heaters etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered, 12 and over post free.



ELECTRONICS (CROYDON) LTD
Dept. PW, 266 London Rd., Croydon CRO 2TH
Also 102/3 Tamworth Road, Croydon

a good communications receiver with either internal or external 100kHz marker of known accuracy are the basic alternatives. If an existing v.f.o. of known accuracy is obtainable, this can make things much easier.

Having connected the necessary d.c. supply to the v.f.o., set the trimmer capacitor to about mid-point and the tuning capacitor to maximum value (vanes fully meshed). Loosely couple the output to the receiver aerial input and allow to warm up for 10 to 15 minutes. Next search around 3.5MHz on the receiver dial, the b.f.o. being switched in first. When the beat note is heard, note the frequency on the receiver dial. If no beat note can be found, check that the v.f.o. output is present using an oscilloscope or valve-voltmeter.

With the beat frequency noted, set the receiver dial accurately to 3.5MHz using the 100kHz marker to ensure accuracy. Now adjust the trimming capacitor in the v.f.o. until the beat note is obtained on exactly 3.5MHz. If the original beat frequency was high, VC2 should be increased and if it was low, decreased. The setting of VC2 should be carried out with care, the trimming tool being removed after each adjustment as a small hand capacity effect is almost unavoidable. With this frequency correctly set on zero beat, the v.f.o. dial can be marked at this point. No further trimming should now be required.

The receiver dial is next set to 3.6MHz, again using the crystal marker, and the v.f.o. tuning capacitor slowly adjusted until the beat note is again heard. Having set VC1 for exactly zero beat, mark the appropriate point on the scale. This procedure is repeated for 3.7 and 3.8MHz. The upper limit of 3.8MHz will vary slightly between different units due to differences in stray capacitance.

The mid-points of 50kHz steps and 10kHz subdivisions can only be accurately marked if the receiver dial has suitable calibration points or if an existing v.f.o. is available. As the scale divisions are almost linear, however, reasonably accurate subdivisions can be obtained geometrically. When the main scale is fully calibrated, the harmonic calibrations for the other bands (7MHz, 14MHz, etc.) can be completed on the lower scales of the v.f.o. dial. ■

CORRIGENDA

FREQUENCY METER—MAY 1970

Under the heading "Construction" the sentence "Note the breaks in the copper strip at holes D9, D15 and E4" should read "at holes C14, D3 and D9."

SUMS AND CIRCUITS—JUNE 1970

The voltage and current waveforms shown in Fig. 3.3 and 3.4b should be interchanged

In the July issue of the same article the equation on page 192 reading $-1+0.3010=0.6990$ should read $-1+0.3010=-0.6990$.

TEN OR FIFTEEN METRE CONVERTER—JUNE 1970

Figure 1 and the components list should show R3, R8 and R10 as $1k\Omega$ and not $10k\Omega$.

LIGHT OPERATED SWITCH—JULY 1970

The value of R7 both in the circuit and the components list should read $4.7k\Omega$ and not $4.7k\Omega$.

AUDIO EXPANDER/COMPRESSOR—AUGUST 1970

In the components list C11 should have read 100pF and not 100μF. The circuit is however correct.

In Fig. 11, the screening of the wire connected to the slider of S1 section C should be connected to the other screen wires and not to the slider of S1 section B.

boards in the event of a faulty contact or circuit failure.

The last stage is to fit aluminium or wooden rails, one on each side of the case, to prevent the unit tipping forward when the pedals are pressed. Full downward pressure on a pedal should bring it to within half inch or so of floor level. Further pressure would tip the unit forward, hence the need for the rails as shown in Fig. 16.

Amplifier Requirements

Because of the very low frequency of the pedal bass notes a sizeable loudspeaker in a suitable enclosure is necessary if the true bass fundamentals are to be audible. Small organs like the Philicorda have only small loudspeakers which are not suitable for bass reproduction. For organs of this calibre it is best to build a suitable amplifier with an output of 5 to 10 watts which can be incorporated within the speaker enclosure. The speaker should be 10 to 12in. in diameter.

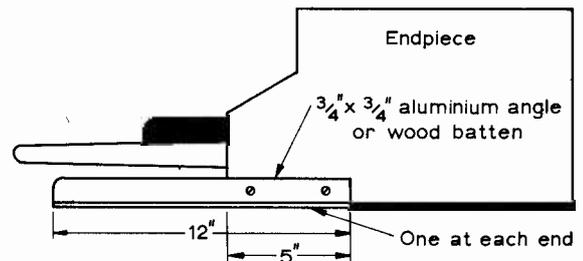


Fig. 16: Fitting of rails to case.

There is no reason why the pedal bass unit described in this article should not be integrated with an amplifier and speaker so designed as to fit beneath small organs like the Philicorda. For portables fed into large power amplifiers with sizeable speakers it should only be necessary to connect the pedal bass unit to a suitable input on the amplifier.

There is of course the question of volume control or 'expression' whilst playing. For small organs where the overall sound output is relatively low it will be sufficient to set the pedal bass sound to an arbitrary level. A pedal type volume control could be used or an extra volume control mechanically coupled to an existing pedal. ■

PROJECT

Autumn

compete
for the
Practical Wireless
"Designer's Trophy"

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.

ALTHOUGH we have described two general-purpose amplifiers in this series, tone control facilities have not been incorporated, mainly due to our limitation on cost. The tone control stage described here is a general-purpose one which can be added to most transistor amplifiers in the early stages. The gain, with the controls in their middle settings, is very small as the amplification of the stage is nearly all used as negative feedback to alter the tone. The circuit shown is not very original, in fact it is widely used in commercial amplifiers.

Performance of this type of circuit is excellent; with reference to 1kHz, frequencies of 100Hz can be boosted or cut by up to 15dB and the same degree of control is available at 15kHz. A low noise transistor, a BC169C, is used so noise introduced by this additional stage is negligible.

THE CIRCUIT

For those unfamiliar with this type of circuit, a quick glance will probably lead to rapid bafflement, but basically the design is simplicity itself.

The input is coupled to the d.c. blocking capacitor C1 and is then applied by one path to the base of the transistor through C3 and a part of VR1, a 100kΩ potentiometer. The actual part of VR1 that it passes through depends on the setting of the control. By another path the signal reaches the transistor via R2 and C5. It will be seen that C5 is paralleled by a part of VR2, again depending on the setting of the control.

These combined signals are applied to Tr1 which has R3, a 10kΩ resistor acting as the collector load and R4 as the base bias. The output is taken from the collector via C7 to the existing volume control.

Also connected to the collector of Tr1 is C6. Now in a common emitter amplifier (which is what we are using here) there is phase inversion, that is the signal at the collector is out of phase with the signal applied to the base. This anti-phase signal is applied to the other side of VR1 and VR2 via an identical network to the one that fed the original signal to these controls.

It will be seen then that both controls are able to select either very little or a considerable amount of the out-of-phase signal and since these networks are frequency selective we are able to achieve a considerable amount of control over the tone.

Careful scrutiny of the circuit will show that a certain degree of negative feedback is applied to the transistor through R4, the base bias resistor, but this is quite small and anyhow is not frequency selective. Many designs decouple this a.c. feedback by using two resistors in series, their common junction being connected to earth via a high value capacitor, such as 100μF; in practice the author has found this to be unnecessary.

No. 18

ADD-ON TONE CONTROL

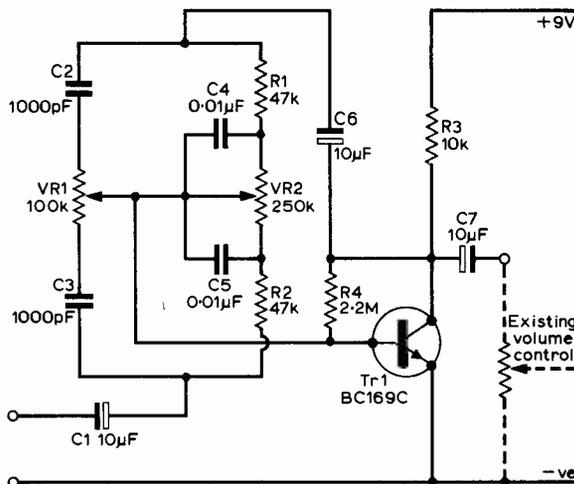


Fig. 1: The circuit of the add-on tone control. VR1 is the treble control, VR2 the bass control.

★ components list

Resistors:

R1 47k Ω	R3 10k Ω
R2 47k Ω	R4 2.2M Ω
All $\frac{1}{8}$ or $\frac{1}{4}$ watt, 5% types	
VR1 100kΩ linear pot. Treble control	
VR2 250kΩ linear pot. Bass control	

Capacitors:

C1 10μF 12V	C5 0.01μF
C2 1,000pF	C6 10μF 12V
C3 1,000pF	C7 10μF 12V
C4 0.01μF	


Transistor:

Tr1 BC169C or BC109


FREQUENCY SELECTIVE NETWORKS

There are probably many readers who are unsure what we mean by "frequency selective networks." In practice these are very simple and can be calculated and designed by even the raw beginner. A.C. theory can be very complicated and describing, from first principles, the operation of capacitors would be hard and is anyway unnecessary; just take it as a fact that the impedance of a capacitor is directly proportional to the frequency and the impedance, in ohms, is equal to $1/(2\pi fC)$ where f is the frequency and C the capacitance in Farads; so that C2 and C3 at 100Hz have a "resistance" of about 1.6MΩ and at 10kHz, 16kΩ. Similarly C4 and C5 have a "resistance" at the same two frequencies of 160kΩ and 1.6kΩ respectively. Substituting these "resistance" values instead of the capacitors we are left with a potential divider (but only of course at a particular frequency) and it will be seen that the gain can be changed by the setting of the controls VR1 and VR2.

SINCLAIR IC-10

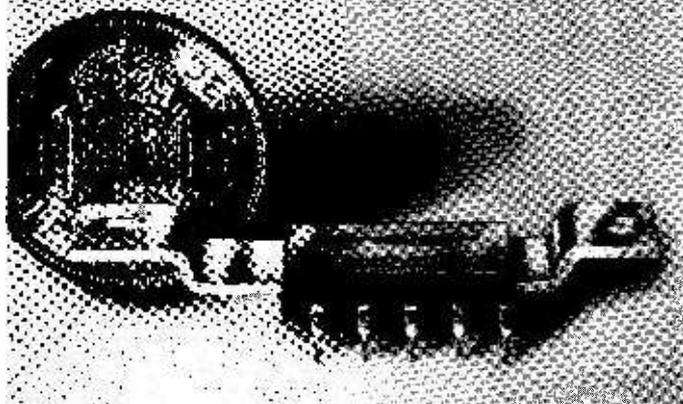

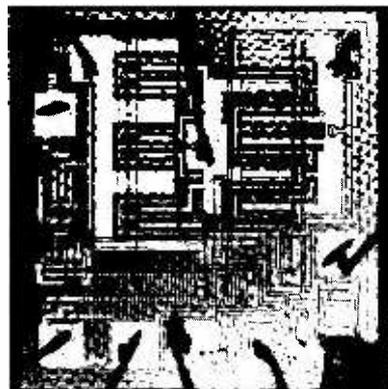MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required as part of the process of producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. This enables us to cover every IC-10 with the Sinclair guarantee of reliability.

■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz \pm 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 · 0.4 · 0.2 inches. 25.6 · 10 · 5 mm.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR


IC.10 with *IC.10 manual* **59/6**

POST FREE

sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET ROAD · CAMBRIDGE
Telephone 0223 52731

Project 60

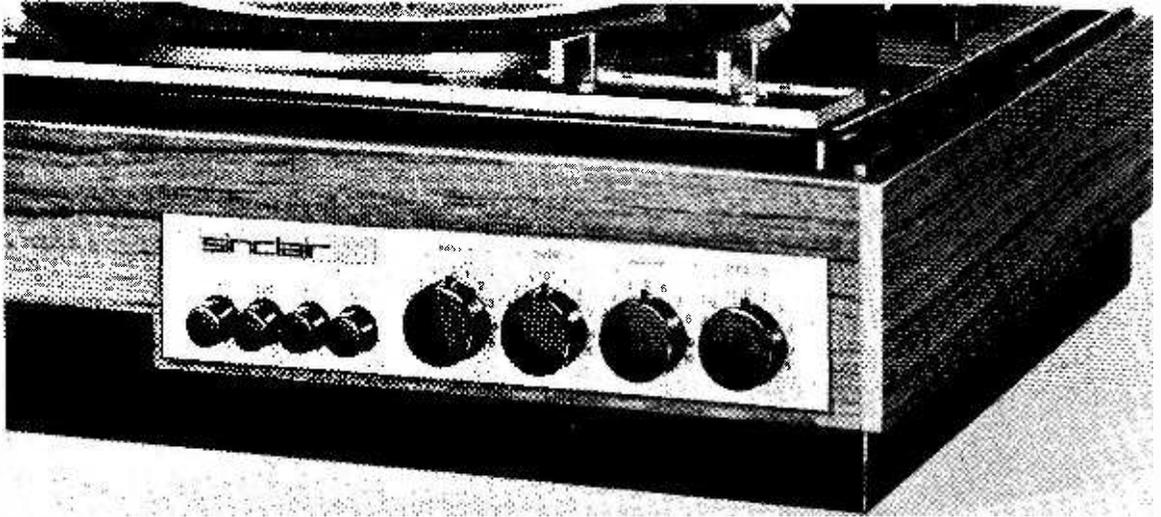

Laboratory standard modular high fidelity

Sinclair Project 60 comprises a range of modules which connect together simply to form a compact stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance and now the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities. The modules are: 1. The Z.30 and Z.50 high gain power amplifiers. 2. The Stereo 60 preamplifier and control unit. 3. The Active Filter Unit. 4. 4 supply units—PZ.5; PZ.6; PZ.7 and PZ.8. In a normal domestic application, there will be no significant difference between PZ.5 or PZ.6 unless loudspeakers of very low efficiency are being used, in which case the PZ.6 will be required. For assemblies using two Z.50's there is the PZ.8 supply unit to ensure maximum performance from these amplifiers. No skill or experience are needed to build your system and the Project 60 manual gives all the instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as new additions are made to the range. A stereo F.M. tuner is next to come. These and all other modules introduced will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe, Project 60 prices are remarkably low.

How to assemble and use Project 60 modules to best advantage in the above and other applications will be found in the fully descriptive Project 60 manual included with Project 60 systems. This 48 page manual is available separately, price 2/6d including postage.

System	The Units to use	In conjunction with	Your Project 60 Units will cost
A Car Radio	Z.30	Existing car radio, Sinclair Micromatic	89/6
B Simple battery powered record player	Z.30	Crystal pick-up, 12 V or more battery supply and volume control	89/6
C Mains powered record player	Z.30 and PZ.5	Crystal or ceramic P.U. Vol. control etc.	£9.9.0
D 20+20 watts RMS stereo amplifier for most needs	Two Z.30s, Stereo 60 and PZ.5	Crystal, ceramic or magnetic P.U., most dynamic speakers, FM tuner, etc.	£23.18.0
E 20+20 watts RMS stereo amplifier for use with low efficiency (high performance) speakers	Two Z.30s, Stereo 60 and PZ.6	High quality ceramic or mag. P.U., F.M. Tuner, Tape Deck, etc. All dynamic spkrs.	£26.18.0
F 40+40 watts RMS deluxe stereo amplifier	Two Z.50s, Stereo 60 PZ.8 and mains transformer	As for E	£32.17.6
G Outdoor public address system	Z.50	Microphone, up to 4 P.A. speakers, 12V car battery with or without converter, controls	£5.9.6
H Indoor P.A	One Z.50, PZ.8 and mains transformer	Mic., guitar, heavy duty speakers etc., controls	£17.8.6
J High pass and low pass filters	AFU	D, E or F as above	£5.19.6
K Stereo F.M. tuner	To be released shortly		

sinclair

SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE

Telephone 0223 52731

TRANSISTORS etc.		OC26	7/6	OC81	2/6
AC107	3/-	OA5	1/6	OC28	8/6
AC126	2/3	OA9	1/6	OC35	8/6
AF115	3/-	OA10	1/6	OC44	2/9
AF116	3/-	OA47	1/9	OC45	2/3
*AF117	4/-	OA81	1/6	OC70	2/3
BFY18	4/6	OA85	1/6	OC71	2/3
BFY61	4/-	OC23	6/6	OC72	2/3
CE113	2/6	OC25	6/-	OC73	2/3
				OC75	2/3
				OC81D	2/6
				OC82D	2/6
				OC140	5/-
				OC169	3/6
				*OC170	4/-
				OC171	2/3
				OC202	4/6
				TK22C	

*WITH 4 LEADS. Many more transistors in our current list.

SILICON DIODE RECTIFIERS—BY 100—2/10 EACH

SIX AMP. SERIES: BY213 300 PIV 4/- BY212 600 PIV 5/-
BY211 900 PIV 6/- BY210 1200 PIV 7/-
THYRISTORS: 5 AMP. SERIES 100 PIV 7/6 200 PIV 9/- 300 PIV 10/6 400 PIV 12/-
800 PIV 25/-
10 AMP SERIES. 50 PIV 10/- 100 PIV 12/6
20 amp & 30 amp Series in our list.

(POSTAGE PACKING & INS. ON ALL ABOVE, 1/- UP TO 11, 12 & OVER Paid
MULLARD STACK F. W. BRIDGE 12A 100 PIV 39/6 (3/-)

ELECTROLYTIC CONDENSERS

Full details of many types from 6d each in our list (see below).
SUB-MIN TRANSFORMER: Output (3 Ω for OC72 etc) 2/9 driver, 3/- (up to 6 either 1/-).
MULTIMETER: 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-5/25/50/500/1K volts D.C.
●10/50/100/500 Ω K volts A.C. ●50μA 2.5mA/250mA D.C. ●0-6K Ω/6 meg Ω.
●100mV/1mA. ●30 to 5x231B. ●Complete with test leads and instructions.
●Over-load protected 1970 model with every refinement **£4.12 6 (2/6)**. JUNIOR MODEL at 4/8 (2/6). 1000 Ω/V described in free list. Spec. subject to slight variation.

SOLDERING IRON. Slim Mod. British High speed, 8 1/2 in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use. 21/- (1/6).

DIAMOND STYLII

Replacements for BSR TC8LP, TC8/S and TC8LP/STEREO;
COLLAJO "O": RONETTE BP40LP; GARRARD GC2LP and GC8LP; ACOS GP67/67; all at 7/6 each (1/-). ACOS GP73 and GP91; BSR ST4 (ST3, ST5, ST9), ST8 (ST9), SOTONE STA, ST A and STAC; PHILIPS AG3306, 3060, (3063, 3066, 3301, 3302, 3304), all at 15/- (1/-). All are of the very highest quality.
DOUBLE DIAMOND TYPES: If you don't use the 78 side—this is the best buy—now available only in ST4 (ST3, ST5), ST9 (ST8), ST A, STAC. 3306. GP91 (for GP92, 93 and 94 Cartridges) and GP91SC for GP91SC cartridges. 30/- each (1/-)
SAPPHIRE all the above 7/6 types only, also ACOS GP27 at 3/3 each (1/-). ACOS GP91 at 7/6 (1/-). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES

All fitted Styl II and Standard fittings, Mono GP67/2, Stereo GP67/2. ●15/-. ●Stereo compatible Mono which also plays Stereo records monaurally with min. wear. GP91SC, 21/-. ●latest Stereo GP93, 25/6. ●Ceramic Stereo top quality for expensive outfits, GP94, 38/6. ●Sonotone stereo 9TACH diamond fitted cartridge 55/- (all at 1/-). More diamond types in list. Goldring cartridges, magnetic types, 850,800, 800E & 800 Super E in stock.

TWO STATION TRANS. INTER-COM. Excellent baby alarm. Instant, easy fitting with leads, 12/- and battery. All require 32/6 (3/-).

TRANSISTOR AMPLIFIER. 3 watt, 9V operation. Size 2 1/2 x 1 1/2 x 1 1/2 (1/6). Extra High Torque MINI-MOTOR, 44 to 12V, 1 1/4 x 1/4 in. 5/- (1/-), 9,000 r.p.m.

SUBSTITUTION BOXES. Capacitance 25/6 (1/6). Resistance 32/6 (1/6). Both full range and complete. Full details in list.

TEST PRODS: Flexible, unbreakable 24in. Red and Black leads, thin 4 1/2 in. prods, 1 1/2 in. plugs 4/9 (1/-). CROC. CLIPS: Plated with screw, or with red/black handles, 6d. each, 3 doz. (1/-). Many other types in list.

RECORDING TAPE

Finest quality British Mylar. STANDARD: 5in. 600ft. 7/3 5 1/2 in. 900ft. 10/-, 7in. 1200ft. 11/3, LONG PLAY 6in. 900ft 10/-, 5 1/2 in. 1200ft. 11/3, 7in. 1800ft.18/- (1/3 reel). Still the finest quality and value obtainable.
MICROPHONES—CRYSTAL MIC91, Hand/desk, 16/3; MIC45, curved hand grip 19/6; CM21, two tone grey hand/desk 10/6 (1/3), Stick "60" 20/3; (1/6 each type). Cream plastic hand type with stand switch 12/6. 2 leads with 2.5 and 3.5 plugs 12/6 (1/3). (3/- per hand) with clip 6/6 (1/-). CM70, Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands. 29/6 (1/6).

DYNAMIC: Cream hand/table 15/6 (1/6). MS10 50K Ω, 34 + pin. with Base. Adaptor 39/6 (2/6). MS11, similar but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6).

CARDIOD DYNAMIC OMNI-DIRECTIONAL: Highly successful "BALL" type, 209, 90K/600 ohms, 22/6. "Uni-directional ball type", switch cord adaptor - DM160—£3.17.6 (both these types 5/-).

MICROPHONE INSERTS: Diameter 1.75in. or 0.9in., either size 5/6 (1/-).
SPEAKERS 12in. round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 37/6 (5/6); or for stereo, 80/- per pair (charges paid), 2 1/2 in. 3 Ω 7/6 (1/-); Limited quantity powerful 2 1/2 in. P.P. transistor speaker, 3 watt, 8 Ω, 4 Ω, 16 Ω, 32 Ω (1/-). HEADPHONES: Stereo Dyn 8-16 Ω 63/- (3/-). EARPIECES with lead and min. jack plus magnetic 1/6 Crystal 4/9 (up to 3 for 1/- on either). State if 2.5mm. plug required. (Crystal 3.5mm. only).

AERIALS CAR TYPES—Telescopic vandal proof locks retracted, 2 keys and all fittings 27/6 (2/6) Superior type, slightly longer, 30/- (2/6).
Extending Aerial for Portals & E.F. Belt 4-section 6 1/2-23", 1" sliding threaded base, needs 1" hole 4/-; 6-section 5 1/2-25 1/2", screw hole in base 4/-; 7-section 5 1/2-32", screw hole in base 7/6; 10-section, 6 1/4", screw hole in base 15/9; ●DISAPPEARING, with swivel and sliding threaded socket, fixing nut on bottom section—8-section 5 1/2-29 1/2", 1" dia. 12/6. ●10-section 7 1/2-56 1/2", 1 1/2" dia. 15/9.

All are strongly plated (P. P. & I. on all above, up to three 1/-)
PLUGS: 5-band, 250V 2/- One hole fixing: SPST 2/3, SPDT 2/9, DPST 3/- DPDT 3/3. Slide type, Sub-min. DPDT 1/6 each. Small DPDT 3 way, center "off" 1/9. Reed magnetic on/off 1/9 (up to three, 1/-; 1d each additional). Rotary Switches etc. in list. Example: 4 pole 3 way 3/9 (1/-)

VIBRATORS: Famous makes only, 12 volt 4 pin non-synch (equiv. 1914) 4/6. 12 volt 7 pin synch. (Equiv. 12SR7) 12/6 (1/- each either type). A few specified other types now available (See list).

MAINS NEON TESTER: Fly leads 2/-, Pocket screwdriver type 3/6. **PLUGS:** Std. Jack, plastic body 2/3. Screened 3/-. **VALVE HOLDERS:** B7G or B9A, 6d. (all above 1/2 up to three). Many more British and Continental standard and miniature PLUGS & SOCKETS detailed in list. Also STANDARD ANTENNA SURPLUS VOLUME CONTROLS.

CONNECTING WIRE: 500 ft. 5c. 1000 ft. 9c. 2000 ft. 18c. Flexible 3/3. Super thin for transistor wiring etc. 3/3 (1/- all types per 5 coils). **PICK-UP WIRE:** Twin Super thin Flex, Screened, Sheathed, 1/3 yd. (6d. up to 6 yds., over 6 yds. post free). **TWIN MIKE CABLE:** 1/6 yd. **SINGLE MIKE CABLE:** 6d. yd. Both flexible, screened and sheathed. (Up to 3 yds. 9d., each additional yard 1d. extra.)

R.F. FIELD INDICATOR, 5-band with antenna, monitoring crystal earpiece, visible indicator etc. 49/6 (3/6) Detail in list.

RETRACTABLE FLEXIBLE LEADS. Space saving "Curly", many uses in car, home and with phono plug each end, 6ft., 4/6; 12ft., 7/9; With phono plug one end, phono socket at other, 6ft., 5/-, 12ft., 8/6 (1/- each all types).

SPECIAL PURCHASE—COMPUTER PANELS, clean and unused.
TYPE "A", 4 1/2" x 4" with eight Mullard OC45 transistors, 24 OA81 diodes, 32 resistors, etc. 8/6 per panel.

TYPE "B" 5" x 4" two Mullard OC43 transistors, six OA47 and four OA91 diodes, resistors and other items 5/6 per panel.

POT CORES type LA2, exactly as sold elsewhere at 15/-. New and unused at 8/6 each (P.P. and 1 all three items 1/- up to 3 and pro rata).

CURRENT LIST With many more items and special offers sent if requested with all orders or free for S.A.E. (Post free overseas). This advertisement cancels all previous ones and lists supplied prior to August 31st 1970.

FELSTEAD ELECTRONICS

(Dept PW35) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regular orders under 5/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire only. Overseas orders welcomed. Air or surface mail at cost. Sent at buyer's risk, unregistered and uninsured unless specified and min. insurance/req. fee of 2/2 sent.

S.A.E. please or all enquiries otherwise regret cannot be replied to.


EX-RENTAL TELEVISIONS
TWO-YEAR GUARANTEE

17" SLIMLINE 405 only
£11 10 0

19" SLIMLINE 405/625
39 Gns.

Carriage and Insurance 30/-
FREE ILLUSTRATED LIST OF TELEVISIONS

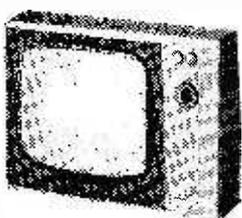17"-19"-21"-23"
WIDE RANGE OF MODELS, SIZES AND PRICES
DEMONSTRATIONS DAILY



TWO-YEAR GUARANTEED TUBES 100% REGUNNED

Slim Line Tubes 110" 17" and 19" 109/6, 21" and 23" 129/6.
Normal Tubes 70" and 90" 17" 99/6, 21" 119/6, 14" and other sizes 79/6.

SPEAKERS 10/-, 2 1/2" 8Ω, 3 1/2" 25Ω, 4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x 3" 3Ω. BRAND NEW, P. & P. 2/-.

RADIO PLAYER CABINET
49/6



Transistors: Mullard matched output kit 7/6, OC81D—2 OC81's. P. & P. FREE.

Transistor Radio Cases: 4 for £1. Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 9/6.

Ferrite Rods 3/6: 6" and 8" complete with LW/MW Coils. P. & P. FREE.

STRIP LIGHT TUBES 3/9 each. 11" (284mm), 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting, etc. 6 for £1. P. & P. free.

Cloth covered. Size 16 1/2" x 14 1/2" x 7 1/2". Takes any modern auto-changer. P. & P. 7/6.

(DUKE & CO. LONDON) LTD.

£21/3 Romford Road, London, E12 Tel. 01-478 6001/2/3

AMATEUR RADIO TECHNIQUES

By Pat Hawker, G3VA

Third edition just published. Revised and enlarged. Now contains 208 pages and nearly 500 diagrams. **22s post paid**

THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA. **23s post paid**

RADIO COMMUNICATION HANDBOOK

over 22,000 copies sold

Now in its second printing

The standard work in its field

RADIO COMMUNICATION HANDBOOK



832 pages of everything in the science of radio communication. The handbook's UK origin ensures easy availability of components. **69s post paid**

Obtainable from:
RADIO SOCIETY OF GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1N 2AE

BRAND NEW

SEMICONDUCTORS & COMPONENTS

(Saturday callers only 5% Discount)

GUARANTEED

TRANSISTORS

2G301	4/-	2N3402	4/6	3N152	22/6	BC168B	2/9	BFY76	3/-	NKT241	5/6
2G302	4/-	2N3403	4/6			BC168C	3/9	BFY77	11/6	NKT 281	5/6
2G303	4/-	2N3404	4/6	R.C.A.		BC169	2/9	BFY85	9/6	NKT 713	4/6
2G306	8/6	2N3405	9/6	400520	10/3	BFY69B	3/9	BFY86	13/6	NKT 781	5/6
2G308	6/-	2N3414	5/6	400521	17/6	BC169C	3/9	BFW88	5/6	NKT10419	5/6
2G309	6/-	2N3415	6/6	40309	6/6	BC170	3/6	BFW59	5/-		
2G371	3/-	2N3416	7/6	40310	9/-	BC171	3/6	BFW60	5/-	NKT10439	4/6
2G374	4/-	2N3417	7/6	40311	7/-	BC172	3/6	BPX25	37/-		
2G381	4/6	2N3420	25/-	40312	9/6	BC175	5/6	BPX29	36/-	NKT10519	6/-
2N404	4/6	2N3422	17/6	40314	7/6	BC182	4/6	BPY10	29/-		
2N695	4/-	2N3680	5/6	40323	7/6	BC192L	2/3	BRX39	9/6	NKT20329	5/-
2N697	4/-	2N3696	5/6	40323	6/6	BC193	4/6	BSX19	3/6		
2N698	5/-	2N3697	4/6	40324	9/6	BC184	4/6	BSX20	3/6	NKT20339	7/6
2N706	2/6	2N3662	7/6	40326	7/6	BC212L	3/6	BSX21	7/6		
2N706A	2/6	2N3663	7/6	40329	6/-	BCY30	5/6	BSX26	9/-	NKY9011	1/6
2N708	3/-	2N3702	2/6	40344	5/6	BCY31	5/6	BSX27	9/6		
2N709	12/6	2N3703	2/6	40347	7/6	BCY32	7/6	BSX28	6/6	NKT80112	1/6
2N718	5/-	2N3704	3/6	40348	10/6	BCY33	4/6	BSX60	16/6		
2N726	6/-	2N3705	3/6	40360	8/6	BCY34	4/6	BSX61	12/6	NKT80113	1/6
2N727	6/-	2N3706	2/6	40361	9/6	BCY38	4/6	BSX76	4/6		
2N914	3/6	2N3707	3/-	40362	11/6	BCY39	8/6	BSX77	5/6	NKT80211	21/-
2N916	3/6	2N3708	2/-	40370	6/6	BCY40	7/6	BSX78	5/6		
2N918	6/-	2N3709	2/-	40406	11/6	BCY42	3/6	BSY24	3/-	NKT80212	17/-
2N929	4/6	2N3710	2/6	40407	8/-	BCY43	3/-	BSY25	3/-		
2N930	5/6	2N3711	2/6	40408	10/6	BCY54	6/6	BSY26	3/6	NKT80213	17/6
2N987	10/6	2N3819	7/6	40410	12/6	BCY58	4/6	BSY27	3/6		
2N1090	6/6	2N3825	25/6	40467A	11/6	BCY59	4/6	BSY28	3/6	NKT80214	17/6
2N1091	6/6	2N3854	5/6	40468A	7/-	BCY60	19/6	BSY29	3/6		
2N1131	5/6	2N3854A	5/6	40600	14/6	BCY70	4/6	BSY32	5/-	NKT80215	17/6
2N1182	6/6	2N3855	5/6	AC107	6/-	BCY71	3/6	BSY35	5/-		
2N1302	3/6	2N3855A	6/-	AC126	4/-	BCY72	3/6	BSY37	5/-	NKT80216	17/6
2N1303	3/6	2N3856	6/-	AC127	5/-	BCZ10	5/6	BSY38	4/6		
2N1304	4/6	2N3856A	7/-	AC128	4/6	BCZ11	7/6	BSY39	4/6	OC20	15/-
2N1305	4/6	2N3857	6/-	AC129	4/6	BD116	22/6	BSY40	6/6	OC22	10/-
2N1306	5/-	2N3858A	6/-	AC178	6/-	BD121	12/6	BSY51	9/6	OC23	10/-
2N1307	5/-	2N3859	5/6	AC187	12/-	BD123	18/6	BSY52	7/6	OC24	11/6
2N1308	6/-	2N3859A	6/6	AC188	7/6	BD124	12/-	BSY53	7/6	OC25	10/-
2N1309	6/-	2N3860	6/-	ACY17	5/-	BD131	19/6	BSY54	8/-	OC26	6/6
2N1607	5/6	2N3866	30/-	ACY18	5/-	BD132	19/6	BSY56	18/-	OC28	12/6
2N1618	5/6	2N3877	8/-	ACY19	5/-	BDY10	27/6	BSY79	9/-	OC29	15/-
2N1631	8/6	2N3878A	12/6	ACY20	5/-	BDY11	37/6	BSY82	10/6	OC30	8/-
2N1632	8/6	2N3884	12/6	ACY21	5/-	BDY17	27/6	BSY90	13/6	OC35	8/-
2N1637	8/6	2N3900	7/6	ACY22	4/-	BDY18	49/6	BSY95A	4/6	OC36	12/6
2N1638	7/6	2N3900A	8/-	ACY28	4/-	BDY19	62/6	BSW41	8/6	OC38	10/6
2N1639	7/6	2N3901	17/6	ACY40	4/-	BDY20	22/6	BSW70	5/6	OC41	4/6
2N1711	5/-	2N3903	7/6	ACY41	5/-	BDY28	19/6	D16P1	7/6	OC42	5/6
2N1889	8/6	2N3904	7/6	ACY44	3/-	BDY60	36/-	D16P2	8/-	OC44	4/6
2N1893	8/6	2N3905	7/6	AD140	3/6	BDY61	36/-	D16P3	7/6	OC45	2/6
2N2147	14/6	2N3906	7/6	AD149	11/6	BDY62	24/6	D16P4	8/6	OC46	3/6
2N2148	12/6	2N4058	3/6	AD150	12/6	BF115	5/-	GET102	6/-	OC70	3/6
2N2160	11/6	2N4059	5/6	AD161	7/6	BF117	9/6	GET113	4/-	OC71	2/6
2N2193	9/6	2N4060	5/6	AD162	7/6	BF163	7/6	GET114	4/-	OC72	2/6
2N2193A	10/6	2N4061	4/6	AF106	3/6	BF167	5/6	GET118	4/-	OC74	6/6
2N2194A	4/6	2N4062	4/6	AF114	5/-	BF173	6/6	GET119	4/-	OC75	4/6
2N2217	5/6	2N4244	9/6	AF115	5/-	GET127	5/6	GET177	5/6	OC76	4/6
2N2218	6/-	2N4255	8/6	AF116	5/-	BF178	18/6	GET183	3/6	OC77	4/6
2N2219	6/-	2N4285	3/6	AF117	5/-	BF179	14/6	GET186	6/-	OC81	4/6
2N2220	5/-	2N4286	3/6	AF118	12/6	BF180	7/6	GET188	4/-	OC81D	4/6
2N2221	5/-	2N4287	3/6	AF119	4/6	BF181	6/6	GET189	4/6	OC83	5/6
2N2222	5/-	2N4288	3/6	AF124	4/6	BF184	6/6	GET189	4/6	OC84	5/6
2N2287	21/6	2N4290	3/6	AF125	3/6	GET185	3/6	GET186	4/6	OC139	6/6
2N2297	6/-	2N4290	3/6	AF126	4/6	BF184	4/6	GET188	4/6	OC170	6/6
2N2303	5/-	2N4291	3/6	AF127	3/6	BF195	8/6	OC170	6/6	OC171	6/6
2N2368	5/-	2N4292	3/6	AF139	7/6	BF196	8/6	MAT100	6/-	OC200	6/6
2N2369	5/-	2N5027	10/6	AF178	11/-	BF197	8/6	MAT101	6/-	OC201	9/6
2N2369A	5/6	2N5028	10/6	AF179	14/6	BF198	8/6	MAT120	6/-	OC202	12/6
2N2410	8/6	2N5029	9/6	AF180	10/6	MAT121	6/6	BP209	6/6	OC208	9/6
2N2483	5/6	2N5030	8/6	AF181	8/6	BP224	6/-	MC140	35/6	OC209	8/6
2N2484	6/6	2N5172	3/-	AP239	9/6	BP225	6/-	MJ400	21/6	OC204	8/6
2N2539	4/6	2N5174	10/6	AP279	9/6	BP237	6/6	MJ420	22/6	OC205	8/6
2N2540	4/6	2N5175	10/6	AP290	12/6	BP238	6/6	MJ421	22/6	OC207	7/6
2N2613	4/6	2N5176	10/6	AP290	12/6	BP244	9/6	MJ430	20/6	OC271	8/6
2N2614	5/-	2N5232	5/6	ASX26	13/6	BFY61	13/6	MJ449	15/6	OC112	12/6
2N2646	11/6	2N5232A	6/-	ASX27	7/6	BFX12	4/6	MJ480	19/6	ORP60	10/-
2N2696	6/6	2N5245	12/6	ASX28	7/6	BFX12X	4/6	MJ481	25/-	ORP61	10/-
2N2711	6/-	2N5246	12/6	ASX29	5/6	BFX13	4/6	MJ490	20/-	P346A	4/6
2N2712	6/-	2N5249	12/6	ASX30	7/6	BFX23	7/6	MJ491	27/6	TIP31A	16/6
2N2713	5/6	2N5249A	12/6	ASX36	4/6	BFX30	7/6	MJ800	43/6	TIP32A	19/6
2N2714	6/-	2N5250	12/6	ASX37	7/6	MJ830	7/6	MJE540	7/6	OC284	12/6
2N2715	6/-	2N5265	62/6	ASX54	5/-	BFX44	7/6	MJE520	17/6	TIS83	4/6
2N2865	12/6	2N5266	5/6	ASX56	7/6	BFX44	7/6	MJE520	17/6	TIS84	4/6
2N2904	7/-	2N5267	52/6	ASZ20	7/6	BFX68	13/6	MJE521	17/6	TIS84	4/6
2N2904A	8/-	2N5305	7/6	ASZ21	7/6	BFX68A	13/6	MPP102	8/6	TIS85	3/6
2N2905	8/-	2N5306	9/6	ATY10	30/-	BFX84	6/-	MPP103	7/6	TIS86	3/6
2N2906	9/-	2N5307	7/6	BC107	3/-	BFX85	7/-	MPP104	7/6	TIS87	3/6
2N2906A	6/6	2N5308	7/6	BC108	3/-	BFX86	6/-	MPP105	6/6	TIS88	3/6
2N2906B	6/6	2N5309	12/6	BC109	3/-	BFX87	10/-	MPS3638	6/6	TIS89	3/6
2N2907	6/6	2N5310	3/6	BC113	5/6	BFX88	5/6	NKT0013	7/-	TIS90	3/6
2N2923	3/6	2N5314	5/6	BC115	6/6	BFX89	12/6	NKT124	6/6	TIS91	3/6
2N2924	3/6	2N5355	5/6	BC116A	7/6	BFX92A	12/6	NKT125	4/6	TIS92	3/6
2N2925	3/6	2N5356	6/6	BC136	6/6	BFY10	6/6	NKT126	4/6	TIS93	3/6
2N2926	3/6	2N5365	9/6	BC123	4/6	BFY11	6/6	NKT128	4/6	TIS96	3/6
Green	2/9	2N5866	6/6	BC122	4/6	BFY12	4/6	NKT135	6/6	TIS91	4/6
Yellow	2/9	2N5867	11/6	BC125	11/-	BFY13	4/6	NKT137	6/6	ZTX107	3/6
Orange	2/9	2N5857	7/6	BC126	11/-	BFY17	4/6	NKT210	4/6	ZTX108	3/6
2N3011	6/6	2N5718A	8/-	BC134	6/6	BFY18	6/6	NKT211	4/6	ZTX109	3/6
2N3014	6/6	2N5905	15/6	BC135	6/6	BFY19	6/6	NKT212	4/6	ZTX300	3/6
2N3053	5/6	2N5920	37/6	BC136	12/6	BFY20	12/6	NKT213	5/6	ZTX301	3/6
2N3054	11/-	2N5102	6/6	BC140	7/6	BFY21	8/6	NKT214	4/6	ZTX302	4/6
2N3055	15/-	2N5103	6/6	BC147	7/6	BFY24	9/6	NKT215	4/6	ZTX303	4/6
2N3133	8/-	2N5104	6/6	BC148	3/6	BFY29	10/-	NKT216	7/6	ZTX304	4/6
2N3134	6/-	2N5141	5/6	BC149	3/6	BFY30	10/-	NKT217	7/6	ZTX500	4/6
2N3135	5/6	2N5092	12/6	BC152	3/6	BFY41	10/-	NKT219	5/6	ZTX601	5/6
2N3136	5/6	2N5093	5/6	BC154	5/6	BFY43	12/6	NKT222	4/6	ZTX602	5/6
2N3390	7/6	2N3883	37/6	BC157	4/6	BFY50	4/6	NKT224	4/6	ZTX503	5/6
2N3391	4/-	2N3128	18/6	BC158	3/6	BFY51	4/6	NKT225	4/6	ZTX504	12/6
2N3391A	4/-	2N3140	19/6	BC159	4/6	BFY52	4/6	NKT229	4/6		
2N3392	4/-	2N3141	19/6	BC160	12/6	BFY53	4/6	N			

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v, 7.5v and 9v. DC. attractive case with indicator light, mains lead out socket, plug and lead. Size 4 1/4 x 3 1/2 x 2 1/2 in.

57/6 P. & P. 2/6



(Extra lead with DIN plug for Cassette Recorders 7/6)

MAINS UNIT

for transistor equipment using 7.5v. Complete with DIN plug for power socket. Can also be supplied for a 6-volt output complete with suitable plug. (State make, model and voltage required.)

45/- P. & P. 2/6

UNIT FOR USE WITH 12V CAR BATTERY
Suitable for running transistor radios etc. (State output reqd. - 6v, 7.5v or 9v) Price 35/- including fused lead. P. & P. 2/6

MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 38/6. For two separate outputs, 4.5v + 4.5v, 6v + 6v, 9v + 9v. 42/6. P. & P. 2/6 per unit. (Please state outputs reqd.)



MAINS UNIT FOR ALL TRANSISTOR RADIOS ETC., USING PP3 TYPE BATTERY. (ALSO AVAILABLE FOR 6V.)

20/- P. & P. 2/-

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.

(Dept. P.W.), 31 Oliver Road, London, E.17

Learn at home... First Class Radio and TV Courses



After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of certificate courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of

'Satisfaction or Refund of Fee'

Write now for your copy of this valuable publication. It may well prove to be the turning point in your career.

Founded 1885—Over 150,000 successes

CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)
(Dept. R15), College House 29/31 Wrights Lane, W.8.

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 40/-, 11 element, 47/6, 14 element, 55/-, 18 element, 62/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6, 11 element, 55/-, 14 element, 62/-, 18 element, 70/-, Chimney Mounting Arrays, Complete, 7 element, 72/6, 11 element, 80/-, 14 element, 87/6, 18 element, 95/-, Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

BBC - ITV AERIALS



BBC (Band 1). Loft, 25/-, External S/D, 30/-, "H", £2.15.0. ITV (Band 3), 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 50/-, 5 element, 55/-, Combined BBC/ITV. Loft 1 + 3, 40/-; 1 + 5, 50/-; 1 + 7, 60/-; Wall mounting 1 + 3, 60/-; 1 + 5, 70/-; Chimney 1 + 3, 70/-; 1 + 5, 80/-, VHF transistor pre-amps, 75/-.

COMBINED BBC1 - ITV - BBC2 AERIALS 1 + 3 + 9, 70/-, 1 + 5 + 9, 80/-, 1 + 5 + 14, 90/-, 1 + 7 + 14, 100/-, Loft mounting only. F.M. (Band 2), Loft S/D, 17/6. "H", 35/-, 3 element, 57/6. External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/6. Outlet boxes, 5/-, Diplexer Crossover Boxes, 17/6. C.W.O. or C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

Callers welcomed — open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 4884



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 vols.) BASIC ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

- '... carefully written ...'
- '... I am very satisfied with these carefully written and well expressed manuals ... A.W., Shanklin.'
- '... valuable assistance ...'
- '... Your valuable assistance has enabled me to find a good position as a Radio and TV Engineer ... D.S., Bristol.'
- '... they are invaluable ...'
- '... I find that as a base for a course in Electronics they are invaluable and I have yet to find anything even to approach the same standard ... H.N., Rotherham.'

A TECH-PRESS PUBLICATION

■ To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

■ Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

■ Tick Set required (Only one set allowed on free trial)

■ BASIC ELECTRICITY BASIC ELECTRONICS
Prices include Postage and Packing.

■ Signature _____
(If under 21 signature required of parent or guardian)

■ NAME _____
■ BLOCK LETTERS
■ FULL POSTAL ADDRESS _____

POST NOW FOR THIS OFFER!!

Build working radio receivers and electronic circuits in an evening



*** NO SOLDERING**

Beginner or advanced student— you learn fast with Radionic kits

Circuits work first time with the Radionic 'no soldering' method. With the X30 kit, build 33 experiments: a printed circuit transistor radio, burglar alarm, morse code buzzer etc. The more advanced kits are suitable for G.C.E., City and Guilds, National Certificate and higher. Every set includes construction notes and all circuit diagrams.

It's so easy for you to build *and* learn because you construct circuits that resemble the theoretical diagram. Re-use components easily, too — they're screw-in-mounted.

Send off this coupon today.

PW2

TO: RADIONIC PRODUCTS LTD.,
St. Lawrence House, Broad Street, Bristol BS1 2HF

Please send me full details of all Radionic Kits/please send me one Radionic Kit X30, for which I enclose £7 19s. 6d.
(delete where inapplicable)

Name _____

Address _____

RADIONIC
RADIO & ELECTRONICS CONSTRUCTIONAL KITS

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS

*** Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—but you learn the *practical* way.**

Now you can learn basic Radio and Electronics at home—the *fast, modern* way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new TECHNATRON Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book —'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court, Aldermaston, Berkshire.

To: B.I.E.T., Dept. 372B ALDERMASTON COURT, ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name _____
 address _____
 age _____

POST THIS COUPON NOW!


TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Total Building Costs **£6.19.6**
Parts Price List and Easy Build Plans 5/- (FREE with parts).

P. & P. 7/6

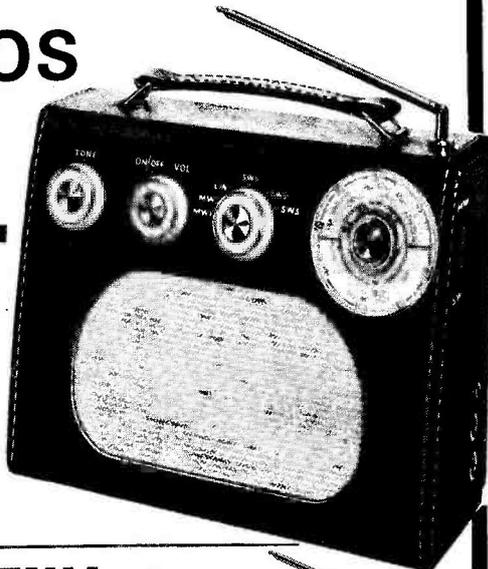

roamer seven mk IV

SEVEN FULLY TUNABLE WAVE-BANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle, Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

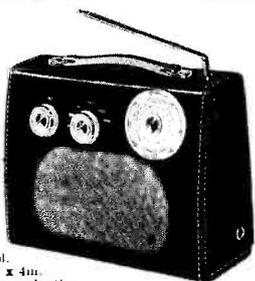


Total building costs
£5.19.6

P. & P. 7/6

NEW! trans eight

SIX WAVEBAND
PORTABLE WITH
3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

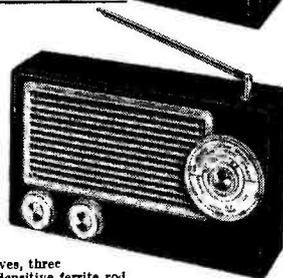


Total building costs **89/6**

P. & P. 5/6

pocket five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND PORTABLE
WITH SPEAKER

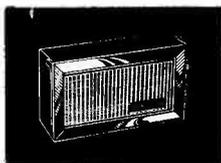Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
44/6

P. & P.
3/6

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND
PORTABLE
WITH SPEAKER

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).




Total building costs
47/6

P. & P.
3/9

roamer six

SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 5 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts). (Note: When present stocks of these cases are exhausted a new case similar to "Transight" will be supplied).

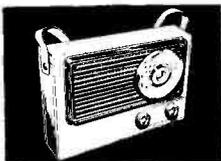

Total building costs
79/6

P. & P.
4/6

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for

Name

Address

PW.22

★ Callers side entrance Stylo Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.
—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 769-0199/1649

1A7	7/9	6BR8	12/6	6K7GT	4/6	10C1	20/-	25L6GT	7/-	150B2	11/6	DK32	7/9	ECH35	11/6	EY86	7/-	PCF80	6/9	PY801	9/6	UCL82	7/6	
1D5	7/8	6B87	25/-	6K8	2/9	10C2	12/6	25Y5	6/-	150C4	9/6	DK91	6/-	ECH42	13/-	EZ35	6/-	PCF82	6/9	R2	7/6	UCL83	11/6	
1H5	7/-	6BW6	14/6	6K8M	11/6	10F1	14/9	25Z4	6/3	801	9/6	DK92	9/-	ECH51	5/9	EZ40	9/-	PCF84	8/-	R19	7/6	UF41	10/6	
1LD5	6/-	6C74	13/-	6K8G	3/-	10F3	13/-	35Z5	8/-	807	9/-	DLK6	7/9	ECH83	9/6	EZ41	9/6	PCF86	9/-	R45-500	80/-	UF80	7/6	
1N5GT	8/-	6C74	5/-	6K9GT	7/-	10F9	10/6	25Z6	8/6	813USA	8/6	DLK6	25/-	ECL80	7/-	EZ80	5/6	PCF801	9/9	S130	40/-	UL41	12/-	
1R4	6/-	6C5G	5/-	6K25	15/-	10F18	8/-	28D7	9/3	120/-	DL92	6/3	ECL82	7/-	EZ81	5/6	PCF802	9/9	SP4	6/-	UL84	7/6		
1S4	5/6	6C6	3/9	6L1	12/-	10L1	8/-	30C1	6/9	813	75/-	DL93	4/-	ECL83	10/3	(Y50)	15/-	PCF803	15/-	SP41	6/6	UM80	5/6	
1S5	4/6	6C8G	6/-	6L6G	7/9	10LD11	10/6	30C15	15/-	866A	15/-	DL94	6/9	ECL86	9/-	GZ30	10/-	PCF806	13/-	SP61	6/6	UL6	21/-	
IT4	4/-	6CD6G	24/-	6L18	6/-	10P3	13/6	30C17	16/-	954	5/6	DL96	7/9	ECL80080	9/-	GZ32	10/-	PCF808	15/6	STV280/30	10/7	UL7	21/-	
3A4	4/-	6CH6	7/6	6Q7G	6/-	11E3	7/0-	30C18	15/-	1625	6/6	DL96	7/6	EP9	20/-	GZ34	11/-	PCF82	7/9	85/-	UL8	21/-		
3Q4	7/9	6CW4	13/6	6Q7GT	8/6	12AT6	4/9	30F5	17/-	40922AR	67/-	DM70	6/-	EP37A	7/-	HN309	20/-	PCF83	10/3	ST2150	12/6	UY1	9/6	
3Q5	7/-	6D6	3/9	6SA7M	7/-	12AT7	6/-	30FL1	15/-	5783	12/-	DX86	6/-	EP39	8/-	K736	13/-	PCF84	8/3	ST255	19/6	UY9	8/3	
384	6/3	6E5	7/6	6SCT	7/-	12AU6	5/9	30FL12	19/-	6168	12/-	DX87	6/6	EP41	10/-	K766	22/6	PCF85	9/3	T41	17/6	UY41	8/6	
3V4	6/9	6F1	12/6	6SCT	6/-	12AU7	5/9	30FL14	15/6	7475	14/-	EB80C	12/-	EP50	5/-	K766	30/-	PCF86	9/3	T41	17/6	UY41	8/6	
4R4G	10/3	6F5G	8/-	6SH7	3/3	12AX7	6/3	30LL5	17/-	A61	9/6	EAB0	3/6	EP80	4/6	K781	35/-	PD500	29/-	U10	7/6	VMP4G	17/-	
4R4G	5/6	6F8G	5/-	6S7	6/-	12BA6	6/6	30LL7	17/-	ATP4	2/3	EAB0	6/6	EP85	7/-	PCF84	20/-	PCF84	20/-	U14	7/6	VMP4B	25/-	
5V4G	8/-	6F8G	6/6	6SK7GT	4/9	12BE6	6/3	30P4	22/6	ATP5	12/-	EAF42	10/-	EP86	6/6	22/6	PCF84	20/-	PCF84	20/-	U19	36/-	VR105/30	6/6
5Y3GT	6/-	6F11	6/6	6SL7GT	6/-	12C8GT	6/6	30P12	16/-	ATP7	8/6	EB41	10/-	EP89	5/6	KT88	34/-	PCF85	7/-	U25	15/6	VR150/30	6/6	
5Z4G	7/-	6F13	6/6	6SN7GT	5/6	12E1	20/-	30P19	15/-	AT9	20/-	EB91	3/6	EP91	3/6	KW46	12/6	PCF86	4/-	U26	15/6	VR25	15/-	
6/30L2	15/-	6F14	12/6	6SQT	7/6	12S6GT	2/6	30P19	15/-	AU2	8/9	EB93	3/6	EP93	3/6	KW46	12/6	PCF86	4/-	U26	15/6	VR25	15/-	
6A7	15/-	6F23	10/-	6U4GT	12/-	12J7GT	6/6	30PL13	19/6	AZ1	9/-	EB93	3/6	EP93	3/6	KW46	12/6	PCF86	4/-	U26	15/6	VR25	15/-	
6A8G	12/6	6F24	14/-	6V6G	7/9	12K7GT	7/-	30PL14	15/6	AZ1	10/-	EB90	4/9	EP183	6/6	ML6	7/6	PL82	8/6	C251	16/3	UY120	12/6	
6A7	4/-	6F25	15/-	6V8M	12/-	12K9GT	8/-	35A5	12/6	CBL31	16/-	EPF90	7/6	EP184	7/6	MLP4	10/-	PL83	7/6	U301	12/6	UV508	35/-	
6AK5	5/-	6F28	14/-	6V6G	4/6	12Q7GT	6/-	35L6	9/-	CCH35	15/-	EPF83	9/-	EL32	3/6	MU14	7/6	PL84	7/6	U403	6/6	WH1M	13/6	
6AM5	4/6	6F32	2/9	6V6GT	6/6	12S4T	8/-	35W4	4/6	CL38	20/-	EPF89	6/6	EL33	12/6	MX40	12/6	PL500	14/6	U404	7/6	XBI-5	5/6	
6AM6	3/6	6G6	3/6	6X4	4/6	12S8GT	6/-	35Z3	10/-	CV450	25/-	EEL1	14/-	EL34	10/6	N78	19/-	PL504	16/-	U801	23/6	XBI-5	5/6	
6AQ5	6/3	6H6	3/6	6X5G	4/6	12SH7	3/6	35Z4	10/-	CV450	25/-	EEL1	14/-	EL34	10/6	N78	19/-	PL504	16/-	U801	23/6	XBI-5	5/6	
6A87G	15/-	6J3M	9/-	6X5GT	6/-	12SJ7	4/9	35Z5	6/6	CY31	8/6	EBL21	27/6	EL41	11/-	NT1	9/6	PL509	23/6	U802	23/6	XBI-5	5/6	
6AT6	4/9	6J3G	4/-	7B6	11/6	12SK7	4/9	37	6/6	DAC92	8/6	EC90	5/6	EL42	11/6	OC2	5/-	PL802	16/6	UBC41	9/3	3EG1	65/-	
6AU6	5/6	6J5GT	5/6	7B7	7/6	12SR7	5/-	42	6/-	DAF91	4/6	EC91	6/-	EL44	11/6	OC3	5/-	PL802	16/6	UBC41	9/3	3EG1	65/-	
6B4G	20/-	6J6	3/6	7C5	22/6	14H7	9/6	50B5	6/6	DAP96	7/6	EC92	5/9	EL95	7/-	OZ4	4/6	PC25	27/6	UBF80	7/6	5CP1	55/-	
6B8G	20/-	6J7M	8/6	7C6	15/-	19A4G5	5/-	50C5	6/3	DCC90	20/-	EC93	6/3	ELL80	20/-	PC86	11/6	PY33	10/3	UBF89	7/6	CV1626	65/-	
6BA6	5/-	6J7G	6/-	7D5	8/-	20D1	10/-	50D6G	31/-	DF33	5/-	EC94	5/6	EM34	16/-	PC88	11/6	PY81	5/9	UC94	8/6	ACR13110	45/-	
6BE6	5/-	6J7GT	7/6	7H7	6/6	20P2	14/-	50L6GT	8/-	DF70	9/-	EC95	5/-	EM80	7/6	PC97	9/6	PC97	9/6	UC95	7/6	UC97	45/-	
6BH6	9/-	6K6GT	8/-	7R7	13/-	20L1	20/-	75	9/6	DF81	4/-	EC96	5/6	EM84	7/6	PC98	11/6	PC98	11/6	UC98	4/6	UC98	46/-	
6B36	9/-	6K7	1/9	7S7	45/-	20P4	20/-	78	5/-	EP92	3/6	ECF80	6/6	EM84	7/6	PC99	10/6	PY500	18/6	UCH42	10/6	46/-	46/-	
6BQT4	7/-	6K7M	6/6	7Y4	9/6	20P5	20/-	80	7/6	DP96	7/6	ECF82	6/6	ESU150	20/-	PC189	10/6	PY800	9/6	UCH81	7/6	VCR517C	46/-	
6BR7	17/-	6K7G	2/-	9BW6	7/-	25A6	5/9	85A2	7/3	DH77	4/9	ECH21	12/6	EY51	7/6	OA10	3/-	OC36	8/6	OC77	8/-	OC122	12/6	

Manufacturers and Export Inquiries Welcome
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Express postage 9d. per valve.
Ordinary postage 6d. per valve. C.W.O. No C.O.D.
Tube postage 10/- each

Special Express Mail Order Service


TRANSISTORS

2G414	6/0	AC128	4/6	AF118	12/-
2N1305	6/0	AC176	6/2	BC108	3/6
2N214	15/6	AC71	4/-	BC109	4/-
2N2369A	5/-	ACY27	5/-	BFY51	5/-
2N2696	6/3	ACY28	4/-	BFY90	12/6
2N2926	3/-	ACY39	12/6	BY100	4/6
2N3705	4/-	AD149	12/-	GET114	4/-
2N3819	8/-	AD161	7/6	GT7M	6/6
AC107	5/6	AD162	7/6	KT274	4/9
AC127	5/-	AF117	4/6	NK713	7/6

SEND S.A.E. FOR LIST OF 3,000 TYPES

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

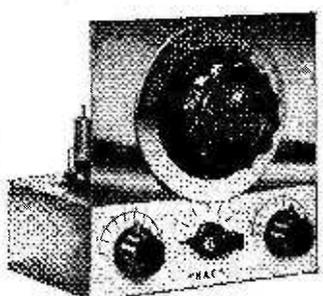

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER
Improved one-valve model "DX" mark 2. Complete kit—price 86/- (post & packing 4/-). Customer writes: "America and Australia received clearly at good volume." Send S.A.E. for test report and testimonials.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

SHORTWAVE TRANSISTOR RADIO

Can be built in one evening

ONLY 45/-



At last! After trying countless circuit designs searching for easy build, work-first-time short waver. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and everyone worked first time) no soldering necessary. 75 stations logged on rod aerial in 30 minutes—Russia, Africa U.S.A., Switzerland, etc. Experience thrilled of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PPS battery. Transistorised (no valves!). Size only 3" x 4 1/2" x 1 1/2". *As tremendous demand anticipated price held to only 45/- + 3/6 p & p.* for all parts including Cabinet, screws, instructions, etc. (Parts available separately). Money back guarantee.

MAKES 5 DIFFERENT TRANSISTOR RADIOS

TOTAL BUILDING PRICE 39/6

Amazing Radio Construction set! Become a radio expert for 39/6. A complete Home Radio Course. No experience needed. Parts including instructions for each design. Step-by-step plan, all Transistors, loud-speaker, personal phone, knobs, screws, etc., all you need. Box size 14" x 10" x 2" (parts avail. sep.). Send only 39/6 + 4/6 P. & P. Money back guarantee.

CONCORD ELECTRONICS LTD. (P.W.11)
8 Westbourne Grove, London, W.2
(near Baywater Tube) (Callers 9-6 Inc. Sat.)

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

JOHNSONS (RADIO)
St. Martin's Gate, Worcester
WR1 2DT

Please mention **PRACTICAL WIRELESS** when replying to advertisements

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDEGE, YORKS.

Tel. Heckmondwike 4285

Amplifier Units Type A1413. Complete with Valves Type 5Z4 and 6V6GT. 230/250 Volt 50 cycles Transformer. Clean Condition. Untested 25/- Carriage B.R.S. 15/-.

Airmileage Units. Complete with 24 Volt Motor, and Gears, etc. Less Relay. Clean Condition. Untested 15/- Carriage B.R.S. 15/-.

New Chassis in Metal Case. 5½ x 5½ x 4". Complete with McMurdo Micronector 18 way Plug and Socket. also 1000 Ohms Relay. 5/- P/P 4/6.

Amplifier and Diode Bridge Unit. Type 17626. Complete with Miniature sealed Relay and miniature Plug and Socket. Ex Units Bargain Price 7/6 Post Paid.

SPECIAL OFFER. Bush 17" T.V. Sets Series 75. 12 Channels Complete and Tested with good Tube £6/10/0. Cabinet Fair. Carriage and Insurance Passenger Train G.B. only 35/-. Untested 17" T.V. Complete 12 Channel 50/- Carriage £1.

Speakers Removed from T.V. Sets. All P.M. 3 Ohms. 5" round 3/- each 6 x 4 3/- each, 7 x 4 5/- each. Slot Speakers 8 x 2½ 5/- each Post on any Speaker 4/-.

8" P.M. Speakers in Cabinet with Volume Control 3 Ohm. Cabinet Condition Poor. Speaker First Class. 10/- Post and Packing 10/- Reclaimed T.V. Tubes with 6 month Guarantee 17" AW 43/80 AW 43/88 40/- MW 43/69 30/- each. All Tubes 15/- Carriage.

VALVE LIST—Ex Equipment, 3 months' guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid.

ARP12 1/6	EY86 5/-	PY33 5/-	6U4 5/-
EB91 9d.	PCC84 2/-	PY81 1/6	6P28 5/-
EF35 3/-	PCF80 2/-	PY82 1/6	10P13 2/6
EBF80 3/-	PCL84 4/-	P230 5/-	185BT 8/6
ECC81 3/-	PCL85 4/-	U191 5/-	20D1 3/-
ECC82 3/-	EF183 4/-	U281 5/-	20P1 5/-
ECC83 4/-	EF184 4/-	U282 5/-	20P3 2/6
ECL80 1/6	PCL82 4/-	U251 5/-	30PL1 5/-
EF50 1/-	PCL83 5/-	6B8 1/8	30P12 5/-
EF80 1/6	PL36 5/-	6BW7 2/6	30F5 2/6
EF91 9d.	PL81 4/-	6K7 1/9	40FL1 5/-
			6/30L2 5/-

If you can put a 'Yes' in every box, you might just make a RADIO TECHNICIAN in Air Traffic Control

An all-consuming interest in telecommunications

At least one year's practical experience in telecommunications, preferably with 'ONC' or 'C and G' technical qualifications

A highly developed sense of responsibility

Willingness to undergo a rigorous programme of training

Aged 19 or over

To the right man, the National Air Traffic Control Service offers the prospect of an interesting and steadily developing career as a Radio Technician in air traffic control.

The work involves the installation and maintenance of some of the very latest electronic equipment at civil airports, radar stations and other specialist establishments all over the country. Important today, the job will become increasingly vital as Britain's air traffic continues to grow, and prospects for promotion are excellent. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over). Scale maximum £1590 (higher rates at Heathrow). The annual leave allowance is good, and there is a non-contributory pension for established staff.

If you feel you can meet the demands of this rather special job—and you have a strong determination to succeed—you are invited to complete the coupon below.

Send this coupon for full details and application form
**To: A J Edwards, C Eng, MIEE, The Adelphi,
Room 705, John Adam Street, London WC2,**
marking your envelope "Recruitment".


Name

Address

PWT/G2

Not applicable to residents outside the United Kingdom

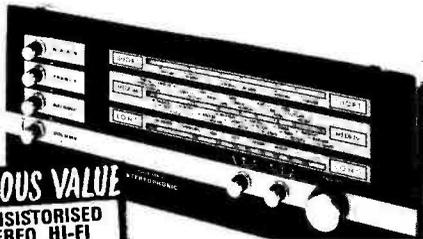NATCS
National Air Traffic Control Service



FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Sereada fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4½" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL
NO TECHNICAL KNOWLEDGE REQUIRED

Only **28 Gns.** + P&P 17/6

Credit terms available, first monthly payment £3.6.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL"

FULLY TRANSISTORISED STEREOPHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY**

10 Watts Total output **38 Gns.** P&P 17/6

17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY

Credit Terms available. First monthly payment

£4.9.10 followed by 9 monthly payments of

£4.9.10. (Total "Credit Sale" Price

£44.18.4.) Send £5.7.4 today.



Callers
Welcome

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name

Address

LEWIS radio 100 CHASE SIDE, SOUTHGATE DEP., P10/70 LONDON, N.14. TELEPHONE 886 3733/9666

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

MISCELLANEOUS

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

BUILD IT in a DEWBOX quality cabinet. 2in.x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

TV NOTES FOR UFO DETECTION, and 2 Optical Detector circuits, 9/6. All-night Optical/Radiation circuit with electronic "memory," 9/6. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

ENAMELLED COPPER WIRE

S.W.G.	Per 1/2 lb reel	Per 1 lb reel
18-22	11/3d	16/6d
23-30	11/9d	17/6d
31-35	12/3d	18/6d
36-40	15/-	24/-
41-44	17/9d	29/6d

Orders despatched by return of post. Please add 1/- per item P. & P. Supplied by: Banner Transformers, 84 Old Lansdowne Rd, West Didsbury, Manchester, 20.

TRADE ENQUIRIES INVITED

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

TOP TRANSISTORS

ACY22 1/9	OC45 1/9	ZTX300 1/9
BC168 1/9	OC71 1/9	2N706 1/9
BC169 1/9	OC72 1/9	2N2926 1/9
BSY27 1/9	OC200 1/9	2N3705 1/9
BFY51 1/9	OC201 1/9	2N3706 1/9
BFY52 1/9	OC202 1/9	2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested, unmarked but guaranteed to be within their correct specification, or money refunded.

ANTEX SOLDER IRON

A lightweight iron with a 15 watt nickel plated bit. Designed to enable you to weld reliable joints accurately. Model CN240 volts. Special low price. Act Now, Only 29/11

MONEY BACK GUARANTEE. P. & P. 1/-

J. M. KING (P)

17 Buckbridge, Portpool Lane, London, E.C.1

PARAPHYSICAL LABORATORY, Downton, Wilts. Telekinetic photographs/data. S.A.E. for list, Samples 20s.

BIG BARGAIN PARCEL 13/- post paid

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

"SHURE" TAPE HEADS

Record/playback and erase in one unit, Mounted on bracket with tape guide etc. 10/- post paid "MARRIOT" Single record/playback heads. 5/- post paid.

PHOTO ELECTRIC SWITCH KIT

Light cell, transistor, relay etc. Elegant case in hammer finish 5 1/2" x 2 1/2" x 4 1/2" fitted with light hood, ideal counter alarm, Dawn/Dusk switch, etc. 35/- Post Paid.

6 OR 12 VOLT FLUORESCENT LIGHTS

12 in. 9 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at 65/6 post paid.

or In kit form 57/6

4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed 72/6 POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cop, Shrewsbury, Shropshire S.A.E. for lists

MUSICAL MIRACLES! Drum, Cymbals, Waa-Waa and Fuzz modules. New unique effects units, Percussion etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches etc. Send S.A.E. NOW! D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

ALL THOSE LITTLE ITEMS which you can never find are available from our stock. Also speaker fabrics, BAF wadding, Peerless speakers, cabinet kits, cross-overs. For full details send 9d in stamps to **Audioscan**, Dept. P.W., 4 Princes Square, Harrogate, Yorks.

LIVE WIRES can be dangerous. Now you can make electrical connections safely, in seconds with the revolutionary new Key-nector. Cuts out plugs, sockets and bare wire dangers. Ideal for bench and high speed testing of electrical equipment. . . a must for the do-it-yourself fan. Send for a leaflet to E. B. Instruments Dept P.W. 49/53 Pancras Road, London N.W.1. (837 7781) Only 46/6d plus postage.

DO-IT-YOURSELF PRINTED CIRCUIT KITS

AMAZING VALUE! Each pack contains

★ P. C. Boards (assorted sizes)

★ Etchant

★ Resist

★ Etching Tank

★ Full instructions

Price 16/- and 30/- (extra large). C.W.O.

CLIFFORD ELECTRONICS, (Dept. P.W.)
14 Lynford Gardens, Edgware, Middx.

AERIALS

BAKER AND BAINES

UHF Aerials BBC and ITV 625

10 ele 42/-, 14 ele 47/-, 18 ele 65/-, 22 ele 75/-, Double 22 ele 160/-. All aerials have composite reflector and tilt clamps which take up to a 2 inch mast.

BBC Aerials

Dipole 35/-, X 43/-, H 48/-.

ITA Aerials

5 ele 39/-, 8 ele 54/-, 11 ele 66/-, Double 5 array 98/-, 8 129/-, 11 161/-.

Combined Aerials

Dipole plus 5 54/-, H plus 5 82/-, X plus 5 90/-, Supplied with 1" or 2" clamps. Loft Dipole plus 5 42/-. This aerial is supplied with loft pole, joint bracket and universal joint.

Diplexers—Triplexers Matched UHF/VHF Diplexers VHF and UHF Pre Amps from 75/- postage 3/-. Poles, Lashings, Clamps, Couplers, etc. Co-Ax at 1/3 and 2/3.

Postage paid on all aerials inland. Accessories postage extra.

PLEASE STATE CHANNELS WHEN ORDERING—MAIL ORDER ONLY

SAE for full lists.

11 Dale Cres, Tupton, Chesterfield

ELECTRICAL

240 VOLT
ELECTRICITY
ANYWHERE



BEST EVER 200/240 VOLTS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY

Exclusive World Scoop Purchase. The fabulous Mk. 12D American Heavy Duty Dynamo Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere.

Brand New and Fully Tested, only £4.19.6 plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. PW, STANFORD ELECTRONICS
Rear Derby Road, North Promenade,
Blackpool, Lancashire.

RECEIVERS & COMPONENTS

E.M.I. LOUDSPEAKERS, 13" x 8" bass, 2 tweeters, crossover, 3, 8, 15 ohms, 75/-, 5" bass, special suspension, 8 ohms, 37/6, 3 1/2" tweeters, 8 ohms, 16/6. Transistors, 2N5172, BC 213L, 2/-, £1 doz. All post free. "Sontel," Dept. X, 183 Clapham Manor St., London, S.W.4.

EMSAC FOR ANTENNA SYSTEMS AND CONVERTERS. Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. **ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD.**, Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

COMPLETE RANGE of receivers by Trio, Lafayette, Hallcrafters, etc. Chassis, panels, cabinets. S.a.e. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

RECEIVERS & COMPONENTS
(continued)

VALVE BARGAINS

Any 5, 9/-; 10, 14/-; 100, £5 10s
from the following:

ECC82, ECL80, EF85, EF183, EBF89
EB91, EY86, PCC84, PCC89, PCF80,
PCF86, PCL82, PCL83, PCL84, PL36,
PL81, PY33, PY81, PY82, PY800.

AERIAL BOOSTERS 59/-

Three types of High Gain Transistorised
pre-amplifiers all at the same price

UHF 625 Type L45, Tunable over the
complete UHF Stations

VHF 405 Type L12 with Separate Tuning
for Band 1 and Band 2. Please state
channel numbers

FM UHF RADIO PRE-AMPLIFIER
SAE for Full Details. All complete with
battery and leads. 7 day money back
guarantee if not satisfied

**VELCO ELECTRONICS, 62 BRIDGE ST.
RAMSBOTTOM, BURY, LANCS.**

COMMUNICATIONS RECEIVERS: Ex-
Govt. bargains in the £10 to £20 range.
Example: B40, 640 kHz-30.5 MHz, cleaned,
checked, aligned, with circuit information,
£21. Carriage 40/- (England, Wales). Deposit
on crate £3. Also Murphy CAS and Pye
CAT first-class ex-navy receivers, B41,
CR300, PCR2 and others. Money back
guarantee. Calibrators, VTVMs, headphones,
components, at competitive prices. SAE
details. Phone any time. Callers welcome.
—P. R. GOLLEDEGE, G3EDW, Glen Tor,
Torrington, Devon. (STD 08-052) 2411.

SERVICE SHEETS

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for
most makes and types of Radios, Tape
Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not
available.

**OAKFIELD ENTERPRISES
LIMITED**

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1970 List now
available at 2/-
plus postage

If list is required
indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

SERVICE SHEETS
(continued)

**LARGE SUPPLIER
OF
SERVICE SHEETS**

(T.V., RADIO, TAPE RECORDERS,
RECORD PLAYERS, TRANSISTORS,
STEREOGRAMS, RADIOGRAMS,
CAR RADIOS)

Only 5/- each, Manuals from 10/-
plus large S.A.E.

(Uncrossed P.O. s please, original
returned if service sheets not available.)

**C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11**

We have the largest supplies of
Service Sheets (strictly by return of post).
Please state make and model number
alternative.

Free TV fault tracing chart or TV list on
request with order.

Mail order only.

SERVICE SHEETS (1925-1970) for Tele-
visions, Radios, Transistors, Tape Recorders,
Record Players, etc., by return post, with
free Fault-Finding Guide. Prices from 1/-.
Over 8,000 models available. Catalogue 2/6.
Please send S.A.E. with all orders/enquiries.
Hamilton Radio, 54 London Road, Bexhill,
Sussex.

RADIO, TELEVISION over 3,000 models.
JOHN GILBERT TELEVISION, 1b Shep-
herds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS. Radio, TV etc. 8,000
models. List 2/-. S.A.E. enquiries. TEL-
RAY, 11 Mauldland Bank, Preston.

**PLEASE MENTION
"PRACTICAL WIRELESS"
WHEN REPLYING TO
ADVERTISEMENTS**

FOR SALE

YUKAN SELF-SPRAY 50 PROFESSIONAL PAINT
WEEKS APPROVAL ONLY

Get these air drying **GREY HAMMER**
OR BLACK WRINKLE
(CRACKLE) finishes

Yukan Aerosol spraykit contains 16 ozs. fine
quality durable easy instant colour. No stove baking
required. Hammers available in grey, blue, gold,
bronze. Modern Eggshell Black Wrinkle (Crackle)
all at 15/11 at our counter or 16/11 carriage paid
per push-button self-spray can. Also Durable, heat
and water resistant Black Matt finish (12 ozs. self-
spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable
snap-on trigger handle (value 5/-) for 18/11, carriage
paid. Choice of 13 self-spray paint colours and primer
(floor car quality) also available. Please enclose cheque or
crossed P.O. for total amount direct to:

**YUKAN, 307A, EDGWARE ROAD,
LONDON, W.2.**

We supply many Government Departments, Municipal
Authorities, Institutes and Leading Industrial
Organisations—We can supply you too.

Open all day Saturday, Closed Thursday afternoons.

SEEN MY CAT? 5,000 items. Mechanical
& Electrical Gear, and materials. S.A.E.
K. R. WHISTON, Dept. PW. NEW
MILLS, Stockport.

FOR SALE
(continued)

**MORSE MADE !!
EASY**

FACT NOT FICTION. If you start **BIGHT** you will be
reading amateur and commercial Morse within a month.
(Normal progress to be expected.)

Using scientifically prepared 3-speed records you
automatically learn to recognise the code **RHYTHM**
without translating. You can't help it, it's easy as learning
a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896
send 8d. stamp for explanatory booklet to:
GGCHS (BOX 11), 45 GREEN LANE, PURLEY, SURREY

FOR SALE "Mullard" high speed valve
tester as new complete with index. Offers
invited. Tel: Shelsley Beauchamp 272 or
write W.E.I. Ltd. Sailors Bank, Broad-
heath, Worcester.

WANTED

CASH PAID for New Valves. Payment by
return. **WILLOW VALE, ELECTRONICS,**
4 The Broadway, Hanwell, London, W.7.
01-567/5400-2971.

WE BUY New Valves and Transistors. State
price: **A.D.A. MANUFACTURING CO.,**
116 Alfreton Road, Nottingham.

**WANTED NEW
VALVES ONLY**

Must be new and boxed
Payment by return
WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WANTED NEW VALVES, televisions,
radiograms, transistors, etc. **STAN WILL-
ETTS,** 37 High Street, West Bromwich,
Staffs. Tel.: WES 0186.

WE BUY New Valves, Transistors and clean
new components, large or small quantities,
all details, quotation by return. **WALTON'S
WIRELESS STORES,** 55 Worcester Street,
Wolverhampton.

WANTED EARLY WIRELESS ITEMS
1900-1920. Outside Horn, Hand-operated.
Springless, Gramophones. Please describe
and price wanted. T. Christen, 12 Princess
Terrace, Brighton 7, Sussex BN2-5JS.

VALVES AND TRANSISTORS required in
new condition. Any quantity purchased.
Quotation by return. Langrex, 16A Well-
field Road, Streatham, S.W.16. 01-769-0199.

NEWNES "RADIO & T.V. SERVICING"
1959-65 inclusive. State price/condition.
Thornley, 4 Cavendish Place, Bath.

HI-FI EQUIPMENT

SHURE GOLDRING Cartridges Post Free.
G800, M44/5/7 £7.17.6. M3D £5.5.0. M44E
£8.19.6. M55E £9.19.6. M75E/2 £16.10.0.
GARRARD SP25/2 £10.17.6. AP 75
£16.17.6 p. & p. 7/6. Ultimate Electronics,
38 Achilles Road, London, N.W.6. Mail
Order Only.

METAL WORK

METAL WORK: All types cabinets, chassis,
racks etc., to your specifications. PHIL-
POTTS METAL WORKS LTD., Chapman
Street, Loughborough.

TELEVISION



This private College provides efficient theoretical and practical training in Radio and TV Servicing. One-year day courses, commencing in Sept., January and April, are available for beginners, and shortened courses for men who have had previous training. Write for free prospectus to:—
London Electronics College, Dept. LX/4. 20 Penywern Road, Earls Court, London, S.W.5 Tel. 01-373 8721

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how **ICS** can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON. SW8

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

APPOINTMENTS

BOURNEMOUTH COLLEGE OF TECHNOLOGY

A CAREER FOR MEN OR WOMEN IN

ELECTRICAL OR ELECTRONIC ENGINEERING

University of London External Degree in Electrical Engineering

B.Sc. (Eng.) with Electronics
3 years full-time

Entry requirement:—

Maths (Pure & Applied) } 'A' level
Physics } 'O' level
+ Chemistry }

Study by the sea in Britain's foremost all-seasons resort.

Enquiries for prospectus and further information to:—

The Principal, Room 86,
College of Technology, Lansdowne,
Bournemouth, BH1 3JJ.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

SITUATIONS VACANT

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept 137K), Aldermaston Court, Aldermaston, Berks.

Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and in subsequent years.

Specialist training courses lasting approximately nine months according to the trainee's progress are held at intervals. Applications are now invited for the course starting in January 1971.

During training a salary will be paid on the following scale:—

Age 21	£848 per annum
22	£906 " "
23	£943 " "
24	£981 " "
25 and over	£1,023 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade I scale:—

Age 21	£1,023 per annum
22	£1,087 " "
23	£1,150 " "
24	£1,214 " "
25 (highest age point)	£1,288 " "

then by six annual increases to a maximum of £1,749 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970. Application forms and further particulars from:—

RECRUITMENT OFFICER, Government Communications Headquarters, Oakley, Priors Road, CHELTENHAM, Glos. GL52 5AJ Tel: No. Cheltenham 21491 Ext 2270

ENGINEERS, A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for **FREE 132 page guide: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

BOOKS & PUBLICATIONS

SURPLUS HANDBOOKS

- 119 set Circuit and Notes .. 7/0 p/p 9d.
- 1155 set Circuit and Notes .. 7/0 p/p 9d.
- H.R.O. Technical Instructions .. 6/0 p/p 9d.
- 38 set Technical Instructions .. 6/0 p/p 9d.
- 46 set Working Instructions .. 6/0 p/p 9d.
- 88 set Technical Instructions .. 7/8 p/p 9d.
- BC.221 Circuit and Notes .. 6/0 p/p 9d.
- Wavemeter Class D Tech. Instr. .. 6/0 p/p 9d.
- 18 set Circuit and Notes .. 6/0 p/p 9d.
- BC.1000 (31 set) Circuit and Notes .. 6/0 p/p 9d.
- CR.100/B.28 Circuit and Notes .. 10/6 p/p 1/-
- R.107 Circuit and Notes .. 7/6 p/p 9d.
- AR.88D Instruction Manual .. 18/6 p/p 9d.
- 62 set Circuit and Notes .. 7/0 p/p 9d.
- Circuit Diagram 5/6 each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J BC.348 (E.M.P.), BC.624, 22, 1475 (88), 1392.
- Colour Code Indicator .. 2/6 p/p 6d.
- 52 set Sender and Receiver circuits 8/- post free

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE, 28 TALBOT GARDENS, LEEDS 8

R. F. Units

Type 26 tunes 50 to 65 Mc/s with 7 Mc/s I.F. O/P uses valves EF54 x 2 & EC52 as slow motion drive require 250v H.T. & 6.3v to work, will mod up to 100 Mc/s in new condition with circ.

Price 42/- plus 7/6 post.

RF24 also available swt tuned 20 to 30 Mc/s with 3 x 8P61 valves, new cond with circ.

Price 15/- plus 5/- post.

Test Set 210

V.H.F. osc unit used to test above RF units covers 20 to 85 Mc/s in 4 bands, with 2 Mc/s xtal check. Also as noise generator with 50 Ma meter tuned with large slow motion drive with calibration charts, these have internal P.U. high cycle, require 250v at 40 Ma H.T. and 6.3v 4a o work. Supplied in good condition.

Price 23-5 plus 12/6 carr.

Rx Unit 16048

Special purpose V.L.F. Rx part of Aircraft Landing system, contains large number of modern good quality parts as follows: 8 type LA 2540 Winkors, 4 x OC 450 transistors 811 FNP, 6 x EF72 valves, 5 miniature relays coil IK 2p c/o size 1/2 x 1/2 x 1/2", 2 x 14,000 ohm relays, OB2 105v stab, 85A2 85v stab, 7 x 400 P.I.V. 500Ma diodes, 15v Zener, 2 x 24v relays, also Tant conds, plugs & sks, W, W. pots, etc. Supplied in new condition, in case.

Price 42/- plus 7/6 post.

O/P & Test Unit

Part of above contains 2 x LA2503 Vinkorst 4 x OC450 Transistors, 15v Zener, 4 x miniature relays, 5 x L.V. swt diodes, 3 x EF72 valves, also pots conds etc. Supplied in new condition.

Price 14/- plus 3/- post.

S. A. E. for list or enquiry

A. H. SUPPLIES
57 Main Rd., SHEFFIELD.
S9.5HL.

BRAND NEW AR88D COMMUNICATIONS RECEIVERS. AC mains input 110 volts or 250 volts. Frequency in 6 bands 535 kc/s up to 32 megs, output impedance 2.5-600 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

COMPUTER BOARDS Min 30 transistors and diodes and res. etc. 10 boards at 10/- plus 2/6 p.p.; 25 boards at 22/6 plus 4/6 p.p.

BARGAIN PARCELS 14lb at 29/- plus 6/6 p.p.; 28lb at 55/- plus 12/6 p.p.; 56lb at 90/- plus 25/- p.p. Contain pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £22s. Lucky Dip Service.

FURZILL BEAT FREQUENCY OSCILLATOR 0-10 kc/s, 110/250 volt. Good condition complete with spares. £5.10.0 plus 25/- p.p.

VHF Receiver, Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3.0.0 plus £1 p.p.

VHF AERIAL TUNING UNITS consisting of the following: 1—1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs. with 25/30 watts R.F. input. Size only 5 1/4" x 4 1/4" x 5". Sealed. Price 27/6 p.p. 5/-.

CRYSTALS AS NEW: Hc 6u, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,680; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s and 10 x 1465 Kc/s. 10/- including 1/6 p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS 10% tolerance 1/8 & 1 watt. Perferred values in packets of 10. Our price 10/- per 100, 19/- per 200, 27/- per 300, 500 at 42/6. Our selection. p.p. 1/6 per 100 and 6d. per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details; Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal — 12/- per doz. plus 3/6 p.p.
Trimmers with Xtal — 15/- per doz. plus 3/6 p.p.
Also 20 PF min. brand new air spaced.
10/- per doz. plus 3/6 p.p.

NEW TOGGLE SWITCHES. 250 volt 3-5 amps. 2 pole 2 way. 12/6 dozen, 2/6 post and packing.

SIGNAL GENERATORS OSCILLATOR No. 2. Size 12in. x 3 1/2in. x 9in. Ideal for VHF work. 20-80 Mc/s. Functions are AM/CW. Deviation up to 40 Kc/s R.F. meter. Measuring levels: RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories; 230V AC 12V DC. £20.0.0 plus 15/- p.p.

TF 144 G Signal Generators 85 Kc/s to 25 Mc/s. Good condition and complete with accessories. £22.0.0 plus 30/- p.p.

AERIALS, New Condition. Whip type 11ft 12/6 each. Used condition 12ft 10/- each. All collapsible type. Post and packing 3/6. Bases for the above 5/-, post and packing 2/6.

TELESCOPIC MASTS. New condition, 20ft closes to 5ft 9in. 80/-, carriage 15/-, 34ft closes to 5ft 9in. 120/-, carr. 15/-. Used condition, 20ft 70/-, 34ft 80/-, carr. 15/-. Base for same 20/-, carr. 7/6.

New lengths 50ft Coaxial cable 70 ohms (approx.), coax plugs 5/-, price 20/- each post and packing 2/-.

Magnetic Transducers new, price 7/6 post and packing 2/-.

New Aerial Wire on boards 7/22 uncovered. Length 75ft. 8/- post and packing 2/6.


New small fuse boxes 250 volts 15 amps. 17/6 each post and packing 3/-.

Meters, moving coil ex equipment, good condition. Also 15 Amp DC, 20 Amp DC, 40 Amp DC, And R.F. Thermo Couple Meters 0-1 Amp, 2in diameter 10/-, post and packing 5/-.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY.

A. H. THACKER,
Radio Dept.,
HIGH STREET, CHESLYN HAY,
Nr. Walsall, Staffs.

DIMMASWITCH

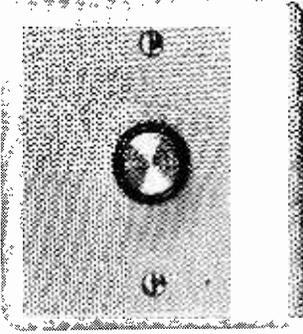

This is an attractive dimmer unit which fits in place of the normal modern light switch. The ivory mounting plate matches modern fittings and the control knob is bright chrome. An ON/OFF switch is incorporated to control 40-600 watts of all lights except fluorescents at mains voltages from 200-250V, 50 Hz.

Competitive products sell at £4.19.6d.—our price is £3 4s. We also offer at £2 14s. a complete kit of parts with instructions enabling you to build this dimmer yourself.

The circuit uses a miniature RCA triac and a diac triggering device to give complete reliability. Radio interference suppression is included.

Post and Packing 1/6d. extra.

Please send Cash with Order to:—

DEXTER & COMPANY

ULVER HOUSE, 19 KING STREET,
CHESTER CH1 2AH.

Tel: Chester 25883

As supplied to H.M. Govt. Departments, Hospitals
Local Authorities, etc.

LOOK AT THESE PRICES

CARTRIDGES

Acos GP67-2, GP91-3SC 22/6; Acos GP93-1 20/8;
Acos GP94-1 33/6; Sonoton 9TACH 39/6; All
above in makers cartons; BSR X4H 30/-

1 WATT AMPLIFIER

Complete with volume control, rectifier, smoothing
ct, fully transistorised, OUR PRICE 27/6

PLUGS & SOCKETS

Phono plugs, red, white, yellow, green, grey, blue,
black 11d 9/- per doz; Coaxial plugs, aluminium 1/6;
Coaxial couplers 1/-; 2 pin DIN plugs 3/-; 3 pin
DIN plugs 3/-; 5 pin DIN plugs 3/5; 2 pin, 3 pin
DIN sockets 1/6; wanders Plugs 6d; sockets 8d;
Banana plugs 1/1, sockets 1/-; 3.5mm J/Plugs 1/6
& 2/6; Standard J/Plugs with solder terminals 2/-;
Chrome 3/-; Side Entry J/Plugs black and chrome
4/9; Insulated j/sockets, o/cct 3/3, c/cct 3/6.

ELECTROLYTIC CAPACITORS

4uF, 150v 9d; 8uF 500v 3/-; 8uF 12v 10d; 8uF +
8uF 450v 4/3; 10uF 150v 9d; 12uF 25v 8d; 16uF
450v 2/9d; 16uF +16uF 450v 4/8; 30uF 10v 9d; 50uF
10v 9d; 100uF 9v 9d; 100uF 12v 9d; 150uF 12v 9d;
320uF 9v 1/-; 1500uF 30v 3/9; 2.5uF 16v 6d;
10uF 16v 1/6; 5000uF 25v 10/-; 10,000uF 25v
15/-; 20,000uF 30v 21/-.

MICROPHONES

Acos Mic 45 22/6; Acos Mic 60 19/11; Planet CM70
30/-; Hand Mike 16/-; Shure 201 25; Shure 444
410.10.0.

VALVES

PY81 7/2; PCL82 7/9; EF183 9/-; EF184 9/-.

GEORGE FRANCIS (Dept PW),

88 Balderton Gate, Newark, Notts.
Telephone: Newark 4783.

AUDIO EFFECTS

5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT. No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils 2T, 0.5 to 1.54 Mhz 3T, 1.67 to 5.3 Mhz 4T, 5.0 to 15 Mhz 5T, 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.

POWER CONTROLLER. Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kV triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £6.9.6. Ready built £9.4.6 plus 5/6 P. P. & Ins.

REVERBERATION AMPLIFIER. Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly three dimensional for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2 in x 3 in x 4 1/2 in. £10.4.0 plus 6/- P. P. & Ins.

VOX SWITCH. This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 42/6. Ready built, tested and guaranteed. 62/6, plus 2/6 P. P.

METRONOME UNIT. Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive black and white polythene case, 37/6 post paid.

MORSE OSCILLATOR. PC board, transistors, high stab. components, battery carrier, car piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid.

STRAIGHT FROM THE PRESS. Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid.

JUST ARRIVED IN STOCK. Texas transistors. Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid.

Free lists with every order. For lists only send 1/6 (deductible from first order).

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

IR5	5/6	DL35	4/9	EL84	4/9	PL82	5/9
185	4/3	DL92	5/8	EY61	7/-	PL83	6/2
1T4	2/9	DL94	6/6	EY86	6/3	PL84	6/-
284	5/9	DL96	7/3	EZ80	4/6	PL500	12/9
3V4	6/6	DY86	5/3	EZ81	4/6	PL504	13/8
6/30L2	11/6	DY87	5/3	KT61	9/3	PY32	10/-
6A4Q5	5/-	EABC80	6/3	KT86	16/6	PY33	10/-
6P25	12/-	EB91	2/-	N78	17/-	PY81	8/-
6BN7GT	4/6	EB338	7/9	PC86	10/3	PY82	8/-
2SL6GT	4/6	EB391	6/-	PC88	10/3	PY83	5/6
30C18	12/9	EC81	3/6	PC97	7/6	PY88	6/6
30FL1	12/6	EC82	4/4	PC900	7/7	PY800	7/6
30L15	12/9	EC83	4/9	PC834	6/3	PY801	7/6
30P4	11/9	EC85	5/6	PC895	9/3	R19	6/8
30P19	11/9	EC85	5/6	PC899	9/3	UB25	12/9
30PL1	12/3	EC81	5/9	PCF80	5/11	U28	11/6
30PL13/14	12/3	EC81	7/7	PCF86	8/9	U91	12/-
30PL14/13/6	12/3	ECL82	6/3	PCF801	6/6	U261	14/-
CC835	13/-	ECL86	7/6	PCF802	8/9	U329	14/-
DAC32	6/9	EF89	4/6	PCF805	12/9	UAC800	6/-
DAF96	7/6	EF89	4/6	PL8611	11/-	UB99	6/8
DF83	7/6	EF86	6/3	PCL82	6/9	UC085	7/8
DF91	2/9	EF89	4/9	PCL83	11/9	UC81	6/6
DF96	7/-	EF91	2/6	PCL86	5/6	UCL82	6/9
DK32	6/9	EF183	5/6	PCL86	8/6	UL84	8/3
DK91	5/6	EF184	6/3	PF2000	11/6	UY41	7/6
DK92	6/3	EL36	9/3	PL8	9/3	UY85	6/3
DK95	7/8	EL33	9/3	PL81	9/3	Z77	7/6

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

BRAND NEW FULLY GUARANTEED TRANSISTORS

SEND FOR **NEW LIST** **NEW PRICES**

1N4001	1/8	AAZ12	4/-	BPY10	19/6
1N4002	1/8	AAZ13	2/6	BBK20	9/6
1N4003	2/-	AAZ17	2/-	BBK23	7/6
1N4004	2/-	AC126	5/-	BBY76	3/-
1N4005	2/6	AC127	5/-	BBY27	4/-
1N4006	4/-	AC127Z	10/-	BBY28	5/-
1N4007	4/-	AC128	5/-	BBY29	5/-
1N4009	1/8	AC153	4/-	BBY50	5/-
1N4148	1/8	AC154	3/-	BBY53	5/-
2G210	12/6	AC189	3/-	BBY66	5/-
2G240	49/6	AC176	5/-	BBY67	5/-
2G301	4/-	AC187	6/-	BBY95A	3/-
2G302	4/6	AC188	6/-	BBY95	3/-
2G303	5/-	ACY17	6/-	CV109	3/6
2G306	6/-	ACY18	4/-	BY103	4/6
2G308	6/-	ACY19	4/-	BY128	3/-
2G309	8/-	ACY20	4/-	BY127	4/-
2G371	4/6	ACY21	4/6	BYZ10	8/-
2G374	5/6	ACY22	3/6	BYZ11	7/-
2G381	6/-	ACY28	3/6	BYZ12	6/-
2G382	6/-	ACY34	4/-	BYZ13	6/-
2G383	5/-	ACY36	5/-	BYZ16	20/-
2N404	4/6	ACY39	11/-	BYZ16	12/6
2N696	3/6	ACT46	8/-	GPT102	6/-
2N697	3/6	AD140	10/-	GPT103	4/6
2N698	8/6	AD149	10/-	MPP102	8/6
2N706	2/-	AD161	7/6	MPP103	7/6
2N707	2/6	AD162	7/6	MPP104	7/6
2N707	9/6	AF102	12/6	MPP105	8/6
2N708	2/-	AF114	6/6	AA5	4/-
2N814	4/6	AF115	6/6	OA7	4/-
2N918	4/6	AF116	6/6	OA9	2/-
2N918	7/6	AF117	5/-	OA10	5/-
2N919	4/-	AF118	12/6	OA47	2/-
2N920	5/-	AF124	6/6	OA70	2/-
2N922	8/6	AF125	6/6	OA71	2/-
2N930	9/6	AF126	4/6	OA73	2/-
2N1131	6/-	AF127	4/6	OA74	2/-
2N1132	6/6	AF139	6/-	OA79	2/-
2N1303	4/6	AF178	9/6	OA81	2/-
2N1304	5/-	AF181	8/6	OA85	2/6
2N1305	5/-	AF186	8/6	OA86	4/-
2N1306	5/-	AF239	8/6	OA89	2/-
2N1307	6/6	AFY19	22/6	OA91	1/6
2N1308	6/6	AFZ11	12/6	OA95	1/6
2N1309	5/-	AFZ12	15/-	OA200	1/6
2N1613	4/6	ASV26	5/-	OA202	2/-
2N2147	15/-	ASV27	8/6	OA210	5/6
2N2160	12/6	ASV28	8/6	OA211	7/6
2N2267	25/-	ASV29	9/6	OA225	7/6
2N2648	10/6	ASV35	2/6	OA228	8/6
2N2904	6/-	ASZ21	8/6	OA229	9/6
2N2905	7/6	AUY10	19/6	OA231	9/6
2N2925	4/-	B3M	19/6	OA234	9/6
2N2926	2/6	BA110	5/-	OA238	9/6
2N3011	5/-	BA Y31	2/6	OC18	8/6
2N3053	5/-	BC108	2/6	OC19	7/6
2N3054	10/-	BC108	2/6	OC20	19/6
2N3065	15/-	BC109	2/6	OC22	9/6
2N3702	2/6	BC113	5/-	OC23	10/-
2N3703	2/6	BC116	8/6	OC24	10/6
2N3704	8/6	BC115	8/6	OC25	10/6
2N3705	3/6	BC137	7/6	OC26	5/-
2N3707	3/-	BC135	6/-	OC28	12/6
2N3709	2/6	BC136	7/-	OC29	12/6
2N3710	2/6	BC137	8/-	OC35	10/6
2N3711	2/6	BC138	9/-	OC36	12/6
2N3730	10/-	BCY12	6/6	OC41	6/6
2N3731	12/6	BCY31	6/6	OC42	6/6
2N3794	2/6	BCY32	10/-	OC43	8/-
2N3819	7/-	BCY33	4/-	OC44	4/-
2N3820	17/6	BCY34	5/-	OC45	2/6
2N3823	17/6	BCY38	6/6	OC46	5/6
2N4058	3/6	BCY40	8/6	OC70	2/6
2N4081	3/-	BCY40	8/6	OC71	3/-
2N4286	3/-	BCY42	5/-	OC72	5/-
2N4288	3/-	BCY43	5/-	OC73	6/-
2N4289	3/6	BCY70	4/-	OC74	6/-
2N4290	3/-	BCZ11	7/6	OC75	5/-
2N4291	3/-	BCZ17	8/6	OC78	7/6
2N4292	3/-	BC148	2/6	OC77	8/-
40361	11/-	BC149	4/-	OC78	5/-
40382	12/-	BP152	6/6	OC81	5/-
25001	10/-	BP184	3/6	OC81D	4/-
28002	10/6	BP185	3/6	OC82	5/-
28003	9/6	BP194	12/6	OC83	5/-
28004	9/6	BEN3000	5/-	OC84	5/-
28005	14/-	BF115	5/-	OC122	10/-
28012	25/-	BF154	8/6	OC123	5/-
28013	20/-	BF158	6/6	OC139	5/-
28017	15/-	BF159	12/6	OC140	8/6
28034	12/6	BF163	8/-	OC141	15/-
28036	25/-	BF167	5/-	OC189	4/-
28320	9/-	BF173	6/6	OC170	5/-
28321	6/-	BF180	7/6	OC171	5/-
28322	7/6	BF181	7/6	OC172	5/-
28333	10/-	BFY30	6/6	OC201	9/6
28394	12/6	BFX88	5/-	OC202	12/6
28512	9/6	BFY20	12/6	OC203	7/6
28701	8/6	BFY50	4/6	OC204	8/-
28702	11/-	BFY61	4/-	OC205	12/6
28731	8/6	BFY52	4/6	OC206	15/-
28732	8/6	BFY53	4/6	OC207	15/-
28739	8/6	BFY64	8/6	OC211	19/6
AA178	8/6	BLY10	20/-	ORP12	10/-
AA Y12	5/-	BLY11	22/6	ORP60	8/-

INTEGRATED CIRCUITS

2N3055	15/-	Mullard I15Watt Silicon Power	25 + 13/- 100 + 11/-
IN4003 and 42-	1 AMP 300-400v		25 + 1/9 100 + 1/6 500 + 1/3
AF139	6/-	Siemens V.H.F.	25 + 5/3 100 + 4/6 500 + 3/9
AF186	8/-	Mullard V.H.F.	25 + 7/3 100 + 6/- 500 + 5/4
OC170	5/-		25 + 4/3 100 + 3/6
OC171	6/-		25 + 5/3 100 + 4/6
BY127	4/6	Mullard 1000v 1 amp Plastic	25 + 3/3 100 + 3/-
BT102/500R	15/-	Mullard Thyristor	500 p.i.v. 6.5a 25 + 12/6 100 + 11/-
OA200/OA202	2/-	SILICON Diodes	25 + 1/6 100 + 1/3 500 + 1/1
OC42	6/-	Mullard	25 + 5/3 100 + 4/9 500 + 4/3
OC45	3/6	Mullard	25 + 3/6 100 + 2/6 500 + 2/-
OC75	5/-	Mullard	25 + 4/3 100 + 3/6 500 + 3/-
OC20	19/6	Mullard 100v	25 + 15/9 100 + 14/6 500 + 13/3
IN4005	2/6	600v 1 amp	25 + 2/- 100 + 1/9 500 + 1/6
IN4006	IN4007	800v 3/- 1000v 4/-	25 + 2/10.....3/3 100 + 2/6.....2/9 500 + 2/3.....2/6
OC139	5/-	Mullard	25 + 4/- 100 + 3/3 500 + 3/-
OC140	7/6	Mullard	25 + 6/- 100 + 5/- 500 + 4/9

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns' Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Colour T.V. Servicing
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

EST. 1891

Dept. 171, Intertext House, Stewart's Road, London, S.W.8.

Please send me the ICS prospectus—free and without obligation. (state Subject or Exam).....

NAME.....

ADDRESS.....

10/70

INTERNATIONAL CORRESPONDENCE SCHOOLS

PLEASE NOTE MINIMUM ORDER SHOULD BE 10/-
Quantity Prices 100+ Phone (01) 723 0401 Ex. 4. All listed devices are from stock at time of going to press. Please add 1/6 post packing to your order.

New Autumn List. New devices. New prices. Ask for List 36. Send for free copy today!
Discounts 10% on 12+ any one type 15% on 25+ any one type

HENRY'S RADIO

Mail Order Dept. Components, Sharn Dorr
102 EDGWARE ROAD, LONDON W.2
Telephone 01-723 1008 9

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/6. No C.O.D. orders accepted

PLEASE NOTE THAT THE VALVES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

PLEASE NOTE THAT ALL PRICES ARE IN DECIMAL PARTS OF £, I.E. IN NEW PENCE

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

0A2	0.88	6AR5	0.85	6EJ7	0.85	6Y6G	0.85
0A3	0.45	6AR6	0.40	6EWE	0.65	7Y4	0.60
0B2	0.85	6AR8	0.85	6F1	0.70	9BW6	0.50
0B3	0.80	6ASTG	0.80	6F5	0.50	10C2	0.50
0C3	0.38	6AT6	0.30	6F6G	0.30	10D1	0.50
0D3	0.35	6AU6	0.25	6F11	0.38	10D2	0.40
1B9GT	0.88	6AV6	0.30	6F13	0.38	10F1	0.30
1L4	0.20	6AW8A	0.55	6F14	0.65	10F9	0.50
1R4	0.55	6BAE	0.25	6F15	0.65	10F18	0.45
1R5	0.55	6BE6	0.30	6F18	0.45	10L1	0.45
1R4	0.27	6BF5	0.80	6F23	0.80	10LD11.0	0.60
1R5	0.25	6BF6	0.50	6F24	0.75	10L13	0.55
1T4	0.25	6BH6	0.45	6F25	0.75	10P14	1.10
1U4	0.27	6BJ6	0.45	6F26	0.35	12AB5	0.80
1U5	0.60	6BK7A	0.55	6F28	0.80	12AC6	0.40
1V2	0.45	6BL7GA	0.75	6F4	0.50	12AD5	0.40
1X2B	0.40	6BN5	0.45	6F5GT	0.50	12AL5	0.45
2DE1	0.35	6BN5	0.43	6F7	0.45	12AQ5	0.43
3A4	0.85	6BN6	0.40	6K6GT	0.55	12AT6	0.30
3B2S	2.15	6BQ5	0.25	6K7	0.35	12AT7	0.33
3BP1	2.75	6BR8	0.65	6K8G	0.85	12AU6	0.30
3Q4	0.40	6B87	1.30	6K23	0.55	12AV7	0.30
3S4	0.85	6B96	0.85	6L6GT	0.75	12AV8	0.35
3Y4	0.45	6BW7	0.70	6L6GT	0.45	12AV7	0.50
3Y4G	0.60	6BX6	0.25	6L7	0.40	12AX7	0.30
3Y4G	0.38	6BZ6	0.35	6L18	0.45	12AY7	0.70
5U4GB	0.42	6C4	0.33	6LD20	0.40	12BTA40.55	0.35
5V4G	0.42	6C9GT	0.40	6N7GT	0.40	12BA6	0.35
5Y3GT	0.92	6CA4	0.28	6P1	0.60	12BA7	0.35
5Z3	0.50	6C2T	0.50	6R28	0.65	12AV6	0.35
5Z4G	0.40	6D40	0.70	6B2H	0.40	12BH7	0.40
6/30L2	0.75	6CDGGA	0.8A	6T7	0.40	12BY7	0.55
6AB4	0.85	6CG7	1.15	6S7	0.35	12K5	0.85
6AF4A	0.50	6CG7	0.50	6SK7	0.35	12K7GT0.35	0.35
6AG7	0.40	6CH6	0.55	6SL7GT0.35	0.35	12Q70.35	0.35
6AH6	0.50	6CL6	0.50	6SN7GT0.35	0.35	12R7	0.45
6AJ6	0.30	6C9G	0.65	6S7	0.35	12S7	0.35
6AK5	0.30	6C7	0.85	6SR7	0.40	20D1	0.80
6AK6	0.57	6D3	0.45	6T8	0.35	20L1	1.10
6AL3	0.43	6D6	0.75	6U4GT	0.60	20P1	0.50
6AL5	0.20	6DK6	0.48	6U8A	0.40	20P4	1.10
6AM5	0.32	6DQ6B	0.83	6V6GT	0.38	20F5	1.20
6AM6	0.33	6A4	0.75	6X7	0.35	20Z4	0.30
6AQ5	0.36	6EA8	0.8	6X5GT	0.30	25L6GT	0.45
6AQ6	0.55	6EH7	0.30	6XS	0.55	25Z4G	0.30

First Quality Fully Guaranteed



ELECTRONIC VALVES

25Z6GT	0.85	50B5	0.45	CY31	0.35	ECC81	0.33
30A5	0.45	50C5	0.40	DAF96	0.42	ECC82	0.30
30A6	0.40	50CD6G1.50	0.40	DF96	0.42	ECC83	0.30
30C1	0.30	50L6GT0.50	0.50	DK40	0.55	ECC84	0.30
30C15	0.30	83A1	1.50	DK92	0.50	ECC85	0.30
30C17	0.35	86A2	0.40	DK96	0.42	ECC86	0.30
30C18	0.75	90AV	2.50	DL96	0.42	ECC89	0.50
30P5	0.35	90C1	0.80	DY86	0.33	ECC91	0.20
30FL1	0.70	90CV	1.25	DY87	0.35	ECC189	0.60
30FL12	0.83	807	0.50	DY802	0.50	ECP80	0.35
30FL14	0.75	811A	1.80	E55L	2.75	ECP82	0.35
30L1	0.40	812A	3.50	E88CC	0.65	ECP83	0.75
30L15	0.85	813	3.75	E130L	5.00	ECP86	0.85
30L17	0.80	860A	0.75	E130P	0.85	ECP90.41.50	0.85
30P12	0.30	8642	0.65	KABC00.25	0.85	ECH42	0.70
30P19	0.80	6080	1.50	EAF42	0.55	ECH81	0.30
30PL1	0.70	6146	1.50	EBC33	0.50	ECH83	0.40
30PL13	0.83	6146B	2.50	EBC41	0.55	ECH84	0.45
30PL14	0.80	6360	1.25	EBC81	0.30	ECL80	0.50
35A3	0.85	6936	0.75	EBC82	0.40	ECL81	0.45
35A5	0.75	7199	0.75	EBF83	0.40	ECL82	0.35
35B5	0.65	7360	1.80	EBF89	0.30	ECL83	0.65
35C5	0.40	7586	1.25	EC53	0.50	ECL84	0.55
35D5	0.70	7895	1.25	EC86	0.60	ECL85	0.65
35L6GT	0.50	9002	0.35	EC88	0.60	ECL86	0.40
35W4	0.30	9003	0.60	EC90	0.33	ECL89	0.50
35Z4	0.30	AZ1	0.55	EC92	0.35		1.50
35Z5GT	0.40	CB1L	0.80	EC89	0.50	EF37A	0.60
60A5	0.70	CB1L1	0.80	EC810	2.25	EF39	0.40
				EY40	0.60	EF40	0.50

EF41	0.65	EZ40	0.45	PCL88	0.80	U78	0.80
EF42	0.70	EZ41	0.45	PCL89	0.85	U191	0.75
EF80	0.25	EZ60	0.85	PD500	1.50	U201	0.85
EF82	0.85	EZ81	0.98	PF60	0.50	U281	0.40
EF85	0.35	GZ501	0.80	PF86	0.80	U282	0.40
EF86	0.30	GZ30	0.40	PF818	0.85	U301	0.40
EF89	0.28	GZ31	0.33	PFL200	0.70	U403	0.50
EF91	0.33	GZ32	0.48	PL33	0.35	U404	0.40
EF92	0.40	GZ33	0.70	PL36	0.55	U801	1.00
EF95	0.30	HABC80	0.80	PL81	0.60	UABC80	0.80
EF97	0.85	HK90	0.45	PL82	0.45	PL82	0.45
EF183	0.30	KT68	1.70	PL83	0.45	PL83	0.45
EF184	0.25	KT78	1.70	PL302	0.80	UBC41	0.50
EF800	1.00	N78	1.15	PL504	0.80	UBC81	0.40
EK90	0.30	PABC80	0.50	PL508	0.90	UBF80	0.40
EL34	0.50	PC86	0.40	PL801	0.80	UBF89	0.35
EL36	0.50	PC88	0.60	PL802	0.75	UBL1	0.50
EL41	0.55	PC88	0.80	PM84	0.50	UBL21	0.60
EL42	0.58	PC87	0.60	PF30	1.20	UC92	0.85
EL81	0.65	PC84	0.40	PC88	0.55	UC85	0.30
EL82	0.65	PC85	0.40	PC89	0.50	UC86	0.30
EL84	0.25	PC86	0.40	PC88	0.55	UC87	0.30
EL85	0.43	PC87	0.50	PC89	0.50	UC88	0.30
EL86	0.40	PC88	0.55	PC88	0.55	UC89	0.30
EL90	0.35	PC89	0.50	PC89	0.50	UC92	0.85
EL95	0.35	PC89	0.55	PC89	0.55	UC91	0.35
EL360	1.15	PC89	0.85	PC89	0.50	UC92	0.85
EL803	1.00	PC89	0.85	PC89	0.50	UC93	0.30
EL821	0.55	PC89	0.80	PC89	0.50	UC94	0.30
EL822	0.90	PC89	0.35	PC89	0.50	UC95	0.30
EL823	0.90	PC89	0.35	PC89	0.50	UC96	0.30
EL824	0.90	PC89	0.35	PC89	0.50	UC97	0.30
EL825	0.90	PC89	0.35	PC89	0.50	UC98	0.30
EL826	0.90	PC89	0.35	PC89	0.50	UC99	0.30
EL827	0.90	PC89	0.35	PC89	0.50	UC100	0.30
EL828	0.90	PC89	0.35	PC89	0.50	UC101	0.30
EL829	0.90	PC89	0.35	PC89	0.50	UC102	0.30
EL830	0.90	PC89	0.35	PC89	0.50	UC103	0.30
EL831	0.90	PC89	0.35	PC89	0.50	UC104	0.30
EL832	0.90	PC89	0.35	PC89	0.50	UC105	0.30
EL833	0.90	PC89	0.35	PC89	0.50	UC106	0.30
EL834	0.90	PC89	0.35	PC89	0.50	UC107	0.30
EL835	0.90	PC89	0.35	PC89	0.50	UC108	0.30
EL836	0.90	PC89	0.35	PC89	0.50	UC109	0.30
EL837	0.90	PC89	0.35	PC89	0.50	UC110	0.30
EL838	0.90	PC89	0.35	PC89	0.50	UC111	0.30
EL839	0.90	PC89	0.35	PC89	0.50	UC112	0.30
EL840	0.90	PC89	0.35	PC89	0.50	UC113	0.30
EL841	0.90	PC89	0.35	PC89	0.50	UC114	0.30
EL842	0.90	PC89	0.35	PC89	0.50	UC115	0.30
EL843	0.90	PC89	0.35	PC89	0.50	UC116	0.30
EL844	0.90	PC89	0.35	PC89	0.50	UC117	0.30
EL845	0.90	PC89	0.35	PC89	0.50	UC118	0.30
EL846	0.90	PC89	0.35	PC89	0.50	UC119	0.30
EL847	0.90	PC89	0.35	PC89	0.50	UC120	0.30
EL848	0.90	PC89	0.35	PC89	0.50	UC121	0.30
EL849	0.90	PC89	0.35	PC89	0.50	UC122	0.30
EL850	0.90	PC89	0.35	PC89	0.50	UC123	0.30
EL851	0.90	PC89	0.35	PC89	0.50	UC124	0.30
EL852	0.90	PC89	0.35	PC89	0.50	UC125	0.30
EL853	0.90	PC89	0.35	PC89	0.50	UC126	0.30
EL854	0.90	PC89	0.35	PC89	0.50	UC127	0.30
EL855	0.90	PC89	0.35	PC89	0.50	UC128	0.30
EL856	0.90	PC89	0.35	PC89	0.50	UC129	0.30
EL857	0.90	PC89	0.35	PC89	0.50	UC130	0.30
EL858	0.90	PC89	0.35	PC89	0.50	UC131	0.30
EL859	0.90	PC89	0.35	PC89	0.50	UC132	0.30
EL860	0.90	PC89	0.35	PC89	0.50	UC133	0.30
EL861	0.90	PC89	0.35	PC89	0.50	UC134	0.30
EL862	0.90	PC89	0.35	PC89	0.50	UC135	0.30
EL863	0.90	PC89	0.35	PC89	0.50	UC136	0.30
EL864	0.90	PC89	0.35	PC89	0.50	UC137	0.30
EL865	0.90	PC89	0.35	PC89	0.50	UC138	0.30
EL866	0.90	PC89	0.35	PC89	0.50	UC139	0.30
EL867	0.90	PC89	0.35	PC89	0.50	UC140	0.30
EL868	0.90	PC89	0.35	PC89	0.50	UC141	0.30
EL869	0.90	PC89	0.35	PC89	0.50	UC142	0.30
EL870	0.90	PC89	0.35	PC89	0.50	UC143	0.30
EL871	0.90	PC89	0.35	PC89	0.50	UC144	0.30
EL872	0.90	PC89	0.35	PC89	0.50	UC145	0.30
EL873	0.90						

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Elec. Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Prac. Electronics — Radar Tech. — Frequency Modulation — Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work — Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Elec. Equipment — Garage Management.

"WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy now—FREE and without obligation.



POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-236 8080. Printed in England by Index Printers. Dunsdale, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2 5s 0d.
PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

• **ELECTRONIC COMPONENTS AND EQUIPMENT**
AUDIO AND TEST GEAR
 356 EDGWARE ROAD LONDON W.2
 TEL. 01-402 4735


• **ELECTRONIC ORGANS PUBLIC ADDRESS**
DISCOTHEQUE EQUIPMENT
 309 EDGWARE ROAD LONDON W.2
 TEL. 01-723 6963

• **HIGH FIDELITY SALES**
AND DEMONSTRATIONS
 354, EDGWARE ROAD LONDON W.2
 TEL. 01-402 5854

OPEN MONDAY TO SATURDAY 9AM TO 6PM. THURS 9AM TO 1PM. OPEN ALL DAY SATURDAY

COMPLETE STEREO SYSTEM FOR £39-10-0

HENELEC 5-5 STEREO AMPLIFIER. Inputs for ceramic cartridge. Aux./Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12½ x 3½ x 6½. Fitted headphone socket.
 Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10watt speakers, twin tweeters and crossover with polished wood cabinets 18" x 11" x 7". Also plinth and cover.

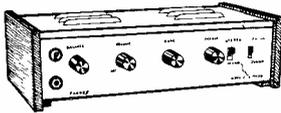


- **COMPLETE STEREO SYSTEM** (Rec. Price £50), **£39-10-0** p.p. 20/-
- **AMPLIFIER ONLY** £13-19-6, p.p. 7/6
- **TE1035 RECOMMENDED STEREO PHONES** 39/6

UNBEATABLE VALUE !!

BUILD THIS VHF FM TUNER

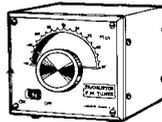
5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.



PARTS TOTAL COST **£6.19.6**, p.p. 3/6
DECODER £3.19.6 (FOR STEREO) p.p. 3/-
 ASK FOR BROCHURE No. 3.

New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silver front. All local and continental stations. Complete detailed instructions.

BUILD YOURSELF A QUALITY RADIO

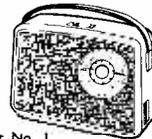

Total cost **£6.19.6**, p.p. 6/6

Ask for Leaflet No. 1.

SINCLAIR EQUIPMENT Z30 75/- each, stereo 60 £8-10-0, PZ5 79/6, PZ6 £6-19-6, Z50 £5-9-6, PZ8 £5-19-6.


SPECIAL OFFER 2 of Z30, stereo 60, PZ5 (usually £23-10) or with PZ6 in place of PZ5 £21 **£19**

WHEN IN LONDON visit the new Disco Centre at "354" and component shop at "356" Edgware Road, W.2.

TEST EQUIPMENT FOR YOUR HOME



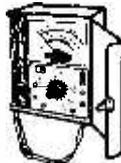AF105 50k/v multimeter (illus.), price £8-10, p.p. 3/6, leather case 28/6
200M 20k/v multimeter price £3-17-6, p.p. 3/-, case 12/6
TE20D RF Generator (illus.), price £15, p.p. 7/6
TE22D Matching Audio Generator, price £17, p.p. 7/6
TE65 Valve Voltmeter, price £17-10-0, p.p. 7/6
 Full details and complete range in catalogue



SLIM POCKET TEST GEAR

- **SIGNAL INJECTOR** 35/- p.p. 1/6
- **SIGNAL TRACER** 29/6 p.p. 1/6

NEW WORLD'S LOWEST COST STEREO MAGNETIC CARTRIDGE O/P 7mV, 20 c/s-20 Kc/s. Diamond Stylus. Fits most decks. Recommended for Quality and Performance. Price 79/6 Model 940



FREE Stock List No. 1617 on request
BEST VALUE IN U.K.

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day. Visit the new Hi-Fi Store

100 STEREO SYSTEMS

LOW CASH AND CREDIT/HIP PRICES (Credit terms from £30 purchase-callers only).



HENRY'S LATEST CATALOGUE

New print. Now 350 pages. 6th Impression

- ★ **COMPONENTS, TEST GEAR**
- ★ **EQUIPMENT, MODULES**
- ★ **SPECIAL OFFERS ETC. ETC.**

Everything for the constructor. Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-

WHY NOT SEND AWAY TODAY?

NEW. 8 page SEMICONDUCTOR LIST FREE no: 36 new ranges and a few circuits.



YOU CAN SAVE 25% brand new GARRARD AND GOLDRING

(Post 7/6) COMPLETE LIST FREE ON REQUEST
 SP25mkII £10-19-6, AP75 £16-19-6, SL65B £14-19-6, SL72B £25 GL69 £22

SPECIAL Above with Sonotone 9tache diam. Add £2, with magnetic add 70/-, with Goldring G800 add £7-10-0

Also Fitted with 9tache diamond 2025TC £9-15-0, 3000LM £9-15-0, Model 50 £9-15-0
 Plinths/Covers: Standard 99/6, p.p. 4/6. De Luxe £8-10-0, p.p. 6/-, SL72B type £8-10-0, p.p. 6/-, GL69 Type £9-15-0 p.p. 6/6.


● Goldring **GL69** with plinth and cover and G800 cartridge (usually £51) £39.10.0. p.p. 12/6.



NEW 25watt and 50watt RMS SILICON AMPLIFIERS


LOOK AT THE SPECIFICATIONS !

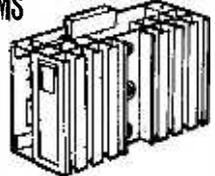- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11c/s to 100kc/s



PA25 10 Silicon Transistors Differential input, 25watts rms into 8ohms, 700mV input. Size only 5" x 3" x 2". 4-hole fixing. 12watts into 15ohms. Supplied with edge connector and harness.

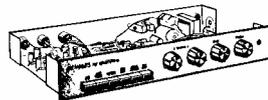PA50 12-Transistor Version, 50watt rms into 3 to 4ohms
 MU442 Power supply for one or two PA25 or one PA50
 ● PA25 £7-10-0, ● PA50 £9-10-0, ● MU442 £6



NEW SELF POWERED PREAMPLIFIERS

Mains operated slim design Preamplifiers for use with any Power Amplifier. All Silicon FET/Transistor designs. Capable of driving up to 4-PA50 Amplifiers. Push Button selection. All facilities.

MODEL FET154 STEREO PREAMPLIFIER

Inputs for mag. Pickup, Tuner/Aux., Tape in and out. Response 20 c/s to 30kc/s. Output adjustable up to 1 volt. ±20db Boost or Cutout Controls. Slim design. Size 12" x 5½" x 1½". Price £16-10-0

MODEL FET 9/4

Mono Preamplifier with built-in MIC MC XEC. Inputs for all Crystal and Ceramic cartridges, Tuner, Tape in and out. O/P and Response as FET154. Size 10½" x 4½" x 1½". Price £12-10-0

NO SOLDERING. JUST PLUG-IN CONNECTORS

ELECTRONIC ORGANS

COMPLETE RANGE OF COMPONENTS IN STOCK FOR ALL PURPOSES

- ★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT VENEERED CABINETS FOR ALL MODELS
- ★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE
- ★ KITS AVAILABLE IN SECTIONS AS REQUIRED
- ★ NEW PAX DISCOTHEQUE CENTRE AT "309"

