

# PRACTICAL WIRELESS

JUNE  
1971

20p

FREE  
COMPETITION  
INSIDE

THE  
'CARLTON'  
A MODERN SILICON SUPERHET



also:  
ELECTRONIC IGNITION SYSTEM  
SIMPLE SIGNAL GENERATOR

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64 for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.

Standard temp. 360°C at 23 watts.  
Special temps. from 250°C—410°C.

\*Additional Stock Bits (illustrated) available

### COPPER

B 38  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12  $\frac{1}{4}$ " — 4.75 mm EYELET BIT

B 58  $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

### LONG LIFE

B 42 LL  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE




Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-822 0201/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

\* Write for price list and catalogue

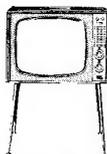

### EX RENTAL TV's

19" — £29-95

23" — £39-95

All Channels 405/625  
2 Years Guarantee.  
Free List by return.

17" Slim line TV's £11-95, 19" Slim line TV's £15-95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1-95. Daily demonstrations to personal shoppers.

### TEAK HI-FI STEREO CABINETS £14-95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1-00.

TRANSISTOR GANG CONDENSERS 30p. Miniature AM precision Tape Motors £1-95 famous German manufacturer. 200/250V. Post 20p.

Transistor Radio Cases: 25p each. Size 9 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ ". P & P. 15p.  
SPEAKERS 50p 2 $\frac{1}{2}$ " 8Ω BRAND NEW. P. & P. 5p.

TRANSISTORS Post Free  
AC 126 AF 179 OC 81  
AC 128 OC 44 OC 81D  
AF 114 OC 45  
AF 117 OC 71 15p each

### POTENTIOMETERS 23p each


Double & Switched	500 KΩ/500 KΩ	3 $\frac{1}{2}$ " shaft
Double & Switched	500 KΩ/100 KΩ	2" shaft
Double & Switched	1 MEG/100 KΩ	1 $\frac{1}{2}$ " shaft

Post. & Pack. 5p.—4 for 10p

### KNOBS 100,000 to clear (Brand New)

100 assorted Radio & T.V. knobs 50p. Postage 10p. (If you require sets 2 to 6 just ask)

### TV TUBES REBUILT GUARANTEED 2 YEARS

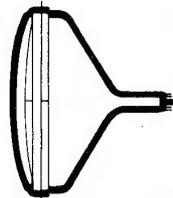

14" — £3-95, 17" & 19" — £5-95,  
21" & 23" — £6-45.

Exchanged Bowls. Carr. 53p.

## DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3 Stamp for Free List

# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

..... Please

6/71


## BRITISH NATIONAL RADIO SCHOOL

# Discosound

## P. A. AND DISCOTHEQUE EQUIPMENT

— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT

AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.

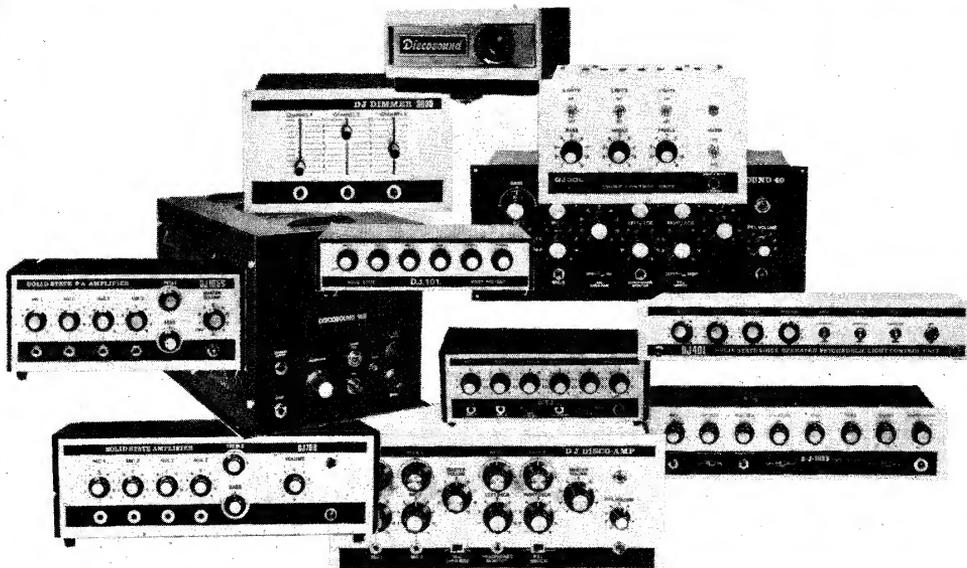

### D.J. 102 Discotheque Mixer Pre-Amplifier

4 inputs each with its own volume control plus master volume control, PFL monitoring and mic override switches. Size 10 $\frac{1}{2}$ " x 4" x 4".

Suggested Retail Price £25-00

### D.J. 105S P.A. Amplifier

4 channel mixing facilities each with separate inputs and volume controls. 30 watts r.m.s. power output A.C. Mains 200/250v A.C. Size 11 $\frac{1}{2}$ " x 5" x 6".

Suggested Retail Price £31-00

### D.J. 70S Integrated Mixer Amplifier

Power output 70 watts r.m.s. 4 channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls. Size 15 $\frac{1}{2}$ " x 5" x 6".

Suggested Retail Price £63-00

### D.J. Disco-Amp

Designed specifically for use with discotheques. Power output 100 watts r.m.s. Two mike inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features.

Front panel size 16 $\frac{1}{2}$ " x 7".  
Suggested Retail Price £85-00

### D.J. 101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. By battery operation. Size 10 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ ".

Suggested Retail Price £14-00

### Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self powered and ideal for use with Discosound 100 Power Amplifier (is capable of running 10 of these power amplifiers—total 1000 watts).

Front panel size 10 $\frac{1}{2}$ " x 7".  
Suggested Retail Price £40-00

### Discosound 100 Power Amplifier

100 watts r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20-20,000 Hz  $\pm$  5db. Distortion less than 1% at 70 watts r.m.s.  $\pm$  1db. Size 10 $\frac{1}{2}$ " x 8" x 7".

Suggested Retail Price £49-50

### D.J. 103S Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphone and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities.

Front panel size 16 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ ".  
Suggested Retail Price £49-50

### D.J. 30L Psychedelic Light Control Unit

3 channel light unit enabling bass, middle and treble frequencies from the amplifier to be operated individually. Handles 1000 watts per channel.

Front panel size 10" x 6".  
Suggested Retail Price £37-50

### D.J. 40L Sound Operated 3 Channel Light Unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source.

Handles 1000 watts per channel.  
Suggested Retail Price £56-25

### D.J. DIMMER 3000

3 channel light dimmer unit offered in two versions: Dimmer 3000—a straight three channel dimmer unit with mains input and three light outputs. Dimmer 3000S—for use in conjunction with D.J.30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size 10" x 6".

Suggested Retail Price £32-50

### Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment.

Size 7 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ ".  
Suggested Retail Price £50-00

A range of complete Discosound systems with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest  
Discotheque Centre — Demonstrations given at any time.


DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01-254 5779

HENRY'S RADIO LTD.,

309 Edgware Road, London W.2. Tel: 01-723 6963
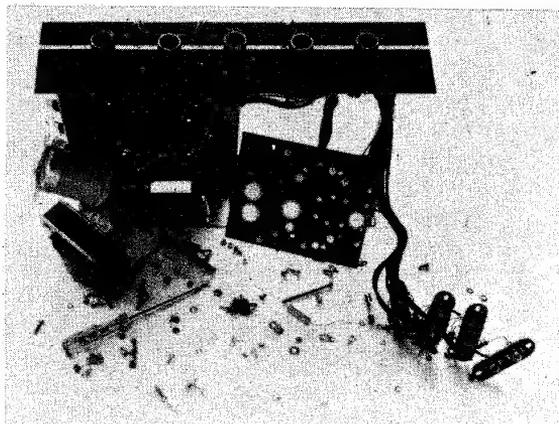
# The first Eagle TSA. 151 stereo amplifier that Gerry Adler got his hands on he broke



The TSA 151. The largest of the Eagle new generation Amplifiers. It uses a completely new solid-state silicon output device to provide a powerful clean 15 watts RMS per channel. It gives an incredible signal to noise ratio. In its attractive all-wood cabinet it even looks good.

And yet Gerry Adler broke it. Quite deliberately. Because Gerry Adler is like that. Just plain destructive. He'll take a piece of equipment and mistreat it. Until he breaks it. Then he'll fix it. Improve it and break it again. And again. And again.

And if it doesn't take more punishment than anything else on the market it doesn't get to carry the Eagle name.

Gerry Adler has a simple business philosophy. Build a better piece of equipment than anyone else on the market, put a good price on it, and you'll sell all you can make.

It's a great reason for buying the TSA 151 or its matching stereo tuner TST 152.

**Eagle International**

we don't stand still

Write or phone Precision Centre,  
Heather Park Drive, Wembley, Middx.  
HAO 1SU Tel: 01-903 0144 for a copy  
of our new catalogue.

# R+TV

RADIO & TV COMPONENTS (Acton) Ltd.

21c HIGH STREET, ACTON, LONDON, W.3. 6NG

323 EDGWARE ROAD, LONDON, W.2.


ALL MAIL ORDERS TO OUR ACTON BRANCH

Terms C.W.O.

All enquires S.A.E.
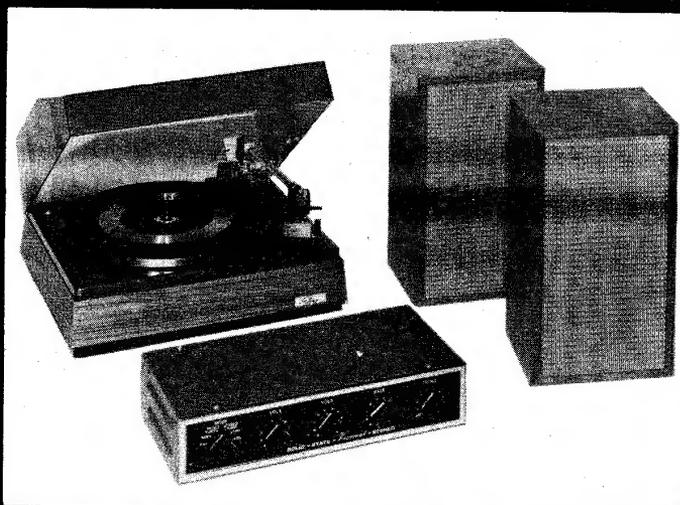
## Complete Stereo System £43

WITH VISCOUNT F.E.T. FIELD EFFECT TRANSISTORS AMPLIFIER



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 Mk III (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½in x 10½in x 6½in, the Duo type 2 speakers are teak finished with matching Vynair grills. They incorporate a 3 ohm, 13in x 8in drive unit and Parasitic tweeter. Max. power handling 10 watts. Price £13.50 per pair plus p. & p. £1.50.

Complete stereo system £43 plus £2.50 p. & p. or with Mk II Amplifier and Magnetic Cartridge £48 & £2.50 p. & p.

*The Viscount* F.E.T. Mk I £14.25 + 75p. p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Specification—Output per channel 10 watts r.m.s. into 3 ohms Frequency bandwidth 20 Hz to 20 kHz ± 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½in. 6in. 2½in. in simulated teak case. BUILT & TESTED.

MkII (MAG P.U.) £15.75 plus 75p. p. & p.

Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1 kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).


## The £25 Stereo system

The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

**SPECIFICATION—**  
R.M.S. power output 3 watts per channel into 10 ohms speakers.

**INPUT SENSITIVITY.** Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

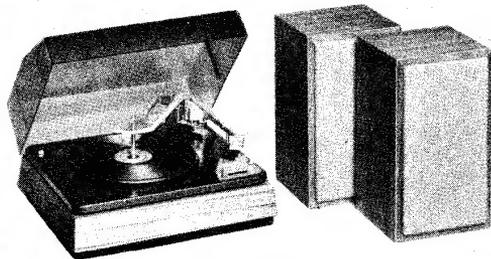**CONTROLS:** 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.




**TONE CONTROL** Treble lift and cut Separate on off switch. A preset balance control.

Duetto integrated transistor stereo Amp.	£9.50	50p
Garrard Changer from	£7.97	50p
Cover and teak finish plinth	£4.75	50p
Duo Type 1 speakers (see opp. page)	£4.20	50p
The above items purchased together.	£25.00	£2.00

# SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

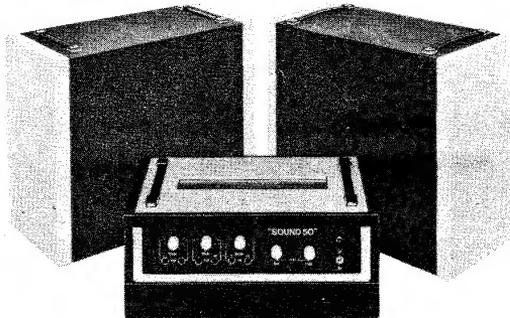

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

**Output Power:** 45 watts R.M.S. (Sine wave drive). Frequency response: —3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. **Speaker Impedance:** 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power. **SPEAKERS!** Size 20" × 20" × 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50** Plus £4 P. & P.

Sound 50 amp and 2 speakers or available separately.

Amplifier £28.50 plus £1.50 P. & P.

Speakers £12.50 each plus £1.75 P. & P.

# LIQUIDATED STOCK DANSETTE TOURISTE MK3 CAR RADIO

## ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold completely built for £15.4.6 (£15.23) Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

See top of previous page for address



## SET OF PARTS

**£6.30**

plus P. & P. 50p.


Circuit diagram 13p. Free with parts

Speaker, baffle and fixing kit

£1.25 extra plus 25p. p. & p.

Postage free when ordered with parts.
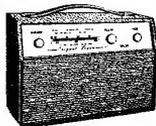
## The ELEGANT SEVEN Mk. III (350m W Output)




7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

**MAINS POWER PACK KIT:** 75p extra.

Price **£5.25** plus 50p. P. & P.

Circuit 13p **FREE WITH PARTS.**

## The DORSET (600m W Output)

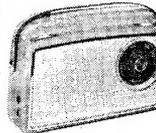

7-transistor fully tunable M.W.—L.W. superhet portable—with baby alarm facility. Set of parts. The latest modulsed and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.


**MAINS POWER PACK KIT:** 75p extra.

Price **£5.25**

plus 50p P. & P.

Circuit 13p

**FREE WITH PARTS**

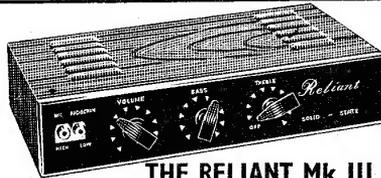

## THE RELIANT Mk III SOLID-STATE GENERAL PURPOSE AMPLIFIER

in simulated teak case **£7.25** plus P. & P. 50p

### SPECIFICATIONS

Output 10 watts. Output impedance—3 to 4 ohms. Inputs 1. -xtal mic 10mV Tone Controls—Treble control range ± 12dB at 10KHz. 2. -gram/radio 250mV. Bass control range ± 13dB at 100Hz. Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than —60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10½in. x 4½in. x 2½in. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Built and tested.

## THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer. It is ideal for wall or shelf mounting either upright or horizontally.

### Type 1 SPECIFICATION —

Impedance 8 or 10 ohms (please state requirement). It incorporates high flux 7in. x 3½in. speaker and 2½in. speaker. Teak finish 11½in. x 6in. x 5½in. £4.20 each. 50p P. & P.

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED

# LEWIS AUDIO

## ECONOMY HI-FI SYSTEMS




Lewis Audio Systems comprise a range of amplifier, speaker, plinth and motor units which can be combined to provide a variety of arrangements to suit personal requirements of size and price. The amplifier delivers power up to 6 watts per channel RMS into 15 ohms for each channel, and each of the three loudspeakers uses a triple loudspeaker unit arrangement. Leaflet of this attractive range free on request.

- The SA. 55 Amplifier
- Compact SC. 18-15 MkII System, illustrated above.
- The plinth units.
- The loudspeakers.
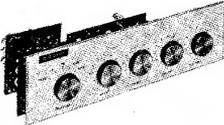
## MARTIN AUDIOKITS

**MARTIN AUDIOKITS** were first to make modular unit construction available to the hi-fi enthusiast keen to save by building his own assembly. **AUDIOKITS** were first to feature "add-on-ability" by which a simple system could be expanded to high performance stereo equipment by the addition of easily added on units. Many who built with **MARTIN AUDIOKITS** years ago continue to enjoy unsurpassed quality and reliability from them to this day. **NOW YOU CAN BUY AUDIOKITS AGAIN** to allow you to build a high fidelity system to your personal choice and which will satisfy completely on performance, simplicity of assembly, robustness and reliability. These units are beautifully engineered and solidly built for a lifetime of trouble-free service. Each unit is complete in itself and requires nothing added; each is tested and checked before leaving factory.



- Robust construction.
- Greater reliability.
- Simple to fit up.
- Money saving, too.

1478E Five stage matched input selector unit; controls and pre-amp; power amp. (10 watts RMS into 15 ohms) power supply; front escutcheon plate mono) Total price £17-50

1478SE Similar to above but for stereo. Total price £29-95

9748SE Stereo assembly for use with high grade ceramic and low power mag. pick-ups. Total price £32-95

All units are obtainable separately. State pick-up when ordering.

Leaflets on request from the makers:  
**LOUIS & LEWIS (ELECTRONICS) LTD.**, 154-155 High Street, Brentford, Middlesex. Phone 01-560 1161

### LOUIS & LEWIS (ELECTRONICS) LTD

Please send details of MARTIN AUDIOKITS .....

LEWIS AUDIO SYSTEMS .....

NAME .....

ADDRESS .....

PW6 .....




## RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.

### LTA 15 WATT AMPLIFIER

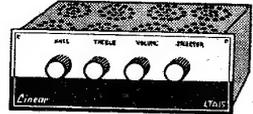**HIGH FIDELITY OUTPUT SWITCHED INPUTS FOR GRAM, 'MIKE', TAPE, AND RADIO**

Frequency Response 10-40,000 cps - 3dB. Bass Control +17dB to -16dB at 40cps. Treble Control: 17dB to -14dB at 14Kcs. Hum and Noise -80dB. Harmonic Distortion 0.2% at rated output. Output for 3-8-15 ohm Loudspeakers.



Recommended **£19**  
 Retail Price  
 Size 9 1/4 x 3 1/4 x 5 1/2 in. approx.

### PTA30 HI-FI PUBLIC ADDRESS AMPLIFIER


**A SUCCESSOR TO OUR POPULAR CONCHORD 30 WATT UNIT**

Input Sensitivity 2 mv (max.)

Output 30 watts.

Output Sockets for Loudspeaker or combination of Speakers with total impedance between 3 ohms and 30 ohms. Three individually controlled inputs for mixing purposes. Housed in fully enclosed stove enamelled steel case. Controls Vol. (1) Vol. (2) Vol. (3) with mains switch, Treble 'lift' and 'cut'. Bass 'lift' and 'cut'.

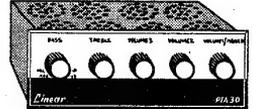Recommended **£24**  
 Retail Price  
 Size 12 x 3 1/4 x 6 in. approx.



**AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS. SUITABLE FOR ANY KIND OF 'MIKE' AND INSTRUMENT PICK-UP. ALSO FOR RADIO, TAPE OR GRAM.**

Please send a stamped addressed envelope for full descriptive details of above units, also TUNER (AMPLIFIERS STEREO and MONO).

If required an attractive wood cabinet with veneer finish can be supplied for any model. Prices from **£3.50**

AVAILABLE FROM YOUR LOCAL HI-FI DEALER  
 Wholesale and Retail enquiries to:

**LINEAR PRODUCTS LTD,**  
 Electron Works, Armley, Leeds

## When in LUTON, BEDS, you must visit the . . .

### SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.  
 Closed all day Wednesday.

**SURPLECTRONICS**  
 216 LEAGRAVE ROAD, LUTON, BEDS

## BAKER I2in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts

Bass Resonance 45 c.p.s.

Voice Density 12,000 gauss

Useful response 3 or 8 or 15 ohm models


45-13,000 c.p.s.

Nett weight 5 lbs.

GUITAR MODEL "GROUP 25" 25 watt rating £7

Latest catalogue 5p with enclosure plans.

**£7**

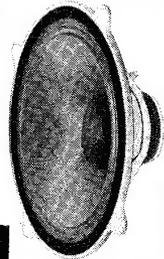

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

## NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. 4 section 24" retractable chrome plated Telescopic aerial for Short Waves for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Parts Price List and Easy Build Plans 25p (FREE with parts).

**Total building costs £6.98**


Overseas P. & P. 90p

Post, packing and insurance 41p.


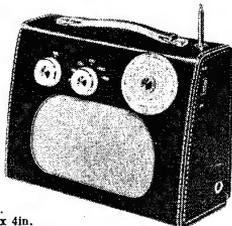
## roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.



**Total building costs £5.98**


Overseas P. & P. 90p

Post, packing and insurance 41p.
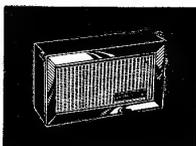
## pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—6 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



**Total building costs £2.23**


Overseas P. & P. 55p

Post, packing and insurance 31p.
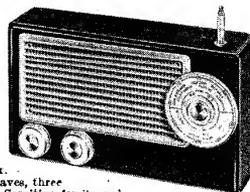
## NEW! trans eight

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



**Total building costs £4.48**

Overseas P. & P. 70p

Post, packing and insurance 31p.

## transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



**Total building costs £2.38**

Overseas P. & P. 55p


Post, packing and insurance 22p.

## IMPROVED MODEL!
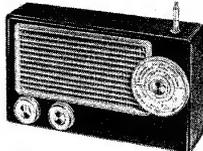
### roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 1½ x 2½in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



**Total building costs £3.98**

Overseas P. & P. 70p

Post, packing and insurance 26p.

★ Callers side entrance Barratts Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- |               |                          |              |                          |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER EIGHT  | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | TRANS EIGHT  | <input type="checkbox"/> |
| POCKET FIVE   | <input type="checkbox"/> | ROAMER SIX   | <input type="checkbox"/> |

Parts price list and plans for .....

Name .....

Address .....

W.30

VALVES		6BA6		6BE6		6CH6		6CG6		6CW4		6D6		6E6		6F6		6G6		6H6		6J6		6K6		6L6		6M6		6N6		6P6		6Q6		6R6		6S6		6T6		6U6		6V6		6W6		6X6		6Y6		6Z6	
1A7GT	40	6B6	25	6C6	25	6D6	25	6E6	25	6F6	25	6G6	25	6H6	25	6I6	25	6J6	25	6K6	25	6L6	25	6M6	25	6N6	25	6O6	25	6P6	25	6Q6	25	6R6	25	6S6	25	6T6	25	6U6	25	6V6	25	6W6	25	6X6	25	6Y6	25	6Z6	25		


### Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V. 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3.20 plus 10p post and packing. Kit Form: £2.70 plus 10p post and packing. Please send C.W.O. to:-

**DEXTER & COMPANY**  
 1 ULVER HOUSE, 19, KING STREET,  
 CHESTER CH1 2AH Tel: 0244-25883,  
 As supplied to H.M. Government Departments,  
 Hospitals, Local Authorities, etc.

### The Unique MULTI-MINI TWIN-VICE

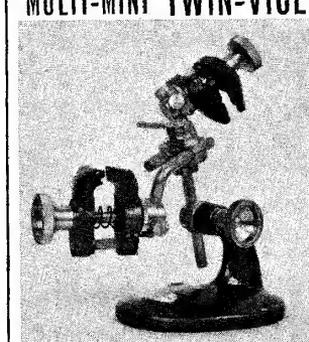


An extra "Pair of hands" for those tricky jobs

**ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.**

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

**TWIN VICE: £5.90 (24p P & P)**  
**ALSO AVAILABLE**  
**SINGLE VICE: £3.37 (20p P & P)**  
**COVENTRY MOVEMENT CO LTD.**  
 Dept. PW1  
 BURNSALL ROAD, COVENTRY CV5 6BU  
 STD 0203-74363

### 4-STATION INTERCOM

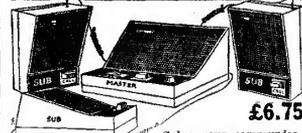

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. £0.40.

**£6.75**

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.95 P. & P. £0.50.

### INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery £0.12. P. & P. £0.25.

### Transistor TELEPHONE AMPLIFIER



Why not boost business efficiency. Take down long telephone messages or converse without holding the handset. A useful office aid. On off switch. Volume Control. Battery £0.12 extra. P. & P. £0.20. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (P.W.5)**  
 169 KENSINGTON HIGH STREET, LONDON, W.8.

ARMSTRONG • TELETON • CONNOISSEUR • KOSS • APOLLO • SHURE • CELESTION

**GARRARD** **PRICES SLASHED! 55%** **GOLDRING**  
BY UP TO 0/ P. & P.

SME • LOWTHER • SINCLAIR • FERROGRAPH • STE-MA • THORENS • BRYAN • PHILIPS • KEF ETC

**WHY PAY MORE? ALL GOODS ARE BRAND NEW & FULLY GUARANTEED FOR 12 MONTHS**



**SUPERB PLYNTHS AND COVERS as illustrated (£3.50 Plus 50p P. & P.)**

Suitable for Garrard AT60, SP25, 2000, 2500, 3000, 3500, 5100, 2025, 1025, SL65B and B.S.R. McDonald range. Superbly finished plinth, ready cut for use (fully assembled). Complete with tinted perspex cover. This unit is finished in Teak polish and will blend in any home. Please state deck when ordering.

**SUPERIOR PLYNTHS AND COVERS for Garrard AP75, AP76, SL72B, SL75B and SL95B (Recommended list price £10-00). (£4-95 Plus 60p P & P)**

**COMPLETE GARRARD SP25 MKIII GOLDRING G800H SUPERB PLYNTH AND COVER £17.50 p.p. £1**

**VISIT OUR 3 STOREY WAREHOUSE PACKED WITH HI-FI & STEREO EQUIPMENT. 1000's OF ITEMS ALWAYS AVAILABLE TO SELECT FROM.**

**2 SHOWROOMS DEVOTED TO DEMONSTRATING SPECIALLY SELECTED SYSTEMS**

**TURNTABLES p.p. 60p**

GARRARD 5100 with Cartridge	£6.75
GARRARD 2025 TC with Sonotone	£27.50
9TAHC Diamond Cart	£8.50
GARRARD 3000 with Sonotone	£9.50
9TAHC Diamond Cart	£10.97
GARRARD AT70MKII	£10.97
GARRARD SP25 MK3	£12.75
GARRARD SL65B	£18.75
GARRARD AP75	£27.50
GARRARD SL72B	£27.50
GARRARD SL75B	£27.50
GARRARD 401	£34.00
GARRARD SL95B	£61.00
THORENS TD125	£61.00

**PICK UP ARMS pp. 35p**

SME 3009/SA	£25.50
SME 30012/S2	£27.50
GOLDRING Lenco L75	£9.99
GOLDRING Lenco L69	£6.75

**STEREO AMPLIFIERS p.p. 50p**

H.L. SA707 with Scratch Filter	£19.00
METRO SOUND ST20	£26.00
AMSTRAD 8000	£20.97
TELETON SA 0206	£18.97
SINCLAIR 3000	£34.00
SINCLAIR 2000	£23.50
SINCLAIR PRO 60/2 Z30/P25	£15.97
QUAD 303 & 33	£27.00
ARMSTRONG 521 (Teak cased)	£43.50
SINCLAIR A.F.U.	£4.50

SAN SUYI DUETTE now in stock special prices on application.

**TUNER AMPLIFIERS pp. 75p**

TELETON MX990 WITH SPKS	£48.50
TELETON R8000 WITH SPKS	£37.00
TELETON CR10T WITH SPKS	£29.00
TELETON TFS50	£53.50
TELETON 7AT1	£81.00
TELETON CR55	£90.00
TELETON 10AT1	£105.00
TELETON 7AT20	£78.00
PHILIPS RH781	£54.00
ARMSTRONG M8 Decoder	£7.00
ARMSTRONG 525	£74.00
ARMSTRONG 526	£82.50

**TUNERS p.p. 50p**

TELETON GT101	£32.97
TELETON STQ204X	£38.97
SINCLAIR 2000	£19.00
SINCLAIR PRO 60	£20.50
ARMSTRONG 523 AM/FM	£42.00
ARMSTRONG 524	£32.00
ARMSTRONG M8 Decoder	£7.00

SAN SUYI DUETTE now in stock

**PERSONAL CALLERS WELCOME.** We are always available to advise on the best system to suit your need and pocket.

**OUR OWN CAR PARK (at rear)**  
 You have no parking problems when you pay us a visit.

**UNBEATABLE VALUE**  
 The largest and best quality range of stock at **LOWEST POSSIBLE PRICES** is usually available.

The prices shown are current at the time of going to press but are liable to alteration. They supercede any previous offer.

Send Postal Orders, Money Orders, Cheques, etc. to

For information only send stamped addressed envelope

**AUDIO SUPPLIES**

**AUDIO SUPPLIES (PW6) 50 STAMFORD HILL LONDON, N.16 (The A.10)**

Open 9.30 a.m. - 6 p.m. Monday to Saturdays. (Fridays to 8.30 p.m.) EASY TO FIND. Tel: 01-806 3611  
 50 yards from (B.R.) Stoke Newington Station. 67, 146, 247, 76, 243 Buses pass our door.

Personal callers please note that cheques are only accepted if accompanied by a bank cheque card. (NOT BARCLAY CARDS)

**CARTRIDGES (p. & p. 12p.)**

GOLDRING G850	£4.20
GOLDRING G800	£6.99
GOLDRING G800E	£11.00
GOLDRING G800 super E	£16.00
SONOTONE 9TAHC	£1.75
SHURE M3d	£4.95
SHURE M445/7/c	£7.20
SHURE M55	£9.20
SHURE M75E	£15.00
SHURE M44E	£8.50

**SCOOP BUY SMC-101 MOVING MAGNET STEREO CARTRIDGE.**  
 PRICE: £3-25.  
**MC1-3 HIGH FIDELITY STEREO MOVING MAGNET CARTRIDGE.**  
 PRICE: £8-00.  
 For complete specification on the above see our March Issue, Page 889.

**SPECIAL OFFERS SPEAKERS**  
 Wharfedale Example: wharfedale unit 3 speaker kit £10-00 — Danton — Triton — Melton — STE — MA  
 Full range in stock at UP TO 40% DISCOUNT FOR PERSONAL CALLERS ONLY.

**HEADPHONES**  
 For 1 month only we offer 25% OFF list price of all KOSS models.  
 Example: PRO4A. List price £28-00.  
**OUR PRICE £21-00 plus 37p p. & p.**

**SAVE OVER 30% ON A COMPLETE SYSTEM**

GARRARD SP 25 MK III	List Price £16-45
PLYNTH AND COVER	£6-00
G800H CARTRIDGE	£13-00
HL AUDIO SA 707	£27-00
2 APOLLO 8 SPEAKERS	£27-50
	£89-95

**OUR PRICE £56-94 + £2-50p. p. & p.**

**WHY PAY MORE—APOLLO 3-WAY SPEAKER SYSTEMS**

The Systems are housed in handsome Slim-Line Cabinets of Modern Design, finished in Polished Teak with Padded Front Panel covered in I.C.I. Vynair Grille.

The **APOLLO 3-WAY SPEAKER SYSTEMS** are designed and built on the Infinite Baffle Principle and are completely Airtight and fully padded to damp out any Panel Resonance. Polished on all sides they can be used either vertically or horizontally and are ideal for Shelf or Wall Mounting.

Crossover Network. Specification: Impedance 4-8 ohms (15-16 ohms to order). Power Handling 10 watts RMS (20 watts peak). Frequency Range 50 Hz to 18,000 Hz. Size 21 x 11½ x 9½. Finish Polished Teak.  
**OUR PRICE £13.47 each (65p. p. & p.).**

**APOLLO-15 3-WAY SPEAKER SYSTEM**  
 Impedance 8 ohms. Power Handling 15 watts. RMS (30 watts peak). Frequency Range: 35 to 18,000Hz. Colour: Teak. Size 21 x 15 x 7½ in.  
**PRICE £18-50 each (p. & p. £1-00).**

**APOLLO-8 3-WAY SPEAKER SYSTEM**  
 As above but 7 watts RMS (14 watts peak). F.R. 55 to 18,000 Hz. Size 20 x 12 x 8 in.  
**£10-12 each (50p p. & p.).**


The **APOLLO-16 3-WAY SPEAKER SYSTEM** employs a specially designed 10in. Bass Unit which has a high efficiency Anisotropic Ferrite Magnet and two 4in. Treble Units and LC

As above but 5 watts RMS (10 watts peak). F.R. 75 to 18,000 Hz. Size 14½ x 8 x 6 in.  
**PRICE £6.97 each (37½p p. & p.).**

# COMET

## HI-FI DISCOUNT WAREHOUSES

DRIVE-IN CAR PARK

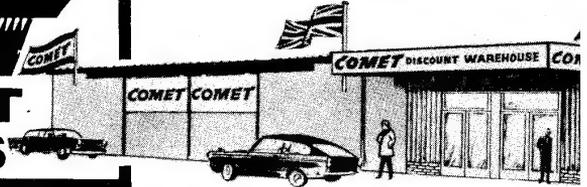

Rec. Retail Price Comet Price

### STEREO AMPLIFIERS

ALBA UA 700	34-50	26-00
ARMSTRONG 521	56-00	44-30
*DULCI 207	26-00	17-50
DULCI 207M	32-00	22-25
FERROGRAPH F307	59-00	48-00
GOODMANS Maxamp	54-00	38-00
LEAK Stereo 30 Plus	58-50	44-75
LEAK Stereo 30 Plus, in teak case	62-10	49-50
LEAK Stereo 70	69-00	55-00
LEAK Stereo 70, in teak case	75-00	59-50
*LINEAR LT 65	21-00	17-00
METRO SOUND HT20	36-00	28-00
PHILIPS RH 591	79-00	61-50
PHILIPS RH 590	52-00	39-50
PHILIPS RH 580	29-00	23-00
PIONEER SA500	62-10	43-00
PIONEER SA700	98-00	70-00
PIONEER SA900	134-10	97-00
PIONEER Reverberation	45-50	33-00
ROGERS Ravensbourne	59-50	47-00
ROGERS Ravensbourne (cased)	64-00	50-00
ROGERS Ravensbrook Mk. II	47-50	38-00
ROGERS Ravensbrook (cased)	52-50	42-00
Mk. II	35-00	26-00
SINCLAIR 2000	23-90	17-00
SINCLAIR PROJECT 60/2 X 230/ PZ1	34-86	25-50
SINCLAIR PROJECT 60/2 X 250/ PZ2/trans.	5-95	4-95
SINCLAIR AFU	61-95	48-00
SINCLAIR Neoteric	45-00	36-00
SINCLAIR 3000	29-00	20-00
TELETON SAQ 206 (new release)	185-00	139-00
VOLTEX 100w. Stereo Discotheque, 8 electronically mixed inputs		

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

### TUNERS

*ARMSTRONG 523 AM/FM	53-76	45-00
*ARMSTRONG 524 FM	41-89	35-00
ARMSTRONG M8 Decoder	9-50	8-00
*DULCI FMT 7 FM	26-00	22-00
DULCI FMT 7 Stereo	31-80	25-00
GOODMANS Stereomax	82-52	49-95
LEAK Stereofetic Chassis	66-50	52-00
LEAK Stereofetic in teak case	75-50	59-00
PHILIPS RH 690	47-00	39-00
PHILIPS RH 691	89-00	75-50
PIONEER TX500 AM/FM	77-94	64-00
PIONEER TX900 AM/FM	153-69	125-00
ROGERS Ravensbrook chassis	81-80	65-00
ROGERS Ravensbrook	45-01	40-00
ROGERS Ravensbrook (cased)	51-26	43-00
TELETON GT 101	45-50	34-00
TELETON 201X FM	38-00	30-00


All above Tuners are complete with MPX Stereo Decoder except where starred.

### TUNER/AMPLIFIERS

AKAI AA 8500	229-00	181-00
AKAI 6600	142-53	112-00
ARENA R500	82-00	67-00
ARENA 2400	90-30	72-00
ARENA 2700	105-00	85-00
ARENA T1500F	72-45	60-00
ARENA T8000	303-45	258-00
ARMSTRONG M8 Decoder	9-50	8-00
ARMSTRONG 525	91-89	77-00
ARMSTRONG 526	104-71	87-00
GOODMANS Module 80, 35w. R.M.S.	95-00	75-00
GOODMANS 3000	77-73	53-00
MIDLAND 19/542	49-56	37-50
PHILIPS RH 790	139-00	112-00
PIONEER SX770 AM/FM	150-43	126-00
PIONEER SX990 AM/FM	194-74	150-00
PIONEER 440	111-10	89-00
*TELETON F2000	51-80	32-00
TELETON T.A.T. 20	105-00	80-00
TELETON 10A/T1 150w. RMS	160-00	109-00
TELETON TF550	82-50	56-00
TELETON TFS 90LA MW/LW/VHF	87-90	64-90
*TELETON R3000 with Speakers	63-25	50-00
TELETON CR65	120-00	95-00
WHARFEDALE 100.1	149-00	119-00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

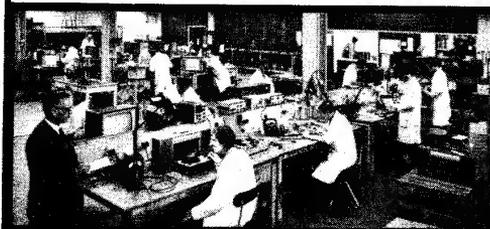All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.



### COMET for after-sales service THROUGHOUT THE U.K.

Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, and Bridlington

Rec. Retail Price Comet Price

### PICKUP ARMS

GOLDRING Lenco L75	12-33	10-50
GOLDRING Lenco L69	9-29	7-00
SME 3009 with S2 Shell	34-47	28-00
SME 3012 with S2 Shell	35-71	31-50

### CARTRIDGES

GOLDRING 800	13-00	7-50
GOLDRING 800H	10-69	8-00
GOLDRING 800E	18-88	12-25
GOLDRING 800 Super E	26-01	20-00
*GOLDRING CS90 Stereo	5-20	4-25
*GOLDRING CS91/E	7-81	6-25
GOLDRING G850	6-50	5-25
EMPIRE 1002E/X	63-00	52-50
EMPIRE 999VE/X	44-50	36-00
EMPIRE 999TE/X	27-80	22-50
EMPIRE 999SE/X	21-00	17-50
EMPIRE 999E/X	16-50	13-00
EMPIRE 999/X	11-50	9-25
EMPIRE 909E/X	12-85	10-25
EMPIRE 909/X	9-00	7-50
EMPIRE 909E/X	9-75	8-00
ORBIT Magnetic NM 22	Special Price 2-90	
PICKERING V15 AC2	8-40	7-00
ORTOFON SL19E	29-65	23-75
ORTOFON 2X15K Transformer	7-00	5-25
SHURE M3DM	7-41	5-25
SHURE M31E	12-05	9-00
SHURE M32E	11-10	8-75
SHURE M32E-X	10-20	8-50
SHURE M44-5	11-10	8-50
SHURE M44-7	10-20	8-00
SHURE M44C	10-20	8-00
SHURE M44E	12-05	9-50
SHURE M55E	12-95	10-25
SHURE M75G	17-80	14-00
SHURE M75-5	16-70	13-00
SHURE M75EJ	18-45	16-00
SHURE M75E-95G	23-15	18-00
SHURE M75E	21-30	16-00
SHURE M75E/D19	23-15	19-00
SHURE V15-11	40-76	30-00
SHURE V15-11-7	38-90	29-00

Starred cartridges above are ceramic. All others are magnetic.

### TURNABLES

GARRARD AP76 turntable, complete with Goldring G.600 Cartridge base and cover.		
Special Price 30-95		
GARRARD SP25, Mk III fully wired with Goldring G800 Magnetic Cartridge. Complete with base, plinth and cover.		
Special Price 21-98		
GARRARD 2025 fully wired with Sonotone 9TA HC Cartridge complete with base and cover		
Special Price 15-50		
GOLDRING 705/P turntable, complete with Goldring G850 cartridge, base and cover	25-00	15-95
DUAL 1219 transcription	60-40	50-00
DUAL 1205 transcription	42-82	35-00
GARRARD SP25 Mk III	16-45	11-90
GARRARD SL65 B	21-25	15-90
GARRARD SL75 B	39-20	29-50
GARRARD SL85 B	50-01	38-50
GARRARD 401	38-07	29-50
GARRARD SL72 B	33-11	27-90
GARRARD 3500, with GKS Cartridge	17-23	12-90
Base and Cover to fit GARRARD SP25, SL65, SL85B and 3500	Special Price 4-00	
GARRARD 40B	13-84	10-97
GARRARD AP 76	29-01	21-50
GOLDRING GL69 Mk. II	26-63	22-50

Rec. Retail Price Comet Price


GOLDRING GL69 P Mk. II	35-14	29-50
GOLDRING GL75	38-41	33-90
GOLDRING GL75 P	46-94	41-90
GOLDRING Covers for 69P and 75P	4-21	3-50
GOLDRING C99-plinth and cover for 69P	11-45	9-90
GOLDRING G99	26-00	23-90
GOODMANS 3025	37-74	26-90
McDONALD MP 60	15-75	12-95
McDONALD 910	20-00	16-50
Base and Cover for McDONALD MP 60 and 610	Special Price 4-50	
PHILIPS 225	20-00	17-00
PHILIPS GA 146	31-50	25-00
PHILIPS 202 Electronic	69-00	57-50
PIONEER PL 12A with base & cover	49-93	37-95
THORENS TX 25 cover	8-85	7-00
THORENS TD125	79-04	64-95
THORENS TD150A Mk. II	46-16	35-95
THORENS TD125AB	120-20	100-00
THORENS TD150AB Mk. II	49-96	42-95
THORENS TX11 Cover	4-43	3-95

### SPEAKERS

ARENA HT 16	13-00	10-95
B & W Model 710	139-50	115-00
B & W DM3	63-00	53-00
B & W DM1	32-00	25-50
CELESTION Ditton 120	24-00	18-00
CELESTION Ditton 15	32-00	25-50
CELESTION Ditton 25	65-00	52-00
GOODMANS Miniater	25-00	21-20
GOODMANS Magister	62-50	49-50
GOODMANS Maxim	20-39	16-75
GOODMANS Mezzo 3	34-00	26-50
GOODMANS Magnum K2	44-00	33-00
KFF Cresta	22-17	18-00
KELETRON KN 500 4 speaker system (pair)	23-00	17-95
KELETRON KN 700 4 speaker system (pair)	27-50	21-95
KELETRON KN 1000 4 speaker system	19-25	14-95
KELETRON KN 1500 4 speaker system	24-75	19-95
KELETRON KN 2000 4 speaker system	28-75	21-95
LEAK 200	24-95	18-90
LEAK 300	32-50	23-95
LEAK 600	49-50	36-90
LOWTHER Acousta (with PM6)	45-50	38-50
LOWTHER Acousta (with PM7)	53-00	46-00
LOWTHER Ideal Baffle	35-50	30-00
METRO SOUND HFS 20 (pair)	39-00	33-95
METRO SOUND HFS 10 (pair)	27-44	22-95
PHILIPS RH481	11-00	9-25
PHILIPS RH482	18-00	15-00
SINCLAIR Q18	8-98	8-00
STE-MA 275 3 speaker system	23-10	15-00
WHARFEDALE Speakers		
Airedale	69-50	56-00
Denton	19-95	15-90
Super Linton	24-95	20-50
Melton	32-50	25-50
Dovedale 3	42-50	32-50
Rosedale	65-00	52-50
Triton (pair)	59-90	49-90
Unit 3 Speaker Kit	13-00	10-50
Unit 4 Speaker Kit	18-00	14-25
Unit 5 Speaker Kit	26-00	20-50

### CHASSIS SPEAKERS

GOODMANS Axiote 8	8-10	6-50
GOODMANS Twinaxiote 8	9-17	7-50
GOODMANS Axiom 10	9-16	7-75
GOODMANS Axiom 80	28-31	21-75
GOODMANS Axiom 201	14-45	10-95

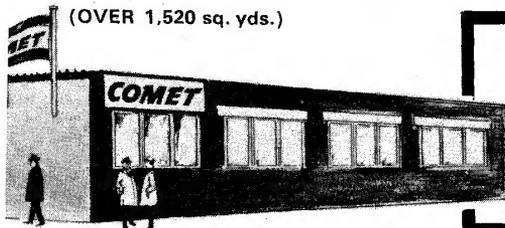

(OVER 1,520 sq. yds.)

# OVER 1000 ITEMS ALWAYS IN STOCK

ALL FULLY GUARANTEED -  
WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

	Rec. Retail Price	Comet Price
GOODMANS Axiom 301.....	20-70	15-75
GOODMANS Audiom 8P.....	5-55	4-25
GOODMANS Audiom 10P.....	6-05	3-60
GOODMANS Audiom 51.....	12-05	7-95
GOODMANS Audiom 61.....	18-95	14-98
GOODMANS 12P.....	12-37	10-00
GOODMANS 15P.....	20-00	16-97
GOODMANS Audiom 18P.....	34-00	26-97
GOODMANS Twin Axiom 10.....	10-23	8-25
GOODMANS ARU 172.....	4-50	3-50
GOODMANS Trebox 100.....	8-60	6-00
GOODMANS Trebox 5K/20XL.....	9-70	7-50
GOODMANS Midax.....	12-95	9-00
GOODMANS Attenuator.....	3-55	2-50
GOODMANS Crossover Networks XO 950/3000.....	9-75	7-25
GOODMANS Crossover Networks 950.....	7-40	5-75
GOODMANS Crossover Networks XO/5000.....	2-65	2-00
WHARFEDALE 8 in. Bronze/RS/DD.....	5-00	4-00
WHARFEDALE Super 8/RS/DD.....	8-50	7-00
WHARFEDALE Super 10/RS/DD.....	14-00	11-50
WHARFEDALE WMT 1 Matching Transformer.....	0-84	0-75

### HI-FI STEREO SYSTEMS (complete)

ARENA MR15.....	143-00	115-95
ALBA UAS52.....	4-00	35-95
ALBA UA662.....	62-97	47-95
Bush System 749/746/764.....	102-65	82-65
DECCA Sound 603.....	72-50	59-95
DECCA Sound 604.....	140-45	92-95
DECCA Sound 1203.....	97-50	79-95
DECCALIAN 5, complete with stand.....	65-59	52-95
EKCO SRG 609.....	30-50	26-95
EKCO ZUS.....	165-00	135-00
FERGUSON 3422.....	87-85	69-95
FERGUSON 3423.....	118-25	94-95
FERGUSON 3424.....	120-15	99-95
FERGUSON 3425.....	145-10	114-00
FIDELITY Music Master UA2.....	48-00	35-95
FIDELITY Music Master UA1.....	98-00	82-95
GOODMANS Teleton 3000 Suite.....	140-45	92-95
H.M.V. 2416.....	129-70	104-95
H.M.V. 204/5/8.....	202-85	165-00
K.B. KA1250, complete with two 653 speakers.....	72-00	59-95
K.B. KA1250, complete with two 651 speakers.....	83-00	65-95
LEAK 30/GOLDRING/WHARFE-DALE.....	182-65	142-95
LEAK 70/THORENS/WHARFEDALE.....	218-72	169-95
MARCONI Unit 4.....	77-45	66-95
MARCONI Unit 3.....	95-00	69-95
METROSOUND Stereo 1010.....	77-32	65-95
PHILIPS GF823.....	51-50	41-95
PHILIPS GF824.....	69-50	56-95
PHILIPS GF823.....	67-50	55-95
PHILIPS GF834.....	88-00	73-95
PHILIPS 882 (less L/S).....	99-00	78-50
PHILIPS GF417.....	99-50	82-95
TELETON 2360F, with Stereo Radio.....	75-00	53-95
TELETON CRIOT 2025/1003, with Stereo Radio.....	62-10	45-95
TOSHIBA SP9507.....	248-00	175-00
ULTRA 6405.....	79-75	66-95

### TAPE RECORDERS AND TAPE DECKS

AKAI M10L.....	245-05	189-00
AKAI X200D.....	190-00	159-95
AKAI X5000 W/L.....	177-98	140-00
AKAI X330.....	342-57	269-00
AKAI X-330D.....	312-50	245-95
AKAI X-360.....	360-08	284-00

	Rec. Retail Price	Comet Price
AKAI X-360 D-deck.....	318-92	243-00
AKAI 1800SD.....	199-42	167-00
AKAI 1710L.....	89-85	65-95
AKAI CR80 8-track stereo recorder.....	115-03	99-95
AKAI CR80D 8-track stereo tape deck.....	95-00	79-95
AKAI 4000 4-track Stereo.....	124-90	99-95
AKAI 4000 D 4-track Stereo deck.....	89-95	69-95
BUSH TP 60 Cassette Tape Recorder.....	29-40	24-95
BUSH TP 70 Cassette Battery/Mains Tape Recorder.....	29-95	23-95
BUSH Discassette DC70.....	21-95	18-95
FERGUSON 3252.....	104-30	83-95
FERGUSON 3245 Twin track.....	38-00	29-95
FERGUSON 3246 4-track.....	44-10	34-95
FERGUSON 3247 4-track.....	49-65	39-95
FERGUSON 3248 4-track.....	55-65	43-95
FERROGRAPH 722.....	286-41	219-00
FERROGRAPH 702 2 track tape deck.....	228-71	193-00
FERROGRAPH 704/W 4 track tape deck.....	228-71	193-00
GRUNDIG C200L Cassette.....	39-90	29-95
GRUNDIG TK 141 (4-track).....	81-85	49-95
GRUNDIG TK 121 (Twin-track).....	56-85	43-95
GRUNDIG TK 146 (4-track Auto).....	68-14	53-95
GRUNDIG TK 149 4-track.....	57-63	47-95
MIDLAND TC 144 cassette.....	18-00	13-95
PHILIPS 2202 Cassette.....	29-90	23-95
PHILIPS 2205 Cassette.....	43-15	34-95
PHILIPS 2400 Stereo Cassette (Less L/S).....	68-00	59-95
PHILIPS 4404 4-track stereo recorder.....	95-00	72-95
PHILIPS 4407 4-track stereo recorder.....	110-00	89-95
PHILIPS 4302 Twin Track Auto.....	39-00	32-00
PHILIPS 4500 4-Track Stereo Tape Deck.....	126-00	96-95
PHILIPS 4408 4-Track Stereo.....	139-00	109-00
PHILIPS 4307.....	49-50	38-95
PHILIPS 4309.....	60-50	46-50
PYE Cassette Recorder/Radio (Batt./Mains).....	45-50	36-95
TELETON 811 Batt./mains cassette.....	29-50	17-50
TELETON FXB 910 D 4-track Stereo.....	67-50	52-00
TELETON TRC 130 cassette, with VHF/AM radio. Battery/mains twin motors.....	41-75	31-90
TELETON TC10 cassette, battery/mains.....	27-75	20-00
TOSHIBA GT 840 S.....	110-00	67-95
TOSHIBA GT 801V Twin Track.....	45-15	25-95
TOSHIBA 850 SA.....	94-00	59-95

### BASES AND COVERS

GARRARD WB1 Base.....	3-68	3-25
GARRARD WB4 Base.....	5-69	4-75
GARRARD SPC 1 Cover.....	3-74	3-00
GARRARD SPC 4 Cover.....	4-44	3-75
Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500.....	Special Price	4-00
GOLDRING Plinth 75.....	8-52	7-00
GOLDRING Plinth 69.....	8-52	7-00
GOLDRING Covers for 69P and 75P.....	4-21	3-50
THORENS TX25 (for TD125AB).....	8-22	6-50
THORENS TX11 Cover.....	4-11	3-75
Base and Cover for TD 125.....	15-18	12-50
SME Plinth System 2000.....	39-20	31-25
MOTORBOARDS only.....	4-95	3-00

### TEAK CASES

Leak 70/30 Amp. case.....	7-50	6-50
Leak Tuner case.....	7-50	6-50
Leak Double case for amp. & tuner.....	10-50	8-95

## COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use

	Rec. Retail Price	Comet Price
GOODMANS AUDIO SUITE, Goodmans Maxamp stereo amplifier, Goodmans stereomax AM/FM Tuner with decoder, Pair of Goodmans Magnum K2 speakers, Garrard AP76 turntable in base, complete with cover and Goldring 6800 Cartridge, Beautifully finished in walnut.....	257-13	169-95
METROSOUND 448 8-track stereo play-back unit complete with 2 HFS 10 Speakers.....	83-56	70-95
TELETON Stereo 8 track tape Audio system complete with speakers.....	54-75	48-00
GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge, Teleton 203 or 206 Stereo Amplifier 12 watts RMS, and 2 KELETRON KN500 Speakers, each speaker in a 4 speaker system.....	88-33	58-95
PIONEER PL 12 turntable, Goodmans Maxamp, Shure M55E Cartridge, 2 Keletron KN 700 speakers (each speaker cabinet contains 4 speakers).....	144-38	105-00
GARRARD AP76 turntable complete with Goldring 6800 Cartridge, base and cover, Rogers Ravensbrook Amplifier in teak case and 2 Goodmans Minister Speakers.....	142-41	108-50
GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING 8900E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers.....	200-50	154-20
THORENS TD 150AB Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Wharfedale Dovedale 3 Speakers.....	226-87	175-00
THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-11 Cartridge, GOODMANS Maxamp, GOODMANS Steromax AM/FM Tuner, 2 GOODMANS Magister Speakers.....	422-48	300-00



All in-stock items delivered by  
**SECURICOR**  
WITHIN 72 HOURS  
(Add £1.50 only for Securicor delivery)  
ALL GOODS FULLY INSURED AGAINST  
LOSS OR DAMAGE WHILE IN TRANSIT

Open daily to the public from 9-0 A.M. until—  
5-30 P.M. MON.  
1-0 P.M. TUES.  
3-0 P.M. WED.  
8-0 P.M. THUR.  
8-0 P.M. FRI.  
5-30 P.M. SAT.  
Customers are welcome to call—Ample car parking facilities

## Complete Price List FREE on request!

# COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407996 and 407877  
(Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE Tel. 32055 (5 lines)  
(Dept P.W.) Teesway, Portrack Lane, North Teeside Tel. 66132/65215  
Industrial Estate, Teesside, TS18 2RH

(Service Dept., New Road Side, Horsforth, Leeds)  
Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.  
Add 75p for postage, packing and insurance on all orders (Cartridges 20p)  
or, if Securicor delivery required, add £1.50 only.  
Make cheques, Money Orders payable to "COMET".

# TECHNICAL TRAINING

*in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- Radio Operator Certificates
- General Certificate of Education, etc.

Now available Colour T.V. Servicing Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



#### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept: 171, Intertext House, Stewarts Road, London, S.W.8.  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME .....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....

AGE.....OCCUPATION..... 6/71

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

#### RACK CABINETS

These are a fully enclosed 19" cabinet, overall size 37" x 22" x 22" fitted hinged rear door with lock removable side panels and adjustable front panel mounting positions, usable size 31 1/2" x 19", modern style cabinet finished in light hammer grey. Supplied in good condition with pull out drawer.

Price £8 plus £1 carr.  
or less drawer £7 plus £1 carr.

#### BC221 Mains Power Units

200/250v I/P provide o/p of 135v at 20 Ma from electronic stabiliser and 6.3v A.C. for heaters, fitted control panel C core transformer, with terminal connections, fit in battery compartment of BC221. Supplied in new condition with circ. and mains lead.

Price £6 plus 60p carr.

#### Rx/Ind APN-9

Combined swt tuned Rx and Ind. unit with 3BP1 tube 34 octal type valves, 100 Kc crystal unit and a large number of other parts, see April P.V. for full details. Supplied new with circ. etc.

Price £8 plus 75p carr.

#### R.F. 26 TUNING UNITS

These tune 50 to 65 Mc/s but can be modified up to 100 Mc/s use 3 valves R.F. Mix and L.O. 7 Mc/s I.F. O/P fitted 40-1 S.M. drive supplied in good cond. with circ. Price £2-10 plus 40p. post. 3645 I.F. & O/P unit for above with circ.

Price £1-50 plus 75p carr.

#### G.P.O. Style Hand Sets

Fitted press to talk swt., these have low Res earpiece and moving coil mike, supplied new and boxed with lead.

Price 80p plus 20p post.

#### 270° Radio Altimeters

Meter 3 1/2" sq., basic movement 1.5 Ma. also available with 6.5 Ma basic, fitted on/off and range swt. Supplied in new cond.

Price 80p plus 15p post.

#### Rx Unit 16048

Special purpose V.L.F. Rx contains large number of modern parts as follows, 8 type LA2503 Vinkors, 4 sil transis, 6 type EF72 valves, 5 miniature relays, 2 high res. relays, OB2 and 85A2 stab. valves, 7 400 P.I.V. diodes, plugs and sks, Tant conds, etc., etc. Supplied in new cond.

Price £2-10 plus 40p carr.

#### Misc Items

Speaker units 8" 3 ohm spk in case size 18 x 18 x 8" with 600 ohm line trans, new, £2-90. Osc. unit with valves 12AT7x3, 6EP1x2, LA2, jack sk, coax sk etc new, 70p. RF24 tuning unit swt tuned 20/30 Mc/s with circ, £1, O/P and Test unit with 2 vinkors, 4x Sil transis, 4x min relays coil I K 2p c/o, new 85p. Meters 1 Ma edgewise near scale 0 to 2000 yds size 3 x 1 x 3/4 tested, £1. Tube type 3BP1 with base and Mu met shield with connections, 3" green screen ideal scope use. £2-50. Control unit with 2x 500 Ua basic movement meters, 3x yax swts, pots etc new, £2. Valves 6SN7 5 for 50p, Miniature plugs and Sks 18 way 15p, 14 way 10p, Mains Trans all 230v Pria type A. Sec 490-400-0-400-490v @ 200 Ma, 5v 3a, 6.8v 4a 6.3v 1-6a, 12v 1a, £2-55. Type C. Sec 50v 1a, 6.3v 3a £1-50. Meters 1-0-1 Ma 3/4" Fl Rd tested £1-45. Mercury swts small type 2 for 25p. Panel fuse holders take 1 1/2" fuses 3 for 30p. Precision Resistors dual 500K 1% can be connected to give 250K, 500K and 1 Meg new, 30p. Joy Stick controllers give X&Y o/p from 2x20K precision pots. £1-50. Scope Trolleys by Cossor, £4-75, Conds 8uf 750v 2 for 60p, 4uf 750v 2 for 40p, 8uf 1kv 2 for 90p. Helical Pots 500 ohm, 2-5K, 50K, 85p. Pot. Cores LA66 4 for 50p, LA2503 Vinkor 4 for 50p, Heat Sinks finned in matt black size 1 1/2 x 9 x 1" drilled for 4 T.O.3 transis with 4 x 1 ohm res, £1, Relays coil 6 or 12v DC 1 N.O. 20a contact 40p, T.S.210 covers 20 to 85 Mc/s in 4 bands with xtal check req 250v and 6-3, £3-90. Amplifier units mains I/P (reg pre amps) Lowcher 2xEL34 O/P used cond, £9. Quad 11 2xKT66 O/P new cond both tested, £11. Circuit Diagrams 1392 and 1475(88) Rx 30p ea, Scopes CD513 2 set of 3 circs, £1-50, CD518 (CT316) 50p, 13A 50p, Dumont 208 and OS-8, 50p, USM-25 (OS-4) 2 circs £1, T.S. CT38 late series 50p, T.S.219 50p.

The above goods are ex equipment unless otherwise stated. Prices of misc. items include postage, carriage charges apply to mainland only S.A.E. for list or enquiry.

## A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9.5HL.



# LIND-AIR AUDIO

## C.1001 MULTI-TESTER.




Size of meter 4 1/2 x 3 1/2 x 1 in. Complete with case.

£4.25. P. & P. 17 1/2p

Overload protection. 20,000 opv. AC volts 10, 50, 250, 1,000v. DC volts 0-55, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-60K 0-6 Meg ohm. Decibels -20 to +29dB.

## SINCLAIR PROJECT 60

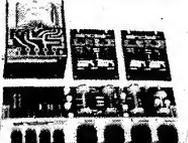

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. £30 24 watt Power Amplifier £4.47 1/2. (2 required).

Stereo Sixty Control/Pre-amplifier £9.97 1/2.

PZ.5 Power Supply Unit £4.97 1/2.

SINCLAIR PROJECT 60 Package deal price £19.95. P. & P. 62 1/2p

Project 60 is supplied complete with instruction manual and templates for pinth mounting.

## CARTRIDGE BARGAINS

A.D.C. 220X	£6.12 1/2
A.D.C. 220XE	£9.96 1/2
A.D.C. 860XE	£15.52 1/2
A.D.C. 990XE	£18.81
Audio Technica AT66-7D	£6.12 1/2
Audio Technica AT66-5D	£6.12 1/2
Audio Technica AT66	£6.12 1/2
Decca Deram Stereo	£5.12 1/2
Decca Deram Mono	£3.15
Goldring G800	£12.75
Goldring 800T	£10.50
Goldring G800 E	£16.50
Goldring G800 Super E	£28.00
Goldring G850	£26.50
Shure M3DM	£7.41
Shure M44 7	£10.15
Shure M31 E	£12.00
Shure M35 E	£12.50
Shure M75 E	£22.80
Shure V15 II	£40.75
Sonotone 9TAHCD	£2.75

Full range of diamond styli available for most current ceramic and crystal cartridges. All at £1.25 each. P. & P. 5p. Please state cartridge make and type number.

## GARRARD HI-FI TURNTABLES




3025 T/C with stereo cartridge	£9.97 1/2
3000 with Sonotone	£10.97 1/2
9TAH CD stereo cartridge	£10.97 1/2
SP25 Mk III	£11.97
SL65 B	£15.97 1/2
Base and cover for above	£2.97 1/2
AP76	£18.50
SL72 B	£24.97 1/2
SL76 B	£28.55
SL95 B	£39.45
Base and cover for above	£8.97 1/2
401	£28.50

P. & P. Decks 62p. Base & Cover 50p. Deck/Case/Cover 57p.

THIS MONTH'S SPECIAL OFFERS! SP25 Mk III with base £12.97 1/2. P. & P. 75p SP25 Mk III with Sonotone 9TAHCD cartridge and base £13.73 1/2. P. & P. 75p.

## C.1050 MULTI-TESTER

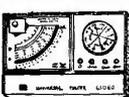

DC Current: 0-120 uA, 0-300 mA. Resistance: 0-50K, 0-5 Meg (R x 1K)

Decibels: -20 to +17dB. (R x 10) £5.97 1/2. P. & P. 17 1/2p

10,000 opv. RANGES: DC Voltage: 0.3-15-150-600-1200 Volt (10,000 ohms per Volt). AC Voltage: 0.6-30-300-1200 Volt (5,000 ohms per Volt).

## SINCLAIR IC-10 INTEGRATED CIRCUITS

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 6 years. £2.97 1/2. P. & P. 7 1/2p

SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v at 0.5 amp. 82p. P. & P. 12 1/2p


## VHF AIRCRAFT BAND CONVERTER Model VHF.105

When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 110-135 Mc/s. can be obtained. All transistor, 9v battery operation. Fully tunable 18 1/2 in. x 7 section telescopic aerial. Size 4 x 2 1/2 x 1 1/2in.



OUR PRICE £3.60 P. & P. 10p

## C.1052 MULTI-TESTER

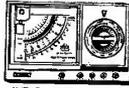

DC Current: 0, 0.01, 0.1, 1, 10, 100 mA. Resistance: 0, 5K, 50K, 500K, 5 M ohms. Decibels: -20 to +63dB. £7.35. P. & P. 17 1/2p

RANGES: AC Voltage: 6, 30, 120, 300, 1200 (15,000 ohm/V) DC Voltage: 0.6, 3, 15, 60, 300, 1200 (30,000 ohm/V)

## UNILEX AUDIO MODULES



Build a stereo amplifier for as little as £16.75. Send 25p for Mullard "Do It Yourself Stereo" booklet. All items in stock.

## LA.20 STEREO SYSTEM



Only takes a few minutes to set up the Lind-Air LA 20 Stereo Amplifier with the Garrard 3025 T/C Record Changer fitted stereo cartridge and a pair of Lind-Air General Purpose speakers and you have a superb stereo system at a money saving price. Total Rec. Price £53.47 1/2.

Price £41.47 1/2. C. & Ins. £1.75

## SM-370 MULTI-TESTER



20,000 opv. RANGES: DC Voltage: 0.5-25-100-500-1000V (20,000 ohms/V). AC Voltage: 0.5-25-100-500-1000V (20,000 ohms/V). DC Current: 0-50 uA, 0-250 mA. Resistance: 0.5K, 5K, 50K, 500K, 5 M ohms and 30K ohms at centre scale). Decibels: -20dB to +15dB. £3.55. P. & P. 17 1/2p

## E.M.I. LOUDSPEAKERS



MODEL 450 13 1/2" x 8" elliptical with twin tweeters. 8 ohm impedance. 10 watts. Brand New, guaranteed. Lind-Air Price £3.97 1/2. P. & P. 22 1/2p

MODEL 150 13 1/2" x 8" elliptical. 3 and 15 ohm impedance. 10 watts. Lind-Air Price £2.97 1/2. P. & P. 22 1/2p


## DE-LUXE STEREO HEADPHONES



With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug. £2.97 1/2. P. & P. 17 1/2p

STEREO HEADPHONE JUNCTION BOX Enables stereo headphones to be used with any amplifier. £1.47 1/2. P. & P. 12 1/2p

## S-DeC BREADBOARD

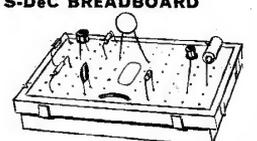

Solderless breadboard panels, for fast reliable component connections. Single DeC. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. £1.00. P. & P. 17 1/2p

## BATTERY ELIMINATOR



Enables transistor equipment to be operated from AC mains. 6/9/12v. output selector switch and position trigger control. complete with mains lead, connecting leads and instructions. £2.97 1/2. P. & P. 17 1/2p

## CELESTION LOUDSPEAKERS

7" x 4" elliptical. 8 ohms. New and guaranteed. £1.37 1/2. P. & P. 22 1/2p


CABINETS FOR ABOVE Teak finish with cloth fronts. £2.47 1/2 each. P. & P. 22 1/2p

## HI-FI CATALOGUE

100 pages fully illustrated with 8 page P.A. section. All leading makes and accessories plus details of Budget Stereo systems. 25p P. & P. 5p



## WELLER "EXPERT" SOLDERING GUN

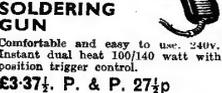

Comfortable and easy to use. 240v. AC. Instant dual heat 100/140 watt with two position trigger control. £3.37 1/2. P. & P. 27 1/2p

## 4-DeC KIT, Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £3.95. P. & P. 22 1/2p

T-DeC KIT £2.50. P. & P. 17 1/2p

S-DeC STOR £2.50. P. & P. 22 1/2p

18-19, TOTTENHAM COURT ROAD, LONDON, W.1. Tel: 01-580 2255  
25, TOTTENHAM COURT ROAD, LONDON, W.1. Tel: 01-580 7679  
53, TOTTENHAM COURT ROAD, LONDON, W.1. Tel: 01-637 1601  
94-96, UPPER PARLIAMENT STREET, NOTTINGHAM. Tel: 40403 (STD 0602)  
149, FLEET STREET, LONDON, E.C.4. Tel: 01-353 1419

All mail orders and enquiries to: Dept PW6  
53 TOTTENHAM COURT ROAD,  
LONDON, W.1. Tel: 01-637 1601

Open: Tottenham Court Road 9-6 Mon to Sat (Thurs until 7); Fleet Street 9-6 Mon to Fri, 9-1 Sat; Nottingham 9-6 Mon to Sat (Weds until 7.30)

# BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

## FULLY TESTED AND MARKED

AC107	15p	OC170	23p
AC126	13p	OC171	23p
AC137	17p	OC300	25p
AC128	13p	OC201	25p
AC176	25p	20301	13p
AOY17	15p	26303	13p
AF239	37p	2N1392-3	40p
AFY26	50p	2N1304-5	25p
AF139	37p	2N1306-7	30p
BC154	25p	2N1308-9	35p
BC171-BC107	13p	2N1339-FET	45p
BC173-BC108	13p	2N3844A	25p
BF194	18p	<b>POWER TRANSISTORS</b>	
BF274	15p	OC20	50p
BFY50	20p	OC23	30p
BSY23	37p	OC25	40p
BSY26	13p	OC26	25p
BSY27	13p	OC28	40p
BSY28	13p	OC26	25p
BSY29	13p	OC36	37p
BSA95A	13p	AD149	30p
OC41	13p	AU Y10	£1.25
OC44	13p	2N3055	35p
OC45	13p	28034	25p
OC71	13p	<b>DIODES</b>	
OC72	13p	AA Y42	10p
OC81	13p	OA91	8p
OC81D	13p	OA79	8p
OC139	13p	OA81	8p
OC140	17p	IN914	7p

## NEW UNMARKED UNTESTED PAKS

H10	25	Mixed volts 1½ watt Zener Top Hat type.	50p
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	50p
B66	150	High quality Germ. Diodes. Min. glass type.	50p
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	50p
H15	30	Top Hat Silicon Rectifiers 750 mA. Mixed volts.	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types.	50p
H16	8	Experimenters' Pak of Integrated circuits. Data supplied.	50p
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes. Mixed voltages.	50p
H20	20	BY126/7 type Silicon Rectifiers 1 amp plastic. Up to 1,000 volts.	50p
H6	40	250mW. Zener Diodes DO-7 min. Glass Type. AV.40% Good.	50p

## NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt. .5 to 2 ma.	50p
B8	4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100	50p
B79	4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	50p
B81	10	Reed Switches, mixed types, large and small.	50p
B99	200	Mixed Capacitors, Post and packing 13p. Approx. Quantity counted by weight.	50p
H4	250	Mixed Resistors, Post and packing 10p. Approx. Quantity counted by weight.	50p
B7	40	Wirewound Resistors. Mixed Values. Postage 7p.	50p
H9	2	OC71 Light Sensitive Photo Transistors.	50p
H12	20	NKT155/259 Germ diodes, brand new stock clearance.	50p
H18	10	OC71/75 unoded black glass type PNP Germ.	50p
H19	10	OC81/81D unoded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP silicon unoded toleson.	50p
H29	20	OA47 gold bonded diodes coded MCS2.	50p

**FREE!** Packs of your own choice up to the value of 50p with orders over £4.

## RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 370. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

**P1** PLEASE ASK FOR PAK P1. ONLY 50p  
10p P. & P. on this Pak

## COLOUR T.V. LINE OUTPUT TRANSFORMERS. Designed to give 25KV when used with HL509 & PF500 valves. As removed from colour receivers at the factory.


ONLY £1 each. Post & Packing 25p

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS and CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.
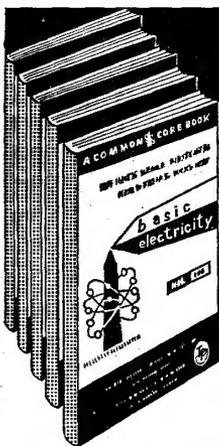
## P.O. RELAYS 8 FOR

Various Contacts and Coil Resistances. £1  
Post & Packaging 25p



# YOURS FREE FOR 7 DAYS

## The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 vols.)** **BASIC ELECTRONICS (6 vols.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

### WHAT READERS SAY

"BEST BOOKS IN THIS COUNTRY"  
"On going through these books I have found they are the best books I have ever had in this country."

"KEY TO THE KNOWLEDGE"  
"Your books have been the key to the knowledge I have needed."  
J.M., Horsham.

"UNDERSTAND THE BASIC FACTS"  
"This is the first time I have been able to understand the basic facts as all other books are too complicated."  
L.W., Sheffield.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. BASIC ELECTRONICS £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS   
Prices include Postage and Packing.

Signature \_\_\_\_\_  
(If under 21 signature required of parent or guardian)

NAME \_\_\_\_\_  
BLOCK LETTERS

FULL POSTAL ADDRESS \_\_\_\_\_

**POST NOW FOR THIS OFFER!!**

## FIND BURIED TREASURE! TREASURE LOCATOR FULLY TRANSISTORISED

NOW TRY HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorized metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phone used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COPPER, IRON, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC.** Outdoors or indoors. *Extremely sensitive, will signal presence of certain objects buried several feet below ground!* No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is easy as A.B.C.



ONLY  
**£2-37**  
(47/6)

Fully transistorized—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2" x 10" x 2 1/2". Great demand expected at this remarkably low price. **ORDER WHILE PRESENT STOCKS LAST.** All parts including detector head, case, nuts, screws, wire, simple instructions etc. etc. **ONLY £2-37 (47/6)** x 23p (4/6) p. & p. (Telescopic handle as illustrated £1-75 (35/-) extra). Parts available separately. Made up boxes worth £15!

## BUILD 5 RADIO AND ELECTRONIC PROJECTS



TOTAL BUILDING PRICE **£1-97**


(39/6)  
Amazing Radio Construction set! Become a radio expert for £1-97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each project. Illustrated Step-by-step plans, all Transistors, loudspeaker, personal

phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only **£1-97 (39/6)** + 23p (4/6) p. & p.

## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

**CUTS OUT NOISE POLLUTION—SOOTHES YOUR NERVES!** Don't underestimate the uses of this fantastic new design—the **RELAXATRON** is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. *A group of Dentists have experimented on patients with this pink noise—NO ANESTHETICS WERE USED!* The noise ostensibly created a most definite reaction on these patients' nervous systems with the results that their pain systems were blocked. **IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron.** Once used you will never want to be without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. **TAKE IT ANYWHERE,** pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost all-time!) **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only **£2-25** + 25p (4/-) p. & p. (Parts available separately.)

only **£2-25**  
(45/-)

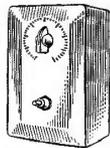

## GET A GOOD NIGHT'S SLEEP—EVERY NIGHT!

### INGENIOUS ELECTRONIC SLEEP INDUCER

**CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT?** Then build this ingenious electronic sleep inducer. *It even stops by itself so you don't have to worry about it being on all night!* The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether. *The effect it has on people is amazingly very similar to hypnosis.* A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. *Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included.* No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. **THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75** + 25p (5/-) + 5/- p. & p. (parts available separately.)




only **£2-75**  
(55/-)

## EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT
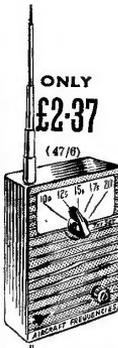
### V.H.F. AIRCRAFT BAND CONVERTER

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. *Eavesdrop on exciting cross-talk between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tensions on talk downs.* Be with them when they have to take nerve ripling decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC., ETC. CLEAR AS A BELL. This fantastic fully transistorized instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portable!) **NO CONNECTIONS WHATSOEVER NEEDED.** Use indoors or outdoors. **THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW. ONLY £2-37 (47/6)** + 23p (4/6) p. & p. for all parts, including case, nuts, screws, wire, etc. etc. (parts available separately.)



ONLY  
**£2-37**  
(47/6)




ONLY **£2-25**  
(45/-)

## SHORTWAVE TRANSISTOR RADIO

### Can be built in one evening

At last! After trying countless circuits searching for the best build, work first-time short wave. Giving advanced world-wide performance, we chose this 'Sky Roma'. Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 78 stations logged on rod aerial in 30 mins.—Russia, Africa, U.S.A., Switzerland, etc. Experience thrills of world wide news, sport, music, etc. *Eavesdrop on unusual broadcasts.* Uses PP3 battery. Transistorised (no valves). Size only 3" x 4 1/2" x 1 1/2". As tremendous demand anticipated price held to only **£2-25 (45/-)** + 17p (5/6) p. & p. for all parts incl. Cabinet, screws, instructions etc. (Parts available separately.)

## REAL WORKING ELECTRONIC ORGAN

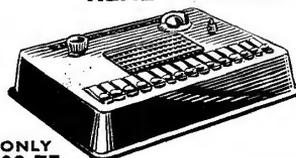


ONLY **£2-75**  
(55/-)

Anyone from nine years upwards can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low, low building price. **ONLY £2-75 (55/-)** + 23p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, volume control, wire, nuts, screws, simple instructions etc. etc. Use standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

## READY BUILT & TESTED

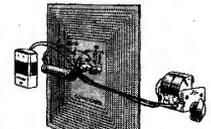
### Treasure Locator Module

**BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE.** Ready built and tested—just plug in a PP3 battery and phones and it's working. Put it in a case, screw a handle on and **YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £30!** Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—**EASILY LOCATES GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC. ETC.** Signals exact location by "beep" pitch increasing as you near buried metallic objects. **PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN!** You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. **ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4-95** + 30p extra (99/- + 6/-) etc. (High quality Danish Stethoscope headphones £2-75 (55/-) extra if required.)



only **£4-95** (99/-)

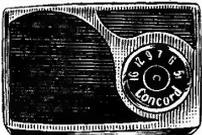**UNIQUE RADIO FOR BEDROOM ONLY OR OFFICE**  
No batteries no electricity, never wears out



Tune in your favourite programmes or the news, or sports in the Office or in your bedroom. Use sensitive, germanium diode originally evolved from wartime radar. Never buy a battery. Never use electricity. Never replace. Covers all medium waves. Clear beautiful tone. Size 4 1/2" x 2 1/2" x 1 1/2" in beautiful case. **ONLY 7 CONNECTIONS AND IT'S WORKING.** No soldering necessary. **CAN BE BUILT ALMOST BLINDFOLD IN UNDER 15 MINUTES!** Ideal for absolute beginner from 8 years of age upwards. **SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS. ONLY £1-25 (25/-)** + 13p (2/6) p. & p. for all parts including beautiful case. Germanium semiconductor, tuning condenser, personal phone, wire, nuts, screws. **SIMPLE AS A.B.C. INSTRUCTIONS.** (Parts available separately.)

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

**CONCORD ELECTRONICS LTD (Dept. PW20)** 8 Westbourne Grove, London W.2.  
(Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema)  
Callers Welcome 9 a.m.-6 p.m. inc. Saturday

# Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)

Transistors etc. AC126 12½p. AF115 15p. AF116 15p. AF117 20p. OA5 7½p. OA10 7½p. OA81 7½p. OA85 7½p. OC23 32½p. OC25 37½p. OC26 37½p. OC28 42½p. OC35 42½p. OC44 14p. OC45 12½p. OC71 12½p. OC72 12½p. OC75 12½p. OC81 12½p. OC81D 12½p. OC82D 12½p. OC170 20p. OC171 12½p. Many more in list. S.D.R. BY100 800piv 14p. 6 amp series: BY213 300piv 20p. BY212 600piv 25p. BY211 900piv 30p. BY210 1200piv 35p. (Charges 6½p. up to 11, paid for 12 and over). Sub-Min Transformers: OUTPUT (3 Ω for OC72, etc.) 14p. (up to 6 6½p.). MULTIMETER. Our famous 2000 Ω per V £4-62 (15p.). Details and other in list. SOLDERING IRON. Slim, modern, British high-speed 81", all parts replaceable, highest quality, full guarantee: £1-74 (10p). DIAMOND STYLII Replacements for BSR TC8/LP, TC8/8, TC8LP/STEREO; COLLARO '0': RONETTE BF 40LP; GARRARD GC2/LP and GC8/LP; ACOS GP65/67, all at 40p (6p). ACOS GP73, GP91; BSR ST4 (ST3, ST5), ST8 (ST9); SONOTONE 8TA, 9TA, 9TAHC; PEEIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304); Garrard GKS25 all at 75p (6p). All are of the very highest quality. DOUBLE DIAMOND: ST4 (ST3, ST5); ST10 (ST9, ST8); 9TA, 9TAHC 3306, GP91 (For GP92, GP93, GP94 cartridges); GP91SC for all GP91-SC Cartridges: All at £1-50 each (6p). PICK-UP CARTRIDGES All standard fittings and stylii. MONO GP67/2 75p. STEREO COMPATIBLE (MONO) GP91/SC £1-05. STEREO GP93 £1-27½. STEREO CERAMIC GP94 £1-92½. SONOTONE STEREO 9TAHC(DIA.) £2-37½. GOLDRING G850-£4-87½. G800 £8-50. G3000 £13-50. G800 SUPER E £19-50 (6½p all types or Res., Post 22½p.). STYLII FOR ALL ABOVE TYPES, including GOLDRING available. RECORDING TAPE. Still the finest quality British Mylar available: Standard 5" 600 ft. 36p. 5½" 900 ft. 56p. LONG PLAY 5" 900 ft. 50p. 5½" 1200 ft. 56p. 7" 1800 ft. 90p. (7½p on 5" and 5½"). MICROWAVES Crystal Mic 91, hand/desk 81p. MIC45 Curved metal handrip £1-00. CM21 Grey hand desk 52½p. Stick '60' £1-02½. CM70 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands £1-47½ (all 9p) LAPEL (or hand) with clip 32½p (6p). All are fitted with leads. Dynamic. Cream hand/table MINY 7½p (20p). MS10 50K Ω for desk, tapered with base and slide-out adaptor £1-97½. MS11. Similar, but fixed on swivel swan neck to switch-fitted base £2-22½. (Either 15p). Type 209 Cardioid ball, 50K/600 Ω, omni-dir. built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £6-30. DM160. Non-Dir. Ball, 50K cable, adaptor £3-87½ (27½p either). MICRAPHONE INSERTS, Dia., 1-75" OR 0-9" either size 27½p (6p). EARPIECES with lead & min. jack plug (2-5 or 3-5 mm., state which). Magnetic 9p. Crystal (3-5 only) 24p. (Up to 3 for 6p on up). HEADPHONES De-luxe STEREO 8-16 Ohms, £2-47½. Sams, fitted vol. control each 4-20p. Both have lead and stereo jack plug (17½p). HIGH RES. 2000 ohm. Adjustable 92½p (10p). SPEAKERS. 12" ROUND fitted tweeter, 3 or 15 Ω (state which) £1-97½ (27½p) of for Stereo £4-25 pair, carr. paid 2½", 3 or 8 Ω (state which) 37½p (6p). EMI 13" x 8", 3, 8 or 15 Ω (state which) £2-12½ (25p); with single flared para. tweeter cone 8 or 15 Ω (state which) £2-27½ (25p); with two tweeters and crossover network 8 or 15 Ω (state which) £3-75 (25p). VIBRATORS. Genuine Plessey 12V 4-pin non-synch. 121HD4, 27½p. 12V 7-pin Synchron. (12SR7) 62½p (All types 64p per vibrator). CONNECTING WIRE. Packs of 5 coils assist ca. coil 5yds. Solid core 14p (6p). Flexible 16p (7½p). Super thin for transistor wiring 16p (6p). PICK-UP WIRE. Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds.—over free). RECTRACTABLE Flex. Leads. (Curlys) 6ft. phonoplug ea. end 22½p. 12ft 39p. 6ft. phono plug/phonosocket other end 25p. 12ft. 42½p. (6p per lead all types). BATTERY ELIMINATOR. 240V AC input 3, 6, 7½ & 9V. DC output at 400 mA. Two switches, leads, pilot light and universal adaptor for all trans. appliances including all makes cassette tape recorders and players £3-15 (24p). SEND SAE for full free lists. Small 3W and 7½W trans. amplifiers. Electrolytics, Vol. controls, all types of radio switches, car and portable expanding aerials, headphones, test prods, all types of Brit. & Cont standard and min. plug and sockets, S.D.R.'s resistors, croc. clips (various) terminals, etc., etc. and many "Special Offer" lines at lowest possible prices.

## BRAND NEW

SGS/FAIRCHILD SILICON NPN TRANSISTORS.			
BD 112 AUDIO	80 volts	20 watts	TO3 32p. (10 for £2-50)
BD 116 AUDIO	80 "	20 "	TO3 45p. (10 for £4-00)
CP400 REGULATOR	40 "	15 "	TO3 37½p.
CP401 REGULATOR	60 "	15 "	TO3 37½p.
CP402 REGULATOR	100 "	15 "	TO3 42½p.
CP404 AUDIO	80 "	15 "	TO3 37½p.
CP430/			
431 AUDIO	100 "	30 "	TO3 37½p.
CP433 AUDIO	120 "	40 "	TO3 42½p.
CP702 AUDIO	60 "	15 "	TO3 37½p.
CP704 RF or SERVO	80 "	30 "	TO3 47½p.
BLY68 AUDIO	100 "	25 "	TO3 50p.
BLY72 HIGH POWER	80 "	100 "	75p.
CP703 HIGH CURRENT RELAY	60 volts	5 watts	32½p.
BFW76 MICROWAVE OSCILLATOR	4GHZ	30 volts	1 watt £1-00
2N3646 HIGH SPEED SWITCH	40 volt	1 amp	22½p.
2N4075 AUDIO	100 volts	30 watts	55p.
2N4076 AUDIO	100 "	30 "	45p.

VARICAP DIODES  
BBY10 6.3pF. BBY11 10pF. BBY12 12pF. 25p each  
INTEGRATED CIRCUITS, FLIP PACKS.  
USA 998979X. 4 CHAS MADE BINARY. 75p.  
U3T.771139X. DUAL DIFFERENTIAL COMPARATOR 75p.  
U3H.771239X. DC AMP. up to 30 MHz. 75p.  
U31.993151X. CLOCKED FLIP FLOP. 62½p.  
CHARGES:—6½p up to 11, paid for 12 and over.

ANNUAL HOLIDAYS. No orders or correspondence received after May 21st will be dealt with until June 10th.

## FELSTEAD ELECTRONICS (PW)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE  
Cash with order only. No COD or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage, unacceptable. SAE please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

## RSGB BOOKS FOR YOU

### VHF-UHF MANUAL

By G. R. Jessop, C Eng, MIERE, G6JP

2nd edition. Considerably enlarged and revised. Transmitters, receivers and test equipment for use at vhf and uhf are all fully covered on a practical basis in this new edition. £1-80 post paid

### RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical and constructional fields. A superb hard-bound volume. £3-50 post paid

### AMATEUR RADIO TECHNIQUES

By Pat Hawker, G3VA

Third edition. A source of many useful circuits and aerials incorporating the latest amateur techniques. Contains 208 pages and nearly 500 diagrams. £1-13 post paid


These are three of a complete range of technical publications, log books and maps, all obtainable from:

### RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE
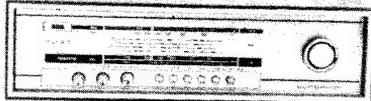
## FANTASTIC BARGAIN OFFER! TRANSEUROPEAN

Transistorised Stereophonic High Fidelity AM/FM Tuner Amplifier System.



This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in. matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price.

Easily fitted no technical knowledge necessary.

SPECIAL OFFER

£44

Credit Terms available. First monthly payment of £5-83 followed by 9 monthly payments of £4-95. Total Credit Sale Price £69-50. Send £5-83 today.

### FABULOUS VALUE

Transistorised Stereo Hi-Fi Record Player Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10in. x 6in. speakers and the latest 4 Speed BSR Stereo/Mono Record Changer.

£90

P. & P. 88p

Credit terms lastly payment £2-46 followed by 9 monthly payments of £3-38 (Total c/s price £33-80). Send £4-26 today.

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.

CALLERS WELCOME

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name .....


Address .....

..... P.6/71

Post coupon NOW for... FREE leaflets

LEWIS radio 100, Chase Side London N.14 Tel: 01-886 3733/9666

**★ TRANSISTORISED FM TUNER**

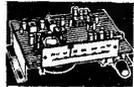

TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2 in. 1 F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £8-87 1/2. P. & P. 12 1/2p. Stereo multiplex adaptors £4-97 1/2.

**AVO CT471A MULTIMETER**

Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures A/C/D Voltages 15mV to 1,200V. A/C/D Current 12mA to 1.2 Amp. Resistance 12 ohm to 120 MΩ. H.F. V.H.F. U.H.F. Voltage with multiplier 4v to 400v up to 50 Mc/s, 40mV to 4v up to 1,000 Mc/s. Offered in perfect condition. £55 each. Carr. 50p.

**CRYSTAL CALIBRATORS NO. 10**



Small portable crystal controlled wavemeter. Size 7 x 7 x 4 in. Frequency range 500 Kc/s-10 Mc/s (up to 40 Mc/s on harmonics). Calibrated dial. Power requirements 300V D.C. 15mA and 12V D.C. 0.8A.

Excellent condition. £4-47 1/2. Carr. 37 1/2p.

**B.C. 221 FREQUENCY METERS**

Latest design 120 KHz-50 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. Carr. 50p.

**AM/FM SIGNAL GENERATORS**

Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airtec. Frequency coverage 20-50 Mc/s. AM C/W/FM. Incorporates precision dial, level meter, precision attenuator 1kV-100mV. Operation from 12 volt d.c. or 0/110/200/250 volt A.C. Size 12 x 8 x 9 in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. £1.

**AVO CT.38 ELECTRONIC MULTIMETERS**

High quality 97 range instrument which measures A.C. and D.C. Voltage, Current, Resistance and Power Output. Range 0-1000V D.C. current 10mA-25 amps. Ohms, 0-1000 meg Ω A.C. volt 100V-250V (with R.F. measuring head up to 250 Mc/s). A.C. current 10mA-25 amps. Power output 50 micro-watts-5 watts. Operation 0/110/200/250V. A.C. Supplied in perfect condition complete with circuit lead and R.F. probe. £85. Carr. 75p.

**ADMIRALTY 62B RECEIVERS**

High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 150-300 Kc/s, 560 Kc/s-1.5 Mc/s, 3.0-30.5 Mc/s I.F. 500/Kc/s. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/230 volt A.C. Offered in good working condition. £22-50. Carr. £1-50. With circuit diagrams. Also available B41 L.F. version of above, 15 Kc/s-700 Kc/s. £17-50. Carr. £1-50.

**TO-3 PORTABLE OSCILLOSCOPE**

3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 30pF X amp. sensitivity 0.0v p-p/CM. Bandwidth 1.5 cps-500KHz. Input Imp. 2 meg Ω 30pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external Illuminated scale 140 x 215 x 350 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £37-50. Carr. 50p.

**TO-2 PORTABLE OSCILLOSCOPE**

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CF2-1 MHz. Input Imp. 2 meg Ω 25 P.F. Illuminated scale. 3in. tube, 115 x 180 x 230mm. Weight 8 1/2. 220/240 V a.c. Supplied brand new with handbook. £22-50. Carr. 50p.

**SEW PANEL METERS**

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

**NEW "SEW" DESIGNS!**

**CLEAR PLASTIC METERS**  
TYPESW.100  
100 x 80 mm.

20V D.C. £2-97  
50V D.C. £2-97  
60-0-60μA £2-97  
1 amp. D.C. £2-97  
100-0-100μA £2-97  
1 amp. D.C. £2-97  
300V A.C. £2-97  
1mA £2-97  
VU Meter. £2-75

50V D.C. £2-97  
50V D.C. £2-97  
300V D.C. £2-97  
1 amp. D.C. £2-97  
100-0-100μA £2-97  
1 amp. D.C. £2-97  
300V A.C. £2-97  
20V D.C. £2-47  
VU Meter. £2-75

**BAKELITE PANEL METERS**  
TYPE S-80  
80 mm square fronts

50μA £2-10  
50-0-50μA £2-97  
100μA £2-97  
100-0-100μA £2-97  
1 amp. D.C. £2-97  
1mA £2-97  
20V D.C. £2-47  
VU Meter. £2-75

50V D.C. £2-97  
50V D.C. £2-97  
300V D.C. £2-97  
1 amp. D.C. £2-97  
100-0-100μA £2-97  
1 amp. D.C. £2-97  
300V A.C. £2-97  
20V D.C. £2-47  
VU Meter. £2-75

**"SEW" CLEAR PLASTIC METERS**

Type MR.55F. 4 1/2in. x 4 1/2in. fronts.

50mA £2-80  
100mA £2-80  
500mA £2-80  
1 amp. £2-80  
5 amp. £2-80  
30 amp. £2-80  
20V D.C. £2-80  
50V D.C. £2-80  
150V D.C. £2-80  
300V D.C. £2-80  
15V A.C. £2-80  
300V A.C. £2-80  
8 Meter 1mA £2-80  
VU Meter. £2-80  
1 amp. A.C.\* £2-80  
5 amp. A.C.\* £2-80  
10 amp. A.C.\* £2-80  
20 amp. A.C.\* £2-80  
30 amp. A.C.\* £2-80

Type MR.38P. 1 1/2 3/8in. square fronts.

50μA £2-60  
50-0-50μA £1-97  
100μA £1-97  
100-0-100μA £1-75  
200μA £1-75  
500μA £1-50  
1mA £1-37  
1-0-1mA £1-37  
2mA £1-37  
5mA £1-37  
10mA £1-37  
50mA £1-37  
100mA £1-37  
150mA £1-37

50μA £2-60  
50-0-50μA £1-97  
100μA £1-97  
100-0-100μA £1-75  
200μA £1-75  
500μA £1-50  
1mA £1-37  
1-0-1mA £1-37  
2mA £1-37  
5mA £1-37  
10mA £1-37  
50mA £1-37  
100mA £1-37

Type MR.52P. 2 1/2in. square fronts.

50-0-50μA £2-80  
100μA £2-80  
100-0-100μA £2-80  
200μA £2-80  
500μA £2-80  
1mA £2-80  
5mA £2-80  
10mA £2-80  
50mA £2-80  
100mA £2-80  
1 amp. £2-80  
5 amp. £2-80  
10 amp. £2-80  
20 amp. £2-80  
30 amp. £2-80

10V D.C. £2-80  
20V D.C. £2-80  
50V D.C. £2-80  
150V A.C. £2-80  
300V A.C. £2-80  
8 Meter 1mA £2-10  
VU Meter. £2-10  
1 amp. A.C.\* £2-80  
5 amp. A.C.\* £2-80  
10 amp. A.C.\* £2-80  
20 amp. A.C.\* £2-80  
30 amp. A.C.\* £2-80

Type MR.45P. 3in. square fronts.

50μA £2-85  
50-0-50μA £2-10  
100μA £2-10  
100-0-100μA £1-97  
200μA £1-97  
500μA £1-80  
500-0-500μA £1-80  
1mA £1-50  
1-0-1mA £1-50  
2mA £1-50  
5mA £1-50  
10mA £1-50  
50mA £1-50  
100mA £1-50  
150mA £1-50

10V D.C. £2-80  
20V D.C. £2-80  
50V D.C. £2-80  
150V A.C. £2-80  
300V A.C. £2-80  
8 Meter 1mA £2-87  
VU Meter. £2-95  
1 amp. A.C.\* £1-50  
5 amp. A.C.\* £1-50  
10 amp. A.C.\* £1-50  
20 amp. A.C.\* £1-50  
30 amp. A.C.\* £1-50

**"SEW" BAKELITE PANEL METERS**

Type MR.65. 3 1/2in. x 3 1/2in. fronts.

50μA £2-75  
50-0-50μA £2-75  
100μA £2-75  
100-0-100μA £2-60  
200μA £2-60  
500μA £2-37  
1mA £2-10  
5mA £2-10  
10mA £2-10  
50mA £2-10  
100mA £2-10  
1 amp. £2-10  
5 amp. £2-10  
10 amp. £2-10  
20 amp. £2-10  
30 amp. £2-10  
5V D.C. £2-10

10V D.C. £2-10  
20V D.C. £2-10  
50V D.C. £2-10  
150V A.C. £2-10  
300V A.C. £2-10  
8 Meter 1mA £2-27  
VU Meter. £2-37  
90mA A.C. £2-10  
100mA A.C. £2-10  
200mA A.C. £2-10  
300V A.C. £2-10  
1 amp. A.C.\* £2-10  
5 amp. A.C.\* £2-10  
10 amp. A.C.\* £2-10  
20 amp. A.C.\* £2-10  
30 amp. A.C.\* £2-10

50μA £2-85  
50-0-50μA £2-10  
100μA £2-10  
100-0-100μA £2-60  
200μA £2-60  
500μA £2-37  
1mA £2-10  
5mA £2-10  
10mA £2-10  
50mA £2-10  
100mA £2-10  
1 amp. £2-10  
5 amp. £2-10  
10 amp. £2-10  
20 amp. £2-10  
30 amp. £2-10

**SEW EDUCATIONAL METERS**

Type ED.107. Size overall 100mm x 90mm x 108mm.

50μA £4-50  
100μA £4-25  
1mA £2-97  
50-0-50μA £4-25  
1-0-1mA £2-97  
1A d.c. £2-97  
5V/50V d.c. £4-25

20V d.c. £2-97  
50V d.c. £2-97  
300V d.c. £2-97  
Dual range  
500mA/5A d.c. £4-25  
5V/50V d.c. £4-25

**EDGWISE METERS**

Type FE.70. 3 1/2 3/8in. x 1 1/2 3/8in. x 2 1/2 in. deep.

50μA £2-80  
50-0-50μA £2-97  
100μA £2-97  
100-0-100μA £2-75  
200μA £2-75

500μA £2-80  
1mA £2-87  
300V A.C. £2-87  
VU Meter. £2-87

**MARCONI TF142B DISTORTION FACTOR METERS.** Excellent condition. Fully tested. £20. Carr. 75p.

**TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE**



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R 1Ω-11.1 meg Ω, G Ranges ±1% 1Ω-11.1 HENRYs Ranges ±2% C 10pF-1110μmFd. 6 Ranges ±1% 1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2 in. £20. P. & P. 25p.

**COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES**

D.C. coupled. Band width 0-10 Kc/s. Part order. £25. Carr. £1-50.

**CLASS D WAVEFORMERS**

A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. £8-97 1/2. Carr. 37 1/2p. Or brand new £7-97 1/2. Carr. 37 1/2p.

**LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS**

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 6k Ω. Operation 200/250V. A.C. Supplied in perfect order. £12-50. Carr. 50p.

**MARCONI TF855 VIDEO OSCILLATORS**

0-5 mc/s Sine Square Wave £45. Carr. £1.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**

2 pF-2000 mFd 2 ohms 200 meg ohms. Also checks impedance, turns ratio, insulation. 200/250V. A.C. Brand New. £17-50. Carr. 37 1/2p.

**MARCONI TF195M BEAT FREQUENCY OSCILLATORS**

0-40 kc/s. £20. Carr. £1-50

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**

Operative over amazingly long distances. Separate call and press to talk buttons. 2-way connection, 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8-97 1/2. P. & P. 17 1/2p.

**Latest Catalogue**

Our latest edition giving full details of a comprehensive range of H.I.P.I. EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. (10's) 248 pages, fully illustrated and detailing thousands of items at bargain prices.



**SEND NOW!**  
● ONLY 37 1/2 p  
P & P 10p

G. W. SMITH & CO (RADIO) LTD.  
Also see next two pages

# SEMI-CONDUCTORS/VALVES

## BRAND NEW & FULLY GUARANTEED

TRANSISTORS				VALVES			
IN914	7p	AC187	30p	BY194	15p	0A2	88p
IN4001	1p	AC188	30p	BY126	15p	0B2	45p
IN4002	9p	AC177	30p	BY127	20p	0Z4	30p
IN4003	10p	AC118	25p	BZ110	40p	1L4	27p
IN4004	10p	AC119	25p	BZ111	35p	1R5	85p
IN4005	12p	ACY30	25p	BZ112	30p	1S6	25p
IN4006	15p	ACY21	25p	BZ113	25p	1T4	25p
IN4007	20p	ACY22	17p	MA490	97p	1U4	27p
IN4148	7p	ACY28	17p	ME481	1.25	1U5	50p
IN4054	22p	ACY40	15p	MFF102	42p	2D21	35p
2G301	20p	AD140	50p	MFF103	35p	3Q4	40p
2G302	25p	AD149	50p	MFF104	37p	3R4	40p
2G303	25p	AD191	37p	MFF105	40p	3V4	45p
2G305	30p	AD162	37p	NK7213	25p	6R4	40p
2G308	30p	AP114	25p	NK7214	15p	6U4	35p
2G309	30p	AP115	25p	NK7216	37p	6V4	45p
2G311	30p	AP116	25p	NK7217	40p	6X4	45p
2G374	27p	AP117	25p	NK7294	22p	5Z4G	40p
2G381	25p	AP118	25p	NK7291	27p	630L2	75p
2N398	15p	AP119	25p	NK7261	20p	6A7	25p
2N697	17p	AP124	25p	NK7212	25p	6A7G	40p
2N698	42p	AP126	17p	NK7272	25p	6AK5	30p
2N704	10p	AP127	17p	NK7271	25p	6AL5	30p
2N708	15p	AP130	30p	NK7275	25p	6AL5	20p
2N914	25p	AP178	47p	NK7278	25p	6AM3	30p
2N916	25p	AP180	47p	NK1281	27p	6AQ5	35p
2N918	27p	AP186	40p	NK1282	27p	6BE6	35p
2N929	25p	AP239	42p	NK7406	75p	6AT5	30p
2N930	25p	AS926	25p	NK7773	25p	6AT6	35p
2N1131	30p	BC119	10p	NK10459	85p	6BE6	30p
2N1132	35p	AS928	25p	0A5	20p	6RH6	45p
2N1302	30p	AS717	10p	0A4	10p	6R5	25p
2N1303	35p	AY110	97p	0A47	10p	6BQ7A	40p
2N1304	25p	BC119	10p	0A47	10p	6BR7	85p
2N1306	25p	BC107	12p	0A70	10p	6BR7	85p
2N1306	25p	BC108	12p	0A79	10p	6BR8	85p
2N1307	25p	BC119	10p	0A79	10p	6BR8	85p
2N1308	30p	BC113	10p	0A85	12p	6BR8	85p
2N1309	25p	BC116	10p	0A80	10p	6B7Z	25p
2N1613	25p	BC126	10p	0A91	7p	6C4	35p
2N1715	25p	AY110	97p	0A45	10p	6C4	35p
2N1889	35p	BC147	17p	0A200	10p	6CL6	50p
2N1893	50p	BC148	18p	0A202	10p	6CW4	65p
2N2147	75p	BC149	18p	0A210	17p	6E	60p
2N2180	40p	BC172	17p	0C139	87p	6E6G	60p
2N2183	47p	BC172	17p	0C20	97p	6F13	35p
2N2217	40p	BC177	25p	0C22	80p	6F14	35p
2N2218	30p	BC186	25p	0C23	60p	6F15	35p
2N2219	30p	BC182L	10p	0C24	60p	6E18	45p
2N2368	17p	BC184L	10p	0C25	87p	6E23	30p
2N2369	20p	BC212L	12p	0C26	25p	6E36	20p
2N2370	25p	BC213	12p	0C27	25p	6E36	20p
2N2484	35p	BCY31	30p	0C29	62p	6G5	20p
2N9613	30p	BCY32	30p	0C35	50p	6J5GT	30p
2N2464	50p	BCY33	30p	0C36	62p	6J5	25p
2N2904	30p	BCY34	30p	0C41	55p	6I7	45p
2N2923	17p	BCY38	40p	0C43	30p	6K8G	35p
2N2924	17p	BCY42	15p	0C44	17p	6L6GT	40p
2N2925	17p	BCY43	15p	0C45	17p	6L6D	50p
2N2926	15p	BCY44	15p	0C46	27p	6G7	40p
2N2927	15p	BCY45	15p	0C70	12p	68A7	40p
2N2929	15p	BCZ11	40p	0C71	15p	68Y7	35p
2N3033	35p	BD123	30p	0C72	15p	68Y7	35p
2N3034	40p	BD123	30p	0C73	30p	68K7	35p
2N3055	75p	BD124	30p	0C74	30p	68L7	35p
2N301A	30p	BF115	25p	0C75	25p	68N7	35p
2N3415	37p	BF116	25p	0C76	25p	68P7	40p
2N3670	15p	BF167	25p	0C77	40p	6U4	40p
2N3702	15p	BF173	30p	0C78	30p	6V6	25p
2N3703	15p	BF174	30p	0C79	30p	6V6GT	27p
2N3704	17p	BF181	37p	0C81D	30p	6X4	30p
2N3705	16p	BF182	32p	0C83	25p	6X50	30p
2N3706	22p	BF184	25p	0C84	25p	6X50GT	27p
2N3707	17p	BF185	25p	0C89	25p	10C2	10p
2N3708	17p	BF184	17p	0C140	17p	0E70	97p
2N3709	17p	BF195	15p	0C169	20p	10P12	55p
2N3730	15p	BF300	37p	0C170	25p	10P14	41.20
2N3711	15p	BF224	30p	0C171	30p	12AT6	30p
2N3819	15p	BF225	30p	0C200	40p	12AT7	30p
2N3903	20p	BF244	47p	0C201	80p	12AU7	30p
2N3904	25p	BFX11	22p	0C202	75p	12AX7	30p
2N3905	25p	BFX13	25p	0C203	40p	12AV6	30p
2N3906	30p	BFX29	30p	0C204	40p	12EA6	35p
2N4063	17p	BFX30	32p	0C205	62p	12EB6	35p
2N4069	25p	BFX44	37p	0C207	75p	12BH7	40p
2N4061	15p	BFX85	40p	0CP71	87p	19A45	35p
2N4062	22p	BFX86	32p	0RP13	60p	20D1	45p
2N4288	16p	BFX87	32p	0RP60	60p	20F2	75p
2N4287	17p	BFX88	25p	P346A	55p	20L4	41.10
2N4288	16p	BFY18	25p	PL4001	14p	20P1	50p
2N4289	17p	BFY20	62p	PL4002	15p	20P2	60p
2N4290	15p	BFY50	22p	PL4003	16p	20P4	41.10
2N4291	15p	BFY61	25p	PL4004	17p	20P5	41.20
2N4292	16p	BFY52	22p	PL4005	19p	25L6	45p
2N5354	37p	BFY90	67p	PL4006	20p		
2N5355	17p	BX119	17p	PL4007	24p		
2S102	17p	BX120	17p	T1843	40p		
2S103	37p	BX121	37p	T1844	12p		
2S104	37p	BX178	15p	T1845	17p		
40550	55p	BSY28	15p	T1846	17p		
40581	55p	BSY27	15p	EC107/8/9			
40582	60p	BSY28	17p	25 + 10p			
AC107	37p	BSY38	20p	100 + 8p			
AC126	25p	BSY39	20p	100 + 7p			
AC127	25p	BSY61	32p	23N0556			
AC128	25p	BSY66	30p	25 + 8p			
AC164	15p	BSY96A	15p	100 + 5p			
AC176	25p	BY100	15p				

### THYRISTORS

FIV	50	100	200	300	350	400
1A	25p	27p	37p	40p	—	47p
3A	80p	87p	40p	45p	—	50p
5A	—	55p	85p	—	—	75p
7A	—	55p	85p	70p	—	97p

### ZENER DIODES

300mv. (3.3 to 33v) 15p; 1.5 watt (2.4 to 40v) 20p; 40 watt (3.9 to 100v) 25p.

### INTEGRATED CIRCUITS

L909 40p; L914 40p; L933 60p; IC-10 25.50; SL403 \$2.25; MC1303 \$2.62; MC1304 \$2.75; PA246 \$2.45; CA3005 \$1.17; CA3011 74p; CA3092 \$1.65; FCH131 50p; FCH181 50p; FCH141 25p; FJH171 25p; FJH181 25p; FJH221 25p; FJH231 25p; FJH241 25p; FJH251 25p; FJH261 25p; FJH271 25p; FJH281 25p; FJH291 25p; FJH301 25p.

# HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE  
SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



# GARRARD

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

- 40 Mk II stereo \$3.40 SL72B \$28.97
- 2028T/C stereo \$3.87 AP76 \$30.97
- 3000 stereo \$10.50 SL75B \$28.50
- SP25 Mk III \$11.75 406B \$28.50
- SL63B \$14.97
- Carriage 50p extra each item.
- TEAK PLINTHS & PERSEF COVERS
  - 1. For SP26, SL65, SL65, 3000, 2025 T/C 2025, 1000. \$3.97.
  - 2. For AP76, SL75, SL95. \$5.97.
  - 3. For SP23 etc. to operate with lid in place \$5.97. Carriage 37p extra type. Full range of Garrard accessories available.




### SPECIAL OFFERS!

Garrard SP25 MK III fitted Goldring G800 cartridge and wooden plinth and plastic cover. Ready wired. Total list price \$35.  
OUR PRICE \$20.95 Carr. 60p

GOLDRING G800/2 Attad Goldring G800 cartridge complete with deluxe base and cover. Total list price \$20.80.  
OUR PRICE \$13.99 Carr. 50p

### TELETON SPECIAL OFFER!

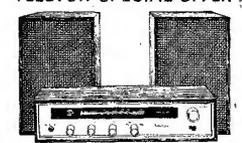

GR10T AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR SA1003 SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception. A.F.C., built-in M.F.X. Cee/X-TAL. Input. Total list \$59.25. OUR PRICE \$29.95. Carr. 62p.

B.S.R. McDONALD  
MP60 \$11.95 \$10 \$16.95  
\$10 \$12.95 \$10 \$18.95  
Carriage 37p extra each item

### GOODMANS SPECIAL OFFERS!

MAXAMP 30 Stereo Amplifier 15 + 15 watt r.m.s. with matching STEREO MAX AM/FM Tuner. Total list price \$39.95.  
OUR PRICE \$29.95 Carriage \$1

### GOODMANS SPEAKERS!

MAXIMS OUR PRICE \$38.60 pr. Carr. 50p.  
MINISTERS OUR PRICE \$39.97 pr. Carr. 50p.  
MEZZO III OUR PRICE \$25.50 pr. Carr. 50p  
MAGNUM 22, task. OUR PRICE \$33.00 each Carr. 50p  
MARMOR, task. OUR PRICE \$38.50 pr. Carr. 50p  
MARIMBA OUR PRICE \$35.00 pr. Carr. 50p.  
MAGISTER OUR PRICE \$41.50 each Carr. \$1

### TAPE CASSETTES

Top quality in plastic library boxes.  
C90 60 min 48p. 3 for \$1.22.  
C90 90 min 62p. 3 for \$1.86.  
C120 120 min 75p. 3 for \$2.17.  
Cassette Head Cleaner 50p. Post Extra.

### HOSIDEN DHO45 2-WAY STEREO HEADSETS

Each headphone contains a 2 1/2 in. woofer and a 1 in. tweeter. Built in individual level controls. 8 Ohm imp. 25-18,000 cps with cable and stereo plug. \$5.97 P. & P. 13p.

### TELETON SAQ-206 STEREO AMPLIFIER

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal. aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. Rec. List \$29. OUR PRICE \$19.97 Carr. 37p.

### AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities.  
5in. 225ft. L.P. acetate ..... 17p  
3 1/2in. 600ft. T.P. mylar ..... 50p  
5in. 600ft. std. plastic ..... 75p  
5in. 900ft. L.P. acetate ..... 50p  
5in. 1,200ft. D.P. mylar ..... 75p  
3 1/2in. 1,200ft. L.P. acetate ..... 62p  
3 1/2in. 1,500ft. L.P. mylar ..... 30p  
5in. 1,500ft. D.P. mylar ..... \$1.12  
3 1/2in. 2,400ft. T.P. mylar ..... \$1.97  
7in. 1,200ft. std. acetate ..... 62p  
7in. 1,500ft. L.P. acetate ..... 75p  
7in. 1,800ft. L.P. mylar ..... \$1.00  
7in. 2,400ft. D.P. mylar ..... \$1.25  
7in. 3,600ft. T.P. mylar ..... \$2.25  
Postage 10p. Over \$3 post paid.

### TE-1085 STEREO HEADPHONES

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY \$1.97. P. & P. 12p.

### SINCLAIR EQUIPMENT

Project 60. Package offers.  
2 x Z90 amplifier, stereo 60 pre-amp, PZ5 Z90 power supply. \$16.75 Carr. 37p.  
Or with PZ6 power supply \$18.95 Carr. 37p.  
2 x Z50 amplifier, stereo 50 pre-amp, PZ6 power supply. \$20.25 Carr. 37p.  
Transformer for PZ8. \$2.97 extra.  
Add to any of the above \$4.97 for active filter unit and £12 for a pair of Q15 speakers.  
Project 60 FM Tuner \$20.97. Carr. 37p.  
All other Sinclair products in stock.  
2000 Amplifier \$2

**RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES**

5 MHz Pass Band, Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 milli sec/cm. Supplied complete with all accessories and instructions E87. Carr. paid.



**MARCONI T/44/TF956 AF Absorption Wattmeter**  
1 1/2 watts to 6 watts.  
220 Carr. £1.

**TE111. DECADE RESISTANCE ATTENUATOR**

Variable range 0-111dB. Connection Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB - 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.65dB. Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new, £27.50. P. & P. 25p.

**BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR**

Size 18-200,000 Hz. Square 18-50,000 Hz. Output max. 10 dB (10 K ohms) Operation in battery. Attractive 2-tone case 7 1/2 x 5 x 2 1/2. Price £17.50. Carr. 17p.

**TE-16A Transistorised Signal Generator**. 5 ranges 400KHz - 30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. 400KHz to 100 KHz. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. £7.97. P. & P. 20p.

**BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR**

New high quality portable instrument. Size 1 1/2 x 4 1/2 x 100 KHz. Square 20 Hz to 20 KHz. Output max + 10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price £27.50. Carr. 25p.

**TE-40 HIGH SENSITIVITY A.C. VOLTMETER**

10 meg. input 10 ranges: 0.1/0.001/1/5/10/30/100/300V. R.M.S. 400-12 Meg. Decibels -40 to +80dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.50. Carr. 25p.

**TE-65 VALVE VOLTMETER**

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistances up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional probes available: R.F. £9.12; H.V. £9.50.

**MULTIMETERS for EVERY purpose!**

**TECH PT-34**. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100K. £1-97. P. & P. 12p.

**HONOR TE-10A**. 20K Ω Volt 0/5/50/500/5,000 v. D.C. 10/50/100/500/1,000 v. A.C. 0/50mA/2.5mA/250mA D.C. 0/60K/6 meg. ohm. -20 to +42 dB. 10-0-100 mfd. 0/100-0.1 mfd. £3-47. P. & P. 15p.

**MODEL TE-200** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000 V.D.C. 0/10/50/250/1,000 V.A.C. 0/50 mA/250 mA. 0/60K/6 meg Ω. -20 to +42 db. £5-75. P. & P. 15p.

**MODEL 500** 50,000 O.P.V. with overload protection. mirror scale 0/5/2-5/10/25/100/250/500/1,000V. D.C. 1/2-5/10/25/125/500/1,000V. A.C. 0/50mA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω. £5-97. Post paid.

**MODEL TE-70** 30,000 O.P.V. 0/3/15/60/300/600/1,200V. D.C. 0/6/30/120/300/1,200V. A.C. 0/30mA/3/30/60/300mA. 12 amp. D.C. 0/60K/6 Meg Ω. £3-17.50. P. & P. 15p.

**MODEL TE-90** 50,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/600/1,200 v. D.C. 0/6/30/120/300/1,200 v. A.C. 0/30mA/60/300mA. 12 amp. D.C. 0/60K/6 Meg Ω. -20 to +42 db. £7-50. P. & P. 15p.

**MODEL TE-100** 100K Ω Volt. 5in. mirror scale. Built-in meter protection 0/5/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. A.C. 0/10mA/6/30/300mA/12 amp. 0/2K/200K/2M/20M Ω. -20 to +17 dB. £12.50. P. & P. 17p.

**MODEL AS-100D**. 100K Ω Volt. 5in. mirror scale. Built-in meter protection 0/5/12/60/300/600/1,200 v. D.C. 0/6/30/120/300/600 v. A.C. 0/10mA/6/30/300mA/12 amp. 0/2K/200K/2M/20M Ω. -20 to +17 dB. £12.50. P. & P. 17p.

**MODEL 5025**. 57 Ranges. Giant 5 1/2 in. Meter. Polarity Reverse Switch. Sensitivity: 50K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 1.25, 2.5, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +81.5 dB. £8-97. P. & P. 17p.

**MODEL 5025**. 57 Ranges. Giant 5 1/2 in. Meter. Polarity Reverse Switch. Sensitivity: 50K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 1.25, 2.5, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2 K, 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +80 db. £12.50. P. & P. 17p.

**MODEL TE-12**. 0/100 O.P.V. 0/10/50/250/500/1,000/1,200/3,000/6,000V. D.C. 0/6/30/120/300/600/1,200V. A.C. 0/60mA/6/60/300/600mA. 0/6K/60K/600K/60 Meg Ω. 0/2mfd. £5-97. P. & P. 17p.

**MODEL 5025**. 57 Ranges. Giant 5 1/2 in. Meter. Polarity Reverse Switch. Sensitivity: 50K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 1.25, 2.5, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2 K, 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +80 db. £12.50. P. & P. 17p.

**MODEL 5025**. 57 Ranges. Giant 5 1/2 in. Meter. Polarity Reverse Switch. Sensitivity: 50K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 1.25, 2.5, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2 K, 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +80 db. £12.50. P. & P. 17p.

**MODEL 5025**. 57 Ranges. Giant 5 1/2 in. Meter. Polarity Reverse Switch. Sensitivity: 50K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 1.25, 2.5, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2 K, 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +80 db. £12.50. P. & P. 17p.

**FTC-401 TRANSISTOR TESTER**

Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £5-97. P. & P. 15p.

**75° WIDE ANGLE 12A METERS**


MW1-6 60mm square £8-97  
MW1-8 80mm square £9-97  
P. & P. extra



**UNR-30 RECEIVER**  
4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. £16-75. Carr. 37p.

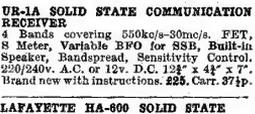**WS8 TRANCEIVERS**

Large quantity available for EXPORT! Excellent condition. Enquiries invited.



**UR-1A SOLID STATE COMMUNICATION RECEIVER**  
4 Bands covering 550kc/s-30mc/s. FET, 8 Meter, Variable BFO for SSB, Built-in Speaker, Bandspread, Sensitivity Control. 250/240V. A.C. or 12V. D.C. 12" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

**LAFAYETTE HA-800 SOLID STATE RECEIVER**

General coverage 150-400kc/s. 850 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable BFO, noise limiter. 8 Meter. Bandspread. RF Gain. 15" x 9 1/2" x 8 1/2". 250/240V. A.C. or 12V. D.C. Brand new with instructions. £45. Carr. 50p.

**LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER**

8.5-4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54 mc/s. Dual conversion, 2 mech. filters, product detector, variable BFO, 8 Meter, 100KΩ calibrator. 220/240V. A.C. or 12V. D.C. 15" x 9 1/2" x 8 1/2". Brand new with instructions. £57.50. Carr. Paid. (100kc/s. Crystal £1.97) extra.)

**FULL RANGE OF TRIO EQUIPMENT IN STOCK**

**EDDYSTONE VHF RECEIVERS** Model 770R 150-165 Mc/s. Excellent condition. £150  
**VOLTAGE STABILISER TRANSFORMERS** 180-230V. Input. Output 230V. Available 150w or 225w. £12-50. Carr. 25p.

**AUTO TRANSFORMERS**

6/115/230V. Step up or step down. Fully shrouded.  
150 W. £8-97. P. & P. 17p  
300 W. £8-25. P. & P. 22p  
500 W. £9-71. P. & P. 32p  
1000 W. £7-25. P. & P. 37p  
1500 W. £8-97. P. & P. 42p

**SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS**

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20V-230V. Model MR 2305 5 amp. 68 x 46 x 43mm £8-97. Model MR 2310 10 amp. 90 x 65 x 60mm £11-97. Postage 12p.

**POWER RHEOSTATS**

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/2 in. dia. shafts. Bulk quantities available.  
25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 72p. P. & P. 7p.  
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, £1.05 P. & P. 7p.  
100 WATT. 16/10/35/50/100/250/500/1000 or 2500 ohms, £1-97. P. & P. 7p.

**"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS**

Excellent quality. Low price. Immediate delivery

MODEL S-280	MODEL S-200 B
General Purpose	Panel Mounting
Bench Mounting	
1 Amp	25-50
2.5 Amp	25-50
5 Amp	25-50
8 Amp	25-50
10 Amp	25-50
15 Amp	25-50
20 Amp	25-50

Special discounts for quantity

**230 VOLT A.C. 50 CYCLES RELAYS**

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots 450) Quantities available.

**G.W. SMITH & CO. (RADIO) LTD**

27 TOTTENHAM CT. RD LONDON, W.1 Tel: 01-636 3715  
3 Lisle Street, London, W.C.2 Tel: 01-437 8204  
34 Lisle Street, London, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1 1/2 DAY THURSDAY)

All Mail Orders to -  
11-12, Pocklington Green,  
London W.2  
Tel: 01-262 6562  
(Trade supplied)

# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 4in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.

## ADASTRA DOUBLE



5 stereo solid state amplifier housed in handsome cabinet veneered in natural teak. Size 11½ x 6 x 5½in. 10 Transistors—power output 5 watts peak per channel. 220-240v A.C. Output impedance 12 to 15 ohms (our Cowdrey speaker system eminently suitable). Smart blue escutcheon. £14.70. P. & P. 60np.

## ELF

An extension speaker of quality, 9 x 5½ x 3½in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm speaker. The baffle is half inch thick. A real bargain at £1.90. P. & P. 36np.



## SPEAKER MATCHING TRANSFORMERS

3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.

## VYNAIR


Widths from 40 to 54 in., 75np yd. off roll. P. & P. 10np, ¼ yard 40np. P. & P. 10np. Send 5np stamps for samples.

## MONO

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.
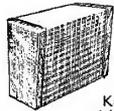
## CARTRIDGES

Stereo: Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output. £1.40. S106 High Output £1.40. Acos GP93 I Sapphire, £1.90. GP94 I Sapphire, £2. TA700 equivalent to B.S.R. SX1M, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.




## IMP

Wedge shaped extension speaker 7½ x 6½ x 4in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36np each

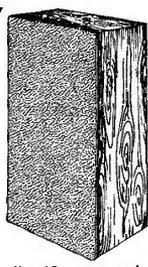
## THE SHELLEY

Size 21 x 11 x 6½in. An extremely elegant speaker system made of 12mm chipboard covered with teak leathercloth with mottled Vynair front. This unique system uses three ex TV speakers. Carefully matched and tested. Will handle 10 watts and will match 8 ohms impedance. If preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4.95 plus 70np P. & P. MATCHING TRANSFORMER for 15 ohms 80np post free.


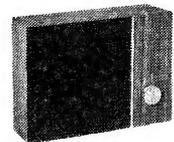
## CAXTON COLUMN

This is a column cabinet 23½ x 5½ x 5½in. deep finished in black or woodgrain cloth with blue or grey Vynair front. Keyhole slot for wall mounting. Fitted with three speaker units. 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at £2.95. P. & P. 57np each.



## THE FIESTA £2.95

P. & P. 36np. Brit. Isles. Fitted with 7 x 3 Speaker and Volume control. Teak veneered with Black Vynair.

## TRANSISTOR SPEAKERS

3 in. 35 ohm. 50np. P. & P. 7np.

## SPEAKERS

E.M.I. 13½ x 8in, 3 ohm £2.50, 15 ohm. P. & P. 30np. E.M.I. 3in tweeter 95np. P. & P. 10np. E.M.I. 13½ x 8in, fitted two 2½in. tweeters, 15 ohm £4.50. P. & P. 30np. E.M.I. 13½ x 8in, (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. E.M.I. Crossover 85np. P. & P. 5np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 70np. P. & P. 5np. Xtal lapel Mike, 40np. P. & P. 5np. Tel. P.U. 65np. P. & P. 5np.

## BROADWAY ELECTRONICS

(Nr. Tooting Broadway Underground Station) 92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984 (Closed all day Wednesday)

Your **STARTER QUESTION** is  
*"What is today's most useful electronics catalogue?"*

... and your **BONUS QUESTION** is  
*"What goes up and at the same time comes down?"*

**HOME RADIO**  
COMPONENTS CATALOGUE

**24-hour Phone Service Ring: 01-648 8422**

The answer to the Starter question is obvious—the ubiquitous HOME RADIO COMPONENTS CATALOGUE. You all got that right! And the answer to the Bonus question is—the same! May we explain "this most ingenious paradox?" The price is now 50 pence, but with each catalogue we now include 10 vouchers each worth 5 pence, when used as directed. This means that if you spend a quite modest sum in ordering components from us over a period the catalogue will have cost you *nothing*—bar 20 pence for post and packing. So then—for today's most useful electronics catalogue, 50p if you call and collect, or 70p if you send the coupon with a cheque or Postal Order. Join the winning team—act now!

**POST THIS COUPON with your cheque or postal order for 70 pence**

Please write Name and Address in block capitals.

Name .....

Address .....

.....

**HOME RADIO (Components) LTD.**  
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.




# LOOK!

**PRACTICAL!**

**VISUAL!**

**EXCITING!**

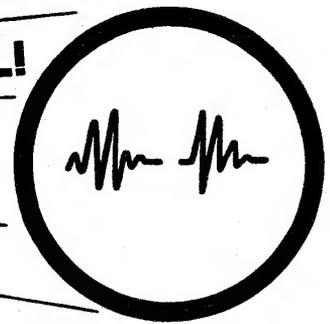


*a new 4-way method of mastering*

# ELECTRONICS

*by doing — and — seeing . . .*

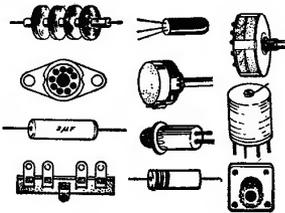
## 1 ▶ OWN and HANDLE a

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



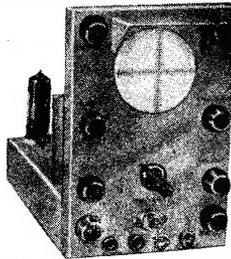
## 2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**


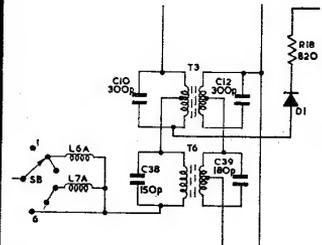
## 3 ▶ READ and DRAW and UNDERSTAND CIRCUIT DIAGRAMS



## 4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS .....PLEASE P.W.6

# PRACTICAL WIRELESS

VOL 47 NO 2

Issue 772

JUNE 1971

## TOPIC OF THE MONTH

### Not so Free!

THE long awaited White Paper on commercial local radio contained few real surprises but, for those viewing the advent of non-BBC local stations with concern, it carries some reassurances. The basic concept—given elsewhere in this issue in greater detail—is for the establishment of a 60-station network of stations under the aegis of the ITA (to be renamed the Independent Broadcasting Authority) in competition with 20 BBC local stations.

This, no doubt, disappointed the supporters of "free radio", the more extreme of which seemed to envisage a local station in every garden shed, a set-up not so much free as anarchistic. But the facts remain that if standards are to be preserved, the small local station serving up to 100,000 population would be lucky to break even.

The Minister of Posts and Telecommunications wasted little time in presenting his White Paper, following election pledges, but it is obvious that he saw clearly some of the dangers inherent in setting up local commercial radio. He therefore insists that local stations must offer a truly public service, that they must maintain high standards, not least in the provision of news and news commentary programmes, and that the programmes must maintain a wide appeal. It is obvious that he is aware of the lamentable standard of small budget stations in the USA. Consequently the first IBA stations will serve the large conurbations.

The matter of frequency allocation, however, strikes us as reeking of indecision. Transmissions will be on v.h.f./f.m. but with medium wave a.m. support. Ostensibly the reason for this is to permit as many listeners as possible to hear the new stations. Yet, in the White Paper itself, it is admitted that whereas m.w. coverage for the 60 stations would be 70% in daylight hours, this will drop to 25% at night! Therefore, for most people without v.h.f. receivers, their local radio station will vanish beneath the mush in the evenings. So, if they want to listen after dark they will *still* need to buy a v.h.f. receiver. This seems to be analagous to the situation with TV after the war when the decision was made to re-start on the outdated 405-line system instead of opting for a system more in keeping with the times—a change that *had* to be made, anyway, before many years.

Paragraph 9 in the White Paper, however, has its feet firmly on the ground. It points out that the IBA stations have a formidable challenge. They must bring in new listeners, yet they will not be able to provide for as broad a range of different audiences as can the BBC with its four national services and its local network. Formidable may be an understatement. We wish the IBA stations the best of luck. They will probably need it!

W. N. STEVENS—*Editor.*

## NEWS AND COMMENT

Leader	119
News . . . News . . . News . . .	120
Electronotes by <i>S. Ginsberg</i>	143
MW Column by <i>Charles Molloy</i>	147
Commercial Radio in Britain by <i>Halvor Moorshead</i>	148
On the Short Waves by <i>Malcolm Connah and David Gibson, G3JDG</i>	150
Practically Wireless by <i>Henry</i>	154

## CONSTRUCTIONAL

The "Carlton" Silicon Superhet Receiver by <i>Eric Dowdeswell</i>	122
X Two Heat Soldering Iron by <i>H. C. Bennett-Clark</i>	129
X Take 20, No. 26, Light Flasher by <i>Julian Anderson</i>	138
Simple Signal Generator by <i>R. F. Graham</i>	140
Electronic Ignition System by <i>S. Soar</i>	144
Crystal Band-Edge Marker by <i>A. S. Carpenter, G3TYJ</i>	157
Station Focus Six Receiver, Part 2 by <i>F. G. Rayer</i>	162

## OTHER FEATURES


X SERVICING—Part 2 by <i>G. J. King</i>	130
P.W. Prize Crossword	152
Going Back by <i>Colin Riches add Arthur Dow</i>	158
I.C. of the Month (Motorola MC 1335P) by <i>L. A. J. Ireland</i>	165

**JULY ISSUE WILL BE PUBLISHED  
ON JUNE 4th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

# NEWS... NEWS... NEWS...

## ITT Electronic Voltmeter

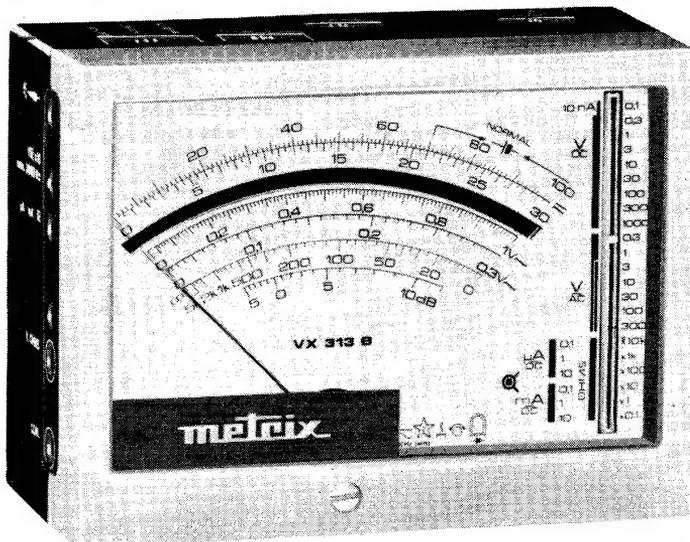

The VX313B electronic voltohmmeter nanoammeter has been introduced by ITT Metrix and is available from ITT Components Group Europe. The instrument makes extensive use of solid-state circuitry to achieve a compact size.

The VX313B can be used for measuring a.c. voltages up to 300V from 30Hz to 1MHz, d.c. voltages up to 1000V, d.c. currents up to 10mA and resistances up to 50 megohm. Equipped with a shock-proof taut band suspension centre pole meter movement, the VX313B is very sensitive. With the exception of the 0.1 and 0.3V

ranges (10 megohm input resistance) it features a constant 100 megohm input resistance on all d.c. ranges.

A full range of accessories is available including an r.f. probe for measurement of 0 to 30V, 10kHz to 50MHz a.c. voltages; crystal tees for measurements up to 1000MHz at 2V; and a 30kV e.h.t. d.c. probe. Current measurements from 5 to 150A can be made using 100mV and 300mV shunts, and 10 kilohm test probe leads are available for d.c. voltage measurements in r.f. circuits. ITT Electronic Services, Edinburgh Way, Harlow, Essex.

### Horsham A.R.C.

The above club has recently been revived after a lapse of 32 years. Meetings are held on the 1st. Wednesday of each month at the "Swan" in West Street, Horsham, Sussex.

Morse instruction is given every Monday and Friday at G3VPO (Chairman) Horsham 60216.

The Hon. Sec., R. J. Polley, G3PYC, 81 Beech Road, Horsham, would welcome ANY news of the original club or its members.

### Apollo Postscript

Is the interest in space exploration declining as it is generally believed? Viewing figures for Apollo 14 seem to challenge this. Intelsat, the international consortium whose satellites beamed the TV pictures of the flight around the world, say that an estimated 650 million looked in on the mission. In Britain alone, audiences ranging from 20 to 35 million saw highlights of the Apollo 14 Moon landing mission.

### "Vintage" QSL Card

D. H. Adams, Lecturer in charge of the Electrical Department, Barry College of Further Education, recently sent us a special QSL card. It commemorates a unique Vintage Radio occasion—the first transmission over water conducted by Marconi and Kemp.

Kemp's diary and photographs of Post Office technicians together with Marconi and some of his equipment are included on the card.

The Barry College of Further Education Radio Society GW3VKL commemorate the event annually by establishing a special station, GB3FI on Flatholm Island. This year they will be on the Island on Sunday 23rd. May, operating on all h.f. bands (10-160m) and 2m v.h.f.

For our "Going Back" enthusiasts, in May 1897, Marconi and Kemp conducted experiments in radio communication from Flatholm Island in the Bristol Channel, Lavernock Point (Glamorgan, Wales) and Brean Down (Somerset, England). During these tests, radio signals were transmitted for the first time across water and between two countries.

The station at Lavernock Point will be GW3VKL/P. G3XZW/P (Taunton and District A.R.C.) will be operating from Brean Down.

### H.A.C. Prices

H.A.C. Short Wave Products advise us that they have available a new price list, showing today's decimal prices for all products.

They are pleased to be able to assure readers, however, that they have made no increase whatsoever, and that their prices remain as previously. The two most popular kits, as advertised in our periodical are priced as follows: Model "DX" mark 2. ex works £3.30. Model "K" ex works £5.25.

### Shining Light

If you're interested, the table lamp and shade on this month's cover can be obtained from Gamages Ltd., High Holborn, London.

# NEWS... NEWS... NEWS...

Dynatron have been in negotiation with Olson Electronics of Akron, Ohio, U.S.A., for some time past culminating with a recent visit to the Dynatron Factory at Maidenhead by Mr. Sidney L. Olson, President, and the signing of a contract to supply several hundred of '90' Series, Model STA90, Tuner/Amplifiers for sale in his branches across the U.S.A.


The demand in many overseas markets is for audio equipment far more powerful than that normally acceptable by the U.K. buyer, output powers of 40 Watts per channel and above are considered normal.

Dynatron '90' Series fulfils this requirement with its 45 x 45 Watts output RMS and highly sophisticated tuner specification designed with both home and overseas markets in mind.

L. H. (Laurie) Skeet, Export Sales Executive for Dynatron, advises that he will be delighted to receive enquiries for both Direct and Personal Export and will ensure these receive his personal attention; he can be contacted on Maidenhead (0628) 23331, Extension 53.

The photograph illustrates the Standard Model STA90 priced at £165.

## USA Export Order for Dynatron

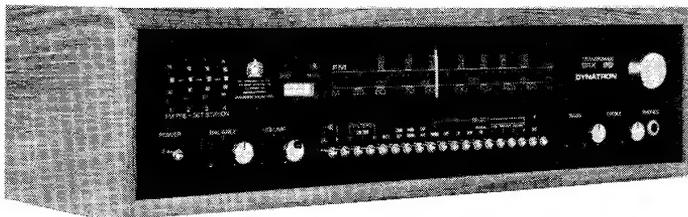

## A New I.C.

SGS announce the TBA651, a new linear circuit, which has been designed for use in high quality car radios and radio receivers. It combines the functions of an r.f. amplifier, oscillator, mixer and i.f. amplifier. As the device contains an internal voltage regulator, it can be operated with a supply voltage from 4.2-18 volts. The range of applications for the circuit is considerably increased by its ability to perform at a frequency up to 27MHz.

A typical S/N ratio of 26dB can be achieved for an input of 10 $\mu$ V.

This device is supplied in a 16 lead plastic split DIP Package. Technical Bulletin reference 108 is available covering this device. SGS (United Kingdom) Limited, Planar House, Walton Street, Aylesbury, Bucks.

## Soldering Kit

Antex announce their "SK2" kit which includes the following: 240 volts—15 watt miniature soldering iron fitted with  $\frac{3}{16}$ in. bit, 2 spare bits  $\frac{5}{32}$ in. and  $\frac{3}{32}$ , coil of cored solder, heat sink, 1A fuse and the booklet "How to Solder."

The new kit is presented in a polystyrene pack, protected by a cardboard sleeve. The booklet "How to Solder" is now printed in three languages and the kit is also available in 220 volts, 115 volts or 100 volts for sale on the European, American and Japanese markets.

The recommended retail price in the U.K. is £2.40. Anglo-Netherland Technical Exchange Ltd., Mayflower House, Plymouth, Devon.



## Bib's Latest



Two new additions to the BIB range of accessories are a stylus balance and cassette case.

The stylus balance, manufactured from non-magnetic alloy and fitted with a non-scratch base is calibrated to be accurate within  $\frac{1}{4}$  gram from  $\frac{1}{4}$  to 5 grams. Price is £1.80.

The cassette case is covered in hide-effect p.v.c. and holds 12 cassettes. The lid is held by a rotary fastener. Price is £1.50. Bib Division, Multicore Solders Limited, Hemel Hempstead, Herts.

## Do You Fancy a Bit?


A new design service for special purpose soldering bits has been introduced by Adcola Products Ltd. A new division has been formed to design and manufacture soldering bits to meet customers' requirements. Special purpose soldering bits can be manufactured in copper and can be iron-plated to provide long working life.

The service is equally suitable for small or large quantities and is complementary to the range of 70 standard soldering bits—copper and iron plated—produced by Adcola.

# THE 'CARLTON'

## A MODERN SILICON SUPERHET RECEIVER

ERIC DOWDESWELL

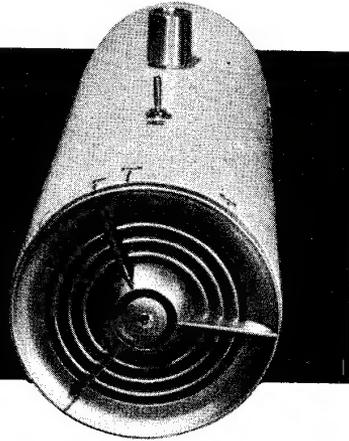

IT is surprising what good quality the average small portable transistor radio can provide if the output is fed into a speaker a bit larger in size than that in the set. For some time the author has used one of the imported tubular extension speakers which are quite cheap and consist of a 3in. speaker in a decorative tube with a long lead and plug.

As it was a bit of a bother to carry around the house both the set and the speaker it seemed to be an obvious solution to build a set into the speaker tube itself. The tube can easily accommodate a circuit board, battery and ferrite rod aerial without using up too much of the enclosed space which gives the speaker its pleasant tonal qualities.

Basically the circular plastic grille furthest from the speaker is used as a tuning dial with a wave-change switch and a volume control/on-off switch

brought through the top of the speaker tube.

The resulting complete radio set has proved very satisfactory, the quality usually provoking pleasant surprise from those that hear it.

### THE CIRCUIT

The circuit is a hybrid one using discrete transistors and an integrated circuit. The superhet, Fig. 1, uses three 2N2926G n.p.n silicon transistors in the mixer/oscillator and i.f. stages, the output being detected and fed to an MFC4000P integrated circuit audio amplifier or "gain block."

The MFC4000P was described in "IC of the Month" (PW, Sept. 1970) to which article reference can be made for detailed description of its operation. Briefly it contains six transistors, three diodes and three resistors but its outstanding feature is its small size,

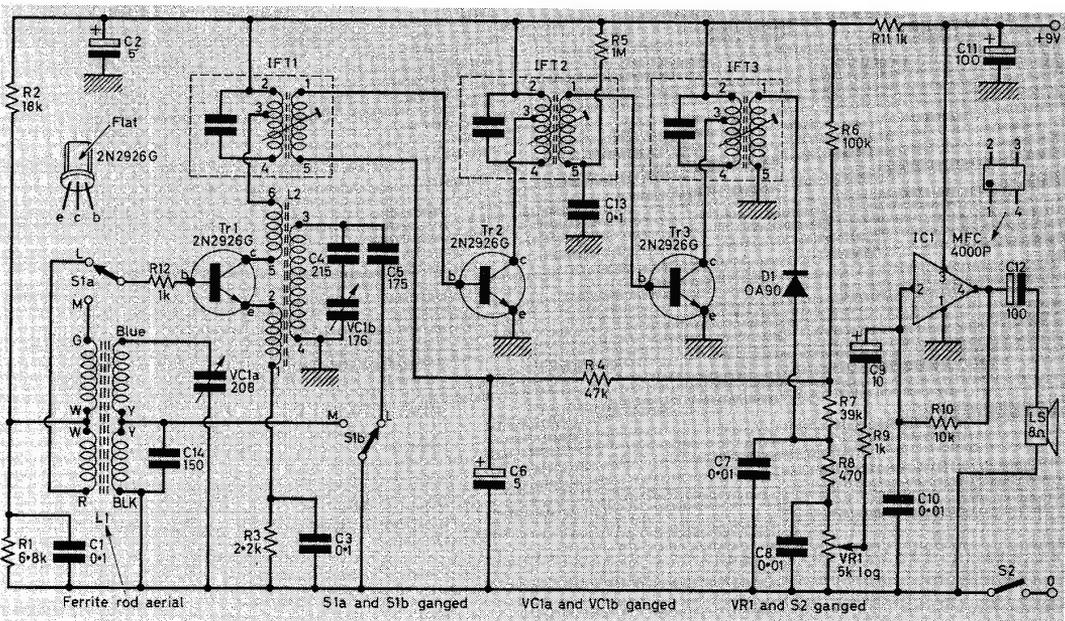


Fig. 1. Circuit diagram of the 'Carlton' receiver with lead-out connections of the transistors and integrated circuit.

being only approximately  $\frac{1}{4} \times \frac{1}{4} \times \frac{1}{8}$  in., with just four leadout wires.

A ferrite rod aerial L1 covers the medium and long wavebands the input and oscillator L2 circuits of Tr1 being tuned by the two-gang capacitor VC1a-b, the band being selected by S1a-b.

The output of the single-tuned i.f.t.1 is fed to the first i.f. amplifier Tr2 the gain of which is controlled by the voltage fed through R4 from the signal diode D1. Tr3 and i.f.t.3 form the second i.f. amplifying stage. Diode D1 has a small reverse bias applied to it to improve its efficiency at low signal levels. A further reference to this diode will be made later.

The low level audio signal from D1 goes to the volume control VR1 which feeds the integrated circuit IC1. R10 constitutes a feedback path which fixes the frequency response of the audio amplifier. The speaker is fed from the output of the i.c. via the blocking capacitor C12. It will be noticed that no audio transformers are required anywhere in this particular circuit.

## THE CONSTRUCTION

A piece of Veroboard holds the majority of the components, only the wavechange switch and the volume control/on-off switch being mounted on the tube. These are connected to the board with flexible

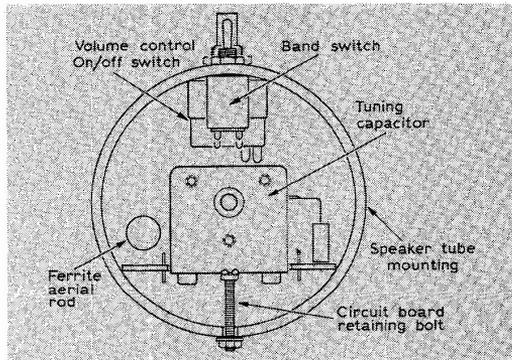


Fig. 2. Disposition of the circuit board and major components inside the speaker tube.

leads. The width of the board is fairly critical because when it is placed inside the tube the spindle of the tuning capacitor must be central in the tube since the end cap of the tube is used as the tuning dial, see Fig. 2.


The first step is to carefully remove the end cap from the speaker tube by easing it out slowly all round using the blade of a small screwdriver, avoiding any damage to the tube end. A hole  $\frac{1}{4}$  in. in diameter should be drilled in the centre of the cap to take the tuning capacitor spindle.

At this point it is a good idea to clean away any surplus glue or paper from around the inside edge of the tube using a round file and to check that the end cap is an easy fit inside the tube.

Cut a piece of plain Veroboard (0.15 x 0.15 in. matrix) slightly wider than the dimensions given in Fig. 3, trim the corners as shown and cut out the rectangular portion to accommodate the tuning capacitor. Attach the capacitor to the board by soldering the two tags on the rear (oscillator) section


to the two Veroboard pins C5 and M5, Fig. 3.

Place the board inside the tube so that the capacitor spindle is just projecting and then slide the end cap over the spindle. When the board is at the right height the end cap will just fit nicely into the tube. If the spindle is too high reduce the width of the board slightly until the cap fits in the tube as described. In practice, if the width given for the board is adhered to and the specified tuning capacitor used the height will be right first time.

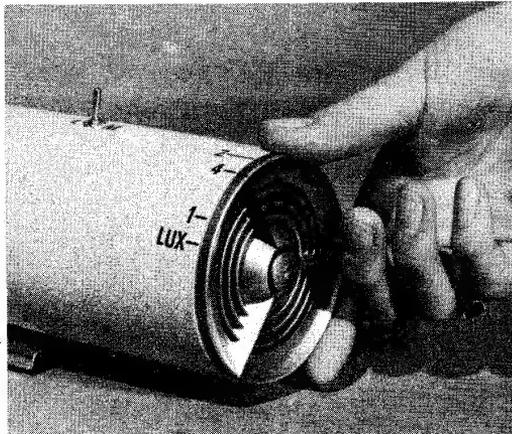

The end cap of the extension speaker becomes the tuning dial with appropriate station markings.

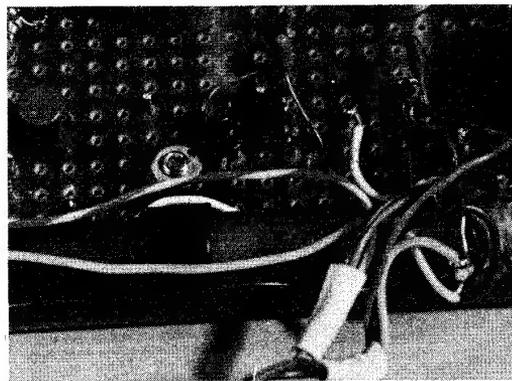The remainder of the Veroboard pins should now be inserted into the board using the proper insertion tool, supporting the board from the back to prevent it cracking, Fig. 3. The clearing holes for the i.f.t. and oscillator coil soldering lugs can be drilled easily, as they are just enlargements of existing holes, using a  $\frac{1}{8}$  in. diameter drill.



A close-up of the integrated circuit audio 'gain-block'. Its small size can be appreciated by comparing it with the 0.15 x 0.15 in matrix Veroboard.

The i.f.t.'s and oscillator coil can be fitted by pushing the lugs through holes in the board and bending over the screening can tags flat against the board. Note that all six lugs are present on the oscillator coil L2 the identifying red spot being between lugs 1 and 6.

Veroboard pins are used to support the transistors and the i.c., these components being soldered to the

pins only **after** all the wiring has been completed and checked.

Complete the wiring, Figs. 3 and 4, using bare 22 s.w.g. copper wire. The interconnections are so short and stiff that insulated wire is not necessary except in one or two places where wires cross close to each other. The connections to the ferrite rod aerial coils should be made with flexible wire, coloured as suggested, as it is necessary to move the coils along the rod during the alignment process.

Initially fix the coils at the ends of the rod with plastic tape.

The wires to the waveband switch and the volume control/on-off switch should be left long enough to enable these controls to be fitted to the top of the speaker tube, Fig. 5. Allow a couple of inches extra which can be trimmed off later.

Check and double check the wiring especially that to the bandswitch as the stage has now been reached when the transistors and the i.c. can be soldered into

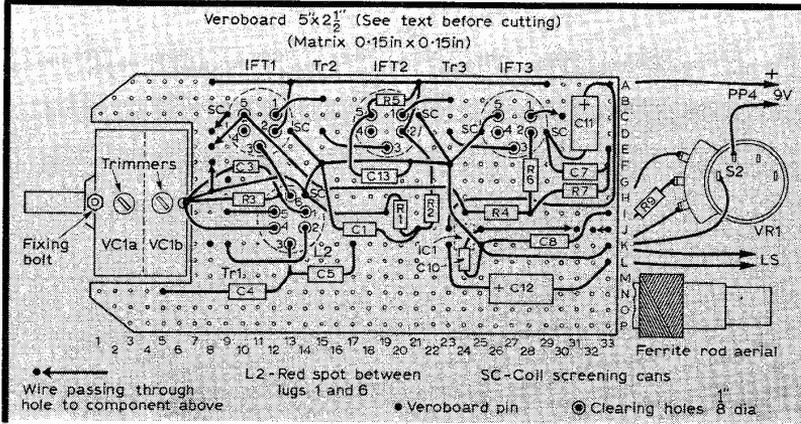


Fig. 3. Wiring diagram of the underside of the circuit board with interconnections to the volume control/on-off switch and speaker. Compare this with the photograph below showing the completed board. Note that the tuning capacitor is fixed to the board by soldering the lugs of the two sections to pins in the Veroboard.


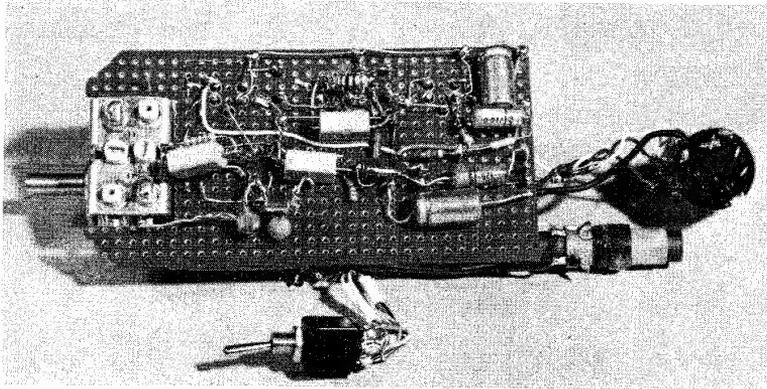


Fig. 4. Remainder of the wiring, on top of the circuit board. Connections to the ferrite aerial are made with flexible wire to permit the two coils to be moved along the rod for alignment purposes. The negative side of diode D1 goes to resistor R8. A photograph of this side of the circuit board appears on the next page.

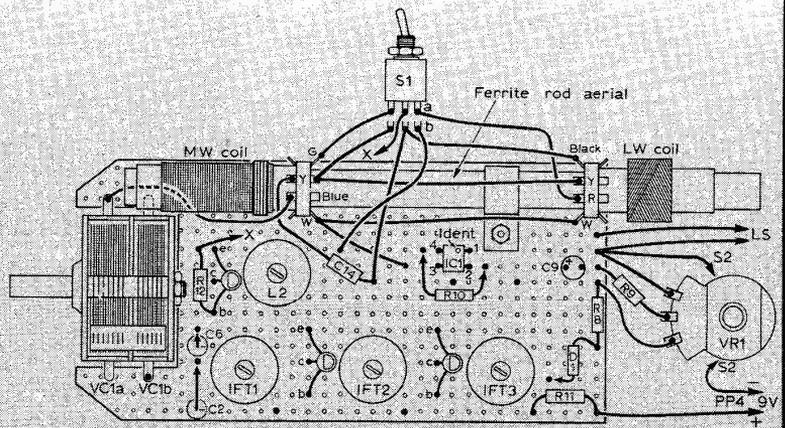

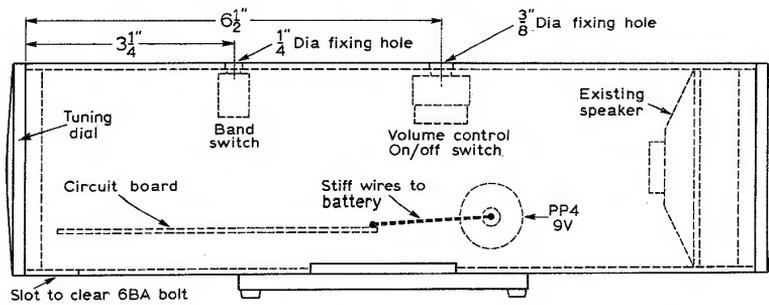


Fig. 5. This side view of the extension speaker shows the position of the volume control etc. in the prototype receiver. The flexible wires to the band-switch should be kept as short as possible. The PP4 battery is not suspended in mid-air, as it would appear, but rests on the curved sides of the tube.

position. With the transistors, grip all three leads with a pair of long-nosed pliers, close to the body of the transistor, then tin the ends of the leads. While still gripping the leads solder the ends to the appropriate pins making absolutely sure that the connections are right. See Fig. 1 for the lead-out connections. A hot soldering iron and speed are the essence of this operation.


With the i.c., tin each lead-out wire as with the transistors, using the pliers as a heat sink, then solder all four to the correct pins. Note that pin 1 is the identifying pin, see Fig. 4.

A 6BA bolt, 1in. long, has a flat filed on its head and it is then soldered to the centre earth tag underneath the tuning capacitor, Fig. 2. This bolt

Switch to the m.w. band and adjust the two trimmers on VC1a and VC1b to their mid-way positions. Set the tuning to the dial position for the local BBC4 station and adjust the core of oscillator coil L2 until the station is heard. Having got a signal tune each of the i.f.t.'s, beginning with i.f.t.3 and working forward, for best signal strength. Use only the proper trimming tool for these cores or damage will result.

Find a station such as Radio 1 on 247m. at the low end of the dial and adjust the trimmer on VC1a for best volume. Tune to a station at the top end, such as Radio 3, moving the m.w. coil along the ferrite rod for maximum signal.

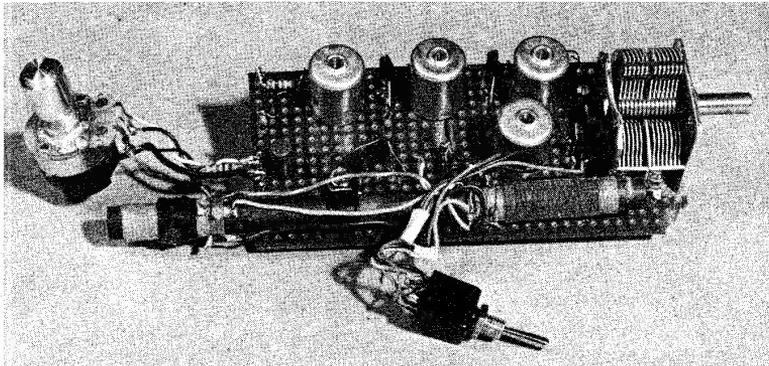Return to the low end of the band and adjust the calibration against a station of known wavelength,



fits into a slot in the bottom edge of the speaker tube where, with nuts and washers it retains the circuit board in its correct position in the tube, Fig. 5. The holes for the volume control and the bandswitch are drilled in the top of the tube, using Fig. 5 as a guide.

### THE ALIGNMENT

The existing long lead from the speaker is connected to the circuit board as shown in Fig. 4. Connect the battery terminal clips to the board with short stiff wires, the battery resting on the bottom of the tube, Fig. 5.

To assist in the alignment of the set a temporary dial drawn on stiff paper or card, Fig. 6, should be stuck to the front of the tuning capacitor and a pointer knob put on the spindle ensuring that minimum capacity coincides with left hand end of the dial markings.

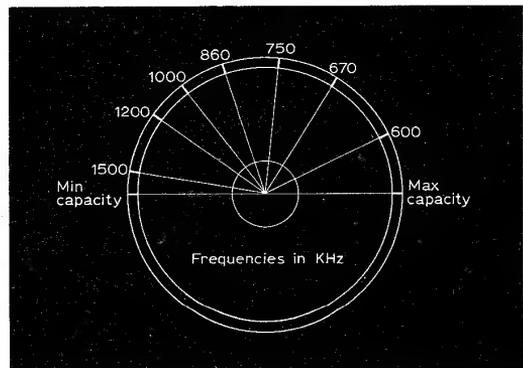


Fig. 6. Alignment of the finished receiver will be considerably facilitated by copying the above dial on to thin card and sticking it temporarily to the front of the tuning capacitor.

using the trimmer on VC1b.

Switch to the l.w. band and tune in Radio 2 on 1500m. and slide the l.w. coil along the ferrite rod for best results.

It is advisable to go over the alignment procedure once more after the set is working properly on both bands only this time use weak but steady signals for the alignment of the i.f. stages and the m.w. and l.w. coils on the ferrite rod. This will reduce any effect the a.g.c. may have on the apparent signal strength. In fact a voltmeter connected to the a.g.c. line will provide a much more precise means of alignment than the ear.

The set is now ready for final fitting to the tube. Remove the temporary dial and pointer. The circuit board can now be slid into the speaker tube, the control spindles manipulated into their respective holes and fitting the retaining nuts. The end grille, now the tuning dial, is fitted over the end of the tuning capacitor and into the end of the tube. The circuit board is adjusted until the end of the spindle is just flush with the dial. Tighten the nuts holding the 6BA bolt but do not overtighten as this will risk cracking the board. Remove the dial and put a small amount of Araldite or similar cement in the depression inside the dial, replace the dial on the spindle and leave overnight for the cement to set hard.

Turn the dial maximum anti-clockwise and mark a line across the edge of the dial and onto the tube

to indicate the high frequency end of the tuning range. Tune in the various BBC stations on m.w. and mark the tube accordingly. Do the same for Radio 2 on l.w. The complete dial markings are shown in the photographs. There is no reason, of course, why the markings should not be in wavelength or frequency or both. The bandswitch is marked to indicate its position for the m.w. and l.w. bands.

## NOTES

Although these tubular extension speakers are no longer imported there are many thousands in use and they can still be obtained in radio shops at around £1 each. The model used here is the TTC K3001 with plastic end caps but there is another model around that has pressed metal caps. If this model is used make quite sure that the end cap used for the dial is an easy rotating fit on the tube before glueing it to the tuning capacitor spindle.

Reference was made earlier to resistor R7, 39k $\Omega$  in the diode detector circuit. Its optimum value will depend upon the diode actually used. Once the set is working properly, switch it off, remove R7 and fit a 50k $\Omega$  potentiometer in its place on temporary wires. Switch on and adjust the value of the pot. for best quality of sound. The actual position is quite critical making a significant difference to the overall results. Switch off and remove the pot. from the circuit and measure the resistance of that part which was in circuit. Choose and solder in a fixed resistor as near as possible to that value.

Don't forget that since the set uses a ferrite rod aerial it will be highly directional and should always be turned to provide maximum signal strength. ■

## ★ components list

### Resistors

R1 6.8k $\Omega$	R7 39k $\Omega$ *
R2 18k $\Omega$	R8 470 $\Omega$
R3 2.2k $\Omega$	R9 1k $\Omega$
R4 47k $\Omega$	R10 10k $\Omega$
R5 1M $\Omega$	R11 1k $\Omega$
R6 100k $\Omega$	R12 1k $\Omega$

All  $\frac{1}{2}$ W 10%. \* See text  
VR1/S2 5k $\Omega$  log pot. with switch

### Capacitors

C1 0.1 $\mu$ F	C8 0.01 $\mu$ F
C2 5 $\mu$ F 12V	C9 10 $\mu$ F 12V
C3 0.1 $\mu$ F	C10 0.01 $\mu$ F
C4 215pF 5%	C11 100 $\mu$ F 12V
C5 175pF 5%	C12 100 $\mu$ F 12V
C6 5 $\mu$ F 12V	C13 0.1 $\mu$ F
C7 0.01 $\mu$ F	C14 150pF 5%

VC1a-b 208+176pF variable (Jackson Type 00)

### Semi-conductors

Tr1 2N2926G	Tr3 2N2926G
Tr2 2N2926G	D1 OA90
IC1 MFC4000P	

### Inductors

L1 Ferrite rod aerial m.w. and l.w. (Weyrad RA2W)
L2 Oscillator coil (Weyrad P50/1AC)
IFT1 IF Transformer (Weyrad P51/1)
IFT2 IF Transformer (Weyrad P51/2)
IFT3 IF Transformer (Weyrad P50/3V)

### Miscellaneous

Tubular radio extension speaker, type TTC Model K3001 or similar.  
Veroboard, plain, 5  $\times$  2 $\frac{1}{2}$ in. (see text) matrix 0.15  $\times$  0.15in.  
Veroboard pins.  
Battery 9V (PP4) and connectors.

# TELEVISION

## JUNE ISSUE

### BASIC TV CIRCUITS FOR THE CONSTRUCTOR

This month we start a new series on basic "building block" circuits for the constructor. A new circuit will be presented each month and the complete series will enable a high-quality monochrome TV receiver to be constructed. As the 405- and 625- line circuits are separate either a dual- or single-standard set can be built up. We start off with a three capacitor i.f. strip for the 405-line standard.

### ADDING AFC

Tuning on u.h.f. can drift for a number of reasons. The best answer is to add a.f.c. to your receiver. A practical add-on circuit is presented for controlling a varicap diode in the u.h.f. oscillator tuned circuit, with detailed instructions on setting up.

## ON SALE-MAY 22

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts.

from £1.70

*Sign here..!*

for your miniature soldering iron.


**SK2 Soldering kit**

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with 1/16" bit, 2 spare bits 5/32" and 3/32". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".



£2.40


**SK1 SOLDERING KIT**

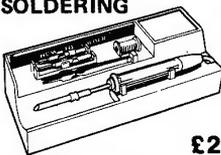

£2.75


In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted 1/16" bit. Spare bits 3/32" and 5/32". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder"

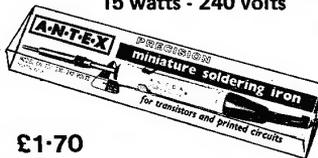**Model CN 240/2  
15 watts - 240 volts**



£1.70

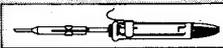Fitted with nickel plated 3/32" bit and packed in handy transparent box.



**Model G** - 18 watts. Fitted 3/32" bit. Spare bits 1/8", 1/16" and 1/4" available. For 240 or 220 volts. **£1.83**



**Model F** - 40 watts. Fitted 5/16" bit. Spare bits 3/32", 1/8", 1/16", 1/4" available. For 240, 220, 110, 20 volts. From **£2.38**

**Model E** - 20 watts. Fitted 1/4" bit. Spare bits 3/32", 1/8" and 1/16" available. For 240, 220 or 110 volts. From **£1.80**

**Model ES** - 25 watts. Fitted 1/8" bit. Spare bits 3/32", 1/16" and 1/4" available. For 240, 220 or 110 volts. From **£1.83**



**PRECISION MINIATURE SOLDERING IRONS**

Antex, Mayflower House, Plymouth, Devon. Telephone: Plymouth 67377/8. Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
  - Please send me the following
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

PW.5

**Fully guaranteed  
Individually packed  
VALVES**

B12H	£1.75p	ECH900	62p	OA2	35p
CY31	35p	ECL80	50p	OA5	12p
DAF96	35p	ECL82	35p	OA10	30p
DF96	37p	ECL86	65p	OA20	10p
DK96	41p	ECL88	40p	OA25	10p
DL92	32p	EF36	17p	OA30	10p
DL94	40p	EF37A	40p	OA35	10p
DL96	41p	EF39	45p	OA39	10p
DM70	30p	EF40	50p	OA40	10p
DY86	45p	EF41	60p	OA45	10p
DY87	55p	EF42	60p	OA47	10p
DY89	45p	EF43	47p	OA48	10p
ES80C/01	£1.35p	EF46	35p	OA49	10p
E180CC	45p	EF48	31p	OA50	10p
E181CC	45p	EF49	31p	OA51	10p
E182CC	45p	EF50	31p	OA52	10p
E183CC	45p	EF51	31p	OA53	10p
E184CC	45p	EF52	31p	OA54	10p
E185CC	45p	EF53	31p	OA55	10p
E186CC	45p	EF54	31p	OA56	10p
E187CC	45p	EF55	31p	OA57	10p
E188CC	45p	EF56	31p	OA58	10p
E189CC	45p	EF57	31p	OA59	10p
E190CC	45p	EF58	31p	OA60	10p
E191CC	45p	EF59	31p	OA61	10p
E192CC	45p	EF60	31p	OA62	10p
E193CC	45p	EF61	31p	OA63	10p
E194CC	45p	EF62	31p	OA64	10p
E195CC	45p	EF63	31p	OA65	10p
E196CC	45p	EF64	31p	OA66	10p
E197CC	45p	EF65	31p	OA67	10p
E198CC	45p	EF66	31p	OA68	10p
E199CC	45p	EF67	31p	OA69	10p
E200CC	45p	EF68	31p	OA70	10p
E201CC	45p	EF69	31p	OA71	10p
E202CC	45p	EF70	31p	OA72	10p
E203CC	45p	EF71	31p	OA73	10p
E204CC	45p	EF72	31p	OA74	10p
E205CC	45p	EF73	31p	OA75	10p
E206CC	45p	EF74	31p	OA76	10p
E207CC	45p	EF75	31p	OA77	10p
E208CC	45p	EF76	31p	OA78	10p
E209CC	45p	EF77	31p	OA79	10p
E210CC	45p	EF78	31p	OA80	10p
E211CC	45p	EF79	31p	OA81	10p
E212CC	45p	EF80	31p	OA82	10p
E213CC	45p	EF81	31p	OA83	10p
E214CC	45p	EF82	31p	OA84	10p
E215CC	45p	EF83	31p	OA85	10p
E216CC	45p	EF84	31p	OA86	10p
E217CC	45p	EF85	31p	OA87	10p
E218CC	45p	EF86	31p	OA88	10p
E219CC	45p	EF87	31p	OA89	10p
E220CC	45p	EF88	31p	OA90	10p
E221CC	45p	EF89	31p	OA91	10p
E222CC	45p	EF90	31p	OA92	10p
E223CC	45p	EF91	31p	OA93	10p
E224CC	45p	EF92	31p	OA94	10p
E225CC	45p	EF93	31p	OA95	10p
E226CC	45p	EF94	31p	OA96	10p
E227CC	45p	EF95	31p	OA97	10p
E228CC	45p	EF96	31p	OA98	10p
E229CC	45p	EF97	31p	OA99	10p
E230CC	45p	EF98	31p	OA100	10p

**TRANSISTORS, ZENER DIODES etc.**

SPECIAL OFFER	OC25	37p	OC200	37p	2N3054	95p	AD149	55p	BY213	20p
OC28	25p	OC201	47p	2N3055	75p	AD161	85p	BY216	65p	
OC30	25p	OC206	65p	2N3701	25p	AD162	85p	CR81/10	25p	
OC32	25p	IN21	17p	2N3711	25p	AF118	35p	CR81/20	37p	
OC39	25p	IN21B	25p	2N5102	25p	AF127	17p	CR81/30	37p	
OC45	12p	IN25	60p	40982	67p	AF189	37p	CR81/35	37p	
OC48	12p	IN24	10p	40983	67p	AF198	37p	CR81/40	37p	
OC49	12p	IN70	7p	3F100	67p	AF186	45p	CR83/05	30p	
OC70	12p	IN702-72369	3F155	32p	AFY191	112p	CR83/20	37p		
OC71	12p	IN746A	3N128	87p	ASY28	27p	CR83/30	45p		
OC72	25p	series 25p	2N139	£1.37p	ASY28	27p	CR83/50	45p		
OC73	30p	IN821A	£1.05	3N140	95p	ASY87	47p	CR83/05	25p	
OC74	10p	IN746A	3N128	87p	BAW19	27p	CR83/40	50p		
OC75	25p	IN822A	£1.30	3N154	90p	BC107	15p	GE115	50p	
OC76	25p	IZM7E	35p	3N159	£1.45p	BC107	15p	GE115	50p	
OC77	25p	IZM7E	35p	3F155	45p	BC108	15p	GE115	50p	
OC78	25p	OC81D	25p	12FR60	72p	BC113	8p	GE115	50p	
OC79	25p	OC81DM	25p	1ZT10	83p	BC118	7p	GE115	50p	
OC80	25p	OC82DM	15p	2C403	15p	BC138	25p	GE115	50p	
OC81	25p	OC83	25p	IN4785	55p	BC138	25p	GE115	50p	
OC82	25p	OC83B	15p	2N277	50p	BC138	25p	GE115	50p	
OC83	25p	OC84	25p	2N918	37p	BC138	25p	GE115	50p	
OC84	25p	OC85	25p	2N104	35p	BC138	25p	GE115	50p	
OC85	25p	OC86	25p	2N1308	25p	BC138	25p	GE115	50p	
OC86	25p	OC87	25p	2N1307	25p	BC138	25p	GE115	50p	
OC87	25p	OC88	25p	2N1307	25p	BC138	25p	GE115	50p	
OC88	25p	OC89	25p	2N1307	25p	BC138	25p	GE115	50p	
OC89	25p	OC90	25p	2N1307	25p	BC138	25p	GE115	50p	
OC90	25p	OC91	25p	2N1307	25p	BC138	25p	GE115	50p	
OC91	25p	OC92	25p	2N1307	25p	BC138	25p	GE115	50p	
OC92	25p	OC93	25p	2N1307	25p	BC138	25p	GE115	50p	
OC93	25p	OC94	25p	2N1307	25p	BC138	25p	GE115	50p	
OC94	25p	OC95	25p	2N1307	25p	BC138	25p	GE115	50p	
OC95	25p	OC96	25p	2N1307	25p	BC138	25p	GE115	50p	
OC96	25p	OC97	25p	2N1307	25p	BC138	25p	GE115	50p	
OC97	25p	OC98	25p	2N1307	25p	BC138	25p	GE115	50p	
OC98	25p	OC99	25p	2N1307	25p	BC138	25p	GE115	50p	
OC99	25p	OC100	25p	2N1307	25p	BC138	25p	GE115	50p	

**COLMOR ALL valves guaranteed**


5Y4G	35p	12K8GT	37p	5938	£1.12p
5Y4G	35p	12Q7GT	37p	6057	50p
5Y4G	35p	12R7GT	37p	6060	37p
5Y4G	35p	14S7	37p	6064	35p
6AB7	20p	19A4Q5	35p	6065	65p
6AC7	15p	19G3	£2.50p	9080	£1.37p
6AL6	57p	19G6	£1.00p	6146	£1.40p
6AK5	25p	19H4	£4.50p	8020	£1.75p
6AK8	32p	20P4	87p	9001	15p
6AL6	10p	20L6GT	37p	9002	22p
6AL6	10p	30C16	75p	9003	50p
6AM6	15p	30C17	80p	9004	12p
6AN8	60p	30C18	75p	9006	12p
6AQ5	30p	30P5	85p	C.R. Tubes	
6AL6	10p	30FL1	75p	VCR37	£4.50p
6B6GT	25p	30FL2	85p	VCR17B	£3.50p
6B7	32p	30FL3	46p	VCR17C	£7.50p
6B7GT	37p	30FL4	77p	5FP7	£1.32p
6B7	32p	30L15	80p	88D	£8.00p
6B7GT	37p	30L16	80p	88T	£9.00p
6B7GT	37p	30L17	80p	88L	£9.00p
6B7GT	37p	30L18	80p	88M	£9.00p
6B7GT	37p	30L19	80p	88N	£9.00p
6B7GT	37p	30L20	80p	88P	£9.00p
6B7GT	37p	30L21	80p	88Q	£9.00p
6B7GT	37p	30L22	80p	88R	£9.00p
6B7GT	37p	30L23	80p	88S	£9.00p
6B7GT	37p	30L24	80p	88T	£9.00p
6B7GT	37p	30L25	80p	88U	£9.00p
6B7GT	37p	30L26	80p	88V	£9.00p
6B7GT	37p	30L27	80p	88W	£9.00p
6B7GT	37p	30L28	80p	88X	£9.00p
6B7GT	37p	30L29	80p	88Y	£9.00p
6B7GT	37p	30L30	80p	88Z	£9.00p
6B7GT	37p	30L31	80p	88A	£9.00p
6B7GT	37p	30L32	80p	88B	£9.00p
6B7GT	37p	30L33	80p	88C	£9.00p
6B7GT	37p	30L34	80p	88D	£9.00p
6B7GT	37p	30L35	80p	88E	£9.00p
6B7GT	37p	30L36	80p	88F	£9.00p
6B7GT	37p	30L37	80p	88G	£9.00p
6B7GT	37p	30L38	80p	88H	£9.00p
6B7GT	37p	30L39	80p	88I	£9.00p
6B7GT	37p	30L40	80p	88J	£9.00p
6B7GT	37p	30L41	80p	88K	£9.00p
6B7GT	37p	30L42	80p	88L	£9.00p
6B7GT	37p	30L43	80p	88M	£9.00p
6B7GT	37p	30L44	80p	88N	£9.00p
6B7GT	37p	30L45	80p	88O	£9.00p
6B7GT	37p	30L46	80p	88P	£9.00p
6B7GT	37p	30L47	80p	88Q	£9.00p
6B7GT	37p	30L48	80p	88R	£9.00p
6B7GT	37p	30L49	80p	88S	£9.00p
6B7GT	37p	30L50	80p	88T	£9.00p

**INTEGRATED CIRCUITS—MANY OTHERS IN STOCK**  
 RCA, CA 3005 wide band R.F. Ampl. 300mW diss £1.25  
 CA 3012 wide band ampl. 150mW diss £1.10  
 CA 3020 Audio power ampl. £1.37  
 CA 3036 Audio pre-amp. £1.50  
 S.T.C. MIC 9201E Digital dual 4 input gates £1.50  
 MIC 709-L linear operational ampl. £1.50  
 MIC 9005D Highspeed flip-flop £2.70  
 General Electric PA 230 £1.12; PA 234 £1; PA 237 £1.87  
 Mullard TAA 300 £1.97; TAA 320 57p

**Colomr (Electronics) Ltd.**  
 170 GOLDHAWK ROAD, LONDON W12.  
 Tel: 01-743 0999  
 Open 9-12.30, 1.30-5.30 p.m. Thursday 9-11 p.m.

**METERS** Full List of our very large stock of meters on request.

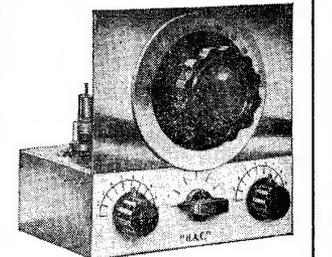**H.A.C. SHORT-WAVE KITS**  
**WORLD-WIDE RECEPTION**



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hazas, etc.

**NEW "DX" RECEIVER**  
 Improved one-valve model "DX" mark 2. Complete kit—price £3.30 (post & packing 20p). Customer writes: "Australia, India and America at loud volume. ... I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."  
 Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "R" plus (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

**"H.A.C." SHORT-WAVE PRODUCTS**  
 29 Old Bond Street, London W.1

**Fingers**

The more 'fiddly' the job, the more you depend on your finger-tips. Make sure minor burns and blisters don't rob them of their skill.

Apply BURNEZE, pronto! This unique scientific aerosol cools the heat out of a burn in just 8 seconds, anaesthetizes pain, reduces swelling. BURNZE - the clever tip for burnt finger-tips.

From chemists.

 **Potter & Clarke Ltd**  
 Croydon CR9 3LP

**LOOK AT THESE PRICES**

**CARTRIDGES**  
 Acos GP67-2, GP91-35C £1.12; Acos GP93-1 £1.35; Acos GP94-1 £1.68; Sonotone 9TACB £1.97; All above in makers cartons; BSR X4H £1.50.

**FS 2500 STEREO AMPLIFIER**  
 5 watts per channel; In attractive Cabinet, P.U. Radio & Tape inputs Tape output & Speaker outputs Dm. 12" x 5" x 3". Our Price £18.97.  
 SP25 MK3 £18.97.

**PLUGS & SOCKETS**  
 Phone plugs, assorted colours 41p; 45p per doz; Coaxial plugs, aluminium 7p; Coaxial couplers 7p; 2 pin DIN plug 15p; 3 pin DIN plug 15p; 5 pin DIN plug 17p; 2 pin, 3 pin & 5 pin DIN sockets 7p; Wandler plug 25p; sockets 21p; Banana plug 5p. Sockets 5p; 3.5mm J/Plugs 7p and 12p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 25p; Insulated J/sockets—o/cot 16p, c/cot 17p.

**ELECTROLYTIC CAPACITORS**  
 4uF 150V 4p; 8uF 500V 15p; 8uF 12V 4p; 8uF + 8uF 450V 21p; 10uF 150V 4p; 12uF 25V 4p; 16uF 450V 14p; 16uF + 16uF 450V 23p; 30uF 10V 4p; 50uF 10V 4p; 100uF 9V 4p; 100uF 12V 4p; 150uF 12V 4p; 330uF 9V 5p; 1500uF 30V 10p; 10uF 16V 7p; 5000uF 25V 50p; 10,000uF 25V 7p; 20,000uF 30V 10.05.

**MICROPHONES**  
 Acos Mic 45 £1.12; Acos Mic 60 99p; Planet CM70 £1.50; Hand Mike 75p.

**VALVES**  
 P781 80p; PCL82 80p; EF189 45p; EF184 45p.

PLEASE NOTE CHANGE OF ADDRESS  
**GEORGE FRANCIS (Dept PW),**  
 12-14, Middle Gate, Newark, Notts.  
 Telephone: Newark 4723.




# SOLDERING IRON

H. C. BENNETT-CLARK

**M**Y soldering iron was a nuisance. It was either too hot or too cold. Too hot if it had been left on, unused, and too cold when I had only just turned it on.


The solution is to leave it on the whole time but to reduce the power when it is standing by; one friend has a Variac specially for this job but who wants to tie up five quids worth of useful Variac in this way?

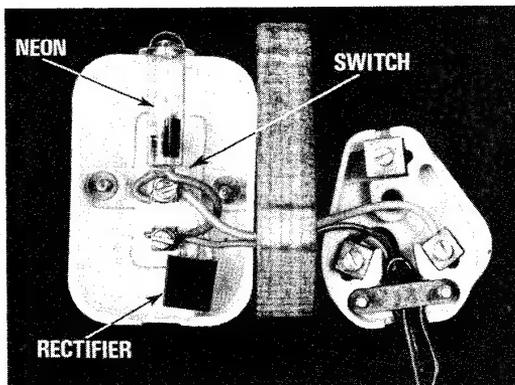My solution is to put a silicon rectifier in series with the soldering iron element (Fig. 1). As this cuts one half cycle, the power is halved when the switch is open and full power is produced by closing the



switch. The mains neon shows when the iron is on at half power.

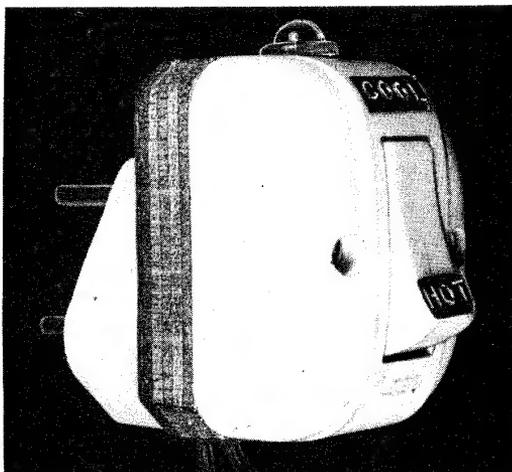Since the rectifier does not get hot, it can be mounted inside a suitable switch screwed on the back of the soldering iron mains plug. The Bakelite top of the plug is replaced by a block of  $\frac{1}{2}$  in. plywood



drilled to recess the terminal screws of the plug pins. Two wires pass through the plywood block: one goes from the live pin to one side of the switch and the other from the live side of the element to the other side of the switch. The neutral wire of the element is connected to the neutral plug pin. The rectifier and mains neon are connected across the switch. The mains neon is held in a groove filed in the switch housing. The switch is screwed to the wooden block and the plug is screwed to the other side.

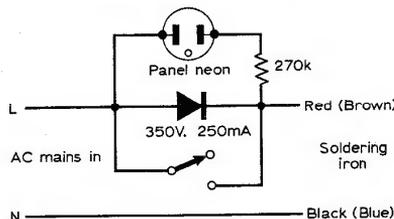


Fig. 1: The circuit of the two heat soldering iron.

When switched to "cool", the iron, a 25 watt Henley Solon, will melt solder and is ready for full scale soldering within about 10 seconds of switching to "Hot". The bit life, since the modification, has been much extended and the tip does not become covered in oxide.

The switch is a "VETO" from Woolworth's and, for the rectifier, any component with a 250mA 350V p.i.v. (or greater) rating that is small and cheap will do. A BY100 is ideal for this purpose.

Notice that I have not earthed my iron; this may not be strictly safe but I do not have disasters through soldering the "hot" end of a live circuit and, to me, this is worth the small risk. ■

## PSST! WANT TO BE AN AUTHOR?

A high proportion of the articles in *Practical Wireless* are submitted by readers who want their hobby to pay it's way (plus a good bit over). The Editor always welcomes articles from new authors; these should, if possible, be typewritten, double spaced and should conform generally, with regard to length and type, to existing articles. All circuits etc. are redrawn before publication but the originals should be as clear as possible. Photographs of the equipment are helpful but if this is difficult these can be done in our own studios. All components used must be available with the source of unusual items given.

All published material is payed for at attractive rates. Further information is available from the Editor.

# SERVICING

## AN INTRODUCTION TO FAULT-FINDING

### PART 2

G. J. KING

FOLLOWING THE INTRODUCTION OF THE SERIES BY H. W. HELLYER, CO-AUTHOR G. J. KING GUIDES THE READER THROUGH THE CIRCUITRY OF TYPICAL A.M. AND COMBINED A.M./F.M. RECEIVERS AS A NECESSARY PRELUDE TO ACTUAL SERVICING TECHNIQUES BEGINNING NEXT MONTH.

MY thanks to Mr. Hellyer for setting the stage, so to speak, allowing me to launch straight into basic circuitry and servicing techniques.

Radio receiver design has developed essentially into the following:

1. Relatively simple receiver
2. Radiogram
3. Hi-fi receiver or system.

### COMMON FEATURES

All have the common features of (i) the front-end which includes the frequency changer and sometimes an r.f. amplifier in front, (ii) the i.f. channel which feeds into the second detector and (iii) the audio channel which feeds into the speaker. When considering any circuit in electronics it is always desirable to break it up into sections or 'blocks', and this, for the basic radio receiver, is done in Fig.1.

Even the simplest of receivers has this sort of section make-up, with the more expensive ones carrying greater section detail. For example, a cheap a.m. portable has the ferrite rod aerial signal coupled straight into the frequency changer stage, which is commonly a single transistor stage performing the dual functions of mixing and local oscillator generation, while a more expensive f.m. model would be expected to have at least one r.f. amplifier stage and possibly two transistors for frequency changing, one working as the mixer and the other as the local oscillator. Moreover, the r.f. amplifier and possibly the mixer would be designed round field effect transistors (f.e.t.'s) rather than the ordinary type of bipolar transistor, such devices yielding improved linearity over bipolars, with a consequent improvement in the rejection of intermodulation components and hence spurious signals.

### FRONT-END BASICS

The front-end thus accepts the aerial signal and heterodynes this with the local oscillator signal to provide the required intermediate-frequency (i.f.) signal. The i.f. signal can be equal to the sum or difference between the local oscillator and the incoming signal.

The first makes the oscillator frequency higher than the incoming frequency by the i.f. and the second makes the oscillator frequency lower than the incoming frequency by the i.f. Either arrangement works equally well and both are found in practice, but the choice is sometimes based on the required tuning range and frequency band and the possibility of fundamental or harmonic radiation from the local oscillator affecting neighbouring radio and television receivers.

The simplest receiver, therefore, has two variably-tuned circuits at the front-end, one to tune the incoming signal and the other to tune the local oscillator so that over the tuning range this remains exactly out of step with the incoming signal tuning to yield the i.f. difference. This is where the front-end alignment comes in.

Receivers with one or more r.f. stages have an extra variably-tuned circuit for each stage. The number of front-end stages can thus be gleaned by counting the number of variable elements in the tuning gang. Simple sets have a two-gang capacitor, and more exotic models capacitors with three or, perhaps, four ganged sections. Sometimes there might be two r.f. stages tuned by a single gang (making three ganged sections in all). This is when the r.f. section consists of one tuned stage and one untuned stage. There are a few models with two r.f.

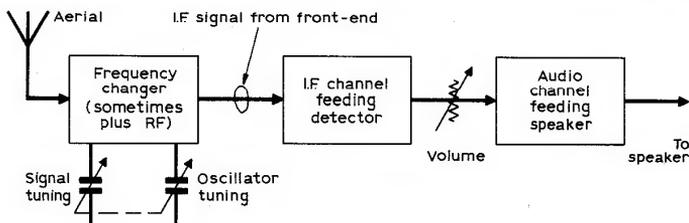



Fig. 1. The circuit of a basic superheterodyne receiver is broken up into blocks or sections to assist in the discussion of receiver circuitry.

# Build yourself a



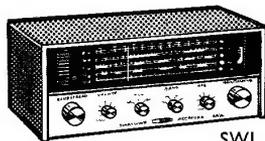
# great name HEATHKIT


You too can join the millions of satisfied Heathkit builders who have discovered the easy way to build better products than they could buy . . . have fun . . . and enjoy substantial savings in the process. Heathkit models are the beginner as well as the experienced man's first choice. Everything you need right down to the last nut and bolt is included in every kit. The wonderful step-by-step assembly manual is the last word in clarity. Want to know more . . . your first step is to send for the Free Heathkit catalogue and discover the unique satisfaction you can get from building the best.




SWL

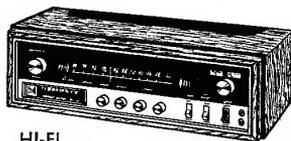

HI-FI

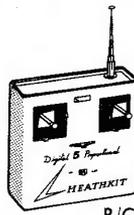

R/C

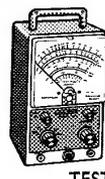

TEST



#### HOW TO BUY YOUR HEATHKIT

Orders for mail order dispatch from the factory may be placed at the London or Birmingham Heathkit Centres or by post to the Gloucester factory. Such orders are at 'direct-from-factory' prices which are lower than retail prices.

Goods may be purchased at the Heathkit Centres at retail prices.

Goods may be purchased at the Gloucester factory Showroom at 'direct-from-factory' prices.

**London Heathkit Centre**, 233 Tottenham Court Road.  
Open Monday to Saturday 9 a.m. — 6 p.m. Phone 01-636 7349.

**Birmingham Heathkit Centre**, 17-18 St. Martin's House, Bull Ring.  
Open Tuesday to Saturday 9 a.m. — 6 p.m. Phone 021-643 4386.

**Gloucester factory Showroom**, Bristol Road, Gloucester.  
Open Monday to Saturday 9 a.m. — 5 p.m.

Please send me FREE Catalogue

NAME .....

ADDRESS .....

51/6/71



A Schlumberger Company

**HEATH (GLOUCESTER) LTD.**  
GLOUCESTER GL2 6EE

**BRAND NEW GUARANTEED**

**SEMICONDUCTORS & COMPONENTS**  
SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA) IN U.K.

**RETURN OF POST SERVICE**

**TRANSISTORS**

2G301	80p	2N3403	22p	40390	32p	BC184	15p	BSX27	47p	NKT275	20p
2G302	80p	2N3404	22p	40310	45p	BC212L	13p	BSX28	32p	NKT281	27p
2G303	80p	2N3405	45p	40311	35p	BCY30	27p	BSX60	32p	NKT401	37p
2G304	41p	2N3411	22p	40312	47p	BCY31	30p	BSX61	32p	NKT402	30p
2G305	80p	2N3416	22p	40314	37p	BCY32	50p	BSX76	22p	NKT403	22p
2G309	80p	2N3416	37p	40320	47p	BCY33	25p	BSX77	27p	NKT404	62p
2G371	15p	2N3417	37p	40323	32p	BCY34	30p	BSX78	27p	NKT405	75p
2G374	30p	2N3570	11.25p	40324	47p	BCY38	40p	BSY10	27p	NKT406	62p
2G381	22p	2N3572	27p	40326	47p	BCY39	60p	BSY11	27p	NKT451	62p
2N404	22p	2N3605	27p	40329	80p	BCY40	60p	BSY24	15p	NKT452	62p
2N696	30p	2N3606	27p	40334	27p	BCY42	15p	BSY25	15p	NKT463	47p
2N697	20p	2N3607	22p	40347	77p	BCY43	15p	BSY26	17p	NKT603	32p
2N698	35p	2N3702	12p	40348	52p	BCY44	22p	BSY27	17p	NKT618F	32p
2N706	12p	2N3703	12p	40360	42p	BCY58	22p	BSY28	17p	NKT674F	32p
2N706A	12p	2N3704	17p	40381	47p	BCY59	22p	BSY29	17p	NKT707F	30p
2N708	15p	2N3705	15p	40382	77p	BCY60	27p	BSY32	35p	NKT715	30p
2N709	62p	2N3706	12p	40370	23p	BCY70	20p	BSY36	35p	NKT781	30p
2N718	25p	2N3707	15p	40406	47p	BCY71	42p	BSY37	35p	NKT10418	30p
2N726	30p	2N3708	09p	40407	27p	BCY72	17p	BSY38	22p	NKT10439	30p
2N727	30p	2N3709	10p	40408	52p	BCZ10	27p	BSY39	22p	NKT10439	30p
2N914	17p	2N3710	11p	40410	62p	BCZ11	42p	BSY40	22p	NKT10519	32p
2N916	17p	2N3711	11p	40478A	27p	BD116	11.25p	BSY61	32p		32p
2N918	30p	2N3715	22.50p	40485A	35p	BD121	65p	BSY62	32p	NKT2022	32p
2N929	22p	2N3716	22.50p	40600	57p	BD123	82p	BSY63	37p		47p
2N930	27p	2N3791	22.75p	AC107	30p	BD124	82p	BSY64	40p	NKT20339	32p
2N1090	22p	2N3819	35p	AC126	30p	BD181	75p	BSY66	40p		37p
2N1081	22p	2N3823	27p	AC127	25p	BD182	75p	BSY67	40p	NKT8011	27p
2N1181	25p	2N3824	27p	AC128	30p	BDY10	11.25p	BSY79	45p		37p
2N1132	25p	2N3854A	27p	AC184	27p	BDY11	11.25p	BSY82	52p	NKT80112	37p
2N1802	17p	2N3855	27p	AC176	25p	BDY17	11.25p	BSY90	57p		37p
2N1303	17p	2N3856	27p	AC178	25p	BDY18	11.25p	BSY92	52p	NKT80113	37p
2N1304	22p	2N3856	30p	AC188	27p	BDY19	11.25p	BSW41	42p		11.12p
2N1305	22p	2N3856A	35p	AC177	27p	BDY20	11.25p	BSW70	27p	NKT80211	37p
2N1306	25p	2N3858	35p	AC178	25p	BDY58	27p	C11	75p		32p
2N1307	25p	2N3858A	35p	AC179	25p	BDY59	27p	C42	27p	NKT80212	32p
2N1308	30p	2N3869	27p	ACY20	25p	BDY61	11.25p	C425	55p		32p
2N1309	30p	2N3869A	32p	ACY21	25p	BDY62	11.25p	C428	40p	NKT80213	32p
2N1507	17p	2N3860	30p	ACY22	25p	BDY65	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY66	25p	C428	27p	NKT80214	32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY67	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY68	25p	C428	27p	NKT80215	32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY69	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY70	25p	C428	27p	NKT80216	32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY71	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY72	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY73	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY74	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY75	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY76	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY77	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY78	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY79	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY80	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY81	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY82	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY83	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY84	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY85	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY86	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY87	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY88	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY89	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY90	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY91	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY92	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY93	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY94	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY95	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY96	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY97	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY98	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY99	25p	C428	27p		32p
2N1513	25p	2N3866	30p	ACY28	30p	BDY00	25p	C428	27p		32p

**TTL LOGIC I.C. NEW LOW PRICES**

	1-	25-	100-	1-	25-	100-
SN7400	24	99	499	SN7460	24	99
SN7401	24	99	159	SN7461	24	99
SN7402	25p	20p	18p	SN7462	25p	85p
SN7403	25p	20p	18p	SN7463	25p	85p
SN7404	25p	20p	18p	SN7464	25p	85p
SN7405	25p	20p	18p	SN7465	25p	85p
SN7406	25p	20p	18p	SN7466	25p	85p
SN7407	25p	20p	18p	SN7467	25p	85p
SN7408	25p	20p	18p	SN7468	25p	85p
SN7409	25p	20p	18p	SN7469	25p	85p
SN7410	25p	20p	18p	SN7470	25p	85p
SN7411	25p	20p	18p	SN7471	25p	85p
SN7412	25p	20p	18p	SN7472	25p	85p
SN7413	25p	20p	18p	SN7473	25p	85p
SN7414	25p	20p	18p	SN7474	25p	85p
SN7415	25p	20p	18p	SN7475	25p	85p
SN7416	25p	20p	18p	SN7476	25p	85p
SN7417	25p	20p	18p	SN7477	25p	85p
SN7418	25p	20p	18p	SN7478	25p	85p
SN7419	25p	20p	18p	SN7479	25p	85p
SN7420	25p	20p	18p	SN7480	25p	85p
SN7421	25p	20p	18p	SN7481	25p	85p
SN7422	25p	20p	18p	SN7482	25p	85p
SN7423	25p	20p	18p	SN7483	25p	85p
SN7424	25p	20p	18p	SN7484	25p	85p
SN7425	25p	20p	18p	SN7485	25p	85p
SN7426	25p	20p	18p	SN7486	25p	85p
SN7427	25p	20p	18p	SN7487	25p	85p
SN7428	25p	20p	18p	SN7488	25p	85p
SN7429	25p	20p	18p	SN7489	25p	85p
SN7430	25p	20p	18p	SN7490	25p	85p
SN7431	25p	20p	18p	SN7491	25p	85p
SN7432	25p	20p	18p	SN7492	25p	85p
SN7433	25p	20p	18p	SN7493	25p	85p
SN7434	25p	20p	18p	SN7494	25p	85p
SN7435	25p	20p	18p	SN7495	25p	85p
SN7436	25p	20p	18p	SN7496	25p	85p
SN7437	25p	20p	18p	SN7497	25p	85p
SN7438	25p	20p	18p	SN7498	25p	85p
SN7439	25p	20p	18p	SN7499	25p	85p
SN7440	25p	20p	18p	SN7500	25p	85p
SN7441	25p	20p	18p	SN7501	25p	85p
SN7442	25p	20p	18p	SN7502	25p	85p
SN7443	25p	20p	18p	SN7503	25p	85p
SN7444	25p	20p	18p	SN7504	25p	85p
SN7445	25p	20p	18p	SN7505	25p	85p
SN7446	25p	20p	18p	SN7506	25p	85p
SN7447	25p	20p	18p	SN7507	25p	85p
SN7448	25p	20p	18p	SN7508	25p	85p
SN7449	25p	20p	18p	SN7509	25p	85p
SN7450	25p	20p	18p	SN7510	25p	85p
SN7451	25p	20p	18p	SN7511	25p	85p
SN7452	25p	20p	18p	SN7512	25p	85p
SN7453	25p	20p	18p	SN7513	25p	85p
SN7454	25p	20p	18p	SN7514	25p	85p

**SILICON RECTIFIERS**

PV1
-----

transistors arranged in a cascade circuit which requires only one section of the tuning gang.

## TUNING SYSTEMS

Sometimes the tuning is accomplished not by ordinary capacitor sections but by either variable inductors or varactor capacitors. For tuning, of course, we require a combination of inductance and capacitance and to change the tuned frequency we can alter either the capacitance or the inductance. When the inductance is altered dust-iron cores are arranged to move inside the formers, these being mechanically linked with the tuning system.

Varactor tuning is a recent innovation and it is based on the change in capacitance which occurs between the elements of a semi-conductor diode when the reverse bias across it is altered. When a diode is in forward conduction there is no electronic demarcation between the p and n zones. However, in reverse biasing, a 'barrier' develops at the zone junction and the width of this increases as the reverse bias is increased. This is reflected as an increase in capacitance as the reverse bias is decreased, going into a short-circuit when the biasing changes from reverse to forward. Of course, the design is such that the biasing never goes forward (not normally, anyway; a fault condition resulting in this would put the whole of the front-end out of action).

Each circuit to be tuned (r.f., mixer and local oscillator) has its own varactor, which is the name given to junction diodes designed specifically to exploit the capacitance feature as efficiently as possible, the variable biasing for tuning coming from

a potentiometer geared to the tuning system.

Owing to the relatively small capacitance swing, varactor tuning is confined essentially to f.m. receivers, f.m. tuners and to the f.m. front-end of a.m./f.m. receivers. The a.m. section is almost always capacitively-tuned, even today.

Modern receivers commonly embody a v.h.f. (f.m.) front-end unit complete, which is often 'imported' in the form of a single unit. The a.m. section is then an integral part of the receiver design, using its own capacitors. To illustrate this, Fig. 2 shows a valve-type receiver with the tuning coupled to the gang on the left for a.m. and the screened unit adjacent, with its tuning mechanism also coupled to the main drive, for v.h.f. f.m.

A more advanced version is shown in Fig. 3, which is the Swedish Sonab R7000 receiver. This is all-transistor, f.m. only and uses varactors for tuning

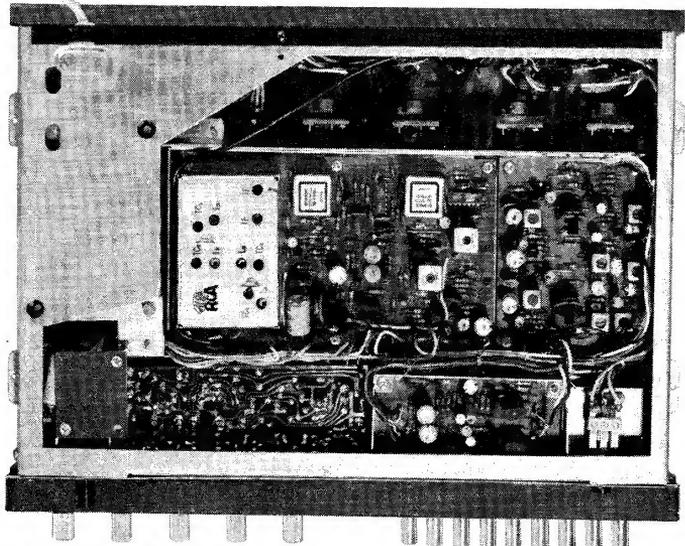


Fig. 3. A view of the Sonab R7000 receiver, for f.m. only. All tuning is by varactors, the complete tuning unit being contained in the large screened box at the left.

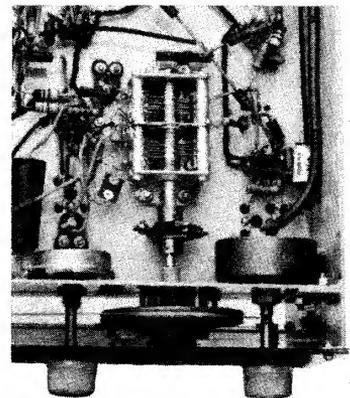
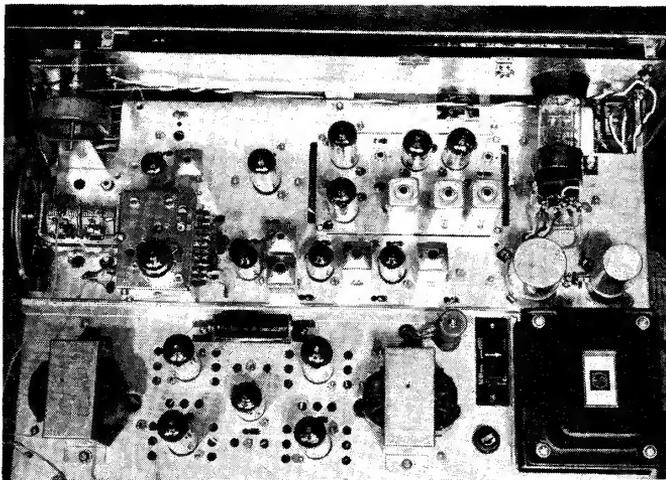


Fig. 2. In this receiver the main f.m. tuning mechanism is coupled to the gang capacitor at the left, used in the a.m. channel. Fig. 4. (above) shows a simple two-gang capacitor in a home-made v.h.f. tuner.

which are biased simultaneously for the correct capacitance by a potentiometer. The self-contained v.h.f. f.m. section (with varactors) constitutes the screened unit on the left-hand side.

An earlier v.h.f. f.m. tuner is shown in Fig. 4. This home-made set is seen to employ capacitor tuning, one section being for the mixer input and the other for the local oscillator. Nowadays, however, the majority of f.m. receivers and tuners of any consequence carry a variably tuned r.f. stage. Inexpensive models and portables, though, might well have an untuned r.f. stage, these then showing a tuning capacitor with only two ganged sections. It is just as well to get all these factors sorted out, since successful servicing demands intimate knowledge of the receiver.

The trend is for more receivers, even cheap portables, to carry an f.m. section so that they can tune to the 'local' v.h.f. stations at least. To be up-to-date, therefore, a substantial part of this series is bound to delve into f.m. techniques and servicing problems quite extensively. Nevertheless, a.m. is still used either by itself or linked to f.m., the latter constituting the a.m./f.m. receiver.

Whether dual or single system, the i.f. on a.m. is almost exclusively 470kHz and on f.m. 10.7MHz. Such output from the appropriate front-end is then conveyed to the i.f. channel.

## DESIGN VARIATIONS

This is where we can see some variation in detail. An a.m. only receiver has a relatively simple i.f. channel of, perhaps, only two transistor stages, depending on its price category. This would feed into a simple diode a.m. detector and thence, via the volume control, to the audio channel, which commonly carries three transistors.

The a.m./f.m. receiver might be similarly endowed so far as a.m. is concerned; but for f.m. would carry a separate i.f. channel feeding into the f.m. detector, thence via switching and the volume control to the audio channel, as shown in Fig. 5. This is the least complex type of dual receiver to service, for

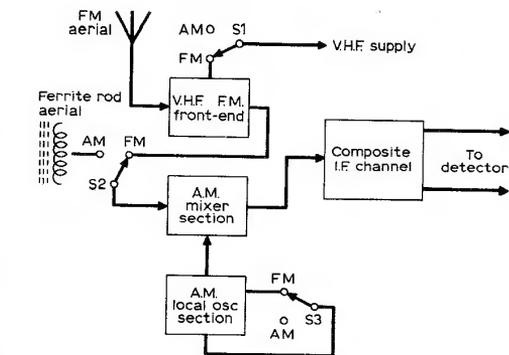
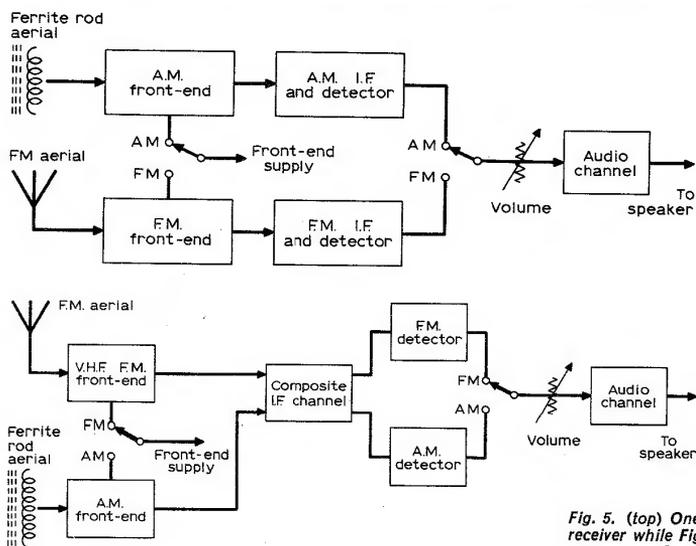


Fig. 7. This particular design variation helps to eliminate switching.

apart from the audio department, each standard runs its own way. Thus, failure of one standard only would mean at least that the audio channel is working and that the trouble must lie either in the affected front-end or i.f./detector channel (or, perhaps, in the a.m./f.m. switching). Similarly, failure of both standards would point strongly to audio channel or power supply trouble.

Receivers adopting this design philosophy are few; current practice favours the use of a combined a.m./f.m. i.f. channel. Indeed, this is a reflection from the early days of dual-system receivers. It is made possible because of the wide difference between the i.f.'s of a.m. and f.m. (470kHz and 10.7MHz). Each i.f. stage, therefore, can be loaded to respond to both the a.m. i.f. and to the f.m. i.f. without interaction. This merely means that two sets of i.f. transformers are located in the grid and anode or base and collector circuits, the i.f. signal then sent through from the selected tuner neatly getting to the appropriate detector without the need for elaborate switching. The final i.f. stage goes into two branches, via 470kHz and 10.7MHz transformers, to feed the a.m. and f.m. detectors. The idea is illustrated in Fig. 6, and this is the most important block diagram so far given. The a.m./f.m. switches are ganged, of course, and coupled to the band-change switch.

Deviations from this are found, a common one lies in the use of the a.m. mixer/oscillator (frequency changer) transistor as an extra i.f. amplifier on the f.m. standard. This enhances the f.m. i.f. gain which is desirable to ensure full 'limiting' on relatively weak signals over the f.m. i.f. pass-band, which needs to be significantly wider (up to 260kHz to the -6dB points) than that of a.m. to handle the multiple f.m. sidebands and also to accommodate the sub-channel information without distortion when the receiver carries a stereo decoder.

Deviations from this are found, a common one lies in the use of the a.m. mixer/oscillator (frequency changer) transistor as an extra i.f. amplifier on the f.m. standard. This enhances the f.m. i.f. gain which is desirable to ensure full 'limiting' on relatively weak signals over the f.m. i.f. pass-band, which needs to be significantly wider (up to 260kHz to the -6dB points) than that of a.m. to handle the multiple f.m. sidebands and also to accommodate the sub-channel information without distortion when the receiver carries a stereo decoder.

Fig. 5. (top) One possible arrangement for a combined a.m./f.m. receiver while Fig. 6. (bottom) illustrates the more common configuration using a composite i.f. channel.

The block diagram in Fig. 7 shows the deviation just explained. Switches S1, S2 and S3 tell the story. S1 energises the v.h.f. f.m. front-end on f.m. and removes the supply on a.m.; S2 switches the v.h.f. f.m. front-end i.f. to the a.m. mixer section on f.m., while disconnecting the ferrite rod aerial; and S3 mutes the a.m. local oscillator on f.m., restoring it on a.m. S2 switching implies that the a.m. mixer section must also be loaded with dual i.f. transformers (the primaries at the anode or collector at least) at 470kHz and 10.7MHz. This is, in fact, true, as we shall see later.

Block diagrams in Figs. 5, 6 and 7 show a ferrite rod aerial at the a.m. front-end. Almost all receivers, even very expensive hi-fi species, get their a.m. signals by way of such an aerial; and this applies also to inexpensive, small and large portables. The ferrite rod aerial is a highly efficient device and it can collect more signal with less interference (giving a good signal-to-interference ratio) than long-wire or rod-type outdoor aerials, when it is properly orientated. However, the efficiency diminishes with increasing frequency, so in the short-wave bands and certainly at v.h.f. a 'long-wire' or tuned dipole aerial is required (the tuned dipole certainly for v.h.f. f.m. reception).

Some receivers try to make do with a compressed v.h.f. dipole fitted into the wooden or plastic cabinet, while f.m. portables can provide sometimes fair results from local stations by way of a built-in telescopic aerial, but this is definitely not the best way of securing the potential attributes of the f.m. system of broadcasting! Pickup efficiency of such rods is likely to improve marginally with the new 'slant' plane of signal polarisation, but currently only one or two stations of the BBC are so engineered.

Unsuccessful attempts have been made to simulate at v.h.f. the convenience and efficiency of the ferrite rod aerial; but to date we still need a good v.h.f. f.m. aerial to obtain the best results from this service, especially when advantage is to be taken of the stereo information multiplexed on some v.h.f. f.m. signals.

The ferrite rod aerial is a tuned device and it takes the place of the aerial coil of earlier receivers. Two windings provide for long-wave and medium-

wave tuning and sometimes there is a third winding for coupling to an external aerial when the receiver is operated under screened conditions, such as in a metal caravan or motor car.

## AM RECEIVER

The circuit of a six transistor a.m. only receiver is given in Fig. 8. I have divided this into the three sections of the block diagram, Fig. 1. Thus VT1 is the frequency changer transistor whose base receives signals tuned by the ferrite rod aerial. Windings L2 and L4 are for medium and long wave respectively, while windings L3 and L5 couple the tuned signal to the transistor base, the appropriate winding being selected by wavechange switch sections S3m and S41.


Aerial section of the tuning gang is C1 with trimmer C2 in parallel this combination being connected to L2 or L4 by S1m and S21, also wavechange switch sections. Winding L1 provides for external aerial coupling.


Local oscillator coils are L6, L7 and L8, with tuning provided by C8 section of the gang and C9 trimmer in parallel. Wavechange switch section S51 introduces extra parallel capacitance for long-wave operation. Part of this capacitance is in the form of l.w. trimmer C11, the remainder being provided by C10. Capacitor C7 in series with the oscillator tuning acts as a fixed padder to provide the correct signal/oscillator tracking (at the i.f. difference) over the bands. The trimmers mentioned and also the cores in the i.f. transformers determine the overall alignment. This subject will be dealt with fully by Mr. Hellyer later.

The i.f. signal is developed across the windings of the first i.f. transformer L9/10, the tapping on the primary providing the correct coupling impedance.

The i.f. channel features the two transistors VT2 and VT3, the second i.f. transformer L11/12 coupling one to the other and the third coupling VT3 to the second detector MR1, via windings L13/14. Primary taps are also provided on these i.f. transformers for impedance matching at the collector circuits. This is fairly common practice to avoid undue damping by

Fig. 8. The operation of this six transistor a.m. receiver is described in the text.

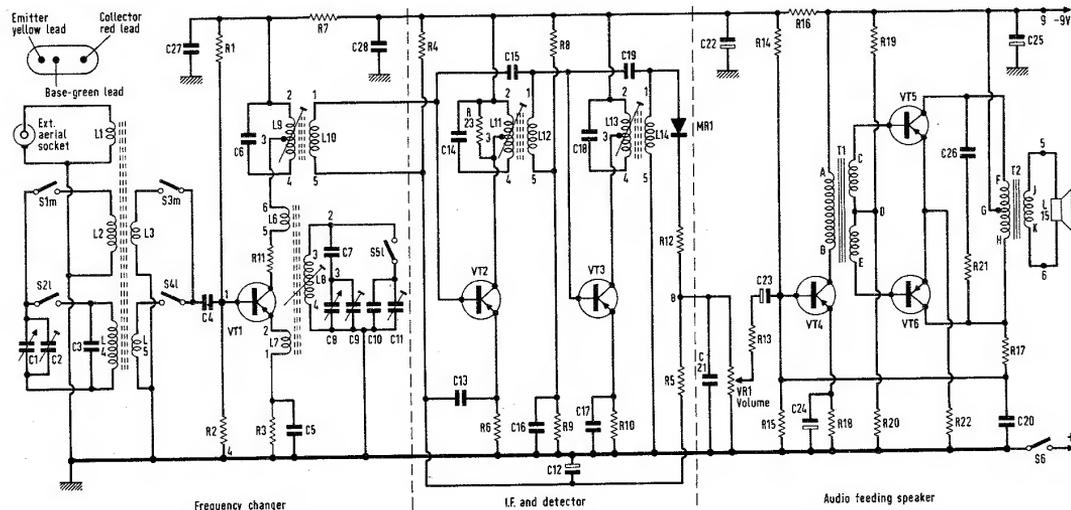

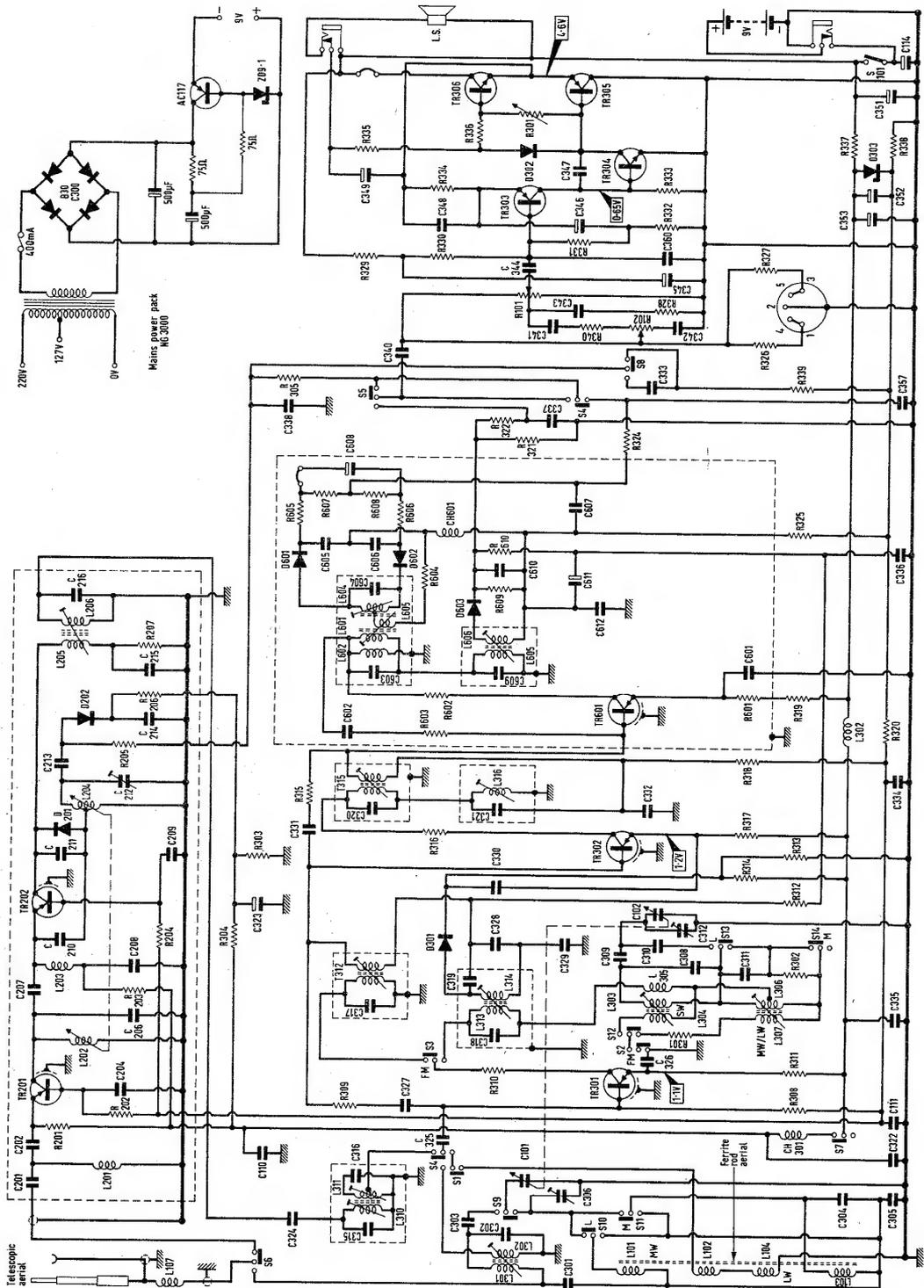

the relatively low collector impedance.

Detector load consists of R12, R5 and R4 in series, but only R5 is concerned with the resulting audio signal. Residual i.f. signal is bypassed by C21, while C12 clamps the bottom of R5 to chassis so far as the audio signal is concerned. Thus the audio appearing across R5 is applied in parallel to the volume control and thence, via the slider, to the base of the first audio transistor VT4.

The d.c. component of the 'detected' i.f. signal modifies the static current in VT2 base feed resistor R4 in such a way that the gain of this i.f. transistor is caused to fall as the strength of the received signal rises, and vice versa. This provides automatic gain control (a.g.c.). What happens is that as the signal level rises, so the cathode of MR1 reflects a positive potential to VT2 base circuit, thereby making the base go less negative with respect to emitter. Since VT2 is a p-n-p device, this reducing negative base potential automatically reduces the emitter current and hence the gain of the stage. Capacitors C15 and C19 in the circuits of the second and third i.f. transformers provide a small amount of negative feedback to neutralise the intrinsic positive feedback via the transistors which could otherwise cause oscillation.

The audio channel is straightforward. VT4 is the driver transistor which feeds push-pull signals to the bases of the two output transistors VT5/VT6. This pair is biased towards class B working by the potential-divider resistors R19/20 in the base circuit, which means that the collector current is almost zero when there is no signal drive. True class B implies zero collector current, but it is necessary to bias for a small current to avoid discontinuity of the transfer characteristics of the output pair at the point of intersection. If the quiescent current is too small this discontinuity effect is revealed by an unpleasant type of distortion, called crossover distortion, which I shall have more to say about later when I shall be dealing with amplifier fault finding.

## AM/FM RECEIVER

Fig. 9 gives the circuit of the ITT-KB KR612 a.m./f.m. receiver. The v.h.f. f.m. unit is at the top left-hand corner, containing two transistors, TR201 the r.f. amplifier and TR202 the self-oscillating mixer. Before I describe this, let us investigate the signal paths involved in this model.

I.F. output from the v.h.f. front-end comes from i.f. transformer L205/206 and is conveyed to a band-pass coupling L310/311 and from there to TR301 base when switch section S1 is in the f.m. position. TR301 is the a.m. frequency changer, which acts as an extra i.f. amplifier on f.m. (see Fig. 7). The a.m. oscillator circuit is muted on f.m. by switch section S2, while section S3 couples the primary of the f.m. i.f. transformer T312 to TR301 collector circuit. The top of the secondary conveys the signal to the base of the second i.f. transistor (on f.m.) TR302.

This transistor's collector is loaded into the second i.f. transformer T315, which is for f.m., in series with the a.m. i.f. filter L316, this responding only on a.m.

The signal from T315 secondary is passed to the base of TR601, and the collector of this transistor is also loaded into series-connected f.m. and a.m. transformers which feed the appropriate detectors. The top transformer, L601/604/605, feeds the f.m. ratio detector diodes D601/602, while that below, L605/606, feeds the a.m. detector diode D603.

RESISTORS		CAPACITORS	
R201	750	C110	220pF
R202	2K2	C111	200pF
R203	1K	C112	100pF
R204	500K	C201	270pF
R205	500K	C202	100pF
R206	500K	C203	100pF
R207	50	C204	100pF
R208	50	C205	220pF
R209	50	C206	220pF
R210	50	C207	4.7pF
R211	150K	C208	300pF
R301	51K		
R302	51K		
R303	51K		
R304	51K		
R305	51K		
R306	51K		
R307	51K		
R308	51K		
R309	51K		
R310	270		
R311	270		
R312	31K		
R313	22K		
R314	22K		
R315	22K		
R316	50		
R317	50		
R318	50		
R319	3K3		
R320	1K		
R321	270K		
R322	2K2		
R323	2K2		
R324	2K2		
R325	10		
R326	100K		
R327	4K7		
R328	15K		
R329	15K		
R330	150K		
R331	1K8		
R332	2K2		
R333	2K2		
R334	2K2		
R335	80		
R336	47		
R337	47		
R338	1K5		
R339	4K7		
R340	4K7		
R601	1K2		
R602	10		
R603	10		
R604	10		
R605	1K8		
R606	680		
R607	680		
R608	15K		
R609	10K		
R610	20K		
R101	100K		
R102	100K		
C601	100pF	C331	90pF
C602	100pF	C332	100pF
C603	100pF	C333	100pF
C604	100pF	C334	47KpF
C605	100pF	C335	100pF
C606	100pF	C336	100pF
C607	100pF	C337	4K7pF
C608	100pF	C338	100KpF
C609	100pF	C339	100KpF
C610	100pF	C340	100KpF
C611	100pF	C341	100KpF
C612	100pF	C342	22KpF
C613	100pF	C343	100KpF
C614	100pF	C344	100KpF
C615	100pF	C345	500pF
C616	200pF	C346	250pF
C617	200pF	C347	680pF
C618	200pF	C348	680pF
C619	200pF	C349	1000pF
C620	200pF	C350	1000pF
C621	200pF	C351	1000pF
C622	200pF	C352	1000pF
C623	200pF	C353	1000pF
C624	200pF	C354	1000pF
C625	200pF	C355	1000pF
C626	200pF	C356	1000pF
C627	200pF	C357	1000pF
C628	200pF	C358	1000pF
C629	200pF	C359	1000pF
C630	200pF	C360	390pF
C631	200pF	C601	47KpF
C632	200pF	C602	47KpF
C633	200pF	C603	51pF
C634	200pF	C604	48pF
C635	200pF	C605	200pF
C636	200pF	C606	200pF
C637	200pF	C607	200pF
C638	200pF	C608	200pF
C639	200pF	C609	200pF
C640	200pF	C610	200pF
C641	200pF	C611	200pF
C642	200pF	C612	200pF
C643	200pF	C613	200pF
C644	200pF	C614	200pF
C645	200pF	C615	200pF
C646	200pF	C616	200pF
C647	200pF	C617	200pF
C648	200pF	C618	200pF
C649	200pF	C619	200pF
C650	200pF	C620	200pF

Fig. 9 (facing page) is the circuit of the KB KR612 a.m./f.m. receiver whose operation is discussed in the text. The above table of component values for this circuit should prove helpful. (Note: 5K1 is 5.1 K $\Omega$  etc. 2K2pF is 2200pF etc.)

Output from the f.m. detector comes from C607 and gets to the volume control R101 through R324, switch sections S4/S5 and C340 (R102 is the tone control.)

The switch sections so far considered handle the a.m./f.m. changeover and we have explored the f.m. signal paths. Now, on a.m. S1 removes the v.h.f. tuner i.f. output and connects TR301 base to the ferrite rod aerial, S2 removes the a.m. oscillator muting and introduces the oscillator coils, S3 removes the f.m. i.f. transformer T312 and in place connects the a.m. i.f. transformer L313/314, while S4/S5 change over the detector outputs, the a.m. detector output then being fed to R101 volume control from R322, S5 and C340. Under this condition the receiver is of similar style to that of Fig. 8.

Now to get back to the v.h.f. front-end. This is tuned by variable inductors (permeability tuning); L202 tuning the r.f. transistor output and L204 the v.h.f. local oscillator. This tuning is ganged mechanically, in the same way as tuning capacitors (denoted by the dotted line between the two inductors).

R.f. transistor TR201 is in common base mode, meaning that the input signal is applied to the emitter, the base 'earthed' to signal by C204 and the tuned output being taken from the collector. Incidentally, switch section S6 supplies signal to the f.m. front-end from the telescopic aerial and transfers the aerial to the ferrite rod circuit on a.m., this giving enhanced signal pick-up under certain conditions.

The emitter circuit of TR201 is broadly tuned over Band II by the pi-network C201/C202 and L201, providing the input coupling. The transistors are p-n-p

Continued on page 153

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.**

**I**N Take 20 No.11 a "Novelty Light Flasher" was described, operated by a conventional multivibrator. At the time the article was presented mainly as a description of the operation of the multivibrator circuit. You may think that just over a year is rather a small gap to describe yet another light flashing circuit as there can be little demand for them but the circuit produced here has such advantages that I feel its inclusion is justified. It has a considerable number of advantages over other circuits I have seen and is cheaper to build than the previous circuit.

The light output is extremely high—far higher than you would expect from a torch operating with the same type of bulb; the reasons for this are given later.

Deaf people often make use of lights for receiving signals where those with normal hearing use a bell—telephones and door bells are the first cases that spring to mind. A flashing light is far, far more noticeable than one many times brighter that stays on continuously—ambulances, police cars and breakdown vans are cases in point.

Warning devices in electronic equipment are often arranged to complete a circuit to a bulb and this little simple circuit can be wired up so that the warning is a series of flashes. Car warning lights can readily be modified to use this circuit.

I use the circuit shown here, built into a simple wooden box and carry it with my car tools so that if there is a breakdown it can be set to flash away beside the car, warning other drivers of the dangers.

So, you can see that there are plenty of uses for such a circuit—no doubt the ingenious constructor will be able to think of many more.

## The Circuit

The circuit makes use of a rather special version of the multivibrator and regular readers may notice a similarity with the rain alarm and the metronome projects described before in this series.

Only two transistors, one resistor and a capacitor are used although for versatility in being able to modify the flashing rate, the resistor is made up from one fixed and one variable.

The circuit produces a series of pulses which have the effect of turning Tr2 alternatively completely on and completely off so that pulses of very nearly 9V are applied across the bulb which is normally intended for 3V operation. The bulb is one of those usually used for torches, they are widely available and all Woolworth stores have them. They have 3.5V stamped on them just above the thread. Holders for these bulbs are also available and these are inexpensive and save soldering directly on to the base of the

## No. 26 LIGHT FLASHER

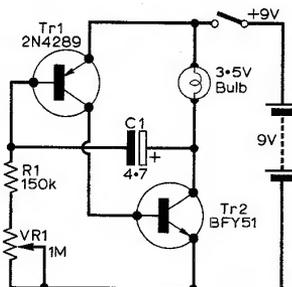


Fig. 1: Circuit of the 'Take 20' light flasher.

bulb, an operation which is not always easy.

Although 9V is applied to the bulb, no harm has befallen those used in various prototypes. Light output is very much higher than for normal operation due to the high voltage applied and possibly reaches 10W though this is very hard to measure. However, it is operating not continuously but as a series of pulses and the filament has time to recover before blowing. The same applies to the battery which receives a real caning during the short periods but this, like the bulb, has time to recover before the next demand is made of it.

The larger layer batteries such as the PP9 are best but for operation inside a car, or near it, the 12V internal battery will be fine.

Neither of the transistors in the circuit are expensive. The BFY51 is a semi-power silicon type and N-P-N while the 2N4289 is one of the cheapest plastic silicon P-N-P types available.

The flashing rate is determined by VR1 and this will vary between several flashes a second to one every five or six seconds. For normal fixed operations R1 can be increased and selected for the required rate. The capacitor can of course be raised in value for longer delays but its working voltage should be at least 12V.

Construction for a circuit of this simplicity does not of course matter and should present no problems. If VR1 is left out the wiring can even be done around the bulb holder. ■

### P.W. BINDERS

Preserve your copies of Practical Wireless. Don't let them become torn and dirty—buy a hard-cover binder for 75p from:

**Binding Department,  
IPC Magazines Limited,  
Tower House,  
Southampton Street,  
London, W.C.2.**

Price includes post and packing.

# PRACTICAL WIRELESS

## PW 'partygram'


INCLUDING RADIO 1 AND 4

Those sounds you get from a one valve record player, straining to reach 2 watts, really won't do any more; so we are offering you the "Partygram"—a modern solid state design producing 10 watts of beautiful sound.

Separate treble and bass controls give you full control over the output and the dulcet tones are fed to a speaker that will make most commercial record players blush!

And there's more. An optional transistor m.w. tuner is featured and with this the press of a button converts the "Partygram" to receive Radio's 1 and 4.

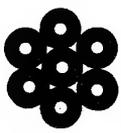Beautiful Beat, Blues or Beethoven is what we promise with the "Partygram": the full description is covered in P.W., starting in the next issue.



ALSO:

### ENLARGER TIMER

No relays, high accuracy and wide range are the ideal features you expect in a good timing unit. This project has all these, and although specifically designed as an enlarger timer, it is also suitable for other uses. Timing accuracy is better than  $\frac{1}{4}$  sec. per minute and timing period can be set between 1 second and 80 seconds. The controlling device is a TRIAC used with four other transistors.

### SIMPLE FET RECEIVER


You've read about f.e.t.'s—they're transistors that are a lot like valves—but we bet that many of you haven't tried them yet. Here is a golden opportunity to get in on the act with a simple project with great potential; three plug in coils give coverage of 20 metres to 580 metres and there are a lot of stations in this part of the spectrum. Low cost, simple construction, high performance and an excellent introduction to the f.e.t. is what we offer—full details in the July issue.

Plus all the regular features: 'Take 20' for the beginner, 'I.C. of the Month' for the experimenter, 'Going Back' for the nostalgic and 'News' to keep you up to date with developments. All this and more in the July Issue—on sale June 4th—Price 20p.

ALL FEATURED IN THE JULY ISSUE ON SALE JUNE 4th



# SIMPLE SIGNAL GENERATOR

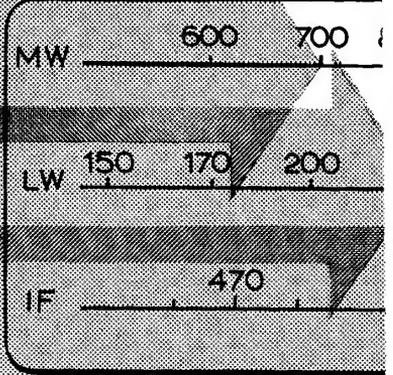

**T**HIS is a transistor signal generator operating from an internal 9V battery, covering 150kHz to 30MHz in five bands. An audio output is also available, for the testing of a.f. circuits. The generator uses easily obtainable coils which considerably eases construction.

## CIRCUIT

Fig. 1 is the circuit, Tr1 being an f.e.t. operating as an r.f. oscillator, with Tr2 as audio oscillator. The radio frequency signal produced by Tr1 is modulated by Tr2, so that it carries an audio tone which can be heard on a receiver.

The band switch has three poles. S1 switches the gate circuit to L1, L2, L3, L4 or L5, which are tuned


by VC1. The small fixed capacitors C4, C5 and C6 are to obtain suitable band coverage on the last three ranges.



Section S2 switches the drain to the feedback windings, drain current being obtained through R4 and one half of the secondary of the audio transformer T1. C7 is an r.f. by-pass capacitor. S3 shorts out the next-larger inductor to the actual one in use, to avoid possible absorption effects due to the natural frequencies of coils not in circuit.

Tr2 obtains feedback from the transformer T1 generating an audio tone, taken to R4. C8 governs the depth of modulation.

Audio obtained through C11 is taken to VR1 and

Fig. 1. Complete circuit of the Simple Signal Generator.

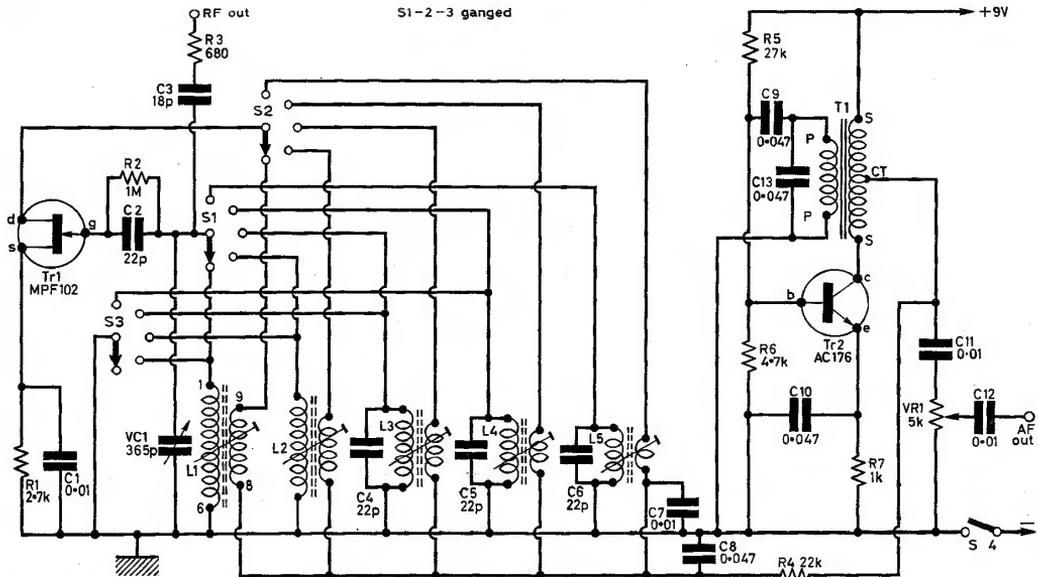

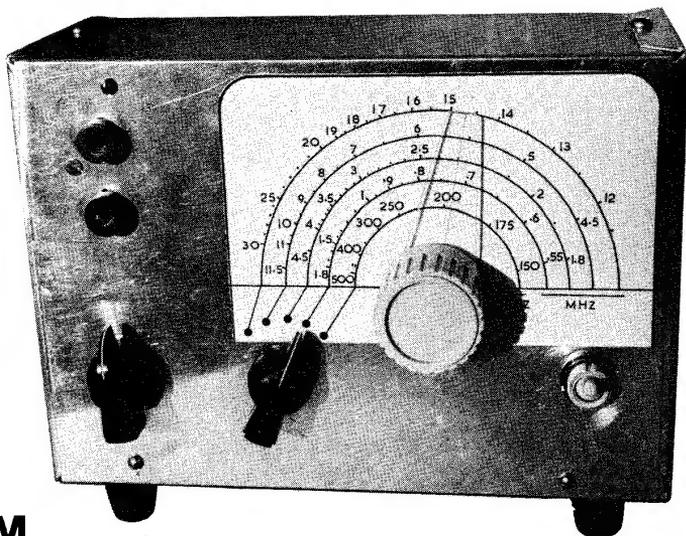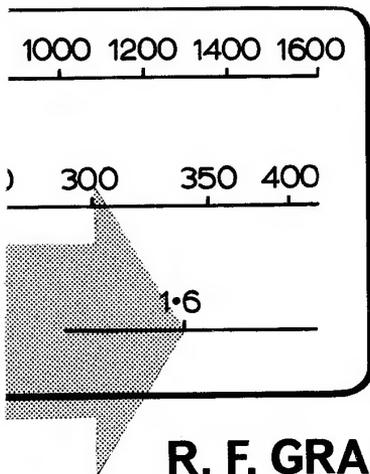

## R. F. GRAHAM

is available at the a.f. output socket with C12 isolating external d.c. circuits. VR1 controls audio output, as required when testing various stages in an a.f. amplifier or receiver.

RF output is taken through C3 and R3, to the r.f. output socket. It was decided not to switch VR1 into this circuit, because an ordinary small potentiometer does not perform very well as an attenuator at high frequencies. Instead, in those circumstances where a change in r.f. signal strength is required, the output leads can be moved or changed to alter coupling. For many purposes the output lead can be placed near the receiver aerial lead or ferrite aerial. Or the output lead can be twisted for an inch or so with an insulated wire, which is in turn taken to the aerial socket of the receiver, or r.f. or i.f. circuit points.

The r.f. output is modulated at all times by the audio tone, so can be tuned in on any type of ordinary receiver.

**Inductors.** The coils listed are of a type intended for valve equipment, and thus suit the high-impedance gate circuit of the f.e.t. Tr1. L4 and L5 are positioned for short leads to the switch. The ranges obtained are approximately as follows:—

Range 1	150-500kHz
Range 2	550-1800kHz
Range 3	1.8-4.5MHz
Range 4	4.5-11.5MHz
Range 5	11.5-30MHz

It was found that the highest-frequency coil L5 was manufactured with an interwound primary to give tighter coupling, and to obtain correct feedback on this range leads to tags 1 and 6 are reversed, compared with the other coils.

## CONSTRUCTION


Most of the components are assembled on a paxolin panel  $6\frac{3}{8} \times 2\frac{1}{2}$ in, Fig. 2 which is later attached to the panel by two brackets. There should be about  $\frac{1}{8}$ in. clearance between board and panel, as shown, to

take the flanges of the sides of the case.

Holes for the coils and other items are drilled as in Fig. 2. Most of the small parts are then wired in. When the board is fixed to the panel, it is about  $1\frac{1}{2}$ in. from the top edge of the panel.

**Transistors.** A transistor holder was employed for Tr1, which is inserted only after wiring is finished. The holder is a push-fit in a hole in the paxolin but adhesive can be used if necessary. Take care that Tr1 is so placed that drain, source and gate leads come as in Fig. 2. Tr2 is an n.p.n. audio transistor. Its leads are passed through small holes and soldered as shown.

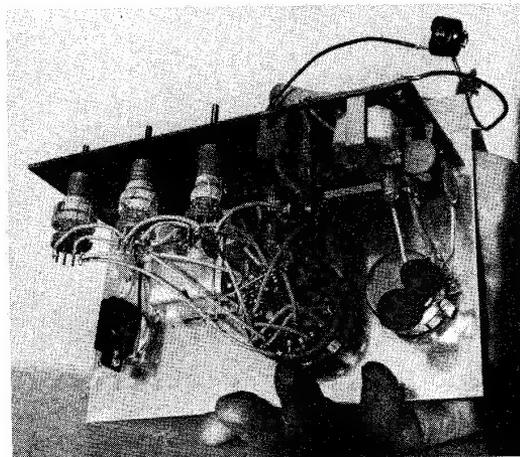**Panel.** This is  $7 \times 5$ in. and VC1 is fixed  $2\frac{1}{2}$ in. from the top edge by three short countersunk bolts. VR1, the bandswitch, and S4 are placed as shown. Two insulated sockets are provided for a.f. and r.f. output, a lead with plug being inserted in the required



General view of the generator. The paxolin panel carrying the majority of the components is mounted towards the top of the front panel.



When no other calibrated equipment is available, fit a 0-100 scale to the generator. Obtain several calibration points for each range, by tuning in known transmissions, or using harmonics. Mark these on a graph so that readings for 100kHz, 1MHz or other appropriate intervals can be taken from the graph and transferred to the appropriate scale.

## ★ components list

<b>Resistors:</b>		
R1 2.7k $\Omega$	R3 680 $\Omega$	R5 27k $\Omega$
R2 1M $\Omega$	R4 22k $\Omega$	R6 4.7k $\Omega$
	R7 1k $\Omega$	
All $\pm$ W 10%		
VR1 5k $\Omega$ potentiometer, linear		
<b>Capacitors:</b>		
C1 0.01 $\mu$ F disc	C6 22pF SM	C11 0.01 $\mu$ F disc
C2 22pF SM	C7 0.01 $\mu$ F disc	C12 0.01 $\mu$ F 350V disc
C3 18pF SM	C8 0.047 $\mu$ F	C13 0.047 $\mu$ F
C4 22pF SM	C9 0.047 $\mu$ F	
C5 22pF SM	C10 0.047 $\mu$ F	
VC1 365pF air spaced variable (Jackson O)		
<b>Semiconductors:</b>		
Tr1 MPF102	Tr2 AC176	
<b>Inductors:</b>		
L1 Range 1 Blue	L4 Range 4 Blue	
L2 Range 2 Blue	L5 Range 5 Blue	
L3 Range 3 Blue		
All above for use with valves (Denco Ltd)		
<b>Cabinet:</b>		
Flanged plate, 2 off, CU147, 7 x 3in.		
Flanged plate, 2 off, CU145, 5 x 3in.		
Flanged plate, 2 off, CU168, 7 x 5in. (Home Radio)		
<b>Miscellaneous:</b>		
On-off switch, 3 pole 5 way wafer switch.		
Transistor holder (3-wire) for MPF102.		
T1, audio driver transformer. Knobs, Feet.		
Output Sockets (2).		

Reversed connections to any feedback winding, tags 8 and 9, will prevent oscillation on that range. Should oscillation become weak towards the l.f. end of Range 5, the leads to tags 1 and 6 can be reversed as well as tags 8 and 9. This increases effective coupling and feedback.

The position of the coil cores also has some influence on oscillation, as well as band coverage. Should it prove necessary, the value of R4 can be changed, to adjust the drain voltage.

## USES

To test a.f. circuits, work backwards from the output stage. When the faulty stage is passed, the signal will cease. The usual detailed tests then only need be made to this stage.

When aligning r.f. mixer or oscillator circuits, it is usually best to have the receiver volume control near maximum and to keep signal strength down by placing the generator lead to give suitable coupling to the ferrite aerial or aerial socket, or to a short wire in the socket.

Do not make any connection to any receiver or other equipment operated from the mains in which the chassis or other parts are connected directly to the mains. ■




IT is a never-ending source of wonder that the makers of integrated circuits seem to be able to get more and more devices on smaller and smaller substrates. The very latest from this wonderland of semiconductorian Lilliput is an m.o.s. (metal oxide silicon) chip or substrate which performs all the digital functions required for a five-digit panel meter.

Packaging is a 30-lead dual in-line configuration which is hermetically sealed. This chip incorporates five decade counters, four further binary shift registers, 20 shift register stages acting as buffer storage, 13 further shift registers, 12 set-reset bistables and some 70 other gates of various complexities. There are over 1,000 m.o.s.t. devices on the chip which measures an amazing 0.137 inches by 0.117 inches.


Besides the counting logic and buffer storage, this chip also accommodates automatic over-range and under-range indication. Thus, if a meter is clipped onto a piece of equipment which provides, across the test points, say, 500V, then the auto-ranging circuitry will ensure that the meter is automatically set to the correct range to accommodate this.

To replace this chip with TTL devices, commonly housed in 16-pin dual in-line packages, you would need around 20 of them. If you now multiply 20 (the number of packages) by 16 (the number of leads which need to be mounted and soldered) you arrive at 320. In terms of production and number of individual joints, compare the 320 with the mere 30 required for the new chip and you will appreciate the advantages of the device.

Do you own a motor car? Where is it now? Are you sure? The safety of a motor car is often a very precarious thing. When you go into the cinema and leave your car outside, there is no real guarantee that it will be there when you come out. Supposing it were stolen or interfered with half way between Peyton Place and Coronation Street while you were watching the Tele. Now you can be sure and take steps to prevent your precious mobile being touched. A company in Britain is making an ingenious device which you can carry, unobtrusively, in your pocket. Directly any one switches on the ignition of your car, a bleeping alarm sounds to let you know. But don't panic. When the bleeping starts, all you have to do is to flick a switch on your receiver. This will immediately make the ignition system in your car inoperative. This could be a winner for preventing crime and shows another application of electronics. It's getting so's an honest crook can't make a decent living anymore.

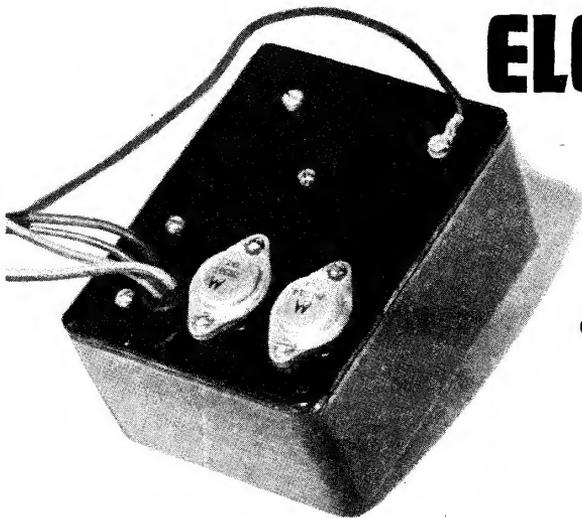

# ELECTRONIC IGNITION SYSTEM

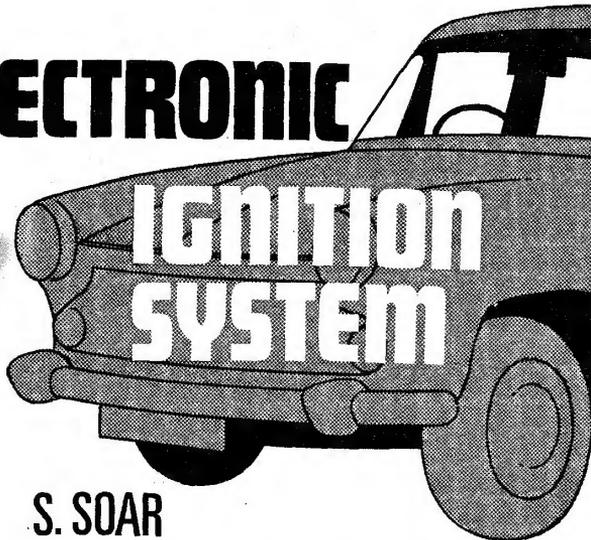

S. SOAR

**T**HE car ignition system is often neglected by the enthusiast who, whilst spending considerable effort to enhance his car's performance with the addition of special carburettors, manifolds, pistons, cam-shafts, etc., often writes off the electrics with perhaps the addition of a sports coil.

The unit described has many advantages over the usual coil ignition system, the principle being the now well-accepted 'capacitor-discharge' system. Although the advantages make this system of particular interest to the competition motorist, the average motorist might well consider its adoption for the advantages of less maintenance, reduced petrol consumption and easier starting in below-zero conditions.

Some of the advantages of capacitor discharge over the normal inductive discharge ignition can be listed as follows:—

1. Easier starting especially in very cold or damp conditions.
2. Increased combustion efficiency resulting in improved performance and economy.
3. Ignition remains 'in tune' over a much wider range of contact breaker and plug gap settings.
4. Erosion of contact breaker and plug electrodes virtually eliminated, resulting in these components having a life of some 4 to 6 times normal expectancy.
5. Misfiring due to contact breaker bounce at high speed eliminated.
6. Rise time of the output high voltage pulse is typically 2 to 5 microseconds in comparison with 100 to 200 microseconds for inductive discharge systems. Leakage losses due to fouled spark plugs, moisture on leads and distributor cap, etc., are therefore much reduced and less energy is absorbed in these losses.
7. Voltage at the contact breaker is reduced from around 300 to 12 volts; failure due to breakdown of capacitor or insulation is therefore virtually eliminated.
8. Coil does not overheat if the ignition is inadvertently left switched on with the engine stopped.


9. The engine can be easily cranked or push-started by connecting a 6 volt dry battery in place of the accumulator.

Other less obvious advantages include longer battery life, less strain on dynamo and reduced wear on starter motor and gear brought about by easier starting especially in sub-zero conditions.

The system has been designed around the standard coil and contact breaker to facilitate easy interchange of the two systems.
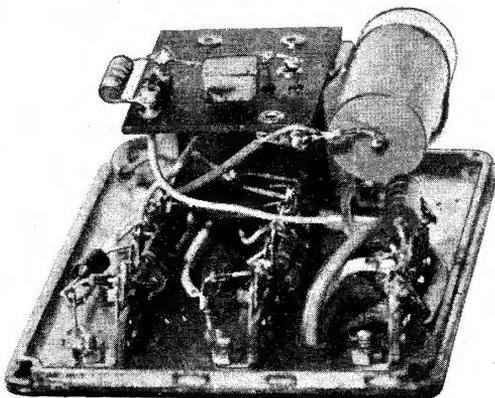
## DESIGN

Basically the unit consists of a convertor which generates around 450 volts and charges a storage capacitor. A silicon controlled rectifier is then triggered to discharge the stored energy into the ignition coil. Referring to Figs. 1 and 2, it can be seen that, with the s.c.r. triggered, C1 and the coil form an oscillatory circuit and as the current swings to zero,



*This photograph, with the heading photograph, shows the general method of construction. Component layout is not critical.*

the s.c.r. turns off, current can no longer flow and energy remaining in the circuit is stored in C1. The convertor increases this charge and the cycle is complete.

The use of 'backswing' to partially recharge C1 increases the efficiency and a convertor capable of 30 to 40 watts is adequate for engines of up to twelve cylinders.


In designing the convertor it was decided that the following characteristics were desirable:—

1. Overshoot should be controlled and utilised to charge C1 to a high value with engine speed low and decreased battery potential on starting.
2. Frequency of operation such that transformer is reasonably small and low priced.
3. Mechanical construction to be simplified by adopting a common collector circuit and

mounting the power transistors directly into the case side, thus overcoming the complication of insulation and improving heat dissipation.

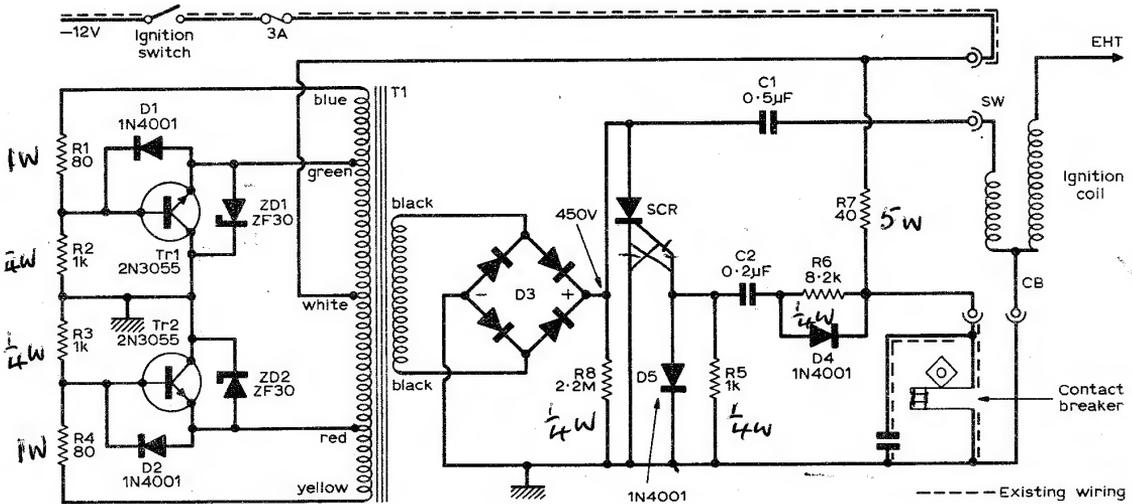
4. Because the s.c.r. imposes an intermittent short on the convertor, some form of protection is necessary. A transformer with moderate leakage reactance fulfills this requirement by causing the convertor to operate at a much higher frequency during short circuit conditions. It was noted that the change from short circuit to normal operation occurred instantly, thus overcoming the disadvantage of many inherently short circuit proof convertors which cease oscillating on short circuit and have a delay before restarting.

Zener diodes ZD1 and ZD2 were chosen to limit the overshoot voltage to a safe level. Omission of



▲ Fig. 1: Circuit of the unit for use with cars having a positive earth system.

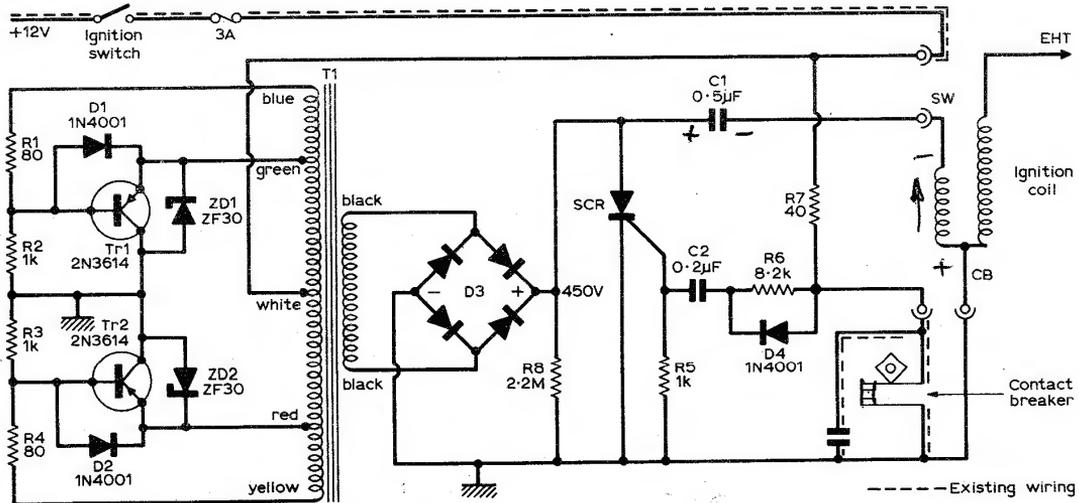▼ Fig. 2: This circuit is intended for use with negative earth systems.



these components would result in Tr1, Tr2, C1, D3 and the s.c.r. being subjected to excessive voltage. Diodes D1 and D2 protect Tr1 and Tr2 from being reverse biased.

### THE TRIGGER CIRCUIT

A major feature of the trigger circuit is that misfiring due to contact breaker bounce is eliminated. Diode D4 transmits the trigger pulse via C2, C2 then discharges through R6 thus forming a delayed recovery. Fig. 3 shows output from contact breaker when bounce occurs and voltage available to trigger s.c.r.

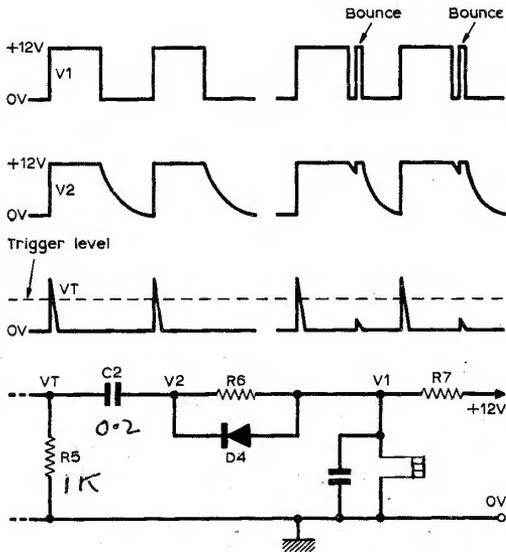


Fig. 3: The waveforms, upper right, show the spurious pulses due to contact breaker 'bounce' in conventional ignition systems. The waveforms, upper left, indicate the clean triggering pulse obtained with the capacitive-discharge system.

### ★ components list

<b>Resistors</b>	
R1 80Ω 1W	R5 1kΩ ½W -
R2 1kΩ ½W	R6 8.2kΩ ½W -
R3 1kΩ ½W	R7 40Ω 5W -
R4 80Ω 1W	R8 2.2MΩ ½W -
<b>Capacitors</b>	
C1 0.5μF 600V	C2 0.2μF 100V
<b>Semi-conductors</b>	
Tr1, Tr2 Positive earth system: 2N3055	
Negative earth system: 2N3614	
(Obtainable from Jermyn Industries, Sevenoaks, Kent.)	
D1, 2, 4, 5 1N4001 D3 Bridge Rectifier (4 x BY100)	
ZD1, 2 ZF30 (30V 400mW)	
SCR CRS1/40 (400V p.i.v. 1A)	
<b>Transformer</b>	
T1 Type P1/6 (Available from Magtor Ltd., 68 Dale Street, Manchester. £1.50 inc. p/p.)	

The prototype was bench tested with a conventional contact breaker, motor driven, and a 10cm diameter sphere gap used to compare maximum output voltage of capacitor discharge ignition and inductive discharge systems. Fig. 4 shows the result obtained with a battery potential of 14V. Output was measured at reduced battery potential, and at 7 volts (normal for starting in freezing conditions) spark voltages of approximately 30kV for c.d.i. and approximately 10kV for inductive discharge were recorded.

Since the engine requires some 10 to 15kV minimum on starting this latter figure demonstrates why many cars suffer from grinding paralysis in cold weather.


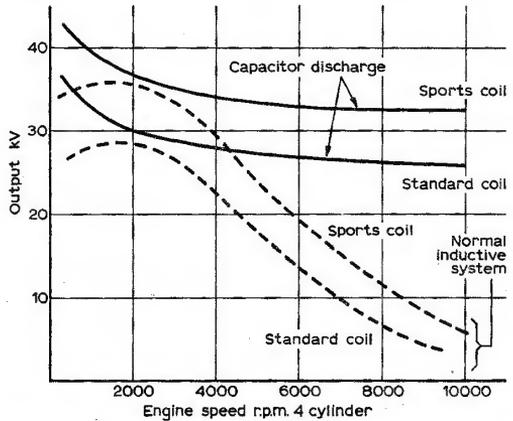


Fig. 4: Comparison of coil output against engine speed for standard and sports coils for both systems of ignition.

Fig. 5: This graph illustrates the greatly reduced load on the battery with the c.d. ignition system.

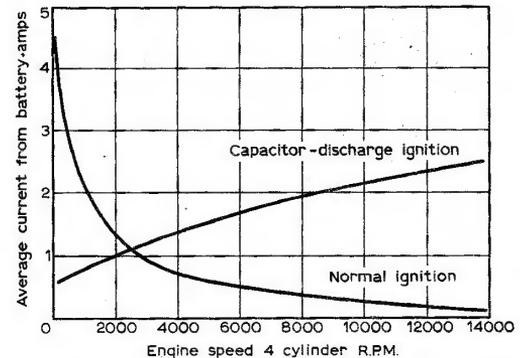

It can be seen from Fig. 5 that the demand on the battery with c.d.i. is very much less at starting. In fact, with c.d.i. the engine can be cranked or push-started with a 6V torch battery in place of the 12V accumulator, whereas the coil ignition system requires a supply capable of supplying a considerable current.

### CONSTRUCTION

Construction can follow any number of variations, the prototype being constructed in a diecast case 4½ × 3½ × 2in. Points worth noting are that part of

the circuit is low voltage and part operates at up to 450V, so adequate insulation must therefore be used and care taken to appreciate the shock hazard if the unit is operated with cover removed.

A certain amount of heat is generated especially in the transformer core and it is therefore advisable to mount the completed system away from the exhaust manifold. The addition of cooling fins to the exterior of the case was found to be an advantage if the unit is used on 8 and 12 cylinder cars where the demand on the system is greater.

In use it was found to be advantageous to increase plug gap setting to around 0.050in. Starting is definitely improved, so, too, is acceleration and flexibility. The prototype has completed some 8,000 miles and approximately 500 hours of bench testing at a simulated engine speed of 9,000 r.p.m. (4 cylinder). ■



1971

This year we shall be sponsoring another Project Autumn competition. The rules have been amended so that the PW "Designer's Trophy 1971" will be awarded to the author of the best constructional article published in PW issues dated July 71 to March 72 inc. This allows submitted articles to be published as soon as possible and for authors to be paid without delay.

Full details and rules in the July issue of PW, on sale 4th June.

**SUBMIT YOUR ARTICLES NOW**

## MAXWELL

by G8DSH



## THE MW COLUMN

MAY to July is the season for receiving medium wave stations in East and South Africa. Listen from 0200hrs GMT until sunrise for Johannesburg 1286kHz and Bloemfontein 782kHz. Although never strong, Johannesburg is consistent throughout the summer and has been logged by a number of DXers in the UK. Lourenco Marques 917kHz in Mozambique is another regular. It broadcasts in English but can only be heard before 0300hrs when European interference starts to become troublesome. Further north in Zambia, Kitwe on 1070kHz has been heard signing on at 0255hrs. Others from this area that sign on at 0300hrs are Dar es Salaam, Tanzania on 656kHz; Nairobi, Kenya with 100kW on 746kHz and Mbali, Uganda 638kHz. The BBC Eastern Relay on 1410kHz is located on Masirah Island in the Arabian Sea to the south of Muscat and Oman. This station broadcasts for most of the night in Arabic, Persian or Urdu and is often heard in this country.

E. Cox of Downpatrick N. Ireland asks for details of books that cover MW DXing. The few on DXing that are available are concerned mainly with the short waves, though "How to Listen to the World," published by the World Radio and TV Handbook Co, Copenhagen, does devote some space to the MW's as well. Practical Wireless occasionally has articles on MW DXing; the most recent was in April 1970 while constructional details of the PW Medium Wave Loop appeared in November 1966. Back issues can usually be obtained by advertising in technical or club magazines. There are also a number of DX programmes that give news and information on the medium waves. The English version of "Sweden Calling DXers" is on 1178kHz at 2245hrs GMT every Tuesday and includes news about the MW's and events on international matters. "DX Juke Box," a weekly programme of Radio Nederland has a MW feature on the 4th Thursday of the month. Details are available from Postbus 222, Hilversum, Holland. Deutschlandfunk 1286kHz carries "DX Circle" at 1800hrs on alternate Wednesdays. This programme is presented by Alan Thompson, Secretary General of the European DX Council and it covers both medium and short waves.

Brazil is well represented on the medium waves during the summer, stations in Rio de Janeiro and Sao Paulo being particularly prominent. Although they can be logged from midnight onwards they are at their best in the half hour before sunrise. Portuguese is the language and the majority are commercially owned, usually by local newspapers who give their name to the station. Callsigns are allocated but seldom used over the air. Look for PRA3 Radio Mundial on 860kHz; PRF4 Radio Journal on 940kHz; PRE8 R. Nacional 980kHz; PRE3 R. Globo 1180kHz; PRG3 R. Tupi 1280kHz; all in Rio. From Sao Paulo there are PRB9 R. Record 1000kHz which has been heard in English; PRG2 R. Tupi 1040kHz; PRG9 R. Nacional 1100kHz. Other cities heard include Belem with ZYE25 R. Dif. Liberal on 1330kHz and Belo Horizonte with PRH6 R. Guarani 1340kHz. PRH6 verifies readily with a QSL card and pennant.

Charles Molloy

# COMMERCIAL RADIO...

**I**N about two years, if Government plans go through, the first commercial radio station on the British mainland will take to the air and the BBC monopoly in sound broadcasting will be no longer.

How these stations will develop, what their programming will consist of, and who will listen to them is a matter of conjecture but a mass of information from overseas is available and from this we can at least make a good guess as to what will happen.

## The White Paper

The Government's White Paper—and remember that it is as yet only a proposal and not legislation—lays down plans for 'up to sixty' local commercial radio stations financed entirely by spot advertising.

The paper makes it quite clear that these stations should be essentially local in character and that the programmes should be concentrated on local interest. Locally produced programmes will fill the majority of the schedule, though it is suggested that the stations could be linked for the networking of 'news, music and other programmes.'

The overall authority over these stations will be vested in a revamped ITA which at present operates the transmitters and controls, to a certain degree, the ITV programme companies. This will be renamed the IBA (Independent Broadcasting Authority) and although other sections of the lay press seemed surprised at this, the original policy statement of the Government, while still in opposition (published in full in *Practical Wireless* May 1969) made it quite clear that this was planned.

The BBC loses a little by the proposals but on the other hand in certain aspects gains quite a lot. The BBC Radio 4 regional programmes in England would disappear on the medium waveband, being replaced by a single programme; Radio 1 on 1214kHz has set the pattern and shown that this can operate successfully. Three frequencies would be released for other uses by this, one of which will be allocated to the BBC Overseas Services.

On the other hand, medium wave frequencies would be allocated to all the twenty BBC Local Radio Stations so that, with the 60 proposed commercial ones, about 80 new stations will be fitted into the medium waves. In addition back-up channels on v.h.f. will be provided for the new stations and to this end the higher frequency end of Band II will be transferred from mobile services to broadcasting. This is the part of the band which at present is used by the police and other services.

# IN BRITAIN

## HALVOR MOORSHEAD

Programme contracts will be granted in much the same way as the present TV contracts. The IBA will select the company who *they* feel will best serve the particular area and will be responsible for vetting programme schedules and for the actual transmitters; for this the stations would pay a levy and presumably it would operate on the TV principle of charging a levy according to the station revenue, rather than on the cost of providing the service. Thus, small stations may well be provided with transmitter facilities below cost price, this being offset by heavy charges made on the larger stations.

Commercial stations would only be granted a franchise for a limited period and if they failed to live up to their promises, or another applicant appeared better, the franchise would not be renewed (as was the case in TV with TWW).

The stations would be introduced over a period, but, unlike the BBC Local Stations, the larger cities and conurbations would have the service first.

The Government White Paper also makes provisions limiting ownership of stations and suggests that local newspapers would have 'first refusal' for stations in their area, though outright ownership by local papers would not be allowed.

Massive profits, of the type that the commercial TV stations made in the early 1960's, are precluded in the White Paper.

## Frequency Allocations

Until recently the Post Office and the BBC had denied that any frequencies at all could be found for further sound broadcasting stations in the medium waveband—this was of course the reason for shutting down the 'Pirates' rather than giving them frequencies. How is it then that 80 stations can be fitted in?

Two frequencies will be made available by the reorganisation of the Radio 4 wavelengths. In addition there are the two International Common Frequencies, 1434kHz and 1594kHz. Radio 3 would lose 1546kHz which is at present used for low power relay stations in certain parts of the country and be confined to 647kHz. Thus, before anything spectacular takes place, five new frequencies become available. In addition the Government intend to invoke Article 8 of the Copenhagen Convention (the international European agreement governing allocation of frequencies).

In simple language this allows member countries to broadcast on frequencies allocated to other countries as long as such transmissions do not cause interference and that the country using that frequency does not object. Far fewer frequencies are made available by this provision than may at first appear because of the chaotic conditions prevailing, but some frequencies at least can be found. Whatever happens, and however the stations are organised, it is certain that several stations will be sharing each frequency.

The White Paper suggests that major cities such as London will have more than one station and even puts forward the idea of London having two stations from the outset. 60 stations would allow for a coverage of 70% of the population of the United King-

dom and, roughly converted into siting, this would mean that most cities of 100,000 or more population would have a station.

By international standards this would make the local stations very large. In the USA there is a radio station for every 30,000 people, in Australia a commercial station for every 100,000 and 60 stations for Britain would mean one for every 900,000. These are only average figures but it does indicate that stations are not going to find it hard going and are unlikely to be run by the proverbial 'one man and a dog.' New York City alone supports nearly 60 stations and most of them make good profits so it can be seen that London, which is of a similar size, will have no trouble in supporting more than two stations.

Many areas will be served by several stations, even if there is only one station locally, as coverage is bound to overlap to such an extent that an average of three stations would be heard. This in itself is likely to damage the local identity of the stations. How will it be possible for a station in the Luton/Dunstable area (which will probably have a station) to be kept from aiming its programmes at the Greater London Area where the audience might be twenty times that which they can obtain locally, enabling the station to charge vastly higher advertising rates? This is not covered in the White Paper and would be almost impossible to legislate against. This is a considerable weakness in the 'local' emphasis of the proposals.

## Programmes

The critics of commercial radio say that the stations will be all "pop and ads", while the supporters say that first of all it doesn't matter and secondly that stations are bound to concentrate on local affairs.

Almost certainly some of the stations will concentrate on little else but pop music and hope to take away audience from Radio 1. They will probably be successful. To judge commercial stations on the "pirates" would be a mistake. Their very location made it almost impossible to put out anything but recorded music and of course the proposed stations will have no such limitations.

The second commercial station in any area may well find the potential audience for pop music very well catered for with Radios 1, 2 and other commercial stations and could well find the largest audience among the more traditional listeners. There is a strong tendency in the USA for stations to move out of the pop field and more and more are concentrating on news, talks and features. Those best at doing pop programmes are staying in the field but they no longer rule the airwaves as they once did. The BBC was very successful at combating ITV by changing their programme patterns and this will almost certainly apply to radio, making the competition for audiences even keener.

There is also the aspect of the BBC Local Stations. At present they are limited to an hour a day each of "needle time", that is the time that they are allowed to put out locally originated recorded music. The commercial stations will not be hampered by such restrictions (the White Paper makes this clear) and almost certainly the same rule will apply to BBC local stations—it would be unfair to expect them to be restricted by conditions not applicable to the new stations.

Local news and events do not seem to be popular features on radio (although the new stations may change this) and so it seems that we can expect almost anything in the way of programming. The audience that the BBC "Dales" programme attracted would be regarded with envious eyes by many commercial concerns. The audience for plays and news programmes is very high and commercial stations may well compete for this audience.

The field is wide open and although we can certainly expect a lot more broadcast music, there will be many other programmes catering for most sections of the community.

## Finance

Commercial contractors will be responsible for selling time for spot commercials and naturally they will charge as much as they can for this. The amount of time that can be sold will probably be limited by the IBA to about six minutes an hour (the same as for TV).

A general guide is that for a 30 second spot, advertisers would be prepared to pay between 10p and 20p per thousand listeners (Manx Radio on the Isle of Man rates are about 15p per thousand). Thus stations in large conurbations may attract well over 100,000 listeners and could charge £10 to £20 per spot but if programmes were networked a programme attracting the audience that Tony Blackburn does at present could charge £500 for a 30 second spot (which is very cheap by TV comparison)!

From this it can be deduced that commercial radio will not be a place to sell your car or even for your local store to advertise its bargains. The same money can be far better used in the local press.

Contrary to the general train of thought it is more likely that the advertisers would be mostly those who at present use TV or the provincial evening papers. Local papers generally rely on very local advertising—and to a large extent on classified ads—and these are not applicable to the much wider and less selective medium of radio.

There is little doubt that commercial radio, when it is fully developed, will be very big business and £30 million a year is the sort of figure we can expect.

## Set Design

One can only hope that British industry rises to the occasion and meets the demand for new sets; for many people will have to get new sets. The fact that all the stations will broadcast on v.h.f. will, it can be hoped, give a fillip to this band. This is especially likely as reception after dark of the medium wave stations will be poor and the difference will become very much more apparent than it is at the moment. May we hope that this new market is met by decent and inexpensive v.h.f. sets made in this country rather than imports from the Far East.

All-in-all commercial radio will bring about major changes in many fields—from the nation's listening habits to the content of PW but we have still about two years to wait; the Government are thinking that the first stations will take to the air in the spring of 1973. Much may change in the meantime—Parliament has still to debate it and the Labour Party are opposed to the plans, but this is unlikely to stop it. We can only wait to see what happens. ■

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE postal dispute being over your reports are starting to get through again, the first one coming from new reporter **Howard Stephenson** of Newcastle-upon-Tyne. Howard does not mention what equipment he uses but he must have used more than his ears to hear:

- 4783 *Radio Mali* in French at 2145.
- 4800 *Radio Lara, Venezuela*, music at 2330.
- 4807 *St. Denis, Reunion*, ORTF relay at 2100.
- 4850 *R. Mauritania*, news in French followed by Arabic music, close at 2230.
- 4900 *Radio Juventud, Ven.*, pop music at 0000.
- 4910 *R. Conakry, Guinea*, 'La voix de la Revolution' news in French at 2300.
- 4940 *R. Abidjan, Ivory Coast* in French at 2250.
- 4995 *R. Brazil Central*, music and ads.
- 5015 *Windward Islands B.S.*, English at 2345.
- 5035 *R. Bangui, Central African Rep.*, English at 2045.
- 5047 *R. Lome, Togo* with African music at 2100.
- 15105 *R. Rural, Brazil*, Portuguese talk at 2100.
- 15225 *R. Cultura de Bahia, Brazil*, soccer, 2000.

**Terry Gibbs** of Swindon is a regular reporter to this page and this time his log includes:

- 4920 *R. Progreso, Honduras* at 0000.
- 9705 *Mexico* in English at 0015.
- 9655 *Thailand* using a new frequency and also on 11905.
- 11920 *Bucharest, Rumania* in English at 1500.
- 17820 *R. Ankara, Turkey* in Turkish every Sunday at 0605.

**Nigel Milner** of Sutton Coldfield has been tuning his Invicta, 5-valve superhet through the bands and has come up with the following stations:

- 9640 *R. Kuwait*, news in English at 1700.
- 9710 *R. Nederland, Bonaire* in English at 0800.
- 11720 *R. Trans Europe* in English at 1100.
- 11840 *R. Portugal DX Club* in English at 1900.
- 11880 *R. Mexico, XERH* with news at 2200.
- 15230 *BBC, Atlantic relay, Ascension Island*, 1700.
- 17885 *HCJB, Quito, Ecuador* in English at 2000.

**J. Childs** of Blackheath, London SE3 has had a Skyrover II receiver for one month; connected to a 100 foot long-wire it enabled him to hear:

- 6130 *HCJB, Quito, Ecuador*, Religious Service at 0800.
- 17705 *Radio Havana, Cuba* with news at 2015.
- 21590 *Radio Canada International* at 1835.
- 25790 *Radio South Africa* noted at 1000.

**F. Wakeman** of Basingstoke has a Philips 5-valve domestic superhet and a 100 foot long-wire brought him the following:

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 4990 *Radio Kiev, Ukraine* at 1930-2000.
- 5920 *Radio Kiev, Ukraine* at 1930-2000.
- 6095 *Radio Baghdad, Iraq* at 1800 and at 1930.
- 6130 *HCJB, Quito, Ecuador*, 0730-0830.
- 7120 *Radio Kiev, Ukraine* at 1930-2000.
- 7245 *Radio Austria* at 1000-1030.
- 9390 *Radio Tirana, Albania*, 1630-1700.
- 11755 *Radio Finland*, in Finnish at 2000-2030.

**Graham Close** of Diss in Norfolk is still using his "old GEC heap" but he has constructed an a.t.u. which has improved reception:

- 4823 *Hanoi, Vietnam*, announcements in English at 2225.
- 5058 *Radio Tirana, Albania* at 2100.
- 6540 *Pyongyang, N. Korea* in English at 1850.
- 7065 *Radio Tirana, Albania* at 1930.
- 9620 *Radio Cairo*, announcements at 1730.
- 9725 *Radio Haiti* at 1245.
- 9730 *Radio Australia* in English at 0800.
- 11735 *Radio Morocco*, music at 1500.
- 11740 *Radio Australia* in English at 1000.
- 11820 *Radio Trans Europe* at 1050.
- 11960 *AIR, Delhi* at 2030.
- 15250 *Radio RSA, South Africa* at 1755.
- 15300 *NHK, Japan* in English at 2130.
- 15345 *Radio Kuwait* at 1600.
- 15400 *Radio Kuwait* at 1600.
- 17885 *NHK, Japan*, Oriental music at 0700.
- 17890 *HCJB, Quito, Ecuador* at 2320.

### Author's Note

The standard of reports sent to this page has been dropping noticeably over the last few months. I would, therefore, be grateful if all intending reporters bore the following points in mind:—

All reports should be in frequency order and the frequency should be given as accurately as possible. The full name of the station should be given together with the country from which it operates. The next item should either be details of the programme heard or the language used. The final item should be the time at which the broadcast was heard in GMT.

The equipment used is also of interest as it enables readers to make a comparison between their results and those of the reporter.

---

Reports should arrive by the 15th of the month and be addressed to the author at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

---

# SHORT WAVES

**S**UMMERTIME is aerial time, and, I hope, with the better weather, will come a renewed interest in that solitary slither of wire you claim to be the antenna. Funny things aeriels, most of them are "suck-it-and-see" affairs, even the ones in the handbooks. A good thing about aeriels is that it is seldom possible to do much damage to the receiver by trying out a different type.

How about spending a quiet evening to work out two different types of aeriels to try this summer. Try and design your own. How about a short vertical loaded with a coil at the bottom. Try tapping the coil, tuning it in series with a capacitor and again in parallel with the same capacitor. See what difference the new aerial makes to reception. If you are really serious about aeriels, and some amateurs make this fascinating field a favourite study, then you should number, amongst your treasured possessions, a grid dip oscillator and if possible, an antenna noise bridge.

One good way to begin is to measure yourself some electrical half wavelengths of coaxial cable at the particular frequencies of interest. Why half a wavelength? Because the impedance at one end of it will be repeated at one half wavelength further down the line. So, if you want to be sure that the impedance your cable sees up in the air at the antenna terminals is the same one your bridge is looking at on the ground, start slicing those halfwaves. Many circuits have appeared in *Practical Wireless* for grid dippers and both these and antenna noise bridges are sold commercially. Let me know how your wire wonders work.

## From the Post

Letters received have given a few hints and tips on items picked up by the simple art of r.f. eavesdropping (Well done, spies). **Stephen Burrell** (Gosport) says that a new one to listen for on or around 14.25MHz is AX9YR located on Cocos Keeling Island. Daytime is apparently the best time to QRX. Note from **Gordon Mayer** (London), that it is not advisable to send a QSL card to TR8VW in Gabon unless it is enclosed in a sealed envelope with no mention of amateur radio or callsigns etc. on the envelope. Anyone hearing TR8VW and sending confirmation please observe this request.

**Brian Gibson** (Chelmsford—no relation), underlines an item mentioned in the R.S.G.B. publication *Radio Communication* in January. This concerns G3ZGO receiving permission to use slow scan television on 14MHz and 2 metres. A thought here for those who would like to try their hand at something different.

Two meters only had one pair of faithful earholes tuned to it judging from this month's postbag. **J. Roberts** (Wigan) Logged these around 144.41MHz on s.s.b.; G3BA, G3EHM, G3JWZ, G3PFR, G3UDA, G3UQH, GW3UCB/P, G3VNQ, G3VKV, G8ASG,

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz ● Times in GMT

G8BCG, G8CVB. Gear is homebrew using an f.e.t. converter and tunable i.f. Other gear includes equipment for 70cm. but the only station heard recently is GB3SC on 433.5MHz. How about a squirt of seventy cents from you licensed types?

**Nicholas Hingley** (Halesowen), uses a T28 and a Unica UNR-30. Antenna is 66ft. end-fed bagged; GD3GMH, GI3WFA, GM3YCM and GM3YRK on Topband all on s.s.b. Eighty metres produced; ON5DO/AP, K4ADY, MP4BLJ, PZ1CU, WA2HNO/TF, WA6EGL/TF, VE1BT, VE1HP, ZB2A, ZC4IK, ZM4KE, 6W8DY, 9H1BL. Nicholas is 15 years old and current plans include the building of a 144MHz receiver.

Who's bought themselves a 9R-59DS and finding it a "pleasure to operate"? Ten out of ten if you said "**Richard Mortimer**" (Cardiff). Previous receiver was an H.A.C. model DX. A Mortimer-type meander through the wilds of 3.5MHz revealed; CM2RX, DL8PC, EA3RF, HB9AVQ/MM, HR2GK, KZ4MU, LA0AD, ON5VT, VP7NS, W/SH, XE1KB, YN1HSM, ZL4KE, ZL4NH. Antenna is a quarter-wave inverted 'Vee' and the transmission mode, I suspect, was phone, probably s.s.b. (*Is there any other?—Ed*).

**Stephen Kaye** sends a drawing of his aerial as seen by an ailing wood pigeon. The configuration looks intriguing, somewhat reminiscent of a varicose vein on a Japanese beetroot. The AR88D gets the other end of this 250ft. affair shoved smartly up its aerial socket and as a result gave the following information of happenings on eighty metres; EA8GZ, MP4BHH, VE1EI, W5/LR/TF, ZB2A, 6W8DY.

The same set up was exposed to 14MHz (or vice versa) and the following stations heard; CR7IK, CT2AK, FG7XL, HR2WTA, KH6CF/TF, LU3DSS, MIB, PY1NBG, PZ2AC, TR8MC, VE1AJ/M, VE3DBT, VE6AAV, VE8RCS, VP2VQ, VP7BJ, YV5CKR, ZE4JW, ZP5CF, ZS5XA, ZS6BLA, 4X4BL, 5Z4MO, 9H1CD, 9J2PV, 9Y4VV.

"By the time you receive this log I will have a 15 metre dipole", writes **Julian Iredale** (Llandudno). Meanwhile, back at the 132ft. long wire, the CR-70A and PR-30 responded to 14MHz s.s.b. signals from; CT3AN, EA6AL, JA1MIN, KL7HEU/P, SU1MA, VK5CI, VK6US, VP2MY, W6BH, W6JY, XE1PAY, ZL3FO, ZS4LF, 3A2FL, 4U1TU.

**S. Wainwright** (St. Helens), 9R-59DS, PR-30, 100ft. long wire did an audio survey of fifteen metres. Results include; AP2KS, CR4BC, EA8GZ, EL9C, ET3USA, F9VN/P/FC, FG7XLI, HS1ABU, OD5BA, PJ9VR, TA1SK/P/4X, VQ9RK, W6MSM, 4Z4KM, 4X4VB, 5Z4GK, 5N2AAE, 7Q7BC, 9G1WW.

A lean time for contest types because the merry month of May doesn't seem to have a serious contest in it. Never mind, the break can be spent plucking up the receiver ready for National Field Day which takes place this year on June 5-6.

*Logs, in alphabetical order please, to arrive by the 15th of the month to:*

**12, Gross Way, Harpenden, Herts.**



# PRIZE CROSSWORD

## WIN A £10 VOUCHER

### COMPETITION No. 2


#### How to enter

COMPLETE the crossword below and you will have the opportunity to win one of **five** £10 vouchers, exchangeable with an advertiser in **Practical Wireless**. The prizes will be awarded for the first five correct solutions checked on the closing date.

Send the completed form, with your full name and address in block letters, and post it in a sealed envelope to: **PRACTICAL WIRELESS CROSSWORD COMPETITION, 1-2 Bear Alley, Farringdon Street, London EC4X 1AJ (Comp.)** to arrive not later than the closing date: **Tuesday 15th June, 1971.**
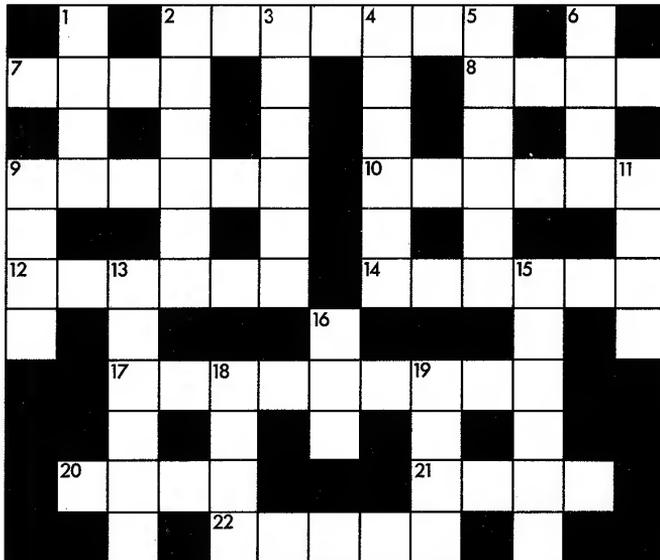
#### Rules

Entry is open to all readers in Great Britain, Northern Ireland and the Channel Isles, except employees (and their families) of IPC Magazines Ltd. and the printers of Practical Wireless. There is no entry fee, but each solution must be completed in ink or ballpoint pen on the proper printed coupon cut from Practical Wireless and bear the entrant's own full name and address. The Editor's decision in all matters is final and binding. No correspondence can be entered into. The winners will be notified and the result announced in the earliest possible issue of Practical Wireless.



Mr./Mrs./Miss .....

Full Address.....

Post to: PRACTICAL WIRELESS CROSSWORD COMPETITION  
1-2 Bear Alley, Farringdon Street, London, EC4X 1AJ (Comp.).

Closing date: 15th June, 1971

Cut out along this line

#### Clues Across

2. What a nice girl and a common component do when under current pressures. (7)
7. Well, a penalty or is it's effect only marginal? (4)
8. This may well snare an unwanted frequency. (4)
9. A final one of these is not usually welcome. (6)
10. Old cable covering. (6)
12. Brings a change to it's senses. (6)
14. Put in an active microphone element. (6)
17. A midget's greeting at high frequency. (9)
20. None is disarranged to produce an inert gas (4)
21. Faraday's one was not designed to hold wild beasts. (4)
22. I suppose a transistor junction does this. (5)

#### Clues Down

1. A pure wave form familiar in trigonometry. (4)
2. Although they pass on they are still with us. (6)
3. He soldiers on but is left out to make a good join. (6)
4. Sounds very much like a style I used to play records.(6)
5. Instead of wandering off these capacities can be difficult to get rid of. (6)
6. This leads to two types of field. (4)
9. and 16. N (4,3)
11. A tax applied to spirits and tobacco and sometimes used with a cycle. (4)
13. Displayed by a numicator. (6)
15. Basic force. (6)
16. See 8 Down.
18. This part of the loudspeaker is often conically shaped. (4)
19. Spark paths. (4)

# CROSSWORD No. 1

## WINNERS and SOLUTION

The Practical Wireless Crossword Competition No. 1 (in the February issue) was badly affected by the postal strike. Because of this entries were accepted until a week after the postal strike had ended. The first five correct entries opened win a £10 voucher, exchangeable with any advertiser in Practical Wireless.

The winners of competition No. 1 were:

Mr. H. R. W. Thurlow  
Gravesend, Kent

Mr. L. Reynolds  
Bath, Somerset

Mr. W. Bamford  
Hemel Hempstead, Herts.

Mrs. G. Rawling  
Keighley, Yorkshire

Mr. S. Turner  
Warrington, Lancs.

### SOLUTION TO COMPETITION No.1

1	C		2	E		3	M		4	B		5	S		6	G
7	R	A	D	I	O	S			8	F	A	C	T	O	R	
	I		I	T			9	D		F		O		E		
10	T	E	T	R	O	D	E		11	F	O	R	C	E		
	I		O	R		C				L		M		N		
12	C	O	R	E			13	R	E	G	E	N				
	S		S		14	B		I		D		15	L		16	D
					17	V		A		L		V		E		
19	S		20	P		S				21	S		M		T	
22	C	E	L	L	S			23	R	E	C	E	I	V	E	
	O		A		C		S			O		T		C		
24	O		U		T		P		25	E		F		F		E
	P		E		T					F		R		S		

### Servicing—Part 2 continued from page 137

type, which means that the emitters must be returned to a positive source, and this occurs through R201 for TR201 and R203 for TR202. The collectors are returned to negative chassis potential.

Automatic gain control (a.g.c.) is applied to the base of each transistor, via R202 to TR201 and R204 to TR202. The potential for this is picked up from the ratio detector.

### AUTOMATIC FREQUENCY CONTROL

Diode D202 is a varactor for automatic frequency control (a.f.c.). It shunts the v.h.f. oscillator inductor L204, in parallel with the trimmer C212. Reverse bias is obtained from zener diode D303 (bottom right of diagram) and applied through resistive circuits.

The ratio detector is returned to zener cathode through R325, while the varactor cathode is returned to the zener anode through R206, choke CH301, S7 and CH302. Static reverse biasing of the varactor is completed by its anode going to the zener cathode through S8 and R339.

The ratio detector (R606/R608 junction) is also connected to the varactor anode through R205, R305, S4 and R324.

Now, the two sides of the ratio detector mentioned represent 'points of balance,' so that when a station is tuned correctly the potential between the two sides is essentially zero. However, should the tuning tend to drift or be in initial error, then a positive or negative potential (depending on whether the tuning error is high or low) develops between the two points. This modifies the reverse biasing of the varactor in such a manner as to change its capacitance, providing tuning correction, (a.f.c.).

On a.m. a.f.c. is not required, of course, but a.g.c. is applied to TR302 from the a.m. detector, via R610 and R312. De-emphasis is given to the f.m. audio by R324 and C357, these components being out of circuit on a.m.

Switch sections S9, S10 and S11 are concerned with wavechange (long and medium) switching of the ferrite rod aerial, while S12, S13 and S14 change the wavebands of the a.m. local oscillator. This style of receiver thus contains two primary switching modes, for switching over a.m. and f.m. and for switching the a.m. wavebands. Some receivers have short-wave bands in addition to long and medium waves.

The audio section in Fig. 9 differs from that in Fig. 8 in that an n-p-n transistor TR304 is used to drive, from its collector, a pair of complementary output transistors, TR305/TR306. To get push-pull drive the bases of the pair need to be driven in the same polarity. This is because one is p-n-p (TR305) and the other n-p-n—hence the term complementary. The first audio transistor is TR303 and the set of four are d.c. coupled, with feedback (to reduce distortion and enhance frequency response) from the emitters of the output pair (where the speaker is connected) to the emitter of TR303. I shall be having more to say later in the series about negative feedback and about audio stages in general.

The Fig. 9 receiver is essentially for 9V battery operation, but the inset at the top right shows the circuit of a power unit for mains operation. This has a mains transformer with fully isolated primary and secondary windings (essential for safety), a bridge rectifier with a 500µF reservoir capacitor and a series regulator transistor with a base reference potential stabilised by a zener diode.

**END OF PART TWO**

# practically wireless

commentary by **HENRY**

No. 80

## Durability

**I** WONDER what the world of five thousand years hence will think when they open the time capsule in Osaka Castle Park.

This was a collection of bits and pieces representative of 1970, including a photomask made by IC technology, a microbook and a plutonium timepiece, buried by Matsushita as part of their contribution to EXPO 70, in Japan.

If the whole exhibition, which covered a site of 815 acres near Osaka, gave contemporary visitors a feeling that H. G. Wells had been actively engaged on the overall design, and that the intention was to afford a glimpse of 'things to come', then future historians will scan the records and think us a very peculiar bunch.

One of our peculiarities is the economic value we put on electronic goods. Built-in obsolescence is a taboo phrase. Yet the logic of disposability is inescapable. With all our sophisticated techniques of mass production, it should be possible to make a cheaper version, though less rugged, of practically any piece of radio or electrical equipment. When it breaks, chuck it!

It should be—probably is: but we are not yet, as a society, ready for such techniques. We want our gear to last and last and last . . .

Henry was tickled to see an interview of Michael Holroyd a while ago in the S\*ND\*Y T\*M\*S.



Exploded in a photographer's face.

Philip Oakes had asked this eminent biographer about his electronic aids. Mr. Holroyd admitted that he could not get on with them.

'I have the sort of memory that tells me, eventually, that what I want is in the fourteenth drawer on the left-hand side.'

He was hesitant about photocopying. Someone had once told him that the ink faded in time. '... imagine that! Archives of blank sheets . . .' What if the timebomb explodes in Osaka Castle Park to reveal that the microdot has been overexposed to the plutonium clock and is now a mass of magnified squiggles? What *will* they think of us?

But the bit that got Henry was the reference to Mr. Holroyd's brief venture into tape recording. '... one exploded in a photographer's face and he was almost choked by the escaping tape.'

That wouldn't have happened with a Ferrograph. I've known them smoke a bit—but explode, never!

Some little while ago there was a flurry of panic amid the radio service fraternity, when one manufacturer, bringing out his range of 'packaged circuits', foretold the end of the diagnostic wizard. Armed with his AVOMeter (another item that seems to go on for ever, I may say) and extensive knowledge of the problems likely to beset wireless equipment, he happily pulled it to pieces on the kitchen table, waved his magic wand (25-watt Solon, not even a Weller, thermostatically controlled!) and departed to the strains of happy music.

In my business, I've had numerous requests to service such disposable items as Philips Popmaster radios, built around their printed circuit, designed neither to be treated roughly nor repaired. They are first-generation disposable items. Some of the IC designs we are seeing now follow along similar lines. You don't try and mend them.



What did Mrs. Henry donate to the jumble sale?

The irony is that many items we would like to see disposable—or, at least, dispensable—linger on forever, as unwearable as one's old Harris Tweed gardening jacket.\*

To quote a *Daily Mail* leader of last Christmas, 'In spite of Biblical injunctions against possessions, there are some adjuncts to living we grow ridiculously fond of.'

Like a Williamson amplifier, for instance, the 'Premier' TV that actually worked first time, old jazz records, or an F.G. Rayer Shortwave Three. '... there is a range of household goods, the detritus of modern living, which annoys because we'd like to get rid of it but can't.'

Like my old wind-up gramophone, the mains-energised speakers that 'just may come in handy one day' and a few blocks of paper capacitors with screw terminals that would at least add mass to the loudspeaker cabinet if I eventually decided to use them as part of a crossover unit.

I'd dispose of them, sure; like I'd dispose of the Ferro 4A if someone decided to get rid of their Series Seven at a knock-down price. *That's* what Henry means by disposability.

\*That reminds me. What *did* Mrs. Henry donate to the jumble sale last week?

# COMPLETE STEREO SYSTEM

FOR ONLY

# £40.95

CARRIAGE £1.75



**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on off switch. Brushed aluminium front panel. Solid teak cabinet. Size 12 x 4½ x 3½in. high (Amplifier available separately if required £14.95 Carr. 40p.)

**PREMIER STEREO SYSTEM "TWO"**  
As system "ONE" above but with Garrard SP25.  
**PREMIER PRICE £47 Carr. £1.75**

## PREMIER QUALITY MICROPHONES

Precision made, beautifully designed and offering reliability at reasonable price.

**PANON MKC-52 DYNAMIC WITH BUILT-IN VOLUME CONTROL**

Frequency response 50-13,000 Hz. Dual impedance 50K ohms (-52 db) and 150 ohms (-71 db) Cardioid uni-directional. On/Off volume control. Die cast body satin chrome finish. Complete with 20ft. cable and stand adaptor.

**PREMIER PRICE £7.97, P. & P. 20p.**

**PANON MKC-55 DYNAMIC**

Frequency response 60-13,000 Hz. Impedance 50K ohms. (-55 db) Cardioid uni-directional. Die cast body satin chrome finish. Complete with 20ft. cable and stand adaptor.

**PREMIER PRICE £6.97, P. & P. 20p.**

**PANON MKO-47 MINIATURE DYNAMIC**

Frequency response 60-13,000 Hz. Impedance 50K ohms (-59 db). Can be used with stand, hand held or around neck. Die cast body satin chrome finish. Features removable windscreen. Complete with 8ft. cable, stand adaptor and Lavalier cord.

**PREMIER PRICE £5.97, P. & P. 20p.**

**PANON MKO-45 3-WAY DYNAMIC**

Frequency response 60-12,000 Hz. High impedance. Complete with 8ft. cable, table stand and Lavalier cord.

**PREMIER PRICE £2.87, P. & P. 20p.**

**PANON MKC-54 DYNAMIC**

Frequency response 60-13,000 Hz. Impedance 50K ohms (-60 db) and 150 ohms (-71 db). On/Off switch. Complete with 20ft. cable and stand adaptor.

**PREMIER PRICE £2.97, P. & P. 20p.**



MKC-52



MKC-55



MKC-54



MKO-47




MKO-45

## E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 9½in tweeters and crossover network. Impedance 8 or 15 ohms. Handling capacity 10W. Brand new.

**£3.47 P. & P. 40p**

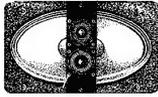

## HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

**£2.47 P. & P. 20p.**



STEREO STETHOSCOPE SET Low imp. £1.25

P. & P. 10p.

MONO STETHOSCOPE SET Low imp. 52p, P. & P. 10p.

## VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2½in. suitable for crystal microphone low impedance microphones, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, photophone output. Attractive teak wood grain finish case.



MONO MODEL £3

STEREO MODEL £3.47 P. & P. 12p



## TAPE CASSETTES

C60 (60 min.)	37p	3 for £1.05
C90 (90 min.)	62p	3 for £1.80
C120 (120 min.)	87p	3 for £2.55

All cassettes can be supplied with library cases at 3p. extra each

## METER BARGAINS



**MODEL GT-800 MULTIMETER**  
A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 ohm pV). AC Voltage: 10, 50, 250, 1,000V (1,000 ohm pV). DC Current: 1mA, 100mA. Resistance: 0-100K ohms. Decibels: -10 +22dB (at AC 10V range) £2.47, P. & P. 17p.



**MULTIMETER 20,000 O.P.V.**  
Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4½ x 3¼ x 1". RANGES—DC Voltages: 0, 0.5, 5, 50, 500mA. Resistance: 0, 6k, 60k, 6M, 60M (30, 3k, 30k, 300k ohms at centre scale). Capacity: 10µf to .001µf. 50µf to 1µf. Decibels: -20 to +22 db. £4.90, P. & P. 17p.



**MODEL CT-620 MULTIMETER**  
RANGES—DC Voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). AC Voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). DC Current: 0, 50mA, 0.5, 5, 50, 500mA. Resistance: 0, 6k, 60k, 6M, 60M ohms. Decibels: -20 db to +62 db in 5 ranges. £5.82, P. & P. 17p.




**MODEL CT-330 MULTIMETER**  
A de-luxe, accurate and high sensitivity instrument. Low-resistance selector switch, clear scales and rugged meter movement. RANGES—DC Voltages: 5, 25, 50, 500, 2,500V (20,000 O.P.V.). AC Voltages: 10, 50, 100, 500, 1,000V (10,000 O.P.V.). DC Current: 50mA, 2.5, 250mA. Resistance: 6k, 6M ohms. Decibels: -20 to +22 db. Capacitance: 10µF to 0.100µF, 0.100µF to 0.1µF. £7.35, P. & P. 17p.



**MODEL 630 MULTIMETER**  
RANGES—DC Voltages: 0, 3, 15, 60, 300, 600, 1,200V (30,000 ohms/V). AC Voltages: 0, 6, 30, 120, 600, 1,200V (15,000 ohms/V). DC Current: 0, 0.03, 3, 30, 300mA. Resistance: 0, 16k, 160k, 1.6M, 16M ohms (10, 100, 10k, 100k ohms at centre scale). Decibels: -20 to +63 db. £7.97, P. & P.

## SP25 MKIII SPECIAL!

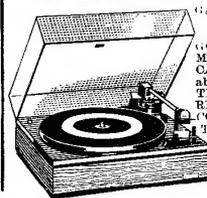

GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 850 or AT58 MAGNETIC STEREO CARTRIDGE as available COMPLETE IN TEAK FINISH WITH RIGID PERSPEX COVER.

Total list price over £29.

**PREMIER PRICE**

**£19.90**

P. & P. 50p.

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP8 3" 250' P.V.C.	88p	LP6 5½" 1200' POLYESTER	62p
TT8 3" 450' POLYESTER	87p	DT6 5½" 1800' POLYESTER	£1.12
DT3 3½" 600' POLYESTER	57p	TT6 5½" 2400' POLYESTER	£1.37
SP5 5" 600' P.V.C.	45p	SP7 7" 1200' P.V.C.	62p
LP5 5" 900' P.V.C.	50p	LP7 7" 1800' ACETATE	75p
DT5 5" 1200' POLYESTER	75p	DT7 7" 2400' POLYESTER	£1.25
		TT7 7" 3000' POLYESTER	£2.50

TAPE SPOOLS 3" 10p, 5", 5½", 7" 9p.  
Post and Packing 5" 5p, 6", 5½", 7" 10p. (3 reels and over Post Free).



# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



## SIMPLE SHORTWAVE RECEIVERS



by F. A. Baldwin  
**FOUR BASIC DESIGNS**  
1, 2 and 3 VALVES

If you are interested in the hobby of receiver construction and short wave listening this is the book for you. It covers the whole field of s.w.'ing from construction to operating.

140 pages

**PRICE 80p**

Copies may also be obtained direct from the Publishers 86p including postage.

Published by:  
**Data Publications Ltd.**  
57 Maida Vale, London, W.9

## RADIO CONSTRUCTOR

MAY issue contains  
**NON-OVERLOAD POWER SUPPLY**

★  
**TRANSISTOR R.F. PRESELECTOR**  
★  
**LCR TONE CONTROL CIRCUIT**  
★  
**PLUS MANY OTHER PROJECTS**  
★  
**ON SALE NOW 20p**

Copies may also be obtained direct from the Publishers 24p including postage.  
Published by:

**Data Publications Ltd.**  
57 Maida Vale, London, W.9

## RADIO CONSTRUCTOR

## poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker



Super-thin construction permits new installation ideas.

Power capability: 20 watts peak  
Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input  
Input impedance: 8 ohms  
Operating temperature range: -20°F to +175°F  
Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16"  
Weight: 19 ounces

£ 5.75 (p&p20p) each

Stereo pair £11.40 post free

**web europa**

P.O. Box 162 Bushey  
Watford WD2 1LF

Est. 1943 **JOHNSONS** Tel: 24864

**New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast.** Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post paid, direct from makers. S.A.E. for literature.

**JOHNSONS (RADIO)**  
St. Martin's Gate, Worcester  
**WR1 2DT**

(A Division of the G-SAN ORGANIZATION)

## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE

IR5	-27 DK32	-38 EF91	-12 PL36	-49
IR5	-31 DK91	-27 EP183	-28 PL81	-46
IT4	-16 DK92	-41 EP184	-30 PL82	-31
3S4	-28 DK96	-37 EL33	-54 PL83	-84
3V4	-37 DL35	-33 EL84	-24 PL84	-31
630L2	-57 DL92	-28 EY31	-35 PL800	-64
6A05	-25 DL94	-37 EY36	-31 PL504	-55
6BW7	-57 DL86	-37 EZ50	-25 PY32	-54
6F23	-70 DY86	-26 EZ81	-23 PY33	-54
6F25	-60 DY87	-26 K791	-54 PY81	-26
2EL9GT	-22 EAB080	-31 K795	-82 PY82	-26
30C15	-62 EB91	-11 N78	-55 PY800	-25
30C18	-63 EBC33	-38 PC86	-49 PY801	-25
30F5	-72 EBF69	-30 PC88	-49 R19	-31
30FL1	-63 EBC31	-17 PC97	-39 U26	-58
30FL14	-70 EBC82	-20 PC900	-35 U26	-59
30L15	-60 ECC83	-23 PCC84	-31 U191	-60
30L17	-71 ECF80	-28 PCC89	-46 U251	-70
30P4	-60 ECF82	-28 PCC189	-50 U29	-70
30P19	-60 ECH35	-37 PCF85	-39 UABC80	-35
30PL1	-61 ECH81	-28 PCF85	-45 UBF89	-31
30PL14	-67 ECL80	-33 PCF801	-32 UOC85	-36
CH33	-65 ECL82	-11 PCF899	-44 UCH81	-32
DAC32	-33 ECL86	-37 PCF895	-83 UCL82	-34
DAF91	-21 EFB39	-22 PCL82	-33 UCL83	-49
DAF96	-35 EFB50	-24 PCL84	-35 UFB89	-30
DF33	-37 EFB56	-28 PCL85	-42 ULS4	-32
DF91	-18 EFB86	-31 PCL88	-40 UY85	-27
DF96	-35 EFB89	-24 PFL200	-54 Z77	-18

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra. Office address, no callers.

**GERALD BERNARD**

83, OSBALDESTON ROAD,  
STOKE NEWINGTON,  
LONDON, N16

**BRAND NEW AR8SD COMMUNICATIONS RECEIVERS.** AC mains input 110 volts or 250 volts. Frequency in 6 bands 535 kc/s up to 32 megs, output impedance 2-5-600 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

**COMPUTER BOARDS** Min 30 transistors and diodes and 700 etc. 10 boards at 50p plus 121p p.p.; 25 boards at £1.12p plus 221p p.p.

**BARGAIN PARCELS** 14lb at £1.45 plus 32p p.p.; 28lb at £2.75 plus 62p p.p.; 56lb at £4.50 plus £1.25 p.p. Contains pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £25. Lucky Dip Service.

**FURZHILL BEAT FREQUENCY OSCILLATOR** 0-10 kc/s, 110/250 volt. Good condition complete with spares. £5.50 plus £1.25 p.p.

**VHF Receiver, Type 715**, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3 plus £1 p.p.

**VHF AERIAL TUNING UNITS** consisting of the following: 1-1/4" 500 micro/ampmeter, 1 small 2-gang 75 PF capacitor, 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 35/30 watts R.F. input. Size only 4 1/4" x 4 1/4" x 8" Sealed. Price £1.37p p.p. 20p

**CRYSTALS AS NEW:** Hc 6u, 5,345; 5,030; 5,005; 4,942; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s and 10 x 7465 Kc/s. 50p each plus 2p p.p.

**SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS.** 10% tolerance 1/2 & 1 watt. Preferred values in packets of 10. Our price 50p per 100, 50p per 200, £1.35 per 300, 50p at £2.12p. Our selection, p.p. 8p per 100 and 24p per extra 100.

**TRIMMER BARGAINS.** These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details. Contents 12 trimmers, some ceramic caps. Xtal frequency 33RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal—60p per doz. plus 17p p.p.  
Trimmers with Xtal—75p per doz. plus 17p p.p.  
Also 30 PF min. brand new air spaced.  
50p per doz. plus 17p p.p.

**HERO MXS IN NEW CONDITION** with 5 general coverage coil units including spare set of valves less power supply. Tested £25 p.p. £1.50.

**ANY HEIGHT AERIAL TUBULAR SECTIONS** 1" dia x 3 ft. long. Brass screw in type, copper coated and painted. New 20p each, p.p. 5p. each. Minimum order 6.

**SIGNAL GENERATORS OSCILLATOR No. 2.** Size 13in. x 3 1/2in. x 5in. Ideal for VIFP work. 20-50 Mc/s. Functions are AM/CW. Deviation up to 40 Kc/s RF meter. Measuring levels: RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories: 280V AC 12V DC. £20 plus 75p p.p.

**AERIALS NEW CONDITION.** Whip type 4ft. 25p, 14ft 77p. Used condition 4ft. 20p, 14ft. 62p. All collapsible type p. and p. 4ft. 10p, rest at 17p. Bases for above 25p, p.p. 12p. New matching unit coax connection for above 30p, p.p. 5p.

Huge release of valves for the 62 set TX/RX, in original rubber packing consisting of QV0477 x 61M, ARP12 etc, 10 valves in all at the bargain price as seen £87p plus 17p p.p.

New Headphone and Mike rubber muff type. Low impedance. 97p. p. & p. 17p.

New Aerial Wire on boards 7/22 uncovered. Length 76ft. 40p, 90ft. 47p, 100ft. 55p, p.p. 12p. used condition 50p, p.p. 17p.

Headphones, ex Gov. DLR No. 5 high impedance. New 87p 17p p.p. Used condition 62p 17p p.p.

Meters moving coil ex equipment, good condition. Also 20 amp DC, 40 amp DC, and R.F. Therm-Couple Meters 0-1 amp and 0-2.5 amp, 2in. diameter. 50p post and packing 25p.

Heavy New Coax Cable 750HM will handle at least 1KW 50ft length, Plug on end, £1.70p + 30p p.p.

Also 1/2 75 ohm Coax in 50ft coils with BNC plugs good condition, price £1 + 30p p.p.

2 BNC plugs on short length coax cable large size low loss plugs 40p + 5p, p.p.

Block Type capacitor TCC SUP + 15% 350 VDC WKG 60°C, 250 VDC WKG 70°C Type 62 CIM Price 40p + 13p, p.p. New.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

**A. H. THACKER,**

Radio Dept.,  
HIGH STREET, CHESLYN HAY,  
Nr. Walsall, Staffs.

# CRYSTAL BAND-EDGE MARKER

A.S. CARPENTER G3TYJ

**A**LTHOUGH many receivers in use at amateur and s.w.l. locations are fitted with a band-edge marker; many are not, and in these cases it becomes very difficult to locate any amateur band precisely. This is especially true if the receiver in use is of the general-coverage type. Ex-services receivers such as the CR100 for example fulfil the listening needs of many and, although some excellent specimens of this type are in use, their 'drifty' nature offers a further hazard to band-edge finding and retention.

In more sophisticated receivers designed especially for the amateur bands the problem is simplified by incorporating a built-in 'Marker' whilst a further refinement may be provision of limited panel control of the local oscillator frequency. Some receivers fitted with a marker are the Heath RA-1, Eddystone 888A and EA12 and the Star SR550. In the SR550 receiver, for example, one merely selects the desired amateur band, places the scale pointer at the l.f. band end and switches in the built-in calibrator—which uses a 3.5MHz crystal. The local oscillator is then made to fall into step with the marker signal by means of a panel-fitted 'Set' control.

The facility for accurate amateur l.f. band edge location, although useful to s.w.l.'s, is even more important to the c.w. transmitting fraternity and since the amateur c.w. segments are always low of those used for a.m. or s.s.b., precise location of l.f. band ends is essential.

Where no calibrator or marker is in existence, it is an easy matter to provide a self-contained unit that will enable the user to locate all amateur bands '80' through to '10' quickly and reliably. A pocket-sized, self-powered crystal controlled l.f. band edge marker can in fact be constructed in a single evening and will cost but £2 approximately after allowing inclusion of a new crystal of accuracy 0.005%.

Since the author usually finds it a chore connecting and disconnecting 'outboard' items it is a good plan to arrange for the Marker to be left permanently in position close to the receiver with which it is to be used. This is easily done and Fig. 1 shows how

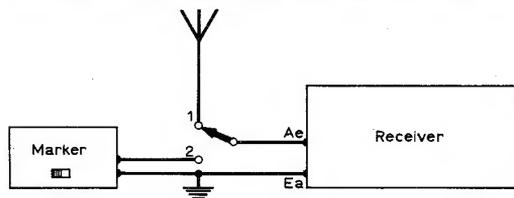


Fig. 1.

simple switchery can be employed to select either the aerial or the Marker at the same time permitting no Marker signals to reach the aerial direct. If a further switch section is added the d.c. power supply required by the marker can also be controlled. With these considerations in mind the simple Marker

shown in Fig. 2 was evolved, the end product being found completely satisfactory for the purposes required of it. The device should not of course be confused with a Crystal Calibrator which is a more sophisticated item with extended facilities.

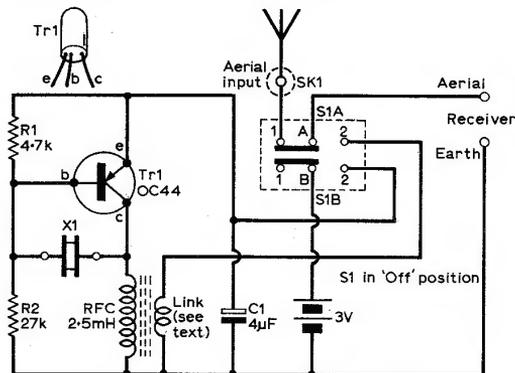


Fig. 2: The circuit of the band-edge marker.

## CIRCUIT



Looking at Fig. 2 it is noted that oscillations are produced at the crystal frequency due to X1 being connected between base and collector of Tr1, output being developed across choke R.F.C. and thereafter inductively coupled for connection to the receiver. Depending upon the potential applied and the type of transistor used the current drain demanded is of the order of 2mA when the circuit is functioning from 3V. Prohibitively high current will flow if the circuit is in a non-oscillating state so this enables one to make a post-construction test using a test-meter set to read say 0.50mA initially.

Switch S1 enables the user to leave the Marker in position near the receiver at all times. When S1 is in the position indicated, the aerial is fed direct through to the receiver and the Marker is 'dead'. Moving the slide switch to its alternative position disconnects the aerial and connects the receiver aerial socket to the Marker outlet at the same time applying battery power to the Marker. In this position a very strong marker signal will be received if the receiver is tuned to 3.5MHz whilst additional 'harmonic markers' will be tuneable at 7, 10.5, 14, 17.5, 21, 24.5, 28MHz and so on. The markers grow less strong as the receiver is tuned towards higher frequencies but detection is still easy even at 28MHz and higher. To aid recognition, the receiver b.f.o. and 'S' meter can be made use of temporarily.

Some of the harmonic markers available, viz: those at 10.5, 17.5 and 24.5MHz may be of little practical use to those interested purely in amateur band location and can be disregarded.


—continued on page 161

# GOING BACK...

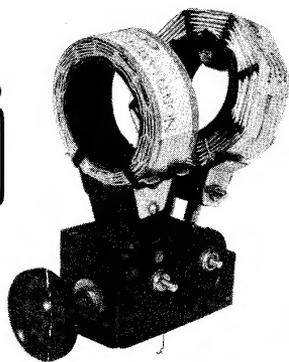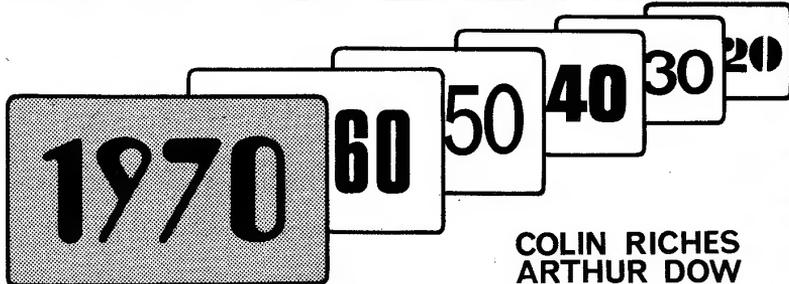

COLIN RICHES  
ARTHUR DOW

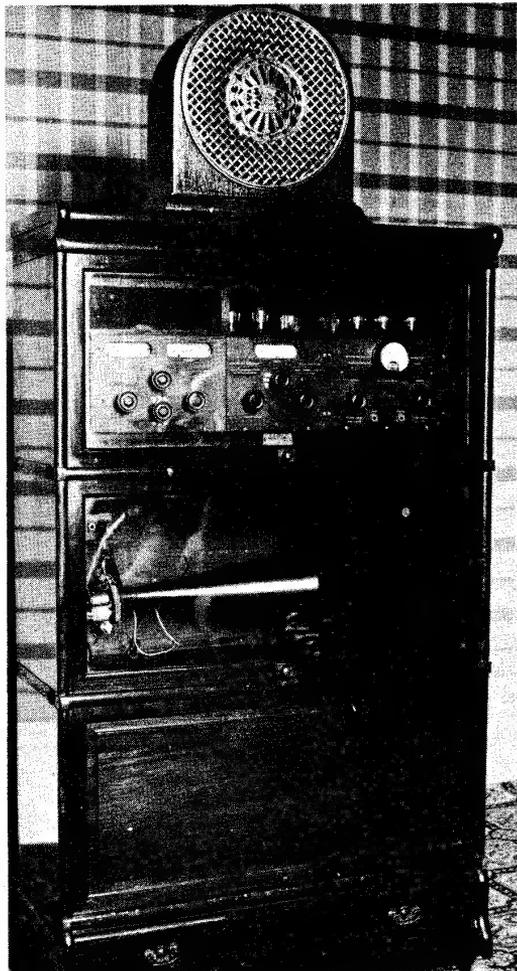**E**DWARD Harrison of Rochdale, Lancashire, writes to tell us that the set in the photograph was manufactured by the Radio Communication Co., 34/35 Norfolk Street, London, W.C.2—their general range of sets being “Polar” Radiophones. Its type is RA33, 34, 35 and has seven valves. There



were *originally* bright emitters—5 “R” or “ORA” and two “PA3” or “LS3”. The present valves are PMX5X (Mullard) R5V, PM5X and two PM6’s. The extension speaker on top is an Amplion brass fret and reentrant horn. The three sections of the receiver can clearly be seen. They are h.f., i.f. and a.f. amplifiers. The three white slots shown are three interchangeable coils. The small plate on the bottom is engraved: “Supplied and fitted by Harry Crompton, Radio Engineer, 61 Cateaton Street, Bury”. The next lowest compartment shows the Amplion 2k $\Omega$  loudspeaker unit with a slender horn reaching into the mahogany slatted sound box. The third and lower compartment contains the 6V accumulator—an Exide charger—a Philips h.t. only unit with valve rectifier and six h.t. tapings.

The last licence Mr. Harrison has knowledge of was in 1943 but after all these years with new accumulator, external wiring renewed, cleaning of tarnished contacts and terminals, the set works very well. It has, of course, the 9V grid bias battery.

It is interesting to note, he says, that The Radio Communication Co. was one of the original firms that formed the British Broadcasting Company Limited in 1923. This set must therefore be prior to 1927.

A few foreign stations can be tuned in after dark with the limited aerial (from window side to gutting).

He only has one complete set of coils—these cover 350-500m and means that he is at the moment limited to Radio 1. Also, Mr. Harrison is looking for two sets of coils—either Range 4A (1200-1800m) or Range 3 (1000-20000m). Can anyone help him?

## W. E. Audio Amp.

We recently heard from Mr. Alan Douglas (the electric organ expert) that he was interested in the old Western Electric audio amplifier shown in the February “Going Back” article. He informs us that he has had several of these units from time to time.

Alan states that he had one of the first amateur stations in this country in 1912 and did a lot of experimental work on speech modulation of arc transmitters. He was also the designer of the first self-contained commercial portable radio set.

Alan goes on to say, “The Western Electric amplifier shown in the March issue reminds me of several interesting details. This audio circuit was designed

## TRANSISTORS

**NEW LIST—NEW PRICES  
SEND FOR FREE CATALOG TODAY**

**BRAND FULLY  
NEW GUARANTEED**

2N404	22p	BAY81	7p	BFY73	17p
2N596	17p	BC138	17p	BFY74	40p
2N897	17p	BC107	12p	BFY90	65p
2N706	10p	BC108	12p	BSX20	17p
2N706A	12p	BC109	12p	BSX21	37p
2N930	25p	BC110	12p	BSY96	15p
2N1131	30p	BC114	85p	BSY96A	15p
2N1132	30p	BC116	32p	BSY96A15p	
2N1302	20p	BC116	40p	BY109	15p
2N1303	25p	BC116A	45p	BY126	15p
2N1304	25p	BC115	37p	BY127	20p
2N1305	25p	BC119	50p	BY182	85p
2N1306	25p	BC134	87p	BY210	20p
2N1307	25p	BC135	30p	BY211	35p
2N1308	30p	BC136	35p	BY212	30p
2N1309	25p	BC137	40p	BY213	25p
2N1613	22p	BC138	40p	BY2161.00p	
2N1711	25p	BC147	17p	GET102	30p
2N1712	75p	BC148	17p	GET111	40p
2N2160	65p	BC149	20p	GET880	37p
2N2218	80p	BC154	87p	GET882	25p
2N2219	82p	BC157	20p	MAT100	25p
2N2222	30p	BC158	17p	MAT101	30p
2N2222A	37p	BC159	20p	MAT120	25p
2N2369	20p	BC177	25p	MAT121	30p
2N2484	85p	BC178	25p	MJE2801	21.37p
2N2486	75p	BC178	17p	MJE2802	21.37p
2N2904	30p	BCY30	25p	MJE2870	87p
2N2904A	32p	BCY31	30p	MJE2870	87p
2N2905	37p	BCY32	30p	MJE2870	87p
2N2906	30p	BCY33	30p	MJE2870	87p
2N2906A	32p	BCY34	30p	MJE2870	87p
2N2907	37p	BCY38	40p		
2N2926	15p	BCY39	40p	MPP102	42p
2N2931	25p	BCY41	15p	MPP103	40p
2N2935	85p	BCY41	15p	MPP106	40p
2N2936	85p	BCY42	15p	MPP106	40p
2N2937	75p	BCY43	20p	NKT213	25p
2N2925	1.10	BCY48	25p	NKT214	15p
2N2925	1.10	BCY49	25p	NKT213	25p
2N2925	1.10	BCY50	20p	NKT217	40p
2N2925	1.10	BCY51	20p	NKT227	20p
2N2925	1.10	BCY52	15p	NKT407	75p
2N2925	1.10	BCY53	15p	NKT407	75p
2N2925	1.10	BCY54	15p	NKT407	75p
2N2925	1.10	BCY55	15p	NKT407	75p
2N2925	1.10	BCY56	15p	NKT407	75p
2N2925	1.10	BCY57	15p	NKT407	75p
2N2925	1.10	BCY58	15p	NKT407	75p
2N2925	1.10	BCY59	15p	NKT407	75p
2N2925	1.10	BCY60	15p	NKT407	75p
2N2925	1.10	BCY61	15p	NKT407	75p
2N2925	1.10	BCY62	15p	NKT407	75p
2N2925	1.10	BCY63	15p	NKT407	75p
2N2925	1.10	BCY64	15p	NKT407	75p
2N2925	1.10	BCY65	15p	NKT407	75p
2N2925	1.10	BCY66	15p	NKT407	75p
2N2925	1.10	BCY67	15p	NKT407	75p
2N2925	1.10	BCY68	15p	NKT407	75p
2N2925	1.10	BCY69	15p	NKT407	75p
2N2925	1.10	BCY70	15p	NKT407	75p
2N2925	1.10	BCY71	15p	NKT407	75p
2N2925	1.10	BCY72	15p	NKT407	75p
2N2925	1.10	BCY73	15p	NKT407	75p
2N2925	1.10	BCY74	15p	NKT407	75p
2N2925	1.10	BCY75	15p	NKT407	75p
2N2925	1.10	BCY76	15p	NKT407	75p
2N2925	1.10	BCY77	15p	NKT407	75p
2N2925	1.10	BCY78	15p	NKT407	75p
2N2925	1.10	BCY79	15p	NKT407	75p
2N2925	1.10	BCY80	15p	NKT407	75p
2N2925	1.10	BCY81	15p	NKT407	75p
2N2925	1.10	BCY82	15p	NKT407	75p
2N2925	1.10	BCY83	15p	NKT407	75p
2N2925	1.10	BCY84	15p	NKT407	75p
2N2925	1.10	BCY85	15p	NKT407	75p
2N2925	1.10	BCY86	15p	NKT407	75p
2N2925	1.10	BCY87	15p	NKT407	75p
2N2925	1.10	BCY88	15p	NKT407	75p
2N2925	1.10	BCY89	15p	NKT407	75p
2N2925	1.10	BCY90	15p	NKT407	75p
2N2925	1.10	BCY91	15p	NKT407	75p
2N2925	1.10	BCY92	15p	NKT407	75p
2N2925	1.10	BCY93	15p	NKT407	75p
2N2925	1.10	BCY94	15p	NKT407	75p
2N2925	1.10	BCY95	15p	NKT407	75p
2N2925	1.10	BCY96	15p	NKT407	75p
2N2925	1.10	BCY97	15p	NKT407	75p
2N2925	1.10	BCY98	15p	NKT407	75p
2N2925	1.10	BCY99	15p	NKT407	75p
2N2925	1.10	BCY00	15p	NKT407	75p

## HENRY'S LOW COST INTEGRATED CIRCUITS

**WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW CERAMIC FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS**

Part Number	Description	Price 1-49	Price 50-99	Price 100+	Price 500+
7400	Quad 2-Input NAND Gate	25p	20p	18p	15p
7401	Quad 2-Input NAND Gate Open Collector	25p	20p	18p	15p
7402	Quad 2-Input Positive Nor Gate	25p	20p	18p	15p
7404	Hex Inverter	25p	20p	18p	15p
7405	Hex Inverter with Nor Collector	25p	20p	18p	15p
7410	Triple 3-Input NAND Gate	25p	20p	18p	15p
7411	Single 8-Input NAND Gate	25p	20p	18p	15p
7412	Dual 4-Input Buffer Gate	25p	20p	18p	15p
7441	BCD to Decimal Decoder and NIX Driver	£1.00	80p	80p	75p
7442	BCD to Decimal Decode (TTL)	£1.00	80p	80p	75p
7450	Dual 2-Input and/or/not Gate—Expandable	25p	20p	18p	15p
7453	Single 3-Input and/or/not Gate—Expandable	25p	20p	18p	15p
7460	Dual 4-Input—Expandable	25p	20p	18p	15p
7470	Single JK Flip Flop—Edge Triggered	40p	35p	30p	25p
7472	Single Master Slave JK Flip Flop	40p	35p	30p	25p
7473	Dual Master Slave JK Flip Flop	45p	40p	35p	30p
7474	Dual D Flip Flop	45p	40p	35p	30p
7475	Quad Bistable Latch	£1.00	80p	80p	75p
7476	Dual Master Slave Flip Flop with Preset	50p	45p	40p	35p
7483	Four Bit Binary Counter	£1.00	80p	80p	75p
7480	BCD Decoder	£1.00	80p	80p	75p
7482	Divide by 12, 4 Bit Binary Counter	£1.00	80p	80p	75p
7483	Divide by 16, 4 Bit Binary Counter	£1.00	80p	80p	75p
7484	Dual Entry 4 Bit Shift Register	£1.00	80p	80p	75p
7485	4 Bit Up Down Shift Register	£1.00	80p	80p	75p
7486	5 Bit Shift Register	£1.00	80p	80p	75p

Data available for above series in booklet form, price 10p. (Ref. No. 30)  
Larger quantity prices Extra. 4 Dual Inline 14 Pin Sockets 30p each, 16 Pin 85p each

## TRIACS GENERAL ELECTRIC

P.I. Cur. (All stud mounting)  
Type Volts rent 1-49 50+ 100+ 500+ 1000+

8C36A	100	3amps	80p	75p	65p	60p
8C36B	400	3amps	80p	75p	65p	60p
8C36C	400	3amps	£1.00	85p	75p	70p
8C40A	100	6amps	£1.00	85p	75p	70p
8C40B	200	6amps	£1.20	£1.00	85p	80p
8C40C	400	6amps	£1.20	£1.00	85p	80p
8C45A	100	10amps	£1.25	£1.10	£1.00	90p
8C45B	200	10amps	£1.25	£1.20	£1.10	£1.00
8C45D	400	10amps	£1.50	£1.35	£1.20	£1.10
8C50A	100	15amps	£1.75	£1.50	£1.35	£1.20
8C50B	200	15amps	£1.75	£1.50	£1.35	£1.20
8C50D	400	15amps	£2.00	£1.75	£1.50	£1.35
8C40E	200	6amps	£1.50	£1.25	£1.10	£1.00
8C40F	100	10amps	£1.75	£1.50	£1.35	£1.20
8C50E	500	15amps	£2.25	£2.00	£1.75	£1.55
DIAC	8T2	20p				

Larger quantity prices extra. 4 Dual Inline 14 Pin Sockets 30p each, 16 Pin 85p each

## R.C.A. INTEGRATED CIRCUITS

LINEAR TYPES

CA3005	£1.95	CA3095	£1.95
CA3011	75p	CA3096	90p
CA3012	90p	CA3098	85p
CA3014	£1.45	CA3041	£1.10
CA3015	£1.10	CA3043	£1.40
CA3020	£1.95	CA3044	£1.95
CA3021	£1.55	CA3046	85p
CA3023	£1.25	CA3048	£2.25
CA3026	£1.00	CA3051	£1.15
CA3028A	£1.30		

Data Notes 10p (Ref. No. 30)

## INTEGRATED CIRCUITS

MFC4000P	Motorola	£1.18
IC.10	Sinclair	£2.75
FA246	7 Watt	£2.45
TAA263	Mullard	£1.97
TAD100	Mullard	£1.75
TAD110	Mullard	£1.87
MC1503	Motorola	£2.40
UL900	Fairchild	40p
UL914	Fairchild	60p
UL923	Fairchild	40p
LSX90C	Fairchild	7p
MC1304	Motorola	£2.75

## ZENER DIODES

400 M/W 5%	1 Watt 5%
Miniature	Plastic Wire Ends
BYZ Range	6.8 Volt all voltages to 100 Volts
All voltages 3.3 Volt—33 Volt.	25p each.
15p each.	25+ ..... 18p
25+ ..... 15p	100+ ..... 18p
100+ ..... 10p	500+ ..... 15p
500+ ..... 8p	1000+ ..... 12p
1000+ ..... 8p	Any one type.

## ZENER DIODES

3 Watt Plastic	7 Watt 5%
Wire Ends 5%	Mounting 5%
All voltages 6.8	All voltages 5.1—100 Volts.
-100 Volts. 80p	each.
25+ ..... 27p	25+ ..... 35p
100+ ..... 25p	100+ ..... 30p
500+ ..... 23p	Any one type.
1000+ ..... 21p	
Any one type.	

## MINIATURE POTTED BRIDGE RECTIFIERS (SILICON) SIZE 1 x 1 x 1/4 in.

Cur. Type P.I.V. rent 1-49 50+ 100+ 500+ 1000+

1002	100	2amps	80p	75p	60p	45p
2002	200	2amps	70p	65p	50p	35p
4002	400	2amps	80p	75p	60p	45p
6002	600	2amps	80p	75p	60p	45p
1004	100	4amps	70p	65p	50p	35p
2004	200	4amps	75p	70p	55p	40p
4004	400	4amps	80p	75p	70p	65p
6004	600	4amps	80p	75p	70p	65p
1006	100	6amps	75p	70p	55p	40p
2006	200	6amps	75p	70p	65p	50p
4006	400	6amps	£1.10	£1.00	80p	65p
6006	600	6amps	£1.25	£1.10	£1.00	80p

## SEMI-CONDUCTORS

**LOOK AT THESE PRICES FOR QUANTITIES FROM STOCK**

AFI14 Mullard	25p	AFI15 Mullard	25p
25 + 20p		25 + 20p	
100 + 17p		100 + 17p	
500 + 15p		500 + 15p	
AFI16 Mullard	25p	AFI17 Mullard	25p
25 + 20p		25 + 20p	
100 + 17p		100 + 17p	
500 + 15p		500 + 15p	
2N3055	75p	2N3819 Texas	35p
Mullard 115watt Silicon Power		25 + 30p	
25 + 65p		100 + 25p	
100 + 35p		500 + 23p	
		1000 + 20p	
BFY90	65p	2N2644	50p
1000 M/C/S		Motorola Unijunction	
25 + 40p		25 + 44p	
100 + 55p		100 + 37p	
500 + 50p		500 + 33p	
AFI39	30p	AFI86	40p
Siemens V.H.F.		Mullard V.H.F.	
25 + 25p		150 + 35p	
500 + 19p		100 + 30p	
		500 + 25p	
OC170 Mullard	25p	BYZ13	25p
25 + 21p		Mullard 6a 200V	
100 + 17p		25 + 20p	
500 + 15p		150 + 17p	
		500 + 15p	
OC171 Mullard	30p	BC107, BC108, BC	

This MONTH'S Best Buy . . .




### AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £10.40) Our Price £5.90 + 23p p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

\* High-fidelity reproduction due to broad frequency response (20-20,000Hz)  
 \* Substantially increased stereo effect \* Headphones fit the head gently and do not shift \* Earpieces fit ears snugly (Cardanic suspension) \* Tone quality superior to conventional loudspeakers. \* Only expensive studio loudspeakers can match the reproduction quality of the K50. \* Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.

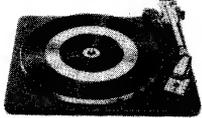


### GARRARD SP25

mk III £12.50 Plus 50p carriage  
 Normal price £15.57

Single record playing unit. Features include cue and pause and automatic pick-up return and switch off.

Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug. 53p extra.  
 AP75 Complete with base and cover £25 plus 75p carriage.

### PLUGS?

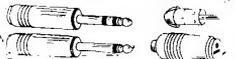

Pack 107 5-Pin Din .. 20p  
 Pack 108 3-Pin Din .. 18p  
 Pack 135 1/2" Jack .. 25p  
 Pack 130 1/2" Jack Stereo .. 48p  
 Pack 103 Loudspeaker Plug .. 15p  
 Pack 100 Phono Plug .. 6p  
 Pack 230 3-Pin Socket .. 23p  
 Pack 238 5-Pin Socket .. 30p  
 Pack 234 Loudspeaker Socket .. 30p

Ready-made Leads  
 3-pin to 3-pin Din .. 63p  
 3-pin to open end .. 53p  
 5-pin to 5-pin Din .. 80p  
 5-pin to open end .. 85p  
 5-pin to 4 phono plugs .. 93p  
 Speaker lead Din to spade 12ft 38p.  
 Extension lead Din plug to socket 12ft 55p  
 All leads approx. 6ft. in length. Post free, by return.




### PLINTH & COVER £5.25

Unbeatable Value plus 50p p. & p  
 Suitable for AT60; SP25; 3000; 2500; 3500. Superb finish. Spindle can be left in position with cover on. Cover of neutral smoke tint perspex.  
 Also available for AP75; SL99; SL75 £6.88 plus 50p carr.

Replacement Stereo DIAMOND STYLI  
 8TA 9TA 9TAHC  
 GP81 S14 ST19  
 EV26 GC8 75p each  
 others on request +13p p. & p.  
 Countdown SPEAKER  
 Teak Cabinet

£12 Insurance & carr. 30p

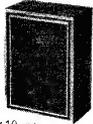A speaker of outstanding specifications and technical merit. Solid teak cabinet size 14" x 10" x 4". Originally designed for use with our Countdown stereo budget system but now available separately.



### EMI 10w matched loudspeaker set 450

Our price £3.75 plus 25p p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies.  
 Also 350 KIT 20W  
 Frequency range: 20 to 20,000Hz.  
 Normal price £12.50 plus 40p p. & p.  
 Also 150 KIT 10W £2.50 plus 40p p. & p.  
 3, 8 or 15 ohms



### SINCLAIR Project 60

SAVE nearly £5 Normal price £23.90

Designed for building into plinths etc., complete with two Z30 Output stages (20 watt) and power supply unit. Send S.A.E. for full technical brochure.  
**SINCLAIR 2000 Mk. 11 AMPLIFIER SAVE £6.30 Our price £28.00**

### Magnetic cartridges

Diamond £4.75

stylus plus 13p p. & p.

Today's value £6.

Stylus replacement can be carried out without removing cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) £1.25 + 13p. p. & p.



### SONOTONE Cartridge ...

(Fitted Diamond Stylus)

(Ceramic) list price £4.10

Sensitivity: 9TAHC 55mV/cm/sec

rms minimum at 45° at 1,000Hz measured on 13p

plus Decca SX12057 p. & p.

£2.50

## M & B COMPONENTS (LEEDS) LIMITED

(Incorporating M & B Radio)

Tel. 0532-35649. P.O. Box 125, 38 Bridge End, Leeds LS1 4EW

### MB2/20A TWO METRE TRANSCEIVER

Ideal for mobile, portable or fixed station use operating directly from a 12vdc supply using an internal transistor inverter. Only requires connection to speaker, aerial and 12vdc supply to become fully operational. Fitted with press to talk microphone. Transmitter uses 4 valves in the r.f. stages giving approx. 20 watts r.f. modulated by a high level amplitude modulation transistor mod. Switchable high and low power. All drive stages monitored by a panel mounted meter which also reads p.a current and acts as a receiver 'S' meter. Receiver uses 7 valves and 20 transistors in a double superhet circuit with tuneable front end. Transistorised tuneable oscillator. Very effective noise limiter and muting circuit to silence receiver in the absence of signals. Current consumption 2.9A on Rx, 4.15A on S/Bye, 8A on transmit high power. 12 1/2" wide x 7 1/2" high x 14" depth. Originally xtal controlled on both Tx and Rx for commercial use therefore using high quality components. Transmitter xtal controlled using HC6U xtal x18. Supplied with xtal fitted as near as we can supply to a frequency of your choice. 4 metre version to order. £50

### 6 TO 12 VOLTS D.C. TRANSISTOR CONVERTERS

Brand new of well known British manufacture, 6vdc input 12vdc output at 5 amps conservatively rated. £5.40

### VHF AERIAL BASES

Brand new aerial base with provisions for tuning the Tx and Rx to the aerial independently. Contains a 12v vhf aerial c/o relay. £1.25

### AD108D MARCONI COMMUNICATION RECEIVERS

9 miniature valves plus xtal filter and tuneable b.f.o. covering 260 to 510Kc/s and 2 to 18.5Mc/s in 4 switched bands. Slow motion dial with logging scale. Originally intended for 24vdc operation but supplied with details for converting to mains operation. In very clean tested condition. £16.15

### VHF FM/MW/LW TRANSISTOR RADIO PANELS

Brand new panels of well known British manufacture less vol. and tone control. Ferrite aerial and wavechange switch. Uses 10 transistors in all. £2.15

### TRANSISTOR 455Kc/s FM I.F. PANELS

Brand new but faulty 6 transistor panels, usually low in gain. 70p

### TRANSISTOR MODULATOR FRONT END

Brand new transistor modulator front end panel, supplied complete with circuit of full modulator. Was used to drive an NKT404 which drove a pair of NKT404s in push pull. Fitted with mod filter circuit and pre-set gain control. £1.20

### R1933A VHF RECEIVER UNIT

18 miniature valve vhf receiver unit requiring power unit and oscillator circuit to complete. Very broadband tuning. Ideal conversion to 2 metres, 4 metres or aircraft bands. £2.55

### GEIGER COUNTERS

Well known contamination meters comprised of main unit fitted with meter, probe and lead supplied in carrying haversack. Meter marked in MILLIROGENTENS/HOUR. Audio output available from socket on front panel. Each one supplied in new or as new condition.  
 Model 1. Fitted with vibrator p.s.u. using 4 pen cell batteries. £4.85  
 Model 2. Fitted with battery holder for 2 150v batteries. £4.15

### TRIPOLET SIGNAL GENERATORS

100Kc/s to 120Mc/s in 10 switched fundamental bands, 1Mc/s xtal marker. Facilities for wavemeter operation. American manufacture.  
 Grade 1 £15.50 Grade 2 £10.50 Graded by appearance only.

ALL PRICES INCLUDE CARRIAGE U.K.

BRAND NEW COSSOR RADIOTELEPHONES ETC. PLEASE SEND FOR LISTS OF ALL ITEMS IN STOCK.

# J. J. FRANCIS

(WOOD GREEN) LTD  
 123 ALEXANDRA ROAD, HORNSEY,  
 LONDON, N.8. Tel: 01-888 1662

to drive the Western Electric balanced armature 750 ohm loudspeaker, which appeared in two forms; one to stand on a table with a vertical ebonite horn; and the circular "Kone" instrument, which remained in use for many years. The balanced armature movement operated a circular varnished linen corrugated diaphragm only 2in. in diameter but it was so efficient that ten of these units, connected to square section wooden horns, covered the whole of the Wembley Exhibition in 1924.

Incidentally the gain of the Western Electric amplifier was varied by tapping on the secondary of the input transformer, and the thoriated ribbon filaments of the 216A valves, though glowing like indirectly heated cathodes, were in fact extremely low temperature "bright emitter" valves. The vacuum in these was so good that up to 800 volts could be applied, and they were often used as transmitting valves.

I wonder how many readers can recall other audio curiosities *before* the time of valve amplifiers? Can anyone remember the Brown Frenophone? A slowly rotating metal cylinder was partly encircled by a cord on one end of which was a Brown "A" type earpiece; the other end was attached to a carbon microphone capsule. The idea was that the signals from the "A" type reed pulled the cord, but the friction from the cylinder caused the stretch to be amplified and this made the carbon button give out an enhanced replica of the signal. Much distortion, and not so good as the original Brown microphone

amplifier, in which a larger version of the "A" type reed drove two microphone buttons in push-pull, the output being combined in a transformer. Incredible though it may seem, this device was actually used in aircraft as a speech amplifier in the earlier days of the 1914/18 war. The differential carbon button microphone was later extensively developed by the Western Electric Co., many being used by the BBC. I gave my first broadcasts on these from the Glasgow station 5SC in 1923/4.

Mention of the Cambridge experiments with G9BIB and the earth rods reminds me of the power buzzer, used in the first war. The object of this was to create so much interference that no enemy trench radio set could operate. This it certainly did! The device weighed some 8lbs and rapidly exhausted any accumulator fated to energise it. Two massive pole-pieces carried windings after the style of an induction coil but capable of giving heavy currents at many hundreds of volts. Two bayonets were inserted into the ground to form a V about 50/60ft. in length, then connected by telephone wire to the buzzer. An immense interference field was set up in this primitive directional array. Interference was in fact the order of the day at that time, some observation aircraft actually having spark transmitters.

Other curios I have had from that period included a Newton airship rotary converter, 12V to 1200V; one of the beautiful Newton propeller-driven 300Hz aircraft alternators; and the 6 valve RAF Mk. 10 receiver with remote control."

#### Crystal Band-Edge Marker —continued from page 157

The prototype Marker is completely self-contained and is built into a tobacco tin. Since it uses a HC6U type crystal there is adequate space but if a FT243 based type or if a different battery is preferred a larger tin is recommended.

The oscillator proper is accommodated on a piece of 0.1in matrix Veroboard which requires no preparation whatever; it should have a total of six conductor strips each possessing seven holes. The crystal holder is soldered direct to two of the strips at one end over two holes; leadouts emanate from the end opposite.

The layout used is shown clearly in Fig. 3 together with all wiring. It is important when soldering items in position to take sufficient care to bend over slightly various lead-outs on the conductor side; simple 'spot-joints' will eventually prove unsatisfactory.

Miniature items are used throughout and in order that the lid can be fitted on completion the transistor 'shell' is carefully laid on its side. Resistor R1 is initially mounted vertically as shown inset then later bent slightly to one side so as not to foul the lid.

The only item to be modified is the R.F. choke and on to this some six turns of fine d.s.c. copper wire (stranded wire is not suitable), as is to be found on some discarded tuning coils, is wound centrally; the ends are fed to the holes indicated.

The completed Veroboard assembly can be secured to the tin interior either by glueing the crystal holder to it with Araldite or by using a stiff copper wire soldered to it from the conductor strip nearest the battery. A piece of stiff card should also be glued to the tin interior to lie directly underneath the Veroboard assembly to act as a simple insulator in case of accidents. The locations of the battery, aerial socket, switch and outlet grommet are clearly indicated.

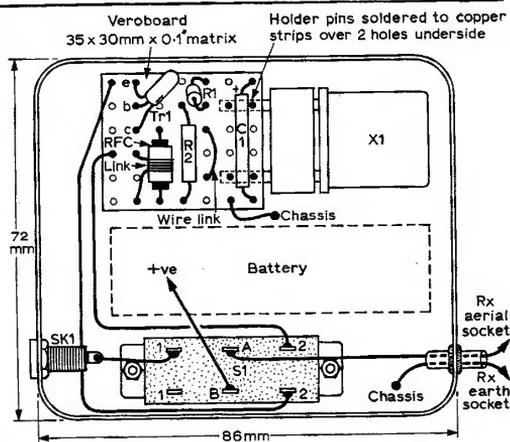


Fig. 3: Suggested layout inside a tobacco tin.

#### TESTING

Initially a meter should be inserted in a series with the battery and the current drain checked as was mentioned earlier and/or the output may be coupled to a suitable oscilloscope if available. If all is well the aerial may be removed from the receiver and applied to the Marker socket SK1, the leads from the Marker being connected to the receiver aerial and earth sockets.

When the Marker switch is placed at position '2' strong signals should be locatable on the receiver at the frequency points listed earlier. Moving the Marker switch back to position '1' will reconnect the aerial to the receiver which will then function as normal.

# CONCLUDING the STATION FOCUS SIX

F. G. RAYER

## Ferrite Aerial

THAT listed has two mounts which clip to the rod, and these are bolted as in Fig. 2. The winding L1 is for medium wave tuning, and L2 consists of six turns of 26 s.w.g. cotton covered or similar insulated wire, wound on top of L1, as in Fig. 2. L1 has wire ends, which are ready tinned and being of Litz wire are best left full length.

Wind excess wire at end 1 round the paxolin former, in the same direction as the winding L1, and secure with tape or adhesive, with a little slack to reach VC3. Wind end 2 in the same way, leaving about 1/2 in. free. L2 is then wound on in the same direction as L1, and secured with tape or adhesive. Connect L2 to end 2 as in Fig. 2, and take a connection to the positive line at the frame of VC1/2. Place sleeving over the other end of L2 (lead 3) and take this to C3.

The bandswitch is 2-pole 2-way with two contacts unused. When it is in the 200kHz position, A and B close, Figs. 1 and 2, so that TC1 with C2 in parallel is placed across VC1 and L1. In this position C and D also close, so that TC2 is across L3 and VC2.

## Alignment

Before first switching on, set R16 to near minimum resistance. Place a meter in one battery lead. Note the current taken, which may be around 6-8mA. With no signal carefully move the slider of R16 to increase resistance, until current has risen by about 4mA.

If no meter is available, tune in a signal and slowly move the slider of R16 until reproduction is clear and normal volume is obtained.

Bringing too much of R16 into circuit will increase the current taken by the output pair. With good volume, current peaks will be 30mA or higher.

When first testing the receiver, leave the collector end of R18 disconnected. With a signal tuned in, bring the free end of R18 into contact with the collector circuit, as in Fig. 3. If volume falls, and quality of reproduction improves, this is the correct phase, and the lead is soldered on.

Should volume increase, or oscillation or distorted

reproduction begin when this connection is made, feedback is positive. To correct this, take the free end of R18 to the other collector of the output pair of transistors.

**IF Alignment.** IFT1 and i.f.t.2 each have two cores, while i.f.t.3 has a single core. These are best adjusted with a proper tool, or with a slip of paxolin carefully shaped to fit. A metal screwdriver is unsuitable, and in any case a wedge-shaped blade may break the cores.

To adjust by ear, tune in a weak signal, with VR1 at maximum volume, and rotate each core for best volume.

A high resistance voltmeter may be clipped across VR1, and the cores can be adjusted for maximum a.g.c. voltage.

**Oscillator and Aerial.** To adjust medium wave band coverage, set TC3 about half closed, nearly close VC1/2 and adjust the core of L3 to bring in 550kHz from a signal generator. Open VC1/2, and adjust TC3 for 1600kHz.

If no signal generator is available, adjust the core and TC5 until tuning in known stations shows that coverage is suitable.

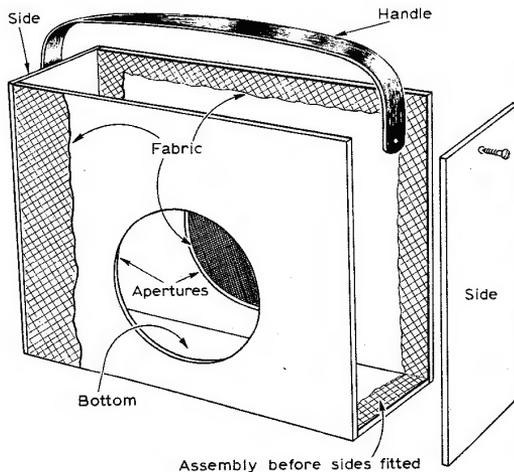


Fig. 4. Constructional details of the cabinet.

Tune in a signal with VC1/2 nearly full open, and peak signals with VC3. Then find a transmission with VC1/2 almost closed, and slide L1 along the ferrite rod for best results.

Check that VC3 can be rotated to peak signals on any frequency, with the aerial closed or extended. VC3 should not need to be fully open, or fully closed. If it is, adjust TC3 and the position of L1 until VC3 never needs to be at either minimum or maximum capacitance.

Switch to 200kHz and set VC1/2 about half-closed. Rotate TC2 to tune in the BBC on this frequency, and peak the aerial circuit with TC1. VC1/2 will then tune a narrow band around 200kHz.


## Cabinet Construction

The cabinet is made in the form of an open-topped case, into which the receiver is lowered, Fig. 4. Internal dimensions must be a little oversize, so that

continued on page 166

# Lasky's

## EXCLUSIVE DIGITAL CLOCK SCOOP!

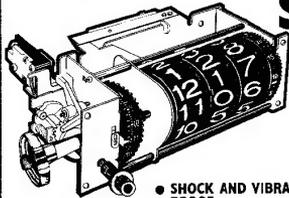

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM. "Sleep" switch, 10 minute division "click" set alarm (up to 12-hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light etc. at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4 1/2" x 1 1/2" x 3/8" (overall from front of drum to back of switch) SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS

**LASKY'S PRICE £6.95** Post 18p  
SPECIAL QUOTATIONS FOR QUANTITIES

## NEW ENJOY PERFECT STEREO AS YOU DRIVE WITH THE NEW FANTAVOX 8 TRACK STEREO CAR PLAY SYSTEM

SIMPLE ONE HANDED OPERATION—SAFE AND EASY TO USE WHILE DRIVING



The newest and most efficient personal car entertainment yet—already a fantastic success in the U.S.A. AND NOW IT'S HERE! Accepts any of the 1000's of pre-recorded 8-track cartridges now available giving up to 1 hour each. Channels change automatically giving non-stop continuous play. Super elegant appearance (mounts either vertically or horizontally) with high quality matching surface mounting speakers specially designed for really dynamic stereo. All solid state (10 transistor) circuit. High 4 watts per channel output. Playback system 8-track, 4-channel with automatic or manual push button channel selection. Volume, tone and balance controls. Super simple one hand operation—safe and easy to use while driving. Power requirements 11-16v. DC negative earth. Line protection fuse fitted. Finished in matt black with satin chrome trim—size only 7(D) x 6(W) x 2 1/2in. (H). Speakers housed in matching black with chrome trim housings. Complete with all necessary connecting leads, mounting bracket and instructions.

**LASKY'S PRICE £22.50** Post. 35p.

COMPLETE WITH MATCHING STEREO SPEAKERS  
Full range of pre-recorded 8 track cartridges available from stock.

**OUT NOW** Lasky's 1971 Audio Tronics catalogue. 1,000's of items covering every interest in radio hi-fi, tape, construction, test, etc. Send your name and address and 13p for post and inclusion on our regular mailing list.


## Lasky's Radio Limited

Branches  
207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271  
33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833  
Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity  
42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
**NEW CITY BRANCH NOW OPEN**  
109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812  
Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

## AUTO RUBY

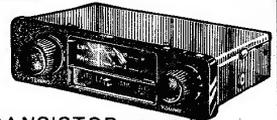

Two waveband all TRANSISTOR car radio

A new two waveband all transistor car radio that really breaks the quality/price barrier. Covers full med. and long wavebands with slide switch wave change. Fully transistorised for superior sensitivity and reliability. Large easy to grip controls. Illuminated dial. Externally adjustable aerial trimmer ensures maximum output. Operating on all 12v. DC system. Negative or positive earth. Standard size 6 1/2(W) x 4 1/2(D) x 2 1/2in. (H). Black with chrome trim. Complete with speaker, baffle, mounting brackets and instructions. Fully guaranteed.

**GREAT VALUE £9.95** Post 25p.

## BSR McDONALD

MP 60 4 speed Single Play unit  
**LASKY'S PRICE £12.50**

post 35p  
with Plinth & Cover £15.75 post 40p

610 4 speed Automatic Turntable  
**LASKY'S PRICE £15.45**

post 35p  
with Plinth & Cover £18.75 post 40p

510 4 speed Automatic Turntable  
**LASKY'S PRICE £13.45** post 35p  
with Plinth & Cover £16.95 post 40p

310 4 speed Automatic Turntable  
with Plinth & Cover £13.45 post 40p.

**LASKY'S PRICE £9.95** post 35p

**NEW McDONALD 210** Complete package system 4-speed minichanger unit. Comp. with BSR SC7M Stereo Ceramic cartridge. With base cover £11.95 post 35p.

## SONY TFM 8030L SCOOP

High performance 11 transistor Battery/Mains portable radio

This top quality solid state receiver is now available from Lasky's at over 27% below the manufacturer's list price making it without a doubt the SCOOP of 1971! Look at these outstanding features. Covers MW, LW and FM (VHF), 11 transistor circuit for high sensitivity and stability. Powerful output to 5" P.M. Dynamic speaker. AFC for drift-free VHF reception. Push button wavechange selectors and tone control. Three power sources—4v battery (Ever Ready PP9 or equiv.), household mains or car battery with adaptors. Dial light for use in the dark. External jacks for earphone, tape recording, external power input and car aerial. Ultra modern styling and superb finish with padded leatherette covered cabinet for superior sound. Chrome trim, strong carrying handle. Technical Spec: Freq. range FM 87-108 MHz, LW 150-285kHz, MW 530-1,605kHz. Circuit: 11 transistors, 7 diodes. Directional telescopic aerial for FM, internal ferrite bar for LW/MW. Size: 9 1/2 (w) x 8 7/8 (h) x 3 1/2 (d). Complete with earphone and battery.

LIST PRICE £29.75 **LASKY'S PRICE £21.50**



Optional extras: AC-90E AC adaptor £4.00; DCC-128 stabilised car battery cord £6.00. Post FREE if bought with radio.

## SPEAKER SCOOP! 12" TANDBERG HT120-4

Superb bass woofer specially made by Goodmans for Tandberg. SPEC: 12" paper cone. Voice coil 14in. 42 impedance. Gap flux 15,500 gauss. Power handling 20W. Fundamental resonance 30Hz.  
**LASKY'S PRICE £9.50.** POST 20p


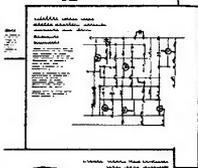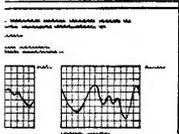
# Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics Your first day on Television: 7th September, 1971



This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course.

That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Complete the coupon below and we will send you the details about training for an exciting, new career.

To: The Pembridge College of Electronics, (Dept. PW.3), 34a Hereford Road, London, W2 5AJ.

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME .....

ADDRESS .....

# WICKS FOR BARGAINS

**E.A. STEREO AMPLIFIER:**  
5 watts per channel; In attractive afromosia veneered sleeve. Controls: On-off volume; Bass; Treble; Balance; Selector; Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs; Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14 1/2"W x 9 1/2"D x 45"H approx. £16.50 inc. post.

- Guaranteed all brand new best quality goods. No rubbish.
- Mail order only.
- By return Post service.
- All enquiries SAE please.

**3 WAY SPEAKER SYSTEM:**  
8" twin cone Bass speaker and 3" tweeter, fitted in extremely elegant teak veneered cabinet. Size: 18 1/2"H x 11 1/2"W x 10"D. 8 ohms handle 10 watts. £7.50 inc. Carr.

**GARRARD OFFERS**  
Garrard SP25 Mk III (Rec. Price (£16.44) Our Price £11.25. Carr. & Ins. 50p.

Garrard SP25 Mk III ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23.79). Our Price £16. Carr. & Ins. 75p.

Or with choice of fitted cartridges. SP25 Mk III/Sonotone 9TAHC (Rec. Price £27.89) Our Price £18. Carr. & Ins. 75p.

SP25 Mk III/Shure M3DM (Rec. Price £31.62) Our Price £20. Carr. & Ins. 75p.

SP25 Mk III/Goldring G800 (Rec. Price £36.79) Our Price £21. Carr. & Ins. 75p.

SP25 Mk III/Shure M55E (Rec. Price £36.76) Our Price £21. Carr. & Ins. 75p. Note! Garrard SL65B (Automatic Changer version of SP25 Mk III) alternatively supplied—please add £3 to above prices.

Garrard AP76 (Rec. Price £28.88)

Our Price £20.85. Carr. & Ins. 50p.

Garrard AP76 ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs).

Please state choice. (Rec. Price £40.88).

Our Price £27. Carr. & Ins. 75p.

**OR WITH CHOICE OF FITTED CARTRIDGES.**

Garrard AP76/Shure M3D (Rec. Price £48.29) Our Price £30.55.

Carr. & Ins. 75p. Garrard AP76/Shure

M55E (Rec. Price £53.85). Our Price

£33.35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price

£53.85) Our Price £33.35. Carr. & Ins. 75p.

Garrard 2025TC fitted with stereo/mono cartridge. £8.99. Carr. Paid.

**TEAK PLINTH & PERSPEX COVER**

Ready cut to take 2025TC, SP25 III, SL65B

available at £4.99. Carr. & Ins. 35p.

**CARTRIDGES**

Sonotone 9TAHC dia. Rec. Price

£4.10. Our Price £1.99

Shure M3DM (Rec. Price £7.41) Our

Price £4.87.

Shure M55E (Rec. Price £12.97)

Our Price £9.50.

Goldring 800 (Rec. Price £13.00)

Our Price £7.50.

Goldring 800 H (Rec. Price £10.69)

Our Price £6.99.

P & P 18p any type

**SERVICE SHEETS**  
1,000's on all makes T.V.'s, Radios, Tape Recorders, Record Players. 13p incl. post. Please state model. Cheques & open P.O.'s returned if sheets not available.

**HI FI STEREO HEADPHONES**  
(Value £5.00)  
Only £2.25 inc. post.

**SPEAKER CLOTH**  
Best quality. Width 36". Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line, yds and yds must go.

**PLUGS, SOCKETS AND LEADS.**

Phono plugs; 3p each  
30p per dozen.  
2 pin Din sprk. plugs  
10p each.  
3 pin Din plugs.  
15p each  
5 pin Din plugs.  
15p each.  
5 pin Din sockets (chassis) 7p each.  
Stereo Jack Sockets c/cct. 15p each.  
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.  
8ft. stereo lead 5 pin Din to open end. 45p  
6ft. stereo lead 2 phono to open end. 37p  
12ft. spkr lead 2 pin Din to open end. 40p.  
Please add P & P 5p.


**100 Mixed Resistors**  
1/2 watt 10% all best quality (no ex government) 40p.

**POTS**  
100K x 100K lins & Logs. stereo. 35p inc. post.  
100K DP switch stereo. log. 45p inc. post.  
50K single Balance. 15p inc. post.

**4 B.A. BRASS NUTS**  
50 for 25p inc. post.

**SPEAKER CABINETS**  
Attractively veneered in afromosia, black front. Size approx. 7 1/2"W x 9 1/2"D x 4 1/2"H. Ready cut to take 8" x 5" speaker. £1.99. P. & P. 12p. extra.

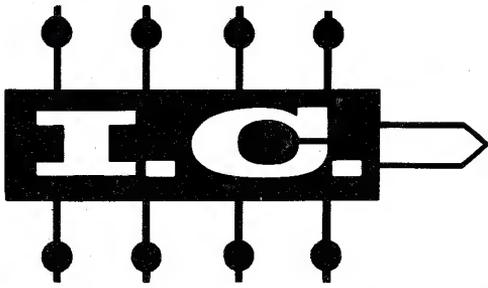**D. T. WICKS & CO. 49 North Station Rd, Colchester, Essex.**  
Tel: (0206) 78807



# OF THE MONTH

L.A.J. IRELAND

Number 20

The Motorola MC 1335P FM/TV Tuning Indicator


**T**UNING indicators for standard a.m. radios are very simple; the receiver generally incorporates an automatic gain control system, which monitors the mean amplitude of the incoming signal and by means of a voltage bias adjusts the gain of the i.f. stages to avoid overloading the detector. Any device which indicates visually the presence of this a.g.c. bias voltage is an effective tuning indicator. In the old days with valve radios, one simply applied the a.g.c. voltage to the grid of a miniature cathode ray tube; transistor sets may employ a buffer transistor driving an "S" meter or a lamp. A tuning indicator is more useful, but less simple with f.m. systems, such as that used in v.h.f. broadcasting or for the sound channel of 625 line TV, where the difficulty of accurate tuning should by now be evident to every viewer. It is precisely to cope with this problem that Motorola have introduced the MC1335P integrated circuit.

First, an examination of the principle of operation of the unit. It is intended to function in a ratio detector circuit, which demodulates an f.m. signal by producing a voltage output dependent on the deviation of the applied frequency at any instant from the resonant frequency of the circuit. Since the frequency swings above and below the carrier frequency, it

follows that when the circuit is correctly tuned to an incoming signal, the voltage produced by the ratio detector averages to zero, while any detuning produces a standing d.c. potential, whether positive or negative. It follows that a circuit which identifies a null voltage will prove an acceptable f.m. tuning indicator.

The circuitry on the MC1335P chip is illustrated in Fig. 1. It is evidently based on the differential amplifier principle, familiar by now from a number of examples already examined in this series of i.c. notes. It is followed by a Schmitt trigger, a circuit in which the output transistor is either saturated or cut off depending on the input conditions. At any time when the input is zero, the trigger is saturated, and a lamp in the collector circuit of the final transistor pair will light. The potential produced across the ratio detector by even a slight detuning will switch the trigger circuit, cutting off the collector current to the lamp. It must further be remembered that there is another condition in which the ratio detector will produce a null output, and that is when no signal is

Fig. 1. With the transistors encircled, this circuit should help in following the operation of the MC1335P.

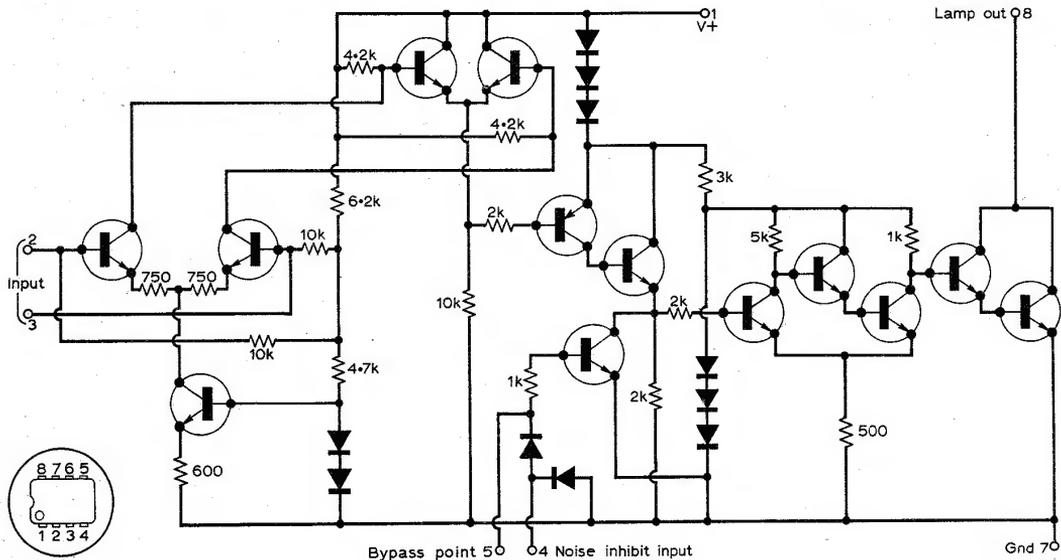

being received. Some may prefer to operate the indicator in this mode, in which the lamp is extinguished as a station is approached, lighting again as perfect tuning is achieved. However, the designer of the circuit added a refinement which permits the extinguishing of the lamp under "no signal" conditions also. When no station is tuned in, the "front end" of the tuner and the i.f. amplifier stages will produce their own device noise, together with the inevitable random aerial noise. Since these effects are random, the effect on the ratio detector must result in a d.c. null output, but an r.m.s. a.c. value can still be applied to the noise level. If applied to pin 4 of the i.c., this a.c. will be rectified by the integral diodes and smoothed by the capacitance at pin 5, to produce a d.c. bias on the associated transistor. The trigger will be cut off and the lamp extinguished. In many cases, particularly in TV applications, the "no signal" noise level will be sufficiently high to operate the inhibit circuit directly; higher quality audio systems will require a noise amplifier as shown in the practical circuit of Fig. 2. Again, individual experiments may be necessary to determine how elaborate a noise amplifier is required; a single transistor stage may suffice, or alternatively one of the many general purpose integrated amplifiers for small signal applications previously treated in these columns.

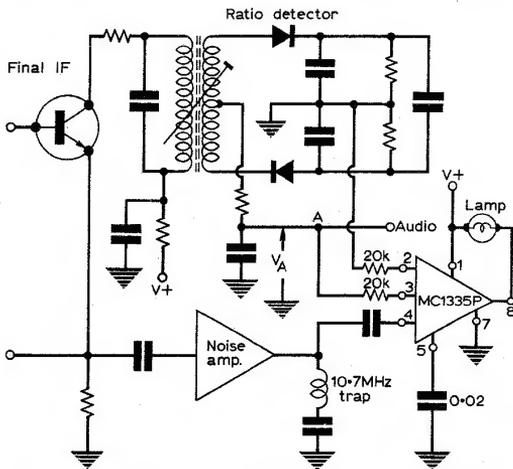


Fig. 2. A practical application of the MC1335P tuning indicator.


The circuit will operate on h.t. supplies of up to 20 volts, and the lamp should be chosen to draw a maximum of 40Ma at the applied d.c. voltage. This is because the saturated condition results in a collector voltage of under 1 volt at pin 8 of the i.c. For operation on battery supplies it is advisable to choose a lamp rated at about the battery voltage but with only that current rating which renders it effectively visible under operating conditions; when the lamp is extinguished the standby current drawn by the circuit is approximately 5.5Ma. Finally, it may be noted that teachers and others interested in instrumentation may find the device a useful null indicator for bridges and other experimental systems. The device is presented in a miniature 8-pin dual in-line plastic package, pin 1 being identified by an index mark. The device is available from Jermyn Industries, Vestry Estate, Sevenoaks, Kent; or other Motorola stockists.

## Station Focus Six—continued from page 162

the receiver can be fitted in.

Front and back are hardboard, approximately 8 x 6<sup>5</sup>/<sub>8</sub>in. With apertures about 3<sup>1</sup>/<sub>4</sub>in. in diameter cut in each piece, about 3<sup>1</sup>/<sub>4</sub>in. clear of the bottom. The bottom is three-ply about 8 x 3in. with sides, also three-ply, 6<sup>3</sup>/<sub>8</sub> x 3<sup>1</sup>/<sub>2</sub>in. All the pieces should be sand-papered smooth, and the edges checked. Dust them off before fixing them together.

The meeting edges of front, back and bottom are smeared with a quick-setting adhesive and these pieces fixed together with a few small panel pins. When the adhesive is dry, a single piece of fabric about 10in. wide and 20in. long is glued on, so as to cover the outer surfaces, and overlap inside. Adhesive should be applied to the edges of the front, bottom and sides. The fabric is cut to suit at the corners, folded over inside, and glued here also.

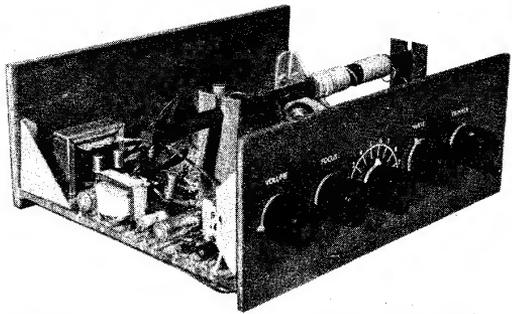

This view shows the mounting arrangements of the ferrite rod aerial.

The sides are varnished and allowed to dry before fitting them. The edges of the parts already assembled are spread with adhesive and the case placed on one end, with the sides in position, and left with a weight on top until the adhesive is hard. The carrying handle is a simple loop, fixed with screws.

It is a good idea to check that the cabinet dimensions are correct before the final glueing together. Tack the sides and bottom together with panel pins as suggested but do not drive them right in. The completed set can be lowered into the framework and any adjustments made to ensure a good fit.

## Notes

It was found that the brass rod of L3 projected at the front (Fig. 3 side), so a portion was cut off to clear the cabinet. The rod, with core, is completely unscrewed to do this, then replaced and locked with a nut.

The receiver can be operated from a 7<sup>1</sup>/<sub>2</sub>V battery such as the RD38, or a 9V supply from a PP9. The AD38 battery takes a non-reversible two-pin plug, and the PP9 requires battery clips. If lamp batteries are ever used they must never be connected with the wrong polarity.

In use, it will be found that the "station focus" control is very helpful with m.w. tuning, especially at the h.f. end of this band, where many transmissions can be heard after dark. This control has virtually no effect on 200kHz, where tuning with VC1/2 is easy. ■

# BI-PAK SEMICONDUCTORS

**SILICON RECTIFIERS—TESTED**

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	4p	5p	5p	7p	14p	21p	47p
100	4p	5p	5p	7p	14p	21p	75p
200	5p	8p	9p	14p	20p	24p	21
400	6p	11p	7p	20p	27p	37p	25
600	7p	16p	10p	28p	34p	45p	25
800	10p	17p	13p	25p	37p	55p	25
1000	11p	25p	15p	30p	48p	63p	25
1200	—	35p	—	35p	57p	75p	—

**NEW LOW PRICE TESTED S.C.R.'s**

PIV	1A	3A	7A	10A	16A	30A
	TO5	TO66	TO66	TO43	TO45	
50	28p	25p	47p	50p	53p	1-18
100	26p	33p	53p	58p	63p	1-40
200	35p	47p	67p	61p	75p	1-40
400	43p	47p	77p	75p	93p	1-75
600	53p	57p	77p	87p	81-25	—
800	63p	70p	90p	1-20	21-50	24

**2A POTTED BRIDGE RECTIFIERS. 200V. 50p**

**TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 75p each.

**DUAL-IN-LINE LOW PROFILE SOCKETS**  
14 AND 16 Lead Sockets for use with Dual-In-Line Integrated Circuits.

		Price each	
Order No.	1-24	25-99	100 up
TS914	14 pin type	33p	27p 25p
TS816	16 pin type	43p	37p 34p

**2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS.** OUR PRICE 25p each. Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqty. TTX300. 5p each. Any Qty.

# SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

**Unequaled Value and Quality**  
Satisfaction GUARANTEED in Every Pak, or money back.

**Pak No.**

U1	120 Glass Sub-min. General Purpose Germanium Diodes.	50p
U2	60 Mixed Germanium Transistors AF/RF	50p
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	50p
U4	40 Germanium Transistors like OC81, AC128	50p
U5	60 200mA Sub-min. Sil. Diodes	50p
U6	30 Silicon Planar Transistors NPN sim. BSY95A, 2N706	50p
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	50p
U8	50 Sil. Planar Diodes 250mA OA200/209	50p
U9	20 Mixed Volts 1 watt Zener Diodes	50p
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	50p
U13	30 PNP-NPN Sil. Transistors OC200 & 2S104	50p
U14	150 Mixed Silicon and Germanium Diodes	50p
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	50p
U16	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	50p
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	50p
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	50p
U19	25 Silicon NPN Transistors like BC108	50p
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	50p
U21	30 AF Germanium alloy Transistors 2G360 Ser. & OC71	50p
U23	30 Mat'd like MAT Series PNP Transistors	50p
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	50p
U25	25 300Mc/s NPN Silicon Transistors 2N708, BSY27	50p
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min.	50p
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	21
U29	10 1-amp SCR's TO85 can up to 600 PIV CR51/25-600	51
U31	20 Sil. Planar NPN trans. low noise AMP 2N3707	50p
U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	50p
U33	15 Plastic case 1 amp Silicon Rectifiers 1N4000 series	50p
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2N302/4	50p
U35	25 Sil. Planar trans. PNP TO-18 2N2906	50p
U39	25 Sil. Planar NPN trans. TO-5 BFY50/51/52	50p
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2N332	50p
U38	20 Fast Switching Sil. trans. NPN 400 Mcs 2N8011	50p
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	50p
U40	10 Dual trans. 6 lead TO-5 2N2660	50p
U41	25 RF Germ. trans. TO-1 OC45 NKT72	50p
U42	10 VHF Germ. PNP Trans. T-1 NKT967 AF117	50p

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

# UNIUNCTION

UT46. Eqty. 2N2646 Eqty. TIS43. BEN3000 27p each 25-99 25p, 100 UP 20p

**NPN SILICON PLANAR**  
BC107/S/9 10p each, 50-99 9p, 100 up 5p each, 1,000 off, 7p each. Fully tested and coded TO-18 case.

**120VDC NIXIE DRIVER TRANSISTOR**  
Sim. BSN23 & C407, 2N1938 FULLY TESTED AND CODED ND120, 1-24 17p each, TO-5 NPN 25 up 15p each.

**AD181 PNP AD182 PNP**  
OUR LOWEST PRICE OF 63p PER PAIR.

**2N3055 115 WATT SIL. POWER NPN.**  
OUR PRICE 63p EACH

**FET'S**  
2N3819 ..... 40p  
2N3930 ..... 30p  
MPF105 ..... 43p

# PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 13 boards 50p+15p p. & s. 100 boards \$3 & 30p p. & p.

# FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V. 400mW (DO-7 Case) 13p ea. 10W (Top-Hat) 17p ea. 10W (SO-16 Stud) 25p ea. All fully tested & 3% tol. and marked. State voltage required.

# BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Description	Price and Qty.
		1-24 25-99 100 up
BP00 7400N	Quad 2-Input NAND GATE	23p 20p 15p
BP01 7401N	Quad 3-Input NAND GATE—OPEN COLLECTOR	23p 20p 15p
BP04 7404N	HEX INVERTER	23p 20p 15p
BP10 7410N	Triple 3-Input NAND GATE	23p 20p 15p
BP20 7420N	Dual 4-Input NAND GATE	23p 20p 15p
BP30 7430N	Single 8-Input NAND GATE	23p 20p 15p
BP40 7440N	Dual 4-Input BUFFER GATE	23p 20p 15p
BP41 7441N	BCD to decimal decoder and N.I.T. Driver	87p 77p 67p
BP42 7442N	BCD to decimal decoder (TTL O/P)	87p 77p 67p
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	23p 20p 15p
BP53 7453N	Single 8-Input AND/OR/NOT GATE—expandable	23p 20p 15p
BP60 7460N	Dual 4-Input—expandable	23p 20p 15p
BP70 7470N	Single JK Flip-Flop—edge triggered	35p 32p 29p
BP72 7472N	Single Master Slave JK Flip-Flop	35p 32p 29p
BP73 7473N	Dual Master Slave JK Flip-Flop	43p 40p 37p
BP74 7474N	Dual D Flip-Flop	43p 40p 37p
BP75 7475N	Quad Bistable Latch	47p 45p 43p
BP76 7476N	Dual Master Slave Flip-Flop with preset and clear	47p 45p 43p
BP83 7483N	Four Bit Binary Adder	87p 77p 67p
BP90 7490N	BCD Decade Counter	87p 77p 67p
BP92 7492N	Divide by 12 4 Bit binary counter	87p 77p 67p
BP93 7493N	Divide by 16 4 Bit binary counter	87p 77p 67p
BP94 7494N	Dual Entry 4 Bit Shift Register	87p 77p 67p
BP95 7495N	4 Bit Up-Down Shift Register	87p 77p 67p
BP96 7496N	5 Bit Shift Register	21-10 21-00 90p

Data is available for the above Series of I.C.'s in booklet form price 124p each.

**GERM. POWER TRANS.**

Type	Price each
OC20	50p
OC22	30p
OC23	33p
OC25	25p
OC26	25p
OC28	40p
OC29	40p
OC35	33p
OC36	40p
AD140	40p
AD142	40p
AD149	43p

**D1D1 Silicon Unilateral switch 50p each.**  
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**EX-EQUIPMENT**  
AF117 transistors. Large cut 4 lead type. Leads cut short but still usable, real value at 15 for 50p.

**AP299 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 960 MHz. USE AS REPLACEMENT FOR AP199-AP195 & 100's OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE: 1-24 87p each, 25-99 84p each, 100+ 20p each.**

**SILICON HIGH VOLTAGE RECTIFIERS**  
10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 80p each.

# TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	Description	Price
UI000	12 x 7400N	50p
UI001	12 x 7401N	50p
UI002	12 x 7402N	50p
UI003	12 x 7403N	50p
UI004	12 x 7404N	50p
UI005	12 x 7405N	50p
UI010	12 x 7410N	50p
UI020	12 x 7420N	50p
UI040	12 x 7440N	50p
UI041	5 x 7441AN	50p
UI042	5 x 7442N	50p
UI050	12 x 7450N	50p
UI051	12 x 7451N	50p
UI060	12 x 7460N	50p
UI070	8 x 7470N	50p
UI072	8 x 7472N	50p
UI073	8 x 7473N	50p
UI074	8 x 7474N	50p
UI075	8 x 7475N	50p
UI076	8 x 7476N	50p
UI077	8 x 7477N	50p
UI078	5 x 7480N	50p
UI079	5 x 7482N	50p
UI080	5 x 7483N	50p
UI081	5 x 7489N	50p
UI082	5 x 7489N	50p
UI083	5 x 7489N	50p
UI084	5 x 7489N	50p
UI085	5 x 7489N	50p
UI086	5 x 7489N	50p
UI087	5 x 7489N	50p
UI088	5 x 7489N	50p
UI089	5 x 7489N	50p
UI090	5 x 7489N	50p
UI091	5 x 7489N	50p
UI092	5 x 7489N	50p
UI093	5 x 7489N	50p
UI094	5 x 7489N	50p
UI095	5 x 7489N	50p
UI096	5 x 7489N	50p
UI097	5 x 7489N	50p
UI098	5 x 7489N	50p
UI099	5 x 7489N	50p
UI100	25 x ASST'D 74's	21-50

Packs cannot be split but 25 assorted pieces (our mix) is available as PAK UI0X1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

# RTL FAIRCHILD (U.S.A.) I.C.'s

**RTL Micrologic Circuits**

Epoxy case To-5 temp. range 15°C to 55°C	1-11	12-24	25-99	100+
µL 900 Buffer	40p	35p	33p	27p
µL 914 Dual two-input GATE	40p	35p	33p	27p
µL 923 J-K Flip-flop	53p	50p	47p	45p

Full data and circuits for IC's in Booklet form price 7p each.

# LINEAR I.C.'s

Type No.	Case	Leads	Description	Price
BP201C—SL201C	TO-5	8	G.P. Amp	1-24 25-99 100
BP701C—SL701C	TO-5	8	OP Amp	53p 53p 45p
BP702C—SL702C	TO-5	8	OP Amp Direct O/P	63p 53p 45p
BP702—72702	D.L.L.	14	G.P. OP. Amp (Wide Band)	53p 45p 40p
BP702—72709	D.L.L.	14	High OP Amp	53p 45p 40p
BP709P—µA709C	TO-5	8	High Gain OP. Amp	53p 45p 40p
BP741—72741	D.L.L.	14	High Gain OP. Amp (Protected)	75p 60p 50p
µA709C—µA709C	TO-5	6	R.F.—IF Amp	45p 38p 27p
TAA295	TO-72	4	A.F. Amp	70p 60p 50p
TAA293	TO-74	10	G.P. Amp	90p 75p 70p

ALL PRICES IN NEW PENCE.  
Please send all orders direct to our warehouse and despatch department.

# BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERTS.

Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. GIRO No. 388-7006

### CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

This compact unit (size 8 1/2" x 5 1/2" x 3" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (600 watts light output each colour) Send S.A.E. for further details. Price £18.50 P. & P. 88p.



# CRESCENT

## RADIO LTD

11 & 40 MAYES RD  
LONDON N22 6TL

888-3206

MAIL ORDER DEPT.  
No. 11  
MAYES RD,  
LONDON  
N22  
6TL

PLEASE NOTE PRICES IN DECIMALS

### TRANSFORMER SCOOP

Primary 220, 250 v. fused. Secondary, 220 v. at 50ma. 6.3v at 1 amp. Overall size 2 1/4" x 2" x 3 1/2" high.

63p each. P. & P. 15p.



Our new branch is now open:

13 SOUTH MALL,  
EDMONTON GREEN,  
EDMONTON, N.9

Phone 01-893-1655

Carrying an ever-increasing stock of components, electrical, surplus and HI-FI

---

### BARGAIN COMPUTER BUMPER BOARDS

Many Resistors, Condensers, Diodes and Transistors (minimum of 4 transistors on each board). 5 BOARDS FOR 120p. Post Free.




### ACOS STETHOSCOPE

Used but in good condition. For personal listening and monitoring with tape recorders, transistor sets and record players. 200 ohm DC resistance. 5 ft. lead. 30p. Postage 8p.
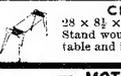
### CHROME TV STAND


28 x 8 1/2 x 16 1/2 high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at 163p. Post 25p



---
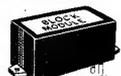
### SOLID STATE BLOCK MODULES

Phono pre-amp E1311 input 100k; gain 25dB max out 8 volt; max input 50mV. Tape pre-amp as above E1313. Power amp E1314 input 1,000 ohms gain 20dB 300mW. Organ tone eq. E1315 tone freq. 200-1K. Hz output 80mW. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at £1.25 P. & P. 10p



### LIGHT DIMMER

The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from, off to full brightness. Power—up to 300 watts interference suppressed

£2.75 + P. & P. 8p.



### SHELF UNIT

Two teak finish shelves on a black frame (overall size 28" x 25" x 12" deep). This unit is wall mounting. 250p. Post Free



---

### TUAC HIGH POWER AMPLIFIER

● True 100 watts output  
● Studio switch, for lower power work, but with same tone.  
● Over 30dB of treble boost and full bass response.  
● Full power—four ohms  
● 10-30,000 Hz response  
● Ideal for holders (blue plastic)  
● Negligible distortion right up to full output  
Price £39.00 Postage 50p

FULL 12 MONTH GUARANTEE

### COMPONENT CENTRE

8" x 8" one sided printed circuit board 10p each  
BY100 type rectifier 800 pIV 750mA 18p each  
4-pin transistor holders 5p each  
2" 8 ohm loudspeaker 30p each  
2 1/2" 8 ohm loudspeaker 35p each  
U2 battery holders (blue plastic) 5p each  
10 ohm w/w pots 12p each  
OC81 double heat clips 8p each  
Tape recorder rev. counters 25p each

Please include P. & P.

### STEREO HEADPHONES

All Types 8 ohm

SH1650 22.98  
SDH28 illus. 22.98  
SDH29 24.00  
SDH292—with volume controls each set 23.50  
SDH205V—Good quality type volume controls 25.50  
Postage—20p on all types.

---

### G.E.C. RATCHET RELAY

No RELIA/008/07 Coil—375 Ω 3-make break contacts. 1-changeover. All New and Boxed. 30p each. Post 5p.

### FLICK SWITCHES

250 volt 3A. Single Pole on/off. 1 1/2" nylon Toggle. 18p Plus Postage 5p

### DWELL TIME UNIT

These small units contain the following components:  
● 700 ohm DPDT relay with base, 1 1/2" 250v. paper, 0.01µF 400v. paper, 500µF electrolytic, 5 diodes OC200 transistor, a 2N2926 type transistor unmarked, a skeleton pre-set pot, 4 pin DIN plug & socket, 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many time fixing devices. + P. & P. 43p



## BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722 9090

OA2	.30	6F13	.33	10P18	.33	30P12	.75	DH75	.25	ECR50	.33	EM80	.33	N339	1.25	PL202	.60	UF80	.85	AC157	.25	BF180	.30	OA202	1.10
OB2	.30	6F18	.45	12A6	.63	30P12	.80	DH77	.20	ECF82	.33	EM81	.42	P61	.50	PL500	.88	UF85	.84	AC166	.25	BF181	.40	OC23	.38
1A7GT	.37	6P23	.72	12AC6	.40	30P14	.78	DK40	.55	ECF86	.65	EM84	.34	PABCO80	.35	PL504	.68	UF86	.63	AC168	.38	BF185	.40	OC23	.38
1H5GT	.35	6P24	.68	12AD6	.40	30P11	.32	DK92	.45	ECF80	.42	10EM87	.38	PC86	.52	PL505	1.44	UF89	.84	AC176	.55	BFY60	.20	OC24	.38
1L4	.13	6P25	.65	12AB6	.48	30L15	.64	DK96	.64	ECF87	.42	10EM88	.38	PC88	.52	PL508	1.40	UL1	.45	AC178	.45	BFY21	.10	OC28	.43
1N5GT	.30	6P28	.70	12AT6	.23	30L17	.78	DL96	.37	ECM42	.64	UY81	.35	PC95	.53	PL509	1.44	UL8	.33	AC177	.25	BFY92	.20	OC26	.38
1U5	.28	6H6GT	.15	12AT7	.19	30F4MR	.98	DM70	.30	ECM81	.29	EY83	.55	PC97	.40	PL802	.75	UM80	.33	AC173	.20	BY100	.18	OC26	.25
184	.24	6J5G	.19	12AU6	.24	30P12	.69	DM71	.38	ECM83	.40	EY84	.50	PC900	.38	PM84	.59	UY10	.33	AC179	.18	BY105	.18	OC28	.20
1U4	.22	6J6	.18	12AU7	.23	30P19	.64	DW41	.41	ECM84	.38	EY86/7	.35	PC94	.42	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
1U5	.48	6J7GT	.38	12AX7	.23	30P11	.69	DW4	.40	ECM82	.38	EY91	.53	PC900	.38	PM84	.59	UY10	.33	AC179	.18	BY105	.18	OC28	.20
2D21	.35	6K7G	.10	12BA6	.30	30P12	.37	50W	.35	ECM85	.50	EZ40	.40	PC94	.42	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
3D5	.19	6K7GT	.23	12BE6	.30	30P13	.75	DY86/7	.20	ECM84	.60	EZ41	.43	PC95	.53	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
3Q4	.38	6K8G	.20	12BH7	.40	30P14	.75	DY86/8	.48	ECM85	.55	EZ20	.23	PC98	.53	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
3Q6GT	.35	6L6GT	.30	12E1	.85	30P15	.98	EB0F	1.20	ECM86	.40	EZ31	.24	PC98	.53	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
35A	.29	6L7GT	.63	12V7GT	.33	35L6GT	.44	EB3F	1.20	EF22	.60	EZ20	.22	PC98	.53	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
3V4	.32	6L18	.45	12E5	.50	35W4	.25	EB3C	.60	EF36	.33	PW4/600	.75	PC98	.53	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
5V4G	.38	6L20	.48	12K7GT	.34	35Z4GT	.24	E180F	.96	EF7A	.38	PW4/600	.75	PC98	.53	PM84	1.18	UY21	.55	AC174	.18	BY114	.18	OC28	.20
5Y3GT	.28	6N7GT	.40	12Q7GT	.30	E182CCL	1.18	EF39	.40	GZ30	.35	PL805/85	SP43	.45	SP91	.33	VP41	.38	AF239	.38	MI	.15	OC81	.13	
5Z4G	.35	6Q7	.63	12A7GT	.50	16L6GT	.45	E1143	.58	EF40	.50	GZ32	.45	PCP80	.67	YP801	.34	U45	.78	AF106	.50	GD9	.20	OC70	.13
6Y90L2	.58	6Q7G	.30	.40	.72	E250	.18	EF41	.50	GZ33	.70	PCP80	.67	YP801	.34	U45	.78	AF106	.50	GD9	.20	OC70	.13		
6A9G	.38	6R7	.55	12SC7	.35	5E42	.45	E47E	.88	EF42	.38	GZ34	.53	PCP80	.67	YP801	.34	U45	.78	AF106	.50	GD9	.20	OC70	.13
6A9G	.15	6R7G	.35	12SC7	.35	5E42	.45	E47E	.88	EF42	.38	GZ34	.53	PCP80	.67	YP801	.34	U45	.78	AF106	.50	GD9	.20	OC70	.13
6A9G	.25	6S47M	.35	12SH7	.22	AC2/PEN	EA742	.50	EF80	.25	HL2SD	.40	PCP80	.67	YP801	.34	U45	.78	AF106	.50	GD9	.20	OC70	.13	
6A15	.12	6S47GT	.33	12SK7	.24	.68	EB34	.20	EF83	.48	HL41DD	.98	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15		
6A05	.28	6S67	.33	12SQ7GT	.24	AC2/PEN	EA742	.50	EF80	.25	HL2SD	.40	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15		
6A76	.20	6S87	.58	.50	DD	.98	EB40	.48	EF86	.32	HN309	1.40	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15		
6A06	.25	6S17	.35	1487	1.15	AC2/PEN	EA742	.50	EF80	.25	HL2SD	.40	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15		
6A76	.30	6S7GT	.33	19A05	.24	AC2/PEN	EA742	.50	EF80	.25	HL2SD	.40	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15		
6B86	.13	6S7GT	.33	20P2	.70	.98	EBF80	.34	EF92	1.13	KT2	.25	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15		
6B46	.28	6V86	.18	20L1	.98	AC/TH1	50	EBF83	.40	EF97	.55	KT8	1.75	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B76	.24	6V9GT	.75	25Z40	.30	CVY1	.35	ECF89	.25	EF98	.65	KT44	1.00	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B16	.43	6X4	.22	20P3	.60	AL60	.78	EBL21	.60	EF183	.30	KT66	.65	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B16	.43	6X5GT	.22	20P4	.93	ATP4	.12	ECM86	.63	EF184	.30	KT88	1.70	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B7A	.38	7B6	.55	20P5	1.00	AZ1	.40	ECM88	.60	EB90	.38	KTW1	6.80	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B17	.70	7B7	.35	21A6	.29	AZ1	.48	EC92	.48	EB92	.48	KTW2	.88	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B83	.63	7C6	.30	25L6G	.29	AZ1	.43	EC93	1.68	EL34	.53	KTW3	.50	PEN4DD	UABCO80	.33	VL120	.60	BA116	.25	MAT120	.38	OC82	.15	
6B66	.72	7H7	.28	25Y5	.38	B36	.38	EC94	.60	EL37	.87	MHLD6	.75	PL82	.38	UCL83	.50	AC127	.20	BF159	.25	OA91	.09	OC205	.38
6B77	.65	7R7	.85	25Y6G	.43	CY1C	.58	EC98	1.19	EL41	.45	N78	2.05	PL83	.38	UCL83	.50	AC128	.20	BF162	.20	OA95	.09	OC205	.38
6B76	.33	8Y7T	.75	25Z40	.30	CVY1	.35	EC99	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6C9	.73	10C1	1.25	25Z5	.40	DAC32	.35	EC98	.25	EL41	.50	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6CD6G	1.15	10C2	.50	25Z6G	.43	DAP91	.22	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6C16	.38	10P1	.75	30C1	.30	DAF96	.35	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6C15	.43	10P9	.45	30C15	.65	DF33	.39	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6C4	.63	10P18	.38	30C17	.30	DF91	.64	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6F1	.63	10L1D11	.53	30C18	.64	DF96	.35	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6F6	.63	10P13	.65	30P5	.80	DF97	.63	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38
6F6G	.25	10P14	1.10	30P11	.64	DF93	.30	EC98	.25	EL42	.42	N308	.38	PL84	.38	UCL83	.50	AC128	.20	BF173	.38	OA200	.09	OC205	.38

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business—Cash or cheque with order only. Post/packing 0.03 per item, subject to a minimum of 0.09. Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 0.03 extra per order. Complete catalogue with conditions of sale price 0.07 post paid. Business hours Mon-Fri. 9-5.30 p.m. Sat. 9-1 p.m.

We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

# new

## Super IC-12



### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

**Price:** including FREE printed circuit board for mounting. **£2.98** Post free

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project 60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.

Sinclair Radionics Ltd., London Rd, St. Ives  
Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311

**sinclair**

# Sinclair Project 60



the world's most advanced high fidelity modules

**Sinclair Project 60** presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.


Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

**sinclair**

System	The Units to use	together with	Cost of Units
A Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
B Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
C 20+20 W. R.M.S. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	<b>£23.90</b>
D 20+20 W. R.M.S. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
E 40+40W. R.M.S. deluxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains trnsfrmr</b>	As for D.	<b>£34.88</b>
F Outdoor P.A. system	<b>Z.50</b>	Mic., up to 4 P.A. speakers controls, etc.	<b>£5.48</b>
G Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>
H High pass and low pass filters	<b>A.F.U.</b>	C, D or E	<b>£5.98</b>
J Radio	<b>Stereo F. M. Tuner</b>	C, D or E	<b>£25.00</b>

# Sinclair Project 60

## Z.30 & Z.50 power amplifiers

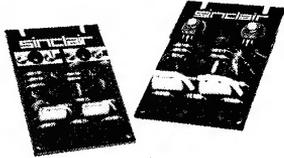

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z50 units are interchangeable with Z.30s in all applications).**

### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300 000 Hz  $\pm 1$  dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB un-weighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size  $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$  in.


### Z.30

Built tested and guaranteed with circuits and instructions manual **£4.48**

### Z.50

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

## Power Supply Units

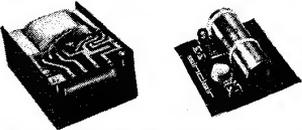

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ-5 30 volts un-stabilised £4.98**

**PZ-6 35 volts stabilised £7.98**

**PZ-8 45 volts stabilised**

(less mains transformer) **£7.98**

**PZ-8 mains transformer £5.98**

## Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

## Stereo 60 pre-amp/control unit



Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

### SPECIFICATIONS

**Input sensitivities:** Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve  $\pm 1$  dB: 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV.

**Output:** 250mV

**Signal-to-noise ratio:** better than 70dB.

**Channel matching:** within 1dB.

**Tone controls:** TREBLE + 15 to -15dB at 10KHz; BASS + 15 to -15dB at 100Hz.

**Front panel:** brushed aluminium with black knobs and controls.

**Size:**  $8\frac{1}{2} \times 1\frac{1}{2} \times 4$  ins.

Built, tested and guaranteed.

**£9.98**

## Active Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28k Hz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

**£5.98**

## Stereo FM Tuner



### first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

### SPECIFICATIONS:

**Number of transistors:** 16 plus 20 in I.C.

**Tuning range:** 87.5 to 108 MHz

**Capture ratio:** 1.5dB

**Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for full limiting.

**Squelch level:** 20 $\mu$ V.

**A.F.C. range:**  $\pm 200$  KHz

**Signal to noise ratio:**  $\geq 65$  dB

**Audio frequency response:** 10Hz—15KHz ( $\pm 1$  dB)

**Total harmonic distortion:** 0.15% for 30% modulation

**Stereo decoder operating level:** 2 $\mu$ V

**Pilot tone suppression:** 30dB

**Cross talk:** 40dB

**I.F. frequency:** 10.7 MHz


**Output voltage:** 2 x 150mV R.M.S.

**Aerial Impedance:** 75 Ohms

**Indicators:** Mains on; Stereo on; tuning indicator

**Operating voltage:** 25-30 VDC

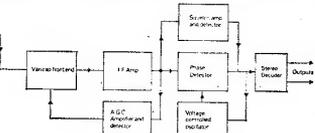**Size:** 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free

To: **SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ**

Please send \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

for which I enclose cash/cheque/money order.

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

# Sinclair Q16/Micromatic

## Q16 High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies without loss.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

## Specifications:

**Construction:** Special sealed seamless sound or pressure chamber with internal baffle.

**Loading:** up to 14 watts RMS.


**Input Impedance:** 8 ohms.

**Frequency response:** From 60 to 16,000 Hz. confirmed by independently plotted B and K curve.

**Driver unit:** Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension for excellent transient response.

**Size and styling:** 9 $\frac{3}{4}$  in. square on face x 4 $\frac{3}{4}$  in. deep with neat pedestal base. Black all over cellular foam front with natural solid teak surround.

**Price £8.98.**

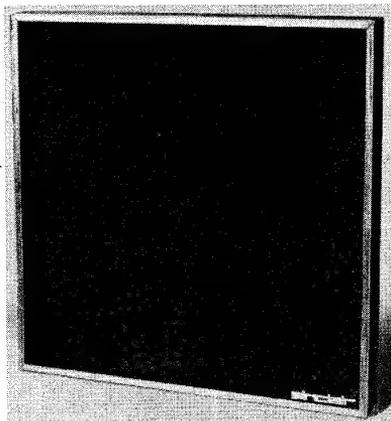

## Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided, matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

## Specifications:

**Size:** 36 x 33 x 13 mm (1.8 x 1.3 x 0.5 in.)

**Weight:** including batteries, 28.4 gm (1 oz.)

**Case:** Black plastic with anodised aluminium front panel and spun aluminium dial.

**Tuning:** medium wave band with bandspread at higher frequencies (550 to 1,600 KHz).

**Earpiece:** Magnetic type.

**On/off switching:** By inserting and withdrawing earpiece plug.

Kit in pack with earpiece, case, instructions and solder **£2.48.**

Ready built, tested and guaranteed, with earpiece **£2.98.**

*Two Mallory Mercury batteries type RM675 required from radio shops, chemists, etc.*



To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

for which I enclose cash/cheque/money order

Name

\_\_\_\_\_

Address

\_\_\_\_\_

PW671

Sinclair Radionics Ltd., London Rd. St. Ives  
Huntingdonshire PE17 4HJ.  
Telephone St. Ives (048 06) 4311

**sinclair**

# STEPHENS

ELECTRONICS,  
P.O. BOX 26,  
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS  
GUARANTEE  
Satisfaction or money  
refunded.

## GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE 1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ81	50p	ECF80/2	47p	DL803	85p	PC855	48p	PY83	50p	UL41	57p	6AR5	33p	6E37	35p	6SK7	32p	12BB6	32p	30PL1	77p
AZ90	60p	ECF86	55p	DL821	55p	PC858	72p	PY88	41p	UL44	57p	6AR6	32p	6E38	35p	6SK7	32p	12BB7	32p	30PL3	90p
CB11	30p	ECI35	67p	DL830	75p	PC859	61p	PY90	£1.00	UM30/4	45p	6AR5	35p	6F1	70p	6SN7GT	30p	12B7	50p	30PL4	85p
CB13	85p	ECI42	58p	EM84	85p	PC8189	51p	PZ99	30p	UY41	45p	6A57G	30p	6F8	45p	6S97	40p	12K3	50p	35A3	50p
CY31	35p	ECI81	51p	EM71	62p	PCF80	51p	QQU02-6	£2.10	U25	75p	6AT6	35p	6F6G	25p	6SR7	37p	12K7G	35p	35A5	55p
DAF91	41p	ECI82	40p	EM80	40p	PCF82	52p	QU03-10	U26	U26	75p	6AU6	29p	6F11	32p	6T8	32p	12Q7G	25p	35B5	65p
DAF96	41p	ECI85	47p	EM81	42p	PCF84	47p	QV02-11	£1.25	U191	72p	6AV6	30p	6F12	32p	6U4GT	62p	12S7	25p	35C5	35p
DF91	45p	ECI88	40p	EM84	37p	PCF86	41p	U192	75p	U192	75p	6B6E	30p	6F13	35p	6U8	35p	12S7G	35p	35D5	85p
DF96	45p	ECL82	40p	EM87	55p	PCF200/1	81p	U193	81p	U193	81p	6B6E	30p	6F14	30p	6V6GT	30p	12SH7	25p	35L4G	47p
DK91	57p	ECL83	57p	EM91	32p	PCF801	61p	U201	75p	U201	75p	6B16	42p	6F15	35p	6X4	25p	12S7	25p	35W4	25p
DK96	47p	ECL86	47p	EY11	40p	PCF802	61p	U220	£2.40	W239	55p	6B16	42p	6F16	40p	6X5GT	27p	12SK7	40p	35Z5	55p
DL92	37p	ECL800	47p	EY80	45p	PCF806	65p	TT21	£2.40	OA2	35p	6B18	42p	6F17	35p	6Y2	30p	12SL7GT	40p	35Z6G	25p
DL94	37p	ECL800	47p	EY81	40p	PCF806	61p	TT22	£2.50	OA3	35p	6B18	42p	6F18	40p	6Y4	60p	12SQ7	40p	50A5	65p
DL96	40p	EF89	52p	EY83	55p	PCF808	67p	U18/20	67p	OA3	35p	6B18	42p	6F19	40p	6Y4	60p	12SQ7	40p	50A5	65p
DM70	32p	EF90	40p	EY86	40p	PCF200	70p	U20	67p	OB2	35p	6B18	42p	6F20	40p	6Y4	60p	12SQ7	40p	50A5	65p
DY86/7	45p	EF83	40p	EY87	42p	PCF82	51p	U25	75p	OC3	35p	6B18	42p	6F21	40p	6Y4	60p	12SQ7	40p	50A5	65p
DY802	42p	EF85	41p	EY88	42p	PCF83	51p	U26	75p	OC3	35p	6B18	42p	6F22	40p	6Y4	60p	12SQ7	40p	50A5	65p
ES5L	£2.75	EF86	60p	EZ35	27p	PCF84	51p	U31	40p	OD3	35p	6B18	42p	6F23	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES8CC	40p	EF89	40p	EZ40	45p	PCF85	52p	U37	£1.50	Q4	35p	6B18	42p	6F24	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10L	£4.50	EF91	42p	EZ41	45p	PCF86	51p	U50	35p	Q4	35p	6B18	42p	6F25	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10F	95p	EF92	50p	EZ40	45p	PD500	£1.52	U52	30p	Q4	35p	6B18	42p	6F26	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10C	52p	EF93	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F27	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10D	52p	EF94	47p	EZ20	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F28	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10E	52p	EF95	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F29	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10F	95p	EF96	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F30	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10G	95p	EF97	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F31	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10H	95p	EF98	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F32	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10I	95p	EF99	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F33	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10J	95p	EF100	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F34	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10K	95p	EF101	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F35	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10L	95p	EF102	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F36	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10M	95p	EF103	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F37	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10N	95p	EF104	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F38	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10O	95p	EF105	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F39	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10P	95p	EF106	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F40	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10Q	95p	EF107	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F41	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10R	95p	EF108	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F42	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10S	95p	EF109	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F43	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10T	95p	EF110	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F44	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10U	95p	EF111	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F45	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10V	95p	EF112	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F46	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10W	95p	EF113	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F47	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10X	95p	EF114	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F48	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10Y	95p	EF115	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F49	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES10Z	95p	EF116	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F50	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES11	95p	EF117	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F51	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES12	95p	EF118	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F52	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES13	95p	EF119	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F53	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES14	95p	EF120	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F54	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES15	95p	EF121	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F55	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES16	95p	EF122	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F56	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES17	95p	EF123	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F57	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES18	95p	EF124	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F58	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES19	95p	EF125	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F59	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES20	95p	EF126	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F60	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES21	95p	EF127	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F61	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES22	95p	EF128	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F62	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES23	95p	EF129	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F63	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES24	95p	EF130	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F64	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES25	95p	EF131	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F65	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES26	95p	EF132	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F66	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES27	95p	EF133	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F67	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES28	95p	EF134	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F68	35p	6Y4	60p	12SQ7	40p	50A5	65p
ES29	95p	EF135	47p	EZ21	27p	PL200	75p	U78	25p	5R4G	55p	6B18	42p	6F69	35p	6Y4	60p	12			

## DISCO THE QUE EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.II AMPLIFIER PR. R.S.C. L12/25 25W L/S in cabinets Terms: Deposit £9 and 9 monthly payments of £5 (Total £54)	£33.50 £19.00 <b>£48</b> carr. £1	PACKAGE PRICE
F.A.L. PHASE 50 MK.II AMPLIFIER P.E. FANE POP 50 L/SPEAKERS Terms: Deposit £20.50 and 9 monthly payments of £5 (Total £55.50)	£32.50 £21 <b>£49.50</b> carr. £1	PACKAGE PRICE
F.A.L. PHASE 100 AMPLIFIER PR. L125 50W L/S in cabinets Terms: Deposit £22 and 9 monthly payments of £11 (Total £121)	£62.95 £59.80 <b>£110</b> carr. £1.50	PACKAGE PRICE
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 L/SPEAKERS Terms: Deposit £14 and 9 monthly payments of £10 (Total £104)	£62.95 £42 <b>£94</b> carr. £1.50	PACKAGE PRICE

### AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 lines 15 Watt 15 ohm high quality speaker, crossover unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.75**

OR SENIOR 15 WATT INC. HF126  
16,000 LINE SPEAKER carr. 35p **£6.75** Carr. 30p

### AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF501D 8" 8W	£2.71	HF120D 12" 15W	£4.49
HF102D 10" 10W	£3.40	HF128 12" 15W	£5.25
HF130 12" 15W	£3.99	HF126D 12" 15W	£5.75

### FANE 807 HIGH FIDELITY LOUSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Contains 2 P.T.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 20 Hz to 15 KHz. Impedance 3 or 8-15 Ω. Gauss 10,000. Remarkable value. **£3.50**

### HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 25p. per enclosure

J25 Size 16 x 11 x 9in. Pressurized. Gives pleasing results with any 8in. Hi-Fi speaker.	<b>£4.75</b>
BE8 For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported.	<b>£5.75</b>
SE10 For outstanding results SE12 For excellent performance with 12in. Hi-Fi speaker and Tweeter.	<b>£5.99</b>
Size 24x15x10in. F.t.d.	<b>£6.99</b>

### R.S.C. PLINTHS

for Record Playing Units, cut for Garrard 1025, 2025, 3000, A.T50, SP25.

WITH TRANSPARENT PLASTIC COVER **£6.30**

LEADING MAKES HI-FI EQUIPMENT AT CLEARANCE PRICES AVAILABLE AT BRANCHES ONLY

### R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BM1 An all-dry battery eliminator. Size 8 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram £3 or assembled ready for use £8.50

### R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.5% at 1,000 c.p.s. Separate Bass and Treble. Input selector switch. Output for 3-15 ohm speakers. Max. sensitivity 5mV. Output rating L.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2in. Attractive brushed silver finish face plate 10 1/2 x 3 1/2in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.50** Carr. 40p

OR FACTORY BUILT WITH 18 MONTHS GUARANTEE **£9.45**

### R.S.C. ALL HI-FI 12-14 WATT AMPLIFIER

PUSH-FULL OUTPUT. Two input sockets with sep. vol. controls for existing. High sensitivity, 6 valves. Bass and treble controls. Response ±3dB 30-20,000 c.p.s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.I.V.'s. High Impedance "mikes". For Musical Instruments etc.

Std. AC mains. For 3 & 15 ohm speakers. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 60p **£10.50**

8A2 for lead. Twin handled metal cover **£1.75**

Factory built **£14.75** or Dep. £3 and 9 mthly pymts of **£1.50** (Total **£17.40**)

## R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS



All types 15 Ohms covered in Raxine Tysanite  
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C48S 25-30 WATTS Fitted four 8" high flux 8 watt speakers. Fitted four 12" 11,000 lines 15 watt speakers. Overall size approx 48 x 10 x 9 in. Carr. 50p Terms: Dep £3 and 9 monthly payments of £2 (Total £21)	TYPE C412S 50 WATTS Terms: Dep. £4 and 9 monthly payments of £2 (Total £21)	TYPE C4100 100 WATTS INC. four 12" 50 watt speakers. Overall size approx 58 x 16 x 14 x 9 in. Carr. 75p Terms: Dep. £4 and 9 monthly payments of £2 (Total £21)
---	--	--

TYPE C4100 100 WATTS INC. four 12" 50 watt speakers. Overall size approx 58 x 16 x 14 x 9 in. Carr. 75p  
Terms: Dep. £4 and 9 monthly payments of £2 (Total £21)

### 30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.

A 2 or 4 input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Resin covered cabinet with handles. Attractive black/gold F.V.C. face. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet.

Terms: Deposit £3.70 and 9 monthly payments of £2.10 (Total £22.80) **£19.95** Carr. 65p

### HIGH QUALITY LOUSPEAKER UNITS

IN TEAK VENEERED CABINETS L13 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State impedance required.	L12 12" 25 WATT 10,000 lines 15 ohms.	L125 12" 50 WATT Two tone Raxine and vinyl finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. 75p
---	---	---

**£5.25** carr. 40p **£9.50** carr. 40p **£29.50**

### R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating.

Loudspeaker unit optional horizontal or vertical mounting. **£60**

★ Two extra heavy duty 12in. Loudspeakers. Carr. £1.50

★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet.

Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total £67.75)

### FAL PHASE 50 MKII AMPLIFIER 50V FAL PHASE 100 AMPLIFIER 100V

Solid state 4 Separately controlled inputs. Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speakers/3-30 ohms. Size 17" x 7" x 7 1/2" 200-250v. A.C. mains. L.H.F.M. Output rating. Or deposit £8 & 9 monthly payments £3.50. Total £27.50. Carr. 65p	Solid State 4 Separately controlled inputs Plus master volume control. Ind. Bass and Treble Controls. Output for speakers/3-30 ohms. Protective circuit to guard against damage from accidental shorts. L.H.F.M. Output rating. Or deposit £15 & 9 monthly payments £2.85. Total £68. Carr. 75p. Send S.A.E. for leaflets.
---	--

### FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis. All sizes approx.

'POP' 100 8" 100 Watt 14,000 gauss 8/150	'POP' 60 15" 60 Watt 13,000 gauss 8/150	'POP' 50 12" 50 Watt 13,000 gauss 15 Ω
---	--	---

Dep. £6 and 9 monthly payments £2-10 (Total £24-90) **£22.05**

Dep. £3.80 and 9 monthly payments. **£12.90** (Total £15). FOR BASS GUITAR, ELECT. ORGAN, ETC.

Dep. £2 and 9 monthly payments **£1.15** (Total £23.85). Full suitable all purposes.

### R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level -70dB. Response ±3dB 30-20,000 c.p.s. All high grade components. Valves 6F86, 6F86, 6CC81, 807, 6X4. Separate Bass and Treble Controls. Sensitivity 35 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, for Electronic Organ, Guitar, String Bass, etc. Gram, Radio etc. For 2 separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes. 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with wiring diagram and instructions. Twin-handled perforated cover. 12 months' guarantee for £19.75

Terms: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet. Carr. 65p

### RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

Primarys 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.

250v. 60mA, 6.3v. 2a.	90p
250-0-250v. 60mA 6.3v. 2a.	90p

FULLY SERUED UPRIGHT MOUNTING

250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a.	£1.25
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£1.99
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£1.99
300-0-300v. 150mA, 6.3v. 4a., c.t., 6.3v. 1a.	£2.40

For Mullard 510 Amplifier . . . . . £4.00

350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 2a.	£1.99
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.40
425-0-425v. 80mA, 6.3v. 2a., c.t., 5v. 3a.	£4.49
425-0-425v. 200mA, 6.3v. 4a., 6.3v. 2a., 5v. 3a.	£4.00
450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a.	£4.99

TOP SERUED DROPTYPE

250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a.	£1.20
250-0-250v. 100mA, 6.3v. 3.5a.	£1.40
250-0-250v. 100mA, 6.3v. 2a., 6.3v. 1a.	£1.45
350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a.	£1.50
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£1.99
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 1a.	£1.99
300-0-300v. 150mA, 6.3v. 4a., 0-5-6.3v. 1a.	£2.35

Suitable for Mullard 510 Amplifier . . . . . £2.35

350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. **£1.99**

350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. **£2.35**

FILAMENT OR TRANSISTOR POWER PACK

Types 0.3v. 1.5a. 45p; 6.3v. 2a. 49p; 6.3v. 3a. 69p; 6.3v. 5a. £1.15; 12v. 1a. 50p; 12v. 3a. or 24v. 1.5a. £1.20; 0.9-1.8v. 1.5a. 99p; 0-12-25-42v. 2a. £1.60
---

CHARGER TRANSFORMERS 0-9-15v. 11a. 95p; 21a. 99p; 5a. £1.10; 5a. £1.30; 5a. £1.49; 8a. £1.55

AUTO (Step Up/Step Down) TRANSFORMERS

0-110/120v. 250-220-250v. 60-80 watts 99p; 150 watts, £1.70 250 watts £2.40; 500 watts £5.25.
---

OUTPUT TRANSFORMERS

Standard Pentode 6,000 Ω or 7,000 Ω to 3 Ω 45p
Push-Pull 8 watts EL84 to 3 or 15 Ω 75p
Push-Pull 10 watts 6V6, ECL86 to 3, 6, 8 or 15 Ω
Push-Pull EL84 to 3 or 15 Ω 10-12 watts . . . . . £1.20
Push-Pull Ultra Linear for Mullard 510, etc. £1.99
Push-Pull 15-18 watts, sectionally wound - 6L6, 6X06, etc. for 3 or 15 Ω . . . . . £1.20
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, K766 etc. to 3 or 15 Ω £2.80

SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 65p; 100mA, 10H, 200 Ω 65p; 50mA, 10H, 350 Ω 45p; 60mA, 10H, 400 Ω 25p.

SEMI-CONDUCTOR RECTIFIERS F.W. (Bridged)

All 6/12v. D.C. output. Max. A.C. input 1.5v. 1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 5a. 80p.
--

# Introducing R.S.C. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

Only high grade components by leading manufacturers.  
COMPLETE KIT OF PARTS **£25 Carr. 65p**



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONE CONNEX.
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

Or FACTORY BUILT with 12 months guarantee Dep. £5-75 and 9 monthly payments £3-50 (Total £37-25) **£33-75**  
Or FACTORY BUILT in cabinet as illustrated Dep. £6 and 9 monthly payments £3-88 (Total £40-74) **£36-75**

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS. FOUR DIODES, FOUR RECTIFIERS.  
TECHNICAL DETAILS (Applying to each channel where appropriate)  
CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance. Plus Ceramic Mag P.U. Switch.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.  
HUM & NOISE - 75dB Min. Vol. - 85dB Full Vol. HARMONIC DISTORTION FREQUENCY RESPONSE: -30B 7Hz to 70KHz 0 1/2% at 1000 Hz 10 Watts  
TREBLE CONTROL: +16dB to -12dB at 14KHz  
BASS CONTROL: +17dB to -16dB at 40Hz  
CROSS TALK - 58dB  
SENSITIVITIES: Disc Mag. 2.5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.  
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

## R.S.C. HIGH FIDELITY STEREO PACKAGE OFFERS

- ★ Four fully wired units ready to 'plug in'.
- ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
- ★ GARRARD SP25 MKIII Turntable on Plinth with cover
- ★ GOLDDRING CS90 Ceramic Pickup Cartridge with diamond stylus
- ★ PAIR OF STANWAY II Speaker Units **£79-80**

Matching as recommended for optimum performance. Send S.A.E for coloured brochure showing other money-saving offers.



Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

- ★ TA12 AMPLIFIER 6.5+6.5 watt in veneered housing
- ★ GARRARD SP25 MK III Player unit on Plinth
- ★ GOLDDRING CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ PAIR OF DORCHESTER Loudspeaker Units **£58**

Or Deposit £7-15 and 9 monthly payments £6-35 (Total £64-30). Trans. Plastic Cover £3-15 extra.

Package as above but with Garrard 3000 Auto-changer and Sonotone 9FA Ceramic Cartridge in lieu of SP25 and CS90 **£51-75** £1-25  
Or Deposit £6 and 9 monthly payments £5-70 (Total £57-30) Trans. Plastic cover £3-15 extra.

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
- ★ Goldring Magnetic P.U. Cartridge.
- ★ Pair of Stanway II speaker units **£96-75**

ATTRACTIVE TEAK or AFROROMSIA VENEERED CABINETS and PLINTHS

TERMS AVAILABLE ON ALL PACKAGE OFFERS

### 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in.
- ★ Response 30-20,000 c.p.s.
- ★ Impedance 15 ohms
- ★ COMPLETE KIT Carr. 63p **£22**
- ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-50 and 9 monthly payments £2-25 (Total £24-75).

DEMONSTRATIONS AT ALL BRANCHES

### HIGH FIDELITY LOUDSPEAKER UNITS

- Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.
- DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 13mm. **£9-45** Carr. 40p.
- STANWAY II Size 20 x 10 1/2 x 9 1/2in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives **£17-85** smooth realistic sound output. See 'package offers' for illustration


### RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups, etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v A.C. mains operation. Attractive silver finished metal facia plate & matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£9-99**  
Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated **£12-50** carr 40p. or dep £2 and 9 mthly pymts. £1-45 (Total £15-05)


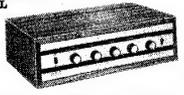
### R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL  
Designed for optimum performance with any crystal or ceramic gram. P.U. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 8-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. Factory built with 12 months guarantee **£19-50** or Deposit £3 and 9 monthly pymts £2-05 (Total £21-45). Or in Teak veneer housing **£15-50** Carr. 40p. or dep £3 and 9 mthly pymts. £2-55 (Total £25-05). Send S.A.E. for leaflet **£23**



## AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

### 5 + 5 WATT OUTPUT

GARRARD 3200 CHANGER WITH LOW MASS PICK-UP ARM AND STEREO CARTRIDGE.  
CONTROLS: TREBLE, BASS, VOLUME, STEREO, BALANCE.  
Operation on 200-250v. A.C. mains.  
Output rating, I.H.F.M



### PAIR OF LOUDSPEAKER UNITS

incorporating high flux 8 x 5 ins. speaker.  
Size approx. 13 x 7 1/2 x 8 1/2 ins.  
Price complete **£42** Carr. £1-25  
ONLY  
Terms: Deposit £5-50 and 9 monthly payments £4-50 (Total £46.)

### LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER £8 (KITS OF PARTS EXCEPTED)  
**INTEREST CHARGES REFUNDED**  
ON CREDIT SALES SETTLED IN 3 MONTHS

## WIN A CASSETTE TAPE RECORDER THIS MONTH—FULL DETAILS AT ALL BRANCHES

- BRADFORD 10 North Parade, (Half-day Wed.) Tel. 25349
- BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) Tel. 021-236-1279
- DERBY 26 Osaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH 133 Leith St. (Half-day Wed.) Tel. 556 5766
- GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Hencorner Lane, Leeds 13. Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied. S.A.E. please with enquiries. Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 LEICESTER
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) LEEDS Tel. 28252
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL LIVERPOOL
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 LONDON
- 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 MANCHESTER
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 MIDDLESBROUGH
- 41 Blakett Street (Opp Fenwick's Score) (Half-day Wed.) Tel. 21-469 3573 NEWCASTLE UPON TYNE
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 SHEFFIELD

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the **practical way.**

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it’s as fascinating as a hobby**

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

### New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of “**OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO**”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.

## FREE

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Dept. 372B, ALDERMASTON COURT, READING RG7 4PF



## POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. 372B, Aldermaston Court, Reading RG7 4PF  
Please send books and full information — **FREE** and without obligation.



NAME..... AGE.....

ADDRESS.....

.....

OCCUPATION.....

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**



**COMMUNICATION RECEIVERS** from the U.S.A. The go ahead in specialist radios **UNIQUE** in VHF frequencies **UNSURPASSED** in performance & styling

They **NOT ONLY** receive Aircraft, Shipping (VHF and SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hams, Gas, Electric and Water Boards, Public Services and many other Commercial and Industrial Radio Telephone mobile transmissions ...

**BUT ALSO** Classical Music, Pop and All That Jazz !!!

**TURN ON TO INSTANT SOUND** ... These are Communications receivers and unique entertainment sources in one neat, transistorised portable package. They keep exciting Aircraft, Shipping, RT mobiles plus Medium Wave, FM National and Local broadcasts at your fingertips. Both are extremely reliable and feature large powerful PM dynamic wide range speakers, switchable AFC to prevent FM drift, tone control, dial lighting, sensitive swivel telescopic VHF and rod aerial, precise slide rule vernier tuning, external aerial and earphone sockets (cuts off speaker for private listening). Earpiece supplied. Operate from standard batteries or mains.


**MODEL MPR 3005 5 BAND**



**EXCLUSIVE 39.50**  
MEDIUM WAVE 530—1605Kcs  
MARINE 1.4—4.6Mcs  
FM/VHF 87—108Mcs  
AIRCRAFT VHF 108—136Mcs  
HIGH VHF/PB 146—176Mcs  
Batts. incl. Plus 62½p P/P

Impressive finish in Walnut with deep Chrome die-cast side panels and grained inserts. Trimmed with brushed Aluminium and black speaker grille. Log scale for easy tuning. Size 9½" x 12" x 4". Wt. 5½lbs. approx.

**MODEL MPR 3016 6 BAND**

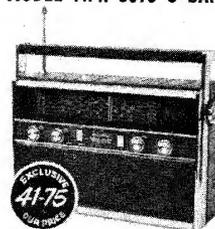

**EXCLUSIVE 41.75**  
SAME BANDS & FREQUENCIES AS MODEL MPR 3005 PLUS ADDED FEATURE OF SW 5.0—12.0Mcs (with Fine Tuner). Batts. incl. Plus 62½p P/P

Styled in elegant black case with luxury Chrome trim, soft padded speaker grille, die-cast sides and walnut insert. Size 8½" x 11" x 3¾". Wt. 5lbs. approx.



The latest in contemporary U.S.A. innovation

**HEAR T.V. SOUND**

All channels 2-13 (Also UHF in many areas)

### MODEL MPR 3073. THE FIRST IN T.V. SOUND PORTABLES.

Sensitive swivel telescopic aerial receives LOCAL AND DISTANT TV TRANSMISSIONS. PLUS FULL MEDIUM WAVE AND VHF/FM BANDS TO RECEIVE YOUR USUAL NATIONAL AND LOCAL RADIO STATIONS. This unique model has stylish leatherette trim, handsome walnut grain inserts and smart chrome trim. 22 transistor/diode superhet circuit. AFC, AGC, Tone Control, Slide rule tuning. Works from standard batteries or mains. Earpiece supplied for private listening. Log scale for easy tuning.



### STOCKTON PARTNERS

(Dept PW), Importers & Distributors, Brightgate, Grimsby. Tel: 0472 64196/58815. Suppliers to Government Depts., Industry, etc.

Plus 50p P/P. Batts. incl.  
BANDS :  
MW 535—1605Kcs  
FM/VHF 88—108Mcs  
TV 1.58—88Mcs  
TV 2.175—218Mcs

# ELECTROVALUE

**EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS**

**BARGAINS IN NEW SEMICONDUCTORS** all power types supplied with free insulating sets  
MANY ITEMS AT NEW REDUCED PRICES

1N914	5p	2N2905A	47p	40361	55p	BC148	9p	BFX87	28p
1N4148	5p	2N2924	20p	40362	68p	BC149	10p	BFX88	28p
2N696	20p	2N2925	22p	AC107	46p	BC153	19p	BFT50	23p
2N897	22p	2N2926	11p	AC126	20p	BC164	20p	BFV51	20p
2N706	12p	2N3053	27p	AC127	20p	BC157	12p	BFY52	23p
2N930	28p	2N3055	65p	AC128	20p	BC168	11p	B8X20	17p
2N1131	38p	2N3702	12p	AC153K	22p	BC159	12p	CA07	17p
2N1132	40p	2N3703	13p	AC174	15p	BC167	11p	MC140	25p
2N1302	19p	2N3704	13p	AC178	15p	BC168	10p	MPS6581	35p
2N1303	19p	2N3705	13p	AC179	15p	BC169	11p	MPS6534	30p
2N1304	22p	2N3706	13p	AD140	59p	BC177	14p	NKT211	25p
2N1305	22p	2N3707	13p	AD142	59p	BC178	13p	NKT212	25p
2N1306	23p	2N3708	13p	AD149	60p	BC179	14p	NKT214	23p
2N1307	38p	2N3709	13p	AD161	38p	BC182L	10p	NKT274	18p
2N1308	38p	2N3710	13p	AD162	38p	BC183L	10p	NKT403	65p
2N1309	38p	2N3711	13p	AF114	30p	BC184L	11p	NKT405	73p
2N1613	23p	2N3794	15p	AF115	30p	BC212L	18p	OC71	29p
2N1711	26p	2N3819	35p	AF117	28p	BC213L	18p	OC81	25p
2N1893	54p	2N3906	35p	AF124	30p	BC214L	18p	OC83	20p
2N2147	48p	2N4058	19p	AD127	30p	BCY70	19p	ZTX300	17p
2N2218	34p	2N4059	10p	AF139	38p	BCY71	38p	ZTX301	17p
2N2218A	48p	2N4060	11p	AF239	27p	BCY72	15p	ZTX302	22p
2N2219	38p	2N4061	11p	AS728	37p	BF115	22p	ZTX303	22p
2N2319A	38p	2N4062	12p	AF127	27p	BF167	18p	ZTX304	27p
2N2270	62p	2N4124	18p	BC107	12p	BF173	19p	ZTX500	18p
2N2369A	19p	2N4126	27p	BC108	11p	BF194	14p	ZTX501	21p
2N2453	35p	2N4284	15p	BC109	12p	BF195	15p	ZTX502	25p
2N2454	36p	2N4286	15p	BC120	15p	BFX29	31p	ZTX503	27p
2N2646	54p	2N4289	15p	BC126	22p	BFX34	25p	ZTX504	25p
2N2904A	45p	2N4291	15p	BC147	10p	BFX35	34p	ZTX530	27p
2N2905	44p	2N4292	15p						

Appointed distributors for

**SIEMENS (U.K.) LTD.**  
**NEWMARKET TRANSISTORS**  
**E. GRINSTEAD ELECTRONIC**  
**COMPONENTS**

## PEAK SOUND PRODUCTS

### BAXANDALL SPEAKER SYSTEM

Designed by Peter Baxandall.  
Superb reproduction for its  
size. Handles 10 watts with  
ease. Uses ELAC 16 Ω 59M109  
speaker Unit Kit £18.00 nett;  
built £10.42 nett.



## MAINLINE AMPLIFIER KITS

RCA/SOS designed main amplifier kits.

Input sensitivity 500-700mV for full output into 8 Ω.

Power Kit price Suitable unreg. power supply

12W	25W	40W	70W
£25.40 nett	£5.50 nett	£10.50 nett	£12.80 nett
£4.82	£4.32	£6.03	£6.87

## 30 WATT BAILEY AMP. PARTS

Sensitivity 1.2V for full output into 8 Ω

Transistors and PCB for two channel £6.36

Transistors and PCB for two channel £12.72

Capacitors and resistors (metal oxide) £1.95 per channel

Complete unregulated power supply kit £2.75

Suitable heatsink 10DN 400C, 55p

## INTEGRATED CIRCUITS

PLESSEY SL408A Now only £2.10 nett 3W into 7.5 Ω for

18V supply. Application data sent 10p.

SINCLAIR IC10 complete with instruction book giving

amplifier circuit details and range of applications. £2.95 nett.

Components pack for stereo inc. mains transformer, controls etc. £4.75 nett.

## S-DeCs puts an end to birds nesting

Components just plug in—saves time—allows re-use of

components. S-Dec (70 points), £1.00

Complete T-Dec, may be temperature-cycled (208 points)

£2.50 Also 1u-Decs and IC carriers.

## NEON INDICATOR LAMPS

Chrome bezel, round red NR/R, 24p; chrome bezel, round

round amber NR/A, 24p; chrome bezel, round clear

NR/C, 24p. Neon, square red type LS5C/R, 17p; amber

type LS5C/A, 17p; clear type LS5C/O 17p. All above are

for 240v. mains operation. Filament types: 6v. 0.04A square

red type LS5C/R-6v., 20p; 6v. 0.04A amber type LS5C/A-6v.,

20p; 6v. 0.04A clear type, LS5C/O-6v., 20p; 6v.

0.04A green type LS5C/G-6v. 20p; 12v. 0.04A LS5C/R-12v.

22p; 23v. 0.04A LS5C/R-23v., 25p.

## DIN CONNECTORS

Lowspeaker .. 2-pole 12p 10p

Audio .. 3-pole 13p 10p

Audio .. 4-pole 14p 12p

Audio .. 5-pole 180deg. 15p 12p

Audio .. 5-pole 240deg. 15p 12p

Audio .. 6-pole 15p 13p

## CORED SOLDER—60/40 alloy, 20 s.w.g. 8oz. reel, 65p.

1lb. reel £1.20.

Handbook of transistor equivalent and substitutes, 40p.

(Postage 3p if ordered alone).

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	9	8	7-5
C	1/8W	5%	4.7 Ω-330K Ω	E24	1	0-8	0-7
C	1/4W	10%	4.7 Ω-10M Ω	E12	1	0-8	0-7
C	1/2W	5%	4.7 Ω-10M Ω	E24	1-2	1	0-9
C	1W	10%	4.7 Ω-10M Ω	E12	2-5	2	1-8
MO	1/2W	2%	10 Ω-1M Ω	E24	1	0-5	3
WW	1W	10% ±1/30 Ω	0.2 Ω-3.9 Ω	E12	7	7	6
WW	3W	5%	12 Ω-10K Ω	E12	7	7	6
WW	7W	5%	12 Ω-10K Ω	E12	7	7	6

C = carbon film high stability low noise  
MO = metal oxide Electroil TR5 ultra low noise  
WW = wire wound Plessey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 33, 43, 51, 62, 75, 91 and their decades.

## ZENER DIODES

5% full range E24 values; 400mW: 2.7V to 30V 15p each  
1W: 6.8V to 82V 27p each 1.5W: 4.7V to 75V 60p each  
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

## CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.

Single gang linear 220 Ω to 2.2M Ω 12p

Single gang log 4.7K Ω to 2.2M Ω 12p

Dual gang linear 4.7K Ω to 2.2M Ω 42p

Dual gang log 4.7K Ω to 2.2M Ω 42p

Log/antilog 10K, 47K, 1M Ω only 42p

Any type with A D.P. mains switch, extra 12p

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

## CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω

470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K,

1M, 2M, 5M, 10M Ω Vertical or horizontal mounting 5p each.

## ENAMELLED COPPER WIRE even No S.W.G. only.

2oz reel 16 S.W.G. 25p; 24-30 S.W.G. 30p; 32-34 S.W.G. 35p;

36-40 S.W.G. 35p; 40z reel 16-22 S.W.G. only 42p.

## MULLARD polyester C280 series

260V 20% 0.01; 0.022; 0.033, 0.047 3p ea. 0.068;  
0.1, 0.15 4p, 0.22 5p, 10%; 0.33 7p, 0.47 8p, 0.68 11p,  
1μF 14p, 1.5μF 21p, 2.2μF 24p.

## MULLARD SUB-MIN ELECTROLYTIC

0.426 range axial lead 6p each

Values (μF/V): 0.04/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10;

4/40; 5/64; 6/4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64;

12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10;

32/40; 32/64; 40/16; 40/25; 50/6.4; 50/25; 50/40; 64/4;

64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10;

125/16; 100/2.5; 200/6.4; 200/10; 200/4; 320/2.5; 320/6.4;

400/4; 500/2.5.

## LARGE CAPACITORS

High ripple current types: 1000/25 25p; 1000/50 41p;

1000/100 32p; 2000/25 37p; 2000/50 67p; 2000/100 51.44;

2500/64 77p; 2500/70 98p; 5000/25 62p; 5000/50 £1.10;

5000/100 £2.81; 10000/25 £1.40; 10000/50 £2.40.

## COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

## POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2.

Overseas orders welcome: carriage and insurance charged at cost.

Send S.&E. for latest list. Prices subject to alteration without notice.

# ELECTROVALUE

(Dept. PW.671) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475

# Practical Wireless Classified Advertisements

## MISCELLANEOUS

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send 4 x 3p stamps NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 50p). No callers please, mail-order ONLY.

**AUDIOSCAN** Dept. PW7  
4, PRINCES SQUARE,  
HARROGATE, YORKS.

## AE 396

### PICK-UP CONVERSION KIT

To replace E.M.I. Double 'C' cartridge, comprising pick up head shell, turn-over holder and dual sapphire cartridge. Mono only. Full D.Y. instructions supplied.

£3.72

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,  
Chilton Works, Garden Road,  
Richmond, Surrey.

## MUSICAL MIRACLES

WAA-WAA Pedal. Complete kit of all electronic parts, robust cabinet, mechanism & instructions. Huge sales, well proven design. Only £2.45 complete. Or built & tested £4.75 post free. Rhythm Box. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtrots etc., cost under £1. Organ Percussion units £14. Bass pedal and other fascinating effects, fuzz, reverb etc. Send 15p for list. D.E.W. Ltd., 254 Ringwood Rd., Ferndown, Dorset.

## ENAMELLED COPPER WIRE

S.W.G.	Per 1/2 lb reel	Per 1 lb reel
18-22	£0.62 <sup>1</sup> / <sub>2</sub>	£0.92 <sup>1</sup> / <sub>2</sub>
23-30	£0.65	£0.97 <sup>1</sup> / <sub>2</sub>
31-35	£0.67 <sup>1</sup> / <sub>2</sub>	£1.02 <sup>1</sup> / <sub>2</sub>
36-40	£0.82 <sup>1</sup> / <sub>2</sub>	£1.32 <sup>1</sup> / <sub>2</sub>
41-44	£0.97 <sup>1</sup> / <sub>2</sub>	£1.62 <sup>1</sup> / <sub>2</sub>

Orders despatched by return of post. Please add £0.12<sup>1</sup>/<sub>2</sub> per item P. & P.

Supplied by: Banner Transformers, Brooks St., Higher Hillgate, Stockport, Cheshire.

TRADE ENQUIRIES INVITED

## TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1-90

ACV22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee. P. & P. 10p.

J. M. KING (E)  
17 Buckridge, Portpool Lane,  
London, E.C.1

## NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateur, Mobile, Radio 2, 3, 4, etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only £3.40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12p. P. & P. Free.

Cheques, Postal orders to:

Dept. F.W.,  
Galleon Trading Co., 25 Avelon Road,  
Romford, Essex

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2 1/2in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

## THE NEW

### ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available —full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2p stamp.

**FANTASTIC REDUCTIONS.** Sinclair IC10 integrated amplifier with instructions £2.43. T-DeCs £2.10. S-DeCs 95p. Modern miniature meters, 1 1/2in square, similar to SEW38P, 50 or 100 microamps £1.50. Sinclair micromatic receivers' kit £2.20, assembled £2.70, batteries 27p extra. PNP Silicon transistors 2S500 series, untested but at least 80% are perfect 50 for 40p, 100 for 70p, data supplied. Sinclair Project 60 offers. Two Z50 amplifiers, Stereo 60 pre-amp, PZ5 power supply £18.75, or with PZ6 power supply £20.75. Two Z50 amplifiers, stereo 60 pre-amp, PZ8 power supply £20.75. Transformer for PZ6 £3. Q16 loudspeaker £7.90. Project 60 tuner £20.75. All items are brand new. Money refunded if dissatisfied. Postage 37p on Project 60 orders, 10p on others. Swanley Electronics, 32 Goldsel Rd., Swanley, Kent.

**PROFESSIONAL** quality/famous name tape. Brand New. Makers' boxes. 5 1/4 in 1,200ft £1.05; 5 1/4 in 1,800ft £1.50; 5 1/4 in 2,400ft £2.00; 7 in 3,600ft £3.00. British made. Tellerhurst Ltd., 5 Creswick Avenue, Rayleigh, Essex.

## 12 VOLT FLUORESCENT LIGHTS



Best Power Cuts, 12 ins 8 watt Tube, Ideal for Caravan, Tent, Emergency Lighting etc. Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12V. Equipment.

Unbeatable at **£3-30** post paid  
or in kit form **£2-90**

## 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **£3-63** POST PAID

SALOP ELECTRONICS Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

**MODULES.** Epoxy resin moulded, size 12mm x 30mm dia approx. Written guarantee. Data supplied to make a variety of projects.

**M1. AUDIO AMP.** 1 watt output, 7 1/2-15v supply, requires speaker, volume control and battery. £1-25.

**M2. INTERCOM AMP.** Requires only speaker, switch and battery to make a very sensitive intercom, etc. 90p.

**M3. AUDIO TONE GENERATOR.** Can be used for signal injector, organ, Morse practice, etc., adjustable frequency. 55p. A. MANLEY, 13 Randisbourne Gardens, Bromley Road, London, S.E.6.

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37 1/2p each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond Surrey.

**ENGINEERING SERVICE** for constructors. Lathe work, milling, sheet metal, castings, etc. S.A.E. for details. Chelmsford Machine Tool Company, P.O. Box 55, Chelmsford CMI 2AU.

## SERVICE SHEETS

**SERVICE SHEETS.** TV, Radio, etc., 25p. Large stocks. S.A.E. with enquiries please, callers welcome. K. L. Bower, 35 Briarwood Drive, Wibsey, Bradford.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p.

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS" Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

## C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

**SERVICE SHEETS (1925-1971)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**RADIO, TELEVISION** over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

**RADIO/TV SERVICE SHEETS and MANUALS**

S.A.E. with enquiries please. Mullard Valve and Semiconductor Data Book, 25p. Mazda Valve and Tube Data Booklet, 25p. Brimar Valve and Tubes Data List, 20p. Resistor Colour Code Indicator, 13p.

**BELL'S TELEVISION SERVICES**  
Albert Place, Harrogate, Yorks HG1 4QA  
Tel. 0423-86844

**TRADER SERVICE SHEETS**

30p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

**OAKFIELD ENTERPRISES LIMITED**

29 CHURCH ROAD,  
TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1970 List now available at 10p. plus postage

If list is required indicate with X

From .....  
Address .....

enclose remittance of .....  
(and a stamped addressed envelope)  
s.a.e. with enquiries please

**MAIL ORDER ONLY (February PW)**

**WANTED**

**CASH PAID** for New Valves. Payment by return. **WILLOW VALE ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

**TOP PRICES PAID** for NEW VALVES popular T.V. and Radio types.  
**KENSINGTON SUPPLIES (C)**,  
367 Kensington Street, Bradford 8,  
Yorkshire.

**WANTED NEW VALVES**, televisions, radiograms, transistors, etc. **STAN WILLETT'S**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

**WE BUY** New Valves and Transistors. State price: **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

**HIGHEST CASH PRICES** for Tape Recorders, 9.30-5. Immediate quotations. 01-472 2185.

**WE PURCHASE NEW VALVES**

new and boxed only  
Payment by return  
**WILLIAM CARVIS LTD.**  
103 North Street, Leeds 7

**FOR SALE**

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. **K. R. WHISTON**, Dept. PW, NEW MILLS, Stockport.

**AUSTRALIAN READERS!** SEND S.A.E. FOR ELECTRONICS CATALOGUE. **HOBIPAK**, P.O. Box 224, Carlton South, 3055, Victoria, Australia.

SO PROFESSIONAL THE YUKAN AEROSOL WAY -

Get these NOW! air drying GREY HAMMER OR BLACK WRINKLE (CRACKLE) Finishes

Yukan Aerosol sprays contain 453p. fine quality durable easy instant spray. No stove baking required. Hammers available in 453p. size. Modern Eggshell Black Wrinkle (Crackle) all at 89p at our counter or 99p. carriage and car push-button self-spray can. Also Durable, heat and water resistant; Black Flat finish (389p. self-spray cans only) 75p. carriage pad.

SPECIAL OFFER: 1 can only optional transferable snap-on trigger handle (value 250p for 99p. carriage pad). Choice of 12 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

**YUKAN, LONDON, W2 1BN**

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—we can supply you too.

Open all day Saturday. Closed Thursday afternoons.

**MORSE MADE !! EASY**

**FACT NOT FICTION** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:  
**69HSO (Box 19), 45 GREEN LANE, PURLEY, SURREY**

**SITUATIONS VACANT**

**CRANFIELD INSTITUTE OF TECHNOLOGY**

invites applications for appointment as

**RADIO ENGINEER**

in the Department of Flight to maintain the VHF/UHF communication, navigation, and instrument landing system equipment. £30 6s for a 40 hour week of five days, rising with service to £32 13s p.w. Local Government super-annuation, excellent working conditions, 3 weeks annual holiday increasing to 4 weeks, sick pay scheme. Subsidised transport over a wide area. Application form from Staff Records Officer, Cranfield Institute of Technology, Cranfield, Bedford.

**EAGLE INTERNATIONAL** require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-636 0961.

**METAL WORK**

**METAL WORK:** All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

**BOOKS & PUBLICATIONS**

**INTERESTED IN RTTY?** Then buy a copy of our booklet **RTTY** the easy way. 15p post paid from Miss Southby, B.A.R.T.G., 51 Norman Road, Swindon, Wilts.

**LADDERS**

**VARNISHED TIMBER LADDERS** from manufacturer. Lowest prices anywhere. 15½ ft. extd. £6-20. 17ft. ext. £6-50. 20ft. ext. £7. 21½ ft. ext. £7-75. 24½ ft. ext. £8-90. 29ft. ext. £10-25. 31½ ft. triple ext. £12-25. 36ft. triple ext. £16. Carr. 80p. Free lists. Also Aluminium Ext. & Loft Ladders. Callers welcome.—(Dept. W.L.S.) Home Sales, Baldwin Road, Skourport, Worcs. Phone 02-993 2574. Placing order on C.O.D.

**EDUCATIONAL**

**RADIO OFFICER** training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

**MEN!** You can earn £50 p.w. Learn Computer Operating. Send for FREE brochure—London Computer Operators Training Centre, C94 Oxford House, 9-15 Oxford Street, London, W.1.

**R.T.E.B. Certs.**, City & Guilds. Colour TV, Radio, Computers, Radio Amateurs' Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—**FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept. 137K, Aldermaston Court, Reading RG7 4PF.

**A.M.S.E. (Elec.)**, City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on 'Satisfaction or Refund' terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio & TV., etc. Send for full details and illustrated book—**FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept 168K, Aldermaston Court, Reading RG7 4PF.

**TRAIN FOR SUCCESS WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how **ICS** can help you in your career.

**ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON. SW8**

Queen's Award to Industry

# A PROUD DAY FOR REDIFON

THE Queen's Award to Industry for 1970 was formally presented to Redifon Limited and Redifon Air Trainers Limited on June 8 by Field Marshal Sir Gerald Templer, Her Majesty's Lieutenant for Greater London.

## New marine radio telephone

MARINE Division has introduced a new SSB radio-telephone for operation in the marine 2 MHz band. It is designed to satisfy all current and future international regulations covering the phasing out of DSB transmissions, and to meet type approval

# TEST ENGINEERS

£1248-£1749+

Continuing expansion means we need more test engineers with the practical experience and real technical knowledge to work on the alignment and testing of HF and VHF equipment.

Theoretical and practical experience of semi conductors, SSB and frequency synthesis will be a great advantage.

Age is not important, since initial earnings will be directly related to experience.

You could start at £1248, but for more senior personnel this could be in excess of £1749

Benefits include Pension, Life Assurance, 3 weeks holiday.

Ring or write with brief details to:  
Norman Manion,  
REDIFON LIMITED  
Broomhill Road, Wandsworth,  
London SW18. 01-874 7281

**REDIFON** 

A Member Company of the Redifusion Organisation



## Redifon

REDIFON LTD. has won an order from Cable and Wireless to supply radio transmitting and receiving equipment for a new ground-to-air service in the Seychelles, where an airport is under construction for the first regular air service to the islands by land-based aircraft. Valued at over £25,000, contract also includes the provision of transmitters for a radio beacon which, while operating in the aeronautical

## A NEW MILITARY RADIO STATION

A NEW 100 watt SSB (single sideband) military radio station, developed by the Communications Division is now in quantity production and delivery of an order valued at £156,000 for the Royal Air Force has already been completed.



# TELEVISION AND RADIO TRAINING

(DAY ATTENDANCE COURSES)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of one year's duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Radar and Radio Transmission are also available following the TV course. Write for prospectus to: London Electronics College, Dept. B/4, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373 8721.

## RECEIVERS & COMPONENTS

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards **50np** + 7np P. & P. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for **£1**. P. & P. 18np. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board + components. 2 boards (4 x OC28) **50np** + 6np P. & P.

9 OA5, 3 OA10, 3 Pot. Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for **£1** + 25np P. & P.

**LARGE CAPACITY ELECTROLYTICS**  
10000MFD 30V **40np** + 6np P. & P.  
16000MFD 12V **40np** + 6np P. & P.  
or **£3.50** per doz. Carr. 50np

**250 MIXED RESISTORS** **62np**  
½ & ¼ watt.

**150 MIXED HI STABS** **62np**  
½, ¼ & 1 watt 5% and better.

**EXTRACTOR/BLOWER FANS**  
(PAPST)  
100 CFM 2800 RPM 4½in x 4½in x 2in. Ideal for kitchen extraction, instrument cooling, etc., etc. **£2.5** + 25np P. & P. 240V AC 50Hz.

**DIODES** ex EQPT: SILICON  
1 Amp 1000 PIV. 4 for **50np**.  
20 Amp 150 PIV. 4 for **£1**. + 5np P. & P.

**BARGAIN RELAY OFFER**  
Single pole change over silver contacts. 25V to 50V. 2.5kΩ coil. 8 for **50np**. + 5np P. & P.

**KEYTRONICS** mail order only  
**52 EARLS COURT ROAD,**  
**LONDON W8** **01-478 8499**

## FREE STORAGE UNIT

with every purchase over **£2**

**5 WATT R.M.S. I.C. (10 WATTS) PEAK**  
PA246 Audio Amp with circuits **£2.40**  
With all components **£2.94**

**LOW NOISE HI-STABS**  
½ watt 5% all E24 values 3 for 2p plus p.&p. 6p  
up to 50 resistors + 1p for each additional 60.

**MULLARD C280, C426, C437**  
electrolytics and many other new component bargains, for details see

**FREE CATALOGUE p. & p. 3p.**  
p. & p. on all orders other than resistors 6p.

## CHROMASONIC ELECTRONICS

56, Fortis Green Road, London,  
N10, 3HN

## Stella Nine Range Cases

### LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7½" Height
6½"	3½"	90p	£1.05	£1.23
6½"	4½"	96p	£1.23	£1.40
8½"	3½"	£1.05	£1.40	£1.40
8½"	6½"	£1.40	£1.74	£2.00
10½"	7½"	£1.88	£2.28	£2.45
12½"	3½"	£1.40	£1.74	£2.03
12½"	5½"	£1.85	£2.25	£2.43
12½"	8½"	£2.30	£2.74	£2.93
14½"	3½"	£1.65	£2.03	£2.25
14½"	9½"	£2.73	£3.50	£3.65
16½"	6½"	£2.45	£2.93	£3.24
16½"	10½"	£3.15	£4.05	£4.45

Cases—Post 25p. per order.  
Discounts available on quantities.

## CHASSIS IN ALUMINIUM, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2½" Walls

6" x 3"	33p	10" x 7"	51p	14" x 3"	44p
6" x 4"	34p	12" x 3"	40p	14" x 9"	84p
8" x 3"	39p	12" x 5"	45p	16" x 6"	64p
8" x 6"	46p	12" x 8"	64p	16" x 10"	95p

Chassis—Post 15p. per order.  
Discounts available on quantities.

Electro magnetic counters. New Boxed. 500 ohm 4 digit 30p post free.  
Copper Laminate Board 1½" single sided. 12" x 12" 30p. post free.

P.O. relays (600 Type) 500 ohm + 500 ohm. 1 make 1 break 2 change over New boxed 30p post free.  
Heavy duty sliding reostat. 1 ohm 12 amp New boxed £1.25p. post free.

## E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

## MICROCIRCUITS:

709	40p	PA237	£1.57	7410	22p
741	73p	SL402A	£1.75	7420	22p
PA230	92p	MEL 11	47p	7430	22p
PA234	87p	D40C1	67p	DIL conn.	25p

## TRANSISTORS:

ME0402	21p	ME4102	12p	2N172	7p
ME0412	20p	ME6101	15p	2N3055	60p
ME4101	11p	MP8111	36p	BFX 86	23p

## ½W ZENER DIODES:

4.7V	12p	6.2V	12p	9.1V	12p
------	-----	------	-----	------	-----

## RECTIFIERS AND DIODES:

1N4001	7p	1N4004	10p	1N914	4p
--------	----	--------	-----	-------	----

## JEF ELECTRONICS (P.W.6)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O. P.&P. 5p per order. Overseas 40p. Money back if not satisfied.

"THYRISTORS". Approx. 3 amp 400 P.I.V. 5 for 50p p.p. 5p extra, minimum order 50p. P. R. Hyams, 46 Eastern Avenue, Swindon, Wilts.

**COMPLETE RANGE** of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets. S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-265 7829.

## AERIAL BOOSTERS

We make four types of r.f. high gain transistorized pre-amplifiers:  
Wideband Radio Type L10 **£2.50**  
This covers the Medium and Short Wave.

V.H.F. F.M. Radio Type L11 **£3**

This covers the V.H.F. radio band.

V.H.F. Television Type L12 **£3**

Please state Band and I and III.

U.H.F. Television Type L45 **£3**

Tunable over the U.H.F. band.

S.A.E. for Details.

## VALVE BARGAINS

Any 5—45p: 10—60p: 100—£5.50: ECC82 ECL80, EF80, EF85, FF133, FBF89, FB91, EY86, PCC84, PCC89, PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY81, PY82, PY801, PY800, 30L15. Postage & packing 10p.  
7 day Money Back Guarantee.

## VELCO ELECTRONICS

62 Bridge St, Ramsbottom, via Bury, Lancs.

## EX RENTAL TVS

17" Semi Slim (90 degree tube) **£2**  
17½" Slimline (110 degree tube) **£5**  
19" Slimline **£8**  
19" 3 channel sets (when available) **£15**  
All TVs sold complete but unserviced, 12 channel tuners, reasonable cabinets, plus carriage **£1**.

## PERFECT SPEAKERS EX TV

PM 3 ohm (minimum order two) 5" round, 8" by 2" rectangular—12½p each. Add 7½p per speaker postage and packaging.

## VALVES EX EQUIPMENT

EB91	5p	EY60	17p	PCF80	7p	PY81	15p
EBF80	12½p	30PL13	30p	PCC89	12½p	PY800	15p
ECC82	12½p	830LZ	12½p	PCL85	22½p	PY92	7p
ECL80	7p	30L15	12½p	PCL84	17½p	PY33	25½p
EF80	12½p	30F4	12½p	PCL82	17½p	U191	17½p
EF85	12½p	PC97	17½p	PCL86	17½p	6F23	17½p
EF183	12½p	PCF86	17½p	PCL83	12½p	30PL1	22½p
EF184	12½p	PC84	7p	PL36	22½p	30P12	20p
				PL81	17½p	30F5	11p

On two valves or more 5p postage and packaging.

## UHF TUNERS

To suit Ferguson 850 900 Chassis **£2.50p** P. & P. 50p

Dept. T.S.

## THORNBURY TRADE DISPOSALS

Thornbury Roundabout, Leeds Rd., Bradford  
Telephone 685670

**EX-GOVT. COMMUNICATIONS RECEIVERS.** calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

**RECEIVERS & COMPONENTS**  
(continued)

**BRAND NEW COMPONENTS** by return. Electrolytics 15 or 25V 1-10 mfd. 3.5p; 20-100 mfd. 4p; Mylar Film 100V .001, .002, .005, .01, .02 2p; .04, .05, .1 2.5p; Mullard miniature Carbon Film Resistors E12 Series 1/2W 10-10MΩ 8 for 5p. Postage 5p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

**AMERICAN COMPUTER PANELS.** Total transistors + 30 First Grade components. Details transistors supplied. 3-55p, post 15p. Assorted Components, 71b £1.50. C.P. Computer Panels 5-BC108 Diodes 4-50p, post 15p. J.W.B. Radio, 75 Hayfield Rd., Salford 6, Lancs. Mail Order only.

**PADGETTS**  
**RADIO STORES**  
OLD TOWN HALL,  
LIVERSEDGE, YORKS  
TEL. HECKMONDWYKE 4285

**40 ONLY.** The much sought after Sighting Computer Mark XI VA. For the model maker. Condition Good. £2.50p. Carriage £1.00.  
**AMPLIFIER UNIT TYPE A1418.** Complete with 5Z4 and 6V6GT valves 250/230 volt, 60 cycle. Transformer, Clean Condition, Untested. £1.25p. Carriage 75p.  
**AIR POSITION INDICATORS.** Contains Gears, Ball Races, Dimmer Springs, Lamps, Four numbered counters, 24 volt Motor etc. Great interest to the model maker. In good condition, 75p. Carriage 50p.  
**GROUND POSITION INDICATOR.** Contains 24 volt lamp, Prisms Mirror, Gears. Could interest schools and model makers. 75p. Carriage 75p.  
**NEW BOXED UNIT TYPE 8197.** Contains two Toggle D.P.S.T. switches, also one Press Toggle D.P.S.T. Sixteen Miniature, 500 Ohm. Pre-set Pots R.X./T.X. switches etc. 25p. P. & P. £21p. £3.00 per dozen. Carriage paid.  
**TOGGLE SWITCHES.** Ex Units D.P.D.T. 10p. D.P.S.T. 5p. S.P.S.T. Spring Loaded 10p. D.P.S.T. Press Button Spring Loaded 10p. P. & P. on any switch 4p. Doz. Post Paid.  
**G.P.O. RELAYS E&-UNITS.** 400 Ohms and 600 Ohms. 50p per doz. P. & P. 25p. Sample Relay 6p. P. & P. 5p.  
**MINIATURE BRASS LAMP HOLDER.** 10p. P. & P. 5p. 90p per doz. Post Paid. Base Board Type.

**RECLAIMED T.V. TUBES** with 12 months' Guarantee. 17" AW 43/80 £1.50p. MW 43/69 £1.50p. AW 43/88 £2.00. Carriage and Insurance on any tube £1.00.  
**12 CHANNEL COMPLETE UNTESTED T.V. SETS.** £2.50p. Carriage and Insurance £1.50.  
**SPEAKERS REMOVED FROM T.V. SETS.** All 8 Ohm and P.M. 8x4 15p. 7x4 25p. 8x24 25p. Post on any Speaker 30p.  
**VALVE LIST**—Ex Equipment 3 months' guarantee. Single valves. Post 8p. Over 3 valves P. & P. Paid.

ARP12	5p	PC084	10p	PY82	25p
EB91	4p	PCF80	10p	PZ30	25p
EF85	15p	30P12	95p	U191	25p
EB70	15p	15p	U201	25p	
EC081	15p	PCL84	20p	6BW7	10p
EC082	15p	PCL82	20p	6U4	25p
ECL80	10p	PCL83	25p	6P28	25p
EF50	5p	PL36	25p	20D1	15p
EF80	8p	PL81	20p	20P1	25p
EF91	4p	PY83	25p	20P3	15p
EY86	25p	PY81	8p	30T4	25p

**INTER-LOCKING PLASTIC STORAGE DRAWERS**  
*"NEAT! HANDY! TIDY!"*



**A PLACE FOR EVERYTHING—EVERYTHING IN ITS PLACE**  
**DISCOUNT PRICES**

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

**BUY AT TRADE PRICES!**  
**SINGLE UNITS** (5" x 2 1/2" x 2 1/2") Usually 15p each, **OUR PRICE: £1.35 Dozen.**  
**DOUBLE UNITS** (8" x 4 1/2" x 2 1/2") Usually 25p each, **OUR PRICE: £1.25 Dozen.**

**PLUS QUANTITY DISCOUNTS!**  
Order £5 and over Deduct 5% in the £.  
Order £10 and over Deduct 7 1/2% in the £.  
Order £20 and over Deduct 10% in the £.  
Pack./Post./Carr.: Add 30p to all orders under £5. Orders over £5 P/P/C Free. Quotations For Larger Quantities. All Prices Tax Paid.

**IVORYET LIMITED** (Dept PW6)  
124 CRICKLEWOOD BROADWAY, LONDON N.W.2

**NEW RANGE U.H.F. TV AERIALS**

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
Loft Mounting Arrays. 7 element £2.25. 11 element £2.62. 14 element £3.00. 18 element £3.50. Wall mounting with Cranked Arm. 7 element £3.25. 11 element £3.75. 14 element £4.12. 18 element £4.50. Chimney Mounted Arrays complete. 7 element £4.00. 11 element £4.37. 14 element £4.75. 18 element £5.25. Complete assembly instructions with every aerial. Low Loss co-axial cable 8 1/2 yd. King Teleboosters—Lab gear U.H.F. Boosters for £3.75. Belling Lee 'Concord' all band V.H.F./U.H.F. mains operated pre-amp £7.50. State clearly channel number required on all orders. p.p. Aerials 40p. Accessories 15p. C.W.O. or C.O.D.

**BBC-ITV-FM AERIALS**  
B.B.C. (Band 1) Loft £1.25. Wall S/D £1.62. 'H' array £3.00. ITV (Band 3) 5 element loft array £2.25. 7 element £2.75. Wall mounting 5 element £3.25. Combined BBC/ITV loft 1 + 5 £2.75. 1 + 7 £3.37. Wall mounting 1 + 5 £3.87. Chimney mounted 1 + 5 £4.50. Preamps for £3.75. Combined BBC/ITV/BBC 2 aerials 1 + 5 + 9 £4.00. 1 + 5 + 14 £4.50. 1 + 7 = 14 £5.00. Available loft only. FM radio loft S/B 97 1/2p. 'H' £1.92. 3 element array £2.87. Standard co-axial cable 5p yd. Coax plugs 8p. Outlet boxes 30p. Diplexer crossover boxes 87 1/2p p. & p. Aerials 40p; accessories 15p C.W.O. or C.O.D. (Min C.O.D. charge 17 1/2p.) 5p for fully insulated lists.

Callers welcomed—open all day Saturday.  
**K.V.A. ELECTRONICS (Dept. P.W.)**  
40-41 MONARCH PARADE,  
LONDON ROAD, MITCHAM,  
SURREY 01-648 4884



**AIRCRAFT BAND RADIOS**

Mirage FM/MW/Air ... .. £15-00  
Flight 2 MW/Air... £10-50 Koyo 5 MW/SW/FM/Air/PSB ... .. £34-00  
Flight 3 MW/FM/Air £14-00 Juliette MW/MB/FM/Air/PSB ... .. £38-00  
Interceptor MW/Air £14-50 Imperial SW1/2/MB/LW/MW/FM/Air/PSB £55-00

**Special Offers** Flight 4 MW/FM/(88-108) Air(108-140) Public(140-175) £16.95 (listed @ £18-50)  
Waltham LW/SW/MW/FM/Air/PSB (88-175) £33-00 (listed @ £36-85)  
Koyo 8 SW1/2/MB/LW/MW/FM/Air/PSB £45-00 (listed @ £55-00)  
Koyo 8 Deluxe, with BFO ... .. £48-00

Money-Back Guarantee  
Mail Order

**LANGTON'S RADIO** Full Lists Free Counter Service  
58 HIGH STREET, ROCESTER, STAFFS., ST14 5JU. Tel. 388




**AMPEX 7-5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run, 600 rpm ±5% speed adjustment, internal AF/RF suppression. 2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16-50. Our price £4-25. P. & P. 25p. Mu-metal enclosure available 75p each.

**AMPEX.** Dynamic stick microphone, high impedance, low noise. Offered well below makers price at £6-50 P. & P. 25p.

**Special offer of AMPEX professional tape heads, mu-metal shrouded.** (Designed for model AG20). Full track record, or playback, £3.00. Erase head £2.00. Set of 3 with mounting bracket and cover £7.50. Half track record or playback only, £4-50 each or £5-50 per pair with bracket and cover. Carriage paid.

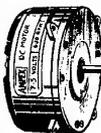**GEARED MOTORS**  
**ELECTRO CONTROL (CHICAGO).** Shaded pole 240v. 50 Hz. 110 rpm. 16 lb./in. £2.25. P. & P. 25p. 200 rpm 10 lb./in. £2.50. P. & P. 25p.  
**MYCALEX.** Open frame, shaded pole motors. 240v. 50 Hz. 7 rpm. 28 lb./in. 80 rpm. 12 lb./in. £2.25 each. P. & P. 25p.



**PROGRAMME TIMER BY HONEYWELL**  
A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Originally cost £15-00 plus. Many applications such as lighting effects etc. New in original makers cartons. First class value at £5-75 plus 25p. P. & P.

**Brand New "DISCUS" Centrifugal Blower** by Watkins & Watson. 240v. 50 Hz. Powered by A.E.I. continuous rating 2850 rpm motor. Cowl diameter 10". Quiet flange 2" I.D. Coupling flange supplied. These superb precision units are ideally suited for Organ construction. Offered at approx. half makers price £12-50. Carriage £1-50




**VINKOR POT CORE ASS. TYPE LA.2103.** Normal price £1.48. Our price 75p

**CRYSTAL OVENS G.C.** Type QC840. 6/12v., AC/DC 75°C. Takes 2 1/2" min. crystals. Similar to above 12v only by SNELGROVE (Toronto). £1-50. P. and P. 25p.

**ERNEST TURNER 800µA METER.** 160Ω movement, 2" case elliptic, plastic front. Green-Red-Green uncalibrated scale £1-50 each. Carriage paid.

**PAINTON BOURNS TRIMPOTS.** 1k, 2k, 2.5k, 5k, 10k, 20k, 50k, 500k. Other Trimmer pots in stock. RIL 10k. MOR-GANITE 1k. MEC 200 12 (tubular) 50Ω. Any 3 for £1-10 carr. paid.

**DEAC. RECHARGEABLE PERMA-SEAL** Nickel-Cadmium Batteries. Type 900B. 1.22v at 800 mA (10-hr. rate). Size 90 mm x 13.5 mm. Weight 40 gr. Unused 63p ea. P. & P. 12p.

**"DECCO" MAINS SOLENOID.** Compact and very powerful. 16 lb. pull. 3/8" travel which can be increased to 1" by removing captive-end-plate. Overall size 2" x 2 1/2" x 2 1/2" high. £1-50. P. & P. 25p.

**"MAGNETIC DEVICES"** Mains Solenoid: 2" x 1 1/2" x 1 1/2" approx 2lb. pull. Plunger Travel 1 1/2" New in makers boxes; offered at half original cost. 75p. p & p. 25p.




**ELECTRO-TECH SALES, 284 PENTONVILLE ROAD LONDON N1. Tel. 01-837-7401/2 OPEN 9.30 - 6pm. SATS. 9.30 - 1pm. CALLERS WELCOME**

**Push Button Switch, Type 14 D.M.G.** A very fine switch made by Honeywell. The switch is intended for mounting on panel through oblong hole. No screws required for fixing, its sprung clips secure it quite firmly. The operating button is approximately 1 in. dia. round and dished for ease of operation. Has 2 sets of 10 amp c/o contacts. Spring loaded, returns to normal when pressure released. Ideal for instrument or quality gear. Price 40p. 24 per dozen.

**12v. Fluorescent Light.** This uses 12 in. 8 watt tube, is energized by transistor inverter thus gives maximum light for minimum battery drain. Ideal for caravan, boat or van interior light. Not a kit, but made up on aluminium body and ready to install. Complete with tube 24. Post 20p.

**Sew-rite Pump Motor.** Very powerful series wound so easily controllable from speed point of view, size 3 1/2 in. x 3 in. approx. For mains working. Price £1.75 plus 30p post and insurance.

**Mains Operated Solenoid Model TT2.** A small one but has a powerful pull, size approx. 1 1/2 in. x 1 1/2 in. 1 1/2 in. 4 in. pull Mains operated, 85p—model 400/1 medium size 2 in. x 2 in. x 1 in. approx. 4 in. pull —80p. plus 20p post.

**TT10.** A very powerful solenoid with 1 1/2 in. long pull, as fitted to many automatic washing machines etc. Size 3 in. x 2 1/2 in. x 2 1/2 in. Mains operated. £1.80 plus 25p post and ins.

**Cold Room or Air-Conditioning Thermostat.** This is calibrated from 30 to 60 F. and operates in the reverse way to normal thermostats, i.e. switches on with a rising temperature. In a new wall mounting case, size 2 1/2 in. x 1 1/2 in. Made by famous Teddington company. Limited quantity, £1.75 each.

**110 R.P.M. Geared Motors.** This is a powerful 2-pole mains operated induction motor in a heavy construction and size as that used in record players, but much more powerful (1/2 in. stack). Gear box is sealed and the final drive shaft is 1 in. long x 1/4 in. diameter. £1.75. Postage and insurance 25p.

**Hearing Aid Amplifiers.** 3 transistors and associated condensers and resistors on a little printed circuit board, the whole thing only about half as big as an Onkyo transistor radio. Mainly for hearing equipment then these may well be just what you are looking for. £1.75 each.

**Mains Solenoid Operated Water Valve.** Normally closed opens when activated. Nylon body as used in many automatic washing machines. The mains solenoid is completely embedded in a resin jacket thus making it absolutely waterproof. Many uses include automatic control of plant watering. Model 1 for 2 small size connectors. Model 2 for one small and one large hose connector. Price 95p. £10 dozen.

**Mains Solenoid Operated Water Valve.** Normally open, closes when activated. This is made by Asco their type No. 8030 A2. This is a heavy and somewhat superior water valve with an all-metal body suitable for connecting in line with 1/2 in. pipe. The solenoid is not waterproofed but is enclosed in a metal casing with an conduit entry. To facilitate electrical connection the solenoid casing may be rotated through 360 degs. Well made, should give years of trouble free service. Price £1.75, post and insurance 30p.

**Amplifier, Main transformer, 50v. 1 1/2 amp.** Upright mounting with fixing brackets and metal shrouds to contain magnetic field, 50 c.p.s. primary tapped 200/250v., in 10v steps, separate screen, 2 secondaries, one 250-250v., at 2 amps and the other 110v., at 10 MA. Open construction with mounting feet. £2.25p, post 30p.

**Mains Transformer, 25-0-25v. 2 amps, 50 c.p.s.** primary tapped 200/250v., in 10v steps, separate screen, 2 secondaries, one 250-250v., at 2 amps and the other 110v., at 10 MA. Open construction with mounting feet. £2.25p, post 30p.

**Multi-Range Test Meter.** Handy slip-in-your-pocket size, 3 angled movement gives wide easily read scale, 8 ranges, D.C. volts 0.15-150-1000 A.C. volts 0.15-150-1000 D.C. current 0-150MA. Resistance 0-100k. A very well made tester, 100-o.p.v. ideal for most jobs. Japanese made, of course, and very robust. Buy one of these and save your expensive instruments for precision jobs. Price £2. Post and insurance 20p.

**Air Spaced Tuning Condenser.** 2 gang with slow motion spindle (standard 1/2 size). Exact capacity not known, but estimated at approximately 300 p.f., and 250 p.f. 45p. 25 doz.

**Micro Switch, reference RW18.** An ultra sensitive switch operated by spring lever only slightest pressure needed to operate. Contacts rated at 10 amps. Price 30p.

**500K. Edgewave Control Pot-Meter.** Morganite, approximately 1 1/2 in. dia. useful size and standard replacement in many T.V. sets. 12p. £1.20 per dozen.

**Pre-Set Pot Meters.** With integral bakelite control knob, all by Morganite, Weiswyn or similar quality makers. Standard size (approximately 1 in. dia.) suitable for pre-set or variable circuits. Low values are wire wound. The following values are in stock, 220ohm, 330ohm, 300ohm, 1k, 5k, 50k, 100k, 10p. each. £1 per dozen.

**1 Watt Transistor Amplifier.** Japanese made, very good quality. Panel size approx. 5 1/2 in. x 2 in. 5 transistors, 84 ohm output, operates from 9v battery or from mains with 12v transformer. £1.25p.

## 20 AMP ELECTRICAL, PROGRAMMER

**Learn in your sleep!** Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm hose to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp Switch, which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 6 1/2 x 11 x 2 1/2 in. oesp. Metal encased, glass fronted with chrome surround. Offered at £2.40 plus 25p postage and insurance.



## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available, £1.90 plus 13p post & p. **NEW IKW MODEL**

## INSTRUMENT SWITCHES

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	60p	60p	60p	60p	60p	33p	33p	33p	33p
2 poles	60p	60p	60p	60p	60p	33p	33p	55p	55p
3 poles	60p	60p	60p	60p	21	55p	55p	75p	75p
4 poles	60p	60p	60p	21	21	55p	55p	90p	90p
5 poles	60p	60p	21	21	21	40p	75p	75p	£1.15
6 poles	60p	£1	£1	£1	£1	40p	75p	75p	£1.35
7 poles	60p	£1	£1	£1.40	£1.80	95p	95p		
8 poles	£1	£1	£1	£1.40	£1.80	95p	95p		
9 poles	£1	£1	£1.40	£1.40	£2.20	£1.15	£1.15		
10 poles	£1	£1	£1.40	£1.80	£2.20	£1.15	£1.15		
11 poles	£1	£1.40	£1.40	£1.80	£2.20	£1.85	£1.85		
12 poles	£1	£1.40	£1.40	£1.80	£2.60	£1.85	£1.35		

## BALANCED ARMATURE UNIT

500 ohm, operates speaker or microphone, so useful in microcom or similar circuits. 6/8 ea., £3.10.0 doz.

## MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available, 800, 850 and 1100 r.p.m. from either or both of the nylon sockets (Where the heater of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2in. diameter, 5in. long. Price 90p plus 25p, p. & ins. 12 or more post free.




## AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or retractable. Suitable for 12v positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. 26 plus 25p post and ins.


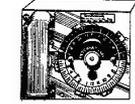
## INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 5/- upwards with circuit and technical data of each. Complete parcel only £1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**



## 24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. £2.50 post and ins. 23p. Additional time contacts 50p pair

## DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 sets of heavy cables. Wired up ready to work. £2 less plus £2.25 with fitted 13 amp plug; £2.40 with fitted 15 amp plug, plus 23p P. & I.



## BARGAIN OF THE YEAR

### MICROSONIC KEYPCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/2 x 3 1/2 in.—complete with soft leather zipped bag. Specification: Circuit: 7 transistor superheterodyne. Frequency range: 230 to 1500 Kc/s. Sensitivity: 5 μv/m. Intermediate frequency: 465 Kc/s or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only £1.25 less batteries plus 13p. post for £7.27 post free. Pair of rechargeable batteries and charger 85p.




## 4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. Ex equipment but little used—as good as new offered at approx. half price. 25 plus 75p. post and ins.



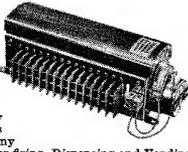
## HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signaling, etc. Price from maker probably over £10 each. Special snip price £5.75 plus 20p post and insurance. Don't miss this terrific bargain.



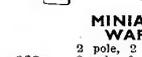
## NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic push-rod suitable for operating, 5p each, 45p doz.


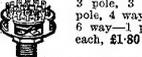
## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 1/2 pole, 12 way. All at 18p each, £1.50 dozen, your assortment.



## WATERPROOF HEATING ELEMENT

26 yards length 70w. Self-regulating temperature control, 50p post free.

## MICRO SWITCH

5 amp, changeover contacts, 9p each, £1 doz. 15 amp, Model 10p each or £1.05 doz.



Where postage is not stated then orders over £3 are post free. Below £3 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

**ELECTRONICS (CROYDON) LTD**  
Post & Trade orders to Dept. P.W. J. Bull (Electrical) Ltd.,  
7 Park Street, Croydon CRO 1YD Callers to 102/3 Tamworth Road, Croydon

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 12½p in £ for postage and handling  
MINIMUM CHARGE 12½p. No C.O.D. orders accepted  
Please note that the valves offered below are not necessarily of U.K. origin

Relait Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

0A2	0.38	6AQ6	0.55	6F1	0.70	9RW6	0.50
0A3	0.45	6AR5	0.35	6F5	0.50	10C2	0.50
0B2	0.35	6AR6	0.40	6F9G	0.30	10D1	0.50
0B3	0.80	6AR11	1.25	6F11	0.38	10D2	0.40
0C3	0.32	6AS6	0.55	6F13	0.38	10F1	0.30
0D3	0.35	6AS7G	0.80	6F14	0.65	10F9	0.50
1B3GT	0.38	6AT6	0.30	6F15	0.65	10F18	0.45
1CP31	6.00	6AU6	0.25	6F18	0.45	10L1	0.45
1L4	0.20	6AV6	0.30	6F23	0.30	10L11	0.60
1R4	0.35	6AW8A	0.55	6F24	0.75	10P13	0.55
1R5	0.35	6BA6	0.25	6F25	0.75	10P14	1.10
1R4	0.27	6BE6	0.30	6F29	0.35	12AB9	0.60
1S5	0.25	6BF6	0.50	6F28	0.60	12AC9	0.60
1T4	0.25	6BF6	0.50	6J4	0.50	12AL5	0.45
1U4	0.27	6BH6	0.45	6J5GT	0.30	12AQ5	0.45
1U5	0.50	6BJ6	0.45	6J7	0.45	12AT6	0.30
1Y2	0.45	6BK7A	0.55	6K5GT	0.30	12AT7	0.38
1X2B	0.40	6BN5	0.43	6K7	0.35	12AU6	0.30
2D21	0.35	6BN6	0.40	6K8G	0.35	12AV7	0.30
3A4	0.35	6BQ5	0.25	6K25	0.75	12AV6	0.38
3C8	0.45	6BR6	0.50	6L6GT	0.40	12AV7	0.40
3BP1	2.75	6BR7	1.30	6L7	0.40	12AX7	0.50
3Q4	0.40	6HW6	0.85	6L18	0.45	12AX7	0.70
384	0.35	6HW7	0.70	6L20	0.40	12B44	0.65
3V4	0.45	6HX6	0.40	6P3GT	0.30	12B46	0.25
5R4G	0.60	6BZ5	0.95	6P1	0.60	12BA7	0.35
5U4G	0.33	6C4	0.33	6P25	1.25	12BDE	0.35
5U4GH	0.42	6CGT	0.40	6P28	0.35	12BH7	0.40
5V4G	0.42	6CK7A	0.55	6P28	0.60	12C7G	0.45
5Y3GT	0.35	6CD6GALL15	0.847	0.40	12K5	0.55	
5Z3	0.50	6CG7	0.50	6S07	0.35	12K7G	0.35
5Z4G	0.40	6CH6	0.55	6SK7	0.35	12Q7G	0.35
6S02L	0.75	6FL6	0.50	6ST7G	0.35	12AT7	0.35
6A4	0.35	6CW4	0.68	6SN7G	0.35	1487	0.80
6AFA4	0.50	6CV5	0.43	6S07	0.40	20D1	0.45
6A97	0.40	6CZ7	0.45	6SR7	0.40	20P1	1.10
6AH6	0.50	6D3	0.45	6T7	0.50	20P4	1.10
6AJ8	0.30	6DC6	0.75	6U4GT	0.60	20P4	1.10
6AK5	0.30	6DK6	0.48	6U8A	0.40	20P5	1.20
6AK6	0.57	6DQB	0.63	6DQB	0.35	25C5	0.60
6AL3	0.43	6E3	0.45	6T7	0.35	25L6GT	0.45
6AL5	0.20	6EA8	0.58	6XGT	0.35	25Z4G	0.30
6AM5	0.32	6EH7	0.30	6X8	0.55	25Z6GT	0.65
6AM6	0.32	6EJ7	0.35	6Y6G	0.65	30A6	0.45
6AQ5	0.35	6EW6	0.63	7Y4	0.60	30A83	0.40

First Quality Fully Guaranteed



BRAND

ELECTRONIC VALVES

30C1	0.30	60L6GT	0.50	DK40	0.55	6CC83	0.30
30C18	0.30	65A2	0.40	DK92	0.50	6CC84	0.30
30C17	0.35	90A2	2.40	DK96	0.42	6CC85	0.40
30C18	0.75	90A7	2.50	DL96	0.42	6CC88	0.40
30P5	0.35	90C1	0.60	DM140	0.65	6CC89	0.50
30F11	0.70	90CV	1.25	DY36	0.38	6CC91	0.50
30FL12	0.33	807	0.50	DY87	0.35	6CC189	0.60
30FL14	0.75	812A	3.50	DY802	0.50	6CC90	0.35
30L1	0.40	813	3.75	EB8C	0.65	6CC92	0.35
30L18	0.35	866A	0.75	EB10F	0.95	6CC96	0.45
30L17	0.30	5642	0.65	EB10F	2.90	6CC94	0.40
30P12	0.80	6080	1.50	ABBC800	0.35	6CC95	0.35
30P19	0.30	6146	1.50	RAF24	0.55	6CC97	0.30
30P21	0.70	6146B	2.50	EB33	0.50	6CC98	0.40
30PL13	0.33	6360	1.25	EB34	0.55	6CC99	0.40
30PL14	0.90	6870	2.50	EB38	0.30	6CC100	0.40
30A3	0.55	6899	2.15	EBF80	0.40	6CC101	0.40
30A5	0.75	686A	0.75	EBF83	0.40	6CC102	0.45
30B5	0.65	7360	1.80	EBF89	0.20	6CC103	0.45
30C5	0.45	7586	1.25	EC53	0.50	6CC104	0.45
30D1	1.10	35D5	0.70	7895	1.25	EC86	0.40
30E1	0.30	9002	0.35	EC88	0.50	EC186	0.40
30E4	0.30	9003	0.50	EC90	0.38	ECLL800	0.35
30E7	0.60	AZ1	0.48	EC91	0.50	EP37A	0.60
30E8	0.30	AZ31	0.55	EC92	0.35	EP39	0.40
30E9	0.30	CBL1	0.80	EC93	0.50	EP40	0.40
30A5	0.70	CBL3	0.90	EC801	0.25	EP41	0.35
30B5	0.45	CY31	0.35	EC80	0.60	EP42	0.70
30C5	0.45	DF96	0.42	EC81	0.33	EP43	0.55
30D5G1.65	0.65	DF96	0.42	EC82	0.30	EP44	0.55

6F93	0.55	6Y88	0.43	PCL89	0.90	U79	0.80
6F95	0.35	E240	0.45	PCL800	0.93	U191	0.75
6F86	0.30	E241	0.45	PCL801	0.70	U201	0.35
6F89	0.28	E280	0.25	PD500	1.50	U261	0.40
6F91	0.33	E281	0.28	PF80	0.60	U282	0.40
6F92	0.40	GY501	0.80	PF818	0.85	U281	0.40
6F95	0.30	GZ30	0.40	PFL200	0.70	U403	0.50
6F97	0.65	GZ31	0.38	PL38	0.35	U404	0.40
6F98	0.35	GZ32	0.48	PL36	0.55	U801	1.00
6F183	0.30	GZ33	0.70	PL81	0.50	UAB80	0.40
6F184	0.35	GZ34	0.60	PL82	0.45		
6F800	1.00	HA80800.45	0.45	PL83	0.45	UAF41	0.50
6F804	1.25	HK90	0.35	PL84	0.40	UAF42	0.55
6K90	0.30	KT66	2.05	PL89	0.80	UB41	0.50
6L33	1.25	KT88	2.00	PL604	0.80	UB91	0.40
6L34	0.50	N78	1.45	PL608	0.90	UBP90	0.40
6L37	1.25	PC88	0.80	PL609	1.30	UBP98	0.35
6L41	0.55	PC88	0.80	PL801	1.80	UBL1	0.50
6L42	0.58	PC97	0.60	PL801	0.80	UBL21	0.60
6L51	1.50	PC90	0.45	PM84	0.50	UC92	0.35
6L83	0.40	PC94	0.40	PM84	0.50	UC93	0.40
6L84	0.25	PC85	0.40	PM84	0.50	UC92	0.35
6L85	0.43	PC88	0.65	PM84	0.50	UC92	0.35
6L86	0.40	PC89	0.60	PM84	0.50	UC92	0.35
6L90	0.35	PC89	0.60	PM84	0.50	UC92	0.35
6L95	0.35	PC85	0.40	PM84	0.50	UC92	0.35
6L96	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L97	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L98	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L99	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L100	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L101	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L102	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L103	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L104	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L105	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L106	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L107	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L108	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L109	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L110	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L111	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L112	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L113	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L114	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L115	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L116	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L117	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L118	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L119	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L120	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L121	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L122	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L123	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L124	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L125	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L126	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L127	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L128	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L129	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L130	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L131	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L132	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L133	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L134	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L135	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L136	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L137	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L138	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L139	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L140	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L141	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L142	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L143	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L144	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L145	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L146	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L147	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L148	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L149	0.45	PC85	0.40	PM84	0.50	UC92	0.35
6L150	0.45	PC85	0.40	PM84	0.50	UC92	0.35

## TRANSISTORS

2N404	0.17	28102</
-------	------	---------

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomms.**  
C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.

Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**

Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T., and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D258, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



# BIET

## POST THIS COUPON TODAY

To: B.I.E.T., Dept D258, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name..... Age.....

Address.....

..... Occupation.....

**B.I.E.T - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-624 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-6s.  
PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

# HENRY'S RADIO LIMITED

## ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

### TRANSISTOR AMPLIFIERS

NEW RANGES NOW IN STOCK  
(Leaflets Ref. No. 6 and 8)  
Post etc. 20p

4-300 4 TR 9V 300mW	£1.75
104 4 TR 9V 1W	£2.12
304 4 TR 9V 3W	£2.47
555 6 TR 12V 3W	£2.75
PA7 6 TR 16V 7W	£3.62
608 6 TR 24V 10W	£4.12
410 4 TR 28V 10W	£4.97
MPA12/3 6 TR 18V 12W	£4.50
MPA12/156TR36V12W	£5.25
Z30 9 TR 30V 20W	£3.75
PA25 10 TR (Spl) 25W	£7.50
Z50 30V 40W	£5.47
PA50 12TR (Spl) 50W	£9.50
100 100W with Power Supply	£45.00

Post 45p

### OPTIONAL POWER SUPPLIES

Post etc. 20p.		
P500	(One or Two) for 104, 304	£2.62
P520	(One or Two) for PA7	£3.47
MU24/40	(One or Two) for MPA12/3 or MPA12/15	£4.50
PZ5 for Z30	or PZ6 for Z30	£6.97
PZ8 for Z50	Transformer	£2.25
P11 for 608	P15 for 410	£2.62
MU42 for 1 or 2	PA25 or 1 only PA50	£6.50

SINCLAIR PROJECT 60 PACKAGE DEALS  
2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply. £16.75. Carr. 40p. Or with PZ6 power supply £18.25. Carr. 40p. 2xZ50 amplifier, stereo 60 pre-amp, PZ6 power supply. £20.25. Carr. 40p. Transformer for PZ8 £2.25 extra. Any of the above with Active Filter unit add £4.75 or with pair Q16 speakers add £15. Also new FM Tuner £21.

### BUILD THIS VHF FM TUNER



5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO.  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

TOTAL £6.97 p.p. 20p  
Cabinet 100p, Decoder Kit £5.97, Tuning meter £1.75  
Mains unit (optional) Model PS900 £2.47  
Mains unit for Tuner and Decoder PS1200 £2.62

### BUILD YOURSELF A QUALITY RADIO



Excellent printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.  
Total cost £6.98 p.p. 35p.  
All parts sold separately.

Ask for leaflet No. 1.

### HI-FI TO SUIT EVERY POCKET



### CHOOSE 100 STEREO FROM

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only)  
**FREE**—Stock list No. 16/17 on request—BEST VALUE IN U.K.

### HENRY'S LATEST CATALOGUE



Now 350 pages.  
WHY NOT SEND AWAY TODAY

- ★ COMPONENTS, TEST GEAR
- ★ EQUIPMENT, MODULES
- ★ SPECIAL OFFERS, etc. etc.

Everything for the constructor. Complete with 50p value discount vouchers for use with purchases. Price 50p Post Paid.


- FREE** 8 page Transistor, IC, Diode lists No. 36
- FREE** 20 page Organs to Build brochure No. 9
- FREE** Decks and Hi-Fi Stock Lists No. 16/17
- FREE** PA, Disco and Lighting List No. 18
- FREE** Quotations for all Electronics—send list and S.A.E.
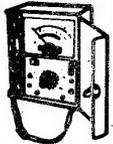
### TEST EQUIPMENT FOR HOME, SCHOOL & PROFESSIONAL USE




AF105 50k/volt multimeter (illus.). Price £8.50, p.p. 20p. Leather case £1.42. 200H 20k/volt. Price £3.87, p.p. 20p. Case 62p  
500 30k/volt multi-meter. Price £8.87, p.p. 20p. Leather case £1.50.  
THL 33 2k/volt. Price £4.12, p.p. 15p. Leather case £1.15  
TE65 Valve voltmeter (illus.). Price £17.50 p.p. 40p.  
SE250B Pocket pencil signal injector. Price £1.75 Post Paid.

SE500 Pocket pencil signal tracer. Price £1.50 Post Paid.  
TE20D RF generator Price £15. p.p. 40p  
TE22D Matching audio generator. Price £17. p.p. 40p.  
TE15 Grid dip meter. Price £12.50, p.p. 40p  
TO3 Scope 3" tube. Price £37.50, p.p. 50p.  
TE22 Audio Generator £17. p.p. 40p



(GET A COPY OF OUR LATEST CATALOGUE FOR FULL SPECIFICATIONS AND FURTHER RANGES.)

### NEW MINIATURE LOW COST AMPLIFIER

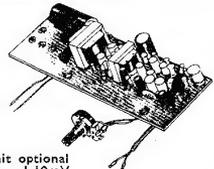

MODEL 4-300

9 volt operated or mains unit optional transformer (MT98 70p). 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fitted volume control and leads. Size 5 1/4" x 1 1/2" x 3/4". Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.

PRICE £1.75

p.p. 15p  
Complete with FREE leaflet No. 8.

### STC TIME DELAY MODULE



Ideal for experimenters, educational projects as well as for practical uses. Delay adjustable 3-15 secs. Operates 9-12 volts. Heavy Duty Relay Contacts. Complete with suggested applications sheet. Price £1.75 Post Paid.


### GARRARD TAPE DECK



9 volt operated 2-speed tape deck fitted Record/Replay & track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9" x 6 1/2" x 1 1/2". Takes up to 4" spools. Supplied Brand New.

Price £9.97  
P. & P. 33p  
3 1/2" Tape  
300' and spool 40p

### HENELEC SELF-POWERED PRE-AMPLIFIERS

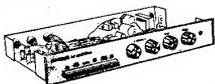

Designed for use with PA25 and PA50 Amplifiers GOLD AND SILVER FINISH, Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.

- ★ FET9/4. Mono with built-in mic. mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12.50 p.p. 20p.
- ★ FET154 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16.50 p.p. 25p

SLIM, MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS FET's and IC's. DIN SOCKETS, Etc. fitted. Self powered.

PUSH-BUTTON SELECTION. ±20dB BASS AND TREBLE BOOST & CUT  
All inputs provided plus TAPE RECORD and REPLAY.


Also suitable for use with any power amplifier. Suggested types PA25, PA50, MPA12/3, MPA12/15

**SIMPLICITY TO MOUNT—EASY TO USE—DESIGNED FOR QUALITY, PERFORMANCE AND PRICE**  
All units no soldering—just edge connectors and plugs AS SPECIFIED FOR MANY "PRACTICAL WIRELESS" 1970 PROJECTS

### 25 WATT AND 50 WATT SILICON AMPLIFIERS
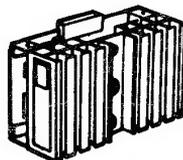
#### LOOK AT THE SPECIFICATIONS

- ★ At full power 0.3% distortion.
- ★ At full power—1dB 11c/s to 40 kc/s.
- ★ Response—1dB 11 c/s to 100 kc/s.
- ★ Rise time 2µ sec.
- ★ Short circuit proof plus limiting cct.



PA 25 10 transistor all silicon differential input 400mV sensitivity, 25 watts Rms into 8 ohms. Supplied with edge connector harness size 5" x 3" x 2".  
PA 50 12 transistor version 50 watts Rms into 3 to 4 ohms. Size 5" x 3" x 4".  
MU 442. Power supply or one or two PA 25 or one PA 50  
PA 25 £7.50; PA 50 £9.50. MU 442 £6.00 P. & P. 20p each.

Electronic Components & Test Gear Centre  
356 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 4736  
OPEN 9 a.m. to 6 p.m. MONDAY TO SATURDAY

High Fidelity Sales & Demonstrations Centre  
354 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre  
309 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 6963

Mail Orders. Special Bargain Shop. Industrial Sales  
303 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 1008/9  
OPEN ALL DAY SATURDAY

**\*WHY PAY £40 OR MORE?**

VHF FM.MW. A.F.C. PLUS SPECIAL AIRCRAFT WAVEBAND!

COMPLETE PORTABLE HIGH FIDELITY COMMUNICATIONS & RADIO RECEIVER

OUR PRICE POST ETC. £11.97p 38p

FREE TO EVERY PURCHASER "AIRCRAFT SPOTTER" HIGH POWER "BINO-SCOPE" BINOCULARS

PICKS UP AIRCRAFT TRANSMISSIONS (control to aircraft, etc.), SHIPS AT SEA, POP PIRATES TAXIS, AMBULANCES, LOCAL RADIO STATIONS, CONTINENTAL STATIONS, ALL BBC, VHF & MANY, MANY, MANY MORE, including fascinating public service transmissions that are not allowed to mention! A miracle of advanced technology! You get far, far more than an ordinary radio! An instrument that will bring a new dimension to your world of sound!

Frequency range: MW 540—1600 KHz, FM 89—108 MHz, Air 108—138 MHz, Intermediate Frequency: MW 455 KHz, FM 10.7 MHz, Air 10.7 MHz, 18 SEMI-CONDUCTORS: Transistors 11, Diodes 6+ Thermister! Automatic frequency control 'locks-in', eliminating drift. Pinpoint stations selection! Built-in adjustable 8-section 31" telescopic aerial. Lowest price ever! Tremendously strong leather-grained case with carry handle, 10 1/2" x 6 1/2" x 4" overall approx. Written guarantee. Only £11.97p, carr. etc., 38p—with FREE pair of "aircraft spotter" high power "bino-scope" binoculars with built-in filters for viewing in strong sunlight & independent left & right eye focus. Send or call. \*Compare it with sets costing £40 or more! Refund if not delighted. BONUS OFFER: Shoulder strap, earphone for personal listening & batteries, all for 23p extra, if required.

SHOPERTUNITIES LTD. Dept. WP/6, 164 UXBURIDGE ROAD, (facing Shepherd's Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7). Also 37 High Holborn, London, W.C.1 (Wed. 1, Thurs. 7). Both stores open from MONDAY-SATURDAY 9-6.

ONLY FROM US! FIRST SHIPMENT JUST ARRIVED!

BRAND NEW 1971 Model! RUSSIAN WORLD BEATER!

WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!

6 WAVEBAND 10 TRANSISTOR PORTABLE RADIO

WORLD WIDE RECEPTION £9.97p

THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER! BOX POST ETC. 43p

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

THE LATEST 1971 MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO. DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £24 radios! \* Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2" length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial. UNIQUE! Elegant Black, White and Chrome finish case. SIZE 10 1/2" x 8" x 3 1/2" overall approx. Beautifully designed, made to give years of perfect service. With WRITTEN GUARANTEE, manual with simple operating instructions and circuit diagram. ONLY £9.97, POST ETC. 43p. Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

**PHOTOELECTRIC KIT**

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.

**PHOTOELECTRIC KIT £1.95**

Postage and Pack. 15p (UK)

Commonwealth: SURFACE MAIL 20p AIR MAIL £1.00

Australia, New Zealand, S. Africa, Canada and U.S.A. Also Essential Data Circuits and Plans for Building 10 Advanced Designs

**INVISIBLE BEAM OPTICAL KIT**

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, building plans, etc. Price £1.00 Postage and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p, Air Mail 30p.

**LONG RANGE INVISIBLE BEAM OPTICAL KIT**

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.50. Postage and Pack 5p (U.K.). Commonwealth: Surface Mail 15p, Air Mail 50p.

**JUNIOR PHOTOELECTRIC KIT**

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price £1.00. Postage and Pack. 5p (U.K.). Commonwealth 10p; Airmail 20p.

**JUNIOR OPTICAL KIT**

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photo-cell receiver for use with Junior Photoelectric Kit. Price 50p. Post. and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p; Air Mail 20p.

**VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED**

**SETS** 1R5, 1S5, 1T4, 354, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.02. DAF96, DF96, DK96, DL96, 4 for £1.04.

L47GT	-87	2SL6GT	-85	DL35	-25	EL90	-26	PCF808	-72	UAB80	-85
1H5GT	-86	25U4GT	-57	DL92	-28	EL200	-62	PCL82	-38	UAF42	-51
1N6GT	-88	30C1	-80	DL94	-37	EM80	-41	PCL83	-30	UB41	-52
1R5	-28	30C15	-63	DL96	-38	EM81	-37	PCL84	-37	UB80	-84
1R5	-21	30C17	-80	DY86	-28	EM84	-33	PCL85	-45	UF89	-83
1R4	-18	30C18	-87	DY87	-28	EM87	-37	PCL86	-41	UCC84	-85
384	-28	30G6	-78	EAB80	-32	EY51	-36	PCL88	-72	UC86	-86
3V4	-37	30FL1	-63	EAF42	-50	EY86	-32	PCL89	-77	UC80	-38
5V4G	-37	30FL12	-72	EB91	-11	EZ40	-43	PEN44	-42	UCH42	-82
FX3GT	-80	30FL14	-72	EB338	-40	EZ41	-43	PEN36C	-70	UCH81	-32
2Z4G	-37	30L1	-32	EB341	-54	EZ80	-48	PEN20	-48	UC82	-82
6J0L2	-58	30L15	-62	EB300	-22	EZ81	-24	PL86	-49	UC83	-55
6AL5	-11	30L17	-72	EBF80	-33	EZ30	-37	PL81	-46	UF41	-83
6AM6	-12	30P4	-65	EBF89	-31	EZ82	-43	PL81A	-51	UF89	-83
6AQ5	-28	30P12	-77	ECC81	-18	EZ84	-50	PL82	-33	UL41	-60
6AT6	-22	30P19	-65	ECC82	-33	KV41	-27	PL83	-33	UL44	£1.00
6AU6	-22	30PL1	-83	ECC83	-35	KV61	-55	PL84	-33	UL84	-85
6BA6	-22	30PL13	-88	ECC88	-28	KV66	-33	PL500	-65	UM84	-22
6BE6	-22	30PL14	-70	ECC804	-60	LN319	-63	PL504	-67	Y41	-41
6BJ6	-42	30PL16	-90	ECCF80	-30	LN329	-27	PL608	£1.17	Y85	-25
6BW7	-60	35L6GT	-43	ECCF82	-30	LN339	-63	PM84	-37	VP4B	-77
6CD6G	£1.10	35W4	-28	ECH35	-30	N78	-87	PK26	£1.17	Z77	-22
6FL4	-45	35Z4GT	-25	ECH42	-63	P61	-50	PT82	-55	Transistors	
6F2S	-71	807	-45	ECH81	-29	PAB30	-35	PT83	-56	AC107	-17
6F2S	-62	6063	-62	ECH83	-41	PC86	-51	PY81	-27	AC127	-18
6K7G	-12	AC/VP2	-77	ECH84	-37	PC88	-51	PY82	-27	AD140	-87
6E6G	-17	AZ31	-55	ECL20	-35	PC96	-42	PY83	-28	AF115	-30
6F2S	-60	B349	-65	ECL82	-33	PC97	-40	PY88	-35	AF116	-30
6SL7GT	-27	B729	-62	ECL86	-40	PC900	-37	PY800	-37	AF117	-30
6V6G	-20	CCH35	-67	EF39	-23	PC884	-32	PY801	-37	AF118	-30
6V6GT	-32	CL33	-92	EF41	-60	PC885	-60	R19	-32	AF125	-17
6X4	-23	CY31	-38	EF50	-24	PC888	-65	R20	-65	AF127	-17
6X50GT	-28	DAC32	-38	EF85	-51	PC889	-47	U25	-68	OC26	-25
6F13	-60	DAF91	-21	EF86	-51	PC889	-51	U26	-65	OC44	-19
12AH3	£2.25	DAF96	-36	EF89	-28	PC8805	-65	U47	-68	OC45	-12
12AT7	-18	DF33	-38	EF91	-13	PCF80	-30	U49	-65	OC71	-12
12AU6	-28	DF91	-16	EF183	-22	PCF82	-32	U78	-24	OC72	-12
12AU7	-23	DF96	-16	EF184	-32	PCF86	-47	U91	-62	OC75	-12
12AX7	-28	DE77	-22	EF80	-22	PCF800	-67	U183	-42	OC81	-12
19BG6G	-87	DK32	-37	EL33	-53	PCF801	-65	U261	-72	OC81D	-12
20F2	-67	DK91	-28	EL34	-49	PCF802	-45	U301	-52	OC82	-12
20F3	-55	DK92	-42	EL41	-54	PCF805	-67	U329	-72	OC82D	-12
20F4	-82	DK96	-38	EL44	-24	PCF806	-60	U801	-38	OC170	-32

**YORK ELECTRICS Mail Order Dept.**  
335 BATTERSEA PARK RD., LONDON S.W.11  
Send S.A.E. for full details, a brief description of all Kits and Projects

**READERS RADIO**  
85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.  
Tel. 01-550 7441.  
Postage on 1 valve 5p, on 2 or more valves 3p per valve extra.  
Any parcel insured against damage in transit 3p extra.