

PRACTICAL WIRELESS

OCTOBER
1972

20

**FREE INSIDE
PRACTICAL
AERIAL
DATA
WALL CHART**

THE

PW

PRE-TUNED

CAR/PORTABLE

RADIO

also:

**AUDIO REFERENCE SOURCE
'LOGIPROBE' FOR DIGITAL IC's**



RSC HIGH-FIDELITY STEREO PACKAGE OFFERS

Four fully wired units ready to 'plug in'.
 ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
 ★ GARRARD SP25 MK III Turntable on Plinth with cover
 ★ GOLDRING G850 Magnetic cartridge with diamond stylus
 ★ PAIR OF STANWAY II Speaker Units
 Special Total Price **£87.95**
 Carr. £1.50

Terms: Deposit £12.77 and 9 monthly payments £9.39 (Total £97.28).

★ Super 30 Amplifier (15 + 15 watt) in veneered housing
 ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
 ★ Goldring Magnetic P.U. Cartridge.
 ★ Pair of Stanway II speaker units.
 Special Total Price **£98.63** Carr. £1.50

Terms: Deposit £13.63 and 9 monthly payments £10.62 (Total £109.21).



ATTRACTIVE TEAK OR AFROMOSIA VENEERED CABINETS AND PLINTHS
 Send S.A.E. for coloured brochure showing other money saving offers.

★ TA12 AMPLIFIER 6.5 + 6.5 watt in veneered housing
 ★ GARRARD SP25 MK III Player unit on Plinth
 ★ SONOTONE 9TA1HC Ceramic P.U. Cartridge with diamond stylus
 ★ PAIR OF DORCHESTER Loudspeaker Units
 Special Total Price **£59.00**
 Or Deposit £8.40 + 9 monthly payments £6.32 (Total £65.28). Carr. £1.25
 Trans. Plastic Cover £3.15 extra.

PACKAGE AS ABOVE but with Garrard 3000 Autochanger and Sonotone 9TA Ceramic Cartridge in lieu of SP25
 Carr. £1.25
 Or Deposit £7.50 and 9 monthly payments £5.64 (Total £58.26)
 Trans. Plastic cover £3.15 extra.

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms
 ★ Performance comparable with units costing considerably more.
 Consists of (1) 2in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4.60 and 9 monthly payments £2.47 (Total £26.83).

COMPLETE KIT **£23**
 Carr. 65p


DEMONSTRATIONS AT ALL BRANCHES

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.
 DORCHESTER (Illustrated) Size 16 x 11 x 9in. approx. Range 45-15,000 c.p.s. Rating 6-10 watts. Fitted high flux 13 x 8in. **£9.45** Carr. 40p.
 Dual Cone speaker. Imp. 3 or 15 ohms.
 STANWAY II Size 20 x 10 1/2 x 9 1/2 in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for **£19.35** illustration Carr. 50p

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal face plate and matching control knobs.

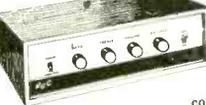

COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagrams and instructions **£11.50** Carr. 40p

Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated **£14.99** or dep. **£2.20** and 9 monthly payments **£1.70** (Total £17.50).

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction.
 OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£6.95** Carr. 35p



AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.
 Exceptional performance at low cost.
 HF808T 8" 10W £2.88 HF120D 12" 15W £4.99
 HF102D 10" 10W £3.40 HF128 12" 15W £5.75
 HF120 12" 15W £4.50 HF126D 12" 15W £8.25




FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high tone response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. **£3.85**
 PLEASE STATE IMPEDANCE WHEN ORDERING



R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL
 Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs.
 COMPLETE KIT OF PARTS WITH FULL **£15.50** Carr. Factory built with WIRING DIAGRAMS & INSTRUCTIONS **£19.50** Dep. **£3** and 9 monthly payments **£2.15** (Total £22.95). Or in Teak veneer housing **£23** Dep. **£3** & 9 monthly payments **£2.55** (Total £25.95). Send S.A.E. for leaflet.

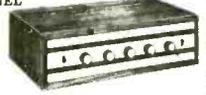

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.
 JEB Size 16 x 11 x 9in. SE8 For optimum performance with any 8in. Hi-Fi spkr. Size 22 x 15 x 9in. **£6.47**
 8in. Hi-Fi speaker. **£5.35**
 SE10 For outstanding results with 10in. Hi-Fi spkr. Size 24 x 15 x 10in. P.t.d. **£6.74**
 SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter Size 25 x 16 x 10 1/2 in. **£7.87**




R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML. An all-dry battery eliminator. Size 5 1/4 x 4 1/2 in. approx. Completely replaces batteries supplying 1.5v and 90v. to battery radio where A.C. mains 200/250v. 50c/s is available.
 COMPLETE KIT **£3.25** ASSEMBLED READY **£3.75** WITH DIAGRAM FOR USE



R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. - 2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 2 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.75** Carr. 40p.
 OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£10.95**

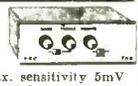

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

Only high grade components by leading manufacturers.
 COMPLETE KIT OF PARTS OR FACTORY BUILT with 12 months guarantee. Dep. **£5.75** and 9 monthly payments **£3.50** (Total £37.25).
 OR FACTORY BUILT in cabinet as illustrated. Dep. **£7** and 9 monthly payments **£3.99** (Total £42.91)
 TECHNICAL DETAILS (Applying to each channel where appropriate)
 CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble and Balance. Plus Ceramic Mag P.U. Switch.



PRINTED CIRCUITRY TWENTY SILICON TRANSISTORS. FOUR DIODES. FOUR RECTIFIERS

★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
 ★ PUSH-BUTTON SELECTOR SWITCHING
 ★ NEON INDICATOR
 ★ JACK SOCKET FOR HEADPHONES
 ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC. REGARDLESS OF PRICE. WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

OUTPUT: 15 watts R.M.S. (Continuous) Into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.
 HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION
 FREQUENCY RESPONSE - 30B 7Hz to 70kHz 0-1% at 1000 Hz 10 Watts
 TREBLE CONTROL: +16dB to -12dB at 14kHz
 BASS CONTROL: +17dB to -16dB at 40Hz
 CROSS TALK - 58dB
 SENSITIVITIES: Disc Mag. 2.5 mV. Ceramic 35mV. Radio 120mV. Tape 120mV.
 REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

RSC STEREO HI-FI TUNER NOW AVAILABLE. Visually matches Super 30 MkIII £44.95

RSC GROUP/DISCO UNITS

Units listed below



50 WATT SPEAKER



100 WATT AMPLIFIER



TWIN TURNTABLE WITH PREAMP FGI/2A

(a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEAD-
 PHONES
 (c) MATCHING DYNAMIC 'MIKE'
 (Attached to headphones)
 (d) PAIR 50 WATT SPEAKERS
 Black Rexine covered
 Cabinets
 Size approx. £72-85
 18" x 18" x 8"
 (a) (b) (c) & (d)

Terms on Amps. Speakers and Head-
 phone/Mike. Deposit £15 and 18
 monthly payments of £3-95 (Total
 £86-10).

R.S.C.TDI DISCO NSOLE
 Incorporating twin Garrard SP25
 Mk.III turntables and Ceramic
 Cartridges with diamond stylus.
 Separate Vol. controls for each
 turntable. Also MOUNTING
 FACILITIES, plus Treble and Bass
 Controls. Separate input for 'mike'
 with vol. control switch. Black
 Rexine covered Cabinet with lid.
 see illus. on left
 Carr. £1-25
 Or Dep. £13-25 and
 9 mthly pymts £6-75
 (Total £74) Or Dep. £15 and 18 mthly
 pymnts £3-66 (Total £79-03)
£67-10

R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair
 TYPE C410 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C48S 25-30 WATTS
 Fitted four 8" high flux 8 watt speakers
 Overall size approx. 48 x 10 x 10
 Terms: Dep. £3 and 9 monthly
 payments £2 (Total £22) Carr. 50p.

TYPE C412S 50 WATTS
 Fitted four 12" 11,000 line 15 watt
 speakers: Overall size approx. 56 x 14 x 9 1/2
 Terms: Dep. £4 and 9 monthly pay-
 ments £3-37 (Total £34-33) Carr. 75p

£65

TYPE C4100 200 WATTS Inc. four 12" 50 watt speakers for conserva-
 tive raking. Extra heavy construction. Size approx. 68 x 16 x 10" Acoustically
 filled and pressurised. Terms: Dep. £11 and 9 mthly. pmts. £6-75 (Total £71-75). Carr. £1

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE
 High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100Watt 14,000 gauss 8/150	15" 60 Watt 14,000 gauss 8/150	12" 50 Watt 13,000 gauss 150
£22-95	£12-90	£10-90
Dep. £6 and 9 mthly payments £2-20 (Total £25-80)	Dep. £3-30 and 9 monthly payments. £1-30 (Total £15).	Dep. £2 and 9 monthly pay- ments £1-20 (Total £12-80)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes. 200-250V. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete Kit of parts with wiring diagram and instructions. Twin-handled perforated cover. £15-75

Or factory built with EL34 output valves and 12 months' guarantee for £19-75
 £1-80. Or factory built with EL34 output valves and 12 months' guarantee for £19-75
TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet.

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. or Dep. £1 and 9 mthly free payments 75p (Total £7-75).

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary.

Primaries 200-250V. 50c/s. Screened
MIDGET CLAMPED TYPE 21 x 21 x 2 1/2 in.

260v., 60mA, 6-3v. 2a	90p
200v.-0-250v., 60mA 6-3v. 2a	£1-05

FULLY SHROUDED UPBRIGHT MOUNTING

250-0-250V. 60mA, 6-3v. 2a, 0-5-6-3v. 2a	£1-40
250-0-250V. 100mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-45
300-0-300V. 100mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-20
300-0-300V. 130mA, 6-3v. 4a, c.t., 6-3v. 1a	£2-65

For Mullard 510 Amplifier

350-0-350V. 100mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-20
300-0-350V. 150mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-45
425-0-425V. 200mA, 6-3v. 4a, c.t., 6v. 3a	£4-95
425-0-425V. 200mA, 6-3v. 4a, c.t., 6v. 3a, 5v. 3a	£5-10
450-0-450V. 250mA, 6-3v. 4a, c.t., 6v. 3a	£5-50

TOP SHROUDED DROP-THRO' TYPE

250-0-250V. 70mA, 6-3v. 2p, 0-5-6-3v. 2a	£1-35
250-0-250V. 100mA, 6-3v. 3a, 0-5-6-3v. 2a	£1-55
250-0-250V. 100mA, 6-3v. 2a, 6-3v. 1a	£1-40
300-0-300V. 80mA, 6-3v. 2a, 0-5-6-3v. 2a	£1-65
200-0-250V. 100mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-20
300-0-300V. 100mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-20
300-0-300V. 130mA, 6-3v. 4a, c.t., 6-3v. 1a	£2-60

Suitable for Mullard 510 Amplifier

350-0-350V. 100mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-40
350-0-350V. 150mA, 6-3v. 4a, 0-5-6-3v. 3a	£2-80

FLYBANK OR TRANSISTOR POWER PACK

Elements 6-3v. 1-5a. 49p; 6-3v. 2a. 54p; 6-3v. 3a. 76p;	6-3v. 6a. £1 30; 12v. 1a. 55p; 12v. 3a. or 24v. 1-5a £1-35; 0-9-18V 1 1/2 £1-10; 0-12-26-42v 2a £1-76.
---	--

CHARGER TRANSFORMERS 0-5-15V. 1 1/2A. 90p
 2 1/2A. £1-10; 3A. £1-25; 5A. £1-45; 6A. £1-65; 8A. £2-00

AUTO (Step UP/step DOWN) TRANSFORMERS
 0-110/120V. 200-230-250V. 60-70 watt £1-10,
 150 watt, £1-90 250 watt £2-75; 500 watt £5-75

OUTPUT TRANSFORMERS
 Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p
 Push-Pull 8 watt EL34 to 3 Ω or 15 Ω. £1-37
 Push-Pull 10 watt 6V8, ECL86 to 3, 5, 8 or 15 Ω £1-87
 Push-Pull EL84 to 3 or 15 Ω 10-12 watts. £1-85
 Push-Pull Ultra Linear for Mullard 510, etc. £2-20
 Push-Pull 15-18 watt, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω. £1-99
 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3-30

SMOOTHING CHOKES 150mA, 7-10H. 250 Ω
 70p; 100mA, 10H, 200 Ω 60p; 80mA, 10H, 350 Ω 50p; 60mA, 10H, 400 Ω 25p.

SELENIUM RECTIFIERS F. W. (Bridged)
 All 6/12V. D.C. output. Max. A.C. input 18V.
 1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

Package	Price
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95
PR. FANE POP 25/2 25W L/SPEAKERS	£13-50
Terms: Deposit £6-50 and 9 monthly payments of £4-75 (Total £45-38)	£45 carr. £1
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95
PR. FANE POP 50 L/SPEAKERS	£21-80
Terms: Deposit £10 and 9 monthly payments of £5-25 (Total £57-25)	£52 carr. £1
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95
PAIR L12/25 25W L/S in cabinets	£23-90
Terms: Deposit £12 and 9 monthly payments of £5-75 (Total £81-75)	£56 carr. £1-25
F.A.L. PHASE 100 AMPLIFIER	£81-95
4 FANE POP 50 L/SPEAKERS	£43-80
Terms: Deposit £15-95 and 9 monthly payments of £10-50 (Total £110-45)	£99-95 carr. £2

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH
 L125 50 WATT Fitted pair of 12" 50
 watt high flux speakers for conservative
 rating. Impedance 8-15 ohms. Carr. £1-50
 Or deposit £4-50 and 9 monthly pmts. of £3-82. Total £37-08

L12/25 12" 25 WATT 10,000 lines	£11-95	L13 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State imped- ance required. Carr 40p	£5-25
------------------------------------	---------------	---	--------------

FAL PHASE 50 MK.III AMPLIFIER 50W

Solid state. 4 Separately controlled inputs
 Plus master vol. control. Ind. Bass and Treble
 Controls. Protective circuit to guard against
 damage from accidental short. Output for
 Speakers 3 to 30 ohms. Size 17" x 7" x 7".
 200-250V. A.C. mains. Output 50 watts music rating.
 Or deposit £7-25 & 9 monthly payments £3-50. Total £38-75.
£34-95 Carr. 75p.

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted)
INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

R.S.C. Branches listed below open all day Saturdays

BRADFORD 10 North Parade (Half-day Wed.). Tel. 25349
BLACKPOOL (Agent) O & C Electronics

227 Church Street

BIRMINGHAM 30/31 Great Western Arcade,
 Tel. 021-236 1279 (Half-day Wed.)

DERBY 26 Osmaston Rd., The Spot (Half-day Wed.).
 Tel. 41361

DARLINGTON 18 Priestgate (Half-day Wed) Tel 68043

EDINBURGH
 101 Lothian Rd. (Half-day Wed.). Tel. 229 9501
 GLASGOW 326 Argyle St. (Half-day Tues.).

HULL 91 Paragon Street (Half-day Thurs.). Tel. 20505.
LEICESTER 32 High Street (Half-day Thurs.). Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Biggate
 (Half-day Wed.). Tel. 28252

LIVERPOOL 73 Dale Street (Half-day Wed.).
 Tel. 236 3573

LONDON 238 Edgware Road, W.2. (Half-day Thurs.).
 Tel. 723 1629

MANCHESTER 60A Oldham Street, (Half-day Wed.).
 Tel. 236 2778

MIDDLESBROUGH 106 Newport Rd. (Half-day Wed.).
 Tel. 47096

NEWCASTLE UPON TYNE
 24 Newgate Shopping Centre (Half-day Wed.). Tel. 21469
NOTTINGHAM 19/19A Market Street (Half-day Thurs.).
 Tel: 48068

SHEFFIELD 13 Exchange Street (Castle Market Bldgs.)
 (Half-day Thurs.). Tel. 20716

SUNDERLAND 5 Market Square
 Tel. 70573

NOW THREE NEW BRANCHES

19/19A MARKET STREET
NOTTINGHAM
 ALSO 5 MARKET SQUARE
SUNDERLAND
 8 LITTLE UNDERBANK
STOCKPORT
 AND NEW MUCH LARGER PREMISES
 24 NEWGATE CENTRE, NEWCASTLE

RSC

HI-FI CENTRES LTD.

MAIL ORDERS & EXPORT ENQUIRIES TO:—
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 13.
 Tel: Pudsey (09735) 77631.

TERMS C.W.O. or C.O.D. No C.O.D. under £1.
 POSTAGE 25p EXTRA UNDER £2. 30p EXTRA
 OVER £2 OR AS QUOTED. TRADE SUPPLIED.
 S.A.E. PLEASE WITH ENQUIRIES.
 SUPPLIERS TO GOVERNMENT DEPARTMENTS.
 EDUCATION AUTHORITIES, SCHOOLS,
 HOSPITALS, H.M. FORCES ETC.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose
 unit for lead, rhythm, bass guitar,
 vocalists, gram, radio, tape. Peak
 Output rating. Loudspeaker unit
 optional horizontal or vertical
 mounting.

* 2 extra heavy duty 12in. 60W L'spkrs.
 * Four Jack inputs and two Volume
 Controls for instant use up to four pick-ups
 or "mikes". Bass and Treble controls.
 Credit Terms: Deposit £15 & 9 monthly
 pmts of £6-25 Carr. £2 (Total £71-25)

£65 Send S.A.E. for leaflet.

RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group.

A 4 input, 2 vol. control Hi-Fi 30 watt unit
 with Separate Bass and Treble controls.
 Current valves. Peak output rating. Strong
 Rexine covered cabinet with handles.
 Attractive black/gold P.V.C. fascia. Neon
 indicator. For 200-250V. A.C. mains. For 3
 or 15 ohm speakers. Send S.A.E. for leaflet.
 Terms: Deposit £4-40 and 9 monthly pay-
 ments of £2-40 (Total £28-00).

£23-50 Carr. 65p



ORGAN KITS

Build your own Electronic Organ, if you want the best value for your money. Yes you really save over 50% and get the best and up-to-date designs. There are four models to choose from.

- ★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, at £103.00, P/P £1.50.
- ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato built in amplifier and 50 watt 12" Goodmans speaker at £167.00, P/P £5.00.
- ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, Wah Wah, etc. at £406.00. Carr. paid on complete kit U.K. only.
- ★ Console—2 x 5 octave keyboards and 32 note pedal boards, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572.55 carr. paid on complete kit U.K. only.

We regret H.P. facilities are not available, but components can be bought separately. Trade and overseas enquiries welcomed. Send 25p for latest catalogue.

Please call in for demonstration. Business hours: 10 a.m. to 7 p.m. Monday to Saturday. Thursday closed.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE RD., LONDON
S.W.18 TEL: 01-870 4949

Bus numbers 37, 220, 225, 168 pass the door. 10 minutes walk from East Putney or 15 minutes walk from Putney Bridge Underground Stations.



MICROJET WELDER
A TINY FLAME UP TO 5000°F!
WELDS DC METALS
SOLDERS

£11.50

INC. 3
FLAME TIPS

A precision tool using a combination of butane and compressed oxygen. U.S.A. manufactured. Gives two sizes of flame of pencil lead thickness. Adjustable temperatures up to 5,000°F. Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc. gold and silver. Ideal for electronics and electrical engineering, jewelers, clock-makers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 oxygen and 1 butane cylinders £1.50 inc. post. Complete with instructions. Our price £11.50 + 31p P. & P. Send £11.81.

SUITABLE FOR ALL DOMESTIC
APPLIANCES & POWER TOOLS
INTRODUCTORY
PRICE ONLY



TWIST FREE STORAGE

WITH THE
**SAFE-WAY
MAINLINE
EXTENSION LEAD**

Store cable neatly. Heavy duty 3-core cable fitted unbreakable rubber standard 13 amp fused 3-pin plug & 3-pin socket. Saves trouble fitting yourself. For Domestic Appliances, Garden Power Tools, Hedge Trimmers, Mowers, etc. 30ft. app. cable & FREE storage reel £1.99 + 41p p. & p. Send £2.10. 15ft. app. £1.20 + 35p p. & p. 50ft. app. £2.20 + 41p p. & p. 75ft. app. £3 + 50p p. & p. 100ft. app. £3.75 + 65p p. & p. 50ft. app. 'Rover-point' cable with winder reel, socket, 1000' carry handle. £3.99 100' p. & p.

£1.69



13 AMP DISTRIBUTION PANEL

From
Only
£2.40

Safe and quick. FOUR 13 amp 3-pin shuttered Socket Outlets Red neon warning indicator operates when in use. Only £2.40 + 35p p. & p. Total £2.75. Also De Luxe Model (illus.) PLUS Magnetic Contact Breaker—If you draw too much current it switches off automatically. PLUS 30ft. (9 metres) approx. lead. £8.75 + 40p p. & p. Total £9.15. Bonus offer: If required, set of four fused 13 amp plugs 50p extra. Post free if ordered with above.

TWIN-BEAM SPEC. LAMP—Worn just like a pair of spectacles. Two powerful spot lamps illuminate working area. Can be worn with Binocular Magnifier. Battery operated. Only £1.90 + 10p p. & p. Send £2.

JOHN DUDLEY & CO. LTD. Dept. WP2, 301 Cricklewood Lane, Child's Hill, London, NW2. Tel. 01-458 5917 Callers welcome



BINOCULAR MAGNIFIER

FOR PRECISION CLOSE-UP WORK—LEAVES BOTH HANDS FREE

See close-up work with less eye strain & fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glass-works. Can be worn over normal glasses. An essential for modelling, industry, home and workshop. Stamp collecting. Jewellers, watchmakers and any fine work 2½ x magnification. £4.95 + 35p p. & p. Send £5.30. 3 x model 50p extra. State model.


ONLY
£4.95

See close-up work with less eye strain & fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glass-works. Can be worn over normal glasses. An essential for modelling, industry, home and workshop. Stamp collecting. Jewellers, watchmakers and any fine work 2½ x magnification. £4.95 + 35p p. & p. Send £5.30. 3 x model 50p extra. State model.

6

gang socket units

wall mounting or
bench mounting

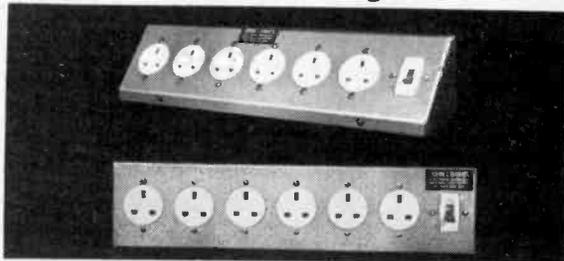

DIMENSIONS: 18 ins x 4½ ins. x 2½ ins. approx.

CONSTRUCTION: Metal box, hammer grey finish. Mk 13 amp Sockets. 45 amp Double pole switch internally wired.

PRICES: £4.87 each inc. carr. Cash with order. State if wall or bench socket is required. Quotation for 10 or more. Wholesale enquiries welcome.

MANUFACTURED BY


JOHN I. OAKES
NAYLAND · COLCHESTER · ESSEX
Telephone: Nayland 262405

AUDI SUPPLIES THE BIG DISCOUNT HOUSE

WE HAVE **SLASHED** PRICES AS NEVER BEFORE
ON THE FOLLOWING TOP QUALITY MAKES OF EQUIPMENT
BOWERS & WILKINS • BSR • AMSTRAD • ADC • AUDIO TECHNICA • CAMBRIDGE
AKAI • ROLA CELESTION • DECCA • EAGLE • EMPIRE • FIDELITY • FERROGRAPH
GARRARD • GOLDRING Lenco • KOSS • KEF • HOWLAND & WEST • METROSOUND
LEAK • WHARFEDALE • QUAD • ROGERS • SINCLAIR • VICEROY • PHILIPS • PICNEER
ROTEL • REVOX • SANSUI • SCAN ELTRA • TRANSCRIPTORS • SONAB • SME
PEERLESS • SONATONE • SHURE • ORTOFON • KORTING • NEAT • SENNHEISER *etc.*

**ADC
10E MKIV**
PRICE
£20.50
p.p10p.

**SYSTEM
AS 2000**

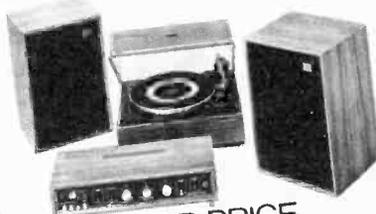

OUR PRICE
£69 p.p. £1-50
SAVE OVER £53

**GOLDRING
G 800 E**
PRICE
£8.99
p.p 75p

**BOWERS
& WILKINS
DMI SPEAKERS**
PRICE PER PAIR
£54
pp 75p.

**GARRARD
SP 25 MK III**
with Goldring G800
Deluxe Plinth & Cover
PRICE
£17.50
pp 75p

AUDIO SUPPLIES LTD., Dept. PW/10 50 STAMFORD HILL, LONDON N.16 Tel: 01-806 3611

ALSO AT:-

12 London Road, North End
Portsmouth, Hants.
120 Notting Hill Gate,
London W.11.

OPENING IN TOTTENHAM
COURT ROAD, W.1. DURING
AUGUST AND IN BIRMINGHAM
DURING SEPTEMBER

WE SPECIALISE IN MAIL ORDER/PERSONAL
CALLERS WELCOME. Send Cheques, Money
Orders, P/O, Giro, Bank Draft or Cash (Registered).
24 Hour Securicor delivery £1.50 extra to Postage
and Packing. Personal Callers: Note: We are easy
to get to by Public Transport.
Open: Mon., Tue., Wed., Thur., 9.30 to 6.00 p.m.
LATE NIGHT FRIDAY: 9.30 to 7.30 p.m. Sat:
9.30 to 5.00 p.m. Send large stamped addressed
envelope with all correspondence (except orders).
Cheques are only accepted from Personal Callers

if backed by a relevant bank cheque card.
Payment by Barclaycard accepted by
arrangement. All prices are subject to changes
as and when necessary. Credit facilities
available on purchases of £50 or more for
Personal Callers only. Send for further details.
For any information on goods write to manu-
facturer or importer concerned NOT US. This
advertisement is a small selection from our
most comprehensive quality range. Send 5p and
large S.A.E. for our complete price list.

Have fun with electronics...



Radionic Construction Kits



NO SOLDERING BATTERY OPERATED

Build your own radio receiver and many exciting experiments with the unique printed circuit board and mounted components. Easy to build, no soldering, battery operated, plus a fully illustrated instruction manual giving precise directions for each experiment. Ideally suitable for both the experimenter and beginner.

Radionic Products Limited

St. Lawrence House, Broad Street, Bristol BS1 2HF.
Tel: 0272 25351

Member of the ESL BRISTOL Group of Companies.

PHILIPS


Please send me literature on Radionic radio and electronics construction kits.

NAME _____

ADDRESS _____

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

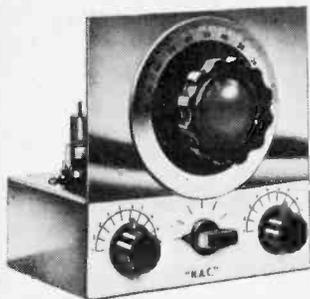

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hama, etc.

NEW "DX" RECEIVER


Improved one-valve model "DX" mark 2. Complete kit—price £3.30 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail orders only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

CAPACITOR DISCHARGE IGNITION KIT

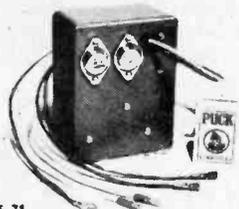

PW JUNE 71

A comprehensive kit of parts with detailed constructional details, ready drilled diecast case, screws, leads, terminals etc.

Available in both 6 and 12v versions. State whether positive or negative earth. £8.75 incl. p. & p. De-coupling kit for impulse tachometer and interference suppression. £1.00 incl. p. & p.


All our kits use guaranteed quality components and have been approved by the Author.

MAGTOR LTD.

68 DALE ST., MANCHESTER
M1 2HS 061 236 3031

The BATTERIES That Won't Let You Down! RECHARGEABLE

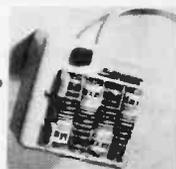Mallory Cells in U2, U11 and Penlite U7 sizes, Kestrel Battery Charging Unit



Uses:

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you *must* have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestrel Charging Unit which has been specially designed for these new type batteries.

PRICES

Batteries U2 equiv. £1.38

Penlite U7 equiv. 50p

U11 equiv. £1.03

Charging unit £3.90 with one battery holder

KESTREL

Bush & Meissner

Send to:
275 WEST END LANE
LONDON, N.W.6
01-794 9611

RTVC THE

THE FABULOUSLY SUCCESSFUL VISCOUNT III AUDIO £52 complete

14 + 14 watts r.m.s. 40Hz to 40kHz $\pm 3\text{dB}$. Total distortion at 10 watts at 1kHz -0.1%

This is real value for money! We have designed 2 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For both systems we have chosen the famous Garrard SP25 Mk. III deck which comes with fitted magnetic cartridge, simulated teak plinth and tinted acrylic dust cover. The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

SPEAKERS

Duo Type II Size approx. 17in. x 10 $\frac{1}{2}$ in. x 6 $\frac{1}{2}$ in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts, 8 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

Duo Type III Size approx. 23 $\frac{1}{2}$ in. x 11 $\frac{1}{2}$ in. x 9 $\frac{1}{2}$ in. Drive unit 13 $\frac{1}{2}$ in. x 8 $\frac{1}{2}$ in. with H.F. speaker. Max power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

SPECIFICATION

14 watts per channel into 3 to 4 ohms. (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0.1%. P.U.1. (for ceramic cartridges) 150mV into 3 Meg. P.U.2. (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within $\pm 1\text{dB}$ R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal-to-noise ratio: (all controls at max) -P.U.1. and radio -65dB, P.U.2 -58dB. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ x 9in. x 3 $\frac{1}{2}$ in.

BRITISH MADE—12 MONTHS WRITTEN GUARANTEE

Send S.A.E. for fully illustrated brochure

-ONLY FROM US

PRICES: SYSTEM 1

Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00+£1.50 p&p
Total	£59.00

Available complete for only £52 + £3.50 p&p

PRICES: SYSTEM 2

Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00+£1.50 p&p
Total	£77.00

Available complete for £69 + £4 p&p



MUSIC MAKERS

UNISOUND FOR THE NEW SOUND

AT £25

The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds!

Amplifier is based on the famous Mullard Unilux system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13" x 8" EMI Twin-cone speakers ready for mounting in their elegant cabinets, which simply need screwing and gluing together. All glue and screws supplied.

Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.

£25 complete plus £2.80 p. & p.
Diamond Stylus £1.25 extra.

Power output: 4 watts per channel into 8 ohms.
Inputs: 120 mV (for ceramic cartridges).
Stereo headphones with adaptor £4.00

UNISOUND MODULES ONLY £6.95

If you prefer, you can buy the three modules—pre-amplifier, power supply/dual power amplifier, and control panel—by themselves for only £6.95. P. & P. 50p extra.

No soldering, just simply screw together with screwdriver supplied. Their overall specification is the same as shown for the complete Unisound console, using the high efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum.



ANRTVC EXCLUSIVE DESIGN

A 'NATURAL' ONLY FROM THE TOURIST PB CAR RADIO KIT

ANRTVC

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms. Power consumption is less than 1 amp.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale for easy reading at night. Chassis size is: 7in. wide, 2in. high and 4 1/2 in. deep (excluding front panel, etc.).

- ★ Circuit diagram and comprehensive instructions 50p, free with parts.
- ★ Fully retractable, lockable, Car aerial £1.25 post paid.

Price only £7.00 + 50p p&p. 8 ohm speaker with baffle and fixing strips £1.50 post free if bought with kit + 25p p&p.

If you can solder on printed circuit board you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.



RELIANT MK.IV

- ★ 5 Electronically Mixed Inputs. ★ 3 Individual Mixing Controls. ★ Separate bass and treble controls common to all 5 inputs. ★ Mixer employing F.E.T. (Field Effect Transistor). ★ Solid State Circuitry. ★ Attractive Styling. ★ Finished in solid teak

INPUTS:—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram., Tuner, Monitor, Organ, etc.). All 250mV sensitivity. **CONTROLS:**—3 Volume controls. Bass control range: -13dB @ 60Hz. Treble control range ±12dB @ 15KHz. Separate ON/OFF Switch. Neon indicator. **POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohm speaker. **SIGNAL/NOISE:**—Better than -60dB on Inputs 3, 4 and 5 & -50dB on 1 & 2. **SUPPLY:**—220-250 AC Mains. **SIZE:**—12 1/2" x 6" x 3 1/2".

£10.50
plus p. & p. 60p

VISIT OUR SHOWROOMS

ANRTVC

S.A.E. for fully illustrated leaflet.


Radio and TV Components (Acton) Ltd.
21C High Street, Acton, London W3 5NG
323 Edgware Road, London, W2.

Mall orders to Acton. Terms C.W.O. All enquiries S.A.E.

LIGHT DIMMER KIT.

The unique Jermyn design with so many attractive features:

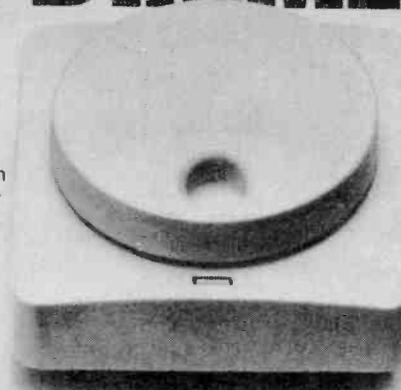1. True dimming action. Switch OFF/ON to full brightness, then turn for progressive dimming.
2. Finger hole makes operation easy and pleasant and enables any degree of brightness to be re-set.
3. Permanent beta-light glow means switch can always be found in the dark.




4. Handsomely styled body, suitable for mounting on standard or plaster-depth walls.

5. Load 300 W i.e. enough for 3 or 4 lamps per switch.

Price in kit form £2.80 inc. p & p.

All components included. Also available ready made-up £3.80.

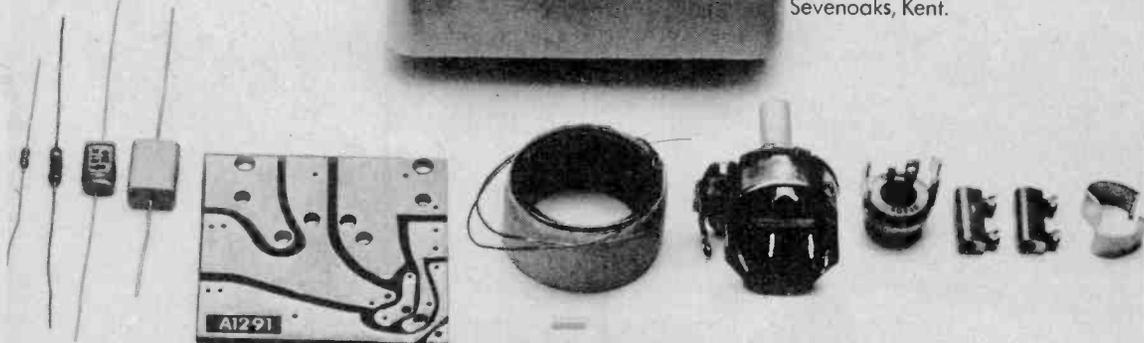Send cheque/P.O. to Jermyn Industries, Vestry Estate, Sevenoaks, Kent.



PRICE IN KIT FORM £2.80

introducing

ARROW ELECTRONICS LTD.

"Service the way it ought to be!"

an associate Company of LST ELECTRONIC COMPONENTS LTD

When it comes to retail distribution we're head and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way.

Here at Arrow Electronics fast, reliable service is law!

We offer a rapid, same day turn round on all mail received up to 3 pm on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

Our no fuss, no bother ordering system is a joy to behold. We'll give you all the forms and envelopes you could possibly need. Combine them with our simple Catalogue Coding and hey presto, you can order and order, time and time again without the slightest error or mistake.

You'll always be up to date with us—we're continually adding to our high quality stock range and always up dating our catalogue.

Get to know us and you'll soon raise your hat to our customer discount—it's tops with a total order value discount of 10% on orders exceeding £4.00.

Now's your chance to get to know us better. Our brand new Catalogue is now awaiting you, hot from the presses!

The New Arrow catalogue features the following:-

- Extended Ranges of Bridge Rectifiers
 - Capacitors
 - Interference Suppression Kits
 - Low Cost Integrated Circuit Mounting Pins
 - Knobs
 - Light Emitting Diodes
 - A Novel Logic Testing Instrument giving immediate visual indication
 - Magneto Resistors
 - Optically Coupled Isolators
 - Extended Range of Potentiometers
 - Medium current and High current Rectifiers
 - Temperature controlled Soldering Irons
 - Extended Range of Thyristors
- and many other items of great interest to the home constructor.

Arrow Electronics Limited
Dept. PW1.
7 Coptfold Road
Brentwood Essex
Tel: Brentwood 219435

Shoot me
your catalogue

I enclose PO/Cheque for 10p.
Name
Address
PW1



The other pocket calculators neatly into your briefcase.

The Sinclair Executive is the world's smallest and lightest electronic calculator.

How light? Just 2½ oz. Less than the bunch of keys you're probably carrying now.

And how small? It's 5½ inches long, 2¼ inches wide, and an incredible ⅜ inch thick – same as a cigarette.

Yet this featherlight wafer of British technology offers more than some desk-top models.

With its brilliant 8-digit display it adds and subtracts, of course. It multiplies and divides – and by a constant figure over and over again, if you want it to (to work out discounts for example, for currency conversions, or for percentages). It works to 2, 4 or 6 decimal places – or it allows the decimal point to float. It rounds off automatically to the nearest decimal place.

The Secret of the Sinclair Executive
The Executive's 'brain' is an electronic marvel – a 7,000-transistor integrated circuit (the largest ever produced for commercial use).

But the real genius lies in the circuitry linking the brain, the batteries, the keyboard and the display. Circuitry soaks up power, which is why other pocket calculators have to use large batteries – and that, in turn, makes them bulky.

In the Executive, the Sinclair flair for miniaturisation has developed circuitry which absorbs virtually no power. Tiny hearing-aid batteries take up the minimum space, allow an elegantly slim case, and

give a full three-months average life. Yet small though it is, the Executive is far from frail. Every one is covered by an unbeatable five-year guarantee.

Smallest... lightest... and quite exceptionally powerful!
The easiest way to test the Executive's full performance is to try it for yourself.

You'll find the Executive at

**HENRY'S
RADIO LTD.**

354 Edgware Road,
London, W.2.
Tel: 01-402 5854

**ELECTRONIC AND
AUDIO SPECIALISTS
FOR 30 YEARS.**

**Highly recommended
calculator by us
for all trades and
professions.**



HENRY'S RADIO LTD. AUDIO-ELECTRONICS SPECIALISTS

303, 309, 354, 356, 404 and 406 EDGWARE ROAD, LONDON, W.2.
Open 9 a.m. - 6 p.m. 6 days a week.

FROM STOCK
£79
POST PAID

**10 DAY MONEY
BACK GUARANTEE**
Also full back-up
service facilities
and guarantee.

LINEAR

AMPLIFIERS FOR GUITAR PICK-UPS GRAM PICK-UPS RADIO or TAPE

OVERLOAD PROTECTION INCORPORATED. SOLID STATE CIRCUITRY

Suitable for application of Loudspeakers impedances between 3 and 30 ohms. Combinations not to measure less than 6 ohms across both speaker output jacks simultaneously.

The Amplifier cover is made of rigid plastic, bonded metal on the top and two sides. Finished in Black to suitably contrast with anodised metal control panel. Size approx. 14" x 4 1/8" x 9 1/2".



Rec. Retail
Price

£39-75

GENERAL PURPOSE AMPLIFIER

Model 40/60 40 - 50 Watts Output Power

Four individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

Compact size, robust construction. Ideal for clubs, hotels, restaurants, schools etc.

Inputs for almost any type of microphone

GENERAL PURPOSE GROUP/DISCO AMPLIFIER Model T40/60D

40 - 50 Watts Output Power

Three individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

Compact size. Robust construction. Ideal for discotheques, clubs, hotels, schools, etc. Inputs for most types of microphones. Facilities for headphone monitoring with changeover switch from input (1) to input (2).

Rec. Retail Price
£49-50



Wholesale and Retail enquiries to the Manufacturers Send S.A.E. for leaflet/s All Linear Amplifiers Guaranteed for 12 Months

LINEAR PRODUCTS LTD., Electron Works, Armley, Leeds. LS12 3SA Tel. 630126

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88-108Mcs, with circuit diagram. £2.10p.

B.F.W. 10 Fet. New (unmarked) 5 for £1 00p.

SPECIAL OFFERS of Unmarked Tested Power Transistors.

2N3055 Silicon NPN 30p each 4 for £1.

2N3054 Silicon 20p each 3 for 50p.

Plastic 40 Watt NPN 25 Volt 20p each 3 for 50p.

P-C BOARDS (not computer panels).

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor £1.50 the three.

Encapsulated bridge rectifier (ilt usd 3 3mdh) 100 PIV 2 amps. 50p each.

Transistor F.M. Stereo Multiplex Decoder. Size: 5 1/2" x 2 1/2" x 1 1/2". As used in well known British stereo units with circuit. £3.75.

GARRARD SP25 MK. II less Cartridge. £10.50.

10 VOLUME CONTROLS consisting of 2 off each.

100K log. ganged L/S—20K log. ganged L/S

470K log. D/P Switch—10K lin. L/S—50K lin. L/S. £1.25.

4 PHONO SOCKETS ON PANEL. 10 panels for £1.25.

12 PLASTIC KNOBS. Chrome and Gold, 3 types—4 off each—spring clip £1.25.

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. £1.00.

All items post paid in
GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

PADGETT'S RADIO STORE

OLD TOWN HALL, LIVERSEDGE,

YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

SPEAKERS EX TV SETS. Sound tested 7" x 4", 6" x 4", 8" x 2 1/2", all 30hm pm 25p each. Post on any speaker 10p.

Valve Voltmeter. Type CT34. Ohms Range 1K To 10 Meg in 5 Ranges. Volts Range 2.5 To 450 V AC DC. Untested Clean Condition. Less Batteries. £5. Carriage & Ins. £1.

T.V. Chassis. Plenty of spares on them. Free of Charge—Callers only. Up to one doz. per customer.

Latest Air Ministry Release Radio Receiver. Type R4187. 2.8 To 18 MHz in Three Bands. Complete with 17 Miniature Valves. 26 Volt Motor. Power supply Motor and Manually Tuned. Very Clean. But not tested. £5. Carriage and Ins. 75p.

Control Unit. Type 4190. Complete with three miniature valves. 1 1/2" 500uA meter. Six relays, model makers motor with gears, 24 press buttons. Lots of spares. Clean condition. £1.50. Carriage and ins. 75p.

Every one loves a bargain. And these T.V. sets we offer are the best you will find at the price.

Complete untested T.V. sets with all valves back and knobs BBC1 and ITV. 17" 90° tube £2. 17" 110° tube £3. 19" slim £5. Carriage and ins. £1.50.

We are now breaking up many Silmline Sets. Send S.A.E. and please quote model and serial number and part you require.

For example tested L.O.P.T. £1.45. Fireball Tuners with Valves 75p. Droppers all types 50p.

Breaking up Ferguson Type 506T. Tested L.O.P.T. £1.45. Post paid. Fireball Tuner Unit with Valves less knobs 75p post paid. S.A.E. for other spares for this set.

Reclaimed T.V. Tubes. All with 12 months guarantee.

AW43/88. £1.50. AW43/80 £1.50. MW43/69 £1. Special Offer. Brand New Brimar Tubes C17PM £1. Many older types in stock. Carriage and ins. on any tube £1.50.


Valve list ex equipment. All valves tested on a Mullard valve tester before despatched. 3 months guarantee on all valves. Single valves P/P 3p. Over post paid.

ARP12	5p	PCC84	5p	U191	20p
EB91	4p	PCF80	5p	U251	12p
EF80	8p	PCL82	12p	6BW7	10p
EF85	12p	PCL83	12p	6U4	10p
EBF80	12p	PCL84	12p	20P1	20p
EBF89	12p	PL36	20p	20P3	10p
ECC81	10p	PL81	17p	30D1	10p
ECC82	12p	PY81	8p	30P4	10p
ECC83	12p	PY33	17p	30F5	10p
ECL80	8p	PY82	8p	30P12	20p
EF91	4p	PL82	8p	30FL1	20p
EY86	20p	PL83	8p	6/30L2	20p
EP50	60p per doz.				

Bib

HI-FI ACCESSORIES

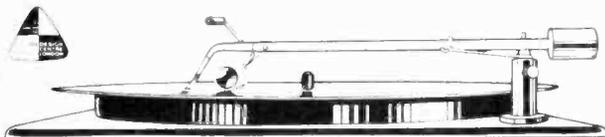RECOMMENDED BY LEADING EQUIPMENT MANUFACTURERS AND AUDIO SPECIALISTS




GROOV-KLEEN Modern automatic record cleaner.

- Removes and collects dust without using liquid
- Improves reproduction
- Reduces record & stylus wear
- Operates silently.
- Armrest incorporated
- Beautifully finished in Chrome, bright anodised Aluminium & shiny black


Model 42 £1.95

The popular priced Model 50 GROOV-KLEEN has all the features of the Model 42 but is made in high quality plastic. The base is finished in matt black and the cranked arm is white

NEW!

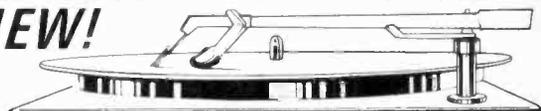

Model 50 £1.26

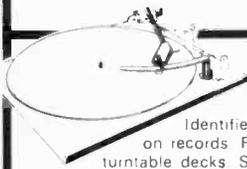

Record Cue & Swinger Detector

Identifies selected items on records. Fitted easily to all turntable decks. Scale moves clear of records, cannot touch pick-up cartridge. Detects swingers when rectified improves reproduction.

Patent No 2460/72


Ref 47 £1.45

HI-FI Stereo Hints and Tips



2nd Edition completely revised. How to make the most of your equipment by John Borwick BSc. Technical Editor of 'The Gramophone'. 48 Pages of useful information with 54 invaluable reference charts and illustrations for Hi-Fi enthusiasts.

Ref 56 32p

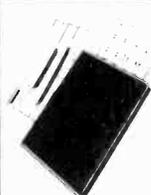

Indexa Record

Gramophone record filing and index system. Finds 1-100 instantly. Luxury padded index book, 100 pairs of numbered sleeve labels. Pad of coded printed pages.

Ref A £1.58½

Stylus Balance




Precision built. Calibrated. Measures stylus pressure within ¼ gramme. In plastic container.

Ref 32A £1.45

Stylus & Turntable Cleaning Kit

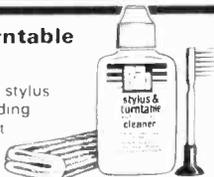Anti-static cleaner, stylus brush on free-standing base and absorbent cleaning cloth.



Ref B 34p

Tape Editing Kits— in Wallets

Tape splicer, cutter, marker, splicing tape. Reel or cassette labels. Instructions. For ½" tape.

Ref 23 £1.36

For cassettes

Ref 24 £1.50



12in Record Sleeve Protectors

Keep record sleeves like new in longlasting clear plastic.



Ref 44 44p per 5 pack



Recording Tape Splicer


Fitted with clamps for holding tape for diagonal or butt splices. On non-slip base, complete with tape cutter and instructions.

Model 20 99p

Cassette Tape Recorder Care Kit

To clean tape heads safely and easily, and for joining and editing tapes precisely. Packed in plastic box.

Ref 26A £2.10

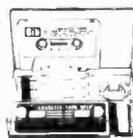

Cassette Head Cleaning Tape

For all cassette machines. Removes oxide and dirt from heads. Packed in plastic "library" case.

Ref 31 56p



Packed in attractive bubble pack, without "library" case.

Ref 31a 47p

Cassette Case

High quality black padded PVC, case with carrying handle for home and car. Holds 12.

Ref 34 £1.34



8 Track Cartridge Case

Identical in style to cassette case. Holds eight.

Ref 35 £1.59

Record Dust Off

Ideal for removing dust from records quickly and easily.

Ref 48 20p



Spirit Level


Essential to assure correct tracking and to minimise stylus & record wear.

Ref 46 56p

Spirit Level

Essential to assure correct tracking and to minimise stylus & record wear.

Ref 46 56p

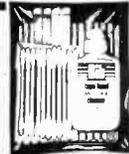

Compact Tape Head Cleaning Kit

Non-Flam cleaner, 4-Head Tools, 10 sticks and cloth in wallet. Recommended by Ferrograph, Revox and Tandberg.

Ref J 49p

8 Track Cartridge Tape Head Cleaner

Maintains tape heads in clean condition. Recommended use after every 5 hours playing. Complete with dust cover.

Ref 41 96p



Hi-Fi Cable & Flex Tidy

Shortens without cutting inter-unit cables, speaker leads, mains flex. Made of unbreakable plastic. Pack of five.

Ref D/2 16p

Cassette Salvage Kit

Contains razor cutter, two tape winders and a spare casing, enables a welded cassette to be opened for repair.

Ref 29 44p



Other Lines Include

- Splicing Tape Ref 33 23p
- Hi-Fi Solder Pack Ref 37 15p
- Anti-Static Hi-Fi Cleaner Ref P 24p
- Tape Reel Labels Ref T1 12p
- Cassette Title Labels Ref T4 18p
- Cassette Wallet Ref 39 58p
- Wire Strippers and Cutters Model 3A 32p, Model 6 50p, Model 8 58p
- Cassette Re-record Kit Ref 54 44p

Available from good audio shops, if unobtainable send direct plus 20p P & P for amounts up to £3. Over £3 postage free UK only.

Bib Sales, Dept PW PO Box No. 78, Hemel Hempstead, Herts. Tel: Hemel Hempstead 3636

LOW VOLTAGE D.C. POWER UNITS

I/P 115v 50c/s these provide a smoothed DC O/P of 0 to 26v at 3 amps., this can be adjusted from front panel by means of a small Variac; uses Silicon Rect and Choke I/P filter, fitted overload swt; compact size 7 x 7 x 13". Supplied in good condition with plug connections. Ex USAF surplus. Price £6-00 plus £1-00 carr.

WAVEMETER & OSC UNIT

Combined W.M. & Osc unit, covers range 150 to 230 Mc/s with cal charts; supplied with spares, instructions etc., for use on 115v 50c/s. New condition. See September Practical Wireless or write for further details.

Price £15-00 plus £1-50 carr.

CATHODE RAY TUBES

Type 7BP7A, 7" flat face tube, 7 Kv EHT, 6-3v heater. Are Emag Focus and Deflection; long persistence blue with yellow afterglow. Suitable slow scan T.V. Flying Spot Scanners, T.V. to scope conversion etc. Supplied new, boxed, with connections. Price £1-25 plus 30p post

LARGE TRANSISTOR PANELS

Plug in frame unit with a number of printed circs fixed to it; these contain a number of 2N560 transistors; these are a Silicon N.P.N. type Vc 60v Ic 100 Ma, Col disp 500 Mil/W cut off freq. 50 Mc/s; also contain close tol resistors, metal fittings, etc. Size of panel 13 x 12". Good condition. All parts can be removed. Ex USAF surplus. We supply two panels with not less than 40 2N560s.

Price £1-00 plus 37p post for two

MISCELLANEOUS ITEMS

JOY STICK CONTROL UNITS give control in N.S. & E.W. directions with 4 swts. £1-20. CROSS POINTER IND meter unit with two separate units in same case, approx. 115 Ua each, possible use in Stereo balance circs. £1-40. HEADPHONE MATCHING TRANS with 5ft cord and standard jack plug 4000 to 250 ohm enables low imp phones to be used on high imp circs. New. 50p. TRIMMER CONDS 20pf air spaced ceramic base screwdriver adjustment. New. 10 for 50p or £4-00 per 100. TAG STRIPS solder type 24 way. New. 10 for 25p. CONTROL UNIT with valves 6BA6, 12AU7, 6AS6, pot core 1½ x ¾, 1uf 1% cond., 24v relay, V/H & scrs. New. Boxed. 95p. DYNAMOTOR UNITS two types, both 12v DC I/P fully enclosed American surplus type A 220v DC O/P at 100 Ma £1-25, Type B 440v DC O/P at 200 Ma £1-75. Both spares for TCS. DIODES 800 P.I.V. at 1 amp, new 12 for £1-00. TRANSISTORS type OC42 long lead on boards with parts, 12 for 50p. RELAYS 12v 180 ohm coil contacts 4 pole c/o MBB 50p. RADIAC SURVEY METERS portable unit as 3, ranges 3, 30 & 300 Rongt per Hr with carrying case, battery operated gen on batteries supplied. New cond. £3-00. MORSE KEYS fully enclosed key on base with send receive swt, adjustable with circ or morse osc £1-10. BATTERIES lead acid type 6v 40 A/Hr in metal case with filling inst. New £2-75. SPEAKER UNITS P.A. type by Truvox in a sloping front case, size 9" x 9" x 8", 8 ohm spk with 600 ohm line trans. Good cond. £2-75. INVERTORS 28v DC I/P, 115v 400 c/s 180 watts O/P all transistor single phase. New by Cossor £12-50. SILICON DIODES type ZR22 rated 200 P.I.V. at 8 amps. 4 for 60p. R1155B Rx 5 bands S.W.3 to 18.5 Mc/s, supplied tested and alignment checked with circ. £18-00.

CIRCUIT DIAGRAMS

R1155, B, F, L, N with values 50p. R1392, R1475 30p. B40 50p. CT38 50p. W.M. Class D No. 2 30p. Scopes CD518 (CT316) 50p. 13A 50p. 1035 Mks 1, 2 and 3 all 50p ea. 1049 Mk 3 50p. Sig Gens TF144G 50p. TF801A 75p. American types ARR-2 30p. APN-9 30p. OS-8 50p. Dumont 208 750. STC R4187 Rx with values £1.

Above prices include post or carr. All above goods ex equip. unless stated otherwise. Carriage charges apply to U.K. mainland only. S.A.E. with enquiries.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL

HANDY MEN SWEAR BY IT

IT'S WHAT THE
TRADE USES

Swarfega



cleans hands

Manufactured by

deb CHEMICAL PROPRIETARIES LIMITED,
BELPER, DERBY, DE5 1JX

BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts
Bass Resonance 45 c.p.s.
Flux Density 12,000 gauss
Voice Coil impedance 3 or 8 or 15 ohm models
Response 45-13,000 c.p.s.

£7

POST
FREE

GUITAR MODEL "GROUP 25"
Heavy duty 25 watt rating £7
20 plans, cubic tables, crossover data and
Catalogue 42p post free. Catalogue only 5p.

Baker Reproducers Ltd.

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-484-1445



MINIATURE POWER DRILLS

Capable of Drilling Mild Steel

IDEAL FOR PRINTED CIRCUITS
PRECISION DRILLING,
CUTTING, GRINDING

12 volt D.C.;



PRICES FROM £3-00

EXPO DRILLS LTD.,
DEPT. PW1, 62 NEAL STREET, LONDON, W.C.2

TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London, W.C.1.

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 80p (FREE with parts).

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)

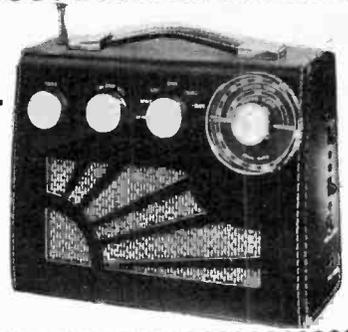

ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


ROAMER SEVEN MK IV

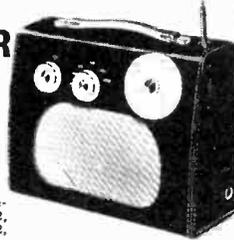

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

Total building costs **£5-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


ROAMER SIX

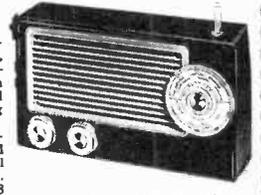

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P. P. & Ins. 30p. (Overseas P. & P. £1)

POCKET FIVE

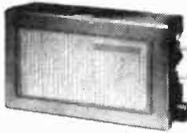

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5½ x 1½ x 3½in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-29** P. P. & Ins. 21p. (Overseas P. & P. 63p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 22p. (Overseas P. & P. 63p)


TRANS EIGHT

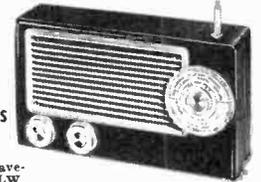

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

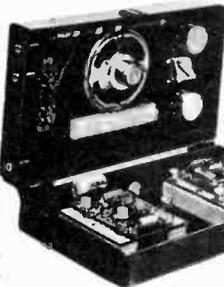Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 3 inch Speaker: Terminal Strip: Ferrite Rod Aerials: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: Diodes: Resistors: Capacitors: Three ½ Knobs.
Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)

FULL AFTER SALES SERVICE

• Callers side entrance Barratts Shoe Shop
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61 HIGH STREET BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for

Name

Address

PW46

COMET HI-FI discount warehouses



NEW LOW PRICES

STEREO AMPLIFIERS

	Rec. Retail Price	Comet Price
ALBA UA 700	37-93	24-95
ALPHA 212 by Highgate	37-75	26-95
AMSTRAD Stereo 8000 Mk 2	27-95	14-50
AMSTRAD I.C. 2000	42-95	27-95
ARMSTRONG 521	59-00	44-95
DULCI 207M	29-00	20-50
FERROGRAPH F307 Mk. II (cased)	64-00	44-95
GOODMANS Maxopt	54-00	34-95
H.L. Audio Phoenix 707	29-00	15-95
JVC Nivico MCA 104Z	85-00	70-95
MCA 105E	130-50	110-95
MCA V5E Quadraphonic	89-00	74-95
MCA V9 Quadraphonic	148-00	124-95
LEAK Delta 30 (cased)	69-50	48-95
LEAK Delta 70 (cased)	85-00	57-95
METROSOUND ST20E	39-50	25-50
METROSOUND ST60	70-00	46-25
PHILIPS RH581	70-00	54-95
PHILIPS RH580	52-00	36-50
PHILIPS RH580	29-00	20-50
PIONEER SA500A	45-50	32-95
PIONEER SA600	89-60	57-50
PIONEER SA800	119-85	75-95
PIONEER SA1000	133-83	86-95
PIONEER SA1000	147-83	93-75
PIONEER QL600 Quadraphonic converter	76-60	48-50
QD 210 Quadraphonic decoder	42-85	29-95
QA 800 Quadraphonic	179-05	113-68
QC 800 Quadraphonic pre-amp.	123-50	71-95
QM 800 Quadraphonic pow. amp.	152-88	93-95
Reverberation 202W	51-05	33-95
RANK Rotel 210	34-90	23-95
RANK Rotel 310	47-50	31-95
RANK Rotel 610	74-50	48-95
ROGERS Ravensbrook	64-50	45-50
ROGERS Ravensbourne (cased)	69-50	48-50
ROGERS Ravensbrook Mk. II	50-50	35-95
ROGERS Ravensbrook (cased) Mk. II	55-50	39-95
SINCLAIR 2000	35-00	22-95
Project 60/2 x Z30/PZ5.	23-90	15-95
Project 60/2 x Z50/PZ3/trans.	34-86	21-95
Project 605	29-95	18-90
AFU	5-98	4-50
Neoteric.	61-95	42-93
3000	45-00	29-50
TELETON SAQ 206B.	33-00	20-50
307	33-00	20-50
GA202 15 watt RMS Par. Chn.	42-75	28-95
WHARFEDALE Linton Amplifier	65-00	39-95
All take both ceramic and magnetic cartridges.		

	Rec. Retail Price	Comet Price
AMSTRAD Multiplex 3000 FM	36-50	27-95
*ARMSTRONG 523 AM/FM	52-88	39-95
*ARMSTRONG 524 FM	40-87	31-95
*ARMSTRONG M8 Decoder	9-50	8-95
*DULCI FMT.7 FM	24-43	17-50
DULCI FMT.7S Stereo	32-89	24-50
GOODMANS Stereomax	75-74	46-95
JVC Nivico		
MCT V5E AM/FM Quadraphonic	86-89	69-95
MCT V7E AM/FM Quadraphonic	122-42	98-95
LEAK Delta FM	79-50	53-95
LEAK Delta AM/FM	89-50	65-95
PHILIPS RH 690	44-15	31-95
PIONEER TX500 AM/FM	70-93	49-95
PIONEER TX600 AM/FM	100-37	68-95
RANK Rotel 320	53-38	38-95
RANK ROTEL 620	86-33	63-95
ROGERS Ravensbourne chassis	57-95	43-95
ROGERS Ravensbourne Intek case	62-63	47-95
ROGERS Ravensbrook Par. Chn.	42-75	28-95
ROGERS Ravensbrook (cased)	48-00	35-95
SINCLAIR 2000	45-00	31-95
SINCLAIR 3000	45-00	31-95
SINCLAIR Project 60 tuner (stereo)	25-00	17-50
TELETON GT202	46-75	30-95
All above Tuners are complete with MPX Stereo Decoder except where starred.		

TUNER/AMPLIFIERS

	Rec. Retail Price	Comet Price
AKAI CR80T FM/AM Tuner Amplifier with built in Eight Track Tape Recorder	149-84	89-95
AKAI A.A. 8500	228-34	175-00
AKAI 6500	145-26	109-00
AKAI 6300	129-75	97-95
AKAI 6200	97-09	74-95
ARENA 2600	111-30	65-95
ARMSTRONG M8 Decoder	9-50	6-95
ARMSTRONG 525	90-14	69-95
ARMSTRONG 526	102-72	77-95
CARLTON M4000 AM/FM with 8 track player and speakers.	69-95	39-95
GOODMANS Module 80, 35w RMS	89-02	67-95
GOODMANS Module 80 Compact	160-38	122-95
GOODMANS Module 110 FM/MW/LW/SW 100w RMS	131-22	100-95
JVC Nivico VR 901 M/FM	96-96	81-95
VR 5521 AM/FM and SEA	165-00	139-95
4VR 5414 Quadraphonic	212-00	179-95
LEAK Delta 75	175-00	124-95
MIDLAND 19/542	49-56	36-75
PHILIPS RH 790	134-00	74-95
PIONEER SX525	135-80	94-95
SX626	181-59	126-95

TUNER/AMPLIFIERS—continued

	Rec. Retail Price	Comet Price
SX727	224-61	157-95
SX828	281-52	197-95
ROGERS Ravensbrook Chassis	96-57	73-95
ROGERS Ravensbrook (cased)	105-35	79-95
ROTEL RX200	89-02	64-95
ROTEL RX150	67-93	49-95
TANDBERG 1171 MPX	103-03	84-95
TANDBERG TR200 MPX	86-23	79-95
TANDBERG TR1000 FM MPX(teak)	149-56	124-95
TELETON F2000	51-50	27-25
TELETON CR55	125-26	68-50
TELETON R8000 AM/FM	42-16	21-95
All the above take magnetic cartridges except		
Teleton F2000 and R8000 which take ceramic only.		
All include MPX Stereo Decoder with the exception of		
Armstrong where M8 decoder is extra.		

TURNTABLES

	Rec. Retail Price	Comet Price
GARRARD SP25 Mk III	16-17	10-25
GARRARD SL65B	20-93	13-95
GARRARD SL95B	44-21	32-95
GARRARD 401	39-04	27-95
GARRARD SL72B	32-60	21-95
GARRARD Zero 100A	57-42	40-95
GARRARD Zero 100S	52-83	38-50
GARRARD WB4 base Mk III to fit Zero 100 & Zero 100S	6-55	4-95

The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.

GARRARD SP25 Mk III with Goldring G.800	Special Price £18-50
MCDONALD MP60 with Goldring G800	Special Price £18-50
MCDONALD MP60 with SHURE M 44/7	Special Price £19-50
MCDONALD MP60 with SHURE M 44/E	Special Price £20-25
GARRARD AP76 with Goldring G800	Special Price £28-25
GARRARD AP76 with Shure M55E	Special Price £30-95
GARRARD AP76 with Shure M75EJ	Special Price £33-50
GARRARD 2025 with Sonotone 9T4HC	Special Price £12-95
GOLDRING 705/P with G850	£26-00 £10-95
GOLDRING GL75 with G800	Special Price £36-75
THORENS 150 AB with TX11 cover	Special Price £47-95
Shure M55E cartridge	£60-46 £47-95

Base and Cover to fit GARRARD

SP25, SL5, SL65B	Spec. Price 3-80
GARRARD 40B	1-63 10-95
GARRARD AP76	28-44 17-95
GOLDRING GL69 MKII	26-86 18-50
GL69P Mk. II	35-23 25-25
GL75	39-06 26-95
GL75P	47-43 33-50
Cover for 69P and 72P	4-36 3-70
Cover for 75P Deluxe	4-18 3-95
C99—plinth and cover for G99.	10-75 8-95
GOLDRING G99	27-90 19-25
GOLDRING G101P/C	27-90 19-95
GOLDRING GL72 Chassis	27-90 19-95
GOLDRING GL72P	36-27 25-95
GOLDRING GL85	61-03 42-95
GOLDRING GL85P	70-80 49-95
LEAK Delta	69-50 49-95
JVC Nivico SRP 473 Quadraphonic, including plinth and cover	69-50 58-95
MCDONALD MP60	14-80 9-95
610	18-79 12-95
HT70	20-68 14-50
HT70 inc. plinth and cover.	29-89 20-95

Base and Cover for MP60 and 610

PHILIPS 202 Electronic	Spec. Price 3-95
PHILIPS 308 transcription unit complete with base and cover	64-65 49-50
PHILIPS GA 105 with base, cover and cartridge	36-55 28-50
PIONEER PL12A cover with base & cover	20-00 13-95
THORENS T295 cover	47-15 32-95
THORENS TD125	8-26 6-60
THORENS TD125 Mk. II	76-73 58-95
THORENS TD125A B	61-03 42-95
THORENS TD125A B Mk. II with TP 18 arm	115-69 89-95
THORENS TD150 Mk. II	115-69 93-95
THORENS TD150A Mk. II	33-64 26-95
THORENS TD150A B Mk. II	43-09 32-95
THORENS TX11 Cover	46-63 36-95
WHARFEDALE Linton with base and cover and Shure M44-7 cartridge	4-13 3-50
37-50 25-95	

SPEAKERS

AKAI SW155	59-50	39-95
AMSTRAD 138 (pair) 13" x 8" twin cone teak	26-00	14-95
B & W DM2	159-50	111-95
B & W DM2	60-76	47-95
B & W DM3	63-00	45-50

SPEAKERS—continued

	Rec. Retail Price	Comet Price
B & W DM1 (pair)	75-20	57-25
CELESTION County	23-97	18-50
CELESTION Ditton 120 (pair)	56-40	39-95
CELESTION Ditton 15	37-40	27-95
CELESTION Ditton 25	32-07	24-75
CELESTION Ditton 44	54-00	38-95
CELESTION Ditton 66	99-00	70-95
FERROGRAPH S1 inc. stand	95-00	69-95
GOODMANS Havant (pair)	54-42	39-95
GOODMANS Magister (pair)	50-62	35-95
GOODMANS Double Maxim	65-63	44-95
GOODMANS Mezzo 3	35-70	23-95
GOODMANS Magnum K2	46-20	28-95
GOODMANS Dimension 8	72-44	48-95
GOODMANS DIN 20NT Kit	12-19	8-95
KELETRON KN400 2-speaker System (pair)	15-86	11-95
KN600 3-speaker System (pair)	26-46	17-50
KN800 3-speaker System	15-90	9-95
KN1100 4-speaker System	20-40	12-95
KN1600 3-speaker System	25-20	15-95
KN2100 3-speaker System	30-60	19-95
LEAK 150 (pair)	50-00	34-95
LEAK 250 (pair)	63-00	45-95
LEAK 600	49-50	32-45
LINEAR 10 watt teak (pair)	Sp. Price	13-85
METROSOUND HFS 103 (pair)	29-21	21-50
METROSOUND 202	25-50	14-75
METROSOUND Duplex 15	56-00	37-95
METROSOUND Duplex 25	56-00	37-95
PHILIPS RH 402 (pair)	44-70	33-95
PHILIPS 406	34-00	25-95
PIONEER CS53	44-25	28-95
SINCLAIR Q16	8-88	6-75
STE-MA 450	25-00	16-95
TANDBERG TAN 7	27-22	22-95
TANDBERG Tan 11 (pair)	36-94	31-20
TANDBERG Tan 12 teak (pair)	48-82	41-40
TANDBERG Tan 25 teak (pair)	66-08	55-95
TANDBERG Tan 50 teak	65-00	49-95
TELETON 8000 (pair)	21-18	17-95
THORPE Grenville TG 100 (pair)	28-95	17-95
Grenville TG 200 (pair)	41-95	25-95
Grenville TG 300 (pair)	55-95	31-95

WHARFEDALE

Linton Mark II (pair)	42-00	27-95
Melton Mark II	52-88	33-95
Melton Mark II	35-00	23-95
Dovedale 3 Mark II	47-50	30-50
Rosedale	65-00	44-25
Trilton III (pair)	65-00	44-95
Unit 1 Speaker Kit	12-50	8-75
Unit 4 Speaker Kit	19-00	12-25
Unit 5 Speaker Kit	27-50	17-60

CHASSIS SPEAKERS

GOODMANS Twin-Axiom 8	8-65	6-95
Twin Axiom 10	9-58	7-50
Axiom 401	17-68	11-95
Axiom 8P	5-20	4-15
Axiom 10P	4-50	4-50
Axiom 12P	13-00	9-25
Axiom 15P	21-00	14-95
Axiom 18P	35-70	24-95
Axiom 200 400 watts DIN	12-00	8-95
Axiom 100	4-50	3-20
Centon G800 Super E	6-90	4-90
Midex 1650	13-59	9-50
Attenuator	3-73	2-70
Crossover Network XO/950	7-77	5-45
WHARFEDALE 8in. Bronze/RS/DD	4-75	3-40
Super 10RS/DD	8-50	6-25
Super 10RS/DD.	14-00	9-95
WMT1 Matching Transformer	0-84	0-70

CARTRIDGES

AMSTRAD 900C	4-95	3-50
AMSTRAD 900D	7-50	5-50
AMSTRAD 900 EX	11-00	8-75
AUDIO TECHNICA AT66	6-47	3-60
GOLDRING G850	6-10	2-95
GOLDRING G800	12-21	4-50
GOLDRING G800E	17-67	7-50
GOLDRING G800 Super E	24-41	15-95
*GOLDRING CS90 Stereo	4-38	3-95
*GOLDRING CS91/E.	7-33	5-50
EMPIRE 1000ZE/X	59-12	44-95
EMPIRE 999VE/X	42-14	32-50
EMPIRE 998TE/X	24-58	19-25
EMPIRE 990SE/X	19-90	15-25
EMPIRE 998E/X	15-57	11-50
EMPIRE 909E/X	12-12	8-25
EMPIRE 908E/X	9-37	7-15
ORBIT Magnetic NM 22	Sp Price	2-75
ORTOFON M15E	27-60	22-75
SHURE M31E	6-10	3-75
SHURE M32E	11-63	6-95
SHURE M32-3	10-73	6-50
SHURE M44-G	9-84	7-65
SHURE M44-7	6-50	4-95
SHURE M44-C	7-90	4-90
SHURE M44E	7-90	4-90
SHURE M45E	6-60	4-95
SHURE M75G	9-70	5-95
SHURE M75G	14-70	8-45

OVER 1000 ITEMS ALWAYS IN STOCK

All items brand new and fully Guaranteed and backed by after-sales service

— latest models in manufacturers' sealed cartons



COMET for after-Sales Service THROUGHOUT THE U.K.

Pictured, Service Dept. at Clough Rd., Mill, also at Birmingham, Bridlington, Concaster, Edinburgh, Gosle, Leeds, Leicester, Rochdale, Sheffield, Stockton, Wakefield and York.

	Rec. Retail Price	Comet Price
CARTRIDGES—continued		
SHURE M75-5	13.60	7.90
SHURE M75EJ	15.40	9.25
SHURE M75E	19.00	11.50
SHURE M75 ED	19.00	11.50
SHURE M75/95G	20.80	12.95
SHURE V15-11	39.40	26.95
*SONOTONE BT/AHC Diam/Seaph	3.75	1.45

Starred cartridges above are ceramic. All others are magnetic.

	Rec. Retail Price	Comet Price
BASES AND COVERS		
GARRARD WBI Base	3.78	3.20
WB4 Base	5.60	4.70
SPC1 Cover	3.68	2.90
SPC4 Cover	4.38	3.50

Special offer of Base and Cover to fit SP25, SL55, SL65B and 3500 Special Price 3.90

	Rec. Retail Price	Comet Price
WB4 base Mk IIZ to fit Zero 100 and Zero 100S	6.55	4.95
GOLDRING Plinth 75	8.37	7.00
GOLDRING Plinth 69	8.37	7.00
GOLDRING Covers for 69P and 72P	4.36	3.70
Cover for 75P De Luxe	4.88	3.95
THORENS TX25 (for TD125AB)	8.26	6.90
THORENS TX11 Cover	4.13	3.50
Base and Cover for TD125	12.39	10.50

	Rec. Retail Price	Comet Price
SME Plinth System 2000 with motor-board	46.20	34.50
MOTORBOARDS only	5.85	4.45
SME Pl1 Spacer	0.98	0.75

	Rec. Retail Price	Comet Price
BLANK TAPES		
SCOTCH DYNARANGE CASSETTES		
C60	0.71	0.45
C90	0.99	0.55
C120	1.48	0.80

	Rec. Retail Price	Comet Price
SCOTCH HIGH ENERGY COBALT CASSETTES		
C60	1.45	0.95
C90	1.90	1.25

	Rec. Retail Price	Comet Price
SCOTCH Low Noise 8—TRACK BLANK CARTRIDGES		
40 mins	1.50	0.95
80 mins	1.80	1.10

	Rec. Retail Price	Comet Price
SCOTCH LONG LIFE SPOOLED TAPES		
8" L.P. 900	1.41	0.95
5 1/2" L.P. 1200	1.76	1.20
7" L.P. 1800	2.52	1.70

	Rec. Retail Price	Comet Price
SCOTCH DYNARANGE SPOOLED TAPES		
5 1/2" L.P. 1200	2.11	1.40
7" L.P. 1800	2.99	1.95

Package 1-tapes, cassettes and 8T cartridges 1-9 Items 5p per order. Packs of ten post free.

	Rec. Retail Price	Comet Price
HI-FI STEREO SYSTEMS COMPLETE		
ALBA UA552	47.75	29.95
BUSH A1005	69.89	53.25
DANSETTE Consort Stereo	34.43	24.95
DANSETTE 4005	71.45	53.25
DECCA Sound 613	Special Price	49.95
DECCA Sound 614	Special Price	52.95
DECCA Sound 1204	Special Price	76.95
DECCA Compact 2	Special Price	99.95
DECCA Compact 3	Special Price	99.95
DECCA 403	Special Price	44.95

	Rec. Retail Price	Comet Price
ELIZABETHAN LZ101	58.33	41.85
FERGUSON 3425	136.35	102.75
FERGUSON 3450 with Radio	101.70	79.95
FERGUSON 3451 with Radio	101.70	79.95
FIDELITY UA2 Music Master	43.50	30.95
UA1 Music Master with Radio.. Stereo Nine	100.00	69.95
	38.50	23.00

	Rec. Retail Price	Comet Price
GOODMANS Module 80 compact system FM/35 watts. RMS (Less L/S)	165.00	125.75
HMV 2451	122.00	95.95
HMV 2452	66.00	48.95
HMV 2450 with Stereo Radio	138.00	108.95
KB1025 with 657 speakers	48.25	37.95
KB 2250 with 658 speakers	124.00	95.95
KB 2010 with 658 speakers	101.50	77.95
MARCONI 4452	77.00	56.95

	Rec. Retail Price	Comet Price
HI-FI STEREO SYSTEMS—continued		
PHILIPS 825	49.50	38.95
PHILIPS 826	75.00	52.95
PHILIPS 835	69.50	49.55
PHILIPS 836	95.00	69.95
PYE Black Box unit stereo 1022	90.93	68.95
RIGONDA Parly Time	27.50	19.95
STEEPLETONE stereo system	41.75	25.95
TELETON STP 8-track stereo system	57.50	38.95
TELETON R 8000 Tuner/Amplifier with stereo decoder, Garrard 2025 TC turntable and one pair of Teleton 8000 speakers	87.95	47.80
ULTRA 8028	59.95	44.95
ULTRA 6450	74.20	54.95
ULTRA 6454	38.85	29.95
ULTRA 6455	41.35	31.95

Full range of headphones, Pick Up Arms & Heads available at discounted prices.

	Rec. Retail Price	Comet Price
TAPE RECORDERS AND TAPE DECKS		
AKAI 1720L 4-track Stereo	87.36	59.95
AKAI 4000D 4-track stereo deck	93.65	64.95
AKAI CR80D 8-track stereo tape deck	85.02	58.45
AKAI CR80 B-track stereo recorder	106.39	74.00
AKAI CR80T 8-track stereo recorder and tuner/amplifier	149.84	89.95
AKAI X200D	157.93	100.45
AKAI GX220D	223.00	164.95
AKAI 1800SD	162.79	102.30
AKAI 2000SD	289.07	223.30
FERGUSON 3247 4-track	47.95	34.95
FERGUSON 3248 4-track	53.75	39.95
FERGUSON 3252 4-track	98.00	74.95
FERGUSON 3258 4-track	70.45	51.95
FERROGRAPH 702/4 Dolby	264.38	224.50
FERROGRAPH 702H Dolby	274.95	233.50
FERROGRAPH 722/4 Dolby	301.98	255.95
FERROGRAPH 722H Dolby	312.85	264.95
FERROGRAPH 702-2-track tape deck	224.43	170.65
FERROGRAPH 704/W 4-track deck	224.43	170.65
FERROGRAPH 722	262.03	190.13
FERROGRAPH 724	262.03	190.13
FIDELITY BRAEMAR 4-track	34.75	19.95
GRUNDIG TK 121 twin track	56.25	38.95
GRUNDIG TK 141 4-track	62.10	44.95
GRUNDIG TK 146 4-track Auto	66.95	48.95
GRUNDIG TK 147 4-track Auto	98.65	74.95
GRUNDIG TK 148 (4-track auto 2 speed)	74.10	56.95
PHILIPS 4303 Twin-track	39.46	24.95
4307 4-track	48.65	34.95
4308 De Luxe 4-track	56.85	41.45
4404 4-track stereo recorder	89.25	65.95

	Rec. Retail Price	Comet Price
TAPE RECORDERS—continued		
4407 4-track stereo recorder	166.50	139.95
4418 4-track stereo	189.75	139.95
4450 4-track stereo	272.50	199.95
4500 4-track stereo tape deck	124.30	91.65
TANBERG 2000 (Stereo)	125.61	103.95
TANBERG 1841 4-track stereo tape deck	66.09	48.75
TANBERG 3021X twin track stereo	104.00	80.95
TANBERG 3041X 4-track stereo	104.00	80.95
TANBERG 4021X twin track stereo	169.12	135.50
TANBERG 4041X 4-track stereo	169.12	135.50
TANBERG 6041X 4-track stereo	182.73	145.25
TANBERG 6021X twin track stereo	182.73	145.25

	Rec. Retail Price	Comet Price
TAPE RECORDERS (CASSETTES)		
AKAI CS 350 recorder	125.83	92.95
AKAI CS 50D Deck	104.46	77.95
AKAI GXC 40D Tape Deck	92.26	68.25
AKAI GXC 40D Recorder	111.75	83.95
APCO Batt./Mains with AM/FM Radio	35.00	22.95
BUSH Discassette DC70	20.62	15.95
BUSH TP60	27.62	15.95
BUSH TP 66 Batt./Mains	28.18	21.50
BUSH TP 70 battery/mains	28.18	19.95
CARLINE LCR500	Sp. Price	11.95
DANSETTE DCT105	20.62	14.95
DECCA 2000 (batt./mains)	Sp. Price	22.95
DECCA CR1000 Cassette Recorder with VHF Radio	Sp. Price	32.95
EKCO 350 Bt./Mns. VHF/MW Radio	37.52	28.75
EKCO 351 Battery/Mains	23.23	18.45
FERGUSON 3240 with case	24.90	15.95
FERGUSON 3253	43.55	31.95
FERGUSON 3262 Battery/Mains	30.15	22.95
GRUNDIG C200 De Luxe	37.95	26.95
GRUNDIG C210 batt./mains	48.75	36.95
GRUNDIG C410	41.55	29.95
HARVARD Elite with AM/FM radio batt./mains	42.00	23.95
JVC NIVICO 9420 L/S with AM/FM radio batt./mains	61.45	42.95
PHILIPS R.R. 392 with MW/VHF Radio Cassette	49.95	36.55
2202	22.85	17.95
2204 battery/mains	29.10	23.95
3302	20.35	15.95
2400 stereo less L/S	66.10	51.95
PYE 9109	20.37	14.95
PYE 9118 Stereo	66.10	49.95
PYE 9119	29.11	22.95
TELETON TRC 130 with VHF/AM radio battery/mains	42.50	28.00
TC110 battery/mains	27.50	18.50

COMPLETE HI-FI SYSTEMS Completely wired mounted and ready for use

H.L. Audio Phoenix 707 amp. McDonald MP60 turntable, complete with base, cover and Shure M44/7 cartridge. Fully wired plus 2 Thorpe Grenville 100 loudspeakers	213.37	134.15
ROTEL RA 210 amplifier with McDonald MP60, base cover and Goldring G800 magnetic cartridge. Plus two Linear 10 watts speakers (Teak)	88.91	56.40
AMSTRAD IC2000 integrated circuit amp. 20 watts per channel, with McDonald MP60 turntable, plinth, cover and Goldring G800 cartridge. Plus two Wharfedale Denton Mk. II speakers	114.96	74.40
PIONEER SA500A amp. with McDonald MP60 turntable, plinth, cover and Shure M44-E cartridge. Plus two Wharfedale Denton speakers	113.90	81.15
PHILIPS RH802 Stereo Tuner/Amplifier/Player. 2 x 15 watts. LW/MW1/MW2/SW/FM. MPX with GP400 magnetic cartridge. Speakers extra	155.00	118.95
ARMSTRONG 525 FM Tuner/Amplifier. 25 watts RMS per channel, teak case, with M8 MPX Decoder. Goldring GL75 turntable, plinth, cover and G800 cartridge, plus two Wharfedale Dovedale III speakers	247.91	174.65
ARENA 2600 Tuner/Amplifier. FM/MW/LW 49m. Band. Marine Band. 15 watts. RMS per channel. Five pre set F.M. Stations and manual tuning with Garrard AP76 plinth, cover and G800 cartridge. Plus two Goodmans Havant speakers	213.37	134.15
ROTEL RX150 Tuner/Amplifier, AM/FM. MPX with McDonald MP60 plinth, cover and G800 cartridge, plus two Wharfedale Denton Mk. II speakers	139.94	96.40
AKAI CR80T Tuner/Amplifier, AM/FM. MPX with 8-track Stereo Recorder/Player, with McDonald MP60, plinth, cover and G800 cartridge. Plus two Wharfedale Linton Mk. II speakers	231.85	144.40
TELETON CR55 Tuner/Amplifier. AM/FM MPX with Garrard AP76 Turntable, plinth, cover and Shure M75EJ magnetic cartridge. Plus two Wharfedale Dovedale 111 speakers	266.10	163.00
PIONEER SX525 Tuner/Amplifier, including MPX Decoder with Pioneer PL12AC turntable, including plinth, cover and Shure M55E cartridge. Plus two Pioneer CS53 speakers	281.15	191.75
LEAK Delta 75. AM/FM tuner/amplifier, with LEAK Delta transcription deck, complete with plinth, cover and cartridge. Plus two Leak 600 speakers	326.50	239.80

FREE Technical Advisory Service. If in doubt ask us! Price list on request

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) OR, IF SECURICOR DELIVERY REQUIRED ADD £1.75 ONLY. Make cheques, MONEY ORDERS payable to "COMET".

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

OPEN DAILY TO THE PUBLIC FROM:
 9am-8pm Monday
 9am-1pm Tuesday
 9am-8pm Wednesday
 9am-8pm Thursday
 9am-8pm Friday
 9am-5.30pm Saturday

- Dept. PW BIRMINGHAM: Heeley Road, Selly Oak B29 6EY. Tel.: 021-472 6181.
- Dept. PW BIRMINGHAM: Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley. B26 1BJ. Tel.: 021-706 0684.
- Dept. PW EDINBURGH: 1 Newhaven Road EH6 5QX. Tel.: 554 8501 (5 lines).
- Dept. PW HULL: Reservoir Road, Clough Road HU6 7QD. Tel.: 46441 (6 lines).
- Dept. PW LEEDS: 78 Armley Road LS12 2EF. Tel.: Leeds 40551 (16 lines).
- Dept. PW STOCKTON: Teasway, Portrack Lane, Teesside TS18 2RH. Tel.: 66132/65215.
- Dept. PW ROCHEDALE: Corner of Well 11th Lane and Queensway. Tel.: 50606.
- Dept. PW LEICESTER: Syston Street. Tel.: 0533 52236.
- Dept. PW SHEFFIELD: The Mill, 1 Loxley Rd., Mallin Bridge, S6 4TN. Tel.: 0742 3417216.

SECURICOR
 SPECIAL DELIVERY SERVICE

All in-stock items delivered by SECURICOR within 72 hours. (Add £1.75 only for Sector delivery)

ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHES YOUR NERVES! Don't underestimate the value of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost self-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones. Components, nuts, screws, wire, etc. no soldering. £2.75+25p p. & p. Parts available separately.



Only £2.75

FIND BURIED TREASURE! Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC. Extremely sensitive, will signal presence of certain objects buried several feet below ground. No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age onwards, with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY £2.95 + 25p p. & p. (Sectional handle as illustrated 95p extra). Parts available separately. Made up looks worth £15!

Eavesdrop on the exciting world of Aircraft Communications V.H.F. AIRCRAFT BAND ONLY £2.85

Listen in to AIR-LINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting conversations between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, BINGWAT, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even TVI portables). NO CONNECTIONS WHATSOEVER NEEDED. SEND ONLY £2.85 + 20p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

Amazing Radio Construction set 1. Becomes a radio expert for £2.45. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all included. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send £2.45 + 20p p. & p.

BUILD 5 RADIO AND ELECTRONIC PROJECTS

only £2.45



Build 5 radio and electronic projects. Includes: Amazing Radio Construction set 1, Home Radio Course, and a kit with 5 projects. Price £2.45 + 20p p. & p.

CONCORD ELECTRONICS LTD. (PW10) 8, Westbourne Grove, London, W.2.

ELECTRONIC ORGAN




ONLY £3.25

Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc. Fully transistorised. SELF CONTAINED LOUDSPEAKER. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED. No soldering necessary. Simple as ABC to make. Anyone over nine years can build it easily in one short evening following the fully illustrated step-by-step, simple instructions. ONLY £3.25 + 25p p. & p. for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4.95

FULLY TRANSISTORISED PRIMITIVE CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, serve a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! £4.95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2.75 extra if required.) EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

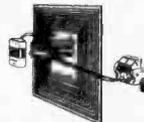

SHORTWAVE TRANSISTOR RADIO



only £2.75

Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2" Only £2.75 + 20p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

INGENIOUS ELECTRONIC SLEEP INDUCER


ONLY £3.25



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of tones, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. SEND £3.25 + 25p p. & p. (parts available separately).

Callers welcome

4-STATION INTERCOM

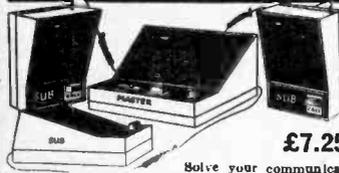

£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. £0.40.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.40 P. & P. £0.55

INTERCOM/BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. £0.25.

Transistor TELEPHONE AMPLIFIER



£2.99

Why not boost efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p. extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.8) 169 KENSINGTON HIGH STREET, LONDON, W.8.

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

250 MIXED CAPACITORS 62p
Plus 9p P. & P.

700C OPERATIONAL AMPLIFIER T05
8 lead I.C. 1 off 50p. 50 off 35p.
100 off 25p.

250 MIXED RESISTORS 62p
1 & 1/2 watt.

150 MIXED HI STABS 62p
1/2, 1 & 1 watt 5% & better.


QUARTZ HALOGEN BULBS
12V 55W for car spot lights, projectors, etc.
50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES
with dial but without bell. 85p each. P. & P. 30p.
£1.75 for 2. P. & P. 50p.

BARGAIN RELAY OFFER
Single pole change over silver contacts 25V to 50V. 2-8k Ω coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

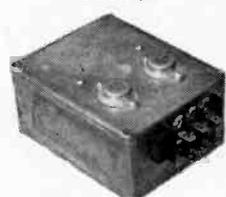PRACTICAL WIRELESS ELECTRONIC IGNITION SYSTEM



This Capacitor-discharge Electronic Ignition system was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the Standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the De-luxe version containing a ready-built, roller-trimmed printed circuit board and fully machined die-cast case with electrical connection block. Each kit is supplied with a custom wound transformer, first-grade components and full construction details. Suitable for 12V. systems only, pos. or neg. earth. All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, refundable on purchase of kit.
Price: Standard kit £7.25 post free
De-luxe £8.75 post free
Trade enquiries invited. Mail order only.
State pos. or neg. earth when ordering.

DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET, WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

Use Antex low-leakage soldering irons



220-240 Volts or 100-120 Volts

Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".

Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8".
2 other bits available 3/32" and 3/16".

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be re-ved

PRICE: £1.75 (rec. retail)
Suitable for production work and as a general purpose iron

Model CCN 220 volts or 240 volts

The 15 watt miniature model CCN, also has negligible leakage.

Test voltage 4000v. A.C.

Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available 1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

A SELECTION OF OTHER SOLDERING EQUIPMENT.



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 1/16" to 3/16". Voltages 240, 220, 110, 50 or 24
PRICE: £1.70 (rec. retail)

MODEL CN2


Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1.70 (rec. retail)



MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.
PRICE: £1.83 (rec. retail)

MODEL SK.1 KIT

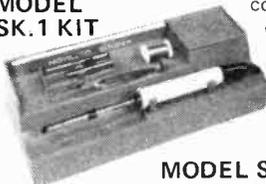

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75
(Rec. retail)

MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder and booklet "How to Solder"

PRICE £2.40
(Rec. retail)

MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder."
PRICE £1.95
(Rec. retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from: —
ANTEX LTD. FREEPOST
(no stamp required) **Plymouth**
PL1 1BR Tel: 0752 67377

- Please send the ANTEX colour catalogue.
 Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME _____

ADDRESS _____

PW/10

THE MIDLAND NATIONAL AMATEUR RADIO & ELECTRONICS EXHIBITION AT THE GRANBY HALLS LEICESTER OCTOBER 26th to 28th 1972

SPONSORED BY THE AMATEUR
RADIO RETAILERS ASSOCIATION

COME AND SEE THE LATEST
DEVELOPMENTS IN RADIO
COMMUNICATIONS AND
ELECTRONICS. WORLD-WIDE
CONTACTS FROM THE
EXHIBITION.

LARGE CAR PARKS
EASY ACCESS FROM M1
MOTORWAY.

ADMISSION 20p.
THIS INCLUDES A CHANCE TO
WIN A PIECE OF THE BEST IN
RADIO EQUIPMENT.

OPENING TIMES THUR.-FRI. 26th.-27th.
12 NOON to 9pm.

SATURDAY 28th. 10am. to 7pm.

OVERSEA VISITORS FROM PARIS-FRANKFURT
-AMSTERDAM & BRUSSELS. PLEASE CONTACT:
"MIDWAY LTD." 40A HILLSIDE, CASTLE
DONNINGTON, Nr. DERBY. FOR INFORMATION
REGARDING INCLUSIVE AIR CHARTER FLIGHTS
TO AND FROM THE SHOW.

DISCOUNTS UP TO

60%

**Global's GOLDEN
Guarantee**

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE
IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY
DEFECTIVE WE WILL REPLACE THE SAID GOODS
WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE
COVERED BY MANUFACTURERS 12 MONTHS
GUARANTEE

**SPECIAL
OFFER £17-95**

Garrard SP25 Mk. III
Goldring G800
Teak plinth and tinted cover. All
leads supplied.
Please add £1-25 for P & P.

TUNERTABLES

Please add 75p for P. & P.
Garrard SP25 Mk. III £10-25
Garrard AP76 £17-75
Garrard SL65B £12-65
Garrard 401 £26-50
Garrard Zero 100 (Auto) £38-75
Garrard Zero 100 (Single) £31-55
Garrard SL72B £23-50
Garrard SL75B £25-50
Garrard SL95B £34-25
BSR MP60 £9-45
Goldring GL72 £21-75
Goldring GL72/P £27-95
Goldring GL75 £25-75
Goldring GL75/P £34-25
Goldring 101/PC £20-00
Wharfedale Linton & cart. £27-95
Thorens TD125 £57-00
Thorens TD125AB £88-00
Thorens TD150 Mk. II £26-00
Thorens TD150A Mk. II £33-50

AMPLIFIERS

Please add 75p P. & P.
Amstrad 8000 Mk. II £16-25
Amstrad C2000 £27-45
Amstrad Integra 4000 £21-95
Armstrong 521 (teak cased) £43-95
Alpha Highgate 212 £24-95
Alpha Highgate FA300 £30-95
Alpha Highgate FA400 £31-95
Leak Delta 30 £48-75
Leak Delta 70 £57-95
Metrosound ST20E £24-45
Metrosound ST60 £45-95
Pioneer SA1000 £94-00
Rogers R/brook (Chassis) £35-00
Rogers R/brook (Cased) £37-00
Rogers R/bourne (Chassis) £41-55
Rogers R/bourne (Cased) £47-50
Sinclair PRO60 2 x Z30/PZ5 £14-95
Sinclair PRO60 2 x Z30/PZ6 £17-00
Sinclair PRO60 2 x
Z50/PZ8/Trans £21-50
Sinclair AFU (Filter Unit) £4-40
Sinclair 605 £18-50
Sinclair 2000 Mk. II £21-50
Sinclair 3000 Mk. II £29-50
Wharfedale Linton £37-50
Goodmans Max Amp £37-95
Teleton SAQ306 £22-50
Rotel RA 210 £24-50
Rotel RA 310 £31-00
Rotel RA 610 £48-50

TUNERS

Please add 75p P. & P.
Amstrad Multiplex 3000 £28-75
Armstrong 523 £39-50
Armstrong 524 £30-95
Rogers Ravensbrook FET4
(Chassis) £31-00
Rogers Ravensbrook FET4
(Cased) £35-00
Rogers Ravensbourne FET4
(Chassis) £43-00
Rogers Ravensbourne FET4
(Cased) £48-00
Sinclair PRO60 (Module) £16-50
Sinclair 2000/3000 Tuner £31-95
Leak Delta FM (Cased) £54-75
Leak Delta AM/FM (Cased) £48-50
Alpha Highgate FT 150 £34-95

TUNER/AMPLIFIERS

Please add 75p for P. & P.
Alpha Highgate 150 £44-25
Armstrong 525 (Teak cased) £67-95
Armstrong 526 AM/FM
(Teak cased) £77-75
Leak Delta 75 £124-75
Philips RH781 £50-00
Philips RH702 £82-50
Teleton 2100 £29-95
Goodmans One Ten £99-50
Rogers R/brook (Teak) £48-50
Rogers R/brook (Chassis) £72-75
Alpha FR 3000 £66-00

SPEAKERS

Please add £1-25 P. & P. per pair
Amstrad 138 £15-95
Wharfedale Denton 2 £30-25
Wharfedale Linton 2 £37-75
Wharfedale Melton 2 £48-45
Wharfedale Dovedale 3 £60-95
Celestion Dilton 120 £37-54
Celestion Dilton 15 £52-00
Celestion Dilton 25 £87-00
Goodmans Double Maxim £48-25
Goodmans Mezzo 3 £44-95
Goodmans Magister £74-00
Sinclair Q16 £12-50

£3-20



Plus 35p p. & p.
Finished in teak veneer with tinted
dust cover fully assembled. For
Garrard SP25; 2025TC; 3000;
AT60; 2000; 2500; 3500; 5100;
1025; SL65B; Also for BSR
McDonald MP60 and others.
For AP76; AP75; SL72B; SL75;
SL95B; £4-20 plus 55p P. & P.
Also finished in walnut to match
Japanese equipment—at no extra.

CARTRIDGES

Please add 10p for P. & P.
Goldring G850 £3-25
Goldring G800 £5-75
Goldring G800E £8-50
Goldring G800 Super E £14-35
Shure M3D £3-85
Shure M44E £5-65
Shure M55E £5-85
Shure M75E Type 2 £10-35
Sonotone 9TAHC £1-75



All prices correct
at time of press
E. & O.E.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept(PW14)174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue,
Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to

6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque,
Money Order, Bank Draft, Giro or Cash by Registered
Mail. **CALLERS:** Please note that cheques can only be accepted together
with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS
on main road leading to the East and West Country

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-20	AD162	0-33	BC148	0-10	BD137	0-45	BF188	0-40	OC19	0-35	2G371	0-16	2N2219	0-20	2N3054	0-46	2N4059	0-10		
AC113	0-20	AD161	0-33	BC149	0-12	BD138	0-50	BF194	0-12	OC20	0-83	2G371B	0-12	2N2220	0-22	2N3055	0-50	2N4060	0-12		
AC115	0-23	AD162 (MP)	0-33	BC150	0-18	BD139	0-55	BF195	0-12	OC22	0-38	2G373	0-17	2N2221	0-20	2N3091	0-14	2N4061	0-12		
AC117K	0-20		0-55	BC151	0-20	BD140	0-60	BF196	0-14	OC23	0-42	2G374	0-17	2N2222	0-20	2N3391A	0-16	2N4062	0-12		
AC122	0-12	AD1740	0-50	BC152	0-17	BD165	0-80	BF197	0-14	OC24	0-56	2G377	0-30	2N2368	0-17	2N3392	0-14	2N4284	0-17		
AC125	0-17	AF114	0-24	BC153	0-28	BD176	0-80	BF200	0-45	OC25	0-38	2G378	0-18	2N2369	0-14	2N3393	0-14	2N4285	0-17		
AC126	0-17	AF115	0-24	BC154	0-30	BD176	0-80	BF222	0-35	OC26	0-25	2G381	0-16	2N2369A	0-14	2N3394	0-14	2N4286	0-17		
AC127	0-17	AF116	0-24	BC157	0-18	BD177	0-85	BF257	0-45	OC28	0-50	2G382	0-16	2N2411	0-24	2N3395	0-17	2N4287	0-17		
AC128	0-17	AF117	0-24	BC158	0-12	BD178	0-85	BF258	0-60	OC29	0-50	2G401	0-30	2N2412	0-24	2N3402	0-21	2N4288	0-17		
AC132	0-14	AF118	0-35	BC159	0-12	BD179	0-70	BF259	0-85	OC35	0-42	2G414	0-30	2N2646	0-47	2N3403	0-21	2N4289	0-17		
AC134	0-14	AF124	0-30	BC160	0-45	BD180	0-70	BF262	0-55	OC36	0-50	2G417	0-25	2N2711	0-21	2N3404	0-28	2N4290	0-17		
AC137	0-14	AF125	0-25	BC161	0-50	BD185	0-65	BF263	0-55	OC41	0-20	2N388	0-35	2N2712	0-21	2N3405	0-42	2N4291	0-17		
AC141	0-14	AF128	0-28	BC167	0-12	BD186	0-65	BF270	0-35	OC42	0-24	2N388A	0-55	2N2714	0-21	2N3414	0-15	2N4292	0-17		
AC141K	0-17	AF127	0-28	BC168	0-12	BD187	0-70	BF271	0-30	OC44	0-15	2N404	0-20	2N2904	0-12	2N3415	0-15	2N4293	0-17		
AC142	0-14	AF139	0-30	BC169	0-12	BD188	0-70	BF272	0-80	OC45	0-12	2N404A	0-28	2N2904A	0-21	2N3416	0-28	2N5172	0-12		
AC142K	0-17	AF178	0-50	BC170	0-12	BD189	0-75	BF273	0-35	OC70	0-10	2N524	0-42	2N2905	0-21	2N3417	0-28	2N5457	0-32		
AC151	0-15	AF179	0-50	BC171	0-14	BD190	0-75	BF274	0-35	OC71	0-10	2N527	0-49	2N2905A	0-21	2N3525	0-75	2N5458	0-32		
AC154	0-20	AF180	0-50	BC172	0-14	BD195	0-85	BFW10	0-80	OC72	0-14	2N598	0-42	2N2906	0-15	2N3646	0-08	2N5459	0-40		
AC155	0-20	AF181	0-45	BC173	0-14	BD196	0-85	BFX29	0-27	OC74	0-14	2N599	0-45	2N2906A	0-18	2N3702	0-10	2N5460	0-42		
AC156	0-20	AF186	0-45	BC174	0-14	BD197	0-90	BFX84	0-22	OC75	0-15	2N696	0-12	2N2907	0-20	2N3703	0-10	2N5461	0-42		
AC157	0-24	AF239	0-37	BC175	0-22	BD198	0-90	BFX85	0-30	OC76	0-15	2N697	0-13	2N2907A	0-22	2N3704	0-11	2N5462	0-42		
AC165	0-20	AL102	0-65	BC177	0-19	BD199	0-95	BFX86	0-22	OC77	0-25	2N698	0-24	2N2925	0-14	2N3705	0-10	2N5463	0-55		
AC166	0-20	AL103	0-65	BC178	0-19	BD200	0-95	BFX87	0-24	OC81	0-15	2N699	0-35	2N2924	0-14	2N3706	0-09	2N5464	0-70		
AC167	0-20	ASX26	0-25	BC179	0-19	BD205	0-80	BFX88	0-22	OC81D	0-15	2N706	0-08	2N2925	0-14	2N3707	0-11	2N5465	0-84		
AC168	0-24	ASX27	0-30	BC180A	0-24	BD206	0-80	BFY50	0-20	OC82	0-15	2N706A	0-08	2N2926 (G)	0-12	2N3708	0-07	2N5466	0-84		
AC169	0-14	ASX28	0-25	BC181	0-24	BD207	0-85	BFY51	0-20	OC82D	0-15	2N706	0-12	2N2926 (H)	0-12	2N3709	0-09	2N5467	0-84		
AC176	0-20	ASX29	0-25	BC182	0-10	BD208	0-95	BFY52	0-20	OC83	0-20	2N711	0-30	2N2926 (Y)	0-11	2N3710	0-09	2N5468	0-84		
AC177	0-24	ASX50	0-25	BC182L	0-10	BDY20	1-00	BFY53	0-17	OC84	0-20	2N717	0-35	0-20	2N717	0-35	0-11	2N3711	0-09	2N5469	0-84
AC178	0-28	ASX51	0-25	BC183	0-10	BF115	0-24	BPX25	0-85	OC139	0-20	2N718	0-24	2N2926 (O)	0-10	2N3819	0-28	2N5470	0-84		
AC179	0-28	ASX52	0-25	BC183L	0-10	BF117	0-45	BX19	0-15	OC140	0-20	2N718A	0-50	0-20	2N718A	0-50	0-10	2N3820	0-28	2N5471	0-84
AC180	0-17	ASX54	0-25	BC184	0-12	BF118	0-70	BX20	0-15	OC169	0-25	2N726	0-28	2N2926 (B)	0-10	2N3821	0-35	2N5472	0-84		
AC180K	0-20	ASX56	0-25	BC184L	0-12	BF119	0-70	BY25	0-15	OC170	0-25	2N727	0-28	2N2926 (R)	0-10	2N3823	0-28	2N5473	0-84		
AC181	0-17	ASX76	0-25	BC185	0-28	BF121	0-45	BSX26	0-15	OC171	0-25	2N743	0-20	0-20	2N743	0-20	0-10	2N3904	0-30	2N5474	0-84
AC181K	0-20	ASX77	0-25	BC186	0-28	BF123	0-50	BSX27	0-15	OC200	0-25	2N744	0-20	0-20	2N744	0-20	0-10	2N3905	0-30	2N5475	0-84
AC187	0-22	ASX58	0-25	BC207	0-11	BF125	0-45	BSX28	0-15	OC201	0-28	2N914	0-14	2N3010	0-70	2N3906	0-28	2N5476	0-84		
AC187K	0-20	ASZ21	0-40	BC208	0-11	BF127	0-50	BSX29	0-15	OC202	0-28	2N918	0-10	2N3011	0-14	2N3906	0-27	40361	0-40		
AC188	0-22	BC107	0-09	BC209	0-12	BF152	0-55	BSX38	0-18	OC203	0-25	2N929	0-21	2N3053	0-17	2N4068	0-12	40362	0-40		
AC188K	0-20	BC108	0-09	BC212L	0-11	BF163	0-45	BSX39	0-18	OC204	0-25	2N930	0-21	0-21	2N930	0-21	0-10	2N4069	0-40	40363	0-40
ACY17	0-25	BC109	0-10	BC213L	0-11	BF164	0-45	BSX40	0-18	OC205	0-25	2N706	0-12	0-12	2N706	0-12	0-10	2N4070	0-40	40364	0-40
ACY18	0-20	BC113	0-10	BC214L	0-14	BF165	0-70	BSX41	0-28	OC809	0-40	2N1132	0-22	0-22	2N1132	0-22	0-20	2N4071	0-40	40365	0-40
ACY19	0-20	BC114	0-15	BC225	0-25	BF166	0-48	BSX42	0-12	P346A	0-20	2N1302	0-14	0-14	2N1302	0-14	0-10	2N4072	0-40	40366	0-40
ACY20	0-20	BC115	0-15	BC226	0-35	BF167	0-55	BSX43A	0-12	P397	0-42	2N1303	0-14	AA119	0-08	BY133	0-21	OA10	0-35	40367	0-40
ACY21	0-20	BC116	0-15	BCY30	0-24	BF168	0-56	Bu105	2-00	OCPT1	0-43	2N1304	0-17	AA120	0-08	BY164	0-50	OA47	0-07	40368	0-40
ACY22	0-18	BC117	0-15	BCY31	0-26	BF169	0-60	C11E	0-50	OPF12	0-43	2N1305	0-17	AA125	0-08	BYX38/30	0-40	OA79	0-07	40369	0-40
ACY27	0-18	BC118	0-10	BCY32	0-30	BF169	0-40	C400	0-30	OPF60	0-43	2N1306	0-21	AA130	0-08	BYZ11	0-35	OA81	0-07	40370	0-40
ACY28	0-19	BC119	0-30	BCY33	0-22	BF162	0-40	C407	0-25	ORP61	0-40	2N1307	0-21	AAZ13	0-10	BYZ10	0-35	OA82	0-07	40371	0-40
ACY29	0-35	BC120	0-80	BCY34	0-25	BF163	0-40	C424	0-20	ST140	0-12	2N1308	0-23	BA100	0-10	BYZ11	0-30	OA85	0-09	40372	0-40
ACY30	0-28	BC125	0-12	BCY70	0-14	BF164	0-40	C425	0-50	ST141	0-17	2N1309	0-23	BA116	0-21	BYZ12	0-30	OA90	0-08	40373	0-40
ACY31	0-28	BC126	0-18	BCY71	0-18	BF165	0-40	C426	0-35	T1843	0-30	2N1613	0-20	BA126	0-22	BYZ13	0-25	OA91	0-08	40374	0-40
ACY34	0-21	BC132	0-12	BCY72	0-14	BF167	0-22	C428	0-20	UT46	0-27	2N1711	0-20	BA148	0-14	BYZ16	0-40	OA95	0-07	40375	0-40
ACY35	0-21	BC134	0-18	BCZ10	0-20	BF173	0-22	C441	0-30	VC61	0-20	2N1880	0-32	BA153	0-12	BYZ17	0-35	OA290	0-06	40376	0-40
ACY36	0-22	BC135	0-12	BCZ11	0-25	BF176	0-35	C452	0-30	2G302	0-19	2N1890	0-45	BA155	0-14	BYZ18	0-35	OA292	0-07	40377	0-40
ACY40	0-17	BC136	0-15	BCZ12	0-25	BF177	0-35	C444	0-35	2G303	0-19	2N1893	0-37	BA156	0-13	BYZ19	0-28	SD10	0-05	40378	0-40
ACY41	0-18	BC137	0-15	BD121	0-60	BF178	0-30	C455	0-22	2G304	0-24	2N2147	0-72	BY100	0-15	CG62	0-05	SD19	0-05	40379	0-40
ACY44	0-35	BC139	0-40	BD123	0-65	BF179	0-30	MAT100	0-19	2G306	0-40	2N2148	0-57	BY101	0-12	(Eq) OA91	0-05	IN34	0-07	40380	0-40
AD130	0-38	BC140	0-30	BD124	0-60	BF180	0-30	MAT101	0-20	2G308	0-35	2N2160	0-60	BY105	0-17	CG651	0-05	IN34A	0-07	40381	0-40
AD140	0-48	BC141	0-30	BD131	0-50	BF181	0-30	MAT120	0-19	2G309	0-35	2N2192	0-35	BY114	0-12	CG651	0-05	IN34B	0-08	40382	0-40
AD142	0-48	BC142	0-30	BD132	0-60	BF182	0-40	MAT121	0-20	2G339	0-20	2N2193	0-35	BY126	0-14	(Eq) OA70	0-05	IN34C	0-08	40383	0-40
AD143	0-38	BC143	0-30	BD133	0-65	BF183	0-40	MPI102	0-42	2G339A	0-16	2N2194	0-35	BY127	0-15	OA79	0-06	IN41JB	0-08	40384	0-40
AD149	0-50	BC145	0-45	BD135	0-40	BF184	0-25	MPI104	0-37	2G344	0-18	2N2217	0-22	BY128	0-15	OA5	0-35	IN921	0-10	40385	0-40
AD181	0-33	BC147	0-10	BD136	0-40	BF185	0-30	MPI105	0-37	2G345	0-16	2N2218	0-20	BY130	0-16	OA5SL	0-21	IN95			

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV1A	3A	5A	5A	7A	10A	16A	30A
T05	T06	T06	T06	T04	T04	T04	T04
50	23	0.25	0.35	0.35	0.47	0.50	0.53
100	0.25	0.35	0.47	0.47	0.50	0.53	1.40
200	0.35	0.37	0.49	0.49	0.57	0.61	1.60
400	0.43	0.47	0.56	0.56	0.67	0.75	0.93
800	0.53	0.57	0.68	0.68	0.77	0.97	1.25
1000	0.63	0.70	0.80	0.80	0.90	1.20	1.50

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.05	0.05	0.07	0.14	0.21	0.60
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
800	0.07	0.16	0.10	0.25	0.34	0.45	1.86
1000	0.10	0.17	0.11	0.25	0.37	0.50	2.00
1200	0.11	0.25	0.14	0.30	0.46	0.63	2.50
				0.38	0.57	0.76	

TRIACS

VBO	2A	6A	10A
TO-1	TO-66	TO-88	
\$p	2p	\$p	
100	80	50	76
200	50	60	90
400	70	75	1-10

DIACS

FOR USE WITH TRIACS	
BR100 (D32)	37p each

FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 50p each pak

EN2960 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 25p each.

120 VCB MIXIE DRIVER TRANSISTOR. Sin. BSX21 & C407 2N1893 FULLY TESTED AND CODED ND. 120-1.24 17p each. TO.5 NPN. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 eqvt. ZTX300 5p each. Any Qty.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP TO-3 case. G.P. BRAND NEW TO-3 CASE. POSS. REPLACEMENT. — OC25-29-30-35-36. NKT 401-403-404-405-406-450-451-452-453. TI027-3028, 2N250A, 2N456A-457A-458A, 2N611 A & B, 2G220-222. ETC. VCB0 80V VCE0 50V IC 10A PT. 30 WATTS Hfe 36-170. PRICE 1-24 43p each 25-99 40p each 100 up 36p each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCB0 250V/VCE0 100V/IC 6A/50 Watts. HFE type 20T/5MHZ. OUR PRICE EACH: 1-24 100 up 45p 25-99 40p

AD161/162 PNP M/P COMP GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE

2-23V. 400mV (DO-7 Case) 13p ea. 11V (Top Hat) 25p ea. All fully tested 5% tol. and marked. State voltage required.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each

NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS.

50 v RMS 32p each
100 v RMS 37p ..
400 v RMS 46p ..
Size 15 mm x 6 mm.

UNIJUNCTION

UT46. Eqvt. 2N2846, 30vt. T1843. BEN3090 27p each, 20-99 25p 100UP 20p.

CADMIUM CELLS

ORP12 43p
ORP60, ORP61 40p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSF. 17/28/85A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906. BCY70. When ordering, please state preference NPN or PNP.

20	For	0-50
50	For	1-100
100	For	1-75
500	For	7-50
1000	For	13-100

SIL. G.P. DIODES 2p

300mV 30. 0-50
40PIV(Min.) 100. 1-50
Sub-Min. 500. 1-50
Full Tested 1,000. 9-00
Ideal for Organ Builders.

2N3055

115 WATT SIL. POWER NPN 50p EACH

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-50
U 2	60 Mixed Germanium Transistors AF/RF	0-50
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-50
U 4	40 Germanium Transistors like OC81, AC128	0-50
U 5	60 200mA Sub-Min. Silicon Diodes	0-50
U 6	30 Sil. Planar Trans. NPN like BBT96A, 2N706	0-50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000-50	0-50
U 8	50 Sil. Planar Diodes DO-7 like 250mA like OA200/202	0-50
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-50
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0-50
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-50
U 12	12 Silicon Rectifiers Epoxy 500ma up to 800 PIV	0-50
U 13	30 PNP-NPN Sil. Transistors OC900 & 2S 104	0-50
U 14	150 Mixed Silicon and Germanium Diodes	0-50
U 15	25 NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	0-50
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-50
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-50
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-50
U 19	25 Silicon NPN Transistors like BC105	0-50
U 20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-50
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-50
U 22	30 MADT's like MHz Series PNP Transistors	0-50
U 23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-50
U 24	25 300 MHz NPN Silicon Transistors 2N708, BBY27	0-50
U 25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-50
U 26	12 NPN Germanium AF Transistors TO-18 like AC127	0-50
U 27	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/26-600	0-50
U 28	15 Plastic Silicon Planar Trans. NPN 2N2926	0-50
U 29	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-50
U 30	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0-50
U 31	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-50
U 32	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0-50
U 33	25 Silicon Planar Transistors PNP TO-18 2N2906	0-50
U 34	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-50
U 35	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0-50
U 36	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-50
U 37	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0-50
U 38	10 Dual Transistors 6 lead TO-5 2N2060	0-50
U 39	25 RF Germanium Transistors TO-5, OC45, NKT72	0-50
U 40	10 VHF Germanium PNP Transistors TO-18 NKT667, AF117	0-50
U 41	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-50
U 42	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-50
U 43	7 3A SCR. TO66 up to 600PIV	1-00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP 225 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

F.E.T.'S
2N3819 35p 2N5458 50p
2N3820 50p 2N6459 40p
2N3821 35p BFW10 40p
2N3823 30p MFP105 40p

NEW EDITION 1971

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

SILICON 50 WATTS MATCHED NPN/PNP BIP 1NPN TO-3 Plastic. BIF 20 PNP. Brand new. VCB0 100V/VCE0 50V/IC 10A. HFE type 100T/3mHZ. OUR PRICE PER PAIR: 1-24 prs 60p 25-99 prs 55p 100 prs 50p

QUALITY TESTED SEMICONDUCTORS

Pak No.	Contents	Price
Q1	20 Red spot transistors PNP	0-50
Q2	16 White spot R.F. transistors PNP	0-50
Q3	4 OC 77 type transistors	0-50
Q4	6 Matched transistors OC44/45/81/81D	0-50
Q5	4 OC 75 transistors	0-50
Q6	5 OC 72 transistors	0-50
Q7	4 AC 128 transistors PNP high gain.	0-50
Q8	4 AC 126 transistors PNP	0-50
Q9	7 OC 81 type transistors	0-50
Q10	2 AC 71 type transistors	0-50
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-50
Q12	3 AF 116 type transistors	0-50
Q13	3 AF 117 type transistors	0-50
Q14	3 OC 171 H.F. type transistors	0-50
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-50
Q16	2 GBT880 low noise Germanium transistors	0-50
Q17	5 NPN 2 x ST.141 & 3 x ST.140	0-50
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-50
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-50
Q20	4 OC 44 Germanium transistors A.F.	0-50
Q21	4 AC 127 NPN Germanium transistors	0-50
Q22	20 NKT transistors A.F. R.F. coded	0-50
Q23	10 OA 209 Silicon diodes sub-min.	0-50
Q24	8 OA 81 diodes	0-50
Q25	15 IN914 Silicon diodes TS PIV 75mA	0-50
Q26	8 OA95 Germanium diodes sub-min IN69	0-50
Q27	2 10A PIV Silicon rectifiers IS425R	0-50
Q28	2 Silicon power rectifiers BYZ 13	0-50
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-50
Q30	7 Silicon switch transistors 2N706 NPN	0-50
Q31	6 Silicon switch transistors 2N708 NPN	0-50
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0-50
Q33	3 Silicon NPN transistors 2N1711	0-50
Q34	7 Silicon NPN transistors 2N2969, 500MHz (code P397)	0-50
Q35	3 Silicon PNP TO-5. 2 x 2N2904 & 1 x 2N2905	0-50
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0-50
Q37	3 2N3053 NPN Silicon transistors	0-50
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-50

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Resistance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and e Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and instructions. Price each: \$3-35

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	— 12 x 7400	0-50	UIC46	— 5 x 7446	0-50	UIC86	— 5 x 7486	0-50
UIC01	— 12 x 7401	0-50	UIC47	— 5 x 7447	0-50	UIC90	— 5 x 7490	0-50
UIC02	— 12 x 7402	0-50	UIC48	— 5 x 7448	0-50	UIC91	— 5 x 7491	0-50
UIC03	— 12 x 7403	0-50	UIC49	— 5 x 7449	0-50	UIC92	— 5 x 7492	0-50
UIC04	— 12 x 7404	0-50	UIC51	— 12 x 7451	0-50	UIC93	— 5 x 7493	0-50
UIC05	— 12 x 7405	0-50	UIC53	— 12 x 7453	0-50	UIC94	— 5 x 7494	0-50
UIC06	— 8 x 7406	0-50	UIC54	— 12 x 7454	0-50	UIC95	— 5 x 7495	0-50
UIC07	— 8 x 7407	0-50	UIC80	— 12 x 7460	0-50	UIC96	— 5 x 7496	0-50
UIC10	— 12 x 7410	0-50	UIC70	— 8 x 7470	0-50	UIC100	— 5 x 74100	0-50
UIC13	— 8 x 7413	0-50	UIC72	— 8 x 7472	0-50	UIC121	— 5 x 74121	0-50
UIC20	— 12 x 7420	0-50	UIC73	— 8 x 7473	0-50	UIC141	— 5 x 74141	0-50
UIC30	— 12 x 7430	0-50	UIC74	— 8 x 7474	0-50	UIC151	— 5 x 74151	0-50
UIC40	— 12 x 7440	0-50	UIC75	— 8 x 7475	0-50	UIC154	— 5 x 74154	0-50
UIC41	— 5 x 7441	0-50	UIC76	— 8 x 7476	0-50	UIC193	— 5 x 74193	0-50
UIC42	— 5 x 7442	0-50	UIC80	— 5 x 7480	0-50	UIC199	— 5 x 74199	0-50
UIC43	— 5 x 7443	0-50	UIC81	— 5 x 7481	0-50			
UIC44	— 5 x 7444	0-50	UIC82	— 5 x 7482	0-50			
UIC45	— 5 x 7445	0-50	UIC83	— 5 x 7483	0-50			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAK NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES— 18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593. OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.

All mail orders please add 10p post and packing. Send all orders to BI-PAK P.O. Box 6, WARE, HERTS. All mail orders please add 10p post and packing. Send all orders to BI-PAK P.O. BOX 6, WARE, HERTS.

- the lowest prices!

74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS



	1	25	100+		1	25	100+
SN7400	0-15	0-14	0-12	SN7472	0-29	0-28	0-24
SN7401	0-15	0-14	0-12	SN7473	0-37	0-35	0-32
SN7402	0-15	0-14	0-12	SN7474	0-37	0-35	0-32
SN7403	0-15	0-14	0-12	SN7475	0-45	0-43	0-42
SN7404	0-15	0-14	0-12	SN7476	0-40	0-39	0-38
SN7405	0-15	0-14	0-12	SN7480	0-87	0-84	0-88
SN7406	0-35	0-31	0-28	SN7481	£1-20	£1-15	£1-10
SN7407	0-35	0-31	0-28	SN7482	0-87	0-86	0-85
SN7408	0-18	0-17	0-16	SN7483	£1-10	£1-05	£0-95
SN7409	0-18	0-17	0-16	SN7484	£1-00	£0-95	£0-90
SN7410	0-15	0-14	0-12	SN7485	£3-60	£3-50	£3-40
SN7411	0-25	0-24	0-23	SN7486	0-32	0-31	0-30
SN7412	0-35	0-31	0-28	SN7489	£5-50	£5-25	£5-00
SN7413	0-29	0-28	0-24	SN7490	0-87	0-84	0-88
SN7416	0-43	0-40	0-38	SN7491	£1-00	£0-96	£0-90
SN7417	0-43	0-40	0-38	SN7492	0-67	0-64	0-68
SN7420	0-15	0-14	0-12	SN7493	0-67	0-64	0-68
SN7422	0-50	0-48	0-45	SN7494	0-77	0-74	0-68
SN7423	0-50	0-48	0-45	SN7495	0-77	0-74	0-68
SN7425	0-50	0-48	0-45	SN7496	0-87	0-84	0-78
SN7427	0-45	0-42	0-40	SN74100	£1-65	£1-60	£1-55
SN7428	0-70	0-65	0-60	SN74104	0-97	0-94	0-88
SN7430	0-15	0-14	0-12	SN74105	0-97	0-94	0-88
SN7432	0-45	0-42	0-40	SN74107	0-40	0-38	0-36
SN7433	0-80	0-75	0-70	SN74110	0-55	0-53	0-60
SN7437	0-64	0-62	0-60	SN74111	£1-25	£1-15	£1-10
SN7438	0-64	0-62	0-60	SN74118	£1-00	0-95	£0-90
SN7440	0-15	0-14	0-12	SN74119	£1-35	£1-25	£1-10
SN7441	0-87	0-84	0-58	SN74121	0-40	0-37	0-34
SN7442	0-87	0-84	0-58	SN74122	£1-40	£1-30	£1-10
SN7443	£1-30	£1-25	£1-20	SN74123	£2-80	£2-70	£2-60
SN7444	£1-80	£1-77	£1-75	SN74141	0-67	0-64	0-58
SN7445	0-97	0-94	0-88	SN74145	£1-50	£1-40	£1-30
SN7447	£1-00	0-97	0-95	SN74150	£2-00	£2-70	£2-50
SN7448	£1-00	0-97	0-95	SN74151	£1-00	0-95	0-90
SN7450	0-15	0-14	0-12	SN74153	£1-20	£1-10	0-95
SN7451	0-15	0-14	0-12	SN74154	£1-80	£1-70	£1-60
SN7453	0-15	0-14	0-12	SN74155	£1-40	£1-30	£1-20
SN7454	0-15	0-14	0-12	SN74156	£1-40	£1-30	£1-20
SN7460	0-15	0-14	0-12	SN74157	£1-90	£1-80	£1-70
SN7470	0-29	0-28	0-24				

LINEAR I.C.'s—FULL SPEC.

Type No.	Price		
	1-24	25-99	100 up
BP 201C—8L201C	83p	55p	45p
BP 701C—8L701C	63p	50p	45p
BP 702C—8L702C	63p	50p	45p
BP 702—72702	53p	45p	40p
BP 709—72709	36p	34p	30p
BP 709P—7A709C	36p	34p	30p
BP 711—72710	44p	42p	40p
BP 711—7A711	45p	43p	40p
BP 741—72741	75p	60p	50p
7A708C—7A703C	28p	26p	24p
TAA 263—	70p	60p	55p
TAA 293—	90p	75p	70p
TAA 350—	170p	158p	150p

S.G.S. BA1000 2-63

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	Price		
	1-24	25-99	100 up
BP930	12p	11p	10p
BP932	13p	12p	11p
BP933	13p	12p	11p
BP935	13p	12p	11p
BP936	13p	12p	11p
BP944	13p	12p	11p
BP945	25p	24p	22p
RP446	12p	11p	10p
BP948	25p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP963	40p	38p	35p
BP904	40p	38p	35p
BP907	40p	38p	35p
BP909	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR118	3015P Mintron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1-70	£1-55	£1-90

All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each		
	1-24	25-99	100 up
Epoxy TO-5 case			
uL800 Buffer	35p	33p	27p
uL814 Dual 21/p gate	35p	33p	27p
uL923 J-K flip-flop	50p	47p	45p

Date and Circuits Booklet for IC's Price 7p.

DUAL IN LINE SOCKETS.

14 & 16 Lead Sockets for use with

	Price each		
	1-24	25-99	100 up
DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-99 100 up			
TSO 14 pin type	30p	27p	25p
TSO 16 " " "	35p	32p	30p

LOW COST No.


BP8 14	15p	13p	11p
BP8 16	18p	14p	12p

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0-1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

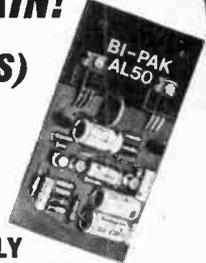

- ★ Frequency Response 15Hz to 100,000—1dB. **ONLY £3.25p each**
- ★ Load—3, 4, 8 or 16 ohms.
- ★ Distortion—better than -1% at 1KHz.
- ★ Signal to noise ratio 80dB.
- ★ Supply voltage 10-35 Volts.
- ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer MT80, the unit will provide outputs of up to 1-5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:- Discos Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2-95**

TRANSFORMER BMT80 £1-95 p. & p. 25p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz - 20KHz ± 1dB
Harmonic Distortion	better than 0-1%
Inputs : 1. Tape Head	1-25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1-5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than - 65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £11-95

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23-00 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS



Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

look! electronics really mastered

... practical
... visual
... exciting!

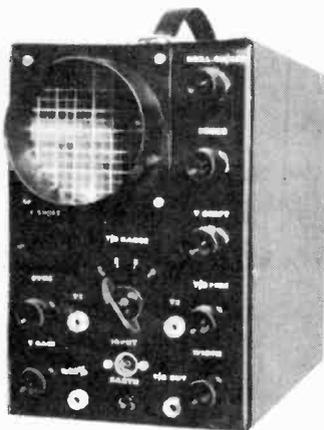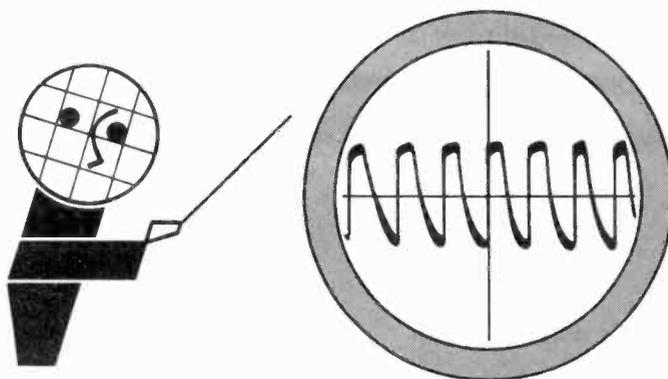no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

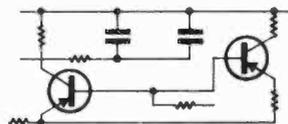2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL102

special free gift also to all our students

PRACTICAL WIRELESS

VOL 48 NO 6

Issue 788

OCTOBER 1972

Wires and Waves

ASKED what type of aerial he uses, an enthusiast of the new generation might well reply "What's an aerial?". Apart from those multi-rod devices on the roof associated with television, the aerial is usually just another component fitted snugly inside the case of a transistor radio.

DX enthusiasts and amateur transmitters are, of course, alive to the importance of the external aerial, but there must be thousands of would-be DX-ers battling against the odds by trying to find exotic stations on ordinary transistor radios and relying only on the pickup capabilities of the internal ferrite rod assembly or at best a diminutive pull-out rod. While some success is possible under these conditions, experienced listeners will testify as to the vastly improved results obtained by using a well-designed external system, perhaps terminated in an aerial tuning unit.

It is not, however, just a matter of throwing out a random piece of wire and hoping for the best. Some thought must be given to the wavebands on which peak performance is wanted and the directions from which optimum reception is needed. In fact, devising an aerial can be quite as absorbing as the building of active equipment.

The erection of an aerial system is more an art than a science, because the siting and lengths of wire are somewhat empirical. Formulae for dimensions and directions are based on the ideal conditions obtained in "free space" but the average amateur is rarely fortunate enough to have unrestricted space and a clear open site. The immediate terrain and features (hills, large buildings, etc.) may modify the ideal calculations and so there is a fruitful field here for experimentation.

Once embarked on the subject of aerials, it is a short step to begin thinking about what happens between the transmitter and the receiver. Here again is a complete field for exploration. One of the first things that an embryo DX-er has to learn is how the various phenomena associated with radio wave propagation are going to affect his listening activities. A good aerial system coupled with a knowledge of propagation are the foundations for successful long distance listening.

That there is a need for information on aerials is borne out by the many letters we have received asking for help in this direction. The wall chart enclosed with this issue should provide all the basic material for those wishing to install a good aerial system, or improve their existing set-up, and it is complementary to the DX Data Chart supplied with the March issue.

We have also included in this issue, an introductory article on radio wave propagation, which it is hoped will provide a further stimulus to investigation into this somewhat neglected, yet vital, sphere of interest.

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	487
News . . . News . . . News . . .	488
MW Column by <i>Charles Molloy</i>	498
Electronotes by <i>S. Ginsberg</i>	502
Letters	505
Practically Wireless by <i>Henry</i>	506
CQ! CQ! CQ!	510, 540
On the Short Waves by <i>Malcolm</i> <i>Connah and David Gibson, G3JDG</i>	527

CONSTRUCTIONAL

Audio Reference Source by <i>E. Buckland</i>	494
The "Logiprobe" by <i>Laurence Cook</i>	501
Take 20, No. 41, Frost Alarm by <i>Julian Anderson</i>	509
Pre-Tuned Car/Portable Radio by <i>R. H. Longden</i>	512
Transmitter for Two Metres, Part 2 by <i>F. G. Rayer, G3OGR</i>	516
Experimenters Corner, Intercomm Calling System and 25W a.c. to d.c. inverter	518

OTHER FEATURES

Principles of Propagation by <i>Henry Hatch</i>	490
Transistor Circuitry for Beginners, Part 11 by <i>H. W. Hellyer</i> and <i>Michael Hollier</i>	520
Going Back by <i>Colin Riches</i> and <i>Arthur Dow</i>	524
Gas Filled Valves, Part 2 by <i>I. R. Sinclair</i>	531
IC of the Month, Motorola MFC 6040 Electronic Attenuator by <i>L. A. J. Ireland</i>	540

FREE—AERIAL DATA WALLCHART

Some Readers may be aware of a slight loss of quality in printing. This is due to a shortage of our usual paper which has been brought about by the Dock Strike.


**THE NOVEMBER ISSUE WILL BE
PUBLISHED ON OCTOBER 6th**

©IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

Nip-E-Board

Remember some time ago we mentioned Nippiboard — the etched P.C. Board? Well now NIP Electronics, the manufacturers have announced additions to their range.

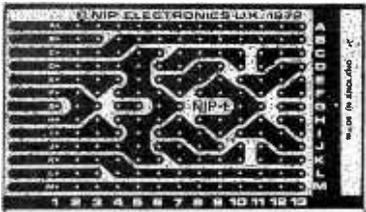The Nip-E-System provides for a number of basic etched printed circuit board arrangements that can be used in many circuit applications immediately. The user then goes ahead with the component layout assembly and wiring, knowing that he does not need to worry about special designs or messy etching procedures. The basic layout design




STANDARDISED PCB FOR TRANSISTORS


procedures and photographic image transference have been done for the constructor. All the user needs to do is apply the standardised pattern to his circuit and assemble the components. Connectors are available as part of the Nip-E-System for single row and double row pattern arrangements of discrete or integrated circuits or both.

With the boards you get a choice of ready-made paper base laminate or epoxy glass fibre board $\frac{1}{16}$ in. (1.58mm.), a hole matrix 0.1in. (2.54mm.) \times 0.15in. (3.81mm.) and a choice of drilled or undrilled boards. A choice of board for discrete components only or a mixture of integrated circuits and discrete components is available and there is a choice of board size to take up to about

PCB FOR I.C.

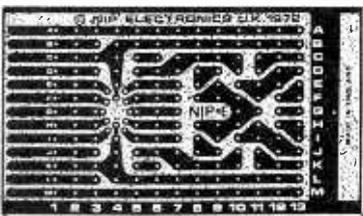


Gas igniter

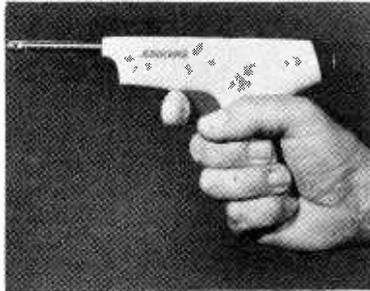

No, it's not a device for "doing-in" Editors—it's a piezo electric gas igniter! It's guaranteed for ten years, does not need any batteries or flints, you don't have to plug it in the mains or hold it under a hot tap! While you pause for breath, we'll explain:

The device, made in Germany by Junkers, operates on the principle that if a sudden force is applied to the interfaces of various crystals, an electric charge results. In practice, when the trigger on this igniter is pressed, it releases a "firing" pin which deforms the piezo crystal and causes a discharge voltage in the region of 20kV to appear at the end of the pistol "barrel". The end of the barrel is designed like a car

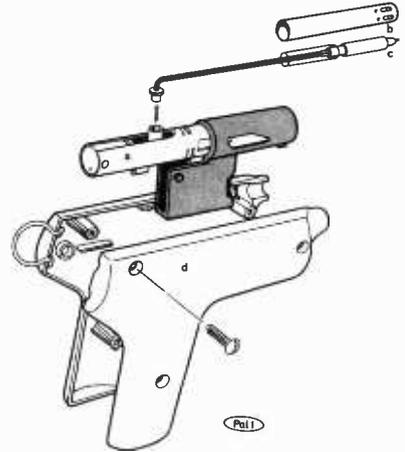

sparkling plug so that the spark (of 50 μ S duration) jumps from the centre electrode to the barrel wall thus igniting the gas it is held near.

In the sketch (a) is the crystal mounting and housing unit. (b) and (c) are the points the spark jumps from and (d) is the plastic housing of the complete unit.

The Junkers Piezo Electric Gas Igniter is priced at £2.25 plus 15p postage and packing and may be obtained from *Servitronix Limited*, 572 Kingston Road, Raynes Park, London, S.W.20.

26 transistors (possibly more) in the 11E to 18E series or up to eight integrated circuits plus 16 transistors in the 21E to 28E series.

Constructors can have plug-in contacts for 14-way or 30-way gold-plated edge connectors (as supplied) for single row or double row boards, contact pitch 0.1in. (2.54mm.).

The customer chooses the size most suitable to his application and the Company supplies a ready-made Nip-E-Board.

The boards are reasonably priced and they certainly help to make construction much easier and far neater.

If you would like further details of prices, accessories and layouts, drop a line to *NIP Electronics*, P.O. Box 11, St. Albans, Herts. They will be pleased to send readers their comprehensive free booklet on the Nip-E-System.

Anyone help?

Our squadron has recently started a radio section, and all projects are of a self help basis, thus you may understand that supplies and money are very limited. The boys' ages vary from 13 years to 16 years.

I would be most obliged if through your column, I might request any radio hams etc who have surplus to requirements any books, components or radio equipment, to contact us.

All expenses for postage and packing would be refunded, and all communications acknowledged.

Please address all letters, parcels, etc. to:—Mr. G. H. Barker, "Training Officer", 2380, A.T.C. Dartmouth Sqdrn., "The Lodge", Longcross Cemetery, Townstal Road, Dartmouth, South Devon.

BI-PRE-PAK LTD.

Due to a printer's error in our August issue an incorrect price was quoted for the Complete Telephone as offered for sale by the above Company. The correct price should have read 95p. We offer our apologies to BI-PRE-PAK LTD. and to any readers who may have been inconvenienced by this error.

Decoder

Motorola Semiconductors have announced the type MC1310 monolithic f.m. broadcast receiver stereo decoder which requires no external tuning inductors. Stereo channel separation is stated to be 40dB at 1kHz, with 0.3% total harmonic distortion.


Dymo Star 1710

We recently had the opportunity to try out the Dymo Star 1710 labelling machine. This machine is ideal for stamping out the wording for the front panels of equipment.

Letter selection is made by turning the dial wheel until the required character appears in the letter slot.

Technical symbol and character wheels may be fitted to this machine quite simply and different colour tapes are available.

Full instructions are provided with each Dymo Star.

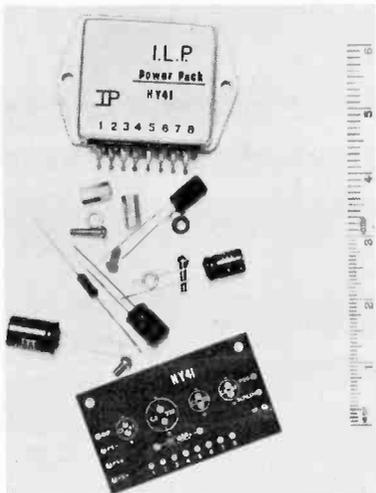**IC power amp**

The HY41 is a linear integrated circuit, power amplifier with an output of 20 Watts r.m.s. into 4-16Ω having a total harmonic distortion of less than 0.15% (typical 0.05%) at 1kHz into 8 ohms.

P.C. board, resistor, capacitors, hardware mountings and comprehensive manual are all included in the basic kit, no further components being required in constructing a complete power amplifier of high performance.

Internally the HY41 is based on proven circuit techniques developed over recent years and is sufficiently versatile to provide power not only for Hi-Fi but for public address systems and industry.

Supplied by the Canterbury Company I.L.P. (Electronics) Ltd., the HY41 requires no adjustment whatsoever and can be assembled without recourse to sophisticated measuring equipment or electronics know how. *I.L.P. (Electronics) Ltd., Crossland House, Nackington, Canterbury, Kent.*

Rover-point

Nettle Accessories Limited, a member of the Aerialite Group of Companies, announce the introduction of a portable extension lead to their range of electrical accessories, known as the "Rover-point".

It consists of a 15 metre length of white 0.65 sq. mm. 3 core, P.V.C. cable, contained in a moulded plastic reel. A flush 13A socket is incorporated into the reel, and the cable is supplied complete with 13A plug.

The reel has a handle that can be utilised for carrying or hanging, and its rotating section is provided with two projections to facilitate easy rewinding.

Suitable for feeding loads of up to 1kW, with the cable fully extended and 500W with the cable coiled on the reel, "Roverpoint" sells at a recommended retail price of £3.99. *Nettle Accessories Limited, Warren Street, Stockport, Cheshire.*

**Sonex 73**

Sonex 73, the high fidelity equipment exhibition organised by British Audio Promotions, will be held at the Excelsior Hotel, London, from March 30 to April 1.

Erie catalogue

Erie Electronics have published a new comprehensive catalogue of their electronic components. It covers all product ranges, and catalogue contains specifications on all Erie distributor sales, Erie Electronics and Erie Controls products, as well as information on Erie thick film devices and Toshiba semiconductors. Copies are available from Erie Electronics Ltd., South Denes, Great Yarmouth, Norfolk.

Chadacre Electronics

Please note their new address: 63 Stratford Broadway, London, E-15. Telephone 01-534 1207.

DESPITE the use of high-power transmitters, used in conjunction with aerial systems of considerable gain and directivity, as well as extremely sensitive receiver techniques to accomplish a high standard of world-wide h.f. communication, the final merit of reception is controlled by many natural causes and variations.

The Pioneers

The medium through which a radio wave must propagate, termed the *Ionosphere*, determines this final pattern of reception including field strength, fading and even "black outs." The early pioneers were well aware of the electro-magnetic wave with its effects though proof of its vast potential only came when Guglielmo Marconi established contact between Bournemouth and the Isle of Wight in 1898. This was followed by an even greater breakthrough in 1901 when he transmitted the first telegraph signal from Poldhu, Cornwall to be intercepted at St. Johns, Newfoundland.

Research in this field by many workers revealed great discoveries. The name of mathematician Oliver Heaviside in England, who propounded the existence of a *Conducting Layer* in the upper atmosphere in 1892, as well as the work carried out by Kennelly in the U.S.A. as early as 1902 can never escape mention. Sir E. V. Appleton and M. A. F. Barnett, who determined the position of the *Heaviside Layer* in

on the atmosphere will show considerable variations when we consider the changes from day to night, the four seasons of the year and the eleven year cycle of the sun's regular variation. This solar cycle appears to follow an average change of 11.4 years; from one of minimum activity to maximum in 4 years and falling from maximum to the next minimum in 7 years. (The last maximum occurred in 1968 and present predictions are estimating the next minimum will occur in 1975). Differences of this kind affect the conditions of the atmosphere and as a result have considerable influence on the propagation of radio waves. The solar radiations affect the atmosphere and cause it to assume a "mirror-like" reflecting surface which return radio waves to earth.

Ionization

The radiation from the sun unsettles and excites the normal arrangements of the atoms and molecules of gas. This brings about a condition known as *ionization*; the atoms of gas become incomplete, having lost some of their electrons.

The region of ionization will, therefore, consist partly of free electrons and this process will continue so long as the earth's rotation permits that region of the atmosphere to be exposed to the sun.

After sunset this process ceases and the free electrons rejoin their "mother" atoms, a process known as *recombination*, and this region will fall in ionized

PRINCIPLES OF propagation HENRY HATCH

1925, are also great names that we associate with early radio experiments.

The many effects acting in different ways on radio signals during their passage from transmitter to receiver is indeed a great scientific subject—yet perhaps to the majority of readers the fascination lies in the fact that, even by using only simple equipment, signals may be intercepted from the other side of the world.

Sun and Atmosphere

Let us consider how transmission of this kind is possible. A mode of propagation of this kind requires two essential and indispensable components, the atmosphere and the sun. The atmosphere, forming a gaseous envelope surrounding our planet, consists mainly of two gases, nitrogen and oxygen. This atmosphere is subjected to the full exposure and effect of the sun's rays, not only those of heat and visible light but of other radiations, including ultra-violet, gamma and X-rays, all bombarding our atmosphere after a journey of some 93 million miles. The effect of these rays falling on our atmosphere permits long distance radio communication.

The Solar Cycle

The difference in the amount of sunlight falling

density. The ionized region is called a *Layer* and is able to reflect the wave back to earth though it must be remembered that radio (like light waves) travel only in straight lines. To make use of this reflecting property the transmitted signal must be beamed in a skyward direction, as well as towards that part of the earth where it is to be heard. For long distance communication the radiated signal must leave the earth at a low angle so that the first encounter with the ionosphere will be as far away as possible. In the same way a signal with a high angle of elevation will reach the layer at a much closer distance and may be regarded as being more suitable for reception in a nearby area.


Bending

It should be mentioned at this stage that the rays of the sun will be first absorbed by the upper part of the atmosphere so that the overall density of the layer will show some variation. The radio signal coming up from the earth's surface will first enter an area of comparatively low density but as it enters deeper into the ionized region it will encounter an area of greater free electron density. The wave will meet an adverse force, presenting some opposition to its progress. It is convenient to think of the radio wave behaving in a similar way to light when considering how it is turned in the ionosphere to be

returned to earth (both travelling at a speed of 186,000 miles per second).

Hop and Skip

The word *Refraction* or *Deflection* explains this particular point in that a ray is changed in its course after entering a medium differing in density from one through which it has already passed. In this way the wave will be turned away from its original path and, providing the density of the medium and the frequency of the vibration are suitable, a point will be reached where the wave will be turned from its original route so as to follow a parallel course with the layer. Eventually it will be completely turned and leave the ionosphere at a similar angle as that of entry. The wave will return to earth having accomplished its first *Hop*—leaving a *Skip* distance between the sending and receiving points suggesting an area of silence existing between them. This is not so because the width of the transmitting beam will usually cover a considerable angle and the random scatter of the downcoming wave due to irregularities of the ionosphere tends to fill in this void. The second hop is made possible by an

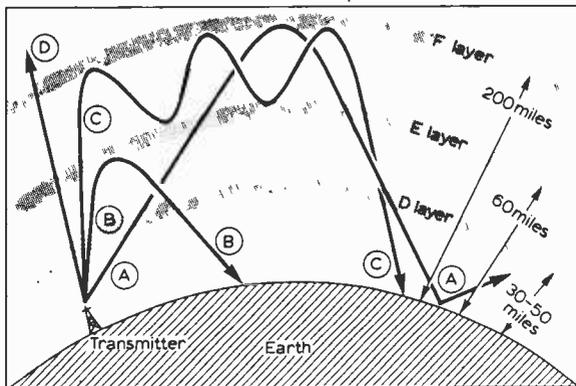

Representation of the various methods by which radio waves are propagated. The main layers (D, E and F) are shown with their approximate heights above the earth's surface; the F layer is shown simplified—see text. The wave A is the normal long hop transmission; further reflection may take place when it meets the earth's surface. For reception in nearby areas the signal is beamed at a higher angle and is reflected by the E Layer.

C shows a form of propagation that is thought to occur at times. A number of reflections take place between the upper layers before the signal is returned to earth. If the angle of radiation is too high (and the frequency unsuitable) the waves will be lost in space as shown by D.

upward reflection from the earth's surface but the effectiveness of this is somewhat variable. It will depend upon the texture of the particular area of the earth's surface. Sea water is excellent, next comes pastoral land, while at the lower end of the scale desert areas may be regarded as poor; all have different conduction values. There is no rigid limit as to how many hops may take place since these are governed by the height of the layer at the time of transmission, the radiation pattern given by the aerial and the distance to be covered as well as the original transmitted power.

Some idea of a professional mode of transmission may help to make this point clear; the path from the United Kingdom to India needs three such hops and that to Australia six or seven. It will now be clear that although the wave will follow only a straight

line, the curvature of the earth has been overcome by each individual hop although so far the ionosphere has been considered as one reflecting region. This is not so and it does in fact consist of several parts, each playing a different role and each one having a profound effect upon the wave.

D Layer

The basic structure of the ionosphere starts with that area known as the *D layer*, situated between 30 and 50 miles above the earth; this becomes very dense by day but falls to a very low level—almost non-existent—at night. During the hours of daylight it will cause considerable attenuation of the signal due to absorption, particularly to the lower frequencies. This effect is well known to the medium wave DXer as long distance reception on this band is virtually confined to the 'locals' until after sunset when the D Layer will begin to fail.

E Layer

The *E Layer* (sometimes known as the *Kennelly-Heaviside Layer*) lies about 60 miles above the earth and although not the most important part of the ionosphere, it is responsible for the reflection of both medium and short waves.

A particular development of the E region, which at times can produce really sensational forms of propagation, is that known as *Sporadic E*. As the term implies this condition is irregular and cannot be forecast with any accuracy. An increase in ionization takes place usually around noon in our latitude. These abnormal conditions permit the reflection of very high frequencies and even enable TV signals to be observed from distant stations.

F Layer

The topmost layer is that known as the *Appleton* or *F Layer*. The height varies from about 200 miles upwards and ionization is mainly confined to nitrogen as at this height oxygen becomes rare. The F Layer is frequently considered as the most important. It becomes divided into two parts during daylight, the upper part designated as *F₂* and the lower portion *F₁*. After sunset, and prior to dawn, it assumes the form of only one layer.

Frequency Choice

Having examined the structural and reflecting arrangements which affect the wave, let us now consider how these various parts are put to practical use. Most of us are aware of the general rule that high frequencies are most useful by day and the lower ones give the best performance by night, although the exact choice of frequency used is critical if reception is to be of a standard worthy of being termed a service. Indeed, numerous observations are needed to formulate the vast number of short wave schedules published in advance which have to take into account the many factors already mentioned.

Ionosphere Sounding

Such information is compiled by "sounding" the ionosphere. A radio wave with an adjustable frequency is sent vertically upwards to a layer so that it is able to engage it at right-angles and then the

Radio Propagation Characteristics

Frequency	Day	Night
A. 100kHz-400kHz	Reception very dependent on power of station. Reliable reception possible at distances of 1000 miles or more.	
B. 400 kHz-1.5MHz	Ground wave reception only, usually no more than 200 miles but certain winter conditions can increase this to 1000 miles.	'Skip' takes place and reception of stations up to 1000 miles is common with not infrequent reception of stations at much greater distances.
C. 1.5MHz-3MHz	Similar to B but distant reception more common.	Varies with conditions but similar to, and usually better than, B.
D. 3MHz-8MHz	Similar to C but distant stations much easier and more reliable. Distances of several thousand miles especially at night.	
E. 8MHz-15MHz	Generally the best frequencies for DX but ground wave absorption limits local reception.	Often good for long distance reception but depends on conditions and time of year.
F. 15MHz-25MHz	As for E but DX, although often better, is more dependent on conditions.	Usually poor for long distance reception but dependent on time of year and conditions.
G. 25MHz-45MHz	Highly dependent on conditions—sometimes excellent DX is possible but more often unsuitable.	Local reception only.
H. 45MHz-120MHz	Local reception except for occasional 'freak' conditions, usually associated with high pressure areas—when stations several hundreds of miles away can be received.	
I. 120MHz-250MHz	As for H but freak conditions much less common.	
J. 250MHz-1GHz	Local reception only—rarely more than 30 miles. Signals absorbed very easily. Very occasional freak conditions give reception of stations at a few hundred miles.	

frequency is adjusted so that it can be observed to either penetrate the ionosphere or be reflected back to earth. When this frequency is found—the highest limit to which the frequency can be raised and retain its reflection—it is known as the *Critical Frequency*.

Having obtained this frequency it may be increased up to three or even five times, provided the wave is radiated in such a manner and angle that it will meet the layer at a slanting or oblique angle. Such arrangements may appear straightforward but in the case of a multi-hop circuit—perhaps one crossing the equator or a dusk and night period—the requirements become complex, requiring many calculations and even some compromises to meet the variations over the path. The wave for reflection from the F Layer will, even during its first hop, need to be strong enough not only for reflection but to overcome losses through absorption when it passes through the D and E regions. It will, in fact, have to pass through these lower layers on two occasions even during its first hop.

S.I.D.

We often hear on the amateur bands comments such as "Conditions aren't too good today". Such remarks refer to changes in propagation which can broadly be placed in two categories, one type of disturbance is referred to as a *Dellinger* or *SID* (*Sudden Ionospheric Disturbance*). This is often of a sensational effect happening in a very short time—so suddenly that the receiving equipment is often suspected. The effect is brought about by solar action

which causes an overwhelming ionization of the D Layer leading to almost complete absorption.

The lower frequency end of the shortwave band is most affected and signals in this part may even become inaudible. The higher frequencies are less affected and will be the last to suffer losses and the first to return to normal. The duration of such disturbance is usually short lived.

When the face of the sun looking towards the earth is subjected to an eruption, solar flare (often called a sun spot) this brings about the emission of numerous kinds of radiation. These vary in their intensity but when of a great magnitude, may persist for a long period. For these reasons this kind of unsettled condition may reoccur with a complete rotation of the sun in approximately 28 days. The *Dellinger* or *SID* will normally only effect that side of the earth facing the sun.

Ionospheric Disturbance

A more prolonged type of disturbance known as an *Ionospheric Disturbance*—or *Storm*—may also be associated with solar conditions and often occurs some 30 hours after observation of changes on the surface of the sun. The general merit of reception falls considerably with deep and sometimes rapid flutter fading due to a lower and variable density of the F Layer.

Having described such adverse conditions, the reader may begin to wonder how a wave survives for so many thousands of miles, and especially as variations in the signal strength may be as much

as 1000 to 1, yet so much in modern receiver design is included to bring these variations to a stable and acceptable listening quality. The information given in the chart headed "Radio Propagation Characteristics" should be of value in helping to choose the correct wave bands.

Reception Reports

Considering the complexities and variations in propagation it is not surprising that all broadcasting organisations giving a service in the international broadcasting bands welcome accurate reception reports from listeners.

Considerable sums of money are spent each year to inform the listener of recommended frequencies and times of operation. Even after a schedule is published, the broadcaster is still in need of accurate information regarding the level of interference, as the shortwave bands are so congested—a situation which will become worse as we move to solar minimum conditions and the higher frequency bands become less useful.

Medium Waves

Most of these remarks have concerned the short waves or high frequencies as these are the ones most used for long distance reception. However, reception of distant stations is also possible in the medium wave band (525-1605kHz). MW Dxing is made especially difficult due to the large number of high powered stations operating in Europe. This wave band is basically designed for local reception and there are far fewer opportunities for long distance listening, even after midnight. Owing to so many broadcasters extending their hours of broadcasting such services frequently include an aerial system designed to avoid the sky wave and emphasise the ground wave. This reduces after dark interference and at the same time permits an economy by the sharing of frequencies. Listening to stations operating in the MW band is in any case confined to the hours of darkness if reception from a great distance is the aim. After dark these frequencies are reflected by the E Layer; the D Layer at night being almost non-existent. There are cases, however, when frequencies approaching 2MHz find reflection from the F Layer, having penetrated the E region.

Other Bands

Other bands are subjected to other influences; remarkable reception due to tropospheric propagation in the VHF and UHF bands occurs occasionally. An outstanding example of the abnormal mode of propagation is that in earlier sunspot maximum periods, BBC Television pictures have been resolved as far away as the West Indies and South Africa.

Many listeners appear to associate bad weather, such as rain and fog, with either good or bad reception but there is no real evidence to substantiate this, at least not as far as the medium and shortwave bands are concerned. As the frequency is increased towards the microwave portion of the spectrum, that above 1000MHz, these and other factors have to be taken into account.

At a recent press conference given by the GPO Telecommunications Department, many interesting facts were disclosed concerning the adverse effects of rainfall over even short path transmissions on these channels. ■

your PRACTICAL AERIAL DATA WALL CHART

WE expect rather a lot of our receivers don't we? In the early days of radio most homes sported a beautiful long wire aerial but with the tremendous improvement in receiver design and the vastly improved sensitivity we seem to have forgotten just how important a decent aerial is. Some receivers now being marketed claim that the silly little telescopic aerial which is an integral part of the set is all that is needed—rubbish!

For good DX results three things are needed, all of about equal importance: the receiver, the skill of the listener and the aerial. The receiver will cost quite a bit of money and the skill can only be learned with time; on the other hand an aerial will cost very little—wire isn't all that expensive after all—and the erection will take only a few hours.

The type of wire is far from critical. Hard drawn copper is possibly the best, it doesn't stretch, but it is expensive. One of the best, and cheapest forms is aluminium garden binding wire. 250ft. reels cost only about 30p.


Ex-Government aerial wire is still available on the surplus market and this is excellent; it is usually made up from one strand of copper surrounded by steel wires for strength.

On the Wall Chart we have tried to deal with *practical* types; it is all very well to read about wonderful professional arrays but few of us have the room or the money to pay for the tall masts required. Instead we have dealt with the types that readers are likely to have space for. Even if you live in a small flat you will usually be able to find room for a pretty good Whip Type, or even an Inverted L.

The chart deals with aeriels but of course any signals induced into them will only be with respect to earth and a good earth should be used. One always used to see comments such as ". . . the earth wire can be taken to a cold water pipe . . ." but in these days of plastic plumbing this will not always work. A good earth can be made by soldering a wire to a piece of copper clad board—such as is used for making printed circuits; this should be buried as deep in the ground as can be managed and a bucket of water should then be poured over it to make the earth resettle around it. The size of the board is not critical but the larger the better. The wire from this earth to the receiver should be of very low resistance and as short as possible. ■

reference source

E. BUCKLAND

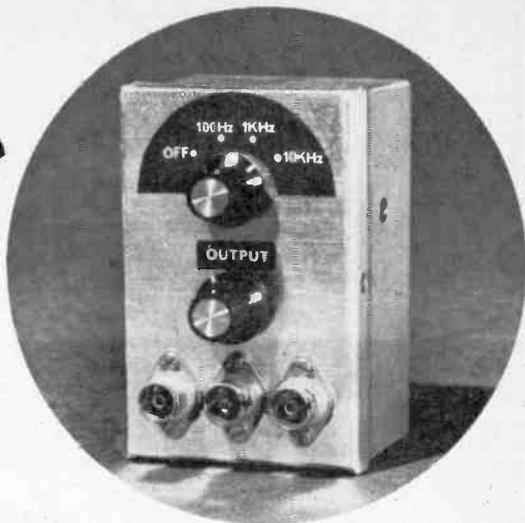

NO one would deny that a full-range, full-facility audio signal generator is not useful. The author has a good one (built from a design published in *Practical Wireless* some years ago) and it is continually in use for designing, testing and trouble shooting but only a few of the facilities account for 95 per cent of the usefulness. Most of the time the frequency is left on 1kHz and only the calibrated output is used. When the frequency is varied it is nearly always at the spot frequencies of 100Hz, 1kHz and 10kHz. Nearly all signal generators have a switch to give either a sine-wave or square-wave output. This is frequently used but it is rare that the type of wave-form matters very much. Where it does matter, it is nearly always the square-wave that is required.

The main signal generator was found to be so useful that the author decided on building another, this time to be battery operated for portability. Bearing in mind the points made above it was also decided to make a far simpler and less expensive version, incorporating only the most useful facilities.

This unit gives a constant square-wave output—irrespective of battery voltage and other factors—at three spot frequencies: 100Hz, 1kHz and 10kHz. The output is continuously variable over a wide range. To simplify the switching, the on-off switch is incorporated with the frequency selector and the decade outputs are provided from separate output sockets.

The complete unit is very small, fitting nicely into a small aluminium box, 4in. x 2½in. x 2in. and the total cost is only a fraction of that for a full facility audio signal generator.


This makes an excellent “back-up” unit but even by itself it should be useful for those without an a.f. signal generator.

THE CIRCUIT


The signal oscillator is a basic multivibrator, made up from Tr1 and Tr2. Both halves of this are identical, with similar base bias resistors and the same collector load, although for Tr2 this is a variable potentiometer and not a fixed resistor as that for Tr1.

The values of the coupling capacitors are altered by the main switch, SW1, and one of three capacitors can be selected. This balance in the two sections ensures a square wave output with a 1:1 mark space ratio, not vital but easy to incorporate and occasionally useful. The values of the bias resistors etc., ensure that the transistors are driven on hard when they are turned on, this ensures that the output will be constant.

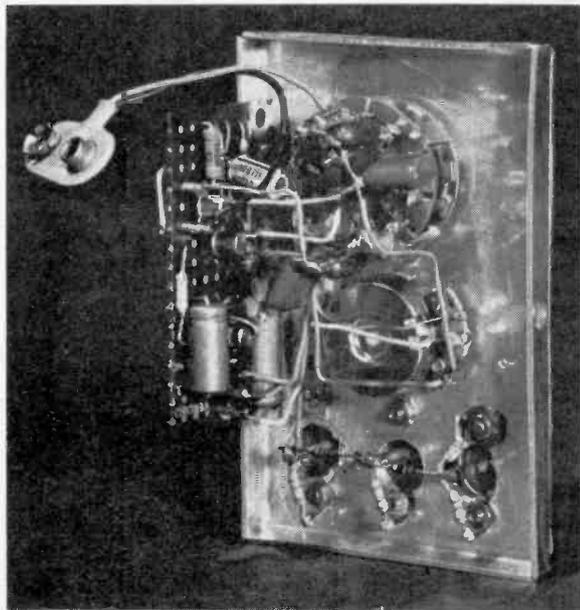The output is taken from the collector load of Tr2, the slider of VR1 is connected via C2 to the base of the emitter-follower Tr3. The high value of C2 is deliberate, this will ensure no degradation of the tops and bottoms of the square wave at 100Hz. Tr3 was found necessary to isolate the output from the



Internal view of the prototype.

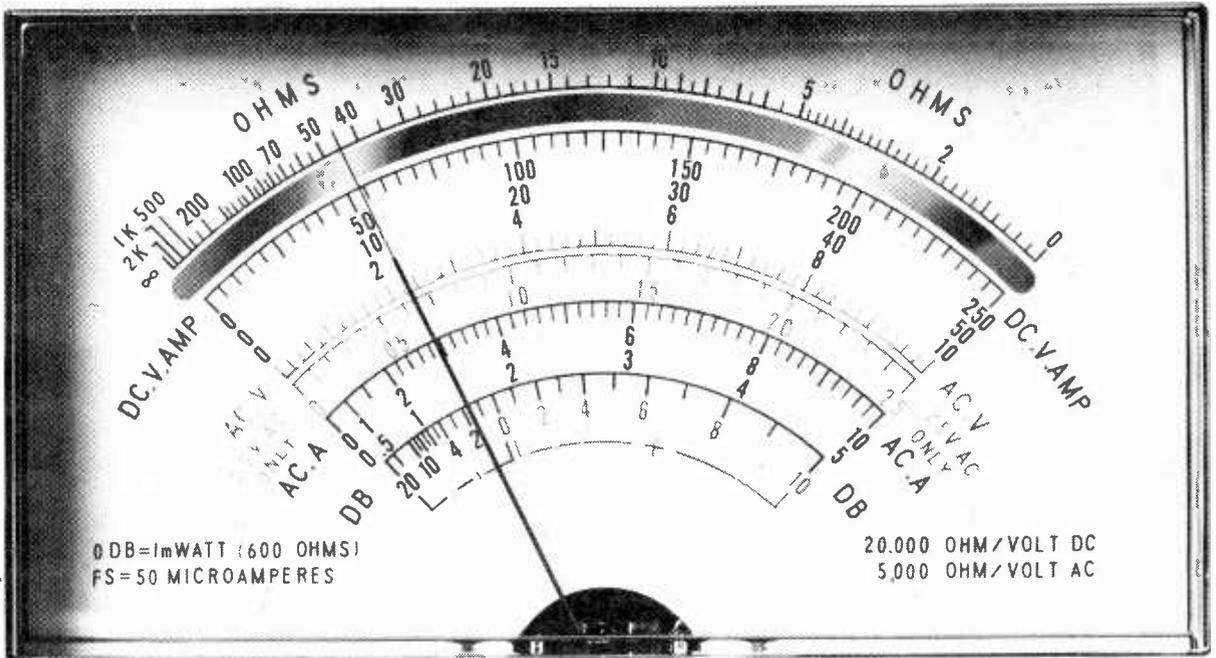

You can see why we sell a lot of multimeters.

Ours are so much easier to read.

The Eagle K1400, for instance, has a big open face and a beautifully laid-out mirror scale.

Decibels and AC Voltage are picked out in red, and the others in black. Which makes it all crystal clear.

The K1400 is easier to use, too. There are two knobs: the left for functions, the right for range limits.

Again, you can't go wrong. Everything's clearly marked, including the 'Off' position which protects the meter movement against knocks and bangs.

And, of course, Eagle's exclusive overload protection circuit is built in.

All Eagle test equipment is like this. Simple to use. Reliable. Backed by a full two year guarantee.

And like H. W. Hellyer, one of the country's leading technical experts said, "Not by any means expensive: it is well worth what it costs."

If you send us the coupon, we'll send you our catalogue.

*R.E.R. - September, 1971.

SPECIFICATION Ranges - K1400

D.C. Volts: 0-0.25, 1, 2.5, 10, 50, 250, 1,000 and 5,000 volts.

Input resistance: 20,000 ohms/volt.

Accuracy: better than $\pm 3\%$ full scale.

A.C. Volts: 0-5,000 volts in six ranges, steps similar to above.

Input resistance: 5,000 ohms/volt.

Accuracy: better than $\pm 4\%$ full scale.

D.C. Amps: 0-50 microamps, 1 mA, 10, 100, 500 mA and 10 amps.

Accuracy: better than $\pm 3\%$ full scale.

A.C. Amps: 0-10 A in 4 ranges, steps as before.

Accuracy: better than $\pm 4\%$ full scale.

Resistance: 0-20 M ohms in 3 ranges.

Accuracy: better than $\pm 3\%$ of scale length.

Decibel scale: -20 to +50 dB.

Standard level: 0 dB = 1 mW, 600 ohms load.

Frequency Response: 10-100,000 Hz for 2.5V, 10V and 50V ± 0.5 dB.

Size: 6 $\frac{3}{8}$ x 8 x 3 $\frac{3}{8}$ in. **Weight:** 3 $\frac{3}{8}$ lb.

Rec. Retail Price: £28.00



Eagle International

Eagle International Precision Centre Heather Park Drive
Wembley HA0 1SU Telephone 01-903 0144

Please send me your catalogue with full details of Eagle multimeters and other test equipment.

Name _____

Address _____

PW1

NEW FROM SAXON

STANDARD & CUSTOM-BUILT SOUND EQUIPMENT MUSICAL INSTRUMENTS, NEW & SECOND-HAND

THREE LOW-PRICED AUDIO MODULES — 100W — 35W — 25W (all rms ratings)

SA100 £10.90 carr. free
16 transistors—6 diodes
4½" x 4" x 1"

SA35 £4.45 carr. free
8 transistors—2 diodes
4" x 3" x 1"

SA25 £2.95 carr. free
8 transistors—2 diodes
4" x 3" x 1"

COMPLETELY BUILT AND TESTED — SATISFACTION GUARANTEED

Employing the latest silicon devices these three modules excel in the field of low-cost high quality audio. All three modules are short and open circuit proof and the 100 watt module has further protection against overheating and faulty inductive loads. All modules may be used with a wide range of supply voltages and loads. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRAORDINARILY LOW PRICES POSSIBLE.



BRIEF SPEC. FOR ALL THREE MODULES

Response	15-40,000 Hz ± 1 dB
Distortion	0.2% @ 1 kHz
Loads	4-8-16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100

ALL MODULES ARE CONSTRUCTED ON GLASS FIBRE P.C. BOARD

STABILIZED SUPPLIES

PS45—supplies two SA25 or two SA35. Fully assembled and tested, £2.85. MT45 to suit the above module £2.85. Carr. PS45 free, MT45 20p.

SPECIAL OFFER. Complete power supply if purchased with either two SA25 or two SA35, only £5.00.

PS70—Complete supply for two SA100's including mains transformer for music use, £7.75. Carr. 45p.

SOUND to LIGHT CONVERTER

This single channel light unit is the ideal low-priced addition to the D.J.'s equipment. It will operate from the bass notes thus flashing lights up to 1000 watts in time with the music. Complete with control and attractive case—fully tested and guaranteed.

£8.90

Carr. Free

120 WATT MODULE for 8 ohm systems.

Rugged transformer driver stage. **£13.90** carr. 20p or with supply **£18.95** carr. 40p.



GOODMANS 12P

12" 50W 8/15Ω only **£10.90** carr. 30p

Famous British 25W 12" loudspeaker only **£4.95** carr. 20p



CSE AMPLIFIER £32 carr. free. 70W cont. R.M.S. 100W music. Two inputs, bass, treble. FULLY GUARANTEED.

SAXON 100 AMPLIFIER. FET inputs four channels 100 watts R.M.S. 8 ohms, £48.50. 50W version, £37.75.



ANOTHER SAXON PRICE BREAK-THROUGH!

STEREO CONTROL UNIT only £15.80

Carr. Free

MONO VERSION with P.F.L. still available at £6.50, carr. 20p
SATISFACTION GUARANTEED

A UNIT TO SATISFY ALL THE NEEDS OF A HIGH QUALITY DISCOTHEQUE

LOOK AT THESE FEATURES

- ★ Left/right fader, treble and bass controls for decks.
- ★ Microphone input with own volume, treble and bass controls.
- ★ Headphone monitoring (P.F.L.) with 100mW undistorted output.
- ★ Master volume control—output levels up to 1 volt.
- ★ Suitable with all power amplifiers or with the SAXON SA series of amplifier modules.



- ★ Built-in mains operated power supply, or may be battery operated.
- ★ 20-25,000Hz response.
- ★ -65dB noise level.
- ★ Accepts all ceramic cartridges.
- ★ 26dB tonal variation.
- ★ Smart black panel.

(Illustration shows Mono Unit only)

S.A.E. WITH ALL ENQUIRIES PLEASE — TELEPHONE ORDERS & EXPORT ENQUIRIES WELCOME

CALLERS AND MAIL ORDER
327-331 Whitehorse Road,
West Croydon CR9 2HS. 01-684 6385

SAXON ENTERTAINMENTS

CALLERS ONLY:
6a Delce Road, Rochester, Kent,
Medway 44203

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker
Super-thin construction permits new installation ideas.



Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-3/4" x 1-11/16". Weight: 19 ounces.

£6.50 each Stereo pair £12.50 post free

web europa


P.O. Box 162, Watford WD1 1AA

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT PRICES

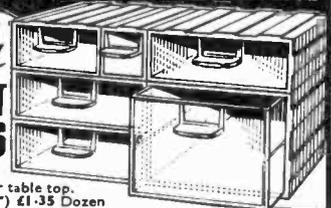

SINGLE UNITS (5" x 2½" x 2½") £1.35 Dozen
DOUBLE UNITS £2.25 Dozen
TREBLE (3D) £2.35 for 8
DOUBLE TREBLE 2 draws in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8.

5 SIZES ALL INTERLOCK

PLUS QUANTITY DISCOUNTS! Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7½% in the £. Order £20 and over Deduct 10% in the £. Pack./Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free.

IVORYET LIMITED

(Dept PV10) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2

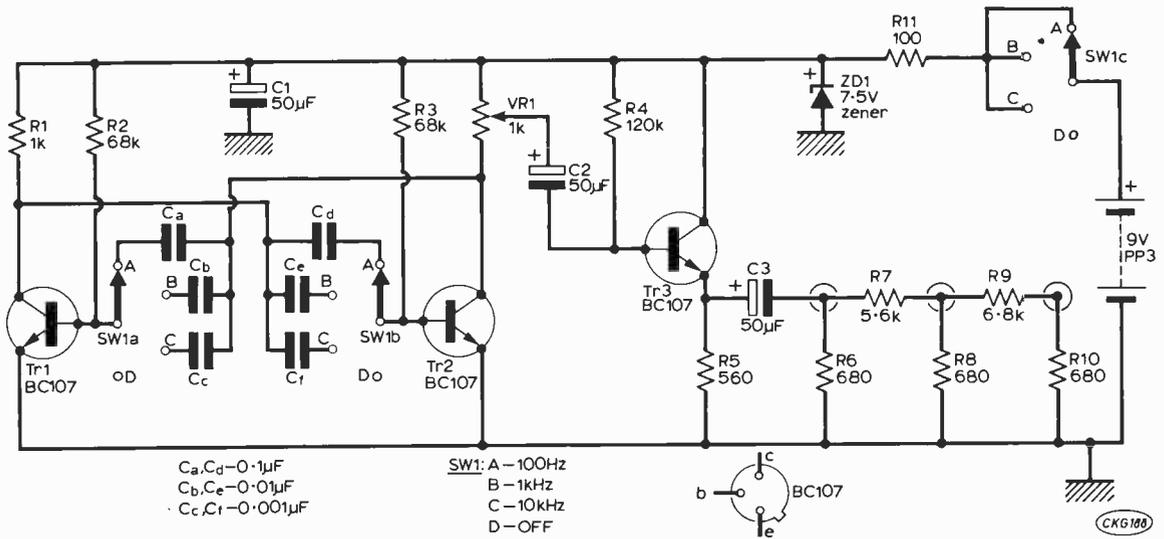


Fig. 1: Complete circuit of the Audio Reference Source.

multivibrator. As this stage contributes no gain it may be thought that the output network could be connected directly to the slider of VR1 but this would vary the load at the collector of Tr2 and affect the frequency and level. The inclusion of Tr3 makes certain that this interaction is minimal.

The output from the emitter of Tr3 is taken via the d.c. blocking capacitor C3 to a decade attenuator. At each of these output sockets the output is one tenth that of the previous one.

Because of the operation of a multivibrator, we can always be sure that the output will be constant, irrespective of frequency as long as the supply voltage is constant. This is done by including a zener diode with a rating of 7.5V in the positive supply line, the voltage drop taking place across the resistor R11. SW1 is a three-pole, four-way switch; three of the sections are used to alter the frequency of operation of the multivibrator, the fourth section acts as the on-off switch.

The whole circuit is very simple as can be seen from Fig. 1. BC107 transistors are specified but BC108, BC109 or their plastic versions (BC168 and BC169) can also be used, as can a 2N2926. None of

★ components list

Resistors

R1	1k Ω	R7	5.6k Ω
R2	68k Ω	R8	680 Ω
R3	68k Ω	R9	6.8k Ω
R4	120k Ω	R10	680 Ω
R5	560 Ω	R11	100 Ω
R6	680 Ω		

All resistors $\frac{1}{4}$ W, 5 per cent types.
 VR1 1k Ω linear pot., carbon track

Capacitors

C1 50 μF 10V min.	C_a, C_d 0.1 μF Mylar or ceramic
C2 50 μF "	C_b, C_e 0.01 μF " "
C3 50 μF "	C_c, C_f 0.001 μF " "

Semiconductors

Tr1 BC107 see text	Tr3 BC107 see text
Tr2 BC107 " "	ZD1 7.5V, 50mW zener diode

Miscellaneous

SW1, three-pole, four-way rotary switch; 3 off coax sockets—see text; battery clip; Veroboard, 16 x 9 holes, 0.15in. matrix; small aluminium case with lid.

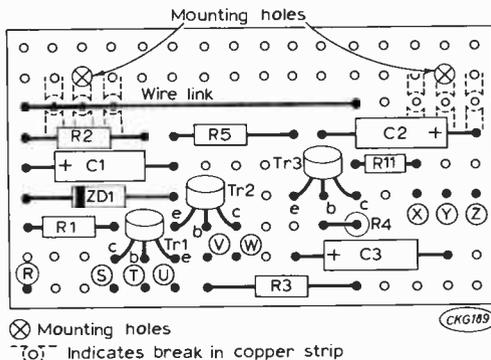


Fig. 2: The component layout on Veroboard. The only breaks in the copper strip are those near the mounting holes.

these changes will affect the constant output which is controlled by the supply voltage and nothing else.

VR1 should of course be a linear control and the associated knob can be calibrated if required.

The capacitors in the multivibrator may not give the exact frequency specified, this will depend on their tolerance, but it should be close enough for all practical purposes.

The unit takes only a small current and this is adequately provided for by a PP3 battery.

CONSTRUCTION

The component layout of such a unit is far from critical but that used in the prototype is both simple and neat. The majority of the components are mounted on a small piece of 0.15in. matrix Vero-

board, 16 holes by 9 holes; this can be cut from a standard 2½in. width. The component layout is shown in Fig. 2. Various take-off points are letter coded R to Z to tie up with the main wiring diagram in Fig. 3.

No breaks are necessary in the copper conducting strip of the Veroboard other than those near the mounting screws. The battery negative is taken to the board by a wire running from a small solder tag which fits under one of these mounting screws.

The frequency determining capacitors are mounted directly onto the switch SW1, this can be seen from the photograph of the prototype.

The output sockets are mounted next to each other and the attenuating resistors are wired directly to these, the chassis connections being taken to solder tags under the mounting screws. Coax output sockets were used on the prototype mainly to continue standardisation in the author's test equipment but other types—such as phono sockets—can be used.

The component board is held onto the chassis by means of a short length of aluminium angle bracket.

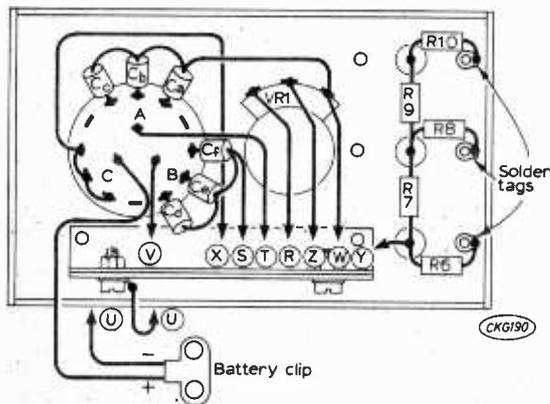


Fig. 3: The wiring diagram. The letters R-Z match up with those in Fig. 2.

CALIBRATION

It is not possible to say what the exact output will be for any particular version, this depends on the saturation of the individual transistors, but what can be said is that it will not vary with frequency or battery voltage. If a highly accurate output is required this is best measured on a 'scope. The output can also be reduced to a reference figure by wiring in an extra resistor between the collector of Tr2 and VR1. If the output is say 2V and the maximum output wanted is 1V then a 1kΩ resistor will be required. The output from the prototype is 1.8V and this level has been found sufficient. The output from the other decade outputs is 180mV and 18mV at maximum output. ■

BACK NUMBERS

We regret that the back numbers department of P.W. has now closed and consequently we are unable to supply these. Requests for specific back issues can usually be included in our 'CQ' section; there is no charge for this but it is a service between readers and P.W. is unable to meet any of these requests.

CHARLES MOLLOY

THE Medium Wave Column

NEWCOMERS to the medium waves are often surprised at the number of West African countries that can be heard on this band. La Voix de la Revolution located at Conakry in the Republic of Guinea, is a conspicuous signal on 1403kHz after 2300hrs GMT. Programming is African in style with announcements in French. The new high power broadcaster at Bissau, Portuguese Guinea can be logged on 1070kHz between 2300hrs and 0100hrs GMT with pop music, announcements and news being in Portuguese. From the Canary Islands, the high power Radio Nacional Espana outlet in Tenerife is a strong signal on 620kHz after 2300hrs. Programmes are in Spanish and there is interference at times from Batra in Egypt. Dakar, Senegal on 764kHz can be heard on weekdays with African music and French announcements after Sottos, Switzerland closes down. From the Republic of Zaire (Congo) the station at Kinshasa on 692kHz is on the air all night and is audible, with African programming after the East German station on this frequency signs-off, usually at 0100hrs GMT on weekdays. Radio Nigeria at Enugu is on 1320kHz until sign-off at 2300hrs GMT. Programmes are in English and can be found during the last half hour of transmission, as a weakish signal between the European channels 1313kHz and 1322kHz. Another English speaking broadcaster is occasionally heard on 629kHz. This is ELBC at Monrovia, Liberia which closes down at 0045hrs GMT and is usually logged towards the end of its transmission.

A new broadcaster in North Africa has appeared on the Long Waves. It is located in Algeria and is audible in the UK during the evening on 254kHz (1181m); a channel it shares with Lahti, Finland. Programmes are in French and reception reports, which are requested over the air, should be sent to Radio Television Algerienne, 21 Boulevard des Martyrs, Algiers, Algeria. This is the second North African to appear on the LWs in recent years. Azilal, Morocco is on 209kHz with programmes in Arabic and can be logged after dark with some interference from Kiev on the same channel. The range of long wave stations increases considerably at night—Europeans fade-in regularly along the eastern seaboard of North America after local sunset. Stations heard in the UK by the writer include Reykjavik, Iceland on 209kHz at 0100hrs GMT; Ashkhabad, Turkmenia on 200kHz after Droitwich signs-off; Ankara, Turkey 182kHz with sign-off at 1930hrs GMT; Baku, Azerbaijan on 218kHz at 0100hrs GMT; Novosibirsk 272kHz at 0130hrs and Omsk 394kHz at 1900hrs. In Europe, the long waves covers 151kHz to 282kHz but in Asiatic Russia the band extends to 400kHz. Regulars to be heard in the "hf" section are Orenburg 300kHz; Kharkov 384kHz and Minsk 400kHz.

Please send logs and information about the medium waves to the author at 132 Segars Lane, Southport PR8 3JG.

INCREASE YOUR KNOWLEDGE



Established 1891


MANY COURSES TO CHOOSE FROM incl.
 RADIO & TV ENGINEERING & SERVICING,
 TRANSISTOR & PRINTED CIRCUIT SERVICING,
 COLOUR TV SERVICING, ELECTRONICS,
 NUMERICAL CONTROL ELECTRONICS,
 TELEMTRY TECHNIQUES, CONTROL SYSTEMS,
 ELECTRONICS FOR AUTOMATION,
 COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

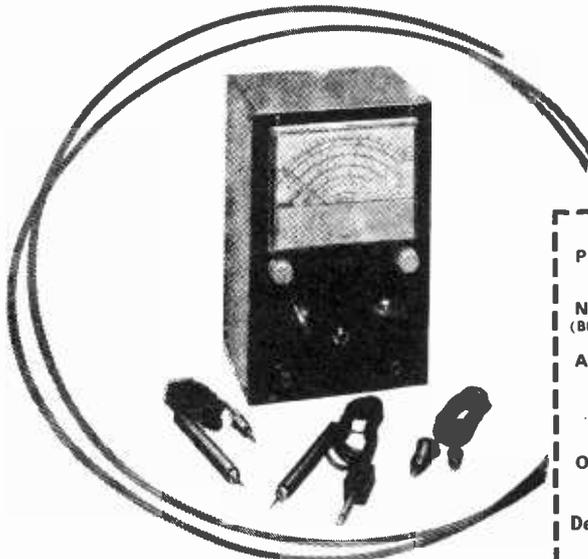C. & G. Telecommunication Technicians' Certificates
 General Radio Communications Certificate
 Radio Amateurs' Examination
 General Certificate of Education, etc.

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

C & G Radio Servicing Theory

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

Accredited by the CACC.

PLEASE SEND FREE BOOK ON.....

NAME
 (BLOCK CAPITALS PLEASE)

ADDRESS

OCCUPATION..... AGE

INTERNATIONAL CORRESPONDENCE SCHOOLS
 Dept. TA28, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.

BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 18 1/2 x 11 1/2 in.

Above motor board 3 1/2 in. below motor board 3 1/2 in. with STEREO and MONO XTAL £8.75 Post 25p.

MONO-COMPATIBLE £7.75 Post 25p.

Plays all records



RCS DE-LUXE 3 WATT AMPLIFIER. Ready made tested. Printed circuit. 3 watts output. Tone and volume controls. Completa with two knobs, output valve and rectifier and high performance loudspeaker. Double wound fully isolated mains transformer. A.C. Mains 200/250V. Response 50-18,000 cps. Sensitivity 200mV. £4 Post 25p.

R.C.S. PORTABLE PLAYER CABINET
Really smart appearance with space for R.O.A. Amplifiers and most modern autochangers. Size 17 x 15 x 6 in approx. Metal fittings. Carrying handle. £4 Post 25p.

Popular colours. Two-tone finishes covered. £4 Post 25p.

GARRARD DISCO DECK £10 Post Free

4 speeds. Plays all sizes of records. 4 pole heavy duty motor. 9 in. steel turntable. Plug in head complete with stereo/mono cartridge. Adjustable stylus pressure. Automatic. Brown and Cream finish. AC mains 110/240V. Base plate size 18in. x 8in. Operating area 14in. x 12 1/2in. Above motor board 3in., below motor board 3 1/2in. Ideal for Home Hi-Fi or Discobote.



GARRARD AUTOCHANGERS with Sonotone Cartridges Stereo Diamond and Mono Sapphire. Model 1085 £10. Model 5500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER £4-50
Turntable, 4-speed motor and separate pick-up

HI-FI PICK-UP CARTRIDGES. Diamond LP/Stereo Stereo/Mono 9TA £2-50; GP4 £2-50; GP3 £2-00; Sapphire Mono GP91 £1-50; Power-point LP/78. 60p.

E.M.I. WOOFER AND TWEETER KIT £5-75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet. 4oz. Gauss 18,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 8 in. square has a special light-weight paper cone and magnet 10,000 lines. Crossover condenser supplied.

Impedance Standard 8 ohms
Maximum Power 12 watts
Useful Response 25 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in., £9 POST 25p
MODERN TEAK DESIGN



WEYRAD P50-TRANSISTOR COILS

EA2W Ferrite Aerial. 72p	Spare Cores 3p
Osc. P50/LA10 33p	Driver Trans. LFDT4 50p
I.F. P50/CC 470 kc/s. 36p	Printed Circuit, PCA1 58p
3rd I.F. P50/SC 36p	1.5 Tuning Gangs 65p
P51/1 or P51/2 38p	Weyrad Booklet 10p
P50/3V 36p	OPTI 58p

Mullard Ferrite Rod 8 x 1 in., 20p. 6 x 1 in., 20p.

VOLUME CONTROLS 800hm Coax 4p. yd.

Long spindles. Midget Size 8 h. Ohms to 2 Meg. LOG or LIN. 1/2 15p. D.P. 25p. 50 yd. 42p.

STEREO L/S 85p. D.P. 75p.
EDGE 5K. S.P. Transistor 25p

8in ELAC HI-FI SPEAKERS £3-75

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts music power.



BLANK ALUMINIUM CHASSIS 18 s.w.s. 2in. sides. 7 x 4in. 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 99p; 11 x 3in. 50p; 16 x 10in. 21p.

ALUMINIUM PANELS 18 s.w.s. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 3in. 16p; 10 x 7in. 10p; 12 x 5in. 20p; 12 x 8in. 28p; 16 x 8in. 28p; 14 x 9in. 24p; 12 x 12in. 40p; 16 x 10in. 50p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p.
3 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way or 4 p. 8-way, or 4 p. 3-way 25p.

TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 28p.

"THE INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER
200/250V. A.C. £2-35 Post Leadst. S.A.E. 15p



R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifier and Double Wound Mains Transformer input 200/240V. A.C. Output voltage available 5 or 9 or 12 or 15 or 18 or 20V. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in. FREE

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12V or E.T. line 200-300V. D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2 in. Response 25 cps. to 25 Kc/s. 26dB gain. For use with valve or transistor equipment. £9p Post Full instructions supplied. Details S.A.E. 90p 10p

NEW TUBULAR ELECTROLYTICS	CAF TYPES	
3/350V .. 14p	250/25V .. 14p	50-80/250V .. 25p
4/350V .. 14p	500/25V .. 20p	90-110/250V .. 25p
8/450V .. 14p	1000/25V .. 25p	32-32/250V .. 15p
16/450V .. 16p	1000/50V .. 47p	32-32/450V .. 33p
32/450V .. 20p	8+8/450V .. 18p	32+50/250V .. 50p
25/25V .. 10p	8+16/450V .. 20p	32+32+32/250V .. 42p
100/25V .. 10p	16+16/450V .. 25p	100+50+50/250V .. 48p
100/25V .. 10p	25+25/250V .. 25p	

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 8, 16, 25, 30, 50, 100, 200mF. 18V. 10p.
500mF. 18V. 15p; 25V. 20p; 50V. 30p.
1000mF. 18V. 17p; 25V. 25p; 50V. 47p; 100V. 70p.
2000mF. 8V. 25p; 25V. 45p; 50V. 57p.
2000mF. 50V. 65p; 5000mF. 25V. 47p; 50V. 65p.
5000mF. 5V. 23p; 18V. 42p; 25V. 70p; 50V. 85p.

OKRAMIO 1pF to 0.01 mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 250V-0.1 4p, 0.5 15p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 5p; 0.47 25p. SILVER MICA. Close tolerance 1%; 2-2-500pF 5p; 500-8-200 pF 10p; 2,700-5-500pF 8p; 8,200pF-0.01, 1mF 20p; each. TWIN GANG. -0.0-0.208pF +170pF, 65p; slow motion drive 45p; small 8-200pF 45p.

SHORT WAVE SINGLE 10pF 30p; 25pF 55p; 50pF 55p.
NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p.
RESISTORS, 1/4 w., 1 w., 20%; 1/2 w., 5p to 10 ohms to 10 meg HIGH STABILITY. 10 ohms to 10 meg. 10p.
Ditto 5% Preferred values 10 ohms to 10 meg. 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 3 ohms 10p

GARRARD DECADEC SP25 MK II RECORD PLAYER

With Stereo/Mono Demam Cartridge transcription head and arm Four speeds. 10 1/2 in. turntable. Anti-ramble filter Bias compensation. Laboratory motor.



SPECIAL PRICE £18-50 Post 25p

METAL PLINTH & PLASTIC COVER
Cut out for most Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 x 7 1/2 in. Post 25p

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH AT SAME PRICE £5-50

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp.	£1-50
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2-50
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£3-00
300-0-300 v. 120 mA. 6.3 v. 4 a. CT; 6.3 v. 2 a.	£3-25
MINIATURE 200. 200 mA., 6.3 v. 4 a. CT; 6.3 v. 2 a.	75p
MIDGET 20v. 45 mA., 4.5 v. 2 a. 2 1/2 x 2 1/2 in.	90p
MINI-MAINS 20v. 100 mA. 1 1/2 x 1 1/2 x 1 1/2 in.	50p
HEATER TRANS. 6.3 v. 3 a.	60p
Ditto tapped sec. 1.4 v., 2.3 a., 5.6 v. 1 1/2 amp.	95p

GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 6, 8, 10, 12, 15, 18, 24 and 30 v. £2-25
1 amp. 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 45, 60. £2-25
2 amp. 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 45, 60. £2-25
5 amp. 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 45, 60. £2-75

AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 100w. £2-25; 500w. 26-25; 750w. 21; 1000w. 214.

CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V. 1 1/2 amp. £2-50; 2 amp. £3-50; 4 amp. £2-50.

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p
LUCAS 12V500 Bridge 70V 5 amp 21.

E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. £3-95
Size 3 or 8 or 15 ohm.
(As Illustrated) Post 25p

With fared tweeter cone and ceramic magnet. 10 watts. £1-95
Bass res. 45-60 cps.
Flux 10,000 gauss.
State 3 or 8 or 15 ohm. Post 25p

Teak Cabinet Size 16 x 10 x 9 in. Post 25p £5

ALL MODELS "BAKER SPEAKERS" IN STOCK
Hi Fi Enclosure Manual containing 20 plans, crossover data and cubic tables. 42p. Post Free

BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 8 or 8 or 15 ohms. Post Free

Module kit. 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
18 inch 28 watt £7	18 inch 35 watt £9	15 inch 15 watt £19
8 or 8 or 15 ohm	8 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fitted wood front For 12in. or 10in. dia. speaker 20 x 12 x 9in. 49. Post 25p For 18 x 8in. or 8in. speaker 18 x 10 x 9in. 25. Post 25p For 10 x 8in. or 8in. speaker 16 x 8 x 8in. 24. Post 25p

LOUDSPEAKER CABINET WADDING 18in. wide, 16p ft.

GOODMANS 6 1/2 in. HI-FI WOOFER
3 ohm, 10 watt. Large ceramic magnet. Special Cambria cone surround. Frequency response 20-18,000 cps. Ideal P.A. Columns. Hi-Fi Enclosures Systems, etc. £4



ELAC CONE TWEETER
The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. £1-90 Post 10p

SPEAKER COVERING MATERIALS. Sample Large S.A.E. Horn Tweeters 2-18Kcs/a., 10V, 8 ohm or 15 ohm £1-50. De Luxe Horn Tweeters 2-18 Kcs/a., 15V, 15 ohm £2. TWO-WAY 5000cps 3 or 8 or 15 ohm 95p.

SPECIAL OFFER! 80 ohm 2 1/2 in.; 2 1/2 in.; 35 ohm. 3 in; 25 ohm. 2 1/2 in. dia.; 3 in dia.; 6 x 4 in.; 8 x 5 in. £1 EACH
15 ohm. 3 1/2 in. dia.; 6 x 4 in.; 7 x 4 in.; 3 ohm. 2 1/2 in. 3 in. 5 x 3 in.

LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 1/2 in. £1-50; 5 x 6 in. £1-60; 8 x 2 1/2 in. £1-50; 8 in. £1-75; 10 x 6 in. £1-90.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 3in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 3 or 8 or 15 ohm models £2.00 each. Post 15p.

VALVE OUTPUT TRANS. 25p; **MIKE TRANS.** 50-1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free



BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite serial. 9 volt. £4-50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4-80. £3-50

BARGAIN FM TUNER. 88-108 Mc/s. 6 Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch. £12-50

BARGAIN FM TUNER as above less cabinet £8-85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3-50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 35p.
BALANCED TWIN FEEDERS 30 ohms 5p yard.
JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 8-mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 2-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 5p; CANS 5p.

E.M.I. TAPE MOTORS Post 15p.
120v. or 240v. A.C. 1,200 r.p.m. 4 pole
135mA. Spindle 0.187 x 0.75 in. £1-25
Size 3 1/2 x 2 1/2 x 2 1/2 in. (Illustrated)

BALFOUR GERM MOTORS
120v. or 240v. A.C. 1,200 r.p.m. 4 pole
50mA. Spindle 3/8 x 3/8 in. Post 15p
2 1/2 x 2 1/2 x 1 1/2 in.

'THE Logiprobe'



LAURENCE COOK

THE circuit to be described was designed to fulfil the need to see what was going on in TTL logic systems without having to use a voltmeter to determine whether a "1" or "0" existed at any point. To give a positive indication of the presence of a logic level it was decided at the outset to have two lamps, corresponding to a "0" or "1". Neither lamp would light with the probe either floating or at an inadmissible voltage (e.g. 1.2V).

Since the probe has been completed, it has proved extremely useful to me (and to those who have borrowed it!) and will doubtless soon repay its cost in time saved tracking down faults. It may even encourage people to "have a go" at logic circuitry, since it quashes the familiar cry, "I can't see what's going on inside those bugs".

CIRCUIT

Only four transistors, four resistors, two diodes and two bulbs are used (see Fig. 1). A few moments spent studying the circuit should enable one to spot

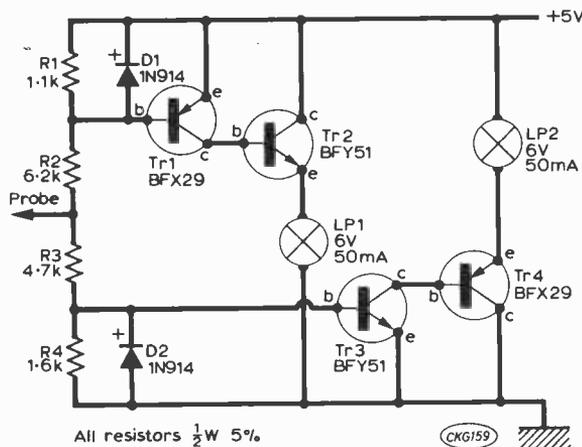


Fig. 1. Circuit of the Logiprobe.

the fact that it is really two circuits, one the inverse of the other; that is, Tr3 and Tr4 are arranged in a similar fashion to Tr1 and Tr2 but "upside down". The reason for this is simple.

With the probe on a logic "0" the voltage at Tr1 base, determined by the divider chain and probe voltage ($>0.8V$) causes Tr1 to turn on. Tr1 collector goes towards +5V and Tr2 emitter does the same, since Tr2 operates in common collector mode. LP1 therefore lights, indicating a logic "0". Similarly a logic "1" at the probe causes the voltage at Tr3 base to turn Tr3 on, and so Tr4 drives LP2, which lights up.

The resistors in the divider chain are of such values as to keep both lamps off when the probe is either floating or between 0.8V and 2.4V with respect to earth. Should the probe be accidentally touched on a voltage below earth or above +5V, then D2 or D1 respectively conduct to prevent the reverse base-emitter voltages of Tr3 or Tr1 being exceeded. Resistors R2 and R3 limit this current, but it is inadvisable to deliberately look for trouble by touching the probe onto higher voltage rails for long periods.

CONSTRUCTION

The logiprobe is assembled on a piece of 0.15 in. matrix veroboard (see Fig. 2.), with flying leads for supply and lamps. This enables it to be housed in any convenient small plastic box. The probe may be made from an old ball-point pen. It is largely a matter of choice how one terminates the supply leads, but since the supply must be the same as that of the TTL circuitry to be tested, then small insulated crocodile clips would be handy.


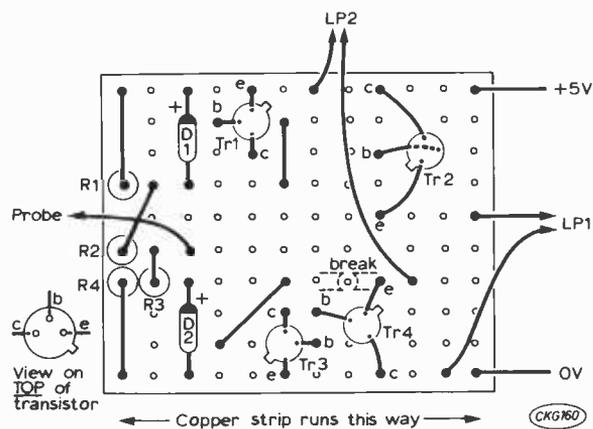


Fig. 2. Layout of the Logiprobe on a small piece of veroboard. Note that transistor leadout connections are shown as seen from on top. Compare this layout with photograph of completed unit.

Start by cutting a piece of veroboard to the right size for the box, then solder flying leads as shown. Next solder in the resistors, diodes and transistors. Use a heatsink and a small well-tinned iron just in case the resistor values are altered by overheating them, since these determine the levels at which LP1 and LP2 light. For this reason R1 to R4 should be 5% or better, and not nasty old things out of that TV set recently butchered! Finally solder LP1 and LP2 onto their respective leads.

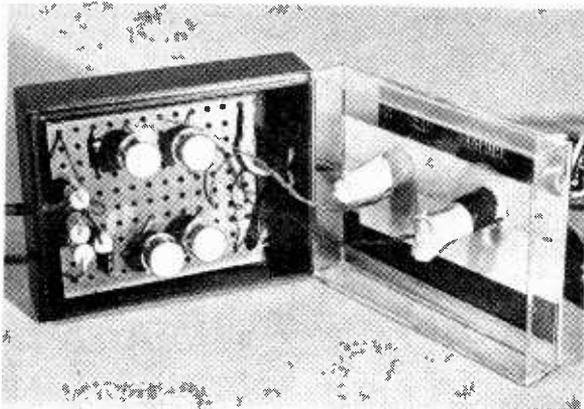

The lid of the box carries the two lamps which should be of differing colours, representing "0" or "1". The lamp terminals are insulated to prevent short circuits when the lid is fitted to the box.

TESTING

Connect the logiprobe to a 5V supply. If all is in order both lamps will be off. If not, either the supply is wrong, or a mess has been made of the board. Look for blobs of solder bridging the copper strips and get rid of them! If both or either of the two lamps are still on, make sure that everything is connected the right way round; we all make mistakes!

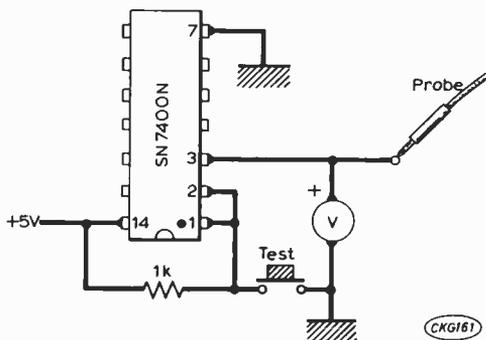


Fig. 3. Test set-up using an integrated circuit.

Touching the probe to earth or +5V should light LP1 or LP2; just to make sure all is well try the probe on an i.c. output with a voltmeter as a temporary check. (See Fig. 3).


Finally, a word of warning. Unless one is prepared to fiddle for hours with stacks of resistors, use the components specified. If you can't resist trying different transistors, at least use silicon of a similar type.

When your logiprobe is finished you'll wonder how you managed without it. But keep it hidden or people will borrow it from you!

BINDERS/INDEX for PW

Binders, costing £1 and indexes priced at 10p are obtainable from Information Bureau, Carlton House, Great Queen Street, London, W.C.2. Post and packing are free.

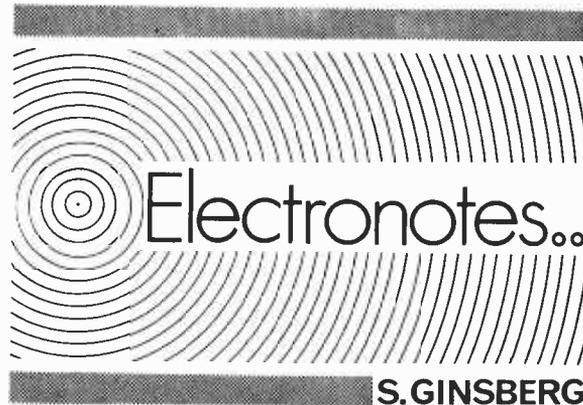Please state which volume number is required on your binder otherwise a blank one will be supplied.



ONE so often reads about the amazing advances and research programmes which take place in other parts of the globe. It is, therefore, refreshing to hear of some work which is being done in this country. This is particularly so since the establishment in question is the Post Office Research Department at Dollis Hill.

Workers at Dollis Hill are experimenting with those intriguing things called magnetic bubbles. A new generation of words is now fast coming into being. For example, a "bubble eater" and a "keyhole generator" are commonplace.

Basically, one method of employing magnetic bubbles is to lay down a series of minute conductive elements in the form of "T" shapes. These are typically formed of nickel-iron and are of the order of $1\mu\text{m}$ thick. The idea is that a tiny magnetic bubble can be transferred from one "T" to the next and even annihilated. Thus the bubbles can be used as a means of storing data. The bubbles themselves are only some $10\text{-}18\mu\text{m}$ in diameter.

The workers at Dollis Hill have developed, and I kid you not, a bubble detector bridge (see what I mean about the terminology?). The idea is an extremely clever one. Four minute resistive arms of a bridge circuit are formed by a deposition of a very thin nickel-iron alloy which is less than 1000\AA thick. The resistivity of this alloy changes whenever it is subjected to a magnetic field. Thus, when a magnetic bubble arrives at the bridge, its magnetic field will affect, say, two of the "resistors" effectively altering their resistances and thus unbalancing the bridge.

This work is impressive and follows closely on the heels of a previous announcement of work done here on transistors rated at around 1.5 Watts in the 4GHz region. These transistors were reported to have base widths of only 0.14 microns. Truly it is a small world.

Occasionally one hears news which is disturbing. Not only because of the actual content and what it implies, but also because of the reliable source from which it comes. This piece of news concerns lasers. One can use a laser beam and modulate it, thus using it to convey communications. If you "shine" a laser beam down a light fibre you can carry it from one place to the next. Again, it is possible to get quite a few "channels" on a laser beam, far more than you can on a single, comparable coaxial cable, for example. The thought now goes that for all communications work, land lines etc., lasers plus light fibres will be used. If this is true, then it could mean our old friend the coaxial cable is on the way out!

ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £80 radios! *You can't lose, we'll refund instantly if you are not astounded! Elegant black and chrome finish, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer and sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the far corners of the earth 24 hours a day, including all normal transmissions, VHF, AM, FM, MW, LW, USW, plus local and new stations not yet operational and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities and spares available for years and years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions and circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra). **BOX, POST, ETC. 50p.** ***BUT WAIT**, for only 55p extra you get the sensational "**COMPUTERISED**" **WORLD TUNING GUIDE** (it enables you to time, pinpoint and get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard "longlife" batteries **PLUS** ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY!** Send today or call at either store. It's a chance of a lifetime that nobody can afford to miss.

JUST ARRIVED! THIS YEAR'S NEW *COMPUTERISED? RUSSIAN MIRACLE!

BRAND NEW SPACE AGE model SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

THE FABULOUS ASTRAD 17

THIS OFFER ONLY FROM US!

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

PORTABLE RADIO & COMMUNICATIONS RECEIVER



28 TRANSISTORS AND DIODES! WAVEBANDS: STANDARD LONG and MEDIUM PLUS 5 SHORT WAVEBANDS PLUS ULTRA SHORT WAVES (V.H.F. AM, FM, MW, LW, USW.)

***COMPARE ITS PERFORMANCE with £80 RADIOS!**

BATTERY MODEL £20.75 BOX POST ETC. 50p
MAINS/BATTERY ELIMINATOR £1.48 extra

FIRST TIME EVER! *NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE! NO MORE GUESSWORK! INSTANT DATA at your fingertips - enables you to TUNE IN A FLASH to transmissions the world over!

SHOPERTUNITIES FOR BARGAINS!

ANOTHER EAST EUROPEAN MIRACLE!

FANTASTIC 2-in-1 PERSONAL PORTABLE and CAR RADIO

NOW WORLD WIDE RECEPTION

IN YOUR CAR TOO! (RUNS OFF 12V CAR BATTERY)

4 WAVEBAND VHF AM FM LONG & SHORT WAVEBANDS

FANTASTIC PRICE £19.95 BOX, POST ETC. 45p



Position it for CAR RADIO, results will justify! OR detach & use carry handle for PORTABLE with its own batteries!

TRY AND WATCH IT FOR UNDER £35!

FANTASTIC! Brand spanking new. Another East European Miracle! This incredible 2-in-1 Radio! First class makers—because of our crazy price, our contract stipulates we must NOT mention name! Beautifully made. 9 x 5 x 2 1/2 inches overall approx. Every up-to-date technological improvement. **15 SEMI-CONDUCTORS** + 9 Transistors + 5 Diodes + Stabiliser! **FOUR WAVEBANDS!** Yes, VHF Model with AM/FM Long and Short wavebands! Will get stations around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in Turret Tuner! **BATTERY MODEL** runs on standard batteries, usink car battery only! Don't you think it's miraculous? Span the Oceans and pull in hundreds of transmissions day and night, including short wave—even in car! **BUT WAIT**—simply remove Radio from car, "snap on" optional carry handle **AND YOU HAVE A DE-LUXE PORTABLE**, with additional upright tuning dial. **WRITTEN GUARANTEE**. Only £19.95 box, post 45p. *Sprung all metal matching detachable carry handle (as illus.) **AND set of batteries only 25p extra** if required. Match with sets costing £35 or more. Refund guaranteed.

Send quickly to our Uxbridge Road address or call at either store. (COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising Office at Holborn stores.)

SAVE £20.25 NOW!

THIS FANTASTIC OFFER ONLY FROM US!

Fabulous BRAND NEW SOLID STATE

This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



WITH REMOTE CONTROL MICROPHONE

OUR PRICE £23.75 CARR. ETC. 35p

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards.) We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio **AND** Cassette Tape Recorder & Player combined and it also runs off standard batteries or mains. (Simply plug in the 220/240v. AC line cord. Record and play back anything, anywhere! Even tape direct from the radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44!** **WE OFFER AT ALMOST HALF PRICE!** Wonderful features: * Press-button Keyboard Control Panel or check/record/level indicator or "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in. approx.) Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tape that are obtainable everywhere. The amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus B.B.C. National, VHF. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £4.65 more for a Car Radio or Car Cassette player **ALONE!** £23.75, CARR. ETC. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send today or call at either store.

BONUS OFFER: Batteries and Cassette Tape 25p extra if required.

Dept. WP/23, 164 UXBRIDGE RD., LONDON, W12 8AQ (Thurs. 1, Fri. 7) (facing Shepherd's Bush Green). Also 37 High Holborn, London W.C.1 (Thursday 7 p.m.). Both Mon. to Sat. 9 a.m.-6 p.m.

SHOPERTUNITIES LTD.

TOP DISCOUNTS + EASY TERMS

Stereo amplifiers. p. & p. 75p

Armstrong 521	£45.00
Braun CSV300	£95.00
Cambridge P40	£68.00
Cambridge P50	£71.00
Cambridge P100	£114.00
Ferroglyph F307/2	£47.00
Metro-sound ST20E	£25.00
Nikko TRM300	£32.00
Nikko TRM400	£41.00
Nikko TRM1200	£92.00
Rogers Ravensbrook (T)	£44.00
Rogers Ravensbourne (Ch)	£50.00
Tripletone 8+8	£26.00
Quad 33/303	£92.00
Radford SC24/SPA50	£160.00
Also Sansul, Teac, Revox, in stock.	

Tuner amplifiers p. & p. 75p

Armstrong 525	£72.00
Armstrong 526	£79.00
Armstrong M8	£7.50
Goodman's Module 80	£70.00
Goodman's One-Ten	£105.00
Leak Delta 75	£125.00
Pioneer SX1500TD	£170.00
Pioneer SX2500	£225.00
Scan-Dyna 2000	£78.00
TEAC AG7000	£180.00
Sonab R7000	£210.00
Sonab R4000	£125.00
Also Sansul in stock.	

TOKAI AM/FM MPX, 20/20 RMS PER CHANNEL ONLY £60.00

Tape/cassette decks

p. & p. £1.50

Grundig TK121, TK141, TK146, TK248 at 40% of normal list price.	
Harman Kardon CAD5	£125.00
Sansul SC700	from stock
TEAC A110	£65.00
TEAC A-350	£135.00
Philips N2400	£58.00
Wharfedale DC9	£92.00
Ferroglyph 724	£215.00
Revox 1102/3	£192.00
TEAC A3300	£110.00
Sanyo MR805	£79.00

Loudspeakers p. & p. 75p

B & W DM3	£45.00
B & W Model 70	£115.00
Cambridge Audio R50	£80.00
Celestion Ditton 120	£38.00
Ditton 15	£30.00
Ditton 44	£40.00
Ditton 66	£75.00
Dynaco A25/2	£28.00
Goodman's Magnum K2	£32.00
Goodman's Double Maxims	£27.00
Heco P4000	£35.00
Heco P2000	£26.00
Leak 600	£26.00
Kef Chorale	£34.00
Leak 600	£30.00
Tannoy 12" unit	£34.00
Tannoy 15" unit	£34.00
Tannoy 12" Lancaster	£50.00
Tannoy 15" Lancaster	£52.00
Wharfedale Denton 2	£14.00
Wharfedale Linton 2	£18.50

Cartridges (post free)

Shure M44E	£7.35
M55E	£8.00
M75-G	£11.20
M75-ED/2	£15.00
V15	£29.00
Goldring G800	£6.00
G800SE	£16.00
G850	£3.50
Audio Technica AT66	£4.00

PICKERING V15/C AC £3.50

Headphones p. & p. 25p

Pioneer SE30A	£8.50
Pioneer SEL-40	£10.50
Pioneer SE-50	£13.00
Sansul SS10	P.O.A.
Sennheiser HD414	£8.00
Koss PRO4AA	£22.00

Colour Televisions

p. & p. £2.00

Wega 915	£320.00
Grundig 717	£300.00
Sony 12"	£175.00
Teleton 12"	£138.00
Also Philips, 1TT-KB.	

Tuners p. & p. 50p

Armstrong 523	£41.00
Armstrong 524	£32.00
Braun CE251	£100.00
Philips RH691	£79.00
Radford FM3	£63.00
Pioneer TX-500	£52.00
TEAC AT-100	£80.00

Tone arms p. & p. 30p

S.M.E. 3009/S2	£24.50
S.M.E. 3012/S2	£25.50
Goldring L75	£10.00
Goldring L69	£7.00

LOW H.P. DEPOSITS!

10% DOWN up to 48 months to pay on any items

All equipment guaranteed new and in makers' own boxes. Finest after sales services. First year parts and labour free. Money credited within 7 days if not satisfied. Majority of orders by return of post.

+ Demonstrations

SOUTHERN AUDIO SERVICES

43, High Street, Kingston-on-Thames, Surrey. Tel: 01-549 3194 (3 lines)

TV's 19" NOW £11.95

TWO YEARS' GUARANTEE ALL MODELS


405/625: 19" £25.95

FREE 23" £35.95

CATALOGUE CARR £1.95

COLOUR TV 19" £145 OR 25" £185

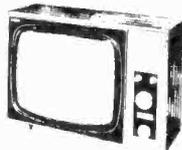LIMITED SUPPLY, REGRET PERSONAL CALLERS ONLY A SELECTION OF RECENT YEARS MODELS U.K. MANUFACTURE



TV TUBES REBUILT GUARANTEED 2 YEARS

17" and 19" £5.95; 21" and 23" £6.45 Exchange Bowls carr. 55p



COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 22p. Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.

Record Player Cabinets. £3.75p Designed for the modern auto-changer. Size 17" x 15" x 7 1/2". p.p. 55p.

Radio: £3.95 8 transistor LW/MW. Free case, battery. Post 15p. Precision Tape Motors: £1.95. 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free. Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.

Press Button VHF Tuner 75p. Brand new, takes PCF806, PCC89. Post 25p.

Valve ELL80 50p SPECIAL OFFER POTS: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg/100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12. Phone 01-478 6001-2.3

WILSIC SOUND EFFECTS KITS WAH-WAH PEDAL KIT (Illustrated)



Kit comprises a SELECTIVE AMPLIFIER MODULE KIT to convert the FOOT VOLUME CONTROL PEDAL (as photo) to Wah-Wah operation. Amplifier module £1.75, pedal unit £5.13. COMPLETE KIT £6.50 add 38p for assembly of module, but please note we cannot supply kits fully built.

REVERBERATION UNIT KIT. For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. COMPLETE KIT £9.50 (excluding case £7.50). Assembled and tested £12.50. VIBRATO UNIT KIT. Foot pedal unit with variable speed and depth controls. COMPLETE KIT £5.25.

SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)

WILSIC ELECTRONICS LTD.

6 COPLEY ROAD, DONCASTER, YORKS.

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed—build as you learn with the exciting new "Technatron" kit. No

Extras. Tools, transistors, meter etc. All supplied. You could build a radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV, ELECTRONICS, C & G, TELECOMMS ETC.

Dept. B35 Aldermaston Court, Reading RG7 4PF

Name.....

Address.....



Age

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

CQ complaint

I wish to make a complaint regarding an advertisement in your CQ column of June 72.

I supplied a S.A.E. and requested lists of issues especially Nov. 71 from a reader.

This was over a month ago and as yet have received no word from him. I think he must be collecting 3p stamps!

Would you please put an advert in your CQ column for me? I require Nov. 71 *Practical Wireless* or a copy of the article on the organ.—**M. F. Longmore**, (31 Kent Ave., Larne, Co. Antrim, N. Ireland).

Construction award

The 2nd G3XBF Constructors Award, sponsored by the Barking Radio and Electronics Society G3XBF—Affiliated to the Radio Society of Great Britain will be held on Thursday, November 9th, 1972 at the new BRES HQ: Westbury Recreation Centre, Westbury School, Ripple Road, Barking, Essex, at 7.45 pm.

Talk-in facilities are: 160m-G3XBF, on 2m—G8EAY/A, (TX 145.0). Judges: G. M. C. Stone, CEng, MIEE, MIERE, G3FZD, Council Member and v.h.f. Manager RSGB. D. A. Findlay, DFC, FCA, G3BZG, General Manager and Secretary RSGB. R. S. Hewes, G3TDR, Region 7 Representative RSGB.

There will be an award for each section and an overall winner. Each award will consist of a hand produced certificate and a worthwhile cash prize.

A film will be shown during the judging and refreshments will be available. Closing date for entries Wednesday, October 25th, 1972. Entry forms and further information may be obtained from **Alan P. Foss**, G8EAY, 73, Coolgardie Avenue, Chigwell, Essex. (01-500 6034).

VHF hope

So interesting is your August editorial on "Hope for VHF" that I could write sufficient about it to fill another!

VHF has not "caught on" for several reasons, and I will list a

few technical ones first. A v.h.f. radio costs $1\frac{1}{2}$ to 3 times as much as a comparable type for m.w. Invariably it uses at least two more transistors, which, so far as batteries are concerned, raise the quiescent current by about 10 per cent, and this is aggravated by the fact that v.h.f. oscillators are not only less stable in the face of falling voltage, but in fact actually cut out completely when the battery has still an appreciable amount of "life" in it usable on m.w. With battery manufacturers seemingly not knowing where to stop with their price-rises, and many of the receivers being of the "pocket" type, the matter speaks for itself.

But away from technical aspects, the BBC HAS something to answer for. As an example, take Sundays on Radio 4.

At 8.20 a.m., v.h.f. and m.w. part company, and unless one wants a Pakistani programme, he scraps his m.w. and goes v.h.f. But some 45 minutes later he is assailed by "Open University", so, out has to come his trusty m.w. I have always said that v.h.f. and m.w. should never part course, and neither should have Radios 1 and 2, because in the latter case the 247m. transmission was to fill up locally the areas not well served by Droitwich on 1500m. Since the service areas of the v.h.f. stations more nearly coincide with the centres of Pakistani population this would be the more logical frequency for that service, but better still these should be on the "Local" stations, since for a large part of their time they just repeat BBC programmes available at better quality on the regional stations a little along the dial. In North-Northumberland, listeners have to rely upon m.w. because v.h.f. is not reliable there, and there is no Pakistani population either!

I run a v.h.f. tuner to Mr. Cameron's excellent design a year or two ago in "P.W." and it does enable me to hear the broadcast distortion more clearly, for the programmes are either full of badly received telephoned matter, or of the "popular" type to which a bit of distortion makes little difference anyway.—**James W. Robson**, (Newcastle Upon Tyne).

Thanks

In the issue August 1972 your contributors H. Hellyer and M. Hollier continue with Part 9 of their excellent series "Transistor Circuitry for Beginners".

Their style is lucid and most readable, and in this issue we were particularly gratified to note their suggestion, page 341, "if Mullard Ltd. didn't exist, they would have had to be invented".

We especially appreciate their acknowledgement of (sic), "a direct crib from Chapter 3 of the Mullard Transistor Handbook". It is perhaps carping to indicate that reference should be made to the end of Chapter 2, and that the title used is ambiguous, in connection with other Mullard publications. For the benefit of readers wishing to supplement the information provided by your contributors the correct title should be "Transistor Audio and Radio Circuits".

L. W. Owers, Manager—Educational Service, Mullard Ltd.

VHF services

With regard to your editorial column in the August *Practical Wireless*, I would, as a newcomer to the arts of practical electronic work, like to make one comment.

Although your column makes a fair general statement, I feel that one reason for the lack of use of v.h.f. services is the fact that reception in many areas (for example the Pennine valley in which I live) is very difficult. This problem may, I suppose, be overcome by the erection of a dipole aerial but the average radio listener is still faced with the fact that very few of the popular battery operated portables are equipped to take a coaxial or twin feeder from an external aerial (idea for a future article?). The so-called "v.h.f. telescopic aerials" fitted to these sets are virtually useless in these sheltered areas.

Of course, when one writes to the BBC commenting on the problems of receiving Radio 3 on Medium Wave, they in turn refer one to the v.h.f. services! Do they realise that v.h.f. is not easily available to all?—**T. D. Jackson** (Lancashire).

practically wireless

commentary by **HENRY**

No. 92

what you mean is...

PICTURE, if you can, the tele-pundits squaring-off across the studio table, dissembling when flummoxed, leaping eagerly into the subject when a question slots into their pigeon-hole of knowledge. The scene is familiar.

But have you ever been exasperated by the overbearing type who listens with evident impatience to his opposite number's bumbblings, then thrusts in with the verbal pike off: "What you mean is . . ." and proceeds to expound his own meaning?

I think we could do with a few of those pikers in the hushed rooms and holy corners where Users' Manuals, Operating Handbooks and Service Instructions are compiled. In one classic example of the dismantling instructions for a Japanese radio-cum-portable tape recorder, a sequence of nearly a dozen operations had to be made to get the chassis from the cabinet. Following the quaint orders was bad enough, but after action 3 one reached an impasse. The next step in the sequence could only be taken if you tugged, pulled, shoved, wrenched and twisted the loudspeaker mounting. Some plastics break with a gut-rending "Crack", don't they?

The solution comes, after one failure, at about Stage 12, when



Leaping eagerly into the subject.

we are told: "Before unloosing the regulator board, take off the two clips marked A and B in diagram."

But even when meanings are explicit there can be an embarrassing contretemp. Five times in a fortnight, soon after Garrard brought out their SP25 Mark III autochanger, we had to explain patiently to new users that rejecting during Manual Play required one to flick the lever to Auto and then bring it back to Manual. If you left it in the Auto position, the pickup arm would reject—sure—but cycling commenced and the record would be replayed in the selected size position. The instructions are there, plainly enough on Page Nine of the handbook issued with the gramophone deck, but who reads handbooks?

Not so good are those handbooks, usually printed in several expensive colours and all sorts of languages from Serbo-Croat to Sanskrit, which have such convoluted language that the English version is as ambiguous as the hieroglyphics.

Henry has whiled away many hours cross-referencing the English with adjacent columns of French and German, which deluded tutors were under the impression he had learned in his younger days.

Instructions in some strange Scandinavian tongue translate curiously if one attempts to be literal. Take the phrase: "Nun das Stromkabel in eine Steckdose anschliessen." That comes near the beginning of the Bedienungsanleitung (which everybody knows is the manual de Instrucciones) for the Sanyo STD-100 stereo cassette recorder.

Well, if we have to cope with the Common Market, let's have a go. Looks like a tale about this nun who climbs some mountain to get more living room. And lower down we see . . ." *reglers so einstellen, dass optimale Aufnahmequalität erzielt wird.*" That one



Who reads handbooks?




is obvious: "if you've go to instal it regularly, cheer up and do not use that naughty word."

It becomes quite deflating to learn that the first phrase tells you to plug the power cord into an a.c. outlet, while the second is about adjusting the input level for optimum recording quality.

The section in Japanese was most intriguing, especially as English words like ON, OFF and EJECT larded the text like plums in a pudding.

Henry has campaigned for years to make suppliers add at least a circuit diagram to their equipment, and to put the specifications where they can be seen. In the June issue of *Hi-Fi News*, the B & O publicity boys mention that they always include a circuit diagram in a cute little pocket inside each piece of their equipment. In the same issue, a reader tells us he could not get a service manual with his tape recorder. He received, instead, a courteous letter pointing out that it was not Company policy to supply service manuals to the consumer public.

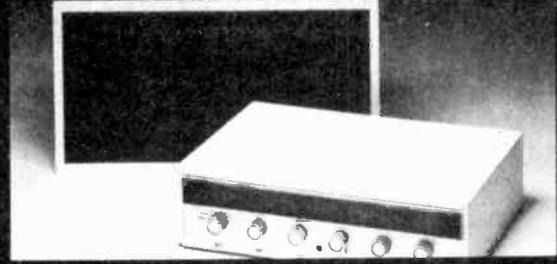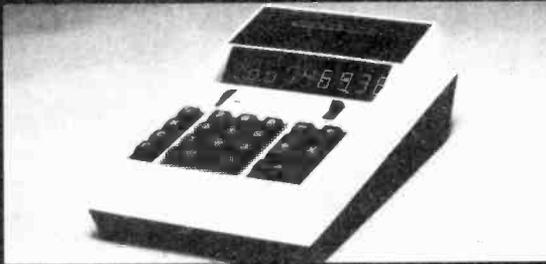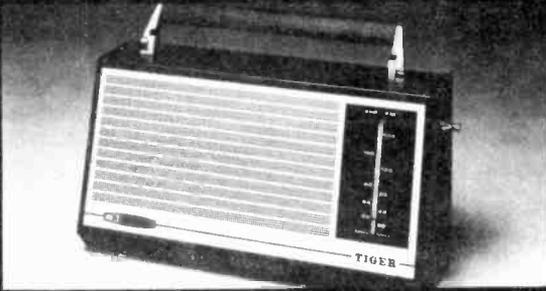He answers that he, too, has a policy, which stated quite simply says: "No Manual—No Machine." Henry feels that more people should wield that pike.



You can make any of these just as well as we can. And save yourself money into the bargain.

We at Heathkit do all the donkey-work – the rest is up to you. If you're handy with a soldering iron, pliers and screwdrivers you'll have no difficulty putting the bits and pieces together in a few hours. Even if you're not used to soldering you can still do it. Because we tell you how in an introductory booklet. And we give you bits and pieces to practise on before you take the plunge

Just think what you could make yourself this weekend.

How about building the world's first electronic calculator kit? It's easier than you think. The new Heathkit IC-2008 desk-top calculator adds, subtracts, multiplies and divides up to eight digits. Electronically you can multiply or divide a series of numbers by a pre-selected figure; fix the decimal point in one of eight positions or in a floating decimal mode. And a ninth display tube indicates overflow. It's smart.

highly sophisticated – and shows a big saving over the ready-built price.

Or you could make yourself an IB-1101 frequency counter! New from Heathkit, it has a range from 1 Hz to over 100 MHz – and an input frequency that'll accept levels from below 50 mV to over 2000V. The decimal point is automatically placed with range selection. A truly professional piece of equipment.

Maybe radio is more in your line. Well, you could make our new version of the successful Tiger transistor portable – the Tiger FM. Designed specifically for the high-quality sound of VHF broadcasts (BBC radio 2, 3, 4 and local stations), it's particularly easy to build. Ideal for beginners.

And if you're bored with teak or walnut finishes on audio equipment, you'll be glad to know that we do Hi Fi in colour. You can choose from snow white or sunshine orange, besides the usual teak or walnut. That goes

for our AA14 30 watt stereo amp, AR14 tuner/amp, and Trent speakers.

If you want a demonstration of any Heathkit equipment we'll be pleased to see you at either of our showrooms – 233 Tottenham Court Road, London W.1 (open 9-6, six days a week), and 17-18 St. Martin's House, Bull Ring, Birmingham (open Tues-Sat, 9-6).

Like we said, you can make them all as well as we can. But if, by any remote chance, you do manage to go wrong with your assembly, we'll put you right again. In fact, that's a firm guarantee.

You simply can't fail.

Want to know more? Mail the coupon for our free catalogue – it's packed with Heathkit goodies.



Please send me the FREE 1972 Heathkit catalogue.

Name

Address

HEATH (Gloucester) Ltd., Gloucester GL2 6EE.

PW 10/72

HEATHKIT

Schlumberger

We won't let you fail.

POWERTRAN ELECTRONICS

APPOINTED DISTRIBUTORS

FOR THE

'TEXAN'


TEXAS INSTRUMENTS DESIGNED

& APPROVED FULL KIT



Specialists in high quality kits for high quality audio equipment. Previously concentrating on advanced Wireless World designs (pre-amps, power amplifiers from 10 to 100 watts, power supplies, tape recorder) we now proudly add the Practical Wireless TEXAN to our range.

SLIDER POTENTIOMETERS

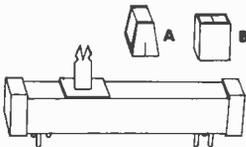

- Single: log or lin 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M **35p**
- Dual: log or lin 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M **55p**
- Balance: special dual track 10K **60p**
Black/Chrome knob: type A or B **12p**
- ### 23mm CARBON POTENTIOMETERS
- Single: lin 1K to 2M2 **12p**
log 4K7 to 2M2 **12p**
- Dual: lin or log 4K7 to 2M2 **35p**
Balance: 10K log/A log **40p**
- Balance: Purpose designed; better than Log/A Log. No attenuation at midpoint. 22K only **45p**

£28.50 post (UK) 45p

INCLUDES TEAK CASE

SEMICONDUCTORS

2N699	0.30	40361	0.40	MPSA66	0.40
2N1613	0.20	40362	0.45	MPS905	0.20
2N1711	0.25	BC107	0.08	WPSU05	0.60
2N2924G	0.10	BC108	0.08	MPSU55	0.70
2N3053	0.20	BC109	0.08	SN72741P	0.95
2N3055	0.45	BC125	0.15	SN72748P	0.95
2N3442	1.20	BC126	0.15	THB11	1.10
2N3702	0.11	BC182K	0.10	TIP29A	0.50
2N3703	0.10	BC212K	0.12	TIP30A	0.60
2N3704	0.10	BC182L	0.10	TIP31A	0.60
2N3705	0.10	BC184L	0.11	TIP32A	0.70
2N3706	0.09	BC212L	0.12	TIP33A	1.00
2N3707	0.10	BC214L	0.14	TIP34A	1.50
2N3708	0.07	BF257	0.55	TIP41A	0.74
2N3709	0.09	BF259	0.60	TIP42A	0.90
2N3710	0.09	BFX29	0.30	TIP3055	0.40
2N3711	0.09	BFY50	0.20	1808T20	0.50
2N3819	0.23	MJ481	1.20	1840K20	1.40
2N3904	0.17	MJ491	1.30	IN914	0.07
2N3906	0.20	MJE521	0.70	IN916	0.07
2N4058	0.12	MPSA05	0.30	1544	0.05
2N4062	0.11	MPSA12	0.55	15920	0.10
2N4302	0.60	MPSA14	0.35	153062	0.25
2N4357	0.30	MPSA35	0.35	5B05	1.20
2N5830	0.30	MPSA65	0.35		

THYRISTORS

PIV	1A	3A	7A	16A	1A	1.5A	3A
50	25p	27p	45p	60p	7p	8p	19p
100	27p	30p	50p	65p	7p	9p	20p
200	35p	37p	55p	75p	8p	10p	22p
300	40p	4.5p	60p	85p	9p	11p	25p
400	45p	50p	65p	90p	10p	12p	26p

RECTIFIERS

Components available in separate packs
Eg.
Resistors and capacitors £ 3.70
Switches and controls £ 2.35
Fibre Glass PCB £ 2.50
Semiconductors £ 8.35
For other parts and full specification please see our free list.

FOR FREE ILLUSTRATED LIST PLEASE WRITE TO

DEPT. D

22 THE PANTILES BEXLEYHEATH KENT

UK POST FREE EXCEPT WHERE STATED OVERSEAS AT COST
MAIL ORDER ONLY

THE ULTIMATE IN COMMUNICATIONS RECEIVERS

WORLD MASTER 8 WAVE BANDS

+ WORLD MAP & TIME ZONE DIAL

Brings INSTANT WORLD-WIDE RECEPTION at the press of a button. Sensational scoop purchase of this just-released model enables us to offer a truly advanced communications receiver at a previously unheard of price (similar models can cost £190 or more). The 8 WAVEBANDS enables you to cover the world at the press of a button. You might even pick up a world scoop on this world-wide receiver! As well as all the usual BBC Programmes you can pick up Local Radio Stations (including new stations yet to be introduced). *Pop Pirates. *Aircraft (control to pilot—pilot to control). *Shipping. *Taxi. *RAC. *AA. *Fire and Ambulances; *Continental and 100s more too numerous to list, from Australia, Africa, America, India, Europe. You'll get your hour of enjoyable listening on this superb receiver 24 hours a day—7 days a week. A complete hobby in itself. Enjoy the exciting cross-talk between control towers and airline pilots—listen to the progress of an ambulance on its way to an accident—hear the deep-sea trawler captain's ship-to-ship and ship-to-shore conversations. PLUS many more exciting and absorbing Public Service Band transmissions we are not allowed to mention. This set has been manufactured by one of the most advanced companies in radio and electronic communications and carries their FULL WRITTEN GUARANTEE. Attractively finished in Leatherette and stainless steel to add quality and distinction to any living-room. Completely portable using standard batteries (obtainable anywhere)—or can be plugged directly into mains. 14 Transistors, 9 diodes, 1 thermistor, internal ferrite rod antenna and external Telescopic Antenna. Tone, volume and tuning controls. Very latest keyboard push-button waveband selector. Dial light (analsin use in darkness). Special WORLD-WIDE DIAL and WORLD MAP enables you to tell the correct time in any country of the world (essential for world listening). Hi-fidelity ear-phone automatically cuts out main speaker when in use. Freq. Long Wave 150-350 Kcs. Medium 535-1605 Kcs. Marine 1.6-4.5 Mcs. Short Wave 4-12 Mcs. Short Wave 12-24 Mcs. FM/VHF 88-108 Mcs. AIRCRAFT 108-135 Mcs. PUBLIC SERVICE BANDS 135-174 Mcs.



CASH PRICE **£28.50**

+ 50p p. & p. or sent for £7.50 deposit and 50p. p & p and 6 monthly payments of £4.40 (Total £33.90)

COMPARE OUR PRICES

Speaker Bargains

E.M.I. 13 x 8 in 3, 8 & 15 OHMS	
PLAIN	£2.00
WITH TWEETER	£2.25
TWIN TWEETER	£3.50
8 x 5 in 3, 8 & 15 OHMS	£1.30
CERAMIC MAGNET	£2.25
7 x 4 in 3 & 8 OHMS	£1.05
FANE 8" OHM DUAL CONE	£2.50
CELESTION 8" 15 OHM	£2.00
GOODMANS 10 x 8 3 OHM	£1.75
ADASTRA TOP 20 12" 25 WATT 8 or 15 OHM	£5.50
BAKER GROUP 25 12" 25 WATT 8 or 15 OHM	£5.50
2 1/2" 40 OHM	50
KIT-FORM CABINETS TEAK (17" x 10" x 7") with a 13 x 8 or 8" CUT OUT	£2.75
(PLEASE SPECIFY CUT OUT)	
POSTAGE 25p per SPEAKER	

Microphone Bargains

MIC45 "ACOS" metal case, crystal hand	95
CM 20 Crystal Hand	45
DX168 Dynamic Stick	90
DX143 Dynamic, cassette-type stick	£1.00
MIC60 "ACOS" stick crystal	£1.00
CM70 PLANET stick metal, switch crystal	£1.45
OM180 Dynamic uni-dir, ball metal	£3.75
UD130 50K/600 OHM uni-dir, ball metal	£4.50
TW209 LESSON DUAL IMP	£5.75
GIUITAR MIKE	45
LAPEL TYPE, crystal	60
POSTAGE 17p each.	

Multitesters

1,000 OHMS/VOLTS	£2.50
2,000 OHMS/VOLTS	£2.75
10,000 OHMS/VOLTS	£5.00
50,000 OHMS/VOLTS	£10.00
100,000 OHMS/VOLTS WITH TRANSISTOR TESTER	£15.00
POSTAGE 17p each.	

Stylis

SAPPHIRE — TC8LP, GC3, GC2, GP65/67, BF40LP, STUDIO LP	20
S/OIAMOND as above	40
D/OIAMOND all popular types	£1.45
POSTAGE 3p per stylus.	

Cartridges with standard fittings & stylis

ACOS GP91/SC STEREO COMPATIBLE	£1.05
ACOS GP94 STEREO CER.	£1.90
ACOS GP95 STEREO CRYST.	£1.35
9THAC SONOTONE STEREO CERAMIC (DIAMOND)	£2.00
ACOS GP67/2C MONO CRYST.	85
ACOS GP101 COMP. CRYST.	75
POSTAGE 05p per CARTRIDGE	

Panel Meters

2" SQ.	£1.50
0-500ma, 0-1ma, 0-10ma, 0-100ma	
0-500ma, 'S' METER	
POSTAGE 17p each.	

Cassettes (Low Noise)

C60	40p	C120	80p
C90	60p		
POSTAGE 3p each.			

Tapes — "MYLAR" base finest quality British made.

5" 600 ft 36p	5 1/2" 1800 ft 85p
5" 900 ft 45p	7" 1200 ft 55p
5" 1200 ft 60p	7" 1800 ft 80p
5 1/2" 900 ft 40p	7" 2400 ft 95p
5 1/2" 1200 ft 55p	
POSTAGE 7p each.	

SEND 25p FOR COMPLETE CATALOGUE

RIVERSDALE ELECTRONICS

Mail Order Department, P.O. Box 470, Manchester M60 4BU.

ALL OUR MERCHANDISE IS FULLY GUARANTEED

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

At this time of year the nights are closing in and unless something miraculous occurs, winter will follow shortly. As a nation we are supposed to ignore that season until it actually happens; iced points on the railways and the resulting chaos is just one example. However *Take 20* is going to set an example to the nation with this month's circuit—a Frost Alarm. You may think that such a project has few uses, but think about it. Freezing pipes in the loft can be prevented, the greenhouse heating can be turned on and the fruit growers can take the necessary precautions if you are given some warning that the air temperature is approaching 0°C. The circuit falls within our £1 limit but if it is to become a permanent fixture, rather than built up for interest, a mains operated power supply must be used, batteries are quite unsuitable unless you are prepared to keep switching the unit on and off.

We are calling the circuit a Frost Alarm but it can be made to operate over a wide range of temperatures, it is simply a matter of adjustment. The alarm device is a bulb which will light as soon as the temperature falls below the preset level. The warning device can be situated in any convenient position where it will be seen easily with the temperature sensor up to 100 yards away. This is the main advantage; you don't have to go out in the cold to look at a barely readable mercury thermometer.

The Circuit

The circuit of the frost alarm is shown in Fig. 1. The temperature sensing device is a thermistor. This is a device whose ohmic resistance varies with the temperature. At 25°C the resistance of the one specified is about 4.7kΩ. Above this the resistance falls to a low level but below it the resistance increases. On the one used for the prototype this was measured as 8kΩ at 0°C.

The thermistor is wired in series with a variable resistor, VR1, and the junction of these is taken to the Schmitt Trigger circuit which comprises Tr1 and Tr2. The voltage at the junction of TH1 and VR1 will depend on two factors; the temperature and the setting of VR1. We can easily arrange for this voltage to be just sufficient to bias Tr1 into conduction and set VR1 so that when the temperature falls, and TH1 increases in value, that Tr1 will have insufficient voltage at the base to maintain conduction.

While Tr1 is switched on, Tr2 will be held switched off since the saturation voltage (which is that voltage between the emitter and the collector when the transistor is fully conducting) is below that necessary to bring Tr2 into conduction. The connection of these two transistors is such that when one is conducting, the other is off and vice versa. The switching action is very rapid and very positive. We have explained

No. 41 FROST ALARM

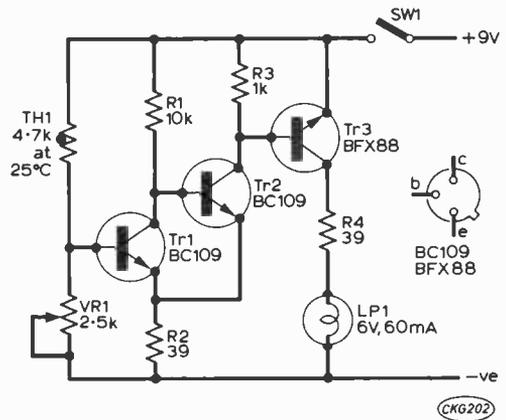


Fig. 1: The circuit of the Frost Alarm.

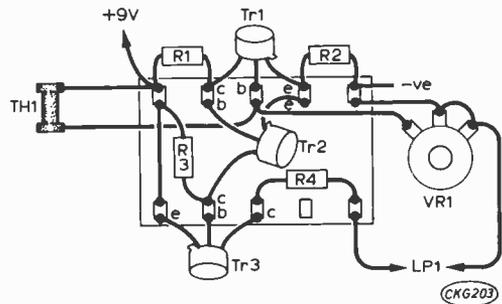


Fig. 2: Suggested component layout on tag-board.

★ components list

R1	10kΩ 5% ½W	1p
R2	39Ω 5% ½W	1p
R3	1kΩ 5% ½W	1p
R4	39Ω 5% ½W	1p
VR1	2.5kΩ lin. pot	12p
TH1	VA1066S, 4.7kΩ thermistor (Henry's Radio)	20p
Tr1	BC109	10p
Tr2	BC109	10p
Tr3	BFX88	20p
LP1	6V, 60mA bulb	5p
Bulbholder		11p
SW1	On-off switch	7p
		<hr/> 99p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

the operation of this circuit before in this series in more detail. When Tr2 is off there will be no voltage drop across R3 and so Tr3 will be off. When Tr2 is on, this will turn on Tr3 and current will pass through the bulb. The reason for R4 is only because 9V bulbs

do not seem widely available, unlike 6V versions, and this resistor prevents the bulb being overloaded. A switch is shown only for convenience. If a mains operated power supply is used, as it should be, the switch should be on the input to this. As we mentioned before the thermistor can be connected to the circuit by a long length of wire, as the resistance of this will be negligible compared to that of the device itself.

Calibration

It is not too difficult to calibrate VR1. Put the thermistor with its leads into a small plastic bag and put this into a bowl of water and melting ice. The temperature among the melting ice will be 0°C but this may mean that the warning will come too late. If a decent sized bowl is used, it is better to calibrate using the water temperature at the bottom of the bowl, here the temperature will be 4°C. Once calibrated the unit can be tested by putting it into a fridge, checking the switch-on temperature against a mercury thermometer. The inside of a fridge should be just above freezing, say 3°C or so.

A suggested layout on a small tagboard is shown in Fig. 2.



Practical Wireless Designer's Trophy

1972

To encourage new authors, entries for the 1972 Trophy will be restricted to readers who have not previously had an article published in PW. This leaves the field wide open for those wanting to try their hand at writing technical constructional articles. Contestants will not be in competition with well-known authors, only with other newcomers, so the cup can only be won by a new writer. **It Could Be You.**

TURN YOUR CONSTRUCTIONAL PROJECT INTO CASH—AND MAYBE WIN THE CUP! RULES

CO! CO! CO! CO! CO! CO! CO!

ISSUES WANTED

...November and December (and October) 1971 issues of P.W.—P. G. Quatermain, 138 Three Bridges Road, Crawley, Sussex, RH10 1JP.
 ...August 1967 to January 1968 issues of P.W.—M. Shipton, 48 Clockhouse Lane Collier Row, Romford, Essex.
 ...P.W. May 1968, also RX/TX not Ex-army.—C. Boswell, 120 Abergele Road, Colwyn Bay, Denbighshire.
 ...P.W. June 1969 or copy of article on the P.W. 12 Amplifier Part 3 Included in this edition. Will buy or borrow.—Nick Salmon, 20 Bridge Street, Rugby, Warks.
 ...issues of P.W. containing the Hawaiian Guitar article.—H. Powers, Burbage Hinckley, Leicestershire.
 ...April 1954 Practical Television.—P. Brocombe, 2 Brede Valley View, Icklesham, Sussex.
 ...issue containing gen on P.W. Multimeter.—S. C. Burns, Worley, Wors.
 ...P.W. August 1971.—W. Heasman, 20 Myrtle Crescent, Slough, Bucks, SL2 5BB.
 ...back numbers of P.W. since August 1971.—Q4132503 FS Sebbage, W. R., Sergeants Mess, R.A.F. Laarbruch, BFPO 43.
 ...issue of P.W. for May and June 1971 on payment.—G. Probert, 54 Replingham Road, Southfields, London, S.W.18.
 ...June 1965 issue of P.W.—A. Hughes, 16 Triton Fields, Kennington, Ashford, Kent.
 ...August 1971 of P.W.—R. Green, 22 Branksome Close, Norwich, Norfolk, NOR 51D.
 ...copy of P.W. for November 1970. Good price paid.—B. Thomas, 48 Musgrove View, Leeds, LS13 2QN.
 ...buy or loan Aug. 1971 P.W.—A. C. Wray, 12 Lansdowne Square, Rodwell, Weymouth, Dorset.
 ...December 1968 and January 1969 issues of Television.—H. Gillott, 5 The Close, Birchanger Road, S.E. 25 5BW.
 ...Practical Wireless Issues Jan. to July (Incl.) 1971. In exchange for Israeli mint stamps, postcards or international coupons as requested.—Z. B. Sadeh, P.O. Box 128, Dimona, Israel.
 ...P.W. Feb. 1972, March 1972.—E. Marsh, 118 Knightsbridge Road, Solihull, Warwickshire.
 ...P.W. Feb. 1972. I will photostat required article (oscilloscope) and return, with postage.—J. Badger, 8 Hunger Hill Road, Whiston, Rotherham, S60 4BA.
 ...P.W. November 1970 and October 1970.—M. D. Jawle, Laxmi Nivas 77/79, Mughbat Lane, Girgaum Bombay 4, India.
 ...P.W. Vol. 45 No. 7 for data on Pedal steel Guitar.—A. Nicholson, 7 Blawarthill Street, Glasgow, G14 0EB.
 ...P.W. November 1970.—J. F. Glavin, 3 North Lodge, Northlands, Salthill, Chichester, Sussex.
 ...P.W. Feb. 1971 issue or the circuit diagram for P.W. Stereo tape recorder.—C. Daniels, 22 Hadfield Street, Stabrook Georgetown, Cooperative Republic of Guyana South America.
 ...P.W. Feb. 1972 (first part of the transistorised Oscilloscope).—D. R. Gardiner, 12 Lambley Lane, Burton Joyce, Nottingham, NG14 5BG.
 ...Jan./Feb./March and August 1970 issues P.W.—A. W. Please state price.—C. J. Toplis, 14 Beech Avenue, Darwen, Lancs.
 ...P.W. Dec. 1971 will pay full price.—C. Jones, 45 Currock Park Avenue, Carlisle, CA2 4DJ.
 ...blueprint published in Practical Wireless issue November 1964. The Autocrat Car Radio.—N. W. Davidson, "Church View", Upper Ballinderry, Co. Antrim, N. Ireland.
 ...P.W. Jan. and Feb. 1972.—A. M. Denning, 6 Reginald Road, Northwood, Middx.
 ...September 1971 to January 1972 issues of P.W.—A. Conble, 1 Courtral Avenue, Helensburgh, Dumbartonshire.
 ...Television Nov. 1970 (Murphy Conversion Plinth).—R. Malcolm, 66 Low Garth, Kendal.
 ...1958-1971 P.W. 1969-1971 P/Electronics. Face Value Plus postage.—N. Hughes, 24 Peter St., Eccles, Manchester, M30 0JF.
 ...P.W. for May 1971 which includes Station focus six.—S. Vinden, Burcott Hall, Forn, Wing, Leighton Buzzard, Beds. LU7 0JP.
 ...P.W. for Sept. 1964, Jan. to May inclusive for 1968, January 1967, Aug. 1967, Dec. 1967, April 1968, June 1968, Nov. 1968, April 1969, May 1969, June 1969, July 1969, Aug. 1969, Sept. 1969, May 1970, Dec. 1970, Feb. 1971, July 1971, Aug. 1971, Oct. 1971—D. G. Harrington, Carbrae, 25 Poynter Road, Bush Hill Park, Enfield, Middlesex.
 ...P.W. January and February 1972 issues wanted.—D. Kathrecha, 405 Sydenham Road, Croydon, Surrey.

1. The winning entry will be chosen by a panel of judges from among articles published in issues of PW dated September 1972 to August 1973 inclusive. The Editor's decision on all matters arising will be final.
2. The winner of the competition will receive and retain outright the PW Designer's Trophy 1972. Other prizes will be awarded to the best runners-up. Articles will be paid for shortly after publication.
3. The competition is open only to authors who have not previously had any work published in PW.
4. Articles submitted for the competition should conform to the general style of material published in PW and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
5. Articles should, preferably, be typed using double spacing, leaving wide margins, on one side only of each sheet. Circuit diagrams and any other drawings must be separate and numbered to agree with the text. Author's roughs must be clear enough to permit re-drawing. Components list must also be separate and laid out to the standard PW format.
6. Photographs of the equipment are desirable and should be in black and white, sharp and clear. Photographs may be identified by sticking a label on the reverse instead of writing on the back of the photograph itself.
7. Components used in the design must be readily available from retail sources.
8. Articles should be sent to the Editor, Practical Wireless, Old Fleetway House, Farringdon Street, London, E.C.4. Authors will be advised as soon as possible of the acceptance or rejection of their articles. Equipment, the subject of an article, must not be sent to the Editor until advised to do so.
9. Employees and staff of PW are not eligible for entry to this competition.

SUBMIT YOUR ARTICLES NOW

IN NEXT MONTH'S

PRACTICAL WIRELESS

EXTRA THE OF hi-fi abc SUPPLEMENT

The prospective buyer of hi-fi equipment can rightly feel a little bemused as he attempts to make sense of the welter of technical literature showered on him by manufacturers. With the audio 'season' now upon us we thought readers would like hi-fi expert Gordon King to explain and comment on the confusion of hi-fi jargon that now besets the man-in-the-street. Hi-fi is not cheap. A study of our ABC will ensure that your money is well spent.

8 WATT SILICON AUDIO AMPLIFIER

The falling cost of silicon output transistors now makes them an attractive alternative to germanium types. This article describes a high specification, all-silicon, 8W power amplifier with a suitable power supply. In addition a circuit is given for a matching high quality preamplifier.


SIMPLE RF SIGNAL GENERATOR

One of the problems in building test gear is range switching. This project uses plug-in coils (no switching) meaning, of course, that these are not permanently 'tied-up' in the circuit. The signal generator has wide coverage with outputs of r.f. modulated r.f. and audio.

MANY OTHER CONSTRUCTIONAL ARTICLES PLUS ALL THE REGULAR FEATURES. PRICE 20p.


ALL IN THE NOVEMBER ISSUE ON SALE 6th. OCTOBER

PW REVERBERATION UNIT

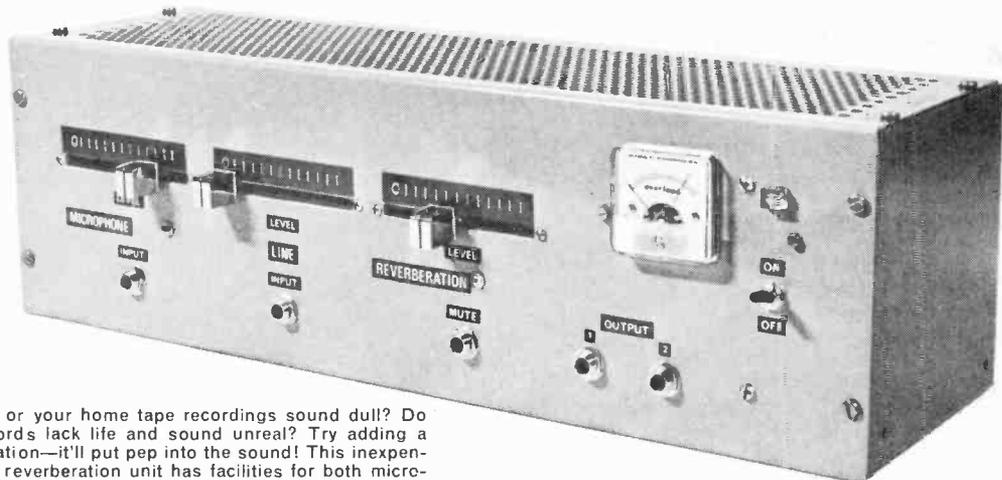

COVER PROJECT

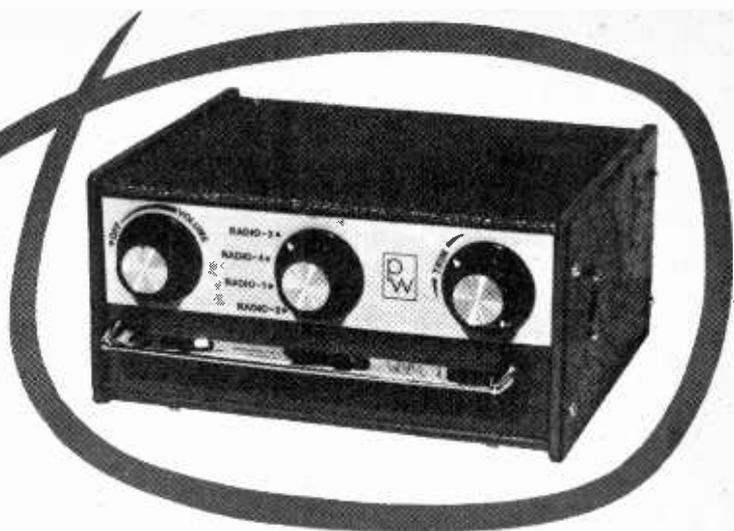Does your group or your home tape recordings sound dull? Do your old '78' records lack life and sound unreal? Try adding a touch of reverberation—it'll put pep into the sound! This inexpensive, high quality reverberation unit has facilities for both microphone and line inputs and full control is provided over the reverberation level.



R. H. LONGDEN

THE PRE-TUNED CAR/PORTABLE RADIO

FOR general use it is an advantage to have a receiver with a number of pre-selected stations available so this receiver is pre-tuned to four frequencies with provision for adding two more stations, or variable tuning, if wanted later. Three m.w. stations are available, with one l.w. station for reception of the BBC on 1500m. This is very convenient for day to day use and reception of a variety of programmes.

Reception normally is on the loudspeaker but there is provision for plugging in a personal earphone or headset, when this is more convenient for listening. A car aerial connector socket is provided, so that the receiver can be placed in a car where the use of pre-set station selection is a decided advantage. The receiver shape allows it to rest on a parcel shelf with its speaker upwards, or suspended under a shelf with the speaker downwards.

A diode output socket is fitted which is of advantage when a tuner is required for a tape recorder or other audio equipment. The receiver audio stages may then provide a signal for monitoring purposes.

The circuit is shown in Fig. 1 and is a straightforward and reliable one using easily obtained components. L1 is the ferrite aerial rod, and section S1a of the 6-way switch selects TC1, TC2, TC3 or TC4 pre-set trimmers, to give automatic tuning of the wanted stations. L1, TC4 and the parallel capacitor C1 provide l.w. reception, no additional winding being required.

Switch S1b similarly selects one of four oscillator trimmers, TC5 to TC8, and these tune the oscillator coil L3 to the required frequency. In practice, it is sometimes found that changes in battery voltage, temperature or slight changes in oscillator capacitor values, throw some pre-set stations slightly off tune. This is avoided by using a small panel control VC1, which can if necessary be adjusted to compensate. In use, the trimmers are set with VC1 half closed, then it is only necessary to adjust VC1 if signals are heard to be off-tune.

It will be noted that alignment between L1 and L3, throughout one or more fully variable tuning ranges, is not necessary, as when ordinary tuning is used. There are thus no ganging difficulties here, as it is only necessary to adjust pairs of capacitors TC1/TC5, TC2/TC6 etc., for the wanted stations.

As the ferrite rod aerial is unsatisfactory in a vehicle, coil L2 allows a car aerial to be coupled to the receiver.

The 2-stage i.f. amplifier has three single-tuned i.f.t.'s, and a.g.c. via R9 from the detector diode D1. Audio signals may be taken directly from the diode circuit by the outlet provided. VR1 is then turned to zero, unless audio signals for monitoring are wanted from the receiver.

The remaining outlet is for a personal earphone or headset, when required, inserting the plug silencing the receiver speaker. A large external speaker can also be plugged into this socket.

SWITCHED CAPACITOR ASSEMBLY

This consists of the switch, with eight pre-sets and C1, wired on a paxolin panel 4 x 2in., as in Fig 2. TC1 and TC5 are both 60pF max as are TC2 and TC6. These were set for 1214kHz, Radio 1 and

1088kHz, Radio 4. TC3 is 50-450pF, and TC7 is 20-250pF, for 647kHz, Radio 3. For 200kHz, Radio 2 TC8 is 450pF and TC4 is 1250pF with C1 1000pF in parallel.

It is unlikely that other values will be wanted for TC1 and TC5. TC2 and TC6 can be 100pF if a lower frequency than about 1088kHz is needed here, or may have small fixed capacitors in parallel. In some parts of the country Radio 2 on 200kHz may not be required when TC4 and TC8 can then be 100-400pF, for an additional m.w. station in which case C1 is omitted. Ranges with the pairs of pre-sets overlap considerably. The oscillator circuit requires less capacitance than the aerial circuit.

Washers on the switch keep leads and tags clear of the metal panel of the receiver and when the assembly is wired, it is fixed with the selector switch nut.

CIRCUIT BOARD

This is 5 x 3in., a piece 1 $\frac{3}{4}$ x 1 $\frac{3}{4}$ in. being cut out to accommodate the speaker, as in Fig. 3. Wiring will be simplified if the perforated board is cut so that there are 19 rows of holes one way, and 32 rows the other. Components can then be placed with their

wire-ends exactly as shown, and wiring will closely follow the diagram of the underside of the board.

Holes have to be drilled for L3 and the i.f.t.'s. A very small round file will be found useful to obtain a fit if any holes prove to be out of position. The identification spot on L3 falls between pins 1 and 6, and these pins should come as in Fig. 4.

Check resistor values as they are inserted, and note also the polarity of the electrolytic capacitors and diode D1. When some components are in position, turn the board over and connect as in Fig. 4, snipping off excess wire.

If each item and its leads are marked in coloured ink or pencil on the drawing as inserted and connected, it is unlikely that anything will be overlooked, or wrongly connected. It may prove helpful to use red 1mm sleeving on positive circuits, black on negative and some other colour for remaining connections.

Pieces of coloured sleeving about $\frac{3}{8}$ in. long can be put on the transistor wires. This will identify them, and also hold these at a suitable height from the board.

Transformer T1 is held by its leads plus a little adhesive. Other driver transformers of similar type will give the same results, but connections must be

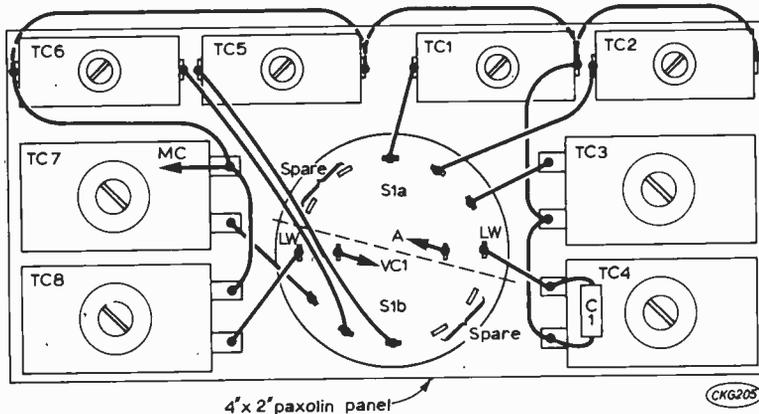
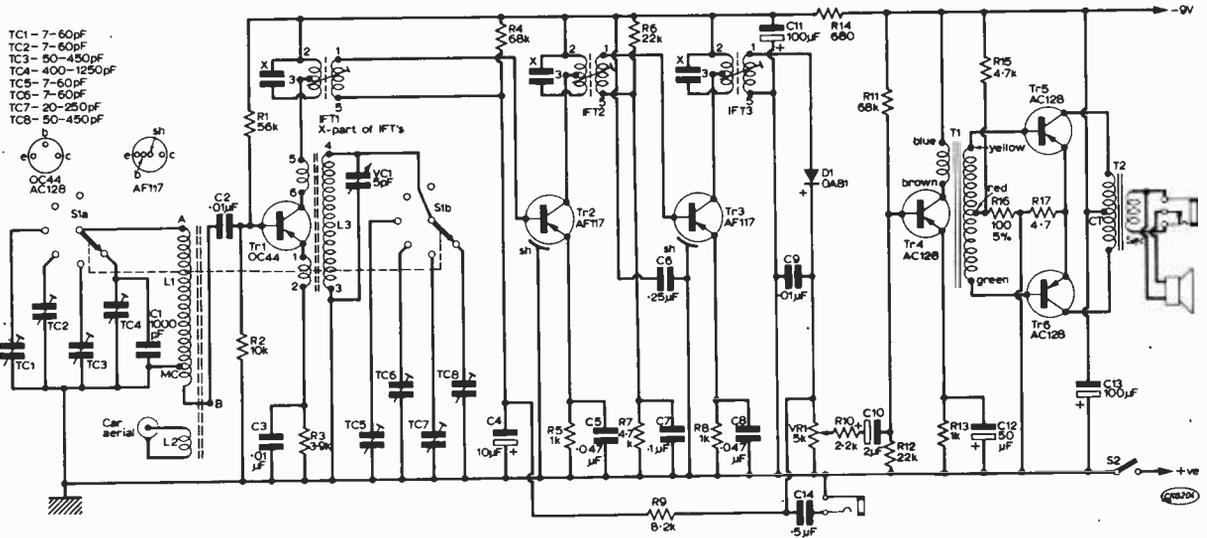


Fig. 1: above, shows the complete circuit diagram for the PW pre-tuned radio, together with the base data for the transistors. Values of pre-set trimmers TC1-8 are tabulated separately. Fig. 2: left, gives the layout of the trimmer capacitors and connections to station selector switch, all mounted on a separate paxolin panel.


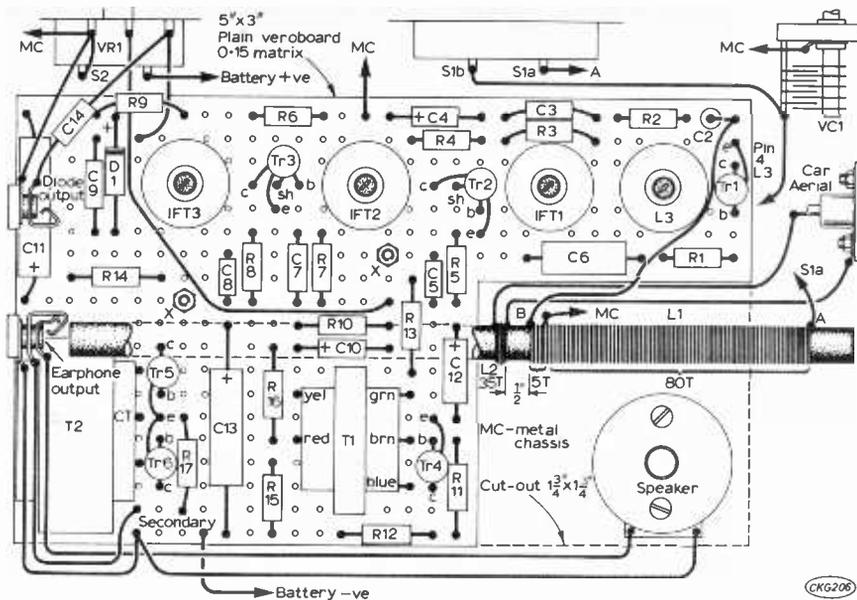


Fig. 3: above, layout of components on the front of the veroboard panel. For clarity the framework of the speaker has been omitted. Fig. 4: right, shows the component wiring on the reverse side of the board. Note polarity of electrolytic capacitors and diode D1.

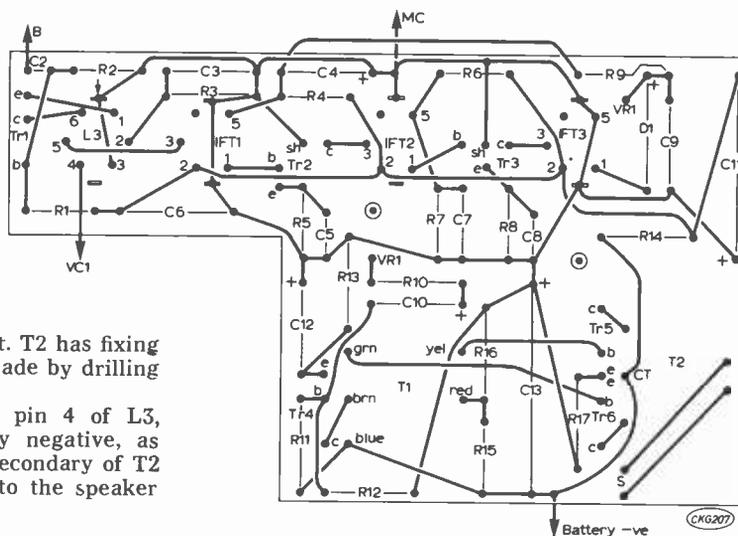The photograph at the bottom of the page is a general view inside the receiver which may be compared with Fig. 3 above.



taken from the maker's data or leaflet. T2 has fixing lugs which pass down through slots made by drilling small holes close together.

Leave flying leads from D1, R10, pin 4 of L3, earth (positive) line, C2, and battery negative, as shown in Fig. 3. Two leads from the secondary of T2 are anchored on the board and run to the speaker circuit.

FERRITE AERIAL


L1 is wound with 24 s.w.g. enamelled wire, with turns side by side, on a 6 x 3/8 in. diameter rod. Anchor the wire 1/2 in. from one end, at A, Fig. 3, with tape or adhesive. Wind on 80 turns and form loop of wire at MC. Continue for a further 5 turns in the same direction and finish off at B. A lead runs from MC on the aerial winding to MC at TC7, Fig. 2, A runs to S1a, and B to C2.

The aerial is mounted by cutting two strips of paxolin about 2 x 1/2 in. and mounting these with small brackets held under bolts that secure the speaker. A "V" is cut in the end of each strip, and the rod held by thin string round it and through small holes in the strips.

L2 is 35 turns of any thin insulated wire, placed on the rod about 1/2 in. from B.

The car aerial socket is mounted on the right side of the case, viewing the receiver from behind, Fig. 3.

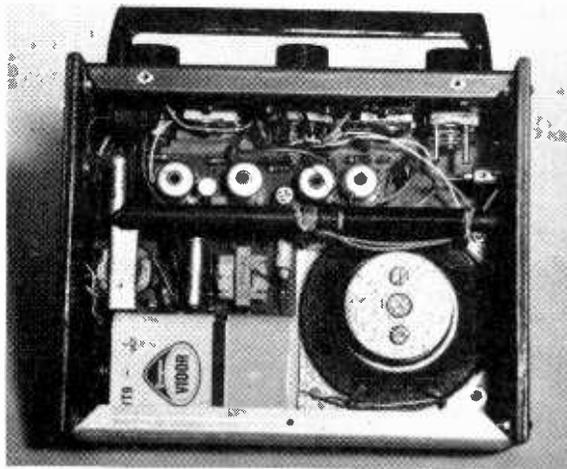The diode output socket is near VR1, on the side of the case, and C14 is for d.c. isolating purposes.



★ components list

Resistors

R1 56k Ω	R7 4.7k Ω	R13 1k Ω
R2 10k Ω	R8 1k Ω	R14 680 Ω
R3 3.9k Ω	R9 8.2k Ω	R15 4.7k Ω
R4 68k Ω	R10 2.2k Ω	R16 100 Ω 5%
R5 1k Ω	R11 68k Ω	R17 4.7 Ω
R6 22k Ω	R12 22k Ω	All 10% $\frac{1}{4}$ W
VR1 5k Ω log potentiometer with switch, S2		

Capacitors

C1 1000pF SM	C8 0.047 μ F
C2 0.01 μ F	C9 0.01 μ F
C3 0.01 μ F	C10 2 μ F 6V
C4 10 μ F 6V	C11 100 μ F 12V
C5 0.047 μ F	C12 50 μ F 6V
C6 0.25 μ F	C13 100 μ F 12V
C7 0.1 μ F	C14 0.5 μ F 150V

TC1 7-60pF	TC5 7-60pF
TC2 7-60pF	TC6 7-60pF
TC3 50-450pF	TC7 20-250pF
TC4 400-1250pF	TC8 50-450pF

All compression trimmers

VC1 5pF variable (Jackson C804)

Semiconductors

Tr1 OC44	Tr4 AC128
Tr2 AF117	Tr5 AC128
Tr3 AF117	Tr6 AC128
D1 OA81	

Miscellaneous


L1-2, see text. L3, oscillator coil (Osmor PW/01). IFT1 (Weyrad P51/1). IFT2 (Weyrad P51/2). IFT3 (Weyrad P50/3V). T1, driver transformer (Osmor QXD1). T2, output transformer 6.2:1 CT (Henry's MOP). Switch S1a-b, rotary water switch, 2 pole 6 way. Speaker 3 $\frac{1}{2}$ in. 3 Ω . Universal chassis flanged members, 7 x 3in. (2) (Home Radio). Knobs (3). Handle. Veroboard, plain, 0.15in. 5 x 3in. Coaxial aerial socket. Output jacks (2, 1 shorting type). Battery PP9 and clips.

The a.f. output jack socket is below this, and has contacts which open when the plug is inserted. It is connected as in Fig. 3, so that inserting a plug breaks the internal speaker circuit.

CABINET

The receiver can be tested out of its case, by wiring the circuit board to VR1, VC1, and S1a-b, as in Fig. 3.

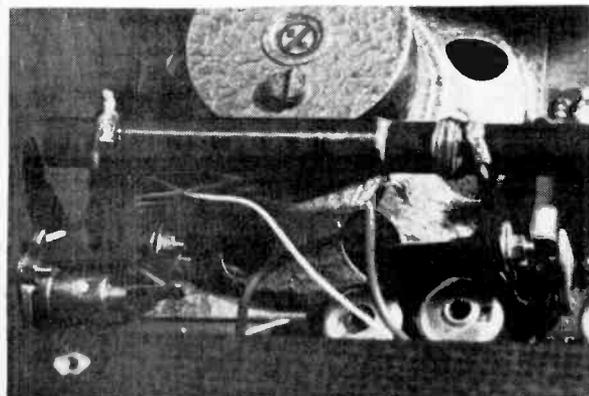Close-up shot of the method of attaching the ferrite rod to paxolin brackets.



The leads MC from VR1 and VC1 go to tags bolted to the panel flanges.

The parts of the cabinet are quite easily prepared, and holes should of course be drilled before fitting the speaker or any other items.

Top and Bottom These are 7 x 3in. flanged universal chassis members. Punch the top for VR1, S1a-b and VC1, and drill holes for the handle fixing bolts. Drill the front flanges for 6BA bolts or self-tapping screws (to secure the front) and the back flanges for self-tapping screws. Cover the top with self-adhesive material of the required colour.

Sides Each side is 3-ply, 6 $\frac{1}{8}$ x 3 $\frac{5}{8}$ in., to allow overlapping the front and back, with a small projection at the top and front. The end flanges of the top and bottom are secured to the sides by two bolts in each position.

Front and Back These are 3-ply, each 7 x 6in. Place the speaker to the bottom right, mark its fixing holes, and cut an aperture to match the speaker cone. Put the circuit board in place, and drill the two holes X-X in Fig. 3, through board and front, so that the board can later be fixed in this position.

Speaker Fitting Pass two countersunk headed 6BA bolts through from the front, to hold the speaker and also the brackets for the ferrite rod supports. Use other bolts or small wood-screws for the remaining speaker fixing holes.

Circuit Board Two countersunk bolts are put through the holes which match with X-X, and held with nuts. Extra nuts are then put on, so that when the circuit board is on these bolts, a clear space of $\frac{3}{8}$ in. or so remains between it and the case front, to clear the wiring. Nuts at X-X then hold the board in place.

Finishing A piece of fabric about 8 x 8in. of the required colour has its top edge placed between the plywood front and the top flange. Temporarily fold this fabric over the knobs, so that the screws holding the front to the flange can be tightened. Also spread Bostik 1 or other adhesive along the top edge of the front. Screw the case bottom to the front. The fabric is then drawn taut over the whole front, and is folded over and fixed with adhesive at the case bottom, and front edges. The two sides are then fitted with bolts or screws.

TUNING ADJUSTMENTS


The receiver is tested and tuned before fixing it in the case, as mentioned. If no signal generator is available, the i.f.t. cores are adjusted for best volume, any transmission being tuned in by means of a pair of trimmers. Once this has been done, the cores need no further adjustment.

When setting the trimmers for the wanted stations, deal with each pair of trimmers in turn, according to the position selected by the rotary switch. The position of the core of L3 has considerable influence on frequency, so needs to be left alone once a suitable setting has been located. VC1 is half closed while adjusting the trimmers.

Pre-sets having a range of 7-60pF will cover about 1500-1000kHz in aerial and oscillator positions. For oscillator tuning, 20-250pF trimmers will cover the remainder of the m.w. band, with 50-450pF trimmers for aerial tuning. For 200kHz, extra capacitance is necessary, up to about 450pF for oscillator, and 2,000pF for aerial circuits.

TRANSMITTER for 2 metres

PART 2 F. G. RAYER G30GR

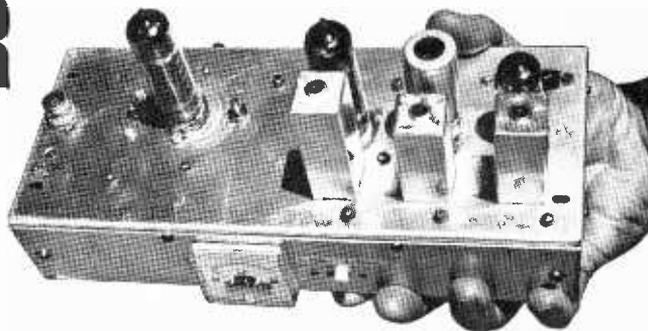

POWER SUPPLY/MODULATOR

This power-supply/modulator was made for use with the 2-metre Transmitter described last month, for which it will provide all power requirements, and adequate modulation. It is only necessary to insert an octal plug from the transmitter into the modulator. The modulator is designed to have other uses, to increase its utility, as follows:—

- (1) It will supply approximately 12 to 15W of audio for one or more speakers.
- (2) It will modulate a transmitter of up to about 25W d.c. input where the transmitter has its own power supply.
- (3) It will supply power and modulation for a transmitter in the 10W power range.
- (4) The modulator can be switched off, leaving 300V at 120mA available for, say c.w. working.
- (5) Optional choke input drops the supply to about 240V for receiving equipment and similar uses.

An h.t. current meter is included to check working of the modulator and associated equipment, and an h.t. "ON" switch allows the modulator and a transmitter used with it to be switched on and off.

CIRCUIT

The circuit is shown in Fig. 1. The first section of the double triode 12AX7 is an amplifier for the usual type of crystal microphone, with contact potential

bias from R1. Potentiometer VR1 is the audio gain or modulation level control. The triode 6C4 is a phase-splitter, driving the two 6BW6's of the output stage, V3 and V4. This is a very straightforward and troublefree circuit.

The h.t. circuit is well smoothed, by C10, C11 and L1 while R16 is a safety bleeder resistor. Some modification to working conditions can easily be made, if better suited to other associated equipment.

HT Voltage. With the values given, the h.t. supply is 300V when loaded to 120mA. If R14 and R15 are each 270Ω, the supply obtained is 280V when loaded with 100mA. A terminal board with pairs of small terminals is fitted under the chassis, so that the positive connection to C11 can be interrupted. The power supply then works as a choke input circuit, giving a reduced supply of about 240V at 120mA.

Output Stage. Operating conditions with cathode bias provide about 9 watts of audio with 250V, and about 12 watts with 285V. For modulating a transmitter the audio output required is about half the d.c. input of the transmitter, say 7 to 8 watts, for a 15 watt d.c. input. If wished, it will be found that R12 can be considerably increased in value, to reduce the current taken by the 6BW6's, without loss of audio quality.

Modulated HT. This is derived from the h.t. line and secondary of T1, the fixed ratio transformer being intended for a p.a. load of about 3 to 8kΩ.

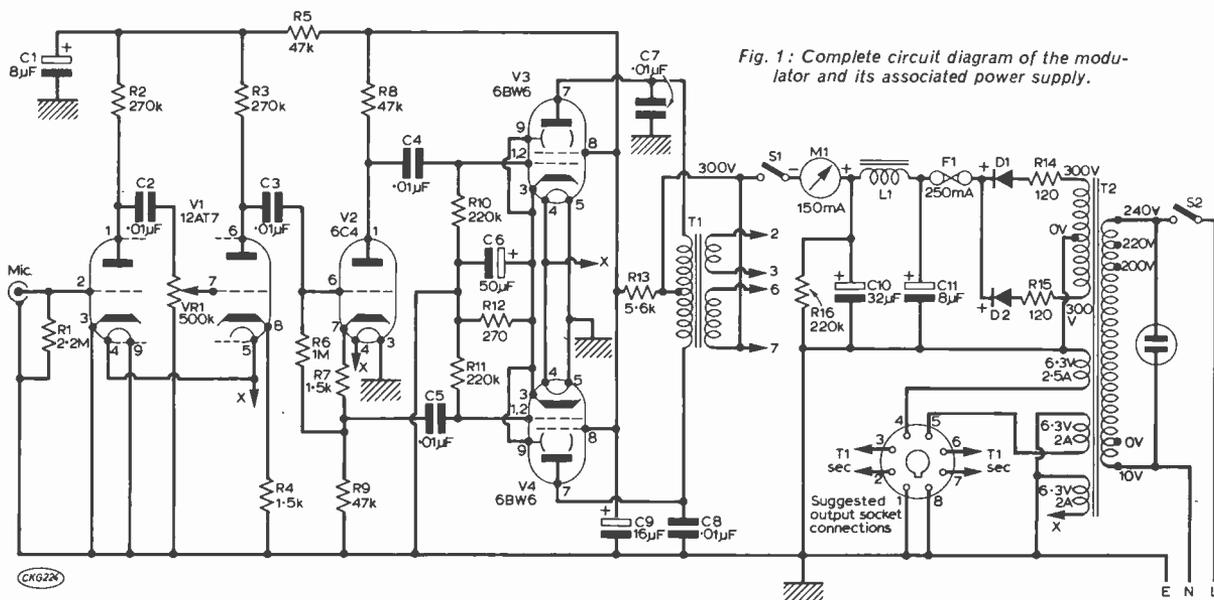


Fig. 1: Complete circuit diagram of the modulator and its associated power supply.

★ components list

Resistors

R1	2·2M Ω $\frac{1}{2}$ W 10%	R9	47k Ω $\frac{1}{2}$ W 5%
R2	270k Ω $\frac{1}{2}$ W 10%	R10	220k Ω $\frac{1}{2}$ W 5%
R3	270k Ω $\frac{1}{2}$ W 10%	R11	220k Ω $\frac{1}{2}$ W 5%
R4	1·5k Ω $\frac{1}{2}$ W 10%	R12	270 Ω 2W 10%
R5	47k Ω $\frac{1}{2}$ W 10%	R13	5·6k Ω 1W 10%
R6	1M Ω $\frac{1}{2}$ W 10%	R14	120 Ω 2W 10%
R7	1·5k Ω $\frac{1}{2}$ W 10%	R15	120 Ω 2W 10%
R8	47k Ω $\frac{1}{2}$ W 5%	R16	220k Ω 1W 10%
VR1	500k Ω log. potentiometer		

Capacitors

C1	8 μ F 450VW	C7	0·01 μ F 750VW
C2	0·01 μ F 350VW	C8	0·01 μ F 750VW
C3	0·01 μ F 350VW	C9	16 μ F 450VW
C4	0·01 μ F 350VW	C10	32 μ F 450VW
C5	0·01 μ F 350VW	C11	8 μ F 450VW
C6	50 μ F 50VW		

Valves


V1	12AT7	V3	6BW6
V2	6C4	V4	6BW6

MISCELLANEOUS

Valveholders, B9A with skirt and screening can (1), B9A plain (2) B7G with skirt and screening can (1). Meter M1, 150mA. Toggle switches (2). Microphone socket. Octal valveholder, for power outlet. Mains neon indicator. Fuse, 250mA and holder. D1/D2 silicon rectifiers, 1000 p.i.v. 1A or better. Chassis 10 x 7 x 2in. L1, about 10H at 120mA. T1, modulation transformer Type 223 (Garex, Chinnor, Oxon) T2, mains transformer to provide 300-0-300V at 120mA, 6·3V at 2·5A and 6·3V 2A twice (Douglas, Parmeko etc.).

A multi-ratio transformer may be used for other load impedances. The transmitter d.c. input is VxI, for example, 300V at 40mA or 12 watts. So the transmitter p.a. modulating impedance is approximately V/I or 300/0·04=7·5k Ω . (For the impedance calculation, remember to add the p.a. screen grid current to the p.a. anode current.)

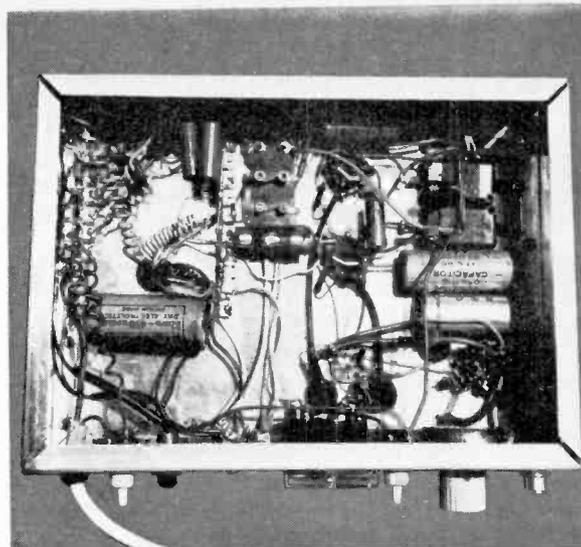Unmodulated HT. This is derived from the h.t. line, after the switch, to allow metering of the total h.t. drain, and control of h.t. to the transmitter. When using the 2-metre transmitter described, more grid current that required was available, so h.t. to the



Underneath the chassis. Suggested layout of the major components should be followed. Otherwise component positioning is not particularly critical.

earlier stages was reduced to about 260V by placing a 1k Ω /2W resistor in series with pin 7 of the octal socket, Fig.1.

CONSTRUCTION

This is on a 10 x 7 x 2in. "universal chassis" so that the front runner can be prepared for the meter, etc., before it is fixed in position. Securing bolts for the mains transformer and modulation transformer also pass through the side and back flanges for additional strength and rigidity.

In the layout adopted, the microphone socket and VR1 are to the left, adjacent to the 12AX7 holder. Grid leads here are screened, and clear of heater wiring. The 6C4 is towards the centre, and the two 6BW6's in line towards the back, with the modulation transformer to the left, and the mains transformer to the right. This leaves the front right of the chassis for the smoothing choke. The only live circuits above the chassis are leads to the choke, and these were covered with tape.

The front runner carries the following, left to right:—microphone socket, VR1, h.t. switch, meter, octal socket, AC "ON" neon indicator, AC switch, and outlet for the mains lead. Transmitters, speakers or other associated equipment employ octal plugs wired to match.

The small terminal board mentioned has two terminals wired to the modulation transformer secondary, so that it can be shorted in a few moments with a wire link for c.w. when the same equipment is also used for a.m. If frequent changes are made from c.w. to a.m. in this way a switch can be placed across the secondary.


The modulator should never be used without a load connected to the modulation transformer.

AERIALS


The output of the transmitter can be matched into any of the usual aerials requiring a low impedance feed.

A simple dipole will give good results over local

—continued on page 540

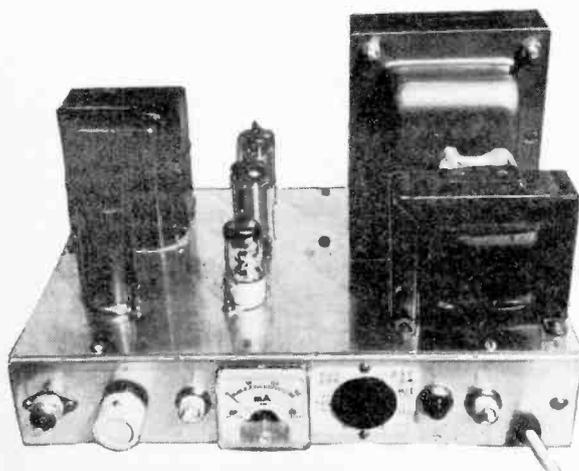

General view of the prototype chassis.

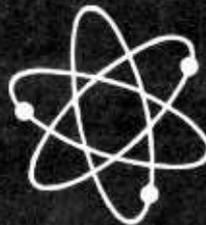

INTERCOMM CALLING SYSTEM R. A. BUTTERWORTH

MOST intercomms use three wires or a complicated relay/switch system. The system described here uses only two wires and can be adapted to any amplifier already available providing it has both input and output transformers. The two wire cables connecting the units can be any cheap twin type. A bonus in this system is that only one *Slave* unit is necessary because by paralleling several pairs at a convenient junction point, communication can be had from any two points.

In the author's arrangement the *Master* unit is usually in the shack at the bottom of the garden but the *Slave* can be in the lounge (telephone) hall (door bell) and bedroom or kitchen. By moving the units and plugging in, communication can be had between any two locations. Another bonus is that the units consume current only when communication/calling is made.

OPERATION

Figure 1 is the full schematic of the author's unit to enable the reader to follow the way in which the unit operates. With SW3 "OFF", when SW1 or SW2, which are spring loaded, are pressed it causes a loud bleep in the other unit's loudspeaker in the following manner. If the master wishes to call the remote unit, SW1 is pressed, shorting contacts 5 and 6, thus completing the positive line through the primary of the input transformer/switch/speech coil of the loudspeaker to the common line. The amplifier is in operation and at the same time the current through the primary winding induces a low frequency note in the secondary which is amplified. Contacts 2 and 3 have been connected at the same time so that the *Slave* speaker is connected to the output of the amplifier so the resultant amplified audio note (generated in the input transformer) is heard in the *Slave's* speaker. Switch 3 is now operated to await the reply, if no response, put SW3 "OFF" and press SW1 again. Once contact is established, the *Master* controls all Speak/Listen operations and switches "OFF" SW3 ready for the next call. A similar operation takes place when the *Slave* wishes to call the *Master*. The 50 μ F electrolytic blocks what would otherwise be a direct d.c. connection but not the audio signal. It will become obvious that the *Master*

can monitor the *Slave* by simply switching "ON" SW3 and so act as a baby alarm, telephone/door bell warning.

Any pair of miniature 3 Ω speakers can be used and the transformers are a pair of miniature transistor single ended output (3 Ω) types. The potentiometer VR1 is a preset skelton type, the required volume, once set, does not require further adjustment. As will be seen from Fig. 1, SW1 is a DP/DT type, SW2 is a SP/ST, and SW3 a simple ON/OFF type. Switches 1 and 2 are, of course, biased types (spring loaded); there are many varieties on the

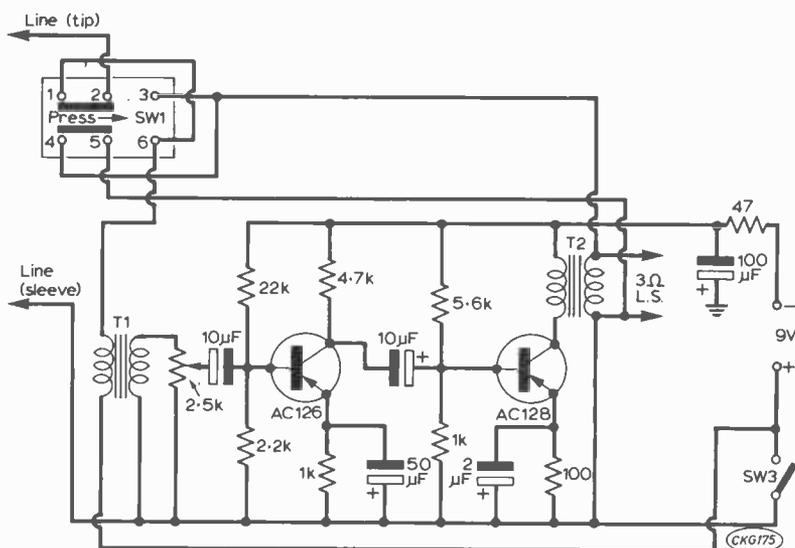


Fig. 1: The circuit of the Master unit—see text for an explanation of the unusual calling system.

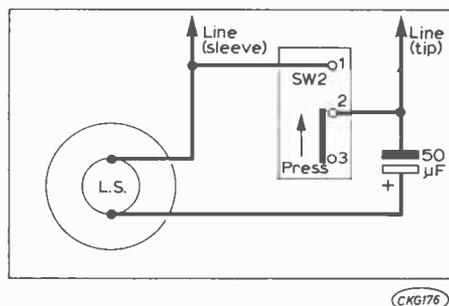


Fig. 2: The circuit of the Slave unit.

market, the most easily available is the toggle type, but the constructor has a choice.

As stated at the beginning, the main reason for offering yet another intercomm unit is the novel method of calling and the use of only two wires. This gives a versatile and flexible installation, well worth

the few hours needed to construct. It may interest the reader to know that this method of calling was developed as a result of a mistake made when making up a conventional system and to the best of the writer's knowledge has never been used before.

25W D.C. to A.C. INVERTER

S. SOAR

THE inverter described here will operate 240V 50Hz appliances of up to 25W consumption. It was originally built to drive an electric shaver or a 25W soldering iron from a car battery.

The circuit is a simple resistance coupled inverter with a square wave output of 240V 50Hz.

Considering the circuit in Fig. 1, assume that Tr1 starts to conduct; voltage induced in N1 rapidly drives Tr1 into saturation and biases Tr2 off. Flux increases in the transformer core until saturation is reached which results in a sudden rapid increase in current in Tr1. This current exceeds the current which Tr1 can supply with the available drive, Tr1, therefore, comes out of its saturated state. Voltage induced in N1 falls to zero as the transformer core saturates and Tr1 is returned to the "off" state, this ends the first half cycle. Flux collapse in the transformer core results in an induced voltage in such a direction as to turn Tr2 on so initiating the start of the second half cycle.

★ components list

R1, R2	100Ω, 2W
Tr1, Tr2	OC35
Fuse	5 Amps
Transformer:	Type P2/2 available from Magtor Limited, 68 Dale Street, Manchester 1.

Construction is straightforward and operation is little affected by position of components. However, it is advisable to keep interconnections as short as possible to reduce inductance.

Since transistors Tr1 and Tr2 are not operating at maximum load, large heat-sinks are not necessary and the entire unit can be inserted in a metal case measuring only 3in x 3in x 4in. Care must be taken to ensure that the collectors of both transistors are isolated from each other, this can most easily be done by mounting these in the side of the case on insulating washers, alternatively a plastic case can be used.

If a d.c. output is required, this can be easily obtained by connecting a bridge rectifier to the secondary, since the output is square wave, smoothing represents no problem and a capacitor of 2μF will suffice for most requirements.

It is not recommended that half wave rectification be used as this will tend to saturate the transformer core in one polarity only and this may cause malfunction of the inverter.

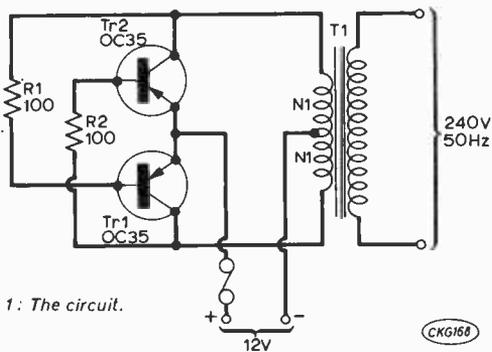


Fig. 1: The circuit.

Performance

No Load Input current 700mA (8.4W)
Load 15W Input current 2.0A, efficiency 62.5%
Load 25W	... Input current 2.8A, efficiency 75%

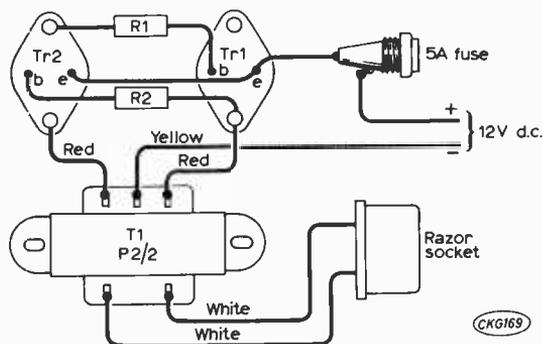



Fig. 2: Wiring of 25W inverter

MAXWELL

by G8DSH



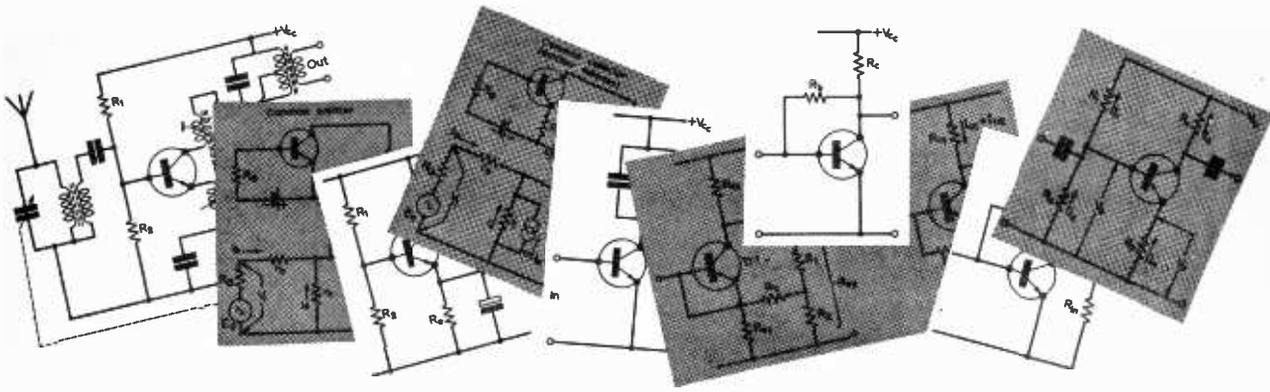"—about eighty turns tapped ten turns up, please!"



TRANSISTOR CIRCUITRY for beginners

H.W. HELLYER & MICHAEL HOLLIER

PART 11

A breather

Before we can progress with our look at transistor circuits, we must halt, survey the battlefield of some of our illusions, and reconnoitre the lines of our next advance.

In other words, having taken single stage circuitry and combinations of stages, we must now consider the effect of the sub-circuits on those before and those after. The more we delve into transistor circuitry, the less we can regard each "block" as an entity unto itself. Black boxes, so beloved of the academic, are seldom darker than a shade of mottled grey when we come to put them into practice.

One such circuit concept, that seems primarily to make hay of basic theory, is the so-called "virtual earth".

We have reached a stage in our talk about circuits where we can see, without the aid of equivalent transistor circuits or little arrows showing electron flow, that the d.c. conditions and the a.c. conditions in any given configuration will be different, though interdependent.

As an example, consider the plain problem of decoupling. In your humble transistor radio you have a perfect example. As you bothered your neighbours on the beach with Bach's Partita and Fugue while all they wanted was to be Woganised (how I've longed to do that!) the signal current in the power supply circuits were being bypassed from the battery by a relatively hefty electrolytic capacitor. Fig. 55 illustrates this, and shows that the h.t. line

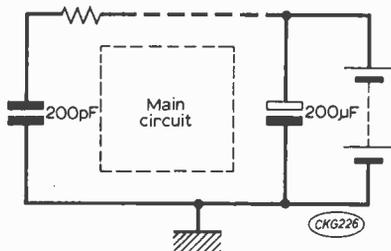


Fig. 55: Simple decoupling. The capacitors represent a virtual short-circuit to signal currents.

is, as far as the a.c. signals are concerned, at the same potential as the chassis.

From there, it is a small step to think in terms of impedance and frequency rather than resistance and direct current when considering a signal-handling circuit.

Why, for instance, do we need that hefty capacitor back there, across the supply, when the decoupling of the tuner section is efficiently performed by a fraction of a microfarad? The answer lies in the frequency. At the supply, signal currents at audio frequencies are having to be bypassed, and 2000µF to a 100Hz signal is an impedance (a.c. resistance) of 0.81ohm.

At the front end, taking the FM radio that you, of course, will be using, despite the BBC's recent retrograde step to duplicate local radio on medium waves, the frequency you want to bypass is somewhere near a million times as great and so the capacitance need only be a millionth of the former, that is 2 picofarad against 2,000 microfarad, to have the same effect. Of course, to safeguard over a wider bandwidth, the actual value will be a couple of hundred picofarad,

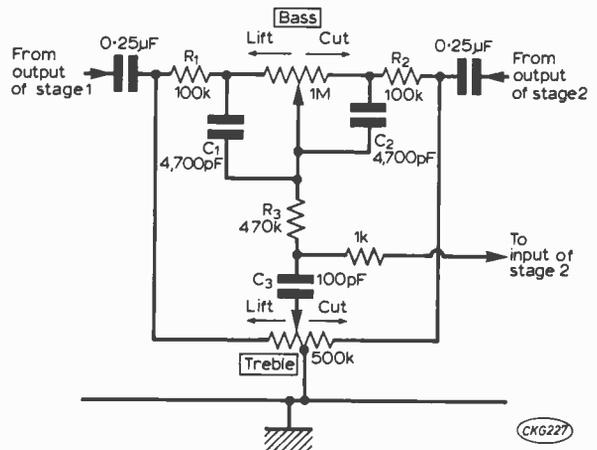


Fig. 56: The original Baxandall tone control circuit, to suit an input of less than 10kΩ, for use with an SP61 valve.

but the comparison—and the point—remains. When considering circuits, you must consider the effect of the a.c. signals they will be handling as well as the d.c. conditions that provide basic biasing, etc.

Virtual earths

Which brings us back to the concept of the virtual earth. Fig. 56 shows a simple circuit, again a practical one, and very familiar, that of the Baxandall tone control circuit, widely used in all sorts of constructions, and not always completely understood. If it serves no other purpose, it should remind us that Peter Baxandall dreamed this one up in 1952, based on an SP61 valve (or, in war surplus terms, a VR65).

The underlying reason for choosing such an example is (a) to make the opportunity of talking a bit more about feedback, (b) to introduce tone control circuitry, which will feature in our next constructional project and (c) to get over as well as we can, to satisfy a number of enquirers, the concept of the “virtual earth”.

Feedback has featured already in our potted circuits, d.c. feedback to bring bias conditions to the operating state we require and a.c. feedback to regulate the signal flow through a stage, and, as we shall have to consider later, to make a stage non-linear in an especially controlled way (as, for example, in designing an RIAA corrected magnetic pickup pre-amplifier).

The whole point about the Baxandall tone control circuit, first considered in a *Wireless World* article of October 1952, is that its action depends on negative feedback and that it requires an understanding of the virtual earth concept to grasp its principles of operation. Having once got hold of this, we can step forward briskly into the world of “closed-loop gain” and “variable feedback control”, which scares so many students away from what is really quite elementary circuitry. Incidentally, the virtual earth concept preceded Baxandall by quite a few years and he was quick to give credit to Professor F. C. Williams for the coining of the term.

Feedback

Enough waffling: Feedback is the principle of taking part of the output from a stage, or stages, and applying it to the input. If it is positive feedback, the signal you re-apply to the input is in phase, and thus aids the input, eventually driving the stage beyond its working limits. Control this positive feedback and you have a simple oscillator—the more output it delivers, the more it wants to deliver, until it blocks the stage off, things revert to normal, and away we go again.

But we are more concerned at this juncture with negative feedback. If you are audio-oriented (as you must have guessed by now that Mike and I are!) you will have read all manner of attributions for negative feedback. In the late Forties and early Fifties there were so many articles on negative feedback, interlaced with symbolic formulæ, that one would have imagined it could cure all amplifier ills from operator's twitch to the galloping parasitics!

In fact, the principle is simple: take off a portion of the output signal from a stage (or stages) and apply it to the signal in such a way as to oppose the input, i.e., in antiphase, and you have a method of

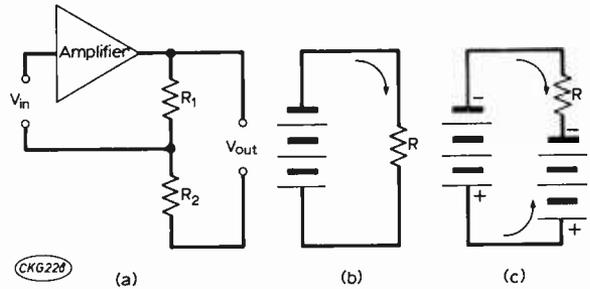


Fig. 57: (a) Negative feedback in series with the input signal. If $R_1 = R_2$ the gain is unity. (b) a battery analogy, with no feedback. (c) with feedback equal to the drive, voltage across R is virtually zero.

exercising control that depends on the nature of the input—it is to some extent, and within certain limits, self-regulating.

When we take a brief recap. of some previous articles in this series, we shall also appreciate that negative feedback from the output to the input of an amplifier stage *effectively changes the impedance* as well as reducing the gain.

This is important, and I am not going to insult regular readers by going, chapter and verse, over our earlier chats about R_{IN} and R_{in} , etc. But to summarise a few points, take a look at Fig. 57(a). Here we have an amplifying stage with a signal voltage applied and negative feedback in series with that input signal. (Again, this is important).

Let's assume, for easy figuring that the amplifier has an open-loop gain of 100. That's to say, it would increase its applied signal 100 times if there was no extra circuitry to consider. Then, commonsense tells us that if the values of R_1 and R_2 are the same, the gain will be unity, not 100 times, because the feedback is in series with the input. To get the hang of this, we have to look at things in terms of the impedance that the signal “sees”. Fig. 57(b) shows a battery driving a current through a resistor. The battery “sees” the impedance of the resistor. But what if, Fig. 57(c), we put another battery of the same sort in series with R ? We haven't changed the value of R but little or no current flows—so the *effective* impedance seen by the source voltage, the prime battery, is now high.

Back to the amplifier

Let's now get back to our amplifier with its feedback and instead of applying the feedback in series as before, we shall apply it in parallel, Fig. 58(a). Again, $R_1 = R_2$. But as the feedback is now in parallel with the input signal, we can see, applying the battery analogy, in Fig. 58(b) that it effectively shorts out the signal. In other words, adding V_1 to V_2 produces an *effective* zero.

Sorry about that repetitious word “effective”, but if I say “this is zero”, some pedant is going to hurl a wad of mathematical treatises at me to prove that Isaac Newton never went near the orchard, or something!

Go back to that mini-circuit of Fig. 58(a) and you can now see that the voltage at the junction X of R_1 and R_2 is very low indeed. Not zero, for we have to take into account the voltage across the amplifier, and the best we can say is that the voltage at this junction, R_1/R_2 , is very low, virtually at

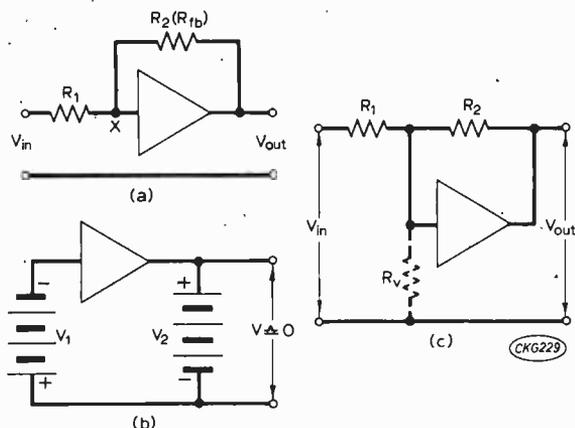


Fig. 58: (a) Parallel feedback, point X is virtual earth point. (b) battery analogy repeated. (c) choice of amplifier gain and resistors gives virtual impedance, dotted, between virtual earth point and true earth.

earth potential. Hence the term, virtual earth. From this, it follows that the input impedance of the circuit is low at this point.

Here, we have one of the bones of contention over which audio pundits have worried, and with which we shall not concern ourselves now—suffice to say, the source signal “sees” an impedance equal to R_1 in parallel with whatever the virtual resistance R_v in Fig. 58(c) may be, while the amplifier sees an impedance of about R_v . And the beauty of this arrangement is that by juggling with amplifier gain and feedback component values, we can make the input match our source exactly, for best signal energy transfer conditions, while making our amplifier “see” a source resistance (impedance) that is just right for its job. In many audio applications, an impedance of around 600Ω would do us very nicely for lowest noise conditions, and this case can be met quite easily.

The important factor to remember is that the imaginary resistor we produce by the virtual earth application is approximately equal to the value of R_2 divided by the amplifier gain. Its value is not affected by R_1 . There is no need for R_1 and R_2 to be equal in all cases, although we have chosen this circumstance for ease of explanation—the performance depends on the ratio between resistor values.

Back to Baxandall

So now back to Baxandall, and a circuit that originated from valved techniques.

This time we shall split the circuit into its “Lift” and “Cut” conditions first, showing the virtual earth points. Forget, at the moment, the tapped potentiometer of Fig. 56 and consider the treble lift circuit. This, shorn of all extraneous detail, could be redrawn as Fig. 59(a). If V_R is made low enough so that the voltage at the slider when in the middle of its travel is not affected by the current supplied by C (even at higher frequencies) then the total current flowing toward the virtual earth point, X , is $I_1 + I_2$. I_1 is approximately equal to V_{in}/R_{in} and I_2 depends on the value of capacitance. If we make R_{fb} equal to R_{in} , merely to simplify combination of lift and cut control, and call this simply R , then the output voltage has one component independent of frequency, for a constant value of V_{in} while the

other one, leading in phase by 90° is both proportional to frequency and to k which is the fraction of the potentiometer setting.

What this means, in practical terms, is that for any particular potentiometer setting the response of the cut circuit will be down by the same number of decibels as the lift circuit is up. As we know from Baxandall tone controls published many times before, the curves are a mirror image of each other. This is one of the virtues of the control.

The tapped control is just a convenience and it can be seen that there is actually a small voltage between the centre point of the practical circuit (Fig. 56) and virtual earth, across the capacitor. But its value makes this voltage practically negligible.

A look at the combined bass control in its simplified layout of Fig. 59(c) may help to understand better the working of the tone control. To give level

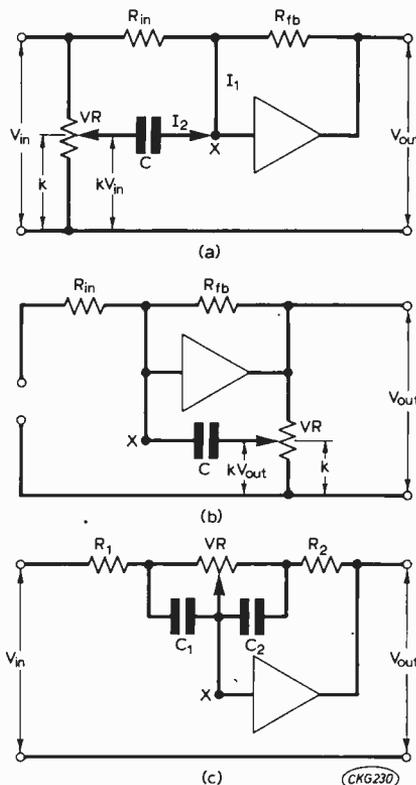


Fig. 59: Fundamental Baxandall treble lift circuit. (b) treble cut circuit. (c) bass lift and cut section of combined circuit.

response at mid-setting, R_1 and C_1 are the same as R_2 and C_2 . At middle and high frequencies the potentiometer, V_R is almost shorted out by the low reactances of C_1 and C_2 , so we are back to Fig. 58(a) with $R_{in} = R_{fb}$ and unity gain. As the frequency of the signal falls, the gain rises (or, if the potentiometer setting is changed, falls to the level determined by the response curve), and, just as with the treble circuit, the curves are mirror images.

The symmetrical beauty of the finished control, with components calculated to suit Baxandall's original case, the $VR65$ valve, a high-gain pentode, can be seen in Fig. 56. One of the interesting points about its chosen values is that the treble response will be up or down 3dB at full lift or cut settings of the control when the reactance of C_3 is numerically

equal to $R1 + 2R3$. The values of $C1$ and $C2$ must be equal, as are $R1$ and $R2$, for reasons already stated, and values are chosen to give the correct bass response.

In practice

Coming to the present time, we can see an example of virtual earth circuitry used in the much-vaunted input stage of the Cambridge P40 amplifier, Fig. 60, where the aim was to get a high-gain, low-noise input amplifier, controlled so that the local feedback loop alters the gain, and thus provides a volume control right at the front of the circuit, in a low-signal level stage—just where we are told never to put it! The aim succeeded to some extent, because there was indeed a very low-noise result, and the overload capability, where most input amplifiers fall down badly, was a phenomenal 60dB.

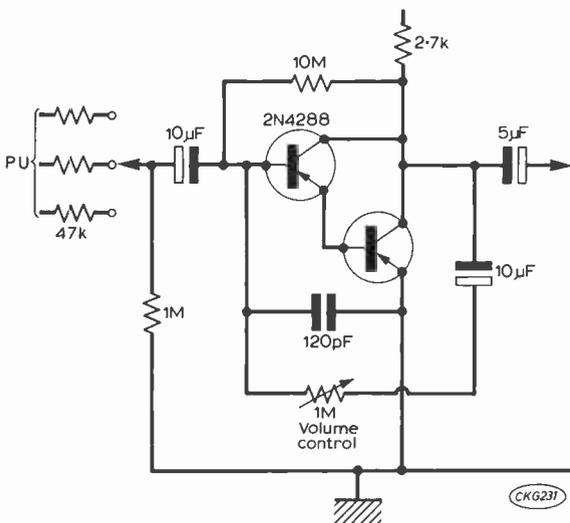


Fig. 60: Virtual earth input stage used in Cambridge P40 and P50 amplifiers.

But later versions of Cambridge amplifiers reverted to an uncontrolled input stage and put the virtual earth amplifier in the second stage, mainly because the original design gave a peculiar volume control "law". You see, the accepted use of a control is a 20dB attenuation when the knob is half-way from maximum (or the slider half retarded). By putting a twin-gang 1MΩ log law potentiometer in the virtual earth feedback circuit, Cambridge limited the attenuation to between 3 and 6dB for the same movement, with its action accelerating as it was turned farther down.

To get the range of input levels, the control had to be shunted with a 47kΩ resistor, except in the Pickup 1 mode, so except in this mode, only about three-quarters of the control action was effective. Later versions use a 50kΩ linear potentiometer to get the approximate log law (using the fixed resistor, 22kΩ, across part of it).

So we have now considered practical ways of using virtual earth circuitry, and can go on to the even more practical matter of building a circuit whose action may not seem quite so mysterious.

TO BE CONTINUED

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunications Techns'. Certs.
 - Radio Amateurs' Examination
 - General Radiocommunications Certificate
 - C. & G. Radio Servicing Theory
 - General Certificate of Education, etc.
- Now available Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

Accredited by the CACC

Member of the ABCC

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam)

NAME (BLOCK CAPITALS PLEASE)

ADDRESS

AGE.....OCCUPATION

INTERNATIONAL CORRESPONDENCE SCHOOLS


Dep: TB28 Intertext House, Stewarts Road, London, S.W.8 4UJ

ICS

GOING BACK...



COLIN RICHES
ARTHUR DOW

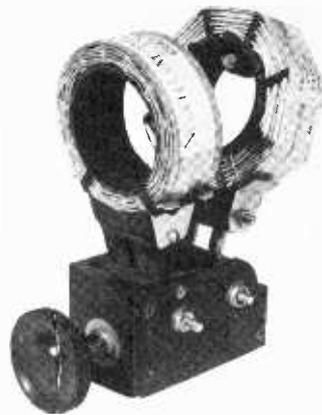

DEVOTEES of this column will be highly delighted at the publicity currently being given by the Post Office to the 50th. anniversary of broadcasting in this country by issuing a set of three postage stamps to commemorate the event. Since we mentioned the subject in the last issue details of the stamps have been released by the Post Office and they are reproduced here.

The 3p stamp depicts six of the many types of microphones used in broadcasting since 1922. Observant old-timers will recognise the Marconi-Sykes electromagnetic microphone of 1924 as well as the Marconi-Reisz carbon microphone of 1926 among the collection. On the 5p stamp a typical domestic wooden horn loudspeaker of the 1920's is illustrated. Some readers may recall the S.G. Brown conical horn speaker and the Amplion horn of the same period.



No doubt there are many of these speakers still hidden away in attics and cupboards so let us hope that this invaluable publicity will cause the public at large to appreciate the value and significance of

these treasures from the early days of wireless and thus prevent their needless destruction.

The third stamp, for 7½p, brings us right up to date with a fine illustration of one of the latest colour TV cameras as used by both the BBC and the independent TV companies.

The fourth stamp, to be issued at the same time as the other three, is for 9p and shows an early form of spark transmitter as used by Marconi in establishing wireless contact between Lavernock Point, Glamorgan, and Brean Down, Somerset, in May 1897. On the 75th. anniversary of this historic event the name of George Kemp is coupled with that of Marconi. Kemp was a Post Office engineer loaned to Marconi as a senior assistant. Their experiments resulted in the first successful tests over water and, incidentally, the first between two countries.

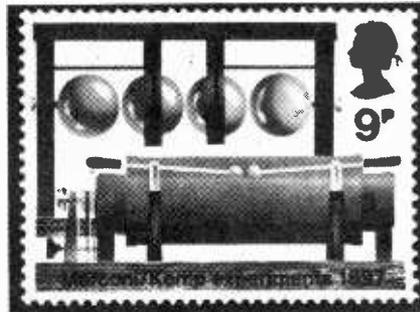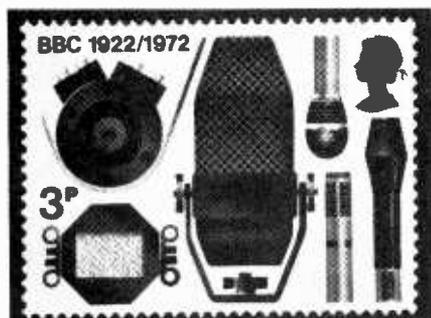All four stamps are the work of David Gentleman who was also the designer of the Philympia series of stamps issued in 1970. The anniversary stamps described will be on sale on September 13th.




The 3p stamp is printed in several shades of grey with black, brown and yellow while the 5p stamp is grey, beige, red, brown, black and umber. The 7½p stamp featuring the TV camera also has several shades of grey combined with black and red. The 9p Marconi-Kemp commemorative issue combines light and blue grey with black, yellow and brown. A special first-day cover and two pictorial hand-stamps are being provided by the Post Office.



"Where can I get exclusive units at lowest prices?..."

ROC ELECTRONICS!

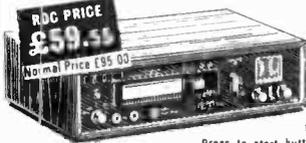

ROC PRICE
£59.95
Normal Price £95.00

8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST
The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual over-ride.

Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed 3 1/2 ips (9.5 cm). Frequency response: playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect on a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut. Including connecting leads.



ROC PRICE
£28.00
Normal Price £30.70

A-3000 36-WATT SOLID STATE STEREO AMPLIFIER
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front—all the controls you're ever likely to need plus a headphone socket. On the rear—signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux. Tape Play. Size: 345mm x 300mm x 130mm.

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted—for under £45.00. Saving over £10.00 on the normal retail value. Up-to-the-minute controls for bass and treble, separate volume and balance controls. Headphone socket on front panel. Push-button input controls—magnetic phono (high/low) tuner, aux. mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono—50db; tuner/aux—65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



As reviewed in "POPULAR HI-FI" February 1972


ROC PRICE
£35.20
Normal Price £55.50



ROC PRICE
£31.20
Normal Price £50.00

OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz. AM: 525-1605 kHz. FM Sensitivities: FM, 3µV; AM, 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

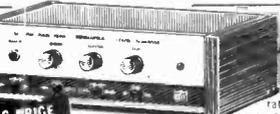

ROC PRICE
£12.45
Normal Price £21.00

REALISTIC SA-100B 8-WATT STEREO AMPLIFIER

Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/line and tuner and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.



EAGLE LC.05 STEREO MAGNETIC CARTRIDGE
For fabulous reproduction at a very low price, you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: ±1.5dB. Channel separation: 20dB. Recommended stylus pressure: 2.4 grams. Compliance: 3 x 10⁻⁶ cm/dyne. **ROC PRICE** £4.75



EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE
Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ±1dB. Channel separation: 28dB. Compliance: 12 x 10⁻⁶ cm/dyne. **ROC PRICE** £6.37



"WATTS" RECORD CLEANERS
The original "Dust Bug" Automatic Record Cleaner keeps your records clean as they play. £1.16 Watts Disc Preparer. Keeps new records like new—for perfect record reproduction. 35p



R.307 TRANSISTORIZED STEREO PRE-AMPLIFIER
Now your amplifier that could only reproduce ceramic or crystal pick-up cartridges, can accept signals from moving-magnet cartridges! The R.307 steps up signals from between 5-20mV to 200-800 mV. Input: 5-20mV. Equalisation: RIAA. Output: 220-800mV flat. Frequency range: 20-22,000 Hz. Dimensions: 3 1/2" x 1 1/2" x 2 1/2". Supply: 240 VAC. **ROC PRICE** £4.92



15-FOOT STEREO HEADPHONE EXTENSION CORD R.362
Fitted with heavy duty 3-circuit stereo plug at one end and a matching stereo socket at the other. **ROC PRICE** £1.30



R.361 STEREO HEADPHONE "Y" ADAPTOR
R.361 Enables you to use two sets of stereo headphones from a single socket. Fitted with male plug and two female sockets. **ROC PRICE** £1.30



ROC PRICE
£10.50
Normal Price £15.70

OLSON AM-357 4-WATT STEREO AMPLIFIER
Here's marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3db. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.



ROC PRICE
£27.25
Normal Price £39.95 each

25-WATT 3-WAY CRYSLER 'LIVING ACE-5b' SPEAKER CE-5b
This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units on 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.




ROC PRICE
£27.55
Normal Price £42.00

OLSON AM/FM/MPX STEREO TUNER AMPLIFIER SSA-18
This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received—that's the time to switch to 'Stereo'! The SSA-18 has all the facilities you'd expect to find on tuners costing twice as much—separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz. AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.




ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317
This exclusive ROC Stereo Chassis is completely self-contained and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 6 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45dB.

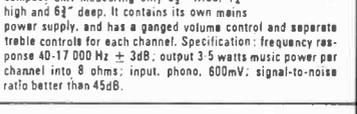

ROC PRICE
£15.10
Normal Price £25.20


OLSON AM-372 18-WATT STEREO AMPLIFIER
Here's a really good amplifier at a really down-to-earth price—nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you—reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

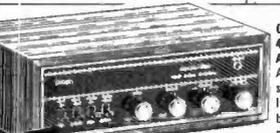

ROC PRICE
£24.10
Normal Price £39.80

OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3-0mV RIAA, crystal phono 100mV; tape 160mV; tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well—sounds even better!

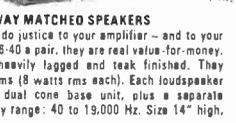

R.446 3-WAY MATCHED SPEAKERS
These will do justice to your amplifier—and to your pocket. At only £16.40 a pair, they are real value for money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.

ROCELECTRONICSLTD
M. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211
CALLERS WELCOME 9-6 MON TO SAT,
LATE NIGHT THURSDAY 7 PM

Return-of-post mail order service. Orders over £10 post free (UK only). Add 25p for P & P to orders under £10. HP terms available for callers




BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON S.W.17 01-672 3984
(Nr. Tooting Broadway Underground Station)
(Closed all Wednesday)

THE SHELLEY

Size 21 x 11 x 6 1/2 in.

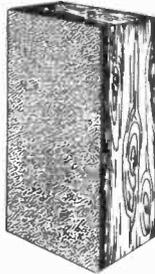An extremely elegant speaker system made of 12mm. chipboard covered with black leathercloth with mottled Vynair front. This unique system uses three ex-TV speakers. Carefully matched and tested. Will handle 10 watts and will match 8 ohms impedance. A real bargain at £5.15 plus 70p. British Isles. Send for Hi-Fi & Electronic Catalogue 7p. each.



CARTRIDGES—Stereo

Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93/1 Sapphire, £1.90. GP94 1 Sapphire, £2. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.

CARTRIDGES—Mono

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.


FARRADAY

5 1/2" x 11" x 4 1/2" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front 3ohm ex. tv speaker. £2.90 P & P 25p



ELF

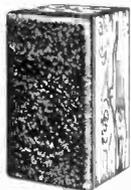An extension speaker of quality; 9 x 5 1/2 x 3 1/2 in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm ex-TV speaker. The baffle is half inch thick. A real bargain at £1.92 1/2. Post and packing. 37 1/2 p.



SPEAKER MATCHING TRANSFORMERS 3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.

HI-FI STEREO HEADPHONES

Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms. frequency range 30-15,000 Hz 6ft. cord and standard stereo plug. Only £2.57 1/2. P. & P. 27 1/2 p.



STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.50. P. & P. 13p.




VYNAIR

Widths from 50 to 54 in., 75np yd. off roll. P. & P. 10np, 1/2 yard 40np. P. & P. 10np. Send 5np stamps for samples.

£3.15

P. & P. 61p

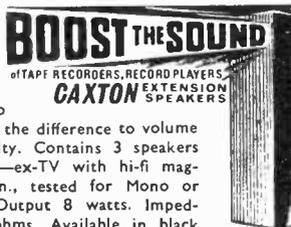Makes all the difference to volume and quality. Contains 3 speakers in series—ex-TV with hi-fi magnet recon., tested for Mono or Stereo. Output 8 watts. Impedance 9 ohms. Available in black leathercloth. Size 23 1/2" x 5 1/2" x 5 1/2". Keyhole slot for wall mounting. Twin connecting cable 12yds., 35p min.



ELECTRONIC VALVES

DY86	0.23	PC97	0.36	PY83	0.26
DY87	0.23	PCC84	0.28	PY500	0.95
EABC80	0.30	PCC89	0.43	PY800	0.32
EB91	0.09	PCC189	0.47	PY801	0.32
ECC81	0.15	PCF80	0.27	UABC80	0.30
ECC82	0.18	PCF86	0.44	UCC85	0.34
ECC83	0.24	PCF802	0.38	UCC81	0.30
ECL80	0.25	PCF806	0.56	UCL82	0.31
EF80	0.22	PCF808	0.68	UL41	0.54
EF85	0.26	PCL82	0.30	UY85	0.24
EF86	0.28	PCL83	0.55	6/30L2	0.58
EF89	0.23	PCL84	0.33	6AT6	0.18
EF91	0.12	PCL85	0.37	6AU6	0.20
EF183	0.26	PCL86	0.37	6BA6	0.20
EF184	0.28	PFL200	0.51	6BE6	0.21
EH90	0.35	PL36	0.47	6F23	0.67
EL41	0.53	PL81	0.43	12AT6	0.23
EL84	0.22	PL82	0.29	12AU7	0.15
EY51	0.30	PL83	0.31	12AU7	0.18
EY86	0.28	PL84	0.29	12AX7	0.24
EZ80	0.20	PL500	0.61	12BA6	0.30
EZ81	0.21	PL504	0.61	12BE6	0.30
PC86	0.45	PY81	0.23	35W4	0.23
PC88	0.45	PY82	0.24	50C5	0.32

POSTAGE: 1 VALVE 5p, EACH ADDITIONAL VALVE 1p. ORDERS OVER £5 POST FREE. CASH WITH ORDER ONLY.

Quotations for any type not listed send SAE.

NO CALLERS. ALL VALVES GUARANTEED AND INDIVIDUALLY BOXED.

EXPRESS MAIL ORDER

SEND TO :—

ARCHES 1150/1152
41 NORWOOD RD., LONDON, S.E.24

RSGB BOOKS FOR YOU

Just Published

New (fourth) edition of the ever-popular **AMATEUR RADIO TECHNIQUES** by Pat Hawker, G3VA

Aimed at extending the reader's awareness of new devices and techniques. Provides a source book for many useful circuits and aeriels. An ideas book rather than a constructional manual, but an ideas book that will prove its value time and time again. Substantially enlarged edition comprising 256 pages with over 600 diagrams. New material and features include more emphasis on integrated circuits, a quick guide to digital electronics, and much additional information on the cure of TV interference and on aeriels.

£1.80 including postage and packing

RAE MANUAL

by G. L. Benbow, G3HB Sixth (1972) edition

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. A completely re-written edition brought fully up to date to meet the present examination syllabus requirements.

96 pages

90p post paid

These are two of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY of GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

FOR a change this month I think it will be useful to all readers if we start with some news of DX stations around the world. The source of the information is Sweden Calling DXers and my own listening efforts.

BOLIVIA: The Bolivian station on 4845 is CP-72, *Radio Fides de La Paz*. This station is scheduled to broadcast from 1030 to 0330 GMT only but has been heard on an extended schedule. The station has also been heard in Europe on 4875kHz.

CP-103, *Radio 27 de Diciembre*, listed on 3350kHz is presently operating on 3439kHz with sign-off at 0215 GMT or later.

BRAZIL: The new European service from *Radio Nacional de Brasilia* has been noted on 15450kHz with weak signals and splash from VOA, *Monrovia*, on 15445kHz at 2245. The programme consists of Brazilian music and short talks in English, reports are requested.

MONGOLIA: *Radio Ulan Bator* has introduced a Russian service which is on the air on Tuesdays at 1030 and on Fridays at 1040. These broadcasts have been heard on 7260kHz, the station announces 41°3, 48 and 1321 metres.

PARAGUAY: ZPA-1, *Radio Nacional, Asuncion* can be occasionally logged on 4615kHz with special sports newscasts in Spanish after 2200 hours.

SWEDEN: Due to heavy interference on 15105kHz during the broadcasts in English and Swedish to the Far East at 1230-1330, *Radio Sweden* has moved this transmission to 17815kHz as from Thursday 22nd June. Reports will be much appreciated. A change of frequency for South Asia at 1400-1530 is also being considered.

The first report this month comes from Mervyn Winters of Greenisland, Co. Antrim who used an AR88 with a 12 foot whip antenna to pull in several interesting stations including:

- 4980 *Ecos del Torbes* in Spanish at 2350
- 4995 *R. Brazil Central*, LA music at 2340.
- 6030 *RSA, South Africa* noted at 2355.
- 6140 *RNE, Spain*, English to NA at 0110.
- 9570 *R. Australia* noted at 0714.
- 11620 *AIR, Delhi*, India at 1930.
- 11720 *R. Nacional de Brasilia* at 2307.
- 15018 *R. Hanoi*, N. Vietnam in English at 2015.
- 15190 *R. Ankara*, Turkey in English at 2200.
- 21570 *R. Japan* in English to Europe at 0800.
- 21605 *R. Kuwait* in Arabic at 0900.

Roger Hunter of Carmarthen has added a PR 30 preselector to his Codar CR-70A receiver enabling him to hear the following stations:

- 6025 *R. Portugal* in English at 2058
- 6080 *R. Berlin International* at 2145.
- 7235 *R. Australia* with Newsreel at 1000.
- 9009 *Kol Israel*, 'In the Jewish World' at 2115.

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 9640 *TWR, Monte Carlo*, DX programme at 0945.
- 11755 *R. Finland* in English at 1815.
- 15105 *R. Japan*, news and comment at 2000.
- 17735 *R. Free Europe*, music at 1740.
- 21545 *R. Ghana*, talk in English at 1050.
- 21595 *CBC, Canada* in English at 1900.

Michael Berry of Dewsbury in Yorkshire has again used his outdoor vertical wire and Eddystone EB-35 receiver to good effect, hearing:—

- 3264 *R.T.V. Congolaise* noted at 1910.
- 4765 *R.T.V. Congolaise* in French at 2100.
- 4832 *R. Capital, Costa Rica* in Spanish at 0205.
- 4880 *R. Once Sesenta*, Peru in Spanish at 0335.
- 4940 *R. Yaracuy, Venezuela*, Spanish at 0135.
- 4965 *R. Santa Fe, Colombia*, Spanish at 0430.
- 4970 *R. Rumbos, Venezuela*, Spanish at 0435.
- 4980 *Ecos del Torbes, Ven.*, Spanish at 0025.
- 5030 *R. Reloj Continente, Ven.*, Spanish at 0310.
- 6255 *Schulungssender, Austria*, German at 1245.
- 11862 *R. Lubumbashi, Zaire* in French at 1655.
- 11865 *R. Club Pernambuco, Brazil* at 0330.

Nigel Knowlman of Cullompton in Devon has a Lafayette HA-600A and a 50 foot inverted L antenna, this combination enabled him to hear the following stations:—

- 11520 *R. Bangladesh* in English at 1745.
- 11720 *R. Nacional de Brasilia* in English at 0700.
- 11940 *R. Bucharest, Romania*, English at 1300.
- 11955 *FEBA, Seychelles* in English at 1730.
- 15170 *Beirut, Lebanon* in English at 1830.
- 15185 *Voice of Nigeria*, English at 0700.
- 17655 *R. Cairo, U.A.R.*, English at 1800
- 17815 *HCJB, Quito, Ecuador*, English at 1945.

Next month the series of instructional articles for newcomers will continue with a discussion of the various types of aerials. This will include details of construction and the advantages and disadvantages of the various types.

Reports should arrive by the 15th of the month and be addressed to me at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

OUR "CQ" COLUMN

If you wish to have a "CQ" request in *Practical Wireless*, we would be grateful if you could write it out in the same style we print it. This helps us to help you by saving time trying to take extracts from long letters and deciphering names and addresses.

SHORT WAVES

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

IT'S September already and the summer has almost gone. This is sad news for the sun bathers but good news of the l.f. enthusiasts. How about having a really good "go" at topband this year? Once the leaves turn and the darker evenings arrive you can be sure of hearing a few interesting tweets on 160 metres. Quite a number of European countries are active as are stations from further afield. You only need to monitor the bottom 50kHz of the band (i.e. from 1800kHz to 1850kHz) to hear quite a bit of topband d.x. The American stations are usually active at the very edge of the band and usually on c.w. Stewart, W1BB, is a good one to listen for and a few VO and VE stations have put in an appearance from time to time.

Czechoslovakia is a country well represented on 160 metres. Apparently, novice licences are awarded and OL stations are limited to 10W on 160 and 2 metres. What a splendid idea. There was a time when the British Post Office exercised its wisdom and imposed a 10W limit plus c.w.—only for the first year—Ah, happy days. Rumour has it that LU (Argentine) EL and ZS will be in evidence on 160 metres which should offer a challenge from sitting comfortably on 14MHz and just letting the d.x. drop into ones lap.

Letter from Peter Martin (Nottingham) informs that KR6 stations are now signing KA6 and that 7P8AM is on from Lesotho—anyone heard him yet? He also mentions the RSGB news Bulletin Service. The latter is broadcast on Sundays on both eighty metres and two metres and is put out from various parts of the country, so you should have no problems in receiving all the latest information on Amateur radio, both for licensed operators and s.w.l.s. Time depends on which area you're in. However, try listening on 3.6MHz at 0930 for transmissions from Bromley in Kent.

Speaking of the RSGB, don't forget that many of its members put out special slow morse transmissions to help those trying to get up to the magic twelve words/minute. These stations are on from all over the country and at many different times. There is almost certainly somebody on in your locality—usually on topband. The RSGB will give you all the information (you get this and many other things all the time if you become a member).

Alan Smith (Nelson) took "one of my rare trips down on to eighty metres". Reward was ZD8RR at 5 and 7 but Alan queries the authenticity of this station. Any offers? Gear in use is a JR310 and a twiddle on twenty revealed squirts of s.s.b. from; CE3AIU, CO2FA, CX2AL, CX2BR, EL2GY, FC9VN, FM7WN, HC1HV, HC1SS, HC2HM, HK3COC, HK6CBS, HV3SJ, LU3FAQ, LX1DV, OD5HD, PY2BCQ, PY4EP, PZ6AA, SL2ZZM, TI2FCD, TI8PE, TR8GD, VE1RB, VE2WY, VE3BYI, VE5AZ, VE7MT, VE7YF, VK2AVA, VK2BHR, VK3MO, VK4SD, VK5DK, VK6TW, VK7RX, VO5GJ, VP1TB, VP2GB, VP2MZ, VP7NO, VP9HA, VQ9MC, VQ9R, VR1FL, VU2HLU, W8JXM, W9YRA, XE1DO, XE1EH, ZD3D,

ZD7SD, ZE1CS, ZE6JS, ZL1GY, ZL2FA, ZL4CO, ZM2TG, ZP5CF, 4X4NJ, 4X4VB, 8P6EK, 9J2DT, 9K2CA, 9K2CI, 9M2CP, 9M2CW, 9V1QJ. Antenna was a sneaky sixty foot end fed.

R. Dickens (Shepherds Bush) has a "modified" R1155 and a 20ft. aerial. He reports signals from many EU stations on 3.5MHz but also includes a couple of goodies heard in the form of M1B and 6W8DY. Best on 7MHz was 4U1ITU.

G. Benson (G8FBL) tells gleefully of contacts made by special station GB3CRC run by the Chad Radio Club, Lichfield. Over 300 contacts were made including chats on 21MHz with CT2BG, CX4CR, HC1RF, 7Q7BQ, 9H1DL, 9J2TB and 9Q5RA—no mention of mode. (Don't tell me, brightly coloured flags and it was a clear day!)

"I wonder how much of the inside is original", says an unsigned letter from Nicholas Dean of Loughborough. The antenna is a 20 metre bow tie (bet it suites you and, of course, you'll get d.x. in necks to no time) at 20ft and fed into an a.t.u. It is then pressed into service on 3.5MHz. Signals received from; CE8AA, CN8BQ, CT1HE, CT2BG, PY2FYQ, ZB2A, ZL6MP, ZS1MH, 4X4UF, 7X0GF, 9Q5BJ.

Graham Armstrong (Jedburgh) reports hearing some good EU d.x. on topband; DL5XF, GI3GRD, GW3UPK. He reports a station on c.w. signing 2LO which will doubtless raise a smile. (LO LO, what's all this then?). Anyone else hear this character? Apparently he was on for at least a week.

David Lawley (Gravesend) sends in some interesting sigs heard on 160 metres. Among the c.w. offerings are; DL9KR, EI9J, EL2CB, GC3ZES/A, GM2HCZ, GW3UCB, OK1HBT, OL1AOH, OL1APC, OL5APO, PA0PN (on s.s.b.).

B. Spencelayh (Enfield) has got his version of the Deluxe 9/12 receiver (PW April/May 1972) perking. First attempts on 21MHz brought sigs from; EA3SA, HB9AJQ, JA4BLY, OD5LX, VQ9MC, WA1JTT, W9YFV, 4X4HK, 4Z4MO, 5H3JL, 9J2SS, 9M2DQ.

Happenings for September include the Harlow Mobile Rally on September 24 at Magdalen Laver, near Harlow. Contests in my little black book include: September 9-10, WAE phone contest; 10, 3.5MHz field day; 17, final d.f. round at Oxford.

ELECTRONICA 72

Electronica 72, recognised by many as the most important trade fair in the electronics industry, will take place this year at Munich, Germany, from November 23-29. Included in the exhibits will be components and assemblies, production facilities, testing apparatus, information and training. Running at the same time as the exhibition will be the conference Mikroelektronik consisting of some 40 lectures.

Garrard Record Players



SP25 Mk. III
Deck Only

4 speed
Automatic Single Player

Lasky's price **£11-50**

Garrard SL95B Deck	£35-00
Add £9-00 for Garrard Base & Cover. C & P	£1-50
Garrard AP76 deck only	£23-00
Garrard 40B deck only	£9-50
complete with stereo cartridge	£11-50
Garrard SL55B deck only	£9-00
Garrard 2025TC deck only	£7-95
complete with KS40A stereo ceramic cartridge	£43-90
Garrard ZERO 100 Automatic	C & P £2-75
	£42-75

Garrard ZERO 100S Single Player
C & P £1-50
£42-75

Garrard Plinths & Covers

WB4 Mk. II plinth	£5-45
SPC4 Mk. II cover	£4-25
Price together	£8-70
WB1 Plinth	£3-70
SPC1 cover	£3-60
Price together	£6-30

SP 25 Package

SP25 Mk. III Single player	List	£15-85
AD76K stereo magnetic cartridge	List	£4-35
Lasky's teak plinth & cover	List	£4-75

Total List Price £24-95

Package Price **£18-50**

AP 76 Package

AP76 Single Player	List	£29-26
SHURE M44E Cartridge	List	£8-59
Lasky's Base and Cover	List	£5-95

Total List Price £43-80

Package Price **£35-00**

CARRIAGE—all units

DECK ONLY 50p. PLINTH & COVER ONLY 25p.
DECK WITH PLINTH AND COVER 75p.

TWO BAND CAR RADIO

WI700 MW/LW
By famous maker



Two waveband all transistor car radio that covers full Medium and Long wavebands with slide switch wave change. Long wavebands with slide switch wave change. Large easy to grip controls. Illuminated dial with "easy to read" scale. Externally adjustable aerial trimmer. Powerful output through either one or two speakers. Operates on 12 volt D.C. Negative or positive earth. Standard size 6 1/2in (W) x 4 1/2in (D) x 2in (H). Black with chrome trim. Complete with speaker, baffle, leads, mounting brackets.

LASKY'S ONLY **£7-50** C & P 25p
PRICE

NEW DIGITAL CLOCK

NOW WITH ILLUMINATED DIAL EXCLUSIVELY FROM LASKY'S

The clock measures 5 1/2 W x 2 1/2 H x 3in D (overall from front of drum to back of switch). SPEC.: 210/240V a.c. 50Hz operation; switch rating 250V, 3A. Complete with instructions. ● COMPLETE WITH KNOBS. FEATURES: ● MAINS OPERATION ● 12-HOUR ALARM ● AUTO "SLEEP" SWITCH ● HOURS, MINUTES AND SECONDS READ-OFF ● FORWARD AND BACKWARD TIME ADJUSTMENT ● SILENT OPERATION ● SHOCK AND VIBRATION PROOF ● BUILT IN ALARM BUZZER

SPECIAL QUOTES FOR QUANTITIES LASKY'S PRICE **£6-75** C & P 25p



SINCLAIR PHASE LOCK LOOP STEREO FM TUNER

Incorporates varicap diodes, printed circuit, coils, squelch circuit I.C. Decoder, etc., supplied completely built and tested and ready to be mounted into any cabinet you choose. It may be used with any High Fidelity Amplifier. Power requirements 25/30V DC. Size 8 1/2 x 1 1/2 x 3 1/2". LIST PRICE **LASKY'S PRICE £15-75** C & P 25p
PZ5 power supply £4-15 extra.



EAGLE AM/FM POCKET TRANSISTOR RADIO

This super compact two-band radio **ORIGINALLY COST £9-81!** The ideal pocket set for all ages. Receives all Med. wave and FM stations (local news, etc.)—separate tuning scales. Grey/chrome trim cabinet with carry strap. Excellent tone. Uses single PP3 type battery. Telescopic FM aerial. Size: 4 1/2 x 2 1/2 x 1 1/2in. comp. with battery and ear-piece. LIST PRICE **LASKY'S PRICE £4-75** C & P 15p



LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Single	5	10	15
C60	28p	£1-37	£2-70	£3-99
C90	38p	£1-86	£3-67	£5-42
C120	48p	£2-35	£4-63	£6-84

Each cassette individually boxed in Philips, type plastic library.
C & P: each 7p, 5—25p, 10—40p, 20—68p.

Leak Speaker "Scoop"

Leak 150 Speakers
List price £49-00 per pair

Lasky's Price **£38-95** C & P £2-00


Leak 250 Speakers

List price £63-00 per pair
Lasky's Price **£48-95** C & P £2-00

Leak 600 Speakers

List price £99-00 per pair
Lasky's Price **£68-75** C & P FREE

BSR TAPE DECK SCOOP

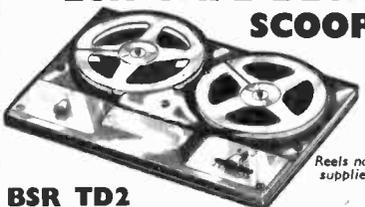


BSR TD2

FANTASTIC VALUE, ONLY Lasky's can offer you a tape deck at such an amazing price. The BSR TD2 tape deck operates by a simple reliable mechanism using the minimum of controls.

Available with 1/2 track or 1/4 track mono or stereo heads. Incorporates fast wind and fast rewind, records at 3 1/2 ips. giving up to 3 hrs playing time, takes up to 5 1/2in. spools. Size 1 1/2in. x 8 1/2in. front to rear, 2 1/2in. below plate, 1 1/2in. above plate.

ALSO SUITABLE FOR USE AS A TAPE TRANSPORTER
LASKY'S PRICE **£8-95** C & P 35p

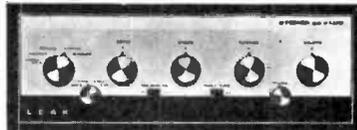LEAK BARGAINS STEREO 30 PLUS amplifier (cased)



List Price £62-50
PRICE **£43-95** C & P 75p

STEREO 70 amplifier (cased)

List Price £75-00
PRICE **£54-95** C & P 75p

LEAK WOOD CASES

Teak or walnut case for Stereofetic tuner only.

List Price £7-37
LASKY'S PRICE **£2-50** C & P 35p

Teak or walnut double case for Stereo 30 or Stereo 70 and Stereofetic tuner.

List Price £10-37
LASKY'S PRICE **£4-95** C & P 35p

LEAK TRUSPEED



2 speed belt drive turntable comp. with plinth, cover and SHURE cartridge.
LIST PRICE £69-50

LASKY'S PRICE **£47-50** C & P £1-50

RADIO BARGAINS

Nordmende Galaxy 4000

AM/FM/LW/SW Battery/Main Portable Radio


Both these sets offer fantastic quality and almost unbelievable value! Each superbly finished in teak black and chrome. Covers medium, long and FM waves plus 3 band spread short wave ranges. Fitted with slider volume and tone controls. Size: 13 1/2 x 7 1/2 x 3in. Power: Batteries/Mains 220/240, 50/60Hz.

ORIGINAL LIST PRICE £49-50

LASKY'S PRICE


£36-50

C & P 25p

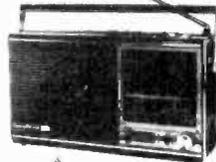

Nordmende Galaxy 6000

ORIGINAL LIST PRICE £69-50

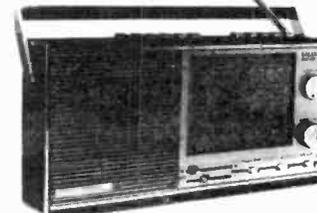

AM/FM/LW/SW Battery/Main Portable Radio

Covers medium and long waves, FM (local) and world-wide short waves cover in 6 band ranges. Size: 16 1/2 x 8 x 3in. Filter switch, ext. speaker socket, tape record and record player socket. Batteries or 220/240v. Mains, 50/60Hz.

LASKY'S PRICE **£44-50** C & P 35p

Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON. W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON. W.1 Tel: 01-636 2605

Open all day 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON. E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON. W.1 Tel: 01-580 2573

Open all day 9 a.m. - 6 p.m. Monday to Saturday

NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON. E.C.4 Tel: 01-353 5812

Open all day Thursday early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELI ST. TOWER HAMLETS, LONDON. E.1 Tel: 01-790 3321



GAS FILLED VALVES and TUBES

I. R. SINCLAIR

discharge has started, it cannot be stopped by any voltage applied to the trigger electrode, only by dropping the anode-to-cathode voltage below a level called the "sustaining voltage." Fig. 10 shows the characteristics of a typical trigger tube, the H1VAC XC23.

Applications

Figure 11 shows a trigger tube used as a pulse amplifier. The trigger pulse causes current to flow,

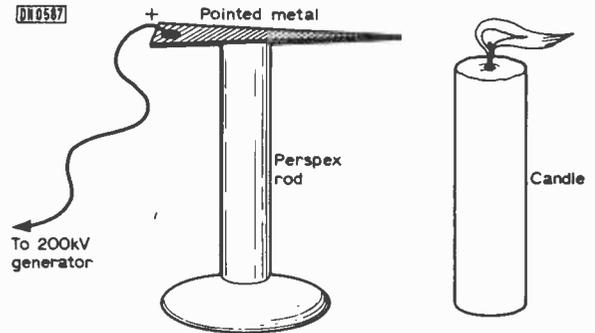


Fig. 9: The high concentration of electric charge around a point causes ionisation of the air. The movement of ions of the same sign away from the point creates a wind capable of blowing out a candle.

PART TWO

Trigger tubes

THE discharge between the anode and cathode in a gas-filled tube can be started in ways other than that of raising the voltage to striking voltage. One of these ways is to use a trigger electrode to generate ions which will then carry the current of the main discharge. The trigger electrode is a pointed wire very close to the unheated cathode and pointed to the cathode surface. Because of the close spacing, it is easy to start ionisation with a small voltage applied between trigger and cathode, as the creation of ions is dependent on field strength (volts per metre spacing).

In addition to this effect, ions are discharged at high speed from a pointed wire due to the particularly high field strength around points. The old electrostatic experiment of blowing out a candle with a point discharge from an electrostatic generator is an illustration of this effect (Fig. 9). With the voltage between anode and cathode less than the striking voltage but above the running voltage, current will start to flow only when the discharge is triggered by the injection of ions from the trigger circuit. This is achieved by applying a small positive pulse at the trigger electrode. The amplitude and width of this trigger pulse must be above certain critical values (depending on the shape and spacing of the electrodes) to start the main discharge. Once the main

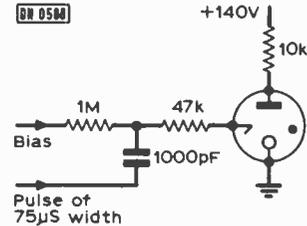


Fig. 10: Characteristics of the Hivac XC23. With bias at 0V, pulse amplitude for transfer equals 91-98V; with bias of +80V, pulse required is 20V min.; trigger resistance equals 47kΩ. Deionisation time is 2mS (time for which $V_a = 0$ to switch off tube).

so that a negative voltage pulse is generated in the anode load resistor and a positive pulse in the cathode load resistor. The voltage drop can be designed to be sufficient to cause the tube to extinguish at the peak of the pulse, so that the tube is ready to fire again at the next trigger pulse. The repetition rate which can be used is limited by the time which must be allowed for all the ions created in the first discharge to recombine before the full voltage is again applied between anode and cathode. For this reason, trigger tube circuits working at rates greater than 4kHz are seldom found, and the circuits are notable for the use of capacitors to spread pulse widths out rather than to sharpen them, as is usually the case.

Figure 12 shows a ring counter circuit using gas trigger tubes. This type of counter circuit is not so familiar to constructors as the binary counters used in transistor circuits, and a description of its opera-

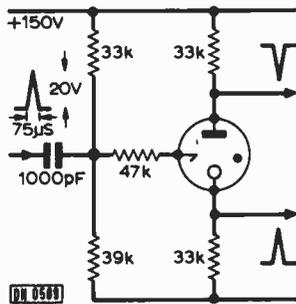


Fig. 11: If the negative pulse is not needed, a capacitor can be connected from anode to earth. The discharge of this will then provide the cathode pulse and the anode load can be raised so that the anode recovers slowly and the tube has ample time to switch off.

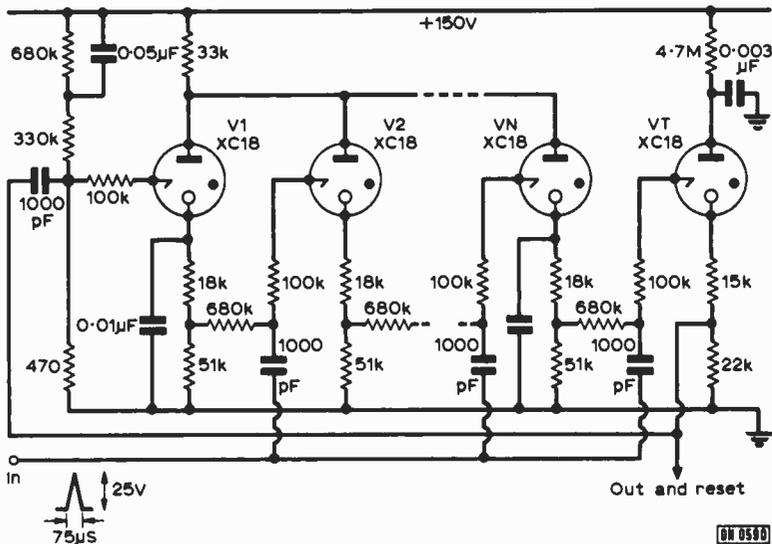


Fig. 12 (right): Ring counter circuit working at 500Hz.

tion might be of interest. The basic principle of any ring counter is that a set of bistable elements is connected in a closed ring in such a way that each trigger pulse fed to a common point turns on the element next to the one previously on, and also turns off that previous element. In the circuit of Fig. 12, imagine that V2 is passing current and that the rest of the tubes are not. Because of the current in V2, there will be a voltage positive to earth developed across the resistor in the cathode lead of V2, and this voltage will bias the trigger electrode of V3 (not shown, but wired in exactly the same way as V2) positive, not enough to fire the tube but enough to make certain that a trigger pulse of about 50V will fire V3. This value of trigger pulse is not sufficient to fire any tube whose trigger electrode is not raised in voltage already, so when a pulse is received at the common input terminal and applied to all the trigger electrodes, V3 is the only tube to fire. When V3 fires, however, the voltage in the common anode line drops, and this drop of voltage is sufficient to extinguish the discharge in V2. The result is that the discharge has moved one tube on with the receipt of one trigger pulse. This action continues from tube to tube as each pulse is received, until the last tube in the set, Vn, is glowing. In a ring-of-ten counter, this would be the tube indicating number nine, and wired to the number nine indicator of a display. This tube is connected to a transfer tube, Vt, and when the next trigger pulse is received, Vt will fire, causing a positive pulse to appear at its cathode load resistor. Vt will extinguish immediately after, however, as the value of its anode load is far too high to permit a continuous discharge, and the current which does flow is due to the capacitor between anode and earth discharging through the tube. The positive pulse at the cathode switches on V1, which has a positive bias on its trigger electrode already, and is also the zero indicator. The same positive pulse is also used as the output pulse of the counter stage, carrying to the next counting ring or to some other output.

Counting tubes

The action of a trigger tube, in which the trigger

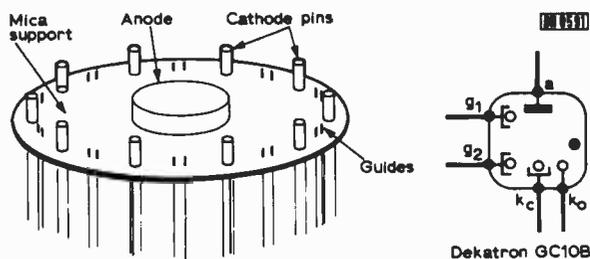


Fig. 13: On the left is shown the principle of construction of a Dekatron; the symbol of the Dekatron GC10B is shown right).

electrode starts off a discharge path which can then spread to the nearest anode, can be used in a tube in which the discharge is passed from one cathode to another, and which also makes use of the fact that the glow in a gas discharge is concentrated at the cathode. The best-known example of this technique is the well-known DEKATRON counting tube in which a central anode rod is surrounded by ten cathode rods (see Fig. 13). The structure of different types of Dekatrons differs in detail, but the type GC10B can be taken as an example of the way in which these fascinating tubes work. In the GC10B, the cathode pin which is used to indicate zero is taken to a base connection (k_0), and all the other cathodes are connected together and taken to another base connection, k_c . At the opposite end, the pins are visible through the glass end of the tube, and the glow round any particular cathode can be clearly seen. Escutcheon plates with the numbers 0-9 can be fitted against the end of the tube and lined up so that the zero of the escutcheon is adjacent to the zero pin of the tube, and the other numbers line up with successive cathodes.

To transfer the discharge from one electrode to another, guide electrodes are used. These are pins located in pairs between the cathodes; all the first pins of each pair in clockwise order are connected together and taken to base connection G_1 , and the second pins of each pair are brought together to the G_2 base connection.

ATTRACTIVE DISCOUNTS ON MANY ITEMS

ELECTROVALUE Electronic Component Specialists

TRANSISTORS

Brand new—no seconds or surplus. Highest quality and reliability. Insulating sets FREE with power types.

MANY HUNDREDS OF DIFFERENT TYPES IN STOCK—THEY'RE ALL IN OUR NEWEST CATALOGUE

1N4148	4p	AF139	33p
1N5399	24p	AF239	36p
2N2046	37p	BC107	13p
2N3055	65p	BC10	12p
2N3702	10p	BC109	14p
2N3703	10p	BC148	9p
2N3704	10p	BC177	15p
2N3819	25p	BC184L	11p
2N4286	15p	BC212L	14p
2N4289	15p	BD130	65p
2N4443	85p	BD131	77p
2N5082	42p	BD132	81p
2N5085	48p	BD135	26p
2N5192	77p	BD136	27p
2N5195	90p	BDY50	97p
2N5457	30p	BFY21	20p
40361	45p	BFY51	30p
40382	45p	BBY39	30p
40432	160p	BY164	45p
40512	179p	MJ481	120p
40669	120p	MJ49	135p
AC128	21p	MJE30	68p
AD142	50p	OA91	6p
AD149	68p	OC35	63p
AD16	42p	SC2N	12p
AD162	40p	SD4	9p


T03 Transistor Covers, ea. 7p

RESISTORS 10% - 5% - 2%

Code	Power	Tolerance	Range in ohms	Values 1 to 9	10 to 99	100 up
C	1/8W	5%	4.7-470K	E24	1	0-8
C	1/4W	10%	4.7-10M	E12	1	0-8
C	1/2W	5%	4.7-10M	E24	1-2	0-9
C	1W	5%	4.7-10M	E12	2-5	2-9
MO	1/2W	2%	10-1M	E24	4	2 net
WW	1W	10%	0.22-3.9	E12	7	6

Codes: C—carbon film high stability low noise
MO—metal oxide ElectroSil TR3 ultra low noise
WW—wire wound Plessey

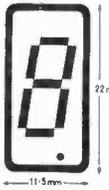Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 72, 91 and their decades. Prices are in pence each for same ohmic value and power rating. NO T mixed values. (Ignore fractions of 1p on total value of resistor order).



MINITRON DIGITAL INDICATOR

TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V D.C. per segment. A limited number of alphabetical symbols also available. In 16 lead DIL case

£2.00
£1.36


Suitable BCD driver type FLL121T nett.
DIL Socket: 16 lead 30p.

No. 3015G showing + or - and fig. 1 and decimal point £2.00.

PRECISION COMPONENTS

Resistors by Rivin 0-1% to 0-01% £1-£2.
Capacitors by MFD 0-01µF-22µF 1% 70p to £1.

SLIDE POTENTIOMETERS

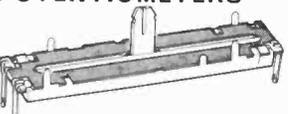

Robust construction, smooth silent action. In values from 4K7 to 1 megohm, linear or log, each 26p. Light grey ecogothon, 10p. Knobs flat, grip type in black/Red/Green/ Yellow/Blue/Light Grey/Dark Grey or White each 5p.

We are appointed stockists for SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Eremco-Wolf "Solderstat" irons we offer this light weight model HMS in 16 or 24 watt, ratings 220/240V a.c. £1.87 nett

INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON

complete with temperature setting control, nett £9.20

DE-SOLDER BRAID 50p

NIPPIBOARD multipurpose component

mounting boards in various working area combinations. 1A one pattern on one board 15p.
2A 2 patterns side by side 28p.
2AS dual channel 28p.
3A 3 patterns alongside 38p.
4AS dual channel 2 above, 2 below 44p.
In full range up to 10A.

TYGAN 36" x 27" £1.58, 18" x 27" 83p.
VYNAIR 36" x 25" 93p. 15" x 25" 50p.
(Pattern Book 3p & S.A.E.)

SIEMENS TTL I.Cs

Prices quoted here are nett.

FLH101 (7400)	80p	FLJ21 (7475)	45p
FLH201 (7401)	20p	FLJ141 (7474)	45p
FLH191 (7402)	20p	FLJ151 (7475)	45p
FLH291 (7403)	20p	FLJ131 (7476)	45p
FLH211 (7404)	25p	FLH221 (7480)	68p
FLH271 (7405)	25p	FLH231 (7482)	87p
FLH381 (7408)	25p	FLH241 (7483)	1.82
FLH391 (7409)	25p	FLH341 (7486)	33p
FLH111 (7410)	20p	FLH191 (7490)	80p
FLH351 (7413)	35p	FLJ221 (7491)	AN) 1.28
FLH121 (7420)	20p	FLJ171 (7492)	85p
FLH131 (7430)	20p	FLJ181 (7493)	80p
FLH141 (7440)	24p	FLJ231 (7494)	1.13
FLH101 (7414)	1.22	FLJ191 (7496)	87p
FLH121 (7442)	1.18	FLJ161 (7498)	80p
FLH361 (7443)	1.45	FLJ261 (7498)	1.48
FLH371 (7444)	1.45	FLJ301 (74100)	1.64
FLH151 (7450)	20p	FLJ281 (74104)	43p
FLH161 (7451)	20p	FLJ271 (74107)	52p
FLH171 (7453)	20p	FLK101 (74121)	48p
FLH181 (7454)	20p	FLJ201 (74190)	1.80
FLY101 (7466)	20p	FLJ211 (74191)	1.80
FLJ101 (7470)	45p	FLJ241 (74192)	1.74
FLJ111 (7472)	32p	FLJ251 (74193)	1.74

BAXANDALL SPEAKER

As designed by P. J. Baxandall and originally described in "Wireless World". Complete kit inc. speaker and special cabinet kit (18" x 12" x 10") cut to size. 10 watt RMS/15Ω loading. Part cost of carr. and ins. in U.K. 60p

Speaker unit and equaliser kit post free nett £4.81. Pack flat cabinet assembly (all cut to shape) natural teak finish £9.00 nett. Part cost of carr. in U.K. 60p.

CARBON SKELETON PRE-SETS

Small high quality, type PR linear only: 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.

ZENER DIODES 5% full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 48p each.

Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

MINIATURE TOGGLE SWITCHES 2A/250V. DP/DT, 48p.

MAINLINE AMPLIFIER KITS 70 watt power amp. module kit, £12.80 nett. Power supply kit, 26.50 nett.

SIEMENS THYRISTORS 0.8A—400V 56p; 600V 80p. 3A—400V 70p; 600V 88p.

Q.E.D. High quality amplifier systems. Built to your personal specifications. Enquiries invited. Please quote P.W.8.

SIEMENS CAPACITORS

POLYCARBONATE—5% TOLERANCE

250V, up to 0-1µF; 100V/0-1µF and above
0-01; 0-012; 0-015; 0-018; 0-022; 0-027; 0-033; 0-047; 0-056 each 4p
0-068; 0-082; 0-1; 0-12; 0-15 each 4p.
0-18; 0-22; each 5p.
0-27; 0-33; 6p; 0-397p; 0-478p; 0-56 10p; 0-68 11p; 1µF 13p.

ELECTROLYTIC (values in µF/V)

0-47/100; 1/100; 2-2/63; 4-7/35; 10/25; 22/16; 47/10; 47/25; 100/10; 22/3—each 7p.
10/63; 22/35; 47/35; 100/16; 100/25; 220/6; 220/10; 220/16; 470/3 each 7p.
47/60; 47/63; 100/35; 220/16 each 8p.
100/50; 220/35; each 10p; 100/63; 470/25; 1000/10 each 12p
220/63; 470/35; 1000/16; each 17p.
1000/25—20p; 470/63; 1000/35 each 23p; 2200/25—38p.
1000/63; 2-200/35; 4-700/16—each 40p.
Tantalum and other capacitors etc.—see latest 1972 Catalogue—issue No. 6.

1972 ELECTROVALUE CATALOGUE (NO.6)

3rd printing 96 pages plus cover. More items, more information, more diagrams than ever. Latest price and information details. Post free in U.K.—10p.

NEWMARKET LINEAR I.Cs

LIC 709C/14 Dual in line—34p | 709C/5, T05 39p
LIC 741C/14 Dual in line—40p | 741C/5, T05 42p

CARBON TRACK POTENTIOMETERS

long spindles. Double wipers for low noise. SINGLE GANG P-20 lin. 100Ω to 2-2MΩ. 12p; Single gang log, 4-7KΩ to 2-2MΩ. 12p; Dual gang linear 4-7KΩ to 2-2MΩ. 42p; Dual gang log, 4-7KΩ to 2-2MΩ. 42p; Log/antilog, 10K, 22K, 47K, 1MΩ only 42p. Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra. Only decades of 10, 22 & 47 available in ranges quoted. DUAL CONCENTRIC in any combination of P-20 values as above, 60p; with switch, 72p. Knobs, pair 24p

DISCOUNTS

10% on orders £5 to £15.
15% on orders over £15. No discount on items marked Nett. Prices subject to alteration without notice.

POSTAGE AND PACKING


FREE unless otherwise stated. Handling surcharge 10p on mail orders under £2. Overseas orders: carr. & Insurance charged at cost. U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

ENQUIRIES FROM TRADE AND OTHER LARGE QUANTITY USERS INVITED.

ELECTROVALUE

(Dept. P.W. 1072) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 OHB
Hours: 9—5.30; Sat. 1 p.m. Tel.: Egham 3603 (STD 0784-3) Telex 264475
ELECTROVALUE LTD—AN INDEPENDENT COMPANY SINCE ITS ESTABLISHMENT ORIGINALLY IN 1965

LINDAIR (ELECTRO-TECH) LTD

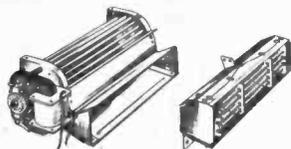

TANGENTIAL HEATER

Silently driven by a shaded pole Molecax motor. Compact, powerful and quiet running with aluminium impeller (outlet $6\frac{1}{2} \times 1\frac{1}{2}$). Mains voltage. PLUS matching heater unit with spiral element. May be switched for 500 or 1,000 watts. PRICE ONLY P. & P. 40p

£1.60

SYNCHRONOUS AUTO-RESET PROCESS TIMER

By LONDEX LIMITED

Type IMP Mk. 2. Brand New and Boxed. These well known timers are already in world-wide use and are perfect for Industrial Electronic Timing. Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be interconnected to give control of a series of processes. 230/250v. 50Hz, also available 60Hz. 15 minutes full scale, 15 secs. per division. Driven by self-starting 1/20 motor. Contact rating 5 amp at 250v. a.c. Incorporates solenoid operated clutch. Also, lever actuated micro switches. Normal price probably in excess of £16. Complete with multi-pin connector as illustrated.

OUR PRICE ONLY

£6.50



SEEN THIS ?

This is the only way we could illustrate this fabulous item.

NORPLEX the famous American fibre-glass copper-clad laminate. Finest quality with Woven Glass base of Epoxy-resin. Excellent mech. and elec. conductive properties. Heat Resistant. Ideal for P.C.s., etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST. Sizes: 12" x 24", 24" x 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single sided copper with thicknesses of $\frac{1}{32}$ ", $\frac{1}{16}$ ", $\frac{3}{32}$ ", also Double sided $\frac{1}{32}$ ", $\frac{1}{16}$ ", $\frac{3}{32}$ ".

PRICE ONLY £1 per sq. ft. £8 per full sheet. P. & P. 25p up to 4 sq. ft. Over 4 sq. ft. (cut sizes only) Post FREE. Full sheets post by rail G.B. only £1 one or more sheets.

MICRO-LITES

Wonderful engineering—micro miniature incandescent lamp small enough to pass through the eye of a needle! 1,000's of uses. Will operate from the output of a transistor. Rating: 1.6v, 10-15ma. Size 4.4×1.4 mm. dia. Leads 23mm. These fantastic lamps have a life expectancy of 1,000 hrs.

OUR PRICE

£3.25

per doz. Free P. & P.



NEW AND UNUSED

Postal or carriage charges are for Great Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50, cash with order please.


FURTHER BULK PURCHASE

SILVANIA MAGNETIC SWITCH

NOW COMPLETE WITH REFERENCE MAGNET! A magnificently activated switch. Vacuum sealed in a glass envelope. Silver contacts normally closed, rated 3 amp at 120v, 11 amp at 240v. Size (approx.) $17\frac{1}{2} \times 17 \times 2$ " dia. Ideal for Burglar Alarms, Security systems, etc., and wherever non-mechanical switching is required. New Lower Prices. Only £2.10 for 12, £8 for 50 or £15 for 100 complete with magnet.

£2.10

PROGRAMMER TIMER BY HONEYWELL

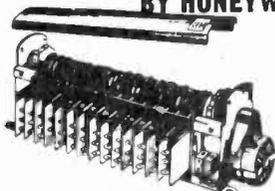

A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of £15.00 plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p P. & P.

£5.75

315, EDGWARE ROAD, LONDON W2. Tel: 01-262 2251. Open 9 a.m.-6 p.m. MON to SAT

SAVE TIME AND MONEY

LIST PRICE **£6.25** | OUR PRICE **£4.84**



As supplied by us to SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets $21\frac{1}{2} \times 11\frac{1}{2} \times 6\frac{1}{2}$ ". Size of drawers $6\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ ". Other sizes available. Callers welcome Mon-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. NEW as illustrated OUR PRICE ONLY £4.84 plus 35p carriage on orders less than £10. Money back guarantee. SEND FOR FREE COLOUR BROCHURE.

TRADE AIDS

(DEPT. PW3), 111 CHILTERN DRIVE, BERRYLANDS, SURBITON, SURREY

01-399 4383
100 yds. Berrylands Railway Station.

TRANSFORMERS

DOUGLAS GUARANTEED 12 or 24 volts

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS†	£0.91 9p
12V x 2 500 mA x 2	MT213 CT†	£0.87 19p
12V x 2 1A x 2	MT 71 AT†	£1.45 24p
12V x 2 2A x 2	MT 18 AT†	£2.08 30p
12V x 2 3A x 2	MT 70 AT†	£2.59 32p
12V x 2 4A x 2	MT 108 AT†	£2.92 34p
12V x 2 6A x 2	MT 72 AT†	£3.38 42p

30 volts. All tapped at 0-12-15-20-24-30V

Out. put	Ref. No.	Price P.P.	Out. put	Ref. No.	Price P.P.
500 mA	MT 112 CT†	1-12 16p	3A MT 20 AT	2-64 32p	
1A	MT 79 AT†	1-55 29p	4A MT 21 AT	3-10 40p	
2A	MT 3 AT	2-23 30p	5A MT 51 AT	4-31 42p	

50 volts. All tapped at 0-19-25-33-40-50V

500 mA	MT 102 AT†	1-45 24p	3A MT 105 AT	3-91 41p
1A	MT 103 AT	2-00 39p	4A MT 106 AT	5-09 41p
2A	MT 104 AT	3-10 32p	6A MT 107 AT	7-47 50p

60 Volts. All tapped at 0-24-30-40-45-60V.

500 mA	MT 124 AT†	1-46 30p	2A MT 127 AT	3-18 41p
1A	MT 126 AT	2-24 32p	3A MT 125 AT	4-59 41p

AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 115 CT	£0.89 16p
75 VA		MT 64 AT	£0.78 30p
150 VA	0-115-200-220-240	MT 6 AT	£2.15 82p
200 VA		MT 65 AT	£3.00 32p

400 V. Output at 60 HZ. Ref. IT3 AT Price P. & P. £2.80 20p
C-D Ignition system by R. M. Marston


EQUIPMENT RANGE

Sec. Output (r.m.s.)	Ref. No.	Price P. & P.
3-0-3 V.	200 mA MT 238 CS†	£0.89 8p
0-0-0 V.	100 mA MT 13 CS†	£0.91 6p
12-0-12	50 mA MT 239 CS†	£0.91 8p
20-0-20	30 mA MT 241 CS†	£0.91 8p
0-20 x 2	300 x 2 MT 214 CT†	£1.21 10p
0-0-0 x 2	500 mA x 2 MT 207 CT†	£1.46 19p
0-15-20 x 2	500 mA x 2 MT 205 AT†	£2.12 29p
0-15-27 x 2	500 mA x 2 MT 203 AT†	£2.45 29p
0-15-27 x 2	1A x 2 MT 204 AT†	£2.42 30p
10-12-0-12-20	700 mA (d.c.) MT 221 AT†	£1.11 26p

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; † with interwinding screen; ‡ untapped 240V Primary; † Primary tapped at 210-240V. other Primaries tapped at 200-220-240V. Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD. (DEPT. M06PW), Thames St., LOUTH, Lincs. LN11 7AD

RADIO BARGAINS

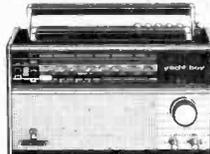

Grundig Mariner TR865	£35.00
Grundig Solo Boy	£16.50
Grundig Music Boy	£26.00
Grundig TR600	£28.50
Grundig Elite Boy 210	£29.00
Grundig Elite Boy 500	£26.50
Grundig Melody Boy 500	£26.50
Grundig Melody Boy 1000E	£41.50
Grundig Satellit 1000	£125.00
Grundig Ocean Boy 3005	£62.00
Grundig Yacht Boy	£34.50
Grundig RF430	£26.50
Koyo KTR1661 8w.b.	£40.25
Koyo KTR 1663 or 1664 8w.b.	£47.50
Koyo KTR1770 11w.b.	£66.00
Alwa AR158	£31.00
Toshba IC70	£16.50
Alwa AR158 6w.b. (Inc. air)	£31.00
Hitachi WH1160 with D.F.	£22.50
ITT/KB Golf	£26.50
ITT/KB Touring Int. Marine	£45.00

FREE With each set "Guides to Broadcasting Stations" (160 pages)

WILMSLOW
AUDIO, Dept. PW,
10 Swan St. Wilmslow,
Cheshire, SK9 1HF

The action is as follows (Fig. 14): with about 475V applied to the anode through an 820kΩ resistor, and other details as shown in Fig. 14, a discharge must exist between the anode and one cathode. Since all the cathodes are joined together, and since the running voltage of a gas discharge is well below the striking voltage, once one cathode has started a discharge it cannot spread to any other cathode except by the action of the guides which will be described, unless one cathode is made more negative than any other. The only cathode with which this can be done is the zero cathode which is taken to a separate pin, so that the Dekatron can be made to read zero when power is first applied, or when a fresh count is wanted.

If now all the first guides (G_1) are pulsed negative, the glow will shift from the cathode to the nearest guide 1 and stay there. If the second guides are now pulsed negative just as the first guides are rising again in voltage, the discharge will shift to the nearest G_2 , which will again be one step clockwise. When this guide's voltage rises again, the glow transfers to the next cathode, which is one cathode on from the starting point. The result is that every time a set of pulses is applied to the guides, the glow shifts clockwise from one cathode to the next, and so counting has been achieved. This process continues until the glow lands on the zero cathode, which is taken to the -20V line through a 150kΩ load resistor, so that a positive pulse is obtained across the resistor whenever the glow lands on zero. This can be used to transfer the count to the next stage, as the positive pulse can be inverted by a valve or trigger tube and processed to provide the double pulse needed for the next stage.

The Dekatron system is at present the most economical method of counting and displaying, since both operations are achieved in one tube. It is, however, essential that the circuits published by HIVAC should be adhered to exactly. Any variation in the pulse width and amplitude, or in the time lag between the pulses applied to guides 1 and 2 can cause misfiring, and most of the problems encountered in Dekatron circuits are easily cured by attention to the pulse system. Fig. 14 shows the circuits which should be used for driving with single pulses, double pulses and sine waves respectively. The sine wave circuit is of particular interest, as the 50Hz mains provide an accurate frequency standard for digital clocks, the design of which is particularly easy using Dekatrons.

Not every count is to ten, however, particularly in the case of digital clocks, and the Dekatron Selector tubes such as the type GS10C are designed with this in mind. Each cathode is taken to a separate pin on the 12-pin base, with the anode as a centre pin, and can be wired as a counter or as a transfer cathode. A transfer cathode is one which passes the count as a pulse to the next stage, and also acts as the zero to which some other cathode will reset. This enables us to have any count up to nine followed by a zero, and the range has been extended by tubes which count to 12. Another advantage of the selector type of tube is that it no longer ties us to the Dekatron type of display, but enables us to display on a Digitron type of tube, described later.

The standard range of Dekatrons includes counters and selectors working at rates up to 4kHz, but another range of Dekatrons using a third set of guides connected to the reset line through a 220kΩ resistor, and an output cathode guide connected to

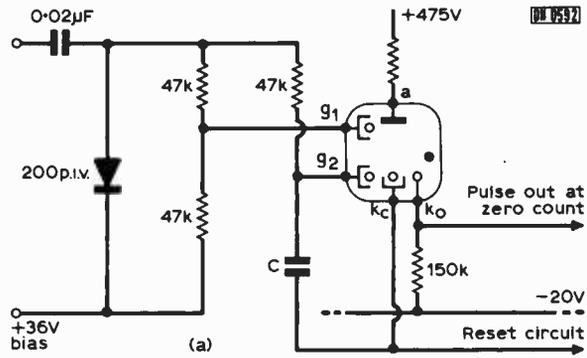


Fig. 14a: Integrated pulse drive. The value of C depends on the pulse width and repetition rate being used.

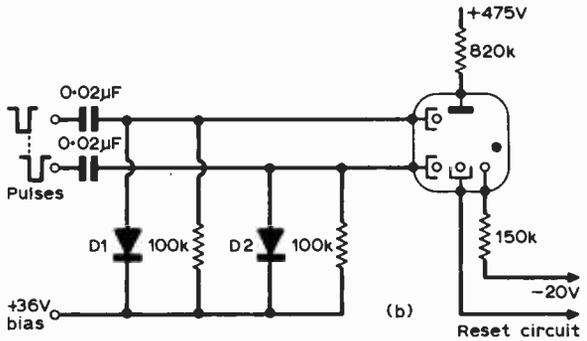


Fig. 14b: Double pulse drive for the GC10B.


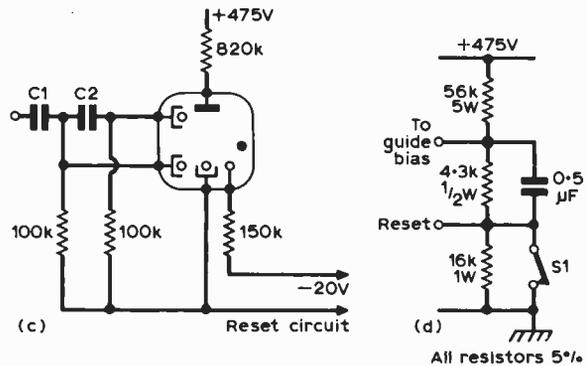


Fig. 14c: Sine-wave circuit (left)
 Frequency 50Hz 100Hz 200Hz 500Hz 1kHz 2kHz 4kHz
 C1 (μF) 1.5 0.82 0.33 0.15 0.082 0.033 0.015
 C2 (μF) 0.1 0.05 0.02 0.01 0.005 0.002 680pF
 Reset circuit is shown on right. To reset, S1 is opened, taking cathode Kc and guides to +120V and so transferring the glow to Ko.

the output cathode by a 220kΩ resistor, can be operated at speeds up to 20kHz.

Alpha-numerical indicators

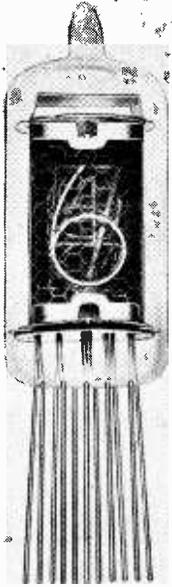As we have seen earlier, when a voltage is applied between the anode and the cathode of a gas-filled tube, a glow appears round the cathode. When a.c. is applied, of course, both electrodes are seen to glow.



A typical gas filled read-out tube. When a voltage is applied between the anode and cathode a glow appears around the cathode. By making the cathode in the shape of numbers or letters, it will glow when the voltage is sufficiently negative to cause striking.

The glow is due to the recombination of ions which have been formed by collisions and is most noticeable at the cathode because this is the place where electrons are being rapidly accelerated in the face of negative ions moving in the opposite direction. The glow exactly surrounds the shape of the cathode, and does not extend to more positive electrodes.

If the cathode is made in the shape of a letter or a number, this figure or number will be seen as a glowing shape whenever the cathode is sufficiently negative to the anode to strike and run. If a number of separately connected wires are shaped in the form of numbers 0-9, each number will display only when the wire forming it is sufficiently negative to the anode to form a gas discharge.

The *Hivac* Numicators are tubes of this type, and the range of types is large. Tubes may be viewed end-on or side-on according to the type of construction of the tube. Numicators can be driven from Dekatrons, provided that trigger tubes or other inverter stages are used to change the positive pulses at the cathodes of the Dekatron to the negative pulses used at the cathodes of the Numicator. Perhaps "pulse" is a misleading word in this application, because the top of the pulse will be as long in the time sense as the figure is to be displayed.

Most Numicators are designed for steady operation, but some are intended to be used in what is called the "anode stroking technique," often used in connection with digital counters.

Digital counters can readily be arranged to give a readout whenever a clock pulse is received, and the readout can be converted to decimal form and used to drive Numicators. Considerable economy in circuitry can be arranged if the decimal readout is attached to all the Numicator cathodes; for example, in a five figure readout, there would be one decimal converter with the zero output connected to all the five Numicator zeros, the "one" output to all the Numicator "ones", the "two" to all the "twos" etc. The decimal output and the tubes are then switched in sequence, so that the units tube has its anode volts pulsed just as the decimal output gives the unit figure pulse to all the Numicator cathodes, with the result that only the units tube displays a figure. On the next pulse, the tens tube is activated to display

the decimal output from another store, so that each tube flashes a digit in sequence. Because of the clock pulse rate used, the display looks continuous. This is not a technique which would be used in small counters, but it is extremely useful in small computers, particularly in conjunction with integrated circuit counters.

Thyratrons

Thyratrons are the big brothers of trigger tubes. Like trigger tubes, they are made to conduct by the application of a positive pulse to a third electrode; unlike trigger tubes, they use hot cathodes and can operate at very high voltages indeed—one type listed by *English Electric* quotes a peak forward voltage of 120kV and with large currents, up to several thousand amps, flowing. Small thyratrons are made in glass envelopes and resemble output valves at first sight, the larger types have ceramic casings.

The small type of Thyratron has a heated cathode, a grid similar to the control grid of an output valve, and an anode which is often finned and connected to a thick pin set in the glass bulb for maximum heat dissipation. In operation, the heaters must be switched on before high voltage is applied, this is usually done automatically by means of a thermal delay circuit, since failure to observe the correct delay period would be fatal to the thyratron. When the heaters have reached full temperature, the grid voltage can be applied, this is a negative bias sufficient to prevent any electrons passing the grid, enough, in fact, to prevent electrons from being emitted to any noticeable extent from the cathode. The positive anode voltage can then be applied.

If the grid is now pulsed positive, the tube conducts strongly due to the ionisation of the gas by the electrons from the cathode, and this current will continue until the voltage at the anode is reduced to a low value. After a short "recovery time", the tube can be fired again if the anode voltage has also recovered to its previous value. What makes the thyratron unique is its ability to switch very high currents very rapidly and at a high forward voltage. By very rapidly, we mean delay times of around 20-120 nanoseconds in the most advanced types.

Thyratrons are used to control spot welders, to pulse radar transmitter magnetrons, and to operate other short time, high energy devices such as the *Kerr Cell* used in high speed photography. They also find extensive use in large invertors (converting a.c. to d.c.) such as are used at each end of the cross-channel d.c. cable. One intriguing use is as "electronic crowbars". In modern electronic equipment, protection against faults by means of fuses is not very effective because of the time which a fuse needs to blow. Even if this time is measured in milliseconds, much damage can be done, and the idea of the electronic crowbar is a device which will come into operation much more quickly than a fuse, shorting out the voltage across the circuits and taking the current which will eventually blow the fuse. This use demands a device which can be switched into conduction very quickly and which will take a large current in the time before a fuse blows—the Thyratron is ideal, though for the smaller sizes thyristors are taking over. ■

The Author gratefully wishes to acknowledge the help of HIVAC LTD. in the preparation of this article.

Disco

SOUND & LIGHTING EQUIPMENT

from 4 SPECIALISED DISCO STUDIOS

HIGH POWER SPEAKER SYSTEMS

Strong leather cloth finish 1" board, fully lagged. Fitted high efficiency 8 or 16 ohm speakers.

PRINCE. 50 watt rms. 12". Size 24" x 16" x 12".
CONSORT. 100 watt rms. 2-12" speakers. Size 36" x 18" x 12".
MAJESTIC. 100 watt rms. 15" Crescendo. Size 38" x 24" x 16".
SOVEREIGN. 100 watt rms. 18" Bass. 12" Full range. Size 50" x 26" x 14".

FULL RANGE OF MICROPHONES, STANDS, ETC. ALWAYS IN STOCK



SOUND CONTROLLED AND SOUND TO LIGHT UNITS

Mid, Treble and Bass Channels, up to 1kw of lamps per channel plus override switching.

DJ80L. Sound to light. Takes output from most amplifiers. Adjustable levels.

DJ40L. Sound controlled version. Built in microphone, no connections required.

ASSEMBLED DISCO THEQUES

DISCO-PLINTH. Consists of 2 turntables fitted with high quality ceramic cartridges. The unit has a built in cross-fade rotary control for transferring the sound from left to right decks. The unit has no amplification built in and must be used with amplifiers such as the D.J. 105S or D.J. 70S. Size 32" x 14" x 7" (incl. lid). **£55-00**

DISCO-IMP. The latest addition to the Disco sound range of discotheques. Even smaller and more compact than the Disco-Mini, it contains all the necessary features for the smooth running of a mobile unit. Size 29" x 18" x 7". **£79-00**

DISCO-MINI. Complete portable Disco with built-in full function preamplifier/mixer. For use with any power amplifier such as "Discmaster". Size 30" x 20" x 8". **£98-50**

DISCO-STANDARD. Has all the facilities of the Disco-Mini with the addition of a built-in 100 watt power amplifier making it a completely self contained disco unit. A V.U. meter gives visual indication of output levels. Size 32" x 27" x 7 1/2". **£180-00**

DISCO-SUPER. A slightly larger version of the Disco-Standard. Fitted individual controls for both mic. and deck inputs plus a cross-fade for deck to deck transfer. A built in P.F.L. cueing system, mic. over-ride, also a V.U. meter gives visual indication of output levels.


DJ. 301. (3000w) 3-channel psychodelic light unit is a standard fitting. Deck cut out switches are also featured for ease of cueing. Size 28" x 27" x 10". **£224-00**

DISCO-SUPREME. All facilities of the Disco-Super plus a third turntable which can be used for Jingles or other effects without using the main deck system. Flexi lights are also fitted. Size 50" x 27" x 10". **£261-00**

PA-DISCO AMPLIFIERS



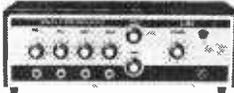DISCO-AMP. 100 watt rms. output for 8-16 ohms, 4 channel inputs, 2-mic, 2 decks. Separate volume control plus masters. Response 30Hz -30KHz, distortion less than 1%. Treble/Bass/PFL/Mic over-ride etc. Panel size 16 1/2" x 7".



DJ70S MIXER/AMPLIFIER. 70 watt rms. output for 8-16 ohms. 2-mic, 2-aux/decks. Master volume/Bass/Treble. Size 15 1/2" x 5" x 6".

DJ.105S. 30 watt rms. version. Size 11 1/2" x 5" x 6".

DISCMaster SLAVE AMPLIFIER. 100 watt rms. for 8-16 ohms. **£59-50**

NEW D.J. 500 SERIES P.A. AMPLIFIERS

50 WATT, 70 WATT & 100 WATT MODELS

This new range incorporates many features that make them ideal for the professional user, clubs, discotheques, factories etc. Fibre glass P.C. Boards are used throughout with low noise silicon transistors, high stability resistors, generally rated components and hand work assembly to ensure reliability and quality.

★ Exclusive "Fall Safe" Electronic Protection circuit.

★ Fault Condition warning lamp.

★ Built in bass boost

below 30 Hz.

★ 4 channel mixer with slider controls.

All three amplifiers have a built in emitter follower output socket for connecting a slave amplifier to enable the power output to be increased up to 1000 watts or more if required. A matching range of slave power amplifiers and a separate matching 100v line transformer is available

SPECIFICATION

Frequency Response 50-20,000 Hz ± 3db (10dB Bass Boost at 30 Hz)

Signal/Noise Ratio better than -60db.

Harmonic Distortion less than 1%

Speaker Impedance 8-16 ohms.

Inputs: Mic 1 & 2 5mV at 50K ohms (50 or 600 ohm to order)


Aux 3 & 4 100mV at 1 meg ohm.

Size (all models) 15 1/2" x 5" x 6".

Power Output: Model D.J.500 — 50 watts R.M.S. **£56-25**

(at 8 ohms) Model D.J.700 — 70 watts R.M.S. **£87-50**

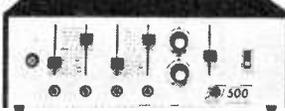Model D.J.1000 — 100 watts R.M.S. **£79-00**



DISCO MINI

Hardly larger than a suitcase yet contains all the necessary features for a high quality mobile unit. The pre-amp has separate tone controls for both mic. and decks, and each input has its own individual volume controls and inputs, plus the addition of a cross fade for deck to deck sound transfer. A built in P.F.L. system for cueing, together with mic-over-ride facility are standard on all units. Response 20-20,000 Hz. Mic. input 5mV. 50K. Output 1 volt.

McDonald M.P.90 Turntables are used with high quality ceramic cartridges, and each deck has its own individual cut out switch fitted. This unit is suitable for Discos or Clubs having a power amplifier, or for use with the Discmaster 100 watt power amplifier as above. Size 32" x 20" x 8". **£98-50**.



EFFECTS PROJECTORS



A small selection from our vast stock.

DISCO COLT. 150 watt.

LIQUIMATIC MINI. 50 watt Q1 with 6" wheel

DISCOWHEEL. 50 watt Q1 with quick change

Cassette.

GNOME 150. 150 watt Q1 with Cassette.

LIQUIMATIC. 150 watt Q1 with 6" wheel

PLUTO TUTOR-2. 250 watt Q1 with Cassette

and 8" wheel.

TUTOR-2. with Liqueplode Tank

KALEIDOSCOPE LENS. (for Tutor-2) 8"

Liquid Wheel and Crystal Wheel Liquid

Cassette and Moire (24 different types to

choose from). Portable Hi-Power Strobes.

YOU WILL BE SURPRISED BY THE

LOW PRICES & PERFORMANCE

SDL POWER SPEAKERS

High efficiency 12" speakers. Ferrite magnets. Heavy duty voice coils and cones for Disco and Group use.

18" 50 watt rms. 8 ohm Full range.


18" 25 watt rms. 15 ohm Mid-Treble.

15" 50 watt rms. 15 ohm. Full range.

15" 100 watt rms. 15 ohm. Bass.

18" 100 watt rms. 15 ohm. Bass.

DISCO SPOT BANK

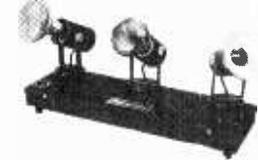

Designed to take three E/8 Type spot or colour bulbs up to 150 watts each. The unit is of all metal construction and has one 3-pin mains input socket plus one 3-pin mains output socket for connecting more than one bank together if required. The unit can be left free-standing or wall mounted if needed. Black crackle finish gives the unit a very professional appearance.

Size 18" x 6" x 7" (excluding bulbs)

Also in stock: Ultra Violet Spot Lamps and Fluorescent Lamps, Standard and Colour Spot Lamps and Fittings, Rotating Colour Displays, Flexlights, Fibre Optics, Dimmers, Flashers Effects Folds, etc. Your enquiries invited.

MIXER UNITS

DJ.101. Battery powered, 6-channel, variable levels, 3 x 50k mic., 1 x 100mV. aux., 2 x 100mV p.u. Output 250mV.

DJ.102. Mains operated, 4-channel, variable levels. 2 x 50k mic., 2 x 100mV p.u. PFL control, master volume, mic. over-ride, output variable 0-500mV.

DISCO 40. Pre amp part of Disco amp (see above). All facilities. Output will drive up to ten 100 watt amplifiers.

Discoscene

536, Sutton Road,
Southend, Essex.
(0702) 611577

Discosound

122, Balls Pond Road,
London, N.1.
(01) 254 5779

Discosound

(Birmingham) Ltd.
494, Bristol Road,
Selly Oak, B'ham 29.
(021) 472 1141

Henry's Disco

309, Edgware Road,
London, W.2.
(01) 723 6963

CHECK WITH YOUR NEAREST STUDIO FOR LATEST PRICES AND DETAILS (TRADE AND RETAIL SUPPLIED)

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1

THE VALVE SPECIALISTS Telephone 01-722-9090

OA2	.30	8BR7	.79	6R7M	.55	128K7	.24	150B2	.58	EBF83	.38	EL85	.38	EL34	.44	MHL26	.75	PL509	1.30	UM80	.33	AC156	.20	BCY33	.20	OA81	.09
OB2	.30	8BR8	.63	68A7GT	.38	14H7	.48	807	.59	EBF89	.38	EL86	.38	EL35	1.00	P61	.44	PL802	.75	UY41	.38	AC157	.25	BCY34	.23	OA85	.08
OZ4	.25	6BW6	.72	68A7M	.38	14S7	.75	5702	.80	EBL21	.60	EL87	.23	EL36	.74	PAFC80	.32	PM84	.31	UY85	.32	AC165	.25	BCY38	.23	OA90	.13
1A3	.23	6BW7	.50	68C7GT	.33	19A5	.53	5763	.55	EC86	.59	EL88	.53	EL37	.23	PC86	.44	FX4	1.38	UY11	.32	AC166	.25	BCY39	.25	OA91	.09
1A7GT	.38	6B26	.31	68G7GT	.33	19B9G6	.30	AC/PEN	.98	EC88	.59	ELL80	.75	EL42	.53	PC88	.44	FP33/2	.50	UI2/14	.38	AC176	.55	BF158	.29	OA200	.09
1B3GT	.35	6CB6A	.28	68H7	.53	19G66	.50	AC2/PEN	.98	EC92	.34	EM80	.37	EL41	.50	PC95	.53	PY80	.38	U19	1.73	AC177	.55	BF159	.25	OA202	.10
1H5GT	.38	6C4	.28	68J7	.35	20D4	1.05	DD	.98	ECC32	1.50	EM81	.37	EL84	.21	PC900	.29	PY82	.23	U22	.39	AC178	.25	BF163	.20	OC23	.38
1L4	.18	6C9	.73	68K7GT	.23	20F2	.85	AC6/PEN	.38	ECC33	1.50	EM83	.75	EL85	.40	PC824	.27	PY83	.26	U25	.53	AC179	.19	BF180	.30	OC24	.38
1N6GT	.87	6CD6G	1.08	68Q7GT	.38	20L1	.98	AC/TH1	.50	ECC40	.60	EM84	.31	EL86	.38	PC845	.24	PY86	.31	U45	.78	AC180	.18	BF181	.40	OC25	.38
1R5	.28	6CG8A	.50	60F4GT	.60	20P1	.50	AC/TP	.98	ECC81	.18	EM85	1.00	EL87	.23	PC888	.39	PF600	.95	U52	.30	AC181	.19	BF185	.45	OC28	.60
1R4	.22	6CH6	.33	6V80	.17	20P3	.78	AL60	.78	ECC82	.19	EM87	.43	EL88	.53	PC89	.42	PF800	.42	U51	.60	AC182	.18	BF194	.15	OC29	.38
1U4	.29	6CL6	.48	6V6GT	.27	20P4	.59	ATP4	.12	ECC83	.21	EM81	.29	EL89	.53	PC8189	.48	PF801	.21	U251	.65	AC183	.18	BF195	.25	OC35	.38
1U5	.48	6CM7	.50	6X4	.20	20P5	1.00	AZ1	.40	ECC84	.28	EM81	.35	EL90	.53	PC8780	.26	PZ30	.48	U301	.40	AD140	.36	BFY51	.19	OC36	.48
2D21	.35	6C05	.30	6X5GT	.25	25A6G	.29	AZ31	.46	ECC85	.32	EM81	.54	EL91	.53	PC8200	.68	R16	1.75	V7501	.15	AF117	.19	BYZ11	.25	OC74	.23
2GK5	.50	6C7	.43	7B6	.58	25L6G	.20	AZ41	.53	ECC88	.35	EM84	.50	EL92	.53	PC8289	.17	R17	.88	VU111	.44	AF121	.30	BYZ12	.25	OC75	.11
3A4	.25	6D0W	.50	7B7	.52	25Y5G	.43	CL33	.90	ECC189	.48	EM87/6	.27	EL93	.53	PC8183	.54	R19	.28	VU120	.60	AF124	.25	BYZ13	.25	OC76	.15
3D6	.19	6DT6A	.50	7H7	.28	25Z4G	.23	CV3	.53	ECC807	.59	EM88	.40	EL94	.53	PC8284	.32	SP1	.33	VU120A	.60	AF125	.17	CG126	.20	OC77	.27
3Q4	.38	6EWF6	.55	7K7	.65	25Z5	.40	CV1C	.53	ECC807	.59	EM88	.40	EL95	.53	PC8505/85	.27	TH33	.98	VU133	.35	AF126	.18	FBY14	.23	OC78	.15
3QG5T	.35	6F1	.59	7Y4	.80	25Z6G	.43	CV31	.29	EF80	.27	EZ41	.42	EL96	.53	PC860	.26	TP2620	.98	W107	.50	AF129	.65	FBY41A	.23	OC78D	.15
384	.23	6F6	.63	7Z4	.50	30A5	.44	DAF91	.20	EF82	.25	EZ80	.19	EL97	.53	PC8636	.36	UBA80	.30	W729	.60	AF178	.68	GD9	.20	OC81	.11
4C86	.50	6F13	.38	9BW6	.50	30C15	.55	DAF96	.33	EF86	.64	EZ81	.20	EL98	.53	PC8640	.14	UAF24	.49	X41	.50	AF180	.48	GET113	.20	OC81D	.11
5CG8	.50	6F14	.40	9D7	.78	30C17	.74	DP91	.14	EF804	.34	FW4/800	.75	EL99	.53	PC8640	.14	UBC41	.45	Transistors		AF186	.65	GET118	.20	OC82	.11
5T4	.30	6F18	.45	10C2	.49	30C18	.58	DP96	.34		2.10	GY601	.75	EL100	.53	PC8640	.14	UBC81	.45	Diodes		AF189	.65	GET119	.20	OC82D	.11
5U4G	.30	6F23	.65	10DE7	.50	30F3	.51	DH76	.28	ECH21	.63	GZ30	.33	EL101	.53	PC8640	.14	UBF80	.28	2N404	.18	BA102	.45	GET173	.38	OC83	.20
5V4	.25	6G07	.65	10E7	.75	30F11	.58	DK40	.55	ECH42	.37	GZ32	.39	EL102	.53	PC8640	.14	UBF99	.28	2N2297	.18	BA103	.14	GET187	.43	OC84	.24
5Y3GT	.25	6E25	.51	10F9	.45	30FL2	.58	DK92	.35	ECH81	.25	GZ33	.70	EL103	.53	PC8640	.14	UBF99	.28	2N2297	.18	BA116	.25	GET187	.15	OC123	.23
5Z4G	.38	6F28	.60	10F18	.35	30FL12	.67	DK96	.35	ECH83	.38	GZ34	.47	EL104	.53	PC8640	.14	UC92	.35	2N3053	.33	BA129	.13	GET187	.22	OC139	.22
5Z4GT	.38	6F32	.15	10LD11	.53	30FL14	.66	DL96	.25	ECH84	.34	GZ37	.67	EL105	.53	PC8640	.14	UC88A	.33	2N3121	2.50	BA130	.10	GET187	.22	OC140	.25
6J30L2	.53	6GH8A	.50	10P13	.54	30L15	.55	DM70	.30	ECL80	.28	HABC80	.44	EL106	.53	PC8640	.14	UC85	.33	2N3709	.20	BA153	.10	GET189	.23	OC162	.25
6A8G	.38	6GK5	.50	10P14	1.08	30L17	.65	DM71	.38	ECL82	.28	HBL23D	.40	EL107	.53	PC8640	.14	UCF80	.31	2N3988	.50	BC107	.13	M1	.15	OC172	.35
6AC7	.15	6G07	.50	12A6	.63	30P4MR	.95	DY87/6	.25	ECL83	.62	HL41DD	.98	EL108	.53	PC8640	.14	UCF80	.31	2N3988	.50	BC108	.13	OA5	.28	OC280	.23
6AG5	.25	6H07	.40	12AC6	.15	30P12	.65	EY80	.29	ECL84	.54	HL42DD	.50	EL109	.53	PC8640	.14	UCF80	.31	2N3988	.50	BC109	.13	OA9	.13	OC291	.24
6AK7	.25	6J5G	.19	12AD6	.40	30P19/	.60	EB00C	1.65	ECL85	.54	HN309	1.40	EL110	.53	PC8640	.14	UCF80	.31	2N3988	.50	BC115	.15	OA10	.43	OC292	.43
6AK6	.30	6J5GT	.29	12AE6	.48	30P4	.55	EB00F	1.20	ECL86	.33	HVR2	.53	EL111	.53	PC8640	.14	UCF80	.31	2N3988	.50	BC116	.25	OA47	.10	OC293	.30
6AM8A	.50	6J6	.18	12AT6	.23	30PL1	.57	EB3F	1.20	EF22	.63	HVR2A	.53	EL112	.53	PC8640	.14	UCF80	.31	2N3988	.50	BC118	.25	OA70	.15	OC294	.30
6AN8	.49	6J7G	.24	12AT7	.16	30PL13	.75	EB80C	.60	EF40	.49	KT2	.26	EL113	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY10	.45	OA73	.15	OC295	.43
6AQ5	.21	6J7(M)	.38	12AU6	.21	30PL14	.62	E920C	.40	EF41	.58	KT41	.98	EL114	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY11	.45	OA73	.15	OC296	.43
6AR5	.30	6JUS4	.50	12AU7	.19	30PL15	.87	E180F	.90	EF42	.58	KT44	1.00	EL115	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY12	.60	OA73	.15	OC297	.43
6AT6	.18	6K7G	.10	12AX6	.28	35A3	.43	E182CC1	.00	EF73	.75	KT66	.80	EL116	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY13	.60	OA73	.15	OC298	.43
6AU6	.19	6K8G	.16	12AX7	.21	35L6GT	.42	E1148	.53	EF80	.21	KT81	2.00	EL117	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY14	.60	OA73	.15	OC299	.43
6AV6	.28	6L1	.98	12BE6	.30	35W4	.23	EAT6	.88	EF93	.54	KTW61	.63	EL118	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY15	.60	OA73	.15	OC300	.43
6AW8A	.54	6L6GT	.39	12BE6A	.30	35Z4GT	.24	EABCS0	.29	EF85	.25	KTW62	.63	EL119	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY16	.60	OA73	.15	OC301	.43
6AX4	.39	6L7	.38	12BH7	.27	35Z5GT	.30	EAC91	.38	EF86	.27	KTW62	.63	EL120	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY17	.60	OA73	.15	OC302	.43
6BG	.18	6L18	.44	12J7GT	.33	50CD6G	.50	EAF42	.45	EF89	.23	KTW62	.63	EL121	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY18	.60	OA73	.15	OC303	.43
6BA6	.19	6L19	1.38	12K5	.50	EY801	.50	EP91	.17	EF90	.23	KTW62	.63	EL122	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY19	.60	OA73	.15	OC304	.43
6BE8	.50	6LD20	.48	12K7GT	.34	50EH5	.55	EB34	.20	EF92	.28	KTW62	.63	EL123	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY20	.60	OA73	.15	OC305	.43
6BE6	.20	6N7GT	.40	128C7	.35	50L6GT	.45	EB91	.10	EF98	.65	KTW62	.63	EL124	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY21	.60	OA73	.15	OC306	.43
6BH6	.43	6G7GT	.43	128G7	.23	8A2	.43	EBCA1	.43	EF183	.25	KTW62	.63	EL125	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY22	.60	OA73	.15	OC307	.43
6BJ6	.39	6Q7M	.43	128H7	.15	8A3	.40	EBPC1	.29	EF184	.27	KTW62	.63	EL126	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY23	.60	OA73	.15	OC308	.43
6BQ7A	.38	6R7G	.35	128J7	.23	90C1	.59	EBF80	.30	EH90	.34	KTW62	.63	EL127	.53	PC8640	.14	UCF80	.31	2N3988	.50	BCY24	.60	OA73	.15	OC309	.43

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business - Cash or cheque with order only. Post/packing 3p. per item, subject to a minimum of 9p. per order. Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p. extra per order. Complete catalogue with conditions of sale price 7p. post. Business hours Mon.-Fri. 9-5.30 p.m. Sats. 9-1 p.m.
 * We do not handle second nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux instantly cleaning heavily oxidised surfaces. No extra flux is required.

IDEAL FOR HOME CONSTRUCTORS



Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges


EASY-TO-USE DISPENSERS



Size 5 (Savbit) 18swg, 18p (illustrated)
 Size 19A (60/40 alloy) 18swg, 18p
 Size 15 (60/40 alloy) 22swg, 22p

BIB WIRE STRIPPER AND CUTTER

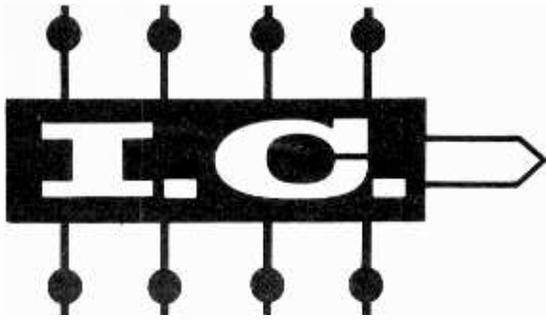Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4&6BAspanner ends, ground cutting edges Price 32p. Also available, de luxe Model 8. Price 58p



OF THE MONTH

L.A.J. IRELAND

Number 33

Motorola MFC6040 Electronic Attenuator

ACOUSTIC feedback—that deafening howl which occurs when a microphone picks up the sound from the loudspeakers of a public address system and thereby completes a feedback loop, setting the whole system into oscillation—will be familiar to readers. It is particularly embarrassing when, for example, an announcer is using a microphone with a considerable length of cable, and by moving to a new location initiates this response from a previously well-behaved system. It would therefore be convenient if, in addition to his microphone, the announcer could have to hand the gain control of the amplifier, so that it could be adjusted for best results from his own position, without having an assistant constantly at the amplifier controls.

However, it is not a practical proposition to remove the volume control of the amplifier to the end of a long cable for such remote operation. There would be a considerable increase in the noise level of the system, despite the best efforts to screen the cable; there is also the consideration that the audio signal may have been amplified prior to the volume control, and at the higher level, may itself produce some feedback effects due to the stray capacitance of the cable.

It may be suggested that a volume control could be incorporated in the microphone case, to control the signal level before it is applied to the amplifier; however, the microphone may not be the sole signal source. It is common practice to use several inputs to a public address system, with part of the pre-amplifier stages acting as an audio mixer, so it would be desirable for the remote unit to control the gain of the "mixed" signal, rather than just that of the microphone channel.

What is required, therefore, is a method of remote control of amplifier gain which does not involve long signal-carrying cables, is therefore impervious to noise and does not introduce feedback or degrade signal quality. It is just this requirement which is satisfied by the new Motorola Electronic Attenuator integrated circuit, type MFC6040.


Operation

In operation, the device is inserted in series with the master gain control of the mixer section of the preamplifier, and, depending on the setting of a remote potentiometer, attenuates the signal applied to its input terminal. Only a d.c. potential appears on the leads to the remote potentiometer; capacitive

effects are therefore irrelevant. The leads may be of any desired length and need not be screened. All the difficulties visualised above are therefore avoided.

Practicalities

It is possible to obtain microphone cable in which two conductors are incorporated within the braiding. One of these may then be used in the conventional fashion, applying the microphone signal between it and the screening. The other can then be used for the remote control potentiometer, with the screening as an earth return. There is no question of capacitive crosstalk as the control connection is decoupled at the i.c. by a $50\mu\text{F}$ capacitor.

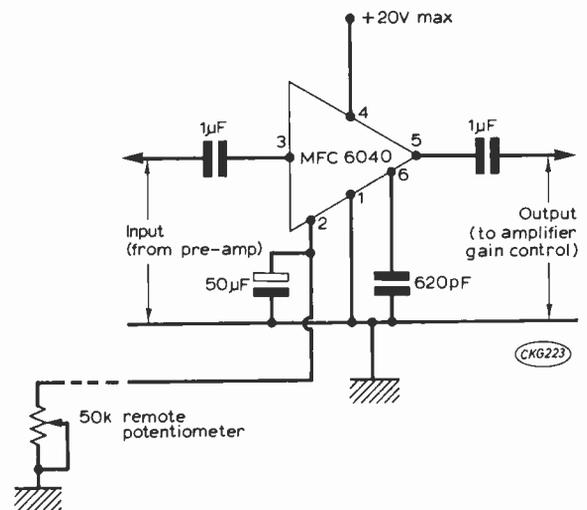

Wiring for an amplifier remote gain control system using the Motorola MFC6040 integrated circuit.

The circuit indicates the connections and components required for the provision of the remote control facility outlined. A beginner should find little difficulty in assembling it on a piece of veroboard, and it can easily be accommodated close to the master gain control inside even the most compact amplifier. A d.c. supply of 20V max. is required to

operate the i.c.; this is commonly available in modern transistor amplifiers and for mobile operation the 12V car battery supply is adequate. The i.c. itself is presented in a miniature 6-pin epoxy package with pin 1 indexed.

Alternatives

Alternative applications will be evident to the experimenter. The unit can clearly be employed as an audio automatic gain control by rectifying part of the output of the unit and applying it to pin 2 as a control voltage. Similarly, feedback systems can be designed which produce a control voltage dependent on signal frequency, for pre-emphasis or de-emphasis operations, or to investigate Dolby effects. A suitable low-frequency signal applied to pin 2 could be used for tremolo. It is clear, then, that the field for experiment with the MFC6040 is extremely wide, and we are likely to hear much more of it.

2 METRE Tx —continued from page 517

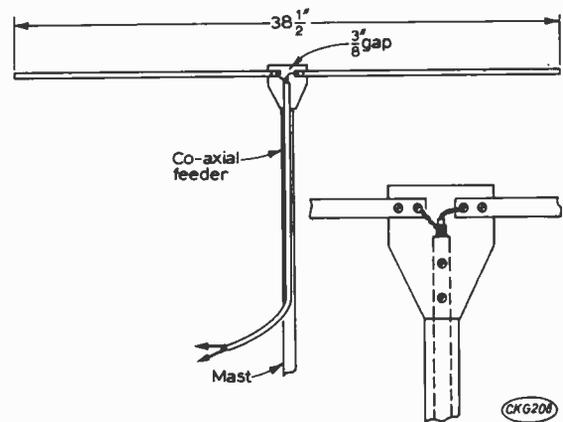


Fig. 2: Construction of a simple half wave dipole for 2 metres.

ranges. One can easily be made, using $\frac{1}{4}$ in. aluminium tubing, as shown in Fig. 2, the elements being bolted to a piece of insulating material. A more weather-proof aerial can be made on the same lines, but using a closed box as fitted to TV and similar aeriels. This aerial is easily raised on a light mast or post, with the co-axial feeder running down to the transmitter. ■

TELEVISION

OCTOBER ISSUE

COLOUR TV DELAY LINES

Why are delay lines necessary in a colour receiver, what do they do and how do they do it? We have not previously taken a close look at this aspect of colour television but we shall be doing so this month, in particular to see how the PAL delay line acts as a comb filter to separate the U and V components of the transmitted chrominance signal.

RECEIVER-MONITOR

A simple conversion of a domestic receiver to act as a monitor, not only to accept CCTV signals—from a camera or videotape recorder—but also to provide demodulated off-air signals to drive other monitors, for mixing in a CCTV studio or to feed to a videotape recorder.

WIDEBAND BAND 1 PREAMPLIFIER

The latest Roger Bunney preamplifier gives a gain of some 25dB over channels E2-4 (48-65MHz), using five BF180 transistors and providing two separate outputs. It is extremely stable over the bandwidth and may be used for DX work or for small relay systems, especially where Band 1 channels are used for distribution after frequency translation from the higher channels.

SERVICING TV RECEIVERS

The next chassis we are covering is that used in the Bush/Murphy TV141/TV148/V153/V159 series.

COLOUR RECEIVER PROJECT

Details this month of cabinet construction.

PLUS ALL THE REGULAR FEATURES

ON SALE SEPTEMBER 18

CQ! CQ! CQ! CQ! CQ!

ISSUES WANTED

- ...August 1971 Practical Wireless.—F. Maxwell, 21 Byron Close, Buyton, Liverpool, Lancs.
- ...Feb. and March 1972 Practical Wireless.—G. Lane, 18 Hertford Road, New Barnet, Herts.
- ...May 1969 Practical Wireless.—T. Ardley, 17 Elmwood Road, North Shields, Northumberland.
- ...Issues of Practical Wireless containing article on Pedal Steel Guitar.—B. R. Currow, 31 Acorn Grove, Ditton, Maldstone, Kent.
- ...November 1971 Practical Wireless.—B. Featherstone, 24 Glenville Road, Rustington, Sussex.
- ...Issues of Practical Wireless containing article on Expander/Compressor.—S. Butt 6 Childs Gate, Shotley Gate, Ipswich, Suffolk.
- ...Issues of Practical Wireless containing article on Pedal Steel Guitar.—B. S. Wylie, Daffs Tankerneas Lane, Kirkwall, Orkney.
- ...all issues of Practical Wireless that contain "Transistor Circuitry for Beginners". B. P. Bamfield, 256 Stephenson Avenue, Leamore, Walsall, Staffs.
- ...March 1965 Practical Wireless.—W. A. Dorloff, Block A3 Flat, 6 Bleomendhal Flats, Kotehena, Colombo 13, Ceylon.
- ...Issues of Practical Wireless containing articles on Beginners Guide to Transistor Circuitry.—K. McIlroy, 24 Deramore Drive, Portadown, Co. Armagh.
- ...Practical Wireless November 1970, T.V. June 1971.—J. F. Glavin, North Lodge, Northlands, Salthill, Chichester, Sussex.
- ...Issues of Practical Wireless containing details of 19 set circuits.—C. A. Campbell 7 Fairfax Crescent, Barley, Bradford, 4, Yorks.
- ...Issues containing details on Electric Steel Guitar.—R. J. Saunders, Carpenter & Joiners, 20 Berkeley Avenue, Chesham, Bucks.
- ...Practical Wireless October 1971 and November 1971.—L. Herman, 58 Herongate Road, Wanstead, E.12.
- ...Practical Wireless June 1966 and December 1971.—D. Whalley, 17 Mornington Rise, Matlock, Derbyshire.
- ...back issues of P.W. and P.E. required containing articles on electronic organs.—H. D. Briggs, 53 Gilkin Road, Admaston, Telford, Salop.
- ...wanted back number of P.W. Feb. 1971 second part to P.W. Stereo Tape Recorder.—D. C. Bathurst, 7 Keates Est., Kyerdale Road, Stoke Newington, N16 7AD.
- ...back issues of P.W. in good clean condition (in binders if possible) especially 1970, 1969 and 1968 complete volume.—B. G. J. Simeon, P.O. Box 213, Mahe, Seychelles, Indian Ocean.
- ...P.W., Oct. 1971—Feb. 1972 (inclusive).—J. S. Gaythorpe, 36 Granville Terrace, Gisleigh, Nr. Leeds, Yorks. LS20 9DY.
- ...P.W. November 1971—Vol. 47, Nos. one, two, three, four, five, six—E. Blackman, 80 Myatt Avenue, Parkfields, Wolverhampton, WV2 2DN, Staffs.
- ...P.W. May 1971, and June 1971.—H. Hunt, 13 Chiltern Drive, Walshaw, Bury, Lancs.
- ...Issues of P.W. with article on F.E.T. Transistor Voltmeter.—F. M. Milburn Esq., Pitts Farm House, Vantly Lane, Linton, Kent.
- ...Issues of P.W. containing articles on decoders.—D. E. Rosa Esq., Lord Mayor Hospital, Allian, Herts.
- ...P.W. October 1967, December 1970, April 1971, August 1971.—R. J. S. Gowe Esq., Celtic Fields, Celtic Way, Bleadon Hill, Weston-Super-Mare, Som., BS24 0NA.
- ...Issues of P.W. containing details of the "Sixteen" multimeter.—H. E. Lupton Senior Lecturer in Educational Psychology, Saint Martin's College, Lancaster.
- ...January 1968 with details of P.W. clubman Mark I. Will buy or hire and will pay for postage.—M. Ferrall, 17 Priory Road, Cottingham, Yorkshire.
- ...Dec. 1971 P.W.—P. A. Townaend, 24 Ronald Drive, Rayleigh, Essex.
- ...P.W. DCC. 67.—Carl's Radio and T.V. Engineers, 11 Scott Vale, Sheepridge, Huddersfield.
- ...P.W., August 1971.—C. J. Rayner, 6 Westley Road, Fornhal All Saints, Bury St. Edmunds, Suffolk.
- ...Issues of Practical Wireless containing the Explorer VHF Receiver or Just loan the above issue C1967.—A. J. Bartlett, 4 Keisall Close, Kidbrook, London, SE30 0JJ.
- ...P.W. for Jan. and Feb. 1971.—M. F. Bowen, 44 Elder Crescent, R.A.F. Wattisham Ipswich, Suffolk.
- ...August and September 1969 Issues of Practical Television.—N. F. Beardmore, 9 Aider Road, Precoat, Lancs. L34 2SG.
- ...Digital Frequency Counter/Timer.—E. De Smedt, Bureau D'Etudes, 9 Avenue de Levie Mirepoix, 1060 Bruxelles.

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS
SOLE AGENTS FOR SOLID STATES DEVICES INC., (U.S.A.), IN U.K.


RETURN OF POST SERVICE

TRANSISTORS

2G301	0-15	2N2924	0-12	2N5174	0-22	AF116	0-25	BC307	0-09	BF271	0-21
2G302	0-15	2N2925	0-12	2N5175	0-22	AF117	0-25	BC307A	0-09	BF272	0-21
2G303	0-25	2N2926	0-12	2N5176	0-22	AF121	0-22	BC307VI	0-09	BF273	0-21
2G306	0-30	Green	0-10	2N5245	0-43	AF125	0-20	BC308	0-08	BF274	0-21
2G309	0-30	Yellow	0-10	2N5190	0-22	AF126	0-20	BC308B	0-08	BF457	0-46
2G344A	0-25	Orange	0-10	2N5191	0-22	AF127	0-20	BC309	0-09	BF458	0-47
2G345B	0-25	2N3062	0-12	2N5192	0-22	AF130	0-25	BC309A	0-09	BF459	0-47
2G371	0-15	2N3054	0-47	2N5193	1-01	AF170	0-25	BC309B	0-09	BF521	0-20
2G374	0-15	2N3054	0-47	2N5194	1-10	AF172	0-25	BC310	0-25	BF522	0-20
2G381	0-25	2N3055	0-60	2N5195	1-46	AF178	0-55	BC313	0-30	BF529	0-22
2G417	0-20	2N3390	0-20	2N5245	0-43	AF179	0-55	BC327	0-21	BF588	0-27
2N109	0-49	2N3391	0-20	2N5407	0-35	AF180	0-50	BC328	0-19	BF589	0-30
2N174	1-40	2N3439	0-22	2N5458	0-33	AF186	0-40	BC337	0-17	PFW10	0-61
2N176	0-75	2N3392	0-18	2N5459	0-33	AF200	0-35	BC338	0-17	PFW11	0-61
2N274	0-75	2N3393	0-12	3N128	0-63	AF239	0-38	BCY32	0-50	BFX20	0-25
2N335	0-75	2N3394	0-12	3N138	1-37	AF240	0-38	BCY32	0-50	BFX30	0-25
2N561	0-95	2N3402	0-17	3N199	1-36	AF279	0-47	BCY33	0-50	BFX37	0-33
2N376	1-00	2N3403	0-19	3N140	0-76	AF280	0-47	BCY34	0-50	BFX44	0-33
2N384	0-93	2N3404	0-24	3N141	0-89	AFY42	0-65	BCY38	0-40	BFX63	0-48
2N388A	0-40	2N3405	0-27	3N142	0-84	AFY41	0-65	BCY39	0-40	BFX68	0-30
2N404	0-25	2N3414	0-10	3N143	0-84	AL102	0-60	BCY40	0-50	BFX84	0-24
2N404	0-25	2N3415	0-10	3N152	0-79	AL103	0-70	BCY42	0-15	BFX85	0-29
2N456	0-75	2N3416	0-15	3N153	0-74	AY226	0-25	BCY43	0-15	BFX86	0-24
2N456A	0-75	2N3417	0-21	3N154	0-74	AY227	0-20	BCY48	0-18	BFX87	0-27
2N457A	0-80	2N3570	1-25	3N159	1-00	AY228	0-25	BCY69	0-19	BFX88	0-25
2N491	3-25	2N3671	1-12	3N187	1-30	AY229	0-30	BCY66	0-58	BFX89	0-35
2N584	0-25	2N3572	0-27	3N201	2-07	AY230	0-27	BCY72	0-52	BFY10	0-45
2N591	0-25	2N3573	0-11	3N201	1-05	AY235	0-60	BCY70	0-60	BFY11	0-45
2N696	0-15	2N3703	0-10			ASZ21	0-55	BCY71	0-22	BFY17	0-90
2N697	0-15	2N3704	0-11	40050	0-50	AU103	1-25	BCY72	0-12	BFY18	0-35
2N698	0-25	2N3705	0-10	40251	0-58	BC107	0-12	BCY87	0-47	BFY19	0-35
2N699	0-29	2N3706	0-90	40309	0-28	BC108	0-11	BCY88	2-40	BFY20	0-50
2N706	0-10	2N3707	0-11	40310	0-37	BC109	0-12	BCY89	0-80	BFY29	0-40
2N706A	0-12	2N3708	0-12	40313	1-05	BC114	0-12	BCY90	0-36	BFY37	0-29
2N708	0-25	2N3709	0-90	40313	1-05	BC114	0-12	BCZ11	0-60	BFY41	0-43
2N709	0-88	2N3710	0-90	40316	0-44	BC115	0-15	BD115	0-75	BFY43	0-65
2N711	0-30	2N3711	0-90	40318	0-97	BC116	0-15	BD116	0-75	BFY50	0-16
2N718	0-21	2N3712	0-08	40322	1-00	BC116A	0-18	BD121	0-75	BFY51	0-16
2N720	0-80	2N3713	1-05	40361	0-87	BC117	0-21	BD123	0-82	BFY52	0-16
2N720	0-80	2N3714	1-15	40362	0-40	BC118	0-11	BD124	0-80	BFY53	0-15
2N721	0-55	2N3715	1-25	40363	0-27	BC119	0-20	BD129	0-87	BFY56	0-65
2N914	0-15	2N3720	0-30	40363	0-61	BC121	0-20	BD131	0-75	BFY64	0-41
2N916	0-17	2N3723	0-40	40389	0-37	BC123	0-25	BD132	0-75	BFY75	0-28
2N918	0-30	2N3724	3-33	40394	0-58	BC125	0-15	BD135	0-88	BFY76	0-24
2N919	0-20	2N3725	4-19	40406	0-50	BC126	0-20	BD136	0-44	BFY77	0-24
2N929	0-14	2N3726	5-95	40407	0-81	BC132	0-30	BD137	0-47	BFY78	0-36
2N930	0-14	2N3727	4-84	40408	0-41	BC134	0-11	BD138	0-55	BFY90	0-55
2N1090	0-30	2N3728	2-25	40409	0-49	BC135	0-15	BD139	0-82	BFY99	0-35
2N1091	0-32	2N3729	1-15	40409	0-49	BC136	0-15	BD140	0-73	BFX19	0-13
2N1131	0-20	2N3780	4-50	40410	0-33	BC137	0-15	BDY10	1-25	BFX20	0-14
2N1132	0-20	2N3781	3-67	40411	1-40	BC138	0-24	BDY11	1-50	BFX21	0-20
2N1184	1-27	2N3782	3-37	40438	1-44	BC140	0-30	BDY17	1-50	BFX26	0-34
2N1302	0-18	2N3789	1-76	40467A	0-57	BC141	0-34	BDY18	1-75	BFX27	0-34
2N1303	0-18	2N3790	1-90	40468A	0-35	BC142	0-18	BDY19	1-97	BFX28	0-25
2N1304	0-20	2N3791	2-00	40468A	0-87	BC144	0-24	BDY28	1-35	BFX29	0-27
2N1305	0-20	2N3792	2-20	40600	0-80	BC144	0-24	BDY38	0-65	BFX30	0-25
2N1306	0-22	2N3794	0-10	40601	0-65	BC145	0-21	BDY60	0-90	BFX59	0-78
2N1307	0-22	2N3819	0-26	40602	0-40	BC147	0-10	BDY61	0-85	BFX60	0-54
2N1308	0-25	2N3820	0-48	40604	0-45	BC148	0-09	BDY62	0-75	BFX61	0-42
2N1309	0-25	2N3823	0-62	40636	0-33	BC149	0-11	BF115	0-25	BFX76	0-15
2N1485	0-80	2N3824	0-75	40673	0-60	BC154	0-09	BF119	0-48	BFX77	0-20
2N1487	0-20	2N3825	0-20	40673	0-35	BC157	0-11	BF121	0-25	BFX78	0-28
2N1613	0-20	2N3854	0-16	AC1107	0-18	BC158	0-10	BF123	0-27	BFY24	0-20
2N1613	0-38	2N3854A	0-16	AC1113	0-18	BC159	0-10	BF125	0-25	BFY26	0-20
2N1637	0-38	2N3855	0-16	AC1117	0-20	BC160	0-11	BF127	0-27	BFY26	0-20
2N1638	0-38	2N3856	0-16	AC1121	0-11	BC161	0-10	BF129	0-20	BFY27	0-15
2N1671	1-00	2N3856	0-16	AC1126	0-20	BC168B	0-10	BF153	0-29	BFY28	0-15
2N1701	1-10	2N3856A	0-16	AC1127	0-20	BC168C	0-10	BF154	0-16	BFY38	0-15
2N1702	2-15	2N3858	0-16	AC1128	0-20	BC169B	0-11	BF158	0-23	BFY39	0-15
2N1711	0-17	2N3858A	0-16	AC1128	0-20	BC169B	0-11	BF159	0-27	BFY51	0-25
2N1893	0-34	2N3859	0-16	AC142K	0-25	BC189C	0-11	BF160	0-23	BFY62	0-25
2N2102	0-30	2N3859A	0-16	AC151V	0-12	BC170	0-11	BF160	0-23	BFY62	0-25
2N2147	0-70	2N3860	0-75	AC152V	0-15	BC172	0-11	BF163	0-20	BFY63	0-25
2N2148	0-70	2N3860A	0-75	AC153	0-19	BC182	0-10	BF166	0-85	BFY66	0-79
2N2192	0-40	2N3877	0-25	AC153K	0-22	BC182L	0-10	BF167	0-18	BFY65	0-15
2N2192A	0-40	2N3877A	0-25	AC178	0-18	BC183	0-09	BF173	0-19	BFY78	0-40
2N2193	0-58	2N3878	1-22	AC178	0-18	BC183L	0-09	BF177	0-25	BFY79	0-40
2N2193A	0-61	2N3879	1-01	AC178K	0-17	BC184	0-17	BF178	0-31	BFY80	0-45
2N2194	0-27	2N3900	0-20	AC178K	0-17	BC184L	0-17	BF178	0-31	BFY80	0-45
2N2194A	0-27	2N3900A	0-21	AC181K	0-23	BC186	0-25	BF180	0-35	BU104	1-42
2N2195	0-37	2N3901	0-32	AC181K	0-23	BC186	0-25	BF181	0-34	BU105	2-25
2N2195A	0-37	2N3901A	0-32	ACY17	0-15	BC204	0-11	BF182	0-40	C111	0-58
2N2218A	0-18	2N3904	0-22	ACY18	0-15	BC205	0-10	BF183	0-40	C407	0-13
2N2219	0-20	2N3905	0-21	ACY20	0-20	BC206	0-11	BF184	0-17	C424	0-15
2N2219A	0-20	2N3906	0-22	ACY21	0-18	BC207	0-10	BF185	0-17	C425	0-39
2N2220	0-30	2N4036	0-40	ACY22	0-13	BC208	0-09	BF194	0-14	C426	0-25
2N2221	0-20	2N4037	0-40	ACY28	0-18	BC209	0-10	BF195	0-15	C428	0-25
2N2221A	0-22	2N4058	0-12	ACY29	0-42	BC211	0-30	BF196	0-15	C444	0-28
2N2222	0-20	2N3059	0-90	ACY38	0-55	BC212	0-10	BF197	0-16	D40N3	0-62
2N2222A	0-38	2N4060	0-11	ACY40	0-17	BC212L	0-12	BF198	0-18	ET111	0-46
2N2368	0-11	2N4061	0-11	ACY41	0-17	BC214	0-13	BF199	0-18	ET113	0-25
2N2369	0-12	2N4077	0-17	ACY44	0-31	BC236	0-18	BF200	0-40	ET114	0-20
2N2369A	0-17	2N4302	0-22	AD136V	0-84	BC237	0-08	BF224J	0-14	ET115	0-20
2N2646	0-45	2N4303	0-25	AD140	0-60	BC238	0-08	BF225J	0-19	ET119	0-35
2N2647	1-20	2N4913	0-80	AD142	0-50	BC239	0-08	BF227	0-22	ET120	0-40
2N2711	0-12	2N4914	0-87	AD143	0-45	BC239	0-08	BF238	0-22	ET135	0-20
2N2712	0-12	2N4915	0-95	AD149V	0-58	BC253	0-23	BF245	0-33	ET136	0-20
2N2713	0-17	2N4916	0-11	AD149V	1-23	BC257	0-08	BF246	0-43	ET138	0-20
2N2714	0-12	2N4917	0-77	AD150	0-55	BC258	0-08	BF247	0-49	ET173	0-15
2N2904	0-18	2N4918	0-58	AD150	0-55	BC258	0-08	BF247	0-49	ET173	0-15
2N2904A	0-29	2N4919	0-53	AD161	0-33	BC259	0-11				

Sinclair Project 60

Project 60 Stereo FM Tuner

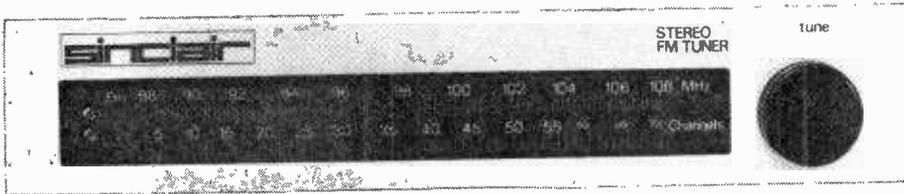

Built and tested.
Post free.
£25


with phase lock-loop principle

Amongst the many advanced electronic features to be found in this remarkable stereo tuner, use of the phase lock loop principle ensures standards of audio quality better than from any other method of detection yet used. Varicap diode tuning, accurately formed printed circuit coils, an I.C. in the special stereo decoder section and switchable squelch circuit for silent tuning between stations contribute to the unsurpassed performance of this tuner, irrespective of price consideration. But the Project 60 FM Stereo Tuner is far from expensive – indeed, it offers fantastic value for money and will bring the thrill of stereo radio to many who previously may not have been able to afford it. The tuner may be used with any good system as well as Project 60, but if you use it with other Project 60 modules, you will find the matching front panels particularly impressive in appearance as well as function.

SPECIFICATIONS

Number of transistors: 16 plus 20 in I.C.
Tuning range: 87.5 to 108MHz.
Sensitivity: 7µV for lock-in over full deviation.
Squelch level: typically 20µV
Signal to noise ratio: ± 65dB.
Audio frequency response: 10Hz–15KHz (± 1dB).
Total harmonic distortion: 0.15% for 30% modulation.
Stereo decoder operating level: 2µV.
Cross talk: 40dB.
Output voltage: 2 · 150mV R.M.S max. (typically 2 · 50mV, stereo)
Operating voltage: 25–30V DC at 100mA.
Indicators: Stereo on; tuning
Size: 93 × 40 · 207mm.

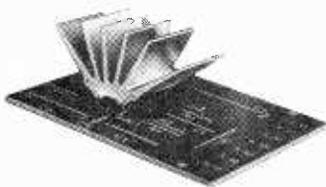Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak), 6–8Ω. **Frequency Response:** 5Hz to 100KHz ± 1dB **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V) **Load Impedance:** 3 to 15 ohms **Input Impedance:** 250 Kohms nominal **Power Gain:** 90dB (1,000,000,000 times) after feedback **Supply Voltage:** 6 to 28V **Quiescent current:** 8mA at 28V. **Size:** 22 · 45 · 28mm including pins and heat sink.

Manual available separately 15p post free

With FREE printed circuit board and 40 page manual

£2.98 Post free

Project 605



The easy way to buy and build Project 60

Project 605 is one pack containing one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting

Complete Project 605 pack with comprehensive manual, post free **£29.95**

Everything you need to assemble a superb 30 watt high fidelity stereo amplifier without having to solder.

sinclair

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311


the world's most advanced high fidelity modules

Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual **Z.30 £4.48** **Z.50 £5.48**

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to provide unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and are intended for use principally with other units in the Project 60 range. Their performance and design are such, however, that Z.50s and Z.30 may be used in a far wider range of applications.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).— Power Outputs:
Z.30 15 watts R.M.S. into 8 ohms using 35 volts 20 watts R.M.S. into 3 ohms using 30 volts
Z.50 40 watts R.M.S. into 3 ohms using 40 volts 30 watts R.M.S. into 8 ohms using 50 volts
Frequency response: 30 to 300,000Hz - 1dB **Distortion:** 0.02% into 8 ohms. **Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω) For speakers from 3 to 15 ohms impedance. **Size:** 14 x 80 x 57mm.

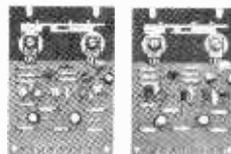

Stereo 60 Pre-amp/control unit

Built, tested and guaranteed **£9.98**

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio - up to 3mV Mag. p.u. 3mV correct to R.I.A.A. curve ± 1 dB - 20 to 25,000 Hz. Ceramic p.u. - up to 3mV. Aux - up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE - 12 to -12dB at 10KHz. BASS - 12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.



A.F.U. High & Low Pass Filter Unit

Built, tested and guaranteed **£5.98**

For use between Stereo 60 unit and two Z.30s or Z.50s. The unit is very easily mounted and is unique in that the cut-off frequencies are continuously variable. As attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. There are two filter sections - rumble (high pass) and scratch (low pass). H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. Operating voltage from 15 to 35V. Current 3mA. **Size:** 66 x 40 x 90mm.



Power Supply Units

Designed specifically for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 or PZ.8 where a stabilised supply is essential.

PZ.5 30 volts un stabilised **£4.98**
PZ.6 35 volts stabilised **£7.98**
PZ.8 45 volts stabilised
 (less mains transformer) **£7.98**
PZ.8 mains transformer **£5.98**



Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (**£25**) & A.F.U. (**£5.98**) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

SINCLAIR RADIONICS, ST IVES, HUNTINGDONSHIRE PE17 4HJ

Please send _____

I enclose cash/cheque/money order

Name _____

Address _____

PE 1072

sinclair


SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts

r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-16 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. PRICE \pounds 10.50. P. & P. 25p.

De Luxe Stereo Amplifier

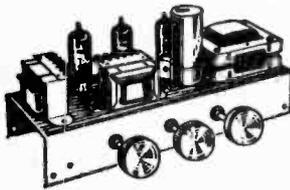

A.C. mains 200-240 v. Using heavy duty fully isolated main transformer with full wave rectification giving a steady smoothing with negligible hum.

Valve line up:—2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of a separate Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE \pounds 28.92 P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp continuous (1 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested.

PRICE \pounds 4.50 P & P 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4 in. FIVE for 50p. P. & P. 13p.

COILED SPRING BACK TELEPHONE CABLE. Closed approx. 10" extends to 36". 4 core or 6 core. 25p each P. & P. 5p. 5 or more post free. LIMITED NUMBER!

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS Giving 13 alternatives. Primary: 9-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price \pounds 1.75 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240v. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 88p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 1.38. P. & P. 30p.

SPECIAL MAINS TRANSFORMER 200/240v. A.C. Input 35v at 1 1/2 amp A.C. output overall size 2 1/2" x 2 1/2" x 3" approx. Suitable drop through or vertical mounting 75p. P. & P. 30p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.
With latest mono compatible cartridge \pounds 6.97 Carr. 50p.
With stereo cartridge \pounds 7.97 Carr. 50p.
LATEST GARBARO MODELS. S.A.E. for latest Prices!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL68B, AT60 etc. or B.S.R. C109, C129, A21 etc. Choice of Black leatherette or Teak grain finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover).
PRICE \pounds 5.50. P. & P. 60p.

LATEST ACOS GP91/18C mono compatible cartridge with 1/0 stylus for LP/EP/78. Universal mounting bracket. \pounds 1.50 P. & P. 8p.

SONOTONE STEREO COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY \pounds 2.50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. \pounds 3. P. & P. 10p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. \pounds 1.63 P. & P. 10p.
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only \pounds 1.50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE \pounds 3.75 P. & P. 40p.
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE \pounds 4.88 P. & P. 50p.

DELUXE QUALITY PORTABLE R/P CABINET MK II.
Uncut motor board size 14 1/2 x 12in. clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARBARO changer or Single Player (except AT60 and SP25). Size 18 x 15 x 5in. PRICE \pounds 4.76. P. & P. 50p.

SPECIAL OFFER ! HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE \pounds 8.40 Carr. 65p

Cabinet Available Separately \pounds 4.50 Carr 60p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter \pounds 8.50 Carr. 65p

LOUDSPEAKER BARGAINS

5in. 3 ohm \pounds 1.05. P. & P. 15p. 7 x 4in. 3 ohm \pounds 1.15. P. & P. 20p. 10 x 6in. 3 or 15 ohm \pounds 1.90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet \pounds 1.62. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet 3, 8 or 15 ohm \pounds 3.20. P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network \pounds 4.20. P. & P. 30p. E.M.I. 13 x 8in. twin cone (parasitic tweeter) 8 ohm \pounds 2.25. P. & P. 30p.

BRAND NEW, 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production from renowned British maker. Now fitted with Hifux ceramic ferrobar magnet assembly \pounds 2.85. Guitar models: 25w. \pounds 6.50, 35w. \pounds 5.50. P. & P. 35p. E.M.I. 3 1/2in. **HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 98p each. P. & P. 13p.

12in. "RA" TWIN CONE LOUSPEAKER, 10 watts peak handling, 8 or 15 ohm \pounds 2.20. P. & P. 30p. 35 ohm SPEAKERS 5in. only 80p. P. & P. 13p.

"POLY PLANAR" WAFFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11 1/2 x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only \pounds 5.75 each. P. & P. 25p.

VYNAIR & BEKINS SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually \pounds 1.75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexiform ear-cups. Wired and fitted with standard stereo 3 1/2 jack plugs. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE \pounds 2.95. P. & P. 15p.


HIGH IMPEDANCE CRYSTAL STICK MIKES.
OUR PRICE \pounds 1.05. P. & P. 8p

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-15v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 88p. P. & P. 13p.

CENTRE ZERO MINATURE MOVING COIL METER. 100uA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

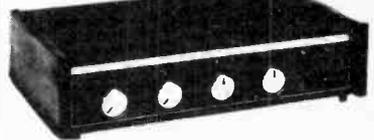HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knob, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Overall gain approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35w. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT \pounds 10.50 P. & P. 15p
(Magnetic input components 80p extra)
POWER PACK KIT \pounds 3.00 P. & P. 30p
CABINET \pounds 2.00 P. & P. 30p

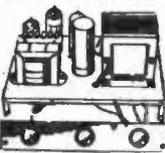(Post Free if all units purchased at same time)
Full after sales service
Also available ready built and tested \pounds 21.00. Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, turn record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records, A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only \pounds 4.75. P. & P. 30p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. \pounds 3.98. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL83 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.

BARGAIN PRICE \pounds 7.75 P. & P. 35p

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to be made each other. Fully brushed section wound output transformer to match 3-16 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY \pounds 7.97 P. & P. 55p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

AERIALS - AERIALS - AERIALS

The most talked about subject on the bands, in the Club, at the Rally . . . the most neglected and yet the most vital part of any SWL and Amateur Station.

EARTHS! Less talked about and even more neglected than Aerials—BOTH ARE VITAL FOR FIRST CLASS RESULTS!!!

PARTRIDGE solved the AERIAL PROBLEM, regardless of site restrictions over 10 years ago. And now, with the World's first Commercially made ARTIFICIAL EARTH, the OTHER END of your problem is now taken care of.

When you buy PARTRIDGE products, you are buying 50 years of professional experience, from SPARK, fixed and rotary, POULSEN ARC, T.P.T.G. and seagoing "SAUSAGE" aerials, to the WORLD'S MOST VERSATILE & COMPACT 6 band AERIAL SYSTEM, the JOYSTICK Variable Frequency Antenna, protected by Patents and Trade Marks the World over.

For the vital "bits" in between the all important AERIAL and EARTH, PARTRIDGE supply an exciting range of CASH SAVING PACKAGE DEALS involving Transceivers, Receivers, Transmitters, matching speakers and headphones, SWR meters, and the famous PARTRIDGE SPACE AGE EXPORT RANGE and low cost BUDGET LINE of AERIAL and EARTH equipment.

START THE SEASON with a PARTRIDGE PACKAGE, send 3p stamp for illustrated details NOW (before the advancing YEN and V.A.T. put a premium on your pleasure).

BOX 5

PARTRIDGE ELECTRONICS LTD.

G3CED

BROADSTAIRS, KENT

G3VFA

Phone: (Thanet) 0843 62535, or 62839 during cheap periods for advice or C.O.D. orders.

REMEMBER—WASTED POWER MEANS T.V.I. and INDIFFERENT REPORTS AND POOR RECEPTION



**become
a RADIO-AMATEUR!**

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

**BRITISH NATIONAL RADIO &
ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WB102
BLOCK CAPS please

E.M.I. 13 x 8in HI-FI SPEAKERS-LATEST MODEL

Two 2½" Tweeters + crossover unit. 8 Ohms 10 Watts. R.M.S. up to 16 K/cs. £3.35 p & p 40p.

Suitable teak enclosure £5.00 + 40p p & p.

E.M.I. 13 x 8in BASS SPEAKERS. 8 Ohms 12 Watts R.M.S. 20 Watt peak. Complete with crossover unit. £5.00 p & p 45p.

Suitable teak enclosure with tweeter hole £5.50 + 40p p & p.

BUSH PROFESSIONAL STEREO PHONES. £10.50 + 25p p & p.

BUSH A220 Amp 10 Watts per channel £30.00 + 75p p & p.

AMSTRAD 8000 Mk II £16.00 + 75p p & p.

AMSTRAD IC2000 £25.00 + 75p p & p.

TELETRON SAQ 307 £22.50 + 75p p & p.

TELETRON TUNER AMP F2100 £35.00 + 75p p & p.

100 WATT ALL-PURPOSE AMPLIFIER

★ 100 watts continuous sine wave output into 8 ohms.

★ 4 high impedance inputs, allowing mixing facilities for all types of equipment to match any signal.

Input 1 250mV } Suitable for crystal or ceramic cartridge radio
Input 2 100mV } tuner, etc. Input impedance 500K.

Input 3 5mV } Suitable for all mics and guitars. Input impedance
Input 4 5mV } 100K.

★ Separate volume controls on each input.

★ Master volume, treble and bass controls.

★ 40db variation on treble control at 12KHz.

★ 40db variation on bass control at 60Hz.

★ Frequency response 20Hz-25KHz ± 2db.

★ Short and open circuit protection on output stage.

★ Standard 240V-120V mains operation. £54.20 carriage free.

LINVALE RADIO LTD
48 HOE STREET
LONDON E.17 01-520 7546

HENRY'S - Your complete Semi-Conductor Store!

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T FAIRCHILD



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
SN7400	0.20	0.18	0.16	SN7450	0.20	0.18	0.16	SN74145	1.50	1.40	1.30
SN7401	0.20	0.18	0.16	SN7461	0.20	0.18	0.16	SN74150	3.85	2.95	2.15
SN7402	0.20	0.18	0.16	SN7453	0.20	0.18	0.16	SN74151	1.10	0.95	0.90
SN7403	0.20	0.18	0.16	SN7454	0.20	0.18	0.16	SN74153	1.85	1.27	1.20
SN7404	0.20	0.18	0.16	SN7460	0.20	0.18	0.16	SN74164	2.00	1.75	1.55
SN7405	0.20	0.18	0.16	SN7470	0.20	0.27	0.25	SN74165	1.55	1.47	1.35
SN7406	0.30	0.27	0.25	SN7472	0.30	0.27	0.25	SN74166	1.55	1.47	1.35
SN7407	0.30	0.27	0.25	SN7473	0.40	0.37	0.35	SN74187	1.80	1.70	1.60
SN7408	0.20	0.19	0.18	SN7474	0.40	0.37	0.35	SN74180	2.60	2.40	2.25
SN7409	0.45	0.42	0.35	SN7475	0.55	0.52	0.50	SN74181	2.60	2.40	2.25
SN7410	0.20	0.18	0.16	SN7476	0.45	0.42	0.39	SN74182	3.40	3.25	2.70
SN7411	0.25	0.22	0.20	SN7480	0.80	0.75	0.67	SN74183	3.40	3.25	2.70
SN7412	0.42	0.40	0.35	SN7479	1.25	1.15	1.10	SN74184	2.75	2.30	2.10
SN7413	0.30	0.27	0.25	SN7482	0.87	0.80	0.79	SN74176	1.60	1.35	1.20
SN7416	0.30	0.27	0.25	SN7483	1.00	0.90	0.85	SN74177	4.00	3.50	3.00
SN7417	0.30	0.27	0.25	SN7484	1.00	0.85	0.80	SN74186	4.00	3.50	3.00
SN7420	0.20	0.18	0.16	SN7486	0.45	0.41	0.38	SN74187	6.25	5.80	5.10
SN7422	0.48	0.44	0.40	SN7490	0.75	0.70	0.65	SN74170	4.10	3.55	3.05
SN7423	0.48	0.44	0.40	SN7491	1.00	0.95	0.90	SN74174	2.00	1.75	1.30
SN7425	0.42	0.39	0.35	SN7492	0.75	0.70	0.65	SN74175	1.35	1.27	1.15
SN7428	0.50	0.45	0.42	SN7494	0.80	0.75	0.70	SN74176	1.60	1.35	1.20
SN7430	0.20	0.18	0.16	SN7495	0.80	0.75	0.70	SN74177	1.60	1.35	1.20
SN7432	0.42	0.39	0.35	SN7496	1.00	0.97	0.95	SN74180	1.55	1.35	1.20
SN7433	0.70	0.61	0.44	SN7497	8.25	5.00	5.00	SN74182	2.40	2.00	1.80
SN7437	0.85	0.60	0.50	SN7498	8.25	5.00	5.00	SN74183	2.40	2.00	1.80
SN7438	0.85	0.60	0.50	SN7499	8.25	5.00	5.00	SN74184	2.40	2.00	1.80
SN7440	0.20	0.18	0.16	SN74100	2.50	2.30	2.00	SN74185	2.40	2.00	1.80
SN7441	0.75	0.72	0.70	SN74101	1.45	1.35	1.20	SN74186	1.95	1.80	1.75
SN7442	0.75	0.72	0.70	SN74102	1.45	1.35	1.20	SN74187	1.95	1.80	1.75
SN7443	1.00	0.95	0.90	SN74103	1.45	1.35	1.20	SN74188	1.95	1.80	1.75
SN7445	2.00	1.75	1.60	SN74104	0.50	0.45	0.40	SN74189	2.00	1.90	1.80
SN7446	2.00	1.75	1.60	SN74105	0.50	0.45	0.40	SN74190	2.00	1.90	1.80
SN7447	1.75	1.60	1.45	SN74106	0.50	0.45	0.40	SN74191	2.00	1.90	1.80
SN7448	1.75	1.60	1.45	SN74107	0.50	0.45	0.40	SN74192	2.00	1.90	1.80
				SN74108	0.80	0.70	0.60	SN74193	2.00	1.90	1.80
				SN74109	0.80	0.70	0.60	SN74194	2.50	2.25	1.90
				SN74110	1.90	1.78	1.65	SN74195	1.85	1.70	1.60
				SN74111	0.60	0.55	0.50	SN74196	1.50	1.40	1.30
				SN74112	1.95	1.25	1.10	SN74197	1.50	1.40	1.30
				SN74113	0.75	0.72	0.67	SN74198	4.60	3.70	3.35
				SN74114	1.00	0.95	0.90	SN74199	4.60	3.70	3.35


PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER

LARGER QUANTITY PRICES PHONE (01) 402 4891
 TEXAS HANDBOOK NO. 2, I.C. 700 PAGES DATA 60p. POST 20p.
 HIGH POWER SN 74 LOO } Now in stock—send
 LOW POWER SM 74 LOO } for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA530 10p	BC147 12p	BV105 2.25	OC44 15p	T1843 35p	2N3055 55p
AA542 15p	BC182 10p	BV109 15p	OC45 15p	V405 25p	2N3440 75p
AZ123 10p	BC182 10p	BV126 15p	OC57 50p	ZTX108 12p	2N3442 15p
AC107 35p	BC214 15p	BV127 15p	OC71 15p	ZTX300 12p	2N3525 75p
AC126 25p	BCY32 75p	BVZ13 35p	OC72 25p	ZTX301 15p	2N3614 55p
AC127 25p	BCY34 35p	C106D 85p	OC77 45p	ZTX302 18p	2N3615 75p
AC128 25p	BCY39 1.00	GET111 55p	OC81 85p	ZTX341 20p	2N3702 10p
AC176 25p	BCY42 45p	GET115 55p	OC83 85p	ZTX300 18p	2N3704 10p
AC187 25p	BCY47 25p	GET380 45p	OC140 55p	ZTX303 17p	2N3705 10p
AC188 25p	BCY55 2.50	LM309K	OC170 25p	ZG301 30p	2N3714 1.80
AC177 30p	BCY70 15p	(T03) 1.87	OC201 30p	2N404 20p	2N3771 1.75
ACY20 20p	BCY71 20p	MAT121 25p	OC210 75p	2N627 35p	2N3773 2.00
ACY21 20p	BCY72 15p	MJE340 50p	OC201 75p	2N696 15p	2N3790 2.25
ACY39 35p	BCY87 2.80	MJE370 70p	OC202 80p	2N697 15p	2N3819 35p
AD140 50p	BD121 95p	MJE520 75p	OC203 50p	2N708 10p	2N3820 50p
AD149 50p	BD132 80p	MJE290 25p	OC271 1.25	2N830 20p	2N3866 85p
AD161 35p	BD131 75p	ORP1 1.10	ORP1 1.10	2N987 45p	2N3903 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF117 80p	BF115 25p		P346A 20p	2N1132 25p	2N4061 12p
AF118 50p	BF167 25p	MFP105 40p	RA8310AF	2N1302 18p	2N4062 12p
AF124 50p	BF173 25p	NKT14 20p		2N1304 22p	2N4126 15p
AF133 30p	BF179 30p	NKT216 40p	RA8508AF	2N1305 22p	2N4871 35p
AF198 40p	BF180 30p	NKT217 40p	TA2263 75p	2N1307 25p	2N4873 30p
AF239 40p	BF194 15p	NKT403 70p	TLL209 39p	2N1613 20p	2N4877 55p
ASB27 30p	BF195 15p	NKT404 50p	TIP29A 50p	2N1671 1.00	2N5012 1.00
ASB28 25p	BF861 25p	OA5 50p	TIP30A 60p	2N2147 75p	2N5018 8.25
BA102 30p	BF898 25p	OA10 30p	TIP31A 60p	2N2160 59p	2N5025 8.90
BA115 7p	BFX13 25p	OA81 15p	TIP32A 70p	2N2217 25p	2S801 50p
BA145 15p	BFX34 75p	OA91 7p	TIP33A 1.00	2N2221 20p	2S803 50p
BAX13 5p	BFX37 30p	OA200 7p		2N2222 1.00	2S824 85p
BAX16 7p	BFX88 20p	OA262 10p	TIP34A 1.50	2N2369A	40360 50p
BC107 10p	BFY50 20p	OC16 75p			40361 50p
BC108 10p	BFY51 20p	OC20 95p	TIP35A 2.50	2N2906 20p	40362 50p
BC109 10p	BFY52 20p	OC23 85p		2N2925 (all	40408 50p
BC108C 12p	BFY64 50p	OC28 85p	TIP36A 3.00	encls) 10p	40488 75p
BC113 15p	BFY90 50p	OC28 85p	TIP41A 7p	2N3053 20p	40636 1.10
BC117 20p	RLY36 8.00	OC35 50p	TIP42A 85p	2N3054 50p	40430 1.00
BC121 10p	BSX20 15p	OC36 65p			
BC143 35p	BSY27 15p	OC42 40p			

INTEGRATED CIRCUIT SOCKETS

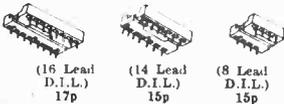

QUANTITY DISCOUNTS

10% 12+ ; 15% 25+ ; ANY ONE TYPE
 20% 100+ ; 25% 250+
 From above sections except Integrated Circuits and Special Offers where discounts are included.
 Minimum order value £1 please.
 Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC/S		All Colours	
25 + 20p		25 + 9p	
100 + 17p		100 + 8p	
500 + 15p		500 + 6p	
		1000 + 5p	
AF117 Mullard	25p	2N3819 Texas	35p
25 + 17p		25 + 10p	
100 + 15p		100 + 25p	
500 + 12p		500 + 20p	
		1000 + 15p	
OC170 Mullard	25p	BC107, BC108, BC109	10p each
25 + 20p		All Makes	
100 + 18p		25 + 8p	
500 + 15p		100 + 7p	
1000 + 13p		500 + 6p	
		1000 + 5p	
BY127 Mullard	15p	AD161, AD162	35p each
25 + 12p		25 + 32p	
100 + 10p		100 + 28p	
500 + 9p		500 + 25p	
1000 + 8p		1000 + 22p	
OA202	10p	2N3053	20p
25 + 8p		25 + 18p	
100 + 7p		100 + 15p	
500 + 6p		500 + 12p	
1000 + 5p		1000 + 10p	
OC35 Mullard	50p	2N3055	55p
25 + 45p		25 + 50p	
100 + 40p		100 + 45p	
500 + 35p		500 + 38p	
1000 + 30p		1000 + 30p	

PLESSEY INTEGRATED CIRCUIT
 3 Watt Amplifier SL403D
 Complete with 8-page
 booklet, circuits
 and data.

£1.50 each



TRIACS

STUD WITH ACCESSORIES

Type	Volts	Price
3 AMP RANGE		
SC35A	100	75p
SC35B	200	75p
SC35D	400	85p
6 AMP RANGE (TO48)		
SC40A	100	85p
SC40B	200	90p
SC40D	400	£1.00
SC40E	500	£1.20
10 AMP RANGE (TO48)		
SC45A	100	95p
SC45B	200	£1.00
SC45D	400	£1.25
SC45E	500	£1.45
15 AMP RANGE (TO48)		
SC50A	100	£1.25
SC50B	200	£1.35
SC50D	400	£1.65
SC50E	600	£1.85
DIAC D32 25p		
TRIACS		


SINCLAIR 3000 ONLY *£32.50

SINCLAIR PROJECT 60S

The easy new way to buy and build project 60. Comes in one handy pack containing PZ5, two Z30 amplifiers. Stereo 60 and the new master-link module, which has all the input sockets and output components needed. Special cut to length leads make all soldering unnecessary.
ONLY *£18.80

SINCLAIR PROJECT 60

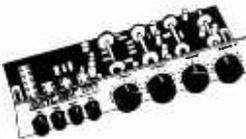Z30 £3-50
Z50 £4-25
PZ5 *£3-70
PZ6 *£5-99
PZ8 with trans *£7-32
Q18 *£6-85
AFU £4-50



Stereo 60 Preamp/Control Unit .. £7.80
Project 60 kit (see below) .. £2.50
Stereo 60/2 Z30/PZ5 .. *£15.30
Stereo 60/2 Z30/PZ6 .. *£17.60
Stereo 60/2 Z50/PZ8/Trans .. *£21.80
Project 60S .. *£18.80
Project 60 FM tuner .. *£19.50


PROJECT 60 KIT

Our extremely popular kit contains the extra capacitors, DIN plugs and sockets, cables and wire holder needed to complete Project 60 at the attractive price of £2.50.

S-DECS AND T-DECS


The breadboards for the transistor age.

S-DECS £1.40
T-DECS £2.80
µ-DEC A £3.00

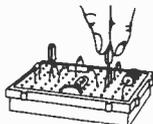

Carriers with sockets to mount 14 and 16 pin in line ICs on T-DeC and µ-DeC A £1.25.

SINCLAIR SUPER IC12

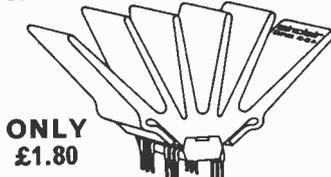

ONLY £1.80

Complete with free printed circuit board and 44 page instruction book.

IC12 KITS

POWER UNIT Components for a 28V 0.5 Amp power unit ideal for all versions *£2.00. Also suitable Sinclair PZ5 *£3.70.

LOUD SPEAKER Specially chosen for the IC12. 5" x 8 ohm £1.00. 5" x 8" x 8 ohm £1.45. 10" x 6" 15 ohm *£2.00.

BASIC KIT Contains components for the P.C. board and volume and simple tone controls. Mono version £1.10. Stereo model with balance control £2.39

DELUXE KIT Contains components for P.C. board and volume and full treble and bass controls. Should be used with one of preamps below. Mono unit £1.30. Stereo model with balance control £2.79.

PREAMP KIT Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1.28. Stereo £2.28. Type 2 for ceramic or crystal pickups. Mono 48p. Stereo 96p.

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent.

Mail order only. Postage 37p per order on orders containing one or more items with prices marked with an *. Postage on other orders 10p.



LOUDSPEAKER

BARGAINS

Fane Pop 100 Watt 18" 8/15 ohm £19.50
Fane Pop 60 Watt 15" 8/15 ohm £11.15
Fane Pop 50 Watt 12" 8/15 ohm £9.25
Fane Pop 25/2 12" 25 watts £5.40
Fane Pop 15 12" 10 watts £4.00
Baker Group 25 12" 3, 8 or 15 ohm £5.75
Celestion PS8 for Unilux £2.35
EMI 13 x 8, 3, 8 or 15 ohms £2.25
EMI 13 x 8 d/cone 3, 8 or 15 ohms £2.60
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms £3.60
Richard Allen 8" 3, 8 or 15 ohm £2.35
Fane 8" dual cone 808T £2.85
Fane 3" d/cone roll surround 807T £3.50
Elac 59RM109 8" x 5" 15 ohm £2.70
Elac 59RM114 9 x 5 8 ohm £2.70
Elac 6 1/2 d/cone 8 ohm £2.25
Elac 4" tweeter 8 ohm £1.50
Crossover for above (post free) £1.50
Richard Allen 12" 3 or 15 ohm £2.50
Goodmans 8 P, 8 or 15 ohm £4.75
Goodmans 10 P, 8 or 15 ohm £5.25
Goodmans 12 P, 8 or 15 ohm £10.50
Goodmans 15 P, 8 or 15 ohm £17.00
Goodmans 18 P, 8 or 15 ohms £27.50
2" 2 1/4" or 3" 80 ohm or 2 1/4" 64 ohm .65
7" x 4" 3 or 8 ohm £1.50
8" x 5" 3 or 8 ohm £1.50
10" x 6" 3, 8 or 15 ohm £2.00
Phillips 5" 8 ohm £1.95

FREE with orders over £6—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect. Prompt despatch p. & p. 25p per speaker.

WILMSLOW AUDIO, Dept. PW

10 Swan St., Wilmslow, Cheshire, SK9 1HF

EX-RENTAL TV's (UNTESTED)

Complete with 13 channel tuners. Good cabinets.

Carriage £1.50 extra.
19"/21" slimline (110° tube) .. £5.00
23" slimline £7.50
19" BBC 2 sets £14.50

TUBES EX EQUIPMENT (Tested)

SINGLE PANEL
19"/21" any type £3.00
23" any type £4.00
TWIN PANEL (BONDED)
19" bonded £5.00
All tubes add £1 carriage.

VALVES EX EQUIPMENT

EB91	5p	30L15	12p	PL36	22p
EBF80	12p	30P4	12p	PL81	17p
ECC82	12p	PC97	17p	PY81	18p
ECL80	7p	PCF86	17p	PY800	18p
EF80	12p	PC84	7p	PY82	7p
EF85	12p	PCF80	7p	PY33	22p
EF183	12p	PC089	12p	U191	17p
EF184	12p	PCL86	22p	8P23	17p
EY86	17p	PCL82	17p	30PL1	22p
30PL13	20p	PCL86	17p	30P12	20p
630LZ	12p	PCL83	12p	130F5	10p

Add 24p per valve p. & p., orders over £1 p. & p. free

UHF TUNERS

For Ferguson 850 900 chassis. Adaptable for most UHF Chassis £2.50, p. & p. 50p.

SLOT METERS

Smiths reconditioned switchmaster MK III. Decimalized. Perfect working order. 12 for £25 delivered. For sample send £2.50 c.w.o.

TRADE DISPOSALS (Dept. PW/TS)

Thorbury Roundabout, Leeds Ed., Bradford. Telephone 0274/865670

BARGAIN PRICE

BRAND NEW HARTLEY OSCILLOSCOPES CT916 in original packing. Band width up to 6 Mc/s. Mains supply. Price £40, p. & p. £1.50p.

NEW 8in. SPEAKERS 15 ohms 75p. p. & p. 10p.

BARGAIN PARCELS 14lb at £1.45 plus 32p p.p.: 28lb at £2.75 plus 52p p.p.: 56lb at £4.50 plus £1.25 p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E460 4/B/16 4VH, medium Persistence, green. Ideal scope tube. Also 09J 4 1/2 in. dia. Length 15in. Also 7BP7 and 3FP7 All unused as new. Price £1.40 post paid.

NEW HEAVY COAX CABLE dia. 1" 70 ohms approx. 50ft. lengths £1.40, p. & p. 30p. 100 ft. lengths £2.70, p. & p. 50p.

AERIALS New Condition Whip Type. 4ft. 20p; 11ft. 75p, all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 62p, p. & p. 25p. New matching unit coax connection for above, 80p, p. & p. 5p.

MARCONI HEADPHONES. Boxed as new 60 ohms £1.25 carriage paid.

CRYSTALS AS NEW: Hc 6a, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s. 50p each plus 8p p.p.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-260 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal—60p per doz. plus 17p p.p. Trimmers with Xtal—75p per doz. plus 17p p.p.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1" dia x 3 ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p, p. & p. 5p each. Minimum order 6.

AS NEW AERIAL TUNER UNIT No. 6 BF, consisting of 1 1/2 inch 500 micro/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5 1/2" x 4 1/2" x 5". Price £1.50 carriage paid.

HEADPHONES DI. High impedance. Good condition 75p, p. & p. 10p.

R209. Set of valves 62p, p.p. 25p.

NEW AERIAL WIRE ON BOARDS 7/8 UNCOVERED. 75ft. 40p, 90ft. 47p, 100ft. 50p, p. & p. 20p.

MUIRHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:
1. To Measure Gain up to 50 dba.
2. To Measure Loss up to 45 dba.
3. To Compare Power levels (A.F.).
4. As an Audio Frequency Generator covering 100 Hz. to 41 kHz. With a dial setting accuracy of ±0.5 Hz. Output: -1 M/V into 600 Ω. Complete with mains power unit. Tested. Good Condition. £12, p. & p. 75p.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition. £1 each section. Carriage 35p each section.

1" 75 ohms Coax in 50ft coils with BNC plugs good condition. price £1 + 30p. p.p.

8in. METERS. 0-50 volts. 0-40 amps. 0-20 amps. All moving coil. 62p, p.p. 12p.

SLIDING RESISTORS. 12 amp, 1ohm. Approx. 9in. long. 1-4 amp., 14 ohms. Approx. 7in. long. As new Ex Eq. 75p, p.p. 15p.

QUOTATIONS FOR QUANTITY.

AS NEW UNUSED REJECTOR UNITS for rejecting unwanted signals. Four ranges 1-2-10 Mc/s. £1.50 p. & p. 20p each.

AS NEW UNUSED AERIAL VARIOMETER. Cylinder design 10" x 4 1/2", suitable for tuning most aerials for signal strength. £1.50 p. & p. 20p.

NEW HEADPHONES AND MIKE RUBBER muff type low impedance 97p p. & p. 17p.

TF1449 SIGNAL GENERATORS. Good condition £18 p. & p. £1.50

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER,

Radio Dept.
HIGH STREET, CHESLYN HAY.
Nr. Walsall, Staffs.

DRILL CONTROLLER NEW IKW MODEL

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. \$1.50 plus 13p post and insurance. Made up model also available. \$2.25 plus 13p post & p.



MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 3 x 2 1/2. \$1.50 each.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic push-rod suitable for operating, 6p each, 45p doz.



MICRO SWITCH

5 amp changeover contacts, 9p each, 13 amp model 10p each or \$1.05 doz.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 2 way—2 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 20p each, \$1.80 for ten, your assortment.




WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.



ISA ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp, on/off switch. Switch on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price \$1.95 + 20p p & p or with glass front chrome bezel 75p extra.

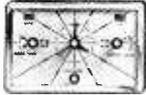

TREASURE TRACER MARK II

Complete Kit (except wooden batteries) to make the metal detector similar to the circuit in Practical Wireless August issue. \$3.95 plus 20p post and insurance.



SNAP ACTION SLIDE SWITCH

Rated 5a. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. 5p each, 10 for 45p.




NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hivac XN. 3, Price \$1.45 each, 10 for \$13.



12 WAY SUB-MINIATURE MULTI-CORE CABLE

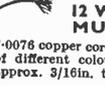7-0076 copper cores each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.




LIGHT CELL

Almost zero resistant in sunlight increases to 10 K Ohms in dark or dull light, epoxy resin cased. Size approx. 1in. dia. by 1/2in. thick. Bated at 500 MW, wire ended, 48p with circuit. Also ORP 12 light cell 46p.



MAINS TRANSISTOR POWER PACK

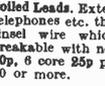Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: FP1, FP3, FP4, FP6, FP7, FP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only \$1 plus 20p postage.




GOOD COMPANION

We can now offer these again in modular version using Mullard AF & IF Modules and Radio-mobile Permeability Tuner. Shouldn't take more than an evening to make. Cabinet size approx. 11" wide x 8" high x 3" deep. Complete assembly instructions—\$4.75 plus 20p post & ins.



RADIO STETHOSCOPE

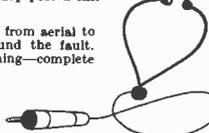Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. \$2—minus stetho-est instead of earpiece 75p extra post and ins. 20p



STANDARD WAFER SWITCHES

Standard 1/4" wafer—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	40p							
3 poles	40p	40p							
4 poles	40p	40p							
5 poles	40p	40p							
6 poles	40p	40p							
7 poles	70p	70p							
8 poles	70p	70p							
9 poles	70p	70p							
10 poles	70p	70p							
11 poles	70p	70p							
12 poles	70p	70p							

THYRISTOR LIGHT DIMMER

For any lamp up to 200 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price \$2.50 plus 20p post and insurance.



MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 500mW into 8 ohms speakers. Input suitable for crystal mic. or pick-up 9V battery operated. Size 2in long x 1 1/2in wide x 1 1/2in high. SPECIAL SNIP PRICE 65p each, 10 for \$5.80.



THIS MONTH'S SNIP

REPEATING TIME SWITCH

1 or 2 on/off per 24 hours. Repeats until re-programmed. Switches up to 15 amp. Switching time completely adjustable through 24 hours. Precision made with 24 hour dial. Miniature—will fit into 2" cube. Mains operated clock but switch may be isolated for switching battery sets. Ideal for—shop window lighting, anti-theft devices, central heating control and many other automatic processes. Price with instructions \$2 each + 20p post and insurance.



HORSTMANN 'TIME & SET' SWITCH

(A30 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc. up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around \$5. Special snip price \$1.50 Post and ins. 23p.



HONEYWELL THERMOSTAT

Made by Honeywell for normal air temperatures 40°-90°F (5-25°C). This is a precision instrument with a differential which can be adjusted to better than 1/2° F. A mercury switch breaks on temp. rise—the switch is operated by a coiled bi-metal element and adjustable heater is incorporated for heat anticipation. Elegantly styled and encased in an ivory plastic case with clear plastic windows thermometer above and control processing. Regular price probably around \$5. Special snip price \$1.25 each or ten for \$11.25.




ZPM—MODULATION MOTOR

Could also be used to open ventilators, doors, valve, damper etc. particularly suitable for remote control. Made by Satchwell. Essentially a reversible geared motor fitted with internal limit switches to stop it at the end of its travel. Size approx. 6" x 6" x 5 1/2" and weighing approx. 10 lbs. This is extremely powerful and would lift a heavy door or open a long line of ventilators. To operate this motor you put the 50 cycle supply through a change over switch. For instance a thermostat with change-over contacts could automatically regulate the temperature in a growing house, chicken hatchery etc. An indicator on the motor graduated 0-10 shows the state of open or close. Also internally fitted is a variable resistor; wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if both direct from Satchwell, our price complete with step down Transformer is \$15.




INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPV matched pair. Regular price of parcel well over \$5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only \$1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

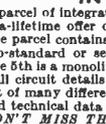

MULLARD I.F. MODULE

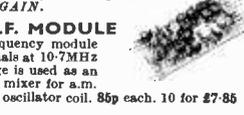This is a fully screened intermediate frequency module for amplification and detection of f.m. signals at 10-7MHz and a.m. signals at 470kHz. The first stage is used as an i.f. amplifier for f.m. and a self oscillating mixer for a.m. operation, in conjunction with an external oscillator coil. 85p each, 10 for \$7.85 100 for \$62.50p. With connection dig.



EDUCATIONAL KITS—all with pictorial instructions

THIS BALANCE KIT FREE Eagle educational kits. Japanese made these are even better value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 7 kits \$2.50 with free balance kit.



KA2 Lens Kit. Eleven parts, including candle one concave lens, one convex lens, stage and all frame, etc. Watch light rays bend as they pass through different lenses.

KA3 Water Pump Kit. Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Three types of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle.

KA4 Buzzer Kit. Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch result in an operating buzzer.

KA5-2 Pole Motor Kit. Twenty-four parts, including enamel wire, armature and pole piece, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.

KA7 Electro-Magnet Kit. Fifteen parts, includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.

KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. Conduct illustrates and educational projects to learn the application of "OHM'S LAW" and see the difference in current and resistance with different types and lengths of wire.

KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.

TAPE HEADS

Miniature size 1/4" square front x 1/4" deep. Under-stand made for Truvox. Double wound, maybe wired in series or parallel for high or low impedance working. Each supplied with matching erase head. 2 track 60p pair, 4 track 75p pair. Less 10% 10 or more pairs.

KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate. Instrument Motors fitted with Gear Box. These made by Smiths Industries are as fitted into electric clocks, chart recorders etc. Motor size approx. 1 1/2" dia. x 1" deep. Gear box attached approx. 2" diameter x 1/2" thick with good length of spindle. Most motors are fitted with a 1/2" long x 1/2" diameter drive spindle. Suitable for 200/240v mains 50 c.p.s. unless marked otherwise. Following speeds available—3 revs per min., 15 revs per min., 30 revs per hour, 6 revs per hour (60 cycles), 4 revs per hour (60 cycles), 2 revs per hour, 8 revs per hour, 6 revs per day. All \$1 each or 10 for \$8.

Micro Switch. Made by Burgess. 15 amp off/on—normally closed. Size 1 1/2" x 1/2" x 1". Price 15p each or 10 for \$1.35. Operation is by pressure on tiny ball.

2 Amp Switched Sockets. Oblong, brown bakelite surface mounting—2 pin Standard domestic type. 10p each or 10 for 90p.

Surface Switches. 5 amp British make. Brown bakelite—oblong—1 way 10p each, 2 way 15p each.

Torch Bulbs. Empire made. 2.5v and 3.5v. Boxes of 25—25p or 10 boxes for \$2.25.

3 Core Maroon Cotton Covered Flex. Very best makers but old coloured code. 6 amp—23/36 x 100 yd coil \$2 plus 50p, 15 amp—70/36 x 60yd coil \$2.95 plus 50p post.

Delay Switch. Glass tubular encased on 4 pin base gives a delay of 60 secs. when 3v are applied to the electrically isolated heater. Delay can be shortened to approx 1 second by increasing the heater voltage up to 6 or 7v. Price 50p each or 10 for \$4.50.

Miniature Tubes. These are approx. 1/2" diameter and need miniature bi-pin end connectors. 3 sizes available:—9" 6 watt, 12" 8 watt, 21" 13 watt. All are 65p each. Less 10% on 10 or more.

A.C. Mains Buzzer. These are open constructions intended for fitting into instruments etc. Size approx. 1 1/2" x 1 1/2" x 1" deep x 1/2" wide. 25p each, 10 for \$2.25.

4 Watt Amplifier Module. Made by Mullard Ref. No. EP9000. Part of the Unilex system. This has an output of 4 watt speech and music into a 12-15 ohm speaker. A powerful amplifier with a thousand uses—completely encased. Size approx. 2 1/2" x 1 1/2" x 1 1/2". Screw down input and output terminals. Price \$1.45 each or 10 for \$13.05.

Pre-Amplifier Module. 2 channel for Stereo. Input sensitivity 320mV. Part of the Mullard Unilex system and completely encased. Size 4" x 4" x 1". Screw down input and output terminals. Price \$1.80 each or 10 for \$16.20.

Where postage is not stated then orders over 25 are post free. Below 25 add 20p. Semiconductor add 5p post. Over £1 post free. S.A.E. with enquiries please.

J. BULL (ELECTRICAL) LTD.

(Dept. P.W.), 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, Croydon.

All prices in pounds and new pence

VALVES		6BA6		25 6J6		20 7C5		11-13 128R7		40 137		40 DAF91		30 EBL31		60 N108		11-50 PL508		90 UABC80			
1A7GT	45	6B6	30	6J7M	45	7C6	75	14H7	50	42	40	DAP96	30	EC80	35	EL92	65	OA2	38	PL509	11-10	UAF42	55
1CP31	57-00	6BH6	70	6J7GT	70	7D5	60	19AQ5	50	50B5	50	DC99	11-35	EC81	35	EL94	25	OC3	38	PL802	95	UBC41	50
1D5	50	6B7A	45	6K8GT	45	7H7	60	20P1	50	50C5	50	DF33	55	EC82	30	EL95	35	OZ4	40	PX4	52-50	UBC81	40
1H5	50	6BR8	90	6K7M	60	7H7	75	20P2	70	50CD6G	11-20	DF70	45	EC83	30	ELL80	11-00	PC86	60	PX25	52-50	UBF80	40
1NSGT	55	6BR7	11-80	6K7GT	35	9BW6	60	20P5	11-20	78	45	DF96	45	EC84	30	EM80	45	PC87	60	PY33	63	UBF89	35
1R5	40	6BW6	85	6K8M	60	10C2	63	25A6	35	80	55	DF92	50	EC85	40	EM81	60	PC97	50	PY81	30	UCB4	48
1R4	30	6BW7	80	6K8G	40	10P1	75	25L8GT	50	85A2	50	DF92	50	EC86	40	EM84	35	PC88	40	PY82	35	UCB8	40
1R5	30	6C4	33	6K8GT	50	10F3	60	20Y5	65	150B2	60	DK32	45	EC87	45	ECH42	75	PC89	50	PY83	38	UCF90	55
1T4	30	6C9G	35	6K25	75	10F9	60	25Z4	30	150C4	60	DK91	40	EC88	45	ECH42	75	PC89	50	PY83	38	UCF90	55
3Q4	40	6C6	25	6L6G	50	10F18	50	25Z5GT	55	801	60	DK92	55	EC89	45	EZ41	50	PCF86	60	R19	75	UCL83	60
3Q5	40	6C6DG	11-25	6L8	45	10LD11	65	25Z6	65	807	50	DK96	50	EC90	45	EZ80	27	PCF86	60	R19	75	UCL83	60
3Q5	50	6CH6	60	6Q7G	40	10P13	60	30C1	30	813USA	53-75	DL66	11-25	EC91	35	EZ81	29	PCF86	60	R19	75	UCL83	60
3R4	35	6CW4	65	6Q7GT	42	11E3	54-00	30C15	30	30C18	80	DL92	35	EC92	35	EZ91	30	PCF86	60	R19	75	UCL83	60
3V4	48	6D6	35	6S47M	40	12A7E	30	30C17	90	941	60	DL92	35	EC93	40	EZ91	30	PCF86	60	R19	75	UCL83	60
5R4GY	75	6E5	80	6S47M	75	12A7T	30	30C18	80	1025	55	DL94	48	EC94	40	EZ91	30	PCF86	60	R19	75	UCL83	60
5U4G	35	6F1	70	6S47M	40	12A7U	30	30C19	85	4022AR	55-50	DL95	50	EC95	40	EZ91	30	PCF86	60	R19	75	UCL83	60
5Y3GT	40	6F6G	35	6S47GT	30	12A7X	30	30FL12	11-20	7193	30	DL96	45	EC96	45	EZ91	30	PCF86	60	R19	75	UCL83	60
5Z4G	40	6F8G	50	6S47GT	40	12A7Y	30	30FL14	85	7475	50	DL96	45	EC97	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6J30L2	80	6F11	40	6S47GT	35	12B2E6	40	30FL15	85	A81	48	DL96	45	EC98	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6A7	75	6F13	45	6S47GT	35	12C8GT	35	30FL17	90	ATP4	60	DL96	45	EC99	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6A8G	40	6F14	70	6S47GT	40	12E1	52-20	30P4	11-12	ATP5	60	DL96	45	EC100	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AK5	35	6F23	85	6U4GT	65	12J5GT	30	30P12	30	ATP7	60	DL96	45	EC101	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AM5	35	6F24	75	6U5G	40	12J7GT	50	30P19	85	AU2	54-00	DL96	45	EC102	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AM6	38	6F28	65	6V6G	60	12K8GT	50	30P13	93	AZ1	55	DL96	45	EC103	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AQ5	38	6F32	65	6V6GT	40	12Q7GT	40	30P14	90	AZ31	55	DL96	45	EC104	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AR7G	85	6G6	25	6X4	35	12S47GT	50	35A6	75	CB131	11-00	DL96	45	EC105	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AT6	35	6H6	23	6X5G	40	12S7GT	35	35A7	60	CB135	75	DL96	45	EC106	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6AU6	25	6J5M	50	6X5GT	40	12S8T	75	35Z3	70	CY30	63	DL96	45	EC107	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6BA6	11-00	6J5G	50	7B6	70	12S8T	40	35Z4GT	60	CY31	43	DL96	45	EC108	45	EZ91	30	PCF86	60	R19	75	UCL83	60
6B9G	25	6J5GT	30	7B7	50	12S8T	60	35Z5	60	DAC32	50	DL96	45	EC109	45	EZ91	30	PCF86	60	R19	75	UCL83	60

Transistors		BFY50		22 OA91		07 OC170		25		Integrated Circuits		7437		65 7473		40 7493		75 74123		11-35 74176		11-35 74176	
1N914	07	2N3702	10	BZY88	15	OAZ207	47	OC200	40	7400	20	7423	48	7440	20	7475	65	7496	21-00	74145	11-50	74191	11-95
18113	25	2N3819	10	CR61-40	47	OAZ210	52	OC200	40	7401	20	7425	48	7441	20	7482	87	7497	26-25	74150	11-10	74193	22-00
18202	23	2N4209	30	GET102	30	OAZ224	45	OC200	40	7402	20	7427	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2G302	22	AAZ12	15	GET882	25	OAZ241	22	OC200	40	7403	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2G371	22	AC126	20	GET882	25	OAZ241	22	OC200	40	7404	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N404	20	AC127	25	GJ7M	37	OAZ246	23	OC200	40	7405	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N697	15	AC128	20	K8100A	20	OAZ246	23	OC200	40	7406	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N706	10	AC129	20	MJE230	87	OC35	90	OC200	40	7407	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N1132	25	ACY39	30	MJE285	OC44	17	ZTX500	16	7406	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00	
2N1305	22	AD140	20	MJE285	OC44	17	ZTX503	17	7407	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00	
2N2147	75	AD149	50	MJE3055	87	OC57	60	ZTX531	25	7408	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2160	60	AD161	37	NKT212	27	OC58	60			7409	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2218	20	AF115	25	NKT214	15	OC59	65			7410	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2219	20	AF117	25	NKT223	33	OC71	12			7411	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2369A	15	AS Y28	25	NKT251	24	OC72	20			7412	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2444	11-61	BC107	10	NKT713	25	OC81	20			7413	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2446	45	BC108	10	OA70	10	OC81D	20			7414	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2904	20	BC109	10	OA71	10	OC82	25			7415	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N2926	10	BC169C	15	OA81	08	OC82D	20			7416	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00
2N3055	75	BF898	28	OA85	12	OC84	25			7417	20	7428	48	7442	75	7480	80	7497	26-25	74150	11-10	74193	22-00

RST VALVE MAIL ORDER CO.
 16a WELLFIELD ROAD, LONDON SW16 2BS
 Special Express Mail Order Service
 Send large S.A.E. for list. Phone 677 2424 (4 lines)
 Express postage 1p per transistor, over 10 post free. Integrated Circuits & Valves 5p, plus 1p for each additional item, over £5-00 post free.

Train for television

Course commences 6th September, 1972

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
 (Dept. PW12 34a Hereford Rd., London W2 5AJ)

TEXAN 20+20 WATT. STEREO AMPLIFIER

Electro Spares can now supply all the components to build the "Texan" Amplifier, featured in *Practical Wireless* May/June 1972. All components are brand new with fibre glass p.c. board, all metalwork, knobs, finished silver trim front panel, etc. etc.

TOTAL COST OF COMPLETE COMPONENTS ONLY £27.85—POST FREE!

All components are available separately, to enable the constructor to obtain just what parts he requires at any one time. Please send S.A.E. for free list.

SPECIAL CONTEMPORARY STYLE SLIMLINE METAL CASE WITH WOODEN END CHEEKS IS NOW AVAILABLE FOR THIS AMPLIFIER—DETAILS INCLUDED WITH ALL LISTS, OR AVAILABLE

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

TYPE SW.100
100 x 80 mm.

50μA	23-60	20V. D.C.	23-10
50-0-50μA	23-45	50V. D.C.	23-10
100μA	23-45	300V. D.C.	23-10
100-0-100μA	23-35	1 amp. D.C.	23-10
500μA	23-20	5 amp. D.C.	23-10
1mA	23-10	300V. A.C.	23-10
		VU Meter	23-75

BAKELITE PANEL METERS

TYPE S-80
80 mm. square fronts

50μA	23-20	50V. D.C.	23-60
50-0-50μA	23-10	300V. D.C.	23-60
100μA	23-10	1 amp. D.C.	23-60
100-0-100μA	23-00	5 amp. D.C.	23-60
500μA	23-75	300V. A.C.	23-60
1mA	23-60	20V. D.C.	23-20
		VU Meter	23-37

"SEW" CLEAR PLASTIC METERS

Type MR.55P. 4 1/4 in. x 4 1/4 in. fronts.

50μA	23-60	150V. D.C.	23-60
50-0-50μA	23-10	300V. D.C.	23-60
100μA	23-10	15V. A.C.	23-60
100-0-100μA	23-00	300V. A.C.	23-60
200μA	23-00	8 Meter 1mA	23-87
500μA	23-60	VU Meter	23-60
500-0-500μA	23-80	1 amp. A.C.	23-60
1mA	23-60	5 amp. A.C.	23-60
1-0-1mA	23-80	10 amp. A.C.	23-60
5mA	23-80	20 amp. A.C.	23-60
10mA	23-80	30 amp. A.C.	23-60

Type MR.55P. 2 1/2 in. square fronts.

50μA	23-10	10V. D.C.	23-00
50-0-50μA	23-60	20V. D.C.	23-00
100μA	23-60	50V. D.C.	23-00
100-0-100μA	23-50	150V. D.C.	23-00
200μA	23-60	15V. A.C.	23-10
1mA	23-00	300V. A.C.	23-10
5mA	23-00	8 Meter 1mA	23-10
10mA	23-00	VU Meter	23-80
50mA	23-00	1 amp. A.C.	23-00
100mA	23-00	5 amp. A.C.	23-00
1 amp.	23-00	10 amp. A.C.	23-00
5 amp.	23-00	30 amp. A.C.	23-00

Type MR.55P. 3 1/4 in. x 3 1/4 in. fronts.

50μA	23-37	10V. D.C.	23-20
50-0-50μA	23-75	20V. D.C.	23-20
100μA	23-75	50V. D.C.	23-20
100-0-100μA	23-65	150V. D.C.	23-20
200μA	23-60	15V. A.C.	23-10
500-0-500μA	23-20	300V. A.C.	23-10
1mA	23-20	150V. A.C.	23-10
5mA	23-20	300V. A.C.	23-10
10mA	23-20	500V. A.C.	23-10
50mA	23-20	5 Meter 1mA	23-27
100mA	23-20	15V. A.C.	23-87
200mA	23-20	50mA A.C.	23-20
1 amp.	23-20	100mA A.C.	23-20
5 amp.	23-20	200mA A.C.	23-20
10 amp.	23-20	500mA A.C.	23-20
15 amp.	23-20	1 amp. A.C.	23-20
20 amp.	23-20	5 amp. A.C.	23-20
30 amp.	23-20	10 amp. A.C.	23-20
50 amp.	23-20	20 amp. A.C.	23-20
5V. D.C.	23-20	30 amp. A.C.	23-20

*** MOVING-IRON ALL OTHERS MOVING COIL**
Please add postage

SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	25-00	20V. d.c.	24-80
100μA	24-85	50V. d.c.	24-40
1mA	24-40	300V. d.c.	24-40
50-0-50μA	24-65		
1A d.c.	24-40	Dual range	
5A d.c.	24-40	500mA/5A d.c.	24-65
10V. d.c.	24-40	5V/50V d.c.	24-65

Type MR.39P. 1 21/32 in. square fronts.

200mA	21-60	300mA	21-60
500mA	21-60	500mA	21-60
750mA	21-60	1 amp.	21-60
2 amp.	21-60	5 amp.	21-60
10 amp.	21-60	3V. D.C.	21-60
3V. D.C.	21-60	10V. D.C.	21-60
10V. D.C.	21-60	15V. D.C.	21-60
20V. D.C.	21-60	20V. D.C.	21-60
30V. D.C.	21-60	100-0-100μA	21-75
150V. D.C.	21-60	200μA	21-65
500V. D.C.	21-60	500-0-500μA	21-60
300V. D.C.	21-60	1mA	21-60
750V. D.C.	21-60	1-0-1mA	21-60
15V. A.C.	21-60	5mA	21-60
50V. A.C.	21-70	10mA	21-60
150V. A.C.	21-70	20mA	21-60
300V. A.C.	21-70	50mA	21-60
500V. A.C.	21-70	100mA	21-60
8 Meter 1mA	21-70	150mA	21-60
VU Meter	21-60		

Type MR.45P. 2 1/2 in. square fronts.

50μA	22-25	5 amp.	21-70
50-0-50μA	22-10	10V. D.C.	21-60
100μA	22-10	20V. D.C.	21-60
100-0-100μA	21-87	50V. D.C.	21-60
200μA	21-87	300V. D.C.	21-60
500μA	21-75	15V. A.C.	21-80
500-0-500μA	21-70	300V. A.C.	21-80
1mA	21-70	8 Meter 1mA	21-85
5mA	21-70	VU Meter	22-25
10mA	21-70	1 amp. A.C.	21-70
50mA	21-70	5 amp. A.C.	21-70
100mA	21-70	10 amp. A.C.	21-70
500mA	21-70	20 amp. A.C.	21-70
1 amp.	21-70	30 amp. A.C.	21-70

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/4 in. square fronts.

1 amp.	21-95
2 amp.	21-95
5 amp.	21-95
15 amp.	21-95
30 amp.	21-95
50 amp.	21-95
5V. D.C.	21-95
10V. D.C.	21-95
20V. D.C.	21-95
50V. D.C.	21-95
150V. D.C.	21-95
300V. D.C.	21-95
50V. A.C.	21-95
150V. A.C.	21-95
300V. A.C.	21-95
500μA	22-20
500mA A.C.	21-95
1 amp. A.C.	21-95
5 amp. A.C.	21-95
10 amp. A.C.	21-95
20 amp. A.C.	21-95
30 amp. A.C.	21-95
50 amp. A.C.	21-95
VU Meter	23-10

EDGWISE METERS

Type PE.70. 3 1/8 17/32 in. x 1 15/32 in. x 2 1/2 in. deep

50μA	23-10	500μA	22-75
50-0-50μA	23-00	1mA	22-45
100μA	23-00	300V. A.C.	22-45
100-0-100μA	22-90	VU Meter	23-40
200μA	22-90		

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!

HIOKI MODEL 720X
20,000 O.P.V.
Overload protection
5/25/100/500/1000 VDC.
10/50/250/1000 VAC.
50μA/250mA. 20K/2 meg
ohm. — 5 to + 62db.
24-97. P. & P. 15p.

MODEL PL436
200Ω/Volt D.C.
8KΩ/Volt A.C.
Mirror scale.
-6/3/12/30/120/600V
D.C. 3/30/120/600V
A.C. 50/600A/60/
600 mA. 10/100K/
Meg/10 Mms/5
-20 to +46db. 24-97J P & P 12p

MODEL 5025 57 Ranges,
Giant 5 1/4 in. Meter, Polarity
Reverse Switch.
Sensitivity: 50K/Volt D.C.
5K/Volt A.C. D.C. Volts:
125, 25, 1.25, 5, 10, 25,
50, 125, 250, 500, 1,000V.
A.C. Volts: 1.5, 3, 5, 10, 25,
50, 125, 250, 500, 1,000V.
D.C. Current: 25, 501A, 2.5, 5, 25, 50, 250,
500mA, 5, 10 amp. Resistance: 2K, 10K,
100K, 1MEG, 10 MEG. Decibels: -20 to
+85 db. 21-50. P. & P. 17p.

HIOKI MODEL 700X
100,000 O.P.V. Overload
protection. Mirror scale.
-3/8/1-2/1-5/3/6/12/30/60/
120/300/600/1200VDC
1.5/3/6/12/30/60/150/300/600/
1200 V.A.C.
15/30μA/3/6/30/60/150/300mA
6/12 AMP. DC. 2K/200K/2
Meg/20 Meg ohm -20 to
+63 db 21-50. P. & P. 20p.

ROUND SCALE TYPE PENCIL TESTER

MODEL TS.68
Completely portable, simple
to use pocket sized tester.
Ranges 0/3/30/300V AC
and DC at 2,000 o.p.v.
Resistance 0-20K
ONLY 21-97 P. & P. 13p

**TMK MODEL 117 F.E.T. ELECTRONIC
VOLTMETER**
Battery operated,
11 meg input, 26
ranges. Large 4 1/2"
mirror scale. Size
3 1/2" x 4 1/2" x 2 1/2".
DC VOLTS 0.3-
1200V. AC VOLTS
3-300V RMS. 8-0-
800V P-P. DC CUR-
RENT 12-12MA.
Resistance up to 2000ohm.
-20 to +51 db. Complete with leads/instruc-
tions. 21-70. P. & P. 20p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal
generator covering
120 Kcs-500 Mc/s on
6 bands. Directly cali-
brated Variable R.F. at-
tenuator, audio output,
Xtal socket for calibra-
tion. 220/240V. A.C.
Brand new with instruc-
tions \$15. Carr. 37p.
Size 140 x 215 x 107
mm.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20cps to 200
kc/s on 4 bands.
Square: 20cps to
30 kc/s. Output
impedance 5,000
ohms, 200/250V.
A.C. operation.
Supplier's brand
new and guaran-
teed with instruc-
tion manual and leads. 21-75. Carr. 37p.

TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering
120 kc/s-260
Mc/s on 6 bands.
Directly calibrated
variable R.F. at-
tenuator. Operation
200/240V A.C.
Brand new with in-
struction. \$15
P. & P. 37p. S.A.E.
for details.

240° Wide Angle 1mA Meters
MW1-6 60mm square 23-97J
MW1-8 80mm square 24-97J
P. & P. extra

MODEL LT.101 1000 O.P.V.
0/10/250/1000
0/10/50/250/1000 V. A.C.
0/1/100 M.A. 0/150 K ohms.
21-97. P. & P. 15p.

TMK MODEL MD.120
Mirror scale. 20K/Volt D.C.
10K/Volt A.C. 30/60/300/
600/3,000 V. D.C. 6/12/20/
1,200 V.A.C.
Current 0-60μA/0-12/0
300mA. 0-60K/0-6 MegΩ.
-20 to +63 db. 24-82J
P & P 15p

MODEL 500 30,000 O.P.V.
with overload protection
mirror scale 0/5/2-5/10/25
100/250/500/1,000V. D.C.
0/2-5/10/25/100/250/500/
1,000V. A.C. 0/50μA/5/50/
500mA. 12 amp. D.C.
0/60K/8 Meg/60 Meg Ω.
28-87J. Post paid.

TMK LAB TESTER.
100,000 O.P.V. 6 1/4 in.
Scale Buzzer Short Cir-
cuit Check. Sensitivity:
100,000 O.P.V. D.C. 5K/
10Volt A.C. 10 D.C. Volt:
5, 2.5, 1.0, 50, 250, 1,000
V. A.C. Volts: 3, 10, 50,
50, 250, 500, 1,000V.
D.C. Current: 10, 100μA,
10, 100, 500mA, 2.5, 10
amp. Resistance: 1K, 10K, 100K, 10MEG,
100MEG Ω. -20 to +49 db.
Plastic Case with Carrying Handle. Size:
7 1/4 in. x 6 1/4 in. x 3 1/4 in. 21-90. P. & P. 25p

RUSSIAN 22 RANGE MULTIMETER

Model U457 10,000 o.p.v.
A first class versatile in-
strument manufactured in
U.S.S.R. to the highest
standards. Ranges: 2-5/10/
50/250/500/1000V D.C. 2-5/
10/50/250/500/1000V A.C.
DC Current 100 μA/1/10/
100mA/1A. Resistance
300 ohms/3/30/300K/3m Ω.
Complete with batteries—
test leads, instructions and
sturdy steel carrying case.
OUR PRICE 25-97 P. & P. 25p.

TO-3 PORTABLE OSCILLOSCOPE

3in. tube, Y amp. Sensitiv-
ity 0.1v p-p/CM. Band-
width 1.5 cps-1.5 MHz.
Input Imp. 2 meg Ω 25pF
X amp. Sensitivity 0.9v.
p-p/CM. Bandwidth 1.5cps-
800KHz. Input Imp. 2
meg Ω 20pF. Time base.
5 ranges 10 cps-300KHz.
Synchronization. Internal/
external. Illuminated scale. 140 x 215 x 330
mm. Weight 15lb. 220/240V. A.C. Supplied
brand new with handbook. 240-00. Carr. 50p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or
bench mounted.
Basic meter meas-
ures 1 volt D.C.
but can be used to measure a wide range of
AC and DC volt. current and ohms with
optional plug in cards. Specification: Accu-
racy: ±0.2 ±1 digit. Resolution: 1mV.
Number of digits: 3 plus fourth overrange
digit. Overrange: 100% (up to 1999). Input
Impedance: 1000 Meg ohm. Measuring cycle:
1 per second. Adjustment: Automatic zero-
ing, full scale adjustment against an internal
reference voltage. Overload: to 100V. D.C.
Input: Fully floating (3 poles). Input power:
110-230V. A.C. 50/60 cycles. Overall size:
5 1/4 in. x 2 1/8 in. x 8 3/16 in. AVAILABLE
BRAND NEW AND FULLY GUARAN-
TEED AT APPROX. HALF PRICE.
249-97J. Carr. 50p.

G. W. SMITH & CO (RADIO) LTD.
Also see next two pages

SEM-CONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415		2N4568		BC114		BFW90		NKT219	
2G301	80P	2N3416	22P	2N4569	35P	BC115	15P	BPW91	22P	NKT223	30P
2G302	20P	2N3417	37P	2B102	25P	BC116	15P	BPX12	22P	NKT224	22P
2G303	20P	2N3439	130P	2B103	25P	BC117	15P	BPX13	22P	NKT225	22P
2G306	42P	2N3440	97P	2B104	25P	BC118	15P	BPX29	25P	NKT229	30P
2G308	30P	2N3535	15P	2B302	60P	BC121	20P	BPX30	25P	NKT237	35P
2G309	30P	2N3566	22P	2B303	60P	BC122	20P	BPX37	30P	NKT238	25P
2G371	15P	2N3568	25P	2B304	60P	BC125	15P	BPX44	37P	NKT240	27P
2G374	20P	2N3569	25P	2B305	60P	BC126	20P	BPX68	87P	NKT241	27P
2G381	22P	2N3570	125P	2B306	60P	BC134	12P	BPX84	25P	NKT242	20P
2N388A	49P	2N3572	97P	2B307	60P	BC136	12P	BPX87	25P	NKT243	62P
2N404	20P	2N3573	27P	2B308	60P	BC137	15P	BPX86	25P	NKT244	17P
2N696	15P	2N3606	27P	2B309	60P	BC138	20P	BPX88	20P	NKT262	30P
2N697	15P	2N3607	22P	2B310	47P	BC140	35P	BPX89	62P	NKT263	20P
2N698	25P	2N3638	18P	2B311	47P	BC141	35P	BPX93A	70P	NKT264	20P
2N699	30P	2N3638A	20P	2B312	47P	BC146	10P	BPY18	25P	NKT265	20P
2N706	10P	2N3641	18P	2B313	47P	BC149	12P	BPY19	25P	NKT274	20P
2N709A	12P	2N3642	18P	2B314	47P	BC149	12P	BPY21	42P	NKT275	25P
2N708	15P	2N3643	20P	2B315	47P	BC152	17P	BPY24	42P	NKT276	25P
2N709	62P	2N3644	25P	2B316	47P	BC153	20P	BPY29	40P	NKT281	27P
2N718	25P	2N3645	25P	2B317	47P	BC154	20P	BPY30	40P	NKT401	87P
2N718A	30P	2N3691	15P	2B318	47P	BC157	15P	BPY41	50P	NKT403	75P
2N726	30P	2N3692	18P	2B319	47P	BC158	12P	BPY43	42P	MKT407	55P
2N727	30P	2N3693	15P	2B320	47P	BC160	35P	BPY50	20P	NKT404	55P
2N914	17P	2N3694	18P	2B321	47P	BC167	11P	BFY51	20P	NKT405	75P
2N916	17P	2N3707	10P	2B322	47P	BC167B	10P	BFY52	15P	NKT406	82P
2N918	30P	2N3703	10P	2B323	47P	BC168C	11P	BFY53	15P	NKT451	62P
2N929	22P	2N3704	11P	2B324	47P	BC169B	11P	BFY56A	57P	NKT452	62P
2N930	20P	2N3705	10P	2B325	47P	BC169C	18P	BFY76	42P	NKT453	62P
2N987	40P	2N3706	9P	2B326	47P	BC171	15P	BFY77	25P	NKT713	20P
2N1090	22P	2N3707	11P	2B327	47P	BC171	15P	BFY90	65P	NKT717	42P
2N1091	22P	2N3708	7P	2B328	47P	BC172	15P	BFY21	42P	NKT724	27P
2N1131	22P	2N3709	10P	2B329	47P	BC172	15P	BFY24	42P	NKT725	25P
2N1132	25P	2N3710	9P	2B330	47P	BC173	15P	BFY29	40P	NKT726	20P
2N1302	17P	2N3711	12P	2B331	47P	BC177	20P	BFY30	40P	NKT727	25P
2N1303	17P	2N3713	18P	2B332	47P	BC178	20P	BFY32	42P	NKT731	20P
2N1304	22P	2N3714	20P	2B333	47P	BC179	20P	BFY33	42P	NKT732	20P
2N1305	22P	2N3715	12P	2B334	47P	BC182	15P	BFY34	42P	NKT733	20P
2N1306	25P	2N3716	12P	2B335	47P	BC182L	10P	BFY35	42P	NKT734	20P
2N1307	25P	2N3717	12P	2B336	47P	BC183	15P	BFY36	42P	NKT735	20P
2N1308	25P	2N3718	12P	2B337	47P	BC183L	10P	BFY37	42P	NKT736	20P
2N1309	25P	2N3719	20P	2B338	47P	BC184	11P	BFY38	20P	NKT737	20P
2N1507	17P	2N3820	50P	2B339	47P	BC184L	11P	BFY39	20P	NKT738	20P
2N1613	20P	2N3823	50P	2B340	47P	BC185	11P	BFY40	20P	NKT739	20P
2N1631	35P	2N3824	50P	2B341	47P	BC185L	11P	BFY41	20P	NKT740	20P
2N1632	35P	2N3825	50P	2B342	47P	BC186	11P	BFY42	20P	NKT741	20P
2N1637	80P	2N3825A	27P	2B343	47P	BC187	27P	BFY45	15P	OC28	25P
2N1638	27P	2N3825A	40P	2B344	47P	BC187L	12P	BFY46	15P	OC28	25P
2N1639	27P	2N3826	30P	2B345	47P	BC187L	12P	BFY47	15P	OC28	25P
2N1701	16P	2N3826A	30P	2B346	47P	BC188	11P	BFY48	15P	OC28	25P
2N1711	24P	2N3826A	40P	2B347	47P	BC188C	11P	BFY49	15P	OC28	25P
2N1889	32P	2N3854	30P	2B348	47P	BC189	11P	BFY50	15P	OC28	25P
2N1893	32P	2N3855	27P	2B349	47P	BC189C	11P	BFY51	15P	OC28	25P
2N2147	72P	2N3859A	32P	2B350	47P	BC189C	11P	BFY52	15P	OC28	25P
2N2160	57P	2N3860	30P	2B351	47P	BC189C	11P	BFY53	15P	OC28	25P
2N2193	40P	2N3866	15P	2B352	47P	BC189C	11P	BFY54	15P	OC28	25P
2N2193A	42P	2N3877	40P	2B353	47P	BC189C	11P	BFY55	15P	OC28	25P
2N2194	27P	2N3877A	40P	2B354	47P	BC189C	11P	BFY56	15P	OC28	25P
2N2194A	34P	2N3890	37P	2B355	47P	BC189C	11P	BFY57	15P	OC28	25P
2N2217	20P	2N3900A	40P	2B356	47P	BC189C	11P	BFY58	15P	OC28	25P
2N2218	20P	2N3901	37P	2B357	47P	BC189C	11P	BFY59	15P	OC28	25P
2N2219	20P	2N3903	20P	2B358	47P	BC189C	11P	BFY60	15P	OC28	25P
2N2220	20P	2N3904	25P	2B359	47P	BC189C	11P	BFY61	15P	OC28	25P
2N2221	25P	2N3905	30P	2B360	47P	BC189C	11P	BFY62	15P	OC28	25P
2N2222	20P	2N3906	27P	2B361	47P	BC189C	11P	BFY63	15P	OC28	25P
2N2222A	25P	2N4058	12P	2B362	47P	BC189C	11P	BFY64	15P	OC28	25P
2N2297	30P	2N4059	10P	2B363	47P	BC189C	11P	BFY65	15P	OC28	25P
2N2368	15P	2N4060	12P	2B364	47P	BC189C	11P	BFY66	15P	OC28	25P
2N2369	15P	2N4061	12P	2B365	47P	BC189C	11P	BFY67	15P	OC28	25P
2N2369A	15P	2N4062	12P	2B366	47P	BC189C	11P	BFY68	15P	OC28	25P
2N2410	42P	2N4063	12P	2B367	47P	BC189C	11P	BFY69	15P	OC28	25P
2N2483	27P	2N4248	15P	2B368	47P	BC189C	11P	BFY70	15P	OC28	25P
2N2484	32P	2N4249	15P	2B369	47P	BC189C	11P	BFY71	15P	OC28	25P
2N2539	22P	2N4250	18P	2B370	47P	BC189C	11P	BFY72	15P	OC28	25P
2N2540	22P	2N4254	42P	2B371	47P	BC189C	11P	BFY73	15P	OC28	25P
2N2613	35P	2N4256	42P	2B372	47P	BC189C	11P	BFY74	15P	OC28	25P
2N2614	30P	2N4264	17P	2B373	47P	BC189C	11P	BFY75	15P	OC28	25P
2N2646	49P	2N4265	17P	2B374	47P	BC189C	11P	BFY76	15P	OC28	25P
2N2711	25P	2N4286	17P	2B375	47P	BC189C	11P	BFY77	15P	OC28	25P
2N2712	25P	2N4287	17P	2B376	47P	BC189C	11P	BFY78	15P	OC28	25P
2N2713	27P	2N4288	15P	2B377	47P	BC189C	11P	BFY79	15P	OC28	25P
2N2714	30P	2N4289	17P	2B378	47P	BC189C	11P	BFY80	15P	OC28	25P
2N2904	50P	2N4290	12P	2B379	47P	BC189C	11P	BFY81	15P	OC28	25P
2N2904A	25P	2N4291	15P	2B380	47P	BC189C	11P	BFY82	15P	OC28	25P
2N2905	25P	2N4292	15P	2B381	47P	BC189C	11P	BFY83	15P	OC28	25P
2N2905A	20P	2N4294	17P	2B382	47P	BC189C	11P	BFY84	15P	OC28	25P
2N2906	20P	2N4303	47P	2B383	47P	BC189C	11P	BFY85	15P	OC28	25P
2N2906A	25P	2N4964	16P	2B384	47P	BC189C	11P	BFY86	15P	OC28	25P
2N2907	23P	2N4965	18P	2B385	47P	BC189C	11P	BFY87	15P	OC28	25P
2N2923	15P	2N5027	52P	2B386	47P	BC189C	11P	BFY88	15P	OC28	25P
2N2924	15P	2N5028	37P	2B387	47P	BC189C	11P	BFY89	15P	OC28	25P
2N2925	15P	2N5029	47P	2B388	47P	BC189C	11P	BFY90	15P	OC28	25P
2N2926G	10P	2N5030	42P	2B389	47P	BC189C	11P	BFY91	15P	OC28	25P
2N2926G	10P	2N5172	12P	2B390	47P	BC189C	11P	BFY92	15P	OC28	25P
2N2926Y	10P	2N5174	52P	2B391	47P	BC189C	11P	BFY93	15P	OC28	25P
2N3011	20P	2N5175	52P	2B392	47P	BC189C	11P	BFY94	15P	OC28	25P
2N3014	32P	2N5176	45P	2B393	47P	BC189C	11P	BFY95	15P	OC28	25P
2N3053	18P	2N5232A	30P	2B394	47P	BC189C	11P	BF			

Practical Wireless Classified Advertisements

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. The advertiser warrants that the advertisement does not contravene any of the provisions of the Trade Descriptions Act, 1968.
2. The Publishers reserve the right to refuse or withdraw any advertisement.
3. Advertisements accepted for publication cannot be cancelled without the Publishers' express consent.
4. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences however caused.

Miscellaneous

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW
(S.A.E. for details)


TO: 'BOFFIN PROJECTS'
DEPT. KW2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p post free.

"SHORTWAVE Voices of the World," £1.55; an exceptional book. "SWL address book," Stations' QSL Policies, £1.35. "World Radio TV Handbook," December 1971, £2.80. Under £2, postage 10p. Deliveries First Class Mail, send 3p for price list. Send no money—COD 25p. David McGarva, Box 114A, Edinburgh EH1 1HP.

12 VOLT FLUORESCENT LIGHTS

(as illustrated)

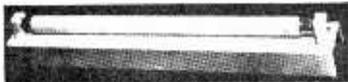

Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt £3.60 post paid
21 ins. 13 watt £4.60 post paid

Callers welcome.

For lists or enquiries, large s.a.e.

SALOP ELECTRONICS, 23 WYLE COP
SHREWSBURY, SHROPSHIRE.

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

Classified advertisements 9p per word (minimum 12 words). Semi-display setting £6.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Darned Electronic Wizardry

by Dewtron

Famous kits, e.g. waa-waa complete kit £2.95; Puzz kit £4.75. auto rhythm, modules from £18 per set. Ring Modulator modules £7 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

TAPE HEADS PICK-UP CARTRIDGES

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required.

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,
Chilton Works, Garden Road,
Richmond, Surrey.

PRINTED CIRCUIT BOARD

In 6 standard widths: 2in, 2½in, 3in, 3½in, 4in, and 5in x any length. 1/16in Fibreglass, single sided, 2p per 3 sq. inches. Doublesided, 1p per sq. inch. P. & P. 5p per order. S.A.E. Quotations for other sizes and quantity discounts.

J. KNOPP, 11 Connaught Gardens, Braintree, Essex, CM7 6LY. Tel. Braintree 25254.

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (G)

17 Buckridge, Portpool Lane, London, E.C.1



Build your next project in a BEC (Book End Chassis)—a new concept in Chassis buying. No cabinet to build when you have finished. Contemporary design with wooden end cheeks. 3 sizes. These cabinets are adaptable to all projects in P.W. and P.E., Texan, Gemini etc. Send large S.A.E. for details.

H. M. ELECTRONICS, 275a Fulwood Road, Sheffield, S10 3BD Phone 55951 anytime

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

Ladders

LADDERS. Timber 20ft, £7.80; 29ft, £11.20. Carr. 80p. Brochure (Dept. WLS), Home Sales, Baldwin Road, Stourport, Worcs. Callers Welcome. Phone 02-993 5222. Ansafone installed.

Tape Recorders

ROBIN HOOD (NOTTM) LTD.

Special Offer—Post Free. First Class British Made

Non-stretch Mylar Tapes

5½ins. ½" x 900ft. 55p

5½ins. ½" x 1200ft. 60p

7ins. ½" x 1200ft. 60p

7ins. ½" x 1800ft. 85p

10% discount on orders over £5

23 Wadham Road, Woodthorpe, Nottingham

Hi-Fi Equipment

Peerless

HI-FI LOUDSPEAKERS

... Acclaimed by the Experts

MULTI-UNIT SYSTEMS

IN KIT FORM

MATCHING CABINET KITS

ALSO AVAILABLE

Full details & address of your local dealer from:

P.F. & A.R. Helme Ltd. (Dept PW10)
Summerbridge: Harrogate HG3 4DR
Yorks. Tel. Darley 279 (STD 0423-72)

Books and Publications

COMPONENT CATALOGUE AND DISCOUNT VOUCHERS
25p Post FREE (UK)

W.E.C. LTD.
HIGH ST., RIPLEY, Surrey



THE PICTURE BOOK METHOD OF LEARNING

BASIC ELECTRICITY 5pts £4.50. **BASIC ELECTRONICS** 6pts £5.40. **BASIC TELEVISION** 3pts £3.60

(Postage and Packing included)

The Pictorial Approach Manuals assure the quickest and soundest method of gaining mastery over these subjects. The clear and concise illustrations make study a real pleasure. Your money refunded if not completely satisfied is your 100% Guarantee. Free Illustrated Prospectus on request.

Send now to **SELRAY BOOK CO., 60 HAYES HILL, BROMLEY BR2 7HP**

Educational

LEC

TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing September 11th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. A/10, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

CIE, AMSE, City & Guilds, etc. Thousands of exam successes. Postal Courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept H.8), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

RADIO, TV, RTEB CERTS., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book FREE: BIET (Dept. H.7), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS RD., LONDON, SW6 4UJ

Direct from the Manufacturers
U.H.F. AERIALS

EASY ASSEMBLY KITS

10 Element
£1.25 **SAVE 40%**
on normal retail price

14 Element **£1.50** 18 Element **£1.75**

Mix. Clamp optional extra

Ready assembled add 20p allow 32%p. carriage and packing. Please state which channels or group.

APEX AERIALS (P.W.)

ALBAN WORKS, MARY ST., JOHNSTONE, RENFREWSHIRE



GENUINE FULL SIZE 18 element TV aerial
as used by leading TV companies

FOR ONLY **£1.99**
+ 35p cart



ITV BBC1 & 2 BLACK/WHITE & COLOUR

Guaranteed Perfect Pictures. Save ££s. We supply this genuine U.H.F. aerial for only £1.99, can be fitted outside or inside. Quality made, technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice.

Money Back Guarantee. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters.

Send direct to Dept (D) PW10 219 Mansfield Rd., Nottingham.

IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists

BAINES FOR HIGH FREQUENCY AERIALS

UHF Multibeams by J Beam
MBM 10 £2.10 MBM 18 £2.90 MBM 30 £3.90 MBM 46 £6.00 2MBM 46 £15.20 4MBM 46 £33.00 UHF Diplexers £1.00. Log Periodic £5.25.

VHF Aerials
FM2 £2.00 FM3 £3.00 FM4 £5.00 FM6S £7.80 BBC D and ITA 5 £2.70 ITA 5 element £2.00 ITA 8 element £2.70.

Pre-amps:
Masthead £7.00 Colourbooster £3.88 Wideband Masthead £9.50 Co-ax VHF 5p UHF 9p. Please state channels on all orders

R Baines

11 Dale Cres., Tupton, Chesterfield. S42 6DR

Situations Vacant

HIGH SALARY AND A SECURE FUTURE

Get into the Computer Industry the fast, easy way. In only 4 weeks we can train you for a career as a **COMPUTER OPERATOR**. With pay prospects of £2,500 p.a. **JOBS GALORE!** Train with LCOTC and our exclusive appointments bureau—one of the leaders of its kind in the world—introduces you to eager computer users. Find out more FREE and without obligation. Write or telephone TODAY!

London Computer Operators Training Centre
E93, Oxford House
9-15, O. lord Street, W.1.
Telephone: 01-734 2874

127, The Piazza, Dept. E93,
Piccadilly Plaza, Manchester 1.
Telephone: 061-236 2935

RADIO OFFICERS

DO YOU HAVE PMG I, PMG II, MPT 2 YEARS OPERATING EXPERIENCE?
Possession of one of these qualifies you for consideration for a Radio Officer post with the Composite Signals Organisation.

On satisfactory completion of a 7-month specialist training course, successful applicants are paid on scale rising to £2365 pa; commencing salary according to age—25 years and over £1664 pa. During training salary also by age, 25 and over £1238 pa with free accommodation.

The future holds good opportunities for established status, service overseas and promotion. Training courses commence at intervals throughout the year. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:

RECRUITMENT OFFICER (TRO 37), GOVERNMENT COMMUNICATIONS HEADQUARTERS,

Room A/1105, Oakley Priors Road, CHELTENHAM, Glos. GL52 5AJ

Telephone: Cheltenham 21491, Ext. 2270

WE ARE Importers and distributors of important professional motion picture equipment.

WE ARE looking for service mechanics with all types of background for our modern and happy service department.

WE ARE Inviting all service mechanics who are looking for a better deal to contact:— Mr. Shaw or Mr. Davis,

AV DISTRIBUTORS LONDON LTD., 26 PARK ROAD, BAKER STREET, LONDON NW1 4SH. Tel No: 01-935-8161/2

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Tel. Hastings 29066.

NIP-E-BOARD

PRINTED CIRCUIT SYSTEMS
FOR DISCRETE AND INTEGRATED
COMPONENTS AND CIRCUITS

Standardised multi-purpose boards
SAMPLE PACKS - 3 DIFFERENT SIZES WITH FULL DETAILS IN EACH

SRBP Un drilled 95p Drilled £1-84

GLASS FIBRE Un drilled £1-09 Drilled £2-15

Please state whether for i.c.s or discrete transistors.

SPECIAL OFFER! FREE Mounting Pillars with above pack

STARTER PACKS of mixed un drilled boards (small) 50p & 70p

CARD HANDLES - 5p. Gold plated Edge Connectors 14-way 35p

Insulated Mounting Pillars - from 3p each 30-way 60p

NIP ELECTRONICS DEPT. NE, P.O. Box 11, St Albans, Herts

PLANNING CHART SUPPLIED WITH BOARDS

Quantity discounts. We supply retail trade, industry, export, schools

Build the TEXAN hi-fi amp

Kit price only
£28.50
(incl. case)



Pack 1. RESISTORS	80p
Pack 2. SMALL CAPS	£1.50
Pack 3. LARGE CAPS	£1.40
Pack 4. SUNDRIES	£1.90
Pack 5. SWITCHES	90p
Pack 6. CONTROLS	£1.45
Pack 7. SEMI COND	£8.25
Pack 8. TRANSFORMER	£4.95
Pack 9. P.C. BOARD	£2.50
Pack 10. CHASSIS etc.	£4.20

Post extra - parts available separately.
Send for list.

Kits also available for

- ★ Radio Control Systems
- ★ Digital Clock Systems
- ★ Integrated Circuit Amplifiers (to 50W)
- ★ Hi-Fi Pre-amps
- ★ Stabilized Power Supply Units

TELERADIO HI FI, 325 Fore Street,
London, N.9.
01-807 3719

Trampus electronics

All Brand New, Money Back
Guaranteed, Fast Service.
5V DIGITAL INDICATOR
0-9 DP, with socket £1.49
7447 driver £1.49. SAE free
data. LED micro type £6.99.
LIGHT EMIT DIODES. Visible
red 1-5V & red panel clip £1.99.
Infrared £1.49. ORP 13 40p.
IC Photo Detector/amp 44p.
ZENERES BZ788 400mV 12p.



CAPACITORS
25V 10/50/100 uF 5p. DISC 22 pF to 0.1uF 4p.
0.1 to 5 uF 5p. RESISTORS 1W 0.5% 11p
ULTRASONIC transducer transmit/receive £2.
DIL SOCKETS, plastic for 74N etc. 14 & 16 Pin 18p.
TEXAN: 72741 80p. 72748 80p. IN 4002 5p.
TIP 41A £1. TIP 42A £1.30. BC182 11p. BC212 18p.
BC107 8p. BC108 8p. BC109 8p. BC177/9 17p.
2N3055 40p. JET 2N 3819 25p. ME 0404/2 17p.
ME 0411-2 18p. ME 4001 12p. ME 4102 11p.
2N 3702/3/4/5/6/7 11p. 2N3708/9/10/11 5p. AC 125/
6/7/8, AC 127/8, AF 117 all 16p each. T18 43 28p.
BFF 51 16p. 2N2926Y 9p. 2N3053 19p. 2N706A 12p.

INTEGRATED CIRCUITS with data.
709 T05 23p. DIL 30p. 741 T05/DIL 20p 710 37p.
748 30p. TAD100/110 RX £1.75. Data Booklet 15p.
STEREO: MPX Decoder £1.67. Dual Preamp £1.49.
AUDIO AMP 8-WAY HI FI £1.29. 703 RP 69p.
GAS detector: Smoke, Butane, Petrol etc. £2-18.
FREE CATALOGUE SAE DATA SHEETS 5p ea.
C.W.O. P & P 7p. Overseas 35p. Discount 10+ %
P.O. BOX 29, BRACKNELL, BERKS.

RAPID SERVICE - GOOD VALUE Money Back Guarantee

MICROCIRCUITS: 709 30p; 710 36p; 723 71p; 741 32p;
748 40p; PA230 90p; PA234 84p; 8L402A £1; 8L702C
40p; SN76013 (like IC12) £1.24; 74 SERIES TTL: 00
16p; 01 18p; 02 18p; 04 18p; 08 18p; 10 18p; 11 21p; 20
16p; 30 19p; 40 16p; 47 £1.35; 51 18p; 72 30p; 73 41p;
74 33p; 75 44p; 81 £1.28; 86 41p; 90 75p; 91 £1.21.
RECTIFIERS 1 AMP: 50V 3p; 100V 4p; 200V 5p; 400V
6p; 600V 9p; 800V 12p; 1000V 14p. 3 AMP 200V 11p;
400V 12p. TRIAC 10 AMP 600V £1.20. SCR 1-6 AMP
600V 75p. TRANSISTORS: 2N2926 RED 6p; ORANGE
7p; GREEN 9p; 2N3054 38p; 2N3055 42p; 2N3819 25p;
BC107B 9p; BC108A 8p; BC108C 9p; BC109C 9p; BC115
20p; BC179 18p; BCY 70 10p; BCY 71 22p; BD142 25p;
BF115 20p; BFX86 16p; BFY00/51/52 10p; OC44/45/71/
72 12p; OC81 19p; ME SERIES: 0401 19p; 0402 18p;
0404-2 16p; 0411 18p; 0412 19p; 0413 14p; 0414 24p;
1002 10p; 1120 16p; 3001 16p; 4101 10p; 4102 11p;
4103 10p; 6001 12p; MEF104 42p; MEL11 35p; MEL12
44p; MP8111 32p; MP8112 42p; IC SOCKETS 14 pin
DIL 12p. SOLDERCONS 0-7p per pin. LED 45p. PC
MARKER 80p.

JEF ELECTRONICS (P.W.10)

York House, 12 York Drive, Grappenhall, Warrington,
WA4 2EJ. Mail Order Only. C.W.O. P & P 9p per order.
O/secs 65p. Discounts start at 10% for 10+. List free
on application. NEW FULL SPEC. GOODS.

SOUND SUPPLIES (Electronics) Co. Ltd.

P.A. EQUIPMENT. Marshall amps, instru-
ments and guitars, etc. TOA and Eagle
amps and accessories, Resio mics, etc.
COMPONENTS: Resistors, capacitors,
plugs, sockets, cables, audio leads, semi-
conductors, valves, voice board, etc., for
the constructor.
Power packs and car droppers for the
cassette recorder or radio.
S.A.E. for list and enquiries. P.A. list 15p
12 Smartis Lane, Loughton, Essex
Tel. 01-508 2715 Closed all day Thursday

FERRIC CHLORIDE

ANHYDROUS, 1 lb 40p + 15p post, 10 lbs £3.50 +
60p post.

REED SWITCH UNITS

Contains 31 1A. 250V. REEDS mounted round a
drum. Magnet inside operates them, also 1% R.a.
plugs etc. £1.25 + 25p post. GREENWELD (PW5),
24 Goodhart Way, W. Wickham, Kent. 01-777 2001.

NEW POTENTIOMETERS, 4p. Resis-
tors, 50 16p. Magnetic counters 10p.
6BA Bolts 10p 100. Samples and lists
20p. Post extra. We buy communica-
tions receivers for cash. S.a.e. Derwent
Radio, Scarborough.

RECEIVERS and accessories. B40/62B
fine-tuning, S-meter and product de-
tector kits and information. SAE
details. P. R. Gollidge, G3EDW, Glen
Tor, Torrington, Devon. Tel: 08-052
2411.

THE WORLD RENOWNED "GLOBE KING" SHORT WAVE RADIO KITS now back in production!

New, exciting range of short-wave units covering
10 to 350 metres. Transistor 9v. and AC mains
versions. Ideal for Flats etc.—range the World
with just 25' length of wire or Rod aerial
Acclaimed by professional and amateur alike
"Globe-King" receivers are in use all over the
world. Modern technique plus a precision mechani-
cal standard opens up a new era for this famous
product. Send for free copy of our interesting
literature, price lists, and order form—kindly
enclose self-addressed long envelope. Overseas
inquiries must be accompanied with International
Reply Coupon. (See also our advert on page 568).

JOHNSONS (RADIO)

St. Martins Gate, Worcester, WRI 1DT
(a John Banner Co.)

GEIGER COUNTERS

(FOR MAINS OR PORTABLE
BATTERY USE)

Latest Home Office release and probably the last,
of this well known Contamination Meter No. 1, this
very useful instrument is used for the measurement
of Radio-Activity. Indicated on an Internal Meter
scaled 0.1 to 10 milli Rontgens/Hour, a socket is also
provided for additional sound Monitoring on Head-
phones. This Instrument is housed in a Strong light
Alloy Case, placed in a carrying Haversack with
shoulder strap. Containing Cable and Hand held
Probe. Instruction Card, plus the latest plug in Vi-
brator Power Unit, which uses current small Transistor
Radio Batteries (4 Mallory Long Life RM12 or
4 EverReady H.P.7 or equivalent makes).



For Mobile use anywhere. (Cost Gov. approx. £70
each). Supplied Brand New in Carton only £5.50
carr. 50p. An additional plug in Power Unit for
Laboratory use, operating from 100-120 volts or 200-
250 volts A.C. Mains is also available. Supplied Brand
New in Carton at only £2.50 post 25p. Headphones (not necessary) if required £1.50
A few Geiger Counters as above but not boxed in cardboard cartons, available
at only £4.50.

JOHNS RADIO Dept. D, 424 Bradford Road,
Batley, Yorks. Phone Batley 7732

REED COILS

3, 6, 9, 12, 24V Miniature 27p
Small 27p
Standard 34p

P & P. 7p on all orders.

REED PUSH BUTTON SWITCHES

Momentary Action
1 contact £1-00
2 contacts £1-25
Illuminated 1 contact £1-30
Illuminated 2 contacts £1-55

REELS OF ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g. 50, 100 & 200 grams. Send for prices

C.B.M. ELECTRONIC COMPONENTS LTD.

26 Avon Trading Estate, Avonmore Road, London, W.14

REED SWITCHES

Large range of many sizes, types
and manufacture
Popular types:
E Small n/o 10 for 50p
A Miniature n/o 24p each
B Standard c/o 40p each

REED RELAYS

Many versions available, popular
types: 3, 6, 9, 12, 24V
Miniature 1/A normally open 56p
Small 2/E 1 contact 36p
2/EE 2 contacts 44p
2/EE 3 contacts 52p
STD 3/B change over 87p

★ SERVICE SHEETS • MANUALS • BOOKS ★

SERVICE SHEETS OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK ON RADIOS, TV'S, R. PLAYERS AND T.RECORDERS, ETC... SERVICE SHEET 30p + Postage PLEASE ENCLOSE S.A.E. WITH ENQUIRIES... Catalogue 20p.

NEW BOOKS & PUBLICATIONS	PRICE + P & P
23. FOUNDATIONS OF WIRELESS AND ELECTRONICS by M.G. Scroggie. 552 pages.	£3.00 25p
24. WIRELESS SERVICING MANUAL by W.T. Cocking. 286 pages	£1.50 15p
25. BEGINNER'S GUIDE TO RADIO by G.J. King. 7th Edition. 204 pages	£1.00 15p
47. RAPID SERVICING OF TRANSISTOR EQUIPMENT by G.J. King. 160 pages	£1.50 15p
48. BEGINNER'S GUIDE TO ELECTRICITY by Clement Brown. Assoc. Brit. I.R.E.	£1.00 10p
49. BEGINNER'S GUIDE TO ELECTRONICS by Terence L. Squires. AMIERE	£1.00 10p
50. BEGINNER'S GUIDE TO TRANSISTORS by J.A. Reddihough	£1.00 10p
51. PRINCIPLES OF SEMICONDUCTORS by M.G. Scroggie. B.Sc.Eng. F.I.E.E. 156 pages	£1.50 15p
52. THE PRACTICAL AERIAL HANDBOOK by G.J. King. 232 pages	£2.70 20p
70. TRANSISTOR EQUIVALENTS AND SUBSTITUTES HANDBOOK by B.B. Boboni. 78 pages	£0.40 7p
71. RADIO AMATEURS OPERATORS HANDBOOK by Data Publications Ltd., 80 pages	£0.45 7p
82. QUESTIONS & ANSWERS ON ELECTRIC MOTORS by A.J. Coker.	£0.60 10p
83. QUESTIONS & ANSWERS ON ELECTRICITY by K.G. Jackson	£0.60 10p
84. QUESTIONS & ANSWERS ON ELECTRONICS by Clement Brown. Assoc. Brit. I.R.E.	£0.60 10p
99. RADIO SERVICING by G.N. Pochett. Vol.1. Basic Electrotechnology.	£0.60 10p
100. RADIO SERVICING by G.N. Pochett. Vol.2. Intermediate Radio Theory.	£0.90 10p
101. RADIO SERVICING by B. Foxord, B.Sc.Eng. C.Eng. M.I.E.E. Vol.3. Final Radio Theory	£0.75 10p
102. RADIO SERVICING by G.N. Pochett. Vol.4. Fault-Finding	£0.70 10p

Send S.A.E. for Free LISTS of Practical and Technical Books on Radio & Television now available to

BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorks. Tel. 0423-86844

Receivers and Components

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateur, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p.&p 10p U.K. only.

Illustrated catalogue of selected kits and components. 15p P&P free.

Galleon Trading Co.
12, Burns Way,
Corningham,
Stanford-Le-Hope,
Essex.

BRAND NEW COMPONENTS BY RETURN. Electrolytics 16V or 25V—1, 2, 2, 4, 7, 10 mfd's—3/2p, 22, 47—4p, 100—5p. 50V—1/2p extra. Subminiature bead-type tantalums—1/35V, .22/35V, .47/35V, 1/35V, 2/2, 35V, 4/7/35V, 10/16V—8p. Mylar Film 100V—001, 002, .005, .01, .02—2p, .04, .05—2 1/2p, .068, .1—3p. Polystyrene 63V—10 pf.—10,000 pf. E.12 series—2p. Mullard miniature Carbon Film Resistors E12 series 1/3W 10—10MΩ 8 for 5p. Insured postage 8p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

AARVAK ELECTRONICS Soundlight. Convertors 3 Channel 1.2kW £17. 3kW £25. Strobes 1 Joule £16. 4 Joule £25. Mail or call, 74 Bedford Ave., Barnet, Herts. 01-449 1268.

PRECISION POLYCARBONATE CAPACITORS

FRESH STOCK — FULLY TESTED

Close tolerance. High stability. All 83V d.c.

0.47µF: ±5% 80p; ±2% 40p; ±1% 50p
1.0µF: ±5% 40p; ±2% 50p; ±1% 60p
2.2µF: ±5% 60p; ±2% 60p; ±1% 75p
4.7µF: ±5% 70p; ±2% 90p; ±1% 115p
6.8µF: ±5% 95p; ±2% 11.15; ±1% 11.80
10µF: ±5% 11.10; ±2% 11.40; ±1% 11.80
15µF: ±5% 11.80; ±2% 12.10; ±1% 12.70

TANTALUM BEAD CAPACITORS—Values available 0.22, 0.47, 1.0, 2.2, 4.7, 6.8 µF at 35V, 10 µF 25V, 15 µF 20V, 22 µF 15V, 33 µF 10V, 47 µF 6V, 100 µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (72 capacitors) £5.

NEW!—TRANSISTORS. BC107, BC108 BC109, All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices.

POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1. All brand new and marked.

SPECIAL OFFER—400 mW Zeners. Values available 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ± 5% at 5 mA. All new and marked. Price 12p each, 5 for 50p, 12 for £1.00.

RESISTORS. Carbon film 1W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47 and 0.5µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2in x 1in, 45p; 2.0µF, size 2in x 1in, 75p each.

C.D.I. (CAPACITOR DISCHARGE IGNITION).—440V A.C. capacitors listed above are ideal for use as discharge capacitors in popular ignition systems. Approved for P.E. Scorpio and P.W. (June 1971) systems. Improved reliability.

5p post and packing on all orders below £5. V. ATTWOOD, DEPT. D2, P.O. Box 8, ALRESFORD, HANTS.

MORSE PRACTICE OSCILLATORS

Consisting of Integrated Circuit, Loudspeaker, and battery fully wired, 85p, post 5p.

available from:

The Amateur Radio Shop (G4MH)
13 CHAPEL HILL, HUDDERSFIELD
Tel: 20774

VERNITRON CERAMIC RESONATORS for i.f. filtering. FM4, 10.7MHz (bandwidth 235kHz), matched pair £1.50. 455kHz types: TF-01A, 38p; TO-02A, 45p; TF-04 442, 40p; TFN-3A kit, £1.50; TFN-3ADX, £1.50; TF-2D5, 40p. Data supplied with orders. Mail order only, U.K. post 5p. AMATRONIX LTD., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

BUILD YOUR OWN LIQUID OIL WHEEL PROJECTOR SUITABLE FOR DISCO OR HOME ENJOYMENT — TOP QUALITY

6 inch dia. MULTICOLOURED OIL WHEEL

plus

1 R.P.M. MINIATURE GEARED MOTOR COMPLETE KIT. £6.50. incl. postage.

C. T. ELECTRONICS

267 ACTON LANE, LONDON W4 01-994 6275

SURPLUS ELECTRONICS WAREHOUSE NOW OPEN AT 20-24. BEAUMONT RD, LONDON, W.4. Thousands of component and equipment bargains.

NEW VALVES! GUARANTEED AND TESTED

24-HOUR SERVICE

1R5	25	80FL14	67	EABC80	80	EF91	12	PCCI89	48	PY82	24
185	21	80FL17	68	EB91	28	EF92	28	PCF80	25	PY800	30
1T	14	80P19	68	EC33	38	EF183	26	PCF86	44	PY801	30
384	24	80PL1	68	EF89	27	EF184	27	PCF801	27	R19	27
3V4	48	80PL13	67	EBC81	17	EL33	54	PCF802	38	U25	63
6/30L2	52	80PL14	68	ECC82	18	EL84	21	PCF805	58	U26	54
6AQ5	21	DAF91	21	ECC83	21	EV51	38	PCL82	28	U191	57
6BW7	48	DAF96	25	ECP82	28	EY86	27	PCL83	58	U281	60
6F1	57	DF91	14	ECH35	58	EZ80	19	PCL84	31	U329	65
6F23	67	DP96	25	ECH42	58	EZ81	21	PCL85	38	U801	75
6F25	40	DK91	25	ECH81	28	KT61	54	PCL86	85	UF89	29
68N7GT	28	DK92	47	ECL80	25	LT66	75	PFL200	40	UCCF5	84
12AU7	18	DK96	48	ECL82	27	N78	85	PL36	45	UCH81	28
25L8GT	18	DL92	24	ECL86	22	PC86	44	PL81	41	UCL82	21
30C15	58	DL94	46	EP39	38	PC88	44	PL82	29	UF89	28
30C17	75	DL96	36	EP80	22	PC97	35	PL83	31	UL84	27
30C18	58	DY86	21	EP85	28	PC90	28	PL84	28	UY41	37
30P5	63	DY87	21	EP86	28	PC94	28	PL500	59	UY85	22
30PL1	59	DY802	28	EP89	24	PC89	41	PL504	59	W77	42
								PY81	28	Z77	18

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no callers.

GERALD BERNARD 83 Osbaldeston Road, Stoke Newington, London N.16

BELLING LEE INSULATED TERMINALS. Red or Black, 6 amp. max. 10p pair, pp 34p

BERCOSTAT WIREWOUND RHEOSTAT. 50 volt, 800 Ω 25 watts, 2" dia. 25p. pp 71p.

FINNED ALUMINIUM HEATSINK 9" x 11". Ready Drilled. 80p. pp 61p

SMITHS CIRCULAR TAPE POSITION INDICATORS Resettable. 50p. pp 5p.

G.E.C. 5 AMP 240 VOLT A.C. CIRCUIT BREAKER. 75p. pp 101p.

SUB MIN CROC CLIPS. Red or Black, insulated 4p. Min. quantity, 6 pp 34p.

GARRARD MAG TAPE DECKS. 14ips, 50v solenoid operated brakes etc., Mains voltage motors 87-50 each, pp 21-23.

4 1/2" FLANNAIR FANS. Complete, capacitor, ex-equip. 2,800 r.p.m. 43-50. pp 40p.

ELECTRIC MOTORS, HOOVER OR CROMPTON PARKINSON. 250v. Single Phase A.C.

1/2 h.p. 1,440 r.p.m. 23-75 pp 21-00

1/2 h.p. 1,425 r.p.m. or 2,800 r.p.m. 26-75 pp 21-25

1/2 h.p. 1,440 r.p.m. 22-25 pp 75p

AUDIO CONNECTORS

3 pin Din Plug 18p each

5 pin Din Plug A type, B type . . . 18p ..

2 pin Din Speaker Plug/socket . . . 10p ..

3 pin Din Line Socket 18p ..

3-6mm Jack Plug Screened 10p ..

Standard Jack Plug 10p ..

Screened Standard Jack Plugs . . . 15p ..

Stereo Jack Plug 18p ..

Screened Stereo Jack Plug 18p ..

Phono Plugs: Red or Black 3p each.
pp on above items 34p.

B.S.R. MINI AUTO-CHANGER
Mono Cartridge 24-75 pp 30p.

MAINS NEONS.
Red or Green. Size: 1/2" x 1 1/2" 15p, pp 34p.

LEVER ACTION P.O.1000 TYPE SWITCHES.
Lock 4-pole changeover 15p, pp 34p. (ex-equip.)

Lock 2 Pole Changeover 10p pp 34p. (ex-equip.)

AUDIO LEADS
Screened Phono Leads 46" long, 15p

3-5 mm JACK/3-5mm JACK 7' 6" long 40p

5-Pin Din A Type, 5-PIN A TYPE. Approx 5' long
70p. pp above items 44p.

PIEZO DYNAMIC MICROPHONE
50k Ω 21-00 pp 8p.

MULLARD SCREW TERMINAL CAPACITORS
4,500 uf 64v. 7100 uf 40v. 50p each pp 10p.

BELLING LEE 1.5 amp in-line rubber covered
interference suppressor 25p pp 8p.

RUBBER 3 PIN 5 AMP NON REVERSIBLE CABLE
CONNECTORS 20p pp 54p.

SOLENOIDS 12 VOLT PULL ACTION
2" x 1" x 1/2" 40p pp 8p.

SIEMENS MINIATURE RELAY. Double pole
changeover dust cover/base 48v 2500 50p pp 5p new.

OMRON MK2 MIDGET POWER RELAY. 12v DC
Double pole Changeover. New. 70p pp 5p.

STC MINIATURE RELAY 280 Ω Perspex Cover
6-15v new, 85p pp 5p.

GARDNER'S POTTED TRANSFORMER 0-250v
Input: 18v 500mA/50v 150 mA, 6v 250 mA Output.
Size 3" x 2 1/2" x 2 1/2", 21-00, pp 20p. Ex equip tested.

TELESCOPIC AERIALS
Chromed 7" closed 28" extended 6 section ball
jointed base 23p pp 8p new.

MULLARD 4 DM 160 INDICATORS in plastic
holder/crop ex-equip. size approx. 1 1/2" x 1 1/2" x 1/2"
30p pp 8p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200
Diodes: 1 red relay: 1 AZ 229 zenner ass. capacitor/
resistors. Power supply 22v 250 mA DC. Output
240v. AC 21 pp 20p ex-equip.

TOGGLE SWITCHES. Single pole Double Throw
ex-equip. new condition. 50p doz. pp 13p.

PAINTON PLUG SOCKETS Type 159 series working
voltage 350v AC/DC current max. 3 amp AC/DC
7 pin plug & socket 50p pp 6p. 15 pin plug & socket
21 pp 6p. 31 WAY PLUG & SOCKET. 21-50.
pp 8p.

CASH WITH ORDER PLEASE

FIELD ELECTRIC LIMITED

3 Shenley Road,
Borehamwood, Herts.
Adjacent Elstree Mainline Station
Tel: 01-953 6009.

WOT MORE?

2N3819 29p, 2N5245 44p. F.E.T. Design ideas by Texas 12p. p.&p. 6p

Transistors, Resistors, Capacitors, Chips, Vero board, and more, send S.A.E.—The F.E.T. KING, 518 Nestrop Road, M/C 19 3JL

TV Line out-put transformers

Replacement types ex-stock.
For "By-return" service, contact:
London: 01-948 3702
Tidman Mail Order Ltd., Dept. PW,
236 Sandycroft Rd., Richmond, Surrey
TW9 2EG
Valves, Tubes, Condensers, Resistors,
Rectifiers and Frame out-put Transformers
also stocked.
CALLERS WELCOME

B.H. COMPONENT FACTORS LTD.

DEPT. PW
For Eagle, Sinclair, Data Books and Components,
4W 5% resistors 1p, or 50p/100.
Electrolytic C426 4/40, 8/40, 10/16, 32/10,
25/25, 100/6-4 all 4p. IN914 6p, 100V 1A
Bridge 35p, Panel neon 15p. Mains Trans-
formers 32-0-32 at 150mA 50p Bargain
Electrolytics. send for list. Electrolytic 100/50
10p, 500/25 10p, 1000/12 12p, 1000/25 25p,
1,000/50 35p, uL914 30p, 7,400/01/10/30 15p.
Free list. CWO. pp UK 10p. Discount £10-
10%. Money back guarantee. Brand new to
spec. P.O. Box 18, Luton, Beds, LU1 1SU.

INCOMPARABLE V.H.F. KIT

Johnsons CV2—unique triple-purpose (Con-
verter, Receiver, Tuner-Feeder) kit for the
Amateur enthusiast. Fantastic transistorized
performance. World Wide Sales. Complete
kit of top grade parts with coils covering
80-180 MHz, plus easy/build diagrams and
instructions. £4 direct from makers or
S.A.E. for free literature.

Crystal Set Kits—one or two waveband
now available. Send S.A.E. for free literature.
See also advert. on page 557.

JOHNSONS (RADIO)

St. Martins Gate, Worcester, WRI 2DT
Est. 1943 (a John Banner Co. Tel. 24864

RADIOSPARES (R.S.) COMPONENTS
specified for projects in this, and
other magazines supplied on request.
S.A.E. with all enquiries. The Hobbies
Shop, 32 The Parade, Cwmbran Town
Centre, Cwmbran, Mon.

SANKEN HYBRID HI-FI AUDIO AMPLIFIER Integrated Circuit



We have made a fortunate
purchase of these 25 watt
audio amplifier modules
from which you can build
your own quality equip-
ment. Requires only the
addition of 3 capacitors and
a resistance (apart from
power supply). Two mod-
ules provide 50 watts of
power. Heat sink require-
ments are simple. Distortion
at 1KHz. (10 watts) is only
0.2%!

Price: 25 watt amplifier type 1025A £7-95 (P/P 15p)
including technical data. Leaflet available. (50w
version can be supplied).

A complete kit is available to make a 25 watt +
25 watt stereo outfit (giving 100 watts of music
power) and this incorporates an integrated circuit
pre amplifier of very low distortion, plus P.S.U.
Price is only £37-50 and a case to suit can be supplied.
Demonstrated at our showrooms.

Teleradio Hi-Fi

325, FORE STREET, EDWINTON, LONDON N.9.
01-807-8719

Versatile

10 in ONE



"MINI-LAB" Comprising
AC/DC Voltmeter : Audio Generator :
Resistance Substitution : Capacitance
Substitution : DC Ammeter : Battery
Supply : RF Signal Generator : RF
Field Strength Indicator : Ohm Meter

All you need for testing. Money
back guarantee. £11-25
+ 25p P. & P.

Cash with order or write for data sheet to:

RSL Components, (Dept. PW),
Crickfield Lane, Bishops Stortford, Herts

For Sale

MORSE MADE EASY!!

FACT NOT FICTION. If you start RIGHT you will be
reading amateur and commercial Morse within a month
(normal progress to be expected).

Using scientifically prepared 3-speed records you
automatically learn to recognise the code RHYTHM
without translating. You can't help it, it's as easy as
learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only 23-30, Complete Course 24-60
(Overseas £1-00 extra) details only, 4p stamp. 01-860 2896

G8HSC (Box 10), 46 GREEN LANE, PURLEY, SURREY

**YUKAN 50 PROFESSIONAL THE
SELF-SPRAY YUKAN AEROSOL WAY-
Get these air drying GREY HAMMER
NOW! OR BLACK WRINKLE
(CRACKLE) finishes**

Yukan Aerosol sprays contain 85% fine quality particles every instant
spray. No spongy looking particles. Finishes available in grey and black
12p each pp 10p. Modern Egghead Black Wrinkle (Contract) 20p pp 10p
12p each (each 12p can get 1/2) £7p per brush bottom self spray can 21
p each. Also available heat and water resistant 85p. Black wrinkle
12p self spray cans only, 75p can pp
SPECIAL OFFER! One can for 50p (non-refundable) when you top up
order 2nd can for 25p. 75p. 100 cans for £10.00 (13 self spray 200m can
only) (14 200m) (100 available)
Price: 10 cans £10.00 for less amount direct to
DEPT PW YUKAN, 307a EDGWARE ROAD, LONDON W2 1BN
Customer Department. Min. 10p. Authorised
YUKAN Ltd. using Industrial Organisations—We can supply you too
Order at our Saturday 'Closed' Thursday afternoons

SEEN MY CAT? 5,000 items. Mechan-
ical & Electrical Gear, and materials.
S.A.E. K. R. WHISTON, Dept. PW,
NEW MILLS, Stockport.

TELEPHONE ANSWERING machines.
New and Reconditioned. £55/160.
STAM CO, 182a New North Road, N1.
01-286 6119.

Wanted

TOP PRICES PAID FOR NEW VALVES
popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8.
Yorkshire.

HIGHEST POSSIBLE cash prices for
Akai, B & O, Brenell, Ferrograph,
Revox, Sanyo, Sony, Tandberg, Uher,
Vortexion, etc. 9.30-5.00. 01-242 7401.

CASH PAID for New Valves. Payment
by return. WILLOW VALE, ELEC-
TRONICS, 4 The Broadway, Hanwell,
London, W.7. 01-567/5400-2971.

WE BUY New Valves, Transistors and
clean new components, large or small
quantities, all details, quotation by
return. WALTON'S, 55 Worcester
Street, Wolverhampton.

VALVES

**SAME DAY SERVICE
NEW! TESTED! GUARANTEED!**

SETS

1R5, 1R5, 1T4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for £1.12. DAF96, DF96, DK96, DL96, 4 for £1.65.

1R5	28	30C15	58	EAF42	60	EM80	38	PCF808	68	U801	80
1R5	22	30C17	76	EB91	10	EM81	38	PCL82	80	UABC80	82
1T4	16	30C18	58	EBC33	40	EM84	82	PCL83	57	UAF42	50
384	26	30C18	58	EBC41	54	EM87	50	PCL84	34	UB041	45
3V4	47	30FL1	65	EBC81	30	EY81	36	PCL85	38	UBF80	34
5U4G	41	30FL12	69	EBC90	22	EY86	39	PCL86	38	UBF89	32
5V4G	35	30FL14	68	EBF80	32	EY87	29	PCL88	65	UC84	32
5Y3GT	34	30L1	29	EBF83	39	EZ40	43	PCL800	76	UC85	35
5Z4G	35	30L15	70	EBF89	29	EZ41	43	PCL805	38	UCF80	32
6/90L2	54	30L17	67	ECC81	17	EZ80	22	PENA4	77	UCH42	58
6AL5	11	30P4	63	ECC82	20	EZ81	23	PEN36C	70	UCH81	32
6AM6	13	30P12	69	ECC83	35	EZ90	25	PEL200	52	UCL82	32
6AQ5	22	30P19	65	ECC85	34	GZ30	34	PL36	49	UCL83	55
6AT6	20	30PL1	60	ECC804	54	GZ32	40	PL81	44	UP41	52
6AU6	20	30PL13	89	EFC80	31	GZ34	48	PL81A	47	UF89	30
6BA8	20	30PL14	85	EFC82	26	KT41	77	PL82	31	UL41	58
6BE6	21	35L6GT	40	ECH35	55	KT61	55	PL83	33	UL84	30
6BJ6	41	35W4	25	ECH42	59	KT66	78	PL84	20	UM84	22
6BW7	52	35Z4D6T	25	ECH81	29	LN319	49	PL600	63	UY41	39
6FL4	40	50C/D6G	68	ECH83	40	LN329	72	PL504	63	UY85	25
6F23	68	AC/VP2	77	ECH84	36	LN339	63	PM84	33	VP4B	77
6F25	53	B349	65	ECL80	35	N78	87	PX25	95	W77	43
6J7G	48	B729	62	ECL82	31	P61	40	PY32	52	Z77	22
6K70	12	CC135	67	ECL86	35	PARC80	34	PY33	52	Transistors	
6K8G	17	CY31	20	EF41	57	PC88	47	PY81	25	AC107	17
6Q7G	35	DAF91	22	EF41	57	PC88	47	PY82	25	AC127	18
6SN7GT	30	DAF96	36	EF80	32	PC96	42	PY83	26	AD149	27
6V6G	28	DF91	16	EF85	28	PC97	36	PY88	33	AF115	20
6V8GT	28	DF96	36	EF86	30	PC900	29	PY800	34	AF116	20
6X4	23	DH77	20	EF89	26	PC84	29	PY801	34	AF117	20
6X5GT	28	DK32	33	EF91	13	PC85	23	R19	30	AF125	17
10P13	58	DK91	28	EF92	27	PC88	38	R20	56	AF127	17
12A7H	2-95	DK92	50	EF98	46	PC89	48	U26	64	OC24	12
12AT8	17	DK96	45	EF183	28	PC189	48	U26	56	OC44	12
12AU7	20	DL35	40	EF184	31	PC805	56	U47	64	OC45	12
12AX7	22	DL92	28	EH90	34	PCF80	29	U49	56	OC71	12
19B6G	80	DL94	47	EL33	55	PCF82	33	U52	31	OC72	12
20P2	67	DL96	38	EL34	45	PCF86	48	U78	24	OC75	12
20P3	75	DY86	24	EL41	54	PCF80	58	U91	59	OC81	12
25L6GT	19	DY87	24	EL80	23	PCF801	58	U183	42	OC81D	12
26U4GT	67	DY802	33	EL95	33	PCF802	40	U261	84	OC82	12
30C1	28	EABC80	32	EL500	62	PCF805	58	U301	38	OC82D	12
						PCF806	56	U329	66	OC170	23

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per. valve extra)
Any parcel insured against damage in transit 3p extra.


MW/LW TRANSISTOR RADIO



Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as a set for more than £17. Coverage 192-555m-1070-1870m. 9 volt 6 transistor superhet using 3 AF117 in RF and IF stages powered by a two stage AF amplifier using 3 x AC128. Output approx. 500mW. Also works off car-aerial. Ply case, rexine covered. Requires PPT battery, price 221p extra. 3 1/2in. high-quality speaker. Price 28 plus 40p P. & P. Size 8 1/2" x 6" x 3".

STEREO AMPLIFIER Type SHV—2 x 3 watts

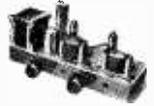Fully built. Separate vol., base and treble controls each channel; 12 x 4 1/2 x 6in high. RECT. ECC83, 2 x ECL86 valves. G.P. trans. for 3-ohm speakers. Double wound mains trans. Suitable for crystal, ceramic cartridge, tuner, etc. 200-250V a.c. mains. 28 (50p) P. & P.



I.C. MODULE 40p. (10p. post). Length 2 1/2" over bracket, x 1 1/2" over tags. With instr. diagram to build stabilised power supply, motor speed control, door buzzer, current meter, windspeed wiper speed control, saw-tooth gen., variable timer, pulse gen. Width of module 2".

VHF/FM Tuner for 88-102 MHz. Self-powered for 200-250vac. Valves ECC85, EF89, 6BW7, ECC82, 2 diodes, metal rect. Chassis 8" x 6" x 8 1/2". German front end. Price 28 (40p post).

Kit and wiring instrs. for 12V windscreen wiper speed control; metal box 3 1/2" x 3 1/2" x 1 1/2" with fixing strap, relay and all compnts. £1.50 (post 20p).

STEREO JUNCTION BOX. Price £1 (16p post) Fitted DIN speaker sockets and fixing strap. Permits operation for stereo headphones or speakers from speaker terminals or sockets on amplifiers not fitted with headphone socket. Size 3 1/2" x 3 1/2" x 1 1/2".

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240. CLOSED WEDNESDAY. S.A.E. for enquiries please.

INDEX TO ADVERTISERS

A. H. Supplies	476	F.E.T. King	558	Oakes, J. I.	466
Amateur Radio Shop	556	Felstead Electronics	530	Padgetts Radio Store	474
Antex Ltd.	481	Field Electric Ltd.	558	Partridge Electronics Ltd.	546
Apex Aerials	555	Galleon Trading	556	Pembroke College	550
Arrow Electronics Ltd.	472	Gladstone Radio	559	Powertran Electronics	508
Attwood, V.	556	Global Audio Discount Warehouse	482	R.D.I.	554
Audio Supplies Ltd.	467	Government Communication Headquarters	555	Radio Component Specialists	500
Baines, R.	555	Greenwell Electronics	557	Radio Exchange Co.	477
Baker Reproducers	476	H. Electronics	557	Radio & T.V. Components (Accon) Ltd.	470, 471
Bell's Television	556	HAC Shortwave Products	468	Radio Society of Great Britain	526
Bentley Acoustic Corporation Ltd.	538	Hadley, C.	544	Radionic Products Ltd.	468
Bernard, Gerald	557	Harverson Surplus Co. Ltd.	545	Readers Radio	559
B.I.E.T.	504, cov iii	Heath (Gloucester) Ltd.	507	Riversdale Electronics	508
Bib Sales	475	Helme, P. F. & A. R. Ltd.	554	ROC Electronics Ltd.	525
Bi-Pak Semiconductors	483, 4, 5	Henry's Radio Ltd.	473, 547, cov iv	Robin Hood (Nottn) Ltd.	554
Boffin Projects	554	Home Radio (Components) Ltd.	469	RSC Hi-Fi Centres Ltd.	465, cov ii
British National Radio & Electronic School	486, 546	I.C.S.	499, 523, 555	RSL Components	558
Broadway Electronics	526	Imperial Trading	555	R.S.T. Valve Mail Order Co.	550
Bull, J. (Electrical) Ltd.	549	Ivoryet Ltd.	496	Salop Electronics	554
Bush & Meissner	468	Jef Electronics	557	Saxon Entertainments	496
C.B.M. Electronic Components Ltd.	556	Jermyn Industries	472	Scientific & Technical	508
C.T. Electronics	557	Johns Radio	556	Selray Book Co. Ltd.	555
Carrana, C.	556	Johnsons (Radio) Ltd.	557 & 558	Sinclair Radionics Ltd.	542, 3
Colomor (Electronics) Ltd.	530	Kensington Supplies	558	Shopertunities Ltd.	503
Component Factors	558	Keytronics	480	Smith, G. W. & Co. (Radio) Ltd.	551, 2, 5
Comet High Fidelity Discount Warehouses	478, 9	King, J. M.	554	Sound Supplies Ltd.	557
Concord Electronics Ltd.	480	Knopp, J. F. D.	554	Southern Audio Services	504
D.E.W. Ltd.	554	Lasky's Radio Ltd.	529	Speaker Selection	538
Daber Electronic Products	480	Lewis Radio	530	Suprlectronics	474
DEB Chemicals (Swarfega)	476	Linavale Radio Ltd.	546	Swanley Electronics	548
Discosound	537	Lindair (Electro-tech) Ltd.	534	Teleradio Hi-Fi	558
Douglas Electronics Industries Ltd.	534	Linear Products Ltd.	474	Thacker, A. H.	548
Dudley, J. & Co. Ltd.	466	London Computer Operators Training Centre	555	Thornbury Trade Disposals	548
Duke & Co. (London) Ltd.	504	London Electronic College	555	Tidman Mail Order	558
Eagle International	495	Magtor Ltd.	468	Trade Aids	534
Electronics, H.M.	554	Marktyme	544	Trampus Electronix	557
Electrospares	550	Marshall, A. & Son	541	W.E.C. Ltd.	554
Electrovalve	533	Morse	558	Web Europa	496
Elvins Electronics Musical Instruments	466	Multicore Solders Ltd.	538	West London Direct Supplies	480
Expo (Drills) Ltd.	476	NIP Electronics	557	Wilmslow Audio	534, 548
Express Mail Order	526	National Amateur Radio & Electronics Exhibition	482	Wilsc Electronics Ltd.	504
				York Electronics	544
				Yukan Self Spray	558
				Z & I Aero Services	560

Head Office and Warehouse
 44A WESTBOURNE GROVE
 LONDON W2
 Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
 When sending cash with order, please include 12½p in £ for postage and handling
 MINIMUM CHARGE 15p. No C.O.D. orders accepted
 Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop
 85 TOTTENHAM COURT ROAD
 LONDON W1
 Tel: 580 8403
 Open all day Saturday

OA2	0.40	6AR5	0.55	6F1	0.75	7Y4	0.75
OA3	0.48	6AR6	0.55	6F5	0.75	9BW6	0.70
OB2	0.40	6AR11	1.25	6FG0	0.45	10C2	0.80
OB3	0.70	6AR5	0.50	6F11	0.50	10D1	0.85
OC3	0.40	6AR7G	0.85	6F13	0.50	10D2	0.55
OD3	0.40	6AT7	0.38	6F14	0.70	10F1	0.75
1B3GT	0.45	6AU6	0.50	6F15	0.65	10F9	0.55
1L4	0.25	6AV8	0.40	6F18	0.50	10F18	0.80
1R4	0.50	6AW8A	0.55	6P23	0.90	10L1	0.60
1R5	0.45	6BA6	0.28	6P24	0.80	10LD11	0.70
1R4	0.30	6BE6	0.32	6P25	1.00	10P13	0.75
1R5	0.30	6BF6	0.55	6P26	1.35	12AB5	0.70
1T4	0.30	6BH6	0.75	6P28	0.70	12AC1	0.60
1U4	0.40	6B16	0.45	6GK6	0.60	12AD6	0.60
1U5	0.75	6BK7A	0.75	6J4	0.90	12AE6	0.80
1V2	0.55	6BN5	0.43	6J5GT	0.40	12AL5	0.55
1X2B	0.55	6BN6	0.60	6J6	0.30	12AQ5	0.50
2A3	0.50	6BQ6	0.25	6J7	0.45	12AT6	0.40
2CW4	0.75	6BR8	0.75	6KGGT	0.75	12AT7	0.40
2D21	0.40	6B7	0.50	6KZ	0.43	12UG	0.45
3A4	0.45	6BW6	0.90	6K8G	0.45	12AV7	0.33
3B1	3.50	6BX6	0.25	6L6GT	0.55	12AV7	0.70
3S4	0.40	6BZ6	0.45	6L7	0.45	12AX7	0.33
5R4QY	0.75	6C4	0.35	6L18	0.50	12AY7	0.75
5U4G	0.40	6CGT	0.55	6LD20	0.50	12AT7	0.40
5Y3GT	0.50	6CDB6A	0.40	6ND7G	0.40	12BA6	0.45
5Z3	0.75	6C6	1.80	6P27	0.50	12BA7	0.50
5Z4G	0.45	6C7G	0.60	6P7	0.50	12BE6	0.50
6J30L2	0.90	6C1H6	0.80	6P8T	0.45	12BH7	0.50
6AB4	0.45	6CL6	0.60	6R8K	0.50	12KX1	1.00
6AP4A	0.60	6CL6	0.90	6SL7G	0.45	12K7G	0.50
6AG5	0.25	6C4W4	0.50	6SOTG	0.45	12QGT0.45	0.55
6AG7	0.45	6CY5	0.50	6SQT	0.50	12SR7	0.50
6AH6	0.80	6C7	0.75	6SR7	0.50	20D1	0.60
6AJ8	0.30	6D3	0.55	6T8	0.38	20L1	1.10
6AK5	0.40	6D6	0.80	6U4GT	0.70	20P1	0.50
6AK6	0.60	6DK6	0.90	6U5G	0.75	35W4	0.40
6AL3	0.43	6DQ8	0.75	6T8A	0.45	35Z3	0.75
6AL5	0.22	6D84	0.25	6V6GT	0.45	35Z4G	0.40
6AM5	0.40	6EA8	0.65	6X4	0.40	35Z6GT	0.70
6AM6	0.37	6EH7	0.30	6XGT	0.45	50A5	0.80
6AQ6	0.40	6EJ7	0.35	6X8	0.85	50B5	0.70
6AQ6	0.72	6EW6	0.70	6Y6G	0.80	50C5	0.80
				6Y6G	0.80	30A6	0.50

First Quality Fully Guaranteed



ELECTRONIC VALVES

30AE3	0.40	50EH5	0.85	DK96	0.60	ECC84	0.80
30C1	0.80	50L6GT	0.60	DL96	0.55	ECC85	0.40
30C15	1.00	50A2	0.55	DM70	0.60	ECC88	0.40
30C17	1.10	50AG	2.40	DM160	0.65	ECC89	0.50
30C18	0.50	50AV	2.50	DY51	0.55	ECC91	0.30
30F5	1.00	50C1	0.75	DY86	0.35	EL222	1.40
30FL1	0.80	50C2	0.40	DY87	0.36	ECC807	1.00
30FL12	1.10	50C3	0.80	DY802	0.37	ECF80	0.35
30FL14	0.90	50C4	0.40	E88CC	0.70	ECF82	0.35
30L1	0.40	50C5	0.85	E180F	1.00	ECF84	0.65
30L15	0.95	50C6	0.70	E180F	2.90	ECF81	0.50
30L17	0.95	50C7	0.60	E180F	2.90	ECF81	0.50
30P12	1.10	50C8	0.70	E180F	2.90	ECF81	0.50
30P19	0.95	50C9	0.55	E180F	2.90	ECF81	0.50
30P21	0.95	50C10	0.55	E180F	2.90	ECF81	0.50
30P22	1.10	50C11	0.55	E180F	2.90	ECF81	0.50
30P23	1.10	50C12	0.55	E180F	2.90	ECF81	0.50
30P24	1.10	50C13	0.55	E180F	2.90	ECF81	0.50
30P100	1.10	50C89	0.55	E180F	2.90	ECF81	0.50

EP95	0.40	GZ32	0.50	PL33	0.40	U403	0.70
EP97	0.85	GZ33	0.75	PL36	0.55	U404	0.70
EP98	0.75	GZ34	0.60	PL37	0.50	U405	0.80
EP99	0.55	HABC800.55		PL38	0.45	UABC80	
EF184	0.35	HK90	0.50	PL83	0.45		0.40
EF804	1.25	KT66	2.35	PL84	0.40	UAF41	0.70
EK90	0.32	KT88	2.25	PL302	0.95	UAF42	0.60
EL34	0.50	N78	1.80	PL304	0.75	UB41	0.65
EL36	0.50	PABC800.40		PL508	0.90	UB42	0.65
EL37	1.70	PC86	0.60	PL509	1.10	UBC81	0.45
EL41	0.75	PC88	0.60	PL801	1.00	UP80	0.40
EL41	0.55	PC92	0.50	PL802	0.95	UP89	0.40
EL83	0.50	PC97	0.50	PM64	0.60	UBL1	0.70
EL84	0.25	PC90	0.48	PY31	0.35	UBL2	0.70
EL85	0.45	PCC84	0.40	PY33	0.63	UC92	0.45
EL86	0.40	PCC85	0				

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you


"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

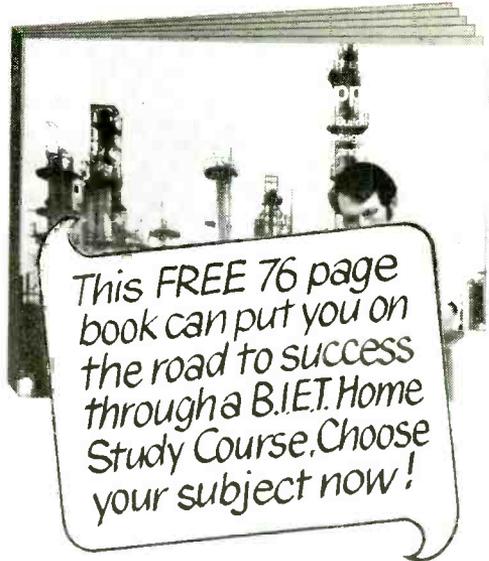These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept, B37, Aldermaston Court, Reading RG7 4PF



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

- | | | |
|--|---|--|
| <p>MECHANICAL
A.M.S.E. (Mech.)
Boiler Inspection & Operation
C & G Eng. Crafts
C & G Fabrication
Diesel Eng.
Eng. Inspection
Eng. Metallurgy
Inst. Eng. & Tech.
Inst. Motor Ind.
Maintenance Eng.
Mechanical Eng.
Sheet Metal Work
Welding</p> | <p>Man. Prod.—cont.
Salesmanship
Storekeeping
Work Study
Works
Management
DRAUGHTSMANSHIP
A.M.I.E.D.
Design of Elec. Machines
Die & Press Tool Design
Electrical
Draughtsmanship
Gen. Draughtsmanship
Jig & Tool Design
Technical Drawing</p> | <p>Constructional-cont.
Building Drawing
Building Foreman
Carpentry & Join.
Civil & Municipal
Engineering
Constructional Engineering
Construction
Surveyors
Institute
Clerk of Works
Council Eng.
Geology
Health Eng.
Heat & Vent.
Hydraulics
Inst. of Builders
Inst. Clerk of Works
Inst. Works & Highway Supers.
Painting & Dec.
Public Hygiene
Road Engineering
Structural Eng.
Surveying</p> |
| <p>ELECTRICAL & ELECTRONIC
A.M.S.E. (Elec.)
C & G Elec. Eng.
C & G Elec. Inst.
C & G Elec. Tech.
Computer Elect.
Elec. Maths
Elec. Science
Electronic Eng.
Electrical Eng.
Install. & Wiring
Meters
& Measuring Instruments</p> | <p>RADIO & TELE-COMMUNICATIONS
Colour TV
C & G Radio/TV/Electronics
C & G Telecomm. Tech.
Prac. Radio & Elec. (with kit)
Radio Amateurs Exam.
Radio Servicing & Repairs
Radio & TV Eng.
Transistor Course
TV Main. & Serv.</p> | <p>GENERAL
Agricultural Eng.
Council of Eng. Inst.
Farm Science
General Education
Gen. Plastics
Pract. Maths
Pract. Slide Rule
Pure & Applied Maths
Refrigeration
Rubber Technology
Sales Engineers
Tech. Report Writing
Timber Trade
University Ent.</p> |
| <p>MANAGEMENT & PRODUCTION
Automatic Control
Computer Prog.
Electronic Data Processing
Estimating
Foremanship
Inst. Cost & Works
Accountants
Inst. Marketing
Management
Metrication
Motor Trade Man.
Network Planning
Numerical Control
Operational Research
Personnel Man.
Planning Eng.
Production Eng.
Quality Control</p> | <p>AUTO & AERO
Aero Eng.
A.M.I.M.I.
A.R.B. Cert.
Auto Engineering
Auto Repair
C & G Auto. Eng.
Garage
Management
MAA/IMI Diploma
Motor Vehicle Mechanics
CONSTRUCTIONAL
A.M.S.E. (Civil)
Architecture
Building</p> | <p>G.C.E.
58 'O' & 'A' LEVELS SUBJECTS
Over 10,000 group passes</p> |
- Coaching for many major exams. including HNC, ONC, C & G, etc.*

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. B37, Aldermaston Court, Reading RG7 4PF

B37



NAME _____
Block Capitals Please
ADDRESS _____

SUBJECT OF INTEREST _____

AGE _____

Accredited by the Council for the Accreditation of Correspondence Colleges.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

U.K.'s LARGEST ELECTRONICS CENTRES!

HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381/8382
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402-5854/4736
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
 303 BARGAIN STORE SPECIAL OFFERS 01-723 1008 All Mail to: 303, Edgware Rd., London, W.2.

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

BUILD THE TEXAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ FREE TEAK CABINET with complete kits!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners, special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.
HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).



(As featured in "Practical Wireless" May to August 1972)

SPECIAL KIT PRICE
£28-50 P & P 45p

★ SLIM DESIGN WITH SILVER TRIM
 Overall chassis size 14" x 6" x 2" high

COMPLETE WITH FREE TEAK CABINET
 Designer approved kits only available from Henry's

RECORD DECKS

CHASSIS (Post 50p)	
SP25/3/10 75 HT70	£15 00
MP60	£10 40
MP610	£14 15
AP76	£18 95
GL72	£22 25
WITH PLINTH/COVER (Post 70p)	
MP60	£17 20
TD150AB HT70	£21 60
HL(GL75) PLI2AC	£41 45
	£35 25
MP610/20 35 BD2	£32 25
CART/PLINTH/COVER (Post 70p)	
(HL) AP76/G800/PC	£29 95
(HL) SP25-3/G800H/PC	£18 95
HT70/G800/PC	£27 00
(HL) 2025TC/9TAHCD/PC	£13 50
MP60/SCSMD/PC	£17 25
(HL) GL75/G800E/PC	£44 15
(HL) GL72/800/PC	£35 50

ULTRASONIC TRANSDUCERS

Operate at 40Kc up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.
 £5 90 per pair. Post 10p

MARRIOTT TAPE HEADS 4 TRACK MONO OR 2 TRACK STEREO

'17' High Impedance	£2 00
'18' Med. Impedance	£2 00
'36' Med.-Low Imp	£3 50
Erase Heads for above 75p	
'63' 2 track mono—Hi Imp.	£1 75
'43' Erase Head for above 75p	

POWER INTEGRATED CIRCUITS

Plessey SL403D—3 watt with 8-page data, layouts and circuits £1 50. P.C. Board 60p. Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1 80. TH9013P—20 watt Power Amp Module £4 57. TH9014P—IC Preamp £1 50. Data/Circuits for above No. 42 10p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
 XN3, XN13, GNL6 0-9 side view with data, 85p.
 GNP7, GNP8 0-9 side view with decimal points and data, 95p.
 3015F 7 seg £2 each. £7 per 4 with data.
 12 and 24 hour clock circuits for above Ref. No. 31 15p.

Miniature Amplifier

5 transistor. 300mW o/p. Fitted volume and sensitivity control, 9 volt operated. £1 75 each P/P 15p.

Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 500K. 1 meg, Log and Lin. 45p each, 10K, 25K, 50K, 100K, Log and Lin ganged. 75p each.

Hi-Fi & Tape Equipment

Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 months Guarantee. Write or call for FREE 16 page lists (Ref. 16/17)

Transistors - IC's - SCR'S - Rectifiers - Triacs, etc. NEW FREE LISTS Ref. No. 36 on request.


LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2 20. Post 22p.
TYPE 150 TC Twin cone version £2 75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms £3 85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7 70. Post 28p.



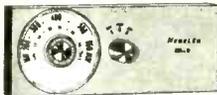POLISHED CABINETS 150, 150TC 450 £4 60. Post 30p.



ML3 MW/LW TUNER TO BUILD

Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/4". TOTAL COST TO BUILD £4 85. Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7 98. p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

TEST EQUIPMENT

SE250B	Pocket Pencil Signal Injector	£1 90
SE500	Pocket Pencil Signal Tracer	£1 50
TE15	Grid Dip Meter 440 KHz-280 MHz	£13 45
500	30 K/V Multimeter	£9 25
	With leather case	£10 50
200H	20K/V Multimeter	£4 20
	With case	£4 95
AF105	50K/V Multimeter	£8 50
	With case	£9 50
U4341	AC/DC Multimeter with transistor tester with steel case	£10 50
TE20D	RF Generator 120KHz-500MHz	£15 95
	Carr.	35p
TE22D	Audio Generator 20Hz-200KHz	£17 50
	Carr.	35p
T03	3" Scope 1 1/2Hz-1 1/2MHz	£39 00
	Carr.	50p
CI-5	3" Pulse Scope 10Hz-10MHz	£39 00
	Carr.	50p
TE65	Valve Voltmeter 28 ranges	£17 50
	Carr.	40p



PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.



DJ30L	3 Channel sound to light unit, 3kw	£28 50
DJ40L	3 Channel Mic (Built in) to light, 3kw	£37 50
DJ70S	70 watt Disco amp/mixer	£49 75
DISCOAMP	100 watt Disco amp/mixer	£67 50
DJ105S	30 watt Disco amp/mixer	£31 00
	Anti-Feedback Quality Mic.	£11 50
SDL	12 1/2 watt 8 ohm Full range speaker	£12 95
DECKS.	Use MP60 or SP25/3 see above	
	Matching cartridge SC5M	£2 62
	FIBRE OPTICS, LIGHTING EFFECTS, PROJECTORS, SPOTS, DIMMERS, MIXERS. Everything for PA—Disco—Lighting. FREE Stock List Ref. No. 18.	

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO.
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6 97, p.p. 20p. Decoder Kit £5 97.
 Tuning meter unit £1 75
 Mains unit (optional) Model PS900 £2 47. Post 20p
 Mains unit for Tuner and Decoder PS1200 £2 62. Post 20p



SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!


Z30	£3 57	Z50	£4 37
STEREO 60	PZ5	£3 97	
	£7 97	PZ8	£4 77



PZ6 £6 37;
 Transformer for PZ8 £2 95
 Active Filter Unit £4 45
 Stereo FM Tuner £16 95
 IC12 £1 80; Q16's £15 pr.
 Post etc. 20p per item

PACKAGE DEALS

2xZ30, Stereo 60, PZ5	£15 95
2xZ30, Stereo 60, PZ6	£18 00
2xZ50, Stereo 60, PZ8	£20 25
Transformer for PZ8	£2 95
PROJECT 605 KIT	£19 95

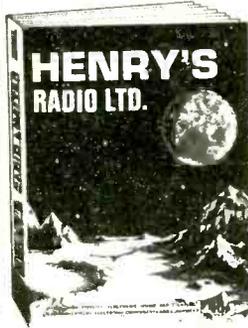

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

Post Paid (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see below.

MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S
 All the parts you need plus Data and Circuits — Get a Catalogue — it's all in there!

Prices subject to change without notice E. & O.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H