

# PRACTICAL WIRELESS

APRIL  
1973

20p

p  
w

**TRICOLOUR**  
Mood Lighting



System

also

**I. C. POWER AMPLIFIER  
DARKROOM EXPOSURE METER**

# PACKAGE PRICE R.S.C. STEREO PACKAGE OFFERS

FOR ILLUSTRATED UNITS  
**ONLY £39-59**

Carr. £1-00  
Or deposit £8-95  
and 9 monthly  
payments £4-22  
(Total £44-92)




GARRARD 2025

R.S.C. A55  
LOUDSPEAKERS



LINEAR 505 AMP

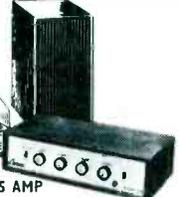

SEND S.A.E. FOR  
FREE COLOUR  
BROCHURE

Individual Rec. Retail Prices  
LINEAR 505 5 + 5 Watt Amplifier £17-50  
GARRARD 2025 Autochanger + K840A Cartridge £13-58  
Teak Veneer Plinth with Transparent Plastic Cover £8-10  
Pair A55 LOUDSPEAKERS (Inc 8" x 6" 10,000 Gauss) £11-50  
**TOTAL £48-68**

**SAVE £31-60**



MONARCH  
SPEAKERS

GOLDRING  
GL72

'SUPER 30' AMP

# HIGH FIDELITY UNITS

PACKAGE PRICE **£99-95** Carr. £1-75

FOR ILLUSTRATED UNITS

Or deposit £15-00 and  
12 monthly payments £8-00  
(Total £111-00)

Individual Rec. Retail Prices:  
GOLDRING GL72 Transcription Turntable + P.U. £31-89  
GOLDRING G800 Magnetic Cartridge £12-81  
DE-LUXE PLINTH with Roll-over Cover £10-50  
Pair R.S.C. MONARCH LOUDSPEAKERS £38-70  
R.S.C. SUPER 30 Mk III AMPLIFIER £38-75  
**TOTAL £181-55**

## FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite core coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency **£9-95** post free  
Response 25 Hz-2 KHz.  
Impedance 8-15 ohms.  
Or Dep. £2-25 & 9 monthly payments. £1 (Tot. £11-25)

## HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or fitted acoustic damping. Ported where appropriate. Credit terms available.  
**DORCHESTER** (Illustrated) Size 16x11x9in. approx. Range 46-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13x8in. **£9-45** Carr. 40p.  
Dual Cone speaker. Imp. 3 or 15 ohms.  
**MONARCH** Size 19x13x9in. approx. Rating 10 watts. Inc. 13x8in. speaker with highly flexible P.V.C. cone surround, long throw voice coil and 10,000 line magnet. High flux pressure tweeter. Handsome design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output.  
See 'package offers' for illustration. Carr. 50p **£19-35**

## RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs.  
**COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT AND COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £11-50** Carr. 40p  
OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £14-99 or dep. £2-20 and 9 monthly payments £1-70 (Total £17-50)



## HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.  
**JE8** Size 16 x 11 x 9in. **SE8** For optimum performance with any 8in. Hi-Fi spkr. Size 22 x 15 x 9in. **£6-47**  
8in. Hi-Fi speaker. **£5-35**  
**SE10** For outstanding results with 10in. Hi-Fi spkr. Size 24 x 15 x 10in. P.t.d. **£6-74**  
**SE12** For excellent performance with 12in. Hi-Fi speaker and tweeter Size 25 x 16 x 10 1/2in. **£7-87**

## AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plastised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Exceptional performance at low cost.  
HF808T 8" 10W £2-88 HF120D 12" 15W £4-99  
HF102D 10" 10W £3-40 HF128 12" 15W £5-76  
HF120 12" 15W £4-60 HF128D 12" 15W £6-86



## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range **£5-95** Carr. 30p  
ensure surprisingly realistic reproduction. **£6-95** Carr. 40p.  
OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£6-95** Carr. 35p



## FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ohm.  
PLEASE STATE IMPEDANCE WHEN ORDERING **£3-85**  
MODEL 803T 8" 15w. with parasitic Tweeter. **£4-95**  
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15.



## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2db. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 9 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7-75** Carr. 40p.  
OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE £10-95



NOW IN STOCK!

## FANE 'CRESCENDO' SUPER EFFICIENT GROUP/DISCO LOUDSPEAKERS

Send S.A.E. for leaflet on this range of extraordinarily efficient units including the very latest BASS CRESCENDO '12' 100 Watts. FULL DISCOUNT to Genuine Trade Customers. CARR. FREE.

## R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

**MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.**  
250v., 60mA, 6.3v. 2a ..... 99p  
250-0-250v., 60mA 6.3v 2a ..... £1-05

**FULLY SHROUDED UPRIGHT MOUNTING**  
250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-40  
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20  
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20  
300-0-300v. 150mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-20  
For Mullard 510 Amplifier. £2-85  
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20  
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-85  
425-0-425v. 200mA, 6.3v. 4a., c.t., 5v. 3a. £4-95  
425-0-425v. 200mA, 6.3v. 4a., 6.3v. 3a., 5v. 3a. £5-10  
450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a. £5-50

**TOP SHROUDED DROP-THRO' TYPE**  
250-0-250v. 70mA, 6.3v. 2a. 0-5-6.3v. 2a. £1-55  
250-0-250v. 100mA, 6.3v. 3a. 0-5-6.3v. 2a. £1-55  
250-0-250v. 100mA, 6.3v. 2a., 6.3v. 1a. £1-80  
350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-85  
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20  
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20  
300-0-300v. 150mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-20  
Suitable for Mullard 510 Amplifier. £2-60  
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20  
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-60

**FILAMENT or TRANSISTOR POWER PAOK**  
Types 6.3v. 1.5a. 49p; 6.3v. 2a. 54p; 6.3v. 3a. 76p;  
6.3v. 5a. £1.00; 12v. 1a. 55p; 12v. 3a. or 24v. 1.5a. £1.35; 0-9-18v 1 1/2a. £1.10; 0-12-25-42v 2a£1.78.

**FULLY GUARANTEED.** Impregnated and interleaved where necessary. Primaries 200-250v. 60c/a. Secondaries

**CHARGER TRANSFORMERS** 0-9-15v. 1a. 99p;  
2 1/2a. £1-10; 3a. £1-25; 6a. £1-45; 6a. £1-65; 8a. £2-00

**AUTO (Step Up/step DOWN) TRANSFORMERS**  
0-110/120v. 200-230-250v. 50-80 watts £1-10,  
150 watts, £1-90 250 watts £2-75; 500 watts £5-75

**OUTPUT TRANSFORMERS**  
Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p  
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 85p  
Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω £1-37  
Push-Pull EL84 to 3 or 15 Ω 10-12 watts £1-35  
Push-Pull Ultra Linear for Mullard 510, etc. £2-20  
Push-Pull 15-18 watts, sectionally wound £1-5, KT66, etc. £1-4 or 15 Ω £1-99  
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3-30

**SELENIUM RECTIFIERS**  
F.W. (Bridge)  
All 6/12v. D.C. output. Max. A.C. input 18v.  
1a, 25p. 2a, 35p.  
3a, 50p. 4a, 65p.  
6a, 80p.

**SMOOTHING CHOKES**  
150mA, 7-10H, 250 Ω 70p; 100mA, 10H, 200 Ω 80p; 100mA, 10H, 350 Ω 80p; 50p; 60mA, 10H, 400 Ω 25p.

## R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

**BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET**  
Only high grade components by leading manufacturers

- \* Push Button Selector Switching
- \* Jack Socket for Headphones
- \* Neon Indicator
- \* Satin Silver Finish Metal Fascia
- \* Solid State Circuitry
- \* Twenty Silicon Transistors
- \* Four Diodes, Four Rectifiers

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 dB.

**COMPLETE KIT (less cabinet). Carr. 65p. Cabinet if req. £5 extra. £25**

**FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £3-99 (Total £42-91). £38-75**

Send S.A.E. for full descriptive leaflet.  
**R.S.C. STEREO FM TUNER.**  
Visually matches Super 30 Mk. III **£44-95**




## 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx. **COMPLETE KIT**  
★ Response 30-20,000 c.p.s. Impedance 15 ohms **£23**  
★ Performance comparable with units costing considerably more Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet.  
(2) 3-way quarter section series cross-over system.  
(3) 8 x 5in. high flux middle range speaker.  
(4) High efficiency tweeter. (5) Appropriate quality acoustic damping material. (6) Handsome Teak veneered cabinet.  
(7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-47 (Total £26-83).



# RSC GROUP/DISCO UNITS

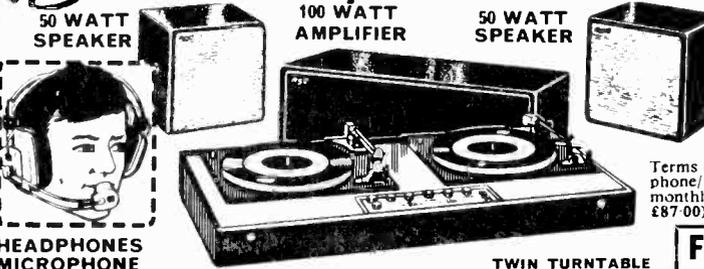

HEADPHONES  
MICROPHONE

TWIN TURNTABLE  
WITH PRE-AMP

## R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS  
All types 15 Ohms covered in Rexine and Vynair  
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN  
TYPE C312 30-40 WATTS Fitted two exceptionally efficient, low feedback bowl chaw-acteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £3 and 9 monthly payments £2.22 (Total £22.98) Carr. 50p.  
TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 55 x 16 x 10". Acoustically filled and pressurised. Terms: Dep. £11 and 12 mthly. pmts. £5.18 (Total £73.16). Carr. £1

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output, Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EP86 EP86, ECC83, EL34, EL34, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and pick-up etc. for mixing purposes, 200-250v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Twin-handled perforated cover £1.90. 12 MONTHS' GUARANTEE. Carr. 65p  
TERMS: Deposit £4 and 9 monthly payments of £2.10 (Total £22.90). Send S.A.E. for leaflet.

## LINEAR T40/60D 50W GROUP/DISCO AMPLIFIER

★ FULL MONITORING FACILITIES  
★ Individual Bass and Treble controls  
★ Twin Jack output sockets for speakers  
★ Input sockets for medium or high impedance Microphones or Guitar P.U.s and Crystal or Ceramic Gram. P.U.s  
★ Frequency response 30-20,000 Hz.  
★ Output overload protection plus double fusing FRONT PANEL (Jack Inputs)  
Gram, Gram, Microphone/Guitar P.U.; plus monitoring socket.  
CONTROLS Vol. (1) (2) (3) and (4), Bass, Treble, Master Vol., Monitor Selection Switch Gram (1) or (2), Mains Switch



£49-50 Carr. free  
Or Deposit £7-50 and 9 monthly payments £5-37 (Total £55-83)  
Simulated black rexine, plastic bonded metal case.  
ALSO STOCKED LINEAR T80/100D £69-75

## FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled Inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating.  
Or deposit £7-25 & 9 monthly payments £3-55. Total £39-20.



£34-95 Carr. 75p


## RSC PHANTOM '50'

Combined 50w Amplifier and 12in. Loudspeaker. For Lead Guitar, mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £8-95 and 9 monthly payments £6 (Total £82-95). Carr. £1-50  
ONLY £55-95


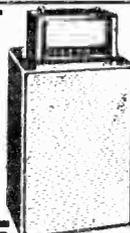
## RSC BASS-REGENT 50 WATT AMPLIFIER


A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocals, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.  
★ Two extra heavy duty 12in. 50w Loudspeakers.  
★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £15 & 9 monthly payments of £8-25. (Total £71-25). Carr. £2



£65

## RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group

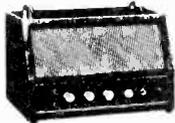

A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £2-40 and 9 monthly payments of £2-45 (Total £26-45). Carr. 65p  
£23-50

NOW FOUR NEW BRANCHES  
NOTTINGHAM 19/19A MARKET STREET  
SUNDERLAND 5 MARKET SQUARE  
STOCKPORT 8 LITTLE UNDERBANK  
COVENTRY 17 SHELTON SQUARE  
NEW LARGER PREMISES AT HULL,  
DARLINGTON & NEWCASTLE See Addresses



HI-FI CENTRES LTD.  
MAIL ORDERS & EXPORT ENQUIRIES TO:—  
AUDIO HOUSE, HENCONNER LANE, LEEDS, 13. Tel: Pudsey (09735) 77681.  
TERMS C.W.O. or C.O.D. No C.O.D. under £1. POSTAGE 25p EXTRA UNDER £2. 30p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED.  
S.A.E. PLEASE WITH ENQUIRIES.  
SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.  
MAIL ORDERS MUST NOT BE SENT TO SHOPS

## PACKAGE OFFER

Units listed below  
(a) 100w POWER AMPLIFIER  
(b) PAIR OF HI-FI HEAD- PHONES  
(c) MATCHING DYNAMIC MIKE (attached to headphones)  
(d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets  
Size approx. 18" x 18" x 8"  
£72-85  
(a)(b)(c)&(d) Carr. £1-25

Terms on Amps, Speakers and Head- phone/Mike. Deposit £15 and 18 monthly payments of £4-00 (Total £87-00).

## RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 Mk.III turntables and Spindles or Acme Cartridges with diamond stylus. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Rexine covered Cabinet with lid. See illus. on leaf.  
Carr. £1-25  
Or Dep. £18-25 and 9 mthly pmts £6-88 (Total £75-17) or Dep. £15 and 18 mthly payments £3-68 (Total £80-16)

£67-10

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE



'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15 Ω	15" 60 Watt 14,000 gauss 8/15 Ω	12" 50 Watt 13,000 gauss 8/15 Ω
£22-95	£12-90	£10-90
Dep. £6 and 9 mthly payments £2-20 (Total £25-90)	Dep. £3-30 and 9 mthly payments £1-30 (Total £12-60)	Dep. £2 and 9 monthly payments £1-20 (Total £12-80)

PAIR SUITABLE ALL PURPOSES

## FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free  
£6-75 or Dep. £1-25 and 9 mthly payments 75p (Total £8-00)

## GROUP/DISCO EQUIPMENT PACKAGE OFFERS

PACKAGE PRICE	PACKAGE PRICE	PACKAGE PRICE	PACKAGE PRICE
F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 25/2 25W L/SPEAKERS Terms: Deposit £6-50 and 9 monthly payments of £4-82 (Total £50-78)	£34-95	£45	£45
F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit £10 and 9 monthly payments of £6-87 (Total £66-83)	£34-95	£52	£52
F.A.L. PHASE 50 MK.III AMPLIFIER PAIR L12/25 25W L/S in cabinets Terms: Deposit £10 and 9 monthly payments of £6-88 (Total £66-92)	£34-95	£56	£56
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 L/SPEAKERS Terms: Deposit £15-95 and 9 monthly payments of £10-78 (Total £112-52)	£61-95	£99-95	£99-95

## HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH  
L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50  
Or deposit £5-80 and 9 monthly pmts. of £3-70. Total £38-80

L12/20 12" 20-25 WATT	L13 13" x 8" 10 WATT
13,000 lines 15 ohms. Carr. 50p.	10,000 lines 3 or 15 ohms. State impedance required. Carr 40p
£11-95	£5-25

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kites Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

V.A.T!  
PRICES QUOTED—INCREASE FROM APRIL 1st.

R.S.C. Branches operate a 5-day week  
Open all day Saturday

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349  
BLACKPOOL (Agent) O & C Electronics 227 Church Street  
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).  
COVENTRY 17 Shelton Square, The Precinct (Closed Wed.).  
DERBY 26 Osmaston Rd., The Spot (Closed Wed.). Tel. 41361  
DARLINGTON 19 Northgate (Closed Wed) Tel 68043  
EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501  
GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158  
HULL 7 Whitefriargate Tel. 20505  
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420  
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252  
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573  
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629  
MANCHESTER 60A Oldham Street, (Closed Wed.). Tel. 236 2778  
MIDDLESBROUGH 106 Newport Rd. (Closed Wed.).  
NEWCASTLE UPON TYNE Tel. 47096  
24 Newgate Shopping Centre (Closed Wed.). Tel. 21469  
NOTTINGHAM 19/19A Market Street (Closed Thurs.).  
SHEFFIELD 13 Exchange Street (Castle Market) (Eids.) (Closed Thurs.). Tel. 20716  
STOCKPORT 8 Little Underbank. Tel: 480-0777.  
SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

# Would you spend an hour a day to earn more money in Electronics - Television - Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

**ICS** your key to the door of opportunity

Tick or state subject of interest and post to:  
International Correspondence Schools, Dept. 232E,  
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest \_\_\_\_\_

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name \_\_\_\_\_

Address \_\_\_\_\_

Occupation \_\_\_\_\_ Age \_\_\_\_\_

Accredited by the Council for the Accreditation of Correspondence Colleges

## SOUND BARGAINS



**BEST OF ALL WORLDS**

VHF, FM, AM, AFC,  
AIR BAND, PUBLIC  
SERVICE AND  
WEATHER BANDS

**BATTERY CHECK INDICATOR**

**GIANT POWER MULTI WAVEBAND BROADCAST RECEIVER**

WITH 3 IN 1 AC/DC POWER SUPPLY SYSTEM  
TUNING/BATTERY plus BUILT-IN BATTERY BOOSTER

**OUR PRICE £10-50**  
+40p P. & P.

No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHER-BAND. Frequency ranges: MW540-1600 KHz, FM88-108MHz, Airband 108-145 MHz, VHF 145-175MHz, 23 semi-control, 31" telescopic aerial. Runs on mains AC 230/250 volts or off 4 U11 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10" x 6" x 3". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. **HURRY!** Limited quantity Fully guaranteed.

---

**OUR PRICE £28-95**  
+50p P. & P.



**8 WAVEBANDS AND WORLD MAP & TIME ZONE DIAL**

Marine 1.6-4.5Mcs. Short Wave 12-24Mcs. FM/VHF 88-108Mcs. Aircraft 108-135 Mcs. **PUBLIC SERVICE BANDS 135-174Mcs.** Fully guaranteed.


Tune into the world with this amazing world radio. A truly exceptional unit in performance and looks - leatherette with stainless steel trim - looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tune, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 353-1605Kcs. Marine 1.6-4.5Mcs. Short Wave 12-24Mcs. FM/VHF 88-108Mcs. Aircraft 108-135 Mcs. **PUBLIC SERVICE BANDS 135-174Mcs.** Fully guaranteed.

*Note: The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.*

**SONIC SOUND AUDIO LTD.** (Dept. PW11), 372 EDGWARE ROAD, LONDON, W.2. Tel. 01-723 0094. Callers welcome Monday to Saturday 9 a.m. - 6 p.m.
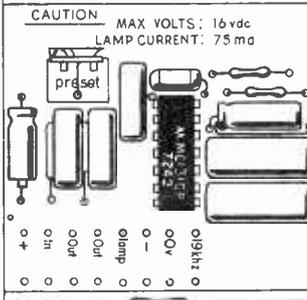
## Stereo radio from your existing tuner.

**CAUTION** MAX VOLTS: 16 vdc  
LAMP CURRENT: 75 ma



A complete set of parts from Jermyn to build a stereo decoder module that will convert your existing mono tuner for stereo reception whilst maintaining a high standard of reproduction.

The distortion is very low (typically 0.3% at 560 mV RMS composite input signal) with 40dB channel separation.

The stereo switching is automatic and there is a light emitting diode which acts as a stereo beacon.

The kit requires no coil and there are no alignment problems.

Fitting: The module requires a 10-16 volt power supply which can normally be tapped off the existing tuner. The signal input is taken off before the de-emphasis circuit which in practice means disconnecting one, or at the most, two capacitors. Any radio engineer will be able to spot these capacitors, but if you're really stuck send the circuit with a SAE to us and one of our engineers will indicate the output point. (This is the full extent of our involvement, no hardware please).

Of course, if you have a modern mono tuner with a multiplex output our module simply plugs in.

The outputs go via a screened twin cable to the tuner inputs of your stereo amplifier.

And the cost? £4.90 for the Kit with 100% tested integrated circuit. Also available assembled and aligned, checked and ready for use at £6.90 (includes 12 month guarantee). Beat that!

To Jermyn Industries  
74 Vestry Estate  
Sevenoaks  
Kent

Please rush me  Kit(s),  made up Stereo decoders.  
I enclose cheque/postal order for £ \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_

Block Capitals Please



# There are 195 other good reasons for buying AMTRON electronic kits

Apart from the five items shown above, there are another 195 kits to choose from in the vast AMTRON range of electronic kits.

A few examples of equipment you can construct from AMTRON kits are:

Power supplies, preamplifiers, amplifiers, L.F. instruments, accessories for musical instruments, amateur and radio control transmitters and receivers, battery chargers, electronic car accessories, psychedelic lighting equipment, measuring instruments, tuners, receivers, I.C. digital equipment.

Only 1st class fully guaranteed components are used —solder is included with every kit.

Prices range from £1.10 to £80 and each kit is sold in protective blister pack containing complete instructions.

*Should you experience any difficulty in obtaining AMTRON Kits please contact us direct.*

PLEASE SEND FOR BROCHURE




TRADE & EDUCATION ENQUIRIES WELCOME

AMTRON U.K. 4 & 7 CASTLE STREET HASTINGS SUSSEX TELEPHONE HASTINGS 2875

TOP QUALITY — LOW COST




AMATEUR RADIO EQUIPMENT

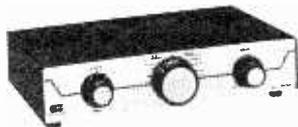
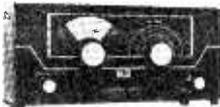
## P.R.40

SOLID STATE  
R.F. PRESELECTOR


The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supercedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1-5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee . . . £8-90 Carriage 30p.


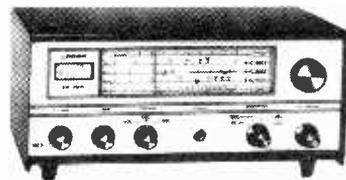
## MULTIBAND-6

SOLID STATE  
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery). £13-20 Carriage 35p. Stamp brings illustrated leaflets.



## CR70A

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built £27-50, Carriage 70p.  
**SEND FOR YOURS TODAY!**

**NOTE:** These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers and are FREE of Purchase Tax. Some portable receivers being advertised as Communication Receivers do not meet these requirements.




ON THE DESIGN STAFF—  
G3SZM G3IRE
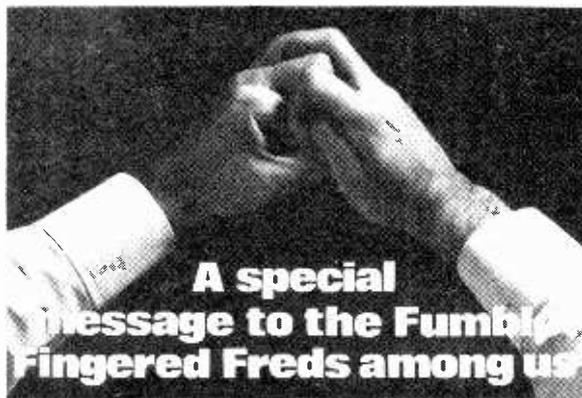
# CODAR

TELECOMMUNICATIONS AND ELECTRONIC  
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS  
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX  
Tel. 090-63-61901 BN15 - 8TZ



## NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself". We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak. Just fit the speaker cloth (supplied) and screw in your speaker.

**HIGH QUALITY  
AT LOW COST**

Send for our free booklet  
"Choosing a Speaker"

**STEPHENSPEAKERS,**  
WILMSLOW AUDIO, Dept. 'PW', Swan  
Works, Bank Square, Wilmslow SK9 1HF

# ELECTROKIT

**SCORPIO CAPACITOR DISCHARGE IGNITION SYSTEM** (P.E. Nov. 1971)

Complete kit with full instruction data £9-50

**"MUSIC MAKER" ORGAN KIT** (P.W. Dec. 1972)  
Kit includes only capacitors, semiconductors, switches, preset and loudspeaker. £2-80 OR

**COMPLETE** kit including above plus resistors, PC board and box £4-40

**TRIFFID RADIO** (P.E. Feb. 1973)

Kit of resistors, Capacitors, Transistors, Diodes, Potentiometer and I.C. £4-95

**LIGHT DIMMER** kit contains all parts including circuit and construction data. Fully suppressed, 480 Watts £2-10

**DRILL SPEED CONTROLLER** (E.E. Aug. 1972)

Complete kit (less MK box, plate and socket) £1-05  
Complete kit including MK box, plate and socket £2-20

P.C. Boards not supplied, unless otherwise stated. We are also able to supply other kits for articles published in *Practical Wireless* and other Electronic magazines. Send for details of other kits available. Please enclose a stamped addressed Envelope.

## ELECTROKIT

12 Lauderdale Road, London, W.9  
Telephone 01 - 286 0011  
MON.-FRI. 9.30-5.30  
THURS. 9.30-6.30

**ZN414 £1.25 POST FREE**  
 The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.  
**I.C. Sockets**  
 Dual-in-line or Zig-Zag (Duni), 14 and 16 pin  
 Our Price 1p per pin

**Slider Pots**

Single	Dual	log	
10K	10 + 10K	or	
25K	25 + 25K	lin	
50K	50 + 50K		knobs
100K	100 + 100K		10p
30p	50p		

**NEW LISTS**  
**LOUDSPEAKERS** No. 4  
**COILS AND INDUCTORS** No. 5  
**TRANSFORMERS** No. 6  
 (postage 5p)

**Diodes & Rectifiers**

AA119 9p	BA156 15p	BY176 £1.50
AA120 9p	BA243 56p	BY182 £1.50
AA129 9p	OA47 10p	BY250 23p
BA102 25p	OA79 9p	IN4001 6p
BA115 17p	OA90 7p	IN4002 7p
BA130 10p	OA91 7p	IN4003 8p
BA145 20p	OA200 10p	IN4004 8p
BA148 20p	BY100 15p	IN4005 10p
BA154 13p	BY126 15p	IN4006 12p
BA155 14p	BY127 15p	IN4007 15p

82YM ZENER SERIES 10p each

**FM TUNER**  
 chassis fully transistorised & v.o. operation.  
**OUR PRICE £8.25**  
 Matching stereo decoder £4.97  
 Ask for model list No. 11.

**VDR's & Thermistors**

A15B 75p	GL23 £1.00	VA1005 15p
C21 15p	R53 £1.32	VA1026 13p
C24 13p	R54 £1.46	VA1033 13p
C213A 13p		VA1040 10p
E298 ED/A258 10p		VA1053 10p
E298 ZZ/06 10p		VA1055S 10p
GL16 £1		VA1034 10p

**Resistors**  
 1/2 watt 5% Carbon Film - low noise  
 Hi-Stabs  
 All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.  
 1 W 10% Carbon Composition 3p each  
 2 W 10% Carbon Composition 6p each  
 2 1/2 W 5% Wire wound 9p each  
 5 W Wire wound 9p each  
 10 W Wire wound 10p each  
 plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.

**SGS**  
**EA1000**  
 3 Watt Audio Amplifier  
 Our Price inc. handbook £2.49

10 - less 15%  
 25 - less 25%  
 100 - less 33%  
 5 Watt Audio Amplifier  
 Our Price £3.99  
 Less quantity discount.

**Potentiometers**



5KΩ	50KΩ	500KΩ	
10KΩ	100KΩ	1MΩ	12p
25KΩ	250KΩ	2MΩ	24p

log or lin less switch (& 1KΩ lin) 24p  
 log or lin with switch 40p  
 dual less switch  
 dual with switch 10K, 100K & 1M log only 52p  
 10K log 10K anti-log less switch 40p

**Eliminators**



9 volt 20mA (PP3)	£1.25
6 volt 50mA	£1.50
9 volt 50mA	£1.50
6 6 volt, 50mA	£2.50
9 9 volt, 50mA	£2.50
7 1/2 volt for cassette recorders	£2.00
6 7 1/2 or 9 volt	£3.00
3, 4 1/2, 6, 7 1/2, 9, 12 or 500mA (illus.)	£3.99

Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts £4.99  
 (p & p. 15p on all types)

**Presets**

Vertical or Horizontal

0.1 watt 5p	0.25 watt 7p		
100 1KΩ	10KΩ	100KΩ	1MΩ
250 2.5KΩ	25KΩ	250KΩ	2.5MΩ
500 5KΩ	50KΩ	500KΩ	5MΩ

**Capacitors**

disc ceramic		low voltage	
0.1μF 18v	5p	0.1μF 30v	5p
0.22μF 18v	5p	0.22μF 6v	5p
0.47μF 12v	5p	0.47μF 3v	5p
ceramic plate		30V	
1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

Ceramic - plate 63V (C333)

1.8pf	8.2pf	33pf	120pf
2.2pf	10pf	39pf	150pf
3.3pf	12pf	47pf	180pf
3.9pf	15pf	56pf	220pf
4.7pf	18pf	68pf	270pf
5.6pf	22pf	82pf	330pf
6.8pf	27pf	100pf	

all 5p. each

polystyrene 160V  
 10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

21μF 3p	0.68μF 3p	47μF 8p
0.15μF 5p	1μF 4p	68μF 11p
0.22μF 3p	1.5μF 4p	11μF 13p
0.33μF 3p	2.2μF 5p	1.5μF 20p
0.47μF 3p	33μF 63p	2.2μF 24p

metallised polyester 400V (C281)

0.1μF 41p	0.47μF 6p	22μF 10p
0.15μF 41p	0.68μF 6p	33μF 14p
0.22μF 41p	1μF 7p	47μF 15p
0.33μF 51p	1.5μF 8p	

silvered mica 1% (-50pf) 500V


2.2pf-820pf 7p	4.7nF-5600pf 19p
1nF-2.2nF 9p	6800pf-0.1μF 29p
2.7nF-3.6nF 16p	

mixed dielectric 600V

0.1μF 7p	0.47μF 7p	22μF 16p
0.22μF 7p	0.68μF 8p	47μF 24p
0.33μF 7p	1μF 8p	1μF 33p

**CHROMASONIC electronics**

**Heat Sinks**

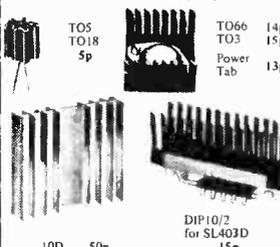

T05 TO18 5p  
 T066 TO3 14p  
 Power Tab 13p  
 DIP10/2 for SL403D 15p  
 10D 50p

**Transistors & Integrated Circuits**

AC107 25p	BC147 10p	BF196 15p	OC81 19p	2N-304 22p	2N5172 15p
AC126 17p	BC148 10p	BF197 15p	OC140 20p	2N1711 25p	LC05T1 £1.50
AC127 15p	BC149 10p	BF272 35p	OC170 25p	2N1893 30p	LC08T1 £1.50
AC128 15p	BC157 12p	BFY50 24p	OC171 30p	2N2906 all 10p	LC07T1 £1.50
AC176 15p	BC158 10p	BFY51 26p	2TX107 15p	2N3053 23p	MC1303L £1.75
AC187 25p	BC159 12p	BRY39 31p	2TX108 12p	2N3054 50p	MC1350 80p
AC187K 25p	BC169 15p	BSX21 26p	2TX109 15p	2N3055 49p	MC1350 75p
AC188 25p	BC268 15p	BSY95A 14p	2TX300 12p	2N3702 12p	MC1351 £1.00
AC188K 25p	BD115 67p	BU105/02 £1.75	2TX301 15p	2N3703 12p	MC1352 £1.00
ACY20 20p	BD131 70p	MJE340 67p	2TX302 20p	2N3704 10p	MFC4000B 49p
AD140 40p	BD132 70p	MPP192 40p	2TX303 20p	2N3705 10p	MFC4010A 55p
AD149 40p	BD133/2M-P 149p	MPP103 37p	2TX304 25p	2N3706 10p	LM380 £1.45
AD151/AD162 60p	BF160 21p	MPP104 37p	ZTX341 20p	2N3707 15p	PA234 £1.99
AF114 18p	BF167 20p	MPP105 45p	ZTX500 15p	2N3708 12p	SL403D £1.50
AF115 18p	BF173 20p	OC28 40p	ZTX502 20p	2N3709 12p	TAD100 £1.50
AF116 18p	BF180 25p	OC35 40p	ZTX503 17p	2N3711 12p	FLTR FILTER LEAFLET £1.90
AF117 18p	BF181 30p	OC44 15p	ZTX504 50p	2N3819 35p	μA710 45p
AF139 28p	BF184 25p	OC45 15p	ZTX531 25p	2N3903 15p	μA723C 95p
BC107 10p	BF185 25p	OC71 11p	2N697 18p	2N3904 17p	μA741C 47p
BC108 10p	BF194 15p	OC72 17p	2N706 12p	2N3905 21p	μA748C 60p
BC109 10p	BF195 15p	OC76 15p	2N708 15p	2N3906 12p	

MAIL ORDERS Where no p. & p. charge is shown, a minimum of 7p applies. p. & p. on overseas orders is charged at cost.  
 ADDRESS TO: Component Dept.  
 56, Fortis Green Road, London N10 3HN  
 Telephone 01-883 3705

mixed dielectric 1000V

1000pf 6p	6800pf 9p	1μF 12p
2200pf 6p	0.1μF 9p	22μF 22p
3300pf 6p	0.22μF 9p	47μF 30p
4700pf 6p	0.47μF 12p	

Ceramic 12KV d.c. 8KV d.c. HI-K 750V

10pf 9p	200pf 9p	1000pf 5p
15pf 9p	220pf 9p	2000pf 5p
22pf 9p	250pf 9p	2000pf 5p
68pf 9p	270pf 9p	3000pf 5p
82pf 9p	300pf 9p	5000pf 5p
100pf 9p	750V DISC	10,000pf 5p
120pf 9p	470pf 5p	feed-through
140pf 9p	1000pf 5p	
150pf 9p	5000pf 5p	
180pf 9p	10,000pf 5p	1000pf 5p

**Mullard B Siemens Electrolytics**

CAP μF	VOLTAGE	4	6.3	10	16	25	40	63
1.5	—	—	—	—	—	—	—	6p
2.2	—	—	—	—	—	—	—	6p
3.3	—	—	—	—	—	—	—	6p
4.7	—	—	—	—	—	—	—	6p
6.8	—	—	—	—	—	—	—	6p
10	—	—	—	—	—	—	—	6p
15	—	—	—	—	—	—	—	6p
22	—	—	—	—	—	—	—	6p
33	—	—	—	—	—	—	—	6p
47	6p	—	—	—	—	—	—	6p
68	—	—	—	—	—	—	—	6p
100	—	—	—	—	—	—	—	6p
150	—	—	—	—	—	—	—	6p
220	6p	—	—	—	—	—	—	6p
330	—	—	—	—	—	—	—	6p
470	—	—	—	—	—	—	—	6p
680	10p	—	—	—	—	—	—	6p
1000	10p	—	—	—	—	—	—	6p
1500	—	—	—	—	—	—	—	6p
2200	—	—	—	—	—	—	—	6p
3300	—	—	—	—	—	—	—	6p
4700	21p	—	—	—	—	—	—	6p

**Veroboard**

Copperclad	Plain
0.1" 0.15" 0.15"	
2 1/2" x 1 1/2" 6p	6p
2 1/2" x 3 1/2" 20p	16p (9)
2 1/2" x 5" 24p	21p (7)
3 1/2" x 3 1/2" 24p	21p (8)
3 1/2" x 5" 27p	27p (10)
17" x 2 1/2" 67p	50p
17" x 3 1/2" 90p	70p
17" x 5" —	75p


Spot-face Cutter 36p  
 Pin Insertion Tool 47p  
 Terminal Pins 18p per pack of 36

**NEW LISTS**  
**BOXES, CHASSIS, etc.** No. 7  
**TRANSISTORS, I.C.'s, etc.** (soon)  
 (postage 5p)

**Aluminium Boxes**  
 Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2 1/2"	5 1/2"	1 1/2"	35p	8p
(8)	4"	4"	1 1/2"	35p	8p
(9)	4"	2 1/2"	1 1/2"	35p	8p
(10)	4"	5 1/2"	1 1/2"	40p	8p
(11)	4"	2 1/2"	2"	35p	8p
(12)	3"	x 2"	x 1 1/2"	32p	9p
(13)	6"	x 4"	x 2"	50p	10p
(14)	7"	x 5"	x 2 1/2"	50p	12p
(15)	8"	x 6"	x 3"	75p	18p
(16)	10"	x 7"	x 3"	85p	20p

**THE TEXAN**

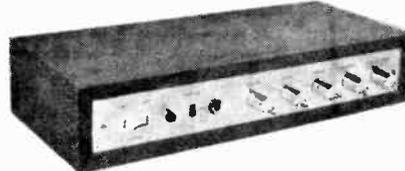

Complete Kit (inc. Teak Case) **£28.50 P&P 45p**

20 Watts per channel integrated stereo amplifier developed by engineers of Texas Instruments Ltd. This designer approved kit has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 at -3dB. The semi-conductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include: bass, treble, volume, balance, on/off, 'on' indicator, headphone sockets, scratch filter, rumble filter, inputs for magnetic phono; tuner; aux; or tape; head etc; input; selector, mono/stereo switch. The construction of this kit was featured in 'Practical Wireless' May - Aug. 1972.

**Quantity Prices on application.**

CAP μF	VOLTAGE	18	25	40	64
500	—	—	—	—	—
1250	—	—	—	—	—
1600	—	—	—	—	—
2000	—	—	—	—	—
2500	—	—	—	—	—
3200	—	—	—	—	—
4000	—	—	—	—	—
6400	—	—	—	—	—

**Ni-Volt Electrolytics**

1.2 4, 8μF 450V	14p	32μF 450V	20p
1μF 450V	15p	50μF 350V	20p
8 8μF 450 V.W	18p	32 32μF 350 V.W	25p
8 16μF 450 V.W	20p	32 32μF 450 V.W	43p
16 16μF 450 V.W	25p	50 50μF 350 V.W	35p


# UNISOUND FOR THE NEW SOUND



AT  
**£26.12**  
INC.  
VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Unilex system brought up-to-date by RTVC using integrated circuits. Turntable is the proven Garrard 2025TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EMI Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. £26.12 complete plus £1.40 packing + £1.40 post. Diamond Stylus £1.25 extra. Stereo headphones with adaptor £4 extra. Send for leaflet.

## AN RTVC EXCLUSIVE DESIGN

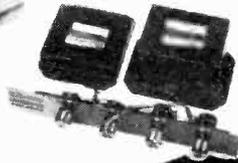

**UNISOUND MODULES ONLY £6.95 + 50p. p. & p.**

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips very low distortion at all power levels, over the audio spectrum.

**RTVC No price in**

If you can solder on printed circuit board you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions

## THE TOURIST PB CAR RADIO KIT AN INCREDIBLE BUY ONLY FROM RTVC



**£7.70**  
inc. vat


The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire. The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7" wide, 2" high and 4½" deep.

\* Circuit diagram and comprehensive instructions 50p free with parts.

\* Fully retractable lockable car aerial £1.25 post paid.

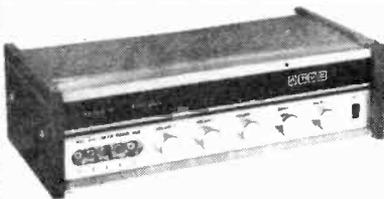**PRICE ONLY £7.70 p. and p. 55p**  
Speaker with baffle and fixing strips £1.50.  
25 p. & p., post free if bought with the kit.  
Send for leaflet.



## RELIANT Mk IV


**A GOOD QUALITY AMPLIFIER—12 Watts £10.50 (inc. VAT). 20 Watts £13.50 (inc. VAT)**

\*5 Electrically Mixed inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV Inputs. 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Power output: 12/20 watts into 8 ohms. Size approx. 12½ x 6 x 3½ ins.

12W version **£10.50** plus 60p  
20W version **£13.50** p & p
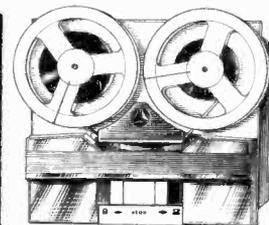
## SOUND 50

**50 WATT AMPLIFIER.** Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. **£38.51** (inc. VAT) £1.50 p. and p.



## PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, less leads. Caters up to 7ins. spools. Unused but store soiled hence no warranty. **£8** plus £1 p & p

\* Denotes VAT has been absorbed in the price without increase on VISCOUNT audio systems.

**Increase with VAT!**

# VISCOUNT III AUDIO STILL ONLY £52\* COMPLETE


**PRICES: SYSTEM 1**  
 Viscount III R 101 amplifier £24.20 + £1 p & p  
 2 Duo Type II speakers £15.40 + £2.20 p & p  
 Garrard SP25 Mk. III with MAG. cartridge plinth & cover £25.00 + £1.75 p & p  
 total £64.60  
 Available complete for only £52\* + £3.50 p & p

**PRICES: SYSTEM 2**  
 Vicount R 101 amplifier £24.20 + £1 p & p  
 2 Duo Type III speakers £35.20 + £3.30 p & p  
 Garrard SP25 Mk. III with MAG. cartridge plinth & cover £25.00 + £1.75 p & p  
 total £84.40  
 Available complete for £69\* + £4 p & p

14 + 14w. r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10w. at 1kHz - 0.1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect, transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.

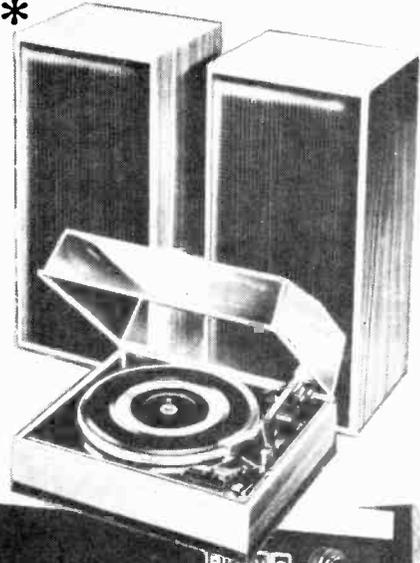The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.



**SPEAKERS:** Duo Type II Size approx. 17in. x 10½in. x 6½in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts ohms. Simulated Teak cabinet. £15.40 a pair (inc. VAT), £3.30 p. and p. Duo Type III Size approx. 23½in. x 11½in. x 9½in. Drive unit 13½in. 8½in. with H.F. speaker. Max. power 20 watts ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet.  
**SPECIFICATION R101:** 14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms.) Total distortion @ 10W 1kHz @ 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within idB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: (all controls at max.)—P.U.1. and radio — 65dB, P.U.2 — 58dB. Cross talk better than — 35dB on all inputs. Size approx. 13½in. x 9in. x 3½in. Send S.A.E. for fully illustrated brochure. 12 month's written guarantee.

**ONLY FROM US**

**TIMES OF OPENING:** Acton—Mon.—Sat. 9.30-5.  
 Closed all day Wed.  
 Edgware Rd.—Mon.—Sat. 9.30-5. Closed all day Thurs

**VISIT OUR SHOWROOMS** **ATVC**  
 Radio and TV Components (Acton) Ltd.  
 21c High Street, Acton, London W3 6NG  
 323 Edgware Road, London W2  
 Mail orders to Acton. Terms C.W.O.  
 Goods not despatched outside U.K.  
 All enquiries S.A.E.

**All prices in pounds and new pence**

VALVES		25 6J6		20 705		21-13 128H7		40 37		40 DAF91		30 EBL31		50 N78		21-50 PL500		80 P403		80	
1A7GT	45 6HJ6	50 6J7M	45 706	20 716	25 741E	50 75	50 75	50 DAF96	45 E936	35 E113	50 E108	21-50 PL504	80 P401	60							
1CP31	27-00 6HJ6	45 6K6GT	45 707	50 716	60 741E	50 705B	50 705C	50 DAF96	45 E936	35 E113	50 E108	21-50 PL504	80 P401	60							
1D5	50 6BR7	50 6K7M	35 787	22-25 20L1	21-10 20L2T	55 D991	50 D992	30 E108	30 E113	30 E118	21-00 PC96	60 P4	22-50 P4C41	50							
1H5	50 6H6B	70 6K7M	35 734	85 20L1	85 20L2	50 D992	50 D992	30 E108	30 E113	30 E118	21-00 PC96	60 P4	22-50 P4C41	50							
18A4GT	55 6H8T	21-30 6K7GT	35 90W6	60 20P5	11-20 71E	45 D996	45 D996	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
1R5	40 6HJ6	85 6K8M	60 716	60 716	60 716	50 D996	50 D996	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
184	30 6H8T	90 6K8M	40 10F1	75 25L40T	50 3A2	50 D996	50 D996	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
185	30 6C4	33 6K8GT	50 10E2	90 25V1	65 10E2	60 D992	60 D992	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
1T4	30 6C5A	35 6K25	75 10F9	60 25V1	30 150V4	60 D991	60 D991	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
2A4	40 6C6	25 6L6G	50 10F18	50 25Z20T	55 801	60 D992	60 D992	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
2Q4	50 6C10R	21-25 6L18	45 10L11	65 20Z6	55 801	60 D992	60 D992	45 E938	40 E941	40 E941	50 P433	60 P433	63 P433	60							
3Q5	50 6C11G	60 6Q7E	40 10P13	60 30P3	30 1310V15	75 D166	11-25 E188	35 E280	27 P436	60 P4	22-50 P4C41	50									
3B4	25 6C14	65 6Q7GT	43 11E2	24-00 30C1	80 806A	75 D166	11-25 E188	35 E280	27 P436	60 P4	22-50 P4C41	50									
3V4	48 616	35 6M7M	40 12A7G	30 20C7	90 954	60 D193	40 E186	40 E186	40 E186	40 E186	50 P433	60 P433	63 P433	60							
3R4GY	75 6E5	21-00 6M7M	75 12A7T	35 20C18	80 1626	55 D191	48 E186	40 E186	40 E186	40 E186	50 P433	60 P433	63 P433	60							
5U4G	85 6P1	70 6M7M	40 12A7G	35 20E1	85 40E2V15	55 D191	48 E186	40 E186	40 E186	40 E186	50 P433	60 P433	63 P433	60							
5V4G	45 6F5G	60 6H7M	40 12A7T	30 20P11	75 5763	70 D192	45 E938	40 E941	40 E941	40 E941	50 P433	60 P433	63 P433	60							
5Y3GT	40 6F6G	35 6H7GT	30 12A7T	30 20P11	11-20 71E	60 D192	45 E938	40 E941	40 E941	40 E941	50 P433	60 P433	63 P433	60							
6Z4G	40 6F6G	50 6H7GT	40 12A7G	40 20P11	85 7475	60 D196	45 E938	40 E941	40 E941	40 E941	50 P433	60 P433	63 P433	60							
6Z0L2	80 6F11	40 6H7GT	35 12B16	40 20P11	85 7475	60 D196	45 E938	40 E941	40 E941	40 E941	50 P433	60 P433	63 P433	60							
6A7	75 6P13	45 6H7GT	35 12B16	40 20P11	85 7475	60 D196	45 E938	40 E941	40 E941	40 E941	50 P433	60 P433	63 P433	60							
6A8G	40 6P14	70 6H7GT	40 12E1	23-00 30P4	11-12 ATP1	60 E180	21-25 K781	21-75 PL86	45 T41	21-00 P436	40										
6A8K	85 6P23	85 614GT	65 12A5GT	30 20P12	80 ATP2	60 E180	21-25 K781	21-75 PL86	45 T41	21-00 P436	40										
6A8S	35 6P24	75 616G	21-00 12A7GT	50 30P19	85 421	24-00 E4F3	55 E936	35	21-13 PENA4	21-00 P16	75 P418	21-25									
6A8T	35 6P25	60 6V63	60 12A7GT	40 20P11	75 475	50 D196	45 E938	40 E941	40 E941	40 E941	50 P433	60 P433	63 P433	60							
6A8U	33 6P28	65 6R6	30 12K8GT	50 20P12	93 421	55 E183	33 E41	65 E936	65 E936	65 E936	65 E936	65 E936	65 E936	60							
6A8V	38 6P32	25 6V6GT	40 12A7GT	40 20P11	90 4231	55 E183	33 E41	65 E936	65 E936	65 E936	65 E936	65 E936	65 E936	60							
6A8W	85 6G6	35 6X4	35 12A7GT	50 25A5	75 C1831	21-00 E9C90	35 E936	35 M14	88 PL6	55 C26	80 P411	75									
6A7E	35 6H6	23 6X5G	40 12A7GT	35 3516	50 C1835	75 E9C90	40 E938	75 M14	40 P41	50 C78	35 P4120	21-00									
6A7G	25 6J5M	50 6X5GT	40 12A7GT	35 35W4	35 C1831	21-30 E9F83	40 E938	75 M14	40 P41	50 C78	35 P4120	21-00									
6B4G	21-00 6J5G	20 716	70 12A7T	35 35Z5	70 C1830	60 E9F89	30 E938	35 M14	40 P41	50 C78	35 P4120	21-00									
6B6G	25 6J5GT	30 716	50 12A7T	40 35Z5	50 C1832	60 E938	30 E938	35 M14	40 P41	50 C78	35 P4120	21-00									

Transistors		1AC128		20 BY106		15 NKT713		25 0C44		17		7430		20 7474		40 74100		22-50 74157		21-80	
1N914	07 2N2919	20 ACY20	20 BZY98	16 0A70	10 0C46	12						7432	42 7475	55 74107	50 74170	24-10					
18J13	25 2N2369A	40 ACY39	50 1381-40	47 0A71	10 0C57	60						7433	70 7476	45 74110	80 74174	22-00					
18202	23 2N2444	15 AD149	50 119003	15 0A81	08 0C58	60						7437	65 7480	45 74111	41 74175	21-35					
2G302	22 2N2646	45 AP115	50 6RT102	30 0A85	12 0C59	65						7438	65 7482	87 74118	21-00 74176	21-60					
2G371	22 2N2904	20 AP117	25 6RT102	25 0A91	07 0C71	65						7440	20 7483	21 74119	21-00 74190	21-95					
2N404	20 2N2926	10 ARV25	25 6RT102	25 0A91	07 0C71	65						7442	20 7484	90 74121	60 74191	21-95					
2N697	15 2N3055	75 BC107	10 MJE2955	10 0A72	50 0C72	20						7443	75 7486	45 74122	21-35 74192	22-00					
2N706	10 2N3702	10 BC108	10 11-37 OAZ222	45 0C81	20							7445	20 7489	75 74123	22-70 74193	22-00					
2N1132	25 2N3819	35 BC109	10 MJE3055	27 0A224	45 0C84	25						7446	20 7490	75 74124	21-00 74194	22-50					
2N1305	22 2A412	30 BC189*	15 NKT212	27 0A224	22 0C120	25						7448	20 7491	80 74125	21-00 74195	21-85					
2N2147	75 2A412	30 BF898	28 NKT214	15 0A224	23 0C171	30						7449	20 7492	75 74126	21-00 74196	21-85					
2N2160	60 AC126	20 BFY50	22 NKT223	30 0A224	23 0C171	30						7451	20 7493	80 74127	21-00 74197	21-50					
2N2218	20 AC127	25 BFY51	20 NKT251	24 0C35	50 0C71	97						7452	45 7492	30 7495	21-00 74198	24-60					
												7453	40 7493	30 7496	21-00 74199	24-60					
												7454	45 7492	30 7496	21-00 74199	24-60					
												7455	20 7498	40 7497	22-50 74196	21-55					

**Integrated Circuits**


7400	20 7411	23 7440	42 7441AN	75 7484	90 74121	60 74191	21-95
7401	20 7412	20 7402	20 7413	30 7414	30 7415	20 7416	20 7417
7402	20 7418	20 7403	20 7419	20 7420	20 7421	20 7422	20 7423
7403	20 7419	20 7404	20 7420	20 7421	20 7422	20 7423	20 7424
7404	20 7420	20 7405	20 7421	20 7422	20 7423	20 7424	20 7425
7405	20 7421	20 7406	20 7422	20 7423	20 7424	20 7425	20 7426
7406	20 7422	20 7407	20 7423	20 7424	20 7425	20 7426	20 7427
7407	20 7423	20 7408	20 7424	20 7425	20 7426	20 7427	20 7428
7408	20 7424	20 7409	20 7425	20 7426	20 7427	20 7428	20 7429
7409	20 7425	20 7410	20 7426	20 7427	20 7428	20 7429	20 7430
7410	20 7426	20 7411	20 7427	20 7428	20 7429	20 7430	20 7431

**RST VALVE MAIL ORDER CO. 16a WELLFIELD ROAD, LONDON SW16 2BS**

Special Express Mail Order Service      TELEX 946708      Send large S.A.E. for list. Phone 677 2424 (4 lines)

Express postage 1p per transistor, over 10 post free. Integrated Circuits & Valves 5p, plus 1p for each additional item, over £5.00 post free

## P. C. BOARDS

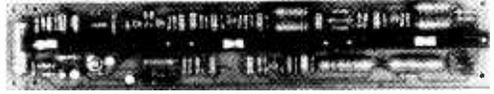

Reverberation Unit PCB.

### FOR P.W. PROJECTS

All PCB's Fibreglass, Drilled, Roller-Tinned Circuit and Layout Diagrams free with each PCB

**REVERBERATION UNIT (Nov/Dec 1972)**  
PCB (2in x 1 1/4in). Specially designed to also hold Slider Pots with spacing compatible with published front panel £1-20  
SET of R's, C's, S/C's, Slider Pots, Transformer £5-95



**8 WATT AMPLIFIER (Nov 1972)**  
PCB (Mono—2 1/2in x 3in) 60p

# look!
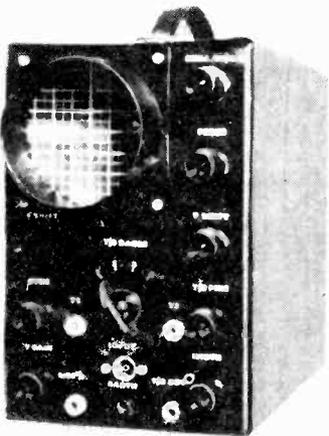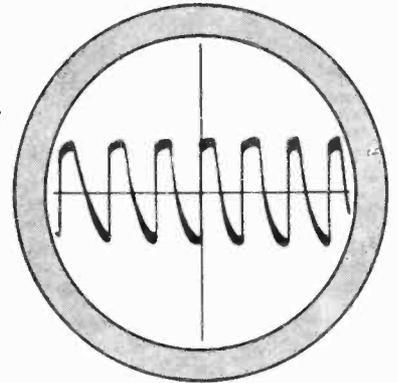
# electronics really mastered

**... practical  
... visual  
... exciting!**

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


### BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
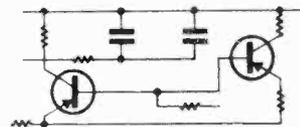
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL43

**special free gift also to all our students**

# ESSENTIAL BOOKS FOR RADIO AMATEURS

## New Edition A GUIDE TO AMATEUR RADIO by Pat Hawker G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.  
90p post paid

## New Book TELEVISION INTERFERENCE MANUAL by B. Priestley G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.  
90p post paid

## RAE MANUAL by G. L. Benbow G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination.  
90p post paid

## RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.  
£4.10 post paid


These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

## RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688


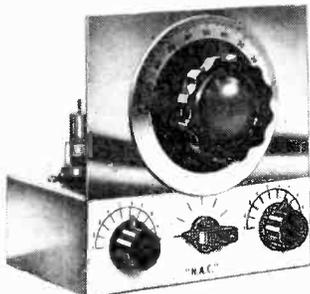
## H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### NEW "DX" RECEIVER

Complete kit—price £3.80 (post & packing 20p). Customer writes: "Australia, India and America at loud volume."—1 am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. **EXCITING COMPETITION for Short-Wave listeners.** Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

## EX COMPUTER PRINTED CIRCUIT PANELS

2 x 4 in. packed with semi-conductors and top quality resistors, capacitors, diodes etc. Our price 10 boards 50p (8p). With a guaranteed min. of 35 transistors—data included.

### SPECIAL BARGAIN PACK

25 boards for £1 (25p).

### ELECTROLYTICS

10,000µ 75v, 33,000µ 40v, 4½ x 2½ in. dia., 25,000µ 25v, 20,000µ 30v, 8,000 55v, 4½ x 3 in. dia. 50p (12p), 15,000µ 15v, 4½ x 2 in. dia. 20p (10p), 2,000µ 25v wire ended, 3 x 1 in. dia. 15p (5p) or 12 for £1.50 (15p).

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

3A STUD RECTIFIERS, 100 p.i.v.

4 for 50p (5p)

ASSORTED RELAYS 8 for £1 (25p)

SUB MIN. CO-AX. PLUGS & SKTS.

4 pairs 50p (5p)

MINIATURE GLASS NEONS

12 for 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES, MIXED

8 for 50p (8p)

PAPST EXTRACTOR/BLOWER FANS

100 cfm 4½ x 4½ x 2 £3.50 (28p)

QUARTZ HALOGEN BULBS

12v 55w 50p (5p)

Postage and package for each item shown in brackets.

## KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD  
LONDON W8.

01-478 8499

## TRANSFORMERS

### DOUGLAS GUARANTEED

12 or 24 volts

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS*†	£0.91 9p
12V x 2 500 mA x 2	MT213 CT*†	£0.87 16p
12V x 2 1A x 2	MT 71 AT*‡	£1.48 24p
12V x 2 2A x 2	MT 18 AT*	£2.06 30p
12V x 2 3A x 2	MT 70 AT*	£2.59 32p
12V x 2 4A x 2	MT 108 AT*	£2.82 34p
12V x 2 5A x 2	MT 72 AT*	£3.33 42p

30 volts. All tapped at 0-12-15-20-24-30V

put Ref. No. Price P.P. Out-Ref. No. Price P.P.

put

500 mA MT 112 CT† 1-12 16p 3A MT 20 AT 2-64 32p

1A MT 79 AT† 1-55 29p 4A MT 21 AT 3-10 40p

2A MT 3 AT 2-23 30p 5A MT 51 AT 4-31 42p

50 volts. All tapped at 0-19-25-33-40-50V.

500 mA MT 102 AT† 1-45 24p 3A MT 105 AT 3-91 41p

1A MT 103 AT 2-00 32p 4A MT 106 AT 5-06 41p

2A MT 104 AT 3-10 32p 6A MT 107 AT 7-47 50p

60 volts. All tapped at 0-24-30-40-48-60V.

500 mA MT 124 AT† 1-46 30p 2A MT 127 AT 3-16 41p

1A MT 126 AT 2-24 32p 3A MT 129 AT 4-59 41p

### AUTO-WOUND RANGE

Power Winding tapped at Ref. No. Price P. & P.

output

20 VA 0-115-210-240 MT 113 CT £0.89 16p

75 VA MT 64 AT £1.79 30p

150 VA 0-115-200-220-240 MT 4 AT £2.15 32p

200 VA MT 65 AT £3.00 32p

400 V. Output at 50 Hz. Ref. IT3 AT Price P. & P.

£2.30 29p

C-D Ignition system by R. M. Marston

£2.30 29p

£2.30 29p

### EQUIPMENT RANGE

Sec. Output (r.m.a.) Ref. No. Price P. & P.

3-0-3 V. 200 mA MT 238 CS\*† £0.89 8p

5-0-5 V. 100 mA MT 13 CS\*† £0.91 8p

12-0-12 50 mA MT 239 CS\*† £0.91 8p

20-0-20 30 mA MT 241 CS\*† £0.91 8p

0-20 x 2 300 x 2 MT 214 CT\*‡ £1.21 16p

0-8-9 x 2 500 mA x 2 MT 207 CT\*‡ £1.46 19p

0-15-20 x 2 500 mA x 2 MT 205 AT\*‡ £2.12 29p

0-15-27 x 2 500 mA x 2 MT 203 AT\*‡ £2.45 29p

0-15-27 x 2 1A x 2 MT 204 AT\*‡ £3.42 30p

10-12-0-12-20 700 mA (d.c.) MT 221 AT\*‡ £1.11 26p

AT indicates open universal fixing with tags; CT is

open U-clamp fixing with tags; CS is open U-clamp

fixing with P.C. spalls; \* with interwinding screen; † un-

tapped 240V Primary; ‡ Primary tapped at 210-240V.


Other Primaries tapped at 200-220-240V.

Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.

(Dept. MO.12PW), Thames St., LOUTH, Lincs. LN11 7AD

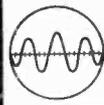MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.



**TUAC**

TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD. 63 MITCHAM ROAD, LONDON SW17 9PG 01-672 3137 9080

**ARE PROUD TO ANNOUNCE AN ENTIRELY NEW RANGE OF PROFESSIONAL STANDARD DISCOTHEQUE EQUIPMENT AND AUDIO MODULES**

**TUAC DISCOTHEQUE MIXER FEATURING AUTO FADE**



£20.00 Complete PSU £3.25 p. & p. 50p.


FEATURES: MIC input with volume and tone control. Automatic MIC override, with a djustable fade depth and sensitivity. fades the music down when you make your announcements, then the music automatically returns to its original level. Left and right deck volume. Master volume, treble and bass controls. Headphone monitor facilities for both decks. Headphone volume control. Automatic/manual override switch. Panel mounting, finished in durable satin enamel. 40V. D.C. operation. Tone control specification as for VAO6 pre-amp.

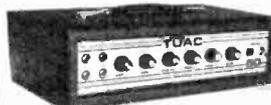**TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last**



£49.50 p. & p. £1.00

100 Watt RMS Sine Wave Slave Amplifier. Suitable for use with above mixer. Slave input, gain control, slave output. Hi/Lo sensitivity switch. Rugged circuit. Rugged leather-cloth covered case. Short and open circuit protection. Over 200 watts peak output. 8Ω output impedance.



£41.25 p. & p. £1.00 100 watt version £60.50 p. & p. £1.00.

50 Watt RMS Sine Wave General Purpose Amplifier. Suitable for Disco, PA, Guitar. 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leather-cloth covered case, short and open circuit protection. Tone control specification as VA08 pre-amp.

**TUAC MICROPHONE MIXERS—battery operated—all steel construction**



£14.12 p. & p. 35p

FEATURES: 4 inputs with adjustable sensitivity, volume and extra wide range tone control on each input. 2 outputs, stereo or mono use. Max output 2V. Low noise silicon transistor line up. 18V. D.C. operation.



£8.25 p. & p. 40p

FEATURES: 2 Inputs with adjustable sensitivity, volume and extra wide range tone control on each input. Single output. Mono use max. output 2V. Low noise silicon transistor line up. 18V. D.C. operation.


**TUAC COMBO AMP.**



£60.00 p. & p. £1.50.

25 Watt RMS Sine Wave Ideal for small groups, club and studio work, 4 inputs, 2 volume controls. Master volume treble, middle & bass. Uses heavy duty Celestion speaker.

**TUAC POWER AMPLIFIER MODULES—TP 100W now with 4 RCA 150 watt output transistors**

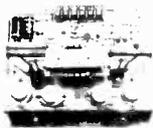

TP100W. T.H.D. at full power 2%

All output power ratings are R.M.S. continuous sine wave using specified supply. Each circuit incorporates a robust driver transformer stage with thermal overload protection and is short and open circuit proof. Full power response 10HZ-20KHZ ±2dB. Input sensitivity 30mV into 3KΩ. Hum and noise better than -70dB. Output impedance 8Ω. Constructed on glass fibre P.C. board. O/P matching transformer 4-8-16-60-100Ω £8.00.

TP100W 100 watts RMS output into 8Ω £15.18 p. & p. 45p. PS100 Power supply and transformer £9.10 p. & p. 50p. PS100/100 Supply for two TP100W modules £18.00 p. & p. 65p.

TP50W 50 watts RMS output into 8-15Ω £10.36 p. & p. 40p. PS50 Power supply and transformer £6.86 p. & p. 50p. PS50/50 Supply for two TP50W modules £11.95 p. & p. 65p. Two TP100W modules can be wired in a bridge output circuit to give a single 200W R.M.S. output into 8Ω using PS100/100 supply. Use phase splitter PS201 to drive modules.

**TUAC PRE-AMPLIFIER MODULES**

**VA06** £3.72 Suitable crystal/ceramic P.U., Mic., guitar, radio tuner, vol., treble & bass controls. Sensitivity 8mV for 30mV O/P. Treble +22 -15dB @ 12KHz. Bass ± 18dB @ 40Hz.

**VA08** £4.22 As VA06, but with extra middle control. Treble +28dB @ 18KHz. Middle +20 -15dB @ 4KHz. Bass +20 -10dB @ 40Hz. Sensitivity 4mV.

**SVA01** £9.47 As VA08 but stereo with bal. control.

**MVA01** £4.50 Suitable for disco, mic., tape input, 2 inputs, with Vol & tone control on each input. Sensitivity 2mV. +25dB @ 12KHz to +20dB @ 40Hz.

**MEVA01** £2.60 Magnetic Cartridge equalisation. Connects to input of VA06 or VA08 with volume control.

**SIPAM** £2.40 Master volume and presence control. High treble boost of +15dB.

**EFVUA01** £2.50 Increases the output of any of the above to 1V. RMS. Low impedance emitter follower output.

Constructed on glass fibre P.C. Board, individually tested.

**NEW RANGE**

**HPA01** £3.72 Headphone Amplifier. 8-15Ω 200mV output. Left right fader. Volume control.

**AMF01** £4.40 Auto Fade Unit. Feed deck and Mic. Pre-amps in. output to power module. With fade depth and sensitivity controls. See spec. on disco mixer.

**PS201** £1.75 Phase Splitter unit to drive two TP100W modules in bridge O/P.

**WAA01** £2.75 WAA-WAA Module. This is an exceptional unit, producing a superb WAA-WAA for guitars. Pedal soon available.

**FUZ01** £4.75 Fuzz Module. Professional standard. Volume, tone & fuzz sustain controls. Case soon available.

**FXD01** £3.17 Frequency Doubler Module. Doubles the frequency of any sinusoidal wave, such as that obtained from the WAA-WAA module.

**TUAC LIGHT MODULATORS**



3 Channel SILMB illus.

Constructed on glass fibre P.C. board, individually tested.

Three channel light modulator will control three separate sets of lights, up to 1000 watts each set. One channel responds to the bass, one to the middle, and one to the high frequencies. Input sensitivity only 0.5 watt/ Three individual controls allow for adjustment of

the three channels, and a master sensitivity control allows for input levels up to 100 watts to be safely accommodated. Full interference suppression. Full wave control. Isolating input transformer does not affect amplifier operation. Fully Fused.

Single Channel version. S2LMD Increased capacity of 1800 watts. Sensitivity control. Isolating input transformer does not affect amplifier operation.

**SILMB 3 Channel** £17.45 p. & p. 35p.

**S2LMD 1 Channel** £6.47 p. & p. 25p.


**POWER SUPPLY UNIT**

For use with all pre-amp modules and discotheque mixer. Output 40V. 100mA £3.25 p. & p. 25p.

ALL PRICES ARE EFFECTIVE FROM 1st APRIL 1973 AND ARE INCLUSIVE OF V.A.T.

POSTAGE AND PACKING 20p EA.

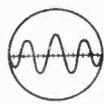ALL TUAC KITS ARE SUPPLIED COMPLETE WITH EASY TO FOLLOW WIRING INSTRUCTIONS AND CIRCUIT DIAGRAM. CALL FOR A DEMONSTRATION OF ANY OF THE ABOVE UNITS. SPEAKERS AND CABINETS ALSO SUPPLIED.



**TUAC**

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE. OUR TECHNICAL STAFF WILL BE PLEASED TO ADVISE YOU ON ANY PROBLEM. ALL TUAC EQUIPMENT CARRIES A 12 MONTH GUARANTEE. TRADE AND EXPORT ENQUIRIES WELCOME.

# DISCOUNTS UP TO

# 60%

## Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

**GARRARD SP25 Mk III Special Purchase.**  
**£17.45**  
 Limited number available  
 Garrard SP25 Mk. III  
 Goldring G800  
 Teak plinth and tinted cover  
 All leads supplied.  
 Please add £1.25 P. & P. & Ins.

### TURNTABLES

**Please add 75p P. & P. & Ins.**  
 Connoisseur BD1 Chassis £12.75  
 Garrard SP25 Mk. III £9.90  
 Garrard AP76 £17.20  
 Garrard SL65B £13.95  
 Garrard 401 £28.75  
 Garrard Zero 100 (Auto) £36.90  
 Garrard Zero 100 (Single) £35.90  
 BSR MP60 £9.40  
 Goldring GL72 £20.90  
 Goldring GL72/P £27.45  
 Goldring GL75 £26.85  
 Goldring GL75/P £34.95  
 Goldring 101/P.C. £20.00  
 Wharfedale Linton + cart. £25.90  
 Thorens TD125AB Mk. II. £27.95  
 Thorens TD150 Mk. II. £91.45  
 Thorens TD160 AB & C £53.95

### TUNERS

**Please add 85p P. & P. & Ins.**  
 Amstrad Multiplex 3000 £27.25  
 Armstrong 523 £39.50  
 Armstrong 524 £31.45  
 Rogers R/brook FET4 (Chassis) £35.75  
 Rogers R/brook FET4 (Cased) £38.95  
 Rogers R/bourne FET4 (Chassis) £45.00  
 Rogers R/bourne FET4 (Cased) £49.50  
 Sinclair PR060 (Module) £16.95  
 Sinclair 2000/3000 Tuner £29.90  
 Leak Delta FM (Cased) £53.60  
 Leak Delta AM/FM (Cased) £63.75  
 Alpha Highgate FT150 £37.95  
 Metrosound FMS 20 £38.65  
 Philips RH 690 £33.00

### TUNER/AMPLIFIERS

**Please add £1 P. & P. & Ins.**  
 Alpha Highgate 150 £49.75  
 Armstrong 525 (Teak cased) £69.45  
 Armstrong 526 AM/FM (Teak cased) £77.25  
 Leak Delta 75 £119.00  
 Teleton 2100 £32.50  
 Goodmans One Ten £98.90  
 Goodmans Mod 90 £85.50  
 Rotel 150 £49.50  
 Rotel 400 £75.50  
 Rogers Ravensbrook (Teak cased) £77.00  
 Rogers R/brook (Chassis) £72.00  
 Alpha FR 3000. New product £72.00

### AMPLIFIERS

**Please add 85p P. & P. & Ins.**  
 Amstrad 8000 Mk. II £14.95  
 Amstrad IC2000 £27.50  
 Amstrad Integra 4000 £22.50  
 Armstrong 521 (Teak cased) £43.90  
 Alpha Highgate 212 £24.85  
 Alpha Highgate FA300 £32.25  
 Alpha Highgate FA400 £35.65  
 Leak Delta 30 £44.85  
 Leak Delta 70 £54.90  
 Metrosound ST20E £24.20  
 Metrosound ST60 £45.95  
 Pioneer SA600 & 610 £57.25  
 Pioneer SA500A £31.95  
 Pioneer SA1000 £96.95  
 Rogers R/brook (Chassis) £37.95  
 Rogers R/brook (Cased) £41.50  
 Rogers R/bourne (Chassis) £49.95  
 Rogers R/bourne (Cased) £52.75  
 Sinclair PR060 2 X Z30/PZ5 £14.70  
 Sinclair PR060 2 X Z30/PZ6 £16.70  
 Sinclair PR060 2 X Z50/PZ8 £22.95  
 Sinclair AFU (Filter Unit) £24.20  
 Sinclair 605 £17.95  
 Sinclair 2000 Mk. II £21.50  
 Sinclair 3000 Mk. II £28.00  
 Wharfedale Linton £39.70  
 Teleton SAQ 307 £22.95  
 Rotel RA310 £34.95  
 Rotel RA610 £52.95

### SPEAKERS

**Please add £1.50 per pair P. & P. & Ins. Price per pair**  
 Amstrad I38 £13.90  
 Wharfedale Linton 2 £28.40  
 Wharfedale Linton 2 £35.40  
 Wharfedale Melton 2 £45.90  
 Wharfedale Dovedale 3 £59.80  
 Celestion Ditton 120 £38.40  
 Celestion Ditton 15 £51.00  
 Celestion Ditton 25 £84.50  
 Celestion County (new prod.) £34.50  
 Goodmans Double Max. £47.40  
 Goodmans Mezzo 3 £45.95  
 Goodmans Magister £82.95

### Special bulk purchase

**£2-90**

Plus 65p P. & P. & Ins.  
 Finished in teak veneer with tinted dust cover. (Fully assembled).  
 For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR, McDonald MP60 and others.  
 For AP76; AP75; SL72B; SL75; SL95B\* £3.90 + 65p P. & P. & Ins.  
 Also finished in walnut to match Japanese equipment—at no extra.

### CARTRIDGES

**Please add 10p P. & P. & Ins.**  
 Goldring G850 £3.35  
 Goldring G800 £4.70  
 Goldring G800E £7.50  
 Goldring G800 Super E £11.15  
 Shure M3D £3.70  
 Shure M44E £4.75  
 Shure M55E £5.55  
 Ortofon SL15 £15.85  
 Sonotone 9TAHC £1.35



All prices correct at time of press E. & O. E. and are subject to alterations

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept (PW4) 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbride Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

**MAIL ORDERS.** Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS** Please note that cheques can only be accepted together with cheque cards (not Barclay Card)

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country



## for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

## EASY-TO-USE DISPENSERS



Size 5  
 Savbit alloy  
 18 swg, 18p (illustrated).  
 Size 19A  
 60/40 alloy  
 18 swg, 18p  
 Size 15  
 60/40 alloy  
 22 swg, 22p

## IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 25p



Size 12 for Service Engineers and Electricians. 75ft of 18 swg Savbit alloy. 75p



## NEW! BIB WIRE STRIPPER AND CUTTER

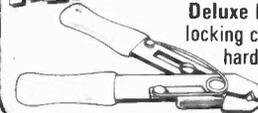

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

## ELEKON SPECIALS

**TWIN POWER SUPPLY PANELS.** contains 2 x Texas 1B1010 Silicon Bridge Rectifiers, 100 P.I.V. at 1A; 1 x Mullard OAZ225 Zener Diode, 7.5V, 10W; 1 x I.T.T. Zener Diode, 5.1V, 1W; 5 x Texas 1B121 Silicon Diodes, 150 P.I.V. at 200mA. Electrolytic Capacitors, 2 x Plessey 1,000µF, 25V; 2 x 50µF, 50V; 2 x Mullard 450µF, 25V; 2 x Mullard 440µF, 25V. Circuit details supplied. Our best ever bargain £1, post 10p.

**ELECTROLYTIC CAPACITORS** µF/V 1250/25, 2000/25, 2500/25, 4700/16, 8000/30, 10,000/15, 10,000/25, 16 + 16/500, 1000 + 1000/30. All at 35p each, post free. 16 + 16/350, 32 + 16/350, 40 + 40/250, 50 + 50/300, 80 + 80/450, 100 + 100/385. All at 25p each, post free.

2000/50, 2500/50, 5000/50, 10,000/50, 12,500/50, 50p each, post free.  
**SOXSOL DE-SOLDER BRAID.** 9 ft. length 50p, 20 ft. length £1.00, 50 ft. length £2.50. Enquiries invited for any Electrolytic Capacitors. Special Bulk Prices. We Guarantee all our Capacitors.

## ELEKON ENTERPRISES

224a St Paul's Road, Highbury Corner, London N.1

## LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed—build as you learn with the exciting new 'Technatron' kit. No

Extras. Tools, transistors, meter etc. All supplied. You could build a radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV, ELECTRONICS, C & G, TELECOMMS ETC.

Dept. BPW14 Aldermaston Court, Reading RG7 4PF

Name.....  
 Address.....

Age..... CV BPW14

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-20	AD162	0-33	BC148	0-10	BD137	0-45	BF188	0-40	OC19	0-35	2G371	0-18	2N2219	0-20	2N3054	0-48	2N4059	0-10
AC113	0-20	AD161 A		BC149	0-12	BD138	0-50	BF194	0-12	OC20	0-83	2G371 B	0-12	2N2220	0-22	2N3055	0-50	2N4060	0-12
AC116	0-23	AD162 (HP)		BC150	0-18	BD139	0-55	BF195	0-12	OC22	0-38	2G372	0-17	2N2221	0-20	2N3391	0-14	2N4061	0-12
AC117K	0-20	AD163	0-55	BC151	0-20	BD140	0-60	BF196	0-14	OC23	0-42	2G374	0-17	2N2222	0-20	2N3391A	0-16	2N4062	0-12
AC122	0-12	AD1740		BC152	0-17	BD155	0-80	BF197	0-14	OC24	0-58	2G377	0-30	2N2368	0-17	2N3392	0-14	2N4284	0-17
AC125	0-17	AD1714	0-24	BC153	0-28	BD175	0-60	BF200	0-45	OC25	0-38	2G378	0-16	2N2369	0-14	2N3393	0-14	2N4285	0-17
AC126	0-17	AD1715	0-24	BC154	0-30	BD176	0-60	BF222	0-95	OC26	0-25	2G381	0-16	2N2369A	0-14	2N3394	0-14	2N4286	0-17
AC127	0-17	AD1716	0-24	BC157	0-18	BD177	0-65	BF257	0-45	OC28	0-50	2G382	0-18	2N23411	0-24	2N3395	0-17	2N4287	0-17
AC128	0-17	AD1717	0-24	BC158	0-12	BD178	0-65	BF258	0-80	OC29	0-50	2G401	0-30	2N23412	0-24	2N3402	0-21	2N4288	0-17
AC132	0-14	AD1718	0-35	BC159	0-12	BD179	0-70	BF262	0-55	OC36	0-50	2G417	0-25	2N2046	0-47	2N3403	0-21	2N4289	0-17
AC134	0-14	AD1724	0-30	BC160	0-45	BD180	0-70	BF262	0-55	OC41	0-20	2N388	0-25	2N2711	0-21	2N3404	0-28	2N4290	0-17
AC137	0-14	AD1725	0-25	BC161	0-50	BD185	0-65	BF263	0-65	OC42	0-24	2N388A	0-55	2N2712	0-21	2N3405	0-42	2N4291	0-17
AC141	0-14	AD1726	0-28	BC167	0-12	BD186	0-65	BF270	0-35	OC42	0-24	2N388A	0-55	2N2714	0-21	2N3414	0-15	2N4292	0-17
AC141K	0-17	AD1727	0-28	BC168	0-12	BD187	0-70	BF271	0-80	OC44	0-15	2N404	0-20	2N2904	0-17	2N3415	0-15	2N4293	0-17
AC142	0-14	AD1739	0-30	BC169	0-12	BD188	0-70	BF272	0-80	OC45	0-12	2N404A	0-20	2N2904A	0-21	2N3416	0-28	2N4294	0-12
AC142K	0-17	AD1778	0-50	BC170	0-12	BD189	0-75	BF273	0-85	OC72	0-10	2N524	0-42	2N2905	0-21	2N3417	0-25	2N4295	0-32
AC151	0-15	AD1779	0-50	BC171	0-14	BD190	0-75	BF274	0-35	OC72	0-14	2N598	0-42	2N2905A	0-21	2N3525	0-75	2N5458	0-32
AC154	0-20	AD180	0-50	BC172	0-14	BD195	0-85	BF270	0-35	OC72	0-14	2N598	0-42	2N2906	0-15	2N3648	0-09	2N5469	0-40
AC155	0-20	AD181	0-45	BC173	0-14	BD196	0-85	BF292	0-27	OC74	0-14	2N599	0-45	2N2906A	0-18	2N3702	0-10	2N8301	0-50
AC156	0-20	AD186	0-45	BC174	0-14	BD197	0-90	BF294	0-22	OC75	0-15	2N606	0-12	2N2907	0-20	2N3703	0-10	2N8302A	0-42
AC157	0-24	AD189	0-37	BC175	0-22	BD198	0-90	BF295	0-80	OC76	0-15	2N607	0-13	2N2907A	0-22	2N3704	0-11	2N8302	0-42
AC165	0-20	AL102	0-45	BC177	0-18	BD199	0-95	BF296	0-32	OC77	0-25	2N608	0-24	2N2908	0-15	2N3705	0-10	2N8303	0-55
AC166	0-20	AL103	0-45	BC178	0-18	BD200	0-95	BF297	0-32	OC77	0-25	2N609	0-24	2N2909	0-14	2N3706	0-09	2N8304	0-70
AC187	0-20	AS724	0-25	BC179	0-18	BD205	0-80	BF298	0-22	OC81D	0-15	2N706	0-08	2N2925	0-14	2N3707	0-11	2N8305	0-84
AC188	0-24	AS725	0-30	BC180	0-24	BD206	0-80	BF299	0-22	OC82	0-15	2N708A	0-09	2N2926 (G)		2N3708	0-07	2N8306	0-84
AC189	0-14	AS728	0-25	BC181	0-24	BD207	0-95	BF301	0-20	OC82D	0-15	2N708	0-12		0-12	2N3709	0-09	2N8307	0-84
AC176	0-20	AS729	0-25	BC182	0-10	BD208	0-95	BF302	0-20	OC83	0-20	2N711	0-10	2N2926 (V)		2N3710	0-09	2N8321	0-55
AC177	0-24	AS730	0-25	BC182L	0-10	BDY20	1.00	BF303	0-17	OC84	0-20	2N717	0-35			2N3711	0-09	2N8322	0-42
AC178	0-28	AS731	0-25	BC183	0-10	BDY20	1.00	BF304	0-15	OC84	0-20	2N717	0-35	2N2926 (O)		2N3819	0-28	2N8322A	0-42
AC180	0-17	AS734	0-25	BC184	0-12	BDY20	1.00	BF305	0-15	OC84	0-20	2N717	0-35	2N2926 (R)		2N3821	0-35	2N8324	0-70
AC180K	0-20	AS735	0-25	BC184L	0-12	BDY20	1.00	BF306	0-15	OC109	0-25	2N726	0-28	2N2926 (B)		2N3823	0-28	2N8325	0-70
AC181	0-17	AS736	0-25	BC186	0-28	BF121	0-45	BF307	0-15	OC171	0-25	2N743	0-20	2N2926 (S)		2N3903	0-28	2N8326	0-70
AC181K	0-20	AS737	0-25	BC187	0-28	BF123	0-45	BF308	0-15	OC200	0-28	2N914	0-14	2N3010	0-10	2N3905	0-28	2N8327	0-70
AC187	0-22	AS738	0-25	BC207	0-11	BF125	0-45	BF309	0-15	OC202	0-28	2N918	0-30	2N3011	0-17	2N3906	0-27	40361	0-40
AC187K	0-20	AS721	0-40	BC208	0-11	BF127	0-55	BF310	0-15	OC203	0-25	2N929	0-21	2N3053	0-14	2N4058	0-12	40382	0-45
AC188	0-28	BC108	0-09	BC109	0-11	BF152	0-45	BF311	0-15	OC203	0-25	2N929	0-21						
AC188K	0-28	BC108A	0-09	BC121L	0-11	BF153	0-45	BF312	0-15	OC204	0-25	2N930	0-21						
AC171	0-25	BC109	0-10	BC121L	0-11	BF154	0-45	BF313	0-15	OC205	0-35	2N1131	0-20						
AC174	0-20	BC113	0-10	BC124L	0-14	BF155	0-70	BF314	0-28	OC309	0-40	2N1132	0-22						
AC179	0-20	BC114	0-15	BC225	0-25	BF156	0-48	BF315	0-28	P349A	0-20	2N1302	0-14	AA119	0-08	BY133	0-21	OA10	0-35
AC180	0-20	BC115	0-16	BC226	0-35	BF157	0-55	BF316	0-25	P357	0-42	2N1303	0-14	AA120	0-08	BY164	0-50	OA47	0-07
AC181	0-20	BC116	0-15	BCY30	0-24	BF158	0-55	BF317	0-25	P357A	0-42	2N1304	0-17	AA121	0-08	BYX38/30		OA70	0-07
AC182	0-16	BC117	0-15	BCY31	0-25	BF159	0-60	BF318	0-25	CI11E	0-50	ORP12	0-42	AA122	0-08	BYX38/30		OA70	0-07
AC183	0-18	BC118	0-10	BCY32	0-30	BF160	0-40	BF319	0-25	U60	0-40	ORP60	0-40	AA123	0-09	BYZ10	0-42	OA79	0-07
AC184	0-19	BC119	0-30	BCY33	0-22	BF162	0-40	BF320	0-25	ORP61	0-40	2N1307	0-21	AA124	0-10	BYZ11	0-30	OA85	0-09
AC185	0-25	BC120	0-80	BCY34	0-25	BF163	0-40	BF321	0-25	BT140	0-12	2N1308	0-28	AA125	0-10	BYZ12	0-30	OA90	0-06
AC186	0-35	BC121	0-12	BCY35	0-14	BF164	0-40	BF322	0-25	BT141	0-17	2N1309	0-28	AA126	0-11	BYZ13	0-30	OA91	0-06
AC187	0-28	BC122	0-18	BCY36	0-18	BF165	0-40	BF323	0-25	BT142	0-17	2N1310	0-28	AA127	0-11	BYZ14	0-30	OA92	0-06
AC188	0-21	BC123	0-12	BCY37	0-14	BF167	0-22	BF324	0-25	BT143	0-20	2N1613	0-20	AA128	0-12	BYZ15	0-30	OA93	0-06
AC189	0-21	BC124	0-18	BCZ10	0-20	BF173	0-22	BF325	0-25	UT46	0-27	2N1711	0-20	AA129	0-12	BYZ16	0-30	OA94	0-06
AC190	0-28	BC125	0-12	BCZ11	0-25	BF176	0-35	BF326	0-25	C441	0-30	2G301	0-09	AA130	0-12	BYZ17	0-35	OA200	0-06
AC191	0-17	BC126	0-15	BCZ12	0-25	BF177	0-35	BF327	0-25	C442	0-30	2G302	0-18	AA131	0-12	BYZ18	0-35	OA202	0-07
AC192	0-18	BC127	0-15	BCZ13	0-25	BF178	0-35	BF328	0-25	C443	0-35	2G303	0-19	AA132	0-12	BYZ19	0-28	8D19	0-05
AC193	0-28	BC128	0-15	BCZ14	0-25	BF179	0-35	BF329	0-25	C444	0-35	2G304	0-19	AA133	0-12	BYZ20	0-28	8D19	0-05
AC194	0-38	BC129	0-15	BD121	0-60	BF178	0-35	BF330	0-25	C445	0-35	2G305	0-24	AA134	0-12	BYZ21	0-28	8D19	0-05
AD130	0-48	BC130	0-15	BD122	0-65	BF179	0-35	BF331	0-25	C446	0-35	2G306	0-24	AA135	0-12	BYZ22	0-28	8D19	0-05
AD140	0-48	BC131	0-30	BD123	0-65	BF180	0-30	BF332	0-25	C447	0-35	2G307	0-24	AA136	0-12	BYZ23	0-28	8D19	0-05
AD142	0-48	BC132	0-30	BD124	0-60	BF182	0-30	BF333	0-25	C448	0-35	2G308	0-24	AA137	0-12	BYZ24	0-28	8D19	0-05
AD143	0-38	BC133	0-30	BD125	0-65	BF183	0-30	BF334	0-25	C449	0-35	2G309	0-24	AA138	0-12	BYZ25	0-28	8D19	0-05
AD149	0-50	BC134	0-45	BD126	0-65	BF184	0-25	BF335	0-25	C450	0-35	2G310	0-24	AA139	0-12	BYZ26	0-28	8D19	0-05
AD181	0-33	BC147	0-10	BD136	0-40	BF185	0-30	BF336	0-25	C451	0-35	2G311	0-24	AA140	0-12	BYZ27	0-28	8D19	0-05

Cut these 3 pages out and keep for reference

### DIODES AND RECTIFIERS

AA119	0-08	BY133	0-21	OA10	0-35
AA120	0-08	BY164	0-50	OA47	0-07
AA121	0-08	BYX38/30		OA70	0-07
AA122	0-09	BYZ10	0-42	OA79	0-07
AA123	0-10	BYZ11	0-30	OA85	0-09
AA124	0-11	BYZ12	0-30	OA90	0-06
AA125	0-11	BYZ13	0-30	OA91	0-06
AA126	0-12	BYZ14	0-30	OA92	0-06
AA127	0-12	BYZ15	0-30	OA93	0-06
AA128	0-				

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	16A	30A
TO3	TO6	TO6	TO6	TO48	TO48	TO48	TO18
50	0-25	0-35	0-35	0-47	0-50	0-53	1-45
100	0-25	0-33	0-47	0-50	0-58	0-93	1-40
200	0-35	0-37	0-49	0-49	0-57	0-61	0-75
400	0-43	0-47	0-56	0-56	0-67	0-75	0-93
600	0-53	0-57	0-68	0-68	0-77	0-97	1-25
800	0-63	0-70	0-80	0-80	0-90	1-20	1-60

## SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
Case	TO-18						
50	0-04	0-05	0-05	0-07	0-14	0-21	0-00
100	0-04	0-06	0-06	0-13	0-16	0-23	0-75
200	0-05	0-09	0-09	0-14	0-20	0-24	1-00
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25
600	0-07	0-16	0-10	0-20	0-34	0-45	1-86
800	0-10	0-17	0-11	0-25	0-37	0-55	2-00
1000	0-11	0-25	0-14	0-30	0-46	0-63	2-50
1200	...	0-33	...	0-38	0-57	0-75	...

## TRIACS

VDOM	2A	6A	10A
TO-18	TO-66	TO-88	
5p	5p	5p	
100	30	50	76
200	50	60	90
400	70	75	1-10

FOR USE WITH TRIACS  
HR100 (D32) 37p each

## FREE

One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 1P1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G3478 OC78
T9	8 2G399A 2N1302
T10	8 2G4417 AF117

All 50p each pak

2N2080 NPN SIL. DUAL TRANS. CODED 25p TEXAS. Our price 25p each.

120 VCB MIXIE DRIVER TRANSISTOR. Sim. BRN21 & C407, 2N1892 FULLY TESTED AND CODED ND 120, 1-24 17p each. TO-5 N.P.N. 25p 15p each.

P.E. trans. suitable for S.I. Organ. Metal TO-18 Eqvt. ZTX300 5p each. Any Qty.

## POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP Coded G.P100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS—OC25-28 29-30-35-36. NKT 401-403-404-406-406-430-451-452-453. T13027-3028, 2N205A. 2N456A-457A-458A, 2N511 A & B. 2G220-222. ETC. VCO 80V VCEO 50V IC 10A PT. 20 WATTS HFE 30-170. PRICE 1-24 43p each 25-99 40p each 100 up 36p each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded E 2400 VCEO 150V VCEO 100V IC 6A/30 Watts. HFE type 20/IT 5MHz. OUR PRICE EACH: 1-24 25-99 50p 100 up 40p

AD161/162 PNP N/P COMP. GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mV (10-7 Case) 13p ea. 14W (Top Hat) 18p ea. 10W (SO-10 Stud) 25p ea. All fully tested. 5% tol. and marked. State voltage required.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each

NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS. 50 v RMS 32p each 100 v RMS 37p 400 v RMS 48p 100PIV 25p. Size 15 mm x 6 mm.

UNIUNCTION UT46. Eqvt. 2N2646, Eqvt. T1843. BEN3000 25p each, 25-99 25p 100PIV 25p.

CADMIUM CELLS ORP12 43p ORP50, ORP91 40p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N708/8. BSY-2728/85A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	5p
50	For	1-00
100	For	1-75
500	For	7-50
1000	For	13-00

SIL. G.P. DIODES 5p 300mW 30 50 401V (Min.) 100 150 Sub-Min. 500 5-00 Pull Tested 1,000 9-00 Ideal for Organ Builders.

2N3055 115 WATT SIL POWER NPN 50p EACH

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

SILICON 50 WATTS MATCHED PNP/PNP BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCEO 100V VCEO 50V IC 10A. HFE type 100/t 3mHz. OUR PRICE PER PAIR: 1-24 60p 25-99 55p 100 pps. 50p

## KING OF THE PAKS Unequaled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-50
U 2	60 Mixed Germanium Transistors AF/RF	0-50
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-50
U 4	40 Germanium Transistors like OC81, AC128	0-50
U 5	60 200mA Sub-Min. Silicon Diodes	0-50
U 6	30 Sil. Planar Trans. NPN like B8Y95A, 2N706	0-50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0-50
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-50
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-50
U 10	20 BA50 charge storage Diodes DO-7 Glass	0-50
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1152, 2N2904	0-50
U 12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-50
U 13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-50
U 14	150 Mixed Silicon and Germanium Diodes	0-50
U 15	25 NPN Sil. Planar Trans. TO-5 like B8Y61, 2N697	0-50
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-50
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-50
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-50
U 19	25 Silicon NPN Transistors like BC108	0-50
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-50
U 21	30 AF Germanium Alloy Transistors 2G300 Series & OC71	0-50
U 22	30 MADT's like MHz Series PNP Transistors	0-50
U 23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-50
U 24	25 300 MHz NPN Silicon Transistors 2N708, B8Y27	0-50
U 25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-50
U 26	30 NKT Germanium AF Transistors TO-1 like AC127	0-50
U 27	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1-00
U 28	15 Plastic Silicon Planar Trans. NPN 2N2926	0-50
U 29	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-50
U 30	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-50
U 31	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-50
U 32	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0-50
U 33	25 Silicon Planar Transistors PNP TO-18 2N2906	0-50
U 34	25 Silicon Planar NPN Transistors TO-5 B8Y60/51/52	0-50
U 35	30 Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0-50
U 36	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0-50
U 37	30 RF, Germ. PNP Transistors 2N1303/5 TO-5	0-50
U 38	10 Dual Transistors 6 lead TO-5 2N2060	0-50
U 39	25 RF Germanium Transistors TO-5, OC45, NKT72	0-50
U 40	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0-50
U 41	25 Sil. Trans. Plastic TO-18 AF. BC113/114	0-50
U 42	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-50
U 43	7 3A SCR. TO-6 up to 600PIV	1-00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP x25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

F.E.T.'S 2N3819 35p 2N458 50p 2N3820 50p 2N5459 40p 2N3821 35p BFW10 40p 2N3823 30p MPP105 40p

## NEW EDITION 1971

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 80p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

SILICON 50 WATTS MATCHED PNP/PNP BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCEO 100V VCEO 50V IC 10A. HFE type 100/t 3mHz. OUR PRICE PER PAIR: 1-24 60p 25-99 55p 100 pps. 50p

## QUALITY TESTED SEMICONDUCTORS

Pak No.	Contents	Price
Q1	20 Red spot transistors PNP	0-50
Q2	16 White spot R.F. transistors PNP	0-50
Q3	4 OC 77 type transistors	0-50
Q4	6 Matched transistors OC44/45/81/81D	0-50
Q5	5 OC 75 transistors	0-50
Q6	4 AC 128 transistors PNP high gain	0-50
Q7	4 AC 126 transistors PNP	0-50
Q8	7 OC 81 type transistors	0-50
Q9	7 OC 71 type transistors	0-50
Q10	2 AC 127/128 Complementary pairs PNP/NPN	0-50
Q11	3 AF 116 type transistors	0-50
Q12	3 AF 117 type transistors	0-50
Q13	3 OC 171 H.F. type transistors	0-50
Q14	7 2N2928 Sil. Epoxy transistors mixed colours	0-50
Q15	2 GET880 low noise Germanium transistors	0-50
Q16	5 PNP 2 x ST 141 & 3 x ST 140	0-50
Q17	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-50
Q18	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-50
Q19	4 OC 44 Germanium transistors A.F.	0-50
Q20	4 AC 127 NPN Germanium transistors	0-50
Q21	20 NKT transistors A.F. H.F. coded	0-50
Q22	10 OA 202 Silicon diodes sub-min.	0-50
Q23	8 OA 81 diodes	0-50
Q24	15 IN914 Silicon diodes 75 PIV 75mA	0-50
Q25	8 OA95 Germanium diodes sub-min IN69	0-50
Q26	2 10A PIV Silicon rectifiers IN425R.	0-50
Q27	2 Silicon power rectifiers BYZ 13	0-50
Q28	4 Silicon transistors 2 x 2N696, 2N708	0-50
Q29	7 Silicon switch transistors 2N706 NPN	0-50
Q30	6 Silicon switch transistors 2N708 NPN	0-50
Q31	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0-50
Q32	1 Silicon NPN transistors 2N1711	0-50
Q33	7 Silicon NPN transistors 2N2369, 500MHz (code P307)	0-50
Q34	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0-50
Q35	7 2N3546 TO-18 plastic 300 MHz NPN	0-50
Q36	3 2N3063 NPN Silicon transistors	0-50
Q37	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0-50

## ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales: Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and e Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and Instructions. Price each: 23 35

## INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	-12 x 7400	0-50	UIC46	-5 x 7446	0-50	UIC86	-5 x 7486	0-50
UIC01	-12 x 7401	0-50	UIC47	-5 x 7447	0-50	UIC87	-5 x 7487	0-50
UIC02	-12 x 7402	0-50	UIC48	-5 x 7448	0-50	UIC88	-5 x 7488	0-50
UIC03	-12 x 7403	0-50	UIC50	-12 x 7450	0-50	UIC92	-5 x 7492	0-50
UIC04	-12 x 7404	0-50	UIC51	-12 x 7451	0-50	UIC93	-5 x 7493	0-50
UIC05	-12 x 7405	0-50	UIC53	-12 x 7453	0-50	UIC94	-5 x 7494	0-50
UIC06	-8 x 7406	0-50	UIC54	-12 x 7454	0-50	UIC95	-5 x 7495	0-50
UIC07	-8 x 7407	0-50	UIC56	-12 x 7456	0-50	UIC96	-5 x 7496	0-50
UIC10	-12 x 7410	0-50	UIC59	-8 x 7459	0-50	UIC100	-5 x 74100	0-50
UIC13	-8 x 7413	0-50	UIC72	-8 x 7472	0-50	UIC121	-5 x 74121	0-50
UIC20	-12 x 7420	0-50	UIC73	-8 x 7473	0-50	UIC141	-5 x 74141	0-50
UIC30	-12 x 7430	0-50	UIC74	-8 x 7474	0-50	UIC151	-5 x 74151	0-50
UIC40	-12 x 7440	0-50	UIC75	-8 x 7475	0-50	UIC154	-5 x 74154	0-50
UIC41	-5 x 7441	0-50	UIC76	-8 x 7476	0-50	UIC193	-5 x 74193	0-50
UIC42	-5 x 7442	0-50	UIC79	-5 x 7479	0-50	UIC199	-5 x 74199	0-50
UIC43	-5 x 7443	0-50	UIC81	-5 x 7481	0-50			
UIC44	-5 x 7444	0-50	UIC82	-5 x 7482	0-50			
UIC45	-5 x 7445	0-50	UIC83	-5 x 7483	0-50			

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593.

OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.

Please note that as from April 1st 10% must be added to all prices.

# the lowest prices!

## 74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

	1	25	100+	1	25	100+	1	25	100+
SN7400	0.15	0.14	0.12	SN7450	0.15	0.14	0.12	SN74123	£2.80
SN7401	0.15	0.14	0.12	SN7451	0.15	0.14	0.12	SN74141	0.87
SN7402	0.15	0.14	0.12	SN7453	0.15	0.14	0.12	SN74145	£1.50
SN7403	0.15	0.14	0.12	SN7454	0.15	0.14	0.12	SN74151	0.90
SN7404	0.15	0.14	0.12	SN7455	0.15	0.14	0.12	SN74153	£1.20
SN7405	0.15	0.14	0.12	SN7456	0.15	0.14	0.12	SN74154	0.80
SN7406	0.25	0.24	0.20	SN7457	0.29	0.28	0.24	SN74155	£1.40
SN7407	0.35	0.31	0.28	SN7458	0.37	0.35	0.32	SN74156	£1.40
SN7408	0.18	0.17	0.16	SN7459	0.45	0.43	0.42	SN74157	£1.90
SN7409	0.18	0.17	0.16	SN7460	0.45	0.43	0.42	SN74158	£1.80
SN7410	0.15	0.14	0.12	SN7461	0.67	0.64	0.63	SN74159	£1.80
SN7411	0.25	0.24	0.20	SN7462	£1.20	£1.15	£1.08	SN74160	£2.40
SN7412	0.35	0.31	0.28	SN7463	0.87	0.86	0.85	SN74161	£2.40
SN7413	0.29	0.28	0.24	SN7464	0.87	0.86	0.85	SN74162	£2.40
SN7414	0.48	0.40	0.38	SN7465	£1.10	£1.05	£0.98	SN74163	£2.40
SN7417	0.43	0.40	0.38	SN7466	£1.00	0.95	0.90	SN74164	£2.25
SN7420	0.15	0.14	0.12	SN7467	£3.80	£3.50	£3.40	SN74165	£2.25
SN7422	0.50	0.48	0.45	SN7468	0.32	0.31	0.30	SN74166	£2.25
SN7423	0.50	0.48	0.45	SN7469	£5.50	£5.25	£5.00	SN74167	£1.80
SN7425	0.50	0.48	0.45	SN7470	0.87	0.84	0.83	SN74168	£2.40
SN7427	0.45	0.42	0.40	SN7471	£1.00	0.95	0.90	SN74169	£2.40
SN7428	0.70	0.65	0.60	SN7472	0.87	0.84	0.83	SN74170	£2.40
SN7430	0.15	0.14	0.12	SN7473	0.87	0.84	0.83	SN74171	£2.40
SN7432	0.45	0.42	0.40	SN7474	0.77	0.74	0.73	SN74172	£2.40
SN7433	0.90	0.75	0.70	SN7475	0.77	0.74	0.73	SN74173	£2.40
SN7437	0.84	0.82	0.80	SN7476	0.87	0.84	0.83	SN74174	£1.95
SN7438	0.64	0.62	0.60	SN7477	£1.65	£1.60	£1.55	SN74175	£1.90
SN7440	0.15	0.14	0.12	SN7478	0.87	0.84	0.83	SN74176	£2.40
SN7441	0.87	0.84	0.82	SN7479	0.87	0.84	0.83	SN74177	£2.40
SN7442	0.87	0.84	0.82	SN7480	0.87	0.84	0.83	SN74178	£2.40
SN7443	£1.30	£1.25	£1.20	SN7481	0.40	0.38	0.36	SN74179	£2.40
SN7444	£1.30	£1.25	£1.20	SN7482	0.55	0.53	0.50	SN74180	£2.40
SN7445	£1.80	£1.77	£1.75	SN7483	£1.18	£1.15	£1.10	SN74181	£2.40
SN7446	0.87	0.84	0.82	SN7484	£1.18	£1.15	£1.10	SN74182	£2.40
SN7447	£1.00	0.97	0.95	SN7485	£1.40	0.37	0.34	SN74183	£2.40
SN7448	£1.00	0.97	0.95	SN7486	£1.40	£1.30	£1.10	SN74184	£2.40



## BI-PAK DO IT AGAIN!

### 50W pk 25w (RMS)

0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER

## THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than 0.1% at 1KHz.

★ Signal to noise ratio 80dB.

ONLY  
**£3.25p** each


★ Supply voltage 10—35 Volts.

★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.  
FULLY BUILT — TESTED — GUARANTEED.



## STABILISED POWER MODULE SPM80

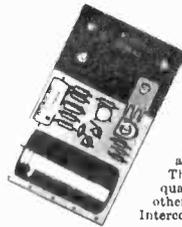

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 25 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2.95**

TRANSFORMER BMT80 £1.95 p. & p. 25p.

## STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

### SPECIFICATION

Frequency Response	20Hz — 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs: 1. Tape Head	1-25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1-5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. Input—equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than — 65dB
Input overload	+ 25dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £11.95  
SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23.00 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006  
Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail.  
Minimum order 30p. Cash with order please.  
Guaranteed Satisfaction or Money Back

## LINEAR I.C.'s—FULL SPEC.

Type No.	Price	1-24	25-99	100 up
BP 201C—81201C	83p	53p	45p	
BP701C—81701C	83p	50p	45p	
BP 702C—81702C	83p	50p	45p	
BP 702—72702	53p	45p	40p	
BP709—72709	36p	34p	30p	
BP 709P—7A709C	36p	34p	30p	
BP 710—72710	44p	42p	40p	
BP 711—7A711	45p	43p	40p	
BP 741—72741	75p	80p	50p	
7A708C—7A703C	28p	26p	24p	
TAA 263—	70p	60p	55p	
TAA 293—	90p	75p	70p	
TAA 360	170p	165p	150p	

G.S.G. EA1000 2-63

## ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	Price	1-24	25-99	100 up
BP930	12p	11p	10p	
BP932	13p	12p	11p	
BP933	18p	12p	11p	
BP935	18p	12p	11p	
BP936	13p	12p	11p	
BP944	18p	12p	11p	
BP945	25p	24p	22p	
RP946	12p	11p	10p	
BP948	25p	24p	22p	
BP951	65p	60p	55p	
BP952	12p	11p	10p	
BP9093	40p	38p	35p	
BP9094	40p	38p	35p	
BP9097	40p	38p	35p	
BP9099	40p	38p	35p	

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

## NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3016F Minitron
Anode voltage (Vdc)	170min	175min	0
Cathode Current (mA)	2.3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All Indicators C-9 + Decimal point. All side viewing. Full data for all types available on request.

## RTL MICROLOGIC CIRCUITS

	Price each	1-24	25-99	100 up
Epoxy TO-5 case				
uL900 Buffer	35p	33p	27p	
uL914 Dual 2/p gate	35p	33p	27p	
uL923 J-K flip-flop	50p	47p	45p	

Date and Circuits Booklet for IC's Price 7p.

## DUAL IN LINE SOCKETS.

14 & 16 Lead Sockets for use with

DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PRICE TYPE No.	1-24	25-99	100up.
TSO 14 pin type	80p	87p	25p
TSO 16 .....	35p	32p	30p

LOW COST No.

BPS 14	15p	13p	11p
BPS 16	16p	14p	12p

# SURPLUS BARGAINS

**INDICATOR C.R.T. 8129** contains tube 3-5" green med persistence, 21 min valves, complete in case size 10 x 10" front 20" deep, this unit contains internal E.H.T. and heater trans for 230v mains, reqs ext 300v DC H.T. Modern well made unit well suited to scope conversion. Good condition. £9.75.

**CONTROL UNIT CAMERA.** Contains meter 2 1/2" dia FSD I Ma special scale markings, 3 x toggle swts, 2 x Ind lamps, push swt etc. supplied in fitted wooden transit case. New condition. £1-85.

**NAVY Rx** type B40 range 640 Kc to 30 Mc/s in 5 bands have int mains P.U. and Spk, xtal cal etc. Supplied tested with circ. Few only £27-00.

**SELECTOR UNIT** Contains meter I Ma scale 0 to 1 and 0 to 180, motor 24v DC with gears, this drives multiway swt also 13 relays, swts, etc. All in useful case size 12 x 6 x 7" £2-60.

**IND UNIT CRT 26** small ind with tube 2-75" with PDA green screen med persis. O.K. for scope use, 7 min valves. All in case size 8 x 8" front 13" deep. Tube connections supplied. £4-10.

**Ae COUPLING UNITS.** Cover range 2 to 5.7 Mc/s intended to match 80 ohm O/P to long wire, contain 2 R.F. ameters, 2 variable inductors with counting dials in plywood cases with circ. £3-00.

**METERS 50 Ua** FSD scale 0 to 3, 30 or 300 sq case 3 x 2 1/2" £1-35. Also 500 Ua scale 0 to 5 size 2 1/2" OSD £1-10. Also on panel 500 Ua scale 0 to 5 size 1 1/2" OSD on panel with swt £1.

**INST SWTS** 2 pole 23 way 2 bank 70p. **CONDS.** -1 uf 1-% 2 for 60p. **POT CORES** 1 1/2 x 1/2" 2 for 60p. **FUSE HOLDERS** miniature type 3 for 30p. **HEAT SINKS** size 1 1/2 x 9 x 1 1/2" ready drilled for 4 T.O.3 types with 4 I ohm res £1-00. **IND 208.** This is a repeater ind with tube 2-75" dia, green med persis with base shield and front plate base conn and volts req. supplied with scan burns £1-55. **TEST UNIT** contains 2 vinkors, 4 Sil transis 15v zener, 4 miniature relays, 3 min valves pots conds. etc. New condition 85p. **BLOWER MOTORS** double ended type 24v DC new £1-60. **SPEAKER UNITS P.A.** type speaker 8 ohm in case size 9 x 9 x 8" with 600 ohm line trans suitable outdoor use. Good condition. £2-75. **BATTERIES** 6 volt lead acid type metal cased 40 amp/hr, size 10 x 9 x 5". New with filling inst. £2-75 **DYNAMOTOR UNITS** 12v DC in 220v 100 Ma DC O/P fully enclosed for TCS Rx £1-50, also 12v in 440v 200 Ma O/P £2-00. **DIODES 800 P.I.V.** 1 amp. New 12 for £1-00. **DIODES 200 P.I.V.** 8 amps ZR22 type 4 for 60p. **TRIMMERS** 20pf air spaced ceramic. New 10 for 50p or £4-00 per 100. Also 10/110 pf ceramic dielectric 5 for 50p. **METER UNIT** part of nav display centering type scale L & R as two coils on magnet enables reading to be controlled from two circs. New condition with circ. 95p. Also available cross pointer ind part of R1155 Rx as two movements of 115 Ua ea. £1-40. **TAG STRIPS** solder type 24 way new 10 for 25p. **VIDICONS** camera tubes E.E. and E.M.I. types graded according to scan marks £9-00 grade A. £6-00 grade B. **JOY STICK CONTROLLERS** give control in N, S, E and W directions with 1 pole c/o micro swts. £1-20 **TRANSFORMERS.** All 230 50 c/s Pria as follows: Sec 1125-O-1125V at 565 Ma. New boxed £7-00. Sec 415-143-0-143-415 at 360 Ma on 415v and 120 Ma on 143v. New boxed £3-00. Sec 350-310-0-310-350 at 220 Ma, 5v 6a, 6-3 5a, 6-3 3a twice and 6-3 1a twice £2-65. Also Pria 210/250 Sec 27v at 41 amps cont new £11-00 **VALVES** 5U4, 6X5, 6X4, 12AT7, 85A2, OB2, 12AX7, 6BH6, 6AK5, 6AK6, 6SN7, 6SK7, 6SJ7, 6H6, 12AU7, 6BA6, 6A56, any 3 for 50p.

**CIRCUIT DIAGRAMS.** R1155, B, F, L, N with values 50p. R1392, R1475 30p. CT38 50p. Scopes CD 518 (CT316), 13a, 1035 Mk. 1, 2, 3, 1049 Mk 3 all 50p. Rx B40 50p. Rx STC R4187 set of circs and parts list £1-00. Sig gens TF144G with values 50p. TF801a with values 75p

All goods ex equipment unless stated otherwise. The above prices include carriage or postage for U.K. mainland. S.A.E. with enquiry.


## A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL
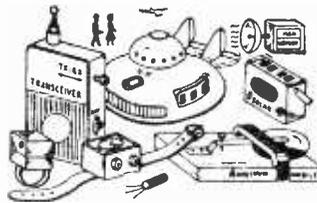
# PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

**CONTENTS:** (1) 2 Copper Laminate Boards 4 1/2in x 2 1/2in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 60 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements.



EXPERIMENTER'S  
PRINTED CIRCUIT KIT  
70p

Postage & Pack. 10p (UK)  
Commonwealth:  
SURFACE MAIL 15p  
AIR MAIL 60p  
Australia, New Zealand,  
South Africa, Canada

- (1) Crystal Set with bi-wire Detector. (2) Crystal Set with voltage-quadrupler detector.
- (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier.
- (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex.
- (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World.
- (10) Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62in x 0-95in x 0-25in. (11) Wristwatch Radio 1-15in x 0-80in x 0-55in. (12) Ring Radio 0-70in x 0-70in x 0-55in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV. Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. (41) Light Dimmer. (42) I.C. Pre-amplifier. (43) I.C. Amplifier. (44) I.C. Intercom. (45) I.C. Radio. (46) Raudive Voices Receiver. (47) Biofeedback Amplifier. (48) Brainwave Detector. (49) Proximity Switch. (50) Laser Projector.
- Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.

**YORK ELECTRICS, Mail Order Dept.**  
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.

# Lasky's Audio-Tronics Catalogue 1973

The great 1973 edition of Lasky's famous Audio-Tronics catalogue is available - FREE on request. The 48 newspaper size pages - many in full colour - are packed with 1,000s of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio Accessories. See the great new Lasky's Credit Plan Scheme - enabling you to buy your ideal choice of equipment on easy terms.

**FREE**

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

.....


PW2

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1



"Where can I get exclusive units at lowest prices?..."

**ROC ELECTRONICS!**

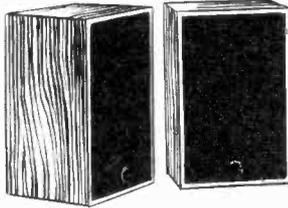

**R.088 MATCHED STEREO LOUD SPEAKERS.** Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9.50 pair.** Normal Price £10.75.

**REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500**

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner aux mono monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz - 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA, tuner aux 250mV. Hum and noise: phono - 50db, tuner/aux - 65db. **ROC PRICE £35.20** Normal Price £55.00



As reviewed in "POPULAR HI-FI" February 1972



**OLSON RA-310 AM/FM/MPX STEREO TUNER**  
This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM 87-108 MHz; AM 525-1605 kHz. FM Sensitivity: FM 3µV, AM 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

**REALISTIC SA-100B 6 WATT STEREO AMPLIFIER**

Here's fabulous, exciting value in miniature! This high quality stereo amplifier measures only 3" wide, 3" high - 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are oiled walnut with matching enamelled metal top. The front panel is satin aluminium and walnut brown enamel. Frequency response is 50 to 10,000 Hz - 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.



**ROC PRICE £12.45** Normal Price £21.00



**TEC HR-007 HEAD-PHONE RADIO**  
When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW. **Normal Price £7.50 ROC PRICE £5.80**



**EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE**  
Here's your opportunity to own a transcription cartridge for the price of a ceramic! Is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: -1dB. Channel separation: 28dB. Compliance: 12 - 10.6 cm/dyne. **ROC PRICE £6.37**



**OLSON AM-395 40-WATT STEREO AMPLIFIER**  
An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3mV RIAA, crystal phono 100mV, tape 160mV, tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!



**R.446 3-WAY MATCHED SPEAKERS**  
These will do justice to your amplifier - and to your pocket! At only £20.00 a pair, they are real value for money. Each cabinet is heavily lagged and leak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a 6 1/2" base unit plus tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.



**A-3000 36-WATT SOLILO STATE STEREO AMPLIFIER**  
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux, Tape Play. Size: 345mm x 300mm x 130mm.

**CONSTRUCTORS KITS**

**TWO TRANSISTOR RADIO KIT**  
Complete with solar cell **£2.50**

**10 PROJECT INTEGRATED CIRCUIT KIT**  
Build a radio, morse key etc. **£3.50**

**SOLAR ELECTRONIC KIT**  
20 ways of harnessing the sun's energy **£4.50**

**TWO OCTAVE ELECTRONIC ORGAN KIT**  
Make your own music. Complete with speaker. **£4.50**



**ROC PRICE £20.00** Normal Price £27.00 per pair.




**OLSON AM-400 4 WATT STEREO AMPLIFIER**  
Here's marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz - 3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV, tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.




**25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-5B**  
This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units: an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.



**PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16**  
This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz; AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

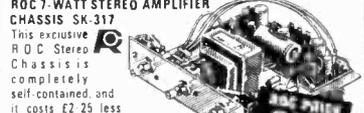

**ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317**  
This exclusive R.O.C. Stereo Chassis is completely self-contained and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 12" high and 6 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45dB.

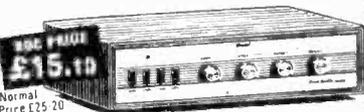

**OLSON AM-372 16-WATT STEREO AMPLIFIER**  
Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV, Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

**ROC ELECTRONICS LTD**

M. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211  
CALLERS WELCOME 9-6 MON. TO SAT.  
ALSO AT 87 TOTTENHAM COURT RD, LONDON W7  
TEL: 01-580 37 39 OPEN 9-6 MON.-FRI, SAT. 9-1



Return-of-post mail order service from Edgware Rd. Orders over £10 post free (UK only). Add 25p for p. & p. for orders under £10. HP terms available for callers.


# BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
THE VALVE SPECIALISTS Telephone 6743

OA2	.30	6V16	.39	8N7GT	.40	12SJ7	.23	50L6GT	.45	FA8C80	.29	EF85	.25	KT44	1.00	PL83	.80	UL41	.54	AC128	.20	BC118	.23	OA70	.15
OB2	.30	6BQ7A	.38	6Q7GT	.43	12SK7	.24	6SA2	.43	EAC91	.38	EF86	.27	KT66	.80	PL84	.28	UL84	.28	AC132	.20	BC110	.45	OA73	.15
OZ4	.25	5BR7	.79	6Q7(M)	.43	12SQ7	.50	85A3	.40	EAF42	.48	EF91	.17	KT81	2.00	PL504/500	UM80	.33	AC164	.25	BCY12	.50	OA79	.09	
LA3	.23	6BR8	.63	6I7G	.35	14H7	.48	90C1	.59	EAF801	.50	EF92	.28	KTW61	.83	PL505	1.30	UY80	.58	AC156	.20	BCY33	.20	OA81	.38
1A7GT	.32	6BR7	1.25	6I7M	.55	14S7	.75	90CG	1.70	EB34	.20	EF93	.65	KTW63	.50	PL508	.90	UI0	.45	AC165	.25	BCY38	.23	OA90	.18
1B3GT	.35	6BW6	.72	6SA7M	.35	19AQ5	.24	1501B2	.58	EB91	.10	EF183	.27	MHL67	.75	PL509	1.30	UI2/14	.38	AC166	.25	BCY39	.25	OA91	.18
1H5GT	.33	6BW7	.50	6S7GT	.33	19A6	.50	807	.59	EB81	.48	EF184	.27	MHL67	.75	PL509	1.30	UI2/14	.38	AC166	.25	BCY39	.25	OA91	.18
1L4	.13	6BZ6	.31	6S7T	.33	2014	1.05	5702	.90	EB81	.48	EH90	.34	PA1	.42	PL802	.75	UI9	1.73	AC168	.38	BCZ11	.38	OA95	.09
1N5GT	.37	6CB6A	.26	6SH7	.53	20P2	.65	5763	.50	EBF80	.30	EL32	.18	PAC80	.32	PM84	.31	U22	.39	AC176	.55	BF158	.29	OA200	.09
1R5	.26	6C4	.28	6S7J	.53	20L1	.98	7475	.70	EBF83	.38	EL34	.44	PC86	.44	PY372	.50	U25	.62	AC177	.28	BF159	.25	OA203	.10
1R4	.22	6C9	.73	6SK7GT	.23	20P1	.50	AC/PEN	.98	EBF89	.26	EL35	1.00	PC88	.44	PY80	.60	U26	.58	AC178	.28	BF160	.20	OC29	.38
1U4	.22	6D9G	1.06	68Q7GT	.38	20P3	.76	AC/PEN	.98	EBL21	.60	EL38	.38	PC89	.42	PY81	.24	U27	.58	AC178	.28	BF160	.20	OC29	.38
1U5	.48	6C8A	.50	6U4GT	.60	20P4	.89	DD	.98	EC36	.59	EL39	.44	PC89	.42	PY81	.24	U27	.58	AC178	.28	BF160	.20	OC29	.38
1D21	.25	6C8E	.38	6V8G	.17	20P5	1.00	AC/PEN	.98	EC38	.59	EM81	.37	PC86	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
2GK5	.50	6CL6	.43	6V6GT	.27	25A6G	.29	AC/TH1	.50	EC92	.34	EM83	.75	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
3A4	.25	6C17	.50	6X4	.20	25L6G	.20	AC/TP	.88	EC93	1.50	EM84	.31	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
3D6	.25	6C55	.30	6X5GT	.25	25V5G	.43	AL60	.78	EC95	.95	EM85	1.00	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
3Q4	.38	6CW4	.63	7186	.58	25Z4G	.28	ATP4	.12	EC90	.60	EM87	.34	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
3Q5GT	.35	6D7E	.50	7187	.58	25Z5	.40	AZ1	.16	EC91	.61	EM87	.34	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
3S4	.33	6D7A	.50	7187	.58	25Z6G	.43	AZ1	.16	EC92	.61	EM87	.34	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
4C8E	.50	6FV6	.55	7187	.58	25Z6G	.43	AZ1	.16	EC92	.61	EM87	.34	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
5C18	.50	6E5	.55	7Y4	.60	30C15	.55	CL33	.90	EC94	.38	EM84	.31	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
5T4	.30	6F1	.59	7Z4	.50	30C17	.74	CV63	.53	EC95	.32	EM85	1.00	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
5U40	.30	6V6	.63	9HW6	.50	30C18	.58	CV18	.53	EC95	.32	EM85	1.00	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
5V40	.33	6V13	.33	917	.78	30F5	.81	CV31	.29	EC91	.61	EM87	.34	PC87	.44	Q875/20	.63	UI11	.44	ADT140	.63	BY114	.18	OC70	.13
5Y3GT	.25	6F14	.40	10C2	.49	30F11	.58	DAF91	.20	EC90	.70	EZ41	.42	PD500	1.44	UBF89	.28	2N2147	.23	AF239	.38	GT119	.20	OC83	.20
5Z1G	.33	6F18	.45	10D4E7	.50	30F12	.58	DAF96	.33	EC90	.70	EZ41	.42	PD500	1.44	UBF89	.28	2N2147	.23	AF239	.38	GT119	.20	OC83	.20
5Z4GT	.38	6F23	.65	10P1	.75	30F12	.67	DC90	.60	EC92	.65	EZ81	.20	PC91	1.38	UC92	.35	2N2053	.33	BA116	.25	GT973	.15	OC139	.23
6J01E2	.53	6A24	.68	10P9	.45	30F13	.47	DF91	.14	ECF86	.64	GV501	.75	PCN45	.40	UC93	.38	2N3053	.33	BA116	.25	GT973	.15	OC139	.23
6A8G	.33	6P25	.51	10F18	.35	30F14	.66	DP96	.34	ECF804	.GZ22	.39	PCN45DD	UC93	.38	2N3121	2.50	BA129	.13	GT987	.23	OC169	.23		
6A17	.15	6P28	.80	10D11	.53	30F15	.55	DH76	.28	2.10	GZ33	.70	PCN45	.75	UCF80	.31	2N3703	.19	BA130	.10	GT987	.23	OC169	.23	
6A15	.25	6P32	.15	10P13	.54	30F17	.65	DK40	.55	ECH21	.63	GZ34	.47	PCN46	.20	UCH21	.60	2N3709	.20	BA153	.15	GT988	.23	OC200	.22
6A16	.50	6H18A	.50	10P14	1.05	30F18MR	.95	DK92	.35	ECH35	.50	GZ37	.67	PCN45DD	UCH42	.57	2N3988	.50	BC107	.13	MI	.15	OC201	.38	
6A15	.75	6K15	.50	12A5	.63	30F12	.67	DC90	.60	ECH42	.57	HABC80	.44	PCN45	.98	UCH81	.29	2S23	.50	BC108	.13	OA5	.28	OC203	.30
6AK5	.25	6U7	.50	12ACG	.40	30F19	.DL92	.23	ECH81	.25	HL23DD	.40	PCNDD	.98	UCH82	.30	AA119	.15	BC113	.15	OA9	.13	OC200	.30	
6AK6	.30	616GT	.15	12AD6	.40	30P4	.55	DL96	.35	ECH83	.38	HL41DD	.98	4020	.88	UCH83	.48	AA129	.15	BC115	.15	OA10	.43	OC205	.43
6AM8A	.50	6J54	.19	12AE6	.48	3CP14	.57	DM70	.30	ECH84	.34	HL42DD	.50	PF1200	.50	UF41	.60	AA129	.15	BC116	.25	OA47	.10	ORP12	.53
6AN8	.49	6J5GT	.29	12AF7E	.23	30P13	.75	DM71	.38	ECL80	.28	HN309	1.40	PL33	.38	UF42	.60	AA129	.15	BC116	.25	OA47	.10	ORP12	.53
6A05	.21	6J6	.18	12AV6	.21	30P14	.62	DY87/6	.22	ECL82	.28	HVR2	.53	PL36	.46	UF80	.35	AC107	.15	LP15	(AC113, AC154, AC157, AA120)	53p			
6AR5	.30	6J74	.24	12AV7E	.28	30P15	.87	DY89	.29	ECL83	.52	HVR2A	.53	PL81	.42	UF85	.34	AC113	.15	per pack, 1—OC81D & 2—OC81, 43p.					
6AT6	.18	6J7(M)	.38	12BA6	.30	35A3	.48	EN8CC	1.65	ECL84	.54	KT2	.25	PL81A	.48	UF86	.53	AC127	.17	1—OC44 & 2—OC45, 43p. 1—OC81D & 2—OC82, 48p. Net of 3—OC83, 53p.					
6AU6	.19	6J8A	.50	12BE6	.30	35105	.70	ER8F	1.20	ECL85	.54	KT41	.98	PL82	.28	UF89	.27	AC127	.17						
6AV6	.28	6K7G	.10	12B17	.27	35L6GT	.42	EB8F	1.20	ECL86	.33														
6AW8A	.54	6K8G	.16	12J7GT	.33	35V4	.23	EB8CC	.60	EP22	.63														
6AX4	.39	6L1	.98	12K5	.50	35Z4GT	.24	EP2CC	.40	EP40	.49														
6B9G	.13	6L6GT	.39	12K7GT	.34	35Z5GT	.30	E180F	.90	EP41	.33														
6BA6	.19	6L7	.38	12J7GT	.23	50C3	.32	E182CC1	.00	EP42	.75														
6BC8	.50	6L18	.44	128C7	.35	50C1DG	.E1148	.53	EP73	.75															
6BE6	.20	6L19	1.38	128G7	.35	50C2G	.21	E1A50	.27	EP80	.81														
6BH6	.43	6L20	.48	128H7	.15	50E15	.55	E1A76	.88	EP93	.54														

All goods are unused, boxed, and subject to the standard 90 day guarantee. Terms of business — 49 Cash or cheque with order only. Post/packing 3p. per item, subject to a minimum of 9p. per order. 58 Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p. extra per order. Complete catalogue with conditions of sale price 7p. post paid. Business hours Mon.-Fri. 9-5.30 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested!" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.
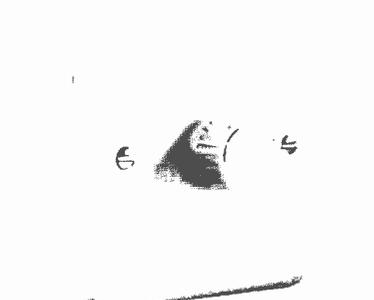
## Vary the strength of your lighting with a DIMMASWITCH




The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescent at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression: 600 Watt £2.20\* Kit Form £2.70\* 300 Watt £2.70\* Kit Form £2.20\*

All plus 10p post and packing. \*from 1st April please add appropriate percentage of V.A.T. increase. Please send C.W.O. to:—

**DEXTER & COMPANY**  
2 ULVER HOUSE, 19 KING STREET,  
CHESTER CH1 2AH Tel: 0244-25883

## VEROBOARD

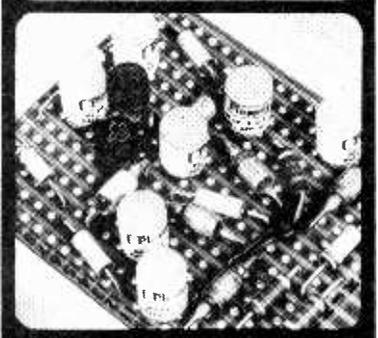

**VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK**  
0.1" and 0.15" pitch, plain and copper clad universal circuit boards.  
AVAILABLE FROM YOUR LOCAL RETAILER



## SAVE TIME AND MONEY

LIST PRICE £6.25 | OUR PRICE £4.84



As supplied by us to SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21 1/2" x 11 1/2" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. NEW as illustrated OUR PRICE ONLY £4.84 plus 8p carriage on orders less than £10. Money back guarantee. SEND FOR FREE COLOUR BROCHURE.

**TRADE AIDS**  
(DEPT. PW9), 111 CHILTERN DRIVE,  
BERRYLANDS, SURBITON, SURREY  
01-399 4383  
100 yds. Berrylands Railway Station.

# NEW! FROM ADCOLA

## THE BEST IN SOLDERING KITS

Styrene packed with see-through top  
Makes the perfect gift!




**Contents**  
**BOX OF SOLDER**  
**TWO SPARE BITS**  
**HINTS ON SOLDERING**  
**686 SOLDERING STAND**  
**646 INVADER SOLDERING TOOL**

### Built to world safety standards

The Adcola Invader Soldering Kit comes to you in a presentation pack!  
 The 'READY TO USE KIT' offers maximum versatility of a 23 watt soldering instrument.

**only £3.99**

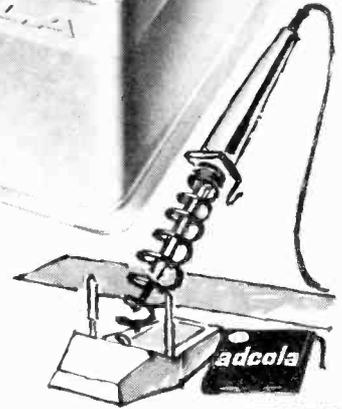

### THE FABULOUS INVADERS

SOLDERING INSTRUMENTS

The number one accepted soldering instrument used by the professional in industry. IS NOW ON OFFER TO YOU.

L 706 19watts £1.96  
 L 646 23watts £2.12  
 L1076 27watts £2.18

No heat sink required. Stock voltages 110v., 220v. and 230/250v.

### L686 SOLDERING INSTRUMENT STAND



The perfect instrument stand for your 'Invader'.

**£1.71**

### MULTI-CHANNELLED SOLDER



Pre fluxed solder 'READY TO USE' produced to B.S.I. 441 IN HANDY SIZES. £0.41 and £1.16

PLEASE SEND ME THE FOLLOWING ITEMS

NAME & ADDRESS \_\_\_\_\_

### INVADER SOLDERING KIT

1076 'INVADER' \_\_\_\_\_

646 'INVADER' \_\_\_\_\_

706 'INVADER' \_\_\_\_\_

686 SOLDERING STATION \_\_\_\_\_

1/2 kg SOLDER REEL \_\_\_\_\_

SMALL SOLDER REEL \_\_\_\_\_

Postage & packing add 10p. free over £2

Enclosing P/O and cheque



ADCOLA PRODUCTS LTD. ADCOLA HOUSE  
 GAUDEN ROAD LONDON, SW4 6LH  
 TELEPHONE: 01-622-0291/3

PW

# COMET HI-FI discount warehouses



## NEW LOW PRICES

	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS are tax free—</b>		
Buy now before V.A.T.		
ALBA U 700	37 95	25 25
ALPHA 212 by Highgate	37 75	23 95
AMSTRAD IC 2000	46 25	27 50
AMSTRAD Integra 4000	35 50	21 50
ARMSTRONG 521	59 00	43 75
FERRROGRAPH F307 Mk. II (cased)	58 00	45 50
GOODWIN RH 25 25	59 95	47 95
GLIXOR MW3000, 15 watts RMS per channel	49 50	23 95
JVC NIVICO VN 300	58 00	48 95
MCA 104Z	85 00	70 95
MCA 105E	130 50	109 95
MCA V5E VN550 Quadrasonic	89 00	74 95
MCA V9E VN880 Quadrasonic	148 00	124 95
KELETRON KSA 700	29 00	17 95
KELETRON KSA 1500	39 00	23 95
LEAK Delta 30 (cased)	69 90	46 95
LEAK Delta 70 (cased)	85 90	57 95
METRO SOUND ST20E	39 50	24 20
METRO SOUND ST60	70 00	45 50
PHILIPS RH521	109 00	89 95
PIONEER SA500A	47 10	32 95
SA600	95 48	57 95
SA800	126 55	75 95
SA1000	155 52	94 95
QL600A Quadrasonic Converter	89 00	78 95
QD 210 Quadrasonic decoder	42 85	29 95
QA 800 Quadrasonic	188 60	122 95
Reverberation 202w	54 95	35 95
RANK ROTEL 210	34 90	22 95
RANK ROTEL 310	52 00	34 95
RANK ROTEL 610	78 50	51 95
RANK ROTEL RA 810	105 50	72 95
RANK ROTEL RA 1210	129 00	89 95
ROGERS Ravensbourne	70 00	53 95
Ravensbourne (cased)	75 00	58 95
Ravensbrook Mk. II	52 50	40 95
Ravensbrook (cased) Mk. II	57 50	43 95
SINCLAIR 2000	35 00	22 95
3000	45 00	28 95
PROJECT 605	29 95	18 90
SOLARVOX 20, 10 watts RMS per channel	39 95	24 95
SOLARVOX 30, 15 watts RMS per channel	46 95	32 95
SOLARVOX MAB01 2 x 8 watts, RMS plus MATRIX 4 channel	38 45	26 95
SOLARVOX MAB13 2 x 18 watts, plus MATRIX 4 channel	51 38	38 95
TANDBERG TA300	69 90	54 95
TANDBERG TA300M	79 50	65 95
WHARFEDALE Linton amplifier	65 00	42 95
All take both ceramic and magnetic cartridges.		

	Rec. Retail Price	Comet Price
<b>TUNERS</b>		
AMSTRAD Multiplex 3000 FM	39 95	28 95
*ARMSTRONG 523 AM/FM	52 68	40 95
*ARMSTRONG 524 FM	40 97	31 95
ARMSTRONG 146 Decoder	9 50	6 95
*DULCI FMT 7 FM	24 43	14 95
GOODMANS Stereomax	75 74	35 95
JVC Nivico MCT V5E/VT500 AM/FM	86 00	69 95
MCT V7E AM/FM	122 42	99 95
LEAK Delta FM	79 50	57 95
LEAK Delta AT/FM	89 50	69 95
METRO SOUND FMS 20	54 92	42 95
PHILIPS RH 690	48 50	31 95
PHILIPS RH 621	109 00	89 95
PIONEER TX500A AM/FM	75 52	50 95
PIONEER TX600 AM/FM	104 57	73 95
RANK ROTEL 320	59 50	42 95
RANK ROTEL 620	93 50	87 95
ROGERS Ravensbourne Chassis	60 29	45 95
Ravensbourne in Teak Case	64 97	49 95
Ravensbrook Chassis	43 90	33 50
Ravensbrook (cased)	49 75	38 50
SINCLAIR 2000	45 00	29 95
3007	45 00	29 95
Project 60 Tuner (stereo)	25 00	17 50
All above Tuners are complete with MPX Stereo Decoder except where starred		

	Rec. Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>		
AKAI CR80T AM/FM Tuner Amplifier with built in Eight Track Tape Recorder	149 84	89 95
AKAI AA8000	139 50	106 95
AKAI AA8080	189 50	149 95
AKAI AA8500	249 00	179 95
AKAI 6300	137 50	79 95
ARENA 2600	111 30	59 95
ARMSTRONG M8 Decoder	9 50	6 95
ARMSTRONG 525	90 14	69 95
ARMSTRONG 526	102 72	79 95
GOODMANS Module 80, 35w. RMS Module 80 Compact	93 00	69 95
Module 90	168 00	127 95
Module 110 FM/MW/LW/SW/100w. RMS	119 00	91 95
Module 130	193 00	105 95
GOODMANS Module 110, Compact	245 00	187 95
JVC Nivico 4MM 1000 Quadrasonic	159 50	134 95
JVC Nivico VR 5500/5501 AM/FM	96 96	81 95
VR 5521L AM/FM and SEA	175 00	146 95
4VR 5414 Quadrasonic	212 00	179 95
KYOTO 1000 AM/FM Tuner/Amplifier with built in Stereo Cassette Recorder. Complete with two speakers and two microphones	85 00	61 95

	Rec. Retail Price	Comet Price
<b>TUNER AMPLIFIERS—continued</b>		
LEAK Delta 75	175 00	129 95
PHILIPS RH 720	215 00	179 95
PIONEER SX525	140 53	88 95
SX626	192 49	134 35
SX727	231 74	162 95
SX828	297 20	208 95
QX 4000 Quadrasonic	225 93	164 95
QX 8000 Quadrasonic	286 24	199 95
ROGERS Ravensbrook Chassis	96 57	73 95
ROGERS Ravensbrook (cased)	105 35	78 45
ROTEL RX 150A	69 90	50 95
ROTEL RX200A	89 50	65 95
ROTEL RX 400A	107 50	78 95
ROTEL RX 600A	149 00	109 95
ROTEL RX 800A	185 50	139 95
ROTEL RX 154A Quadrasonic	129 50	94 95
SOLARVOX TAM 1105 2 x 5 watts RMS AM/FM Multiplex comp. with 2 speakers and featuring Matrix channel	38 50	29 95
TANDBERG TR200 MPX	106 00	85 95
TANDBERG TR1000 FM MPX (teak)	165 00	128 50
TANDBERG TR 1010 AM/FM MPX	169 00	139 95
TELETON CR55	125 26	68 50
TELETON R8000 AM/FM	42 16	21 95
WHARFEDALE LINTON WE40	115 00	95 95
All the above take magnetic cartridges except		
Teleton R8000 and Kyoto 1000 which take ceramic		
only. All include MPX Stereo Decoder with the exception of Armstrong where M8 decoder is extra		

	Rec. Retail Price	Comet Price
<b>TURNABLES</b>		
CONNOISSEUR BD1 kit	13 34	10 95
CONNOISSEUR BD2 Chassis	32 71	25 95
CONNOISSEUR BD2 P/C/SAU2	41 29	33 95
GARRARD SP25 Mk. III	16 17	10 50
GARRARD 40B	13 63	10 95
GARRARD SL65B	20 93	13 75
GARRARD SL95B	49 21	32 25
GARRARD 401	42 88	29 50
GARRARD SL72B	32 60	21 95
GARRARD AP76	28 44	17 25
GARRARD Zero 100A	57 42	38 95
GARRARD Zero 100S	52 83	36 95

The following Turntables are complete with base, plinth, plastic cover and cartridge. Fully wired and ready for use. All at special price.

GARRARD SP25 Mk. 111 with Goldring G800	Special Price £18 50
MCDONALD MP60 with Goldring G800	Special Price £17 50
MCDONALD MP60 with SHURE M 44/7	Special Price £18 95
MCDONALD MP60 with SHURE M 44/E	Special Price £19 95
MCDONALD HT70 with Goldring G800	Special Price £25 50
GARRARD AP76 with Goldring G800	Special Price £26 50
GARRARD AP76 with Shure M55E	Special Price £30 50
GARRARD AP76 with Shure M75EJ	Special Price £32 50
GARRARD 2025 with S onotone 9T4HC	Special Price £12 75
GOLDRING GL75 with G800	Special Price £39 50
GOODMANS TD100 with G800E	75 00 51 95

Base and cover to fit GARRARD	Sp.	Price
SP25, SL55, SL65B		£6 60
GOLDRING G101P/C	29 64	20 50
GOLDRING GL72 Chassis	31 39	20 95
GOLDRING GL72P	40 81	27 50
GOLDRING GL75	41 86	26 95
GOLDRING GL75P	51 62	35 25
GOLDRING GL75P/Cover	87 11	56 95
Cover for 72P	4 71	3 25
Cover for 75P (de Luxe)	5 23	3 50
Cover for 85P	6 98	4 95
C99-plinth and cover for G99	15 35	11 95
GOLDRING G99	29 64	19 25
LEAK Delta	69 50	52 50
JVC Nivico SRP 473 Quadrasonic, including plinth and cover	69 50	58 95
MCDONALD MP60	14 78	9 50
MCDONALD 610	18 75	12 95
MCDONALD 610	20 63	14 50
Base and cover for MP60 and 610	3 85	3 85
PHILIPS GA212 Electronic	69 00	57 50
PIONEER PL12D with base and cover	49 18	34 50
PIONEER PL61 with base and cover	176 83	119 95
THORENS TX25 cover	8 85	6 50
THORENS TD125 Mk. II	82 63	66 50
THORENS TD125AB	115 69	79 95
THORENS TD125AB Mk. II with TP 16 arm	124 54	99 95
THORENS TD160/c including base and cover	69 80	56 95
THORENS TX11 cover	4 49	3 60
WHARFEDALE Linton	37 50	26 95

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
*Speakers are tax free—buy now before V.A.T.		
*AMSTRAD 138 (pair) Teak	26 00	13 95
*AKAI SW 155	64 50	44 95
*B and W Model 70	159 50	109 95
B and W DM2	69 99	47 50
B and W DM4	49 66	37 95
B and W DM5 (pair)	59 48	43 95
CELESTION COUNTY (pair)	47 94	35 95
Ditton 120 (pair)	56 40	38 50
Ditton 15	37 40	26 95
*Ditton 25	65 00	42 50
*Ditton 44	54 00	35 00
*Ditton 66	99 00	70 95
*FERRROGRAPH S1 inc. stand	95 00	67 95
GOODMANS Minister Pair	49 20	35 95
*Dimension 8 (pair)	55 12	39 40
*Magister	65 63	42 50
Double Maxim (pair)	67 40	47 95
*Mezzo 3	35 70	23 45
*Magnum K2	46 20	29 50
Goodwood	55 00	38 95
*Dimension 8	72 44	44 95
DIN 20 NT Kit	12 19	8 50
KELETRON KN 400 2-speaker system (pair)	15 44	11 95
KN600 3-speaker system (pair)	25 82	16 95
*KN800 3-speaker system (pair)	31 30	18 95
*KN100 4-speaker system (pair)	40 80	23 95
*KN1600 3-speaker system	95 24	64 95
*KN2100 3-speaker system	30 60	18 95
LEAK 150 (pair)	50 00	37 50
LEAK 250 (pair)	63 00	47 95
*LEAK 600	49 50	34 50
*LINEAR 10 watt Teak (Pair)	Sp. Price	12 95
*METRO SOUND MFS 103 (pair)	28 21	14 95
*202	21 50	14 75
*Duplex 15	32 00	23 95
*Duplex 25	56 00	37 50
*PIONEER CS53	46 72	29 95
SINCLAIR Q16	8 98	6 50
TANDBERG Tan 7	25 23	14 95
Tan 11 (pair)	40 00	31 95
TL 12 Teak (pair)	55 50	44 50
TL 25 Teak (pair)	71 50	56 95
*TL 50 Teak	68 00	50 95
TELETON R8000 (pair)	21 08	11 95
*THORENS GREENVILLE TG100 (pair)	28 21	14 95
*TG200 (pair)	41 95	24 95
*TG300 (pair)	55 95	29 95
WHARFEDALE Denton Mark II (pair)	42 00	28 95
Linton Mark II (pair)	52 00	37 50
*Milton Mark II	65 00	46 95
*Dovedale 3 Mark II	47 50	32 25
*Rosedale	69 00	44 95
Unit 3 speaker kit	12 50	8 95
Unit 4 speaker kit	19 00	12 95
Unit 5 speaker kit	27 50	18 75
<b>PICK UP ARMS AND HEADS</b>		
AUDIO Technica AT 1005 Mk. 11	18 78	14 25
AUDIO Technica L2 lifts	2 61	1 95
CONNOISSEUR SAU2	14 12	10 95
GOLDRING Lenco 75	13 96	9 25
GOLDRING Lenco L69	10 46	6 50
GOLDRING PH6 Head Shell	2 97	1 99
SME 3009 ser 11 improved	36 75	28 50
SME 3009-S2 ser 11 improved	40 25	30 95
SME S2 Headshell	2 59	1 95
<b>CHASSIS SPEAKERS</b>		
*Items are tax free—buy now before V.A.T.		
GOODMANS Twin-axiom 8	9 12	6 95
Twin Axium 10	10 06	7 50
*Axium 401	17 68	11 95
Axiom 8P	5 49	4 15
Axiom 10P	5 97	4 50
Axiom 12P	13 00	9 15
Axiom 5P	21 00	14 60
*Axiom 18P	35 70	24 45
Axiom 100 40 watts din.	12 00	8 35
*ARU 172	4 50	3 20
*Axent 100	6 90	4 80
*Midax 650	13 39	9 50
*Axiom 401	3 75	2 60
*Crossover network XQ/950	5 45	4 45
WHARFEDALE 8 in. Bronze/RS/DD	4 75	3 30
Super 8/RS/DD	8 50	6 25
Super 10/RS/DD	14 00	9 95
<b>CARTRIDGES</b>		
AMSTRAD 900C	5 32	3 40
AMSTRAD 900D	8 10	5 40
AMSTRAD 900 EX	11 90	8 50
AUDIO TECHNICA AT 66	17 44	12 95
*CONNOISSEUR Ceramic SCU1	6 09	4 95
GOLDRING G850	6 10	3 10
GOLDRING G800	12 21	4 50
GOLDRING G800E	17 67	7 90
GOLDRING G820	11 62	8 25
GOLDRING G820E	17 44	12 95
GOLDRING G820 Super E	23 25	16 25
GOLDRING G800 Super E	24 41	15 25

# OVER 1000 ITEMS ALWAYS IN STOCK

All items brand new and fully Guaranteed and backed by after-sales service

— latest models in manufacturers' sealed cartons



**COMET for after-Sales Service THROUGHOUT THE U.K.**

Pictured. Service Department at Clough Road, Hull. Also at Birmingham, Bridlington, Dagenham, Doncaster, Edinburgh, Gole, Hackbridge, Hayes, Jarrow, Leeds, Leicester, Nottingham, Retford, Rochdale, Sheffield, Teesdale, Wigan, with Engineers covering Tork and Scarborough.

	Rec. Price	Retail Price	Comet Price
<b>CARTRIDGES—continued</b>			
EMPIRE 909E/X	12 79	8 50	
EMPIRE 90EE/X	9 94	6 95	
SHURE M3DM	6 10	3 75	
SHURE M31E	11 63	6 95	
SHURE M32E	10 73	6 50	
SHURE M44-G	8 30	4 95	
SHURE M44-J	7 90	4 50	
SHURE M-44C	7 90	4 90	
SHURE M44E	8 60	4 75	
SHURE M55E	9 70	5 45	
SHURE M75G	14 70	8 35	
SHURE M75-6 (S)	8 36	5 45	
SHURE M75-6	13 60	7 60	
SHURE M75EJ	15 40	8 75	
SHURE M75ED	19 00	10 15	
SHURE M75E/95G	20 80	12 95	
SHURE M91E	18 45	9 95	
SHURE V15-11	39 40	24 95	
*SONOTONE 9TAHC Diam/Saph	3 75	1 45	

	Rec. Price	Retail Price	Comet Price
<b>BASES AND COVERS</b>			
CONNOISSEUR Plinth BDI	5 57	4 50	
CONNOISSEUR Cover	4 17	3 40	
CONNOISSEUR P.U. Mount Board	0 95	0 75	
GARRARD WB1 Base	3 78	2 95	
GARRARD WB4 Base	5 60	4 25	
GARRARD SPC1 Cover	3 68	2 75	
GARRARD SPC4 Cover	4 38	3 25	

	Sp. Price	Retail Price	Comet Price
<b>Special Offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500</b>			
GOLDRING Plinth 75	9 77	6 75	
GOLDRING Plinth 72	9 42	6 50	
GOLDRING Covers for 72P	4 71	3 25	
Cover for 75P De Luxe	5 23	3 60	
Cover for 85P	6 98	4 95	
THORENS TX 25 (for TD125AB)	8 85	6 50	
THORENS TX11 Cover	4 49	3 60	
SME Plinth System 2000 with motorboard	46 20	35 95	
MOTORBOARDS only	5 85	4 45	
SME P1 Spacer	0 98	0 75	

	Rec. Price	Retail Price	Comet Price
<b>BLANK TAPES</b>			
<b>SCOTCH DYNARANGE CASSETTES</b>			
C60	0 71	0 40	
C90	0 99	0 50	
C120	1 49	0 75	
<b>SCOTCH HIGH ENERGY COBALT CASSETTES</b>			
C60	1 10	0 65	
C90	1 45	0 85	
<b>SCOTCH Low Noise 8-TRACK</b>			
<b>BLANK CARTRIDGES</b>			
40 mins.	1 50	0 90	
80 mins.	1 80	1 10	
<b>SCOTCH HI-FI DYNARANGE SPOOLED TAPES</b>			
5" L.P. 900	1 88	1 10	
5 1/2" L.P. 1200	2 20	1 30	
7" L.P. 1800	2 95	1 80	
<b>SCOTCH HI-FI DYNARANGE DOUBLE PLAY</b>			
5" D.P. 1200	2 31	1 40	
5 1/2" D.P. 1800	3 15	1 95	
7" D.P. 2400	4 03	2 50	

Postage—Tape, cassettes and 8T cartridges 1-9 items 5p per order. Packs of ten post free.

	Rec. Price	Retail Price	Comet Price
<b>HEADPHONES</b>			
<b>Are now tax free—buy now before V.A.T.</b>			
AMSTRAD HPS5A	7 50	3 90	
HPS5A with volume control	10 70	6 70	
HPST4 bass and treble controls	13 95	9 90	
AKAI ASE9	7 25	4 25	
AKAI ASE22	11 90	7 25	
AKG K180	28 00	16 95	
AKG K60	15 00	8 95	
AKG 100	8 00	4 95	
AKG 120	10 00	4 50	
KOSS HV1	20 00	15 95	
KOSS ESP-9 Electrostatic	69 00	52 95	
KOSS ESP-6 Electrostatic	45 00	34 95	
KOSS K2 plus 2 Quadrafone	45 00	35 95	
KOSS PRO 5 LJC	30 00	23 95	
KOSS PRO-4AA	28 00	20 95	

	Rec. Price	Retail Price	Comet Price
<b>HEADPHONES—continued</b>			
KOSS KO-727B	16 50	12 45	
KOSS 747	20 00	14 95	
KOSS K-711	10 00	7 75	
KOSS K6	12 50	9 50	
KOSS K6/LC (with volume control)	14 00	10 50	
KOSS K6/LCQ Quadrafone	20 00	16 95	
PIONEER SE 50	21 90	13 25	
PIONEER SE 30A	12 60	8 25	
PIONEER SE 20A	7 88	4 95	
PIONEER SEL 20	10 53	6 80	
PIONEER SEL 40	17 43	11 30	
SOUND MD806	6 50	2 80	
WHARFEDALE DD1	12 50	8 75	
WHARFEDALE ISODYNAMIC	19 95	14 95	

	Rec. Price	Retail Price	Comet Price
<b>HI-FI STEREO SYSTEMS—COMPLETE</b>			
ALBA U 552	47 75	29 95	
BUSH A1005	69 89	50 95	
DANSETTE Consort Stereo	71 43	23 95	
DANSETTE 4005	71 45	49 95	
DANSETTE 4020	47 99	31 95	
DECCA SOUND 613	Sp. Price	46 50	
DECCA SOUND 614	Sp. Price	52 95	
DECCA COMPACT 2 with Radio	Sp. Price	78 95	
DECCA 403	Sp. Price	44 95	
FERGUSON 3450 B with Radio (new model)	79 50	61 95	
FERGUSON 3451 B with Radio (new model)	107 00	82 95	
FERGUSON 3452 B with Radio	41 50	32 95	
FIDELITY UA1 Music Master with Radio	100 00	69 95	
FIDELITY UA2 Music Master	43 50	30 95	
FIDELITY Stereo Nine	38 50	22 95	
G.E.C. 2810	79 00	59 95	
GROSVENOR MPX 8400 AM/FM MPX Tuner/Amplifier, magnetic input with built-in 8-track cartridge player with speakers	69 95	41 50	
HMV 2451	122 00	95 95	
HMV 2452	66 00	49 95	
HMV 2455	175 00	136 95	
KB 1025 with 662 speakers	48 25	37 95	
KB 1250 with KS 653 Speakers	71 00	53 95	
KB 2010 with 658 speakers and Radio	101 50	77 95	
KB 2250 with 658 speakers and Radio	124 00	95 95	
MURPHY 902 Studio 1, with AM/FHF/Radio	84 50	64 95	
MURPHY 940	89 89	52 95	
PHILIPS 808	105 00	74 95	
PHILIPS GF 824	65 30	49 65	
PHILIPS 825	49 50	37 95	
PHILIPS 826	75 00	51 95	
PHILIPS 835 with Radio	69 50	47 95	
PHILIPS 836 with Radio	95 00	67 95	
RIGONDA Party Time	28 50	20 95	
STEEPLETONE Stereo System	41 75	22 95	
ULTRA 6027	57 50	44 95	
ULTRA 6028	59 95	45 95	
ULTRA 6450B (new model) with Radio	79 50	61 95	
ULTRA 6451	79 50	61 95	
ULTRA 6455	41 35	31 95	
ULTRA 6454	38 85	29 95	

	Rec. Price	Retail Price	Comet Price
<b>TAPE RECORDERS</b>			
AKAI 1721L	99 90	73 95	
AKAI 4000 DS	99 50	73 95	
AKAI X201D	179 00	132 95	
AKAI X1810	229 00	169 95	
AKAI GX221D	229 00	169 95	
AKAI GX1900D	239 00	177 95	
AKAI GX370D	350 00	259 95	
AKAI CR80D 8-track stereo tape deck	85 02	55 95	
AKAI CR80 8-track stereo recorder	106 39	69 95	

	Rec. Price	Retail Price	Comet Price
<b>TAPE RECORDERS—continued</b>			
AKAI CR80DSS Quadraphonic	159 50	121 95	
AKAI CR80T 8-track stereo recorder and tuner amplifier	149 84	89 95	
AKAI CR81	109 50	80 95	
AKAI CR81D	89 50	65 95	
FERGUSON 3258 4-track	70 45	51 95	
FERROGRAPH 702/704 Dolby	285 53	241 95	
FERROGRAPH 702H Dolby	297 28	251 95	
FERROGRAPH 722/724 Dolby	326 65	276 95	
FERROGRAPH 722H Dolby	338 40	286 95	
FERROGRAPH 702/704	235 00	172 95	
FERROGRAPH 722/724	276 15	198 95	
FIDELITY Braemar 4-track	34 75	19 95	
GROSVENOR RP000 8-track, record/playback deck	54 50	38 95	
<b>GROSVENOR MPX 8400 AM/FM MPX Tuner/Amplifier, magnetic input with built-in 8-track cartridge player with speakers</b>			
GRUNDIG TK 121 (twin-track)	69 95	41 50	
GRUNDIG TK 141 (4-track)	56 25	39 95	
GRUNDIG TK 146 (4-track auto)	62 10	45 95	
GRUNDIG TK 147 (4-track auto)	66 95	49 95	
GRUNDIG TK 147 (4-track auto)	98 65	76 95	
GRUNDIG TK 148 (4-tr. auto 2 spd.)	74 10	57 95	
GRUNDIG TK 246 4-track Stereo Deck	131 85	101 95	
GRUNDIG TK 3200 Hi-Fi (Battery)	141 10	105 95	
MARCONI 4248 4-track, 2 speed	52 30	39 95	
PHILIPS 4303 Twin-track	39 46	24 95	
PHILIPS 4307 4-track	50 00	35 95	
PHILIPS 4308 De Luxe 4-track	59 00	42 95	
PHILIPS 4416 4-track stereo rdr.	145 00	109 95	
PHILIPS 4418 4-track stereo	200 00	145 95	
TANDBERG 3341X 4-track stereo	129 90	109 95	
TANDBERG 6041X 4-track stereo	199 30	159 95	
TANDBERG 9021X 2-track stereo deck	230 00	194 95	
TANDBERG 9041X 4-track stereo deck	230 00	194 95	

	Rec. Price	Retail Price	Comet Price
<b>TAPE RECORDERS (CASSETTE)</b>			
AKAI CS35D tape deck	79 95	59 50	
AKAI CS35 Stereo inc. Speakers	112 50	82 95	
AKAI GXC 40D tape deck	95 50	67 95	
AKAI GXC 40	112 50	82 95	
AKAI GXC 40T recorder, tuner/amp.	167 50	123 95	
AKAI GXC 45D tape deck	119 90	89 95	
AKAI GXC 46 Dolby tape recorder	152 50	115 95	
AKAI GXC 46D Dolby tape deck	139 50	103 50	
AKAI GXC 65D Dolby auto-reverse deck	154 50	110 25	
BUSH Discassette DC70	20 62	12 95	
BUSH TP 60	27 62	15 95	
BUSH TP 66 Battery/Mains	28 18	21 50	
FERGUSON 3240 with case	24 90	15 95	
FERGUSON 3253 (mains)	42 40	27 95	
FERGUSON 3256 (mains)	37 75	25 95	
FERGUSON 3257	56 45	41 95	
FERGUSON 3257/7 spkrs. for above	16 00	12 00	
GEC CR200 AM/FM Cassette/Radio, Battery/Mains with slide controls	Sp. Price	35 95	
GRUNDIG C210 Batt./mains	48 75	36 95	
HARVARD Elite Cassette/AM/FM Radio (battery/mains)	44 75	23 95	
JVC Nivico 9420 LS with AM/FM radio, battery/mains	61 45	45 95	
JVC Nivico 1710 Radio/Cassette, AM/FM	61 00	42 95	
PHILIPS 2202/2203	24 00	17 95	
PHILIPS 2204 battery/mains	29 10	24 95	
PHILIPS 2405 Stereo with 2 RH401 L/S	72 00	52 95	
PIONEER CT 4141 Dolby Deck	150 02	104 95	
PYE 9116 Stereo	69 90	49 95	
WHARFEDALE Dolby DC9 Mk. II.	119 00	85 95	

FREE Technical Advisory Service. If in doubt ask us! Price list on request. Comet guarantees that all prices quoted are genuine. All offers subject to availability. Add 75p for postage. Insurance and insurance on all orders (Cartridges 20p) OR, IF SECURICOR DELIVERY REQUIRED add £1.95 only. Make cheques, Money Orders payable to 'COMET'.

# COMET HIGH FIDELITY DISCOUNT WAREHOUSES

**OPEN DAILY TO THE PUBLIC FROM:**  
**9am-6pm Monday**  
**9am-1pm Tuesday**  
**9am-3pm Wednesday**  
**9am-6pm Thursday**  
**9am-6pm Friday**  
**9am-5.30pm Saturday**

- Dept. PW BIRMINGHAM: Heeley Road, Selly Oak, B29 6EY. Tel.: 021-472-6112 and at Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley B26 1BJ. Tel.: 021-706-0684
- Dept. PW EDINBURGH: 1 Newhaven Road, EH6 5QX. Tel.: 031-554-4454 (9 lines)
- Dept. PW HULL: Reservoir Road, Clough Road, HU6 7QD. Tel.: 0482 46441 (6 lines)
- Dept. PW LEEDS: 78 Armley Road, LS12 2EF. Tel.: 0532 40551
- Dept. PW SHEFFIELD: The Mill, 1 Lowley Road, Main Bridge, S6 4TN. Tel.: 0742 341721/6
- Dept. PW STOCKTON: Teesway, Portrack Lane, Teesside TS18 2RH. Tel.: 66132165215
- Dept. PW ROCHEDALE: Corner of Well 1<sup>th</sup> Lane and Queensway. Tel.: 50606
- Dept. PW LEICESTER: Syston Street. Tel.: 0533 52236
- Dept. PW WIGAN: Wharf Mill, Princess Street, WN3 4EZ. Tel.: 0942 34741
- Dept. PW LONDON: Hackbridge (nr. Croydon) 193 London Road, Hackbridge, Wallington, Surrey. Tel.: 01-659-0241
- Dept. PW LONDON: Dagenham, Rainham Road South, Dagenham RM10 8ST. Tel.: 01-595-5111
- Dept. PW SUNDERLAND: 4-7 Thomas Street, Sunderland, SR1 1HR. Tel.: 0783 59993
- Dept. PW RENFREW: Blythswood Trading Estate, Argyle Ave., Renfrew, RA4 9EL. Tel.: 041-886 5731
- Dept. PW JARROW: 56/64 Ellison Street, Jarrow NE32 3MT. Tel.: 0632 892211
- Dept. PW SANDIACRE: 121 Town Street, Sandiacre, Nottingham NG10 5DW. Tel.: Sandiacre 6116
- Dept. PW LONDON: Hayes, Silverdals Road, Pump Lane, Hayes. Tel.: 01-573 1841

**SECURICOR**  
 SPECIAL DELIVERY SERVICE  
 All in-stock items delivered by SECURICOR within 72 hours.  
 Add £1.25 only for Securicor delivery.  
 ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

**TRANSISTORISED** F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2-10p.

**B.F.W.** 10 Fet. New (unmarked) 5 for £1-00p.

**PINNACLE LOW NOISE CASSETTES** C60—50p/C90—75p/C120—£1.

**P-C BOARDS** (not computer panels).

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor £1-50 the three.

Encapsulated bridge rectifier (fit used 3 3mdh) 100 PIV 2 amps. 50p each. 3 for £1-25.

Transistor F.M. Stereo Multiplex Decoder. Size: 5½ x 2½ x 1½. As used in well known British stereo units with circuit. £3-75.

**GARRARD SP25 MK. 11** less Cartridge. £10 50.

**10 VOLUME CONTROLS** consisting of 2 off each.

100K log. ganged L/S—20K log. ganged L/S.

470K log. D/P Switch—10K lin. L/S—50K 1in. L/S. £1-25.

**4 PHONO SOCKETS ON PANEL.** 10 panels for £1-25.

**12 PLASTIC KNOBS.** Chrome and Gold, 3 types—4 off each—spring clip £1-25.

**10 COMPUTER PANELS** packed with components including one panel with 2 Power Transistors. £1 00.

**SLIDER CONTROLS** (less knobs)

25K Log or Lin single 30p.

10K—100K Log ganged 50p.

100K—100K Log ganged 50p.

All items post paid in  
**GREAT BRITAIN**

## SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

## TEXAN 20+20 WATT. STEREO AMPLIFIER

Electro Spares can now supply all the components to build the "Texan" Amplifier, featured in *Practical Wireless* May/June 1972. All components are brand new with fibre glass p.c. board, all metalwork, knobs, finished silver trim front panel, etc. etc.

**TOTAL COST OF COMPLETE COMPONENTS  
ONLY £27-85—POST FREE!**

All components are available separately, to enable the constructor to obtain just what parts he requires at any one time. Please send S.A.E. for free list.

**SPECIAL CONTEMPORARY STYLE SLIMLINE METAL CASE WITH WOODEN END CHEEKS IS NOW AVAILABLE FOR THIS AMPLIFIER—DETAILS INCLUDED WITH ALL LISTS, OR AVAILABLE ON RECEIPT OF S.A.E.**

## P. E. 'GEMINI' STEREO AMPLIFIER

**30 Watts (R.M.S.) per Channel into 8 Ohms!!**

**Total Harmonic Distortion 0-02%!!**

**Frequency Response (-3 dB) 20Hz-100kHz!!**

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but it is well within the capabilities of the ambitious constructor.

**We can now supply a reprint of the articles in booklet form, price 55p plus 4p postage, with free complete component price list.**

For free price list only, or a complete free specification, please send a foolscap size S.A.E.


All parts available separately.



**ELECTRO SPARES**

21 BROOKSIDE BAR,  
CHESTERFIELD, DERBYSHIRE.  
QUALITY • SERVICE • VALUE

## HOME RADIO COMPONENTS

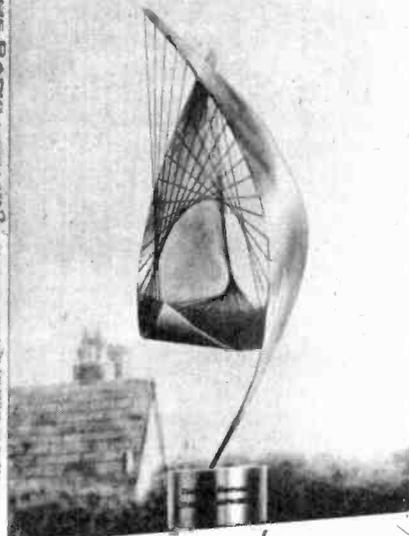

250 pages 11¼" x 8½"

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

**Only 55p.**

plus 20p POST AND PACKING

**POST THIS COUPON**  
with cheque or P.O. for 75p.

# The Catalogue you MUST have!

*Details of our popular  
Credit Account Service  
and our Easy Ordering  
System are included  
in the catalogue.*

Name \_\_\_\_\_

Address \_\_\_\_\_



HOME RADIO (Components) LTD. Regd. No. 912966 London  
Dept. PW, 234-240 London Road, Mitcham CR4 3HD

**YES, YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS!!! ALMOST UNBELIEVABLE!** Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPER SEDES ALL EARLIER MODELS!** will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! \* Send quickly, after receiving goods test 7 days, refund if not delighted. Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF: FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!) Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE 14ins x 10½ins x 4½ins** overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions & circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra). **BOX, POST, ETC. 50p.** BUT WAIT for only 55p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K., when abroad. (NO GUESSING! NO MESSING!) PLUS Standard 'longlife' batteries PLUS ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY!** Shopertunities save you ££'s and ££'s!

**THOUSANDS OF MILES REDUCED TO INCHES?**  
**1973 RUSSIAN RADIO TECHNOLOGY**  
**SHRINKS THE WORLD! \*COMPUTERISED?**



**BRAND NEW FABULOUS ASTRAD 17**  
**PORTABLE RADIO & COMMUNICATIONS RECEIVER**

**WORLD WIDE RECEPTION**  
 INCLUDES TRANSMISSIONS FROM THE FOUR CORNERS OF THE GLOBE!



**28 TRANSISTORS AND DIODES!**  
**WAVEBANDS:**  
 STANDARD LONG and MEDIUM  
 Plus 5 SHORT WAVEBANDS  
 Plus ULTRA SHORT WAVES  
 (V.H.F. AM, FM, MW, LW, USW.)

**BATTERY MODEL £20.75** BOX POST ETC. 50p  
**MAINS/BATTERY ELIMINATOR £1.48 extra**

**FIRST TIME EVER!**  
 \*NOW AVAILABLE WITH **fabulous COMPUTERISED WORLD TUNING GUIDE!**  
 NO MORE GUESSWORK!  
 INSTANT DATA at your fingertips - enables you to **TUNE IN A FLASH** to transmissions the world over!

**THIS OFFER ONLY FROM US!**

**BUY ONE FROM US!** **SAVE £20.25 NOW!**

**fabulous BRAND NEW SOLID STATE** This equipment's got EVERYTHING!

**BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

**RECOMMENDED RETAIL PRICE £44**

**OUR PRICE £23.75** CARR. ETC. 35p

WITH REMOTE CONTROL MICROPHONE

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!) We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM, FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: \* Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** \* "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! \* Separate ON/OFF and HI-LO volume controls! \* Heavy duty built-in speaker! \* Earphone (for personal listening) or "monitoring" and extension speaker sockets! Remote control microphone! \* Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets locally city and regional stations in every part of the country, plus B.B.C. National VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £23.75, CARR. ETC. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, after receiving goods test 7 days, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 25p extra if required.

**FIRST TIME EVER! \*SAVE £14.48!**

**BRAND NEW AC/DC BATTERY/MAINS**

**Cassette TAPE RECORDER & PLAYER**

**FIRST CLASS MAKERS**

With remote control microphone.

**WE COULD CHARGE UP TO £26.97!**

**OUR PRICE £12.49** POST ETC. 31p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £12.49!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest **MASTER SWITCH CONTROL**) AND **AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Tapes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9½in x 5in x 2½in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Recommended selling price £26.97!) **OUR PRICE ONLY £12.49** post, etc., 31p. \* Send quickly, after receiving goods test 7 days—refund if not delighted. **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries AND microphone stand all for 50p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

Dept. WP/29 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7) Also at 37/39 HIGH HOLBORN (opp. Chancery Lane), LONDON, W.C.1 (Thurs 7 p.m.) BOTH STORES OPEN MON TO SAT 9 A.M. UNTIL 6 P.M.


**SHOPERTUNITIES LTD.**

# SAXON ENTERTAINMENTS.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT  
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN  
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.
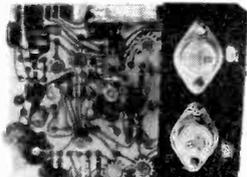
## SA25-SA35-SA100

LOW-PRICED AUDIO MODULES  
FOR DOMESTIC & COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS INCLUDING THESE THREE MODULES.

**SA25 £2.95** carr. free

25 WATTS RMS. 7 transistors 7 diodes.

**SA35 £4.45** carr. free

35 WATTS RMS. 7 transistors 7 diodes

**SA100 £10.90** carr. free

100 WATTS RMS. 17 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE

### BRIEF SPEC. FOR ALL THREE MODULES

Freq. response 15-40,000 Hz  $\pm$  1dB  
Distortion 0.2% at 1 kHz  
Loads 4 to 16 ohms  
Quiescent current 15 mA  
Noise Better than -75 dB  
Supply voltage 25-45 volts SA25/35  
40-70 volts SA100  
Size 4 1/2" x 4" x 1" (SA100)  
4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES FOR

#### THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4.90
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
Stab PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
MT70	Transformer for PS70	£4.90 carr. 40p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free

ALL MODULES ARE BUILT ON  
GLASS FIBRE P.C. BOARD  
AND ARE SUPPLIED FULLY TESTED

## OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE £13.90 + 20p carr. or with supply  
**£18.95** + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

### SPECIFICATION

Power output 120 watts into 8 ohms  
Freq. response 20-20,000 Hz  $\pm$  2dB  
Input sensitivity 200 mV into 10K  
Construction Fibreglass board  
Size 8" x 4" x 4" (5" with supply)  
Low distortion parallel push-pull output stage.




**NEW** 160 watt version & supply **£27.90**
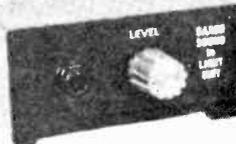
### SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simply itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



**£8.90** carr. free

### THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000-watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue hooded cover. Fully guaranteed.

**£19.75** carr. 30p

MONO VERSION £6.50 carr. 20p (As illustrated. S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



**£15.80** carr. 30p

### SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE. (N.B.—Stereo only has mic input.)

### COMPLETE AMPLIFIERS

The CSE 100. £34.90 carr. free

This versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.



The SAXON 100 £48.50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

### LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5.95 carr. 30p. 15" 50W/8/15 ohm £14.50 carr. 50p.  
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.

### A.K.G. MICROPHONES suitable for disco, group or general P.A. use.

O11DHL rrp £11.00 our price £9.45 post free  
D190C High Z rrp £21.50 our price £17.45 post free  
D1000C 24 ct gold plate rrp £37.00 our price £32.00 post free

SEND SAE FOR  
OUR AKG PRICE  
LIST. DISCOUNTS  
ON ALL MICS.

### CALLERS & MAIL ORDER:

351 Whitehorse Road,  
Thornton Heath, Surrey,  
91-969 3685

### CALLERS ONLY:

OUR NEW  
DISTRIBUTORS

CIRCLE SOUND,  
328-330 The Banks, Rochester.  
Medway A04199

### BUSINESS

HOURS:  
9.30 a.m.  
to 5.30 p.m.

### TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)  
All cash in regd. envelopes please!  
Telephone orders to our CROYDON BRANCH.  
TRADE & EXPORT enquiries invited.

# PRACTICAL WIRELESS

VOL 48 NO 12

Issue 794

APRIL 1973

## The Buyer and VAT

During these last few weeks before Value Added Tax takes effect, readers will be contemplating whether to buy now or wait until after April 1st. It will undoubtedly pay to wait on such items as domestic receivers, some Hi-Fi equipment and electrical goods, but component suppliers are being hard pressed to meet demand before the infliction of VAT.

One way of circumventing purchase tax has been to supply equipment in kit form, but these items in any form will be liable for VAT at one common percentage rate, since VAT is a tax on the basic purchase price or charge for service.

We would expect that all suppliers will make it quite clear to all customers, at the trading premises and through advertisements, whether quoted prices include VAT. The basic retail price should remain the same as now. Whatever you pay for goods or services from April 1st, you should not be paying any purchase tax or selective employment tax levies; you should be paying VAT on top of the normal retail price, based on the Chancellor's Budget announcement on March 6th.

Kit and component prices should not be raised before April 1st and manufactured goods subject to purchase tax of more than 15% should be noticeably reduced after April 1st.

Shopkeepers and other traders are not legally bound to show the amount of VAT in cash transactions; neither will they necessarily show special "tax invoices" for retail sales, but it is worth remembering that if you purchase at a cut price rate, the VAT charged will be correspondingly lower. Goods obtained by hire purchase or credit agreements will be subject to tax at the current rate at the time when transaction documents are signed. Interest rates on these terms are not taxable. Private sales between individuals do not attract VAT because neither party is defined as a "taxable person", unless the seller is a trader required to register with H.M. Customs and Excise.

Our advice to readers who are thinking of buying goods by mail order during March is to determine first whether purchase tax is chargeable; if it is then wait until April. Items not subject to purchase tax (such as components and secondhand or used goods) should be ordered early. If of substantial value, send your order by P.O. "Recorded Delivery" and keep the counterfoil of your Postal Order, Money Order, or cheque.

You should be prepared for a VAT levy on charges for packing service but not for postage.

*continued on next page*

## NEWS AND COMMENT

The Buyer and VAT	1081
News . . . News . . . News . . . <i>by Colin Riches</i>	1082
CQ! CQ! CQ!	1094
Hotlines <i>by Ginsberg</i>	1097
Practically Wireless <i>by Henry</i>	1102
Next Month in Practical Wireless	1103
MW Column <i>by Charles Molloy</i>	1111
Letters	1118
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	1121

## CONSTRUCTIONAL

Improving VHF Radio <i>by A. N. Ainslie</i>	1084
Experimenters' Corner, Novel Tone Generator <i>by N. Naughton</i>	1088
IC Power Amplifier <i>by D. Silvester</i>	1090
"P.W. Tricolour" Mood Lighting System, Part 1 <i>by Jurek Budek</i>	1104
DXers MW Loop Aerial <i>by S. A. Money, G3FZX</i>	1112
Take 20, No. 47. Varicap B.F.O. <i>by Julian Anderson</i>	1126
Darkroom Exposure Meter <i>by A. P. Donleavy</i>	1129

## OTHER FEATURES

Nautical Radio Aids <i>by Ian Sinclair</i>	1098
Going Back <i>by Colin Riches and Arthur Dow</i>	1124

**THE MAY ISSUE WILL BE  
PUBLISHED ON APRIL 6th**

©IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

by  
Colin Riches

## VAT

To the best of our knowledge, the prices quoted in this issue were correct at the time of going to press.

From April 1st 1973, there will be no purchase tax but a large number of goods will carry Value Added Tax. For further details, see our Leader article.

## Tulip Time Rally

The 1973 "Tulip-Time" mobile rally will be held on Sunday May 6th at Surfleet, 4 miles north of Spalding on the A16.

The Spalding and District Amateur Radio Society will also be operating a Special Activity station, GB3STF on 12th-13th May from The Grammar School, Priory Road, Spalding, in connection with the 1973 Tulip Festival. Operation will be on s.s.b./c.w. on all bands 160-10m. with a.m. on 2m. All contacts will be confirmed by special QSL cards.

Of interest to "Going Back" fans—the Wireless Preservation Society will have an exhibition of vintage radio on show to the public. I hope to be able to publish further details later.

## RSGB "Jubilee Year" President



Photograph by P. M. Fletcher.

This picture shows Dr. J. A. Saxton, D.Sc., PhD, CEng, FIEE, FInstP, the new President of the RSGB. On the left of the picture is Swedish Amateur Lt. Col. Per Anders Kinman, SM5ZD, who received the Calcutta Silver Key award. Sir John Eden, the P.M.G. is on the right.

In his address, Dr. Saxton said he felt very proud that he had been chosen as President of the RSGB for its Diamond Jubilee Year. He also said that he was extremely delighted that Sir John had been able to attend and that all there were greatly honoured by his presence.

Dr. Saxton went on to say that the Society would continue to do all in its power to continue to deserve the Ministry's support.

Per Anders Kinman has been made an Honorary Vice President of the RSGB in recognition of his outstanding service with the IARU Region 1 in which he has served for many years.

The Calcutta Key he received was first presented 20 years ago and it has been awarded annually by the RSGB to the person they feel has made, in any one year, the most significant contribution to international friendship and goodwill through the medium of Amateur radio.

## The Buyer and VAT

*continued from previous page*

If you order from a current catalogue or advertisement after April 1st, you should add the VAT percentage rate to the basic retail price shown. Then add the estimated or stated charge for postage and packing. If a service is chargeable, such as equipment repair or consultation, VAT will be levied at the standard rate. Trading in second-hand and used goods will also be taxable under VAT.

Finally, good news for P.W. readers: newspapers and magazines will be "zero-rated", which means that no VAT is chargeable on these. Transactions of any kind in the U.K. for the direct exportation of goods and services are exempt from VAT.

M. A. COLWELL—Editor.

## Feb P.W. Cover

Many enquiries have been received for information on the book and log book shown on the front cover of the February issue of *P.W.* Both can be obtained from the Radio Society of Great Britain, 35 Doughty Street, London, W.C.1. "How to Listen to the World" costs £2 post paid. The log book shown is intended for transmitting Amateurs and costs 60p post paid but another one, intended for listeners, is available at 45p post paid.

## Cordless Iron

This cordless soldering iron comes from the U.S.A. It is completely portable needing no mains power for operation. It has its own power supply which is automatically charged from the stand which itself is connected to the mains. There is a small light near the tip which is very useful for seeing exactly where you are applying heat.

The iron heats up in under 5 seconds and has an "indestructible" iron-plated bit. It costs £9.25 complete with charging stand and fine bit. A heavy-duty bit is also available.

The exclusive distributors in Great Britain are *Pact International Electronics Ltd.*, P.O. Box 19, Royston, Herts, SG8 5HH.



## Sonex 1973

The technical author and writer Donald Aldous will be heading a small team to organise the Special Features at "Sonex '73".

Two recital/lecture sessions will be presented each day at the Exhibition's new venue the *Excelsior Hotel, London Airport, Heathrow*.

Speakers will include Bert Webb, who will lecture on pickups, arms and turntables and Kenneth Shearer, speaking on listening room acoustics.

There will also be a lecture on tape cassettes and an examination of current loudspeakers and trends.

Sonex '73 will run from Friday, March 30th to Sunday, April 1st, inclusive.

## Sound '73

"Sound '73" is the exhibition run by the Association of Public Address Engineers. New P.A. equipment and new techniques in the public address and allied fields will be on show.

As in past years, there will be a lecture programme held in the hotel's "City Room". John Maunder from Shure Electronics will give a lecture and demonstration on microphones on Tuesday, 13th March at 14.30hrs.

Mike Beville from Audio and Design Recordings Ltd. will lecture on Components and Limiters (Wednesday at 14.30hrs.)

On Thursday March 15th at 10.30hrs, a member of the Hornsey College of Art will talk on Industrial design of Public Address Equipment.

Venue will be the Bloomsbury Centre Hotel, March 13-15, from 10.00-18.00hrs.


## Jermyn Inverters

Jermyn Distribution market two inverters, both giving an output of 250V. Input for the 150W version is 12V and for the 300W type, 24V.

A feature of the design enables these inverters to charge the 12/24V batteries up to 10A when plugged into a power socket.

If the mains supply fails, the inverter automatically switches to its "invert mode" providing 240V emergency power immediately.

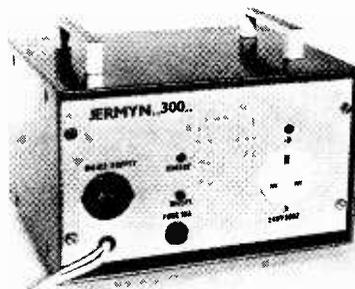Should the unit be accidentally overloaded its drive is so adjusted, that the output voltage falls completely, switching the



## I.E.E. Conferences

The following new conferences to be held in 1973 and 1974 are being organised by the Institution of Electrical Engineers.

"Electrical Signals from the Brain" 27-30 August 1973—in Oxford.

"Symposium on Electromagnetic Wave Theory" 8-12 July 1974—in London.

Further details of the conferences mentioned above are available from the *Conference Department, IEE, Savoy Place, London WC2R 0BL*.


## De-soldering Unit

In the February issue we mentioned the Litesold De-Soldering Unit and a misprint stated the price at £.75. This should have read £2.75. Apologies to Light Soldering Developments and any readers that may have been inconvenienced.

unit off, eliminating any problems.

An internal 15A fuse blows should the battery leads be connected wrongly. Indicator lights illuminate to show whether the unit is charging a battery or providing a 250V 50Hz output.

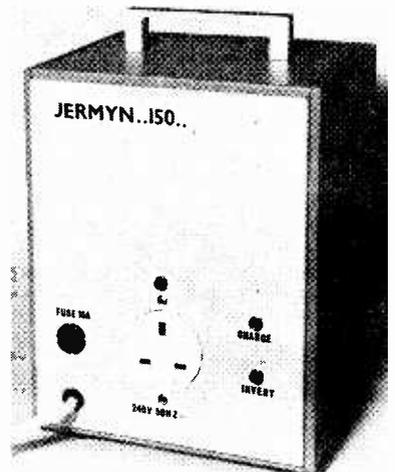Both types of inverter can be obtained in kit form or already built. The kit for 150W costs £25 (£29 built) and 300W £34 (£39 built). *Jermyn Distribution, Vestry Estate, Sevenoaks, Kent*.



# improving VHF radio

A.N. AINSLIE



VHF radio provides a most useful signal source for any hi-fi enthusiast and, despite the 15 kHz frequency limits, the live BBC broadcasts are certainly up to the standards of the finest records.

The advantages are numerous—being a non-mechanical system the distortion is very low and the self-generated noise is also very low, the result being a large dynamic range and the possibility of encoding two channels on a single signal. This, plus the excellent BBC technique, makes f.m. radio an invaluable source of material. Unfortunately there are several difficulties in securing top quality f.m., regardless of the equipment used.

## SIGNAL-TO-NOISE

Referring to Fig. 1, it can be seen that the performance of a receiver depends on the strength of the signal applied to the aerial socket of the receiver. The mono signal-to-noise ratio assumes an optimum value (usually 50 or 60 dB) with only a few  $\mu\text{V}$  input—even on cheap tuners. The signal-to-noise performance does not improve so rapidly on stereo, however, and in many cases could be improved on even with inputs in the region of a few hundred  $\mu\text{V}$ —hence the increase in noise on stereo

in most situations. A person who gets no increase in noise is indeed most fortunate and need read no further!

As regards crosstalk and distortion, these parameters usually reach optimum values with fairly small inputs and usually there is not much improvement to be had by an increase in the signal.

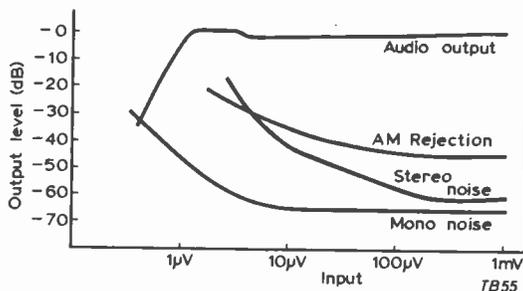



Fig. 1: Graphs comparing receiver performance with the input signal level.

Very few people are fortunate enough to be able to receive "near perfect" stereo without a large aerial, loft or roof mounted. A large aerial, besides having the necessary gain usually has the advantage that it is highly directional and eliminates multipath distortion from reflected signals. In many situations, a reasonably large aerial, three or more elements, carefully sited, and with a low loss feeder gives good stereo but perhaps not of the very highest quality.

The major downfall in domestic stereo reception is that of "stereo" noise—perhaps not excessive but sufficient to mar an otherwise excellent signal. The obvious way to reduce this noise is to increase the signal feeding the tuner by an "aerial amplifier". At present in this discussion we must assume that the amplifier be perfect, having gain but generating no noise itself.
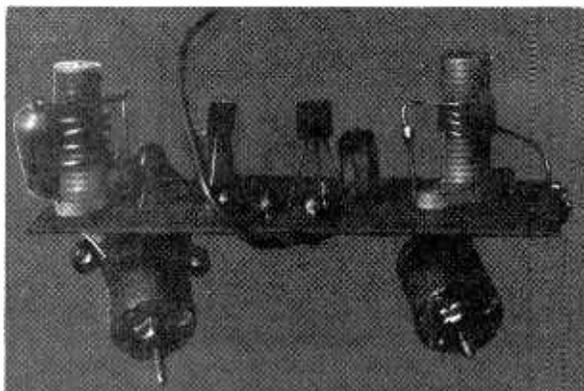
## OTHER NOISE

At this point many readers may well be wondering about the other forms of noise, thermostats, car ignition and other spurious signals. These signals



First of the two VHF amplifiers described in the article. This one uses field-effect transistors.

are picked up by the aerial and sometimes, even, by the feeder, and consequently will be amplified, together with the f.m. signal, by our "ideal" amplifier, which we are using to combat stereo noise. This brings us to the last important parameter of f.m. receivers, amplitude modulation limiting.

The "ideal" f.m. tuner is designed to respond to f.m. only and a.m. signals are rejected to an infinite degree. Unfortunately, no receiver is perfect and some degree of sensitivity to a.m. is unavoidable.

The a.m. limiting of the receiver improves with increasing signal input, as seen from Fig. 1, so that increasing the signal and spurious a.m. together actually reduces the level of audible interference. Unfortunately, when the receiver is switched to receive a stereo transmission, the stereo decoder in the receiver is actually only sensitive to amplitude modulation of the stereo subcarrier. In the decoder some measure of a.g.c. is applied to the subcarrier amplifier and this maintains a constant level of stereo interference from an a.m. signal regardless of the actual input voltage to the tuner.

It can therefore be seen that whilst increasing the tuner input with an "ideal" amplifier, the "stereo" interference level remains substantially constant whilst the "mono" component of the audible interference has been reduced by virtue of the amplitude limiting of the f.m. discriminator.

## AERIALS

Earlier in this discussion, we talked of elaborate and efficient aerial systems but the previous discussion on aerial signal amplification implies that, with a good amplifier, an aerial providing only a minimal "clean" signal can be used to run an f.m. tuner with a high degree of success.

Unfortunately, some tuners are not so sensitive as others and sometimes require millivolts to function at their best. This means considerable amplification of the few tens of microvolts coming from a rather poor aerial!

The better tuners nowadays use f.e.t.'s in the input circuits to keep noise to a minimum and to keep cross modulation low; so any proposed amplifier should have at least as good a performance as the front end of the tuner.

This is very demanding when tuners such as Sony, Radford and Fisher are considered, but it is possible to improve these tuners on a very poor signal by a remarkable degree.

To design an amplifier with a front-end comparable to the best tuners use has to be made of f.e.t. devices which possess the best noise properties of all the common solid state devices presently available and are responsible for the excellent performance of the best tuners.

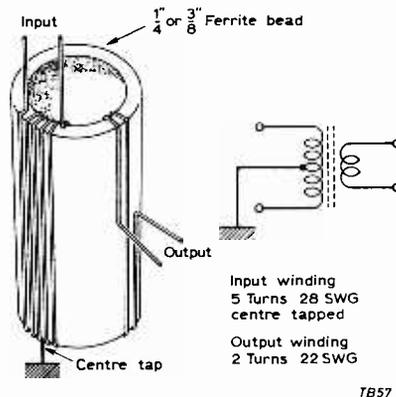


Fig. 3: Details of simple transformer to match balanced 400Ω feeder to 75Ω coaxial feeder.

The design chosen for the amplifiers in this article is not often used with solid state devices but was once very common with valve Band III television tuners. The amplifier is a cascode configuration giving reasonable gain with very low noise and good cross modulation.

The input to the amplifier, Fig. 2, is 75Ω co-axial feeder so Fig. 3 shows a transformer that can be constructed from a small ferrite bead for 400Ω balanced feeder.

## THE PCB

The amplifier can be very easily built on a single piece of printed circuit 4"×2" and it is recommended that fibreglass board be used.

To etch the required print design as shown in Fig. 4 (full size), the diagram is traced on to the copper side of the print with carbon paper and the marked areas painted in with high quality enamel. When the paint is dry, the print is immersed in the etching solution and agitated until completely etched (only paint and base material can be seen). The etching solution can be ferric chloride solution but a useful alternative is "Liquor-Ferri Perchloridi Fort" which is obtainable from chemists and should be used undiluted. Rub the copper surface of the board with "Ajax" or similar scourer before painting, to ensure a clean surface.

The enamel paint can be removed with paint stripper once the etching is complete and the board washed and cleaned with wire-wool. The holes for the components should be drilled with a 1/32" drill, preferably in a wheel brace.

Construction is straightforward except that the f.e.t.'s should be left until last and soldered in with the iron disconnected from the mains—surprisingly little voltage will break down the gate junction.

The coils, Fig. 5, are wound on the formers which are located on the board and stuck with Araldite. The 30pF variable capacitors must be connected so that the rotor is connected to the earth line. The author used 30pF Philips beehive trimmers mounted



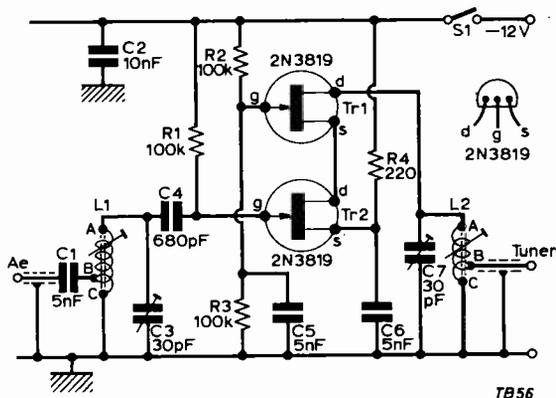


Fig. 2: Circuit of the amplifier using two f.e.t.'s.

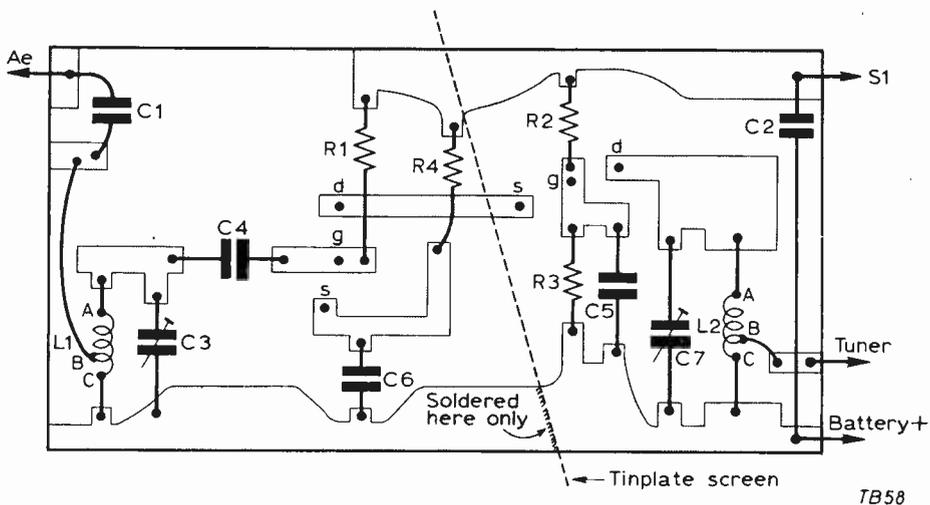

TB58

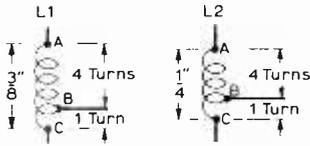

Note:  
L1 and L2 both  
wound on  $\frac{1}{4}$ " Dia  
formers using  
18 SWG copper  
wire

TB59

Fig. 5: Winding information for L1 and L2.

## ★ components list

### FET AMPLIFIER

#### Resistors

R1 100k $\Omega$  R2 100k $\Omega$  R3 100k $\Omega$  R4 220 $\Omega$   
All  $\pm 5\%$

#### Capacitors

C1 5nF 400V C5 5nF 12V  
C2 10nF 12V C6 5nF 12V  
C3 30pF Trimmer C7 30pF Trimmer  
C4 680pF 12V

#### Miscellaneous

Tr1-Tr2, 2N3819. On-off switch. 12V battery. Co-axial sockets (2). PCB, see text. Coil formers.

### BF200 AMPLIFIER

#### Resistors

R1 1.5k $\Omega$  R3 6.8k $\Omega$  R5 10k $\Omega$   
R2 10k $\Omega$  R4 1.5k $\Omega$  R6 6.8k $\Omega$   
All  $\pm 5\%$

#### Capacitors

C1 1nF 400V C6 30pF Trimmer  
C2 30pF Trimmer C7 10nF 12V  
C3 10nF 12V C8 680pF 12V  
C4 680pF 12V C9 1nF Feed-through  
C5 1nF Feed-through C10 30pF Trimmer

#### Miscellaneous

Tr1-Tr2, BF200. On-off switch. 12V battery. Co-axial sockets (2). PCB, see text. Coil formers.

### POWER SUPPLY

#### Capacitors

C1 100nF 1kV C3 2000 $\mu$ F 10V C5 100nF 12V  
C2 2000 $\mu$ F 10V C4 1000 $\mu$ F 15V

#### Miscellaneous

R1, 10 $\Omega$   $\pm 5\%$ . D1-D2, 1N4002. D3, 12V zener 2W, mounted on aluminium  $2" \times 1"$  minimum. T1, 8V bell transformer. Fuse, 1A. On-off DP mains switch. LP1, 3.5V 20mA for FET amp + 2 stages or 3.5V 40mA for FET amp + 4 stages.

Fig. 4: Printed circuit board, for the circuit of Fig. 2, shown actual size.

on the copper side of the board. The resistors should be small low noise types and the capacitors need only be low working voltage.

The completed amplifier should be screened by placing tin plate at the position indicated and soldered to the positive line as support.

The amplifier is mounted in a small wooden box, measuring approx. 4" cube internally, covered inside with tin foil, which is connected to the positive supply line. A front panel can be made from a piece of double-sided copper board with the input and output sockets and the on/off switch. The printed board is soldered to the front panel by the positive line, so earthing the front panel.

With a 12V battery connected, the output is fed to the tuner and the input is fed by an "inefficient" aerial, in most cases a short piece of wire.

With the amplifier on, the tuner is switched to the local stereo station and the tuning capacitors C3 and C7 set midway. The cores in the coils (L1 and L2) are then adjusted to give the strongest signal, best observed on a tuning meter or audibly by judging least noise.

The amplifier is then assembled in the case and the capacitors C3 and C7 tuned to give the best signal. The tuning will be sharp and critical, so care should be taken when adjusting.

The amplifier, when connected between the proper aerial and tuner, should have sufficient gain to overcome most of the tuner noise, without introducing significant noise itself. When used on weak local radio stations, the improvement will be very marked, especially in mono. Unfortunately, this usually requires the amplifier to be re-tuned to the local channels. However, connecting 27 $\Omega$  resistors across L1 and L2 will broaden the bandwidth considerably, enabling the amplifier to be used over a number of channels.

## BF200 AMPLIFIER

However, for many of the "poorer" tuners, this amplifier will still not be good enough to fully drive the tuner on a moderate signal. For optimum stereo in such cases two of the amplifiers could be

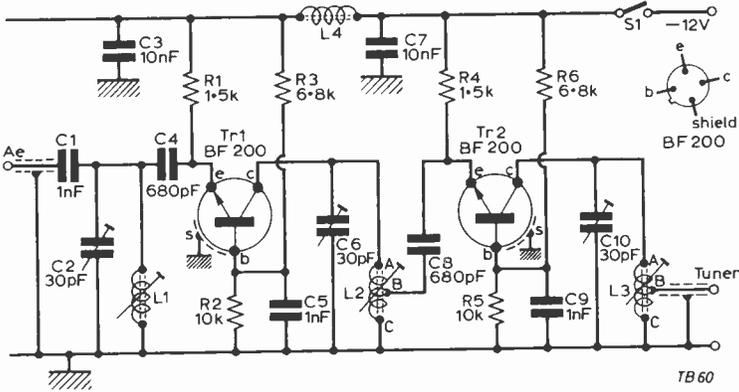


Fig. 6: Circuit of the second amplifier, using BF200 transistors.

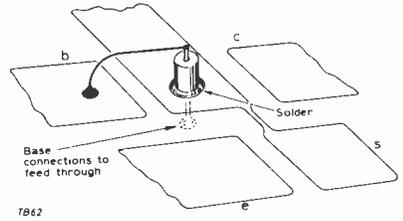


Fig. 8. Method of mounting feed-through capacitors.

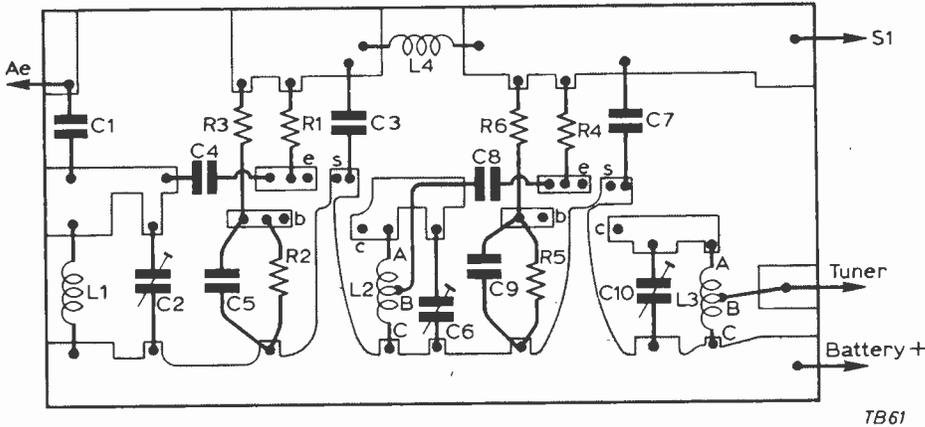


Fig. 7: Illustration, actual size, of the printed circuit board for the BF200 amplifier.


connected in series. The price of f.e.t.'s, however, makes this uneconomical and ordinary low-noise silicon transistors used after the f.e.t.'s work very well. The proposed amplifier, Fig. 6, is two stages of a conventional r.f. amplifier design. Fig. 7 shows a full size print layout for two stages, although for additional gain or bandwidth more stages can be used, although greater than five would be difficult to keep stable.

The board is etched in the same manner as before and a similar front panel and box are prepared. Alignment is the same, tuning the coils and finishing with the capacitors.

The transistors specified are BF200 and these should be used for at least the first two stages to keep the noise level down; after this such transistors as 2N706 work very well. An alternative for the BF200 is BF180 or BF181.

Fig. 8 shows how C5 and C9 are constructed with 1000pF feed-through capacitors. L4 is made by wrapping a few turns of 36s.w.g. d.c.c. copper wire round a ferrite bead. Fig. 9 gives the winding information for L1, L2 and L3.


The two amplifiers just described will enable good stereo to be obtained from a mediocre signal without the need for a "fancy" tuner. The improvement that can be expected depends greatly on the individual circumstances. The author has used the amplifiers with a Sony ST5100 tuner and a poor aerial and found the results almost as good as when a proper aerial was correctly installed on the roof. The cost of a pair of amplifiers is comparable to a decent

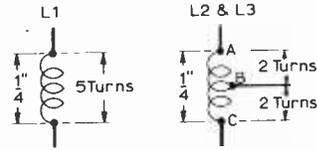

Note:  
L1 L2 & L3 wound on 1/4" Dia formers.  
L1 use 22 SWG copper wire.  
L2 & L3 use 18 SWG copper wire.

TB63

Fig. 9: (above) Details of the three coils shown in Fig. 6. In the photograph (below) the second amplifier board is shown soldered to the front panel consisting of double-sided p.c.b.

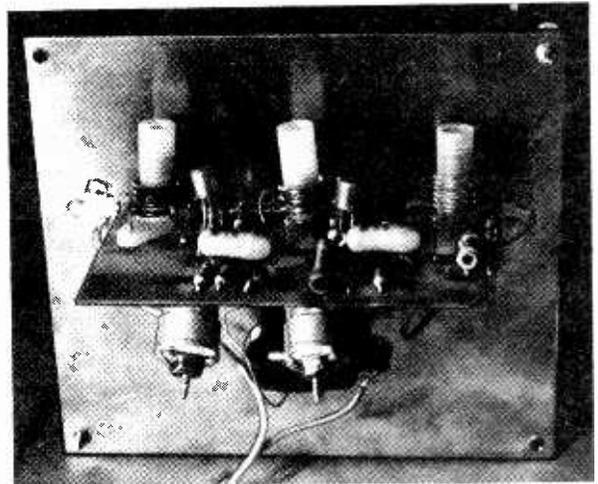

aerial less download and fitting, so financially it is a viable proposition, although not a substitute for a first class aerial.

In order to split one signal to run several outlets and obtain maximum signal at each of the outlets, a star-splitter is used. This arrangement provides correct impedance matching throughout the system.

Figure 10 shows the circuit of a star-splitter. The value of the resistors R depends upon the impedance of the feeders (Z) usually 75Ω, and on the number of outlets (n) which can be as many as required.

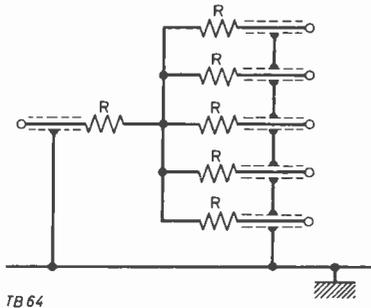


Fig. 10: Circuit of star-splitter enabling several outputs to be obtained from a single input.

The relationship is:—  $R = Z(n-1)/n+1$ . For example, for a splitter for a 75Ω system with two outputs the resistors to the nearest preferred value are 27Ω. Small 1/4W resistors are suitable and indeed preferable to physically larger types.

All of these systems involve a loss of signal and this must be made up by amplification before the splitting. For a distribution system, splitting six or

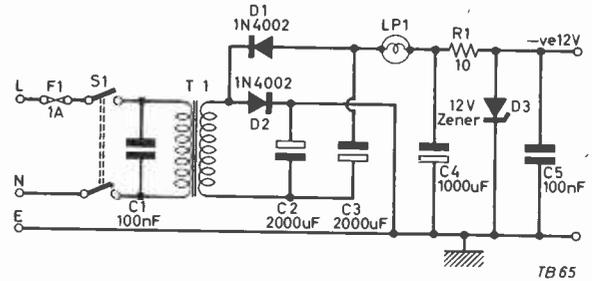


Fig. 11: Suggested power supply for the v.h.f. amplifiers.


eight ways, two f.e.t.'s followed by three transistors should be adequate. One important point to note is that the outputs of the splitter must all be loaded by a 75Ω resistor when not in use, otherwise a loss of signal results and the splitter may form the node of standing waves in the feeder.

If either of the amplifiers is built as a distribution system, it is perhaps a good idea to build a small mains unit to power the whole system. It is desirable that this supply be stabilised to guard against changes in the tuning of the f.e.t.'s if the supply voltage changes.

Fig. 11 gives a circuit of a simple power supply based on an 8V bell transformer with voltage doubling and zener stabilisation. The lamp, LP1, can be used to give on/off indication.

It is hoped that this article has given sufficient information for the home constructor to build an amplifier system to improve the performance of a tuner to reach the very high standards of the B.B.C. stereo transmissions. ■

## EXPERIMENTERS CORNER

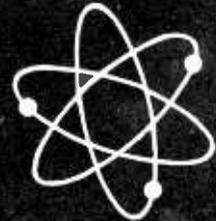

### NOVEL TONE GENERATOR

WHENEVER home constructors and experimenters need to build a source of audio frequency, the choice nowadays is usually a transistor multivibrator. The reasons for this selection are easily understood. It requires few components, avoids the need for a transformer and gives a strong output signal. These virtues outweigh the fact that the square-wave output does not make for a particularly pleasing sound when amplified and fed to a loudspeaker.

In designing the a.f. tone generator to be described, the author set out to devise a circuit which would possess all the aforementioned merits of the multivibrator and at the same time give a better audio tone. In the circuit shown in Fig. 1—which, as a transistor circuit, is thought to be original—the writer believes these objectives have been largely achieved.

### N. NAUGHTON

It will be noticed that the circuit is actually simpler than a multivibrator and basically it is a sawtooth generator. Like all sawtooth generators it depends upon the charge and discharge times of a

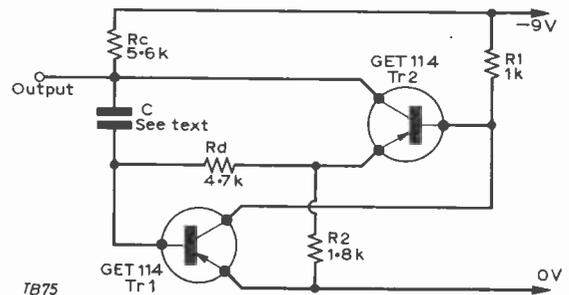


Fig. 1; Circuit of tone generator.

capacitor for its action. But as linearity of the sawtooth ramp is not important for the required purpose, the provision of constant current is omitted in the circuit shown.

In Fig. 1 the two transistors perform the function of switches and the circuit operates as follows:—capacitor C charges via the charging resistor R<sub>c</sub> and the base-emitter junction of Tr<sub>1</sub>. The charging current flowing through the B-E junction turns on Tr<sub>1</sub> and the flow of collector current causes a voltage drop across R<sub>1</sub> which results in the potential on the base of Tr<sub>2</sub> dropping to a level low enough to turn off Tr<sub>2</sub>. As the charge on C rises the charging current diminishes so that the potential on the base of Tr<sub>1</sub> decreases to a point where Tr<sub>1</sub> turns off. The base of Tr<sub>2</sub> now goes strongly negative causing Tr<sub>2</sub> to turn on and C now discharges via Tr<sub>2</sub> into the discharge resistor R<sub>d</sub>. While discharge current is flowing in R<sub>d</sub> it maintains a positive potential on the base of Tr<sub>1</sub> thus preventing further switching action during the period of discharge. When C has discharged, it again draws current through Tr<sub>1</sub> once again turning off Tr<sub>2</sub>. The cycle then repeats.

The foregoing is a simplified description of the operation but many will find it interesting to measure the balance of currents and potentials which exist in the circuit under static conditions when C is removed.

The frequency of oscillation is not readily calculated since it is influenced by several factors one of which will be determined by the type of coupling employed to connect the output. However, for practical purposes values of C ranging between 2 $\mu$ F and 5000pF will cover the audio spectrum.

## APPLICATIONS

A useful feature of the circuit is that it uses only one capacitor. With the values given, the generator should oscillate at any point within the a.f. range the actual point being determined by the value of C selected. Thus it becomes a simple matter to construct a signal generator giving a number of spot frequencies as desired; the only extra components needed being a multi-pole switch and a few capacitors. Many other audio applications will doubtless occur to readers.

For those interested, an interesting feature of the circuit is that because the charge and discharge paths of C are independent, the circuit can readily be made to produce right-handed or left-handed sawtooth waveforms. Moreover, by choice of p.n.p. or n.p.n. transistors, the polarity of either slope can be created as desired at source, thereby eliminating inverting stages. Although some value of R<sub>d</sub> is essential for circuit function, in practice this can be less than 100 $\Omega$  thus allowing fast flyback times. There is no reason why C can not be a very large value electrolytic so that the circuit can easily be adapted for timing application.

## GENERAL

No constructional details are given since the generator will mostly be incorporated in some larger project. Experimenters can assemble the components on a length of Veroboard or tagboard.

As stated at the outset, the circuit is primarily intended as an a.f. generator and the values given have been chosen to give a roughly pyramid waveform at the collector of Tr<sub>2</sub>. A strong output signal is also available at the collector of Tr<sub>1</sub> but this is a

steep sided pulse and the "softer" toned signal at the Tr<sub>2</sub> output can be readily appreciated. Coupling of the output is perhaps best determined to suit the individual case but too tight a coupling to the Tr<sub>2</sub> output is best avoided. This is less important if the Tr<sub>1</sub> output is used.

With the component values given, the circuit places no critical demands on the transistors' characteristics. Seven widely differing types, in various combinations, have been tried with success. However, experimenters using low values of R<sub>d</sub>—especially with a high value of C—should note that Tr<sub>2</sub> must then be a device capable of handling the heavier discharge current. Tr<sub>1</sub> and Tr<sub>2</sub> must both be either p.n.p.'s or n.p.n.'s, the -9V becoming +9V if n.p.n.'s are used. ■

# TELEVISION

## APRIL ISSUE

### TOUCH TUNING

The latest development in television receiver design is touch-sensitive tuning, using touch-button units which provide a completely non-mechanical means of channel changing. A very high-impedance electronic switching circuit selects the required channel when a finger is placed across a pair of contacts to complete the appropriate circuit. Several models featuring touch tuning are now on the market and this month we are investigating the technique and the circuitry involved. The change from mechanical to all-electronic channel selection should improve the stability and reliability of TV tuning.

### BAND III PREAMPLIFIER

Another Bunney wideband aerial amplifier intended for DX work. The two-transistor (BF272) design on-test lifted a weak signal from mere traces of line sync pulses to a solidly locked noisy image. Part of Roger's present programme of improving his DX receiving equipment.

### SERVICING

Plenty on the servicing front this month. John Law in his new fault-finding series investigates the line timebase used in most KB-STC models. Vivian Capel completes his guide to power supply circuit servicing. Les Lawry-Johns starts on the single-standard Bush-Murphy TV181S/V2016 series. And Caleb Bradley takes us further with the BRC 2000 colour chassis.

**PLUS ALL THE REGULAR FEATURES**

**ON SALE MARCH 19**

# IC POWER AMPLIFIER



D. SILVESTER

THE audio amplifier to be described was designed to deliver in excess of 10W r.m.s. into an 8Ω load, whilst being constructed in a 4½in. x 3½in. x 2in. diecast aluminium box. The size of the box is, in fact, limited not by the size of the i.c. but by the passive components, especially the output capacitor which must be included in the circuit. The use of the i.c. has added one inestimable advantage in that the current through (and the power dissipated by) the output stage under overload conditions can be limited. It is thus possible for the output to be short circuited without disastrous results.

The i.c., although capable of giving a 1 watt output without any other transistors, has been primarily designed for use as the driver stage of an amplifier

capable of delivering up to 35 watts into an 8Ω load.

A description of the working of the i.c. has not been included as it is not necessary for the constructor to completely understand the operation of the device for it to be used successfully.

Two transistors in the i.c. are responsible for the current and power limiting facility. It was calculated that under maximum current limiting and with the normal current gain of a power transistor, the output stage of the i.c. would be overloaded. One way of curing this fault is to use a Darlington transistor. This in fact was done, the Darlington pair being contained in the TO3 metal case of the power transistor. The current gain of the complementary Darlington pairs is in excess of 1000.

## CALCULATIONS

The final circuit used for the prototype amplifier is shown in Fig. 1 but since other constructors may wish to use different power supply voltages and load impedances from those used by the author, the method of calculation of the current and power limiting components is given. The basic circuit should be adhered to as it is only the values of R6, R8, R9 and R11 which need to be changed.

The following section shows the worked equations used to give the value of the components in Fig. 1.

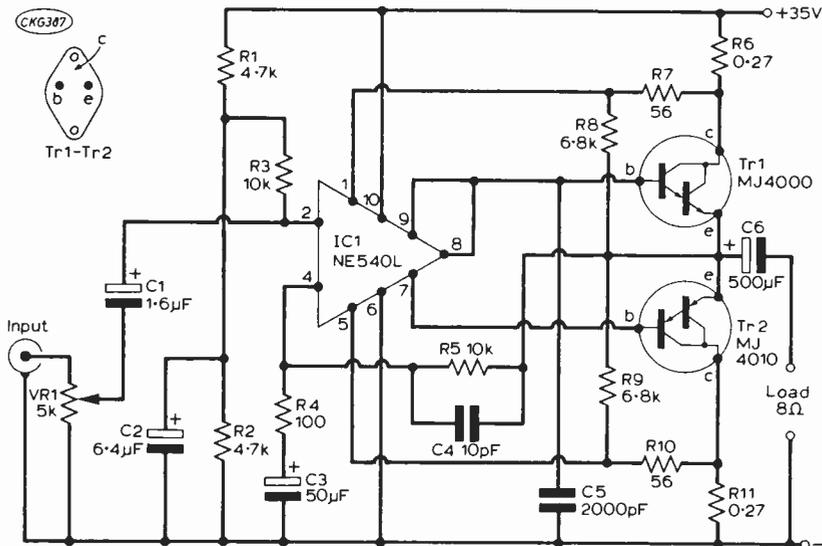


Fig. 1: Circuit diagram of the amplifier and pin connections for the output transistors.

# is this the price you pay?

Probably, if you're still using an ordinary soldering iron. Ordinary soldering irons can cause damage to transistors and integrated circuits — damage which wastes time and costs money. Now, with the unique ANTEX X25 and CCN low leakage soldering irons no harm can come to the most delicate equipment, even when soldered 'Live'. (You could be making quite a saving).



## MODEL X25

220-240 Volts or 100-120 Volts.

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C.

This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.

**PRICE: £1.75**  
(rec. retail)

Suitable for production work and as a general purpose iron.

## MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage.

Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

**PRICE: £1.80** (rec. retail)  
OR Fitted with triple-coated, iron nickel and Chromium bit 1/8".

**PRICE: £1.95** (rec. retail)

## MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110. **PRICE: £1.83** (rec. retail).

## MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE: £1.70** (rec. retail)

## MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220. **PRICE: £1.70** (rec. retail)

## MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"

**PRICE: £1.95** (rec. retail)

## MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. **PRICE: £2.75** (rec. retail)

## MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, stand and "How to Solder" booklet. **PRICE: £2.40** (rec. retail)



From radio or electrical dealers, car accessory shops or in case of difficulty direct from: —  
**ANTEX LTD. FREEPOST**  
(no stamp required) **PLYMOUTH**  
**PL1 1BR** Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
- Please send the following

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME .....

ADDRESS .....

PW4

BRAND NEW

SEMICONDUCTORS & COMPONENTS

GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

Table of transistor components with columns for part number, gain, and price. Includes various types like 2N4931, 2N4932, etc.

TTL. LOGIC I.C. NEW PRICES

Table of TTL Logic ICs with columns for part number, price, and quantity. Includes 7400, 7401, 7402, etc.

SUB-MIN ELECTROLYTIC

Table of sub-mini electrolytic capacitors with columns for value, price, and quantity. Includes values like 0.1, 0.22, 0.47, etc.

SILICON RECTIFIERS

Table of silicon rectifiers with columns for PIV, current, and price. Includes 1A, 10A, 100A, etc.

DIODES & RECTIFIERS

Table of diodes and rectifiers with columns for part number, current, and price. Includes 1N34A, 1N41, etc.

OPTOELECTRONICS

MINITRON 3015F 7-SEGMENT INDICATOR (16 PIN DIL) £2.00. May be driven by SN7447.

VEROBOARD

Matrix 0.15 0.1. 2 1/2 x 3 1/2 in 25p. 2 1/2 x 5 in 25p. 3 1/2 x 3 1/2 in 25p. 3 1/2 x 5 in 25p.

SLIDE POTENTIOMETERS

58 mm. TRACK SINGLE GANGED. LOG or LIN 1k to 1M. 40p each.

MULLARD C280 M/FOIL CAPACITORS

0-01, 0-022, 0-033, 0-047 5p each. 0-068, 0-10 4p each. 0-15, 0-22, 0-33 3p each.

WIRE-WOUND RESISTORS

2-5 watt 5% (up to 270 ohms only), 7p. 5 watt 5% (up to 8-2k only), 9p. 10 watt 5% (up to 20k only), 10p.

"SCORPIO" CAP DISCHARGE IGNITION SYSTEM. (As published in P.E. November 1971). Complete kit £10-00. P. & P. 50p.

POTENTIOMETERS Carbon: Log. or Lin., less switch, 15p. Log. or Lin., with switch, 37p. Wire-wound Pots (3W), 8p. Twin-ganged Stereo Pots, Log. or Lin., 45p.

PRESETS (CARBON)

0-1 Watt 5% VERTICAL 8p. 0-2 Watt 5% OR 0-3 Watt 7p HORIZONTAL 8p.

SPECIAL OFFER

TOSHIBA TH9015F 20 WATT AMP £3-50 TH9014P PRE-AMP £1-25

Post & Packing 13p per order. Europe 25p. Commonwealth (Air) 65p (M.A.). Matching charge (audio transistors only) 15p. extra per pair. Prices subject to stock availability.

Tel. 01-452 0161/2/3 Telex 21492 A. MARSHALL & SON 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2 CALLERS WELCOME HRS. 9-5.30 MON.-FRI. 9-5.0 SAT.

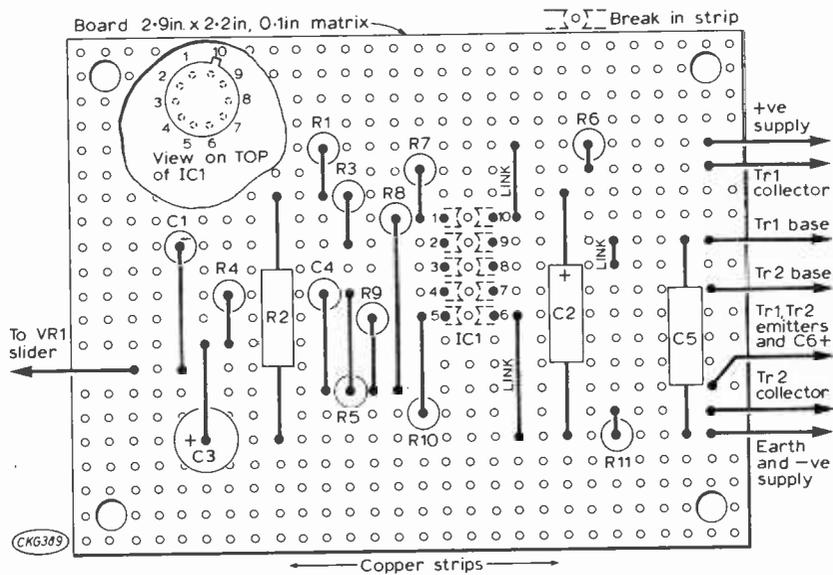


Fig. 3: Component layout on top of veroboard, the copper strips running horizontally underneath.


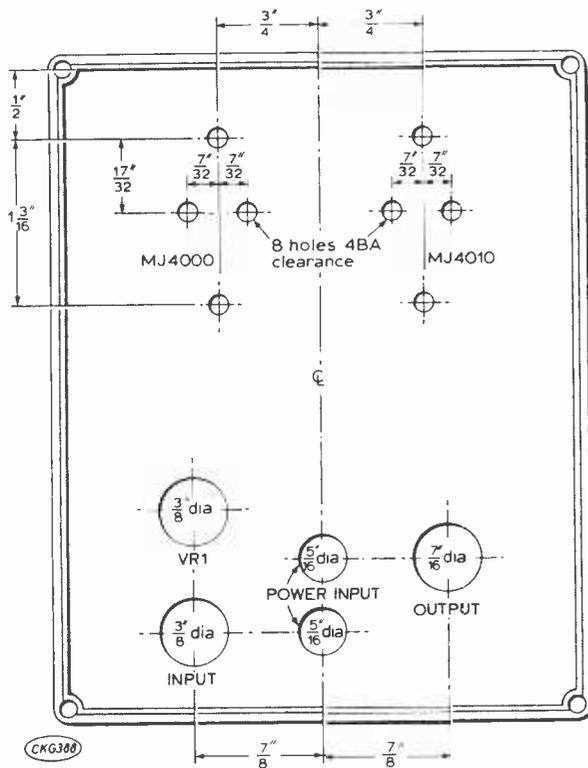


Fig. 2: Drilling details for the box lid on which components are mounted

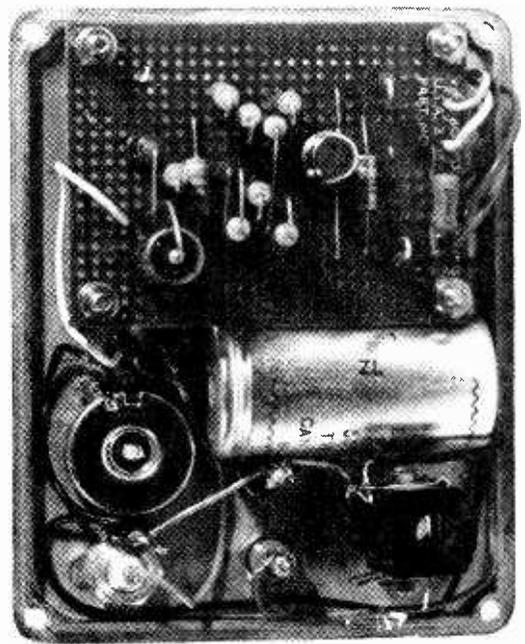They are based on a supply voltage ( $V_{cc}$ ) of 35V and a loudspeaker impedance of  $8\Omega$  ( $R_L$ ). Before beginning the calculations it must be remembered that there are two limitations imposed by the active devices used; the supply voltage must be in the range 10 to 40V, and the maximum current through the transistors Tr1, Tr2 must not exceed 4A. We can calculate:



This view of the completed amplifier emphasises the restrictions on the physical size of the output capacitor C6.

Peak current in transistors is:

$$\frac{V_{cc}}{2R_L} = 2.2A (I_{pk})$$

If this value is above 4A we must use either a lower supply voltage or higher load impedance. To provide current limiting of this value and assuming no voltage drop across R7, R10 we calculate the values of R6 and R11 as:

$$R6 = R11 = \frac{650mV}{I_{pk}} = \frac{0.65}{2.2} = 0.296 \Omega$$

The nearest preferred value of resistor, which must be lower in value than the calculated value, is 0.27Ω. The basis of the working of the power limiting facility is difficult to explain in such a short article but works on the principle that both a high voltage across or a high current through a transistor and its network of resistors (Tr1, R6, R7 and R8) will tend to turn off the transistor. The resistor network acts to sense the power dissipation in the transistor and to limit this dissipation. The value of R7 and R10 is 56Ω. In all cases the value of R8 and R9 is:

$$R8 = R9 = \frac{V_{cc}}{6mA} = 5.8k\Omega$$

The next highest preferred value, 6.2kΩ, is rather difficult to obtain and the value has been increased to 6.8kΩ. The voltage gain of the circuit is 100 and although this may be altered by changing the value of R4, the effect of such a change on the stability of the amplifier is difficult to predict. Under d.c. conditions the capacitor C3 represents an open circuit and the d.c. gain becomes zero, the voltage at the emitters of the two transistors, determined by the ratio of the values of R1 and R2, being at half the supply voltage.

## ★ components list

### Resistors

R1 4.7kΩ	R5 10kΩ	R9 6.8kΩ
R2 4.7kΩ	R6 0.27Ω ±.02	R10 56Ω
R3 10kΩ	R7 56Ω	R11 0.27Ω ±.02
R4 100Ω	R8 6.8kΩ	VR1 5kΩ log

All ½W 5% except R6 and R11

### Capacitors

C1 1.6μF 40V	C4 10pF
C2 6.4μF 25V	C5 2000pF
C3 50μF 35V	C6 500μF 50V

Note: C6 should not be over 2½" long and 1" dia.

### Semiconductors

Tr1 MJ4000 Tr2 MJ4010  
(both with mica washers and bushes)

IC1 NE540L

Available from SCS Components, POB 26, Wembley, Middlesex

### Miscellaneous

Diecast box, 4½" x 3½" x 2". Veroboard 2.9" x 2.2", 0.1" matrix. Input socket, Output jack socket.

The component board is a 2.9in. x 2.2in. piece of 0.1 matrix veroboard, with the copper strips running along the 2.9in. length of the board, Fig. 3. After cutting the strips below the i.c., drilling the mounting holes and cleaning up the rough edges, a few moments should be spent with a meter checking that no lines are shorted together and that the strips below the i.c. are completely severed.

There should be no difficulty in constructing the board, but it is advisable to use different coloured wires for the flexible connections as this assists in the final wiring. The capacitor C6 is held in place by its wire leads, the positive end of the component being connected to the emitter of Tr1. The circuit board is held above the transistors on four 4BA screws with either two sets of nuts and washers or lin. long spacers. The nut heads are stuck on the box lid with epoxy resin adhesive.

The final stage of wiring consists of connecting all the leads from the board to their respective terminations, wiring a negative supply earth lead to the earth end of the output socket, the negative supply socket, and the solder tag on the input socket. Lastly a wire is taken from the centre of the input socket to one side of VR1, the remaining potentiometer connection being taken to earth (the slider goes to the input on the board).

A power supply capable of delivering the maximum requirements of the amplifier must be used. In the author's case a supply of 35V at 2.5A. Under these conditions the amplifier was able to deliver nearly 15W r.m.s. into an 8Ω load. ■

## CQ! CQ! CQ! CQ! CQ!

### ISSUES WANTED

- ... issue of July 1972 P.W. for Texas Amp. Gen.—A. Palfreyman G3UHD, 39 Gledhow Park Avenue, Chapel Allerton, Leeds, LS1 45Z.
- ...1971 Issues of Practical Wireless, January, May & July issues.—Mr. Ong Choo Sian, Flat 12B, Jalan Berhala, Off Jalan Brickfields, Kuala Lumpur.
- ...Practical Wireless No. 5 Vol. 47—1971—E. Blackham, 89 Myatt Avenue, Parkfields, Wolverhampton, Staffs, WV2 2DN.
- ...May, June, July, September Practical Wireless for the year 1971. Also Jan. 71 P.E.—Nolan 274 Park Street, Islington, London, N1. 7VH.
- ...April 1970, Practical Wireless. To buy or borrow. All postage etc. paid.—A. Lythaby, 25 Greenhill Road, Oford, Sevenoaks, Kent.
- ...P.W. issues March 1972 to October 1972, will consider any offer.—Mr. J. Holland, 10 Coburg Road, Ramsey, Isle of Man.
- ...April, June, July 1967 and Feb. 1968 Practical Television—B. C. Meek, 39 Horsebrook Lane, Brewood, Stafford.
- ...(in good condition) August 1971 and April and March 1972 Issues P.W. Full price plus postage paid.—D. Mooney, 85 Aughincork Road, Glenanne, Co. Armagh, N. Ireland.
- ...P.W. Oct. 1971 Wall chart circuit building bricks. December 1971 issue of PW and Oct 1972 Aerial Data Wall Chart of P.W.—Loong Kok Chong, 1477, Main St. Jinjang North K. Lumpur, West Malaysia.
- ...P.T. Nov. 1971 to Feb 72.—K. Dodman, 2 Beaumont Road, Carlton Colville, Lowestoft, Suffolk.
- ...P.W. December 71, January & February 72 on loan. Will be returned.—S. G. Christian, Mulginagar Colony, Block II/B, Nizampura, Baroda, Gujarat State, India.
- ...P.W. containing the article on the Double Conversion Communications receiver. R. Thorneycroft, 12 Orchard Mead, Hatfield, Herts.
- ...Television for March, April, May and June 1972.—R. T. McCoy 34, Karana Avenue Grovedale, Victoria 3221, Australia.
- ...March 1972 "Television" with the servicing of the Bush TV103/TV105.—M. V. Gardner, 180 Clonkeen Crescent, Dun Laoghaire, C. Dublin, Ireland.
- ...issues of P.W. about ten years ago that covered an article on an oscilloscope. I have been given a scope but do not know the function of the controls.—P. Lysler, 17 Lapal Lane North, Lapal, Halesowen, Worcs.
- ...all back issues of P.W.—F. Murphy, 10 Upton Court, Upton, L49 1L6L, Wirral, Cheshire.
- ...issues of P.W. that contained details of capacitive discharge systems.—J. Smith, 9 Amherst Avenue, Handsworth Wood, Birmingham, B20 2LH.
- ...P.W. Jan. 1972, April 1972, E.E. Nov. 1971, Feb. 1972, March 1972. Will pay face value plus postage and packing. All replies answered. Redwood, 45A Lulworth Avenue, Poole, Dorset, BH15 4DH.
- ...P.W. February and April 1972.—Ramesh Udyawar, C/O Pos\* Box 610, Bombay 1, India.
- ...P.W. February 1972 issue containing details of the "Transistor Scope"—Mr. A. Chaplin, 26 Waking Avenue, Shoeburyness, Nr. Southend-on-Sea, Essex.
- ...P.W. January 1972—T. Fresson, Fernlie, Churt, Farnham, Surrey.
- ...May 1972 edition of Television or a photostat of the second part of the colour television project.—C. A. Wilson, 23 Friars Oak Road, Hassocks, Sussex.
- ...P. W. February, March, June and July 1968.—D. Applford, 34, Dennistead Crescent, Headingly, Leeds.
- ...wanted P.W. November 71 to March 72. Mr. C. S. Hodgson, 18 Kensington Avenue, Nornally, Teesside.
- ...January 1972. PW. or circuit and data for B.F.O.—E. Caines, 13 Batts Close, Pannycell Road, Bristol 5.
- ...November and December 1971 of P.W.—G. J. Dummett, 67D Shooters Hill Road, Blackheath, London, S.E.3.
- ...The issues of F.W. for September and October 1971.—J. Balicki, 3 Millfields, Writtle, Essex.

## CONSTRUCTION

The complete circuit is constructed in a diecast aluminium box using the lid to hold all the components and the rest of the box as the cover. Fig. 2 shows the lid marked out for drilling, after which the power transistors are mounted (the NPN transistor Tr1, MJ4000 on the left as seen in Fig. 2) using mica washers with bushes. It is best at this stage to check whether the collectors of the transistors have been accidentally shorted to the box lid. The remainder of components should be fixed to the box lid, a tag washer under the input socket nut providing the main connection to the lid.

# THE FREE HEATHKIT CATALOGUE

.....perhaps the most valuable stereo HiFi/Electronics kit publication available today



**NEW MULTI-SPEAKER KIT**  
Features Four KEF Hi-fi Drive Units. Offers monitor quality at lowest cost.

**NEW AM/FM STEREO RECEIVER KIT**  
Solid State FM IF Circuitry, two IC's, two ceramic filters. "Black magic" lighting.

**NEW PORTABLE ENGINE ANALYSER KIT**  
Versatile automotive testing and troubleshooting.

**LOW-PRICED TESTERS AND INSTRUMENTS**  
for the hobbyist and technician.

**PLUS**  
all the models you have read about in international publications.

**NEW 1214 SERIES STEREO HI-FI**  
Ideal for use for quadrasonic sound.

**the HOW AND WHY OF KIT BUILDING**  
Electronics is fun the HEATHKIT way.

**BUILD YOURSELF A PAIR OF SPEAKERS**  
in an evening - enjoy Stereo sound.

**GET THE BEST IN HI-FI**  
Enjoy worthwhile kit savings.

**SOMETHING FOR ALL THE FAMILY**  
even a battery charger for dad.

**LOW COST STEREO RECORD PLAYER**  
amazing sound value.

It's Free ... it's the latest Hi-Fi/Electronics catalogue from Heath the world-famous electronic kit manufacturers ... and it's yours on request. This latest catalogue will appeal to all the family. Stereo Hi-Fi, Transistor portables, Metal detectors, Electronic calculators etc. etc. You name it, Heath can supply. All models offer unbeatable specifications for price. Excellent continuous credit and no deposit terms available ... this even includes instruments. You cannot afford to miss reading this fine publication ... hurry, send off the coupon for your personal copy today.

Ask  
about our  
**No Deposit  
Terms**

Please send me a FREE Heathkit catalogue

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**HEATH**  
Schlumberger

Heath (Gloucester) Limited, Dept. PW 4/73  
Gloucester GL2 6EE. Telephone 0452 29451

Heath (Gloucester) Limited, Gloucester GL2 6EE

**Fully guaranteed Individually packed VALVES**

B131	£1.75	ECH84	45p	OA2	35p
CV31	35p	ECH200	62p	OB2	35p
DAF96	43p	ECLN90	42p	PAIC80	37p
DF96	45p	ECL82	35p	PC97	47p
DK96	45p	ECL83	70p	PC900	45p
DL92	32p	ECL96	40p	PC94	40p
DL94	45p	EPC36	45p	PC98	50p
DL96	45p	EPC74	£1.25	PC189	55p
DM70	30p	EP40	50p	PC8800	70p
DY86	33p	EP41	50p	PCF80	30p
DY87	32p	EP80	25p	PCF82	33p
DY802	48p	EP83	25p	PCF84	30p
EP802	48p	EP85	35p	PCF86	30p
EP800C/01	£1.00	EP86	30p	PCF90	70p
EP809	42p	EP89	28p	PCF201	73p
EP810C	90p	EP91	30p	PCF801	45p
EP820C	£1.20	EP92	35p	PCF802	50p
EA50	20p	EP183	30p	PCF806	70p
EA800	30p	EP184	35p	PCF808	85p
EA820	62p	EP200	75p	PC11200	70p
EB91	18p	EP141	50p	PC181	47p
EB933	50p	EP184	24p	PC183	30p
EB941	50p	EP185	42p	PC184	42p
EB981	31p	EP186	40p	PC185	42p
EBF80	40p	EP190	35p	PC186	43p
EBF83	40p	EP195	35p	PF1200	61p
EBF89	30p	EP160	85p	PL26	38p
EC801	30p	EP31	25p	PL81	48p
EC802	25p	EP40	40p	PL92	42p
EC803	30p	EP44	35p	PL93	40p
EC804	30p	EP47	70p	PL94	35p
EC805	40p	EP51	40p	PL90	73p
EC806	45p	EP56	40p	PL504	75p
EC808	37p	EP61	40p	PL509	£1.25
EC819	52p	EP68	40p	PL4	22.50
EC820	35p	EP70	50p	PL25	50p
EC822	35p	EP72	50p	PL41	30p
EC823	35p	EP74	50p	PL42	30p
EC824	35p	EP76	50p	PL43	30p
EC825	35p	EP78	50p	PL44	30p
EC826	35p	EP80	50p	PL45	30p
EC827	35p	EP82	50p	PL46	30p
EC828	35p	EP84	50p	PL47	30p
EC829	35p	EP86	50p	PL48	30p
EC830	35p	EP88	50p	PL49	30p
EC831	35p	EP90	50p	PL50	30p
EC832	35p	EP92	50p	PL51	30p
EC833	35p	EP94	50p	PL52	30p
EC834	35p	EP96	50p	PL53	30p
EC835	35p	EP98	50p	PL54	30p
EC836	35p	EP100	50p	PL55	30p
EC837	35p	EP102	50p	PL56	30p
EC838	35p	EP104	50p	PL57	30p
EC839	35p	EP106	50p	PL58	30p
EC840	35p	EP108	50p	PL59	30p
EC841	35p	EP110	50p	PL60	30p
EC842	35p	EP112	50p	PL61	30p
EC843	35p	EP114	50p	PL62	30p
EC844	35p	EP116	50p	PL63	30p
EC845	35p	EP118	50p	PL64	30p
EC846	35p	EP120	50p	PL65	30p
EC847	35p	EP122	50p	PL66	30p
EC848	35p	EP124	50p	PL67	30p
EC849	35p	EP126	50p	PL68	30p
EC850	35p	EP128	50p	PL69	30p
EC851	35p	EP130	50p	PL70	30p
EC852	35p	EP132	50p	PL71	30p
EC853	35p	EP134	50p	PL72	30p
EC854	35p	EP136	50p	PL73	30p
EC855	35p	EP138	50p	PL74	30p
EC856	35p	EP140	50p	PL75	30p
EC857	35p	EP142	50p	PL76	30p
EC858	35p	EP144	50p	PL77	30p
EC859	35p	EP146	50p	PL78	30p
EC860	35p	EP148	50p	PL79	30p
EC861	35p	EP150	50p	PL80	30p
EC862	35p	EP152	50p	PL81	30p
EC863	35p	EP154	50p	PL82	30p
EC864	35p	EP156	50p	PL83	30p
EC865	35p	EP158	50p	PL84	30p
EC866	35p	EP160	50p	PL85	30p
EC867	35p	EP162	50p	PL86	30p
EC868	35p	EP164	50p	PL87	30p
EC869	35p	EP166	50p	PL88	30p
EC870	35p	EP168	50p	PL89	30p
EC871	35p	EP170	50p	PL90	30p
EC872	35p	EP172	50p	PL91	30p
EC873	35p	EP174	50p	PL92	30p
EC874	35p	EP176	50p	PL93	30p
EC875	35p	EP178	50p	PL94	30p
EC876	35p	EP180	50p	PL95	30p
EC877	35p	EP182	50p	PL96	30p
EC878	35p	EP184	50p	PL97	30p
EC879	35p	EP186	50p	PL98	30p
EC880	35p	EP188	50p	PL99	30p
EC881	35p	EP190	50p	PL100	30p
EC882	35p	EP192	50p	PL101	30p
EC883	35p	EP194	50p	PL102	30p
EC884	35p	EP196	50p	PL103	30p
EC885	35p	EP198	50p	PL104	30p
EC886	35p	EP200	50p	PL105	30p

**SPECIAL OFFER 1 p & p TRANSISTORS, ZENER DIODES etc.**

OA15	20p	OC71	12p	1N823A	£1.80	3N154	95p	BC108	10p	GET115	45p
OA10	25p	OC72	20p	1N4785	80p	3N169	£1.45	BC113	10p	GET116	50p
OA70	10p	OC73	30p	1ZM75	35p	12FR60	45p	BC118	20p	GET66	£1.50
OA71	10p	OC75	25p	1ZMT10	35p	12FR80	45p	BC127	15p	GET22	20p
OA73	7p	OC76	25p	1ZT5	67p	40954	£1.25	BF115	25p	NKT304	50p
OA74	7p	OC78	20p	1ZT10	63p	40955	£1.25	BF173	20p	RAS310A	50p
OA79 (6D15)	10p	OC81D	20p	2G385	51p	40636	£1.25	BFY51	20p	3P	30p
OA81	10p	OC81DM	20p	2G403	51p	40668	£1.25	BFY52	20p	3D918	28p
OA91	7p	OC82M	30p	2N1304	32p	40669	£1.40	HS	45p	8D928	31p
OA200	7p	OC83	25p	2N1306	25p	AC127	25p	BS2	47p	8D938	32p
OA210	25p	OC84	25p	2N1307	25p	AC128	20p	BSY29	25p	6K27	40p
OA211	30p	OC122	50p	2N2411	£1.50	AC129	25p	BU100	£1.80	8D988	46p
OA220	55p	OC140	40p	2N2904A	25p	AC176	25p	BYZ13	25p	V405A	40p
OC150	50p	OC170	25p	2N3053	20p	AC177	25p	BYZ16	68p	Z2A51CF	78p
OC22	50p	OC172	37p	2N3054	50p	AD162	35p	CR81/10	25p	ZR11	33p
OC25	40p	OC200	40p	2N3730	50p	AF118	50p	CR81/20	38p	ZR21	46p
OC26	25p	OC201	75p	2N3731	£2.75	AF139	30p	CR81/30	40p	ZR22	42p
OC29	80p	OC206	95p	2N4172	£2.50	AF178	48p	CR81/35	43p	68JG7	25p
OC35	50p	IN21R	30p	3F100	62p	AF186	25p	CR83/05	30p	68JG7	25p
OC36	58p	IN21B	60p	3F120	82p	ASV26	25p	CR83/20	38p	68JG7	25p
OC38	42p	IN43	10p	3FR5	32p	ASV28	25p	CR83/30	40p	68JG7	25p
OC44	17p	IN70	7p	3N128	87p	ASV67	25p	CR82A	65p	68JG7	25p
OC45	12p	IN677	12p	3N139	£1.75	BAW19	20p	CV102	25p	68JG7	25p
OC70	12p	IN702-7058p	3N140	97p	BC107	10p	GET103	23p	7W	0.25	



**ALL valves guaranteed**

6A1	25p	6A2	£4.25	6065	65p
6A6	25p	6A7	£1.50	6083	£1.50
6A7G	35p	19H4	£5.00	6146	£1.75
6B7M	40p	20P4	£1.00	8020	£2.25
6B7GT	52p	25L8GT	40p	9001	20p
6B7K	32p	30C15	70p	9002	25p
6B7G	20p	30C17	80p	9003	50p
6B7K	40p	30C18	70p	9004	15p
6K25	70p	30F3	80p	9006	15p
68A7	40p	30FL1	75p		
68A7GT	32p	30FL12			
68G7GT	25p				
68H7	35p	30FL13	50p	C.R. Tubes	
68J7	37p	30FL14	85p	VCR97	£4.50
68JG7	32p	30L15	80p	VCR157B	£5.50
68K7	40p	30L17	80p	VCR517	£7.50
68L7GT	32p	30P12	80p		
68N7GT	32p	30P19	77p		
68Q7	39p	30P11	75p	8R1	£9.00
68Q7GT	35p	30P13	82p	8R2	£9.00
68V6G	17p	30PL14	90p	8R3	£9.00
68V6GT	40p	35L64	50p	8R4	£9.00
68X4	30p	35W4	35p		
68X5	30p	50C5	45p	Photo Tubes	
68X5GT	37p	50C5	50p	CMU25	
68X6	60p	50C10H6	60p		
68X6GT	60p	50C10H5	60p	931A	£4.00
69-30L2	45p	62A	38p	6097C	£17.50
69-30L3	45p	62B	38p		
69-30L4	45p	62C	38p		
69-30L5	45p	62D	38p		
69-30L6	45p	62E	38p		
69-30L7	45p	62F	38p		
69-30L8	45p	62G	38p		
69-30L9	45p	62H	38p		
69-30L10	45p	62I	38p		
69-30L11	45p	62J	38p		
69-30L12	45p	62K	38p		
69-30L13	45p	62L	38p		
69-30L14	45p	62M	38p		
69-30L15	45p	62N	38p		
69-30L16	45p	62O	38p		
69-30L17	45p	62P	38p		
69-30L18	45p	62Q	38p		
69-30L19	45p	62R	38p		
69-30L20	45p	62S	38p		
69-30L21	45p	62T	38p		
69-30L22	45p	62U	38p		
69-30L23	45p	62V	38p		
69-30L24	45p	62W	38p		
69-30L25	45p	62X	38p		
69-30L26	45p	62Y	38p		
69-30L27	45p	62Z	38p		

**ZENER DIODES**

CR83/05	30p
CR83/20	38p
CR83/30	40p
CR83/35	43p
CR82A	65p
CV102	25p
GET103	23p
7W	0.25

All preferred voltage

68JG7	25p
68K7	40p
68L7GT	32p
68N7GT	32p
68Q7	39p
68Q7GT	35p
68V6G	17p
68V6GT	40p
68X4	30p
68X5	30p
68X5GT	37p
68X6	60p
68X6GT	60p
69-30L2	45p
69-30L3	45p
69-30L4	45p
69-30L5	45p
69-30L6	45p
69-30L7	45p
69-30L8	45p
69-30L9	45p
69-30L10	45p
69-30L11	45p
69-30L12	45p
69-30L13	45p
69-30L14	45p
69-30L15	45p
69-30L16	45p
69-30L17	45p
69-30L18	45p
69-30L19	45p
69-30L20	45p
69-30L21	45p
69-30L22	45p
69-30L23	45p
69-30L	

# HOTLINES

ON RECENT DEVELOPMENTS

FOR some time now, weather satellites have been happily orbiting the earth some 800 miles up. These animals transmit a picture of the earth and a suitably equipped station below can receive these pictures. They show cloud distribution which is useful in helping to guess whether it will rain or not on the following washday.

## 3D RAIN?

Now comes news about a satellite built by the RCA. It is equipped with special sensors and boasts the distinction of being the very first operational satellite to provide a three-dimensional picture of the earth's weather. It is equipped with some very impressive sounding equipment; a scanning radiometer, a very high resolution radiometer and a vertical temperature profile radiometer.

The very high resolution radiometer (v.h.r.r.) has two channels and offers images from both the visible and infra-red regions. It can sense the thermal energy given off by objects below, down to half a mile in area.

Resolution is far better than the pictures provided by television cameras or the radiometers used in earlier satellites. The solar cells in the satellite, NOAA -2, generate some 500 watts and over 10,000 individual cells are used to achieve this power. Who knows—television announcers of the future may be forecasting that three dimensional rain is on the way.

## LIQUID CRYSTALS

It now seems a certainty that liquid crystal displays will have a big impact on the electronics market. I reported these as being already built into a multi-digit display being marketed at the Electronica exhibition in Germany late last year. Now, the U.S. giant, North American Rockwell is reported to be mass-producing liquid crystal devices.

The liquid crystal phenomenon was first discovered way back, as long ago as 1888. The basic principle is that certain liquids become opaque when they are subjected to an electric field. With no field present, they are transparent. The North American Rockwell displays consist of two small plates of glass. Although

these are bonded together, they are separated by a tiny gap—about a thousandth of an inch. This tiny gap is filled with the special liquid which is affected by an electric field. The cell is thus completely transparent.

However, when a small electric field is applied (this takes about 25V to achieve the desired effect) the cell becomes opaque. Without a field, the molecules in the liquid are uniformly and regularly oriented. The application of the electric field causes this molecular structure to become disoriented and the molecules thus scatter the light giving an opaque effect.

The voids or spaces into which the liquid is put can be formed into figures or letters for the purposes of forming a display. Conductors to the liquid are formed from tin oxide which is a transparent conductor. The liquid crystal display draws almost no power—about 10mW or one hundredth of a watt. Perhaps we will have windows some day which will be clear until we press a button?

## OZONE SPEEDS UP RESIST REMOVAL

Integrated circuits (i.c.'s) are delicate little beasts especially during their manufacture. Part of this process is a photographic one. There is a particular stage in the printing of each mask where unwanted photo-resist has to be removed. Considering the size of elements on individual i.c.s this removal is a delicate business. The General Electric Company in the U.S.A. have come up with a new method of removing unwanted photo-resist. It consists of exposing the resist to ultra-violet rays in the presence of air. It takes about 40 minutes for a typical film of resist to be removed. The depolymerisation of the resist happens at a rate of about a thousand angstroms per minute. By injecting 2% ozone gas into the chamber with the specimen the process is speeded up some ten times.

Earlier, I talked of liquid crystals and many have flat in claiming that the solid state flat tube television screen is here. One British manufacturer, however, is obviously unimpressed. Mullard has opened a

new factory in County Durham. The sole purpose is to manufacture shadow mask colour television tubes.

Although only officially opened in December last year, pilot production was already said to be running at the rate of 100,000 tubes delivered from this plant. By the end of this year, production is estimated to be in the region of 500,000 tubes and by the end of this present decade, production will be running at some 900,000 tubes/annum. All this adds up to a lot of colour television receivers—have you got yours yet?

## LASERS ARE BACK

Lasers are back in the news again, this time in America where the Optical Physics Division of the National Bureau of Standards is applying one to monitor pollution. A major contributor to atmospheric pollution is nitrous oxide. It is found lurking in such jolly jollop as flue gases and in the exhaust fumes from motor vehicles.

The laser beam is directed through a magnet whose coils are driven by an audio amplifier and is detected by an infra-red device. The amplifier generates a modulating magnetic field which has the effect of sweeping the absorption line through the laser line. The detector produces a signal which has a direct relationship to the amount of nitrous oxide in the sample being investigated.

Concentrations of nitrous oxide as low as 20 parts per million (p.p.m.) can be detected but workers believe that concentrations right down to 0.1 p.p.m. will be detectable as the method is improved.

## FLYING SPOT

Useful things oscilloscopes. Have you ever wondered just how fast that tiny spot of light travels across the cathode ray tube? Before you start to make calculations, think of the latest fast writing oscilloscope, the HP 184A. The writing speed for this unit is so fast that the spot travels 400cm in one millionth of a second.

*Ginsberg*

# NAUTICAL RADIO AIDS



## IAN SINCLAIR

**E**VER since the day when Marconi equipped the yacht *Elettra* with radio to act as a mobile test-bed, electronics and boats have been closely associated. The first really extensive use of radio was at sea, and after the Titanic disaster all ships were required to keep radio watch continuously for distress signals. The requirement for ships to be fitted with radio and staffed with trained operators did not, however, extend to small boats at that time, and it is only fairly recently that radio and electronic aids for pleasure craft have become more of a necessity for serious boating.

### MARINE HAZARDS

Electronic devices for use at sea present some design problems which do not appear in land-based equipment. The most obvious hazard is moisture, not the fresh water moisture of a foggy day on land but the salt-laden moisture which corrodes its way through soldered joints, cable terminations, plugs and sockets, and most other metal-to-metal joints in a remarkably short time. As well as the corrosion problem, which can be completely solved only by total encapsulation, there is the problem of insulation resistance.

Salt spray is quite a good conductor and in valve equipment in particular, operating at high voltages, protection of equipment from saline elements is a problem to designer and operator alike.

It was largely the water-spray problem, as well as the cost factor, which has kept electronics out of small craft for so long. In large vessels, the radio and radar equipment could at least be mounted in an enclosed space at a reasonable height above the deck, well away from the direct spray except in the most extreme conditions. In small boats, such spray-free havens cannot be found, and there is little chance of keeping the equipment free of water by heating coils, as were once used on bridge-mounted radio and radar.

The advent of solid state equipment has opened up a new dimension in marine applications, especially with the possibility of cutting down on interconnections by using integrated circuits. Vibration is one of the most pressing problems in small craft, where the rumble of even a small diesel engine is enough to loosen plugs from sockets or wires from soldered joints.

Some of the most up-to-date equipment used for pleasure craft can be seen at the annual Boat Show, held each year in London in January. This year you would have found amongst other more glamorous displays, several kinds of communications equipment.

One stand showed a "triple-standard" television receiver, complete with inverter for use with ship batteries, for use in most yachting centres in the world. But for those who insist on wind in their sails, there was a complete analogue computer, taking information on wind speed and direction, water speed, currents, intended course, and displaying the optimum trim on a model.

### RADIO AIDS

Radio is still the mainstay of marine electronics, and it is hardly surprising that there should not be many advances in this direction as there are in instrumentation. The latest ranges of transmitter/receivers are geared to the most recent International regulations, which call for s.s.b. working in the marine bands between 250kHz and 4.1MHz and the use of all solid state equipment has resulted in very compact apparatus.

A large number of v.h.f. and u.h.f. radiotelephones were also shown, and one interesting new development is the Marconi "Pocketphone" intended for communication on large vessels, such as tankers, and during docking and cargo handling operations.

The v.h.f. and u.h.f. equipment uses frequency modulation, and most make provision for the reduction of channel spacings to 25kHz, which will soon be a Post Office requirement. The bands used are within the range 148MHz to 174MHz in v.h.f. and 440MHz to 470MHz in u.h.f. Communications equipment was being shown by (among others) Marconi Marine, Electronic Laboratories (Marine), Ajax Electronics and S.P. Radio A/S of Denmark.

The latter firm was showing a receiver operating under the spray from a waterfall, whose salt content I did not sample, and also showed the "Dual-watch" facility on receivers. This enables the operator to fulfil the requirements of listening for distress signals along with normal working. The distress frequency is preset, so that the set is tuned permanently to that frequency in the watching circuits.

Working can be continued on other channels, and if a signal is received on the distress frequency (or any other being watched) the receiver output is instantly and automatically switched to the watched frequency. A lamp indicator also shows when a call is being received on the watched channel, and flashes during normal operation to show that the watch is being carried out.

### DIRECTION INDICATOR

An interesting device for the small boat is the "Seafix", a hand-held radio direction indicator by Electronic Laboratories (Marine). This consisted of a t.r.f. transistor receiver with "autodyne" detection

over the range 200 to 400kHz, with the calibration most accurate at 300kHz, the centre of the Marine Beacon band.

Switched to NAV, the autodyne circuit is used to receive beacon transmissions, and the highly directional ferrite rod aerial can be used for finding the bearing of the beacon within 2° (at half rated range). Switched to BC, the "Seafix" can be used to pick up the long-wave shipping forecasts broadcast on this band. A stethoscope headset was used in preference to loudspeakers or conventional phones, and water sealing was by the conventional compressed rubber gaskets.

## RADAR

Radar has for a long time been one of the most important navigational aids for larger vessels, but is seldom seen on smaller craft. There are several reasons for this: the cost of any radar installation is high, since it must include the cost of modifications to the vessel as well as the provision of the apparatus.

Radar equipment is often unavoidably large, heavy and dependent on high voltages, since the cathode-ray tube and the magnetron must use high voltages, although it is now possible to replace the klystron local oscillator by Gunn diodes or other semiconductor devices.



The Hepplewhite Marine Check radar detector lets you know if you are on a collision course.

Manufacturers are not dragging their heels over these problems, but are commendably cautious, since they know only too well how much the readings of a radar receiver come to be relied on. Any compression of size or cost must therefore not be made at the expense of accuracy of plotting if we are not to have a rash of "radar-assisted" collisions. All the big names in marine radar (Decca, E.M.I., Marconi Marine) showed small radar outfits, but these were not really intended for the amateur.

The Hepplewhite "Marine Check" is a continuous scanning self-powered instrument designed to minimise risk of collision with other vessels whose radar may not pick up small boats in bad weather or low visibility—the "Marine Check" will however, detect the other vessel's radar transmission and allow you to take avoiding action.

The scanning head is a miniature, precision, solid-state detector and amplifier of continuous, pulsed

and modulated X-band radar transmission (9,000 to 11,500MHz) with electronics mounted in a shock-proof case and will receive radar transmissions at sighting distance.

As the sensitivity is reduced, the directional power of the antenna is proportionately increased to a point where the bearing is located on a narrow sector. If this bearing, which is indicated on a compass scale, remains constant, you may be on a collision course, also as the pulse length increases as the distance decreases, it is possible, within limits to determine if the transmitting vessel is approaching or receding.

The "Seascan" radar by Electronic Laboratories (Marine) is designed for the amateur, and has a power consumption of only 48W from 12V, 24V or 48V battery supplies. The only vacuum devices used are the display tube and the magnetron, the local oscillator being a Gunn diode whilst the magnetron modulator uses a thyristor. Unfortunately no circuit details were available and all the units on the stand were dummies.


One interesting new development in radar for the small craft is a passive radar detector by Hepplewhite Marine. This picks up the X-band (9,000 to 11,500MHz) transmissions from other vessels, and has a small directional aerial consisting of a Perspex "horn" on which waves are guided (along the surface) by the effect of the permittivity of the material. The received radar signals are mixed with the output of a local oscillator, and the beat note amplified. The point of strongest signal can be identified by altering the mixer bias so that only a signal of the maximum strength will produce a beat note; this enables the operator to find the bearing of the craft carrying the radar.

## SPEED MEASUREMENT

Water and wind speed instruments have for a long time been a weak point in the instrumentation of boats. The traditional methods of measuring speed have depended on anemometers for wind speed and submersible "logs" for water speed. The anemometer is the device using three or four cups at the ends of radial rods pivoted so that the effect of wind is to revolve the assembly about its axis. The



The Electra Magnetic Log is an impellerless speed and distance indicator.

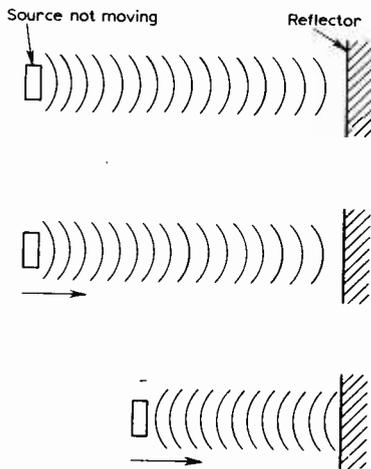

**Fig. 1: The Doppler Principle.**  
 Imagine a transducer giving out sound waves. These waves travel in water at a speed of about 1,000 metres per second. Speed equals frequency multiplied by wavelength.  
 If the transducer moves at a speed "V", the speed of the waves towards the reflector is now 1,000 + V metres per second. We have not changed the frequency of transmission, so the wavelength must now be less.  
 (1,000 + V = f × new wavelength.)  
 The waves are now reflected to a moving object, so that more waves per second hit the receiving transducer. The frequency is now higher by a factor  $\frac{c+V}{c}$  where c is the normal wave speed and V is the speed of the transducer and boat. The final effect is to receive waves of shorter wavelength and higher frequency.

speed of rotation, which depends on the wind speed, is measured by counting the number of switching operations of a reed switch under the influence of a magnet on the rotating shaft. This count is converted into an analogue signal which drives a meter. Wind direction is found by using a vane coupled to a potentiometer to show the angular position by voltage detection on a meter.

The traditional submersible "log" consists of a small propeller whose shaft is held in a casing containing a reed switch. The rotation of the propeller as the "log" is towed behind then registers relative water speed just as the anemometer registers relative wind speed. The snag is that the propeller of the log is easily jammed by anything encountered in the water from jellyfish to seaweed, and this can have the effect of making calculation of speed and distance incorrect.

### SPEED-LOGS


Two novel speed-logs were shown, each representing refreshingly different thinking about the problem. Space Age Electronics showed their Doppler speed log. This uses a ceramic transducer to project a 1MHz sound beam ahead of the ship. Most of the beam is dissipated in the water, but a small part is reflected from the layer of relatively still water (the boundary layer) close to the boat.

When the boat is moving, the reflected frequency is not the same as the transmitted frequency (Doppler Effect). If the boat is moving ahead, the reflected frequency is higher than the transmitted frequency; if the boat moves astern, the reflected frequency is lower.

Referring to Fig. 1, the transmitter, because of its movement, "packs in" more waves between itself and the still layer than it would if it were not moving. Because more waves are travelling, the wavelength seems shorter. Also, when the waves reflect from the boundary layer, the receiver has also moved towards them, making the frequency of the received waves seem higher.

When the reflected wave is detected, the shorter wavelength appears as a higher frequency (speed = frequency × wavelength), whose value depends on the difference between the speed of sound in water and the speed of the boat. By beating the transmitted frequency against the reflected frequency, a measure of speed can be obtained.

The method is dependent on obtaining a reflection from relatively still water, and so the transmitting/

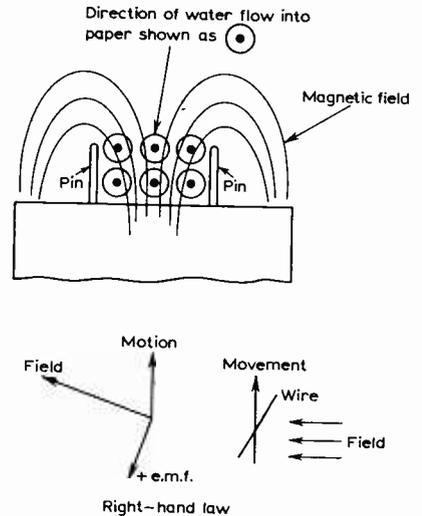

**Fig. 2: An e.m.f. is produced between two metal contacts, providing the direction of flow is at right-angles to the line joining the contacts.**

receiving head must be located where such a layer is within range. Precise location varies from boat to boat. To allow for variations in installation, the calibration is adjustable, so that the distance log can be checked against accurately known distances (between two land-marks, for example). The circuitry uses three integrated circuits, 17 transistors and eight diodes. A "log" accuracy of better than  $\pm 1\frac{1}{2}\%$  (typical) is claimed.

The "Electra" magnetic log, produced by E.M.I. marine uses the magnetohydrodynamic principle for its operation; this is the generation of a voltage by induction when a conducting liquid flows past a magnetic field.


By arranging a magnetic field to cut the direction of water flow at right angles, an e.m.f. is induced between two metal contacts in the moving water, provided that the direction of flow is at right angles to the line joining the contacts (Fig. 2)

The Electra Magnetic Log operates on this principle, but with some ingenious modifications. The magnetic field used is an alternating field. In this way, the voltage generated is also alternating, which disposes of two problems at once. One problem is polarisation; when a steady voltage exists between two contacts in sea water, an electrolysis action takes place causing corrosion of the metal. The use of a.c. avoids polarisation problems and makes it easy to amplify and display the output from the contacts. As with the previous method, the positioning of the measuring head is critical.

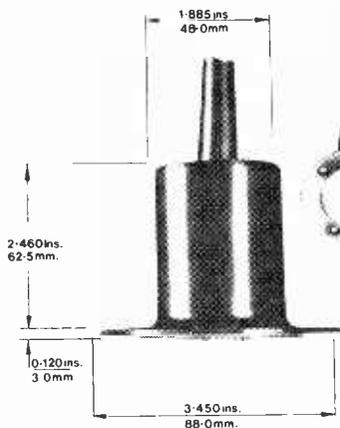
### ECHOSOUNDERS

Echosounders have been used for a considerable time, and changes have been in detail rather than in concept. Basically, a marine echosounder consists of a pulse generator working at ultrasonic frequencies in the region 20kHz to 150kHz (the higher frequencies are used for inshore work). A transducer converts the electrical pulses into sound waves directed from the bottom of the boat into the sea, and a receiver, using the same transducer, detects the pulse reflected from the bottom of the sea.

The shape of the received pulse provides a guide to the nature of the sea bed, for example, a muddy



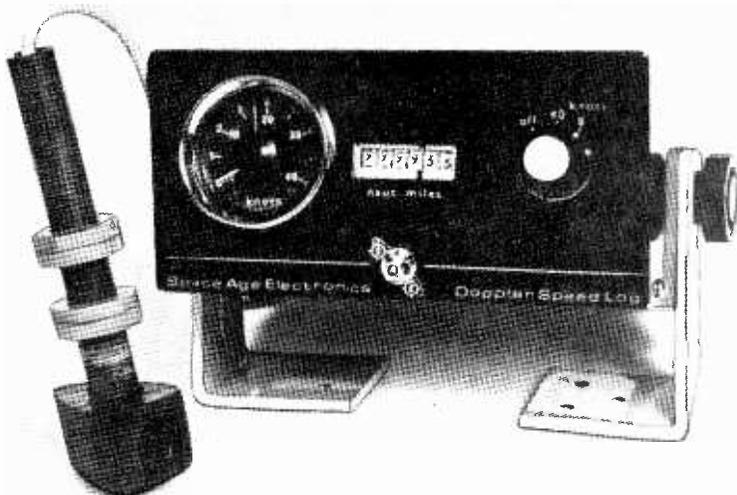The electro-magnetic transducer for the magnetic log. As the boat moves along, a small e.m.f. is produced and sensed by two probes. This signal is then amplified and displayed in speed and distance units.



The Doppler speed-log does not rely on the flow of water to move a mechanical part like an impeller or paddle wheel. A small streamlined transducer, mounted flush with the underside of the hull, transmits a high frequency ultrasonic signal 70cms ahead. A small part of this signal is reflected back from the boundary layer between the hull and the water.

sea bed is indicated by a broad pulse, a sandy bed by a narrow pulse, a rocky bed gives multiple reflections. Pulses received from intermediate depths can indicate shoals of fish. The time delay between transmission and reception is proportional to the depth of sea.

Because the pulses are travelling in the water at the speed of sound (around 1,000 metres per second) rather than at the speed of radar waves in space (some 30 million metres per second), scanning rates have to be lower than the 1,000Hz commonly used in radar. Scanning rates of once per second are common, although this is rather too low for display on a long persistence cathode ray tube screen.

The display method traditionally used is a rotating wheel carrying, or illuminated by, a neon which flashes on transmission of the pulse and again when the echo is received. The stationary bezel round the wheel is then calibrated in metres of depth (now replacing fathoms on the latest charts).

The large number of echo sounders at the show demonstrated several novel points of design. Most interesting was the use of electro-luminescent diodes to replace neons, so avoiding the need to generate a high voltage supply (Brookes & Gatehouse). A common feature of all the echo sounders was the use of high scan rates for the shallow water ranges (up to six pulses per second) so giving better definition in critical conditions.

Lead zirconate titanate crystals were in evidence as transducers, encapsulated in various plastics. For professional use, chart recording echosounders were shown (these, of course, have been around for a long time). The Marconi Marine chart-maker used electrosensitive paper which changed colour when a small voltage was applied between the front of the paper and the back.

### WATER-LEAK AND WATCH

In addition to the displays of electronics for communication and navigation, there were some interesting exhibits in the "miscellaneous" class. Space-Age Electronics were showing their water-leak and watch alarm, and judging by the sound which could be heard all over the first floor of Earls Court, almost every chandlery firm was demonstrating it.

The instrument is basically a conventional leakage detector using stainless steel pins as probes. If the pins are immersed in water for more than four seconds, an alarm is given, but only if the immersion is for longer than four seconds, a time carefully chosen to avoid continual false alarms in heavy seas. When there is no conductivity between the pins, all transistors are biased off, so ensuring practically no standby current. The sound given out is a rising frequency note which is most easily distinguished amongst other sounds.

The watch facility also provided on this instrument gives an alarm note of gradually increasing amplitude every three minutes. If an alarm button is pressed during the alarm, or before it, the instrument remains silent until another three minutes has passed. If the helmsman is asleep and does not press the alarm button, the alarm warning increases to maximum intensity.

### GAS ALARM

The Electra gas alarm, from E.M.I. Marine, is of considerable interest. Unlike previous gas alarms, which used heat conduction from a hot wire to detect changes in the air composition, the Electra gas alarm uses semiconductor sensors. No details were given, but it is possible that the sensors consisted of infra-red electroluminescent diodes and detectors. Any change in the air composition caused by petrol vapour, butane or propane gas, carbon monoxide, smoke, paraffin fumes, diesel fumes is indicated by two visual warnings in the form of a meter reading and a red warning lamp.

In addition, a loudspeaker gives out a 2.5kHz note when the gas concentration exceeds the safe limit. In this way, no panic is caused by small concentrations of gases, since only the discreet visual warning is given, but dangerous amounts operate the audible alarm so that evacuation or other measures can be taken. Remote warnings can also be fitted.

All in all, the Boat Show is developing considerable interest from the point of view of electronic aids. It is unfortunate that so few exhibitors were able to cope with technical queries, but all of them were most helpful.

# practically wireless

commentary by **HENRY**

No. 98  
First in  
the Field

I HAD a chap in the shop today, searching for an SP4. It is true: even in the glitter of a hi-fi establishment, where every prospect teases and only valves are vile, we still get enthusiasts with thirty-year-old equipment, hopeful of our being able to provide the missing link.

Which leads us, philosophically, to a contemplation of some of the 'firsts' we nowadays take for granted.

Example: the quasi-complementary transistor amplifier circuit, which has given us so much trouble since its inception. I have come across the September 1956 copy of *Electronics*, a McGraw-Hill publication, in which R. C. Lin, then of RCA, Princeton, first propounded his output circuit in which, to quote: '... the two upper transistors conduct during the negative half-cycle and the two lower transistors conduct during the positive half-cycle.'

In his summary, he gave amplifier distortion at 100cps (sic) and 400cps as below 1 per cent at six watts, and though he admitted that the distortion might be expected to rise at 5,000cps, he made no mention whatsoever of its fierce spikiness at a fraction of a watt, which is the mariner we've had wrapped around our necks ever since.



The mariner wrapped around our necks.

Inventions, especially world-shaking innovations such as the transistor proved to be, have a habit of spawning themselves much more prosaically than we would like to imagine. No technologist runs screaming through the corridors of the M.I.T. with 'Eureka' echoing behind him. More likely, something as laconic as the 12/29/39: 4.15 p.m. entry in William Shockley's notebook may be handed down to posterity: 'It has today occurred to me that an amplifier using semiconductors rather than vacuum tubes is in principle possible.'

In principle: hardly in practice. He was thinking of a Schottky-barrier FET kind of device, with copper-oxide as the semiconductor. And, as Henry could have told him\*, it didn't work. Instead, the experiments of the team included covering metal points with wax and pushing them down on to p-type silicon treated to give an n-type surface. They surrounded the point with water and found they could obtain power amplification.

To quote Brattain: '... the group was jubilant that day.'

Trouble was that the water would evaporate. Maybe it was all that heavy breathing. So they switched to glycol borate to reduce evaporation. One trouble: amplification was obtainable only below 8Hz—hardly hi-fi yet.

There were lots more experiments, culminating in evaporated gold spots and germanium, and then, on Dec. 23rd 1947, two gold contacts less than two-thousandths of an inch apart were made to the same piece of germanium and the first transistor happened.

No sudden breakthrough—and no inspirational brainchild—and no immediate christening, I may add. It was a month later that a chap called John R. Pierce of the Bell technical staff mooched into Brattain's office and pointed out that the 20dB point-contact amplifier they had made was the



Runs screaming through the corridors.

'... dual of a vacuum-tube, circuit-wise.' He mentioned the important valve parameter, transconductance. Then he went on to talk about its electrical dual, transresistance. To quote Brattain once more: '... then he said 'transistor', and I said, 'Pierce, that is it!!'

What about a few more firsts in our field? Who developed the first p-n junction? Bet you can't even say his name, let alone remember it. Well Henry can, with the benefit of some help from Edward A. Torrero, who is Associate Editor of *Electronic Design*. He was William Pfann (with the aid of a chap called Jack Schaff; let's give credit where it is due). They also worked for Bell Laboratories.

But Bell eschewed silicon for germanium, because the impurities, back in the early 1940's, were easier to control. It was left to Texas Instruments to develop silicon types of transistor, and to Motorola to introduce the diffused base transistor.

So I could continue. Henry hasn't the space to name those to blame.

But the "first" we are all concerned with is that original all-transistor radio. And who made that? A firm called Regency, in 1954. How's that for a significant 'first'?

\* With the benefit of hindsight. Ed.

# EXTRA!!!


## IN NEXT MONTH'S

# PRACTICAL WIRELESS


# SIMPLE PROJECTS FOR THE HOME
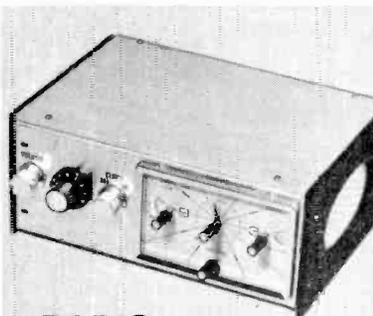
## 8 PAGE SUPPLEMENT


P.W.'s reputation for plenty of simple and straightforward constructional projects is excelled next month by an extra large issue. In addition to the usual constructional articles and features, the May issue will include a special extra 8-page coloured supplement describing eight easy projects for the home, designed and described by one of our top designers; you are bound to find *at least* one of these of interest. This supplement is fully illustrated with all the details on how to build these projects.




**RADIO  
ALARM CLOCK**

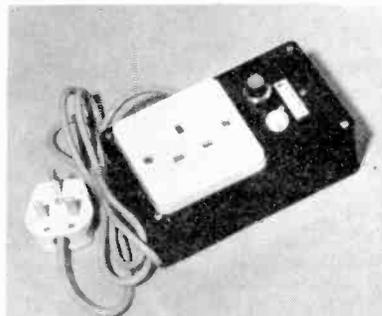

**LAMP DIMMER**

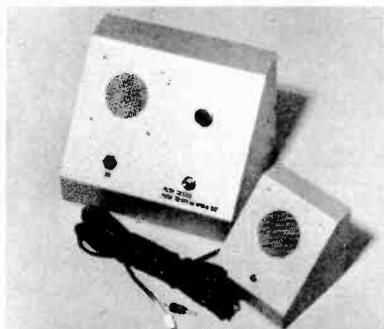

**INTERCOM AMPLIFIER**

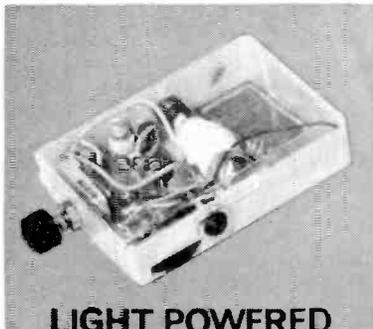


**LIGHT POWERED  
RADIO**



**BABY ALARM**



**TWO TONE  
DOOR BELL**

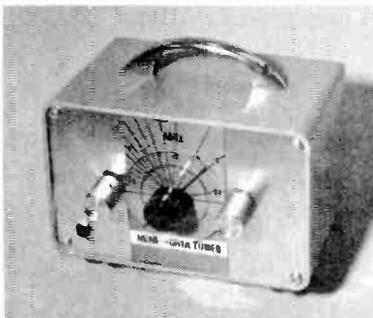

**TAPE TUNER**



**WATER LEVEL  
DETECTOR**

**MANY OTHER CONSTRUCTIONAL  
ARTICLES PLUS ALL THE REGULAR  
FEATURES. PRICE 20p.**

**ALL IN THE MAY ISSUE  
ON SALE 6th APRIL**

Following the success of the Texan amplifier published in this magazine during May to August 1972, the applications laboratory of Texas Instruments Ltd. have developed exclusively for P.W., a compatible unit for the control of Psychedelic lights from a sound source. The initial design features zero voltage control. A more sophisticated design incorporating lamp dimming facilities will also be covered in this series of articles. For stereo operation two P.W. Tricolour units are required.



TR

**I**F I had been asked, a couple of years ago, what 'psychedelic lights' were, I could only have made a wild guess: was it perhaps a medical term referring to some sort of ultra-violet treatment for disorders of the mind? Or, possibly, the latest in pet food, some extra tantalising form of offal? The truth, however, dawned slowly. What my "trendy" young friends were talking about was the latest innovation, the offspring of a marriage between light and music. It was not simply a question of a 'pop' version of 'son et lumière' but a more intimate relationship between the two media. Light could be made to respond directly to sound; flashing furiously for a fanfare, discreetly dimmed for Debussy. It is, however, unlikely that psychedelic lights will be installed in the Royal Festival Hall, but those of our readers who occasionally frequent the discotheque or dance hall will be familiar with this innovation. It is probable, too, that many have given thought to the incorporation of this feature into their own domestic lighting systems. What, it might be asked, does this involve?

In essence a 'psychedelic' light system works like this: sound controlled modulators convert bass, middle and treble frequencies into corresponding bursts of light thus adding a new "visual" dimension to the beat of the music. This is achieved by taking a signal from across the loudspeaker terminals and feeding it into a filter circuit whose output provides pulses which correspond to the sound spectrum—bass, middle and treble and any combinations of these three channels. These pulses then pass through an interface circuit and energise appropriate triacs. The latter, as will be seen, act as electronic switches and turn on the lamps.

This article will attempt to explain fully the construction of psychedelic light control units for both mono and stereo equipment. It is aimed at the home constructor who possesses nothing more than an average amount of skill.

### Zero Voltage Switching

As stated, the lights are turned *on* and *off* by utilising a device called a triac, i.e. a semiconductor bidirectional switch (Fig. 1). This replaces two thyristors connected back to back, thus controlling the positive and negative cycle of the supply voltage. Whereas the thyristor requires a positive gate to cathode voltage and will turn *on* only when the anode voltage is positive with respect to the cathode, triacs will turn *on* when the gate voltage polarity is the same as voltage between mt2 and mt1 (main terminal 2 and 1), i.e. positive for the positive half cycle and negative for the negative half cycle. In addition a triac will turn *on* with the gate negative with respect



- MONO/STEREO CAPABILITY
- ZERO VOLTAGE SWITCHING
- NEGLIGIBLE RADIO INTERFERENCE
- LAMP OVER-RIDE CONTROL
- OPTIONAL LAMP DIMMING


Mood

PART ONE



\* TEXAS INSTRUMENTS LIMITED

# COLOUR

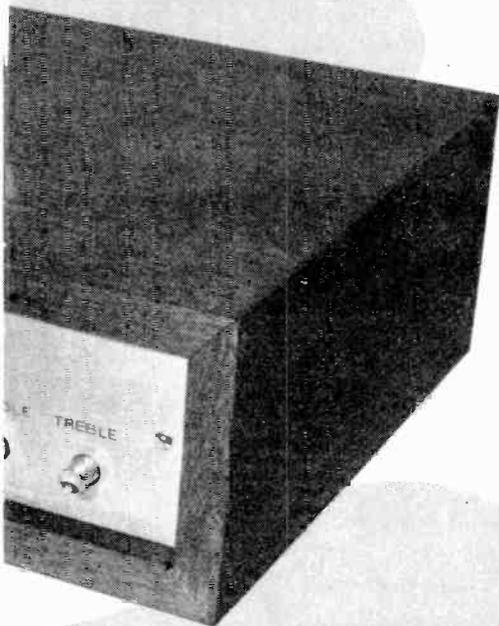

## Lighting System

JUREK BUDEK\*

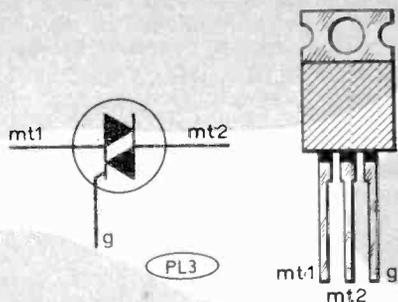


Fig. 1: The TIC225D bidirectional switch

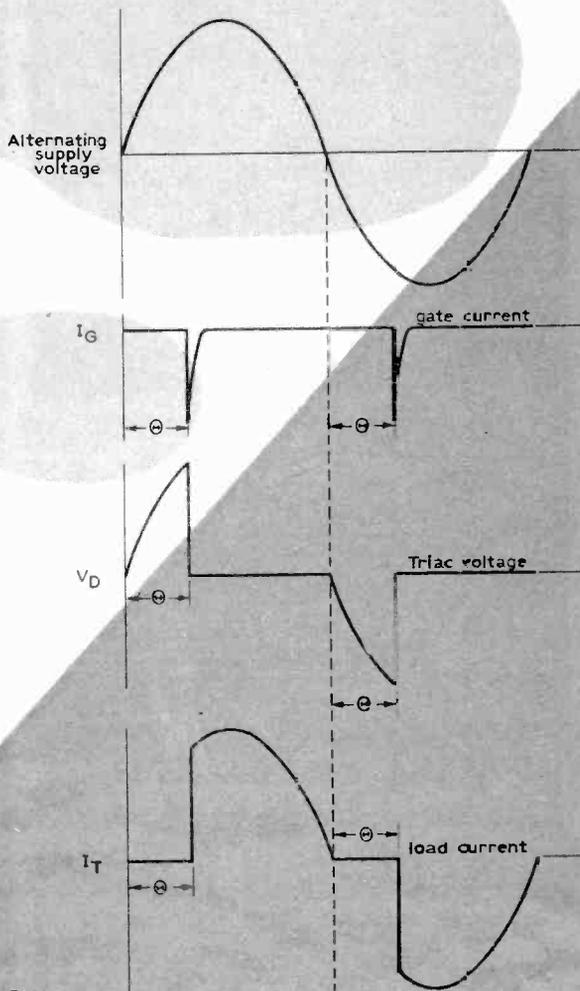


Fig. 2: Waveforms associated with triac switching. Refer to the text for clarification

to the mt1 terminal for either polarity of mt2. It is the latter factor which accounts for the techniques used in the circuits to be discussed in this article.

A further point about the triac is that there is only 2-3 volts between the gate and terminal 1, whereas there may be many hundreds or even a thousand volts between terminal mt2 and mt1.

Triacs used in a phase control mode, as shown in Fig. 2, produce considerable radio frequency inter-

ference (r.f.) due to the step change in current. The noise thus generated is spread by means of conduction through the wiring system or by radiation. Suppressing r.f. becomes more difficult and expensive as the load increases. Uncontrolled switching of "psychedelic" lamps on and off will have a similar effect and will also introduce additional noise in the loudspeakers. A simple solution to this problem is to arrange the switching so that it always takes place at the point where the mains supply voltage crosses zero, as shown in Fig. 3.

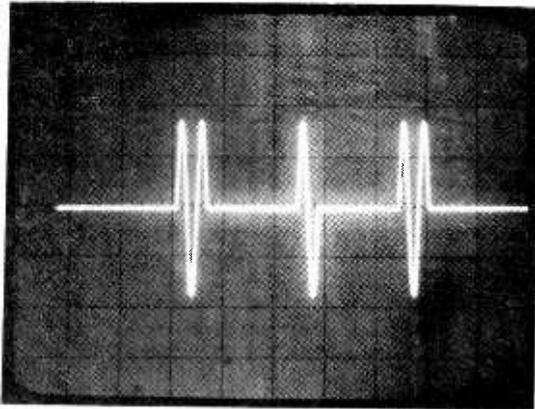


Fig. 3: Waveform depicting zero voltage switching.

This technique is called 'zero voltage switching' or 'burst firing.' In this way isolated numbers of half or full cycles will pass through the lamps and thus avoid step change in currents, which also has the additional advantage of increasing the life of the lamp.

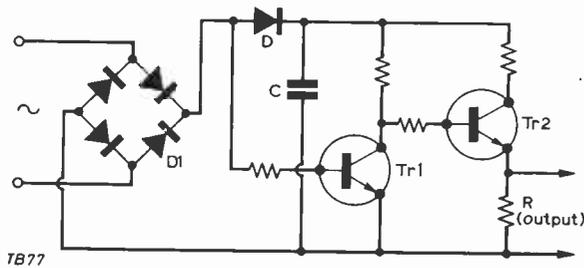


Fig. 4: Basic circuit which generates the pulses at the point of zero voltage crossing.

Fig. 4 shows the circuit used to generate the pulses at the point of zero voltage crossing. Transistor Tr1, whose base is connected to the unsmoothed supply from the bridge rectifier D1 is on most of the time.

However, each time the mains voltage crosses zero, its base voltage is taken below the holding on voltage and it thus turns off, giving positive pulses on its collector. In order to reduce the loading on transistor Tr1, transistor Tr2 has been added. Positive pulses appear as an output across resistor R each time the mains voltage crosses the zero point.

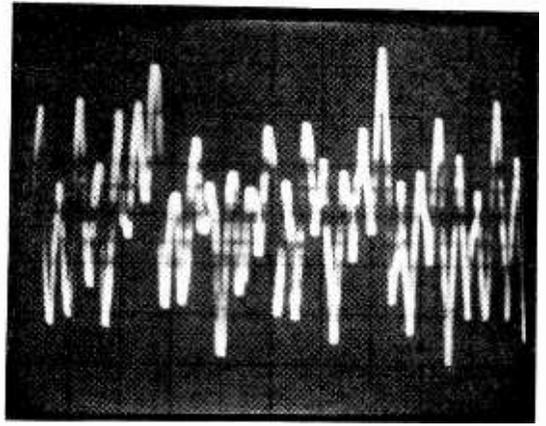


Fig. 5: Typical music voltage waveform at the terminals of a loudspeaker.

In order to control the lamp switching with respect to the frequency bands, we need a circuit which will separate out the low, middle and high frequencies from the voltage waveform appearing at the terminals of a loudspeaker. A typical voltage waveform appearing at this point is shown in Fig. 5.

### Filter

A circuit which separates frequencies into bands is called a filter. There are various types of filters which could be employed; e.g. one commonly used is a resistor/capacitor (r.c.) network for high and low pass filters and an inductor/capacitor (l.c.) network for middle frequencies. The elegant way, however, specially developed for the P.W. Tricolour is to employ integrated circuit (i.c.) operational amplifiers, in a positive fixed-gain configuration, as the active filter element and resistors and capacitors as passive elements. By choosing suitable component values a sharp separation between bass, middle and treble frequencies can be obtained.

The shape of the filter response is determined by a factor known as the damping ratio ( $\zeta$ ). The lower this ratio, the sharper the cut-off and there is a peaking effect. This peaking effect is of no importance in our application. As approximately 1.5 volts is required to turn on the interface circuit, and thus to switch on the appropriate lamps, the filter characteristics are expressed in volts against frequency and not in the more usual decibels against frequency.

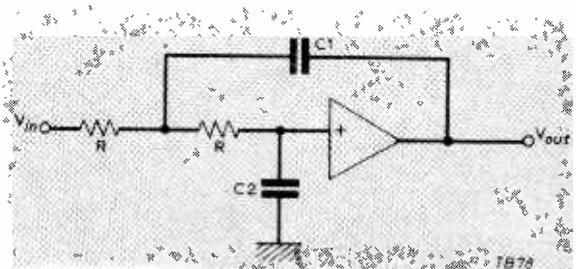


Fig. 6: Basic low pass filter as used in the P.W. Tricolour.

The theory of filter design is quite extensive and complex. We will however only outline the necessary basic concepts and give some simplified formulae.

Let us first look at a basic low pass filter (i.e. one which will stop all frequencies except those below a chosen frequency). The circuit of such a filter is shown in Fig. 6.

Here the angular cut off frequency,  $\omega_0 = \frac{1}{R\sqrt{C_1 C_2}}$

and the damping factor  $\zeta = \sqrt{\frac{C_2}{C_1}}$

Critical damping occurs when  $\zeta = \frac{1}{\sqrt{2}}$

and, for the reason explained before, i.e. to improve the sharpness, this value is reduced to 0.5. From these equations, the filter component values can be established.

The high pass filter (passing all frequencies above a chosen one) is shown in Fig. 7 and again requires only one operational amplifier, two resistors and two capacitors.

Here the angular cut-off frequency,  $\omega_0 = \frac{1}{C\sqrt{R_1 R_2}}$

and the damping factor  $\zeta = \sqrt{\frac{R_1}{R_2}}$

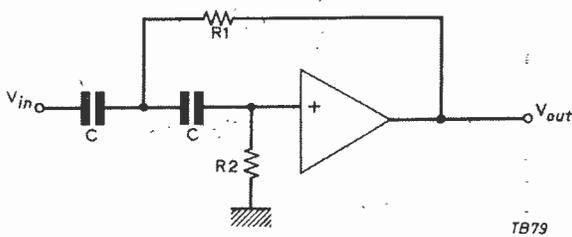


Fig. 7. Basic high pass filter. ▲

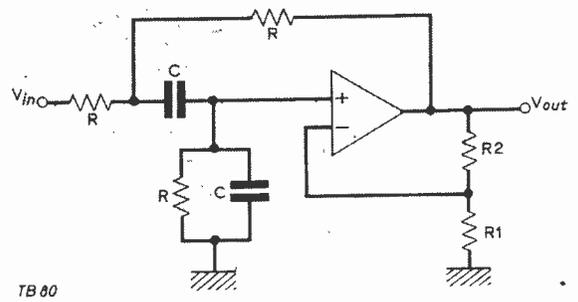


Fig. 8. Basic band pass filter.

Once more from these equations, the filter component values can be established. Finally, the band pass filter; which, of course, as its name suggests, passes a band of frequencies. This, as can be seen from Fig. 8, is a little more complicated than the other two.

The centre angular frequency  $\omega_0 = \frac{\sqrt{2}}{RC}$

and the quality factor  $Q = \frac{\sqrt{2}}{4 - \frac{R_2}{R_1}}$


$Q = \frac{2\Delta f}{f_0}$ , where  $2\Delta f$  is the difference between

two frequencies at which the voltage output of the filter is  $\frac{1}{\sqrt{2}}$  of its maximum value. From the above

formulae, relevant component values can be obtained.

Musically oriented readers will recall the 'unisono' note played on the oboe during the orchestra's tuning-up time, just before the concert begins. This note is middle 'A' with a frequency of 440Hz; a frequency which has been chosen as the centre frequency for the middle band-pass filter in

Rear view of the P.W. Tricolour. ►

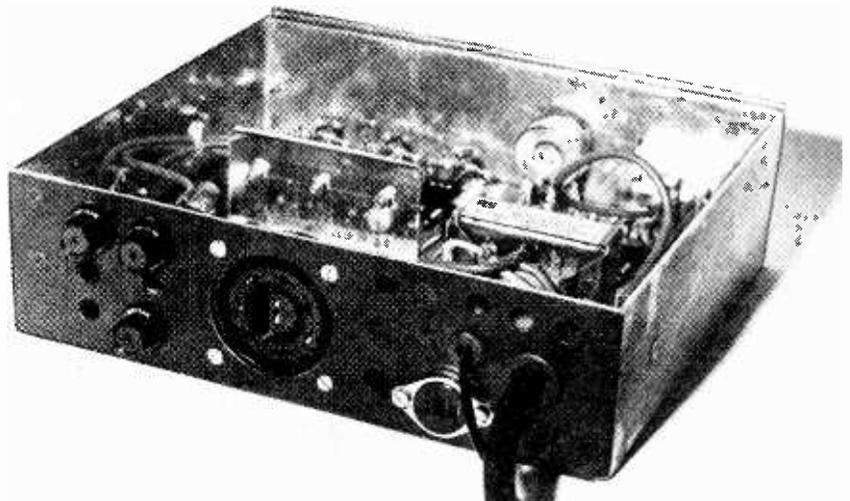

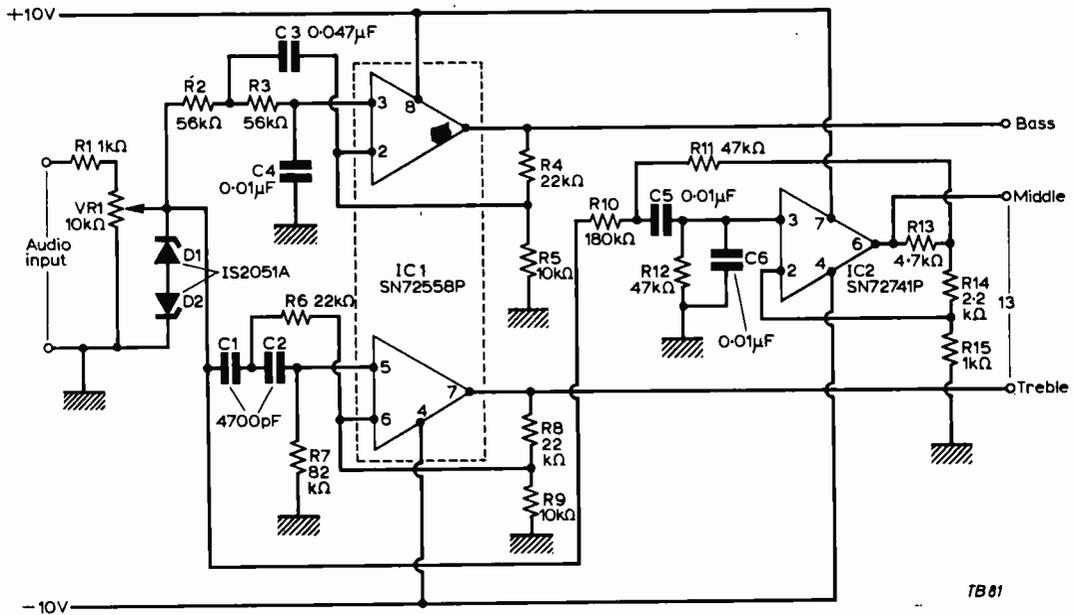


Fig. 9: Complete P.W. Tricolour filter circuit. This unit is used without modification, with either the zero voltage switching unit (Fig. 12) or with the lamp dimming unit, to be described later in this series.

this design. Cut-off frequency for the low pass filter has been chosen to be around 200Hz and that of the high pass filter (treble) about 1kHz.

Based on the above assumptions, a complete filter has been developed with the component values as shown in Fig. 9. The alert reader will notice that some of the component values differ from the figures obtained using the formulae. This has been done intentionally in order to improve the separation between the various frequency ranges.

The input to the filter circuit has been limited to 5 volts peak to peak by using two 5 volt zener diodes connected back to back. Three i.c. operational amplifiers are used. Two of which are contained in one 8 pin package, SN72558P and the other i.c. is contained in a second 8 pin package, SN72741P.

Fig. 10 shows output voltage response of the three filters plotted against frequency for a peak input signal of 0.5 volts. The effectiveness of the filters are obvious. The solid state switches—triacs—turn on their corresponding lamps at filter output voltages equal to and higher than 1.5 volts.

Figs. 11a to 11d show four oscilloscope photographs. These show traces with the vertical axes representing voltages and the horizontal one time. In each instance the four traces were taken simultaneously (i.e. they have a common time axes). In the oscillograms the top trace corresponds to the voltage at the loudspeaker terminal. The other three traces were taken at the outputs of the respective filters.

Fig. 11a was taken at a time when the treble

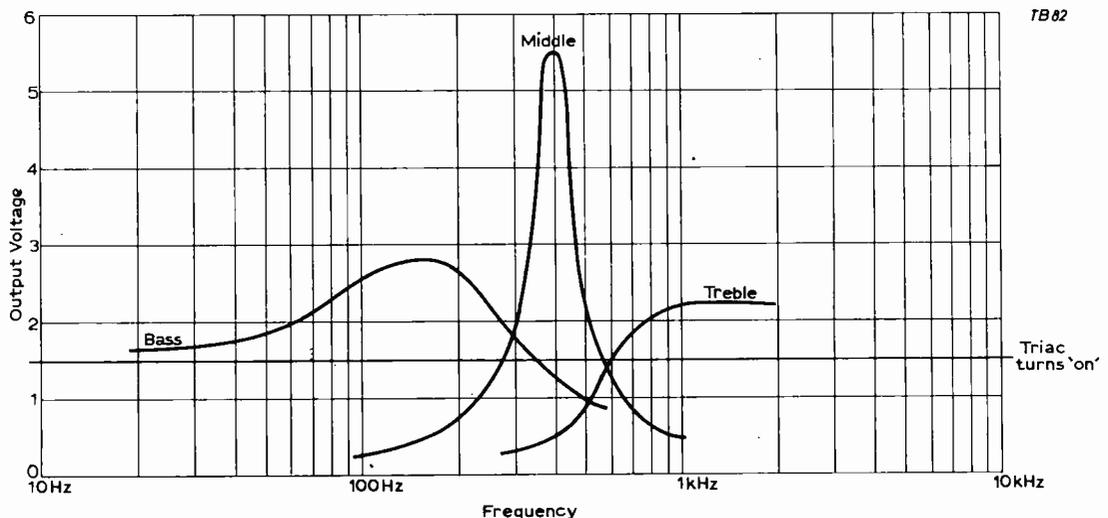


Fig. 10: Output voltage/frequency response of the filter circuit shown in Fig. 9.

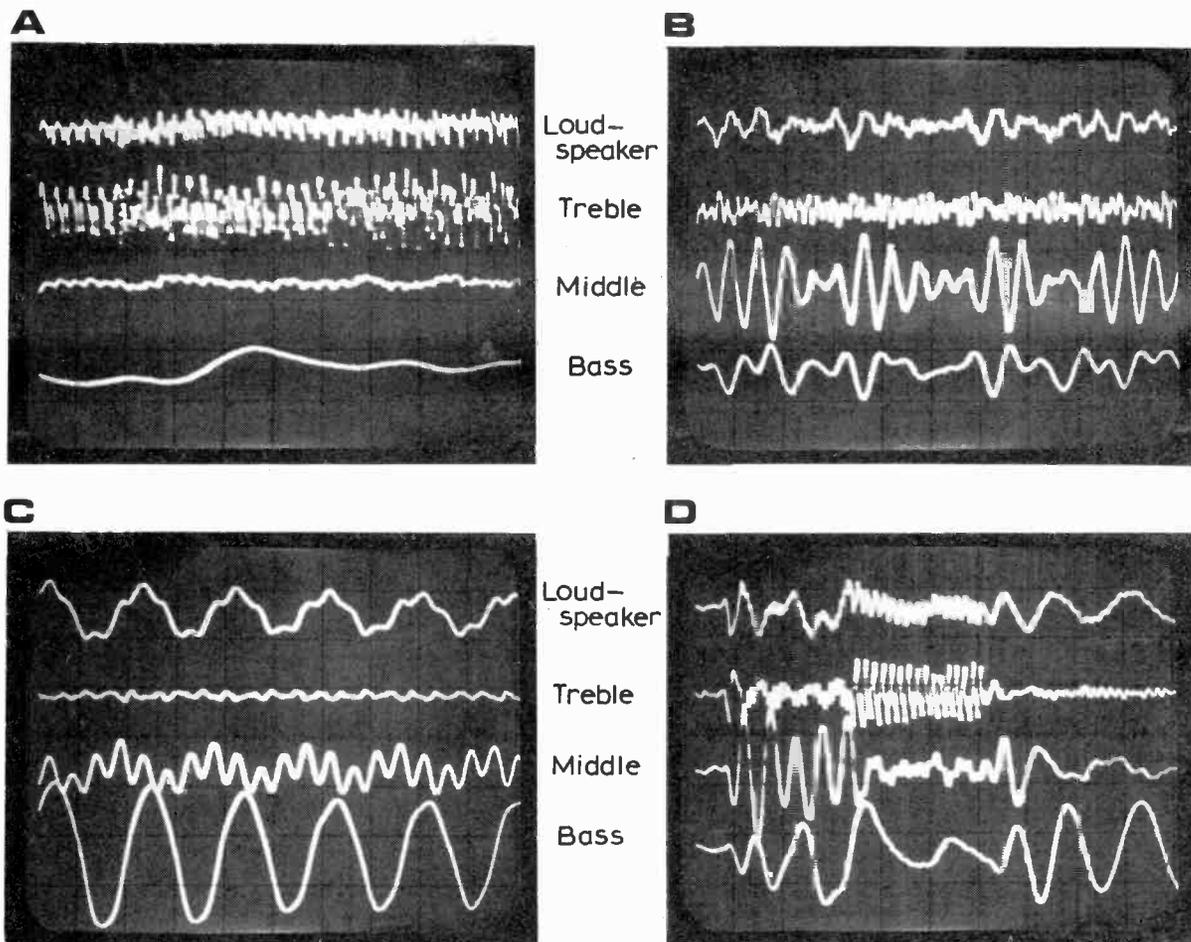



Fig. 11: (a-d) A full explanation of these waveforms is given in the accompanying text.

frequency was predominant. In Fig. 11b the middle frequency is the strongest signal, while in Fig. 11c it is the bass. Fig. 11d shows some interesting combinations of all three frequencies. The middle frequencies predominate at the beginning of the trace, then the treble takes over at the centre of oscillogram and towards the end of the trace it is the turn of the bass to predominate.

A  $10k\Omega$  potentiometer has been added at the input to the filter circuit to allow the voltage level at which the lamps are switched to be controlled. In this way it is possible to establish the best effect for 'soft' or 'party' type music.

The P.W. Tricolour is suitable for use with 4 to  $15\Omega$  loudspeakers. The load represented by the filters is negligible compared to the loudspeaker impedance.

It should be noted that the simple filter circuits illustrated at the beginning of this article used operational amplifiers. An operational amplifier has high input impedance, very high gain, and low output impedance, enabling the filter component values to be determined independent of the amplifier parameters. The amplifiers used were shown having a voltage gain of unity. This means that the output voltage of the high and low pass filters can never

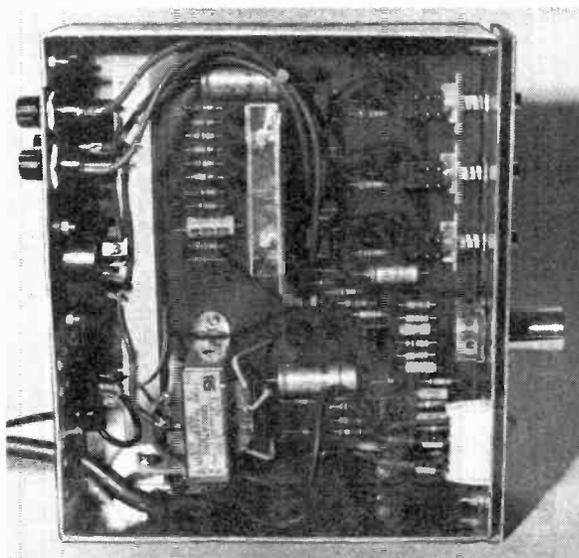

Underside view of the P.W. Tricolour with zero voltage switching.

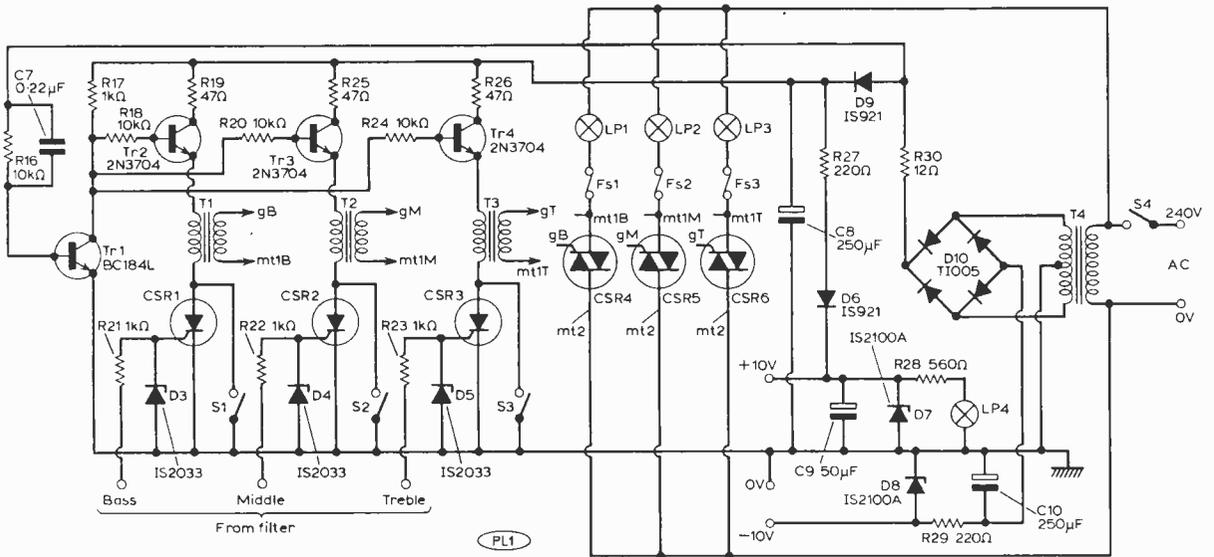


Fig. 12: Zero voltage switching control unit. The positive and negative 10V supply lines are the d.c. supplies to the filter unit (Fig. 9).

be more than the input voltage. In order to achieve voltage gain so that sufficient output can be obtained to drive the interface circuit at low volume levels, the basic circuit must be modified. This involves reducing the proportion of output voltage from the amplifier that is used as feedback to the filter capacitors and resistors. This is achieved by the use of a resistive potential divider at the output of the

amplifier. This is shown in Fig. 9. The resistor ratio determines the gain of the filter in the pass-band.

The P.W. Tricolour is suitable for either mono or stereo record playing. In the case of the stereo system, the lights will flash in accordance with the signals appearing at the terminals of one of the speakers. However, for stereo enthusiasts who wish to use two units, the interconnecting arrangement will

## ★ components list

### Resistors:

R1	1kΩ	R16	10kΩ
R2	56kΩ	R17	1kΩ
R3	56kΩ	R18	10kΩ
R4	22kΩ	R19	47Ω
R5	10kΩ	R20	10kΩ
R6	22kΩ	R21	1kΩ
R7	82kΩ	R22	1kΩ
R8	22kΩ	R23	1kΩ
R9	10kΩ	R24	10kΩ
R10	180kΩ	R25	47Ω
R11	47kΩ	R26	47Ω
R12	47kΩ	R27	220Ω
R13	4.7kΩ	R28	560Ω
R14	2.2kΩ	R29	220Ω
R15	1kΩ	R30	12Ω ½W

All 10% ½W unless otherwise specified

### Capacitors:

C1	4700pF
C2	4700pF
C3	0.047μF
C4	0.01μF
C5	0.01μF
C6	0.01μF
C7	0.22μF
C8	250μF 25V
C9	50μF 25V
C10	250μF 25V

### Transformers:

T1	Pulse trans- former, type PT-ATA ITT Ltd.
T2	
T3	
T4	Miniature mains transformer 240V primary 0-12V, 0- 12V r.m.s. 6VA, type 12V R.S. Components

### Semiconductors:

Tr1	BC184L
Tr2	2N3704
Tr3	2N3704
Tr4	2N3704
D1	IS2051A
D2	IS2051A
D3	IS2033
D4	IS2033
D5	IS2033
D6	IS921
D7	IS2100A
D8	IS2100A
D9	IS921
D10	T1005 Bridge rectifier
CSR1	TIC44
CSR2	TIC44
CSR3	TIC44
CSR4	TIC226D
CSR5	TIC226D
CSR6	TIC226D

Texas Instruments  
Ltd.


### Miscellaneous:

VR1	10kΩ linear potentiometer
FS1, FS2, FS3	5A fuses and panel mounting holders
LP1, LP2, LP3	Colour flood lamps, 240V 100W
LP4	TIL 209 Indicator lamp Texas
S1, S2, S3	Push on-push off
S4	Single pole mains on-off rocker

### Integrated Circuits

IC1	SN72558P	} Texas Instruments Ltd.
IC2	SN72741P	

# THE Medium Wave Column

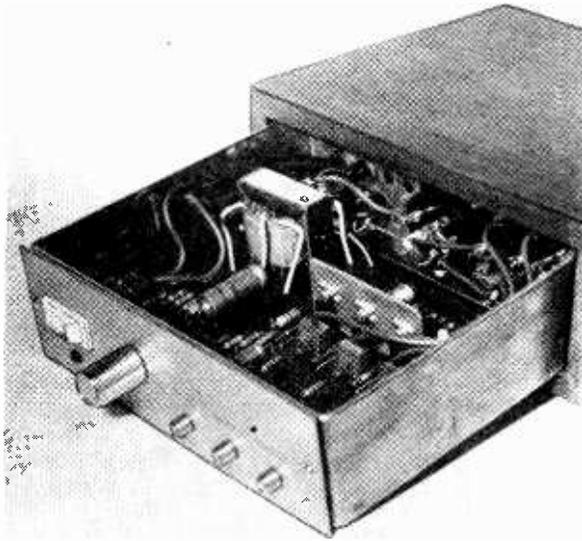

Internal view of the P.W. Tricolour.

be explained later.

Fig. 12 shows the circuit which operates the flashing lights according to the frequency ranges.

Switch S4 controls the mains supply to the unit from a 13A domestic socket. When the a.c. mains power is on the gallium arsenide device LP4 lights. A smoothed d.c. supply for transistors Tr1-Tr4 is obtained from a single phase bridge D10, resistor R30, diode D9 and capacitor C8. The  $\pm 10V$  power supply for the filter circuit is taken from zener diodes D7, D8 and capacitors C9 and C10.

As described previously, the zero voltage crossing pulses are generated at the collector terminal of transistor Tr1. These pulses turn on transistors Tr2, Tr3 and Tr4 via base resistors R18, R20 and R24. When a voltage signal from the filter circuit appears at the input terminals, the corresponding thyristors CSR1, CSR2 or CSR3 will turn on allowing pulses to be present at the respective gate of CSR4, CSR5 or CSR6 which turn them and thus their lamps on. Pulse transformers T1, T2 and T3 are used only for electrical isolation.

Zener diodes D3, D4 and D5 limit the thyristors gate voltages to 3.3V in the positive direction and to under 1 volt during the negative half cycles.

Facilities are provided for 'by-passing' the psychedelic control by closing switches S1, S2 or S3 to allow the lamps to be used as normal lights. The centre tap of the 12.0-12V mains transformer is connected to the chassis and is earthed. Note that the three triacs are mounted on a common heat-sink, which is at the supply line voltage, i.e. 240V.

The author has made arrangements for the supply of all components for the P.W. Tricolour with Henry's Radio Ltd. We understand that a detailed price list will be available from them upon receipt of a stamped addressed envelope.

**TO BE CONTINUED**

**J. KING** (Edinburgh) asks for the times and frequencies of English speaking foreign stations on the medium waves. Among the stronger there are Radio Sweden which is on 1178kHz every night at 2245hrs; Radio Portugal on 755kHz and 1161kHz. also at 2345hrs and the Vatican Radio on 1529kHz at 2100hrs. There are also the American Forces Network (AFN) outlets on 872kHz, 935kHz and 1142kHz. Try for CJON St John's, Newfoundland on 930kHz—it can be found on the low frequency side of AFN on 935kHz after 2330hrs. CJON has been a strong and consistent signal all winter and it has even been heard when conditions have been poor and no other North American could be heard.

**Harold Emblem** (Mirfield, Yorkshire) has received a QSL card (verification) from Radio Zagreb Yugoslavia which transmits on 1133kHz. The address is Radio Televizija Zagreb, PO Box 818, Zagreb Yugoslavia and reports in English are answered. Harold mentions hearing PJA6 Radio Victoria on 925kHz, which is located in the Netherlands Antilles in the Caribbean. It broadcasts religious programmes in English and other languages and is usually heard in this country after midnight.

**Harry Kenyon** (Leeds) has been looking for a published list of medium wave stations. "Broadcasting Stations of the World" published by Iliffe is available in many bookshops price 50p. It covers medium wave stations in Europe and North Africa plus a number of more powerful outlets in other parts of the world, that are usually heard in Europe. There is also a comprehensive list of short wave stations.

**Karl Ritz** (Bicester) sends a programme schedule of BBC Radio Oxford which is now on 1484kHz. Frequencies in use by BBC local radio are 850kHz R. Blackburn, 998kHz R. Solent, 1034kHz R. Medway, R. Sheffield; 1106kHz R. Leeds; 1457kHz R. London, R. Birmingham, R. Newcastle, R. Manchester; 1484kHz R. Brighton, R. Humberside, R. Merseyside. R. Oxford; 1502kHz R. Stoke; 1546kHz R. Bristol, R. Teeside; 1594kHz R. Leicester.

**Kenneth Turner** (Edinburgh) has logged R. Birmingham, R. Stoke and R. Bristol and he reports hearing Manx Radio (Britain's only commercial radio) on 1295kHz and 1594kHz.

**G. H. Esmail** (Bradford) enquires about a suitable receiver for use on the MWs. Serious DXers prefer a communications receiver such as the Trio 9R59DS or the Lafayette HA600 but an ordinary transistor portable will pull-in Europeans and North Africans and if the receiver is rotated to make use of its internal directional aerial, it will be possible to reduce quite a lot of interference.

Please send logs and information about the medium waves to the author at 132 Segars Lane, Southport PR8 3JG.


# DXers MW LOOP aerial

S.A.MONEY G3FZX

**D**URING the next two years the minimum of the current sunspot cycle should occur. Although short wave reception usually suffers at the period of the sunspot minimum the conditions will become very favourable for the reception of DX signals on the medium wave broadcast band. Unfortunately, the interference from European stations, many of which now remain on the air all night, is likely to be much worse than it was during the last sunspot minimum. In order to winkle out the weaker DX signals from the QRM it will be important to choose an effective aerial system as well as a good receiver.

In the late 1950's the writer, in collaboration with Reg Dunkley of Havant, Hampshire, carried out a series of tests to investigate the possibility of using a tuned loop aerial for the reception of DX signals on the medium wave band. These tests showed that although the loop aerial is somewhat less sensitive than the usual outdoor wire type aerial it has several advantages which make it attractive for DX work.

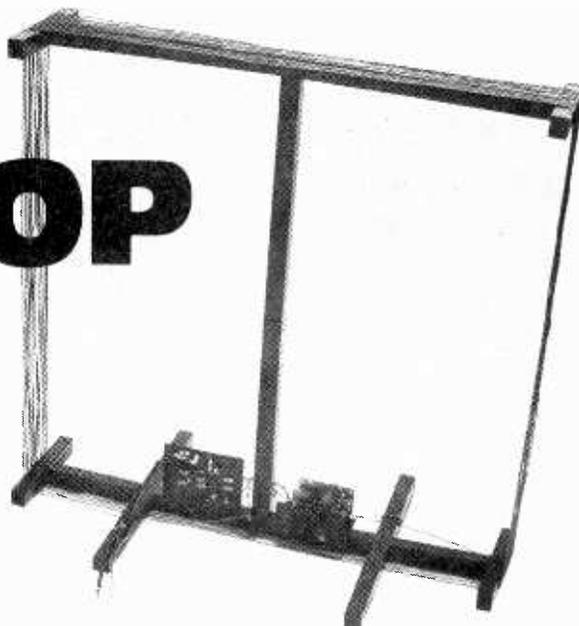Pick-up of background noise and static seems to be rather less on the loop aerial than it is on a wire aerial so that although giving less signal the loop does usually give a better signal to noise ratio.



By rotating the loop aerial its directional properties can be used very effectively to cut down adjacent channel interference from strong European signals. A further advantage of the loop aerial is that it is very compact and hence attractive to the listener who is unable to use a large outdoor aerial system.

The advantages of the loop aerial have, in the past ten years, made it very popular among the medium wave DX enthusiasts in Britain.

Although the basic loop aerial as used by most of these DX'ers is quite effective it is not the optimum arrangement.

In the past year the writer has experimented with methods of improving the performance of this type of aerial. In this article a system is described consisting of a loop aerial and a matching amplifier capable of giving a performance superior to that of the basic loop aerial.

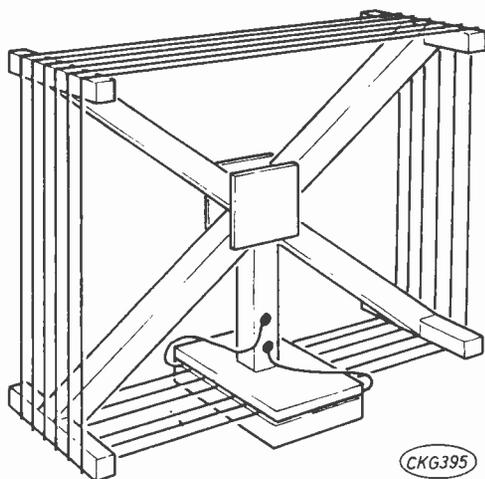


Fig. 1: Configuration of a typical m.w. loop aerial.

## HOW THE LOOP WORKS

Before going on to describe the improved aerial system it would be as well to consider the make up of the basic loop aerial and the way in which it works. This type of aerial used to be a standard fitting in portable radios before the arrival of the ferrite rod aerial.

The loop aerial usually consists of a number of turns of wire wound in the form of a short coil on a large wooden frame. Typical aeriels are square in shape as shown in Fig. 1 although circular or diamond shaped loops will also work. The length of the sides may be from 12in. up to about 4ft. In general the larger size aeriels give greater signal output and rather better directional properties.

Normally the turns of the winding are spaced apart from one another to reduce self capacitance. The whole aerial is then tuned to resonance by a variable capacitor connected across the ends of the loop.

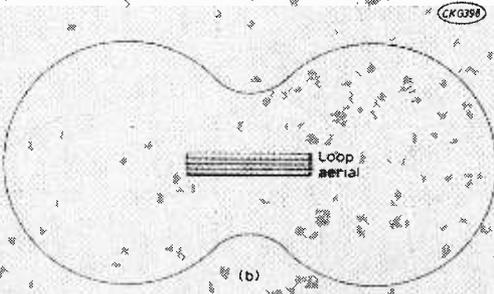
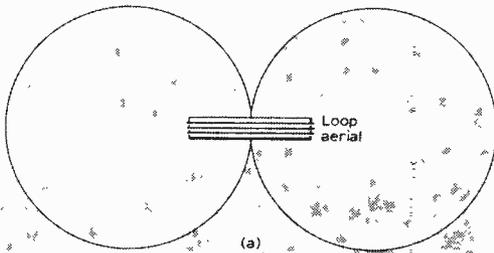
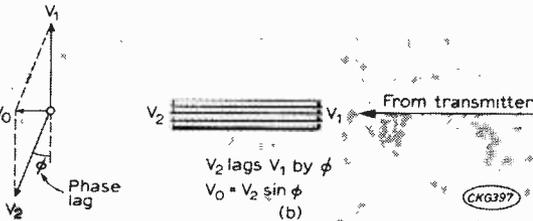
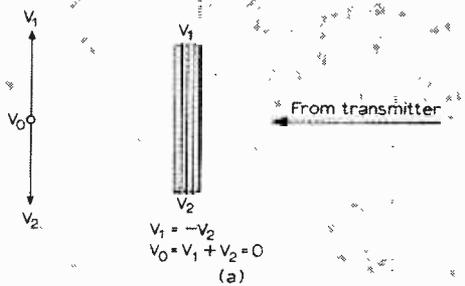
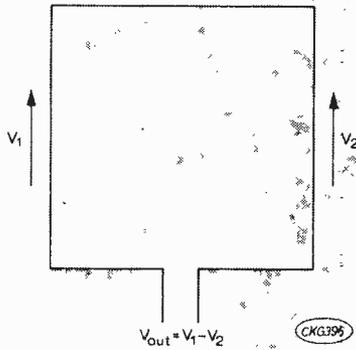


Fig. 2: (top) Voltages induced in a single turn loop. Fig. 3: (centre) indicates how the output of the loop depends on its position relative to the signal source. Fig. 4: (bottom) illustrates the modified pick-up pattern of a loop due to "antenna" effect.

To see how the loop works let us assume that there is only one turn as shown in Fig. 2. When radio waves pass through the loop a voltage will be induced in each of the vertical sides. These voltages are shown as  $V_1$  and  $V_2$ . The relative polarity of the two voltages is indicated by the arrows. It will be seen that the voltage at the terminals of the loop will be made up of  $V_1$  and  $V_2$  connected in series. When the two voltages are connected in this way they will be effectively in opposition to one another so that the resultant output voltage at the loop terminals will be the difference between  $V_1$  and  $V_2$ . In practice the two voltages are alternating and therefore the difference voltage will depend not only upon amplitude but also upon the phase of  $V_1$  relative to  $V_2$ .

Suppose the loop is set up so that it is broadside on to the direction from which the received signal is coming. This is shown in Fig. 3(a) which shows a view looking down on to the aerial. Both vertical sides of the loop will be at exactly the same distance from the transmitter aerial so the induced signal voltages  $V_1$  and  $V_2$  will be of the same amplitude and in phase with one another. At the output terminals the difference voltage produced will be zero since  $V_1$  and  $V_2$  will cancel out exactly. This is known as the 'null' position for the loop since there will be no signal output.

Now let us see what happens when the loop is turned so that it is in line with the direction of the signal being received as shown in Fig. 3(b). In this case one side of the loop is closer to the transmitter than the other. Since the width of the loop is very small compared with the distance to the transmitter the amplitudes of the induced voltages  $V_1$  and  $V_2$  will still be virtually equal. The radio wave will, however, take a finite time to travel from the near side of the loop to the far side so that  $V_2$  will lag behind in phase relative to  $V_1$ . This phase shift of  $V_2$  will produce a difference signal output at the loop terminals. In fact at this position the loop will give its maximum output signal.

The resultant pick up pattern for a loop aerial will be as shown in Fig. 4(a). If extra turns are now added to the loop so that it forms a short coil the voltages produced by each of the turns will add together at the output terminals. As a result the output from the aerial will be proportional to the number of turns used. For a multi-turn aerial the pick up pattern will be the same as for a single turn. A further increase in output can be obtained if the aerial is tuned to resonance by connecting a variable capacitor across the ends of the loop winding.

## "ANTENNA" EFFECT

One of the difficulties which occurs when using a loop aerial is known as the "antenna" or "vertical" effect. Unless the aerial is exactly balanced electrostatically with respect to earth it will act as a normal vertical aerial. A simple vertical aerial picks up the signal at equal strength from all directions in the horizontal plane. Now we get the condition that when the aerial is broadside on to the direction of the signal the voltages  $V_1$  and  $V_2$  cancel as before but the output due to "antenna" effect remains constant. This results in a pick-up pattern like that in Fig. 4(b) where the nulls are less marked and much broader than for a perfect loop.

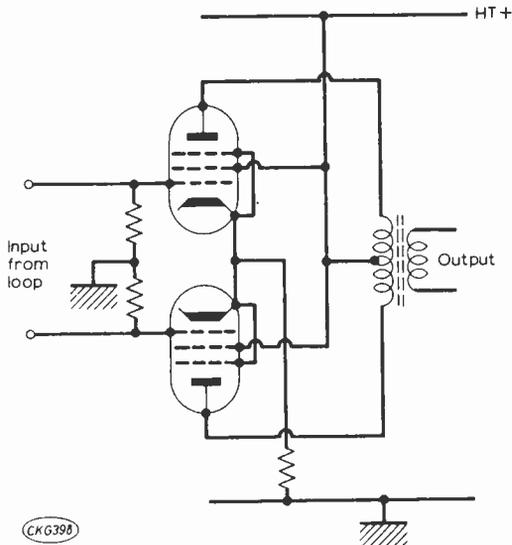


Fig. 5: Basic circuit of an early valve-type balanced input stage.

Perhaps the most obvious method of coupling the loop to the receiver would be to connect it directly across the aerial input terminals of the receiver. This method is rarely successful since the aerial will be unbalanced to earth and "antenna" effect is usually very bad.

For the basic loop aerial used by m.w. DX'ers the usual method of coupling is by means of a link winding. The link usually consists of one turn, or sometimes two, wound on the frame alongside the main winding. This link winding is then connected directly to the receiver input. With a link coupling of this type the aerial usually works quite well except that the link winding itself tends to produce some output due to "antenna" effect.

## DIFFERENTIAL MATCHING AMPLIFIER

Wartime d.f. receivers, such as the R1155, made use of a differential or push-pull amplifier at the input. This type of amplifier uses two valves with

## ★ components list

### Resistors

R1 47k $\Omega$	R5 47k $\Omega$	R9 10k $\Omega$
R2 1k $\Omega$	R6 2.2k $\Omega$	R10 470 $\Omega$
R3 100 $\Omega$	R7 330 $\Omega$	R11 100 $\Omega$
R4 1k $\Omega$	R8 330 $\Omega$	VR1 500 $\Omega$ preset

All  $\frac{1}{2}$ W 5%

### Capacitors

C1 4.7nF polyester	C3 4.7nF polyester
C2 0.1 $\mu$ F foil	

### Semiconductors

Tr1 2N3823	Tr3 2N3823
Tr2 2N706	Tr4 2N3823

their cathodes connected together as shown in Fig. 5. The resistor in the cathode circuit is made large enough so that it acts as a constant-current source. This type of amplifier responds only to differences in voltages between the two grids and will reject any signal common to both grids such as that produced by "antenna" effect in the loop aerial.

A balanced input amplifier using transistors instead of valves is shown in Fig. 6. In order to maintain a high value of Q in the aerial circuit a pair of field effect transistors is used for the differential input stage. This type of transistor has similar characteristics to a valve and gives a much higher input impedance than a normal bipolar type transistor. In this circuit 2N3823 'N' channel field effect transistors are used.

A differential amplifier works most effectively when the common-tail circuit of the input pair is fed from a constant-current source. In the valve version this is achieved by feeding the common cathode point through a large resistor from a negative supply voltage. In the circuit of Fig. 6 the transistor Tr2 is used to provide a constant current feed.

Characteristics of the 2N3823 may vary widely from one transistor to another. For optimum results the two transistors Tr1 and Tr3 in the input stage should either be matched or at least have similar characteristics. This can be checked by using the


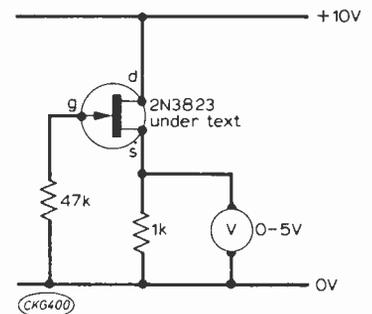


Fig. 6: (left) Complete circuit of the loop matching amplifier. Note that the 2N3823 transistor specified is preferable to the unscreened 2N3823E. Fig. 7: (above) is the circuit of the simple test set-up for checking the characteristics of the f.e.t.'s.

# BRITAIN'S FASTEST SERVICE!

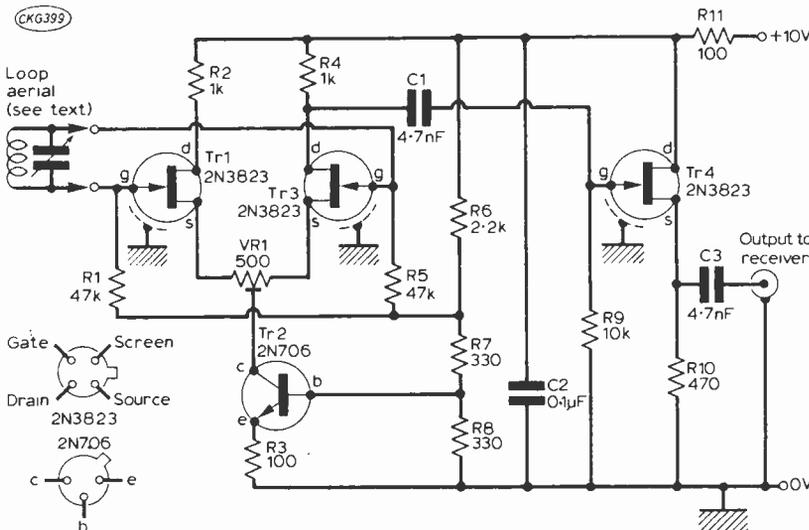

A SELECTION FROM OUR COMPREHENSIVE CATALOGUES

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCY58	18p	CA3043	£1.73	OA81	8p	1N4007	19p	2N6027(D13T1)	45p
AC107	30p	BCY70	15p	CA3044	£1.02	OA90	8p	1N4148	4p		
AC126	28p	BCY72	39p	CA3046	£1.46	OA91	5p	1N5400	14p	3N84	£1.30
AC127	25p	BD124	75p	CA3048	£2.34	OA95	5p	1N5404	18p	3N128	88p
AC128	24p	BD124	75p	CA3052	£1.80	OA200	6p	1N5408	25p	3N140	£1.05
AC128/AC129	36p	BD131	75p	CA3055	£1.80	OA202	7p	1S44	4p	3N152	£1.05
AC151	12p	BD131/132	£1.50	CA3088E	£1.38	OC20	7p	1S920	6p	30155G	£2.00
AC152	15p	BDY20	23p	CA3090Q	£4.70	OC25	37p	1S940	80p	30155G	£2.00
AC153	18p	BF115	92p	CD4001AE	72p	OC28	70p	1S5009	10p	7400	15p
AC176	25p	BF183	35p	CD4009AE	£1.56	OC29	76p	1S5012	80p	7401	20p
AC153/176K	32p	BF167	35p	CD4011AE	72p	OC35	60p	1S5015	75p	7402	20p
AC187	17p	BF173	19p	CD4012AE	£1.16	OC36	63p	1S5018	75p	7403	20p
AC188	23p	BF177	25p	CD4015AE	£3.90	OC41	40p	1S5024	75p	7404	25p
AC187/188K	40p	BF178	31p	CD4017AE	£3.90	OC42	40p	1S5047	75p	7405	25p
ACY17	27p	BF180	35p	CD4018AE	£3.90	OC44	20p	2N4047	23p	7408	25p
ACY18	20p	BF194	15p	CD4020AE	£4.34	OC45	20p	2N696	15p	7409	25p
ACY19	20p	BF195	15p	CD4024AE	£2.78	OC71	20p	2N697	17p	7410	20p
ACY20	20p	BF196	15p	CR17051C	45p	OC72	25p	2N706	30p	7413	20p
ACY21	19p	BF200	35p	CR1401C	60p	OC75	25p	2N706	12p	7420	30p
ACY22	10p	BF254	14p	CRS3/05AF	£1.08	OC76	25p	2N706A	40p	7425	30p
AD140	55p	BF255	19p	CRS3/40AF	£1.53	OC81	20p	2N708	20p	7430	20p
AD149	50p	BFX13	25p	CRS3/40AF	£1.53	OC81D	20p	2N911	20p	7440	20p
AD161	35p	BFX29	25p	CZ6	15p	OC82	20p	2N914	20p	7442	£1.16
AD162	38p	BFX84	25p	D10 (NTGD10)	10p	OC84	25p	2N918	42p	7443	£1.45
AD161/162	24p	BFX85	25p	DIRT	5p	OC88	25p	2N929	25p	7444	£1.45
AF108	24p	BFX86	25p	IRT84	£2.90	OC139	35p	2N930	28p	7445	£2.06
AF114	25p	BFX87	30p	LIC709C/5	£2.90	OC140	35p	2N1131	24p	7446	£1.45
AF115	25p	BFX88	30p	LIC709C/8	£2.90	OC170	24p	2N1132	24p	7447	£1.25
AF116	25p	BFY50	55p	LIC709C/14	£1.02	OC171	30p	2N1302	17p	7450	20p
AF117	25p	BFY51	55p	LIC723C/5	£1.02	OC371M	42p	2N1303	17p	7451	20p
AF118	44p	BFY52	40p	LIC741C/5	45p	ORP60	50p	2N1305	24p	7453	20p
AF124	25p	BFY53	40p	MC1303L	£1.77	ORP61	40p	2N1306	30p	7460	20p
AF125	24p	BFY90	15p	MC1305P	£2.80	ORP69	50p	2N1307	30p	7470	45p
AF126	17p	BP101	75p	MC1307P	£1.65	PN70	8p	2N1308	34p	7472	32p
AF139	30p	BPX66	£1.35	MC1310P	£2.95	PN71	8p	2N1309	34p	7473	45p
AF186	40p	BRX39	40p	MC1312P	£2.75	PN107	7p	2N1559 (CR1)	60p	7474	45p
AF239	36p	BSX19	16p	MC1330P	£2.90	PN108	7p	401C	60p	7475	45p
AF279	47p	BSX20	16p	MC1330P	£2.90	PN109	7p	2N1613	15p	7476	45p
ASV26	30p	BSY27	20p	MC1330P	£2.90	PN3819(2N3819)	7p	2N1711	15p	7480	45p
ASV27	30p	BSY27	20p	MC1330P	£2.90	PN3819(2N3819)	7p	2N1711	15p	7480	45p
ASV28	22p	BSY29	25p	MC4024P	£2.20	ST2	28p	2N1893	54p	7482	£1.32
ASV29	30p	BSY95A	12p	MC4044P	£2.20	SL103A	50p	2N2218	33p	7483	£1.32
BA138	15p	BY100	20p	MFC6030	£1.63	SL403A (Rect)	50p	2N2218A	44p	7486	33p
BA138	15p	BY127	22p	MFC6040	£1.15	SL403A (Rect)	50p	2N2219	38p	7490	33p
BA138	15p	BY127	22p	MFC6040	£1.15	SL403A (Rect)	50p	2N2219A	53p	7491A	£1.28
BB103	18p	BTY79/400R	92p	MFC8010	£1.38	SL803A	60p	2N2368	17p	7493	£1.50
BB104	23p	BTY79	£1.20	MFC8040	£1.24	SL803D	60p	2N2369	17p	7493	£1.50
BB105	32p	BZ88C3V3	13p	MJ5E20	£2.12	TA03D	65p	2N2369	17p	7493	£1.50
BC107	10p	BZ88C3V6	13p	MJ5E20	£2.12	(IC Amp.)	£1.50	2N2369A	17p	7494	£1.50
BC107/BC177	24p	BZ88C3V9	13p	MJ5E20	£2.12	TA263	97p	2N2484	42p	7495	£1.48
BC108	10p	BZ88C4V7	13p	MJ5E21	£1.06	TA293	97p	2N2646	45p	7496	£1.48
BC109/BC178	23p	BZ88C5V6	13p	MJ5E25	£1.26	TA310	75p	2N2904	44p	74100	£1.64
BC109	10p	BZ88C6V2	13p	MJ480	66p	TA320	75p	2N2904A	49p	74107	52p
BC109/BC179	24p	BZ88C6V8	13p	MJ481	£1.25	TA361	97p	2N2905A	75p	74121	£1.50
BC109	10p	BZ88C7V5	13p	MJ802	£4.12	TAD110	£1.97	2N2924	18p	74150	£1.35
BC109	10p	BZ88C8V2	13p	MJ802/MJ4502	£2.00	TIL209	35p	2N2926	26p	74151	£1.35
BC140	30p	BZ88C9V1	13p	MJ900	£1.80	TIP31A	60p	2N3053	27p	74153	£2.00
BC148	8p	BZ88C11V	13p	MJ1000	£1.50	TIP32A	70p	2N3054	50p	74155	£1.55
BC149	10p	BZ88C12V	13p	MJ4502	£4.44	TIP42A	85p	2N3055	50p	74156	£1.55
BC157	12p	BZ88C13V	13p	MPF103(2N5457)	17p	TIS43	£2.90	2N3391A	£1.79	74190	£1.80
BC158	11p	BZ88C15V	13p	MPF103(2N5457)	17p	TIS43	£2.90	2N3525	£1.79	74191	£1.80
BC147/157	22p	BZ88C18V	13p	MPF103(2N5457)	17p	VA1066s	£1.97	2N3702	9p	74192	£1.74
BC148/158	20p	BZ88C20V	13p	MPF104(2N5457)	49p	VA1039	15p	2N3703	9p	74193	£1.50
BC149/159	22p	BZ88C22V	13p	MPF105(2N5457)	49p	VA1040	15p	2N3704	9p	74196	£1.50
BC167	11p	BZ88C24V	13p	NKT0033	46p	W01	31p	2N3705	9p	74197	£1.50
BC168	11p	BZ88C27V	13p	NKT211	25p	W02	31p	2N3706	9p	40325	60p
BC169	11p	BZ88C30V	13p	NKT212	25p	W04	35p	2N3707	9p	40329	60p
BC177	15p	BZ88C32V	13p	NKT213	25p	W06	35p	2N3708	7p	40330	60p
BC178	15p	BZ88C34V	13p	NKT216	46p	ZTX107	50p	2N3710	9p	40331	42p
BC179	14p	BZ88C10V	23p	NKT217	50p	ZTX108	11p	2N3711	9p	40332	62p
BC182	10p	BZ88C11V	23p	NKT218	25p	ZTX109	11p	2N3819	25p	40360	56p
BC182L	10p	BZ88C12V	23p	NKT219	25p	ZTX130	15p	2N3823A	20p	40362	45p
BC183	10p	BZ88C13V	23p	NKT223	25p	ZTX302	15p	2N3826	30p	40406	52p
BC183L	10p	BZ88C14V	23p	NKT223	25p	ZTX303	15p	2N3866	£1.10	40407	40p
BC184	10p	BZ88C15V	23p	NKT224	18p	ZTX304	23p	2N3904	28p	40408	54p
BC184L	12p	BZ88C16V	23p	NKT225	20p	ZTX314	11p	2N3906	28p	40409	54p
BC212	12p	BZ88C17V	23p	NKT225	20p	ZTX314	11p	2N4058	13p	40410	62p
BC212L	12p	BZ88C18V	23p	NKT225	20p	ZTX314	11p	2N4060	11p	40430	£1.22
BC238	10p	BZ88C19V	23p	NKT225	20p	ZTX314	11p	2N4061	11p	40432	£1.90
BC238/308	29p	BZ88C20V	23p	NKT225	20p	ZTX314	11p	2N4062	11p	40468A	£1.95
BC251	9p	BZ88C30V	23p	NKT402	77p	ZTX502	17p	2N4444	£2.20	40512	52p
BC258	9p	CA3004	£2.25	NKT403	65p	ZTX503	17p	2N4871	40p	40576	70p
BC259	9p	CA3005	£1.50	NKT404	65p	ZTX504	40p	2N5245	45p	40600	70p
BC307	12p	CA3011	92p	NKT405	79p	1N914	20p	2N5457(MPF103)	49p	40601	70p
BC308	10p	CA3013	£1.30	NKT406	62p	1N3754	29p	2N5458(MPF104)	49p	40602	45p
BCY30	25p	CA3014	£1.52	NKT713	25p	1N4001	29p	2N5459(MPF105)	49p	40603	70p
BCY31	48p	CA3015	£1.85	NKT713	25p	1N4002	29p	2N5459(MPF105)	49p	40603	70p
BCY32	50p	CA3018A	£1.15	NKT781	29p	1N4003	29p	2N5459(MPF105)	49p	40603	70p
BCY33	20p	CA3020	£1.55	NTGD10	40p	1N4004	40p	2N5459(MPF105)	49p	40603	70p
BCY34	25p	CA3028A	88p	OA47	8p	1N4005	12p	2N5459(MPF105)	49p	40603	70p
BCY38	30p	CA3035	£1.52	OA79	8p	1N4006	15p	2N5777	45p	40739	£1.50

### ELECTROLYTIC AXIAL LEADS

Mfd	Working Voltage	Price	Mfd	Working Voltage	Price
1 0	40v	7p	100	16v	5p
1 0	100v	5p	100	25v	4p
2 2	25v	7p	100	40v	7p
£1 05	63v	5p	100	63v	10p
£1 05	63v	5p	220	25v	6p
4 7	10	5p	220	40v	9p
£2 00	10	5p	220	25v	6p
£2 00	25v	5p	220	40v	9p
10	63v	8p	1000	25v	5p
22	25v	6p	1000	25v	5p
22	40v	6p	2200	25v	30p
47	25v	6p	4700	16v	3p
47	40v	6p			

### CAPACITORS—METALLISED POLYESTER

Stock values: MFD  
0.01, 0.015, 0.022, 0.033  
0.047, 0.068, 0.10  
0.150, 0.220

Price each  
3p  
5p  
7p  
8p  
11p  
14p  
20p  
24p

Order as "Polyesters" + Capacitance.

### CAPACITORS—POLYSTYRENE

Axial leads, Clear encapsulation, 5% Tolerance. 160 volt working.

Stock values  
100pF, 150pF, 220pF, 330pF, 470pF, 560pF, 680pF, 820pF,  
1000pF, 1500pF, 2200pF, 3300pF, 4700pF, 5600pF, 6800pF.

Order as "Polystyrenes" + Capacitance.

Price each  
3p

### ALUMINIUM HEAT SINKS

10DN 34p (Plain All undrilled)  
10DDR 43p (Plain All drilled 2 x To3)

### LOW PRICED DIL IC HOLDERS

DRD 7 14 Pin DIL 15p DRD 8 16 Pin DIL 17p

### NYLON NUTS AND BOLTS

Cheese head screw bolts. Nuts with integral washer. Moulded in high density nylon. Ideal for mounting "live" assemblies, power transistors, etc.

Each pack consists of four nuts and four screw bolts.

||
||
||

# LINEAR


## AMPLIFIERS FOR GUITAR PICK-UPS GRAM PICK-UPS RADIO or TAPE

OVERLOAD PROTECTION INCORPORATED. SOLID STATE CIRCUITRY

Suitable for application of Loudspeaker impedances between 8 and 30 ohms. Combinations not to measure less than 6 ohms across both speaker output jacks simultaneously.

The Amplifier cover is made of rigid plastic, bonded metal on top and two sides. Finished in Black to suitably contrast with anodised metal control panel. Size approx. 14" x 4 1/2" x 9 1/2".

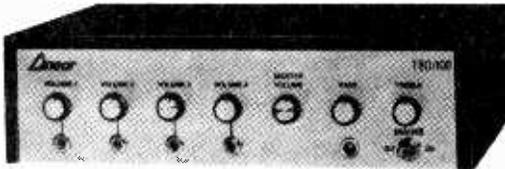From April 1st prices are subject to VAT.



Rec. Retail Price

**£69-75**

## GENERAL PURPOSE AMPLIFIER

Model T80/100 70 - 100 Watts Output Power

Four individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.


Compact size, robust construction. Ideal for clubs, hotels, restaurants, schools etc. Inputs for almost any type of microphone

## GENERAL PURPOSE GROUP/DISCO AMPLIFIER Model T80/100D

70 - 100 Watts Output Power

Three individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'. Compact size. Robust construction. Ideal for discotheques, clubs, hotels, schools, etc. Inputs for most types of microphones. Facilities for head-phone monitoring with changeover switch from input (1) to input (2).

Rec. Retail Price  
**£69-75**

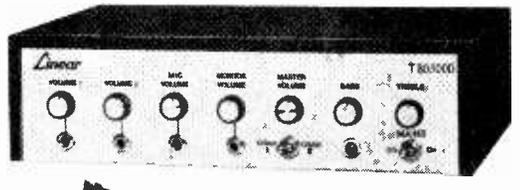

Wholesale and Retail enquiries to the Manufacturers Send S.A.E. for leaflet/s All Linear Amplifiers Guaranteed for 12 Months

**LINEAR PRODUCTS LTD.,** Electron Works, Armley, Leeds. LS12 3SA Tel. 630126

### GUNTON ELECTRONIC IGNITION KIT £9.35 inc. V.A.T.

PRINTED CIRCUIT BOARD DESIGN. ALL METALWORK READY-DRILLED

READY BUILT UNIT GUARANTEED 5 YEARS £11.55 inc. V.A.T. Patents pending 12 volt only—state pos; or neg. earth. Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- ★ Continual Peak-Tuned Performance
- ★ Up to 20% reduced fuel consumption
- ★ Easier All-weather Starting
- ★ Increased Acceleration and Top Speed
- ★ Longer Spark Plug Life
- ★ Increased Battery Life
- ★ Elimination of Contact Breaker Burn
- ★ Purer Exhaust Gas Emission

Kit includes absolutely everything for assembly: Case, Cables, Coil Connectors, Silicon Grease, etc. 8 page illustrated instructions cover fitting of all types of Tachometers. Call in for a Workshop Demonstration. S.A.E. all enquiries please or Phone 33652 (many letters from satisfied customers).



### ALUMINIUM BOXES

Complete with baseplate and screws

At direct from manufacturer prices with return of p post service

Type No.	L	W	D	Price
7*	5 1/2	2 1/2	1 1/2	44p
8*	4	4	1 1/2	44p
9*	4	2 1/2	1 1/2	44p
10*	5 1/2	4	1 1/2	53p
11	4	2 1/2	2	44p
12	3	2	1	39p
13	6	4	2 1/2	59p
14	7	5	2	68p
15	8	6	3	88p
16	10	7	3	96p

\*THESE SIZES ACCEPT STANDARD VEROBOARD RANGE ALL PRICES INCLUDE V.A.T. 20% DISCOUNT ON ORDERS FOR 10 OR MORE BOXES

DEPT. PW 4 ELECTRONICS DESIGN ASSOCIATES 82 BATH STREET, WALSALL WS1 3DE

### FELSTEAD ELECTRONICS (PW 67) LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Caller service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Re greet orders under 25p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas Orders welcomed.

RECORDING TAPE: Finest quality/value British Mylar available: STANDARD 5" 600ft. 40p, 5 1/2" 900ft. 55p; 7" 1200ft. 62p; LONG PLAY 5" 900ft. 55p; 5 1/2" 1200ft. 62p; 7" 1800ft. £1.00 (Charges for 5" and 5 1/2", singles 9p, two to four 8p each; five and over 33p the lot.) For 7", one or two 11p each reel. 3, 4 and 5 reels 33p the lot. 6 reels and over 33p the lot.) Other sizes and accessories in list. CASSETTES in lb cases new type highly improved quality C80 55p, C90 72p, C120 99p (under 5, 3p each; 5 for 17p the lot; any quantity over 5, 28p the lot.)

CARTRIDGES all with standard fittings and styli. Stereo-compatible Mono GP91/8C 98p; STEREO GP93 £1.35, Stereo Ceramic GP04 £1.75. (All at 7p each.) Comparatives shown in List, with more types inc. Sonotone 9TAHC, Stereo Ceramic Diamond £1.70 (7p). DIAMOND STYLI: single tip types: Acos GP37, GP59, GP55/67, GP71, BSR TCS/LP/ST; COLLAR O.P. and DC284, GARRARD G02, G05, G08/10; GCE12, RONETTE BK40, O.P. and T. PHILIPS 3301 (3060, 3066, 3302, 3304), 3010/12/13/16, SONOTONE 19T/20T ALL AT 36p each (7p). SAPPHIRE 18p (7p) DIAMOND DOUBLE TIP TURNOVER TYPES (78 sp. on other side). For ACOS GP73, GP91 (cartridges GP93, GP94 etc.) GP918C (for stereo compat. types) GP104 BSR 8T4 (8T3, 8T5), 8T9 (8T8), 8T12/14/15, SONOTONE 8TA, 9TA, 9TAHC, PHILIPS 3306 3310, 3224, 3228/22 GP280, GARRARD GCM21, and 22, GCS23, GCS25 and 26, GCM21T and 22T, GCM 24T GCS23, GCS25T and 26T, GCM31, GCS36, GCS35, GCS38, K840A, K841B ETC. ALL AT 68p (7p). SAPPHIRE 32p (7p). DOUBLE DIAMOND STYLI: same dia ST/TP tip each side: no 78) All types £1.35 (7p). SAPPHIRE DOUBLE ST/LP, TIPPED 82p (7p). PICK-UP WIRE: super thin flex screened, sheathed, TWIN 7p per yard, 4-core 13p per yard (either up to 6 yds. 7p). Over, charges paid. MICROPHONES: CRYSTAL: LAPEL 1 1/2", clip/hand, lead 3-5mm jack plug 38p (9p), CM20 Cream Plastic hand 58p (9p); CM70 PLANTIC Metal, tapered with neck cord, adaptor for stand £1.95 (11p); "MIC 45" Curved metal hand grip £1.10 (11p) ALL with lead. DYNAMIC: 209 Cardiod Ball, 50K/600 Ω built in volume control, on/off switch, special 20ft lead, the best value anywhere at 26.40 (33p); UD130, uni-dir mesh ball 50K/600 Ω jack plug, cable, adaptor, 25.28 (22p); DM160, omni-dir, Ball mesh, 50K, cable adaptor, jack plug, 24.29 (33p each). SPEAKERS: Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) 28.08 (36p) or pair for stereo 24.65, charges paid; SMALL 2 1/2", 3 Ω, 6 Ω or 8 Ω (state which) 36p (9p). More speakers in List. HEADPHONES: High resistance 2000 Ω adjustable £1.10 (11p). EARPIECES: with lead and min. 2-5mm or 3-5mm (state which) jack plug. MAGNETIC 11p. CRYSTAL (3-5mm plug only) 28p (up to 6 for 9p any size). SOLDERING IRON: Slim, modern, British high speed, 8 1/2", all parts replaceable, highest quality, fully guaranteed £1.29 (11p) TRANSFORMERS: 8ub-min 11 x 11 x 12mm. OUTPUT (3 Ω for OCT2, etc.) 18p or DRIVER 17p (Up to 12 for 7p). CONNECTING WIRE: Packs of 5 coils, each coil 5yds. Assort. coils. 50 LID CORE 18p (7p.) FLEXIBLE CORE 15p (9p). SUPER THIN flexible for transistor wiring, etc. 18p (7p) RETRACTABLE FLEXIBLE LEADS (CURLIES): With phono plug, each end, 6ft 28p, 12ft 44p. With phono plug/phone socket other end 6ft. 28p, 12ft 50p (6p lead any type). VIBRATORS: 12v/4 pin non-synch. 121HD4, 2 1/2" ex. pins, 38p. 8AME but 3 1/2" ex. pins, 18A 18p. 12v/7 pin synch. (128R7) 2 1/2" ex. pins, 72p (9p any type). MAINS NEONS, 7y leads 11p. NEON SCREWDRIVER (pocket tester) 19p (7p either). MAINS BATTERY ELIMINATOR. Input 240v-AC. Output 3, 4f, 6, 7, 9 and 12 volt D.C. by switch selector. On/off switch, pilot lamp, leads, plug to suit most cassette recorders, 24-12 (27p). Highly suitable for all transistor receivers.

SPECIAL NOTICE—BETWEEN FEB. 22nd and MARCH 14th SOME DELAY IN DESPATCH OR ORDERS AND REPLIES TO CORRESPONDENCE MAY OCCUR DUE TO RECONSTRUCTION. ALL ABOVE PRICES HAVE BEEN ADJUSTED TO INCLUDE V.A.T. BUT FOR ALL ORDERS DESPATCHED BY US UP TO MARCH 31st, PRE-VAT PRICES AS PER LAST MONTHS ADVERTISEMENT WILL APPLY.

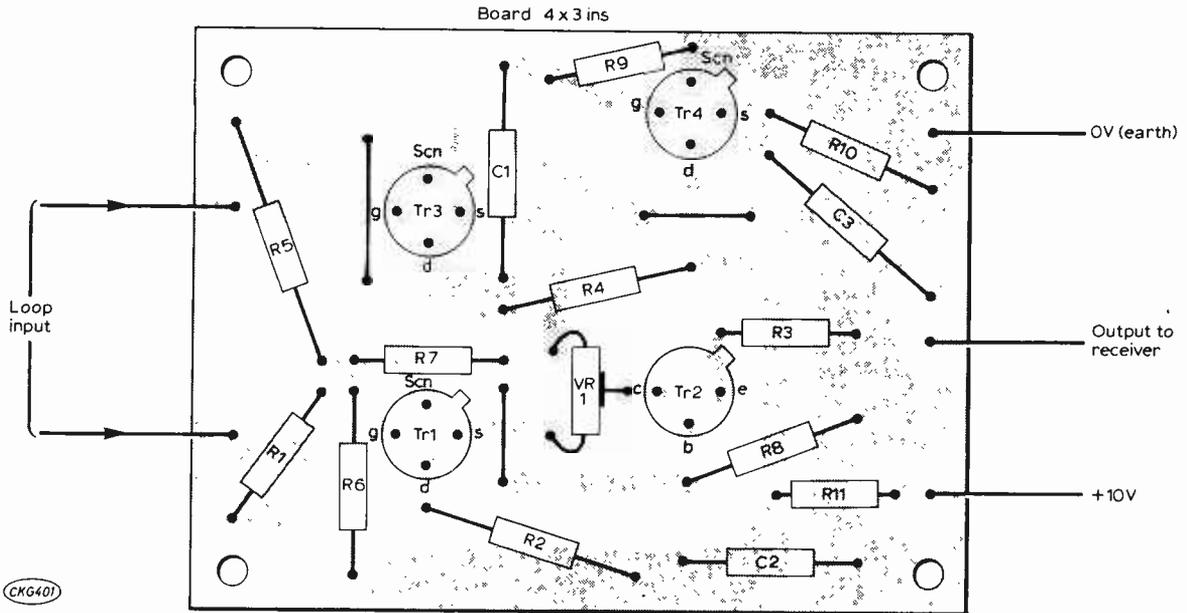



Fig. 8: Full size illustration of the printed circuit board, from the copper side. Small holes are drilled for component leads and the components mounted from the other side of the board.

circuit of Fig. 7 to select two 2N3823 transistors giving a similar voltage drop across the 1k $\Omega$  resistor in the test circuit. The balanced amplifier itself will tend to level out small differences between the transistors.

Transistor Tr4 acts as a source follower and is used to match the output from Tr3 into the low impedance of the cable and the receiver input circuit. Capacitive coupling is used to the output so that if the cable is accidentally short circuited the transistor Tr4 in the output stage will not be destroyed.
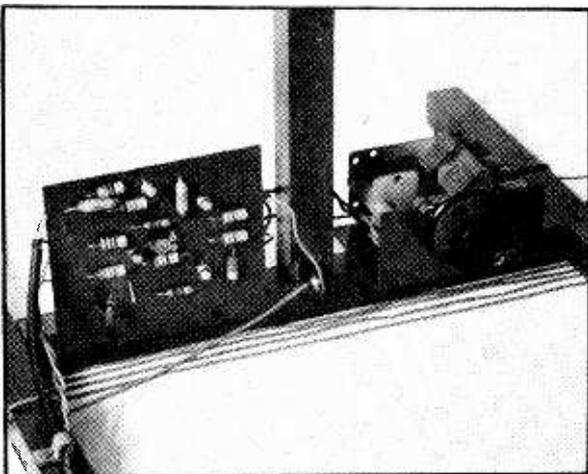
## CONSTRUCTION

It is convenient to build the amplifier on a small circuit board and to mount it close to the tuning capacitor on the main loop frame. A suggested layout for a printed circuit board for the amplifier



Close-up of the matching amplifier and loop tuning capacitor.

is given in Fig. 8. As an alternative the amplifier may be built on a piece of Veroboard. It should be noted that the screen leads of the 2N3823 transistors are connected to earth.

To test the aerial system the input amplifier stage should first of all be balanced. Connect a meter between the drains of transistors Tr1 and Tr3 and adjust the preset resistor VR1 until the voltage is zero. The two transistors will now be drawing equal currents.

Tune in a fairly strong signal from a known direction and rotate the aerial to obtain maximum pick up. At this point the loop should be tuned to resonance by means of the tuning capacitor as indicated by a further increase of signal when resonance is reached.

If the aerial is now rotated so that it is roughly broadside on to the direction of the station being heard a point should be found where the signal falls to a low level. A further small adjustment of VR1 may enable the signal to be reduced even lower.

## THE LOOP

The loop aerial used by the writer has 12 turns on a 24in. square frame. To reduce self-capacitance and give more turns for the same inductance the turns are spaced  $\frac{3}{8}$ in. apart. For the winding 14/0-0076 p.v.c. covered flexible wire is used. Tuning is by a 365pF air spaced variable capacitor across the ends of the loop winding.

Signal pick-up for this loop with its amplifier was found to be some 20dB up on the signal from a 30ft. outdoor wire aerial. Using a Lafayette HE30 receiver the signal reading on the 'S' meter varied from S9+60dB at the maximum pick up point to about S3 when the loop was rotated to the null position. The null point itself is sharp and extends over perhaps only two or three degrees. ■

# LETTERS

The Editor does not necessarily endorse the views expressed by correspondents

## "Mobile" dog sledge

In the February 1973 issue of *Practical Wireless* on page 890 you have a little note about working amateur radio from a dog sledge, stating that this might have been the world's first QSO from a dog sledge mobile installation. I would like to point out to you that there have been a number of radio amateur contacts from dog sledges over the past years. My first contact from a dog sledge installation was made in 1938 and I am quite sure that that was not the first one in the world.

The UK expedition which some years ago tried to reach the North Pole from Alaska also carried amateur radio equipment and had a number of contacts with the outside world. A Norwegian expedition which also some years ago tried to reach the Pole from the northern part of Greenland had practically all their contacts with the outside world made by amateur radio. Both these expeditions relied on dog sledges for their transportation.

In Norway and no doubt also in other countries with similar snow conditions amateur operations from dog sledges are not infrequent, and I myself have done it many times. I thought you might be interested in knowing this. **Lars R. Heyerdahl**, LA6A. (*Oslo 2, Norway*).

## Don't get knotted!

A serious error was made by somebody when he knotted the mains input cable, as illustrated and described in the text on the battery eliminator (on pages 920 and 921).

This can be very dangerous and is specifically outlawed by the Institute of Electrical Engineers in their published regulations.

If a cable is rapidly bent from a straight to a highly twisted configuration, as often occurs when an item is knotted and the knot pulled tight rapidly, the core material may suffer from local fatigue causing cracking of the material. The cracking acts as a resistance to the current flowing through the appliances, hence

local heating occurs.

The error, though dangerous is so common that M. Wallis could be excused it, provided the suggested warning is printed.

I would suggest that one of the plastic cable clamps, to secure mains leads, should be used. **S. A. East**, (*Enfield, Middtsex*).

## Midget radio phones

Over the Christmas holiday I assembled the *Practical Wireless* midget radio, lashed it to the head-band of some wartime crystal 'phones and got good listening for radios 2 and 4 and others between.

The hospital wards being quietish, I set off on some market research; men and women patients listened and all said that such lead-less headphones would be much appreciated, since they currently roll about and pull out the lead, and also cannot use 'phones when sitting out in the middle of the ward. They need to be lighter than my prototype, perhaps built onto a stethophone; and as not a few are hard of hearing, a bit more volume is needed. If we want Radio Humberside or television sound (the ward set provides vision only) we should need something more sophisticated I suppose. Also an experienced Charge Nurse said if 'phones are not on leads I shall need to put them on chains!

Incidentally, when walking home across the common in the fog the wireless 'phones directionality helps personal alignment!—**Dr. H. F. Barnard**, Pathologist *East Riding Group Laboratory, Westwood Hospital, Beverley, Yorks. HU17 8BU*.

## 25 years of transistors

I was especially interested in Mr. R. Collins's article, 25 Years of the Transistor, because he attributed the research and development that led to it to the Bell Company's need for a substitute for the valve in the telephone service, in the 1940's.

I think that there must have been a lot that went before because men were looking for a substitute for the valve as early as

1920, and soon after, in the "Amateur Wireless" of those days, an account was published of a Russian scientist who was experimenting in making crystals perform all the functions of valves.

I remember this well because, as a schoolboy, I put this down as my own scientific basis for an application for an Experimenter's Licence.

Unfortunately, I went to New Zealand afterwards, and lost touch with radio, but I wonder if any other reader can recall what, if any further developments there were in those experiments.—**John Pinches** (*London, N.W.7*).

[A semiconductor substitute for the valve is now in production. It has improved characteristics and longer life and uses field effect transistor principles. This device, called a FETRON, will be described in full in next month's *Practical Wireless*.]—Editor

## CQ! Gambia

We have been asked by the General Manager of the RSGB to publicise the following letter received by him:—

Whilst on a visit to West Africa recently, I was able to visit the transmitting station of Radio Gambia. I was asked to make an appeal to British S. W. listeners to report to them any reception of Radio Gambia in Britain.

The point is that they have received reports and QSL cards from Australia and America, but would very much like to hear from any British listener. I understand that the transmissions are as follows:—

Radio Gambia, 4.82MHz in the 60metre short wave band.

They tell me the best time for a reception would be between 10.30 p.m. and 11.30 p.m. **George Wallace, M.P.** (*House of Commons*).

## DID YOU KNOW . . .

. . . a subscription to *P.W.* for one year costs £2.65 to any part of the world . . .

V.A.T. WILL NOT BE CHARGED IF YOU POST YOUR ORDER BY 31.3.73

**BSR LATEST SUPERSLIM**

**STEREO AND MONO**  
Plays 12", 10" or 7" records.  
Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250v.  
Size 13 1/2 x 1 1/2 in.  
Above motor board 3 1/2 in.  
Below motor board 2 1/2 in.  
With STEREO and MONO XTAL MONO-COMPATIBLE  
Plays all records.



£8.75 Post 25p.  
£7.75 Post 25p.

**BSR JUNIOR**

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono cartridge.  
£4.50 Post 25p.



**E.M.I. WOOFER AND TWEETER KIT £5.75**

Available separately Post 25p  
Wooler £4.25, Tweeter £1.90.  
Comprising a fine example of a Woofer 10 1/2 x 8 in. with a massive Ceramic Magnet, 4400 Gauss, 13,000 lines. Aluminium Cone centre to improve mid and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.  
Impedance Standard..... 8 ohms  
Maximum Power..... 12 watts  
Useful Response..... 35 to 18,000 cps  
Bass Resonance..... 45 cps  
SUITABLE ENCLOSURE 20 x 13 x 9 in. £9 POST 25p  
MODERN DESIGN TEAK WOOD FINISH



**SPECIAL OFFER SMITH'S CLOCKWORK 15 AMP TIME SWITCH**

Single pole two-way.  
Maker's last list price £4.50.  
Brand new and fully guaranteed.  
Surface mounting with fixing screws.  
Will replace existing wall switch to give home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes or 0 to 8 hours.  
OUR PRICE £1.50, P. & P. 15p or £3 pair Post Free. (Please state type when ordering.)



**WEYRARD P50—TRANSISTOR COILS**

RA2W Ferrite Aerial... 72p	Spare Cores..... 3p
Ons. P50/1AC..... 38p	Driver Trans. LEDPA 58p
1 P. P50/2CC 470 kc/s. 36p	Printed Circuit, P50A1 58p
3rd I.P. P50/3CC..... 38p	J.B. Tuning Gang..... 65p
P51/1 or P51/2..... 36p	Werrad Booklet..... 10p
P50/3V..... 36p	OPT1..... 58p
Mullard Ferrite Rod 8 x 1/2 in. 20p, 6 x 1/2 in. 20p.	

**VOLUME CONTROLS**

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or L.N. 1/8, 1/4, 1/2, D.F. 25p.  
STEREO 1/8 55p, D.F. 75p.  
Edge 5K.S.P. Transistor 25p

80 Ohm Coax 4p. yd.  
BRITISH AERIALITE AERAXIAL-AIR SPACED  
40 yd. £1.40; 60 yd. 22p.  
FRINGE LOW LOSS  
Ideal 825 & colour 10p yd.

**8in & 10in ELAC HI-FI SPEAKERS**

Dual cone plasticised roll around. Large ceramic magnet. 50-16,000 cps.  
Bass resonance 55 cps.  
8 ohm coil.  
8 in. 10 watt. £3.75 Post 25p  
10 in. 12 watt music power.



**E.M.I. 13 1/2 x 8in. SPEAKER SALE!**

With twin tweeters and crossover, 10 watt. £3.95  
State 3 or 8 or 15 ohm. (As illustrated) Post 25p  
With flared tweeter cone and ceramic magnet, 10 watts. £2.25  
Bass res. 45-60 cps.  
Flux 10,000 gauss.  
State 3 or 8 or 15 ohm. Post 25p  
**TEAK CABINET £5**



**BRITISH MADE STEREO MULTIPLEX DECODER**

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2 1/2 x 6 1/2 x 1 in. Pre-assembled. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100V input. Full instructions for any FM Tuner. Some technical experience £6.50 Post 50p



BLANK ALUMINIUM CHASSIS 16 s.w.g. 2in. sides. 6 x 4in 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 99p; 11 x 5in. 50p; 16 x 10in. 51p.  
ALUMINIUM PANELS 18 s.w.g. 8 x 4in. 9p; 8 x 6in. 15p; 14 x 3in. 19p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 8in. 28p; 16 x 6in. 28p; 14 x 9in. 34p; 12 x 12in. 40p; 16 x 10in. 50p

**WHARFEDALE SUPER 10" HI-FI SPEAKER**

15 watt 4 to 8 ohms. Response 20 to 12 Kc/s. Bass resonance 42 cps. Massive Ceramic Magnet. Deep fabric cone surround. Cast alloy frame. Weight 5 lbs. Value £10.50

OUR PRICE £5.50 Post 25p

**THE FAMOUS WHARFEDALE SOUND!**

R.C.S. STABILISED POWER PACK KITS  
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240v. AC. Output voltages available 6 or 8 or 12 or 15 or 18 or 20v. DC at 100mA or less.  
PLEASE STATE VOLTAGE REQUIRED. £2 Post  
Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2 in. FREE

**GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE**

Ideal for Mike, Tape, P.U. Guitar. Can be used with Battery £-12v or H.T. Line 200-300V D.C. operation. Size 1 1/2" x 1 1/2" x 1 1/2". Response 25 c.p.s. to 25 Kc/s. 20db gain. For use with valve or transistor equipment. £2 Post  
Full instructions supplied. Details S.A.E. 10p

**NEW TUBULAR ELECTROLYTICS CAN TYPES**

2/350V .. 14p	250/25V .. 14p	50 - 50/350V .. 35p
4/350V .. 14p	500/25V .. 20p	60 - 100/350V .. 58p
8/450V .. 14p	1000/25V .. 35p	32 + 32/250V .. 18p
16/450V 15p	1000/50V .. 47p	32 + 32/450V .. 33p
32/450V 20p	8 + 8/450V .. 18p	350 + 50/325V .. 50p
25/25V .. 10p	8 + 16/450V .. 30p	32 - 32 + 32/350V .. 45p
50/50V 10p	16 + 16/450V 25p	100 + 50 - 50/350V 48p
100/25V 10p	32 + 32/350V 25p	

**LOW VOLTAGE ELECTROLYTICS**

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.  
500mF. 12V. 15p; 25V. 20p; 50V. 30p.  
1000mF. 12V. 17p; 25V. 35p; 50V. 47p; 100V. 70p.  
2000mF. 8V. 25p; 25V. 42p; 50V. 57p.  
2500mF. 50V. 62p; 3000mF. 25V. 47p; 50V. 65p.  
5000mF. 6V. 25p; 12V. 42p; 25V. 73p; 35V. 85p; 50V. 95p.

CERAMIC 1p to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p  
PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p.  
500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p.  
SILVER MICA. Close tolerance 1%, 2.2-500pF 8p; 500-2.20p 1p; 2.700-5.000pF 20p; 6.800pF-0.01mF 30p; each.  
TWIN GANG. +0-0" 200pF + 175pF. 85p; Slow motion drive 365 + 365 with 25 + 25pF. 50p; 500pF standard. 45p; Single gang 600pF. 75p; small 3-rang 500pF. £1.40.  
SHORT WAVE. SINGLE. 100p 30p; 25pF 50p; 50pF 55p.  
NEON PANEL INDICATORS. 250V AC/DC Amber 20p.  
RESISTORS. 1 w. 1/4 w. 1/2 w. 2 w. 5p 10 ohms to 10 meg.  
H.I. STABILITY. 1 w. 2 w. 10 ohms to 6 meg. 10p.  
Ditto 4w. Preferred values 10 ohms to 10 meg. 4p.  
WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each; 2 watt, 1 ohm to 8-2 ohms 10p.  
TAPE OSCILLATOR COIL. Valve Type 35p.

**GARRARD DECCA DISCO DECK**

£18.50 Post 25p  
Single Play Stereo Mono  
Deram transcription head and arm. Four speeds. 10 1/2 in. turntable. Anti-rumble filter. Best construction. Laboratory motor.



**METAL PLINTH & PLASTIC COVER**

Cut out for most Garrard or B.S.R. Most will play with cover in position 12 1/2 x 14 1/2 in. Covered in black leatherette. Post 35p

£4.50

**ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH-AT SAME PRICE**

**MAINS TRANSFORMERS ALL POST 25p each**

250-0-250 80 mA. 6.3 v. 4 amp. £1.50  
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.50  
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3.00  
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. £3.25  
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p  
HEATER TRANS. 6.3 v. 3 a. £1.00  
GENERAL PURPOSE LOW VOLTAGE, Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2.25  
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.25  
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.25  
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.75  
3 amp. 3, 4, 5, 6, 8, 10, 12, 15, £1.00; Ditto 5 amp. £1.20  
3 amp. 3, 5, 8, 10, 13 and 5-0-5 v. £1.30; Ditto 5 amp. £1.50  
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 150w. £2.25; 500w. £2.25; 750w. £1.00; 1000w. £1.20  
CHARGER TRANSFORMERS. Input 200/250 v. for 6 or 12 v. 1 1/2 amp. £1.50; 2 amp. £1.80; 4 amp. £2.50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 5 amp. 85p.  
BATTERY CHARGERS. 1A. £2; 3A. £3; 4A. £4.  
LUCAS 2D8500 Full wave Bridge 70V 5 amp 85p.

**FACTORY ACT! MAINS ISOLATING TRANSFORMER**

Primary 0-110-240 v. Secondary 0-240 v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make. Value £19. OUR SPECIAL PRICE £10 50p.  
Can be used as 800 watt Auto Transformer 240-110v.

**ALL MODELS "BAKER SPEAKERS" IN STOCK**

Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free

**BAKER 12in. MAJOR £9**

P. & p. 25p  
30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms  
Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. P. & p. 25p. £11.50

**BAKER "BIG-SOUND" SPEAKERS**

'Group 25'	'Group 35'	'Group 50'
12 inch £8	12 inch £9	15 inch £20
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	3 or 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS  
For 12in. or 10in. dia. speaker 20 - 13 - 9in. £9. Post 25p  
For 13 x 8in. or 8in. speaker 16 - 10 - 9in. £5. Post 25p  
For 10 - 6in. or 6in. speaker 16 - 8 - 6in. £4. Post 25p  
LOUDSPEAKER CABINET WADDING 15in. wide, 15p ft.

**GOODMANS 6 1/2 in. HI-FI WOOFER £4**

8 ohm, 10 watt. Large ceramic magnet. Special Cambria cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, Hi-Fi Enclosures Systems, etc.  
8in. STANDARD CONE 12W. £4.50, post 25p.

**ELAC CONE TWEETER**

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 2 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. £1.90 Post 10p

**SPEAKER COVERING MATERIALS. Samples Larre S.A.E.**

Horn Tweeters 2-16kc/s. 10W 8 ohm or 15 ohm £1.95.  
De Luxe Horn Tweeters 2-18 Kc/s. 15W. 15 ohm £3.  
TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p.  
LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in. £1.25; 8in. £1.50; 9 x 5in. £1.60; 8in. £1.75; 10 x 6in. £1.90; 10in. £2.00.  
SPECIAL OFFER: 30 ohm 2 1/2 in.; 2 in.; 35 ohm 2 in.; 3 in. 25 ohm 2 1/2 in. dia.; 3 in. dia.; 5 in. dia.; 5 in. dia.; 15 ohm 3 in. dia.; 6 x 4 in.; 7 x 4 in.; 8 x 5 in. £1 EACH  
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4 watt; 10in. 5 watt; 12in. 6 watt 3 or 8 or 15 ohm models £2.20 each Post 15p  
VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms. 80p.

**BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER**

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free



**BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9v. £4.95**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £5.95

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £14.85

BARGAIN FM TUNER as above less cabinet. £9.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor £4.50  
Push-Pull Ready built, with volume control. 9v.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. Line 18p. OUTLET BOXES, SURFACE OR FLUSH. 25p.  
BALANCED TWIN RIBBON FEEDER 300 ohms 5p yard. JACK SOCKET Std. open-circuit 14p. closed-circuit 23p. Chrome Lead Socket 45p. Phono Plug 5p. Phono Socket 5p. JACK PLUGS Std. Chrome 15p; 3-6mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 9p; CANS 9p.

**E.M.I. TAPE MOTORS**

Post 25p  
120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. £1.25  
Size 3 1/2 x 2 1/2 in. (illustrated).  
**E.M.I. GRAM MOTORS**  
120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Spindle 1/2 x 1/2 in. Size. Post 25p. 75p

**337 WHITEHORSE ROAD, CROYDON**

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)  
Buses 50, 68, 159 Rail Selhurst. Tel. 01-684-1665.

**RADIO COMPONENT SPECIALISTS**

Minimum post 15p. Radio Books & Components Lists 10p. (Export: Remit cash and extra postage.)

# STEPHENS ELECTRONICS

DEPT E1  
165 BICESTER RD.,  
AYLESBURY BUCKS

EXPORT ENQUIRIES WELCOMED

UNDER NEW MANAGEMENT  
MR. BRIAN RIXON, B.Sc.

SEND LARGE SAE FOR LISTS

TERMS: Cash, Cheque or P.O. with order only.

0A2	0-40	6AR6	0-85	6F5	0-75	6Y6G	0-80
0A3	0-48	6AR11	1-25	6F6G	0-45	7Y4	0-75
0B3	0-40	6AR5	0-50	6F7	1-50	9B76	0-70
0C3	0-40	6AR7	0-88	6F13	0-60	10C2	0-60
0D3	0-40	6AU6	0-30	6F14	0-70	10D1	0-65
1B3GT	0-40	6AV6	0-40	6F15	0-65	10D2	0-55
1L4	0-25	6AW8A	0-65	6F18	0-50	10F1	0-75
1R4	0-50	6BA6	0-28	6F23	0-90	10F9	0-65
1R5	0-45	6BE6	0-32	6F24	0-80	10F18	0-60
1B4	0-40	6BR6	0-55	6F25	1-00	10L1	0-60
1B5	0-30	6BH6	0-75	6F28	0-35	10LD11	0-70
1T4	0-30	6BJ6	0-55	6F28	0-70	10P13	0-75
1U4	0-40	6BK7A	0-75	6GK6	0-60	12AB5	0-70
1U5	0-75	6BN5	0-43	6J4	0-80	12AC6	0-80
1V2	0-55	6BN6	0-80	6J5GT	0-40	12AD6	0-80
1X2B	0-55	6BQ6	0-25	6J6	0-30	12AE6	0-80
2D21	0-40	6BR8	0-75	6J7	0-45	12AL5	0-55
3A4	0-45	6B7	1-35	6K411	0-80	12AQ6	0-50
3A5	0-75	6BW6	0-90	6K6GT	0-75	12AT7	0-40
3B1	3-50	6BW7	0-90	6K8G	0-45	12AU6	0-45
3B4	0-40	6BX6	0-25	6K25	0-75	12A7U	0-38
3V4	0-65	6BZ6	0-45	6L6GT	0-55	12AV6	0-45
FR4GY	0-75	6C4	0-55	6L8V7	0-70	12AV7	0-70
5U4G	0-40	6CSGT	0-55	6L18	0-50	12AX7	0-33
5V4G	0-50	6CB6	0-40	6LD20	0-50	12AY7	0-75
5Y3GT	0-45	6CD6GA	0-40	6N7GT	0-55	12BA4	0-65
5Z3	0-75	6CG7	1-30	6P25	1-50	12BA6	0-45
5Z4G	0-45	6CG7	0-60	6P28	0-65	12BA7	0-50
630L2	0-90	6CH0	0-60	6Q7	0-50	12BE6	0-50
6A4	0-45	6CL6	0-80	6R7	0-45	12BH7	0-50
6AF4A	0-60	6CU6	0-90	6R8G	0-45	12BY7	0-85
6AG5	0-25	6CW4	0-70	6SK7	0-50	12K5	1-00
6AG7	0-45	6CY5	0-50	6SL7GT	0-50	12K7GT	0-50
6AH0	0-60	6CV7	0-75	6N7GT	0-45	12K7GT	0-45
6AJ8	0-30	6D3	0-55	6R8Q7	0-50	12SR7	0-50
6AK5	0-40	6D3C	0-30	6R7	0-50	20D1	0-60
6AS6	0-60	6DK6	0-80	6R78	0-35	20L1	1-10
6AL3	0-43	6DQ6B	0-75	6U4GT	0-70	20P1	0-50
6AL5	0-22	6D8A	1-25	6U5G	0-75	20P4	1-10
6AM5	0-40	6EA8	0-65	6U8A	0-48	20P5	1-20
6AM6	0-37	6EH7	0-30	6V6GT	0-45	25C5	0-80
6AQ5	0-42	6E7	0-35	6X4	0-40	25LG0T	0-50
6AQ6	0-70	6EW6	0-70	6X5GT	0-45	25Z4G	0-35
6AR5	0-55	6F1	0-75	6X8	0-65	25Z6GT	0-75


QUALITY VALVES  
GUARANTEED. SAME  
DAY DESPATCH  
Tel: Aylesbury 84619

30A5	0-60	50CD6G120	DL96	0-55	ECC88	0-40	
30AE3	0-40	50EH5	0-65	DM70	0-60	ECC89	0-50
30C1	0-30	50L6GT	0-50	DM160	0-65	EC91	0-30
30C15	1-00	85A2	0-55	DY51	0-55	ECC189	0-65
30C17	1-10	90A6	2-40	DY86	0-35	ECC807	1-00
30C18	0-90	90AV	2-50	DY87	0-38	ECCF80	0-35
30F5	1-00	90C1	2-75	EB8CC	0-70	ECCF82	0-35
30FL1	0-80	90CV	0-40	E180F	1-00	ECCF804	1-65
30FL12	1-10	807	0-50	E181F	0-90	ECC42	0-75
30FL14	0-90	813	4-00	EAC800	0-38	ECH81	0-30
30L7	0-40	868A	0-85	EAF42	0-60	ECH83	0-45
30L15	0-95	5642	0-70	EBC33	0-60	ECH84	0-45
30L17	0-95	6080	1-75	EBC41	0-65	ECL80	0-50
30P12	1-00	6146	1-60	EBC81	0-33	ECL81	0-50
30P19	0-95	6146B	2-50	EBC82	0-35	EM84	0-35
30PL1	0-95	6380	1-25	EB38	0-45	ECL83	0-70
30PL12	1-10	6287	0-60	EB78	0-30	ECL84	0-55
30PL14	1-25	7199	0-85	EB131	1-50	ECL85	0-55
35A3	0-60	7360	2-20	EC53	0-50	ECL86	0-40
35A5	0-75	7686	1-50	EC86	0-60	ECL800	
35B5	0-65	7896	1-50	EC88	0-60		2-20
35C5	0-60	A2293	2-20	EC90	0-35	EF37A	1-00
35D5	0-75	AZ1	0-60	EC92	0-45	EP40	0-50
35LGT	0-75	AZ21	0-55	EC93	0-60	EP41	0-65
35W4	0-40	CB11	0-90	ECC35	1-00	EP42	0-70
35Z3	0-75	CB131	1-00	ECC40	0-70	EP80	0-30
35Z40	0-40	CV31	0-50	ECC81	0-40	EP85	0-35
36Z5GT	0-70	DAF96	0-50	ECC82	0-38	EP86	0-30
60A5	0-80	DF96	0-50	ECC83	0-38	EP89	0-28
60B5	0-70	DK92	0-70	ECC84	0-30	EP91	0-37
50C5	0-60	DK96	0-60	ECC85	0-40	EP92	0-35

EF95	0-40	GZ31	0-40	FF818	1-00	1301	0-55
EP7	0-65	GZ32	0-50	FF820	0-85	1403	0-70
EP8	0-75	GZ33	0-75	PL33	0-40	1404	0-70
EF183	0-80	GZ34	0-60	PL36	0-55	1401	0-80
EF184	0-35	HABCO		PLA1	0-50	UABCO	
EP804	1-25		0-55	PLA2	0-45		0-40
EK90	0-32	HK80	0-50	PLB3	0-45	UAF41	0-70
EL33	1-50	KT66	2-35	PLB4	0-40	UAF42	0-60
EL34	0-50	KT68	2-25	PLB6	0-95	UAF43	0-65
EL36	0-50	N78	1-60	PL504	0-75	UAF44	0-55
EL37	1-70	PABCO040		PL508	0-90	UBC81	0-45
EL41	0-75	PC86	0-60	PL509	1-10	UBF80	0-40
EL81	0-55	PC88	0-60	PL801	1-00	UBF89	0-40
EL83	0-50	PC92	0-05	PL802	0-85	UBL1	0-70
EL84	0-25	PC97	0-50	PM84	0-70	UBL21	0-70
EL85	0-43	PC900	0-48	PY31	0-35	UCF42	0-60
EL86	0-40	PC884	0-40	PY33	0-38	UCF85	0-45
EL90	0-42	PC885	0-40	PY80	0-40	UCF90	0-70
EL95	0-35	PC888	0-55	PY81	0-30	UCH21	0-60
EL821	0-60	PC889	0-55	PY82	0-35	UCH42	0-70
EL822	1-40	PCF189	0-60	PY83	0-38	UCH81	0-40
ELL80	0-75	PC8085	0-95	PY88	0-40	UCH81	0-40
EM34	1-00	PC8086	0-95	PY800	0-47	UCL82	0-35
EM71	0-80	PCF80	0-30	PY801	0-40	UCL83	0-65
EM80	0-45	PCF82	0-35	PZ30	0-38	UP9	0-65
EM81	0-60	PCF84	0-60	QQV02-6		UP11	0-60
EM83	0-50	PCF86	0-80		2-25	UP41	0-65
EM84	0-35	PCF87	1-10	QQV03-10		UP42	0-65
EM85	1-00	PCF801	0-50		1-25	UP43	0-65
EM87	0-45	PCF802	0-50	QQV03-20A		UCL82	0-35
EN91	0-40	PCF805	0-90		5-25	UP85	0-40
EY61	0-40	PCF806	0-75	TT21	3-40	UP89	0-40
EY80	0-75	PCF808	0-90	TT22	3-50	UL41	0-65
EY81	0-40	PCF200	0-70	U18/20	0-75	UL64	0-43
EY83	0-55	PC81	0-50	U25	0-85	UM84	0-30
EY86	0-40	PC82	0-35	U26	0-85	UTIN	0-50
EY87	0-45	PC83	0-65	U31	0-70	UT1	1-00
EY88	0-43	PC84	0-45	U37	0-50	UY41	0-48
EZ40	0-50	PC86	0-45	U52	0-40	UY82	0-60
EZ41	0-75	PC88	1-25	U76	0-40	UY85	0-40
EZ80	0-28	PC800	1-10	U78	0-40	WZ29	0-75
EZ81	0-29	PC801	0-95	U91	0-75	Y63	0-75
GT1C	0-90	PC805	0-60	U201	0-50	Z8031	1-35
G5Y01	0-70	PD90	1-30	U281	0-55		
GZ30	0-45	PF86	0-70	U282	0-55		

SINCLAIR EQUIPMENT

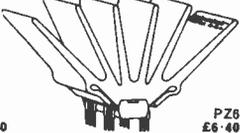IC12 £2-00  
Z50 £4-25  
PZ5 £3-97  
Z30 £3-50  
Project 60 tuner £16-80  
AFU £4-50  
stereo 60 £7-80



KITS OF PARTS FOR THE IC12  
Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version £1-30. Stereo version with balance control £3-00.


POWER UNITS FOR THE IC12  
A set of components to construct a 30V, 0-5 Amp power supply £2-27. Also suitable Sinclair PZ5 fully constructed £3-97.

PROJECT 60 KIT £2-50  
Our extremely popular kit contains the extra capacitors, DIN plugs and sockets, cables and fuse holder needed to complete Project 60.

S-DECS AND T-DECS  
S-DECS £1-44  
T-DECS £2-88  
µ-DEC A £3-00  
16 diil IC carriers £1-25



SINCLAIR EXECUTIVE CALCULATOR

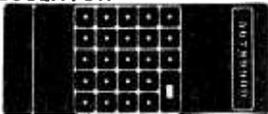

OUR PRICE ONLY £69 (List Price £79).  
SWANLEY ELECTRONICS  
32 Goldsel Road, Swanley, Kent  
Mail order only. Postage 10p per item. Lists 10p. After April 1st please add 10% extra for VAT.

U.H.F. T.V. AERIALS  
SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION


All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS  
7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75.  
WALL MOUNTING c/w WALL ARM & BRACKET  
7 element 3-25, 11 element 3-75, 14 element 4-25, 18 element 4-75. CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT. 7 element 4-00, 11 element 4-50, 14 element 4-75, 18 element 5-25. MAST MOUNTING arrays only. 7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9np yd. KING TELEBOOSTERS from 3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

BBC—ITV—FM AERIALS  
BBC (band 1) Wall S/D 2-00. LOFT inverted 'T' 1-25. EXTERNAL 'H' array only 3-00.  
ITV (band 3) 5 element loft array 2-50.  
7 element 3-00. COMBINED BBC—ITV, loft 1+5 2-75, 1+7 3-50. WALL & CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from 3-75. COMBINED U.H.F.—V.H.F. aerials 1+5+9 4-00, 1+5+14 4-50, 1+7+14 5-00. F.M. RADIO loft S/D 1-00 3 element 3-25, 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

CALLERS WELCOMED  
OPEN ALL DAY SATURDAY  
K.V.A. ELECTRONICS  
40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY  
Telephone 01-648 4884

RADIO BARGAINS

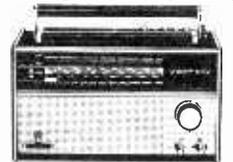

- Grundig Mariner TR865 £35-00
- Grundig Elite Boy 500 bat/mains £27-00
- Grundig Melody Boy 500 bat/mains £27-00
- Grundig Melody Boy 1000 £41-00
- Grundig Yacht Boy 210 £34-50
- Grundig Satellit 1000 £125-00
- Aiwa AR158 6w.b. (inc. air) £31-00
- Koyo KTR 1664 8w.b. £47-50
- Koyo KTR1661 8w.b. £40-25
- Koyo KTR1770 11w.b. £69-50
- ITT/KB Golf Preset £22-50
- ITT/KB Touring Int. Marine £45-00
- Toshiba IC70 £16-50
- Grundig RF430 £26-50

FREE With each set "Guide to Broadcasting Stations" (160 pages)

WILMSLOW  
AUDIO, Dept. PW,  
10 Swan St., Wilmslow,  
Cheshire, SK9 1HF

# ON THE SHORT WAVES

## THE AMATEUR BANDS David Gibson, G3JDG

Frequencies in kHz • Times in GMT

**W**E are running out of frequencies. I know we have certain "Amateur Bands," but some of these are on a shared basis, i.e. we can only use them provided we are not a nuisance to other non-amateur stations using the band.

Many will remember when 40 metres was 300kHz wide—it's now 100kHz wide and intruders still try to drive us off this remaining r.f. island. The only real answer to amateur radio survival is intelligent activity. With a band full of active enthusiasts, intruders will think twice about taking on our "QRM". Those that do would find a few hundred amateurs from dozens of different locations and countries, all suddenly doing tests on that particular frequency. Whether amateur radio loses any more of its r.f. spectrum or indeed a complete amateur band, is entirely up to the people who practise and enjoy our hobby.

A topical example is 4 metres or 70MHz. This band is greedily looked at by many people (non-amateurs) who would like to use the small piece of 4 metres which we still have. Activity on 70MHz is very low from an amateur's point of view, and if activity is not increased, then the authorities may well award the entire 4 metre band to "other services". The argument could well be (and it is a valid one) that since there is so very little amateur activity on 4 metres, then you do not really need that band. So how about some logs for 4 metres?

A 4 metre converter is not a difficult thing to build and would offer a very useful intermediate step in construction practice between the h.f. bands and 2 metres. Constructing a converter for 70MHz is not difficult but needs a little more care than units constructed for the lower frequencies. One excellent idea would be to use 70MHz as a local net band, which would avoid the interference suffered on 160 metres top band, would keep us clear of Loran, which plagues 160, and would increase the level of 4 metre activity dramatically. We have to start somewhere or we could well lose this band. So, 4 metre enthusiasts forward. Let's hear what you hear.

A letter from **Paul Petty** (Canterbury) tells of a useful information service for European stations which transmits on 80 metres between 2100 and 2200 GMT. There is a controller station which is changed daily. Monday's controller is DA1LA. On Wednesdays it is DK8FZ. The purpose of the net is to assemble and disseminate information on DX stations, i.e. future skeds.

Top band enthusiasts will be delighted to hear that G3SZA has been heard on 160 metres in Australia by a VK3 station. Alas callsigns are still changing. MP4 stations have been heard using a new call sign—A4FA. When will we have some callsign stability? And why change from MP4M to A4FA?

Another strange change is that CT1 stations are to use the prefix CT4 during the CQWPX contest

this month. Why is not made clear. First class licence holders in Japan now have two-letter suffix calls and second class licensees will use a JM suffix followed by three letters.

Old hands will be pleased to hear VR6TC on again from Pitcairn Island, and DX enthusiasts who enjoy hearing/working island stations should listen for VQ9HCS who radiates on 15 metres in the afternoons from Aldabra Island.

**Robert Harpur** (Shenfield) tells of two VP8 stations located in South Georgia which can be heard some evenings between 14.125kHz and 14.130kHz. This page commonly informs of stations heard by other short wave listeners and amateurs. The gear is quoted, i.e. receivers, a.t.u. preselectors etc., in this way readers can gauge how their own performance is by direct comparison especially if the report is from someone using similar equipment. It has been suggested it would be nice to actually see some of these stations. Photographs of individual set ups would be of interest to others. Anyone got any really good, sharp photographs of the gear plus themselves. Think of the satisfaction of seeing your trusty old CR100 smiling back at you from the pages of *PW*.

**Peter Franklin** (Skegness) received a UNR30 receiver for Christmas and is busily spoiling the brute with a diet of 100ft. end fed. A preliminary listen on eighty metres brought forth a high level of G activity. Peter queries the call sign G4GJ heard testing a transmitter on 3.8MHz one afternoon. Will the real G4GJ please stand up?

Another eighty metre enthusiast is **Peter Reed** (Brighton) who is the proud possessor of an FTDX401 receiver which apparently has a Japtick UFP. Sorry Peter, I know of no ointment which can cure that. Perhaps you could scrape it off with a bent screw-driver. Peter's log for eighty reads; FL8OM, HS4AGM, 15FLN, JW9QH, M1C, M1I, VE1AIH, VE1IE, VS6DO, VQ9R, W1AA, W1KET, W2APU, W2PV, W3WJD, YA1AH, ZL4KE, ZS1MH, ZS3GH, 5X5N, 9G1DY, 9H1C, 9H5D, all on s.s.b.

**Stephen Mayer** (Poole) has a CR70A receiver fed with a 90ft. wire. This set up brought in stations from most European countries. From further afield; PY2ZAT, W4AG, W5QGZ, all on eighty metres.

Great rejoicing in South Yardley where **David Sharred** has found that his blood pressure and country score have increased in direct proportion to the arrival of a new CR150/2. This, together with sharp ears (no, he's not Mr. Spock) and a 140ft. end fed raised these on 3.8MHz; CT2BG, FP8CT, K1DQV, VE1ADV, VE3CDP/W9, VE7SV, W1CF, W4CC, W5SR, W5SW, WA9PRO, ZL3GS, 4X4UF, 5X5NK, 5X5XM, 9H1C.

**Logs, in alphabetical order please, to arrive by the fifteenth of the month to:**

*12 Cross Way, Harpenden, Herts.*

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE first topic for this month is that of aerial wire. In the February column I asked if anyone knew of a good source for aerial wire. The number of replies was very pleasing and I must apologise for not being able to answer them all personally.

In general, your answers seem to bear out my opinion that it is becoming more difficult to find supplies of good quality aerial wire. The wire which I have always used in the past is that manufactured by a firm called 'Aerialite'. This wire consists of seven strands of copper with very strong insulation which is ideal for the purpose.

Mr. A. E. Halladay informs me that this is still available from a shop called 'Al Radio Components' of 14 The Borough, Canterbury, Kent. The wire is available in lengths of 25, 50 or 75 feet and is very reasonably priced at 14p, 22½p and 29p respectively. A charge of 6p is made for post and packing.

Mr. David Porter writes to say that a firm called Chas. H. Young Ltd of 170-172 Corporation Street, Birmingham, B4 6UD sells Stranded 7/·029 and 32/0·2mm Insulated wire in 140 foot lengths for £1·87. This firm is also a good source for aerial insulators and dipole centre pieces.

Mr. A. A. Smith of Preston in Lancashire suggested the use of a particular type of G.P.O. Telephone wire. This consists of a single strand of steel wire which is covered with a film of copper and then a layer of insulation. It is usually supplied as a twin cable, similar to lighting flex, but this is easily split into two separate wires. The advantage of this wire is the superior strength of the steel core. No supplier is known but the wire should be available from Surplus Stores.

A preselector is basically an r.f. amplifier and, as such, it will improve the performance of almost any receiver. Many receivers do not have an r.f. amplifier stage, the first stage being the mixer and it is with these sets that the most significant improvement in performance will be obtained. If the receiver has one or more r.f. stages incorporated the improvement will not be so marked.

The preselector usually provides a gain of 30dB, which in simple terms is a gain of 32 times, this gain being very useful in the reception of weak signals.

It is worth noting that the most common source of lost efficiency in a receiving system is a mismatch between components of the system. The three common components are the aerial, the preselector and the receiver. In the simplest case of aerial and receiver it is essential to have a good match between the two. If a preselector is added there must be a good match between the aerial and the preselector and also between the preselector and receiver.

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

### READERS' LOGS

The first log comes from **Raymond Mowll**, who enquired about preselectors, his equipment is a Trio 9R59DS and 100 feet of wire. The lack of a pre-selector did not prevent him from hearing:

- 5047 *Togo*, French news and music at 2250.
- 7120 *Kiev*, with Mailbag programme at 0045.
- 7180 *BBC, Tebrau, Malaysia* relay at 1720.
- 9655 *R. Damascus, Syria*, in English at 2040.
- 11710 *RAE, Argentina* with music at 2330.
- 11955 *FEBA, Seychelles* in English at 1745.
- 15140 *R. Havana, Cuba*, commentary at 2100.
- 15375 *R. Nederland, Bonaire*, English at 1830.

**R. M. Witney** of Braintree has been active again with his Skywood CX-203 receiver and 110 foot long-wire hearing the following stations:

- 11730 *Radio Ceylon* at 0140.
- 11815 *Trans World Radio, Bonaire* at 0055.
- 15165 *Radio Denmark* at 2000.
- 15448 *Radio Nacional de Brazilia* in Spanish at 0225.

**Peter North** of Southport has sent in his first report to the column using his Heathkit RG-1 receiver and 24 foot long-wire to hear:

- 4979 *R. Rumbos, Venezuela* in Spanish at 0430.
- 4995 *R. Brazil Central* in Portuguese at 0030.
- 5075 *R. Sulatenza, Colombia*, Spanish at 0130.
- 9550 *RTB, Belgium* in English at 0050.
- 9730 *ETLF, Ethiopia* in English at 0400.
- 9745 *R. Baghdad, Iraq* in English at 1930.
- 11710 *RAE, Argentina* in English at 2300.
- 11720 *R. Nacional de Brazilia* in English at 2230.
- 11805 *R. Globo, Brazil* in Portuguese at 0030.
- 11860 *R. Canada International*, English at 2115.
- 11880 *R. Ankara, Turkey* in English at 2200.
- 11930 *WIBS, Grenada* in English at 2030.
- 11955 *FEBA, Seychelles* in English at 1730.
- 15300 *HCJB, Quito, Ecuador* in English at 1900.
- 15345 *R. Kuwait* in English at 0500.

Reports should arrive by the 15th of the month and be addressed to me at 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

### NEXT MONTH

## ON THE AIR

Our specialist team will present news, views, comment and of course **YOUR LOGS** on the Broadcast Bands (Short Wave and Medium Wave). The Amateur Bands (Short Wave) and

**A NEW COLUMN** specially devoted to

**VHF COMMUNICATION** for amateurs and broadcast stations.

One big regular monthly feature by Malcolm Connah, David Gibson and Charles Molloy.

# Build yourself a TRANSISTOR RADIO

## ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost

**£8-50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

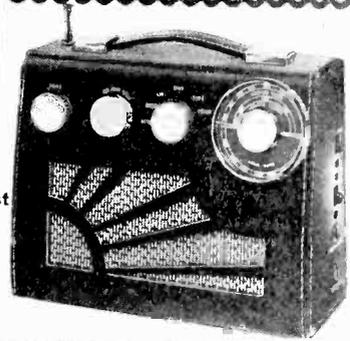

## ROAMER EIGHT Mk I


**NOW WITH VARIABLE TONE CONTROL**



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost **£6-98** P. P. & Ins. 45p.  
(Overseas P. & P. £1)


## ROAMER SEVEN MK IV

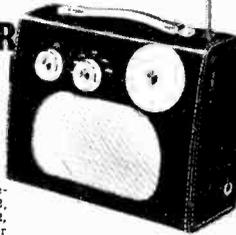

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£5-98** P. P. & Ins. 45p.  
(Overseas P. & P. £1)

## ROAMER SIX

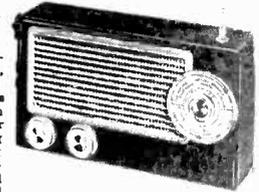

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler band plus an extra Medium wave band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—5 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Easy build plans and parts price list 25p (FREE with parts).

Total building costs **£3-98** P. P. & Ins. 30p  
(Overseas P. & P. £1)

## POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5½ x 1½ x 3¼in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-29** P. P. & Ins. 23p  
(Overseas P. & P. 63p)

## TRANSONA FIVE




**5 TRANSISTORS AND 2 DIODES**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-50** P. P. & Ins. 24p  
(Overseas P. & P. 63p)

## TRANS EIGHT

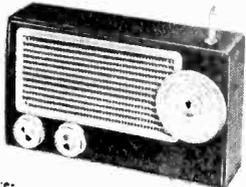

**8 TRANSISTORS and 3 DIODES**

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£4-48** P. P. & Ins. 32p  
(Overseas P. & P. £1)

## NEW! "EDU-KIT"

**BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

**COMPONENTS INCLUDE:**  
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

Parts price list and easy build plans 25p (FREE with parts).  
All parts including **£5-50** P. P. & Ins. 32p  
Case and Plans

(Overseas P. & P. £1)

**FULL AFTER SALES SERVICE**

• Callers side entrance "Lavells" Shop  
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367

I enclose £ \_\_\_\_\_ please send items marked.

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>


Parts price list and plans for

Name \_\_\_\_\_

Address \_\_\_\_\_

PW52

# GOING BACK...

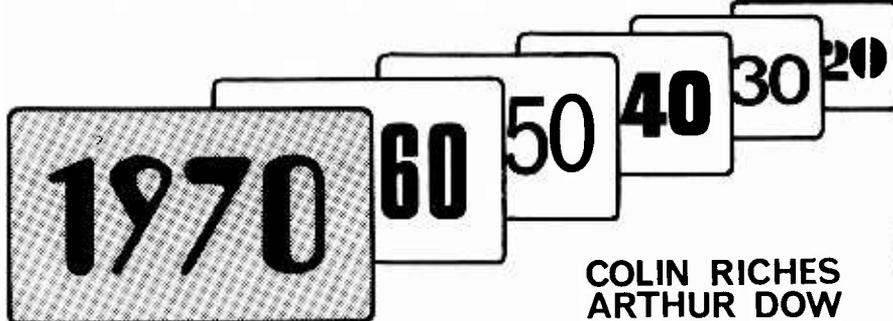

COLIN RICHES  
ARTHUR DOW



**T**HE other month we received a letter from one of our New Zealand readers who informed us that he is an ardent vintage radio equipment collector. He told us that he decided one day to cart all his gear out on to his back lawn (it's baking hot over there at this time of the year) and take some pictures for us to show in the Going Back column.

The reader, **George A. Weston**, says that he would be grateful if anyone could supply him with the exact dates of the British-made sets, so, if anyone wants to contact him, the address is 179 Rosebank Road, Avondale, Auckland, New Zealand.

The items we show in our pictures have all been fully restored by Mr. Weston and where components had to be substituted, he used parts of the same vintage. Likewise, any valves used were of the same period and not later replacement types.

Picture No. (1) is a set made by McMichael. It has MH on the panel and is an all-wave superhet. There are five valves inside the unit and one outside. Date is about 1927.

Next, in picture (2) is a Philips 2516 with valves 506, E415, B443 and date of manufacture is about 1930. The matching speaker is a Baby Grand model 2028 balanced armature cone type that can either hang on the wall or sit on the table as shown.

Set No. (3) is an American "Radiola" model 12/20. Dated about 1925 it has UX199's in all stages except a UX120 as output valve. Case is walnut veneer.

The Gecophone shown in photograph (4) is a 1924 model containing 2 valves and working from batteries. There is one r.f. stage with variometer and a detector stage with condenser-controlled reaction. The valves used are "R" types and the receiver is shown sitting on top of a 2-valve amplifier.

Picture (5) shows a 1924 "B.T.H." crystal set with matching phones. The "driving instructions" are shown in the lid. Also shown is a "Polar Twin" 2-valve battery receiver about 1924 vintage and a Gecophone crystal set c1924 in mahogany case.

The "B.T.H." is called "Radiola"—a name generally associated with RCA in America, indicating a tie-up between manufacturers.

An "Atwater-Kent" model 30 c1926 6-valve set is shown in picture (6). It uses grid stoppers (Cossor system) in lieu of neutralizing. This was the first single-dial model made by this company. Valves are UX201A's in all stages.

No. (7) is an American 1926 "Grebe" MV1 synchrophase 5-valve neutrodyne battery set. Valves

used are UX201A's. The cabinet is mahogany.

A Philips Dutch 2510 1930 vintage 5-valve mains t.r.f. is shown in picture (8). Valves 2 x E442 screen grid, detector E415, output C443 with a 506 rectifier. The case is a metal frame enamelled black with insert panels mottled rich deep red.

Picture (9) shows an American "Gilfillan GN1 c1926 5-valve neutrodyne battery set. This is a de-luxe model with walnut veneer case. It is 3ft long to accommodate "B" batteries. There is a meter for battery checking and three covers on the front drop down. In 1926, this set cost £35.

No. (10) shows a "Claritone" re-entry horn speaker (rear left) made by Automatic Telephone Co., England. It has a heavy cast-iron case and was made in 1924. A B.T.H. horn speaker (rear right) can be seen (c1926). This model has a brown flare with a transfer in black and gold.

Also shown are a "Brown" H4 (front left) (c 1926) a Burndep't "Peter Pan" (c 192??) and a "True Music Minor" (front left)—date not known and no information available.

Photograph No. (11) shows an American cone speaker with a balanced armature. It is made from pressed steel and painted gilt. No. (12) is a cone speaker with a reed unit. It is called a "Mellotone" and the cone is made entirely of cardboard. The stem and base are wooden and the date is April 1926.


In some future Going Back articles we hope to show some more of our readers' collections of vintage radio gear.

## A reader remembers


**R. J. Hall**, 7 Darlington Road, Longrock, Penzance, Cornwall, comments on his early days in radio . . .

"In those days the enthusiast enjoyed winding his own solenoid coils and basket coils, building up variable capacitors from threaded brass rod, brass or aluminium plates and nuts and bolts, and even winding transformers, both r.f. and a.f. I myself have wound more than one mains transformer by hand at 7 turns per volt on a sq. inch core and made speech coil formers and wound them.

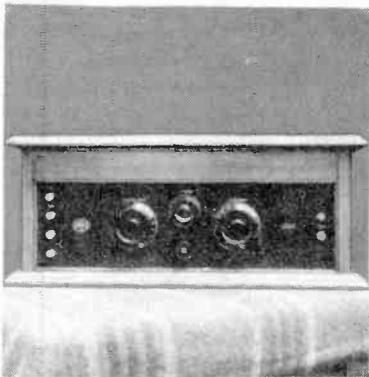
It was common practice in the early days to plan a set and build it on a 'breadboard' layout when it usually worked perfectly but on being tidied up and put into a cabinet it invariably refused to function. In those days radio was a fascinating hobby but since it has become an exact science half the fun has gone".



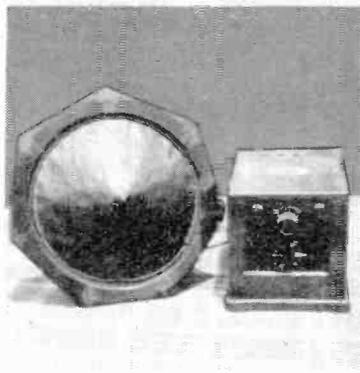
1 McMichael "MH" receiver dated about 1927.



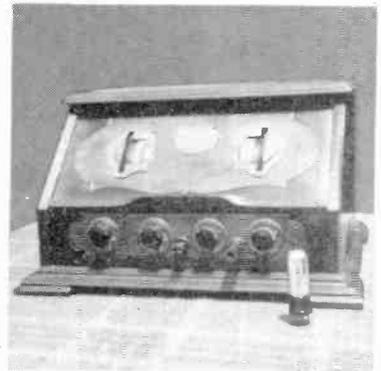
2 The Philips 2516 dated about 1930 and Philips "Baby Grand" speaker




3 R.C.A. model 20 Radiola of 1925.

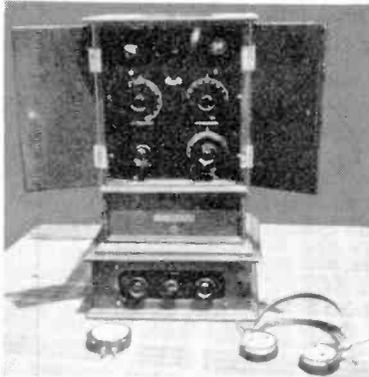

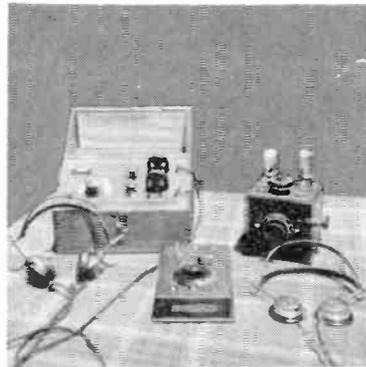4 Gecophone 1924 vintage sitting on a 2-valve amplifier



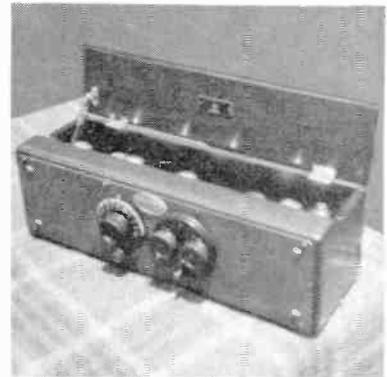
5 B.T.H. crystal set (1924) with Polar Twin and Gecophone set



6 The Atwater-Kent model 30.



7 American Grebe MV1 (1926).

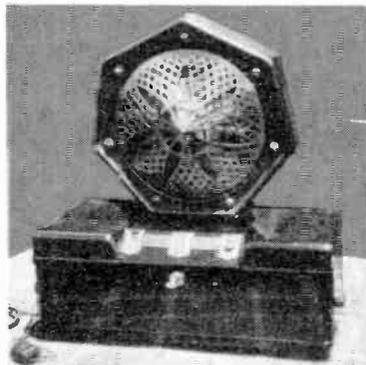


8 Philips 2510 receiver (1930).



9 American Gilfillan GN1 c1926.



10 A selection of vintage speakers.

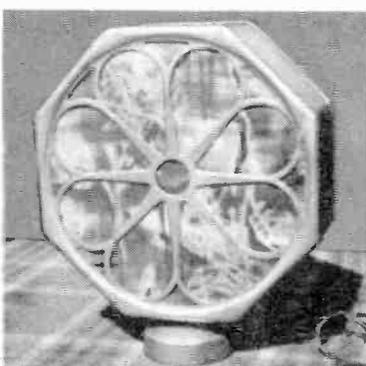

11 American cone speaker with balanced armature.



12 Cone speaker with a reed unit.

# TAKE 20

JULIAN ANDERSON

WHEN a diode is reverse biased it becomes a low value capacitor. Integrated circuits make use of this effect as in this technology it is far easier to incorporate this than a more conventional component. What is more, the actual value of the capacitance depends on the voltage applied. Special diodes are made to make the best use of this effect and are known as *Varicaps* but as we have mentioned, all diodes exhibit this affect, the higher the current rating, the better the affect. We can make use of this effect where a small capacity change is sufficient such as in a b.f.o. and it is this which forms the subject of our project this month. Instead of using a variable capacitor, which would be expensive, we are using a simple potentiometer to alter the tuning.

The complete circuit is shown in Fig. 1. The tuned circuit, which operates round about 465kHz, is made up from C4 and L1. This is coupled to Tr1 for an oscillator, C2 providing the feedback to maintain oscillation.

L1 is the Repanco DRX1 crystal set coil which has both long and medium wave windings, we only use the medium wave winding in our circuit and the connections should run to the common connection of both windings and to the tag that goes to the start of the smaller winding. In the normal state this would be tuned somewhere in the medium wave band and to increase the inductance (and also to give some control over the operating frequency) we fit a dust core into the centre of the coil.

The tuning side is accomplished by VR1, R1, D1 and C1. If a low value capacitor is connected from the collector of the transistor to the negative line this will alter the frequency. We cannot connect the diode directly here as we would affect the d.c. operating conditions of the transistor and so we have to d.c. block this; C1 performs this function.

To alter the capacity of the diode we have to apply d.c. bias to it and this has to be varied. VR1 can be almost any potentiometer from 5kΩ to 500kΩ; all we need is a variable voltage at the slider. R1 has to be included to prevent funny things happening at the extremes of the track.

As regular readers of this column will know, we often use Veroboard but this is of less use at r.f. frequencies and straightforward drilled s.r.b.p. board is better and a layout is shown in Fig. 2. This should cause few problems; the wiring on the reverse side is shown dotted.

When the unit is switched on, the slider of VR1 should be at the centre of the track and then, with the unit near a receiver, the core in L1 should be turned until a whistle is heard on all stations. Whistles may well be heard on one or two stations but this will mean that the frequency, or an harmonic of it, are on top of that station and not on the i.f. When the correct setting has been found VR1 can be adjusted to get the right sort of beat note, it has a fair range both sides of the centre frequency. On the layout a wire is shown marked "To Rx". It will not normally be necessary to make a

## No. 47 VARICAP TUNED B.F.O.

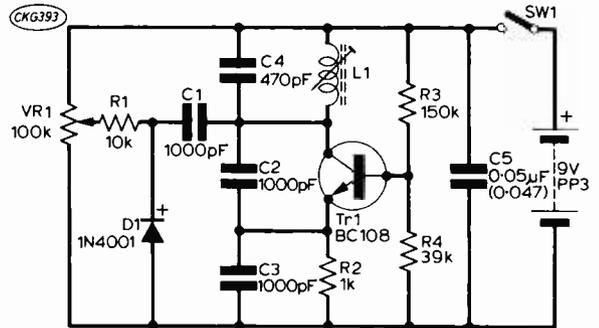


Fig. 1: The circuit - instead of using a conventional variable capacitor, D1 tunes the circuit

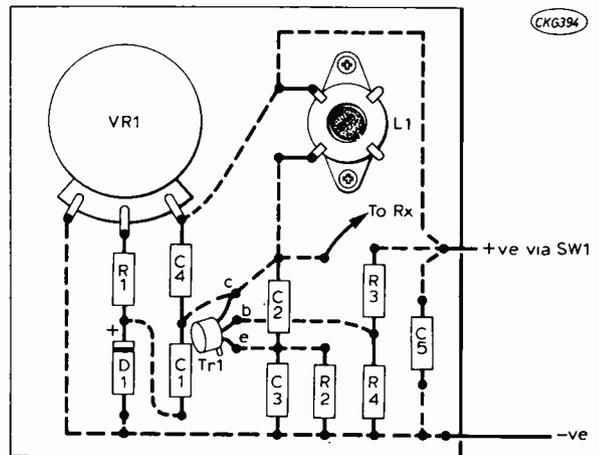


Fig. 2: A suggested component layout on drilled s.r.b.p. board.

### ★ components list

R1	10kΩ ½W, 5 per cent	1p
R2	1kΩ	1p
R3	150kΩ	1p
R4	39kΩ	1p
VR1	100kΩ linear pot	12p
C1	1000pF polystyrene	4p
C2	1000pF polystyrene	4p
C3	1000pF polystyrene	4p
C4	470pF polystyrene	4p
C5	0.05μF Mylar etc.	4p
Tr1	BC108	10p
D1	1N4001	6p
L1	DRX1 crystal set coil	18p
	Dust core to fit L1	3p
SW1	On-off toggle switch	5p
		78p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

connection and this wire may not be needed but if the beat note is a bit weak this wire may be dangled among the components of the receiver's i.f. strip. ■

# Henry's

## YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

### INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIRCHILD



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
RN7400	0.20	0.18	0.16	RN7450	0.20	0.18	0.16	RN74145	1.50	1.40	1.30
RN7401	0.20	0.18	0.16	RN7451	0.20	0.18	0.16	RN74150	3.35	2.95	2.15
RN7402	0.20	0.18	0.16	RN7453	0.20	0.18	0.16	RN74151	1.10	0.95	0.90
RN7403	0.20	0.18	0.16	RN7454	0.20	0.18	0.16	RN74153	1.35	1.27	1.20
RN7404	0.20	0.18	0.16	RN7460	0.20	0.18	0.16	RN74154	2.00	1.75	1.55
RN7406	0.20	0.18	0.16	RN7470	0.30	0.27	0.25	RN74155	1.55	1.47	1.35
RN7408	0.30	0.27	0.25	RN7472	0.30	0.27	0.25	RN74158	1.65	1.47	1.35
RN7409	0.30	0.27	0.25	RN7473	0.40	0.37	0.35	RN74157	1.80	1.70	1.50
RN7410	0.45	0.42	0.35	RN7474	0.40	0.37	0.35	RN74160	2.30	2.40	2.25
RN7411	0.23	0.22	0.20	RN7475	0.55	0.52	0.50	RN74161	2.00	1.80	1.50
RN7412	0.42	0.40	0.35	RN7476	0.45	0.42	0.39	RN74162	3.40	3.25	2.70
RN7413	0.30	0.27	0.25	RN7480	0.80	0.75	0.67	RN74163	3.40	3.25	2.70
RN7416	0.30	0.27	0.25	RN7481	1.25	1.15	1.10	RN74164	2.75	2.30	2.10
RN7417	0.30	0.27	0.25	RN7482	0.85	0.80	0.70	RN74165	4.00	3.50	3.00
RN7418	0.30	0.27	0.25	RN7483	0.80	0.75	0.70	RN74166	4.00	3.50	3.00
RN7419	0.20	0.18	0.16	RN7484	0.90	0.85	0.75	RN74167	2.30	2.00	1.80
RN7420	0.45	0.42	0.35	RN7486	1.45	0.41	0.39	RN74170	4.10	3.55	3.15
RN7422	0.48	0.44	0.40	RN7490	0.75	0.70	0.65	RN74171	2.00	1.75	1.50
RN7423	0.48	0.44	0.40	RN7491	0.90	0.85	0.80	RN74172	1.35	1.27	1.15
RN7425	0.48	0.44	0.40	RN7492	0.75	0.70	0.65	RN74173	1.60	1.35	1.20
RN7427	0.42	0.39	0.35	RN7493	0.75	0.70	0.65	RN74176	1.60	1.35	1.20
RN7428	0.50	0.45	0.42	RN7494	0.80	0.75	0.70	RN74180	1.55	1.30	1.20
RN7430	0.20	0.18	0.16	RN7495	0.80	0.75	0.70	RN74182	2.00	1.80	1.60
RN7432	0.42	0.39	0.35	RN7496	0.90	0.87	0.85	RN74183	2.00	1.80	1.60
RN7433	0.70	0.61	0.44	RN7497	6.25	5.50	5.00	RN74184	2.40	2.00	1.80
RN7437	0.65	0.60	0.50	RN74100	2.50	2.30	2.00	RN74185A	2.40	2.00	1.80
RN7438	0.65	0.60	0.50	RN74104	1.45	1.35	1.20	RN74190	1.95	1.85	1.75
RN7440	0.20	0.18	0.16	RN74105	1.45	1.35	1.20	RN74191	1.85	1.85	1.75
RN7441	0.75	0.72	0.70	RN74107	1.50	0.45	0.40	RN74192	2.00	1.80	1.60
RN7442	0.75	0.72	0.70	RN74108	0.80	0.70	0.60	RN74193	2.00	1.80	1.60
RN7443	1.00	0.95	0.90	RN74118	1.00	0.95	0.90	RN74194	2.50	2.25	1.90
RN7445	2.00	1.75	1.60	RN74119	1.90	1.78	1.65	RN74195	1.85	1.70	1.60
RN7446	2.00	1.75	1.60	RN74121	0.60	0.55	0.50	RN74196	1.50	1.40	1.30
RN7447	1.75	1.60	1.45	RN74122	1.85	1.25	1.10	RN74197	1.50	1.40	1.30
RN7448	1.75	1.60	1.45	RN74123	2.70	2.55	2.47	RN74198	4.60	3.70	3.85
				RN74141	1.00	0.95	0.90	RN74199	4.60	3.70	3.85

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX  
 LARGER QUANTITY PRICES PHONE (01) 402 4891  
 TEXAS HANDBOOK NO. 2, I.C. 700 PAGES DATA 60p. POST 20p.  
 HIGH POWER SM 74 HCO 1 New in stock - send  
 LOW POWER SM 74 LCO 1 for list No. 36

### A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA Y30 10p	BC147 15p	BU105 2.25	OC44 15p	TI843 35p	2N3055 55p
AA Y42 15p	BC169C 15p	BY100 15p	OC45 15p	V405A 25p	2N3440 70p
AA Z13 10p	BC182 10p	BY126 15p	OC57 50p	ZTX108 12p	2N3442 1.25
AC107 35p	BC214 15p	BY127 10p	OC71 15p	ZTX308 12p	2N3525 75p
AC126 25p	BCY32 75p	BYZ13 35p	OC72 25p	ZTX301 15p	2N3614 55p
AC127 25p	BCY33 10p	BYZ14 65p	OC77 65p	ZTX302 18p	2N3615 45p
AC128 25p	BCY39 1.00	GET111 55p	OC81 25p	ZTX341 20p	2N3702 10p
AC176 25p	BCY42 1.00	GET115 55p	OC83 25p	ZTX509 15p	2N3704 10p
AC187 25p	BCY43 1.00	GET880 45p	OC140 55p	ZTX503 17p	2N3705 10p
AC188 25p	BCY55 2.50	LM309K	OC170 25p	2G301 30p	2N3714 1.80
ACY17 30p	BCY70 1.50	(TO3) 1.87	OC171 30p	2N404 20p	2N3771 1.75
ACY20 30p	BCY71 1.50	MAT21 25p	OC204 25p	2N427 35p	2N3773 2.00
ACY21 25p	BCY72 35p	MJE340 50p	OC201 75p	2N696 15p	2N3790 2.25
ACY39 55p	BCY87 2.99	MJE370 70p	OC202 80p	2N697 15p	2N3819 35p
AD140 50p	BCZ11 50p	MJE520 75p	OC203 50p	2N706 10p	2N3820 50p
AD149 50p	BD124 80p	MJE295A	OC211 1.25	2N930 20p	2N3866 85p
AD161 35p	BD131 75p		ORP12 50p	2N987 45p	2N3903 15p
AD162 35p	BD132 80p		ORF60 50p	2N1131 25p	2N3906 15p
AF117 20p	BF115 25p	MJE305S	PF149 20p	2N132 25p	2N3972 2.00
AF118 50p	BF167 25p	NPF105 40p	RA5310AF	2N1302 18p	2N4082 12p
AF124 25p	BF173 25p	NKT214 20p	45p	2N1304 22p	2N4126 15p
AF139 30p	BF179 30p	NKT216 40p	RA5508AF	2N1305 22p	2N4871 35p
AF186 40p	BF180 30p	NKT217 40p	55p	2N1307 25p	2N5457 30p
AF239 40p	BF194 15p	NKT403 70p	TAA 63 75p	2N1308 25p	2N5777 55p
AFY27 30p	BF195 15p	NKT404 50p	TLL49 35p	2N1513 20p	28001 1.00
BF128 25p	BF81 25p	OA5 50p	TIP200 80p	2N1671 1.00	28012 10.00
BA102 30p	BF89 25p	OA10 35p	TIP20A 60p	2N2147 75p	28018 6.25
BA115 7p	BFX13 25p	OA81 10p	TIP21A 60p	2N2160 59p	28026 8.00
BA145 15p	BFX34 75p	OA91 7p	TIP22A 70p	2N2217 25p	28301 50p
BA X13 5p	BFX37 30p	OA200 10p	TIP23A 70p	2N2221 20p	28303 65p
BA X16 7p	BFX88 20p	OC16 75p	TIP30A 60p	2N2222A	28324 80p
BC107 10p	BFY50 20p	OC16 75p	TIP30A 60p	2N2222A	28324 80p
BC108 10p	BFY51 20p	OC20 85p	TIP35A 1.50	2N2369A	40360 40p
BC109 10p	BFY52 20p	OC23 85p	TIP35A 1.50	2N2906 20p	40362 40p
BC109C 12p	BFY60 50p	OC25 40p	TIP36A 2.50	2N2926 (left)	40408 50p
BC113 15p	BFY64 50p	OC28 65p	TIP36A 2.50	2N2926 (right)	40408 50p
BC117 20p	BFX20 15p	OC35 60p	TIP41A 75p	2N3055 35p	40486 75p
BC143 35p	BSY27 15p	OC42 40p	TIP42A 85p	2N3055 35p	40486 75p

**VAT Prices DO NOT include Value Added Tax.** From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay.

### QUANTITY DISCOUNTS

10% 12+ : 15% 25+ ANY ONE TYPE  
 20% 100+ : 25% 250+ TYPE  
 From above sections except Integrated Circuits and Special Orders where discounts are included.  
 Minimum order value £1 please.  
 Postage 7p on all orders.

### SPECIAL OFFERS! SEMI-CONDUCTORS

<b>BFY90</b> 59p	<b>2N2926</b> 10p
1000 MC/S	All Colours
25 + 20p	25 + 9p
100 + 17p	100 + 8p
500 + 15p	500 + 6p
	1000 + 5p
<b>AF117 Mullard 25p</b>	<b>2N3819 Texas 35p</b>
25 + 17p	25 + 30p
100 + 15p	100 + 25p
500 + 12p	500 + 20p
	1000 + 15p
<b>OC170 Mullard 25p</b>	<b>BC107, BC108, BC109 10p each</b>
25 + 20p	All Makes
100 + 18p	25 + 8p
500 + 15p	100 + 7p
1000 + 13p	500 + 6p
	1000 + 5p
<b>BY127 Mullard 15p</b>	<b>AD161, AD162 35p</b>
25 + 12p	25 + 32p each
100 + 10p	100 + 28p
500 + 9p	500 + 25p
1000 + 8p	1000 + 22p
<b>OA202 10p</b>	<b>2N3053 20p</b>
25 + 8p	25 + 18p
100 + 7p	100 + 15p
500 + 6p	500 + 12p
1000 + 5p	1000 + 10p
<b>OC35 Mullard 50p</b>	<b>2N3055 55p</b>
25 + 45p	25 + 50p
100 + 40p	100 + 45p
500 + 35p	500 + 38p
1000 + 30p	1000 + 33p

### ZENER DIODES

400 M/W 5%  
 Miniature  
**BZY 88 Range**  
 All voltages  
 3-3 33 Volt  
 10p each.

25+ 9p  
 100+ 8p  
 500+ 6.5p  
 1000+ 5p

Any one type.

1/2 Watt 5%  
 Wire Ends  
 Metal Case  
 All voltages  
 6-8 100 Volts  
 20p each

25+ 18p  
 100+ 16p  
 500+ 12p  
 1000+ 10p

Any one type.

3 Watt Plastic  
 Wire Ends 5%  
**3EZ Range**  
 All voltages  
 6-8 100 Volts  
 30p each.

25+ 18p  
 100+ 16p  
 500+ 12p  
 1000+ 10p

Any one type.

### LINEAR (O/P AMPS)

702C TO5 / 75p  
 709C TO99 35p  
 709C D.I.L. 35p  
 723C TO99 £1.00  
 All voltages  
 3-3 33 Volt  
 10p each.

25+ 9p  
 100+ 8p  
 500+ 6.5p  
 1000+ 5p

Any one type.

1/2 Watt 5%  
 Wire Ends  
 Metal Case  
 All voltages  
 6-8 100 Volts  
 20p each

25+ 18p  
 100+ 16p  
 500+ 12p  
 1000+ 10p

Any one type.

3 Watt Plastic  
 Wire Ends 5%  
**3EZ Range**  
 All voltages  
 6-8 100 Volts  
 30p each.

25+ 18p  
 100+ 16p  
 500+ 12p  
 1000+ 10p

Any one type.

**PLESSEY INTEGRATED CIRCUIT**  
 3 Watt Amplifier SL403D  
 Complete with 8-page booklet, circuits and data

£1.50 each

### TRIACS

STUD WITH ACCESSORIES

Type	Volts	Price
3 AMP RANGE	P.I.V. 1-11	
RC35A	100	75p
RC35B	200	79p
RC35D	400	85p
8 AMP RANGE (TO48)		

**Why pay more - look at our Fantastic Bargain Offer!**

**PENTHOUSE**

**A COMPLETE AUDIO SYSTEM**

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder. 4 wavebands Long/Medium/Short/VHF. 8 watts per channel (music power) output. The latest BSR CI29 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.


**OUR PRICE £63.00**



Credit terms £6.30 deposit plus £2.00 p. & p. followed by 12 payments of £5.32. Total Credit Terms £70.14 SEND £8.30 TODAY.

**TRANSEUROPEAN**

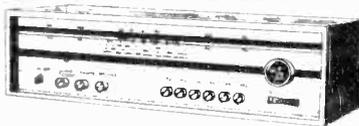
**A TRANSISTORISED HI-FI STEREO RADIOGRAM SYSTEM AT LESS THAN HALF-NORMAL PRICE**



The system includes elegantly styled solid state Teak finish cabinet tuner/amplifier. Push-button selection, 4 waveband VHF/FM, short, medium & long wavebands. The latest 4-speed B.S.R. Mono/Stereo record changer with two 10in. X 6in. matching elliptical speakers. Supplied ready for housing.

**EASILY FITTED - NO TECHNICAL KNOWLEDGE NECESSARY. OUR PRICE £39.95.** Credit Terms of first payment of £3.95, 10 payments of £4.10. Total credit price £44.95, p. & p. £2. SEND £5.95 TODAY

**THE AVON AUDIO SYSTEM**

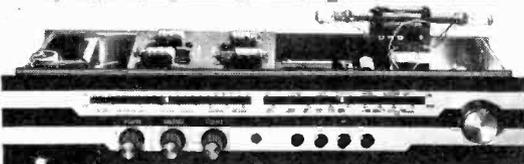

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

**BSR 4 SPEED STEREO/MONO RECORD CHANGER** plays all types or 7in., 10in., and 12in. Mono of Stereo records. Manual or automatic play.

**TWIN ELLIPTICAL SPEAKER.** These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

**EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED.** List Price £45.74. **OUR PRICE £37.00.** Credit Terms £3.70

deposit plus £2 Post & Packing followed by 12 payments of £3.15 (Total Credit Terms £41.50) Don't miss this bargain. **SEND £5.70 TODAY**

**ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE**

**CALLERS WELCOME**

Please send me free details of your range

Name .....

Address .....

PW/4/73

**LEWIS radio** 100, Chase Side London N.14  
Tel: 01-886 3733/9666

Post coupon NOW for... **FREE** leaflets

**NEW**  
ALL SILICON!



**PRACTICAL WIRELESS**

**ELECTRONIC IGNITION SYSTEM**

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, refundable on purchase of kit.

Suitable for 12v or 6v systems with Pos. or Neg. earth.

Price: Standard Kit .....£7.25 U.K. Post Free

De-Luxe Kit .....£8.75 U.K. Post Free

Quantity Discounts:

Trade and Overseas 1-5 Nett 6-9 Less 10%  
Enquiries Invited 10-49 Less 15% 50-99 Less 20%  
Mail Order Only 100-999 Less 25% 1000 up Less 30%

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO ANY V.A.T. ADJUSTMENT.

**STATE POS. OR NEG. EARTH AND 6V OR 12V WHEN ORDERING.**

**DABAR ELECTRONIC PRODUCTS**

98A LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ  
Tel. Walsall 34365

**NEW VALVES! GUARANTEED AND TESTED**

**24-HOUR SERVICE**

1R6	25	DAF91	21	ECC85	31	EL84	20	PCF802	38	U329	65
1S5	21	DAF96	35	ECH35	48	EM30	35	PCL82	28	U801	73
1T4	14	DF91	14	ECH42	58	EM81	35	PCL83	33	UABC80	29
384	24	DF96	35	ECH81	28	EM84	30	PCL84	31	UBF89	28
3V4	46	DH77	18	ECL80	27	EY86	27	PCL85	36	UCH85	32
6/300L2	24	DK91	25	ECL82	27	EZ80	19	PCL80	35	UCH42	58
6AT6	18	DK96	43	ECL86	32	EZ81	21	PFL200	49	UCH81	28
6AQ5	21	DL92	24	EF39	38	KT61	54	PL36	45	UCH81	28
6BW7	48	EL94	47	EF41	56	KT66	75	PL81	41	UCL82	30
6F1	57	DL96	38	EF80	22	N78	10	PL82	39	UF41	49
6F23	64	DY86	21	EF85	28	PC86	44	PL83	31	UF89	28
6F25	49	DY87	21	EF86	27	PC88	44	PL84	28	UL41	52
12AU7	17	DY802	28	EF89	24	PC97	38	PL500	59	UL84	27
25L6GT	18	EABC80	28	EF91	12	PC900	28	PL504	59	UY41	37
30C115	58	EB33	38	EF92	26	PC984	27	PY81	23	UY85	22
30C17	73	EB41	47	EF183	25	PC989	41	PY82	23	W77	42
30F5	60	EBF89	27	EF184	27	PC189	46	PY800	30	Z77	18
30FL1	59	ECC81	15	EH90	33	PCF80	25	PY801	30		
30FL14	67	ECC82	17	EL33	54	PCF86	44	R19	27		
30PL1	58	ECC83	21	EL41	52	PCF801	27	U251	60		

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no callers.

**GERALD BERNARD** 83 Osbaldeston Road, Stoke Newington, London N.16

**4 CHANNEL STEREO CONVERTER**



**TRANSFORMS YOUR STEREO SYSTEM INTO SENSATIONAL QUADRAPHONIC SOUND**

Create a new dimension in sound - sound that engulfs you with natural realism from every corner of your room. Simply wired to your amplifier or Tuner/Amp.

speaker outputs and again into 4 speakers. Neat styling with brushed effect console panel. Peak input power 50w into 8 ohms. Front Hi/Low Level 6dB. Phone jacks for input and output. Size: 6" x 3 1/2" d. x 2" h. Guaranteed.

INTRODUCTION PRICE

**£7.50**

35 P & P

**CCLE** (Dept. PW 2), 43 BARTHOLOMEW CLOSE, LONDON, EC1A 7HP. Tel. 01-600 3211.



**T**HIS instrument was designed for use with a photographic enlarger, to determine the exposure required for any particular print. It is cheap to build and easy to use, with a range up to about 40 seconds.

### THE CIRCUIT

This is shown in Fig. 1. LDR is a light dependent resistor whose resistance varies with the amount of light falling on its face. LDR and VR1 form a potential divider. The potential at point A is determined by the setting on VR1 and on the resistance of the LDR, hence on the light incident on its surface. Tr1 and Tr2 form a Schmitt trigger. The potential at A determines which of these transistors is on and which is off.

Tr2 has a light emitting diode D1 in its collector circuit, which lights when Tr2 is conducting.

To measure the amount of light incident on the meter, VR1 is altered until the extinguishing (i.e. on-off) point of the diode is found. The setting of VR1 is thus a measure of the exposure time required. A knob with a linear calibration around the outside is used to alter VR1.

The unit is sensitive to voltage supply change, hence a zener diode D2 is used to regulate the power supply.

SW1 is a push button switch which is depressed only when making the exposure, hence eliminating the possibility of forgetting to turn the unit off.

### COMPONENTS

Other transistors could be used for Tr1 and Tr2 e.g. 2N2926. VR1 is 50k $\Omega$ . Increasing the value increases the range of the instrument but decreases its sensitivity.

D1 does not have its positive lead marked. This must be found by trial and error or by using a meter.

### CONSTRUCTIONAL DETAILS

The whole unit can be fitted into a small plastic box 4 $\frac{1}{2}$ in. x 3in. as shown in Fig. 2. Veroboard is used to mount the transistors and resistors. Two small holes can be drilled to take the LDR leads, a dab of

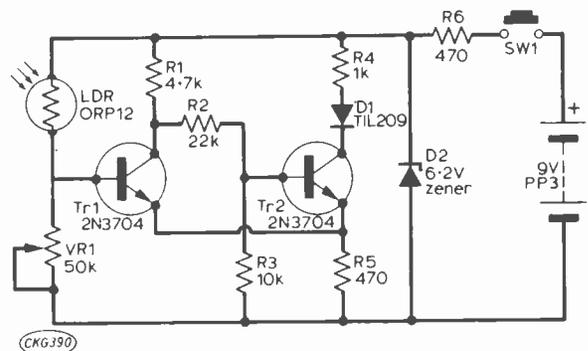


Fig. 1. The complete circuit which is basically a Schmitt trigger.

### ★ components list

#### Resistors

R1 4.7k $\Omega$	R4 1k $\Omega$
R2 22k $\Omega$	R5 470 $\Omega$
R3 10k $\Omega$	R6 470 $\Omega$

All  $\frac{1}{8}$ W, 5% types  
VR1 50k $\Omega$  lin. pot.  
LDR ORP12.

#### Transistors

TR1 2N3704  
TR2 2N3704  
D1 TIL209 (light emitting diode)  
D2 6.2V zener diode.

#### Miscellaneous

9V battery; Battery connector; Veroboard; On-off switch, push button type; Plastic box; Calibrated knob or dial.

glue will hold it in place. Further constructional details are not given since the layout is not critical and most constructors will find it is a simple job to assemble the instrument.

The instrument is now ready for calibrating.

### CALIBRATION

The scale is calibrated in terms of exposure as follows: a piece of clear blank film is put into the


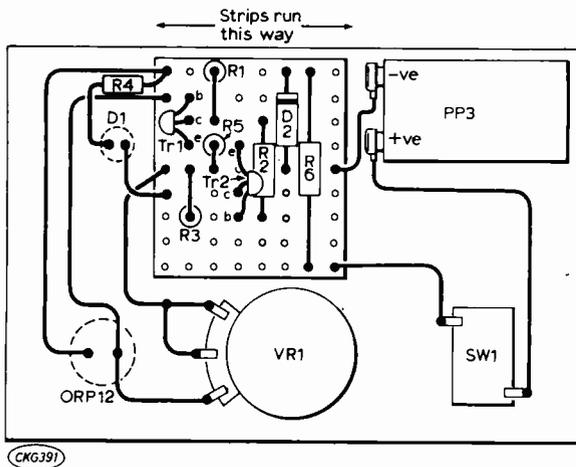


Fig. 2: Constructional details.

Fig. 3: An example of the gradations which will appear on the printing paper; the time of each exposure is marked below.

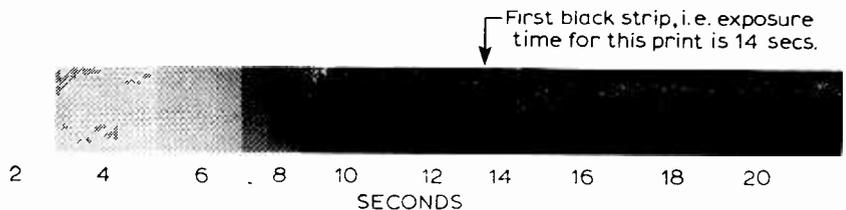

enlarger; all lights in the darkroom are put out except for the enlarger light; the instrument is placed on the easel, SW1 is depressed and VR1 is adjusted so that the diode light just goes from on to off. The reading on the scale is noted. (It is important that the scale reading is always taken from on-to-off since the off-to-on reading is different, owing to hysteresis in the Schmitt trigger.)

A narrow strip of paper is then used for a test strip. Parts of the paper are exposed in multiples of two seconds. The developed strip will look like Fig. 3. There is a gradual transition from light to black. The first black stripe can be judged and the corresponding exposure time also. The scale reading and exposure time are then noted.

The procedure is then repeated for different light readings (scale readings) and a graph of scale reading against exposure time is plotted, Fig. 4.

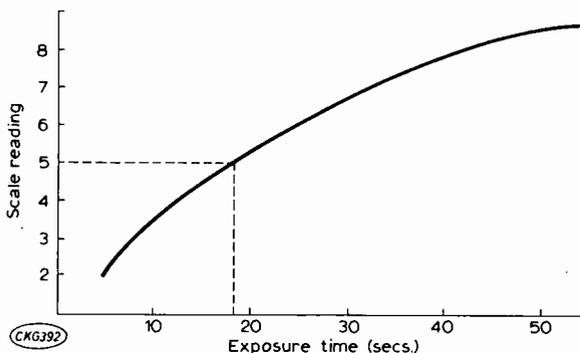


Fig. 4: A calibrated graph relating the knob markings of 1-10 to the time.

For scale readings between 20 and 40 seconds it will be easier if the strips are exposed in multiples of 4 seconds.

A similar calibration graph must be obtained for each different type of printing paper used.

## USING THE INSTRUMENT

Having obtained the graphs, the instrument is simple to use. Place it on the easel such that a clear part of the film e.g. the margin between the frames or an unexposed frame, shines onto the LDR. Find the on-off point of the diode D1 and note the scale reading. From the graph, read off the required exposure time, if the scale reading is 5 then the exposure time is 19 secs. This will give the correct exposure time for all normal negatives with full tonal reproduction.

## CONCLUSION

The instrument is cheap and easy to make, and is

reasonably accurate. Its great advantage is the saving in time, since after initial calibration there is no need to make a test strip for every exposure. ■

**25 YEARS MARCH 1973 page 993.** At the foot of column three: The I.E.R.E. is publishing a collection of 20 papers in their journal on semiconductor subjects.

**DIGITRONIC SOLID STATE DIGITAL CLOCK MARCH 1973 page 1009.** The sentence—There is no need ... harm a LED is to pass too high a current through it (most LEDs work operate on 10–15mA).

### Back Numbers

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless** or **Television**.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

**LARGE STOCKS  
ATTRACTIVE DISCOUNTS  
DEPENDABLE SERVICE**

# ELECTROVALUE

Electronic Component Specialists

## TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 80p  
AC153K pnp germanium low power 25p  
AC176K npn germanium low power 23p  
AD161 npn germanium medium power 42p  
AD182 pnp germanium medium power 40p  
AF139 pnp germanium VHF 33p  
BCN 107 13p; BC708 12p; BC104 13p;  
BC107 10p; BC169 9p; BC169 10p;  
BC177 15p; BC178 14p; BC179 15p;  
BC257 9p; BC258 8p; BC259 9p } npn  
Standard groupings available.  
BD135 npn med power 28p  
BD136 pnp med power 27p  
**DIODES**  
OA90, OA91, OA95 each 6p  
OA200 9p; OA202 10p  
**Other semiconductor**  
AC128 21p; AF117 24p  
BFY51 20p

Full lists and technical data will be found in Catalogue No. 6.


## SIEMENS' THYRISTORS

0-NA 400V 58p, 600V 70p  
3A 400V 80p, 600V 88p

**ZENER DIODES** full range E24 values: 400mW: 2.7V to 30V, 14p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 260F) 4p.

## DIN PLUGS & SOCKETS

by Hirschmann, 4A rating

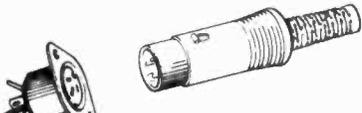


2 way LS—socket 10p; plug 12p, 3 way scr. socket 10p; plug 12p, 5 way scr. socket 12p; plug 15p.

## TRANSISTOR ACCESSORIES

To3 cover 7p  
Heat sink\* 1c/w, type 6W1, un drilled 60p
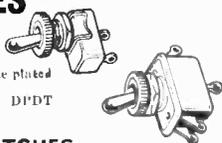
## SWITCHES

1011C SPST toggle 19p;  
409 DPDT toggle 28p. (These are chrome plated 2.5A rating)  
7201 Sub-miniature DPDT 250V ac/2A 48p




## ROTARY SWITCHES

Radionepars Miniature Make-switch (in assembly kit form) 5hwt 48p.  
Waters, MBB-2P5W, 1P11W; 3BM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each, 6p.

## WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p

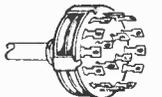

## ELECTROLYTIC CAPACITORS

### AXIAL LEAD

Rated voltage: 3V	6.3V	10V	16V	25V	35V	50V	63V	100V
Capacity $\mu$ F								
0.47							7p	5p
1.0						7p		5p
2.2								5p
4.7								5p
10			7p	5p				5p
22			5p	5p		6p		5p
47	5p		5p	5p		6p		5p
100	5p	5p	5p	5p		7p		15p
220	5p	6p	6p	6p		8p	14p	14p
470	5p	7p	7p	8p		10p	14p	18p
1000	8p	10p	10p	14p		18p	18p	21p
2200	12p	14p	18p	20p		30p	33p	34p
4700	19p	22p	30p	33p				
10,000	31p	33p						

## Polycarbonate -5% Tolerance

250V up to 0.1 $\mu$ F; 100V/0.1 $\mu$ F and above.  
0.047: 0.012; 0.015; 0.018; 0.022;  
0.027; 0.033; 0.047; 0.050; each 4p.  
0.068; 0.082; 0.1; 0.12; 0.15 each 4p.  
0.18; .22; each 5p.  
0.27; 0.33; 6p; 0.39 7p; 0.47 8p; 0.56 10p.  
0.68 11p. 1 $\mu$ F 13p.

## RESISTORS 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9 (see note below)	10 to 99	100 up
C	1/20W	5%	82 $\Omega$ -220K $\Omega$	E12	9	8	7
C	1/8W	5%	47 $\Omega$ -470K $\Omega$	E24	1	0.8	0.7
C	1/4W	10%	4.7 $\Omega$ -10M $\Omega$	E12	1	0.8	0.7
C	1/2W	5%	4.7 $\Omega$ -10M $\Omega$	E24	1.8	1	0.9
C	1W	10%	4.7 $\Omega$ -10M $\Omega$	E12	2.5	2	1.9
MO	1/2W	2%	10 $\Omega$ -1M $\Omega$	E24	4	3	2 net
WW	1W	10% $\pm$ 1/20 $\Omega$	0.22 $\Omega$ -3.9 $\Omega$	E12	7	7	6
WW	3W	5%	1 $\Omega$ -10K $\Omega$	E12	7	7	6
WW	7W	5%	1 $\Omega$ -10K $\Omega$	E12	9	9	8

Codes: C—carbon film, high stability, low noise.  
MO—metal oxide, Electrovol TR5, ultra low noise.  
WW—wire wound, Pleseley.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order).

## EVERYTHING BRAND NEW, GUARANTEED TO MAKERS SPEC. NO SECONDS OR REJECTS


### KNOBS

All grub screw fitting for 1" shafts. Black. For other types—see Catalogue No. 8, P.34



F14 (20mm) pack of 3 32p  
F13 (26mm) pack of 2 88p  
F12 (33mm) pack of 2 40p  
F19 (20mm) pack of 2 32p  
F18 (26mm) pack of 2 38p  
F17 (38mm) pack of 2 40p  
K.B.4 (20mm) pack of 4 40p  
N 30/3 (17mm) aluminium, each 24p

### POTENTIOMETERS

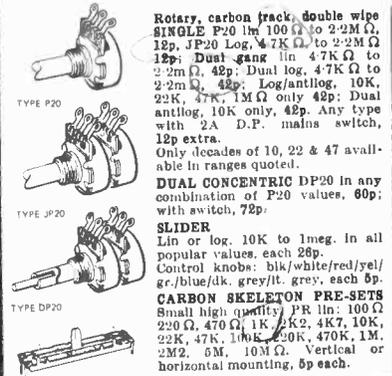

Rotary, carbon track, double wipe  
SINGLE P20 lin 100 $\Omega$  to 2.2M $\Omega$ , 12p, JP20 Log, 4.7K $\Omega$  to 2.2M $\Omega$ , 12p; Dual gang lin 4.7K $\Omega$  to 2.2M $\Omega$ , 42p; Dual log, 4.7K $\Omega$  to 2.2M $\Omega$ , 42p; Log/antilog, 10K, 22K, 47K, 1M $\Omega$  only 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.  
Only decades of 10, 22 & 47 available in ranges quoted.  
DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.  
SLIDER  
Lin or log, 10K to 1Meg. in all popular values, each 28p.  
Control knobs: blk/white/red/yel/gc./blue/dk. grey/lt. grey, each 5p.  
CARBON SKELETON PRE-SETS  
Small high quality P.R. lin: 100 $\Omega$ , 220 $\Omega$ , 470 $\Omega$ , 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M $\Omega$ . Vertical or horizontal mounting, 5p each.

## IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semi-conductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc. information and equivalent tables, etc. Well illustrated (96 pages 5 1/2" x 8 1/2") 25p post free with refund voucher for 25p, allowable on orders over £5 or more.

with 25p refund voucher

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T.

**DISCOUNTS** Not allowed on net prior items. 10% on orders for £5 or more, 15% on orders for £15 or more. Prices subject to alteration without prior notice.

**POSTAGE AND PACKING FREE** SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

U.S.A. CUSTOMERS please contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

# ELECTROVALUE

(Dept. P.W. 4) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB  
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 3603 Telex 264475  
BUS. REG. NO. 1047788. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB

### AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.75 plus 25p post and insurance.



### TAPE HEADS

We are gradually obtaining more information about the Truvox tape heads we have, we are told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs, 1 record and 1 erase head. Price of the 2 track 45p per pair, 4 track 75p per pair. Pair mounted on plate 45p extra.


### MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. £1.50 each.


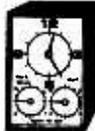
### TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 88p. KNUCKLED MODEL FOR P.M. 50p.



### MAINS CLOCK AND TIME SWITCH

Smith's main's driven clock with 15 amp. programmable switch also notes showing how you can use this to wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keeps pets warm, halves your heating bills, etc., etc. £1.75 + 20p p. & p.

### WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

### IMMERSION HEATERS BY REMLOY

Standard fitting for domestic water tanks, made by the famous Remloy Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 11". 2kw or 3kw. £1.50 plus 40p each post and insurance.



### NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic pushrod suitable for operating. 5p each, 45p doz.



### THERMOSTAT

Continuously variable 30°-90°C. Has sensor bulb connected by 33in. of flexible tubing. On operation a 15 amp 250 volt switch is opened and in addition a plunger moves through approx 1in. This could be used to open valve on ventilator etc. £1.50 plus 25p p. & ins.

### HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C with thermistor as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £2.50.

### NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac. XN.3. Price £1.45 each. 10 for £13.

### 12-WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper cores, each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.

**VAT.** From April 1st. VAT. MUST be added to total order.

### STANDARD WAFER SWITCHES

	Standard size 1 1/2" wafer—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.											
No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way	12 way	12 way	12 way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
3 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
4 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
5 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
6 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
7 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p
8 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p
9 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p
10 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p
11 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p
12 poles	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p	70p

### THYRISTOR LIGHT DIMMER

For any lamp up to 250 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95 plus 20p post and insurance. Industrial model 5A with control knob but not mounted on switch plate, £3.



### HORSTMANN "TIME AND SET" SWITCH

(A 30 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50, p. & ins. 25p.



### 13 AMP TWIN GANG SOCKETS

Offered at less than wholesale price—your opportunity to replace those dangerous adaptors—brown bakelite flush mounting—standard fitting. Unswitched 20p each, separately switched 30p each. Separately switched less 10% ten or more + 20p postage if order under £5.



### 4 WATT AUDIO AMPLIFIER

£1.45

Works off dry batteries, car battery or mains power pack. Only £1.45. This low price possible only because the make is over produced. Unrepeatable—once stocks are cleared. Made by the famous Mullard company and carries their full guarantee. Complete in dustproof case. Amplifier may be used for Mono or Stereo, music or speech. Hundreds of applications. Frequency response 60Hz-16KHz. Supplied complete with connection diagram and operating notes. Postage and Ins. 20p.

FREE. All purchasers receive Mullard booklet "Do It Yourself Stereo" tells all you need to know to build your own stereo system. Write today to avoid missing this terrific offer.

### HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines. Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £5.75 plus 25p post and insurance. Don't miss this terrific bargain.



### MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January '73. All electronic parts £2 post paid.



### DIGITAL COUNTER TIMER


Very stable and reliable crystal controlled circuit. Capable of work in excess of 15 MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case £39.50 or construction data and price list 50p.

### INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards, with circuits and technical data of each. Complete parcel only £1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.

TERMS: 10% discount if ten of an item ordered, send postage where quoted—other terms, post free if order for these over £6.00 otherwise add 20p.

### EXTRACTOR FAN

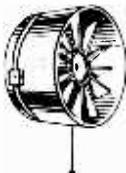

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2.50 plus 30p post and ins.

### QUICK CUPPA

Mini Immersion Heater. 350w 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available same price. Jug heater £1.50 plus p. & p. 14p.



### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1 plus 20p postage.

### TREASURE TRACER

Complete Kit (except wooden battery) to make the metal detector as the circuit in Practical Wireless, August issue. £2.95 plus 20p post and insurance.

### WINDSCREEN WIPER CONTROL

Beat dirty roads, drizzle, fog, etc. Kit of parts to make this useful accessory with circuit details. £2.25.



### 12 VOLT 1 1/2 AMP. POWER PACK

This comprises double-wound 230/240v mains transformer with full wave rectifier and 2000 mfd/50v smoothing. Price £2 plus 20p post & packing.

### I CHIP RADIO

Ferranti's latest device ZN414—gives results better than superhet. Supplied complete with technical notes and circuits. £1.25 each, 10 for £11.

### HI-Q TUNER COMPONENTS

For experimenting with the ZN414. KIT NO. 1. Plessey Miniature Tuning Condenser with built-in LW switch and 3" Ferrit slab and litz wound MW coil, 65p. KIT NO. 2. Air spaced tuning condenser 6" ferrit rod litz wound MW and LW coils, 85p. KIT NO. 3. Air spaced TC with slow motion drive ferrit rod, with litz wound LW and MW coils, £1. KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils, 45p.

### 6 VOLT CLOCK MOTOR

Works from 50 cycle mains through condenser, resistor or step-down transformer. This is a synchronous motor made by Smiths, so it is an extremely accurate speed controller. Very small in size (2 watt) and with a polythene cover. Price 30p each, 10 for £2.70.

### SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated job. 100 watt £2.25 plus post and ins. 20p. BIG JOB 250 watt model £4.75 plus post and ins. 40p.

### MAINS OPERATED SOLENOIDS


Model 772—small but powerful 1" pull—approx. size 1 1/2 x 1 1/2 x 1 1/2". 60p. Model 400/1—1" pull. Size 2 1/2" x 2 1/2" x 1 1/2". 75p. Model TT10—1 1/2" pull. Size 2 1/2" x 2 1/2" x 2". £1.80 plus 20p post and insurance.

### 3 STAGE PERMEABILITY TUNER

Made originally for Radiomobile car radios. This is a medium wave tuner with a frequency coverage 16kc-525kc. Aerial. RF and oscillator sections (long wave coil almost instant heat also illuminated job. 100 watt £2.25 plus post and ins. 20p. BIG JOB 250 watt model £4.75 plus post and ins. 40p.) Model 772—small but powerful 1" pull—approx. size 1 1/2 x 1 1/2 x 1 1/2". 60p. Model 400/1—1" pull. Size 2 1/2" x 2 1/2" x 1 1/2". 75p. Model TT10—1 1/2" pull. Size 2 1/2" x 2 1/2" x 2". £1.80 plus 20p post and insurance.

few inter connection components to make a complete compact receiver. Circuit supplied. Price 65p, less 10% for 10.

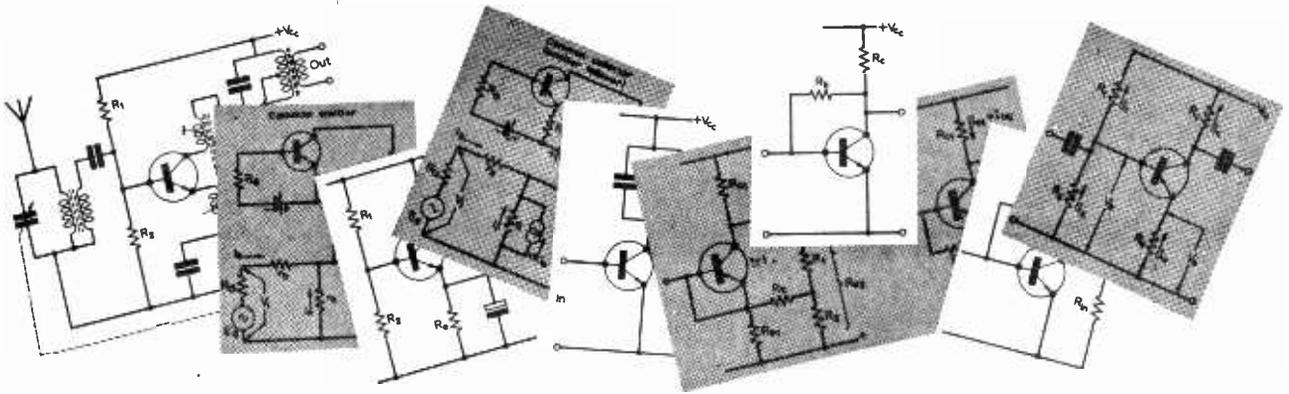**J. BULL (ELECTRICAL) LTD.**  
(Dept. P.W.) 7 Park Street, Croydon CRO 1YD  
Callers to: 102/3 Tamworth Road, CROYDON



# TRANSISTOR CIRCUITRY for beginners

## PART 15

H.W. HELLYER & MICHAEL HOLLIER

### Tone control circuitry

Toward the end of the last part of this series of articles that was published, we were concerned with frequency-dependent feedback. Without being intentionally devious, we skated over some of the finer points and here shall try to keep our promise of digging more deeply into the matter of tone controls, their design and their limitations.

The utter purist will not deign to acknowledge the need for tone controls! Everything should be flat, he says. There should be, he further asserts, no need to alter the frequency response of an amplifier if all the other parts of the audio system are in order. True, but Utopia has not yet arrived, whatever the politicians promise, and there will be nasty pops and crackles from our records, hiss from our tape, peaks and troughs from many a cartridge and even worse deviations by the time the sound escapes from the loudspeakers.

Even then, we are not finished. If the little woman insists on foot-deep rugs and wall-to-wall drapes, or if your pad is scoured to its functional austerity, man, you will need some trimming of the ideally flat response to compensate for—in the first case, the premature absorption of treble, and in the second, the 'hardness' of the sound. Tone controls may be regarded as necessary evil, but as long as we are obliged to have them, let's make sure they do not detract from the best possible performance. And in so many commercial designs, they do.

### First steps

Before delving into the tone control circuit as a whole, we must take a look at the effect of the passive components with a change in frequency. Back in the days when Poppa bought his radiogram because it sounded 'mellow', the tone control was simply a network of passive components, usually across the output stage, with variation of the resistive part of a series capacitor-resistor shunt that drained away progressively more and more of the upper frequencies. It was, in other words, a variable treble-cut device. One or two more enterprising makers

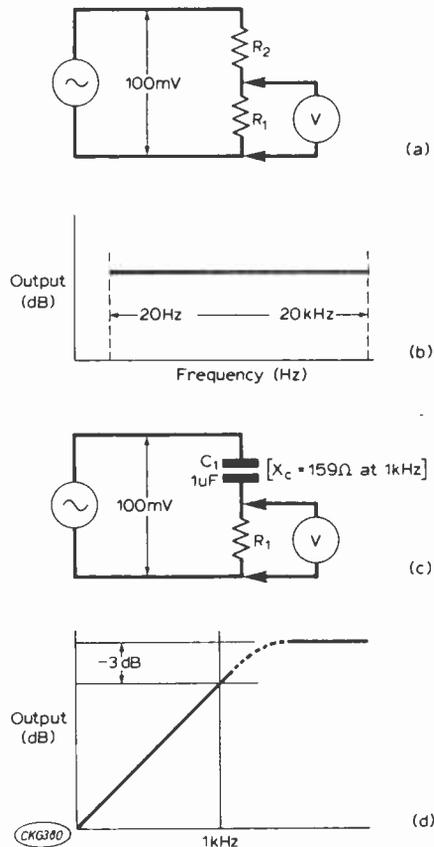


Fig. 74: (a) For a simple resistive network the output shown by the voltmeter is in proportion of the ratio of the resistors to the applied input voltage. In (b) theoretically, the output should not change with frequency, giving a "straight-line" graph. (c) Substituting a capacitor for R2 makes the output frequency dependent while (d) shows an example of the curve we might expect from a simple network such as (c) having a "slope" of 6dB per octave.

fitted alternative resistor-capacitor combinations in the grid circuit of output valves, and others even went so far as to label these Bass or Treble Boost and Cut, but all such passive networks, i.e., those which do not have inbuilt amplification, must attenuate the overall signal.

The point about the passive tone controls is that the attenuation varies the frequency. Take the case of a simple resistive network, as in Fig. 74(a). If we have two resistors of equal value, fed by a signal generator, the output across the measured one will be half the input signal in amplitude, but will not change in frequency. A graph of the situation would be a straight line, as Fig. 74(b).

But if we now substitute the upper resistor with a capacitor, C1 in Fig. 74(c), we find that the measured output will be exactly half the input at

**only one frequency.** Reactance  $X_c = \frac{1}{2\pi fC}$  where  $X_c$  is in ohms, C in farads and f is the frequency at which the test is made, in hertz.

Working out the reactance of a  $1\mu\text{F}$  capacitor at 1kHz, we get  $\frac{10^6}{6.28 \times 1000 \times 1} = 159$  ohms.

But if we now measure the voltage across a similar-value resistor, we find that instead of half the signal input, we have slightly more. Instead of our attenuator dropping the output by 6dB (to half voltage) at 1kHz, it will have dropped the output only 3dB. This is because the voltage across the capacitor is  $90^\circ$  out of phase with the voltage across the resistor. The output voltage ratio is 0.707:1, not 0.5:1. In fact, if we alter the frequency of the generator, we will find that the measured output drops as the frequency falls. The rate of 'slope', as shown in Fig. 74(d), is 6dB per octave, an octave being a frequency change of 2:1.

This 3dB drop has a further significance when we tackle power output stages, for if the drive voltage to the amplifier fell sufficiently for the power output to drop 3dB, this would be the well-known 'half-power-point'. This is the figure normally quoted in amplifier specifications—a point to which we shall return later. Below this -3dB point in Fig. 74(d), the slope of the curve falls away regularly by 6dB per octave, i.e., a ratio of 2:1, a reduction of output by a half each time the frequency is halved.

## Making it active

It helps to regard tone control as a method of frequency correction. The introductory remarks we have made, and references to frequency-dependent

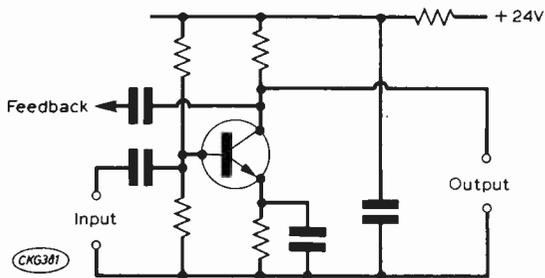


Fig. 75: A collector-follower amplifier arranged so that its output can be measured with and without feedback.

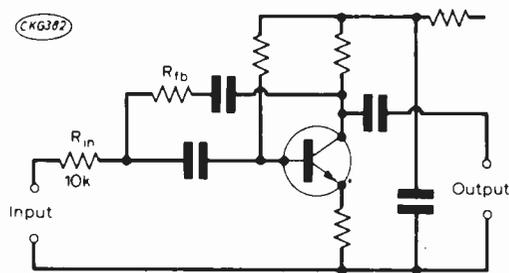


Fig. 76. The basic circuit used for tests.

feed-back in previous articles, should have prepared the regular reader for this approach. Simple tone controls are types of filters. We shall deal thoroughly with filter circuitry later, but at the moment it is necessary to observe that the 'filter' of Fig. 74(c), for example, is called a 'first order filter', having a 'slope' of 6dB per octave. Second order filters have slopes of 12dB/octave and third-order filters, 18dB/octave. As we shall see, real filters, used in well-designed audio amplifiers, should ideally have a third-order slope to be effective.

These filters are passive devices. They contain no amplifying stage or stages to put back the signal attenuated by their action. If we make a marriage of the virtual earth circuitry we talked about in Parts 12 and 13 of this series and the fundamentals of tone control circuitry touched upon in Part 11, we get an amplifier with frequency-dependent feedback, which becomes, if we correctly design it, a better tone control circuit.

First, we need what is known as an 'inverting amplifier'. If you take a look at Fig. 75, you will see that this can be a collector-follower circuit, so arranged that we can measure its gain with or without the feedback. In practice, this is a useful circuit, and the component calculation will be discussed as we go along. It is convenient to use the 24-volt supply described in Part 13, December PW. Fig. 76 shows the circuit devised by Mike and used for tests on the prototype.

With an input from the audio generator, and an output measured with a millivoltmeter, we can measure the open-loop gain. This is the gain of the amplifier with no feedback connected. Here, a word of warning is required: in many erudite theoretical articles, 'open-loop gain' is bandied about freely, but an inspection of the circuit will often show that it would be virtually impossible to measure it in practice. Our aim in this case is to show what we mean by the term, then, by applying the feedback we need, to modify the gain and achieve our controlled response, i.e., effect a tone control.

In our prototype, the open-loop gain, ( $G_0$ ) was 260. It is absolutely essential when carrying out these measurements to mount the circuit in a screened box, use screened input and output leads and make sure our construction is 'solid'. We use Veroboard for convenience: it allows connection of additional components while retaining the versatility of wired circuitry. We use the very convenient Norman Rose aluminium boxes, because they are inexpensive, easily worked for outlet holes, tag-strip mountings, etc., and have a simple lid which not only completes the screening but also affords an easy access for modifications.

**TO BE CONTINUED**

# BI-PRE-PAK

## COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

**ONLY 95p**

POST & PACKING 35p EACH

## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

**ONLY 25p**

POST & PACKING 15p



### TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H9	2	OC271 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short Lead Transistors, NPN Silicon Planar types.	50p
H39	10	Integrated Circuits. 6 Gates BMC 962, 4 Flip Flops BMC 945	50p
H40	20	BFY507, 2N696, 2N1613 NPN Silicon uncodded TO-5	50p

### UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA208	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 type	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BS195A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



OVER **1,000,000** TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

**600,000** Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.  
Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.  
R.F. NPN and switching NPN Types also. Please state type of transistor required when ordering.

ALL AT 500 for £3, 1,000 for £5, 10,000 for £40 P & P 10p/1.000.

### OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.  
TYPE "G" NPN silicon similar ZTX 300 range  
TYPE "H" PNP silicon similar ZTX 500 range

### POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic cased Silicon Power Transistors of latest design. 40watts and 90watts. PNP & NPN types. All types available at the most shattering low prices of all time. All are fully tested, marked and guaranteed!

40W NPN	20p	18p	16p
40W PNP	21p	19p	17p
90W NPN	24p	22p	20p
90W PNP	25p	23p	21p

PAK PAKS of Complementary pairs  
MP40 40W+40W 50p 48p 46p  
MP90 90W+90W 60p 58p 56p

PLEASE STATE IF NPN/PNP OR NPN,NPN ARE REQUIRED.

### A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3.50, **pcst paid.**

A MUST for Colour T.V. Alignment.

### Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

## FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

## 8 RELAYS FOR VARIOUS TYPES £1 P & P 25p

### INTEGRATED CIRCUITS

Clocked Flip Flop	BMC931	20p	18p	16p
Ex. 2/4-input Buffer	BMC932	12p	11p	10p
2/4-input Expander	BMC933	12p	11p	10p
Hex. Inverter	BMC934	12p	11p	10p
Hex. Inverter	BMC935	12p	11p	10p
Hex. Inverter	BMC936	12p	11p	10p
Hex. Inverter	BMC937	12p	11p	10p
Decade Counter	BMC938	25p	23p	21p
Div. by 16 Counter	BMC939	25p	23p	21p
Hex. Inverter	BMC940	12p	11p	10p
Hex. Inverter	BMC941	12p	11p	10p
Type D Flip Flop	BMC942	20p	18p	16p
Ex. 2/4-input Power	BMC944	12p	11p	10p
Clocked Flip Flop	BMC945	20p	18p	16p
4/2 Input NAND Gate	BMC946	11p	10p	9p
Clocked Flip Flop	BMC948	20p	18p	16p
4/2 Input NAND Gate	BMC949	12p	11p	10p
Pulsed Trig. Binary	BMC950	20p	18p	16p
Monostable Multivib.	BMC951	25p	23p	21p
Dual J/K Flip Flop	BMC953	20p	18p	16p
Dual J/K Flip Flop	BMC955	20p	18p	16p
Dual J/K Flip Flop	BMC956	20p	18p	16p
Quad. 2-input Power	BMC958	12p	11p	10p
2/4-input Gate	BMC961	12p	11p	10p
3/3-input NAND Gate	BMC962	11p	10p	9p
3/3-input NAND Gate	BMC963	12p	11p	10p
Audio Amp. 3w. SL403D	£1.50	£1.40	£1.36	
Linear Op. Amp 709C	25p	20p	15p	
Decade Counter SN7490	65p	60p	55p	

### LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile  
16 pin type at 16p each } type

### BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

**B.P.I. Transistor Equivalents and Substitutes:** 40p  
This includes many thousands of British U.S.A., European and C.V. equivalents.

**The Iliffe Radio Valve & Transistor Data Book 9th Edition:** 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Postage and Packing 21p.  
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....

ADDRESS .....

MINIMUM ORDER 50p. CASH WITH ORDER.  
PLEASE. Add 10p post and packing per order.  
OVERSEAS ADD EXTRA FOR POSTAGE

**BI-PRE-PAK LTD** DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF  
TELEPHONE: SOUTHEND (0702) 46344

# SEW PANEL METERS

## CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

- LOW COST
- QUICK DELIVERY
- OVER 200 RANGES IN STOCK
- OTHER RANGES TO ORDER

**Type SW.100 100 x 80 mm.**

50μA	£3-80
50-0-50μA	£3-80
100μA	£3-80
100-0-100μA	£3-70
500μA	£3-50
1mA	£3-40
20V. D.C.	£3-40
50V. D.C.	£3-40
300V. D.C.	£3-40
1 amp. D.C.	£3-40



5 amp. D.C. £3-40  
300V. A.C. £3-40  
VU Meter £4-15

**Type SD.830 82.5mm x 110mm Fronts**

10mA	£2-50
50mA	£2-50
100mA	£2-50
500μA	£2-50
1 amp.	£2-50
1-0-1mA	£2-50
10 amp.	£2-50
5V. D.C.	£2-50
50-0-50μA	£2-70
100μA	£2-70
100-0-100μA	£2-70
200μA	£2-70
500μA	£2-55
1mA	£2-50
5mA	£2-50

500μA £2-75  
100-0-100μA £2-70  
200μA £2-70  
500μA £2-55  
1mA £2-50  
5mA £2-50

500μA £2-35  
1 amp. £2-35  
5 amp. £2-35  
10 amp. £2-35  
5V. D.C. £2-35  
20V. D.C. £2-35  
50V. D.C. £2-35  
300V. D.C. £2-35  
15V. A.C. £2-35  
300V. A.C. £2-40  
VU Meter £2-70

**Type SD.640 63.5mm x 85mm Fronts**

50μA	£2-60
50-0-50μA	£2-55
100μA	£2-55
100-0-100μA	£2-55
200μA	£2-55
500μA	£2-35
1mA	£2-35
5mA	£2-35
10mA	£2-35
50μA	£2-35
100μA	£2-35
100mA	£2-35

500μA £2-35  
1 amp. £2-35  
5 amp. £2-35  
10 amp. £2-35  
5V. D.C. £2-35  
20V. D.C. £2-35  
50V. D.C. £2-35  
300V. D.C. £2-35  
15V. A.C. £2-35  
300V. A.C. £2-40  
VU Meter £2-70

**Type SD.460 46mm x 59.5mm Fronts**

50μA	£2-40
50-0-50μA	£2-35
100μA	£2-35
100-0-100μA	£2-35
200μA	£2-35
500μA	£2-20
1mA	£2-15
5mA	£2-15
10mA	£2-15
50μA	£2-15
100μA	£2-15
100mA	£2-15

1 amp. £2-15  
5 amp. £2-15  
10 amp. £2-15  
5V. D.C. £2-15  
20V. D.C. £2-15  
50V. D.C. £2-15  
300V. D.C. £2-15  
15V. A.C. £2-30  
300V. A.C. £2-30  
VU Meter £2-55

**\*MOVING IRON—  
ALL OTHERS MOVING COIL**  
Please add postage

**Type MR.85P. 4 1/2in. x 4 1/2in. fronts**

50μA	£3-10
100μA	£3-10
500μA	£3-10
1 amp.	£3-10
5 amp.	£3-10
15 amp.	£3-10
30 amp.	£3-20
20V. D.C.	£3-10
50V. D.C.	£3-10
150V. D.C.	£3-10
300V. D.C.	£3-10
15V. A.C.	£3-10
300V. A.C.	£3-10
8 Meter 1mA	£3-15
VU Meter	£3-95

50μA £2-95  
50-0-50μA £3-40  
100μA £3-40  
100-0-100μA £3-30  
200μA £3-30  
500-0-500μA £3-10  
1mA £3-10  
1-0-1mA £3-10  
5mA £3-10  
10mA £3-10

**Type MR.52P. 2 1/2in. square fronts**

50μA	£3-40
50-0-50μA	£2-85
100μA	£2-85
100-0-100μA	£2-75
200μA	£2-55
1mA	£2-20
5mA	£2-20
10mA	£2-20
100μA	£2-20
500μA	£2-20
1 amp.	£2-20
5 amp.	£2-20

10V. D.C. £2-20  
20V. D.C. £2-20  
50V. D.C. £2-20  
300V. D.C. £2-20  
15V. A.C. £2-30  
300V. A.C. £2-30  
8 Meter 1mA £2-30  
VU Meter £2-30  
1 amp. A.C. £2-20  
5 amp. A.C. £2-20  
10 amp. A.C. £2-20  
20 amp. A.C. £2-20  
30 amp. A.C. £2-20

**Type MR.65P. 3 1/2in. x 3 1/2in. fronts**

50μA	£3-70
50-0-50μA	£3-00
100μA	£3-00
100-0-100μA	£2-90
200μA	£2-90
500μA	£2-95
1mA	£2-40
5mA	£2-40
10mA	£2-40
50μA	£2-40
100μA	£2-40
500μA	£2-40
1 amp.	£2-40
5 amp.	£2-40
10 amp.	£2-40
20 amp.	£2-40
30 amp.	£2-55
50 amp.	£2-75
5V. D.C.	£2-40

10V. D.C. £2-40  
20V. D.C. £2-40  
50V. D.C. £2-40  
150V. D.C. £2-40  
300V. D.C. £2-40  
15V. A.C. £2-55  
50V. A.C. £2-55  
150V. A.C. £2-55  
300V. A.C. £2-55  
8 Meter 1mA £2-60  
VU Meter £2-70  
1 amp. A.C. £2-40  
5 amp. A.C. £2-40  
10 amp. A.C. £2-40  
20 amp. A.C. £2-40  
30 amp. A.C. £2-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

**Type MR.38P. 1 2 1/2 3/2in. square fronts**


50μA	£2-30
50-0-50μA	£2-10
100μA	£2-10
100-0-100μA	£1-95
200μA	£1-95
500μA	£1-80
500-0-500μA	£1-75
1mA	£1-75
1-0-1mA	£1-75
2mA	£1-75
5mA	£1-75
10mA	£1-75
50μA	£1-75
100μA	£1-75
150μA	£1-75

5 amp. £1-85  
10V. D.C. £1-85  
20V. D.C. £1-85  
50V. D.C. £1-85  
300V. D.C. £1-85  
15V. A.C. £2-00  
300V. A.C. £2-00  
8 Meter 1mA £2-05  
VU Meter £2-50  
1 amp. A.C. £1-85  
5 amp. A.C. £1-85  
10 amp. A.C. £1-85  
20 amp. A.C. £1-85  
30 amp. A.C. £1-85

**Type MR.45P. 2in. square fronts**

50μA	£2-50
50-0-50μA	£2-30
100μA	£2-30
100-0-100μA	£2-05
200μA	£2-05
500μA	£1-95
500-0-500μA	£1-85
1mA	£1-85
5mA	£1-85
10mA	£1-85
50μA	£1-85
100μA	£1-85
500μA	£1-85
1 amp.	£1-85

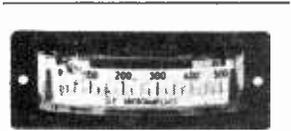5 amp. £1-85  
10V. D.C. £1-85  
20V. D.C. £1-85  
50V. D.C. £1-85  
300V. D.C. £1-85  
15V. A.C. £2-00  
300V. A.C. £2-00  
8 Meter 1mA £2-05  
VU Meter £2-50  
1 amp. A.C. £1-85  
5 amp. A.C. £1-85  
10 amp. A.C. £1-85  
20 amp. A.C. £1-85  
30 amp. A.C. £1-85



### "SEW" EDGWISE METERS

**Type PE.70. 3 1/2 3/2in. x 1 1/2 3/2in. x 1 1/2 3/2in. deep**

50μA	£3-40
50-0-50μA	£3-30
100μA	£3-30
100-0-100μA	£3-20
200μA	£3-20

500μA £3-05  
1mA £2-70  
300V. A.C. £2-70  
VU Meter £3-75

### "SEW" BAKELITE PANEL METERS

**Type MR.65. 3 1/2in. square fronts**

50μA	£3-85
50μA	£3-00
50-0-50μA	£2-60
100μA	£2-60
100-0-100μA	£2-50
200μA	£2-45
500-0-500μA	£2-35
1mA	£2-15
1-0-1mA	£2-15
5mA	£2-15
10mA	£2-15
50μA	£2-15
100μA	£2-15
500μA	£2-15
1 amp.	£2-15

5 amp. D.C. £2-85  
300V. A.C. £2-85  
VU Meter £3-70

**Type S-80 80 mm. square fronts**

50μA	£3-50
50-0-50μA	£3-40
100μA	£3-40
100-0-100μA	£3-30
200μA	£3-05
500μA	£2-85
20V. D.C.	£2-85
50V. D.C.	£2-85
300V. D.C.	£2-85
1 amp. D.C.	£2-85

5 amp. D.C. £2-85  
300V. A.C. £2-85  
VU Meter £3-70

### "SEW" EDUCATIONAL METERS

**Type ED.107. Size overall 100mm x 90mm x 108mm**

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	£5-50
100μA	£5-10
1mA	£4-85
50-0-50μA	£5-10
1-0-1mA	£4-85
1A d.c.	£4-85
5A d.c.	£4-85
10V d.c.	£4-85

20V. d.c. £4-85  
50V. d.c. £4-85  
300V. d.c. £4-85  
Dual range  
500mA/3A d.c. £5-10  
5V/50V d.c. £5-10

## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. 1in. dia. shafts. Bulk quantities available.

**25 WATT.** 10/25/50/100/250/500/1000/2500 or 5000 ohms. 90p. P. & P 10p

**100 WATT.** 1/5/10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.15 P. & P. 15p.

### "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

<b>5-260 General Purpose Bench Mounting</b>		<b>S-280B Panel Mounting</b>	
1 Amp	£7-00	1 Amp	£7-00
2.5 Amp	£8-05	2.5 Amp	£8-05
5 Amp	£11-75	Please add postage	
8 Amp	£15-90	ALL MODELS	
10 Amp	£22-50	INPUT 230 V 50/60 CYCLES	
12 Amp	£28-60	OUTPUT VARIABLE 0-260 VOLTS	
20 Amp	£40-00	Special discounts for quantity	
25 Amp	£58-00		
40 Amp	£82-50		

**AUTO TRANSFORMERS**  
0/115/250V. Step up or step down. Fully shrouded.

80 W	£2-10	P. & P. 18p
150 W	£2-70	P. & P. 18p
300 W	£3-60	P. & P. 23p
500 W	£5-25	P. & P. 33p
1000 W	£7-50	P. & P. 38p
1500 W	£10-20	P. & P. 43p
2250 W	£17-25	P. & P. 50p
5000 W	£35-00	P. & P. £1

**MCA.220 AUTOMATIC VOLTAGE STABILISER**

Input 88 125 VAC or 175 250VAC. Output 120V AC, or 240 VAC. 200 VA rating. £11-97. carr. 50p.

**230 VOLT A.C. 50 CYCLES RELAYS**

Brand new. 5 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

**BH.001 HEAD SET AND BOOM MICROPHONE**

Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. £4 62. P. & P. 15p

**240° Wide Angle 1mA Meters**

MW 1-6 60mm square £3 97  
MW 1-8 80mm square £4 97  
P. & P. extra

**RP214 REGULATED POWER SUPPLY**

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V AC. Size 185 x 85 x 105mm. £8 97 P. & P. 25p.

**PS.200 REGULATED P.S.U.**

Solid state. Variable output 5-20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Input 220/240 V. A.C. Size 7 1/2" x 5 1/2" x 3 1/2". £14-97. P. & P. 25p.

**PS.1000B REGULATED POWER SUPPLY**

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2". £11-97. P. & P. 25p.

**LB4 TRANSISTOR TESTER**

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5v batteries. Complete with all instructions, etc. £4-60. P. & P. 20p.

**LB3 TRANSISTOR TESTER**

Tests IGO and B. PNP/NPN Operates from 6 battery Complete with all instructions, etc. £3 95 P. & P. 20p.

**HOMER INTERCOMS**

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station, £2 97. 3 Station £5 25. P. & P. 15p  
4 Station £8 62. P. & P. 17p.

SEND SAE FOR LIST OF SEMI CONDUCTORS & VALVES

**230V. 240V SMITHS SYNCHRONOUS GEARED MOTORS**

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH ACW; 20 RPH CW; 2 RPH ACW; 30 RPH CW; 50p each Post 12p

**G. W. SMITH & CO. (RADIO) LTD**

Also see next three pages

# MULTIMETERS for EVERY purpose!



**TS60 POCKET MULTIMETER**  
High-precision at low cost. Ranges: D.C. 15V, 150V, 1,000V (10,000 ohms), A.C. 15V, 150V, 100V (1,000 ohms), D.C. Current 150mA. Resistance 100K ohms. £1.85. Post 15p.

**MODEL 1092 TESTMETER**  
3,000 O.P.V.  
0/3/15/150/300/1200 V.  
D.C. 0/6/30/300/300 MA  
0/10K/1 meg Ω  
Decibels -10 to +16db.  
£2.75 each +15p P. & P.




**HIKOKI MODEL 720X**  
20,000 O.P.V.  
Overload protection  
5/25/100/500/1000 V D.C.  
10/50/250/1000 V A.C.  
50μA/250mA, 20K/1/2 meg Ω  
-5 to +62db.  
£4.97. P. & P. 15p.


**HIKOKI MODEL 730X**  
30,000 O.P.V. Overload protection.  
6/30/60/300/600/1200 V D.C. 12/60/120/600/1200 V A.C. 60μA/30 mA/300 mA, 2K/200K/2 megohms. -1 to +63db.  
£6.50. P. & P. 15p.



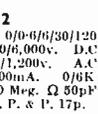
**MODEL TE-12**  
20,000 O.P.V. 0/0-6/1/30/120/600/1200 P.P.V. 0/0.000/6.000V. D.C. 0/6/30/120/600/1200 V A.C. 0/60μA/6/60/600mA. 0/1K/600K/6Meg/60 Meg. Ω 50pF/0-2mF. £5.97. P. & P. 17p.



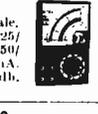
**MODEL TE-200**  
20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50μA/250mA/0/60K/6 meg Ω -20 to +62db.  
£3.95. P. & P. 15p.



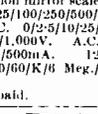**MODEL 500**  
30,000 O.P.V. with overload protection mirror scale 0/5/2/5/10/25/100/250/500/1,000V. D.C. 0/2/5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω.  
£5.97. Post paid.



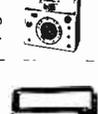**HIKOKI MODEL 750X**  
50,000 o.p.v. 43 ranges 0-3 to 1,200V D.C. 0-3 to 1,200A. A.C. 0-300μA/300mA. 0-3K/30 meg ohms. 10 to +17db.  
£3.97. Post 20p.



**HT10084 MULTI-METER**  
Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection.  
0/5/2/5/10/50/250/500/1000 V D.C.  
0/2/5/10/50/250/1000 V A.C.  
0/10/250μA/2/5/25/250 MA/10 Amp. D.C.  
10 Amp A.C. 0/20K/200K/2 MEG/20 MEG. -20 to +62db.  
£12.50. P. & P. 25p.



**370 WTR MULTI-METER**  
Features A.C. current ranges. 20,000 o.p.v. 0/5/2/5/10/50/250/500 1000 V. D.C. 0/2/5/10/50/250/500/1000V A.C. 0/50μA/1/10/100mA/1/10 Amp. D.C. 0/100mA/1/10 Amp A.C. 0/5K/50K/500K/5 MEG/50 MEG. -20 to +62db.  
£15. P. & P. 25p.




**RUSSIAN 22 RANGE MULTIMETER**  
Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/1000V A.C. DC Current 100mA/1/10/100mA/A. Resistance 300 ohms/3/30/300K/3m Ω. Complete with batteries, test leads, instructions, sturdy steel carrying case. OUB PRICE £5.97. P. & P. 25p.




**ROUND SCALE TYPE PENCIL TESTER MODEL T.S.68**  
Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY £1.97 P. & P. 15p.

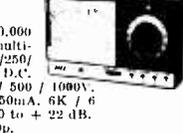
**LT601 MULTIMETER**  
New style 20,000 o.p.v. pocket multi-meter. 5/25/50/250/500/2500 V. D.C. 10/50/100/500/1000V. A.C. 50μA/250mA/6K/6 meg Ω. -20 to +22 db.  
£3.75. Post 20p.



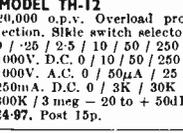
**MODEL TH-12**  
20,000 o.p.v. Overload protection. Slide switch selector 0/2/5/25/10/50/250/1000V. D.C. 0/10/50/250/1000V. A.C. 0/50μA/25/250mA. D.C. 0/3K/30K/300K/3 meg -20 to +50dB  
£4.97. Post 15p.



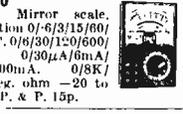
**MODEL TE-300**  
20,000 O.P.V. Mirror scale, overload protection 0/6/3/15/100/300/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30μA/60μA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm -20 to +63 db. £5.97. P. & P. 15p.



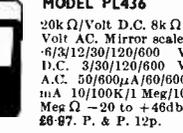**MODEL PL436**  
20K Ω/Volt D.C. 8k Ω/Volt AC. Mirror scale. 6/3/12/30/120/600 V D.C. 3/30/120/600 V A.C. 50/600μA/60/600mA 10/100K/1 Meg/10 Meg Ω -20 to +46db.  
£8.97. P. & P. 12p.



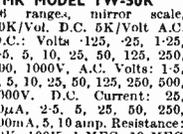
**TMK MODEL TW-50K**  
30 ranges, mirror scale. 50K/Volt. D.C. 5K/Volt. A.C. D.C. Volts: 125, 25, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50mA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +81.5db  
£8.50. P. & P. 17p.




**MODEL K278A**  
Tilt stand suspension. Overload protection. Polarity reversing switch. 30,000 o.p.v. 0/5/2/5/15/50/250/500/1000/2500V. D.C. 0/15/50/150/500/1000V. A.C. 0/50μA/5/50/150/500mA/5A D.C. 0/3K/300K/3 meg. £8.95. Post 20p.



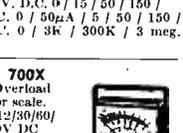**HIKOKI MODEL 700X**  
100,000 O.P.V. Overload protection. Mirror scale. 3/6/1/2/1/5/3/6/12/30/60/120/300/600/1200V DC 1/5/3/6/12/30/60/150/300/600/1200 V A.C. 15/30μA/3/30/60/150/300mA 0/1/2 AMP. DC. 2K/200K/2 Meg/20 Meg ohm -20 to +63db. £13.50. P. & P. 20p.



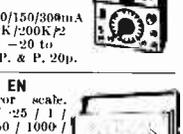**MODEL C-7080 EN**  
Giant 6" mirror scale. 20,000 o.p.v. 0/25/1/10/50/10/50/250/1000/5000V. D.C. 0/2/5/10/50/250/1000/5000V. A.C. 0/250/1000/5000V. 500mA/1/10/100/500mA/10 amp. D.C. 0/2K/200K/2 meg -20 to +50 db.  
£13.95. Post 35p.



**U4312 MULTIMETER**  
Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/3/1/5/7/5/30/60/150/300/600/900 VDC and 75mV. 500V. D.C. 0/1/2/5/10/50/250/1000/5000V. A.C. 0/300μA/1/5/6/15/60/150/600mA/1/5/6 AMP. D.C. 0/1/5/6/15/60/150/600MA/1/5/6 AMP. A.C. 0/200Ω/3K/30K Ω. Accuracy DC 1%. AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9.50 plus P. & P. 25p.



# Selected TEST EQUIPMENT

**FTC-401 TRANSISTOR TESTER**  
Full capabilities for measuring A, B and I.C.O. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £7.50. Post 20p.

**TE-16A TRANSISTORISED SIGNAL GENERATOR**  
5 ranges 400Hz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. £7.97. Post 25p.

**Model 5-100TR MULTIMETER TRANSISTOR TESTER**  
100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC. 0/6/30/120/600. V AC. 0/12/600μA/12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +45db. 0-0.1-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13.50. P/P 25p.

**TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE**  
A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω 11-1 meg Ω 6 ranges ± 1% L.I. H. 111 6 ranges ± 2%. TURNS RATIO 1: 1/100-1: 1/100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2 in. £20. P. & P. 25p.

**MODEL 449A IN CIRCUIT TRANSISTOR TESTER**  
Checks true A.C. beta in/out. Checks Ico. Checks diodes in/out. Checks SCR, etc. Beta HI 10 - 500, LO 2 - 50. Ico 0-3000μA. 220/240 V A.C. operation. £17.50. Post 25p.

**MODEL TE.15 GRID DIP METER**  
Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440Kc/s-280Mc/s in 6 coils. 500μA Meter. 9V battery operation. Size 180 x 80 x 40mm. £12.50. Post 20p.

**TE-20D RF SIGNAL GENERATOR**  
Accurate wide range signal generator covering 120 Kcps 500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions £15. Carr. 37p. Size 140 x 215 x 170 mm.

**BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR**  
Sine 18 x 200,000 Hz. Square 18 x 50,000 Hz. Output max. 10 dBm (10 K ohms) Operation internal batteries Attractive 2-tone case 7 1/2 x 5 x 2 1/2 in. Price £17.50. Carr. 17p.

**MODEL L-55 FET V.O.M.**  
Input impedance 10 meg ohms. 0/3/1/2/6/30/120/600V. D.C. 0/3/12/60/120/600V. A.C. 0/120μA/120mA D.C. 0/1K/100K/10 meg Ω/100 meg ohms £15.97. Post 15p.

**MODEL MG-100 SINE SQUARE WAVE AUDIO GENERATOR**  
Range 19-220,000Hz Sine Wave 19-100,000 Hz Square Wave. Output Sine or Square wave 10v. P. to P. Size 180 x 90 x 90mm. Operation 220/240V. A.C. £17.50. Post 37p.

**CI-5 PULSE OSCILLOSCOPE**  
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz V RMS/100KHz. V RMS/mm. -3/25; Preset triggered sweep 1-3,000usec.; free running 20-200,000Hz in five ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V. AC operation. £39.00. Carr. paid.

**MODEL AT201 DECADE ATTENUATOR**  
Frequency range 0-200KHz. Attenuator 0-111db. 0.1db step. Impedance 600 ohms. Max. Power 30dbm. Size 180 x 90 x 55mm. £12.50. Post 37p.

**TO-3 PORTABLE OSCILLOSCOPE**  
3in. tube, Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2lb. 220/240V. A.C. Supplied brand new with handbook. £40.00. Carr. 50p.

**TE-65 VALVE VOLTMETER**  
28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional probes available: R.F. £212; H.V. £25.50.


**RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE**  
5 mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in. x 4in. C.R.T. Calibrated triggered sweep from 2 usec. to 100 milli-sec. per cm. Free running time base 50 c/s/1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual £87. Carr. Paid.

**MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER**  
Sensitivity 330 ohms/Volt AC and DC. Accuracy 5% D.C. 1% AC. Scale length 165mm. 0/300/750μA/1/5/3/7.5/15/30/75/150/300/750mA/1/5/3/7.5AMP DC 0/2/5/7.5/15/30/75/150/300/750mA/1/5/3/7.5 AMP AC 0/75/150/300/750mV/1/5/3/7.5/15/30/75/150/300/750V DC 0/750mV/1/5/3/7.5/15/30/75/150/300/750V AC. Attenuation cut out. Supplied complete with test leads, manual and test certificates. £49.00. Post 50p.

**G. W. SMITH & CO (RADIO) LTD.**  
Also see opposite page and next two pages
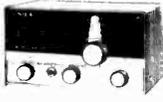
### UNR-30 RECEIVER

4 Bands covering 550Kc/s - 30Mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. £15-75. Carr. 37p.



### UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550Kc/s-30Mc/s. FET 8 Meter. Variable BFO for RSB, Built-in Speaker. Bandspread, Sensitivity Control, 220/240V. A.C. or 12V. D.C. 12 1/2" x 4 1/2" x 7 1/2". Brand new with instructions. £25. Carr. 37p.

### SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and 55 to 30 MHz. Illuminated side rule dial. Bandspread. Aerial tuning BFO. AVC. ANL. 'S' meter. AM/CW/8SB. Integrated speaker and phone socket. Operation 220/240V AC or 12V DC. Size 226 x 266 x 150 mm. Complete with instructions and circuit. £32-50. Carr. 50p.

### LAFAYETTE HA-600 SOLID STATE RECEIVER



General coverage 150-400Kc/s. 550 Kc/s-30Mc/s. FET front end. 2 mech. filters. product detector. variable B.F.O. 8 meter. Meter. Bandspread. R.F. Gain. 12 1/2" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. £50. Carr. 50p.



### TRIO 9RS5DS COMMUNICATION RECEIVER

4 band covering 550Kc/s. to 30 Mc/s. continuous and 4/8 ohm output and phone jack. 8SB-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. 1F frequency 455 Kc/s. audio output 1.5w. Variable HF and AF gain controls 115/250V. A.C. Size: 7 1/2" x 13" x 10" with instruction manual. £49-50. Carr. Paid.

### EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.  
Model 450. 13" x 8" with twin tweeter/crossover. 52-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3-62 each. P. & P. 25p.

### HONEYWELL DIGITAL VOLTMETER VT.100



Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt. current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2. ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2" x 2 1/2" x 1 1/2". AVAILABLE BRAND NEW AND FULLY GUARANTEED. £35-50. Carr. 50p.

## SINCLAIR IC-12




List Price £2-98

OUR PRICE £1-80

P. & P. 10p

### SINCLAIR EQUIPMENT

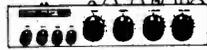

Project 60 Package. 2 x Z30 amplifier, stereo 60 pre-amp. P25 power supply. £15-95 Carr. 37p. Or with P270 power supply £18-00 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp. P24 power supply. £20-85. Carr. 37p. Transformer for P28. £2-97 extra. Add to any of the above £4-45 for active filter unit and £13-00 for pair of Q16 speakers. All other Sinclair products in stock. 2000 Amp £21-95 Carr. 37p. 3000 Amp £28-50 Carr. 37p. Nosterle Amp £43-95. Carr. 37p. IC12 £1-80 p. & p. 10p. NEW PROJECT 605 - £20-97. Carr. 37p.

### SPECIAL OFFER! GOODMAN'S AXIOM 301

Hi Fi 12" 20 watt twin cone full range speaker. 30-16,000 Hz. 16,500 gauss. 8 ohm impedance. Brand new and boxed. (List price £21.72) OUR PRICE £12-50 each. Carr. 50p.



### EA.41 REVERBERATION AMPLIFIER

Self contained, transistorized, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2" x 8 x 4 1/2". £5-97. P. & P. 13p.



### SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo hornkabel II speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead. £12-95 pr. Carr. 50p.



### HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5mV/100mV. Output 50mV. £5-97. P. & P. 15p.



### SPECIAL PURCHASE! NEAT G30J STATIC BALANCE PICK-UP ARMS



Identical specification to NEAT G30 arm but with two-tone chrome and black finish. Complete with head shell, pick up rest and plug in phono leads.

### BRAND NEW—FULLY GUARANTEED ONLY £8-95. P. & P. 25p.

### ARF-300 AF/RF Signal Generator



All Transistorised, compact, fully portable. AF sine wave 15 Hz to 220 KHz. AF square wave 15 Hz to 100 KHz. Output sine/square 10V. P.P. RF 100KHz to 200 MHz. Output 1V. maximum. Operation 220/240V. A.C. Complete with instructions and leads. £29-85. Post 50p.

## AKAI BARGAINS

SUPER MONEY SAVING OFFERS—  
BUY NOW WHILE STOCKS LAST!  
BRAND NEW AND FULLY GUARANTEED



- |                                |         |                          |         |
|--------------------------------|---------|--------------------------|---------|
| 1721 Tape Rec.                 | £73-95  | GXC40 Cassette Rec.      | £82-95  |
| X5000 Tape Rec.                | £98-85  | GXC40D Cassette Deck     | £67-95  |
| GX370 Tape Deck                | £256-85 | GXC40T Cassette/Receiver | £123-95 |
| 4000DR Tape Deck               | £75-85  | GXC45D Cassette Deck     | £89-95  |
| 4000DS Dust Cover              | £4-75   | GXC46D Cassette Deck     | £103-80 |
| X200 Tape Deck                 | £99-95  | GXC45 Cassette/Recorder  | £115-95 |
| X201D Tape Deck                | £132-95 | GXC46D Cassette Deck     | £111-25 |
| X221D Tape Deck                | £189-95 | GXC45D Cassette Deck     | £110-95 |
| GX220D Tape Deck               | £148-50 | CR35D Cassette Deck      | £59-50  |
| GX260D Tape Deck               | £249-40 | AA6300 Receiver          | £79-95  |
| X1810D Tape/8 track Deck       | £189-95 | AA8030 Receiver          | £106-95 |
| GX1900D Tape/Cass Deck         | £177-95 | AA8080 Receiver          | £144-95 |
| X2000SD Tape/Cass/8 Track Rec. | £223-80 | AA8500 Receiver          | £178-00 |
| CR81 8 track Rec.              | £80-95  | ADM11 Microphones (Pair) | £7-50   |
| CR81D 8 track Rec.             | £85-95  |                          |         |
| CR81T 8 track/Receiver         | £115-90 |                          |         |
| CR80DS 8-track                 | £121-95 |                          |         |
| CR8088 8 track system          | £145-00 |                          |         |

(Carrage 50p extra. (Receivers & Decks 75p)

### DOLBY SYSTEM NOISE REDUCTION UNIT



Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 15kHz ± 1dB. 190KHz - 35dB. Size 15 1/2" x 9" x 3 1/2". AC 200/250V. OUR PRICE £32-50 Carr. 50p.

### GENUIE BARGAIN!




KOSS SP.3XC STEREO HEADPHONES  
Response 10-18,000Hz.  
Impedance 4-6 ohms.  
Brand new. Boxed & fully guaranteed.  
(List £9.50).  
OUR PRICE £6.50.  
P. & P. 25p.

### HOSIDEN DH-025 STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-20,000 cps. Complete with lead and plug. ONLY £8-87. P. & P. 12p.

### TAPE CASSETTES

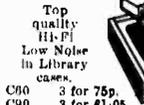


Top quality Hi-Fi Low Noise in Library cases.  
C90 3 for 75p. 10 for £8-85  
C90 3 for £1-05 10 for £8-80  
C120 3 for £1-35 10 for £4-80  
Tape Head Cleaner 30p each.  
P. & P. 10p extra.

### 1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off switch, stereo headphone sockets. 6" x 4" x 2 1/2". £8-95. P. & P. 15p.

### MP7 MIXER PREAMPLIFIER

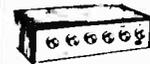

5 microphone inputs, each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3" Inputs Mics: 3 x 3mV 50K ± 3mV 600 ohm. Phono input 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8-97. P. & P. 20p.

### TE-1035 STEREO HEADPHONES



Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable headband. 8 ohm impedance 26-18,000 Hz. With lead and stereo jack plug. ONLY £1-97. P. & P. 12p.

## NEW GARRARD MODULES



Popular range of Garrard decks with 8ure cartridge fitted in deluxe plinth with 8 pins  
SP25 III Module/M75-6 £23-50  
AP26 Module/M75-6 £33-90  
AP96 Module/M75-6 £38-75  
Toro 1008 Module/M93E £52-80  
Carr. 50p extra any item.

### HOSIDEN DH-085 DE-LUXE STEREO HEADPHONES



Features unique mechanical 2 way units and fitted adjustable lever, controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug £7-97. P. & P. 12p.

### SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES




20-20,000Hz. 8-16 ohm. (List £9-95). OUR PRICE £8-75. P. & P. 25p.

### TRANSISTORISED FM TUNER



A TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 1/2". 3 I.F. stages. Double tuned discriminator. Ample output to feed most 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6-37p. P. & P. 12p. Stereo multiplex adaptors £4-97.
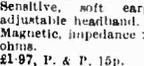
### TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1-97. P. & P. 15p.

### HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases.  
2 channel £52-50 Pair.  
300 mW 300-50p.  
3 channel £79-50 Pair.  
2 watt. Post 50p.

G. W. SMITH & CO (RADIO) LTD.  
Also see previous pages and opposite page

# FANTASTIC OFFER!

## NIKKO TRM 50 STEREO AMPLIFIER



17 + 17 watts rms stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and Tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13" x 9 1/2" x 3 1/2". Unrepeatable offer—limited stocks!

List price £59.50  
OUR PRICE  
**£39.95**  
Carriage 50p

## NIKKO TRM.50 SYSTEM



NIKKO TRM50 17 + 17 watt rms. stereo amplifier, BSR MP60, plinth & cover. Goldring G800 cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE **£104.90** Carr. and Ins. £1.50

## WHARFEDALE LINTON SYSTEM



Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE **£106.00** Carr. and Ins. £1.25  
LINTON RECEIVER SYSTEM **£155.00**, Carr. & Ins. £1.25.

## LEAK DELTA 30 SYSTEM



Leak Delta 30 stereo amplifier, Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE **£123.50** Carr. and Ins. £1.50

## TELETON SAQ206B SYSTEM



Teleton SAQ206B 8 + 8 watt Amplifier, BSR MP60, plinth & cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£54.40** Carr. £1.50  
Amplifier only, £22.95. Carr. 50p.

## AUDIOTRONIC ACR.3500 MW/LW CAR RADIO



Fully transistorised, dual waveband. Size 6 1/2" x 4 1/2" x 2". 12v. D.C. Neg. or Pos. earth. Complete with fixing kit, speaker and leads. ONLY £7.50, Post 20p.

## SUPER BARGAIN! AUDIOTRONIC ACP.8 8-TRACK CAR STEREO TAPE PLAYER



Tone, volume and balance controls. Track selector. Complete with matched pair of stereo speakers, connections and fittings. ONLY £15.95, Post 30p (illus is example only).

## BH.001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal for language teaching, communications. Headphone Imp. 15 ohms. Microphone Imp 200 ohms. £4.82, P. & P. 15p.

# HI-FI EQUIPMENT


## SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR FULL DISCOUNT PRICE LISTS AND PACKAGE OFFERS!


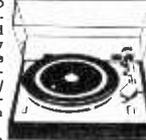
## SAVE £££'s PHILIPS GA308 TRANSCRIPTION TURNTABLE

2 speeds 33 1/3 and 45 rpm. Lightweight tubular counterbalanced arm. Belt driven low speed synchronous motor. Viscous damped pick up lift/lower device. Complete with teak plinth and hinged cover. GA308 less cartridge (List £36.55).  
OUR PRICE **£24.50**, P. & P. 50p.  
GA308 PU with GP400 stereo magnetic cartridge (List Price £47.65)  
OUR PRICE **£39.95** P. & P. 50p.  
LIMITED NUMBER ONLY!



## ROTEL BARGAINS!

All brand new and guaranteed



RA210 Amp ... £22.50  
RA310 Amp ... £34.95  
RA610 Amp ... £48.25  
RX150 Receiver ... £45.95  
RX200 Receiver ... £57.50  
RX400 Receiver ... £70.95  
P. & P. 50p extra any item.

## WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet, 20 watts rms. Brand new £1.50. Carr. 37p.



## HOMER INTERCOMS

Ideal for home office, stores, factories, etc. Supplied complete with batteries, cable and tree instructions.

2 Station, £2.97, 3 Station £5.25, P. & P. 15p  
4 Station £6.82, P. & P. 17p.

CREDIT TERMS FOR CALLERS ACCESS & BARCLAYCARD WELCOME

# V.A.T. INFORMATION

All mail orders received on or after April 1st, will be subject to Value Added Tax.  
**THIS MUST BE ADDED TO THE TOTAL VALUE OF GOODS ORDERED (INCLUDING POSTAGE/CARRIAGE) AND ENCLOSED WITH ORDER.**

## RECORD DECKS (P. & P. 50p)

B.S.R. McDONALD  
C114 Mini £4.97  
C129 Mono £5.50  
C137 £8.95  
MP60 £9.50  
610 £12.95  
810 £31.25  
210/TPD3 £8.75  
MP60/G800 £12.95  
MP60/TPD1 £16.05  
MP60/TPD1/G800 £19.50  
MP60/TPD2 £14.35  
610/TPD1 £18.95  
510/TPD1 £17.95  
HT70 £13.99  
HT70/G800 £17.25  
HT70/TPD1 £20.35  
HT70/TPD1/G800 £23.90  
810 Plinth/Cover £9.25



GOLDRING  
GL69/2 £18.50  
GL72 £20.95  
GL72/P £27.50  
Plinth 69/72 £7.02  
LID 72 £8.25  
GL75 £26.95  
GL75P £35.25  
Plinth 75 £7.35  
LID 75 £8.90  
G99 £19.25  
GL85P/C £26.95  
G101P/C £20.50

HACKER  
GP45/50 £49.50  
T45 Table £4.95  
LEAK  
Delta Turntable £52.50

MICRO-SEIKI  
MR111 £29.50  
MR111 Plinth & Cover £9.50

GARRARD  
2025 T/C Stereo £8.50  
SP25 III/Acos £11.95  
GP104 Ceramic £10.25  
SP25 III £10.25  
SP25 III/M75-6 £15.95

PHILIPS  
GA105 £18.95  
GA160 £27.00  
GA308 Teak £24.50  
GA308PU Teak £29.95  
GA212 £26.75

PIONEER  
PL12D £34.50  
PL15C £51.35  
PLA35 £82.65  
PL50 £11.85  
PL41D £118.50  
PL61 £119.95

THORENS  
TD125 II £66.50  
TD125AB II £99.95  
TX25 £8.95  
TD160C £56.95  
TD150A II £35.95  
TD150AB II £39.95

WHARFEDALE  
Linton Turntable £29.95

PLINTHS & COVERS (P. & P. 50p)  
Budget SP25, etc. £3.20  
Budget AP76/Zero 100S £4.50  
Budget B.S.R. £3.25  
SME 2000 System £34.50

## RECORD DECK PACKAGES (P. & P. 50p)

Decks supplied with stereo cartridge ready wired in plinth with cover.



GARRARD  
2025TC/9TAHCD £12.75  
SP2 III/G800 £18.50  
SP25 III/M75-6 £18.50  
SP25 III/M44-7 £19.75  
SP25 III/M44-E £20.95  
SP25 III/M55E £22.49  
AP76/G800 £27.95  
AP76/M75-6 £20.25  
AP76/M5E £20.50  
AP76/M75EJ £28.50  
AP76/G800E £20.75  
AP76/M4E £20.50  
AP76/M75ED £28.50

B.S.R. McDONALD  
MP60/G800 £17.50  
MP60/M44-E £18.95  
MP60/M44-E £19.95

GOLDRING  
GL75/G800 £30.50  
GL75/G800E £42.50

Tel: 01-837 2232  
Tel: 01-836 3715  
Tel: 01-580 0670  
Tel: 01-437 8204  
Tel: 01-437 3155  
Tel: 01-262 0387

# G.W. SMITH & CO (Radio) LTD

Personal Callers Welcome - All Branches Open 9-6 Mon. to Sat.

10 TOTTENHAM CT. RD. LONDON, W1  
27 TOTTENHAM CT. RD. LONDON, W1  
257/258 TOTTENHAM CT. RD. LONDON, W1  
3 LISLE STREET, LONDON, W.C.2  
34 LIBLE STREET, LONDON, W.C.2  
311 EDWARE ROAD, LONDON, W.2

All Mail Orders to 11-12, Paddington Green, London, W2  
Tel: 01-262 6562

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

# CUSTOM BUILT TO FIT YOUR SHACK AND YOUR POCKET!

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

The Space Age WORLD RECORD award winning 7' 6" long All Band JOYSTICK VFA Antenna—JOYMATCH A.T.U.—TRIO RECEIVER or TRANSCEIVER—Matching HEADPHONES—A COMPLETE STATION IN ONE COMPACT PACKAGE—THE FLAT DWELLER'S DREAM!

1972 JOYSTICK VFA £11.40 (A); JOYMATCH ATU 111 ★ or 111A £11.40 (B); JOYMATCH ATU LO-Z500 £16.45 (C).

**COMMUNICATIONS HEADPHONES £2.60 (D)**  
(All including postage, packing, accessories & insurance.)

**PARTRIDGE PACKAGE No. 1**  
9R59DS receiver .. £49.50  
\* Items (A); (B); (D) above .. £11.00  
Complete Gen. Coverage Station .. £60.50

**PARTRIDGE PACKAGE No. 2**  
JR310 receiver .. £75.00  
\* Items (A); (B); (D) above .. £7.00  
Complete Amateur RX Station .. £82.00

**PARTRIDGE PACKAGE No. 3**  
JR599 receiver .. £185.00  
\* Items (A); (B); (D) above .. FREE  
Complete Amateur RX Station .. £185.00

**PARTRIDGE PACKAGE No. 4**  
TS/PS515 Transceiver 180W .. £210.00  
\* Items (A); (C); (D) above .. FREE  
Complete TX-RX Station .. £210.00

**BARCLAYCARD — ACCESS — PERSONAL LOANS !!**  
ALSO: SP5D SPKR. £4.50; 2M CAR TRANSCIEVER TR7100 £99.50; 2M PERSONAL TRANSCIEVER TR2200 £62.50; OA2 MAINS STABILISER 67p.

**NEW:** World-wide reception on the amazing "DX—CRYSTAL SET" £1.75 (+ 25p) including unique aerial.

## PARTRIDGE BUDGET LINE—

**ARTIFICIAL EARTH—SOLVES YOUR EARTH PROBLEMS £4.80; AERIAL BANDSWITCH—TUNED AERIAL £4.80; A.T.U. KIT—FULL COVERAGE TX/RECEIVER £4.80; ASSEMBLED £5.80.**

(All including Postage, Packing, Accessories & Insurance.)  
Send 3p stamp for full illustrated details of Partridge Products.  
TRIO brochures (state which) 3p stamp extra.

**ADD V.A.T. TO ALL QUOTES FROM APRIL 1st**  
CARRIAGE & INSURANCE EXTRA OVERSEAS.

**BOX 5**  
**PARTRIDGE ELECTRONICS LTD.**  
**BROADSTAIRS, KENT**

Phone: 0843 62535 or 62839 cheap periods.

Picks up ALL THE USUAL BBC Programmes \*All the new local radio stations \*Continental \*World-wide transmissions \*Pop Pirates \*Radio Hams \*Aircraft \*Shipping \*Police \*Taxis \*R.A.C. \*A.A. \*Fire Brigade \*T.V. Sound \*Ambulances and 1,000s more.

**THE BEST PORTABLE RADIO EVER MADE!** We think so. As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE V.H.F. BANDS. Listen to your favourite B.B.C. programme and then—at the flick of a switch—tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the trawlers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, A.A., R.A.C. and 100s of others R.T. mobiles! Extensive shortwave coverage can give you Australia, Pakistan, North America, Far East, etc., etc. World famous manufacturer. **FULL 3-YEAR WRITTEN GUARANTEE.** Beautifully finished in Teak Wood and Stainless Steel. Portable 12in x 9in x 4in, using standard batteries—or can be plugged directly into mains. 14 transistors 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external telescopic antennae—with sockets for additional aeriols, or car aeriols. Automatic Drift-Free Reception. Sliding tone control. Hi-Fidelity earphone for private listening, local DX switch. **FREQUENCIES:** Long W 160-350Kcs. Medium W 540-1605 Kcs. Marine 1.6-4 Mcs Short W 1.37-9 Mcs. Short W 2.9-22 Mcs. F.M. (V.H.F.) 88-108 Mcs. Aircraft (VHF) 108-136 Mcs. Public Service (VHF) 148-174 Mcs.

**NOTE:**—The Ministry of Posts & Telecommunications state a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

Send 5p stamp for Discount Brochure of unusual Frequency Radios **SCIENTIFIC & TECHNICAL (PW4)** Towerfield Trading Estate, Southend, Essex

Baker Loudspeakers full range			
Regent 12in	£8	Superb 12in	£15
Major 12in	£9	Auditorium 12in	£14
Deluxe 12in	£10	Auditorium 15in	£20
		Group 25 12in	£8
		Group 35 12in	£9
		Group 50 15in	£20

Baker Loudspeaker Co., Bensham Manor Passage, Thornton Heath, Surrey. Tel. 01-684 1665

**AUTOMATIC EMERGENCY SUPPLY**  
250v 50Hz—150 watt Inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit—£16.95 + 80p P. & P.

**OTHER INVERTERS AVAILABLE IN KIT FORM**  
150 Watt—£13.50 + 60p P. & P.      75 Watt—£7.80 + 60p P. & P.  
300 Watt—£17.90 + 85p P. & P.      40 Watt—£5.20 + 40p P. & P.  
25 Watt—£2.60 + 20p P. & P.

All above operate from 12v. battery and give 250v.—50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

**SPECIAL OFFER**  
12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc.      12 inch—8 watt—£3.40 post paid.  
21 inch—13 watt—£4.20 post paid. Large discounts available for quantities.

**TEXAN AMPLIFIER**  
Fibre glass P.C. board—£2.00 + 10p P. & P.  
Transformer—£4.00 + 30p P. & P.  
Other components including Teak Cabinet—£24.00 + Postage.

**ASTRO ELECTRONICS**  
6, BARNES ROAD, CHESTERFIELD, DERBYSHIRE



**BARGAIN PARCELS** 14lb at £1.45 plus 32½p p.p.; 28lb at £2.75 plus 52½p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res, Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££s. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 09J 4½in. dia. Length 15in. Also 7BP7. All unused as new. Price £1.40 post paid.

**NEW HEAVY COAX CABLE** dia. ¼" 70 ohms approx. 50ft. lengths £1.40. p. & p. 30p. 100 ft. lengths £2.70. p. & p. 50p.

**AERIALS.** New Condition Whip Type, 4ft. 20p; 11ft. 75p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 62½p. p. & p. 25p.

**CRYSTALS AS NEW.** Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s. 50p each plus 8p p.p.

**OUR SELECTION OF 6-Ex. Equ. METERS** consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2 P. & P. 25p. minimum order of six.

**ANY HEIGHT AERIAL TUBULAR SECTIONS** ¼" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p p. & p. 5p each. Minimum order 6.

**AS NEW AERIAL TUNER UNIT No. 6 RF,** consisting of 1½ inch 500 micro ampmeter 3 gang tuner 75 PF geared BNC type socket size 5½" x 4½" x 5". Price £1.50. p. & p. 25p.

**HEADPHONES DL** High impedance. Good condition 75p. p. & p. 15p. R209. Set of valves 62½p. p. & p. 25p.

**NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED** 75ft. 40p, 90ft 47½p. 100ft. 55p. p. & p. 20p.

**AERIAL MAST POLES** approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition. £1 each section. Carriage 35p each section. ¾" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1 + 30p p.p.

**AS NEW 500ua PENNY SIZE METERS** complete with jack plug price £1 each. p. & p. 10p.

**SLIDING RESISTORS,** 12 amp, 1 ohm. Approx. 9in. long. 1-4 amp., 14 ohms. Approx. 7in. long. As new Ex Eqp. 75p. p.p. 15p.

QUOTATIONS FOR QUANTITY.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

# A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.



## ELECTRONIC ORGAN KITS

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Precussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572.55.

**ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT AND ELECTRICAL HOUSEHOLD APPLIANCES.**

## ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE ROAD, LONDON, S.W.18  
TEL: 01-870 4949



# become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: \_\_\_\_\_  
ADDRESS: \_\_\_\_\_

WB43  
BLOCK CAPS please

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for £1-12. DAF96, DF96, DK96, DL96, 4 for £1-85.

1R5	-28	30C17	-76	EAF42	-50	EM80	-36	PCF808	-68	U801	-75
1B5	-22	30C18	-72	EB91	-12	EM81	-36	PCL82	-80	U8C80	-31
1T4	-16	30P3	-64	EB33	-40	EM84	-52	PCL83	-85	U8C41	-50
3B4	-26	30FL1	-65	EB41	-49	EM87	-60	PCL84	-83	U8C41	-45
3V4	-47	30FL12	-69	EB41	-30	EY51	-36	PCL85	-88	U8F80	-34
5U4G	-31	30FL14	-68	EB90	-22	EY86	-29	PCL86	-87	U8F89	-23
5V4G	-35	30L1	-39	EBF80	-32	EY87	-29	PCL88	-60	U8C84	-23
5Y8GT	-30	30L15	-70	EBF83	-39	EZ40	-39	PCL800	-89	U8C85	-25
6Z4G	-35	30L17	-70	EBF89	-39	E241	-39	PCL805	-88	U8C80	-20
6J30L2	-54	30P4	-65	ECC81	-17	E260	-81	PEN44	-77	U8C42	-58
6AM6	-18	30P12	-69	ECC82	-20	E281	-22	PEN36C	-70	U8C81	-30
6A06	-22	30P19	-65	ECC83	-35	E290	-25	PFL200	-61	U8C82	-33
6AT6	-20	30PL1	-60	ECC85	-34	GZ39	-34	PL36	-48	U8C83	-28
6AU6	-30	30PL13	-69	ECC804	-54	GZ32	-60	PL81	-43	U8F41	-58
6LA6	-30	30PL14	-60	ECC80	-30	KT41	-77	PL8A	-47	U8F89	-80
6BR8	-31	38L6GT	-45	ECP82	-28	KT61	-55	PL82	-31	U8L41	-58
6BJ6	-41	35W4	-25	ECH35	-55	KT66	-78	PL83	-33	U8L84	-30
6BW7	-50	36Z4GT	-25	ECH42	-59	LN119	-63	PL84	-30	U8M84	-23
6F14	-35	50C6G	-68	ECH81	-29	LN329	-80	PL500	-63	U8Y41	-39
6F23	-68	80T	-49	ECH83	-38	LN339	-65	PL504	-63	U8Y85	-25
6F26	-59	ACVP2	-77	ECH84	-35	N78	-21-05	PM84	-80	U8V48	-77
6J5GT	-20	B349	-70	ECL80	-30	P61	-40	PX25	-95	W77	-23
6J7G	-24	B729	-54	ECL82	-29	PABC80	-31	PY32	-82	Z77	-48
6K7G	-12	CCH35	-67	ECL86	-35	PC86	-47	PY33	-82	Transistors	-
6K8G	-36	CY31	-28	EF39	-38	PC88	-47	PY81	-25	AC197	-17
6Q7G	-35	DAF91	-23	EF41	-37	PC86	-42	PY82	-25	AC127	-18
6SL7GT	-32	DAF96	-36	EF90	-23	PC97	-38	PY83	-26	AD140	-37
6SN7GT	-25	DF91	-16	EF85	-28	PC900	-29	PY88	-32	AF115	-20
6V6G	-28	DF96	-36	EF86	-30	PC84	-29	PY800	-31	AF116	-20
6V8GT	-28	DR77	-20	EF89	-26	PC85	-23	PY801	-31	AF117	-20
6X4	-23	DK32	-23	EF91	-13	PC88	-38	R19	-30	AF125	-17
6X6GT	-28	DK91	-23	EF92	-27	PC89	-43	R20	-70	AF127	-17
10F13	-53	DK92	-59	EF98	-65	PC189	-45	U25	-73	OC26	-26
12AT7	-17	DK96	-46	EF183	-27	PC805	-80	U26	-65	OC44	-18
12AU7	-20	DL35	-40	EF184	-29	PCF80	-26	U47	-73	OC45	-18
12AX7	-22	DL92	-31	EH90	-36	PCF82	-33	U49	-70	OC71	-18
19BG6G	-75	DL94	-31	EL33	-55	PCF86	-46	U52	-31	OC72	-18
20P2	-67	DL96	-31	EL34	-48	PCF800	-58	U78	-24	OC75	-18
20F3	-19	DY86	-29	EL41	-54	PCF801	-28	U191	-58	OC81	-18
28L6GT	-27	DY87	-34	EL80	-26	PCF802	-39	U193	-31	OC81D	-18
28U4GT	-27	DY802	-33	EL95	-33	PCF805	-72	U201	-61	OC82	-18
30C1	-26	EABC80	-32	EL500	-62	PCF806	-56	U329	-66	OC82D	-12
30C15	-58	EABC80	-32	EL500	-62	PCF806	-56	U329	-66	OC170	-23

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per. valve extra)

Any parcel insured against damage in transit 3p extra.


## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts

r.m.s. into 8 ohm. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, control panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. **PRICE £10.50. P. & P. 25p.**

## DE LUXE STEREO AMPLIFIER

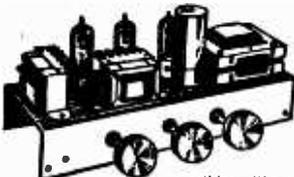

A.C. mains 200-240 v.

U.S. 240 v. heavy duty fully isolated mains transformer with full wave rectification giving adequate

smoothing with negligible hum.

Valve line up:-2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. **PRICE £3.92 P. & P. 45p.**

**POWER SUPPLY UNIT 200/240v.** A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v and 9v, and 12v. at 1 amp continuous (1 amp intermittent).

Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready **PRICE £4.50 P. & P. 35p.**

**BLACK ANODISED 10g. ALUMINIUM HEAT SINKS.** For T03, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

**HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 5 for 50p P. and P. 13p.**

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. Half watt at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. **Price £1.95 P. & P. 30p.**

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. 85p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.45 P. & P. 30p.

**SPECIAL OFFER MAINS TRANSFORMER 200/240v.** A.C. Input 35v at 1 1/2 amp A.C. output overall size 2 1/2" x 2 1/2" x 3" approx. Suitable drop through or vertical mounting 90p. P. & P. 30p.

**CENTRE ZERO MINATURE MOVING COIL METER.** 100uA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 85p. P. & P. 13p.

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

**VAT.** Prices in this advertisement (incl. p. and p.) will be subject to VAT as from 1st April, 1973.

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £6-97 Carr. 50p. With stereo cartridge £7-97 Carr. 50p. **GARRARD SP25 Mk III** with heavy precision machined die cast turntable £10-95, carr. 50p.

### SPECIAL BARGAIN OFFER!

#### PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, C100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). **NOW ONLY £4.50, P. & P. 35p.**

**LATEST AOS EP91/18C** mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

**SONOTONE 5TAH0 COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Sapphire 78. **ONLY £2-50 P. & P. 10p.** Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

**LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. £1-63 P. & P. 10p.

**LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

**QUALITY RECORD PLAYER AMPLIFIER MK II** A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. **PRICE £3-95 P. & P. 40p**

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE £5-25 P. & P. 50p.**

**DELUXE QUALITY PORTABLE R/P CABINET MK II.** Uncut motor board size 14 1/2" x 12in. clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE £4-75, P. & P. 60p.**

### SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.P. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohm impedance.

**OUR PRICE £8.40 Carr. 65p**

Cabinet Available Separately £4-50 Carr 60p  
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £6-50 Carr. 65p

### LOUDSPEAKER BARGAINS

5in. 3 ohm £1.05, P. & P. 15p. 7x4in. 3 ohm £1.15, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.62, P. & P. 20p. E.M.I. 1 1/2" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3-20, P. & P. 30p. E.M.I. 1 1/2" x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4-20, P. & P. 30p.

**BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms.** Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly £6-75. (Guitar models: 25w. £6-75, 35w. £8-50, P. & P. 38p)



### SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2-75. P. & P. 25p.

12in. "EA" TWIN (ONE LOUDSPEAKER, 10 watts peak handling, 3, 8 or 15 ohm £2-50, P. & P. 30p. 35 ohm SPEAKERS 3in. only 85p P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. (can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5-95 each. P. & P. 25p.

**VYNAIR & REKINE SPEAKERS & CABINET FABRICS** app. 54 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 16p per yd (min 1 yd.) S.A.E. for samples.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3 1/2 jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. **PRICE £2-95, P. & P. 15p.**

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1-05, P. & P. 6p

## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magneto cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knob, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M  $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

**AMPLIFIER KIT** . . . . . £10-50 P. & P. 15p  
(Magnetic input components 30p extra)  
**POWER PACK KIT** . . . . . £3-00 P. & P. 30p  
**CABINET** . . . . . £3-00 P. & P. 30p

(Post Free if all units purchased at same time)  
Full after sales service

Also available ready built and tested £21-00. Post Free.  
*Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discophone use, etc.*



### 3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm

speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-95. P. & P. 35p.  
**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4-10. P. & P. 40p.

### HARVERSON'S SUPER MONO AMPLIFIER


A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. **£2.95 P. & P. 35p BARGAIN PRICE**

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull.

Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.

Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. **ONLY £7-97 P. & P. 55p.** Also available ready built and tested £10-97 P. & P. 60p.

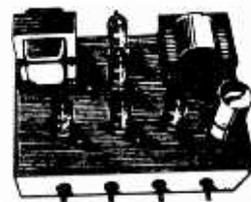

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

## HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

# Sinclair Project 60

## Now—the Z.50 Mk.2

with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual  
£5.48

**Z.30** the power amplifier for quality and economy



with free manual  
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/2 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.


### Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.
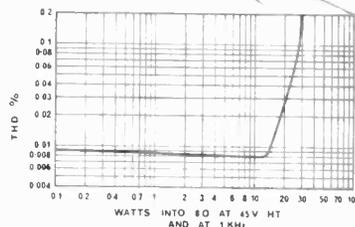
### Brilliant new technical specifications

Input impedance 100 K $\Omega$   
 Input (for 30w into 8 $\Omega$ ) 400mV  
 Signal to noise ratio, referred to full o/p at 30v HT 80dB or better  
 Distortion 0.02% up to 20W at 8 $\Omega$ . See curve  
 Frequency response 10Hz to more than 200 KHz  $\pm$  1dB  
 Max. supply voltage 45v (4 $\Omega$  to 8 $\Omega$  speakers) (50v 15 $\Omega$  speakers only)  
 Min. supply voltage 9v  
 Load impedance – minimum : 4 $\Omega$  at 45v HT  
 Load impedance – maximum : safe on open circuit



## Typical Project 60 applications


System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave deluxe stereo amplifier (60W RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

**sinclair**

# the world's most advanced high fidelity modules

## Stereo 60 Pre-amp/control unit

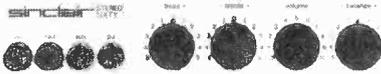

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

**SPECIFICATIONS**—**Input sensitivities:** Radio — up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve —1dB 20 to 25,000 Hz. Ceramic p.u. — up to 3mV. **Aux** — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE: 12 to —12dB at 10KHz. BASS: 12 to —12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed **£9.98**

## Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

**SPECIFICATIONS**—**Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7µV for lock-in over full deviation. **Squelch level:** Typically 20µV. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz — 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2µV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on, tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**
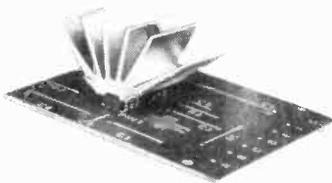
## Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 trans-

istor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

### SPECIFICATIONS

**Output power:** 6 watts RMS continuous (12 watts peak) 8–8Ω. **Frequency Response:** 5Hz to 100KHz ±1dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 30dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual

**£2.98** Post free

## Power Supply Units

### The new PZ.8 Mk.3



The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK 2 amplifiers are used. Nominal working voltage — 45.

PZ.8 Mk 3 — £7.98

(Mains transformer, if required) £5.98

PZ.5 30v un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v stabilised

(not suitable for IC. 12) £7.98

## Project 605



the easy way to buy and build Project 60 without soldering

Project 605 in one pack contains: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free. All you need for a superb 30 watt high fidelity stereo amplifier

**£29.95**

## Order form

Please send

I enclose cash/cheque/money order.

Name

Address

PW4

SINCLAIR RADIONICS, Business Reg. No. 699483; London Rd, St. Ives, Hunts, PE17 4HJ

# sinclair

# Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

## Service Sheets

**SERVICE SHEETS**, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each

**"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"**  
Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

**C. CARANNA**  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

## \* SERVICE SHEETS • MANUALS • BOOKS \*

**SERVICE SHEETS** OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK ON RADIOS, TV'S, R.PLAYERS AND T.RECORDERS, ETC... **SERVICE SHEET** 30p + Postage PLEASE ENCLOSE S.A.E. WITH ENQUIRIES... **Catalogue 20p.**

New Books and Publications	PRICE
Colour Television Servicing by G.J.King 328 pages. A complete servicing guide.....	£4.40
Mazda Book of Pal Receiver Servicing by D.J.Seal 288 pages. Includes fault symptoms	£3.80
Television Servicing Handbook by G.J.King 358 pages A sound introduction to servicing	£3.80
Understanding Television by J.R.Davies 405/625/Colour Edition. 512 pages.....	£2.10
Foundations Of Wireless And Electronics by M.G.Scroggie. 8th Edition. 552 pages....	£3.00
Beginner's Guide To Radio by G.J.King 7th Edition. 204 pages. A must for newcomers.	£1.00
Beginner's Guide To Television by G.J.King 5th Edition. 211 pages. Illustrated.....	£1.60
Colour Television Theory by G.H.Hutson 334 pages. PAL-System principles/circuitry..	£3.85
Electronics in Music by F.C.Judd 169 pages.Circuit designs for the enthusiast.....	£3.15
Model Radio Control by P.Newell 134 pages. Theory and Practice. 100 Illustrations...	£2.25
T.V.Fault Finding Book by Data Publications Ltd. 405/625 Edition. 124 pages.....	£0.50

Note. Postage on all books is now 5p in the £1. Orders over £5.00 post FREE (UK only). . . . .

Send S.A.E. for Free LISTS of Practical and Technical Books on Radio & Television now available to

## BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorks. Tel. 0423-86844

## Aerials

Direct from the Manufacturers  
**U.F.E. AERIALS**  
EASY ASSEMBLY KITS  
10 Element **SAVE 40%**  
£1.25 on normal retail price  
14 Element £1.50 18 Element £1.75  
Most things available  
Ready assembled ads 20p allow 32p carriage and packing. Please state which element or group.  
**APEX AERIALS (P.W.)**  
ALBAN WORKS, MARY ST. JOHNSTONE, RENFREWSHIRE

## BAINES for High Frequency Aerials

UHF Multibeams by J. Beam

MBM 10 £2.20 MBM 18 £2.90 MBM 30 £3.90  
MBM 46 £6.00 MBM 70 £11.00  
VHF FM Aerials  
Dipole £1.40, FM/H £2.00, FM3 £3.00, FM4S £5.55, FM6S £7.80  
Masthead Pre-amps  
Single Stage £5.00, Two stage £8.00, Wideband £7.00  
Accessories: SAE for full list. Co-ax 5p, low loss 9p  
11 Dale Cres., Tupton, Chesterfield S42 6DR

**DIRECT FROM MANUFACTURER**—a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PW), 261 Hardest Street, London, S.E.2A.

## Wanted

TOP PRICES PAID FOR NEW VALVES popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C)**,  
367 Kensington Street, Bradford 8,  
Yorkshire.

**WE BUY** New Valves, Transistors and (clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

## For Sale

### BBC 2 TV'S 7.50 Including Delivery

Thorn 850 Chassis with UHF Tuner. Ex-rental sets sold complete but un-serviced, with repolished cabinets. Rush £7.50. Cash with Order

### U.H.F. TUNERS

For Ferguson 850, 900 Chassis, but adaptable for most D/STD Chassis. £2.50 each. Plus 50p P&P. C.W.O. Send S.A.E. for list of TVs, Tubes, Valves, etc. Allow 10-14 days delivery

### TRADE DISPOSALS (PW),

Midlands & North: 1043 Leeds Road, Bradford 3  
Scotland: Unit 5, Peacock Cross Industrial Estate, Burnbank Road, Hamilton  
Cornwall: Pencoys, Four Lanes, Redruth.

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

## MORSE MADE EASY!!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £3.30. Complete Course £4.50 (Overseas £1.00 extra details only, 4p stamp. 01-660 2896 GSHC (Box 19), 45 GREEN LANE, PURLEY, SURREY

**35! CRYSTAL SET Kits**, plans. D. Sanders, 59 Sweetpool Lane, Hagley, Worcs. DY8 2XA.

## Ladders

**LADDERS**. 20ft, £7.80; 24½ft £9.80. Carr. 80p. Leaflet. (Dept. WLS) Home Sales Ladder Centre, Baldwin Road, Stourport, Worcs. Tel. 029-93 5222.

## Books and Publications

**DENCO CLACTON LIMITED**  
355-7-9 Old Road  
Clacton-on-Sea, Essex

Catalogue 20p post paid  
S.A.E. all enquiries

**WORLD RADIO TV HANDBOOK** (1973 edition) £2.90. Fortnightly World Radio Bulletin (ask for free copy) £3.13. How to Listen to the World. £2.00. SWL Address Book, stations' QSL policies, etc.. £1.60. Confidential Frequency List—Forces, Air, Spy, etc.. £1.80. Shortwave Voices of the World. £1.80. Guide to Broadcasting Stations. 60p.

Prices include First Class postage.

**DAVID MCGARVA (PW)**  
Box 114, Edinburgh, EH1 1HP  
Giro a/c 17 412 0001

**DIGITAL COMPUTER LOGIC** and Electronics. Four volume self-instructional course. £2.95 including p & p. Money back assurance. Cambridge Learning (PW), 8a Rose Crescent, Cambridge.



PROPERTY OF  
A. WILEY (130 CLOVELACE DRIVE PYRFORD)

## Trampus electronics

All Brand New. Money Back if dissatisfied. Fast Service.

**5V DIGITAL INDICATOR** 0-9DP, with socket and red Filter £1.89, 7447 £1.39

**IC GAS DETECTOR.** Smoke, Butane, Vapour, etc. £1.89.

**data 9p. ULTRASONIC TRANSDUCER.** Transmit or receive

**£2. LIGHT EMIT DIODES.** Visible red/panel clip/data, 86p

**INFRARED** (invisible beams) £1.19

**DIGITAL CLOCK** integrated circuit, 28 pin DIL, 12/24 hr, 4/6 digit, £11.50, data 15p. P.C.B. £1.29

**COMPLETE KIT with (P.C.B.)** case £21.

**NEW IC RADIO ZR414** £1.19

**PW TEXAN KIT** less chassis £21.49. PAKS: 1r/semi-conductor £2.49. Caps £2.49. Res £1. Transformer £2.67. TIP 41/42 pair £1.50. 741/748 36p ea.

**INTEGRATED CIRCUITS** with data.

741 Op amp DIL 80p, 709 TO5 21p. DIL 29p, 710 85p, 748 85p, 749 85p. DETECTOR/amp 44p.

**4064/4064E RECEPTORS:** 14 amp 5 or 12 V type £1.87, 723 56p, 555 TIMER/stab oscillator 86p.

**AUDIO AMP 3-5W HI-FI** etc. £1.24. Stereo: Pre-amp £1.49, MPX Decoder for any FM BX £2.69.

74N: Data Booklet 12p, gates 7400 etc. 16p, 7400 69p, 7470/72 29p, 7473 59p, 7492 73p, 7413 82p.

**DIL SOCKETS** low profile 14 or 16 pin, for 74N, 13p.

**SEMICONDUCTORS:**

2N805 29p, BC107 7p, BC108 7p, BC109 8p, AC125/MS2 AC127/6 AC187/8 AF117 16p, AD161/2 86p, BC167/8/9 17p, BC177/8/9 15p, BC182/3/4 11p, BC212/3/4 13p, BCY70 16p, BFY505/1/5 22p, T1843 UJT 29p, 2N706A 12p, 2N2938 19 28p, 2N2939 19 28p, 2N3700 11p, 2N3708 11p, 2N3709 11p, 2N3710 11p, 2N3711 9p, 1A RECTS: 50V 3p, 400V 8p, 50V Bridge 28p, IN914/6 3p, OA90 11p, OA200/202 10p.

**ZENERS:** 4ZV8 400V 10p, 5-1V/10W 29p.

**MINI SCR 4A/400V 55p TRIAC 6A/400V 87p.**

**CAPACITORS:** 25/30 Electrolytic 10/50/100/2F 5p, 200/200F 5p, 1,000µF, 15p. DISC: 22F thro' to 0.047µF, 3p; 0.01 to 0.6p. RESISTORS ¼W 5%, 1p. PRESETS 0.25W, 5p. VERO 16p/23p, etc., DIN plugs, 13p; sockets, 8p.

**A.M. MEDIUM WAVE RADIO KIT £2.89.**

**ELECTRONIC: PW CAR IGNITION KIT, £6.67.**

**FREE CATALOGUE, S.A.E., Data Sht. 8p ea.** C.W.O. P & P 7p. Overseas 35p. Discount 10+10%. P.O. BOX 29, BRACKNELL, BERKS.



## THE TEXAN

NOW ON DEMONSTRATION



Designer approved Kit only £28.50  
Instructions only 35p

- Pack 1. RESISTORS ..... 80p
- Pack 2. SMALL CAPS ..... £1.50
- Pack 3. LARGE CAPS ..... £1.40
- Pack 4. SUNDRIES ..... £1.90
- Pack 5. SWITCHES ..... 90p
- Pack 6. CONTROLS ..... £1.45
- Pack 7. SEMI COND. .... £8.25
- Pack 8. TRANSFORMER .... £4.95
- Pack 9. P.C. BOARD ..... £2.00
- Pack 10. CHASSIS, etc. .... £2.75

Post extra—parts available separately  
Send for list and technical spec.

### Kits also available for

- ★ Radio Control Systems
- ★ Digital Clock Systems
- ★ Integrated Circuit Amplifiers (to 50W)
- ★ Hi-Fi Pre-amps
- ★ Stabilized Power Supply Units

**TELERADIO HI FI, 325 Fore Street,  
Edmonton, London N.9 01-807 3719**  
CLOSED ALL DAY THURSDAY

### CASED AMPLIFIERS

2x ECC83, EL84, E280, 20µV 1/P sensitivity 2 watts  
2x into 7 x 4" 3Q Speaker. All contained in  
polished cabinet with non-standard single motor  
deck. Tested with circuit £3 (£1).

### COMPUTER PANELS

Lots of Transistors inc. Power Types, Diodes, R's,  
C's, Pot Cores, etc. Some boards broken, but good  
value at 1/2s. £1 (25p), 7/1s. £2 (40p).

### 60p COMPONENT PACKS

RESISTORS: 350 carbon 60p (15p); 200 5%  
Hi-stab. 60p 1 anly 2% 60p (8p).

CAPACITORS: 150 Mica, Poly, Ceramic 60p (8p);  
75 Electrolytic 60p (15p); 150 Paper, Foil, Polyester  
60p (15p). Any 5 packs £2.50 (25p).

### FERRIC CHLORIDE

Anhydrous Technical Quality in sealed 1lb packs  
40p (15p), 10lbs £2.50 (50p).

**COMPONENTS:** BC107, 8p ea, 14 for £1  
709C 25p; 741C 25p; 743C 40p; 2N3055 35p.  
IN4003 7p; IN4006 11p; Profom 1610 Light Guide,  
64 Filament 21 per pack, 5 + 80p, 10 + 70p.  
SURPLUS CAPACITORS MF/V: £7/350 6p;  
2/150 2p; 8/350 8p; 4/450 10p; 2/25 5p; 600/50 12p;  
550/6 3p; 1000 + 500/18 12p. Lots of others. Lots  
of Odd Ultras, Tubes, Megohms, Avo's, Sig. Gens.,  
etc. at shop for callers. S.A.E. List. Post in brackets,  
small parts 8p.

### GREENWELD (PW11)

24 Goodhart Way, West Wickham,  
Kent. Tel: 01-777 2001. Shop at 21  
Depton Road, Broadway, S.E.8. Tel: 01-  
692 2009.

**COMPONENTS GALORE.** Pack of 500  
mixed components manufacturers surplus  
plus once used. Pack includes  
resistors, capacitors, transistors,  
diodes, I.C., gang, pots, etc. Tremendous  
value. Send £1 incl. postage  
C.W.O. to Caledonian Components,  
Fosterton Firs, Strathore Road,  
Thornton, Fife.

**RECEIVERS** and accessories. B40/62B  
fine-tuning, S-meter and product  
detector kits and information, SAE  
details. P. R. Gollidge, G3EDW, Glen  
Tor, Torrington, Devon. Tel: 08-052  
2411.

## PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0.47µF: ±5% 80p; ±2% 40p; ±1% 60p  
1.0µF: ±5% 40p; ±2% 60p; ±1% 60p  
2.2µF: ±5% 60p; ±2% 80p; ±1% 75p  
4.7µF: ±5% 70p; ±2% 90p; ±1% £1.15  
8.8µF: ±5% 95p; ±2% £1.15; ±1% £1.60  
10µF: ±5% £1.10; ±2% £1.40; ±1% £1.80  
15µF: ±5% £1.60; ±2% £2.10; ±1% £2.70

**TANTALUM BEAD CAPACITORS**—  
Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7,  
6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF  
15V, 33µF 10V, 47µF 6V, 100µF 3V—all  
at 9p each; 6 for 50p; 14 for £1. Special pack  
6 off each value (78 capacitors) £5.

**NEW!—TRANSISTORS.** BC107, BC108,  
BC109, All at 9p each; 6 for 50p; 14 for £1. All  
brand new and marked. Full spec. devices. May  
be mixed to qualify for quantity prices. AF178—  
42p each; 3 for £1.

**POPULAR DIODES IN914**—7p each, 8 for  
50p; 18 for £1. IN916—9p each, 6 for 50p, 14  
for £1. IS44—5p each, 11 for 50p, 24 for £1.  
All brand new and marked.

**NEW LOW PRICE—400 mW Zeners.**  
Values available 4.7, 5, 6, 6.8, 7.5, 8.2, 9.1, 10, 11,  
12, 13, 15, 15V. Tol. ± 5% at 5 mA. All new and  
marked. Price 10p each, 6 for 50p, 14 for £1.00.  
Special offer 6 off each voltage (66 zeners) £4.50.

**RESISTORS.** Carbon film ¼W 5%. Range from  
2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18,  
22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
High stability, low noise. All at 1p each; 8p  
for 10 of any one value; 70p for 100 of any one  
value. Special development pack—10 off each  
value 2.2Ω to 2.2MΩ (730 resistors) £5.

**440V A.C. CAPACITORS:** 0.1µF, size 1 1/4 in  
x 1/2 in, 25p; 0.25µF, size 1 1/4 in x 1/2 in, 30p; 0.47  
and 0.5µF, size 1 1/4 in x 1/2 in, 35p; 1.0µF, size 2 in  
x 1 in, 45p; 2.0µF, size 2 in x 1 in, 75p each.

**SILICON PLASTIC RECTIFIERS 1-5 AMP**  
Brand new wire-ended DO27, 100PIV at 8p each  
and 4 for 30p; 400PIV at 9p each or 4 for 34p;  
800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5.  
**MARCO TRADING** (formerly V. Attwood)  
Dept. E.1, P.O. Box 8, ALRESFORD, HANTS.

**COMPONENTS**—Integrated Circuits,  
Digital Displays, Diodes, Resistors,  
Capacitors, Switches. List 3p. Cavern  
Electronics, 29 Clarefield Road,  
Leicester LE3 6FB.

**TAPE-HEAD** reconditioning service.  
Guaranteed satisfaction. Send worn  
head with £2 to: Sara Electronics,  
Fawkham Avenue, Longfield, Kent.

**TRANSISTORS:** mint, branded top  
grade AD161 22c pr; 60p; BC107B, 12p;  
BC169C, 10p; 2N2926G, 12p; 2N3702, 10p;  
2N3704, 10p; DIODES: OA90, 6p;  
IN4002, 5p. Mail order only, U.K.  
postage 5p. AMATRONIX LTD., 396  
Selsdon Road, South Croydon, Surrey  
CR2 0DE.

**VISIT AUTO TRACTION.** Thousands  
of bargains in surplus radio equip-  
ment. Meters, motors, relays, TR/TX,  
telephone equipment, aircraft equip-  
ment. SAE enquiries, 27A, Arragon  
Road, Twickenham, Middx. 892 9489.

World-wide acclaim, the incomparable

## GLOBE-KING

Precision standard, inexpensive, low-cost  
valve and transistor Kits for Short-Wave  
10-350 m. V.H.F. 80-180 M/c. Ideal for  
beginners with unique "Easy-Build" dia-  
grams and simplified instructions. Send  
to-day for free literature price list and  
order form, kindly enclose stamped  
addressed envelope (Overseas: Int. Reply  
Coupon). Direct to the sole manufacturer:

**JOHNSONS (RADIO)  
SHAW ST., WORCESTER.  
WR13 3QQ**

Please note new address, city centre.  
Pioneers in DX radio—Established for  
over 30 years.

### NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance  
plus extra amplifier stage, receives aircraft,  
amateurs, mobile, radio 2, 3, 4, etc., this novel  
little set will give you endless hours of pleasure  
and can be built in one evening. Powered by 9 volt  
battery, complete with easy to follow instruction  
and built in jack socket for use with earphones or  
amplifier.

Only £3.50 + p.p. 10p U.K. only.

Illustrated catalogue of selected kits and com-  
ponents. 15p P&P free.

Galleon Trading Co,  
12, Burns Way,  
Corringham,  
Stanford-Le-Hope,  
Essex. SS17 9DE

**13A SCOPE.** Handbook with Circuit  
Diagram—£2.00. Complete range  
spares, probes, transformers, chokes,  
potentiometers, gratulicues, etc. Cheap.  
SAE or phone. CT.316 Scope. Hand-  
book with Circuit Diagram—£2.  
**SPEAKES, 12 Kenley Avenue, Shrews-  
bury. Tel. 56949.**

## NEW RECEIVER MODULE RM-A

A small circuit board, wired, tested and aligned and requiring only addition of tuning capacitor, coils and controls (not included) to make a complete AM CW SSB superhet RX for up to 30 MHz. Headphone output Runs off 6V to 15V. PP0 suitable. Contains RCA IC (equiv. 14 transistors) plus BFO, FET local osc and 2 double-tuned IFT's at 465 kHz. Full instructions and colour coded leads make connection simple, even for beginners. £7.85 post paid. Provides good stable reception of DX on CW SSB or can be used with HF or VHF converters as double superhet. Suitable add-on RF and Audio Amp modules also available from £2. SAE details.

P. R. GOLLEDGE G3EDW  
Glen Tor, Torrington, Devon.  
Tel: 08-052 2411

## Miscellaneous

QUALITY 1/2 Track R/P Heads, mounted in Mumetal Case. 55p each. 117 Horton Road, Brighton, BN1. 7EG.

# Darned Electronic Wizardry

by Dewtron

Famous Kits, e.g. waa-waa complete kit £2.95; Fuzz kit £1.55; auto rhythm modules P & P 20p; min. Rin. Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.L.W. Ltd., 234 Ringwood Road, Ferndown, Dorset.

## TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification, or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACV22	BFY51K	OC72	2N3702
BZ408	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3733
BC169	OC71	2N2928	2N3708

Money back guarantee, P. & P. 10p.

J. N. KING (H)

11, Buckridge, Portpool Lane, London, E.C.1

**HARDWARE**—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwks.

**MANUFACTURER'S SURPLUS, RECORD PLAYER Cabinets** with motor board £3.00. Radio Cabinets make ideal speaker cabinets 13in x 7in x 5in 500V AM/FM gang condensers with 500V drive 25p. UHF/IF Transformers, set including sound discriminator, 75p with data. F/M Tuner with valve £1.50. All items new includes P & P. ARCHER, 9 Pine Grove, Maidstone, Kent.

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2 1/2in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

## RECORD T.V. SOUND

using our loudspeaker isolating transformer. Provides safe connection for recorders. Hi-Fi equipment or extension speakers.

£1 post free. Instructions included.

Crowborough Electronics (PW)  
Eridge Road, Crowborough, Sussex.

## 4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in deluxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 4 connecting wires each 66ft. and other accessories. P. & P. £0.40.

## MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £14.40 P. & P.

## INTERCOM/BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 14p. P. & P. £0.25.

## TELEPHONE AMPLIFIER



£2.99

Why not boost your business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.4)  
169 KENSINGTON HIGH STREET, LONDON, W.8.

## AERIAL BOOSTERS

We make four types of Aerial Boosters. L45 62 S UHF, L12 VHF 405, L11 VHF Radio L10 M/W & S/W. Price L45, L12 & L11 £2.95. L10 £2.45.

## VALVE BARGAINS

Any 5—45p. 10 Top: EC82, EC180, EF50, EF85, EF183, EF184, EF89, EB91, EY86, PCC84, PCC89, PC97, PCF80, PCF85, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY82, PY800, PY801, 30L15, 30C15, 6-30L2.

## 19" UHF/VHF TV £7.50

### THORN 850 SERIES

Untested but with complete set of spare valves. Price £7.50. Carriage £1.50.

## 100 MIXED RESISTORS 60p

From 1/4 watt to 2 watt and from 10-ohms to 10m-ohms our choice.

## 100 MIXED CAPACITORS £1

From 220PFD to 200MFD and from 12v.w to 500v.w—our choice.

POST & PACKING under £1.5p. Over £1.10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

## VELCO ELECTRONICS

62B Bridge Street, Ramsbottom, Bury, Lancs.

## LOUDSPEAKER BARGAINS

Fane Pop 100 Watt 18" 8/15 ohm	£19.50
Fane Pop 60 Watt 15" 8/15 ohm	£11.15
Fane Pop 50 Watt 12" 8/15 ohm	£9.25
Fane Pop 25/12" 25 watts 8/15 ohm	£5.40
Fane Pop 15 12" 10 watts 8/15 ohm	£4.00
Baker Group 25 12" 3, 8 or 15 ohm	£6.60
Baker Group 35 12" 3, 8 or 15 ohm	£8.00
Celestion PS8 for Unilex	£2.35
EMI 13 x 8, 3, 8 or 15 ohms	£2.25
EMI 13 x 8, 3, 8 or 15 ohms	£2.60
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms	£3.80
EMI 13 x 8 type 350 15 watt 8 ohm	£8.00
Richard Allen 8" 3, 8 or 15 ohm	£2.35
Richard Allen 12" dual cone 3 or 15 ohm	£2.50
Fane 8" dual cone 808T 8 or 15 ohm	£2.85
Fane 8" d/cone roll surround 807T 8 or 15 ohm	£3.50
Elac 59RM103 9" x 5" 15 ohm	£2.70
Elac 59RM114 9" x 5" 8 ohm	£2.70
Elac 6 1/2" d/cone 8 ohm	£2.25
Elac 6 1/2" d/cone, roll surround 8 ohm	£3.50
Elac 4" tweeter 8 ohm	£1.50
Crossover for above (p. & p. free)	£1.50
Goodmans 8 P, 8 or 15 ohm	£4.75
Goodmans 10 P, 8 or 15 ohm	£4.75
Goodmans 12 P, 8 or 15 ohm	£10.50
Goodmans 15 P, 8 or 15 ohm	£17.00
Goodmans 18 P, 8 or 15 ohms	£27.50
2", 2 1/2" or 3" 80 ohm	.65
Philips 5" 8 ohm	£1.95
7" x 4" or 8" x 5" 3 or 8 ohm	£1.50
10" x 6" 3, 8 or 15 ohm	£2.00

FREE with orders over £6—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect. Prompt despatch p. & p. 25p per speaker.

## WILMSLOW AUDIO, Dept. PW

10 Swan St., Wilmslow, Cheshire, SK9 1HF

## B.H. COMPONENT FACTORS LTD.

VAT: Please add V.A.T. at the standard rate after April 1st.

**SPECIAL RESISTOR KITS.** (1W or 1/2W 5%, Carbon Film) 10E12KIT, 10 each E12 value, 10ohms-1M. A total of 610. £2.80 net 25E12KIT, 25 each E12 value, 10ohms-1M. A total of 1325. £8.50 net

**MULLARD POLYESTER** (250 250V, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 3p, 0.068, 0.1, 0.15, 3p, 0.25, 5p, 0.33, 7p, 0.47, 5p, 0.68, 1.0, 10p, 15p, 1.5, 2p, 2.2, 23p.

**MULLARD POLYESTER** (296: 160V, (µF) 0.01, 0.015, 0.022, 2p, 0.047, 0.068, 3p, 0.15, 0.22, 3p, 0.33, 5p, 0.47, 6p, 0.68, 1.0, 10p, 400V: (µF) 0.001, 0.0015, 0.0022, 0.0033, 0.01, 2p, 0.015, 0.033, 3p.

**MULLARD ELECTROLYTIC** (425: 5p, each, (µF/V) 0.64/4, 0.7/5, 1.0/6, 1.5/7, 2.2/8, 3.3/10, 4.7/10, 6.8/10, 10/10, 15/10, 20/10, 25/10, 30/10, 33/10, 47/10, 68/10, 80/10, 100/25, 100/50, 125/10.

**HI-VOLT ELECTROLYTIC:** 8/350, 12p 16/350, 17p 22/350, 22p 30/350, 15p 32/350, 22p 100/500, 30p 100/10, 10p 100/25, 2000/12, 2500/12, 15p 1000/50, 33p 2000/25, 25p 2500/25, 30p 3000/50, 65p 5000/50, 85p 2500/50, 55p 1000/100, 60p.

**CERAMIC PLATE, 50V:** (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8 (nF) 0.01, 0.015, 0.022, 0.033, 2p, 0.047, 30V, 5p, 0.1, 20V, 4p.

**CARBON FILM RESISTORS:** 1W, 5%, 10ohms-2.2M: 1W 5%, 25Ω-1M 1p, each or 100 for 55p.

**METAL FILM RESISTORS:** 1W 5%, 27Ω-10M 1p each or 100 for £1.

**VEROBOARD** 0.1 0.15 **CARBON POTS** 3K-2M Log and Lin 2 1/2" x 5" 25p 25p single 15p, single 2 1/2" x 5" 25p 25p with SW. 25p, dual 3 1/2" x 3 1/2" 25p 25p 42p.

Plus, Pkt. 25 8p **SCREENED WIRE** 2 Pin DIN Plug 12p, 8kt, 10p Single 5p/yll., twin 3 Pin DIN Plug 13p, 8kt, 10p 8p, stereo 9p, quad 19p, Panel Neon 240V, 15p.

Priset Skeleton Pots 1K-1M 5p Neon Bulb 90V, wire ended 5 for 20p 1N4001, 6p, 1N4002, 7p, 1N4003, 8p, 1N4004, 9p 1N914, 6p, 7400N, 15p, 7401-7410-7430, 15p 2N706, 10p, 2N914, 30p, BC108, 11p, BFY51, 20p (CWO, po 10p, Discount £10-10%). The above items are only a few taken from our catalogue which is available free. Money back refund.

Dept. PW, 61 CHEDDINGTON RD., PISTONE LEIGHTON BUZZARD, BEDS., LU7 9AQ. Tel.: Cheddington 683446 (STD Code 0296)

**OMNIA PRODUCTS**



**STABILIZED  
AUTO ADAPTOR**

**FOR CAR—CARAVAN—BOAT**

Designed for feeding from 12 volt car battery:—**Cassette recorders, radios, record players, etc.**, operated by dry cell batteries. Gives 3 different outputs (selector switch) 6, 7.5 & 9v; stabilized current for top performance —at no cost. Only £3.50 p. & p. 10p (add 10% VAT 1st April).

**25 Wilbury Gardens Hove Sussex**

**"AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"**

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW  
(S.A.E. for details)

TO: 'BOFFIN PROJECTS'  
DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

**GLASS FIBRE P.C. BOARD.** Large supplies available in single sided one ounce copper 2p per 3 sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.), £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

**FASCIA PANELS** to individual specification in etched aluminium. Hardware supplies for constructors. Printed circuit boards one-off's. Send 5p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

**BEDFORD ELECTRONICS**

2 Grove Place, Bedford  
Bedford 51961

**YOUR LOCAL  
COMPONENTS SUPPLIER**

Free catalogue on request

**12 VOLT  
FLUORESCENT LIGHTS**  
(as illustrated)



Beat power cuts. Be independent ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt £3.60 post paid  
21 ins. 13 watt £4.60 post paid

Callers welcome.  
For lists or enquiries, large s.a.e.  
**SALOP ELECTRONICS, 23 WYLE COP  
SHREWSBURY, SHROPSHIRE.**

Versatile

**10 in  
ONE**



**MINI-LAB**

Comprising:

- AC & DC Voltmeter ● Audio Generator
- Ohm Meter ● Resistance Substitution
- Capacitance Substitution ● DC Ammeter ● Battery Supply ● RF Signal Generator ● RF Field Strength Indicator

This new, unique instrument combines all you need for testing. Money back if not satisfied.

**£11.25**

plus 25p p. & p.

Cash with order or send s.a.e. for illustrated data sheet to:

**J. H. ASSOCIATES LTD. (DEPT PW)**  
Cricketfield Lane, Bishop's Stortford, Herts.

**ENGRAVING.** Give your Fascia Panels that professional look. Have the letters machine engraved. 3p per letter, minimum order 50p. Plus P & P. Colourstones, 9 Broadway Close, Harwell, Berkshire.

Due to Warehouse Clearance we have a few low powered F.M. VHF Wireless Station Type A. A.F.V. No. 88. Contained in two units (1) Transmitter/Receiver, (2) 12 Volt Power Unit and L.F. Amplifier.

The TX and RX are contained in a waterproof diecast Alloy case, using a total of 14 Valves, operates on four switched channels which are Crystal controlled. All 8 Crystals are supplied, and are the same in each set. Therefore all sets will transmit and receive to each other, provided each are switched to the same channel out of the four. The Stations are supplied with Mounting Carriers, 2 Vertical Whip Aerials, plus Aerial Base, Spare Valves, Bulbs, Mounting Screws, Connectors, etc. Including the Operating Manual giving all details, plus circuits of the Wireless set. All above items are individually boxed and wrapped, placed in original Transit case.

**ABSOLUTELY BRAND NEW**

Made by Echo for the Government, no expense spared, few only available at £8.50, carr. £2.

**RADIO TELETYPE TERMINAL SET**

A type AN/80GIA latest Government release of these sought after units, housed in metal case, approx. size 8" x 10" x 1 1/2". Deep. Using a total of 11 Valves, Supply Voltage 115 Volts 50 c/s. Containing meter switched for checking, send and receive Bias, Send and Receive Level, Loop and Plate current, in fair used ex Government condition. Few only available at £7.50, carr. £1.50.

**FREQUENCY SHIFT CONVERTOR AND COMPARATOR**

Type AN/URA-8B for Diversity use or single channels £15 and £10 respectively, Carr. £1.50 and £2.50.

**FREQUENCY METER TS186 D/UP**

Recent Ministry release of this scarce and valued unit, this is basically the VHF/UHF version of the BC221. Range 100 mgs to 10,000 mgs. Distributed over approx. 15,000 dial divisions, each meter (same as the Bc221) contains its own book of Calibration charts, plus circuits and Instruction Book. Contained in Metal Shockproof Transit case, with Supply Cable, Supply 115 volts ± 10% 50 c/s. Output on headphones or meter in the front panel. Accuracy is 0.01%, 0.002% on the Crystal Calibrator check points. Sensitivity for R/F signal input 500 Micro Volts to 1 volt. A plug is also provided for V1010 output for connection to an Oscilloscope, RF input connection is via coaxial cable or standard Wave Guide. Limited number available £18.50, carr. £1.50.

**LARGE QUANTITY OF TELEPRINTER PAPER**

Available, sprocket fed, contained in sealed packs, each pack containing 4 separate wads, price 60p per pack of four packs, post 25p, or wooden crate containing 5 packs = 20 wads £2, carr. 50p.

**CREED TELEPRINTER MOTORS**

For mains 200/250V A.C. for use on 7B Teletypewriters etc., available brand new £2, post 25p.

**MALLORY LONG LIFE BATTERIES**

Type RM12 1.35 volts as used in Contamination Meters No. 1, £1 per box of 50, post 25p. Brand new ex government.

Terms C.W.O. or uncrossed P.O.s in case stocks run out, so we can refund same.

**JOHNS RADIO**

424 BRADFORD ROAD, BATLEY, YORKS.

Phone: BARKLEY 7732

**CHASSIS  
and  
CASES by**




**H. L. SMITH & CO LTD**  
287/9 Edgware Road  
London W2 1BE  
Telephone: 01-723 5891

**CASES ALUMINIUM, SILVER HAMMERED FINISH**

Type	Size	Price	Type	Size	Price
N	8x6x2"	£1.00	W	12x7x7"	£2.50
N	6x6x3"	£1.05	W	15x9x8"	£3.15
N	4x4x2"	80p	Y	8x6x6"	£2.25
U	4x4x4"	95p	Y	12x7x7"	£2.80
U	5 1/2 x 4 1/2 x 4 1/2"	£1.15	Y	13x7x9"	£3.15
U	8x6x6"	£1.45	Y	15x9x7"	£3.35
U	9 1/2 x 7 1/2 x 3 1/2"	£1.55	Z	17x10x9"	£4.15
U	15x9x9"	£3.00	Z	19x10x8 1/2"	£4.35
W	8x6x6"	£1.90			Plus p. & p. *Height

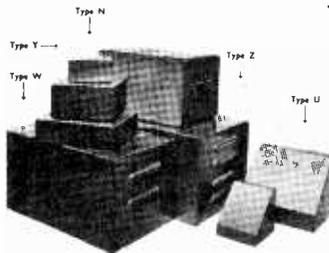Type N has removable bottom. Type U removable bottom or back. Type W removable front. Type Y all screwed construction. Type Z removable back and front.



**BLANK CHASSIS**

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	34p	17p	10x8x2 1/2"	66p	30p
7x4x1 1/2"	33p	18p	12x7x2 1/2"	66p	33p
7x5x2"	40p	19p	12x9x2 1/2"	76p	38p
8x4x2"	38p	19p	13x8x2 1/2"	76p	38p
8 1/2 x 5 1/2 x 2"	44p	21p	14x7x3"	80p	36p
9x7x2"	50p	26p	14x10x2 1/2"	88p	47p
10x4x2 1/2"	50p	21p	15x10x2 1/2"	92p	50p
12x4x2 1/2"	55p	22p	17x10x3"	£1.10	55p
12x5x3"	66p	26p			Plus post and packing

**TO FIT OUR CASES**

7x5 1/2 x 1 1/2"	38p	21p	12x6 1/2 x 2"	60p	33p
7x5 1/2 x 2"	43p	21p	14x8 1/2 x 2"	74p	44p
11x6 1/2 x 1 1/2"	48p	30p	15 1/2 x 9 1/2 x 2 1/2"	94p	52p
11x6 1/2 x 2"	55p	30p	17 1/2 x 9 1/2 x 2 1/2"	£1.05	59p

Plus post & packing

PANELS: Any size up to 3ft. at 36p sq. ft. 16 s.w.g. (18 s.w.g. 32p) Plus postage and packing

# PADGETTS RADIO STORE

## OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

The T.V. Graveyard of the North, as seen on T.V. Close to the Motorway. Plenty of Free Parking Space. Call in and see us any day 9-6. Closed Sunday. Est. 1935.

NEW TOP QUALITY MAINS TRANSFORMERS. 250v-0-250v at 80mA. 6 3v at 4amp. Not to be missed at £1 50 Post Paid. Weight 10lbs.

QUALITY RECORDING TAPES 7" L.P. Tapes 75p, 7" S.T. 60p. 5" L.P. 50p, 5" S.T. 40p. Post on any tape 10p.

TOP QUALITY TAPE CASSETTES. C60. 35p, C90. 45p, C120. 55p P. & P. 12p.  
JAP EAPPIES. 3.5 and 2.5 12p each. P. & P. 3p.

STUDENTS' WIRELESS PROCEDURE TRAINING SET Comprising: Mike, Single L.R. Phone and Connector. In small Wood Case. Good Condition, but Untested. A Gift at £1.25 Post Paid. Complete Untested T.V. Sets, with Back and all Valves, BBCI and ITV 17" 90° Tube £2. 17" 110° Tube £3. 19" Slim £5. Carr. and Ins. £1 50.

Reclaimed T.V. Tubes. All with 12 Months' Guarantee. AW43/88 £1.50. AW43/80 £1.50. MW43/69 £1. Many other Types in Stock. Carriage and Ins. on any Tube £1.50.

½ cwt. of EX GOVERNMENT ELECTRONIC SCRAP. RESISTORS, PANELS, GEARS, ETC. 25p. Carr. 75p.

Ex Equipment Valves. All Tested on our Mullard Valve Tester before despatched. 3 Months' Guarantee on all Valves. Single Valves Post 3p. over Post Paid.

ARPI2	5p	PCF80	5p	PY82	8p
EB91	4p	PCC84	5p	PY33	17p
EF80	8p	PCL82	12p	UI91	20p
EF85	12p	PCL83	12p	6BV7	10p
EBF89	12p	PCL84	12p	6U4	10p
ECC81	10p	PL81	17p	20P1	15p
ECC82	12p	PL82	8p	20P3	10p
ECL80	8p	PL83	8p	30F5	10p
EF50	60p per doz.	PL36	17p	30FL1	20p
EF91	4p	PY81	8p	6'30L2	20p
EY86	20p				

## COMPARE OUR PRICES

<b>Speaker Bargains</b>		<b>Microphone Bargains—continued</b>	
E.M.I. 13 x 8 in 3, 8 & 15 OHMS	£2-00	MIC60 "ACOS" atk crystal	£1-80
PLAIN	£2-25	CM70 PLANET stick metal,	
WITH TWEETER	£7-25	switch crystal	£1-45
Type 350-20 watt with Tweeter	£7-25	DM160 Dynamic uni-dir, ball	£3-75
8 OHM p. & 37p.	£3-50	metal	£4-50
TWIN TWEETER	£1-30	UD130 50K/600 OHM uni-dir,	
8 x 5 in 3, 8 & 15 OHMS	£1-05	ball metal	£4-50
7 x 4 in 3 & 8 OHMS	£2-30	TW209 LESSON DUAL IMP	£5-75
FANE8" 8. OHM DUAL CONE	£1-50	ball metal, uni-dir.	£45
CELESTION 8" 15.OHM	£1-60	GIUITAR MIKE	£40
GOODMANS 10 x 6 3.OHM	£5-75	LAPTEL TYPE, crystal	
BAKER GROUP 25 12" 25	£5-75	POSTAGE 17p each.	
WATT 8 or 15.OHM	£5-75		
21" 8 or 64 OHM p. & p. 10p.	£5-75	<b>Amplifier Modules</b>	
POSTAGE 25p per SPEAKER		One valve chassis Amplifier for	
		record player 2 Watt output, volume	
<b>Kit-Form Cabinets Teak</b>		control and tone control, on/off	
(17" x 10" x 6") with a 13" x 8"	£2-75	switch. £3-50 (P. & P. 25p).	
or 8" CUT OUT	£2-25	3 Watt mono Audio Module (Trans-	
(12" x 12" x 6") with a 8" x 5" or		istorised) £2-50 (P. & P. 10p).	
8" CUT OUT	£2-25	15 Watt Mono Audio Module (Trans-	
(PLEASE SPECIFY CUT OUT)		istorised) £3-95 (P. & P. 10p).	
Add 35p per Cabinet for p. & p.		3 Watt Stereo Module (1½" Watt/	
		Channel) £3-75 (P. & P. 10p).	
<b>Cartridges with standard fittings &amp;</b>		5 Watt Stereo Module (2½" Watt/	
styl		Channel) £5-50 (P. & P. 15p)	
ACOS GP91/25C or GP91/	£1-05	<b>Stereo Headphones</b>	
35C STEREO COMPAT-	£1-90	De-Luxe finish 8-16 Ohm Matching	
IBLE	£1-35	imp. mono/stereo switch complete	
ACOS GP94 STEREO CER.	£2-00	with lead and stereo jack plug only	
ACOS GP95 STEREO CRYST.	£2-00	£2-75 (P. & P. 25p).	
9THAC SONOTONE STEREO	£2-00	<b>NO STEREO PHONO SOCKET ??</b>	
CERAMIC (DIAMOND)	£2-00	Headphone Adaptor only £1-35	
ACOS GP67/2C MONO CRYST.	£2-00	(P. & P. 10p)	
ACOS GP101 COMP. CRYST.	£2-00		
19-TI SONOTONE STEREO	£2-00	<b>Tapes — "MYLAR"</b>	
CRYSTAL	£2-00	base finest	
POSTAGE 5p per CARTRIDGE		quality British made.	
		5" 600 ft 36p	5" 1800 ft 85p
<b>Microphone Bargains</b>		5" 900 ft 45p	7" 1200 ft 55p
MIC45 "ACOS" metal case,	£1-95	5" 1200 ft 60p	7" 1800 ft 80p
crystal hand	£1-95	5½" 900 ft 49p	7" 2400 ft 95p
CM 20 Crystal Hand	£1-95	5½" 1200 ft 55p	
DX143 Dynamic, cassette-	£1-90	POSTAGE 9p each.	
type atk			

**THIS MONTH'S SPECIAL OFFER**  
BIB Groov-Kleen Model 42, effective record cleaner. Retail price £1 95  
Our price £1 50 (P. & P. 15p)

SEND 25p FOR COMPLETE CATALOGUE  
Slight price alterations due to VAT will effect certain of our items after  
April 1st

## RIVERSDALE ELECTRONICS

Mail Order Department W4/73, P.O. Box 470, Manchester M60 4BU  
ALL OUR MERCHANDISE IS FULLY GUARANTEED

## INDEX TO ADVERTISERS

A.H. Supplies	1072
Adcola Products	1075
Amron U.K.	1059
Antex Ltd.	1091
Apex Aerials	1146
Arrow Electronics	1115
Astro Electronics	1140
Attwood, V.	1148
B.H. Components Factors	1149
Baines, R.	1146
Baker Loudspeakers Ltd	1140
Bedford Electronics	1150
Bell's Television	1146
Bentley Acoustic Corporation Ltd.	1074
Bernard, Gerald	1128
B.I.E.T.	1068, Cov iii
Bi-Pak Semiconductors	1069, 1070, 1071
Bi-Pre-Pak Ltd.	1135
Boffin Projects	1150
British National Radio & Electronic School	1065, 1142
Broadway Electronics	1064
Bull, J. (Electrical) Ltd.	1132
C.C.I. Ltd.	1128
Caranna, C.	1146
Codar	1060
Colomor (Electronics) Ltd	1096
Comet High Fidelity Discount Ware-	1076, 1077
houses	1061
Chromasonic Electronics	1061
Crowborough Electronics	1149
D.E.W. Ltd.	1149
Dabar Electronic Products	1128
Denco	1146
Dexter & Co.	1074
Douglas Electronic Industries Ltd.	1066
Duke & Co. (London) Ltd.	1096

Electro-Kit	1060
Electronic Design Associates	1116
Electrospares	1078
Electrovalve	1131
Elekon Enterprises	1068
Elvins Electronic Musical Instruments	1142
Felstead Electronics	1116
Galleon Trading	1148
Gladstone Radio	1096
Global Audio Discount Warehouses	1068
Golledge P. P.	1148
Greenweld Electronics	1148
HAC Short-wave Products	1066
Harverson Surplus Co. Ltd.	1143
Heath (Gloucester) Ltd.	1095
Henry's Radio Ltd.	1127, Cov iv
Home Radio (Components) Ltd.	1078
I.C.S.	1058, 1147
J.H. Associates	1150
Jef Electronics	1147
Jermyn Industries	1058
Johns Radio	1150
Johnson Radio	1148
K.V.A. Electronics	1120
Kensington Supplies	1146
Keytronics	1066
King, J. M.	1149
Lasky's Radio Ltd.	1072
Lewis Radio	1128
Linear Products Ltd.	1116
London Computer Operators Training Centre	1147
London Electronic College	1147
McGarva, David	1146
Marshall, A. & Son	1092
Merlin Supply Co.	1064
Morse	1146
Multicore Services Ltd.	1068
Omnia Products	1150

Padgetts Radio Store	1151
Partridge Electronics Ltd	1140
Phononics	1064
Radio Component Specialists	1119
Radio Book Services	1147
Radio Exchange Co. Ltd.	1123
Radio & T.V. Components (Acton) Ltd.	1062, 3
Radio Society of Great Britain	1066
Readers Radio	1142
Redhawk Sales	1148
Riversdale Electronics	1151
RQC Electronics Ltd.	1073
RSC (Hi-Fi Centres) Ltd.	Cov ii, 1057
R.S.T. Valve Mail Order Co.	1064
Saxon Entertainments	1080
Scientific & Technical	1140
Salop Electronics	1150
Selray Book Co. Ltd.	1147
Semicon Index Ltd.	1147
Sinclair Radionics Ltd.	1144, 1145
Shopertunities Ltd.	1079
Smith, G. W. & Co. Ltd.	1136, 7, 8, 9
Smith, H. L. & Co. Ltd.	1150
Sonic Sound Audio Ltd.	1058
Stephens Electronics	1120
Surplronics	1078
Swanley Electronics	1120
Teleradio Co. Ltd.	1148
Thacker, A. H. & Sons Ltd.	1142
Tidman Mail Order	1147
Trade Aids	1074
Trade Disposals	1146
Trampus Electronix	1148
Trannies	1141
Tuac Ltd.	1067
Velco Electronics	1149
Vero Electronics	1074
West London Direct Supplies	1149
Wilmslow Audio	1060, 1120, 1149
York Electronics	1072
Z & I Aero Services	1152

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 12p in £ for postage and handling  
MINIMUM CHARGE 15p. No C.O.D. orders accepted  
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

0A2	0.40	6AR6	0.85	6F5	0.75	7Y4	0.75
0A3	0.48	6AR11	1.25	6F6G	0.45	9BW6	0.70
0R2	0.40	6AS5	0.50	6F11	0.50	10C2	0.60
0B3	0.70	6AS7G	0.85	6F13	0.50	10D1	0.85
0C3	0.40	6AT6	0.38	6F16	0.70	10D2	0.55
0D3	0.40	6AUB	0.30	6F15	0.45	10P1	0.75
1B3GT	0.45	6AV6	0.40	6F18	0.50	10P9	0.65
1L4	0.25	6AW8A	0.65	6F23	0.80	10P18	0.80
1R4	0.50	6BA6	0.28	6F24	0.80	10L1	0.60
1R5	0.45	6BE6	0.32	6F25	1.00	10LD11	0.70
1R4	0.30	6BP6	0.55	6F26	0.35	10P13	0.75
1R5	0.30	6BH6	0.75	6F28	0.70	12AB5	0.70
1T4	0.30	6DJ6	0.55	6GK6	0.80	12AC8	0.60
1U4	0.40	6BK7A	0.75	6J4	0.60	12AE6	0.80
1U5	0.75	6BN5	0.43	6J5GT	0.40	12AL5	0.55
1V2	0.55	6HN6	0.60	6J6	0.30	12AQ5	0.50
1X2D	0.65	6HQ5	0.25	6J7	0.45	12AT6	0.40
2D21	0.40	6HR8	0.75	6K47	0.60	12AT7	0.40
3A4	0.45	6H87	1.35	6K4GT	0.75	12AU6	0.45
3A5	1.75	6HW6	0.80	6K7	0.43	12AU7	0.33
3BP1	3.50	6BW7	0.90	6K8G	0.45	12AV6	0.45
3B4	0.40	6BX6	0.25	6K25	0.75	12AV7	0.70
3V4	0.85	6BZ6	0.45	6L6GT	0.55	12AX7	0.33
3R4GY	0.75	6C4	0.35	6L7	0.45	12AY7	0.75
3U4G	0.40	6C5GT	0.55	6L18	0.45	12BA4	0.65
3V4G	0.60	6C6B	0.40	6LD20	0.50	12BA6	0.45
5Y3GT	0.45	6CDDGA	0.65	6N7GT	0.55	12BA7	0.50
5Z3	0.75	6C7	1.30	6P28	0.85	12BE6	0.50
5Z4G	0.45	6C7G	0.60	6Q7	0.50	12BH7	0.50
6J30L2	0.80	6CH6	0.60	6SA7	0.45	12BY7	0.65
6A4	0.40	6CL6	0.50	6G7	0.45	12C5	1.00
6AP4A	0.60	6CUB	0.80	6SK7	0.50	12K7GT0.50	
6AG5	0.25	6CW4	0.70	6BL7GT0.45	0.45	12Q7GT0.45	
6AG7	0.45	6CY6	0.50	6BN7GT0.45	0.45	12R7	0.50
6AH6	0.60	6C7Y	0.75	6RQ7	0.50	20R1	0.60
6AJ8	0.30	6D3	0.55	6SR7	0.50	20L1	1.10
6AK8	0.80	6E6	0.85	6T6	0.35	20P1	0.60
6AK6	0.50	6DK6	0.60	6U4GT	0.70	20P4	1.10
6AL3	0.40	6DQB7	0.75	6V5G	0.75	20P5	1.20
6AL5	0.22	6DS4	1.25	6V8A	0.48	25C5	0.80
6AM5	0.40	6EA8	0.65	6V6GT	0.45	25L6GT	0.50
6AM6	0.37	6EH7	0.30	6X4	0.40	25Z4G	0.35
6AQ5	0.42	6EJ5	0.35	6VGT	0.65	25Z5GT0.75	
6AQ6	0.70	6EW6	0.70	6X8	0.65	30A5	0.60
6AR5	0.55	6F1	0.75	6Y6G	0.80	30AE3	0.40

First Quality Fully Guaranteed



ELECTRONIC VALVES

30C1	0.30	50L6GT	0.80	DM160	0.68	ECC88	0.40
30C15	1.00	85A2	0.55	DY51	0.55	ECC89	0.50
30C17	1.10	90A1	2.40	DY86	0.35	ECC91	0.30
30C18	0.80	90AV	2.50	DY87	0.35	EL360	1.15
30F5	1.00	90C1	0.75	DY802	0.37	EL369	0.65
30FL1	0.80	90CV	2.40	E90F	1.10	ELC80	0.35
30FL12	1.10	807	0.50	E88CC	0.70	ELL80	0.75
30FL14	0.80	813	4.00	E180F	1.00	ELM34	1.00
30FL1	0.40	866A	0.35	E810F	2.90	EM71	0.80
30L15	0.85	5642	0.70	EABC800.38		EM80	0.45
30L17	0.95	6080	1.75	EAF42	0.60	EM81	0.60
30P12	1.00	6146	1.60	ECB33	0.60	EM83	0.50
30P19	0.95	6146B	2.50	ECB41	0.65	ECL80	0.50
30P11	0.95	6360	1.25	ECB81	0.33	EM85	1.00
30P13	1.10	6939	2.25	EBF80	0.40	EM87	0.70
30PL14	1.25	7199	0.65	EBF83	0.40	EN91	0.40
35A3	0.60	7886	1.50	EBF89	0.32	ECL84	0.55
35A5	0.75	7895	1.50	ELB31	1.50	EY80	0.75
35B5	0.65	A2293	2.20	EC53	0.50	EY81	0.40
35C5	0.80	AZ1	0.60	EC86	0.60	EY83	0.55
35D5	0.75	AZ31	0.55	EC88	0.60	EY86	0.40
35L6GT	0.75	CB1	0.80	EC90	0.35	EY87	0.43
35W4	0.40	CB131	1.00	EC92	0.45	EY88	0.43
35Z3	0.75	CY1	0.50	EC93	0.60	EZ40	0.70
35Z4G	0.40	CY21	0.50	EC95	1.00	EZ41	0.75
35Z5GT	0.70	DAP96	0.50	ECC40	0.70	EZ80	0.28
60A5	0.50	DF96	0.50	ECC81	0.40	EZ81	0.29
60B5	0.70	DK92	0.70	ECC82	0.33	GTIC	3.00
60C5	0.60	DK96	0.60	ECC83	0.33	GT1601	0.70
60CD6G	1.20	DL96	0.55	ECC84	0.30	GZ30	0.45
60EH5	0.65	DM70	0.60	ECC85	0.35	GZ31	0.40

6F95	0.40	GZ32	0.50	FF818	1.00	U301	0.55
EF97	0.65	GZ33	0.75	FF1200	0.85	U403	0.70
EF98	0.75	GZ34	0.60	PL33	0.40	U404	0.70
EF183	0.30	HABC800.55		PL36	0.55	U801	0.80
EF184	0.35	HK90	0.50	PL81	0.50	UABC80	
EF804	1.25	KT66	2.35	PL92	0.45		
EK90	0.32	KT88	2.25	PL83	0.45	UAF41	0.70
EL34	0.50	N78	1.60	PL84	0.40	UAF42	0.60
EL36	0.50	PABC800.40		PL802	0.65	UB41	0.85
EL37	1.70	PC86	0.60	PL804	0.75	UBC41	0.55
EL41	0.75	PC88	0.60	PL808	0.90	UBC81	0.45
EL81	0.55	PC92	0.95	PL809	1.10	UBF80	0.40
EL83	0.50	PC97	0.50	PL801	1.00	UBF89	0.40
EL84	0.25	PC900	0.48	PL802	0.85	UBL1	0.70
EL85	0.43	PC94	0.40	PM84	0.80	UBL21	0.70
EL86	0.40	PCX85	0.40	PY31	0.35	UC92	0.45
ECC89	0.50	PCX85	0.40	PCX85	0.40	UC92	0.45
ECC91	0.30	PCX85	0.40	PCX85	0.40	UC92	0.45
EL360	1.15	PCX85	0.40	PCX85	0.40	UC92	0.45
EL369	0.65	PCX85	0.40	PCX85	0.40	UC92	0.45
ELC80	0.35	PCX85	0.40	PCX85	0.40	UC92	0.45
ELL80	0.75	PCX85	0.40	PCX85	0.40	UC92	0.45
ELM34	1.00	PCX85	0.40	PCX85	0.40	UC92	0.45
EM71	0.80	PCX85	0.40	PCX85	0.40	UC92	0.45
EM80	0.45	PCX85	0.40	PCX85	0.40	UC92	0.45
EM81	0.60	PCX85	0.40	PCX85	0.40	UC92	0.45
EM83	0.50	PCX85	0.40	PCX85	0.40	UC92	0.45
EM84	0.35	PCX85	0.40	PCX85	0.40	UC92	0.45
EM85	1.00	PCX85	0.40	PCX85	0.40	UC92	0.45
EM87	0.70	PCX85	0.40	PCX85	0.40	UC92	0.45
EN91	0.40	PCX85	0.40	PCX85	0.40	UC92	0.45
ECL84	0.55	PCX85	0.40	PCX85	0.40	UC92	0.45
EY80	0.75	PCX85	0.40	PCX85	0.40	UC92	0.45
EY81	0.40	PCX85	0.40	PCX85	0.40	UC92	0.45
EY83	0.55	PCX85	0.40	PCX85	0.40	UC92	0.45
EY86	0.40	PCX85	0.40	PCX85	0.40	UC92	0.45
EY87	0.43	PCX85	0.40	PCX85	0.40	UC92	0.45
EY88	0.43	PCX85	0.40	PCX85	0.40	UC92	0.45
EZ40	0.70	PCX85	0.40	PCX85	0.40	UC92	0.45
EZ41	0.75	PCX85	0.40	PCX85	0.40	UC92	0.45
EZ80	0.28	PCX85	0.40	PCX85	0.40	UC92	0.45
EZ81	0.29	PCX85	0.40	PCX85	0.40	UC92	0.45
GTIC	3.00	PCX85	0.40	PCX85	0.40	UC92	0.45
GT1601	0.70	PCX85	0.40	PCX85	0.40	UC92	0.45
GZ30	0.45	PCX85	0.40	PCX85	0.40	UC92	0.45
GZ31	0.40	PCX85	0.40	PCX85	0.40	UC92	0.45

## TRANSISTORS

2N696	0.15	AC128	0.15	BD121	0.65
2N697	0.16	AC132	0.35	BD123	0.60
2N698	0.80	AC153	0.20	BD131	0.75
2N705	0.70	AC184	0.15	BD132	0.80
2N708	0.10	AC157	0.17	BF115	0.20
2N708	0.15	AC169	0.10	BF167	0.18
2N763	0.25	AC176	0.17	BF175	0.20
2N929	0.20	AC187	0.25	BF179	0.30
2N930	0.20	AC188	0.25	BF180	0.30
2N987	0.30	ACY17	0.25	BF181	0.30
2N1131	0.25	ACY18	0.20	BF184	0.20
2N1132	0.25	ACY19	0.25	BF185	0.20
2N1184	1.25	ACY20	0.20	BF194	0.14
2N1302	0.17	ACY21	0.20	BF195	0.14
2N1303	0.17	ACY22	0.10	BF196	0.12
2N1304	0.20	AD140	0.60	BF197	0.12
2N1305	0.20	AD140	0.45	BF200	0.35
2N1306	0.25	AD161	0.35	BFW88	0.25
2N1307	0.25	AD162	0.35	BFW89	0.20
2N1308	0.25	ADZ11	1.25	BFW91	0.20
2N1309	0.25	ADZ12	1.25	BFX88	0.20
2N1613	0.17	AF114	0.17	BFY17	0.40
2N1711	0.20	AF115	0.17	BFY19	0.25
2N1766	0.75	AF116	0.17	BFY50	0.20
2N2147	0.75	AF117	0.17	BFY52	0.20
2N2160	0.60	AF118	0.30	BFY26	0.17
2N2217	0.25	AF125	0.20	BSY28	0.15
2N2218	0.20	AF127	0.20	BSY27	0.15
2N2219	0.20	AF180	0.35	BSY28	0.15
2N2369A	0.15	AF181	0.35	BSY65	0.20
2N2477	0.65	AF186	0.40	BSY95A	0.12
2N2646	0.40	AF239	0.35	OC16	0.50
2N2905	0.25	AFZ11	0.45	OC22	0.60
2N2923	0.12	AFZ12	1.00	OC23	0.60
2N2924	0.13	ASV26	0.25	OC24	0.60
2N2926	0.10	ASV27	0.30	OC25	0.35
2N3053	0.20	ASV28	0.25	OC26	0.25
2N3054	0.50	ASV29	0.30	OC28	0.50
2N3055	0.60	ASV54	0.25	OC29	0.60
2N3133	0.25	ASZ15	0.70	OC36	0.45
2N3134	0.25	ASZ16	0.70	OC37	0.45
2N3391	0.17	ASZ17	0.75	OC42	0.20
2N3392	0.17	ASZ18	0.75	OC44	0.1

# FREE!

## Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW03, Aldermaston Court, Reading RG7 4PF.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2.65.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.



CUT OUT THIS COUPON  
Tick or state subject of interest.  
Post to address below.

<b>MECHANICAL</b>	<b>Man. Prod.—cont.</b>	<b>Constructional-cont.</b>
A.M.S.E. (Mech.)	<input type="checkbox"/> Quality Control	<input type="checkbox"/> Building
Boiler Inspect.	<input type="checkbox"/> Salesmanship	<input type="checkbox"/> Building Drawing
& Operation	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> Build. Foreman
C & G Eng. Crafts	<input type="checkbox"/> Work Study	<input type="checkbox"/> Carpentry & Join.
C & G Fabricat.	<input type="checkbox"/> Works	<input type="checkbox"/> Civil & Municipal
Diesel Eng.	<input type="checkbox"/> Management	<input type="checkbox"/> Engineering
Eng. Inspection	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> Constructional
Eng. Metallurgy	A.M.I.E.D.	<input type="checkbox"/> Engineering
Inst. Eng. & Tech.	Design of Elec.	<input type="checkbox"/> Construction
Inst. Motor Ind.	Machines	<input type="checkbox"/> Surveyors
Mainten. Eng.	Die & Press Tool	<input type="checkbox"/> Institute
Mechanical Eng.	Design	<input type="checkbox"/> Clerk of Works
Sheet Metal Work	Electrical	<input type="checkbox"/> Council Eng.
Welding	Draughtsmanship	<input type="checkbox"/> Geology
<b>ELECTRICAL &amp; ELECTRONIC</b>	Gen. Draughtsmanship	<input type="checkbox"/> Health Eng.
A.M.S.E. (Elec.)	Jig & Tool Des.	<input type="checkbox"/> Heat & Vent.
C & G Elec. Eng.	Tech. Drawing	<input type="checkbox"/> Hydraulics
C & G Elec. Inst.	<b>RADIO &amp; TELE-COMMUNICATIONS</b>	<input type="checkbox"/> Inst. of Builders
Computer Elect.	Colour TV	<input type="checkbox"/> Highway Sup.
Elec. Maths	C & G Radio/TV	<input type="checkbox"/> Painting & Dec.
Elec. Science	Electronics	<input type="checkbox"/> Public Hygiene
Electronic Eng.	C & G Telecomm.	<input type="checkbox"/> Road Engineer.
Electrical Eng.	Tech.	<input type="checkbox"/> Structural Eng.
Install. & Wiring	Prac. Rad. Elec. (with kit)	<input type="checkbox"/> Surveying
Meters	Radio Amateurs Exam.	<b>GENERAL</b>
& Measuring Instruments	Radio Servicing & Repairs	<input type="checkbox"/> Agricultural Eng.
<b>MANAGEMENT &amp; PRODUCTION</b>	Radio & TV Eng. Trans. Course	<input type="checkbox"/> Council of Eng. Inst.
Computer Prog.	TV Main. & Serv.	<input type="checkbox"/> Farm Science
Electronic Data Processing	<b>AUTO &amp; AERO</b>	<input type="checkbox"/> General Educat.
Estimating	Aero Eng.	<input type="checkbox"/> Gen. Plastics
Foremanship	A.M.I.M.I.	<input type="checkbox"/> Pract. Maths
Inst. Cost & Man. Accounts	A.E.C. Cert.	<input type="checkbox"/> Pract. Slide Rule
Inst. Marketing	Auto Engineer.	<input type="checkbox"/> Pure & Applied Maths
Management	Auto Repair	<input type="checkbox"/> Refrigeration
Metrication	C & G Auto. Eng. Garage	<input type="checkbox"/> Rubber Tech.
Motor Trade Man. Network Plan.	Management	<input type="checkbox"/> Sales Engineers
Numerical Cont.	MAA/IMI Dipl.	<input type="checkbox"/> Tech. Report
Operational	Motor Vehicle Mechanics	<input type="checkbox"/> Writing
Research	<b>CONSTRUCTIONAL</b>	<input type="checkbox"/> Timber Trade
Personnel Man.	A.M.S.E. (Civil)	<input type="checkbox"/> University Ent.
Planning Eng.	Architecture	
Production Eng.		

Coaching for many major exams. including ONC, C & G, etc.

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW03 QN BPW03  
Aldermaston Court, Reading RG7 4PF

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by C.A.C.C.  
**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# Henry's

## YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

### BUILD THE TEXAN

★ FREE TEAK CABINET with complete kits!

**FEATURES.** New slim design with 6 - IC's, 1C Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

**FACILITIES.** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request). Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE **£28.50** P & P 45p

COMPLETE WITH FREE TEAK CABINET  
Designer approved kits distributed by Henry's!

### 20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



★ SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14 1/2" x 6" x 2" high

**ELECTRONIC KITS**  
Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

**IC RECEIVER**  
ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973, Practical Electronics, February 1973. Price £1.20.

**BATTERY TAPE DECK**  
Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9.50, post 30p.

**LEARN A LANGUAGE**  
Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £1.49 per cassette. £5.50 per set of four.

**DISCO SPOTBANK**  
£12.75. p. & p. 35p.

### LOW COST HI-FI SPEAKERS




E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.  
**TYPE 150** 6 watt, 3, 8 or 15 ohms £2.20, Post 22p.  
**TYPE 150 TC** Twin cone version £2.75, Post 22p.  
**TYPE 450** 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85, Post 25p.  
**TYPE 350** 20 watt with tweeter and crossover. 8 and 15 ohms. £7.70, Post 28p.



**POLISHED CABINETS.** 150, 150TC, 450 £4.60, Post 30p. ASSEMBLED IN POLISHED CABINETS (8 ohms)  
**SERIES 6** (Assembled 150 T/C) per pair £16.50, Post 70p  
**SERIES 8** (Assembled 450) per pair £18.95, Post 70p

### ML-3 MW/LW TUNER to BUILD

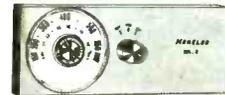

Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". **TOTAL COST TO BUILD** £4.85, Post 15p. All parts sold separately. Leaflet No. 6

### "BANDSPREAD" PORTABLE TO BUILD




Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. **TOTAL COST TO BUILD** £7.98, p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

### CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid (40p FOR CALLERS)  
**PLUS! FIVE 10p VOUCHERS**

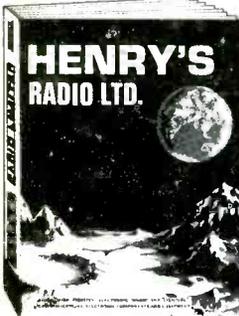Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1. for catalogue by post only. All other mail and callers to "303" see above.



### TEST EQUIPMENT

Just a selection!

- SE250B Pocket Pencil Signal Injector £1.90
  - SE500 Pocket Pencil Signal Tracer £1.50
  - THL33D Robust 2k Volt £4.55 with case £4.95
  - TE15 Grid Dip Meter 40 KHz-280 mHz £13.45
  - 500 30 K/V Multimeter £9.25
  - With leather case £10.50
  - 200H 20K/V Multimeter £4.20. With case £4.95
  - AF105 50K/V Multimeter £8.50. With case £9.50
  - U4341 AC/DC Multimeter with transistor tester with steel case £10.50
  - TE20D RF Generator 120KHz-500MHz £15.95. Carr. 35p
  - TE22D Audio Generator 20Hz-200KHz £17.50. Carr. 35p
  - CI-5 3" Pulse Scope 10Hz-10mHz £39.00. Carr. 50p
  - TE65 Valve Voltmeter 28 ranges £17.50. Carr. 40p
- ALL NOMBREX MODELS IN STOCK



### PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

- DJ30L 3 Channel sound to light unit, 3kW. £29.50
  - DJ40L 3 channel Mic (built-in) to light, 3kW. £38.75
  - DJ70S 70 watt Disco amp/mixer. £49.75
  - DISCOAMP 100 watt amp/mixer. £68.85
  - DJ105S 30 watt Disco mic/mixer. £32.25
  - Anti-Feedback Quality Mic. £11.50
  - DJ500 50 watt PA Amplifier £43.95
  - DJ700 70 watt £52.75
  - GROUP 300 150 watt rms "Group" Valve Amplifier £86.00
- FIBRE OPTICS LIGHTING, — MICS, EFFECTS, PROJECTORS, SPOTS, DIMMERS — STANDS, MIXERS, SPEAKERS. Everything for PA — Disco — Lighting. **FREE Stock List Ref. No. 18**
- PORTABLE DISCOS — DETAILS ON REQUEST
  - CREDIT TERMS FOR CALLERS



### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO.  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. **TOTAL £6.97**, p.p. 20p. Decoder Kit £5.97. Tuning meter unit £1.75. Mains unit (optional) Model P5900 £2.47, Post 20p. Mains unit for Tuner and Decoder P56/12 £3.25, Post 20p



### SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

- Z30 £3.57; Z50 £4.37
- STEREO 60 PZ5 £3.97
- £7.97; PZ8 £4.77
- PZ6 £6.37;



Transformer for PZ8 £2.95  
Active Filter Unit £4.45  
Stereo Filter Tuner £16.95  
IC12 £1.80; Q16's £15 pr.  
Post etc. 20p per item

### PACKAGE DEALS

- Post 25p
- 2xZ30, Stereo 60, PZ5 £15.95
- 2xZ30, Stereo 60, PZ6 £18.00
- 2xZ50, Stereo 60, PZ8 £20.25
- Transformer for PZ8 £2.95
- PROJECT 60S KIT £19.95

### HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE. 24 page detailed brochure (Ref. No. 17). You can see the savings!

### EMI HIGH QUALITY CASSETTES

The best UK low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	RRP each	3 for	6 for	10 for
C60	71p	1.02	2.00	3.10
C90	98p	1.47	2.85	4.65
C120	1.48	1.80	3.50	5.60

Full guarantee. Post paid. See earlier page of this magazine for transistors and semi-conductor devices. Huge range of transistors and semi-conductors in stock. Free brochure (Ref. 36) on request.

### ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits. £5.90 per pair. Post 10p

### MARROT TAPE HEADS

- 4 TRACK MONO
- 2 TRACK STEREO
- '17' High Impedance £2.00
- '18' Med. Impedance £2.00
- '36' Med.-Low Imp. £3.50
- Erase Heads for above 75p
- '63' 2 track mono—Hi Imp. £1.75
- '43' Erase Head for above 75p

### 7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)  
XN3, XN13, GN6 0-9 side view with data, 85p.  
GNP.7, GNP.8 0-9 side view with decimal points and data, 95p.  
301 SF 7 seg £2 each. £7 per 4 with data.  
12 and 24 hour clock circuits Ref. No. 31 15p.

### Miniature Amplifier

5 transistor, 300mW o/p. Fitted volume and sensitivity control, 9 volt operated. £1.75 each P/P 15p.

### Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K. 1 meg, Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged. 60p each.

### VAT

Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay.

**Henry's RADIO LIMITED**  
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
354-356 High Fidelity and Tape Equipment 01-402 5854/4736  
309 PA-Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW

Open - 9 am - 6 pm  
6 days a week  
(309 closed Thursday)  
All stores open all day Saturday